

EVERYDAY

858

OCTOBER 1992

ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

FULLY S.O.R. £1.80

**EXTENDED RANGE
CAPACITANCE METER**

VERSATILE INTERCOM

**FREE
INSIDE**

**MARCO
TRADING**

32-PAGE CATALOGUE

LIGHTS ON WARNING

WHISTLE SWITCH

**Plus ALTERNATIVE ENERGY-3;
CIRCUIT SURGERY; ACTUALLY DOING IT;
AMATEUR RADIO AND MORE**



EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY



ABC
CONSUMER PRESS

VOL. 21 No. 10 OCTOBER 1992

The No. 1 Independent Magazine for Electronics,
Technology and Computer Projects

ISSN 0262 3617

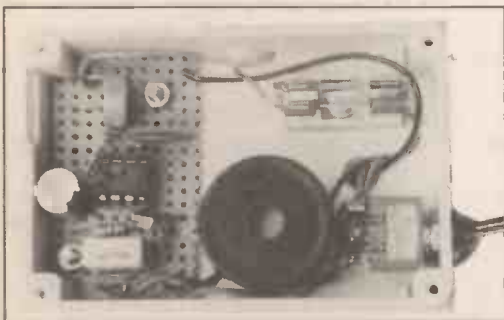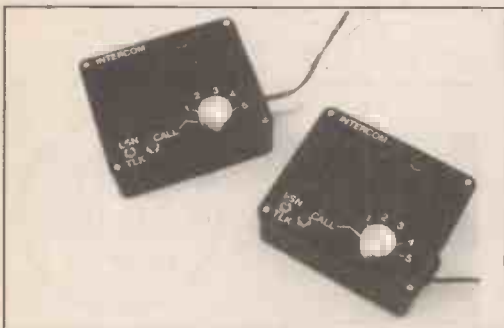PROJECTS... THEORY... NEWS...
COMMENT... POPULAR FEATURES...



© Wimborne Publishing Ltd 1992. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our November '92 Issue will be published on Friday, 2 October 1992. See page 611 for details.

Projects

- EXTENDED RANGE CAPACITANCE METER** 620
by Steve Knight
Test those unmarked or dubious capacitors for value and leakage
- TRAFFIC LIGHT SYSTEM** by J. Hewes 636
Appropriate for everyone from the model maker to highway code trainer
- WHISTLE SWITCH** by Steven Holland 640
One whistle and it's on, another and it's off, a very adaptable design
- VERSATILE INTERCOM** by I. A. Duncombe 646
Any number of stations plus a conferencing facility
- LIGHTS ON WARNING** by T. R. de Vaux-Balbirnie 662
For the forgetful car owner, avoid that embarrassing flat battery

Series

- CIRCUIT SURGERY** by Mike Tooley 626
Our clinic for constructors – your problems solved
- ALTERNATIVE ENERGY – 3** 628
by T. R. de Vaux Balbirnie
If you ever go across the sea to Denmark – more on wind power
- ACTUALLY DOING IT** by Robert Penfold 634
Front panels and project building
- INFORMATION TECHNOLOGY AND THE NATIONAL CURRICULUM** by T. R. de Vaux-Balbirnie 656
Part Twelve: Ohms law and power calculations
- INTERFACE** by Robert Penfold 666
Bar code software
- AMATEUR RADIO** by Tony Smith G4FAI 676
Amateurs To The Rescue!; New Radio Spectrum Review; New Rechargeable Battery

Features


- EDITORIAL** 619
- EVERYDAY NEWS** 643
News and new products from the world of electronics
- FOR YOUR ENTERTAINMENT** by Barry Fox 645
Doomed CD-ROM; Not A Lot Of People Know This!
- SHOPTALK** with David Barrington 660
Component buying for EE projects
- DOWN TO EARTH** by George Hylton 668
Simulated Reactances
- EVERYDAY READOUT** 669
Your letters about our subject
- ELECTRONICS VIDEOS** 670
A new addition to our range of educational videos
- DIRECT BOOK SERVICE** 671
Selected technical books, EE books and all Babani books by mail order
- PRINTED CIRCUIT BOARD SERVICE** 674
A special PCB SALE (while stocks last) – boards for EE projects
- FREE – MARCO 32-Page Autumn Catalogue**
between 644/645

ADVERTISER'S INDEX 680


Readers Services • Editorial and Advertisement Departments 619

EASY-PC PCB and Circuit Diagram CAD

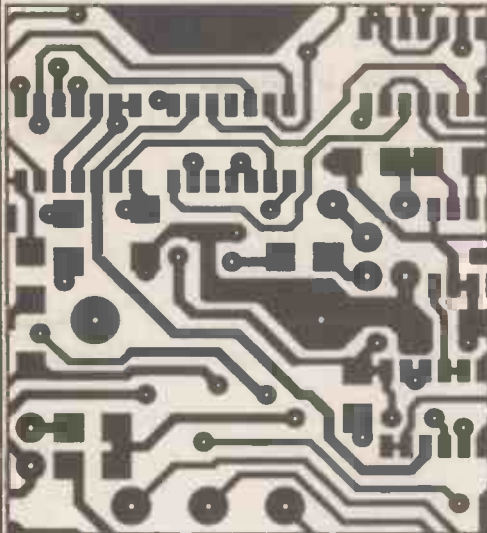Forget using tapes and lightbox! Create your Circuit Boards using CAD - like the professionals.



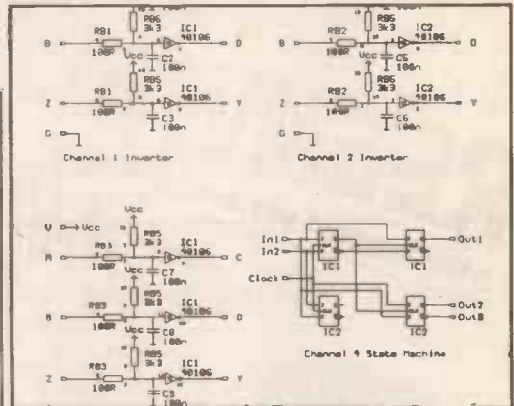- Runs on PC/XT/AT etc. with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design Schematics Single and Double sided and Multilayer boards including Surface Mount.
- Standard output includes Dot Matrix / Laser / Inkjet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Extremely powerful.
- Very easy to use.



EASY-PC

Technical support is free, for life!


**Only
£98.00!**

Plus P&P+VAT

Over 13,000 Installations in 70 Countries Worldwide!


Options:-500 piece Surface Mount Symbol Library £48, 1000 piece Symbol Library £38, Gerber Import facility £98.

**DIGITAL
SIMULATION £195**

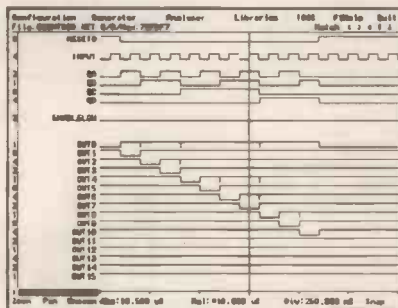


- At last! A full featured Digital Circuit Simulator for less than £1000!
- PULSAR allows you to test your designs without the need for expensive test equipment.
- Catch glitches down to a pico second per week!
- Includes 4000 Series CMOS and 74LS Libraries. 74HC/HCT libraries only £48.00 each.
- Runs on PC/XT/AT/286/386/486 with EGA or VGA.

**ANALOGUE
SIMULATION £195**

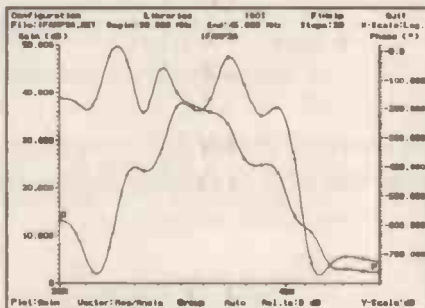

- NEW powerful ANALYSER III has full graphical output.
- Handles R's, L's, C's, Bipolar Transistors, FET's, OP-amp's, Tapped and Untapped Transformers, and Microstrip and Co-axial Transmission Lines.
- Plots Input / Output Impedance, Gain, Phase & Group Delay.
- Covers 0.001 Hz to > 10GHz
- For PC/XT/AT/286/386/486 with EGA or VGA.
- Very fast computation.

**SMITH CHART CAD
£195**

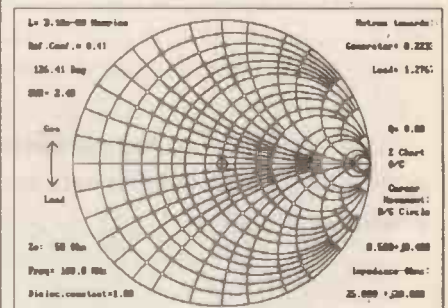

- Z-MATCH II simplifies RF matching and includes many more features than the standard Smith Chart.
- Handles transmission line transformers, stubs, discrete components, S Parameters etc.
- Supplied with many worked examples.
- Superbly easy to learn and use.
- Runs on IBM PC/XT/AT/386/486, CGA, EGA, VGA.
- Ideal for Education and Industry.

For full information, Write, Phone or Fax:-

Number One Systems Ltd. I

REF: EVD, HARDING WAY, ST.IVES, HUNTINGDON, CAMBS, ENGLAND, PE17 4WR.

Telephone: 0480 61778 (7 lines) Fax: 0480 494042

International: +44-480-61778, Fax: +44-480-494042 ACCESS, AMEX, MASTERCARD, VISA Welcome.

- TECHNICAL SUPPORT FREE FOR LIFE!
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

FREE 196 Page GREENWELD CATALOGUE

- the biggest yet and packed with components, kits, tools etc.

21st Anniversary Issue

In addition to the merged titles next month is significant because it represents 21 years of EE. We have some special features looking at future technology - the next 21 years!



TEACH-IN '93

It is a tradition; roughly every two years since issue No. 1 we publish a new and completely different Teach-In series. The last one was Design Your Own Circuits, this one is aimed at GCSE and 'A' level students.

If you are taking electronics or technology at school or college, this series is for you.

If you just want to learn the basics of electronics then this series is for you.

If you are teaching electronics or technology you must make sure you see it.

The series will be invaluable if you are considering a career in electronics or even if you are already training in one. Or if you just want to brush up on your knowledge.

Don't miss the start of Teach-In '93 next month.

To go with the series there is a very comprehensive and exciting Mini Lab. This enables the construction and testing of both demonstration and development circuits. This learning aid brings electronics to life in an enjoyable and interesting way: you will both see and hear the electron in action!

Later there is an additional Micro Lab microprocessor add-on system that will appeal to higher level students and those that wish to develop microprocessor projects.

In addition to all the above there will be the usual varied range of news, features and regulars including the following projects:

Altimeter, Personal Stereo Amp and a Reaction Timer.

DON'T MISS YOUR COPY!

Fill in the Shop Save card in this issue or take out a subscription now (see page 667). The demand for copies will be very high!

Please notice our new logo. From next month we will be joined by the present readers of Practical Electronics. We have purchased that title and will merge it with EE.

EVERYDAY
WITH **PRACTICAL**
ELECTRONICS

NOVEMBER ISSUE PUBLISHED FRIDAY, 2nd OCTOBER 1992

NEXT MONTH

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all of our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3-12V operation. 500m range.....£16.45

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter
Just 17mm x 17mm including mic. 3-12V operation. 1000m range.....£13.45

STX High-performance Room Transmitter

Hi performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range.....£15.45

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9-12V operation. 3000m range.....£16.45

VXT Voice Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range...£19.45

HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply for long-term monitoring. Size 30mm x 35mm. 500m range.....£19.45

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range.....£22.95

SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires-SCDM connected to receiver. Size 32mm x 37mm. 1000m range.....£23.95

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9-12V operation.....£22.95

ATR2 Micro Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line.....£13.45

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range.....£15.95

TLX700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range.....£13.45

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range.....£16.45

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation.....£22.95

CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation.....£30.95

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation.....£50.95

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180 MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range.....£40.95

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range.....£40.95

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m.....£35.95

QRX180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as a pre-built and aligned module ready to connect on board so no difficulty setting up. Outpt to headphones. 60mm x 75mm. 9V operation.....£60.95

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcomed on 0827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

★★★ Specials ★★★

DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way dit switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits).....£50.95
Individual Transmitter DLTX.....£19.95
Individual Receiver DLRX.....£37.95

MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle. Size 27mm x 60mm. 9V operation. 250m range.....£20.95

DEPT. EE

THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY, NEAR AATHERSTONE,
WARWICKSHIRE CV9 2LE

VISITORS STRICTLY BY APPOINTMENT ONLY




0827 714476

**SUMA
DESIGNS**

LAST CHANCE TO SEND FOR OUR 32 PAGE SUMMER SALE LIST!! SALE ENDS SEPT 30th


AMSTRAD PC1640 COMPUTER OFFER

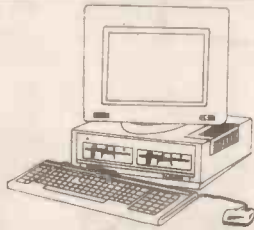

Brand new base unit, keyboard, mouse and manual. Completely standard machine fitted with 2 x 5.25" disk drives, only being sold so cheaply as we have no monitor to go with them!

Amazing Price! - £99.95

3.5" DISK DRIVE

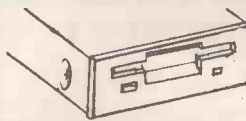


Model FD9. Brand new and boxed, this cased 3.5" 720k unit comes complete with cables and instructions. Plugs into printer port.

Superdeal Price £24.95


C64 GAMES CONSOLE

Value Pack **£49.95**

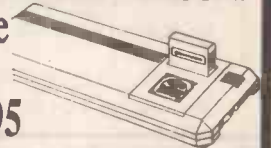

Z9109 New and boxed games machine based on the popular C64 computer - you get the console, power supply, TV lead, Cheetah joystick and 4 game cartridge - Flimbo's quest, Fiendish Freddy, Klax and International Soccer.

VHF/UHF TV RECEIVER/CONVERTER

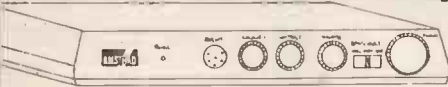


Z8991 Amstrad MP3 computer modulator/converter.

A complete, fully tunable VHF/UHF TV receiver with RGB and composite video out, and sound on the internal speaker. For use with the Amstrad CTM644-2 monitor specifically, or can be used with any colour/mono home computer monitors that have a 15.625kHz line frequency. Grey case 330x250x50mm. Controls: contrast, colour, tuning, volume and band select (VHF-L, VHF-H, UHF) RGB output on 8 pin DIN skt, and composite video. Intended for European market - needs 2 ceramic filters changing. Parts and instructions supplied. Needs stabilized 12V DC, either from monitor or separate power supply (our AL12, DB14 is ideal).

ONLY £14.95

AMSTRAD CLOCK TIMER

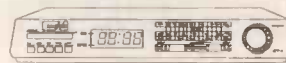

Z8999 Model CT1 - in plastic case that sits under monitor. MW/LW/FM receiver with 3" speaker, + digital clock with alarm and snooze facilities.


Great Value £7.95

ATARI 2600 GAMES CONSOLE

Complete and boxed with joystick, power supply, TV lead and games cartridge (centipede). Not new, but fully checked and working

Special Price

£29.95

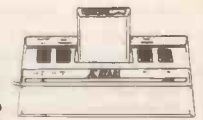

AMSTRAD GX4000 HOME ENTERTAINMENT SYSTEM




ONLY £29.95

- *Games Console
- *2 Control Paddles
- *TV lead
- *Burnin' Rubber Cartridge
- *Power Supply
- *Instruction Books

Inputs for 2 paddles, analogue joysticks, light gun/pen etc. Outputs: UHF, RGB on 8 pin DIN skt, SCART skt, stereo sound 3.5mm skt. Uses 168 pin dedicated chip, Z80A CPU, AY-3-8912 sound chip, UMI234 UHF modulator

commodore

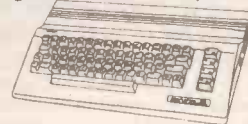Scoop purchase of a major store's returns. Fully checked in good working order in original boxes. Save up to 50%!!




Z9105 Basic C64 computer with power supply and TV lead
Z9106 NightMoves/Mindbenders Pack. This contains the C64 Computer, C2N datacorder, 2 joysticks and 9 cassettes inc Trivial Pursuit, Confuzion etc

£60
£75

THE 'Greenweld Guardian' IS OUR MONTHLY NEWSLETTER FREE TO ALL BARGAIN LIST SUBSCRIBERS - ONLY £6 A YEAR FOR THE NEXT 12 ISSUES OF ALL OUR LISTS!!

CASIO

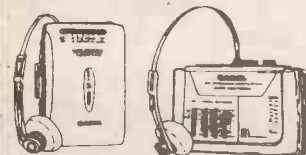Casio have just introduced a range of personal stereos and portable audio equipment at very competitive prices:



- W880 Bass boost, auto stop, belt clip **£8.99**
- AS51R As above but with AM/FM radio **£15.99**
- AS500R As AS51R, but with auto reverse **£23.50**
- W120 As AS500R but with graphic equalizer **£27.99**




- CP80 Bass boost, AM/FM/LW radio, single cassette, 6W PMPO **£32.95**
- CP200 Bass boost, AM/FM/LW radio, twin cassette, hi-speed dubbing, graphic equalizer, 8WPMPO **£42.95**
- CD510 CD player, twin cassette, AM/FM/LW radio + lots of other features, 45W PMPO **£159.95**

FOREGROUND MUSIC SPEAKERS

High quality for pubs, clubs etc. Bass unit, mid and 2 tweeters. Moulded cabinet with adjustable bracket. Max power 80W. Size 275x170x125mm. 4R imp.

Less than half price! £39.95 per pr!

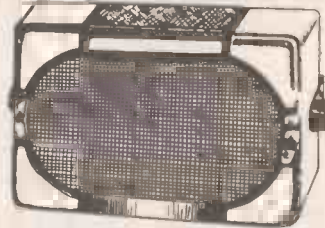

INSULATION TEST UNIT

Y136C 500V tester that can be used with most digital meters. 2 ranges covering 100k-1999M. Supplied with leads, batts, instructions and carry case. Original trade price **£34**

£12.95

CAMERA CLEARANCE

110 & 35mm - all are returns, some have small parts missing, but great value for lenses, electronics etc (most have built in flash units)

5 for £10

STEREO AUTO-REVERSE CASSETTE MECHS

Z5405 High quality heavy duty all metal construction stereo cassette player mechanism, probably intended for continuous background music. This is a lovely bit of kit - starts playing as soon as a cassette is inserted. Has fast forward, rewind and eject keys. It's bi-directional, and the sensing circuit automatically reverses the tape at the end. Has a Canon motor and works off 12V DC. Great value at **£4.95**.


NEW POWER SUPPLIES

Z5406D High efficiency step down power regulator module by SGS. This is a GSR400 type, as listed by Farnell at **£41.11** each. Output is 7V @ 4A from a DC input of 10-46V. Possible uses include battery charger, or put two together and use 24V lorry battery to power car equipment. Our special price - just **£5.75** each.

Z5409 Eurocard size - 160x100mm by Protek. 115/230V input, Outputs: +5V @ 3A; +12V @ 2A; -12V @ 0.25A Price **£8.95**

UHF TUNER

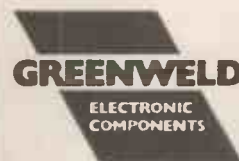Z2648 UHF TV tuner - at least, the front end. Fagor SUF743 has a co-ax socket inset into the screened case 65x50x20mm. Inside the PCB has some surface mount bits + BF966S, BF970 and BF199 transistors and a few coils. Giveaway Price 2 for **£10.00**



All 1 off and pack prices include VAT, qty prices do not. P&P **£2.50** per order (£9 next day) Min Credit Card **£12**. Official orders from Education welcome; min invoice charge **£15**. Payment is accepted by cheque, PO, cash (inc foreign currency banknotes), book tokens, Access, Visa, Connect. Our stores have enormous stocks - we are open from 9-5.30 Mon-Sat. Come and see us!



Tel: (0703) 236363
Fax: (0703) 236307

27D PARK ROAD, SOUTHAMPTON, SO1 3TB

BARGAINS - 14 New Ones This Month

PROJECT BOX a first-class, Japanese two-part moulding size 95mm x 66mm x 23mm. Held together by 2 screws, this will hold a PP3 battery and a PCB and is ideal for many projects. To name just a few, the washer bottle monitor, the Quicktest and the model railway auto signal, described in last month's issue of E.E. This is nicely finished and very substantial. You get 2 for £1, Order Ref. 876.

HOLD IT MAGNETIC BASE embedded in a circular metal shallow disc, diameter approximately 65mm (2 1/2"), is the most powerful magnet. We have yet to find anyone who can remove this with his fingers. Ideal for adding extra shelves inside a metal case or to glass without drilling. Its uses, in fact, are innumerable. Price £2 each, Order Ref. 2P296.

AMSTRAD EXPANSION BUS BOARD - their part no. Z70901. Just one IC is missing from its socket so it is quite likely that these boards have never been used. They contain a terrific quantity of very useful parts. There are 4 x 32 way edge connector sockets with gold-plated contacts, 7 crystals, over 40 ICs many of which are plug-in types. There are 5 micro processors Japanese-made, 8 socket connectors with gold-plated pins and hundreds of other small parts. Yours for £10, Order Ref. 10P94.

ANOTHER AMSTRAD BOARD. Reference number 112C 2001-3501. This has 6 plug-in ICs, 2 of which are 3500 DI types but the really important one is the Japanese-made D78310CW. In addition to the ICs there are 2 microprocessors, 1 SCR, 10 various transistors, over 10 diodes, 4 electrolytics, 1 Piezo sounder, 2 power transistors and a miscellaneous collection of other bits and pieces. Obviously cost a small fortune to make, our price to you is £5, Order Ref. 5P192.

WANT A SPARE 3" DISC DRIVE FOR YOUR AMSTRAD? We have, unused and believed O.K., Amstrad 3" disc drives that are all complete but need the front bezel. It shouldn't be too difficult a job to take the bezel off your old one and fit it to this and you should then have a new and perfect 3" disc drive which, as you probably know, are virtually unobtainable now. Price £15 each, Order Ref. 15P45. Or, if you haven't got a drive from which you can remove the bezel, we can supply one, with good bezel but with some other fault for only £5, Order Ref. 5P193. This may seem a lot to pay for the bezel but, remember, you will have a complete set of spare parts for your 3" drive so it really is a bargain.

OPD DUAL MICRO DRIVE UNIT. This is a twin unit, each unit having its own motor, record/playback head and PCB with all electronics. In addition to being a direct replacement in the OPD, this can also be used with the Spectrum or the QL. We have a copy of the procedure necessary and will gladly supply a photostat of this if you require it when you purchase the unit. The price is £5, Order Ref. 5P194.

12V 2A MAINS TRANSFORMER upright mounting with mounting clamp. Price £1.50, Order Ref. 1.5P8.

AM/FM RADIO CHASSIS with separate LCD module to display date and time. This is complete with loudspeaker and its mains powered but is not cased and, as yet, we have no information on how to wire it up. So, if you want a challenge, here it is! By way of recompense we will give the first customer to send us the connection details a £25 credit voucher. The price of the AM/FM radio chassis with LCD module is £3.50, Order Ref. 3.5P5. All purchasers will receive connection details directly we have them.

2, 3 AND 4 WAY TERMINAL BLOCKS the usual grub screw types. Parcel containing a mixture of the 3 types, giving you 100 ways for £1, Order Ref. 875.

12/24V DC SOLENOID. The construction of this is such that it will push or pull as the plunger is a combined rod and piston. With 24V this is terrifically powerful but is still quite good at 12V and, of course, it can be operated by any intermediate voltage with increasing or decreasing power. It has all the normal uses of a solenoid and an extra one, if wired in series with a make and break, this could be a scribing tool for marking plastics and soft metals. We welcome other ideas and will give a £25 credit voucher for any used. Price £1, Order Ref. 877.

2M 3-CORE LEAD terminating with flat pin instrument socket, £1, Order Ref. 879. Ditto but with plug on the other end so that you could use this to extend an instrument lead. £1.50, Order Ref. 1.5P10.

MULTI-CORE CABLES all with 8A 230V cores so suitable for disco and other special lighting effects. With earthable woven screen and thick pvc outer. 3 core, 30p per metre, 16 core, 50p per metre, 18 core, 80p per metre, 25 core, £1 metre and 36 core, £1.50 per metre.

VARIAC an infinitely variable unit gives any voltage from 0-230 a.c. at 1/2A. Obviously an invaluable piece of equipment which should be in every workshop and probably would be except that the usual price for this is £35 plus VAT. Now is your chance to buy one, brand new, at £15 including VAT, Order Ref. 15P42B.

ULTRA THIN DRILLS Actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per pack, Order Ref. 797B.

YOU CAN STAND ON IT! Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools. Internal size approx. 10 1/2" x 4 1/2" x 6" high. These are complete with snap closure lip and shoulder-length carrying strap. Taken from used equipment but in good condition, price £2, Order Ref. 2P283B.

BUILD YOUR OWN NIGHT LIGHT, battery charger or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket. We have two cases, one 3 1/2" x 2 1/4" x 1 3/4" deep, £1 each, Order Ref. 845. The other one is 2 1/2" x 2 1/4" x 1 1/4" deep, 2 for £1, Order Ref. 565.

SAFETY LEADS curly coil so they contract but don't hang down. Could easily save a child from being scalded. 2 core, 5A, extends to 3m, £1, Order Ref. 846, 3 core, 13A, extends to 1m, £1 each, Order Ref. 847, 3 core, 13A, extends to 3m, £2 each, Order Ref. 2P290.

POWER SUPPLY WITH EXTRAS mains input is fused and filtered and the 12V dc output is voltage regulated. Intended for high class equipment, this is mounted on a PCB and, also mounted on the board but easily removed, are 2 12V relays and a Piezo sounder. £3, Order Ref. 3P80B.

5V 2.5A POWER SUPPLY UNIT £5, Order Ref. 5P186.

ULTRA SONIC TRANSDUCERS 2 metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref. 1.5P14.

100W MAINS TRANSFORMERS normal primaries 20-0-20 at 2.5A. or 30V at 3.5A, £4, Order Ref. 4P24. 40V at 2.5A, £4, Order Ref. 4P59. 50 V at 2A, £4, Order Ref. 4P60.

PHILIPS 9" HIGH RESOLUTION MONITOR black & white in metal frame for easy mounting, brand new still in maker's packing, offered at less than price of tube alone, only £15, Order Ref. 15P1.

16 CHARACTER 2-LINE DISPLAY screen size 85mm x 36mm, Alpha-numeric LCD dot matrix module with integral micro processor made by Epson, their Ref. 16027AR, £8, Order Ref. 8P48.

INSULATION TESTER WITH MULTIMETER Internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges. AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50, with leads, carrying case £2 extra, Order Ref. 7.5P14.

MAINS 230V FAN best make "PAPST" 4 1/2" square, metal blades, £8, Order Ref. 8P8.

2MW LASER Helium neon by Philips, full spec. £30, Order Ref. 30P1. Power supply for this in kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well £18, Order Ref. 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £69, Order Ref. 69P1.

1/3 HP 12V MOTOR - THE FAMOUS SINCLAIR C5 brand new, £15, Order Ref. 15P8.

SOLAR CHARGER holds 4 AA nicads and recharges these in 8 hours, in very neat plastic case, £6, Order Ref. 6P3.

FERRITE AERIAL ROD 8" Long x 3/4" diameter, made by Mullard. Complete with 2 coil formers. 2 for £1, Order Ref. 832B.

AIR SPACED TRIMMER CAPS 2-20 pf ideal for precision tuning UHF circuits, 4 for £1, Order Ref. 818B.

FIELD TELEPHONES just right for building sites, rallies, horse shows, etc., just join two by twin wire and you have two way calling and talking and you can join into regular phone lines if you want to. Ex British Telecom in very good condition, powered by batteries (not included) complete with shoulder slung carrying case, £9.50, Order Ref. 9.5P/2.

MAINS ISOLATION TRANSFORMER stops you getting "to earth" shocks. 230V In and 230V out. 150watt upright mounting, £7.50, Order Ref. 7.5P/5 and a 250W version is £10, Order Ref. 10P79.

MINI MONO AMP on PCB. Size 4" x 2" with front panel holding volume control and with spare hole for switch or tone control. Output is 4 watt into 4 ohm speaker using 12V or 1 watt into 8 ohm using 9V. Brand new and perfect, only £1 each, Order Ref. 495.

AMSTRAD POWER UNIT 13.5V at 1.9A encased and with leads and output plug, normal mains input £8, Order Ref. 6P23.

ATARI 65XE at 65K this is quite powerful, so suitable for home or business, unused and in perfect order but less PSU, only £19.50, Order Ref. 19.5P/5B.

80W MAINS TRANSFORMERS two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref. 3P106 the other 40V 2A, Order Ref. 3P107, only £3 each.

PROJECT BOX size approx 8" x 4" x 4 1/2" metal, sprayed grey, louvred ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref. 3P74.

12V SOLENOID has good 1/2" pull or could push if modified, size approximately 1 1/2" long x 1" square, £1, Order Ref. 232.

WATER VALVE 230V operated with hose connections, ideal for auto plant spray or would control air or gas into tanks etc., £1 each, Order Ref. 370.

BUILDING YOUR OWN PSU, battery charger, night light, or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket? We have two cases, one 3 1/2" x 2 1/4" x 1 3/4" deep, £1 each, Order Ref. 845. The other one is 2 1/2" x 2 1/4" x 1 1/4" deep, 2 for £1, Order Ref. 565.

EXPERIMENTING WITH VALVES don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250V at 75mA and 6.3V at 3A. £5, Order Ref. 5P167.

15W 8 OHM 8" SPEAKER & 3" TWEETER made for a discontinued high quality music centre, gives real hi-fi, and only £4 per pair, Order Ref. 4P57.

3V SOLAR PANEL price £3, Order Ref. 3P99B.

3 GANG .0005 MFD TUNING CONDENSER with slow motion drive. Beautifully made by Jackson Brothers and current list price is probably around £20. Yours for £5, Order Ref. 5P189.

STEREO HEADPHONES extra lightweight with plug, £2 each, Order Ref. 2P261.

BT TELEPHONE LEAD 3m long and with B.T. flat plug ideal to make extension for phone, fax, etc. 2 for £1, Order Ref. 552.

WATER PUMP very powerful with twin outlets, an ideal shower controller, mains operated, £10, Order Ref. 10P74. Ditto but with a single outlet. Same price & order ref. Please specify which one you require.

0-1MA FULL VISION PANEL METER 2 1/2" square, scaled 0-100 but scale easily removed for re-wiring, £1 each, Order Ref. 756.

PCB DRILLS 12 assorted sizes between .75 and 1.5mm, £1 the lot, Order Ref. 128.

Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing.

Orders over £25 post free.

M & B ELECTRICAL SUPPLIES LTD

12 Boundary Road, Hove,
Sussex BN3 4EH

Telephone (0273) 430380

Fax or phone (0273) 410142

LIMITED SUPPLY ITEMS are only described in our newsletter. Over 50 appear in our current issue. If you order something this month you will receive this and the next three issues posted to you free of charge.

THIS MONTH'S NIP is a first-class, battery operated, fan. Japanese-made (Nippon), this is approximately 93mm square, its optimum voltage is 12 but it operates very well with only 6V when the current is only 100mA. Brushless, so there are no parts to wear out, nor will this interfere with your computer. Price only £4, Order Ref. 4P65. Mains power supply unit to operate this at variable speeds, £2, Order Ref. 2P3.

JUST ARRIVED a 5" 20W 4ohm, mid-range speaker, £3, Order Ref. 3P145 and a matching 4ohm 20W tweeter, £1.50, Order Ref. 1.5P9.

HART

HART AUDIO KITS - YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HART KITS give you the opportunity to build the very best engineered hifi equipment there is, designed by the leaders in their field, using the best components that are available.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

In short HART is your 'friend in the trade' giving you, as a knowledgeable constructor, access to better equipment at lower prices than the man in the street.

You can buy the reprints and construction manual for any kit to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

Our list will give you fuller details of all our Audio Kits, components and special offers.

AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hifi system. This kit is your way to get EK performance for a few tenths of the cost!. Featured on the front cover of 'Electronics Today International' this complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic:- "The external view is that of a thoroughly professional piece of audio gear, neat elegant and functional. This impression is greatly reinforced by the internal appearance, which is redolent of quality, both in components and in layout." Options include a stereo LED power meter and a versatile passive front end giving switched inputs using ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility so that for use with tuners, tape and CD players, or indeed any other 'flat' inputs the power amplifier may be used on its own, without the need for any external signal handling stages. 'Slave' and 'monobloc' versions without the passive input stage and power meter are also available. All versions fit within our standard 420 x 260 x 75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised, and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/heatsink fitted with IEC mains input and output sockets. All the circuitry is on professional grade printed circuit boards with roller tinned finish and green solder resist on the component ident side, the power amplifiers feature an advanced double sided layout for maximum performance. All wiring in this kit is pre-terminated, ready for instant use!

RLH11 Reprints of latest articles.....£1.80
K1100CM HART Construction Manual.....£5.50

LINSLEY HOOD 1400 SERIES ULTRA HIGH-QUALITY PREAMP

Joining our magnificent 80 Watt power amplifier now is the most advanced preamplifier ever offered on the kit, or indeed made-up marketplace. Facilities include separate tape signal selection to enable you to listen to one programme while recording another, up to 7 inputs, cross recording facilities, class A headphone amplifier, cancellable 3-level tone controls and many other useful functions, all selected by high quality relays. For full details see our list.

LINSLEY HOOD 'SHUNT FEEDBACK' R.I.A.A. MOVING COIL & MOVING MAGNET PICKUP PREAMPLIFIERS



Modern, ultimate sound systems are evolving towards built-in preamplifiers within or near the turntable unit. This keeps noise pickup and treble loss to a minimum. We now offer two units, both having the sonically preferred shunt feedback configuration to give an accurate and musical sound, and both having the ability to use both moving magnet and moving coil cartridges.

Kit K1500 uses modern integrated circuits to achieve outstanding sound quality at minimal cost. The very low power requirements enable this unit to be operated from dry batteries and the kit comes with very detailed instructions making it ideal for the beginner. K1500 Complete kit with all components, printed circuit board, full instructions and fully finished case.....£67.99
Instructions only.....£2.80
Kit K1450 is a fully discrete component implementation of the shunt feedback concept and used with the right cartridge offers the discerning user the ultimate in sound quality from vinyl disks. Can be fitted inside our 1400 Preamp, used externally or as a standalone unit. It has a higher power requirement and needs to be powered from our 1400 Series preamplifier or its own dedicated power supply. K1450 Complete kit of board mounting parts for discrete component RIAA preamplifier.....£61.06
1500/2-B Case to suit, including Hardware...£39.52
K1565 Power Supply in matching case. Features shielded toroidal transformer and upgrade path to full preamp power supply.....£79.42

ALPS PRECISION LOW-NOISE STEREO POTS.



To fulfil the need for higher quality controls we are now importing an exciting new range of precision audio pots in values to cover most quality amplifier applications. All in 2-gang stereo format, with 20mm long 6mm dia. steel shafts. Now you can throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Motorised versions have 5V DC Drive motor.

2-Gang 100K Lin.....£8.67
2-Gang 10K & 50K Log.....£9.40
2-Gang 10K Special Balance, zero crosstalk and zero centre loss.....£10.48
2-Gang 20K Log (Volume Control) MOTORISED.....£19.20
2-Gang 10K Special Balance, MOTORISED, zero crosstalk and < 10% centre loss with near Log/Antilog Tracks).....£19.98

STUART REEL-TO-REEL TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias circuit system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allows a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. Ideal for bringing that old valve tape recorder back to life. Suitable stereo heads are in our head list. This basic kit is suitable for advanced constructors only. K900W Stereo Kit with Wound Coils and Twin Meter Drive.....£123.93
RJS1 Reprints of Original Descriptive Articles.....£3.60

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are suitable for use with any high quality cassette deck. Switched bias and equalisation to cater for chrome and ferric tapes. Very versatile, with separate record and play circuits and easy to assemble on plug-in PCBs. Complete with full instructions. Complete Stereo Record/Play Kit.....£62.58
VU Meters to suit.....(Each) £3.99
RLH1 & 2 Reprints of original Articles.....£2.70

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. For top performance cassette recorder heads should be replaced every 1,500 hours. Fitting one of our high quality replacement heads could restore performance to better than new! Standard inductances and mountings make fitting easy on nearly all machines (Sony are special dimensions, we do not stock) and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users.

HC80 NEW RANGE High Beta Permalloy Stereo head. Modern space saver design for easy fitting and lower cost. Suitable for chrome metal and ferric tapes, truly a universal replacement head for everything from hi-fi decks to car players and at an incredible price too!.....£8.30
HS16 Sendust Alloy Stereo Head.....£21.49
HRP373 Downstream Monitor Stereo Combination Head.....£53.90
HC15 Special Offer of Standard Quality Stereo R/P Head with slight face scratches.....3 for Only £4.80
HQ551A 4-Track RECORD & Play Permalloy Head for auto-reverse car players or quadraphonic recording.....£8.75
HM120 Standard Mono R/P Head.....£3.44
H524 Standard Erase Head.....£1.90
H561 Hi Field Erase Head for METAL Tapes.....£3.49
SM150 2/2 (Double Mono) DC Erase Head.....£5.20
HQ751E 4/4 True 4-Track Erase Head.....£57.06

REEL TO REEL HEADS

999R 2/4 Record/Play 110mH. Suits Stuart Tape Circuits.....£13.34
998E 2/4 Erase Head 1mH. Universal Mount. Suits Stuart.....£11.96

TAPE RECORDER CARE PRODUCTS

DEM1 Mains Powered Tape Head Demagnetizer, prevents noise on playback due to residual head magnetisation.....£4.08
DEM115 Electronic, Cassette Type, demagnetizer.....£8.61

Send or 'phone for your copy of our List (50p) of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write or telephone your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows: -INLAND Orders up to £20 - £1.50
Orders over £20 - £3.50 Express Courier, next working day. £10 (For safety all computer parts are only sent by courier) OVERSEAS - Please see the ordering information with our lists.



QUALITY
AUDIO KITS

24 hr. SALES LINE
(0691) 652894

ALL PRICES
INCLUDE VAT
AT 17.5%

HART
HART ELECTRONIC KITS LTD.
6 PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

Everyday Electronics,



SHOP OPEN 9-5 Mon-Fri 9-2 Sat --- OFFICIAL ORDERS WELCOME --- KIT LIST - S.A.E

VERSATILE BBC INTERFACE

A comprehensive interface which allows the BBC computer to be connected safely to a wide range of input and output devices. Two leads connect the interface to the User Port and the Printer port. The interface connects to the 'real world' via standard screw terminal blocks. Up to 16 outputs (all via plug-in single pole change over relays - 8 supplied) and 8 fully protected inputs. L.e.d. status monitoring is provided on all input and output lines. The interface requires an independent 12Volt supply.

KIT 844.....£51.95

STEPPING MOTOR DRIVER & INTERFACE

A single board stand-alone stepping motor driver with built in oscillator and speed control circuits. A computer is not required with this board which will drive most unipolar 4 phase motors. Variable Acceleration, Speed, and Direction, may be controlled in HALF STEP, FULL STEP, and ONE PHASE modes. Up to 35V and 1.5A per phase. L.e.d. mimic display. Connector is provided for a computer port. The Kit includes our MD35 motor

KIT 843 £29.95 - BUILT £44.95

DIGITAL LCD THERMOSTAT

A versatile thermostat using a thermistor probe and having an I.c.d. display. MIN/MAX memories, - 10 to 110degrees celsius, or can be set to read in Fahrenheit. Individually settable upper and lower switching temperatures allow close control, or alternatively allow a wide 'dead band' to be set which can result in substantial energy savings when used with domestic hot water systems. Ideal for greenhouse ventilation or heating control, aquaria, home brewing, etc. Mains powered, 10A SPCO relay output. Punched and printed case.

KIT 841.....£29.95

4 CHANNEL LIGHT CHASER

A 1000W per channel chaser with Zero Volt Switching, Hard Drive, and full inductive load capability. Built-in mic. and sophisticated 'Beat Seeker' circuit - chase steps to music, or auto when silent. Variable speed and mic. sensitivity control, I.e.d. mimic on front panel. Switchable for 3 or 4 channels. P552 output socket. Suits Rope Lights, Pin Spots, Disco, and Display lighting.

KIT 833.....£32.13

SUPERHET LW MW RADIO

At Last an easy to build SUPERHET AMradio kit. Covers Long and Medium waves. Built in loudspeaker with 1 Watt output. Excellent sensitivity and selectivity provided by ceramic IF filter. Simple alignment and tuning without special equipment. Supplied with pre-drilled transparent front panel and dial, for interesting see-through appearance.

KIT 835.....£17.16

ACOUSTIC PROBE

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches, and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers, and nosy parkers!

KIT 740.....£19.98

PESt SCARER

Produces high power ultrasound pulses. L.e.d. flashes to indicate power output. Battery powered 9 - 12V, or mains adaptor £2.00 EXTRA.

KIT812.....£14.81

KIT HIGHLIGHT

DIGITAL CAPACITANCE METER KIT 493

This has been one of Magenta's best ever kits. It provides clear readings of capacitance values from few pF up to thousands of uF. It is ideal for beginners as there is no confusion over the placing of the decimal point, and it allows obscurely marked components to be identified quickly and easily. Quartz controlled accuracy of 1%, large clear 5 digit display and high speed operation make it a very useful instrument for production and testing departments. The kit is now supplied with a punched and printed front panel as well as the case, all components and top quality printed circuit board. When assembled it looks a really professional job for a limited time this kit is offered at a new low price.



SPECIAL KIT PRICE £34.95
(reduced from £49.95)

MOSFET VARIABLE BENCH POWER SUPPLY 25V 2.5A

Our own high performance design. Variable output Voltage from 0 to 25V and Current limit from 0 to 2.5A. Capable of powering almost anything. Two panel meters indicate Voltage and Current. Fully protected against short-circuits. The variable Current limit control makes this supply ideal for constant current charging of NICAD cells and batteries. A Power MOSFET handles the output for exceptional ruggedness and reliability. Uses a toroidal mains transformer.



KIT 769.....£56.82

8 CHANNEL LIGHT SHOW PROGRAMMABLE SEQUENCER

A superbly finished kit with pre-drilled case and screen printed front panel. This kit uses a microcontroller IC to generate over 100 light sequences. Programs include 3 and 4 channel versions so that existing light units can be used as well as 8 channel arrangements. NEW output design provides foolproof operation with pinspots and other difficult loads. Space in memory for 10 user programs up to 16 steps long. Keypad

KIT 838.....£57.17

BAT DETECTOR

An excellent circuit which reduces ultrasound frequencies between 20 and 100kHz to the normal (human) audible range. Operating rather like a radio receiver the circuit allows the listener to tune-in to the ultrasonic frequencies of interest. Listening to Bats is fascinating, and it is possible to identify various different types using this project. Other uses have been found in industry for vibration monitoring etc.

KIT 814.....£21.44

QUICK CAPACITANCE TESTER

A low cost hand-held audio/visual unit which can identify short, open and working capacitors quickly and with a minimum of fuss. Also gives indication of leakage current. An ideal kit for beginners, built on a single printed circuit board which has large copper areas used as test pads. Only a minimum of wiring is needed. 2 I.e.d.s and a piezo transducer provide the output indication.

KIT 834.....£10.34

IONISER

A highly efficient mains powered Negative Ion Generator that clears the air by neutralising excess positive ions. Many claimed health benefits due to the ioniser removing dust and pollen from the air and clearing smoke particles. Costs virtually nothing to run and is completely safe in operation. Uses five point emitters.

KIT 707.....£17.75

ACTIVE I.R. BURGLAR ALARM

This alarm is useful where ordinary 'passive' (pir) detectors are not suitable. It works by detecting disturbances to its own Short wave infra-red beam. Output is via mains rated relay contacts. Built in timer, and mains transformer.

KIT 700.....£40.74

12V EPROM ERASER

A safe lowcost eraser for up to 4 EPROMs at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790.....£28.51

EE TREASURE HUNTER

Our own widely acclaimed design. This sensitive Pulse Induction metal detector picks up coins and rings etc up to 20 cm deep. Negligible 'ground effect' means that the detector can even be used with the head immersed in sea water. Easy to use, circuit requires only a minimum of setting up as a Quartz crystal provides all of the critical timing. Kit includes search-head, handle, case, PCB and all components.

KIT 815.....£45.95

INSULATION TESTER

A reliable and neat electronic tester which checks insulation resistance of wiring and appliances etc., at 500 Volts. The unit is battery powered, simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. A very popular college project.

KIT 444.....£22.37

3 BAND SHORT WAVE RADIO

Covers 1.6 to 30 Mhz in three bands using modern miniature plug-in coils. Audio output is via a built-in loudspeaker. Advanced stable design gives excellent stability, sensitivity and selectivity. Simple to build battery powered circuit. Receives a vast number of stations at all times of the day.

KIT 718.....£30.30

DIGITAL COMBINATION LOCK

Digital lock with 12 key keypad. Entering a four digit code operates a 250V 16A relay. A special anti-tamper circuit permits the relay board to be mounted remotely. Ideal car immobiliser operates from 12V. Drilled case, brushed aluminium keypad.

KIT 840.....£19.86

PORTABLE ULTRASONIC PESt SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56

LIGHT RIDER DISCO LIGHTS

A six channel light driver that scans from left to right and back continuously. Variable speed control. Up to 500 watts per channel. Housed in a plastic box for complete safety. Built on a single printed circuit board.

KIT 560.....£22.41

LIGHT RIDER 9-12V CHASER LIGHTS

A low voltage DC powered end-to-end type chaser that can be set for any number of lights between 3 and 16. The kit is supplied with 16 I.e.d.s but by adding power transistors it is possible to drive filament bulbs for a larger brighter display. Very popular with car customisers and modellers. L.e.d.s can be randomly positioned and paired to give twinkling effects.

KIT 559.....£15.58

SEE OUR FULL RANGE OF KITS, BOOKS, TOOLS, AND COMPONENTS IN OUR CATALOGUE

HAMEG HM203-7 20 Mhz DUAL TRACE OSCILLOSCOPE & COMPONENT TESTER

Western Europe's best selling oscilloscope - It is RELIABLE, HIGH PERFORMANCE, & EASY TO USE. Sharp Bright display on 8 x 10 cm screen with internal graticule. A special extra feature is the built-in component tester which allows capacitors, resistors, transistors, diodes and many other components to be checked. The quality of this instrument is outstanding, and is supported by a two year parts and labour warranty.

If you are buying an oscilloscope - this is the one. - It costs a fraction more than some other 20 Mhz 'scopes but it is far far superior. Supplied with test probes, mains lead, and manual.

£338.00 £59.15 VAT Includes FREE Next-daydelivery

EDUCATIONAL BOOKS & PACKS

ADVENTURES WITH ELECTRONICS

The classic book by Tom Duncan used throughout schools. Very well illustrated, ideal first book for age 10on. No soldering. Uses an S.DEC breadboard. Book & Components £28.95, Book only £6.25

FUN WITH ELECTRONICS


An Usborne book, wonderfully illustrated in colour. Component pack allows 6 projects to be built and kept. Soldering is necessary. Age 12 on, or younger with adult help. Book & Components £20.88, Book only £2.95

30 SOLDERLESS BREADBOARD PROJECTS

A more advanced book to follow the others. No soldering. Circuits cover a wide range of interests. Book & Components £20.69, Book only £2.95

DC MOTOR/GEARBOXES

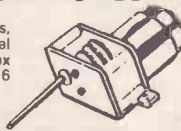Ideal for robots, buggles, and many other mechanical projects. Min. plastic gearbox with 1.5-4.5 V DC motor. 6 ratios can be set up. Small type MGS...£4.77 Large type MGL...£5.58



STEPPING MOTORS

For computer control via standard 4 pole unipolar drivers. MD35 1/4 - standard 48steps per rev...£12.99 MD38 - miniature 48 steps per rev...£9.15 MD200 - miniature 200 steps per rev...£17.10

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

Editorial Offices:

EVERYDAY ELECTRONICS EDITORIAL,
6 CHURCH STREET, WIMBORNE,
DORSET BH21 1JH

Phone: Wimborne (0202) 881749

Fax: (0202) 841692. DX: Wimborne 45314.

See notes on Readers' Enquiries below - we regret that lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY ELECTRONICS ADVERTISEMENTS,
HOLLAND WOOD HOUSE, CHURCH LANE,
GREAT HOLLAND, ESSEX CO13 0JS.

Phone/Fax: (0255) 850596

VOL. 21 No. 10 OCTOBER '92

JOINING IN OUR 21st

From next month you will notice an addition to the title of your magazine. This is because we are being joined by the readers of *Practical Electronics*. We have purchased that title from its present publishers and it will be merged with *Everyday Electronics*.

Some of the titles of our present regular pages will be changed to make PE readers feel at home and *Everyday with Practical Electronics* will continue to develop in the way EE has over the past 21 years.

Significantly the November issue is also our 21st anniversary issue - it will be 21 years to the month since EE was launched out of *Practical Electronics* and now the titles will recombine to form the best possible electronics magazine. Let me assure you that you will not be losing any of your favourite articles or range of projects, in fact we intend to add to the variety as we have always tried to do.

SIGNIFICANT

As indicated above the November issue cover will use a new logo and is based around a symbolic piece of artwork that fits in well with our 21st anniversary and with the merged titles. Both of these designs are shown in our advertisement for next month's issue on page 611.

TEACH-IN

It has been our practice, ever since EE started, to publish a Teach-In series every two years and *Teach-In '93* starts next month. This time it has been very carefully planned to cover the GCSE and "A" level electronics syllabus and our contributors have enlisted the assistance of an experienced GCSE moderator to overlook the work. We will also, with the help of the various examination boards, be publishing past questions and model answers.


To go with the new series a *Mini Lab* has been designed and this incredibly versatile test and development board will also be featured next month. We anticipate that it will become a standard for those learning about, and working with, electronics. If your interest in electronics does not encompass the General Certificate examinations you will still find the whole series very valuable as a complete tutorial in our subject.

DEMAND

Due to the likely high demand for the November issue - it also has a free 196 page catalogue banded to it - it is essential that you make sure your copy is reserved for you. **You really won't want to miss it!**

If you do not already have a standing order or a subscription you can make sure of seeing a copy by filling in the "shop save" card inserted in this issue and handing it to your newsagent, he will then keep a copy for you. If you don't like what you see when he hands you the magazine you are under no obligation to buy it - your newsagent simply returns it and is not charged anything as all copies are on sale-or-return.

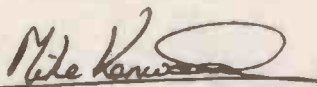What have you got to lose? There is even a free prize draw so you might wind up with a very useful prize - read the shop save card to see what it is.



SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £20. Overseas: £26 (£43.50 airmail). Cheques or bank drafts (in £ sterling only) payable to Everyday Electronics and sent to EE Subscriptions Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: 0202 881749. Subscriptions start with the next available issue. We accept Access (MasterCard) or Visa payments, minimum credit card order £5.

BACK ISSUES

Certain back issues of EVERYDAY ELECTRONICS are available price £2.00 (£2.50 overseas surface mail) inclusive of postage and packing per copy - £ sterling only please, Visa and Access (MasterCard) accepted, minimum credit card order £5. Enquiries with remittance, made payable to Everyday Electronics, should be

sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: 0202 881749. In the event of non-availability one article can be photostatted for the same price. *Normally sent within seven days but please allow 28 days for delivery. We have sold out of Jan, Feb, Mar, Apr, June, Oct, & Dec. 88, Mar & May 89 & Mar 90.*

BINDERS

Binders to hold one volume (12 issues) are available from the above address for £5.95 (£6.95 to European countries and £8.00 to other countries, surface mail) inclusive of post and packing. *Normally sent within seven days but please allow 28 days for delivery.*

Payment in £ sterling only please. Visa and Access (MasterCard) accepted, minimum credit card order £5. Tel: 0202 881749

Editor: MIKE KENWARD

Secretary: PAMELA BROWN

Deputy Editor: DAVID BARRINGTON

Business Manager: DAVID J. LEAVER

Editorial: WIMBORNE (0202) 881749

Advertisement Manager:
PETER J. MEW, Frinton (0255) 850596

Classified Advertisements:
Wimborne (0202) 881749

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self addressed envelope and international reply coupons.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that we cannot provide data or answer queries on projects that are more than five years old.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.


The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We would like to advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the U.K. Readers should check the law before using any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use. The laws vary from country to country; overseas readers should check local laws.

EXTENDED RANGE CAPACITANCE METER

STEVE KNIGHT

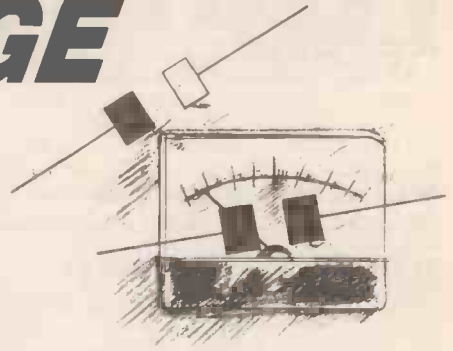

Designed to cover a spread from 2pF to 1μF and 0.5μF to 5000μF, in two switched ranges. A third switched position indicates "leakage current" - useful for checking electrolytics.

IN THE design of analogue type capacitance meters, where the instrument works on the popular principle that the output pulse duration of a monostable or one-shot multivibrator depends upon the time constant used in the feedback path, the main problem involves the measurement of capacities above a few microfarads and the elimination of stray capacitance on ranges below some 100pF. With large values of *C*, the time constant element in the design requires very small values of *R* and this leads to unreliable operation of the monostable or calls for changes in the operating frequency.

As for the strays, these are usually indeterminate and can often be as high as 25pF or so. Any attempt to get accurate readings below a few hundred picofarads is, therefore, a hit-and-miss procedure.

This present design gives a range of capacitance values from about 2pF up to 5000μF in two distinct sections: From 2pF

to 1μF on a low range and from 0.5μF to 5000μF on a high range. Further more, the stray capacitances are "tuned out" within the system so that there is no theoretical lower limit to the measurement range.

An additional feature, particularly, useful when checking electrolytics, is a qualitative measure of leakage current with an applied potential of about 9V. The full circuit diagram for the Extended Range Capacitance Meter is shown in Fig. 1 so from that let us see how the instrument does its stuff.

CIRCUIT DESCRIPTION

We assume for the general circuit explanation that the ganged Mode-Selector switches S1a through to S1g are set on Position 1, the lower capacitance range.

Transistor TR1 is a programmable unijunction type 2N6027 connected up in a self-oscillating mode with a stand-off ratio


determined by resistors R2 and R4. Capacitor C1 charges through the anode (a) resistor R1 and when the anode voltage reaches a point about 0.7V above the potential on the gate (g) the transistor switches on, discharging the capacitor through the cathode (k) resistance R3. The cycle then repeats.

Although the charging characteristic of capacitor C1 is the usual exponential sawtooth, our wanted output across resistor R3 is a short positive-going pulse at a repetition frequency of about 350Hz. The precise value is not important.

These pulses are inverted by transistor TR2 and applied to the trigger and reset inputs (pin 2 and pin 4) of the NE555 timer IC1. In the monostable mode, IC1 output at pin 3 is low until the trigger pulse is applied to pin 2. At that time, the output is driven high for a period determined by the value of the capacitor under test (*C_X*) and the selection of resistors R12 to R16 inclusive, made by Range switch S2.

The capacitor under test *C_X* charges through the selected resistor until it reaches half the supply voltage, that is, about 4.5V. This point comes about by resistor R9 being effectively in parallel with the internal divider chain of the 555 and prevents the capacitor voltage from reaching its usual design level of two-thirds the supply potential.

Fig. 1. Complete circuit diagram for the Extended Range Capacitance Meter. Note that TR1 is a programmable unijunction transistor which is made up from a pnp transistor combined with an npn transistor in a single package

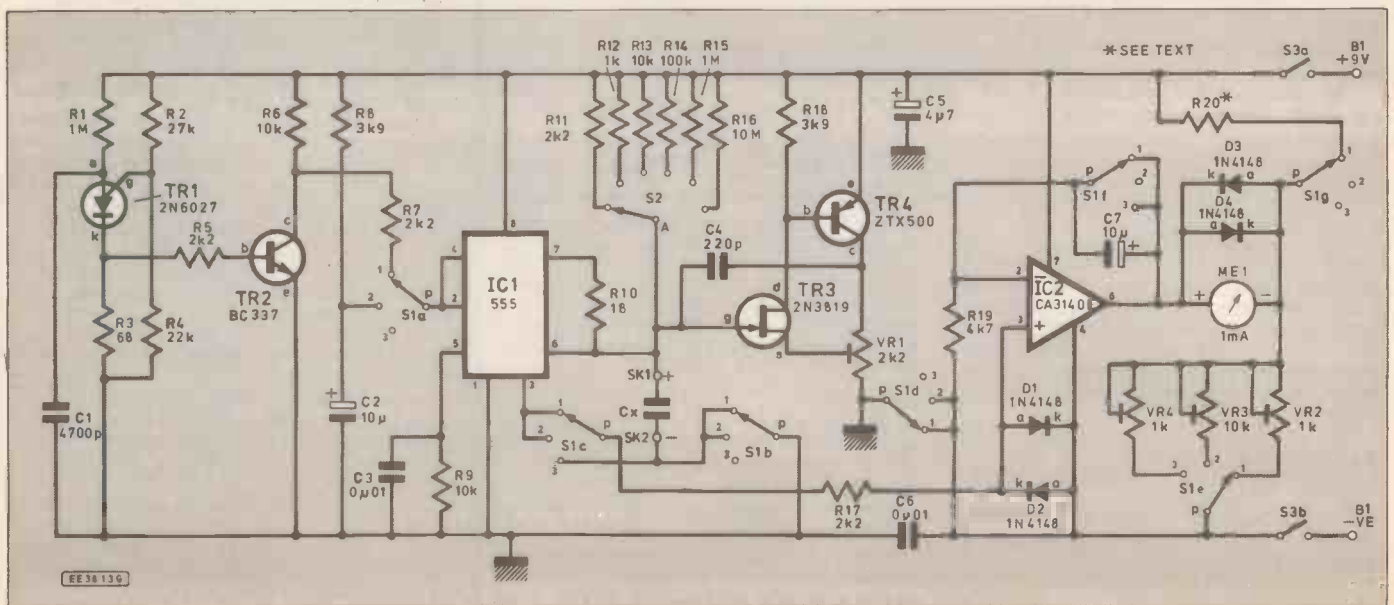

As soon as the "high" point is reached, the timer resets and C_X is discharged through pin 7. The duration of the high state on pin 3 is consequently proportional to the value of C_X , as Fig. 2 illustrates.

ZEROING

All this is quite conventional and in a simple form of this instrument, this waveform, operating at the frequency of the clock, TR1, can be used directly to deflect the pointer of a milliammeter (which will take up a position representing the average value of the waveform) and so indicate on a suitably calibrated linear scale the value of the test capacitor. However, with this elementary arrangement there is a problem with zero setting the meter, particularly on the low capacitance ranges, and the effect of

put which appears with no test capacitor connected can be effectually backed off by putting a reverse d.c. bias on the meter; this then operates as a Set Zero control. However, this leads to an additional panel control which needs adjustment each time the instrument is used.

In this present design, the strays acting across the test terminals (SK1/SK2) are eliminated by making use of the Miller effect in a f.e.t. amplifier and introducing a phase shift around the loop made up of transistors TR3 and TR4 so that an effective capacitive reactance is introduced which cancels out the effect of the strays at source. The theory of such circuits, for anyone who is interested, can be found in a number of textbooks under reactance simulation systems. Setting the method up will be explained later.

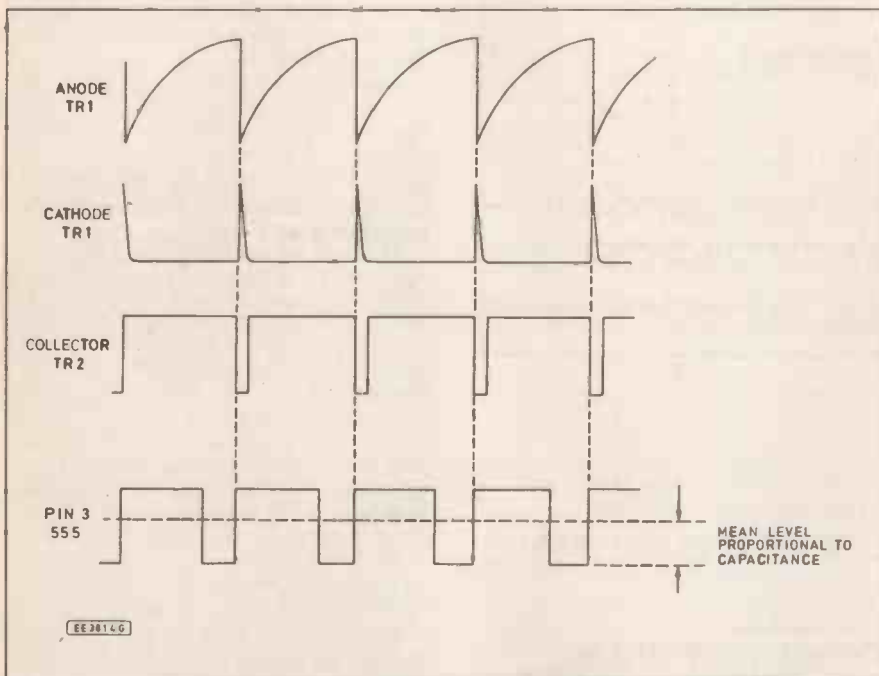


Fig. 2. Waveforms seen at the unijunction TR1, inverting transistor TR2 and the output (pin 3) of the 555 timer IC1.

strays is not positively eliminated by a "backing-off" meter current system.

The rectangular output waveform from pin 3 of IC1 is therefore fed to the non-inverting (+) input pin of IC2, a CA3140 MOSFET input op.amp connected (in this mode) as a unity gain voltage-follower. The input waveform is reduced to about 0.7V amplitude by diode D1 and d.c. restored to the earth line by diode D2. This introduction of an op.amp enables high capacitance to be measured by using it as an integrator over the appropriate ranges.

The indicating meter ME1 is connected to the output (pin 6) of IC2 by way of preset potentiometer VR2 and gives a reading which is the average value of the waveform and hence proportional to the test capacitance.

ELIMINATING STRAYS

So far, so good. But this circuit does not perform too well on the lowest capacitance range (0 - 100pF) because of the presence of strays which, in both the wiring and the effect of the 555, amounted in the original design to something like 35pF.

As mentioned above, the non-zero out-

EXTENDING THE RANGE

To measure capacitances above a few microfarads with this type of circuit normally calls for a much lower clock frequency and an extension of the monostable timing period. By converting the 3140 op.amp (IC2) into an integrator, however, by introducing a capacitor (C7) into the feedback loop and by using a single-shot trigger pulse at the input of the 555 timer (IC1), a simplified arrangement emerges which enables capacitances up to 5000 μ F to be measured with good accuracy.

What the integrator effectively does is to "hold" the meter indication of the mean pulse amplitude while the reading of capacitance is taken. Going back to Fig. 1, when switch S1 is operated to Position 2 (the High Capacitance mode) the normal clock output from the collector of TR2 is disconnected and the input to IC1 is simply derived from the junction point between resistor R8 and capacitor C2.

This may not appear as an input source at first glance but with no supply voltage applied, C2 is uncharged and hence the potential at the input of IC1 is zero. When the supply is switched on, the 555 sees this zero potential as a momentary low, hence the monostable is triggered.

As in the case of the Low Capacitance mode, a high of about 0.7V amplitude is applied to the non-inverting (+) pin of IC2 for the period over which the "test capacitor" is charging to half the supply potential. The effect of the integration which now takes place is that the i.c. output fed to the meter ramps up until at the end of the input pulse the meter reading is proportional to the duration of the pulse and hence proportional, as before, to the value of the test capacitor.

LEAKAGE

Only one other thing need concern us at this point before we move on to the constructional details of this instrument, and that is capacitor leakage. This is of more importance when checking electrolytics or perhaps some of the older



COMPONENTS

Approx cost
guidance only

£25
plus case

Resistors

R1	1M
R2	27k
R3	68
R4	22k
R6	10k (2 off)
R5, R7,	
R11, R17	2k2 (4 off)
R8, R18	3k9 (2 off)
R9	10k
R10	18
R12	1k
R13	10k
R14	100k
R15	1M
R16	10M
R19	4k7
R20	See text

All 0.25W 5% carbon film, except where stated

Capacitors

C1	4700p polycarbonate 5%
C2, C7	10µ tantalum, 16V (2 off)
C3, C6	0µ01 polycarbonate (2 off)
C4	220p polystyrene
C5	4µ7 tantalum, 16V

Switches

S1	7-pole, break-before-make, wafer switch; made up from two 4-pole 3-way wafers
S2	2-pole 6-way rotary switch, Lorlin
S3	Min. d.p.d.t. toggle switch

See
**SHOP
TALK**
Page

Potentiometers

VR1	2k2 min. preset, vertical
VR2, VR4	1k 3/4in. multiturn cermet preset (2 off)
VR3	10k 3/4in. multiturn cermet preset

Semiconductors

D1-D4	1N4148 signal diode (4 off)
TR1	2N6027 Programmable Unijunction Transistor (PUT)
TR2	BC337 npn med. power low freq. transistor
TR3	2N3819 n-channel field effect transistor (f.e.t.)
TR4	ZTX500 pnp small sig. low freq. transistor
IC1	NE555 timer i.c.
IC2	CA3140E MOSFET I/P, Bipolar O/P op.amp

Miscellaneous

ME1	1mA moving coil meter (60mm x 46mm, cutout 38mm)
-----	--

Metal case, size approx. 205mm x 152mm x 92mm; 8-pin d.i.l. socket (2 off); screw terminal post - one red, one blue; 4mm socket, yellow; plastic 28mm diameter, collet fixing, knob (with red cap) - 2 off; PP3 battery and connector; stranded connecting wire; fixing nuts and bolts; stand-off spacer; solder tag; solder, etc.

Printed circuit board available from *EE PCB Service*, code EE804.

paper types which may have been stored for some years.

For this test, switch S1 is now moved to Position 3; in this mode all the active components except IC2 are rendered inoperative by switch section S1d. IC2 reverts to its voltage-follower configuration by way of S1f, while the capacitor leakage current (if there is one) is forced to flow to the negative rail by way of limiting resistors R11, R17 and diode D1.

The voltage developed across diode D1 is applied to IC2 input, pin 3, and a deflection indicative of the level of leakage appears on the meter ME1. Because of the diode

characteristic, the indication is approximately square law and a separate calibration graph can be drawn up to rationalize the current readings in microamps leakage. It is often only sufficient to know whether a leakage is excessive or otherwise.

CONSTRUCTION

The prototype model was built (after half a dozen bread-board assemblies!) on to a small single-sided printed circuit board. (This board is available from the *EE PCB Service*, code EE804). All components except the meter, R20, D3 and D4 and the two-wafer ganged switch (S1a-S1g) are

mounted on the board and the whole assembly fits into a suitable case.

Probably the best approach is to wire up the ganged switch S1 assembly first, the various outgoing and interconnecting wires being shown in Fig. 3. Twelve leads from the actual switch tags go to the printed board and these are numbered as are the corresponding points on the board to which they are later attached.

Terminal pins are best used at the board points as it is then easier to remove a wire if a mistake is made. The specified switch is a two-wafer job, each wafer being 4-pole, 3-way, though only seven of the available eight poles are used.

It is not particularly important which banks are used for the required seven switches; what is important is that the wiring is carefully checked and that different coloured leads are used to avoid any later confusion. Use thin flexible, multi-coloured, stranded wire rather than solid; 7/0.2mm is adequate.


Note that resistor R20 is mounted directly on the switch itself, not on the board. The end of this resistor which is shown going to +V conveniently connects to the On-Off/One Shot switch S3 which is next to S1 on the suggested front panel layout.

CIRCUIT BOARD

The details of the printed board component layout and full size underside copper foil master pattern is shown in Fig. 4. There should be no problems in wiring the board up, but the usual care must be exercised with the transistors, diodes and tantalum capacitors with regard to polarity. The markings on tantalums are often notoriously difficult to interpret.

Although the prototype had solder pins mounted on the component side of the board to make the necessary connections to the Mode switch S1, this did tend to pack the wires between board and rear of the front panel when assembled. So it is possibly better to have the pins available on the copper side of the board as this makes for much easier soldering.

It seems best if all components are mounted on the rear of the front panel of

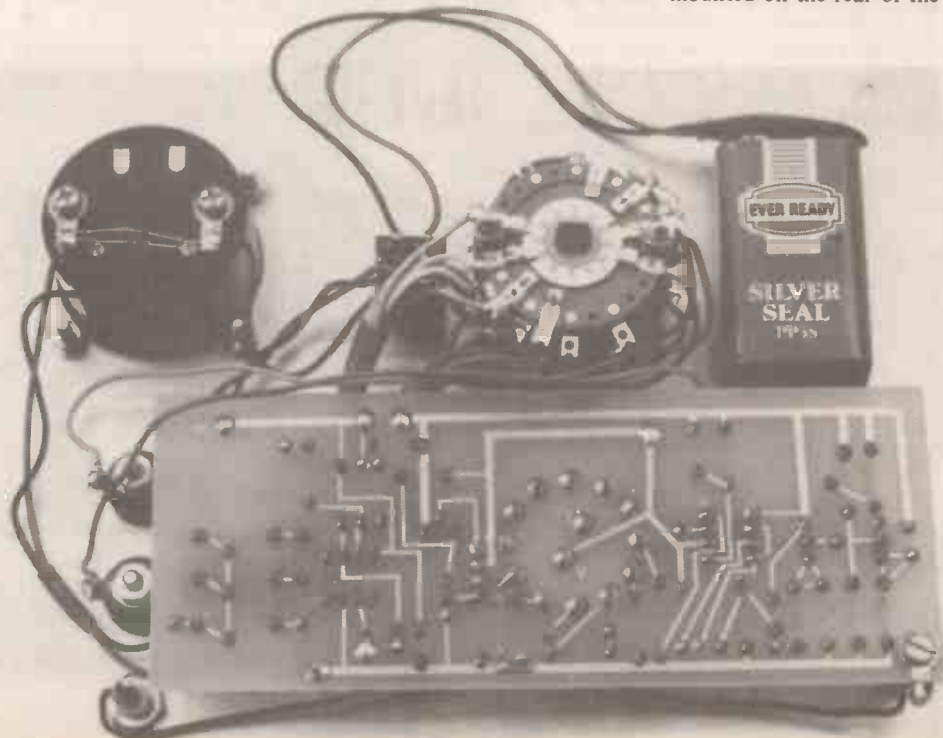

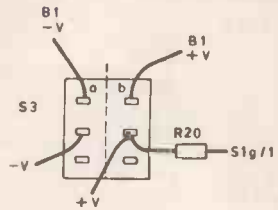
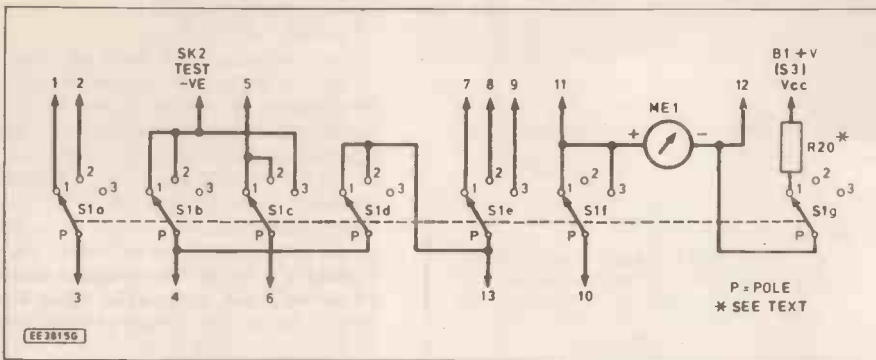


Fig. 3. Wiring to the ganged mode switch wafers. It is best to wire up the switch first, using multicoloured stranded leads for interconnecting to the circuit board. The numbers on the lead-off wires should be taken to identical ones on the p.c.b. The wiring to the On/Off switch S1 is shown above right.

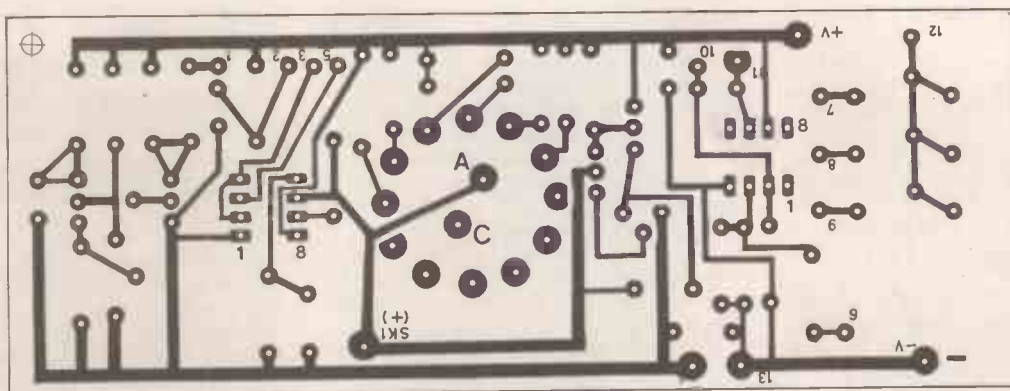
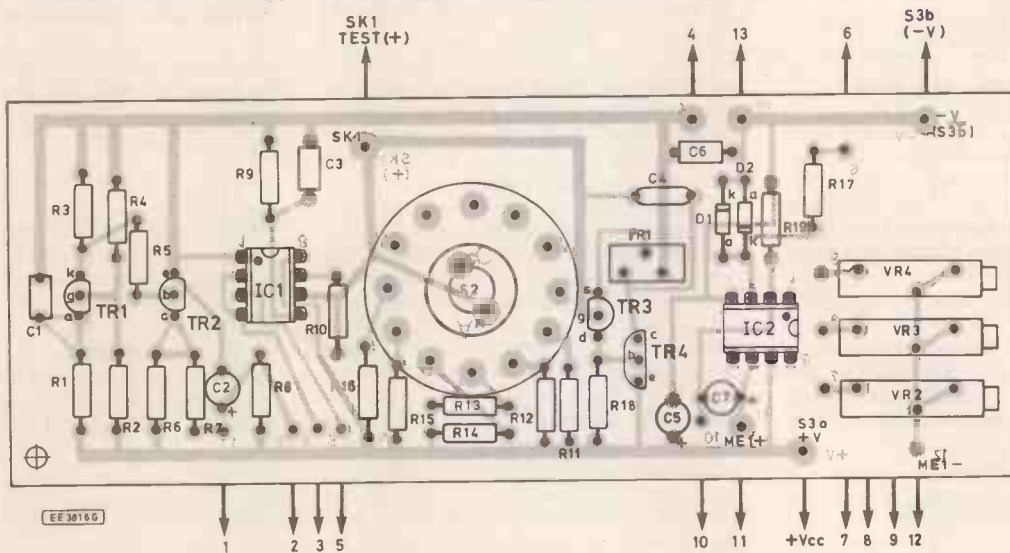
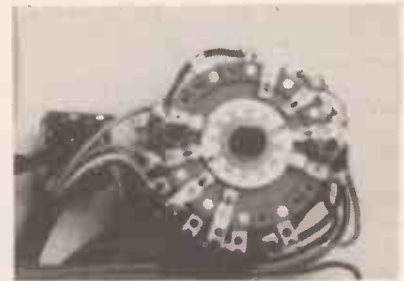
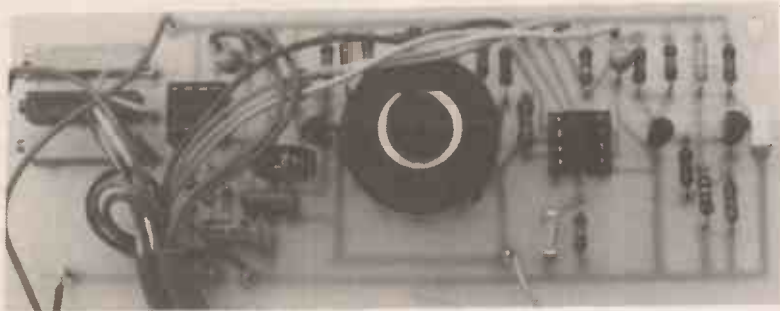


Fig. 4. Printed circuit board component layout and full size copper foil master pattern. The small numbers on the track-side are included for those who wish to wire switch S7 directly to the copper pads/pins side. The "leads" around the component side are to assist topside wiring, if preferred.

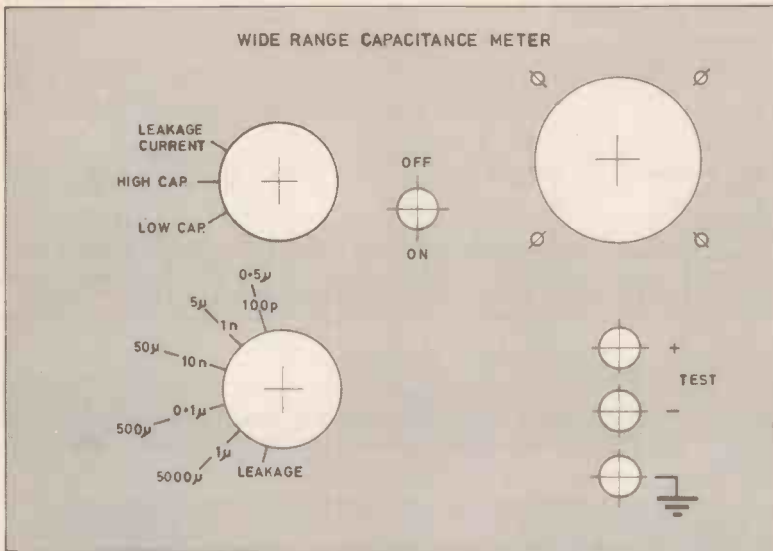


Fig. 5. Suggested front panel (half full size) layout and lettering. The drilling sizes will depend on the components used.

the box which will house the instrument. No specific case was chosen, but the one used has a 205mm x 152mm (8in. x 6in.) panel and a box depth of 92mm (3½in.).

The assembly can be comfortably housed on a panel size down to about 165mm x 127mm (6½in. x 5in.) and a suggested front panel layout is shown in Fig. 5 and the photo. This gives quite an attractive appearance when carefully labelled with rub-down lettering, but if you fancy any other arrangement by all means do your own thing.

There is nothing critical about the layout, but try to keep all the interconnecting wires as short as practicable (not tight!) especially the two to the Test terminals, whatever layout you plump for. Don't twist these last two wires together or the total strays might exceed the capabilities of the correcting circuitry.

The circuit board is fixed to the front panel by the bush and nut mounting of Range switch S2. To prevent the possibility of the board rotating if the fixing of the switch works loose, an additional support should be provided by means of a 16mm (½in.) spacer securing the board to the panel at some other convenient point.

CALIBRATION

Provided that the assembly is correct and there are no faulty components, this instrument is very easy to set up. We start with the Low Capacitance range in conjunction with the setting of the stray compensating preset control VR1 and the selection of resistor R20 if needed.

You will need as a minimum requirement a 100pF capacitor, one per cent or better, though it is useful if you can get hold of one per cent types of values 1nF, 10nF and 0.1µF. The first two of these are readily available from a number of advertisers.

LOW CAP

First of all, set all the preset potentiometers to about their mid-travel positions. Set the Mode switch to Low Capacitance and the Range switch to 100pF. Connect the accurate 100pF "test" capacitor across the test terminals SK1/SK2, then switch on.

Adjust preset VR2 to give a full scale reading (f.s.d.) on the meter. Remove the capacitor and adjust preset VR2 very carefully to obtain a minimum reading on the meter.

Now replace the test capacitor, readjust

VR2 for full scale deflection; remove the capacitor and readjust VR2 for a minimum. This procedure may be repeated if necessary until no further changes can be produced.

It may happen that despite the elimination of the stray capacitance a very small residual reading may be evident with no test capacitor connected. This comes about from the still finite pulse width from the 555 timer.

If this is no worse than, say, a part of a scale division, ignore it; otherwise add resistor R20 at this stage to bring the reading to zero. A 100k resistor in the prototype did this, but some slight variation is possible; if you choose a value too low the meter will show a small negative reading.

This completes the calibration of the Low Cap range; if you have other accurate capacitors within the range 1nF to 1µF use them to verify that the other ranges are o.k. In all cases, it is preferable to switch off when a capacitor is changed as your body capacity can send the meter over to full scale, particularly on the two lowest ranges.

HIGH CAP

The problem of calibrating the High Cap range is getting hold of accurate high value capacitors. Electrolytics are out of the question, of course, but fortunately for this project with its lowest "high" range of 0.5µF, any capacitor from 0.1µF to 0.5µF (or suitable parallel combinations to make up a value within this range) will do for the calibration.

With the instrument switched off, connect the known capacitor to the Test terminals, set the Mode switch to High Cap and the Range switch to the 0.5µF position. Now switch on; the meter reading will rise rapidly as the integrator IC2 output ramps upwards, and after a second or two will come to rest at some definite point.

Now adjust preset VR3 to set the meter reading to coincide with the value of the known capacitor. This then completes the "high" calibration.

Notice the procedure for measurement on the High range: the instrument *MUST* be switched off when the capacitor is connected and the range selected, and then switched on. This switching operates the "single-shot" triggering of the 555 timer IC1 and initiates the integration process.

If there is any drift of the reading on this range, suspect a possible leakage in C7, the integrating capacitor.

LEAKAGE TESTING

The following check gives an indication of the leakage current with about 7.5V applied across the test capacitor. To set the system up, switch both Mode and Range switches to Leakage, put a shorting link across the test terminals SK1, SK2, switch on and adjust preset VR4 to give a full scale reading.

As already mentioned, the meter reading (apart from the 1mA f.s.d. obtained in this setting-up procedure) is not directly indicative of the actual leakage current because of the effect of the non-linearity of diode D1. Fig. 6 shows the graph connecting the meter reading with the true leakage current. For example, if with a particular electrolytic as the test capacitor the meter read 0.8mA (remember, it is a 1mA meter) the true leakage current would be about 150µA.

Below a reading of 0.4mA the leakage is less than a few microamps. Mica, silvermica, polythene, polycarbonate and similar types of capacitor will normally give a zero reading, but some older paper types may show small leakages if they have been stored for some time.

Electrolytic capacitors on the other hand will display small leakages in nearly every instance, but these should not normally exceed a few micro-amps; the leakage goes up with the capacity in

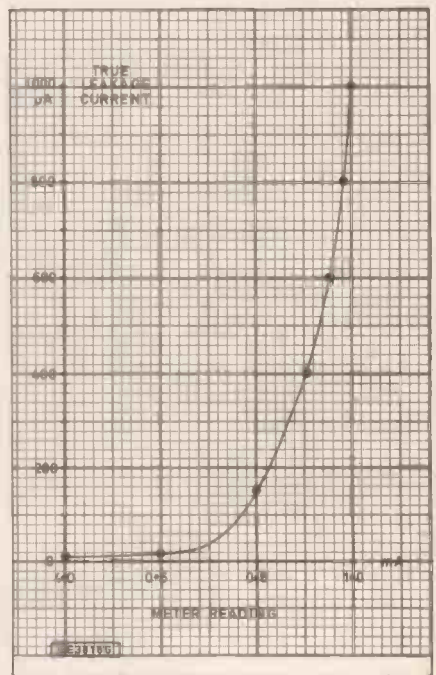


Fig. 6. Typical calibration curve determining the "true leakage current".

general terms. If an electrolytic has been on the shelf for some time it will show a high leakage for a short while, but reforming will take place in the leakage mode and the meter reading should fall back accordingly.

Always make sure that capacitors, particularly large electrolytics, are completely discharged before attaching them to the Test terminals.

You can plot your own graph by observing the meter readings obtained from a range of known resistors connected across the Test terminals, deducing the true current from Ohm's law. □

DELICIA

ELECTRONICS LTD

**DELICIA ELECTRONICS LTD,
DELTA ENTERPRISES INC,
14 ST. MERYL PARK,
GLEN ROAD,
BELFAST BT11 8FY,
N. IRELAND.
TEL: (0232) 61 1995**

DELICIA ELECTRONICS, EUROPE'S, BIGGEST, BEST, CHEAPEST SWITCHBOARD MANUFACTURER

VHF/FM TRANSMITTERS,

FM MICROPHONE -

Up to 2½ miles radius (2 watts output, runs for weeks on one 9 volt battery) **£24.99.**


TRANSMITTER, 250mW,

MINI BUG, fully tunable on FM. 9V DC.

£14.99.


BROADCAST TRANSMITTERS,

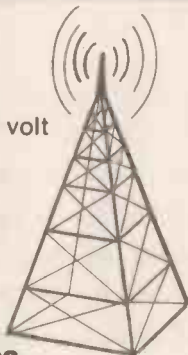To Radio Authority restricted licence standards, from, **£35, to £63.**



TELEPHONE EQUIPMENT.

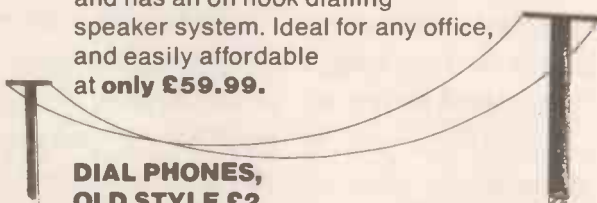(PLESSEY). Has an input/output, of 12 phone lines, 10 extension lines, conference facility, hold, recall, and has an on hook dialling speaker system. Ideal for any office, and easily affordable **at only £59.99.**



**DIAL PHONES,
OLD STYLE £2**

MAIN COMPUTER FOR A NETWORK OF COMPUTER TILLS AS USED IN NEXT SUPER STORES COMES WITH MONITOR.

It has a 132 key qwerty keyboard, key lock, daisy wheel printer, and a second screen at the back to show the shop name, SLIGHT CIRCUIT PROBLEM WITH THE MONITOR (EASILY REPAIRABLE), NORMALLY WORTH WELL

OVER A THOUSAND POUNDS, **OUR PRICE £75.** EVEN THE PARTS ARE WORTH MUCH MORE.



SWITCH BOARDS,


MINI RECORDING STUDIO EQUIPMENT, (DELICIA PRO 2000 NIVAG).

This device can record from a microphone, guitar, and other instruments (syncro) on to an audio cassette. Comes with V.U. meters and LED warning lights and amplifier, assorted faders and pots. **ONLY £65.**

MINI DISCO MIXING UNIT,

(DELICIA PRO 1000 ANOR),

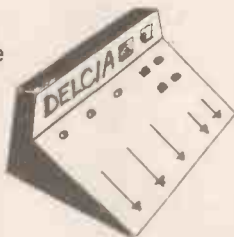This device can mix a microphone on top of music outputs, from record decks and tape players (not supplied). It is also capable of mixing and fading music from deck to deck, **£65.**



MUSIC TO MICROPHONE BROADCAST MIXING DECK AND AMPLIFIER,

(DELICIA PRO 200 APOLLO),

This deck is all that is needed for mixing music to a transmitter, **£65.**

PHONE EQUIPMENT,

ZEON DATA BANK PHONE DIALLER,

Stores up to 120 names, phone numbers, addresses, and appointments, it also has a calculator and can automatically dial phone numbers you have stored, (a real executive toy)

ONLY £23.99.



ZEON



**COMPUTER HARD AND FLOPPY DISK DRIVES
WORTH AT LEAST £13 OUR PRICE £3.99 EACH.**

BASF C60 AUDIO TAPES, ONLY 59p EACH.

ORDERING INFORMATION

ALL PRICES INCLUDE V.A.T. & P&P. NO MINIMUM ORDER CHARGE.


PRICES ARE SUBJECT TO CHANGE WITHOUT WARNING, PRICES WERE RIGHT AT TIME OF GOING TO PRESS.

MAKE CHEQUES AND POSTAL ORDERS PAYABLE TO DELICIA ELECTRONICS

THE DELICIA CATALOGUE FOR 1992-3 IS AVAILABLE FREE OF CHARGE AT THE ABOVE ADDRESS.

CIRCUIT SURGERY

MIKE TOOLEY B.A.

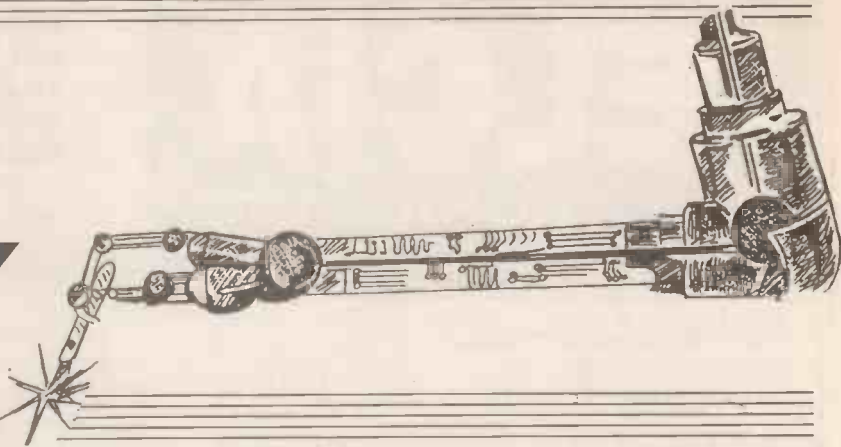

Welcome once again to Circuit Surgery, our regular clinic for readers' problems. This month we have some useful points relating to the selection of fuses for use with low voltage high current d.c. power supplies. We also revisit the timer software described in August's installment of Circuit Surgery and help to sort out some of the confusion which surrounds the pin connecting conventions used with some of the more popular silicon transistors. There is also a circuit which can be used to increase the video signal gain provided by a monitor or colour TV receiver.

Fuses – Their Uses and Abuses

Malcolm Taylor writes from Kent to ask me whether I could give some advice on suitable types and ratings for fuses used in a low-voltage power supply. Malcolm's letter includes a number of interesting observations together with some useful suggestions and so I make no apologies for quoting it in its entirety:

"I am building a high-current d.c. power supply which produces an output of 13.5V at 10A. The supply uses a 2N3055 silicon power transistor as I have a plentiful supply of these and they seem to be extremely rugged.

I am feeding the base terminals of the series pass transistors from the output of a "jacked-up" 7812 regulator. Initial experiments with a transformer rated at 12V and 10A proved to be unsuccessful. Instead I had to use a component rated at 15V 12A together with a hefty bridge rectifier and two parallel connected 6800µF electrolytic capacitors.

Other measures taken to prevent the output voltage dropping when on-load include the use of some very hefty wiring. This runs from the transformer to the bridge rectifier and the two reservoir capacitors and also from the output terminals to the series pass transistors and a single earth/common point. Wire stripped from off-cuts of domestic mains wiring was found to be ideal for this purpose!

I calculated the required current rating (and allowing for a reasonable margin) before fitting a pair of 1A mains fuses in series with the mains supply to each pole of the on/off switch. However, one or other of the fuses seemed to blow as soon as the unit was switched on. A pair of 5A fuses tend to remain intact but have also blown on one or two occasions when the unit is first switched on. Can you tell me what causes this problem and what the fuse rating should be?

The circuit of Mr Taylor's simple yet effective power supply is shown in Fig. 1. The output voltage of the regulator (normally 12V) is increased by raising the voltage at the common terminal with

respect to ground. This is quite a useful technique particularly when the desired output voltage does not coincide with the voltage provided by a fixed voltage regulator.

Mr Taylor's problem arises from the very high "in-rush" current which occurs at the instant of switching on as C1 and C2 take charge for the first time. Furthermore, if the mains switch closes at, or near, the positive or negative peak of the mains voltage, a very appreciable current will be drawn from the mains, albeit momentarily. Once the capacitors have become charged, the mains current will settle to a relatively small value (about 1A when the supply is fully loaded).

The two mains fuses should be 20mm "high breaking capacity" (HBC) anti-surge components rated at 2A and fitted in suitable panel-mounted fuseholders. The anti-surge characteristic of the mains fuses will ensure that they do not rupture when the unit is first switched on and the reservoir capacitors charge for the first time.

It is important to note that the anti-surge fuses may not protect the power supply

under all eventualities as they still exhibit a finite rupturing time. A sudden short-circuit across the output will produce a very large current within the series pass transistors TR1/TR2. Under these circumstances, the fuses will rupture in a few milliseconds but this may just not be fast enough to protect the power transistors!

Pin connections

Mr Walton writes from Northampton with a timely warning to readers:

"I recently purchased some plastic transistors for use in a constructional project. After a lot of detective work I discovered to my amazement that these transistors seem to have totally different connections from those specified in the article. Why should this be?"

Well Mr Walton, it is an unfortunate fact of life that transistor pin connections are not standardised for a given encapsulation and "plastic" transistors are a particularly good example of this!

At a guess, I suspect that the transistors which you mention have been supplied in TO92 packages (see Table). Unfortunately there are at least four different pinout

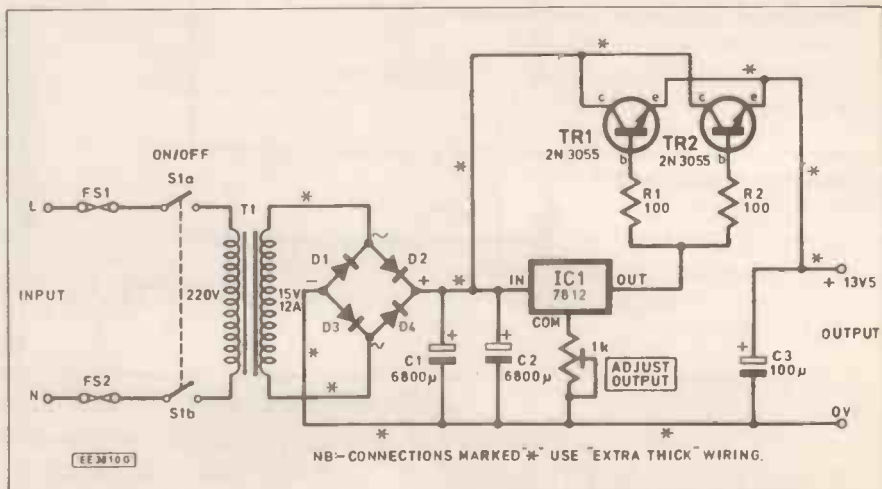


Fig. 1. Mr Taylor's high current power supply.

connecting conventions in common use for this type of encapsulation:

Package	Pins			Examples		Underside view
	1	2	3	NPN	PNP	
TO92a	b	c	e	BC182L, BC183L, BC184L	2N3702, 2N3703, BC213L, BC214L	
TO92b	b	e	c	BF594, BF595, BF694		
TO92c	e	b	c	BC547, BC548, BC549	BC327, BC557, BC558	
TO92d	c	b	e	2N3903, 2N3904, 2N4400, 2N4401	2N4402, 2N4403	

Many component suppliers include transistor pin connecting information within their catalogues and others can supply this information if requested. Finally, a copy of the latest *Towers International Transistor Selector* can be a very worthwhile investment. This book contains tabulated data on over 29,000 transistors and it includes encapsulation and connecting information.

Video signal booster

Video enthusiast, *David Thomas* writes from Swansea with an interesting request:

"I have made a number of modifications to a 14in. portable colour TV receiver, including external composite and RGB video inputs. This seems to work well on a variety of signal sources but one snag is that there appears to be insufficient gain in the video amplifier stages as I need to keep the contrast control fully advanced. Can you suggest how I can add some extra gain to the circuit? (PS: I have tried a single-stage common-emitter amplifier but this simply inverts the signal!)"

From the information which you supply David, I have ascertained that the d.c. level at the base of the video output stage is at about 7.2V. This is important since it will be necessary to preserve this d.c. level in our added circuitry (the stage must be d.c. coupled as it has to cope with a video signal). The circuit of the variable gain video booster is shown in Fig. 2.

In order to produce an overall phase shift of 360 degrees, I have used a direct coupled two-stage amplifier in which both transistors operate in common emitter mode. The first transistor is an npn device whilst the second is pnp.

The first stage operates with a collector current of nominally 2mA whilst the second operates at 4mA. The values of collector and emitter resistors can be calculated quite easily and the nearest preferred values used in the circuit. The BC184 and

BC212 transistors are readily available, the former having a minimum h_{FE} of 240 (at $I_C = 2mA$) whilst the latter provides a minimum h_{FE} of 50 (at $I_C = 4mA$). As is conventional, the higher gain device is used in the first stage.

It is important to note that I have incorporated a large amount of negative feedback in both stages in order to increase the bandwidth and reduce the stage gain to a manageable amount. The gain of the first stage is adjustable from about 1 to 50 whilst the second has a gain of about 5.5.

Timer software revisited

In August's *Surgery* we described a computer program for designing 555 timer circuits. Several of you have asked for a GWBASIC version so here it is:

```

100 '
110 '555 timer circuit designer
120 '
130 'Initialise
140 '
150 KEY OFF
160 ON ERROR GOTO 1060
170 SCREEN 0
180 COLOR 1, 2, 3
190 ULS + STRING$(31, CHR$(205))
200 '
210 WHILE 1
220 '
230 'Display main menu
240 '
250 :
260 CLS
270 PRINT ULS
280 PRINT "555 TIMER I.C. CIRCUIT
DESIGNER"
290 PRINT ULS; ""
300 PRINT " Select timer configuration..."
310 PRINT "[M] = monostable"
320 PRINT "[A] = astable"
330 PRINT "[Q] = quit"
340 RS = ""
350 WHILE INSTR(" MAQmaq", RS) < 2
360 RS = INKEY$
370 WEND
380 IF RS = "Q" OR RS = "q" THEN LS:
END

```

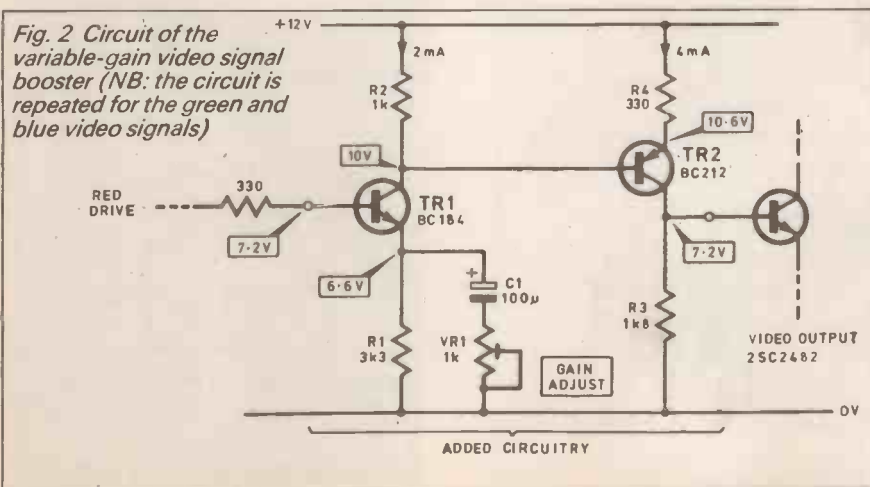


Fig. 2 Circuit of the variable-gain video signal booster (NB: the circuit is repeated for the green and blue video signals)

```

390 '
400 PRINT ULS
410 IF RS = "M" OR RS = "m" THEN
GOSUB 450
420 IF RS = "A" OR RS = "a" THEN
GOSUB 690
430 WEND
440 '
450 :
460 PRINT " Monostable timer
configuration..."
470 INPUT " Timing period (in ms)"; T
480 'Recommend a value for c
490 CREC = T / 100
500 CREC = INT(1000 * CREC) / 1000
510 PRINT ULS
520 PRINT " Recommended value for the"
530 PRINT " timing capacitor is";
540 PRINT USING "###.###"; CREC;
550 PRINT " uF"
560 PRINT ULS
570 R = 0
580 WHILE R > 1 * 10 ^ 3 OR R < 1
590 INPUT " Capacitor value (uF)"; C
600 R = T / (1.1 * C)
610 PRINT ULS
620 PRINT " Timing resistor = ";
630 PRINT USING "#####.#"; R;
640 PRINT " kohm"
650 WEND
660 GOSUB 970
670 RETURN
680 '
690 :
700 PRINT " Astable timer
configuration..."
710 INPUT " Capacitor value (uF)"; C
720 PRINT ULS
730 PRINT " NB: High time must be
greater"
740 PRINT " than low time..."
750 PRINT ULS
760 T1 = 0
770 T2 = 1
780 WHILE T1 < 1.05 * T2
790 INPUT " High output time (ms)"; T1
800 INPUT " Low output time (ms)"; T2
810 WEND
820 R2 = T2 / (.693 * C)
830 R1 = T1 / (.693 * C) - R2
840 F = 1.44 / ((R1 + (2 * R2)) * C)
850 PRINT " R1 = ";
860 PRINT USING "#####.#"; R1;
870 PRINT " kohm"
880 PRINT " R2 = ";
890 PRINT USING "#####.#"; R2;
900 PRINT " kohm"
910 PRINT " P.r.f. = ";
920 PRINT USING "###.###"; F;
930 PRINT " kHz"
940 GOSUB 970
950 RETURN
960 '
970 :
980 PRINT ULS
990 PRINT " Press any key to continue..."
1000 RS = ""
1010 WHILE RS = ""
1020 RS = INKEY$
1030 WEND
1040 RETURN
1050 '
1060 :
1070 PRINT ULS
1080 PRINT " An error has occurred!"
1090 GOSUB 970
1100 RESUME 250

```

Next month: Next month's *Surgery* will be dedicated to the "audio enthusiast"; we shall be describing some simple analogue circuitry for compressing audio signals. We also provide details of a 30V power supply for use with a valve preamplifier.

In the meantime, if you have any comments or suggestions for inclusion in *Circuit Surgery*, please drop me a line at: Faculty of Technology, Brooklands College, Heath Road, Weybridge, Surrey, KT13 8TT. Please note that I cannot undertake to reply to individual queries from readers however I will do my best to answer all questions from readers through the medium of this column.

ALTERNATIVE ENERGY



T. R. de VAUX BALBIRNIE **PART 3**

If you ever go across the sea to Denmark ...

IN the previous parts of this series we have looked at the need to seek alternative energy supplies. In the next two parts we shall examine several of these. However, this month will be devoted to *wind power* because this method shows great promise and has reached the stage of large-scale commercial development. Some countries, such as Denmark, already generate a significant fraction of their total electricity requirement using wind power.

North-West Denmark, parts of the U.K. (especially in Scotland) and the west coast of Ireland share some of the most favourable climate in Europe for wind energy abstraction. Fig. 1 shows a Wind Map of Europe with the darker areas indicating the best places for large-scale exploitation.

GROWING UP

If anyone thinks that wind energy technology resembles an episode of *Last of the Sum-*

mer Wine or is best suited to eccentric boffins with equipment collapsing all around, they had better think again. Over the past 15 years, wind power has grown up. It has become serious, technologically advanced – and is here to stay. There are now about 30 wind turbine manufacturers operating – mostly in the European Community.

The purpose of a wind turbine is to extract as much movement energy (kinetic energy) as possible from the wind and turn it into kinetic energy in the blades. The slowly-moving blades are attached to a *rotor* which will then have its shaft speed increased using a gearbox and hence operate a generator to produce electricity. All the mechanical parts will be situated at the top of a tall tower in a housing called the *nacelle*.

A large modern wind turbine will have *variable pitch* blades – that is, the angle which the blades make along the longitudinal axis may be varied (compare with

feathering of an oar in rowing). This angle should be capable of being varied during operation to present the greatest area to the wind at low wind speeds and to gradually reduce it as the wind speed increases.


It is usually necessary to provide a means of steering the blades to face the wind – i.e. controlling the *yaw* – since the wind direction varies from day to day. This involves turning the nacelle on a *yaw ring*. A practical wind turbine must also be capable of being stopped in a reasonably short time for maintenance work to be carried out and also more rapidly in an emergency.

MICROPROCESSOR CONTROL

Although the wind provides a free source of power, it is also a very variable resource. It turns out that although the basic principle of the wind turbine is simple, its design is

Fig. 1. The European wind atlas

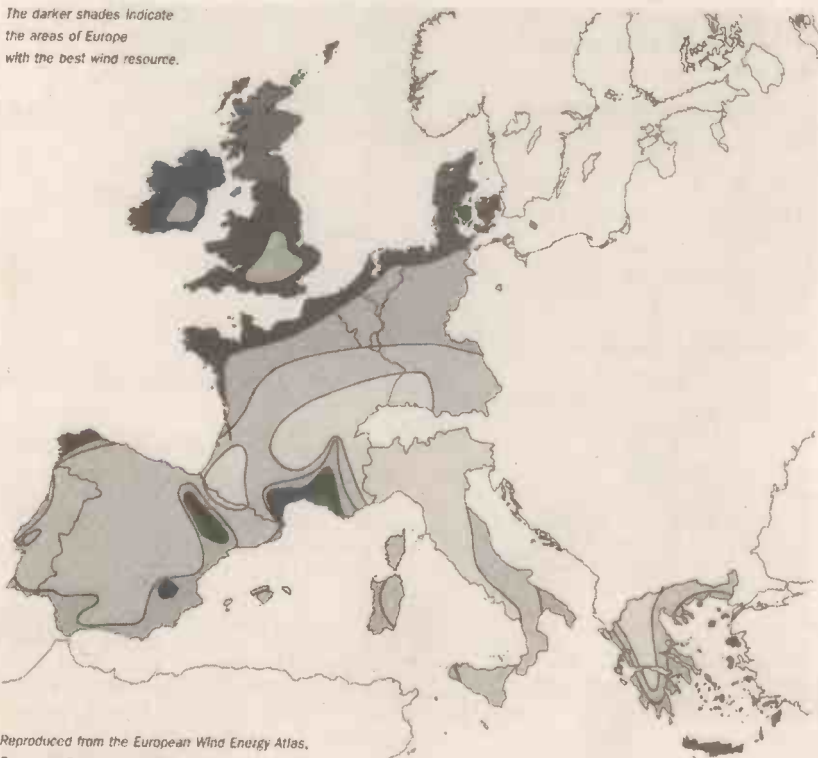The darker shades indicate the areas of Europe with the best wind resource.



Reproduced from the European Wind Energy Atlas, Troen and Pedersen, 1989. The atlas was prepared before the unification of Germany





The Vestas factory showing the test turbine and, in the foreground, turbine blades ready for transporting.

fairly complex. In practice, the control systems for yaw and pitch mentioned above are placed under microprocessor control.

Traditionally, the Danes, Dutch and Germans have relied in the past on the wind as a source of power more than the British. It is then hardly surprising that they have been quick to exploit the new market in modern wind turbines.

Denmark leads the way in wind technology and is practising what she preaches by making a commitment to generate 10 per cent of her electricity requirement this way by the end of the century. In fact, she is already well on the way to achieving this. A referendum of the Danish people indicated a wish to steer clear of atomic energy so this country remains free of nuclear power stations.

Denmark began a major wind turbine installation programme some 15 years ago and since then has accelerated her wind power contribution to meet the 10 per cent target. With the total average Danish demand standing at some 18,000MW, 1800MW is needed from wind turbines or the equivalent output of one very large conventional power station.

A trip to Denmark seemed a good idea to see at first hand what we can learn from a well-organised programme of research and development coupled with a serious view of alternative energy methods in general. We chose the Vestas factory as our chief point of call together with a visit to a large collection of turbines on a wind farm.

OFF TO DENMARK

At the Vestas factory, wind turbines are developed, manufactured, marketed and serviced for the home market and for export to all parts of the world. Vestas is a wholly Danish-owned company employing about 500 people with the present structure having come about through the amalgamation of Vestas Wind Systems and Danish Wind Technology at Viborg. Vestas have had many years of experience in the manufacture and maintenance of almost 4000 wind turbines installed worldwide.

The Vestas wind turbine manufacturing plant is situated on the west coast of mainland Denmark (Jutland) in the small village of Lem near Ringkøbing. The fibreglass section and mechanical construction plant are separate but close to one another.

We were welcomed and shown around by Tom Pederson. His enthusiasm for wind technology in particular and alternative energy in general showed in all he said. He explained that the company in Lem had been well established in the engineering field for many years, manufacturing a variety of

machines such as pumps. With the need for wind turbine development and manufacturing work, it was simply coincidence that the geographical situation of the area was ideal for testing purposes.

MANUFACTURING

Vestas make as much as they can themselves, Tom Pedersen told us. However, some of the specialized components such as the generators and gearboxes are bought-in under contract from various suppliers – Vestas have no wish to enter this type of specialized manufacturing field. The blades are the subject of continuous research carried out by Vestas themselves.

The blades are manufactured in the glass fibre section where over the years more than 7000 have been produced. Blades are currently made from glass-fibre re-inforced with epoxy resin and polyester.

Vestas products are under constant development. Currently they manufacture a range of four wind turbines all having the familiar three-blade form and looking similar apart from size. The latest and largest in the range is the V39-500kW model. The others are the Windane 34-400kW, the V27-225kW, shown on the previous page (developed from the previous V25-200kW unit) and the smallest in the range – the V20-100kW developed from the old V17-75kW unit. The smaller turbines still in widespread use all over the world are no longer made.

A Danish Wind farm sited close to the Vestas factory.



The rating figure is, of course, the *maximum* output and is obtained above a specified wind speed. The approximate height of the tower for the largest model is 40m, 30m for the 400kW and 225kW models and 23m for the “baby” of the range. The diameters swept by the blades vary from 39m to 20m.

Tom Pedersen told us that improved efficiency combined with economic forces dictate gradual but ever-increasing power outputs. In this way, the customer is provided with the cheapest generation of one kilowatt-hour. This is at present achieved with the 500kW model. As our host told us – “As we get better, it may be that the norm approaches 1MW.”

SALES


We walked outside to see rows of completed wind turbines (without the blades since these are fitted when the unit is on site) and also some erected ones used for testing purposes. “That one over there is the 500kW turbine – it looks the same as the 225kW one, doesn’t it? Go up to it, though, and you will see that it is a lot bigger”.

The plant keeps up a continuous output of completed wind turbines whether sold or not. In this way, Vestas can cope with sudden demand as sometimes happens when one customer recommends another and so sets off a chain reaction. Although the company’s products are sold all over the world, a large proportion are exported to the USA – as of 1st December, 1991 a total of 2607 units were installed there, chiefly on various wind farms in California.

The largest group of similar units is the set of 98 V27-225kW turbines at Tehachapi with a total generating capacity of over 22MW. Most turbines are supplied on an enclosed tubular tower with internal access ladder. This form of construction provides a very elegant appearance. The towers are painted white to blend in with the sky-line. Galvanized lattice towers may be supplied as an alternative but, although cheaper, do not look so good.

COMPUTER CONTROL

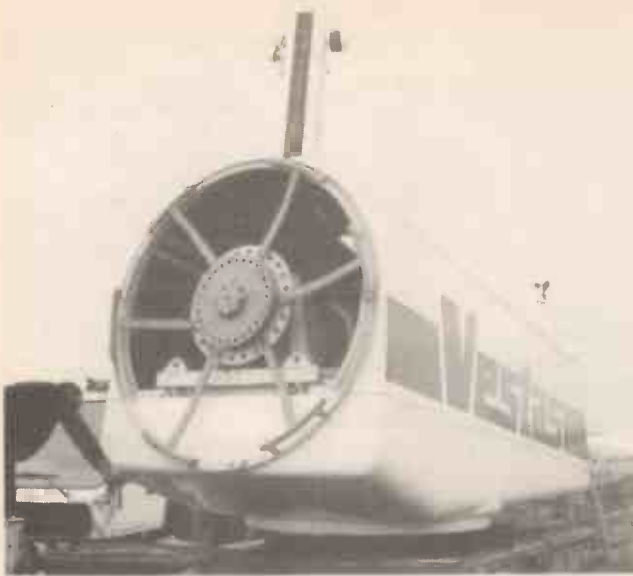Since the aim is to extract as much energy as possible from the wind, certain measurements need to be made continuously and some form of control/monitoring applied.



The nacelle which houses the generator.



A generator for the V27-225kW turbine.

Wind direction is monitored using a wind vane and wind speed using an anemometer both mounted on the top of the unit at operational height. These devices contain optoelectronic transducers which feed information to the microprocessor-based control unit at the base of the tower.

Information from the wind vane instructs the nacelle carrying the rotor to turn (yaw) to face the wind while information from the anemometer shuts down the turbine if the wind speed becomes too low or too high. At all times, the microprocessor regulates the pitch of the blades on the three larger models. Thus, at low wind speeds the area presented to the wind is high and gradually reduces as the wind speed increases. The power output is then substantially constant between certain limits.

The smallest of the range – the V20-100kW – does not have variable pitch – it is said to be *stall regulated*. We asked about the software. "We write it ourselves – this means that we can fine-tune it as we make minor changes to the design."

NATIONAL GRID

In practice, when on-site the wind turbines will be connected to a National Grid system. In this way, electricity may be sold at a premium rate (as non-fossil fuel energy) and electricity bought from the grid when the wind is insufficient.

A common misconception is to think that the speed of rotation of the rotor depends on the wind speed as in a traditional windmill. This cannot be so since the speed of rotation must synchronize with the existing supply on the grid and therefore turn at a specific speed. In Europe, the grid supply provides 50Hz a.c. (that is, 50 complete waves per second). The a.c. generator in the wind turbine must therefore do likewise.

Providing there is sufficient wind, the speed of the rotor will increase until synchronization is reached whereupon the unit "locks" and an electronic control unit switches the output through to the grid. The rotor will then continue to run at synchronization speed (in the case of the 500kW turbine this is 30r.p.m.) as it "pushes" energy into the system.

As the wind speed increases, the rotor continues to turn at the same speed but the force on the rotor eventually reaches the point where damage could be caused. At a certain

wind speed, therefore, the control system disconnects the output and the blades are fully feathered so that minimum blade area faces the wind. No power is then delivered and the blades come to rest.

If the wind speed becomes too low to allow synchronization, the output is once again disconnected. In the USA the mains frequency is 60Hz and modifications for this market are needed to take account of the higher frequency. Fig. 2 shows the output of a 500kW turbine as a function of wind velocity. It will be seen that full rated power

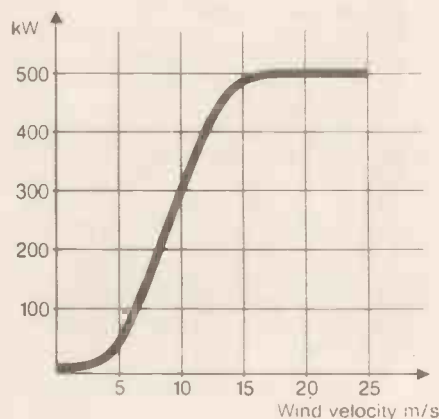


Fig. 2. Power output curve for the 500kW turbine.

is obtained at speeds above 16m/s – 36 m.p.h. (Force 7) with automatic shut-down at 25m/s – 56 m.p.h. (Force 10).

CONTROL SYSTEM

We went through the door into the tower of the V27-225kW test unit to see the control system in operation. A display on the panel gives information concerning output power and other operating parameters such as temperatures at various parts of the turbine. Remote monitoring of these functions is possible over a telephone line if required.

There is also a meter which looks very much like a household electricity consumption meter but here it is used for the reverse process – to provide data on the amount of energy supplied to the grid and hence the payment to be made to the operator for the electricity generated.

As mentioned previously, a wind turbine needs brakes. For normal stopping of the machine for maintenance, full feathering of the blades is sufficient. This brings the turbine to rest in a gentle and controlled way which causes least strain on the mechanical components. In an emergency, there is a more violent means of arresting it using hydraulic brakes combined with full feathering of the blades.

Braking is applied to the high-speed gearbox shaft and uses disc brake calipers fitted with non-asbestos linings. Although applying these brakes stops the turbine very quickly, this method was not demonstrated to us since it puts a great deal of strain on the mechanical parts – rather similar to the brakes on a car being applied as hard as possible.

If overspeed of the rotor should be combined with a fault in the controller, an independent monitor will activate the emergency stopping procedure automatically.

Inside the plant again, we walked past a large concrete-lined hole in the floor. "Not a swimming pool for the staff", Tom Pederson told us. "It's being prepared for tests on the 500kW turbine – this has some very heavy components and present facilities are inadequate". This reference to a swimming pool led me on to talk about staff relations. "Everyone works together like one happy family, really" was the reply.

WIND FARM

Leaving the factory and following directions given by our host, we drove the short distance to the wind farm. Here, in one ambitious project, 100 units of various types and power outputs operate side by side and row by row: 35 units of 75kW, 34 units of 90kW, 2 units of 200kW and 29 units of 225kW combine to provide a total rated output of 12.6MW.

Some of these units now appear small by today's standards – if they were all 500kW units, the output power would be 50MW. Listening carefully – there was no traffic or other noise – we confirmed that the noise of the turbines on a wind farm is negligible – some rushing sound and a very little mechanical noise. We also noted that most of the land is still capable of being farmed in the traditional way.

The wind farm is unmanned apart from times when a fault develops or when servicing is required. Wind turbines like other

mechanical devices need to be serviced and this involves a short period of non-production once a year.

EUROPEAN INSTALLATIONS

By December, 1991 Vestas had installed 1001 wind turbines on her own soil, 721 of these standing alone with the rest grouped together in wind farms. The smallest installed turbine has a capacity of 55kW and the largest one 400kW. The following table shows the number and type of Vestas wind turbines installed in various other European countries together with the nominal total capacity (in MW).

TABLE 1

Country	No of turbines	Capacity (MW)
Germany	74	13.63
Sweden	28	5.22
Norway	8	2.53
U.K.	8	1.33
Spain	8	1.06
Turkey	1	0.55
Italy	1	0.40
Greece	4	0.24
France	1	0.20

We left Denmark very impressed. By the way, if any readers wish to take a motoring holiday in Denmark they will be pleasantly surprised by the uniformly excellent road system, the lack of traffic in rural areas and the courtesy and good command of the English language by the Danes. Low national speed limits and well-disciplined driving makes motoring a pleasure.

You will not have to drive far before seeing a wind turbine. One point – there is a rule whereby all cars must use dipped headlights even during the day. British drivers tend to forget.

VESTAS AT HOME

Vestas supplied the turbines – ten WD 34-400kW units – for the UK's own Delabole Wind Farm in Cornwall. This is situated two miles from the North Cornwall coast approximately 240m (787ft) above sea level and this turns out to be an ideal location for wind energy exploitation. The wind farm covers some 140 acres with units placed 250m apart – a total installed output of 4MW.

A £26M hospital – the Wansbeck General Hospital – is under construction in Ashington, Northumberland. This is designed to open in 1993 with a view to serving a population of 190,000. The innovative design shows clearly what savings can be made and could be a model for similar schemes in the 21st century. The idea is to cut the projected energy costs by £135,000 – that is, by 60 per cent.

The hospital is sited in an area of high wind and a Vesta wind turbine has been chosen to generate a substantial amount of the total electricity requirement – around 20 per cent. The use of a wind turbine in this situation is thought to be a world "first". A computer will monitor energy demand of the complex and call on various types of generator – oil, gas, wind – or the national Grid to provide the most economic energy at any given time.

Use of high-efficiency insulation and double-glazing maximize energy savings as does the use of natural light wherever possible. Plans for an on-site incinerator/generating plant are also in hand – more about this type of scheme will be discussed in Part 5 of this series (December, 1992 issue).

WIND SHELTER

The Wood Green Animal Shelter in Cambridgeshire has also taken innovative measures to save energy and to protect the environment. This organisation is a charity which relies on the generosity of supporters so the more cash saved in terms of energy bills, the more work it is able to do. Preliminary studies into the feasibility of using wind energy were begun in 1988.

Since the site is not ideally placed, there was some scepticism at the time as to whether sufficient wind was available for the successful operation of a wind turbine. The Shelter planned their research well, calling on the help of the Cavendish Laboratory in nearby Cambridge and local air force stations to provide data concerning wind speed and direction for the previous ten years.

The University of East Anglia Climatic Research Unit was also called in to collate the information and run a computer program aimed at predicting the likely wind strength and direction over the next ten years. All this amassed data confirmed that the scheme was not only possible but made economic sense too. The wind turbine chosen was a Vestas V27-225kW unit.

The Wood Green shelter needs electricity to run a restaurant, an education department for the College of Animal Welfare and various veterinary facilities as well as the power needed for the welfare of the animals placed in its care. A non-fossil fuel contract was set-up and signed in 1990 whereby the Shelter agreed to sell total production from the wind turbine to the electricity company until 1998.

The electricity needed for the shelter is then purchased from the grid in the usual way. This has the advantage that the electricity generated sells at a special premium rate – some 50 per cent more than it is purchased for. Also, a suitable supply is always available irrespective of the amount of wind from day to day or hour to hour. It turns out that, in cash terms, the payback period of the turbine will be approximately three years with present rates of interest.

Apart from one very early malfunction, the turbine has continued to operate up to expectations. It has even become a landmark and a local tourist attraction.

U.K. CONTRIBUTION

All the foregoing may suggest that we in Britain are sitting twiddling our thumbs. However, this is not the case for here there is a great deal of important development and manufacturing work going on. As well as the popular type of medium-power turbine, we have specialist companies producing both the very large and small power devices. Britain also makes a contribution in the field of vertical axis wind turbine technology of which more will be said presently.

Marlec Engineering in Northampton manufacture the Rutland Windcharger range of small wind turbines. These have been in production for over ten years now and are exported worldwide. Marlec Engineering were, in fact, awarded the Queen's Award for Export Achievement in 1989.

A WEG MS-3 wind turbine sited at Carmarthen Bay.



WINDCHARGERS

The Windchargers are not intended to be used as stand-alone generators but are designed specifically to maintain the charge in 12V or 24V (there are two separate versions) lead-acid ("leisure-type") batteries which may then be used to supply power for lights, television, water pumps, refrigerator, etc. They are thus ideal for use in remote buildings, holiday homes, caravans, boats etc.

The design of the actual generator is innovative with much use being made of glass reinforced polyester resin. In the smaller - 910 series - the blades trace a circle approximately 90cm (3ft) in diameter and are made from thermosplastic.

A useful feature is the low wind speed needed for cut-in (i.e. for charging to commence) - only 4 m.p.h. (1.8 m/s) corresponding to Force 2. The full rated output of 50W is available at 10 m/s (Force 5). In a good situation it can be seen that a 60Ah leisure-type battery could be fully charged from scratch in 15 hours approximately.

The manufacturers therefore provide control gear to prevent damage to the battery in the event of long periods of high wind. There are special-purpose versions of the 910 series with the same specification but with particular applications in mind - one is specially designed for marine use, for example.

The Furlmatic 1800 is the big brother of the 910 with a rated output of 250W. The blades on this sweep a diameter of 180cm (6ft) approximately. Charging with this model begins with a wind speed of 5 m.p.h. (2.3m/s corresponding to Force 2 approximately) with full output achieved at 22 m.p.h. (10 m/s or Force 5).

It is interesting to note that the same company supply solar cell panels with a rated power output of between 5 and 60W in bright sunshine depending on size. An interesting idea is to use a *hybrid* charging system - that is, battery charging being provided part by wind generator, part by solar panel. This will provide more balanced charging throughout the year compared with one method used alone. Thus, in the winter there is likely to be less sun but more wind and in the summer the reverse.

POWERFUL STUFF

At the high-output end of the market, the Wind Energy Group, Ltd (WEG) produce the MS-3, 33m diameter wind turbine. The Wind Energy Group is a joint company formed between British Aerospace, p.l.c. and Taylor Woodrow Construction, Ltd. This company has been the Department of Energy's main contractor in the field of wind energy since the late 70's. Research and development work has included site selection, wind measurement, grid connection studies, windfarm development and performance monitoring.

WEG, Ltd. has some 40 professional engineers working on the wind energy programme with the capability of drawing on the huge resources of the parent companies. The MS-3 is a 2-blade design, the blades themselves being made of wood epoxy composite. Full pitching and yaw adjustment are featured using electromechanical control and all placed under microprocessor management.

Emergency braking is provided by disc brakes applied to the gearbox high speed output shaft. The tower is of galvanized steel, 25m high. The full rated power of the MS-3 - 300kW - is obtained with a wind speed of 11.5m/s (25.5 m.p.h. or Force 6). This output is then maintained up to 25m/s

(56 m.p.h.) when the automatic cut-off system operates.

Remote control or monitoring of functions may be carried out using a modem link with a telephone line if required. The MS-3 may be seen operating in Wales, Scotland, Northern Ireland, Italy and in California where a single well-sited turbine can generate the electrical requirements of 300 homes. This corresponds to an annual output of more than 1MWh at a mean wind speed of 7.5m/s and at a cost of 5p per kWh.

The MS-3 is an ideal turbine for grouping with others in wind farms and will be used extensively for this purpose in 1992. In 1984, WEG supplied a 5MW wind farm in the California desert with 20 250kW 3-bladed 25m turbines. This was through a joint venture between WEG and US Windpower Inc. the largest windfarming company in the world.

A 20m diameter 250kW WEG wind turbine was erected on Orkney and this has been producing power since July, 1983. Later, the mighty 60 metre LS-1 (Large-Size 1) was constructed by the Department of Energy and the North of Scotland Hydroelectric Board - a joint venture by Taylor Woodrow, British Aerospace and GEC. This was inaugurated in November, 1987 and with a rated output of 3MW is sufficient to supply the total electricity needs of 2000 homes. The LS-1 (shown in Part 2) is the most powerful wind turbine ever constructed in the UK and is still one of the largest in the world.

VERTICAL AXIS TURBINES

Renewable Energy Systems, Ltd in Hemel Hempstead take a different approach to wind turbine technology. Here, the sails

rotate *horizontally* - that is, turning on a vertical axis (see photograph) Vertical axis turbines have the advantage of being able to use the wind from whatever direction it blows without having to rotate the whole mechanism.

The design of the blades takes the form of an aerofoil which synchronizes with the 50Hz grid at 33 r.p.m. The prototype VAWT 260 was designed and constructed with financial assistance from the Department of Trade and Industry and the European Community. This demonstration unit was erected on St. Mary's, Isles of Scilly in 1988 where it was connected to the island's diesel-fired electricity network operated by the South Western Electricity Board.

The VAWT 260 has a rated output of 100kW with a 10.5m rotor diameter and blades measuring 13.3m tip to tip. Two generators are situated together with the gearbox and control circuitry at ground level. The use of two generators maximizes the output under all operational wind conditions with cut-in occurring at 5m/s. The maximum service wind speed is 23m/s.

The VAWT 260 is suitable for remote and island communities and may be grouped into windfarms.

Next month we shall continue with our study of Alternative Energy sources by taking a look at *water power* - use of the tides, waves and hydroelectric schemes. We shall also look at the use of hydrogen obtained from water to be used as a fuel to power a car.

The VAWT 260 vertical axis wind turbine. In this design the generators can be sited at ground level.




IMPORTS **EASY** PC FILES
UPGRADE DISCOUNT AVAILABLE

Finally...an exceptional PCB and Schematic CAD system for every electronics engineer!

BoardMaker 1 is a powerful software tool which provides a convenient and professional method of drawing your schematics and designing your printed circuit boards, in one remarkably easy to use package. Engineers worldwide have discovered that it provides an unparalleled price performance advantage over other PC-based systems.

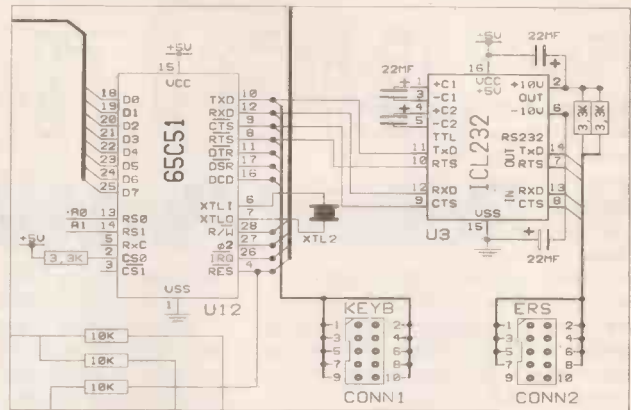BoardMaker 1 is exceptionally easy to use - its sensible user interface allows you to use the cursor keys, mouse or direct keyboard commands to start designing a PCB or schematic within about half an hour of opening the box.



Produce clear, professional schematics for inclusion in your technical documentation.

HIGHLIGHTS

Hardware:


- IBM PC, XT, AT or 100% compatible.
- MSDOS 3.x.
- 640K bytes system memory.
- HGA, CGA, MCGA, EGA or VGA display.
- Microsoft or compatible mouse recommended.

Capabilities :

- Integrated PCB and schematic editor.
- 8 tracking layers, 2 silk screen layers.
- Maximum board or schematic size - 17 x 17 inches.
- 2000 components per layout. Symbols can be moved, rotated, repeated and mirrored.
- User definable symbol and macro library facilities including a symbol library editor.
- Graphical library browse facility.
- Design rule checking (DRC)- checks the clearances between items on the board.
- Real-time DRC display - when placing tracks you can see a continuous graphical display of the design rules set.
- Placement grid - Separate visible and snap grid - 7 placement grids in the range 2 thou to 0.1 inch.
- Auto via - vias are automatically placed when you switch layers - layer pairs can be assigned by the user.
- Blocks - groups of tracks, pads, symbols and text can be block manipulated using repeat, move, rotate and mirroring commands. Connectivity can be maintained if required.
- SMD - full surface mount components and facilities are catered for, including the use of the same SMD library symbols on both sides of the board.
- Circles - Arcs and circles up to the maximum board size can be drawn. These can be used to generate rounded track corners.
- Ground plane support - areas of copper can be filled to provide a ground plane or large copper area. This will automatically flow around any existing tracks and pads respecting design rules.

Output drivers :

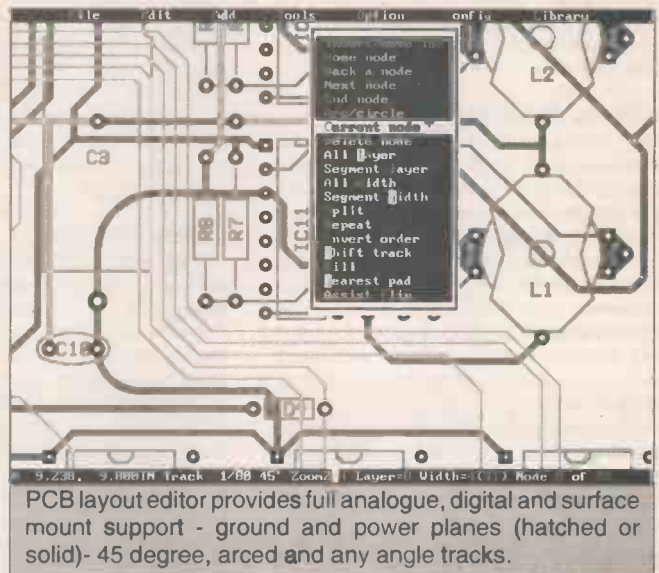- Dot matrix printer
- Compensated HP laser printer
- PostScript output.
- Penplotter driver (HPGL or DMPL).
- Photoplot (Gerber) output.
- NC (ASCII Excellon) drill output.



PCB layout editor provides full analogue, digital and surface mount support - ground and power planes (hatched or solid)- 45 degree, arced and any angle tracks.

£95

Despite its quality and performance, BoardMaker 1 only costs £95.00. Combine this with the 100% buy back discount if you upgrade to BoardMaker 2 or BoardRouter and your investment in Tsien products is assured. Price excludes carriage and VAT.

Don't take our word for it. Call us today for a FREE demonstration disk and judge for yourself.



tsien

Tsien (UK) Limited
Cambridge Research Laboratories
181A Huntingdon Road
Cambridge CB3 0DJ
Tel 0223 277777
Fax 0223 277747

All trade marks acknowledged

ACTUALLY DOING IT!

by Robert Penfold

READ with interest the recent correspondence in *Everyday Readout* (August and September 1992 issues) concerning what might be termed the "nuts and bolts" side of electronic project construction, and the usability of finished projects.

If you have some electronic projects published, very early in the proceedings you learn that you cannot please everyone. In fact it seems to be hard to please anyone much of the time. Whichever way you do something, there will always be constructors who have to do things differently!

DO YOUR OWN THING

I do not regard this as a bad thing, and I do not expect constructors to produce perfect clones of my designs. Part of the fun is doing things your own way, and customising designs. With modern circuits and circuit building methods it is often very difficult to make worthwhile modifications to the electronics. The mechanical side of things is a different matter though, and in the majority of cases there is plenty of scope for "doing your own thing".

The instructions for building most projects go into great detail about the electronics, but are rather sketchy about the mechanical side of things. This is a sensible approach, since there is little point in providing front panel drilling details if more than 90 per cent of constructors will use a different case and their own layout.

Precise drilling details are normally only given where it is important to get things just right, such as where a project has been miniaturised, and there is barely room for everything inside the case. With this type of project you would be well advised to follow the suggested layout as accurately as possible. Otherwise you might find that the proverbial quart does not fit into the pint pot.

PRACTICAL CONSIDERATIONS

Apart from a very few awkward projects, there is little risk in doing your own thing with the mechanical side of construction. If the layout is particularly critical for some reason, there should be a warning to this effect somewhere in the text. You have to be sensible in your approach though, and need to plan things out carefully.

Probably the most common error is to choose a case that is too small. A case may accommodate all the loose components with masses of room to spare, but might still prove to be inadequate to take everything in made-up form. A reasonable amount of space is

required between controls and sockets if the finished unit is to be usable.

Some layouts look quite plausible, but you find that when a plug is inserted into a socket it becomes virtually impossible to get at one or two of the controls. It is not just a matter of getting everything into the case. With everything installed, will you be able to wire the off-board components to the circuit board?

My usual approach to designing front panel layouts is to actually place all the control knobs on the front panel, and to then shuffle them around until I have found a layout that looks reasonably good and is usable. For something like a jack socket, use the fixing nut to reserve its front panel space, and bear in mind that in use there will be something plugged into it.

COMPROMISE

Although it would be nice to be able to put any control wherever you liked, remember that there are practical limitations, and compromise will often be necessary. The layout must avoid lots of long connecting wires and a "rats nest" of crossed-over wires inside the case. This is not just a matter of making the interior of the unit look pretty.

With messy wiring it is relatively easy to make a mistake when wiring-up the front panel components. It also makes fault finding more difficult if the project should ever need servicing. Of greater importance, with many projects long and crossed over wires could prevent the unit from working properly. With sensitive audio and radio equipment it is normally essential to have the wiring short and direct if instability is to be avoided.

Another consideration is that the component on the inside of the case can be much bigger than the control knob on the outside. Modern potentiometers are quite small, as are most other controls, but be careful to leave enough room for any large components. This mainly means switches, and rotary switches in particular.

Once you have arrived at a satisfactory layout, it is just a matter of carefully measuring the positions of all the components, and drawing-up a plan of the front panel. After double checking everything, and making sure that you have not overlooked anything that must be mounted on the front panel, you can transfer the design to the front panel and drill all the holes.

MAKING YOUR MARK

Marking the drilling positions onto aluminium panels is usually quite easy. Soft pencils and many types of fibre-

tipped pen will mark these panels quite well, but the marks can be easily polished out once the drilling has been completed. As aluminium is a very soft metal it is essential not to mark the panel with a hard grade of pencil, or anything else that could leave deep scratches. The exception is where the panel will eventually be covered with some sort of veneer. Paint will not necessarily cover scratches properly.

Some aluminium cases are supplied with a protective covering of plastic. It is best to leave this covering in place until as late in the proceedings as possible. A fibre-tipped pen having a spirit based ink will mark the plastic very well, but little else will.

With a metal panel it is essential to use a centre-punch to provide a small indentation to guide the point of the drill. Centre-punches also work quite well with soft plastics, but should not be used on hard plastics (where they could easily result in the panel badly cracking). With hard plastics it is better to use a sharp bradawl, using as little pressure as possible. Hard plastics should be drilled very carefully, again using as little pressure as possible.

CLAMPING

If the front panel can be removed from the case it can be clamped onto the workbench and is then easily worked. Fit a scrap piece of wood or particle board under the panel to protect the workbench. A couple of wooden "pads" can be used to prevent the clamps from damaging the finish of the panel.

With non-removable panels you must improvise, and do the best you can. Working on a panel under these circumstances is much easier if you have three or four arms, or can get someone to help hold things in place. With an awkward case it is even more important than normal that you do not rush things. A "bull in a china shop" approach is never the right one for project construction. Proceed steadily and very carefully.

With so many cases made from either soft metal or plastic, or a hard but brittle plastic, I prefer to use a hand drill when producing the holes. A large heavy-duty type is well suited to this type of work, or an old "brace and bit" style drill is even better (but very difficult to obtain these days). With either type of drill you can proceed gently and slowly, with good control over what is happening.

The problem with power drills is that they tend to "snatch" their way through soft materials, rather like a corkscrew going into a cork. This tends to produce rough results, and is a bit dangerous since you are not in total control of the drill. With hard plastics a power drill can easily produce a badly cracked-up panel.

If you really must use a power drill I would recommend using some sort of variable or multi-speed type, with the drill set at a low speed. This ensures that everything happens at a slow enough speed for you stay in control of the situation. It is more than a little helpful if the drill is mounted in a drill stand. Sharp drill bits are less likely to "snatch", and will give neater results.

CONTROL MOUNTING

Virtually all controls are mounted via a threaded bush and a mounting nut. The main exceptions are the rocker and slider switches. These can be difficult to get

Fig. 1 (left). Rotary potentiometers and some other rotary controls have a lug which fits into a small hole drilled in the front panel

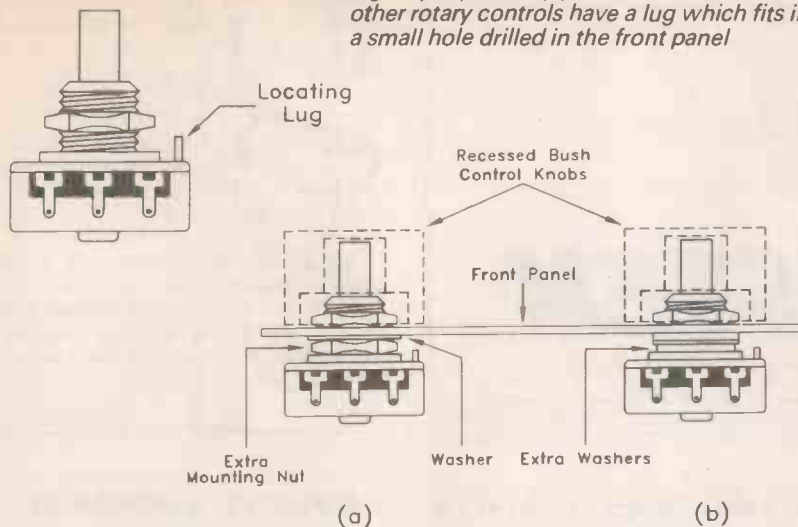


Fig. 2. In home constructor equipment the lugs on rotary controls are normally unused, as they do not reach the panel.

properly fixed in place, and are probably best avoided until you have gained a reasonable amount of experience at project building.

The normal size components require 10 millimetre diameter mounting holes. The miniature types usually require 5 or 6.35 millimetre diameter mounting holes. Component retailers' catalogues provide a lot of physical information about components, including mounting hole sizes, but you can easily measure the bush diameter using a ruler.

It is advisable to drill a small guide hole of around three millimetres in diameter first, and to then drill this out to the required final size. This helps to minimise any "wandering" of the holes.

LOCATING LUGS

If you look at some potentiometers you will find that each one has a small lug somewhere on the front (as in Fig.1). This is also present on some rotary switches and a few other types of rotary control. The general idea is to make a hole for this lug in the front panel, and it then ensures that the control does not rotate out of position if the mounting nut should become a little loose.

The home constructor normally ignores

this lug. If a control should become loose, you can soon tighten it again. Commercial electronic equipment often has all the controls mounted on the real front panel, with a dummy panel in front of this for decorative purposes. Most home constructor equipment does not have the dummy panel. If holes for the lugs were drilled in the front panel, they would probably be clearly visible, giving a very rough appearance to the finished unit.

The lug does not normally reach the front panel anyway. Some extra washers or an additional fixing nut are used over the mounting bush so that it does not protrude through the front panel any further than is really necessary (Fig.2). This enables the control knob to fit close to the panel, which gives a neat appearance.

Most of the control knobs available to amateur users have the collar that fits onto the control's spindle well recessed into the knob. These knobs can be fitted virtually flush against the front panel.

DUMMY PANEL

If you would like to take the commercial approach and fit a dummy panel, it is not difficult to do this. The panel can be made from 18, 20, or even 22 s.w.g. aluminium, since it is under no strain. The simplest ap-

proach is to drill it with holes to fit over the bushes of the controls, to fit it in place, and then fit the control knobs. This leaves the dummy panel with no proper method of fixing, and just the control knobs to keep it in place.

This may not seem to be a very good way of tackling the problem, but in practice it works better than you might think. It is a system I have seen used on several pieces of ready-made audio equipment.

If you are not happy with a "floating" dummy panel, a few blobs of Blue-Tack will fix it to the main panel and ensure that the finished unit is rattle-free. Alternatively, the panel can be bolted in place, as shown in Fig.3. This provides a very secure method of fixing, but the screw heads will slightly spoil the appearance of the panel. Another option is to use some nuts over the control bushes to fix the dummy panel firmly in place. This is the neatest solution where it is possible, but in many cases you will find that there is not enough of the bush protruding through the panel.

When using a dummy panel you must include holes in the front panel to accommodate the lugs on the controls. Alternatively, the lugs can be filed down. You must use one method or the other, or the controls will not fit perpendicular to the panel.

Clearly the dummy panel method is only applicable to certain types of case, where the presence of the extra panel will not be obvious. It is usable with many instrument cases, and will give a very neat finish indeed if the panel is covered with a brushed aluminium effect veneer.



The neat and simple front panel arrangement used on this month's Capacitance Meter.


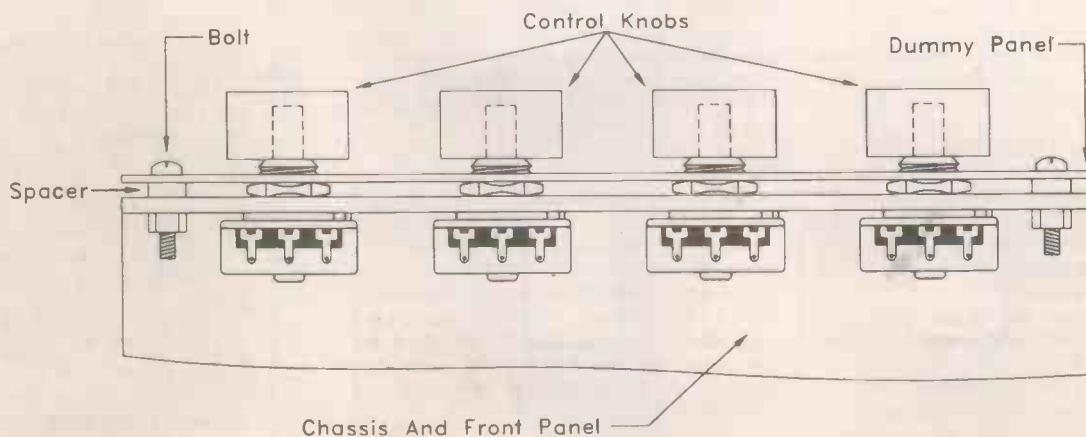


Fig. 3. Using a dummy panel. It does not have to be bolted in place, dummy panels are often left "floating".

TRAFFIC LIGHT SYSTEM

J. HEWES

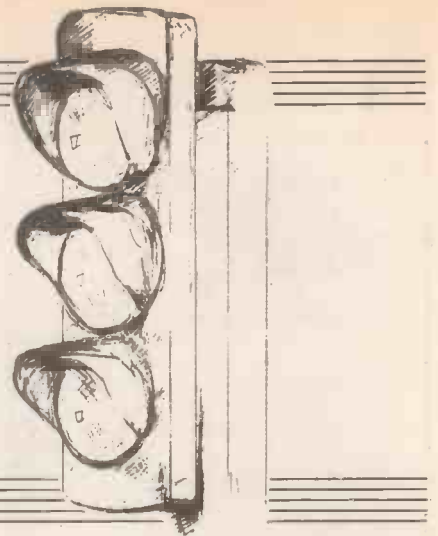

HIGHWAY CODE TRAINING • MODEL CARS • MODEL RAILWAYS • Can be used to operate up to four sets of l.e.d.s; two sets of low current (50mA to 100mA) lamps; or trigger relays to switch high current lamps - 12V 24W.

HOW IT WORKS

The control circuit diagram of Traffic Light System is shown in Fig. 1. The circuit consists of an astable clock (IC1) driving a T-type flip-flop (IC2) which has a buffer (IC3) connected to its output.

The clock and flip-flop control the traffic light sequence as shown in Fig. 2. The amber and green times can be varied independently

TRAFFIC light circuits are very popular with electronics constructors and modellers judging by the author's experience from a school electronics club. The circuit is a classic of electronics text books, but these circuits tend to be unsatisfactory for construction for a number of reasons: generating lights for just one road, equal amber and green times; 5V power supply required; no p.c.b. layout, etc.

The traffic light system described here was designed to meet the different requirements of several club members without modification to the control circuit. It can be used to operate up to four sets of l.e.d.s, or two sets of low current (50mA-100mA) lamps, or to operate relays to switch high current lamps such as 12V 24W types.

Applications can therefore range from miniature traffic lights on model railways, through small lights for model cars, to nearly full size lights to assist cyclists learning the Highway Code. The control circuit will operate from a wide range of power supply voltages, from 4.5V to 18V.

Fig. 1. Circuit diagram of Traffic Light System control circuit. The circled letters refer to locations on the "lights" interconnecting terminal block TB1.

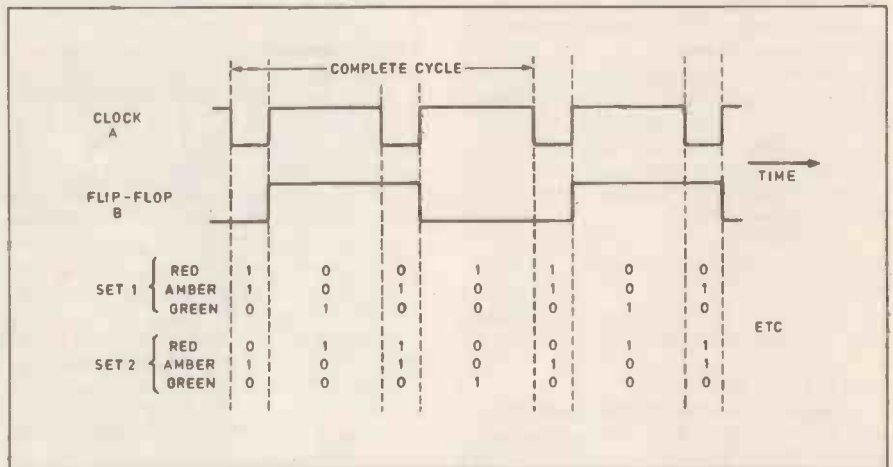
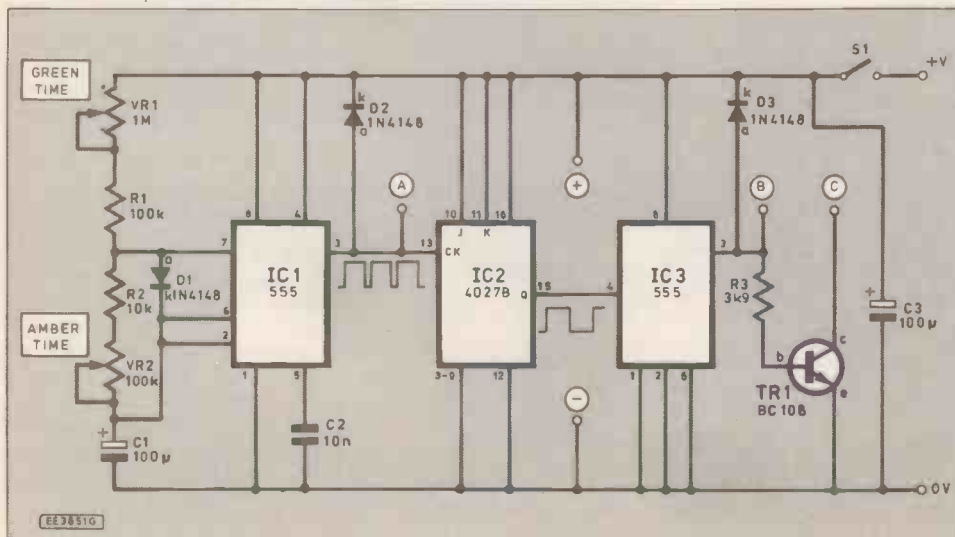


Fig. 2. Traffic light control sequence. 0 = lamp off; 1 = lamp on.

The design of a suitable traffic light post is left to the constructor since this depends greatly on the application and on the skills of the constructor.

so that an appropriate combination can be selected for the chosen application. The amber time can be varied from 0.7s to 7.7s and the green time from 7s to 77s.

The amber control adjusts the space (low) time of the clock signal from IC1 and the green control adjusts the mark (high) time. Normally the green time is much longer than the amber time so the clock signal has a large mark-to-space ratio.

The red and red-and-amber times are equal to the green and amber times respectively. The system is not quite like real traffic lights in that there is never a time when all lights are red, however the extra complexity this involves is not justified for model systems and the difference is unlikely to be noticed by most people.

Only one of the flip-flops in the 4027B dual JK flip-flop, IC2, is used in this circuit. This is connected to operate as a T-type flip-flop so that it changes state every time it receives a rising-edge clock input.

The flip-flop output from IC2 is incapable of supplying the necessary current to operate the traffic lights

COMPONENTS

CONTROL CIRCUIT

Resistors

R1 100k
R2 10k
R3 3k9

All 0.25W, 5% carbon film (or equivalent)

Potentiometers

VR1 1M rotary carbon, lin.
VR2 100k rotary carbon, lin.

Capacitors

C1, C3 100µ axial elect., 25V (2 off)
C2 10n metallised polyester

Semiconductors

D1-D3 1N4148 silicon diode (3 off)
TR1 BC108 npn transistor
IC1, IC3 NE555 timer (2 off)
IC2 4027B dual JK flip-flop

Miscellaneous

S1 Single pole on/off switch
Plastic case, size at least 100mm x 75mm x 40mm; 8-pin d.i.l. socket (2 off); 16-pin d.i.l. socket; battery clip; 9V battery (or alternative, see text); 5-way terminal block (2A); stranded connecting wire; solder etc.

The printed circuit board is available from the *EE PCB Service*, code EE806.

L.E.D. SETS

Red l.e.d. (2 off)
Yellow (or amber) l.e.d. (2 off)
Green l.e.d. (2 off)
470 ohm 0.25W resistor (6 off)
Stripboard, size 9 strips x 5 holes (2 off); 4-core signal cable, length to suit application (2 off).

These quantities are for two l.e.d. sets, all quantities should be doubled for four l.e.d. sets.

LOW CURRENT LAMP SETS

Either: Lamp and holder, e.g. m.e.s. 6V 60mA (6 off)
1N4001 silicon diode
4-core signal cable, length to suit application (2 off)
Colour filters (red, amber and green) if not in lampholders.
Or: Grain of wheat lamp, red (2 off)
Grain of wheat lamp, amber (2 off)
Grain of wheat lamp, green (2 off)
1N4001 silicon diode
4-core signal cable, length to suit application (2 off).

HIGH CURRENT LAMP SETS

Single pole 10A on/off switch
Fuse (e.g. 13A) and holder
6-way 10A terminal block
SPCO relay (e.g. 12V coil, 5A contacts)
DPCO relay (e.g. 12V coil, 5A contacts)
Lamp and holders (e.g. s.b.c. 12V 24W) (6 off)
Colour filters (red, amber and green) if not in lampholders
2-core 13A mains flex or alternative to suit application

Approx cost guidance only

£11

plus lamp sets

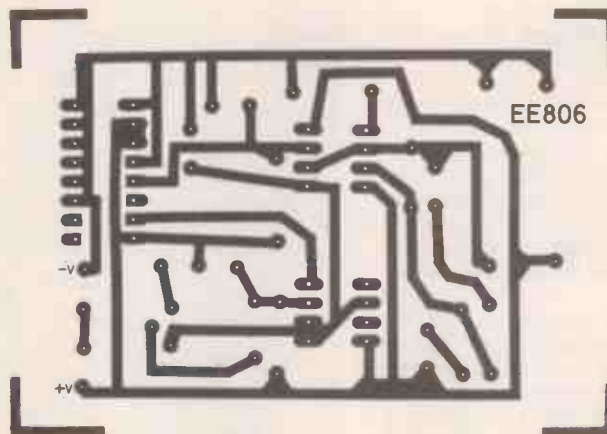
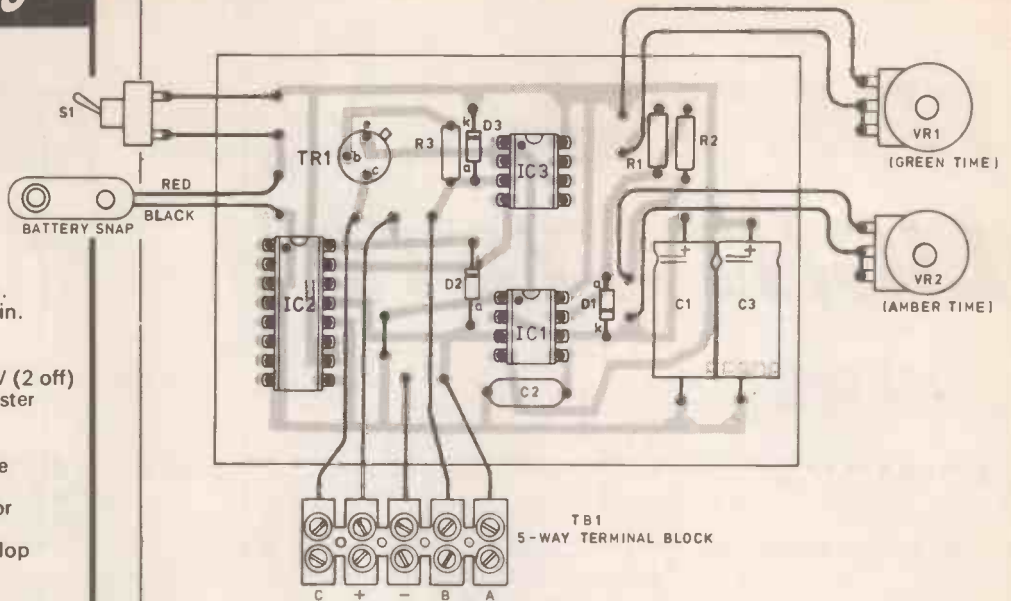


Fig. 3. Printed circuit board component layout, interwiring to board and full size copper foil master pattern.

or relays, so it is buffered by IC3 which is a 555 timer. This is an unusual use for a 555 timer, but its ability to sink or source up to 200mA is ideal for this circuit and it is simpler and cheaper than using transistors to form a suitable buffer.

Diodes D2 and D3 are connected between the outputs of the 555s (IC1, IC3) and the positive supply to protect them from the high voltage spikes generated if relay coils are connected to the control circuit. Transistor TR1 is used to provide an inverse of the flip-flop output.

The "signal" l.e.d.s, lamps or relays are connected to the control circuit by means of a 5-way terminal block TB1. The five connections to this block are as follows:

- A: Output from clock
- B: Buffered output from flip-flop
- : Negative supply
- + : Positive supply
- C: inverted output from flip-flop via transistor TR1

CONSTRUCTION

The component layout of the control circuit and a full size copper track pattern for the printed circuit board are shown in Fig. 3. This board is available from the *EE PCB Service*, code EE806.

The components may be added to the board in any convenient order, except IC1, IC2 and IC3 which should not be inserted in their sockets until all the soldering is completed. Notice that the board includes one link wire near IC2.

Take care to insert the electrolytic capacitors C1 and C3, the diodes D1-D3, and the transistor TR1 the correct way round. If you are not experienced at soldering it would be wise to use a heatsink (such as a crocodile clip) when soldering the diodes and transistor because they can be damaged by excess heat.

Label the terminal block "A B - + C" as shown to prevent confusion when connecting the l.e.d.s, lamps or relays.

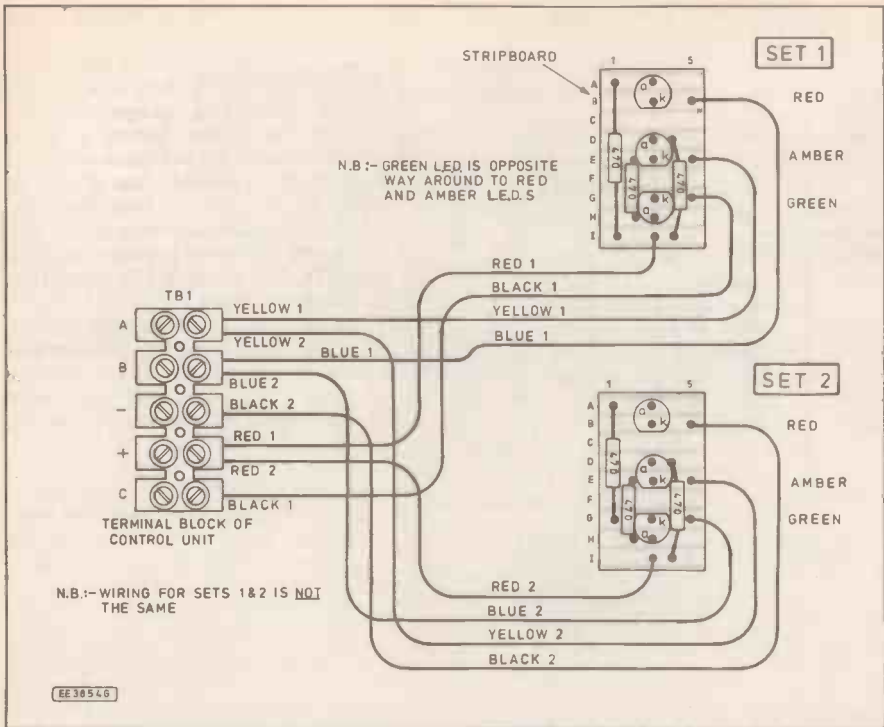


Fig. 4. Wiring between the terminal block and l.e.d. boards.

WIRING FOR L.E.D.s

The control circuit can operate up to four sets of l.e.d.s, but these instructions are for two sets because the wiring for the third and fourth sets is identical. They are simply wired in parallel to the terminal block. Each set of l.e.d.s requires three resistors which can be included on the piece of stripboard holding the l.e.d.s as shown in Fig. 5.

Note that the connections to the terminal block and the arrangement of resistors is *not* the same for each set of l.e.d.s. In each case the green l.e.d. is inserted the opposite way round to the red and yellow (amber) l.e.d.s. It is possible, but difficult, to obtain amber l.e.d.s.; however yellow should be satisfactory.

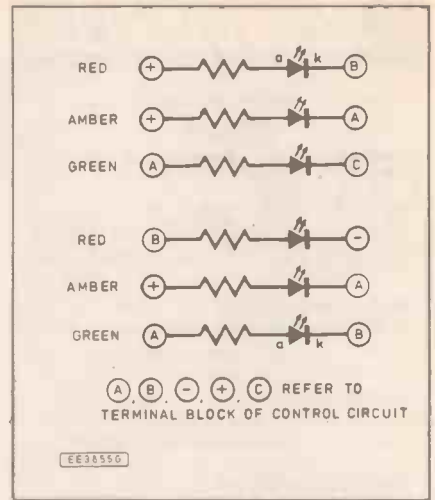


Fig. 5. Circuit connections to the l.e.d.s and limiting resistors. See text for resistor values.


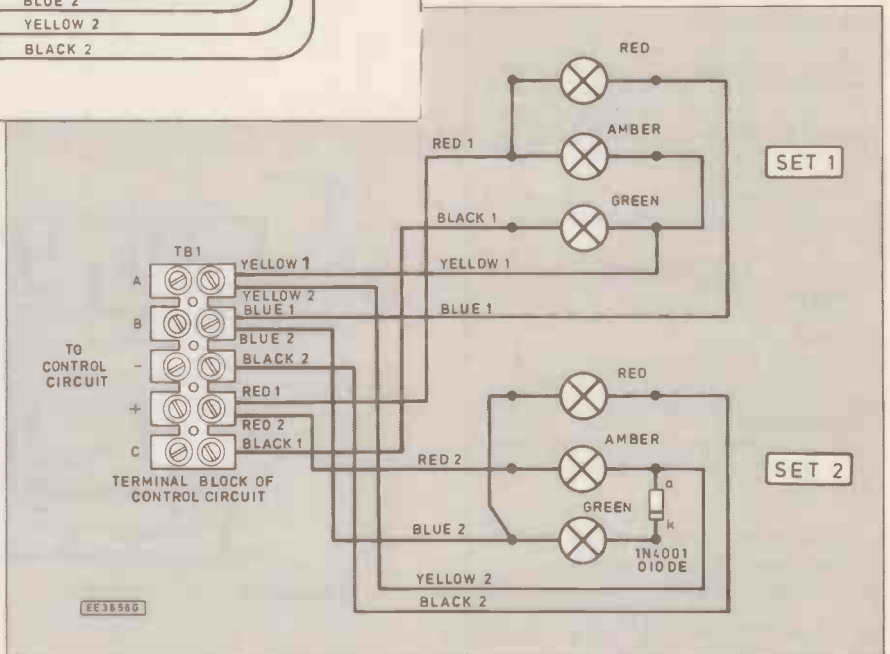


Fig. 6. Wiring details for low current lamp version.

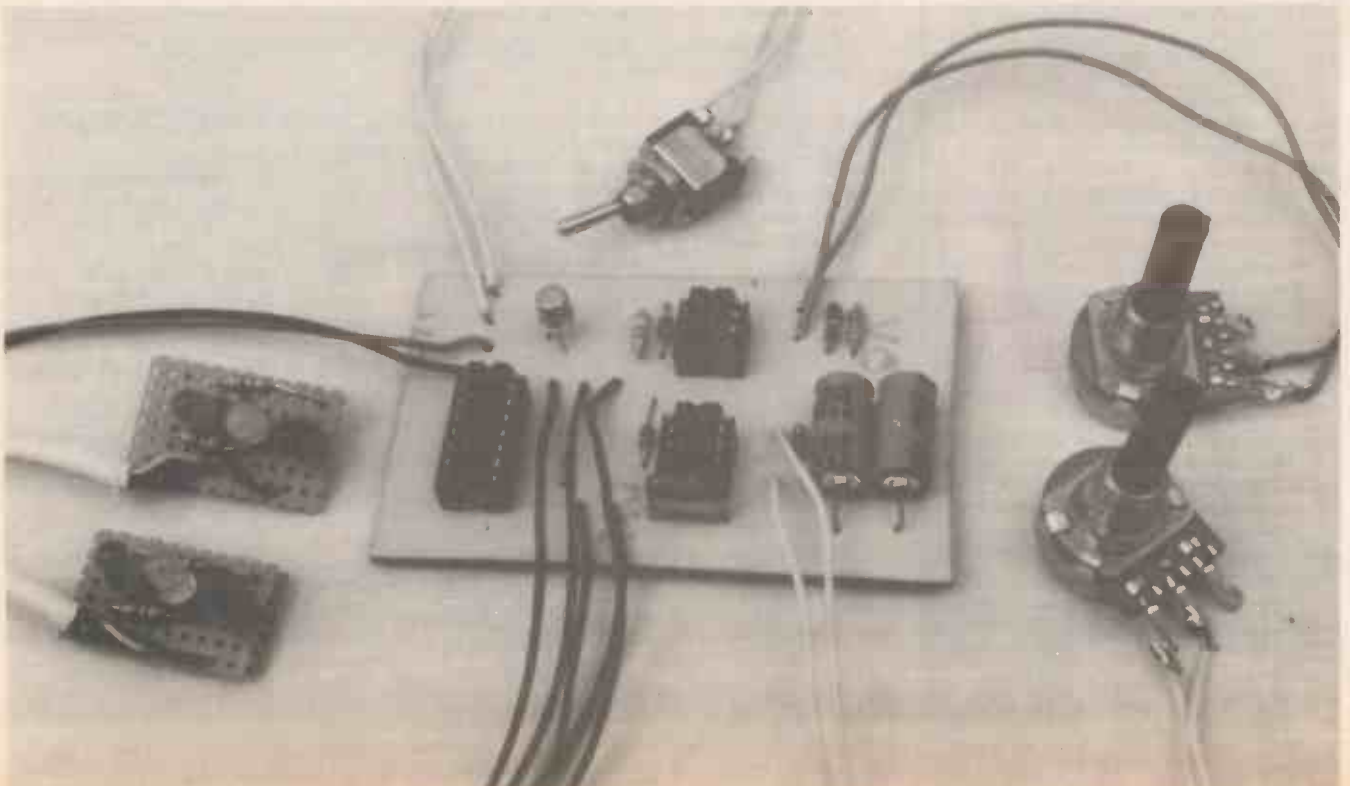

The 470 ohm resistors shown are suitable for most l.e.d.s up to 9V, but for 12V use 680 ohm and for 16V use one kilohm. Fig. 5 shows the l.e.d. and resistor connections for the benefit of constructors who wish to mount the resistors on a separate board to give a smaller traffic light.

LOW CURRENT LAMPS

The control circuit can operate up to two sets of low current (50mA-100mA) lamps which should be connected as shown in Fig. 6. One set requires a diode, and note that the connections for each set are *not* the same.

Two types of lamps are likely to be of interest: 6V 60mA m.e.s. lamps, which can be used with a supply of up to 9V; and "grain of wheat" lamps which normally operate from a 12V-16V supply and consume about 50mA. Lamps which require

HIGH CURRENT LAMPS USING RELAYS

High current lamps consuming more than 100mA can be operated by the control circuit by using suitable relays to switch the high current. How the relays should be connected to the control circuit, which already includes diodes (D2 and D3) to protect the i.c.s from the high voltages produced when the relay coils are switched off, is shown in Fig. 7.

These instructions assume the use of a 12V car battery as a power supply, but experienced constructors may like to consider other arrangements, bearing in mind that the control circuit must have a smooth supply and that it could be independent of the lamp supply if necessary. The author *does NOT* recommend the use of mains lamps, especially if the system is to

operate outside, since this introduces a quite unnecessary risk of electric shock unless proper precautions are taken.

There is no danger of electric shock from a 12V car battery, but there is a serious, and often overlooked, danger of severe burns and fire if the battery is short circuited because it can provide a current of 100A or more. A suitable fuse *MUST* be included in the positive lead from the battery, together with a switch with a *high current* rating. For many applications, such as using 12V 24W lamps, a 13A mains type fuse is a suitable choice.

It is important to connect the battery direct to the relays and lamps as shown and not to the control circuit. This is because the copper tracks on the printed circuit board cannot pass the large currents drawn by the lamps.

The battery clip and switch should be omitted from the the control circuit board unless the control circuit is to have its own battery, in which case the wire to "+" on the terminal block TB1 should be omitted.

All wiring to the lamps and battery must be capable of passing the required current, 4-core signal cable for example is not suitable because it is usually rated at 1A. The best choice is likely to be 6A mains flex and two pieces of 2-core flex must be run to each set of traffic lights. The arrangement of the connections on the relays must be checked carefully by referring to the supplier's data or catalogue.


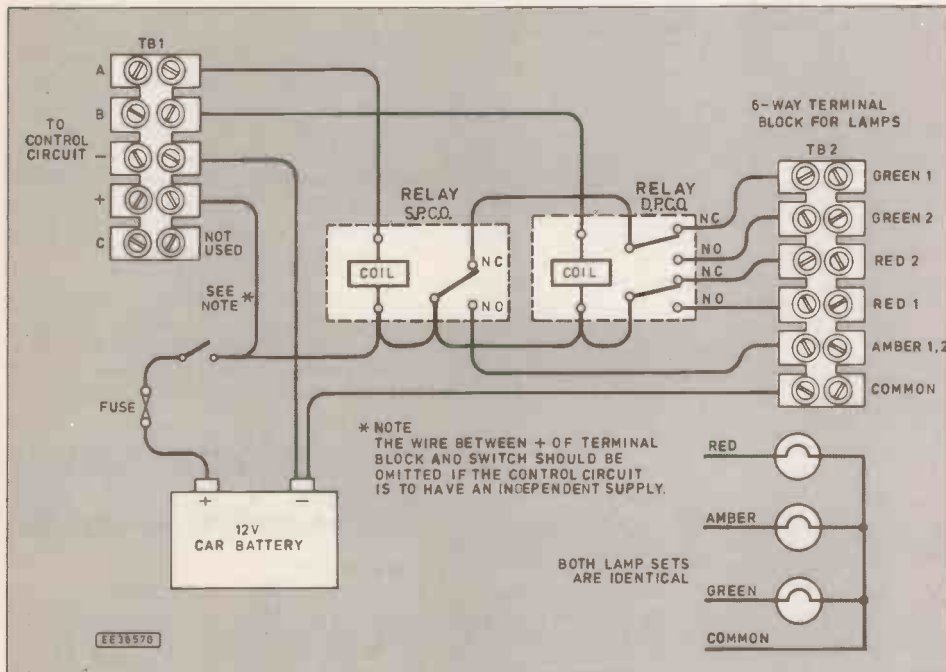
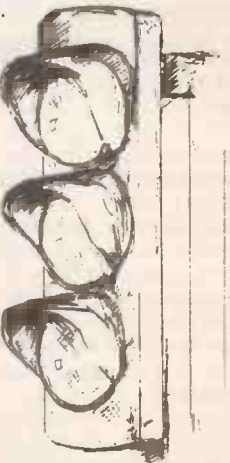


Fig. 6. Wiring details for the use of relays and high current lamps, in-line fuse *MUST* be included in the positive car battery lead. The lead from the "plus" terminal of TB1 must also be removed if the control circuit is to have an independent supply.

more than 100mA (such as standard torch bulbs) are not suitable unless they are switched on and off by relays, as described in the following section. If clear lamps are used it will be necessary to use suitable colour filters; some lampholders have these built in.

Grain of wheat lamps are excellent for miniature model lights because they are only about 3mm in diameter and have wires attached. They are normally available in red, amber and green as well as clear. Unfortunately they are not listed in most electronics catalogues, but they can be obtained from some model shops.

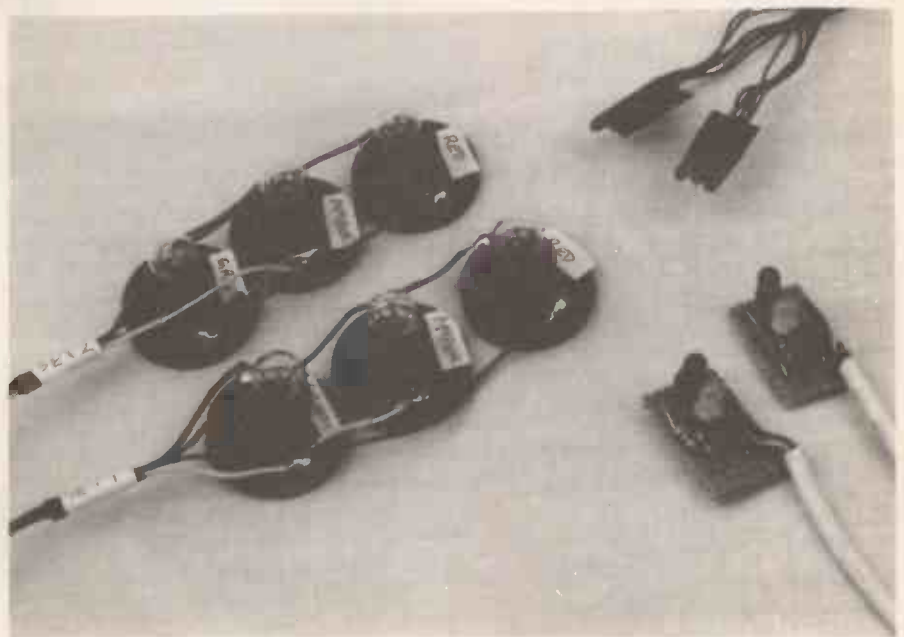The three different sets of lamps that have been used with the traffic lights system. Left to right, i.e.s. bulbs, "grain of wheat" lamps and i.e.d. boards.





WHISTLE SWITCH

STEVE HOLLAND

Whistle once, it's on; whistle again and it's off. Easy to build versatile project

THE IDEA of this project is to be able to switch electrical items on and off remotely, simply by WHISTLING. As long as you are able to whistle, of course, there should be no problem.

The circuit, is very simple as it uses a dedicated integrated circuit. With just a few external components, it can be used in many different applications.

CIRCUIT DESCRIPTION

The full circuit diagram for the Whistle Switch, excluding the mains transformer secondary winding connections at the input terminals, is shown in Fig. 1 and is based around the UM3763 whistle switch i.c.

The i.c. output is switched each time it detects a sound, via MIC1, in its frequency range. A single whistle will switch the output on, then a further whistle will switch it off and so on.

The main problem is that the i.c. only requires a 3V power supply. The unit also has to be versatile enough to be able to switch relays and bulbs of 12V or over.

The circuit board is supplied with 9V to 15V d.c. or a.c. from a mains transformer secondary winding and this power is then

rectified by diode D1. Capacitor C1 then smooths out the supply.

Resistor R1 is used to supply the voltage for the Zener diode D2, which then regulates the voltage to 3V. At point A, a voltage of 9V to 20V may be present; at point B, there should be exactly 3V present.

The voltage at point A, can be used to supply the relay or a bulb. The voltage at point B supplies the whistle switch IC1.

The "sound" sensor for this project is an electret microphone insert with a frequency response of around 50Hz to 8kHz. A small piezoelectric transducer was tested but it gave no response whatsoever and so the insert (MIC 1) was used instead, as this gives maximum performance.

The output from IC1 pin 8 triggers transistors TR1 and TR2 via resistors R4 and R5, which will in turn activate the output - i.e. a 12V relay or bulb. If a load greater than 60mA is to be drawn then a larger switching transistor must be used. For example, a BFY50 or BFY51 should be adequate for switching up to 1A.

CONSTRUCTION

The Whistle Switch is built on a small single-sided printed circuit board (p.c.b.).


The component layout and full size copper foil master pattern is shown in Fig. 2. This board is available from the EE PCB Service, code EE805.

Construction should cause very few problems. Before soldering any components check all the tracks of the p.c.b. to make sure there are no breaks or shorts.

When all is well proceed to solder the diodes into their correct positions noting as always their polarity. Do *not* forget the Zener can only go in one place. The Zener is only tiny so be careful not to damage it due to over heating whilst soldering.

Next, solder in the three capacitors, also noting the polarity of C1, and C2. Solder in the six resistors, two transistors and the 8-pin i.c. socket. Finally, insert and solder in the solderpins and/or connecting wires and the relay RLA.

Fig. 1. Circuit diagram of the Whistle Switch.

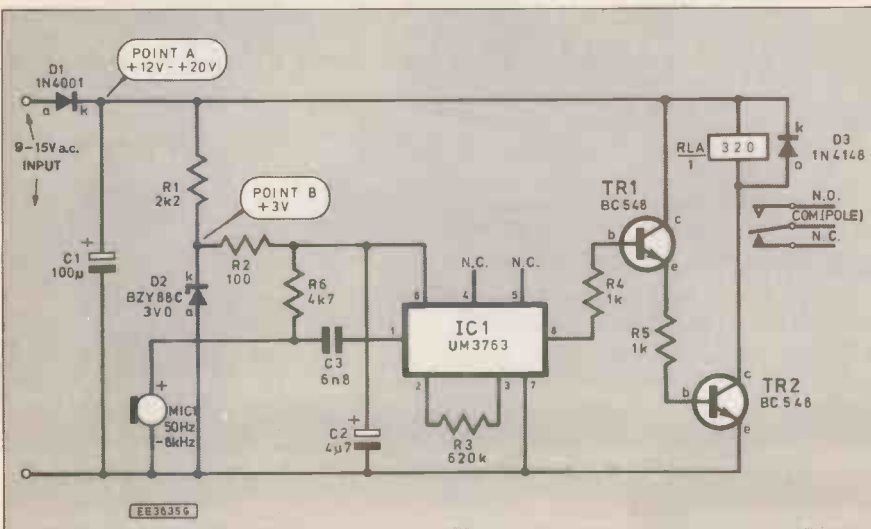

COMPONENTS

Resistors

- R1 2k2
- R2 100
- R3 620k
- R4, R5 1k (2 off)
- R6 4k7

All 0.25W 5% carbon film

See
**SHOP
TALK**
Page

Capacitors

- C1 100µ radial elect., 35V
- C2 4µ7 radial elect., 16V
- C3 6n8 ceramic disc

Semiconductors

- D1 1N4001 1A 50V diode
- D2 BZY88C3V0 500mW 3V Zener diode
- D3 1N4148 70mA 100V diode
- TR1, TR2 BC548 npn transistor (2 off)
- IC1 UM3763 whistle switch

Miscellaneous

- MIC1 Omnidirectional electret microphone insert
- RLA 12V 320 ohm coil relay, single-pole changeover mains contacts

Printed circuit board available from the EE PCB Service, code EE805; single-core screened cable; solder pins; solder, etc.

Suitable a.c. or d.c. supply e.g. mains transformer with 12V secondary rated to drive the load used, or plug top power supply with 9V to 15V output at the required current (100mA for relay unit).

Approx cost guidance only

£9

plus supply

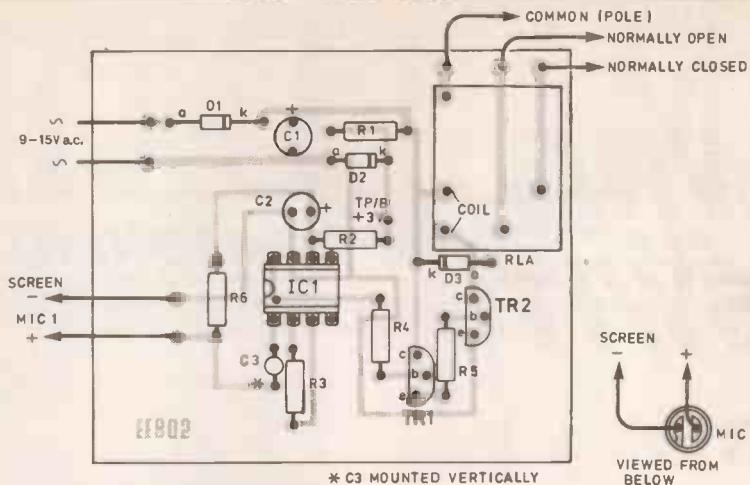
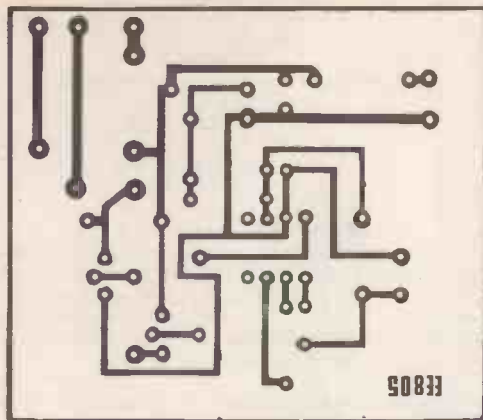


Fig. 2. P.C.B. layout and wiring for the Whistle Switch.

Check the board for any "dry" joints or solder blobs that are causing any shorts. If all is well then the board should be powered up *without* the whistle switch i.c.

TESTING

Once the p.c.b. has been powered up, the following spot checks can be made. At this point check both voltages at point *A* and point *B* and make sure they are correct.

Point *A* can be anywhere from about 9V to 20V and point *B* should be at 3V. If not check and make sure the polarity of the Zener diode D2 is correct, as this will damage itself and IC1.


When you are happy that all is well, switch off the power and insert the whistle switch i.c. and power up again. Now WHISTLE! You should hear the relay operate with each whistle. A little practice may be necessary for you to find the higher and lower frequency limits.

IN USE

By using the relay contacts, you are able to use this "sound switch" in anything you want – the choice is yours.

One idea may be to connect it to a mains table lamp and simply by whistling it will activate the light.

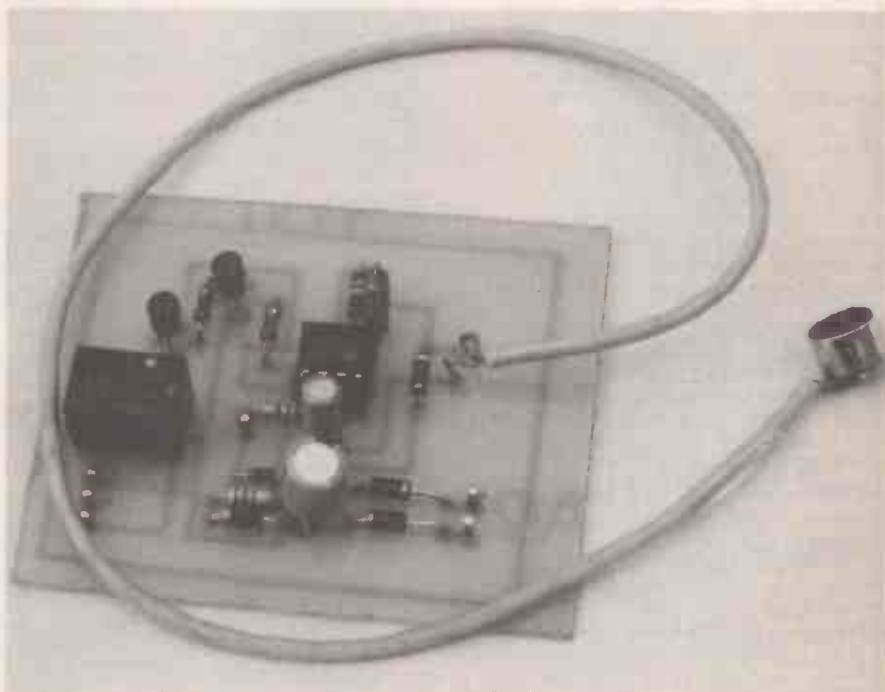The specified relay can be used to switch up to 3A a.c. inductive loads. However if you intend to switch mains appliances the unit must be housed in a fully enclosed Earthed metal box and the supply must be



The prototype unit, the circuit and relay have been changed in the final version.

suitably fused. Do not attempt to switch mains appliances unless you are experienced in wiring to the mains – it can

kill. Remember that if you connect a mains appliance mains voltages are then present on the p.c.b. □

EVERYDAY ELECTRONICS BINDERS



Don't let your valuable issues of EE get binned, burned or bitten (by the dog). Get one of our exquisite orange hard-back binders, slip each issue into it as you get them and you will always know where they are – we hope!

Binders to hold one volume (12 issues) are available from Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH for £5.95 (£6.95 to European countries and £8.00 to other countries, surface mail) inclusive of postage and packing. **Payment in £ sterling only please.**

Binders are normally sent within seven days of receipt of your order but please allow up to 28 days for UK delivery – more overseas.



MAILTECH

ELECTRONIC COMPONENTS

OPTO DEVICES – LEDs – ETC

PHOTO SENSITIVE SCR
Mounted on a PCB. No data,
60p each, 2 for £1.00

7 SEG DISPLAY
MAN6610 2 digit 0-6" high com anode, amber
60 p each, 4 for £2.00

OPTO-ISOLATOR OP12252
50p each 10 for £4.00

SLOTTED OPTO
£1.00 each

LEDs – LEDs – LEDs

5mm rnd red/yellow/green/amber 10p each 12 for £1.00 any mix
5mm rnd high brightness red/green 20p each 6 for £1.00 any mix
5mm rnd flashing red 60p each, yellow/green 70p each
5mm rnd bi-colour 20p each, tri-colour 30p each
Rectangular 6 x 6 x 2mm red stackable 10p each 12 for £1.00
LED mounted in chrome bezel red, yellow or green

LED mounted in a black bezel red only 30p each, 4 for £1
PLASTIC BEZEL for 5mm rnd leds 25p each, 5 for £1.00
20 ASSORTED FULL SPEC LEDS. Various shapes and colours £1.00

ALARM CONTROL UNIT

Single zone alarm control unit built into a domestic light switch box. Ideal for home, caravan, boat, garage, shed etc.

Facilities: – Normally closed loop for pir sensors, door/window contacts etc.

Normally open loop for pressure mats.
24-hour loop for personal attack button
Visual indication that the system is operational.

Automatic entry/exit delay.
Automatic system reset.
Alarm output cmos logic level.

PRICE COMPLETE WITH FULL INSTRUCTIONS £8.95
BELL/SIREN INTERFACE BOARD COMPLETE £3.95
BELL/SIREN INTERFACE PCB ONLY £1.50

PASSIVE INFRA-RED ALARM SENSORS

SUB-MINIATURE PASSIVE
INFRA-RED SENSOR ONLY
£5.95

Brand new passive infra-red sensor, measures only 33mmW x 24mmH x 29mmD. Logic level output. Full data and application notes supplied.

EX INSTALLATION SENSORS tested working.
Type 1. Measures 180 x 112 x 70mm with walk test led, relay output and tamper protection. 12 volt dc supply required £8.50 ea
Type 2. As above but a smaller unit 123 x 62 x 50mm £11.75 ea

DOOR/WINDOW CONTACTS
Surface or flush mounting, white £1.10 ea
JUNCTION BOX
white 6 way 60p

Please note: There may be variations in the size of the above passive infra red sensors depending on stock at the time of ordering. But the unit will certainly be within the stated sizes.

DUAL TECH SENSOR Microwave and passive infra-red combined. Separate led indication for each function. Measures 120 x 75 x 50mm. Relay output 12 volt dc tamper protection £29.95 ea

BREADBOARDS – CAPACITORS – SOLAR CELLS – HEATSHRINK – ETC

SOLAR CELL 2 volt 150mA max, size 60 x 100mm £1.35 ea 5 for £6
HEATSHRINK SLEEVING 8mm dia x 40mm long 5 lengths for £1.00
BNC SOCKETS 50 ohm single hole fixing 50p ea 10 for £4.00
MIN BNC PLUG AND SOCKET 2 pairs for £1.50
PIEZO TRANSDUCER 5 assorted types £1.00

MERCURY TILT SWITCH
Standard on/off £1.00 each
4 Contact (Directional) £1.50 each

PIEZO VIBRATION SENSOR
with data sheet £1.00 each

BREADBOARD
173 X 65mm 840TP £5.25 each
TEXTOL ZIF SOCKET
28 pin zero insertion socket £5.95 each
SOLID STATE RELAY
Switch mains up to 7 amp 12 or 5 volt control voltage both types £2.95 ea

6 VOLT NI-CAD PACK 5AA NI-CADS, fast charge type £3.95
CAPACITOR 10,000 mfd 25 volt with fixing clip 60p each
CAPACITOR 470 mfd 400 volt £1.50 each 4 for £5.00
CAPACITOR 0.1mfd 63volt 6p each 10 for 50p
EPROMS 27C256 – 30 27C512 – 25. Once programmed but never used eprom. Mounted on a plastic carrier, can easily be removed from the carrier or used with a low insertion force socket.
27C256 £1.00 each 6 for £5.00 27C512 £1.20 each 5 for £5.00
Suitable low insertion force socket 28 pin 40p ea 3 for £1.00
MULTITURN PRESETS 20mm RECT, 500R, 1K, 5K, 10K, 20K, 50K, 100K 1MO. 40p ea, 3 for £1.00

All prices include VAT.
Please add 75p carriage to all orders

PROJECT BOXES A range of high quality boxes moulded in black high impact ABS, easily drilled or punched to produce a professional looking end product

TYPE	W	L	H	PRICE
T2	75	56	25	£0.77
T4	111	57	22	£0.92
MB1	79	61	40	£1.35
MB2	100	76	41	£1.47
MB3	118	98	45	£1.71
MB4	216	130	85	£5.19
MB5	150	100	60	£2.35
MB6	220	150	64	£3.95
MB7	177	120	83	£3.42
MB8	150	80	50	£2.22

All sizes are in millimetres

SPECIAL OFFER – PROJECT BOX
As above boxes 50 x 70 x 25mm
60p each 10 for £5.00

KEY SWITCH
3 Position keyswitch
£2.35

MICRO SWITCH roller arm operation spdt 40p each
MINIATURE TOGGLE SWITCHES

spdt	60p each	spdt 3 position c/off	70p each
dpdt	70p each	dpdt 3 position c/off	80p each
3 pdt	90p each	spdt 3 position c/off biased both ways	70p each
4pdt	£1.20 each	dpdt 3 position c/off biased one way	80p each
spdt biased	60p each		

MINIATURE TOGGLE SWITCH pcb mounting 3pdt 50p each 10 for £4.00

MINIATURE PUSH TO MAKE SWITCH 50p each

DIL RELAYS 5 volt dp/changeover 60p 10 for £5.00
12 volt dp/changeover 80p 10 for £6.00

RELAY 10 amp contacts sp/changeover 12 volt coil £1.20 each

CAR HORN RELAY in metal can with fixing lug, s/pole on 10 amp contacts £1.00 each 6 for £5.00

20 AMP RELAY dp on 12 volt coil £1.50 each 4 for £5.00

REED RELAY 12 volt 50p each 10 for £4.00

240 VOLT AC RELAY. 3-pole c/o 10 amp contacts £1.50 each 4 for £5.00

12 VOLT DC RELAY BOARD A useful PCB (196mm x 71mm) with 3 x s/pole c/o relays and 1 x d/pole c/o relay. Connections to relay contacts and coils are brought out to pcb mounting terminal blocks £1.00 each 6 for £5.00

DIL SKTS

8 pin	10 for	£0.60
14 pin	10 for	£0.90
16 pin	10 for	£1.00
18 pin	10 for	£1.00
20 pin	8 for	£1.00
24 pin	8 for	£1.00
28 pin	6 for	£1.00
40 pin	5 for	£1.00

'D' CONNECTORS

	plug	socket	cover
9 pin	30p	30p	35p
15 pin	40p	40p	35p
25 pin	50p	50p	40p

ALL COMPONENTS FULL SPECIFICATION DEVICES

LCD DOT MATRIX GRAPHICS DISPLAY.

MADE BY HITACHI,
PART No LM225.
Module size:
270w x 150h x 13t,mm.
Display area:
239w x 104h mm.
No. of dots 640 x 200.
Data sheet supplied.
ONLY £23.50.

30,00 SWITCHES TO CLEAR. MIN TOGGLES, ROCKER, TAB, SLIDE, ETC. 45 ASSORTED SWITCHES FOR ONLY £8.95.

SEMICONDUCTORS – TRANSISTORS – ICs – DIODES – REGULATORS – ETC

2N3702	10p ea 12 for £1.00	VOLTAGE REGS
BC337	10p ea 12 for £1.00	7812/7805/7912/7905
2N3904	10p ea 12 for £1.00	all 35p each, any 4 for £1.20
TIP31B	30p ea	AD592An Temperature Sensor i.c.
TIP 3055	90p ea	mounted on 1.5m screened lead
2N3055H	60p ea	complete with data and
2N3771	£1.20 ea	application notes £1.50 ea
741 op-amp	25p ea 5 for £1.00	LM3914/LM3915 Bargraph ics £2.95 ea
555 timer ic	30p ea 4 for £1.00	LM317T Variable voltage regulator
LM324 quad op-amp	30p ea 4 for £1.00	mounted on a small heat sink
1N4007 diode	20 for £1.00	4 for £1.00

Dept EE, Mailtech
PO Box 16 Ludlow
Shropshire
SY8 4NA
Tel: 058 474475

EVERYDAY NEWS

TOSHIBA
YEAR OF INVENTION

Regional semi-finalists for the Toshiba Year of Invention have recently been announced. There are forty-four in all and among them are a number of young inventors, with electronic innovations.

FENCING TARGET

In common with most novice fencers, 16-year-old Katherine Brown from Raynes Park in London found that she had problems co-ordinating her speed and point control. During practice at Wimbledon Fencing Club, she came up with the idea of a fencing "dartboard" and developed it into the Electronic Point Efficiency Exerciser (EPEE). Now her invention has won Katherine a place in the regional semi-finals of the national Toshiba Year of Invention competition, organised by the Confederation of British Industry.

"There is no value in being faster than your opponent if you keep missing him," she says. "Nor is it much good being perfectly on target if he has time to parry you. At present, the only way to achieve both point control and speed is through boring and repetitive exercises."

Fellow club members had rigged up a number of training devices involving golf balls on strings and electric bell pushes, with varying success. *"None of these was very effective because the fencer could choose the area to attack, thus removing the element of surprise that forces you to make split-second decisions,"* said Katherine. *"I began to develop an alternative as part of my final project for GCSE craft, design and technology."*

EPEE is an electronic target or lunging pad, powered by a six volt battery. It uses a system of logic gates, a binary counter and a pulse generator to indicate an area of the target to be attacked, limit the time available for that attack and provide a response to the success or failure of the attack.

Accurate judging in fencing competitions is now achieved through the use of electric foils, stainless steel lamé jackets and body wires connected to score boxes.

Katherine used this technology as the basis for her invention. *"My design is a padded rectangular board, about 60cm by 40cm, covered in a grid pattern of lamé fabric,"* she explained. *"There are lights at the corners of each fabric rectangle, which flash on and off."*

"If the fencer's electric sword comes into contact with the target area, buzzers sound and a bulb lights up. If he/she misses, nothing happens, but other rectangles continue to flash in sequence. The time limit can be slowed down or speeded up to allow beginners or experienced fencers to use the device."

At the moment, Katherine's electronic lunging pad stands against the wall to prevent it from retreating under impact, but she is investigating other support methods that would also retain height adjustability for use by children and the growing number of wheelchair-bound fencers. With the increasing popularity of fencing worldwide, she believes there is a large potential market for her invention.

Now about to embark on her A-levels at Tiffin Girls School, Kingston-upon-Thames, Katherine has set her sights on a career in nuclear physics.

SWITCH MODE AMP

Other regional finalists include Swansea schoolboy, Jonah Nutgens who has designed a new lightweight power amplifier ideally suited for miniature hi-fi and disco equipment.

Fourteen-year-old Jonah, who lives at Reynoldston and attends Bishopston Comprehensive School, said he got the idea for the switch mode power amplifier from a light dimmer circuit layout in an electronics project book.

"The main benefits of a switch mode amplifier are that it is cheaper, smaller and lighter than a normal amplifier, because it does not require a large heatsink or a large transformer - both expensive items. This makes it ideal for use in miniature hi-fi's - and easier to transport for discos and stage amplifications. It is 'environmentally friendly' because it uses less electricity."

He explained that in a normal amplifier the voltage sent to the loudspeakers is controlled by changing the resistance of two transistors. It is the resistance of the transistors that causes heat to be generated. In his switch mode design the output transistors are switched on and off many thousands of times per second, giving an output voltage proportional to the time the transistor is kept on. Because the resistance of the transistor is either very high or very low, very little heat is produced.

TEXT PHONE

Richard Mead, 16-year-old schoolboy from Cheltenham College, has for the second time, won a place in the regional semi-finals of the competition. Last February Richard received £5,000 as winner of the schools category for his Powersave energy monitor. His new idea, called Textcall, is a design for a simple-to-use telephone for people with hearing difficulties. Although most learn to lip read and use sign language, the telephone presents an additional problem.

Up to now telephone communication has been almost impossible, the only solution

being the use of a textphone or computer modem link, where the user types his or her message into a computer, which is then transmitted via telephone modem to a terminal at the other end of the link. Such systems are expensive, cumbersome and require a unit at each end of the telephone link.

Richard Mead's Textcall requires only one unit at one end of the telephone line. It does not require a transmission unit as messages are sent using the dialling tones of an ordinary tone-dialling 'phone.

The number keys one to nine on a 12-button key pad of the telephone each represent three letters of the alphabet. The bottom three keys, the star, zero and hash symbols are used to identify which of the three letters was meant. A simple sequence of two presses per letter is used to enable rapid transmission of any alphabet letter.

The tone sequences are received by a Textcall unit attached to the ear piece of the non-hearing person's telephone, which decodes these sequences into letters and words, and then displays them so that they can be read. Assuming the non-hearing person can speak and the original sender can hear, the message can be answered verbally. If not, a second Textcall unit can be fitted, enabling two-way communication between two deaf people.

Richard had the bright idea for Textcall when his sister complained about the difficulty she had communicating with a deaf friend outside school time. He began working on his idea as a GCSE electronics project and has now developed a prototype receiver and hopes a microprocessor will eventually carry out the basic logic functions of the unit.

He says his idea is principally for use by deaf people and hopes to interest the Government and other organisations who spend considerable funds installing complicated systems to help these people.

Textcall requires nothing more than one unit, a regular telephone and several keypad overlays which are distributed to those who might call the user, showing them how to send each letter. Richard believes there is nothing available to complete with its simplicity or value for money.

FINALS

Regional judges will be visiting all the semi-finalists, chosen from 4,333 entries. Regional finalists will be announced during September, each of whom will win Toshiba equipment worth approximately £2,000 and at the judges discretion, financial assistance to help develop their inventions for the finals.

The Toshiba Year of Invention, now in its fifth year, offers total prizes valued in excess of £100,000.

POCKET-SIZED EPROM ERASER

A new compact and lightweight UV EPROM eraser, specifically designed for technicians in the field and electronic enthusiasts has been launched by Ultra-Violet Products Ltd. The portable DE-1 can erase EPROMS in about two minutes, is battery-operated and easy to use.

Depending on their size, three to eight EPROMS are simply placed on the eraser's foam padded tray and a UV lamp unit is lowered onto the components. A specially tailored vertical sliding mechanism helps the operator to adjust the lamp to the correct height above the EPROMS.

Weighing only 335 grams and measuring just 3.8cm x 8cm x 17.5cm, the DE-1 readily fits into a pocket or tool kit and is particularly useful when a mains power supply is not at hand. The 4 watt, 254nm UV light source is powered by four standard batteries which operate for at least five hours. The DE-1 retails at £22.00.

Ultra-Violet Products Ltd., Dept. EE, Science Park, Milton Road, Cambridge CB4 4FH. Tel: 0223 420022. Fax: 0223 420561.

CIRCUIT SOFTWARE

DEVELOPED by Interactive Image Technologies Ltd., based in Toronto, Canada, *Electronics Workbench* is a powerful software program that allows electronics students and enthusiasts to build and simulate analogue and digital circuits on a computer. The components are those found in any electronics lab and the traces on the simulated instruments are the same as you'd get on real equipment – at a fraction of the cost.

The software consists of two modules. The analogue module simulates the analogue parts and instruments. The digital module provides ideal digital parts and instruments needed to build and test logic circuits.

Both modules are claimed to be simple and intuitive to use with the same click-and-drag interface. If the circuit gets too big for the screen you can scroll and keep building. Because the wires are routed automatically and a grid is available, even complex circuits are readable. All commands can be issued from menus with a mouse, and common operations also have keyboard short-cuts.


You can cut, copy and move groups of parts, or put parts into a "black box" called a macro. Even put one macro inside another to simplify complex circuits. Macros can be used simultaneously

in many places in a circuit, and are stored in the parts bin for later use.

Analogue Module includes: SPICE simulation; Transient and steady-state analysis; Resistors, capacitors, inductors, transformers, diodes, Zener diodes, bi-junction transistors, l.e.d.s, bulbs and fuses; A.C. and D.C. voltage and current sources; Function generator for square, triangular and sinusoidal waves; Multi-meter; Dual-trace oscilloscope (1Hz to 999MHz); Bode plotter (-200 dB to +200 dB).

Digital Module includes: Simulation of ideal logic; AND, OR, XOR, NOT, NAND and NOR gates, RS, JK and D flip-flops, half-adder, seven-segment display, l.e.d. and voltmeter; Word generator (16 eight-bit words); Eight-channel logic analyzer (hexadecimal and graphical display); Logic conversion (gate, NAND gate, truth table and boolean expression representations); Logic simplification (Quine-McClusky).

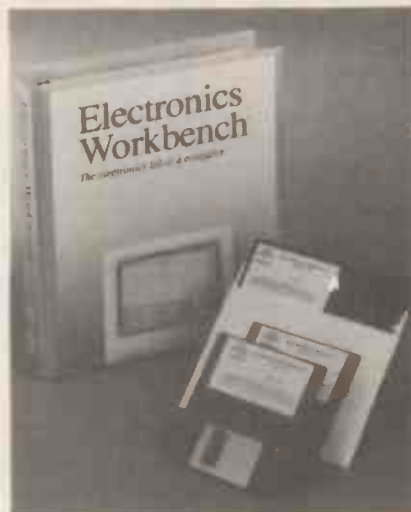Various versions are available to suit a range of PCs and monitors (including a Macintosh Version). The single user Professional Version costs around £190. For more information contact LJ Technical Systems, Dept EE, Francis Way, Bowthorpe Industrial Estate, Norwich, NR5 9JA. Tel: 0603 748001. Fax: 0603 746340.



MICROSOFT COMPLAINT UPHELD

Last month Barry Fox took Bill Gates and Microsoft to task in *For Your Entertainment*. Barry also mentioned that he had made a complaint to the ASA concerning Microsoft's advertisements for Windows 3.0. Microsoft claimed that the average time a computer user takes from scratch to master Microsoft Windows 3.0 software was two hours thirty minutes, Barry disputed this and, not surprisingly in our view, the ASA upheld the complaint.

Apparently Microsoft have agreed to amend the advertisement if it is used again – maybe they would do better to spend the time on improving the product! Egg on face for Microsoft and their advertising agency Ogilvy and Mather Advertising. Well done Barry. Another step in the right direction for usable software.

By the way our computer left the last line off Barry's piece last month (human error not software this time). The missing words are "had trouble with an earlier version". If you are still looking for the ending – sorry.

21 YEARS FREE COMPETITION


As a small "advanced" celebration of 21 years of EE we present an easy to enter FREE competition.

Just for those readers that actually read each page – and have done so since the first issue – we have a bit of fun and a dozen new Maplin Catalogues to give away. Thanks Maplin for the prizes.

All you need to do is to send in, on a postcard or the back of a stuck down envelope, the name of the author of the first *Teach-In* and the author of the first *Shop Talk*. Yes both titles have been running since issue No. 1, in November 1971.

As a tie breaker the "dancer" (we use the term loosely) on page 36 of issue No. 1 is the present editor, suggest what he might be saying. Keep it clean, we will publish the best/funniest (if any) and give the names of the prize winners in the December issue. All entries to our editorial address (see page 619) by October 7th 1992.

So come on all you long standing readers let's hear from you.

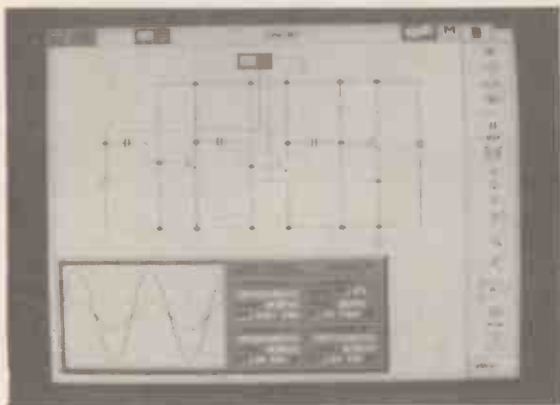

COMPACT I.C. TEST

The ChipMaster Compact from ABI Electronics Ltd is claimed to be the first 40-pin full functional i.c. test incorporated into a battery operated handheld unit.

The unit features a single wide entry zero insertion force socket which accommodates all d.i.l. packages while the integral dot matrix l.c.d. display shows test results, i.c. function and pin data. The unit accepts i.c. codes directly from the keypad or will perform a search to identify the device from their characteristics.

It is claimed that unknown, unmarked and housecoded devices can thus easily be identified and tested. Intermittent and temperature related faults are easily found using conditional loop modes. The ChipMaster Compact has many applications anywhere where verification of an i.c. is required. It costs less than £300.

The ChipMaster Compact is based on the ChipMaster product which ABI has been marketing for two years. It has enjoyed considerable success in diverse markets from research and development to quality and education. This development extends its application to those areas where portability is important.

ABI Electronics Ltd., Dept. EE, Mason Way, Platts Common Industrial Park, Barnsley, South Yorkshire, S74 9JG. Tel. 0226 350145 Fax. 0226 350483.



FOR YOUR ENTERTAINMENT

by Barry Fox



Doomed CD-ROM

Every day I become more sure that there is no mass market future for CD-ROM as a PC peripheral. The system is fine for "vertical" applications, where the PC and ROM drive are set up to run one piece of business software. But any attempt at using the same PC/ROM hardware "horizontally", to run a variety of ROM discs, is doomed to failure.

The root cause of the problem is the "open architecture" of the PC world. With no tight standard specification for competitors to follow (like the standards for music CDs, cassette tapes or mains voltage) hardware and software from different sources will be just sufficiently different to make compatibility a matter of pot luck.

Virgin's software division recently sent me a copy of "North Polar Expedition", a CD-ROM based on expeditions by Sir Ralph Fiennes. I did as the instructions told me and typed "Go" at the DOS prompt for the ROM drive.

The screen went blank and threw up an error message. "Sorry, you have insufficient memory". But my 386 PC has two megabytes of memory, and QEMM memory management to make the best use of it.

The error message on screen told me to try typing "NP", which I did. The computer then locked itself into a cycle of displaying "Invalid directory" over and over again.

After a cold re-start I tried running British Telecom's Phone Disc CD-ROM of telephone directories, just to check that the system was not faulty. Phone Disc ran smoothly.

I also tried running the Polar CD-ROM from my multitasking software, Desqview. I got the same error message, but this time the whole system crashed.

On re-booting I found a string of problems. The crash had corrupted a large and valuable data file. Luckily I had a recent back-up so only lost a few entries. But the crash had also corrupted the MSCDEX extension to the MS-DOS operating system which is needed to control a CD-ROM drive. It had also corrupted the .EXE file for my wordprocessor.

It took me four hours to find backups and original source file discs, and rebuild the hard disk. I may yet find other files which the crash corrupted.

The instruction manual for the Polar CD-ROM has a section on troubleshooting. It tells me to go through my Config and Autoexec files, looking for drivers to remove. I should also reduce the number of files and buffers. And because other software will need more files and buffers, I should keep and load a special copy of my Config file for running the Polar CD-ROM.

Hey, I've got a better idea. Why don't I leave things as they are and not bother to run the Polar CD-ROM.

If I want to run the Polar program I will wait until it is available on a "closed architecture" system, like CD-I, where the hardware and software specification is so tight that any program disc is guaranteed to run on any hardware system. I look forward to the day, too, when manufacturers will build CD-I players into TV sets, where they surely belong, along with a plug in keyboard to make searching for text data far easier than with a mouse and on-screen menu.

Not A Lot Of People Know This!

It is now nearly two years since unified Germany stopped using SECAM for what had previously been East Germany, and switched to PAL. This happened without any publicity. Even the date of the transition is hazy. Some say January 1991. Others are more specific and say the switch was thrown on 9 December 1990.

What matters is that by 1991 SECAM was out of Germany. It was was out because it was out of the question for Germany, the country which had invented PAL, to go on using France's SECAM anywhere in its new territory.

The change was easy for the East German broadcasters. Many were already using component video studio equipment which needed no conversion. It was only necessary to convert a few transmitters.

All the West German transmitters serving the border areas and Berlin were already beaming PAL programmes into the East. And the East had long since given up trying to stop people watching Western TV, for instance by tricking young schoolchildren into drawing the clock which they saw on their TV screen at home;

the East and West used different clocks. It is now very hard to buy new professional SECAM equipment from previous suppliers Thomson and BTS.

There were few complaints from viewers. Since the Eastern authorities relaxed their grip on TV viewing, many people in East Germany had already bought dual standard TV sets capable of receiving PAL and SECAM. They had been using them to watch West German TV programmes which were far more interesting than the drab political diet authorised in the East.

Many people were flush with hard currency exchanged for the toy money previously used in the East. With their new money some bought cheap PAL sets brought in from China. Many bought European sets made by Grundig, Thomson and Philips. Others bought Japanese equipment.

So 1991 was a boom year for the electronics companies in Europe. This disguised the downwards spiral which is best shown by the offtake (that's sales and rental deliveries to homes) of colour TV sets in the isolated UK.

The UK offtake in 1983 was 3.32 million. By 1988 it had climbed to 4.43 million. The number has fallen each year since then, to 3.33 million in 1991, and is expected to be lower again this year.

The East Germans who could afford a TV set have now bought one and there is no more free money to spend. Many ex-Easterners are out of work because the industries they worked for were uncompetitive and folded. So they have little hope of earning spare cash. The manufacturers had geared up to a longer boom and ended up overstocked and filling their warehouses.

This is why German broadcast research facility IRT is now hatching plans to switch other Eastern bloc countries from SECAM to PAL. The most likely first on the list is Czechoslovakia.

In France many sets are already dual standard, PAL and SECAM. French viewers watch PAL programmes from all the surrounding countries. There would be no great problem in switching France from SECAM to PAL, and it would generate some extra sales. But politically it would be dynamite for France to abandon the home-grown system it originally adopted to try and protect its national industry.

VERSATILE INTERCOM

I. A. DUNCOMBE



A single "master" design, with good quality audio, range over 30m (100 ft), that can be linked to as many identical stations as required. A "conferencing" set up is also possible

INTERCOMS come in various shapes and sizes, from the simple two station connected by wires types to the more elaborate f.m. multi-station wireless types. All have their advantages and disadvantages, some of the more pertinent are compared below:

Two Station A.M. Wire Connected

- 1 Simple electronics, often using the loudspeaker as the microphone leading to poor quality.
- 2 Incapable of being expanded. The master may call the slave and the slave may call the master, but a slave may not call another slave, if one was to be connected.
- 3 Does not suffer from any mains-bourne interference.
- 4 Extremely cheap and cost effective.

Two Station F.M. Wire Connected

- 1 More Complicated electronics but slightly better audio quality.
- 2 and 3 As above.
- 4 Not particularly cheap but still worthwhile.

Two Station A.M. Wireless

- 1 Much more complicated electronics having to modulate the audio onto the mains supply.
- 2 As above.
- 3 Severe interference from mains click's and pop's. Could also itself cause interference to other sensitive devices connected to the same mains supply.
- 4 Much increased cost with no real advantages over wire connected types.

Two Station F.M. Wireless

- 1 Complex electronics but vastly improved audio quality.
- 2 As above.
- 3 Not subject to any interference but could still cause interference itself.
- 4 Cost is high but probably the ultimate in intercoms.

MULTI-STATION INTERCOMS

Up till now we have not considered multi-station systems. These are vastly more complicated either in the connection between each unit, or in the case of wireless types, the electronics.

A simple system consisting of, say master and several slaves are a distinct possibility for wire connected units, but only the "normal" operation of master-to-slave or slave-to-master is possible. A slave cannot call another slave. In this instance of course the wiring between each unit is much more complicated.

With a.m. wireless systems the situation is on one hand simplified and on the other more complicated! As of necessity, each unit must be a master, that is, each unit must be capable of sending and receiving independently. This makes it easier for any unit to call any other unit.

On the other hand only one connection, or conversation between any two units can take place at any one time. Any other unit wishing to call will interrupt the existing connection.

This disadvantage is easily rectified if an f.m. system is used. Since the audio signal must be modulated onto a sub-audio signal and then passed through the mains, it is easy to select different send and receive frequencies for each master unit. In this way multi-connections can take place over the same mains supply.

VERSATILE INTERCOM

The design presented here does not pretend to overcome all the disadvantages set out above, nor is it the ultimate in design. It is essentially a single unit, or station which can be very easily expanded to as many stations as required.


It does however possess several distinct advantages which, when compared with the initial cost rather outweighs the disadvantages:

- 1 Audio quality is particularly good, employing a microphone instead of using the loudspeaker to perform the same function. Surprisingly, this does not add any considerable cost to the unit as a whole.
- 2 Each unit is a master making several connections possible. Indeed even a "conference" facility is possible as we shall see later.
- 3 Interference is no problem.
- 4 Cost is moderately high but not excessive.

DESIGN CRITERIA

As mentioned earlier, one of the disadvantages of simple intercoms is the lack of

Fig. 1. Principle of operation of the Versatile Intercom.

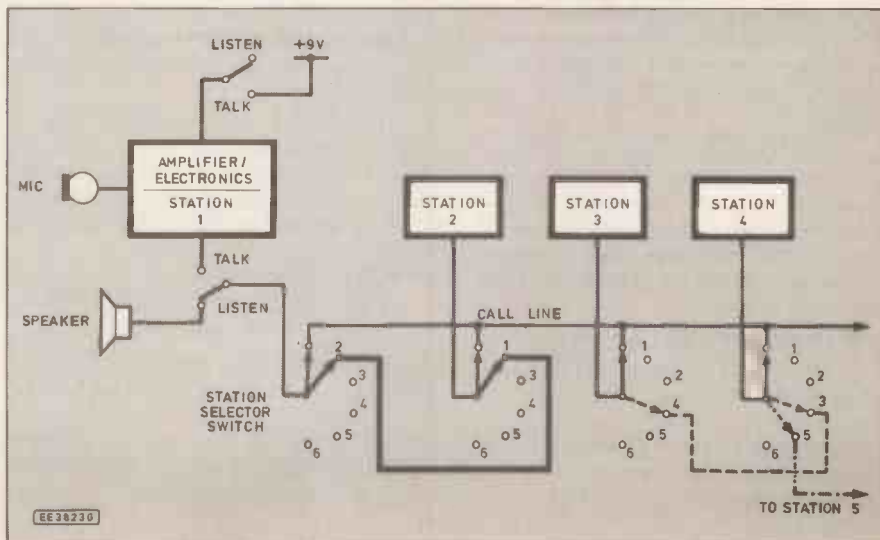

good audio quality. This was the main requirement for this design, and was achieved by using a microphone insert instead of using the loudspeaker. The reason is often put down to cost, but a 90p microphone insert is hardly a worthwhile argument.

The second requirement was to be, to a certain extent, multi-station. As was indicated earlier, if each unit is a master then slave-to-slave communication is simple.

A third and important requirement was that each unit must be permanently *un-connected* to any source of supply voltage until each was used. It is often found in other intercom systems that the batteries or other supply are always connected, although obviously not drawing too much current.

In achieving this requirement the use of a power supply was a distinct possibility, eliminating the cost of buying batteries.

Each unit being a master and each having its own power supply, the connection between each unit is made by three wires. This greatly simplifies the switching and allows the microphone to be permanently connected to the electronics, whilst the speaker is connected so that it is always in the "Listening" mode.

PRINCIPLE OF OPERATION

The principle of operation is shown in the system block diagram, Fig. 1. This shows one unit with the microphone permanently connected to the electronics and the simple on/off switching used. The loudspeaker is connected, via the station selector switch, to a common connection between all other units. We shall call this connection the "Call Line".

In the normal position the Listen/Talk switch is biased to be always in the listening mode and with the power source disconnected. Thus all units are "listening" on the "call line".

STATION-TO-STATION

Consider now if, say Station One wishes to call Station Two, this is shown by the heavy line. The user of Station One ensures that the Station Selector switch is set to the "call" position. He/she then switches the station to the talk mode and by pressing a switch causes a tone to be heard not only at Station Two, but *all* other stations connected to the system.


By announcing after the tone with whom he wishes to communicate, it should be clear to other stations listening who is being called. Once Station Two answers, each station then selects the appropriate position on the selector switch and a private conversation will have been set up.

Now consider if say Station Four wishes to call Station Three, this is shown in the diagram by the dotted line. Station Four follows the procedure just described for calling, and once Station Three replies, each set their station selector switch to the correct position. Thus, two *independent* conversations have now been set up on the same circuit.

CONFERENCING

The conference facility is a little arranged, but is the best that could be accomplished with such a simple switching system.

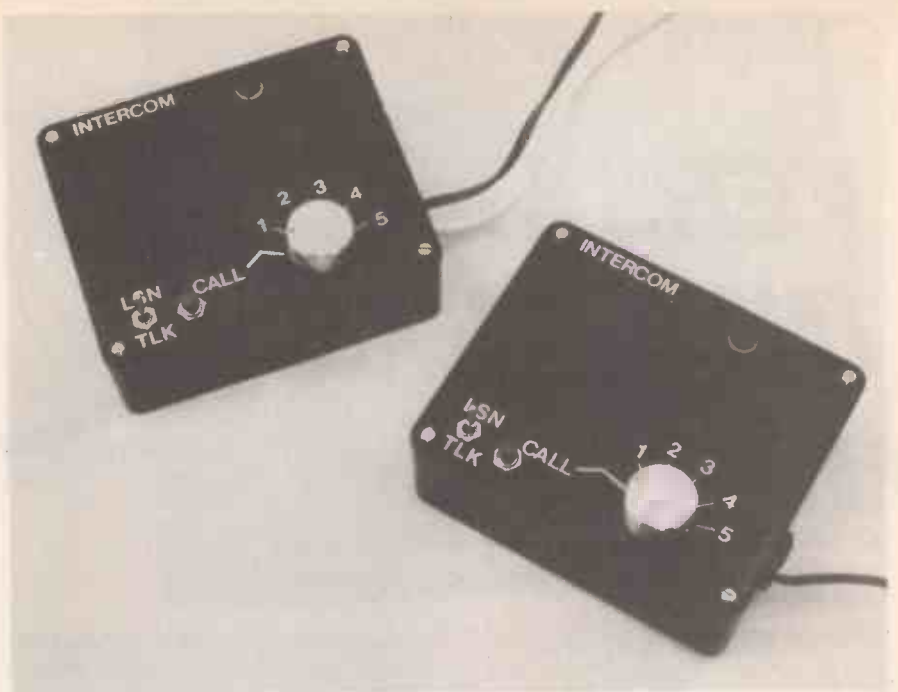Assuming that Station (1) wishes to call a conference with Stations (2) and (3) but not (4). He simply follows the same calling procedure using the "call line". Once each



station has replied they remain on the "call line" and the conference follows.

It is assumed that Station Four will very kindly set the station selector switch to an arbitrary position and not listen in! The conference facility is not private.

If more than four stations are on the circuit, it is quite in order for say, Station (4) to call Station (5) on the "call line", and then for each to set up their own private connection (dashed/dot line). Only a brief interruption of the "conference" will have taken place.

One disadvantage should now be apparent. If any station does not return the Station Selector switch to the "Call" position, it cannot be contacted further. The only way it could be called, is if the station

previously in contact with it calls on the direct connection as shown previously by the heavy and dashed lines.

CIRCUIT DESCRIPTION

The full circuit diagram for the Versatile Intercom is shown in Fig. 2. The power supply circuits are shown in Fig. 3.

Two i.c.s are used as the basis, with IC1 operating as a pre-amplifier and IC2 as a power amplifier. Transistor TR1 operates as a tone generator.

Pre-amplifier

Resistors R1 and R2 form a potential divider applying about 1.5V to the condenser microphone insert MIC1. This voltage may

COMPONENTS

Resistors

R1	15k
R2	10k
R3	680
R4, R5	47k (2 off)
R6	22k
R7	12k
R8, R9	120 (2 off)
R10	1k5

All 0.3W 10% carbon film

Capacitors

C1, C4, C8, C9	100n Mylar or polyester (4 off)
C2	560p polystyrene
C3, C5	4µ7 radial elect, 16V (2 off)
C6	100µ radial elect, 16V
C7	1000µ radial elect, 16V
C10	47n Mylar or polyester

Semiconductors

D3	5mm Red light emitting diode
TR1	2N2646 unijunction transistor
IC1	LF351 op-amp
IC2	LM380N audio amplifier

Miscellaneous

MIC1	600 ohm condenser microphone insert
LS1	8 ohm, 75mm dia. loudspeaker
S1	d.p.d.t., biased one way min. toggle switch
S2	1-pole 6-way rotary switch
S3	s.p.s.t. press-to-make switch
Plastic ABS case, size 118mm x 98mm x 45mm; stripboard, size 20 strips x 36 holes; control knob, 22mm diameter; i.e.d. mounting clip; screened cable; 8-pin i.c. socket; 14-pin i.c. socket; plastic screw terminal block, 7-way; connecting wire, hardware etc.	

BATTERY VERSION ADD

B1	PP3 battery
PP3	battery clip; 12mm (1/2in) "Terry" clip

MAINS VERSION ADD

T1	mains transformer: 240V primary; 9V-0V-9V 100mA secondary
D1, D2	1N4002 1A 100V rec. diode (2 off)
C11	100n Mylar or polyester
C12	1000µ radial elect, 16V
Stripboard, size 10 strips x 20 holes; mains cable	

See
SHOP
TALK
Page

Approx cost
guidance only

Per Unit: £18 (Mains) £15 (Batt)



vary and is not too critical. The output from the microphone insert is applied, via the d.c. blocking capacitor C1 and input resistor R3, to the inverting input, pin 2 of IC1.

Resistors R4 and R5 bias the non-inverting input, pin 3, at about half the supply voltage, and C3 provides d.c. stabilisation, and also filters out any hum or noise on the supply lines. Capacitor C2 provides a slight amount of low frequency cut, improving the audio, which often sounds "muffled" with inexpensive intercoms.

Resistor R3 matches the impedance of the microphone insert, typically 600 ohms, to the inverting input, pin 2 of IC1. Together, resistors R6 and R3 set the gain of the i.c. at about 32.

Amplifier

The boosted output from IC1 is passed to the non-inverting input, pin 2 of IC2 via d.c. blocking capacitor C4. This i.c. has a fixed gain of around 40 and provides just a little less than one watt output. Capacitor C5 provides hum rejection, and capacitors C7 and C8 provide filtering of the supply lines for both battery and mains supplies.

The output from IC2 is connected via

capacitor C6 and one half of the Talk/Listen switch, S1a, to the pole of S2 and hence to other units.

TONE GENERATOR

The tone generator, which is used to call other units, is based around a unijunction transistor TR1. A tone is required, as calling by voice may get lost in the background noise.

The circuit may look unfamiliar to many readers. It is a relaxation oscillator using a

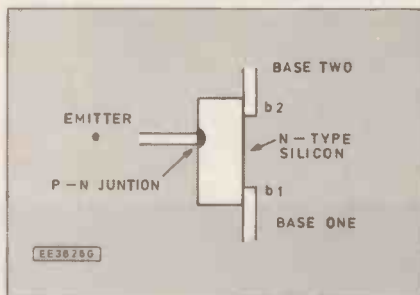


Fig. 4. Unijunction transistor construction.

unijunction transistor. UJT's, as they are often called, are not found very often in designs nowadays so a detailed explanation will be given.

Unijunction

First refer to Fig. 4, this is a schematic of a UJT. It has a single layer of, say, *n*-type silicon with two ohmic connections at each end, and a *p-n* junction near the centre. The two end connections are called base one (b1) and base two (b2), while the junction is called the emitter (e).

If the junction is reverse biased, the resistance between b1 and b2 is fairly high, having a typical resistance of >10k. By forward biasing the junction the resistance can be substantially reduced to just a few tens of ohms.

Oscillator

Refer now to the main circuit diagram Fig. 2. It is assumed that when power is first applied, capacitor C10 is uncharged and the emitter of TR1 is near 0V.

Current flows via R7 charging C10. As the capacitor follows the normal exponential law, a point is reached where the emitter junction becomes forward biased. At this point, around half the supply voltage, the junction conducts and the resistance between b1 and b2 falls.

The reduction in resistance allows the emitter junction current to flow to the most negative part of the circuit. In this case it is towards 0V. The emitter junction is effectively at ground potential and C10 discharges. This discharge causes a pulse to appear at the emitter.

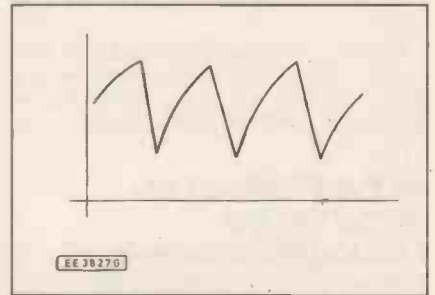


Fig. 5. Oscillator saw-tooth output waveform.

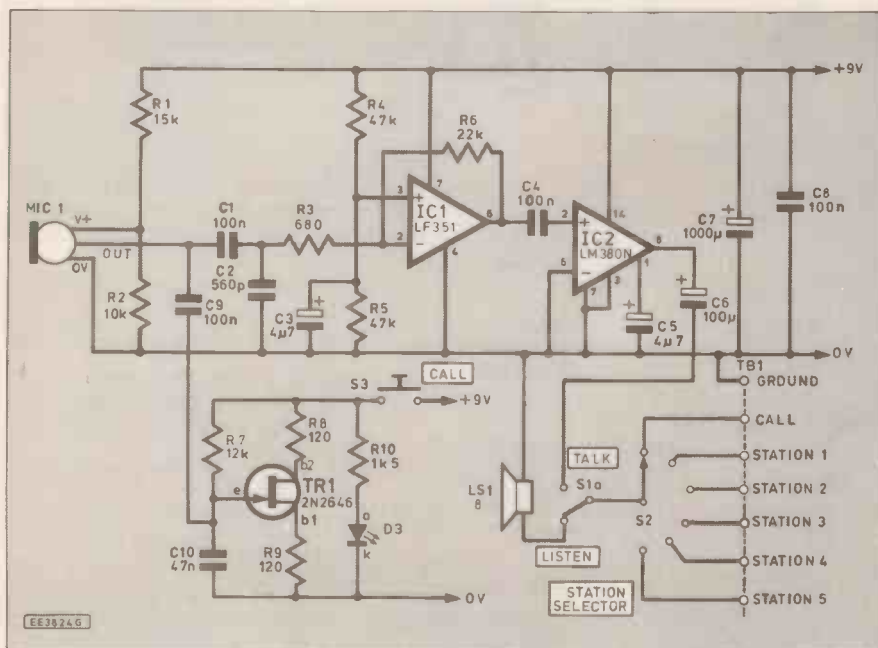


Fig. 2. Circuit diagram, excluding power supply for the Versatile Intercom.

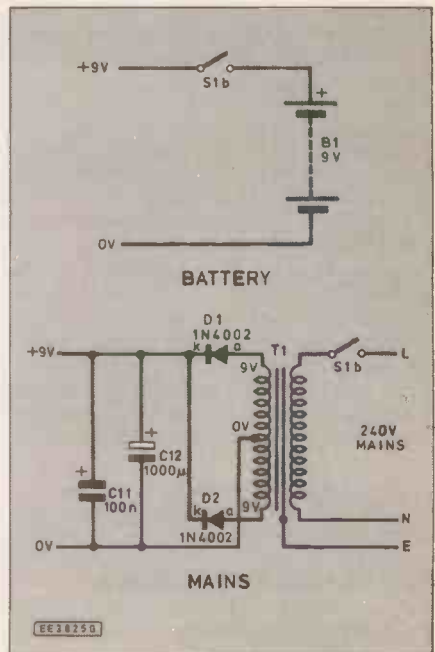


Fig. 3. Battery and mains power supply

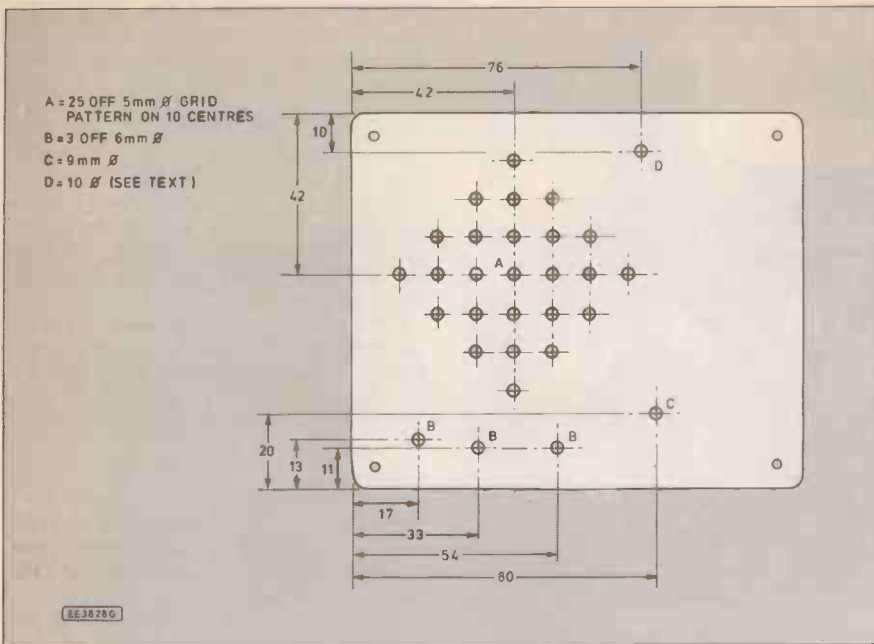


Fig. 6. Front panel drilling details for both versions.

As the capacitor continues to discharge a point is reached where the junction potential falls below the turn-on voltage of TR1, and the resistance between b1 and b2 begins to rise. This increase in resistance allows the emitter potential to return back to its previous state and the cycle repeats.

With the values given the cycle repeats at a rate approximately equal to 0.8RC, and produces an audible output with a frequency of around 1.7kHz. The waveform generated, Fig. 5, is called a "sawtooth" and gives quite a "rasping" sound.

Push switch, S3 connects power to this part of the circuit momentarily, thus connecting the "call tone" to the input of IC1. The combination of resistor R10 and l.e.d. D3 provides a simple voltage monitoring circuit giving a rough indication of the state of the battery (if used).

POWER SUPPLY

The two circuit diagrams making up Fig. 3, show the details of the battery and mains circuits.

The basic intercom unit may be powered by either a battery or mains supply. Considering the typical use an intercom might receive in, say, a home environment, there is little to choose between the two.

Of course the battery is initially the cheapest, but in the long run it might be better to consider the mains version. Although the hum level may be inconvenient.

The battery circuit is self explanatory. The second half of S1 (the Talk/Listen switch), simply applies power to the whole circuit.

The mains supply consists of the mains transformer T1, used to step down the mains voltage, and diodes D1 and D2 provides a full-wave rectified d.c. output of about 9V. Capacitors C11 and C12 smooth the d.c. to provide a 9V output.

Notice that in this circuit, the mains supply is switched on and off by S1 (biased off-Listen). Thus in both versions no power is applied to the circuit considerably reducing running costs.

CONSTRUCTION

Construction is best commenced with the case. Drilling details for the case, as used in the prototype, are shown in Fig. 6 (front panel) and Fig. 7 (rear panel). These

measurements may of course be varied depending on the case you are using.

The grid pattern for the loudspeaker should however be adhered to. There is little to be gained increasing the size or number of holes to obtain a louder output.

Holes marked with asterisks are for the mains version only. The dimensions of the two upper holes will depend on the size of mains transformer you are using. The other two holes are used to mount the small power supply stripboard.

Holes marked "B" are for mounting the unit on the wall and could be omitted if desired. They are made by first drilling an 8mm hole and then by using a small needle file to file out the slot.

Make the hole for the microphone insert slightly larger than that indicated. Do not over enlarge though. Push the insert into the hole and secure using clear adhesive (Bostik or similar) on the underside of the panel.

For mounting the loudspeaker, carefully cut out a ring of cardboard equal to the speaker's diameter and about 5mm wide. Very carefully stick this to the loudspeaker using clear adhesive, carefully avoiding the actual speaker cone.


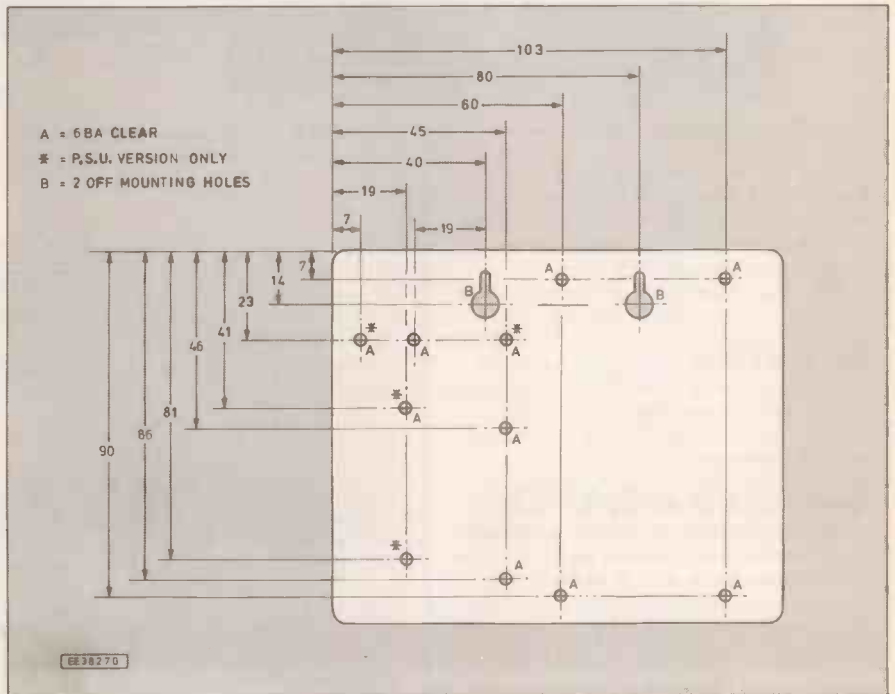


Fig. 7. Drilling details for the rear panel.

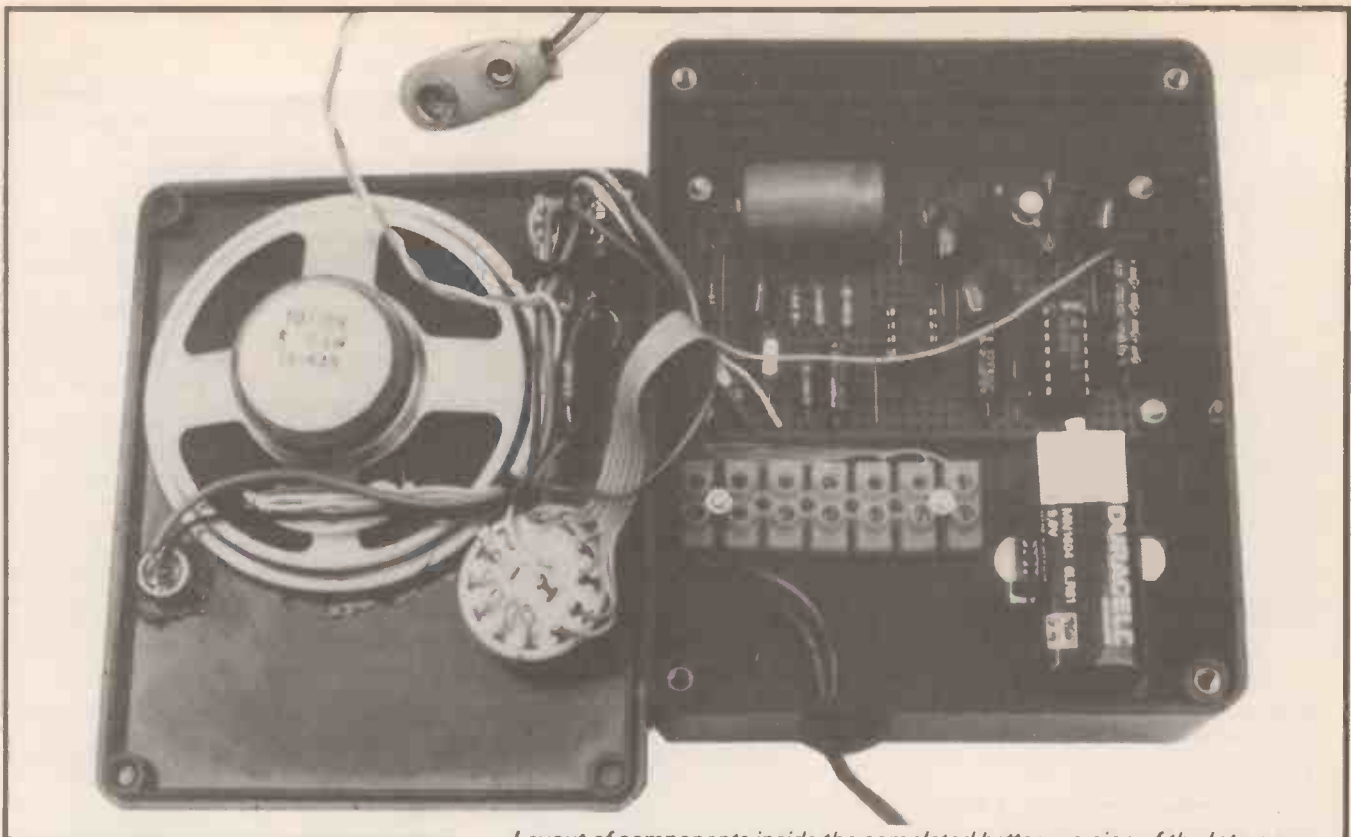



Layout of components inside the completed battery version of the Intercom.

Allow to dry and then fix in place on the front panel using a similar method. The reason for doing this is to avoid damage to the speaker cone, if, for any reason the speaker needs to be removed.

The front panel can be lettered using dry rub-down transfers and then given a coat of clear varnish. Annotate as follows: S1 - LSN & TLK; S3 - CALL and S2 - CALL 1, 2, 3, 4, 5. You can then write the individual locations, bedroom, kitchen etc, of each station on a small piece of card stuck on the front panel.

CIRCUIT BOARD

The main circuit stripboard component layout and details of breaks required in the underside copper tracks is given in Fig. 8. Also shown are details of the small mains supply component board (Fig. 9), less mains transformer.

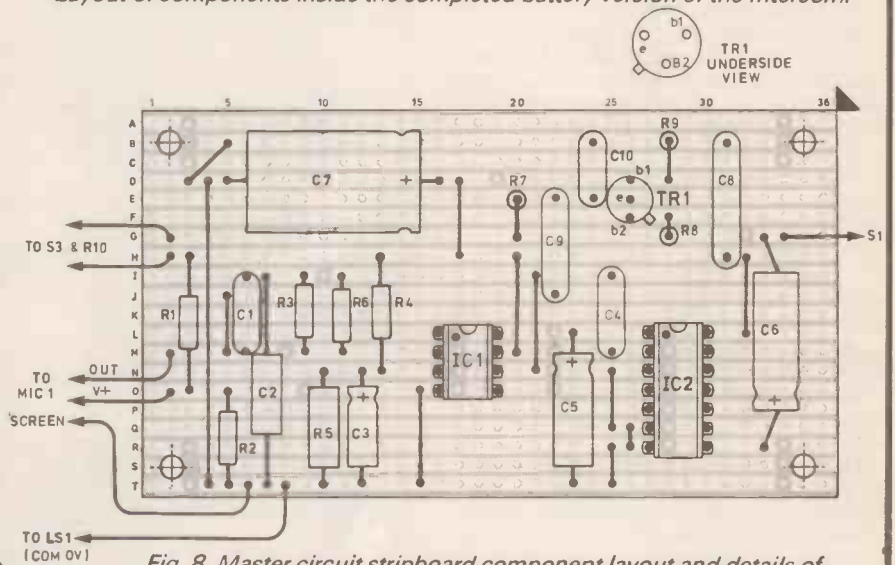


Fig. 8. Master circuit stripboard component layout and details of breaks required in the underside copper tracks.


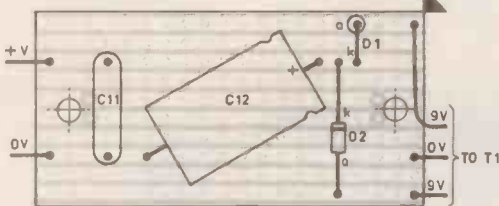
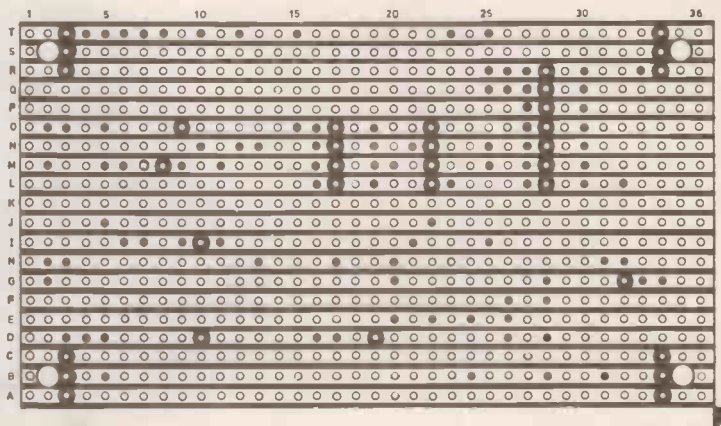


Fig. 9. Mains power supply (p.s.u.) stripboard component layout, less transformer.

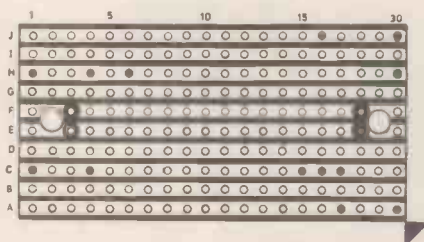

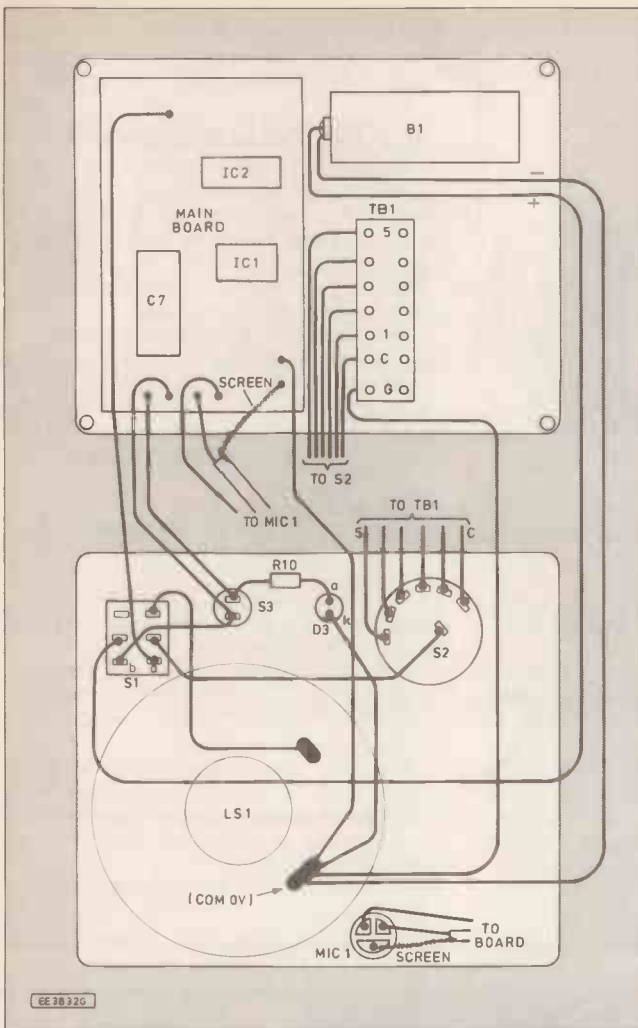


Fig. 10. Interwiring details for the battery version of the Versatile Intercom.

Starting with the main circuit board, the mounting holes are drilled first and then the i.c. sockets are mounted. The breaks in the copper tracks under the i.c.s can be made at this stage, although it might be better to make the remaining breaks as construction progresses.

Wire links can now be fitted followed by the remaining components. Note that the positive end of C6 is in the opposite direction to the other polarised capacitors.

Off-board leads are made using stranded connecting wire about 15cm long. Use different coloured wire to aid identification later.

Turning now to the power supply board (see Fig. 9), follow a similar procedure as before - mounting holes and then copper breaks, finally followed by the other components. Observe the polarity of the diodes and the electrolytic capacitor.

FINAL WIRING

The final interwiring details are shown in Fig. 10. When making connections to the microphone insert try to be as brief as possible with the soldering iron, as the inserts can easily be damaged.

Ribbon cable or stranded wire can be used when wiring S2 to the 7-way screw terminal block TB1. The battery is held in place using a small "Terry" clip.

The stripboard is mounted using short spacers, rubber grommets or just a single nut. There is not a lot of space between the board and loudspeaker and some components on the stripboard may need to be bent over.

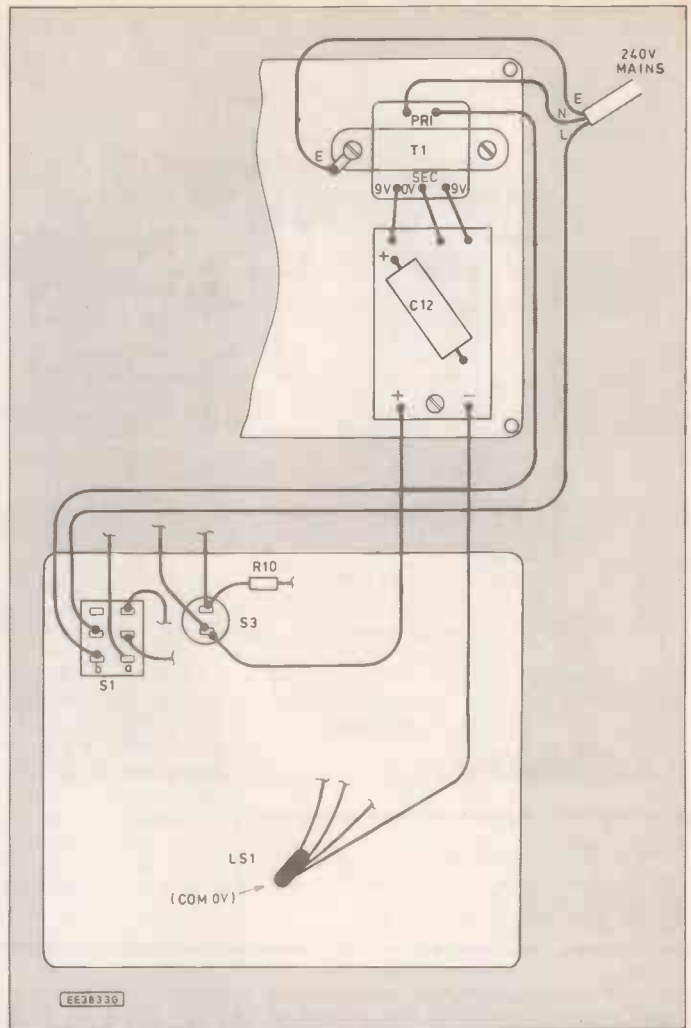


Fig. 11. Final interwiring for the mains version. It is important the S1b tags be covered with insulating tape.

MAINS OPTION

The mains transformer and mains supply stripboard are mounted as shown using holes marked "A*" in Fig. 7. The mains cable can be rated at three amps. Remember to use a solder tag under one transformer fixing hole, to form an "Earth" connection.


It may be necessary to join the individual wires of the mains cable to those of the transformer. If this is the case, you *MUST* use sleeving over the joints. Also use sleeving over *all* the tags on switch S1b.

It is *essential* NOT to connect the wire from S1b to push switch S3 as

shown in Fig. 10. Follow the layout shown in Fig. 11, very carefully, and *check thoroughly* that mains voltages cannot touch any other part of the unit.

Layout of components inside the mains driver version of the Versatile Intercom.

The mains transformer occupies the position of the battery and the p.s.u. board sits below the interconnecting terminal block. Compare with photo on opposite page.

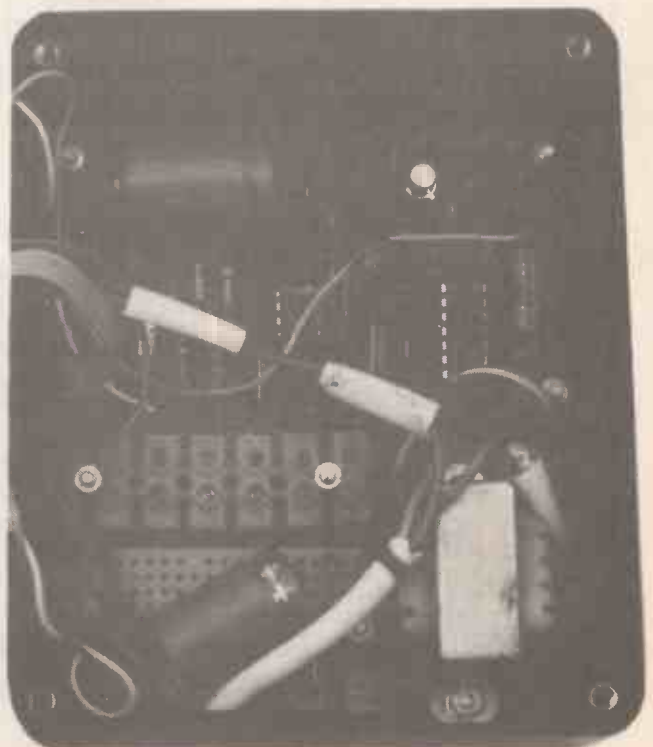

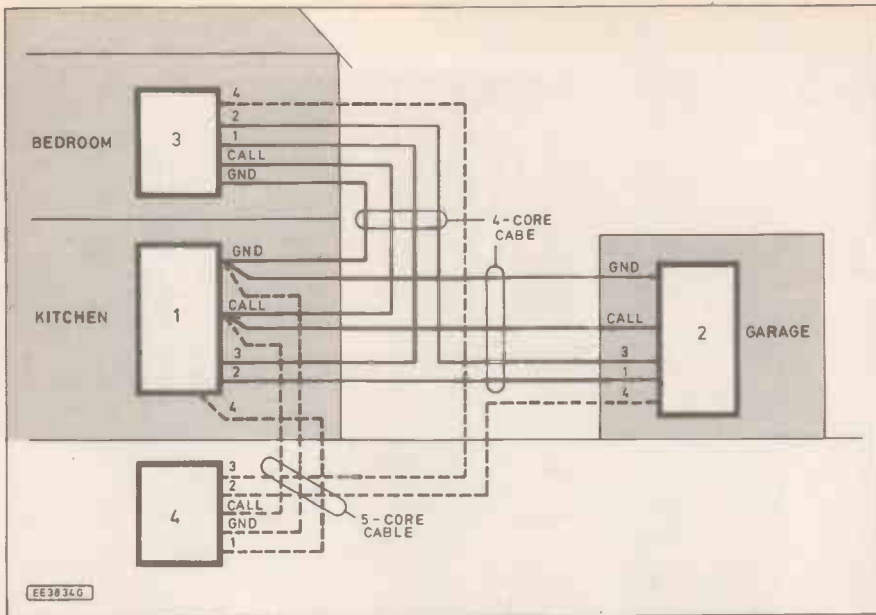


Fig. 12. Typical wiring set-up for a three/four station layout in a home.

Two holes are drilled on the right-hand side of the case to allow the mains cable and connection cable to other units to pass.

TESTING

It is advisable to test all the units (stations) before wiring them together. For this, a second person located some distance away is required. Connect the units together using just a pair of wires, between the ground terminals and the common call line.

Operate switch S1 on one of the units, some background noise should be heard in the second unit. Press and then release the Call button, S3, a tone should be heard. Speak near the microphone. It is not necessary to get too close - arms length is quite sufficient.

Ask the person at the second unit to do a similar test. That is, operate the Talk/Listen switch S1 and then, briefly, the Call button (S3). If you have con-

structed more than two units do the same tests with each one.

If all is well then the units can be located in their final positions and wired permanently.

TYPICAL WIRING

Choose the locations for each unit as required. A typical wiring layout is shown in Fig. 12. Four-core cable, perhaps telephone cable is all that is required to connect three units. Also shown are the connections required if a fourth unit is connected. In this case, five core cable is required.

None of the wiring need be screened, so any type of cable can be used. By careful routing of the cable around the house, the number of cores in each cable can be kept down to the number of stations plus one. So for five stations, 6-core cable is required.

IN USE

Much of the principle of operation has already been discussed, so just a brief reminder.

When you wish to call a particular station, make sure that the Station Selector switch (S2) is in the Call position.

Put S1 to the Talk position and press the Call button. If necessary announce after you release the button to whom you wish to converse. Release S1 to listen.

Once the station answers you can then either select the appropriate position with the selector switch to ensure a private conversation. Or if just a brief word or two, leave the switch as it is.

When finished, be sure to return the Station Selector switch to the Call position. □

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX ★ 031 667 2611

The supplier to use if you're looking for:-

A WIDE RANGE OF
★ COMPONENTS AIMED AT THE ★
HOBBYIST

★ COMPETITIVE VAT INCLUSIVE ★
PRICES

★ MAIL ORDER - generally by ★
RETURN OF POST

★ FRIENDLY SERVICE ★

OPEN:

Monday-Thursday 9.15 - 6.00

Friday 9.15-5.00

Saturday 9.30-5.00

VISA

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60
OUTPUT 0-260V

	Price	P&P
0.5KVA 2.5 amp max	£29.00	£4.65
	(£39.54 inc VAT)	
1KVA 5 amp max	£37.40	£6.25
	(£51.29 inc VAT)	
2KVA 10 amp max	£54.00	£7.80
	(£72.62 inc VAT)	
3KVA 15 amp max	£71.50	£7.80
	(£93.18 inc VAT)	
5KVA 25 amp max	£126.50	
	(Plus Carriage)	

Buy direct from the Importers. Keenest prices in the country

COMPREHENSIVE RANGE OF
TRANSFORMERS-IT-ISOLATION & AUTO
(110-240V Auto transfer either cased with American socket and
mains lead or open frame type. Available for immediate delivery

ULTRA VIOLET BLACK LIGHT

FLOURESCENT TUBES

4ft 40 watt £12.00 (callers only) (£14.10 inc VAT)
2ft 20 watt £7.44 + £1.25 p&p (£10.21 inc VAT)
13in 10 watt £5.80 + 75p p&p (£7.70 inc VAT)
12in 8 watt £4.80 + 75p p&p (£6.52 inc VAT)
9in 6 watt £3.96 + 50p p&p (£5.24 inc VAT)
6in 4 watt £3.96 + 50p p&p (£5.24 inc VAT)

230V AC BALLAST KIT

For either 6in, 9in or 12in tubes: £5.50 + £1.15 p&p (£7.81 inc VAT)

For 13in tubes: £6.00 + £1.35 p&p (£8.64 inc VAT)

400 WATT UV LAMP

Only £38.00 + £4.00 p&p (£49.35 inc VAT)

160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB

Available with B.C. or E.S. fitting. Price inc VAT & p&p: £25.55

12V D.C. BILGE PUMPS

500 GPH 15ft head 3 amp £18.21

1750 GPH 15ft head 9 amp £31.73

Also now available:

24V D.C. 1750 GPH 15ft head 5 amp £32.90

PRICES INCLUDE P&P & VAT

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case. Includes 12in 8 watt 2537 Angst Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £14.00 + £2.00 p&p (£18.80 inc VAT)

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical use etc

Approx 16 joules Adjustable speed £50.00 + £3.00 p&p (£62.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)

SAE for further details including Hy-Light and industrial Strobe Kits.

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p: £27.73.

SOLID STATE HEAT UNIT

Input 230/240V AC, Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case: £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

HEAVY DUTY MOTOR

Crouzet 115V/230V AC heavy duty 1RPM motor. Anticlockwise type B2/015. Size 68mm, diameter x 55mm long. Shaft 6mm diameter x 20mm long. Price inc VAT & p&p: £18.86.

RHEOSTAT

50W 2 ohm 5 amp ceramic power rheostat. price inc VAT & p&p: £10.61

MICROSWITCH

Pye 15 amp changeover lever microswitch, type S171. Brand new, price £ for £7.06 inc VAT & p&p

NMS = NEW MANUF SURPLUS
R&T = RECONDITIONED AND TESTED

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

081-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10

Showroom open
Monday/Friday

VISA
Ample
Parking Space

WHETHER ELECTRONICS IS YOUR HOBBY OR YOUR LIVELYHOOD . . . YOU NEED THE MODERN ELECTRONICS MANUAL



ORDER NOW
ON 10 DAYS
FREE APPROVAL

The essential reference Work

- Easy-to-use format
- Clear and simple layout
- Regular updates
- Sturdy ring-binder
- News of latest developments
- Full components checklist
- Extensive data tables
- Detailed supply information
- Ready-to-transfer PCBs
- Comprehensive subject range
- Accurate assembly instructions
- Concise repair procedures

EVERYTHING YOU NEED TO KNOW ABOUT ELECTRONICS!

If the fascinating and fast-changing world of electronics is your livelihood, your study subject or simply your passion, the new revised edition of **THE MODERN ELECTRONICS MANUAL** is the reference work for you to have at your side.

The base manual contains information on the following subjects:

BASIC PRINCIPLES: symbols, components and their characteristics, passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, operational amplifiers, timers, physics for electronics.

CIRCUITS TO BUILD: construction techniques, radio, telephony, microcomputing, measuring instruments, vehicle electronics, security, audio, power supplies, electronic music (over 25 different projects).

REPAIRS AND MAINTENANCE: radio, television, audio/hi-fi, telephones.

DATA: diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors.

The manual also covers **Safety, Specialist Vocabulary with Abbreviations and Suppliers.**

OVER 1,000 pages, A4 format weighing over 3.5kg.

Now - at last - the most comprehensive reference work ever produced at a price you can afford, the new revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the essential information you need.

Over 1,000 pages of well-organised and clearly explained information is brought to you by an expert editorial team whose combined experience ensures the widest coverage.

Regular supplements to this unique publication, each around 160 pages, mean that you will always be kept abreast of the latest developments from the UK, USA and Europe as they occur

ALL-IN-ONE AND EASY-TO-USE

A sturdy ring-blnder allows you to use the manual on your workbench. The looseleaf format also means you can slot in the regular updates as they arrive – so all your information is there at a glance.

EXTENSIVE GLOSSARY

Should you come across a technical word, phrase or abbreviation you're not familiar with – simply turn to the glossary included in the manual and you'll find a comprehensive definition in plain English.

REGULAR UPDATES

Unlike a book or encyclopedia, the manual is a living work – continuously updated by new material. Recent or upcoming supplements include radio, superconductors, electric motors, basic electronic building blocks for beginners which can be joined together to construct elaborate circuits, filters, IBM PC and compatibles (including use of PC cards). Supplements are sent to you approximately every two months.

Each supplement contains approximately 160 pages – all for only £23.50 + £2.50 p&p. You can of course return any supplement which you feel is superfluous to your needs.

RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular articles in our updating supplements. Our unique updating system is based on answers from readers request questionnaires. Through this service you are able to let us know exactly what information you require in your manual. You can also contact the editor directly in writing if you have a specific technical request or query relating to the manual.

ASSEMBLING ...

There's nothing to beat the satisfaction of creating your own project. From basic principles to circuit-building, the manual describes clearly, with appropriate diagrams, how to assemble radios, loudspeakers, amplifiers, micro-computers and measuring instruments.

The new revised edition of The Modern Electronics Manual contains practical, easy-to-follow instructions for building and programming your own computer. It shows you how to make fun gadgets such as a remote control door opener and a digital rev. counter for your car. It also tells you how to construct useful devices like test gear, security and baby alarms – plus – many more popular devices.

**Wimborne Publishing Ltd., 6 Church St, Wimborne, Dorset BH21 1JH
Tel: 0202 881749 Fax: 0202 841692**



THE MODERN ELECTRONICS MANUAL

New Revised Edition of Basic Work: Now contains over 1,000 pages of information.

Regular Updates: Approximately 160-page supplements of additional information which are forwarded to you immediately on publication. These are billed separately and can be discontinued at any time.

Presentation: Durable looseleaf system in large A4 format (197mm × 210mm)

Price of the Basic Work: £39.95 + £5.50 p&p (to include a recent supplement).

YES please send me on 10 days free approval **THE MODERN ELECTRONICS MANUAL**. If I decide to keep the manual, I shall then pay **only £39.95** plus £5.50 postage and packing at the end of the 10 days approval period. I shall also receive the appropriate Updating Supplements several times a year. These are billed separately and can be discontinued at any time.

FULL NAME
(PLEASE PRINT)

ADDRESS.....

..... POSTCODE

I AM OVER 18

SIGNATURE.....

(Parent or guardian must sign if under 18)

ORDER FORM

Simply complete and return the order form to the following address

**The Modern
Electronics Manual
Wimborne Publishing Ltd
6 Church Street
Wimborne Dorset BH21 1JH**

OVERSEAS ORDERS: All overseas orders must be prepaid but are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the manual return it within a month for a refund of the purchase price (you do have to pay the postage). Add the following amounts to the price of the manual to cover postage:

- EIRE £10.50 (air mail only)
- EUROPE (including C.I.S.) £21.00 (air mail only)
- MIDDLE EAST/FAR EAST/INDIA } £20 surface
- AFRICA/SOUTH AFRICA } £37 air
- SOUTH AMERICA }
- REST OF THE WORLD £25 surface, £31 air


Note surface mail can take around 8 weeks to some parts of the world. Each manual weighs about 4.5kg when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.

INFORMATION TECHNOLOGY

AND THE NATIONAL CURRICULUM

T. R. de VAUX BALBIRNIE

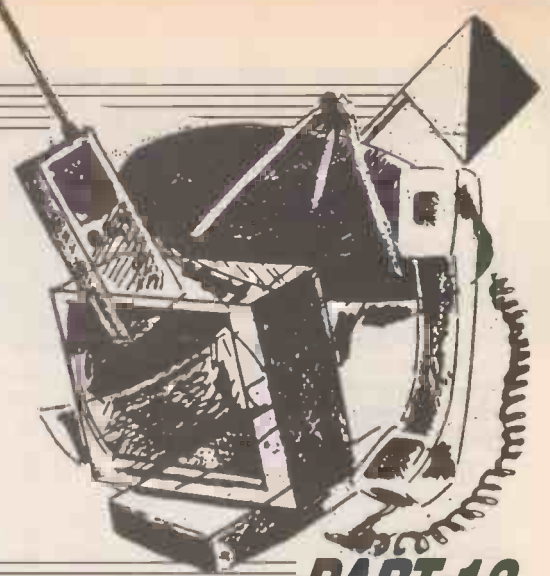

PART 12

THIS is the final article in a 12-part series concerning Information Technology, electrical measurements, electrical calculations and related matters in the Science National Curriculum.

This month we shall look at Ohm's Law, power calculations and potential dividers. We shall also discuss measuring instruments – ammeters, voltmeters and oscilloscopes – how they are used in circuits and the degree of trust we should put in their readings.

In an effort to avoid mathematical detail there have been, up to now, a few things left unsaid. The National Curriculum requires a knowledge of Ohm's Law and the ability to do power calculations. Students pursuing GCSE science, electronics, and technology courses need to be able to do this type of calculation.

ELECTRICAL QUANTITIES

There are two main electrical quantities which may be measured directly – current and voltage. Looking at it very simply, current is the flow of electric charge in a circuit (that is, it is related to the number of electrons passing a point per second). Electric current, then, is rather like water current.

Voltage, on the other hand, is the driving force which pushes the electrons along – this may be provided by a battery, dynamo, solar cell, etc. Voltage may be likened to the height through which water falls to make it flow.

It may be helpful to refer to Parts 2 and 6 in this series (December, 1991 and April, 1992 issues) since in these there was some basic information about simple series and

parallel circuits. To measure the current (I) flowing through, for example, a bulb we use an ammeter connected in series with the circuit (see Fig. 1). The meter will then give a reading in amps (A). In practice the meter will often be a milliammeter measuring in thousandths of an amp (mA) or a microammeter reading in millionths of an amp (μ A).

To measure voltage a voltmeter is used, connected in parallel with the circuit component in question. Fig. 2 shows three separate voltmeters being used to measure the voltage (V) across the battery and across each bulb in the circuit. Students should be encouraged to build these circuits and take readings, several things emerge. Firstly the current is found to be the same throughout a series circuit.

The ammeter could be placed anywhere and the reading would be the same. One common mistake is to think that the current becomes weaker as it flows through the various components. A practical point about traditional pointer-on-scale ammeters and voltmeters is that they are polarised – they must be connected the correct way round or the pointer will try to move backwards.

CURRENT IN A PARALLEL CIRCUIT

In a branched circuit (for example, the parallel circuit shown in Fig. 3) the current entering a junction is found to equal the current leaving. Suppose, for example, the

readings A1, A2 and A3 on the milliammeters are 20mA, 15mA and 5mA respectively. The current flowing into point X (20mA) is the same as the total current flowing out of it i.e. (15mA + 5mA).

If we measure the voltage directly across the battery and across the individual circuit components (see Fig. 2) it is found that the supply voltage is equal to the sum of the voltages across the bulbs. For example, if the battery voltage is 6V, it may be found that 3.5V exists across one bulb and 2.5V across the other one.

Perhaps the biggest mistake made by students is to talk about the "voltage flowing" in a circuit. This is nonsense and anything which can be done to prevent it would be welcomed by the examinations boards. Unfortunately, "voltage flowing" is a term often seen in the media and even used by professionals who should know better. Only charge or current flow. Students must always be encouraged to say "voltage across".

OHM SWEET OHM

Ohm's Law relates the three main quantities – current, voltage and resistance. Resistance (measured in ohms, Ω) is a measure of how difficult it is for current to flow in circuit. Taking the water analogy one stage further, a high resistance is rather like a narrow-bore hosepipe – the water flows through it with difficulty. Large resistances are often expressed in thousands ($k\Omega$) or millions ($M\Omega$) of ohms.

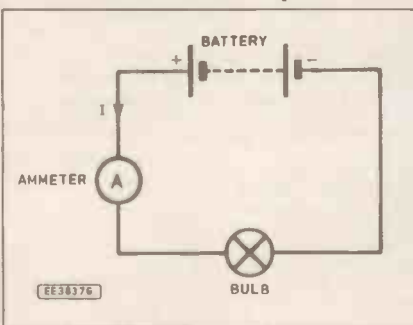


Fig. 1. Connecting an ammeter in circuit.

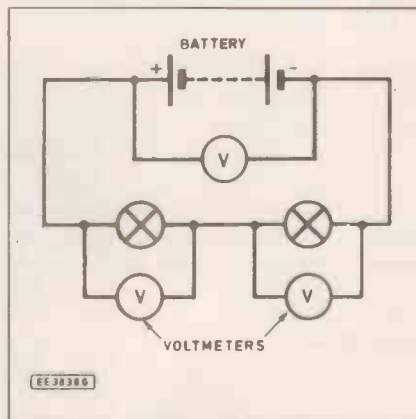


Fig. 2 Voltmeters connected in a circuit.

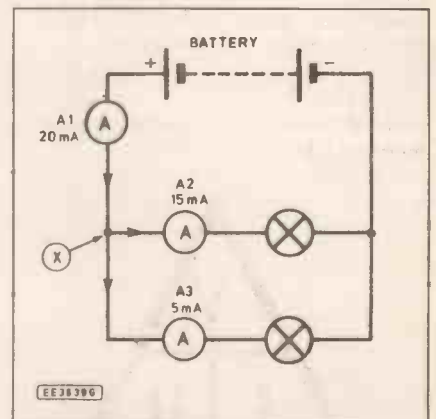


Fig. 3. Currents at a junction.

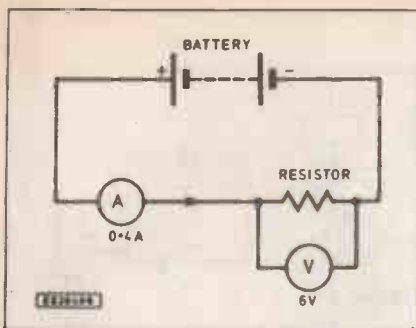


Fig. 4. Measuring voltage across a resistor.

The resistance of a circuit component is equal to the voltage across it divided by the current flowing through it – this is called *Ohm's Law*. Consider the circuit shown in Fig. 4. Suppose the current flowing through the resistor is 0.4A and the voltage across it 6V. The value of the resistor is given by:

$$R = V/I = 6/0.4 = 15 \text{ ohms}$$

We must be careful if the current is expressed in *milliamperes* (mA) or *microamperes* (μ A) instead of amps. These would need to be converted into amps (by dividing by one thousand or one million respectively) before being used in the formula above. Similarly, if a voltage is given in mV (millivolts) this must be divided by 1000 to turn it into volts.

Examples: A 16V supply is connected to a buzzer and a current of 20mA flows. Find the resistance of the buzzer.

$$R = V/I = 16/0.02 = 800 \text{ ohms}$$

A 3V battery is connected to a resistor and the current flowing is found to be 15 μ A. Find the resistance.

$$R = V/I = 3/0.000015 = 200,000 \text{ ohms (200k}\Omega\text{)}$$

A 20mV supply is connected to a coil of wire and a current of 0.1A flows. Find the resistance of the wire:

$$R = V/I = 0.02/0.1 = 0.2 \text{ ohms}$$

TRIANGLE

The foregoing is all very well if it is the resistance which is needed, knowing the current and voltage. However, it often happens that we wish to find the current or the voltage knowing the other two. For this, we use *swapped around* versions of *Ohm's Law*. Mathematically-inclined readers will have no difficulty seeing that these alternative versions are true:

$$I = V/R \text{ and } V = I \times R$$

Some students find *The Triangle* a useful memory aid:



The idea is to cover up the quantity to be found and *The Triangle* will tell you what you need to do with the other two.

In any *Ohm's Law* calculation, we must first be clear which quantity out of V, I and R we wish to find, check that we know the other two, then use the appropriate equation. Students should get into the habit of (a) stating the correct version of the formula they are going to use, (b) putting the numbers into it, (c) working out the numerical answer and (d) putting the correct unit at the end. In this way, if an error is made, any marks due for the *method* will be gained – in practice, this could be most of the marks.

Use *The Triangle* to check the following examples:

Examples: A 12V supply is connected to a motor of resistance 24 ohms. Find the current flowing in the motor windings.

$$I = V/R = 12/24 = 0.5A$$

A coil of wire of resistance 200 ohms has a current of 20mA flowing through it. Find the voltage of the supply.

$$V = I \times R = 0.02 \times 200 = 4V$$

(Note that *The Triangle* here puts I and R on the same line and this means *multiply*.)

CHARGE AND ENERGY

Charge (Q) is the quantity of electricity flowing through a circuit component. Its unit is the coulomb (C). To calculate charge, multiply the current by the time, t, (in seconds) during which it flows.

Example: A current of 2A flows through a lamp for 2 minutes (120 seconds). Find the total charge flowing.

$$Q = I \times t = 2 \times 120 = 240C$$

When electricity flows through a component, energy is converted into some other form or forms. In the case of a lamp it is *light* and *heat* energy which are produced. Energy (E) is measured in joules (J). When 1C is carried through 1V, 1J of energy is converted. The following equation then holds true:

$$E = V \times Q$$

Examples: 240C flows through a bulb when 12V is measured across it. What is the total energy converted into heat and light?

$$E = V \times Q = 12 \times 240 = 2880J$$

POWER TO THE PEOPLE

A similar equation to *Ohm's Law* is used if we wish to find the *electrical power* (P) of a piece of equipment. Power is expressed in *watts* (W) and is a measure of the amount of energy converted per second by the device.

The formula used for *electrical power* must not be confused with *Ohm's Law*. Whereas *Ohm's Law* relates Voltage, Current and Resistance, the power formula relates Voltage, Current and Power. This is the Power Formula:

$$P = I \times V$$

Examples: A soldering iron is connected to the 240V mains supply and a current of


100mA flows. Find the power of the soldering iron.

$$P = I \times V = 0.1 \times 240 = 24W$$

As with *Ohm's Law*, there are also *swapped around* versions of the power formula and we use the appropriate one for the job. These are:

$$I = P/V \text{ and } V = P/I$$

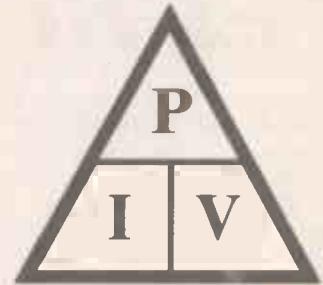Again, *The Triangle* comes to the rescue:



This is used like the *Ohm's Law* triangle – cover over the quantity you want to find. Check *The Triangle* in the following:

Example: a 750W electric iron is connected to a 250V supply. Find the current flowing.

$$I = P/V = 750/250 = 3A$$

A 10W lamp has 0.2A flowing through its filament. Find the voltage of the supply:

$$V = P/I = 10/0.2 = 50V$$

We must be careful when the power is expressed in *kilowatts* (kW) that is, *thousands* of watts. This must be *changed* into *watts* (by multiplying by one thousand) before using it in the power formula.

Example: a 2.4kW electric kettle is connected to the 240V mains. Find the current flowing in the element.

Firstly, 2.4kW = 2400W then:

$$I = P/V = 2400/240 = 10A$$

We may use the above formula to calculate *fuse values* – the correct fuse to be used in a mains plug, for example.

Example: a 600W coffee-maker is connected to the 240V mains supply. What value of fuse should be used in the plug?

$$I = P/V = 600/240 = 2.5A$$

– so a 3A fuse will be adequate.

TWO STAGES

Sometimes we need a *two stage* calculation to solve a problem – that is, *Ohm's Law* followed by the *power formula*.

Example: A heating coil, having a resistance of 100 ohms, is connected to a 50V supply. Find the power of the heater.

We notice that neither *Ohm's Law* nor the power formula can find this directly. However, *Ohm's Law* may be used to find the current and then the power formula may be applied.

$$I = V/R \text{ (Ohm's Law)} = 50/100 = 0.5A$$

$$\text{Then } P = I \times V \text{ (power formula)} = 0.5 \times 50 = 25W$$

In electronics work, the power formula

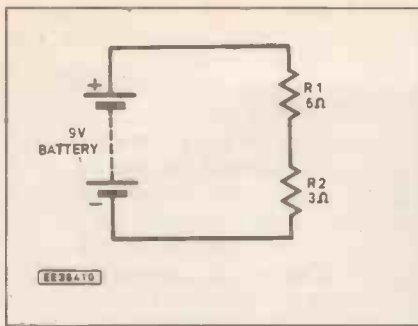


Fig. 5. A potential divider.

is often used to select the correct power rating of a resistor to make sure that it will not burn out or overheat in service. Small resistors of the type normally encountered in project work often have a power rating of 0.25W or 0.5W.

Example: A 220 ohm resistor is to be connected to a 9V supply. Find the minimum adequate power rating of the resistor.

$$I = V/R \text{ (Ohm's Law)} = 9/220 = 0.041A$$

$$P = I \times V \text{ (power formula)} = 0.041 \times 9 = 0.37W$$

Thus, we could use a 0.5W rating resistor but a 0.25W one would overheat.

Engineers doing this sort of calculation regularly use combined equations which work in one operation. However, for occasional use, learning them is not really worthwhile.

POTENTIAL DIVIDERS

Several times in this series we have touched on the subject of *potential dividers* but have avoided exploring the topic in any detail. However, students do need to know a little about it.

A potential divider (sometimes called a voltage divider) is formed when two (or more) resistors are connected in series with a power supply. It is almost always sufficient to consider only *two* resistors in a potential divider and this is what we shall do here. Since a potential divider is a series circuit, we find that some of the supply voltage appears across one resistor and the rest across the other one.

A potential divider circuit consisting of the pair of resistors, R1 (6Ω) and R2 (3Ω), connected to a 9V battery is shown in Fig. 5. It is a relatively simple matter to calculate the voltage appearing across either resistor. In this example, the total resistance is 9 ohms. Since a 9V supply is used, the current flowing through the resistor chain can be found using Ohm's Law:

$$I = V/R = 9/9 = 1A$$

Remembering that the same current – 1A – flows through *both* resistors, the voltage appearing across the 6 ohm resistor can be found, again, by using Ohm's Law:

$$V = I \times R = 1 \times 6 = 6V$$

and the voltage across the 3 ohm resistor will be:

$$V = I \times R = 1 \times 3 = 3V$$

As expected, the individual voltages add up to 9V – the voltage of the supply.

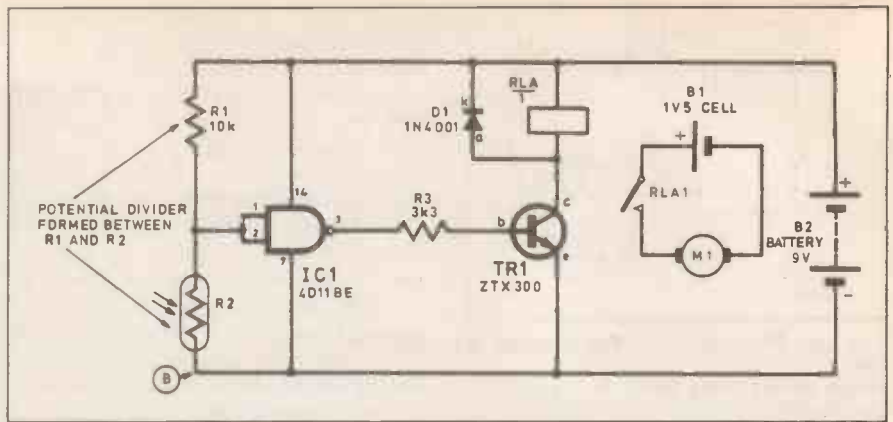


Fig. 6. Motor control circuit.

We also notice that the voltage splits into parts in *proportion to the individual resistances* – that is, there is twice as much voltage appearing across the 6 ohm resistor as the 3 ohm one.

In simple examples it is often possible to find these voltages by common sense without the need to do a calculation. Suppose in a potential divider one resistor had a value of 20 ohms and the other 4 ohms and they are connected across a 12V supply. There must be *five times* more voltage across the 20 ohm resistor than across the 4 ohm one. There must therefore be 10V across the 20 ohm resistor and 2V across the 4 ohm one.

Potential dividers are useful in *control systems*. Remember the motor control circuit which was used in Part 7 of the series (May, 1992 issue) – this is reproduced again as Fig. 6. A potential divider is formed between fixed resistor, R1, and light-dependent resistor, R2. When the light level falls, the resistance of the LDR rises. The voltage appearing across the LDR will therefore also rise. This is used to operate the NOT gate in the manner discussed at the time.

THE POTENTIOMETER

Consider the potentiometer circuit shown in Fig. 7 – a potentiometer is familiar as the volume control in a radio, television or amplifier. Here, a sliding contact can be moved along a track. The track may be *circular* (rotary potentiometer) or *straight* (linear potentiometer). The resistance of the potentiometer, as marked on the body, is the total resistance of the track measured from end to end (i.e. between points A and C).

Imagine we have a 1 kilohm (1k) potentiometer with the sliding contact set at the middle of the track – Fig. 7(a). There will then be 500 ohms above and 500 ohms below the sliding contact. This may be regarded as a potential divider with equal "arms". If the supply voltage is 9V as shown, then there will be 4.5V between points C and B.

If the sliding contact is moved to a higher position (Fig. 7b), the voltage between points C and B will rise (because there is a higher resistance between these points) and if it is taken lower (Fig. 7c), there will be a smaller voltage. In this way, a potentiometer can "tap off" a smoothly-varying voltage from zero to full supply voltage. This is useful in many circuits. Students should build the potentiometer circuit shown in Fig. 7 with a voltmeter connected as shown to check its operation for themselves.

THE WHOLE TRUTH

Supposing we wish to use a voltmeter to check the voltage across the lower 100k resistor in the potential divider shown in Fig. 8(a). Before the voltmeter is connected, the potential divider has equal arms so there will be equal voltages across each – that is, 3V. When the voltmeter is connected, there is now a problem because the voltmeter itself has resistance – in this case 50k – and this is connected in parallel with the lower arm (Fig. 8b). This, in effect, alters the potential divider and leads to a false reading. We say that the potential divider has been *loaded*.

Where two resistors, R1 and R2, are connected in parallel, their combined resistance (that is, the single resistor

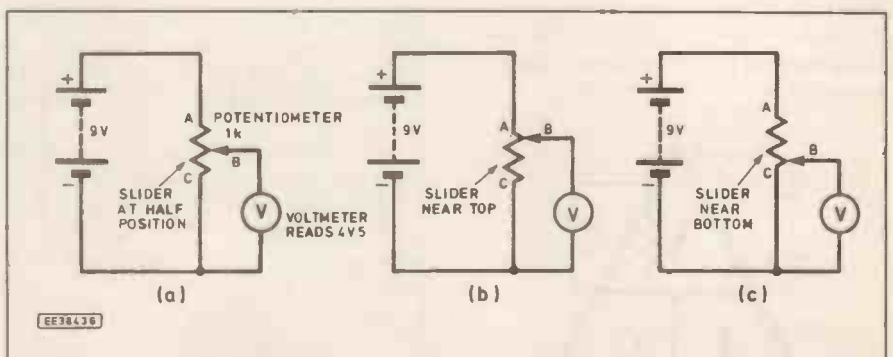


Fig. 7. Potentiometer circuits.

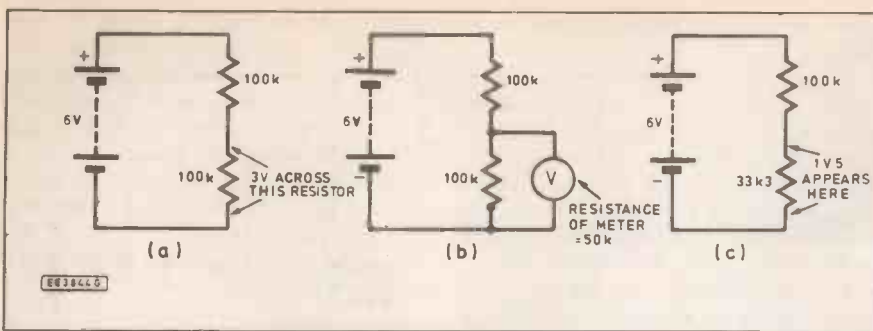


Fig. 8. Loading a potential divider.

which could replace them), R , is given by the formula:

$$1/R = 1/R_1 + 1/R_2$$

Applying this to the voltmeter and lower arm of the potential divider in Fig. 8b:

$$1/R = 1/100,000 + 1/50,000 = 0.00001 + 0.00002 = 0.00003$$

$$R = 1/0.00003$$

$$R = 33,300 \text{ ohms (33.3k)}$$

The point to note here is that the presence of the voltmeter has effectively reduced the value of the lower limb of the potential divider. The total resistance is now 133,300 ohms so the current flowing from the 6V battery will now be:

$$I = V/R = 6/133300 = 0.000045A$$

The voltage appearing across the voltmeter (and hence the reading) will therefore be:

$$V = I \times R = 0.000045 \times 33300 = 1.5V$$

This is important. The voltage without the meter present was 3V. Now that the meter is included, the reading is only 1.5V i.e. the reading is *distorted*. This does not mean that the meter is *inaccurate* – it provides a faithful reading of the voltage which now exists – not as it was before it was connected.

DISTORTION

This distortion is rather like a school inspector coming round to observe a lesson. The fact that he or she is in the classroom means that the lesson will not proceed in the way it would have done had he or she not been there. That is to say, *the very thing which was to be observed has changed*.

Users of voltmeters must always be on their guard for this. Whenever a voltage is measured across a resistor, perhaps in the course of fault-finding, it may be that the reading is not true. Further calculation will show that, providing the resistance of the meter is much greater than the other

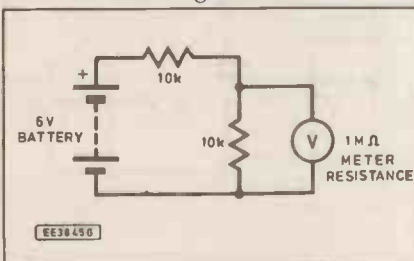


Fig. 9. Using a high resistance voltmeter.

resistors in the potential divider, the loading effect will be small. The worst distortions occur when the voltmeter has a resistance approaching – or even less than – the other resistor values as in Fig. 8.

To illustrate this, suppose we use a meter with a resistance of 1M – a *high-resistance* voltmeter. The meter is now placed in the potential divider circuit shown in Fig. 9. to measure the voltage across the 10k resistor in the lower arm. Before the voltmeter is connected there will be an equal split of supply voltage between top and bottom arms – i.e. 3V. With the voltmeter present we must first calculate the effective resistance of the voltmeter and 10k resistor in parallel:

$$1/R = 1/R_1 + 1/R_2 = 1/1000000 + 1/10000 = 0.000001 + 0.0001$$

$$1/R = 0.000101$$

$$R = 1/0.000101 = 9,901 \text{ ohms}$$

The total resistance is now 19,901 ohms so we can now calculate the current flowing in the potential divider chain:

$$I = V/R = 6/19901 = 0.0003A$$

So the voltage recorded by the meter is:

$$V = I \times R = 0.0003 \times 9901 = 2.97V$$

Here, the voltmeter has made very little difference to the value of the lower limb of the potential divider and hence to the voltage existing across it. This is because the resistance of the voltmeter is very high.

As a general rule, the higher the resistance of a voltmeter, the better. Electronic voltmeters now commonly have a resistance of 10M and these will cause little disturbance unless, of course, the other resistors in the circuit are of this order of magnitude and, unfortunately, this may very well be the case with modern equip-

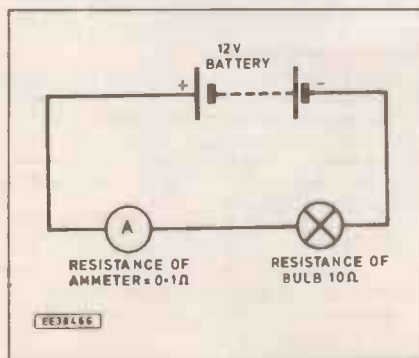


Fig. 10. Effect of an ammeter in circuit.

ment! Pointer-on-scale voltmeters have a lower resistance and their readings must be treated with caution.

AMMETERS

Like a voltmeter, an ammeter also causes a disturbance to the circuit in which it is connected. The ammeter has a resistance of its own and the current being measured flows through this as well as the other circuit components. This reduces the current to a value less than it would have been if the ammeter had not been there.

Unlike a voltmeter, it can be seen that there will be least disturbance to the "true" current if the ammeter has as *low* a resistance as possible – that is, a resistance very low compared with other resistances in the circuit. Refer to Fig. 10. Here an ammeter of resistance 0.1 ohms is measuring the current flowing through a bulb of resistance 10 ohms, from a 12V battery. Before the ammeter is connected, the current will be:

$$I = V/R = 12/10 = 1.2A$$

With the ammeter in the circuit, the total resistance is now 10.1 ohms so the current will be:

$$I = V/R = 12/10.1 = 1.19A$$

Thus, the ammeter has made very little difference to the current flowing in the circuit. This exercise should be repeated using a meter resistance of 1 ohm instead of 0.1 ohm and the results compared.

SCOPE FOR STUDY

One of the most useful instruments available is the *oscilloscope*. This can be used as an a.c. or d.c. voltmeter, as a timing device and also to display waveforms. It is therefore a very *versatile* instrument. However, the information obtained from an oscilloscope may also need *interpretation*.

An oscilloscope appears rather like a small television set but often it has a *green* screen. The screen has a *graticule* in front marked off rather like graph paper in squares (divisions) and measurements can be made from this.

When first switched on, we normally see a spot of light or a horizontal line on the screen. If it is a spot of light, we need to turn on the *timebase* and this makes the spot sweep across the screen from left to right to give a line. A control can alter the sweep speed as required within wide limits – this is usually expressed in seconds per division. School oscilloscope timebase settings often vary between one second per division and one microsecond (one millionth of a second) or less per division.

At the slowest sweep speeds, the spot will be seen to move from left to right then suddenly re-appear (flyback) at the left-hand side of the screen to start another sweep. This display is familiar in hospitals as an electrocardiograph to monitor the heartbeat.

At slightly higher timebase speeds, the spot appears as a flickering line on the screen but at greater speeds the flickering

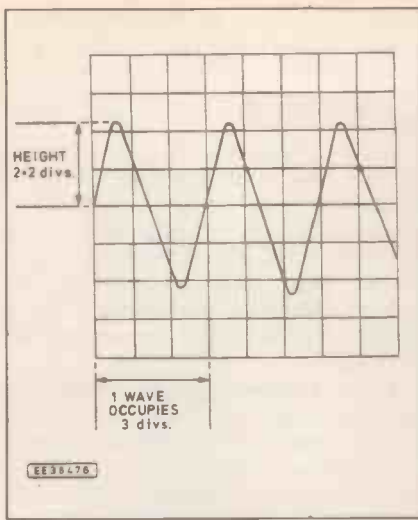


Fig. 11. An oscilloscope display.

disappears. We call the horizontal motion the *X* direction and various controls refer to it. For example, the *X*-shift moves the line to the left or right, *X*-gain makes the line longer or shorter, etc.

Y-WORRY

If all an oscilloscope did was move a spot or line in the *X*-direction this would not be very useful or interesting. However, by making connections to an input socket on the front panel, we can move the line in a *vertical* direction (called the *Y*-direction) at the same time. We can

also position it vertically using the *Y*-shift control.

A control on the panel (often marked "V/div") determines the *voltage* required at the input socket to move the line up or down by one division. This is called the *Y*-sensitivity. One very basic use for an oscilloscope is as a *voltmeter*. By connecting a battery or other supply to the input socket and adjusting the "V/div" switch to a convenient setting, the line will move up (or down) on the screen. By noting how far it moves on the graticule and by knowing the V/div. setting, the voltage may be calculated.

Example: A bulb is connected to a battery and the voltage across the bulb is found by connecting an oscilloscope across it. The *Y*-sensitivity switch is set to 2 V/div. The line moves up on the screen a distance of 3.4 cm. Find the voltage across the bulb:

$$V = 2 \times 3.4 = 6.8V$$

The input resistance of an oscilloscope is very high so it behaves as a near-perfect voltmeter. Note that the sweep speed is irrelevant for voltage measurements. The timebase is simply made fast enough to provide a flicker-free display.

Using an oscilloscope as a voltmeter may not seem very useful since an ordinary voltmeter could be used and would be easier to read. However, if the voltage to be measured was a.c. (alternating

current) rather than d.c. (direct current), *waves* would be displayed. It would now be possible to read off the *peak* (highest) value and, by looking at the *X*-calibration, the time taken for one wave (time period, *T*) could be found.

Consider the typical display shown in Fig. 11. Here, the timebase is set to 10ms per div. and the *Y*-sensitivity to 2V/div. The peak voltage and time period of the wave are found thus:

$$\text{Peak } V = V/\text{div.} \times \text{divs.} = 2 \times 2.2 = 4.4V$$

$$T = T/\text{div.} \times \text{divs.} = 0.01 \times 3 = 0.03s \text{ (30ms)}$$

We can find the *frequency*, *f*, of the wave (the number of waves per second measured in Hz) by using the formula:

$$f = 1/T$$

$$\text{In this case: } f = 1/0.03 = 33.33\text{Hz}$$

Apart from the above uses, we may use an oscilloscope as a display device. Various shapes of wave may be fed in and the result observed on the screen. This is invaluable for fault-finding – perhaps looking for distortion – in electronic circuits. □

That concludes the series. We hope it has been found enjoyable and useful either for general reading or as a source of information for school and college courses.

SHOP TALK

with David Barrington

Versatile Intercom

We do not expect too many problems to arise when shopping for parts for the *Versatile Intercom* as there is plenty of room for adaption.

The unijunction transistor should be fairly widely available, the one used in the model being purchased from Cricklewood Electronics (☎ 081 452 0161). The Listen/Talk toggle switch must be the biased "one way" type and is stocked.

The microphone insert used in the model was also bought from the above mentioned company. This is a electret condenser type having an impedance of 600 ohms, frequency response 50 to 20,000Hz and powered from a 1.5V supply. When soldering to the microphone insert be as quick as possible with the soldering iron as they definitely do *not* like heat!

The small cases used in the two prototype were obtained from Greenweld (☎ 0703 236363), code V216. As a point of interest we see they have just received a delivery of quantities of solar panels and kits.

If you opt for the mains operated version, remember to cover *ALL* solder joints to mains carrying leads, i.e. transformer connections, with insulating sleeving. The biased switch S1 must be mains rated and the connecting tags, once soldered of course, must also be covered with insulating sleeves. Do not forget to *omit* the lead from S1b to the push switch (shown in the battery version) for the mains model.

The inclusion of the additional supply smoothing capacitors C11 and C12 for the mains set-up was found to be necessary to reduce "mains hum".

Some additional interesting information supplied by the author is that the battery has been in use for over a year now. Also, to use the unit as a "baby alarm" simply replace the Listen/Talk switch S1 with a non-biased type.

Whistle Switch

Several changes have been made to the original prototype version of the *Whistle Switch* shown in the photograph of the article.

The UM3763 whistle switch i.c. is a special "custom" device and was purchased from one of the Maplin stores, code UJ47B (UM3763). The omnidirectional mic. insert was purchased from the same source, type EM-6; the EM-4 could also be used. The mic. insert has built in f.e.t., is rated at 1 kilohm impedance, frequency response of 50Hz to 8kHz and will run from 1.5V to 9V supplies. Identical ones, with the same spec., should be carried by most of our components advertisers.

The relay used in the prototype was fairly low rated and has been replaced by a miniature, high power, mains one. This relay has contacts rated at 240V a.c., 30V d.c., and current rating 10A d.c. resistive and 3A a.c. inductive. The coil operating voltage is from 9V to 19.2V and coil resistance is 320 ohms. This relay is listed by Maplin, code YX97F (10A Mains Rly).

As mains voltage and current may be present on the circuit board, depending on application, it is suggested that the copper tracks from the relay switching contacts be "thickened" by soldering lengths wires along their lengths. Alternatively, mains leads could be soldered direct to the switching contacts.

The printed circuit board is available from the *EE PCB Service*, code EE805 (see page 675).

Extended Range Capacitance Meter

We have only encountered one small problem likely to cause constructors concern when sourcing components for the *Extended Range Capacitance Meter* and that is the programmable unijunction. The 2N6027 seems to appear in only the Cricklewood, Greenweld and Electromall listings.

Unlike normal unijunctions, this three-pin device has its pinouts labelled k, g and a. To add to the confusion, Maplin list the BRY39 as an equivalent to the 2N6027, but this is a four lead device. To use as a programmable unijunction it tells you that the cathode gate (G_k) should not be used.

The panel meter used in the model is the 1mA 100 ohm type T24 from Electrovalue (☎ 0784 433603). However, identical dimensions and ratings appear in most of our component advertiser's current listings.

The printed circuit board for the capacitance meter is available from the *EE PCB Service*, code EE804 (see page 674).

Traffic Light System

Looking down the list of components for the *Traffic Light System*, everything seems straightforward until you come to the lighting circuits. The l.e.d.s and m.e.s. bulbs and holders should be stocked by most component suppliers, but the "grain of wheat" lamps may only be carried by the larger model shops.

When building up the "high current" lamp version it is important that the wiring to the lamps can handle the required current. The use of 6A mains flex or high current auto-wire (from motor spares shops) may be best here.

If powering the high current version from a car battery, a suitable in-line safety fuse *MUST* be included in the positive (+) lead from the battery. Note also the higher rating of the output terminal block TB2 and the high current rating of the relay contacts and on/off switch. It is important to connect the car battery *directly* to the relays and lamps.

The printed circuit board is obtainable from the *EE PCB Service*, code EE806 (see page 674).

Lights-On Warning

We cannot foresee any component sourcing problems for those wishing to build the car *Lights-On Warning* project. The Scotchlok connector and 3A auto-type wire can be purchased from most car spare parts counters.

The 12V piezoelectric sounder, is the type with an integral drive circuit and operates at a resonant frequency of about 2 to 3kHz.

Everyday Electronics, October 1992

LIGHTS-ON WARNING

T. R. de VAUX-BALBIRNIE



Essential for the absent-minded - an anti-theft facility too!

THE Lights-On Warning has been designed to serve those absent-minded readers who leave their car lights switched on and return to find the battery "flat".

If the lights are switched on and a door is opened, the Lights-On Warning gives a signal in the form of a high-pitched pulsing tone. This acts as a reminder to switch them off. If the lights are to be left on intentionally, then the warning is simply ignored since it will go off when the door is closed from the outside.

The circuit draws current from the car battery so needs no independent supply. With the lights off, the current requirement (continuous current drain) is 100µA approximately and this may be regarded as negligible. With the unit operating, the circuit requires 15mA approximately.

The whole device is mounted in a plastic box size 75mm x 50mm x 25mm with a piece of screw terminal block mounted on the base to which the external connections are made. There is also a two-position switch on the side to select the operating mode - *normal* or *anti-theft*. The purpose of this will be described presently.

The car must be fitted with the usual type of courtesy light(s) which operate when a door is opened so this point should be checked before beginning construction work. Check also whether the car has a delay unit or other modification to the courtesy light circuit. If it has, the Lights-On Warning may not work.

ANTI-THEFT FACILITY

When the Normal/Anti-Theft switch is set to the *anti-theft* position, a warning is given when a door is opened irrespective of whether the lights are on or not. Thus a thief on opening the door will trigger the unit, hear the warning sound, and assume that some more sophisticated circuit or alarm has been put into action.

In practice, this usually means that he will leave the car quickly and try his luck elsewhere. Most car break-ins are of the opportunist kind and anything out of the ordinary is likely to deter a potential thief.

If the circuit is left in anti-theft mode by mistake, this will be self-checking since the user will realize this when the door is next opened and the warning sounds. The anti-

theft switch could be omitted if desired - if, for example, the owner has fitted a real car alarm.

HOW IT WORKS

As stated previously, this circuit is triggered by the existing interior light (courtesy light) circuit. Fig. 1 shows the usual arrangement. Switch S1 is one of two or more spring-loaded normally-closed switches mounted in the car door pillars.

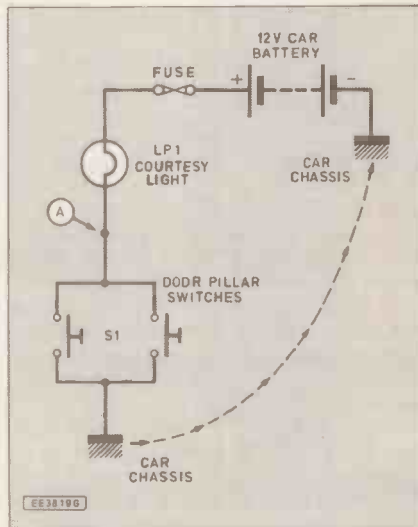


Fig. 1. Vehicle interior courtesy light circuit.

One contact of each switch is permanently connected to the car chassis ("earth"). The negative car battery terminal is also connected to the car body.

The doors, when closed, press the switches and hold their contacts in the *open* position. Current is therefore prevented from flowing from the car battery. When a door is opened, one of the sets of door switch contacts are closed by spring pressure and a circuit is completed from the battery positive terminal through the existing fuse, courtesy light bulb(s) LPI and switch S1 hence to the battery negative terminal via the car bodywork (dotted line).

With S1 contacts open (door closed) point A will have a voltage of +12V (via LPI) between itself and the car chassis. When the

contacts close (door open) the voltage falls to zero since Point A is now connected direct to the car chassis. It is these voltage levels which operate the device.

CIRCUIT DESCRIPTION

The full circuit diagram for the Lights-On Warning is shown in Fig. 2. The existing car courtesy light section appears to the left of the dotted line, but note that only one door pillar switch is shown.

The circuit is built around a bipolar 555 timer IC1. With switch S1 set to *normal* and with the car sidelights on, operating current is supplied from the lighting circuit via fuse, FS1 and diode, D1. With S1 set to *anti-theft*, current is supplied direct from the car supply.

The timer IC1 is used in astable mode. This means that the output (pin 3) switches on and off continuously as long as a supply is connected and pin 4 (reset input) is high (near positive supply voltage).

The rate at which pulses are provided depends on the values of fixed resistor, R3, preset potentiometer VR1 and capacitor, C2. VR1 will be adjusted at the end of construction to provide four pulses per second approximately - this providing the "right" sound.

The reset pin (4) of IC1 is kept low (negative supply voltage) while the vehicle doors are closed to disable the i.c. and so prevent it from providing pulses. This is done by the inverting action of transistor, TR1 and associated components.

With the doors closed, the pillar switches are held in the open condition. Current then flows to TR1 base through the existing fuse, courtesy light bulb and resistor, R1. This turns the transistor on and collector current flows through resistor, R2. The collector is now low and this low state is applied to IC1 pin 4.

When a door is opened, the pillar switch contacts close and point A is effectively connected to the car chassis. TR1 base receives no current and the transistor turns off. IC1 pin 4 is now high and IC1 is enabled - pulses are then provided at pin 3 and the audible warning device, WD1, connected to it operates.

Note that with the door closed, TR1 base current is insufficient (100µA approximately) to make the car interior courtesy lamp glow. It is essential to buy the correct type of audible warning device as specified in the components list. Devices which require external drive circuitry would not work in this circuit.

PROTECTION

Diode, D1, protects the circuit from the effects of reversed battery polarity if connected up incorrectly to the car system. Fuse, FS1, provides protection in the event of excessive current being drawn from the car battery – perhaps due to a short-circuit formed by faulty construction. *For safety reasons, it is therefore essential* to include this fuse in the circuit.

Capacitors C2 and C3 are necessary for

the board to clear the lid securing pillars in the specified box (see photograph). Follow with the track breaks (do not forget those between the rows of IC1 pins) and solder the four topside inter-strip link wires into position as indicated.

Mount the on-board components noting that capacitor C3 and diode D1 are polarity-sensitive and must be connected the correct way round. Take care also over the orientation of transistor, TR1.

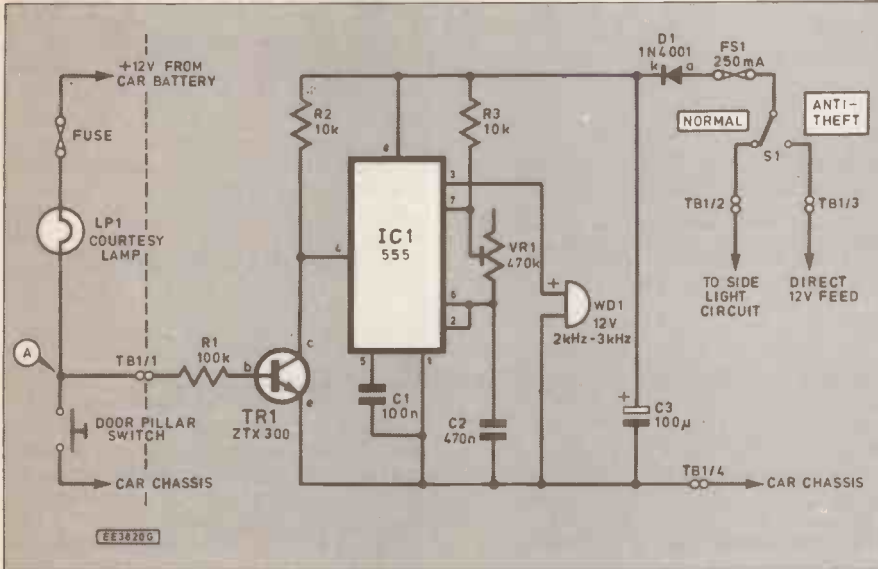


Fig. 2. Complete circuit diagram for the Lights-On Warning. The circuit to the left of the dotted line is the car "courtesy light" section.

stable operation of IC1. Note that if no anti-theft facility is required, switch S1 is simply omitted and the fuse FS1 connected directly to the terminal block point TB1/2. TB1/3 is then redundant.

CONSTRUCTION

Construction of the Lights-On Warning is based on a circuit panel made from a piece of 0.1in. matrix stripboard, size 10 strips \times 17 holes. Full topside component layout and underside details of breaks in the copper tracks are shown in Fig. 3.

Begin construction by drilling the two mounting holes and filing off the corners of

Complete the circuit panel by soldering 8cm pieces of light-duty stranded connecting wire to copper strips D, F and I on the left-hand side and to strips C and J on the right-hand side. Insert the i.c. into its socket with the correct orientation and adjust preset VR1 to approximately mid-track position.

Prepare the box by drilling holes in the base to align with those already made in the circuit board, for the fuseholder, audible warning device (depending on the type) and switch, S1 (if required). Drill two holes in the base of the box for the four-section (three-section if S1 has been

COMPONENTS

See
SHOP
TALK
Page

Resistors

R1 100k
R2, R3 10k (2 off)
All resistors 0.25W 5% carbon.

Potentiometer

VR1 470k sub-min. preset, vertical

Capacitors

C1 100n ceramic
C2 470n ceramic
C3 100 μ p.c.b. elect., 16V

Semiconductor

D1 1N4001 50V 1A rec. diode
TR1 ZTX300 npn silicon transistor
IC1 NE555V bipolar timer i.c.

Miscellaneous

S1 Miniature 2-way slide or toggle switch
WD1 12V piezoelectric audible warning device, with internal drive circuitry. 2kHz-3kHz operating frequency

FS1 25mm chassis fuseholder and 250mA fuse to fit
TB1 3A screw terminal block – 4 sections required (or 3 sections – see text).

Stripboard, 0.1in. matrix size 10 strips \times 17 holes; plastic box, size approx. 75mm \times 50mm \times 25mm; 8-pin d.i.l. socket; 3A auto-type wire; stranded connecting wire; Scotchlok car connectors; small fixings; solder, etc.

Approx cost
guidance only

£9

omitted) piece of screw terminal block TB1. Drill a hole to accommodate the wires passing through from the circuit panel to the terminal block.

Referring to Fig. 4, mount the remaining components using a piece of cardboard on the underside of the circuit board to provide some padding. Use small fixings for circuit board, terminal block, audible warning device and switch (if of this type) mounting.

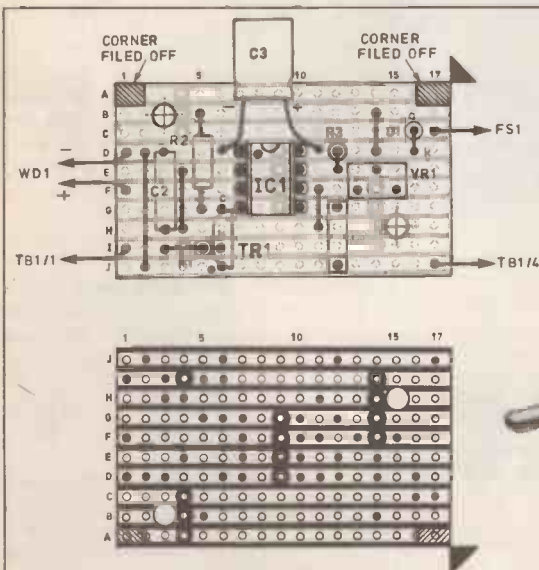


Fig. 3. Stripboard component layout and details of the breaks required in the underside copper tracks.

The completed unit. The interconnecting terminal block is fixed to the outside bottom of the case.



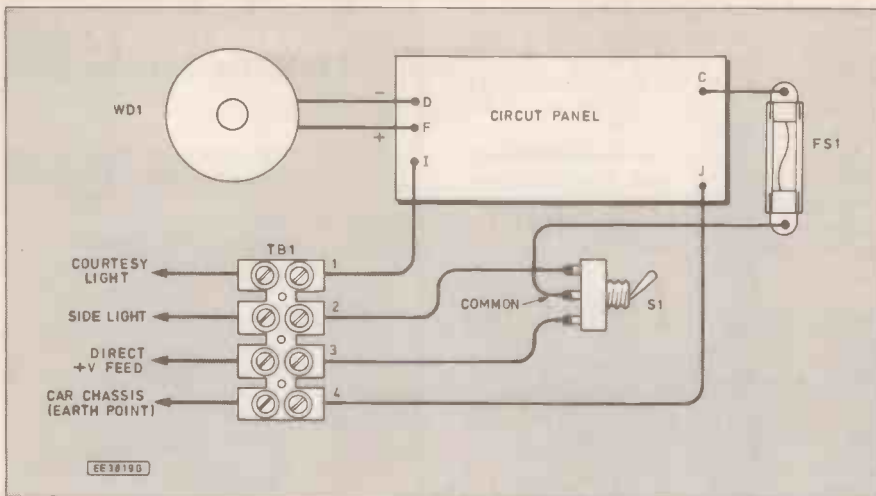


Fig. 4. Interwiring from the circuit board to the off-board components. A hole is drilled in the bottom of the case to allow leads through to the terminal block.

Complete the internal interwiring shortening any wires as necessary. Note that the audible warning device is polarity-sensitive so must be connected in the correct sense as indicated.

For audible warning devices having no fixing holes, an adhesive fixing pad is acceptable to attach it to the case but make sure that it is secure and will not break free in service. Drill a few small holes in the lid of the box above WD1 position to allow the sound to pass out.

Note that everything is mounted in the main section of the case with nothing on the lid. This minimises strain on the internal wiring. Leave the lid off the case for the moment.

TESTING

The unit may be tested and adjusted using a 9V battery as a power supply before installing it in the car. Note, however, that the sound will be slightly quieter than it will be when connected to the 12V car supply.

Connect short pieces of stranded wire to TB1 terminals one, two and four. Insert the fuse and switch S1 (if used) to normal operation. Connect TB1/2 to the positive terminal of the battery and TB1/4 to the negative one. The buzzer should bleep regularly.

Now, touch the wire connected to TB1/1 on to the battery positive terminal. The buzzer should go silent. Adjust preset VR1 to provide the pulse rate required.

INSTALLATION

Before installing the Lights-On Warning in the vehicle, first disconnect the car battery completely. For all external TB1 connections, it is essential to use light-duty auto-type stranded wire. Do not use any other

type. Where any wires pass through a hole drilled in metal, a rubber grommet must be used.

Referring again to Fig. 4, carry out the external wiring. Connect TB1/2 to the live side (that is, the side which is NOT connected to the car chassis – “metalwork”) of one of the sidelights.

This may be done by referring to the wiring diagram of the car, locating the correct colour of wire and making an in-line connection using a Scotchlok connector (these are available from car accessory shops). Do NOT use makeshift connecting methods such as breaking the wire and using p.v.c. taped joints.

Now make a similar connection between TB1/1 and the side of the courtesy light

which is connected to the pillar switch (this could be made at the pillar switch itself if this is easier). Note that some cars have separate courtesy light circuits – one for each side of the car. It so, wire into the driver's side.

If using the anti-theft facility, you will also need a connection which is “live” all the time (that is, independent of the ignition switch) made to TB1/3. This must be made at the outlet side of an existing low-current fuse at the fusebox. It would be possible to use the courtesy light live feed wire for this purpose – again, make an in-line connection using a Scotchlok.

Make an “Earth” (car chassis) connection to TB1/4. If a suitable existing earth point is not available nearby, drill a small hole in a metal part, scrape away the paint around it and use a small crimp-type eyelet secured with a self-tapping screw.


After making all TB1 connections, fit the lid and mount the unit in its final position using a small plastic bracket or a self-tapping screw through the back. Finally, reconnect the car battery and check the system for correct operation. It may be found necessary to tape over some or all of the holes if the warning is too loud.

If the unit is left in anti-theft mode for a long period, for example while on holiday, there will be a continuous current requirement of 15mA. A well-charged battery will be able to supply this for several months so there should be no problem.

Note that if the side lights are switched on and the courtesy light is operated manually, or if the courtesy lamp bulb blows, the unit will sound. This is unlikely to be of much concern.

No more flat batteries with the Lights-On Warning! □

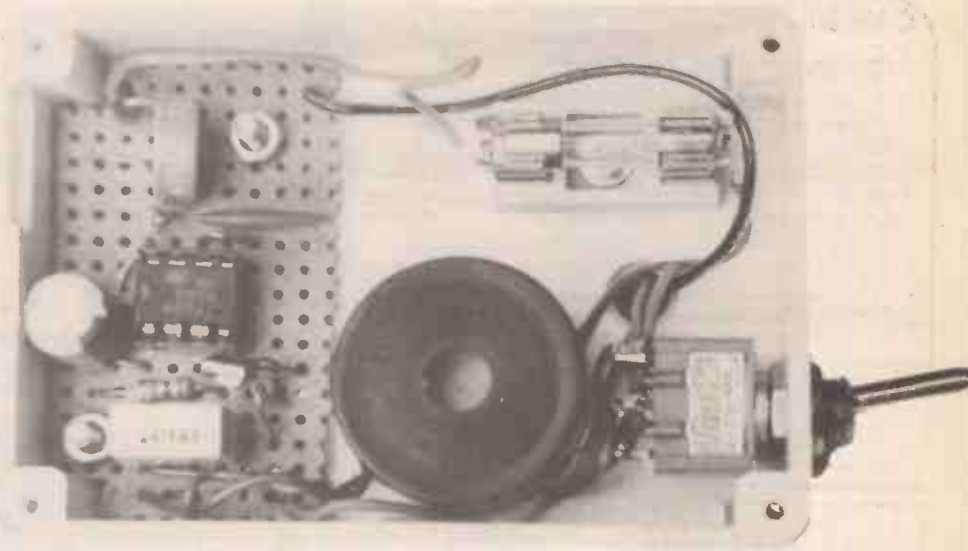Layout of components inside the small plastic case.




EVERYDAY WITH PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

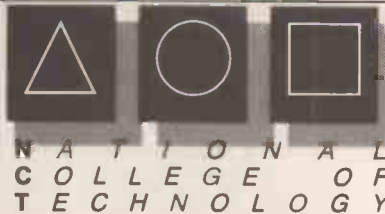Watch out for the new logo incorporating Practical Electronics next month – see the editorial page for more details.





DISTANCE LEARNING COURSES

The National College of Technology offer a range of packaged learning short courses for study at home or in an industrial training environment which carry national BTEC awards. Study can commence at any time and at any level enabling you to create a study routine to fit around existing commitments. Courses on offer include:

Analogue Electronics
Digital Electronics
Fibre/Optoelectronics
Programmable Logic Controllers

Tutor support and BTEC certification are available as options with no travelling or college attendance required. These very popular courses which are ideal for vocational training contain workbooks, audio cassette lectures, PCB's, instruments, tools, components and leads as necessary to support the theoretical and practical training. Whether you are a newcomer to electronics or have some experience and simply need an update or certification, there is probably a distance learning course ready for you. Write or telephone for details to:

National College of Technology
NCT Ltd., PO Box 11
Wendover, Bucks
Tel: (0296) 624270

CAMBRIDGE COMPUTER SCIENCE LIMITED

LCD modules	16 char by 1: £4.00, 20 char by 2: £6.00, 40 char by 1: £8.00
5.25" Disk Drives, 80 Trk, DSDD	£25.00 each
5.25" Disk Drives, 80 Trk, DSDD Used, No Wty	£9.00 each
(The £15.00 drives are sold on a strictly "as is" basis)	
5.25" Disks, DSDD, 48tpi, boxes of 10 (free disk cleaner with 5 boxes)	£3.00/box
Digital multimeter, 14 ranges, inc. leads & manual	£16.00 each
Apricot Disk drive PSU 5V @ 2.5A, 12V @ 2A	£10.00 each
5V @ 6A PSU	£4.90 each
5V @ 10A PSU	£8.40 each
Disk Drive Data lead BBC Micro to Disk Drive(s)	Single 2.00 Dual £4.00 each
Disk Drive Power lead BBC Micro to Disk Drive(s)	Single 2.00 Dual £4.00 each
8086 CPU chips	£2.00 each
Z80A CPU, CTC, PIO	£1.20 each; DMA £2.00; £4.50 all 4
27128 EPROMS (EX equipment)	£1.20 each or £3.00/5
256K DRAM (EX equipment)	£0.40 each
1Mbit-10 DRAM (EX equipment)	£1.40 each
256K Byte DRAM Modules, removed from equipment	£6.00 each
16, 18 & 20 pin dll low profile IC sockets 0.3" wide	£0.40/10; £3.00/100
22 & 24 pin dll low profile IC sockets 0.4" wide	£0.40/10; £3.00/100
24, 28, 32, 40 & 48 pin dll low profile IC sockets 0.6" wide	£0.40/10; £3.00/100
Circuit tester, finds faults in TTL & CMOS logic circuits, inc leads	£3.00 each
Metal project boxes drilled & painted but unused 28 x 32.5 x 5cm	£5.00 each
Used computer cards many useful components (large ones socketed)	
Floppy disk card (NEC FDC chip)	£1.00 each
CPU card (8088, Z80 & EPROMS)	£3.00 each
Keyboards, full qwerty, number pad and LCD	£8.00 each
Desktop computer case with 200W mains PSU (used)	£30.00 each

Prices include postage. Add 50p (plus VAT) to orders below £5.00. All items new unless stated.
Add 17.5% VAT to all prices. Send an SAE for our latest list or for more info.
Dept EE, 374 Milton Road, Cambridge CB4 1SU
Tel: 0223 424602, 0831 430496 or 0831 430552 (Mail order only)

CONTROL PORT for PCs

This I/O Port follows the general approach of the 'INTERFACING to PCs' series in this mag, BUT allows user's prototype control circuitry to be set up and run OUTSIDE the PC.

The double sided pcb fits into an I/O slot, and a ribbon cable terminating in a D-25 plug allows the control of projects with little risk to the PC. On board facilities include: 8-bit A-D, 8-bit D-A, 8 inputs, 8 latched outputs, 3 strobes and 1 IRQ.

Available as:

- Etched double sided board with full instructions for drilling/assembly/testing using BASIC.....£12.50
- Complete I/O card with ribbon cable and BASIC test programs. (Built and tested).....£29.00

Also available: Test pod with D-25 socket providing analogue and digital test signals/outputs for the I/O card, with BASIC test programs on disc.....£17.00

All above prices include P&P. Mail Order only from:

R. BARTLETT,
17, LIME TREE AVENUE, TILE HILL,
COVENTRY CV4 9EY

OUT NOW!

Summer '92 Electronic Constructors Catalogue



Many new
products including:

- **Audio Amplifier Modules**
Range of 14 high power audio modules, encapsulated to an integral heatsink in Bi-polar, MOSFET and Class A formats with power outputs from 15 to 180 watts.
- **Books**
18 new titles from the top electronics publishers.
- **Burglar Alarm**
Volumetric alarm triggered by change in air pressure eg an opening door, easy to install - no wiring required.
- **Spectrum Analyser Adaptor**
Converts a conventional scope into a low cost, 250MHz spectrum analyser.
- **Low Profile Mains Transformers**
Encapsulated, top quality PCB mounting mains transformers.
- **Airband Scanning Receiver**
100 programmable channels, covering civil and military frequencies.
- **Stereo Valve Amplifier**
Top quality stereo hi-fi amp from Velleman - at a very competitive price!
- **Extended Ranges**
of connectors, equipment cases, filters, crystals, fuses, fans, kits, ATUs, semiconductors, loudspeakers, sounders and toroidal transformers.

With 24 product sections, 192 pages,
3000+ lines and £££s of discount vouchers,
be sure to get your copy now!

Available from most newsagents or
directly from Cirkit.

£1.70
+ 30p p&p

Cirkit



CIRKIT DISTRIBUTION LTD

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ
Telephone (0992) 444111 · Fax (0992) 464457

INTERFACE

Robert Penfold



THIS month we continue with the bar code reader circuit. Before proceeding to the software side of things I would like to suggest a few minor changes to the bar code reader circuit.

The prototype functioned well for some time, but then developed a tendency to latch-up. This would seem to be due to a problem with the CA3140E. The modern versions of this component have a tendency to latch-up when used in the comparator mode with a low supply voltage. The best solution to the problem is to use a CA3130E instead.

Interface

The output of the reader circuit is capable of driving most digital inputs properly, but I ran into difficulty when trying to interface it to port A of an 8255A card. Reducing R8 from 470 ohm to 220 ohm ensures that the output can drive any five volt logic input.

Despite the inclusion of a trigger stage in the circuit, glitches can still occur as the output switches from one state to the other. More hysteresis can be introduced to the trigger circuit by making R5 lower in value. However, a lot more hysteresis could severely "smear" the output signal, possibly making it impossible to find a setting for VRI that permits both wide and narrow bars to produce proper output signals. It is better to have the software filter out the odd glitch here and there.

It was my original intention to interface the bar code reader to the joystick port of a PC. Initial experiments were not very successful though, so I eventually interfaced it via an 8255A. Details of interfacing an 8255A to the PC have been provided in previous *Interface* articles, and there are commercial 8255A cards available. I used a Maplin 24 line PC I/O card, and this kit offers a relatively cheap and simple means of interfacing user add-ons to a PC.

The 8255A is at addresses from &H300 to &H303 (768 to 771 in decimal), and the output of the bar code reader connects to input D7 on port A. Obviously the reader program will need slight modification if the circuit is interfaced to the PC by some other means.

Experiment with the setting of VRI. There will be a small range of settings that give output pulses from both wide and narrow bars, but some settings are much better than others at discriminating between the two bar widths.

The best setting is not necessarily one that accurately reflects the two to one ratio of the bar widths. A setting that results in the narrow bars only just being detected seems to give an enhanced ratio, making it easier for the software to distinguish be-

Experimental barcode reading program

```
'Set up port
OUT 771, 128

'This array is deliberately made oversize to allow for possible stray reads
DIM v%(1 TO 40)
CONST TRUE = -1, FALSE = 0

'This is the start of the outer program loop
DO WHILE INKEY$ = ""
  DO
    'wait for white paper
    LOOP UNTIL INP(768) = 0
    BEEP
    DO
      'now wait for black bar
      LOOP UNTIL INP(768) = 128

    'Set up variables used in the read loop
    count% = 0
    ind% = 1
    test% = 128
    endit = FALSE
    DO
      'This loop continues as long as the port value
      'does not change
      DO WHILE test% = INP(768)
        count% = count% + 1
        IF count% > 10000 THEN
          endit = TRUE
          EXIT DO
        END IF
      LOOP
      'Disregard any stray zero reads
      IF count% <> 0 THEN
        'black bars stored as negative values
        IF test% = 128 THEN count% = -count%
        v%(ind%) = count%
        ind% = ind% + 1
        test% = INP(768)
        count% = 0
      END IF
    LOOP UNTIL endit

    REDIM bars%(-1 TO 8)
    n% = -1
    zerocount% = 0
    FOR i% = 1 TO ind% - 2
      'find and store negative values
      IF v%(i%) < 0 THEN
        bars%(n%) = v%(i%)
        n% = n% + 1
        IF n% > 8 THEN EXIT FOR
      END IF
    NEXT i%

    'This loop finds the narrowest bar
    'This will often be the first bar
    minwidth% = bars%(-1)
    FOR i% = 0 TO 8
      IF bars%(i%) < minwidth% THEN minwidth% = bars%(i%)
    NEXT i%

    'This loop finds the widest bar
    'This should be the last bar
    maxwidth% = bars%(8)
    FOR i% = 0 TO 7
      IF bars%(i%) > maxwidth% THEN maxwidth% = bars%(i%)
    NEXT i%

    'The valread% variable must be zeroed for each swipe
    valread% = 0
    FOR i% = 0 TO 7
      'Find the wide bars...
      IF (bars%(i%) - minwidth%) < (maxwidth% - bars%(i%)) THEN
        '...and add in the appropriate value
        valread% = valread% + 2 ^ i%
      END IF
    NEXT i%
    PRINT "Value read: "; valread%
  LOOP
```

tween the two bar widths. It would probably be worthwhile using a multi-turn trim-pot for VRI.

Software

The software provided is not intended to be a fully-finished program, but is intended to show the principles involved. In par-

ticular, it includes no error checking. With any bar code system there will inevitably be errors. Apart from anything else, it is probable that some of the bar codes will not be in perfect condition and properly readable.

Before using the program in any serious application it would be essential to add at

least a basic form of error checking to the system. The program is suitable for initial experimentation and can be altered and extended as needed.

A problem with the IBM PC is that the standard timer has a granularity of only 18.2 milliseconds, approximately 1/55 of a second. This is woefully inadequate for this purpose. It is possible to reprogram the timer, but this would be beyond the scope of this project. Instead, this program uses a free-running loop, and judges the widths of the bars by the number of times round.

Loops

The whole program is a succession of loops. The first loop continues until the value read from the port is 0, indicating that the sensor has been placed on the paper. The program beeps at this point to show that it is ready to start reading. The second loop waits until the reading is 128, indicating that the first bar has been encountered.

The program then enters the free-running loop. This counts as long as the value read from the port, recorded in the variable test%, remains unchanged. When the value read changes, the count in count% is stored in the array v%(), the array index (ind%) is incremented, test% is set to the new value, and count% is zeroed. Note that the readings for the bars are stored as negative values, the white spaces as positive values.

The terminating method for this loop is admittedly clumsy. It occurs when the value stored in count% exceeds 10,000. This value should never be reached when scanning, unless you move the sensor exceeding slowly, but it ends the loop reasonably quickly when the sensor is lifted from the paper. Note that this value was determined for a 33MHz 386 machine. It may need to be reduced on slower machines.

This procedure will sometimes pick up stray zero readings. For this reason, a test is included for these readings, and they are not stored in the array.

Bars

This program only uses the black bar values, not the white spaces, so the next stage is to select these, and store them in an array called bars%(). This is a dynamic array, declared with REDIM, so it is automatically zeroed each time through the program.

This part of the program is a fairly straightforward loop which finds negative (i.e. less than zero) values in v%() and transfers them to bars%(), using n% as an index to bars%(). Note the declaration of bars%(). It has 10 values, from -1 to 8. This is so that the eight bars in the middle, which represent binary digits, have the conventional 0 to 7 indexes. This simplifies programming later on.

The method used here to determine whether a bar is wide or narrow is to find the widths of the widest and narrowest bars (the two next FOR...NEXT loops), and then to determine which value each digit bar is nearer. This method is crude, but has proved successful.

If the width of a bar is nearer to the widest, it is regarded as a 1. If nearer to the narrowest, it is regarded as a 0. Using i% as an index to the bars%() array in a FOR...NEXT loop, and with index values from 0 to 7, the value can be recreated by adding 2 to the power of i% to the value for each wide bar. The finished value is printed out.

In Use

Provided everything is set up correctly the system provides a high degree of reliability, but the occasional wrong answer does crop up. Results are best if the "pen" is swept at a slow to medium speed. Moving it fast across the bar codes

invariably produces an incorrect reading. The hardware seems to be able to keep up with fast sweeps, so the problem is presumably a software one, or is perhaps due to variations in the speed of the pen.

Do-it-yourself barcodes certainly provide an interesting line of investigation for the experimenter, and provided you have suitable computer hardware, the cost is very low.

Smoking Trains

A letter published in a recent *Everyday Readout* warned of the dangers, or supposed dangers, of using pulse type model train controllers. I have used these for many years, and cannot really agree that there is any risk involved. If smoke starts to rise from a model train this surely reflects deficiencies in the overload protection, and has no bearing on the system of control in use.

The pulsed controller design featured in a previous *Interface* article does not have any form of built-in overload protection. However, the mains power supply unit includes a monolithic voltage regulator which provides fold-back current limiting.

A stalled motor might try to draw a very high current, but the current limiting circuit would actually ensure that the current flow was less than the normal maximum level. This makes it almost impossible to burn out a motor, even if you deliberately try to do so.

The criticism of noise from the motor is a more valid one, and there is no easy solution to this. It can be worthwhile trying slightly different timing capacitor values in the controller, so as to produce different operating frequencies.

Due to mechanical resonances, the motors are more efficient sound generators at some frequencies than at others. Using a very low pulse frequency avoids the problem completely, but the results look rather jerky and unrealistic.

EVERYDAY WITH PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

SUBSCRIPTION ORDER FORM

Annual subscription rates (1992/3):
UK £20.00. Overseas £26.00 (surface mail)
£43.50 (airmail)

To: Everyday Electronics, 6 Church Street
Wimborne, Dorset BH21 1JH

Our subscriptions represent excellent value for money with no price rises for a year! Your copy will arrive on your doormat before you see them on the bookstalls - post office willing!

Name.....

Address.....

I enclose payment of £..... (cheque/PO
in £ sterling only payable to Everyday Electronics)
Access or Visa No.




--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Signature.....

Card Ex. Date.....

Please supply name and address of card-holder if different from the subscription address shown above.

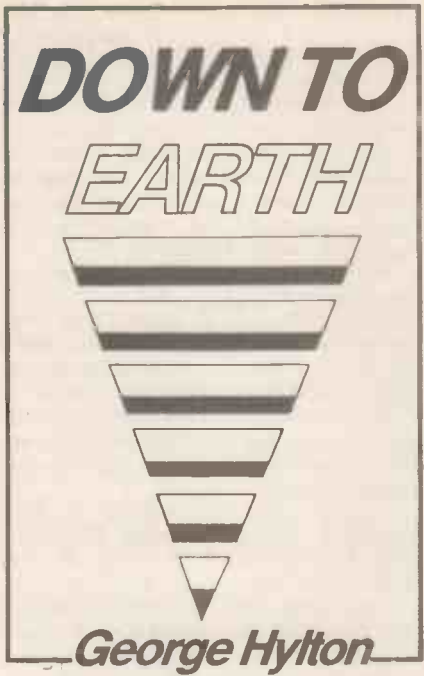Subscriptions can only start with the next available issue. For back numbers see the Editorial page.



SIMULATED REACTANCES

A bedside clock radio worked well in my flat, but not in my son's. The problem showed up when he tried to listen to 198kHz (the BBC's long-wave Radio Four transmission).

This frequency is used, outside domestic broadcasting hours, to carry the *BBC World Service*, which he likes to listen to in the very early morning.

The poor reception was probably caused by the screening effect of the steel-girder frame used in constructing the 1930s block of flats where my son lives. Mine dates from 1835, before steel frames had come into use.

Experience shows that even in a metal-framed structure there is often some spot where reception is good. It may well be, of course, that the good-reception spot isn't a convenient one for keeping the radio, but it might still be possible to place an aerial at the good spot and connect it to the radio by some sort of feeder cable.

A loop or frame aerial made by wrapping one or more turns of wire round a large vertical support such as a picture frame or the back of a wardrobe is a good bet. Calculations showed that a single large turn picks up more signal than a number of smaller turns made with the same piece of wire.

This, however, raised a practical problem which is the real subject of this article. So I'll set aside my particular problem and look at this more general one, which may well be of more interest to readers.

LOOP CIRCUITS

The equivalent circuit of an "untuned" loop or frame aerial (Fig. 1a) contains the inductance (L) of the wire, its resistance (R) and a "generator" which represents the signal voltage induced in the wire by passing radio waves.

An untuned loop is usually an insensitive aerial because the amount of current which can be driven by the signal voltage is restricted by the impedance of the loop inductance. By adding the correct capacitance (C , Fig. 1b) the impedance of the inductance is cancelled and the

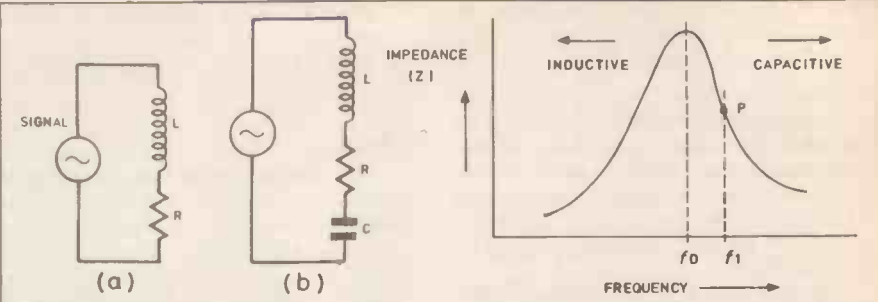


Fig. 1(a). Equivalent circuit of an untuned loop aerial (frame aerial); (b) Tuned loop.

Fig. 2. Impedance-frequency curves for parallel resonant circuit.

only impediment to current flow is the resistance R .

It is easy to make R small. A large current then flows at the series-resonant frequency. This sets up a large (comparatively) voltage across C , and also a large magnetic field inside the loop. Either voltage or current or field can be made use of.

In an ordinary long or medium wave receiver there is an internal "tuned" loop (on a ferrite-rod aerial). Energy has to be transferred to this internal loop from the external one. To use the field you just place the receiver close to the loop and orient it for good pickup.

To use the loop current you pass it through one turn of insulated wire wrapped round the receiver's cabinet, in the right way to couple to the ferrite rod aerial. With either method a large external loop can give a substantial boost to signals, and without the need for any electronics. (It's not usually practicable to use the loop voltage on long waves, though you can do so with a short wave loop by weak capacitive coupling to the "whip" aerial).

TUNING PROBLEMS

The snag appears when you discover how low the loop inductance is. A single-turn loop run round my bookcase (about a metre square) turned out to have an inductance of about $8\mu\text{H}$. This was about twice what I expected, but even so it needs about 8000pF (80nF) to tune to 198kHz .

To tune such a loop I could connect a fixed capacitor then make the loop bigger or smaller to set the frequency. Inconvenient!

One alternative is to connect a small variable inductor in series with the loop, or a larger one in parallel. This is more practical, but I didn't have a suitable coil to hand, and being lazy didn't want to go to the trouble of winding one. What I did have was a collection of i.f. transformers, frequency 455kHz or thereabouts, with a low-inductance coupling winding for driving the base of a transistor.

OFF-TUNE LC CIRCUITS

The impedance versus frequency curve for a parallel-tuned circuit (Fig. 2) shows the familiar peak at the resonant frequency f_0 . Below f_0 the impedance falls sharply as frequency is reduced.

Now, the impedance of an inductance falls like this, so the tuned circuit below f_0 behaves as an inductance of sorts. Above f_0 the impedance falls as frequency rises.

This is rather like a capacitance. Varying the tuning moves the curve to the right or left.

At frequency f_1 , the response is set at P . If the peak tuning now shifts to a rather higher frequency P moves up closer to the peak. This means that the capacitive reactance is greater, which means that the effective capacitance is lower.

In the same fashion, tuning to a lower frequency moves P down to a lower impedance point, indicating a higher effective capacitance. In this off-tune condition the LC circuit can be used as a sort of variable capacitance.

LOOP TUNING

To apply this to the loop-tuning problem the LC is connected in series with the loop (fig. 3a). As the frequency rises the impedance shows a high peak at

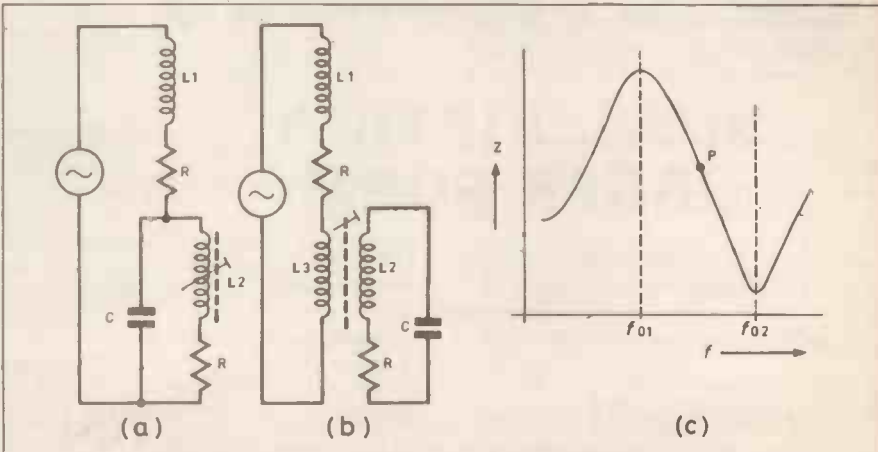


Fig. 3(a). An LC circuit can be substituted for C in Fig. 1a. (b) The effective size of C is magnified by transformer (c) Impedance-frequency graph.

f_{01} , the resonant frequency of C and $L2$, then a dip at f_{02} where $L1$ series-resonates with the capacitive region of the $C, L2$ response.

This shows that if $L1$ is the inductance of a loop aerial tuning can be effected by means of the added $C, L2$ circuit. However, this is only of use if the effective capacitance has the correct value to tune $L1$ to the wanted frequency. With my $L1$ of $8\mu\text{H}$ we need an effective capacitance of about 80nF .

Consideration of the response shown in Fig. 2 tells you that the impedance on the capacitive side of the peak is high, certainly higher than the impedance of C on its own. So Fig. 3a doesn't help unless C is higher than the value needed to resonate $L1$ in the absence of $L2$. We know that this value of C is uncomfortably high, so Fig. 3a isn't any use.

Fortunately there's an easy way out. A winding ($L3$, Fig. 3b) on $L2$, with a much smaller number of turns than $L2$, steps down the impedance. A lower capacitive impedance means a higher effective capacitance, which is what we need.

This is where my i.f. transformers come in. The low-impedance coupling winding provides about the right amount of impedance reduction. The tuned frequency of the i.f. transformer (455kHz) is wrong, or course, but easily reduced

by adding more capacitance. The actual amount needed is affected by the number of turns on the coupling winding and has to be found by trial and error. For the record, my particular transformers were tuned to 455kHz with 200pF . To get 198kHz with the loop connected this had to be increased to 1330pF . Turning the tuning "slug" (ferrite core) then gave the range $174\text{kHz}-203\text{kHz}$.

IN THE FRAME

This arrangement gave quite good boosting of the signal. However, for my son's problem I ended up by using a different solution: a multi-turn coil round a picture frame. By adjusting the number of turns this could be set to tune to 198kHz with a fixed capacitance of 3300pF .

I thought that, being smaller, the picture frame aerial would be easier to position to find the best signal. In fact it turned out that it worked well enough when placed close enough to the receiver to give magnetic-field coupling. Even though signal strength was low in this position the picture frame was so much more effective than the internal ferrite-rod aerial that an adequate signal was picked up.

By making my large loop I had, in fact, over-engineered the job. The large loop

does, however, have possible use as a means of DX-ing long and medium wave stations. And anyway it was fun experimenting.

For anybody who wants to try out the large-loop idea one simple rule gives a pointer to the capacitance needed to retune the i.f. transformer. The loop inductance being in parallel with the coupling winding causes an increase in the tuned frequency of the i.f.t.

It follows that the added capacitance must be greater than what is needed to tune the i.f.t. to the wanted frequency before the loop is connected. If you know the value of the built-in capacitance, this total capacitance is easily calculated.

Divide the nominal frequency of the i.f.t. by the wanted frequency, square the answer and multiply the built-in capacitance by it.

Example: i.f. = 450kHz , built-in capacitor 200pF , wanted frequency 150kHz : $450/150 = 3$; $3^2 = 9$; total capacitance needed = $9 \times 200 = 1800\text{pF}$. With the loop in situ more than this is needed, but you are in the right area.

For the record, my i.f.t. needed a total of 1056pF for 198kHz , in the absence of the loop. With my loop connected the value required turned out to be 1330pF total.

EVERYDAY READOUT

WOOFER

Dear Ed.,

I was intrigued to see the idea of using two speakers face to face in the project *Sub-Woofers* by Paul Henderson in the August issue of *EE*.

Presumably this means that the external speaker could transmit twice its normal maximum rating, half from its own magnet/coil assembly and half by air pressure from the internal speaker. Would the speaker surround be able to take this?

Similarly the internal speaker cone could move twice its rated maximum displacement and in this case would the speaker box be large enough?

If the author is right and the face to face speaker arrangement gives twice the output for a given box size, then this seems to me to be quite a breakthrough in the quest for smaller loudspeaker cabinets.

My own interest is more in P.A. work and I would like to ask for the author's views on the feasibility of using two speakers face to face, together with a piezo-electric tweeter to cover the audio range - say 45Hz to 16kHz . The circuitry would then be the sub-woofer circuit of the article together with a direct connection to the normal power amplifier output. This would hopefully give the boosted low frequencies together with the unboosted remainder of the audio range. I shall be grateful for your comments.

C. F. Stevenson
London SW19

I would first like to thank Mr. Stevenson for his letter regarding the Sub-Woofers project. Unfortunately he appears to have got the wrong end of the stick regarding how the system operates. Both drivers are connected face to face and are operated electrically in antiphase. The result is that both speaker

cones move in the same direction and act as a single cone.

The advantage of this mode of operation are far from obvious, at first sight. However doubling the mass of the moving cone allows a 50% reduction in the case volume over that required with a single speaker. Furthermore the two drivers are working as a mechanical analog to a push-pull output stage. The push-pull action leads to the elimination of even harmonic distortion. In speaker systems frequency doubling, second harmonic distortion, is the major non linearity at low frequencies.

So by using two speakers in this manner we both halve case size and eliminate the major source of distortion. These two factors, taken together, more than justify the extra expense of a second driver.

As far as the system as a whole is concerned the sensitivity is the same as if a single driver had been used.

As for the possibility of using the Sub-Woofers as part of a full range system I can see no insuperable obstacles. Removing the top cut filter will give the Sub-Woofers a response that extends to the upper midrange while preserving the bass. A piezo tweeter could be simply connected in parallel with the woofers to produce the required response. I must stress that I haven't tried this myself and I can foresee a possible problem with diffraction effects caused by the outward facing speaker magnet in the midrange.

Paul Henderson

FULL CERTIFICATE

Dear Ed.,

I read with interest the item about City and Guilds in *Everyday News* (July '92). But what I would like to know is why they won't allow anyone to take the 726/361 Final on advanced level in Digital Electronics.

I, like thousands of other unemployed people, go on E.T. courses to obtain a C&G qualification, but after completing the 341 you find they will not send out the 361 documentation. Admittedly the course is interesting but if you are after a "full" certificate you are wasting time and money, in fact, for those on E.T., Government money.

My tutor rang them and they said there was no call for this level, but in fact I had written to them and my tutor rang them on an earlier occasion and was informed to the effect that there was not a fourth level. We persisted because four levels are quoted in their booklets.

I wonder if you could print a statement from them on their policy concerning this matter, or print something to say those who wish to take the fourth should persist in applying to C&G. May I say that we use your *Introductory Digital Electronics, Teach-In 4* book and very useful it is to.

J. G. Wood
Newport

I have checked out the position relating to the module on Digital Electronics raised by J. G. Wood.

Information Technology (7261) is a modular scheme intended to cover the complete range of IT at four levels. Not every topic area is yet covered at four levels.

New modules are being developed all the time in response to demand from centres, but we have had to establish a priority rating and, at present, module 361 is quite a long way down the list. That situation is unlikely to change in the short term unless we have evidence of great demand.

In summary, therefore, the documentation required by Mr. Wood cannot be sent to him because there is none to send. Notwithstanding this, a full Certificate (or depending upon the mix of modules, a Diploma or Advanced Diploma) is still available and Mr. Wood's Centre should also be eligible for ET funding.

If his centre wishes to submit their own proposals for a centre-devised version of module 361, City and Guilds will be pleased to vet them for technical content and administer the scheme in the normal way. Application should be made to Division 13.

I trust this answers all the points raised by Mr. Wood in his letter.

A. A. W. Sich
Head of Marketing
and Public Relations
City and Guilds

VIDEOS ON ELECTRONICS

Everyday Electronics is pleased to announce the availability of a range of videos designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They should prove particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc.

The first four videos available are:

- ★ **1** *Electronics And You – Part 1: D.C. Series and parallel circuits and the use of a digital multimeter. Running time approx. 51 mins.*
Order code VT1 **£29.95 inc. VAT**
- ★ **2** *Part 2: A.C. Coils, capacitors, transformers and other a.c. devices. Running time approx 62 mins.*
Order code VT2 **£29.95 inc. VAT**
- ★ **3** *Part 3: Semiconductors. Basic semiconductor theory plus fifteen different semiconductor devices explained. Running time approx. 56 mins.*
Order code VT3 **£29.95 inc. VAT**
- NEW** ★ **4** *Part 4: Power Supplies. A step by step look at how they work plus trouble shooting tips. Running time approx. 56 mins.*
Order code VT4 **£29.95 inc. VAT**

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier.

To order see our Direct Book Service "Ordering Details" – the postage for tapes is the same as for our range of books and you can order tapes and books at the same time and pay only one lot of postage.

(All videos are to the UK PAL standard on VHS tapes)

£29.95
each

UCANDO
VCR EDUCATIONAL PRODUCTS COMPANY

Part 2
Alternating Currents

VT202


UCA
VCR EDUCATIONAL PRODUCTS COMPANY

Semiconductors

VT203


PHOTOTRANSISTOR

Emitter Base Collector

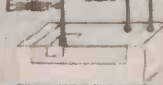

Showing Large Base Area

PHOTOTRANSISTOR

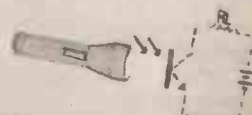

DIRECT BOOK SERVICE

The books listed have been selected by Everyday Electronics editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page. For another selection of books see next month's issue.

EVERYDAY ELECTRONICS DATA BOOK

Mike Tooley BA

(published by EE in association with PC Publishing) This book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous examples showing how theory can be put into practice using a range of commonly available "industry standard" components and devices.

A must for everyone involved in electronics!
256 pages

Order code DATA £8.95

ELECTRONICS TEACH-IN No. 3 - EXPLORING ELECTRONICS (published by Everyday Electronics)

Owen Bishop

Another EE value for money publication aimed at students of electronics. The course is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. The book does not contain masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

Exploring Electronics contains more than 25 useful projects, assumes no previous knowledge of electronics and is split into 28 easily digestible sections.
88 pages (A4 size)

Order code T13 £2.45

COMPUTERS AND MUSIC - AN INTRODUCTION

R. A. Penfold

Computers are playing an increasingly important part in the world of music, and the days when computerised music was strictly for the fanatical few are long gone. Computer-based music systems in the past have tended to be either horrendously expensive, very crude, or both. These days, prices are much more modest and the potential of the equipment is much greater. Consequently a lot of musicians are being tempted into the unfamiliar territory of computer music systems.

If you are more used to the black and white keys of a synth keyboard than the QWERTY keyboard of a computer, you may be understandably confused by the jargon and terminology bandied about by computer buffs. But fear not, setting up and using a computer-based music making system is not as difficult as you might think.

This book will help you learn the basics of computing, running applications programs, wiring up a MIDI system and using the system to good effect, in fact just about everything you need to know about hardware and the programs, with no previous knowledge of computing needed or assumed. This book will help you to choose the right components for a system to suit your personal needs, and equip you to exploit that system fully.
174 pages

Temporarily out of print

A CONCISE INTRODUCTION TO MS-DOS

N. Kantaris

This guide is written with the non-expert, busy person in mind and, as such, it has an underlying structure based on "what you need to know first, appears first". Nonetheless, the guide is also designed to be circular, which means that you don't have to start at the beginning and go to the end. The more experienced user can start from any section.

The guide covers versions 3.0, 3.1 and 3.2 of both PC-DOS and MS-DOS as implemented by IBM and other manufacturers of "compatible" microcomputers, including the AMSTRAD PCs. It covers both floppy disc-based systems and hard disc-based systems.
64 pages

Order code BP32 £2.95

Special Everyday Electronics Books

ELECTRONICS TEACH-IN No. 4 INTRODUCING DIGITAL ELECTRONICS (published by Everyday Electronics)

Michael J. Cockcroft

Although this book is primarily a City & Guilds Introductory level course (726/301), approximately 80% of the information forms a very basic introduction to electronics in general, it therefore provides an excellent introductory text for beginners and a course and reference book for GCSE students.

Full details on registering for C&G assessment, details of assessment centres, components required and information on the course in general are given.

The City & Guilds introduction to module 726/301 reads: "A candidate who satisfactorily completes this module will have a competence to identify basic components and digital integrated circuits and connect them together to form simple working circuits and logic units." This provides an excellent introduction to the book.
112 pages (A4 size)

Order code T14 £2.95

ELECTRONIC PROJECTS - BOOK 1

Published by Everyday Electronics in association with Magenta Electronics.

Contains twenty of the best projects from previous issues of EE each backed with a kit of components. The projects are: Seashell Sea Synthesiser, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16K Sideways Ram, Simple Short Wave Radio, Insulation Tester, Stepper Motor interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser Isolator, Bat Detector, Acoustic Probe, Mains Tester and Fuse Finder, Light Rider - (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.
128 pages (A4 size)

Order code EPT £2.45

ELECTRONICS TEACH-IN No. 5 GUIDE TO BUILDING ELECTRONIC PROJECTS

Published by EVERYDAY ELECTRONICS

Due to the demand from students, teachers and hobbyists we have put together a range of articles from past issues of *Everyday Electronics* that will assist those involved with the construction of electronic projects.

The book contains the complete *Project Development for GCSE* series.

Contents: Features - First Steps in Project Building; Building with Vero; Project Development for GCSE; Getting your Project Working; Guide to Printed Circuit Boards; Choosing and Using Test Equipment - The Multimeter, The Oscilloscope, P.S.U.s, Logic Probes, Digital Frequency Meters, Signal Generators, etc; Data - Circuit Symbols; Component Codes; Resistors; Identifying Components; Capacitors; Actually Doing It - Understanding the Circuit Diagram, Component Codes, Mounting circuit boards and controls, Understanding Capacitors; Projects - Lie Detector; Personal Stereo Amplifier; Digital Experimenter's Unit; Quizmaster; Siren Effects Unit; UV Exposure Unit; Low-cost Capacitance Meter; Personal Radio.
88 pages (A4 size)


Order code T15 £2.95

ELECTRONICS TEACH-IN 88/89 - INTRODUCING MICROPROCESSORS

Mike Tooley BA (published by Everyday Electronics)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc. Starting with basic terminology, integrated circuits, logic families and numbering systems the text builds in stages, with revision and assessments built in, up to programming, languages, flow charts, etc. The course is ideal for the newcomer to the subject.
80 pages (A4 size)

Order code T1-88 89 £.45

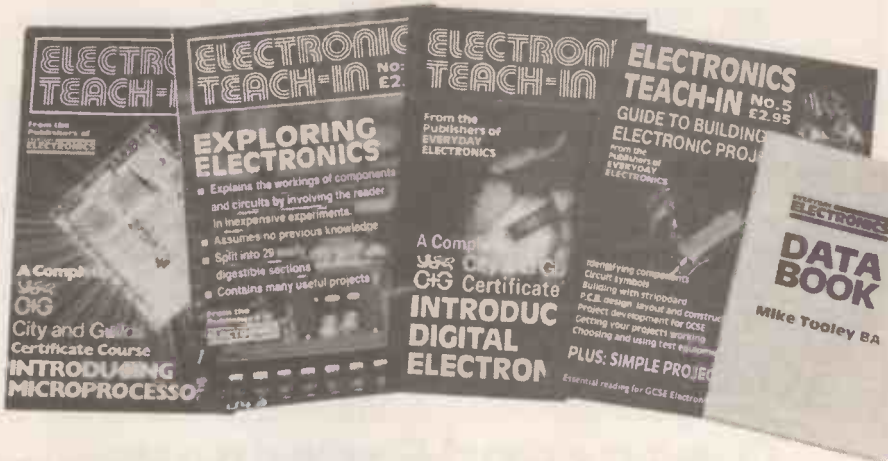

Computers and Computing

COMPUTERS AND MUSIC - AN INTRODUCTION

R. A. Penfold

Computers are playing an increasingly important part in the world of music, and the days when computerised music was strictly for the fanatical few are long gone. Computer-based music systems in the past have tended to be either horrendously expensive, very crude, or both. These days, prices are much more modest and the potential of the equipment is much greater. Consequently a lot of musicians are being tempted into the unfamiliar territory of computer music systems.

If you are more used to the black and white keys of a synth keyboard than the QWERTY keyboard of a computer, you may be understandably confused by the jargon and terminology bandied about by computer buffs. But fear not, setting up and using a computer-based music making system is not as difficult as you might think.

This book will help you learn the basics of computing, running applications programs, wiring up a MIDI system and using the system to good effect, in fact just about everything you need to know about hardware and the programs, with no previous knowledge of computing needed or assumed. This book will help you to choose the right components for a system to suit your personal needs, and equip you to exploit that system fully.
174 pages

Temporarily out of print

A CONCISE INTRODUCTION TO MS-DOS

N. Kantaris

This guide is written with the non-expert, busy person in mind and, as such, it has an underlying structure based on "what you need to know first, appears first". Nonetheless, the guide is also designed to be circular, which means that you don't have to start at the beginning and go to the end. The more experienced user can start from any section.

The guide covers versions 3.0, 3.1 and 3.2 of both PC-DOS and MS-DOS as implemented by IBM and other manufacturers of "compatible" microcomputers, including the AMSTRAD PCs. It covers both floppy disc-based systems and hard disc-based systems.
64 pages

Order code BP32 £2.95

HOW TO CHOOSE A SMALL BUSINESS COMPUTER SYSTEM

D. Weale

This book is for anyone intending to buy an IBM compatible computer system, whether it is their first system or a replacement. There are sections on hardware, application and systems programs and how to actually make your choice as well as sections on the law, ergonomics and a glossary of common terms.

The text contains many useful tips and some warnings (which could save much effort and expense).
114 pages

Order code BP323 £4.95

AN INTRODUCTION TO 68000 ASSEMBLY LANGUAGE

R. A. & J. W. Penfold

Obtain a vast increase in running speed by writing programs for 6800 based micros such as the Commodore Amiga, Atari ST range or Apple Macintosh range etc., in assembly language. It is not as difficult as one might think and this book covers the fundamentals.
112 pages

Order code MP184 £2.95

THE ART OF PROGRAMMING THE ZX SPECTRUM

M. James, B.Sc., M.B.C.S.

It is one thing to have learnt how to use all the Spectrum's commands and functions, but a very different one to be able to combine them into programs that do exactly what you want them to. This is just what this book is all about - teaching you the art of effective programming with your Spectrum.
144 pages

Order code BP119 £2.50

A Z80 WORKSHOP MANUAL

E. A. Parr, B.Sc., DC.Eng., M.I.E.E.

This book is intended for people who wish to progress beyond the stage of BASIC programming to topics such as machine code and assembly language programming, or need hardware details of a Z80 based computer.
192 pages

Order code BP112 £3.95

NEWNES COMPUTER ENGINEER'S POCKETBOOK

(Second Edition)

Michael Tooley

An invaluable compendium of facts, figures, circuits and data, indispensable to the designer, student, service engineer and all those interested in computer and microcomputer systems. It will appeal equally to the hardware or software specialist and to the new band of "software engineers". This data is presented in a succinct and rapidly accessible form so that the book can become part of an everyday toolkit.
205 pages (hard cover)

Order code NE01 £10.95

UNDERSTANDING PC SPECIFICATIONS

R. A. Penfold

If you require a microcomputer for business applications, or a high quality home computer, an IBM PC or compatible is often the obvious choice. They are competitively priced, and are backed up by an enormous range of applications programs, hardware add-ons, etc. The main difficulty for the uninitiated is deciding on the specification that will best suit his or her needs. PCs range from simple systems of limited capabilities up to complex systems that can happily run applications that would have been considered beyond the abilities of a microcomputer not so long ago. It would be very easy to choose a PC system that is inadequate to run your applications efficiently, or one which goes beyond your needs and consequently represents poor value for money.

This book explains PC specifications in detail, and the subjects covered include the following: Differences between types of PC (XT, AT, 80386, etc); Maths co-processors; Input devices (keyboards, mice, and digitisers); Memory, including both expanded (EMS) and extended RAM; RAM disks and disk caches; Floppy disk drive formats and compatibility; Hard disk drives (including interleave factors and access times); Display adaptors, including all standard PC types (CGA, Hercules, Super VGA, etc); Contains everything you need to know if you can't tell your EMS from your EGA!
104 pages

Order code BP182 £3.95

Audio and Music

ELECTRONIC PROJECTS FOR GUITARS **NEW**

R. A. Penfold

This book contains a collection of guitar effects and some general purpose effects units, many of which are suitable for beginners to project building. An introductory chapter gives guidance on construction.

Each project has an introduction, an explanation of how it works, a circuit diagram, complete instructions on strip-board layout and assembly, as well as notes on setting up and using the units. Contents include: Guitar tuner; Guitar preamplifier; Guitar headphone amplifier; Soft distortion unit; Compressor; Envelope waa waa; Phaser; Dual tracking effects unit; Noise gate/expander; Treble booster; Dynamic treble booster; Envelope modifier; Tremolo unit; DI box. **110 pages** **Order code PC110** **£8.95**

PREAMPLIFIER AND FILTER CIRCUITS **NEW**

R. A. Penfold

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases).

The preamplifier circuits featured include:- Microphone preamplifiers (low impedance, high impedance, and crystal); Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation; Crystal/ceramic pick-up preamplifier; Guitar pick-up preamplifier; Tape head preamplifier (for use with compact cassette systems).

Other circuits include:- Audio limiter to prevent overloading of power amplifiers; Passive tone controls; Active tone controls; PA filters (highpass and lowpass); Scratch and rumble filters; Loudness filter; Audio mixers; Volume and balance controls.

No constructional details are given - but most of the circuits are relatively simple. **92 pages** **Order code BP309** **£3.95**

PRACTICAL MIDI HANDBOOK

R. A. Penfold

The Musical Instrument Digital Interface (MIDI) is surrounded by a great deal of misunderstanding, and many of the user manuals that accompany MIDI equipment are quite incomprehensible to the reader.

The Practical MIDI Handbook is aimed primarily at musicians, enthusiasts and technicians who want to exploit the vast capabilities of MIDI, but who have no previous knowledge of electronics or computing. The majority of the book is devoted to an explanation of what MIDI can do and how to exploit it to the full, with practical advice on connecting up a MIDI system and getting it to work, as well as deciphering the technical information in those manuals. **128 pages** **Order code PC101** **£6.95**

PREAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases).

The preamplifier circuits featured include:- Microphone preamplifiers (low impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A.

equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include:- Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters (highpass and lowpass). Scratch and rumble filters. Loudness filter. Audio mixers. Volume and balance controls. **92 pages** **Order code BP309** **£3.95**

MUSICAL APPLICATIONS OF THE ATARI ST's

R. A. Penfold

The Atari ST's are now firmly established as *the* computers to use for electronic music applications. The range and sophistication of these applications are much greater than most people may realise, but there are still a lot of misconceptions about just what can and cannot be achieved. This book will help you sort out the fact from the fallacy and to get the most musically from the ST's.

A wide selection of topics are covered, including the internal sound chip; MIDI; applications programs such as sequencing and score writing, etc; simple but useful add-on projects and MIDI programming. **90 pages** **Order code BP246** **£5.95**

AN INTRODUCTION TO LOUSPEAKERS AND ENCLOSURE DESIGN

V. Capel

This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally there is a step-by-step description of the construction of the Kapellmeister loudspeaker enclosure. **148 pages** **Order code BP256** **£2.95**

ACOUSTIC FEEDBACK - HOW TO AVOID IT

Feedback is the bane of all public address systems. While feedback cannot be completely eliminated, many things can be done to reduce it to a level at which it is no longer a problem.

Much of the trouble is often the hall itself, not the equipment, but there is a simple and practical way of greatly improving acoustics. Some microphones are prone to feedback while others are not. Certain loudspeaker systems are much better than others, and the way the units are positioned can produce or reduce feedback. All these matters are fully explored as well as electronic aids such as equalizers, frequency-shifters and notch filters.

The special requirements of live group concerts are considered, and also the related problem of instability that is sometimes encountered with large set-ups. We even take a look at some unsuccessful attempts to cure feedback so as to save readers wasted time and effort duplicating them.

Also included is the circuit and layout of an inexpensive but highly successful twin-notch filter, and how to operate it. **92 pages** **Order code PP310** **£3.95**

COMPUTERS AND MUSIC. See Computers section

Project Building

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold

We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects. **96 pages** **Order code BP110** **£2.50**

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s. **80 pages** **Order code B1121** **£2.50**



A BEGINNERS GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold

The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronic theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor. **166 pages** **Order code BP285** **£3.95**

BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also include examples in the form of simple projects. **112 pages** **Order code 227** **£1.95**

ELECTRONIC SCIENCE PROJECTS

O. Bishop

These projects range in complexity from a simple colour temperature meter to an Infra-red laser. There are novelties such as an electronic clock regulated by a resonating spring, and an oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. The way they work, and how to build and use them are fully explained. **144 pages** **Temporarily out of print**

ELECTRONICS SIMPLIFIED - CRYSTAL SET CONSTRUCTION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Especially written for those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. It is designed for all ages upwards from the day one can read intelligently and handle simple tools. **80 pages** **Order code BP92** **£1.75**

GUIDE TO BUILDING ELECTRONIC PROJECTS

Published by *Everyday Electronics*

See the first page of books - ELECTRONICS TEACH-IN No.5 - for full details.

ELECTRONICS PROJECT BOOK

Published by *Everyday Electronics* in association with *Magenta Electronics*.

See the first page of books for full details.

Theory and Reference

ELECTRONIC HOBBYISTS HANDBOOK

R. A. Penfold

Provides an inexpensive single source of easily located information that the amateur electronics enthusiast is likely to need for the day-to-day pursuance of this fascinating hobby. Covers common component colour codes. Details the characteristics and pinouts of many popular semiconductor devices, including various types of logic ICs, operational amplifiers, transistors, FETs, unijunctions, diodes, rectifiers, SCRs, diacs, triacs, regulators and SMDs, etc. Illustrates many useful types of circuits, such as timers and oscillators, audio amplifiers and filters, as well as including a separate section on power supplies. Also contains a multitude of other useful data. **88 pages** **Order code BP233** **£4.95**

NEWNES ELECTRONICS POCKET BOOK

E. A. Parr

Newnes Electronics Pocket Book has been in print for over twenty years and has covered the development of electronics from valve to semiconductor technology and from transistors to LSI integrated circuits and microprocessors. To keep up to date with the rapidly changing world of electronics, continuous revision has been necessary. This new Fifth Edition takes account of recent changes and includes material suggested by readers of previous editions. New descriptions of op.amp. applications and the design of digital circuits have been added, along with a totally new chapter on computing, plus other revisions throughout. **315 pages (hard cover)** **Order code N102** **£10.95**

ELECTRONIC MODULES AND SYSTEMS FOR BEGINNERS

Owen Bishop

This book describes over 60 modular electronic circuits - how they work, how to build them, and how to use them. The modules may be wired together to make hundreds of different electronic systems, both analogue and digital. To show the reader how to begin building systems from modules, a selection of over 25 electronic systems are described in detail, covering such widely differing applications as timing, home security, measurement, audio (including a simple radio receiver), games and remote control. **200 pages** **Order code BP266** **£3.95**

FROM ATOMS TO AMPERES

F. A. Wilson

Explains in crystal clear terms the absolute fundamentals behind electricity and electronics. Really helps you to discover and understand the subject, perhaps for the first time ever.

Have you ever: Wondered about the true link between electricity and magnetism? Felt you could never understand the work of Einstein, Newton, Boltzmann, Planck and other early scientists? Just accepted that an electron is like a little black ball? Got mixed up with e.m.f. and p.d.? Thought the idea of holes in semiconductors is a bit much?

Then help is at hand with this inexpensive book, in as simple a way as possible and without too much complex mathematics and formulae. **244 pages** **Order code BP254** **£3.50**

PRACTICAL DIGITAL ELECTRONICS HANDBOOK

Mike Tooley (Published in association with *Everyday Electronics*)

The vast majority of modern electronic systems rely heavily on the application of digital electronics, and the *Practical Digital Electronics Handbook* aims to provide readers with a practically based introduction to this subject. The book will prove invaluable to anyone involved with the design, manufacture or servicing of digital circuitry, as well as to those wishing to update their knowledge of modern digital devices and techniques. Contents: Introduction to integrated circuits; basic logic gates; monostable and bistable devices; timers; microprocessors; memories; input and output devices; interfaces; microprocessor buses. Appendix 1: Data. Appendix 2: Digital test gear projects; tools and test equipment; regulated bench power supply; logic pulser; versatile pulse generator; digital IC tester; current tracer; audio logic tracer; RS-232C breakout box; versatile digital counter/frequency meter. Appendix 3: The oscilloscope. Appendix 4: Suggested reading. Appendix 5: Further study. **208 pages** **Order code PC100** **£6.95**

ELECTRONICS - A "MADE SIMPLE" BOOK

G. H. Olsen

This book provides excellent background reading for our *Introducing Digital Electronics Teach-In* Book and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity. **330 pages** **Order code NL10** **£4.95**

Testing and Test Gear

HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT

R. A. Penfold

This book explains the basic function of an oscilloscope, gives a detailed explanation of all the standard controls, and provides advice on buying. A separate chapter deals with using an oscilloscope for fault finding on linear and logic circuits. plenty of example waveforms help to illustrate the control functions and the effects of various fault conditions. The function and use of various other pieces of test equipment are also covered, including signal generators, logic probes, logic pulsers, and crystal calibrators. **104 pages** **Order code BP267** **£3.50**

Circuits and Design

PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 2

R. A. Penfold

This book is designed to aid electronic enthusiasts who like to experiment with circuits and produce their own projects, rather than simply following published project designs.

Contents: Amplifiers—low level discrete and op-amp circuits, voltage and buffer amplifiers including d.c. types. Also low-noise audio and voltage controller amplifiers. Filters—high-pass, low-pass, 6, 12, and 24dB per octave types. Miscellaneous—i.e. power amplifiers, mixers, voltage and current regulators, etc.

112 pages Order code BP118 £1.95

MODERN OPTO DEVICE PROJECTS

R. A. Penfold

In recent years, the range of opto devices available to the home constructor has expanded and changed radically. These devices now represent one of the more interesting areas of modern electronics for the hobbyist to experiment in, and many of these have useful practical applications as well. This book provides a number of practical designs which utilize a range of modern opto-electrical devices, including such things as fibre optics, ultra bright l.e.d.s and passive IR detectors etc.

While many of these designs are not in the "dead simple" category, they should be within the capabilities of anyone with a reasonable amount of experience in electronics construction and some of the more simple designs are suitable for beginners.

104 pages Order code BP194 £2.95

ELECTRONIC ALARM CIRCUITS MANUAL

R. M. Marston

One hundred and forty useful alarm circuits, of a variety of types, are shown in this volume. The operating principle of each one is explained in concise but comprehensive terms, and brief construction notes are given where necessary.

Aimed at the practical design engineer, technician and experimenter, as well as the electronics student and amateur.

124 pages Order code BP111 £12.95

DIGITAL LOGIC GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops

thoroughly and from the beginning. This is not a constructor's book in the sense of presenting circuits to build and use, it is for the user who wants to design and troubleshoot digital circuitry with considerably more understanding of principles.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages Order code PC106 £8.95

ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS

Robert Penfold

Robots and robotics offer one of the most interesting areas for the electronics hobbyist to experiment in. Today the mechanical side of robots is not too difficult, as there are robotics kit and a wide range of mechanical components available. The micro controller is not too much of a problem either, since the software need not be terribly complex and many inexpensive home computers are well suited to the task.

The main stumbling block for most would-be robot builders is the electronics to interface the computer to the motors, and the sensors which provide feedback from the robot to the computer. The purpose of this book is to explain and provide some relatively simple electronic circuits which bridge this gap.

92 pages Order code BP179 £2.95

ELECTRONIC POWER SUPPLY HANDBOOK

Ian R. Sinclair

This book covers the often neglected topic of electronic power supplies. All types of supplies that are used for electronics purposes are covered in detail, starting with cells and batteries and extending by way of rectified supplies and linear stabilisers to modern switch-mode systems, IC switch-mode regulators, DC-DC converters and inverters.

The devices, their operating principles and typical circuits are all dealt with in detail. The action of rectifiers and the reservoir capacitor is emphasised, and the subject of stabilisation is covered. The book includes some useful formulae for assessing the likely hum level of a conventional rectifier reservoir supply.

136 pages Order code BP108 £7.95

HOW TO USE OP-AMPS

E. A. Parr

This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

160 pages Order code BP88 £2.95

MICRO INTERFACING CIRCUITS—BOOK 1

MICRO INTERFACING CIRCUITS—BOOK 2

R. A. Penfold

Both books include practical circuits together with details of the circuit operation and useful background information. Any special constructional points are covered but p.c.b. layouts and other detailed constructional information are not included.

Book 1 is mainly concerned with getting signals in and out of the computer; Book 2 deals primarily with circuits for practical applications.

BOOK 1 112 pages Order code BP130 £2.75

BOOK 2 112 pages Order code BP131 £2.75

PRACTICAL ELECTRONIC DESIGN DATA

Owen Bishop

It's all here! This book is a comprehensive ready-reference manual for electronics enthusiasts of all levels, be they hobbyists, students or professionals.

A helpful major section covers the main kinds of components, including surface-mount devices. For each sort, it lists the most useful and readily available types complete with details of their electronic characteristics, pin-outs and other essential information. A special feature of this section are the easily followed charts and tables which advise the reader on how to select the best type of components for any particular purpose.

Basic electronic units are defined, backed up by a compendium of the most often required formulae.

There are five more extensive sections devoted to circuit design, covering analogue, digital, radio, display, and power supply circuits. Over 150 practical circuit diagrams cover a broad range of functions. The reader is shown how to adapt these basic designs to a variety of applications.

328 pages Order code BP16 £4.95

50 SIMPLE LED CIRCUITS

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components—the light-emitting diode (LED). Also includes circuits for the 707 common anode display.

64 pages Order code BP42 £1.95

BOOK 2 50 more l.e.d. circuits Order code BP87 £1.95

Radio, TV, Satellite

PROJECTS FOR RADIO AMATEURS

AND S.W.L.S.

R. A. Penfold

This book describes a number of electronic circuits, most of which are quite simple, which can be used to enhance the performance of most short wave radio systems.

The circuits covered include:—An aerial tuning unit; A simple active aerial; An add-on b.f.o. for portable sets; A wavetrap for combat signals on spurious responses; An audio notch filter; A parametric equaliser; C.W. and S.S.B. audio filters; Simple noise limiters; A speech processor; A volume expander.

Other useful circuits include a crystal oscillator, and RTTY/C.W. tone decoder, and a RTTY serial to parallel converter. A full range of interesting and useful circuits for short wave enthusiasts.

92 pages Order code BP304 £3.95

AN INTRODUCTION TO AMATEUR RADIO

I. D. Poole

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the century.

This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages Order code BP257 £3.50

SIMPLE SHORT WAVE RECEIVER CONSTRUCTION

R. A. Penfold

Short wave radio is a fascinating hobby, but one that seems to be regarded by many as an expensive pastime these days. In fact it is possible to pursue this hobby for a minimal monetary outlay if you are prepared to undertake a bit of d.i.y., and the receivers described in this book can all be built at low cost. All the sets are easy to construct, full wiring diagrams etc. are provided, and they are suitable for complete beginners. The receivers only require simple aerials, and do not need any complex alignment or other difficult setting up procedures.

The topics covered in this book include: The broadcast bands and their characteristics; The amateur bands and their characteristics; The propagation of radio signals; Simple aerials; Making an earth connection; Short wave crystal set; Simple t.r.f. receivers. Single sideband reception; Direct conversion receiver.

Contains everything you need to know in order to get started in this absorbing hobby.

88 pages Order code BP275 £3.95

AN INTRODUCTION TO SATELLITE TELEVISION

F. A. Wilson

As a definitive introduction to the subject this book is presented on two levels. For the absolute beginner or anyone thinking about purchasing or hiring a satellite TV system, the story is told as simply as such a complex one can be in the main text.

For the professional engineer, electronics enthusiast, student or others with technical backgrounds, there are numerous appendices backing up the main text with additional technical and scientific detail formulae, calculations, tables etc. There is also plenty for the DIY enthusiast with practical advice on choosing and installing the most problematic part of the system—the dish antenna.

104 pages Order code BP95 £5.95

AN INTRODUCTION TO AMATEUR COMMUNICATIONS SATELLITES

A. Pickford

Communications and broadcast satellites are normally inaccessible to individuals unless they are actively involved in their technicalities by working for organisations such as British Telecom, the various space agencies or military bodies, even those who possess a satellite television receiver system do not participate in the technical aspects of these highly technological systems.

There are a large number of amateur communications satellites in orbit around the globe, traversing the globe continuously and they can be tracked and their signals received with relatively inexpensive equipment. This equipment can be connected to a home computer such as the BBC Micro or IBM compatible PCs, for the decoding of received signals.

This book describes several currently available systems, their connection to an appropriate computer and how they can be operated with suitable software.

102 pages Order code BP290 £3.95

AERIAL PROJECTS

R. A. Penfold

The subject of aerials is vast but in this book the author has considered practical aerial designs, including active, loop and ferrite aerials which give good performances and are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

Also included are constructional details of a number of aerial accessories including a pre-selector, attenuator, filters and tuning unit.

96 pages Order code BP105 £2.50

INTERNATIONAL RADIO STATIONS GUIDE

P. Shore

Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around the ever more complex radio bands. This new edition has been completely revised and rewritten and incorporates much more information which is divided into the following sections:

Listening to Short Wave Radio; Choosing a Short Wave Radio Receiver; How to Use the IRSG; Abbreviations; Country Codes; Worldwide Short Wave Radio Stations; European, Middle Eastern and African Long Wave Radio Stations; European, Near and Middle Eastern and African Medium Wave Radio Stations; Canadian Medium Wave Radio Stations; USA Medium Wave Radio Stations; Broadcasts in English; Programmes for DXers and Short Wave Listeners; UK FM Radio Stations; Time Differences From GMT; Wavelength/Frequency Conversion.

226 pages Order code BP255 £5.95

DIRECT BOOK SERVICE ORDERING DETAILS

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add 75p to your total order for postage and packing (overseas readers add £1.50 for countries in Europe, or add £2.50 for all countries outside Europe, surface mail postage) and send a PO, cheque, international money order, (£ sterling only) made payable to Direct Book Service or credit card details (including the card expiry date), Visa or Mastercard (Access) – minimum credit card order is £5 – quoting your name and address, the order code and quantities required to DIRECT BOOK SERVICE, 33 GRAVEL HILL, WIMBORNE, DORSET BH21 1RW (mail order only).

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of Everyday Electronics) before ordering from old lists.

Note – our postage charge is the same for one book or one hundred books!

MORE BOOKS NEXT MONTH

Direct Book Service is a division of Wimborne Publishing Ltd

BABANI BOOKS

We now supply *all* the books published by Bernard Babani (Publishing) Ltd. We have always supplied a selected list of Babani books and you will find many of them described on the previous pages or in next months issue of *Everyday Electronics* (the books with a BP prefix to the order code are Babani books).

Many readers have asked us to also supply various other Babani books, which have a reputation for value for money. Our customers tell us they appreciate our speedy service and low postage charge and they

would like to be able to purchase all the books from us and thus keep the postage charge to an absolute minimum (75p for UK p&p no matter how many books you buy). We are pleased to be able to respond; with the aid of Michael Babani (M.D.) we are now able to meet all your requirements for their books. *If it's Babani and in print we can supply it.* Babani presently list over 180 different technical titles those not described in detail on the previous *Direct Book Service* pages or in next months issue are listed below:

Code	Title	Price	Code	Title	Price	Code	Title	Price
C08	Practical Stereo & Quadrophony Handbook	£0.75	BP145	25 Simple Tropical and MW Band Aerials	£1.75	BP249	More Advanced Test Equipment Construction	£3.50
208	Audio Enthuslast's Handbook	£0.85	BP148	Computer Terminology Explained	£1.95	BP250	Programming in FORTRAN 77	£4.95
214	Solid State Novelty Projects	£0.85	BP149	A Concise Introduction to the Language of BBC Basic	£1.95	BP251	Computer Hobbyists Handbook	£6.95
219	A Practical Introduction to Digital ICs	O.O.P.	BP162	An introduction to Z80 Machine Code	£2.75	BP258	Learning to Program in C	£4.95
BP28	Resistor Selection Handbook	£0.60	BP153	An Introduction to Programming the Amstrad CPC 464 & 664	£2.50	BP259	A Concise Introduction to UNIX	£2.95
BP37	50 Projects using Relays, SCRs and TRIACS	£2.95	BP154	An Introduction to MSX BASIC	£2.50	BP260	A Concise Introduction to OS/2	£2.95
BP39	50 (FET) Field Effect Transistor Projects	£2.95	BP156	An Introduction to QL Machine Code	£2.50	BP261	A Concise Introduction to Lotus 1-2-3 (Revised Edition)	£3.95
BP44	IC 555 Projects	£2.95	BP157	How to Write ZX Spectrum & Spectrum+ Games Programs	£2.50	BP262	A Concise Introduction to Wordperfect (Revised Edition)	£3.95
BP48	Electronic Projects for Beginners	£1.95	BP158	An Introduction to Programming the Commodore 16 & Plus 4	£2.50	BP263	A Concise Introduction to dBASE	£3.95
BP49	Popular Electronic Projects	£2.50	BP159	How to Write Amstrad CPC464 Games Programs	£2.50	BP264	A Concise Advanced User's Guide to MS-DOS	O.O.P.
BP56	Electronic Security Devices	O.O.P.	BP161	Into the QL Archive	£2.50	BP269	An Introduction to Desktop Publishing	£5.95
BP58	50 Circuits Using 7400 Series IC's	£2.50	BP162	Counting on QL Abacus	£2.50	BP270	A Concise Introduction to Symphony	£3.95
BP63	Alternating Current Theory (Elements of Electronics - Book 2)	£3.50	BP171	Easy Add-on Projects for Amstrad CPC 464, 664, 6128 and MSX Computers	£2.95	BP272	Interfacing PC's & Compatibles	£3.95
BP68	Choosing and Using Your Hi-Fi	£1.65	BP174	More Advanced Electronic Music Projects	£2.95	BP273	Practical Electronic Sensors	£4.95
BP74	Electronic Music Projects	£2.50	BP175	More Advanced Electronic Music Projects for the Amstrad CPC 464, 664 and 6128	£2.95	BP274	A Concise Introduction to SuperCal5	£3.95
BP76	Power Supply Projects	£2.50	BP182	MIDI Projects	£2.95	BP276	Short Wave Superhet Receiver Construction	£2.95
BP78	Practical Computer Experiments	£1.75	BP183	An Introduction to CPM	£2.95	BP277	High Power Audio Amplifier Construction	£3.95
BP84	Digital IC Projects	£1.95	BP187	A Practical Reference Guide to Word Processing on the Amstrad PCWB256 and PCW8512	£5.95	BP279	A Concise Introduction to Excel	£3.95
BP86	An Introduction to BASIC Programming Techniques	£1.95	BP189	Using Your Amstrad CPC Disc Drives	£2.95	BP280	Getting the Most From Your PC's Hard Disc	£3.95
BP90	Audio Projects	£2.50	BP190	More Advanced Electronic Security Projects	£2.95	BP283	A Concise Introduction to SmartWare II	£4.95
BP94	Electronic Projects for Cars and Boats	£1.95	BP191	Simple Application of the Amstrad CPCs for Writers	£2.95	BP284	Programming in QuickBASIC	£4.95
BP95	Model Railway Projects	£2.95	BP192	More Advanced Power Supply Projects	£2.95	BP286	A Reference Guide to Basic Electronics Terms	£5.95
BP97	IC Projects for Beginners	£1.95	BP193	LOGO for Beginners	£2.95	BP287	A Reference Guide to Practical Electronics Terms	£6.95
BP99	Mini-matrix Board Projects	£2.50	BP196	BASIC & LOGO in Parallel	£2.95	BP288	A Concise Introduction to Windows 3.0	£3.95
BP106	Modern Op-amp Projects	£1.95	BP197	An Introduction to the Amstrad PC's	£5.95	BP291	A Concise Introduction to Ventura	£3.95
BP109	The Art of Programming the 1K ZX81	£1.95	BP198	An Introduction to Antenna Theory	£2.95	BP292	Public Address Loudspeaker Systems	£3.95
BP114	The Art of Programming the 16K ZX81	£2.50	BP199	An Introduction to BASIC-2 on the Amstrad PC's	£5.95	BP293	An Introduction to Radio Wave Propagation	£3.95
BP122	Audio Amplifier Construction	£2.95	BP230	A Concise Introduction to GEM	£2.95	BP294	A Concise Introduction to Microsoft Works	£4.95
BP125	25 Simple Amateur Band Aerials	£1.95	BP243	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 1: Language	£3.95	BP298	A Concise Introduction to the Mac System & Finder	£3.95
BP126	BASIC & PASCAL in Parallel	£1.50	BP244	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 2: Graphics and Disk Files	£3.95	BP299	Practical Electronic Filters	£4.95
BP128	20 Programs for the ZX Spectrum & 16K ZX81	£1.95	BP245	Digital Audio Projects	£2.95	BP302	A Concise Users Guide to Lotus 1-2-3 Release 3.1	£3.95
BP129	An Introduction to Programming the ORIC-1	£1.95	BP246	Musical Applications of the Atari ST's	£5.95	BP303	Understanding PC Software	£4.95
BP132	25 Simple SW Broadcast Band Aerials	£1.95	BP247	More Advanced MIDI Projects	£2.95	BP307	A Concise Introduction to QuarkXPress	£4.95
BP133	An Introduction to Programming the Dragon 32	£1.95				BP311	An Introduction to Scanners and Scanning	£4.95
BP136	25 Simple Indoor and Window Aerials	£1.75				BP312	An Introduction to Microwaves	£3.95
BP137	BASIC & FORTRAN in Parallel	£1.95				BP313	A Concise Introduction to Sage	£3.95
BP138	BASIC & FORTH in Parallel	£1.95				BP314	A Concise Introduction to Quattro Pro	£4.95
BP143	An Introduction to Programming the Atari 600/800XL	£1.95				BP318	A Concise User's Guide to MS-DOS 5	£4.95
BP144	Further Practical Electronics Calculations & Formulae	O.O.P.				BP325	A Concise User's Guide to Windows 3-1	£4.95

IF NO PRICE IS SHOWN THE BOOK IS OUT OF PRINT (O.O.P.)
SEE PREVIOUS PAGE FOR FULL ORDERING DETAILS

PCB SERVICE

Printed circuit boards for certain EE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Electronics*, 6 Church Street, Wimborne, Dorset BH21 1JH. Cheques should be crossed and made payable to *Everyday Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail.
Please check price and availability in the latest issue.

Boards can only be supplied on a payment with order basis.

SALE! All p.c.b.s on this page reduced to **1/2 PRICE**

(Just send half the price shown, while stocks last.)
PCBS ON OPPOSITE PAGE PRICES AS SHOWN

PROJECT TITLE	Order Code	Cost
Video Guard Alarm	FEB '87 556	£3.80
Computer Buffer/Interface	MAR '87 560	£3.32
Fridge Alarm	MAY '87 565	£3.00
Mini Disco Light	JUNE '87	(sorry sold out)
Fermostat	JULY '87	(sorry sold out)
Monomixer	571	£4.75
Noise Gate	SEP '87 577	£4.41
BBC Sideways RAM/ROM	NOV '87	(sorry sold out)
Pseudo Echo Unit	DEC '87	(sorry sold out)
Game Timer	FEB '88 583	£3.55
SOS Alert	MAR '88	(sorry sold out)
Pipe & Cable Locator	APR '88	(sorry sold out)

PROJECT TITLE	Order Code	Cost
Multi-Chan Remote Light Dim Relay/Decoder	JUNE '88 601	£4.86
Power Supply	603	£3.00
Video Wiper	JULY '88 612	£6.75
Tea Tune Thermostat	AUG '88 609	£3.00
Time Switch	614	£4.84
Suntan Timer	610	£3.07
Car Alarm	615	£3.12
Eprom Eraser	OCT '88 620	£4.07
Doorbell Delay	NOV '88 616	£3.56
Infra-Red Object Counter (Set)	622/3/4	£9.28
Downbeat Metronome	DEC '88 629	£4.84
Phasor	631	£5.64
Continuity Tester	FEB '89 619	£2.67
Mini PSU	636	£3.23
Sound-to-Light Interface	MAR '89 637	£6.24
Midi Pedal	639	£7.00
Midi Merge	640	£3.00
Audio Lead Tester	641	£5.77
Light Sentinel: Main Board	APR '89 632	£9.20
Remote Interface (4 bds)	633	£4.59
4-Channel Auto-Fader Interface	642	£6.80
Electron A/D Interface	MAY '89 645	£4.84
Spectrum EPROM Programmer	JUNE '89 628	£7.87
Programmable Pocket Timer	JULY '89 648	£3.82
Electronic Spirit Level	AUG '89 649	£3.85
Distance Recorder	651	£5.23
Xenon Beacon	SEP '89 650	£4.13
Probe Pocket Treasure Finder	653	£4.12
Power Supplies: Fixed Voltage	654	£4.08
Variable Voltage	655	£4.48
Music on Hold	OCT '89 646	£3.85
Power Supplies - 25V 700mA	656	£4.35
30V 1A	657	£4.55
EE Seismograph - Control	658	£4.08
Detector	659	£4.22
Lego/Logo & Spectrum	660	£6.49
Wash Pro	NOV '89 643	£3.83
Logo/lego & Sepctrum Interface	664	£5.60

PCB SERVICE

See opposite page for ordering details.

PROJECT TITLE	Order Code	Cost
Biofeedback Monitor - Front End Processor	NOV 89 661 662	£4.52 £4.56
EEG Electrode Impedance Meter	DEC 89 665	£3.98
Biofeedback Signal Generator	JAN 90 666	£4.08
Quick Cap Tester	FEB 90 668	£3.92
Weather Stn: Anemom. - Freq./Volt Board	670	£3.94
Optional Display	669	£3.73
Wind Direction	673/674	£4.22
System Power Supply	675	£3.59
Prophet In-Car Ioniser	676	£3.18
Weather Stn: Display Driver	MAR 90 672 & 678	£4.22
Display and Sensor	671	£4.47
Fermostat Mk2	677	£4.28
Superhet Broadcast Receiver/Tuner/Amp	679/680	£4.22
Stereo Noise Generator	APR 90 681	£4.24
Digital Experimenter's Unit - Pulse Generator	682	£4.46
Power Supply	683	£3.66
Enlarger Timer	684	£4.28
Weather Stn: Rainfall/Sunlight Display	685	£4.27
Rainfall Sen and Sunlight Sen	686/687	£4.16
Amstrad Speech Synthesiser	MAY 90 689	£4.68
80 Metre Direct Conversion Radio	JUN 90 691	£4.95
Mains Appliance Remote Control	JUL 90	
Encoder Board A	694	£6.61
Encoder Board B	695	£4.78
The Tester	696	£4.15
Mains Appliance Remote Control	AUG 90	
Mains ON/OFF Decoder	697	£4.55
(5 or more 697's ordered together £3.25 each)		
Simple Metronome	698	£3.94
Hand Tally: Main Bd and Display Bd	SEP 90 699, 700	£10.95
Alarm Bell Time-Out	701	£4.10
Mains Appliance Remote Control		
Temperature Controller (p.c.b. only)	702	£5.20
Ghost Waker	OCT 90 703	£4.32
Frequency Meter	704	£5.25
Freq. Meter/Tachometer	NOV 90 705	£3.98
EE Musketeer (TV/Video/Audio)	706	£5.78
Colour Changing Christmas Lights	DEC 90 707	£4.39
Microcontroller Light Sequencer	708/709	£10.90
Versatile Bench Power Supply Unit	710	£4.24
Teach-In '91, Part 1 - L200 Module	711	£3.93
Dual Output Module	712	£4.13
LM723 Module	713	£4.21
Spatial Power Display	JAN 91 714	£5.33
Amstrad PCW Sound Generator	715	£5.03
Teach-In '91, Part 2 - G.P. Transistor Amp	717	£3.77
Dual Op.Amp Module	718	£3.83
Intercom (Teach-In '91 Project 2)	JAN 91 719	£4.41
Analogic Test Probe	720	£3.24
MARC Phone-In	FEB 91 721	£6.87
Teach-In '91 Part 3 - TBA820M Amplifier	723	£4.05
High Quality Power Amp	724	£4.93
Bench Amplifier (Teach-In '91 Project 3)	725	£4.45
Gingernut 80m Receiver	FEB 91 726/7/8	£3.06
R.F. section (726), Voltage Regulator (727)		per board
Audio Amplifier (728)		£8.16
Pocket Tone Dialler	MAR 91 729	£4.36
Battery To Mains Inverter	730	£4.97
Simple Basic Alarm	731	£4.50
Car Code Lock (pair)	732a/b	£4.69
Teach-In '91 Part 4 -	MAR 91	
Sinusoidal Oscillator	733	£4.39
8038 Oscillator	734	£4.15
Waveform Generator (Teach-In '91 Project 4)	735	£4.72
Humidity Tester	APR 91 716	£4.97
Model Train Controller (double-sided)	736	£9.75
Electronic Die (Teach-In '91 Project 5)	737	£4.93
Teach-In '91 Part 5 - Digital Counter Module	738	£4.35
Modular Disco Lighting System	MAY 91	
Switched Power Output Module	739	£5.91
Digital LCD Thermostat-Control Board	740	£4.05
-Power/Relay Board	741	£3.76
Pulse Generator (Teach-In '91 Project 6)	742	£4.97
Teach-In '91 Part 6 - Timer Module	743	£4.62
Digilogue Car Tachometer	JUN 91 744	£5.63
Modular Disco Lights - Simple Chaser	745	£5.00
Sweeper Module	746	£5.17

PROJECT TITLE	Order Code	Cost
Automatic Light Control - PSU Board	JUN 91 747	£4.88
Logic Board	748	£5.17
Radio Receiver (Teach-In '91 Project 7)	749	£4.57
Teach-In '91 Part 7 - R.F. Amplifier Module	750	£4.23
Modular Disco Lights - Masterlink	JULY 91 752	£6.36
Ultrasonic Proximity Meter		
Display Unit (753) & Sensor Unit (754)	753/754	£7.06
Disco Lights (Teach-In '91 Project 8)		
PSU and Pre-amplifier	755	£4.54
Low, Mid, High Filter/Triac (set of 3 boards)	756	£11.00
Teach-In '91 Part 8 - Solid State Switch Module	757	£4.24
Mod. Disco Lights - Pattern Gen	AUG 91 760	£6.79
Teach-In '91 Part 8 - Light Sensitive Switch	761	£4.74
Opto-Link (Teach-In '91 Project 9) - Transmitter	762	£4.85
Receiver	763	£4.88
Portable PESt Scarer	764	£3.77
Capacitance Meter	SEP 91 751	£5.17
Modular Disco Lights - Dimmer Interface	765	£8.17
Mod. Disco Lights	OCT 91	
VU Sound Module (Double-sided)	767	£8.68
UV Exposure Unit	768	£4.63
PC-Scope Interface - Main Board	769	£6.95
Expansion Plug (Double-sided)	770	£5.96
Mod. Disco Lights	NOV 91	
Superchaser (Double-sided)	771	£6.91
Supersweep (Double-sided)	772	£8.26
Bicycle Alarm	773	£5.01
Darts Scorer	774	£7.90
Knockerbox	DEC 91 775	£5.35
Signal Generator - Main Board	776	£7.46
PSU	777	£4.73
Mind Machine - Main Board	778	£7.00
Auto Nightlight	779	£5.03
Mind Machine - Programmer Board	JAN 92 780	£7.39
Transistor Checker	781	£4.63
Stepping Motor Driver/Interface	782	£10.39
Micro-Sense Alarm	783	£5.42
Telesound	FEB 92 784	£4.66
Programmable Timer	785	£4.63
Auto Garage Light	MAR 92 786	£6.10
Versatile BBC Computer Interface	787	£11.59
Economy Seven Timer	788	£5.20
Sonic Continuity Tester	APR 92 789	£4.79
Telephone Ringer	790	£5.46
Experimental Weighing Scale	MAY 92 792	£5.17
12V Drill Charger/PSU (both boards)	793	£5.31
Digital Servo Interface	JUNE 92 791	£4.73
Tie Pulsar	794	£5.19
CCD Reverb Unit	795	£6.39
Switch-Mode Power Supply	796	£7.01
UV Exposure Timer	JULY 92 797	£5.33
Cricket Game	798	£6.77
Quick Prom	799	£5.61
Gas Alarm	AUG 92 800	£5.47
Dual Metronome	801	£6.74
Ultrasonic Tape Measure	SEP 92 802	£6.06
Quicktest	803	£4.82
Extended Range Capacitance Meter	OCT 92 804	£5.63
Whistle Switch	805	£4.89
Traffic Lights System	806	£5.04

EE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name.....

Address.....

VISA

I enclose payment of £..... (cheque/PO
in £ sterling only to
Everyday Electronics)
Access (MasterCard) or Visa No.
Minimum order for credit cards £5

--	--	--	--	--	--	--	--	--	--


Signature..... Card Ex. Date.....

Please supply name and address of card-holder if different from the address shown

BLOCK CAPITALS PLEASE

REPORTING AMATEUR RADIO

Tony Smith G4FAI

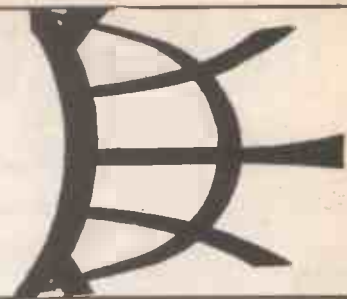

AMATEURS TO THE RESCUE!

The days of amateur radio coming to the rescue of seafarers in distress are not yet over. A recent report in the *W5YI Report*, an amateur radio newsletter published in the USA, describes how three amateurs in Hawaii assisted a ship in trouble on June 7 this year.

The amateurs were in the shack of Jim Reid, KH6/W6KPI, who runs the intriguingly titled "Lawailoa Bed and Breakfast Retreat for Hams" on the island of Kauai. At 0240 UTC, John Hamby, WB4UZW, was talking to friends in North Carolina and Virginia on the 20 metre band when the trio, completed by Bill Tise, KB4UZN, suddenly heard a distress call breaking in on the conversation and signing "WYZ 2403". This claimed an emergency situation on board a ship off the coast of Cuba with its navigation system no longer working after the ship had been struck by lightning.

At first this was thought to be a hoax but the breaker identified himself as the skipper of the commercial vessel *Sea Harvest* out of Fort Meyers, Florida. Not knowing where he was or where he was headed he was worried that he might enter hostile Cuban waters. He had stopped his engine and had begun making distress calls without getting a response, finally moving into the amateur band to seek help.

John contacted an amateur friend in North Carolina who called the Coast Guard. Within minutes NMA-Miami, a Coast Guard communications station, appeared on the amateur frequency calling *Sea Harvest* but the ship could not hear it.

SOS LIGHT SIGNALS

For the next few hours Jim Reid's station relayed information between *Sea Harvest* and the Coast Guard with the three amateurs taking it in turns at the microphone. The ship reported pitch dark clouded skies with frequent squalls and lightning strikes.

An unidentified vessel approached and the Coast Guard suggested the ship send SOS light signals. The unlit mystery vessel gave no response but circled the *Sea Harvest*, gradually closing in.

With all messages still relayed through Hawaii, the Coast Guard was informed that the other vessel appeared to have about 50 men on deck, none of whom spoke English. The Coast Guard suggested several Spanish phrases for the captain to shout, such as "Which way is Cayman Island?" and "Which direction is south?"

By this time, other amateurs were on frequency, following the drama, and a Mexican station suggested he shout "ayuda", the Spanish word for "help". Eventually the Spanish-speaking sailors understood and pointed to the south. The captain took this to mean this would keep

him clear of Cuban waters, and the other boat sailed away to the east.

Sea Harvest and the Coast Guard finally established direct radio contact and the ship was directed to start its engine and sail south out of harm's way. At 0635 UTC the three amateurs in Hawaii signed off. The captain, Eddie Jacobsen, expressed his deep thanks to them and all the other amateurs who had helped with the relay link, marvelling that he could obtain help literally from the other side of the planet via amateur radio. He and the Coast Guard then changed over to a marine frequency.

Interestingly, Jim Reid is currently involved with a local restriction that could force him to lower his 45 foot antenna to 30 feet and has to appear before a hearing to argue why the extra height is necessary. Without that extra height his station might never have established contact with the *Sea Harvest*, and it is to be hoped that the hearing will recognise that on occasions amateur radio can be very much more than "just a hobby".

NEW RADIO SPECTRUM REVIEW

The President of the Board of Trade has announced a third radio spectrum review by an independent committee, this time to examine the frequency range 28-470MHz which among other services contains several amateur radio bands.

According to a DTI press release of July 14, this frequency range is one of the most intensively used parts of the radio spectrum and demand for access is increasing. The aim of the review is to examine existing and planned use of the spectrum and to make recommendations on that use taking into account national and international developments in radiocommunications, current and foreseen.

The Committee will welcome evidence from those having an interest in use of this part of the radio spectrum and will complete its report by October 1993. The amateur bands concerned are: 28-00-29-70; 50-00-52-00; 70-00-70-50; 144-0-146-0; and 430-0-440-0 MHz, and presumably the Radio Society of Great Britain (RSGB) will be submitting evidence to the Committee relating to amateur use of these frequencies.

PREVIOUS RECOMMENDATIONS

When management consultants previously reported to the government on the possible benefits of introducing market forces and a price mechanism into radio spectrum management (reported in this column August 1987) the RSGB over-optimistically anticipated that amateur radio would fall well outside the scope of that review.

In fact, the report, while recognising that amateurs have a special place in the radio spectrum, recommended against further frequency allocations for amateurs

and suggested that reductions of existing allocations might be considered.

After the report was published, the Society was apparently still confident that amateur radio was safe in the face of ever-increasing commercial demands for limited spectrum and one can only hope they were right. In the USA, however, amateurs have already lost the 220-222 MHz band as a result of pressure from the giant United Parcel Service (UPS) and, again according to the *W5YI Report*, the Federal Communications Commission (FCC) currently has 60,000 applications for licenses in that band, including 174 for nationwide channels.

A warning note can be detected in a repeated call from the FCC's Chairman for authority from Congress to auction licenses to the highest bidder rather than simply charge processing fees. With governments everywhere continually looking for extra revenue it must surely be only a question of time before the radio spectrum is commercially valued. It will then be the task of the RSGB and other national radio societies to fight to ensure that the traditional non-commercial use of the spectrum by amateurs can continue to exist within such a framework.

NEW RE-CHARGEABLE BATTERY

After writing recently about the reservations and provisos necessary to obtain optimum performance from NiCad batteries (EE, December 1991), I was interested to discover that an article in *Batteries International*, January 1992, reports that reusable 1.2 volt alkaline-manganese (RAM) high energy cells are expected to be marketed sometime soon, possibly at half the cost of equivalent size NiCad cells.

Apparently, in the 1960's Ever-Ready (US) sold a rechargeable version for portable TVs and lanterns which was withdrawn later due partly to safety considerations. Recent technology has overcome the original problems and the new product is claimed to have advantages over NiCads and even lead acid batteries (in a flat-plate version).


An AA-size RAM, for instance, is claimed to produce 2000mAh of energy compared with 500-600mAh for the same size standard NiCad. Other advantages claimed include a charge retention period of up to three years compared to 3-6 months for NiCads, no "memory" effect, and non-toxicity in mercury-free versions.

From the information given it sounds as if these new batteries will overcome most of the disadvantages of NiCads in amateur radio which I described previously. I hope, however, that the price of chargers won't be exorbitant and that at least one version will be available to charge ten cells in one go!

**1992
CATALOGUE
NOW FREE**

CRICKLEWOOD ELECTRONICS

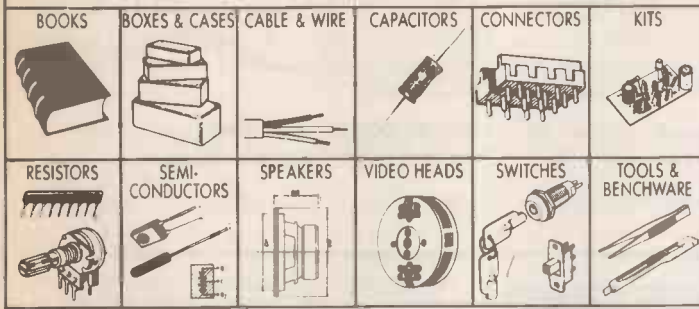CRICKLEWOOD ELECTRONICS LTD, 40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
Tel: 081 452 0161 Fax: 081 208 1441



SEND NOW FOR THE **CRICKLEWOOD ELECTRONICS** COMPONENT CATALOGUE
ONE OF THE BEST RANGES AVAILABLE

Name.....
Address.....
.....
.....

LOW COST 418MHz UHF RADIO SWITCHING

AS USED BY THE PROFESSIONAL SECURITY MARKET

Incorporating the latest Surface Acoustic Wave technology, the system consists of a small "zero-power", UHF transmitter with digital encoder and a UHF receiver unit with digital decoder and momentary output. Transmitter available either as fully assembled unit in its own key-lob case which is fully MPT approved (codes set by cutting tracks) or in kit form with 8-way DIL switch. Receiver also available in two kit forms, one which uses cut tracks to set code (over 13,000 codes available), the other uses an 8-way DIL switch (256 codes).

Kit Sizes:	Tx 45 x 30mm	Rx (both) 45 x 55mm
Kit Supplies: Tx 3-15V	Rx (both) 9-15V	Range: Up to 100m
Approved Key-lob Transmitter: TXKF.....	£25.99	
Individual Kit Transmitter: TXKT.....	£15.99	
Individual Kit Receiver (8-way DIL switch): RXDS.....	£19.99	
Individual Kit Receiver (Cut Tracks): RXCT.....	£18.99	
1 x TXKF + 1 x RXCT: SYS1.....	£39.99	
1 x TXKT + 1 x RXDS: SYS2.....	£29.99	

Quantity Discounts Available. Please allow 28 days for delivery
Cheques/POs to:

BLB Electronics

341 Darwen Road, Bromley Cross, Bolton BL7 9BY

LEDs 3mm or 5mm red or green 6p each, yellow 11p each. High intensity red, green or yellow, 5mm 30p each.
Cable ties 1p each, £6.95 per 1000, £49.50 per 10,000.
Stepping motor 4 phase 12V 7.5' step 50 ohms.....£8.95
SAA1027 stepping motor driver chip.....£3.95
FM Transmitter kit, good quality sound.....£8.60
High quality photo resist copper clad epoxy glass boards
Dimensions single sided double sided
3x4 inches £0.95 £1.07
4x8 inches £2.40 £2.68
6x12 inches £6.37 -
12x12 inches £10.66

Rechargeable Batteries

AA (HP7) 500mAh.....£0.99
AA 700mAh.....£1.95
C 2AH with solder tags.....£3.60
D 4AH with solder tags.....£4.95
1/2AA with solder tags.....£1.55
AAA (HP16) 180mAh.....£1.75
AA 500mAh with solder tags.....£1.55
C (HP11) 1.8AH.....£2.20
D (HP2) 1.2AH.....£2.60
PP3 8.4V 110mAh.....£4.95
Sub C with solder tags.....£2.50
1/3 AA with tags (Philips CTV).....£1.95
Standard charger, charges 4 AA cells in 5 hours or 4Cs or 4Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time).....£5.95
High power charger, as above but charges the Cs and Ds in 5 hours; AAs, Cs and Ds must be charged in 2s or 4s.....£10.95

Special offers - please check for availability
F cells 32dia x 87mm.....£3.95
F cell with solder tags, 1.2V.....£4.30
42mm x 16mm dia. 1.2V.....£1.45
Stick of 4 171mm x 16mm dia., with red & black leads 4.8V.....£5.95
4 cell battery 94mm x 25mm dia. (1/2C cells).....£3.50

Computer grade capacitors with screw terminals
3800µf 20V £2.50; 8700µf 10V £1.95;
8600µf 15V £2.95; 10000µf 16V £1.50
7 segment common anode led display, 12mm.....£0.45
LM2931 AT 5.0 low drop out 5V regulator TO220 package.....£0.85
7812 and 7912 12V 1A regulators.....£20.00 per 100
LM337K TO3 case variable regulator.....£1.60
BS250 P channel mosfet 45p, BC559 transistor per 100 £3.95
74LS05 hex inverter.....£10.00 per 100
Used 8748 Microcontroller.....£3.50
SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet.....£1.95
AM27502.....£1.25 each; 90p 100 +
CD4007UB.....10p 100 +, 6p 1000 +
TV Mains switch, 4A double pole with momentary contacts for remote control, pack of 10 £3.95
box of 60 £19.95

DC-DC converter, Reliability model, V12P5, 12V in 5V 200mA out, 300V input to output, isolation with data, £4.95 each or pack of 10 - £39.50
Hour counter used 7 digit 240V ac 50Hz.....£1.45
Resistor pack 2500 resistors 1/8-2W 50 different values.....£9.95

Resistor jumbo pack 25000, 1/4 and 1/2W resistors our choice of values and size, will be mainly in boxes or rolls of 1000, 2000 and 5000 of one type.....£26.00
Qwerty keyboard, 58 key good quality switches, new.....£5.00
Qwerty keyboard with serial output, no data (used).....£6.00
Polyester capacitors, box type, 22.5mm lead pitch
1µf 250V dc 20p each, 15p 1000+, 10p 1000+
2.2µf 250V dc 30p each, 20p 100+, 15p 1000+
3.3µf 100V dc 30p each, 20p 100+, 15p 1000+
1µf 50V bipolar electrolytic axial leads, 15p each, 7.5p 1000+
0.22µf 250V polyester axial leads, 15p each, 100+ 7.5p each
Philips 123 series solid aluminium axial leads
33µf 10V & 2.2µf 40V 40p each, 25p 100+
Multilayer AVX ceram capacitors, all 5mm pitch, 100V 100pf, 150pf, 220pf, 10,000pf (10n)
10p each, 5p 100+, 3.5p 1000+
Wetwyn W23 9W 120 ohm 35p each, 20p 100+
680 ohm 2W metal film resistor, 4p 100+ 2p 1000+

Solid carbon resistors, very low inductance, ideal for RF circuits, 27ohm 2W, 68ohm 2W 25p each, 15p each 100+, we have a range of 0.25W, 0.5w, 1w and 2w solid carbon resistors - please send SAE for list

Intelligent 4 digit alphanumeric (5x7 dot 0.145") red LED display, 12 pin 0.6 inch wide package, Siemens type DLRT1414 £2.50 each, £2.00 30+, data sheets £1.00
AMD 27256-3 Eproms £2.00 each, £1.25 100+
DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each, 40p 100+

MODEMS
V22/V22bis IBM PC internal full length card modem, BT approved, can be set to com 1 or 2, 1200/2400 baud with software and manual, not Hayes compatible, made by Plessey.....£55.00
V32 9600 baud and 4800 baud GEC Plessey telecom external modem, model 9632, Hayes compatible and BT approved, with auto call, auto answer, using V25, V25bis and Hayes AT protocols and V54 remote + local diagnostics. It does not work on slower speeds, V22/1200 baud etc and needs 1 internal dip switch to be switched on to select Hayes commands. It comes with a 100+ page comprehensive A4 size manual. An all together brilliant machine for only.....£199 + VAT = £233.83

All products advertised are new and unused unless otherwise stated.
Wide range of CMOS TTL 74HC 74F Linear Transistors kits, rechargeable batteries, capacitors, tools etc. always in stock
Please add 95p towards P&P
VAT included in all prices

JPG ELECTRONICS
276-278 Chatsworth Road
Chesterfield S40 2BH
Access/Visa Orders:
(0246) 211202
Callers welcome

Hesing Technology

Cromwell Chambers, 8 St. Johns Street,
Huntingdon, Cambs. PE18 6DD

Tel: (0480) 433156
Fax: (0480) 214488

TEST EQUIPMENT


Supply
Maintenance
Commissioning

SYSTEM CONSULTANCY

Replacement Parts
Supply of Service &
Operators Manuals
Components

Distributors for:

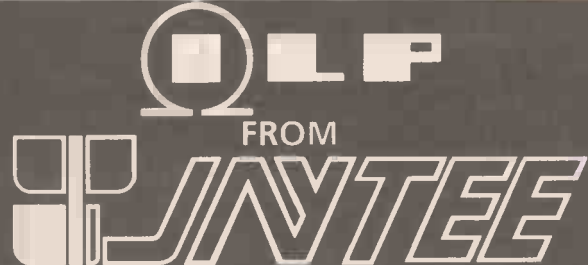WAUGH INSTRUMENTS, RAMTEST LTD., KRENZ ELECTRONICS, PANTHER



New for 1992

★ **New MOSFET Amplifiers**
improved range of SMOS modules
30W, 30+30W, 60W, 120W

★ **20 watt Class A Amplifier**

★ **Low profile PCB Transformers**

a range of encapsulated transformers
4VA, 6VA, 10VA, 18VA, 24VA, 30VA

Write or phone for data and prices...
which include details of standard range of toroidal transformers and audio modules.

No price increase for 1992

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254. Fax: (0227) 365104

EE reaches twice as many UK readers than any other independent monthly hobby electronics magazine, our audited ABC sales figures prove it. EE has been the leading independent monthly magazine in this market for the last seven years

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+ VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+ VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Electronics. VAT must be added. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 881749.

For rates and information on display advertisements (1st page and larger spaces) please contact our Advertisement Manager, Peter Mew on 0255 850596.

SERVICE MANUALS

Available for Most Equipment
TV, Video, Audio, Test etc
Any Age, Make or Model

Write or Phone for Quotation

MAURITRON (EE)

8 Cherry Tree Road
Chinnor, Oxfordshire

OX9 4QY

Tel: (0844) 351694

Fax: (0844) 352554

SOLAR PANELS

Special offer 12V nom (20V o/c) 80mA. 12" x 6" pre wired Amorphous Silicon panel £4.50 includes P&P. Many other sizes, wind generators and other products.

Orders to (Cat 2 x 1st class stamps)

Robert Keyes, 4 Glanmor Crescent
Newport Gwent NP9 8AX

AT LAST, HERE IT IS

'The World Of Bugs And Minitransmitters'
Dozens of circuits in one book. Limited edition, 1,000 copies only available.

Special Offer Price £7.95

Inc. Post & Packing. Cheques/PO's to:

Gainsford Electronics
71 Gainsford Road
Southampton SO2 7AW

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY

1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps d.c. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection

Fully variable
Operates from 240V a.c.
Compact Unit.
Size 9 x 5 1/2 x 3in.



£45 inc. VAT

+ Post and insurance £4

NEW MODEL. Up to 38volts d.c. at 6 amps 10 amps peak. Fully variable Twin panel meters. Size 14 1/2 x 11 x 4 1/2in. £96 inc VAT. Carr £6.

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 081-684 1665

List. Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT AN EQUAL OPPORTUNITIES PROGRAMME

O.N.C., O.N.D. and H.N.C.

Next course commences
Monday 21st September 1992
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EE) 20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: 071-373 8721

N. R. BARDWELL LTD (EE)

200	Signal diodes 1N4148.....	£1.00
75	Rectifier Diodes 1N4001.....	£1.00
75	Rectifier Diodes 1N4003.....	£1.00
50	Rectifier Diodes 1N4007.....	£1.00
56	Rectifier Diodes 1N5401.....	£1.00
10	NE555 Timer i.c.s.....	£1.00
5	741 Op Amp i.c.s.....	£1.00
8	C10801 400V 6 amp thyristors.....	£1.00
8	BF751 Transistors.....	£1.00
30	BC478 Transistors.....	£1.00
30	MPSA92 Transistors.....	£1.00
25	Ass'd. high brightness l.e.d.s.....	£1.00
50	Axial l.e.d.s (Diode package) wide angle red.....	£1.00
50	Rectangular red l.e.d.s.....	£1.00
20	Miniature axial l.e.d.s super bright red.....	£1.00
24	Miniature red l.e.d.s 3mm dia.....	£1.00
12	Ass'd. seven segment displays.....	£1.00
4	.43" Com. anode seven segment displays.....	£1.00
100	22NF 100V radial film capacitors.....	£1.00
100	33NF 50V radial film capacitors.....	£1.00
200	Ass'd. disc ceramic capacitors.....	£1.00
80	4U7 16V Radial electrolytics.....	£1.00
75	4U7 63V Radial electrolytics.....	£1.00
80	10U7 16V Radial electrolytics.....	£1.00
50	10U7 50V Radial electrolytics.....	£1.00
80	22U7 25V Radial electrolytics.....	£1.00
60	33U7 16V Radial electrolytics.....	£1.00
60	22U7 50V Radial electrolytics.....	£1.00
50	47U7 50V Radial electrolytics.....	£1.00
80	100U7 10V Radial electrolytics.....	£1.00
50	220U7 16V Radial electrolytics.....	£1.00
60	470U7 10V Radial electrolytics.....	£1.00
40	100U7 10V Radial electrolytics.....	£1.00
30	Ass'd. IF transformers.....	£1.00
48	Ass'd. coil formers.....	£1.00
100	Ass'd. RF chokes.....	£1.00
30	Ass'd. dif sockets up to 40 pin.....	£1.00
30	Assorted socket/comms/edge-dll-sil-etc.....	£1.00
20	1 inch Glass reed switches.....	£1.00
10	4P 3W MBB min. rotary switches.....	£1.00
20	Min SP/CO slide switches.....	£1.00
20	Magnetic ear pips plus lead & plug.....	£1.00
1	Peltier effect heat pump.....	£1.95
1	10 watt Stereo amplifier, 4 controls plus data.....	£2.95
1	10mm Flashing l.e.d. red.....	£0.75
1	10mm Ultra bright l.e.d. red 300 MCD.....	£0.60

Prices include VAT, postage £1.00. Stamp for Lists

288 Abbeydale Road, Sheffield S7 1FL
Phone (0742) 552886. Fax (0742) 500689

THE BRITISH AMATEUR ELECTRONICS CLUB

exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.

For details, write to the Secretary

Mr J. S. Hind, 7 Carlyle Road
West Bridgford, Nottingham NG2 7NS
Space donated by Everyday Electronics

Fuselodge Ltd.

267 Acton Lane
Chiswick, London W4 5DD

Telephone/Fax

081-994

6275

We stock a large range of Electronic components, semiconductors, switches, resistors, capacitors, transformers, fans, cables, leads, boxes, tools, etc. Power supplies, test equipment. Custom made S.M. power supplies.

Mall order & Credit Cards accepted

NEW VHF MICROTRANSMITTER KIT

Tunable 80-135MHz, 500 metre range, sensitive electret microphone, high quality PCB.
SPECIAL OFFER complete kit ONLY £6.95
Assembled and ready to use £9.95 post free.
Credit card orders telephone 021 411 1821. Fax 021 411 2355
Send 2x1st class stamps for Catalogue. Cheques/P.O.s payable to:

QUANTEK ELECTRONICS

Kits Dept. (EE), 3 Houlday Road, West Heath,
Birmingham B31 3HL
SHOP NOW OPEN - CALLERS WELCOME

Miscellaneous

G.C.S.E. ELECTRONICS KITS at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT ELECTRONICS, 70 Oxford Road, Clacton CO15 3TE.

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poynings Drive, Sussex BN3 8GR, or phone Brighton 720203.

STUDY ELECTRONICS on the BBC Micro. An interactive approach to learning. Four program titles available 'Introduction to Electronics Principles', 'Electronics Mathematics', 'Digital Techniques' and now 'Programming for Electronics'. Programs include theory, examples, self test questions, formulae, charts and circuit diagrams. User inputs and calculated outputs, £29.95 each plus £2p&p. Cheque or Postal Order to E.P.T. Educational Software, Pump House, Lockram Lane, Witham, Essex CM8 2BJ. Please state BBC 'B' or Master series and disc size.

ENCAPSULATED POWER AMPLIFIERS, 2.2W. Dimensions 40 x 35 x 20mm. Internal heatsink, only four connections. SAE Data sheet 1, £3.29; 2+, £2.99. Bulk discounts. David Leitch, 48 Frere Avenue, Fleet, Hants GU13 8AP.

BARGAIN clearout bags of new assorted components only £3 inclusive. 091 5489279.



Cooke International FOR SALE

USED TEST EQUIPMENT
Scopes, Sig. Gens, PSU's, Power Meters, DVM's, Oscillators, Attenuators, etc.

Open Mon-Fri 9am-5pm or Phone
Copy Service for Workshop Manuals available

SATURDAYS
BARGAIN STORE OPEN 10am-4pm
CASH ITEMS TO CLEAR.

Contact: Cooke International, Units 4/5,
Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex PO22 0EB
Tel: 0243 545111 Fax: 0243 542457
Wide range of items available. Send SAE for lists

Typefit

The Typesetting programme for all your Typesetting needs.

If you need typesetting for your Adverts, Brochures, etc. Typefit can help you. Please telephone

0202 882299

MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 10 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 100 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for **FREE INFORMATION** on the course of your choice. (Tick one box only)

Electronics	<input type="checkbox"/>	TV, Video & Hi-Fi Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Refrigeration & Air Conditioning	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCSE/GCE/SCE over 40 examination subjects to choose from			

Name _____ Address _____

ICS International Correspondence Schools Dept ECS A2
312/314 High Street, Sutton, Surrey SM1 1PR or 041-221 7373 (24 hours).

Technical Information Services

76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML9 1HE

Tel. (0698) 884585 Mon-Fri 8.30am - 5.00pm

Tel. (0698) 883334 Outwith business hours

FAX facility available all day on both lines

Write now with an SAE for your

FREE QUOTE FREE VOUCHERS & FREE CATALOGUE

Remember, not only do we have EVERY service sheet ever produced, but we also have

THE WORLDS LARGEST COLLECTION OF SERVICE MANUALS

& WE ARE SOLE SUPPLIERS OF VARIOUS FAULT-FINDING GUIDES REPAIR MANUALS & TECHNICAL MANUALS

CTV, Video, CD, Hi-Fi, Camcorder, Satellites, Computers, Domestic Equip', ...etc.

DATA REFERENCE MANUAL "...essential for the serious electrician"
FREE updating and a 10% discount voucher only £5.95
Incorporates Unique Model Identification and Chassis Data

Millions of quality components at lowest ever prices!

Plus Tools, Watches, Fancy Goods, Toys.
Mail order UK only.

All inclusive prices -

NO post, or VAT etc to add on.

Send 34p stamped self addressed label or envelope for catalogue/clearance list.

At least 2,100 offers to amaze you.

Brian J Reed

6 Queensmead Avenue, East Ewell

Epsom, Surrey KT17 3EQ

Tel: 081-393 9055

COMPONENTS

For TV ★ Video
Audio ★ Computer

WE CAN SUPPLY A VAST RANGE OF SPARES for many makes of TV, Video, Computer & Audio Equipment. WRITE (Encl. s.a.e. please) or PHONE FOR A 'PRICE & AVAILABILITY' on your requirements. **0452 526883**

COMPUTER SPARES

AMSTRAD/SINCLAIR	ATARI
40010 G. Array.....£18.86	CO25913 DMA (ST).....£33.24
PCW 9512 Serv. Manual £14.49	User Manual (STFM).....£10.00
CPC464 Serv. Manual.....£8.67	PC900V/H11L3 (ST).....£2.88
AY38912.....£7.06	ROM Basic (XE/L).....£4.58
SED9420CAC.....£14.93	THERMISTOR (ST-PSU).....£1.37
STK7356.....£12.49	CNY65 (ST-PSU).....£4.42
TEA2000.....£4.49	PC713V (STE-PSU).....£2.94
TMS4532-NL.....£1.72	25C2331 (ST-PSU).....£1.59
UL46C001E.....£17.81	COMMODORE
ULA7K010/400056.....£16.72	17.7344MHz Xtal.....£4.99
ZTX650.....£0.49	C64C User Manual.....£4.39
ZX8302(OL).....£10.98	C64 User Manual.....£4.25
ZX8401.....£7.94	6510 CPU.....£10.03
Spec. #2 ROM.....£16.89	6526 CIA.....£11.11
Spec. 48K Speaker.....£1.74	6569 VIC.....£19.95
Spec. 48K Membrane.....£4.73	8520 Amiga.....£11.25
+128K Membrane.....£8.39	8565 VIC.....£23.96
Spec. DC Skt. (PCB).....£0.89	906114-01 PLA.....£9.24
EPSON	251641-02 PLA.....£4.06
C78010BD003 CPU.....£30.24	MB81416-12 DRAM (C16) £4.99



MARAPET (EEK)
1 HORNBEAM MEWS
GLOUCESTER GL2 0UE

Order by Post or Phone. We accept payment by VISA, ACCESS, DELTA, SWITCH, Cheque or P.O. Post & Packing is £1.20. No VAT to add on.
All items subject to availability.
Prices can change without notice.

19" RACK MOUNTING EQUIPMENT CASES

This range of 19" rack cases features satin black finished 16SWG (1.5mm) steel front panels (no fixing holes visible), with the rear box assembly constructed from 20SWG (9mm) steel. The standard units are 10" (254mm) deep. 19" project cases only 4" (101mm) deep and are available in the following popular sizes:

PROJECT CASES		
Type	Height	Price
PU1	1 1/2" (44mm)	£18.02
PU2	3" (88mm)	£20.07
PU3	5 1/2" (133mm)	£22.11
PU4	7" (178mm)	£24.16
PU6	10 1/2" (266mm)	£28.25

EQUIPMENT CASES		
Type	Height	Price
U1	1 1/2" (44mm)	£22.33
U2	3" (88mm)	£25.85
U3	5 1/2" (133mm)	£29.38
U4	7" (178mm)	£31.72



Delivery included (UK only).
All prices include VAT.
BLANKING PANELS, RACKING CONSOLES and RACK CABINETS are also available.
Please send SAE for details.
Tel: 0272 373883 for Access/Visa Sales or cheque with order to:

RACKZ PRODUCTS
PO Box 1402 Mangotsfield, Bristol, England, BS17 3RY

A. C. ELECTRONICS SURVEILLANCE?

Easy-Build Kits or Built Units.

Microtransmitter, 15mm x 25mm, received on standard VHF radio; kit £5.99, built £9.99 (picks up whispers and transmits up to 1/2 mile). Telephone transmitter, can be hidden in handset; kit £5.99, built £9.99. "Stinger" shock circuit, can run off 9V battery, unpleasant shock, originally for electric fences etc; kit £11.99, built £19.99. Lots of locksmith tools, transmitters in calculators, plug-in adaptors, alternative technology plans, surveillance kits etc.

Send 4 x 1st class loose stamps for list - Cheque/POs to:

A.C. ELECTRONICS, Dept. E.E.
53, WOODLAND WAY, BURNTWOOD,
STAFFS WS7 8UP.

CREDIT CARD ORDERS: 0543 676477 (24 hours).

MAIL ORDER ONLY.


Devices not licenceable or BT approved.



The UK Distributor for Standard Toroidal Transformers

* 106 types available from stock

* Sizes from 15VA to 625VA

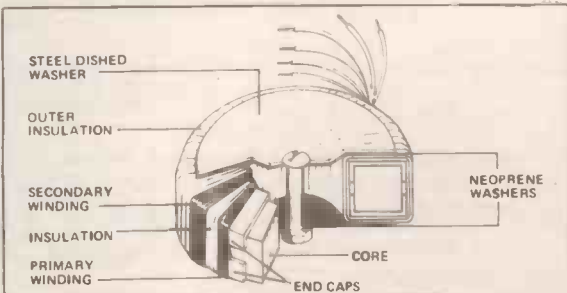

Write or phone for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254

Metal detector boards with Data has tuner, mode, discriminate, headphone jack, on/off volume & push button facilities.....£7.95 ea*

35mm Camera returns with auto flash, wind on etc.....£6 ea or 2 for £10

100k Lin. Joystick, mech.....£1*

Dictaphone cassette, mech/record erase playback heads, 6V solenoid, motor, hall effect switch.....£2.00 ea*

T.V./Printer stands.....£3.95 ea

Bicc-Verro Easiwire construction kit.....£4.95 ea*

Dot matrix LCD 10x2 lines.....£3.75 ea*

40 characters x 1 line dot matrix LCD with data.....£15.00*

2 digit 16 segment VF display with data.....£2.95 ea*

4 digit intelligent dot matrix display.....£6.00*

17 segment V.F. display with driver board and data.....£2.99 ea*

8 digit liquid crystal display.....£1.75 ea*

4 digit LCD with 7211 driver chip.....£3.50 ea*

Digital clock display.....£2.50*

11 key membrane keypad.....£1.50 ea*

Keyboard 392mm x 180mm/100 keys on board + LCD + 74HC05/80C49 easily removable.....£4.95

19" 3U sub rack enclosures.....£8.95

12V stepper motor, 48 steps per rev, 7.3° step angle.....£3.95 ea*

Stepper motor board with 2 slotted opto + 2 mercury tilt switches.....£3.95 ea*

1000 mixed 1/2 watt 1% resistors.....£4.95 ea

250 electrolytic axial + radial caps.....£4.95 ea

200 off mixed polyester caps.....£7.95*

100 Mixed trimmer caps popular values.....£4.95*

100 off Phono plugs (red/black/grey).....£3.50*

50 Mixed terminal blocks.....£2.95

25 off asst. buzzers & sounders.....£4.95*

Cable box UHF modulator/video preamp/transformer/R's + C's/leads.....£6.95

1000 off mixed Multilayer Ceramic Caps.....£7.95

Solar cell modules 0.45V 700mA.....£2.95 ea*

B.B.C. Micro to disc drive lead.....£1.50*

Car Burglar alarm vibration auto entry/exit delay.....£5.95 ea*

Single zone alarm panel auto entry/exit delay housed in domestic light socket.....£9.95 ea*

P.C. P.S.U. 50 watt 115-230V input + 5V 4A + 12V 2.5A output with built in fan, IEC inlet + on off.....£9.95 ea

STC P.S.U. 240V input 5V 6A output (converts to 12V 3A details available).....£5.95 ea

240V input 5V 10A output (converts to 12V 5A no details).....£5.95 ea

6000z line output transformers.....£1.25 ea

240V in 0-12V 0.75A out transformer.....£1.75*

240V in 0-28V 62VA out transformer.....£2.75

Transformer + PCB gives 2x7.5V 32VA with skt for 5 or 12V regulator, will power floppy drive.....£3.75 ea

Ultrasonic transducers (transmit + receive).....£1.50 pair

3 to 16V Piezoelectric sounders.....50p

9V DC electromechanical sounder.....50p

24V DC electromechanical sounder.....50p

2A 250V keyswitch 3 position key removable in two positions.....£1.50*

DIL switches PCB MT 3/4/6 way.....35p

5V SPCO SIL reed relay.....40p

5V 2PCO DIL miniature relay.....60p

12V 2PCO or 4PCO continental relay.....60p

12V 10A PCB MT (to make contact) relay.....95p*

3 to 12V electro magnetic acoustic transducer with data.....75p*

2.4576/8.8329/21.10 MHz crystals.....50p ea*

Bridges 25A 200V.....£1.00

2A 100V.....50p

3lb Mixed components pack.....£4.95

25 off mixed relays.....£5.95*

40 off mixed toggle switches.....£9.95*

50 off mixed switches, toggle, rocker, slide, micro.....£9.95

Miniature axial chokes 0.1, 0.18, 0.12, 0.33, 0.39, 0.15, 1, 3.3UH.....10p ea, 100 for £7.50*

250 off 16/22/24/40 way IC Skts.....£4.95*

Crystal Oscillators 10/24/48 MHz.....£1 ea*

Spider Plug Leads.....75p ea*

QUANTITY DISCOUNTS AVAILABLE PLEASE RING

We also buy all forms of electronic components, p.s.u.'s, disk drives etc. Lists to below address.

ALL PRICES INCLUDE V.A.T. PLEASE ADD £2.00 p&p EXCEPT ITEMS MARKED * WHICH ARE 50P. SAE FOR BULK BUYING LIST PAYMENT WITH ORDER TO:

**Dept EE, COMPELEC,
14 Constable Road
St. Ives, Huntingdon,
Cambs PE17 6EQ
Tel/Fax: 0480 300819**

ADVERTISERS INDEX

A.C. ELECTRONICS.....	679	JPG ELECTRONICS.....	677
AUTONA.....	614	MAGENTA ELECTRONICS.....	617
N. R. BARDWELL.....	678	MAILTECH.....	642
R. BARTLETT.....	665	MAPLIN ELECTRONICS Cover (iv)	679
BK ELECTRONICS.....	Cover (iii)	MARAPET.....	679
BLB ELECTRONICS.....	677	MAURITRON.....	678
BRIAN J. REED.....	679	M&B ELECT. SUPPLIES.....	615
BULL ELECTRICAL.....	Cover (ii)	MODERN ELECTRONICS MANUAL.....	654/655
CAMBRIDGE COMP. SCIENCE.....	665	NATIONAL COLLEGE OF TECH.....	665
CIRKIT DISTRIBUTION.....	665	NUMBER ONE SYSTEMS.....	610
COMPELEC.....	680	OMNI ELECTRONICS.....	652
CRICKLEWOOD ELECTRONICS.....	677	PICO TECHNOLOGY.....	614
CR SUPPLY COMPANY.....	614	RACKZ PRODUCTS.....	679
DELICIA ELECTRONICS.....	625	RADIO & TV COMPONENTS.....	661
DISPLAY ELECTRONICS.....	653	SERVICE TRADING CO.....	652
ESR ELECTRONIC COMP.....	618	SHERWOOD ELECTRONICS.....	680
GREENWELD ELECTRONICS.....	613	SMART HOUSE SYSTEMS.....	614
HART ELECTRONIC KITS.....	616	STEWART OF READING.....	614
HESING TECHNOLOGY.....	677	SUMA DESIGNS.....	612
ICS.....	679	TECHNICAL INFO. SERVICES.....	679
JAYTEE ELECTRONIC SERVICES.....	677 & 679	TSIEN.....	633
		TYPESETTING BUREAU.....	680

SHERWOOD ELECTRONICS

9 Lower Birchwood, Somercotes, Derbyshire DE55 4NG

*** SPECIAL OFFER ***

Choose any 2 packs FREE with every 10 £1 packs purchased.

SP1 15 x 5mm Red Leds	SP37 20 x 100uf/35V radial caps.
SP2 15 x 5mm Green Leds	SP38 25 x 47uf/25V radial caps.
SP3 12 x 5mm Yellow Leds	SP42 200 x Mixed 0.25W C.Film resistors
SP6 15 x 3mm Red Leds	SP44 12 x 5mm Leds-4 ea. Red, Grn., Yel.
SP7 12 x 3mm Green Leds	SP47 5 x Min.push button switches
SP8 10 x 3mm Yellow Leds	SP102 20 x 8 pin DIL sockets
SP10 100 x 1N4148 diodes	SP103 15 x 14 pin DIL sockets
SP11 30 x 1N4001 diodes	SP104 15 x 16 pin DIL sockets
SP12 30 x 1N4002 diodes	SP105 6 x 74LS00
SP18 20 x BC182 transistors	SP109 15 x BC557 transistors
SP20 20 x BC184 transistors	SP112 6 x Cmos 4093
SP23 20 x BC549 transistors	SP119 6 x Cmos 4072
SP25 5 x 555 timers	SP121 8 x Rect. Red Leds 5 x 2mm
SP26 5 x 741 Op-amps	SP122 8 x Rect. Green Leds 5 x 2mm
SP28 6 x Cmos 4011	SP123 5 x Rect. Yellow Leds 5 x 2mm
SP36 25 x 10uf/25V radial caps.	SP125 10 x 1000uf/16V radial caps

RESISTOR PACKS - 0.25W C.Film		
RP3 5 each value - total 365	£2.30	
RP7 10 each value - total 730	£3.95	
RP10 1000 popular values	£5.35	

Catalogue - price £1
Contains £2 vouchers redeemable
against orders

Cheques or P.O. to **NO VAT** Please add £1 P&P to all orders
SHERWOOD ELECTRONICS

Typefit

THE TYPESETTING BUREAU LTD

PC page make-up software and typesetter output bureau

*"For serious document production it
knocks other DTP software into
the proverbial cocked hat."*

Those are the words of Jim Tyler, an independent journalist after reviewing Typefit for "Micro Computer Mart". His letter to us went on to say:

"I spent two years editing a magazine, I have been involved in running a DTP bureau and I currently make my living writing classic car restoration manuals for a division of Reed Business International. I would choose Typefit for any of these roles."

No we did not pay him anything - he did not even get a free copy of our software (Typefit only costs £225 + VAT anyway). And just for the sceptics he is not a personal friend, relative or shareholder in the company.

His sentiments are backed up by our customers, some of which have changed from other well-known DTP packages costing much more - they tell us Typefit is more

versatile and provides them with use of a better range of quality typefaces (230 different fonts).

With Typefit you do your own Typesetting, proof and correct your work, we provide the expensive phototypesetter and fonts to give you top quality 2000 dot per inch bromide output.

Before investing in any other DTP package and especially before spending a small fortune on a specialist typesetting computer or other equipment, please investigate Typefit.

Please send me more information on Typefit

Name.....

Address.....

.....

..... Post Code.....

Tel:.....EE

BUYER'S GUIDE TO ELECTRONIC COMPONENTS 1993

Maplin



BS 5750
Part 2 1987

Level B:
Quality Assurance
RS12750



Order your copy of the New MAPLIN Catalogue on sale NOW!
Pick up a copy from any branch of WHSMITH or from our chain of shops for just £2.95 or
post this coupon now to receive your copy for just £3.45 inc. p&p. If you live outside the
U.K. send £5.50 or 14 IRC's for Airmail in Europe/ surface mail outside Europe,
or £10.65 or 27 IRC's for Airmail outside Europe.
I enclose £3.45/£5.50/£10.65 (delete as applicable).

Name.....
Address.....
Post Code.....
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England,
SS6 8LR.
EE93

**Over 700 product packed pages with
hundreds of brand new products.
On sale now, only £2.95**

Available from all branches of WHSMITH and
Maplin shops nationwide. Hundreds of new
products at super low prices!

MARCO TRADING

INCORPORATING
EAST CORNWALL COMPONENTS

AUTUMN 1992

SUPPLEMENT

**FANTASTIC
OFFER
TWO-WAY TRANSCEIVER**
(Order Code B123)

ONLY £17.50

(Catalogue Price £27.50)
WHEN YOU SPEND OVER £30



**FULL DETAILS
SEE PAGE
27**

Access



**PHONE
YOUR
ORDER
IN TODAY**

VISA

Access



**PHONE
YOUR
ORDER
IN TODAY**

VISA

**Telephone:
0939 232763**

**Fax:
0939 233800**

POST & PACKING NOW £3.00!!

Yes, it's gone up but so has the quality of service. Using another carrier – delivery is guaranteed within 3 days of leaving our premises. We think it's well worth the little extra. If you want the next day delivery simply add £9.00 P&P to your order.

MARCO TRADING The Maltings, High Street, Wem, Shrewsbury SY4 5EN. Tel 0939 232763

CAR AMPLIFIERS



ORDER CODE: CAR/CPA100

2 x 60W CLASS A AMPLIFIER B005LA (CPA 100)

Class A stereo in-car amplifier capable of delivering 2 x 60W stereo or 120W mono in bridge mode. Inputs are low level phono, with left and right level controls. Full thermal and overload protection.

Output power 2 x 60W stereo 0.1%THD
 120W mono 0.1%THD
 Signal to noise ratio >80dB
 Frequency response 20-20000Hz
 Input sensitivity 100mV-3V adjustable
 Input impedance Low level input 20kΩ
 Output impedance 4Ω
 Power 14.4Vdc 15A
 Dims 240 x 120 x 50mm


£41-50

2x 200W CLASS A AMPLIFIER B005M CPA200

High power class A amplifier capable of delivering 2x 200W stereo or 400W mono in bridge mode. Inputs are direct from the speaker outputs of the car radio/cassette or low level phono inputs, with left and right level controls. Full thermal and overload protection.

Output power 2x 200W stereo 0.08%THD
 400W mono 0.2% THD
 Signal to noise ratio >90dB
 Frequency response 10-50000Hz
 Input sensitivity 100mV-3V adjustable
 Input impedance High level input 100Ω
 Low level input 20kΩ
 Output impedance 4Ω
 Damping factor >180 into 4Ω
 Power 14.4Vdc 43A nom
 Dims 240 x 180 x 50mm

£109-50

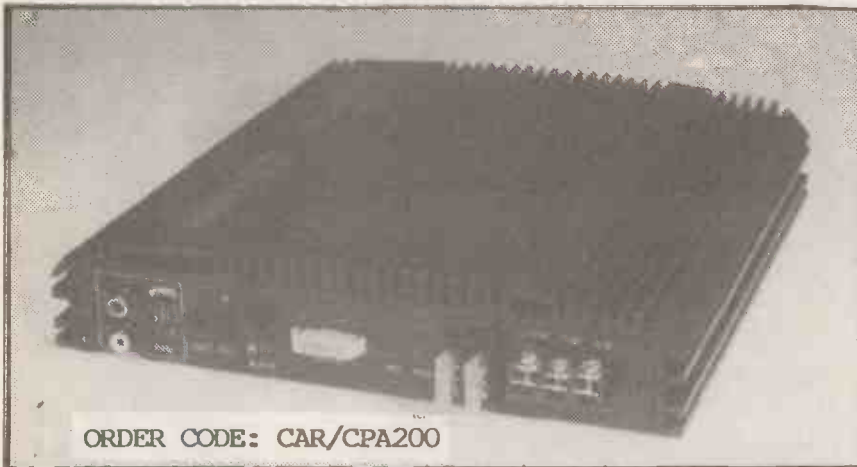


ORDER CODE: CAR/CPA200

4 x 120W CLASS A AMPLIFIER B005N (CPA504)

High power 4-channel class A amplifier, capable of delivering 4 x 120W or 2 x 240W in bridge mode. Inputs are direct from the speaker outputs of the car radio cassette, or low level phono inputs with left and right level controls. Full thermal overload protection.

Output power 4 x 120W or 2 x 240W (bridged)
 Signal to noise ratio >90dB
 Frequency response 10-50000Hz
 Input sensitivity 100mV-3V adjustable
 Input impedance High level input 100Ω
 Low level input 20kΩ
 Power 14.4Vdc 60A
 Dims 400 x 240 x 50mm

£120-75

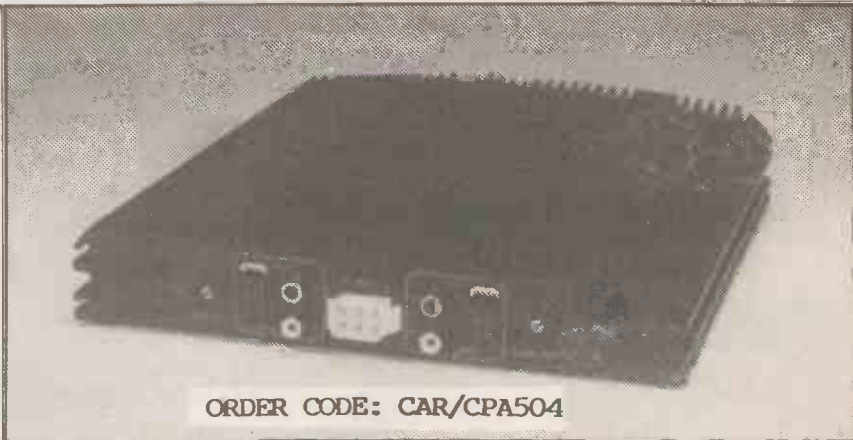

ORDER CODE: CAR/CPA504

ATTENTION RETAILERS.....
WHOLESALE/QTY PRICES ARE
AVAILABLE ON THESE AMPS.

EQUALIZER/BOOSTER


Slimline 7-band equalizer/booster with 60W total output power into 4 speakers. Built-in 3.5mm stereo headphone socket. Twin 5 LED power level indicators. Front/rear fader control. Mounting hardware included.

Output power 30W per channel
 Frequency response 20 - 20000Hz
 Input impedance 23Ω
 Control frequencies 60, 150, 400, 1k, 2.4k, 6kHz, 15kHz
 Control range 12dB boost or cut
 Output impedance 4 - 8Ω
 Power 12 - 14Vdc negative earth
 Dims 149 x 133 x 28mm



£24-99

G211

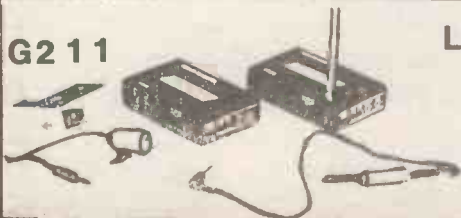

LIST PRICE: £49-50
SALE PRICE

£39-50

WIRELESS MICROPHONE

A 3-channel 2-part wireless microphone system designed for use with video cameras. The tie-clip mic has a remote belt clip transmitter with on/off switch. The receiver has a hot shoe for mounting on the video camera. The system allows greater mobility with a microphone than can be achieved with the camcorder mic.

12V CAR/CARAVAN ACCESSORIES



Hand held, HALOGEN spotlight with a **55watt** bulb, producing more than 250,000 candle power, directed by a concave, electro-plated reflector. Supplied complete with hanging loop and 3.6 Metres of coiled lead with a cigar plug fitted. These lights are a **must** for cars, vans, caravans, boats etc. The beam on these lights is **VERY** impressive.

POWER.....12VDC 55Watts
DIMS.....125 X 125 X 140mm Approx.

	1+	4+	10+	100+
PRICE:	£5-75	£5-50	£5-00	£4-25

ORDER CODE: OPTO/QHS

CAR POWER LEAD

Very handy lead, fused 3A cigar plug connected to a moulded 2.1mm DC power plug. Lead length approx. 2 Metres.

Colour: Black


	1+	10+
ORDER CODE: CAR/P.LEAD	£1-50	£1-25



CAR EXTENSION CONNECTOR

Every car, van, caravan & motorhome should have one of these! It is a cigarette lighter socket connected to a pair of colour coded crocodile clips. This clever lead is **INVALUABLE!!**

	1+	4+
ORDER CODE: CAR/JL	£2-99	£2-50

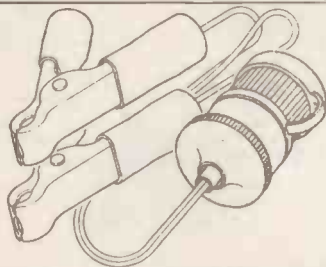

PLUG-IN FLASHING LED

A flashing LED built into a car cigar plug to act as a visual warning/deterrent that alarm may be fitted. Simply plug the device into your cigar socket. Won't flatten your car battery and it may stop your vehicle being stolen! All for £1-95!!

ORDER CODE: CAR/B200Z PRICE: £1-95



CAR LITTER BAG (LEATHERETTE)

Not quite in our normal sphere of business but we were so impressed with this product. Simply attach the bag behind the headrest. If you have children you **MUST** buy at least one of these!!

ORDER CODE: CAR/LIT £5-99ea 2 for £10



TRAVEL KETTLE - 12VDC

Supplied complete with mounting stand,

Plugs directly into a car cigar lighter socket for power. A 'power-on' light is on the kettle base. Ideal for cars, caravans, motorhomes, camping etc etc.

Power.....12Vdc 9A Capacity.....0.5pints
Dimensions: 143 X 125 X 112mm (approx)


END OF SEASON SALE PRICE: £11-50 2 for £10



CONNECTORS

1/2" JACK PLUGS AND SOCKETS - MONO AND STEREO


	1+	10+	
C001	1/2" Mono Plug Unscreened.....	26p	22p
C002	1/2" Mono Plug Screened.....	58p	52p
C003	1/2" Stereo Plug Unscreened...	36p	32p
C004	1/2" Stereo Plug Screened.....	88p	82p
C005	1/2" Mono Chassis Socket 2 Tag	30p	26p
C006	1/2" Mono Chassis Socket 4 Tag	38p	34p
C007	1/2" Stereo Chassis Skt. 6 Tag	40p	35p
C008	1/2" Mono Line SKT. Unscreened	33p	29p
C009	1/2" Mono Plug Right Angle Unscreened.....	40p	36p
C010	1/2" Mono Plug Right Angle Screened.....	46p	42p
C011	1/2" Mono Unswitched Open Chassis socket.....	44p	38p
C012	1/2" Mono Switched Open Chassis socket.....	52p	48p

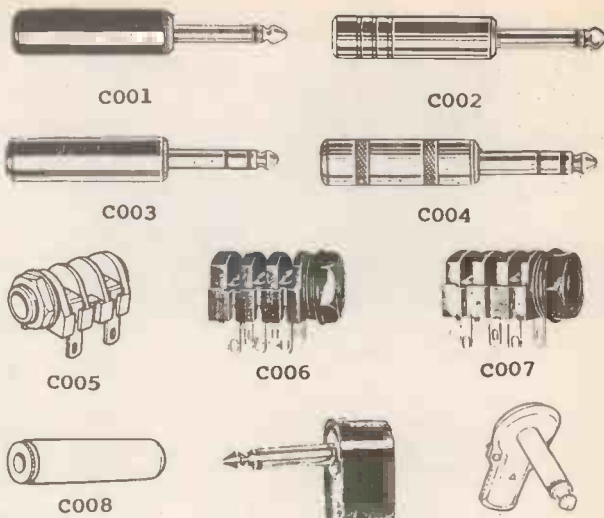

1/2" JACK PLUGS MONO AND STEREO - PROFESSIONAL


A range of top quality mono & stereo professional plugs and sockets. All metal, fully screened bodies with coiled spring flex outlet. Top part of cover is sleeved in coloured plastic for easy identification. Covers are knurled for firm grip.

	1+	10+	
C012A	..MONO PLUG BLACK	85p	75p
C012B	..MONO PLUG RED	85p	75p
C012C	..MONO PLUG ORANGE	85p	75p
C012D	..MONO PLUG YELLOW	85p	75p
C012E	..MONO PLUG BLUE	85p	75p
C012F	..MONO PLUG GREY	85p	75p
C012G	..MONO LINE SOCKET RED	105p	95p
C012H	..MONO LINE SOCKET BLACK	105p	95p
C012J	..MONO LINE SOCKET BLUE	105p	95p
C012K	..MONO LINE SOCKET YELLOW	105p	95p
C012L	..STEREO PLUG BLACK	110p	99p
C012M	..STEREO PLUG RED	110p	99p
C012N	..STEREO	110p	99p

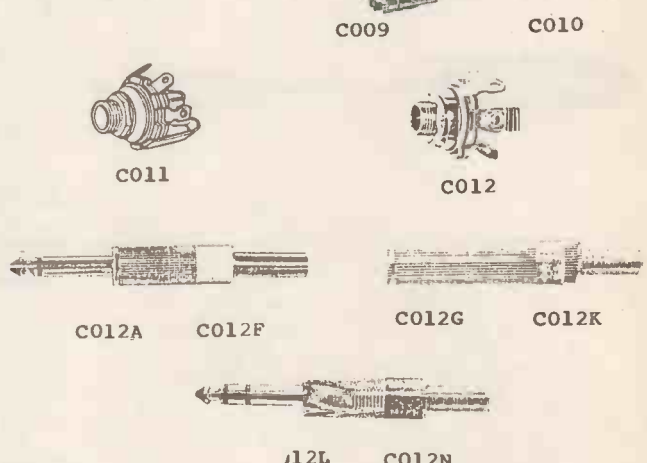


2.5mm JACK PLUGS AND SOCKETS - MONO AND STEREO

	1+	10+	
C013	2.5mm Mono plug Unscreened..	16p	12p
C014	2.5mm Mono Plug Screened....	38p	34p
C015	2.5mm Stereo Plug Unscreened..	55p	50p
C016	2.5mm Mono Chassis Socket...	24p	21p
C017	2.5mm Mono Line Socket Unscreened.....	21p	18p

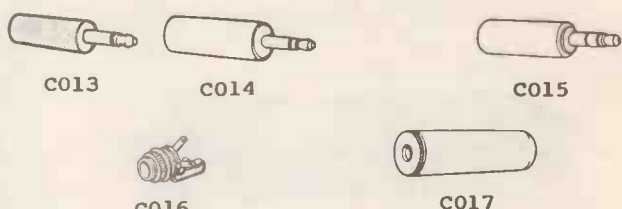

3.5mm JACK PLUGS AND SOCKETS - MONO AND STEREO

	1+	10+	
C018	3.5mm Mono plug Unscreened..	16p	13p
C019	3.5mm Mono Plug Screened....	35p	30p
C020	3.5mm Stereo Plug Unscreened	25p	20p
C021	3.5mm Stereo Unscreened Right Angle.....	28p	24p
C022	3.5mm Stereo Plug Screened..	58p	52p
C023	3.5mm Mono Chassis Socket...	24p	22p
C024	3.5mm Mono Line Socket Unscreened.....	24p	22p
C025	3.5mm Stereo Line socket Unscreened.....	25p	23p
C026	3.5mm Stereo PCB Socket Switched.....	22p	19p
C027	3.5mm skeletal chassis Stereo socket. Plastic unswitched..	42p	38p
C028	3.5mm skeletal chassis Stereo socket. Plastic switched....	49p	44p

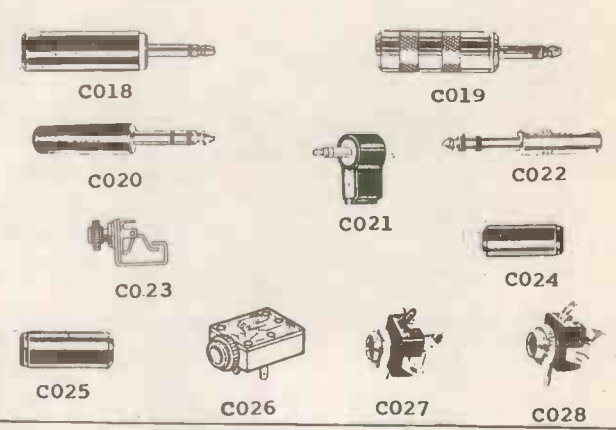

DIN PLUGS AND SOCKETS

PLUGS - All with grey plastic covers and cable grips. 7 & 8 pin are BLACK

CHASSIS SOCKETS - All metal except for 2 pin which is moulded plastic.

IN-LINE SOCKETS - All with GREY covers except for 7 & 8 pin which are BLACK

PLUGS	CODE	1+	10+	CHASSIS SOCKETS	CODE	1+	10+	LINE SOCKETS	CODE	1+	10+
2 pin	C100	14p	12p	2 pin	C102	12p	10p	2 pin	C103	14p	12p
3 pin	C104	20p	18p	3 pin	C105	29p	27p	3 pin	C106	30p	28p
4 pin	C107	26p	24p	4 pin	C108	30p	28p	4 pin	C109	30p	28p
5 pin	C110	180° 22p	20p	5 pin 180°	C111	32p	29p	5 pin 180°	C112	32p	29p
5 pin	C113	240° 26p	24p	5 pin 240°	C114	32p	29p	5 pin 240°	C115	32p	29p
5 pin	C116	360° 26p	24p	5 pin 360°	C117	30p	28p	5 pin 360°	C118	32p	29p
6 pin	C119	26p	24p	6 pin	C120	33p	30p	6 pin	C121	33p	30p
7 pin	C122	28p	26p	7 pin	C123	33p	30p	7 pin	C124	33p	30p
8 pin	C125	38p	35p	8 pin	C126	42p	39p	8 pin	C127	40p	36p



CONNECTORS

2mm CONNECTORS

C250	Plastic Plug	Red	14p	11p
C251	Plastic Plug	Black	14p	11p
C252	Plastic Plug	Green	14p	11p
C253	Plastic Plug	White	14p	11p
C254	Plastic Plug	Blue	14p	11p
C255	Plastic Plug	Yellow	14p	11p
C256	Socket	Red	16p	14p
C257	Socket	Black	16p	14p
C258	Socket	Green	16p	14p
C259	Socket	White	16p	14p
C260	Socket	Blue	16p	14p
C261	Socket	Yellow	16p	14p

2mm BINDING POST - 10A

High quality nickel brass terminal.
2mm socket in top of terminal.

C262	Binding post	2mm Red	45p	40p
C263	Binding post	2mm Black	45p	40p

PHONO PLUGS

Plastic covers, solder terminals.

C290	Red	15p	12p
C291	Black	15p	12p
C292	White	15p	12p
C293	Blue	15p	12p
C294	Yellow	15p	12p
C295	Green	15p	12p
C296	Grey	15p	12p

High quality, soft plastic covers, solder terminals, cable protector.

C296	Red	18p	15p
C297	Black	18p	15p
C298	Metal Phono plug (Screened)	28p	26p

High grade, metal phono plugs with coloured plastic ID band on cover with matching cable protector.

C299	Red	28p	25p
C300	Black	28p	25p
C301	Green	28p	25p
C302	Blue	28p	25p
C303	Yellow	28p	25p

PHONO SOCKETS

High grade, metal phono line socket with coloured ID band on cover with matching cable protector

C325	Red	28p	25p
C326	Black	28p	25p
C327	Green	28p	25p
C328	Blue	28p	25p
C329	Yellow	28p	25p

Plastic in-line, plastic with solder terminals.

C310	Red	14p	12p
C311	Black	14p	12p
C312	White	14p	12p
C313	Blue	14p	12p
C314	Yellow	14p	12p
C315	Green	14p	12p
C316	Grey	14p	12p

Single phono socket on paxolin. Dia 25mm.

C317	12p	10p
------	-----	-----

Single chrome chassis socket with colour coded insulator.

C318	Red	20p	18p
C319	Black	20p	18p
C320	White	20p	18p
C321	Blue	20p	18p
C322	Yellow	20p	18p
C323	Brown	20p	18p
C324	Green	20p	18p

CO-AXIAL SOCKET - PANEL MOUNTING

Push-in Needs 18 x 18mm mounting hole.

C356	22p	20p
------	-----	-----

CO-AX PLUG - Metal

C357	25p	22p
------	-----	-----

CO-AXIAL CHASSIS SOCKET.

C358	20p	18p
------	-----	-----

CO-AXIAL LINE SOCKET - Metal

C359	44p	40p
------	-----	-----

CO-AXIAL LINE CONNECTOR - Joins two coax plug

C360	20p	18p
------	-----	-----

4mm CONNECTORS

SOLDERLESS - Hard plastic, screw terminals

C270	4mm Plug	Red	15p	12p
C271	4mm Plug	Black	15p	12p

SOCKETS - Single nut fixing.

C272	Socket	Red	18p	16p
C273	Socket	Black	18p	16p
C274	Socket	Green	18p	16p
C275	Socket	Yellow	18p	16p
C276	Socket + Tag	Red	12p	10p
C277	Socket + Tag	Black	12p	10p

4mm BINDING POST - High quality

C280	4mm Binding post	Red	42p	38p
C281	4mm Binding post	Black	42p	38p
C282	4mm Binding post	Blue	42p	38p
C283	4mm Binding post	Green	42p	38p
C284	4mm Binding post	Yellow	42p	38p

PHONO PLUG - GOLD PLATED

Gold plated, knurled body, coiled spring cable outlet. Coloured ID marker bands on body.

C340	Red	85p	75p
C341	Black	85p	75p
C342	White	85p	75p

PHONO LINE SOCKET - GOLD PLATED

Gold plated line sockets with coloured ID bands on body. Knurled body coiled spring cable protector. Solder terminals. Matches above plugs.

C343	Red	90p	80p
C344	Black	90p	80p
C345	White	90p	80p

PHONO CHASSIS SOCKETS - GOLD PLATED

Gold plated, chassis sockets with coloured insulators. Single hole fixing.

C346	Red	60p	55p
C347	Black	60p	55p
C348	White	60p	55p



C350



C351



C352



C353



C354



C355

CAR AERIAL CONNECTORS

Skeleton Plug.

C350	24p	22p
------	-----	-----

Plastic Plug - Solderless, & screw on cap.

Colour: Black

C351	42p	38p
------	-----	-----

LINE SOCKET - Plastic body, solderless.

C352	48p	44p
------	-----	-----

CHASSIS SOCKET - Panel cut out 12.7mm

C353	33p	30p
------	-----	-----

CIGAR PLUG - Fused with 5A fuse. Solder term

C354	£1-15	£1-05
------	-------	-------

CIGAR PLUG - Non fused.

C355	25p	22p
------	-----	-----

CO-AXIAL PLUG - Turned Brass

Very high quality.

C361	55p	50p
------	-----	-----



C356



C357



C358



C359



C360



C361

COMPONENT KIT SALE

Resistor Kit - 0.25W (5 off)

A pack containing 305 resistors. Values as listed below. Each value individually packed and each bag marked with the values enclosed.

Contents: 5 off each value:

10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M.

Order Code: 1+ 5+
KIT/RES/25/5 ~~£3.75~~ ~~£3.25~~

SALE PRICE £2-99

Resistor Kit - 0.25W (10 off)

A pack containing 610 resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 10 off each value:

10R, 12R, 15R, 18R, 22R, 27R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M.

Order Code: 1+ 5+
KIT/RES/25/10 ~~£5.10~~ ~~£4.60~~

SALE PRICE £4-00

Resistor Kit - 0.25W POPULAR

A pack containing a total of 1,000 of 1,000 $\frac{1}{2}$ W 5% carbon film resistors ranging in value from 10R to 10M.

In this pack we have included larger quantities of the more popular values.

Each value individually packed.

Contents:

No.	VALUE	No.	VALUE	No.	VALUE
10 x	10R	10 x	82R	10 x	390R
10 x	12R	20 x	100R	30 x	470R
10 x	18R	10 x	120R	20 x	560R
10 x	22R	10 x	150R	20 x	680R
10 x	33R	10 x	180R	10 x	820R
20 x	47R	20 x	220R	40 x	1K
10 x	56R	20 x	270R	15 x	1K2
10 x	68R	20 x	330R	15 x	1K5
10 x	1K8	10 x	8K2	10 x	39K
25 x	2K2	30 x	10K	30 x	47K
20 x	2K7	15 x	12K	20 x	56K
20 x	3K3	15 x	15K	15 x	68K
15 x	3K9	15 x	18K	10 x	82K
25 x	3K7	20 x	22K	30 x	100K
20 x	5K6	15 x	27K	20 x	120K
15 x	6K8	20 x	33K	15 x	150K
15 x	180K	5 x	820K		
20 x	220K	20 x	1M		
15 x	270K	10 x	2M2		
15 x	330K	5 x	3M3		
10 x	390K	10 x	4M7		
20 x	470K	5 x	6M8		
10 x	560K	20 x	10M		
10 x	680K				

SALE PRICE
£5-50

Order Code: 1+ 5+
KIT/RES/25/POP ~~£6.99~~ ~~£5.99~~

Resistor Kit - 0.5 POPULAR

A pack containing a total of 1,000 $\frac{1}{2}$ W 5% carbon film resistors ranging in value from 2R2 to 10M.

In this pack we have included larger quantities of the more popular values. Each value individually packed.

Contents:

NO.	VALUE	NO.	VALUE	NO.	VALUE
5 x	2R2	10 x	12R	10 x	120R
5 x	2R7	10 x	18R	10 x	150R
5 x	3R3	10 x	22R	10 x	180R
5 x	3R9	10 x	33R	20 x	220R
10 x	4R7	20 x	47R	20 x	270R
5 x	5R6	10 x	56R	20 x	330R
5 x	6R8	10 x	68R	10 x	390R
5 x	8R2	10 x	82R	30 x	470R
10 x	10R	20 x	100R	20 x	560R
20 x	680R	10 x	3K9	20 x	22K
10 x	820R	25 x	4K7	10 x	27K
40 x	1K	20 x	5K6	20 x	33K
10 x	1K2	10 x	6K8	10 x	39K
10 x	1K5	10 x	8K2	30 x	47K
10 x	1K8	30 x	10K	20 x	56K
25 x	2K2	15 x	12K	10 x	68K
20 x	2K7	15 x	15K	10 x	82K
20 x	3K3	30 x	18K	30 x	100K
20 x	120K	10 x	680K		
10 x	150K	5 x	820K		
10 x	180K	20 x	1M		
20 x	220K	10 x	2M2		
15 x	270K	5 x	3M3		
15 x	330K	10 x	4M7		
10 x	390K	5 x	6M8		
20 x	470K	20 x	10M		
10 x	560K				

SALE PRICE
£9-00

Order Code: 1+ 5+
KIT/RES/5/POP ~~£10.75~~ ~~£9.75~~

Resistor Kit - 0.5W (5 off)

A pack containing 365 resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

2K2, 2R7, 3R9, 4R7, 5R6, 6R8, 8R2, 10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M, 1M2, 1M8, 2M2.

Order Code: 1+ 5+
KIT/RES/5/5 ~~£5.40~~ ~~£5.00~~ **£4-50**

Resistor Kit - 0.5W (10 Off)

A pack containing 730 Resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 10 off each value:

2R2, 2R7, 3R3, 3R9, 4R7, 5R6, 6R8, 8R2, 10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M, 1M2, 1M5, 1M8, 2M2.

Order Code: 1+ 5+
KIT/RES/5/10 ~~£8.75~~ ~~£7.75~~ **£7-00**

SALE PRICES ANY QUANTITY

COMPONENT KIT SALE

Resistor Kit - 1W (5 off)

A pack containing 365 1W resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 22K, 27K, 33K, 39K, 47K, 56K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M, 1M2, 1M5, 1M8, 2M2, 2M7, 3M3, 3M9, 4M7, 5M6, 6M8, 8M2, 10M.

Order Code: 1+ 5+
KIT/RES/1/5 ~~£15.25~~ ~~£14.00~~

SALE PRICE £13-00

Ceramic Kit - 50V - Over £9.70 worth at catalogue prices -

A pack containing 125 50V disc and plate ceramics - ranging in value from 1pF to 10nF (0.01mF).

Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

1.0pF, 1.8pF, 2.7pF, 3.3pF, 4.7pF, 5.6pF, 6.8pF, 8.2pF, 10pF, 12pF, 22pF, 27pF, 47pF, 68pF, 82pF, 100pF, 150pF, 180pF, 270pF, 470pF, 560pF, 1000pF, 2200pF, 4700pF, 10nF.

Order Code: 1+ 5+
KIT/CER/50V ~~£3.99~~ ~~£3.50~~ **£3-00**

Electrolytic Kit - Radial - Over £11.00 worth at catalogue prices -

A pack containing 100 miniature radial lead electrolytic capacitors. 12 different values. Each value individually packed.

Contents:

No.	VALUE	VOLTAGE	NO.	VALUE	VOLTAGE
10	1mF	63V	15	10mF	25V
10	2.2mF	63V	10	22mF	25V
10	4.7mF	63V	10	47mF	25V
15	100mF	16V	5	1000mF	16V
5	220mF	16V	2	1000mF	25V
5	470mF	16V	3	2200mF	16V

Order Code: 1+ 5+
KIT/ELECT/RAD £8.50 £7.50

SALE PRICE £7-00

Fuse Kit - 20mm Quick Blow

A pack containing 80 Quick-Blow 20mm Fuses.

Each value individually packed.

Contents:

No.	VALUE	NO.	VALUE	NO.	VALUE
5	x 100mA	10	x 500mA	10	x 3.15A
5	x 250mA	20	x 1A	5	x 5A
5	x 315mA	5	x 1.6A	5	x 6.3A
		10	x 2A		

Order Code: 1+ 5+ **£3-50**
KIT/FUSE/QB2 ~~£4.75~~ ~~£4.25~~

Fuse Kit - 20mm Anti-Surge

A pack containing 80 Anti-Surge 20mm Fuses.

Each value individually packed.

Contents:

No.	VALUE	NO.	VALUE	NO.	VALUE
5	x 100mA	10	x 500mA	10	x 3.15A
5	x 250mA	20	x 1A	5	x 5A
5	x 315mA	5	x 1.6A	5	x 6.3A
		10	x 2A		

Order Code: 1+ 5+
KIT/FUSE/AS2 ~~£8.50~~ ~~£7.50~~ **£7-00**

A pack containing a total of 120 miniature horizontal mounting pre-set potentiometers. A total of 13 different values. Each value individually packed.

Contents:

No.	VALUE	No.	VALUE	No.	VALUE
5	x 100R	5	x 2K2	10	x 47K
5	x 220R	15	x 2K7	20	x 100K
5	x 470R	20	x 10K	5	x 220K
15	x 1K	5	x 22K	5	x 470K
		5	x 1M		

Order Code: 1+ 5+
KIT/POT/HORIZ ~~£7.75~~ ~~£7.25~~ **£6-50**

A pack containing a total of 120 miniature vertical mounting pre-set potentiometers. A total of 13 different values. Each value individually packed.

Contents:

No.	VALUE	No.	VALUE	No.	VALUE
5	x 100R	5	x 2K2	10	x 47K
5	x 220R	15	x 4K7	20	x 100K
5	x 470R	20	x 10K	5	x 220K
15	x 1K	5	x 22K	5	x 470K
		5	x 1M		

Order Code: 1+ 5+
KIT/POT/VERT ~~£7.75~~ ~~£7.25~~ **£6-50**

Zener Diode Kit - 400 M/W

A pack containing 55 zener diodes. 400m/w. Ranging from 3V6 to 30V. Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

3V3, 4V7, 7V5, 8V2, 11V, 12V, 13V, 15V, 16V, 20V, 24V.

Order Code: 1+ 5+ **£3-00**
KIT/ZEN/400 ~~£3.99~~ ~~£3.50~~

Polyester Capacitor Kit

ITT PMT type 100V miniature or similar. Pack contains 110 capacitors. Each value individually packed and each bag marked with the value.


Contents: 10 off each value:

0.01uF, 0.015uF, 0.022uF, 0.033uF, 0.047uF, 0.068uF, 0.1uF, 0.15uF, 0.22uF, 0.33uF, 0.47uF.

Order Code: **£4-00**
KIT/POLY Price £ 5.00

SALE PRICES ANY QUANTITY

F.M. TRANSMITTER

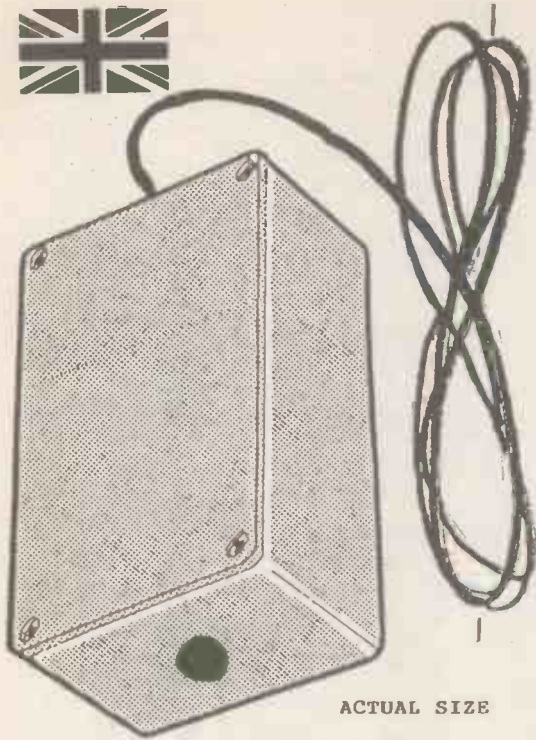

ACTUAL SIZE

Very high quality Mini-Bug, ideal for baby alarms etc etc!!

These units are well tried & tested and may be the best on the market.

Range will depend on terrain, siting of the mini-bug and also the quality of your receiver, but under normal conditions any FM radio will suffice. We have achieved over half a mile!

Simply remove box cover, insert AA battery and tune radio to mini-bug & away you go. Happy listening!! One AA battery lasted over 5 days in continuous with us!. Frequency is adjustable.

Frequency Range..... 85-110MHz
 Power..... AA 1.5V Battery
 Dimensions..... 72 X 46 X 22mm

	+	1+	10+
ORDER CODE: SEC/FMB1		£9-99	£7-50

ALSO AVAILABLE IN KIT FORM SEE OUR RANGE OF COMDEK KITS. UK DESIGNED & PACKED!!

C.C.T.V. EQUIPMENT

C.C.T.V. CAMERA (USED)




A steel cased, closed-circuit monochrome camera. Ideal for internal or external (using a weatherproof housing) security for domestic or commercial property surveillance. All camera's are supplied complete with 16mm lens. Wide angle lens (8mm) are available at extra cost. These units are secondhand & the style & design may differ to the illustration as stock changes. All camera's are thoroughly tested before despatch and should give very long trouble free service. Never mount the camera facing a window or bright light as this will burn the camera tube. Voltage generally 240Vac, if lower, we will supply a power supply.

ORDER CODE: SEC/CAM/USED

PRICE: **£120**

C.C.T.V. MONITOR (USED)

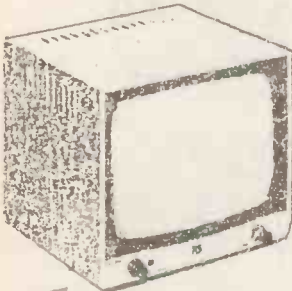


Steel cased, good quality black & white monitors. Depending on availability we can normally offer sizes from 9" up to 17". State your size preference & we will supply nearest size available. All monitors: 240Vac.

ORDER CODE: SEC/MON/USED

PRICE: **£70**

C.C.T.V. CAMERA BRACKET (NEW)

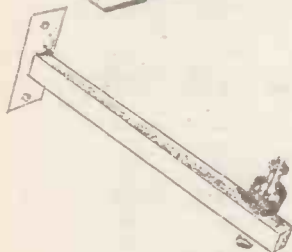

High quality, British made mounting bracket to suit not only our camera's above but any CCTV camera. White, plastic coated steel with standard 1"-20 mount. Locking swivel allows camera to be adjusted and fixed in almost any position.

ORDER CODE: SEC/CB

PRICE: **£7-75**

BUY THE COMPLETE PACKAGE ABOVE I.E.:


1 X Camera, 1 X Monitor, 1 X Bracket

£185

ORDER CODE: SEC/PACK

(EXTRA CARRIAGE ON THE PACKAGE IS £10-00)

OSCILLOSCOPE LEADS (MADE IN UK)

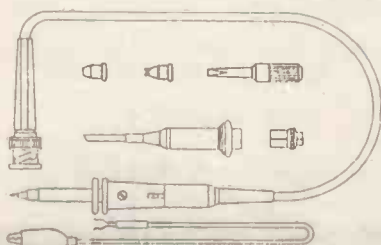

A set of very high quality 'scope' probes. Switched: X1 and X10
 Supplied in neat storage pack & full instructions. **MADE IN UK**

TEST/BS110

PRICE: **£15-50**

LOGIC 4

3 zones each with its own individual function, built in bell timer and keyswitch operation provide effective security with absolute ease of operation. Simple to install & full fitting instructions supplied. Available on its own or as complete Home Alarm Package, see below for special package price.

ORDER CODE - SEC/LGC4 £39-99

FEATURES

- * Keyswitch operated security control unit
- * Selectable part guard zone
- * Selectable PA and tamper loops.
- * Adjustable entry-exit timers.
- * Integral 20 minute bell timer & auto set
- * Latching strobe output.
- * Simple 4 terminal wiring to each zone



OPTIMA XM

Latest updated version of the leading UK selling 'Optima' panel. Rubber keypad, fully selectable 4 digit customer code allows the system to be switched on or off, with the option of omitting zones, quick setting at night and performing simple tests.


Very simple to install supplied complete with full fitting instructions etc. Ideal for either office or home. This panel is also available below as a complete Alarm Package saving even more money.

We have sold hundreds of this truly versatile alarm panel. Our number 1 seller

ORDER CODE: SEC/OPT/XM £49-00

FEATURES

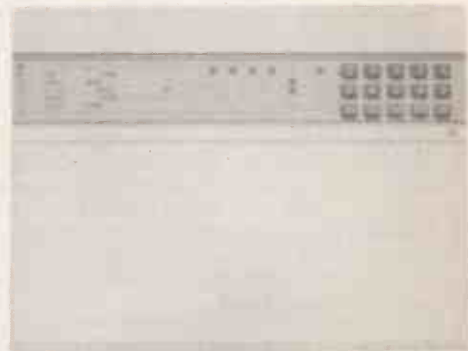- * Keypad operated
- * 4 zones & PA & tamper
- * Built in internal sounder
- * User may omit any zone.
- * Memory recall for last alarm
- * Programmable timers including bell cut off.
- * Quick set feature.
- * Intelligent auto reset and re-arm.




OPTIMA PLUS

As per the Optima XM but also has two communicator outputs thus enabling connection to a British Telecom telephone line. Further technical information is available.

ORDER CODE SEC/OPT/PLUS £75-00

PROTECT YOUR HOME NOW!

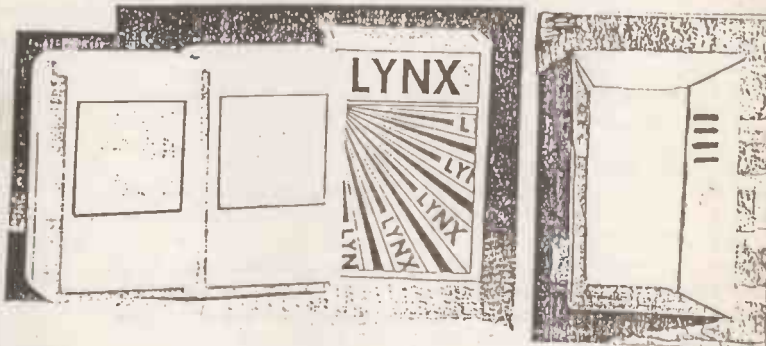

We have sold hundreds of these Home Alarm Packages. They represent truly excellent value for money. It is becoming, sadly, a necessity to protect your home and office with a security system and most important of all, one that can be relied upon!

OK, and now for the contents of your package:

- | | | |
|------------------------------|--------------------------|------------------------|
| * OPTIMA XM or LOGIC 4 Panel | * External Bell Box | * Siren for Bell Box |
| * 2 X Lynx Internal P.I.R.'s | * 2 X Sets Door Contacts | * 100mts Cable & Clips |

*****FULL FITTING INSTRUCTIONS*****

SEC/PACK/LOG £115-00

SEC/PACK/OPT £130-00

* Should you require extra P.I.R.'s for your installation they are available : ORDER CODE: SEC/LYNX PRICE: £29-00 each

ALL PRICES INCLUDE V.A.T.

ADD £3.00 P & P PER ORDER

BOOKS

50 SIMPLE LED CIRCUITS - BOOK 1 (R.N. Soar)
Contains 50 interesting, useful circuits & applications, covering many different areas of electronics using one of the most inexpensive & freely available components - The Light-Emitting Diode (L.E.D.) This book also includes circuits for the 707 common anode display.
This book is ideal for the beginner. (1977 64 pages)
ORDER CODE: BP42 PRICE: £1-95

50 SIMPLE LED CIRCUITS - BOOK 2 (R.N. Soar)
A further range of uses for the simple L.E.D. which complements those shown in Book BP42 (1981 64 pages)
ORDER CODE: BP87 PRICE: £1-95

MODEL RAILWAY PROJECTS (R.A. Penfold)
Provides a number of useful but fairly simple projects for the model railway enthusiast to build, based on inexpensive and easy to obtain components!
The projects covered include controllers, signal & sound effects units and to help construction, stripboard layouts are provided for each project! (1981 112 pages)
ORDER CODE: BP95 PRICE: £1-95

IC 555 PROJECTS (E.A. Parr)
Every so often a device appears that is so useful that one wonders how life went on before we had it! The 555 timer is such a device. Included in this book are basic & general circuits, motorcar & railway circuits, alarms & noise makers as well as a section on the 556, 558 & 559 timers. This really is a super book! (1982 176 pages)
ORDER CODE: BP44 PRICE: £2-95

POPULAR ELECTRONIC CIRCUITS - BOOK 1 (R.A. Penfold)
This book contains a wide range of circuits which are accompanied by a short text giving a brief introduction, circuit description & any special notes on construction & setting up that may be necessary. (1980 160 pages)
ORDER CODE: BP80 PRICE: £2-95

POPULAR ELECTRONIC CIRCUITS - BOOK 2 R.A. Penfold
Again, this book provides a wide range of designs for electronic enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed constructional information. However, where relevant, any special setting up procedures are described. (1982 160 pages)
ORDER CODE: BP98 PRICE: £2-95

ELECTRONIC PROJECTS FOR BEGINNERS (F.G. Rayer)
Contains a wide range of easily constructed projects (including some that require NO Soldering) for the newcomer to electronics.
Includes many actual component & wiring layouts to aid easy & successful construction. (1978 128 pages)
ORDER CODE: BP48 PRICE: £1-95

IC PROJECTS FOR BEGINNERS (F.G. Rayer)
Offers a range of simple projects based around a number of popular & inexpensive linear & digital I.C.'s. With most projects, complete layout and/or point to point wiring diagrams are included to help simplify construction. (1982 112 pages)
ORDER CODE: BP97 PRICE: £1-95

ELECTRONIC PROJECTS FOR CARS & BOATS R. Penfold
Describes fifteen fairly simple projects for use with car and/or boat. Each project has an explanation of how the circuit works as well as constructional details including a stripboard layout. (1981 96 pages)
ORDER CODE: BP94 PRICE: £1-95

POPULAR ELECTRONIC PROJECTS (R.A. Penfold)
Provides a collection of the most popular types of circuits & projects covering a wide range of interests, including Radio, Audio, Household & Test Equipment projects. (1978 144 pages)
ORDER CODE: BP49 PRICE: £2-50

POWER SUPPLY PROJECTS (R.A. Penfold)
Mains power supplies are an essential part of many electronic projects.
This book gives a number of power supply designs, including simple unregulated types, fixed-voltage regulated types, and variable-voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop!. The designs provided are all low-voltage types for semiconductor circuits.
This book should help the reader design their own power supplies.
Included in the last chapter are a number of other types of power supplies including: a cassette power supply, ni-cad battery charger, voltage step up circuit and a simple inverter.
A super book! (1980 96 pages)
ORDER CODE: BP76 PRICE: £2-50

HOW TO USE OP-AMPS (E.A. Parr)
This book has been written as a designers guide covering many operational amplifiers, serving both as a source of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible and it is hoped, easily understandable by most readers, be they engineers or hobbyists! (1982 160 pages)
ORDER CODE: BP88 PRICE: £2-95

HOW TO DESIGN & MAKE YOUR OWN PCB'S R. PENFOLD
Chapter 1: deals with simple methods of copying printed circuit board designs from magazines & books and covers all aspects of simple PCB construction as comprehensively as possible.
Chapter 2: covers photographic methods of producing PCB's.
Chapter 3: deals with most aspects of designing your own PCB layouts. (1980 80 pages)
ORDER CODE: BP121 PRICE: £2-50

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING
R.A. Penfold
We have all built circuits from magazines & books only to find that they did not work correctly, or at all when first switched on! The aim of this book is to help the reader overcome just these problems by indicating how & where to start looking for many of the common faults that can occur during building projects.
Chapter 1: deals with mechanical faults i.e. tracing dry joints, short circuits, broken pcb tracks, etc. The construction and use of a tristate continuity tester, to help in the above, is also covered.
Chapter 2: deals with linear analogue circuits & also covers the use & construction of a signal injector/tracer which can be used to locate & isolate the faulty areas in a project.
Chapter 3: considers ways of testing the more common components such as resistors, capacitors, op-amps, diodes, transistors, SCR's, unijunctions etc. with the aid of only a limited amount of equipment.
Chapter 4: deals with both TTL & CMOS logic circuits & includes the use & construction of a pulse generator to help fault finding. (1982 96 pages)
ORDER CODE: BP110 PRICE: £2-50

GETTING THE MOST FROM YOUR MULTIMETER
R.A. Penfold
It is quite amazing just what you can check & test with a simple multimeter if you know what you are doing! This book tells the full story with Chapter 1 covering the basics and relative merits of analogue & digital instruments. Chapter 2 discussing component checking & Chapter 3 dealing with circuit testing.
A super book & a must for the beginner! (1988 £2-95)
ORDER CODE: BP239 PRICE: £2-95

MODERN OPTO DEVICE PROJECTS R.A. Penfold
Provides a number of circuits including designs for; simple fibre optic audio link, equivalent circuit for RS232C type data transmission & reception; light pen for BBC, Atari, Commodore & Amstrad computers; presence detector, broken beam detector, infra red reflected light sensor; LED stroboscope etc. PCB layouts are included for more critical layouts. (1987 96 pages)
ORDER CODE: BP194 **PRICE: £2-95**

ELECTRONIC SECURITY DEVICES R.A. Penfold
This book, besides including both simple & more sophisticated burglar alarm circuits using light, infra-red & ultrasonics, also includes many other types of circuit as well, such as gas & smoke detectors, flood alarms, doorphone & baby alarms. (1979 112 pages)
ORDER CODE: BP56 **PRICE: £2-50**

MORE ADVANCED ELECTRONIC SECURITY PROJECTS R.A. Penfold
Contains a number of more up to date & sophisticated projects, complete with PCB or stripboard layout, than our original book BP56.
Covers; Opto alarms incl. pyro-sensor, infra-red & fibre optic loop types. A computer based system showing how a home micro fitted with a user port can form the basis of a most sophisticated alarm & monitoring system. Also included are various alarms using; mercury tilt switches, magnetic switches, doppler shift & capacity effect on an RF oscillator etc. (1988 112 pages)
ORDER CODE: BP190 **PRICE: £2-95**

ELECTRONIC HOBBYISTS HANDBOOK R.A. Penfold
The Author has used his vast knowledge of hobby electronics to provide a useful collection of data for the amateur electronics enthusiast, in a single source where it can be quickly & easily located. It includes a great deal of data on likely topics of interest, such as colour codes, IC pinouts, transistor leadout diagrams and data, basic building blocks etc. Some knowledge of electronics may be needed to make use of some of the information, but in most cases appropriate background info. is given. (1987 96 pages)
ORDER CODE: BP233 **PRICE: £4-95**

SIMPLE SHORTWAVE RECEIVER CONSTRUCTION R.A. Penfold
Contains practical designs for building a number of simple Short Wave receivers including full coil winding details! (1990 96 pages)
ORDER CODE: BP275 **PRICE: £3-95**

ADVANCED SHORTWAVE RECEIVER CONSTRUCTION R.A. Penfold
Gives the reader full constructional details, including coil windings of a number of advanced design receivers which should have levels of performance at least equal to that of commercially built sets of similar complexity, you CAN do it! (1990 96 pages)
ORDER CODE: BP276 **PRICE: £3-95**

EXPERIMENTAL ANTENNA TOPICS H.C. Wright
Contains 28 fascinating sections & includes many unusual practical designs which utilise such things as cardboard, cooking foil, plastic bottles, cat food tins etc. (1990 96 pages)
ORDER CODE: BP278 **PRICE: £3-50**

25 SIMPLE TROPICAL & MW BAND AERIALS E.M. Noll
Shows you how to build 25 simple & inexpensive aerials for operation on the medium wave band and on 60, 75, 90 & 120 metre tropical bands. Designs for the 49 metre band are included as well. (1984 64 pages)
ORDER CODE: BP145 **PRICE: £1-75**

25 SIMPLE INDOOR & WINDOW AERIALS E.M. Noll
Written for those of us with limited space in flats or no gardens etc. The 25 aerials in this book have been designed to give surprisingly good results from their limited dimensions. (1984 64 pages)
ORDER CODE: BP136 **PRICE: £1-75**

AN INTRODUCTION TO ANTENNA THEORY H.C. Wright
Deals with basic concepts relevant to receiving & transmitting antennas in a manner which emphasises the mechanism involved with strong diagrammatic support minimises the mathematics used. (1987 96 pages)
ORDER CODE: BP198 **PRICE: £2-95**

AN INTRODUCTION TO AMATEUR RADIO I.D. Poole
Gets you started with the fascinating hobby that enthralled so many the world over.
This book gives the newcomer a comprehensive & easy to understand guide through the subject so that the reader can gain the most from the hobby. It will always be an essential reference book to be used time & time again. Topics include, Operating procedures, jargon & setting up a station, Technical Topics covered include: propagation, transmitters & aerials etc. (1989 160pgs)
ORDER CODE: BP257 **PRICE: £3-50**

AN INTRODUCTION TO VHF/UHF FOR RADIO AMATEURS I.D. Poole
This book covers the essential required to gain the most from using the VHF & UHF bands. Topics covered include: propagation, descriptions of the bands & channels, aerials, receivers, transmitters & a special chapter on scanners. In addition to this repeater & mobile operation together with DXing are included. Also a Packet Radio section. (1990 112 pages)
ORDER CODE: BP281 **PRICE: £3-50**

PUBLIC ADDRESS LOUDSPEAKER SYSTEMS V. Capel
Covers the moving coil loudspeakers, baffles, the basic requirements of a P.A. system, sound patterns, line source, horn loudspeakers, LISCA, low-impedance matching, 100Volt line systems, transmission lines & induction loops etc. (1990 128 pages)
ORDER CODE: BP292 **PRICE: £3-95**

MIDI PROJECTS R.A. Penfold
Provides practical details of how to interface many popular home computers with MIDI systems. Also covers interfacing MIDI equipment to analogue & percussion synthesisers. (1986 112 pages)
ORDER CODE: BP182 **PRICE: £2-95**

AUDIO AMPLIFIER FAULT-FINDING CHART C.E. Miller
This chart will help trace most common faults that might occur in audio amplifiers. Across the top of the chart are two 'starting' rectangles, viz Low/Distorted Sound Reproduction and No Sound Reproduction & after selecting the most appropriate you simply follow the arrows carrying out the suggested checks until the fault is located & rectified. (1987 Chart)
ORDER CODE: BP120 **PRICE: £0-95**

RADIO AND ELECTRONIC COLOUR CODES & DATA CHART B.B. Babani
Covers many colour codes in use throughout the world for mosr radio & electronic components. Includes resistors, capacitors, transformers, field coils, fuses, battery leads, speakers etc. (1971 Chart)
ORDER CODE: BP7 **PRICE: £0-95**

RESISTOR SELECTION HANDBOOK B.B. Babani
Shows how to combine two preferred values of resistors to obtain virtually any required value of resistance. Also includes information on fixed resistors, standard ranges, colour codes & markings, power ratings etc. (1976 48 pages)
ORDER CODE: BP28 **PRICE: £0-60**

HOW TO IDENTIFY UNMARKED IC's K.H. Re CORR
Shows how with the help of a test-meter you can identify an IC by its particular 'signature' when comparing the information recorded with the manufacturers specification. An IC signature is a specially plotted chart produced by measuring the resistances between all terminal pairs of an IC. Originally published in a leading US magazine. (1982 Chart)
ORDER CODE: BP101 **PRICE: £0-95**

FANE LOUDSPEAKER ENCLOSURE DESIGN & CONSTRUCTION BOOK

Published by one of the UK's leading loudspeaker manufacturers, this book contains a very large selection of cabinet designs & enclosures for the loudspeakers generally available today, including most of the ones in our catalogue! Guidelines are given for construction, pointing out the care needed to be given in selecting materials, sealing, making joints, mounting the driver units and wadding the cabinet. Twenty three designs are detailed ranging from Small Bass reflex cabinets using 12" diameter Full Range Drivers through folded horns, to Massive Multi-way High Power systems.

FULLY ILLUSTRATED

ORDER CODE: BOOK/FANE PRICE: £3-50

HOW TO EXPAND, MODERNISE AND REPAIR PC'S AND COMPATIBLES

R.A. Penfold

All the practical information that you are likely to need to upgrade your PC and compatible. Also contains useful information to help you with your repairs. (1990 176pgs)

ORDER CODE: BP271 PRICE: £4-95

PROGRAMMING IN QUICKBASIC

N. Kantaris

QuickBASIC is one of the most popular structured dialects of BASIC running on the IBM and compatible computers. QuickBASIC statements are introduced and explained with the help of simple programs. This enables the user to build up a considerable library of their own programs & procedures which become building blocks of advanced programming techniques. (1990 160 pages)

ORDER CODE: BP284 PRICE: £4-95

A CONCISE INTRODUCTION TO VENTURA

J.W. Penfold

This book gets the Desktop Publisher stated with this incredible Desktop Publishing Package. (1990 80 pages)

ORDER CODE: BP291 PRICE: £3-95

A CONCISE INTRODUCTION TO WINDOWS 386

N. Kantaris

Shows the PC user all they need to know when using Windows (Version 3) (1990 80 pages)

ORDER CODE: BP288 PRICE: £3-95

A CONCISE INTRODUCTION TO GEM

J.W. Penfold

GEM is a system of computer control consisting of pictorial representations of files & operations which are then manipulated using the 'mouse'.

This book explains to the beginner all they need to know about GEM. (1989 80 pages)

ORDER CODE: BP230 PRICE: £2-95

AN INTRODUCTION TO PROGRAMMING THE COMMODORE 16 & PLUS 4

R.A. Penfold

Helps you to learn to use and program these two Commodore machines with the minimum of difficulty by expanding and complementing the information supplied in the manufacturers own user manual. (1985 128 pages)

ORDER CODE: BP158 PRICE: £2-50

USING YOUR AMSTRAD CPC DISC DRIVES

J.W. Penfold

Everything you are likely to need to know to enable you to get the maximum from your Amstrad. Covers such things as tracks, sectors & formatting, AMDOS & CP/M operating systems including rules and regulations, filing from BASIC, file copying & transfer, program development including MERGE & CHAIN MERGE; CP/M turnkey discs etc. (1986 96 pages)

ORDER CODE: BP189 PRICE: £2-95

HOW TO WRITE AMSTRAD CPC464 GAMES PROGRAMS

W. Simmister

Written as a step by step guide to assist in writing your own graphics games programs. Starts at the basic level progressing to a 3D game. Also applicable to the CPC664 & 6128. (1985 144 pages)

ORDER CODE: BP159 PRICE: £2-50

LOGO FOR BEGINNERS

J.W. Penfold

The ideal book for those who want to start programming in LOGO. Starts at the beginning and progresses right up to the elements of artificial intelligence.

ORDER CODE: BP193 PRICE: £2-95

A CONCISE INTRODUCTION TO MS-DOS

N. Kantaris

This guide is written with the 'busy' non-expert in mind, although the more experienced user can start from any section. The guide explains:

How the DOS operating system is structured so you can understand what happens as soon as you switch on your computer. How to use the DOS commands. How to use the EDLIN line editor to fully configure your system by writing your own CONFIG.SYS and AUTOEXEC.BAT files.

How directories and sub-directories can be employed. How to write your batch files. How to manage your systems environment. The guide covers versions 3.0, 3.1 and 3.2 of both PC-DOS and MS-DOS as implemented by IBM and IBM compatibles. It covers both floppy & hard disc based systems. (1987 64 pages)

ORDER CODE: BP232 PRICE: £2-95

AN INTRODUCTION TO PROGRAMMING THE BBC MODEL B MICRO

R.A. & J.W. Penfold

Written for readers wanting to learn more about programming and how to make best use of the incredibly powerful model B's versatile features. Most aspects covered. (1984 144 pages)

ORDER CODE: BP139 PRICE: £1-95

COMPUTER TERMINOLOGY EXPLAINED

I.D. Poole

Explains a wide range of terms that form the computer jargon used by enthusiasts and which also appears in books & magazines. Also includes a reference guide to the more commonly used BASIC commands found on most microcomputers. (1984 96 pages)

ORDER CODE: BP148 PRICE: £1-95

AN INTRODUCTION TO COMPUTER COMMUNICATIONS

R.A. Penfold

Provides details of the various types of modem and their suitability for specific applications plus details of connecting various computers to modems and modems to the telephone system. Also information on common networking systems and RTTY. (1986 80 pages)

ORDER CODE: BP177 PRICE: £2-95

20 PROGRAMS FOR THE ZX SPECTRUM & 16K ZX81

S. Daly

Don't be put off by the title if you are a non-sinclair enthusiast. All these programs were written & tested on the ZX81 and Spectrum machines but most will run on any computer with a good BASIC interpreter and at least 5K of RAM. Copious notes are given on each of the programs including the changes required on Non-Sinclair systems. (1983 128 pages)

ORDER CODE: BP128 PRICE: £1-95

BASIC AND LOGO IN PARALLEL

S.J. Wainwright

A book comparing & contrasting BASIC & LOGO. LOGO is not only an educational language but it can also be used for other applications as this book will show. Included is a LOGO graphics interpreter written in BBC BASIC. (1987 96 pages)

ORDER CODE: BP196 PRICE: £2-95

AN INTRODUCTION TO MSX BASIC

R.A. Penfold

MSX BASIC is the "universal" Japanese version of the BASIC language that will enable the same software to be simply run on machines manufactured by a number of different makers. This book helps you get to grips with this fascinating concept. (1985 128 pages)

ORDER CODE: BP154 PRICE: £2-50

GETTING THE MOST FROM YOUR PC HARD DISK

R.A. Penfold

Shows in simple terms how to get the best from your PC Hard Disk (1990 96 pages)

ORDER CODE: BP280 PRICE: £3-95

50 (FET) FIELD EFFECT TRANSISTOR PROJECTS

F.G. Rayer

FET's find applications in a wide variety of circuits. The projects described here include radio-frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers & tone controls, as well as various miscellaneous devices useful in the home.

The FET used in most cases is not critical and many types will perform satisfactorily. The FET is a low noise, high gain device with a multitude of uses, the dual gate being of particular use in mixers etc. (1977 112 pages)

ORDER CODE: BP39

PRICE: £2-95

ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS

R.A. Penfold

Provides essential information & circuits on computer control of electric motors (including stepper types), plus a range of useful sensors including visible light, infra-red & ultrasonic types. (1986 96 pages)

ORDER CODE: BP179

PRICE: £2-95

A BEGINNERS GUIDE TO MODERN ELECTRONIC COMPONENTS

(R.A. Penfold)

It is easy for newcomers to electronics to become confused by the wide range of components currently available. There are now a great many different types of components on offer often with several variations on each type! This book contains an invaluable amount of information to assist in component selection.

This really is a must for all. (1990 178 pages)

ORDER CODE: BP285

PRICE: £3-95

MODERN OP-AMP PROJECTS

R.A. Penfold

Includes a wide range of constructional projects which make use of the specialised op-amps that are now available, including low noise, low distortion, ultra-high input impedance, low slew rate & high output current types. (1982 112 pages)

ORDER CODE: BP106

PRICE: £1-95

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

A. Michaels

Helps the reader to find equivalents/substitutes for a popular user-oriented selection of European, American & Japanese transistors. Also shows material type, polarity, manufacturer & typical use. This book really is a must for both hobbyist & engineer. (1981 320 pages)

ORDER CODE: BP85

PRICE: £3-95

REMOTE CONTROL HANDBOOK

O. Bishop

This replaces our original book BP73 and is aimed at the electronics enthusiast who wishes to experiment with remote control in its many aspects & forms. (1988 240pgs)

ORDER CODE: BP240

PRICE: £3-95

50 CIRCUITS USING GERMANIUM SILICON & ZENER DIODES

R.N. Soar

This book contains 50 very interesting & useful circuits & applications, covering many different areas of electronics, using one of the most inexpensive components - the diode. Includes the use of germanium & silicon signal diodes, silicon rectifier diodes and zener diodes, etc etc. (1977 64 pages)

ORDER CODE: BP36

PRICE: £1-50

TRANSISTOR RADIO FAULT-FINDING CHART

C.E. Miller

Used properly, it should enable the reader to trace most common faults quite quickly. Across the top of the chart will be found four rectangles containing brief descriptions of these faults, i.e. sound weak but distorted, set dead, sound low or distorted and background noise etc. One then selects the most appropriate of these following the arrows, carries out the suggested checks in sequence until the fault is cleared.

A most useful book! (1980 chart)

ORDER CODE: BP70

PRICE: £0-95

MORE ADVANCED USES OF THE MULTIMETER

R.A. Penfold

A sequel to book BP239, showing the reader some more advanced & unusual applications of a simple multimeter. (1989 96 pages)

ORDER CODE: BP265

PRICE: £2-95

AUDIO PROJECTS

This book covers in detail the construction of a wide range of audio projects. The text has been divided into the following main sections:

Pre-amplifiers & Mixers, Power Amplifiers, Tone Controls and Matching, Miscellaneous Projects.

All the projects are fairly simple to build and to assist the newcomer to the hobby, a number of board layouts & wiring diagrams are included. (1981 96 pages)

ORDER CODE: BP90

PRICE: £2-50

50 PROJECTS USING RELAYS, SCR's & TRIACS

F.G. Rayer

Relays, SCR's & TRIACS have a wide range of applications. These may extend over the whole field of motor control: dimming and heat control; delayed timing, & light sensitive circuits and include warning devices, various novelties, light modulators, priority indicators, excess voltage breakers etc etc.

This book gives tried & practical working circuits which should represent the minimum of difficulty for the enthusiast to construct. (1977 112pages)

ORDER CODE: BP37

PRICE: £2-95

30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1

Each project, which is designed to be built on a 'Protobloc' or less common now 'Verobloc', is presented in a familiar fashion with a brief circuit description, circuit diagram, component layout diagram, component list & notes on construction & use where necessary. Wherever possible, the components used are common to several projects hence only a modest number of components required with a budget to match! This book has been recommended by BICC-VERO! (1982 160 pages)

ORDER CODE: BP107

PRICE: £2-95

30 SOLDERLESS BREADBOARD PROJECTS - BOOK 2

R.A. Penfold

The companion book to Book 1 (BP107) and presented in exactly the same way using the 'protobloc' method. However, all the projects in this book are based on CMOS logic I.C's whereas Book 1 used Linear I.C's. The information in Book 1 regarding identifying components is NOT repeated in this book so we strongly suggest the beginner buys Book 1 first! Once again, this book is recommended by BICC-VERO! (1983 160 pages)

ORDER CODE: BP113

PRICE: £2-25

BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS

R.A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that they can build with confidence electronic projects regularly featured in popular magazines & books. Also includes examples of simple projects. (1977 112 pages)

ORDER CODE: BOOK/227

PRICE: £1-95

ELECTRONIC MUSIC PROJECTS

R.A. Penfold

Provides the constructor with a number of practical circuits for the less complex items of electronic music equipment including such things as Fuzz Box, Waa Waa pedal, sustain unit, reverberation & phaser units. The text is divided into 4 chapters as follows:

Chapter 1: Guitar effect units, Chapter 2: General effects units, Chapter 3: Sound generator projects, Chapter 4: Accessories. (1980 112 pages)

ORDER CODE: BP74

PRICE: £2-50

MORE ADVANCED ELECTRONIC MUSIC PROJECTS

R.A. Penfold

Intended to complement the first book (BP74) by carrying on where it left off and providing a range of slightly more advanced & complex projects. Included are popular effect units such as 'Flanga', phaser, Mini-chorus & 'Ring' modulator units. Some useful percussion synthesisers are also described & together these provide a comprehensive range of effects including: Drum, Cymbal & Gong type sounds!

ORDER CODE: BP246

PRICE: £2-95

LOUDSPEAKER SALE

EMINENCE

Eminence is the worlds leading supplier of loudspeakers, used in the cabinets and amplifiers built by all the major M.I. manufacturers in the U.S.A. This range of loudspeaker is a versatile range for guitar and bass instrument sound production. The linen edge gives a smooth sound and excellent bass response; particularly suited to bass guitars, keyboards and bass driving in multi-way enclosures and P.A. systems.



EM8-100



EM8-100

Nominal Chassis Diameter: 8", 203.2mm
 Impedance: 8Ω or 16Ω
 Power Rating: 100W_{RMS}
 Resonance: 72Hz
 Usable Freq Range ±6dB: 72Hz to 4kHz
 Average Sensitivity 1W@1m: 97dB
 Magnet Weight: 38oz
 Magnet Gap Depth: 0.312", 8mm
 Voice Coil Diameter: 2.0", 50.8mm

SUGGESTED APPLICATIONS

Performance optimised for midrange use over a bandwidth of 400Hz to 4kHz in multiway systems. Also suitable for vocal PA., keyboards, discotheque, monitors and bass guitar.

£29-99
~~£34-00 each~~
~~£67-00 pair~~
ANY QTY



EM10-100



EM10-100

Nominal Chassis Diameter: 10", 254mm
 Impedance: 8Ω or 16Ω
 Power Rating: 100W_{RMS}
 Resonance: 71Hz
 Usable Freq Range ±6dB: 70Hz to 7kHz
 Average Sensitivity 1W@1m: 97dB
 Magnet Weight: 38oz
 Magnet Gap Depth: 0.312", 8mm
 Voice Coil Diameter: 2", 50.8mm

Performance optimised for lead guitar. Also suitable for bass guitar, vocal P.A., keyboards, discotheques, club music systems and stage monitors.

£33-00
~~£39-59 each~~
~~£72-00 pair~~
ANY QTY



EM12-100PE



EM12-100PE

Nominal Chassis Diameter: 12", 304.8mm
 Impedance: 8Ω or 16Ω
 Power Rating: 100W_{RMS}
 Resonance: 94Hz
 Usable Freq Range ±6dB: 95Hz to 6kHz
 Average Sensitivity 1W@1m: 99dB
 Magnet Weight: 38oz
 Magnet Gap Depth: 0.312", 8mm
 Voice Coil Diameter: 2", 50.8mm

SUGGESTED APPLICATIONS

Performance optimised for lead guitar.

£34-00
~~£41-31 each~~
~~£75-00 pair~~
ANY QTY



EM12-300



EM12-300

Nominal Chassis Diameter: 12", 304.8mm
 Impedance: 8Ω or 16Ω
 Power Rating: 300W_{RMS}
 Resonance: 47Hz
 Usable Freq Range ±6dB: 46Hz to 5kHz
 Average Sensitivity 1W@1m: 103dB
 Magnet Weight: 95oz
 Magnet Gap Depth: 0.375", 9.53mm
 Voice Coil Diameter: 3.0", 76.2mm

SUGGESTED APPLICATIONS

Performance optimised for sound reinforcement systems. Also suitable for lead and bass guitar, keyboards, guitar combos, club music systems and stage monitors.

£59-99
~~£74-00 each~~
~~£135-00 pair~~
ANY QTY



EM15-200




EM15-200

Nominal Chassis Diameter: 15", 381mm
 Impedance: 8Ω or 16Ω
 Power Rating: 200W_{RMS}
 Resonance: 46Hz
 Usable Freq Range ±6dB: 45Hz to 5kHz
 Average Sensitivity 1W@1m: 99dB
 Magnet Weight: 56oz
 Magnet Gap Depth: 0.375", 9.53mm
 Voice Coil Diameter: 2.5", 63.5mm

SUGGESTED APPLICATIONS

All bass applications, including bass guitar.

£55-00
~~£69-00 each~~
~~£125-00 pair~~
ANY QTY

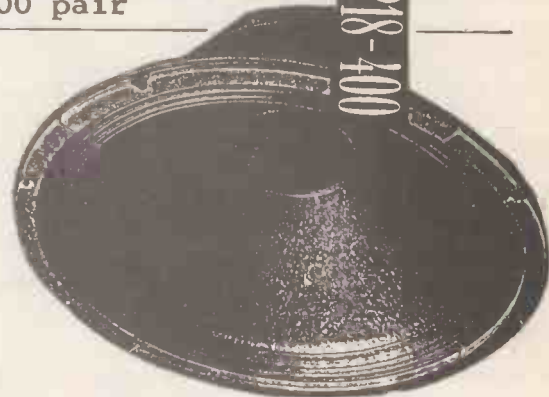

EP18-400


Nominal Chassis Diameter: 18", 457.2mm
 Impedance: 8Ω or 16Ω
 Power Rating: 400W_{RMS}
 Resonance: 33Hz
 Usable Freq Range ±6dB: 30Hz to 8000Hz
 Average Sensitivity 1W@1m: 98dB
 Magnet Weight: 95oz
 Magnet Gap Depth: 0.375", 9.53mm
 Voice Coil Diameter: 3", 76.2mm

~~£142-00 each~~
~~£255-00 pair~~

£110-00
ANY QTY

LOUDSPEAKER GRILLS - STEEL

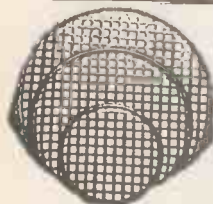Very high quality, BLACK finish with rubber Very strong and available in 8 sizes.



CODE	SIZE	1+	4+
L001	5"	£1-30	£1-15
L002	6"	£1-45	£1-30
L003	8"	£1-80	£1-65
L004	10"	£2-20	£2-00
L005	12"	£2-70	£2-45
L006	15"	£3-60	£3-27
L007	18"	£6-95	£6-35

CLAMP KIT



Speaker grill fixing kit. Contains 4 each: Screws Self fixing nuts Steel clamping plates

ORDER CODE: LSP/CKIT

1+ 10+ 100+
 £1-25 £1-12 88p

ALL PRICES INCLUDE V.A.T.

ADD £3.00 P & P PER ORDER

COMDEK HOBBY KITS

For those of you who are not yet familiar with the COMDEK range of Kits, we would advise you that ALL of these Kits are designed & packed in the UK. All PCB's are Silk-Screened and not only designed in the UK but also UK made!

THE GOLDEN RULE FOR KIT ASSEMBLY IS SIMPLE.....READ THE INSTRUCTIONS BEFORE YOU START!!

TWIN ALTERNATE LED FLASHING UNIT - RED

(PCB SIZE: 45 X 30mm)

Two Red LED's which flash alternately at a fully adjustable rate operating on a voltage from 3V up to 15V, at approx. 25mA depending on voltage it is run at.

Ideal for battery use using either AA, C, D or PP3 size battery. Can also be used 'In-Car' at 12V and can also be used with the Comdek Anti-theft unit listed below.

Applications include: Burglar & Car Thief deterrent, model construction, name badge sign, jewellery etc etc.

	1+	4+	10+
ORDER CODE: COM/KIT/004	PRICE: £5-75	£5-25	£4-75

TWIN ALTERNATE LED FLASHING UNIT - RED and GREEN

(PCB SIZE: 45 X 30mm)

Two LED's, one Red and one Green which flash alternately at a fully adjustable rate operating on a voltage from 3V up to 15V, at approx. 25mA depending on voltage used.

Ideal for battery use using either AA, C, D or PP3 size battery. Can also be used 'In-Car' at 12V and can also be used with the Comdek Anti-Theft unit listed below.

Applications include: Burglar & Car Thief deterrent, model construction, name badge sign, jewellery etc etc.

	1+	4+	10+
ORDER CODE: COM/KIT/001	PRICE: £5-99	£5-50	£5-00

CABLE AND METAL DETECTOR

(PCB SIZE: 60 X 40mm)

A super kit, using a ferrite antenna. The 'Detection' range is up to approx. 6cm. Complete with LED for visual indication. Operates at 3Volts using 2 X AA batteries.

Applications include: Detecting cables in walls, under floors, detecting hidden pipes, nails in wood.

	1+	4+	10+
ORDER CODE: COM/KIT/002	PRICE: £5-95	£5-45	£4-95

F.M. MINI-TRANSMITTER

(PCB SIZE: 40 X 25mm)

A super quality, very small mini-bug, ideal for baby alarms etc!! Simply runs off 1 X AA (1.5V) battery! We had a unit running for over a week none stop! Whilst range is always difficult to quote because it depends on location & conditions, we have achieved over half a mile! A well tried & tested unit, excellent value for money.

	1+	4+	10+
ORDER CODE: COM/KIT/003	PRICE: £7-50	£6-85	£5-99

ELECTRONIC ACUPUNCTURE

A new kit to our range, but we think you will love it. Based on the ancient practise of Acupuncture but instead of using needles we use electronics! And very effective it is too. This kit operates, as they say, in accordance with the electrical acupuncture method. A fully illustrated leaflet is included for the treatment of many ailments. Come on, give it a go!

Operates on between 3v and 12V.

- | | | | |
|--|--|---|---------------------------|
| * arthritic pain or a sprain.
shoulders | * Lumbago or back aches
* muscle pain | * Stimulates blood circulation
* arm & leg neuralgia | * strained
* neuralgia |
|--|--|---|---------------------------|
- * and lots more!!!

	1+	4+	10+
ORDER CODE: COM/KIT/005	PRICE: £8-95	£8-00	£6-75

CAR, MOTORHOME, VAN ANTI-THEFT UNIT - AT1

(PCB SIZE: 80 X 60mm)

A brand new design and indeed a very clever device which gives 100% peace of mind to the vehicle owner and causes the would be car thief 100% frustration! This unit may also be used 'alongside' an existing car alarm. So, what's so special about this device?

Most alarms require the owner to activate them when you exit the vehicle, which can easily be overlooked or simply forgotten. The AT1 circuit overcomes this by activating the moment the ignition is switched on or the vehicle is 'Hot wired' making it impossible to forget. From the moment the ignition is first switched on the AT1 circuit starts timing. When the engine has started the unit must be 'de-activated' otherwise, and this is the clever bit, the engine will cut out.

The method of de-activating the unit is set by the installer. We recommend wiring up to one or more switches i.e. rear window de-mist, wipers, interior light, etc etc, the choice is yours! You can of course wire up to a concealed switch.

Therefore, until the chosen switch/switches are 'switched' ON/OFF, the AT1 will NOT De-activate and the engine will stop after the pre-set time.

Every AT1 is pre-set at approx. 20 seconds but this may be shortened or lengthened to suit your requirements up to 130 seconds. This time of course, governs how far your vehicle will travel before the engine cuts out!

The car thief will then be faced with the problem of not only the engine cutting out but then failing to re-start! The thief will not hang around to 'repair' the vehicle. Simple!

A Red LED is supplied with kit which may be fitted to the dashboard and will remain lit all the time acting as a deterrent to any would be car thief.

Suitable for both Electronic & Non-Electronic Ignition cars. Full fitting instructions are supplied with the assembly instructions.

Such a success has this kit been that we can now offer a ready built unit. See below for prices.

	1+	4+
ORDER CODE: COM/KIT/AT1	PRICE: £15-00	£12-50

READY BUILT CAR, MOTORHOME, VAN ANTI-THEFT UNIT

Supplied ready built and housed, simply follow the installation instructions and fit to your vehicle.

	1+	4+
ORDER CODE: COMDEK/BUILT/AT1	PRICE: £25-99	£24-00

SUPER SOLDER SALE

High grade 60/40 tin/lead alloy solder available in both 18swg & 22swg, in a choice of reel sizes from 18gms to 500gms ($\frac{1}{2}$ Kg). Manufactured to BS219. Contains 5 cores of type 362 non-corrosive flux. Melting temperature is 188°C. **NOW JUST LOOK AT OUR AMAZING PRICES**

18swg (1.2mm)

Reel Size	Approx. Length	ORDER CODE	1+	10+	100+
18gms	3 Metres	SOLD/18/3Y	65P	50P	40P
200gms	21 Metres	SOLD/18/200	£2-25	£2-00	£1-60
500gms ($\frac{1}{2}$ Kg)	52 Metres	SOLD/18/500	£4-75	£4-25	£3-50
22swg (0.71mm)					
200gms	62 Metres	SOLD/22/200	£2-35	£2-10	£1-75
500gms ($\frac{1}{2}$ Kg)	153 Metres	SOLD/22/500	£4-79	£4-30	£3-60

REMEMBER: BUY 100 REELS OF 18swg 500gms & PAY ONLY £2-98 + VAT PER REEL!

SOLDERING IRON STAND - Heavy Duty

Suitable for use with ANTEX and most other leading makes of soldering irons. The heavy base makes it very stable. Supplied complete with sponge

ORDER CODE: SOLD/814

PRICE: £2-99



**WHOLESALE
PRICES AND
EX-STOCK
NOW!!**

EXTERNAL HALOGEN FLOODLIGHT & P.I.R.

A high power security floodlight with built-in PIR detector which reacts to body heat switching on the floodlight whenever somebody approaches within the detection zone. The PIR is adjustable for horizontal and vertical angle and contains a photo detector to prevent daylight operation.

Power: 220-240Vac.

- * Choice of 200W, 300W or 500W lamp.
- * Adjustable range up to 15 Metres.
- * Adjustable 'Time On' 9 secs to 10 mins.
- * Twilight setting is adjustable.

If you don't state a lamp wattage preference 500watt will be sent.



SALE PRICE £29-99 (Incl. Lamp)

PROTECT YOUR HOME NOW!



ALL PRICES INCLUDE V.A.T.

14


ADD £3.00 P & P PER ORDER

POTENTIOMETERS and P.C.B.'s

ROTARY POTENTIOMETERS - Single

A range of British Made, carbon track, potentiometers with 1/2" dia. plastic spindle and PCB mounting terminals.

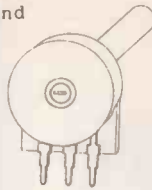Fixing Hole.....10.5mm
 Spindle Dia..... 6.35mm(1/4")
 Spindle Length.....55mm
 Power rating.....0.4W LIN, 0.2W LOG
 Max Volts.....500Vdc
 Tolerance.....+20%



Supplied complete with fixing nut and locking washer. Available in LIN and LOG.

LIN: 470R, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M0, 2M2, 4M7.

LOG: 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M0, 2M2.

ORDER CODE: POT/LIN or LOG + Value Required


	1+	10+	100+
PRICE:	64p	56p	48p

ROTARY POTENTIOMETERS - Stereo

Same technical spec. as above single pots. Supplied complete with fixing nuts etc. Values same as above Single pots.

ORDER CODE: POT/DUAL/ LIN or LOG + Value required.

	1+	10+	100+
PRICE:	£1-70	£1-55	£1-25

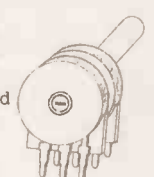


ROTARY POTENTIOMETERS - Switched - DPST 4Amp

Same technical spec. as above single & dual pots. Supplied complete with fixing nuts etc. Values as above.

ORDER CODE: POT/SW/LOG or LIN + Value required

	1+	10+	100+
PRICE:	£1-60	£1-50	£1-35

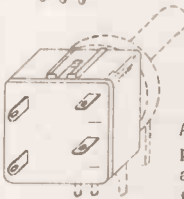

STRIPBOARD

STRIPBOARD - Copper Clad

A good quality stripboard with 0.1" spaced holes.

CODE	SIZE	Tracks	Holes	PRICE
PCB/500	25X64	9	25	22p
PCB/505	64X95	24	37	69p
PCB/515	95X127	36	50	£1-15
PCB/535	95X432	36	170	£4-50
PCB/540	119X455	46	179	£5-50

MATRIX BOARD - Plain

Plain board with no copper strips. Holes also on a 0.1" grid.

PCB/0585	95X127	36X50 Holes	£1-15
PCB/0595	119X455	46X179 Holes	£5-00

STRIPBOARD CUTTER

Simply insert tool at the point where break is required and twist clockwise!

ORDER CODE: PCB/TOOL PRICE: £2-50

TERMINAL PINS

Press fit terminal pins for use with stripboard. Single sided pins are NOT suitable for the above Matrix board. Pack Qty: 100 pins

ORDER CODE: PCB/SINGLE 85p per pack
 ORDER CODE: PCB/DOUBLE £1-50 per pack

PROTOBLOC PROTOTYPING BOARDS

Protobloc 2

Protobloc 2 has a total of 840 tie points consisting of two sets of 64 rows of 5 interconnected sockets plus 4 rows of 50 interconnected sockets running alongside, suitable for use as power supply rails. All contact positions are clearly defined on an alphanumeric grid. ABS polymer board mounted on an adhesive foam base. Will accommodate up to seven 16 pin devices.

ORDER CODE: PCB/PB2 PRICE: £6-50

PROTOBLOC BOARD

TYPE: Y035G

2420 contacts arranged in six blocks of 64 rows of 5 interconnected sockets on a standard 0.1" pitch. Supplied mounted on a baseboard with 4 X 4mm sockets. Dimensions: 243 X 195 X 20mm.

ORDER CODE: PCB/Y035G PRICE: £19-99

PHOTO-ETCH PCB - Economy

Good quality board, manufactured in FRG-50 laminate with positive working UV sensitive resist. Boards are protected by a black sensitive film.

SIZE (mm)	ORDER CODE	1+	10+
100 X 160	PCB/PB/SS1	£1-75	£1-60
100 X 220	PCB/PB/SS2	£2-25	£2-00
114 X 203	PCB/PB/SS3	£2-30	£2-05
12" X 18"	PCB/PB/SS4	£12-95	£11-75

Double sided available in above sizes, please telephone for prices.

PHOTO-ETCH PCB - Professional

Photo resist boards in FR4 Epoxy Glass coated with positive working UV sensitive resist. Boards are supplied with protective black plastic film.

SIZE (mm)	ORDER CODE	1+	10+
100 X 160	PCB/FR4/SS1	£2-60	£2-34
100 X 220	PCB/FR4/SS2	£3-25	£2-95
203 X 114	PCB/FR4/SS3	£3-10	£2-80

ULTRAVIOLET EXPOSURE UNIT WITH TIMER



An ultraviolet unit for preparing photo-resist boards as per above. 1:1 artwork using Alfac type transfers on translucent drafting film. Simply place on the glass screen with the photo-board on top. Complete with built-in 6 minute timer. 2 X 8watt UV tubes (replaceable) and full instructions! Comes with 13A plug fitted!

ORDER CODE: PCB/UV1 PRICE: £79-50

FERRIC CHLORIDE

Crystals

Ferric chloride etchant in crystalline form. Pack weight: 500gm to produce approx 1 litre of concentrated solution.

ORDER CODE: PCB/ETCH PRICE: £3-50

DEVELOPER

Developer crystals for use with our photo-resist board above. Contains enough to make approx. 500ml of solution.

ORDER CODE: PCB/DEV PRICE: £1-00

POLISHING BLOCK

Super quality, after use simply wipe away traces of the abrasive. Dims: 30 X 40 X 20mm


ORDER CODE: PCB/BLCK PRICE: £1-65

RADIUS AID - CIRCULAR PROTRACTOR - With Bevel

Contains 16 circles with radii ranging from 1mm up to 15mm. Overall dia: 115mm
 Material: Glass-clear Dunilon

PCB/71F

PRICE: £1-85

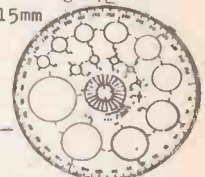

ARTWORK DRAFTING FILM

Used with drafting tapes & transfer film master artwork for the layout of PCB's. Pack contains 5 sheets 0.003in single matt polyester film & one sheet 0.005in film printed with 0.1in grid for accurate layout of pads/symbols.

Size: 248 X 148mm

ORDER CODE: PCB/ART £3-99 per pack

**MONITOR
SALE**

**£10-00
EACH !!**



We have a large quantity of Black & White monitors, intended for CCTV application, that are faulty, or picture quality is not up to scratch. These monitors HAVE NOT been checked by our engineers! It simply costs us too much money. Therefore we are selling them off at a silly price to make space. First come first served, No Guarantees and NO RETURNS for any reason!

ORDER CODE: SO/MON/CC PRICE: £10-00

**STERNICE HIGH WATTAGE WIREWOUND RESISTORS
BRAND NEW! Very very large!!**

Marked as follows:

STERNICE RWST 50.373 180ohm 5% X.9

Dimensions: 370mm length. 50mm Dia.
Weight: 2kg. Complete with fixing bracket.

Two values available: 100ohm & 180ohm.

Value	ORDER CODE	1+	10+
100ohm	SO/661A	£4-99	£3-50
180ohm	SO/662	£4-99	£3-50

CONTROLLED BRIDGE RECTIFIER 'SPECIAL'

PACE-Pak (Brand New) International Rectifier Pace-pak modules give single phase bridge configurations of thyristors & diodes, mounted on an aluminium substrate to provide a completely isolated assembly.

Farnell current price £23-30 each plus VAT!



Body: H=14 (excl terminals), W=48, D=32
Base plate: W=64, D=32, Fixing Centres=49.5



25A 1200V (Type P135)

ORDER CODE: SO/663

PRICE: £9-99

TRANSFORMER

(Brand New)

Super quality transformer. Limited quantity.

Primary: 0-10-220-240-380-415V

Secondary: 0-17V 250mA

0-17V 250mA

Fixing Centres 75mm. Height: 50mm

Top dims: 60 X 70mm.

ORDER CODE: SO/664

PRICE: £3-50



CAPACITOR

ARCOTRONICS

No info, only whats on the capacitor:

VISCONOL 8uF ±20% 1000VDC WKG at 70°C

650VDC WKG at 100°C

DIMS: H 120mm W 85mm D 65mm

2 contacts on top of capacitor.

ORDER CODE: SO/665

PRICE: £2-50

HEATSINK

(USED)

Still has a couple of SEMIKRON SKT 24/12C fitted. (Bolted On). Maybe SCR's. Not all checked so if you get one with a different component fitted DON'T ask to send it back!!


ORDER CODE: SO/666

PRICE: £1-50



WE BUY SURPLUS STOCK

**RSGB CALL BOOK
1991-1992**

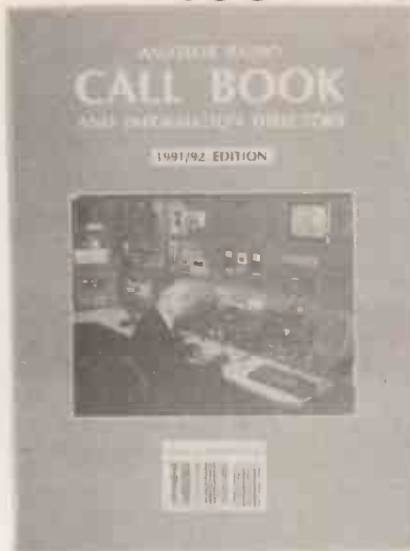

**LESS
THAN
HALF
PRICE!!
£2-99**

The Official RSGB (Radio Society of Great Britain) Call Book & Information directory. This publication is a must for anyone with an interest in Amateur Radio. 430 pages! Lists all UK & EIRE Call signs with names & addresses and is packed with information including: Abbreviations, Awards, Band Plans, Beacons, Clubs, Contests, EMC, Licensing Info., Locators, Morse Info, News, Packet nodes, Propagation, QSL, Planning Permission, RAE, Raynet, Repeaters, RSGB Info., Safety, Satellites, Special Event Stations ETC ETC.

DIMS: 200 X 270mm.

NORMAL PRICE IS OVER £7-00 !!!!!

SALE PRICE £2-99



**BROADBAND RADIO
RECEIVER**

A handheld radio with a range covering: CB, FM, TV, AIR Band & PB Band. Built in telescopic aerial Squelch, volume & tuning controls & Band selector switch.

FREQUENCY RANGE:

AIR	108-145MHz
PB	145-176MHz
WB	162.5MHz
TV	54-87MHz
FM	88-108MHz
CB	1-80 Channels

Power: 4 X AA
(Batts Not Incl)
DIMS: 93X198X50

£17-50

**WIREWOUND POTENTIOMETERS 10K Tol ±20% 3 WATTS.
AB**

Very high quality, Made in UK.

Current Trade price: £4-76 each plus VAT!!!!

Dia: 45mm Shaft Length: 40mm


LIMITED QUANTITY...Hurry Hurry.

ORDER CODE: SO/667

PRICE: £2-50 each!

SINCLAIR KEYBOARD OFFER

ZX SPECTRUM +2A/+3/+3A

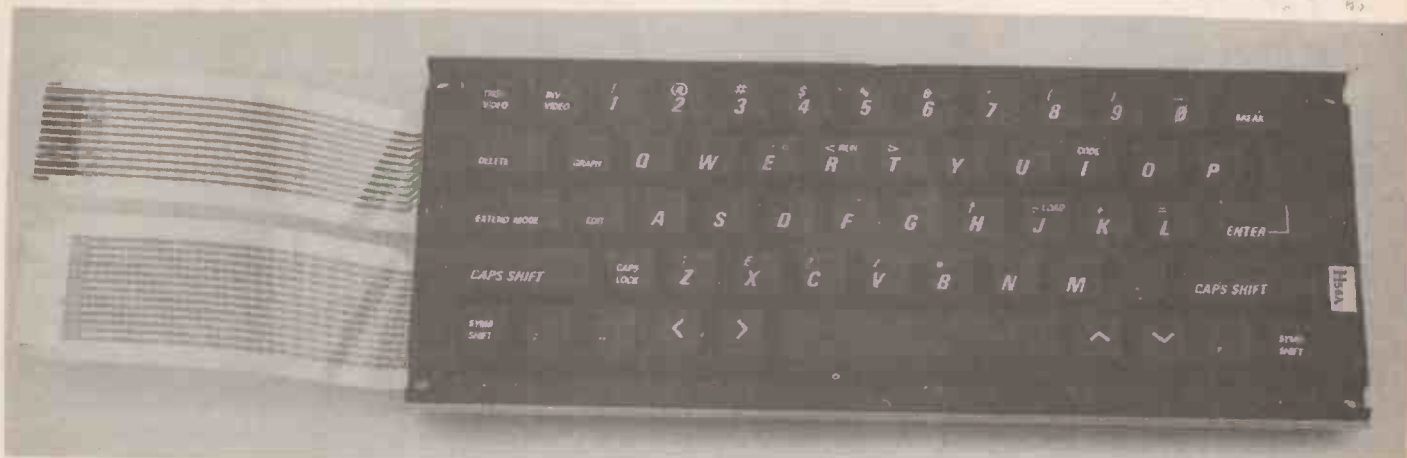

Those of you who service/repair Sinclair computers will know what a real bargain these are. However, only limited stocks so hurry, hurry! These keyboards are made by Amstrad!

ALL BRAND NEW!!

Marked as follows: 40060/B ESU2456A .

At time of printing, the Trade price for this keyboard is £26-06 + VAT!!

ORDER CODE: SO/668

SALE PRICE: £6-50 2 FOR £11-50

PACKING TAPE CLEARANCE!!

Such a success was our Summer Sale of Parcel tape that we sold out!! However, we have just taken delivery of 6,000 reels of packing tape but not brown in colour but clear. Very high quality and a **tremendous** saving on the normal price. Hurry, hurry, this well sell out quickly!

REMEMBER.....ALL OUR PRICES INCLUDE V.A.T.!!!

Length: 66 Metres

NORMAL PRICE IS £1-15 per REEL!!

WIDTH: 50mm

Colour: Clear

	1+	10+	100+
SUPER SALE PRICE:	65P	55P	48P

RECHARGEABLE BATTERIES - NI-CADS

At time of printing our Ni-Cads are Hitachi with the exception of the PP3. Should the Hitachi be unavailable we will supply a suitable alternative brand.

We guarantee our batteries may be charges 1000 times!

Type	Volt	Ah	Order Code	1+	10+
AAA	1.2V	180mAh	BAT/AAA	£1-50	£1-30
AA	1.2V	500mAh	BAT/AA	95p	85p
C	1.2V	1.2Ah	BAT/C	£1-95	£1-80
C	1.2V	2.0Ah	BAT/CI	£3-40	£3-20
D	1.2V	1.2Ah	BAT/D	£2-00	£1-85
D	1.2V	4.0Ah	BAT/DI	£4-75	£4-50
PP3	9V	110mAh	BAT/PP3	£3-90	£3-75

NI-CAD BATTERY CHARGER

Capable of charging all the above sizes i.e.

4 X AAA, AA, C or D sizes
2 X PP3

White in colour, free-standing unit with LED 'charging' indicators. A built in tester is provided for 1.5V batteries.

Power: 240Vac

Dims: 180 X 85 X 50mm

BAT/CHARGE/UNIB	1+	10+
	£4-99	£4-75

ALL PRICES INCLUDE V.A.T.

17

ADD £3.00 P & P PER ORDER

SUPER PACK SALE

Our Component Packs were such a success when introduced in our Summer Supplement that we have increased the range. We have added approx. 17 more packs to our range and we will be adding even more over the next few months. For those of you who have already purchased some of our packs 'Thank You' for making them a success and for those who have not yet purchased any do so now and save money!

KNOB PACK

A pack containing an assortment of knobs, both rotary and slider. Some push On and some are screw fixing.

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/018

SALE PRICE: £4-50

SEVEN SEGMENT DISPLAY PACK

A most useful pack of assorted displays, may contain Red, Green, Single digit, double digit large & small. A very mixed pack.

Total Pack Qty: 20 Assorted

ORDER CODE: PACK/019

SALE PRICE: £3-00

0.5W Resistor Pack

A good assortment of good quality 0.5W Carbon Film resistors mainly 5% tolerance. Many preferred values included. A super buy.

Total Pack Qty: 1000 assorted

ORDER CODE: PACK/020

SALE PRICE: £2-00

ZENER DIODE PACK

A good selection of assorted voltages, from 3.0v to 180v and wattages 250mW to 5Watt.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/024

SALE PRICE: £2-75

VOLTAGE REGULATOR PACK

A most useful pack containing a good selection of assorted fixed and maybe variable regulators. Both +ve and -ve, from 100mA to 5A. Plastic and metal. Excellent value for money.

Total Pack Qty: 25 Assorted.

ORDER CODE: PACK/025

SALE PRICE: £5-00

PLUG TOP MAINS FUSE PACK

A pack of assorted 1" mains fuses. Anything from 3A to 13A. Super value for money.

Total Pack Qty: 40 assorted

ORDER CODE: PACK/029

SALE PRICE: £4-25

SLIDER POT PACK

A pack of metal and plastic mono and stereo sliders, Log and Lin. Values may range from 250 ohms to 1Meg

Total Pack Qty: 25pcs

ORDER CODE: PACK/030

SALE PRICE: £2-50

TUBULAR CERAMIC PACK

A good mixture of capacitors, anything from 1pF up to 10,000 pf. Radial leads ideal for PCB mounting.

Total Pack Qty: 100pcs

ORDER CODE: PACK/031

SALE PRICE: £1-50

TUNGSTEN DRILL BIT PACK

A mixed pack of metric solid tungsten carbide drill bits suitable for drilling glass fibre based pcb's and general hobby use. Original price was £4-20 each bit!!

Mixed sizes, anything from 0.4mm up to 3.0mm.

Total Pack Qty: 10 pcs.

ORDER CODE: PACK/033

SALE PRICE: £3-50

ELECTROLYTIC PACK

A good assortment of both axial & radial capacitors. Some radial's are already pre-cropped for PCB mounting. These packs contain a good selection of voltages from 10V to 1000V and values anything from 1.0uF to 1000uF.

This pack is excellent value for money.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/021

SALE PRICE: £2-50

DISC CERAMIC PACK

A super selection of assorted values and voltages. Many popular values are included. Voltages, anything from 5 to 1KV. Values, anything from 1.0pF to 0.1uF. Great value for money.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/022

SALE PRICE: £1-50

POLYSTYRENE PACK

A very useful range of assorted values and voltages of polystyrene capacitors. Many preferred values included.

Values range from 10pF to 0.01uF, and voltages up to 400V.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/023

SALE PRICE: £1-50

BRIDGE RECTIFIER PACK

A very mixed pack, excellent value for money. May contain voltages from 50 to 1000v and up to 10 Amps.

Total Pack Qty: 25pcs

ORDER CODE: PACK/026

SALE PRICE: £5-50

CABLE TIE PACK

A mixed pack of assorted length cable ties and maybe black ones.

Total Pack Qty: 100pcs

ORDER CODE: PACK/027

SALE PRICE: £2-00

HEATSHRINK PACK

A super pack, very high quality heatshrink sleeving. Much of it is British made.

A very good assortment of both colours and sizes.

Total Pack Qty: 10 Lengths approx 12" in length.

ORDER CODE: PACK/028

SALE PRICE: £1-25

500V SINGLE LAYER-CERAMIC PACK

A useful assorted pack of these very high quality capacitors. Very small, 8-16mm dia. Normal price over 50p each! Super value.

Total Pack Qty: 50pcs

ORDER CODE: PACK/032

SALE PRICE: £2-00

CALCULATOR PACK

A mixed pack of calculators! Hand held, mains desk type, printers, non-printers, cased, uncased, damaged cases, bits missing! You name it - this pack has it! Lots of useful bits. Sold by weight. Total Pack Weight: 10Kg

ORDER CODE: PACK/034

SALE PRICE: £5-00

SUPER PACK SALE

PRE-SET PACK

A mixed pack of various pre-sets. Miniature, standard, 0.1W, 0.25W, vertical, horizontal.

Assorted values from 100R to 1Meg.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/001

SALE PRICE: £3-00

POTENTIOMETER PACK

A mixed pack of pots single, dual, slider, convergence - in fact almost every kind of pot.

Assorted values ranging from 10R to 1Meg.

These really are super value.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/002

SALE PRICE: £4-50

VOLTAGE DEPENDANT RESISTOR PACK

A good mix of different types of V.D.R's
50-500V Super Value

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/003

SALE PRICE: £3-00

WIREWOUND RESISTOR KIT

A very mixed pack of assorted wirewound resistors. Mixed wattages and values, many popular values. A really good value pack.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/004

SALE PRICE: £2-50

DIL SOCKET PACK

A good assortment of various IC sockets which may range from 8 pin to 64 pin!

Generally low profile. May also include gold plated, turned pin, wirewrap etc.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/009

SALE PRICE: £8-00

SUPADRIV. Self Tapping Pack HARDWARE

A super pack of a mixture of No4 X $\frac{1}{2}$ and No6 X $\frac{1}{2}$. All Pan head hardened steel type AB bright zinc.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/010

SALE PRICE: £1-00

MIXED SELF-TAPPING SCREW PACK HARDWARE

A good mixture of various self-tapping screws of assorted types, lengths etc. All top quality. Length's 5-10mm

Total Pack Qty: 200 assorted

ORDER CODE: PACK/011

SALE PRICE: £1-50

PRE-SET PACK 0.25W

A super selection of 0.25W Pre-sets mainly Piher enclosed, AB etc.

Both vertical & horizontal and many popular values. Values may range from 100R to 10Meg!

Total Pack Qty: 100 pcs Assorted

ORDER CODE: PACK/016

SALE PRICE: £2-50

POLYESTER PACK

A good assortment of various polyester capacitors. Both Radial and Axial styles, values ranging from 0.01uF up to 2.2uF and voltages from 63V to anything up to 1000V!

This pack is very good value for money.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/017

SALE PRICE: £2-50

TANTALUM BEAD CAPACITOR PACK

A random selection of tantalum bead capacitors of assorted voltages and values. Many popular values.

Total Pack Qty: 50 pcs

ORDER CODE: PACK/005

SALE PRICE: £2-50

TRANSISTOR PACK

A mixed pack of various transistors, many popular types including:

AC169, BC107, BC125, BC147, BC148, BC158, BC182A, BC237, BC328, BC558, BCY72, 2N2907A, TIP126, TIP141, TIS90, 2N2222A, etc etc.

Over £17-00 value at current catalogue prices!!

Total Pack Qty: 100 pcs

ORDER CODE: PACK/006

SALE PRICE: £4-99

INTEGRATED CIRCUIT PACK

A super value pack containing all types of i.c's many popular types included.

All are new and full spec.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/007

SALE PRICE: £5-00

TRIMMER KIT

A useful kit containing a selection of 'ceramic' trimmers.

Values include: 2-7pF, 4-15pF, 6-25pF, 8-30pF.

Working voltage: 250Vac

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/008

SALE PRICE: £2-99

M5 & M6 Pack

A mixed pack of steel screws, a mixture of Pan Head Supadriv and Allen type. Length's 20-30mm All super quality and a real bargain!

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/012

SALE PRICE: £1-00

M4 Mixed Pack

A mixed pack of small M4 bolts - various lengths and types, pan, cross etc.

All the highest quality. Length's 5-20mm

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/013

SALE PRICE: £1-50

MIXED HARDWARE JUMBO PACK

A super Jumbo pack containing all types of bolts, screws, washers. All mainly small types and high quality. Also nuts etc. Length's 10-45mm

This pack is really super value for money.

We are selling this pack by weight: 1Kg.

This is up to 1000 pcs depending on sizes.

Pack Size: 1Kg

ORDER CODE: PACK/014

SALE PRICE:

FUSE PACK

A super pack containing an assortment of fuses which could include 20mm 32mm 1", fast blow, slow blow, in fact any type of fuse. Many popular sizes and values.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/015

SALE PRICE: £2-50

SURPLUS STOCK WANTED

ALL PRICES INCLUDE V.A.T.

19

ADD £3.00 P & P PER ORDER

SUPER PACK SALE

TRANSFORMER PACK

A super pack containing various small transformers, all being 220/240V primary. The secondary outputs will vary anything from 4.5V up to 12V.

Mainly chassis type but maybe some PCB types included. Current ratings anything from 200mA to 1Amp.

Total Pack Qty: 20pcs

ORDER CODE: PACK/035

PRICE: £15-00

WALKMAN PACK

Yes, you read it right! A very mixed pack of walkmans which may be complete, bits missing, working, non-working, cased or uncased. A very mixed pack at a very cheap price.

Feeling lucky? NO GUARANTEES!

Makes may include: AIWA, SANYO, SONY, JVC, MURPHY, etc.

Total Pack Qty: 4 pcs approx.

ORDER CODE: PACK/036

PRICE: £10-00

WATCH PACK

Another very mixed pack which may include LCD, LED, gents, boys, ladies, girls watches.

Watches may or maynot have straps, bracelets fitted. Having just seen a bracelet for sale for over £7-00 this pack is a winner!

Sold by weight, but you should get 6-10 watches.

Total Pack Weight: 1kg

ORDER CODE: PACK/037

PRICE: £5-00

MOTOR PACK

A good mixture of mainly 3-12Vdc motors but maybe a couple of 110V or 220v/240v included for good measure.

Total Pack Qty: 10pcs

ORDER CODE: PACK/038

PRICE: £5-00

SWITCH PACK

An assortment of switches which may include: rocker, illuminated, rotary, toggle, micro, push, slide, etc.

Total Pack Qty: 20 pcs

ORDER CODE: PACK/039

PRICE: £2-25

POWER SUPPLY PACK

An assortment of mainly 220/240V 2 pin low voltage power supplies useful for running calculators, radio's, walkman's etc. Most fit the standard UK shaver socket.

Total Pack Qty: 10pcs

ORDER CODE: PACK/040

PRICE: £5-99

BATTERY HOLDER PACK

A useful pack of assorted battery holders, ranging from maybe AAA up to D size. Some solder, some PP3/PP9 and some wire ended!

Total Pack Qty: 20 pcs

ORDER CODE: PACK/041

PRICE: £3-50

RUSSIAN TEST/CHART RECORDER PART PACK

We have just found in one of our warehouses a very large qty. of complete, part complete and spares for, chart recorders and some multimeters, from a large parcel that we purchased several years ago. Some of you may remember Z & I Aero Services Ltd ???

The chart recorders were mainly the H3020 series and the multimeters were the U4324 type. No promises but ALL IS MADE IN THE USSR!!!!

(As it was called)

Although sold by weight, if you find an item enclosed of partic. interest we may be able to quote you for it but only for quantity please.

Total Pack Weight: 10Kg

ORDER CODE: PACK/042

PRICE: £10-00

SOLDER PACK

A mixed pack of both 18swg & 22swg solder. Each pack contains 10 assorted 12" lengths of solder.

ORDER CODE: PACK/043

PRICE: £1-50

CONNECTOR PACK

A useful pack containg a wide & varied selection of assorted connectors. Typical types may include: D type, IDC, Edge, Audio, Chassis, Line etc. In fact almost any type including popular ones.

Total Pack Qty: 25pcs

ORDER CODE: PACK/044

PRICE: £5-99

DIN CONNECTOR PACK

An assorted pack of DIN plugs, sockets chassis & line.

Total Pack Qty: 25pcs

ORDER CODE: PACK/045

PRICE: £4-50

PVC SLEEVING PACK

Assorted diameters & colours of PVC sleeving. Diameters may range from 2mm up to 19mm.

These packs are super value.

Total Pack Qty: 10 lengths each approx 12" long

ORDER CODE: PACK/046

PRICE: £1-25

TV DROPPER PACK

This pack contains a random selection of very assorted values of TV Replacement Droppers.

Packs may include droppers for Philips, Thorn, Pye, Decca etc etc.

Total Pack Qty: 15pcs

ORDER CODE: PACK/047

PRICE: £6-50

MULTI-SECTION ELECTROLYTIC PACK

A super mixed pack of multisection electrolytics. Widely used in TV sets etc.

The original prices of some of these capacitors was over £5-00 each!!

These really are good value.

Total Pack Qty: 10pcs

ORDER CODE: PACK/048

PRICE: £5-50

0.25W RESISTOR PACK

Assorted values, some popular because we are overstocked, others simply values we don't stock. Either way, these really are a bargain.

A minimum of 10 different values.

All 0.25W carbon film, 5% tolerance.

Total Pack Qty: 1000pcs

ORDER CODE: PACK/049

PRICE: £1-99

GOODY PACK

This pack contains a random selection of very assorted components including:

Resistors, Capacitors, Connectors, IC's, Diodes, Potentiometers and much much more.

Many of the items are to a much higher spec. than those usually available to the hobby market. These packs really are a bargain. These packs are sold by weight.

Total Pack Weight: 1kg

ORDER CODE: PACK/050

PRICE: £2-50

MAGAZINE PACK

A random selection of Electronic Magazines! Some maybe old, some maybe new but whatever you get it will be interesting reading. Ideal for those winter nights!

Total Pack Qty: 10 Magazines

ORDER CODE: PACK/051

PRICE: £4-50

REMEMBER: UNLESS STATED OTHERWISE, ALL OF OUR PACKS CONTAIN NEW & UNUSED COMPONENTS!!

DON'T DELAY....ORDER YOUR MONEY SAVING PACK TODAY!!

12VOLT FLUORESCENT LIGHTS



A very attractive **twin** tube fluorescent light complete with two 12Volt 8Watt fluorescent standard type & size tubes.

White plastic case with clear plastic ribbed diffuser and ON/OFF switch.

The light is fitted with approx. 90cms. of twin flex for connection to 12V battery or other 12V power supply. Cable is colour coded for polarity identification.

These lights are ideal for Caravans, Boats, Vans, Camping etc etc.

Overall dimensions: 370 X 65 X 41mm

	1+	10+	50+	100+
ORDER CODE: OPTO/TFL12	£6-50	£5-75	£5-25	£4-95

SINGLE 12Volt Fluorescent Light

Identical to the above unit but SINGLE tube fitting.

ORDER CODE: OPTO/SFL12	£6-00	£5-25	£4-75	£4-50
------------------------	--------------	-------	-------	-------

SPARE TUBES



Standard 12V fluorescent tube suitable not only for our lights above but for most other makes. Tube length is approx: 300mm incl. pins.

Colour: White.

	1+	10+	50+	100+
ORDER CODE: OPTO/TUBE	£1-50	£1-25	£1-00	85p

SPARE TUBE - 'WARM' WHITE

Identical to the above tube but more suited for the caravan/camping application. This tube gives a 'warmer' light.

	1+	10+	50+	100+
ORDER CODE: TUBE/WW	£1-95	£1-75	£1-50	£1-25



PORTABLE 12V FLUORESCENT LIGHT - 12volt

Free-standing or hanging (Hanging hook supplied), with approx. 5 Metres lead terminating in standard car type cigar plug. Ideal for use in Car, Boat, Caravan, Van, Camping etc.

Sealed unit therefor completely weatherproof, they even float on water!!

The fluorescent light is 12Volt & 10Watts.

Overall dimensions: 430 X 30MM dia.

	1+	10+	50+	100+
ORDER CODE: OPTO/PEL12	£5-99	£5-50	£5-00	£4-75

WE ARE THE IMPORTERS OF THESE ITEMS. LARGER QTY. PRICES AVAIL.

ALL PRICES INCLUDE V.A.T.

21

ADD £3.00 P & P PER ORDER

HOBBY KITS

ELECTRIFYING APPARATUS

...generates a weak adjustable high tension of approx. 80-300V out of 3-6V(Max 9V). May be used by anglers to catch worms etc.

Max. current 50-250mA

KIT/B007

PRICE: £8-35

FOG HORN 5Watts

...generates a deep, noisy sound similar to the fog horns of ships! Operating voltage 4.5-12V, Max 5Watts depending on the voltage. Suitable for 8ohm speakers.

KIT/B015

PRICE: £5-99

TEST OSCILLATOR

This is a close range test only transmitter, which can be tuned between 88-108MHz and used to service radio receivers by using the unmodulated carrier. This kit must NOT be used to transmit over any distance!

KIT/B018

PRICE: £6-85

12V to 240VAC INVERTER

Transforms voltage from 12V car battery to 240VAC voltage approx. (adjustable) 50Hz. The required transformer & cooling unit are NOT included in this Kit. Precise information on standard transformers are given in the Kit assembly instructions. Max. 120Watts.

KIT/B038

PRICE: £9-25

LIGHT BARRIER 12V

A light barrier kit which uses an LDR (Light Dependant Resistor) to trigger the relay on. Can be used to switch on an alarm, open a door, or simply used as a security twilight switch. A light source is required which shines onto the LDR of the kit, if this light source/beam is broken the relay will pull on.

Max relay current is 5A. Requires 12V supply.

KIT/B045

PRICE: £9-75

THERMO SWITCH

Turns the relay on or off at a pre-fixed temperature. This instrument may be used as a thermostat, ice warning system, frost detector etc etc. Temperature range is approx: -30 to +150°C. Operating Voltage: 12V. Relay switching capacity: 5A.

KIT/B048

PRICE: £9-85

ULTRASONIC DOG WHISTLE

The ultrasonic dog whistle emits high powered sounds which although audible to dogs mostly undetectable to the human ear. The output frequency is through a special piezo loudspeaker and is adjustable between 8000 & 25,000Hz. Requires a PP3 9V battery.

KIT/B179

PRICE: £7-50

12V-24V SPEED CONTROL

Suitable for the operation of miniature DC drills. A rectifier is fitted in the circuit and only requires a transformer of 12-24V secondary depending on the required voltage. Suitable for use up to 3A current input.

KIT/B180

PRICE: £6-45

ION GENERATOR

Regenerates negatively loaded air particles (air-ions) & helps to produce a healthy climate which can reduce troubled sleep, aggressiveness, headache's etc.

Input: 6-18Vdc. Output 2-7Kv Current limit protection 200uA.

KIT/B137

PRICE: £9-95

CAR ANTENNA AMPLIFIER

This amplifier is connected between the antenna and the radio using co-ax cable, 60-75ohm. Gain Max. 22dB. Frequency range: 0.5-150MHz (Approx)

KIT/B068

PRICE: £5-99

SPY STETHOSCOPE

Using an earpiece the spy stethoscope allows you to listen through thin walls, doors, windows etc, due to a highly sensitive pre-amplifier & microphone. Suitable for monitoring animals etc!

KIT/B069

PRICE: £20-50

MW & SW DIODE RECEIVER

'Detector-receiver' for approx. 2-9MHz. This radio works on the same principle as the very first radio receivers! It does NOT require an operating voltage. Super educational kit for beginners.

KIT/B076

PRICE: £10-75

PARABOLIC MICROPHONE

Highly sensitive microphone. If mounted into a semi-circular reflector (half a plastic ball) noise & voices several hundred metres away may be heard & recorded! Ideal for animal observance, detectives etc.

Headphone connection: 8ohm. Requires 9V supply/battery.

KIT/B085

PRICE: £10-35

ROBOT VOICE

This kit modulates the human voice with an adjustable frequency to produce robot like sounds. This sound then requires amplification i.e. by an amplifier or tape recorder.

Requires 9-12V supply.

KIT/B107

PRICE: £9-60

DOG BARKING - ELECTRONIC

Generates a dog barking sound. Suitable for use with an 8ohm speaker. Operating voltage: 9-12V. The barking is stored on a special speech-synthesizer IC.

KIT/B155

PRICE: £19-50

MW TESTING TRANSMITTER

A close range test only oscillator which can be used as an unmodulated carrier to test radio receivers in the MW band. This kit must NOT be used to transmit over any distance!

KIT/B144

PRICE: £4-99

HI-FI AMPLIFIER 200W

KIT/B125

PRICE: £26-99

METRONOME

An electronic metronome which has an adjustable time signature between 30-300 beats per minute. The sound of each beat is clearly indicated by the loudspeaker.

Requires 4.5-6V supply.

KIT/B082

PRICE: £8-50

VHF RECEIVER

Frequency approx. 79-110MHz. Sensitive FET input circuit based on the shuttle principle. Operating voltage: 9V. At the output use either a high impedance ear-piece or an amplifier. Output approx. 10mV, 50K.

KIT/B100

PRICE: £10-95

MODULES

MOTORBIKE ALARM

This waterproof & shakeproof module will automatically switch on a horn or siren if the motorbike is moved. Can also be used to protect other items. Additional items required: power supply (Bikes battery), SPST switch, horn or siren. Max current: 1Amp.

KIT/M073

PRICE: £4-50

MICROWAVE LEAKAGE INDICATOR

This module is used as an microwave oven leakage tester, and will light up the LED if any radiation escapes through defective door hinges, rubber seals or shieldings.

Requires a 9V battery.

KIT/M058

PRICE: £6-00

VOLTAGE TRANSFORMER

Suitable for driving cassette decks, portable radio's etc. requiring 6V, 7.5V, or 9VDC from a 12V car battery or other 12V supply. Max load 800mA.

KIT/M015

PRICE: £5-65

INTERFERENCE FILTER-MAX 20Amp

High capacity mains filter has a ring core choke & must be connected within the mains supply that requires filtering.

KIT/M041

PRICE: £8-00

SPECIAL OFFERS

SELLOTAPE SALE

Standard Reels of Sellotape, made by 3M.

WIDTH: 3/4" Length: 66 Metres

Normal Price: 60p per reel!!!

ORDER CODE: SO/SELL


SALE PRICE: 50P 10 FOR £4-00

BT 4 way plug to 25 way 'D' Socket Lead
A short lead, BT 4 way plug to 25 way 'D' socket using BT flat style cable. 4 core, pins 2,3,5 & 7 connected on the 25 way 'D'.
Lead Length: Approx 175mm

ORDER CODE: SO/625

PRICE: 50p

MOULDED 13A PLUG & LEAD

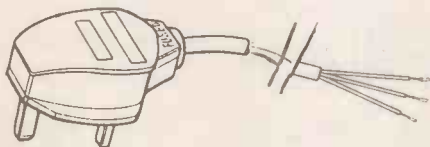


A non-rewireable standard VOLEX 13A plug fused with 3A fuse, moulded to a 2 Metre length of 3 core 0.5mm cable. The free cable end has stripped conductors ready for fitting to your equipment.

COLOUR: BLACK

ORDER CODE: SO/612	PRICE:	1+	10+
		£2-00	£1-75

BT Type Line Cord - BT Approved

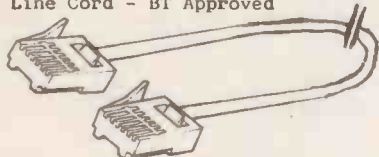


50P ANY QTY

Line Cord, Plug to Plug. BT standard cord set used when modifying existing equipment. Plugs each end are 4 way.

LENGTH: 3 Metres	1+	10+	100+
SO/613	PRICE: £1-25	£1-00	88p


IEC MAINS LEAD Belling Lee UK 6A 250V

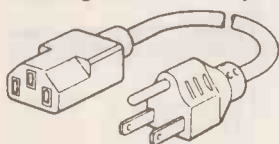

A non-rewireable IEC socket moulded to a 2M length of 3 core 0.75mm cable terminating with a USA plug. For UK use simply cut off USA plug and fit UK 13A plug.
Rating: 10A @ 115V. 6A @ 250V. Colour: GREY

ORDER CODE: SO/614	1+	10+	25+
PRICE:	£1-50	£1-25	£1-10

COMPUTER MODEM LEAD

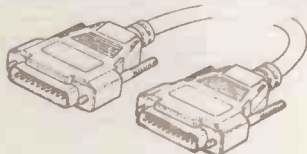

RS232 - RS232 25 way 'D' plug to 25 way 'D' plug. 9 pins connected.

Snap-fit covers allowing you to open and re-wire the pin configuration if required.

Length: 1.5 Metres (Approx)

ORDER CODE: SO/615

PRICE: £2-75

MOTOR RUN CAPACITORS - 440V 5% TOL.



Stud mounting capacitors suitable for motor start/run and other similar applications. Connections via double 6.35mm tabs. Manufactured to BS5267.

Current list price is over £6 each plus VAT!

15uF 440V DIMS: 115mm X 45mm Dia.

20uF 440V DIMS: 135mm X 45mm Dia.

15uF 440V ORDER CODE: SO/631 PRICE: £3-50 each

20uF 440V ORDER CODE: SO/632 PRICE: £4-00 each

IEC MAINS LEAD - Right Angle - Belling Lee 6A 250V



SO/618

A non-rewireable right angle socket moulded to approx. 2 metres of 3 core 0.75mm cable terminating in prepared ends ready for wiring to your equipment.

Length: 2 Metres PRICE: £1-00 each COLOUR: BLACK

AVO PANEL METERS Type T60/2481



Marked 50-0-50uA

Internal Resistance 400 ohm.

Dims: 70 X 60mm (Approx)

Zero adjustment on front of meter.

As you would expect from AVO, made to the highest quality. Limited qty. available.

ORDER CODE: SO/628 **£5-00** PRICE: ~~£6-50~~

COMPUTER CURLY LEAD

A 15 way 'D' plug fitted to approx. 1 metre of black 4 core curly lead with prepared ends on the other end.

Lead stretches to approx. 3-4 metres.

ORDER CODE: SO/620 PRICE: £1-00 each

CAPACITOR SALE

2200uF 35Volt Ideal for power supplies. Super quality, made by Matsushita (Panasonic) in Japan. Only available while stocks last. RADIAL LEAD

Dims: Length 30mm, Dia. 16mm. Lead length approx. 30mm.

ORDER CODE: SO/621	PRICE:	1+	10+	100+
		50p	45p	35p

L293B SGS Bridge Driver 16 pin DIL

Only a few hundred available at this once only price. 25 pcs to a tube.

ORDER CODE: SO/622	1+	25+	100+
	£1-50	£1-25	£1-00

MAINS SUPPRESSION CAPACITOR

ISKRA 0.1uF 250Vac X2

A radial lead boxed metallised polypropylene mains suppression capacitor. Approved to VDE-0565 Class 2. Epoxy resin encapsulated in flame retardant plastic case. Iskra Type: KNB1532

Dims: W 18mm. H 7mm. D 13mm Pitch: 15mm

Tolerance: ±20%

ORDER CODE: SO/627	1+	10+	100+
PRICE:	20p	18p	15p

SPECIAL OFFERS


PHOTO-TRANSISTOR Siemens Type: SFH309-5

Case: T1 (3mm)
Sensitivity: 1.0-2.0 @ 0.5mW/cm²
Half Angle: 32°
Peak Response: 900nm
Response: 10 tr(US)
Short lead is connector.
Lead pitch: 2.54
We have large qty's in stock.



	1+	10+	100+	1000+
ORDER CODE:	38p	35p	25p	20p
	SO/601			

SCHRACK RELAY TYPE: RP-03 10 12

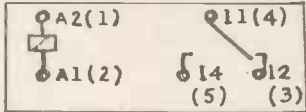

Internationally approved heavy duty PCB mounting relay in industry standard dimensions with 1 form C contact rated at 8Amps. Mounted on 0.1" grid.

Switching voltage: 380Vac max.
8A 250Vac Dims: 28 X 25 X 11mm

Nominal V DC: 12V 270 ohm

	1+	10+	100+	1000+
ORDER CODE:	38p	35p	25p	20p
	SO/602			
	£1-00	90p	65p	55p

(We still have approx 3,000 in stock!)

EPROM LABELS 16.5mm X 5.08mm OK INDUSTRIES TYPE CODE: 1/100A/10

A dual purpose label designed for use on Eproms or similar devices where the chip requires protection from the effects of light. These labels are also handy for marking devices or junction identification. Supplied on roll sheets which have pin-feed holes along the edge thus allowing them to be printed on a computer printer.

Total qty. per full rel: 3350 Labels (Approx)


	QTY	PRICE
ORDER CODE: SO/600	60 Labels	50p
	180 Labels	£1-40
(Full reel)	3350 Labels	£22-50

IEC LEAD - CURLY

6A 240Vac Right Angle IEC plug fitted to 3core 0.75mm black curly cable. Stretches to approx. 2.5metres.

	1+	10+
ORDER CODE: SO/604	£1-00	90p

TERMINAL BOX - 12Vdc

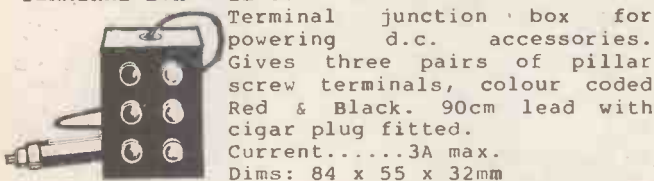

Terminal junction box for powering d.c. accessories. Gives three pairs of pillar screw terminals, colour coded Red & Black. 90cm lead with cigar plug fitted. Current: 3A max. Dims: 84 x 55 x 32mm

	1+	10+
ORDER CODE: SO/158	£1-50	£1-25

TOROIDAL TRANSFORMER Made in UK Manufacturer: St Ives Windings.

PRIMARY: 0-120V
0-120V

SECONDARIES: 9V at 4Amps
15-0-15v at 500mA

Dims: 75mm Dia 38mm Thick

Original Price in tens £24 each
ORDER CODE: SO/268 PRICE: £9-99



DIL SWITCH - 10 Way - Low Profile

Alco Type: ADF10
Very high quality. 0.1" pitch. Black with white switches. Length: 27mm. DIL package. 20 pin
At time of printing we have over 20,000 pcs in stock. 15pcs per tube.

	1+	15+	90+	900+
ORDER CODE: SO/608	50p	45p	39p	30p


HI RES MONITOR Made in UK GREEN SCREEN
Very high quality monitor, complete apart from the case.
Resolution at Centre is 900 lines therefore ideal for computer applications.
Simply input 12V @ 1.2A.

COMPOSITE VIDEO!

Supplied complete with full handbook and circuit diagram and full parts list. (Manual available seperately £2-00 each)
SPEC:

CRT Size	7" (178mm)
Power	12V/1.2A
Line Frequency	15-19KHz
Vertical Frequency	50-60Hz
Resolution at Centre	900 lines
Linearity	<2%
EHT Typical	12.0kV
Line Blanking	12-7.5uS
Vertical Blanking	750uS
Video Input unterminated	12K terminated
Video Response	22MHz
Video Rise/Fall	17ns
Video in for 35V output	1Vp-p

ORDER CODE: SO/MONITOR	PRICE: £19-99
	2 for £35-00

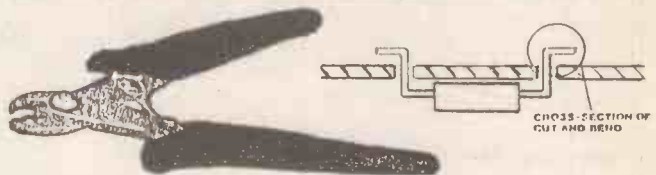

CUT AND BEND

Cuts & bends component leads in one action (see drawing). A quick & easy method of retaining mounted components. Ideal for development work. Components can be removed & reused after desoldering at a later time. Cutting capacity 1mm dia. copper wire. Special cushion grip handles. Very high quality, manufactured in Italy.

Length: 128mm Weight: 70gms
Normal Catalogue Price: £4-95

ORDER CODE: TOOL/SC/TP30	SALE PRICE: £2-99
--------------------------	-------------------




CUT and CLENCH

A stepped edge provides a cutting & clenching action which will cut & splay copper leads out to approx. twice the original diameter. (See drawing). Provides a permanent & secure method of retaining components, particularly useful in production. Cutting capacity 1mm dia. copper wire.

Length: 128mm Weight: 70gms

Special cushion grip handles. Made in Italy.
Normal catalogue Price: £4-99

ORDER CODE: TOOL/SC/TS30	SALE PRICE: £2-99
--------------------------	-------------------

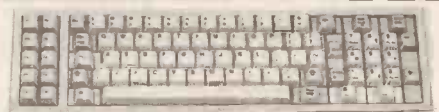

SIMILAR TO ABOVE KEYBOARD

KEYBOARD - Clare BRAND NEW
Uncased Brand new keyboards manufactured by Clare General Instrument Corp.
Alphanumeric - separate numeric keypad.
Overall dims: 480 X 160mm.

ORDER CODE: SO/472	SALE PRICE: £4-50 each
--------------------	------------------------

SPECIAL OFFERS

MICROPROCESSOR BOARD

A very high quality PCB manufactured by Ferranti still in its original packaging.

All Microprocessors are 'plug-in'.

2 X Z0803006PSC (40pin) 1 X Z0801604PSC (48pin)

1 X Z8001B1 CPU (48pin) 4 X 27256-20 (28pin)

1 X AM8152ADC (48pin) 1 X AM27128A (28pin)

1 X AM8052-5LC (68pin PLCC) Dated 1984

Over 40 assorted IC's soldered plus numerous resistors, caps., crystals etc etc.

BOARD DIMS: 220 X 225mm

ORDER CODE: SO/648

PRICE: £15-00

SILVERED MICA 0.01uF 500V 1%

Type: RDM30FD103-F03 CDE

Super quality, good high voltage at a low price.

DIMS: Height 20mm Width 20mm Depth 7mm

Lead Pitch: 10mm (Lead length: 35mm)

The current distributor price for a 350V version is over £1-85 each plus VAT!!!

Several thousand avail.

ORDER CODE: SO/649

1+

10+

100+

PRICE: 50p

45p

35p



ANGLE SCREWDRIVER

USAG 340 Each end has flat blade 13mm tip. Very high quality, marked Vanadium USAG Extra 2 X 13.

ORDER CODE: SO/650

PRICE: £1-00 each

POLYESTER 0.22uF 400V

ITT Made

Radial Lead. Lead Length: 15mm. Pitch: 22.5mm

Dims: H 19mm W25mm D 10mm

ORDER CODE: SO/651

1+

10+

100+

PRICE: 20p

18p

14p



COMMUNICATIONS INTERFACE PCB - Processor Board

Sorry, no further info. but board populated with several 6800, 6116, 2764, series chips (All plug-in).

Phono sockets, resistors, caps., etc etc.

Board Size: 465mm X 195mm

ORDER CODE: SO/652

PRICE: £5-00

MULLARD TRIMMER CAPACITOR

Mullard type: 808 series. 2-40pF 250V

Super quality at a very special price while stocks last!

Mullard Code: 808-11409. Value: 2-40pF 250Vdc

Distributor price is 24p ea + VAT on 100's!!!

ORDER CODE: SO/626

1+

10+

100+

PRICE: 25p

23p

20p



ORDER CODE

1+

10+

100+

SO/MAX

85p

75p

60p

SO/SKC

65p

55p

40p

TANT BEAD SUPER SALE

We have just purchased over 150,000 tantalum bead capacitors and can offer very attractive prices while stocks last.

VALUE/Voltage	1+	10+	100+	1000+
1.0uF/35V	10p	8p	5p	3p
2.2uF/16V	11p	9p	6p	4p
4.7uF/35V	16p	12p	9p	7p
10uF/16V	20p	15p	10p	8p
10uF/35V	24p	18p	13p	10p



Lead Spacing: 5mm Approx Lead length: 5mm

TELEFUNKEN - Selection guide Transistors & Diodes.

38 pages, packed with full specifications, drawings, pin-outs and cross-references.

Contents: BA204-2N4036

A super booklet full of useful data.

Dims: 270mm X 210mm

ORDER CODE: SO/654

PRICE: £1-00

BULGIN Panel Mounting AA Battery Holder


Takes 3 AA Batteries (Bulgin Type: B13/1)



Panel mounting battery holder. Flush fitting bayonet cap with coin slot for tightening. Mounting is from rear of panel, fixing by screws through front flange.

ORDER CODE: SO/635

PRICE: £1-00 each

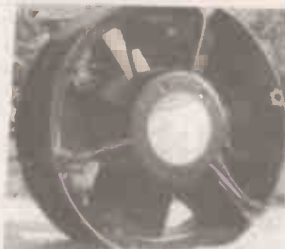

PAPT FAN - TYPE 6124 (172 X 55mm) 206cfm

Aluminium fan, impeller of fibreglass reinforced plastic. Electronically commutated dc motor. Counterclockwise rotation viewed from rotor, air output over struts!! OK? (Supplied with FREE guard) All brand new, still boxed, very high quality. List price is over £85-00 each!!!

ORDER CODE: SO/256A SALE PRICE: £10-00 each any qty.

EBM FAN - Type W2G075-AE21

80mm X 80mm (Depth 38mm)

Super quality, latest model. Run at 12Vdc. (Will run on voltage between 8v and 16vdc.)

2.6Watts, 3450u/min. Made in Germany.

All aluminium construction. Trade price over £30 each!

ORDER CODE: SO/257 SALE PRICE: £7-50 ea

AUDIO CASSETTES

Used once and bulk erased. ALL FULLY GUARANTEED Over the last 12 months we have sold over 55,000 of these tapes and demand is still growing.

At time of printing we have two makes available.

MAXELL UDI-90 & SKC GX90 Ferro Position


Both tapes are supplied complete with inlay cards.

Both tapes are 90 Minutes.

SPECIAL OFFERS

5 1/4" Computer Disks - 3M
 Type: 744 D-O SS DD
 Single sided double density soft sector.
 Limited qty, only a few hundred boxes. First come first served!
ORDER CODE: SO/636 **PRICE: £2-00 per box of 10**


MODEM LEAD

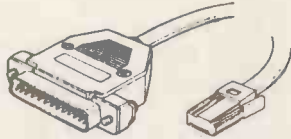

25-Way 'D' Plug connected to a BT 4 way plug.
 Length: Approx. 3 Metres.

ORDER CODE: SO/637 **PRICE: £3-50**

Adjustable Feet for Tube Fitting

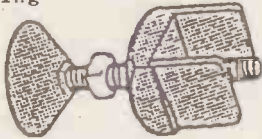

High quality feet for fitting to most makes of 25mm square tube. Each pack contains:
 4 X Threaded Feet. 4 X Metal Cap. 4 X Tightening Nut. Current Trade price is £4-70 plus VAT per pack! Remember, all our prices include VAT.

ORDER CODE: SO/638 **PRICE: £3-00 per pack**

CENTRONICS PLUG - MALE - 50 Way Amphenol Type: 226 B-50-U



50 Way plug (Without strain relief) Very high quality. Only a couple of hundred available.

	1+	10+
ORDER CODE: SO/639	£1-10	£1-00

0.1uF 63V 5% Metallised Polyester Capacitor

Very small capacitors, ideal where space is restricted. Overall width is only 7.5mm. Lead pitch is 5mm.

We have a substantial quantity of these capacitors so if you use large quantities contact us now.

ORDER CODE: SO/640	1+	10+	100+	1000+
PRICE:	5p	4p	3.5p	2.5p



FARNELL SWITCH MODE PSU - 240Watts G Series

Model: G12 20A

They seem unused but no promises. Copy of manual available with orders upon request. These units are in the current Farnell catalogue at over £395 each!

INPUT: 115-120/240Vac

OUTPUT: 8 to 12.6V (Adjustable) 20 Amps

Dims: 88 X 160 X 194

SALE PRICE: £150-00 each

Multi-channel Photodarlington Optocoupler Siemens Type: 1LD32 8 pin DIL




2 input opto-coupler with darlington output
 This device can be used to replace 4N32's or 4N33's in applications calling for several single-channel couplers on a board.

Continuous Forward Current.....	80mA
Peak Reverse Voltage.....	3V
Photodarlington Sensor (Load Circuit)	
Power Dissipation @ 25°C Ambient.....	150mW
Derate Linearly from 25°C.....	2.0mW/°C
Collector (Load) Current.....	125mA
Collector-Emitter Breakdown Voltage (BVceo)....	30V
Emitter-collector Breakdown Voltage (BVeco)....	5V

8 pin DIL package.

ORDER CODE: SO/643	1+	10+
PRICE: 45p	40p	40p

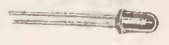INFRA-RED EMITTERS Type: OP161SLA T1 (3mm) Package.



Gallium arsenide infrared emitting diodes moulded in clear plastic, mini-axial package. The lensing effect of the package allows a radiation half angle of 8° measured from the optical axis to the half power point. Lead spacing is 0.100" (2.54mm) to allow mounting in standard sockets.

Continuous Forward Current.....	50mA
Peak Forward Current (pulse width=1usec 300pps).....	3.0A
Reverse Voltage.....	2.0V
Power Dissipation.....	100mW

At time of printing we have several thousand pcs of this item if you require large quantity's.

	1+	10+	100+
ORDER CODE: SO/644	45p	40p	25p

PAIR - INFRA-RED EMITTER & DETECTOR T1 (3mm) Package.



No info on these pairs but we are fairly sure that the emitters are OP161SLA as detailed above with matching detector. But no promises! Each pair is in a small holder.

ORDER CODE: SO/645 **PRICE: £1-00 per pair**


0.01uF 2000V Wima Type FKP-1 Tol: 5%



Width: 30mm Height: 20mm Depth: 11mm
 Lead Pitch: 27.5mm

ORDER CODE: SO/646 **PRICE: 50p each**

2200uF 63V Electrolytic PCB/Stud Fixing

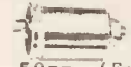

Dimensions: Dia. 35mm Height. 50mm (Excluding thread)

Supplied complete with fixing nut and washer.

ORDER CODE: SO/647	1+	10+
PRICE: 50p	45p	45p

2200uF 100V PCB Electrolytic

Miniaturized versions ensures a saving of space in compact power supply design. PCB snap-in terminals on a 10mm pitch for direct mounting into 2mm dia. holes. Super quality, super price!

ORDER CODE: SO/310

PRICE: £1-50 each



We may purchase your excess stock! Contact us now.

DESCRIPTION

QTY.

**UNIT
PRICE**

**TOTAL
PRICE**

SUB.TOTAL

SPECIAL OFFERS

— BUY A PAIR OF HAND HELD TRANCEIVERS FOR ONLY £27-50 —



2 Way Hand Held Crystal Control Transceivers. Built in telescopic aerial, call button, transmit/receive key, on air indicator. Simply require PP3 battery!!

Operating Frequency.....49MHz
 Transition Power.....100MHz
 RANGE: Up to one mile depending upon conditions.
 Oscillation.....Crystal control
 Power.....9V(PP3)

ORDER CODE: B123

PRICE: £27-50

OR PAY ONLY £17-50 WHEN SPENDING £30

OR MORE & USING THE ENCLOSED ORDER FORM

COMMODORE (CBM) Charger/Power Supply
 A good quality power supply offering the electronics hobbyist/enthusiast the opportunity to purchase a quality unit that is fairly simple to alter the specification of, at a very attractive price. Plenty of room in the case to add zener's, voltage regulators etc.

Input: 220V-240V (Switchable)

Output: 7.2Vdc @ 225mA
 7.0Vac @ 45mA

DIMS: 100 X 55 X 60mm


Mains Lead: Approx. 400mm

Output Lead: Approx 2.25 Metres. Fitted with a moulded plug (Non-standard)

Several thousand of these units at time of printing.

ORDER CODE: SO/659 1+ 10+ 100+

PRICE: £2-99 £2-50 £1-99

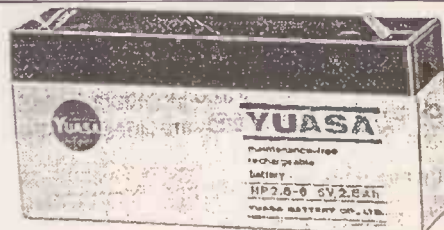

YUASA CODE: NP10-6

Dims: 101 X 151 X 50mm

Terminals: Spade Type,

Weight: 2.2Kg

6V 10Ah

We have a limited stock of Yuasa Sealed Lead Acid batteries which when checked at random found are not accepting a full charge. On the few that we have found to be like this we have found with patience, most eventually came up to full specification.

However, time is money as they say and so we are selling off these batteries at a very reduced price. We are selling these batteries with **NO WARRANTY WHATSOEVER** and therefore it is a case of taking a chance!

NO RETURNS WILL BE ACCEPTED!

The normal price of these batteries is approx. £16-95 each.

SO/656. 1+ 5+ 10+
 £5-00 £4-50 £3-50

SHARP RADIO CASSETTE - Model QT-F10E

A super radio cassette Recorder offered at a fraction of the normal price.

Although some are refurbished they are all guaranteed by us for 3 months from date of purchase. In the unlikely event of any problem we would repair or exchange at our discretion.


Features include:

- * Auto Stop
- * Battery Operated (5 X AA) NOT Included
- * Recording from Radio using Built-In Mic. is possible.
- * Recording external sound is of course possible
- * Earphone socket is fitted.
- * FM Range: 87.6MHz - 108MHz
- * AM Range: 526.5KHz - 1606.5KHz.
- * Some are complete with carrying case.

Limited quantity are available!

ORDER CODE: SO/658

PRICE: £12-50

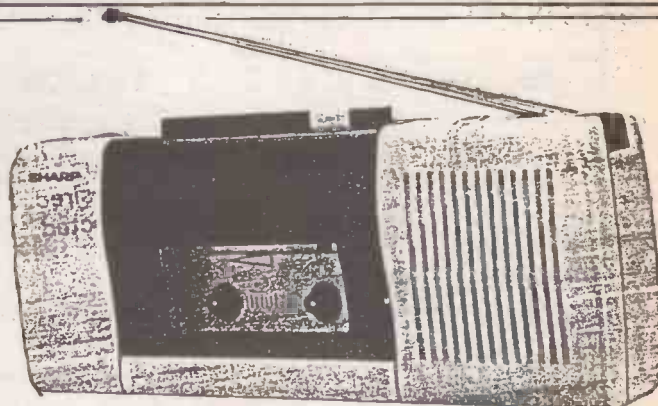

ALL PRICES INCLUDE V.A.T.

27

ADD £3.00 P & P PER ORDER

SURFACE MOUNT SPECIAL

We have just taken delivery of more than 1 million pcs. of Surface Mount Components! If you are a manufacturer using Surface Mount Technology, you will find our prices just incredible....but hurry! At these prices we expect to sell out fast. For the hobbyist who perhaps has not tried Surface Mount components now's your chance at a fraction of the normal cost.

TANTALUM Bead Capacitor (Branded AVX) QTY: 150K
 Value: 1.0uF 35V ORDER CODE: SO/670
 PRICE: £1-00 per 50 £1-75 per 100 £15-00 per K

TRANSISTOR BCW31 (SOT-23) Philips
 Bipolar, general purpose. NPN 32V 100mA 350mW
 Total quantity available: 85,000 pcs.
 ORDER CODE: SO/671
 PRICE: £2-00 per 50 £3-50/100 £30-00 per K

MURATA CAPACITORS 50Volt

Value	TOL	ORDER CODE	per 100	per 1000
27pF	5%	SO/672	£1-75	£12-50
100pF	20%	SO/673	£1-75	£12-50
270pF	10%	SO/674	£1-75	£12-50
390pF	5%	SO/675	£1-75	£12-50
470pF	10%	SO/676	£1-75	£12-50
47nF	10%	SO/677	£2-00	£15-00
220nF	20%	SO/678	£2-50	£20-00

RESISTORS 0.125W (1/8W) 1206 Case Generally 1% & 2%
 We have over 50,000 pcs of each value listed below.

100R, 180R, 220R, 820R, 1K8, 4K7, 10K, 22K, 33K, 39K, 47K, 68K, 100K, 130K, 200K, 220K, 680K, 1M0, 1M5, 10M0.

ORDER CODE: SO/679/Value Required
 PRICE: £1-00 per 100 £7-50 per 1000

LOW POWER ZENER 350mw PHILIPS
 Only two values available but at very reduced prices:


BZX84C-4V7 32,000 pcs. ORDER CODE: SO/680
 BZX84C-5V1 18,000 pcs ORDER CODE: SO/681
 PRICE: £2-00 per 50 £3-00 per 100 £20 per 1000

SURFACE MOUNT JUMBO PACK
 A random mixed pack including a selection of the above surface mount components. These packs are made up at random. NO CONTENTS LIST!!
 Total Pack Qty: 100pcs
 ORDER CODE: PACK/052 PRICE: £2-00

TELEX FOR SALE!! CHEETAH 87 BRITISH TELECOM
 We don't use our Telex machine now, its all done by Fax. However, we paid nearly £3,000 for ours a few years ago and we understand that some industries still prefer Telex for overseas communication. Perhaps your company is one of those?? Or maybe you have always wanted to own a telex!! Ours is being offered at a very very cheap price to clear. Remember, one only!!

ORDER CODE: SO/TELEX PRICE: £350-00
 (And we will throw in any spare paper rolls we may have!)

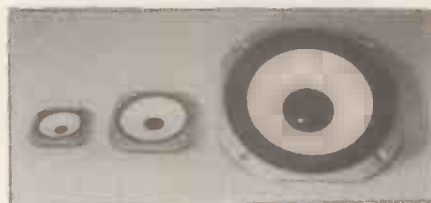VALVE SPECIAL - TY4-400 MULLARD BRAND!
 Only a few of these but yes, they are Genuine Mullard valves. A real bargain and of course, they are ALL BRAND NEW!!
 ORDER CODE: SO/682 PRICE: £175-00



A super set of 3 speakers which are all mounted in Aluminium Bezels for front loading.
 The set comprises of:

- 10" Woofer 8ohm 40Watts. Rubber Foam edge, White Paper Cone.
- 4 1/2" Mid-Range 8ohm. White Cone, enclosed back
- 3" Tweeter 8ohms. White Cone. Enclosed back.

ORDER CODE: SO/683 PRICE: £15-00 per set

MARCO TRADING

***** INCORPORATING *****

EAST CORNWALL COMPONENTS

THE MALTINGS, HIGH ST. WEM, SHREWSBURY, SY4 5EN

TEL: 0939 232763 TEL:0939 232689 FAX: 0939 233800

BRANCHES	
<p>SUPERTRONICS, 65 HURST STREET, BIRMINGHAM. B5 4TE</p> <p>TEL & FAX: 021 666 6504</p>	<p>WALTONS, 55A WORCESTER STREET, WOLVERHAMPTON. WV2 4LL</p> <p>TEL & FAX : 0902 22039</p>