

"ELSTREE SIX" WINS WORLD'S CHAMPIONSHIP

MODERN WIRELESS

1/6
MONTHLY



Vol. VI. No. 6.


Edited by
J. H. REYNER
B.Sc. (Hons.), A.M.I.E.E.

NOVEMBER, 1926.


P. T. V. Galn. Darbnica
kwa. raksta № 2/11
10.16.

The "DRAWING ROOM FIVE"

By
JOHN UNDERDOWN

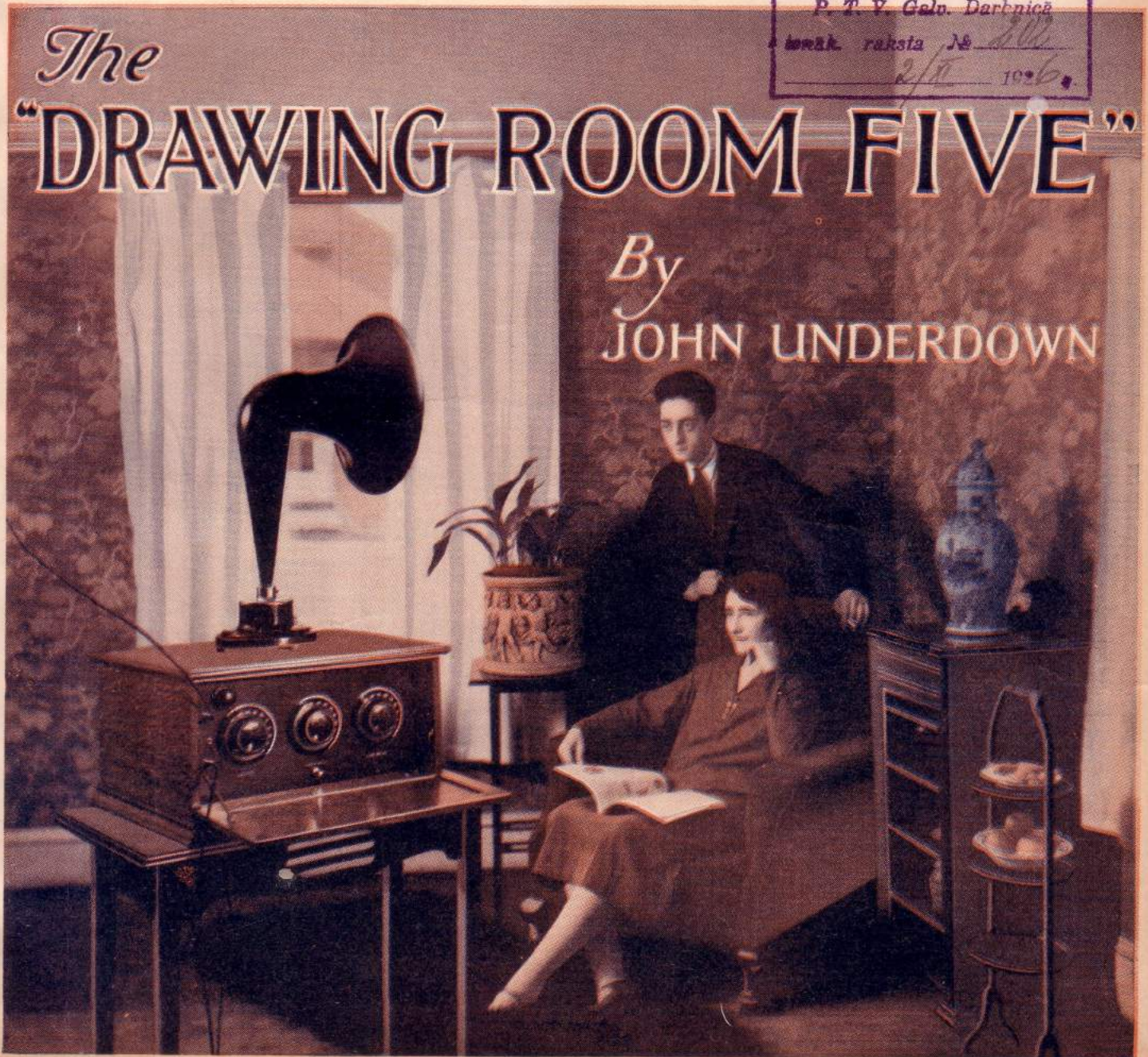

Below the Pyrometer scale

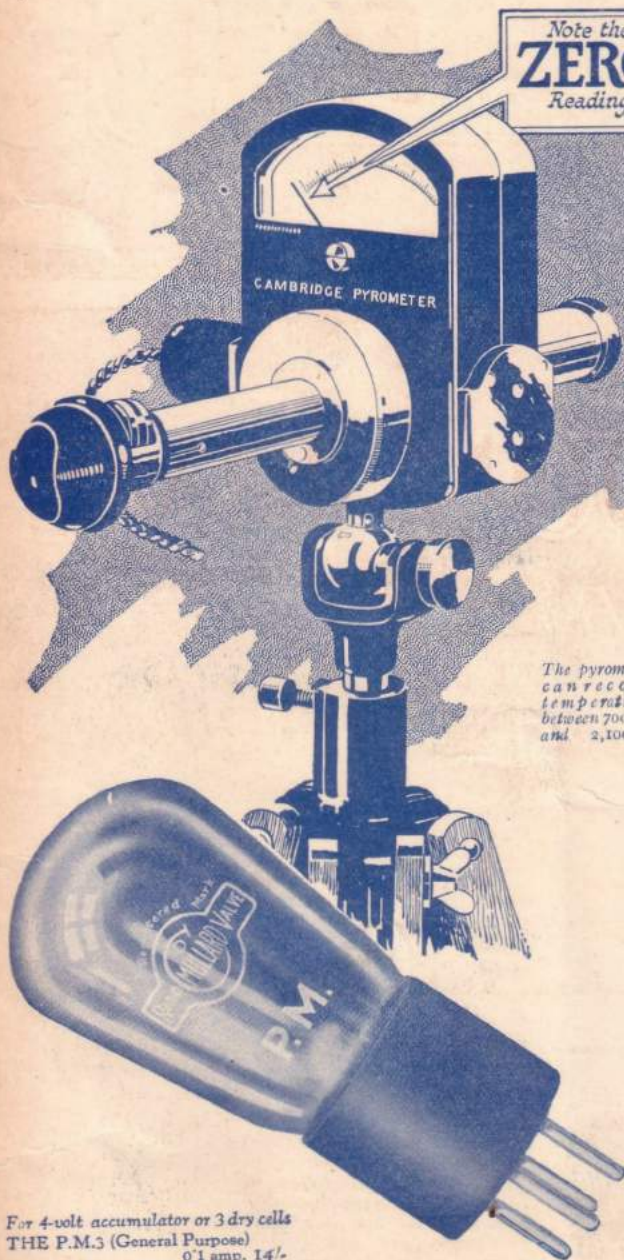

The pyrometer can record temperatures between 700°C. and 2,100°C.

THE LOW OPERATING TEMPERATURE OF THE WONDERFUL MULLARD P.M. FILAMENT.

The pyrometer can no longer claim to record the operating temperatures of all valve filaments

The wonderful P.M. Filament has a working temperature that is as low as 180 degrees below the pyrometer scale.

No sign of glow can be discerned from this unique filament with its striking economy of heat.

You will appreciate the greatly increased valve life that can be secured with this P.M. Filament.

Nothing is sacrificed.

With the P.M. Filament you receive up to 5½ times the emission of an ordinary filament.

The current consumption [only one-tenth ampere] makes your accumulator charges last seven times as long.

In addition, the P.M. Filament is so tough and well-supported that it cannot be broken except by the very roughest handling.

For continuous satisfaction give your receiver valves with the wonderful P.M. Filament and make your radio better, stronger and 85% more economical.

ASK YOUR RADIO DEALER FOR MULLARD P.M. VALVES.

- For 4-volt accumulator or 3 dry cells
 THE P.M.3 (General Purpose) 0'1 amp. 14/-
 THE P.M.4 (Power) 0'1 amp. 18/6
 For 6-volt accumulator or 4 dry cells
 THE P.M.5 (General Purpose) 0'1 amp. 18/6
 THE P.M.6 (Power) 0'1 amp. 18/6
 For 2-volt accumulator
 THE P.M.1 H.F. 0'1 amp. 14 -
 THE P.M.1 L.F. 0'1 amp. 14/-
 THE P.M.2 (Power) 0'15 amp. 18/6

These prices do not apply in Irish Free State.

**British
made in a
British
Factory**

Mullard

THE · MASTER · VALVE

Galvendrabnica

CONTENTS

VOL. VI.

MODERN WIRELESS

No. 6

	PAGE
The "Drawing-Room Five"	531
By JOHN UNDERDOWN.	
In Passing	536
Random Notes	538
By A. V. D. HORT, B.A.	
"Elstree Six" Wins World's Championship ...	540
More "Elstree Six" Appreciations	542
Some Further Notes on the "Solodyne" ...	545
A "Push-Pull" Three	549
By STANLEY G. RATEE, M.I.R.E.	
Head of Radio Press Retires	553
The "Elstree Six"	565
"Solodyne" Successes	569
Triumph for Elstree Design	570

	PAGE
Regular Programmes from Continental Broadcast Stations	573
Edited by Capt. L. F. PLUGGE, B.Sc., F.R.Ac.S., F.R.Met.S.	
Day and Night Effects	576
By G. P. KENDALL, B.Sc.	
The Loewe Valve	580
What Jack Shall I Need?	582
By A. V. D. HORT, B.A.	
Neatness and Efficiency	590
By H. BRAMFORD.	
For the Short-Wave Novice	597
By L. H. THOMAS (6QB).	
Points about Battery Eliminators	604
By J. H. REYNER, B.Sc. (Hons.), A.M.I.E.E.	
Tested by Ourselves	612

Edited by J. H. REYNER, B.Sc. (Hons.), A.M.I.E.E.

RADIO PRESS LTD., BUSH HOUSE, STRAND, LONDON, W.C.2.

Telephone: City 9911


Nothing contained herein is to be regarded as permission or encouragement to infringe any patent rights.

TABLE 1			TABLE 2			
Coil	Inductance in microhenries	Self-capacity in micro-microfarads	Coil	Parallel capacity in micro-microfarads	Wave-lengths in metres	Effective resistance in ohms.
35	61	15	35	300	264	2.8
40	90	15	40	"	318	2.9
50	150	9	50	"	406	3.3
60	200	13	60	"	472	4.4
75	295	12	75	"	573	5.3
100	540	11	100	"	774	6.6
150	1,110	12	150	"	1,250	15.8
200	2,220	17	200	"	1,580	19.7
250	3,070	17	250	"	1,860	24.9
300	4,800	14	300	"	2,320	28.2

Results of independent H.F. tests made by the N.P.L.

Here are the figures — judge for yourself!

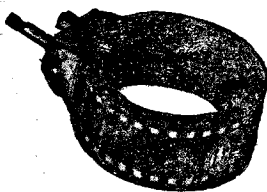The National Physical Laboratory figures fully bear out our claim that the LEWCOS Coil is the most efficient produced. In the design of radio inductances, the smaller the R/L value for any circuit, the greater is the selectivity and the signal strength. This fact has predominated over all other considerations in producing Lewcos Inductance Coils with the



result that we can publish without fear the R/L values for LEWCOS Inductance Coils as obtained from the N.P.L. measurements together with the wave length at which measurement was made. LEWCOS Coils make all the difference in reception. Ask your wireless dealer to demonstrate the Lewcos Coil on his set. Descriptive leaflet gladly sent on application.

LEWCOS Inductance COIL

The LONDON ELECTRIC WIRE COMPANY and SMITHS, LIMITED

Phone: Clerkenwell 1388

Playhouse Yard, Golden Lane, London, E.C.1

Telegrams: Electric, London

JUDD

CLEARTRON VALVES

1926-1927 NEW MODEL



YOUR SAFEGUARD

THE multiplicity of Radio Valves now upon the market is almost bewildering. This makes it the more incumbent upon careful users to pick and choose. The only American Designed Valve "Made in Britain's Newest Factory" is

14/- CLEARTRON 18/6

which embodies the latest research work in the art of Wireless on both Continents.
 The Highest Vacuum } in the HI-VAC Valve. The Sturdiest Construction } meaning
 known to Science and Strongest Filaments } LONG LIFE
 and that well-known

Majestic Volume and Operatic Purity
 above all

THE IRONCLAD GUARANTEE

(your safeguard).

The only Valve on the market which offers INSTANT REPLACEMENT WITHOUT COST OR QUESTION, if the user is not wholly satisfied!
 Would CLEARTRON dare to make this unique offer if CLEARTRON Valves did not perform 100%?
Send for our 1926/27 New Catalogue.

CLEARTRON RADIO LIMITED

1, CHARING CROSS, LONDON, S.W.1.


Works: BIRMINGHAM.

Telephone: Regent 2351-2.

Telegrams: "Cleartron, Westrand, London."

THE "DRAWING ROOM FIVE"

By JOHN UNDERDOWN

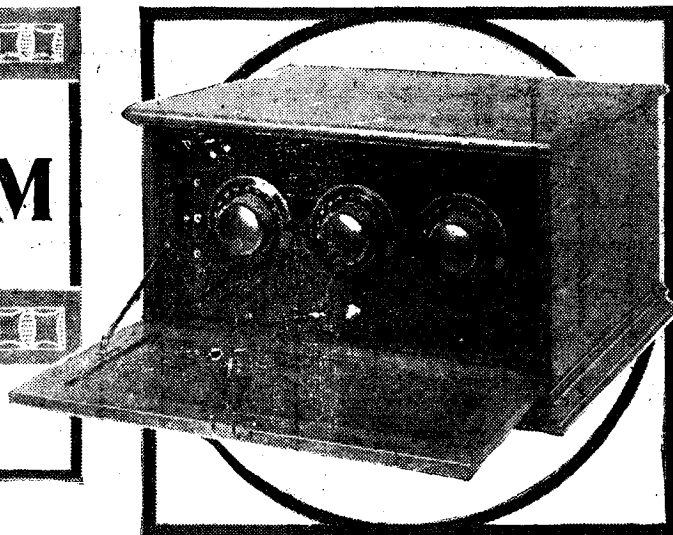

The set described in this article has been designed with the object of giving good all-round results. It will give excellent reproduction from the local station and very good loud-speaker signals on many British and Continental stations. A volume control is provided which enables very loud signals to be adjusted to the strength required.



THE excellent reproduction which may be obtained from a correctly operated detector and two or three valve resistance-coupled amplifier receiver is too well appreciated to need comment here, and a set, therefore, on these lines, but with a stage of high-frequency amplification, on modern lines, to give added range and selectivity, will make its appeal. The set about to be described utilises a simple and popular circuit, the tuning coils being screened in order to eliminate interaction between the high-frequency circuits and also direct pick-up

when the set is used near to a powerful broadcasting station.

Compact Layout

The combination of screened coils

which in turn makes wiring extremely simple. For use comparatively close to the local station in cases where it is impossible to erect a reasonable outdoor

Stations Heard on the Loud-Speaker.


Liege.	Nottingham.	Oslo.	Newcastle.
Kiel.	Madrid.	Bournemouth.	Birmingham.
Lyons.	Breslau.	Hamburg.	Frankfurt.
Toulouse.	San Sebastian.	Dublin.	Brussels.
Barcelona.	Manchester.	Glasgow.	Daventry.
			Radio-Paris.

on the high-frequency side and resistance coupling on the note magnifier side makes it possible to obtain a very compact lay-out,

aerial, a frame may be substituted in place of the aerial tuning coil, this arrangement introducing no tendency towards instability, since interaction between the frame and the high-frequency transformer is prevented by the latter being screened. The frame therefore can be orientated without readjustment of the neutralising condenser being necessary, as is sometimes the case where unscreened coils are used for the H.F. coupling.

Good Selectivity

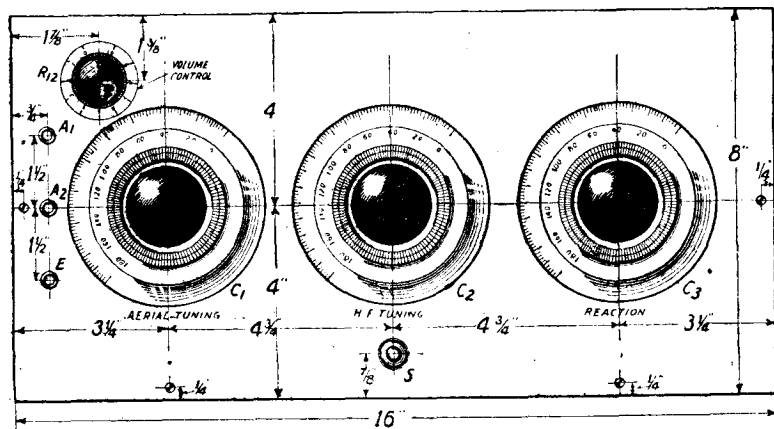Tested about twelve miles south-east of 2LO, that station gave excellent volume and quality when an ordinary frame with 2 ft. sides was employed, whilst on the outside aerial selectivity of a high order was obtained, it being possible to receive Manchester with London working, traces of the London transmission being heard only during the silent portion of the Manchester



The set may be used with a frame or outside aerial as desired. Blue-print No. 184a (free).

THE "DRAWING-ROOM FIVE"—
(Continued)

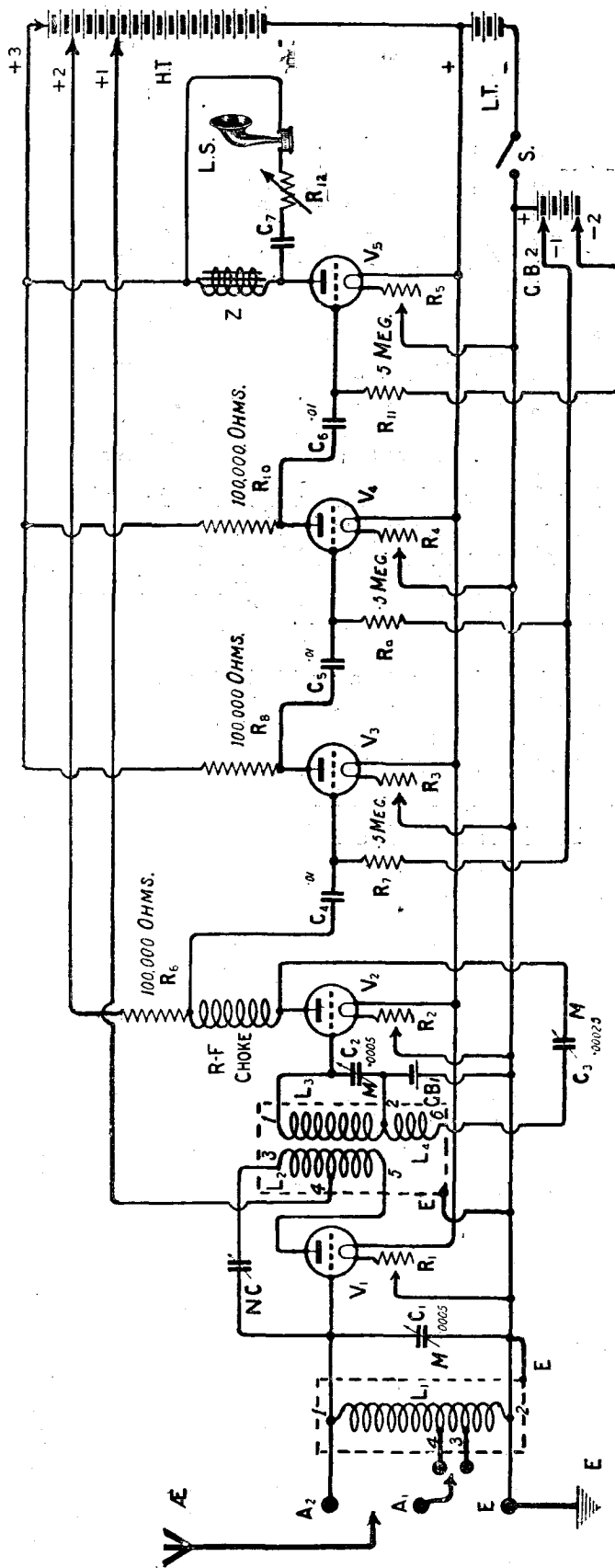


Fig. 1.—The theoretical circuit. Screened coils are employed to prevent direct pick-up and to enable a frame aerial to be used.

programme. Bournemouth was quite free of London and came in at satisfactory loud-speaker strength. In the course of an hour's test on a Sunday evening, between 7 and 8 o'clock, twenty Continental transmissions were tuned in upon the loud-speaker, ranging in strength from fair to really good. Of these transmissions, mostly unidentified, but of German, Spanish and French origin, eight were of adequate strength and sufficiently free from interference to be really worth listening to.


The Circuit

In character the circuit is straightforward and simple, the technical details being given in Fig. 1. When an outside aerial is used it is connected to the tuned grid coil L_1 by the usual auto-coupling arrangement, only one socket, A_1 , for this purpose appearing on the front panel and a flex lead being utilised which may be taken to either of two tapings on the coil. An extra terminal, A_2 , is incorporated so that a frame may be used, this latter being connected between the A_2 and E sockets. When this is done, of course, the aerial coil L_1 is not required. The high-frequency valve is coupled to the detector by means of a standard split-primary transformer, this providing a very simple neutralising arrangement. Reinartz type reaction is obtained by employing the standard transformer reaction winding. This necessitates that a radio-frequency choke coil be placed in the plate circuit of the detector valve, and here a plug-in coil is used, since the size may be changed when it is desired to go from the lower to the upper broadcast waveband. Incidentally, this choke serves a further useful purpose in keeping high-frequency currents to the H.F. and detector portion of the set, and the tendency of resistance-coupled note magnifiers to amplify high-frequency currents is thus counteracted.

Rectification

Rectification is effected by the lower anode-bend method, and to simplify matters the usual potentiometer is omitted, since by varying the detector H.T. voltage adequate control is obtained. In practice the detector grid bias

GIVES PURE REPRODUCTION

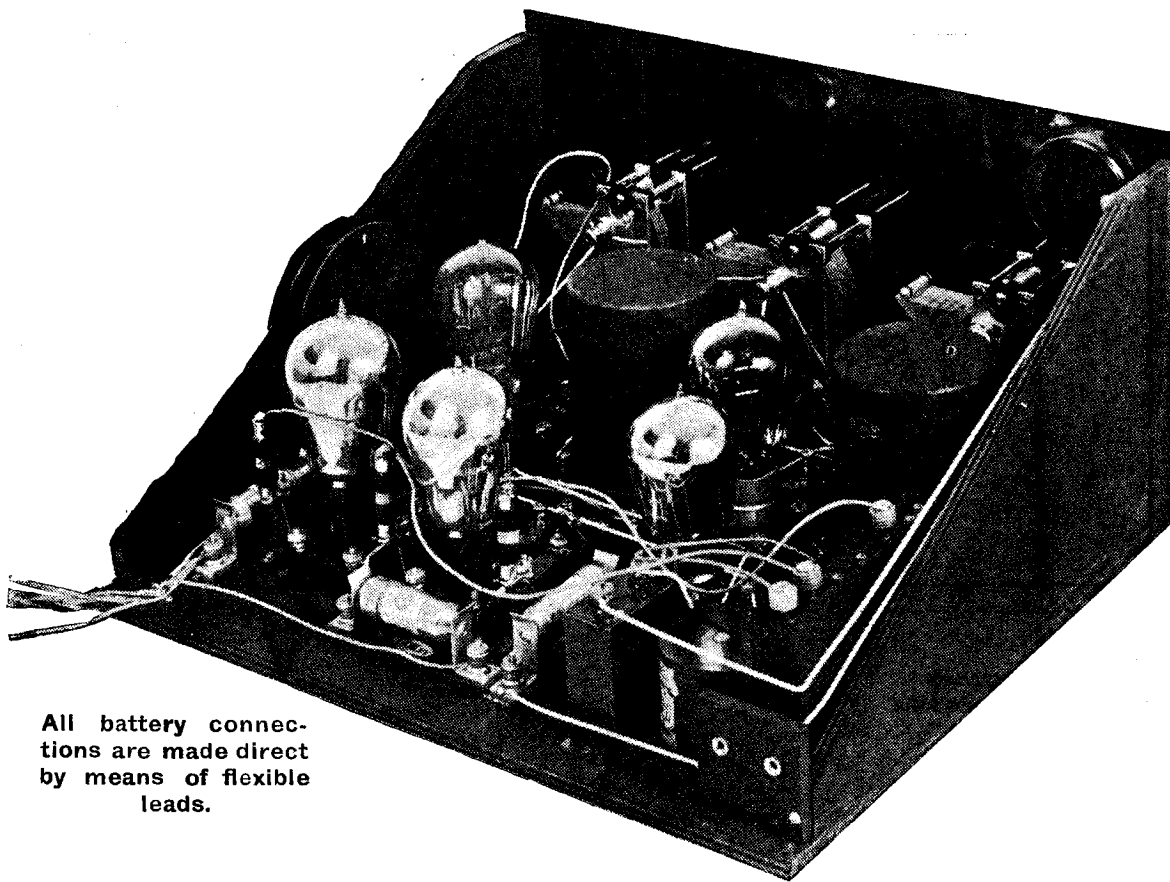

All battery connections are made direct by means of flexible leads.

battery, G.B.I., may generally be a single dry cell when resistance-coupling type valves are used for V_2 .

A Filter Circuit

The resistance coupling for the three note magnifiers follows standard lines, but in the plate circuit

of the last a filter circuit is incorporated in order that the loud-speaker may have to carry only the fluctuating currents representing signals, this being beneficial from the point of view of protecting the windings. The Duvolcon resistance R12 in series with the loud-speaker is for the purpose of volume control.

The Panel

The design of the receiver is such that only a small panel 16 in. by 8 in. is required, and on it are mounted the aerial tuning condenser to the left-hand side, that tuning the secondary of the high-frequency transformer in the centre and the reaction condenser

COMPONENTS REQUIRED

One Radion panel, 16 ins. by 8 ins. by 3/16th in. thick (American Hard Rubber Co. (Gt. Britain), Ltd.).

One cabinet to take above panel and baseboard, (Pickett's).

Five Clearer-tone valve holders (Benjamin Electric, Ltd.).

Five baseboard mounting rheostats (Lissen, Ltd.). (These should be chosen to suit the valves to be used.)

Three 100,000 ohms anode resistances and bases (Varley Magnet Co.).

Two .0005 S.L.F. condensers (Jackson Brothers).

One .00025 S.L.F. condenser (Jackson Brothers).

One neutralising condenser (A. F. Bulgin and Co.).

One single-coil holder (A. F. Bulgin and Co.).

Three .01 T.C.C. fixed condensers (Telegraph Condenser Co., Ltd.).

One 2 mfd. Mansbridge type condenser (Telegraph Condenser Co., Ltd.).

One standard audio-choke (Beard and Fitch, Ltd.).

One filament "on and off" switch (Igranic Electric Co., Ltd.).

Three ½ megohm grid leaks (Igranic Electric Co., Ltd.).

One aerial coil and one split-primary H.F. transformer and screening cases (Bowyer-Lowe, Burne-Jones, Collins n. Efesca, Lewcos or Peto-Scott).

One Duvolcon (Dubilier Condenser Co. (1925), Ltd.).

One ebonite sub-panel, about 2 ins. square and ¼ or 3/16th in. thick.


Five Eelex sockets (J. J. Eastick and Sons).

Thirteen Eelex or Clix plugs.

A quantity of Glazite wire, rubber-covered flex, heavy twin flex, screws, etc.

Radio Press Panel Transfers.

THE "DRAWING ROOM FIVE"—(Continued)

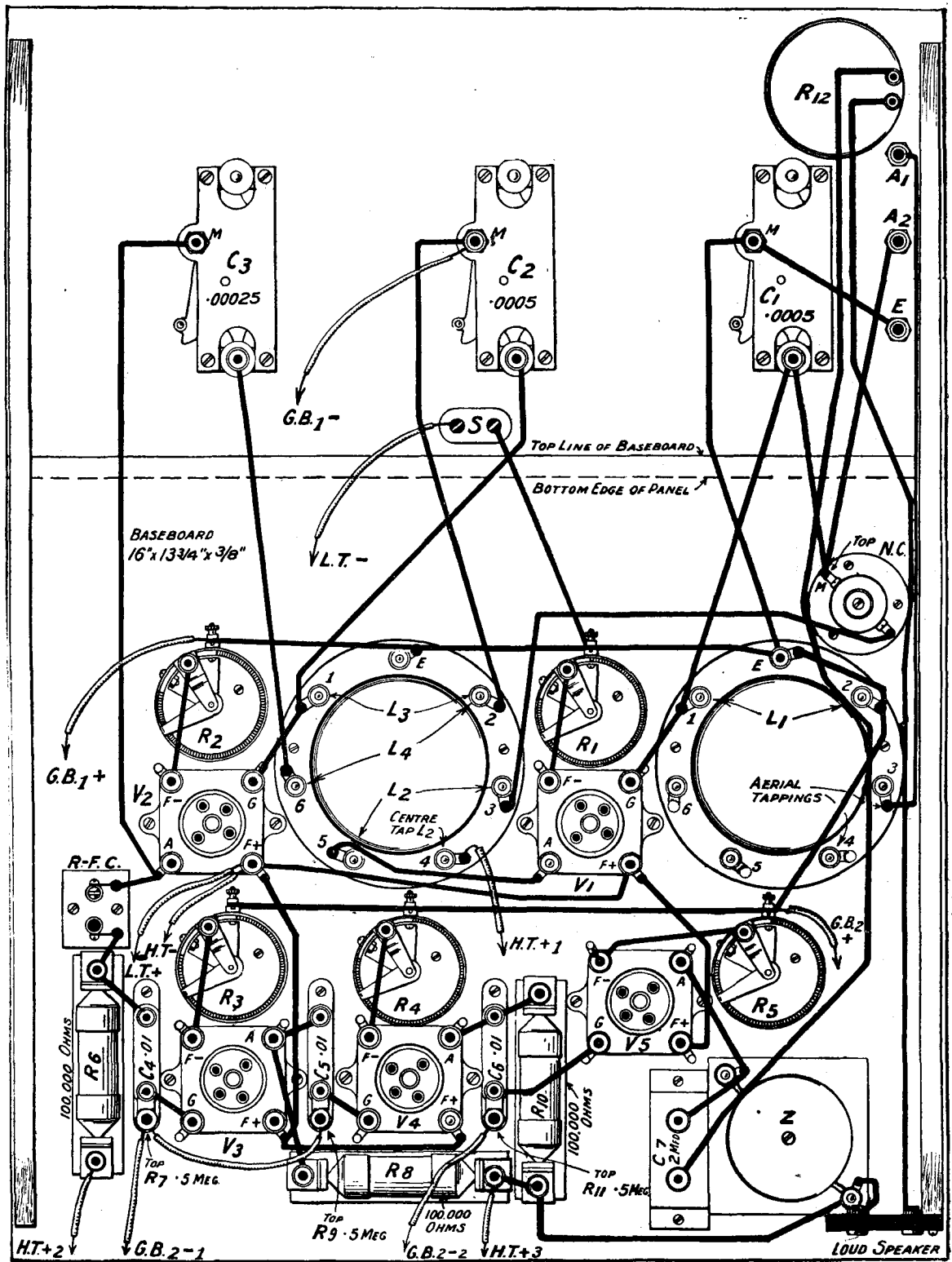

The wiring diagram. Note that no battery terminals are used, direct flexible connections being employed instead. Blue print No. 184b (free).

IDEAL FOR THE HOME

to the right-hand side. Incidentally this latter control may be used with impunity when the high-frequency valve is properly neutralised, since the circuit is then of non-radiating type. The three Elex sockets on the left-hand side are, reading from top to bottom, that for the outside aerial, the second for one side of a frame, if used, and the other for the earth lead, or alternatively the other side of the frame.

Simplifying Wiring


To make the wiring easy, where leads are very short, I have used bare 20-gauge tin copper wire, since it would be difficult to wire here with stouter wire, which latter is therefore used for the longer leads where rigidity is required. For the L.T. battery leads twin red and black covered flex has been used, whilst for the H.T. battery connections rubber-covered flex is employed.

Battery Leads

The usual terminal strip for H.T. and L.T. connections has been omitted, for the sake of simplicity, and leads are taken directly to the batteries concerned, only one small hole in the right-hand back corner of the cabinet being required for

this purpose. For the loud-speaker connections, two sockets, on a small ebonite sub-panel, are re-

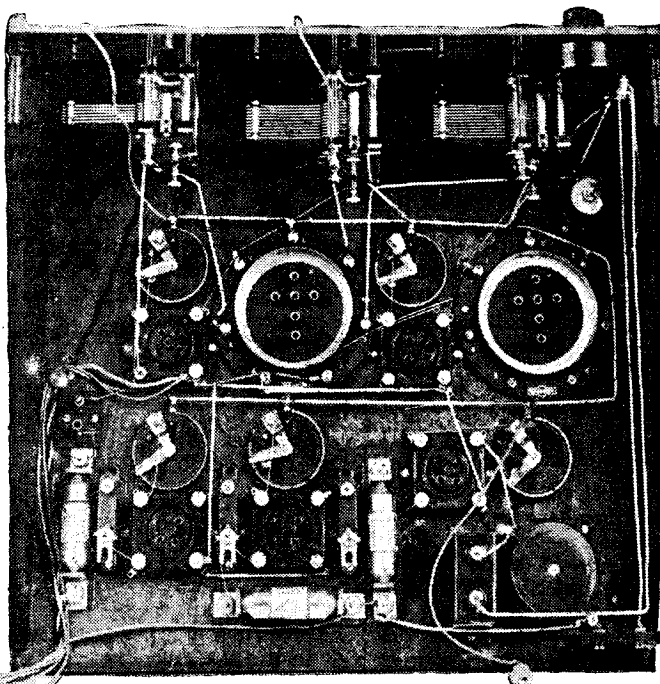quired and two small holes in the left-hand back corner of the cabinet
(Concluded on page 621.)



A plan view of the receiver showing the method of laying out the components on the baseboard.

WIRING INSTRUCTIONS

Join E to moving plates of C1; moving plates of C1 to E of screen base for L1; E of screen base for L1 to one side of S, and one side of R1; same side of R1 to E of remaining screen base; E of same screen base to one side of R2; attach flex lead to same side of R2 for GB1+. Also join E of screen base for L1 to terminal 2 of L1; terminal 2 of L1 to one side of R5; same side of R5 has flex lead joined to it for GB2+, and is connected to one side of R4; same side of R4 to one side of R3.

Join fixed plates of NC to terminal 3 of L2.

Join A2 to moving plates of NC; moving plates of NC to fixed plates of C1; fixed plates of C1 to terminal 1 of L1; terminal 1 of L1 to G of V1.

Join A1 to aerial tapping 3, with flex wire.

Join flex lead to remaining side of S for LT-.

Join F+ of V5 to F+ of V1, F+ of V1, to F- of V2; F+ of V2 has two flex leads joined to it for HT- and LT+ and is connected to F+ of V3; F+ of V3 to F+ of V4.

Join F- of V1 to remaining side of R1.

Join F- of V2 to remaining side of R2.

Join F- of V3 to remaining side of R3.

Join F- of V4 to remaining side of R4.

Join F- of V5 to remaining side of R5.

Join flex lead to terminal 4 of L2 for HT+ 1.

Join A of V1 to terminal 5 of L2.

Join fixed plates of C2 to terminal 1 of L3; terminal 1 of L3 to G of V2.

Join terminal 2 of L3 to moving plates of C2; join flex lead to moving plates of C2 for GB1-.

Join fixed plates of C3 to terminal 6 of L4.

Join moving plates of C3 to A of V2; A of V2 to pin of holder for R - F.C.

Join socket of holder for R - F.C. to one side of R6; same side of R6 to one side of C4.

Join other side of C4 to G of V3 and one side of R7.

Join A of V3 to one side of C5 and one side of R8.

Join G of V4 to remaining side of C5; same side of C5 to one side of R9.

Join other side of R9 to remaining side of R7 with flex lead, and join flex lead to same side of R7 for GB2 - 1.

Join A of V4 to one side of C6; same side of C6 to one side of R10.

Join G of V5 to remaining side of C6; same side of C6 to one side of R11.

Join flex lead to other side of R11 for GB2 - 2.


Join A of V5 to one side of Z and one side of C7.

Join one loud-speaker terminal to remaining side of Z; same side of Z to remaining side of R10; same side of R10 to remaining side of R8; join flex lead to same side of R8 for HT+3.

Join flex lead to remaining side of R6 for HT+2.

Join remaining loud speaker terminal to one side of R12.

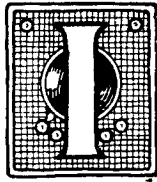Join other side of R12 to remaining side of C7.




I HAVE long been a most profound admirer of the fellows who write the gossip pages in the illustrated daily papers. Must it not be delightful to spend one's whole time calling upon Lady This or the Duke of That, to pass the time of day with the leading figures of Society whenever one meets them, to be on back-slapping terms with all the celebrities of the stage, the police court, the betting ring and the treasure-hunting field? But above all things what I most admire is the infinite capacity of these writers for consuming luncheon and their wonderful power of being in at least four places at one and the same time in case of need. I always study their writings closely, to my own great profit. The first paragraph almost invariably begins "Lunching yesterday at the Ritz. . . ." A little lower down the column you find, "Whilst enjoying a light luncheon at the Carlton . . ." Two or three paragraphs with no reference to food follow, then we find "There was quite a crowd yesterday at the Savoy

tingham in the morning, lunched at four different London restaurants, spent the afternoon at Newmarket, had tea in Hampstead, Mayfair and Richmond, dined sirp'y all over the p'ace, attended the Tattoo at Aldershot in the evening and tripped off a good day's work by supping in most parts of the West End, after dropping in for a foxtrot or two at half-a-dozen different night clubs.

Those Seats of Learning

I love, too, the pleasant friendly way in which they write of those who sit in the seats of the mighty, all of whom they have known since boyhood days. "Strolling down Piccadilly yesterday," you read, "I ran into Lord 'Wuffles' Bilger, who was bemoaning the fact that his valet would not allow him to wear pea-green socks and a scarlet tie. Wuffy, as we used to call him at Cambridge, always had an eye for colour. . . . As I turned into Bond Street I met Captain Bingo Punter, who told me something of his latest venture. I remember when we were at Oxford together how he always said that one day. . . . Continuing my stroll down Regent Street I found myself face

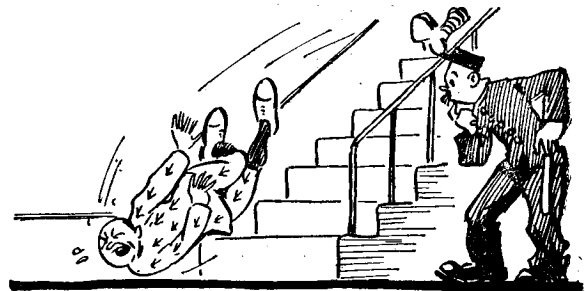Angostura Bitters tripped over her umbrella and fell literally into my arms. 'The catch of the season,' she cried gaily, as I picked myself up from the gutter. . . . Only those who were at Harrow with him realise what a wit Lord Tufto Bandyshanks is. I shall never



—he kicked me downstairs.

forget his retort to the headmaster when he was about to be publicly birched before the whole school for some minor demeanour. 'This will teach you to mend your ways!' thundered the headmaster, brandishing his horrid weapon. 'Please, sir, it wasn't me,' said young Bandyshanks without hesitating for a moment. . . . Turning into the Haymarket, I observed Colonel Gore - Blusterby chatting with Prince Potzanparski. When I was at Eton with the Prince and at Rugby with the Colonel. . . ."

What About Us?

This is all very well, but what I want to know is where do we poor wireless folk come in? Why should we not run up against or run into or run over or even run down? Day after day I have searched the gossip columns for a little paragraph such as "Dropping into Lockhart's yesterday I found the Listener-in lunching off sausages and mashed. I have always thought that he was quite one of the best-looking men about Town, and he is of course renowned for his excellent taste in clothes. As I passed over to chat with him I noticed that he was striking a note of chaste originality by sporting



"The catch of the season," she cried gaily.

when I dropped in for lunch. . . ." Another most interesting pursuit is to compute the miles covered in a day by the writer.

A Busy Day

The record is, I believe, held by one fellow who last summer attended the Test Match at Not-

to face with Sir Ian McKelpie, who had amassed a fortune by selling breeks to Hielanders. In those far-away University days at St. Andrew's we always prophesied that 'Potty,' as we called him affectionately, would go far. . . . I was just stepping into a taxi in Piccadilly Circus when Lady

IN PASSING — (Concluded)

patent leather boots, spats, jazz stockings, plus-fours and a frock coat. The Old Borstalian's tie in a made-up bow round a celluloid collar added just that little touch of colour that all really well-turned-out men value so greatly. When we were at Dartmoor together I was the Listener's fag, and I shall

a few steps down the street when I observed Senatore Mark O'Nee about to enter a taxi. Sweeping off my hat and brushing aside the attendant commissionaire I hastened to open the door for him. Feeling in his waistcoat pocket, he produced a small something which he placed into my palm. It was a



"Ecco!" I cried, bursting into Italian.

never forget the kind and fatherly manner in which he kicked me downstairs whenever his eggs were not boiled to his liking." That, I think, would be the stuff to give them. If, instead of references to politicians, artists and other queer creatures who do not matter two hoots, we had jolly little paragraphs about wireless people, I am sure that the circulation of the morning papers would rapidly double itself. As I am always ready to step into any breach I will now proceed to a few model paragraphs, giving intimate information about some of the greatest of the great for your edification and for the instruction of those who fill the gossip pages.

A Safety Valve

I was just being flung out of the Air Force Club, into which I had strayed by mistake, one day last week when I collided with Captain Pullhard, who was coming in. As we sat together upon the steps, he recovering the wind which I had knocked out of him and I setting my somewhat dishevelled raiment in order, I ventured to ask him the time. "Two o'clock," he said. "A.m.?" I queried. "No, p.m.," he thundered with majestic volume. A spiritualist once told me that Captain Pullhard had a remarkably fine aura.

A Treasured Tip

I had hardly taken more than

uttered when I held open the door of his taxi was no exception to the rule. "Paddington," he said, sinking into his corner.

High-Frequency Choking

Toddlng into the Ritz to see if there was anybody there who might stand my lunch I came across the genial Captain Chuckersley in the act of engulfing oysters. "Ecco!" I cried, bursting into Italian and slapping him upon the back. " *! ? *** — % % % \$ £ C @ ! ! !," he screamed as soon as he was able to speak after dealing with an oyster that had taken the wrong turning; "Please don't do it."

No Luck

Entering Bush House, I sauntered jauntily into the Editorial sanctum and was promptly pushed out.

An Old Friend

Crossing the Strand I made my way into Simpson's, where the very first person that I saw was my old friend Professor Goop. Just as I arrived at his table he was raising

his voice to anathematisise the waiter. "No less than an hour ago," he shouted, "I ordered a chop lightly done. Will you tell me why on earth you have not yet brought it—or have I eaten it?" The waiter having assured him that he had duly put away his chop, Professor Goop was about to rise from his table when I pointed out that I should be delighted to lunch with him. "In that case, my dear fellow," he said, with a beaming smile, "we will begin all over again—waiter, two chops—and now let me show you my new circuit. This roll represents a centre-tapped inductance, whilst here (he picked up a fork) we have a neutralising condenser. This spoon is a 100,000-ohm resistance and the ash tray is a choke with a value of one millihenry. We will use glasses to represent the valves." He took his own and mine, but as he was still two short he went across to a table on his left and borrowed two foaming beakers. The owners of these were still arguing the point when the Professor, who was apparently entirely deaf to their entreaties, discovered that he had nothing to represent the high-tension battery.



He borrowed two foaming beakers.


A Sad Shock

He was just sallying forth in search of this when the manager arrived, supported by two stout fellows, and before you could say Llanfair . . . gogogoch, the Professor and I found ourselves outside on the pavement. I did not mind this so much, but the most unkind of all was that the Professor complained that the rough treatment he had received had entirely taken away his appetite, the result being that I had to go and buy my own lunch.



RANDOM NOTES

By A. V. D. HORT, B.A.

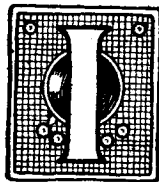

SEE that a suggestion was made recently by a French scientist that the services of wireless might be utilised to regulate the clocks in observatories in all parts of the world. With modern appliances an accuracy of one-thousandth part

of a second can be assured in the checking of time. The idea of thus synchronising the clocks of the world is certainly intriguing, but it must be remembered that such a system would presumably be finally dependent on some one master clock, with which the others would be synchronised. One foresees that complications might arise if the master clock failed in its duties!


IT appears that the B.B.C. are contemplating ambitious educational schemes. Mr. J. C. Stobart, speaking at a conference in Cambridge of the British Institute of Adult Education, outlined as a possibility of the future a regular series of half-hour broadcast educational talks; these would presumably be followed at intervals by examinations in the subjects discussed. This would enable the listener to acquire learning without leaving his own fireside.

Such a scheme would be dependent on the provision of definitely alternative programmes, so that listeners would not feel that they were being "forcibly fed" with educational talks.

BESIDES the National concerts which are being organised by the B.B.C., a series of International concerts is to be given on the first Tuesday of each month. The music of the

following countries will be heard during the coming winter season :—November, Italy ; December, Germany ; January, France ; February, Czecho-Slovakia ; March, Holland.

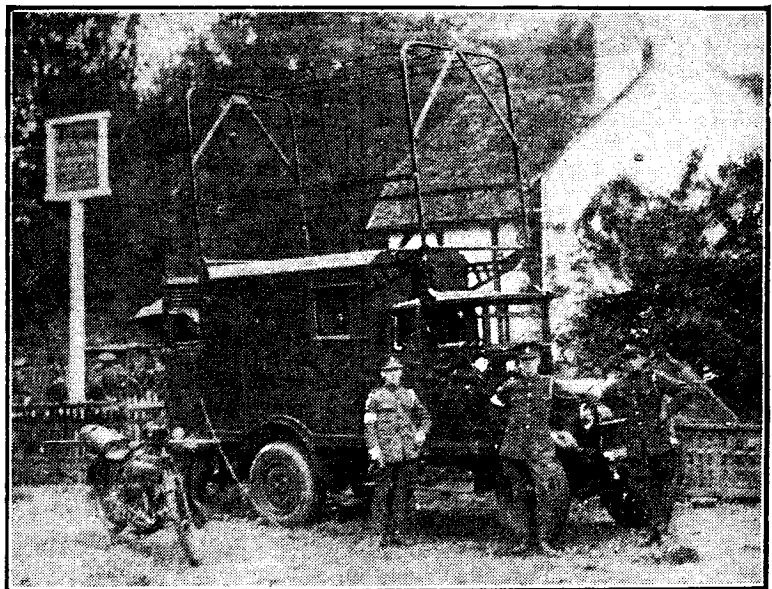DURING the past few years little radical alteration has been made in the electrode design of three-electrode receiving valves. Of different shapes, sizes and materials, there is a



A wireless equipment van of the type used during the recent Army exercises in Hampshire.

great variety, but the generally "accepted" relative disposition of electrodes has remained unchanged. Designers are, on the other hand, constantly endeavouring to modify and improve on the construction of the filament, and one design which has recently been patented aims at doing away altogether with the conventional filament-heating system.

RANDOM NOTES — (Concluded)

In this new valve the arrangement of the electrodes, too, is altered, the filament being outside the grid and anode. The "filament" cannot strictly bear that name at all, since it consists of a cylinder coated to improve emission of electrons. This cylinder is heated by means of an electric heater, which presumably may be supplied with current from the mains or some similar source. Something of this nature has been attempted previously in valve design, and it remains to be seen whether this new patent will prove to be a sound proposition.



IT is curious what a number of people there are who appear to imagine that it is unnecessary to take out a wireless licence until the set is in working order. There have been several cases in the courts lately when the plea was put forward that the set did not work, so that no licence was taken out. The regulations state, of course, that a licence must be taken out before the apparatus is installed.



A POINT which was noticeable at the National Radio Exhibition this year was that there appeared to be much more "courage" displayed in the design of receivers than hitherto. I mean by this that there seems to be a movement towards making the wireless receiver a piece of furniture, designed on sufficiently attractive lines to allow it to take its place naturally in a room. There will probably always be a certain number of people who like to hide the receiver in some way, often by dressing it up as though it were something else. On the other hand, now that the receiver is becoming, or rather already is, accepted as a necessity and is no longer regarded as a toy, it is only to be expected that the majority of listeners should wish for an instrument which will be no more conspicuous among the furniture than a piano or a gramophone.

Some very attractive cabinet work was to be seen at the Exhibition, the increasing use of wooden panels and "fall-fronted" cabinets helping to make the receiver blend with other furniture in a manner which is hardly possible when ordinary black ebonite is there to catch the eye.




IT is becoming the accepted practice in many modern receivers to use one rheostat, or better


still, one fixed resistor, to regulate the filament current of more than one valve in a multi-valve set. In a set using two stages of high-frequency amplification, for example, if similar valves are used for both stages, one resistance may quite well be used to control the two. This leads to a slight difficulty when it comes to neutralising the high-frequency stages, assuming as a matter of course in these days that they *are* neutralised. Each stage has to be dealt with separately, and in the older style of receiver each valve would be turned out separately on its own rheostat. It is possible to remove the valve and wrap a piece of thin paper round one of the filament legs in order to prevent it lighting. This, however, is not always easy to do, and if a burnt-out valve of similar type to that in use is available this may be used to get a rough adjustment of the neutralising condenser.

The procedure is to insert the "dud" valve

in the holder and set the neutralising condenser in the ordinary way, after which the proper valve is replaced and any small extra adjustment is made. Slight differences in the spacing of the electrodes of the two valves will probably prevent the setting obtained in the first instance from being absolutely correct, but an approximate setting may readily be found in this manner. The final adjustment can then be made by rotating the tuning controls in step and noting whether oscillation occurs at any point.

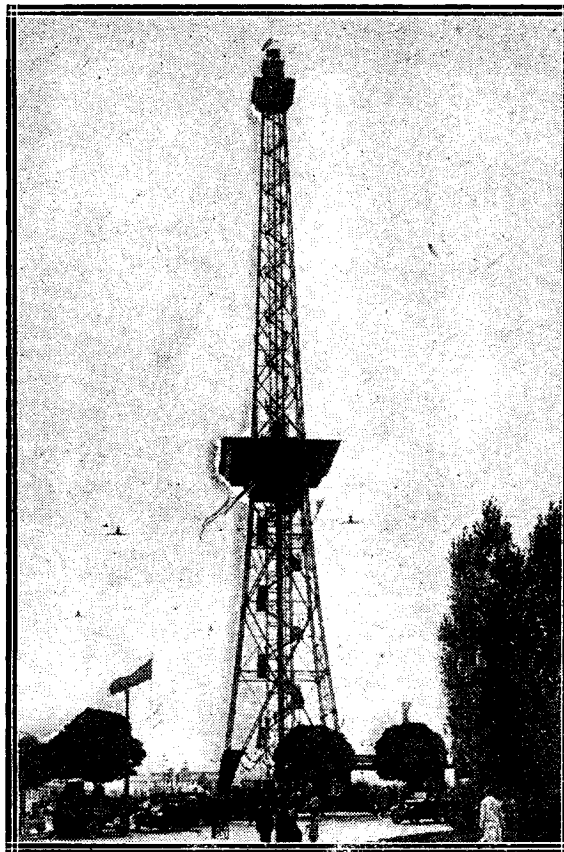

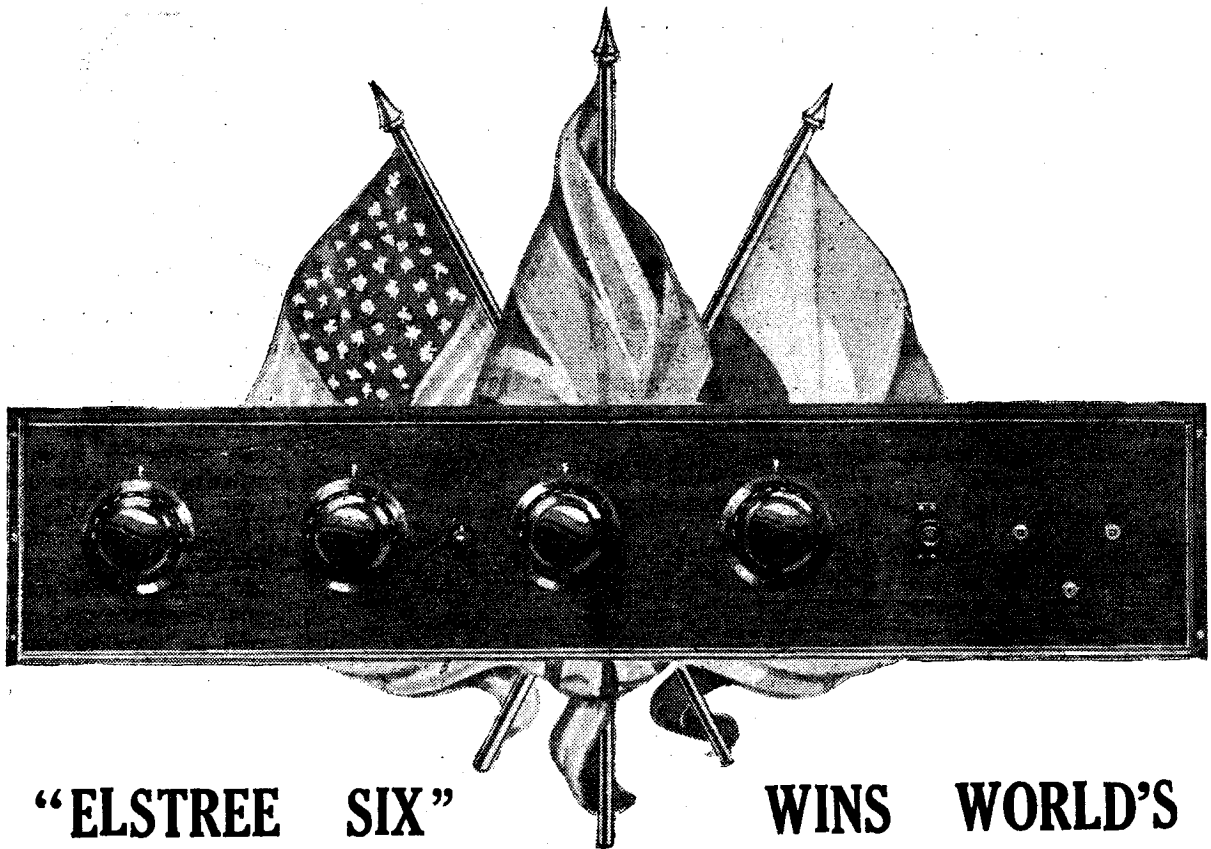The steel mast of the broadcasting station at Berlin. A novel feature of the tower is a restaurant situated approximately 200 feet above the ground.



“ELSTREE SIX” WINS WORLD'S CHAMPIONSHIP

Radio Press Star Design Gets Premier Award in Dutch International Competition


Amateurs of all nationalities were invited to submit wireless apparatus constructed by themselves for competition in the International Radio-Amateur Festival, held in Amsterdam between September 18th and 26th. The aim of the Amsterdam Radio Society, organisers of the festival, was to encourage the spirit of good will between Dutch radio amateurs and their friends in all countries.

The result of this international competition, open to the world, has gained for a Radio Press reader and a Radio Press design the first place. THE GOLD MEDAL OF THE COMPETITION, THE HIGHEST DISTINC-

TION POSSIBLE, HAS BEEN AWARDED TO AN “ELSTREE SIX” set, entered by Mr. R. W. Emerson, of 3, St. Ann's Terrace, St. John's Wood, London, N.W.8. Mr. Emerson is interested in the construction of wireless sets purely as a hobby, being engaged in the fur business.

THE “ELSTREE SIX” ENTERED FOR COMPETITION WAS IDENTICAL IN LAYOUT AND CONSTRUCTION WITH THE ORIGINAL “ELSTREE SIX,” the Radio Press Star Set of which a full description was published in the June issue of “Modern Wireless.”

THE WINNER TELLS HIS STORY.

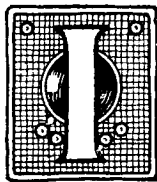

HAVE been asked by the Editor if I would give Radio Press readers an account of my visit to the Amsterdam Radio Exhibition, also as to why I chose the “Elstree Six” for the competition.

First of all, as to why I chose the “Elstree Six.” When the basis of

this circuit appeared in *Wireless Weekly* on April 7, 1926, Vol. 8, No. 8, I was rather impressed with its possibilities, especially as to the elimination of the parasitic oscillations which are sometimes present in split coil neutrodyne circuits, but I decided to wait a little (as I was still experimenting with another receiver) to see if Radio Press went any further with this,

and I was very pleased to see it arrive in the circuit of the “Elstree Six” which appeared in the June number of *Modern Wireless*. I then decided to leave the other set and make up one stage of H.F. on this principle before making the set, to see how it functioned, and I then tried it in front of a five-valve set, and found it quite good and stable. This settled it, so I started and

THE WINNER'S STORY—(Contd.)

made a set of coils, and built up the set; but, unfortunately, my first attempt was a complete failure, as I was only guided by the wiring diagram, and as I did not get the exact distance between the coils the set failed absolutely to neutralise. Eventually I was able to obtain a full-size blue print, and I made the set again after measuring this, and when it was finished and I had put the last wire on and connected up, it neutralised first time. Although my aerial is screened on all sides and 60 ft. long, and no down lead at all and an earth lead of about 40 ft. to an earth tube, I can hear Bournemouth any day free from London and as loud, and only being one mile away from 21.0's aerial I think this speaks very highly for the set. I have a choice of 20 stations any evening, weather conditions permitting, and I have tuned in over 40 stations on the loud-speaker.

The tuning is fairly sharp but easy, as the dials can be set to give the same setting for each condenser, and I would advise any reader who is in doubt as to what set to make to set about it now and make one, and I am sure they will not be sorry. If any such reader lives within riding distance of my house




Mr. Emerson's "Elstree Six" won this gold medal (the premier award).

I should be pleased to demonstrate this set to him, and give him every assistance to make a success.

The Visit to Holland

Now regarding my visit to Holland, I was very much surprised to receive a message to the effect that I had won premier prize in the International Competition, which was the gold medal, and I thought it only right that I should go over and receive this signal honour at the hands of the Society, so I wired to the Secretary to the effect that I would come over to receive same, also to bring greetings from British amateurs. I arrived at Amsterdam at 8.30 a.m., where I was met by the Chairman and

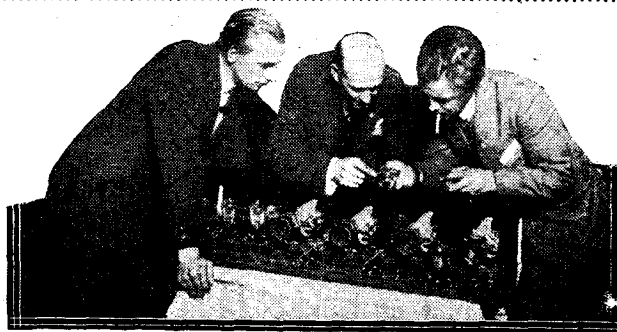

The winner (centre) describing his "Elstree Six" to two of the officials of the Amsterdam Festival.

Treasurer of the Amsterdam Radio Society, who escorted me to the Belle Vue Hall, where the Exhibition was taking place, and on my arrival, as a mark of esteem, was greeted with "God Save the King" by the band. I was then introduced to all the committee and some of the judges, including Herr Idzerda, the owner of the celebrated PCGG station, of whom British amateurs have all heard before broadcasting commenced.

Prize Distribution

At 8.30 on Sunday evening the distribution of the prizes took place, and I was duly presented with the gold medal, and this was added to by a very kind speech of congratulation by the Chairman, which was translated into English for me by him.

On Monday morning I made a tour of all the stands to see the sets and components that were being offered, which sets were mostly of the straight type and five-valve Aperiodic 2H.F. type.



Mr. R. W. Emerson.

I was rather disappointed at the small amount of components that were made by the Dutch manufacturers, the majority of components being either German or American, but there were a few British parts there; also loud-speakers. During the afternoon I was taken round the town and shown the interesting parts, also the Rembrandt Galleries, by Herr Kroon, and after the exhibition was entertained by several of the exhibitors at the Hotel Americain, where the health of the British amateurs was toasted, and hopes expressed that the relationship between the Dutch and British amateurs would be more firmly united.


During the evening I proposed giving a special demonstration of the "Elstree Six" for the benefit of the exhibitors and public, but although I tuned in several stations, atmospherics were so bad that reception was absolutely spoilt, but they heard sufficient to show the capabilities of the set, and I made several of the persons present work the set themselves, and as a result I have got to send sets of parts to assemble there for demonstration purposes! I was unable to repeat this on Tuesday, as the set had to be packed ready for despatch to London on Tuesday morning.

A Final Message

I should especially like to thank Herren Verkoeven, Nassau, Tooren, and Bontikoe Irving for the way they did everything to make my

(Concluded on page 505.)

MORE "ELSTREE SIX" APPRECIATIONS

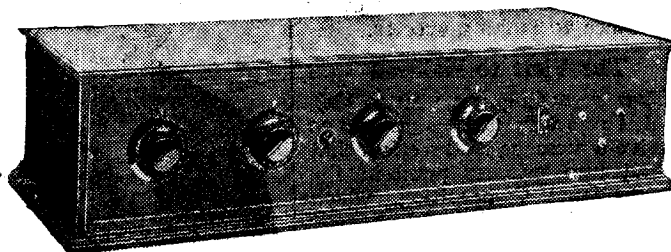

*Letters from
enthusiastic builders.*

"Willing to Demonstrate"

SIR,—Further to my letter *re* my results with the "Elstree Six," which you published in the August number of MODERN WIRELESS, I would like to state that I am willing to demonstrate my "Elstree Six" to anyone interested (by appointment, of course). I have already had some twenty or so visitors, and all have been delighted with the results, followed by wholesale scrapping of old sets and the building of "Elstree Six" sets. If you care to make my offer known to your readers I will do my best to give any assistance possible.—Yours truly,

SIDNEY JOHN ALAND.

9, Kilmaine Road,
Fulham.

"Every Station"

SIR,—As a dealer I was interested in the reports of the "Elstree Six" and its claims for selectivity and distant reception and the ability to tune in so many stations on the loud-speaker. I obtained the necessary components strictly to specification and assembled the set, with the result that I am able to tune in every station, both long and short wave, on the identical condenser settings as given in MODERN WIRELESS of June and July.—Yours truly,

W. B. FORD.

Merly Wimborne.

"Very Satisfactory"

SIR,—*Re* results obtained from the "Elstree Six," I am pleased to state that this receiver has been working now for a month and the results obtained, up to the time of writing, are very satisfactory. I have certainly not yet received 70 stations, but I feel quite sure that with a little more practice, the number of stations I receive will compare very

favourably with the number of stations that the set is claimed to receive.


May I mention that I have been a constant reader of both the MODERN WIRELESS and *Wireless Constructor*, having built several of your designs.—Yours truly,

W. HARVEY.

Gates-head-on-Tyne.

"Almost Incredible"

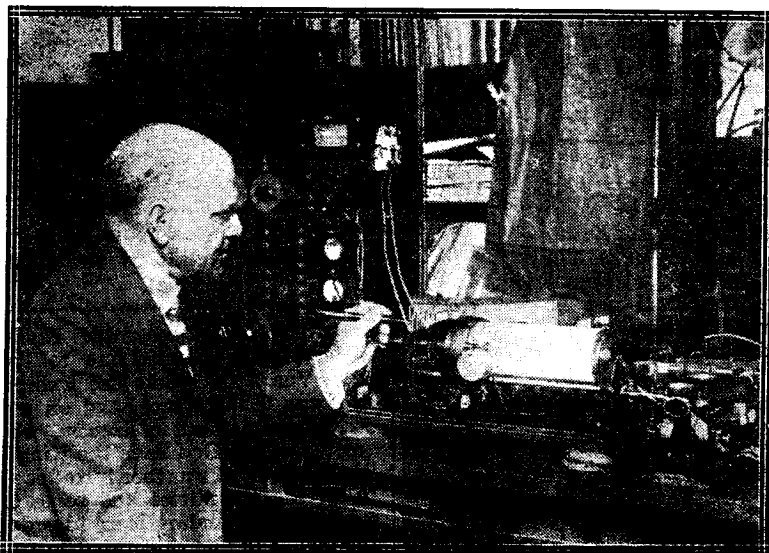SIR,—I have just returned from the Channel Islands, where I have been demonstrating the "Elstree Six." This receiver is the finest I have yet handled for simplicity of working, and the way station after station can be tuned in is almost incredible; as regards



Part of the apparatus used at the weather forecast bureau at Washington, U.S.A., by means of which weather forecast maps are transmitted and received by wireless.

An article is being prepared giving further details, operating notes, etc. of the Screened Coil Superheterodyne described in our last issue. It was unfortunately impossible to include it this month, since it is desired to give details of the results obtained with a number of makes of intermediate transformers, some of which are not yet available for testing.

volume and purity of tone, everyone who has heard it agrees that they have never heard its equal. The receiver, as I have proved by my demonstrations, is fully up to your claim for it. All B.B.C. stations could be heard quite clearly for over 500 yards away.

Wishing you every success, and I hope for nothing better than the "Elstree Six."—Yours truly,
Stoke Newington. C. WILSON.



Treasures which crumbled at a touch

NOT so long ago the whole world was thrilled with the accounts of the exquisite treasures being exposed to the light of day at Luxor. Superb jewels worth a king's ransom—marvellous carvings typical of the splendour of the Pharaohs—georgous sepulchral furniture—and most wonderful of all, tapestries and draperies which, until they were moved, retained the beauty and freshness of the day they were woven.

But—whilst the jewels, the carvings and the furniture have now been added to the museums—the fabrics and the tapestries have gone for ever. Their delicate, gossamer-like threads could not withstand even the most careful handling. After thirty centuries, the fibres had lost their pliability—at a touch they shivered into a thousand fragments.

This tragedy of crumbling treasures affords a striking parallel for wireless enthusiasts. Once the filament of a valve is crystallised

with age it is liable to become fractured at the slightest blow. Even the ordinary wear and tear of everyday use will shorten its life. Now, however, a filament has been discovered which—because it operates almost without heat—permanently retains its pliability. Age cannot affect it. Even after several thousand hours of use its electronic emission is as prolific as ever. This Kalenised filament is one of two vital improvements introduced by Cossor this season. The other is Co-axial Mounting—a system of construction acknowledged to be one of the greatest steps forward in valve design for several years. Ask your Dealer to-day for our latest Folder describing the many exclusive features of these new valves.

Read about their amazing economy—their greater sensitivity and improved tone, but above all, their guaranteed uniformity of performance. Never before have such remarkable valves been available.

The new Cossor Point One

With Black Band. An ideal supersensitive Detector. Consumption .1 amp. at 1.8 volts

14/-

The new Cossor Point One

With Red Band. Pre-eminent among H.F. valves. Consumption .1 amp. at 1.8 volts

14/-

The new Cossor Stentor Two


With Green Band. For Power Valve use—ideal for Super Sets. Consumption .15 amp. at 1.8 volts

18/6

Cossor Valves

TESTED RADIO
BOWYER-LOWE
APPARATUS

- FOR PERFECT RECEPTION

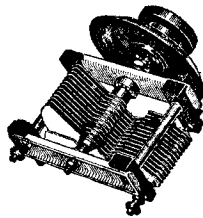

POPULAR CONDENSERS

The "Popular" condenser, owing to its design, provides a precision corrected square law condenser at a low price. The rotor is electrically connected to the girder and plates, while the fixed plates are held at four points by ebonite insulators. Supplied with 3-in. dials.


.0003 M.F. 10/-
.0005 M.F. 10/6



COIL SCREENS

These coil screening boxes provide a very efficient method of utilising screened coils. The sockets are standard. The box is of polished aluminium and screws into the base screen, thus providing a perfect electrostatic screen.


Screen and Base 15/-

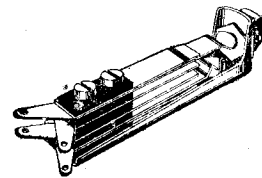

JACKS

The introduction of Bowyer-Lowe Jacks provides the wireless constructor with components which are far superior in design and manufacture to anything hitherto available.

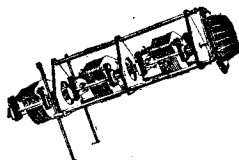
Single circuit, open 2/2
Single circuit, closed 2/7
Double circuit, closed 3/-
Filament, single control 2/9
Filament, double control 3/3



GANG CONTROL CONDENSERS

This condenser has been designed for use in single control receivers and is provided with three independent condensers of .0005 M.F. capacity, insulated from one another but controlled from one dial. A simple means is provided for varying the relative positions of the rotors so that the different coils and transformers can be balanced.

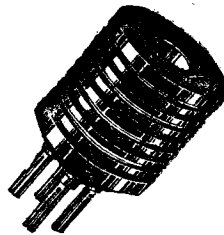
With 4-in. dial £3 13 0
Without dial £3 10 0



H.F. TRANSFORMERS

These transformers are section wound with the Primary and Secondary loosely coupled, and are highly efficient. The primary is tuned by means of a .0003 M.F. variable condenser to the stated range. Every transformer is matched to a standard and no particular selection is needed for multi stage H.F. working.

Each 9/-


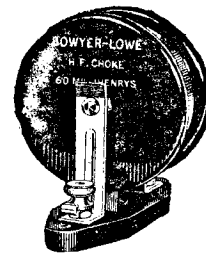


H. F. CHOKE

The graduated sizes of the air core high frequency chokes available in this series enables the best size to be selected for any circuit, as changes can be very quickly made. The chokes are machine-wound of low self capacity, while the sizes will cover most needs of the amateur.

2, 5, 10, 20, 40, 60 Millihenries, 7/-
Base for Chokes 2/-

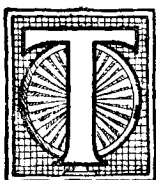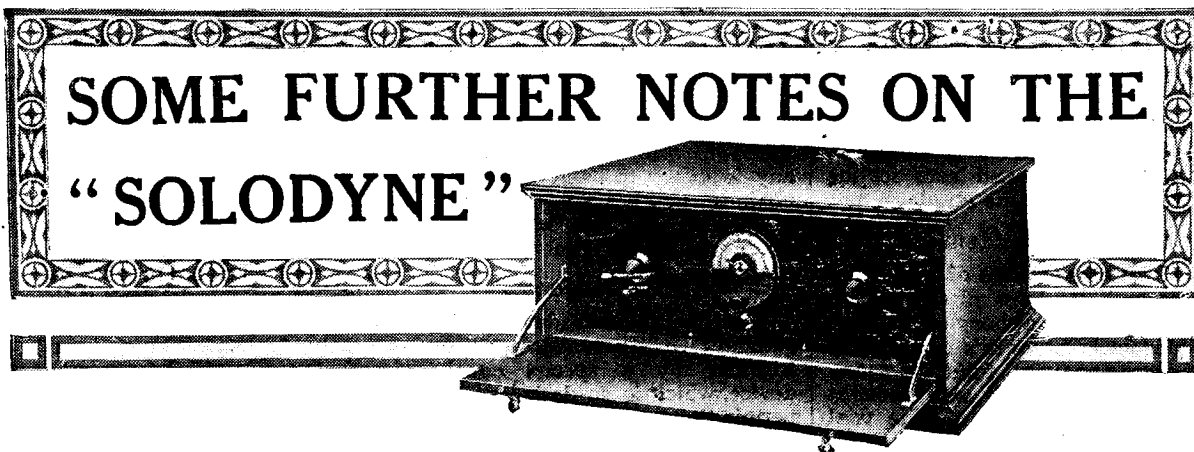ANNOUNCEMENT BY THE BOWYER-LOWE CO., LTD., LETCHWORTH, HERTS.



HERE are many readers who have by now constructed the "Solodyne" and are obtaining their first results with this receiver.

As far as can be seen at present little difficulty is being experienced in obtaining satisfaction, but there appears to be one or two small points upon which further information is desirable.

One of the queries which is often raised is that of the reaction control. This at times is inclined to be "ploppy," and not to give the full and progressive increase of signal strength which is desirable. This will be found in practically every case to be due to the fact that the receiver has not been properly balanced up.

Balancing

In last month's issue instructions were given concerning the method of balancing up and neutralising this receiver. It will be remembered that the sequence of operations was briefly as follows:


1. Tune to the local station.
2. Adjust aerial condenser until aerial circuit is approximately in tune.
3. Neutralise the first valve by removing the fixed resistor and adjusting the neutralising condenser until a zero is obtained.
4. Neutralise the second valve in a similar manner.
5. Tune in to a distant station.
6. Balance up all the circuits again.

Now it is in this final balancing up that the satisfactory operation of the receiver is obtained. With an

approximate balance it is possible to obtain quite a variety of stations, but they lack the kick and volume that one would expect, and moreover the reaction control is not smooth and progressive.

An Interesting Point

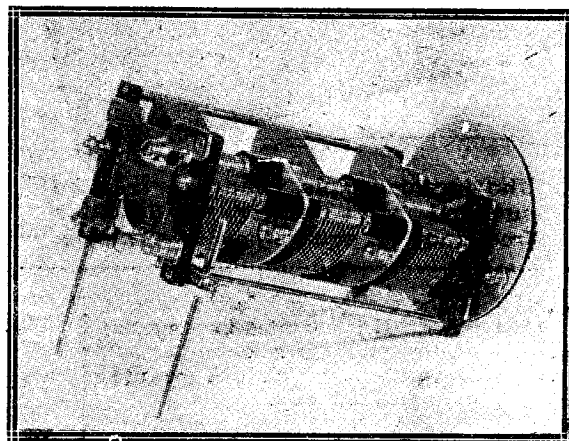If this is found to be the case, then a little more care should be taken in the balancing operations. It may be that several attempts have to be made in order to obtain a final state of affairs, but this is a matter which will quite easily be found by trial. As a matter of fact



the Ormond triple "gang" condenser.

the second "Solodyne" receiver which we constructed down at Elstree behaved in a remarkable manner, and we began to wonder if there was not some fluke in the construction of the first one which gave such excellent results, because the second model was at first disappointing in its performance.

It was not until we had tested the receiver in quite a number of different places, expecting to find a fault, that we turned our atten-

tion again to the balancing of the various condensers, and after re-adjusting them some three or four times, tuning in different stations on which to re-balance, we found that the trouble really lay in this aspect of the question.

Choosing Distant Stations

It is essential to choose the distant station which is crisp and clear cut. This nowadays is a matter of some difficulty owing to the continual heterodyning which is only too prevalent. It is usually possible with a little care to find some station somewhere about the middle of the dial on which the tuning is sharp and well defined, and on this station the balancing operation should be carried out.

Particular care should be paid to the balancing of the second and third condensers. The aerial condenser can always be balanced quite easily, but the other condensers are apt to be a little critical. The definite test as to whether the circuit is properly balanced up really lies in the reaction control, and it will be found that when the last two circuits are correctly adjusted the reaction will cause a progressive

smooth increase in signal strength until the receiver finally oscillates.

Aerial Circuit

The aerial circuit also affects the reaction control to a small extent, but this can be slightly out of balance without causing serious trouble. We have dwelt upon this subject at some length because this is really the only part of the operation of the receiver on

SOME FURTHER NOTES ON THE "SOLODYNE"—(Concluded)

which any trouble is likely to be experienced, and it is simply a matter of time and care for the correct results to be obtained.

Triple Condensers

Many other makes of triple condensers have been placed on the market, and although, as was stated in last month's issue, many of these appear to fulfil the necessary conditions, it was thought desirable to make a definite trial of these alternative condensers before definitely recommending them for use in the "Solodyne" receiver. This has been done in the case of several of the alternative condensers, while certain other makes are at present undergoing test and will be reported on next month.

Cyldon Condenser

This condenser is made up by mounting three standard Cyldon condensers on an ebonite base plate. Each of the condensers is provided with a long rocker arm, all of these being linked up by a solid rod. Thus the rotation of the first condenser carries with it the other two. Independent adjustment of each condenser is possible by unscrewing a set screw and advancing or retarding the condenser by means of a tommy bar. The adjustment in practice was found to be quite simple, and the results obtained with this condenser were very satisfactory.

Three-hole-fixing is provided with a special support to take the weight of the remote end. Any tendency to hand effect is avoided by an earth shield which completes a well-constructed unit.

Ormond Condenser

This condenser comprises three Ormond units mounted in a skeleton chassis, and provided with an insulated coupling between the several condensers. By undoing the screw and rotating the spindle of the condenser in question with the tommy bar provided, the condensers may be balanced up as required. Feet are provided to take the weight of the end of the condenser, single hole fixing being

utilised at the panel end. An earth shield is also provided to avoid any tendency to hand effect. Self-aligning ball-bearing construction is adopted, and the whole makes a very neat and useful component.

Utility Condenser

This unit is made of three standard Utility condensers linked together by a special coupling device, which is so designed as to permit the variation of the settings


time, if there is any slight discrepancy between the second and third coils, it can be allowed for by means of this balancing condenser.

Provided that these three coils used for tuning purposes are accurately matched, as is in fact the case with the commercial screened coils, then this method of compensation appears to be quite sound, and in actual practice this has proved to be the case. This condenser has been tried in an actual "Solodyne" receiver and has given results equally as good as those obtained with the original method of compensation.

The method has the advantage that either Square-law or S.L.F. condensers may be utilised, whereas this is not the case with the ordinary method of compensation by rocking the rotors of the various condensers.

The L.F. Side

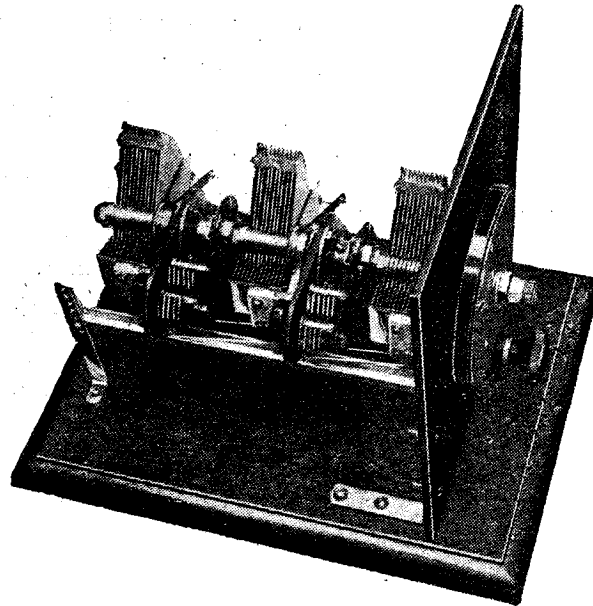With the "Solodyne" receiver, as with the "Elstree Six," the low-frequency side is quite standard, and can be altered if desired by the constructor. For example, some constructors may prefer instead of using a volume control to insert jack switching so that they may cut out the last stage altogether. This has been tried out experimentally and is perfectly satisfactory.



The Igranic triple condenser can be supplied with either straight-line frequency or square-law type plates.

of the condensers relative to each other. It is mounted in a suitable chassis and gives quite a neat arrangement which can be used quite satisfactorily.

Igranic Condenser

Messrs. The Igranic Electric Co. have submitted to us a "gang" condenser for use in the "Solodyne" which uses a somewhat different principle of compensation. The arrangement consists of three standard condensers mounted up in a gang, while two small balancing condensers are connected across the second and third condensers respectively. It is suggested that these two condensers may be set to a value which will duplicate the effect of the aerial capacity connected across the tapped portion of the first tuned circuit. At the same



LATE NEWS.

THE "SOLODYNE" IN CHICAGO.

Following on the result of the success of a Radio Press Star Design at the World's Fair, New York, we have received cabled news of further interesting successes at Chicago. From the meagre information at hand, it would appear that a "Solodyne" receiver constructed by Mr. Anspach, of Dartford, Kent, has won a first prize, and that the "Mewflex," set constructed by Master J. A. E. Black has secured the second award. Mr. Anspach, who has for many years been an enthusiastic home constructor, occupies a position of responsibility in the works of a well-known manufacturing chemists, and Master Black needs no introduction. These results are, of course, subject to written confirmation, and further details will be given in our next issue.



Build your own loud speaker

GONE ARE the days of troublesome 'phones. The LISSENOLA brings loud speaker convenience to every home at a record in low price. For 13/6—less than the cost of headphones—you can buy this wonderful loud speaking unit, needing only the addition of a horn to make it a powerful, full-sized instrument yielding results equal to an expensive speaker. And you can build a horn yourself—with each LISSENOLA we give you full size exact patterns and clear instructions how, for a few pence, you can build a big horn of proved efficiency. In addition, the LISSENOLA will fit the tone arm of any gramophone. The secret of this efficiency rests in the remarkably effective manner in which the electro-magnetic sound-reproducing system is concentrated.

Compare the price last

—before you buy go to your dealer and make this test: Ask him to put on the best loud speaker he has in stock—then use the same horn on the LISSENOLA, and see if you can notice any difference.

THE LISSENOLA

Now no home need lack a loud speaker.

Full directions for making this horn are given with every "Lissenola."

A cone diaphragm loud speaker can easily be constructed. The illustration shows one method of mounting.

The "Lissenola" instantly converts any gramophone into a loud speaker.

The "Lissen" Reed attachment (pat. pending) for use with cone diaphragm loud speaker. Price, 1/-




PRICE

13/6

EACH.

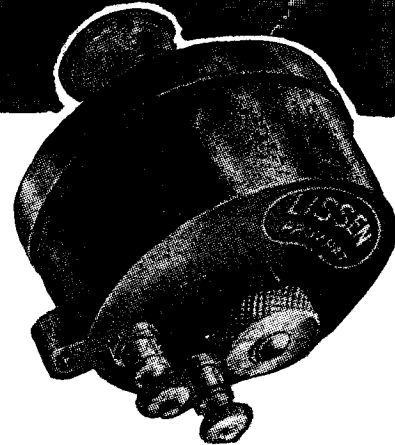The illustration shows the effective horn you will build yourself—it can be covered with fancy paper, or wallpaper, and painted so as to resemble a factory article. Get a LISSENOLA for your home.




By using the Lissen Reed (sold separately for 1/-) the Lissenola will carry a cone or any other diaphragm working on the reed principle.

Your dealer will gladly demonstrate and supply, or the Lissenola can be obtained post free by return from the makers—

LISSEN LIMITED,

20-24, Friars Lane, Richmond, Surrey.

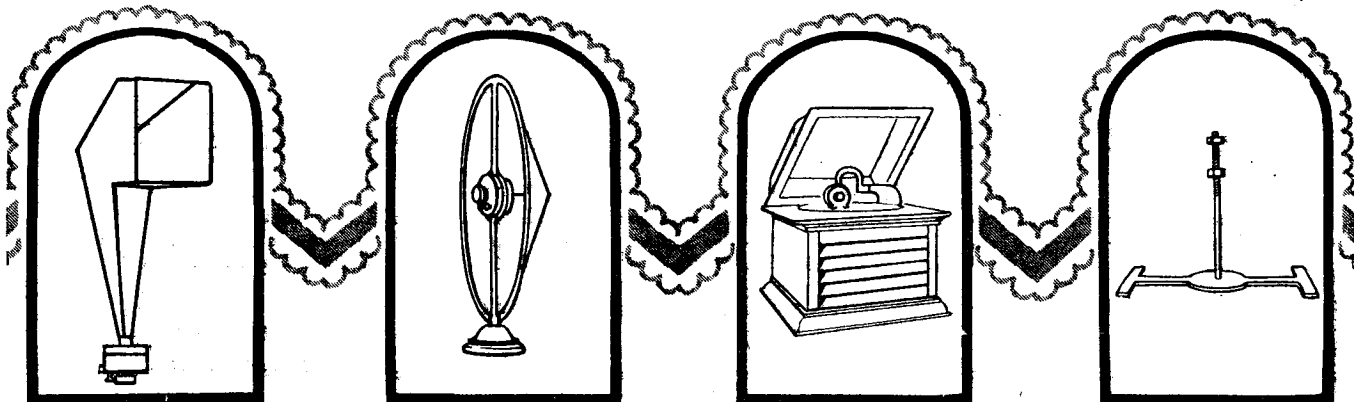Phone: Richmond 2285 (4 lines). Grams: "Lissenium," Phone, London.
Managing Director: T. N. COLE.



Tell the Advertiser you saw it in "MODERN WIRELESS."

AMPERITE

"means right amperes"

A BASIC NEED IN EVERY
CIRCUIT



The Self-Adjusting Rheostat

1. Eliminates hand rheostats—thereby simplifying control and giving compactness.
2. Greatly simplifies set wiring, therefore makes for greater efficiency.
3. Prolongs life of valves from 2 to 3 times.
4. No moving parts—therefore no grinding noises.
5. Permits use of various types of valves or combination of valves.
6. No filament meters necessary.
7. Brings the most out of each individual valve—automatically—no guessing.
8. Makes perfect valve operation absolutely fool-proof.

AMPERITE operates on the thermo-electric principle. Contains a specially treated filament hermetically sealed in a glass tube and surrounded by an inert gas. This filament has the unique property of automatically changing in resistance as the L.T. battery voltage changes—so that a practically constant current is maintained in the valve filament. Consequently the valves are constantly operated at maximum efficiency. No knob to turn. Nothing to get out of order. Amperite mounts conveniently inside the set. Really takes the place of a good hand rheostat, a delicate meter and an expert operator.

Tested by the Elstree Laboratories and used in the "Elstree Six" and other good receivers.

Write for
FREE

24 page circuit booklet.

THERE IS AN AMPERITE FOR ALL STANDARD VALVES.
THE FREE BOOKLET WILL GIVE YOU FULL
INFORMATION.

5/- each with base.

AMPERITES ARE SOLD BY ALL HIGH-CLASS DEALERS.



If unable to obtain write direct to:—

ROTHERMEL RADIO CORPORATION of Gt. BRITAIN LTD.,

Telephone:
Mayfair 578-9.


24-26, Maddox Street, Regent Street,
LONDON, W.1.

Telegrams:
Rothermel "Wesdo" London.

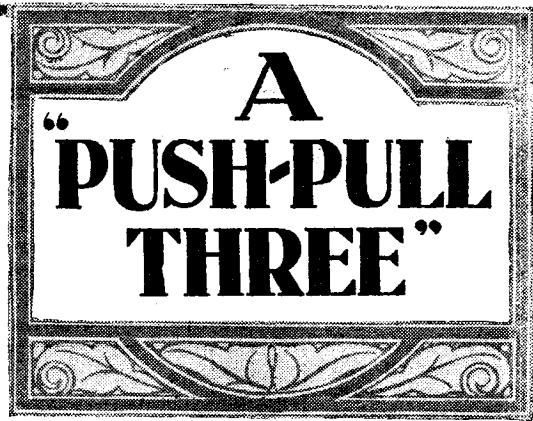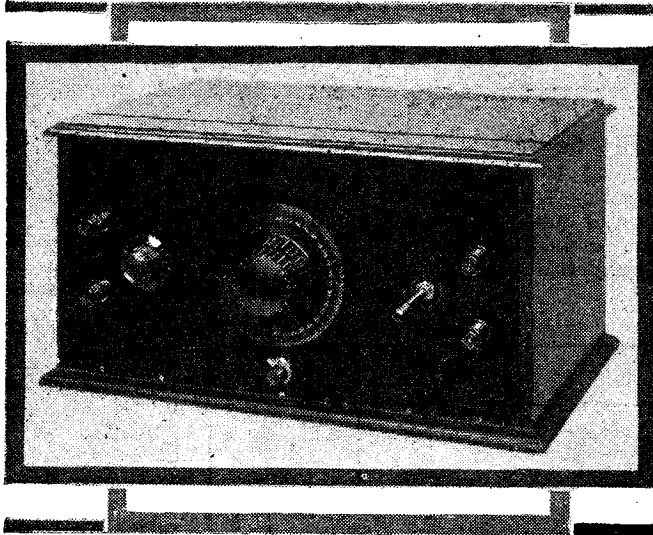

By
STANLEY G. RATTEE, M.I.R.E.

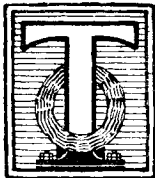Have you a stock of general-purpose valves which you want to use in a loud-speaker set? Here is a design for a receiver which employs such valves throughout and yet gives really good loud-speaking.



HE purpose of the receiver to be described is to enable the local and Daventry stations to be received at loud-speaker strength up to distances of 15 and 100 miles respectively.

This does not necessarily mean that the instrument is useful only for this class of work, for by using telephones instead of a loud-speaker many of the Continental stations can be tuned in at good strength.

A Question

It is possible that some readers will ask themselves why push-pull amplification is used in this particular set, since the low-frequency stages are preceded only by a detector valve. It is true that the grid swing with this arrangement in normal circumstances is not so great as would justify the use of push-pull amplification and power valves, but the present arrangement allows, and is intended to allow, the use of general purpose valves throughout in order to produce results which are not appreciably different from those given by power valves when used in an ordinary straight L.F. amplifier.

The Transformers

The transformers used in this form of amplification are different

from those usually associated with low-frequency work in that the first is arranged with a split-secondary while the second has a split primary, there are therefore five terminals on each transformer instead of four.

ing distortion arising from this cause.

Use as a Family Set

The receiver as illustrated has been in use for some weeks now as a family loud-speaker set, and for

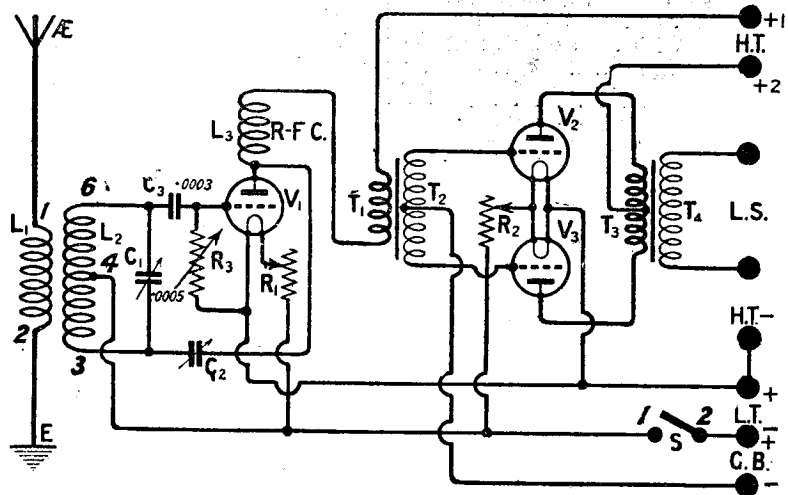


Fig. 1.—The theoretical circuit. C₃ is the reaction control condenser.

The connections when using these components are such that the two low-frequency valves are in parallel, and in consequence the signal energy is split up equally between the two valves, reducing very largely the possibility of overloading them, and thus prevent-

this purpose has been used with three .06 valves and an 80 volt high-tension battery.

The simplicity of the panel and the fact that an "on and off" switch is incorporated renders the receiver particularly suitable for use by womenfolk who, so far as

A "PUSH-PULL THREE"—(Continued)

my experience goes, are usually somewhat frightened of more than one knob; visions of burnt out valves and other disasters looming largely in their minds should they touch the wrong one.

Reaction is incorporated in the set and is controlled by a small condenser of the neutralising type, and in order that there may not be any difficulty in making the receiver oscillate with this small condenser when various valves are used a variable grid leak is also provided.

Points in Design

In order that the set may be reasonably selective for those occasions when it is desired to listen to distant stations on telephones, the receiver is designed for use with "fieldless" coils of the plug-in type, thus allowing an inductive coupling to be used for the aerial circuit. With the exclusion of the aerial, earth and loud-speaker

The Circuit


The theoretical circuit accompanying this article shows L_1 and L_2 as the aerial and grid coils, and these are embodied in the "fieldless" component previously referred to.

vided, the centre point being connected to the H.T. positive. The two ends of the primary windings are each taken to the plates of the low-frequency valves, while the loud-speaker is connected across the secondary winding.

It will be further noticed that the L.F. valve filaments are controlled by a common rheostat, and since this is done for simplification, it is recommended that the valves V_2 and V_3 be of the same type, particularly as a common grid bias is used.

Components and Materials

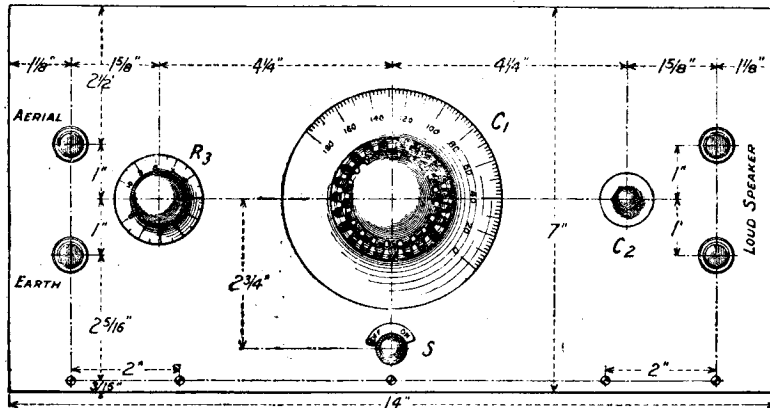There will be found separately a list of components and materials used in the set as illustrated, and though it is not advised that values where given be departed from, it may be taken that other suitable components will be found in the advertisement pages with the exception of the transformers, these being of special type only



The panel drilling diagram. Blue-print No. 183a is obtainable free of charge.

The form of reaction used is, it will be seen, of conventional type and is controlled by the condenser situated between the radio-frequency choke and one of the ends of the coil L_2 .

The first transformer it will be noticed is arranged with a centre

point being connected to the H.T. positive. The two ends of the primary windings are each taken to the plates of the low-frequency valves, while the loud-speaker is connected across the secondary winding.

COMPONENTS REQUIRED

- Cabinet to take panel and baseboard, 14 in. by 8 7/8 in. by 3/4 in. (Camco).
- Ebonite panel, 14 in. by 7 in. by 3/16 in. (Camco).
- "Yaxley" switch. (Rothermel Radio Corporation, Ltd.).
- "Duvarileak" variable grid leak. (Dubilier Condenser Co., Ltd.).
- "Neutravernia" condenser. (Gambrell Bros., Ltd.).
- .0003 fixed condenser. (Dubilier Condenser Co., Ltd.).
- .0005 S.L.F. condenser. (Ormond Engineering Co., Ltd.).
- Three "Lotus" valve-holders. (Garnett, Whiteley and Co., Ltd.).
- Two "Push-Pull" transformers. (Radio Instruments, Ltd.).
- Two baseboard mounting rheostats. (A. F. Bulgin and Co.).
- One "Fieldless" coil and six socket base. (Lissen, Ltd.).
- Radio frequency choke. (Varley Magnet Co.).
- Ten terminals: "Aerial," "Earth," "L.S." (2), "L.T.-," "L.T.+", "G.B.-," "H.T.-," "H.T.+1" "H.T.+2." (Belling and Lee, Ltd.).
- Panel brackets. (Burne-Jones and Co., Ltd.).
- Quantity No. 16 "Glazite" and wood screws.
- Ebonite terminal strip, measuring 6 in. by 2 in. by 3/16 in.

terminals, all the terminals are fitted to an ebonite strip situated at the back of the set, thus doing away to some extent with the untidiness of trailing battery wires. The American type of cabinet is adopted so that valves and coil may be enclosed, and a lid is provided to permit of access to the interior.

tapping which is connected to the grid bias negative, the two ends each being connected to the grid of a valve; this particular transformer is called the "input" transformer.

The second transformer is different from the first in that instead of having a centre tapped secondary, it is the primary which is thus pro-

vided, the centre point being connected to the H.T. positive.

just recently placed upon the market. The tuning condenser used is fitted with a slow motion device, and in distant reception this refinement will be found exceedingly useful; the receiver can, however, be easily operated quite satisfactorily without using this device.

Evening News OCTOBER 7 1926.

DANCING AND

WOULD ALMOST PERFECT
G. WIRELESS.

WITH LONDON DEMONSTRATION NO
ONE SHOULD MISS.

MUSEUM CONCERT.

From Our Wireless Correspondent.

During the past few months I have been asked almost daily: "Where can I go and hear a wireless set that will give me a fair idea of what a first-rate reproduction of music sounds like?"

Until very recently no such set has been permanently available for public demonstration as far as I know but now any London listener may obtain a free hearing of the very latest model of receiver and loud-speaker

Most up-to-date apparatus has been installed in the wireless section of the Science Museum in South Kensington.

After 4 p.m., on every afternoon except Mondays and Thursdays this set is at work receiving the London programme, with a strength and purity unrivalled by any apparatus I have ever heard.

7-Valve Set.

The expert in charge of the wireless section of this museum told me many details which will interest enthusiasts.

The set is one of 7 valves. The first one stage of high-frequency amplification, followed by a detector. The rectification used is a secret. I understand, a decidedly new form of anode

The set referred to in the "Evening News" article is fitted with "CYLDON" Condensers—which is further testimony to their ability to meet the exacting conditions necessary for such demonstrations. If YOU too wish for perfect reception, you MUST fit "CYLDON" Condensers.

Still further triumphs for CYLDON Condensers

- 1. Premier Award.** Mr. R. Waldo Emerson, who was awarded the International Gold Medal for 1926 by the Amsterdam Radio Society for his "Elstree Six" has written us saying that his success was due "in great measure" to his use of "CYLDON" Condensers.
- 2. Second Prize.** Radio World's Fair, New York, September, 1926. 2nd. Prize awarded in senior section of the Junior Competition for a "Mewflex" Receiver fitted with "CYLDON" Condensers.
- 3 Third Prize.** Radio World's Fair, New York, September, 1926. 3rd. prize awarded in the multi-Valve Class in the International Competition for the 'All British' Set. "CYLDON" Condensers and Temprytes were fitted.

The above competitions were open to the world—including American and European receivers. Verb. sap.

Three Popular "Cyldon" Condensers


Triple-gang Condenser	- - -	Price £3 - 10 - 0	without dial.
2-gang Condenser	- - -	" £2 - 10 - 0	" "
4-gang Condenser	- - -	" £4 - 10 - 0	" "

Get full particulars of all CYLDON Products from your dealer or write direct to the makers. Other CYLDON Condensers comprise Square-Law, Square Law Dual Pattern, and the S.L.F. model. 4-in. Knob Dial, supplied free with Square Law and Dual Models, and 2/- extra with S.L.F. or 2, 3, and 4-gang models.

CYLDON


(pronounced Sil-don)

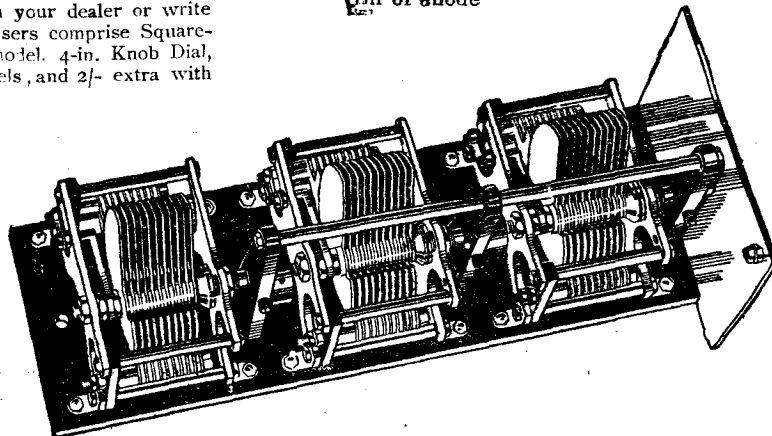SYDNEY S. BIRD & SONS
"Cyldon" Works, Sarnesfield Road,
Enfield Town, Middlesex.
Telephone: Enfield 0672.



Tell the Advertiser you saw it in "MODERN WIRELESS."

Igranic Triple Gang Condenser

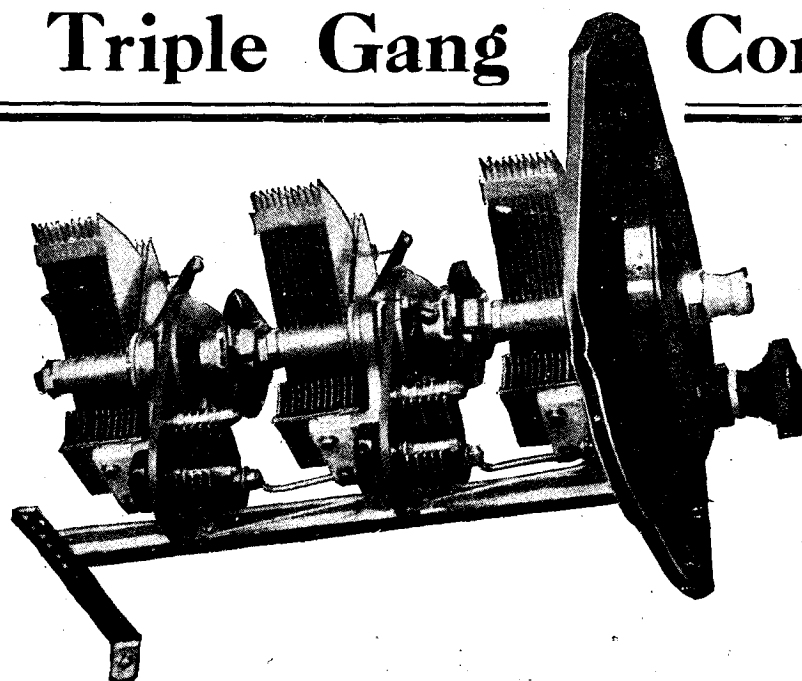

The Triple Gang problem solved


IGRANIC CENTRE TAPPED "XLLOS" (EXTRA LOW LOSS) COILS.

Igranic Centre-Tapped "XLLOS" Coils are particularly suitable for modern neutrodyne circuits.

Igranic Centre-Tapped "XLLOS" Coils actually contain two separate inductances, which may be used separately or may be joined in series to form a single coil from which a centre tapping may be taken.

Five sizes, giving wavelengths of approximately 110 to 3,500 metres.

No. 1 ...	7/-	No. 4 ...	9/3
No. 2 ...	7/6	No. 5 ...	10/6
No. 3 ...	8/3	Mounting Base	4/6

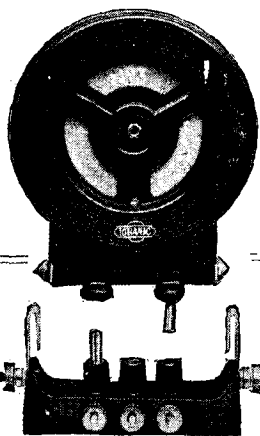

THE new Igranic Triple Gang Condenser successfully overcomes the difficulties of tuning three circuits with a single control. Two miniature condensers are incorporated in easily accessible positions so that each circuit can be exactly equalised, after which all tuning is effected through the main control knob.

The Igranic method of equalising the three circuits does not necessitate altering the relative settings of the three main condensers, and the wavelength variation for a given movement is the same in each condenser, thus preserving the accurate square-law characteristic of the Igranic Triple Gang Condenser over its whole range.

The Igranic Triple Gang Condenser is unique. It makes the tuning of the "Solodyne" as simple as a single-valve receiver.

PRICE £3 15 0

PRICE without equalising condensers, but with adjustable couplings £3 10 0

Igranic Triple Gang Condensers are built up from three Igranic-Patent .0005 mfd. Square Law Condensers. The whole construction is particularly robust; losses and minimum capacity are negligible, and the movement is extremely smooth.

The Igranic Indigraph Vernier Knob and Dial is particularly recommended for tuning. PRICE 7/6

See the full range of Igranic Radio Devices at Stand No. 55, Manchester Wireless Exhibition, Oct. 26 to Nov. 6

SEND FOR THE NEW IGRANIC CATALOGUE J. 149

IGRANIC ELECTRIC CO., LTD.

149, QUEEN VICTORIA STREET, LONDON.
Works: BEDFORD.

A "PUSH-PULL THREE"—(Continued)

Wiring in Imagination

With all the components collated together and the panel drilled in accordance with the instructions laid out in the drawing illustrating the panel layout, arrange the components upon the baseboard in such a manner as to simplify the wiring. Do not, of course, depart from the layout given, but make sure that the components chosen are


Connecting Up

The wiring up of the receiver in such a manner as to produce the theoretical circuit illustrated is but to copy the directions given in the wiring diagram. The connections to the "fieldless" coil base are numbered and the terminals 4 and 5 should be joined together and regarded as the centre tapping of the grid coil L_2 . The

The low-tension negative terminal is also used as the grid bias positive so the connection from the centre tapping of the "input" transformer secondary is taken to the only grid bias terminal so marked.

Care Needed

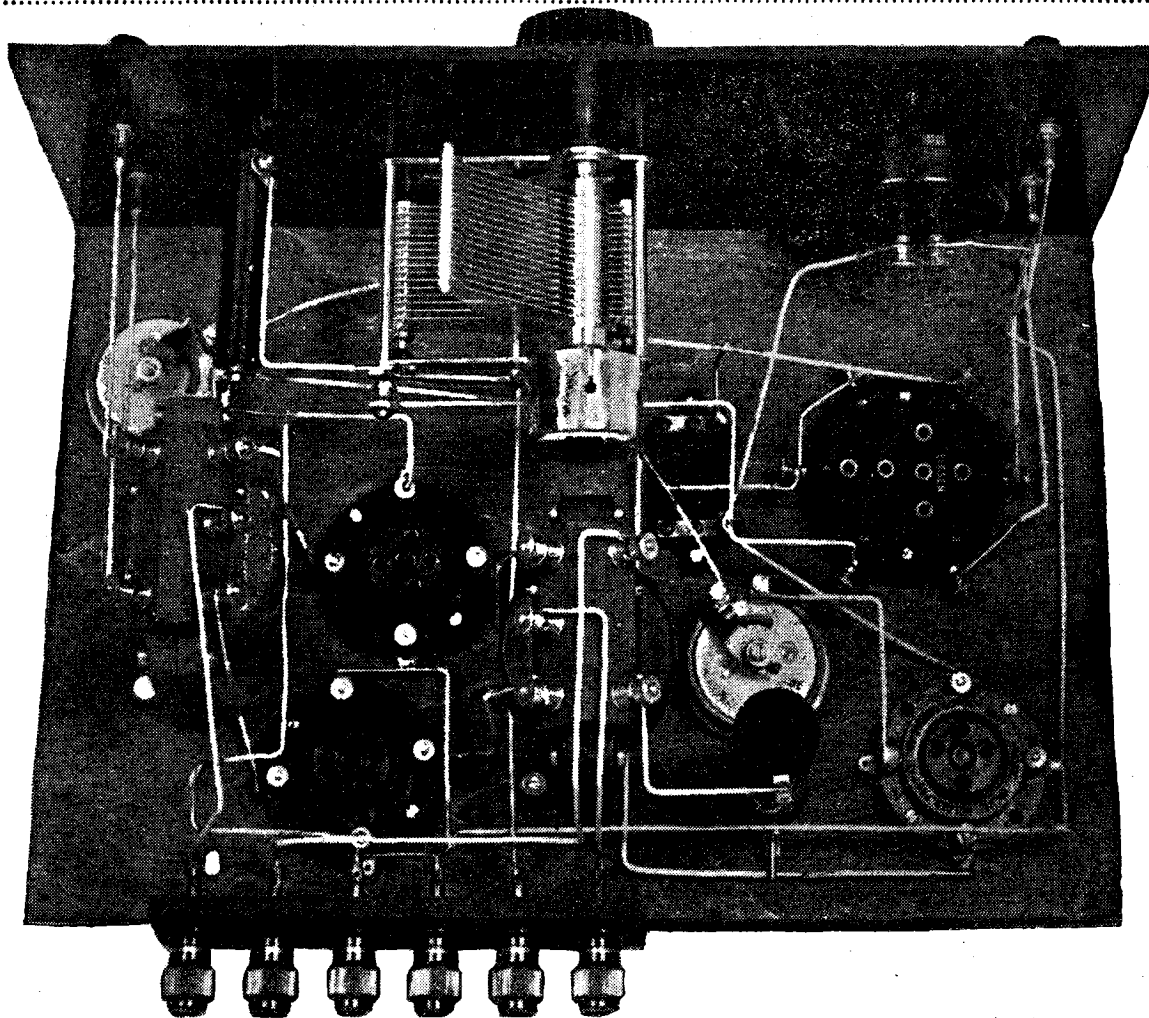When actually connecting up every care must be taken to keep




This view of the components mounted on the baseboard will help the constructor in wiring up the set.

placed the best way round for any connections before securing them to the baseboard. Imagine the connections between the various points and make up in your own mind the most attractive manner in which to wire up. If the components as listed are used, then, of course, all that is necessary to do is to copy the practical wiring diagram.

layout is such that the grid terminals of valve holders come immediately opposite the ends of the secondary windings of the transformers, to which they are connected, while similarly the two anode terminals of the L.F. valves come immediately near to the ends of the primary winding with which they are connected.

the wiring clear of the baseboard mounting rheostat, otherwise difficulty may arise when it is required to carry out any adjustment of these components; similarly the wiring to the base of the "fieldless" coil should also be done with care to ensure that the coil will not foul when it is inserted in its base.

A "PUSH-PULL THREE"—(Continued)

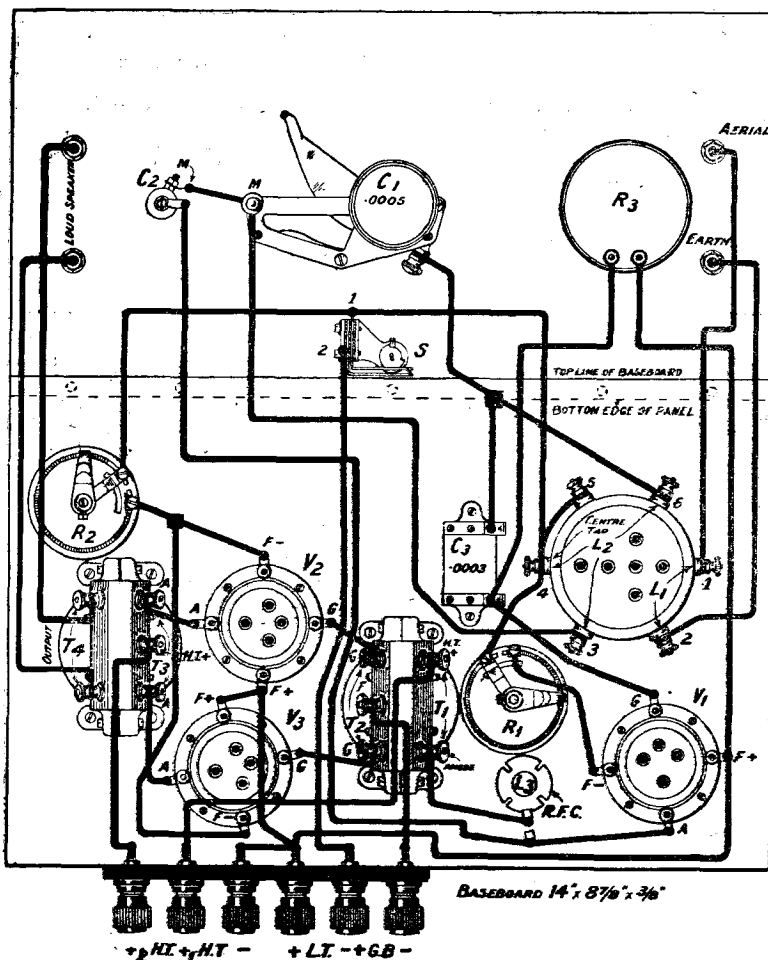

The switch S controls the valve filaments. Blueprint No. 183b may be obtained free.

The wiring to the valve holders and transformers should also be done in such a way as to give clearance to the valves when they are inserted, and though these are obvious points which everyone knows, they are nevertheless points which one frequently forgets in one's haste and enthusiasm.

Testing the Receiver

After the wiring has been completed and checked against the practical wiring diagram the batteries may be connected and the receiver tested for working.

First place in position the "fieldless" coil, turn the switch to the off position and connect the low-tension battery across the appropriate terminals. Insert the valves in their sockets and ascertain that the filament resistances give ade-


quate control of the brilliancy of the valves, not forgetting to turn the switch to the on position before doing so; in carrying out this test it should be remembered that the two low-frequency valves are controlled by a common rheostat.

Upon this part of the wiring proving correct, connect the two H.T. + terminals together and apply, say, 3 volts of the H.T. battery across the H.T. negative and either of the H.T. + terminals and note the valve as to any alteration in brilliancy; if there is any change, then the wiring must be incorrect and checked once more against the wiring diagram.

Assuming, however, that everything is satisfactory, remove the wire joining the two H.T. + terminals together and apply a voltage of about 60 to H.T. + 1 and 80 to 120 to H.T. + 2. Connect the positive of the grid battery to L.T. negative and the negative of the same battery to the G.B. — terminal, using as a start 4½ volts.

Turn the reaction condenser in an anti-clockwise direction as far as it will go, connect the aerial, earth and a pair of telephones to the appropriate terminals.

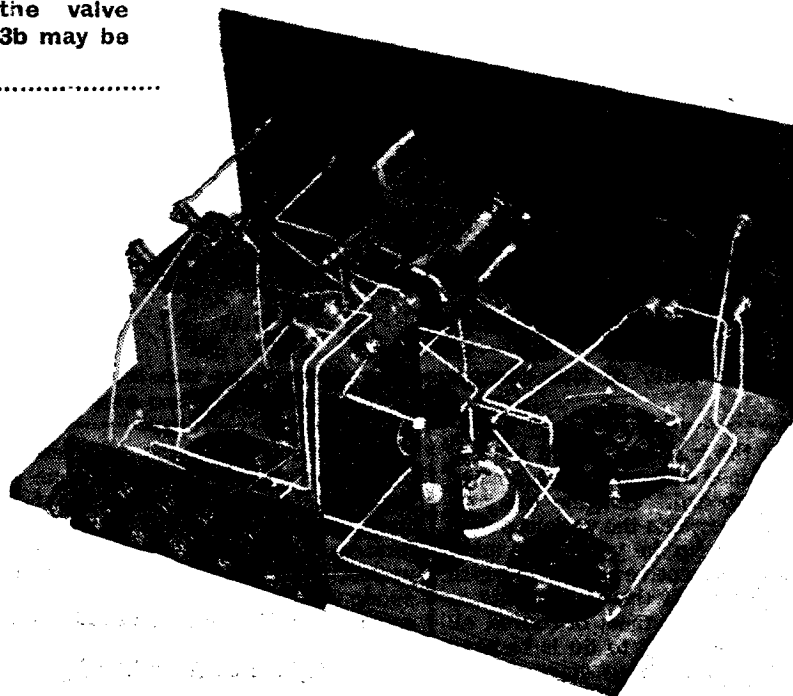The photograph shown below will assist in following out the connections to the fieldless coil base.



HITCH YOUR AERIAL TO A "STAR"!

We supply all RADIO PRESS "STAR" SETS either as finished Receivers or in parts for home-assembly.



The "ELSTREE SOLODYNE"

" 5 valves —
1 dial — 50
stations" —

Radio Press Test Report.

Every finished instrument bears the signature of Capt. W. R. TINGEY, A.M.I.R.E. (late of Radio Press Research Laboratories), who is now in charge of our Test Department.

If you want an efficient and handsome receiver ready built, you cannot do better than purchase one of these "Star" sets from us. They are designed by experts, made by skilled workmen and thoroughly tested on a large number of British and Foreign stations at full loud-speaker strength. These sets are installed free within 50 miles of any one of our branches.

Should you prefer to assemble your own set—and there is no finer hobby for the long evenings—you can do so under our famous "Pilot" Service, with every assurance that your efforts will be successful. Write for details* of this service, and mention the type of set you want.

IN EITHER CASE WE GUARANTEE YOU GOOD RESULTS!

Prices of "STAR" Sets.

"Elstree Solodyne."

	£	s.	d.
Finished Instrument, royalty paid	27	7	6
Set of Copex Screened Coils, 250/550m	3	11	0
Other parts required	10	17	6
Black Ebonite Panel, matted and drilled	11	6	
Mahogany Panel, matted and drilled	18	6	
Polished Mahogany Cabinet	4	5	0

"Mewflex Three."

Finished Instrument, royalty paid	26	3	6
Set of Copex Screened Coils, 250/550 m	3	15	0
Other parts required	10	3	0
Panel, matted and drilled	14	6	
Polished Mahogany Cabinet	4	5	0

"Distaflex Two."

Finished Instrument, royalty paid	23	19	6
Set of Copex Screened Coils, 250/550m	3	15	0
Other parts required	9	18	0
Panel, matted and drilled	11	6	
Polished Mahogany Cabinet	3	10	0

* Send three penny stamps for the new edition of our booklet giving illustrated details of many of the latest Radio Press Receivers. Much useful information on assembling, soldering and testing is also included.



THE PILOT MANUAL

You will be delighted with the amazing results! This set built with our Copex "O/C" type coils recently secured the highest award for European sets in the International Amateur Competition held in conjunction with the New York Exhibition.

	£	s.	d.
Finished Instrument, royalty paid	38	0	0
Set of Copex Screened Coils, 250/550 m, with diagram of connections...	5	0	0
Other parts required	16	5	6
Polished Mahogany Cabinet, with drilled panel and baseboard	6	0	0

If a complete set of parts is ordered, Marconi Royalties at the rate of 12/6 per valve holder are payable.

PETO-SCOTT CO., LTD.,

Head Office (Mail Order): 77, City Road, E.C.1.

LONDON, 62, High Holborn, W.C.1
WALTHAMSTOW, 230, Wood Street,

Branches:

PLYMOUTH, 4, Bank of England Place,
LIVERPOOL, 4, Manchester Street.

P.S. 6081

Tell the Advertiser you saw it in "MODERN WIRELESS."

555

Improve your Set
with
KEYSTONE
Components!

"Keystone" Neutralising Condensers.

A thoroughly efficient article, designed to suit the capacities of all types of valves. Beware of imitations which, owing to incorrect design, may not neutralise your valves properly. When ordering these condensers for a Radio Press "Star" set, please indicate which set you are building.

For board mounting

5/-

For panel mounting,


6/3

Balancing Condensers

Similar in design to the above, but having two sets of fixed plates instead of one ... 7/6

"Keystone" Fixed Resistors.

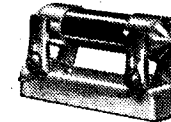Our latest product. Recommended for all receivers which use fixed resistors. Available in the following types:—



No. 4 for 25 amp. valves with 6 V accumulator.
No. 17 for '06 amp. valves with 4 V accumulator.

Price, complete with base, 2/6 each.

"Red Triangle" Panels make Perfect Sets.

One of these famous panels, guaranteed free from surface leakage, will improve reception on your set—and it will also considerably enhance its appearance. Panels cut dead to size and sold in sealed wrappers:—
Black, matt both sides. } 3d. per sq. in.
Black, polished one side, matt }
one side. Both 1/4 in. thick.
Mahogany, polished one side, 3/16 in. thick, 1d. per sq. in.

N.B.—All Radio Press sizes kept in stock.

"Keystone" Connecting Wire.

The use of coloured insulated wires improves the appearance of a set and simplifies the wiring. Keystone wire is of the highest grade, well insulated, and supplied in the following colours: Red, Green, Black, White, Yellow.
10 ft. coils, any colour ... 9d.
Packets of five 2 ft. lengths, assorted colours 10d.

"Keystone" Super-Het. Constructional Portfolio.

Before you commence building a Super-Het, send for this portfolio, which contains full-size blue prints of the famous Keystone 7 Valve Super Het. With the portfolio we will send you, free of all cost, the Keystone Book, giving minute instructions for the assembly, wiring and operation of this superb receiver. 48 pp, fully illustrated. 3/-

STOP PRESS

THIS MONTH'S SET.

The Drawing-Room Five, the Push-pull Three, and other receivers described in this issue are available as finished instruments or in parts for home assembly in the same manner as the other sets mentioned on this page. Write at once for detailed price list.

DYNAMIC CURVES


IT'S THE CURVE THAT COUNTS !

Every operating merit of a valve, except its life, shows up in its characteristic curves provided the right ones are chosen. Every S.T. valve is designed to give the right *Dynamic* curve.

An ordinary or *static* curve (see broken line) is taken with a fixed anode voltage while the S.T. Dynamic curve (thick line) takes into consideration the fact that as the grid voltage falls or rises so the anode *voltage* increases and decreases—due to the output impedance (e.g., loudspeaker, transformer or resistance). Judging a valve by its ordinary curve is like estimating the speed of a racing car while it is stationary.

The Dynamic curve given is that of the S.T. 63 Super Power Valve. See how dead straight it is over a very wide grid voltage range and you will feel that this loudspeaker valve can justifiably be called "The Valve with the Golden Voice."

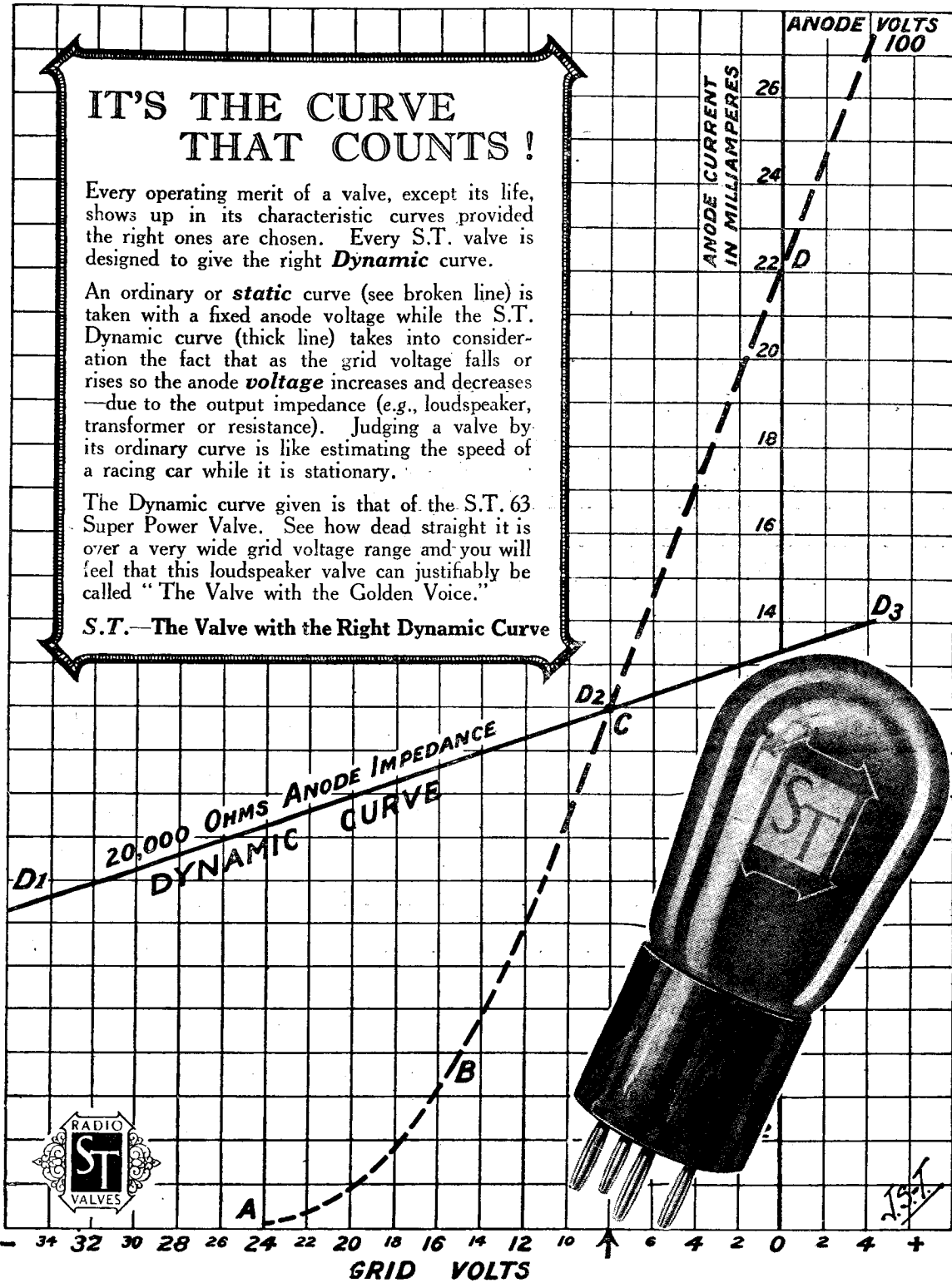S.T.—The Valve with the Right Dynamic Curve



A "PUSH-PULL THREE"—(Continued)

Adjusting the Voltages

By turning the variable condenser slowly throughout its range the local station will soon be tuned in at good strength, whereupon turn the reaction condenser ever so

until the desired effect is obtained. If, on the other hand, the receiver tends to oscillate too easily reduce the voltage connected to the H.T. + 1 terminal until a smooth control is given by the reaction condenser.

clear, using as high a value of grid volts as possible without losing signal strength or spoiling in any way the results formerly obtained.

Operating the Set

Once the two filament resistances have been adjusted to suit the valves chosen the switch may be used as the only necessary means of switching off; similarly, after the correct high tension and grid voltage have been found these two need not be touched, subject to age and so on.


Tuning is performed by means of the variable condenser C_1 , and stations should only be sought when the reaction condenser is set so that the receiver is well under control. In the event of the set being adjusted close to the oscillation point when it is desired to reduce the reading of C_1 , then the reaction condenser should be turned a little in an anti-clockwise direction before doing so, otherwise it is conceivable that considerable interference will result from permitting the set to oscillate.

Valves

The receiver has been tried with valves of all types and makes, using 2, 4 and 6 volts as the low tension supply, and satisfactory results have been obtained with all of them.

For purposes of general listening the receiver has for a long time been fitted with ordinary general-purpose .06 valves for reasons of economy in filament current, with the relatively low H.T. voltage of 80 applied to the anodes of the low frequency stages.

(Concluded on page 622.)

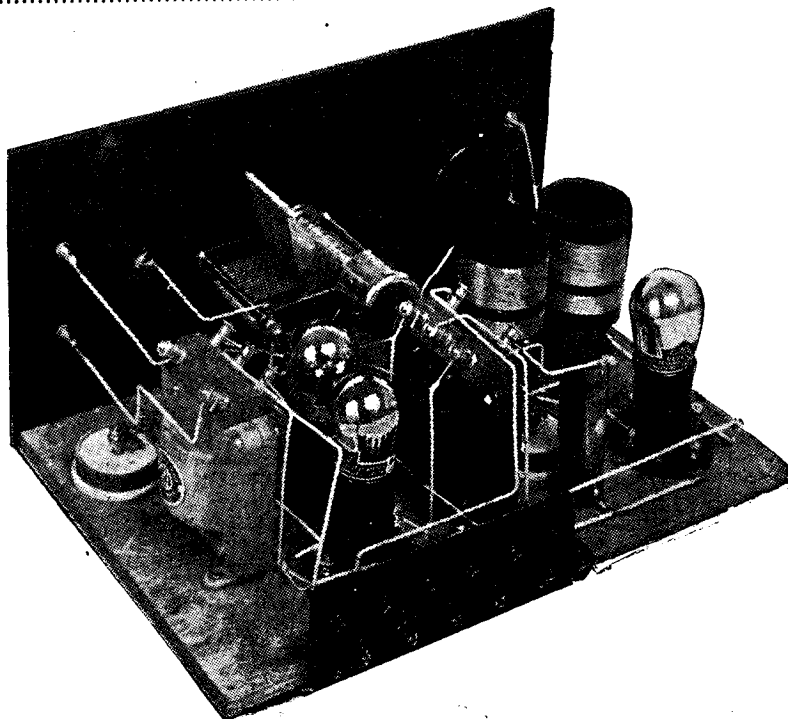

Good results can be obtained with ordinary general purpose valves in the L.F. stages.

slowly in a clockwise direction until the receiver is just off oscillation. Should the set show no inclination to oscillate when the reaction condenser is turned, turn the grid leak knob either one way or the other

Keeping the H.T. + 2 terminal connected to a suitable tapping on the H.T. battery, tune in the local station to its loudest volume once more and adjust the grid voltage until signals are pure and

WIRING INSTRUCTIONS

Join one side of R_2 to contact 1 of S ; contact 1 of S to terminal 4 of L_2 ; terminal 4 of L_2 to one side of R_1 and terminal 5 of L_2 .

Join contact 2 of S to $LT-$

Join G of V_3 to one "Grid" terminal of T_2 .

Join remaining side of R_2 to $F-$ of V_2 and $F-$ of V_3 .

Join remaining side of R_1 to $F-$ of V_1 .

Join $F+$ of V_3 to $F+$ of V_2 ; $F+$ of V_2 to $LT+$; $LT+$ to $HT-$ and $F+$ of V_1 ; $F+$ of V_1 to one side of R_3 .

Join earth to terminal 2 of L_1 .

Join aerial to terminal 1 of L_1 .

Join remaining side of R_3 to one side of C_3 ; same side of C_3 to G of V_1 .

Join terminal 6 of L_2 to remaining side of C_3 , and fixed plates of C_1 .

Join A of V_1 to one side of L_3 ; same side of L_3 to fixed plates of C_2 .

Join terminal 3 of L_2 to moving plates of C_1 ; moving plates of C_1 to moving plates of C_2 .

Join remaining terminal of L_3 to "Anode" terminal of T_1 .

Join centre terminal of T_2 to $GB-$.

Join "HT+" terminal of T_1 to $HT+1$.

Join remaining "Grid" terminal of T_2 to G of V_2 .

Join A of V_2 to one "Anode" terminal of T_3 .

Join A of V_3 to other "Anode" terminal of T_3 .

Join one side of T_4 to one loud-speaker terminal.


Join other loud-speaker terminal to remaining side of T_4 . Join $HT+$ of T_3 to $HT+2$



HEAD OF RADIO PRESS RETIRES

*Mr. Scott-Taggart's Decision
to Enter Valve Business*

Will Probably Continue to Write

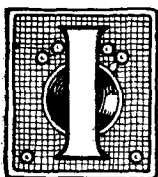

It will, no doubt, come as a great surprise to readers of MODERN WIRELESS to hear that Mr. John Scott Taggart, F.Inst.P. A.M.I.E.E., the founder and head of the great Radio Press organisation, has retired in order to enter the valve business.

To those who know him the step which he has now taken is not altogether surprising. His whole technical life has been devoted to a study of the manufacture and use of the valve. Behind the scenes he has done a great deal to assist the radio industry and valve industry,

and it is only logical for him to market a series of valves bearing his name, which will carry with them a reputation which has always belonged to one who has devoted the whole of his interest to this section of radio.

It is probably news to a large number of readers of MODERN WIRELESS that Mr. John Scott-Taggart has already been a valve manufacturer. The present time is an appropriate one to know what must be one of the most interesting and unusual careers.


Early Days

Before the war, Mr. Scott-Taggart was a keen amateur, and 13

years ago he was writing articles, although only at school. He had one of the relatively few transmitting stations in those days, and possessed the call sign LUX.

During the war, Mr. John Scott-Taggart served from 1914 to 1919, first in the Seaforth Highlanders, and later in the Royal Engineers. Enlisting as a private, he was rapidly promoted to Sergeant-Instructor of Signalling.

He was later promoted in the field to commissioned rank, and was first in the results of every examination on valves held at the General Headquarters in France.

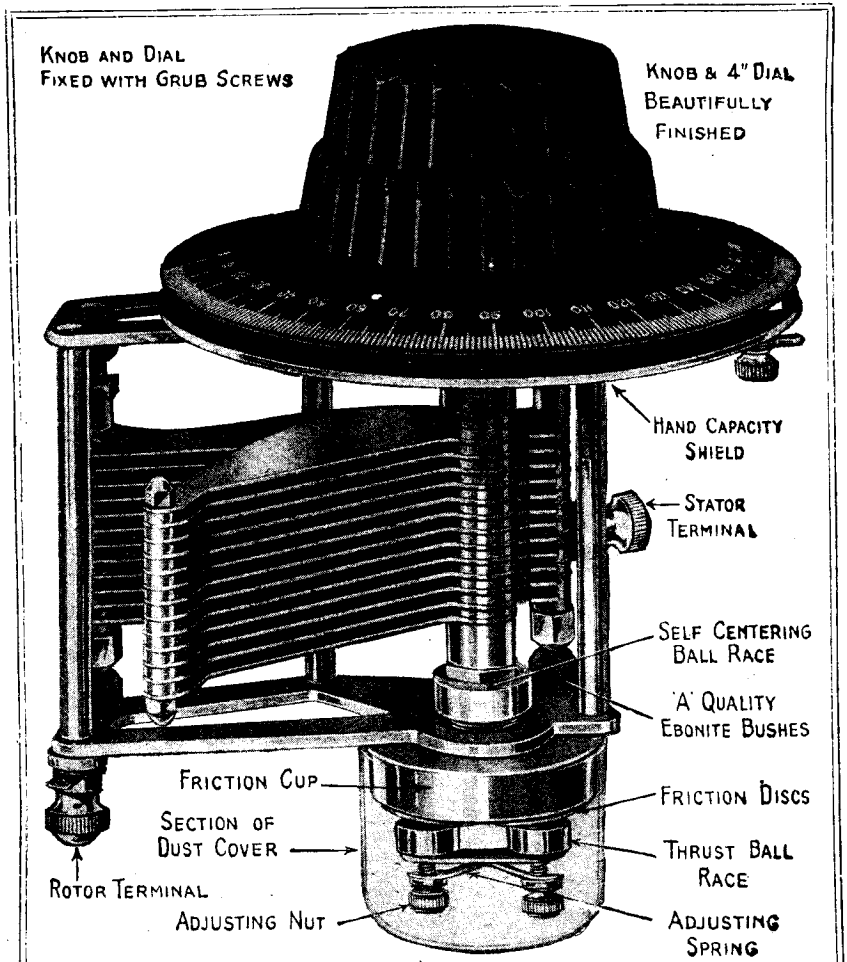

(RATIO 55-1)

PATENT APPLIED FOR

**This is the World-Famous Ormond S.L.F. Condenser
HERE IS YOUR FINAL CHOICE
OF A CONDENSER—BUY IT NOW!**



**199-205 PENTONVILLE ROAD, KING'S CROSS
LONDON, N.1.**

Telephone . Clerkenwell 9344-5-6

Telegrams : "Ormondengi, Kinross"

FACTORIES: WHISKIN ST. AND HARDWICK ST., CLERKENWELL, E.C.1

Continental Agents:

Messrs. PETTIGREW & MERRIMAN Ltd., "Phonos House," 2 and 4, Bucknall Street, New Oxford Street, W.C.1.

ORMOND S.L.F. CONDENSERS

RATIO - 55-1

The Ormond S.L.F. Condenser is by far the best Condenser to use, and the markings on the dial enable you to pick up any station with the minimum of trouble and without any unnecessary calculations. Precise tuning adjustments with noiseless operation are ensured by the general sound construction of this newest ORMOND product. The famous ORMOND SLOW MOTION FRICTION DRIVE (Ratio 55-1) is incorporated and special ball bearings give liquid-like movement to every turn of the knob. This world-famous ORMOND component is easy to mount, having one and three holes for fixing, with both terminals and soldering tags for connections. If you have not yet received a copy of the new Ormond catalogue, write for one to-day.

EXTRAORDINARILY LOW PRICES

**Prices : With 4 inch
Bakelite Knob :**

.0005 microfarad	-	20/-
.00035 ,,	-	19/6
.00025 ,,	-	19/-

**Prices : With Dual
Indicator Dial :**


.0005 microfarad	-	21/6
.00035 ,,	-	21/-
.00025 ,,	-	20/6

Ormond S.L.F. Condensers are obtainable from all dealers.

Orders can now be taken for the ORMOND TRI-GANG CONDENSER eminently suitable for the Elstree Solodyre Receiver. Price £2, complete with anti-capacity shield, knob and dial.

THE ORMOND S.L.F. ENABLES YOU TO PICK UP STATIONS WITHOUT CALCULATIONS

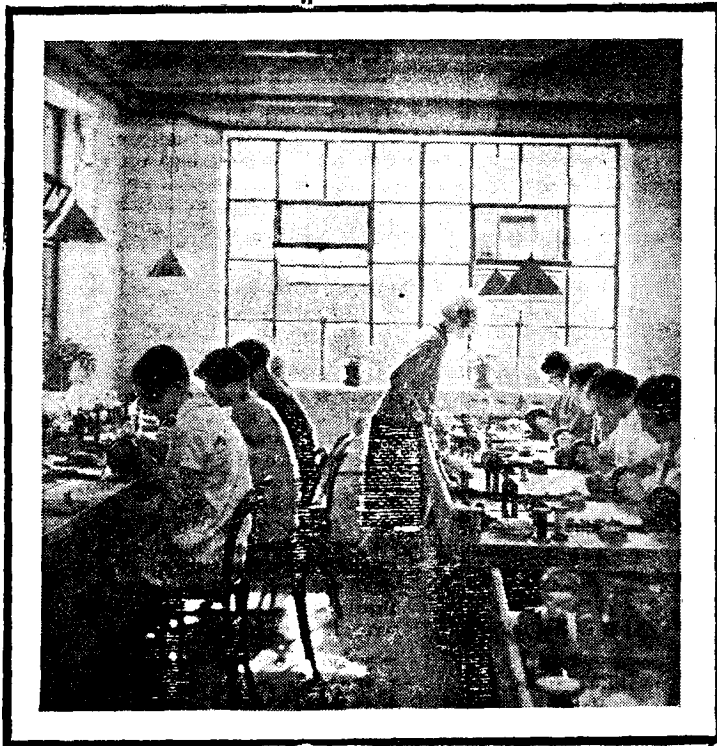Tell the Advertiser you saw it in "MODERN WIRELESS."




Type A2
Headphones

Brown A2 Headphones are famous for their astonishing sensitiveness, astounding responsiveness and superior tone. Many crystal users have obtained a large increase in volume by their use, while valve users in many countries prefer them for long distance reception. **30/-**
In resistance of 2,000 ohms.

The World's Ears in the making

LONG before Broadcasting was ever thought of in England, the name **Brown** was indubitably bound up with Wireless Headphones. On the high seas, ships' operators relied upon them to receive vital messages; on the fields of war, when thousands of precious lives depended upon messages going through, the army put their faith in **Brown A** type 'phones; the Navy, many other Government services, and the World's Cable Companies—all have for long chosen the **Brown** as the supremely sensitive and utterly dependable Headphone.

What better recommendation could you desire than the faith so many vital Services have placed in the **Brown**? Whether you buy the famous original **A**-type, the new **A2** (unequalled anywhere at thirtyshillings) or the popular Featherweights, you know you are getting a headphone constructed on the same unique **Brown** principals, with the same **Brown** high standard of manufacture, and which, you can be sure, will give the same **Brown** incomparable service. Don't ask for Headphones—follow the experts' choice and say "**Brown**."

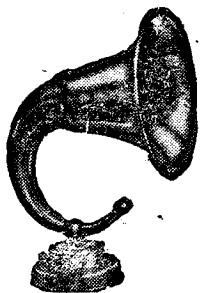

Brown H.Q. Loud Speaker
—one of the range of nine,
from 30/- to £15 15s.

Brown

S. G. BROWN, LTD., Western Avenue, North Acton, W. 3.

Retail Showrooms: 19, Mortimer Street, W. 1.; 15, Moorfields, Liverpool; 67, High Street Southampton.
Wholesale Depots:—2, Lansdowne Place, West Bath; 120, Wellington Street, Glasgow; 5-7, Godwin St., Bradford;
Cross House, Westgate Road, Newcastle; Howard S. Cooke & Co., 59, Caroline St., Birmingham;
N. Ireland: Robert Garmany, Union Chambers, Union St., Belfast.

Gilbert Ad. 6055

HEAD OF RADIO PRESS RETIRES—(Continued)

Pioneer Work on Valves

As a wireless officer in the Royal Engineers, he took part in fighting on Vimy Ridge in April, 1917, and was one of the very first to use valve transmitters in warfare. Later in the year, he became an Instructor at the 1st Army Signal School, giving courses of lectures on the

of the division were broken by shell fire, and the direction of operations was carried out entirely by the wireless system, which extended to the front line trenches. For work on this occasion, Mr. John Scott-Taggart was mentioned in despatches.

The part played by wireless in

experimental work during rest periods. He also continued to write articles for the technical Press, which disclosed for the first time the great usefulness of the three-electrode valve. Professor Fleming, in his book on the valve, quoted large extracts from these articles, and in his Preface paid a very generous tribute to the original author.

During this period, Mr. Scott-Taggart developed a valve attachment for trench work which eliminated the high-tension battery, and at the time of the Armistice, according to the statement of Colonel Trew, who was the officer in charge of wireless of the B.E.F., this valve attachment was to be fitted to all trench sets.

A Standard Text Book

Immediately after the war, Mr. John Scott-Taggart completed a book entitled "Thermionic Tubes in Radio Telegraphy and Telephony." It is, to-day, the standard text-book on the valve, and is easily the largest book on the subject.

In 1919, Mr. Scott-Taggart took charge of valve manufacture at the lamp works of The Edison Swan Electric Company, Limited. His work was principally the manufacture of different types of valves for the Government, and in view of



The training of Army wireless operators is carried out on up-to-date valve apparatus

valve. Although he had been engaged in active service, Mr. Scott-Taggart had written articles for *The Wireless World* in 1917, and later in the year he wrote the first article dealing in a comprehensive manner with the characteristic curves of valves. This article was entitled, "On Characteristic Curves and their Use in Radio Telegraphy and Telephony," and was also published in *The Wireless World*.

Although investigators in the services had, no doubt, similar information, Mr. Scott-Taggart had to investigate the whole question of characteristic curves from the beginning, and carried out a very laborious set of measurements, which formed the basis of what is one of the first real published analyses of "families" of valve curves.

Wireless Proves Its Worth

At the beginning of 1918, Mr. John Scott-Taggart joined the 55th Division, just before the battles of Festubert and Givenchy, in the La Bassée sector. On April 9, 1918, a fierce attack was made along the whole British front, and due to a flanking movement the original site of the 55th divisional headquarters was actually captured while the front remained substantially unaltered.

The whole of the communications

this division may be judged from the fact that the wireless section under his command possessed the highest percentage of decorations for gallantry of any wireless section in the British Army. Later in the year, during the final fighting, Mr. John Scott-Taggart was awarded the Military Cross for "gallantry

Without valves the production of the compact transmitter and receiver shown would have been virtually impossible.



in maintaining wireless communications under fire."

Continuous Experiment

Although not enjoying the advantages of a more sheltered technical post, Mr. John Scott-Taggart maintained the closest technical interest in valve work, and carried out much

the very strict specifications and the fact that every valve was rigidly tested by the Government Departments concerned, it proved an excellent training in a particularly difficult process of manufacture. It is interesting to note that the first valves specifically designed for amateur use were designed by Mr.

HEAD OF RADIO PRESS RETIRES—(Concluded)

Scott-Taggart, and were called E.S.₂ and E.S.₄ valves. These were different from the standard service type of valve which was then the only one readily available to the British public.

Wide Experience

Mr. Scott-Taggart left the Edison Swan works to join the Radio Communication Co., Ltd., which, as readers may know, carries on a big business in ship wireless installations with activities in this country as regards general wireless work which are only second to the Marconi Co. Mr. Scott-Taggart became head of the department dealing with inventions and patents, and was second in seniority to the chief engineer.

He held this position for several years, and during this time acted as patent adviser to the Mullard Radio Valve Co., and in fact prepared the original defence in the patent law-suit which that company had with the Marconi Co., which finally resulted in the House of Lords' decision for the Mullard Co.

The Negatron

It was during his stay with the Radio Communication Co. that Mr. Scott-Taggart's invention, the Negatron valve, was adopted for use in continuous wave reception on dozens of liners, which to-day receive their news bulletins on this ingenious valve which gives a negative resistance effect. This valve, like many of Mr. Scott-Taggart's principal inventions, has no application to broadcasting, but has valuable uses in "commercial" wireless.

Distinctions

Mr. Scott-Taggart is a Fellow of the Institute of Physics, and at the time of his election was the youngest to have achieved that distinction, which is one of the highest professional diplomas in physics. He is also an Associate Member of the Institution of Electrical Engineers, besides holding similar membership in the French, Belgian and American Institutions of Electrical Engineers. Many of his writings, including text-books on the valve, have been published in foreign countries, and he is an honorary member of the German Radio Society.

Mr. Scott-Taggart has lectured



The development of short wave technique allows of the use of small portable aeriols.

before the British Association, and at one time devoted considerable attention to the fostering of the Radio Society movement. He was a member of the Council of the Radio Society of Great Britain, and president of several Radio Societies.

Radio Press, Limited

In 1922, Mr. Scott-Taggart established Radio Press, Ltd., as a radio publishing organisation, and has built up the business to its present successful state. Those who have worked with him have been greatly influenced by his enthusiastic aim at technical accuracy in the articles and efficiency in the receiver designs published.

The slightest error in one of his papers has always been followed by what has almost amounted to a court of inquiry to see exactly how the error arose. With regard to the receiver designs, he leaves behind a tradition of seeing that every set is put to exhaustive test and reaches a very high standard before a description is published.

Founding Elstree

It is partly in this account that he conceived the idea, most unusual for a publishing firm, of establishing special laboratories, where apparatus could be put through

exhaustive tests and new ideas and designs tried out. The result was the Elstree Laboratories. Mr. Scott-Taggart has amply justified his views on the sound design of receiving apparatus by the production of such receivers as the "Elstree Six," "Solodyne," "Elstreflex," "Magic Five," and other leading designs emanating from the Elstree Laboratories.

The New Company

It is not illogical that Mr. Scott-Taggart should desire to enter the valve business. He possesses all the necessary qualifications for success in this branch of work. We feel convinced that he would not have taken this step unless he were wholeheartedly confident of the product his company is to produce. He is probably the only person in this country who has acquired a wide reputation as an expert on the use of valves as well as their manufacture. The average valve maker is rather inclined to look upon a valve as a form of lamp, and rather to ignore the suiting of the valve to the circuit in which it is to be employed. The use of proper valves for certain purposes is a comparatively recent development, and no doubt Mr. Scott-Taggart's unique experience of modern receiver designs will be an important factor in his new activities.

The Future

On the technical side of Radio Press, Ltd., there are able engineers who will take Mr. Scott-Taggart's place, and the existing traditions will be carried on exactly as before. We have made arrangements whereby we shall from time to time publish articles from Mr. Scott-Taggart's pen, and we are sure that readers will join with us in wishing him every success in his new sphere of activities.


A New Appointment

Some twelve months ago Mr. Scott-Taggart resigned the managing directorship of Radio Press, Ltd., so the actual management of the business remains, as heretofore, in the hands of Mr. Robert A. Lodge, A.S.A.A. Mr. J. H. Reyner, B.Sc., A.M.I.E.E., has been appointed technical manager of the company—an appointment which, we feel sure, will meet with satisfaction in every quarter.



*A Name to Conjure
with in the world
of Broadcasting*

HART BATTERIES

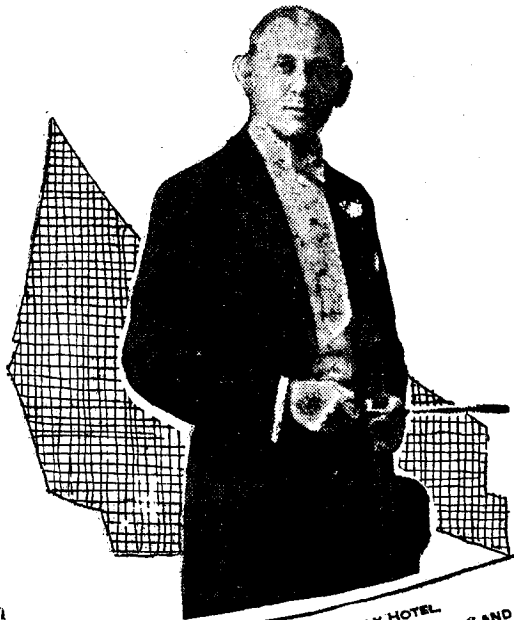

ENSURE
*A marked increase in Volume
of tone & freedom from distortion*

says- '**DE GROOT**'
THE FAMOUS VIOLINIST OF THE
PICCADILLY HOTEL

There are models of "HART"
BATTERIES for all wireless
circuits. Write to-day to
Department M. W. 3. for
illustrated leaflets and full
particulars.

WE ARE EXHIBITING AT THE MAN-
CHESTER WIRELESS EXHIBITION
OCT. 26 TO NOV. 6, STAND No. 42.

THE PICCADILLY HOTEL,
PICCADILLY AND REGENT STREET,
LONDON, W. 1.

Messrs. Hart Accumulator Co. Ltd.,
Stratford, E. 15.

Dear Sirs,
I have been immensely pleased with the very excellent
results of substituting a "HART" High Tension Accumulator for the
dry battery previously in use with my wireless set. The reception
generally has been tremendously improved, whilst I have also
noticed a marked increase of volume of tone and freedom from
distortion, which, in the case particularly of delicately phrased
musical items, is, of course, a pronounced asset to critical
listeners.

I am happy to recommend "HART" High Tension Accumulators
as infinitely superior to dry batteries, the relatively short life
of which, in my opinion, constitutes not the least of their many
disadvantages.

Yours sincerely,
De Groot

July 21st. 1926.

HART

THE BATTERY OF QUALITY

NATIONAL WIRELESS WEEK
NOVEMBER 7-13.
LET YOUR FRIENDS LISTEN

HART ACCUMULATOR CO. LTD. STRATFORD LONDON E.15


Tell the Advertiser you saw it in "MODERN WIRELESS."

LEAVING GRID LEAKS ON OUR FACTORY ROOF TO TEST THEM




A case of LISSEN FIXED GRID LEAKS was left on the roof of the LISSEN factory during the summer of 1925—they were soaked by rain, they were baked by the sun—then they were handed over to the LISSEN research department, and carefully tested—in every grid leak the resistance was found unchanged and true to the marked value.

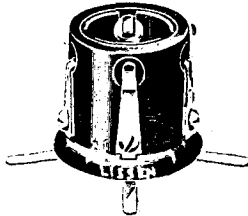All capacities, previously 1/8, NOW 1/- each.



DOUBLE PURPOSE VALVE HOLDER.

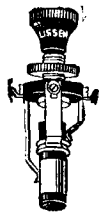Can also be used for panel mounting by bending the springs straight—low loss, low capacity, meaning better, clearer signals. LISSEN VALVE HOLDER, previously 1/8, NOW 1/- each.




REAL RADIO SWITCHES.

There is a LISSEN switch for every radio switching need. Your dealer has them all, or if any difficulty send direct.

- LISSEN 2-way switch, previously 2/9, NOW 1/6.
- Series-parallel switch, previously 3/9, NOW 2/6.
- Double Pole Double Throw, previously 4/-, NOW 2/6.
- Key Switch, previously 2/6, NOW 1/6.

LISSEN
SERIES-
PARALLEL
SWITCH

WON'T WARP, TWIST, BEND OR BREAK.

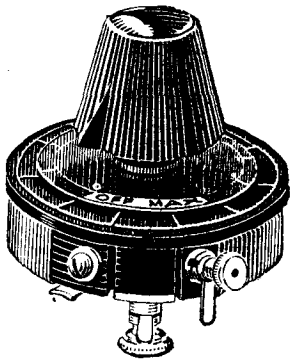

No chance of this with a LISSEN wire-wound rheostat or potentiometer—no shorted turns—no development of faults in use—no chance of arcing, noise or flickering. And every contact brush of every LISSEN wire-wound rheostat and potentiometer moves with firm and positive action along the wire, yet never harshly.

PREVIOUSLY HIGH-PRICED but now largely reduced because of our new direct-to-dealer policy which cuts out wholesale profits.

NOW 2/6

LISSEN 7 ohms wire rheostat, patented, previously 4/-.
LISSEN 34 ohms wire rheostat, patented, previously 4/-, NOW 2/6

- LISSEN Dual wire rheostat, patented, previously 6/-, NOW 4/6
- LISSEN POTENTIOMETER, 400 ohms, previously 4/6, NOW 2/6

EVERY ONE LISSEN ONE-HOLE FIXING, TOO. Insist on seeing a LISSEN before you buy any other.

IMPORTANT TO THE TRADE.

Retailers who have not already been notified of our new direct-from-factory-to-dealer distributing policy should in their own interests communicate with us without delay. All orders must now be sent to us at Richmond and not to usual factor.

LISSEN LIMITED, Lissenium Works,
20-24, FRIARS LANE, RICHMOND, SURREY.

Managing Director: T. N. COLE. L 80

A Musical Authority on A Musical Instrument

MR. JOHN ANSELL, the well-known Musician and Conductor of the Wireless Symphony Orchestra, writes:—

Gentlemen,

I am, frankly, delighted with my Curtis Double Circuit Super-Het. 8, incorporating the Curtis Cabinet Loud Speaker.

As a conductor and critical musician, possibly I expect more from a wireless receiving set than the average listener. It may interest you, therefore, to have my assurance that the volume and clarity of tone are indeed a revelation to me, whilst the wonderful selectivity of your Curtis set is proving most valuable.

The taste and exquisite finish of your "Windsor" cabinet model have already evoked the admiration of my many musical friends.


As advised by you I am using Hart Accumulators for both my Low and High Tension Supply, and these are functioning admirably.

Yours faithfully,

(Signed) JOHN ANSELL.

Then, for
"A Revelation in volume and clarity of tone . . ."

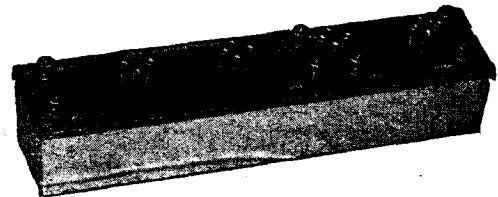BUILD YOUR OWN CURTIS DOUBLE SUPER-HET 8 WITH



The Curtis Intermediate Unit

A complete component, consisting of the Intermediate Frequency and Filter transformers with corresponding valve sockets and accessories wired up, mounted in box and tested ready for use in any Supersonic circuit as a single unit.

HOME CONSTRUCTORS' TREATISE, 2s. 6d., containing Circuit diagram; 2, simplified layout and wiring charts; 3, Instructions for operation; 5, complete schedule of components.

GENUINE CURTIS PRODUCTS ALONE CAN GUARANTEE

That Perfect Quality of Reproduction with our unique system of
SERVICE AFTER PURCHASE.

PETER CURTIS, LTD.,
11, RED LION SQUARE, LONDON, W.C.1

Phone: Chancery 7543. Telegrams: "Paracurtis, Holb."
MANCHESTER - - 312, DEANS GATE.

THE "ELSTREE SIX"

Further hints on operation together with some notes upon suitable alternative components which have been tried at Elstree.



NUMBER of enquiries have been received from readers regarding the low-frequency side of the "Elstree Six" circuit. In some cases readers do not wish to utilise two low-frequency stages, but would be content with only one, or perhaps none. Others have enquired whether the use of low-frequency transformers specified is of any great moment.

As a matter of fact the low-frequency side of this receiver is absolutely straightforward and does not affect the operation of the high-frequency side to any extent. Those readers who wish to utilise other transformers in place of those specified may do so without any detriment to the operation of the receiver, provided that the transformers actually employed are of a reasonable standard of efficiency.

Alternative Transformers

One or two alternative transformers have been tried in the circuit. Two Ferranti A.F.3 transformers operate very satisfactorily. It is sometimes found that there is a tendency to whistle, but if this is the case, a leak of .25 megohms placed across the secondary of the second transformer will overcome this difficulty. Eureka transformers have also been employed in the circuit quite as successfully, while the well-known multi-ratio transformers made by Messrs. Radio Instruments provide a very useful combination in that the suitable tapping for the particular valve in use may readily be chosen.

These transformers are only a few of the suitable alternatives, and the fact that any particular transformer is not mentioned in this list does not preclude its use in the "Elstree Six." As has been previously stated, provided the transformer is of a suitable ratio

and of sufficiently high standard it can be used quite satisfactorily.

Wavelength Ranges

Many readers have queried the apparent discrepancy between the results obtainable on the lower wavelength range, and that of the Daventry waveband. On the lower range the axis of the Dimic coils and the plug-in primary are approximately the same. Using the long range Dimics, however, with a standard form of plug-in primary, this is no longer the case, and in fact coupling between the two is somewhat weaker than is desirable.

This results in a certain weakening in the signal strength on the higher range, but this may be overcome by either raising the long-

same, and they should be so connected that the direction is the same as on the standard plug-in coils.

The "Unimic" Coil

Messrs. McMichael have recently produced an interesting coupling unit specially designed to replace the plug-in primary which was used in the original model. These coils, which are known as "Unimic" coils, consist of a small coil arranged to fit into a special form of rocking holder. By this means the actual degree of coupling between primary and secondary may to some extent be varied if it is found desirable.

For the shorter waves these coils consist of a short length of flanged tube similar to that on which the Dimic coils themselves are wound, carrying a single layer winding, while for the longer range the Unimic coil is similar to one-half of the Dimic coil for the particular range specified. By means of the mountings provided it is possible to maintain the axis of the primary and secondary coils the same both for short wave and the long wave coils.


Actually the winding is so designed that there is no danger of resonance between the primary and one-half of the secondary winding, the numbers of

turns being suitably proportioned to avoid any effect of this at all. Unless this is done there is a danger of trouble due to unexpected oscillation in the circuit.

Dual Condensers

We have received other makes of dual condensers which may be used satisfactorily in the "Elstree Six" circuit. Messrs. Ormond Eng. Co. have produced a dual model of their well-known instrument which is quite suitable in this circuit, and Messrs. Burne-Jones have also submitted a dual condenser which has given satisfactory results.

The use of the specified H.F.

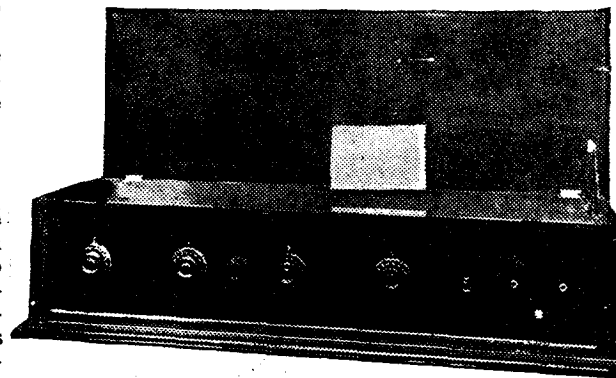

The "Elstree Six" receiver was described in the June issue of this journal.

wave Dimic coils on extension pieces, so that the axis of these coils come into line with the axis of the plug-in primaries. Alternatively a much smaller plug-in primary coil may be used. Again, the primary coil may be of a very much smaller diameter, wound if necessary with a much finer wire. Home-made hank-wound coils may be utilised, such coils having about 300 turns wound on a 1 in. diameter former. If these coils are then fitted with standard two-pin plugs they will be found to constitute quite satisfactory primaries for the longer range. Care should be taken to keep the direction of the windings of the primary coils all the

FURTHER HINTS ON THE "ELSTREE SIX"—(Concluded)

chokè is not essential, and any of the various makes of high-frequency chokes now on the market may be employed in the circuit provided they are of adequate quality. The same remarks apply to the potentiometer, for which any well-made component will suffice.

Resistances

We have recently tried a set of four Mullard wire-wound resistances in the "Elstree Six" with entirely satisfactory results. The same remarks apply to the Dubilier wire-wound resistance, so that either of these two components may be used as suitable alternatives to the Varley resistances which were originally specified.

Filament Switching

Several readers have enquired as to whether it would not be possible to incorporate a filament switching jack in the last stage, so that the last valve may be cut out of circuit when not in use. This course is quite feasible, and in fact has been done in many cases with entirely satisfactory results. Since the last valve is provided with a separate filament resistor, no difficulty is experienced when this valve is cut in or out of circuit.

Fixed Resistors

In this connection the use of fixed resistances in the "Elstree Six" may be discussed. The original circuit included Amperites, which are a form of automatic resistance. They pass substantially the same current irrespective of any variation in the voltage of the accumulator within certain limits. The valve therefore passes its true current irrespective of the condition of the accumulator.

If fixed resistors are used then the adjustment of the filament current is automatic, only as long as the voltage of the accumulator remains at 2 volts per cell, when the valve will carry its correct current. The voltage of an accumulator, however, does not vary considerably in use, and for most practical purposes a fixed resistor is perfectly satis-

factory. The modern valve is sufficiently flexible to give quite satisfactory results over a fairly wide range of filament currents. The use of fixed resistors, therefore, in the majority of cases is quite permissible, and no loss of efficiency will be occasioned by their use.

H.F. Transformers

There is one point which has perhaps not been sufficiently emphasised in connection with the

Primary Coils

The arrangement therefore is very flexible, and the reader can suit himself as to the particular combination he uses. When endeavouring to receive stations operating very close in wavelength to the local station the coils in the primaries should be reduced in size until the requisite selectivity is obtained. If, on the other hand, it is desired to increase the strength of a distant station which is not coming through as well as is desired, then the size of the primary coils should be somewhat increased.

When receiving stations close to the local station in wavelength something must be sacrificed, either signal strength or selectivity, but once a little experience is gained in the handling of the receiver, the flexibility obtained by this interchangeability will then become appreciated. It is often found, for example, that the changing of one of the primaries only will make all the difference between satisfactory reception and doubtful signal strength or selectivity.

A Station for nearly Every Degree

Sir,—The results obtained with the "Elstree Six" are far beyond my expectations. For selectivity, distance and pure volume I do not think it will ever be improved upon.


As an example of selectivity, Madrid, Manchester, Bournemouth, Hamburg, Newcastle and Dublin are easily separated, and, for distance, Rome and Berne are a fair test. The neutralising, and tuning are quite simple compared with several smaller sets I have used.

Thanking you for your work in turning out such a fine set.—Yours truly,

W. N. BATES

Congleton.

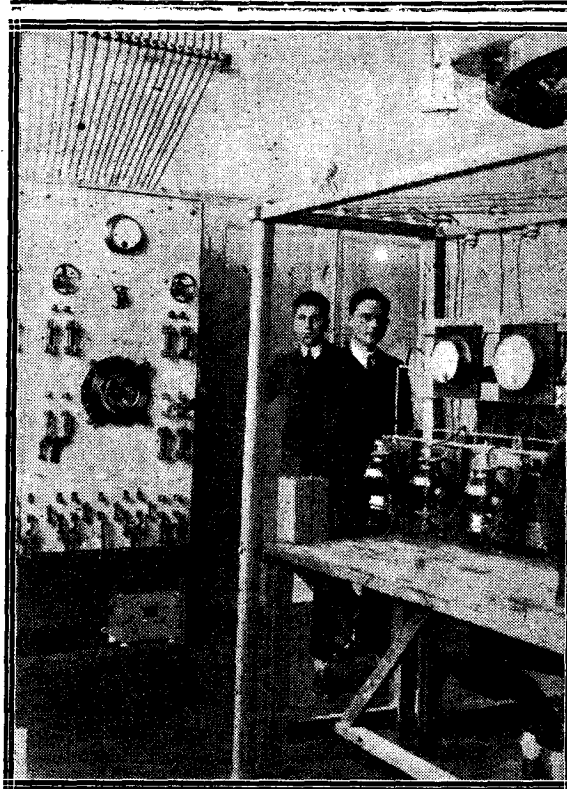P.S.—I have logged a station for nearly every condenser degree between 38 and 118.



A portion of the television laboratories at Maimaison, which are under the direction of Henri Fenal. Some of the transmitting valves may be seen above.

"Elstree Six" circuit, and that is the flexibility which is obtained owing to the fact that the coupling between the primary and secondary of the high-frequency transformers is variable. If the size of the primary winding is increased then the signal strength will also be increased, but at the same time the selectivity will be cut down. Conversely, if an increased selectivity is required, then the size of the coil in the primary may be reduced, and the required selectivity can be obtained at the expense of a certain degree of signal strength.



Distortion—visible or audible ?

WHEN little Willie takes photographs you must have noticed how the buildings often look as if they are falling down. Frequently this is due to the distortion caused by the use of an inferior and uncorrected lens. It is distortion made visible to the eye. But every wireless enthusiast knows the distortion which comes from the use of uncorrected L.F. Transformers. Just as an anastigmatic lens is scientifically corrected against distortion of every kind and is guaranteed to give a faithful

image, so a Eureka Transformer is scientifically corrected and guaranteed to give faithful reproduction. It is a matter of precise mathematics and expert knowledge. The Eureka stands in a class by itself. It has no laminated core and its improved method of "stratum-winding" ensures greater volume with an even amplification of all frequencies. Again and again has it been proved to be the one L.F. Transformer which really "re-creates the living Artiste."



Eureka Concert Grand

A superb L.F. Transformer hermetically enclosed in a coppered steel case proof against atmospheric influences. For second stage use there is the No. 2 which is designed for work in perfect partnership with the Concert Grand. Designed under identical principles.

Concert Grand 25/- No. 2 21/-

Eureka Reflex

For reflex work a special Eureka is available. Gives an exceptional volume of mellow clear tone. Fully guaranteed 15/-


Eureka Baby Grand

For those who cannot afford the necessary higher price of the larger Concert Grand we have introduced the Baby Grand. Fully up to the same high standards of workmanship and carrying the same generous guarantee. Chosen by many manufacturers of Broadcast Receivers.

No. 1 15/- No. 2 15/-

Eureka L.F. Choke Unit

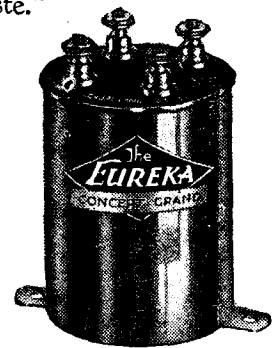The L.F. Choke method of amplification is gaining in popular favour among seasoned experimenters. The Eureka Choke Unit, incorporating grid leak and condenser is the finest instrument of its type. Fully guaranteed 25/-





Portable Utilities Co., Ltd., Fisher St., W.C.1.

Sole Manufacturers of Eureka Radio Products

Re-creates the **EUREKA** Living Artiste

Gilbert Ad. 6966

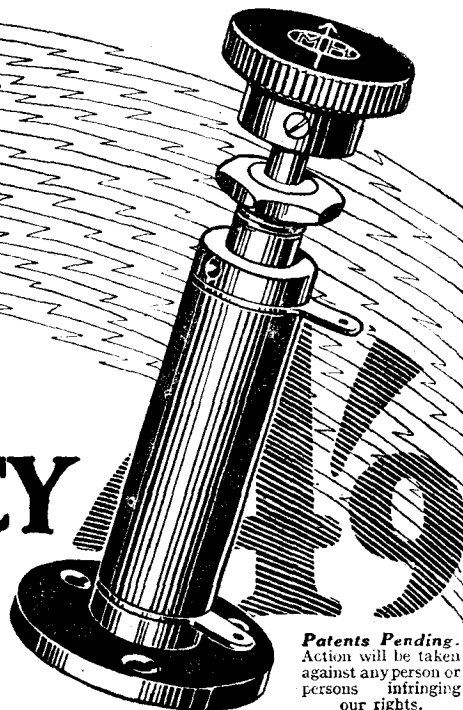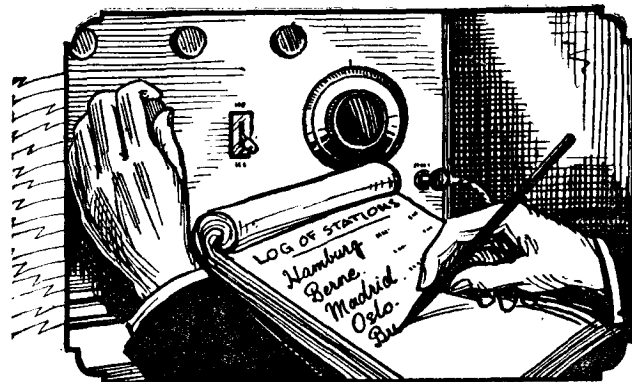Tell the Advertiser you saw it in "MODERN WIRELESS."



Patents Pending.
Action will be taken
against any person or
persons infringing
our rights.

The Secret of H.F. EFFICIENCY

THE success achieved by the Radio Press designs at the "Radio Wor d's Fair" held in New York in Sept. 1926 (open to all comers) is now common knowledge. The Mewflex, one of the winning designs at New York, includes in the specification the **MH** Balancing Condenser.

The secret of H.F. Efficiency is correct balancing of the valve capacities. The unique design of the **MH** Balancing Condenser incorporates the following advantages in a compact and highly finished unit at a moderate price:—

1. High insulation resistance, so that no losses are added to the circuit.
2. High breakdown voltage, to eliminate risk of burnt out valves and ruined high-tension batteries.
3. Calibration to allow of re-setting to suitable values.
4. Precise adjustment, to enable the critical operation of balancing to be effectively and easily performed.
5. Ease and adaptability in fixing for either baseboard or panel mounting.

PRICE **4/9** EACH.

Demand **MH** Components if you seek efficiency.

BRITISH, BEST AND CHEAPEST IN THE LONG RUN.

MH MICA FIXED CONDENSER

The **MH** Mica Fixed Condenser can make all the difference, whatever the circuit, between a receiver that shows a consistently good performance and one that is as unreliable as the weather. **MH** Condensers are made in all standard capacities and are supplied with or without base or clips.

Prices (in Cartons) Unmounted.
(Two Clips are supplied with each Condenser.)

0.0001 to 0.0009μF(030) 2/6	each
0.001 to 0.01μF(031) 3/-	"
0.015 to 0.02μF(034) 4/-	"

Telephone :
Slough
441-442.

L. M. MICHAEL LTD
Manufacturers of Wireless and Scientific Apparatus
WEXHAM ROAD, SLOUGH, BUCKS

Telegrams :
Radiather,
Slough.

NATIONAL WIRELESS WEEK
Nov. 7th-13th.
Let your Friend Listen.



Pool's Advertising Service, Ltd.

"SOLODYNE" SUCCESSES

Appreciations from readers who have built the well-known Elstree "Solodyne" receiver. Two of them are willing to demonstrate its capabilities to any interested enthusiasts.

Will Demonstrate

SIR,—I am sending you a report on the Elstree "Solodyne," which I have just completed.

The set is certainly all you claim it to be, and I find the dial readings are practically identical to those published by you, and this has been a great advantage in identifying the numerous stations received. I will not enumerate them all as they correspond to the principal stations in your list.

Everything is quite straightforward, and anyone who can use a soldering iron could make it successfully. I find that by removing the fixed resistors of the H.F. valves, and connecting the aerial to P.3 of the triple condenser, the set works as D. and 2LF with reaction, and gives tremendous volume on the local station, and is capable of receiving such stations as Hamburg, Frankfurt and many others on L.S.

I am using Cossor A valves for the first three and P.M.2s for the last two, and am using R.I. multi-ratio transformers. I am limited to an indoor aerial and also have to take the earth wire out of the window and 20 ft. down to the garden, which is not exactly ideal.

Needless to say I am highly delighted with the results obtained both as regards range and volume and great simplicity, and shall be pleased to let anyone interested try it for themselves, if they care to make an appointment.—Yours truly,
F. M. SEARS.

627, Barking Road, E.13.

"Tone Wonderful"


SIR,—I have now got the "Solodyne" working well and I am entirely satisfied with the results I am getting, in fact I consider it is better than the super-het I was using before, although that was very good. I only got it working last Saturday, October 2nd, and I have already logged at least 46 stations, all (most of them good strength) on

the loud-speaker. Of course, some fading badly at times. A lot of other stations are heterodyned, and I am sure it is possible to get the 50 or even more.

The selectivity is very good, and on a good night I can cut out Cardiff (our local station) and get London very loud indeed by using a good deal of reaction and bringing the tone control nearly down to it.

tested out within a mile of 6 LV, who was tuned out *absolutely* when any other station was being received. I cannot speak too highly of the "Solodyne"; the perfect ease of control, and the way one station after another comes rolling in, is nothing short of uncanny. To sum the receiver up, it is the most wonderful I have ever heard, seen, or handled. Please make whatever

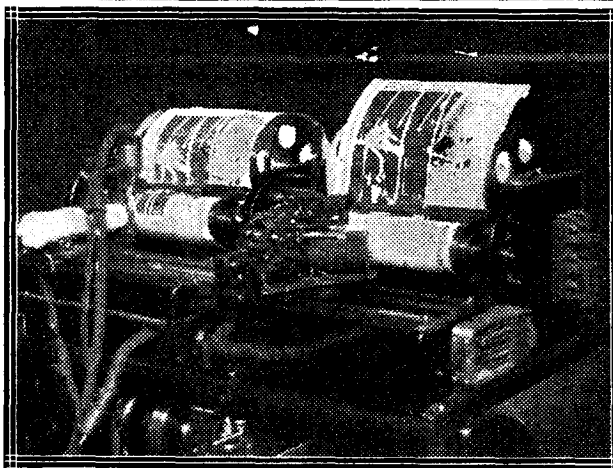Some of the "Photo-radiogram" receiving apparatus at Radio House. This instrument was employed in the reception of the photographs of the Dempsey-Tunney fight.



minimum. The volume is excellent and the tone is absolutely wonderful.

I enclose a list of stations I have received, and where I have put a query it means I have not absolutely identified the station, but have gone by the dial in MODERN WIRELESS, and they are different from any other stations in the list.

If anyone likes to come and hear the set at the address below they are very welcome.—Yours truly,
W. MAURICE BROWN.

8, Trewartha Park,
Weston-super-Mare.

[The list of stations has been omitted owing to the pressure upon our space.—Ed.]

"Uncanny"

SIR,—I am sending you my opinion of the "Solodyne." It was

use you wish of this testimonial. To my mind, it is a receiver everyone should know about.—Yours truly,
Liverpool. D. MELLOR.

LECTURE AT CROYDON.

On the evening of the 18th October, a short lecture and demonstration of the Elstree "Solodyne" were given before the Croydon Wireless Society, under the chairmanship of Mr. Elsdon, at 128A, George Street, Croydon. There was a good attendance and the members present showed great interest in the set. Some of the members had themselves built the "Solodyne" and were glad of the opportunity of obtaining first-hand advice on the handling and adjustment of the set.

TRIUMPH FOR ELSTREE DESIGN

Thirteen-Year-Old Boy's Success at New York Radio Exhibition

"MEWFLEX" WINS SPECIAL CUP

A specially interesting feature of the Great Annual Radio World's Fair at New Madison Square Garden, New York, was the international competition for home constructed sets of all types. The principal class and the only one in which Radio Press readers entered was the multi-valve category (3 or more valves).

Entries were invited from all over the globe, and many sets were sent in by British amateurs, a truly international contest of set builders resulting. The awards were made on a basis of "workmanship, appearance, volume, distance, selectivity and tone," a body of leading American experts, headed by Dr. Alfred Goldsmith, being the judges.

The result has proved to be a triumph for Elstree, and has once again shown the outstanding excellence of Radio Press Star designs. The second prize in the class for competitors under sixteen years of age was won with a "Mewflex" receiver entered by J. A. E. Black, of Mill Hill School, a thirteen-year-old British competitor. This set also won a special cup for general fine workmanship. Below the young prizewinner tells why he decided to make the "Mewflex."



WHEN I decided to make up a set for the International Competition the first question that naturally presented itself was, what set should I construct? Should I build a three-, four-, five- or six-valver? At the time there was

the "Elstree Six" or the "Solodyne," "Magic Five," or some other Star set.

For a three-valve set the "Mewflex" is the best I have ever heard. Prague came in at full loud-speaker strength when London was on. London of course, was faintly audible, but only interfered in the intervals. Over forty stations were logged on this Radio Press set, all coming in at loud-speaker strength. The volume which the set gives on all stations is remarkable for three valves, and London (the local station) is much too loud, but this is beautifully controlled by the volume control, which enables one to bring the local station in with a purity and clarity of tone that speaks well for the design of the receiver.

The lay-out is extremely compact and neat. Although it is a small receiver as regards valves, the circuit makes the number of components necessarily fairly large, but four tuning dials, a

filament switch and the volume control are all the knobs on the panel, and this makes for a very neat appearance.

These are the main reasons for which I chose the "Mewflex." It took me about a week to complete it and test it. All the tests were most satisfactory, and I am firmly of the belief that when conditions for wireless reception become better in the winter

the set will give really great results. Selectivity combined with ease of control make the receiver a pleasure to operate and its economy in valves a boon to all who have to carry their accumulators far to be charged. At first when I tested it I had no reaction, as one of the coils was dud. However, I logged Oslo, Frankfurt (loud-speaker strength), San Sebastian, Milan, Hamburg, London, Birmingham and others, even with that handicap. On the whole the "Mewflex" is a three-valve set of remarkable capabilities, selective, and gives the utmost volume for the number of


valves. When it returns from America I am discarding an efficient five-valve receiver which I now use for the "Mewflex" thus using half the current for H.T. and L.T. and getting better and purer results.

J. A. E. BLACK.



On the right, Master J. A. E. Black, and, left, a "photo-radiogram" as it was received in New York. It was transmitted in response to a cable from the Exhibition authorities.

SIX COUNTRIES ON ONE VALVE!

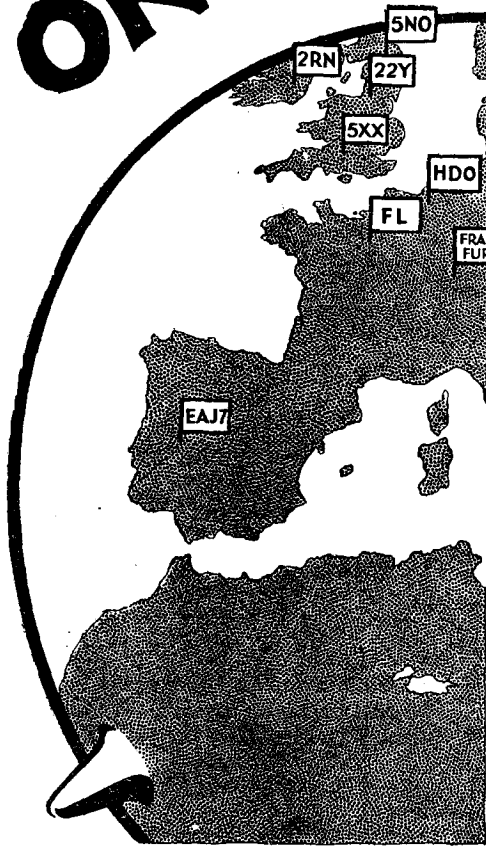

Extract from "Radidea's" article in the "Manchester Evening Chronicle," September 30th, 1926.

"During the week-end I have been testing one of the new BENJAMIN SP. 55 Valves, this being a 6-volt power valve. It has an anode impedance of 3,500 ohms, an amplification factor of 6, with short-path construction and dull-emitter filament.

I used the new reflex unit, which is described in the forthcoming new edition of the "Wireless Guide," and obtained a volume equal to any two-valve set employing a detector and one stage of L.F.

This unit was connected to the new Chronicle Crystal Set, giving full loud-speaker volume from MANCHESTER; in fact, too loud for an ordinary sitting-room. I started off with HILVERSUM on Sunday, tuning in the morning service at 9.45, followed by HAMBURG at 11 a.m. giving a lesson in some other language. FRANKFURT was tuned in at noon, and I listened to a most excellent concert for nearly one hour, and immediately the MANCHESTER Station closed at 6 p.m. I tuned in COPENHAGEN, giving the time signal and chimes.

At the close of the Manchester transmission I tuned in DUBLIN, followed by BRESLAU UNION RADIO, MADRID, and the lady giving the late news from ROME. The church service from NEWCASTLE was heard distinctly and I logged 22 amateur transmitters during the day.

DAVENTRY was at good loud-speaker strength, and the transmission from PARIS, Eiffel Tower, was good 'phone strength.

As I pointed out a few weeks ago, this type of valve is

the finest in the world for a reflex set, giving full volume with a beautiful quality."


- S.P. 18 RED - 14/- Fil. Volts 1.6, Amps. '3
- S.P. 18 GREEN 14/- Fil. Volts 1.6, Amps. '3
- S.P. 18 BLUE- 14/- Fil. Volts 1.6, Amps. '09
- D.E. 55 - - 18/6 Fil. Volts 3.5, Amps. '09
- S.P. 55 BLUE- 18/6 Fil. Volts 5.5, Amps. '09
- S.P. 55 RED - 22/6 Fil. Volts 5.5, Amps. '25

THE BENJAMIN ELECTRIC LTD.,
Brantwood Works, Tottenham, London, N.17

BENJAMIN VALVES (SHORTPATH)



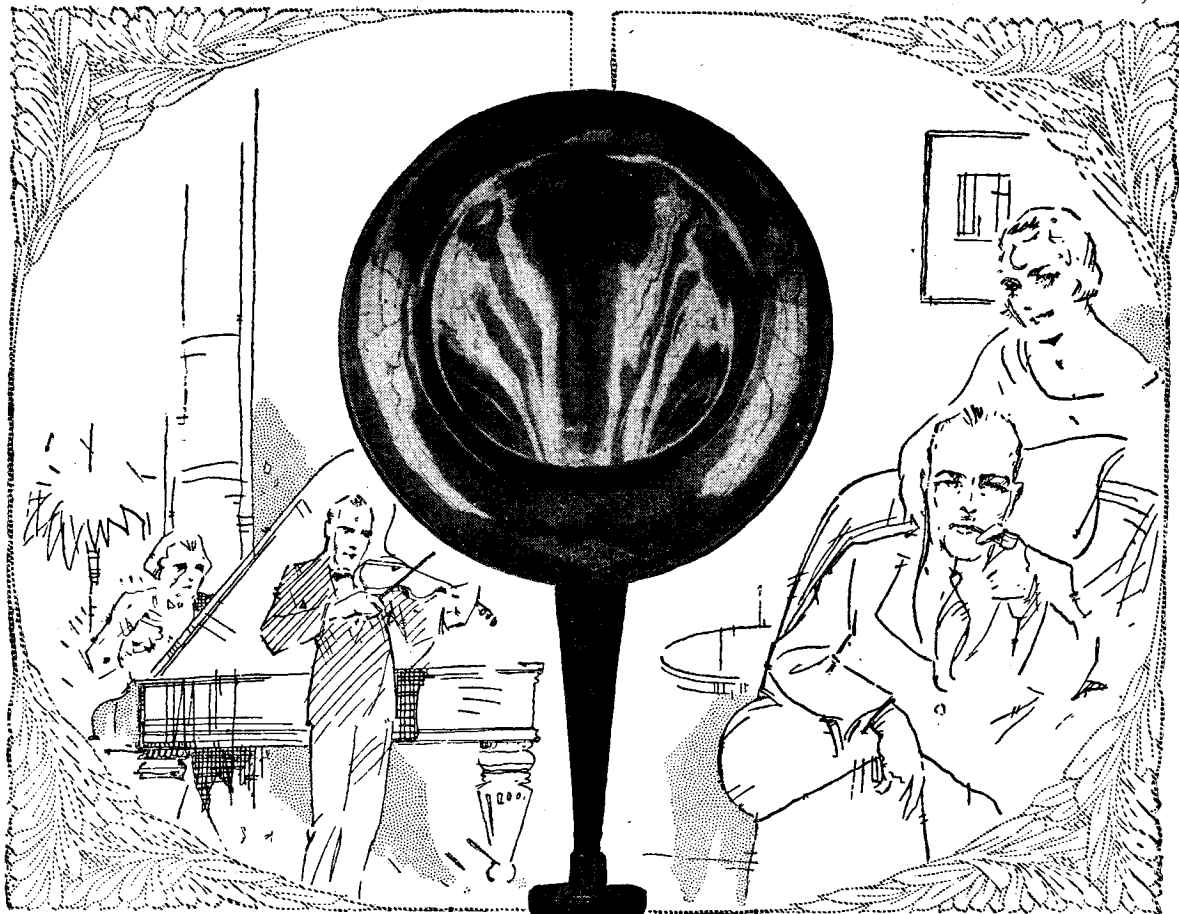Tell the Advertiser you saw it in "MODERN WIRELESS."




GOLDEN HARMONY

CLEAR at a whisper—clear at the heavy volume of a brass band . . . the "Concert Grand" brings a wealth of mellowness, and faithfully reproduces the sounds originated in the broadcasting studio.

The instrument is unequalled for its freedom from "throaty" noises, because the copper used in the construction of the horn is in a natural, unstressed state

and its frequency of vibration is out of range of that of any note which the loud speaker may be called upon to reproduce. It gives that full richness which only copper can give.

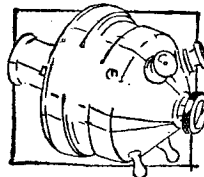The magnetic system—a vitally important part of every loud speaker—is the result of much study and experimental work. Your dealer will supply you. **Price - £5 : 10 : 0**



THE "GRAMO-SPEAKER."

The "Gramo-speaker" is a little brother to the "Concert Grand." In a moment it will turn your Gramophone into a splendid loud speaker, or it can be fitted to home made or purchased horns of ordinary design. It makes a most useful extra loud speaker at a nominal price, for your nursery or for entertaining your domestic staff. It is not an adapted "Earpiece" with the diaphragm held in place by a screw-on cap, ready to loosen through its own vibration. It is a real loud speaker unit with an adjustable magnetic system (loud speaker size) fitted with permanent magnets of cobalt steel and a diaphragm firmly clamped between ground metal surfaces. For performance, finish and price it is the best of its kind. Ask your dealer to show it to you. Its price is only 13/6.

- OTHER T.M.C. RADIO SPECIALITIES.**
- LOUD SPEAKERS.**
- "Standard" 24 5 0
 - "Junior" ... 21 17 6
 - "Minor" ... 17 6
- CRYSTAL SETS.**
- From 12s. 6d. to
 - 22 7s. 6d.

- OTHER T.M.C. RADIO SPECIALITIES.**
- HEADPHONES.**
- No. 3. (Light weight) in cardboard box 17/6
 - No. 2a. Heavier Model 15/-
 - Push lined cases, 2/6 extra.
- LOW-CAPACITY KEYS.**
- No. 1. 12 point, 3 position 7/-
 - No. 2. 6 " 2 " 6/-
 - No. 3. 24 " 3 " 15/3

Prices do not apply to Irish Free State.


TMC

Ask for the new T.M.C. Catalogue.

Telephone Manufacturing Co. Ltd.
HOLLINGSWORTH WORKS, WEST DULWICH, S.E. 21

Phones: Sydenham 2460-1.

Telegrams: "Bubastis, Dullox, London."

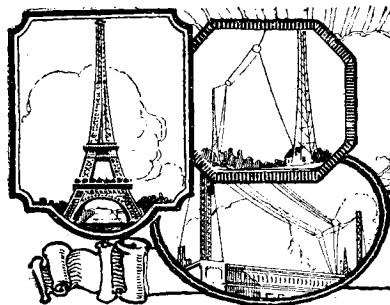

Regular Programmes from Continental Broadcast Stations

Edited by CAPTAIN L. F. PLUGGE,
B.Sc., F.R.Ae.S., F.R.Met.S.

Times reduced to Greenwich Mean Time.

Corrected up to October 11th, 1926.

G. M. T.	Name of Station.	Call Sign and Wavelength.	Closing Time or Approx. Duration.
WEEKDAYS.			
a.m.			
6.30	Eiffel Tower ..	FL 2650 m.	10 mins.
7.55	Amsterdam ..	— 1950 m.	10 mins.
7.56	Eiffel Tower ..	FL 2650 m.	5 mins. Sp.
8.10	Eiffel Tower ..	FL 2650 m.	15 mins.
8.10	Ecole Supérieure ..	FPTT 458 m.	15 mins.
9.25	Eiffel Tower ..	FL 2650 m.	5 mins. Sp.
10.25	De Bilt ..	KNMI 1100 m.	5 mins.
11.0	Eiffel Tower ..	FL 2650 m.	11.30.
11.40	Hilversum ..	NSF 1050 m.	10 mins.
11.57	Nauen ..	POZ 3100 m.	8 mins. Sp.
p.m.			
12.30	Eiffel Tower ..	FL 2650 m.	10 mins.
12.30	Radio-Paris ..	CFR 1750 m.	2 p.m.
12.35	De Bilt ..	KNMI 1100 m.	5 mins.
2.0	Zurich ..	— 513 m.	5 p.m.
2.30	Union-Radio ..	EAJ7 373 m.	3.30 p.m.
3.0	Eiffel Tower ..	FL 2650 m.	3.30 p.m.
3.0	Königswusterhausen ..	AFT 1300 m.	5.30 p.m.
3.30	Milan ..	IMI 320 m.	5.0 p.m.
3.30	Breslau ..	— 418 m.	4.0 p.m.
3.40	Kiev ..	— 900 m.	5 p.m.
4.0	Voxhaus ..	b 504 m. and 571 m.	6.30 p.m.
4.10	Amsterdam ..	— 1950 m.	10 mins.
4.30	Radio-Paris ..	CFR 1750 m.	5.40 p.m.
4.40	Hilversum ..	NSF 1050 m.	5.40 p.m.
4.45	Eiffel Tower ..	FL 2650 m.	15 mins.
5.0	Breslau ..	— 418 m.	7 p.m.
5.0	Salamanca ..	EAJ22 405 m.	6.0 p.m.
5.0	San Sebastian ..	EAJ8 343 m.	7 p.m.
5.0	Munster ..	ms 410 m.	6.30 p.m.
5.15	Stuttgart ..	— 446 m.	6.30 p.m.
5.15	Eiffel Tower ..	FL 2650 m.	10 mins.
5.30	Rome ..	— 425 m.	7 p.m.
5.30	Frankfurt ..	— 470 m.	6.30 p.m.
5.30	Leipzig ..	— 452 m.	6.30 p.m.
6.0	Leningrad ..	— 940 m.	9 p.m.
6.0	Hamburg ..	ha 392.5 m.	7.30 p.m.
6.0	Radio-Barcelona ..	EAJ1 325 m.	7 p.m.
6.0	Brunn ..	— 521 m.	8.0 p.m.
6.0	Eiffel Tower ..	FL 2650 m.	7.0 p.m.
6.0	Moscow ..	— 450 m.	8 p.m.
6.30	Zurich ..	— 513 m.	9 p.m.
6.40	Hilversum ..	NSF 1050 m.	10 p.m.
7.0	Union-Radio ..	EAJ7 373 m.	8 p.m.
7.0	Königsberg ..	— 463 m.	8 p.m.
7.0	Radio-Cadiz ..	EAJ3 357 m.	9 p.m.
7.0	Voxhaus ..	b 504 m. and 571 m.	Midnight.
7.0	Munich ..	— 485 m.	11 p.m.
7.0	Stockholm ..	SASA 430 m.	10 to 11 p.m.
7.0	Oslo ..	— 382 m.	9 or 11 p.m.
7.0	Munster ..	ms 410 m.	10.0 p.m.

G. M. T.	Name of Station.	Call Sign and Wavelength.	Closing Time or Approx. Duration.
p.m.			
7.0	Berne ..	— 435 m.	9.30 p.m.
7.0	Leipzig ..	— 452 m.	2 to 3 hrs.
7.0	Königswusterhausen ..	AFT 1300 m.	Midnight.
7.0	Stuttgart ..	— 446 m.	11 p.m.
7.0	Geteborg ..	SASB 287 m.	10 or 11 p.m.
7.0	Mabno ..	SASC 270 m.	10 or 11 p.m.
7.0	Sundsvall ..	SASD 545 m.	10 or 11 p.m.
7.0	Bcden ..	SASE 1200 m.	10 or 11 p.m.
7.0	Lausanne ..	HB2 850 m.	8.30 p.m.
7.0	Copenhagen ..	— 347.5 m.	9.30 or 11.
7.0	Radio-Wien ..	— 531 m. and 582.5 m.	9.30
7.0	Prague ..	— 368 m.	9.0 p.m.
7.0	Eiffel Tower ..	FL 2650 m.	10.30 p.m.
7.0	Bratislava ..	— 300 m.	9 p.m.
7.0	Bilbao ..	EAJ9 415 m.	9.30 p.m.
7.0	Radio-Cartagena ..	EAJ16 335 m.	9 p.m.
7.15	Frankfurt ..	— 470 m.	10 or 11 p.m.
7.15	Geneva ..	— 760 m.	9 p.m.
7.15	Breslau ..	— 418 m.	9 or 11 p.m.
7.30	Hamburg ..	ha 392.5 m.	10 p.m.
7.55	Eiffel Tower ..	FL 2650 m.	5 mins. Sp.
8.0	Königsberg ..	— 463 m.	10 p.m.
8.0	Radio-Bruxelles ..	SBR 487 m.	10.10 p.m.
8.0	Ecole Supérieure ..	FPTT 458 m.	11 p.m.
8.0	Rome ..	IRO 425 m.	11 p.m.
8.12	Milan ..	IMI 320 m.	11 p.m.
8.30	Radio-Toulouse ..	— 430 m.	11 p.m.
8.30	Budapest ..	— 560 m.	11 p.m.
8.30	Radio-Paris ..	CFR 1750 m.	10 or 11 p.m.
9.0	Radio-Béziers ..	— 95 m.	1 hour.
9.0	Radio-Viscaya ..	EAJ11 418 m.	11.30 p.m.
9.0	Radio-Barcelona ..	EAJ1 325 m.	2 to 3 hrs.
9.0	San-Sebastian ..	EAJ8 343 m.	11 p.m.
9.0	Radio-Catalana ..	EAJ13 460 m.	Midnight.
9.0	Salamanca ..	EAJ22 405 m.	11 p.m.
10.0	Union-Radio ..	EAJ7 373 m.	Midnight.
10.20	Eiffel Tower ..	FL 2650 m.	5 mins.
10.44	Eiffel Tower ..	FL 2650 m.	3 mins. Sp.
11.57	Nauen ..	POZ 3100 m.	8 mins. Sp.
SUNDAYS.			
a.m.			
7.56	Eiffel Tower ..	FL 2650 m.	5 mins. Sp.
9.25	Eiffel Tower ..	FL 2650 m.	5 mins. Sp.
10.0	Hilversum ..	NSF 1050 m.	11 a.m.
11.30	Königswusterhausen ..	AFT 1300 m.	12.30 p.m.
11.30	Union-Radio ..	EAJ7 373 m.	12.30 p.m.
11.57	Nauen ..	POZ 3100 m.	8 mins. Sp.
p.m.			
12.14	Eiffel Tower ..	FL 2650 m.	10 mins.
12.45	Radio-Paris ..	CFR 1750 m.	1.45 p.m.
2.10	Hilversum ..	NSF 1050 m.	4 p.m.

G. M. T.	Name of Station.	Call Sign and Wavelength.	Closing Time or Approx. Duration.	G. M. T.	Name of Station.	Call Sign and Wavelength.	Closing Time or Approx. Duration.
SUNDAYS (Contd.)							
p.m.				p.m.			
2.30	Union-Radio ..	EAJ7 373 m.	3.30 p.m.	7.30	Voxhaus ..	b 504 m. and 571 m.	Midnight.
2.30	Zurich ..	— 513 m.	5 p.m.	7.40	Hilversum ..	NSF 1650 m.	10.40 p.m.
4.0	Munster ..	ms 410 m.	7.30 p.m.	8.0	Milan ..	IMI 320 m.	11 p.m.
4.30	Milan ..	IMI 320 m.	6 p.m.	8.0	Oslo ..	— 382 m.	11 p.m.
4.40	Bloemendaal ..	— 315 m.	2 hrs.	8.0	Radio-Cartagena ..	EAJ16 335 m.	10 p.m.
5.30	Leningrad ..	— 940 m.	7 p.m.	8.0	Hamburg ..	ha 392.5 m.	11 p.m.
6.0	Brunn ..	— 521 m.	9 p.m.	8.0	Budapest ..	— 560 m.	Midnight.
6.0	Leipzig ..	— 452 m.	Midnight.	8.0	Eiffel Tower ..	FL 2650 m.	10 mins.
6.0	Radio-Castilla ..	EAJ4 340 m.	8 p.m.	8.0	Königswusterhausen ..	AFT 1300 m.	Midnight.
6.0	Radio-Barcelona ..	EAJ1 325 m.	8.50 p.m.	8.0	Munster ..	— 410 m.	10 p.m.
6.15	Goteborg ..	SASB 287 m.	9.15 p.m.	8.0	Rome ..	IRO 425 m.	9.30 p.m.
6.15	Stockholm ..	SASA 430 m.	9.15 p.m.	8.10	Radio-Agen ..	— 318 m.	15 mins.
6.15	Sundsvall ..	SASD 545 m.	9.15 p.m.	8.10	Königsberg ..	— 463 m.	10 p.m.
6.15	Boden ..	SASE 1200 m.	9.15 p.m.	8.15	Copenhagen ..	— 347.5 m.	11.30 p.m.
6.15	Malmö ..	SASC 270 m.	9.15 p.m.	8.15	Geneva ..	— 760 m.	1 hour.
6.30	Eiffel Tower ..	FL 2650 m.	7.55 p.m.	8.15	Radio-Bruxelles ..	SBR 487 m.	10 p.m.
7.0	Munich ..	— 485 m.	10.30 p.m.	8.25	Breslau ..	— 251 m.	Midnight.
7.0	Berne ..	— 435 m.	9.30 p.m.			and 418 m.	
7.0	Prague ..	— 308 m.	8.30 p.m.	8.30	Marseilles ..	PTT 351 m.	9.30 p.m.
7.0	Radio-Wien ..	— 531 m.	9.30 p.m.	8.30	Ecole Supérieure ..	FPTT 458 m.	11 p.m.
		and 582.5 m.		8.30	Radio-Toulouse ..	— 430 m.	11 p.m.
7.0	Lausanne ..	HB2 850 m.	8 p.m.	8.30	Frankfurt ..	— 470 m.	Midnight.
7.0	Stuttgart ..	— 446 m.	10 p.m.	8.30	Radio-Paris ..	CFR 1750 m.	10.45 p.m.
7.0	Zurich ..	— 513 m.	9 p.m.	9.0	Radio-Viscaya ..	EAJ11 418 m.	11.30 p.m.
7.0	Hamburg ..	ha 392.5 m.	8 p.m.	9.0	San Sebastian ..	EAJ8 343 m.	11 p.m.
7.0	Breslau ..	— 251 m.	8 p.m.	9.0	Salamanca ..	— 405 m.	11 p.m.
		and 418 m.		9.10	Eiffel Tower ..	FL 2650 m.	11 p.m.
7.0	Helsingfors ..	— 522 m.	9.30 p.m.	9.15	Petit Parisien ..	— 333 m.	10.30 p.m.
7.0	Warsaw ..	— 480 m.	10 p.m.	9.30	Radio-Catalana ..	EAJ13 462 m.	Midnight.
7.0	Radio-Cadiz ..	EAJ3 357 m.	9 p.m.	10.0	Union-Radio ..	EAJ7 373 m.	1 a.m.
7.0	Barcelona ..	— 325 m.	9 p.m.	10.44	Eiffel Tower ..	FL 2650 m.	3 mins. Sp.
7.30	Bilbao ..	EAJ9 415 m.	9.30 p.m.	11.57	Nauen ..	POZ 3100 m.	8 mins. Sp.

A WONDERFUL PRODUCTION

The December issue of MODERN WIRELESS will be

A SPECIAL CHRISTMAS DOUBLE NUMBER.

Mr. J. H. REYNER, B.Sc. (Hons.), A.M.I.E.E., will describe The "Isocoil" Receiver, a remarkable new design.

Other items will be:—

A Simple H.T. Unit for the A.C. Mains, by the ELSTREE LABORATORIES.

Limits in H.F. Amplification, by J. H. REYNER, B.Sc. (Hons.), A.M.I.E.E.

A Five-Valve Set employing a special L.F. circuit, designed for maximum purity of reproduction.

A Striking Article describing a neutralising scheme of great interest to every wireless enthusiast, by C. P. ALLINSON, A.M.I.R.E.

A Crystal Controlled 45-Metre Transmitter, by J. H. D. RIDLEY (G.5 NN).

Further Hints on the "Elstree Six" and "Solodyne" Receivers.

Special Contributions will also appear from the pens of Capt. H. J. ROUND, M.I.E.E.

G. P. KENDALL, B.Sc., A. JOHNSON-RANDALL, STANLEY G. RATTEE, M.I.R.E.,

A. V. D. HORT, B.A., JOHN UNDERDOWN, and other well-known writers.

OUT DECEMBER 1st.

Price 1/6

QUIET reigns as the moon rises slowly over the desert and throws into relief those great towering monuments erected thousands of years ago by the ancient Pharaohs. Many dynasties have fallen since first those pyramids were built by the genius and toil of a bygone age. But to-day they stand against the moonlight as they did centuries ago—symbols of eternity.


The spirit which animated those great architects finds to some extent a parallel in the genius and skill which have produced the S.T. Valve. It is not enough that it gives superb performance as its dynamic curves clearly show. The strength and tone given by S.T. valves are ensured month in and month out by the new Barget process, which gives the highest vacuum hitherto obtained, and by the use of the torodium filament, which is made of a new alloy of precious metals emitting a copious stream of electrons without visible glow and yet which is as tough and resilient as a steel cable.

S.T.
Limited,



2,
Melbourne
Place,
LONDON,
W.C.2.

For Types and Prices, see page 595.

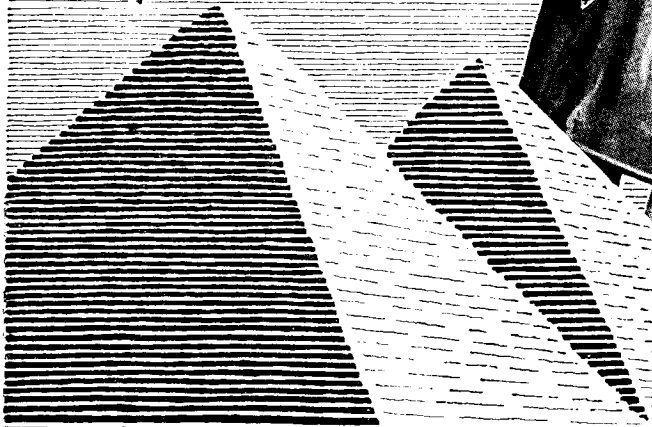

Built like the Pyramids—to last



DAY and NIGHT EFFECTS

By G.P. Kendall, B.Sc.

In this interesting article the author explains in a simple manner the wide variation between the daylight and night ranges of a given receiver. The big difference which does exist is not always fully appreciated by the wireless enthusiast.



“WELL, that is very good, but what will it do in daylight?” The beginner is apt to find such remarks as this rather disconcerting when made by an experienced friend to whom he is relating stories of the powers of his latest receiver, such as bringing in Aberdeen on the loud-speaker with only three valves, and so on, for he does not always feel that they are quite justified.

A Misconception

At first, one finds that a set will bring in such and such results on a certain occasion, and one is apt to assume that that is the standard of reception of that particular receiver, and that one can claim such results to one's friends without mentioning anything about conditions. As a matter of fact, the pertinent question above relates to an aspect of reception which has a most powerful influence upon the behaviour of any given set, and since it is one to which many people do not attach sufficient importance, it is intended in these notes to give some idea of the allowances which

should be made for varying conditions of darkness and daylight and so on.


A Wide Variation

Now, it must be realised at the very outset that there is a most enormous difference between the

having some good form of reaction circuit for the detector and perhaps one or two stages of low-frequency amplification, it is no uncommon thing to find that quite a large number of main stations can be received after dark, with a good sprinkling of Continentals, some even coming up to loud-speaker strength. During the day time, however, it is a most unusually good receiver of this type which will bring in anything except perhaps one or two of the nearest stations.


An Example

This effect was, perhaps, better appreciated in the days when crystal receivers were our main standby, and as an example I would quote the figure of 200 miles which used to be given as a standard range of a 1½ kilowatt ship's spark transmitter, when used with a standard receiver. This was regarded as the definite guaranteed range of the installation, but plenty of sea-going operators will remember occasions on which they covered distances of the order of 1,000 miles with this equipment, but practically always during the night. By day, signals from the more distant stations faded away com-

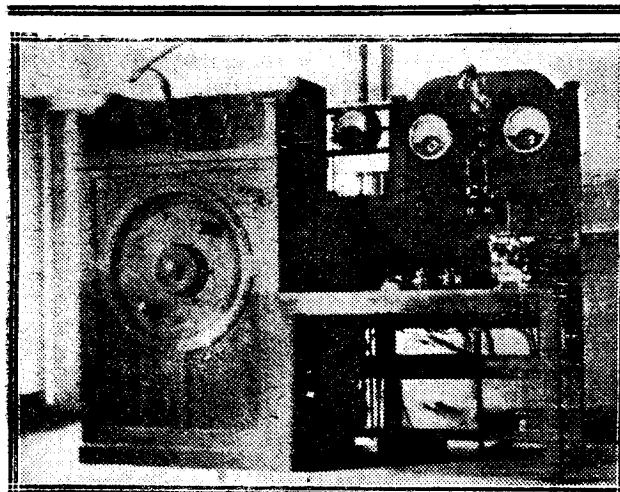

Part of the spark transmitting gear at the Helsingfors station. The broadcasting equipment is housed in the same building.

behaviour of any given set by day and after darkness has fallen, the difference in the case of quite simple sets being such as to make it seem an altogether different instrument during the day time. In the case of, say, a receiver employing no high-frequency amplification, but

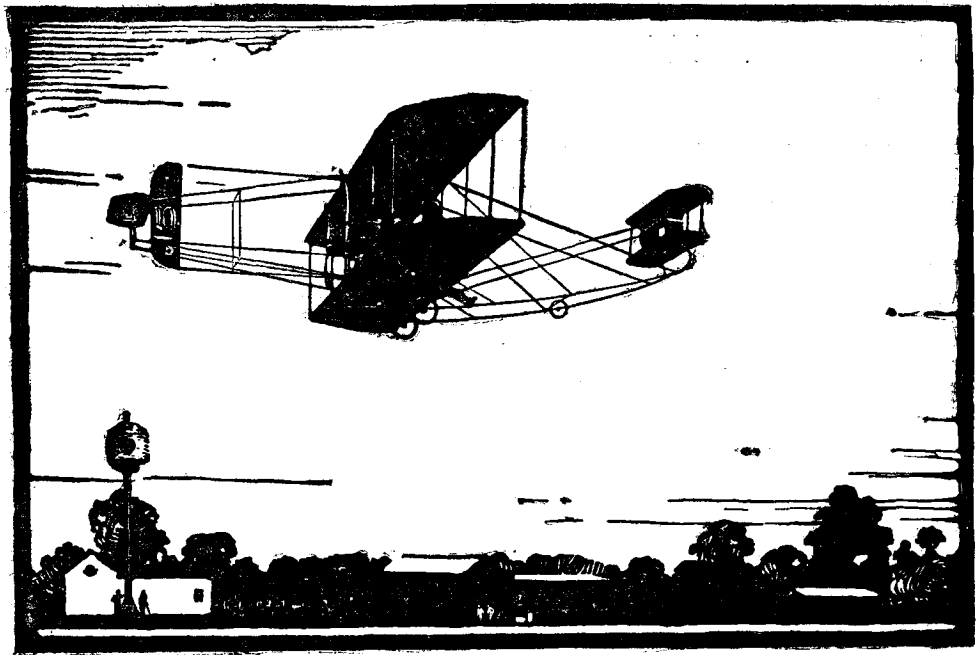

In 1910

In 1910 arose the problem of designing condensers for aircraft wireless sets.

The glass Leyden jars of those days were too bulky and too fragile, and there was no other suitable condenser made.

Thus it was that William Dubilier turned his attention to the subject and commenced his pioneer experiments. He immediately realised that to design a condenser which should be compact, unbreakable, and at the same time efficient under the high frequencies and voltages of wireless circuits would call for much specialised research.

He was successful in that same year in producing the first con-


denser to meet these requirements. Its dielectric was Mica.

Three years later, encouraged by the War Office, he commenced upon the manufacture of condensers on a large scale, and the Dubilier Condenser Company at once assumed the leadership which it holds to this day.

For sixteen years we have specialized in the manufacture of wireless condensers, and for all products bearing our name we have continuously insisted upon that high standard of efficiency which we as Radio Engineers know to be so essential.

Naturally this high standard implies a slightly increased selling price, but it undoubtedly results in the production of condensers in which you can have complete confidence.

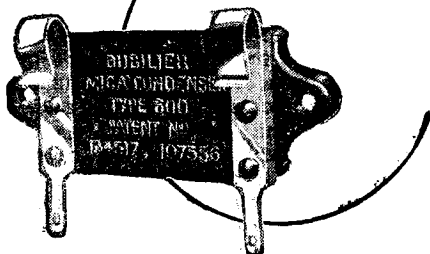And the possession of such condensers is essential to good results whether you build a crystal set or conduct laboratory research.



Specify—

DUBILIER

ADVERT. OF THE DUBILIER CONDENSER CO. (1925) LTD.,
DUCON WORKS, VICTORIA ROAD, NORTH ACTON, W.3.
TELEPHONE: CHISWICK 241-2-3.

E.P.S. 229

Tell the Advertiser you saw it in "MODERN WIRELESS."

DAY AND NIGHT EFFECTS—(Concluded)

pletely, and the range came down to something in the neighbourhood of the standard figure of 200 miles.

Using a simple crystal receiver for the reception of ship stations the effect is most marked, and would probably surprise many of those who regard a crystal set as merely something for receiving a broadcasting station at distances of the order of, perhaps, 20 miles.

Try It

This is quite an interesting thing to try for those who have crystal receivers which will tune to the standard ship wave of 600 metres, and they will find that during the day they only hear ships' signals at intervals, perhaps, from only two or three stations during quite a considerable period. This, of course, depends to some extent upon where the set is used, but in general you will find that as darkness falls, signals begin to increase in volume and in number in quite a surprising fashion, until finally, when night has fallen, there is quite a lively amount of traffic going on, and the headphones are rarely silent for long.

With a Single-Valve Set

With such a set as a single-valve reaction receiver, one can demonstrate these effects almost as strikingly, using the various broadcasting stations as the sources of test signals. For example, in my locality if I listened in with an average single-valve reaction receiver, with finely controlled reaction operated at a safe distance below the oscillation point, it would be found that the only stations which can be heard with any degree of reliability (other than the local one) during daylight, are Birmingham and Bournemouth, limiting one's search, of course, to the shorter waveband.

As darkness falls, the German stations begin to come in, as a rule somewhat ahead of the other

British stations. Soon afterwards, the northern British stations, such as Newcastle and Glasgow, begin to be heard, and when once darkness has fully set in, it is generally possible to pick up Aberdeen.

We begin to see, then, that the really severe test of capabilities of a receiver is to be found in its use in daylight, and it must be regarded as a rule that the simpler types of sets will not do very much during the day. To obtain really long distance results with them is usually a matter of reception during the hours of darkness.

To bring in plenty of distant


erratic that they form a very interesting subject for observation.

Probably the most striking example of such a field of observation open to the average listener is to be found in the reception of the American broadcasting stations, which, as is now well known, can often be picked up with quite simple sets during the winter months, at favourable hours. It will be noted that I have qualified the statement just made in two ways; first, "during the winter months" and secondly, "at favourable hours."

Although, of course, I should not like to say that American stations are never heard during the summer, it is very unusual for them to come in during the period of long days and short nights, and it is chiefly in the winter that they can be picked up.

Conditions

Then, as to favourable hours, I do not recollect ever having heard of an American station on the normal broadcast band between 200 and 600 metres ever having been heard during the hours of daylight, and the study of the conditions and times under which various American stations are heard in this country forms a really quite interesting subject for observation, by anyone possessing the necessary moderately sensitive receiver

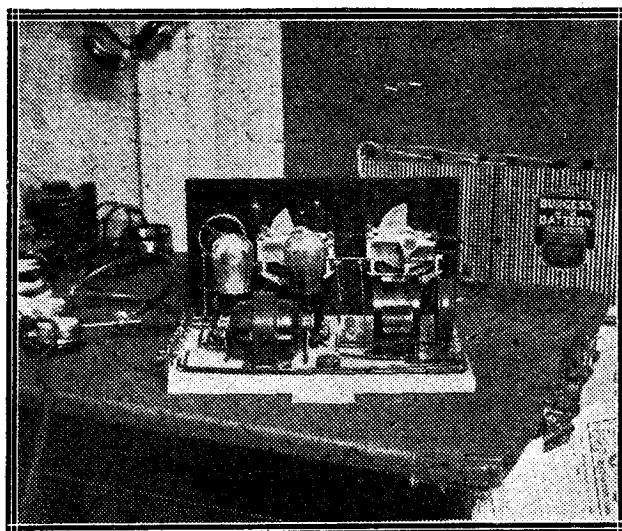

The apparatus owned by Mr. E. S. Strout, Junr., an American amateur, with which he successfully communicated with the Byrd Polar Expedition after the historic flight across the North Pole.

stations in daylight with any degree of certainty, we must realise that we need something more than a simple type of set, but, on the contrary, we require something with really efficient high-frequency amplification, like one of the more modern types of sets, or a superheterodyne.

An Interesting Field

Although the beginner is often a little incredulous as to differences in reception during day and night until he has gained a little experience, as a matter of fact these differences are so great and so

and time for listening.

An Interesting Study

It is quite an interesting study to note the exact readings upon the dials for a few of the more commonly received American stations, and to listen for them carefully one evening as darkness is spreading across the Atlantic, and note when the carrier waves begin to be perceptible, observing how they grow in strength as darkness falls all the way across the ocean, till finally some of them become of quite passable strength, with, of course, the usual spells of fading.

At last an Accumulator which can be charged quickly but discharged slowly

AFTER successfully solving the problem of the H.T. Accumulator, Oldham now presents in the new O.V.D. a slow discharge Accumulator incorporating entirely new principles of construction. With the growing popularity of Dull Emitter Valves

there has been an incessant demand for a small accumulator suitable for use with two- and three-valve sets, capable of holding its charge over long periods without sulphation. Read below and see how, in the new O.V.D., Oldham has now overcome every previous obstacle.

ON the introduction of the Dull Emitter Valve, a new problem began to loom on the horizon for the accumulator manufacturer. With the valve-maker producing valves of almost negligible consumption it became increasingly obvious that old ideas had to be swept overboard. The old idea was that an accumulator should last the average valve set anything from a week to a fortnight and should then be recharged. That was alright with bright emitters consuming .75 amp. each, but when consumption was dropped to one tenth of an ampere at 2 volts, a new kind of accumulator became necessary. An accumulator which would hold its charge for weeks on end without the necessity of recharging.

Oldham solves the problem of re-charging

Here, then, was the problem — how should it be solved? One way would be to increase the thickness of the plates. But this introduces another difficulty — the difficulty of recharging. Obviously a thick plate will hold its charge for many weeks. It won't buckle and it is reasonably free from the risk of sulphation. But it cannot easily be recharged. It must be charged slowly and for a long period on end. Compare the thick plate if you like to a thick mass of absorbent material dipped in liquid. It will take a long time for moisture to penetrate to its inmost recesses, but cut it in strips and the liquid can take effect at once. That was exactly what Oldham did. The new Oldham O.V.D. plate is the equivalent of a thick plate made up of laminations. Electrolyte can penetrate completely through the plate and get to work upon its several surfaces. So the new O.V.D., therefore, incorporates every advantage of a thick plate with none of its disadvantages. It can be charged



Type O.V.D.

2 volts—for use with Dull Emitter Valves. Fitted with the new Laminode Plate. Dimensions 6 ins. by 3 ins. by 2½ ins. 10 amp. hours.

5/6

quickly—that is to say, at the normal accumulator charging rate. There is no fear that it can be damaged during charging. And it will readily take up its charge.

A plate that cannot buckle or sulphate

The new O.V.D. plate, owing to its exceptionally rigid girder-like construction, cannot buckle. Nor can it sulphate even if left for months without being recharged. Owing to the internal construction of the stout glass cell no separators are necessary.

The new O.V.D. supplied charged ready for use

This new Accumulator is supplied "dry charged." This means that it has already been charged at the factory. Merely add acid and wait for a short while for the cell to get active and it can be used at once. Think how this will benefit you. No long first charge to delay you. The O.V.D. can come straight off the dealer's shelf to your home and within an hour can be delivering its stored-up energy.

Every O.V.D. made under the Special Activation Process

The famous Special Activation Process which has made the name Oldham a household word for reliable accumulators is used in the O.V.D. Its Laminode Plates are manufactured under the same conditions as other Oldham plates. As a result the same high standard of efficiency is available. At the low price of 5/6 the new O.V.D. offers remarkable value. Its stout clear-glass container—rugged enough to withstand even the hardest knocks—its coloured terminals of generous size—and its non-splash vent cap bespeak the quality product. Ask your Dealer about it to-day.

Oldham & Son, Ltd., Denton, Manchester

London Office and Service—
6, Eccleston Place, S.W.1

Phone: Sloane 2701



Makers of the Oldham
H.T. Accumulator,
famous for its expanding
bookcase principles of
construction.

Gilbert Ad. 6069

Tell the Advertiser you saw it in "MODERN WIRELESS."

THE LOEWE VALVE


An Interesting Demonstration at Elstree



At the Radio Press Laboratories on the evening of September 20, an interesting demonstration of a remarkable new German valve was given by the inventor, Dr. Loewe, in the presence of Mr. John Scott-Taggart and members of the staff. The main feature of this valve is that the one evacuated bulb may contain the necessary components for a complete amplifier of two stages. In the case of the two valves demonstrated, for instance, one was arranged internally to give the equivalent of the ordinary detector and two resistance coupled note magnifier circuit, while the other consisted of two high-frequency valves in one, coupled on the well-known T.A.T. principle.

Compact Sets

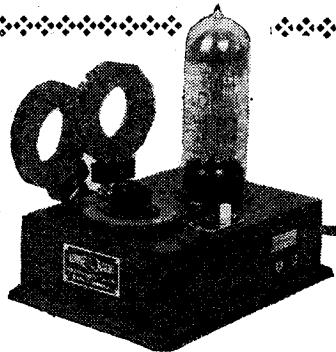
It naturally follows that when valves of this type are incorporated in a receiver there will be practically no additional components to include,



able compactness may be gathered. A simple form of reaction circuit is used, and very powerful results are obtained from the local station, with excellent quality of reproduction.


The Circuit

The receiver upon which the main demonstration was performed is equivalent to a five-valve receiver, two of the special valves being used in this case. The first of these is a two-stage high-frequency amplifier on the T.A.T. principle while the other is similar to the valve just described. The circuit is given on page 619, and is quite straightforward, except for the positively biased extra grids of the H.F. amplifier. Two tuned circuits are incorporated, these being separated by an "aperiodic" coupling in the form of a resistance. This latter is found to give good results even on the lower broadcast waves, and the explanation may be found in the very short wiring existing in the valve.

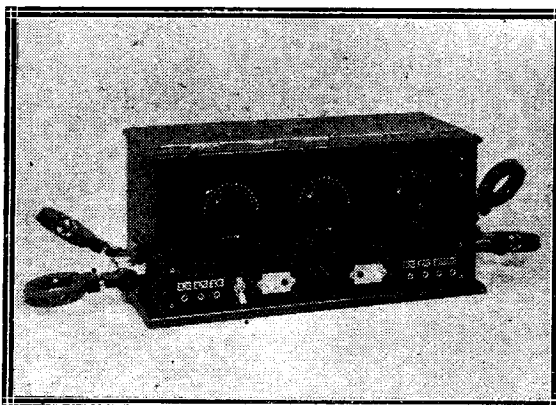

A close up view of the larger set. It embodies a two-stage H.F. Amplifier coupled by means of the T.A.T. principle.

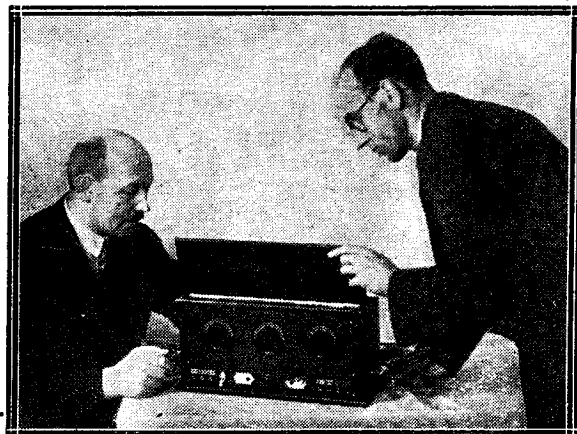Below: Dr. Loewe is seen explaining the arrangement of his larger set to Mr. G. P. Kendall (standing.)



and it becomes possible to build extremely compact sets.

Receivers Demonstrated

Two receivers employing these valves were shown by Dr. Loewe, the smallest of which employed one valve to give a detector and two low-frequency stages. A photograph of this set is given, from which an impression of the remark-

Long Wave Efficiency

When working on the longer waves, however, such as that used by Daventry, a distinct increase in efficiency was noticeable, as is generally the case with resistance-coupled H.F. amplifiers.

The receiver gave very interesting results, ten foreign stations as well as several B.B.C.

(Concluded on page 619.)

J do you remember — the first radio unit you made?

how you bought a sheet of ebonite and hacked it to size (or thereabouts) with a hack saw?

how the drill burrowed its protesting way through the gritty material, and smothered you and the kitchen with dust?

think of your early radio experiences when you see one of



at your dealer's. examine its smooth edges accurately ground dead to size.

see how its perfect polish (non-metallic) has been kept free from blemish by the damage-proof carton in which it comes.

take a shred off its edge with a penknife (if your dealer doesn't object) to judge its wonderful drilling and tapping qualities


and then say "Thanks. I'll take this — it's one of



Stocked by all reputable radio dealers in the 21 standard sizes in black and mahogany (polished surface) and in fine S.B. matt (black).

Discriminating buyers of complete radio units always look for the Ebonart tag.

EFESCA

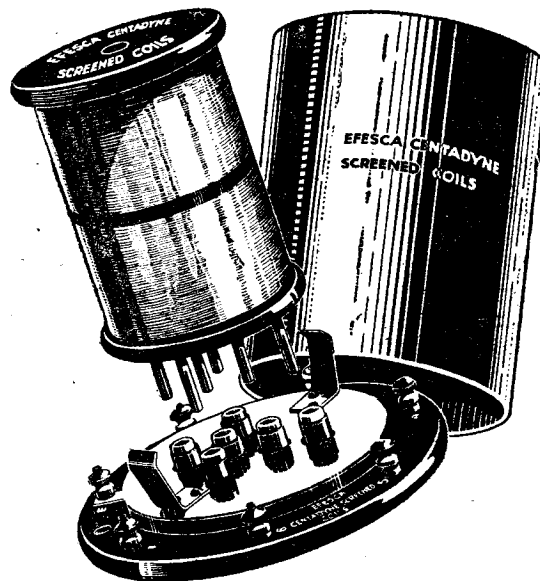

"CENTADYNE" Screened Coils

FOR NEUTRALISED CIRCUITS

Made to Elstree Laboratories specification and officially approved.

SUITABLE for all star and other circuits described in MODERN WIRELESS, "Wireless Constructor" and "Wireless," employing 6-pin standard coils.

PRICES. Coils with 6-pin plugs.


	250 to 550 metres	1000 to 2000 metres
Aerial Coils, split primary	4/6	4/6 each.
H.F. Transformers, split primary and optional reaction	7/6	7/6 each.
H.F. Transformers, split secondary	7/6	7/6 each.
Reinartz Coils... ..	7/6	10/- each
Copper Screen with 6-pin base	15/-	each.

Unshielded 6-pin base for standard Coils when used without screen... .. 4/- each.

FROM ALL WIRELESS DEALERS.

Ask your retailer or write for Catalogue 573/2 of Efesca Components and circuits employing them.

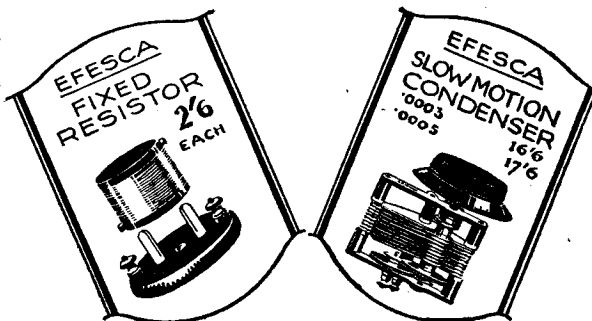FALK, STADELMANN & CO. LTD.
83/83, FARRINGTON ROAD, LONDON, E.G.1.
and at Glasgow, Manchester, Birmingham, Newcastle & Dublin.




If you are thinking of buying a finished Set, hear a demonstration of Efescaphone Sets at our Showrooms

WHAT JACK SHALL I NEED?

By A. V. D. HORT, B.A.

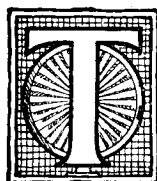All constructors of wireless receivers should have some knowledge of the construction and operation of that useful switching device—the plug and jack. The following article will tell you all about the more commonly used types.



THE use of jacks as a means of carrying out one or more switching operations is finding an increasing popularity with set designers. Jacks have, among others, these points to recommend

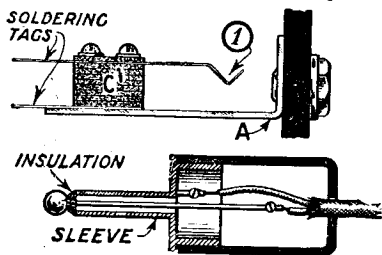


Fig. 1.—The construction of plugs and jacks is simple to understand.

.....
 them to the constructor: they give a neat appearance to the panel, they form a convenient means of switching, and they cannot be tampered with without the plug employed with them.

Jacks are used not only in wireless apparatus: they find a very extensive application in telephone switchboards, either with plugs and cords for making the connections, or in the form of "key" switches, which are really only key-operated jacks.

The constructor who is making up a wireless receiver, and who wishes to use jacks, may well be puzzled by the different types available. Each jack has its own special function, the insertion or withdrawal of the plug switching circuits in or out, as required. Thus, there are "Single Circuit Closed," "Single Open Circuit," and "Single Open Circuit Filament Control" jacks, to quote examples. Perhaps these terms convey little to the reader if he is not well acquainted with jacks, and some explanation of them may be helpful.

A Simple Form

Before passing on to discuss individual types of jacks, it may assist the reader to grasp the principles of the jack if Fig. 1 is considered. Here we have a "Single Open Circuit" jack, the simplest form which is used.

L.F. Switching

Now jacks are not to be recommended for use in the high-frequency

stages of a receiver, since they introduce unwanted capacities in the circuit. In practice, jacks are almost invariably employed in the low-frequency circuits, usually for placing the telephones or loud-speaker in circuit.

Explanatory Details

The jack shown in Fig. 1 has two

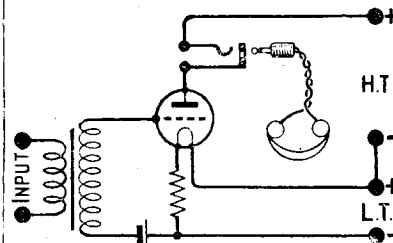


Fig. 2.—The plug and jack of Fig. 1 are commonly employed as shown above.

.....
 essential parts—the "body" A and the springy contact blade (1). C is an insulating block separating

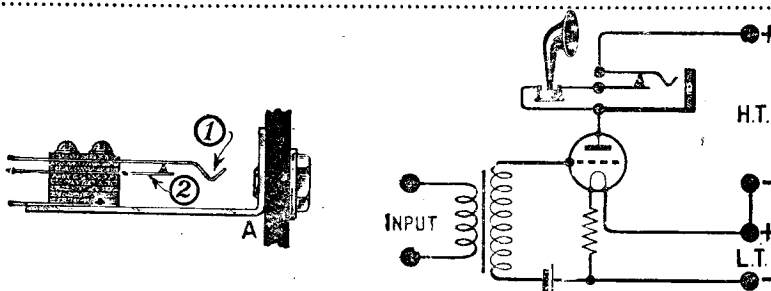


Fig. 3.—The Single Circuit Closed jack possesses an additional contact (2), and may be used as seen in the theoretical diagram.

.....
 frequency stages of a receiver, since the method of their construction almost inevitably introduces considerable

.....
 drops into the nick behind the tip of the plug, making a firm contact and locking the plug in position.


STARTLING THE TRADE WITH A NEW LISSEN TRANSFORMER.

URNS RATIO
3 to 1
RESISTANCE
RATIO
4 to 1

Price

8'6

and guaranteed
for 12 months.

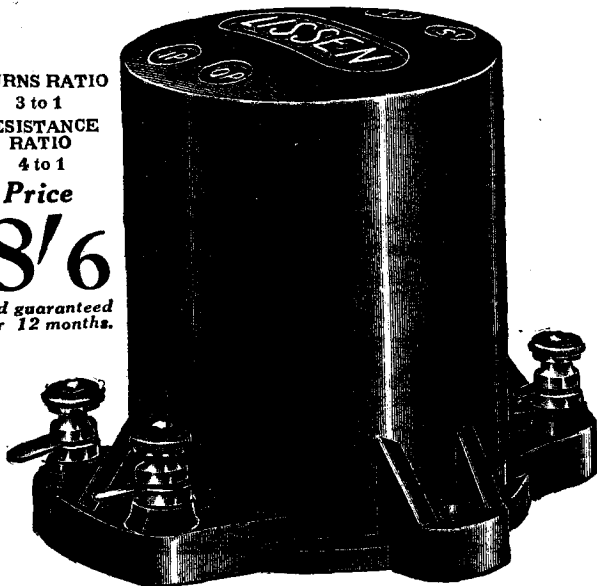

Powerful amplifiers now within the reach of all!

TRADER buyers who came to us during the first few days of the Olympia Exhibition scarcely believed it when we told them the price of this new LISSEN part. After taking away samples, however, many of them came back to order and to urge for quick delivery—those who did not come back ordered direct to factory—ORDERED AFTER PROVING PERFORMANCE.

Private users who have also tested have told us they have found the results equal to expensive transformers they were previously using.

We knew all this would be the case, BECAUSE THIS NEW LISSEN TRANSFORMER WAS MADE PURPOSELY TO EQUAL THE PERFORMANCE OF EXPENSIVE TRANSFORMERS AND SO GOOD IS IT THAT WE HAVE UNHESITATINGLY WITHDRAWN IN ITS FAVOUR ALL OUR OWN HIGH PRICED MODELS, which have been on the market and largely sold for nearly four years past. Pure, powerful, economical, amplification is now at last within the reach of all.

By ourselves distributing direct to the retail trade we have cut out all wholesale profits. This new policy coupled with our ambitious production programme, has been a big factor in enabling us to sell the new LISSEN TRANSFORMER at its remarkably low price. Nobody should now pay highly to get a high grade transformer. Compare this new LISSEN against any for tone, purity and power. IT AMPLIFIES EVERY NOTE—EVERY HARMONIC—EVERY OVERTONE.

You can get it at your dealers, or direct from factory if any difficulty. If you are not satisfied with it after seven days' test, take it back to your dealers or send it back to us. You will find it suits every set and every valve you will want to use.

Include no postage if you send direct, but please send dealer's name and address.

**LISSEN LIMITED, Lissenium Works,
20-24, Friars Lane Richmond, Surrey.**

Managing Director T. N. COLE.

Use it for 1, 2 or 3 stages L.F. L74

Consistently perfect reception



Duo- triangular filament suspension

A comparison between the principles applied in different branches of engineering science is always interesting. Here for instance on the one hand, we have the Warren Girder—typical of some of the world's big engineering feats—built up triangle after triangle, each adding stability to the structure as a whole, and on the other, intriguingly similar, the Six-Sixty method of filament suspension in which a corresponding degree of stability is ensured by a dual system of triangles.

But in addition to the inherent stability of the Duo-Triangular system of suspension, this construction renders it unnecessary to assemble the filament in tension and enables equal and relatively short supports to be employed, with the result that the filament is in perfect alignment, and all possibility of displacement in any direction is eliminated. In the usual type of valve with one long and two short supports, the same degree of stability is not possible owing to the greater tendency to bend on the part of the longer support.

We have then, a perfectly designed construction in which the relative positions of filament, grid, and anode are absolutely fixed, thereby ensuring uniformity of results and consistently perfect reception.

And remember, Duo-Triangular Filament Suspension means increased electronic emission, since the length of filament is almost twice that in the usual type—and what a filament!—absolutely no sign of "glow" when operating at the rated voltage, and a current consumption of only '1 amp.

After exacting and exhaustive tests, Messrs. A. J. Stevens & Co. (1914), Ltd., have decided to standardise Six-Sixty Valves in their famous "Symphony" Range of Receivers.



**S.S.2A. H.F.
and L.F.**

D.E. 1.8 volts, '1 amp.,
H.F., L.F., and Detector .. 14/-

S.S.10.

D.E. 2 volts, '15 amp.,
Power Amplifier, 18/6

S.S.7.

D.E. 3.7 volts, '1 amp.,
Power Amplifier, 18/6

S.S.S.

D.E. 3.4 volts, '1 amp.,
General Purpose, 14/-

These prices do not apply
in the Irish Free State.

Descriptive leaflet
S.S.9-26 giving full
particulars of complete
range, free on
application.

SIX-SIXTY VALVES
Better by Six times Sixty



The Electron Co., Ltd., Triumph House, 189, Regent Street, London, W.1. 3A

Announcing A GREAT

IN this, the first announcement of the new S.T. series of valves, I would, as the designer, like to make some preliminary remarks.

I have for several years watched valve development very closely, noticing the advantages and disadvantages of every type and every process. When I decided to enter the manufacturing field myself, I resolved to combine the best features of existing valves with my own ideas. The Company of which I am now managing director has acquired a licence under all the leading patents which have contributed to valve development in order that we shall not be hampered in any way in producing the best. Although this has added to the manufacturing cost and minimises the profit, I was not prepared to place a valve bearing my name on the market unless it represented the highest technique in valve manufacture and design.

While head of the Elstree Laboratories, my duties included the technical criticism of existing valves and acquiring an intimate knowledge of their respective advantages and limitations, and I would not have produced a series of valves unless I believed they would stand out above others.



John Scott-Taggart, F.Inst.P., A.M.I.E.E.

THE S

FOR STRENGTH

NEW VALVE

IT is because I feel acutely that my technical reputation is staked on these valves, that I propose—having satisfactorily established the design and manufacture—to satisfy myself that *each* valve is within the necessary specification, and then to initial every carton to certify that the valve is fully up to standard.

In launching a new valve, no risks can be taken. The valve you buy will have been tested under my personal supervision—a laborious task—but then the whole business of S.T. valves will be run on personal lines. I do not believe in treating valves as a species of electric lamp or as so much merchandise. Every valve I sell, every valve you buy, is a valve in which I shall retain a personal interest. Each valve is designed for a specific purpose, although the series have many merits in common. I have aimed at a high mutual conductance, a large filament operating at a very low temperature, and taking a minimum of current, a long life for the valve, a high vacuum, a big factor of safety in every direction, robustness, and absolute uniformity. The S.T. valve is strong, entirely non-microphonic and foolproof, but is built like a chronometer.

For types and prices see page 595.

John Scott-Taggart

T
VALVE
AND TONE



S.T. LIMITED
2, MELBOURNE PLACE,
ALDWYCH—W.C.2


Tell the Advertiser you saw it in "MODERN WIRELESS."

WHAT JACK SHALL I NEED? — (Continued)

A "Single Open Circuit" jack is normally used to place the telephones or loud-speaker in circuit, as shown in Fig. 2. The telephones are connected to the terminals of the plug, H.T. positive and the anode of the valve being connected to the contact blade and body of the jack respectively.

Simultaneous Control

This simplest form of jack may

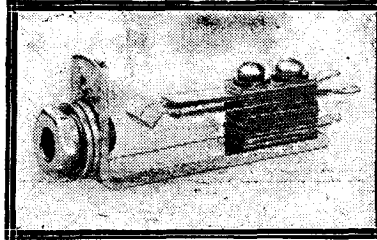

Although possessing many advantages for L.F. work, jacks should not be used on the H.F. side.

Closed Types

If one contact is added to the jack, we have the "Single Circuit Closed" type, shown in Fig. 3, in which a suitable circuit for employing the extra contact is also given. In the normal state, the blade (2) is in contact with blade (1). When the plug is inserted, it makes contact with (A) and (1) in the usual way, and at the same time lifts (1) away from (2). In the circuit shown the loud-speaker is permanently wired in circuit. The insertion of a plug connected to the telephones puts them in circuit, disconnecting the loud-speaker. It will be noted that one side of the loud-speaker is still connected to the "live" circuit.

The Double Circuit Jack

When it is desired, by inserting the plug, to cut out altogether the apparatus normally connected in circuit, a "Double Circuit Closed" jack may be used, as shown with a suitable circuit in Fig. 4. In this

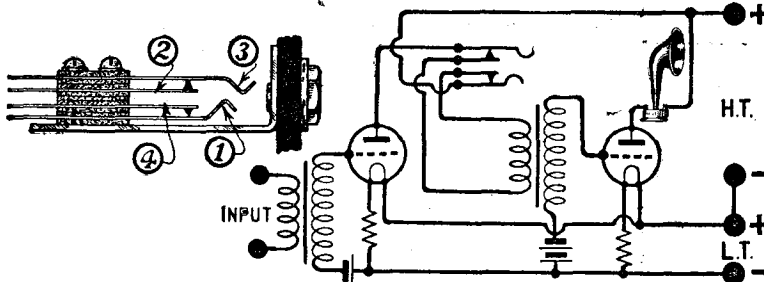


Fig. 4.—The Double Circuit Closed jack is frequently used for cutting out a note magnifying valve.

be taken as a guide to other types, illustrating a rule which applies to them all. The telephones, or similar apparatus to be connected in the anode circuit, are connected to the plug. The body and "V" shaped contact in the jack, or in "Double Circuit" jacks the two "V" shaped contacts, are connected in the anode circuit. Any other contacts there may be are used for filament control or other switching, these operations being controlled simultaneously with the insertion of the plug—i.e., putting the telephones in circuit.

Having now dealt with the "Single Open Circuit" jack, we

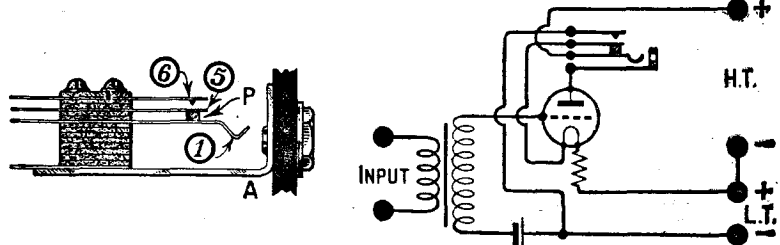


Fig. 5.—The jack depicted above is simply an elaboration of that shown in Fig. 1—two further contacts being added for filament control.

may proceed to develop this by adding other contact blades. The same type of plug is, of course, used throughout.

jack no electrical use is made of the body (A). Two contact blades (1) and (3) are used, (3) taking the place of the body and making contact with the sleeve of the plug.

The blades (2) and (4) are here normally in contact with blades (1) and (3), the insertion of the plug pushing the latter pair apart and breaking both contacts.

Filament Control

So far the jacks discussed have been those dealing with anode circuit connections only. If the filament of the valve could be switched on by the act of connecting the telephones in circuit, the utility of the system would be greatly enhanced. This is made possible by the addition of further contacts, as shown in Fig. 5, illustrating the "Single Open Circuit Filament Control" jack. Here the blade (1) and the body


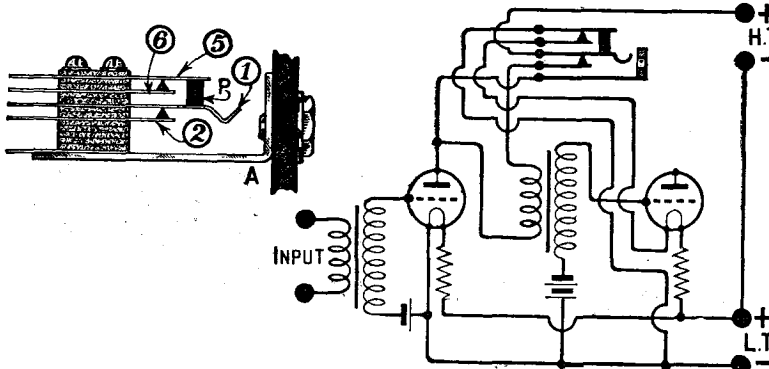


Fig. 6.—This type of jack switches out the filament of the last valve and places the telephones or loud-speaker in the anode circuit of the first L.F. valve.

EDISON BELL RADIO

A RADIO MASTERPIECE.

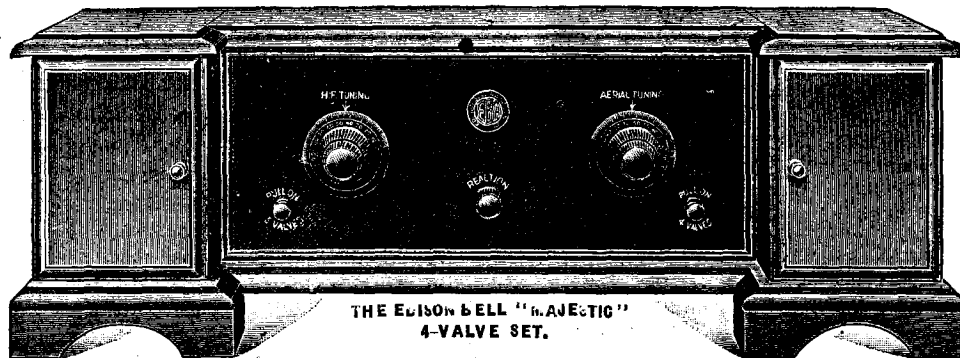

THE EDISON BELL "MAJESTIC" 4-VALVE SET.

This super 4-valve set, which appeals to novice and expert alike, was the most outstanding exhibit at the National Radio Exhibition. A special feature, in addition to the wonderful selectivity, charming appearance and expert workmanship of this set, is its compactness. H.T. and L.T. batteries are enclosed in the set itself, compartments for same being provided at either end of the cabinet, as will be seen in the above illustration. Embodying as it does the very latest improvements, this set will appeal to all.

TESTED 500 VOLTS
FLAT TYPE




PRICE £15-0-0

Valves, Batteries, Marconi Licence extra)

EDISON BELL LIMITED, LONDON, S.E.15
and at Huntingdon.


TESTED 500 VOLTS
UPRIGHT TYPE

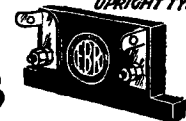

INSIST ON EDISON BELL CONDENSERS

THEY ARE BRITISH MADE AND GUARANTEED BY A NAME WITH 30 YEARS REPUTATION BEHIND IT

MAGNUM SCREENED COILS

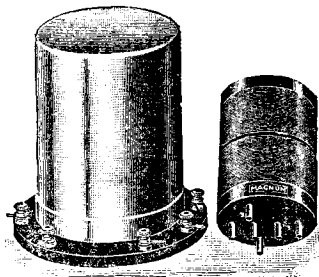

NEW STANDARD COILS AND PRICES.

MAGNUM Screening Box, complete with 6-Pin base
(Standard spacing and cross formation) ... 15/-

Split Primaries.

Aerial Coil	250/550	6/-
H.F. Transformer	250/550	10/-
Aerial Coil	1000/2000	6/-
H.F. Transformer	1000/2000	10/-

Split Secondaries.

H.F. Transformer	250/550	10/-
H.F. Transformer	1000/2000	14/-

Reinartz Coil... ..	250/550	10/-
Reinartz Coil... ..	1000/2000	14/-

Price per set of 3 Screens and Coils, 250/550,
for the Elstree Solodyne ... £3 11 0

Set of Screens and Bases I.F. Transformers,
Filter and Oscillator for the 8-Valve
Super-Het. described in Oct. issue ... £8 10 0

NOTE.—Where a complete set of Components,
together with a drilled panel, is purchased, Royalties
at the rate of 12s. 6d. per valve holder are payable.

The following Sets ready wired and tested:—
ELSTREE SIX £29 0 0
ELSTREE SOLODYNE £25 0 0
Plus Marconi Royalties at 12/6 per valve holder.

FILAMENT TRANSFORMER AS USED IN THE
CHARGING UNIT DESCRIBED IN OCT. ISSUE,
OPERATING FROM 200/240 VOLTS A.C. TO
3, 5 OR 8 VOLTS. 25/-

CONSTRUCT

THE DRAWING ROOM 5.

As described in this issue by Mr. John Underdown.

1 Mahogany Cabinet with baseboard ...	£ 9. d.	1 16 0
1 Radiator Panel, 16 by 8 by 3/4 ...	10 8	7 6
1 Duvolcom (Dubilier) ...	13 9	12 6
5 Benjamin Valve Holders ...	12 6	
3 Edison Baseboard Rhicostats ...		1 2 6
3 Varley Anode Resistances, 100,000, and bases ...	1 3 0	1 0 0
2 Jackson S.L.F. Condensers, .0005 ...	10 0	5 0
1 Jackson S.L.F. Condenser, .00025 ...	5 0	1 9
1 Neutralising Condenser ...	1 9	7 0
1 Single Coil Holder ...	7 0	4 8
3 T.C.C. Condensers, .01 ...	4 8	10 6
1 T.C.C. Condenser, 2 mfd. ...	10 6	2 6
1 Success Audio Choke ...	2 6	6 9
1 Igranite "On and Off" Switch... ..	6 9	1 10 0
3 Igranite Grid Leaks and Clips ...	1 10 0	6 0
2 Magnum Screening Boxes with Bases ...	6 0	
1 Magnum Aerial Coil, 250/550 ...		10 0
1 Magnum Split Primary Transformer, 250/550	10 0	1 3
5 Etelex Terminals	1 3	1 8
Connecting Wire	1 8	
		11 3 0

Any of above parts supplied separately as desired.
We specialise in and can supply Components for all
Sets described in this and all Radio Press publications,
including—

- THE ELSTREE SIX.
- THE ELSTREE SOLODYNE.
- THE MEWFLEX THREE.
- THE NIGHT HAWK.
- THE DISTAFLEX TWO, Etc., etc.

Lists on receipt of stamp.

BURNE-JONES & CO., LTD.,


Manufacturing Radio Engineers,

MAGNUM HOUSE,

296, Borough High St., London, S.E.1

Telephone: Hop 6257.
Telegrams: "Burjomag, Sedist, London."
Cables: "Burjomag, London."


MAGNUM VOLUME CONTROL AS USED IN THE PRIZEWINNING MEWFLEX.

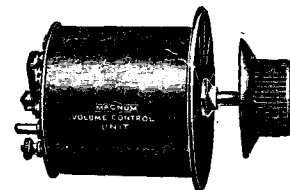

No. 1662.

A new Magnum product for controlling the volume from
Loud-speaker without sacrifice of quality. Wire-
wound, Non-Inductive. One hole fitting

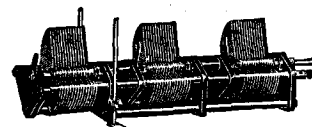Price 15/-
Size, 4 in. long by 2 1/2 in. dia.



MAGNUM GANG CONDENSER


Recommended for the Elstree Solodyne £3 10 0

MAGNUM DUAL CONDENSER

Recommended for the Elstree Six... £1 1 0

Tell the Advertiser you saw it in "MODERN WIRELESS."

WHAT JACK SHALL I NEED? —(Concluded)

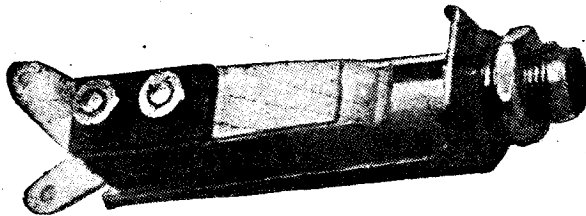

A photograph of the simplest jack used—the Single 'Open Circuit' type.

perform the same functions as in the "Single Open Circuit" jack of Fig. 1. Two additional blades (5) and (6) are added above blade (1), these two being normally separated by a small gap. P is a pin of insulating material attached to blade (5) and resting on blade (1). Insulation is necessary here, since blade (1) is in the anode circuit and (5) in the filament circuit. The insertion of the plug pushes (5) into contact with (6), thereby completing the filament circuit.

A further development results in the "Single Closed Circuit Filament Control" (Fig. 6), which is the "Single Circuit Closed" jack (Fig. 3) with filament control added. In this case, the filament circuit also is normally "closed," blades (5) and (6) being in contact, to be

separated by the insertion of the plug.

Obviously, the last two jacks described may be obtained with the filament control either "open" or "closed," so that the insertion of the plug switches a valve on or off as required.

Other Uses

Further, by combining the two arrangements, we can have double filament control (Fig. 7), the plug switching on one valve and switching off another. The types described above, however, are those which are most commonly met with, more elaborate jacks being developments on the same general principles.

It should be noted that it is not essential to use the plug for the anode circuit of the set. It may

be preferred to plug in, for example, the low-tension battery, completing the anode circuit with the subsidiary contact blades. The method of use which has been described is, however, the conventional one, and the one which is generally accepted as the most convenient.

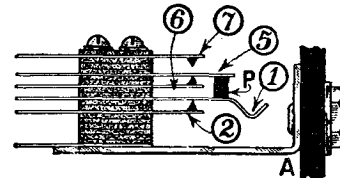



Fig. 7.—Double Filament Control is featured in some of the larger specimens.

A point worth noting is that jacks should always be connected so that the H.T. + contact goes to the same side of the telephones when the plug is inserted. It is common practice to arrange for the tip of the plug to be connected to H.T. positive, but this is not essential.

SUCCESS RADIO PRODUCTS

"SUCCESS" SUPER III. RECEIVER.

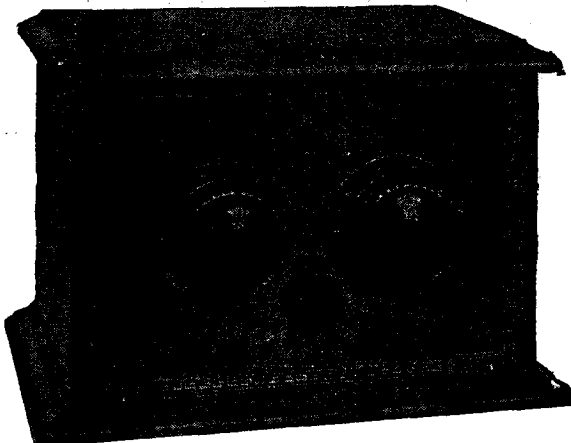FINEST Three Valve Receiver manufactured. Metal oxydised silver panel and cabinet to match. Terminal board and L.S. jack at rear of cabinet. No unsightly wires. A perfect receiver.



Tunable from 40 to 2,500 metres S.L.F. Condensers, 100 to 1 slow motion. Single filament control. Perfect selectivity. Perfect loud speaker reproduction in any part of British Isles.

Complete with all accessories, including LOUD SPEAKER (Royalties paid),


£ 17 : 10 : 0

BEARD & FITCH, LTD.,
34, AYLESBURY STREET,
LONDON, E.C.1.

As used in the
"Night Hawk"
 by Mr. Percy W. Harris
 and in other well-known
 Receiving Sets

**Eleven exclusive
 Eureka features**

- 1 Absolute rigidity of fixed plates ensured by unit construction.
- 2 Moving plates clamped together to permit fine spacing with absolute security.
- 3 Special method of construction eliminates the possibility of fixed and moving plates short circuiting.
- 4 Ball-bearings ensure smooth silken action under all conditions.
- 5 Dual connections (cone and pigtail) guarantee continuously silent performance.
- 6 Electrical losses so low as to be quite negligible. An invaluable feature for short-wave use.
- 7 Generous and readily accessible soldering tags.
- 8 Equipped for panel mounting as one-hole or four-hole, whichever preferred.
- 9 Positive stops at both ends of scale.
- 10 Compact design permits a panel depth when closed of less than two inches. The .0005 mfd. Ortho-cyclic takes up much less room than most .0003 mfd. condensers.
- 11 Highly polished and beautifully finished throughout—a perfect example of British craftsmanship.

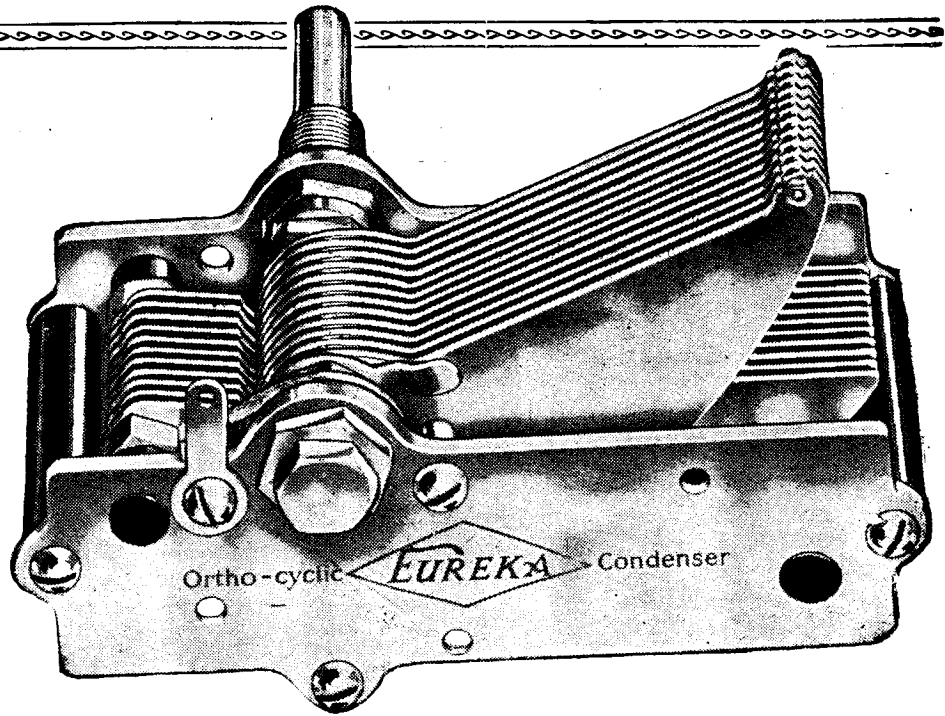

N O W !

**Space out your Stations as
 evenly as the rungs of a ladder**

At last there is available a British Condenser which takes out all the guesswork of station finding and ensures a standard of selectivity which is almost incredible. The new Eureka Ortho-cyclic is a fine precision-made instrument designed to give mathematically equal spacings between all wavelengths throughout the whole of the scale. Within the first 15 degrees on the dial you will find 15 wavelengths of 10 kilocycles separation. Fifteen only—one to each degree! And the same precise separation will be found all through the scale. Yet in the ordinary condenser used under the same conditions you would find 51

wavelengths crowded into the same 15 degrees. An absurd overcrowding just where you need the greatest separation to ensure workable selectivity. No wonder wave-traps and similar gadgets are necessary to separate the wanted from the unwanted stations. Add to this astounding performance a host of other electrical and mechanical features and you'll understand why the Eureka Ortho-cyclic is unrivalled for performance, uniformity and enduring dependability. Before choosing your variable condenser ask to see the Eureka. To every discriminating wireless man its beautiful workmanship will be irresistible.

Portable Utilities Co., Ltd. (Eureka Radio Products), 8 Fisher St., London, W.C.1

Prices:

.0003 mfd. 14/6
 .0005 mfd. 15/6

EUREKA
ORTHO-CYCLIC

Manufactured by the
 makers of the famous
 Eureka Transformer


Tell the Advertiser you saw it in "MODERN WIRELESS."

NEATNESS AND EFFICIENCY

A crystal set with aerial and detector taps

By H. BRAMFORD

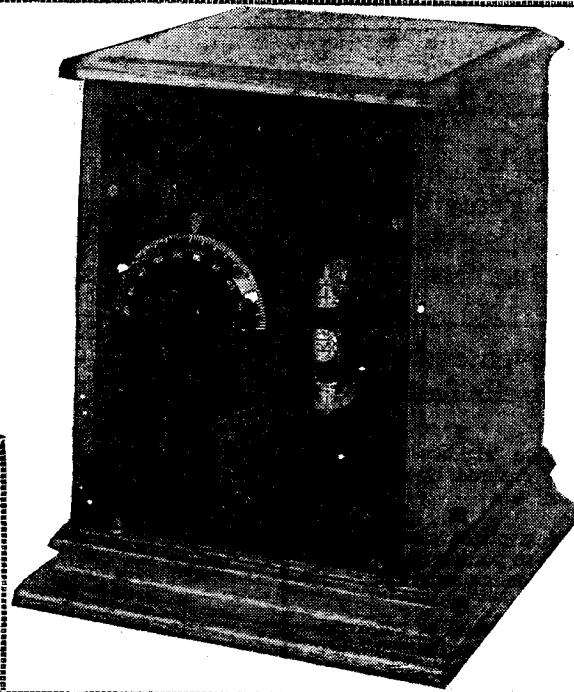This little set employs a tapped home-wound inductance which permits the use of "auto-coupling" and a variable crystal tap, both resulting in increased selectivity without loss of signal strength.



DESIRABLE feature at the present time is selectivity, not only in valve receivers but also in crystal receivers. At the same time, a crystal receiver should fundamentally be of simple design and construction. Simplicity helps to make for efficiency as regards

the same time it presents a neat and pleasing appearance when completed. A list of the components required to build this set is given on another page.

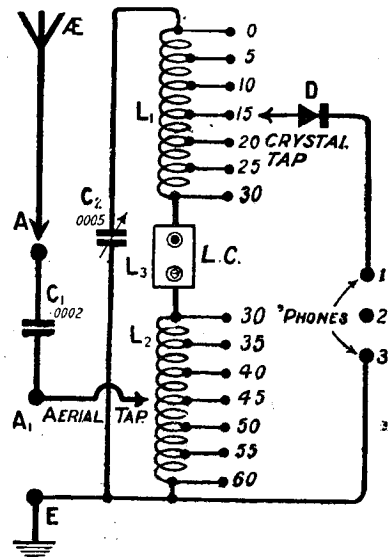


Fig. 1.—Complete details of the circuit employed are given in this theoretical diagram.

signal strength, and selectivity is desirable in order to be able to comply with the present conditions. The receiver about to be described in this article embodies these two features, inasmuch as it is simple to construct, simple to operate, and gives efficient results. Further, it is not an expensive set to make, while at

Details of Construction

To carry out the construction of the receiver, first proceed to drill the panel in accordance with the details and dimensions given in the front of panel diagram. Having done this, proceed to secure the panel to the wood baseboard and side brackets by means of the four countersunk wood screws, as indicated. Next mount upon the panel the six terminals, and the crystal detector, leaving the assembly of the variable condenser to a later stage to facilitate the ease of the process of wiring up. Before proceeding any further, it is advisable to construct the tapped coil.

The Tapped Coil

First cut off a length of cylindrical former having an external diameter

of 2 in. The former should be approximately $3\frac{1}{2}$ in. long. Commence from the right-hand side of the former, the winding being made with the wire specified in the list of materials. First secure the beginning of the winding by

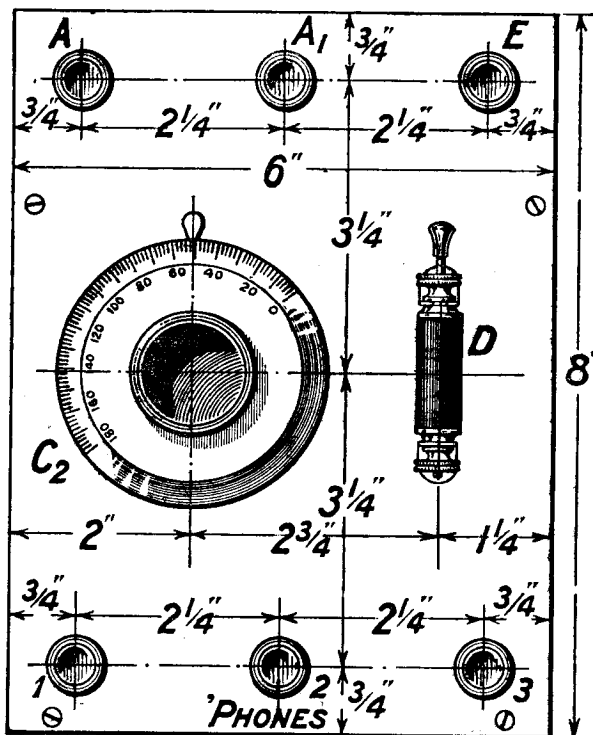


Fig. 2.—The three 'phone terminals permit two pairs of telephones to be used in series.

Pat. No. 256833
Pro. Pat. No. 20339



The Grid Leak is not discernible, being totally enclosed in Bakelite Valve Holder Base.

Something new and good in component design

The latest LOTUS triumph is a Combination Grid Leak and Valve Holder which eliminates unnecessary wiring and soldering and makes for economy in cost and space.

Guaranteed efficient in construction and design.

From all Radio Dealers

Combination Grid Leak and Terminal Valve Holder	3/9
Terminal Valve Holder	2/6
Valve Holder without Terminals	2/3

All Anti-Microphonic Type.

LOTUS

Combination


GRID LEAK AND BUOYANCY VALVE HOLDER
Anti-Microphonic

Garnett, Whiteley & Co. Ltd.
Lotus Works, Broadgreen Road, Liverpool.

Makers of the famous "Lotus" Vernier Coil Holders

ASK YOUR DEALER for the new S.L.F.

The New J.B., S.L.F. Condenser is made on lines similar to our Low Loss Type (Pat. No. 241805). In addition, its many excellent new features include Special Bearings Top and Bottom which eliminate springs. Side and End play in the centre spindle is impossible. The Top Bearing is of large diameter and friction-lined, which ensures an absolutely smooth movement. The brass vanes are supported at tips to ensure accurate spacing. End plates are highly polished and all fittings are heavily nickel-plated.

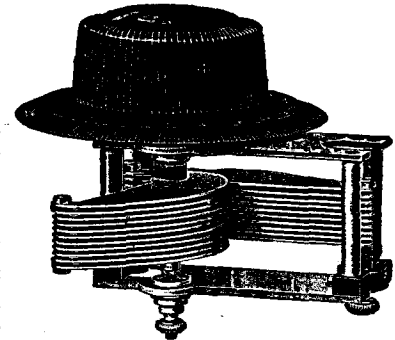

Fitted with 1/4" shaft, sold complete with 4" Dial and is more compact than most S.L.F. Condensers.

	Retail Prices:		
.0005 mfd. 11/6
.00035 mfd. 10/6
.00025 mfd. 10/-

Two of our new .0005 mfd. Straight Line Frequency Condensers, and one .00025 of the same type have been specified for the 5-valve Receiver described in this issue of *Modern Wireless*,—another proof of the remarkable efficiency and perfect workmanship of our instruments. Our extensive range includes types suitable for all the big sets recently published, and we guarantee that J.B. Condensers—the skilled product of experienced specialists—are unsurpassed by any on the market to-day, either for quality, efficiency, or price.

Particulars of the new J.B. Gang Control Dual Condenser on application.


THE LOWEST LOSSES YET!

THAT'S the claim we make for the new J.B. Condenser. The losses are, in fact, absolutely negligible. For instance, with the .0005 model the total losses measured at a million cycles are .02 ohms.

This is a fact established by an N.P.L. Test, and gives an added point of superiority to the J.B. which, while combining features of mechanical excellence, is logically an instrument for the radio man seeking a precision condenser.

	PRICES:	
.001 mfd. 17/6
.00075 " 16/3
.0005 " 15/-
.0003 " 13/3
.00025 " 13/3
.0002 " 13/-
.0001 " 12/9

GEARED MODEL.

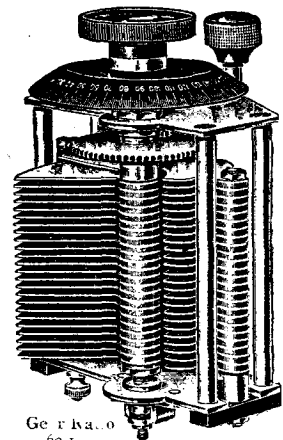


Ger. k a. o 60-1

Pat. Nos. 241805 & 246009.

.0005 mfd. Twin Low Loss Condenser, complete with 4in. Bakelite Dial, for the Elstree Six, Distallex, Mewflex and Elstreflex, 21/- each. | .0005 mfd. Triple Gang Control Condenser for the Solodyne. Complete unit, less dial, £2 : 7 : 6.

JACKSON BROS.
8, POLAND ST- OXFORD ST
LONDON - W.1.
(First Floor) Telephone: GEF. RARD 7414

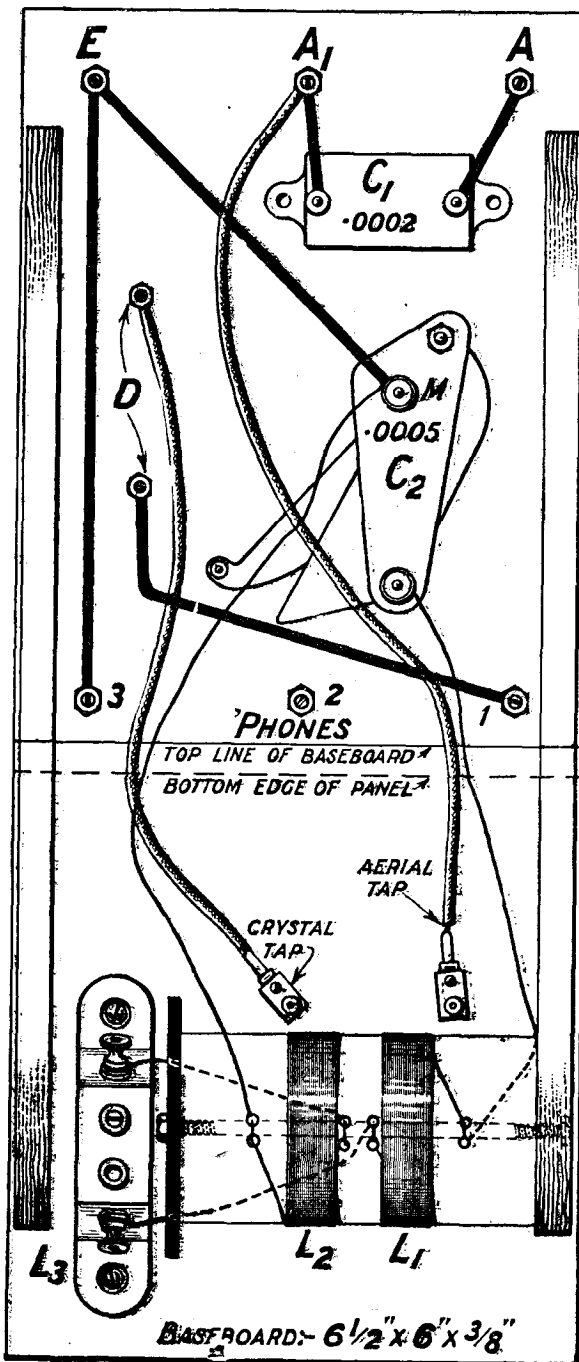Tell the Advertiser you saw it in "MODERN WIRELESS."



A SELECTIVE CRYSTAL SET (Continued)

passing through two small holes previously made in the former, as shown in the back of panel diagram. At the first turn make a tapping; the method of doing this will be described later. Make a further tapping at the 5th, 10th, 15th, 20th, 25th and 30th turn. At this point secure the wire by means of two further holes made in the former, and finish by taking end through the inside of the former and cutting off. If the winding is close wound it will occupy a distance of approximately $\frac{7}{16}$ th of an inch. Commence a second winding in a similar manner, $\frac{7}{16}$ in. away from the previous winding. This winding should be in a similar direction, that is to say, clockwise. Secure the beginning of the winding as before, making a tap at the first turn, and further taps at the 5th, 10th, 15th, 20th, 25th and 30th turn. At the 30th turn, finish off the winding by securing as before and passing the end of the wire through to the inside of the former and cutting off. Thus we have at present two separate windings upon the ebonite former.

Fig. 3.—This practical wiring diagram will be found simple to follow. Note how the cylindrical coil is mounted, the threaded rod shown dotted, passing along the axis of the coil.

Making the Tappings

Care should be taken in making theappings, as the wire is of a somewhat fine gauge, and due consideration should be given to this fact. The simplest way of making suchappings, which incidentally occasions the least possible amount of trouble, is as follows: At each tapping point make a small loop with the wire, and twist it closely with the fingers. Pliers should in no case be used, as this might easily result in over twisting and breaking the wire. Each tapping is twisted thus and made as the winding is proceeded with, and they should be spaced somewhat apart from each other, as shown in the drawing. When the winding is completed, the problem presents itself of removing in the best possible way the silk covering from the wire of the twistedappings. This is quickly and easily done by placing a lighted match under each tapping until the silk covering is burnt away. Theappings should then be lightly scraped with a sharp knife in order to clean them, after which they may be bent over in order to strengthen them and make them more rigid.

Assembly


The coil thus made may now be assembled upon the wood side support, as shown in the back of panel

COMPONENTS REQUIRED

- One panel measuring 8. by 6 by $\frac{3}{16}$ in. (any good make).
- One cabinet with baseboard $6\frac{1}{2}$ in. deep, and wooden side pieces (Pickett's).
- One S.L.F. variable condenser .0005 (K. Raymond).
- One fixed condenser, .0002 (Efasca).
- One automatic loading coil socket for baseboard mounting (Athol or any other good make);
- One permanent crystal detector (Radio Instruments).

- A piece of ebonite former 2 in. external diameter by $3\frac{1}{2}$ in. long.
- Small quantity of No. 28 D.S.C. copper wire (40 ft.) (London Electric Wire Co.).
- Glazite for wiring.
- Two short lengths of insulated flex.
- Two spring clips. (Peto Scott).
- Six terminals. (Beiling and Lee).
- One Decko dial indicator (A. F. Bulgin).
- Four $\frac{3}{8}$ in. counter-sunk wood screws.

2-VALVE SETS.

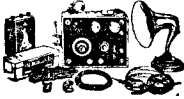

Sets complete with following accessories:
 Long distance 2-valve L.F. and Detector Receiver in handsome polished cabinet. Includes set as shown: 1 power, 1 .06 D.E. valves, tuning coils, H.T. 50-v., L.T. Aerial Equipment, 7 L.T. and L.T. Leads, 2 pairs of 4,000 ohms phones, or LOUD SPEAKER. (Marconi Tax Paid.) £4 19 6 The Lot, Carr. and Pack., 5/-
H.F. ADPHONES, all 4,000 ohms. **N. & K. STANDARD PATTERN N. & K. GENOINE**, new light-weights, 11/6, 13/8. Dr. Nesper, 10/6 and 12/11. Telefunken, adjustable, genuine (20/- model), 14/11. Brunet, 11/9, 12/11, 14/6. 3 models.
BRITISH HEAD- PHONES: Brown's Featherweight, 20/-; **Brown's A Type** (Reed), 20/-; **B.T.H.**, 15/-; **Sterling**, 21/-; **Western Electric**, 20/-; All makes stocked.

THORPE K4 VALVES! (5-pin) 9/6. Limited number. **Fine British Valves Smash High Prices! FOSKATON (RUBON)** 2-volt .06 6/11 3-2.5 .06 6/11 Post 6d. each.
RECOGNISED WEST END DISTRIBUTOR of the manufacturers of Edison Bell, Jackson's (J.B.), Polar, Igranic, Peerless, Eureka, Ferrant-Amplion, Magnum, Burnard, Lotus, Duallier, Marconi, Dorwood, Sterling, Sacco S. B.T.H., McMichael, Lisken Utility, R.L., Bowyer-Lowe, Forno, Brunet, Ormand, Newey, P. and M., etc., etc.
HOK S.—Gamos H.F., 6/8; Lissen H.F. or L.F., 10/- each. Success L.F. or H.F., 10/- each. A.J.S., 15/-, with unit 20/-.

SEE K. RAYMOND'S NAME ON PREMISES. THIS WILL ASSURE YOU GETTING THE GOODS ADVERTISED. PLEASE ASK "IS THIS RAYMOND'S?"

H.T. BATTERIES— Eveready, 21/-; L.T. 12/8; 108-v., 21/-; L.T. 12/8; for D.E. Valves, 7/6 and 9/-; Siemens H.T., 60-v., 12/6; Hellensen 60-v., 14/6. Various 1.5 D.E. Batteries 1/6 to 2/6.
EBONITE, "Grade A," cut while you wait, 3/16 at 4d. per sq. in. ch. 1/- at 2d.
"J.B."—All lines stocked S.L.F. (Brass), .0005, 11/6; .00035, 10/6. Post 6d. set. 4 in. Dial included.

DON'T FORGET TO READ THIS:
 29, Barrington Road, Brighton, S.W.9.
 30th September, 1926.
 "May I be allowed to congratulate you on the wonderful 2-valve set which you are selling for £4/19/6 complete.
 "I was fortunate enough to purchase one of these sets this week, and after very thorough tests it has proved to be perfect in every detail, giving very fine clear results, and I shall be only too pleased to recommend this set to all my friends.
 "Yours faithfully,
 "JOHN F. DREW."

ORDERS BY POST MUST BE ACCOMPANIED BY SUFFICIENT TO PAY POSTAL CHARGES.
VALVES—Cosmos S.P. 13, Red or Green, 14/-; New Erie, Sp. 14/-; All Mullard, Ediswan, Orsam, Marconi, Cosmoc, Bright, D.E. and Power, 8/-, 14/-, 18/6, 22/6, 24/6, 29/-, 29/-; Mullard PM 1, 2, 3, 4, 5, 6 stocked.

K. RAYMOND
 Hours 9.15 to 7.45
 Saturday 9 to 8.45
 Sunday 11 to 1

L I S S E N

LISSENOIA, 13/6. L.F. TRANSFORMER, 8/6, 35 OHM RHEOSTAT, 2/6. H.F. OR L.F. CHOKE, 10/-. FIELDLESS COILS, 10/-. GRID LEAKS, F. 1/-. DIALS, VARIABLE, 2/6. ALL PARTS AVAILABLE. POST EXTRA.

KAYRAY
S.L.F. CONDENSERS
 LATEST MODEL NOW READY
 With knob and dial
7/11



.0005 or .0003 Aluminium Vanes Bakelite End.
 Please note Test Report F.D., 27/26, "Amateur Wireless."
Bra's Valves 10/6 (This has 4 in. Dial) POST 6d. per set.

OUR NOTED 1-VALVE and CRYSTAL SET, in solid polished cabinet, complete with valves, phones, H.F. and L.T. Units, Aerial Equipment, Daventry Coil. Extraordinary values.
 45/11. Carriage, 2/-.
ASTOUNDING 2 Valve AM-VALUE in L.F. Amplifier, 25/11, or COMPLETE with valves, polished box, H.T. and L.T. Units, 44/6. Carriage 1/6.

Ormond products. SQUARE LAW LOW-LOSS. .0005, 9/6; .0003, 8/6 (1/6 each less no vernier). Friction Geared .0005, 15/-; .0003, 14/6; .00025, 13/6. Straight Line Frequency Friction Geared. .0005, 20/-; .00025, 19/6. S.L.F., .0005, 12/-; .00025, 11/6. **SQUARE LAW LOW-LOSS DIAL**, .0005, for Bistree Six, 12/11 each. Ormond Friction Dial, 10/6. Filament Rheostats, 2/6. 6 ohms or 30 ohms, 2/6. Potentiometer, 400 ohms, 2/6. L.K. Surodial, latest model, 15/-.

GRAMM TRIPLE-HONEY-60M. INDUCLANCE COILS. 30, 2/9; 40, 2/9; 50, 2/9; 60, 3/1; 75, 3/3; 100, 3/6; 150, 3/9; 200, 4/-; 250, 4/6; 300, 4/9; 400, 5/6; 500, 7/-; 750, 9/6; 1250, 14/-; 1500, 18/-; ALL PARTS STOCKED.

BARGAIN DEPT Make quantities of window-soiled and goods which have been taken in exchange for sale at ridiculous prices. Bargains not sent by post.

Low Loss Square Law This variable Condenser is simply marvellous value. It cannot be equalled in price or quality. .0005 or 4/11 Post 6d. set .0003
VERNI B 1/- each extra.
BURN & JONAS (Magnum Screened Coils, as delivered. Baseboard, N. Condensers, 5/-; Twin Set, Low Variable, 22/6. Magnum West End Depot.

ACCUMULATORS. 2-v. 40, 7/11; 2-v. 60, 9/6; 2-v. 30, 12/6; 2-v. 100, 14/6; 4-v. 40, 12/11; 4-v. 60, 17/11; 4-v. 80, 22/6; 6-v. 30, 28/6; 6-v. 30, 35/6. ALSO good make, 1/8 extra on each of above. Post 1/-.

AMPLION LARG STOCKS OF LOUD SPEAKERS. 38, 48, 69/-; ALL CABINET MODELS and attachments stocked.

GRAHAM - FARISEH

WEST END DEPOT. Sold on Money Back Guarantee. Fixed Condensers, 1/-, 1/6; .0003 and Grid Leak, 2/- for Series and Parallel; Grid Leaks 1/3 each.

P ILLIPS "T TROD" 4 Electrode Valve, Double Grid 8/11. Post 6d. each.

Detex Calibro Dials, 5/9; Detex Verno Dials, 4/6; Ecco H.T. Units, 55/-; Igranic Tone Control, 6/3; Star "T" Coils for Reimartz B.450, 2/6; 5X.X, 3/6; Ormond Neutralising, 4/- (for Base or Panel).

Radio Micro Valves. .06 3-v., 6/11; .25, 3-v., 6/11; Power 3, 3/6; Power 1, 9/11. (Power are 3-4 volts). Phillips 4-Electrode, 4-pin for Untidyne, 8/11. Post 6d. each.

EVERYTHING IN DEMAND Stocked for Wireless.


SCREENED COILS with base, by Burn-Jones, Magnum, and Lewcos. All Orders in Rotation.

CALE'S COLUMN

NOT SENT BY POST. Terminals with N. and W., 1d.; Nickel, 1d. Spade Base, 6 a 1d. Soldering, 3d. doz. 25 Bushes, 1d. Screw Vandyer Plugs, 2d., 3d., 4d. pair. Plug and Socket, R. or B., 3d. Staples 4 a 1d. Valve Plus, 2 a 1d. 4 or 25.A. Rod, 3d. it. Earth Tubes—Copper, 2/3; .25, 5/-; Fine 7/22. Aerial, 100 ft. 1/11; Special heavy-weight, 2/3. Phosphor Bronze, 49 strands, 100 ft., 1/- (limited). Twin Flex, R. & B., 12 yds., 1/4, 1/6, 2/-; miniature silk (Twin Flex, 6 yds., 6d.; Marconi Lightning Flex, 6 yds., 9d. Insulators, 2 for 1d. Tinned Copper, 1/16th sq. 1d. 2 ft.; D.C.C. Wire, 4th. reel, 20g, 9d.; 22g, 10d.; 24g, 11d.; 26g, 1/-; 28g, 1/1. Battery Boxes, with clips, covered leatherette, 2/11; Metal, 3/9. Ebbotte Grade "A," cut while you wait, 3/16th is 1d. sq. in., 10 is 7d. sq. in. Stock sizes cheaper: 7 by 8, 1/3; 6 by 6, 1/3; 8 by 6, 1/3; 9 by 6, 1/11; 10 by 3/-; 12 by 9, 4/-. Also cheaper quality for crystal sets. Special offer in Crystal Sets, 6/11, 7/6, 8/11, 9/6, 12/6. Also in enclosed cabinet, wonderful value, 18/11. American B.T. type oak cabinets, with baseboard, take 12 by 8 ebonite, 10/6; 12 by 9, 11/9; 16 by 8, 16/11, 18/11. Any size in 3 days. Handsome pane switches, SPDT, 1/8; SPDT 1/- (highest quality). Lightning Arresters, 1/-; Wave-length Permanent Det., 6d. Red Diamond Perm. Detector, 2/-; Labret, 2/6; Bronze, 2/6; R.L., 6/-; Crystals: Shaw's Genuine Hertzite, sealed, 8d.; Neutron Wya., 1/6; Day-zite, 2/6. Splendid enclosed Crystal Detectors, on baseboards, 1/3, 1/6. Micrometer, 1/5. Service do., 2/9 with crystal. P. and P. Switches, 1/-; Non-microphonic V.H., 1/3. Solid Rod Bb., 1/6. Baseboard, 8d. 2-way sealed Coil-Holders, 1/4, 3/11. Penton, Lotus, Polar, Newey stocked. Back of panel, W.L.L., 4/11; Kay Ray, 3/11. 20-v. H.T. Accumulator Unit—the top and all plates are removable, can be replaced or cleaned. The world's greatest bargain, per 20 volts, 5/6, 28 drills (not-h. fixing, 1/3. Phone Conds, 1/-, 1/3. L5 dl., 1/6. 1/8. H.F. and L.T. Leads, 4-wire, 1/11. One old friend, Crown "Polo" H.T. Batteries, 60-volt (not one in 1,900 has to be returned). I will change any faulty. Price 6/11. Adico, Ever-ready, Siemens, Hellensen, 60-v. and 100-v. all 11. Batteries here (Columbia always stocked). Roll up your list for a special quotation.

Grand Value in NON-MICROPHONIC VALVE HOLDERS. Board Mounting, 1/6.

Better be safe than sorry!

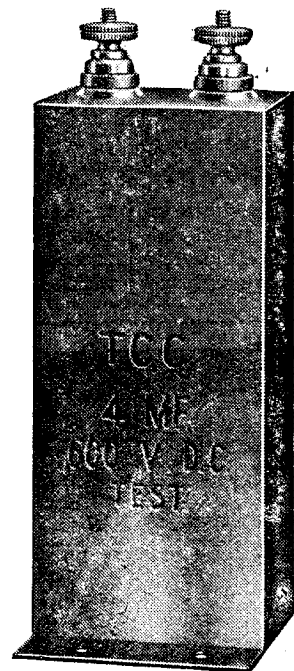

Q See that your Battery Eliminator employs T. C. C. Condensers

MOST Battery Eliminators contain Condensers which have to stand up to the full voltage of the mains. The mains supply is often as high as 250 Volts A.C., and ordinary condensers tested to 300 volts cannot be guaranteed to stand up to this pressure for a long period.

T.C.C. High-voltage Condensers. Built and tested to withstand 600 volts, the T.C.C., having been used on domestic lighting supply for a number of years, is perfectly safe and absolutely reliable. For behind it are twenty brimming years of experience in Condenser-making—years during which millions of Condensers, from large 4-ton Power models (consistently used by the G.P.O., Admiralty, War Office and Cable Companies), to the famous little green 1½-ounce Wireless Condensers have been used. In the name of safety, could there be a better choice for a Battery Eliminator than T.C.C.?

Therefore, for safety's sake, use—or see that your Battery Eliminator utilizes—the special



T.C.C. 600 volt D.C. Test Mansbridge Condensers for Battery Eliminators come in capacities of 5, 1, 2, 4, 5, 8 and 10 mfd.

T.C.C. Condensers (Tested & Guaranteed) for Battery Eliminators

Advt. Telegraph Condenser Co., Ltd., N. Acton, W.3. G.A. 6085

K. RAYMOND 27 & 28a, LISLE STREET, LEICESTER SQUARE, W.C.2.
 Back of Dal's Theatre. Nearest Tube, Leicester Square. Phone: Ger a 4637.

A SELECTIVE CRYSTAL SET—(Concluded)

WIRING INSTRUCTIONS


Join terminal A to one side of C1.
 Join other side of C1 to A1, and connect flex wire with spring clip on end to A1.
 Join flex wire with spring clip on end to one side of detector.
 Join other side of detector to 'phone terminal 1.

Join 'phone terminal 3 to E; E to moving plates of C2; moving plates of C2 to end of L2.
 Join fixed plates of C2 to beginning of L1.
 Join end of L1 to socket of holder for L3.
 Join beginning of L2 to pin of holder for L3.

diagram. This is simply done by securing by means of a brass rod, two nuts, and a piece of ebonite strip. It should be remembered

to the baseboard itself. Before assembling the variable condenser, proceed with the necessary wiring, which is tabulated. When we come to the point where it is necessary to make the connections to the variable condenser, this component may be mounted upon the panel.

The loading-coil holder chosen is designed in such a way that when the loading coil is pulled out it automatically short-circuits the holder. No shorting plug is therefore necessary when employing this particular holder. To tune in the local station, connect the aerial to terminal A or A₁, as may be desired, place the aerial tap somewhere between 30 and 60 of L₂, and the crystal tap between 0 and 30 of L₁. The best positions should be obtained by experiment. The crystal tap should not be taken below the 30th turn, as this would result in an appreciable difference in signal

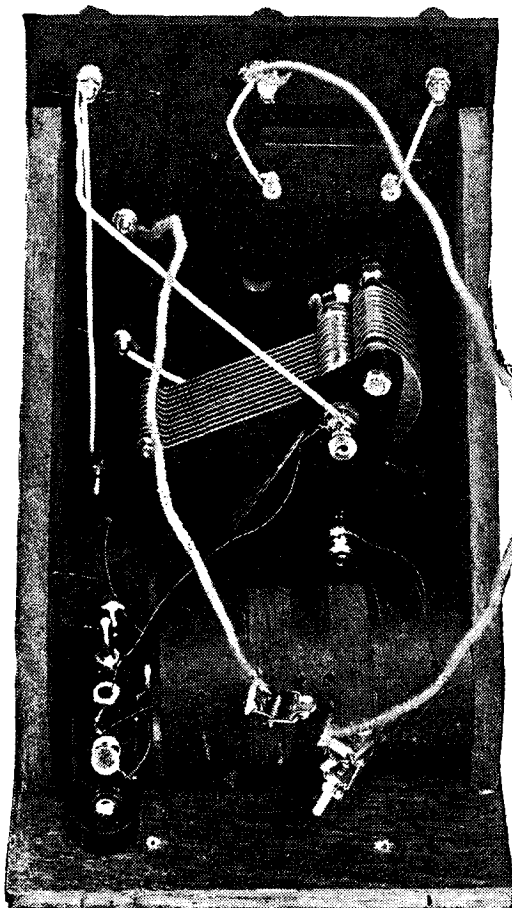

The small amount of wiring necessary may be gathered from this back-of-panel view.

that before the former is thus secured the four loose ends of the windings, which pass from the inside of the former, should be arranged conveniently for the connections to be made. When the former is secured, the loading coil socket may next be screwed on

telephone terminals are provided, thus enabling one or two pairs of 'phones to be used.

Operation

The operation is simple and easy. For reception from the local station no loading coil is necessary.

The Circuit

From the theoretical circuit shown, it will be seen that constant aerial tuning may be employed by connecting

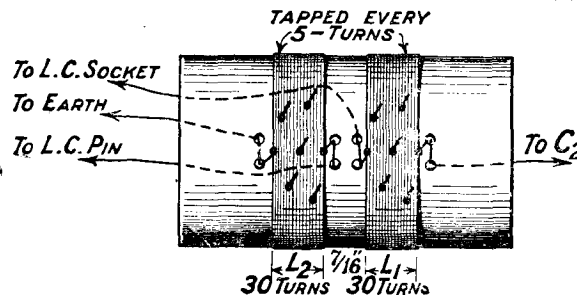


Fig. 4.—This diagram shows the method of winding the coil, and also its correct connections when completed.

the aerial to terminal A, and ordinary tuning by connecting the aerial to A₁. The value of the C.A.T. condenser chosen is .0002 microfarads. The aerial tap is used principally between tappings 30 to 60, which represent L₂. L₃ represents the loading coil. The earth in every case is connected to terminal E. Three

strength. On the other hand, the aerial tap may be taken, if desired, to almost any tapping, but the best results will probably be obtained when used as specified. With the crystal detector adjusted, it is only necessary to tune in the local station by means of the variable condenser, C₂. When 5XX is to be received it will be necessary to plug in a loading coil in the region of 200 or 250.

Test Report

The set was tried out some ten miles north-east of 2LO on a moderate out-door aerial. Both the local and high-power stations were received with ease at excellent signal strength, also Morse and one or two amateurs below 360 metres. Using two pairs of 'phones no drop in signal strength was noticeable.



TYPES & PRICES.

2 VOLT	4 VOLT	6 VOLT
<p>H. F. S.T. 21.</p> <p>Filament 1.8 volts. " 0.1 amp. Anode 40-120 volts. Impedance 26,000 ohms. Amplification 16.</p> <p>An excellent valve for H.F. amplification and resistance capacity coupling. It is also to be recommended as a detector valve.</p> <p>Price 14/-</p>	<p>H. F. S.T. 41.</p> <p>Filament 3.7 volts. " 0.1 amp. Anode 40-120 volts. Impedance 20,000 ohms. Amplification 14.2.</p> <p>This is an efficient H.F. valve more particularly designed for neutrodyne circuits. It brings in the distant stations with ease. This valve may be used as the first L.F. and as the detector valve. It is the valve for resistance capacity coupling.</p> <p>Price 14/-</p>	<p>H. F. S.T. 61.</p> <p>Filament 5.6 volts. " 0.1 amp. Anode 50-120 volts. Impedance 20,000. Amplification 19.3.</p> <p>This efficient H.F. valve is particularly to be recommended for all neutrodyne types of circuit, while it may also be used for resistance-capacity coupling. It makes an excellent detector.</p> <p>Price 18/6</p>
<p>L.F. S.T. 22.</p> <p>Filament 1.8 volts. " 0.1 amp. Anode 40-120 volts. Impedance 16,000 ohms. Amplification 10.</p> <p>This valve is for the first stage of a low frequency amplifier and will give undistorted reproduction. It may also be used for H.F. amplification, especially in neutrodyne circuits, and for detection.</p> <p>Price 14/-</p>	<p>POWER S.T. 42.</p> <p>Filament 3.8 volts. " 0.1 amp. Anode 40-120 volts. Impedance 4,800 ohms. Amplification 5.76.</p> <p>An excellent power amplifier recommended for first and also the second stage of L.F. although the S.T.43 is the ideal loudspeaker valve in the 4 volt class.</p> <p>Price 18/6</p>	<p>POWER S.T. 62.</p> <p>Filament 5.6 volts. " 0.1 amp. Anode 80-120 volts. Impedance 6,000 ohms. Amplification 8.3.</p> <p>This power valve is the best of its class and makes a good 1st and 2nd L.F. valve. It is intended especially as a good all-round power valve.</p> <p>Price 18/6</p>
<p>POWER S.T. 23.</p> <p>Filament 1.8 volts. " 0.15 amp. Anode 80-120 volts. Impedance 6,000 ohms. Amplification 6.</p> <p>A magnificent 2 volt power valve giving superb reproduction when used as the last valve of a set when a loudspeaker is employed. Note its low impedance and the high amplification factor for such a valve.</p> <p>Price 18/6</p>	<p>SUPER POWER S.T. 43.</p> <p>Filament 3.8 volts. " .25 amp. Anode 120 volts. Impedance 3,000 ohms. Amplification 4.</p> <p>This valve is the only standard 4 volt valve in the super power class, hitherto confined to 6 volt valves. It is "the valve with the golden voice" and is capable of great volume and exceptional purity of tone.</p> <p>Price 22/6</p>	<p>SUPER POWER S.T. 63.</p> <p>Filament 5.6 volts. " .25 amp. Anode 120 volts. Impedance 3,000 ohms. Amplification 4.</p> <p>This is "the valve with the golden voice." It is an entirely new class of valve having very long dead-straight dynamic curve giving exquisitely pure loudspeaker reproduction.</p> <p>Price 22/6</p>

Advt. of S.T. Ltd., 2, Melbourne Place, W.C.2.

Tell the Advertiser you saw it in "MODERN WIRELESS."

Cossor Valve Chart for Radio Press Sets

(See our advertisement on Page 543.)

IN view of the considerable number of these designs now available and their wide variation in appeal, we have prepared a special chart to assist valve users in selecting the correct types of Cossor Valves to use. This

chart embodies the results of our own investigations in combination with the staff of Radio Press, Ltd., and should be carefully followed if the best results are to be obtained.

The Elstree Six




For this set you will require three Cossor Point One Red Band Valves, and three Stentor Two's. Apply 120 volts to H.T.+1, and commence with 60 volts on H.T.+2. This latter voltage may need adjusting for the best results. The grid bias voltages on the last two valves should be 3 volts with 100 volts H.T.

The Distaflex

We recommend the use of two Stentor Two Valves for this Set, with anode voltage up to 150 volts. The grid bias is applied by separate batteries, which should be equal in voltage, 3 volts for 100 volts H.T., increasing up to 6 volts for 150 volts H.T.


The Elstree Solodyne

Here you will want two Point One Red Band Valves for the first two stages, a Point One Black Band for the detector valve, and two Stentor Two's for the low frequency stages. Apply 70 volts to H.T.+3 for the H.F. valves, 60 volts to H.T.+2 for the detector, while the voltage on H.T.+1 for the low frequency valves may be anything up to 150 volts. Grid Bias voltage of 3 or 4 1/2 volts on G.B.-1 and G.B.-2, according to the H.T. voltage on the note magnifiers.

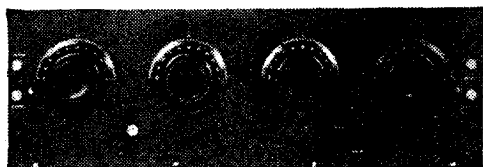

The Spanspace Three

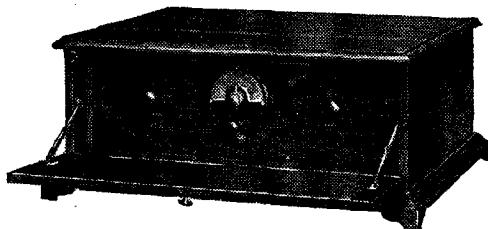We recommend the following combination. One Point One Red Band, one Black Band and one Stentor Two. The anode voltage for the first two valves may be 60 to 70 volts, while for the L.F. valve the voltage may be pushed up, the maximum being 150 volts. Grid bias up to 6 volts with the maximum H.T.



The Mewflex

This being a Reflex Receiver, a somewhat unusual arrangement of valves is called for, the following being the order: One Point One Red Band, One Stentor Two, and One Point One Black Band, for the first, second and third stages respectively. Apply 60-70 volts on H.T.+1 for the detector, and 100 to 120 on H.T.+2 for the first and reflex valves. The grid bias battery should be of 3 or 4 1/2 volts, according to the anode voltage.

The Magic Five

The combination of Cossor Valves recommended for this receiver is three Point One Red Band Valves followed by two Stentor Two's. Apply 70 volts to H.T.+1, and up to 150 volts to H.T.+2. The grid bias battery should be provided with tappings from 1 1/2 volts upwards, as G.B.1 will need 1 1/2 volts, G.B.2 and G.B.3 requiring from 3 to 6 volts according to the H.T. voltage.

The Night Hawk

Three Point One Red Band Valves for the high frequency amplifiers and two Stentor Two Valves in the last two stages. Apply 70 volts to the first valves by means of the tapping H.T.+1, and give the last two valves as much as you can up to 150 volts on H.T.+2. Grid Bias will be 3 volts for 100 H.T., increasing to 6 volts as the anode voltage is increased up to 150 volts.

The Drawing Room Five

Required: One Point One Red Band, one Black Band, two Red Band and one Stentor Two in the order given. The anode voltage on H.T.+1 for the H.F. valve should be 70 volts, 60 volts being a convenient value for the detector valve, the terminal being H.T.+2. For the resistance-coupled amplifiers apply up to 150 volts at the terminal H.T.+3, and adjust the grid bias for the first two L.F. valves to about 3 volts, the grid voltage for the last valve being up to 6 with 150 volts H.T.

Types and Prices :

BLACK BAND.	RED BAND.	STENTOR TWO.
For Detector.	For H.F. Con-	With Green
Consumption	sumption	Band. Power
1 amp. at 1 1/2	amp. at 1 1/2	Valve. Con-
volts.	volts.	sumption
		amp. at 1 1/2
		volts.
14/-	14/-	18/6

THE WINNER'S STORY

(Concluded from page 541)

visit a success, including arranging visits to valve works, high-power stations, and other points of interest, and for the way they studied my personal comfort. As a final paragraph, I was given a message to deliver to Radio Press readers to the effect that should they be in Amsterdam, if they will call at the office at Achterburgwae, 75, they will receive a cordial welcome.

R. Waldo Emerson

St. John's Wood,
London, N.W.8.

AN INEXPENSIVE RADIO PRESS STAR SET

A FURTHER addition to the series of Radio Press Star Sets is the "Spanspace Three," a set with which it is possible to obtain high selectivity combined with complete stability. These desirable features are incorporated in a set which is by no means expensive to construct, the total cost of the components required, including the cabinet, being in the neighbourhood of £8.

The "Spanspace Three" is described by G. P. Kendall, B.Sc., in the November issue of the *Wireless Constructor*, which is now on sale.


A further attraction of this issue of the *Wireless Constructor*, and one which makes it all the more vital that you should secure your copy at once, is the inclusion of a Free Gift Constructional Envelope describing how to make the "Midget Reflex" receiver. This envelope is similar in style to the Radio Press envelopes, normally sold at 2s. 6d., and contains photographs and full-size blue prints. The Free Gift of the "Midget Reflex" constructional envelope will create an enormous demand for the November issue of the *Wireless Constructor*, and you should make sure of your copy at once. The price is 6d., as usual.

Cossor Valves

Issued by A. C. Cossor, Ltd., Highbury Grove, London, N.5.

G.A. 6045.

Galvenā darbnica

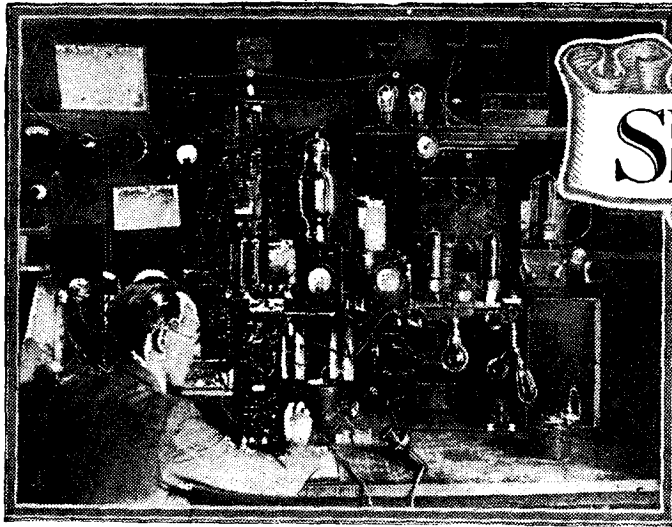

For the Short-Wave Novice

By
L.H. THOMAS (6QB)



As the writer hinted in a previous article on the subject of short-wave reception, the novice to this branch of wireless will quickly find out that the only way in which a short-wave receiver differs from an ordinary broadcast set is that

the coils have fewer turns, the condensers are smaller, and the spacing of the components must be planned rather more carefully, in order to eliminate any slight losses which might prove troublesome on these short waves.

A Difficulty

The chief difficulty which besets the beginner, however, is usually that he does not know what to listen for, or even, in some cases, on what wavelength he is listening. Although there are many commercial stations working on the shorter waves which might serve admirably as "landmarks," several of them work simultaneously on three or four wavelengths, and are thus apt to cause trouble.

45 Metres

If the reader is familiar with the Morse code, he will at once be able to identify the wavelengths of 45 metres or thereabouts, since this is the wave allotted for use by British amateurs. At most times of day or night at least twenty or thirty of them can usually be heard, so that there will be little doubt about that particular wavelength!

The procedure adopted by amateur stations when calling one another is very well known, but for the benefit of the absolute newcomer to this type of work a few words on the subject will not be out of place.

Intermediates

Each country in which amateur stations are licensed is allotted an "intermediate" letter or letters, which are sent immediately before the call-sign of the station, and serve to identify him. A list of these letters appears on this page.

These "intermediates" serve as a very useful and clear indication of the location of any trans-

NATIONALITY PREFIXES OR "INTERMEDIATES"

A: Australia	EG: Egypt	MF: Morocco	SS: Straits Settlements
AI: Tripoli, Africa	F: France	N: Holland	T: Poland
AU: Alaska	FI: French Indo-China	O: South Africa	TJ: Trans-Jordania
B: Belgium	G: Great Britain	OE: Austria	TU: Tunis
BE: Bermuda	GI: Northern Ireland	P: Portugal and Madeira	U: United States
BO: Bolivia	GW: Irish Free State	PE: Palestine	W: Hungary
BZ: Brazil	H: Switzerland	PI: Philippine Islands	X: Portable Stations
C: Canada	HU: Hawaii	PR: Porto Rico	Y: Uruguay and India
CH: Chile	I: Italy	Q: Cuba	YS: Yugo Slavia
CO: Colombia	IC: Iceland	R: Argentine and Russia	Z: New Zealand
CR: Costa Rica	J: Japan	S: Finland	
CS: Czecho-Slovakia	K: Germany	SM: Sweden	
CZ: Canal Zone, Panama	KY: Kenya Colony	SR: Salvador	
D: Denmark	L: Luxembourg		
E: Spain	LA: Norway		
	M: Mexico		

FOR THE SHORT-WAVE NOVICE—(Concluded)

mitting station that may be heard on short waves, and are used as follows:—

Australian (A) 3BQ, calling British (G) 2SZ, would transmit—2SZ 2SZ 2SZ *ga* 3BQ 3BQ, etc., and 2SZ would reply—3BQ 3BQ 3BQ *ag* 2SZ 2SZ, etc. Similarly, French (F) 8BV would call United States (U) 1CH as follows: 1CH 1CH 1CH *uf* 8BV 8BV 8BV. The letter nearest to the actual call-sign of the station being received indicates his nationality.

Times to Listen

During the day, on wavelengths between 30 and 50 metres, signals come in well from practically every country in Europe. Those from the more distant countries, generally speaking, become stronger towards the evening, and die out as darkness approaches. After dark the American signals, as well as those from various countries more than 3,000 miles distant, commence to come through. Brazilian stations are particularly strong between about 10.30 p.m. and midnight, and after midnight the United States stations reach a good strength, and may be well received until the early hours of the morning.

At about 6.30 a.m. New Zealand and Australia may usually be heard, and the former country may also be received on occasions at 6.30 p.m.

The chief point to remember is that the distant signals are often stronger than those from the nearer countries, so that it is not good practice to pick out weak signals in the hope that they are "DX." It is, in fact, best to listen to *everything* that you hear.

Modifying a Broadcast Receiver

It is often somewhat of a problem to the newcomer to short-wave work whether to build a special receiver for the purpose, or to modify the design of his broadcast receiver in such a way that it will work efficiently down to about 20 metres. This is, of course, much more easily done to-day, with the numerous makes of improved components upon the market, than it could have been done

a few years ago. In the issue of *Wireless* published on July 31, the writer described an "All-Wave Single-Valve Set," in which "Dimic" coils were used. These are quite suitable for short-wave reception on account of the low-capacity mounting employed in conjunction with them. Short-wave low-loss coils with the standard plug-and-socket base are marketed by at least one firm, and there is no reason why a receiver should not be used in conjunction with plug-in coils to cover all ranges from 15 to 20,000 metres.

Size of Condensers

The condensers, however, are apt to be rather troublesome in this case, since .0002 is quite a large value when we are concerned with waves between, say, 30 and 50 metres; anything larger may be unmanageable. Normally, a broadcast set would employ variable condensers with a capacity higher than this, generally about .0005. An easy way out of the difficulty is to make some arrangement whereby a small fixed condenser can be connected in series with the variable. The effective capacity of the latter may thus be reduced to a convenient value.

Layout

As far as the lay-out of an "all-wave" receiver is concerned, the chief point is, of course, to keep the coils in such positions that their fields will be quite clear of any large metal objects, such as L.F. transformers, variable condenser end plates, etc.

Aerial Coupling

The method of coupling the aerial to the set also needs a little alteration; it will certainly not do to take it direct on to the grid condenser—the receiver will not oscillate in these circumstances. It may, however, be connected to this point in series with a very small condenser, such as one of the many makes of neutralising condensers now on the market. Alternatively, it may be coupled inductively to the set, or may be tapped on to the grid coil at a point near the filament end.



The transmitting station owned by Mr. W.G. Sherratt, who was one of the first amateurs to establish two-way communication with Mosul, Mesopotamia.

YOU will have no difficulty in finding "THE DAILY CHRONICLE" Wireless Programme!

THIS IS A SPECIMEN.

TO-DAY'S WIRELESS PROGRAMMES.

LONDON (2LO): 365 Metres.
 1.52-2. Time from Greenwich, Camille Costantini's Orchestra, from Restaurant Frascati
 2.5-3.5. Mr. Gerald Gould and Mrs. Mary Somerville: Reading and Writing
 4.5-5. Time from Greenwich, Ethel M. Hewitt: Woman Doctors Through the Centuries
 6.15-6.50. Organ Recital by Ewaldine Foort, relayed from New Gallery Kloman.
 7.15-8.15. Children
 8.15-8.45. Radio Dance Band, directed by Sidney Brown
 9.45-10.15. Week's Work in the Garden, by the Royal Horticultural Society
 10.15-10.45. Weather and News
 10.45-11. Dr. G. C. Simpson: Thunder storm
 11.15-11.45. Mrs. Neville Chamberlain: Tuberculosis—a Preventable Disease
 12-12.15. The Passing of the Third Floor Back, arranged for broadcasting and presented by R. E. J. Harrison, Irish Book Company, Dublin
 12.15-12.45. Amy Fitzsimons-Thomson, Edmund Keay, Michael Hogan, Hector Albus, Philip Wade and Ion Swinley
 1.30-1.45. Mr. Oliver Lodge: Atoms and Worlds: The Atom of Electricity
 1.45-2. Maurice Cole (piano): Berberber
 2-2.15. Time from Greenwich, Weather and News: Local Announcements
 2.15-2.45. Philharmonic Piano Quartet: Charles Kelly (piano), Paul Beard (violin), Frank Vostok (viola), John C. Rock (violinello), Dorothy Neville (White mezzo-soprano). Narrative Poetry by Mrs. Harts, read by Richard Clowdes by Savary



Mr. Jerome K. Jerome.

3.5-4. The Passing of the Third Floor Back, arranged for broadcasting and presented by R. E. J. Harrison, Irish Book Company, Dublin
 4.15-4.45. Amy Fitzsimons-Thomson, Edmund Keay, Michael Hogan, Hector Albus, Philip Wade and Ion Swinley
 4.45-5. Mr. Oliver Lodge: Atoms and Worlds: The Atom of Electricity
 5-5.15. Maurice Cole (piano): Berberber
 5.15-5.45. Time from Greenwich, Weather and News: Local Announcements
 5.45-6.15. Philharmonic Piano Quartet: Charles Kelly (piano), Paul Beard (violin), Frank Vostok (viola), John C. Rock (violinello), Dorothy Neville (White mezzo-soprano). Narrative Poetry by Mrs. Harts, read by Richard Clowdes by Savary

BOURNEMOUTH (8BM): 386 Metres.
 3.45-4. Miss Wiltake: The Beginning of Personal Surprises, 4.45-5. Wireless String Orchestra, conducted by Capt. W. A. Featherstone, with Ben Brammall (baritone), 5.15-5.45. Children, 6.45-7.15. Picture House Orchestra, conducted by Paul Simpson, 7.45-8.15. Billy Barrow (tenor), 8.15-8.45. Billy Barrow (tenor), with Winifred Gled and Will Crane and Gary
BIRMINGHAM (5IT): 478 Metres.
 3.45-4. The Station Pianoforte Quartet: Leader, Frank Cantello, relayed from the Birmingham Weekly Post Wireless Exhibition, 4.45-5. Mr. J. Ernest Jones: Dr. Johnson and the Ladies, 5.15-5.45. Children, 6.45-7.15. Picture House Orchestra, conducted by Paul Simpson, 7.45-8.15. Billy Barrow (tenor), 8.15-8.45. Billy Barrow (tenor), with Winifred Gled and Will Crane and Gary

WHO'S WHO.

Mr. Jerome Klapka Jerome, a radio version of whose "The Passing of the Third Floor Back" will be broadcast at 8.0 to-night, has in his day played many parts—including a few as actor. He has also been schoolmaster, journalist and editor. He established his reputation as a humorist with "Three Men in a Boat," and as a more serious novelist with "Paul Kelver." Showing distant kinship with David Copperfield, his work bears resemblance in that it is the author's "favourite child."

"The Passing of the Third Floor Back" provided Sir J. Forbes Robertson with one of his most successful parts, "The Stranger"—to be played to-night by Mr. Ion Swinley.

Miss Irene Rooke, the "Miss Kite" of the play, after graduating with the Best Greek Comedy, made her first London appearance in 1897 as Ophelia to the Hamlet of Mr. Gordon Craig. She was a leading member of Miss Horniman's company at the Gaiety, Manchester, and since then has made regular appearances in the West-end theatres.

Dr. G. C. Simpson, who speaks on "Thunderstorms" at 7.10, has been director of the Meteorological Office since 1920.

DAVENTRY (5XX): 1,800 Metres.
 10.30 a.m.—Time Signal and Weather
 11.30 a.m.—Radio Quarter and Margaret Farrell (tenor), Winifred Brown (soprano)
 12-12.15. Time from Greenwich
 12.15-12.45. Radio Quarter and Margaret Farrell (tenor), Winifred Brown (soprano)
 1.30-1.45. Weather and News, 1.45-2. Shipping Forecast, 2-2.15. Programme, 2.15-2.45. Time from Greenwich, 2.45-3.15. Café de Paris Dance Band, from the Café de Paris
FOREIGN STATIONS.

Station	Time	Length	Time	Length
London	11.30-12.15	45	11.30-12.15	45
Paris	11.30-12.15	45	11.30-12.15	45
Birmingham	11.30-12.15	45	11.30-12.15	45
Bournemouth	11.30-12.15	45	11.30-12.15	45
Cardiff	11.30-12.15	45	11.30-12.15	45
Daventry	11.30-12.15	45	11.30-12.15	45
Hull	11.30-12.15	45	11.30-12.15	45
Nottingham	11.30-12.15	45	11.30-12.15	45

CARDIFF (5WA): 353 Metres.
 3.15-3.45. Mr. Isaac J. Williams: The Arts and Crafts, 3.45-4.15. Station Trio: Frank Thomas, violin; Frank Whitwell, violoncello; and Vera McComb Thomas, pianoforte, 4.15-4.45. Mr. J. Kyrle Fletcher: The Land of Arthur Machan, 5.45-6.15. Children, 6.45-7.15. E. K. 7-15 a.m.; Man and His Place in the Old Stone Age, 6.15-6.45. B.B. from London, 6.45-7.15. The Station Orchestra, conducted by Warwick Braithwaite, with Kate Winifred, soprano, 7.15-7.45. Episode of the Franco-French War, by John Oswald, 7.45-8.15. Gaiety Club: John T. Vaughan, Kate Lawley, 8.15-8.45. Evans, Lillian Mills and Donald Davies, 8.45-9.15. Orchestra from London, 9.15-9.45. Mr. Favourite, 9.45-10.15. Water Glycerin, 10.15-10.45. Walter Glynn



Miss Irene Rooke.

THINGS WORTH LISTENING FOR FROM NORTHERN STATIONS.
GLASGOW (5SC): 422 Metres.
 8.15-8.45. National Broadcasting Conference relayed from the McLehlan Galleries, Glasgow. Speakers: Sir John Gillies, M.P. (Secretary of State for Scotland), Sir Wallace Davies and Vincent Charbonnet, 8.45-9.15. Sir Wallace Davies on Broadcasting and Scottish Artistic Life, 9.15-9.45. Community Singing, conducted by Sir Wallace Davies, with the assistance of Robert Burnett, baritone, and the Glasgow Station Choir
MANCHESTER (2ZY): 378 Metres.
 10.15-11.15. George Proctor, a comedy by James Rodson. Cast includes: W. E. Dickman, Lucie Rogers and Hylda Melville. The S.O.S., dramatic sketch in one act by Adam Gowans White. Cast includes: M. H. Spottell, W. E. Dickman and Charles Nesbit. Presented by Victor Swire, Musical Inspector
HULL (5KH): 325 Metres.
 7.30 a.m. 11.15 a.m.—Symphony of Wax come to H.H.H. The Prince of Wales on his visit to Hull
NOTTINGHAM (5NG): 323 Metres.
 8.15-8.45. Third Concert of the Community Singing Society, relayed from the Albert Hall. Artists: Miss Sharpe, soloist, Harold Williams (baritone), John Leary (tenor), and the Nottingham Philharmonic Society, conducted by E. E. Hodgkinson and Alfred C. Page.

HULLO! EVERYBODY IS YOUR RECEPTION GOOD, ARE YOU GETTING THE MOST FOR YOUR ENERGIES? THE BENNETT COLLEGE WILL SHOW YOU HOW TO INCREASE YOUR EARNING POWER. HULLO! AMERICA!! HULLO! AFRICA!! HULLO! PARIS!!

WE TEACH ALL THE FOLLOWING SUBJECTS.

Having helped thousands of others to achieve success and advancement, it may be possible that we can help YOU. I am assisted by a large and expert staff, and the advice we give is sound. If we cannot help you we will say so; if we can we will tell you how. We have FREE booklets setting out the possibilities in connection with each of the subjects shown in the lists; send for the one in which you are interested, or ask for MY PRIVATE ADVICE, which also is free. You incur no obligation.

Have You ANY Ambition?

Most moderate charges, payable monthly. ALL Text Books free. No extra fees.

EXPERT TUTORS FOR EVERY DEPARTMENT.

COMMERCIAL
 Accountancy
 Advertis. Writing
 Salesmanship
 Army Cadet. Courses
 Auctioneering & Estate Agency
 Audit ng. Banking
 Book-keeping
 Commercial Arithmetic
 General Education
 Company Law
 Costing, Economics
 English and French
 Executorship Law
 Foreign Exchange
 General Education
 Modern Business Methods
 Police Entrance and Promotion Courses
 Secretaryship
 Workshop Organisation

TECHNICAL—contd.
 Concrete and Steel
 Draftsmanship
 Electricity, Engineering
 Engineering Costing,
 Quantities & Specification
 Foundry Work
 Heat Engines
 Internal Combustion Engines
 Marine Eng. B.O.T.
 Mathematics, Matriculation
 Metallurgy, Mining
 Mine Surveying
 Motor Engineering
 Naval Architecture
 Pattern Making
 Quantity surveying
 Sanitation, Shipbuilding
 Structural Engineering
 Surveying and Levelling
 Telegraphy & Telephony
 Town Planning
 Wireless Telegraphy
 Works Managers' Course

TECHNICAL
 Applied Mechanics
 Architectural Drawing
 Building Construction
 Clerk of Works' Duties
 Boiler Engineering
 Boiler Making
 Chemistry
 Civil Engineering

Yours sincerely,
J. Bennett

WE SPECIALISE IN PREPARATION FOR ALL EXAMINATIONS. WE GUARANTEE TUITION UNTIL SUCCESSFUL.

Note Address: **The BENNETT COLLEGE** Dept. 134 Sheffield

The Bennett College SHEFFIELD Dept. 134

To see on Page 2 of "THE DAILY CHRONICLE" Every Day.



Resiston comes in 17 stock sizes in Black or Mahogany-grained finish. Each Panel is protected by its own stout manilla envelope—your safeguard.

The Hall Mark



of a good Panel

Advt. American Hard Rubber Co., (Brit.) Ltd., 13a, Fore St., E.C. 2

Panel Talks: No. 2.

How can you tell a Panel's insulation qualities?

It does not take an expert to discern the superiority of one valve over another. Or the inferiority of a variable condenser of one make compared with someone else's. Yet how many amateurs know when they buy a panel whether it is efficient electrically, or whether it will only nullify the many hours spent in building a Set?

In choosing a Panel you cannot go on appearance. Only the most elaborate electrical tests can reveal to you the percentage of its insulation qualities. What then are you to do? There is one safeguard; the Hall Mark borne by every Panel made by the American Hard Rubber Co., (Brit.) Ltd., is your guarantee of perfect, hundred-per-cent insulation—in the twin

names "Radion" and "Resiston" is the key to panel-satisfaction. Resiston—like Radion—Panels are manufactured only from a basis of hard rubber—the most efficient insulating material known to Science. If you, therefore, fit a Resiston Panel to your Set you are certain that not one-per-cent of the incoming currents is lost—your signals will ever be strong and clear.

Gilbert Ad. 6077

Tell the Advertiser you saw it in "MODERN WIRELESS."



IN THE
HELLESEN
DRY BATTERIES

What truer index of quality would you desire?
THE BEST IN THE WORLD to-day as they have always been since the day they were first placed on the market, 40 years ago.

Sound construction based on ceaseless research and proved experience, expert workmanship, the realisation that an increasing market demands not only an increased output, but a better product—these are the factors which govern the Helleesen standard of production as they also form the reason why, if you buy a Helleesen Dry Battery to-day, you buy **THE BEST IN THE WORLD.**

Having chosen the best H.T. Dry Battery, a **HELLESEN**, ensure the absolute maximum service by choosing a type suitable for your set. Ask your dealer, he will advise you, or write us and we will be pleased to give you full particulars.

60 volt "WIRIN" 12/6; 99 volt "WIRUP" 21/-
(Postage Extra.)

All types, voltages, etc., in Double and Treble Capacities. Dry Batteries for Low Tension, Hand and Pocket Lamps.

From all Radio, Electrical and General Stores, Harrods, Selfridge's, Barker's, Whiteley's, etc., or direct from


A.H. HUNT, LTD. (Dept. 5), CROYDON, SURREY.

Write for leaflet No. 155a.



The "All-British Six"
(to be described in the next issue of the "Wireless Constructor")
uses **Copex O.C. Coils**

(with the patented feature).

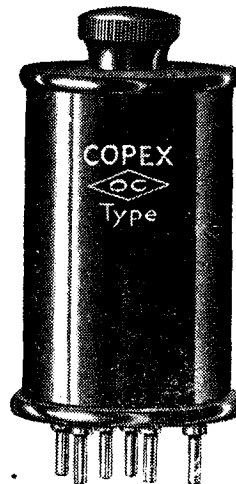

THIS Receiver won the third prize in the recent New York International Competition for Amateur Constructors' Sets (Multi-Valve Section). The successful entrant was Mr. H. E. Hassall, of London, who thus gained the highest award for any European entry. Mr. Hassall will describe his set in next month's issue of the "Wireless Constructor."

We definitely state that this Receiver is superior to any other Six-Valve Set now on the British market.

The principal advantages of Copex "O.C." Coils over all other screened coils are:—

1. Oscillation is rendered **PERFECTLY** under control.
2. High Amplification.

These factors are due to an improved and patented method of construction. Here are the prices of **Copex Coils.**

Copex Copper Screen and 6-pin base ... 15/-

Copex "O.C." Type Split Secondary Transformer 250/550M. ... 10/6

Full details of Copex Coils and Screens appear in the Copex Folder. Send a 2d. stamp for a copy to-day.

Patentees and Sole Manufacturers—

(Wound with Litz wire)

PETO-SCOTT Co., Ltd., 77, City Rd., E.C.1

Branches at 62, High Holborn, W.C.1, Walthamstow, Plymouth & Liverpool.


Copied by Many—Equalled by None

P.S. 6081



The "Eelex"
Multiple Connector Complete
Price **5/6**

Non-reversible, detachable name plates, built with Eelex standardised Plugs and Sockets. All parts are standard, detachable and interchangeable. Coloured flexibles can be supplied in the following colours: red, blue, green, yellow, black, white and maroon at 1/4d. per yard. If at any time sets change so that multiple connectors are no longer required, then the parts can be put to other uses. It will pay you to adopt the Eelex Standardised system of Connections.

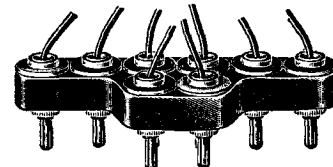

Send to-day for the Free **EELEX** List M.W.3



Eelex House, 1'8 Bushill Row.

EXPERTS IN RADIO ACOUSTICS SINCE 1908

THE "SOLODYNE"

A READER'S OPINION

SIR,—It is with very great pleasure that I give you herewith my results with the "Solodyne."

May I say, first of all, that I was doubtful that "one knob control" would be efficient, and so I left out the L.F. circuit and also used an old panel.

The wiring was finished on Sunday at 2.30 p.m., when I had a try out. As, judging by the state of the ether, several hundred others were also trying out, I switched off and waited for 3.30.

By 3.50 p.m. (i.e., within 20 minutes) I had neutralised, adjusted the variable condensers and received eight stations. In the evening I made a "tour" of the dial, but was much too interested to log anything. It was astonishing to hear station after station come in as the dial was rotated.

On Monday night I added a stage of L.F. Please note.—One stage L.F. Result: 32 stations on the loud-speaker.

A number of others were heard, but not logged as they were not loud-speaker strength. A further stage of L.F. would no doubt have brought these up, and the volume control would certainly have been needed to reduce the strength of a number of the 32.

Last night I went round the stations again and had the same excellent results. Need I say that I am highly satisfied? As the set is so ridiculously easy to operate, why not call it a family set?

In conclusion, may I congratulate you on the production of such a wonderfully efficient circuit?—Yours truly,

D. F. HOGAN.

Sheffield.


SCREENED COILS

The design of the screened coils used in Radio Press sets is the result of a careful combination of high efficiency and compactness. After experiments at Elstree certain standards have been found necessary and unless these are adhered to loss of efficiency may result.

At the time of going to press the following have been examined by Elstree and found to conform to the standard specification:—Bowyer-Lowe, Collinson, Copex, Efesca, Lewcos, Magnum.

IS THIS WHAT YOU'RE LOOKING FOR ?

TESTING the new 2-valve receiver at our Works at Slough, on a standard P.M.G. aerial, we tuned in the two Paris stations, London, Daventry, Bournemouth, Birmingham and Newcastle on the loudspeaker. This despite bad screening set up by a large power station not more than 50 yards from the vicinity of the laboratory. We were testing on 66 volts only. You can expect even better from the 3-valve Brandeset.

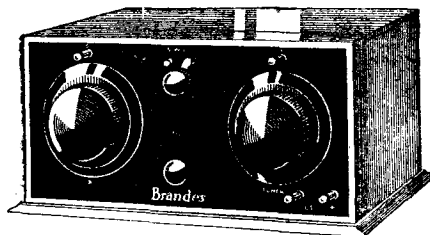

THE BRANDESET II.

The new Brandes 2-valve set features simplicity of control and ingenious compactness. Condenser dial, filament rheostat, reaction dial and "throw-over" switch for long or short wave tuning complete the panel controls. Straight line frequency condenser tuning and grid-bias

is employed. The standard coil is suitable for Daventry and no "plug-in" coils need be purchased. The L.T., H.T., and grid-bias leads are plated into one cable from rear of set.

£6 10

(Exclusive of Marconi Royalty and Accessories.)



THE BRANDESET III.

The new Brandes 3-valve receiver employs the same ingenious characteristics as the Brandeset II, except that an extra stage of Audio Frequency is employed. It has straight line frequency condenser tuning, grid-bias, and is adapted to long and

short wave tuning. Both receivers give most excellent loudspeaker reproduction on a number of stations, and are specially designed for this purpose.

£8 10

(Exclusive of Marconi Royalty and Accessories.)

Brandes

From any reputable Dealer.

BRANDES LIMITED · 296 REGENT ST. · W.1

Tell the Advertiser you saw it in "MODERN WIRELESS."


SUPER POWER



THIS is the valve with the golden voice. The very long straight Dynamic curve of the S.T. 63 and its low mean differential A.C. resistance enables it to handle the strongest signals without a trace of distortion. Try it in your last valve holder and this leader of the super-power class will give a richness of tone which you have never before achieved.

The S.T. 63 is not merely intended for demonstrations, but also for exquisite reproduction in your own drawing room. The sudden glorious high notes of a soprano or the rich low notes of the organ often cause an increase of 1,000% in the "grid voltage swing" of your valve and the ordinary power valve, perfectly competent to handle music of average strength, fails ignominiously. The S.T. 63, however, cannot "blast," but responds lightly and faithfully to every fluctuation in the music and gives that sense of reality which brings the artist to your own fireside.

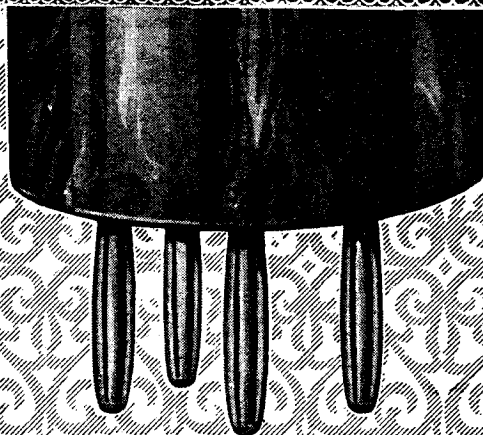Type S.T. 63 Price 22/6. S.T., Ltd., 2, Melbourne Place, W.C.2.





Performance tells

The long period of research, and expert workmanship, that have produced "Powquip" Components, would have been of no avail if the components had failed to give, not only good, but perfect performance. In the "All-Europe" Loud Speaker Set, described in "Amateur Wireless" the wonderful results obtained are only possible with the use of "Powquip" Components. A new folder giving full details of this set, and the "Powquip Coil" and "Wireless" Booklets, which will give you extra help, can be obtained on application to your dealer or to the address below.

- POWQUIP - COMPONENTS Make good sets better.

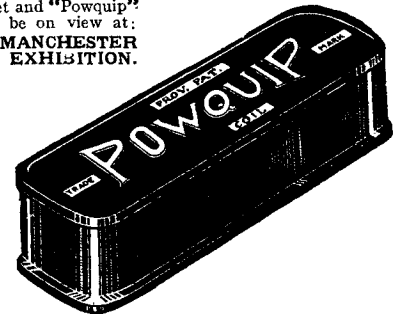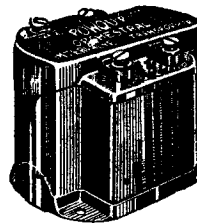The All-Europe Set and "Powquip" Components will be on view at:
STAND 63, MANCHESTER WIRELESS EXHIBITION.



THE POWER EQUIPMENT CO., LTD.,
Kingsbury Works, The Hyde, Hendon, N.W.9

ETHERPLUS

ETHERPLUS GRID LEAK

1/6
each




1/6
each

The only efficient medium priced Grid Leak. Guaranteed to be within 5% of the stated resistance. Absolutely reliable under all climatic conditions. Resistances from 25 to 5 Megohms.

From all dealers or from **M. & A. WOLFF**, 9-15, Whitecross St., LONDON, E.C.1.

FORMO

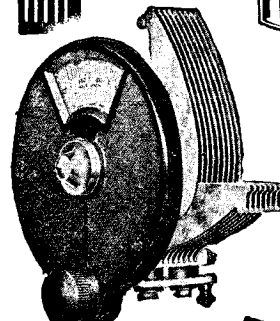

ULTRA LOW LOSS
Straight Line Frequency Condenser
Cone Bearings, Braced Vanes, Positive Collector. A real precision job.
Condenser only 0003 mfd 0005 mfd 9/-
Condenser with plain Dial Standard 10/6
No. Shaft
New Vernier Logging Dials 6/-
Reduce on Ratio 10 to 1. No Backlash.

THE FORMO COMPANY,
Crown Works, Cricklewood, N.W.2
Phone: Hamp. 1757
Manchester: Mr. J. B. Leves,
28, Fartley St., Levenshulme
Phone: Heaton Moor 47

See page 617 for Formo Transformer.

**News in
Advertisements**

A special high voltage blocking condenser for use in battery eliminators, working off the electric light mains, has been placed on the market by the Telegraph Condenser Company.

* * *

A loud-speaker on the easy payment system is advertised by W. Bullen.

* * *

A three-valve set, tunable from 40 to 2,500 metres, with silver oxydised metal panel and cabinet to match, is advertised for £17 10s. complete with all accessories, including loud-speaker by Beard and Fitch, Ltd.

* * *

The Duvarileak, a new variable grid leak, is announced by the Dubilier Condenser Co., Ltd.

* * *

Messrs. Gent and Co. advertise an H.T. battery eliminator working off A.C. mains.

* * *

A new accumulator for use with dull emitter valves is being advertised by Oldham and Sons, Ltd., of Manchester.

**A Reader's Results
with
The "Elstree Six"**

SIR,—I have built an "Elstree Six," and have had it in use during the last three weeks. I can get all the B.B.C. main stations on the loud-speaker during daylight or dark, and a large number of the Continental stations in daylight or dark, all tuned in on the loud-speaker, without any use of 'phones.

On an indoor aerial of insulated wire, about 40 feet long, strung four times across the room from the picture moulding, starting with Aberdeen, which is our local station, I can put the following stations on the loud-speaker: Aberdeen, Leipzig, Radio-Toulouse, Rome, Glasgow, Newcastle, Dublin, Hamburg, Bournemouth, Union Radio Madrid, Prague and London.

With best wishes for your continued success on the road to further improvements.—Yours truly,


A. W. CARDNO.

Peterhead.

EXPERTS IN RADIO ACOUSTICS SINCE 1908

JUST TO REMIND YOU

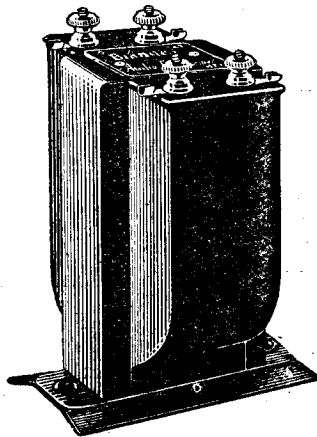WHEN you're wanting "pukka" telephones for long range work, don't forget that Brandes Matched Tone are still far and away the best. And if you are building, the 1st and 2nd stage Brandes Transformers are admirably efficient. Look at the prices!



AUDIO TRANSFORMERS

The Brandes 1st stage Transformer has a high voltage amplification ratio of 1-5. This, together with a straight line amplification curve, means that the amplification is constant over a wide band of frequencies, thus eliminating resonance.

Ratio 1-5 (black case).

The 1-3 Transformer amplifies over speech, pianoforte and harmonic ranges equally well. Mechanically protected and shielded against interaction. Terminals and outside soldering tags.

17/6

Ratio 1-3 (brown case).



MATCHED TONE HEADPHONES

The whole secret of Matched Tone is that one receiver refuses to have any quarrel with its twin. Ably schooled in these generous sentiments by our specially erected Matched Tone apparatus, their

synchronised effort discovers greater sensitivity and volume and truer tone. There is no possibility of the sound from one earpiece being half a tone lower than its mate.

20/-




Brandes

From any Reputable Dealer

BRANDES LIMITED - 296 REGENT ST., W.1

POINTS ABOUT BATTERY ELIMINATORS

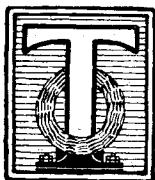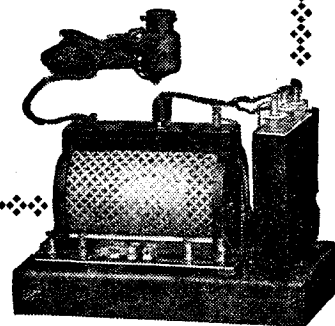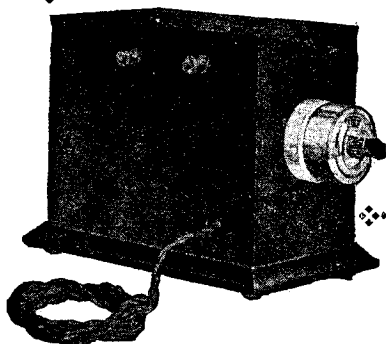By **J. H. REYNER**,
B.Sc. (Hons), A.M.I.E.E.




THE use of alternating current mains for a variety of wireless purposes is becoming increasingly popular. We have on the one hand a fair number of devices for charging low-tension accumulators from the alternating current mains. Such devices usually consist of a transformer which reduces the voltage of the mains to something of the same order as that of the battery. (Actually, of course, the secondary voltage is a little higher than the voltage of the batteries being charged, so that it can pass a current against the back E.M.F. of the battery itself.) The low-voltage alternating current is then rectified either by means of a mechanical arrangement such as

example, an ordinary two-electrode valve, then this is all that is required, because the valve will not pass more than a certain current, and in this way the charge is more or less self-regulating somewhat as in the charging set which appeared in last month's issue.

If, on the other hand, the rectifier is not limiting, then it is neces-

current, and finally there is usually some arrangement to enable different values of high-tension voltage to be tapped off the units, so obtaining different anode potentials suit-

Fig. 2.—A simple rectifying arrangement. C₁ and C₂ are smoothing condensers.

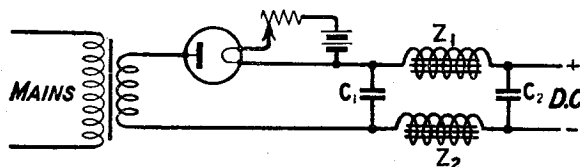

sary to see that the voltages are in the correct relation. For example, it would not be possible to charge a 60-volt accumulator direct from a 240-volt main with a rectifier which was not limiting, and it would be necessary in this case to utilise a step-down transformer to reduce the voltage of the mains to something like 80 to 100 volts.

able for the different stages in the receiver.

Underlying Principles

Now there is no doubt that arrangements such as these will be used in increasing quantities in the future, and it is desirable, therefore, that the user or prospective user should have some idea of the underlying principles upon which their operation is based. The average man has some idea that alternating current mains produce current

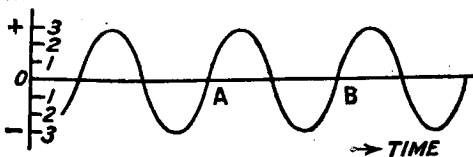


Fig. 1.—One complete cycle is denoted by the distance A B.


a vibrating reed, or by some other form of rectifier such as the Nodon valve, or some arrangement of this nature.

Charging H.T. Batteries

Another application of the alternating current mains is to the charging of high-tension accumulators. In such cases the step-down transformer may usually be dispensed with, and it is then only necessary to connect the mains direct on to the accumulator to be charged through a suitable rectifying device. If the rectifier is of a saturating type, such as, for

Battery Eliminators

Apart from the charging of H.T. accumulators, we have an increasing number of battery eliminators, the purpose of which is to supply high-tension voltage for the receiver direct from the mains without the use of any accumulator or any other battery. Such arrangements comprise—firstly, a rectifying system which converts the alternating current into uni-directional current; secondly, a smoothing system is necessary in order to smooth out the variation and fluctuation on the rectified A.C., and so convert it into more or less unvarying direct

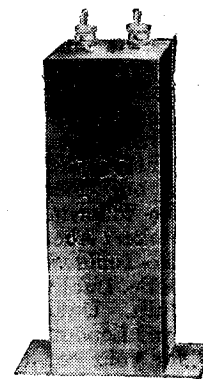


The smoothing condensers used in A. C. work should have an adequate factor of safety against breakdown.

which goes backwards and forwards, and by the use of these various devices one half of the current is


Cheaper and Better Jacks

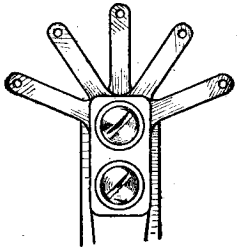Ashley Radio Jacks are made of nickel silver springs, with pure silver contact and Bakelite insulation throughout. Tags are tinned and spread fan wise for easy soldering.



Note the Prices below:


Showing how tags are fanned.

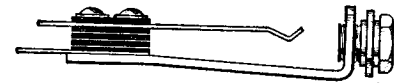


JACK No. 1. Single Circuit (Open) 1/3




JACK No. 2. Single Circuit (Closed) 1/6

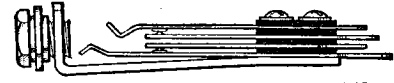

JACK No. 3. Double Circuit. 1/9

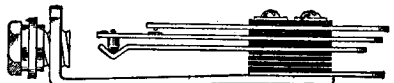

JACK No. 4. Filament Single Control 1/9

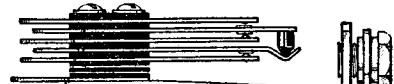

JACK No. 5. Filament Dbl. Control. 2/3

Telephone Plug



Price 1/6

Occupies less space than any other Plug. Metal parts, highly nickelled and polished. Bakelite insulation throughout, suitable for spade or pin tags, and any type of flexible or solid wire connection.

Ashley Radio

Ashley Wireless Telephone Co. (1925), Ltd.
Finch Place, London Road, Liverpool.


POINTS ABOUT BATTERY ELIMINATORS. — (Contd.)

wiped out, leaving only the currents in the same direction.

While this theory is correct in its essentials, there are one or two points upon which further information is desirable, and I propose in this article to dwell upon the theory of rectified alternating currents in a little greater detail. The subject is one of considerable interest and is also quite simple if tackled from common-sense principles. It is necessary, however, to go into the subject more or less from the beginning in order to obtain a clear idea of what is actually happening.

A.C. Waveform

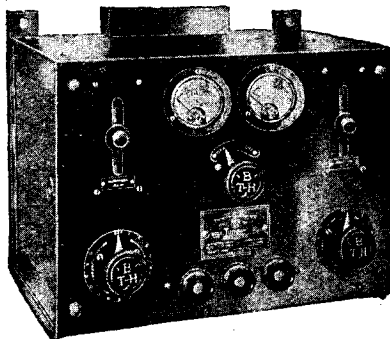Now the alternating voltage supplied by the ordinary house wiring mains is of the form shown



Battery charging units effect a considerable saving in cases where both H.T. and L.T. accumulators are used.

in Fig. 1. In one instant the voltage is zero. It then commences to grow in strength until it reaches a maximum, after which it dies away again to zero. It now commences to grow to a maximum again, but this time in the opposite direction, after which it once more falls to zero.

Thus the actual value of the voltage across the mains is continually varying, and this periodic change takes place many times per second. The actual number of complete changes per second—that is to say, between the points A and B in Fig. 1—is known as the periodicity or frequency of the system.


Frequency Values

In this country there is a diversity of frequencies. In the early days when alternating current was

TANGENT H.T. BATTERY ELIMINATOR

ELIMINATE RADIO H.T. BATTERIES!

Use the A.C. Mains.

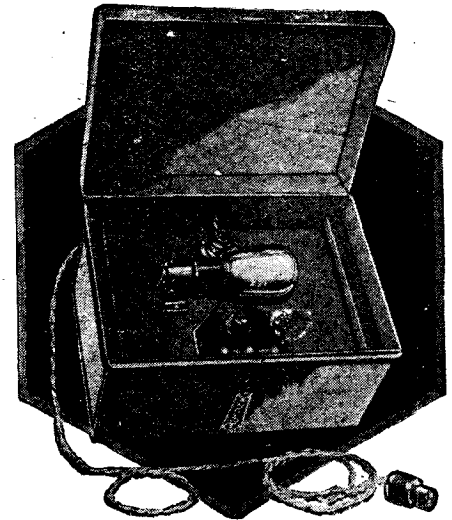

Absolutely silent in operation. Ample anode voltage and current. All component parts can be supplied separately if desired. The output is ample for even a large receiving set—20 milliamps with a variable detector voltage and amplifier voltage of 160.

Price, complete in metal case with connecting plug .. £7 15 0

Plus Marconi Royalty, 12s. 6d.

Ask for Leaflet 123A.

London: 25, Victoria Street, S.W.1.




Newcastle-on-Tyne: Targent House, Blackett Street.

GENT & CO., Ltd., Faraday Works, Leicester

Tell the Advertiser you saw it in "MODERN WIRELESS."

THE NEW LOTUS JACKS & PLUGS

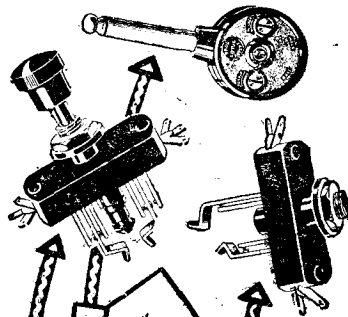

LOTUS JACK PLUGS
 Designed for use with Lotus best Bakelite plugs. The wires are placed in slots and fixed in position by a screw.
 Price: 2/-

LOTUS JACK SWITCHES
 This push-pull switch is designed to occupy the minimum space, being only 1 1/2 in. deep. Of the finest Bakelite, it has nickel silver springs and contacts of pure silver. Soldering contacts can be made to suit any wiring.
 Prices:
 No. 9, as illus. 4/-
 Others from 2/-

LOTUS JACKS
 Designed to take up the least space, the length back of panel being 1 1/2 in. Made from the best Bakelite with nickel silver springs and contacts of pure silver. Soldering contacts can be brought into any position.
 Prices:
 No. 3 as illus. 2/6
 Others from 1/3

The name 'LOTUS' is your guarantee of sound results and solid satisfaction.

From all Radio Dealers



JACKS-SWITCHES-PLUGS

Made by the makers of the famed 'LOTUS' Vernier Coil Holders and 'LOTUS' Buoyancy Valve Holders.

Garnett, Whiteley & Co., Ltd.
 Lotus Works,
 Broadgreen Road, Liverpool.

POINTS ABOUT BATTERY ELIMINATORS—(Contd.)

first introduced, there was a tendency to design the electrical side of the plant to suit the steam-engine or other prime mover which was provided, and which in the majority of cases was already in existence. This led to the adoption of all sorts of freak values of frequency.

is produced. If a current is passed through a wire, then a certain heating effect is obtained depending upon the resistance of the conductor and the amount of current flowing through it. If an alternating current is passed through the same wire, the heating effect is still

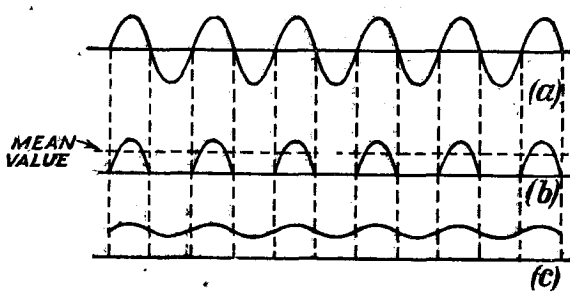


Fig. 3.—Showing how the A.C. wave form finally becomes a simple D.C. ripple after rectification and smoothing.


Standardisation

There is a distinct tendency nowadays, however, to the adoption of a single frequency of 50 cycles per second, although for power work the frequency of 25 cycles per second is also used to a considerable extent. In America, on the other hand, everything is standard 60-cycle frequency, and this naturally considerably simplifies the design of apparatus, not only in the wireless field, but throughout the whole electrical industry.

Voltage Rating

Now with a direct current mains we specify the actual voltage between two mains, and this is fixed and definite in value. What are we to specify, however, in the case of alternating current mains, where the value of the voltage is continually fluctuating? The same difficulty arises in the case of an alternating

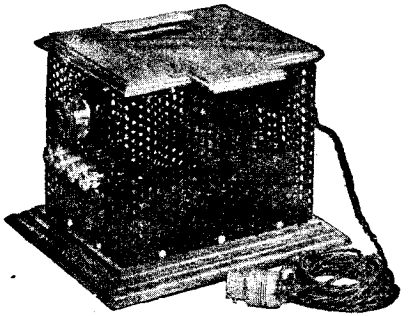produced, and this gives the clue, as it were, to the method of defining the value of an alternating current. The value is so chosen that the



H.T. units of this type may be plugged into any existing lamp socket.

current shall produce the same heating effect as a direct current. If, therefore, we pass an alter-


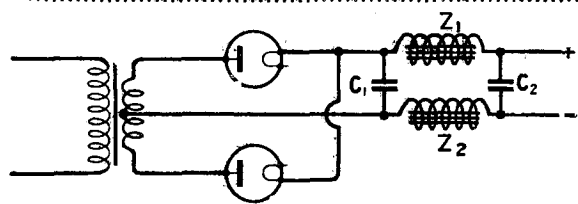


Fig. 4.—The theoretical circuit of a double wave rectifier. To retain simplicity the filament connections to the valves are not shown.

current which fluctuates in a similar manner to that of the voltage, and whatever arrangement of specification is adopted it must be suitable for both voltage and current. Now there is one property of current which is always the same, and that is the heating effect which

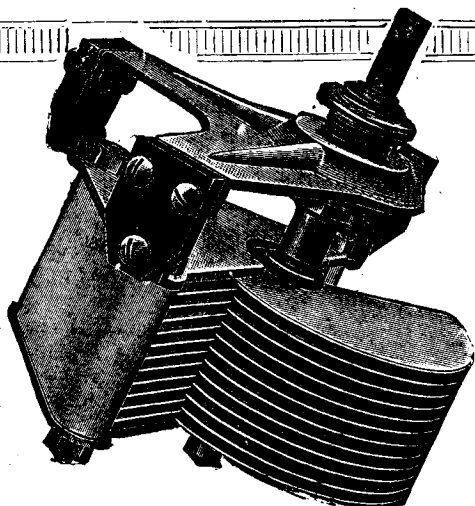nating current through a wire and obtain a certain increase in temperature, we can then pass a direct current through the wire and obtain the same temperature rise. If the value of the direct current, as measured by an ordinary ammeter, is 3 amperes, then the value of the



Prices:
Vernier Pattern
from 13.-
Without Vernier
from 7/6
(0002 mf.)

Utility

GUARANTEED

COMPONENTS

Wireless enthusiasts who "know" fit "Utility" Components. Here is the "Utility" Low Loss Condenser. The centre spindle rotates on ball bearings, all brass parts are nickel plated, pigtail connection from moving plates, one end plate only is used and all sources of loss have been reduced to a minimum. There is no better Condenser than "Utility"—and no difficulty in obtaining genuine "Utility" Components, since all good dealers stock them.


Insist upon "Utility" No-Capacity Change Over Switch, Micro Dial, Jack and Plug, Push-Pull Switch.

WILKINS & WRIGHT LTD
KENYON ST. *Utility* BIRMINGHAM
WORKS

CAXTON 4-VALVE CABINET

Made for Sets "All Concert Receiver,"
"Fieldless Coil Three Valve Set,"
"Any Valve Low Frequency Amplifier."

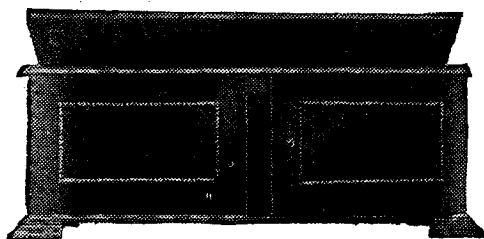Special Cabinets made to customer's measurements.
Prices Quoted.



Cash with Order. Fumed Oak ...	£1 5 0
Dark or Jacobean Oak ...	£1 10 0
Real Mahogany ...	£1 14 0

Detachable 7" deep Base Board to mount 16" by 8" panel to slide out of Cabinet front.
The two beaded front doors as illustrated, placed 2 ins. in front of the enclosed panel at 10/- extra.


Ebonite or Radion Panels Supplied and perfectly Fitted at low extra cost.

All Polished with the new enamel that gives a glass hard surface that cannot be soiled or scratched. **SENT FREE.**—Catalogue of standard Wireless Cabinets in various sizes and woods.

Packed and delivered free in U.K.

No. C2

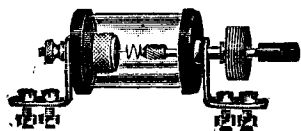CAXTON WOOD TURNERY CO., Market Harborough




"Duco" Crystal Detector (Enclosed Horizontal Type) Heavily nickel-plated brass fittings and ebonite insulation. Panel mounting.
No. RC95/1 Each 2/9

The Secret of CRYSTAL SET EFFICIENCY

Stability—the essential to satisfactory crystal reception—is dependent on the Crystal Detector. The perfect detector is practically unaffected by vibration, remaining stable where other types would fail.

"DUCO" CRYSTAL DETECTORS guarantee stability. Their design and construction provides for rigidity, and the micrometer movement ensures the very finest adjustment. Supplied in two models—perfectly dustproof—these detectors are appreciated by thousands of Crystal Set users, and are available at exceptionally low prices.

SPECIFY "DUCO" TO YOUR DEALER.

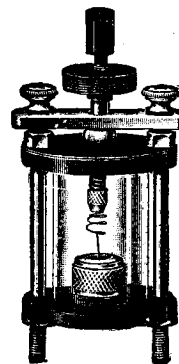

"Duco" Crystal Detector (Enclosed Vertical Type) Turned from solid ebonite, with nickel-plated fittings. Panel mounting. No. RC95/2. Each 2/9.

Brown Brothers

— Allied Companies —
THOMSON AND BROWN BROTHERS LTD
BROWN BROTHERS (IRELAND) LTD
— WHOLESALE ONLY. —
GREAT EASTERN STREET, LONDON, E.C.2
126, George St., Edinburgh, and Branches.

POINTS ABOUT BATTERY ELIMINATORS—(Contd.)

alternating current is said to be 3 amperes as well.

Root-Mean-Square Value

Now, obviously, the actual heating effect will vary from instant to instant. When the current is zero there is no heating effect at all, and when the current is at a maximum we have a much larger heating effect. The temperature which the wire will attain if an alternating current is passed through it, therefore, is the result of a mean heating effect which will be something less than the maximum.

Actually the heating effect in a wire can be shown to depend upon the square of the current at any instant. Therefore the mean heating effect is proportional to the mean value of the square of the current at each instant. The equivalent mean value of the current, therefore, is the square root of this *mean-square* value, and this has given rise to the expression *root-mean-square* value of the current or voltage.

This somewhat complicated way of choosing a mean value is neces-

sary owing to the fact that the heating effect (and in general the power produced in any electrical circuit) is proportional to the square of the current, or what is the equivalent, the product of the voltage and the current. The actual average value of the current itself is a different value altogether, and

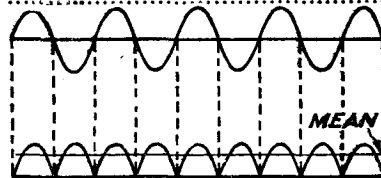


Fig. 5—The rectified voltage after two-wave rectification is as shown above.

is actually somewhat less than the root-mean-square or R.M.S. value. In the case of an ordinary alternating current of sine wave form, the R.M.S. value is 1.1 times the mean value.

Maximum Voltage


The point which should be noted is that the rated value of any alter-

nating current mains is considerably less than the maximum voltage, which may be nearly 50 per cent. higher than the R.M.S. or rated value. This fact was mentioned last month in discussing the H.T. charging unit, and it is a point which is often overlooked. It has an important bearing upon the design of apparatus for operation of alternating current mains, since the various components have to be designed to withstand a higher voltage than appears to be the case at first sight.

Smoothing Condensers


This particularly refers to the use of condensers in smoothing units and similar devices. It is necessary in such to employ fairly large condensers to act as reservoirs or smoothing condensers in such circuits and so to reduce the fluctuation to a small value. The circuit shown in Fig. 2 is a representative case. Here the alternating voltage from the mains is stepped down to a suitable value by means of the transformer. The output from the

A word from Professor Low

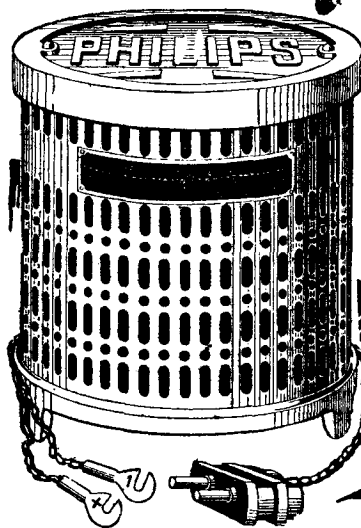

"There seems no end to their utility, and I have seldom come across apparatus so capable of hard use without requiring any attention whatever. They are excellent in every way."

(Signed) A. M. LOW.

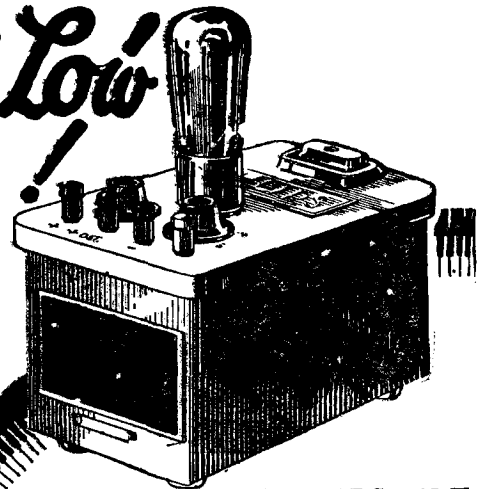

PHILIPS H.T. SUPPLY UNIT
GIVES AN UNLIMITED AND STEADY FLOW OF CURRENT THAT WILL OPERATE A SET OF ANY SIZE AT A COST THAT IS ALMOST NEGLIGIBLE. WHILE IN ACTION IT IS PERFECTLY CLEAN AND SILENT.

Price Complete **£7.10.0**

Both Units are suitable for alternating current only.



PHILIPS RECTIFIER
CHARGES RADIO BATTERIES SILENTLY AND CLEANLY, AUTOMATICALLY REGULATING THE CURRENT SUPPLY. IT NEEDS NO ATTENTION, JUST A PLUG TO BE INSERTED IN AN ELECTRIC LAMP SOCKET, THE WIRES TO BE CONNECTED TO THE BATTERY, AND THE WHOLE OUTFIT CAN BE FORGOTTEN.
Price Complete **£4.15.0**

Advt: Philips Lamps, Ltd., Philips House, 145, Charing Cross Rd., London, W.C.2.


Tell the Advertiser you saw it in "MODERN WIRELESS."

**POINTS ABOUT BATTERY
ELIMINATORS — (Contd.)**

secondary of the transformer is then rectified by means of an ordinary two-electrode valve, and this gives us pulsating current of the form shown in Fig. 3 (b).

These pulsating currents may be considered as being made up of a mean value, and a ripple or fluctuation on top. Now we have to eliminate this ripple as far as possible, and leave ourselves with the steady component of the rectified voltage, and this is done by a combination of choke coils and condensers.

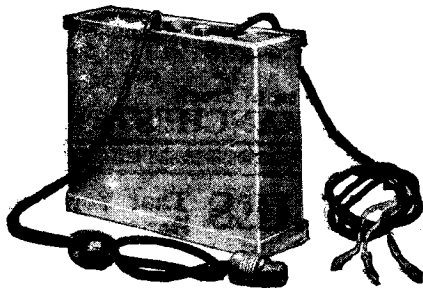The condensers take a little time to charge up, and this tends to resist the rise in voltage above the mean value, while they also take a certain time to discharge and thus



An H.T. Battery eliminator is quite a simple and compact device.

oppose any fall in the voltage on the other hand.

Choke Coils

The choke coils, while offering very little opposition to the direct current, tend to oppose any change in the current, and thus further assist in reducing the actual value of the fluctuation. The final result, therefore, is that the voltage output appears somewhat as shown in Fig. 3 (c), which will be seen to be a constant value with only comparatively small fluctuations.


Double-Wave Rectifiers

In Fig. 4 we have a double-wave rectifier in which both halves of the alternating current have been rectified. This arrangement demands the use of a split transformer, so that one half of the wave can go through one rectifying valve and the other half through the other one. The two rectified outputs are arranged to be both in the same direction, and the

EXPERTS IN RADIO ACOUSTICS SINCE 1908

**TWO NEW
CONE SPEAKERS**

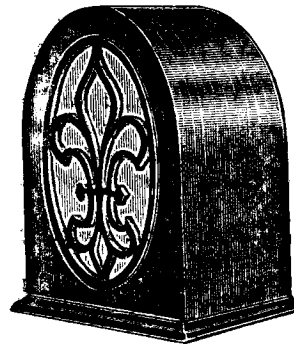THE Ellipticon has been described as "the best loudspeaker on the market" by one who is fully qualified to judge, and who has no personal interest in our success. And we honestly consider that it is one of the best instruments we have ever turned out. The Tablecone, too, can really be said to be superior to similarly priced Cones.




THE ELLIPTICON

(Registered Trade Mark)

The new Brandes Cone. Undoubtedly the best loudspeaker produced, it brings tone of great depth and sweetness. The cone has a large vibrating area and a driving unit of special design. The magnets in the unit are unusually large. There is no diaphragm but a small arma-

ture which, actuated on the "push-pull" principle, reacts to the faintest impulse. The specially designed cabinet "reflects" the sound in rich and mellowed tones.
Height .. 13 1/2 ins.
Depth .. 7 1/2 ins.
Width .. 10 1/2 ins.

£5 10

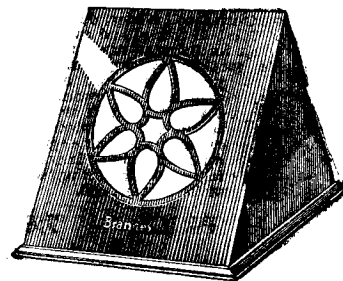

THE TABLECONE

Attractive cabinet of unique design, finished in dark walnut. The cone unit is fitted with a large magnet and the circular diaphragm has an extremely sensitive driving unit which provides plenty of volume with unblemished tone.

Supplied complete with cord connection. It has a genuine claim to be superior to any similarly priced cone speaker.
Height .. 10 ins.
Depth (at base) 11 1/2 ins.
Breadth .. 9 1/2 ins.

£2 15

Brandes

From any reputable Dealer.

BRANDES LIMITED • 296 REGENT ST. • W.1

Newey "4 Point" Condenser

An Unsolicited Testimonial

60, MELBURY GARDENS,
COTTENHAM PARK,
LONDON, S.W.20.

Dear Sirs,

I recently purchased three of your Four Point Newey Condensers for test. I had them so wired up in my receiver that on pushing down a switch I had another set of condensers made by — in circuit.

On the 24th of September, at 2.34 a.m., I was able to tune in the whole of the Dempsey-Tunney fight, from both K.D.K.A. and Station 2X.H.F., each about R.5. On pushing over the switch and tuning round I could receive nil except X's and morse.

They are the finest piece of workmanship I know of.

Yours faithfully,

(Signed) M. F. W.


6/10/26.

The original of the above letter can be seen at our offices, Phonos House, Bucknall Street, W.C.2.

The Newey Four Point Condenser is perfectly designed and constructed, and is made by All-British Labour in All-British Factories from the finest available materials.

PRICE complete with knob and dial: .0005 mfd., 17/6
.0003 mfd., 15/-

THE NEWEY VERNIER COIL HOLDER

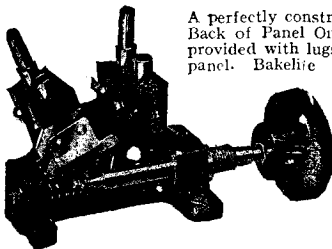

A perfectly constructed coil holder, designed for Back of Panel One-hole fixing, and in addition provided with lugs for fixing in any position on panel. Bakelite moulding throughout. Worm geared by means of metal segment and worm, and fitted with patent stop plate to prevent overwinding in extreme positions — gearing ratio 3 to 1, giving fine critical tuning and permitting the use of the heaviest coil.

PRICE - 7/6

NEWEY SNAP TERMINALS.

The Terminal with 1,000 uses. No Set complete without them.

The use of these Snap Terminals which have been reduced in price and are now only

1d. each (nickel plated 1½d.).

ensures Convenience, Simplicity, Multi-purpose, Certain Contact, Finish.

Experimental sets in boxes.

Brass 1/6. Nickel plated 2/-.

Adapters supplied in sizes
No. 2 and No. 4 B.A.


Ask your nearest dealer for the Newey Catalogue of Radio Components. If you have any difficulty, write direct.

Sole Distributors:

PETTIGREW & MERRIMAN (1925), Ltd., Phonos House,
2 & 4, Bucknall St., New Oxford St., London, W.C.2 (and Branches),
Telephone: Gerrard 4243-49. Telegrams: Merrigrew, Westcent, London.

ARTCRAFT Cabinets "Popular Type"

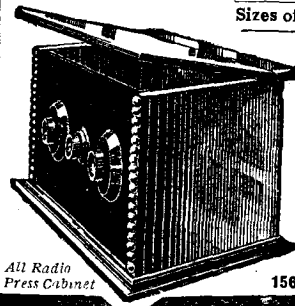Oak or Mahogany Cabinets of Artcraft design and construction are a credit to the set you build



Sizes of "Artcraft Popular Type" Cabinets

Panel Size Depth.	Price in	
	Oak.	Mahog.
9 x 6 x 6	6/0	10/0
10 x 8 x 6	8/0	12/0
12 x 10 x 8	12/0	16/0
14 x 10 x 8	14/0	18/0
16 x 8 x 8	14/0	19/0
18 x 12 x 9	21/0	29/0

Baseboards Free. Hinged Lids 1/6 extra
CARRIAGE PAID England & Wales
Illustrated Catalogue Post Free.

The ARTCRAFT Co.
156, CHERRY ORCHARD RD., CROYDON.

BUSH HOUSE

Established in the Electrical Trade since 1900.

The Largest Wireless House outside London.

CALL IN AND SEE US:
PARTS FOR

ELSTREE SIX; SOLODYNE
and all other POPULAR CIRCUITS.

Do not fail to write for it—it is sure to be in stock.


SEND FOR LIST NOW.

60 Volt Ansil H.T. Batteries 7/6 Guaranteed
100 " " " - 12/6 and post free
9 Volt Grid Bias " - 1/- over 5/-

All makes of Valves in Stock.

35, SHUDEHILL, MANCHESTER

H.T. BATTERIES That You Can Depend Upon.

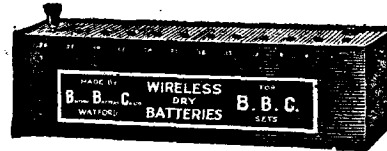

No. 4w. 36 Volts. 6/6

No. 5w. 60 Volts. 11/-

No. 6w. 9 Grid Bias 2/-


No. 10w. 4½ " " 1/-

PRICES INCLUDE WANDER PLUG CARRIAGE PAID.

No. 4w. and 5w. 3 volt tappings.
No. 6w. and 10w. 1½ volt tappings.

No. 1w. 4½ Volts. Standard Pocket Lamp Size; with patent spiral wire terminals and plug sockets to take Wander Plugs. Used Units replaced easily.

To connect in series types 1w. and 8w., insert straight Terminal in Spiral of next battery. Bend spiral and thus ensure permanent electrical connection without soldering.
Note:—1 doz. = 54 volts. PRICE 7/- PER DOZ. with Plug, car. paid.

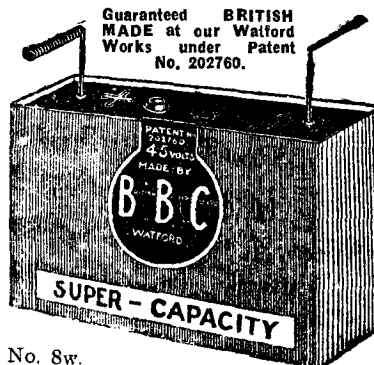


No. 8w.

To be obtained from your local dealer or direct from the
BRITISH BATTERY CO., LTD., CLARENDON RD., WATFORD, HERTS

No. 1w.
No. 8w 4½ volts Super. Capacity.
Extra Large size Unit with Patent Spiral Wire Terminal and Plug Socket to take Wander Plug. Capacity four times that of No. 1w.

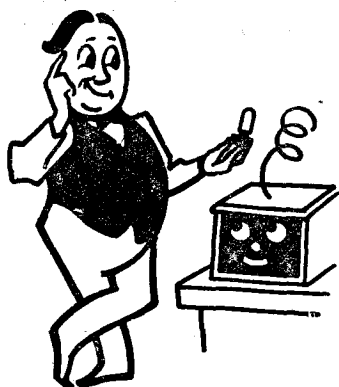
Size 3½ x 1½ x 3 inches.
PRICE 18/- PER DOZ. CARRIAGE PAID.



An idea!


GRID-LEAK and Condenser mounted out of the way on a BENJAMIN Anti-Microphonic Valve Holder. Space saved, wiring and mounting simplified. Troubles arising from faulty connections and spacing avoided. Cost of Grid-Leak clips and mounting screws saved.

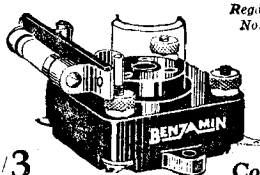Remember, also, that the BENJAMIN Anti Microphonic Valve Holder is not only infinitely superior to all its imitators in design and finish, but in actual performance too.



Regd. Design No. 722528

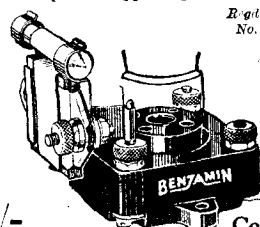5/3 Complete
VALVE HOLDER, GRID-LEAK & CONDENSER
 A Dubilier Dum-tohm 2 meg. Grid-Leak is fixed on to a rigid insulating bar by means of nickel-plated copper clips.



Regd. Design No. 722529

7/- Complete
VALVE HOLDER, GRID-LEAK & CONDENSER

Nickel-plated copper clips carry a Dubilier fixed Condenser .0003 in addition to the Grid-Leak. Series or parallel.

BENJAMIN VALVE HOLDER
 without Leak or Condenser. **Price 2/9**

From all good Dealers

BENJAMIN

BRITISH MADE

Clearer-Tone, Anti-Microphonic
VALVE HOLDER


THE BENJAMIN ELECTRIC LIMITED
 Tottenham, London, N.17

POINTS ABOUT BATTERY ELIMINATORS — (Contd.)

resultant rectified voltage before smoothing is as shown in Fig. 5. It will be seen here that the ripples are of twice the frequency and are also not so serious in character. The higher the frequency of the fluctuations the more readily can they be smoothed out, since the size of the condensers and choke coils necessary is considerably smaller. For this reason it is customary to use double-wave rectification where possible, since this considerably simplifies the smoothing operation.

An Important Point

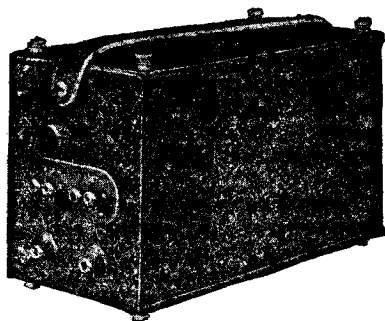The particular point to notice is that the smoothing condensers connected across the output circuits have to withstand the full value of the alternating voltage. The recti-




This battery eliminator is no larger than a medium sized hand camera.

fied output before smoothing rises from zero to the full value of the alternating current, and consequently the condenser must be able to withstand this voltage, which, as we have seen, is considerably in excess of the average value.

Shunting Values

Owing to the size of the condensers required, which are of the order of 2 to 4 microfarads or more, it is customary to employ paper-insulated condensers of the Mansbridge pattern. These condensers are constructed with a specially prepared paper having a metal deposit on one side which forms the plates of the condenser itself, while the paper constitutes the insulation. The material is actually a specially prepared form of the ordinary paper often used for wrapping up

(Concluded on page 616).

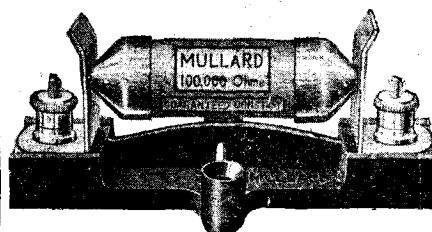

SILENT CONSTANT ROBUST

It is personal experience that counts; special sets and other people's experience are certainly of interest, but your own experience on the set that you have built, are building, or intend building is the one satisfactory test for a wire-wound resistance.

Uniformity in value, silence in operation, mechanical strength and purity of tone. Surely you are the best judge of these characteristics.

The Mullard standard of production allows one result and one only. Complete satisfaction, however severe the test.

Mullard EVER-REST Wire Wound
Anode Resistance (80,000 and 100,000 ohms) - - - 5/-

Complete with Holder 6/6

Other Values to Specification.


Mullard Grid Leaks and Condensers, Type Grid B 0.5 to 5.0 megohms ...	2/6
Type Grid B, combined with .0003 mfd. Condenser Type MA ...	5/-
Type MA Condenser .0001 to .0009 mfd. ...	2/6
Type MB Condenser .001 to .01 mfd. ...	3/-

Leaflet M.W. free on request.



WIRE WOUND ANODE RESISTANCE

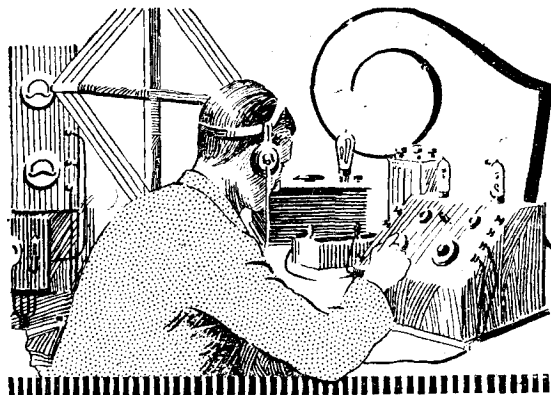The MULLARD WIRELESS SERVICE Co., Ltd.
 Mullard House, Denmark St., London, W.C.2.




Tested by Ourselves

Neutralising Condenser

MESSRS. Peto Scott Co., Ltd. have sent us one of their new pattern of neutralising condensers for test.

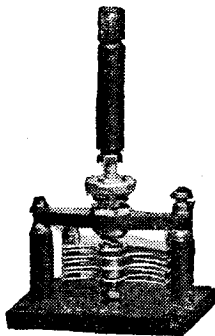In this component the spindle which carries the moving plates passes through a bush located in the centre of a bridge piece of insulating material, which is carried at the top of two pillars of similar substance fixed to the base. This forms the main bearing of the spindle, the bottom bearing being



The Peto Scott Neutralising Condenser

carried in a small metal bush screwed into the base. The fixed plates are placed well away from the moving plates, so as to obtain a low minimum, which is further provided for by the special curved shape of the opposing edges of the plates. The spindle is provided with a lock nut, so that the condenser may be locked, after the correct setting is obtained. Terminals or soldering tags may be employed when making connections.

It should be noted that two terminals are provided, one at either end of the bridge piece which carries the spindle for the moving vanes, but only one of these is in actual contact with the spindle. Care should be taken, therefore, to ensure that the terminal to which connection is made is the right one.

On test the component showed a minimum capacity of 2 micro-micro-


farads, the maximum being 19. This is quite satisfactory for all practical purposes, and can be considered as complying with the standard specification.

Battery Switch

MESSRS. Rothermel Radio Corporation of Great Britain Ltd. have submitted to us for test one of their "Yaxley" battery switches.

As the name implies, this component is intended for insertion in one of the battery leads for use as an "on-and-off" switch. A small lever actuates a cam made of insulating material, which presses against a spring contact as the knob is rotated, thus closing the circuit.

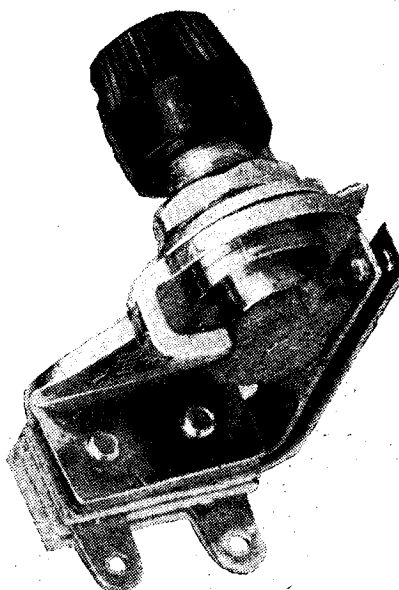Connections may be made by means of two soldering tags, and a positive stop is provided for "on" and "off" positions, which are indicated by means of a small engraved plate placed in position on the panel under the fixing nut.




The "Yaxley" battery switch.

The lever on the switch knob also serves to lock the knob on the spindle, and it is provided with a knurled end for easy withdrawal.

We can recommend this component as being a workmanlike job, and it provides a satisfactory means of making or breaking the low-tension circuit.

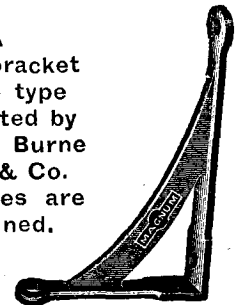A panel bracket of the type submitted by Messrs. Burne Jones & Co. The faces are machined.



Panel Brackets

MESSRS. Burne-Jones and Co., Ltd., have sent us samples of their "Magnum" Panel Brackets for test. These brackets, which appear to be constructed of cast aluminium, though light in weight, are solid and robust in construction, while both faces have been machined so that when in use the panel will be held at true right angles to the baseboard.

Each arm of the brackets is provided with two holes for fixing purposes, and this accessory can specially be recommended in cases where heavy components are mounted on the panel.

Filament Rheostat

WE have received samples of baseboard mounting Filament Rheostats from Messrs. Lissen, Ltd.

These rheostats are similar in construction to their well-known panel mounting type in that the winding is carried on a strip of insulating material which is bent round a

THE NEW MAGNETIC MICROPHONE BAR AMPLIFIER

An efficient NON-VALVE NOTE AMPLIFIER which yields Three to Ten-fold Amplification from the Phone Terminals of any Crystal or Valve Set.

NO ACCUMULATORS REQUIRED. NO H.T. BATTERIES.

Six pairs of Wireless Headphones, or any 2,000-ohms Loud Speaker may be operated from a single 3-volt Dry Battery.

LOW CURRENT CONSUMPTION

The Magnetic Microphone Bar Amplifier uses less than $\frac{1}{4}$ of an ampere, one 3-volt dry cell, at a cost of $3\frac{1}{2}$ lasting upwards of 300 working hours.

No Diaphragms. No Distortion. No fragile parts. Nothing to get out of order. No microphonic noises. Unaffected by vibration. Compact and easily portable. ANYONE CAN ADJUST IT.

Amplified Speech and Music as clear as from a good Valve Set. A boon to persons of impaired hearing

OF INTEREST TO MUSIC LOVERS.


Horns for Lissenola Gramophone Attachment.

Prices	8 in.	7/6	10 in.	10/6
	12 in.	13/6	14 in.	17/6

Swan-neck pattern, 1/- extra.

We stock components, valves and accessories of every description for sets described in this and in all other Wireless Publications. We have a highly-organised and efficient Mail Order Department, and guarantee not only safe but prompt delivery. Why waste time and money when you can send your order direct to us. Your enquiries will receive our careful and prompt attention.

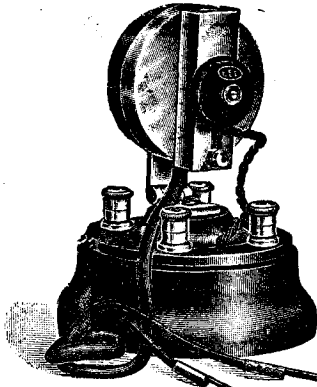Economic Electric Ltd 10, FITZROY Sq. LONDON W.1.



PRICE complete

38/-

No separate Transformer required

Pasta en Tolegrafia Virevaidos
MODERN WIRELESS
Galvena darbonica

The Duvarileak



The Variable Grid Leak
that remains
variable

No Dubilier product is placed on the market until we can be absolutely certain of its giving perfectly satisfactory results in use.

The Duvarileak has been in the experimental stage for three years.

The final result is that this Grid Leak will show a smooth and uniform variation of resistance from zero to five million ohms. More important still, by successfully discovering a resistance element of extremely hard surface and by arranging a ball-bearing contact (see inset) we have assured that the wear in operation will be negligible.

This means that the Duvarileak will, throughout its life, give a **constant resistance value for any given setting of the dial.**

Like all Dubilier products, the Duvarileak can be relied upon to give the utmost efficiency in service—it is, in fact, the perfect variable Grid Leak at last.

As seen in the illustration, it has one-hole fixing and a dial scale by which the resistance may be set.

The Duvalcon for Loud Speaker Volume control is the same in appearance and price as the Duvarileak, and is suitable for use with any Loud Speaker.


Price 7/6 of all Dealers.



ADVERTISEMENT OF THE DUBILIER CONDENSER CO. (1025), LTD., DUCON WORKS, VICTORIA ROAD, N. ACTON, W.3. TELEPHONE: CHISWICK 2241-2-3. E.P.S. 228

Cheaper than Using the Mains.

A SENSATION AT OLYMPIA EXHIBITION

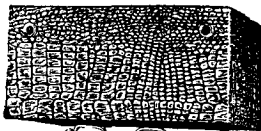

Eliminators Eliminated by

WESTAM
EVERLASTING

H.T. ACCUMULATORS

Recharge twice a year only

6^D a Volt. 2 Amps.

Entirely British. Fully Guaranteed.


60 Volt. Model, 30/-

Also 20, 30, 90, 100 & 120 volt.

Scrap your Dry Battery.


Catalogue and spare parts list from your dealer or

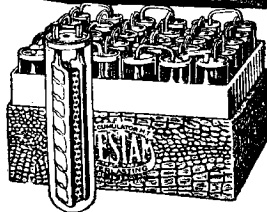WESTAM ACCUMULATORS,
CLEMENTS Rd., LONDON, E.6



Patent No. 1093626.

"TURRET" MASTS

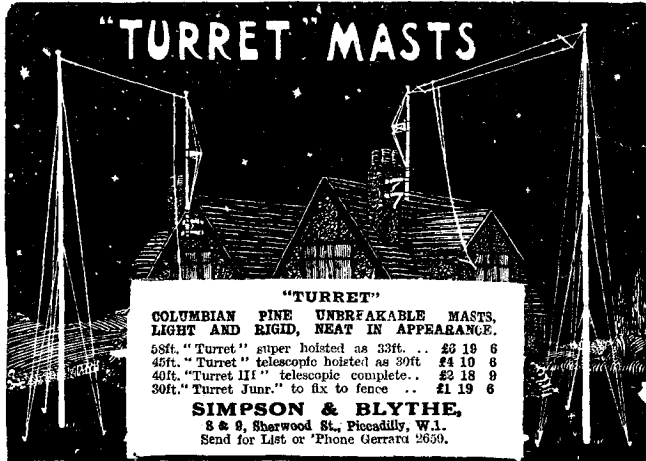

"TURRET"


COLUMBIAN PINE UNBREAKABLE MASTS,
LIGHT AND RIGID, NEAT IN APPEARANCE.

58ft. "Turret" super hoisted as 33ft. ... £5 19 6
45ft. "Turret" telescopic hoisted as 30ft. ... £4 10 8
40ft. "Turret III" telescopic complete... £2 18 9
30ft. "Turret Junr." to fix to fence ... £1 19 6

SIMPSON & BLYTHE,

8 & 9, Sherwood St., Piccadilly, W.1.
Send for List or Phone Gerrard 2650.

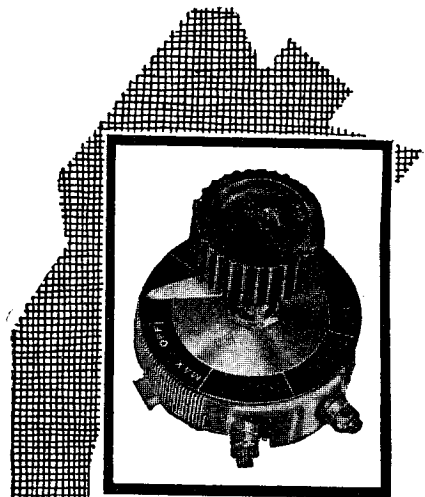Tell the Advertiser you saw it in "MODERN WIRELESS."



**The 'PEERLESS'
Junior
RHEOSTAT**

*Sales
now over
1/2
MILLION*

THE amazing popularity of "Peerless products" can be judged from the fact that the Rheostat illustrated here has already passed the HALF-MILLION Sales figure.

It has many good selling features. An OFF position is provided while definite stops make SHORT CIRCUIT IMPOSSIBLE. The resistance element is immune from damage. Will safely carry current of two valves.

Complete with nicked dial and one hole fixing. Three types; size 1 1/2" dia., 1/2" high, 6, 15 or 30 ohms.

2/6


Write for full details.

**NATIONAL WIRELESS
WEEK NOV. 7th to 13th**

Let your friends listen

**The Bedford
Electrical & Radio Co Ltd**

22, Campbell Road, Bedford.

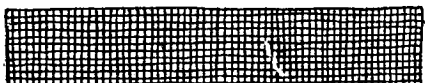

TESTED BY OURSELVES—(Contd.)

moulded insulating former. Terminals or soldering tags are provided for making connections, while a special short spindle is employed so that the rheostat may be mounted flat on the baseboard. The resistance can be set to any required value within its limits, and so long as an "on" and "off" switch is included in circuit need not be altered again.

The rheostats received were of the bright emitter type, and when placed on test it was found that they all had a resistance of 7 ohms, which is the figure given by the makers. The maximum position gives less than one-tenth of an ohm, while the wire employed is of a heavy gauge, so that several amperes can be passed through this resistance without overheating.

This component is robust in construction, and can be recommended for use.

Duros High-tension Unit

MESSRS. A.F.A. Accumulators Ltd. sent us for test one of their Duros high-tension units.

This unit is of monoblock construction, compact in size and light in weight. When discharged at a rate of 60 milliamperes its capacity is stated to be 1,800 milliamperere hours.

The plates are separated from each other by a strip moulded into the glass container, while the top of the cell is filled in with pitch, tappings being provided at every 2 volts. The vent plugs are held together on a common strip of india-rubber, this being an excellent idea, since the single vent plugs do not get lost.

Several of these units have been in use for some months as a 60-volt high-tension battery, and when originally charged their voltage was found to be in the neighbourhood of 66 volts. After two months' use the voltage still registers above 60, and the cells appear to be in excellent condition in every way; the battery is silent in action.


The makers advise giving this cell a slight boosting charge every four to five weeks, but this has not been found necessary in the case of the unit under test.

Although we have not as yet been able to give this cell a very stringent test, the results so far obtained are very favourable, and we have no hesitation in recommending this high-tension unit.

Velvet Contact Rheostat

MESSRS. M. and A. Wolff have sent us one of their "Ether-plus" velvet rheostats for test.

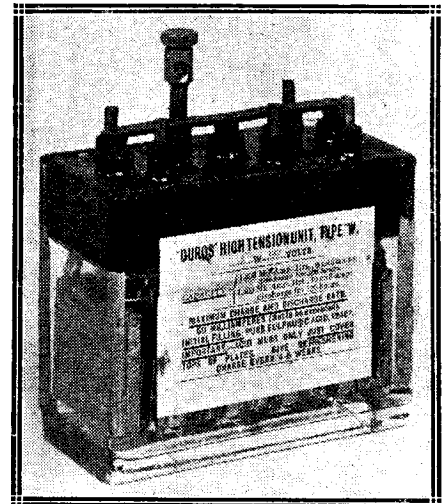The resistance element of this component is carried on a strip of fibre round which it is wound, the fibre being bent in a circle, and the two ends being fixed to a small



The Duros high-tension unit.

metal bracket. The spindle which carries the moving contact to the resistance passes through a bush fixed in the centre of the metal bracket, this bush also serving to fix the component to the panel. A small moulded knob provided with a pointer serves to control the amount of resistance in the circuit, while a clearly marked scale is provided with the instrument.


When placed on test it was found that the value of the resistance was exactly 30 ohms, which is the maker's rating. The moving contact was extremely light and amply bears out the maker's claim of velvet contact.

The component is neat and compact in construction, and its general finish is satisfactory. We can recommend it for all purposes where a 30-ohm resistance capable of carrying about half an ampere is required.



**USE
DRY CELLS INSTEAD
OF ACCUMULATORS**

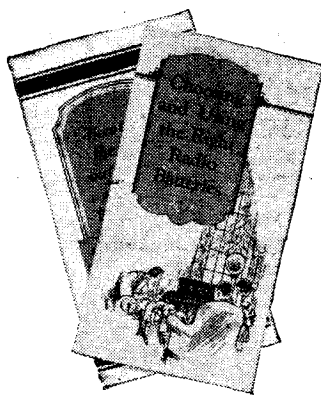COLUMBIA Dry Batteries are much safer, cleaner and convenient to handle, besides eliminating trouble and expense occasioned by the frequent recharging needed by the ordinary accumulator. You can eliminate the inconvenience of storage batteries entirely—there is a Columbia Dry Battery for every radio battery need.



Send for our useful and informative battery instruction books, "How to get the most out of your radio batteries" and "Choosing and using the right radio batteries." They are sent post free on request.

**Columbia
Dry Batteries**

Ask your Dealer for full particulars concerning the complete range of Columbia Batteries or send direct to us.

J. R. MORRIS,
15-19, Kingsway, LONDON, W.C.2.

Telegrams: Colcarprod, London.
Phone: Gerrard 3038.

Scottish Agent:
John T. Cartwright, 3, Cadogan Street, Glasgow.


**TESTED BY
OURSELVES
(Concluded)**

*"Formo" Variable
Condenser*

WE have received a Straight-Line-Frequency Condenser for test from Messrs. Formo, Ltd.

The construction of this component incorporates several novel features. Only a single bearing is employed, and this is of the cone type, arrangements being made for adjustments in the case of wearing. The stator plates are supported at one place only, the insulation being arranged so as to be out of the main field of the condenser.

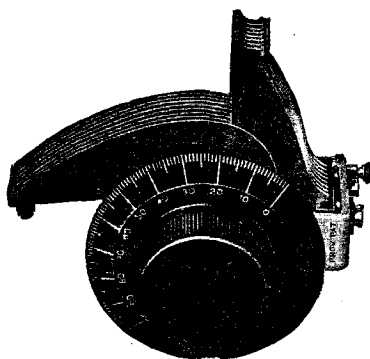As in most S.L.F. condensers, the vanes are somewhat long, and in order to eliminate any possibility of irregular spacing at the tip, small supports to both the rotor and stator vanes have been fitted. The component is of the one-hole fixing type, and is provided with a standard quarter-spindle for the



**The Formo S.L.F. variable
condenser.**

dial. Connections may be made to it either by terminals or soldering tags, as desired, while, as an additional means for connecting to the rotor plates, a copper pigtail is provided.

The capacity of the condenser is rated at .0003 by the makers and when placed on test its actual value was found to be .0003. Its minimum value was .00002 while at broadcast frequencies its losses were negligible.

The instrument is robustly constructed and well finished, and can be fully recommended.



**A Remarkable
Record**



The long line of successes which has marked the growth of Varley Bi-Duplex Wire-Wound Anode Resistances constitutes a truly remarkable record. Practically all the "Star" sets of 1926—sets which but recently have won high International Honours both in New York and Amsterdam—contain our famous Resistances. We reprint below a letter we have received from the winner of the Premier Award at the Amsterdam Radio Exhibition.

5, St. Ann's Terrace,
St. John's Wood, N.W.8.
10th October, 1926.

Messrs. The Varley Magnet Co.

Dear Sirs,—I am very pleased to tell you I have succeeded in winning the Gold Medal at Amsterdam with an "Elstree Six." When I constructed this set I was very careful to select my parts not for price but efficiency, and in doing so I selected your Anode Resistances which in my opinion are a very skilful and workmanlike product.

I have used a great number of these in the course of my experiments and sometimes they have carried 250-300 volts, but I have never found one that has failed yet, a fact which speaks very highly for them. Anyone who uses Resistances and wishes for a reliable one cannot do better than select the Varley.

I am, yours faithfully,
(Sd.) R. W. Emerson.

Varley Anode Resistances have achieved a still more remarkable record in that only one out of the enormous numbers sold has been returned as faulty.

Readers will be interested to know that the Varley Multi-cellular H.F. Choke is ideal for the "Elstree Six," the "Elstree Solodyne," the "Davlou Three," etc., sets which were published prior to the marketing of this remarkably efficient component.

Descriptive leaflets giving full particulars of sizes, prices, etc., on application.



THE VARLEY MAGNET CO.
Proprietors, Oliver Pell Control, Ltd.
Granville House, Arundel Street,
London, W.C.2. Telephone: City 5393.


POINTS ABOUT BATTERY ELIMINATORS—(Concluded from p. 611)

packets of tea. Such condensers are quite satisfactory in use, provided they are suitably chosen for the particular circuit in which they are to be employed.

Factor of Safety

Obviously, these condensers will not stand up to such a high voltage as a mica or oil-insulated condenser, but to obtain the requisite capacity with mica insulation would not only be extremely expensive, but would also be excessively bulky. Moreover, with suitable precautions the paper-insulated condenser is perfectly satisfactory and there is no need to go to the extra expense. In many cases, however, this heavy strain on the condensers is not sufficiently appreciated, and condensers are employed having an inadequate factor of safety.

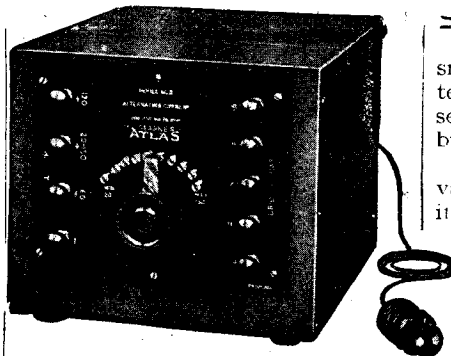The usual type of paper-insulated condenser is tested at a D.C. voltage of 300 volts. This gives an adequate factor of safety where the condenser is used as a by-pass condenser in a receiver, where the maximum H.T. voltage is 120 or 150 volts. In the case of a smoothing unit, however,



Grid Bias is provided for on this H.T. unit.

..... it is quite possible that this factor of safety would not be sufficient.

Breakdown Possible

Let us consider the case of a battery eliminator or similar device designed to operate off 240 volt mains. Now 240 volts as we have seen is the rated or R.M.S. value of the mains, and the peak value is considerably higher. With the usual type of sinusoidal wave form, the actual peak value is 1.41 times the R.M.S. value, and in this case works out at 340 volts approximately. Now, if the condensers used in the

smoothing unit have only been tested up to 300 volts, it will be seen that there is a possibility of a breakdown occurring.

With a 200 volts supply the peak value would be 280 volts, so that if this were all that had to be contended with, the ordinary type of condenser would be satisfactory. There is always, however, the possibility of a sudden surge on the line which may cause a momentary rise in the voltage which would put a strain on the condenser considerably over the rated 300 volts.

High Voltage Condensers

There are on the market condensers of this paper-insulated type which are provided with special insulation, and are actually tested on 600 volts D.C.

This, therefore, is a case where the first trouble is the least, and if a mains unit is being designed to operate off a fairly high voltage of over 150 volts, then it is preferable to use the 600 volts type of condenser and so avoid risk of possible breakdown in service.

The Moving Block Cannot Fall

The vernier movement comprises three sets of enclosed precision machine-cut gears, and reduces the speed of the moving block by eight times.

Side plates, coil blocks, and knobs in artistic bakelite mouldings. All metal parts heavily nickel plated. Made for left as well as right hand.

Patent No. 244,251

PRICES :

For outside panel mounting :-	Two-way ... 7/-
Three-way ... 10/6	
For inside baseboard mounting, with 6-in. handle :	Two-way ... 8/-
Three-way ... 12/6	

Made by the makers of the famous Lotus Buoyancy Valve Holder.

LOTUS VERNIER COIL HOLDERS

GARNETT, WHITELEY & CO., LTD., LOTUS WORKS, BROADGREEN RD., LIVERPOOL.

"YOU'LL CONVERT YOUR RIGID HOLDERS NOW."

Fig. 975. Code Word "WOBBLERS"
Per 1/6 Set of 4 (3 black, 1 red)

Full Size Illustration.

Code "DUAL" Word. PURPOSE

DOUBLE ENDED Price 1/9 each THE FOOL-PROOF HOLDER FOR BASE OR PANEL FITTING OR IN ANY OTHER POSITION.

The smallest and neatest combined holder on the market. No joints because the soldering tag is the same piece of wire as the spring. Show cards and display cards free.

Full Size Illustration.

Code "WOBBLY" Word. PRICE 2/3 each. THE IDEAL EXPERIMENTER'S HOLDER TOO SIMPLE TO IMPROVE

For the genuine experimenter who must have a holder without capacity and perfectly sprung, Hunt's "WOBBLY" is ideal. It is impossible to have fewer parts, or to better insulate, separate or spring them. Separately sprung legs are far more effective than a closed-in solid spring top.

Full Size Illustration.

Made under Patent 242057/2A, Prov. Pats. 30670/25 and 40/26, by :- **A. H. HUNT. Ltd. (Dept. 5), Croydon, Surrey.**

Galvanic discharge

CUT THIS OUT FOR CABINETS

Send for FREE list illustrating Cabinets as shown in "Modern Wireless," etc., etc.

NAME


ADDRESS

(Write in block letters please.)

CARRINGTON Mfg. Co., Ltd.
18-20, Normans Buildings, Central St., London, E.C.1.

Trade enquiries especially invited.

Telephone: Clerkenwell 6903.

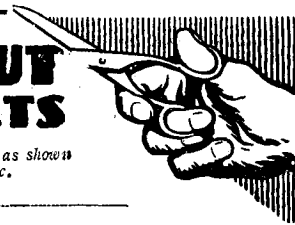


FORMO
A MONUMENT IN THE MARCH OF PROGRESS
The Formo Shrouded Transformer is the universal favourite
10/6 Made in ratios 1-1, 1-2, 1-3, 1-4 & 1-5. 1-3 & 1-5 for first and second stages.
Send for catalogue and descriptive literature of complete Formo range.
THE FORMO COMPANY, Crown Works, Cricklewood, N.W. 2, Phone Hamp. 1157, Manchester—Mr. J. B. Levee, 23, Hartley St. Levenshulme. Phone: Heaton Moor 475. See p. 692 for Formo S.L.P. code list.

QUESTIONS AND ANSWERS COUPON

Modern Wireless Vol. VI. No. 6. Nov. 1926

In future this coupon must be accompanied by a p.o. for 2/6 for each question and a stamped addressed envelope.

FREE BLUEPRINT SERVICE COUPON

Modern Wireless Vol. VI. No. 6. Nov., 1926

This coupon entitles the reader to one blueprint of any set described in the above issue, and must accompany each postal application.


—electric light in your home—?

IF SO WHY NOT GET YOUR H.T. SUPPLY FROM THE MAINS?

You can make sure of a perfect and constant High Tension supply, entirely free from crackling, hum or ripple.

TUDORADIO MAINS UNITS

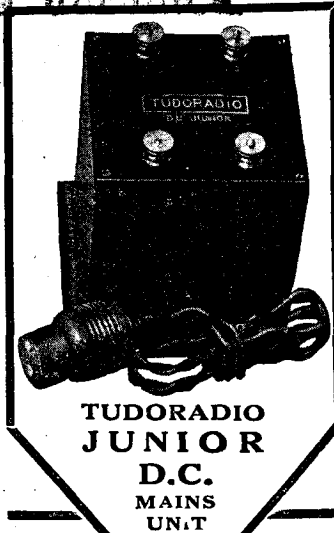can be connected to the nearest lamp socket. Current consumption is negligible, and trouble some and expensive batteries can be done away with once and for all. There are two types: D.C. for direct current and A.C. for alternating currents. There is no risk to your valves or set with either of them. Ask your dealer for details or apply direct to:



TUDORADIO JUNIOR D.C. MAINS UNIT

Output volts 100

Price **35/-** complete

THE TUDORADIO COMPANY, LIMITED, Tudor Works, Park Royal, London, N.W.10.

Telephone: Wemley 41.

OTHER MODELS FOR OTHER SETS

USE

Watmel

PRODUCTS

A LEADING valve manufacturer reports that "exceptionally good loud speaker results" were obtained with the Watmel Auto-Choke. "Speech was clear and sharp and music free from distortion."

Get full particulars of Watmel Auto-Choke, Grid Leak, and Combined Fixed Grid Leak and Fixed Condenser from your dealer, or write direct to manufacturers.

THE WATMEL WIRELESS CO., LTD.,

332a, GOSWELL ROAD, LONDON, E.C.1.

Telephone: Clerkenwell 7990.

Representative for Lancs, Yorks and Cheshire:


Mr. J. B. LEVEE, 23, Hartley St., Levenshulme, Manchester.



100% EFFICIENCY H.T. BATTERY

Constructors' Ideals realised. As tested "M.W." April, 1924, etc. Brass terminalled Giant Unit Dry Cells, 300 per cent. capacity (compare standard cell). 1½ volts, 60 volt, 14/6, carriage 1/6 Replacement cells, 4/- doz. plus carriage. Every cell replaceable. Sacs only, for wet H.T., 2/9 doz. Sample cell or sac, od. Lists free. Prompt delivery. Direct only from maker, saving 50 per cent.

C. A. FINGHETT, Old Armoury, Oswestry

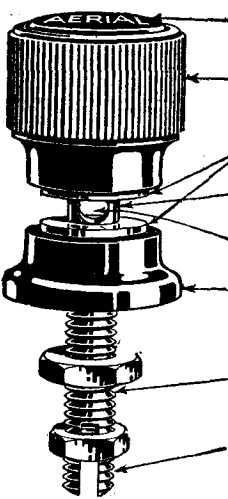

Non-rotating, insulated engraved top.
Highly-finished screw-action Bakelite-insulated head.
Shielded metal clamping faces.
Smooth stem, ensuring that strands of connecting wire will not bind up with thread.
Cross-hole for connections, flush with clamping face.
Highly-finished Bakelite-insulated collar.
Standard 2 B.A. stem with nut.
Transverse slot with clamping nut, eliminating soldering.

Patent No. 248921.
Registered Design No. 715424.

The Belling-Lee Terminal, made with 28 different engravings.
STANDARD MODEL (Bakelite-insulated) (Type B) 9d. each.
POPULAR Model (non-insulated) (Type M) 6d. each.

If you cannot get these at your dealer's, send your order to us, enclosing his name and address.

Illustrated Catalogue free on request.

BELLING-LEE

PANEL FITTINGS

BELLING & LEE, Ltd., Queensway Works, Ponders End, Middlesex, E.P.S.13

MEWFLEX RECEIVER

A winner



REGISTERED TRADE MARK

This set won second prize and a special cup at the NEW YORK INTERNATIONAL COMPETITION. It was fitted with a BECOL EBONITE PANEL.

Panel supplied in the following finishes:—

Size 24 in. by 8 in. by 1/4 in. R quality mat...	7/6
Mahogany grained polished.....	16/-
Superfine polished de luxe.....	24/-
Terminal strip 6 in. by 2 in. by 1/4 in.....	8d.

All leak-free and ready for use.

Extra for packing and postage (panel and strip) 1/-
Described in "Modern Wireless" Sept. issue.

Order immediately.

The BRITISH EBONITE Co. Ltd.

Hanwell, London, W.7.



look for it

The name "Wearite" on any component assures all-British work from design to assembly. Here is just one of the complete "Wearite" range—specially made for first-class construction at a moderate price. Write for descriptive folder of all Wireless parts.

Illustration shows "Wearite" Anti-Microphonic Low Loss Value Socket.
(Pat. applied for) LAS5, 26.

WEARITE

COMPONENTS

Lawashire Agent:
Alexander Standers,
1 B, Cooper Street,
Manchester.
Glasgow Agent:
C. G. Tideman,
47, Garri'h Street,
C.2, Glasgow.

WRIGHT & WEAIRE, LTD.,
740, High Rd., Tottenham, London, N.17
Telephone: Tottenham 3132. Telegrams: Inland, "Writeara, Totilane, London." Foreign, "Writeara, London." 186-3



5/- SECURES

5/- down and 12 monthly payments of five shillings.


"BULLPHONE NIGHTINGALE" LOUD SPEAKER

CLEAR TONE
GREAT VOLUME

POST your deposit of 5/- now and get by return the famous "Bullphone Nightingale" Loud Speaker. Individually tested and guaranteed to be superior to any other Loud Speaker regardless of price, for finish, purity and strength of tone and value. Cash Price 60/-, post free United Kingdom.

Specification.—Height 21 in., Bell Mouth 14 in. Nickel Arm and Stand. Black crystal bell head, as photo. Also de luxe model, mahogany finish bell, same size, 65/- cash or 10/- deposit. List free.

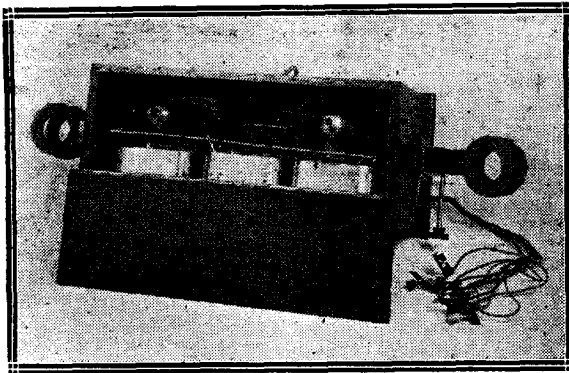W. BULLEN (Dept. M.W.1), 38, Holywell Lane, Lon'on, E.C.2.



The inside of the five-valve set (above) presents a very compact appearance. Below is seen the theoretical diagram of the circuit employed.


THE LOEWE VALVE


(Concluded from page 580.)

stations being tuned in at really good loud-speaker strength, the quality being also very good. Good loud-speaking was obtained from the local station with the H.F. stages cut out of circuit.

From the point of view of selectivity it was found that there was room for improvement. This deficiency in the matter of selectivity may be understood if the high-frequency portion of the circuit be compared with the neutralised tuned amplifiers now coming into general use.

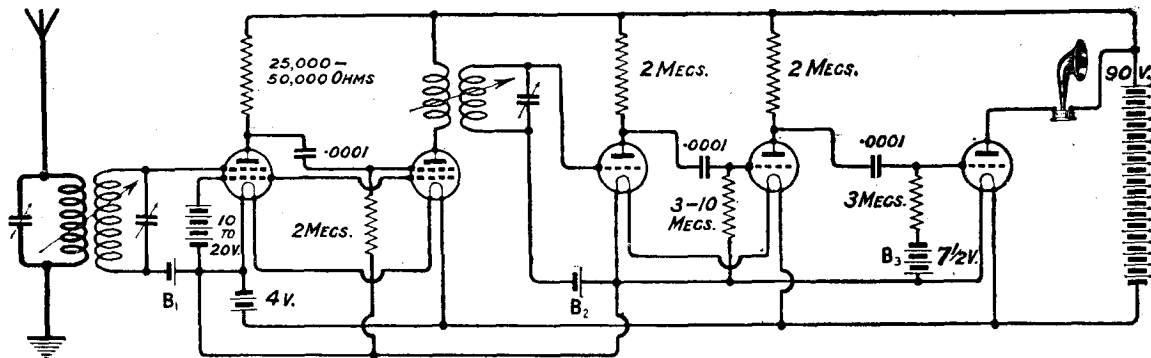Receivers built upon these amazingly compact lines present a strong appeal in view of the range and power obtainable from them, combined with simplicity of control.



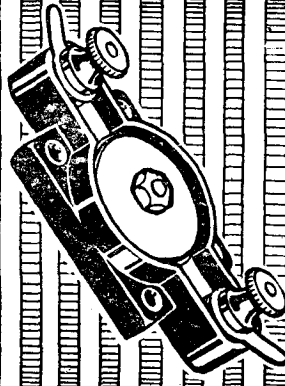

FINSTON Fixed Condensers

This season's improved model is worthy of replacing any you may have in your set.

Ruby Mica and Copper Foil Bakelite moulding. Quality Terminals and Sensible Soldering Tags.

Prices:
 '0001-2-3-4-5-6 and '001 1/- each
 '002-3-4-5 and '005 1/9 each

Get them from your Dealer and write us for Complete Illustrated Folder of all Finston Components.

FINSTON MFG. CO., LTD.
 45, Horseferry Road, London. S.W.1

Parrs Ad.

COLVERN SCREENED COIL and Low Loss Inductance Former

Complete long wave and short wave coil kits wound to standard specification.

The Elstreflex	2 9 0	The Magic Five...	4 7 6
The Monodial	2 10 0	The Elstree Solodyne	4 9 6
The Mewflex	4 14 6	A Four for Range and Selectivity	3 4 0
The Distaflex Two	4 14 6	The Screened Coil Three	2 17 0
		A Three-Valve Trap Receiver...	1 13 6

Copper Screen with Standard 6-pin Base...	8/6
Screen complete with Base and un-wound Coil	12/6
Former and Base, unwound	5/-
Former only	4/-
Base	1/6

COLLISON PRECISION SCREW CO., LTD.,

Walthamstow, London, E.17.
 Provost Works, Macdonald Road.
 Telephone—Walthamstow 532.

Also at 150, King's Cross Road, W.C.1

LUSTROLUX

The Safety Valve



THE OLD WAY



LUSTROLUX WAY

UNLESS you use the British Made Lustrolux your dull emitter valves call for two-point-something or three-point-something volts. You use a 4-volt supply, feed through the rheostat—and trust to luck about overloading.

LUSTROLUX Valves put an end to all that! Whether you want a .06 H.F. Det. or L.F., or a power valve at .34 amps, the Lustrolux Valve calls for **2 VOLTS ONLY.**

Arrange your cells in parallel and get added hours per charge. Lustrolux reception is perfection, and Lustrolux costs are amazingly low. .06 Dull Emitters, 9/-; .34 Power Valve, 11/-

ASK YOUR DEALER.

LUSTROLUX LTD.,
 West Bollington,
 nr Macclesfield.
 Send for Catalogue "M"



"Silvertown"


WIRELESS ACCESSORIES

Quality guaranteed by over 50 years electrical manufacturing experience

SILVERTOWN WIRELESS ACCESSORIES

INCLUDE—

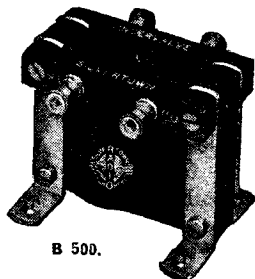- CONDENSERS (All type)
 - CRYSTAL HOLDERS
 - DIALS & KNOBS
 - EARTH PLATES
 - INDUCTANCE
 - SWITCHES (10-way, etc.)
 - INSULATORS ("Everdry," "Featherweight," Cone lead-in, Window Pane, etc.)
 - POTENTIOMETERS
 - RHEOSTATS, FILAMENT (One-hole fixing, etc.)
 - "SILVERVOX" LOUD-SPEAKERS
 - TESTING BUZZERS
 - TRANSFORMERS (all Types)
 - VALVE - HOLDERS, ANTI-MICROPHONIC VERNIOMETERS
- Etc., Etc.



B 500.


INTERVALVE TRANSFORMER.

Guaranteed for 12 months
Price 21/- each.
This Transformer has been adopted by leading manufacturers of Wireless Receiving Sets and discriminating amateurs in all parts of the world. Excellent results have been obtained on tests carried out by the National Physical Laboratory. Copy of the curve can be had on application.

THE SILVERTOWN COMPANY

106, Cannon St., London, E.C.4
Works: Silvertown, E.16.

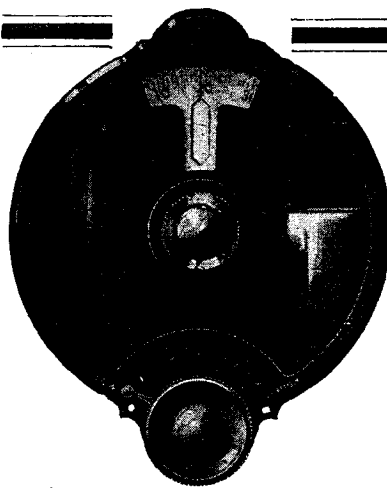BELFAST. GLASGOW. MANCHESTER
BIRMINGHAM. LEEDS. NEWCASTLE-
BRISTOL. LIVERPOOL. ON-TYNE.
CARDIFF. LONDON. PORTSMOUTH.
DUBLIN. SHEFFIELD.



VERNIER CONTROLS

National Velvet Vernier Dial
TYPE B

THE National B has been extensively used in Radio Press Sets and needs no further recommendation. It is made of bronze and brass and outlasts any set in which it is used. Smooth and regular throughout its range. No backlash exists. None can develop. Variable ratios, 6 to 1 minimum, 22

to 1 maximum, obtained instantly by shifting lever.

In pure black bakelite housing to harmonise with your panel. One hole only for mounting. Dual reading for clock or counter clockwise condensers. Post-free 15/-.

Also the National C (illuminated), in appearance similar to type B, but with transparent scale and light behind. Post free 16/6.

Fully illustrated lists (M.W.) of high-class Radio Apparatus free and post free on request.

Hamleys

Estd 1760
HAMLEY BROS. LTD.

200-202, REGENT ST., LONDON, W.1

Telegrams: "Pleasingly, Piccy."

Telephone: Regent 3160 (6 lines).

ELIMINATE HUSKINESS

FROM THIS SEASON'S RADIO
BY FITTING



BRITISH MADE, AUDIO FREQUENCY


TRANSFORMERS



TYPE
AF 3
25/-

TYPE
AF 4
17/6

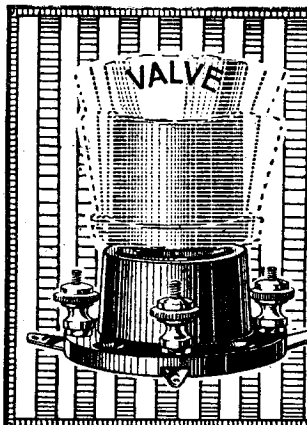ASK YOUR DEALER FOR LEAFLETS W-401 AND W 402



FINSTON Puratone Valve Holder

The name of this valve holder agrees with the quality of reproduction secured when using them in your set.

They eliminate all valve noises and absorb vibration interferences.

AN IDEAL HOLDER FOR PERFECTLY PURE RECEPTION.

Price 2/- each
(See Illustration).

Obtainable from all good dealers. Write for Complete Folder of all our Components.
FINSTON MFG. CO., LTD.,
45, Horseferry Road, London, S.W.1

Parrs Ad.

"Cabinets of Distinction"

FOR RECEIVERS AS DESCRIBED IN THIS ISSUE.

The "Drawing Room Five," (Fall Front Pattern) ..	Panel Size ..	Oak ..	70/-	Mahog. 78/-
The "Push-Pull Three" ..	14 by 7		21/-	23/6
Crystal Set (American Type Cabinet A/M) ..	6 by 8		15/6	16/6

HAND POLISHED, SOLID OAK OR MAHOGANY
COMPLETE WITH SLIDE BASEBOARD.

"PANELS OF DISTINCTION" also supplied.

Write for Illustrated Price List. Trade enquiries invited.

W. & T. LOCK, ST. PETER'S WORKS, BATH

THE "DRAWING ROOM FIVE"—(Concluded from page 535)

serve for the connections to be made here (looking at front).

Valves, H.T. and Grid Bias

For use in a set of this type resistance-coupling valves should be employed for the detector and first two note magnifiers, whilst in the last valve socket a power valve of similar filament voltage rating to the others must be used. It will be found, in most cases, that for the H.F. valve socket a further resistance - coupling type or alternatively an H.F. type will prove satisfactory. On the note magnifiers the maximum H.T. permitted by the maker's rating is to be advised, and generally 100 to 120 volts will prove satisfactory here, in conjunction with 1½ or 3 volts grid bias for G.B. - 1 and 6 or 7½ for G.B. - 2. For the detector valve, this being of resistance-coupling type, 70 to 90 volts proves satisfactory in conjunction with a single dry cell of 1½ volts for G.B.1. On the H.F. valve 60 to 80 volts proves satisfactory with a resistance-coupling type.

Aerial Connection

A suitable aerial coil should be inserted into the L₁ coil base and in the other a split-primary transformer, for the same wavelength range, should be used. With the valves plugged in, first connect the L.T. battery, and if the valves appear to light correctly connect the H.T. negative lead from the set, into the H.T. battery, join all positive leads together and tap into a low voltage socket, of the order of 4 or 6 volts, noting whether the valves light more brilliantly. If they do not do so it is probable that all is correct and the voltages previously indicated should be employed for the various valves or groups of valves.

The Radio Choke


On the lower broadcast range a No. 250 or 300 plug-in coil will serve for the radio frequency choke, but if coils for the 1,000-2,000 metre range are obtained a large choke will be required, Nos. 400 or 500 proving satisfactory.

Neutralising

The neutralising of the H.F. valve is usually by no means critical, and the procedure I generally adopt is to tune in the local station with the first valve extinguished, by placing the first base-board mounting rheostat to the off position, when upon adjusting the neutralising condenser it will be found that a point occurs where signals are reduced to minimum strength or disappear entirely.

Preliminary Testing

For a preliminary test place the reaction condenser, that is, the right-hand condenser at zero setting, and advance the two other tuning condensers by two or three degrees each at a time, when the local station should be heard. The tuning is sharp but throughout the whole lower broadcast range, with the coils which I used, the variation between the two readings was not more than five degrees, so that searching is very easy.

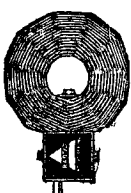

RADIAX COILS
Exceed in efficiency all ordinary types. The standard Low Loss coil is the most efficient form of all the plug-in coils, nothing but wire and air.

No. 25 1/3	No. 100 2/6
35 1/8	150 3/-
50 1/9	200 3/6
75 2/-	250 4/-

THE D.X. COIL.
For distance work gives an auto-coupled circuit without altering your set. Permits a variety of aerial tuning circuits: enables neutralising on anode circuits: makes the poor set good, and the good set a "super". Everyone needs these coils, which positively add selectivity and range.

No. 35 3/-	No. 150 5/6
80 3/6	200 6/-
75 4/-	

Set of 3 21/-
Free chat of circuits with each purchase.

THE NEW SERIES OF SUPER LOW LOSS COILS.
A type is made for all best circuits. Get the special list. These are perfectly made and finished and accurately calibrated and matched. A guaranteed Radiax proposition.

SPLIT SINGLE COILS
for anode tuning and a variety of purposes.


150/400 6/9
200/600 8/-
300/800 8/6
600/1200 8/-
1200/3000 9/-

Three-leg base, 2/3

TRANSFORMER with split primary or secondary.

150/400 10/6
300/600 10/6
600/1200 11/-
1200/3000 12/6

Six-leg base, 2/6

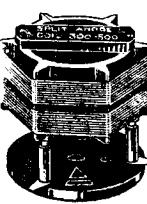

S. L. F. CONDENSER.
Real Low Loss. Smooth movement, perfect finish. A thoroughly reliable component, with dial as shown.

Single .0003 10/6
.0005 11/6


Double for Elstree Six, etc. .0005 17/-

GEARED COIL HOLDER.
Another new Radiax line of wonderful value. Beautifully made and finished. Smooth working and free from backlash.
Cat. No. 895 4/-

H. F. CHOKE.
Low self-capacity type. The successful control of reaction depends upon the Choke coil used. To build a first-class choke is by no means the simple task one might imagine, and much costly and experimental work has preceded the production of the Radiax choke, which is perfect for modern neutrodyne circuits.

Up to 150 metres	.. 7/6
150-4000 metres	.. 8/6

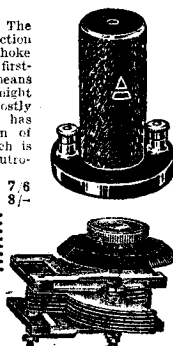GET OUR LIST of newest Low Loss Components.



RADIAX LTD.,
40, ACCESSORY HOUSE, PALM PLACE, HOLLOWAY, LONDON N.7.

ARE YOU BUILDING A WIRELESS RECEIVER ?
—then don't spoil it by using inferior components. Consult us!

GUARANTEED COMPONENT PARTS
for ELSTREE SIX, SOLODYNE, or other Circuits can be supplied for CASH or EXTENDED PAYMENTS. RECOMMENDED Components supplied, NOT SUBSTITUTES.

ELSTREE SOLODYNE.—Components including Bowyer-Lowe Condensers, Lewes Coils and Screens, Peto-Scott Neutralising Condensers, Cydon Resistors, Lissen H.F. Chokes, Cabinet, Ebonite Panel, Glazite Wire, etc. £20 0 0
Or Deposit 24 and the Balance payable over 6 or 12 months.

Wireless Specialists



"SERVICE OUR NAME AND AIM."

Wireless Dept.
273-274, HIGH HOLBORN, LONDON, W.C.1.



PELICAN
SELF-CONTAINED SETS

The two-valve set illustrated gives good loud-speaker strength and pure reproduction up to 20 miles, without either aerial or earth.

Plug-in terminals are fitted so that existing aerial and earth may be used if desired. Provision is made for use of headphones when you wish to tune in other stations.

Loud Speaker, Valves, Batteries, etc., all contained in cabinet.

PRICE COMPLETE and including royalties £19 5 0

Write for Illustrated Folder giving further details and prices of Pelican 1, 3, and 5 Valve Sets.

CAHILL & CO., LTD.,
64, FLEETMAN STREET, LONDON, W.1.

TRIUMPH

2-COIL STAND

Ref. No. C.169
PRICE 5/9




THE LATEST SUCCESS
VELVET VERNIER ACTION
Also FULLY GALVANIZED
TRIUMPH VALVE-HOLDER
(Anti-Microphonic) &
TRIUMPH RHEOSTAT.

ASK YOUR DEALER FOR ILLUSTRATED LISTS,
or send p.c., mentioning "Modern Wireless," to
A. H. CLACKSON, LTD.,
WHITE HART WORKS, LONDON, N.22

BRITISH MADE
DECKOREM

No. 2. PATTERN NO. 1. PATTERN No. 3. PATTERN



DIAL INDICATORS

*Not on ONE Set but
on EVERY ONE of the
best sets in all parts
of the world.*

No. 1. Pattern. Price 9d. Pair
No. 2. " " 3d. Each
No. 3. " " 2d. Each
Highly Nickel-plated.
*Indispensable for Fine
Tuning.*

Obtainable from every dealer.

A.F. BULGIN & CO.

9-11 CUMSTON STREET
TEL. HOLBORN 2072 CHANCERY LANE E.C.4. WORKS CHISWICK

TRADE MARK **FINEST QUALITY**

RED DIAMOND

REGISTERED

R.D. 40 Perm. Detector 2/- each.



Of all high-class Radio Dealers or
sole makers
JEWEL PEN CO. LTD. Radio Dept. 40,
21-2, Great Sutton Street, E.C.1.

LITTLE WIRELESS GADGETS

MAP

The Vernier No. 10. 1/6. 1926.

MAP Co. 246 Gt. Lister St. Birmingham

A "PUSH-PULL THREE"

(Concluded from page 557.)

Long Wave Reception

Should it be desired to receive upon the long wavelengths, the "fieldless" coil should be changed for one of long wave design; beyond this, however, the operation of the receiver is the same in every detail as that obtaining when receiving upon the ordinary broadcast band of wavelengths.

In the Crystal Palace district, where the reception of Daventry is not generally good, the present receiver gives quite good loud-speaker results without forcing the set to the limit of reaction adjustment, while Radio-Paris can also be received at much the same strength, the iron building of the Crystal Palace having some weakening effect upon the Daventry signals.

Results

Though the receiver is not intended for distance work, and it is not suggested that it be used for that class of listening, it is nevertheless possible to tune in a number of stations other than the local one; and as a matter of interest, when using the receiver with telephones as the means of hearing, such stations as Birmingham, Newcastle, Hamburg, Radio-Belgique, Cadiz, Leipzig and Frankfurt have been received at good strength.

Though some of these stations could be heard on the loud-speaker their volume does not justify, in my opinion, their being regarded as being received "on the loud-speaker"; nevertheless, they can be received at quite good telephone strength so long as the receiver is handled with due care and patience.

A LECTURE AND DEMONSTRATION

On November 9th a lecture and demonstration of the Elstree "Solodyne" will be given by Mr. J. H. Reyner, B.Sc. (Hons.), A.M.I.E.E., to the Bournville Radio Society, by whose courtesy we are enabled to offer a limited number of tickets to readers residing in the Birmingham district. Applications should be made at once to the Editor, MODERN WIRELESS, Bush House, W.C.2. Envelopes should be marked "Lecture."

STERLING RECEIVERS SENSATIONAL OFFER

Having purchased a large number of Sterling 2-Valve Loud Speaker Sets, we are offering them to the public on Unprecedented Terms.

A Genuine Sterling 2-Valve Loud Speaker Set. Complete. Ready for Immediate Use. with D.E. .06 Valves. H.T. and L.T. Accumulator, Aerial Equipment and one of our world-famed De Luxe. Excellence Loud speakers. Price £15 15s. Royalties paid.

Terms. 15s. deposit and 15 monthly payments of 20s. Send for one of these Superb Sets at once, as the Number for Sale is limited, and when sold cannot be repeated under double the price.



15/- deposit.

Free Catalogue on Application,
THE WIRELESS DISTRIBUTING CO., LTD.,
(Dept. M.W.)
Wireless House, Stoke Newington, N.16.

A HOME FOR YOUR WIRELESS SET

OUR STANDARD CABINETS

are DUSTPROOF and house the whole apparatus, leaving no parts to be interfered with. Made on mass production lines, hence the low price. Provision is made to take panels from 16 by 7 up to 30 by 18 in.

Special Cabinets for the ELSTREE SOLODYNE, NIGHT HAWK, etc., now ready. Write for free particulars.

MAKERIMPORT Co.
Dept. 2, 50a, Lord Street, LIVERPOOL.



Wireless Constructors!

To wire up your "Elstree Six," "Solodyne," etc., you must have the New and Improved

"MAYMORE" ELECTRIC SOLDERING IRON

Satisfaction Guaranteed

14/6
Post Free.

State voltage when ordering.

GOODWINS M.A. LTD.,
2-4, Edmund St., Birmingham



£2? WOULD you like a Multi-Valve Receiver for 40/- down? In Catalogue "M" are details whereby many well-known sets are obtainable on easy terms. Accessories too! Our technical advice is yours without charge. Write to-day to

New Times Sales Co.,
77, City Road, E.C.1

6140

WIRELESS SERVICE.

A Telegraph Training may enable a youth to qualify for Wireless, but why risk it, when he can take the Training with the Wireless Service behind it? 500 men required in next eighteen months.

Write to-day.

RADIO MARITIME, 7, Broadway Chambers,
Hammersmith, W., and St. Mary Street, Cardiff.

Harmonics with the Best Furniture.
AGAR'S HIGH-CLASS RADIO CABINETS
TO CUSTOMERS' REQUIREMENTS.
W. H. AGAR, 19, Whitecross Place, E.C.2.

WET H.T. BATTERIES


British made (round or square) Leclanche Glass Jars, 2 1/2 x 1 1/2 x 1 1/2, for wet H.T. Units. Wax-d. 1.3 doz. pl. in 1 doz. Zincs, 11 doz. Grade 1 Sacs, 1 doz. Grade 2 Sacs, 1/3 doz. Carriage and packing ext. 6. Finn Glas. Battery Co., 46, St. Mary's Rd., Leyton, E.10



AERMONIC cost a shilling less—and they're better, Air-spaced, Anti-phonio. Beautifully sprung. High insulation. Splendid new design. So don't pay more than 1/9. List Free.

If your dealer does not stock apply to:

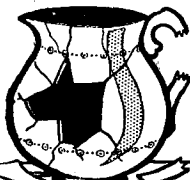JAMES CHRISTIE & SONS, LTD.,
248, West Street, SHEFFIELD.
London Agents: A. F. Bulgin & Co.,
10, Cursitor St., London, E.C.4.



A Better Adhesive for Home Repairs

The new super-adhesive for all repairs of broken china, glassware, etc. Durofix makes a repair of great strength and durability. China and glassware repaired with it can be put into hot water and hot ovens with perfect safety. Try it. In 6d. and 1/- tubs from Ironmongers, etc.

RAWLPLUG

DUROFIX

LIQUID PORCELAIN

Unique preparation for tops, door knobs, etc. Gives glossy white finish, like real porcelain. In tins 1/6 and 2/6 each.

DUROLUSTRE

The super-lacquer that prevents tarnish to all polished metal goods. Sold in tins 1/6 and 2/6 each.

THE RAWLPLUG CO., LTD.
RAWLPLUG HOUSE, CROMWELL RD., LONDON, S.W. 7.

REPAIRS

By specialists skilled in every form of accurate and intricate coil winding.

Headphones, Loud Speakers, and Transformers re-wound, remagnetised and reconditioned

EQUAL TO NEW.

Owing to the rapid growth of business in our REPAIRS Department, we regret that we find it temporarily impossible to maintain our 24 hours' service. Pending extension and reorganisation, a delay of a few days may be unavoidable.

VARLEY Magnet Co.

Renewal Dept.
Woolwich,
S.E.13



Valves Repaired AS GOOD AS NEW!!



(Except Weco S.E.'s and low capacity types.) Minimum D.E. Current C-15 amps when repaired.
At Bright and Dull Emitters. Listed at less than 10%.
Minimum charge 5/-
VALCO LTD. Dept. M.W. Tabor
Grove Wimbledon, SW

OVER 70 STATIONS on the "SOLODYNE"

SIR,—May I offer my most respectful congratulations to the Radio Press on your latest and most astounding Star Set. I have only one objection to raise: modesty, in moderation, is an admirable quality; but do not overdo it.

I only completed my "Solodyne" four days ago, and my bag already is not 50 but well over 70 stations! I must frankly confess that I am astounded at the results; and I should also like to add that I have never handled a set so delightfully easy to manipulate. It took me only two minutes to adjust the neutralising and the gang condensers, and in the next 50 minutes I had identified and logged 35 stations. I have since asked one or two friends of mine, who have never handled a set before, to sit down and tune in; they have done so with very nearly the same ease as I myself have experienced. My own frank opinion is that this set will to a very large extent knock the Super-Het. clean out of the market.

In conclusion I can only tender my very real gratitude to all who have contributed to put this set "into circulation," and to wish for it the success it so richly deserves.—Yours truly,

M. G. FERGUSON.

Holm Leigh, Buxton.

"WIRELESS," The One-Word Weekly.

A New Radio Press Star Receiver




"WIRELESS," the one-word weekly, is now running a series of articles describing the latest Radio Press Star Receiver—the "Monodial": four valves and only one dial.



Why not place a standing order with your newsagent?
2d. Every Tuesday 2d.

BEHIND YOUR PANEL

your coil's are hidden but—

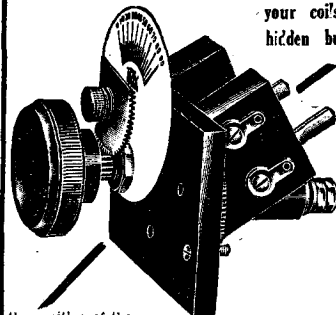

the position of the moving coil is no secret when you use this coil holder. The pointer is geared to move at exactly the same speed as the coil. One hole fixes, No. 272, 5/6
Eric J. LEVER
33, Clerkenwell Green, E.C.1
Phone Clerk. 3014-5


SEND FOR CATALOGUE M 11—JUST OUT



TRIUMPH

CUSHION ANTI-MICROPHONIC VALVE-HOLDER TEST

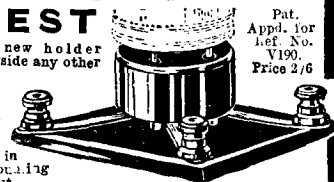this new holder is a guide in any other and you will agree with experts in pronouncing it best.



Pat. Appl. for Ref. No. V190. Price 2/6

NO METAL SPRINGS VIBRATIONS QUICKLY DAMPED

Ask your dealer for free list of

TRIUMPH GUARANTEED COMPONENTS & SETS
or send p.c., mentioning Modern Wireless, to:
A. H. GLACKSON, LTD.,
WHITE HART WORKS, LONDON, N. 22.

PICKETT'S CABINETS



Will improve your Set. Making to **YOUR OWN** sizes and for every Radio Press Set. Sending **ON APPROVAL** Trade Marked and Guaranteed. Send your **own** sizes for Estimates and **LISTS** per return.
Pickett's Cabinet (M.W.) Works, Bexleyheath.



ACCUMULATORS ON EASY PAYMENTS

High Tension Accumulators built up from 20 Volt sections (15/- each). Example: 60 Volt H.T. 45/- CASH, or 12/6 DOWN and 6 monthly payments of 6/-, Carriage Paid. Satisfaction or money back. Write for Lists to **DEPT. 12, Coventry Direct Supplies, Ltd.,** 23, Warwick Row, Coventry. Any Wireless Goods supplied on easy payments.



Tell the Advertiser you saw it in "MODERN WIRELESS."

	PAGE
Agar, W. H.	622, 624
American Hard Rubber Co. (Britain) Ltd.	599
Ashley Wireless Telephone Co.	605
The Arterraft Co.	610
Beard and Fitch	588
Bedford Electrical Co.	614
Belling and Lee	618
Benjamin Electric, Ltd.	571, 611
Bennett College	599
Bird (Sydney S.)	551
Bowyer-Lowe Co., Ltd.	544
Brandes, Ltd.	601, 603, 609
British Battery Co.	610
British Kbonite Co., Ltd.	618
Brown Brothers, Ltd.	607
Brown (S. G.), Ltd.	560
A. F. Bulgin and Co.	622
W. Bullen... ..	618
Burne-Jones and Co., Ltd.	587
Bush House	610
Cahill and Co., Ltd.	621
Carrington Mfg. Co., Ltd.	617
Caxton Wood Turnery Co.	607
James Christie and Sons, Ltd.	623
Clackson (A. H.), Ltd.	622, 623
Cleartron Radio, Ltd.	530
Collinson Precision Screw Co., Ltd.	619
Cossor (A. C.), Ltd.	543, 596
Curtis (Peter), Ltd.	564
"Daily Chronicle"	599
Dubilier Condenser Co. (1925), Ltd.	577, 613
Eastick (J. J.) and Sons	600
Economic Electric, Ltd.	613
Edison Bell, Ltd.	587


Index to Advertisers

	PAGE
Electron Co., Ltd.	583
Falk Stadelmann and Co., Ltd.	581
Ferranti, Ltd.	620
Finchett (C. A.)	617
Finston Mfg. Co., Ltd.	619, 620
Formo Co.	602, 617
Garnett, Whiteley and Co., Ltd.	591, 606, 616
Gent and Co., Ltd.	605
Goodwins (M. A.), Ltd.	622
Hamley Bros., Ltd.	620
Hart Accumulator Co., Ltd.	563
Hunt (A. H.), Ltd.	600, 616
Igranic Electric Co., Ltd.	552
Jackson Bros.	591
Jewel Pen Co.	622
Lever (E. J.)	623
Lissen, Ltd.	547, 564, 583
W. and T. Lock	620
London Electric Wire Co.	529
Lustronix	619
Makerimpot Co.	622
M.A.P. Co.	622
McMichael (L.), Ltd.	568
Morris (J. R.)	615
Mullard Wireless Service Co., Ltd. Cov. ii,	611
New Times Sales Co.	622
Norman Radio, Ltd.	624
Oldham Accumulators	579
Ormond Eng. Co., Ltd.	559
Peto-Scott Co., Ltd.	555, 600
Pettigrew and Merriman (1925), Ltd.	610

	PAGE
Philips Lamps, Ltd.	608
Peckett Bros.	623
Portable Utilities Co., Ltd.	567, 589
Power Equipment Co., Ltd.	602
Radix, Ltd.	581
Radio Instruments, Ltd.	Cover iv
Radio Mariftime	622
Rawpling Co.	623
Raymond (K.)	593
Redferns Rubber Works, Ltd.	581
Rothermel Radio Corporation of Great Britain, Ltd.	548
The Service Co., Ltd.	621
Silvertown Co. (The)	620
Simpson and Blythe	613
S. T., Ltd.	556, 575, 594, 585, 595, 602
Telegraph Condenser Co., Ltd.	593
Telephone Mfg. Co., Ltd.	572
Tudoradio Co., Ltd.	617
Varley Magnet Co.	615, 623
Watmel Wireless Co., Ltd.	617
Westam Accumulators	613
Wilkins and Wright	607, 624
Wireless Distributing Co., Ltd.	622
Wright and Weaire, Ltd.	618
Wolff (M. and A.)	602

"MAKES WIRING A PLEASURE."
**AGAR'S RESIN CORED
 RADIO SOLDER**
 Non-Corrosive. No Flux required.
 Is perfect from all Radio Dealers. Post Free.
W. H. AGAR, 19, WATERLOO PLACE, E.C.2.

CASTLE RADIO CABINETS

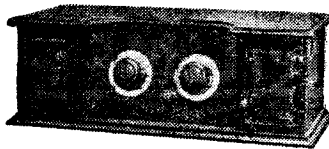

Send for our illustrated List No. 35M. post free.
E. FARNELL & SONS, Birkenhead, L. Bradford.

THE WIRELESS DOCTOR

will call (London and Home Counties) and put you right, if your sets are troublesome. No cure, no charge. Sets installed, maintained and brought up to date. Exclusive Solodyne demonstration.
ALEXANDER LACK, 2a, Woodville Grove, N.16. Call 3687.



CABINETS FOR WIRELESS OR
 GRAMOPHONES AND PARTS.
 Gramophones, Motors, Tricases, Music
 Soundboxes, Horns, Springs, Needles,
 Hinges, Knobs, Lid-stays, Handles,
 cheaper than anywhere else. 64 pages
 illustrations. Catalogue free telling
 how to assemble gramophone sent for
 2d. 25 types of motors from 1/2 cent
 paid. 25 models of gramophones from
 2/6. 4,000 ohm Headphones 3/6. Ac-
 cordions 1/6. Violins 1/6.
 Trade Discount to Regular Dealers.
REGENT FITTINGS Co., "B.W."
 120, Old Street, London, E.C.

BUY BY POST. We pay Postage to anywhere in the B.I.
 Ma. we supply your WIRELESS WANTS BY POST?
 We supply everything Wireless from Terminal to
 Complete Set, at prices as advertised in this
 paper. We can oblige you. Cash with Order.
WRIGHTSON, 1a, Mariners Lane, Tyne mouth
 NORTHUMBERLAND.

ACCUMULATORS.

For super valve sets you require
 super H.C.S. Fit the "Ideal."
 The Perfect Loud speaker Battery.
 Most Moderate Prices. 60, 80, 120
 volt. sets at 34/- 44/- and 63/-.
 Double capacity size. 60 volts.,
 41/6 Carriage Paid. Guaranteed
 one year. Lead set free.
**PEARSON BROS. BEDWORTH,
 NUHEATON**

Make SCREENED COILS at Home

COPPER FOIL 4 in. by 6 in. 3-ounce, D.S.C.
 Wide gauge 2.9 Feet double silk covered, pos-
 itive 6d ample to make the three screened coils Mr.
 Rymer's specification. Details how to make the 5
 foot coils for low cost. Full particulars from
C. WALKER, 110, Thornhill, Ed. Handsworth, Birmingham.

AMATEUR CONSTRUCTORS

PARIS FOR THE
"DRAWING ROOM FIVE"
 described in this issue.

	2 s. d.
1 Radion Black Panel, 16 x 8 x 3/16 ...	10 8
2 Oak American-type Cabinet and Baseboard (Camco)...	1 12 0
5 Valve Holders (Benjamin)	13 9
5 Baseboard-mounting Rheostats (Lissen)	12 6
3 100,000 ohms Anode Resistances with Bases (Varley) ...	1 2 6
2 .0005 S.L.F. Condensers (J.B.)	1 3 0
1 .00025 do. do.	10 0
1 Neutralising Condenser (Bulgian)	3 6
2 Single Coil Holder (Bulgian)	9 9
3 .02 Fixed Condensers (E.C.C.)	7 0
1 2 Mfd. Mansbridge Condensers (T.C.C.)	4 8
1 Standard Audio Choke ("Success")	10 6
1 Filament On-off Switch (Igranic)	2 6
3 1/2 Meg. Grid-leaks (Igranic)	6 6
1 Duvoican (Dubilier)	7 6
5 Sockets (Eastick)	4 8
4 Coils Glazite Wire	6 0
1 Aerial C II 250/550 metres	10 0
2 Split Primary Transformer 250/550 metres	10 0
2 Coil Screens and bases	1 10 0
	£10 18 2

Complete Set of Parts, as specified, including Oak Cab-
 inet, for the **PUSH-PULL THREE** **27 14 7**

We also supply Parts for the following :-

**ELSEEE SIX,
 ELSEEE SOLODYNE,
 2-VALVE SUPER-SET,**

and all other sets described in this paper.

Carriage and Packing Free on inland Orders value £2 and over.

LARGE 145-PAGE ILLUSTRATED CATALOGUE OF
 COMPONENTS, ETC., PRICE 3d.

NORMAN RADIO LTD.

2, NORFOLK STREET, STRAND, LONDON, W.C.2.

Telephone: Central 3206.

"Utility"

GANG CONDENSERS

To all "Solodyne" Builders.

The subject of this advertisement is still another proof of the excellence of "Utility" design and craftsmanship. Much intense experiment is behind its design—experiment which has resulted in the elimination of the undesirable features often met with in this type of condenser.

NOTE THESE POINTS

Individual units are matched before assembly, and then connected by variable coupling—a most efficient and convenient form for this type on the market. It is only necessary to rotate the knob shown in the illustration, and the vernier adjuster to balance out any extra capacities introduced. No other tools, etc., are required.

Fitted with ball bearings throughout. Equipped with "Utility" Micro Dial with ratio of 70:1—ensuring easy and delicate tuning.

Inclusive Price **£2 : 15 : 0**

Send at once for complete details of this instrument and other "Utility" guaranteed components.

WILKINS & WRIGHT, LTD.,
 KENYON STREET,
 BIRMINGHAM.