

PRACTICAL

# ELECTRONICS

DECEMBER 1970

3/6 [17½ NEW PENCE]

and now...  
the **DIGITAL CLOCK**



ALSO INSIDE:

**A War Game — OPERATION "SEASEARCH"**

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

**\*Additional Stock Bits**  
(illustrated) available

### COPPER

- B 38**  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
- B 14**  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE
- B 24**  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE
- B 12**  $\frac{1}{4}$ " — 4.75 mm EYELET BIT
- B 58**  $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

### LONG LIFE

- B 42 LL**  $\frac{1}{4}$ " — 4.75 mm CHISEL FACE
- B 38 LL**  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE
- B 14 LL**  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE
- B 44 LL**  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



\* Write for price list and catalogue

**ADCOLA PRODUCTS LTD.,**  
(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 - Telegrams: Soljoint London Telex - Telex: Adcola London 21851

## EX RENTAL TV's

17"  
SLIMLINE  
405 ONLY  
£11.19.0

2 YEARS' GUARANTEE  
FREE ILLUSTRATED  
LIST OF TELEVISIONS  
17"—19"—21"—23"

19"  
SLIMLINE  
405/625  
BBC 2  
£29.19.0



WIDE RANGE OF MODELS  
DEMONSTRATIONS DAILY



CARR. INS.  
30/-

STEREO RECORD  
PLAYER CABINET &  
MATCHING EXTERNAL  
SPEAKER CABINET £5.19.6



TV TUBES REBUILT  
GUARANTEED 2 YEARS



Cloth covered. Two tone Blue Black.  
Size 14 $\frac{1}{2}$ " 24" 8 $\frac{1}{2}$ " P. & P. 10/6.

Exchanged Bowls. Carr. 10/6.

SPEAKERS GALORE. BRAND NEW 10/- P. & P. 1/- 2 $\frac{1}{2}$ " 8 $\frac{1}{2}$ " 4" 10", 3" 5" 8", 7" 4" and 8" 3" 3".

TRANSISTOR CASES, 5/- each. Cloth covered & plastic. P. & P. 3/-.  
PRESS BUTTON SWITCHING UNITS. 4 Banks 3/6. 6 Banks 5/6. P. & P. 1/-.


TRANSISTORS 2/6 EACH. OC44, OC45, OC71, OC81, OC81D, AF114, AF117, AC128.

**DUKE & CO. (LONDON) LTD.**  
621/3 Romford Road, Manor Park, E.12  
Phone 01-478 6001-2-3 Stamp for Free List
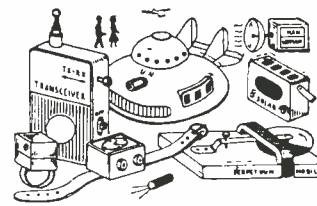
## PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS ON A PRINTED CIRCUIT CHASSIS WITH PARTS AND TRANSISTORS FROM YOUR SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ ". (2) 1 Board for Match-box Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



EXPERIMENTER'S  
PRINTED CIRCUIT KIT

8/6

Postage & Pack. 1/6 (UK)

Commonwealth:  
SURFACE MAIL 2/-  
AIR MAIL 8/-  
Australia, New Zealand  
South Africa, Canada.

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loud-speaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised-Doubling Reflex. (7) Matchbox or Photocell Radio. (8) "TRIFLEXION" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexion" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-82" x .95" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence Required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

**YORK ELECTRICS, Mail Order Dept.**  
335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.



# knight-kits


# FANTASTIC LOW PRICES!

Due to huge purchase these superb U.S.A. construction kits can be offered at 25%—50% off recommended list prices. Absolutely complete with most detailed construction and operating books. Available from all branches or by mail order for 7/6 CARRIAGE AND PACKING on each kit. Two kits or more carr. free.

## KG-865 50 Watt Stereo Amplifier Kit
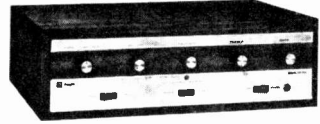
### DELUXE FEATURES


All Silicon Transistors for Stability, Cleaner Sound • Extremely Wide Power Bandwidth and Frequency Response • 50W IHF Power Output • Specially Selected Low-Noise Preamp Transistors • Two Printed Circuit Boards for Fast Easy Assembly • Convenient Front-Panel Stereo Headphone Jack • Teak-finished Extruded Aluminium Front Panel • Two a.c. Convenience Outlets.



Output: 50W IHF, 25W per channel; 34W continuous sine wave • Response:  $\pm 1dB$ , 18 to 30,000Hz • Output Impedance: 4 through 16 ohms, plus stereo headphones • THD Distortion: under 1% at 60Hz and 7,000Hz mixed 4:1 at rated power • Input Sensitivity: Magnetic Phono, 5mV; Tuner and Auxiliary, 500mV • Power Requirement: 230-250V, 50Hz a.c. Recommended List Price £34.19.6; 84 GNS. Assembled 89 GNS. Teak Case 85 Extra

## ALL SILICON TRANSISTORS
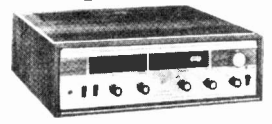
### The NEW KG-980 Stereo FM Receiver Kit




Designed to Satisfy the Most Critical Listener

R.F. and I.F. Panels Assembled and Aligned • Front Panel Stereo Headphone Jack and Speaker Muting Switch • Full Controls including Tape Monitor • 50W IHF Output • Usable I.H.F. Sensitivity:  $3\mu V$  • Frequency Response:  $\pm 1dB$ , 30 to 15,000Hz • Harmonic Distortion: less than 1.0% • A.M. Suppression: more than 30dB • Channel Separation: 30dB • Complementary Transformerless • Power Output: 30W I.H.F. (25W per channel); 34W continuous sine wave • Frequency Response:  $\pm 1dB$ , 18 to 30,000Hz • Power Bandwidth: 20-20,000Hz at 1% Harmonic Distortion • Two R.F. Stages • Stereo indicator light. Recommended List Price £62.19.6; 39 GNS. Assembled 49 GNS. Teak Case 5 GNS. Extra

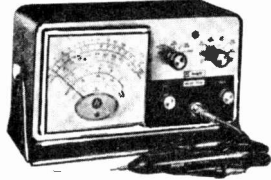
## KG-625 Deluxe 6in Vacuum Tube Voltmeter Kit

Huge 6in Meter Scale • Ranges: d.c. 0-0.5-1.5-5-15-50-150-500-1,500V full scale. • Accuracy:  $\pm 3\%$  of full scale reading • Input Resistance: 11M  $\Omega$  to 1,500V • Ranges: a.c. 0-1.5-5-15-50-150-500-1,500V full scale, 0-4-2-11-42-140-420-1,400-4,200V full scale • Accuracy:  $\pm 5\%$  • Frequency Response:  $\pm 1dB$ , 30Hz to 3MHz;  $\pm 3dB$ , 30Hz to 3MHz • Ohmmeter Ranges: 0-1,000-10,000 ohms; 0-1-10-100-1,000M  $\Omega$  • Battery: 1.5V U2. Recommended List Price £24.19.6; 12 GNS. Kit 620 as Kit 625 (Same Ranges) but 4in Scale: 9; GNS.


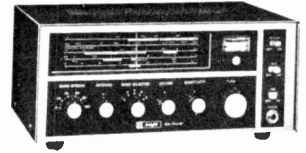
## STAR ROAMER 5-Band Shortwave Receiver Kit

Bandspread: electrical, calibrated 0-100 • Sensitivity: 10  $\mu V$  for 10dB signal-to-noise ratio • I.F. Bandwidth: 5kHz at 6dB down • Beat Frequency: variable, 0-5kHz • Speaker: 4in permanent magnet type • Power Supply: fused, transformer operated • Headphone Output: low impedance • Valve Complements: 1-6BE6, 1-6HR6, 1-12AX7, 1-6AR5 or 1-6AR5 • Power Requirements: 230-250V, 50Hz a.c.; 15W • Covers 200 to 400kHz and 550kHz to 30MHz in 5 Band-switched Ranges • Superheterodyne Circuit includes controlled regenerative I.F. stage • A.V.C. reduces fading and blasting; A.N.L. cuts noise to a minimum • Aerial Trimmer effectively peaks incoming signals for best reception • Illuminated "S" Meter; Large, Easy-to-Read 7in Slide Rule Dial. Recommended List Price £21.19.0; 14 GNS. Assembled Price 19 GNS.




## KG-375A Deluxe Solid-State Auto Analyzer Kit

Tune-up and trouble-shoot any car, perform actual road tests

It's several testers in one... do all this

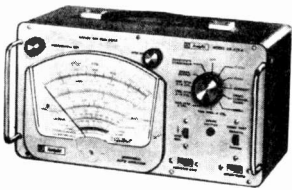Set Engine Idle and Automatic Transmission Shift Points • Detect Condition of Point Surfaces • Detect Distributor Wear • Check Voltage and Current Regulators • Check Generators for both Current and Voltage Output • Find Poor or Open Earth Circuits • Detect Variation in Dwell Angle. Recommended List Price £23.17.9; 16 GNS. Assembled Price 21 GNS.



## 100-in-1 Electronic Science Lab

### LOOK AT THE PROJECTS YOU CAN BUILD


Electronic Scale • Electronic Timer • Signal Generator • Hybrid Light Meter • Signal Injector • Morse Code Buzzer • Electronic Cat • Metronome • Code Flasher • CW Monitor • Ohmmeter • Boat Horn • Hybrid Radio • Hybrid Voice Relay • Air-powered Radio • Polarity Checker • Valve Checker. Includes: • Dual Headset • Photocell • Speaker • Meter • Aerial • Transistors. Recommended List Price £16.8.0; 9; GNS.


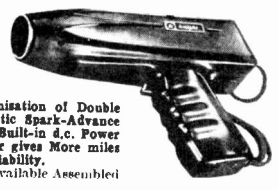
## KG-371 Deluxe Solid-State Timing Light


Performance surpasses assembled units costing much more

Helps Set Ignition Timing • Checks Synchronization of Double Breaker Arms • Checks for Sticking Automatic Spark-Advance Mechanism • Checks Distributor Cam Wear • Built-in d.c. Power Supply • Reliable Solid-State Circuit • Your car gives More miles per gallon; Improved performance; Greater reliability. Recommended List Price £12.10.0; 9 GNS. Available Assembled Only.


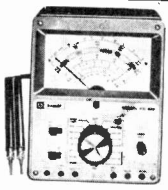
## KG-640 20,000 ohms/Volt VOM Kit

BIG PROFESSIONAL SIZE 6 RANGE MULTIMETER • A.C. Volts (12 Ranges): 0-2-4-5-10-40-80-200-400-800-1,600-2,000-4,000V • D.C. Volts (12 Ranges): 0-0.5-1-5-5-16-40-80-200-400-800-1,600-2,000-4,000V • Output Volts (8 Ranges): 0-2-4-5-10-40-80-200-400V • Resistance (8 Ranges): 0-1,000-100,000 ohms-10 meg. Centre scales at 1, 1,200 and 120K  $\Omega$  • D.C. Current (10 Ranges): 0-50-100-500-500  $\mu A$ , 5-10-20-400mA, 5-16.4 Decibels (12 Ranges): -12 to +74 • D.C. Sensitivity: 20,000 ohms per volt or 10,000 ohms per volt (function of scale multiplier switch) • Frequency Response: 20Hz to beyond 200kHz • Accuracy: d.c. 3%, a.c. 5% • Test Leads: one red, one black, each 18in long • Multiplier Resistors: All 1% carbon film. Recommended List Price £16.19.6; 9; GNS. Assembled Price 12 GNS.



## JASON TAPE

We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

	Standard	Long	Double	Triple
3in. 150ft.	2/3	3in. 225ft.	2/9	3in. 300ft.
4in. 300ft.	4/6	4in. 450ft.	5/6	4in. 600ft.
5in. 600ft.	7/6	5in. 900ft.	10/6	5in. 1,200ft.
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-	5 1/2in. 2,400ft.
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6	7in. 3,000ft.
				7in. 3,600ft.
				8in. 4,800ft.
				8in. 6,000ft.

Postage 1/- reel. Post free less 5% on three reels. Quality and Trade enquiries invited. NOTE. Large tape stocks at all branches.

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear, Rodgers, Truvox, Ferrograph, Wharfedale, etc., etc.

# TECHNICAL TRADING

- All Mail Orders:—
- ★ ARUNDEL 15-17 Queen Street Tel. 3280
  - ★ BRIGHTON 6 Queen's Road Tel. 23975
  - ★ LONDON 10 Tottenham Court Road Tel. MUSEum 2639
  - ★ PORTSMOUTH 350-352 Fratton Road. Tel 22034
  - ★ SOUTHAMPTON 72 East Street Tel. 25851

PERSONAL CALLERS Welcomed at all Branches where there are large Hi-Fi and Component stocks at the keenest prices including:

GARRARD 1025 Autochangers complete with GARRARD STEREO CARTRIDGE 7 1/2 GNS.

MAGNETIC CARTRIDGES Goldring 800H 7 1/2 GNS.

Shriro AT33 £7.10.0 (Both Listed over £10)

# Laskys

## TMK METER KITS

These two meter kits by TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional, circuit and operating instructions.

**MODEL 200** 20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3" x 2" meter. Full scale accuracy: DCV and current:  $\pm 2\%$ , ACV:  $\pm 3\%$ , resistance  $\pm 3\%$ . Special 0.6V DC range for transistor circuit measurements.

### SPECIFICATION

● DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV. ● ACV: 0-6-30-120-600-1,200V at 10K/OPV. ● DC Current: 0-0.6-6-600mA. ● Resistance: 0-10K 100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale). ● Capacitance: 0-002-0.2 $\mu$ F (AC 6V range). ● Decibels -20 to +63dB. ● Output: 0-05 $\mu$ F blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet—Size 5 $\frac{1}{2}$  x 3 $\frac{1}{4}$  x 1 $\frac{1}{2}$ in. Complete with test leads.



**KIT PRICE ONLY 92/-** Post 3/6

**MODEL 5025** 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES

Uses an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is indicated on the meter face. High speed rotary range selection knob; polarity reversal switch, shielded meter movement with overload protection circuit; Special  $\mu$ A and mA measurement ranges.

**SPECIFICATION** DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-0-25-125-500V at 50K/OPV. ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-5-25-125-500V at 5K/OPV. DC  $\mu$ A: 0-25 $\mu$ A at 125mA. 0-50 $\mu$ A at 250mA. DCmA: 0-2.5-25-250mA at 125mV. 0-5-50-500mA at 250mV. DC Amps: 0-5A at 125mV; 0-10A at 250mV. Resistance: 0-10M/ohms. Output: Capacitor (0.1 $\mu$ F, 400V) in series with ACV ranges. Decibels: -20 to +81.5dB. Operates on two 1.5V batts. Black bakelite cabinet, size 5 $\frac{1}{2}$  x 6 $\frac{1}{2}$  x 2 $\frac{1}{2}$ in. Complete with test leads.




**KIT £10.10.0** Post 5/

**MODEL 5025 ALSO AVAILABLE READY BUILT AND TESTED £12.10.0** POST 5-

## TMK 100,000 OPV
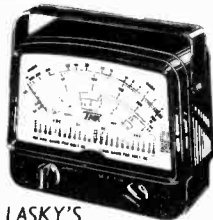
### "LAB MODEL"

A highly accurate yet rugged Multitester using a 10 $\mu$ A meter hand calibrated to a D.C. accuracy of  $\pm 3\%$  of full scale. Special features—ultra large meter scale 6 $\frac{1}{2}$  x 3 $\frac{1}{2}$ in incorporating an entirely new type of range selection panel which gives instant range identification without taking your eyes from the meter. An audible buzzer is provided for easy short testing. SPEC: D.C./V ranges: 0.5, 2.5, 10, 50, 250, 500, 1,000V at 100K/O.P.V. A.C./V ranges: 3, 10, 50, 250, 500, 1,000V at 5K/O.P.V. D.C. current: 0-10, 100 $\mu$ A, 0-10, 100mA, 0-2.5, 10A. Resistance: 0-1K, 10K, 100K, 10M, 100M/ohms. Decibels: -10 to +49.4dB. Continuity test: Audible buzzer. Operates on x 11.5V U2 and x 1.5V B. 154 type batteries. Cabinet size 7 $\frac{1}{4}$  x 6 $\frac{1}{2}$  x 3 $\frac{1}{2}$ in. Weight 4lb.



LASKY'S PRICE **£19.0.0** POST 5-

## SONICS AS-57

### ELEGANT BUDGET PRICED BOOKSHELF SPEAKER SYSTEMS

The AS-57 is a real space saver. This fine miniature high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated listening area. The special high efficiency 5 x 7in full range speaker has a frequency range of 70-18,000Hz with a peak handling capacity of 10 watts. Imp. 8 ohms. Finish: oiled walnut. Size 5 $\frac{1}{4}$  x 15 $\frac{1}{2}$  x 8 $\frac{1}{2}$ in.

LASKY'S PRICE **£15** per PAIR POST 10-


## EXCLUSIVE

### TM-5
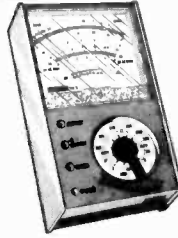
#### 5 K ohms/V POCKET MULTIMETER

Another new look pocket multi-meter from Lasky's providing top quality and value. The "slimline" impact resistant case—size: 4 $\frac{1}{2}$ in x 2 $\frac{1}{2}$ in x 1 $\frac{1}{2}$ in, fitted with extra large 2 $\frac{1}{2}$ in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DC/V: 3-15-150-300-1,200 at 5K/OPV.
- AC/V: 6-30-300-600 at 2.5K/OPV.
- DC Current 0-300 $\mu$ A, 0-300mA.
- Resistance: 0-10k $\Omega$ , 0-1M $\Omega$ .
- Decibels: -10dB to +16dB.
- Complete with test leads, battery and instructions.




LASKY'S PRICE **49/6** POST 2/6

## TM-1 MINI-TESTER

1 K ohms/volt

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to  $\pm 3\%$  of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case—with white and metallic red/green figuring. Ohms zero adjustment.

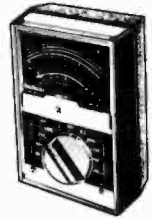- Size Only 3 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in
- DC/V: 0-10-50-250-1,000 at 1K OPV.
  - AC/V: 0-10-50-250-1,000 at 1K OPV.
  - DC CURRENT: 0-1mA, 100mA.
  - Resistance: 0-150k $\Omega$ .
  - Decibels: -10dB to +22dB.
  - Complete with test leads, battery and instructions.



LASKY'S PRICE **39/6** POST 2/6


## AUDIO DEVELOPMENT

### AD-309K
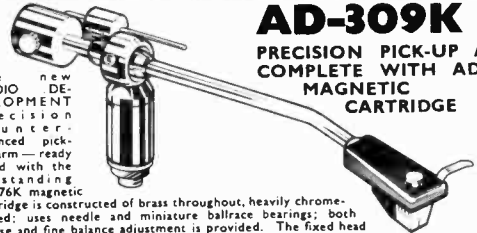
#### PRECISION PICK-UP ARM COMPLETE WITH AD-76K MAGNETIC CARTRIDGE

The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm—ready fitted with the outstanding AD-76K magnetic

cartridge is constructed of brass throughout, heavily chrome-plated; uses needle and mixture ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard  $\frac{1}{2}$ in. mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in. dia. mounting hole.



LASKY'S PRICE **£8.10.0** Post Free

### AUDIO DEVELOPMENT AD-76K

Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. **90/-** Post Free  
Tracking force: 2 gms  $\pm 0.5$  gms.  
Replacement stylus type JS.P1 41/- post free.

### AUDIO DEVELOPMENT AD-96K


Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. **£5.18.6** Post Free  
Tracking force: 2 gms.  
Replacement stylus type Y.960S 51/6, post free.



# Audio Tronics 71 THE AMAZING

Send your name and address now to receive immediately the new 1971 edition of LASKY'S famous Audio-Tronics pictorial catalogue, larger and more comprehensive than ever before, packed with 1000's of items for the Radio and HI-FI enthusiast, electronics hobbyist, serviceman and communications ham. Covers every aspect of HI-FI (including Lasky's budget Stereo Systems and Package Deals) plus Lasky's amazing saving vouchers worth over £32. Send your name, address and 2/6 for post and inclusion on our regular mailing list.

## EXCLUSIVE DIGITAL CLOCK SCOOP!

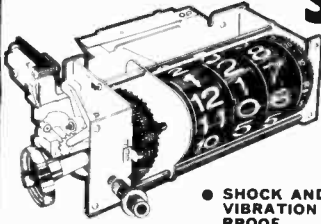

SPECIAL QUOTATIONS FOR QUANTITIES

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM. "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light, etc., at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4 1/4" x 1 3/4" x 3/4" (overall from front of drum to back of switch). SPEC: 210/240V A.C. 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS.

COMPLETE WITH KNOBS.


LASKY'S PRICE **£6.19.6** Post 3/6

KNOBS AVAILABLE SEPARATELY—12/6 per set. Post 1/6

## Garrard SPECIAL OFFER
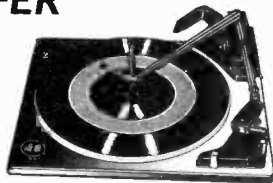
### SL-55

One of the famous Garrard Synchro-Lab Series. Takes 8 Lps. 4-speed auto-changer; incorporating a tubular pickup arm and adjustable stylus force.



Wired for Mono and Stereo. Size 14 in wide, 1 1/4 in front to rear. 4 1/2 in above and 3 in below lower edge of unit plate. NOW AT LASKY'S SUPER SPECIAL OFFER PRICE. Complete with SONOTONE 9TA STEREO CARTRIDGE OTHER GARRARD UNITS FROM STOCK AUTOCHANGERS

SPECIAL OFFER PRICE **£10.19.6**

**SINGLE PLAYERS**  
 SP-25 MK II £11.19.6, AP 75, £18.10.0, AP75 with AD76K mag. cart., £21.10.0.  
 401 Transcription Unit £20.0.0.  
**BASES AND COVERS FOR GARRARD UNITS**  
 Type WB1 and WB5 for models 2025TC, 3000, SL65B 1025, SP25 Mk II Price WB1 £3.16.6. WB5 £5.12.6. Type WB4 for models SL72B, SL75B, SL95B Price £5.12.6. Perspex covers SPC1 for WB1, £3.14.1. SPC4 for WB4 and WB5 (allows unit to be played with the cover in place)—£4.8.0.

## Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271  
 33 TOTTENHAM CT. RD, LONDON, WIP 9RB. Tel: 01-636 2605  
 Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
 109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812  
 152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833  
 Open all day Thursday, early closing 1 p.m. Saturday


**HIGH FIDELITY AUDIO CENTRES**  
 42-45 TOTTENHAM CT. RD, LONDON, WIP 9RD. Tel: 01-580 2573  
 Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
 118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789  
 Open all day Saturday early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

## Astrad ORION

THE WORLD'S SMALLEST 6 TRANSISTOR

TWO WAVEBAND RADIO  
 THOUSANDS SOLD

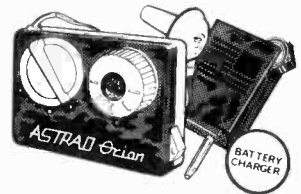

Made to the highest space-age standards—this remarkable micro-size set measures only 1 1/4" x 1 1/4" x 1 1/4" yet it contains 6 transistors and other components combined in a photo etched circuit, only 2 x 1/4" tuning capacitor, ferrite rod aerial, battery, wave band selection switch, etc. Output to a high impedance crystal earpiece, giving ample volume (automatically adjusted) and clear tone. Brief tech. spec.: Waveband coverage—Medium wave 525 to 160kHz, Long wave 150kHz to 480kHz. Sensitivity: 35MV max. Selectivity—10dB (at 30kHz de-tuning). Power source: 1 x 1.4V Mercury battery.

The Orion is supplied fully built and tested complete with battery, left and right fitting earphone supports and attractive black and ivory plastic presentation/carrying case (matching the Orion). Never miss your favourite music, sport, news—the Orion is an ideal gift for all, providing a constant source of enjoyment without disturbing others.


AUTUMN PACKAGE PRICE 57/-

AVAILABLE SEP: RADIO 39/6, Post 2/6  
 Spare batt. 3/6. Charger\* 19/6, Post 2/6  
 (\*enables Orion to be used non stop).

ONLY **39/6** COMPLETE
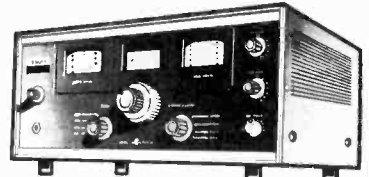
## TRIO 9R-59DE

● 8 valve plus 7 diode circuit continuous coverage from 550kHz to 30MHz with Calibrated Bandspread on 10, 15, 20, 40 and 80 metre bands ● Clear SSB reception is achieved through the use of a product detector. ● Finished in light grey with dark grey case. Fully guaranteed, complete with instruction manual and service data.



**SPECIFICATION:** Frequency Ranges: 550-1,600kHz; 1.6-4.8MHz; 4.8-14.5MHz; 10.5-30MHz. Bandspread: (Direct Reading on Ham Bands) 3-5MHz 80m; 7MHz 40m; 14MHz 20m; 21MHz 15m; 28MHz 10m. Sensitivity: A, B, C Bands—Less than 6dB (for 10dB S/N ratio); D Band—13MHz; Less than 18dB (for 10dB S/N ratio); 23MHz; Less than 10dB (for 10dB S/N ratio). Selectivity: ±5kHz at -50dB. Audio Output: 1.5w. Power Requirements: AC 115/230V, 50/60Hz. Recommended Speaker Type: 4 or 8 ohm. Built-in Circuits: Bandspread; Automatic Noise Limiter (ANL); Automatic Volume Control (AVC); Headphone Jack. Dimensions: 7in H, 15in W, 10in D.

LASKY'S PRICE **£42.0.0** Carriage free

TRIO SP-5D Communications speaker unit

—matching all the TRIO receivers in both style and size. Contains 5 3in elliptical 8 ohms speaker specially designed to give extremely crisp reproduction of voice frequencies. Dark grey metal cabinet—size 7 x 3 1/4 x 3 1/4 in.

LASKY'S PRICE **87/6** Post 5/-

TRIO HS-4 HEADPHONES

Rugged construction plus comfort make these a must for the Ham. Dynamic headset. Input Impedance 8 ohms, matching 4-16 ohms. Max. power 3w. Frequency range 300-3,000Hz.



LASKY'S PRICE **£5.19.6** Post 3/6

## JUST ARRIVED


New Lasky's C60, C90, C120. Exclusively made for us in U.S.A. Great Savings!

	EACH	FIVE FOR	TEN FOR
C 60—7/6	33/-	62/-	
C 90—12/6	56/-	100/-	
C 120—17/6	75/-	139/-	

U.S.A. Cassette head cleaner 10/6. Post 1/-  
 Post 1/- each, five for 2/-, ten for 3/-.



# Build a transistor radio in an evening

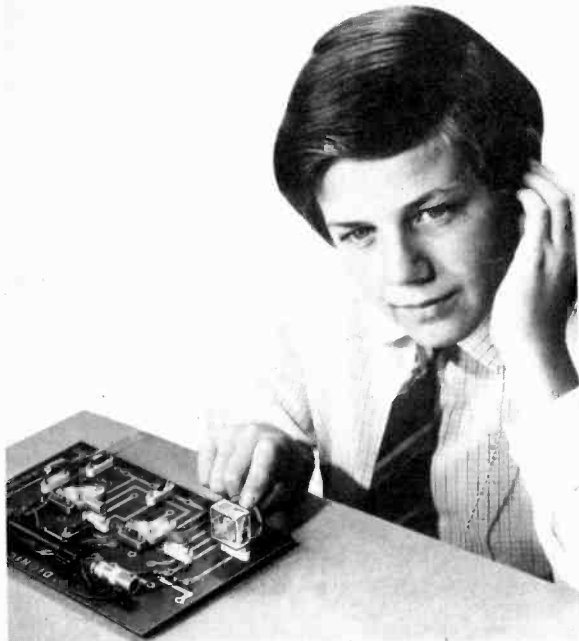

## - learn about radio and electronics at the same time

There's no complicated soldering with the Radionic X30 Kit. The components plug in and your radio will work straight away. Build 33 fascinating experiments: a printed circuit transistor radio, a burglar alarm, a morse code buzzer etc. Radionic kits are safe — they're battery operated. The X30 and more advanced Radionic Kits can help you with your exams too. Send off this coupon today.

TO: RADIONIC PRODUCTS LTD.,  
St. Lawrence House, Broad Street, Bristol BS1 2HF

PE 3

Please send me full details of all Radionic Kits/please send me one Radionic X30 kit at £7 19s. 6d. (Delete where inapplicable)

Name \_\_\_\_\_

Address \_\_\_\_\_



## AMAZING MINI-DRILL

FOR PRECISION MODEL WORK

ABRASIVE  
SPEAR DRILL  
BURR  
MOP  
BRUSH  
+ 6 TOOLS

indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6 p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money Ref. Guarantee.


**MERLIN SUPPLY CO.**

Dept. PE12D, Nailsea, Bristol BS19 2LP


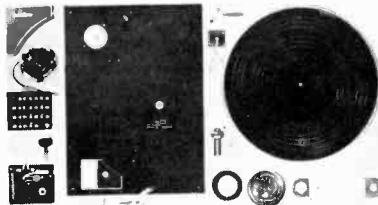
### B.D.1. TURNTABLE KIT

The famous B.D.1. turntable which operates at 33½ or 45 r.p.m. incorporates a flexible belt drive system, virtually eliminating vibration and transmission noise — AND IS NOW AVAILABLE IN KIT FORM! So simple to construct — such a beautiful performance, and now it's so easy to own the best!



Price list and illustrated literature on request to

**A. R. SUGDEN & CO. (Engineers) LTD.**  
Market Street, Brighouse HD6 1DX, Yorkshire. Tel. 2142

### WAH-WAH PEDAL KIT

**SELECTIVE AMPLIFIER MODULE.** The basis of the Wah-Wah pedal. Kit contains all the components to build a 2-transistor circuit module, also the sockets, control, etc., required for the constructor to assemble his own design, 35/-. Assembled and tested module 42/6.

**FOOT VOLUME CONTROL PEDAL.** Foot pedal unit in very strong fawn plastic. Fitted with output lead and plug for connection to guitar amplifier. May be used for volume control or converted to Wah-Wah by adding the module.

Pedal unit now only £5.2.6.  
Complete kit for Wah-Wah pedal now only £6.10.0.  
All post free.


Send 2/6 for our catalogue of components, testmeters, musical electronics and more details of the above items.  
Callers welcome.

**WILSIC ELECTRONICS LIMITED**  
6 COPLEY ROAD, DONCASTER, YORKSHIRE


# Many New Models! in the FREE HEATHKIT 1971 Catalogue . . .



**CONSUMER**

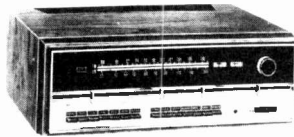

**HI-FI & AUDIO**

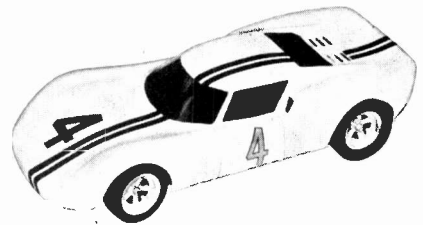

**MODEL R/C CARS**


Here's the bumper Heathkit catalogue for you. Read about the wonder and fascination of kit building . . . see in full colour the world's best values in Hi-Fi Radio, and even model radio control. Get up to date with what's new in scientific instrumentation . . . instruments for test and service . . . in fact there is a Heathkit for almost every purpose, in every walk of life. A wealth of information is all yours for the price of a postage stamp, in the Free Heathkit Catalogue.



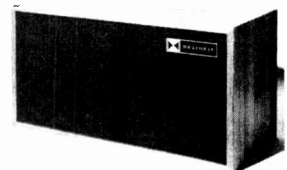**MARINE**

- ★ No previous knowledge of electronics required.
- ★ The constructional manual supplied with every kit shows you how.
- ★ Building Heathkit models is so economic.

- ★ Save up to 50% over factory built equipment.
- ★ Money saving direct from factory prices.
- ★ They make excellent Christmas gifts.



**'TRENT' SPEAKER**



A Schlumberger Company

## HEATH (Gloucester) LTD., GLOUCESTER GL2 6EE

Many other models in wide range

(BLOCK CAPITALS PLEASE)

**FILL IN THE COUPON FOR YOUR  
FREE CATALOGUE TODAY**




Name .....

Address .....

Post Code .....



# Project 60

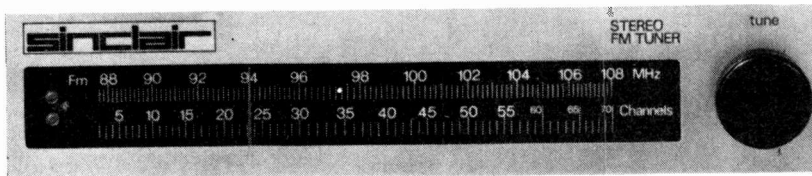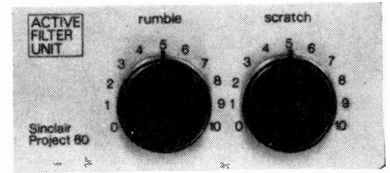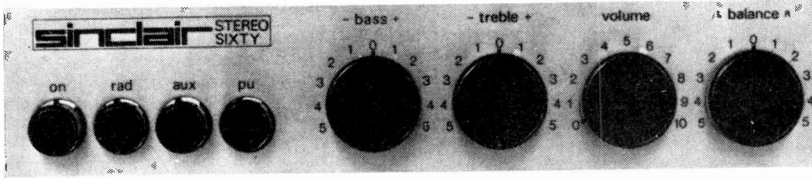

## the world's most advanced high fidelity modules

With the introduction of an entirely new and original high fidelity stereo F.M. tuner, the Project 60 range can be said at this stage to be complete. It offers the constructor a most attractive choice of modular arrangements whereby a high fidelity system can be selected to suit the user's personal requirements. Equally, it is possible to use any Project 60 modules separately or partially grouped and so benefit greatly from the flexibility in use these modules afford. The chart below shows some of the most popular applications for constructors to assemble. The Project 60 manual (free with the modules) suggests others as well and its 48 pages are packed with valuable information. The new tuner, for example can be used with any good high fidelity system as well as Project 60.

Project 60 now falls into four interdependent groups: - 1. The Z.30 and Z.50 amplifiers which have only 0.02% distortion at all output levels and are useful in a wide variety of other applications. 2. The control units comprising the Stereo 60 preamp and control unit and the Active Filter Unit (A.F.U.) with which both high pass and low pass filtering can be introduced between control unit and power amplifiers. 3. The Stereo F.M. tuner as described opposite; and 4. The power supply units PZ.5,

PZ.6 and PZ.8. For most requirements when using Z.30 power amplifiers, the PZ.5 will be perfectly adequate; if low efficiency (high quality) loud speakers are used, the PZ.6 stabilised power supply unit will be used. The PZ.8 will be needed with Z.50s which can be used for any Project 60 system.

Project 60 modules incorporate some of the most advanced circuitry in the world to achieve unsurpassed standards of high fidelity and modern manufacturing techniques enable these modules to be sold at exceptionally attractive prices. Assembling the modules requires no skill or previous experience since the manual supplied with the modules explains clearly how everything can be done with nothing more than the simplest of domestic tools.

### Project 60 manuals

How to assemble and use Project 60 modules to best advantage in the above and other applications will be found in the fully descriptive Project 60 manual included with Project 60 systems. This 48 page manual is available separately, price 2/6d including postage.

System	The Units to use	In conjunction with	Cost of Units	+ Project 60 tuner
A Car Radio	Z.30	Existing car radio, Sinclair Micromatic	89/6	
B Simple battery powered record player	Z.30	Crystal pick-up, 12V or more battery supply and volume control	89/6	
C Mains powered record player	Z.30 and PZ.5	Crystal or ceramic P.U. Volume control etc.	£9.9.0	£34.9.0
D 20+20 watts R.M.S. stereo amplifier for most needs	Two Z.30s, Stereo 60 and PZ.5	Crystal, ceramic or magnetic P.U., most dynamic speakers, F.M. tuner etc.	£23.18.0	£48.18.0
E 20+20 watts R.M.S. stereo amplifier for use with low efficiency (high performance) speakers	Two Z.30s, Stereo 60 and PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc All dynamic speakers	£26.18.0	£51.18.9
F 40+40 watts R.M.S. de-luxe stereo amplifier	Two Z.50s, Stereo 60 PZ.8 and mains transformer	As for E	£32.17.6	£57.17.6
G Outdoor public address system	Z.50	Microphone, up to 4 P.A. speakers, 12V car battery with converter, or 45V d.c., controls	£5.9.6	
H Indoor P.A.	One Z.50, PZ.8 and mains transformer	Microphone, guitar, heavy duty speakers etc., controls	£17.8.6.	
J High pass and low pass filters	A.F.U.	D, E or F as above	£5.19.6	

# sinclair

Sinclair Radionics Limited, 22 Newmarket Road, Cambridge

Telephone (0223) 52731

## Z.30 & Z.50 power amplifiers

The Z.30 together with the Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are the same physical size and may be used with other units in the Project 60 range equally well. For operating from mains, for the Z.30 use PZ.5 for most domestic requirements, or PZ.6 if you have very low efficiency loudspeakers. For Z.50, use the PZ 8 described below.

### SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

#### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms, using 35V; 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms from 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts.

**Frequency response** 30 to 300,000 Hz  $\pm$  1dB


**Distortion** 0.02% into 8 ohms

**Signal to noise ratio** better than 70dB unweighted

**Input sensitivity** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

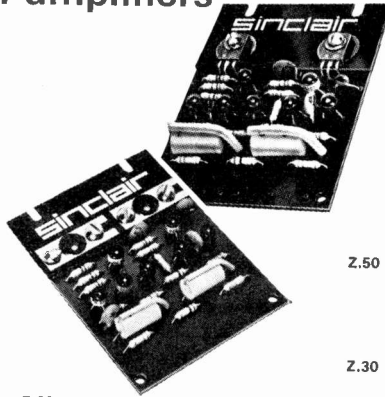Size  $3\frac{1}{2} \times 2\frac{1}{4} \times \frac{1}{2}$  ins.



**Z.30**

Built, tested and guaranteed with circuits and instructions manual

**89/6**

**Z.50**

Built, tested and guaranteed with circuits and instructions manual

**109/6**

## Stereo 60 pre amp/control unit

Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

### SPECIFICATIONS

● Input sensitivities – Radio – up to 3mV, Mag. p.u. – 3mV; correct to R.I.A.A. curve  $\pm$  1dB; 20 to 25,000Hz.


● Ceramic p.u. – up to 3mV; Aux. – up to 3mV.

● Output – 250mV.

● Signal-to-noise ratio – better than 70dB.

● Channel matching – within 1dB.

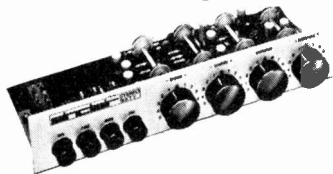● Tone controls – TREBLE +15 to –15dB at 10kHz; BASS +15 to –15dB at 100Hz.



- Front panel – brushed aluminium with black knobs and controls.
- Size  $8\frac{1}{2} \times 1\frac{1}{2} \times 4$  ins.


Built, tested and guaranteed

**£9.19.6**
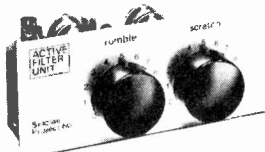
## Active Filter Unit

For use between Stereo 60 unit and two Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The Sinclair A.F.U. is suitable also for use with any other amplifier system.

Two stages of filtering are incorporated – rumble (high pass) and scratch (low pass). Supply voltage – 15 to 35V. Current – 3mA. H.F. cut-off (–3dB)



variable from 28kHz to 5kHz. L.F. cut-off (–3dB) variable from 25Hz to 100Hz. Filter slope, both sections 12dB per octave. Distortion at 1kHz (35V supply) 0.02% at rated output.

Built, tested and guaranteed

**£5.19.6**

## Power Supply Units

The units below are designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 power supply unit to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.


**PZ-5 30 volts un stabilised £4.19.6**

**PZ-6 35 volts stabilised £7.19.6**

**PZ-8 45 volts stabilised**

**(less mains transformers) £5.19.6**


**PZ-8 mains transformer £5.19.6**

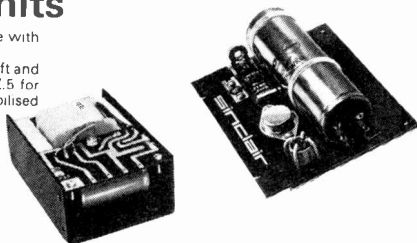

**GUARANTEE** If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

# sinclair

## Stereo FM tuner

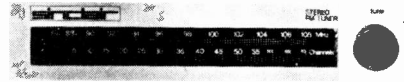

first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time the principle has been applied to an FM tuner with fantastically good results. By the inclusion of other original features such as varicap diode tuning, printed circuit coils and an I.C. in the specially designed stereo decoder, the tuner has an unsurpassed specification, which also incorporates a squelch circuit for silent tuning between stations, A.F.C. and A.G.C. Sensitivity is such that good reception becomes possible in difficult areas, foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of high fidelity, this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. Although the tuner is intended primarily for use with a Project 60 system, it can be used to advantage with any other high fidelity system. It is easily mounted into any cabinet as shown in the manual supplied with it.

### Specifications

Number of transistors 16 plus 20 in I.C.

Tuning range 87.5 to 108 MHz

Capture ratio 1.5dB

Sensitivity  $2\mu\text{V}$  for 30dB quieting  
7 $\mu\text{V}$  for full limiting

Squelch level 20 $\mu\text{V}$

A.F.C. range  $\pm$  200 KHz

Signal to noise ratio > 65dB

Audio frequency response 10Hz–15kHz ( $\pm$  1dB)

Total harmonic distortion 0.15% for 30% modulation

Stereo decoder operating level  $2\mu\text{V}$

Pilot tone suppression 30dB

Cross talk 40dB

I.F. frequency 10.7 MHz


Output voltage 2 x 150mV R.M.S.

Aerial Impedance 75 Ohms

Indicators Mains on ; Stereo on ; tuning indicator

Operating voltage 25-30 VDC

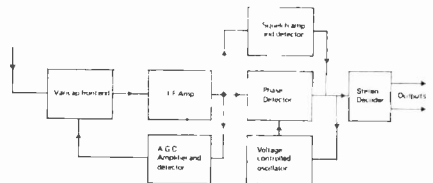Size 3.6 x 1.6 x 8.15 inches; 91.5 x 40 x 207 mm



Price: £25 built and tested. Post free.

To: Sinclair Radionics Ltd., 22 Newmarket Road, Cambridge

Please send



NAME

ADDRESS

for which I enclose cash/cheque money order

PE/12A

# Sinclair IC-10

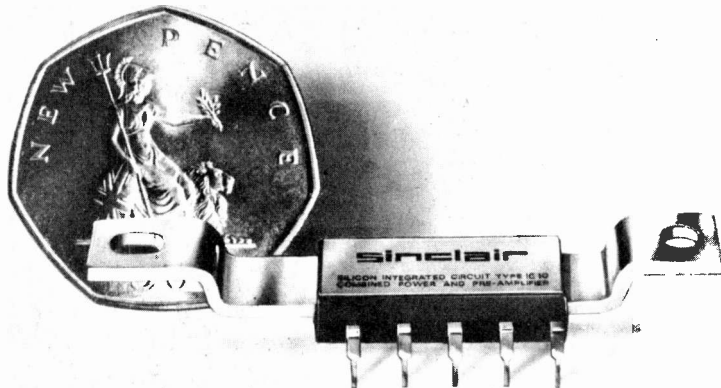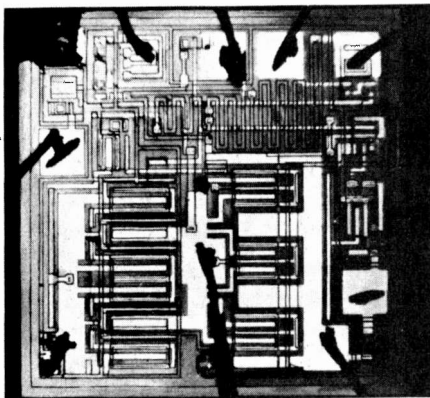

## the world's most advanced high fidelity amplifier

### Specifications

Output: 10 Watts peak, 5 Watts R.M.S. continuous  
 Frequency response: 5 Hz to 100 KHz  $\pm 1$  dB  
 Total harmonic distortion: Less than 1% at full output.  
 Load impedance: 3 to 15 ohms.  
 Power gain: 110dB (100,000,000,000 times) total.  
 Supply voltage: 8 to 18 volts.  
 Size: 1 x 0.4 x 0.2 inches.  
 Sensitivity: 5mV.  
 Input impedance: Adjustable externally up to 2.5 M ohms.

### Circuit Description

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

### Applications

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, has 5 watts R.M.S. output (10w. peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout), etc. Once proven, the circuits can be produced with complete uniformity which enables us to give a full guarantee on every IC-10, knowing that every unit will work as perfectly as the original and do so for a lifetime.

SINCLAIR

**IC-10** with IC-10 manual **59/6**  
 Post free.

To: Sinclair Radionics Ltd., 22 Newmarket Road, Cambridge	
Please send	NAME
.....	ADDRESS
.....	
.....	
for which I enclose cash/cheque money order	PE/12A






## Q.16 High fidelity loudspeaker

Developed out of the revolutionary and much praised design of the original Sinclair Q.14 comes this more advanced version to meet the requirements of even greater numbers of high fidelity enthusiasts. The Q.16 employs the same well proven acoustic principles in which a special driver assembly is meticulously matched to the physical characteristics of the uniquely designed housing. In reviewing this exclusive Sinclair design, technical journals have been loud in their praise for it and it comfortably stands comparison with very much more expensive loudspeakers. The shape of the Q.16 enables it to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures, and with its improved styling, the Q.16 presents an entirely new and attractive appearance. A solid teak surround is used with a special all-over cellular black foam front chosen as much for its appearance as for its ability to pass all audio frequencies unimpaired.

The Q.16 is compact and slim and is the ideal shelf-mounted speaker, and brings genuine high fidelity within reach of every music lover.

### Specifications

Construction:	A sealed seamless sound or pressure chamber is used with internal baffle, all of materials carefully chosen to ensure freedom from spurious tone coloration.
Loading:	Up to 14 watts R.M.S.
Input impedance:	8 ohms.
Frequency response:	From 60 to 16,000Hz, as confirmed by independently plotted B & K curve.
Driver unit:	Specially designed high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension. Excellent transient response is achieved.
Size and styling:	9 $\frac{3}{4}$ " square on face $\times$ 4 $\frac{3}{4}$ " deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.
Price:	£8 19 6.

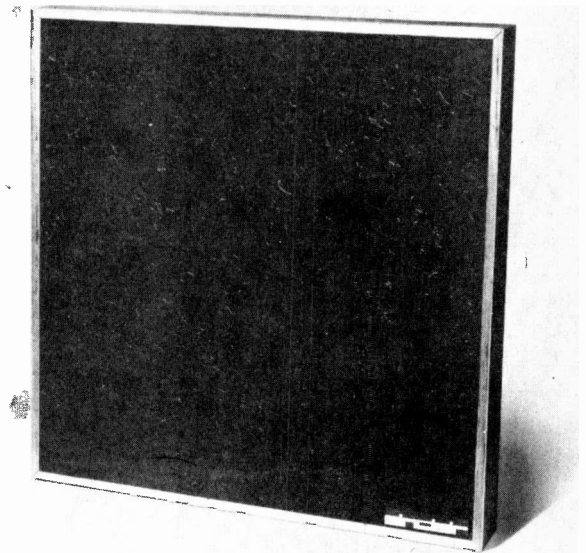

## Micromatic Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation very much easier than with many larger sets. The plug-in high fidelity type magnetic earpiece which matches exactly with the output of the Micromatic provides wonderful standards of reproduction both for speech and for music. Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wristwatch, and dependable under the severest listening conditions.

### Specifications

Size:	1 $\frac{1}{8}$ " $\times$ 1 $\frac{7}{16}$ " $\times$ $\frac{1}{2}$ " (46 $\times$ 33 $\times$ 13mm).
Weight including batteries:	1 oz. (28.35gm) approx.
Tuning:	Medium wave band with bandspread at higher frequency end.
Earpiece:	High-fidelity magnetic type.
Battery requirements:	Two Mallory Mercury Cells, type R.M. 675, for long working life.
Case:	Black plastic with anodised aluminium front panel, spun aluminium dial.
Controls:	Tuning dial, and on/off switching by means of earpiece plug.
Price:	Available in kit form complete with earpiece, case, instructions and supply of solder in fitted pack. 49/6. Ready built, tested and guaranteed. 59/6.



# R+TV

**RADIO & TV COMPONENTS (Acton) Ltd.**

21d High Street, Acton, London W3 6NG


Also at 323 Edgware Road, London, W.2

ALL ORDERS BY POST TO OUR ACTON BRANCH

Terms C.W.O. All enquiries S.A.E.

## Complete Stereo System £41

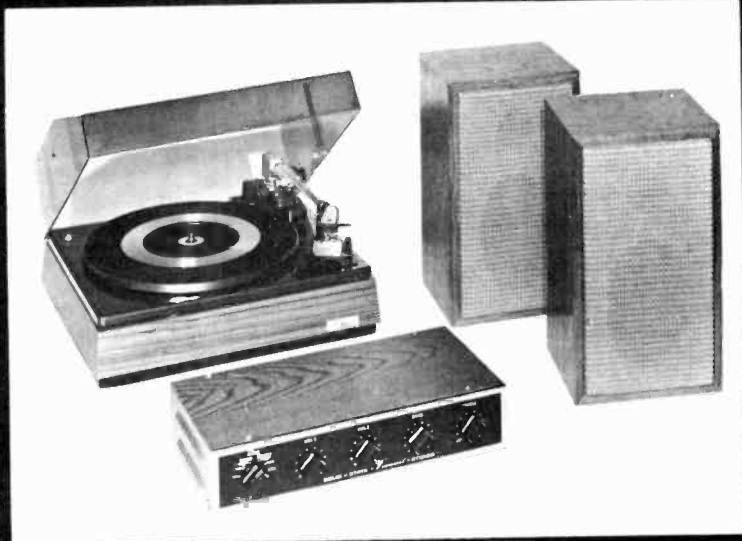**WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER**



This superb stereo system is a real price breakthrough. It comprises the VISCOUNT F.E.T. Mk. I amplifier on which full details are given below, the famous Garrard SP25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½in × 10½in × 6½in, the Duo type 2 speakers are beautifully finished in simulated teak veneer with matching vyna r grills. They incorporate a 10½in × 6½in drive unit and high frequency speaker, both of which are of 3 ohms. impedance. The Duo speaker system is also available separately at **£6.6.0** each plus 15/- P. & P.

Complete stereo system **£41** plus **£2.10.0 P. & P.**

With Mk. II Amplifier and Magnetic Cartridge **£45** plus **£2.10.0 P. & P.**



### The Classic

Simulated teak case

**£9.10**

Plus P. & P. 7.6

#### SPECIFICATION :

Sensitivities for 10 watt output at 1kHz into 3 ohms. Tape Head: 3mV (at 31 i.p.s.) Mag. P.U.: 2 mV. Cer. P.U.: 80mV. Tuner: 100mV. Aux.: 100mV. Tape/Rec. Output. Equalisation for each input is correct to within +2dB (R.I.A.A.) from 20Hz to 20KHz. Tone Control Range: Bass: 13dB at 60Hz. Treble: ±14dB at 15KHz. Total Distortion: (for 10 watt output) < 1.5%. Signal Noise: < -60dB. A.C. Mains 200-250V. Size 12½in long, 4½in deep, 2½in high. **Built and tested.**

### The Viscount F.E.T. Mk. I £14.5.0

Plus 7/6 P. & P.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

#### SPECIFICATION

Output per channel—10W rms. Frequency bandwidth 20Hz to 20kHz ±1dB @ 1W.

Total distortion @ 1kHz @ 9W 0.5%. Input sensitivities—CER. P.U. 100mV into 3 MΩ; Tuner 100mV into 100KΩ; Tape 100mV into 100kΩ.

Overload Factor—Better than 26dB. Signal to noise ratio—70dB on all inputs (with vol. max).

#### Mk. II (MAG. P.U.) £15.15.0

Specification same as Mk. I, but with the following input: Mag. P.U. CER. P.U. Tuner.

Controls—6 position selector switch (3 pos. stereo and 3 pos. mono), separate vol. controls for left and right channels. Bass ±14dB @ 60Hz; Treble (with D.P.S. on/off) ±12dB @ 10kHz.

Tape recording output sockets on each channel. Size 12½in × 6in × 2½in in simulated teak case. Built and tested.

Post & packing 10/- extra.

Spec. on Mag. P.U. 3mV @ 1kHz input impedance 47kΩ. Fully equalised to within ±1dB RIAA. Signal to noise ratio—65dB (vol. max.).



### THE RELIANT Mk. II

SOLID STATE GENERAL PURPOSE AMPLIFIER

**£7.5.0** Plus P. & P. 7.6

Simulated teak case

#### SPECIFICATION: Output: 10

watts into a 3 ohms speaker.

Inputs: (1) for mike (10mV). Input (2) for gram. radio (250mV) individual bass and treble control.

Transistors: 4 silicon and three germanium. Mains input 220/250

volts. Size: 10½ × 4½ × 2½in.



### ELEGANT SEVEN Mk. III (350mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. **MAINS POWER PACK KIT: 9/6 extra.**

**£5.5.0** Plus P. & P. 7.6. Circuit 2.6. Free with parts.

### THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 × 8 × 3in.

**MAINS POWER PACK KIT: 9/6 extra.**

**£5.5.0** Plus P. & P. 7.6. Circuit 2/6. Free with parts.



### LIQUIDATED STOCK

## DANSETTE

TOURISTE MK3

CAR RADIO

ALL TRANSISTOR



Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7" 2" × 4½" deep.

Originally sold completely built for £15.4.6

Circuit diagram 2.6, free with parts

Speaker, baffle and fixing kit

**£6.6.0** plus 7.6 P. & P.

25/- extra plus 4/- P. & P. Speaker postage free when ordered with parts

### SET OF PARTS

**£6.6.0**

plus 7.6 P. & P.

# SOUND 50

## SOUND 50 AMPLIFIER AND SPEAKER SYSTEM

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

**Output Power** 45 watts R.M.S. (Sine wave drive). **Frequency response**—3db points 30 Hz at 18 KHz. **Total distortion** less than 2% at rated output. **Signal to noise ratio**: better than 60db. **Speaker Impedance** 3, 8 or 15 ohms. **Bass Control Range** ±13db at 60 Hz. **Treble Control Range** ±12db at 10 KHz. **Inputs** 4 inputs at 5 mV into 470 K. Each pair of inputs controlled by separate volume control. 2 inputs at 200 mV into 470 K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

**SPEAKERS!** Size 20" x 20" x 10" incorporating Baker's 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.



**COMPLETE SYSTEM £45**

plus 60/- P. & P.

**Amplifier £28.10.0 plus 20/- P. & P. Speakers each £12.10.0 plus 30/- P. & P.**

**RADIO & TV COMPONENTS (ACTON) LTD.**

Post orders to:—21d High Street, Acton, London W3 6NG







Also at 323 Edgware Road, London, W.2

Goods not despatched outside U.K.

Terms C.W.O.


All Enquiries S.A.E.

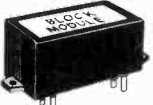

<p><b>BATTERY ELIMINATOR</b></p>  <p>Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2 in. x 1 in. Size approx. 4V 20/6, 6V 29/6, 9V 29/6, 7 1/2V complete with cable and plug for Philips Cassette. <b>39/6</b> each. Plus 2/- P. &amp; P.</p>	<p><b>CRESCENT RADIO LTD</b></p> <p>11 &amp; 40 MAYES ROAD, LONDON N22 6TL 888 3206</p> <p><b>WE HOLD THE LARGEST STOCK OF RETAIL COMPONENTS IN LONDON — SEND 3/- FOR CATALOGUE AND LISTS</b></p> <p>MAIL ORDER DEPT. No. 11 Mayes Rd. LONDON N22 6TL</p>	<p><b>TELETON TYPE NM.33 MAGNETIC CARTRIDGE</b></p> <p>Stereo with diamond styl. This ever popular cartridge now at economy price: Diamond Stylus, 7 mil; Frequency, 20-20kHz; Separation, 20db at 10kHz. <b>79/6</b> Plus 1/6 P. &amp; P.</p>
 <p><b>I.C. MODULE TYPE BP1010</b></p> <p>3W r.m.s. power amplifier and pre-amp. Complete with data sheet. Fully guaranteed. <b>25/-</b> P. &amp; P. 1/6 each. All Sinclair products are in stock. Please include postage with orders.</p>	<p><b>BRITISH RECORDING TAPE</b></p> <p>of the finest quality (all guaranteed). 5in 600ft, 8/6 each, 3 for 24/-, 5 1/2in 900ft, 10/- each, 3 for 28/6, 7in 1,200ft, 11/6 each, 3 for 33/- Please include 1/6 on each order for P. &amp; P.</p>	
 <p><b>SOLID STATE BLOCK MODULES</b></p> <p>Photo pre-amp E1311: input, 100K; gain, 28db; max. out, 3V; max. in, 50mA; power, 9V. Tape pre-amp E1312, as above. Mic. pre-amp E1313, as above. Power amplifier E1314: input, 1,000 ohms; gain, 20db, 300mW; power, 9V d.c. Electronic organ, tone org. E1315: tone freq. Dual flasher E1316: flasher time, 1/4 sec; power, 6V; current, 150mA. We also stock the Morse code practice modules in this range. <b>ALL AT 25/-</b> Plus 2/- P. &amp; P.</p>	 <p><b>EMI SET 850</b></p> <p>A complete speaker system <b>IN KIT FORM</b>. We supply a modern styled leak finish cabinet with black front. Overall dimensions: 14in x 9in x 9in. Made to a very high standard. A 6 1/2in EMI woofer. A 3in tweeter. A crossover network. Acoustic wadding. Output terminals, wire and fixing hardware. Specification: Max. power, 10W; frequency, 65-20kHz; imp. 8-15 ohms. Kit price <b>9 Gns.</b> Plus 7/6 p. &amp; P.</p>	<p><b>MAINS TRANSFORMER</b></p> <p>Fused Primary 240V. at 50MA. Secondary 240V 6.3V at 1A. This transformer is made to a very high standard and is a small size: 2 1/2 in x 2 1/2 in. <b>12/6</b> P. &amp; P.</p>
<p><b>PSYCHEDELIC LIGHT CONTROL UNIT</b></p> <p>Three Channel: Bass-Middle-Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500V lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) <b>£18.10.0.</b> Plus 7/6 P. &amp; P. If you require more information please send S.A.E.</p>	<p><b>IMPORTED PANEL METERS</b></p> <p>KA-38C 1 1/2in 1 1/2in. 50µA, 100µA, 500µA, 1MA, 5MA, 8 meter 13MA, 300V. All at <b>29/6</b> P. &amp; P.</p> <p>KA-65C 3 1/2in 3 1/2in. 300V, 8 meter 500µA, 1MA. All at <b>39/6</b> P. &amp; P.</p>	
<p><b>CRESCENT CASSETTES</b></p> <p>Top quality cassettes at unbeatable prices (complete with standard storage case): C60 7/6, C90 12/6, C120 17/6. Plus 1/- P. &amp; P.</p> <p><b>HIGH QUALITY IMPORTED HEADPHONES</b></p> <p>1,000Ω per phone ... <b>15/11</b> TTC 2,000Ω per phone ... <b>17/6</b> G1105 Plus 2/- P. &amp; P. per pair.</p> 	<p><b>LOW VOLTAGE AMPLIFIER</b></p> <p>5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. Few only at <b>35/-</b> plus 2/6 P. &amp; P.</p>	<p><b>STEREO HEADSET</b></p> <p>8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value <b>5 9/6</b> Plus 4/- P. &amp; P.</p> <p><b>STEREO JUNCTION BOX</b></p> <p>For stereo amplifiers without stereo jack socket. <b>2 5/-</b> Plus 1/6 P. &amp; P.</p> 



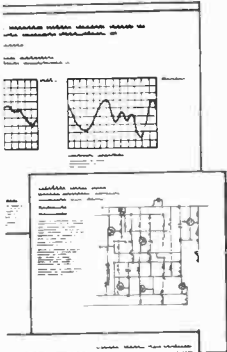
# Your first day on Television 5th January 1971



This is your opportunity to train as a television and radio engineer on our full-time 2 year College Diploma Course. That is the way to get into a rapidly growing industry with a tremendous demand for skilled technicians. You will be given theoretical and practical instruction on colour television receivers, following a syllabus specially designed to cover the new City and Guilds Radio, Television and Electronic Technicians' Course.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

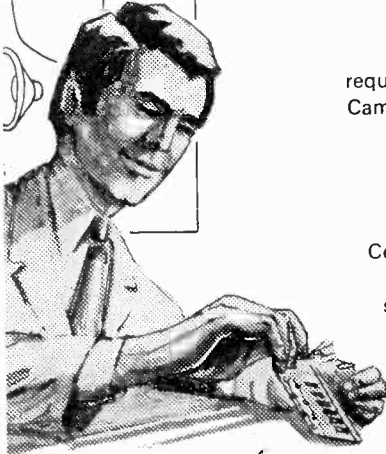Complete the coupon below and we will send you the details about training for an exciting, new career.



To: The Pembridge College of Electronics, (Dept. PE7 ), 34a Hereford Road, London, W2 5AJ.

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

## YATES ELECTRONICS (FLITWICK) LTD.

### RESISTORS

High stability carbon film. Very low noise. 0.5W 5% 4.7Ω to 2.2MΩ 2.5d each, 100+ 2d each, 0.5W 10% 4.7Ω to 10MΩ 2d each, 100+ 1.75d each. Quantity price applies for any selection. Ignore fractions on total order.

### DEVELOPMENT PACK

0.5 watt 5% resistors 5 off each value 4.7Ω to 1MΩ  
325 resistors E12 series 50/-  
650 resistors E24 series 100/-

### 4 WATT WIRE WOUND RESISTORS 1/6 each.

10% 1.0, 1.8, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 ohms.  
5% 10, 15, 20, 25, 39, 50, 100, 200 ohms.

### MULLARD POLYESTER CAPACITORS ±10%

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 6d.  
0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 7d. 0.047μF, 9d.  
0.068μF, 0.1μF, 10d.  
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 7d.  
0.1μF, 9d. 0.15μF, 0.22μF, 10d. 0.33μF, 1/3. 0.47μF, 1/6.  
0.68μF, 2/3. 1.0μF, 2/6.

250V: P.C. mounting miniature ±20%: 0.01μF, 0.015μF,  
0.022μF, 7d. 0.033μF, 0.047μF, 0.068μF, 8d. 0.1μF, 9d.  
0.15μF, 0.22μF, 1/- 0.33μF, 1/4.

### MYLAR FILM CAPACITORS

100V: 0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 6d. 0.05μF,  
0.1μF, 8d. 0.2μF, 1/-

### CAPACITOR DEVELOPMENT PACK

Selection of ceramic and polyester capacitors 100pF to 1.0μF.  
Total 100 capacitors, £2.18.0.

### MINIATURE ELECTROLYTIC CAPACITORS

50μF	6V	16μF	10V	10μF	12V	40μF	16V	16μF	40V
100μF	6V	64μF	10V	16μF	12V	6.4μF	25V	50μF	40V
200μF	6V	125μF	10V	50μF	12V	25μF	25V	2.5μF	64V
320μF	6V	200μF	10V	100μF	12V	8μF	40V	10μF	64V

1/- each

250μF 12V, 100μF 40V 1/6. 1000μF 25 volt 6/- 2500μF 25V 9/- 500μF 50 volts 5/- 1000μF 50 volt 8/-

### CERAMIC DISC CAPACITORS

100pF, 150pF, 220pF, 270pF, 330pF, 470pF, 560pF, 680pF,  
1000pF, 2000pF, 5000pF, 10,000pF, 5d each.

### GANGED STEREO POTENTIOMETERS

½ watt carbon track 5kΩ +5kΩ to 1MΩ +1MΩ log or linear  
8/- each.

### SKELETON PRE-SET POTENTIOMETERS

Linear: 100, 250, 500 ohms and decades to 5M ohm ±20%  
≤250kΩ, ±30%, 250kΩ. Horizontal or vertical P.C.  
mounting (0.1 matrix).

Miniature 0.3 watt 1/- each.

Sub-miniature 0.1 watt 10d each.

### TRANSISTORS

AC126 4/-	AF117 3/6	8FY51 3/9	2N3055 14/6
AC127 4/-	BC107 3/-	8FY52 4/6	2N3703 3/3
AC128 4/-	BC108 2/9	BSY56 6/-	2N3705 3/6
AD140 8/-	BC109 3/-	BSX21 5/-	2N3711 3/3
AF115 3/6	BFY50 4/6	2N2926 2/6	ORP12 9/6

DIODES—OA85, OA91, OA202, 1/6 each

### ZENER DIODE

400mW 5% 3.3V to 33V 3/6

### SILICON RECTIFIERS

IN4001 50V 1A 1/6	IN4006 800V 1A 3/-
IN4002 100V 1A 2/-	IN4007 1000V 1A 3/3
IN4003 200V 1A 2/3	BY124 100V ½A 1/6
IN4004 400V 1A 2/6	BYZ10 800V 6A 7/-
IN4005 600V 1A 2/9	BYZ13 200V 6A 4/-

### VEROBOARD

0.15	0.1	0.15	0.1
Matrix		Matrix	
2½ × 3½	3/3	17 × 3½ (plain)	10/6
2½ × 5	4/-	17 × 2½ (plain)	7/6
3½ × 3½	4/-	2½ × 5 (plain)	3/6
3½ × 5	5/3	2½ × 3½ (plain)	3/-
17 × 3½	15/-	Pin insertion tool	9/6 9/6
17 × 2½	11/6	Spot face cutter	7/6 7/6
17 × 5 (plain)	15/-	Pkt. 36 pins	3/- 3/-

### ROTARY SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, 4/6.

### JACK PLUGS AND SOCKETS

Standard Screened	3/6	2.5mm Insulated	1/6
Standard Insulated	2/9	3.5mm Insulated	1/6
Stereo Screened	7/-	3.5mm Screened	2/6
Standard Sockets	3/-	2.5mm Socket	1/6
Stereo Sockets	3/6	3.5mm Socket	1/6

C.W.O. please. 1/6 post and packing on orders under £1.  
Export Enquiries welcome

8E39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD

## TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2 1/2-750KHz. Bandwidth 0-5 MHz. Sensitivity 33mV/cm. Operating voltage 0/110/200/250V a.c. Supplied in excellent working condition. **\$22.10.0.** Carriage 30/-.

## AVO CT471A MULTIMETER

Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures AC/DC Voltages 12mV to 1200V. AC/DC Current 12uA to 1.2 Amp. Resistance 12 ohm to 120 MΩ HF, VHF, UHF. Voltage with multiplier 4V to 400V up to 60 Mc/s, 40mV to 4V up to 1,000 Mc/s. Offered in perfect condition. **\$55 each.** Carr. 10/-.

## CRYSTAL CALIBRATORS No. 10

Small portable crystal controlled wavemeter. Size 7 7/8" x 4". Frequency range 500 Kc/s. 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. **\$9.6.** Carr. 7/6.

## TAPE CASSETTES

Top quality in plastic library boxes. C60 60 min 8 1/2 for 24/8 C90 90 min 12/6 for 36/- C120 120 min 15/- for 43/6 Cassette Head Cleaner 11/8. All Post Extra.

## CLASS D WAVEFORMERS

A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6V d.c. Ideal for amateur use. Available in good used condition. **\$5.19.6.** Carr. 7/6, or brand new with accessories. **\$7.19.6.** Carr. 7/6.

## B.C. 221 FREQUENCY METERS

latest release 125kHz to 20MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. **\$27.10.0.** each. Carr. 10/-.

## AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Airmec. Frequency coverage 20-50Mc/s. AM C.W./P.M. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12 1/2 x 9 1/2 in. Supplied in brand new condition complete with all connectors fully tested. **\$45.** Carr. 20/-.

## AVO CT.38 ELECTRONIC MULTIMETERS


High quality 97 range instrument which measures a.c. and d.c. Voltage, Current, Resistance and Power Output Ranges d.c. volts 250mV-10,000V (10 megΩ-110 megΩ input). D.C. current 10μA-25A. Ohms. 0-1,000 megΩ a.c. volt 100mV-250V (with R.F. measuring head up to 250MHz) a.c. current 10μA-25A. Power output 50 micro-watts-5 watts. Operation 0/110/200/250V a.c. Supplied in perfect condition complete with circuit lead and R.F. probe. **\$25.** Carr. 15/-.

## ADMIRALTY B.40 RECEIVERS

High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650 KHz-30 MHz. I.F. 600KHz. Incorporates 2 R.P. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/250V a.c. Size 19 1/2 x 13 1/2 x 16in. Weight 114lb. Offered in good working condition. **\$22.10.0.** Carr. 30/-. With circuit diagrams. Also available B41 L.F. version of above. 15KHz-700KHz. **\$17.10.0.** Carr. 30/-.
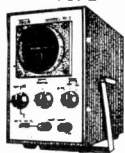
## TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CP8-1 MHz. Input imp. 2 megΩ 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. **\$22.10.0.** Carr. 10/-.



# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC. ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100		TYPE S-80	
100 x 80 mm		80 mm square fronts	
1mA	59/6	50μA	62/6
20V d.c.	59/6	100μA	59/6
50V d.c.	59/6	500μA	52/6
1A d.c.	59/6	1mA	49/6
5A d.c.	59/6	20V d.c.	49/6
300V a.c.	59/6	50V d.c.	49/6
500μA	62/6	VU Meter	78/-

## "SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in 4 1/2in fronts.		Type MR.38P. 1 21/32in square fronts.	
10mA	52/-	150mA	27/6
50mA	52/-	200mA	27/6
100mA	52/-	300mA	27/6
500μA	52/-	500mA	27/6
1A	52/-	750mA	27/6
5A	52/-	1A	27/6
15A	52/-	2A	27/6
30A	52/-	5A	27/6
20V d.c.	52/-	10A	27/6
50V d.c.	52/-	3V d.c.	27/6
300V d.c.	52/-	10V d.c.	27/6
15V a.c.	52/-	15V d.c.	27/6
15V a.c.	52/-	20V d.c.	27/6
300V a.c.	52/-	100V d.c.	27/6
8 Meter 1mA	57/6	300V d.c.	27/6
VU meter	72/-	500V d.c.	27/6
1A a.c.*	52/-	750V d.c.	27/6
5A a.c.*	52/-	15A a.c.*	27/6
10A a.c.*	52/-	50V a.c.*	27/6
20A a.c.*	52/-	150V a.c.*	27/6
30A a.c.*	52/-	300V a.c.*	27/6

Type MR.52P. 2 1/2in square fronts.		Type MR.45P. 2in square fronts.	
50μA	42/-	5A	30/-
50-0-50μA	52/-	10V d.c.	30/-
100μA	42/-	20V d.c.	30/-
100-0-100μA	47/6	50V d.c.	30/-
500μA	45/-	300V d.c.	30/-
1mA	40/-	15V a.c.	30/-
5mA	40/-	300V a.c.	30/-
10mA	40/-	8 meter 1mA	37/6
50mA	40/-	VU meter	45/-
100mA	40/-	1A a.c.*	30/-
500μA	40/-	5A a.c.*	30/-
1mA	40/-	10A a.c.*	30/-
5A	40/-	20A a.c.*	30/-
		30A a.c.*	30/-

## "SEW" BAKELITE PANEL METERS

Type MR.65P. 3 1/2in square fronts.		Type MR.65. 3 1/2in square fronts.	
50μA	67/6	500mA	35/-
50-0-50μA	55/-	1A	35/-
100μA	55/-	5A	35/-
100-0-100μA	47/6	15A	35/-
500μA	42/-	30A	35/-
500-0-500μA	42/-	50A	35/-
1mA	42/-	5V d.c.	35/-
5mA	42/-	10V d.c.	35/-
10mA	42/-	20V d.c.	35/-
50mA	42/-	50V d.c.	35/-
100mA	42/-	150V d.c.	35/-
500μA	42/-	300V d.c.	35/-
1A	42/-	50V a.c.*	35/-
5A	42/-	150V a.c.*	35/-
10A	42/-	300V a.c.*	35/-
50A	42/-	500mA a.c.*	35/-
20A	42/-	1A a.c.*	35/-
30A	42/-	5A a.c.*	35/-
60A	47/6	20A a.c.*	35/-
10V d.c.	42/-	30A a.c.*	35/-
		VU meter	62/-

\* MOVING IRON — ALL OTHERS MOVING COIL Please add postage

## EDGWISE METERS

Type PE.70. 3 17/32in 1 15/32in 2 1/2in

Send for illustrated brochure — Discounts for Quantities

## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range etc-etc. Single hole fixing. 1/2in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms, 14/6. P & P. 1/6. 100 WATT. 10/25/50/100/250/500/1,000/1,500 or 5,000 ohms, 21/-. P & P. 1/6. 100 WATT. 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms, 27/6. P & P. 1/6.

## FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and ICO, npn or pnp. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. **\$6.16.0.** P & P. 3/-.



## MARCONI TF142E DISTORTION FACTOR METERS. Excellent condition. Fully tested. \$20. Carr. 15/-.

## TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-111 megΩ. 6 Ranges ±1%. L. 1 μH - 11 μH. HENRY'S 6 Ranges ±0.5%. C. 10pF - 1110 nF. 6 Ranges ±2%. TURNS RATIO 1.1/1000-1:1100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 2in. **\$20.** P & P. 3/-.

## COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.c. coupled. Band width 1kc/s. Perfect order. **\$25.** Carr. 30/-.

## TE-20RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-250 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. **\$15.0.0.** P & P. 7/6. S.A.E. for details.

## LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s on 2 ranges. Output 500Ω or 5kΩ. Operation 200/250V. A.C. Supplied in perfect order. **\$12.10.0.** Carr. 10/-.

## TE22 SINE SQUARE WAVE AUDIO GENERATORS

200 Kc/s to 20 Mc/s on 6 bands. Square. 20c/s to 30 kc/s. Output impedance 5,000 ohms. 200/250V. A.C. Supplied brand new and guaranteed with instructions. **\$16.10.0.** Carr. 7/6.

## MARCONI TF885 VIDEO OSCILLATORS

0-5MHz. Sine Square Wave. **\$45.** Carr. 20/-.

## LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER

2pF-2,000 mfd 2 ohms-200 megohms. Also checks impedance, turns ratio, insulation, 200/250V a.c. Brand New **\$17.10.0.** Carr. 7/6.

## MARCONI TF195M BEAT FREQUENCY OSCILLATORS

0-40KHz. **\$20.** Carr. 30/-.

## ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons. J1B. AUDIO SIGNAL GENERATOR. 15 c/s to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms. **\$30.0.0.** VM79. UHF MILLIVOLT METER. 100 Kc/s to 1,000 Mc/s. a.c. 10 mV to 3V. D.c. 10 mV to 3V. Current 0-01 μA to 0-3 mA. Resistance 1 ohm to 10 megohm. **\$125.0.0.** TF18. TRANSISTOR TESTER. Full range of facilities for testing PNP or NPN transistors in or out of circuit. **\$37.10.0.** Carriage 10/- per item.

G. W. SMITH & CO (RADIO) LTD. Also see next two pages

# SEMI-CONDUCTORS/VALVES

## BRAND NEW & FULLY GUARANTEED

### TRANSISTORS


LN914	1/6 AC128	4/-	BSY38	4/8	IL4	2/6	25L6	7/8	EL91	5/-
LN4001	2/- AC154	4/8	BSY39	4/8	IL5	7/8	35Z4	8/8	EL95	7/-
LN4002	2/8 AC187	12/8	BSY56	18/-	IN5	5/-	25Z5	8/8	EM80	8/-
LN4003	3/- AC188	7/8	BSY95A	18/-	IT4	4/8	25Z6	11/8	EM81	8/8
LN4004	3/- AC189	7/8	BSY95A	2/6	IT4	4/8	30C15	11/8	EM84	7/8
LN4005	3/8 ACY17	5/8	BY100	3/8	U5	9/8	30C17	16/8	EM85	11/-
LN4006	4/8 ACY18	5/8	BY124	3/8	OA2	8/8	30C18	15/8	EM87	11/-
LN4007	4/8 ACY19	5/8	BY126	4/8	OB2	8/8	30F5	17/8	EY51	8/8
LN4148	1/8 ACY20	5/8	BY127	4/8	OZ4	1/8	30FL1	16/8	EY86	8/8
LN5004	4/8 ACY21	5/8	BYZ10	1/8	OL4	2/8	30FL12	18/8	EY87	8/8
2G301	4/8 ACY28	4/8	BYZ11	6/8	OD21	4/8	30FL14	18/8	EZ40	7/8
2G302	4/8 ACY28	4/8	BYZ12	6/8	Q4	8/8	30L15	17/8	EZ41	9/8
2G303	4/8 ACY40	4/8	BYZ13	5/8	3R4	7/8	30L17	17/8	EZ80	5/8
2G306	7/8 AD140	8/8	MJ480	18/8	3V4	7/8	30L12	18/8	EZ81	5/8
2G308	6/- AD149	11/8	MJ481	20/8	5R4	11/8	30L19	16/8	EZ82	9/8
2G309	6/- AD161	7/8	MPP102	8/8	5C4	8/8	30PL1	16/8	GZ34	11/-
2G371	3/- AD162	7/8	MPP103	7/8	5C4	8/8	30PL13	18/8	K166	27/8
2G374	4/- AF114	5/8	MPP104	7/8	5Y4	6/8	30PL14	17/8	K288	38/8
2G381	4/8 AF115	5/8	MPP105	7/8	5Z4I	7/8	35L6	9/8	MU14	8/8
2N686	4/8 AF116	5/8	NAT213	6/8	6J00L2	15/8	35W4	5/8	PABC80	8/8
2N687	4/8 AF117	5/8	NAT214	4/8	6AC7	4/8	35Z4	5/8	PC86	11/8
2N688	5/8 AF118	12/8	NAT216	7/8	6AG7	7/8	35Z5	7/8	PC88	13/8
2N706	2/6 AF119	4/8	NKT217	8/8	6AK5	8/8	50B5	7/8	PC87	8/8
2N706A	2/6 AF124	4/8	NKT224	6/8	6AK6	11/8	50C5	7/8	PC90	9/8
2N708	3/8 AF126	4/8	NKT241	5/8	6AL5	8/8	6A5	8/8	PC84	8/8
2N914	3/8 AF127	4/8	NKT261	4/8	6AQ5	8/8	807	9/8	PC88	12/8
2N916	3/8 AF139	6/8	NKT274	15/8	6A88	6/8	1625	6/8	PC89	10/8
2N918	4/8 AF138	11/8	NKT272	4/8	6A88	6/8	1625	6/8	PC89	10/8
2N929	4/8 AF180	10/8	NKT274	4/8	6AT6	5/8	5763	13/8	PC189	11/8
2N930	5/8 AF181	8/8	NKT275	4/8	6AU6	5/8	8146	8/8	PCF80	8/8
2N1131	5/8 AF186	9/8	NKT278	8/8	6AV6	6/8	AZ31	10/8	PCF82	8/8
2N1132	6/8 AF239	8/8	NKT381	5/8	6BA6	6/8	CY31	7/8	PCF84	9/8
2N1302	3/8 ASY26	5/8	NKT403	15/8	6BD6	8/8	DF91	9/8	PCF800	15/8
2N1303	3/8 ASY27	7/8	NKT404	15/8	6BH6	8/8	DF96	9/8	PCF801	15/8
2N1304	4/8 ASY28	5/8	NKT405	15/8	6BJ6	8/8	DF91	4/8	PCF801	15/8
2N1305	4/8 ASZ17	8/8	NKT773	5/8	6BQ7A	7/8	DF96	7/8	PCF802	15/8
2N1306	5/- AUY10	30/8	NKT10439	7/8	6BR7	17/8	DK91	7/8	PCF805	10/8
2N1307	5/- BAY31	1/8	OA5	2/8	6BR8	13/8	DK92	9/8	PCF806	15/8
2N1308	6/- BC107	3/8	OA10	2/8	6BW6	16/8	DK96	8/8	PCF808	18/8
2N1309	6/- BC108	3/8	OA47	1/8	6BX7	13/8	DL92	8/8	PC82	7/8
2N1613	5/- BC109	3/8	OA70	1/8	6C4	6/8	DL96	7/8	PCL84	8/8
2N1711	5/- BC113	5/8	OA81	1/8	6CD6	23/8	DM70	6/8	PCL85	9/8
2N1889	8/8 BC116	12/8	OA81	1/8	6CL6	10/8	DY86	6/8	PCL86	9/8
2N1893	8/8 BC125	11/8	OA80	1/8	6CW4	12/8	DY87	7/8	PPL200	11/8
2N147	14/8 BC126	11/8	OA90	1/8	6F1	12/8	EM8CC	12/8	PL26	11/8
2N2160	11/8 BC147	3/8	OA91	1/8	6FG6	15/8	E180F	15/8	PL81	9/8
2N2193	9/8 BC148	3/8	OA95	1/8	6F13	7/8	EAB30	8/8	PL82	9/8
2N2197	5/8 BC149	3/8	OA290	2/8	6F14	12/8	EAF42	10/8	PL83	8/8
2N2218	6/8 BC167	3/8	OA290	2/8	6F15	11/8	EB91	3/8	PL84	7/8
2N2219	6/8 BC172	3/8	OA210	3/8	6F18	8/8	EBC41	10/8	PL500	15/8
2N2369	3/8 BC177	7/8	OC19	8/8	6F18	8/8	EBC41	10/8	PL500	15/8
2N2369A	4/- BC182L	7/8	OC20	15/8	6P23	15/8	EBC81	6/8	PL504	16/8
2N2484	6/8 BC184L	4/8	OC23	10/8	6H6	3/8	EBF80	8/8	PY32	11/8
2N2613	7/8 BC212L	4/8	OC24	11/8	6J4	9/8	EBF83	8/8	PY33	12/8
2N2646	11/8 BCY30	5/8	OC26	10/8	6J5	9/8	EBS9	8/8	PY80	6/8
2N2904	7/8 BCY31	5/8	OC28	10/8	6J6	3/8	ECL82	12/8	PY81	6/8
2N2923	3/8 BCY32	4/8	OC29	12/8	6K8G	9/8	ECC40	11/8	PY88	8/8
2N2924	3/8 BCY33	4/8	OC35	8/8	6L6GT	9/8	ECC84	6/8	PY800	10/8
2N2925	3/8 BCY34	4/8	OC36	12/8	6LD30	6/8	ECC85	5/8	PY801	10/8
2N2926A	2/8 BCY42	3/8	OC41	4/8	6Q7	7/8	ECC88	8/8	U25	15/8
2N2926B	2/8 BCY43	3/8	OC42	5/8	6SG7	7/8	ECC82	7/8	U26	15/8
2N3053	11/8 BCY71	8/8	OC44	4/8	6S7	7/8	ECP86	12/8	U32	6/8
2N3054	11/8 BCY72	3/8	OC46	3/8	6SK7	6/8	ECH21	11/8	U191	14/8
2N3055	11/8 BCZ11	7/8	OC70	3/8	6SL7	6/8	ECH35	12/8	U191	14/8
2N3891A	6/8 BD121	15/8	OC71	2/8	6SN7	5/8	ECH42	13/8	U282	8/8
2N3416	7/8 BD122	12/8	OC72	2/8	6SQ7	6/8	ECH83	8/8	U301	11/8
2N3570	3/8 BF115	5/8	OC73	5/8	6V6G	6/8	ECL80	9/8	U801	20/8
2N3702	3/8 BF117	9/8	OC74	6/8	6V6GT	6/8	ECL82	6/8	UABC80	20/8
2N3704	4/8 BF167	5/8	OC75	4/8	6X4	5/8	ECL33	12/8	UAF42	10/8
2N3705	4/8 BF173	6/8	OC76	4/8	6X5G	5/8	ECL86	8/8	UBC41	9/8
2N3706	4/8 BF180	7/8	OC77	6/8	6X5GT	5/8	E3F37A	8/8	UBF80	7/8
2N3707	4/8 BF181	8/8	OC78	4/8	6X5GT	5/8	E3F39	8/8	UBF89	7/8
2N3708	3/8 BF182	8/8	OC81	4/8	10F1	18/8	E40	14/8	UCC84	9/8
2N3709	3/8 BF184	6/8	OC81D	4/8	10F1	18/8	E41	12/8	UCC85	8/8
2N3710	3/8 BF185	8/8	OC83	5/8	10P14	20/8	E42	10/8	UCC85	8/8
2N3711	4/8 BF194	4/8	OC84	5/8	12AT6	5/8	E40	5/8	UCP80	10/8
2N3819	7/8 BF195	5/8	OC139	6/8	12AT7	4/8	E45	7/8	UCP21	11/8
2N3903	7/8 BF200	10/8	OC140	6/8	12AU7	5/8	E46	6/8	UCP42	13/8
2N3904	7/8 BF224	4/8	OC169	6/8	12AX7	5/8	E49	5/8	UCP81	6/8
2N3905	7/8 BF225	4/8	OC170	6/8	12AV6	6/8	E49	5/8	UCL82	7/8
2N3906	7/8 BF225	4/8	OC171	6/8	12BA6	6/8	E49	5/8	UCL83	12/8
2N4058	4/8 BF244	4/8	OC200	6/8	12BE6	6/8	EF183	6/8	UF41	10/8
2N4059	4/8 BF244	4/8	OC201	9/8	12BH7	6/8	EF184	7/8	UF80	7/8
2N4061	4/8 BF249	7/8	OC202	12/8	19AQ6	6/8	EH90	8/8	UF85	8/8
2N4062	4/8 BF249	7/8	OC203	8/8	20D1	9/8	EL34	10/8	UF89	7/8
2N4063	4/8 BF249	7/8	OC204	8/8	20P2	15/8	EL33	10/8	UF41	12/8
2N4287	3/8 BFX44	7/8	OC205	8/8	20L1	20/8	EL41	11/8	UF94	8/8
2N4288	3/8 BFX45	7/8	OC207	12/8	20P1	12/8	EL42	11/8	UY41	8/8
2N4289	3/8 BFX46	7/8	OC211	8/8	20P3	12/8	EL41	10/8	UY41	8/8
2N4290	3/8 BFX47	7/8	OC212	10/8	20P4	20/8	EL44	5/8	VR105/30	5/8
2N4291	3/8 BFX48	7/8	OC213	10/8	20P5	20/8	EL45	8/8	VR160/30	5/8
2N4292	4/8 BFX12	12/8	P46A	2/8						
2N4293	4/8 BFX13	4/8	PL4001	2/8						
2N4294	4/8 BFX14	4/8	PL4002	3/8						
2N4295	4/8 BFX15	4/8	PL4003	3/8						
2N4296	4/8 BFX16	4/8	PL4004	3/8						
2N4297	4/8 BFX17	4/8	PL4005	3/8						
2N4298	4/8 BFX18	4/8	PL4006	4/8						
2N4299	4/8 BFX19	4/8	PL4007	4/8						
2N4300	4/8 BFX20	4/8	PL4008	4/8						
2N4301	4/8 BFX21	4/8	PL4009	4/8						
2N4302	4/8 BFX22	4/8	PL4010	4/8						
2N4303	4/8 BFX23	4/8	PL4011	4/8						
2N4304	4/8 BFX24	4/8	PL4012	4/8						
2N4305	4/8 BFX25	4/8	PL4013	4/8						
2N4306	4/8 BFX26	4/8	PL4014	4/8						
2N4307	4/8 BFX27	4/8	PL4015	4/8						
2N4308	4/8 BFX28	4/8	PL4016	4/8						

### VALVES

LN914	1/6 AC128	4/-	BSY38	4/8	IL4	2/6	25L6	7/8	EL91	5/-
LN4001	2/- AC154	4/8	BSY39	4/8	IL5	7/8	35Z4	8/8	EL95	7/-
LN4002	2/8 AC187	12/8	BSY56	18/-	IN5	5/-	25Z5	8/8	EM80	8/-
LN4003	3/- AC188	7/8	BSY95A	18/-	IT4	4/8	25Z6	11/8	EM81	8/8
LN4004	3/- AC189	7/8	BSY95A	2/6	IT4	4/8	30C15	11/8	EM84	7/8
LN4005	3/8 ACY17	5/8	BY100	3/8	U5	9/8	30C17	16/8	EM85	11/-
LN4006	4/8 ACY18	5/8	BY124	3/8	OA2	8/8	30C18	15/8	EM87	11/-
LN4007	4/8 ACY19	5/8	BY126	4/8	OB2	8/8	30F5	17/8	EY51	8/8
LN4148	1/8 ACY20	5/8	BY127	4/8	OZ4	1/8	30FL1	16/8	EY86	8/8
LN5004	4/8 ACY21	5/8	BYZ10	1/8	OL4	2/8	30FL12	18/8	EY87	8/8
2G301	4/8 ACY28	4/8	BYZ11	6/8	OD21	4/8	30FL14	18/8	EZ40	7/8
2G302	4/8 ACY28	4/8	BYZ12	6/8	Q4	8/8	30L15	17/8	EZ41	9/8
2G303	4/8 ACY40	4/8	BYZ13	5/8	3R4	7/8	30L17	17/8	EZ80	5/8
2G306	7/8 AD140	8/8	MJ480	18/8	3V4	7/8	30L12	18/8	EZ81	5/8
2G308	6/- AD149	11/8	MJ481	20/8</						
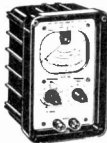
### RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0.2µsec to 100µsec/min.  
Supplied complete with all accessories and instructions. £87. Carr. paid.




### MARCONI CT44/TF956 AF ABSORPTION WATTMETER

1 µwatt to 6 watts.  
£20. Carr. 20/-.
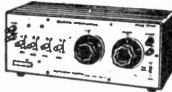
### TELLI DECADE RESISTANCE ATTENUATOR

Variable range 0-11dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0-1dB × 10) + (1dB × 10) + 10 + 20 + 30 + 40dB. Frequency: i.e. to 200kHz (-3dB). Accuracy: 0-0.5dB. +4 indication dB (-0.01). Maximum input less than 4W (50V). Built in 900 Ω load resistance with internal/external switch. Brand new £27.10. P. & P. 5/-.



### BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR



Attractive two-tone case 7 1/2" x 5 1/2" x 2 1/2". Price £17.10. Carr. 3/6.



**TE-16A Transistorised Signal Generator.** 6 ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 kHz modulation. 5 1/2" x 3 1/2" x 3 1/2". Complete with instructions and leads. £27.19. P. & P. 4/-.

### BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR



New high quality portable instrument. Sine 1Hz to 100kHz. Square 20Hz to 20kHz. Output max. +10dB (10k Ω). Operation 220/240V a.c. Size 216mm x 150mm x 120mm. Price £27.10. Carr. 5/-.

### T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0.1 / 0.03 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. 4cs. 1.2Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. £17.10. Carr. 5/-.



### TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms, 220/240V a.c. operation. Complete with probe and instructions. £17.10. P. & P. 6/-. Additional Probes available: R.F. 42/6. H.V. 50/-.

### AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.  
160 W. £2.2.6. P. & P. 3/6  
300 W. £3.5.0. P. & P. 4/6  
500 W. £4.10.0. P. & P. 6/6  
1,000 W. £6.10.0. P. & P. 7/6  
1,500 W. £8.10.0. P. & P. 8/6  
7,500 W. £15.10.0. P. & P. 20/-

### SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 230/240V a.c. Output continuously variable from 20V to 230V.  
Model MR2306 5A 68 x 46 x 43mm. £8.7.6. Model MR2310 10A 90 x 68 x 60mm. £11.9.0. Postage 2/6.

## MULTIMETERS for EVERY purpose!



**TECH PT-34.** 1,000 O.P.V. 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA. £16.00. P. & P. 2/6.



**MODEL TE-200.** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50µA/250mA. 0/60K/6 meg. -20 to +62dB. 75/- P. & P. 3/-.



**MODEL TE-70.** 30,000 O.P.V. 0/3/15/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/300/300mA. 0/16K/160K/1.5M/16 meg. £5.10.0. P. & P. 3/-.



**TMK MODEL TW-50K.** 46 ranges, mirror scale. 50K/Volt d.c. 5K/Volt a.c. D.C. volts: 0-125, 0-25, 1-25, 2-5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. volts: 1-5, 3, 1,000V. A.C. volts: 1-5, 3, 1,000V. D.C. current: 25, 50µA, 2-5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 10K, 100K, 1 meg., 10 meg. Decibels: -20 to +81.5dB. £8.17.6. P. & P. 3/6.




**TE-800 20,000 Ω/VOLT GIANT MULTIMETER.** Mirror scale and overload protection. 6in full view meter. 2 colour scales. 0/2.5 / 10 / 250 / 1,000 / 5,000V a.c. 0/25/12.5/10/50/250/1,000/5,000V d.c. 0/50µA/110/100/600mA/10A. d.c. 0/2K/200K/20 meg. ohm. £15.0.0. P. & P. 5/-.



**MODEL 502S.** 57 ranges, giant 5 1/2in meter, polarity reverse switch. Sensitivity: 50K/Volt d.c. 5K/Volt a.c. D.C. volts: 0-125, 0-25, 1-25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. current: 25, 50µA, 2-5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 2K, 10K, 100K, 1 meg., 10 meg. Decibels: -20 to +85dB. £12.10.0. P. & P. 3/6.
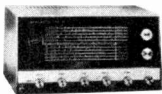
### LAFAYETTE HA-600 SOLID STATE RECEIVER



General coverage 150-400kHz, 550kHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter, Bandsread, RF Gain. 15in x 9 1/2in x 8 1/2in. 220/240V a.c. or 12V d.c. Brand new with instructions. £45. Carr. 10/-.

### TO-3 PORTABLE OSCILLOSCOPE



3in. tube. Y amp. Sensitivity 0.1V p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF. X amp. sensitivity 0.9V p-p/CM. Bandwidth 1.5 cps-800 KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £37.10.0. Carr. 10/-.



### "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

MODEL S-260 General Purpose Bench Mounting		MODEL S-260 B Panel Mounting	
1A	£5.10.0	1A	£5.10.0
2.5A	£6.15.0	2.5A	£6.12.6
5A	£9.15.0	Please add postage	
8A	£14.10.0	ALL MODELS	
10A	£18.10.0	INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT	
12A	£21.0.0	VARIABLE 0-280 VOLTS	
20A	£37.0.0	Special discounts for quality	

**HONOR TE.10A.** 20K Ω/Volt 5/25/50/250/500/2,500V d.c. 0/50/100/500/1,000V a.c. 0/50µA/2.5mA/250mA d.c. 0/6K/6 meg. ohm. -20 to +22dB. 10-0, 100 mfd. 0-100-0-1 mfd. 69/6. P. & P. 5/-.



**MODEL TE-300.** 30,000 O.P.V. Mirror scale, overload protection. 0/0.6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. -20 to +63dB. £5.19.6. P. & P. 3/-.



**MODEL TE-90.** 50,000 O.P.V. Mirror scale, overload protection. 0/0.3/3/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/6K/160K/1.6/16 meg. -20 to +63dB. £7.10.0. P. & P. 3/-.



**TMK MODEL TW-20CB.** Features Resettable Overload Button. Sensitivity: 20K Ω/Volt d.c. 5K Ω/Volt a.c. D.C. volts: 0-0.5, 2-5, 10, 50, 250, 1,000V. A.C. volts: 0-0.5, 10, 50, 250, 1,000V. D.C. resistance: 0-0.5, 0.5, 5, 50, 500mA, 10A. Decibels: -20 to +63dB. £11.10.0. P. & P. 3/6.




**MODEL AS-100D.** 100K Ω/Volt. 5in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V d.c. 0/6/30/120/300/600V a.c. 0/10µA/6/60/300mA/12A. 0/2K/200K/2M/200M. -20 to +17dB. £12.10.0. P. & P. 3/6.



**TMK LAB TESTER.** 100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 Ω/V d.c. 5/Volt a.c. D.C. volts: 0.5, 2.5, 10, 50, 250, 1,000V. A.C. volts: 3, 10, 50, 250, 500, 1,000V. D.C. current: 10, 100µA, 10, 100, 500mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 10 meg, 100 meg. Decibels: -10 to +49dB. Plastic case with carrying handle, size 7 1/2in x 6 1/2in x 3 1/2in. £18.18.0. P. & P. 6/-.


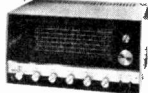
### LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER



3-8.4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54MHz. Dual conversion, 2 mech. filters, product detector, variable BFO. 8 Meter, 100kHz calibrator. 220/240V a.c. or 12V d.c. 15in x 9 1/2in x 8 1/2in. Brand new with instructions. £57.10.0. Carr. paid (100KHz Crystal 39/8 extra).

### LAFAYETTE PF60 VHF FM RECEIVER



Solid State. 152-174MHz. Fully tuneable or crystal controlled (not supplied). Built in Speaker, Squelch and Volume Controls. 220/240V a.c. or 12V d.c. Brand new with instructions. £37.10.0. Carr. 10/-.

### UNR-30 RECEIVER



4 Bands covering 500KHz-30MHz. B.F.O. Built in Speaker. 220/240V a.c. Brand new with instructions. £19.18.0. Carr. 7/6.

### WS62 TRANSCEIVERS

Large quantity available for EXPORT! Excellent condition. Enquiries invited.

### UR-1A SOLID STATE COMMUNICATION RECEIVER



4 Bands covering 500KHz-30MHz. FET, 8 Meter, Variable BFO for 8SB. Built in Speaker, Telescopic Aerial, Bandsread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2in x 4 1/2in x 7in. Brand new with instructions. £24. Carr. 7/6.

### FULL RANGE OF CODAR AMATEUR EQUIPMENT IN STOCK


### LAFAYETTE LA-324 STEREO AMPLIFIER



Solid State. 12.5W r.m.s. per channel. 20-20,000Hz ±1dB. Inputs Mag/Cer/Tuner/Aux. Output 4-16". Headphone socket, tape output. Black and brushed aluminium front panel. 10 1/2in x 3 1/2in x 8 1/2in. £24. Carr. 7/6.

### FULL RANGE OF PARTRIDGE JOYSTICK AERIALS IN STOCK

### TRIO 9R59DE COMMUNICATION RECEIVER

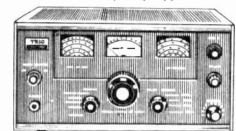

4 bands 500KHz-30MHz. 8 Meter, Variable B.F.O., Bandsread, 7in x 15in x 10in. 115/250V a.c. Brand new with instructions. £42. Carr. Paid. Full Range of other Trio Products in stock.  
JR.5008E Amateur Receiver £65.0.0  
JR.310 Amateur Receiver £77.10.0  
TS.510 Amateur Transceiver £180.0.0  
SP5D Matching Speaker £4.7.6  
HS4 Headphones £5.19.6

### VOLTAGE STABILISER TRANSFORMERS

180-260V input. Output 230V. Available 180V or 225V. £12.10.0. Carr. 5/-.

### EDDYSTONE VHF RECEIVERS MODEL 770E.

19-165 Mc/s. Excellent condition. £150.

### TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £8.19.6. P. & P. 3/6.



## G.W.SMITH & CO. (RADIO) LTD

All Mail Orders to -  
147, Church Street, London, W.2  
Tel: 01-262 8562  
(Trade supplied)

3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)



OPEN DAILY  
9.15 a.m.-6 p.m.  
(Closed all day  
Thursday)

# Garland Bros. Ltd.

DEPTFORD BROADWAY (Corner of Brookmill Road)  
LONDON, S.E.8

TELEPHONE  
01-692 4412

## OSMABET LTD.

We make transformers amongst other things

### MAINS TRANSFORMERS

Prim 200/240V a.c. TX1 425-0-425V 250 mA, 6-3V 4A CT, 6-3V 4A CT, 0-5-6V 3A, 135/-; TX2 250-0-250V 150 mA, 6-3V 4A, CT, 0-5-6V 3A, 78/8; TX3 300-0-300V 120 mA, 6-3V 2A, CT, 6-3V 2A, 6-3V 1A, 78/8; TX8 250-0-250V 65 mA, 6-3V 1.5A, 42/-; MT1 200V 30 mA, 6-3V 1A, 24/-; MT2 230V 45 mA, 6-3V 1.5A, 28/8; MT3 250V 60 mA, 6-3V 2A, 37/8; MT3 Prim 110/240V Sec 250V 100 mA, 6-3V 2A, 45/-.

### MULTIVOLT TRANSFORMERS

Prim 200/240V a.c. OMT3/1 one tapped sec. 5-20-30-40-60V giving 5-10-15-20-25-30-35-40-55-60, 10-0-10, 20-0-20, 30-0-30V a.c. 1A, 45/-; ditto transformer 2A OMT4/2, 67/8; OMT5/1 one tapped sec. 40-50-60-80-90-100-110V, giving 10-20-30-40-50-60-70-80-90-100-110V, 10-0-10, 20-0-20, 30-0-30, 40-0-40, 50-0-50V a.c. 1A, 67/8.

### LOW VOLTAGE TRANSFORMERS

Prim 200/240V a.c.: 6-3V 1.5A, 16/8; 3A, 20/-; 6A CT, 34/-; 12V 1.5A, 21/-; 3A CT, 34/-; 6A CT, 45/-; 18V 1.5A CT, 26/8; 24V 1.5A CT, 34/-; 3A CT, 56/8; 5A, 75/-; 8A, 112/8; 12A, 165/8.

### MIDGET RECTIFIER TRANSFORMER

For FW rectification, size 1 1/2" x 1 1/2". Prim 200/240V a.c., output PPT1 0-0-0V 0-3A, PPT2 12-0-12V 0-25A, PFT3 20-0-20V 0-15A, 22/8 each.

### OUTPUT TRANSFORMERS

Mullard 510 UL, 67/8; 7W stereo UL, 80/-; 3W PPS, 30/-; P.P.11K/3-8-15ohm, 21/-; Multi ratio 7/10W, 33/-; 30W (KT66, etc.), 135/-; 3-15ohms, 78/8; 50W (6L34 KT66, etc.), 135/-; 100W (E134 KT66, etc.), 225/-; standard 3-W O/P 5K/3ohm or 10K/3ohm, 14/8; auto matching transformer 10W, 3-8-15 ohm up or own, 15/-; 100V line trans. to order.

### LOUDSPEAKERS

New, boxed, famous makes, 25W, 110/-; 35W, 130/-; 50W, 180/-; 60W, 215/-; 100W, 350/-; E.M.I. 13" x 8in, 10W, 3, 8 and 15ohms at 45/- each; H.P. 13" x 8in, 10W speakers, fitted two tweeters and crossover network 3, 8 and 15ohms, 80/- each.

### BULK TAPE ERASERS

Instant erasure of magnetic tape, demagnetizing of tape heads. 47/6 post 2/6, leaflet S.A.E.

### CAPACITORS

Electrolytics, 1,000mF 25V, 4/8; 2,500mF 50V, 10/8; 6,000mF 15V, 4/8; 1,500mF 150V, 10/8; 10,000mF 25V, 17/8; 64mF 450V, 5/-; 80mF 450V, 5/-; 32mF 500V, 5/-; 100-400mF 275V, 6/-; 60 x 100mF 450V, 7/8; 4mF 350V, 1/8.

Carriage extra all orders

S.A.E. ALL ENQUIRIES PLEASE, MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8YG  
Tel. 958 9314

## THE NEW JULIETTE MPR 3065

is a high quality  
COMMUNICATIONS  
RECEIVER

(replaces NA 5018A)  
Recommended Price  
£42 0 0

Our Price **36 Gns.**




(Cash only) plus 9/- p. & p. Complete with standard batteries and earpiece. BFO (optional extra) add 35/-.

IT NOT ONLY RECEIVES Aircraft, Shipping (VHF & SW), Taxis, Ambulances, Fire Service, T.V. Sound, Hams, Gas and Electric Boards, Public Services and many other radio telephone mobiles—BUT ALSO Classical Music, Pop and all that Jazz.

**TURN ON AND TUNE IN!!!** The **TURN 3065** is a communications receiver and entertainment source in one neat, transistorised, portable package. It keeps aircraft, shipping, RT mobiles, FM and AM broadcasts at your fingertips. Features a colour coded illuminated tuning dial and band selector, AFC, squelch, BFO (optional extra), large speaker. Works off mains or batteries. Size: 10 1/2 x 7 1/2 x 4 inches. **FREQUENCIES:** Medium Wave, 540-1600 Kcs.; Marine, 1.6-4.6 Mcs.; FM/VHF, 88-108 Mcs.; Aircraft, 108-136 Mcs. (Military, Civil and Ground control); High VHF/PB, 146-176 Mcs. (Commercial and Industrial RT mobiles). Availability of mobile transmissions depend on operators in each area.

**STOCKTON PARTNERS (Dept. P.E.)**  
Importers and Distributors  
Brighowgate, Grimsby, Lincs.  
Tel. 0472 64196/58815

## DIMMASWITCH

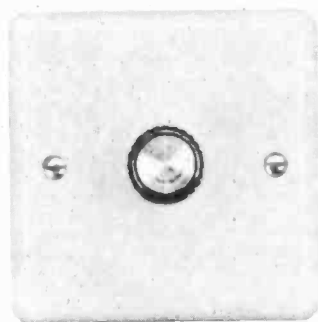

This is an attractive dimmer unit which fits in place of the normal modern light switch. The ivory mounting plate matches modern fittings and the control knob is in bright chrome. An ON/OFF switch is incorporated to control 40-600 watts of all lights except fluorescents at mains voltages from 200-250V, 50 Hz.

Competitive products sell at £4 19s 6d—our price is £3 4s. We also offer at £2 14s a complete kit of parts with instructions enabling you to build this dimmer yourself.

The circuit uses a miniature RCA triac and a diac triggering device to give complete reliability. Radio interference suppression is included.

Post and Packing 1/6d extra.

Please send Cash with Order to:

### DEXTER & COMPANY

ULVER HOUSE, 19 KING STREET  
CHESTER CHI 2AH  
Tel.: Chester 25883

As supplied to H.M. Govt. Departments, Hospitals, Local Authorities, etc.



# ELECTROVALUE

EVERYTHING BRAND NEW & TO SPEC. ● LARGE STOCKS ● NO SURPLUS

## BARGAINS IN NEW SEMICONDUCTORS

Many items at new reduced prices. All power types supplied with free insulating sets

1N914	1/3	2N3706	2/6	40512	39/-	BC147	3/-	BPY51	4/-
1N3754	4/-	2N3707	2/6	40602	9/6	BC148	3/-	BXN20	3/9
1N4148	1/9	2N3708	2/6	AC107	14/6	BC149	3/-	BY164	10/-
1N5054	1/-	2N3709	2/6	AC126	4/-	BC153	7/-	BY238	3/6
1S940	3/6	2N3710	2/6	AC127	4/-	BC154	7/6	C106BJ	14/6
2N696	3/6	2N3711	2/6	AC128	4/-	BC157	3/9	MC140	5/-
2N697	2/6	2N3731	24/-	AC176	6/-	BC158	3/9	MJ480	21/-
2N706	3/9	2N3734	3/-	ACY22	4/6	BC169	3/9	MJ481	27/-
2N1131	6/3	2N3819	7/-	ACY40	4/-	BC167	2/9	MJ491	30/-
2N1132	6/6	2N3820	12/-	ACY41	5/-	BC168	2/3	MPT102	7/6
2N1302	4/-	2N3904	7/6	AD142	14/3	BC169	2/6	NKT403	15/6
2N1303	4/-	2N3906	7/6	AD149	12/-	BC177	6/3	NKT405	1/3
2N1304	4/6	2N4038	4/-	AD161/AD162	12/-	BC178	5/8	OAA7	1/9
2N1305	4/6	2N4039	4/-	(unmatched) 14-	pr.	BC179	6/-	OAO9	1/3
2N1613	6/-	2N4060	4/-	AF114	7/-	BC182L	2/6	OA91	1/3
2N1711	7/-	2N4061	4/-	AF115	7/-	BC183L	2/6	OA95	1/3
2N2147	19/-	2N4062	4/-	AF116	6/6	BC184L	2/6	OA99	3/-
2N2218	9/3	2N4284	3/3	AF117	7/6	BC186	8/6	OA200	1/11
2N2270	9/3	2N4286	3/3	AF124	6/6	BC212L	5/-	OA202	2/-
2N2483	9/3	2N4289	3/3	AF127	7/6	BC213L	5/-	OC71	7/6
2N2484	6/6	2N4291	3/3	AF139	9/6	BC214L	5/3	TIP31A	16/-
2N2646	10/9	2N4292	3/3	AF180	18/6	BCY50	4/-	TIP32A	20/-
2N2904	11/-	2N4410	4/9	AF239	9/9	BD121	21/-	TIP43	10/6
2N2924	4/-	2N5002	12/3	ASY26	6/6	BD123	20/-	ZTX300	3/6
2N2925	4/6	2N5163	5/-	ASY27	8/3	BD124	20/-	ZTX301	3/6
2N2926	2/3	2N5192	25/-	ASY28	8/6	BF167	8/6	ZTX302	4/6
2N3053	5/6	2N5195	28/3	B5041	15/-	BF178	10/6	ZTX303	4/6
2N3054	14/3	2N5457	9/9	BA102	6/-	BF180	12/-	ZTX304	6/9
2N3055	15/-	2N5459	9/9	BA156	4/6	BF195	7/6	ZTX500	5/-
2N3225	10/6	40250	14/3	BM156	4/6	BFY29	6/3	ZTX501	5/-
2N3663	11/6	40361	12/6	BC107	2/6	BFX84	5/9	ZTX502	6/-
2N3702	2/6	40362	18/-	BC108	2/6	BFX85	7/-	ZTX503	5/-
2N3703	2/6	40406	16/3	BC109	2/9	BFX87	5/9	ZTX504	12/-
2N3704	2/6	40408	14/6	BC125	11/-	BFX88	5/3	ZTX330	5/5
2N3705	2/6	40430	37/-	BC126	11/-	BFY50	4/6	ZTX331	6/9

## PEAK SOUND PRODUCTS ENGLEFIELD AMPLIFIER



Build it 12 + 12 watts

Stereo amplifier in modular kit form (including cabinet) 12 watts per channel £38.90. Cabinet kit only £6. These prices nett. As recently reviewed in Hi Fi Sound.

## BAXANDALL SPEAKER SYSTEM



Designed by Peter Baxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 15Ω 69RM109 speaker unit. Kit £13.12.0 nett.; built £19.8.6 nett.

## MAINLINE AMPLIFIER KITS

RCA/SGS designed main amplifier kits. Input sensitivity 500-700mV for full output into 8Ω.

Power	Kit price including components	Suitable unreg. power supply kit
12W	168/- nett	92/-
25W	190/- nett	N/A
40W	210/- nett	115/1
70W	252/- nett	138/10

## 30 WATT BAILEY AMPLIFIER KIT

Sensitivity 1.2V for full output into 8Ω. Transistors and PCBs for one channel £7.5.6. Transistors and PCBs for two channels £14.11.0. Capacitors and resistors (metal oxide) 40/- per channel. Complete unregulated power supply kit £4.15.0.

## ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 3/9 ea. 1W: 6.8V to 82V 9/- ea. 1.5W: 4.7V to 75V 12/- ea. Clip to increase 1.5W rating to 3 watts (type 266F) 9d.

## CARBON TRACK POTENTIOMETERS, long spindles.

Double wiper ensures minimum noise level. Single gang linear 200Ω to 2.2MΩ 2/6  
Single gang log 4.7KΩ to 2.2MΩ 2/6  
Dual gang linear 4.7KΩ to 2.2MΩ 8/6  
Dual gang log 4.7KΩ to 2.2MΩ 8/6  
Log/antilog 10K, 47K, 1MΩ only 8/6  
Dual antilog 10K only 8/6  
Any type with 1A D.P. mains switch, extra 2/3. Please note: only decades of 10, 22 and 47 are available within ranges quoted.

## CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting 1/- each.

## COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

## POSTAGE AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

## THE NEW ELECTROVALUE CATALOGUE

48 pages—thousands of items—packed with information, generously illustrated with product pictures and technical diagrams—2/- post free. Add 4/- if sent overseas by air mail.

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	120W	5%	82Ω - 300KΩ	E12	18d	16d	15d
C	1W	5%	4.7Ω - 330KΩ	E24	2.5d	2d	1.75d
C	1W	10%	4.7Ω - 10MΩ	E12	2.5d	2d	1.75d
C	1W	5%	4.7Ω - 10MΩ	E24	3d	2.5d	2.25d
C	1W	10%	4.7Ω - 10MΩ	E12	6d	5d	4.5d
MO	1W	2%	10Ω - 1MΩ	E24	9d	8d	7d
WW	1W	10%	0.22Ω - 3.9Ω	E12	1/6d all quantities		
WW	3W	5%	12Ω - 10KΩ	E12	1/6d all quantities		
WW	7W	5%	12Ω - 10KΩ	E12	1/6d all quantities		

CODES: C carbon film, high stability, low noise. MO metal oxide ElectroSil T15 ultra low noise. WW wire wound Plessey.

VALUES: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for same ohmic value and power rating. NOT mixed values. (Ignore fractions of 1d on total resistor order.)

## INTEGRATED CIRCUIT AMPLIFIERS

SINCLAIR IC10 complete with instruction book giving amplifier circuit details and range of applications. 59/6 nett. Components pack for stereo inc. mains transformer, controls, etc. £4.15.0 nett.

PLESSEY SL403A. Only 42/6 each nett. 3W into 7.5Ω for 18V supply. Application data 2/- free with two or more.

## WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W 4/9 each

## SLIDER SWITCHES D.P.D.T.

3/- each

## NEON INDICATOR LAMPS all 200/250V

Square bezel, red only 3/9  
Round chrome bezel, red, amber, clear 4/9 each  
Toggle switches, 250V a.c. 15A. Chrome dolly and chrome milled nut S.P.S.T. 3/9; S.P.D.T. 4/6; D.P.D.T. 5/9; S.P.D.T. centre off 5/-

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC (70 points) only 20/-. Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC (208 points) only 50/-. Full range stocked.

## MULLARD POLYESTER C280 series

250V 20%: 0.01, 0.022, 0.033, 0.047, 8d ea.; 0.068, 0.1, 9d ea.; 0.15, 11d; 0.22, 1/-; 10%, 0.33, 1/5; 0.47, 1/8; 0.68, 2/3; 1μF, 2/9; 1.5μF, 4/2; 2.2μF, 4/9.

## MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 1/3 each  
Values (μF/V): 0.64/64, 1/40, 1.6/25, 2.5/16, 2.5/64, 4/10, 4/40, 5/64, 6.4/64, 6.4/25, 8/4, 8/40, 10/2.5, 10/16, 10/64, 12.5/25, 16/40, 20/16, 20/16, 20/64, 25/64, 25/25, 32/4, 32/10, 32/40, 32/64, 40/16, 40/2.5, 50/6.4, 50/25, 50/40, 64/4, 64/10, 80/2.5, 80/16, 80/25, 100/6.4, 125/4, 125/10, 125/16, 160/2.5, 200/6.4, 200/10, 250/4, 320/2.5, 320/6.4, 400/4, 500/2.5.

## LARGE CAPACITORS

High ripple current types: 1000/25 5/6; 1000/50 8/2; 1000/100 16/3; 2000/25 7/4; 2000/50 11/4; 2000/100 28/9; 2500/64 15/5; 2500/70 19/8; 5000/25 12/8; 5000/50 21/11; 5000/100 55/3; 10000/15 17/-; 10000/25 24/6; 10000/50 44/-; 10000/70 61/-.

## MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 1/9; 100/25 1/9; 100/50 2/6; 250/25 2/6; 330/25 2/6; 250/50 3/9; 500/25 3/9; 500/50 4/6; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-.

## SMALL ELECTROLYTICS


Axial leads: 4.7/10, 4.7/25, 5/50, 1/- ea. 10/10, 10/25, 10/50, 33/10, 50/10, 1/- ea. 25/25, 25/50, 47/25, 100/10, 220/10, 1/3 ea.

## ENAMELLED COPPER WIRE even No. SWG.

only: 2 oz. reels: 16-22 SWG 4/3; 24-30 SWG 5/-; 32, 34 SWG, 8/6; 36, 38 SWG, 8/3. 4 oz. reels: 16-22 SWG only 7/6.
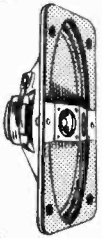
# ELECTROVALUE

Dept. PE12, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY  
Hours: 9-5.30; Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3). Telex 264475



**E.M.I. LOUDSPEAKERS**  
**MODEL 450** 13½" x 8" elliptical with twin tweeters. 8 ohm impedance. 10 watts. Brand New, guaranteed. Lind-Air Price 79/6 P. & P. 4/6.  
**MODEL 150** 13½" x 8" elliptical. 3 and 15 ohm impedance. 10 watts. Lind-Air Price 59/6 P. & P. 4/6.  
**TEAK FINISH SPEAKER CABINETS**  
 Size 16" x 10" x 9". Ideal or above units 49/6

## HI-TONE RECORDING TAPE

**BRITISH MADE TOP QUALITY**

J1001 3"	L.P. PVC 225ft.	5/6	P & P 1/2
J1002 3"	T.P. Poly 600ft.	10/6	P & P 1/2
J1003 5"	L.P. PVC 900ft.	10/-	P & P 1/8
J1004 5"	D.P. Poly 1200ft.	15/-	P & P 1/8
J1005 6½"	L.P. PVC 1200ft.	12/6	P & P 2/6
J1007 7"	S.P. PVC 1200ft.	12/6	P & P 2/6
J1008 7"	L.P. PVC 1800ft.	17/6	P & P 2/6
J1009 7"	D.P. Poly 2400ft.	25/-	P & P 2/6
J1010 7"	T.P. Poly 3600ft.	50/-	P & P 2/6
C60 Cassette (Library cased)		8/6	12 P 1/-
C90 Cassette (Library cased)		13/-	P & P 1/-
C120 Cassette (Library cased)		18/-	P & P 1/-




**DE-LUXE STEREO HEADPHONES**  
 With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug.  
**59/6 P. & P. 3/6.**

## SOLDERING GUN



Comfortable grip with trigger control. "U" shaped 3½" bit to minimise wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use 230-250 volts. 85 watt element 49/6 P. & P. 3/6.

## C1001 MULTI-TESTER

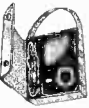

Overload protection. 20,000 opv. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-60K, 0-6 Meg ohm. Decibels -20 to +22dB.

Size of meter 4½ x 3½ x 1in. Complete with case. 85/- P. & P. 3/6

## FIRST TIME EVER! SOLID STATE RADIO HEADPHONES



\* STEREO EFFECT RADIO  
 \* POWERFUL TRANSISTOR RADIO BUILT INTO HEADPHONE WITH TUNING AND VOLUME CONTROLS  
 \* TWIN TELESCOPIC AERIAL RODS  
 \* TWIN MAGNETIC SPEAKERS—ONE IN EACH EARPIECE

Listen to all your favourite radio programmes anywhere and anytime. Lightweight and comfortable to wear. Covers full medium waveband, supersensitive tuning control and variable volume control. Ideal for outdoors and indoors. ONLY £10.19.6. P. & P. 4/6.

## 600 WATT LIGHT DIMMER SWITCH

Same size as standard wall switch and will dim incandescent lighting from full on to off. Heavy plastic box with control knob. LIND-AIR PRICE £41.0. P. & P. 3/6.




## 62D.MULTI-TESTER

20,000 p.p.v. DC voltage 5-25-50-250-500-2.5 K (20,000 ohms per volt). AC voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5 mA, 0-250 mA. Resistance: 0-6K, 0-6 Mg (300 ohm and 30K at centre scale). Capacitance: 10f. to .001 mfd. .001 uf to .1 uf. Decibels: -20 to +22dB. Size 4½ x 3½ x 1in. 71/- P. & P. 3/6.




## S-DEC BREADBOARD

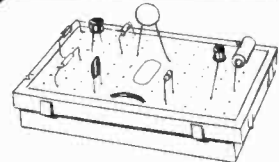

*British Made*  
 Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. 29/8. P. & P. 2/6.  
 4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £5.17.6. P. & P. 8/6.  
 T-DeC KIT £2.10.0. P. & P. 3/6.

## SINCLAIR PROJECT 60

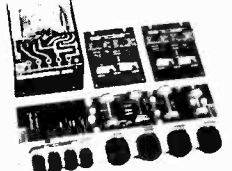

An attractive alternative for the enthusiast at prepared to assemble these excellent modules to make a stereo assembly. Z.30 24 watt Power Amplifier 89/6 (2 required). Stereo Sixty Control/Pre-amplifier £9.19.6 P.2.5 Power Supply Unit £4.19.6. SINCLAIR PROJECT 60 Package deal price 19 GNS. P. & P. 12/8. Project 60 is supplied complete with instruction manual and templates for plinth mounting.

## SINCLAIR IC-10 INTEGRATED CIRCUIT

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONLY 59/6 P. & P. 1/6. SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v. at 0.5 amp. 16/6 P. & P. 2/6.

## "HI-TEN" LOUDSPEAKER

British made full-range 10" unit handles up to 10W. Ceramic magnet. Frequency response, 40Hz-10KHz; imp., 15Ω; flux density, 10,000 lines. 49/6. P. & P. 4/6.



# NEW from Mullard!

## UNILEX Audio Modules

Now you can build your own stereo units as you want them, and entirely in your own home. A good quality stereo amplifier can be built with no electrical knowledge. All solid state—Baxendall tone control circuit—no soldering—terminal block connections throughout.



Everything you need to know about UNILEX SYSTEMS is in the Mullard book "Do it yourself stereo". Superb designs, detailed plans, simple instructions—in non-technical language covering 4 systems in 4 price ranges. Send for your copy now 5/- Post Free.



**UNILEX Audio Modules**

Amplifier Module EP9000	£2.18.0 each
Pre Amplifier Module EP9001	£3. 2.0 "
Power Supply Module EP9002	£4.12.0 "
Control Panel Assembly and Escutcheon Plate	£3. 5.0

**BUILD A STEREO AMPLIFIER FOR ONLY £16.15.0 P. & P. 7/6**

## UNILEX PACKAGE DEALS

Unilex Modules	£16.15.0	Unilex Modules	£16.15.0
Garrard 2025	£11.14.1	Garrard 8P25 Mk II	£15.11.4
Celestion Speakers	£ 5.17.0	B.S.R. C1 Cartridge	£ 3.17.3
	£34. 6.1	Celestion Speakers	£ 5.17.0
LIND-AIR PRICE 28 gns.	P. & P. 20/-	LIND-AIR PRICE 35½ gns.	P. & P. 20/-

## Garrard HI-FI TURNTABLES



2025 T/C with stereo cartridge ...	£8.19.6
3000 with Sonotone	
9TAHCD stereo cartridge.....	£10.19.6
8P25 Mk II .....	£10.19.6
8L65B .....	£15.19.6
Base and cover for above .....	£5.19.6
AP75 .....	£18.10.0
8L72B .....	£24.19.6
8L75B .....	£28.7.0
8L95B .....	£39.9.0
401 .....	£28.10.0
Base and cover for above .....	£5.19.6
P. & P. Decks 12/6. Base & Cover 10/- Deck/ Base/Cover 17/6.	

**SPECIAL OFFERS!**  
 SP25 Mk II with base £14.10.0. P. & P. 15/-.  
 SP25 Mk II with Sonotone 9TAHCD cartridge and base £15.15.0. P. & P. 15/-.  
 Sonotone 9TAHCD cartridge £2.15.0. P. & P. 1/6.

# LIND-AIR AUDIO

# COLOSSAL REDUCTIONS

## OFF AKAI STEREO TAPE RECORDERS

### AKAI 4000 STEREO TAPE RECORDER

SAVE OVER £20




LIST PRICE £124.18.0

LIND AIR PRICE 99 GNS

Carr. & Ins. 35/-  
A complete stereo tape recorder. 2 speeds 3 $\frac{1}{2}$  & 7 $\frac{1}{2}$  i.p.s. and offering full stereo recording and play back facilities.

### AKAI 1710 L STEREO TAPE RECORDER

SAVE OVER £16

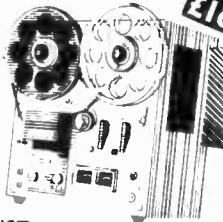

LIST PRICE £89

LIND AIR PRICE 69 GNS

Carr. & Ins. 35/-  
Excellent value for money stereo recorder 3 speeds. Output power 4 watts per channel and every required facility for stereo recording and play back.

### AKAI 4000 D STEREO TAPE DECK

SAVE OVER £17



LIST PRICE £89.19.1

LIND AIR PRICE 69 GNS

Carr. & Ins. 35/-  
The ideal stereo tape deck for use with existing hi-fi stereo systems to give you the full enjoyment of stereo tape recording and play back.

## LA 20 STEREO SYSTEM

SAVE OVER £11



Only takes a few minutes to set up ready for use.

Lind-Air LA20 Amplifier £23.2.0  
Garrard 5-200 Changer with Sonotone Cartridge £11.7.6  
Pair of Lind-Air General Purpose Speakers £19.0.0

Recommended Retail Price £53.9.6

(Also available with Garrard 3000 changer 4 gns. extra)

LIND-AIR PRICE

39 $\frac{1}{2}$  gns.

Carr. & Ins. 35/-

## SAVE £3-15-6

### SCOOP PURCHASE ! !

FAMOUS "SANYO" COLORANO TRANSISTOR PORTABLE RADIO  
Rec. Price £13.15.0



YOURS FOR ONLY 9 $\frac{1}{2}$  gns. P. & P. 4/6

(Four 1P7 Batteries 3/4 extra)  
Elegantly styled quality 10 transistor radio providing wonderful reception of Medium and Long Wave stations plus the new programmes from your local VHF Stations. Grey polystyrene cabinet with silver trim and carrying handle. Size 7" x 4 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ ". Fitted with earphone socket which can also be used for extension speaker. Brand New, in maker's cartons. Complete with earphone, instruction manual and Sanyo Guarantee.

### HI-FI CATALOGUE NOW READY

5/- P. & P. 1/-

Covers all leading makes plus accessories etc. etc. and full details of Lind-Air money saving systems from 39 $\frac{1}{2}$  gns.

Over 100 pages, fully illustrated plus 8 page section of P.A. equipment.

## NEW BRANCH NOW OPEN AT

94-96, Upper Parliament Street, NOTTINGHAM

Telephone: 40403 (STD 0602)

### TELETON SAQ203 TRANSISTOR STEREO AMPLIFIER



Superb quality hi-fi. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble. Attractive oil-walnut cabinet and brushed aluminium front panel.  
List Price £28.7.0

LIND-AIR PRICE

22 Gns.

P. & P. 10/-

### SPECIAL LIND-AIR PURCHASE!

#### FANTASTIC SANSUI 200 AM/FM MULTIPLEX STEREO TUNER AMPLIFIER

Solid state 17 watts music power. Fully tunable over Medium wave and VHF/FM Stereo. Inputs for gram and tape etc. Host of outstanding features—details on request. Rec. Retail Price £89.19.10.

LIND-AIR PRICE £75.12.0 P. & P. 10/-

### BATTERY ELIMINATOR



Enables transistor equipment to be operated from AC mains. 6/9/12v. output selector switch and on/off switch. Case size 4 x 2 $\frac{1}{2}$  x 2 $\frac{1}{2}$ in. complete with mains lead, connecting leads and instructions. 59/6 P. & P. 3/6.

on/off switch. Case size 4 x 2 $\frac{1}{2}$  x 2 $\frac{1}{2}$ in. complete with mains lead, connecting leads and instructions. 59/6 P. & P. 3/6.

### COMPACT 2-WAY INTERCOMS



For table or wall mounting. Smart two tone grey cases size 3 $\frac{1}{2}$  x 1 $\frac{1}{2}$  x 2 $\frac{1}{2}$ in. Complete with lead, staples and 9v battery. 49/6. P. & P. 3/6.

### WHARFEDALE SPEAKER KITS



Complete with all components for building into suitable cabinets.

Unit 3 Kit £11.19.6 each

£21 per pair

Unit 4 Kit £18.0.0 each

28gns. per pair

Unit 5 Kit £23.10.0 each

39gns. per pair

P. & P. 10/- each 15/- pair

18/19, 25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

All Mail Orders and correspondence to Dept. L5/12, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

# WAY OUT— of the component finding maze . . . . .

It may be fun finding your way out of the maze at Hampton Court, but it's not so funny trying to locate and obtain just the components you need for a particular job. In fact, the number of problems and frustrations you can meet is quite a-maze-ing!

There is an easy way out however. Simply get a copy of the Home Radio Catalogue and order whatever you need from the comfort of your easy chair. This famous radio and electronic constructor's "Bible" lists over 8,000 items, more than 1,500 of them illustrated. At only 12/6d (8/6d plus 4/- post & packing) it's a gift—especially as each copy contains 6 vouchers, each worth 1/- when used as directed.

Once you have your Home Radio Catalogue you can make life even easier for yourself by joining our **Credit Account Service**. Then you can order by telephone any time of day or night, Sundays included! No need to bother with postal orders, cheques, registering envelopes every time you order. We send prepaid envelopes and you make only one payment each month. So simple! Write for details or telephone 01-648 8422.

*YOUR FIRST STEP* out of the maze — Post the Coupon with your cheque or P.O. for 12/6d.

The price of 12/6d applies only to catalogues purchased by customers residing in the U.K.


Please write your Name and Address in block capitals

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_



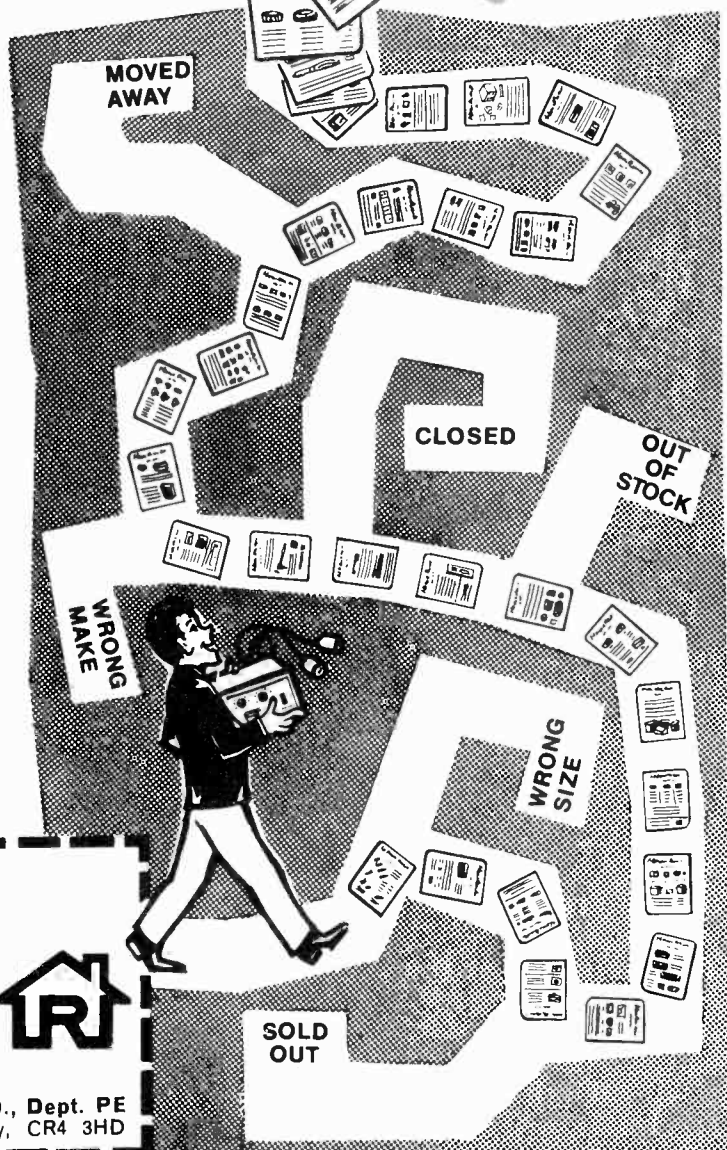HOME RADIO (COMPONENTS) LTD., Dept. PE  
234-240 London Road, Mitcham, Surrey, CR4 3HD



Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD  
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES  
Advertisement Manager D. W. B. TILLEARD

## VIDEO UNLIMITED

**A**FTER years of behind the scenes activity, two different commercial systems for playback of video recordings on standard television receivers have recently been unveiled. The EVR Partnership have launched their video and sound on film system. Rival contenders for this new and important market are Sony of Japan and Phillips of Holland, who are collaborating to produce a video tape system to suit European television standards.

To add yet further complication to the present scene, there is a third system in production, Teldec. This is significantly different from the other two in that it employs a plastic foil disc revolving at 1,500 r.p.m. The promoters are Decca and Telefunken of West Germany.

The outcome of the ensuing battle is anyone's guess at the moment. But it seems unlikely that, in the long run, more than two systems can co-exist on any worthwhile scale. Probably, in the end, a single system will be adopted for world-wide use. The need for interchangeability of video recordings makes this almost imperative.

Major problems in visual recording (as indeed in sound recording), concern scanning and tracking. These problems are mainly of a mechanical nature, and the three companies mentioned above have tackled them in quite different ways. Successfully too, it appears. But the reproducing equipments have yet to be subjected to prolonged use under domestic conditions. Turntables or magnetic heads revolving at the very high speeds demanded suggest some hazards arising.

If one tries to envisage the ultimate in perfection, one is drawn inevitably towards an all electronic concept where complicated high speed mechanisms are unnecessary. And in this connection there is encouraging news from RCA. The Selectavision system under development by this company may prove to be the answer to most—but not all—needs in visual recording and playback in the home. It has the virtue of being almost entirely electronic; and, incidentally, will assuredly gain fame as the first consumer product to employ a laser. But the inability to make home recordings is a handicap of Selectavision, as indeed it is of the other systems mentioned, with the exception of the video-tape system.

The making of visual recordings by private individuals, both "off the air" and with a video camera, is going to be a commonplace and popular activity in due course. Therefore, we may have to become reconciled to two separate approaches, according to the functional requirements. There is a parallel in the audio field, i.e. the record reproducer, and the tape recorder/player.

It looks as though the fate of the home cine projector may be in the balance; but the television receiver will remain even more firmly ensconced in the corner when it has its new associate, the video player.

F.E.B.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

P.E. DIGITAL CLOCK	950
THYRISTOR RELAY UNIT	961
"GEMINI" DUAL PURPOSE STEREO AMPLIFIER	969
OPERATION SEASEARCH	982
ELECTRONIC DICE	997

### SPECIAL SERIES

MAKING THE MOST OF LOGIC IC's—6	990
------------------------------------	-----

### GENERAL FEATURES

THE PROFESSIONAL FINISH	958
INGENUITY UNLIMITED	1002

### BEGINNERS

F.E.T. TIME SWITCH	978
--------------------	-----


### NEWS AND COMMENT

EDITORIAL	949
SPACEWATCH	957
POINTS ARISING	962
MARKET PLACE	965
ELECTRONORAMA	976
NEWS BRIEFS	980

*Our January issue will be published on  
Monday, December 14*



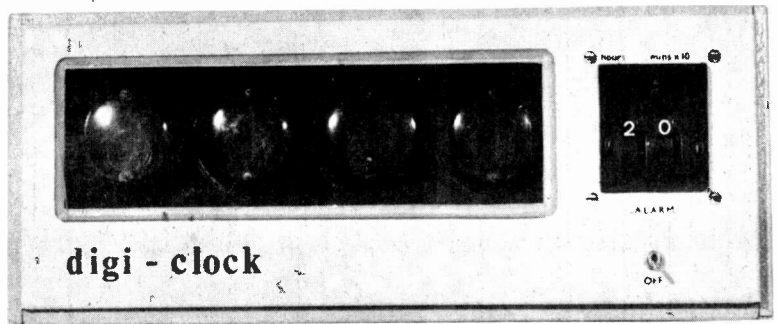- ★ Medium scale integration
- ★ TTL logic i.c.s
- ★ Synchronous alarm
- ★ Reset facility
- ★ Nixie number tubes



THE prices of all integrated circuits have fallen considerably in the last year, and the most dramatic drop of all has been in the price of digital devices. The new low prices have brought even the complex "medium scale integration" TTL circuits into the ever widening sphere of amateur projects. The digital clock described here makes full use of this newly available technology.

The use of both discrete component logic circuitry and RTL i.c.s in attempts to realise a practical clock design proved to have their attendant disadvantages in such a complex system. TTL provides the noise immunity necessary to give reliable time keeping and opens up the possibility of simplifying wiring further by using it in the medium scale integration (MSI) form. (Detailed articles on the functioning of TTL and MSI appear in the current Logic ICs series.)

## DESIGN FEATURES

As can be seen from the photographs in these pages, the clock forms an attractive and useful item of equipment for the home or office.

A Contil MOD-2 case is used to house the design, and the display is provided by four gas-filled number indicating "Nixie" tubes.

An alarm circuit is incorporated, the alarm time being entered by means of thumb-wheel switches which conveniently give an output directly in binary coded decimal form.

The 50Hz from the mains supply is used to drive the clock as this proves to be surprisingly constant in practice, and quite capable of providing the accuracy required. A crystal oscillator could be employed, but it would require extra divider stages, and probably temperature control to gain a significant increase in accuracy.

The circuit employs a total of twenty dual-in-line i.c. packages, fourteen MSI/TTL types, four SSI/TTL types, and two integrated transistor arrays used in the analogue circuitry. Only three discrete transistors and a few diodes are used apart from the i.c.s in the counting and timing circuits.

The logic circuitry is built entirely on two "Dualine" i.c. cards, providing a neat layout and a considerable simplification of the wiring up compared with the perforated s.r.b.p. boards commonly used for such projects. These i.c. cards have provision for either nine or fifteen d.i.l. 14/16 pin packages with ground and

$V_{CC}$  rails provided to each package position. Each i.c. pin is provided with a two hole copper pad for wiring up, and blank holes are available for the use of terminal pins.

Either a single sided 0.1in 22-way edge connector or a 44-way double-sided edge connector is provided on each board, although in this design, to save the considerable expense of sockets, solder terminations are made to these edge contacts.

The circuit boards are mounted flat against the chassis, spaced from it by about  $\frac{1}{4}$ in. The chassis is earthed to act as a ground plane and also to provide screening from the power supply components mounted above.

The power requirements are +5V at up to 1 amp, well regulated and filtered for the i.c.s, and 180V to power the "Nixie" tubes.

A novel voltage regulator circuit, employing fold-back current limiting, and built with an integrated transistor array is used to supply the 5V required by the logic circuitry. A simple Zener diode/emitter follower combination provides the 180V supply for the "Nixies" and decimal point indicator neon. A switch is provided to allow the clock to be run at two fast speeds for initial time setting.

## SYSTEM OPERATION

A block diagram of the clock circuit is given in Fig. 1. The low voltage power supply provides 10V to the low voltage regulator which also uses the 200V supply for biasing. The 5V output from this regulator is used to power all the logic i.c.s, and is decoupled on each board by both tantalum electrolytics and small r.f. capacitors.

The transformer which provides the 200V supply to the "Nixie" regulator also gives a 6.3V 50Hz output which is squared and used as the timing waveform for the clock. This 50Hz is frequency divided by a factor of 3,000 by a series string of four MSI counter i.c.s to provide the one pulse per minute rate required by the clock counters.

These minute pulses are further divided by ten in a decade counter package, the four outputs of which being decoded to ten line decimal and used to drive the 0 to 9 minutes "Nixie". The pulses from the  $\div 10$  package occur once every ten minutes and are used to drive the  $\div 6$  tens-of-minutes counter. The outputs from this are also decoded (three lines to six lines) to drive the tens-of-minutes display.



# FOR AN ALL-ELECTRONIC DIGITAL CLOCK

# DIGI-CLOCK

By R. W. Coles


The pulses from the  $\div 6$  package occur once every hour and are used to drive a  $\div 12$  counter which provides the binary coded decimal inputs to the hours and tens-of-hours display decoder/drivers. Note here that the twelve hour clock system was used for this design to make the clock acceptable for domestic use.

The binary coded decimal outputs of the tens-of-minutes and hours counters are also fed to the alarm circuit, where the digital code is constantly compared with a similar (but negated) binary pattern from the

alarm-time switches. When the alarm time and the display time are exactly equal, the comparator registers this equality, and sets a bistable latch which in turn initiates the alarm sounder.

The oscillator for the alarm sounder can best be described as a "tristable, astable multivibrator" which oscillates alternately at two different audio frequencies producing a rapidly varying bleep tone. When the alarm circuit is active this tone is gated to a speaker to provide an output which is difficult to ignore.

The alarm circuit may be reset by means of a

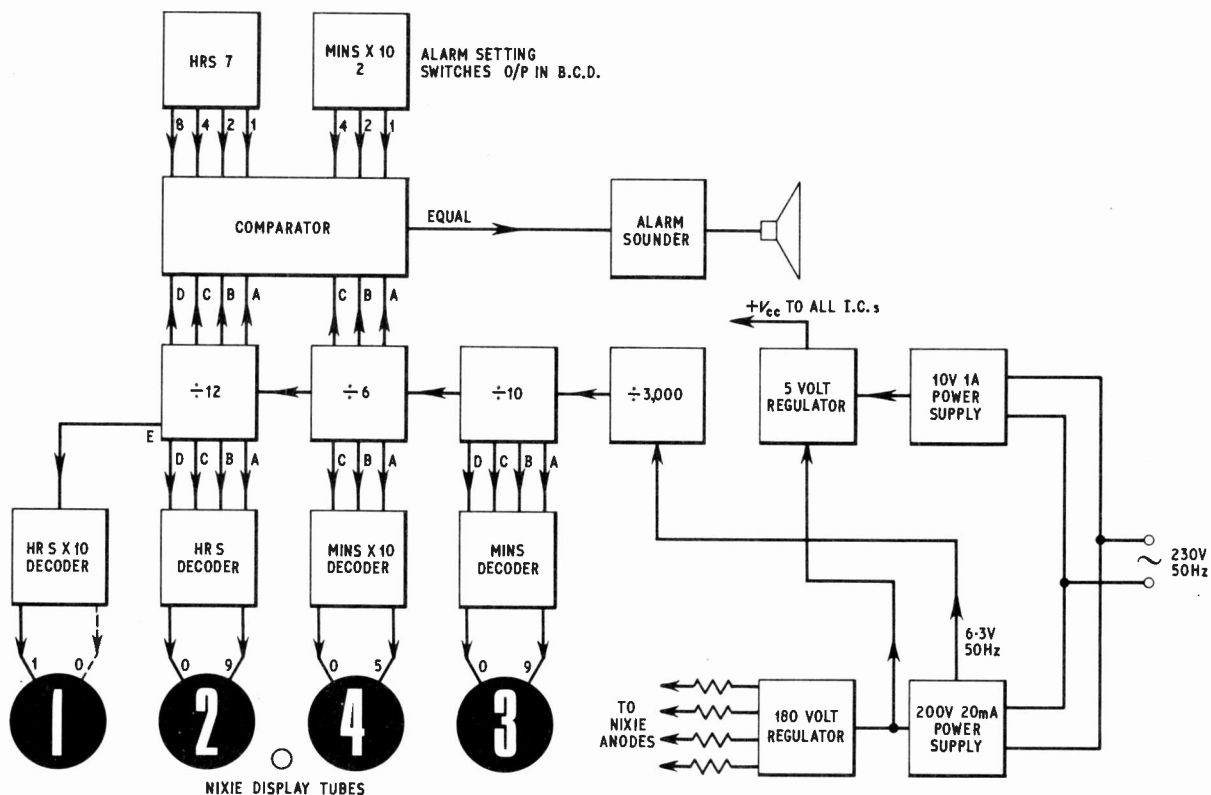

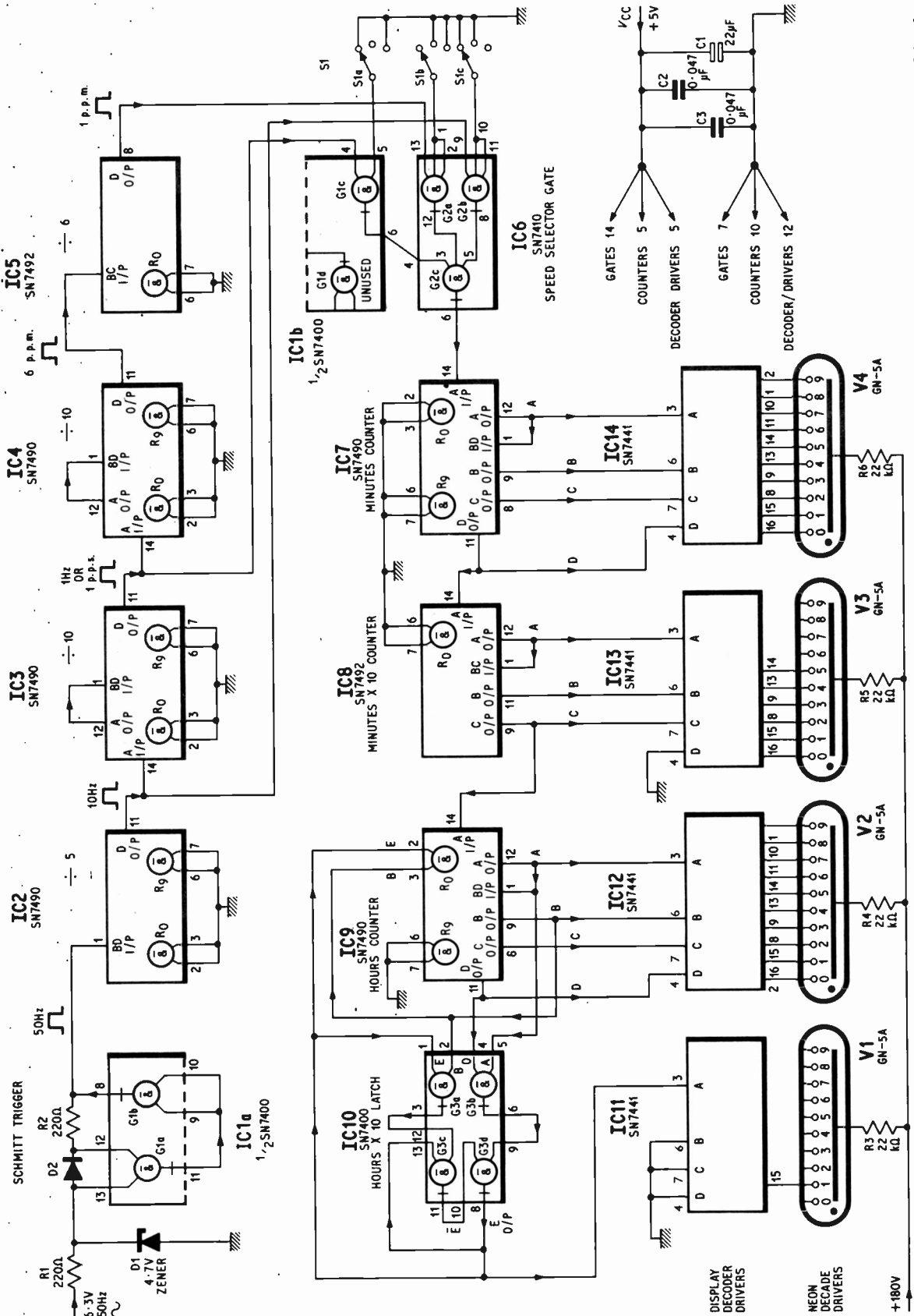


Fig. 2. Circuit diagram of the main clock board only incorporating the dividers, counters and decoder/drivers. All pin connections of the i.c.s which are used in the clock circuit are labelled and numbered. The decoupling capacitors and power supply connections and power supply connections are shown on the right

miniature toggle switch on the front panel, which will also deactivate this circuit altogether when required.

Now that we have a general grasp of the clock operation we can pass on to considering each section in detail, beginning this month with the main clock board. The other sections will follow later together with the appropriate diagrams and components lists.

### MAIN CLOCK CIRCUIT BOARD

All the logic i.c.s for the main clock counting section are mounted on a Dualin-line i.c. printed circuit card type DL110/44. This particular board has positions for fifteen digital integrated logic (DIL) i.c.s; only fourteen are used in this application.

The board also has copper strips for connecting wires and +V<sub>cc</sub> and "ground" runs. At one end is a double-sided 44-way edge connection which is used to carry all the inputs and outputs required.

From the simplified circuit diagram in Fig. 2, it can be seen that the gates are shown individually; the MSI circuits incorporating several flip-flops are given

in block form, to emphasise the treatment of these devices as complete building blocks. The internal logic and pin connections of these devices are given separately in Fig. 3, along with the gate package diagrams.

The SN7490N counter contains four flip-flops grouped to form a divide-by-five counter (BCD), and a separate divide-by-two stage (A). These counters may be used separately or in series to form a decade counter, only one external link wire being required in this mode.

This device also contains two gated reset lines, one of which sets all the flip-flops to the zero state (R<sub>0</sub>), and the other setting the flip-flops to the 1001 condition (R<sub>9</sub>). The reset facility is only used in the hours counter of this clock, so all other reset inputs are grounded to de-activate them.

The SN7492N counter also contains four flip-flops, but in this device they are grouped to form a divide-by-six and divide-by-two stage, which may be used independently or in series to form a divide-by-twelve counter.

One important reservation should be noted here: the BCD stage may be used as a divide-by-six stage in the divider, but its outputs do not follow the binary code in this mode. Where this is necessary, as in the "tens-of-minutes" counter, a divide-by-six stage is formed by cascading the two internal counters, and using the C flip-flop as an output. The binary outputs to be decoded are taken from the ABC outputs in this case.

The SN7441AN decoder/driver package is used, as the name implies, to decode the binary outputs from the clock counters and convert to decimal outputs suitable for driving a high voltage "Nixie" tube. These outputs are taken from the "free" collectors of ten transistors with high collector-breakdown voltage characteristics, provided in the device. The decoding is carried out by an internal gating array, and to provide the same logic and drive capability using small scale integrated (SSI) circuits it would be necessary to use at least five DIL gate packages, and ten discrete transistors, so the advantages offered by the 7441 are obvious.


### DETAILED CIRCUIT OPERATION

The 6.3V r.m.s. 50Hz sine wave input from the power supply, needs to be converted into a square d.c. pulse train before it can be used to drive the divider chain IC2 to IC5.

Zener diode D1 is used to achieve this. D1 is reverse biased until the sine wave input reaches 4.7V positive with respect to ground. At this point it breaks down and limits the positive excursion to this voltage level, in effect giving a square top to the waveform. As the sine wave input swings negative, the same diode conducts in the forward direction, limiting the negative excursion to -600mV.

The d.c. pulses formed in this manner are square topped, but their rise and fall times are much too slow to be used to drive TTL gates directly, as there is a danger of parasitic oscillations during the transition through the gate's active, or threshold, region.

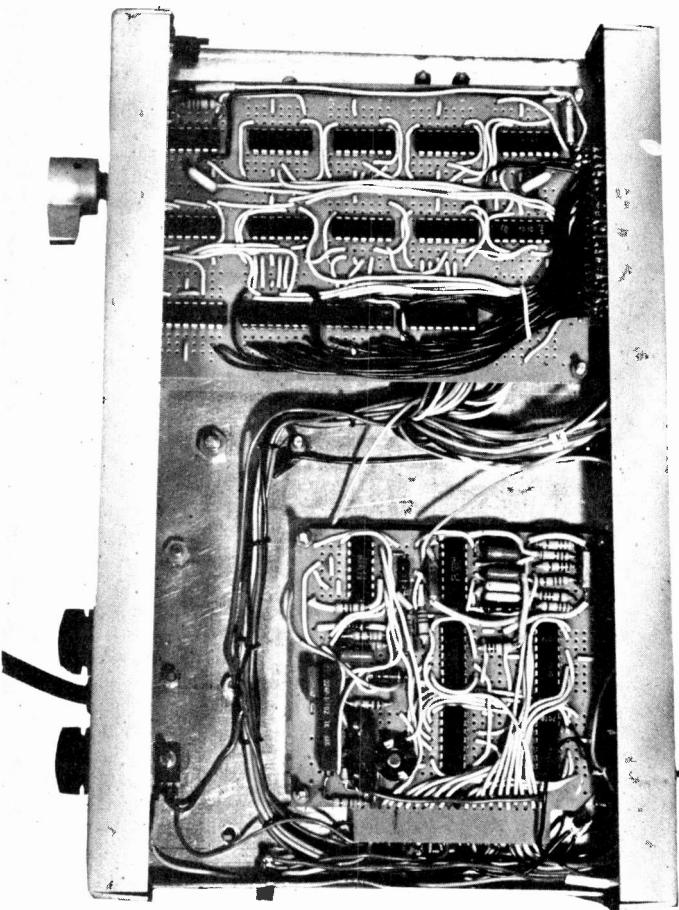This oscillation, which would cause false triggering in the following counters, is avoided by using a Schmitt trigger with positive feedback to speed up the transition. In this circuit two gates from a 7400 package are used to form the Schmitt with d.c. positive feedback via a resistor R2.



Underside view of the clock chassis showing the main Clock Board 'A' at the top and the Alarm Board 'B' at the bottom

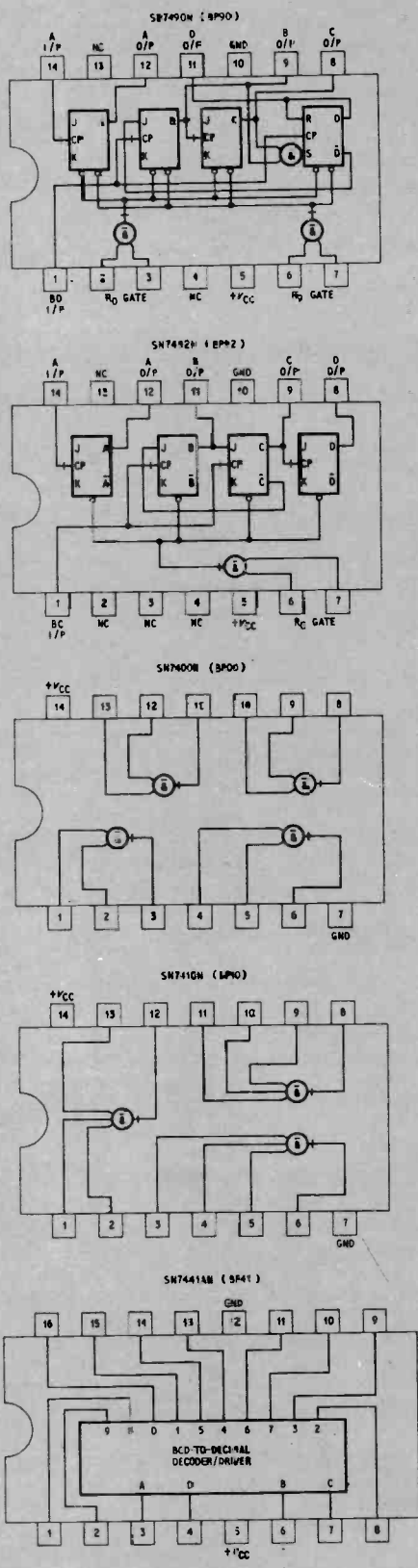


Fig. 3. Arrangement of logic in each i.c. package type with pin connections

The silicon diode D2 is necessary when triggering this kind of circuit from low impedance sources, as in this case. The output produced is a d.c. square wave with very fast positive and negative edges, ideally suited to form the input to the divider flip-flops.

### DIVIDERS

The first divider stage, IC2 is a 7490 used in the divide-by-five mode, giving an output pulse train at 10Hz. The wiring of this stage is very simple, the BD input and the D output being the only connections necessary apart from grounding the resets and wiring up the power lines.

The second divider stage, IC3, is also a 7490, being used this time in the divide-by-ten mode, and giving an output of 1Hz. In this case the A input and the D output are used, and an external link from the A output to the BD input is necessary.

The next two stages divide by sixty to produce minute pulses to drive the clock counter proper. These are arranged so that if necessary they could be decoded in the same fashion as the hours and minutes counters to provide a two-digit "seconds" display.

This type of display was not considered necessary in the prototype, but if the clock is to be used to time, for example, sports events, some constructors may consider the extra expense worthwhile. Of course, if this course is followed, an extra pair of 7441 packages will be required, and there is only room for one of these on the board as it stands.

### TIME CORRECTION

The pulses supplied by IC5 are ready to operate the counting circuits for each display tube. IC6 is a triple 3-input gate package used with one of the spare gates in IC1 to form a speed selector gate. It is used when setting the clock to the correct time initially, and is controlled by S1.

The three gates G1c, G2a and G2b each have one of their inputs connected to one of three timebase speeds, 10Hz, 1Hz, and the normal speed 1 pulse per minute. A three-pole, three-way switch is used to control the other input or inputs in such a way that only one gate is enabled with a "1" input, the others having "0" connected, so that their particular input pulses are not allowed through.

The three gates have active level low outputs (due to the inversion inherent in the NAND gate), and may therefore be fed to a fourth gate, G2c, which is used as a NOR, giving a single output to drive the counters. The control switch is connected as in the diagram; an open circuit represents a 1 input, and a ground connection for a "0".

In retrospect it may be a very good idea to wire the three "1" tags to  $V_{CC}$  through a 1 kilohm resistor, rather than use an open circuit which could lead to noise pick-up. No trouble has been experienced in the prototype from this source, but the fastidious will no doubt wish to incorporate this simple modification, to be absolutely sure.

Some readers may have realised that a one-pole three-way switch could be used to replace the gate/switch system used here. Although this simplification seems worthwhile on a circuit diagram, in practice it would necessitate taking the signal path off the board in a long loop to the switch and back, a distance of well over the maximum of ten inches recommended for single wire driving with TTL circuits.

When the switch is set to the fast position, a complete 12 hour cycle is completed in 72 seconds, making it



easy to set the clock to the correct hour, and when set to the slow position a minute is clocked up every second, facilitating the final setting. In the normal position of course, the clock operates at the speed of real time.

### MINUTES COUNTERS

The 7490 and 7492 packages which form the "minutes" and "tens-of-minutes" counters operate in exactly the same fashion as they did in the divider stages considered previously, except that here the outputs are fed to the 7441 decoder/drivers, to operate the display.

The 7492 is wired in a slightly different way from its division counterpart to facilitate decoding as explained earlier. Only three inputs to the "tens-of-minutes" decoder are needed to provide the necessary six decimal outputs, and the D input from each 7441 is taken to ground to simulate a "0" level.

### HOURS COUNTER

A consideration of the display sequence for the "hours" Nixies reveals that in the 12 hour clock system, no simple count/decode system is possible. Of the several solutions considered, the one used here satisfies the conditions best, and gives a count sequence sufficiently close to the binary coded decimal inputs required by the alarm comparator, that it could be easily altered merely by adding a "1" in an adder circuit.

The "truth-table" for the hours counter and display is given in Fig. 4. A quick glance at the "Hours" column shows that zero hours never occurs (unlike in the 24 hour system) and the start of the sequence can best be taken as 1 o'clock.

Considering the hours Nixie first, it is seen that it starts with a 1, counts normally to 9, then goes to 0 and counts up to 2 before being reset to the start condition.

An immediate snag occurs here because the binary count equivalent to 1 o'clock is 0000, which, when

decoded, drives the 0 output of the 7441. Similarly, at 10 o'clock the equivalent binary count is 1001, which will activate the 9 output of the 7441. Fortunately this problem is easily overcome by wiring the 1 cathode of the Nixie to the 0 output of the 7441, and so on, so that the 0 Nixie cathode ends up wired to the 9 decoder output.

After 10 o'clock the 7490 recycles normally to 0000, and again displays a 1, just as we require. Two counts later it is necessary for the 7490 to be reset forcibly back to one again, as the 12 hour sequence has been completed. This is performed by detecting the "13 o'clock" state with the  $R_0$  reset gate, and immediately resetting. The 7490 thus carries out one full count and one partial count in each 12 hour period.

### TENS OF HOURS COUNTER

Having grasped the principles of the hours sequence, the tens of hours display should follow quite easily, as another glance at the table shows that this Nixie must go to a 1 at 10 o'clock and be reset to 0 at 1 o'clock.

The tens-of-hours count is registered on a simple set/reset bistable formed from two cross-coupled gates in the usual fashion. This latch is set by a further gate at 10 o'clock, when it is opened by the hours count of 1001. The latch is reset by the fourth gate at "13 o'clock", and of course this reset is coincidental with the 7490 reset, and is detected in the same way.

The truth table shows that the logic required to set the latch is  $\bar{A}$  AND  $\bar{D}$ ; the logic to reset both it and the 7490 is  $\bar{B}$  AND  $\bar{E}$ . It follows that 2-input NAND gates are ideal for the job, and in the case of the reset condition the  $\bar{B}$  AND  $\bar{E}$  state is detected simultaneously by gate G3a and the  $R_0$  gate of the 7490.

Decoding of the tens-of-hours latch is not required to drive the Nixie, because when the E output is up a 1 is displayed, and when the E output is up, a 0 is displayed. For the sake of simplicity however, a 7441 is still used to drive this display, using only the A input.

HOUR	TEN HOURS NIXIE	HOURS NIXIE	HOURS COUNT O/P'S				TENS HOURS LATCH O/P
			A	B	C	D	E
1 O'CLOCK	0	1	0	0	0	0	0
2 "	0	2	1	0	0	0	0
3 "	0	3	0	1	0	0	0
4 "	0	4	1	1	0	0	0
5 "	0	5	0	0	0	0	0
6 "	0	6	1	0	1	0	0
7 "	0	7	0	1	1	0	0
8 "	0	8	1	1	1	0	0
9 "	0	9	0	0	1	0	0
10 "	1	0	1	0	0	1	1
11 "	1	1	0	0	0	0	1
12 "	1	2	1	0	0	0	1
			0	1	0	0	1

THIS TRANSIENT STATE DETECTED & COUNTER & LATCH RESET  
7490 RECYCLES  
TENS HOURS LATCH SET

Fig. 4. Truth table for the hours counter and display

## COMPONENTS . . .

### MAIN CLOCK BOARD

#### Resistors

R1, R2 220  $\Omega$  2%  $\frac{1}{2}$ W metal oxide (2 off)

#### Capacitors

C1 22 $\mu$ F 15V tantalum bead type or elect.  
C2, C3 0.047 $\mu$ F 250V met. foil.

#### Diodes

D1 4.7V 400mW Zener (e.g. 1S2047 Texas)  
D2 1N914 silicon diode for switching


#### Integrated Circuits

IC1, 10 SN7400N (BP00)  
quad 2-input gates (2 off)  
IC2, 3, 4, 7, 9 SN7490N (BP90)  
decade counters (5 off)  
IC5, 8 SN7492N (BP91)  
÷ 12 counters (2 off)  
IC6 SN7410N (BP10)  
triple 3-input gate  
IC11, 12, 13, 14 SN7441AN (BP41)  
BCD to decimal decoder/  
drivers (4 off)

Further notes on purchasing i.c.s given in the article "Making the Most of Logic ICs"
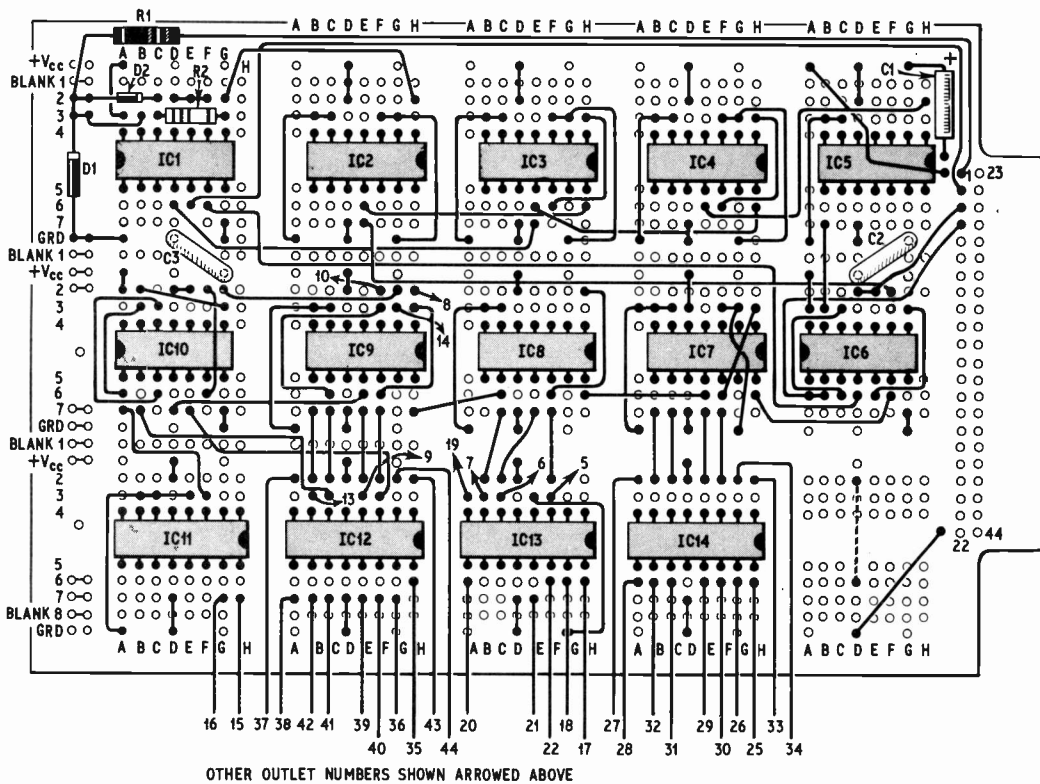
#### Miscellaneous

Dual in line type DLI10/44 printed circuit card  
(Shirehall Electronics Ltd., Station Yard,  
Borough Green, Sevenoaks, Kent.)



OTHER OUTLET NUMBERS SHOWN ARROWED ABOVE

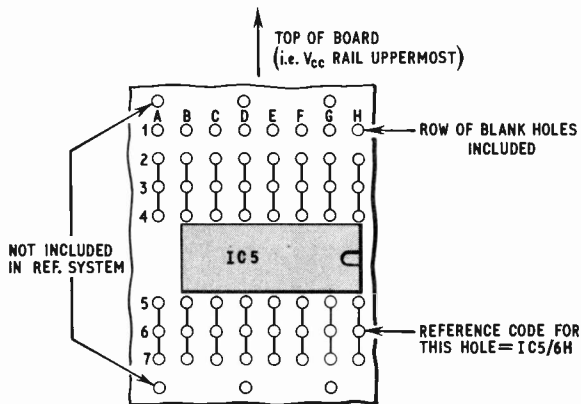


Fig. 6. Interconnection coding of the main clock board outlets for each i.c. position matrix

If desired a couple of discrete transistors could be used instead, driven directly from the complementary E outputs.

This completes the description of the main clock board circuit, except perhaps to mention that the  $+V_{cc}$  rail is decoupled near its edge contact with a  $22\mu\text{F}$  tantalum electrolytic capacitor. Two  $0.047\mu\text{F}$  capacitors, spaced out on the board, effectively remove h.f. noise on this supply line generated by the logic itself. This is normal practice and should be adopted in any i.c. logic application.

### WIRING UP

The board wiring is shown in Fig. 5, and should be carried out with thin flexible p.v.c. covered connecting wire. Interconnections must be kept as short as

Fig. 5. Wiring of the main clock Dualline printed circuit Board 'A' with edge connector outlet coding on lead-out wires. Plain side terminations on top to outlets 1 to 22, copper side terminations to outlets 23 to 44. The ground rail is connected to outlet 11, the  $+V_{cc}$  rail to outlet 12

possible commensurate with a neat layout. Where adjacent printed copper pads are connected (such as on IC6) this may be simply carried out on the underside of the board with a solder run, to save the tedium of producing tiny wire links. Discrete components C1, C2, C3, D1, D2, R1 and R2 are best added after the rest of the wiring.


Wiring to the edge connector is facilitated by using the coding adopted in Figs. 5 and 6.

The wiring is carried out on the top of the board, even that which connects to the upper edge connector pads. The outputs are numbered with their respective circuit references for interconnection at a later stage.

It is recommended that at each stage of wiring up, a circuit is drawn up from the wiring actually carried out so that this may be checked against the circuit given. A mistake could be very difficult to rectify when the faulty link is buried under several other layers of wire.

It is also a good idea to connect the board to a 5V supply and, using a 6.3V heater transformer as a timing input source, check the counter operation before adding the edge connector wiring. Nixie outputs can be checked by connecting a voltmeter across them to ground, and using a 4.7 kilohm resistor to  $V_{cc}$  to simulate a load.

To be continued

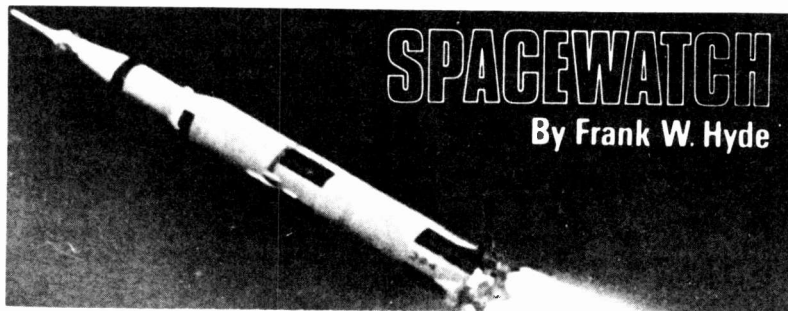

## ITALY TO LAUNCH U.S. SATELLITE

Later this month or early December Italy will have the distinction of being the first foreign country to launch a U.S. satellite. It is part of an agreement signed by the two powers in which the United States will be able to use the Italian built San Marco launch platform.

The use of this facility on the equator will enable smaller launch vehicles to be used. For example, the four stage *Scout* rocket can be used instead of the larger vehicles which would be required at Cape Kennedy to attain equatorial orbit.

The San Marco platform is situated in the Indian Ocean off the coast of Kenya and it is expected that under the present programme NASA will require three launches by the Aerospace Research Centre of the Daglia Studi di Roma (Rome University). These will consist of two astronomy satellites and one scientific satellite.

The Italian launch team have been trained by NASA at the Wallops station in Virginia. They have already made a successful launch from Wallops in 1964, and in 1967 they made an equally successful launch from the San Marco platform.

The actual contract provides for the supply of the satellites and the launch vehicles by NASA. The Italian team will assemble, check out, and launch the satellite. They will also provide some tracking and data acquisition facilities.

The first satellite will be an astronomy unit designated *SAS-A*. The *SAS* spacecraft are unique in their construction and the first one will weigh approximately 320lb. Each group of instruments is in a separate section and connected to a common section containing the power supply, communications, attitude control and any other equipment required to support the mission.

Facilities are available for the mission to take a quick look at the entire sky over a period of six weeks, and then a detailed study of the sky will be made during the remainder of the expected life of the satellite which is about six months.

The *SAS-A* will have about 140lb of the available instrument space for instrumentation dealing

with X-ray sources and the resulting catalogue will be used as a basis for detailed observations from another craft in 1971.

The *SAS-B* spacecraft scheduled for launch in late 1971 will carry a sky mapping system. It will also look for gamma ray sources, an important mission in view of the discovery of high energy gamma rays in the "milky-way".

## SPACE PHENOMENA STUDY

The scientific satellite (*SSS*), which will be called *SSS-A* will undertake the investigation of space phenomena. This will include the study of aurora magnetic storms, the acceleration of charged particles in the inner magnetosphere and electrical currents circulating in the magnetosphere. It will have an apogee of 16,000 miles, an ideal orbit for such investigations.

The *SSS* satellite has had a difficult beginning because it was partly damaged by fire in December 1969. This was due to an outbreak of fire at the Goddard Space Flight Centre, Green Belt. This damage was rectified and the satellite brought back to operational condition and will be ready for launch in the Spring of 1971.

## MOON WATER DIVINING

When the *Apollo 14* is launched on January 31, 1971, the astronauts on landing on the moon will carry out a unique experiment to discover if water does in fact exist on the moon. Some scientists believe that concentrations of ice may be buried near the lunar surface.

Astronaut Edgar Mitchell will be responsible for the equipment and will use a technique similar to that used for oil prospecting. Small explosions are set off on the surface and the shock waves from these explosions penetrate deep into the ground and are bounced back to be detected on the surface. The character, or signature of the trace that is recorded provides a clue to the presence of oil or water bearing layers.

The experiment will be carried out in one of the five hour excursions on the surface in the Fra Mauro region. The astronaut will lay out some 310 feet of cable which will be connected

to three vibration detecting geophones. He will then walk beside the cable and at intervals of fifteen feet fire a device called a "thumper". The "thumper" consists of a short tube with a firing mechanism at the upper end and hollow cylinder at the lower end. In the cylinder there is a plate which will be pressed down on the surface of the moon.

During his walk Mitchell will fire 21 cartridges in this manner, each with the force of a pistol shot and the resulting seismic waves and reverberations will be picked up by the geophones.

This experiment is a bonus arising from the need to get information on the shape of the moon and the structure and thickness of the moon's outer crust.

In addition to the shot firing Mitchell will set up and arm a mortar containing four grenades. The grenades will be set off by radio, from the earth, after the spacecraft has left the moon on its return journey. The grenades will be fired away from the area in which the astronauts have collected samples and will be timed to explode at 500, 1,000, 3,000 and 5,000 feet from their launch point. The vibrations will be detected by the geophones and automatically radioed back to earth for analysis.

The characteristics of these signals which will come from as deep as 1,500 feet will be examined to see whether the moon is layered like the earth or whether it is homogeneous. The results of this analysis will give some idea of the early history of the moon.

The questions that may be answered are whether the moon had a hot molten core like the earth from the beginning of its existence, or whether it cooled off quickly after its formation.

## NEW COLOUR FILM

To study the solar eclipse of March 1970 a new colour film called XRC (Extended Response Colour) was tried out. It has a near human eye response and has a brightness range greater than 10,000 to 1.

The film has a very marked fidelity of colour response and was developed for the use of astronauts on the moon landings where the extreme range of response is very necessary.

The results obtained from the last eclipse by astronomers confirmed a prediction made by Professor C. W. Allen of the London University Observatories. In the Monthly Notices of 1946 he suggested that the corona would become redder as the distance from the photosphere increased. This effect could be quite clearly seen in the recorded photographs using this new film.

Amateur astronomers who have an interest in astrophotography might well try this film for the need for monochromatic filters does not arise.

# THE PROFESSIONAL FINISH

BY M.K.TITMAN B.Sc. (ENG.)

**T**HE second and final part of this article describing technique and working methods used in obtaining a professional finish on home constructed equipment

**W**HEN plastics coated materials are being formed, the plastics should be protected by cardboard stuck on with sticky tape and all markings should be on the internal face. When working in wood the important considerations, especially where furniture finishes are required, are that the edges be perfectly square and straight and the measurements precise, such that square joints and thin, mating gaps result. Work is enhanced by using the saw attachment to an electric drill, since with this attachment a square edge can be achieved and a perfectly straight edge can be formed.

It is important that tools be of the correct type and particularly that saws and chisels be sharp. A material suitable for furniture finishes is Contiboard which is chipboard, veneered on both sides by the same wood sheet; this is particularly important for such things as lids of stereo cabinets. Contiboard has a disadvantage in that some edges are not veneered, but veneering is very simple using Contistrip, which is affixed, using a hot iron, directly onto the sawn edges and results in a very professional and robust finish.

## POLISHING

When working with wood it should also be remembered that apart from good joints and edges, the final polish is of utmost importance. After the wood has been sanded, it must be filled with a grain filler and stained prior to the application of the final polish. A simple and very effective final polish which gives a professional finish in a gloss or matt, can be obtained by the use of polyurethane varnish, which can be applied by French polishing or more easily by direct brush application. When polyurethane varnish is used, the surface should be smoothed with fine glass paper prior to the next coat and the final coat should be burnished with a burnishing powder to give the best results.

## WORKING PERSPEX

Working with Perspex is difficult, especially to maintain a non-scratched finish, but Perspex is usually supplied with a stiff paper covering on both sides and this should be retained, and all the marking carried out on the stiff paper. Care must be taken in cutting Perspex since it is very brittle and sawing should not be carried out unless the sheet is adequately supported very close to the cutting point; this results in continual movement of the sheet in the vice in order to maintain the supported edges near to the cutting point. After cutting to the desired contours, a file can be used to smooth the edges, but again it should be remembered

that the edges must be adequately supported during this operation. Once cut to shape the sheet can be polished using Perspex polish to remove any file marks from the edges or scratches from the surface.

## SURFACE FINISH

The overall surface finish is important since this enhances the artistic impression. Although p.v.c. and fabric covers are sometimes employed, paint is widely used, with grey hammer or black crackle being the past standard for non-commercial units. Manufacturers, however, are drifting increasingly away from this uniformity of colour and using such striking finishes as dark green with red panels or blue hammer with white. Suffice it to say that instrument casing manufacturers never illustrate their catalogues with grey hammer but use bright contrasting colours.

Good paint finishes are not always easy to obtain and care should be taken particularly when plain colours with gloss finish have been chosen. Aerosols should be used as far as possible and the surface cleaned and scratches removed before application of the undercoat. All painting should be carried out in a dust free atmosphere and left undisturbed until completely dry. Hammer and crackle paints should be used for cases with poor surface qualities since they disguise surface irregularities.

## FRONT PANELS

Front panel finishes are usually the weak point of home constructed equipment. Often they are poorly labelled or not labelled at all, whilst the control knobs and indicators are ill matched and of ancient design.

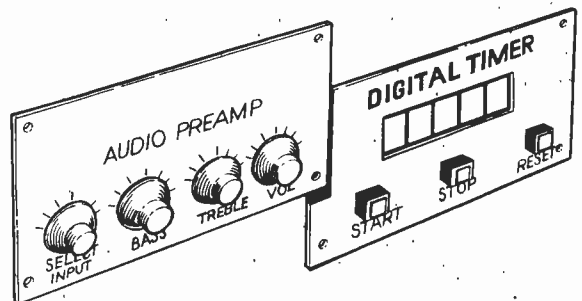


Fig. 5. Typical front panel layouts

Whilst it is true that such units function adequately, the overall impression is poor and such equipment is often difficult to use.

Now contrary to popular opinion, a professional finish can be achieved with little additional effort or cost with the use of modern techniques. The essential feature of the panel layout is that the information should be clear and the controls accessible. Knobs should match each other and either contrast or match the panel colour, whilst their size should enable simple operation and allow room for labelling. Lettering should be clear and in proportion, whilst the general layout should be symmetrical to aid clarity and please the eye. Fig. 5 illustrates some typical layouts that can be utilised to achieve a neat professional appearance.

### FRONT PANEL FINISH

An audio pre-amplifier is shown in Fig. 5; the knobs can be chosen to contrast the panel, whilst lettering is black on white. Adhesive lettering has been used to designate the functions of the controls and sprayed with clear lacquer to reduce wear. The panel finish can be either spray paint or matt finish aluminium—achieved by rubbing the surface with emery until a satin appearance is obtained. This finish is cheap and very effective, but suffers from the disadvantage that constant use of the controls inevitably wears away the lacquer and adhesive lettering. Therefore it is best employed on equipment where the controls are not used excessively.

Where equipment is required for constant use as in the case of test instruments, receivers and transmitters, then the front panel can be covered by a sheet of clear Perspex. This enables constant use without wear and gives an added depth to the gloss finish.

A second style of finish is illustrated by the digital timer shown in Fig. 5. Here the front panel proper is completely covered by a Perspex escutcheon on which the colouring and lettering is on the reverse face. Apart from freedom from wear this system has the considerable advantage that it conceals the metal front panel which can thus be used as a chassis with components mounted directly, using countersunk screws. Other advantages are that illuminated legends can be used and mechanical pointers, level indicators, numerical indicator tubes, etc. are protected by the Perspex. The reverse marking system is used extensively by manufacturers, particularly since it can be mass produced at low cost when the markings are produced by a photographic dye-etching system.

### REVERSE LETTERING

Since the home constructor cannot utilise the photographic-dye system, let us examine alternative methods of producing the same basic finish. Fig. 6 illustrates the steps by which the amateur can fabricate a Perspex escutcheon of this type. First, the basic metal front panel is measured and a sketch produced of the required holes and markings; such a panel is shown in Fig. 6a. The Perspex escutcheon is then cut to size and the holes and cut-outs drilled and formed, as illustrated in Fig. 6b. Fig. 6c shows the marking of the Perspex sheet with legends and designs on the reverse face. Since the lettering is reversed, normal adhesive letters cannot be used, but special purpose reverse lettering is available.

For the photographic enthusiast the reverse lettering can be achieved by photographing white lettering on a black background and glueing the resultant negative to the reverse side of the Perspex sheet. However, since the outline of the negative is always visible, this method is not entirely satisfactory.


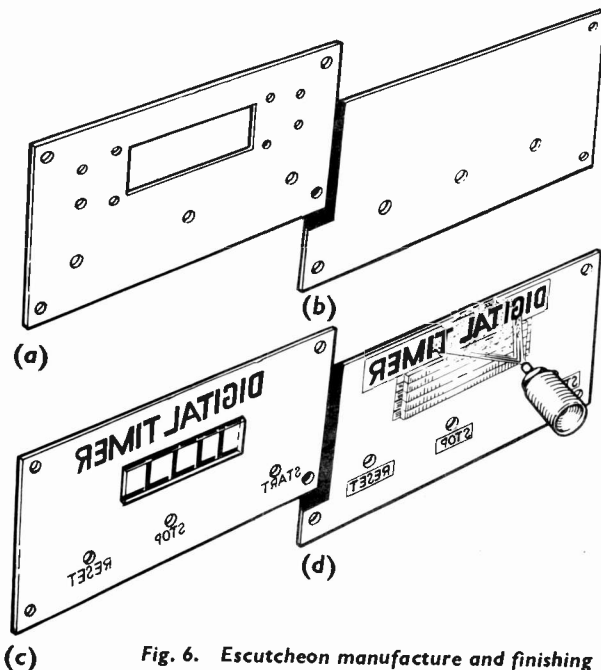


Fig. 6. Escutcheon manufacture and finishing

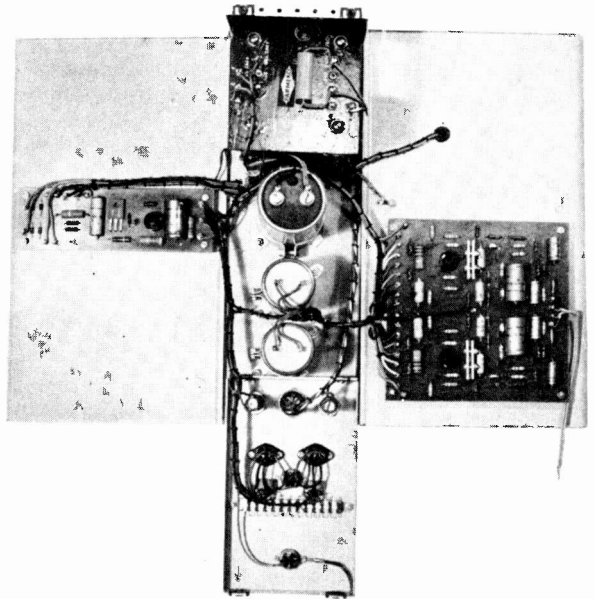

The professional touch to internal layout and finish of the P.E. Gemini stereo amplifier



Generally, the reverse lettering can be achieved with the use of stencils and quick drying paint. This has the advantage of choice of colour but requires the purchase of a set of stencils. Some practise is advisable to achieve spacing and uniformity when reverse stencilling.

When the marking is complete the clear areas for legends and windows are masked and the reverse face sprayed with aerosol paint of the desired colour, as illustrated in Fig. 6d. The result is an escutcheon of professional appearance which will wear well and give a smart and finished appearance to the equipment.

### INTERNAL FINISH

Whilst the internal layout and finish contribute nothing to the artistic effect of an equipment, it is worth mentioning that neat layouts with proper cableforms are also a feature of professional equipment. A neat layout contributes to the ease of servicing and reliability, in addition to the more obvious mass production requirements. Layout naturally is governed by technical considerations and it is preferable that the layout follows the circuit diagram as far as is practicable. Thus the input should be physically removed from the output to aid servicing and eliminate unwanted feedback.

Printed circuits should always be adequately supported to prevent damage and never used to support heavy components. After soldering, the boards should be cleaned and defluxed using carbon tetrachloride and a stiff brush, which results in a better appearance and often highlights bad joints, thus contributing to reliability.

Cableforming aids servicing and repair and allows a neater component density to be achieved. Three methods of cableforming are illustrated in Fig. 7. The most common method, using binding cord, is illustrated in Fig. 7a. This system is time-consuming and presents difficulties should subsequent cable modifications be required, but is very cheap. Fig. 7b illustrates the use of rubber sleeves and, like the binding cord system, gives a neat finish. However, a special tool is used to expand the sleeving and consequently it is not practical for the home constructor.

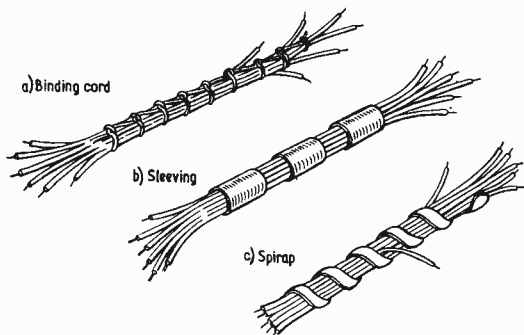


Fig. 7. Methods of cableforming

The third system shown in Fig. 7c illustrates the use of a spirally cut plastics tube available for cableforming. This product, known as Spirap, is easy to use and can be removed and re-used if subsequent modifications are necessary. The disadvantage is that it is more expensive than binding cord and is not always easy to procure.




The professional finish illustrated by the Decca Compact 3
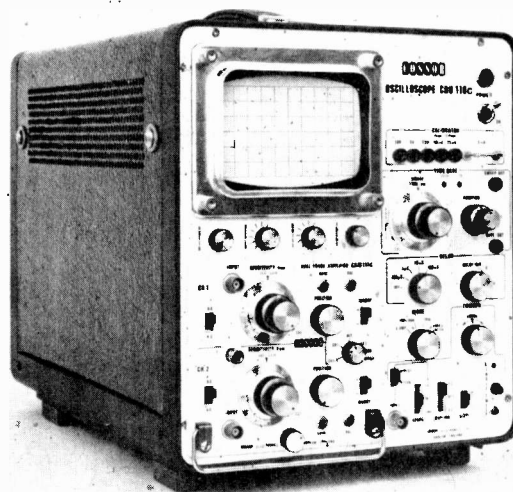
### CONCLUSION

A neat attractive finish is not vital to the performance of electronic equipment and consequently should never deter the home constructor from attempting to build any unit. However, for self satisfaction a good finish is desirable and using the techniques discussed, even a tobacco tin and secondhand components can be fabricated in such a way as to give an acceptable finish.

The first essential is that a professional finish becomes a prime objective of the constructor. Subsequently, using the principles of symmetry, colour and labelling a professional artistic finish will result. ★



Front panel finish of a professional oscilloscope

# THYRISTOR RELAY UNIT

By A.G. Wood

**T**HIS article describes a sensitive electronic relay, the action of which is governed by a sensor or transducer. The applications are dependent on the type of input control devices used; these can include tape recorder auto-stops, burglar or fire alarms, moisture detectors and pump controls.

External control switching is done by means of a relay which is controlled by a thyristor. The circuit is simple and makes use of an electronic method of latching, a facility which is of special use where the unit is to be used as a burglar alarm.

## CIRCUIT ACTION

The circuit of the relay unit is given in Fig. 1. With S1 closed an alternating voltage is induced in the secondary winding of the filament transformer T1. This is rectified by D1 and C1 to provide d.c. for the other circuit elements.

With no conducting path provided between SK1 and SK2 no bias current will pass to TR1 so that this transistor is off. For the thyristor SCR1 to turn on a gate current must be provided and since this current would be the collector output from TR1 the relay is not energised.

With the circuit completed between SK1 and SK2 bias current flows by way of VR1 and R2 to switch on TR1 which in turn makes the thyristor conduct and the relay to operate.


## SENSITIVITY CONTROL

Since the devices that can be connected across the sensor input socket are manifold and will vary in impedance in individual cases, a potentiometer, VR1, is included to provide variable voltage inputs. It therefore acts as a sensitivity control.

Typical devices that can be used with success here are cadmium sulphide photocells, high resistance thermistors, reed switches or Veroboard if this is intended as a moisture sensor.
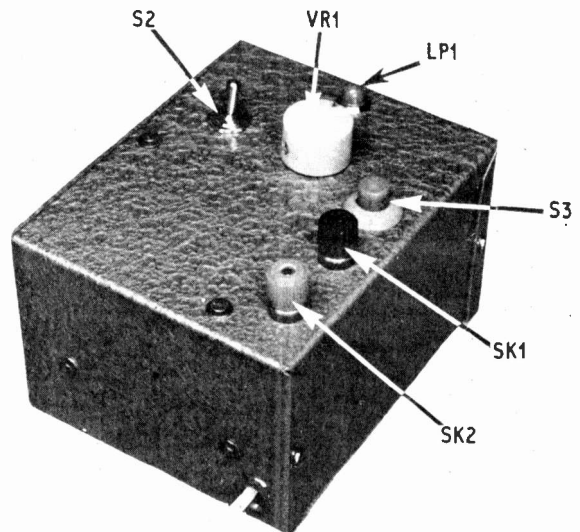
## LATCH FACILITY

With S2 in the "latch" position, the thyristor SCR1 will maintain its conducting state if the sensor input circuit is broken as with the gate current reduced to



Layout of control items on prototype unit

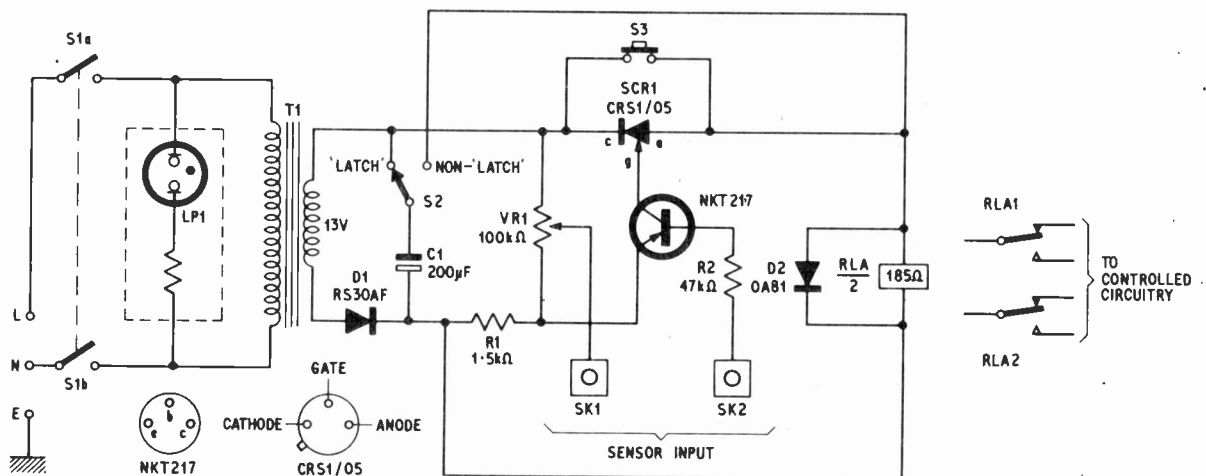


Fig. 1. Circuit diagram of thyristor relay unit

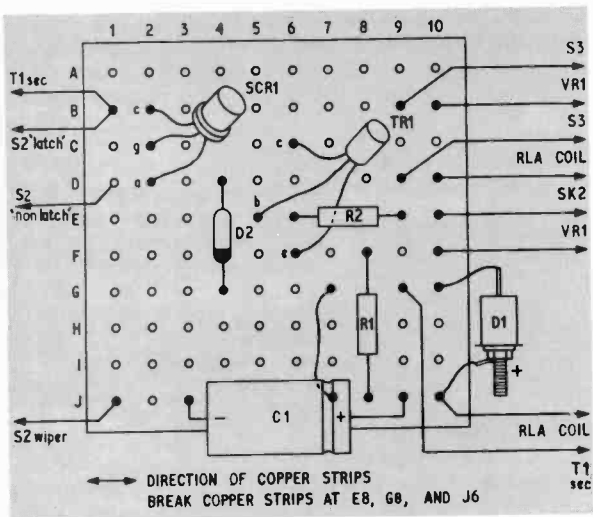


Fig. 2. Component and wiring layout of Veroboard sub-assembly

zero, a thyristor will still remain switched on until the anode current is reduced below its minimum holding value.

In order to release the relay, S3 must be depressed; this short circuits the thyristor so that the relay is completely de-energised when the switch is released.

When S2 is in the "non-latch" position, C1 is removed from the power supply and the voltage applied

## COMPONENTS . . .

### Resistors

- R1 1.5k $\Omega$
- R2 47k $\Omega$
- $\frac{1}{2}$ W 10% carbon

### Capacitors

- C1 200 $\mu$ F elect. 25V

### Transistors

- TRI NKT217

### Thyristor

- SCR1 CRS1/05

### Diodes

- D1 RS30AF
- D2 OA81

### Switches

- S1 Double-pole mains on/off
- S2 Single-pole changeover
- S3 Single-pole push-to-make

### Potentiometer

- VR1 100k $\Omega$  carbon linear

### Relay

- RLA 9V 185 $\Omega$  2-pole changeover  
Contact rating 2A, Omron Type MH2

### Transformer

- T1 Primary 0-230/240V  
secondary 13V, 0.5A

### Miscellaneous

- LPI—Mains neon, diecast box 3in  $\times$  4in  $\times$  5in
- SK1-SK2 Insulated terminals (2 off)

to the circuit consists of halfwave pulses at the mains frequency.

In this case, the thyristor cannot remain in the conducting state; it must be turned on again when the next pulse arrives if the relay is to remain closed. This means that the sensor input circuit conducting the relay will operate and will de-energise when this circuit is open.

In the "non-latch" position, C1 is connected across the relay to prevent chatter.

## CONSTRUCTION

The majority of the circuit components can be mounted on a piece of Veroboard 1 $\frac{1}{2}$ in  $\times$  1 $\frac{1}{2}$ in. A layout for the board assembly is given in Fig. 2.

As component placement and wiring is not critical the smaller items could equally well be soldered to tag strips.

The prototype housing was a 3in  $\times$  4in  $\times$  5in aluminium box. This easily accommodated the filament transformer T1.

Since the Veroboard sub-assembly occupies such a small volume of the box, it is a simple matter to arrange the other components around this, so that interwiring is most conveniently managed. Some idea of this can be gained from the photograph.

Make sure to check the wiring thoroughly before plugging in the mains, as a short circuit could destroy the rectifier diode or thyristor. ★

# POINTS ARISING

## TRIAC LAMP REGULATOR (October 1970)

The meter in the components list should read 0 to 1mA f.s.d.

## "TRANSTAB" POWER SUPPLY UNIT (November 1970)

Page 890, under side heading D.C. AMPLIFIER fifth line should read "... by means of range switch S2b and S2c with VR1."

Fig. 1, Numbering on switch S2b and S2c should be reversed to comply with numbering on S2a, i.e. for S2b, R5 to position 4, R6 to position 3, R7 to position 2, R8 to position 1. For S2c, R9 to position 4, R10 to position 3, R11 to position 2, R12 to position 1.

## INSTALLING AUDIO (Supplement) (November 1970)

Page 15, Fig. 9 caption should read "Phono plug and socket".

## BE SURE OF YOUR COPY

We have many requests for back issues and cannot always guarantee supplies; to make sure of your copies why not take out a yearly subscription.

Subscription including postage for one year to any part of the world £2 5s. 0d. (£2.25).

Subscriptions dept., IPC Magazines Ltd., Carlton House, 68 Great Queen St., London WC2B 5DD.

# Merry Christmas from Antex

## Complete Soldering Kit 55/-

This contains the iron fitted with a  $\frac{3}{16}$ " bit, interchangeable spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ", resin cored solder; felt cleaning pad; stand for soldering iron, and a booklet 'How to solder.' From Electrical and Radio Shops or send cash to Antex.



Model CN 240/2  
15 watts - 240 volts 34/-  
Fitted with nickel plated bit  $\frac{3}{32}$ "  
and in handy transparent pack. From  
Electrical and Radio Shops or send  
cash to Antex.

PRECISION MINIATURE SOLDERING IRONS  
Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296. Giro No. 2581000.

Please send me the Soldering Kit  
 I enclose cheque/P.O./cash value

NAME .....  
ADDRESS .....

# VARIABLE VOLTAGE TRANSFORMERS

## LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cadmium Sulphide PhotoCell, Relay, Transistor and Circuit, etc., 6-12 volt D.C. op. price 25/- plus 2/6 P. & P. ORP 12 including circuit. 12/6 each, Post Paid.



**A.C. MAINS MODEL.** Incorporates Mains Transformer, Rectifier and special relay with 2 5 amp mains c/o contacts. Price inc. circuit 47/6 plus 2/6 P. & P.

## LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take 115C bulb. Separate photo cell mounting assembly for ORP. 12 or similar cell. Both units are single hole fixing. Price per pair £2.15.0. P. & P. 3/6.



## RELAYS

New SIEMENS, PLESSEY, etc. miniature relays at COMPETITIVE PRICES

Coil	Working d.c. Volts	Contacts	Price
Ω	6-9	6M	I.B. 12/6
230	6-12	2 c/o	I.B. 12/6
280	6-12	2 c/o	I.B. 14/6
700	16-24	4 c/o	I.B. 15/6
700	12-24	2 c/o	I.B. 12/6
2500	36-60	6M	I.B. 12/6
5800	80-85	4 c/o	I.B. 12/6
9000	40-70	2 c/o	I.B. 10/-

H.D. Heavy Duty. POST PAID  
I.B. = Including Base

## 'AVO' MODEL 48A

Ex-Admiralty in good condition with instructions, leads, plus D.C. Shunts for 120 Amp. and 480 Amp. A.C. Transformer for 60 Amp. and 240 Amp. Multiplier for 3600 volt. Complete outfit in fitted case. £15.0.0. P. & P. 10/-.

## ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2 batteries. Complete set of parts including speaker, etc. together with full instructions and 10 tunes. Have all the pleasure of building this instrument and finish with a functional and instructive gift for any boy or girl. Price £3.0.0. P. & P. 4/6.

## 10 IN 1 PROJECT KIT

10 easy to build Projects including: Radio, Morse Oscillator, LF Oscillator, etc., etc. A Solar Cell is included in this Kit as alternative power for some of the circuits, also a 14 page step by step instruction leaflet. Price £3.17.6 P. & P. 4/6.

## T.M.C PUSH BUTTON KEY SWITCH

Illuminated No. S.525594 Lock 4 c/o Complete with mounting bracket, push knob and lenses (green, amber, red or clear—state colour preference). Price 14/6 each excluding bulb, post paid. Discount for quantities of 200 and over.



## UNISELECTOR SWITCHES

NEW 4 Bank 25 Way 24V d.c. operation. £5.17.6, P. & P. 2/6  
6 Bank 25 Way 24V d.c. £6.10.0, P. & P. 2/6  
8 Bank 25 Way 24V d.c. operation. £7.12.6 plus 4/6 P. & P.



## MINIATURE UNISELECTOR SWITCH

Ex-Equipment 3 banks of 11 positions plus homing bank. 40 ohm coil. 24-36V D.C. Tested. 22/6, plus 2/6 P. & P.

## VENNER ELECTRIC TIME SWITCH

200/250V Ex. GPO tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2 15s, 15A £3 5s, 20A £3 15s. P. & P. 4/6. Also available with solar dial ON dusk, OFF dawn. Price as above.



INPUT 230/240v. A.C. 50/60—  
OUTPUT VARIABLE 0-260v.

**BRAND NEW**  
Keenest prices in the country.  
All Types (and Spares) from  
1/2 to 50 amp. from stock.

**SHROUDED TYPE**  
1 amp, £5. 10. 0. 2.5 amps, £6. 15. 0. 5 amps, £9. 15. 0. 8 amps, £14. 10. 0. 10 amps, £18. 10. 0. 12 amps, £21. 0. 0. 15 amps, £25. 0. 0. 20 amps, £37. 0. 0. 37.5 amps, £72. 0. 0. 50 amps, £92. 0. 0.



**OPEN TYPE (Panel Mounting)** 1/2 amp, £3.18.6.  
1 amp, £5.10.0. 2 1/2 amps, £6.12.6. Carr. extra on open types.

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V. A.C. operation.

**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £5.5.0 plus 5/- P. & P.

**NEW INDUSTRIAL KIT**  
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-800 f.p.s. Price 9 gns. 7/6 P. & P.

**HY-LYGT STROBE**  
This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £10.17.6. P. & P. 7/6.

**7-inch POLISHED REFLECTOR**  
Ideally suited for above Strobe kits, Price 10/6. P. & P. 2/6 or Post Paid with kits.

## 100 WATT POWER RHEOSTATS (NEW)


AVAILABLE IN THE FOLLOWING VALUES:  
1 ohm, 10 a.; 5 ohm, 4.7 a.; 10 ohm, 3 a.;  
25 ohm, 2 a.; 50 ohm, 1.4 a.; 100 ohm, 1 a.;  
250 ohm, .7 a.; 500 ohm, .45 a.; 1 Kohm,  
280 mA.; 1.5 Kohm, 230 mA.; 2.5 Kohm, 2 a.; 5 Kohm, 140 mA. Diameter 3 1/2 in. Shaft length 2 1/2 in., dia. 1/4 in. All at 27/6 each. P. & P. 1/6.  
50 WATT. 1/5/10/25/50/100/250/500/111/1/5/2/5/5 Kohm All at 21/- each. P. & P. 1/6.  
25 WATT. 10/25/50/100/250/500/111/5/2/5 Kohm. All at 14/6 each. P. & P. 1/6.



**VEEDER ROOT, 230V a.c. 50 cycle, 5-figure counter (non-resettable).** 18/6, P. & P. 1/6.



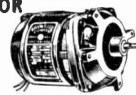**BODINE TYPE N.C.I. GEARED MOTOR**  
(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p., 50 cycle, .38 in. metal core. Timing interval adjustable from a fraction of a second to several minutes by means of external resistor or pot. By adding a 24V Relay many other complex timing Functions are possible. Price: 16/6 incl. circuit. P. & P. 2/6. Suitable relay 10/- post paid.



## SOLID STATE INTERVAL TIMER

24-30V D.C. operation. Stabilised unijunction Timer and S.C.R. (30V 1 amp.), encapsulated in metal case. Timing interval adjustable from a fraction of a second to several minutes by means of external resistor or pot. By adding a 24V Relay many other complex timing Functions are possible. Price: 16/6 incl. circuit. P. & P. 2/6. Suitable relay 10/- post paid.



## MOTOROLA MAC II/6 PLASTIC TRIAC 400 PIV. 8 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price 21/- plus 1/6 P. & P.

## RE-CHARGEABLE BUTTON CELLS

2 1-2V, 250 MA/HR Nickel Cad. Cells, connected to give 2.4V @ 25 milliamp. 10 hour rate, complete with 200/250V A.C. charger. Fully tested and unused. Price 9/6 each plus 1/6 P. & P. or 2 units for £1 post paid.



## INSULATED TERMINALS

Available in red, white, yellow, black, blue and green. New Price 2/- each.



## AUDIO CIRCUIT DESIGN

with  
**SILICON COMPLEMENTARY PAIRS**  
Motorola Publication  
12/6 Postage 1/-

**HOW TO USE INTEGRATED CIRCUIT LOGIC ELEMENTS** by Jack W. Streater. 28/- Postage 1/-.

**THE HI-FI AND TAPE RECORDER HANDBOOK** by Gordon J. King. 40/- Postage 2/6.

**INTRODUCTION TO LOGIC CIRCUIT THEORY** by I. Aleksander. 32/- Postage 1/-.

**TRANSISTOR IGNITION SYSTEMS HANDBOOK** by Brice Ward. 22/6 Postage 1/-.

**TRANSISTOR MANUAL** by General Electric Company. 21/- Postage 1/6.

**BASIC THEORY AND APPLICATION OF TRANSISTORS**, Dept. of the Army Manual. 17/- Postage 1/6.

**SERVICING WITH THE OSCILLOSCOPE** by Gordon J. King. 28/- Postage 1/-.


**TRANSISTOR POCKET BOOK** by R. G. Hibberd. 25/- Postage 1/-.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books  
19-21 PRAED STREET  
LONDON, W.2  
Phone: PADdington 4185  
Closed Saturday 1 p.m.

up to  
**40% OFF**  
Why pay more?

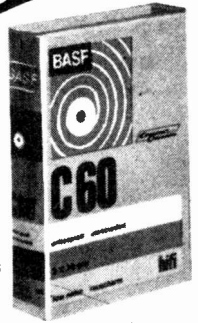Incredible but true! We offer BASF, PHILIPS, SCOTCH tapes and cassettes at prices AT LEAST 5% LOWER THAN ANY OTHER ADVERTISER. This is a genuine 'cut-price' offer.



Send for details NOW!  
**Leda tapes**  
Dept. P.E. 12  
17 Leigh Park Road  
Leigh-on-Sea, Essex

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
Dept. P.E. 57 BRIDGMAN ROAD, LONDON W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN CLOSED SATURDAY  
Personal callers only  
9 LITTLE NEWPORT ST.  
LONDON, W.C.2. Tel. 01-437 0576



# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

## DOUBLE-BEAM OSCILLOSCOPE

Over the last few years a very tight rein on any grants to schools and colleges for purchasing laboratory equipment has been closely scrutinised by educational boards and committees before any purchasing has been given the all clear.

Due to the above conditions it is very difficult to recommend any piece of equipment to schools and colleges unless it will pass the closest scrutiny of cost plus performance appraisal. Available from Z. & I. Aero Services, the C1-16 double beam oscilloscope is value for money at £87, and to be recommended to educational establishments.

This double-beam oscilloscope is a laboratory instrument designed for investigation and measurement of pulsed and periodic waveforms. The timebase is common to both beams and the timebase generator provides triggered and free running sweep.

Both vertical channels are fitted with attenuators which allow signals as large as 100V peak to be fed in. For signals up to 400V peak an external attenuator is used, supplied with the standard equipment. Duration of pulses and time intervals are measured by comparison with preset triggered sweep periods. The accuracy of this is checked with the aid of a quartz crystal calibrator.

A brief technical specification of the C1-16 oscilloscope is: repetition rates of investigated waveforms 50Hz to 10MHz; range of pulse length is 0.35µs to 1sec; range of amplitudes 0.04 to 100V, increasing to 400V with external attenuator.


Characteristics of vertical amplifiers are 0 to 1MHz, amplifier passband at 1dB, and 0 to 5MHz, amplifier passband at 3dB. The sensitivity at medium frequencies at broad passband is 500mm/V. Input impedance is 0.5 megohms ±0.015 megohms shunted by 45pF; with external attenuator 5 megohms shunted by 13pF.

Timebase preset calibrated sweep durations are 0.2, 0.5, 1, 2, 5, 10, 20, 50 and 100 microseconds per centimetre; and 0.2, 0.5, 1, 2, 5, 10,


20, 50 and 100 milliseconds per centimetre. The free running time-base frequency range is 50Hz to 1MHz. Sweep sync voltage and trigger voltage is 0.5V and maximum trigger pulse repetition is 10kHz.

The frequency of the quartz crystal calibrator is 100kHz.

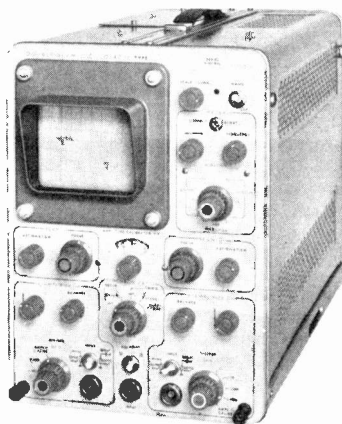Full particulars of the C1-16 oscilloscope is obtainable from Z & I Aero Services Ltd., 44a Westbourne Grove, London, W.2.



C1-16 Oscilloscope from Z. & I. Aero

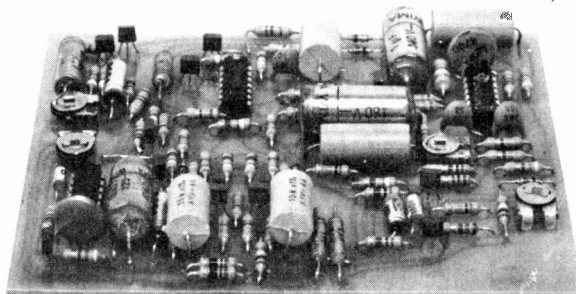

Phase-locked Stereo Decoder Circuit Board Manufactured by Integrex

## STEREO DECODER UNIT

A phase-locked stereo decoder kit is the latest product from Integrex Ltd., P.O. Box 45, Derby, DE1 1TW, to appear on the market.

This unique design avoids the use of inductors and tuned circuits but achieves a high separation.

Based on a phase-locked loop the decoder uses integrated circuits and transistors and is ideally suited for the constructor as it may be "set-up" by using a d.c. voltmeter.

Typical performance figures are: separation 45dB at 1kHz, 40dB at 10kHz; distortion is 0.3 per cent at full modulation. The decoder will accept signals within the range of 130mV r.m.s. to 1.3V r.m.s. A simple change of a resistor will extend the sensitivity to 70mV if required.

In order to match the majority of f.m. tuners a variable gain pre-amplifier is incorporated in the circuit. The decoder requires ±6V at 50mA, or a voltage not less than ±15V (using Zener diodes).

The kit contains 3 i.c.'s, 15 silicon planar transistors, 8 silicon diodes, 62 low noise resistors, 23 capacitors and 4 miniature preset potentiometers, together with a fibreglass board drilled, roller tinned and screen printed with component positions. Input, output, power supply connections, left and right channel outputs are also marked.


The decoder kit costs £8 19s 6d plus 2s 6d postage and packing. Included with the kit is full constructional details. A power supply kit is available at £2 19s plus 3s 6d postage and packing.

## EXTENSION CABLE

A useful product suitable for the workshop is a cable reel, complete with neon indicator, 13A plug and socket with fuse, and spare, available with either 5A or 13A cable, from West Hyde Developments Ltd.

There are two types of reel available: the 5 amp reel with 50ft of cable and a 13 amp reel with 30ft of cable. The price of the extension unit is 99s 6d and is finished in two-tone moulded plastics with a carrying handle and a rewind handle.

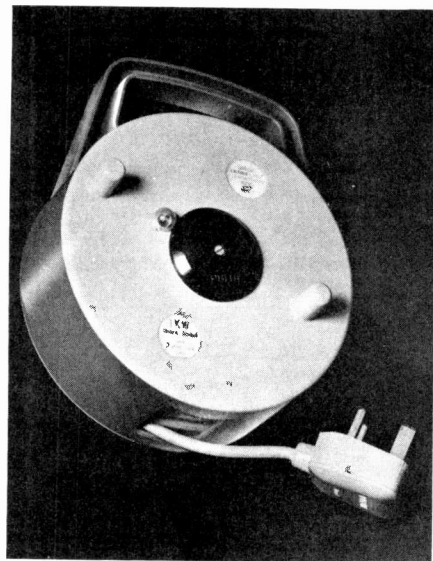Further details are available from West Hyde Developments Ltd., Ryefield Crescent, Northwood Hill, Northwood, Middlesex.



Extension Cable from West Hyde Developments

## LIGHT OPERATED SWITCH

The Transelectric light operated switch has many applications which, it is claimed, are only limited by individuals' own ingenuity.

Triggered by an ordinary light bulb, street lamp, reflected light from bright surfaces or mirrors, infra-red or ultra violet light, it is also claimed to be different from similar devices on the market because it uses a principle they term "wide beam" technique.

Some of the features of the detector unit are: two separate circuit response controls and one light beam sensitivity control; digital counter; and a built-in claxon horn. The unit is powered by batteries, making it portable, or from a special mains unit. The output socket enables a range of accessories to be plugged in, extending the range of applications even further.


In the home the unit can be used as an automatic light switch, porch light switch, intruder and fire alarm, automatic tape control or to switch on the radio, etc.

For shops and offices it can be used as an automatic window advertising display lights switch, counter anti-theft device, customer entrance and exit counter, etc.

For seacraft it is an ideal sentry, protecting gear or monitoring the gangway. With the use of an adapted transmitter and receiver, the owner can be ashore in strange ports and still know the instant a stranger boards his craft. The transmitter and receiver operate on the 27MHz band and no notice is given by the manufacturers that a licence is required to operate the units—perhaps because the operator will be the criminal.




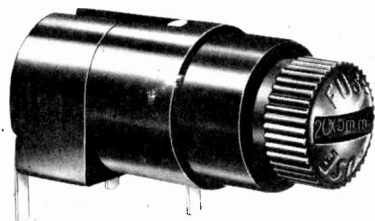**Prowl Alarm produced by Computer Devices**



**Printed Circuit Board Fuseholder marketed by A. F. Bulgin**
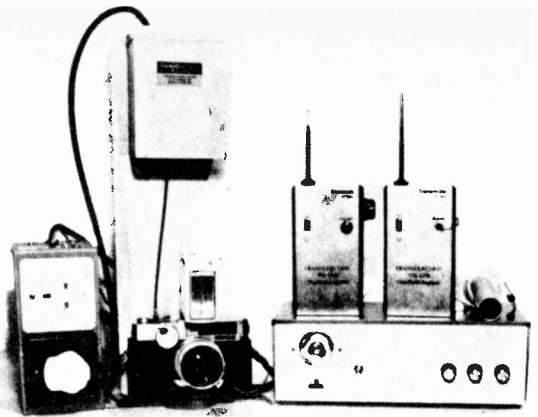
## Transelectric Light Operated Switch and Accessories



Another useful accessory is a camera trigger unit. Full details and price of the Transelectric detector and accessories can be obtained from Transelectric Co. Ltd., 46, Townend Street, Sheffield, S10 1NN.

A more simple and cheap alarm, although less versatile, is the Prowl Alarm from Computer Devices Ltd. This device looks very similar to an ordinary hand torch and is triggered when knocked on its side.

The device is placed on a flat surface, behind doors or windows, inside drawers and cupboards, or a trip cord can be attached to the device and any likely place of entry. Being top heavy it is easily toppled by any intruder and sounds the built-in audible siren. Only a predetermined sequence of switching will silence the alarm.

No price was given but details can be obtained from Computer Devices Ltd., 8, North Street, Guildford, Surrey.

## CIRCUIT BOARD FUSEHOLDERS

The widespread use of printed circuits and more compact units has necessitated the re-design of many components to allow them to be mounted directly on the circuit board. Until recently fuseholders were either mounted on cabinet panels, in a convenient position, or held on circuit boards by wire loops. Now Bulgin's have introduced a new range of fuseholders, type No. F330, designed specially for printed circuit boards.

These holders are moulded from black phenolic with a "D" shaped rear section, the flat part rests on the circuit board to give stability. There are three mounting pins, two common to the rear fuse contact and one for the front contact, arranged in a triangular formation to give a secure fixing against the torque from fuse replacement and renewal. The front of the fuseholder is circular and will protrude through a pre-drilled or punched hole in equipment. The screw-in cap grips the fuse which is withdrawn when the cap is removed.

Addresses of local stockists can be obtained from A. F. Bulgin and Co. Ltd., Bye-Pass Road, Barking, Essex.

## I.C.'s FOR ORGANS

Of particular interest to organ constructors are two MOS Arrays being distributed by WEL Components Ltd.

Designed specifically for electronic organs, type MA70 is a 12  $\sqrt{2}$  divider giving a true semi-tone relationship. Array type MA60 is a six stage binary divider giving six outputs, each 1 octave apart. Thus, the total organ divider functions can be simulated with four MA70 circuits and 12 MA60's.

Designed free of colouration, the organ designer can experiment to find the final colouration system of his own choice. Designers requiring a free phase system could use 30 MA70's.

Further particulars of stockists and cost can be obtained from WEL Components Ltd., 5 Loverock Road, Reading, Berks.

## LITERATURE

During the last few years LST Electronic Components has sold many hundreds of copies of the RCA Hobbies Circuit Manual, reference HM.90. But many customers have complained that they have been unable to obtain the special transistors specified for the many useful and varied circuits described in this book.

After some months of effort, LST have finally managed to publish a short list of direct equivalents and now wish to contact their many customers who have bought this book and inform them that the equivalents chart is available, free of charge.

## NEMATIC CRYSTALS

The mention of nematic crystals and their possible future applications in technology aroused considerable interest when the article on *Conductive Glass* was published in November 1969. The Aldrich Chemical Co. Inc. of Milwaukee, Wisconsin now advise us that a special Liquid Crystal Edition of their journal *Aldrichimica Data* has been issued. It includes an article on the applications of liquid crystals to science.

Copies are available to readers, free of charge, from their British Associates, R. N. Emmanuel Ltd., 264 Water Road, Alperton, Middx.

# LOOK!

**PRACTICAL!**

**VISUAL!**


**EXCITING!**



a new 4-way method of mastering  
**ELECTRONICS**  
by doing — and — seeing . . .

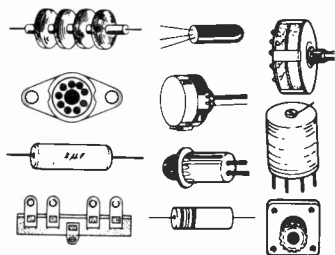
## 1 ▶ OWN and HANDLE a

complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



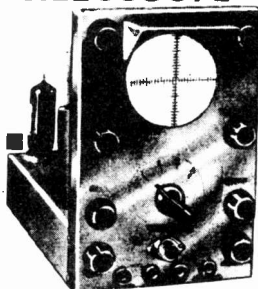
## 2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**



## 3 ▶ READ and DRAW and

**UNDERSTAND**  
**CIRCUIT DIAGRAMS**

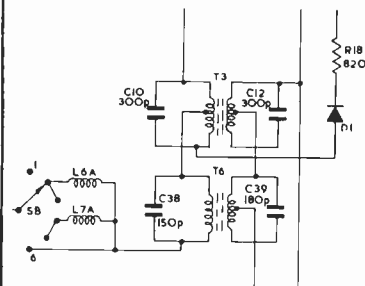

## 4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- |                          |                          |                        |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS      | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS     |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT       | ● D.C. EXPERIMENTS     |
| ● AMPLIFIERS             | ● BASIC RADIO RECEIVER   | ● SIMPLE COUNTER       |
| ● OSCILLATORS            | ● ELECTRONIC SWITCH      | ● TIME DELAY CIRCUIT   |
| ● SIGNAL TRACER          | ● SIMPLE TRANSMITTER     | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.E. 12

# LOW COST ELECTRONIC & SCIENTIFIC EQUIPMENT & COMPONENTS

## MOTORS

### HIGH PRECISION MAINS MOTOR

3000 r.p.m. Made by Croydon Engineering. Panel KA 60 4FB. Suitable for capstan motor. Size 8in long, 4in diameter with 6in diameter flange and 4 fixing holes. These motors are Capacitor Start, Capacitor Run, supplied less Capacitor. Also available 3 Phase. £41.00. each. I.L.S.O. P. & P.

### SYNCHRONOUS MOTORS

200/250V 50Hz self-starting. Model 87 1 r.p.h. 30/... Model 87 1 r.p.h. 30/... Clock Motor 2 r.p.h. 20/... Type MA23 Low Torque Hysteresis Motors, 1/60 r.p.m., 1/20 r.p.m., 1/12 r.p.m., 1 r.p.m., 11 r.p.m. 25/- each. Fitted one-way clutch, 1/12 r.p.m., 1 r.p.m., 1 r.p.m., 1 r.p.m., 30/- each. P. & P. on any of above 5/- each.



### BRAND NEW MOVING COIL DC TEST METERS

Compact and portable. Width 2 1/2in, height 1 1/2in, depth 3in. In black plastic case. Available as follows: 3-0-3V. Prod on Base 0-15V and 0-300V. Dual Range Voltmeter, 0-3V and 0-300V. Dual Range Voltmeter, 0-7.5A. Ammeter. Our Price £11.00 each. P. & P. 5/-.

### BATTERY OPERATED NEW L TRANSISTOR TESTERS

Type TR285 for checking leakage current and gain current of pop transistors. Audio and Meter for calibration purposes. Our Price: £8.10.

### AVOMETERS

These well-known portable test instruments have been overhauled and are offered complete with leads, crocodile clips and prods. Model HR2/HRM 20,000ohm/V d.c., 1,000ohm/V a.c., £16.10. Model 75, £15.10. Model 48A, £12. Model 47A, £12. Model 40, £11. P. & P. on any of above £1. Model 47A or 48A (dependent upon availability) complete with voltage multiplier for 480V and 3,600V. Current Shunts for 120A and 480A. Current Transformer for 20A and 60A. In special wooden box, £15.10. Carriage £1. (N.B. Model 47A and 48A are similar instruments).



AVO Cases, Leather, £1. P. & P. 5/-. Wooden box to take meter, £1. P. & P. 7/6.

### EX-AIRCRAFT

Moving Coil Radiometers in "AS NEW" Condition by Sangano Weston, 24V. Mainly calibrated °C. 2 1/2in 2 1/2in 3in. This precision instrument has many applications. £8. P. & P. 5/-.

### BLOWER MOTORS

"AS NEW", 240V, 16W, 50Hz, 3,000 r.p.m. Shaded pole motor; 2 1/2in dia. cast aluminium fan, £2.10. P. & P. 6/-.

### SELECTOR BOARDS

"X" "Y" Matrix for programming, 20 37, £9.10. P. & P. 7/6. 50 24, £12.10. P. & P. 10/-. Diode Pins to suit, 1/3 each.

### OSCILLOSCOPE TYPE CT 52

A very handy miniature portable instrument for general purpose applications. 2 1/2in diam. tube. Wave form investigation from 10Hz-20MHz. Pulse monitoring duration 50 microseconds to 0.1 microsecond. Time base free running 10Hz-40kHz. Also single sweep facility from 50 microseconds to 3 microseconds. "Y" Amplifier Delay Line Calibration Voltage. Power supply 110-250V 40/60Hz. 50W. Supplied with metal carrying case. L. 13in. H. 5in. W. 5 1/2in. Weight 14 1/2lb. Price £22. P. & P. 30/-.



### PRECISION MULTI-TURN POTENTIOMETERS IN STOCK

PANEL LAMPS  
Robust superior design, 1in dia. to fit 1in hole, 1in O/A length. Available Red or Green, 15 for 30/-, P. & P. 5/-. With Press to Test facility, 1in dia. to fit 1in hole, 1 1/2in O/A length. Available White or Red, 12 for 30/-, P. & P. 5/-. Both types take 6mm Midget Flange Bulbs.

## STOCK CLEARANCE

In order to give clearance in our new stores the following scientific equipment is being sold at realistic prices. All items are offered in "As is condition".

- (1) R.F. Oscillator Advance P1, 6 ranges, 100kHz to 100MHz. Attenuator 1V to 100mV. Audio frequency O/P. Mains 1/P. Carriage £1. £5
- (2) Low Frequency Oscillator Dawe 400C, 0-1Hz to 1kHz. Fitted C.R.T. Frequency Comparator. Mains 1/P. Carriage 30/ £12
- (3) Phisimeter TS 13C/AP EX-USA Battery Powered, P. & P. 10/ £5
- (4) A.F. Analyser by Dawes, 7 Ranges 2-5Hz to 8kHz. Carriage 30/ £25
- (5) Pulse Analyser, Dynatron Radio Ltd. N/101, Carriage 30/ £8
- (6) Directional Coupler to 50ohm line. P. & P. 10/ £7.10.0
- (7) Time Interval Meter, Carriage £1 £4
- (8) Standard Resistance Box, Decade steps 0-9999, 4 dials by Evershed & Vignoles. P. & P. 10/ £5
- (9) Valve Tester "Windor" Taylor. Model 45B. Damaged Meter. P. & P. 4/ £3
- (10) Valve Voltmeter, Marconi TM45. Mains 1/P. Range 1.5-150V a.c./d.c. Carriage £1 £5
- (11) Electro Static Voltmeter, 0-6kV, 3 1/2in dia. P. & P. 10/ £5.10.0
- (12) Valve Voltmeter, CT54. Battery Powered by Electronic Instruments. Carriage £1 £8
- (13) Phase Sensitive Voltmeter, 2 meters EX Equipment. Carriage £2 £5
- (14) Stabilised d.c. Power Supply. Mains 1/P. d.c. O/P. 2.5-10V at 100mA, H. 9in, W. 9in. Carr. £1 £7.10.0
- (15) Variable d.c. Power Supply. Mains 1/P. d.c. O/P. 0-300V at 150mA, 6-3V a.c., height 9in, width 9in, depth 3in. Carriage £1 £7
- (16) D.C. Stabilised Power Supply. Electronic Instruments. Mains 1/P. d.c. O/P. 0-300V at 100mA, a.c. 6-3V at 3A, width 1 1/2in, height 9in, depth 9in. Carriage 30/ £9.10.0
- (17) TV Waveform Generator "CHAN-NEL" Bruns, Ltd. Carr. £1 £5
- (18) Noise Generator, CT410. V.G. Condition. Mains 1/P. Carr. £1 £25

### MINIATURE UNISELECTORS

3 bank, 12 way, 250 ohm, 24V. Type 2200A. Supplied complete with plug-in base. Size 3in 1 1/2in 2in. A very neat precision component. Price £4.19.6. P. & P. 5/-.



### STANDARD CELL, MUIRHEAD D550A

1.01830V at 20°C. £11.00. P. & P. 5/-.

### TRANSISTORISED MULTILINE COMPARATOR.

Vanner Type T839, £5. P. & P. 5/-.

### TELEPHONE DIALS

Clear peepers. No markings. £1. P. & P. 5/-.



### OSCILLOSCOPES

Callor collects. Sold "AS IS" Condition. Concor 1035 Mk. 1 £12.10.0  
Furzehill 0110 £10.10.0  
Airmec 723 £7.10.0  
Airmec 830 £7.10.0  
Solartron D200 £10.0.0  
Dumont 241 £8.0.0

### COUNTERS

HIGH SPEED IMPULSE COUNTERS  
by Davis, Wynn & Andrews, 4in dial and pointer registers up to 100 and 4-digit counter, both manually resettable. The drive to the counter is by air inverse escapement so that there is no loading of the pointer mechanism when digits are changed and adjustable pawls are unnecessary. Coil resistance 100 ohms for nominal volt operation, but the device works reliably from 20V at rates up to 10 impulses/sec. In circuit with a thyatron, or neonatron counting rates up to 100 impulses/sec are possible provided pulse width is restricted to keep mean current to 100mA. New. £8.0.0. P. & P. 7/6.



New, 24V 5 Digit, Non-resettable, 500 ohm coil, 1in 1in 4in, £11.50. P. & P. 5/-. Similar to above but next size larger. Displaying 1in digits only 0-9. In "AS NEW" Condition. £21.50. P. & P. 5/-.

### BRAND NEW 4 Digit

Resettable Counter  
by conebridge Type ATC & F4E. Operating voltage 12V d.c. 120mA. Reset 12V d.c. 10 impulses/second. W1in, H2 1/2in, D4in. Panel mounting. Price £5.00. P. & P. 5/-.

### 4 DIGIT NON-RESETTABLE COUNTER

Totalising 10 impulses per second. Length 3 1/2in 1 1/2in 1 1/2in. 24V d.c., 300 ohm. Price 6/8. P. & P. 5/-.



### 6 DIGIT ELECTRICAL IMPULSE COUNTER

with electrical and mechanical reset counter driven by 110V DC. 4400 ohms coil. Reset 110V DC 800 ohms coil. Housed in plastic-alloy case. The units can be interlocked with each other to give vertical or horizontal displays. Price 59/6. P. & P. 5/-.

### VEEDER ROOT & 6 DIGIT COUNTER

Suitable for counting all kinds of production runs, business machine operation. Mechanically driven. Reset type KA 1357, manual knob. Ex-equip. but new condition. Special price 25/- plus 5/- P. & P.

### 3 DIGIT RESETTABLE COUNTER

Totalising 48V d.c. at 48mA; 10 impulses/sec. Length 4in 2in 1in. Price £3.15.0. P. & P. 5/-.

### 6 DIGIT RESETTABLE COUNTER


Totalising 240V 50Hz. Viewing window 2in 1in. Ex-equipment. Price 55/-, P. & P. 5/-.

### 6 DIGIT TOTALISING NON-RESETTABLE COUNTER

Mechanical operation. Chromium finish. Length 1 1/2in 2 1/2in 2in with viewing window 2in 3 1/2in. Ex-equipment. Price 9/6. P. & P. 2/6.
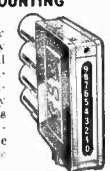
### BERKELEY DECIMAL COUNTING UNIT 0-9

4 valve double triode type 2065 special quality Unit plugs into standard octal base. Modular construction with 10 miniature neon lamps on display panel. Power supplies 0.5V, a.c., 150V d.c. Cut-on Cut-off 15V. Size 5 1/2in 5 1/2in 3in. Price 65/-. P. & P. 5/-.



### MINIATURE DIGITAL DISPLAY

Operates on a rear projection 0-3V pilot lamp. Character size 1/4 high, 0-9 digits with degree symbol, i.e. (4°). Dimensions 1 1/2" x 1 1/2" x 1 1/2" deep, 1 1/2" high. List price 6/8. Our price 49/6. P. & P. 5/-.

### EAC DIGIVISOR Mk. II DIGITAL READ-OUT DISPLAY

Uses a sensitive moving coil movement to project digits 0-9 on to a viewing screen via an optical lens system. Image height: Lamp 6-3V. Sensitivity 250 microamp. Dimensions L. 4 1/2" W. 2 1/2" H. 1 1/2". Price £3.10.0. P. & P. 5/-.



### SOLENOIDS

High quality solidly constructed solenoids. Actuated by 42V 45 ohm coil. Overall length 3 1/2" 1" square with a 1" travel of the shaft. 8/8. P. & P. 3/-. 24V. 70 ohm. Armature 1 movement. Lug type fitting. L. 1 1/2" W. 1 1/2" H. 1 1/2". Price 4/6. P. & P. 2/6.

## LAMPS

250V, 15W, M.B.C. Panel lamps. Ideal making up displays, etc. Length 2 1/2in 1 1/2in dia. Special offer, 10 for £1. P. & P. 5/-.

## NEW TRANSISTOR TESTERS

Battery powered for checking leakage current and gain of P.N.P. transistors, meter and audio indication. Siemens Ediswan Type R2925. W. 7 1/2", H. 4 1/2", D. 2". £8.10.0. P. & P. 7/6.

## MINIATURE MOVING COIL RELAY S115


By Sangano Weston, suitable for D.C. circuit. A high sensitivity relay more sensitive than the electromagnetic type. Single Coil Resistance 310 micro amps, 315 Ohm. List price £4.10. Our price 20/-. P. & P. 5/-.

## NUMICATORS

Fig. size 16mm. Cold cathode gas filled in line 0-9 digital display tubes. Long life expectancy. Minimum striking voltage 180V. Side reading Type XX 13 and XX 8 number. Price 18/6 each. P. & P. 2/6.
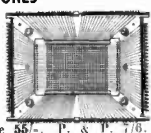
## MEMORY CORE STORES

42 52 2K bit ferrite core store complete with 84 O.A.10 load diodes. Ideal for building computer store or holding information in binary form. Price 55/-. P. & P. 7/6. Handbook available on how to use core stores. 2/6.



## LINEAR THYRISTOR CONTROLLED LIGHT DIMMER—BRAND NEW

High grade full wave bridge circuit gives linear control of light brightness. Ideal for controlling room lighting and a.c./d.c. commutator motors fitted to portable electric hand drills. Fits standard 2in conduit box. 240V, 50Hz, 600W. Price 59/6. P. & P. 2/6.



## AVO TRANSISTOR ANALYSER CT 446

A portable direct-reading instrument capable of giving accurate transistor measurements in the grounded emitter configuration. Battery power unit 1.5V to 10.5V in 5 steps. Base current 0-10A, 1-40mA, Collector current 250mA. Size: 151 9/16in. Weight with batteries 15lb. Price £42.10.0. Carriage extra.

## RAPID HEAT SOURCE

from brand new Infra Red Tubular Quartz Lamps. Ideally suited as heat source for Drying Ovens, Egg Hatching, Incubators, etc. 240V, 1,440W, 20,000 Angstroms. Length 12in 2in dia. Price 15/-. P. & P. 5/-.

## BRAND NEW HIGH CAPACITY ELECTROLYTIC CAPACITORS at a fraction of original prices by MALLORY or SPRAGUE


Capacity In Microfarads	Working Voltage	Surge Voltage	Price
3,500	25	35	10/-
5,000	25	61	20/-
7,750	10	15	10/-
20,000	30	45	25/-
25,000	25	40	15/-
25,000	50	65	30/-
27,000	15	20	20/-
30,000	32	35	25/-
35,000	15	20	10/-
37,000	15	20	20/-
40,000	10	12	10/-
40,000	25	30	25/-
55,000	15	20	20/-
90,000	10	14	20/-

P. & P. 5/- on single item.
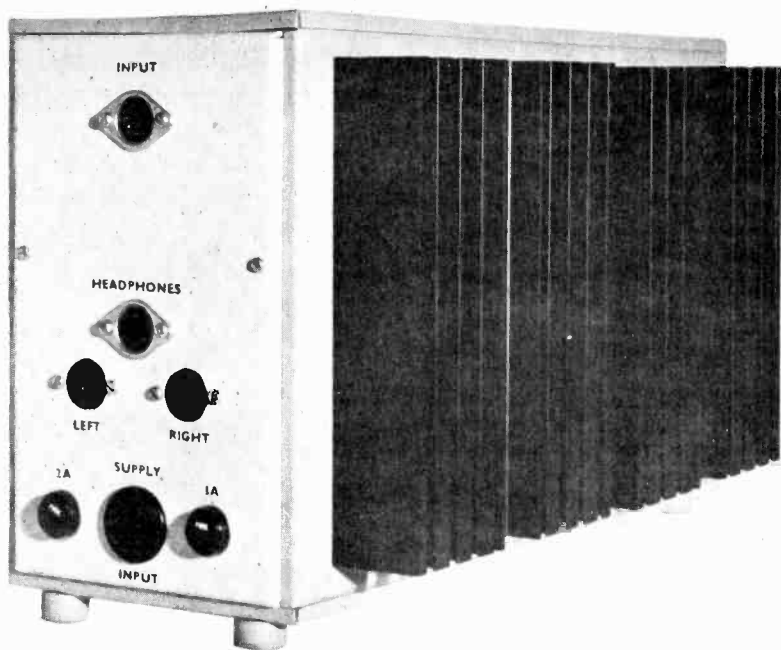
## ELECTRONIC BROKERS LTD.

(Dept. PE), 49-53 PANCRAS RD · LONDON NW1  
01-837 7781 TELEX 267307  
Open Mon.—Fri. 9—6 p.m.

By D. S. GIBBS and  
I. M. SHAW (FERRANTI LTD)



RE  
GEMINI

# DUAL PURPOSE PART TWO STEREO AMPLIFIER


**T**HIS month we complete construction details of the main amplifier unit. Setting up instructions are also given; components lists appeared last month.

## CONSTRUCTION—CIRCUIT BOARDS

Most of the small components for the main amplifier and the power supply are mounted on two fibreglass printed circuit boards. Scale drawings of these boards are given in Figs. 13 and 14. Turret tags are inserted at all the points where wire connections are made to the board. Whilst not essential it does lead to a neater finished article, but as a second best the connecting wires can be inserted through the turret tag holes and soldered onto the copper directly. The following instructions apply to the turret tag version only.

Twenty-three tags are needed for the main amplifiers and 12 for the power supply. The component layouts are given in Figs. 13 and 14 and no explanations are necessary for this stage of the operation. Flying leads should be soldered to all the turret tags using p.v.c. insulated wire of a suitable size such as 14/0076 except those to the output transistors TR12, TR13, TR112, TR113 and transistor TR3, which should be left unconnected. The input turret tags to the main amplifier should also be left unconnected.

It will be seen from the photograph of the main amplifier board that transistors TR7, TR10 and TR11 are thermally connected. Drawings of these clips are given in Fig. 17, of which two are required per channel. They are connected together by 6B.A. bolts and care must be taken to see that when in situ they do not touch any of the other components or transistor wires. Transistor lead connections are given in Fig. 16.

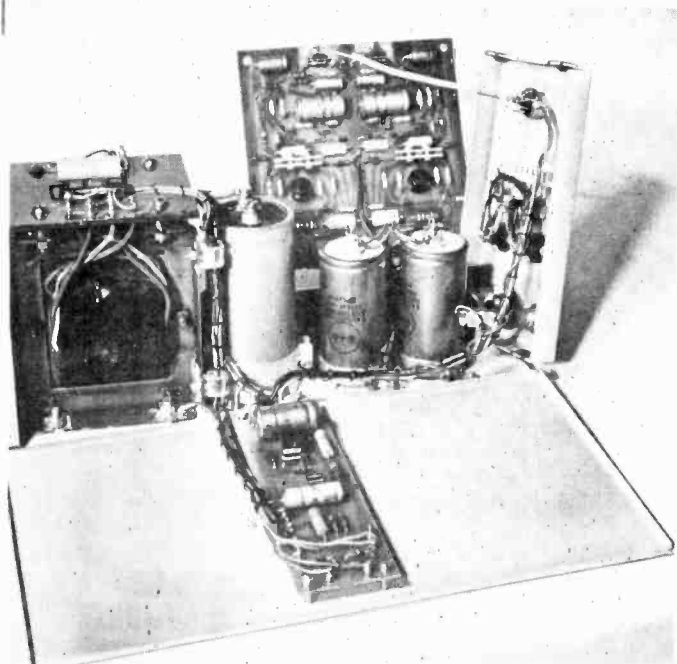





# MAIN AMPLIFIER

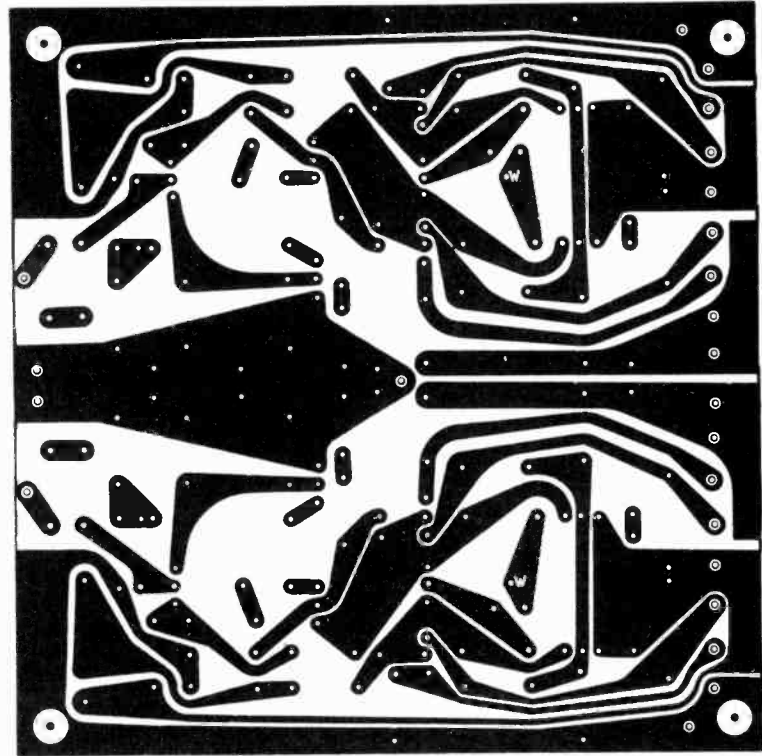
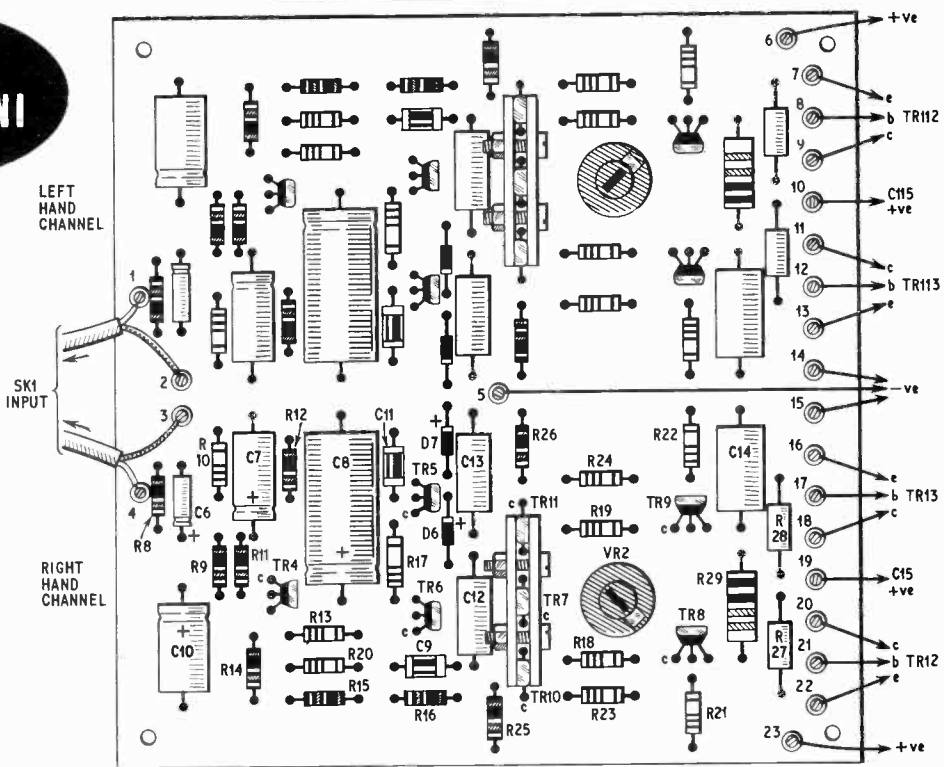


Fig. 13. Layout and wiring diagram of both channels of the main amplifier printed circuit board. Finished size of this board is 5 5/8 in square


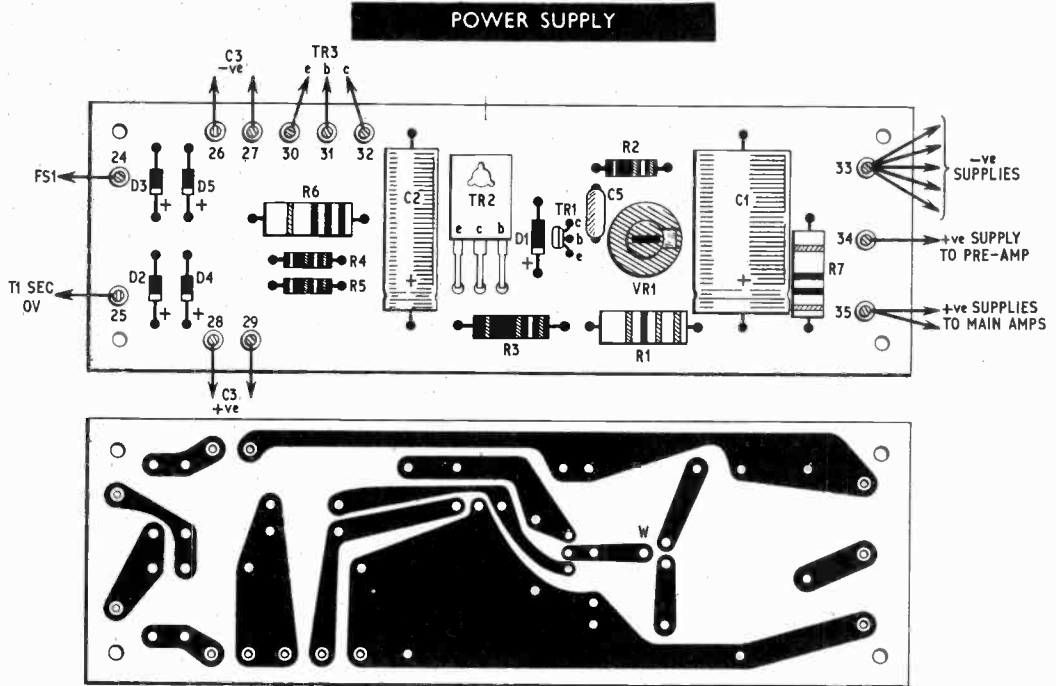
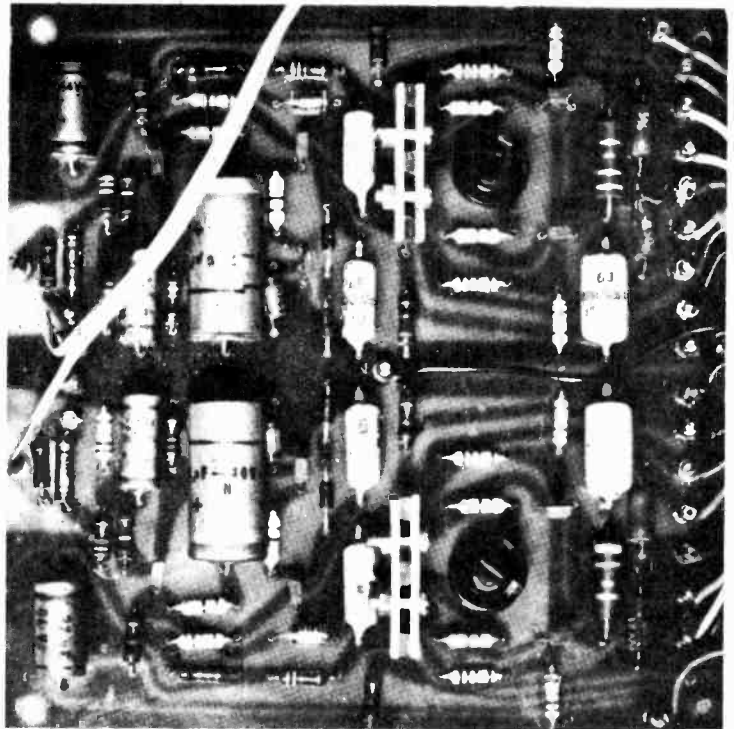


Fig. 14. Layout and wiring diagram of the stabilised power supply printed circuit board. Finished size of this board is  $6\frac{3}{8}$ in by 2in

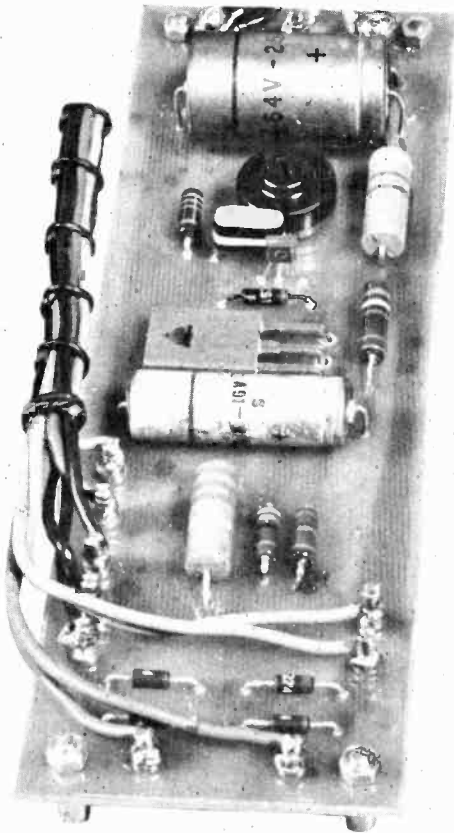

## DRILLING

Both the main amplifier and pre-amplifier are housed in Contil Mod-2 cases of the types given in the components list. The panels and heatsinks should be drilled as indicated in Figs. 18 to 22, and all burrs removed with a file or large drill. Please note that if different components are used such as a different mains transformer or tagstrip then the hole positions must be modified to suit.

## LABELLING

The main amplifier front panel should be given a light coat of Letracote Gloss and then the sockets and fuses labelled with black Letraset as in the photographs.

Two more coats of Letracote Gloss should then be applied, allowing suitable drying times.

## HEATSINKS

Transistors TR12, TR13, TR112, TR113 are mounted on heatsink A and transistor TR3 on heatsink B. All these devices are supplied with a mica washer and a shakeproof washer, and they should be mounted as shown in Fig. 15, preferably with a smear of silicon grease on each side of the mica washer. When the heatsinks are fastened to the case the transistors will be inaccessible, therefore the wires must be connected at this stage, suitably colour coded. All holes must be deburred and transistors fitted with 4B.A. nylon screws.

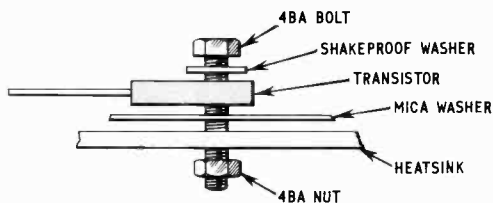


Fig. 15. Mounting details for transistors mounted on heat sinks

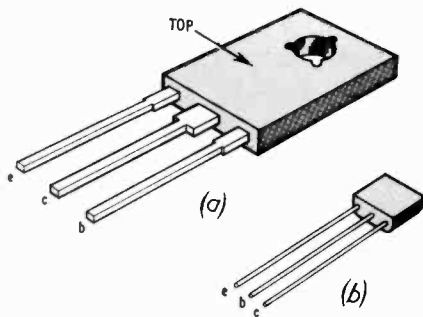


Fig. 16. Transistor connections (a) Motorola transistors as used for TR2, 3, 12, 13, 112 and 113, (b) Ferranti transistors as used for TR1, 4 to 11 and 104 to 111

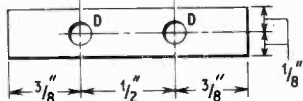


Fig. 17. Thermal clips for the driver transistors; manufacturing details—two required per channel— $\frac{1}{16}$  in Dural

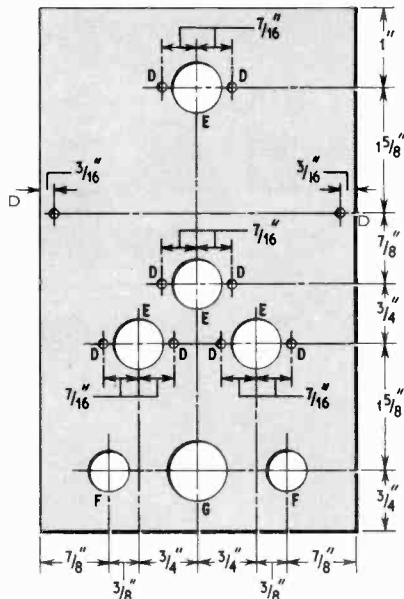


Fig. 18. Drilling details of the main amplifier front panel—no holes are necessary in the back panel or lid of the case

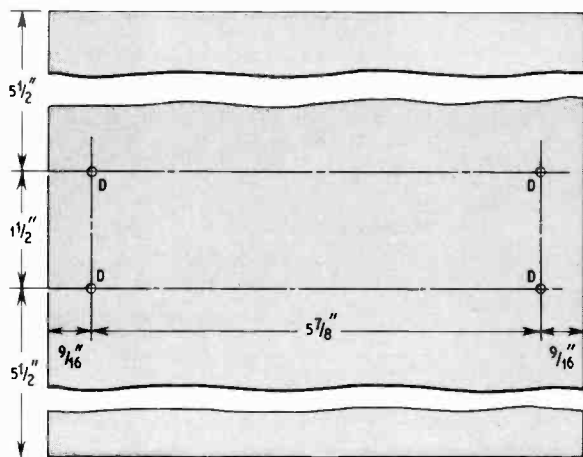
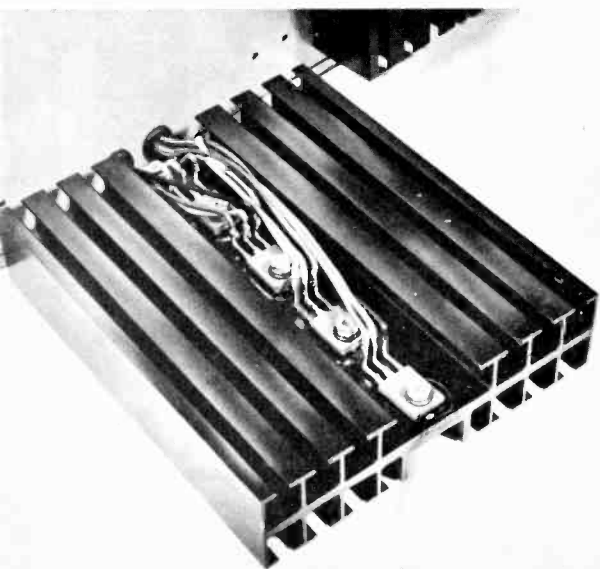


Fig. 19. Drilling details of the power supply board side of the case

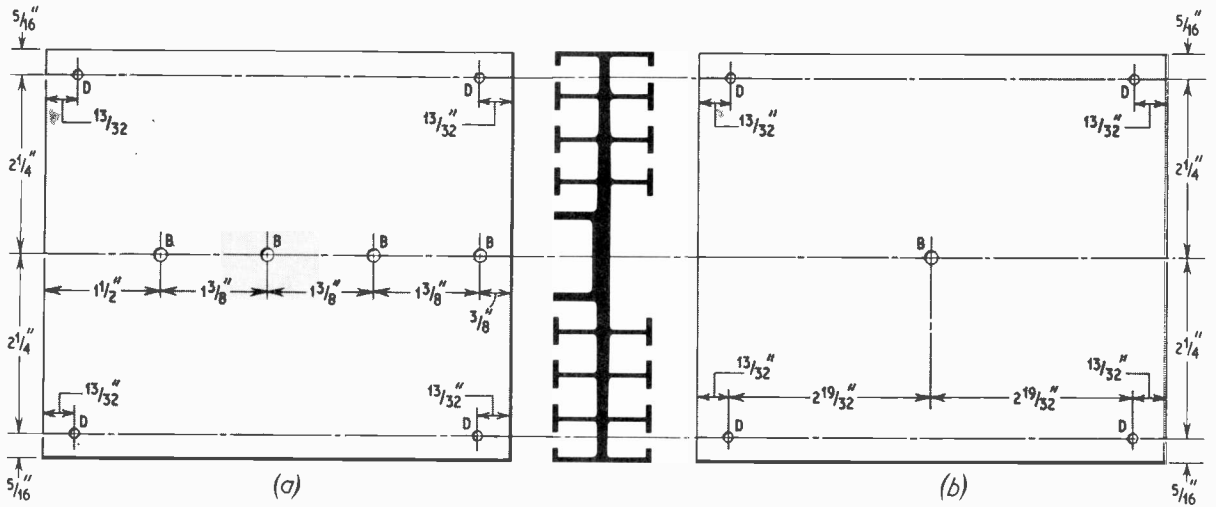


Fig. 20. Heat sink drilling details, (a) heatsink A for transistors TR12, 13, 112 and 113, (b) heat sink B for transistor TR3

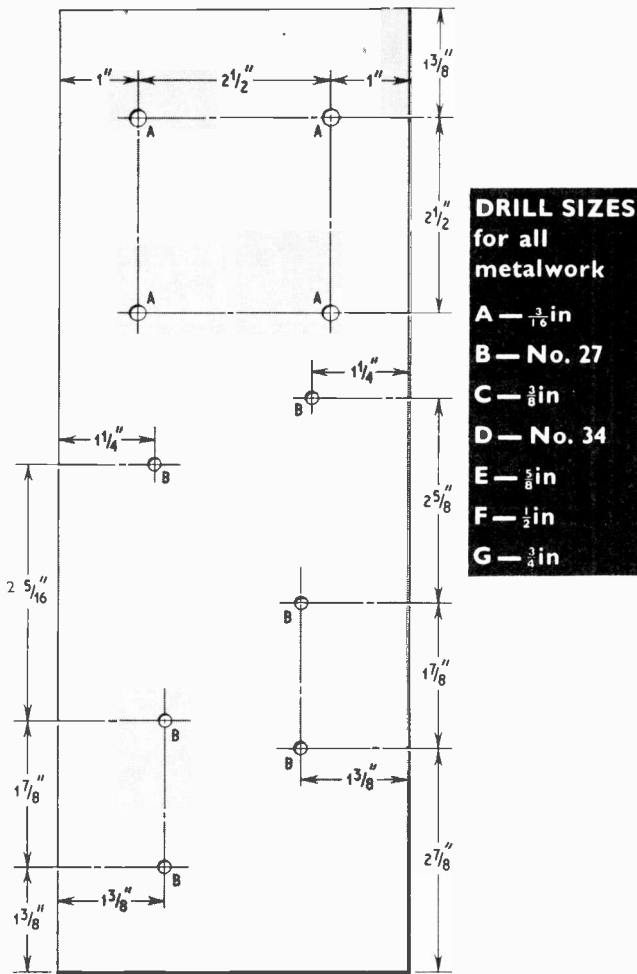


Fig. 21. Drilling details of the base of the main amplifier case

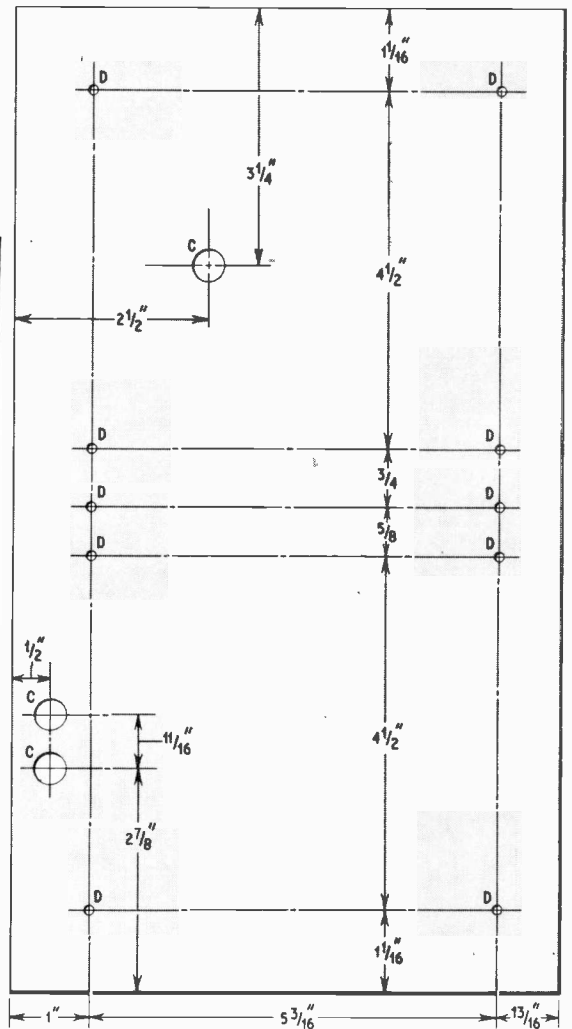


Fig. 22. Drilling details of the heatsink side of the main amplifier case

## ASSEMBLY

The front panel should now be assembled with the tag-strip, sockets and fuses using Fig. 23 as a guide. The main transformer, C3, C15, and C115 are bolted to the base plate. The printed circuit boards must be mounted as indicated in Fig. 23 on 1/2 in spacers noting that the two central screws of heatsink A must be fitted before the main amplifier printed circuit board, since the board will mask the holes for the heatsink when fitted. The other two fixing holes for the heatsink are common to the printed circuit board. The wires from the power transistors pass through the three 1/2 in holes fitted with grommets.

## WIRING


The 12 wires from the transistors on heatsink A are wired to the appropriate tags on the main amplifier board. Components R30, R31 and L1 and their counterparts in the other channel should be connected as in Fig. 23 and all the rest of the interconnections

made between the panels as in Fig. 23. The twin screened lead must still not be connected and the wire from the centre of the main amplifier printed circuit board to the negative output of the power supply printed circuit board, must not be taken along the same route as the two other negative return wires between these boards.

If this warning is not heeded and these cables run parallel, even for a few inches, the increase in distortion due to induction will be quite alarming. Also four leads, two positive and two negative, must be taken from the power supply board to capacitor C3 to reduce the ripple voltage before stabilisation. Two wires, with the appropriate tags linked are not sufficient due to the high ripple currents involved.

The mains connections from the socket are simply wired directly to the appropriate tap on the mains transformer via the mains fuse FS1. The earth wire must be connected only to the electrostatic screen on the mains transformer and not to the case, since this will be earthed via the pre-amplifier.

**Fig. 23. Layout and wiring diagram of the main amplifier.** Wires coded with a number are connected to the pin of that number on the power supply or main amplifier printed circuit boards. See notes in text concerning connection of C3 and negative return lead from pin 5 to pin 33

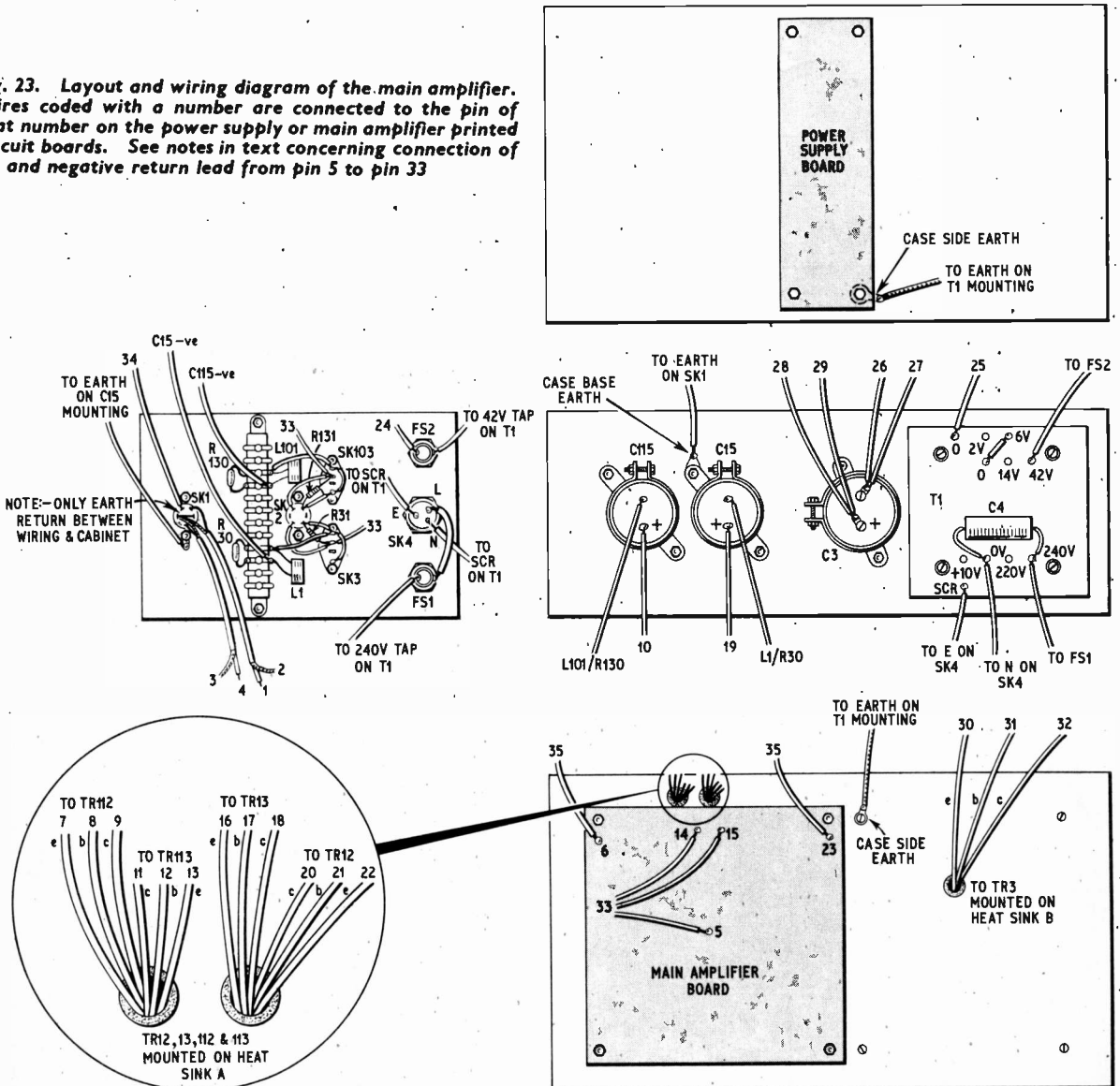



Capacitor C4 should be connected across the mains winding of the mains transformer with its leads suitably sleeved. It must be ensured that the panels are electrically connected by removing paint at the touching points, if necessary, in order to have a completely screened amplifier and power supply.

The leads to the power supply positive output from the main amplifier board are left disconnected to facilitate the setting up procedure. After all the wiring has been completed it must be thoroughly checked for "expensive" mistakes before switching on.

#### SETTING UP

With a 100V f.s.d. d.c. meter across the main output of the power supply the mains power should be applied. The output voltage should rise to approximately 55V. This should be adjusted to 55V by VR1 and the amplifier allowed to warm up for 5 minutes; the voltage can then be readjusted. Potentiometers VR2 and VR102 are set to maximum resistance, i.e. clockwise and counter clockwise respectively and a 100mA f.s.d. d.c. meter connected between the power supply main positive output and the right-hand channel supply input wire. Potentiometer VR2 should be adjusted to give 42mA, the amplifier allowed to warm up for a few minutes and then readjusted. The left-hand channel amplifier must be similarly adjusted using VR102.


#### ASSEMBLY

The front and rear panels are fastened loosely by the bottom screws and the heatsink side supported in the correct position. The screened cable from the input of the main amplifier can now be connected to the input socket, taking care to distinguish left from right (see Figs. 13 and 23). The other side panel is placed in position and fastened with the top in place.

**Note:** It is regretted that the following errors occurred in the first part of P.E. Gemini:

1. Specification—pre-amplifier signal to noise ratio, weighted figures are referred to the 30-phon curve.
2. Page 862, last paragraph—the word linear should be Lin—the person's name.
3. Page 863, second paragraph of Circuit Description—Transistor TR11 should be included in the first line.
4. Caption to Fig. 4 should read "cascode output" not "cascade".
5. Page 864, second paragraph—TR6 should be TR8.
6. Components, power supply—C5 should be 0.1 $\mu$ F polyester Mullard.
7. Fig. 11a—the oscillogram was taken at 10kHz into 8 ohms.
8. Fig. 11c should be rotated through 180 degrees.

Next month: pre-amplifier details

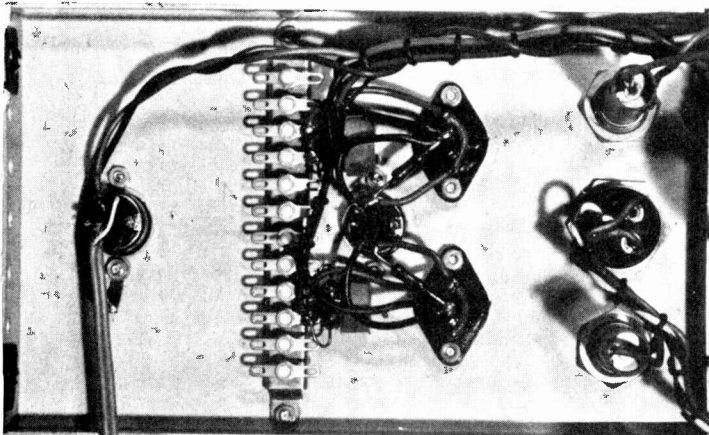

# YOUR WAY AHEAD

## Sonic Obstacle Locator...

An experimental project utilising audible sound to detect the presence of objects in fog, smoke, or driving snow. The prototype has been utilised on a motor car with astounding results, it could also prove invaluable for the small boat owner, as an intruder alarm, or for educational purposes—food for thought.

## Wash Wipe...

An intermittent wiper control that will also operate electric washers for car windcreens. Designed for the not-so-modern car; uses a unijunction oscillator and a thyristor for switching.

..... Some of the features in the January Issue of

**PRACTICAL ELECTRONICS**

JANUARY ISSUE  
— ON SALE DECEMBER 14 —

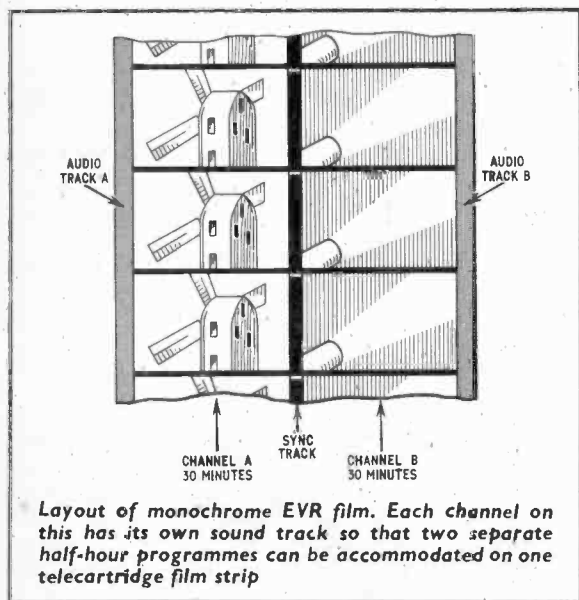
**ORDER YOUR COPY NOW!**



The EVR teleplayer can be connected directly to a domestic television set to provide pictures and sound from the telecartridge microfilm



General view of the Electron Beam Recorder in use at the EVR processing plant. The special clothing worn by the operators together with the filtered air supplied maintains the high degree of cleanliness required in the manufacturing process



Layout of monochrome EVR film. Each channel on this has its own sound track so that two separate half-hour programmes can be accommodated on one telecartridge film strip

**E**LECTRONIC video recording (EVR) has just been launched in this country by the internationally owned EVR Partnership. This entirely new system of recording sound and vision on microfilm enables reproduction of professionally recorded programmes simply by plugging into the aerial socket of a 625 line television receiver.

A reproducer, or teleplayer, is needed to process the film information. Here an electronic scanner converts the film recording into electrical signals that a television set can use.

Programmes come in the form of cartridge films. With a monochrome cartridge there can be two half hour programmes with appropriate sound and with colour cartridges one half hour programme is accommodated.

# ELECT

The Videocassette player connected to a colour television receiver. The tape can be stopped at any point in the programme, removed without rewinding and replaced with another cassette




**A**S A STRONG contender in this potential world market the Sony Corporation of Japan unveiled in London recently their colour videocassette system using the magnetic tape method. At present the system is only suitable for use with any NTSC colour (the system adopted by the U.S. and Japan) or black and white television receivers.

The outstanding feature of the Sony system is that it uses a Videocassette not unlike the standard audio tape cassette. The playing time of the videocassette is approximately 10 minutes, is capable of 200 playings and is easily loaded or removed from the playback unit.

The tape takes 2½ minutes to rewind and a taped programme can be erased easily and as frequently as on audio tape. The tape can be returned to the programme's supplier for re-recording another programme. An adaptor for recording direct from the television will also be available.

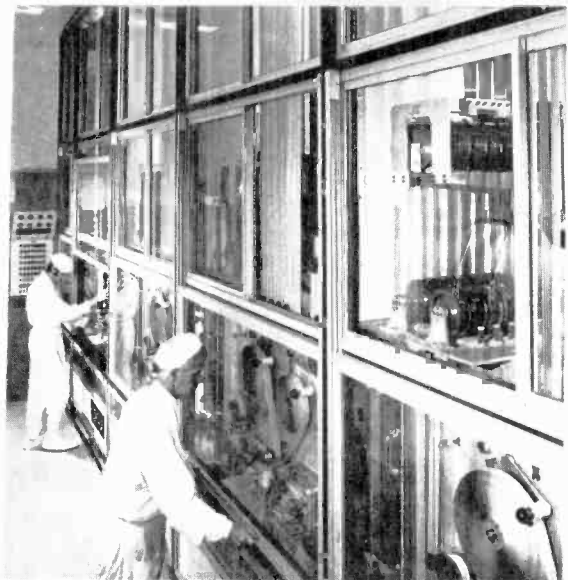The tape has two sound tracks and can be used for dual track stereo or monaural sound. In the case of a foreign movie or the teaching of a



*The high speed photographic printer in use. Here the special 35 mm EVR print stock can be seen on the feed and take-up reels in each of the four print sections*



*Incoming visual material supplied by programme owners being monitored by engineers*

At first, production of telecartridges is being confined to the educational and instructional field. Subsequently, EVR will move into the entertainment market.

To provide cartridges for the United Kingdom and overseas markets, a multi-million pound processing plant has been built at Basildon in Essex.

In the manufacturing process conversion to the EVR telecartridge format first requires that the incoming film or videotape programme to be copied, is reproduced as a 40mm master film.

This is made using an Electron Beam Recorder. In this system, an electron beam, modulated by the programme information, is made to bombard the special master film. Two visual tracks are laid on it with a centre synchronising track.

Print copies of the master are made in a high speed

multiple copying machine. Here the two sound tracks are also laid. Finally, the film stock from the printer is developed, spliced into individual 8.75mm strips and then spooled into the EVR cartridges.

The capacity of the plant is several thousand cartridges a day.

Production will concentrate initially on monochrome film cartridges; full scale colour cartridge manufacture is planned for early 1972.

Under license, Rank-Bush Murphy Ltd., will begin production of the Teleplayer next January. Selling will be direct to users at a price of £360.

Telecartridge selling prices, rental charges and distribution will be decided by the programme owners. As an example, prices of telecartridges being produced are in the range £20 to £40 for purchase and 30s. to 50s. for hiring.


# RONORAMA LOOKS AT VIDEO RECORDING

foreign language, the programme can have narration in two different languages so that it can be heard in either one or both languages simultaneously.

The playback machine (right) operates just like any other tape playback machine but is plugged directly into the television aerial input socket. The television will not require any modification and being fully compatible the set can be colour (NTSC) or black and white.


The Sony Colour Videocassette system will be available in the U.K. late 1971 and will cost approximately £260. It is estimated that the player will cost £200, the 10 minute tape £10 and the adaptor for recording direct from the television £50.

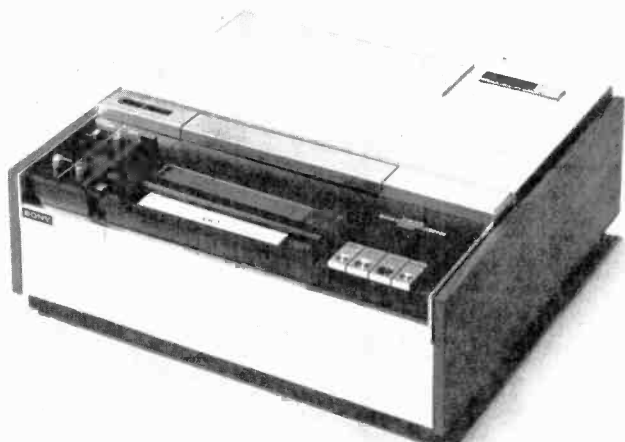In order to create a tape library Sony intends to make its facilities available to the motion picture and television industries, music and record companies, publishers and educational institutions. Sony believes this will create, for these industries, a new medium for educating and selling to the public.—Video taped P.E. each month?



*The tape player features an automatic tape threading system*

# F.E.T. TIME SWITCH

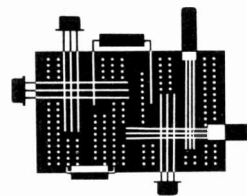

THE circuit to be described consists of an accurate timing circuit, an electronic switch and a lamp driver which provides a visual indication when a set time interval has elapsed. A relay can be substituted for the lamp if other external circuitry needs to be switched.

Intervals of from 5 to 65 seconds can be set and this upper limit can be extended to 10 minutes with suitable resistor substitution.

## FIELD EFFECT TRANSISTOR

If a resistor and a capacitor are connected to a battery of  $E$  volts as shown in Fig. 1a, then the voltage that will appear across the capacitor will take the form given in Fig. 1b. A capacitor and resistor so arranged have a time constant which is the time in seconds for the voltage  $V_c$  to reach approximately two thirds of the applied voltage and is given as  $CR$  seconds.

In the circuit of Fig. 2 the resistance/capacitance timing network combines VR1, R1 and C1. To make use of the voltage that appears across the capacitor a special type of transistor, TR1, is used. This has the full title of an n-channel field effect transistor and its most important quality is that of having a very high input impedance when its gate and source are reverse biased.

A high impedance device is very important in this position as it prevents current leaking from the capacitor and so upsetting extended charging intervals.

## TRIGGER LEVEL

At the moment when S2 is closed the capacitor C1 is discharged and the voltage at the gate of the field effect transistor is 0V. Some current, known as drain current, does flow through the device effectively reverse biasing the gate and source. This voltage is about 1V in practice.

With the switch S2 closed, C1 commences to charge at a rate which depends on the value of resistance in series with it.

In Fig. 3 is given the growth curves of capacitor voltage for three different values of resistance. It can be seen from the graphs that the  $CR$  time constants, or time taken to reach approximately 6 volts varies considerably with each resistance/capacitance combination. Also, the lower part of each curve is essentially linear.

If we can arrange to switch, or trigger the indicator lamp with a low voltage on C1 then any later calibration of VR1 will be found to be linear, that is, the movement of the slider will vary directly with the interval required.

## COMPONENTS . . .

### Resistors

R1 100k $\Omega$	R4 1.5k $\Omega$	R7 4.7k
R2 120 $\Omega$	R5 5.6k $\Omega$	R8 22 $\Omega$
R3 6.8k $\Omega$	R6 1k $\Omega$	

All  $\frac{1}{2}$  watt 10% carbon

### Capacitors

C1 100 $\mu$ F tantalum elect. 12V

### Diodes

D1 Z3.9 3.9V 250mW Zener  
D2\* OA81

### Potentiometer

VR1 1M $\Omega$  carbon linear

### Transistors

TR1 2N3819  
TR2-TR4 ZTX300 (3 off)

### Switches

S1 Single pole, push-to-make  
S2 On/off toggle

### Relay

RLA\* Two pole two way 6 volt operated 185 ohm coil (Omron Type MH2)

### Lamp

LPI 6V 0.06A

### Miscellaneous

T-Dec, connecting wire

\* Diode D2 and Relay RLA are alternatives to R8 add LPI (see Fig. 2).


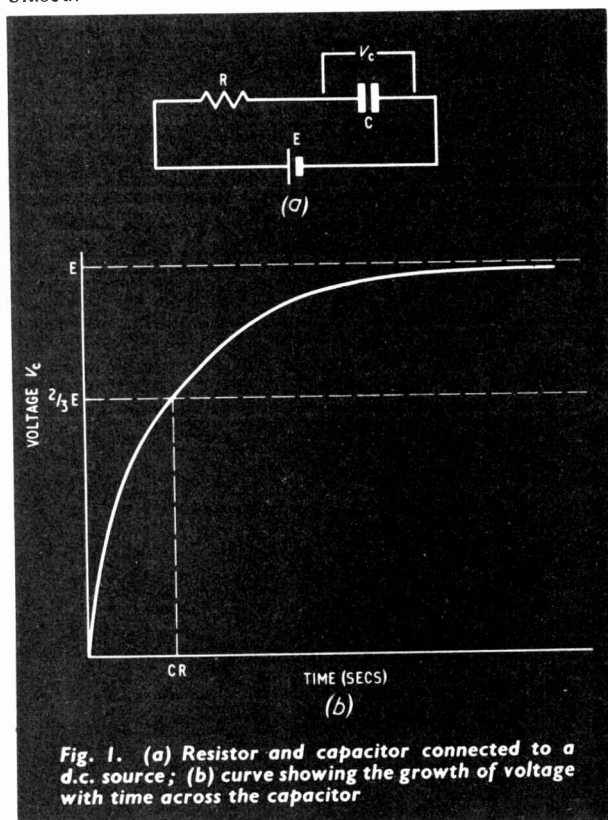


Fig. 1. (a) Resistor and capacitor connected to a d.c. source; (b) curve showing the growth of voltage with time across the capacitor

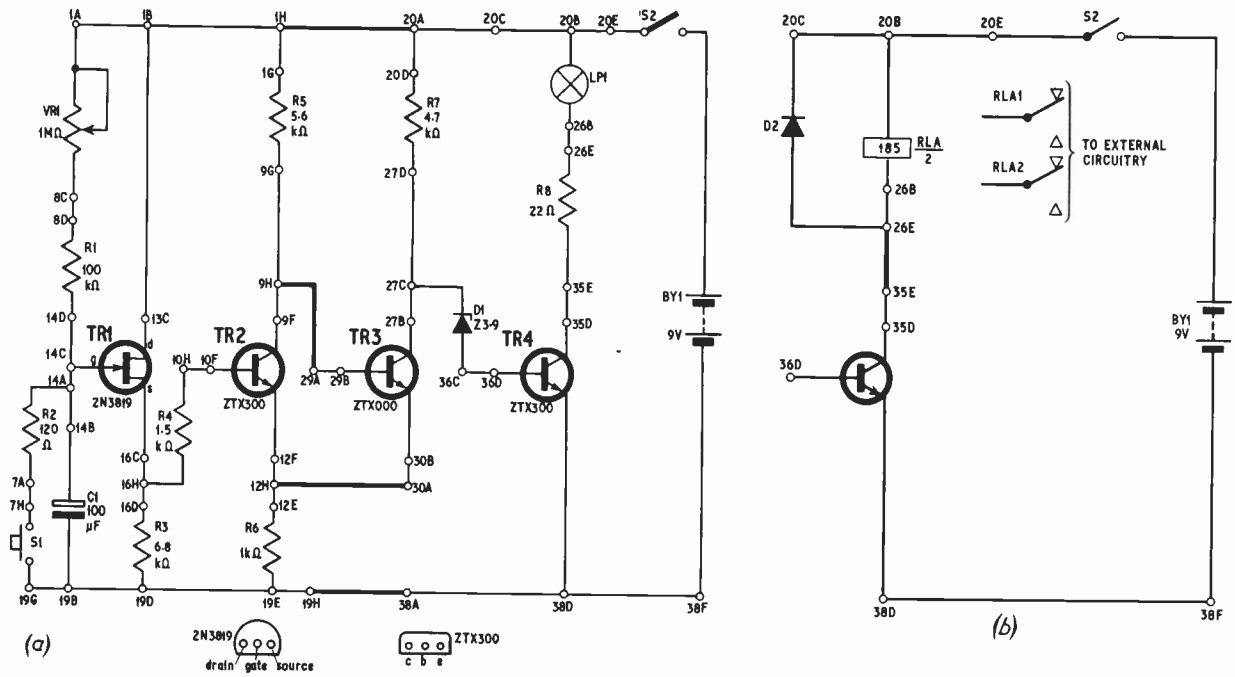

**Fig. 2. (a) Circuit diagram of time switch. The thick lines indicate link wires on the T-Dec assembly; (b) substitution of a relay at the collector of TR4. Items needed for this modification are marked with an asterisk in the components list**


The switching voltage, or trigger level, is arranged for approximately 3V at which point TR2 will turn on.

**SCHMITT TRIGGER**

With the rise of voltage on C1 towards the trigger level, the reverse bias on TR1 falls and the drain current increases so that the source voltage follows the gate.

The transistor pair comprising TR2 and TR3 constitute, in effect, an electronic toggle switch with a very rapid action. In the quiescent state with the lamp switched off, TR2 is off and TR3 on.

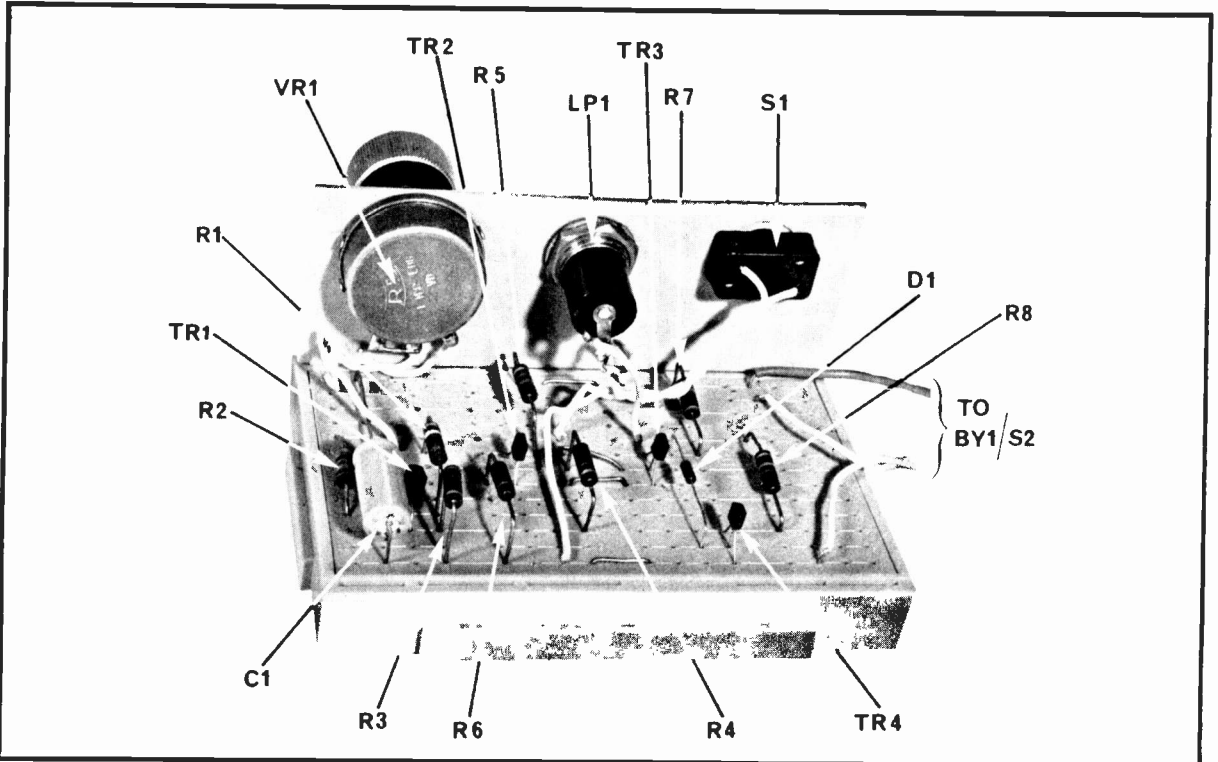The voltage at the collector of TR3 is not sufficient to turn TR4 on, it being less than the 3.9V of the Zener diode D1. As TR3 is conducting, its collector current





# NEWS BRIEFS

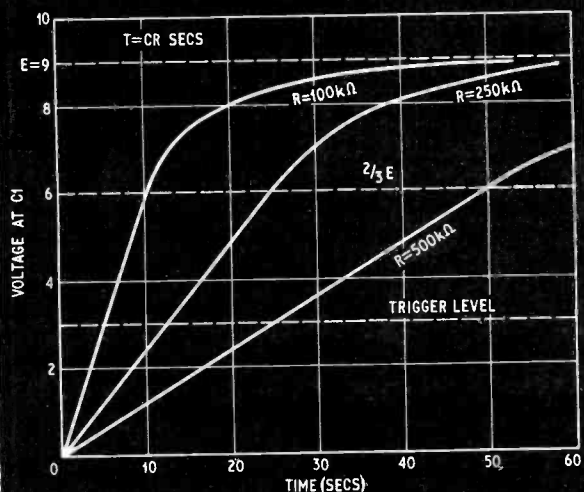


Fig. 3. Three graphs showing how variations of resistance at VRI produce different charging rates at the timing capacitor C1. A trigger level that falls on the linear parts of the curves makes for time calibration linearity

passes through R6 and produces a volt drop which reverse biases the base and emitter of TR2.

The trigger voltage at the base must exceed this voltage to turn on the transistor and when it does the voltage at its collector and emitter so arrange as to turn off TR3.

## LAMP DRIVER

As TR3 switches off, the collector voltage rises. When it exceeds the 3.9V of the Zener diode D1, this conducts and switches on the lamp driver TR4 so that nearly all of the line volts appear across R8 and LP1.

The resistor R8 is included to reduce the cold filament current of the lamp as the initial resistance of this is very low.

If the lamp driver TR4 was in any way directly coupled to the slowly rising voltage at R3 the lamp turn on would be gradual. The inclusion of the Schmitt trigger circuit ensures an instantaneous switching action.

## TURN OFF

To turn off the lamp, the voltage at R3 must be reduced by about a volt below the trigger voltage of the Schmitt circuit.

With S1 depressed C1 discharges through R2 on a short time constant. As the gate of TR1 moves towards 0V the gate-to-source junction becomes reverse biased. This means a reduction in drain current so that the voltage at R3 falls below the trigger voltage and turns off TR2 and consequently the lamp.

## RELAY SUBSTITUTION

If external circuitry, requiring larger power, is to be switched then a 6V relay can be substituted provided that the coil resistance is above 120 ohms. In this application R8 can be deleted.


A diode should be connected in parallel with the coil as in Fig. 1b, to suppress transient voltage spikes which could damage TR4.

To extend the timing range from 1-10 minutes a 10MΩ potentiometer should be substituted for VRI. ★
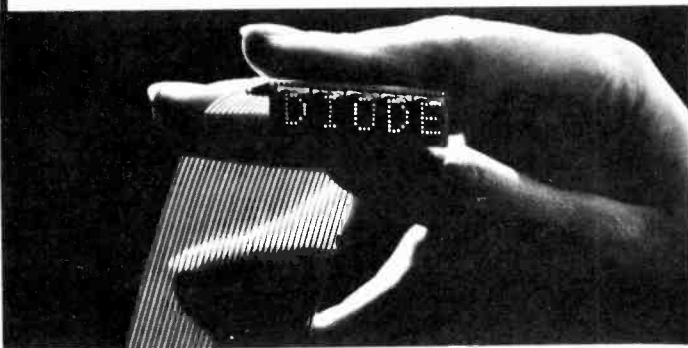
## Diode Display

SIGNIFICANT new work on small size, solid-state data displays is being carried out at the Research Laboratories of The Marconi Company, on behalf of Marconi Radar Systems. Tiny slices of glass ceramic, no larger than a finger tip, each carry a matrix of Gallium Arsenide Phosphide, light-emitting diodes, which can be switched on to provide a pattern of brightly lit red dots, making up high contrast letters, numbers or symbols, as shown below.

The major features of this development are in the production of a display format in which the total area of each character display module is completely utilised as a display, and in the development of a matrix addressing system.



## Printed Circuit Developments

PALMBOARD, a series of partly processed standard printed circuit boards, which can be tailor-made to individual designs, particularly suited to the needs of the small processor, captive laboratory and consumer, has been introduced by the Printed Circuits division of Palmer Aero Products Limited at Camberley, Surrey.

Individual designs are applied to the partly finished board to coincide with in-built contacts and a hole matrix system. Boards can be brought to completion in the minimum of time making a very attractive proposition in terms of reduced delivery times, and effect a substantial reduction in cost due to standardisation and the instant readiness from stock.

The case of printed circuits has recently been extended to car instrument panels, the photographs below show Pressac printed circuits incorporated in Ford Cortina and Rover 2000 TC panels. The panel used on the Ford motor car is a flexible circuit that folds around the instruments to provide the connections.



# The 'KIT IDEA' by HEATHKIT

Kit building is so easy the  
Heathkit way


TRY IT FOR YOURSELF

START WITH A SMALL  
BUT VERY USEFUL KIT

**THE NEW HEATHKIT  
BATTERY CHARGER**

PRICE ONLY

**£2.18.0** plus 6/- Carr.

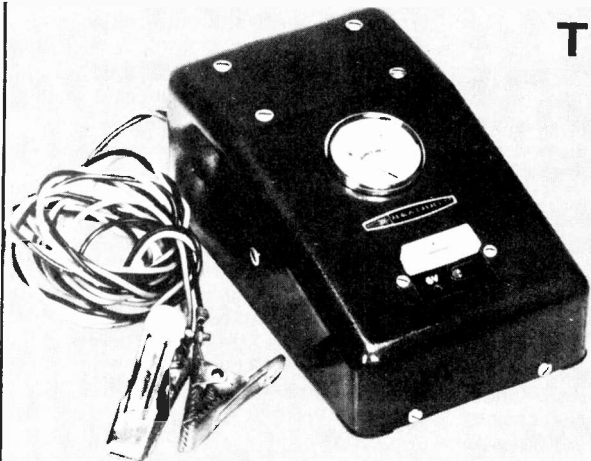

- POWERFUL OUTPUT—UP TO 4 AMPS • FULLY FUSED
- SOLID KNOCKABOUT CASE • SAFE DOUBLE WOUND TRANSFORMER • FOR 6V OR 12V CARS • ROBUST AMMETER

Here's the easy to build, inexpensive kit to introduce you to kit building. As well as the fun and fascination of building it yourself you get do-it-yourself savings. The clear, simple, fully illustrated instructions make assembly foolproof. This is the battery charger to keep your car battery in top working condition. Hurry, and make sure of your order today. P.S. — This also makes an excellent seasonal present.

**HEATHKIT**

A Schlumberger Company

**HEATH (Gloucester) LTD., GLOUCESTER GL2 6EE**

(BLOCK CAPITALS PLEASE)

Please send me a battery charger  
kit for which I enclose £3.4.0  
including carriage.

Name .....

Address .....

Post Code .....

25/12A

# Subject: OPERATION 'SEASEARCH'

AN ELECTRONIC WAR GAME BY D. R. DAINES

**T**HE sea is a big place. One of the problems facing the Royal Navy in the last war was that of patrolling extended shipping lanes with depleted forces. This in turn put a premium on the ability of commanders to anticipate where the enemy was likely to strike next. Operation Seasearch does just that.

## DESCRIPTION

The unit houses two games—the present one and another to be described later. Since both games utilise much common wiring, housing the two games within the same case affects a considerable saving. The game to be played is selected by turning a three-pole two-way switch.

Everyone is familiar with the lettered system of co-ordinates to describe the position on a map of any feature (see Fig. 1). Two twelve-way rotary switches are used in this game to denote the position of each ship. One switch determines the North/South position and the other the East/West position. Each player has two ships under his control, hence a total of eight switches and knobs are needed. The knobs are placed in such a position that each player may easily conceal his switch settings yet also be able to manipulate them readily.

Between the players is a map representing the North Atlantic, marked off in squares to correspond with the positions of the switches. There are also three pushbuttons, only two of which are used in this game. Depressing one will cause a lamp number 1 to be projected onto the map if contact has been made with the raider. Depressing the other will cause a number 2 to be projected if contact has been made with the raider's supply ship. The lamps are concealed underneath the map and when lit project an appropriate number onto it.

## METHOD OF PLAY

The "Redland" player has a surface raider and a supply ship. The "Blueland" player has a destroyer and a cruiser. The raider is positioned west of the Azores, position Gh (Fig. 1); the supply ship to Cayenne, position Ca; the Cruiser to Scapa Flow, position L1; and the destroyer to Gibraltar, position Lh; play now begins. The "Red" player "moves" his raider one square in any direction—representing one day's sailing—and for the simplest possible game ignores the supply ship completely. The "Blue" player now moves both of his ships, attempting to catch the raider with either. At the completion of his move he presses the "raider" pushbutton. If he has succeeded in getting either of his ships in the same square as the (unseen) raider the lamp will glow and the game ends.

The raider scores automatically whenever he positions his ships on a shipping lane. This causes a lamp to light, projecting a "3" onto the map. The raider scores one merchant ship sunk for each move that he is on a shipping lane, and the fact that the lamp lights is an indication to the "Blue" player that his opponent is somewhere on one of the lanes, thus helping to narrow the search. Further play details will be given at the end of this article.

## CIRCUIT

In Fig. 2, switches S1a and S2a are each one wafer of two twelve-way two-pole switches. They control the position of the raider. Switches S3 and 4 are also twelve-way (see components list) and control the position of the supply ship. At the other end of the unit, switches 5 and 6 control the destroyer and 7 and 8 the cruiser. All East/West co-ordinate switches are wired in parallel as shown, as are all the North/South co-ordinates. Jumper wires connect the centre of switches 5 and 6 and the centre of switches 7 and 8. The outputs are from the centre tags of S2 and S4, through pushbuttons to their respective lamps.


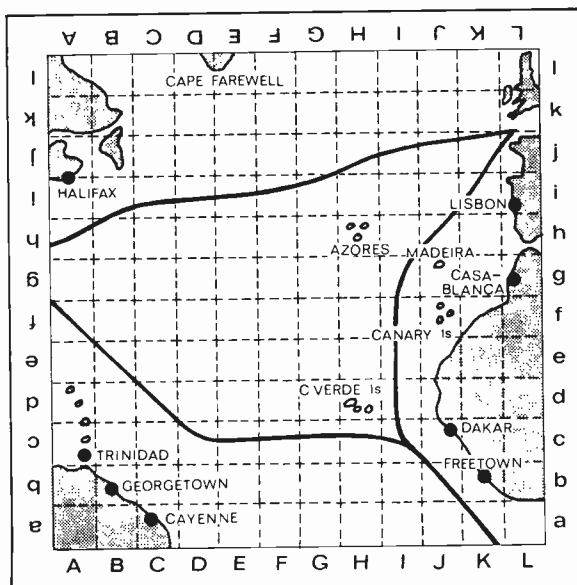


Fig. 1. Map (7in x 7in) of the North Atlantic, showing shipping lanes, used for the basis of Operation Seasearch

# ROC ELECTRONICS

## 50 PROJECT ELECTRONIC KIT Model R.130

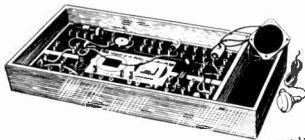

King of the Roc Electronic Kits is the Giant R.130 which makes up into no less than 50 separate projects including Radio Receivers, Transmitters, Tachometer, Rain Alarm, Testers, Electronic Switches, Amplifiers and even an Electronic Target Game. As well as earphone, speaker, meter, relay, transformer, solar cell, buzzer, etc., etc., the R.130 is supplied complete with a fitted hardwood case and clear detailed instructions for all 50 projects.

**PRICE £7.19.0**

## 20 PROJECT SOLAR ELECTRONIC KIT Mod. R.128

This ultra modern Project Kit is shaped for the space age. Carried inside a transparent domed 4 1/2 in capsule the R.128 comes complete with a self-contained solar cell to power any one of 20 projects ranging from a one transistor radio to a Morse set complete with key and Morse training code. Supplied complete with easy to follow instructions and even the cement to assemble this unique electronic space capsule.

**PRICE £4.10.0**

## 2 OCTAVE ELECTRONIC ORGAN KIT Mod. R.129

Complete with a music book containing 10 easy to play songs the R.129 solid state organ kit covers 2 full octaves. Sliding into a fitted hardwood case the top panel carries the key assemblies and all the components including the loudspeaker. Like all Roc Electronic Kits every item is included down to the last nut and bolt so that the constructor can start assembly within minutes of opening the package.

**PRICE £4.10.0**

## 10 PROJECT INTEGRATED CIRCUIT KIT Model R.127

Using a robust Solid State Integrated circuit the R.127 kits will build any one of these projects: (1) Germanium Radio, (2) Test Oscillator, (3) Morse Telegraph Training Set, (4) L.C.I. Transistor Radio, (5) Germanium 1 Transistor Radio, (6) Record Player Amp, (7) Continuity Tester, (8) AF Signal Tracer, (9) Radio Transmitter, (10) Water Purity Tester.

**PRICE £3.10.0**

## 2 TRANSISTOR SOLAR RADIO KIT Model R.126

Like all Roc Electronic Kits the R.126 uses reliable no-solder connections to produce a complete 2 transistor radio in under 2 hours. As well as battery operation the kit is supplied complete with a solar cell to provide power from the Sun or any strong light source.

**PRICE £2.10.0**

## CRYSTAL RADIO KIT Model R.125

This easy to build Radio is based on the same circuit developed by Marconi for the very first radio transmission but uses a modern ferrite core for maximum efficiency. A perfect introduction to Radio Theory.


**PRICE £1.10.0**

## 5 WATT STEREO INTEGRATED AMPLIFIER CHASSIS Model R.123

Mounted on a heavy gauge chassis the fully transistorised R.123 stereo amplifier is completely self-contained even down to ganged volume and separate tone controls. For a simple stereo amplifier of excellent quality all you have to provide is the cabinet and control knobs.

**SPECIFICATION:**  
Output: 5W total, 2.5W per channel.  
Input sensitivity: 600mV at 2.2Mohms.  
AC 240V operation.

**PRICE £4.19.0**

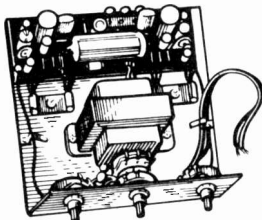

## 5 WATT 8 TRACK CARTRIDGE STEREO AMPLIFIER Model R.133

Just slot in one of the many 8 track cartridge tapes available for a continuous programme of your favourite music. A manual programme override switch enables you to switch from one track to the next at the push of a button at the same time a numbered indicator lights up to show which track is playing. Beautifully finished in an oiled walnut cabinet the R.133 is mechanically engineered to provide long and reliable service. **SPECIFICATION:** Tape speed: 9.5 cm/sec (3 1/2 i.p.s.). Wow & flutter: better than 0.3%. Frequency range: 40-12,000Hz. Cross talk: better than 40dB at 1,000Hz. Output: 5W total, 2.5W per channel. Amplifier outputs: 200mV.

**PRICE £36.0.0**



## STEREO HEADPHONES Model R.328

Built up to a standard not down to a price, the R.328 stereo headphones represent a breakthrough in value for money.


A valuable addition to any stereo installation they will provide many hours of listening pleasure.

**SPECIFICATION:**  
Matching impedance: 8-16 ohms.  
Frequency range: 30-15,000Hz.

**PRICE £2.8.0**


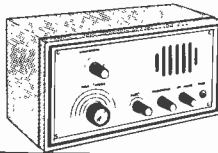
## FOUR BAND SHORT WAVE RECEIVER KIT Model R.140



This excellent transistorised battery operated kit will not only provide hours of entertainment when made up but also in its construction. It receives the normal broadcast band 550kHz to 1.6MHz and on short wave 1.5-30MHz in three bands.

The 32-page manual not only shows step by step instructions on how to assemble the kit but also includes a guide on broadcasting stations throughout the world.

**PRICE £9.8.0**



## PROFESSIONAL SOLID STATE FOUR BAND COMMUNICATION RECEIVER Model R.135

This is the communication receiver that you have long been waiting for. Fully transistorised and continuous coverage from 555kHz to 3MHz in four bands including illuminated electronic bandspread for 100-20 metres. Also incorporated is an internal speaker, automatic noise limiter, 8S/AM/CW Switch, AVC Switch, S Meter, Receive and Standby Switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. The R.135 will run off of 240V a.c. dry batteries or any 12V d.c. negative ground source.

**PRICE £45.0.0**



## 10 WATT BUDGET STEREO ALL TRANSISTOR AMPLIFIER Model R.136



Ideal as a second stereo system or for the newcomer to Hi-Fi who wishes to upgrade existing equipment the R.136 sounds every bit as good as it looks. As well as inputs for crystal or ceramic cartridge the R.136 has a Stereo Tuner input which accepts the matching R.134 Stereo AM/FM Tuner.


The sixth Finish front panel carries a stereo headphone socket as well as volume, balance, tone, enclosure.

**SPECIFICATION:** Output: 10 watts total, 5 watts per channel. Frequency Range: 35-18,000Hz. Inputs: Phono and Tuner.

**PRICE £13.0.0**



## AM/FM/MPX STEREO TUNER Model R.134

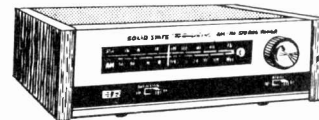

Perfect Matching Unit to the R.136 Amplifier. The R.134 Stereo Tuner is designed to give years of reliable performance. The Tuning Band covers AM & FM with a separate stereo beam to indicate when stereo broadcasts are being received.

**SPECIFICATION:**  
FM: frequency range: 88-108MHz. Stereo Usable sensitivity: 18µV. Stereo separation: 26dB at 1kHz. Image rejection: 55dB. AM: frequency range: 535-1,605kHz. Usable sensitivity: 250µV.

**PRICE £21.0.0**



## 4 WATT STEREO FM/AM/MPX TUNER AMPLIFIER Model R.124

Another Roc Exclusive offering top value for money performance the R.124 is a Stereo Tuner/Amp with facilities only usually found in much more expensive units. Features like separate bass and treble controls, automatic frequency control switch and stereo headphone socket give the R.124 a price to specification ratio second to none.

Housed in a handsome walnut cabinet the classical low line styling of the R.124 will grace any home. **SPECIFICATION:** FM: Frequency Range: 88-108MHz. Usable sensitivity: 20µV. Stereo Separation: 26dB at 1kHz, 20dB minimum. Image Rejection: 55dB. AM: Frequency Range: 535-1605kHz. Usable sensitivity: 300µV. Audio Section: Total Output Power: 4W. Phono Input: 200mV at 1MΩ. Tape Input: 100mV at 100KΩ.

**PRICE £29.19.0**



H.P. Terms available for personal callers on purchases over £30.



**RETURN OF POST MAIL ORDER SERVICE Dept. PE**

Orders under £10 please add 5/- post and packing. Orders over £10 sent post free.

**ROC ELECTRONICS LIMITED**

193 EDGWARE ROAD LONDON W2 1ET

TELEPHONE: 01-723 6211

Shop open 9-6 Monday-Saturday

# STEPHENS

**ELECTRONICS**  
P.O. BOX 26  
AYLESBURY, BUCKS.

**SEND S.A.E. FOR LISTS**  
**GUARANTEE**  
Satisfaction or money  
refunded

## GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE 1 YEAR'S GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS

AZ31	10/	EC80/2	9/8	EL803	17/	PCC85	8/8	PY83	10/	UL41	11/8	GAR5	8/8	6EH7	8/8	6SG7	8/8	12BE6	8/8	30P18	7/
AZ50	12/	ECF85	11/	EL821	11/	PCC88	14/	PY88	8/8	UL84	11/	GAR6	8/8	6EJ7	7/8	6BJ7	7/8	12B17	7/8	30P19	15/
CB11	16/	ECH35	13/8	ELL80	15/	PCC89	12/3	PY20	20/	UM80/4	9/8	GAS5	7/	6EW	12/	6SK7	8/8	12B7	10/	30P11	15/8
CB13/1	17/	ECH42	13/3	EM34	16/	PCC189	12/3	PY20	20/	UY41	8/8	GAS7	16/	6F1	14/	6SL7GT	8/8	12K6	7/8	30P13	18/
CV31	7/	ECH81	10/3	EM71	15/8	PCC80	10/3	QVQ02-6	42/	UY85	6/8	6AT6	8/	6F5	8/	6SN7GT	8/	12K7GT	7/	30P14	17/
DAF91	8/3	ECI83	8/	EM80	8/	PCF80	10/8	QVQ03-10	125	15/	6AU6	8/8	6F6G	8/8	6F6G	8/8	12QGT	8/	35A3	10/	
DAF96	8/3	ECI84	8/	EM80	8/	PCF80	10/8	QVQ03-10	125	15/	6AV6	8/8	6F11	8/8	6F11	8/8	12RGT	7/	35A5	11/	
DF91	8/	ECL80	9/8	EM84	7/8	PCF86	12/3	QVQ03-12	136	25/	6B6	8/8	6F12	4/8	6F8	8/8	12RGT	7/	35B5	13/	
DF96	9/	ECL82	9/8	EM87	11/	PCF2001	16/3	R19	13/	13/	6B6	8/8	6F12	4/8	6F8	8/8	12RGT	7/	35C5	13/	
DK91	11/8	ECL83	11/8	EN91	6/8	PCF80	12/3	R20	15/	W229	11/	6B6	8/8	6F13	7/	6U4GT	12/8	12RGT	7/	35D5	13/
DK96	11/8	ECL86	9/8	EY51	8/	PCF802	12/3	R20	15/	W229	11/	6B6	8/8	6F14	12/	6U8	7/	12RGT	7/	35E5	13/
DL92	7/8	ECL1800	30/8	EY80	8/	PCF802	12/3	R20	15/	W229	11/	6B6	8/8	6F15	11/	6V6GT	8/8	12RGT	7/	35F5GT	8/8
DL94	7/8	EF39	10/8	EY81	8/	PCF802	12/3	TT1	48/	0A2	8/8	6BL8	10/	6F18	8/	6X4	5/	12S7GT	8/	35G5	11/
DL96	9/8	EF80	8/	EY81	8/	PCF802	12/3	TT2	50/	0A3	8/8	6BL8	10/	6F22	8/	6X8GT	8/	12S7GT	8/	35Z4G	5/
DM70	8/3	EF83	10/8	EY86	8/	PCH200	14/	U20	13/8	0H2	6/8	6BN5	8/8	6F23	15/8	6Y6G	12/	12RGT	7/	35Z5GT	7/8
DY86/7	8/	EF85	8/3	EY87	8/8	PCL82	10/3	U25	15/	0C3	7/8	6BR7	15/	6F25	15/	7Y4	12/	1487	10/	60A5	13/
DY802	8/6	EF86	13/3	EY88	8/8	PCL83	10/3	U26	15/	0Q4	6/8	6BR7	15/	6F28	14/	9B6G	8/8	20D1	9/	60B5	7/
E85L	55/	EF89	8/	EZ35	5/8	PCL84	10/3	U31	30/	384	7/	6B6W	16/8	6F29	8/	10D1	8/	30P1	10/	60L6GT	8/
EECC	8/	EF91	8/	EZ40	8/	PCL85	10/3	U37	30/	384	7/	6B6W	16/8	6F30	8/	10D2	8/	30P2	10/	60M5	17/
E30F1	42/	EF92	10/8	EZ41	8/	PCF500	30/8	U92	8/	5R4Y4	11/	6B6W	16/8	6F31	8/	10D3	8/	30P3	10/	60N5	48/
E180F	19/	EF93	9/8	EZ80	5/8	PF1200	14/9	U76	5/	5U4G	8/	6B6Z	6/8	6J5GT	8/	10F1	8/	30P4	20/	60P5	12/
EABC80	10/8	EF95	12/8	EZ90	5/	PL36	12/9	U78	5/	5U4C/B	7/8	6B6Z	6/8	6J5GT	8/	10F18	8/	30P5	20/	60Q5	25/
EA42	10/8	EF183	11/3	GS10C	100/	PL38	11/8	U91	15/	5U4C	7/8	6C5GT	7/	6K6GT	10/	10L1	8/	30P6	20/	60R5	25/
EB33	11/	EF184	7/	GY501	18/	PL81	10/3	U93	15/	5U4C	7/8	6C5GT	7/	6K6GT	10/	10L1	8/	30P7	20/	60S5	25/
EB41	9/8	EF800	20/	GZ30	7/8	PL81A	10/3	U93	15/	5U4C	7/8	6C5GT	7/	6K6GT	10/	10L1	8/	30P8	20/	60T5	25/
EB081	8/8	EF804	20/	GZ32	9/8	PL85	10/3	U282	8/	6J30L2	15/	6C8C	5/8	6K28	15/	12A3C	7/8	30A3	8/	866A	14/
EB090	8/8	EF811	15/	GZ33	18/	PL84	8/3	U301	11/8	6A3A	8/8	6C8D6A	28/	6J5GT	8/	12A3C	7/8	30A5	15/	866B	14/
EBF80	8/	EL34	10/8	GZ34	11/	PL80	16/8	U403	10/	6A4A	9/8	6C8E7	9/	6L1	6/8	12A15	8/	30C17	15/	866C	27/8
EBF89	8/	EL36	9/8	HK90	8/8	PL504	17/	U404	10/	6A4A	9/8	6C8E7	9/	6L1	6/8	12A15	8/	30C18	15/	866D	27/8
EB91	5/3	EL41	11/	HL92	7/	PL505	29/	U401	20/	6A1B	8/8	6C8E7	9/	6L1	6/8	12A15	8/	30C19	15/	866E	27/8
EC53	10/	EL42	11/8	HL94	8/	PL509	30/8	U403	10/	6A1B	8/8	6C8E7	9/	6L1	6/8	12A15	8/	30C20	15/	866F	27/8
EC86	12/	EL81	10/	KT66	27/8	PL802	17/3	UB41	9/	6A65	5/8	6C8E7	9/	6L1	6/8	12A15	8/	30C21	15/	866G	27/8
EC88	12/	EL83	8/3	KT88	33/	PL805	17/3	UC85	9/	6A66	5/8	6C8E7	9/	6L1	6/8	12A15	8/	30C22	15/	866H	27/8
EC90	6/8	EL83	8/3	KT88	33/	PL805	17/3	UC85	9/	6A66	5/8	6C8E7	9/	6L1	6/8	12A15	8/	30C23	15/	866I	27/8
EC92	6/8	EL85	8/8	N78	21/	PY33	12/8	UC42	13/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C24	15/	866J	27/8
EC93	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C25	15/	866K	27/8
EC94	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C26	15/	866L	27/8
EC95	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C27	15/	866M	27/8
EC96	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C28	15/	866N	27/8
EC97	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C29	15/	866O	27/8
EC98	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C30	15/	866P	27/8
EC99	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C31	15/	866Q	27/8
EC100	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C32	15/	866R	27/8
EC101	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C33	15/	866S	27/8
EC102	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C34	15/	866T	27/8
EC103	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C35	15/	866U	27/8
EC104	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C36	15/	866V	27/8
EC105	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C37	15/	866W	27/8
EC106	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C38	15/	866X	27/8
EC107	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C39	15/	866Y	27/8
EC108	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C40	15/	866Z	27/8
EC109	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C41	15/	866AA	27/8
EC110	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C42	15/	866AB	27/8
EC111	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C43	15/	866AC	27/8
EC112	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C44	15/	866AD	27/8
EC113	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C45	15/	866AE	27/8
EC114	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C46	15/	866AF	27/8
EC115	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C47	15/	866AG	27/8
EC116	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C48	15/	866AH	27/8
EC117	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C49	15/	866AI	27/8
EC118	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C50	15/	866AJ	27/8
EC119	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C51	15/	866AK	27/8
EC120	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C	13/8	6Q7	7/8	12A17	8/	30C52	15/	866AL	27/8
EC121	6/8	EL86	8/8	PAIC80	8/	PY80	6/8	UC181	10/8	6A13	8/8	6D6C									

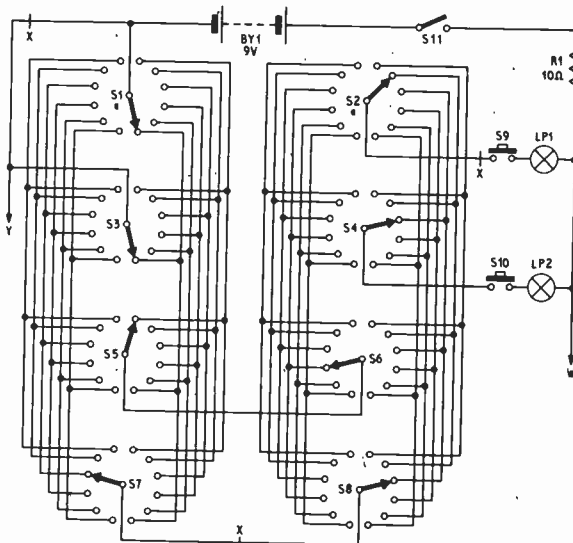
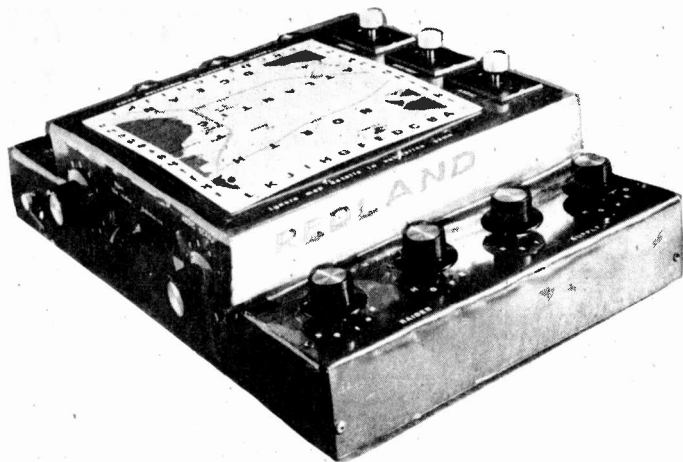


Fig. 2. Wiring diagram of the switches controlling the positions of the four ships, also showing contact indicator circuits

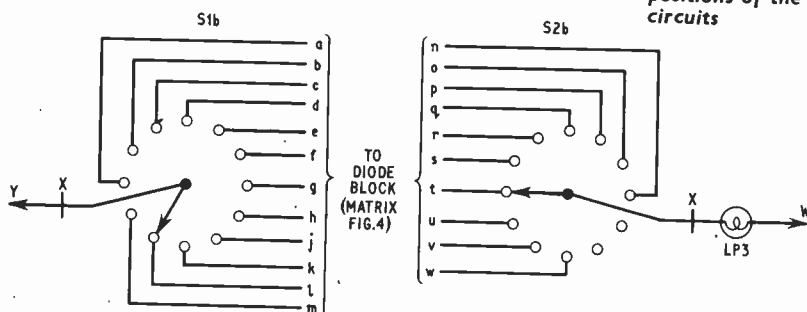


Fig. 3. Wiring of raider automatic score switching

## COMPONENTS . . .

Switches	For Operation Seasearch	If both games to be built (Where different)
S1	2p 12w	
S2	2p 12w	
S3	1p 12w	2p 12w
S4	1p 12w	
S5	1p 12w	
S6	1p 12w	
S7	1p 12w	2p 12w
S8	1p 12w	
S9	1p make, push button	2p make (or two separate 1p)
S10	1p make, push button	2p change over (or DPDT)
S11	S.P.S.T. toggle	

(All rotary Maka switches except where stated)

**Miscellaneous**

LPI—3 6.3V 0.06A (MES bulbs clip-on holders—3 off)  
 8 skirted knobs with pointers  
 Veroboard 3in x 3in (2 off)  
 DI—29 small glass point-contact diodes (29 off)  
 R1 10 ohm ½ watt resistor  
 BY1 9V battery, type PP 6  
 Aluminium, pop rivets, 4B.A. nuts, screws and washers.  
 Letraset card, cellophane, etc.

It will be seen that when S5 coincides with the position of either S1a or S3, current will pass to S6. Then if S2a or S4 coincide with S6, one of the lamps will glow; this illustrates a serious snag. If together the positions of the four ships form a rectangle, both lamps will glow but neither ship will have been detected! Hence the use of the pushbuttons. Pressing the detection pushbuttons S9 and S10 one at a time prevents the malfunction when the ships are at opposite corners of a rectangle.

There is another important reason for the use of push buttons. If a searching ship wishes to move one square diagonally—say from Af to Bg (Fig. 1)—he would have to turn both of his control switches. Since he is unlikely to turn them together, he would in fact search an extra square—say from Af to Ag and then to Bg. With pushbuttons he must complete his move before determining whether or not he is successful.

## DIODE MATRIX

The raider's automatic score indication is illustrated in Figs. 3 and 4. The second pole of switch S1a is used to feed current to a diode matrix which will pass on to switch S2a only when S1a coincides with the North/South of a shipping lane. Similarly, the second pole of S2a will pick off current from the matrix only when it coincides with the East-West of the shipping lane. Together, the diodes and the switches will therefore only conduct current when switches S1a and S2a exactly coincide with a particular shipping lane square.





### BSR 4-SPEED SUPERSLIM AUTO RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 13 1/2" x 11 1/2" x 4 1/2". Above motor board 3 1/2". Below 2 1/2". AC 200/250v.

with STEREO/MONO XTAL £7 Post 5/-

BSE UA70 Stereo/Mono Transcription Auto Changer. Calibrated Stylus Pressure. BSR Minichanger UA50 Stereo/Mono. Plays 12", 10" or 7" records. Size 12 1/2" x 8 1/2". AC 200/250v. Post 5/-.

**£14**

**£8**



### GARRARD PLAYERS with Sonotone 9TA Cartridges.

Stereo Diamond/Mono Sapphire. SP25 Mk II £15.

AT80 Mk II Stereo £15. Model 3000 Stereo £13. Post 5/-.

RECORD PLAYER PORTABLE CABINET. Space for amplifier and autochanger. Post 5/-.

RC8 DE-LUXE 3 WATT AMPLIFIER. Ready made tested. 2-stage with triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer. Knobs, loudspeaker, valves ECL82, EZ80. Response 50-12,000 cps. Sensitivity 200mV. Post 5/-.

RC2 2 WATT AMPLIFIER with loudspeaker and valves UCL82 and UY85. Post 5/-.

R.C.S. TEAKWOOD BASE Ready cut out for mounting (state player make and model). 77/6

R.C.S. PLASTIC COVERS FOR ABOVE BASE. 77/6

Durable thin plastic, attractive appearance.

EMI PICK-UP ARM. Complete with mono cartridge 30/-.

EMI JUNIOR 4 SPEED RECORD PLAYER. Mains. £3

operated motor, turntable and pick up. Post 5/-.

HI-FI PICK UP CARTRIDGES

GP94 55/-, GP98 45/-; GP91 30/-; GP87 19.6, ACOS LP. only 10.6. All standard fixing complete with stylus.

### CRYSTAL MIKE INSERTS

1 1/2" dia. 6.6. ACOS 1 1/2" dia. 12.6. BM3, 1" dia. 9.6

### PORTABLE TELEAMPLIFIER

Portable mini p.a. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive rexine covered cabinet, size 12" x 9" x 4 1/2". with powerful 7" 4in. speaker and four transistor one watt power amplifier. Uses 2F9 battery. Brand new with famous makers' guarantee. 75/-.

Post 5/-.



### WEYRAD P50 - TRANSISTOR COILS

RAWF Ferrite Aerial 13/- Spare Cores 6d.

Osc. P50/1A 6/- Driver Trans. LFDT4 10/-

I.F. P50/2CC 470 kc 6/7 Printed Circuit, PCA1 10/-

3rd I.F. P50/3CC 6/7 J.B. Tuning Gank 11/-

P51/1 or P51 2 6/7 Weyrad Booklet 2/-

P50/3V 6/7 OPT1 11/-

Mullard Ferrite Rod 8 1/2 4/- 6 1/2 5/-

### VOLUME CONTROLS 80 Ohm Coax 9d. yd.

Long spindles, Midger. Size BRITISH AERIALITE

5 K. ohms to 2 Meg. LOG or AERIAL-AIR SPACED

LIN. L/S 3/-. D.P. 5/- 40 yd. 28/-; 60 yd. 40/-

STEREO L/S 1 1/2. D.P. 15/- FRINGE LOW LOSS 2/-

Edge 5K. S.P. Transistor, 5/-; Ideal 625 lines

### WIRE-WOUND 3-WATT POTS

Wire-wound 3-watt Small type with small knob. STANDARD SIZE POTS.

Values 10 Ohm to 30 K. 5/- LONG SPINDLE

Carbon 30 K to 2 meg. 8/- 10 OHMS to 100 K. 8/-

### VEROBOARD 0-15 MATRIX

21 5in. 3/8. 21 3 1/2in. 3/2. 31 3 1/2in. 3/8. 31 5in. 5/2.

EDGE CONNECTORS 16 way 5/-; 24 way 7/6.

PINS 36 per packet 3/4. FACE CUTTERS 7/6.

S.R.P. Board 0-15 MATRIX 2 1/2in. wide 6d. per lin.

3 1/2in. wide 9d. per lin.; 5in. wide 1 1/2 per lin. (up to 17in.).

S.R.P. undrilled 1/2in. Board 10 8in. 3/-.

### BLANK ALUMINIUM CHASSIS.

18 s.w.g. 2 1/2in. sides. 7 x 4 1/2. 6/-; 11 3in. 7/6; 11 7in. 9/6; 13 9in. 10.6; 15 14in. 15/-; 9 7 2in. 8.6; 14 11 2in. 14.6.

### ALUMINIUM PANELS 18 s.w.g. 12 12in. 6/6; 14 9in. 5/6; 12 8in. 4/6; 10 7in. 3/6; 8 6in. 2/6; 6 4in. 1/-.

### 1 1/2inch DIAMETER WAVE-CHANGE SWITCHES.

2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 4/6 each. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way. 1 water 12/-, 2 water 18/- 3 water 24/-, 4 water 30/-, 5 water 36/-, 6 water 42/-.

### TOGGLE SWITCHES.

sp. 2/6; sp. dt. 3/6; dp. 3/8; dp. dt. 4/6

### ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms Super Sensitive 35/-

LOW RESISTANCE HEADPHONES 3-5 ohms 39/6

DE LUKE STEREO HEADPHONES 8 ohms 85/-

### "THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER

47/6

Post 2/6

200/250 v. A.C. Leaflet S.A.E.

Minimum Post and Packing 2/6.



### GENERAL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE

for Mike, Tape, P.U., Guitar.

Battery 9-12v. or H.T. Line 200-300V. D.C. operation. Size 1 1/2" x 1 1/2" x 1". Response 25 cps. to 25 Kc/s. 26 db gain.

For use with valve or transistor equipment. Full instructions supplied. Brand new. 17/6 Post 2/6.

Guaranteed. Details S.A.E.

### NEW TUBULAR ELECTROLYTICS

CAN TYPES	11-	7-	11.6	3.6	9.6	9.6	9.6
2/350V .2/8	100/25V .2/8	16 + 16/500V	50/50V .2/8	50 + 50/350V	8 + 8/450V	3 + 3/250V	3 + 3/250V
4/350V .2/8	250/25V .2/8	60 + 100/350V	16/450V .2/8	8 + 16/450V	8 + 16/450V	8 + 16/450V	8 + 16/450V
8/450V .2/8	500/25V .2/8	100 + 100/350V	32/450V .2/8	3 + 16/450V	3 + 16/450V	3 + 16/450V	3 + 16/450V
16/450V .2/8	8 + 8/450V	3 + 3/250V	25/25V .2/8	16 + 16/450V	32 + 32/350V	32 + 32/350V	32 + 32/350V
50/50V .2/8	32 + 32/350V	100 + 50 + 50/350V	50/50V .2/8	32 + 32/350V	50/50V .2/8	50/50V .2/8	50/50V .2/8

### SUB-MIN. ELECTROLYTICS

2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/6.

CERAMIC 1pF to 0.01mF, 9d. Silver Mica 2 to 5000pF, 9d. PAPER 350V-0.1 9d. 0.5 2/6; 1mF 3/-; 2mF 150V 3/-.

50V-0.001 to 0.05 9d; 0.1 - 0.25 1/6; 0.47 5/-; 1.00V-0.001, 0.002, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1, 2.8.

SILVER MICA. Close tolerance 150, 200, 2-500pF 1/6; 500-2,200pF 2/-; 2,700-5,600pF 4/-; 6,800pF 4/-, mid 6/- each.

TWIN GANG. "0-0" 208pF + 178pF, 11/-; Slow motion drive 365pF + 385pF with 25pF + 25pF, 11/-; 500pF slow motion, standard 9/-; small 3-gang 500pF 22/-.

SHORT WAVE SINGLE. 25pF, 50pF, 11/-.

CHROME TELESCOPE AERIALS 23in. Swivel base 5/-.

TUNING MICA. Close tolerance 100pF, 300pF, 500pF, 7/- each.

TRIMMERS. Compression 3pF, 5pF, 10pF, 15pF, 20pF, 30pF, 40pF, 50pF, 60pF, 70pF, 80pF, 100pF, 150pF, 180pF, 250pF, 1/6; 800pF, 750pF, 2/-; 1000pF, 2.6.

RECTIFIERS CONTACT COOLED half wave 60mA 7/6; 85mA 9/6. SILICON BYZ13 10/-; BY100 10/-.

Full wave Bridge Rectifiers 75mA 10/-; 150mA 19/6.

EK-GOVT. RECTIFIERS 250v. 200mA 6/-.

NEON FLUO. INDICATORS 250v. AC Red or Amber 4/-.

RESISTORS. 250 ohms, 10 ohms to 10 meg. 10/-; 1w, 1/2w, 1w, 2w, 3w, 5w, 10w, 15w, 20w, 30w, 40w, 50w, 60w, 70w, 80w, 100w, 150w, 200w, 300w, 400w, 500w, 600w, 700w, 800w, 1000w, 1500w, 2000w, 3000w, 4000w, 5000w, 6000w, 7000w, 8000w, 10000w, 15000w, 20000w, 30000w, 40000w, 50000w, 60000w, 70000w, 80000w, 100000w, 150000w, 200000w, 300000w, 400000w, 500000w, 600000w, 700000w, 800000w, 1000000w.

HIGH STABILITY. 1w, 2%, 10 ohms to 10 meg. 2/-.

Ditto 5%. Preferred values 10 ohms to 22 meg. 9d.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100 K. 2/- each; 2 watt, 1 ohm to 8 ohms. 2/-.

### Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key

1in. 1/8in. 17/8 1 1/4in. 19/8 1 1/2in. 2 1/4in. 2 3/4in. 44/3

1in. 1/8in. 19/8 1 1/2in. 20/8 1 3/4in. 2 1/2in. 57/3

1in. 1/8in. 1 1/4in. 19/8 1 1/2in. 2 1/4in. 2 3/4in. 39/9 1in. sq. 36/6

### TRANSISTOR MAINS POWER PACKS. FULL WAVE

9 volt 50mA. Size 4: 2 1/2in. Metal case. 78/-

Crackle finish. Output terminals, On/off switch.

Half Wave 9 volt 50mA. Size 2: 1 1/2in. Snap terminals 36/-

### MAINS TRANSFORMERS

250-0-250 50 mA. 6.3 v. 2 amps, centre tapped 22/-

250-0-250 80 mA. 6.3 v. 4 amp. 28/-

250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-

350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-

300-0-300 v. 120 mA. 6.3 v. 4 a. C.T., 6.3 v. 2 a. 50/-

MINIATURE 200 v. 20 mA. 6.3 v. 1.5 a. 2 1/2in. 15/-

MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2in. 18/-

HEATER TRANS. 6.3 v. 1, 2, 3, 4, 5, 6.3 v. 1, 15/6

Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1, 15/6

GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5.

6.3, 8, 10, 12, 15, 18, 24 and 40 v. 2 a. 40, 45, 60, 38/-

1 amp, 8, 10, 12, 15, 18, 24, 30, 36, 40, 45, 60, 38/-

AUTO TRANSFORMERS 0-115-230 v. Input Output, 80w. 18/6; 150w. 38/-; 500w. £5; 1000w. £12.

### CHARGER TRANSFORMERS.

Input 200-250v for 6 or 12v., 1 amp, 24/-; 4 amp, 38/-.

### FULL WAVE BRIDGE CHARGER RECTIFIERS:

for 12v. outputs. 1 amp, 8/-; 2 amp, 11/-; 4 amp, 17/-.

### COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE 3/6.

OUTLET BOXES. SURFACE OR FLUSH 5/-.

### BALANCED TWIN FEEDERS 1/- yd. 80 ohms or 300 ohms.

JACK SOCKET Std. open-circuit 2.8, closed circuit 4.6;

Chrome Lead Socket 6. Phono Plug 1 1/2. Phono Socket 1/2.

JACK PLUGS Std. Chrome 2/6. Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/6; 5-pin 2/-.

DIN SOCKETS Lead 3-pin 3/6; 5-pin 5/-.

DIN PLUGS 3-pin 3/6; 5-pin 5/-.

VALVE HOLDERS. 1/-; CERAMIC 1/6; CANS 1/-.

### E.M.I. 13 1/2 x 8in. LOUSPEAKERS

With flared tweeter cone and ceramic magnet. 10 watts.

Bass res. 45-60 cps. 45/-

Flux 10,000 gauss.

State 3 or 8 or 15 ohm. Post 2/6 each

Also with twin tweeters. £4

With crossover. 10 watt.

State 3 or 8 or 15 ohm. Post 2/6 each

Recommended Teak Cabinet Size 16 10 9in. Post 2/6 £5

### MINI-MODULE LOUSPEAKER KIT

10 WATT 65/- CARRIAGES.

Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohms.

TEAK VENEERED BOOKSHELF ENCLOSURE. 18" x 10" x 9" in. Modern Scandinavian style. £5 Post 5/-.

fluted front design for Mini-Module.

### RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME.

337 WHITEHORSE ROAD, CROYDON

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665

### ALL MODELS "BAKER SPEAKERS" IN STOCK

## BAKER 12in MAJOR £9

30-14,500 c.p.s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 cps. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and £11.10 instructions.

### BAKER "GROUP SOUND" SPEAKERS - 8 or 15 ohm.

'Group 25'	'Group 35'	'Group 50'
12 watt £7	12 watt £9	15 watt £19
25 watt	35 watt	50 watt

### TEAK HI-FI SPEAKER CABINETS. Plated wood front.

For 10 or 12in round Loudspeaker ..... £9.0.0

For 13 8in or 8in round Loudspeaker ..... £5.0.0

For 15in, 18in or 9in round Loudspeaker ..... £4.0.0

LOUDSPEAKER CABINET WADDING 18in wide. 3/1-1t

### TWO-WAY CROSSOVER NETWORK 3,000 c/s

With variable tweeter attenuator giving accurate high low frequency balance. Mounted on panel 5 1/2in. x 4in. with control knob, tweeter and woofer leads and input terminals. Suitable for 3 to 8 ohm impedance. Post 2/-.

### Horn Tweeters 2-16kc/s. 10W 8 ohm or 15 ohm 29/6.

De Luxe Horn Tweeters 2-18 Kc/s, 15W, 8 ohm 59/6.

ELAC Moving Coil De Luxe Cone Tweeters 3 or 15 ohm 35/-.

### TWO-WAY 3000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 19/-.

SPECIAL OFFER: 80 ohm. 2 1/2in. dia.; 35 ohm. 3in. 25 ohm. 3in. dia.; 7 4in. 9 5in. 8 1/2in. 3in. dia.; 3 ohm. 2 1/2in. 5in. 3in. 7 4in. TYPE LOUSPEAKERS P.M. 3 OHMS. 6in 22/8; 8 5in. 25/-; 8 2 1/2in 18/-; 8in 35/-; 10 6in 38/-.

ELAC WOOFER. 8 watts max. 20-10,000 cps. 8 or 15 ohm. 36/-.

ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm 50/-.

RICHARD ALLAN TWIN CONE LOUSPEAKERS 8in or 10in or 12in. 3 or 15 ohm 38/-.

OUTPUT TRANS. EL84 etc. 5/- MIKE TRANS. 50-15/-.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. GOODMAN OUTPUT TRANSFORMER 4 watt push pull for 3, 8 and 15 ohms 17/6.

### VHF-FM TUNER FRONT END 88-108 Mc's

Transistor FM tuner oscillator and frequency changer printed circuit. Slow motion tuning gang condenser. Ready wired and tested including two transistors AF124 and AF125. A total of 28 components. Size 2 1/2 x 2 1/2in. Requires I.F. and Detector stages 10.7 Mc/9.9 Volt. Connection details supplied but we have no further information available.

45/- Post Free

### ALL EAGLE PRODUCTS SUPPLIED AT LOWEST PRICES. ILLUSTRATED EAGLE CATALOGUE 6/- Post free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 1/2 x 5 1/2 4in. £10

BARGAIN FM TUNER as above. Chassis only, less cabinet £7.10

FM STEREO MULTIPLEX ADAPTOR for above or general use. Ready made with 4 transistors, 6 diodes £5

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.10

### RADIO BOOKS (Postage 9d.)

Practical Radio Inside Out ..... 4/6

Practical Stereo Handbook ..... 3/6

Super-sensitive Transistor Pocket Radio ..... 3/6

Radio Valve Guide, Books 1, 2, 3, or 4 ea. 5/- No. 5 ea. 6/-

T.V. Fault Finding 405/625 lines ..... 10/-

Transistor Communication Sets ..... 6/-

Wireless World Radio Valve Data ..... 10/-


Transistor Circuits for Radio Controlled Models ..... 7/6


Coil Design and Construction ..... 5/-

22 Circuits for Micro-Alloy Transistors ..... 5/-

### E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. a pole 135mA. Spindle 0-187 x 0.75in. Size 3 1/2 x 2 1/2 x 2 1/2in. (Illustrated). Post 2/6. £25/6
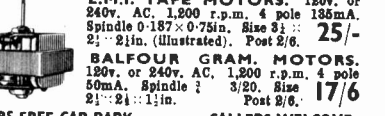
### BALFOUR GRAM. MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 x 3/32in. Size 2 1/2 x 2 1/2 x 1 1/2in. Post 2/6. £16/6



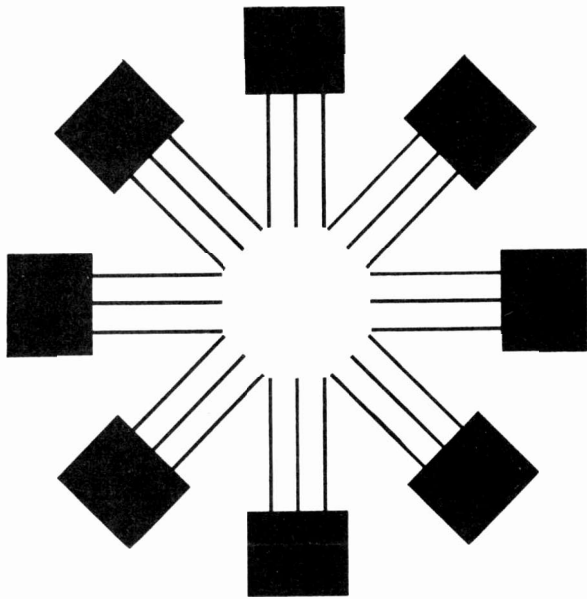

# FERRANTI

## leaders in advanced electronics

Ferranti offer a wide and varied range of circuits and silicon transistors including, at low prices plastic encapsulated types for high quality audio equipment.

Ferranti E-Line Transistors are specified in quantity by 'Practical Electronics' for their electronic organ, and for their new high fidelity amplifier which was demonstrated at the Audio Fair and featured in this issue.

Write for publication **ESB45070** on *E-Line Transistor Applications*

FERRANTI LIMITED,  
ELECTRONICS DEPARTMENT,  
GEM MILL, CHADDERTON,  
OLDHAM, LANCS.

Telephone: 061-624 6661. Telex: 668038

## R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, WELLFIELD RD., S.W.16

SPECIAL EXPRESS MAIL ORDER SERVICE

1N21	3/6	28308	9/-	BCY64	7/3	GET116	6/-	OC20	20/-
1N21B	5/-	28501	5/-	BCY60	19/-	GET118	4/-	OC22	8/-
1N23	4/-	28703	12/6	BCY70	6/-	GET119	4/-	OC23	8/6
1N85	17/6	3N143	19/-	BCZ11	6/-	GET120	6/6	OC24	9/-
1N253	10/-	A13759	4/-	BD121	19/-	GET587	8/6	OC25	7/6
1N256	10/-	AA129	5/-	BD123	22/6	GET872B	6/-	OC26	6/-
1N645	5/-	AAZ12	3/6	BD124	12/-	GET873	3/-	OC28	12/6
1N725A	4/-	AAZ13	3/-	BDY11	5/6	GET875	6/-	OC29	14/6
1N4007	4/6	AC107	5/6	BF115	5/6	GET880	8/9	OC30	6/-
18021	4/-	AC126	4/-	BF117	10/-	GET882	6/-	OC35	6/3
18113	3/-	AC127	5/-	BF167	6/6	GET885	10/-	OC36	8/6
18130	2/6	AC128	4/6	BF173	7/3	GEX35	4/6	OC38	10/3
18131	2/6	AC129	7/6	BF181	6/-	GEX44	1/6	OC41	4/6
2G220	12/6	AC187	11/-	BF184	7/6	GEX941	4/-	OC42	5/-
2G240	3/6	AC188	11/-	BF186	6/-	GJ3M	7/6	OC43	9/-
2G301	3/6	ACY17	4/6	BF194	5/3	GJ5M	7/6	OC44	4/-
2G306	8/6	ACY18	4/-	BF195	5/6	HG1005	10/-	OC45	3/3
2G371B	4/-	ACY19	5/-	BF196	5/6	MAT100	6/-	OC48	12/6
2G381A	4/6	ACY20	5/-	BF197	5/6	MAT101	8/3	OC59	17/-
2G403	10/-	ACY21	4/6	BFX12	5/6	MAT120	5/9	OC70	3/6
2G414	6/-	ACY22	4/-	BFX13	5/6	MAT121	6/-	OC71	3/-
2G417	6/-	ACY27	5/-	BFX29	12/-	MJ420	22/-	OC72	4/-
2N214	8/6	ACY28	4/-	BFX30	8/6	MJ421	22/-	OC73	7/3
2N404	6/-	ACY39	12/6	BFX35	19/6	NKT128	6/-	OC74	4/6
2N247	9/6	ACY40	4/-	BFX43	8/3	NKT135	5/3	OC75	4/6
2N697	4/-	ACY41	5/-	BFX44	8/3	NKT136	5/3	OC76	3/1
2N698	4/6	ACY44	7/6	BFX68	13/-	NKT210	6/6	OC77	8/-
2N706	3/-	AD140	8/-	BFX68A	13/6	NKT211	6/6	OC78	3/6
2N706A	3/6	AD149	12/-	BFX85	10/-	NKT212	5/4	OC78D	3/3
2N708	4/-	AD160	10/-	BFX86	9/6	NKT213	4/4	OC79	5/-
2N709	12/6	AD181	7/6	BFX87	9/6	NKT214	6/4	OC81	4/-
2N711	7/6	AF106	10/6	BFY20	12/-	NKT215	4/6	OC81D	3/-
2N987	10/6	AF114	5/-	BFY21	8/6	NKT216	5/4	OC81DM	3/-
2N990	6/6	AF115	5/9	BFY24	9/-	NKT217	8/4	OC81M	22/6
2N1091	6/6	AF116	4/6	BFY41	9/6	NKT219	6/6	OC82	3/-
2N1131	8/6	AF116	4/6	BFY43	12/6	NKT221	5/6	OC82D	3/-
2N1132	7/6	AF117	4/6	BFY50	5/-	NKT223	6/6	OC83	4/6
2N1302	4/-	AF118	12/-	BFY51	6/-	NKT224	4/9	OC84	4/9
2N1303	4/3	AF119	5/-	BFY53	5/6	NKT225	4/9	OC114	7/6
2N1304	4/9	AF124	5/-	BFY77	12/-	NKT227	5/9	OC122	12/6
2N1305	5/-	AF126	5/-	BFY90	12/6	NKT229	5/9	OC123	4/4
2N1306	5/-	AF127	4/6	BSX27	10/-	NKT237	7/9	OC139	7/6
2N1307	5/-	AF139	7/6	BSX60	18/6	NKT238	5/9	OC141	6/6
2N1308	6/-	AF178	12/6	BSX81	12/-	NKT240	6/6	OC141	12/3
2N1309	6/-	AF179	12/6	BSY26	3/6	NKT241	6/6	OC169	6/-
2N1420	7/3	AF180	12/-	BSY27	4/-	NKT251	4/9	OC170	5/6
2N1507	5/8	AF181	8/-	BSY51	10/-	NKT261	4/9	OC171	6/-
2N1626	7/6	AF186	11/-	BSY78	9/3	NKT274	5/-	OC172	7/-
2N1909	4/5	AFY19	22/6	BSY79	9/3	NKT275	5/-	OC200	5/6
2N2147	16/6	AFZ11	6/-	BSY82	10/-	NKT277	4/9	OC201	8/6
2N2148	12/-	AFZ12	6/6	BSY83	11/-	NKT403	9/9	OC202	8/6
2N2160	14/-	AFZ21	6/6	BSY84	12/-	NKT404	12/6	OC203	6/6
2N2193	5/6	ASY26	5/6	BY100	4/6	NKT713	7/6	OC204	5/6
2N2287	20/6	ASY27	7/6	BY213	5/-	NKT773	6/-	OC205	9/-
2N2297	6/-	ASY28	5/3	BY211	5/-	NKT777	7/6	OC206	14/6
2N2369A	6/-	ASY29	6/-	BYZ11	7/6	NKT80113	7/6	OC207	7/6
2N2410	10/6	ASY36	5/6	BYZ12	6/-	078B	20/-	OC450	6/-
2N2411	6/6	ASY50	5/-	BYZ14	27/6	OA6	3/6	OC470	6/-
2N2412	6/6	ASY51	7/6	BYZ16	17/6	OA10	3/1	OCP71	20/-
2N2483	5/6	ASY63	4/9	C111	13/-	OA47	2/-	PS144	4/-
2N2484	7/6	ASY64	4/9	C20A	12/6	OA70	1/6	S19T	6/-
2N2846	11/6	ASY82	5/-	CR81/05	5/-	OA71	2/-	SAC40	6/-
2N2636	5/3	ASY86	6/6	CS4B	37/6	OA73	2/-	SFT308	7/6
2N2904	7/6	ASZ17	13/6	CS10B	67/6	OA74	4/-	SJ052F	7/6
2N2904A	8/-	ASZ20	7/3	CV101	5/-	OA79	1/9	ST722A	5/-
2N2906	8/-	ASZ21	7/6	CV253	20/-	OA81	1/8	ST7231	12/6
2N2907	7/6	ASZ23	19/6	CV254	20/-	OA82	2/-	SX68	4/6
2N2926	3/-	AU110	19/6	CV2184	32/6	OA86	4/6	SX68UH	4/6
2N2924	4/6	BC107	3/6	CV2185	32/6	OA88	4/6	SX631	7/6
2N3014	7/6	BC108	3/6	CV2229	10/6	OA91	1/6	SX631UC	10/-
2N3054	11/-	BC109	3/6	CV2923	4/6	OA95	1/6	SX680T	4/-
2N3055	14/6	BC113	6/3	CV4073	3/6	OA202	2/-	SX753	15/-
2N3705	4/6	BC115	6/6	CV4074	3/6	OA210	6/6	SZ33C	12/-
2N3706	4/6	BC116	11/6	CV4075	3/6	OA211	10/-	V15/30P	15/-
2N3707	4/-	BC118	6/6	CV5108	80/-	OA220	11/-	V30/201P	9/6
2N3708	4/-	BC121	4/-	CV7183	30/-	OA2202	7/6	XA122	6/-
2N3709	4/-	BC125	13/6	CV7312	10/-	OA2203	8/-	XA124	4/-
2N3710	4/-	BC126	13/-	CV7324	10/-	OA2204	8/-	XA142	5/-
2N3819	8/-	BC140	11/-	CV7341	6/-	OA2207	7/6	XA143	5/-
2N3820	20/-	BC145	15/-	CV7347	4/-	OA2208	6/6	XA162	5/-
2N3823	17/-	BC147	4/9	CV7351	12/6	OA2210	6/6	XA162	8/6
2N3900	10/6	BC148	4/6	D246	7/6	OA2212	9/6	XB101	8/6
2N3900A	11/-	BC149	5/-	DD006	7/6	OA2214	9/6	XB105	6/6
2N5027	10/6	BC157	4/-	DD007	8/-	OA2216	9/6	XB518	6/-
2N5028	11/6	BC160	12/6	DD008	7/6	OA2218	9/6	Z2A82CR	5/-
2N5307	7/6	BCY31	7/6	GD3	6/6	OA2222	9/6	ZR24	12/6
2N5308	7/6	BCY32	7/6	GD4	7/-	OA2224	9/6	ZS32A	6/-
2N5309	11/-	BCY33	5/6	GD5	6/6	OA2241	7/6	ZT21	6/-
2N5005	14/-	BCY34	5/-	GD6	6/-	OA2242	9/6	ZT43	5/-
28013	15/-	BCY38	5/6	GD8	5/-	OA2246	4/6		
28013A	16/6	BCY39	7/-	GET102	5/-	OC16	15/-		
28301	12/6	BCY40	7/6	GET113	5/-	OC16T	16/6		
28304	9/-	BCY42	3/-	GET114	4/-	OC19	8/6		

TRANSISTORS (POSTAGE, PACKING & INSURANCE) 1/3 PER ORDER

SEND S.A.E. FOR LIST OF 3,000 TYPES—  
VALVES, TUBES AND TRANSISTORS

TERMS

C.W.O.  
no C.O.D.

OPEN DAILY TO CALLERS

Mon.-Sat. 9 a.m.-5.30 p.m. Closed Sat. 1.30 p.m.-2.30 p.m.  
Tel. 01-769 0199/1649

Construction of the matrix is given in Fig. 4. Two pieces of Veroboard are mounted back to back with the strips running in opposite directions. Suitable  $1\frac{1}{2}$  inch bolts provide rigidity and correct spacing. The diodes are then mounted between the boards with their positive ends all the same way up. Twelve wires are taken off to switch S1a and ten to switch S2b. If the circuit does not work correctly, simply reverse the wires to the wipers. Points Y and W in Figs. 2 and 3 are connected to their respective letter. Points X in Figs. 2 and 3 are points at which it is necessary to affect a change when changing over from this game to the later addition. They are best left as they are for the time being, but reference will be made to them later.

## CONSTRUCTION

In the prototype, aluminium sheet was cut and bent-up as per Fig. 5 to form the chassis but as nothing is critical in this layout, the constructor may adopt any layout or method of construction that he fancies.

Holes for controls and lamp apertures were cut with a chassis punch before the chassis was bent and pop rivetted. Details of the lamp mountings are given in Fig. 6, which also shows how the numbers—black Letraset on cellophane—were projected up onto the map. Fig. 7 gives details of a simple battery holder bent up out of aluminium and screwed to the chassis.

When complete, the aluminium was given a coat of navy-blue paint and the Letraset co-ordinates added to match the knob positions on all eight knobs.

## THE MAP

Map details are given in Fig. 1; a square of good quality card  $7\text{in} \times 7\text{in}$  is the base. Three holes were cut with the chassis punch to match the lamp holes in the aluminium, and then the map marked out on paper, was stuck on leaving a  $\frac{1}{2}$  inch margin all round. In the prototype a pleasing effect was gained by using sticky coloured paper—blue for the sea and green for the land—but it might just as well be drawn on cartridge paper. The squares are hatched in with a mapping pen. Note that the lettering round the edge is designed to be read from both sides.

When the map is complete it can be covered over with clear Fablon an inch oversize all round, the excess being carefully wrapped underneath. A strip of cellophane is stuck over the holes in the aluminium, and large Letraset numerals applied to it in the centre of each hole—number 1 for LP1, 2 for LP2 and 3 for LP3. Finally the map was mounted on top, using small self-tapping screws. It will thus be seen that over each lamp is a hole in the aluminium and card, a strip of cellophane with a black numeral, and the thin map protected by clear Fablon. When the lamp glows, a circle of light appears through the map with a number in it.

## WIRING UP

When the case is complete and the controls mounted, wiring may begin. Complete the wiring in Fig. 2 first. Provided that care is taken correctly to identify the wiper and the first tag of each switch, no trouble should be encountered, but the work is greatly facilitated by the use of colour-coded twelve-core cable, if any is available.

Test the wiring before proceeding to Figs. 3 and 4. When the diode matrix is first assembled, four holes may be made under the map. Short bolts through

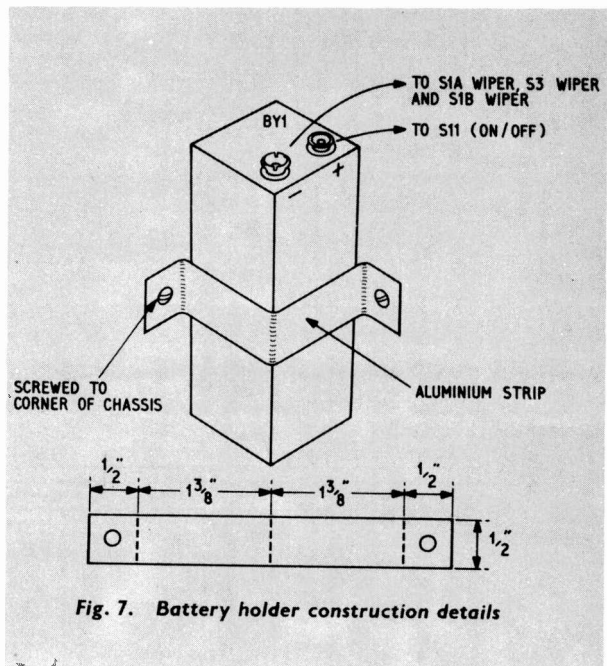


Fig. 7. Battery holder construction details

these, with stand-off spacers will securely hold the matrix block in position. An on/off switch S11 may be placed at one side of the game.

## VARIATIONS

When the above-described very simple (and infuriating!) game has been mastered, any or all of the following variations may be tried.

1. Each player is "Red" in turn. He keeps a score for the opponent to beat.

2. For every move that the raider scores, he rolls a dice. The result indicates the number or tonnage of shipping sunk that day.

3. If a 5 or 6 is rolled, one of the stricken merchant ships manages to radio her position before she goes down. The raider must reveal his whereabouts.

4. The raider must make contact with the supply ship every ten moves or less. Failure to do so means that she runs out of supplies and scuttles herself.

5. Between contacts, the supply ship must call at any neutral port, where her presence is revealed by "Blue" agents.

6. Any ship entering a square which is crossed by a section of coast is spotted by enemy agents and must announce her position.

7. When contact between enemy ships is made, a dice is rolled. The result indicates the number of daylight hours left and also the number of attempts the "Blue" player has of rolling a six. If he fails, the "Red" may slip away in the gathering dusk.

8. An arbitrary points value is awarded to each ship, say 5 to the supply ship, 10 to the raider, 15 to the destroyer and 25 to the cruiser. This is the accumulative score to be made against it before it is sunk. When contact is made, a dice is rolled for hours of daylight. Each player rolls that number of dice to score against the other. If the "Red" is still afloat he may slip away to continue his deprivations elsewhere.



Another game entitled "Submarine Chaser" which can be added to the above unit, will be described in a future issue.

# MAKING THE MOST OF LOGIC IC's

PART SIX—By R. W. GOLES

## TTL BINARY ADDER

FROM the details given in Part 5 on TTL gates it should be possible to use them to practical advantage. This article describes a simple binary adder as a forerunner to their use in other designs.

As an example, let us investigate the logic required to produce a circuit which will add together two binary numbers, and any carry figure which may have been generated in previous addition, with the result that a sum and a carry output is produced.

### BOOLEAN ALGEBRA

In has been the policy in this series to assume that the reader has a knowledge of the binary number system, but not necessarily a wide knowledge of logic simplification, or Boolean algebra.

Boolean algebra is not the same as ordinary algebra, but it is easy to understand if denary counting is temporarily ignored. It is based on the processing of information in two-digit code, 0 and 1. In the counting sequence of denary calculation the next figure after 9 is 0. So in binary code, the next figure after 1 is 0 with a carry 1 passed to the next column on the left. Bearing in mind that the solution to be presented could be reduced in its complexity by the proper application of Boolean Algebra, let us see just how simple it is to work out gate arrangements for any desired result.

The first thing to do is draw up a table of all the possible combinations of inputs which will be presented to the adder. As the inputs consist of three separate digits, A, B, and the "carry" from a previous addition, C, there can be a total of eight combinations. Following the simple rules for binary addition we can then add to the table the outputs which each of these combinations will be required to produce.

Remembering that 0 plus 0 gives a sum output of 0, 0 plus 1 gives a sum output of 1, and 1 plus 1 gives a 0 output and a carry 1 output, the table so derived will be as shown in Fig. 6.1. To produce a logic 1 output when a particular input combination exists, it is simply

necessary to connect the true inputs to a 3-input gate, in this case a TTL NAND gate which will then produce an output only for this combination.

Notice that the gate produces a logic 1 output when its input conditions are satisfied, but this is a negative logic 1, because of the inverting action of a NAND gate. Several of these combinations give a sum output, several give a carry output, and one of them gives both.

It is not necessary however, for all of the sum or carry combinations to be present at the same time (this is impossible anyway) so we can write that for a sum output, combinations 2 or 3 or 5 or 8 must be present, otherwise there will be no sum output. The same principle applies to the carry output, and the conditions are 4 or 6 or 7 or 8.

### NEGATIVE LOGIC NAND

To give this result, we need two 4-input OR gates, one for sum and one for carry. Now a TTL NAND gate fed with negative logic inputs behaves as a NOR gate (this principle was explained in the article on RTL). If the shift register used provides complementary outputs, these gates will not be necessary.

The operation in this configuration is quite simple. Before the first clock pulse arrives, the first set of digits are already present at the inputs of the adder, which will therefore have produced sum and carry outputs. These will be waiting to be clocked into their respective stores.

Assume that the sum output is connected to a third shift register, which will store the answer to the sum of the two words, and is consequently connected to the common clock line.

At this stage the carry store will be empty (i.e. it will contain a logic 0) as there have been no previous additions. When the clock pulse arrives, several things will happen at once:

1. The sum output will be stored in the third register.

	INPUTS			OUTPUTS	
	A	B	CARRY IN C	SUM	CARRY OUT
1	0	0	0	0	0
2	1	0	0	1	0
3	0	1	0	1	0
4	1	1	0	0	1
5	0	0	1	1	0
6	1	0	1	0	1
7	0	1	1	0	1
8	1	1	1	1	1

Fig. 6.1. Truth table requirement for a binary full adder. Sum output should be produced when inputs are (A, B, C) or (A, B, C) or (A, B, C) or (A, B, C). Carry output should be produced when inputs are (A, B, C) or (A, B, C) or (A, B, C) or (A, B, C)

# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service


## NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7" 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9" 7" 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 5/- (FREE with parts).

Total building costs **£6.19.6** P. & P. 7/6



## roamer seven mk IV

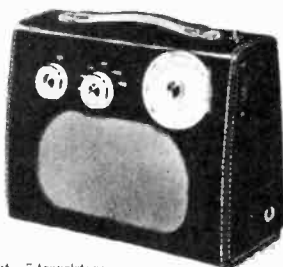


7 FULLY TUNABLE WAVE BANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7" 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9" 7" 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts).

Total building costs **£5.19.6** P. & P. 7/6 Personal Earpiece with switched socket for private listening, 5/- extra.

## NEW!
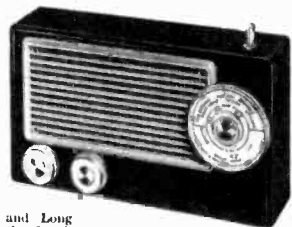
### transeight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER




Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9" 5 1/2" 2 1/2in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts).

Total building costs **89/6** P. & P. 5/6 Earpiece with switched socket for private listening 5/- extra.
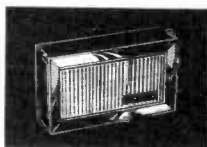
## pocket five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND  
PORTABLE  
WITH SPEAKER



Attractive black and gold case. Size 5 1/2" 3 1/2in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages 5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs **44/6** P. & P. 3/6

## transona five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND  
PORTABLE  
WITH SPEAKER




Attractive case with red speaker grille. Size 6 1/2" 4 1/2in. 1 1/2in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs **47/6** P. & P. 3/9
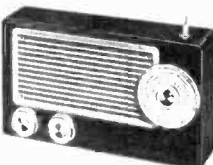
## IMPROVED MODEL! roamer six

SIX WAVEBAND PORTABLE  
WITH 3in. SPEAKER



Attractive black case with red grille and cream knobs and dial polished brass inserts. Size 9" 5 1/2" 2 1/2in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. (Carrying strap 2/6 extra). Easy build plans and parts price list 2/- (FREE with parts)

Total building costs **79/6** P. & P. 4/6

## RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked  
 ROAMER EIGHT  ROAMER SEVEN   
 TRANSEIGHT  POCKET FIVE   
 TRANSONA FIVE  ROAMER SIX

Parts price list and plans for.....

Name.....

Address.....

\* Callers side entrance Stylo Shoe Shop  
 \* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

PE24



# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

AC107	3/-	OC170	4/6
AC126	2/6	OC171	4/6
AC127	3/6	OC200	5/-
AC128	2/6	OC201	2/6
AC176	5/-	2G301	2/6
AF239	3/-	2G303	2/6
AF186	7/6	2N711	10/-
AF139	10/-	2N1302-3	4/-
BC154	7/6	2N1304-5	5/-
BC171 = BC107	2/6	2N1306-7	6/-
BC172 = BC108	2/6	2N1308-9	7/-
BF194	2/6	2N3819FET	9/-
BF274	3/-		
BSY50	4/-	<b>Power Transistors</b>	
BSY25	7/6	OC20	10/-
BSY26	2/6	OC23	6/-
BSY27	2/6	OC25	5/-
BSY28	2/6	OC26	6/-
BSY29	2/6	OC28	5/-
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/6
OC44	2/6	AD149	6/-
OC45	2/6	AUY10	25/-
OC71	2/6	2S034	5/-
OC72	2/6	2N3055	12/6
OC73	3/6	<b>Diodes</b>	
OC81	2/6	AA42	2/-
OC81D	2/6	OA95	2/-
OC83	4/-	OA79	1/9
OC139	2/6	OA81	1/9
OC140	3/6	IN914	1/6

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

## CLEARANCE LINES

DON'T MISS THIS LAST CHANCE ONLY A FEW LEFT

### UHF/VHF T.V. TUNER UNITS

TU.2 CONTAINING 2 AF186's & 2 AF178's PRICE 10/-

TU.3 CONTAINING 2 AF186's & 2 AF178's PLUS WAVEBAND SLIDER SWITCH P. & P. 2/6 EACH UNIT PRICE 12/6

All the units have many other components, e.g. Capacitors, Resistors, Coils and tuning condensers, etc. Although these are manufacturers rejects they are not beyond repair as has been proven by many of our customers.

**ALL TUNER UNITS ARE SUPPLIED WITH CONNECTION DATA**

### COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25 kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each post and packing 4/6

### SPECIAL LINE

1 AMP Bridge rectifiers..... 1 Square 100 PIV. = 5/- 400 PIV. = 6/6 800 PIV. = 8/-

### 1970 MULLARD DATA BOOKS

Data and equivalents on semiconductors, valves and tubes..... PRICE 4/- P. & P. 6d.

### I.C. PANELS—FEW ONLY—50/- EACH

Each panel contains:—  
16-Dual 2 1/2 P NOR gates MC714G. 1-Dual 3 1/2 P NOR gate MC715G. 1-J.K. flip flop MC723G. 29-BSY95A or 2S95A and 1 V405A transistors.

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output. Pair	10/-
B81	10	Reed Switches, mixed types large and small	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400 Ω Dark 1M Ω	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45	10/-
B92	4	NPN Sil. Trans. AO6 = BSX20, 2N2369 500 MHz, 360mW	10/-
B93	5	GET113 Trans. equiv. to ACY17-21 PNP Germ.	10/-
B99	200	Mixed Capacitors. Postage 2/6. Approx. quantity, counted by weight	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-
H4	250	Mixed Resistors. Postage 2/- Approx. quantity, counted by weight	10/-
H7	40	Wirewound Resistors. Mixed types and values. Postage 1/6	10/-
H8	4	BY127 Sil. Recs 1000 PIV. 1 amp. plastic	10/-
H9	2	OCF71 Light Sensitive Photo Transistor	10/-

## RETURN OF THE UNBEATABLE P.I PAK.

### NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS, IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.I ONLY 10/- 2/- P. & P. on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car.

**20/- each**

FREE CATALOGUE AND LISTS for:—

**ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART**

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

**P.O. RELAYS 8 FOR 20/-**  
Various Contacts and Coil Resistances. No individual selection. Post & Packing 5/-

## SPECIAL OFFER

**GERMANIUM BRIDGE RECTIFIERS  
GEX 541 FINNED**

SINGLE PHASE 12 Amp. 48 Volts  
THREE PHASE 18 Amp. 74 Volts  
Ideal for Battery Chargers or Power Units

Offered at fraction of makers' cost Only 12/6 Each Post & Packing 2/6

## NEW UNMARKED UNTESTED PAKS

B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can	10/-
B83	200	Trans. manufacturer's rejects all types NPN, PNP, Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	10/-
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes Mixed Voltages	10/-
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	10/-
H10	25	Mixed volts, 1 1/2 watt Zeners. Top hat type	10/-
H11	30	MAT Series "alloy" pnp Transistors	10/-
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	10/-
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	10/-
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts	10/-

**FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS**

# BI-PRE-PAK LTD

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

- The carry output will be stored in the carry store.
- The word in both register A and B will be shifted one place to the right, therefore a new pair of digits will be supplied to the adder.
- As a consequence of operation 2, a new carry input will also be presented to the adder inputs.

The word "new" used in the previous list does not imply that the digits supplied to the adder after the clock pulse are necessarily different from those preceding them; this depends on the contents of the shift registers of course.

The above operations will be repeated for every clock pulse; the total number of clock pulses depending on the word length stored in the shift registers. At the end of the series of clock pulses the sum of the two words will be stored in the third register, and registers A and B will be empty. As the outputs from the gates which detect the eight possible combinations are in the negative logic convention, we can use a NAND gate to provide the required NOR functions.

If the use of the dual polarity logic system is a little confusing, just try the logic diagram shown in Fig. 6.2 with voltage levels, imagining the gate circuitry inserted instead of the logic symbols. Positive levels will represent a 1 at the inputs to the three input gates, zero levels will represent a 1 at their outputs. Zero voltages represent 1 at the inputs of the 4-input gates, and positive voltages will represent 1 at their outputs.

## SERIAL ADDITION

The dual polarity logic system is just a way of describing the action, the electrical circuit action is always the same.

The logic diagram shows the full adder connected to perform "serial addition". The digits to be summed are fed to the adder one pair at a time from two shift registers, A and B, which could contain any number of separate digits, the total number in each register being described as the "word-length".

The carry input is fed into the adder from a carry store, which is simply a clocked bistable used to provide a delay of one clock period. The input to the carry store is provided by the carry output of the adder, and as the bistable used in this position may be any one of the various TTL flip-flops, the precise input terminal has not been named.

The adder requires seven 3-input gates which are available three in a package. Two spare gates are left in the three packages necessary, but these can be put to good use as inverters of the shift register outputs as shown. Remember that both true and inverted inputs to the adder are needed, so these spare gates serve the purpose admirably.

There are a number of disadvantages in the method of serial addition, when used in a high speed computer, because it is quite a slow process, requiring  $N$  shift pulse periods to complete the process.

Using the adder we have designed, it is possible to build a system which will add two words together in only one clock period, but to achieve this it is necessary to use a separate adder circuit for each bit of the word. The basic principle of this sort of addition is shown in Fig. 6.3.

The four adders each have an exclusive pair of digits supplied to them, one from each register, the carry output from the first adder is connected directly to the carry input of the next and so on, no carry store being necessary. Remember that a TTL gate has a specified propagation delay, so it will take a finite time for the final sum outputs to become established.

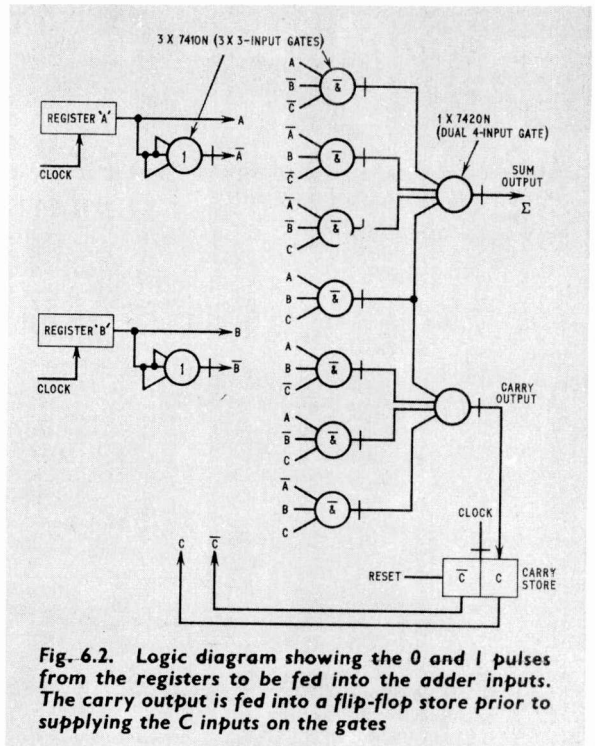


Fig. 6.2. Logic diagram showing the 0 and 1 pulses from the registers to be fed into the adder inputs. The carry output is fed into a flip-flop store prior to supplying the C inputs on the gates

The limiting factor here is the fact that the carry output from the first adder can affect the sum output of the final adder. The time taken for the carry to propagate through the four adders can be many times (eight to be exact) the delay of a single gate. With a longer word length the delay will of course be correspondingly longer.

It is obvious that this method is much faster than serial addition. Not surprisingly, the name used for this system is "parallel addition".

Having now gained some confidence in the use of TTL gates, it is now time to proceed to the perhaps more interesting subject of flip-flops, and all their diverse uses.

## DEVICE IDENTIFICATION

Logic integrated circuits are coded differently by the various manufacturers, even though many of them are electrically identical. The TTL family is probably the worst in this respect, because so many manufacturers,

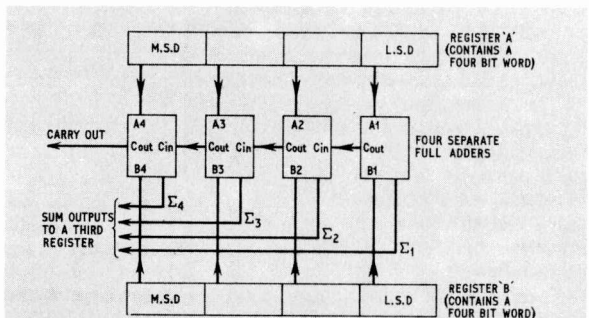


Fig. 6.3. System for adding two words together, each supplied from a 4-bit (binary digit) register. A full adder is used for each bit. L.S.D. is the least significant digit and M.S.D. is the most significant digit

Table 6.1. TTL PACKAGES

Texas Instruments	Mullard	A.E.I.
7400	FJH131	880
7401	FJH231	
7402	FJH221	
7410	FJH121	870
7420	FJH111	816
7430	FJH101	808
7440	FJH141	855
7441	FJL101	
7450	FJH151	
7451	FJH161	840
7453	FJH171	
7454	FJH181	
7460	FJY101	806
7470	FJJ101	
7472	FJJ111	825
7473	FJJ121	
7474	FJJ131	These A.E.I. devices are shown as nearest equivalents, there may be some pin differences between the Texas 74 and Mullard FJ ranges.
7475	FJJ181	
7476	FJJ191	
7490	FJJ141	
7492	FJJ251	
7493	FJJ211	

Table 6.2. LOGIC IC AVAILABILITY

SUPPLIER	RTL	DTL	TTL
Bi-Pak Ltd.	Fairchild TO-5 epoxy resin range ML914 to ML923 15 to 55°C	Motorola DIL plastic range MC844P to MC862P 0 to 70°C	Full range of 74 series devices including MSI in plastic DIL SN7400N to SN7496 0 to 70°C and fall-outs
A. Marshall Ltd.	Motorola DIL plastic range MC724P to MC799P Fairchild ML900 Series 15 to 55°C	Mullard FC series	Full range of Mullard FJ and Texas 74 series in plastic DIL 0 to 70°C
Bi-Pre-Pak Ltd.		A.E.I. DIL plastic range SP616A to ST680A. Mixed temperature ranges	A.E.I. DIL and Flat Pack. SP806A to NE880J. Mixed temperature ranges
L.S.T. Electronic Components Ltd.	Fairchild TO-5 epoxy range ML914 to ML923 15 to 55°C	Also R.C.A., Mullard, General Electric, and Texas types available	

Logic ICs are available from other sources and readers are recommended to study the advertisements for more details.

both in Europe and the U.S.A., have their own range of these devices, in some cases using an individual coding system, even though their circuits are produced under licensing agreements with the two or three design originating companies who hold the patents.

Fortunately, however, even in the most complex type number, there is generally a central group of two or three figures which tells us all we need to know to identify a particular logic circuit, all the other letter and figure prefixes and suffixes giving ancillary information about operating temperature range, package outline, and package material. It is usually only this ancillary coding which varies depending on the manufacturer.

To take a notorious example, the DTL flip-flop, used in the slide projector timer described in the October issue, could have been specified as either U6A994559X (Fairchild), or MC845P (Motorola), or 9945 (S.G.S.), or MIC 945 (S.T.C.). These devices are electrically identical, the only difference being in the type of package material used, for example, ceramic or plastic.

The important figure group in this example is 845/945, which not only tells us that the devices are interchangeable, but also that they are in different package materials, the other information being irrelevant for our purposes. Even TTL devices can be identified in this simple way, though in this case there are three or four basic systems to which the search can be narrowed, after which a reference table is necessary.

Such a cross reference guide is given in Table 6.1; although by no means complete, it does list the TTL devices currently advertised.

### REJECT DEVICES

Identifying reject i.c.s which are not marked in any way is well nigh impossible and without identification

the devices are useless. All is not lost, however, because manufacturers usually stamp the underside of the package with the basic code group referred to above before they test them, making the task quite simple.

An SN7474N fallout from the Bi-Pak range, for instance, is marked "74", and an SN7490N from the same range is marked "90", thus conveying all the information necessary, and enabling the experimenter to re-test them to discover their usefulness.

It is surprising, in fact, just how many of these reject circuits appear to be fully serviceable when tested. Of course, even those which have faults often contain other logic functions which are still useable, and are ideal for experimenters on a low budget, if he can identify the useful part of the package. One example is where one gate of a four gate package may be faulty, the other three may still be useable.

Many advertisers in this magazine now supply logic i.c.s originating from a variety of manufacturers, in either fully tested or fall-out form, and Table 6.2 will enable prospective constructors to decide just which devices, of those available, will suit their needs best.

One last word of advice, learn to recognise by the number codes which types are manufacturer's fall-outs. Remember also that these packages do not quite come up to the rigid industrial specifications laid down, although they may be put to some use by the experimenter, and may be fair value for money.

Next month's article will look into TTL flip-flops in more detail and describe their use in counting circuits and as shift registers and stores. This part will be particularly useful to readers interested in the Digital Clock, as will the following article on medium scale integration.

# COMPLETE STEREO SYSTEM

FOR ONLY

# 39 GNS

CARRIAGE 35/-



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6. Carr. 7/6). Now Available MATCHING F.M. TUNER 21gns.

## PREMIER STEREO SYSTEM "TWO"

As system "ONE" above but with Garrard SP25.


PREMIER PRICE 45 Gns. Carr. 35/-

## AURIGA 8 WAVEBAND TRANSISTOR PORTABLE

Covers Medium, Long and six Short Waves and includes many features not normally found in this price range. Ten transistors and two diodes. Push-Pull output. Press-button dial illumination.

Volume, tone, tuning and wavechange controls. Telescopic aerial. Uses 6 x 1 1/2 V batteries. Sockets for external batteries, tape recorder and aerial. Elegant black and chrome cabinet. Size 11in x 3 1/2in x 7 1/2in.

PREMIER PRICE 15 Gns. Carr. 7/6

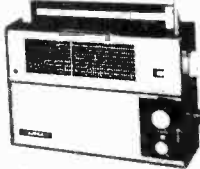

## TELETON SAQ203E STEREO AMPLIFIER



A small but powerful amplifier designed for stereo hi-fi reproduction. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble, Stereo/Mono slide switch. Stereo headphone socket. Attractive oiled walnut cabinet with brushed aluminium front panel. List Price £28.7.0.

PREMIER PRICE 22 Gns. Carr. 10/-

## PREMIER STEREO SYSTEM "FOUR"

Teleton SAQ203E Amplifier (as above) £23.2.0  
Garrard SP25 £11.19.6  
Shure M3D £6.19.6  
Teak base and cover £5.10.0  
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers £26.5.0

Total cost if purchased separately £73.16.0

PREMIER PRICE 65 GNS. Carr. 35/-

## VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 1/2 x 3 1/2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phonoplugs output. Attractive teak wood grain finish case. Mono Model 59/6 Stereo Model 69/6 Carr. 2/6



## TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc. 65/- P. & P. Carr. 4/-



## E.M.I. 13x8in. HI-FI SPEAKERS



Fitted two 2 1/2 in tweeters and crossover network. Available with 8 or 15 ohm impedance. Handling capacity 10W. Brand new.

79/6 Carr. 7/6



## HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2 in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedances. Complete with 6ft. lead and stereo jack plug. 49/6 Carr. 2/-

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6  
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/6  
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-

## SPECIAL OFFER!



Garrard SP25 Mk. II Single Record Player. Fitted Goldring 850 Magnetic Stereo Cartridge. Complete in Teak Plinth with Rigid Perspex Cover. Total list Price over £24.  
PREMIER PRICE 18 Gns. Carr. 10/-



## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	5/6	LP6 5 1/2" 1200' P.V.C.	12/6
TT3 3" 450' POLYESTER	7/6	DT6 5 1/2" 1800' POLYESTER	22/6
DT3 3 1/2" 600' POLYESTER	11/6	TT6 5 1/2" 2400' POLYESTER	27/6
SP5 5" 600' P.V.C.	8/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	LP7 7" 1800' P.V.C.	15/-
DT5 5" 1200' POLYESTER	15/-	DT7 7" 2400' POLYESTER	25/-
		TT7 7" 3600' POLYESTER	50/-

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/9  
Post and Packing 3" 1/-, 5", 5 1/2", 1/6, 7" 2/- (3 reels and over Post Free.)



## "WELLER EXPERT" SOLDER GUN

Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat 100/140 watt. 240 volt A.C. 67/6 Carr. 2/-

"Weller Marksman" Soldering Iron Lightweight, 3/4" pencil bit. 25 watt. 240 volt A.C. 31/6, Carr. 2/-

## POCKET SIZE MULTI-TESTER

With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 19 Ranges: 0-5-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-50µA-2.5mA-250mA D.C. 0-6000 ohms-6 megohms, 10µ µ-0-001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. 44.19.6 Carr. 3/6

## MIDLAND CASSETTE TAPE RECORDER 12-115

Solid state incorporating piano key controls for trouble-free 2-track recording. Inputs for mike and aux. Earphone socket. Complete with batteries and earpiece. Size 10 1/2 in x 5 1/2 in x 2 1/2 in.  
PREMIER EXCLUSIVE: £16.10.0 Carr. 7/6



## TAPE CASSETTES

C60 (60 min.) 7/6 3 for 21/-  
C90 (90 min.) 12/6 3 for 36/-  
C120 (120 min.) 17/6 3 for 51/-  
Carr. 1/-

All cassettes can be supplied with library cases at 6d extra each.

# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



# Mullard

## TECHNICAL BOOKS

### Power Engineering using Thyristors

Part 1. Techniques of  
Thyristor Power Control

A new book to bridge the gap between electrical power engineering and electronics. Including postage 32/-

### Data Book 1970

Gives Mullard abridged data on valves, picture tubes, semiconductors and components used in consumer electronics.

Paper bound. Including postage 4/9

### Transistor Audio and Radio Circuits

For radio receivers, radiograms, record players, tape recorders, hi-fi equipment.

Over 200 pages packed with the most up to date information.

Bound in cloth. Including postage 32/-

### Electronic Counting Circuits. Techniques. Devices.

The increasing use of mechanization and automation in factories has given rise to an increased interest in counting. This present book is intended to help engineers to use electronics to solve their counting problems as simply or as cheaply as possible.

220 pages fully illustrated. With diagrams. Including postage 29/-.

### Semiconductor Devices

This book is an introduction to Semiconductor Electronics and its contents should be readily understood. The subject is treated non-mathematically. Numerous illustrations and diagrams. Including postage 8/6.

### A programmed book on Semiconductor Devices

This book is an integral programme which is a form of self instructional text.

Size 12ins. x 8ins. Numerous illustrations and diagrams. Including postage 14/-.

### Magnadur magnets for dc motors

Magnadur is a ceramic magnetic material characterised by an exceptionally high coercive force and extremely high resistivity. The book deals solely with the use of permanent magnets in D.C. motors. Bound in board. Numerous illustrations and diagrams. Including postage 16/6.

Post now to: Dept. M  
**SELRAY BOOK COMPANY**  
60 Hayes Hill Bromley BR2 7HP

## Take your Wellerchoice\* in Soldering




### Low Initial Cost \*

Low initial cost Marksman irons, to cover most soldering needs. Screw-in tips on 15W and 25W make it easier to change the tips, which are nickel-plated and factory pre-tinned for longer life. The shanks are stainless steel to concentrate heat at the tips.
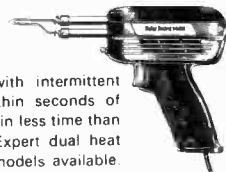
### Instant Heat for Rapid Soldering \*

Instant heat soldering guns to deal with intermittent soldering. Working heat is reached within seconds of pressing the trigger, so the job is finished in less time than it takes for a normal iron to heat up. Expert dual heat (100/140W) and Heavy Duty (275W) models available. Alternative tips available for plastics working.



# Weller Electric Limited

Redkiln Way, Horsham, Sussex

Tel: 0403 61747


Send 1/- for New Comprehensive I.C. and Semiconductor price list (24 pages)

## INTEGRATED CIRCUITS

### NEW LOW PRICES • FULLY GUARANTEED

RCA		MOTOROLA		FAIRCHILD		TEXAS TTL		MULLARD TTL		MULLARD LINEAR	
CA3000	36/-	MC724P	17/6	L900	1/5	SN7400N	18/-	FJH101	17/6	TA241	32/6
3005	24/-	MC788P	19/6	L914	8/6	SN7401N	18/-	FJH121	17/6	242	85/-
7	53/-	MC789P	17/6	L923	12/6	SN7402N	18/-	FJH141	17/6	243	30/-
11	15/-	MC790P	27/6	L702C	36/6	SN7403N	18/-	FJH161	17/6	263	15/6
12	18/-	MC792P	17/6	L709C	21/-	SN7404N	19/3	FJH171	18/3	293	19/6
13	21/-	MC798P	17/6	L710C	21/-	SN7405N	19/3	FJH221	17/6	300	38/-
14	25/-	MC799P	17/6	L711C	21/-	SN7410N	18/-	FJH251	27/6	350	35/-
18	17/-	MC1304P	29/6	L716C	21/-	SN7413N	22/-	FJH121	37/6	350	29/6
18A	22/-	MC708P	58/6	L736C	56/-	SN7420N	18/-	FJH141	62/6	360	38/-
19	17/-	MC7490P	69/6			SN7430N	18/-	FJH191	37/6	360	38/-
20	26/-	MC788P	19/6			SN7430N	18/-	FJH251	62/6	360	38/-
20A	32/-	MC838P	130/-			SN7440N	18/-	FJY101	16/-	360	38/-
21	32/-	MC1552G	89/6							811	89/-
22	26/-	MC1435P	85/-							TAB101	19/6
23	26/-	MC1709CG	18/-							TAD100	39/6
26	20/-									TAD110	39/6
28A	15/-										
28B	21/-										
29	18/-										
29A	33/-										
30	28/-										
35	25/-										
36	15/-										
39	17/-										
41	22/-										
42	22/-										
43	28/-										
44	24/-										
45	26/-										
46	15/-										
47	28/-										
48	41/-										
49	32/-										
50	37/-										
51	27/-										
52	33/-										
53	10/-										
54	22/-										
55	48/-										
59	33/-										
64	24/-										

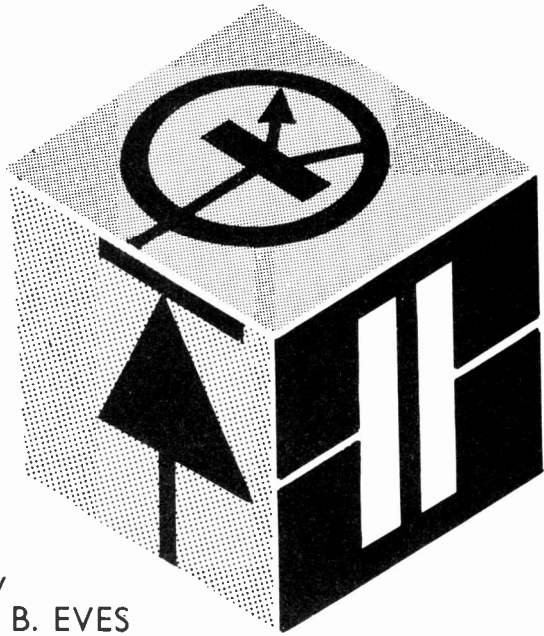Post & Packing 1/6 per order. Data sheet free if ordered with ICS.  
**TELEPHONE 01-452 0161 A. MARSHALL & SONS LTD. 21422**  
 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2  
 CALLERS WELCOME 9-5.30 SATURDAY 9-5  
**SEE OUR MAIN ADVERTISEMENT ON PAGE 1005 FOR SEMICONDUCTORS**



By  
E. B. EVES

# ELECTRONIC DICE

IN the construction of an electronic random number generator, such as an electronic dice or die there must be no bias towards any of the possible results. Bias might occur in two ways; firstly due to electronic unbalance and secondly due to human bias. Both can be eliminated by allowing the circuit to rest in each of the possible states for a very short time, say, less than  $\frac{1}{100}$  second. The time in each state must of course, be equal.


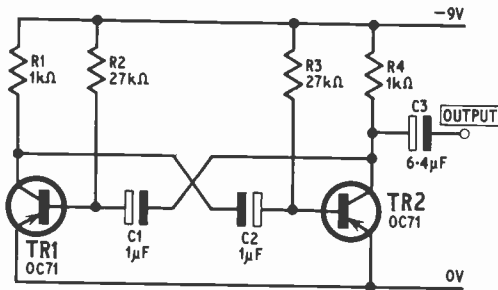


Fig. 1a. Multivibrator pulse generator for the electronic dice

Fig. 1b. Basic bistable circuit, three such circuits are used to form the divide-by-six ring circuit. Capacitor C4 is not required in bistables 1 and 2

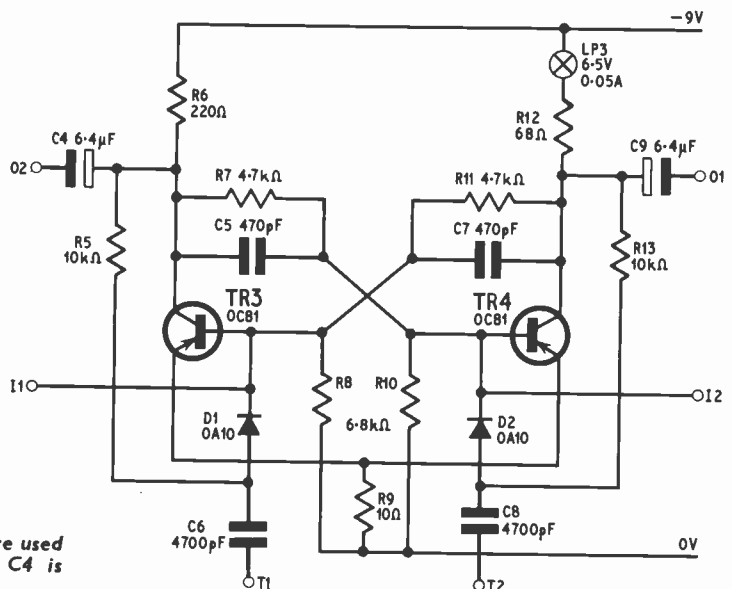

## CIRCUIT

By using a multivibrator (Fig. 1a) running at about 150–200 Hz to drive a “divide-by-six” ring circuit (Fig. 1b)—that is one which returns to its original state after six pulses have been applied to its input—bias towards one result is eliminated. If the multivibrator is connected to the ring circuit by means of a push button (S1) being depressed, the ring circuit cycles until the button is released. The state of the ring circuit will, therefore, depend on the length of time the button is depressed.

If the cycle time of the multivibrator was slow enough it would be possible to “guess” the state of the ring circuit and, therefore, bias the result. Because the switching from one state to the next occurs 150 to 200 times a second this form of bias is eliminated. As the ring circuit switches once every full cycle of the multivibrator and the period of this is constant, over short times, the time spent in each state is constant, thus eliminating electronic bias.

## CONSTRUCTION

The design of the layout may be done on printed circuit board or on copper clad Veroboard. The suggested layout for components and copper connections are shown in Figs. 2 and 3.

Board 1 is the driving multivibrator, board 2 is the basic module of the ring counter, three such boards being required. Capacitor C4 is not required on bistables 1 and 2.

## DICE BOX

The design of the dice box may be varied to suit individual requirements, and materials available. The box in the suggested design (see Fig. 5) is made from opal perspex. The “3” face has the lamps mounted behind the “spots” which are holes drilled through with inserts of clear Perspex rod with Letraset numbers on them. The “one” face has a small on/off switch mounted at its spot. The other faces have the spots drilled part way through and painted black.



# COMPONENTS . . .

## Resistors

- R1 1k $\Omega$
  - R2 27k $\Omega$
  - R3 27k $\Omega$
  - R4 1k $\Omega$
  - R5 10k $\Omega$
  - R6 220 $\Omega$
  - R7 4.7k $\Omega$
  - R8 6.8k $\Omega$
  - R9 10 $\Omega$
  - R10 6.8k $\Omega$
  - R11 4.7k $\Omega$
  - R12 68 $\Omega$
  - R13 10k $\Omega$
- } 3 off each
- All  $\pm 10\%$ ,  $\frac{1}{4}$ W carbon

## Capacitors

- C1 1 $\mu$ F elect. 16V
  - C2 1 $\mu$ F elect. 16V
  - C3 6.4 $\mu$ F elect. 16V
  - C4 6.4 $\mu$ F elect. 16V
  - C5 470pF
  - C6 4,700pF
  - C7 470pF
  - C8 4,700pF
  - C9 6.4 $\mu$ F elect. 16V
- } 3 off each

## Semiconductors

- TR1, 2 OC71 (2 off)
- TR3, 4 OC81 (3 pairs)
- D1, 2, OA10 (3 pairs)
- D3 OA81

## Miscellaneous

- LPI-3 6.5V, 0.05A MES bulb and holder (3 off)
- S1 push to make microswitch
- BY1, 2  $\times$  4.5V batteries
- Veroboard  $2\frac{1}{2}$ in  $\times$   $1\frac{3}{8}$ in (4 off)
- Plain s.r.b.p.  $2\frac{1}{2}$ in  $\times$   $1\frac{3}{8}$ in (2 off)
- Opal perspex  $\frac{1}{8}$ in  $\times$   $3\frac{1}{2}$ in  $\times$   $3\frac{1}{2}$ in (6 off)
- Perspex rod  $\frac{3}{8}$ in diam  $\times$   $\frac{3}{4}$ in (3 off)

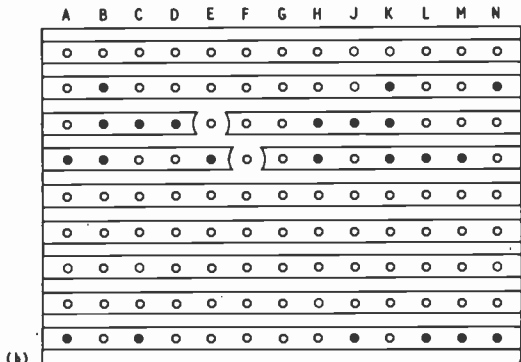
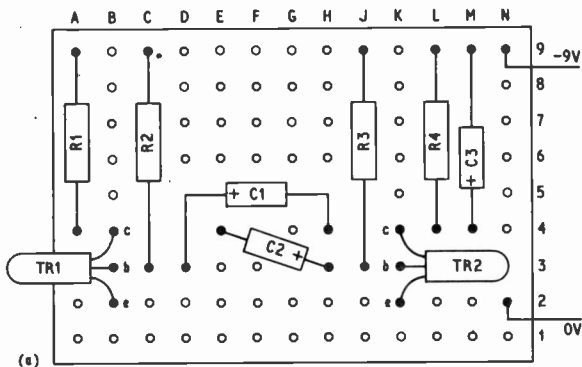
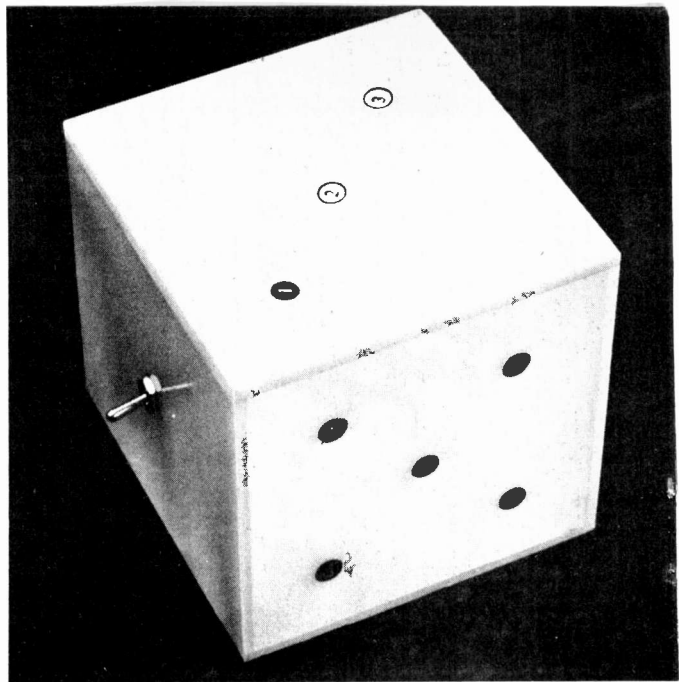


Fig. 2. Layout and wiring of the multivibrator


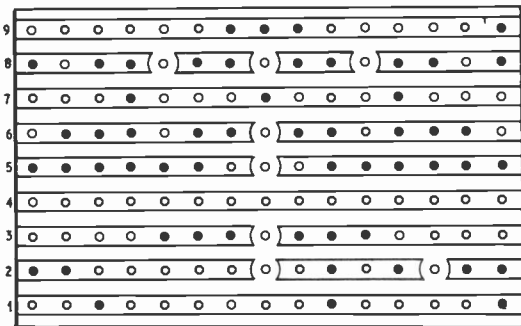
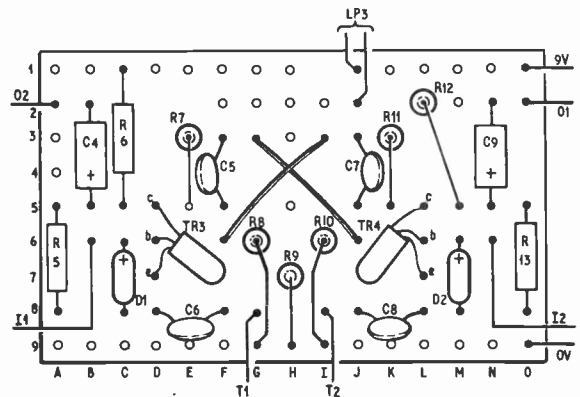


Fig. 3. Layout and wiring of one bistable

# YOURS FOR 7 DAYS FREE!

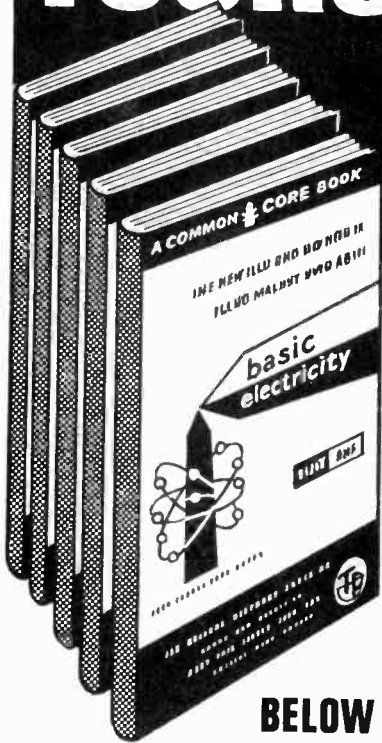

## The 'PICTURE BOOK' way of learning BASIC ELECTRICITY (5 VOLUMES) BASIC ELECTRONICS (6 VOLUMES)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects, TO TRY IT, IS TO PROVE IT

### BELOW ARE EXTRACTS FROM THE MANY LETTERS RECEIVED

#### What readers say...

**"COMPLETELY SATISFIED"**

"I would like to say I am completely satisfied with the Basic Manuals." *A. C., Rotherham.*

**"CANNOT SAY ENOUGH IN PRAISE"**

"I cannot say enough in praise of your wonderful Basic Manuals." *B. J., Stoke Poges.*

**"KEY TO LEARNING"**

"They are the key to learning and thank you again for your valuable Basic Manuals." *D. D., Glasgow.*

**"RECOMMEND TO ANYBODY"**

"I shall be delighted to recommend to anybody interested in broadening their knowledge of Electricity and Electronics." *K. L., Leeds.*

**"ALL YOU CLAIM THEM TO BE"**

"They are all you claim them to be, a delighted customer." *K. P., Worthing.*

**"GOOD, SOUND, EASY TO READ"**

"These manuals are good, sound, easy to read. They are the best I have ever set eyes upon." *P. L. J., London, S.E.1.*

**"A MATHEMATICAL IDIOT"**

"They have an easy approach to learning that a mathematical idiot like myself can easily understand." *K. L. Y., Ashton-u-Lyne.*

**"EXPRESS MY SATISFACTION"**

"I am pleased to express my satisfaction with your splendid manuals." *J. L. P., Mansfield.*

**"ENJOYING READING"**

"I am thoroughly enjoying reading your manuals. It is a delight to get to grips with these subjects." *A. P. L., Borough Green.*

**"ABLE TO UNDERSTAND THE BASIC FACTS"**

"This is the first time I have been able to understand the basic facts." *L. P., Edenbridge.*

**"THESE MANUALS ARE MY BIGGEST ASSET"**

"I am delighted to tell you that these manuals are my biggest asset, a possession that I shall never part with." *S. A., Davenport.*

**"THEY LIVE UP TO YOUR PUBLICITY IN EVERY WAY"**

"I am pleased to write and say that your manuals live up to your publicity in every way." *L. D. N., Liverpool.*

The series will be of exceptional value in training mechanics and technicians in Electricity and Electronics.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- . Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20- each. BASIC ELECTRONICS 90/- . Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS

Prices include Postage and Packing.


Signature .....  
(If under 21 signature required of parent or guardian)

NAME .....  
BLOCK LETTERS .....  
FULL POSTAL ADDRESS .....

PE

**DON'T MISS THIS OFFER! POST NOW!**
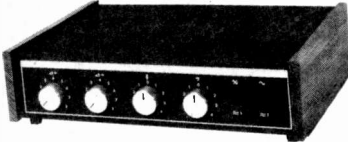
## STEREO 8 + 8 MK. II HI-FI AMPLIFIER KIT



Our popular Stereo 8+8 Mk. II now further improved incorporating high quality ready drilled printed circuit board for easy construction.

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 8.5W r.m.s. per channel into 5 ohms. Frequency response:  $\pm 3dB$  15-30,000Hz. Sensitivity: 50mV into 1M $\Omega$ . Full power bandwidth:  $\pm 2dB$  20-14,000Hz. 1M $\Omega$ . Full power bandwidth:  $\pm 2dB$  20-14,000Hz. (Readings taken at 8.3V into 5 ohms) Bass boost approx. to  $\pm 12dB$ . Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 0.6 amp. PRICES: AMPLIFIER KIT, **£10.10**, P. & P. 3/-. POWER PACK KIT, **£3.00**, P. & P. 5/-. CABINET, **£3.00**, P. & P. 5/-. (Post Free if all units purchased at same time.) Also available STEREO 10 ohm. As above but 10W per channel. PRICES: AMPLIFIER KIT, **£12.00**, P. & P. 3/-. POWER PACK KIT, **£3.10**, P. & P. 5/-.  
**STOCKISTS OF SINGLAI EQUIPMENT**  
Z.30 Amplifier **£9/6**, p. & p. 2/6.  
Stereo 60 Pre. Amplifier **£9.19/6**, p. & p. 5/-.  
PZs Power Supply **£4.19/6**, p. & p. 3/6.  
PZs Power Supply **£7.19/6**, p. & p. 3/6.  
IC.10 Integrated Circuit **£9/6**, p. & p. 2/-.  
**HI-FI STEREO HEADPHONES**  
Adjustable headband with comfortable flexiform ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE **£9/-**, P. & P. 3/-.

### LOUDSPEAKER BARGAINS

3in 4 ohm 10/-, P. & P. 1/6. 5in 3 ohm 16/-, P. & P. 3/-. 7 x 4in 3 ohm **£1/-**, P. & P. 4/-. 10 x 6in 3 or 15 ohm **35/-**, P. & P. 6/-. E.M.I. 8 x 5in 3 ohm with high flux magnet **26/-**, P. & P. 4/-. E.M.I. 13 x 8in 3 ohm with high flux ceramic magnet **42/-**, (15 ohm 48/-), P. & P. 6/-. E.M.I. 13 x 6in, 3 or 15 ohm with two built-in tweeters and crossover network 4 gu. P. & P. 6/-.

**BRAND NEW.** 12in 15W II/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiFux ceramic ferrobar magnet assembly **£5.10.0**, P. & P. 7/6. Guitar models: 25W **£6.10.0**, 35W **£8.10.0**, P. & P. 7/6. **E.M.I. 3in HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3, 8 or 15 ohm **18/6** each. P. & P. 2/6.

12in "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 15 ohm, **37/6**, P. & P. 6/-. **35 OHM SPEAKERS.** 3in 14/-, P. & P. 2/6.

**MAGNAVOX DESK TYPE MOVING COIL MICROPHONE.** Medium impedance. Brand New—Special Price **42/-**, P. & P. 2/6.

**SINGLE HEADPHONE.** With aluminum headband. Approx. 200 ohm 5/-, P. & P. 1/6.

**CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity, 18/6, P. & P. 1/6.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** O.T.R. PRICE **21/-**, P. & P. 1/6.

**HIGH IMPEDANCE DYNAMIC STICK MIKES.** High sensitivity, 39/6, P. & P. 2/6.

**SPECIAL OFFER: PLESSEY TYPE 29 TWIN TUNING GANG.** 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Size approx. 2x1x1/2in. Only **8/6**, P. & P. 2/6.

**HONEYWELL MICROSWITCHES S/P. C/O.** Push-button action. Rating 250V. AC at 15 amps. Size approx. 1 1/2" x 1 1/2" x 1/2". 5/- each. P. & P. 1/6 (6 or more post free).

**TELESCOPIC AERIALS WITH SWIVEL JOINT.** Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from to approx. 22 1/2". Maximum diameter 1 1/2". 5/- each. P. & P. 1/6.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0.20-240V. Secondary combinations: 0.5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V. at 2 amps full wave. Size 3inL x 3inW x 3inD. Price **35/-**, P. & P. 6/-.  
**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V. Sec. 0-0-9 at 500mA. 14/-, P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 17/6, P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6, P. & P. 3/6. Tapped Primary 200-220-240V. Sec. 21-5V at 500mA. 12/6, P. & P. 2/6.

**BATTERY CHARGER TRANSFORMERS.** 200/240V. input. Nominal output for 6 or 12V. batteries 3 amps. Size approx. 3" x 2 1/2" x 2 1/2". Brand New. Price **21/-**, P. & P. 5/-.  
**HIGH GRADE COPPER LAMINATE BOARDS** 8 x 6 x 1/4in. FIVE for 10/-. P. & P. 2/-.  
**Open 9-5.30 Monday to Saturday**  
**Early closing Wed. 1 p.m.**  
A few minutes from South Wimbledon Tube Station

## SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynal front. Size 16 1/2in high x 10 1/2in wide x 6in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3 or 15 ohm impedance.

**Our Price £8.80** Carr. 10/-.

Also available in 8 ohm with EMI 13in x 8in bass speaker with parasitic tweeter, **£6.10.0**, Carr. 10/-.


### STOCKISTS OF SINGLAI EQUIPMENT

Z.30 Amplifier **£9/6**, p. & p. 2/6.  
Stereo 60 Pre. Amplifier **£9.19/6**, p. & p. 5/-.  
PZs Power Supply **£4.19/6**, p. & p. 3/6.  
PZs Power Supply **£7.19/6**, p. & p. 3/6.  
IC.10 Integrated Circuit **£9/6**, p. & p. 2/-.  
**HI-FI STEREO HEADPHONES**  
Adjustable headband with comfortable flexiform ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE **£9/-**, P. & P. 3/-.

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 20dB. Solid encapsulation size 1 1/2 x 1 1/2 in. Brand new—complete with instructions. Price **17/6**, P. & P. 2/6.
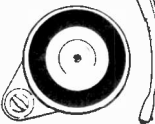
### SPECIAL PURCHASE! E.M.I. 4-SPEED PLAYER



Heavy 8 1/2in. metal turntable. Low flutter performance 200/250 V shaded motor (90 V tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY **63/-**, P. & P. 6/6.

**BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST** (as above). Fitted mono t/o stylus and cartridge for LP/78. ONLY **20/-**, P. & P. 1/6.

### QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 1/2 x 6h. Ready built and tested. PRICE **75/-**, P. & P. 6/-. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE **97/6**, P. & P. 7/6.


### DE LUXE QUALITY PORTABLE R/P CABINET MK II

Uncut motor board size 14 1/2 x 12in., clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE **79/6**, P. & P. 9/6.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving cool lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY **£7.19/6**, P. & P. 8/6. Also available ready built and tested complete with std. input sockets, **£9.19/6**, P. & P. 8/6.  
**BRAND NEW TRANSISTOR BARGAINS.** GET 15 (Matched Pair) 15/-; V15/10P, 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G339 (NPN) 3/-. Set of Mullard 6 transistors OC44, 2-OC45, AC128D, matched pair AC128 25/-; ORP12 Cadmium Sulphide Cell 10/6. All post free.  
**VERY POWERFUL COMPACT MOTOR**  
For 12V. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" x 1 1/2" dia. Free shaft 1/8" dia. x 1/4" L. Ideal for Model Makers, etc. ONLY **7/6** each P. & P. 1/-. 3 or more post free (A few 6v. versions also available).


## DE LUXE STEREO AMPLIFIER

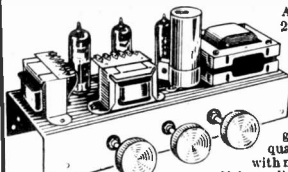

A.c. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Valve line up—2; ECL82 Triode Pentodes. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. PRICE **£8.18/6**, P. & P. 8/-.  
**4-SPEED RECORD PLAYER BARGAINS**  
Mains models. All brand new in maker's packing.  
**LATEST B.S.R. C100/A21 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge **£6.19/6**, Carr. 6/6. With stereo cartridge **£7.19/6**, Carr. 6/6.  
**LATEST GARRARD MODELS.** All types available 1025, 2025, SP25, 3000, AT80, etc. S.A.E. for Latest Prices!  
**PLINTE UNITS** cut out for Garrard Models 1025, 2025, 2000, 3000, 3500, etc. With rigid transparent plastic cover. Special design enables above models to be used and kept in position. Also suitable for housing AT60 and SP25. OUR PRICE **£5.15/6** complete. P. & P. 8/6.  
**LATEST ACOS GP91/18C Mono Compatible Cartridge** with t/o stylus for LP/EP/78. Universal mounting bracket. 30/-, P. & P. 1/6.  
**BONOTONE STARC compatible Stereo Cartridge** with diamond stylus 50/-, P. & P. 2/6.  
**LATEST BONOTONE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. 32/6, P. & P. 2/6.  
**LATEST BONOTONE T/O Mono Compatible Cartridge** for EP/LP/78 mono or stereo records on mono equipment. 30/-, P. & P. 2/6.
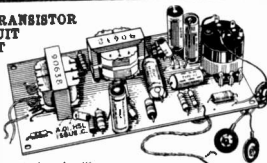
### HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT



Type T1. Output in excess of 1 1/2 watts. All standard British components. Built on a printed circuit panel size 6 x 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or 81 Mullard AC 128D and matched pair of AC128 o/p) 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with kit). All parts sold separately. SPECIAL PRICE **49/6**, P. & P. 3/6. Also ready built and tested, 55/-, P. & P. 3/6.

### 3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. w x 4in. d x 4 1/2in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and lends extended for remote mounting of controls. Complete with knobs, valves etc., wired and tested for only **£4.15/0**, P. & P. 6/6.  
**BSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **79/6**, P. & P. 6/6.  
**HARVERSON'S SUPER MONO AMPLIFIER**  
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3 1/2 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY.  
**OUR ROCK BOTTOM BARGAIN PRICE** **55/-** P. & P. 6/6.

## HARVERSON SURPLUS CO. LTD.


170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL INQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Fig. 4. Interboard wiring diagram switch S1 is a micro-switch

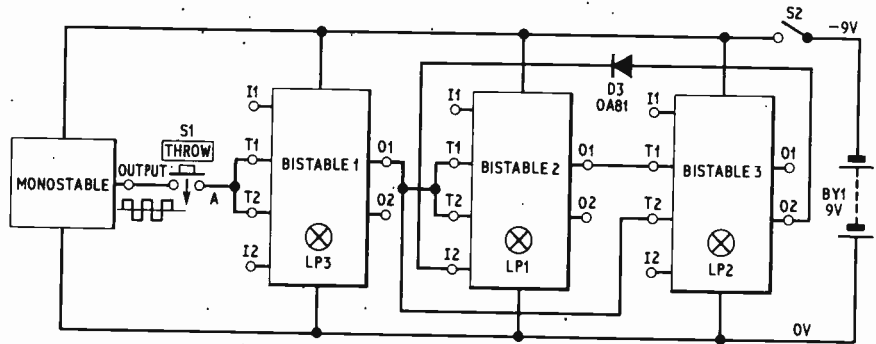

The face opposite to the "3" has no spots but has a microswitch button mounted through a hole in it. This is adjusted so that when the dice is lifted the switch is activated and is depressed when the box is put down. The sides and top of the box may be glued together, the base being fixed by means of four countersunk screws. If two 4.5 volt batteries are used they may be fixed to the base by means of Terry clips and electrical contact made to brass strips, mounted on the "one" spot side of the box, by the spring contacts on the battery.

The circuit boards are mounted on four lengths of studding, suitably spaced apart and screwed into the top surface of the box. The lamps are mounted above these boards on a plain piece of laminate and positioned so that they coincide with the Perspex rods. They should be shielded with aluminium foil to prevent light leaking to the wrong rod. The microswitch is mounted on a fifth board below the circuit boards which is adjustable on the studding by means of nuts and springs. The studding may be used as the power supply rails to the boards if required.

### TESTING THE CIRCUIT

Before wiring the boards together they should be checked individually. Check the multivibrator board connections then apply the battery, observing correct polarity. The output should be fed to an oscilloscope, if possible, or via a suitable attenuator to an audio amplifier; A note should be heard in the second case.

The inputs T1 and T2 should be coupled together on the bistable boards for the test and the lamps wired in.

When the voltage is applied and a pulse of about 6V put onto the trigger inputs T1 and T2 the lamp should switch.

If all boards are working they should now be wired together as shown in Fig. 4. Note that diode D7 is part of the interboard wiring and not included on any board.

When the three "ring" boards have been connected and checked, the power rail should be connected. One, two or all three lamps should light. A 6 to 9V pulse may now be fed into the input at A (Fig. 4); the lamps should change state. Apply a total of six pulses and note the state of the lamps. Apply six more pulses and the lamps should be in the same state again without having repeated any combination, if this is not the case the interboard wiring should be checked. If working properly the multivibrator may be brought into use to supply the pulses. When contact is made at A by the microswitch all the lamps should glow until the switch is released when one, two or all should

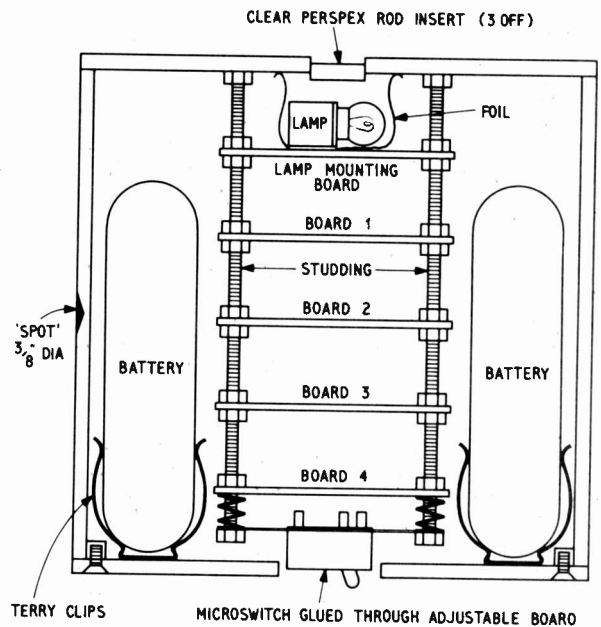


Fig. 5. Suggested design and construction of the electronic dice


turn fully on and the remaining lamps, if any, should switch off. Pressing and releasing the microswitch should give a random selection of lights.

The circuit may now be inserted into the box. The numbers applied to the Perspex "spots" should be carefully placed over the correct lamp, i.e., 1 over LP1, 2 over LP2, and 3 over LP3.

When installed, the microswitch should make and break as the box is lifted and put down.
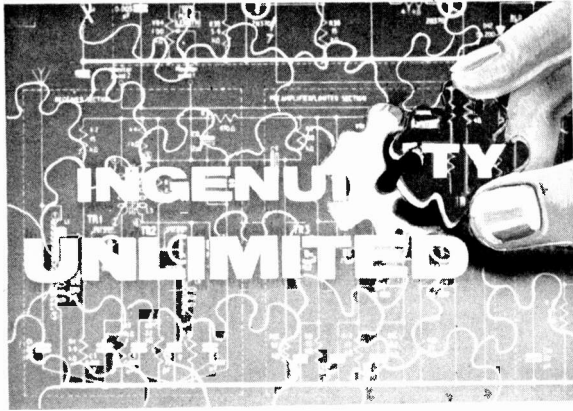
### TO PLAY

Switch on the power switch. The first player lifts the "die" and puts it down. The sum of the illuminated numbers on the top face is the score for that throw. The next player then lifts and replaces the box again scoring the total shown. ★



A selection of readers' suggested circuits. It should be emphasized that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merit.

## FUZZ CIRCUIT

THE CIRCUIT diagram in Fig. 1 is my design for a simple "Fuzz Box", which readers may be interested to experiment with.

The circuit is basically a two transistor pre-amplifier followed by a Schmitt trigger. The pre-amplifier section was designed with variable gain, so that background noise and internal feedback would not operate the trigger.

Since the signal from a guitar contains many harmonics, it is likely that "double-triggering" could occur if certain precautions were not taken. To cure double triggering the values of R5, R7 and C3 were determined by experiment. Capacitor C3 also determines the tone of the fuzz effect. If triggering still occurs then a 10 kilohm resistor inserted between TR2 collector and TR3 base may cure it.

The square-wave output signal is fed via C4 to the attenuating network made up of C5 and VR2. The values of the latter components set the maximum gain of the circuit at slightly more than unity.

Some readers may consider this to be a "waste" of the amplifying powers of TR1 and TR2 and might choose to use the pre-amplifier section for other purposes. A treble booster could be made by switching in the primary windings of an inter-valve transformer across the input.

S. Sharpes,  
Brough, Yorks.

## METAL LOCATOR

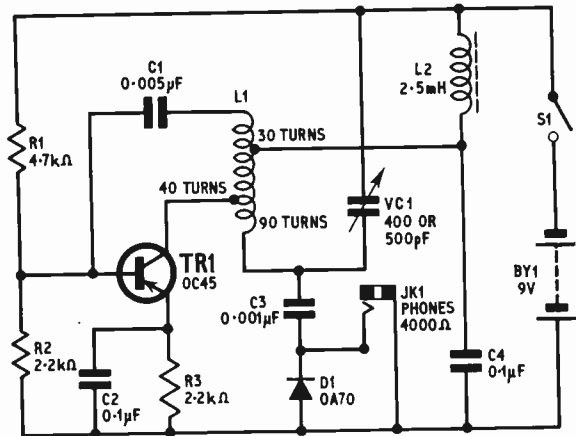


Fig. 1. Single transistor metal locator

ONE of my more unusual circuits is a simple transistor metal detector shown in Fig. 1. It has a current drain of only 1.5mA from the battery.

The OC45 transistor oscillates in the common emitter configuration at a frequency of about 200Hz, using a Hartley type circuit. The frequency of oscillation can be altered by means of the timing capacitor VC1. The output from the oscillator has a low frequency component, which, after detection by the diode D1, is heard in the headphones.

All the components may be mounted on Veroboard and housed in a plastics case, except the search coil. The coil was wound on a table tennis bat, but any 5in diameter former will suffice. The coil is made by pile winding 160 turns of 28 s.w.g. enamelled wire on the former and tapping off at 30 and 70 turns.

Transistors other than OC45 will work, but they must have an alpha cut-off frequency of at least 6MHz. Headphones of 2 kilohm or 4 kilohm impedance can be used.

The detector may be used to a depth of 1 ft. When the search coil is brought near a non-ferrous metal object, the inductance is reduced which increases the frequency of oscillation. Ferrous objects cause a rise in inductance and a fall in frequency of oscillation. With certain settings of the tuning capacitor, the note in the headphones stops completely, giving a very positive indication.

K. A. Coward,  
Durban, S. Africa.

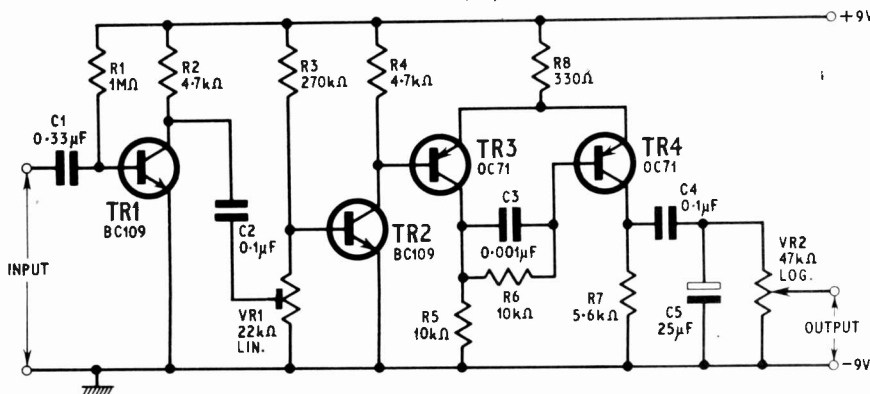


Fig. 1. A simple four transistor "fuzz" circuit for use with all types of electronic and electric musical instruments

### ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price - new and unused only **39/6**, less than the value of the clock alone plus and insurance 2/9.



### FLUORESCENT CONTROL KITS

Each kit comprises seven items - Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A - 15-20W 19/6. Kit B - 30-40W 19/6. Kit C - 80W 23/6. Kit E - 65W 23/6. Kit F for 8ft. 125W tube 35/-. Kit MF1 is for 6in, 9in and 12in miniature tubes. 19/6. Kit MF2 for 2 1/2in miniature tube. 20/-. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 8/6 on first kit then 3/6 for each kit ordered. Kit F 6/6 then 4/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

### BLANKET SWITCH

Double pole neon let into side so luminous in dark. Ideal for dark room light or for use with waterproof element - new plastic case. 5/6 each. 3 heat model 7/6.



### BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1A. Listed at 27/6 each we offer these while our stocks last at only 12/6 each.



### REED SWITCHES

Glass encased, switches operated by external magnet - gold welded contacts. We can now offer 3 types:

**Miniature.** 1in long - approximately 3/4in diameter. Will make and break up to 1A up to 300 volts. Price 2/6 each, 24/- dozen.

**Standard.** 2in long - 3/4in diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 3/6 each, 18/- per dozen.

**Flat.** Flat type, 2 1/2in long, just over 1/4in thick, flattened out, so that it can be fitted into smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each, 33/- dozen.

Small ceramic magnets to operate these reed switches 1/3 each, 18/- dozen.

### HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-equipment.

100 mfd. 25V, 1/3 each 12/- doz.

200 mfd. 25V, 1/3 each 15/- doz.

250 mfd. 50V, 3/3 each 30/- doz.

400 mfd. 40V, 4/4 each 46/- doz.

500 mfd. 12V, 2/- each 11.0 doz.

500 mfd. 25V, 3/6 each 36/- doz.

500 mfd. 50V, 4/6 each 48/- doz.

500 mfd. 350V, 8/6 each 24.10 doz.

1000 mfd. 12V, 3/- each 21.10 doz.

1000 mfd. 18V, 3/4 each 34/- doz.

1000 mfd. 64V, 7/4 each 80/- doz.

2000 mfd. 25V, 6/8 each 79/- doz.

5000 mfd. 12V, 4/9 each 22.5 doz.

10,000 mfd. 6V, 5/9 each 23.0 doz.

10,000 mfd. 15V, 8/6 each 24.10 doz.

15,000 mfd. 10V, 10/6 each 25.0 doz.

60,000 mfd. 8V, 22/- each 41.0 doz.

70,000 mfd. 13V, 40/- each 220.0 doz.

### TELESCOPIC AERIAL

for portable, car radio or transistor. Chrome plated six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6. Knuckled model for FM, 10/-.

### TOGGLE SWITCH

3 amp, 250V with fixing ring. 1/6 each, 15/- doz.

### 80 OHM BALANCED ARMATURE EAR PIECE

Suitable as microphone or loudspeaker, 4/6 each.

### 3 STAGE PERMEABILITY TUNER

This Tuner is a precision instrument made by the famous "Cydron" Company for the equally famous Radionobile Car Radio. It is a medium wave tuner (but set of longwave coils available as an extra if required) with a frequency coverage 1620 kc/s-825 kc/s and intended to operate with an I.F. value of 470 kc/s. Extremely compact (size only 2 1/2 x 2 1/4 in thick) with reduction gear for fine tuning. Sulp price this month 28/6, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier. Post Free.



### HORSTMANN "TIME AND SET" SWITCH


(A 15 amp switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch-on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around 25. Special snip price 20/6, p. & ins. 4/6.

### DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive motors, oven, blower heater, etc. 8/6 each, plus 3/6 post and insurance, 6 or more post free.




### ATLAS SLIMLINE FLUORESCENTS

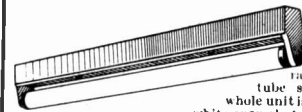

Fluorescent lighting units made by the famous Atlas company, with super silent polyester filled choke and radio suppressed starter. The whole unit is beautifully made and finished white enamel. Amazingly economical. Measures 2ft. long. Is fitted in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer, 39/6 with tube. Assembled ready to install. 4ft. twin model 59/6, post & ins 6/6. 5ft. twin with diffuser, regular price 21, our price 210, carr 1. Postage and insurance 6/6 extra.

320 VOLT MAINS OPERATED KLAXON HORN

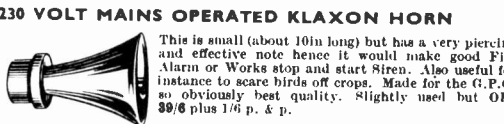This is small (about 10in long) but has a very piercing and effective note hence it would make good Fire Alarm or Works stop and start Siren. Also useful for instance to scare birds off crops. Made for the G.P.O. so obviously best quality. Slightly used but OK. 39/6 plus 1/6 p. & p.




### THIS MONTH'S SNIP

**40 WATT 12in HI-FI SPEAKER.** Is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and public address. Handling 40W R.M.S. - Cone moulded fibre - Freq. response 30-10,000 c.p.s. - specify 3 or 15 ohms. Chassis diam. 12in - 12 1/2in over mounting lugs. Overall height 5 1/2in. A 10 speaker offered this month for 25.10 plus 7/6 post and ins.


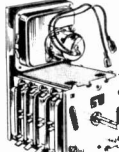
### MOTORISED CAM SWITCH

Made by the famous meter company Chamberlain and Hookham, these have a normal mains 200-240V motor which drives a ratchet mechanism so geared to give one ratchet action per minute on a wheel with 60 teeth thus a complete revolution of the cam takes place in one hour. The cam operates 8 switches (6 changeover and 2 on/off thus 480 circuit changes per hour are possible). Contacts, rated at 15A have been set for certain switch combinations but can, no doubt, be altered to suit a special job. Also other water or devices can be attached to the shaft which extends approximately one inch. 47/6, p. & ins. 4/6.



### BARGAIN OF THE YEAR MICROSONIC KEYCHAIN RADIO

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 1 1/2 in - complete with soft leather zippered bag. Specification: (Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1,600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 465Kc/s or 455Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly - offered without guarantee except that they are new. Price only 24/6 plus 2/6 post and insurance, less batteries. 6 for 27, post free. Rechargeable batteries 8/6 pair.




### 1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a huge clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch 22/6.



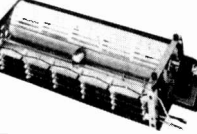
### 3kW TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing 215 and more. We have a few only. Comprises motor, impeller, and two elements allowing 3 heat switching and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 2kW model 59/6, 3kW model 89/6. Postage and insurance 6/6. Control switch 5/6.



Where postage is not stated then orders over 25 are post free. Below 25 add 2/9. Semiconductors add 1/- post. Over 21 post free. S.A.E. with enquiries please.

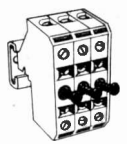**Mains Connector.** A quick way to connect equipment to the mains safely and firmly. Disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7.029 cables. 12/6 each.



### CONTROL DRILL SPEEDS


**DRILL CONTROLLER**  
Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions 19/6, plus 2/6 post and insurance. Made up model also available 37/6 plus 2/6 p. & p.

**BALANCED ARMATURE UNIT**  
500 ohm, operates speaker or microphone, so useful in intercom or similar circuits. 6/6 each, 23.10 doz. 80 ohm model 5/6.


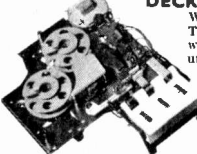
### BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2in deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type supplied complete with 2 spools ready to install. Record, Playback is the sensitive M4 type intended for use with transistor amplifier. Unused, ex-equipment. Price 79/6. Post and insurance 4/6.



### PROTECT VALUABLE DEVICES FROM THERMAL RUNAWAY OR OVERHEATING

Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg.C. to 190deg.F. or with the dial removed range setting is between 80 to 800deg.F. Price 10/-.



### THYRISTOR LIGHT DIMMERS

Will dim incandescent lighting up to 600W from full brilliance to out. Assembled and wired ready to install. 59/6.



### MINIATURE WAFER SWITCHES

2 pole, 2 way - 4 pole, 2 way - 3 pole, 3 way - 4 pole, 3 way - 2 pole, 4 way - 3 pole, 4 way - 2 pole, 6 way - 1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.



### WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

### 0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- dozen



### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 10/6 plus 3/6 postage.

### MICRO SWITCH

5 amp, changeover contacts, 1/9 each, 18/- doz. 15 amp Model 2/- each or 21/- doz.



## ELECTRONICS (CROYDON) LTD

Dept. PE, 266 London Road, Croydon CR0 2TH

Also 102/3 Tamworth Road, Croydon



# FIND BURIED TREASURE!

TREASURE LOCATOR—  
NOW IT'S HERE AT LAST.



After experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects. It signals exact location (no phones used). **FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS, ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground! Can be built with ease in one short evening with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions. Fully transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 3/4in x 10in x 2 1/2in. Great demand expected at this remarkably low price—All parts including detector head case, nuts, screws, wire, simple instructions, etc. Send now 47/6 plus 6/6 P. & P. (Telescopic handle as illustrated 25/- extra.) Parts available separately. Made up looks worth £15.

ONLY  
**47/6**

necessary. Size of detector head 13 3/4in x 10in x 2 1/2in. Great demand expected at this remarkably low price—All parts including detector head case, nuts, screws, wire, simple instructions, etc. Send now 47/6 plus 6/6 P. & P. (Telescopic handle as illustrated 25/- extra.) Parts available separately. Made up looks worth £15.

READ PEOPLE'S MINDS—TEST THEIR NERVES—BEAT THEM AT CARDS—TEST THEIR MENTAL ABILITY, ETC. ASTONISHING


## ELECTRONIC BRAINBOX



57/6

Make this an exciting Christmas. If you've seen a giant computer on show at an electronics exhibition, you will have seen people of all ages queuing to pit their abilities against the giant electronic brain. There is tremendous fascination that attracts ordinary people and professional engineers alike to electronic games of skill, chance and mystery. With this "Brainbox" you will be able to perform mind-boggling feats. **THE MIND READING DEVICE** will make people swear you have telepathic powers. **THE AMAZING CARD TRICK UNIT** completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. **THE ELECTRONIC NERVES TESTER** puts your friends to a very lively test. It gives out fall and finish signals (the winner is the person with lowest number of fall signals). Can be adjusted from the weakest to strongest electronic twist to it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof, uses standard battery. Size 18in x 12in x 6in (Max.). You can play all these games and more besides. **WE GUARANTEE THAT ANYONE CAN EASILY ASSEMBLE THESE PROJECTS IN UNDER ONE HOUR!** No soldering, pictorial, step-by-step illustrated instructions. ONLY 57/6 plus 6/6 P. & P. for all parts including chassis, switches, stylus, signalling lights, wire, nuts, screws, etc. etc. (PARTS AVAILABLE SEPARATELY). FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.

## REAL WORKING ELECTRONIC ORGAN

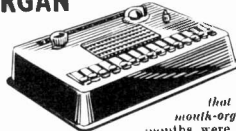


ONLY  
**55/-**

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Eight months were spent in creating and fully transistorised, no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", "Silent Night", "Auld Lang Syne", and lots of similar tunes on this real working electronic organ. Size 13 1/2in x 10in x 2 1/2in. Uses standard battery. Have the thrill and excitement of building it together with the pleasure of playing a real electronic organ. Play it anywhere. No soldering necessary. Easy as A.B.C. to make following the fully illustrated, step-by-step instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low price. ONLY 55/- + 4/6 P. & P. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformers, volume control, wire, nuts, screws, instructions, etc. (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Your money refunded in full if not 100% delighted.
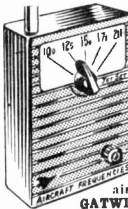
## LISTEN TO AIRCRAFT COMMUNICATIONS JUST OUT V.H.F. AIRCRAFT BAND CONVERTER



ONLY  
**47/6**

Listen in to AIRLINES, PRIVATE PLANES, JET PLANES. Eavesdrop on exciting cross-talk between pilots, ground approach, ground control, airport tower. Hear for yourself the disciplined voices hiding tensions on talk-downs. Be with them when they have to take nerve-ripping decisions in emergencies—tune in to the international distress frequency. Covers aircraft frequency band including HEATHROW, GATWICK, LUTON, BINGWAY, PRESTWICK, ETC. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No soldering necessary. Fully illustrated simple worked instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2in x 3 1/2in. All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny pocket radios). **NO CONNECTIONS WHATSOEVER NEEDED.** Use indoors or outdoors. SEND NOW. ONLY 47/6 for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately).

**CONCORD ELECTRONICS LTD.** P.E.13 · 8 WESTBOURNE GROVE · LONDON · W.2  
(Near Bayswater Tube) Callers welcome. 9-6 including Saturdays

# SAVE MONEY NOW!


On the famous S.D.C. DeC range of solderless breadboards

We are pleased to announce that greatly increased demand has enabled us to slash the prices of our S-DeC range. In addition we offer Practical Electronics readers a special reduction in the price of T-DeC for one month only.

**S-DeC** Available as single packs with accessories and control panel NOW AT 20/- or the DeCSTOR double pack containing 2 S-DeCs, accessories, control panel, all in a plastic storage container. NOW ONLY 50/-. A 4 DeC pack is available, NOW ONLY 78/-.

**T-DeC** Now available to the amateur. 208 connection points. 38 independent junctions. Accommodates I.C.s using standard carriers. Three times the capability for only twice the price! Unit pack with control panel 50/-.

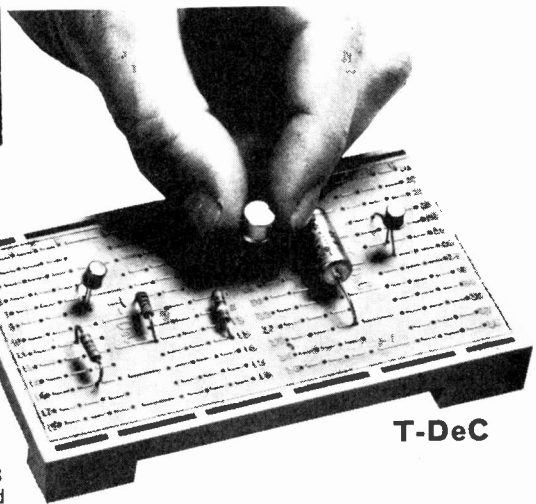**μ-DeC** Primarily for use with integrated circuits; further details on request.



T-DeC

**SPECIAL OFFER — 7/6 OFF T-DeC**

Normal recommended retail price of 50/-

Take this coupon to your local stockist who will supply one T-DeC for . . . **42/6d**

**S.D.C. ELECTRONICS (SALES) LTD.**

34 Arkwright, Astmoor Industrial Estate, Runcorn, Cheshire. Tel.: Runcorn 5041

Offer closes 15th December 1970

**BRAND NEW**

**SEMICONDUCTORS & COMPONENTS**

**GUARANTEED**

**TRANSISTORS**


2G301	4/-	2N3402	4/6	3N142	11/-	BC160	12/6	BFY50	4/6	NKT229	6/-		
2G302	4/-	2N3403	4/6	3N143	13/6	BC167	3/6	BFY51	4/-	NKT237	7/-		
2G303	4/6	2N3404	6/6	3N152	17/6	BC168	3/6	BFY52	4/6	NKT238	5/-		
2G306	8/6	2N3414	4/6	R.C.A.		BC168B	2/9	BFY53	3/6	NKT240	5/6		
2G308	6/-	2N3415	4/6	40050	10/6	BC168C	3/-	BFY56	11/-	NKT241	5/6		
2G371	3/-	2N3416	7/6	40251	17/6	BC169B	2/9	BFY75	6/-	NKT281	5/6		
2G374	4/-	2N3417	7/6	40309	6/6	BC169C	3/-	BFY77	6/-	NKT713	4/-		
2G381	4/6	2N3570	25/-	40310	9/-	BC170	2/6	BFY85	9/-	NKT10419	9/-		
2N404	4/6	2N3572	19/6	40311	7/-	BC171	3/-	BFY90	13/6		6/-		
2N696	4/6	2N3605	3/6	40312	9/6	BC172	3/6	BPX25	37/-	NKT10439	37/-		
2N697	4/6	2N3606	5/6	40314	7/6	BC175	4/6	BPX29	36/-		7/6		
2N698	5/-	2N3607	4/6	40320	6/6	BC182	2/-	BPY10	29/-	NKT10519	29/-		
2N706	2/6	2N3662	7/6	40323	6/6	BC182L	2/-	BRY39	9/6		6/6		
2N708	2/6	2N3663	7/6	40324	9/6	BC183	2/6	BSW41	8/6	NKT20329	8/6		
2N709	3/-	2N3702	2/6	40326	7/6	BC184	3/6	BSW40	5/6		6/6		
2N718	12/6	2N3703	2/6	40329	6/-	BC212L	2/6	BSX19	3/6	NKT20339	3/6		
2N726	5/-	2N3704	3/6	40344	5/6	BCY30	2/6	BSX20	3/6		7/6		
2N727	6/6	2N3705	2/6	40347	7/6	BCY31	5/6	BSX21	7/6	NKT80111	15/6		
2N914	3/6	2N3706	2/6	40348	10/6	BCY32	5/6	BSX26	9/-		19/6		
2N916	3/6	2N3707	2/-	40361	9/6	BCY34	4/6	BSX27	9/6	NKT80112	19/6		
2N918	6/-	2N3709	2/-	40362	11/6	BCY38	4/6	BSX28	6/6		19/6		
2N929	4/6	2N3710	2/6	40370	6/6	BCY39	10/6	BSX61	12/6	NKT80211	22/6		
2N930	5/6	2N3711	2/6	40406	11/6	BCY40	7/6	BSX76	4/6	NKT80211	18/6		
2N1090	5/6	2N3711	2/6	40406	11/6	BCY40	7/6	BSX76	4/6	NKT80211	18/6		
2N1091	4/6	2N3716	5/6	40407	8/6	BCY42	3/6	BSX77	5/6	NKT80212	18/6		
2N1131	5/-	2N3791	85/-	40410	12/6	BCY54	6/6	BSY24	3/-	NKT80213	18/6		
2N1132	5/-	2N3819	7/-	40467A	11/6	BCY58	4/6	BSY25	3/-		18/6		
2N1302	3/6	2N3823	19/6	40468A	7/-	BCY59	4/6	BSY26	3/6	NKT80214	18/6		
2N1303	3/6	2N3854	5/6	40600	14/6	BCY60	19/6	BSY27	3/6		18/6		
2N1304	4/6	2N3854A	5/6	AC107	6/-	BCY70	4/6	BSY28	3/6	NKT80215	18/6		
2N1305	4/6	2N3855	5/6	AC126	4/-	BCY71	8/6	BSY29	3/6		18/6		
2N1306	5/6	2N3855A	5/6	AC127	5/6	BCY72	8/6	BSY32	5/-	NKT80216	18/6		
2N1307	5/-	2N3856	7/-	AC128	4/-	BCY73	8/6	BSY36	5/-		18/6		
2N1308	6/-	2N3856A	7/-	AC154	4/6	BCZ11	8/6	BSY37	5/-		18/6		
2N1309	6/-	2N3858	5/-	AC176	5/-	BD116	22/6	BSY38	4/6		18/6		
2N1507	3/6	2N3858A	6/-	AC187	12/-	BD121	13/-	BSY39	4/6		18/6		
2N1613	5/-	2N3859	5/6	AC188	7/6	BD123	16/6	BSY40	4/6		18/6		
2N1631	7/-	2N3859A	6/6	AC17	5/6	BD124	12/6	BSY51	6/6		18/6		
2N1632	7/-	2N3860	6/6	AC178	5/6	BD125	12/6	BSY52	6/6		18/6		
2N1637	6/-	2N3866	30/-	AC19	3/-	BD132	19/6	BSY53	7/6		18/6		
2N1638	5/6	2N3877	8/-	ACV20	5/-	BDY10	27/6	BSY54	8/6		18/6		
2N1639	5/6	2N3877A	8/-	ACV21	5/-	BDY11	32/6	BSY55	8/6		18/6		
2N1711	5/-	2N3884	12/6	ACV22	4/-	BDY17	30/-	BSY56	18/-		18/6		
2N1889	6/6	2N3900	7/6	ACY28	4/-	BDY18	35/-	BSY57	18/-		18/6		
2N1893	7/6	2N3900A	8/-	ACY40	4/-	BDY19	39/6	BSY58	18/-		18/6		
2N2147	16/6	2N3901	7/6	ACY41	4/-	BDY20	22/6	BSY95A	2/6		18/6		
2N2148	11/6	2N3903	7/6	ACV44	8/-	BDY19	19/6	D16P1	7/6		18/6		
2N2160	11/6	2N3904	7/6	AD140	10/6	BDY60	25/-	D16P2	7/6		18/6		
2N2193	8/-	2N3905	7/6	AD149	11/6	BDY61	25/-	OC41	4/6		18/6		
2N2193A	8/-	2N3906	7/6	AD150	12/6	BDY62	20/-	OC42	5/6		18/6		
2N2194A	8/-	2N4058	3/6	AD161	7/6	BF115	5/6	OC43	5/6		18/6		
2N2217	3/6	2N4059	2/-	AD162	7/6	BF117	9/6	OC44	5/6		18/6		
2N2218	3/6	2N4060	2/-	AF106	8/6	BF163	7/6	OC45	5/6		18/6		
2N2219	3/6	2N4061	2/-	AF106	8/6	BF167	7/6	OC46	3/6		18/6		
2N2220	3/6	2N4062	2/6	AF114	5/6	BF173	6/6	OC47	3/6		18/6		
2N2221	6/-	2N4244	9/6	AF115	6/6	BF177	6/6	OC48	3/6		18/6		
2N2222	5/-	2N4285	3/6	AF117	5/6	BF178	10/6	OC49	3/6		18/6		
2N2287	21/6	2N4286	3/6	AF118	12/6	BF179	14/6	OC77	6/-		18/6		
2N2297	6/-	2N4287	3/6	AF119	10/6	BF180	7/6	OC81	4/-		18/6		
2N2303	3/6	2N4288	3/6	AF124	4/6	BF181	6/6	OC82	3/6		18/6		
2N2368	5/-	2N4289	3/6	AF125	4/6	BF184	5/6	OC83	3/6		18/6		
2N2369	3/6	2N4290	3/6	AF126	4/6	BF185	8/6	OC84	3/6		18/6		
2N2369A	3/6	2N4291	3/6	AF127	3/6	BF194	3/6	OC139	6/6		18/6		
2N2410	8/6	2N4292	2/6	AF139	7/6	BF195	4/6	OC140	6/6		18/6		
2N2483	5/6	2N4303	2/6	AF178	8/6	BF196	8/6	OC170	6/6		18/6		
2N2484	6/6	2N4307	10/6	AF179	14/6	BF197	8/6	OC171	6/6		18/6		
2N2539	4/6	2N5028	11/6	AF180	10/6	BF200	10/6	OC200	7/6		18/6		
2N2540	4/6	2N5029	9/6	AF181	8/6	BF224	4/-	OC201	8/6		18/6		
2N2613	7/-	2N5030	8/6	AF219	9/6	BF225	4/-	OC202	8/6		18/6		
2N2614	5/-	2N5172	2/6	AF279	8/6	BF237	4/6	OC203	8/6		18/6		
2N2646	11/6	2N5174	10/6	AF280	12/6	BF238	4/6	OC204	8/6		18/6		
2N2696	6/6	2N5175	10/6	AFZ11	6/6	BF244	6/6	OC205	12/6		18/6		
2N2711	5/-	2N5176	9/6	ASV26	5/6	BF245	6/6	OC207	13/-		18/6		
2N2712	5/-	2N5232	6/6	ASV27	5/6	BF248	6/6	OCPT1	12/6		18/6		
2N2713	5/6	2N5232A	6/6	ASV27	7/6	BFW59	5/6	ORP12	12/6		18/6		
2N2714	6/-	2N5245	9/6	ASV28	5/6	BFW60	5/6	ORP61	10/-		18/6		
2N2865	12/6	2N5246	8/6	ASV29	5/6	BFW61	9/6	P346A	4/6		18/6		
2N2904	6/-	2N5249	13/6	ASV30	5/6	BFX12	4/6	TIP31A	16/6		18/6		
2N2904A	6/6	2N5249A	13/6	ASV34	5/6	BFX13	4/6	TIP32A	19/6		18/6		
2N2905	7/6	2N5265	65/-	ASV54	5/6	BFX29	6/6	TIS34	12/6		18/6		
2N2905A	8/-	2N5266	55/-	ASV86	6/6	BFX30	6/6	TIS43	8/6		18/6		
2N2906	5/-	2N5267	52/6	ASZ20	7/6	BFX43	7/6	TIS44	2/6		18/6		
2N2906A	5/6	2N5305	7/6	ASZ21	8/6	BFX44	7/6	TIS45	2/6		18/6		
2N2907	6/-	2N5306	8/6	AU10	30/-	BFX68	13/6	TIS46	2/6		18/6		
2N2923	3/6	2N5307	7/6	BC107	2/6	BFX68A	13/6	TIS47	2/6		18/6		
2N2924	3/6	2N5308	7/6	BC108	2/6	BFX84	5/6	TIS48	2/6		18/6		
2N2925	3/6	2N5309	12/6	BC109	2/6	BFX85	6/6	TIS49	2/6		18/6		
2N2926	3/6	2N5310	8/6	BC113	5/6	BFX86	5/6	TIS50	3/6		18/6		
.. Green 2/9	2N5354	5/6	BC115	8/6	BFX87	5/6	NKT0013	9/6	TIS51	2/6		18/6	
.. Yellow 2/6	2N5355	5/6	BC116A	7/6	BFX88	5/6	NKT124	8/6	TIS52	2/6		18/6	
.. Orange 2/6	2N5356	6/6	BC118	6/6	BFX89	12/6	NKT125	5/6	TIS53	4/6		18/6	
2N3011	6/6	2N5357	6/6	BC121	4/6	BFX92A	12/6	NKT126	5/6	TIS54	4/6		18/6
2N3014	6/6	2N5367	11/6	BC125	11/-	BFY93A	14/-	NKT128	5/6	TIS61	5/6		18/6
2N3053	5/6	2N5457	7/6	BC126	11/6	BFY11	8/6	NKT137	6/6	TIS62	5/6		18/6
2N3054	10/-	25005	15/-	BC134	6/6	BFY12	4/6	NKT210	6/6	ZTX107	3/6		18/6
2N3133	5/6	25020	40/-	BC135	8/6	BFY13	4/6	NKT211	6/6	ZTX109	3/6		18/6
2N3134	6/6	25022	10/-	BC136	7/6	BFY17	4/6	NKT212	6/6	ZTX300	3/6		18/6
2N3135	5/6	25036	6/6	BC140	7/6	BFY18	6/6	NKT213	6/6	ZTX301	3/6		18/6
2N3136	5/6	25014	5/6	BC142	3/6	BFY19	6/6	NKT214	6/6	ZTX302	4/6		18/6
2N3390	5/-	25501	6/6	BC148	2/6	BFY20	12/6	NKT215	6/6	ZTX303	4/6		18/6
2N3391	4/-	25502	7/6	BC149	3/6	BFY21	8/6	NKT216	7/6	ZTX304	4/6		18/6
2N3391A	4/-	3N83	8/-	BC152	3/6	BFY24	9/-	NKT217	8/6	ZTX500	4/6		18/6
2N3392	3/6	3N128	14/-	BC154	8/6	BFY29	10/-	NKT219	8/6	ZTX501	5/-		18/6
2N3393	3/6	3N130	15/6	BC157	4/6	BFY30	10/-	NKT223	5/6	ZTX502	5/-		18/6
2N3394	3/6	3N141	14/6	BC158	3/6	BFY41	10/-	NKT224	5/6	ZTX503	5/-		18/6
				BC159	4/6	BFY43	12/6	NKT225	4/6	ZTX504	12/6		18/6

Post & Packing 2/- per order. Europe 5/-; Commonwealth (Air) 13/-; Minimum. Send 6d stamp for price list.

Tel. 01-452 0161/2/3 **A. MARSHALL & SON**  
28 CRICKLEWOOD BROADWAY, LONDON, N.W.2
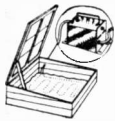
### DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master intercom. Simply plugs together. Originally sold at £10. Special snip price 49/6, plus 3/6 postage.



### Be first this year! SEED AND PLANT RAISING

Soil heating wire and transformer. Suitable for standard size garden frame. 19/6 Post and ins. 3/6.

### 12V EXTRACTOR FAN BY DELCO

Ideal to make heater for Caravan, Car or Boat. 6 Bladed 5in diameter fan inside heavy duty cylinder with 3 point fixing flange. 5 1/2in diameter fixing hole. Length approx. 8 1/2in. Exceptional bargain 27/6 plus 5/6 post and insurance.

### HAPPY FISH

and lively indoor Plants have "LUX GROWTH" lighting which gives U.V. and other rays essential to healthy flora & fauna—Special Trial Offer. 9in U.V. tube complete with choke, starter tube, connections and spring clips—all you need inc. wiring diagram. 39/6 plus 4/6 post & ins.

### 12V 1 1/2amp POWER PACK

Comprises double wound mains transformer with full wave rectifier and 2000 $\mu$ fd smoothing. 27/6 plus 4/6 p. & p.

### 2 1/2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/2 kW), switch central blows cold for summer cooling adjustable thermostat acts as auto control and safety cut-out. Complete kit 23.15.0. Post and ins. 7/6.

### RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only 21 each or 211 per dozen, specify 10 or 15A—simply fit in place of switch.




### VARIAC CONTROLLERS

With these you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. We offer a range of these, ex-equipment but little used and in every way as good as new. Any not so, will be exchanged or cash refunded. 2A £4.19.6, 5A £7.19.6, 8A £12.19.6, 10A £15.19.6.

### STANDARD WAFER SWITCHES

Standard size 1 1/2 wafer—silver-plated 5-amp contact, standard 1in spindle 2in long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	8/6	8/6	8/6	8/6	8/6	8/6	8/6	8/6	8/6
2 poles	8/6	8/6	8/6	8/6	8/6	8/6	8/6	8/6	8/6
3 poles	8/6	8/6	8/6	8/6	8/6	8/6	8/6	8/6	8/6
4 poles	8/6	8/6	8/6	10/6	10/6	10/6	10/6	14/6	14/6
5 poles	8/6	8/6	10/6	10/6	14/6	14/6	14/6	22/6	22/6
6 poles	8/6	10/6	10/6	10/6	14/6	14/6	14/6	26/6	26/6
7 poles	10/6	10/6	10/6	14/6	18/6	18/6	18/6	30/6	30/6
8 poles	10/6	10/6	10/6	14/6	18/6	18/6	18/6	34/6	34/6
9 poles	10/6	10/6	14/6	14/6	22/6	22/6	22/6	38/6	38/6
10 poles	10/6	10/6	14/6	18/6	22/6	22/6	22/6	42/6	42/6
11 poles	10/6	14/6	14/6	18/6	26/6	26/6	26/6	46/6	46/6
12 poles	10/6	14/6	14/6	18/6	26/6	26/6	26/6	50/6	50/6

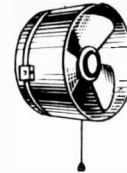

### EXTRACTOR FAN

Cleans the air at the rate of 10,000 cu ft per hour. At the pull of a cord it extracts grease, grime and cooking smells before they dirty decorations. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2in casing with 5 1/2in fan blades. Suitable wherever it is necessary to move air fast. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. 38/6 plus 6/6 post and ins.

### MULTI-SPEED MOTOR

Replacement in many well-known food mixers. Six speeds are available 500, 850 and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 3,000, 12,000 and 15,500 r.p.m. (ideal polishing speeds) from the main drive shaft. This drive shaft is 1in diameter and approximately 1in long. A further point about this motor is that being 230/240V a.c.-d.c. series wound its speed may be further controlled with the use of our Thyristor controller. This is a very powerful and useful motor size approx. 2in diameter x 5in long, mains or 230/240V. Price 17/6 plus 4/6 p. & ins. 12 or more post free.

### MAINS OPERATED CONTACTOR

230/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2 1/2". 19/6 each.

### CORONET CAMERA

at a fraction of maker's price. 19/6 plus P. & P. 2/6 plus this FREE ever-ready drop-front case and shoulder strap. British made with precision auto-focus lens. Perfect pictures in colour and B. & W. 12 pictures on Kodak 127 film. Extremely strong and robust. 14 days' free trial. We guarantee to return your money in full if you can't take perfect pictures.

### THE FULL-FI STEREO SIX

#### The amplifier



sensation of the year You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled and leak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. Price is 28.19.6 plus 7/6 post and insurance.

Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. S.A.E. with enquiries please.

## ELECTRONICS (CROYDON) LTD

Dept. PE, 266 London Road, Croydon CR0 2TH  
Also 102/3 Tamworth Road, Croydon

## NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 45"-; 11 element, 52.6"; 14 element, 60"-; 18 element, 70"-; Wall Mounting with Cranked Arm, 7 element, 65"-; 11 element, 75"-; 14 element, 82.6"; 18 element, 90"-; Chimney Mounting Arrays Complete, 7 element, 80"-; 11 element, 87.6"; 14 element, 95.6"; 18 element, 105.6". Complete assembly instructions with every aerial. Low Loss Co-axial Cable, 1.8 yd. King Teleboosters—Labgear U.H.F. Boosters from 75"-; Belling Lee "Concord" all Band U.H.F. U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. p.p. Aerials 8". Accessories 3". C.W.O. or C.O.D.

### BBC·ITV·FM AERIALS



B.B.C. (Band 1). Loft, 25"-; Wall S.D. 32.6"; "H" array, 60"-; I.T.V. (Band 3). 5 element loft array, 45.6"-; 7 element, 53.6"-; Wall mounting 5 element, 63.6"-; Combined BBC ITV loft 1 + 5, 55.6"-; 1 + 7, 67.6"; Wall mounting 1 + 5, 57.6"; Chimney mounting 1 + 5, 90.6"-; Pre-amps from 75.6".

Combined BBC1 ITV BBC2 Aerials, 1 + 5 + 9, 80.6"-; 1 + 5 + 14, 90.6"-; 1 + 7 + 14, 100.6"-; Available loft only.

F.M. Radio Loft S.D. 19.6". "H" 38.6". 3 element array, 57.6". Standard co-axial cable, 1-yd. Coax plugs, 1.8". Outlet boxes, 6". Diplexer crossover boxes, 17/6. p.p. Aerials, 8"; accessories, 3". C.W.O. or C.O.D. (min. C.O.D. charge 3/6.) 1" for fully illustrated Lists.

CALLERS WELCOMED


OPEN ALL DAY SATURDAY

**K.V.A. ELECTRONICS (Dept. P.E.)**  
40-41 Monarch Parade  
London Road, Mitcham, Surrey  
01-648 4884

## NEW! HANDY! TIDY!
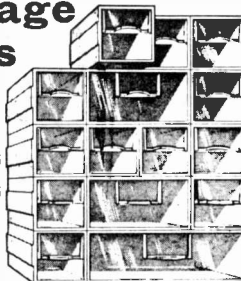
## multi-drawer I-N-T-E-R-L-O-C-K-I-N-G storage units

A PLACE  
FOR  
EVERYTHING  
EVERYTHING  
IN ITS  
PLACE!



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

### BUY AT TRADE PRICES!

**SINGLE UNITS** (5ins x 2 1/2ins 2 1/2ins)  
Usually 2/6 each, **OUR PRICE: 24/- DOZEN**  
**DOUBLE UNITS** (5ins x 4 1/2ins x 2 1/2ins)  
Usually 4/6 each, **OUR PRICE: 40/- DOZEN**

**PLUS QUANTITY DISCOUNTS!**  
Order £5 and over DEDUCT 1/- in the £  
Orders £10 and over DEDUCT 1/6 in the £  
Orders £20 and over DEDUCT 2/- in the £

PACKING/POSTAGE/CARRIAGE: Add 6/- to all orders under £3. Orders £3 and over, packing/postage/carrriage free.

QUOTATIONS FOR LARGER QUANTITIES



(Dept. PE12) 31 ALBERT RD.  
HENDON, LONDON, NW4

## 4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £22.0.0. P. & P. 9/- extra.

## INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Identical as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

### Transistor TELEPHONE AMPLIFIER



Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (PE.12)**  
169 KENSINGTON HIGH STREET, LONDON, W.8


# LST

# ELECTRONIC COMPONENTS LTD

## BETTER QUALITY, SERVICE, PRICES & LARGEST STOCKS

AC107	7/7	BA111	6/-	BFY51	3/9	NKT127	10/6	NKT263	4/8	NKT12429	OC205	9/-	40316	9/3	2N709	8/6	2N3707	2/10	3N142	10/9
AC126	5/1	BC114	3/1	BFY52	4/6	NKT128	10/6	NKT264	4/3		OC206	15/-	40317	7/3	2N711	7/6	2N3708	1/10	3N143	13/3
AC127	4/-	BA313	1/6	BFY90	13	NKT129	8/6	NKT265	5/6	NKT13329	OC207	15/-	40319	10/9	2N711A	7/6	2N3709	2/3	3N152	17/3
AC128	4/-	BC115	6/6	BSX19	3/3	NKT130	6/1	NKT270	2/10	NKT13429	OC271	19/6	40320	7/3	2N743	4/6	2N3710	2/3	AA119	2/1
AC176	5/-	BC118	7/6	BSX20	3/3	NKT141	10/6	NKT272	2/10		ORP12	10/-	40323	6/6	2N744	6/-	2N3711	2/6	AA111	2/1
AC187	6/-	BC125	11/-	BSX21	7/6	NKT142	10/-	NKT273	3/8	NKT16229	ORP60	8/-	40324	9/3	2N919	3/11	2N3820	18/9	AA12	6/-
AC188	6/-	BC126	11/-	BSX26	4	NKT143	9/6	NKT274	2/10		ORP61	8/-	40326	4/9	2N918	8/5	2N3826	25/-	BA110	6/-
AC177	5/9	BC143	15/-	BSY27	4	NKT144	8/-	NKT275	3/4	NKT20329	P346A	3/9	40344	5/3	2N929	5/3	2N3866	25/-	BA110	6/-
AC180	4/-	BC147	2/9	BSY95	2	NKT151	6/-	NKT276	3/6		RASS08AF		40347	7/6	2N930	6/-	2N4037	15/-	BA111	6/-
AC181	3/10	BC148	3/3	BSY95A	2	NKT154	6/-	NKT281	5/-	NKT20339				10/3	2N1131	6/-	2N4058	3/4	BA112	18/-
AC182	3/10	BC149	3/9	BYZ14	3/3	NKT161	6/-	NKT301	18/-	NKT35219	4 SIM	19/-	40360	8/6	2N1132	6/-	2N4059	5/-	BA115	1/6
AC183	3/10	BC169	3/9	BYZ15	3/3	NKT162	6/-	NKT302	12/5		15/9	ST2	9/9	11/6	2N1303	3/6	2N4060	5/-	BA130	3/6
AC184	3/6	BC171	2/-	C111	18	NKT163	6/-	NKT303	17/6	OC19	5/-	T1407	9/8	6/-	2N1304	4/11	2N4061	4/11	BA131	2/6
AC185	3/6	BC182L	2/3	C111E	12	NKT164	6/8	NKT304	9/10	OC22	19/6	T1C45	8/-	11/3	2N1305	4/11	2N4062	4/6	BA132	3/2
AC186	7/6	BC183L	1/10	C26	8	NKT165	6/-	NKT351	10/-	OC22	8/-	T1S44	17/6	10/3	2N1306	6/6	2N4287	3/-	BY127	4/-
AD140	11/6	BC184	3/-	CR1-05C	8	NKT166	6/-	NKT352	17/6	OC23	10/-	T1S44	1/9	27/6	2N1307	6/6	2N4288	3/-	BY120	3/1
AD141	11/6	BCY10	10/-	CR1-40C10	4	NKT201	6/-	NKT353	17/6	OC23	10/-	T1S44	1/9	11/3	2N1308	6/6	2N4289	3/-	BYX36/150	2
AD161	7/6	BCY12	12/-	DET16	12	NKT205	6/-	NKT401	14/6	OC26	6/6	TIP32A	14/10	16/6	2N1309	6/3	2N4290	3/-	BYX36/300	2
AD162	7/6	BCY12	12/-	DET16	12	NKT205	6/-	NKT401	14/6	OC26	6/6	TIP32A	14/10	16/6	2N1309	6/3	2N4290	3/-	BYX36/300	2
AD162	7/6	BCY12	12/-	DET16	12	NKT205	6/-	NKT401	14/6	OC26	6/6	TIP32A	14/10	16/6	2N1309	6/3	2N4290	3/-	BYX36/300	2
AD162	7/6	BCY12	12/-	DET16	12	NKT205	6/-	NKT401	14/6	OC26	6/6	TIP32A	14/10	16/6	2N1309	6/3	2N4290	3/-	BYX36/300	2
AD162	7/6	BCY12	12/-	DET16	12	NKT205	6/-	NKT401	14/6	OC26	6/6	TIP32A	14/10	16/6	2N1309	6/3	2N4290	3/-	BYX36/300	2
AD162	7/6	BCY12	12/-	DET16	12	NKT205	6/-	NKT401	14/6	OC26	6/6	TIP32A	14/10	16/6	2N1309	6/3	2N4290	3/-</		

# DISCOSOUND

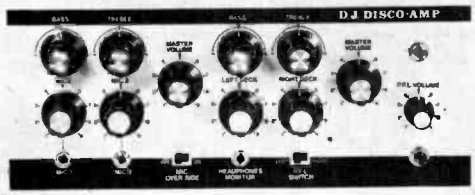

## D.J. DISCO-AMP

Designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

A complete Pre-fade listen (P.F.L.) cueing monitor section is featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half. Specification: Output power 70 watts R.M.S.  $\pm 1$  db at 8 ohms. Frequency response: 30-20,000 Hz  $\pm 3$ db. Harmonic distortion: Less than 1% at full output. Signal/noise ratio: Better than -65db. Inputs: Mic 1 & 2 5 mV at 50 K ohms. Turntable 1 & 2 100 mV at 1 meg ohm.

50 ohm or 600 ohm mic inputs may be ordered at extra cost. Size: Front Panel 16 1/2 in  $\times$  7 in. Cut out 15 1/2 in  $\times$  6 in. Fuses A.C. 1.5 amp (B.S.) mounted on back panel.

**PRICE £85.0.0 inc. P. & P.**



## D.J. 102 DISCOTHEQUE MIXER PRE-AMPLIFIER

Consists of a 4 channel mixer each with its own volume control and a complete P.F.L. monitoring system. Also features a mike cut down switch. For use with amplifiers having tone controls but not having the above facilities. Frequency response 20-20,000 Hz  $\pm 2$ db. Distortion less than 1%. Signal to noise ratio better than -65db. Size 10 1/2 in  $\times$  4 in  $\times$  4 in. Self powered.

**Price £25.0.0 inc. P. & P.**

## D.J. 30L PSYCHEDELIC LIGHT CONTROL UNIT

3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation. Completely built and tested



**PRICE £37.10.0 inc. P. & P.**

For full details of these and all Discosound Products write direct to:

# DISCOSOUND

122 BALLS POND ROAD, LONDON, N.1. Tel. 01-254 5779

Full money back guarantee if returned within 10 days  
All Discosound Products are guaranteed for 12 months  
Demonstrations given at any time

# BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these **EXCLUSIVE LOW PRICES**. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	Similar Types to:- Description	Price and qty. prices		
		1-24	25-99	100 up
BP00 7400N	Quad 2-Input NAND GATE	6/8	5/8	4/6
BP01 7401N	Collector	6/8	5/8	4/6
BP04 7404N	HEX INVERTER	6/8	5/8	4/6
BP10 7410N	Triple 3-Input NAND GATE	6/8	5/8	4/6
BP20 7420N	Dual 4-Input NAND GATE	6/8	5/8	4/6
BP30 7430N	Single 8-Input NAND GATE	6/8	5/8	4/6
BP40 7440N	Dual 4-Input BUFFER GATE	6/8	5/8	4/6
BP41 7441N	BCD to decimal decoder and NIT Driver	22/8	20/-	17/6
BP42 7442N	BCD to decimal decode (TTL O/P)	22/8	20/-	17/6
BP50 7450N	Dual 2-Input AND/OR/NOT GATE—expandable	6/8	5/8	4/6
BP53 7453N	Single 8-Input AND/OR/NOT GATE—expandable	6/8	5/8	4/6
BP60 7460N	Dual 4-Input—expandable	6/8	5/8	4/6
BP70 7470N	Single JK Flip-Flop—edge triggered	9/-	8/-	7/-
BP72 7472N	Single Master Slave JK Flip-flop	9/-	8/-	7/-
BP73 7473N	Dual Master Slave JK Flip-flop	10/-	9/-	8/6
BP74 7474N	Dual D Flip-flop	10/-	9/-	8/6
BP75 7475N	Quad Bistable Latch	11/-	10/-	9/6
BP76 7476N	Dual Master Slave Flip-flop with preset and clear	11/-	10/-	9/6
BP83 7483N	Four Bit Binary Adder	26/-	22/8	20/-
BP90 7490N	BCD Decade Counter	22/8	20/-	17/6
BP92 7492N	Divide by 12 4 Bit binary counter.	22/8	20/-	17/6
BP93 7493N	Divide by 16 4 Bit binary counter.	22/8	20/-	17/6
BP94 7494N	Dual Entry 4 Bit Shift Register	22/8	20/-	17/6
BP95 7495N	4 Bit Up-Down Shift Register	22/8	20/-	17/6
BP96 7496N	5 Bit Shift register	24/-	21/-	18/6

Data is available for the above Series of Integrated circuits in booklet form, price 2/6.

BRAND NEW. FULL TO MANUFACTURERS' SPECIFICATION	Price each		
	1-24	25-99	100 up
BP709 Operational Amplifier, dual in-line 14 pin package = 8N2709 and similar to MIC709 and ZLD709C.	10/8	9/-	8/-

This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

## TTL INTEGRATED CIRCUITS

Manufacturers "Fail outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work, on testing, some will be found perfect.

PAK No.	Qty.	Price	PAK No.	Qty.	Price
UTC00	5	7400N 10/-	UTC73	5	7473N 10/-
UTC01	5	7401N 10/-	UTC74	5	7474N 10/-
UTC02	5	7402N 10/-	UTC75	5	7475N 10/-
UTC03	5	7403N 10/-	UTC76	5	7476N 10/-
UTC04	5	7404N 10/-	UTC80	5	7480N 10/-
UTC05	5	7405N 10/-	UTC82	5	7482N 10/-
UTC10	5	7410N 10/-	UTC83	5	7483N 10/-
UTC20	5	7420N 10/-	UTC86	5	7486N 10/-
UTC40	5	7440N 10/-	UTC90	5	7490N 10/-
UTC41	5	7441AN 10/-	UTC92	5	7492N 10/-
UTC42	5	7442N 10/-	UTC93	5	7493N 10/-
UTC60	5	7460N 10/-	UTC94	5	7494N 10/-
UTC61	5	7461N 10/-	UTC96	5	7496N 10/-
UTC80	5	7480N 10/-	UTC96	5	7496N 10/-
UTC70	5	7470N 10/-	UTCX1	20	ASST'D 74's. 30/-
UTC72	5	7472N 10/-			

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

## DUAL-IN-LINE LOW PROFILE SOCKETS

14 and 16 lead sockets for use with Dual-in-Line Integrated Circuits.

Order No.	Pin type	Price each		
		1-24	25-99	100 up
TS014	14 pin type	7/8	6/-	5/3
TS016	16 pin type	10/-	8/8	7/9

## RTL FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits	Qty.	Price
Epoxy case To-5 temp. range 15°C to 55°C	1-11	12-24 25-99 100 +
$\mu$ L 900 Buffer	8/-	7/- 6/6 5/8
$\mu$ L 914 Dual two-input GATE	8/-	7/- 6/6 5/8
$\mu$ L 923 J-K Flip-flop	10/6	10/- 9/8 9/-
Full data and circuits for I.C.'s in Booklet form price 1/6 each.		
$\mu$ A703E Linear R.F. IF AMPLIFIER	11/-	10/- 9/- 8/3
PLASTIC CASE To-5 6 lead up to 100 m/cs.		

## DTL DIGITAL I.C.'s

DTL dual in-line package.	Price
Type MC844F expandable dual 4-input NAND Power Gate	10/- each
Type MC845P Clocked Flip-flop	15/- each
Type 862 Triple 3 Input NAND/NOR Gate	10/- each

FULL DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

## BI-PAK SEMICONDUCTORS P.O. BOX 6, WARE, HERTS.

Postage and packing add 1/-. Overseas add extra for Airmail. Minimum order 10/-.. Cash with order please.



# VALUE ALL THE WAY


## LINEAR INTEGRATED CIRCUITS

### BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)

BP709C, Operational amp. lifier, 15/- each.  
 BP701C, Operational amp. lifier (with Zener out- put), 12/6 each.  
 BP702C, Operational amp. lifier (with direct out- put), 12/6 each.  
 BP501, Wide band ampli- fier, 18/- each.  
 BP521, Logarithmic wide band amp., 14/- each.  
 BP20C, General purpose amplifier (TO-5 8 lead), (voltage or current amp.), 12/6 each.  
 I.C. Operational Amplifier with Zener output.  
**Type 701C.** Ideal for P.E. Projects. 8 Lead TO-5 case. Full data.

Our price **12/6** each  
 5 off 11/- each. Large Qty. Prices quoted for.

## IC AMPLIFIER

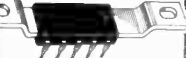

Identical encapsulation and pin configuration to the following: 8L402-3, 1C10 and 1C403. Each circuit incorporates a pre-amp and class A,B Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP.1010. **OUR LOWEST PRICE** 30/- each. 10 up 25/- each.

## MULLARD I.C. AMPLIFIERS

TA243, Operational amp. lifier, 70/- each.  
 TA263, Linear AF ampli- fier, 15/8 each.  
 TA293, General purpose amplifier, 21/- each.

## CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS

Audio Power Amplifier, 30/- each.

## OTHER MONOLITHIC DEVICES

D13D1 Silicon Unilateral switch 10/- each.  
 A Silicon Planar, mono- lithic integrated circuit having thyristor electrical characteristics, but with an anode gate and built-in "Zener" diode between gate and cathode. Full data and application cir- cuits available on request.

## Silicon Microwave Diodes - Sylvania (U.S.A.)

1N218 and 1N218R matched pair 8 Band mixer. Max. overall noise factor 13.7dB at 4,000Mc/s. Brand new and boxed. Clearance Price 6/- pair.

## EX-EQUIPMENT MULLARD

AF117 transistors. Large can 4 lead type. Leads cut short but still usable, real value at 1s for 10/-.

## ADI161 NPN

## ADI162 PNP

MATCHED COMPLE- MENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven out- put stages of Amplifiers and Radio receivers.

**OUR LOWEST PRICE OF 12/6 PER PAIR**

HIGH POWER SILI- CON PLANAR TRAN- SISTORS. TO-3.

FERRANTI ZT1487 NPN

VCE160 1.6 GA

VCE40 Pot. 75W

VEB8 8PF18-45

PRICE 15/- EACH

## 2N3055 115 WATT SIL. POWER NPN

**OUR PRICE 12/6 EACH**

## FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-18V. 400mV (DO-7 Case) 2/6 ea. 11W (Top- Hat) 3/6 ea. 10W (SO-10 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

## BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed Pak No. EQVT

T1 8 2G371A OC71

T2 8 2G374A OC75

T3 8 2G374A OC81D

T4 8 2G381A OC81

T5 8 2G382T OC82

T6 8 2G344A OC44

T7 8 2G345A OC45

T8 8 2G378 OC78

T9 8 2G399A 2N1302

T10 8 2G417 AF117

All 10/- each pack.

## EN600 NPN SIL. DUAL TRANS. CODE D1699

TEXAS. Our price 5/- each.

## 120 VCB NIXIE DRIVER TRANSISTOR.

8 Pin. BSN21 & C407. 2N1893

FULLY TESTED AND CODED ND120. 1-24 3/6

each. TO-5 N.P.N. 25 up 3/- each.

## Sil. trans. suitable for P.E. Organ. Metal TO-18

Eqv. ZT 300 1/- each. Any Qty.

## FREE

One 10/- Check you free with orders valued **£4** or over.

## NPN DIFFUSED SILICON PHOTO-DUO-DIODE TYPE

18701 (2N2175) for Tape Readout, high switching and measurement indicators. 50V. 250mW.

**OUR PRICE 10/- EACH, 50 OR OVER 8/6 EACH, FULL DETAILS.**

## FET'S

2N 3819 10/-

2N 3820 25/-

MPP105 8/-

## LOW COST P.E.T.'S

Fully Tested, Guaranteed Parameters eqvt. to 2N3819, MPP102, 2N-5459. 1-24 7/8 each; 25-95 6/3 each; 100 up 5/6 each. Coded FE19. Full data sent. TO-72 case.

## CADMIUM CELLS

ORP12 8/6

ORP60, ORP61 8/- each

## PHOTO TRANS.

OCPT1 Type. 8/6

## KING OF THE PAKS Unequalled Value and Quality

## SUPER PAKS

## NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	30 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1600 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	25 Silicon NPN Transistors like BC108	10/-
U20	12 1.5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, B8V27	10/-
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces	20/-
U29	10 1 amp SCR's TO-5 can up to 600 PIV CR81/25-600	20/-
U31	20 Sil. Planar NPN trans. low noise Amp 2N3307	10/-
U32	25 Zener diodes 400mW D07 case mixed Volts, 3-18	10/-
U33	15 Plastic case 1 amp Silicon rectifiers 1N4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY50/51/52	10/-
U37	30 Sil. alloy trans. SO-2 PNP. OC200 28322	10/-
U38	20 Fast Switching Sil. trans. NPN, 400Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
U41	25 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked!

## NEW LOW PRICE TESTED S.C.R.'S

1A	3A	7A	16A	30A
(TO-5 (TO-66 (TO-48 (TO-48 (TO-48				
case) case) case) case) case)				
PIV	each	each	each	each
50	4/8	5/-	9/8	10/6
100	5/-	6/6	10/8	12/6
200	7/-	7/6	11/6	15/-
400	8/6	9/6	13/6	18/6
600	10/8	11/8	15/6	25/-
800	12/6	14/-	18/-	30/-

## 2A POTTED BRIDGE RECTIFIERS.

200V 10/-

## TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

## PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/- . Plus 2/- P. & P.

## PLEASE NOTE.

To avoid any further increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organised and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-

## SIL. RECTS. TESTED

PIV	50A	10A	30A
50	1/-	2/9	4/3
100	1/3	3/3	4/6
200	1/9	4/-	4/9
300	2/3	4/6	6/6
400	2/6	5/6	7/6
500	3/-	6/-	8/6
600	3/6	6/9	9/-
800	5/6	7/6	11/6
1000	5/-	9/3	12/6
1200	6/6	11/6	15/-

## TRIACS

VBOM	2A	6A	10A
	(TO-1)	(TO-1)	(TO-1)
100	14/-	15/-	22/6
200	17/6	20/-	28/6
400	20/-	24/-	35/-

## LUCAS 35A SIL. RECTS.

Branded. 400 PIV. Special Price, stud type, flying lead, 22/8 each.

## UNIJUNCTION

UT46. Eqvt. 2N2646. Evt. TIS43. BEN3000 5/8 each. 25-99 5/- 100 UP 4/-

## NPN SILICON PLANAR

BC107/8/9 2/- each, 50-99 1/10; 100 up 1/8 each. Fully tested and coded TO-18 case.

## SILICON HIGH VOLTAGE RECTIFIERS

10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 18/- each.

## QUALITY-TESTED PAKS

6 Matched Trans. OC44/45/81/81D	10/-
20 Red Spot AF Trans. PNP	10/-
16 White Spot RF Trans. PNP	10/-
5 Silicon Rects. 3 A 100-400 PIV	10/-
2 10 A Silicon Rects. 100 PIV	10/-
2 OC1 140 Trans. NPN Switching	10/-
1 12 A SCR 100 PIV	10/-
3 Sil. Trans. 2N5033 PNP	10/-
3 200 Mc/s Sil. Trans. NPN BSY26/27	10/-
3 Zener Diodes 1W 33V 5% Tol.	10/-
4 High Current Trans. OC42 Eqvt.	10/-
2 Power Transistors 1 OC26 1 OC35	10/-
5 Silicon Rects. 400 PIV 250mA	10/-
4 OC75 Transistors	10/-
1 Power Trans. OC20 100V	10/-
10 OA202 Sil. Diodes Sub-min	10/-
2 Low Noise Trans. NPN 2N929/30	10/-
1 Sil. Trans. NPN VCB 100 ZT86	10/-
6 OA81 Diodes	10/-
4 OC72 Transistors	10/-
4 OC27 Transistors	10/-
4 Sil. Rects. 400 PIV 500mA	10/-
5 GET883 Trans. Eqvt. OC44	10/-
5 GET883 Trans. Eqvt. OC45	10/-
2 2N708 Sil. Trans. 300Mc/s NPN	10/-
3 GT31 LF Low Noise Germ. Trans.	10/-
6 1N914 Sil. Diodes 75 PIV 75mA	10/-
8 OA39 Germ. Diodes PNP-sub. min. 1N69	10/-
3 NPN Germ. Trans. 1N773 Eqvt.	10/-
2 OC22 Power Trans. Germ.	10/-
2 OC25 Power Trans. Germ.	10/-
4 AC128 Trans. PNP High Gain	10/-
4 AC127/128 Comp. pair PNP/NPN	10/-
3 2N1307 PNP Switching Trans.	10/-
7 CG62H Germ. Diodes Eqvt. OA71	10/-
3 AF115 Type Trans.	10/-
12 Assorted Germ. Diodes Marked	10/-
4 AC126 Germ. PNP Trans.	10/-
4 Silicon Rects. 100 PIV 750mA	10/-
3 AF117 Trans.	10/-
7 OC81 Type Trans.	10/-
3 OC171 Trans.	10/-
8 2N2926 Sil. Epoxy Trans.	10/-
7 OC71 Type Trans.	10/-
2 28701 Sil. Trans. Texas	10/-
2 10 A 600 PIV Sil. Rects. 1A45R	10/-
3 BC108 Sil. NPN High Gain Trans.	10/-
1 2N910 NPN Sil. Trans. VCB 100	10/-
2 1000 PIV Sil. Rect. 1-5 A R53310 AF	10/-
3 BSY95A Sil. Trans. NPN 200Mc/s	10/-
3 OC200 Sil. Trans.	10/-
2 GET880 Low Noise Germ. Trans.	10/-
1 AF139 PNP High Freq. Trans.	10/-
3 NPN Trans. 1ST141 & 2ST140	10/-
4 Madt's 2 MAT100 & 2MAT120	10/-
3 Madt's 2 MAT101 & 1 MAT121	10/-
4 OC44 Germ. Trans. AF	10/-
3 AC127 NPN Germ. Trans.	10/-
1 2N3906 Sil. PNP Trans. Motorola	10/-
2 Sil. Power Rects. BYZ13	15/-
1 Sil. Power Trans. NPN 100Mc/s	15/-
TK201A	15/-
2 2N132 PNP Epitaxial Planar Sil.	15/-
3 2N697 Epitaxial Planar Trans. Sil.	15/-
4 Germ. Power Trans. Evt. OC16	15/-
1 Unijunction Trans. 2N2646	15/-
2 Sil. Trans. 200Mc/s 60Vct. ZT83/84	15/-
20 NKT Trans. AF. RF. VHF. Coef. Hyst. Evt. List	10/-
2 2N2719 Sil. Epoxy Planar HFE225	15/-
8 BY100 Type Sil. Rects.	20/-
25 Sil. and Germ. Trans. Mixed, all marked, New	30/-

## SEMICONDUCTORS FOR "P.E." 50 + 50AMP.

TYPE	EACH	TYPE	EACH
2N1613	4/6	1N914	1/-
2N3055	12/6	OA200	1/-
2N3820	3/-	BFY51	3/8
2N3704	6/6	BYZ13	4/6
2N3707	3/9	40362	14/-
2N3819	8/-	22V14W Zener	3/8

GIRO No. 388-7006


# BI-PAK



63A  
 High Street  
 WARE  
 Herts.
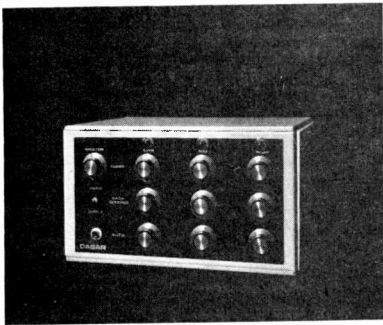
## KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK





## KINETIC LIGHTING EFFECTS

The DABAR range of Kinetic Lighting Effects encompass a wide range of sophisticated colour pulsing and blending units, designed for discotheques, dance halls, restaurants, shop-window displays, etc. Basically 3 facilities are available: A sound to light Psychodelic lighting unit or colour organ. This unit connects directly into an amplifier output or across loudspeakers (with negligible loading effect) and converts the audio frequency signals into a 3-colour light display; the colour depending on the frequency of the signal and the intensity of the light on the loudness of the audio source. Secondly a background control providing a variable minimum ambient lighting level if required and thirdly a colour blender providing a continuously and completely random slowly changing pattern of lights. This is fully automatic requiring no audio input and is controlled by 3 speed-control potentiometers.

Units are available providing loading of either 1kW of lighting per channel (3kW max per unit) or 3kW per channel (9kW max per unit). Latest full-wave Triac circuitry is used and radio-frequency interference filters are fitted in all units.

Case size: 13in x 7in x 9in.


Audio Activated Colour organ incorporating background controls.  
1kW per channel £50      3kW per channel £88

Colour blender:

1kW per channel £40      3kW per channel £78

Audio activated colour organ with background controls and colour blender:

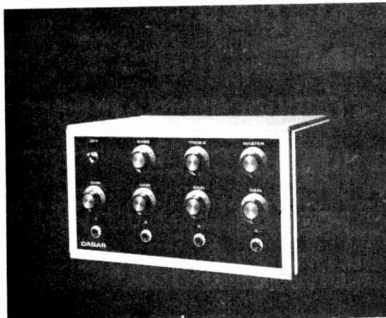1kW per channel £60      3kW per channel £98



## 100 WATT AMPLIFIER

The latest addition to the DABAR range of equipment is a 4 channel integrated Preamplifier and Power amplifier, delivering a full 100W r.m.s. into a 4 ohm load. The amplifier has 4 inputs, each with their own gain control and a further master gain control, treble and bass control. A unique feature of this amplifier is in its versatility of uses. It has been designed to accept plug-in pre-amp cards for each channel thus covering a wide range of applications. The basic unit is supplied with 4 input modules of your choice, but further modules may be purchased at moderate cost, thus enabling, with the minimum of time, effort and outlay the conversion of any one or all channels to accept an entirely different input.

Modules available include: P/U cartridges—crystal, ceramic, and magnetic (equalised R.I.A.A.); Microphones—30-60Ω, 300-600Ω and 50kΩ types. Guitar and two modules for high impedance outputs from tape, tuner, etc., 100mV f.e.t. and IV input.

Case size: 13in x 7in x 9in.

Price complete with 4 modules £109.00

Extra modules £5.00 each.

Please send 1/- in stamps for full descriptive literature.

**TRADE ENQUIRIES WELCOME**

Callers by appointment only. Carriage extra.

## DABAR ELECTRONIC PRODUCTS

98a LICHFIELD STREET, WALSALL, STAFFS. WS1 1UZ  
Tel.: WALSALL 34365

## 1 MILLION SILICON PLANAR TRANSISTORS

### NPN-PNP PLASTIC AND METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

#### TYPE STN18

Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77. Price: 500 £9, 1,000 £15

#### TYPE STP18

Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18. Price: 500 £9, 1,000 £15

#### TYPE STNL

Silicon Plastic Epitaxial Planar Transistors TO-92 case. I.C. 200mA, 300mW medium to high gain, available in npn or pnp and types similar to: npn 2N2926 — 2N2711 — 2N3391 — 2N3707 — 2N3711 — BC167-8-9. Price: 500 £7.10.0; 1,000 £13

#### TYPE STPL

As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL. Price: 500 £7.10.0; 1,000 £13

#### TYPE STNK

Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration, I.C. 200mA, 300mW and similar to BC170-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8. Price: 500 £9.10.0; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.

All goods Ex-stock sent by return. Cash with order please to:

### DIOTRAN SALES

P.O. Box 5, WARE, Herts.

S.A.E. For full list of surplus semiconductors

## VALVES SAME DAY SERVICE

### NEW! TESTED! GUARANTEED!

#### SETS

1R5, 1R5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for 1R5/8, DAF96, DF96, DK96, DL96, 4 for 2R/

1A7GT 7/6	25U4GT11/6	DL92 5/9	EL500 12/6	PCL84 7/6	UAF42 10/3
1H6GT 7/3	30C1 6/8	EM34 6/9	EM34 14/6	PCL85 9/-	UCB41 10/6
1N5GT 2/8	30C15 13/-	DL96 7/3	EM80 8/3	PCL86 8/3	UBF80 5/9
1R5 5/9	30C17 16/-	DX86 5/9	EM81 8/3	PCL88 14/6	UBF89 6/9
1R5 4/3	30C18 13/6	DX87 5/9	EM84 6/9	PCL80015/6	UCC84 7/-
1T4 3/-	30F5 15/6	EAB180 6/6	EM87 7/6	PENA4 8/6	UCC85 7/3
3B4 5/9	30FL1 12/9	EAF42 10/-	EY51 7/3	PEN38G14/-	UCB90 7/3
3V4 6/9	30FL12 14/6	EB01 2/3	EY96 6/6	PFL20011/9	UCB42 12/6
5Y3GT 6/-	30FL14 14/-	ECB33 8/-	EZ40 8/-	PL36 9/9	UCH81 6/6
5Z4G 7/6	30L1 6/8	EB41 10/6	EZ41 8/-	PL81 9/3	UCL82 7/-
6/30L2 11/9	30L15 13/-	EBF80 6/9	EZ80 4/6	PL81A 10/3	UCL83 21/-
6AL5 2/3	30L17 14/9	EBF89 6/3	EZ81 4/9	PL82 6/-	UF41 10/6
6AM6 2/9	30P4 13/-	ECC81 3/9	GZ32 8/9	PL83 6/6	UF85 6/9
6AQ5 5/3	30P12 13/9	ECC82 4/9	GZ34 9/9	PL84 6/6	UF99 6/9
6AT6 4/6	30P19 13/-	ECC83 7/-	KT41 15/6	PL600 13/-	UL41 12/-
6BA6 4/6	30PL1 12/9	ECC85 5/9	KT61 9/9	PL564 13/6	UL44 20/-
6BE6 4/9	30PL13 14/6	ECC804 12/-	KT66 16/9	PL508 2/3	UL84 7/-
6BJ6 8/6	30PL14 14/-	ECF80 6/-	LN329 14/6	PM54 7/6	UM80 5/6
6CB6 4/9	35LGGT 8/9	ECF82 6/-	N78 17/6	PX25 23/6	UM84 4/6
6CD6G 22/-	35W4 4/6	ECH35 6/3	P61 10/-	PY32 10/-	UY41 7/6
6F14 9/-	35Z4GT 5/-	ECH42 12/9	PAB080 7/-	PY33 10/-	UY85 5/9
6P23 13/9	150B2 13/6	EOH81 5/9	PC86 10/3	PY81 5/3	VT48 15/6
6F25 12/6	807 9/-	ECH83 8/3	PC88 10/3	PY82 5/3	W119 7/9
6K71 2/6	0068 12/6	ECH84 3/6	PC89 8/6	PY83 5/9	Z77 4/6
0K8G 3/6	ACV1215/6	ECL80 7/-	PC87 8/6	PY88 6/9	AC107 3/6
6V6G 3/6	AZ31 9/6	ECL82 6/9	PC900 7/6	PY800 7/6	AC127 2/6
6V6GT 6/6	B349 13/-	ECL86 8/-	PC829 8/6	PY801 7/6	AD140 7/6
6X4 4/9	B729 12/6	E37A 4/6	PC85 6/-	R19 6/6	AF115 2/6
6X5GT 5/9	CCH35 13/6	EP39 4/6	PC89 8/6	R29 12/6	AF117 4/-
10F18 7/-	CL33 18/6	EP41 11/6	PC89 8/6	RU2150A	AF117 4/-
10P13 12/-	DA32 7/3	EP83 4/6	PC189 9/9	125 12/6	AF125 3/6
12AH8 45/-	DAF91 4/3	EP86 6/3	PCF80 6/6	U26 12/-	OC26 5/-
12AT7 3/9	DAF96 7/3	EP89 5/3	PCF82 6/6	U47 13/-	OC44 2/6
12AL6 4/9	DF33 7/9	EP91 2/9	PCF86 9/6	U49 12/-	OC45 2/6
12AU7 4/9	DF91 3/-	EP183 5/9	PCF800 13/6	U78 4/9	OC71 6/6
12AX7 4/9	DF96 7/3	EP184 6/9	PCF801 6/9	U191 12/6	OC72 2/6
12K8GT 7/3	DH77 4/6	EP80 4/6	PCF802 9/-	U193 8/6	OC75 2/6
19BG0G17/6	DK32 7/6	EL33 9/9	PCF803 13/6	U251 14/6	OC81 2/6
20F2 13/6	DK91 5/9	EL34 9/6	PCF806 11/3	U301 10/6	OC81D 2/6
20P3 11/9	DK92 8/6	EL41 11/-	PCF808 14/-	U329 14/6	OC82 2/6
20P4 18/6	DK96 7/3	EL84 4/9	PCL82 7/3	U801 19/6	OC82D 2/6
25L6GT 5/-	DL35 5/-	EL90 5/3	PCL83 12/-	UAB080 6/6	OC170 4/6

## READERS RADIO (P.E.)

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.



## KONTAKT 60

**FOR INACCESSIBLE CONTACTS**—More than just a cleaner. **KONTAKT 60** guarantees perfect cleaning of contacts chemically in accordance with today's technology.

**KONTAKT** offers the following advantages:—

1. Dissolves oxides and sulphides the safe way without attacking contact substances.
2. Contains carefully selected solvents which do not attack plastics whereas they do dissolve resinified contact greases and dirt.
3. Contains *no silicone*.
4. Contains a light lubricant in order to avoid the contact paths being corroded.
5. Prevents further oxidation setting in.
6. Prevents "creep" currents.

Because of these outstanding properties **KONTAKT 60** is one of the best and most popular contact cleansing agents in the world.

Users include: Rolls Royce Ltd., C.E.G.B., South of Scotland Electricity Board, Trinity House Workshops, Kolster Brandes, Mullard, Plessey Cos., etc.

### OTHER KONTAKT PRODUCTS ARE:

70 Protective Lacquer                      80 Special Siliconized Polish  
72 Insulating Spray                      100 Antistatic Agent For Plastics  
75 Cold Spray For Fault Location 101 Dehydration Fluid

Write for full details of above complete range of Kontakt products to:—

### SPECIAL PRODUCTS DISTRIBUTORS LIMITED

81 Piccadilly, London, W.1                      01-629 9556



## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75 ft. 18 gauge on plastic reel. Recommended retail price 15/-



### THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170 ft. 22 gauge on plastic reel. Recommended retail price 15/-



### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	3/-*
Size 5 (ill-ustrated)	Savbit	18	3/-*
15	60/40	22	4/-*

\*Recommended Price



### INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6



From Electrical and Hardware shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**

If you're a telecommunications man and match up to the qualifications below cut yourself into a slice of Britain's future



Become a

# Radio Technician

in the fast-growing world of Air Traffic Control

Please send me an application form and details of how I can join the fascinating world of Air Traffic Control Telecommunications

Name .....

Address .....

PET/E2

Not applicable to residents outside the United Kingdom

To: A J Edwards, C Eng, MIEE,  
The Adelphi, Room 705, John Adam Street,  
London WC2N 6BQ,  
marking your envelope 'Recruitment'

**Sending this coupon could be your first step to a job that's growing in importance every year.**

The National Air Traffic Control Service needs Radio Technicians to install and maintain the vital electronic aids that help control Britain's ever-increasing air traffic.

This is the kind of work that requires not only highly specialised technical skills but also a well developed sense of responsibility, and candidates must be prepared to undergo a rigorous selection process. Those who succeed are assured a steadily developing career of unusual interest and challenge. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over); scale maximum £1590 (higher rates at Heathrow). There is a good annual leave allowance and a non-contributory pension for established staff.

You must be 19 or over, with at least one year's practical experience in telecommunications, ('ONC' or 'C and G' qualifications preferred).

## NATCS

National Air Traffic Control Service

# Practical Electronics Classified Advertisements

RATES: 1/6 per word (minimum 12 words). Box No. 1/6 extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London, E.C.4

## MISCELLANEOUS

### PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use R.F. SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM! IF REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"!

### BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY  
Designs by GERRY BROWN and JOHN SALMON  
and presented on TV

### BIG BARGAIN PARCEL 13/- POST PAID

Containing multi-contact relay, transistors, resistors (some high stab), rectifiers, diodes, capacitors, pots, knobs, etc.

### 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **72/6 POST PAID**

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists

**GARRARD RECORD PLAYER UNITS**  
The Garrard 2025TC with (GCS36) Cartridge for Stereo or Mono Records, complete with Plinth and Top Cover.



only £15 plus 10 6 post and packing  
Also available: Garrard SP25 Mk. 1IC with GP93/1 Cartridge, £22. Garrard X30 with GP104 Cartridge, £18. Also manufacturers of HI-FI amplifiers and car radios.

**SUNDERLAND ELECTRICS LTD.**  
48 Princess Street, Manchester M1 6HR  
Tel. 061-236 3652

**MUSICAL MIRACLES!** Drum, Cymbals, Waa-waa and Fuzz modules. New unique effects units, Percussion, etc. Good waa-waa kits 49/-. Famous "Mister Bassman" bass pedal unit. Also bargain components list of reed switches, etc. Send S.A.E. NOW! D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset.

### ENAMELLED COPPER WIRE

S.W.G.	Per 1/2 lb reel	Per 1 lb reel
18-22	11/3	16/6
23-30	11/9	17/6
31-35	12/3	18/6
36-40	15/-	24/-
41-44	17/9	29/6

Orders despatched by return of post. Please add 1/- per item P. & P. Supplied by: BANNER TRANSFORMERS, 84 Old Lansdowne Road, West Didsbury, Manchester, 20. TRADE ENQUIRIES INVITED.

**WATCHES**, chronographs, binoculars, transistor radios. Comprehensive and varied selection. Free illustrated brochure. MARCOT-MAIL, 120 Sidney Grove, Newcastle.

## MISCELLANEOUS (continued)

### NOW FULL SIZE 18 ELEMENT T/V AERIAL TO GIVE BETTER PICTURES



FOR ONLY 39/11 P.P. + 6/10

WHAT A FANTASTIC BUY. SAVE MONEY AND DO IT YOURSELF. RECEIVES BBC1, BBC2 and ITV ON UHF 625 CHANNELS, COLOUR AND BLACK/WHITE.

Yes a full size 18 element Aerial to give better and clearer reception. Ideal for the Do-it-yourself person, easy to fit. Can be used inside or out. Complete with bracket and instructions. Only 39/11 + 6/10 P.P. Money back guarantee.

### IMPERIAL TRADING

Dept. P.E., 45 Arkwright St., Nottingham

## TOP TRANSISTORS

ACY22 1/9	OC72 1/9	2N2926 1/9
BFY51 1/9	OC200 1/9	2N3702 1/9
BFY52 1/9	OC201 1/9	2N3703 1/9
BSY27 1/9	OC202 1/9	2N3705 1/9
OC45 1/9	ZTX300 1/9	2N3706 1/9
OC71 1/9	2N706 1/9	2N3708 1/9

All the above types are available at 16 for £1. Brand New. Individually Tested, unmarked, but guaranteed to be within their correct specification, or money refunded.

### ANTEX SOLDER IRON

A lightweight iron with a 15 watt nickel plated bit. Designed to enable you to weld reliable joints accurately. Model CN240 volts. Special low price. Act Now. Only 29/11.

MONEY BACK GUARANTEE. P. & P. I/-  
J. M. KING (K)

17 Buckridge, Portpool Lane, London, E.C.1

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND 95/- NOW

TO: 'BOFFIN PROJECTS'

DEPT. K2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

We stock all those components and materials required by the home HI-FI constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send 5/- stamps NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 10s.). No callers please, mail-order ONLY.

**AUDIOSCAN** Dept. P.E.12  
4, PRINCES SQUARE,  
HARROGATE, YORKS.

## MISCELLANEOUS (continued)

For all your NAMEPLATES, DIALS, ESCUTCHEONS, INSTRUCTION TABLETS, PRINTED CIRCUITS, on metal, plastics, foils, etc., contact the specialists. Quotations on request.

### RACET DESIGNS

Barnsdale, Nethergate, Westwoodside  
Doncaster, Yorks.

### COMPUTER PANELS AT BARGAIN PRICE.

Few hundred left at 5/- each. 8x0U43 or GET875+24 OASL. Useful length leads. C.W.O.P. & P. 6d each. Mail order only. F. & H. GUY LTD., 80 High Street, Ware, Herts.

**CIRCUIT BOARD ETCHING KITS**, full instructions. 19/6d. C.W.O. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

**BUILD IT** in a DEWBOX quality cabinet 2in x 2in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

**SCRAP VALVES WANTED.** Type TY5-500, TY6-800, TY6-1250A, TY7-6000A, TY8-5-3000, ESA1500, 16P13, BW1169, also similar types. ELECTRONIC HEAT CO., 352 Lower Addiscombe Road, Croydon. Tel. 01-654 7172.

**CLEARING LABORATORY**, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.T.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

**TINY TRANSISTOR MODULES**, can be used as multivibrators, bistables, monostables, code practice oscillators, divide by two circuits, etc. with a few additional components to decide function. Full information with every module. Price £1. MICROTROXIC, 70a Sydenham Park Road, London S.E.26.

**PARAPHYSICAL LABORATORY**, Downton, Wilts. Fascinating international magazines. S.A.E. for list. Parcel 20s.

## FOR SALE

**ELECTRONIC ORGAN** for sale. Solette 5-octave, 13 stops. Built-in speakers. Excellent condition. £65. Can deliver. Box No. 32.

**SEEN MY CAT?** 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

## MORSE MADE !!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 8d. stamp for explanatory booklet to: GSHSC (Box 19), 45 GREEN LANE, FULBY SURREY

**NEW CATALOGUE** No. 18, containing credit vouchers value 10/-, now available. Manufacturers' new and surplus electronic and mechanical components, price 4/6, post free. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

## WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

**HIGHEST CASH PRICES** for good quality Tape Recorders. 9.30 to 5.00. Immediate quotations. Tel. 01-472 2185.

**TOP PRICES PAID**  
for new valves and components

Write:  
**KENSINGTON SUPPLIES**  
(B) 367 Kensington Street  
Bradford 8, Yorks.

## HI-FI EQUIPMENT

**SHURE GOLDRING** Cartridges. Post Free. G800, M44/5/7 £7.17.6. M3D £5.5.0. M44E £8.19.6. M55E £9.19.6. M75E/2 £16.10.0. Garrard SP25/2 £10.17.6. AP.75 £16.17.6. P. & P. 7/6. **ULTIMATE ELECTRONICS**, 38 Achilles Road, London, N.W.6. Mail Order Only.

## SERVICE SHEETS

**SERVICE SHEETS.** Radio, TV, etc., 8,000 models. List 2/-. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

## LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, CAR RADIOS  
5/- EACH, MANUALS FROM 10/-  
PLUS LARGE S.A.E.

(Uncrossed P.O.'s please, original returned if service sheets not available.)  
FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER

**C. CARANNA**  
71 BEAUFORT PARK, LONDON, N.W.11  
MAIL ORDER ONLY

**RADIO TELEVISION**, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Rd., London, W.6 (01-743 8441).

## EDUCATIONAL

**HUNDREDS OF TOP PAID JOBS** in engineering await qualified men. Get a certificate through B.I.E.T. Home study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful FREE book, B.I.E.T., Department 125K, Aldermaston Court, Reading, RG7 4PF.

**A.M.S.E. (Elec.)**, City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio and TV, etc. Send for full details and illustrated book — FREE. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, Dept. 124K Aldermaston Court, Reading, RG7 4PF.

## COLOUR TV SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV engineer technician, and approved by leading manufacturer. Full details from ICS (D.561), Intertext House, London, S.W.8, or phone 01-720 1983.

## RECEIVERS AND COMPONENTS

**PRINTED CIRCUIT BOARDS** for P.E. PROJECTS  
All boards drilled and roller tinned complete with layout drawing.

### EXAMPLES

Marine Tachometer (May 1970) 5/- ea. Musical Stave (May 1970) 8/- ea.  
Waa-Waa pedal Vol. 4 No. 7 2/9 ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 8/6 ea.  
S.A.E. for List. Now available from: HENRY'S RADIO LTD., Edgware Road, London, W.2  
P.H. ELECTRONICS, Industrial Estate, Sandwich, Kent. Tel. 2517

## DRY REED INSERTS

Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 12/6d. per doz.; 75/- per 100; £27.10.0 per 1,000; £250 per 10,000. All carriage paid.

**G.W.M. RADIO LTD.**  
40/42 Portland Road, Worthing, Sussex 0903 34887

## NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only 68/-. P. & P. Free U.K. only

Postal Orders, Cheques to:

Dept. P.E.  
Galleon Trading Co., 25 Avelon Road,  
Romford, Essex

## RECEIVERS AND COMPONENTS

(continued)



Printed circuit boards for Practical Wireless and Practical Electronics projects from September, 1970. All boards are roller tinned, drilled, and have the circuit layout printed in white. S.A.E. for list, including this month's projects.

'MICROBOARD'—just 1.25 ins. by 0.9 ins. Holds a single DIL 14 or 16 leads—ideal for experiments with logic devices. 2/- plus S.A.E.

**ALBOL ELECTRONIC & MECHANICAL PRODUCTS LTD.**  
2 Vine Lane, Tooley Street  
London, S.E.1 Tel. 01-407 4214

## FULL SPECIFICATION COMPONENTS

Electrolytics 50 uf at 50 volts 1/6 each.  
Plessey SL403A I.C. amplifier 44/- each.  
Plessey 5L702C op. amplifiers 21/- each.  
2N1711 silicon planar transistors 5/6 each.  
2N706 3/-; 2N1305 3/3; BC108 2/3;  
2/- p. & p. on orders under £2. Catalogue 1/-.

## SPECIALIST ELECTRONICS CO.

26 York Road, Crosby, Liverpool L23 5TS

**MULLARD CR25 RESISTORS**, 0.4W 5% HS 2.5 x 7mm 1/4 each. 47 Ω-1M Ω. P. & P. 1/-. **SPRING ELECTRONICS LTD.**, 25 Cranley Gardens, Muswell Hill, N.10.

## SITUATIONS VACANT



Established 1891

# TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

## NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

## INTERNATIONAL CORRESPONDENCE SCHOOLS

A WHOLE WORLD  
OF KNOWLEDGE  
AWAITS YOU!

International Correspondence Schools  
(Dept. 152), Intertext House, Stewarts Road,  
London, S.W.8

NAME.....  
Block Capitals Please

ADDRESS.....

AGE..... OCCUPATION..... 12/70

## RECEIVERS AND COMPONENTS

(continued)

**POLYSTYRENE CAPACITORS** 125 or 350V, 150, 180, 330, 390, 560, 680, 820, 1,000, 2,200, 2,700, 5,600, 6,800, 8,200, 125, 15, 22, 100, 220, 1,200, 1,500, 3,300, 3,900, 0-01, 0-012, 0-015; Paper 100V, 100, 1,000, 2,000, 5,000, 3/- doz. Post 1/6.

**COMPUTER PANELS**, 5-BC108 diodes 3/- ea. 4 for 10/-. Post 1/6. 8-OC76 or OC72 or OC42, 8-0A10, 7/8. 8-OC43 or GET875, 24 OA81, 7/8. 8-OC170 diodes, etc. 7/8. 2-OC170, 2 GET875 or 4MD834, 5-100MFD 12V electrolytics, pot. core, etc. 6/-. 10-BSX26. 550MEG silicon npn diodes, etc. 7/8.

**MIXED TRANSISTORS ON PANELS** 50 for 12/8. 100 for 20/-. Panels with capacitors, resistors, diodes, 6 for 5/-. Air spaced trimmers, 25 and 100pF, 2/-. Ceramio 40, 60, 125pF, 6d.

**SEL. RECTIFIER AND VARIABLE RESISTOR** in neat case. Input 15V, output 0-12V at lamp 8/-.  
**MIDGET BELAYS** 1in x 1in x 1in, weigh 1oz. D.P.D.T. carry 2amp at 28V, 700 ohm coil, 10/6. With base, 12/6 Post free.

**M.C. METERS** 2in and 2 1/2in. 3 assorted for 21/-. M.C. Phones and mike, 45ohm, 12/6. P. & P. 2/- unless stated otherwise.

**J.W.B. RADIO**

75 Hayfield Rd., Salford 6, Lancs.

## R & R RADIO

51 Burnley Road, Rawtenstall  
 Rossendale, Lancs

Tel.: Rossendale 3152

VALVES BOXED, TESTED & GUARANTEED

EBF80	3/-	PCC84	3/-	PY81	3/6
EBF89	3/6	PCF80	3/-	PY82	3/-
ECC82	3/-	PCF82	3/6	PY800	3/6
ECL80	3/-	PCL62	4/-	PY801	3/6
EF80	1/6	PCL83	4/-	UI91	4/6
EF85	3/-	PL36	5/-	30F5	2/6
EY86	4/-	PL81	4/-	30P12	4/6
EZ40	4/6	PL83	4/-	30C15	5/-
EBC41	4/6	PY33	3/-	50CD6G	7/6

POST, ONE VALVE 9d. TWO TO SIX 6d.  
 OVER SIX POST PAID.

**DECKS**. Garrard TA Mk II less cartridge, \$5. Decca 4-speed stereo auto change \$5.15 (complete). Balfour auto change \$5.15. Transistors mixed RF and AF unmarked, untested, 50, 7/8. 28300 and 28320 1/- each, 10/- doz. Baby alarm/intercom, 57/- each. C.W.O. Decks carriage included otherwise P. & P. 1/6 in E, minimum 1/6. **ELECTRONIC SERVICES** (CRANLEIGH), Mounthill, Ewhurst, Surrey.

### SUB-MINIATURE RESISTORS

SMALLER THAN A MATCH HEAD!

Microhm with Watt 5%. Values from 51Ω to 100KΩ 10d. each.

Microhm Metal Glue Resistors for the ultimate in D.I.Y. miniaturisation.

Integrated Circuits complete with data:

NS709A Type 709 Op. Amp.	10/-
PA234 1W Audio Amplifier	17/6
PA237 2W Audio Amplifier	31/6
SL402A 2W Audio Amplifier	35/-
D40C1 4W Darlingon Amplifier	13/6
MEL 11 Photo Darlingon Amplifier	9/6
Connectors for D.I.L. i.c.'s	6/-

Transistors:			
2N5172	1/9	BFX86	6/-
ME0412	3/9	BD124	12/-
2N4059	3/6	2N3055	14/-
RCA40583 Trigger Diode			5/3

Silicon Rectifiers:			
50V	1A 1N4000 Series		2/4
100V	1/5	400V	2/-
200V	1/6	600V	2/10
	1/9	800V	
	1,000V	3/4	
200V	1-5A PL4000 Series		2/6
	2/3	400V	

Bridge Rectifiers:			
1A 50V	7/6	1A 200V	8/-
		2A 400V	12/6

### JEF ELECTRONICS (P.E.12)

York House, 12 York Drive, Grappenhall  
 Warrington, Lancs. Mail Order Only  
 C.W.O. P. & P. 1/- per order. Overseas 7/6.  
 Money back if not satisfied.

**A CORNUCOPIA OF COMPONENTS!** Scarce valves, selected TV components, speakers and cabinets. Computer panels—long leads, NOT printed circuits. Transistors, resistors—new and recovered. State your requirements. S.A.E. for details MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

## RECEIVERS AND COMPONENTS

(continued)

**LOGIC I.C.s** from 2/6 each. Transistors similar 2N708 6/8 day. Recovered from computers, all good. **Computer Boards** with 10 transistors, 20 diodes; zeners, resistors, capacitors, trim pots, etc., 3/8 each, 5 for 14/-, 25 for 22.5. Post paid. S.A.E. list, data. PAWSON, 114 South Street, Armadale, W. Lothian.

**SILICON RECTIFIERS** 800PIV 500mA, 2/6; 24/- doz.; 400PIV 500mA 1/-, 0-1μF 500V d.c., 300V a.c. Dubillier Capacitors, 6/- doz., 42/- per 100. 400-200-50-16μF 300V, 6/- each, 23 doz. Acos GP91-35C, 18/-, or 15/- each in doz. Stereo GP-93-1, 24/6. Co-ax sockets on isolation panel, 1/3, 12/- doz., 24 per 100. Jack plugs standard, 1/9, 3-5mm 1/3, 12/- doz., P. & P. 2/- per order. M. DZUBAS, 158 Bradshawgate, Bolton, Lancs.

**BRAND NEW ELECTROLYTICS** 15/16V 0.5, 1, 2, 5, 10, 20, 30, 40, 50, 100mF, 9d. E12 series 5% resistors, Carbon Film 1W 1Ω to 1MΩ, 1-5d. Wirewound 5W 15Ω to 15KΩ, 10d. Postage 1/-. The C.R. SUPPLY CO., 127, Chesterfield Rd., Sheffield, S8 0RN.

**HIGHEST GAIN** low-noise npn, BC169C, hfe=450-900, mint, branded, 4 for 10/-. U.K. post paid. List 6d. AMATRONIX LTD., 396 Selsdon Road, South Croxdon, Surrey, CR2 0DE.

## AERIALS

**NEW...**



**ELECTRICAL CIRCUIT TESTER**

**SAVE MONEY, DO YOUR OWN REPAIRS**

**SIMPLE TO USE**

**ONLY 9/11**  
 + 2/7 PP  
 2 for 22/6  
 Post Paid

A must for the Do-It-Yourself and Professionals. Tests radios, televisions and electrical wiring, and most components including motors, transformers, diodes, fuses, valve filaments and many others. Complete with instructions, free batteries, and of course our money back guarantee. Send now for immediate delivery.

**IMPERIAL TRADING**

Dept. P.E., 45 Arkwright St., Nottingham

## LADDERS

**VARNISHED TIMBER** from manufacturer. Lowest prices anywhere: 15ft. ext., \$5.10; 17ft. ext., \$5.15; 20ft. ext., \$6.5; 21ft. ext., \$7; 24ft. ext., \$8.2; 29ft. ext., \$9.5; 31ft. ext., \$11.2; 36ft., triple ext., \$14.10. Carr. 13/6. Free Lists. Also aluminium ext. and loft ladders. Callers welcome. Dept. P.E., HOME SALES, Baldwin, Road, Stourport, Worcs. Tel. Stourport 2574.

## ELECTRICAL

**240 VOLT ELECTRICITY ANYWHERE**



**BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scoop Purchase. The fabulous Mk.12D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most Brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested. Only £4.19.6 + 10/6 postage. C.O.D. with pleasure, refund guarantee. Please send S.A.E. for illustrated details.

**Dept. PE, STANFORD ELECTRONICS**  
 Rear Derby Road, North Bromesdale  
 Blackpool, Lancashire

## BOOKS AND PUBLICATIONS

### SPECIAL OFFER

THE FIRST VOLUME ON TRANSISTORS  
 in a new series entitled

THE

### SEMICON INDEX

to be published in conjunction with

### AVO LIMITED

will be ready at the end of September

Brochure available

Designed to provide comprehensive technical data on semiconductors and to be updated annually, the first volume covers over 16,000 transistors of international origin with 18 sections, a cross reference index, over 600 outline drawings, CV numbers, equivalents and manufacturers.

Invaluable to all Engineers and Buyers

### SECURE YOUR COPY NOW

Send the special pre-publication offer price

of 79/6d + 5/6d P. & P. direct to

Functional Publication Services Ltd.

29 Denmark Street, Wokingham, Berks.

(Normal price to be £5.5s.)

## AUDIO EFFECTS

5 SHAW LANE, HALIFAX, YORKS.

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

### AMATEUR BANDS ALL TRANSISTOR

**SUPERHET RECEIVER KIT.** No fuse, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Persepe front panel. Push button AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denoc plug in coils 3T. 0-5 to 1.54 Mhz 3T. 1-67 to 5-3 Mhz 4T. 5-0 to 15 Mhz 5T. 10-5 to 5-3 Mhz Range 3T normally supplied with kit. Uses 9 Volt battery. Easy step by step instructions. Complete Kit. \$8.19.6 plus 5/6 P.P. & Ins. Extra ranges 12/- per range.

**POWER CONTROLLER.** Power at your finger tips. Not merely half watt control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3Kw triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions \$8.9.6. Ready built \$9.4 plus 5/6 P.P. & Ins.

**REVERBERATION AMPLIFIER.** Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2in x 3in x 4 1/2in. \$10.4.0. P.P. & Ins. 6/-.

**VOX SWITCH.** This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 42/6. Ready built, tested and guaranteed. 60/6 post paid.

**METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive polythene case, 37/6 post paid.

**MORSE OSCILLATOR.** PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 27/6 post paid.

**STRAIGHT FROM THE PRESS.** Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi, Tape, etc., etc. 32/6 post paid.

**TEXAS TRANSISTORS.** Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 0/6 post paid.





**G. F. MILWARD** MAIL ORDERS: DRAYTON BASSETT, TAMWORTH, STAFFS.

# ELECTRONIC COMPONENTS

Wholesale/Retail: 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

<b>RESISTORS:</b>	
Carbon 1/4W	100 10/-
1/3W	100 10/-
Wirewound, Multitapped	10 10/-
1-3W	20 10/-
5-7W	15 10/-
10W	10 10/-
<b>PAPER CONDENSERS:</b>	
TV types, 500V	50 10/-
Miniature	100 10/-
<b>ELECTROLYTIC CONDENSERS:</b>	
Mains radio/TV types	10 10/-
Transistor types	20 10/-
Mixed high/low voltage	15 10/-
<b>POLYSTYRENE CONDENSERS</b>	
MULLARD POLYESTER CONDENSERS	50 10/-
SILVER MICA	100 10/-
WIRE-WOUND PRE-SET SLIDERS	15 10/-
VOLUME CONTROLS: Double, Mixed	5 10/-
<b>NUTS AND BOLTS: Mixed lengths/types</b>	
8 B.A.	100 10/-
6 B.A.	100 10/-
4 B.A.	100 10/-
2 B.A.	100 10/-
METAL SPEAKER GRILLES: 7 1/2in x 3 1/2in	6 10/-
V.H.F./F.M. TUNERS: Need ECC85	2 10/-
VEROBOARD: Cutter + 5 1/2in x 1in Bds.	10/-

<b>TRANSISTORS:</b>	
P.N.P. Untested	50 10/-
N.P.N.	50 10/-
Light sensitive (OCP71)	5 10/-
Light sensitive diodes	10 10/-
OC44 Mullard. 1st grade	4 10/-
OC45 Mullard. 1st grade	4 10/-
OC22 Mullard. 1st grade	2 10/-
OC25 Mullard. 1st grade	2 10/-
2N378	4 10/-
ASY22	5 10/-
BY127 Rectifiers	4 10/-
1N4007 Rectifiers	4 10/-
STC3/4 200V	6 10/-
Unmarked 200V	10 10/-
Diodes. OA81	40 10/-
<b>WIRE:</b>	
Solid core, insulated	yards 100 10/-
Stranded core, insulated	yards 50 10/-
<b>SOLAR CELLS:</b>	
Selenium, large.	2 10/-
small.	3 10/-
<b>COAX</b>	
Semi air spaced 15 yards	10/-
CRYSTAL TAPE RECORDER MIKES	1 10/-
<b>EARPIECES</b>	
No plug	6 10/-
With 2.5mm plug	4 10/-
With 3.5mm plug	4 10/-

**FREE! FREE! FREE! ONE PACK EXTRA INCLUDED FREE WITH ORDERS VALUE £5. THREE PACKS EXTRA FOR £10 ORDERS.**  
**G. F. MILWARD, Drayton Bassett, Tamworth, Staffs.** Postage (minimum) per order 2/-

**BATTERY ELIMINATORS**  
 The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) 42/6 each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.  
**R.C.S. PRODUCTS (RADIO) LTD.**  
 (Dept. P.E.), 31 Oliver Road, London, E.17


Your local component stockist  
**Eagle Electronics**  
 Eagle St.  
**IPSWICH** 58075

**TELERADIO ELECTRONICS**  
 JOIN THE FASCINATING HOBBY OF RADIO CONTROL. BUILD A SINGLE CHANNEL SYSTEM FOR ABOUT £12 OR A SOPHISTICATED PROPORTIONAL SYSTEM FOR £80  
 Details from the specialists: **TELERADIO CO. (P.E.)**  
 325-7 FORE STREET, EDMONTON, N.9

**gline studios limited**  
 PRINTED CIRCUITS AND PRECISION PHOTO MECHANICAL REDUCTIONS  
 Copthorne Road, Felbridge, Surrey  
 Telephone: East Grinstead 23540 works

**HI-FI ENTHUSIASTS!**  
 Due to popular demand we now offer a new Budget Priced 4-Channel Transistorised Sound Mixer in semi-kit form. Designed for building into consoles, etc., this kit includes P.C. board assembled and tested, knobs, potentiometers, jack sockets, wire solder, etc., plus full instructions. Only £5.3.6 incl. post.  
**DISCOSOUND CONTROL SYSTEMS**  
 19 Nilverton Avenue  
 Sunderland SR2 7TS

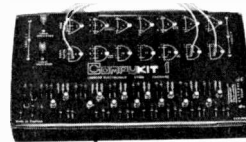**LEARN HOW COMPUTERS WORK WITH KOMPUKIT**




Kompukit I is a practical do-it-yourself teaching aid designed to remove the mystery from digital computers, logic and Boolean algebra. "Cheap, Quick and Clean . . . and, clear winner on all counts" says the Times Educational Supplement. Accompanied by easy-to-follow instruction book.

Ideal as a gift to amateurs, intelligent teenagers, teachers, etc. Unassembled kit, complete, Type CK1/U £10.10.0 (P. & P. 6/-). Assembled, fully tested, ready to use, Type CK1/A £13.5.0 (P. & P. 6/-). Also available Kompukit I Deluxe Model and Kompukit 2 I.C. Patchboard.

Cash with order, or further information, from  
**LIMROSE ELECTRONICS (PE), Lymm, Cheshire**

**BAKER 12in. MAJOR £9**



The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffle **£11.10.0**  
 19" x 12 1/2" in. and instructions.

Latest catalogue 1/- with enclosure plan.  
**Baker Reproducers Ltd**  
 Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

### Mechanical

A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

### Draughtsmanship

A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

### Electrical & Electronic

A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

### Radio & Telecomms.

C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

### Auto & Aero

A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

### Management & Production

Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

### Constructional

A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating  
Architecture  
Builders' Quantities

### General

C.F.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

### General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

# BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D256, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



# BIET

## POST THIS COUPON TODAY

To: B.I.E.T., Dept D256, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

Occupation \_\_\_\_\_

**B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE**

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/asia) Ltd.; South Africa - Central News Agency Ltd.; Rhodesia and Zambia - Kingstons Ltd.; East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £25s. 0d (£2.25). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# HENRY'S RADIO LTD • MAIL ORDER AND INDUSTRIAL SALES DEPT. 303, EDGWARE ROAD LONDON W.2 01 723 1008 9

● **ELECTRONIC COMPONENTS AND EQUIPMENT**  
**AUDIO AND TEST GEAR**  
 356, EDGWARE ROAD LONDON W.2  
 TEL. 01-402 4736

● **ELECTRONIC ORGANS, PUBLIC ADDRESS**  
**DISCOTHEQUE EQUIPMENT**  
 309 EDGWARE ROAD LONDON W.2  
 TEL. 01-723 6963

● **HIGH FIDELITY SALES**  
**AND DEMONSTRATIONS**  
 354, EDGWARE ROAD LONDON W.2  
 TEL. 01-402 5854

OPEN MONDAY TO SATURDAY 9 AM TO 6 PM. THURS 9 AM TO 1 PM. OPEN ALL DAY SATURDAY

## COMPLETE STEREO SYSTEM FOR £39.10.0

HENELEC 5-5 STEREO AMPLIFIER. Inputs for ceramic cartridge, AUX/Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12 1/2 in x 3 1/2 in x 6 1/2 in. Fitted headphone socket.  
 Complete system comprises 5-5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10W speakers, twin tweeters and crossover with polished wood cabinets 18 in x 11 in x 7 in. Also plinth and cover.



- Complete stereo system (Rec. Price £50), £39.10.0, p.p. 20/-
- Amplifier only, £13.19.6, p.p. 7/6.
- TE1025 recommended stereo phones, 39/6.

**UNBEATABLE VALUE!!**

## HENRY'S LATEST CATALOGUE

New print. Now 350 pages. 6th impression.

- ★ **COMPONENTS, TEST GEAR**
- ★ **EQUIPMENT, MODULES**
- ★ **SPECIAL OFFERS, ETC.**

Everything for the constructor

Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-

**WHY NOT SEND AWAY TODAY?**

New 8-page Semiconductor List free No. 36 new ranges and a few circuits.



## BUILD THIS VHF FM TUNER


5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.  
**PARTS TOTAL COST** £6.19.6, P.P. 3/6.  
**ASK FOR BROCHURE** No. 3.

**DECODER £5.19.6**  
**(FOR STEREO)**  
 P.P. 3/-



New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.  
**Total cost £6.19.6, p.p. 6/6.**

**BUILD YOURSELF A QUALITY RADIO**

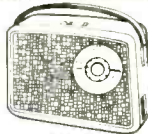

Ask for Leaflet No. 1.

## SINCLAIR EQUIPMENT SPECIAL OFFER

Z30 75/- each, stereo 60 £8.10.0, PZ5 79/6, PZ6 £6.19.6, Z50 £5.9.6, PZ8 £5.19.6.


2 of Z30, stereo 60, PZ5 (usually £23.10) £19 or with PZ6 in place of PZ5 £21

**WHEN IN LONDON** visit the NEW DISCOCENTRE at "354" and COMPONENT SHOP at "356" Edgware Road, W.2
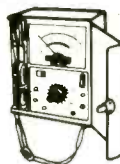
## TEST EQUIPMENT FOR YOUR HOME



AF105 50kV multimeter (illus.), price £8.10.0, p.p. 3/6; leather case, 20/6.  
 200H 20kV multimeter, price £3.17.6, p.p. 3/-; case, 12/6.  
 TE20D R.F. Generator (illus.), price £15, p.p. 7/6.  
 TE22D Matching Audio Generator, price £17, p.p. 7/6.  
 TE65 Valve Voltmeter, price £17.10.0, p.p. 7/6.  
 Full details and complete range in catalogue.



## SLIM POCKET TEST GEAR



- SIGNAL INJECTOR 35/-, p.p. 1/6
- SIGNAL TRACER 29/6, p.p. 1/6

## NEW

**WORLD'S LOWEST COST STEREO MAGNETIC CARTRIDGE O/P 7mV. 20 c/s-20 Kc/s. Diamond Stylus. Fits most decks. Recommended for quality and performance. Model 940. Price 79/6.**

## HI-FI equipment to suit EVERY POCKET



**FREE** STOCK LIST NO. 16/17 ON REQUEST  
 BEST VALUE IN U.K.

Choose from 100 complete stereo systems—Complete range of individual units also in stock. Demonstrations all day. Visit the New Hi-Fi Store.

## 100 STEREO SYSTEMS

**LOW CASH AND CREDIT/HP PRICES**  
 (Credit terms from £30 purchase—callers only)



## YOU CAN SAVE 25% brand new GARRARD AND GOLDRING

(Post 7/6) COMPLETE LIST FREE ON REQUEST

SP25 Mk.II £10.19.6, AP75 £16.19.6, SL65B £14.19.6, SL72B £25, GL69 £22


**SPECIAL OFFER** Above with Sonotone 9TAHC diam. Add £2, with magnetic add 70/-, with Goldring G800 add £7.10.0

Also Fitted with 9TAHC diamond 2025TC £9.15.0, 3000LM £9.15.0, MODEL 50 £9.15.0  
 Plinths/Covers: Standard 99/6, p.p. 4/6. De luxe £8.10.0, p.p. 6/-. SL72B type £8.10.0, p.p. 6/-. GL69 Type £9.15.0, p.p. 6/6.

● Goldring GL69 with plinth and cover and G800 cartridge (usually £51) £39.10.0, p.p. 12/6.


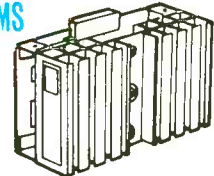
## NEW 25watt and 50watt RMS SILICON AMPLIFIERS



### LOOK AT THE SPECIFICATIONS!

- 0.3% Distortion at full power
- -1db 11c/s to 40kc/s at full power
- Response -1db 11 c/s to 100kc/s

PA25 10 Silicon Transistors. Differential input, 25watt rms into 8ohms. 700mV input. Size only 5" x 3" x 2". 4-hole fixing. 12watt into 15ohms. Supplied with edge connector and harness.

PA50 12-Transistor Version, 50watt rms into 3 to 4ohms

MU442 Power supply for one or two PA25 or one PA50

- PA25 £7.10.0 ● PA50 £9.10.0 ● MU442 £6

## NEW SELF-POWERED PREAMPLIFIERS



Mains operated Slim Design Preamplifiers for use with any power amplifier. All Silicon FET/TRANSISTOR design. Capable of driving up to 4-PA50 amplifiers. Pushbutton selection. All facilities.

### MODEL FET154 STEREO AMPLIFIER

Inputs for mag. Pick-up, Tuner/Aux., Tape in and out. Response 20 c/s to 30kc/s. Output adjustable up to 1 volt. ±20dB boost or cut-out controls. Slim design. Size 12" x 3 1/2" x 1 1/2". Price £16.10.0

### MODEL FET 9/L

Mono Preamplifier with built-in mic. MC X EC input for all crystal and ceramic cartridges. Tuner, tape in and out. D/P and Response as FET154. Size 10 1/2" x 4 1/2" x 1 1/2". Price £12.10.0.

**NO SOLDERING JUST PLUG IN CONNECTORS!**

## ELECTRONIC ORGANS


COMPLETE RANGE OF COMPONENTS IN STOCK FOR ALL PURPOSES

★ MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT VENEERED CABINETS FOR ALL MODELS

★ 49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE

★ KITS AVAILABLE IN SECTIONS AS REQUIRED

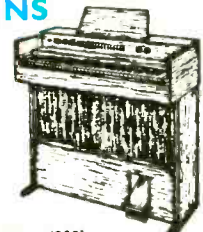**NEW PA and DISCOTHEQUE CENTRE at '309'**



**HENRY'S RADIO LTD FOUR ELECTRONICS CENTRES ALL WITHIN 100 YARDS**  
**303 · 309 · 354 · 356 EDGWARE ROAD LONDON W.2**