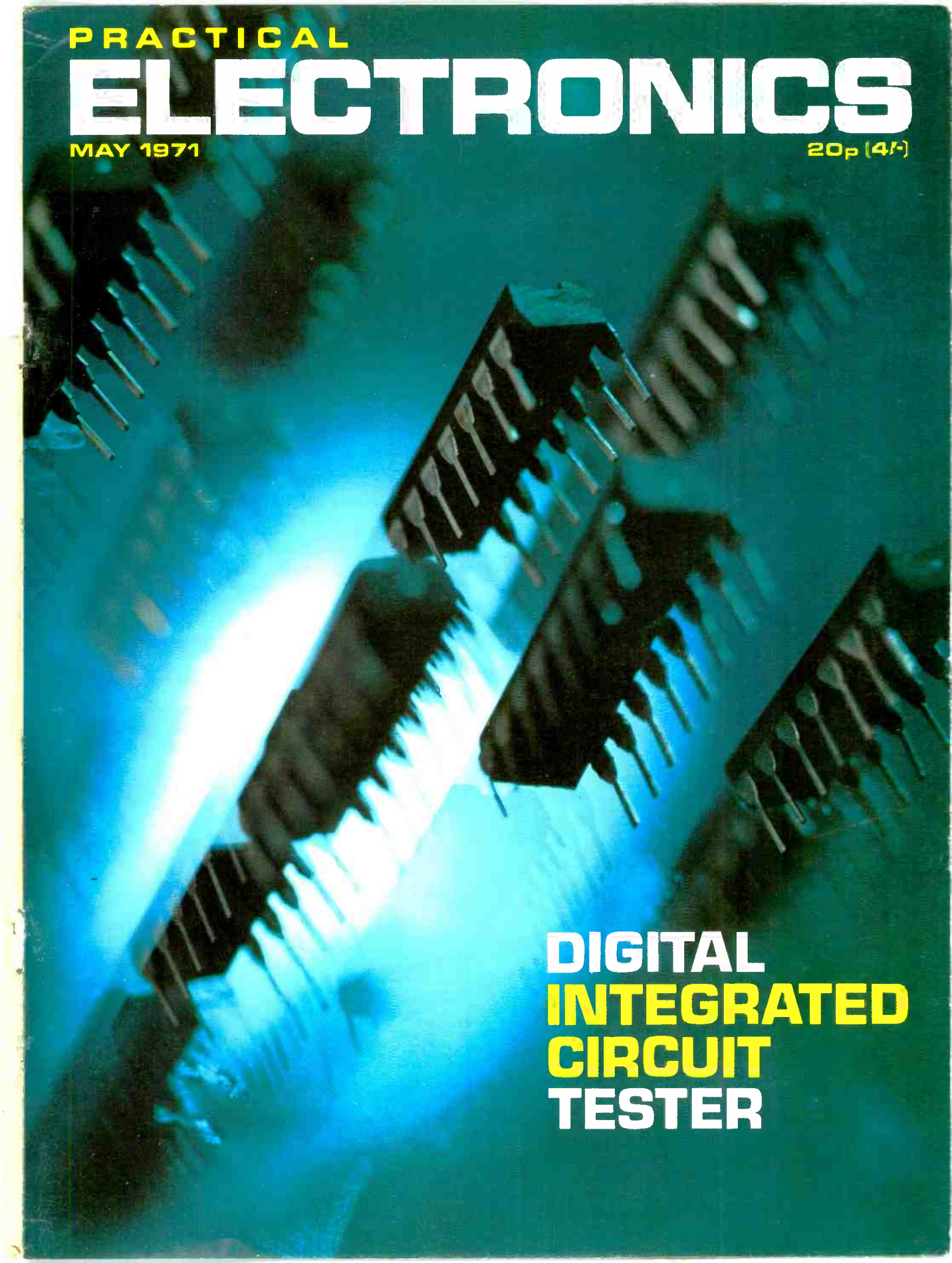


PRACTICAL

ELECTRONICS

MAY 1971

20p (4p)



**DIGITAL
INTEGRATED
CIRCUIT
TESTER**

ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{16}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{16}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE


LONG LIFE

B 42 LL $\frac{1}{16}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

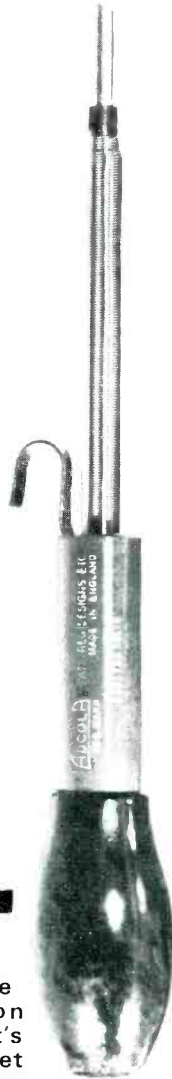B 44 LL $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



ADCOLA PRODUCTS LTD.,

(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.

Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

* Write for price list and catalogue

ERSIN



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75 ft. 18 gauge on plastic reel. Recommended retail price 75p



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170 ft. 22 gauge on plastic reel. Recommended retail price 75p



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	15p*
Size 5 (illustrated)	Savbit	18	15p*
15	60/40	22	20p*

*Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER,

easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 50p




From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

NOW AVAILABLE LASKY'S AUDIO TRONICS CATALOGUE 1971

THERE'S MORE & MORE & MORE FOR EVERYONE!

The great new 1971 edition of Lasky's famous Audio-Tronics catalogue is now available FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape recording and Audio accessories, and introduces LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

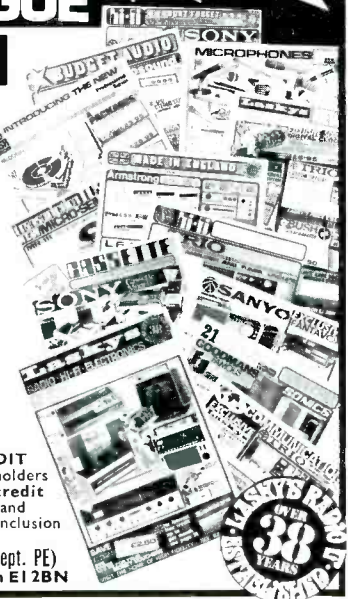LASKY'S RADIO LTD. (Dept. PE)
3-15 Cavell Street, London E1 2BN




Discosound

P. A. AND DISCOTHEQUE EQUIPMENT

— A COMPREHENSIVE RANGE COVERING EVERY REQUIREMENT

AMPLIFIERS, MIXERS, LIGHT CONTROL UNITS.

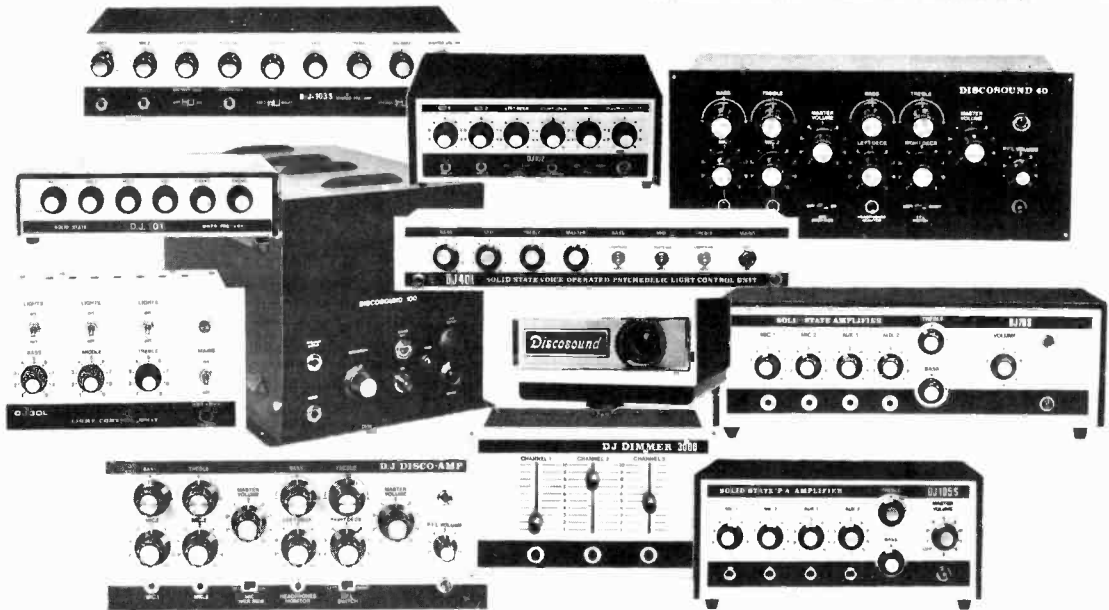

D.J.101 Mixer Pre-Amplifier

Six inputs allow full mixing facilities for all types of equipment. 9V battery operation.
Size: 10½ in x 2½ in x 4½ in.
Suggested Retail Price £14

D.J.102 Discotheque Mixer Pre-Amplifier

Four inputs each with its own volume control plus master volume control, PFL monitoring and mic. override switches. Size: 10½ in x 4 in x 4 in.
Suggested Retail Price £25

D.J.105S P.A. Amplifier

4-channel mixing facilities each with separate inputs and volume controls. 30W r.m.s. power output: a.c. mains 200/230V a.c. Size: 11½ in x 3 in x 6 in.
Suggested Retail Price £41

D.J.70S Integrated Mixer Amplifier

Power output 70W r.m.s. 4-channel mixer with separate inputs and volume controls, plus master volume and separate bass and treble controls. Size: 15½ in x 6 in x 6 in.
Suggested Retail Price £83

D.J. Disco-Amp.

Designed specifically for use with discotheques. Power output 100W r.m.s. Two mic. inputs and two gram inputs, with independent volume controls plus bass and treble controls. Incorporates many exclusive features. Front panel size: 16½ in x 7 in.
Suggested Retail Price £85

Discosound 40 Discotheque Pre-Amplifier

Features independent inputs and volume controls for two microphones and two turntables plus separate bass, treble and master volume controls. Self-powered and ideal for use with Discosound 100 Power Amplifier (is capable of running 10 of these power amplifiers—total 1,000W). Front panel size: 16½ in x 7 in.
Suggested Retail Price £40

Discosound 100 Power Amplifier

100W r.m.s. power amplifier (at 8 ohms) utilising all silicon transistors and features full automatic overload against short or open circuits. Frequency response 20-20,000Hz ±3dB. Distortion less than 1% at 70W r.m.s. ±1dB. Size: 10½ in x 8 in x 7 in.
Suggested Retail Price £49.50

D.J.103S Stereo Pre-Amplifier

A high quality stereo discotheque pre-amp unit. Incorporating two microphone and two turntable inputs each with independent volume control, plus bass, treble, balance and master volume control. Offers full mixing and monitoring facilities. Front panel size: 16½ in x 3½ in.
Suggested Retail Price £49.50

D.J.30L Psychedelic Light Control Unit

3-channel light unit enabling bass, middle and treble frequencies from the amplifier to be operated individually. Handles 1,000W per channel. Front panel size: 10 in x 6 in.
Suggested Retail Price £37.50

D.J.40L Sound Operated 3-channel light unit

Features built-in microphone which eliminates the need for connections to any amplifier or sound source. Handles 1,000W per channel. Front panel size: 16½ in x 3 in.
Suggested Retail Price £56.25

D.J. DIMMER 3000

3-channel light dimmer unit offered in two versions: Dimmer 3000—a straight 3-channel dimmer unit with mains input and three light outputs. Dimmer 3000S—for use in conjunction with D.J.30L Light Control unit only and has three mains inputs and three light outputs. Front Panel size: 10 in x 6 in.
Suggested Retail Price £32.50

Discosound Disco-Wheel

A projector designed to project a range of liquid wheels and colour change wheels for special lighting effects, adding colour and variety to any form of entertainment. Size: 7½ in x 10½ in x 3½ in.
Suggested Retail Price £50

A range of complete Discosound systems with matching Speakers also available.

DISCOSOUND PRODUCTS ARE GUARANTEED FOR 12 MONTHS

For full details of the Discosound range of products call at or write to your nearest Discotheque Centre — Demonstrations given at any time.

DISCOSOUND

122 Balls Pond Road, London N.1. Tel: 01- 254 5779

HENRY'S RADIO LTD.,


309 Edgware Road, London W.2. Tel: 01-723 6963

NEW FROM TRS

This money saving **STEREO 8 + 8 AMPLIFIER**
in a new **PRE-ASSEMBLED MODULAR PRESENTATION**

A new conception in modular assembly which makes construction even easier than ever and results even better. Two pre-amp and two power amp modules, factory built, tested and guaranteed by a world famous maker come to you ready mounted with mains power unit on chassis forming part of the attractive TRS cabinet which simply need wiring for immediate use. A generous 8 watt RMS output per channel into 3-5 ohms is assured. Cabinet with aluminium front, charcoal grey top and wood sides measures 12in x 8½in x 2½in. Very attractive appearance.

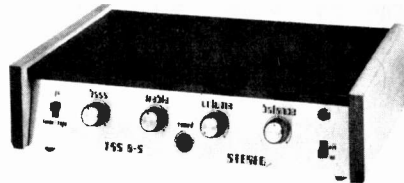- Frequency resp.: 50Hz-16kHz ±3dB.
- Input: 110mV per P.U., radio 240mV.
- Output: 8W per channel. RMS into 3-5Ω. Slightly less per 8-15Ω speakers.
- Record and playback facilities
- Bass/Treble/Volume/Balance /Input/On-off controls.
- Extra easy to install.



Complete kit assembled ready to wire up with mains lead and instructions. Unsurpassed value at only

£17.50

Carriage and packing 38p in U.K.
Descriptive leaflet on request

COMPONENTS CORNER

VYNAIR speaker and cabinet covering by ICI. Send 5p for samples—refund on purchase. 12½p per sq.ft. £1.38 per yd. 48in wide.

BONDACOUT speaker wadding lin thick, 18in wide, per yard 42½p.

VEROBOARD in all latest sizes and forms. inc. 2½in x 3½in, 16p; 2½in x 5in or 3½in x 3½in, 23p; 3½in x 5in, 26p; 17in x 3½in, 75p.

VOLUME CONTROLS. Long spindles all values 5Kohms to 2meg., log or lin., less switch 17½p; with switch 25p.

Twin ganged stereo, 5K to 2meg. less switch, 48p; with switch 100K to 2meg. 52p.

STEREO BALANCE CONTROLS. Log/Anti-log 5K, 10K, ½, 1 or 2meg., 55p.

RESISTORS, CAPACITORS, WIRE, etc., etc.

MORE AMPLIFIERS FROM TRS

MULLARD VALVE AMPLIFIERS

5-10 basic kit (mono) £10.99. Carr. 28p.
2 valve mono pre-amp basic kit for above £7.45. Carr. 28p.

10-10 stereo amplifier kit £18.99. Carr. 63p.

TRS 50 WATT VALVE AMPLIFIER

A ruggedly built unit in ventilated steel case with carrying handles: size 12in x 8in x 8in. Two input channels mixable (10mV and 150mV) bass and treble controls. EL 34's output (mono) in push-pull, with fixed bias. Excellent for P.A., musical group work, etc. Brand new and guaranteed £30. Carriage 75p.

FOR YOUR STEREO 8+8 OR OTHER HI-FI SYSTEMS

Plinth and motor assembly comprising modern style teak finished plinth cut to take famous Garrard AT6 auto/single playing unit wired for stereo, with hard smoke grey perspex lid, Plinth and AT6 less cartridge **£12.50** (Carr. and packing 33p).


SPECIAL CARTRIDGE OFFER TO PURCHASERS OF ABOVE ONLY

Acos stereo 6P93-1 (sapphire) £1.25.
Sonotone 9TA/HC (diamond) £2.
AD96K (Mag., diamond) £3.30.
Various magnetic types from £3.50.

TRS SPEAKER BARGAIN

Ready now — **SPEAKER AND CABINET ASSEMBLY** comprising 8" unit (4 ohms) and easy to put together flat-pack cabinet ported and lined, size 18" x 12" x 9". £3.50 (Carr. 40p).

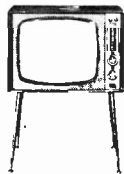TRS RADIO COMPONENT SPECIALISTS
70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY
Tel. 01-654 2188
Open all day Satrs., Weds.—1 p.m. Almost next to Thornton Heath Stn. (S.R.)



EX RENTAL TV'S

19" — £29.95

23" — £39.95

All Channels 405/625
2 Years Guarantee.
Free List by return.

17" Slim line TV's £11.95, 19" Slim line TV's £15.95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1.95. Daily demonstrations to personal shoppers.

TEAK HI-FI STEREO CABINETS £14.95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1.00.

PRESS BUTTON SWITCHING UNITS. 4 Banks 17p. 6 Banks 27p. P. & P. 5p.

Transistor Radio Cases: 25p each. Size 9½" x 6½" x 3½". P. & P. 15p.
SPEAKERS 50p 25 8Ω BRAND NEW. P. & P. 5p.

TRANSISTORS Post Free
AC 126 AF 179 OC 81
AC 128 OC 44 OC 81D
AF 114 OC 45
AF 117 OC 71 15p each

POTENTIOMETERS 23p each

Double & Switched	500 KΩ/500 KΩ	3½" shaft
Double & Switched	500 KΩ/100 KΩ	2" shaft
Double & Switched	1 MEG/100 KΩ	1½" shaft

Post. & Pack. 5p.—4 for 10p


KNOBS 100,000 to clear (Brand New)

100 assorted Radio & T.V. knobs 50p. Postage 10p. (If you require sets 2 to 6 just ask)

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12
Phone 01-478 6001-2-3 Stamp for Free List

TV TUBES REBUILT GUARANTEED 2 YEARS

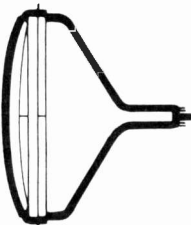

14"—£3.95, 17" & 19"—£5.95,

21" & 23"—£6.45.

Exchanged Bowls. Carr. 53p.

Fingers

The more 'fiddly' the job, the more you depend on your finger-tips. Make sure minor burns and blisters don't rob them of their skill. Apply BURNEZE, pronto! This unique scientific aerosol cools the heat out of a burn in just 8 seconds, anaesthetizes pain, reduces swelling. BURNEZE — the clever tip for burnt finger-tips. From chemists.



Potter & Clarke Ltd Croydon CR9 3LP

FREE FLOG LIST No. 6

Scores Special Bargains

SEND S.A.E. OR CALL AT ANY BRANCH FOR YOURS

HUGE RANGE OF SPECIAL SNIPS —STEREOS, DECKS, TAPE RECORDERS, AMPLIFIERS, SPEAKERS, TRANSISTORS, VALVES, COMPONENTS—NEW BRANCH AT 77 EAST ST., SOFTON.

TECHNICAL TRADING

★ Portsmouth—350 Fratton Rd. Tel. 22034
★ Southampton—72 & 77 East St. Tel. 25851
★ Brighton—6 Queen's Rd. Tel. 23975
★ ARUNDEL—All Mail Order 15-17 QUEEN ST. Tel. 882299

ENORMOUS PURCHASE. GUARANTEED. APPROX. HALF PRICE. **WORLD FAMOUS TAPE**

Standard Play		Double Play	
3in. 150ft. 12p	3in. 300ft. 20p	4in. 300ft. 23p	4in. 600ft. 40p
5in. 600ft. 45p	5in. 1,200ft. 75p	5½in. 900ft. 52p	5½in. 1,800ft. 95p
7in. 1,200ft. 65p	7in. 2,400ft. £1.35	Long Play	
3in. 225ft. 13p	4in. 900ft. 65p	Triple Play	
4in. 450ft. 27p	5in. 1,800ft. £1.13	5in. 900ft. 53p	5½in. 2,400ft. £1.70
5½in. 1,200ft. 65p	7in. 3,600ft. £2.40	7in. 1,800ft. 93p	

★ ARUNDEL—All Mail Order 15-17 QUEEN ST. Tel. 882299
Postage by repl. 3in. 600ft. 43p
Post Free less 5% on three reels.
Quantity and Trade inquiries invited

MAIL ORDER DIVISION

distronic LTD

THE POWER HOUSE

**28 BURNT MILL
ELIZABETH WAY
HARLOW ESSEX
HARLOW 32947**

**Why wait weeks? — ALL OUR ORDERS
DISPATCHED BY RETURN OF POST!
Transistors, Diodes and Integrated Circuits**

A) DIODES & RECTIFIERS	AC142H	20p	BC109	11p	BFX86	30p
	AC142HK	27p	BC113	20p	BFX87	30p
IN4001	AC142K	25p	BC114	20p	BFX88	25p
IN4002	AC187K	} Matched pr. 50p	BC115	25p	BFY34	30p
IN4003	AC188K		BC116A	30p		
IN4004	AC191	15p	BC117	30p		
IN4005	AC192	15p	BC125	20p		
IN4006	AC193	20p	BC126	30p		
IN4007	AC193K	} Matched pr. 60p	BC132	20p		
	AC194K		BC134	20p		
	AC194	20p	BC137	30p		
	AD142	50p	BC142	35p		
	AD262	} Matched pr. 90p	BC143	40p		
	BD162		BC144	35p		
	AD262	35p	BC145	30p		
W005	AD263	40p	BC147	15p		
W01	AF106	25p	BC148	11p		
W04	AF109	35p				
W06	AF139	31p				
	AF166	20p				
	AF170	18p				
	AF172	18p				
	AF200	25p				
	AF201	30p				
	AF239	40p				
	AF239S	45p				
	AL102	60p	BC149	15p		
	AL103	50p	BC153	30p		
	AU103	£1	BC154	35p		

Compare our prices

Please note minimum order 50p

Send 10p for price list or free with order

**Component Discounts
10% on orders over £5**

B) TRANSISTORS	2N696	15p				
	2N930	25p				
	2N930A	30p				
	2N1613	22p				
	2N1711	25p				
	2N2369	20p				
	2N2484	34p				
	2N2605	45p				
	2N2904	36p				
	2N2904A	41p				
	2N2905	46p				
	2N2905A	60p				
	2N3053	22p				
	2N3055	70p				
	2N3442	£2				
	2N3638	25p	AU106	95p	BCY70	26p
	2N3866	£1-50	AU107	70p	BCY71	26p
	2N4347	£1-50	AU108	65p	BCY72	26p
	2N4356	35p	AU110	£1	BF152	25p
	40411	£2-50	AU111	70p	BF153	25p
	AC138	15p	AUY21A	60p	BF158	25p
	AC141	20p	AUY22A	70p	BF159	35p
	AC141H	25p	AUY35	45p	BF160	28p
	AC141HK	25p	AUY37	60p	BF177	25p
	AC141K	27p	BC107	11p	BF178	35p
	AC142	15p	BC108	11p	BF179C	40p

2N3055	70p
115 Watt 15 Amp	
2N3053	22p
1 Amp TO-5	
BC107	11p
Also BC108 and BC109	
AF239	40p
UHF: 5 DB at 800 MHz	
W01	45p
1 Amp, 100 V Bridge Rectifier	
AD262 } PNP Matched	
BD162 } NPN pair	90p
10 Watts, AUDIO OUTPUT PAIR	
AD142	50p
80 Volts, 10 Amp TO-3	
AU103	£1
155 Volts, 10 Amp TO-3	
AU106	95p
320 Volts, 10 Amps	
BC147/8/9	15p
High gain LOCKFIT	
ME1001	10p
45 Volt high gain	
40411	£2-50
30 Amp, 150 Volts	
IN4001	7p
1 Amp, 100 Volts	
BF179C	40p
250 Volts TO-5	
BFY51/2	20p
2N3866	£1-50
1 Watt output at 400MHz	
BC114	20p
High gain: 200 at 1mA	
741C	£1-25
DIP or TO-99	
High gain operational amp. S/C proof	

C) INTEGRATED CIRCUITS	709C (TO-99)	95p
	709C (DIP)	95p
	741C (TO-99)	£1-25
	741C (DIP)	£1-25

POSTAGE & PACKING PLEASE ADD 10p TO YOUR ORDER

The Eagle Annual.

Sorry, no Dan Dare, Digby or P.C. 49. Because this is the new Eagle annual catalogue. And it's packed with interesting things. Like the new TSA 151 stereo amplifier: it uses a new block construction silicon output device for absolute reliability. It's got low noise silicon transistors throughout. Its output is 15 Watts per channel. That's 15 Watts RMS, not an exaggerated figure for maximum music power.

The price? A very reasonable £36.

And for people who like to listen to stereo undisturbed, we've got the new SE 100 headphones.

Dual cone transducers are used throughout, and to keep the weight down, the independent volume controls are

mounted on a separate unit with a pocket clip. £16.00.

Every item in the annual has been specified or selected by Gerry Adler. Eagle is Gerry's baby, and he's very fussy about what goes out under the Eagle banner. He gets very twitchy at the thought of a duff diode. A bit like the Mekon in fact.

But he does it for a reason.

He believes that if the first Eagle product you buy is O.K., you'll come back for more.

That's what's made Eagle a success.

Eagle International
we don't stand still.

Coptic Street, London WC1A 1NR
Tel: 01-636 0964

Headphones/Accessories

SE 28 Studio Stereo Headphones
This studio quality headset offers a really extensive frequency response (20 to 20,000 Hz) by means of dome acoustic chambers and specially designed tweeters. Separate adjustable attenuators are also incorporated in each dome. Complete with stereo jack plug and cable - a first class instrument.

Frequency Range: 20-20,000 Hz. Impedance: 8 ohms per channel. Matching Impedance: 8-16 ohms.



SE 28

SE 80 Studio Stereo Headphones

Based on an entirely new open baffle concept the SE 80 Stereo Headphones have been developed to bring a new standard of comfort to professionals who have to wear a headset for very long sessions. Recording Engineers, Monitor Units, Broadcasters, D.J.'s, etc. Individual slider tone controls complete a list of features which include the use of fine leathers for padding.

Frequency Range: 20-20,000 Hz. Impedance: 8 ohms per channel. Matching Impedance: 8-16 ohms per channel.



SE 80

MMA 309 Headphone and Boom Microphone

Ideally suited to the language laboratory, studio or other professional user, this new headphone and boom microphone are the result of combined UK and American research. A new noise cancelling microphone is inset in a retractable boom which carries the retractable cable internally.

Frequency Range: 50-14,000 Hz. Impedance: 16 ohms. Matching Impedance: 8-16 ohms. Cord length: 1.83 m with jack plug.
Frequency Range: 50-2,000 Hz. Impedance: 16 ohms. Matching Impedance: 16 ohms with jack plug.

MMA 309

SE 100 Professional Stereo Headphones

The SE 100 represents the ultimate development of classic design. Built in differences that are audible include tone corrected dual cone speakers and damped reflex baffles. To keep headset weight to an absolute minimum the independent volume controls are mounted in a separate unit. Leather padding, a 5 metre coiled lead and a moulded stereo jack plug finalise a luxury specification.


Frequency Range: 20-20,000 Hz. Impedance: 8 ohms per channel. Matching Impedance: 8-16 ohms.

SE 100

SE 100 Professional Stereo Headphones

The SE 100 Professional Stereo Headphones are the result of combined UK and American research. A new noise cancelling microphone is inset in a retractable boom which carries the retractable cable internally.

Frequency Range: 50-14,000 Hz. Impedance: 16 ohms. Matching Impedance: 8-16 ohms. Cord length: 1.83 m with jack plug.
Frequency Range: 50-2,000 Hz. Impedance: 16 ohms. Matching Impedance: 16 ohms with jack plug.

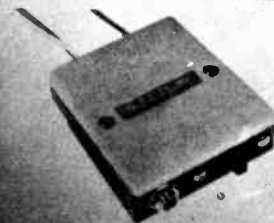

SE 100

JB 3 Stereo Headphone Junction Box

This simple, inexpensive unit is essential to stereo headphone users. It connects to stereo amplifier and loudspeakers, giving attenuated stereo headphone output, with a three-position switch to give headphones only, speakers only, or both together.

Input: Suitable for connection to any amplifier up to 30 watts output. Output: 50 mW. Size: 74 x 80 x 28 mm.

JB 3

YATES ELECTRONICS

FLITWICK LTD

RESISTORS

½W Iskra high stability carbon film—very low noise—capless construction. ¼W Mullard CR25 carbon film — very small body size 7.5 × 2.5mm. 4W Erie wire wound.

Power watts	Tolerance	Range	Valves available	Price	
				1-99	100+
½	5%	4.7Ω-2.2MΩ	E24	1-0p	0-7p
	10%	3.3MΩ-10MΩ	E12	1-0p	0-7p
	10%	1Ω-3.9Ω	E12	1-0p	0-7p
1	5%	4.7Ω-1MΩ	E12	1-0p	0-7p
	10%	1Ω-10Ω	E12	7½p	7½p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.20.
E24 pack 650 resistors £4.20.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2½p. 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3p. 0.047µF, 0.068µF, 0.1µF, 4p. 0.15µF, 6p. 0.22µF, 7½p. 0.33µF, 11p. 0.47µF, 13p.
160V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 3p. 0.1µF, 0.15µF, 0.22µF, 4p. 0.33µF, 6p. 0.47µF, 7½p. 0.68µF, 11p. 1.0µF, 12½p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 3p. 0.033µF, 0.047µF, 0.068µF, 3½p. 0.1µF, 4p. 0.15µF, 0.22µF, 5p. 0.33µF, 6½p. 0.47µF, 8½p. 0.68µF, 11p. 1.0µF, 13p.

MYLAR FILM CAPACITORS

100V: 0.001µF, 0.002µF, 0.005µF, 0.01µF, 0.02µF, 2½p. 0.04µF, 0.05µF, 0.068µF, 3½p. 0.1µF, 4½p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

CAPACITOR DEVELOPMENT PACK

Selection of 100 ceramic and polyester capacitors, 100pF to 1.0µF, £2.90.

ELECTROLYTIC CAPACITORS—One Price—5p Each

Mullard C426 series (µF/V): 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 16/10, 32/10, 64/10, 125/10, 200/10, 10/16, 20/16, 40/16, 80/16, 125/16, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 4/40, 8/40, 16/40, 32/40, 50/40, 2.5/64, 5/64, 10/64, 32/64.

Miniature P.C. mounting (µF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

POTENTIOMETERS

Carbon track 5kΩ to 1MΩ, log or linear (log ½W, lin ¼W). Single, 12½p. Dual gang (stereo), 40p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0.1 matrix).
Sub-miniature 0.1 watt, 4p each. Miniature 0.25 watt, 5p each.

SEMICONDUCTORS

AC126 15p	BFY52 22½p	OC81 15p	2N3055 72p
AC127 15p	BSY56 30p	OC82 15p	2N3702 15p
AC128 15p	BSX21 25p	ORP12 47½p	2N3703 15p
AD140 40p	BY124 7½p	IN4001 7½p	2N3704 17½p
AF115 17½p	BYZ10 30p	IN4002 10p	2N3705 15p
AF117 17½p	BYZ13 20p	IN4003 11p	2N3706 12p
BC107 14p	OA85 7½p	IN4004 12½p	2N3707 18½p
BC108 10p	OA91 7½p	IN4005 14p	2N3708 10p
BC109 10p	OA202 7½p	IN4006 15p	2N3709 11p
BFY50 22p	OC71 15p	IN4007 16p	2N3710 12p
BFY51 19p	OC72 15p	2N2926 11p	2N3711 14p

ZENER DIODES

400mW 5% 3.3V to 30V, 17½p.

VEROBOARD

2½ × 3½	0.1	0.15	17 × 3½ (plain)	0.15	0.1
2½ × 5	22p	16p	17 × 2½ (plain)	37½p	—
3½ × 3½	24p	24p	2½ × 5 (plain)	17½p	—
3½ × 5	24p	24p	2½ × 3½ (plain)	15p	—
3½ × 5	27p	27p	Pin insertion tool	47½p	47½p
17 × 2½	75p	57½p	Spot face cutter	37½p	37½p
17 × 3½	100p	75p	Pkt. 36 pins	15p	15p
17 × 5 (plain)	—	75p			

ROTARY SWITCHES

2P2W, 1P12W, 2P6W, 3P4W, 4P3W, 22½p.

PLUGS AND SOCKETS

Standard ½in screened	17½p	2.5mm insulated	7½p
Standard ½in insulated	14p	3.5mm insulated	7½p
Stereo ½in screened	35p	3.5mm screened	12½p
Standard ½in socket	15p	2.5mm socket	7½p
Stereo ½in socket	17½p	3.5mm socket	7½p

BRUSHED ALUMINIUM PANELS

12" × 6" = 25p; 12" × 2½" = 10p; 9" × 2" = 7p.

C.W.O. please. Post and packing, please add 7½p to orders under £2. Data sheets are available for most of the components listed, and will be sent free on request.

8E39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD

Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)

Transistors, etc. AC126 12½p. AF115 15p. AF116 15p. AF117 20p. OA5 7½p. OA10 7½p. OA81 7½p. OA85 7½p. OC23 32½p. OC25 30p. OC26 37½p. OC28 42½p. OC35 42½p. OC44 14p. OC45 12½p. OC71 12½p. OC72 12½p. OC75 12½p. OC81 12½p. OC81D 12½p. OC82D 12½p. OC170 20. OC171 12½p. Many more in list. S.D.R. BY100 800piv 14p. 6 Amp series: BY213 300piv 20p. BY212 600piv 25p. BY211 900piv 30p. BY210 1200piv 35p. (Charges 6½p up to 11, paid for 12 and over.) Sub-Min. Transformers: OUTPUT (£3 off for OC72, etc.) 14p. (Up to 6 6½p). MULTIMETER. Our famous 20000 Ω per V £46.2½ (15p). Details and other in list. SOLDERING IRON. Slim, modern, British high-speed 8½", all parts replaceable, highest quality, full guarantee: £1.07½ (10p). DIAMOND STYLII Replacements for BSR TC8/LP, TC8/S, TC8LP/STEREO; COLLARO 'O': RONETTE BF40LP; GARRARD GC2/LP and GC8/LP; ACOS GP65/67, all at 40p (6p) ACOS GP73, GP91; BSR ST4 (ST3, ST5), ST8 (ST9); SONOTONE BTA, 9TA, 9TAHC; PHILIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304); Garrard GK525 all at 75p (6p). All are of the very highest quality. Double Diamond: ST4 (ST3, ST5); ST10 (ST9, ST8); 9TA, 9TAHC, 3306, GP91 (For GP92, GP93, GP94 cartridges); GP91SC for all GP91-SC cartridges; All at £1.50 (6p). PICK-UP CARTRIDGES All standard fittings and styli. MONO GP67/2 75p STEREO-COMPATIBLE (MONO) GP91/SC (£1.05). STEREO GP93 £1.27½. STEREO CERAMIC GP94 £1.92½. SONOTONE STEREO 9TAHC (DIA.) £2.37½. GOLDRING GB50 £4.87½. G800 £8.50. G800E £13.50. G800 SUPER £19.50 (6½p all types or Reg. Post 22½p). STYLII FOR ALL ABOVE TYPES, including GOLDRING available. RECORDING TAPE. Still the finest quality Mylar available: Standard 5" 600 ft. 36p 5½" 900 ft. 50p 7" 1,200 ft. 56p. LONG PLAY 5" 900ft. 50p 5½" 1,200 ft. 57p 1800 ft. 90p (7½p on 5" and 5½" 9p on 7"). MICROPHONES Crystal Mic 91, hand/desk 81p. MIC45 Curved metal handgrip £1. CM21 Grey hand/desk 52½p. Stick '60' £1.02½ CM20 "Planet" machined metal tapered stick type with neck cord, adaptor to fit floor stands £1.47½ (All 9p LABEL (or hand) with clip 32½p (6p)). All are fitted with leads. Dynamic. Cream hand/table MINY 77½p (9p) MS10, 50K Ω for desk, tapered with base and slide-out adaptor £1.97½ MS11, similar, but fixed on swivel swan neck to switch-fitted base £2.22½ (Either 15p). Type 209 Cardioid ball, 50K/600 Ω, omni-dir., built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £6.30. DM160, Non-Dir. Ball, 50K Ω, switch, cable, adaptor £3.87½ (27½p either). MICROPHONE INSERTS: Dia., 1.75" OR 0.9" either size 27½p (6p). EARPIECES with lead & min. jack plug (2.5 or 3.5mm, state which) Magnetic 9p Crystal (3.5 only) 24p. (Up to 3 for 6p on any.) HEADPHONES De Luxe STEREO 8-16 ohms, £2.47½. Same, fitted vol. control each earpiece, £4.20. Both have lead and stereo jack plug (17½p). HIGH RES. 2000 ohm. Adjustable 92½p (12½p). SPEAKERS. 12" ROUND, fitted tweeter, 3 or 15 Ω (state which) £1.87½ (27½p) or for Stereo £4.25 pair, carr. paid. 2½" 3 OR 8 Ω (state which) 37½p (6p). EMI 13" × 8", 3, 8 or 15 Ω (state which) £2.12½ (25p); with single flared paper tweeter cone 8 or 15 Ω (state which) £2.27½ (25p); with two tweeters and crossover network 8 or 15 Ω (state which) £3.75 (25p). VIBRATORS. Genuine Plessey 12V 4-pin non-synch. 121HD4, 2½" ex. pins 27½p. Am. 12V 4-pin, non-synch. 7/16chs longer, 22½p 12V 7-pin Synch. (12SR7) 62½p (all types 6½p per vibrator). CONNECTING WIRE. Packs of 5 coils asstd. cols. ea. coil 5yds. Solid core 14p (6p). Flexible 16p (7½p). Super thin for transistor wiring 16p (6p). PICK-UP WIRE. Super thin twin flex, screened and sheathed 6p yd. (6p up to 6yds.—over, free). RETRACTABLE Flex. Leads. (Curlies) 6ft, phono plug ea. end 22½p. 12ft. 39p. 6ft. phono plug/phono socket other end 25p 12ft. 42½p (6p per lead, all types). BATTERY ELIMINATOR. 240 a.c. input 3, 6, 7½ and qv d.c. output at 400 mA, two switches, leads, pilot light and universal adaptor for all trans. appliances incl. all makes cassette t/r recorder and players £3.15 (24p). SEND S.A.E. for full free lists—Teleton and small 3W and 7½W trans. amplifiers, Electrolytics, Vol. Controls, all types of radio switches, car and portable expanding aerials, Meters, Test prods, all types of Brit. & Cont. standard and min. plugs and sockets, SDR's, Thyristors, croc-clips (various), terminals, etc. etc. and many "Special Offer" lines at lowest possible prices.

BRAND NEW

SGS/FAIRCHILD SILICON NPN TRANSISTORS

BD112 Audio, 80V, 20W, TO3, 32½p (10 for £2.50). BD116 Audio, 80V, 20W, TO3, 45p (10 for £4). CP400 Regulator, 40V, 15W, TO3, 37½p. CP401 Regulator, 60V, 15W, TP3, 37½p. CP402 Regulator, 100V, 15W, TO3, 42½p. CP404 Audio, 80V, 15W, TO3, 37½p. CP430/431 Audio, 100V, 30W, TO3, 37½p. CP433 Audio, 120V, 40W, TO3, 42½p. CP702 Audio 60V, 15W, TO3, 37½p. CP704 R.F. or Servo 80V, 30W, TO3, 47½p. BLY68 Audio, 100V, 25W, TO3, 50p. BLY72 High Power, 80V, 100W, 75p. CP703 High Current Relay, 60V, 5W, 32½p. BF76 Microwave, Oscillator, 4GHZ, 30 V I W, £1.00. 2N3646 High Speed Switch, 40V, ½Amp, 22½p. 2N4075 Audio, 100V, 30W, 55p. 2N4076 Audio, 100V, 30W, 45p.

VARICAP DIODES

BBY10, 6-8pf, BBY11, 10pf, BBY12, 12pf, 25p each.

INTEGRATED CIRCUITS, FLIP PACKS

U6A.998979X 4 Cascade Binary, 75p. U3T.771139X Dual Differential Comparator, 75p. U3H.771239X d.c. amp. up to 30MHz, 75p. U31.993151X Clocked Flip Flop, 62½p.

Charges: 6½p up to 11 (paid for 12 and over).

FELSTEAD ELECTRONICS (PE503)

Longley Lane, Gatley, Cheadle, Ches. SK8 4EE


Cash with order only. No C.O.D. or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage unacceptable. S.A.E. please for inquiries or cannot be replied to. Changes apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

Build yourself a



great name HEATHKIT


You too can join the millions of satisfied Heathkit builders who have discovered the easy way to build better products than they could buy . . . have fun . . . and enjoy substantial savings in the process. Heathkit models are the beginner as well as the experienced man's first choice. Everything you need right down to the last nut and bolt is included in every kit. The wonderful step-by-step assembly manual is the last word in clarity. Want to know more . . . your first step is to send for the Free Heathkit catalogue and discover the unique satisfaction you can get from building the best.

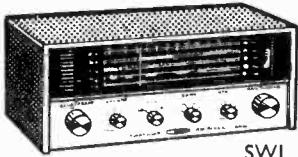

SWL



HI-FI

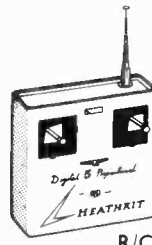

R/C



TEST



HOW TO BUY YOUR HEATHKIT

Orders for mail order dispatch from the factory may be placed at the London or Birmingham Heathkit Centres or by post to the Gloucester factory. Such orders are at 'direct-from-factory' prices which are lower than retail prices.

Goods may be purchased at the Heathkit Centres at retail prices.

Goods may be purchased at the Gloucester factory Showroom at 'direct-from-factory' prices.

London Heathkit Centre, 233 Tottenham Court Road.
Open Monday to Saturday 9 a.m. — 6 p.m. Phone 01-636 7349.

Birmingham Heathkit Centre, 17-18 St. Martin's House, Bull Ring.
Open Tuesday to Saturday 9 a.m. — 6 p.m. Phone 021-643 4366.

Gloucester factory Showroom, Bristol Road, Gloucester.
Open Monday to Saturday 9 a.m. — 5 p.m.

Please send me FREE Catalogue

NAME

ADDRESS

25/5/71



HEATH (GLOUCESTER) LTD.
GLOUCESTER GL2 6EE

PICKS UP AIRCRAFT TRANSMISSIONS (control to aircraft, etc.), **SHIPS AT SEA, TAXIS, AMBULANCES, LOCAL RADIO STATIONS, POP PIRATES, BUSINESS, STATIONS, ALL BBC, VHF & MANY, MANY, MANY MORE**, including fascinating public service transmissions that we are not allowed to mention! A miracle of advanced technology! You get far, far more than an ordinary radio! An instrument that will bring a new dimension to your world of sound! Frequency range: MW 540-1600 KHz, FM 88-108 MHz, Air 108-136 MHz, Intermediate Frequency: MW 455 KHz, FM 10.7 MHz, Air 10.7 MHz. **18 SEMI-CONDUCTORS:** Transistors 11, Diodes 6 + Thermistor! Automatic frequency control "locks-in", eliminating drift. Pinpoint station selection! Built-in adjustable 8-section 31in telescopic aerial. Lowest price ever! Tremendously strong leather-grained case with carry handle. 10 1/2in x 6 1/2in x 4in overall approx. Written guarantee. Only £11.97, carr., etc., 38p—with FREE pair of "aircraft spotter" high power "bino-scope" binoculars with built-in filters for viewing in strong sunlight and independent left and right eye focus. Send or call. Compare it with sets costing £40 or more. Refund if not delighted. **BONUS OFFER:** Shoulder strap, earphone for personal listening and batteries, all for 23p extra, if required.

#WHY PAY £40 OR MORE?

COMPLETE PORTABLE HIGH FIDELITY COMMUNICATIONS & RADIO RECEIVER

PLUS SPECIAL AIRCRAFT WAVEBAND!

OUR PRICE **£11.97** POST ETC. 38p

FREE TO EVERY PURCHASER "AIRCRAFT SPOTTER" HIGH POWER "BINO-SCOPE" BINOCULARS



ONLY FROM US! FIRST SHIPMENT JUST ARRIVED!

BRAND NEW 1971 Model! RUSSIAN WORLD BEATER!

6 WAVEBAND 10 TRANSISTOR PLUS 3 DIODES PORTABLE RADIO

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

£9.97 BOX POST ETC. 43p

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

***COMPARE ITS PERFORMANCE with £34 RADIOS!**



THE LATEST 1971 MODEL, SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection! Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of space and satellite communications. **YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE.** Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over the world—nothing is secret! The radio enthusiast has the world in his hand! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2in length. It's also a fabulous **CAR RADIO**—any speed requires no additional aerial. **UNIQUE!** Elegant Black, White and Chrome finish case. SIZE 10 1/2in x 8in x 3 1/2in, overall approx. Magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST, ETC., 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

STOP PRESS!

You can still order "By Post" THIS WAY:—


Whether you have a bank account or not—GO TO ANY BANK (Barclays if possible) obtain a **BANK GIRO FORM**—pay in the amount to cover your order, (including carriage, etc.), write full name and address and details of your order on reverse side of Giro Form. Address your completed **GIRO PAYMENT/ORDER** to: **SHOPERTUNITIES LTD. (PE/4), C/O BARCLAYS BANK LTD., Coda No. 2013-81, BRITISH MUSEUM BRANCH, LONDON, W.C.1,** and hand to bank cashier. We'll arrange immediate dispatch by carrier. This system of payment can always be used in the future (or for past ads.) if you wish.

SHOPERTUNITIES LTD. & L. Dept. PE/4, 164 UXBRIDGE ROAD (facing Shepherd's Bush Green), LONDON W12 8AQ (Thurs. 1, Fri. 7). Also 37 High Holborn, London, W.C.1 (Wed. 1, Thurs. 7). Both stores open from MON.-SAT. 9-6

NEW! HANDY! TIDY!

multi-drawer I-N-T-E-R-L-O-C-K-I-N-G storage units

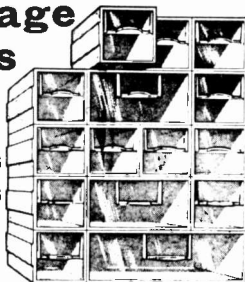A PLACE FOR EVERYTHING EVERYTHING IN ITS PLACE!



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (5ins x 2 1/2ins x 2 1/2ins) Usually 15p each, **OUR PRICE: £1.35 DOZEN**
DOUBLE UNITS (5ins x 4ins x 2 1/2ins) Usually 25p each, **OUR PRICE: £2.25 DOZEN**

PLUS QUANTITY DISCOUNTS!

Orders £5 and over DEDUCT 5% in the £
 Orders £10 and over DEDUCT 7 1/2% in the £
 Orders £20 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 30p to all orders under £5. Orders £5 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID



(Dept. PE5) 124 Cricklewood Broadway, London, N.W.2

4-STATION INTERCOM



£6.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.95. P. & P. 50p extra.

INTERCOM/BABY ALARM



£3.15

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 12p. P. & P. 25p.

Transistor TELEPHONE AMPLIFIER




£2.98

Why not boost efficiency with this incredible De-Luxe business amplifier? Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 12p extra. P. & P. 15p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/5)
 108 KENSINGTON HIGH STREET, LONDON, W.8

The Unique MULTI-MINI TWIN-VICE

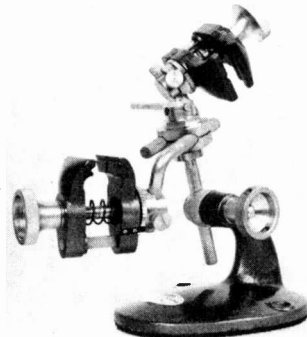

An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (24p P & P)

ALSO AVAILABLE

SINGLE VICE: £3.37 1/2 (20p P & P)

COVENTRY MOVEMENT CO. LTD.
 DEPT. PE 1, BURNSALL ROAD
 COVENTRY CV5 6BU STD 0203 - 74363

HOW TO TELL A STEREO SYSTEM THAT LOOKS GOOD FROM A STEREO SYSTEM THAT SOUNDS GOOD—BEFORE YOU PART WITH YOUR MONEY.


There's only one way to buy stereo equipment. Listen to it. Lots of it. Until you find the sound you like for the money you've got.

Sound advice. But try acting on it in 99% of hi-fi dealers and you'll be asked to show the colour of your money. We at Roc think that's unfair. So we fitted out our store in the Edgware Road with a series of sound systems, so you can hear all the stereo you want until you find the equipment you like. With no hustling.

But if you're one of those poor unfortunates who cannot make it in person, we'll sell you a system by mail. We've got the best range in town from single speakers to complete stereo set-ups.

Here are just six of the systems we've got in stock.

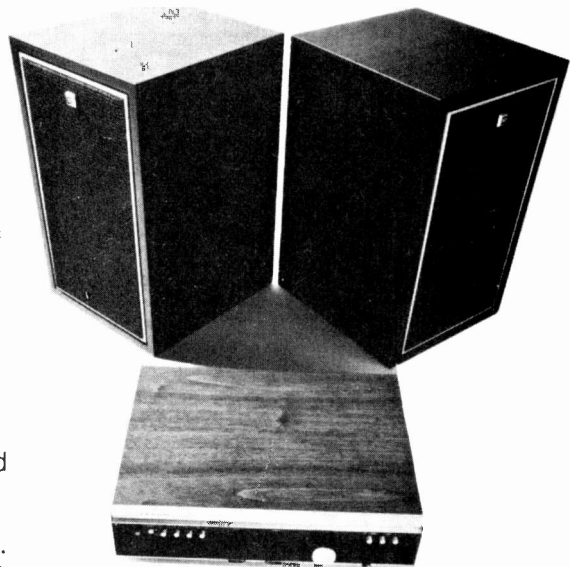Fill in the coupon and we'll have our systems brochure back to you by return.



Name _____
 Address _____


ROC ELECTRONICS LIMITED
 193 EDGWARE ROAD LONDON W2 1ET
 TELEPHONE: 01-723 6211

	Amplifier Output per channel	Speaker Capacity	Turntable	Price
System I.	4 Watts	6 Watts	Garrard 2025TC	£39.90
System II.	8 Watts	10 Watts	As system I.	£49.90
System III.	15 Watts	As System II	III A Garrard 2025TC	£59.90
			III B Garrard SP.25 MK III	£69.90
System IV.	20 Watts	20 Watts	Garrard SP.25 MK III	£79.90
System V	18 Watts	20 Watts	As System IV	£115.00
System VI.	30 Watts	30 Watts	Thorens TD150AB	£182.00

The KJ DISCOUNT AUDIO CATALOGUE

has something for EVERYONE!...

.....the most sophisticated of audio systems, cassette recorders, with musicassettes to go with them. Reel to reel recorders and accessories of every kind. Tapes at such incredible discounts it's too good to be true. Amplifiers, tuners, record players, HiFi for the do-it-yourselfer, headphones, mixers, radios for car and home, clock radios, speakers of all types, P.A. equipment, dust bugs, disc preeners, instalment credit—need we say more? ... we could, but it takes a whole catalogue to do so. Why not send for a copy by filling in the coupon below?

SENT FREE!



K.J. ENTERPRISES (Dept. PE5)
33 BRIDLE PATH, WATFORD, HERTS.

Tel. 25634
Showrooms: 101 ST. ALBANS ROAD, WATFORD, HERTS.

Please send me FREE a copy of the KJ fully illustrated colour discount catalogue by return of post. To:—
BLOCK CAPITALS PLEASE

Name
Address



To K.J. ENTERPRISES (Dept. P.E.5)
33 BRIDLE PATH WATFORD HERTS.

MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES LARGEST RANGE BRAND NEW FULLY GUARANTEED

MOTOROLA

We can now offer the whole vast range of Motorola IC's at industrial distributor prices. Please send 5p for price list. (24 pages).

Examples	5p	Data Sheets
MC724P	0-66	
MC790P	1-24	20-12½ extra
MC1303L	2-70	

FAIRCHILD (RTL)

	1-5	6-11	12+
L900	40p	37p	35p
L914	40p	37p	35p
L923	40p	37p	35p

LINEAR

	1-5	6-11	11-24
UA702A TO5	2-80	2-70	2-75
UA703C TO5	0-77	0-75	0-72
UA703C TO5	1-30	1-25	
UA705A TO6	1-25	1-17	1-12
UA708C DIL	0-65	0-55	0-50
UA709C TO5	0-55	0-52	0-48
UA710C TO5	1-25	1-17	1-12
UA710C TO5	0-70	0-65	0-60
UA716 TO5	1-87	1-75	1-70
UA729C TO5	1-62	1-50	1-42
UA730C TO5	1-80	1-45	1-37
UA741C TO6	0-87	0-80	0-70
UA741C DIL	0-87	0-80	0-70

MULLARD

TTL	5p	SL403A	2-12½
FJH101	0-87½	SL701C	1-45
FJH121	0-87½		
FJH141	0-87½		
FJH161	0-87½		
FJH171	0-91		
FJH221	0-87½		
FJ1101	1-37½		
FJ1121	1-87½		
FJ1141	3-12½		
FJ1191	1-87½		
FJ1251	3-12½		
FJY101	0-80		

PLESSEY

TTL	5p	SL403A	2-12½
SN7400	25p		
SN7401	25p		
SN7402	25p		
SN7403	25p		
SN7404	25p		
SN7405	25p		
SN7406	80p		
SN7408	25p		
SN7409	25p		
SN7410	25p		
SN7411	25p		
SN7413	50p		
SN7420	25p		
SN7430	25p		
SN7440	25p		
SN7441AN	£1		
SN7442	£1		
SN7446	£1-25		
SN7447	£1-10		
SN7448	£1		
SN7450	25p		
SN7451	25p		
SN7453	25p		
SN7454	25p		
SN7460	25p		
SN7472	40p		
SN7473	40p		
SN7474	45p		
SN7475	£1		
SN7476	45p		
SN7483	£1		
SN7486	50p		
SN7490	£1		
SN7492	£1		
SN7493	£1		
SN7495	£1		
SN7496	£1		
SN74107	45p		
SN74153	£1-90		
SN74154	£2-20		
SN74160	£1-80		
T187D1	£1-80		
SN74161/T187D1	£1-80		
T188D1	£1-80		
SN74164	£2-20		
SN74165	£2-25		
SN74192	£2-25		
SN74193	£2-25		

TOSHIBA

TTL	5p	TH0013P	24-57
TH9014P	£1-65		

MULLARD

DTL	5p	MULLARD LINEAR	5p
FCH101	0-87½	TAA241	1-62½
FCH121	1-05	242	4-25
FCH201	1-30½	243	1-60
FCH231	1-50	263	0-77½
FCJ101	1-62½	300	1-75
FCJ111	1-55	310	1-95
FCJ201	1-80	320	0-72½
FCJ211	2-75	350	1-75
FCK101	4-87½	435	1-47½
FCY101	1-05	521	1-28½
		522	2-80
		530	4-95
		570	1-97½
		811	4-45
		TAB101	0-97½
		TAD100	1-97½
		TAD110	1-97½

GENERAL ELECTRIC

TTL	5p	RCA	29A	1-65
PA222	4-37½	30	30	1-40
PA230	1-12½	35	35	1-25
PA234	1-07½	36	36	0-75
PA237	1-87½	38	38	0-85
PA246	2-87½	41	41	1-10
PA264	4-15	42	42	1-10
PA265	5-20	43	43	1-40
PA424	2-25	44	44	1-20
		45	45	1-25
		46	46	0-85
		47	47	1-40
		48	48	2-05
		49	49	1-00
		50	50	1-85
		51	51	1-85
		52	52	1-85
		53	53	0-85
		54	54	1-10
		55	55	2-40
		59	59	1-65
		64	64	1-20

TTL LOGICS

	1-24	25-99	100-499
SN7400	25p	20p	18p
SN7401	25p	20p	18p
SN7402	25p	20p	18p
SN7403	25p	20p	18p
SN7404	25p	20p	18p
SN7405	25p	20p	18p
SN7406	80p	75p	70p
SN7408	25p	20p	18p
SN7409	25p	20p	18p
SN7410	25p	20p	18p
SN7411	25p	20p	18p
SN7413	50p	45p	40p
SN7420	25p	20p	18p
SN7430	25p	20p	18p
SN7440	25p	20p	18p
SN7441AN	£1	90p	80p
SN7442	£1	90p	80p
SN7446	£1-25	£1-10	£1
SN7447	£1-10	£1	90p
SN7448	£1	90p	80p
SN7450	25p	20p	18p
SN7451	25p	20p	18p
SN7453	25p	20p	18p
SN7454	25p	20p	18p
SN7460	25p	20p	18p
SN7472	40p	35p	30p
SN7473	40p	40p	35p
SN7474	45p	40p	35p
SN7475	£1	90p	80p
SN7476	45p	40p	35p
SN7483	£1	90p	80p
SN7486	50p	45p	40p
SN7490	£1	90p	80p
SN7492	£1	90p	80p
SN7493	£1	90p	80p
SN7495	£1	90p	80p
SN7496	£1	90p	80p
SN74107	45p	40p	35p
SN74153	£1-90	£1-70	£1-60
SN74154	£2-20	£1-80	£1-45
SN74160	£1-80	£1-70	£1-60
T187D1	£1-80	£1-70	£1-60
SN74161/T187D1	£1-80	£1-70	£1-60
T188D1	£1-80	£1-70	£1-60
SN74164	£2-20	£1-95	£1-80
SN74165	£2-25	£1-95	£1-80
SN74192	£2-25	£1-95	£1-80
SN74193	£2-25	£1-95	£1-80

Data Sheets all 50-65 per type except L900/914/923 and Plessey 20-12½
8 Pin TO-5 I.C. Holders, 20-52½
14 Pin Dual-in-Line I.C. Holders, 20-32½
16 Pin Dual-in-Line I.C. Holders, 20-45
100 or more gates may be mixed to qualify for the 100+ price. This concession also applies to 25 or more MSI's.

See our ad. on opposite page for transistors, diodes and passive components and P. & P. charges. Many more types in stock and arriving daily. Please inquire.

A. MARSHALL & SON LTD.

LARGEST STOCKS BRAND NEW

SEMICONDUCTORS & COMPONENTS

WIDEST RANGE GUARANTEED

TRANSISTORS

2G301	20p	2N3405	45p	40311	85p	BC172	15p	88W70	27p	NKT238	25p
2G302	20p	2N3414	22p	40312	47p	BC175	22p	88X19	17p	NKT240	27p
2G303	20p	2N3415	22p	40314	37p	BC182	18p	88X21	17p	NKT241	27p
2G306	42p	2N3416	37p	40320	47p	BC183	18p	88X22	17p	NKT242	27p
2G308	30p	2N3417	37p	40323	32p	BC184	15p	88X26	45p	NKT243	27p
2G309	30p	2N3570	11-25	40324	47p	BC212L	12p	88X27	47p	NKT244	17p
2G371	20p	2N3572	87p	40326	37p	BCY30	27p	88X28	32p	NKT245	20p
2G374	20p	2N3566	87p	40329	30p	BCY31	27p	88X29	32p	NKT261	20p
2G381	22p	2N3606	27p	40344	27p	BCY32	25p	88X61	62p	NKT262	20p
2N404	22p	2N3702	12p	40347	57p	BCY33	25p	88X76	22p	NKT264	20p
2N696	20p	2N3703	12p	40348	52p	BCY34	30p	88X77	22p	NKT272	20p
2N697	20p	2N3702	12p	40360	47p	BCY39	60p	88X78	27p	NKT274	20p
2N698	25p	2N3704	17p	40361	47p	BCY40	60p	88Y10	27p	NKT275	20p
2N700	15p	2N3716	12p	40362	57p	BCY42	15p	88Y11	27p	NKT281	27p
2N708	15p	2N3707	15p	40370	32p	BCY43	15p	88Y24	15p	NKT401	87p
2N709	62p	2N3708	9p	40406	57p	BCY54	32p	88Y25	15p	NKT402	90p
2N718	25p	2N3709	10p	40407	40p	BCY58	22p	88Y26	15p	NKT403	75p
2N726	30p	2N3710	11p	40408	62p	BCY59	97p	88Y27	17p	NKT404	62p
2N727	30p	2N3711	12p	40410	62p	BCY60	97p	88Y28	17p	NKT405	75p
2N814	17p	2N3715	22-25	40467A	57p	BCY70	20p	88Y29	17p	NKT406	62p
2N816	17p	2N3716	22p	40468A	57p	BCY71	20p	88Y32	25p	NKT452	62p
2N818	30p	2N391	25-75	40600	57p	BCY72	20p	88Y36	25p	NKT453	47p
2N829	22p	2N3819	9p	AC107	80p	BCZ10	27p	88Y38	25p	NKT503F	32p
2N830	27p	2N3823	97p	AC126	20p	BCZ11	42p	88Y39	25p	NKT674F	30p
2N1090	22p	2N3854	27p	AC127	25p	BD116	42p	88Y40	32p	NKT677F	30p
2N1091	22p	2N3854A	27p	AC128	20p	BD121	65p	88Y51	32p	NKT713	30p
2N1131	25p	2N3855	27p	AC154	22p	BD123	62p	88Y52	32p	NKT781	30p
2N1132	25p	2N3855A	30p	AC176	25p	BD124	62p	88Y53	32p	NKT10419	30p
2N1302	17p	2N3856	35p	AC187	62p	BD130	75p	88Y56	40p	NKT10439	37p
2N1303	17p	2N3856A	35p	AC198	37p	BD132	62p	88Y57	40p	NKT10319	32p
2N1304	22p	2N3858	25p	ACY17	27p	BDY10	11-27	88Y78	45p	NKT2039	37p
2N1305	20p	2N3858A	30p	ACY18	25p	BDY11	11-62	88Y82	52p	NKT80111	77p
2N1306	25p	2N3859	27p	ACY19	25p	BDY17	21-50	88Y86	52p	NKT80113	77p
2N1307	20p	2N3859A	32p	ACY20	25p	BDY18	21-75	88Y90	57p	NKT80133	87p
2N1308	20p	2N3860	30p	ACY21	25p	BDY19	21-97	88Y92	57p	NKT80134	87p
2N1309	30p	2N3861	41-45	ACY22	20p	BDY38	97p	88Y93A	75p	NKT80212	92p
2N1507	17p	2N3877	40p	ACY28	20p	BDY60	21-25	C111	11-75	NKT80213	92p
2N1613	25p	2N3877A	40p	ACY40	20p	BDY61	21-25	C124	27p	NKT80214	92p
2N1631	35p	2N3900	37p	ACY41	40p	BDY62	21-25	C225	55p	NKT80215	92p
2N1632	30p	2N3900A	40p	ACY44	40p	BF115	25p	C428	37p	NKT80216	92p
2N1637	30p	2N3901	97p	ACY44	40p	BF115	25p	C428	37p	NKT80217	92p
2N1638	30p	2N3903	85p	AD140	52p	BF117	47p	C744	40p	NKT80218	92p
2N1639	37p	2N3904	35p	AD149	57p	BF163	25p	D13T1	62p	NKT80219	92p
2N1711	25p	2N3905	37p	AD150	37p	BF167	25p	D1P2	40p	NKT80220	92p
2N1889	32p	2N3906	37p	AD161	37p	BF173	32p	D1P3	37p	NKT80221	92p
2N1893	37p	2N4038	17p	AD162	37p	BF177	30p	D1P4	37p	NKT80222	92p
2N2147	82p	2N4039	10p	AF106	42p	BF178	30p	D1P6	40p	NKT80223	92p
2N2148	57p	2N4060	12p	AF114	25p	BF179	30p	D1P7	40p	NKT80224	92p
2N2160	57p	2N4061	12p	AF115	25p	BF180	30p	D1P8	40p	NKT80225	92p
2N2193	30p	2N4062	12p	AF116	25p	BF181	32p	GET102	30p	NKT80226	92p
2N2193A	42p	2N4244	47p	AF117	25p	BF184	32p	GET113	20p	NKT80227	92p
2N2194A	30p	2N4285	17p	AF118	62p	BF185	42p	GET114	20p	NKT80228	92p
2N2217	27p	2N4286	17p	AF119	20p	BF184	17p	GET118	20p	NKT80229	92p
2N2218	32p	2N4287	17p	AF124	22p	BF195	20p	GET119	20p	NKT80230	92p
2N2219	32p	2N4288	17p	AF125	20p	BF196	20p	GET120	52p	NKT80231	92p
2N2220	25p	2N4289	17p	AF126	20p	BF197	42p	GET121	52p	NKT80232	92p
2N2221	25p	2N4290	17p	AF127	17p	BF200	20p	GET122	52p	NKT80233	92p
2N2222	30p	2N4291	17p	AF127	17p	BF200	20p	GET123	52p	NKT80234	92p
2N2287	11-071	2N4292	18p	AF139	37p	BF224	20p	GET124	52p	NKT80235	92p
2N2297	30p	2N4303	47p	AF178	42p	BF225	20p	GET125	52p	NKT80236	92p
2N2368	17p	2N5027	52p	AF179	72p	BF237	22p	GET126	52p	NKT80237	92p
2N2369	17p	2N5028	57p	AF180	72p	BF238	22p	GET127	52p	NKT80238	92p
2N2369A	17p	2N5029	57p	AF181	42p	BF244	32p	GET128	52p	NKT80239	92p
2N2410	42p	2N5030	42p	AF239	42p	BFW38	27p	GET129	52p	NKT80240	92p
2N2483	17p	2N5172	12p	AF279	47p	BFW59	25p	GET130	52p	NKT80241	92p
2N2484	32p	2N5174	52p	AF280	62p	BFW60	25p	MJ400	01-07	NKT80242	92p
2N2539	22p	2N5175	52p	AFZ11	32p	BFW61	47p	MJ420	01-12	NKT80243	92p
2N2540	22p	2N5176	45p	AFY26	25p	BFX12	22p	MJ430	01-02	NKT80244	92p
2N2613	30p	2N5292A	80p	AFY27	37p	BFX13	22p	MJ440	05-21	NKT80245	92p
2N2614	30p	2N5293	80p	AFY28	27p	BFX29	27p	MJ480	07-10	NKT80246	92p
2N2646	52p	2N5246	42p	AFY29	27p	BFX30	30p	MJ481	01-25	NKT80247	92p
2N2696	32p	2N5249	67p	AFY36	25p	BFX43	37p	MJ491	01-25	NKT80248	92p
2N2711	25p	2N5265	23-25	AFY30	25p	BFX44	37p	MJ500	01-25	NKT80249	92p
2N2712	25p	2N5266	23-25	AFY31	32p	BFX68	37p	MJ520	01-25	NKT80250	92p
2N2713	27p	2N5267	22-22	AFY34	25p	BFX84	25p	MJ530	01-25	NKT80251	92p
2N2714	30p	2N5305	27p	AFY86	32p	BFX85	25p	MJE250	01-25	NKT80252	92p
2N2865	62p	2N5306	27p	ASZ20	37p	BFX87	27p	MJE250	01-25	NKT80253	92p
2N2904	30p	2N5307	87p	ASZ21	42p	BFX88	27p	MJE250	01-25	NKT80254	92p
2N2904A	30p	2N5308	37p	ASZ21	42p	BFX89	27p	MJE250	01-25	NKT80255	92p
2N2905	37p	2N5309	62p	AI103	11-50	BFX93A	62p	MJE3055	01-27	NKT80256	92p
2N2905A	40p	2N5310	42p	BC107	12p	BFY10	32p	MFP102	42p	NKT80257	92p
2N2906	25p	2N5354	27p	BC108	12p	BFY11	42p	MFP103	42p	NKT80258	92p
2N2906A	27p	2N5355	27p	BC109	12p	BFY17	22p	MFP104	37p	NKT80259	92p
2N2907	30p	2N5356	32p	BC110	20p	BFY18	32p	MFP105	37p	NKT80260	92p
2N2923	15p	2N5365	47p	BC113	20p	BFY19	32p	MP83638	32p	NKT80261	92p
2N2924	15p	2N5366	32p	BC115	27p	BFY20	21-60	NKT80013	47p	NKT80262	92p
2N2925	15p	2N5367	37p	BC116A	27p	BFY21	21-60	NKT80014	47p	NKT80263	92p
2N2926	15p	2N5457	37p	BC118	32p	BFY22	21-60	NKT80015	47p	NKT80264	92p
Green	14p	28005	75p	BC121	20p	BFY24	45p	NKT80016	47p	NKT80265	92p
Yellow	18p	28102	22	BC122	20p	BFY25	20p	NKT80017	47p	NKT80266	92p
Orange	18p	28103	25p	BC125	35p	BFY26	20p	NKT80018	47p	NKT80267	92p
2N3011	30p	28103	25p	BC126	35p	BFY29	50p	NKT80019	47p	NKT80268	92p
2N3014	32p	28104	25p	BC140	37p	BFY30	50p	NKT80020	47p	NKT80269	92p
2N3033	25p	28501	32p	BC147	17p	BFY41	50p	NKT80021	47p	NKT80270	92p
2N3034	25p	28502	35p	BC148	12p	BFY43	62p	NKT80022	47p	NKT80271	92p
2N3035	25p	28503	37p	BC149	12p	BFY50	62p	NKT80023	47p	NKT80272	92p
2N3133	30p	3N63	40p	BC152	17p	BFY51	22p	NKT80024	47p	NKT80273	92p
2N3134	30p	3N128	70p	BC152	17p	BFY52	22p	NKT80025	47p	NKT80274	92p
2N3135	25p	3N139	11-27	BC157	20p	BFY53	17p	NKT80026	47p	NKT80275	92p
2N3136	25p	3N140	77p	BC158	17p	BFY56A	30p	NKT80027	47p	NKT80276	92p
2N3390	25p	3N141	75p	BC159	20p	BFY75	30p	NKT80028	47p	NKT80277	92p
2N3391	20p	3N142	62p	BC160	62p	BFY76	30p	NKT80029	47p	NKT80278	92p
2N3391A	20p	3N143	67p	BC167	15p	BFY77	30p	NKT80030	47p	NKT80279	92p
2N3392	17p	3N152	87p	BC168B	14p	BFY90	67p	NKT80031	47p	NKT80280	92p
2N3393	15p	R.C.A.	—	BC168C	1						

R+TV RADIO & TV COMPONENTS (Acton) Ltd.

21d High St., Acton, London W3 6NG
323 Edgware Road, London, W.2
ALL MAIL ORDERS TO OUR ACTON BRANCH
Terms C.W.O. All inquiries S.A.E.

Complete Stereo System £43

WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER



This superb stereo system is a real price breakthrough. It comprises the VISCOUNT F.E.T. Mk. I amplifier on which full details are given below, the famous Garrard SP25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½ in. x 10½ in. x 6½ in., the Duo type 2 speakers are teak finished with matching Vynair grills. They incorporate a 3 ohm 13 in. x 8 in drive unit with parasitic tweeter. Maximum power handling 10 watts, price:

£13.50 per pair plus £1.50 P. & P.

Complete stereo system £43 plus P. & P. £2.50

With Mk. II Amplifier and Magnetic Cartridge £48 plus P. & P. £2.50



THE RELIANT Mk. II SOLID STATE GENERAL PURPOSE AMPLIFIER

£7.25 Plus P. & P. 50p
Simulated teak case

SPECIFICATION: Output: 10 watts into a 3 ohms speaker. Inputs: (1) for mike (10mV). Input (2) for gram. radio (250mV). Transistors: 4 silicon and three germanium. Mains input: 220/250 volts. Size: 10½ x 4½ x 2½ in.



ELEGANT SEVEN Mk. III (350mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board —back printed for foolproof construction. MAINS POWER PACK KIT: (47p) extra.

£5.25 Plus P. & P. 50p. Circuit 13p Free with parts.

THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3 in.

£5.25 Plus P. & P. 50p. Circuit 13p. Free with parts.



SOUND 50 50 WATT AMPLIFIER AND SPEAKER SYSTEM



Output Power: 45 watts R.M.S. (5ine wave drive). **Frequency response:** —3dB points 30Hz at 18KHz. **Total distortion:** less than 2% at rated output. **Signal to noise ratio:** better than 60dB. **Speaker Impedance:** 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power. **SPEAKERS!** Size 20" x 20" x 10" incorporating Baker "12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two-tone colour scheme—Black and grey.

The Viscount F.E.T. Mk. I £14.25 Plus 50p P.&P.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Output per channel—10W rms. into 3 ohms. **Frequency bandwidth** 20Hz to 20KHz ±1dB @ 1W. **Total distortion @ 1kHz @ 9W 0.5%.** **Input sensitivities—**CER. P.U. 100mV into 3 MΩ; Tuner 100mV into 100KΩ; Tape 100mV into 100KΩ. **Overload Factor—**Better than 26dB. **Signal to noise ratio—**70dB on all inputs (with vol. max).

Controls—6 position selector switch (3 pos. stereo and 3 pos. mono), separate vol. controls for left and right channels. **Bass** ±14dB @ 60Hz; **Treble** (with D.P.S. on/off) ±12dB @ 10KHz. **Tape recording output sockets** on each channel.

Size 12½ in. x 6 in. x 2½ in simulated teak case. Built and tested.

Mk. II (MAG. P.U.) £15.75 Post & packing 50p extra.

Specification same as Mk. I, but with the following inputs: Mag. P.U. CER. P.U. Tuner.

LIQUIDATED STOCK

DANSETTE

TOURISTE MK3 CAR RADIO

ALL TRANSISTOR


Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7" x 2" x 4½" deep.

Originally sold completely built for (£15.23)
Circuit diagram 13p, free with parts Speaker, baffle and fixing kit
£1.25 extra plus P. & P. 25p

SET OF PARTS

£6.30 Plus P. & P. 50p

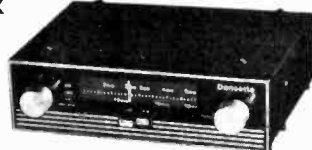Speaker postage free when ordered with parts



COMPLETE SYSTEM £50 Plus £4 P. & P.

Sound 50 amp and 2 speakers

or available separately
Amplifier: £28.50 plus £1.50 P. & P.
Speaker: £12.50 each plus £1.75 P. & P.

Litesold

SOLDERING INSTRUMENTS



- SIX SIZES—10 WATTS TO 60 WATTS
- EXCELLENT THERMAL STABILITY
- STRONG, LIGHTWEIGHT, COMFORTABLY ELEGANT DESIGN
- UNEQUALLED PERFORMANCE
- PUSH-IN BITS, COPPER OR LONG-LIFE
- INDICATOR LAMPS OPTIONAL ON ALL MODELS
- ALL VOLTAGES
- EASY MAINTENANCE

PLEASE ASK FOR NEW LEAFLETS 37/1001/3

LIGHT SOLDERING DEVELOPMENTS LTD

28 Sydenham Road, Croydon CR9 2LL
Telephone 01-688 8589 & 4559



RST VALVE MAIL ORDER CO.
BLACKWOOD HALL,
WELLFIELD RD., S.W.16
SPECIAL EXPRESS MAIL ORDER SERVICE
All orders post free!

	5p		5p		5p		5p		5p
1N21	0-18	AC127	0-25	BF173	0-30	GJ4M	0-38	OC43	0-40
1N23	0-20	AC128	0-25	BF181	0-38	GJ5M	0-25	OC44	0-18
1N85	0-88	AC187	0-80	BF184	0-25	GJ7M	0-28	OC44M	0-18
1N233	0-50	AC188	0-30	BF185	0-25	HG1005	0-50	OC71	0-40
1N256	0-20	AC177	0-30	BF194	0-18	HS100A	0-20	OC43M	0-18
1N645	0-25	AC178	0-25	BF195	0-15	MAT100	0-25	OC46	0-28
1N725A	0-20	AC179	0-25	BF196	0-28	MAT101	0-30	OC57	0-60
1N914	0-08	AC120	0-28	BF197	0-28	MAT120	0-25	OC58	0-60
1N4007	0-28	ACY21	0-28	BF861	0-28	MAT121	0-30	OC59	0-65
18021	0-20	ACY22	0-18	BF898	0-28	MJE320	0-28	OC86	0-60
18113	0-15	ACY27	0-25	BFX12	0-28	MJE2855	1-75	OC70	0-15
18130	0-18	ACY28	0-18	BFX13	0-28	MG3050	0-20	OC71	0-15
18131	0-18	ACY39	0-35	BFX29	0-45	NKT128	0-30	OC72	0-25
18202	0-22	AC140	0-15	BFX30	0-38	NKT129	0-30	OC73	0-30
2G240	1-08	AC141	0-25	BFX35	0-08	NKT211	0-25	OC74	0-30
2G301	0-18	AC144	0-28	BFX63	0-50	NKT213	0-25	OC75	0-25
2G302	0-22	AD140	0-50	BFX84	0-30	NKT214	0-15	OC76	0-25
2G306	0-30	AD149	0-50	BFX85	0-40	NKT216	0-28	OC77	0-20
2G371	0-25	AD161	0-38	BFX86	0-38	NKT217	0-40	OC78	0-18
2G381	0-25	AD162	0-38	BFX87	0-28	NKT218	1-13	OC78D	0-20
2G414	0-30	AF106	0-30	BFX88	0-25	NKT219	0-38	OC79	0-28
2G417	0-22	AF114	0-32	BFY10	1-00	NKT222	0-20	OC81	0-25
2N214	0-48	AF115	0-30	BFY11	1-25	NKT224	0-28	OC81D	0-20
2N247	0-25	AF116	0-32	BFY17	0-25	NKT251	0-24	OC81M	0-20
2N250	0-50	AF117	0-25	BFY18	0-25	NKT271	0-25	OC81DM	0-20
2N404	0-22	AF118	0-25	BFY19	0-25	NKT272	0-25	OC82	0-15
2N697	0-15	AF119	0-25	BFY24	0-45	NKT273	0-20	OC82	0-25
2N698	0-48	AF124	0-25	BFY44	1-00	NKT274	0-20	OC82D	0-15
2N706	0-10	AF125	0-25	BFY50	0-28	NKT275	0-25	OC83	0-25
2N706A	0-18	AF126	0-18	BFY51	0-20	NKT277	0-20	OC84	0-25
2N708	0-15	AF127	0-18	BFY52	0-28	NKT278	0-25	OC114	0-28
2N709	0-28	AF139	0-30	BFY53	0-18	NKT301	0-30	OC122	0-25
2N711	0-30	AF178	0-45	BFY64	0-45	NKT304	0-25	OC123	0-50
2N987	0-53	AF179	0-48	BFY90	0-68	NKT403	0-75	OC139	0-25
2N1090	0-30	AF180	0-53	BFX27	0-50	NKT404	0-63	OC140	0-28
2N1091	0-33	AF181	0-43	BFX60	0-93	NKT678	0-30	OC141	0-68
2N1131	0-30	AF186	0-40	BFX76	0-15	NKT713	0-25	OC199	0-20
2N1132	0-30	AFY19	1-13	BHY26	0-18	NKT773	0-25	OC170	0-20
2N1302	0-20	AFZ11	0-63	BIZ27	0-20	NKT777	0-20	OC171	0-20
2N1303	0-25	AFZ12	0-75	BBY51	0-50	OT7B	0-28	OC200	0-28
2N1304	0-25	ASY26	0-25	BBY95A	0-15	OA2	0-15	OC201	0-48
2N1305	0-25	ASY27	0-38	BBY95	0-15	OA6	0-13	OC202	0-28
2N1306	0-25	ASY28	0-25	BT102/500R		OA47	0-10	OC203	0-68
2N1307	0-25	ASY29	0-30	BT42	0-75	OA70	0-10	OC204	0-40
2N1308	0-30	ASY36	0-25	BTY79/100R	0-98	OA71	0-10	OC205	0-68
2N1309	0-25	ASY30	0-18	BTY79/100R	0-75	OA73	0-10	OC206	0-75
2N1420	0-93	ASY51	0-40			OA74	0-10	OC207	0-75
2N1507	0-28	ASY53	0-30	BTY78/400R	0-75	OA79	0-10	OC460	0-20
2N1526	0-38	ASY55	0-20		1-75	OA81	0-10	OC470	0-20
2N1909	2-25	ASY62	0-25	BY100	0-18	OA85	0-13	OCF71	0-38
2N2147	0-75	ASY86	0-33	BY126	0-15	OA86	0-18	OCF72	0-25
2N2148	0-60	ASZ21	0-43	BY127	0-10	OA90	0-10	ORP60	0-40
2N2160	0-63	ASZ23	0-75	BY182	0-75	OA91	0-08	ORP61	0-48
2N2218	0-30	AUV10	0-98	BY213	0-25	OA95	0-08	S19T	0-20
2N2219	0-38	AU101	1-50	BY213	0-20	OA200	0-06	SAC40	0-25
2N2287	1-03	BC107	0-25	BY210	0-40	OA202	0-10	SFT308	0-28
2N2297	0-30	BC108	0-25	BY211	0-35	OA210	0-25	SFT22	0-28
2N2309A	0-20	BC109	0-25	BY212	0-30	OA211	0-25	SFT23	0-28
2N2513	0-25	BC113	0-50	BY213	0-20	OA2200	0-55	SX68	0-20
2N2646	0-53	BC115	0-33	BY213	0-35	OA2201	0-50	SX631	0-20
2N2712	0-25	BC116	0-40	BY215	1-00	OA2202	0-43	SX635	0-25
2N2784	0-50	BC116A	0-45	YZ16	0-63	OA2203	0-43	SX640	0-28
2N2846	2-25	BC118	0-38	BYZ88CV3		OA2204	0-43	SX641	0-25
2N2848	0-43	BC121	0-20			OA2205	0-43	SX642	0-28
2N2904	0-30	BC125	0-20	CI11	0-65	OA2206	0-43	SX644	0-48
2N2904A	0-33	BC125	0-20	CR81/05	0-20	OA2207	0-48	SX645	0-75
2N2906	0-30	BC126	0-65	CR81/40	0-48	OA2208	0-33	V15/30P	0-60
2N2907	0-38	BC140	0-55	CR8B	3-50	OA2209	0-33	V30/201P	0-28
2N2924	0-23	BC147	0-18	CS10B	2-10	OA2210	0-33	V60/201	0-28
2N2925	0-18	BC148	0-18	DD000	0-15	OA2211	0-33	V60/201P	0-38
2N2926	0-18	BC149	0-20	DD006	0-18	OA2212	0-40	XA102	0-18
2N3024	0-40	BC157	0-20	DD007	0-18	OA2223	0-40	XA102	0-18
2N3025	0-75	BC157	0-20	DD007	0-40	OA2224	0-38	XA151	0-15
2N3702	0-13	BC158	0-20	DD008	0-20	OA2241	0-23	XA152	0-15
2N3705	0-15	BC160	0-13	GD3	0-33	OA2242	0-23	XA161	0-25
2N3706	0-23	BC169	0-13	GD4	0-05	OA2244	0-23	XA162	0-25
2N3707	0-15	BCY31	0-30	GD5	0-33	OA2246	0-23	XB101	0-48
2N3709	0-13	BCY32	0-25	GD8	0-25	OA2290	0-38	XB102	0-10
2N3710	0-13	BCY32	0-50	GD12	0-05	OC16	0-43	XB103	0-25
2N3711	0-13	BCY33	0-20	GET102	0-30	OC16T	0-28	XB113	0-10
2N3819	0-35	BCY34	0-25	GET103	0-23	OC19	0-38	XB121	0-43
2N3820	0-38	BCY38	0-30	GET113	0-20	OC20	0-96	ZR24	0-68
2N3823	0-75	BCY39	0-48	GET114	0-15	OC22	0-45	Z8170	0-10
2N5027	0-53	BCY40	0-43	GET115	0-45	OC23	0-50	Z8170	0-10
2N5098	0-33	BCY42	0-15	GET116	0-50	OC24	0-50	Z8271	0-18
28005	0-75	BCY70	0-20	GET120	0-25	OC25	0-38	ZT21	0-25
28301	0-43	BCY71	0-30	GET872	0-30	OC26	0-25	ZT43	0-25
28304	0-63	BCZ10	0-30	GET875	0-25	OC28	0-63	ZTX107	0-15
28301	0-28	BCZ11	0-38	GET880	0-28	OC29	0-63	ZTX108	0-15
28703	0-63	BD121	0-65	GET881	0-25	OC30	0-40	ZTX300	0-15
AA129	0-20	BD123	0-63	GET882	0-25	OC31	0-50	ZTX304	0-25
AAZ12	0-30	BDY11	1-63	GET885	0-08	OC33	0-50	ZTX304	0-25
AAZ13	0-13	BF115	0-25	GEX44	0-08	OC36	0-63	ZTX500	0-15
AC107	0-38	BF117	0-50	GEX45/1	0-08	OC41	0-25	ZTX503	0-20
AC126	0-25	BF167	0-25	GJ3M	0-25	OC42	0-30	ZTX331	0-20

SEMI-CONDUCTOR SET FOR P. E. GEMINI AMPLIFIER £12.95

SEND S.A.E. FOR LIST OF 3,000 TYPES VALVES, TUBES AND TRANSISTORS

Open daily to callers: Mon.-Sat. 9 a.m.-5.30 p.m.
Closed Sat. 1.30 p.m.-2.30 p.m.

Terms C.W.O. only | Tel. 01-769 0199/1649

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. **£6.97.** P. & P. 17jp.



AVO CT471A MULTIMETER
Battery operated, fully transistorised. Sensitivity 100mΩ/V. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12uA to 1.2 Amp. Resistance 12 ohm to 120 MΩ HF, VHF, UHF. Voltage with multiplier 4V to 400V up to 50 Mc/s, 40mV to 4V up to 1,000 Mc/s. Offered in perfect condition. **£55 each.** Carr. 50p.

CRYSTAL CALIBRATORS No. 10

Small portable crystal controlled wavemeter. Size 7" x 7" x 4". Frequency range 600 Kc/s. 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirement 300 V. D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. **£3.47.** Carr. 37jp.

B.C. 221 FREQUENCY METERS
latest release 125kHz to 20MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. **£27.50 each.** Carr. 50p.

AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. High quality precision instrument made for the industry by Airmec. Frequency coverage 20-80 Mc/s. AM, V.M., F.M. Incorporates precision dial level meter, precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12-8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. **£45.** Carr. £1.

AVO CT.38 ELECTRONIC MULTIMETERS

High quality 97 range instrument which measures a.c. and d.c. Voltage, Current, Resistance and Power Output Ranges d.c. volts 250mV-10,000V (10 megΩ-110 megΩ input). D.c. current 10μA-25A. Ohms 0-1,000 megΩ a.c. volt 100mV-250V (with R.F. measuring head up to 250MHz) a.c. current 10μA-25A. Power output 50 microwatts-5 watts. Operation 0/110/200/250V a.c. Supplied in perfect condition complete with circuit lead and R.F. probe. **£25.** Carr. 70p.

ADMIRALTY 62B RECEIVERS

High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 150-300 Kc/s; 660 Kc/s-1.5 Mc/s; 3-30-350 Kc/s. I.F. 500/KHz. Incorporated R.F. and 31.F. stages, bandpass filter, noise limiter, crystal controlled B.P.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/230V a.c. Size 19 1/2 x 18in. Weight 114lb. Offered in good working condition. **£22.50.** Carr. £1.50. With circuit diagrams. Also available B41 L.F. version of above. 15KHz-700Hz. **£17.50.** Carr. £1.50.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPB-1 MHz. Input Imp. 2 megΩ 25 P.F. Illuminated scale. 120 tube. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. **£22.50.** Carr. 50p.

TO-3 PORTABLE OSCILLOSCOPE

3in tube. Y amp. Sensitivity 0.1V p-p/CM. Bandwidth 1.5 cps-1.5MHz. Input Imp. 2 megΩ 25P F X amp. sensitivity 0.5V p-p/CM. Bandwidth 1-5cps-300KHz. Input Imp. 2 megΩ 30P.F. Time base 5 ranges 10 cps-300KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 30mm. Weight 15lb 220/240V. A.C. Supplied brand new with handbook. **£37.50.** Carr. 50p.

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC. ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100		TYPE S-80	
100 x 80 mm		80 mm square fronts	
500μA	£3.12	50μA	£3.12
1mA	£2.97	50-0-50μA	£2.97
20V d.c.	£2.97	100μA	£2.97
50V d.c.	£2.97	100-0-100μA	£2.97
300V d.c.	£2.97	500μA	£2.62
1A d.c.	£2.97	1mA	£2.47
5A d.c.	£2.97	20V d.c.	£2.47
100μA	£2.87	30V d.c.	£2.47
100-0-100μA	£2.25	300V d.c.	£2.82
		500μA	£2.87
		1mA	£2.47
		5A d.c.	£2.47
		300V a.c.	£2.82
		VU Meter	£3.87

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in x 4 1/2in fronts		Type MR.38P. 1 21/32in square fronts	
50μA	£3.60	150mA	£1.37
50-0-50μA	£3.10	300mA	£1.37
100μA	£2.75	500mA	£1.37
100-0-100μA	£2.30	750mA	£1.37
500μA	£2.87	1A	£1.37
500-0-500μA	£2.60	2A	£1.37
1mA	£2.60	5A	£1.37
1-0-1mA	£2.60	10A	£1.37
5mA	£2.60	20V d.c.	£2.60
10mA	£2.60	50V d.c.	£2.60
		150V d.c.	£2.60
		300V d.c.	£2.60
		15V a.c.	£2.60
		300V a.c.	£2.60
		S Meter	£2.87
		1mA	£2.87
		VU Meter	£3.50
		1A a.c.*	£2.60
		5A a.c.*	£2.60
		10A a.c.*	£2.60
		20A a.c.*	£2.60
		30A a.c.*	£2.60

Type MR.52P. 3 1/2in square fronts		Type MR.45P. 2in square fronts	
50μA	£3.10	50μA	£2.25
50-0-50μA	£2.60	50-0-50μA	£2.10
100μA	£2.60	100μA	£2.10
100-0-100μA	£2.37	100-0-100μA	£1.87
500μA	£2.25	200μA	£1.87
500-0-500μA	£2.00	500μA	£1.60
1mA	£2.00	10mA	£1.50
1-0-1mA	£2.00	50mA	£1.50
5mA	£2.00	100mA	£1.50
10mA	£2.00	500mA	£1.50
		1A	£1.50
		5A	£1.50
		10V d.c.	£2.00
		20V d.c.	£2.00
		50V d.c.	£2.10
		150V d.c.	£2.10
		300V d.c.	£2.10
		15V a.c.	£2.10
		30V a.c.	£2.10
		50V a.c.	£2.10
		150V a.c.	£2.10
		300V a.c.	£2.10
		500V a.c.	£2.10
		S Meter	£2.87
		VU meter	£3.87
		1mA	£2.87
		10mA	£2.10
		50mA	£2.10
		100mA	£2.10
		500mA	£2.10
		1A	£2.10
		5A	£2.10
		10A	£2.10
		20A	£2.10
		30A	£2.10

Type MR.65P. 3 1/2in x 3 1/2in fronts	
50μA	£3.87
50-0-50μA	£2.75
100μA	£2.75
100-0-100μA	£2.60
200μA	£2.60
500μA	£2.37
500-0-500μA	£2.10
1mA	£2.10
5mA	£2.10
10mA	£2.10
50mA	£2.10
100mA	£2.10
500mA	£2.10
1A	£2.10
5A	£2.10
10A	£2.10
20A	£2.10
30A	£2.10
50A	£2.37
10V d.c.	£2.10
20V d.c.	£2.10
50V d.c.	£2.10
150V d.c.	£2.10
300V d.c.	£2.10
15V a.c.	£2.10
30V a.c.	£2.10
50V a.c.	£2.10
150V a.c.	£2.10
300V a.c.	£2.10

"SEW" BAKELITE PANEL METERS

Type MR.65 3 1/2in square fronts	
500μA	£1.75
1A	£1.75
5A	£1.75
15A	£1.75
30A	£1.75
50A	£1.75
5V d.c.	£1.75
10V d.c.	£1.75
20V d.c.	£1.75
50V d.c.	£1.75
150V d.c.	£1.75
300V d.c.	£1.75
30V a.c.*	£1.75
50V a.c.*	£1.75
150V a.c.*	£1.75
300V a.c.*	£1.75
500μA	£2.25
1mA	£2.25
5A	£2.25
15A	£2.25
30A	£2.25
5V d.c.	£2.25
10V d.c.	£2.25
20V d.c.	£2.25
50V d.c.	£2.25
150V d.c.	£2.25
300V d.c.	£2.25
30V a.c.*	£2.25
50V a.c.*	£2.25
150V a.c.*	£2.25
300V a.c.*	£2.25

* MOVING IRON - ALL OTHERS MOVING COIL Please add postage

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm. The a new range of high quality moving coil instruments ideal for school experiments and other bench applications. The 3" mirror scale. The easily accessible to working. Available in the following ranges:

100μA	£4.50	20V d.c.	£3.97
1mA	£4.25	50V d.c.	£3.97
10mA	£3.97	300V d.c.	£3.97
50-0-50μA	£4.25	Dual range 500μA/5A d.c.	£4.25
1-0-1mA	£3.97	5V/50V d.c.	£4.25
1A d.c.	£3.97	Triple range 1mA/10mA/100mA	£4.62
5A d.c.	£3.97		
10V d.c.	£3.97		

EDGWISSE METERS



PE.70 3 1/2in x 1 1/2in x 2 1/2in deep			
50μA	£3.00	500μA	£2.60
50-0-50μA	£2.87	1mA	£2.37
100μA	£2.87	300V a.c.	£2.37
100-0-100μA	£2.75	VU meter	£3.25
200μA	£2.75		

MARCONI TF148E DISTORTION FACTOR METERS. Excellent condition. Fully tested. **£20.** Carr. 75p.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. 6 Ranges ±1%. L. 1 μH - 11.1 HENRY'S. 6 Ranges -2%. C. 10pF ±11.1 μm F.d. 6

Ranges ±2%. TURNS RATIO 1:1/1000-1:1100. 6 Ranges ±1%. Bridge voltage at 1,900 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2in. **£20.** P. & P. 25p.

COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES. D.c. coupled. Band width 1kc/s. Perfect order. **£25.** Carr. £1.50.

TE-16A Transistorised Signal Generator. 5 ranges 400 kHz-30 MHz. An inexpensive instrument for the laboratory. Operates on 9v battery. Wide, easy to read scale. 800 kHz modulation. 5 1/2 x 5 1/2 x 3 1/2in. Complete with instructions and leads. **£7.97.** P. & P. 20p.




LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS. Frequency 0-20 Kc/s on 2 ranges. Output 500Ω or 5kΩ. Operation 200/250V. A.C. Supplied in perfect order. **£12.50.** Carr. 50p.

MARCONI TP885 VIDEO OSCILLATORS. 0-5MHz. Sine Square Wave. **£45.** Carr. £1.

LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER

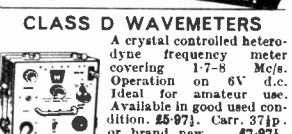2pF-2,000 mfd 2 ohms-200 megohms. Also checks impedance, turns ratio, insulation. 200/250V a.c. Brand New **£17.50** Carr. 37p.




CLASS D WAVEMETERS

A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 8V d.c. Ideal for amateur use. Available in good used condition. **£5.97.** Carr. 37jp. or brand new. **£7.97.** Carr. 37jp.

MARCONI TF195M BEAT FREQUENCY OSCILLATORS. 0-40KHz. **£20.** Carr. £1.50.

Latest Catalogue

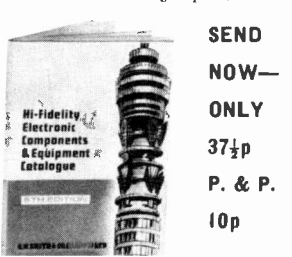Our latest edition giving full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT FREE DISCOUNT COUPONS VALUE 50p (10%). 248 pages, fully illustrated and detailing thousands of items at bargain prices.



SEND NOW— ONLY 37jp P. & P. 10p

G. W. SMITH & CO (RADIO) LTD. Also see next two pages

SEMICONDUCTOR VALVES

BRAND NEW & FULLY GUARANTEED

HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE

SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



GARRARD

FULL CURRENT RANGE OFFERED, BRAND NEW AT FANTASTIC SAVINGS


- 2025T/C stereo £9-87 SL72B £26-97
 40 MKII stereo £8-40 AP76 £20-97
 3000 stereo £10-50 SL73B £30-75
 SP25 MKIII £11-75 SL95B £40-97
 SL65B £14-97 401 £29-37
- Carriage 37 1/2 extra each item.
- TEAK PLINTHS AND PERSEX COVERS
 1. For SP25, SL65, SL55, 3000, 2025T/C, 2025, 1000. £8-97
 2. For AP75, SL75, SL95. £5-97
 3. For SP25 etc. to operate with lid in place £5-97
 Carriage 37 1/2 extra each type.



Full range of Garrard accessories available.

TRANSISTORS				VALVES							
IN914	79	AC187	309	BY100	15p	0A2	389	25Z4	309	EL95	25p
IN4001	89	AC188	309	BY124	15p	0B2	45p	25Z5	45p	EM90	50p
IN4002	99	AC177	309	BY126	15p	0Z4	30p	25Z6	85p	EM81	50p
IN4003	10p	AC178	25p	BY127	20p	1L4	30p	30C15	80p	EM84	35p
IN4004	10p	AC199	25p	BY210	40p	IR5	35p	30C17	85p	EM85	31
IN4005	15p	AC20	25p	BY211	35p	185	25p	30C18	75p	EM87	42p
IN4006	15p	AC21	25p	BY212	30p	IT4	25p	30F5	65p	EY61	40p
IN4007	25p	AC22	17p	BY213	35p	IT4	27p	30FL1	70p	EY86	40p
IN4148	79	BY28	17p	MJ480	97p	3V4	45p	30FL2	85p	EY87	40p
IN6054	25p	AC40	15p	MJ481	£1-25	2D21	40p	30FL4	75p	EZ40	45p
2G301	30p	AD140	50p	MPP102	48p	3Q4	40p	30L15	65p	EZ41	45p
2G302	25p	AD149	50p	MPP103	35p	384	35p	30L17	80p	EZ80	25p
2G303	30p	AD161	37p	MPP104	37p	3V4	45p	30P12	80p	EZ81	25p
2G306	30p	AD162	37p	MPP105	40p	3K4	45p	30P19	80p	GZ32	45p
2G308	30p	AF114	25p	NKT113	25p	5U4	45p	30PL1	70p	GZ34	60p
2G309	10p	AF115	17p	NKT114	15p	5Y4	45p	30PL13	85p	KT66	45p
2G371	25p	AF116	25p	NKT216	37p	5Y3	35p	30PL14	80p	KT88	21-75
2G374	27p	AF117	25p	NKT217	40p	5Z4G	40p	35L6	50p	MU14	60p
2G381	25p	AF118	65p	NKT224	25p	630L2	75p	35W4	30p	PABC80	40p
2N696	17p	AF119	25p	NKT241	27p	6AC7	25p	35Z4	30p	PC86	60p
2N697	17p	AF124	25p	NKT261	20p	6AG7	40p	35Z5	30p	PC88	60p
2N698	15p	AF126	17p	NKT271	25p	6AK5	30p	30B5	45p	PC97	45p
2N706	15p	AF127	17p	NKT272	25p	6AK6	45p	PC97C	45p	PC99	45p
2N708	15p	AF128	17p	NKT274	20p	6AL5	20p	80	50p	PC984	40p
2N914	22p	AF190	52p	NKT275	25p	6AM6	35p	85A2	40p	PC83	50p
2N916	25p	AF181	48p	NKT281	27p	6A86	37p	1825	50p	PCC88	50p
2N918	37p	AF186	40p	NKT403	75p	6AT6	30p	5763	70p	PCCR89	50p
2N929	25p	AF239	42p	NKT404	65p	6AU6	35p	6146	£1-50	PCCR80	34p
2N930	25p	AF240	42p	NKT405	65p	6AV6	35p	AZ31	50p	PCF82	34p
2N1131	30p	AY827	25p	NKT73	25p	6B6A	25p	V31	35p	DAF91	50p
2N1132	30p	AY828	25p	NKT10439	37p	6BE6	30p	DAF96	45p	PCF86	60p
2N1302	20p	AS217	45p	OA5	20p	6BH6	45p	DF91	25p	PCF800	50p
2N1303	20p	AU10	47p	OA10	25p	6BJ6	45p	DF96	45p	PCF802	50p
2N1304	25p	BA331	7p	OA47	10p	6BQ7A	45p	DK91	50p	PCF805	70p
2N1305	25p	BC107	12p	OA70	10p	6BR7	45p	DK92	50p	PCF806	70p
2N1306	25p	BC108	12p	OA79	10p	6BR8	45p	DL92	45p	PCF807	70p
2N1307	25p	BC109	12p	OA81	10p	6BW6	65p	DL94	45p	PCL82	35p
2N1308	25p	BC113	25p	OA85	18p	6BW7	70p	DL96	45p	PCL84	45p
2N1309	25p	BC116	40p	OA90	10p	6E26	35p	DL98	45p	PCL85	40p
2N1613	25p	BC125	55p	OA91	7p	6C4	31-10	DM70	35p	PL86	45p
2N1711	25p	BC128	55p	OA95	7p	6CD6	31-10	DM70	35p	PL87	45p
2N1889	25p	BC147	17p	OA200	70p	6CZ	45p	DY86	35p	PL88	45p
2N1893	25p	BC148	18p	OA202	10p	6C4W	45p	EY87	35p	PL89	45p
2N2147	75p	BC149	80p	OA210	17p	6F1	65p	EB8X3	65p	PL86	45p
2N2160	65p	BC167	18p	OC19	37p	6F6G	30p	E180F	95p	PL81	50p
2N2193	40p	BC172	17p	OC20	97p	6F13	38p	EABC80	35p	PL82	45p
2N2217	40p	BC177	18p	OC22	50p	6F14	65p	EAF42	35p	PL83	45p
2N2218	30p	BC182L	10p	OC23	60p	6F15	65p	EB81	20p	PL84	40p
2N2219	35p	BC184L	18p	OC24	60p	6F18	45p	EB81	20p	PL85	40p
2N2858	17p	BC185	25p	OC25	37p	6F23	30p	EBC41	80p	PL90	75p
2N2869	20p	BC212L	12p	OC26	25p	6H6	20p	EBP80	40p	PY32	50p
2N2869A	20p	BC30	25p	OC28	65p	6J4	50p	EBF83	35p	PY33	65p
2N2484	35p	BCY31	30p	OC29	65p	6J5	50p	EBF89	35p	PY80	25p
2N2613	35p	BCY32	30p	OC30	65p	6J6GT	65p	EEL21	60p	PY81	30p
2N2646	35p	BCY33	35p	OC31	65p	6J6	65p	EC88	60p	PY82	30p
2N2647	35p	BCY34	30p	OC41	25p	6L7	45p	EC88	60p	PY83	35p
2N2923	17p	BCY38	40p	OC42	30p	6K8G	30p	EC840	60p	PY80	50p
2N2924	17p	BCY42	15p	OC44	17p	6L6GT	45p	EC8C4	30p	PY80	50p
2N2925	17p	BCY43	30p	OC45	18p	6LD20	40p	EC8C5	60p	PY80	50p
2N2926	15p	BCY71	30p	OC46	27p	6Q7	40p	EC8C8	40p	U25	75p
2N2926Y	12p	BCY72	15p	OC70	15p	6BA7	40p	ECR80	35p	U26	75p
2N2926Y0	12p	BCZ11	15p	OC71	15p	6B7	45p	ECF82	35p	U30	35p
2N3055	35p	BD121	85p	OC72	25p	6B7J	25p	ECF86	65p	U32	35p
2N3054	50p	BD123	80p	OC73	30p	6B87	35p	ECF87	65p	U31	75p
2N3055	75p	BD124	80p	OC74	30p	6L7	35p	ECF85	60p	U281	40p
2N391A	20p	BF115	25p	OC75	25p	6B87	35p	ECH42	70p	U282	40p
2N3416	87p	BF117	47p	OC78	25p	6BQ7	40p	ECH81	30p	U801	40p
2N3470	£1-35	BF187	20p	OC77	40p	61	40p	ECH83	40p	U801	40p
2N3702	15p	BF189	20p	OC78	25p	6V6G	35p	ECL80	40p	UABC80	50p
2N3703	15p	BF180	37p	OC81	25p	6V6GT	35p	ECL82	35p	UAF42	50p
2N3704	17p	BF181	37p	OC81D	20p	6X4	65p	ECL83	65p	UAF42	50p
2N3705	15p	BF182	37p	OC83	25p	6X4G	65p	ECL86	40p	UC81	40p
2N3706	25p	BF184	25p	OC84	25p	6X4GT	27p	EF37A	60p	UBF80	35p
2N3707	15p	BF185	25p	OC139	25p	10C2	50p	EF89	40p	UBF89	35p
2N3708	17p	BF184	17p	OC140	37p	10F1	50p	EF40	45p	UC84	40p
2N3710	15p	BF193	15p	OC170	25p	10P13	50p	EF41	85p	UC85	40p
2N3711	15p	BF224	30p	OC171	30p	10P14	£1-10	EF42	70p	UC86	55p
2N3819	25p	BF225	30p	OC200	40p	12A7E	30p	EF50	25p	UC81	60p
2N3903	25p	BF244	47p	OC201	30p	12A7F	30p	EF85	35p	UC82	70p
2N3904	25p	BFX12	25p	OC202	75p	12A7G	30p	EF86	30p	UC81	35p
2N3905	25p	BFX13	30p	OC203	40p	12A7H	30p	EF89	25p	UC82	35p
2N4059	17p	BFX30	35p	OC204	40p	12A7J	30p	EF91	33p	UC83	40p
2N4059	25p	BFX30	35p	OC205	65p	12B6	35p	EF92	40p	UF41	60p
2N4059	25p	BFX44	37p	OC207	75p	12BH7	40p	EF183	30p	UF80	35p
2N4061	15p	BFX85	40p	OCPT1	97p	18A0Q	35p	EF184	35p	UF85	40p
2N4062	25p	BFX86	35p	ORP12	50p	20D1	45p	EL33	£1-25	UF89	35p
2N4286	15p	BFX87	35p	ORP90	40p	20F2	75p	EL34	50p	UL41	65p
2N4287	17p	BFY58	25p	P346A	25p	20L1	£1-10	EL41	55p	UL84	30p
2N4288	15p	BFY59	25p	PL4001	14p	20P1	50p	EL42	55p	UY41	45p
2N4289	17p	BFY20	65p	PL4002	15p	20P3	60p	EL51	55p	UY85	30p
2N4290	15p	BFY50	25p	PL4003	15p	20P4	60p	EL54	25p	VR105/30	35p
2N4291	15p	BFY61	20p	PL4004	17p	20P5	£1-30	EL85	45p	VR150/30	35p
2N4292	15p	BFY62	20p	PL4005	19p	25L6	45p	EL91	35p		
2N5354	27p	BFY90	67p	PL4006	30p						
2N5355	27p	BFY91	67p	PL4007	30p						
28102	25p	BSX30	17p	T1843	40p						
28103	25p	BSX31	17p	T1844	40p						
28104	25p	BSX76	17p	T1845	40p						
40250	50p	BSY26	17p	T1846	17p						
40381	55p	BSY27	30p								
40382	50p	BSY28	17p	BC107/8/9	25+						
AC107	37p	BSY38	20p	100+	10p						
AC128	37p	BSY39	20p	500+	7p						
AC127	25p	BSY31	35p	2N3055	50p						
AC128	25p	BSY36	50p	25+	65p						
AC154	15p	BSY56	90p	100+	50p						
AC176	25p	BSY6A	15p								

TELETON SPECIAL OFFER!

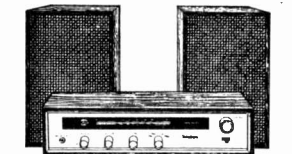

CR10 AM FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR 8A100S SPEAKER SYSTEMS
 Output 4 watts per channel. Excellent reception APC, built-in MPX, Cer/XTAL Input. Total List £50.25. OUR PRICE £29.95. Carr. 8 1/2p.

Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired. £45. Carr. £1.

RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES
5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0.2µsec to 100msec/cm. Supplied complete with all accessories and instructions, £87. Carr. paid.



MARCONI CT44/TF956 AF ABSORPTION WATTMETER

1 m/watt to 6 watts.
£80. Carr. £1.

TELL DECADE RESISTANCE ATTENUATOR

Variable range 0-11dB. Continuous. Unbalanced T and Bridge T. Impedance 600Ω range (0+dB × 10) + (1dB × 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz. (-3dB). Accuracy: 0-05dB. +Indication dB × 0.01. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new £27.50. P. & P. 25p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000Hz; Square 18-50,000Hz. Output max +10dB (10kΩ). Operation Internal batteries. Attractive two-tone case 7 1/2" × 6 1/2" × 2 1/2". Price £17.50. Carr. 17p.

BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1Hz to 100kHz. Square 20Hz to 20kHz. Output max. +10dB (10kΩ). Operation 220/240V a.c. Size 216mm × 160mm × 120mm. Price £27.50. Carr. 25p.

T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: -01 / -003 / -1 / -3 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. 4c/s-12c/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. £17.50. Carr. 25p.

TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms, 220/240V a.c. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional Probes available: R.F. £2.121. H.V. £2.50.

230 VOLT A.C. 50 CYCLES RELAYS

Brand New. 3 sets of changeover contacts at 5 amp rating, 50p each. P. & P. 10p (100 lots £40). Quantities available.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1/4 in. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms, 72p. P. & P. 7p.
50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, £1.06. P. & P. 7p.
100 WATT. 1 1/2/10/25/50/100/250/500/1,000 or 2,500 ohms, £1.87. P. & P. 7p.

ADVANCE TEST EQUIPMENT
Brand new and boxed in original sealed cartons.
VM 79. UHF MILLIVOLT METER. 100 Kcs to 1,000 Mc/s. a.c. 10 mV to 3V. D.C. 10 mV to 3V. Current 0.01 µA to 0.3 µA. Resistance 1 ohm to 10 megohm. £155.
TTL TRANSISTOR TESTER. Full range of facilities for testing PNP or NPN transistors in or out of circuit. £37.50. Carriage 50p per item.

MULTIMETERS for EVERY purpose!

TECH PT-34, 1,000 O.P.V. 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA. d.c. 0/100K. £1.97. P. & P. 12p.

MODEL TE-900, 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50µA/250mA. 0/60K/6 meg. £3.75. P. & P. 15p.

MODEL 500, 30,000 O.P.V. with overload protection, mirror scale 0/5/12.5/10/25/100/250/500/1,000V d.c. 0/2.5/10/25/100/250/500/1,000V a.c. 0/60K/6 Meg. 0/60K/6 Meg. 0/60K/6 Meg. £3.87. Post paid.

MODEL TE-70, 30,000 O.P.V. 0/3/15/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30µA/3/30/300mA. 0/16K/160K/1.6M/16 meg. £5.50. P. & P. 15p.

TMK MODEL TW-50K, 45 ranges, mirror scale. 50K Volt d.c. 5K/Volt a.c. D.c. volts: 0-125, 0-25; 1-25, 2-5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. volts: 1-5, 3, 5, 10, 25, 50, 100, 250, 500, 1,000V. D.c. current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 10K, 100K, 1 meg, 10 meg. Decibels: -20 to +81.3dB. £3.87. P. & P. 17p.

TE-900 20,000 VOLT GIANT MULTIMETER. Mirror scale and overload protection. 8in full view mirror. 2 colour scale. 0/2.5/10/250/1,000/5,000V a.c. 0/25/12.5/10/50/250/1,000/5,000V d.c. 0/150µA/1/10/100/500mA/10A d.c. 0.2K/200K/20 meg. ohm. £15. P. & P. 25p.

MODEL 5025, 57 ranges, giant 5 1/2in meter, polarity reverse switch. Sensitivity: 50K/Volt d.c. 5K/Volt a.c. D.c. Volts: 0-125, 0-25, 1-25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. Volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 2K, 10K, 100K, 1 meg, 10 meg. Decibels: -20 to +85dB. £12.50. P. & P. 17p.

MODEL TR1, 20,000 O.P.V. 0/0.6/30/120/600/1,200/3,000/6,000V d.c. 1/6/30/120/600/1,200V a.c. 0/60µA/6/60/600mA. 0/6K/60K/6 meg/60. Megohm 50PF. 2 MPD £5.97. P. & P. 17p.

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and IC0 npn or pnp. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £6.97. P. & P. 15p.

HOMOR TE.10A, 20kΩ/Volt 5/25/50/250/500/2,500V d.c. 10/80/100/500/1,000V a.c. 0/50µA/2-5mA 250mA d.c. 0/6K/6 meg. ohm. -20 to +22dB. 10-0, 100 mfd. 0-100-0-1 mfd. £3.47. P. & P. 15p.

MODEL TE-300, 30,000 O.P.V. Mirror scale, overload protection 0/0.6/3/15/60/300/1,200V d.c. 0/8/30/120/600/1,200V a.c. 0/30µA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. -20 to +63dB. £5.97. P. & P. 15p.

MODEL TE 80, 20,000 O.P.V. 0/10/50/100/500/1,000V. a.c. 0/5/25/50/250/500/1,000V d.c. 0-5µA. 5/50/500mA/0/4K/60K/600K/6 Meg. £6.87. P. & P. 15p.

MODEL TE-90, 50,000 O.P.V. Mirror scale, overload protection. 003/130/300/600/1,200V d.c. 0/6/30/120/300/1,200V a.c. 0-03/6/60/600mA. d.c. 18K/160K/1.6/16 meg. -20 to +63dB. £7.50. P. & P. 15p.

TMK MODEL TW-200C. Features Resettable Overload Button. Sensitivity: 20KΩ/Volt d.c. 5KΩ/Volt a.c. D.c. volts: 0-5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 0-2.5, 10, 50, 250, 1,000V. D.c. currents: 0-0.05, 0-5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K, 5 meg. Decibels: -20 to +62dB. £11.50. P. & P. 17p.

MODEL AS-100D, 100KΩ/Volt. 5in, mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200V d.c. 0/8/30/120/300/600V a.c. 0/10µA/6/60/300mA/12A. 0/2K/200K/2M/200M. -20 to +17dB. £12.50. P. & P. 17p.

TMK L TESTER. 100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 OPV d.c. 5V/Volt a.c. D.c. volts: 0.5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 2, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100µA, 10, 100, 500mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 1 meg, 10 meg. Decibels: -10 to +49dB. Plastic case with carrying handle, size 7 1/2" × 6 1/2" × 3 1/2". £18.90. P. & P. 25p.

SKYWOOD SW-500

50 KΩ/Volt. Mirror scale DC Volts 0.6/3/12/30/300/600. AC Volts 3/30/300/600. DC Current 20µA/6/60/600mA. Resistance 100K/100K. £7.50. P. & P. 15p.

270° WIDE ANGLE

1mA METERS
MW1-6 60mm square £3.97. MW1-8 80mm square £4.97. P. & P. extra.




UNR-30 RECEIVER
4 Bands covering 55KHz-30MHz. B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £15.75. Carr. 37p.


WSE TRANSCEIVERS
Large quantity available for EXPORT! Excellent condition. Enquiries invited.



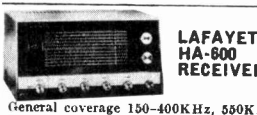UR-LA SOLID STATE COMMUNICATION RECEIVER
4 Bands covering 55KHz-30MHz. FET, S Meter, Variable BFO for SSB. Built in Speaker, Bandspread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2" × 4 1/2" × 7 1/2". Brand new with instructions. £25. Carr. 37p.



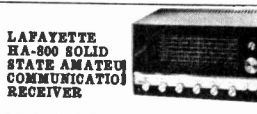LAFAYETTE HA-600 RECEIVER
(General coverage 150-400KHz, 550KHz-30MHz. FET front end, 3 mech. filters, product detector, variable B.F.O., noise limiter, S Meter, Bandspread, RF Gain. 15 1/2" × 9 1/2" × 8 1/2". 220/240V a.c. or 12V d.c. Brand new with instructions. £45. Carr. 50p.



LAFAYETTE HA-600 SOLID STATE AMATEUR COMMUNICATION RECEIVER
3-5-4, 7-7-3, 14-14-35, 21-21-45, 28-29-7, 50-54MHz. Dual conversion, 2 mech. filters, product detector, variable BFO, S Meter, 100KHz calibrator. 220/240V a.c. or 12V d.c. 15 1/2" × 9 1/2" × 8 1/2". Brand new with instructions. £57.50. Carr. paid (100KHz Crystal £1.97; extra).

FULL RANGE OF TRIO EQUIPMENT

EDDYSTONE VHF RECEIVERS MODEL 770E, 19-165 Mc/s. Excellent condition. £150.

VOLTAGE STABILISER TRANSFORMERS
180-260V input. Output 230V. Available 150V or 225V. £12.50. Carr. 25p.

AUTO TRANSFORMERS
0/115/230V. Step up or step down. Fully shrouded.
150W. £2.37. P. & P. 17p.
300W. £3.25. P. & P. 22p.
500W. £4.97. P. & P. 32p.
1,000W. £7.25. P. & P. 37p.
1,500W. £8.97. P. & P. 42p.

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 230/240V a.c. Output continuously variable from 20V to 230V.
Model MR2305 5A 68 × 46 × 43mm, £3.37. Model MR2310 10A 90 × 68 × 46mm, £11.97. Postage 12p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

MODEL S-260 General Purpose Bench Mounting	MODEL S-260 B Panel Mounting
1A	1A
2.5A	2.5A
5A	5A
10A	10A
12A	12A
20A	20A

INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS
Special discounts for quantity

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W1 Tel: 01-636 3715
3 Lisle Street, London, W.C.2 Tel: 01-437 8204
34 Lisle Street, London, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to -
11-12, Paddington Green,
London, W.2
Tel: 01-262 6562
(Trade supplied)

COMPLETE STEREO SYSTEM

FOR ONLY

£40.95

CARRIAGE £1.75



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends. Size 12 x 5½ x 3½in. high (Amplifier available separately if required £14.95, Carr. 40p).

PREMIER STEREO SYSTEM "TWO"

As system "ONE" above but with Garrard SP25.

PREMIER PRICE £47 Carr. £1.75


MIDLAND AM/FM STEREO TUNER AMPLIFIERS

Two new all solid state receivers from Midland at economical prices. Beautifully styled in slimline cabinets

	Model 19-520	Model 19-542
Specifications	19 transistors, 12 diodes, 2 variators	22 transistors, 12 diodes
Tuning range	FM 88-108 MHz AM 635-1635 kHz	FM 88-108 MHz FM Stereo Multiplex AM 635-1605 kHz
Aerial	Internal AM and external FM	Internal AM and external FM
Frequency Response	50-17,000 Hz	35-20,000 Hz
Power Output	2½ watts rms per channel (8 watts music power)	4 watts rms per channel (18 watts music power)
Inputs	Ceramic phono	Magnetic/Ceramic phono and aux.
Speaker impedance	4-8 ohm	8 ohm
Controls	Power on/off, Volume, tone, balance, tuning, AFC, Stereo indicator	On/off, Volume, bass, treble, balance, tuning, AFC, Stereo indicator
Function	AM, FM, FM Stereo, Phono (Stereo indicator light)	AM, FM, FM Stereo, Ceramic, Magnetic, Aux.
Size	15" x 8" x 3½"	16½" x 9½" x 3½"
PRICE	£30.45 Carr. & Ins. 50p	£44 Carr. & Ins. 50p



MODEL 19-520

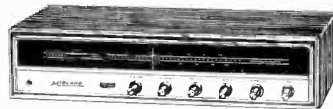


MODEL 19-542

PREMIER STEREO SYSTEM "SIX" SAVE OVER £16

Comprises Midland AM/FM Stereo Tuner Amplifier Model 19-542. Pair of loudspeaker systems as System "ONE". Garrard SP25 Mk. III fitted Goldring Q850 Stereo Cartridge with teak plinth and cover. Total rec. list price over £91.

PREMIER PRICE £75 Carr. & Ins. £1.75

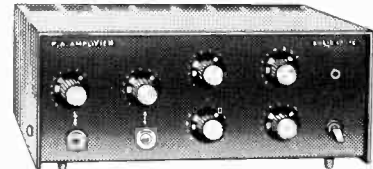50 WATT PUBLIC ADDRESS AMPLIFIER MODEL PA-5000



A top quality amplifier giving 50 watts rms power output (80W peak). Incorporates 8 transistors and 4 silicon diodes (silicon output transistors). Inputs for 2 microphones each with individual volume controls, plus phono/aux. input. Master volume control and Bass and Treble Controls. Well presented front panel for ease of operation, on/off power flick switch and pilot light. Output impedance 4/8/16 ohms Mike 1 and 2 sensitivity 2mV (50kΩ) Phono/Aux 300mV (100kΩ). Frequency response 50-20,000Hz. Fused output and thermal overload protection. A.C. Mains 220-250V, 50/60Hz. Size 13½in x 9in x 3in.

PREMIER PRICE £39 P. & P. 50p

E.M.I. 13x8in. HI-FI SPEAKERS



Fitted two 2½in tweeters and crossover network. Available with 8 or 16 ohm impedance. Handling capacity 10W. Brand new.

£3.47 P. & P. 40p



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.

£2.47 P. & P. 25p

STEREO STETHOSCOPE SET Low imp. £1.25. P. & P. 10p
MONO STETHOSCOPE SET Low imp. 52p. P. & P. 10p

PREMIER EXCLUSIVE!

MIDLAND CASSETTE TAPE RECORDER 12-112



Solid state incorporating Automatic Level Control for trouble-free 2-track recording. Inputs for mike and aux. Earphone socket. Complete with batteries and earpiece. Size 10½in x 5½in x 2½in.

PREMIER PRICE £16.50 P. & P. 40p

POCKET SIZE MULTI-TESTER With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 18 Ranges: 0-5-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-50µA-25µA-250µA D.C. 0-6000 ohms-6 megohms, 10µ mf-0.001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions.

£4.90 P. & P. 17p

SP25 Mk III SPECIAL!



Garrard SP25 Mk. III Single Record Player. Fitted Goldring Q850 Magnetic Stereo Cartridge. Complete in Teak Plinth with Rigid Perspex Cover.

Total list price over £29.
PREMIER PRICE £19.90
P. & P. 50p.



TAPE CASSETTES

C60 (60 min.) 37p 3 for £1.05
C90 (90 min.) 62p 3 for £1.80
C120 (120 min.) 87p 3 for £2.55
P. & P. 5p

All cassettes can be supplied with library cases at 3p extra each.



"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped - attractively boxed.

LPS 3' 250' P.V.C.	28p	LPS 6 1/2' 1200' P.V.C.	62p
ITS 3 1/2' 450' POLYESTER	37p	ITS 6 1/2' 1800' POLYESTER	£1.12
DT3 3 1/2' 600' POLYESTER	57p	DT6 6 1/2' 2400' POLYESTER	£1.87
SP5 5' 600' P.V.C.	42p	SP7 7' 1200' P.V.C.	62p
LP5 5' 900' P.V.C.	50p	LP7 7' 1800' P.V.C.	75p
DT5 5' 1200' POLYESTER	75p	DT7 7' 2400' POLYESTER	£1.25
		TT7 7' 3600' POLYESTER	£2.50

TAPE SPOOLS 3' 5p, 5', 5½', 7' 8p.
Post and Packing 3' 6p, 5', 5½', 7' 10p. (3 reels and over Post Free.)

PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES
Advertisement Manager D. W. B. TILLEARD

SPECIALISED COMPONENTS

THE private constructor needs more ready and direct access to certain types of components, apart from those general purpose parts and semiconductor devices which we must agree are not at all difficult to obtain. But in order to exploit these latter devices fully, it is sometimes necessary to obtain certain special items. Maybe a special kind of semiconductor; some unusual passive component like perhaps a ferrite pot core; or an electro-mechanical part such as an uncommon type of switch, connector, or relay. By "special" we mean an item not normally carried in stock by the average retailer, but listed in a manufacturer's "industrial" or "professional" catalogue. In effect, this usually means that this particular class of component or device is restricted to equipment makers and component distributors, who can order in the requisite large quantity demanded by the manufacturer.

Industrial component distributors by and large are not favourably disposed towards dealings with private individuals. Some will, it is true, supply direct, but they have to insist on a certain minimum order—either in quantity or value. Such a procedure works well enough for the particularly dedicated and prolific constructor who makes a point of finding his way through the distribution network, and has probably established good personal relations with one or more distributors. But countless other constructors would like the opportunity to gain access to a wider range of components, on perhaps less frequent occasions, but without the inconvenience of hunting around for an obliging distributor for each particular special need.

Retail component stockists are the natural source of supply for individual constructors. Through the mail order business many retail firms have established good links with the amateur, wherever he may live. The point has now arisen whether retailers could not improve and expand their service by stocking a more varied range of electronic components including some special items obtainable from the industrial distributors; or at any rate, be prepared to order such special items upon request.

In *Readout* this month we publish two letters relating to this subject, but from different aspects. Firstly, one of our contributors appeals to component manufacturers and trade distributors to consider the needs of amateurs, and also suggests how the latter may further their own cause. Secondly, one of our advertisers offers fellow retailers membership of a co-operative scheme for purchasing special components in reasonable quantities from manufacturers or main distributors. We await with interest any comments on this topic from industry, trade, or individual readers.

F.E.B.

THIS MONTH

CONSTRUCTIONAL PROJECTS

FISH BITE ALARM	382
DIGITAL I.C. TESTER	386
P.E. AURORA	400
WINDSCREEN WASHER TIMER	417

SPECIAL SERIES

MAKING THE MOST OF LOGIC IC's—II	378
-------------------------------------	-----

GENERAL FEATURES

TREMULANT SYSTEMS	372
INGENUITY UNLIMITED	410

BEGINNERS

VOICE OPERATED SWITCH	398
-----------------------	-----

NEWS AND COMMENT

EDITORIAL	371
NEWS BRIEFS	384, 406
SPACEWATCH	409
ON THE FRINGE	413
MARKET PLACE	414
BOOK REVIEWS	421
POINTS ARISING	422
READOUT	425

*Our June issue will be published on
Friday, May 14*

© IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.65 (£2 13s. 0d).

Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202

TREMULANT SYSTEMS

BY F. C. JUBBER

PART ONE ELECTRO-MECHANICAL

THE popularity of electrically amplified and electronic musical instruments such as the electronic organ has resulted in the invention of all kinds of tremulant and vibrato systems as well as a host of other effects such as artificial echo, reverberation and the so called phasing or skying effect.

No effect has ever been produced that enhances musical sound so well as tremulant, which has been used ever since musical instruments, that could be made to produce it, were invented and even longer by anyone able to sing or whistle a musical phrase.

DEFINITIONS

There is some confusion between the terms tremulant, tremolo and vibrato which are defined by music encyclopædias as follows: *Tremulant* generally refers to the effect of making a note rapidly softer or louder i.e., a rapid amplitude variation. *Vibrato* is the effect of altering the pitch of a note rapidly by a very small degree i.e., it is a rapid frequency variation. Some may choose to differ on these definitions but for the sake of clarity, tremulant and vibrato will be used accordingly for the purpose of this article. *Tremolo* normally indicates the rapid repetition of one or more notes.

APPLICATION

The vibrato effect, or rapid pitch fluctuation, is normally produced on instruments like the violin and guitar by the player. The effect can be produced

electronically on instruments with electronic tone generators i.e., electronic organs, in which case a low frequency (5 to 10Hz) sine wave is employed to produce a small variation in the tuning of the tone generators. The tremulant effect can also be produced on certain non-electronic musical instruments by making the sound rapidly softer or louder, depending on the nature and playing technique of the instrument. With electronic organs and any amplified instrument like the guitar, a tremulant can be introduced by rapidly altering the gain of one stage of the amplifier. This is generally accomplished by employing a low frequency sine wave as a voltage control e.g., to control the bias voltage of a valve or transistor.

L.D.R. CONTROL

On most guitar amplifiers this facility is usually wrongly called vibrato and bias control of this kind generally introduces an obnoxious thumping noise, due to harmonics from the low frequency control oscillator. A far better method is to use a light dependent resistor (l.d.r.) as shown in Fig. 1. The lamp is connected in the collector circuit of a voltage level detector, which is driven by a low frequency sine wave oscillator. The sinusoidal fluctuation of light produces a sinusoidal variation in the resistance of the l.d.r.; this method is free from thump.

A novel idea for a tremulant pre-amplifier employing l.d.r.'s, which can be used for portable electronic organs or guitars, will be given in part 2.

The Leslie rotary horn loudspeaker as fitted to many modern electronic organs


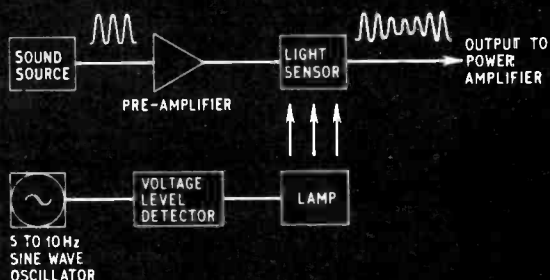


Fig. 1. Block diagram showing method of employing an l.d.r. to obtain tremulant from an amplifier

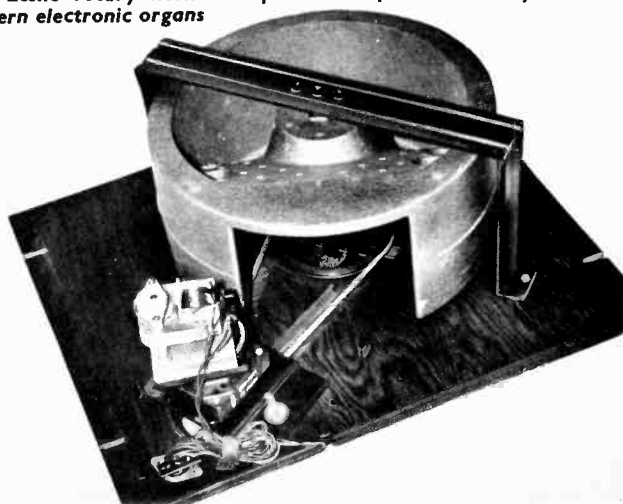

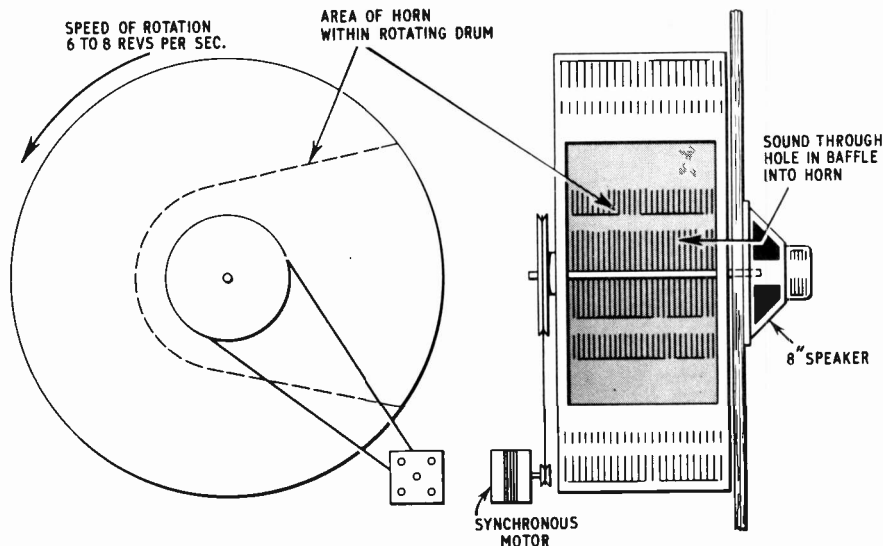


Fig. 2. Mechanical arrangement of rotating horn loudspeaker

ELECTRO-MECHANICAL SYSTEMS

There are several electro-mechanical methods of producing a pleasing tremulant from electronic organs and amplified electric guitars. These employ either rotating loudspeakers or rotating horns or deflectors and many of the systems currently in use are due to Don Leslie and bear his name.

Some manufacturers and users of rotating horn and deflector systems are, however, wrongly under the impression that pitch variation is produced by these devices because of the Doppler effect. Tests made by the author have disproved this, but have shown that the tremulant waveform from such systems is a very complex one. Systems in which the loudspeakers themselves are rotated do produce the Doppler effect as in this case the sound source itself is moving.

VARIATIONS IN MECHANICAL SYSTEMS

The exact acoustical function of rotary horn or loudspeaker tremulant systems will be dealt with in part 2; meanwhile it may be worth examining the various designs currently in use. The most common type employed in smaller electronic organs is the Leslie rotating horn system (see photograph). As can be seen from Fig. 2, the loudspeaker is fixed on a baffle board but "looks" into the rotating horn. These units are installed so that the sound can only come out of the revolving horn. The acoustical nature of the tremulant is mainly one of amplitude fluctuation of the fundamental notes but with considerable variation of their harmonic structure.

Another method, based on the rotating horn system, is one using a rotating deflector as shown in Fig. 3, this is generally used with large loudspeakers. This arrangement is sometimes used in conjunction with the small twin rotating horn system shown in Fig. 4, both assemblies being used together in external tone cabinets with built-in amplifiers and frequency crossover networks (Leslie organ tone cabinets). The small twin horn system shown in Fig. 4 rotates above the sound transducer the sound following the path shown by the arrows.

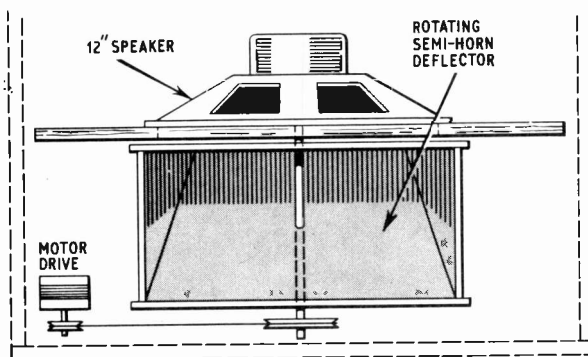


Fig. 3. The rotating deflector system used in Leslie tone cabinets

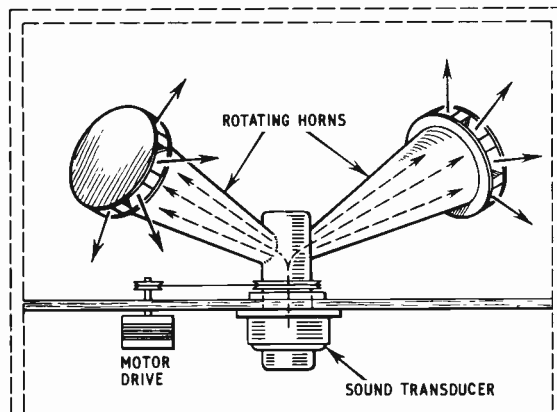


Fig. 4. Rotating twin horn system used in Leslie tone cabinets

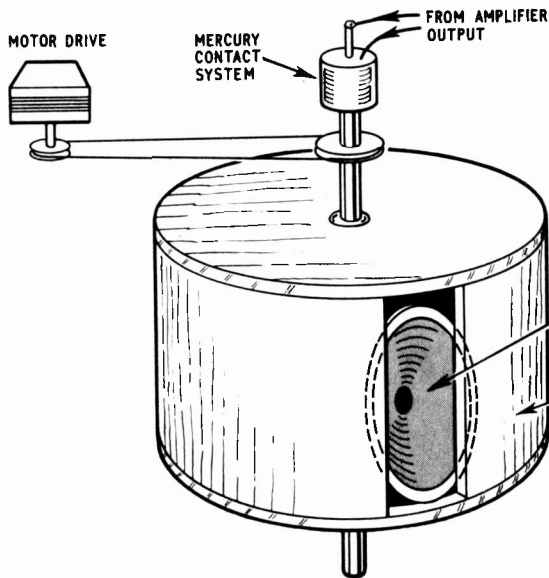


Fig. 5. The rotating speaker drum

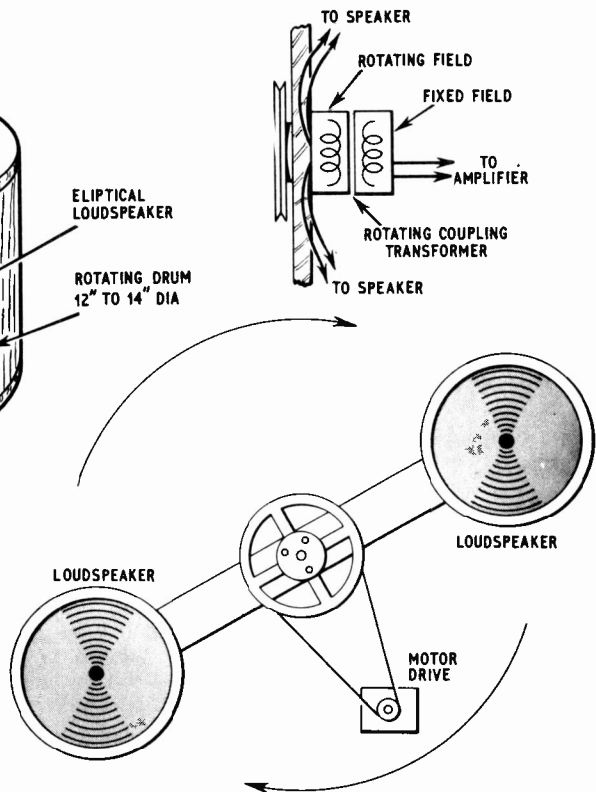


Fig. 6. Rotating twin loudspeaker system

Rotary horn or speaker systems are driven by a synchronous motor with a belt drive and a pulley diameter ratio suitable for turning the system at between five and ten revolutions per second; the usual speed is seven revolutions per second. Sometimes an additional motor or an alternative pulley ratio is used so that the system can be run at about one revolution per second to produce what is known as the "Celeste" effect (slow Leslie) which audibly, is a slow undulation not unlike the slow, rise and fall in level heard from an organ in a large church.

ROTATING SPEAKER

Systems in which the loudspeakers themselves rotate present the problem of electrically coupling the speaker to the amplifier. Slip rings and contacts have been found unsatisfactory because of the low impedance so, as in the example shown in Fig. 5, a mercury contact system is used. The loudspeaker itself is a small elliptical type mounted in a rotating drum. In addition to complex amplitude variation, this system produces a small amount of pitch fluctuation due to Doppler effect.

The arrangement shown in Fig. 6 is used in various ways. In small electronic organs two speakers, normally not larger than eight inches in diameter are mounted one at each end of a rotating arm about 18 to 20 inches across. A special rotating coupling transformer, or mercury contact system, is

used to connect the speakers to the amplifier. The system produces pitch variation due to Doppler effect but as with all rotating speaker systems this tends to be masked by the large amplitude fluctuations that are produced.

A variation of this system is also used in large tone cabinets for Church organs to produce the "Celeste" effect in which case four or more loudspeakers are made to rotate slowly on a radius of approximately 24 inches; the speakers themselves are spaced about four feet apart.

A ROTARY TREMULANT SYSTEM

In order to analyse the tremulant effect produced by a rotating horn system, the model shown in the photographs was constructed to the dimensions given in Figs. 7 and 8. A system of this kind can be used with any electronic organ or a guitar amplifier. As the photograph shows the completed assembly (without external covering) consists of the main baffle board on which is mounted an eight inch loudspeaker, the rotating horn drum and its synchronous drive motor and the framework forming the enclosure. The unit is finally covered with an open weave fabric.

Padding is used between the rear of the loudspeaker baffle and the hardboard back of the cabinet to prevent sound coming from the rear of the speaker. All the sound must therefore radiate, via

the rotating horn, through 360 degrees on a vertical plane around it, hence the reason for covering the enclosure with open weave fabric.

ROTATING HORN

The rotating horn drum is not as difficult to make as it might at first appear. Accuracy is important, however, as the drum must rotate smoothly and almost silently at six to seven revolutions per second. Any mis-alignment of the bearings or distortion in the drum itself will cause vibration and noise.

The drum is constructed from $\frac{1}{8}$ inch thick hardboard to the dimensions given in Fig. 7. First the two discs are cut to 15 inches diameter, one with a centre hole approximately $6\frac{1}{4}$ inches in diameter. The main bearing supports (C)—one on each drum—could be cut from seven inch diameter discs of aluminium, but large holes must be cut in the one fitted on the loudspeaker side. A Ferrograph metal tape spool which comes apart quite easily, thus providing two accurately and ready made supports, was used in the prototype. The actual bearings (A, Fig 8) for the drum were $\frac{3}{8}$ inch bushes with $\frac{1}{4}$ inch holes, extracted from old potentiometers. These are inserted through the spool cheeks.

DRUM WALL

The drum wall is best made by first cutting a piece of hardboard six inches wide and approximately 45 inches long. This must be gradually rolled up, loosely at first, until the roll is finally down to around 12 inches in diameter. Heat will help, but the rolling up must be done in stages, allowing the hardboard to settle for a while by tying a piece of string around it. When it is down to a small roll, leave it tied up, at least over night. It should then remain rolled to approximately the right diameter for the drum faces. Next cut the material so that the ends coincide with the $8\frac{1}{2}$ inch wide mouth of the horn as shown in Fig. 7.

HORN WALL

The horn wall is made from thin plywood, or thick cardboard, rolled carefully to prevent it cracking. This is glued to one face of the drum with impact adhesive and also secured with small wood blocks, glued around the outside as shown. The ends of the horn must also be glued to the ends of the drum wall. The space between the drum wall and the horn wall can be filled with soft loosely packed paper or foam rubber.

The remaining side of the drum is then glued in position and the two straps (E) glued and screwed in place as shown in Figs 7 and 8. Note that the bearing plates (C) and bearings must be fitted before the drum itself is put together. The pulley should be approximately $3\frac{1}{2}$ inches in diameter and fitted so as to stand off the face of the drum by approximately $\frac{1}{2}$ inch as in Fig. 8. It is most important that the drum and its pulley are perfectly aligned and that there is no eccentricity. It might be mentioned here that for the construction of the horn drum and its fittings the usual range of hand tools, plus power drill will be adequate and that the drum and its frame were completed and assembled in a weekend.

FINAL ASSEMBLY

The final stage of assembly is that of the speaker baffle and the drum supporting frame as shown in


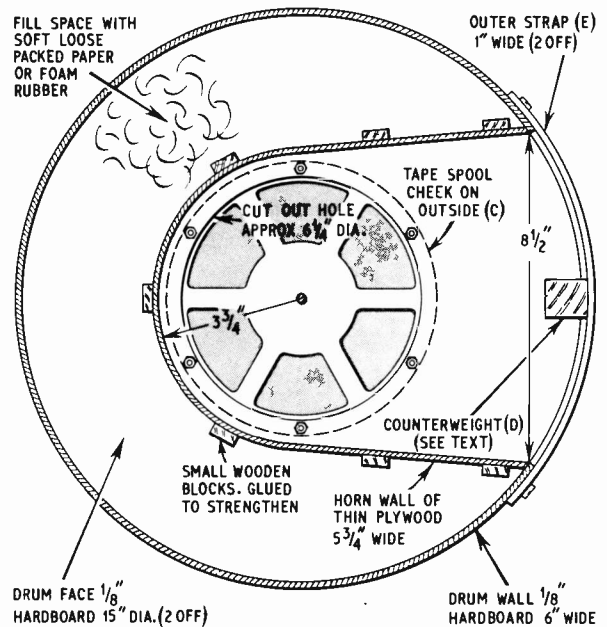


Fig. 7. Construction of the rotating horn drum. This drawing shows the drum with one side removed

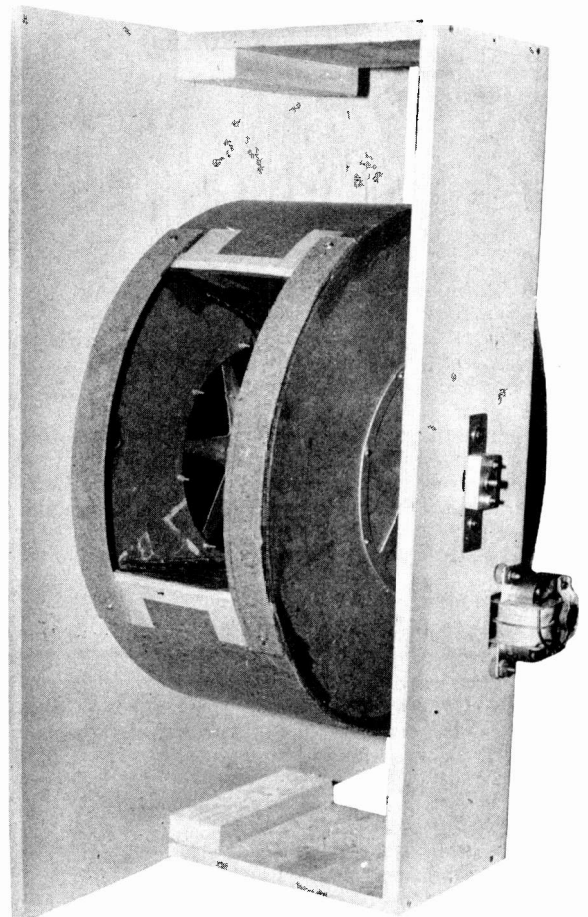

The completed rotary horn and drive system mounted in its supporting frame

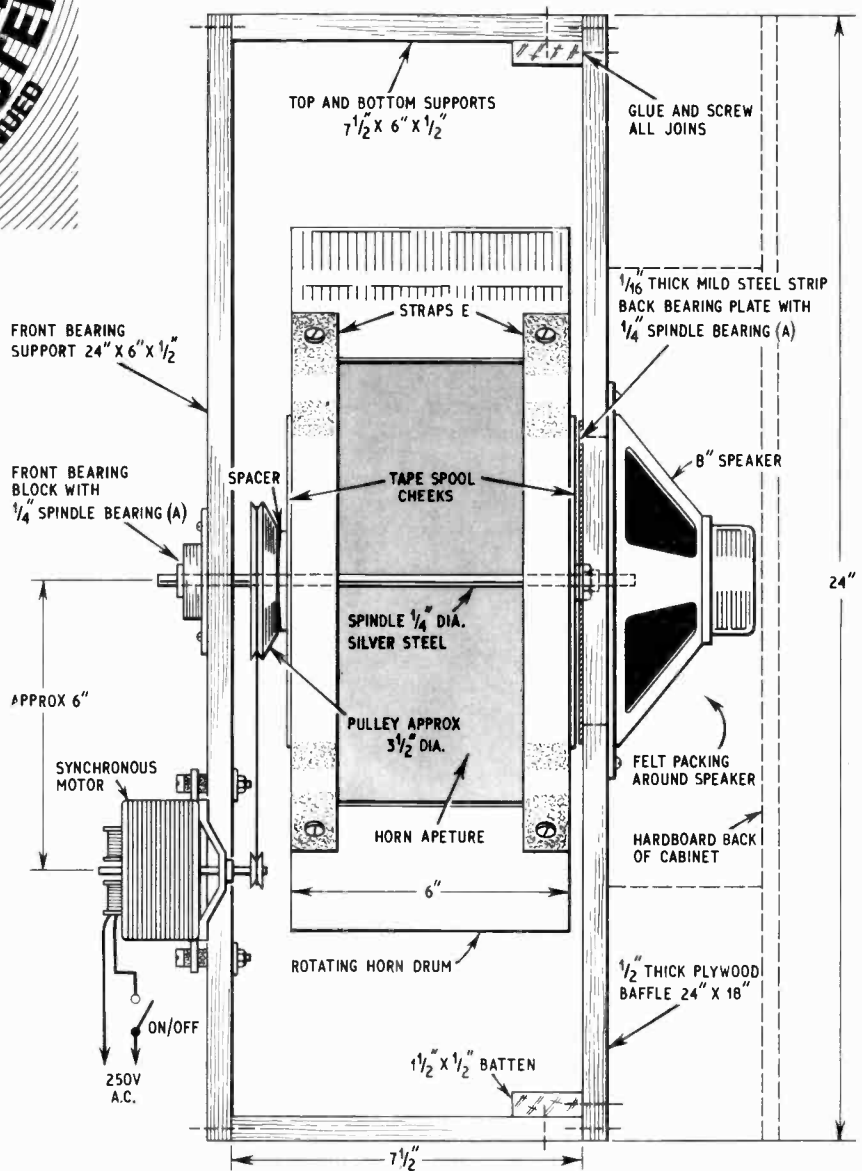


Fig. 8. Completed assembly of rotary horn system in its supporting frame with the drive motor fitted

MATERIALS . . .

(For the construction detailed in this part only)
 Hardboard 1/4 in thick—15 in x 15 in (2 off)
 45 in x 6 in
 11 in x 1 in (2 off)
 Plywood 1/2 in thick—24 in x 18 in
 24 in x 6 in
 7 1/2 in x 6 in (2 off)
 Thin plywood or stout card 27 in x 5 1/2 in
 Hardwood 6 in x 1 1/2 in x 1/2 in (2 off)
 Small hardwood blocks
 Ferrograph tape spool, 7 in diameter metal type


Silver steel rod 1/4 in diameter x 7 1/2 in
 Brass or steel, approx 1 in x 1 in x 1/4 in (2 off), 8 in x 1 in x 1/4 in and 4 in x 1 in x 1/4 in
 Pulley 3 1/2 in diam. and spacer to suit (see Fig. 8)
 Bushes 1/4 in internal diameter (4 off)
 Synchronous mains motor with small pulley (see text)
 Loudspeaker 8 in diameter with impedance and handling capability to suit amplifier used
 Rubber belt
 Screws, glue, 4BA fixings and grommets

Fig. 8. Note the position of the back bearing plate, with a $\frac{1}{4}$ inch bush ($\frac{1}{4}$ inch internal hole) across the speaker opening. The front bearing block on the vertical support comprises a metal plate approximately 4 inches \times 1 inch with a bush (from an old potentiometer) to take the $\frac{1}{4}$ inch diameter spindle that goes right through the drum.

The drive motor may be almost any synchronous tape recorder drive motor, mounted as shown in Fig. 8 on rubber bushes (grommets will do). The diameter of the small drive pulley on the motor may require some thought and experiment, but will normally be $\frac{1}{8}$ to $\frac{1}{2}$ an inch in diameter. A rubber belt of suitable length is used for coupling the motor to the drum pulley.

When the whole assembly (except the speaker) has been completed as shown in Fig. 8, make absolutely sure that it turns freely and accurately. Without the counterweights (shown in Fig. 7) it should revolve freely if pushed and come to rest with the horn mouth uppermost. The counterweights are fitted one each side under the straps E and consist of a small square of brass or mild steel, glued securely in place. When these are fitted, check that the balance is correct, in which case the drum should come to rest at any random point. Under power, the drum will reach speed slowly but should continue to revolve smoothly and quietly. Although a small amount of vibration may be set up in the frame, this should disappear almost completely when the unit is finally secured within the framework of the enclosure.

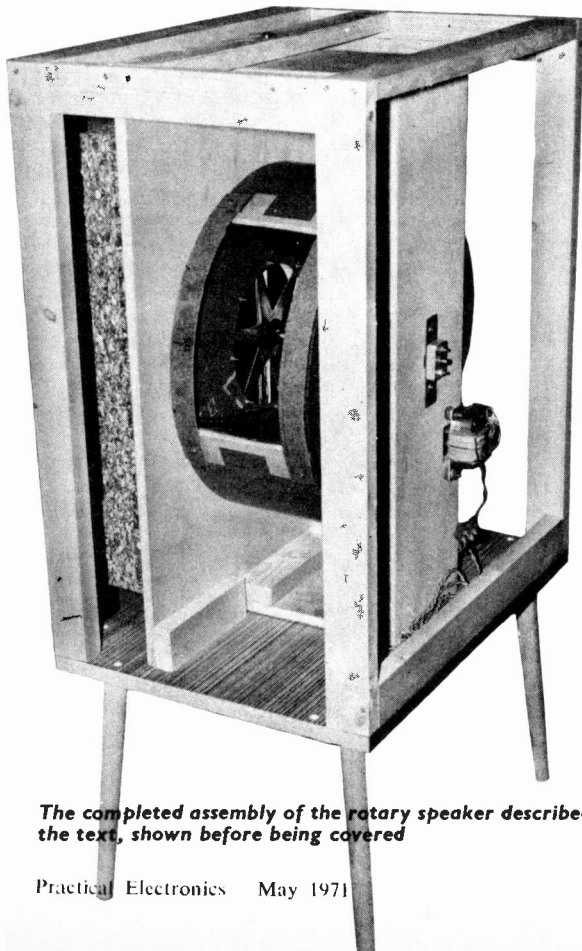Next month: the construction of the enclosure frame, and electronic simulation of rotary speaker tremulant systems.




The completed assembly of the rotary speaker described in the text, shown before being covered

JUNE BUG?

...XEE

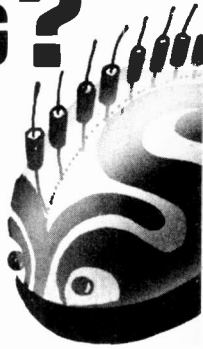Xee utilises DTL integrated circuits in a compact "body" to provide some of the functions of the more simple animal life. Incorporating both tactile and light sensing, this project is not only extremely interesting to build, but also demonstrates a novel way of using electronic circuitry to simulate animal tendencies.



WIND DIRECTION INDICATOR

A reasonably simple project for general interest and weather recording. Using the minimum of components this instrument gives remote indication of wind direction by means of lamps representing eight points of the compass.

AUTOMATIC BATTERY CHARGER

Automatic control of a battery charger is desirable for protection of the battery against over charging and for constantly maintaining a fully charged battery. This article describes the operation and construction of an automatic charger that can supply up to 5 amps; and also the construction of an add-on unit that can automate any standard battery charger.

FIRST OF A NEW SERIES . . .

RADIO ASTRONOMY TECHNIQUES

which will include some worthwhile investigations for amateur workers, and details of the equipment needed for a back-garden radiotelescope.

All in the June issue of

**PRACTICAL
ELECTRONICS**

ON SALE MAY 14

MAKING THE MOST

OF LOGIC IC'S

PART ELEVEN—By R. W. COLES

EMITTER COUPLED LOGIC— Concluding Article

HIGH SPEED LOGIC, HSL, is the last family of integrated circuits to be discussed in this series. The name is a very general one to allow for the fact that there are really two sub-families which use very different circuitry to achieve the same goal of very short propagation times, and thus high operating speeds.

This type of logic is, of course, mainly intended for use in computers and other high speed data handling equipment, where its application allows simple operations (addition for example) to be carried out in less time than would be necessary if, say, RTL were employed to carry them out. Looking at this from a different viewpoint, HSL enables one to build a computer which will carry out more complicated tasks in a realistic time than could be carried out by its predecessors.

Some new areas which are now being exploited by computers which possess this super-speed capability are: the reading of written characters which are not in a special "stylised" font, including signature recognition; the control and real-time analysis of airborne "terrain" radar information, and the ability of "general purpose" computers to handle several jobs or programmes simultaneously.

APPLICATION AREAS

While it is true that computer requirements lead to the development of high speed logic, and will eventually be responsible for the lowering of its price by virtue of the huge volume of devices which will be employed in these machines, it is also true that small quantities of HSL will be found very useful in application areas that are economically within the amateur's reach.

How about an f.m. tuner which is set to the desired channel by a crystal controlled frequency synthesiser with just one crystal? Or a digital frequency counter

which will display directly the frequency of a signal as high as 300MHz? These circuits and many others will become feasible when HSL is used.

SUB-FAMILIES

One technique for increasing the operating speed of digital circuits is that of "current-steering" and this solution to the speed problem was used even before it became available in integrated form, where it now reigns supreme. The basic gate is quite simple in conception and utilises a "longtail pair" as a current switch.

The other solution, which has only recently been introduced, uses a specially modified TTL circuit which includes Shottky barrier diodes as anti-saturation clamps. This last solution is a very exciting development because unlike the current-steering circuits the devices are directly compatible with slower saturated logic forms like DTL and TTL, whose power requirements they share.

CURRENT STEERING LOGIC

This family has many names, and apart from CSL it is also referred to as CML (current mode logic), EECL or E²CL (emitter-emitter coupled logic) and, most popular of all, ECL (emitter coupled logic). The basic ECL gate is shown in Fig. 11.1.

Excellent high speed performance is assured by using a differential amplifier (longtail pair) in which the component transistors do not enter saturation during operation, eliminating transistor storage time prevalent in TTL, DTL and the other saturating logic families. Emitter followers are used as output drivers to provide a high current drive which is capable of a fan-out of 15 ECL gate input loads.

An unusual feature is the provision of both a true and a complementary output which enables the simple gate shown to be used as either an OR or as a NOR gate (or both), in the positive logic convention. By assuming negative logic inputs, this gate becomes either an AND or a NAND, which makes this circuit a universal building brick capable of performing all the basic logic decisions.

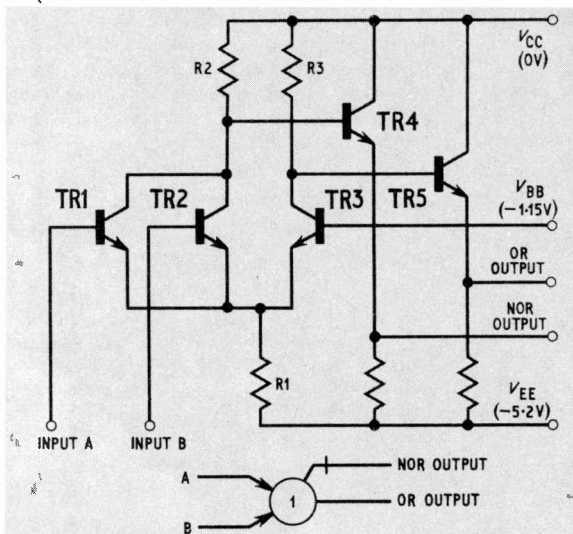


Fig. 11.1. Basic ECL gate (showing positive logic)
Logic level 1 = -0.75V, logic level 0 = -1.55V

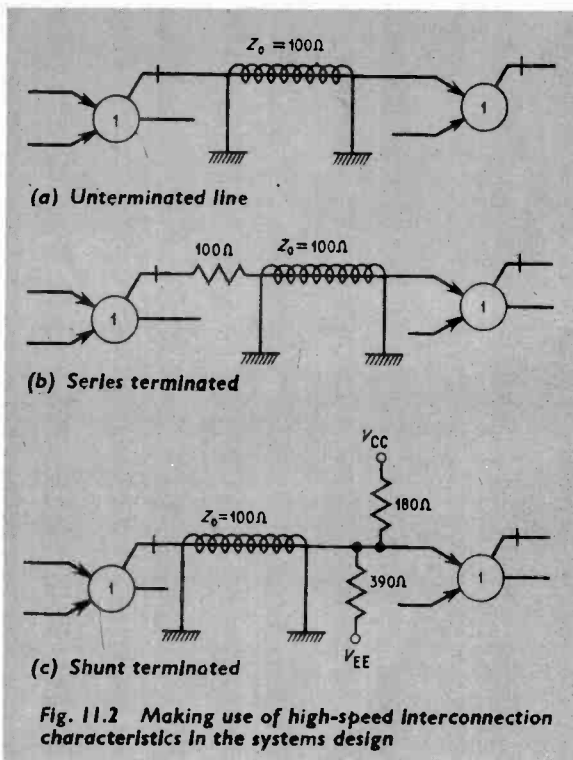


Fig. 11.2 Making use of high-speed interconnection characteristics in the systems design

The dual outputs are provided first because the cascading of gates to turn a NOR into an OR is unacceptable on the grounds of increased propagation delay in high speed systems, and secondly because this useful addition is very easy to incorporate in the circuit where complementary outputs are inherently available from the longtail pair.

OPERATION

The power line voltages are specified quite closely by manufacturers, and Fig. 11.1 gives a typical example where the V_{CC} line is grounded, and the V_{EE} line is run at $-5.2V$.

The V_{BB} line is used only to bias the longtail pair, providing a reference about which the logic swing is centred, and as such could be provided by a potential divider from the other power rails, a technique which is incorporated in some manufacturers ranges of ECL.

In operation, voltages of either plus or minus 400mV (with respect to V_{BB}) are applied to inputs A and B. If both inputs are more negative than V_{BB} , then TR3 will steer the current from R1 through R3, which will have a drop of 800mV across it. The 750mV V_{be} drop of TR5 will subtract from this to give a final OR output of $-1.55V$ (a positive logic 0).

Meanwhile, because very little current will flow through R2, a voltage equal to V_{CC} is present at the base of TR4, giving a final NOR output after the V_{be} drop, of $-750mV$. This re-establishes the input levels of plus or minus 400mV with respect to V_{BB} , ready to drive further gates. In this example the two logic 0 in gave a logic 0 out on the OR pin, and a logic 1 on the NOR pin, just as required.

If any of the inputs become more positive than V_{BB} , then its associated transistor will divert the current from R1 through R2, reversing the situation

in the first example, and giving a 1 out of the OR pin, and a 0 out of the NOR pin.

The uncluttered simplicity of the circuit, coupled with its non-saturating operation, and the use of transistors with very high cut-off frequencies (f_{hft}), gives propagation delays of only one to three nanoseconds, compared with the ten nanosecond performance of the relatively fast TTL gate.

NOISE PERFORMANCE

As the current drawn by a gate is constant no matter what state it is in, very little power line noise is generated by switching transients.

Since the threshold of a gate input is about plus or minus 150mV (with respect to V_{BB}), and since the worst case output levels are about plus or minus 350mV, a d.c. noise immunity of about 200mV (from both 0 or 1) is to be expected.


The main noise problem which arises with logic operating at these speeds is due to ringing and reflections generated by very high frequencies present in the square edges of dynamic gate outputs. The frequencies present, when ECL gates switch, extend into the gigahertz region, making even an inch or so of interconnecting wire act as a significant inductor.

The only solution to problems of this nature is to treat interconnections as transmission lines, using twisted pair for wiring up, and terminating each line in its characteristic impedance which is between 90 to 150 ohms. Professional designers working with printed circuits usually design around 50 ohm lines using multi-layer boards with ground planes.

Fig. 11.2 shows three methods of interconnecting ECL. Using unterminated lines of a twisted pair, interconnections of several inches can be safely handled and fan-out from the end of the line is unrestricted (11.2a). To drive longer lines, termination is necessary to reduce reflections, and there are two methods of achieving this.

Fig. 11.2b shows the simplest terminating arrangement where a resistor equal to the (estimated) Z_0 is placed in series with the line at the driving end; unfortunately, logic swings are of course reduced by half, and noise immunity suffers as a result. This and the next system can be used to drive lines several feet long.

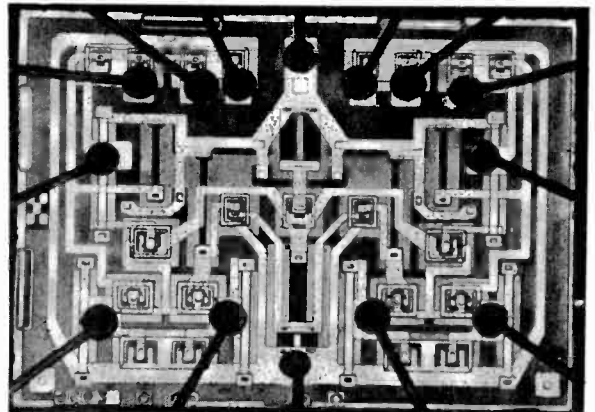By placing a resistance equal to Z_0 in shunt with the line at the remote end, very good driving characteristics can be achieved, with the disadvantage that either a separate supply must be used to terminate the resistor, or a parallel combination such as that shown in Fig. 11.2c must be employed.



Photomicrograph of an ECL double logic gate

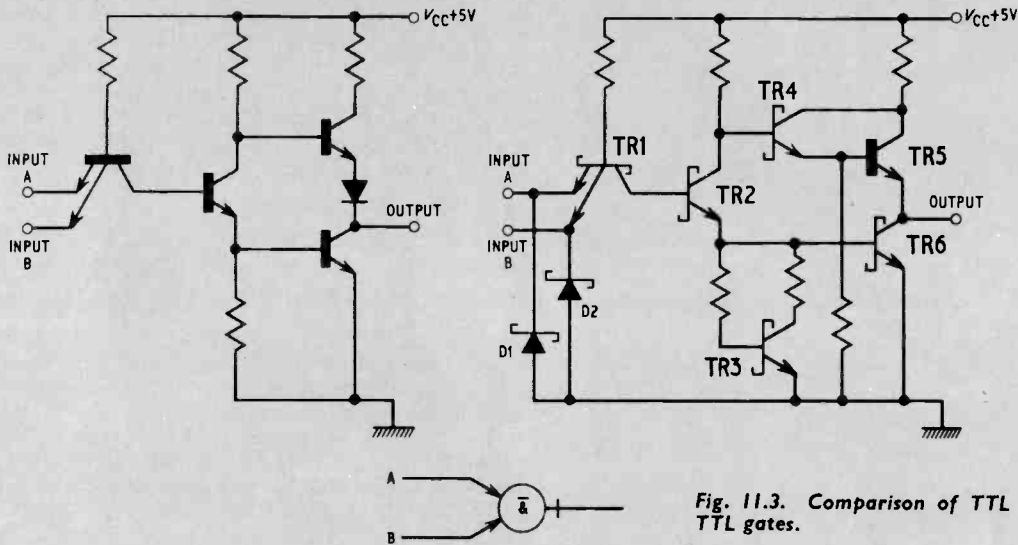


Fig. 11.3. Comparison of TTL and Schottky TTL gates.

FLIP-FLOPS AND MSI

It is likely that the most useful ECL devices for amateur applications will be the flip-flops. At present various ranges are available from different manufacturers to cover the toggle frequency range of 100 to 350MHz. To build counters using ECL flip-flops is relatively easy if binary multiples are required.

If an input frequency is, say, 160MHz, after three ECL flip-flops it is possible to build the rest of the counter with a slower (and cheaper) logic form such as TTL. After three ECL stages the frequency will be down to 20MHz which is within the capability of TTL, although a logic-level interface will be necessary between the two families.

ECL is also produced in the medium scale integration (MSI) form, and although the variety available is not as great as with TTL, a useful range of counters, decoders, and especially arithmetic units, is now available.

One particularly advanced example from the Motorola MECL III range will add together two eight-bit words; the delay from carry in (from a possible previous stage) to carry out (to a possible following stage) is an incredible 10 nanoseconds, or in other words it could add together a hundred million pairs of numbers in one second.

PACKAGES

ECL is available in either the Dual-in-line plastic package or the hermetically sealed (and very expensive) flat-pack.

SHOTTKY CLAMPED TTL

The basic TTL family has become increasingly popular in the last few years, and is without doubt the mainstay of the data-processing industry. TTL is available in the widest number of package functions, and the range is continuously expanding.

The price of this versatile family continues to fall, and it is already cheaper than the less useful DTL devices, prices as low as 10p for a quad 2-input gate package being reported on some large orders. TTL is also available in a wide variety of MSI

packages including quad adders and eight-bit shift registers, making it the only logical choice for medium speed applications (below 50MHz) in new designs.

In our investigation of this family, we concerned ourselves only with the 74 series of devices, which are the most popular; but in parallel with this series are the 74L and 74H devices which extend the usefulness of TTL respectively down and up in the speed range.

Type 74L uses a standard 74 type gate but with larger resistance values to reduce power consumption, whereas 74H uses a slightly modified 74 type gate with lower resistance values to optimise the circuit for high speed operation up to 50MHz.

NEW SERIES 74S

To extend the usefulness of TTL into the speed range above 50MHz, which has always been reserved for ECL devices, is clearly an inviting proposition, despite the technical difficulties involved. This breakthrough has now been made, and Texas Instruments offer several devices using Schottky-clamp technology, in a new series labelled 74S.

Although still in its infancy this new series is set for a great future along with its other TTL relations, with which it is fully compatible in every respect.

A counter which has an input frequency of 100MHz and which is required to divide by 256, can now be built using the combination of two 74S flip-flops, two 74H flip-flops, two 74 flip-flops, and finally two 74L flip-flops. Using slower devices in the succeeding stages in this way gives a dramatic power saving, and is simple to carry out because no interface circuitry is required.

BASIC GATE

The basic STTL gate is shown in Fig. 11.3, alongside the standard 74 series gate for comparison purposes. The basic 74 series gate operates in the saturated logic mode, which means that when any of the component transistors is turned on with a positive voltage on its base, it will "bottom" or saturate, which means, among other things, that its

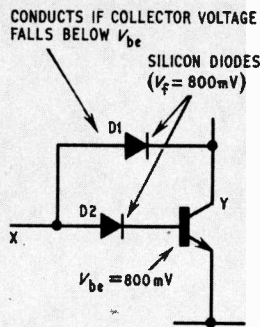


Fig. 11.4. Anti-saturation clamp using common diodes

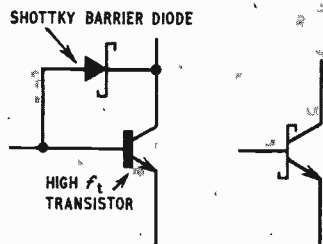


Fig. 11.5. Schottky barrier diode used as an anti-saturation clamp

collector voltage will be lower than its base voltage. Typical values here would be 800mV on the base with 200mV on the collector.

When operated in this manner, transistors are speed limited by the stored charge which has to be removed before the transistor can be turned off. As we have already seen, operating transistors in what is effectively "class A" (ECL) prevents saturation, but techniques of this kind cannot yield a gate which would be compatible with the rest of the TTL family, and therefore must be ruled out.

By connecting an ideal diode from the collector to the base of a transistor, it would be possible to divert base current if the collector voltage fell below V_{be} , and thus to prevent saturation.

This is just fine except for the problem that available diodes are not "ideal", and have a forward voltage similar to the V_{be} of a transistor, but a modification to this idea has been used in the past, and is shown in Fig. 11.4. With the transistor turned on, the voltage at point X will be about $2 \times 800\text{mV}$, or 1.6V.

The diode D2 offsets the V_f of diode D1, so that it will conduct and divert base current if the voltage at point Y falls any lower than 800mV, preventing true saturation of the transistor. The problem with this arrangement is that the silicon diodes used increase storage time effects, and tend to cancel the anti-saturation advantage gained.

SHOTTKY DIODE

In these days of new semiconductor devices seeming to turn up every few weeks, readers may have missed the Schottky-barrier diode, which has proved very useful in microwave applications. The importance of this type of device is that first it has a low forward voltage (V_f) of only 200mV, and second that it has no stored charge because there are no minority carriers. These two characteristics make it ideal for use as an anti-saturation clamp, and in an STTL gate it is used to great advantage across all transistors but one.

Fig. 11.5 shows the way the diode is connected, and also shows the symbol used to denote a clamped

transistor of this type. Other improvements to the 74 type gate include the provision of Shottky input clamp diodes to suppress line ringing and undershoot, which in high speed operation must be minimised.

A compound emitter follower is used in the "active pull-up" section of the output, although this is not new, and is used in the 74H series to give improved performance when driving capacitive lines. Also an extra transistor (TR3), has been incorporated to provide an active "turn-off" for TR6.

Combining saturating and non-saturating design features in this way gives a useful power reduction for the same performance. A measure of this improvement is given by the speed/power product; this could be 10 to 20mW per nanosecond for ECL; is only about 7mW per ns with STTL.

One of the most interesting claims made by the manufacturers of the 74S series is that controlled impedance terminated lines are not required for on-board interconnections, but it is recommended that any constructor using this series uses twisted pairs for such connections.

NOISE PERFORMANCE

Noise immunity of STTL is down on that for the 74 series by about 100mV because of the higher logic 0 level at the output introduced by the non-saturation of TR6.

Fan-out and TTL compatibility are not affected by this increase in level, and an STTL gate will handle ten other 74S inputs or twelve 74 series loads.

At present only a few devices are available in this range, as follows:

SN74S00	quad, 2-input NAND
SN74S20	dual, 4-input NAND
SN74S112	dual edge-triggered JK flip-flop (with preset and clear)

The gates exhibit a propagation delay of typically 3ns and the flip-flops will toggle at 100MHz (typical).

COMPARISON

For the very ultimate in speed performance, ECL still holds the field, and is likely to continue to do so despite the large bite taken out of its slower end by the new STTL. STTL does, however, make a very useful extension to the ever widening application area of the standard TTL, and will soon be found in many frequency counters and synthesisers as well as the inevitable computer arithmetic sections.

I.C. APPLICATIONS TECHNOLOGY

This concludes a long and extensive series of articles on logic i.c.s; some of the devices mentioned in the series are currently obtainable from advertisers, while it is to be hoped that more advanced types will appear later when quantity production is stepped up.

Examples of applications are extremely diverse—some have already been described in this magazine; others will follow. One thing is certain: while the series has been running, the range of devices available and the number of suppliers have increased.

The future of integrated circuits is not in killing off the range of circuitry that can be devised—but in harnessing new technology to the ever demanding requirements of application techniques. This new science is as exciting a prospect as transistors were 20 years ago.



FISH BITE ALARM

By D. R. HAYES

A FISH bite indicator that uses an exposed relay for alarm switching will inevitably run foul of such complications as contact corrosion with exposure to moisture, or line entanglement with the relay. The device to be described has none of these shortcomings, as a sealed reed switch is used.

In principle the switch contacts are held closed by a small permanent magnet which breaks the supply to a multivibrator alarm circuit.


The fishing line is passed between the reed switch and magnet, the latter being free standing. With a bite, the line moves and displaces the magnet so that the supply and alarm are turned on.

OPERATION

The alarm circuit of Fig. 1 consists of a multivibrator circuit, TR1, TR2, the frequency of which is set by C1, R2, R3 and C2.

Square waves produced are applied to the emitter follower TR3 which matches the relatively high output impedance of TR2 to the low impedance of the loudspeaker.

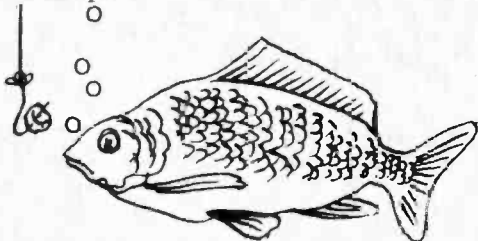The alarm frequency was determined from experiments designed to discover the most penetrating frequency which would be the least likely to be masked by extraneous sounds. A 1kHz note was finally decided upon.



Changes in line voltage have an effect on frequency; a rise in volts causing a rise in frequency and vice versa. However, this tonal variation is not critical and batteries of from 6 to 15 volts are quite acceptable.

CHOICE OF REED SWITCH

Cheap dry reed switches have normally open contacts so they are not much use for direct supply switching in this application. Unfortunately, the cost of a changeover reed switch is about three times

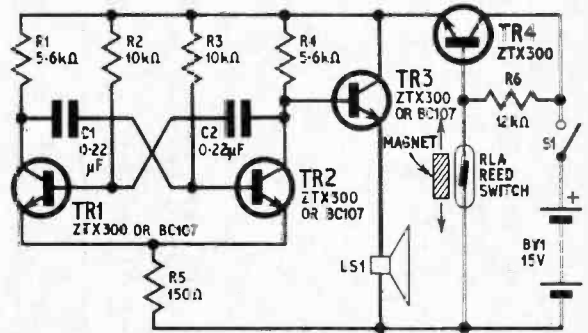


Fig. 1. Circuit of fish bite alarm

COMPONENTS . . .

Resistors

- R1 5.6kΩ
- R2 10kΩ
- R3 10kΩ
- R4 5.6kΩ
- R5 150Ω
- R6 12kΩ
- All 10%, ½ watt carbon

Capacitors

- C1 0.22μF polyester
- C2 0.22μF polyester

Transistors

- TR1-TR4 ZTX300 or BC107 (4 off)

Loudspeaker

- LS1 80Ω, 1½in diameter

Switches

- S1 On/off slide switch
- RLA Dry-reed switch type 6-RSR with short magnet (Radiospares)

Miscellaneous

- Diecast box (Eddystone) 4½in × 3½in × 2in, BY1-15V battery, Bakelite sheet 3½in × 4½in, aluminium 4½in × 3in, copper clad s.r.b.p. board 2½in × 2in
- ½in, 6B.A. tapped stand-off pillars (2 off), ¼in, 6B.A. countersunk screws to suit (4 off), stand-off insulators (2 off)

higher, so some additional circuitry is justified to enable the cheaper switch to be used.

One extra transistor TR4, and its feed resistor, R6, are placed in the supply line so that with the magnet positioned near to the reed switch, this is closed, clamping the base of TR4 to the negative line so that it does not conduct.

When the magnet is disturbed by the line, the reed switch contacts open so that TR4 is biased on via R6.

In the stand-by condition there is a small current drain but, as this is in microamps, it can be ignored.

The circuit will work over a wide range of transistor types, and the remainder of the components can have wide tolerances.


Speaker impedances can range from 3-80 ohms with little performance variation.

CONSTRUCTION


The prototype unit was assembled on a printed circuit board, the etched pattern and wiring details of which are shown in Fig. 2. Apart from the reed switch mounting, component layout is not critical so Veroboard could be used as an alternative.

Since, in the final assembly, a Bakelite lid is interposed between the reed switch and the magnet, it is most important that the former be mounted as close as possible to the lid. With the components specified, the maximum operating distance of the magnet is about 1in.

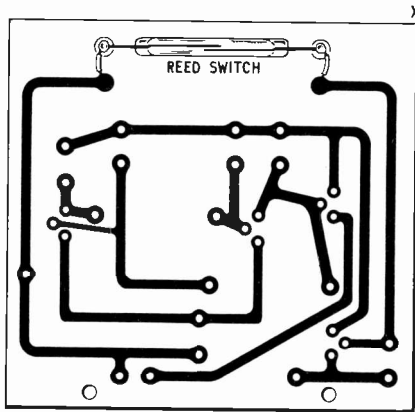Two 1/4in, 8BA stand-off insulators are used to mount the reed switch which appears on the opposite side of the board's small component assembly.



(a)

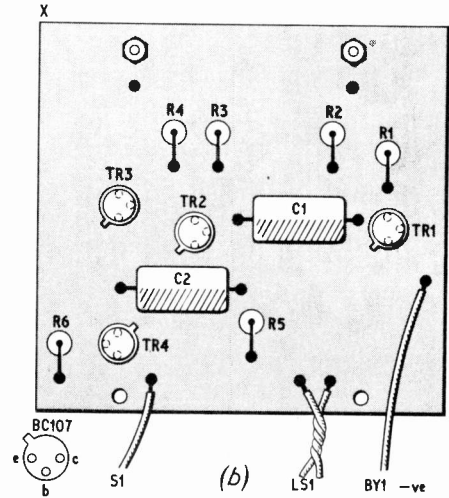

(b)

Fig. 2(a). Etching pattern for copper clad board. (b) The topside of the board with components in position



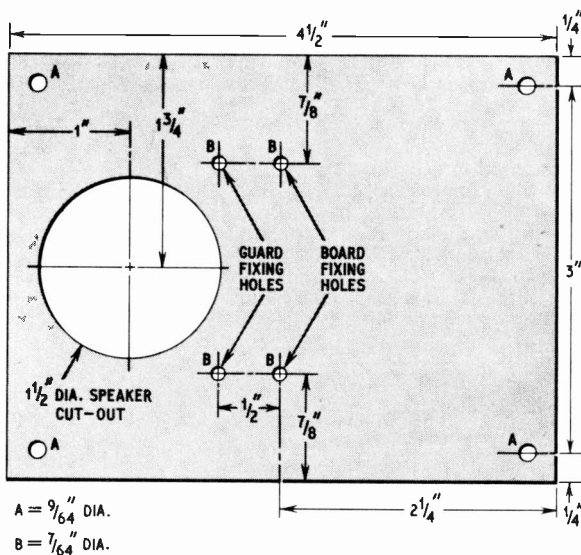


Fig. 3 (above). Drilling details of Bakelite lid

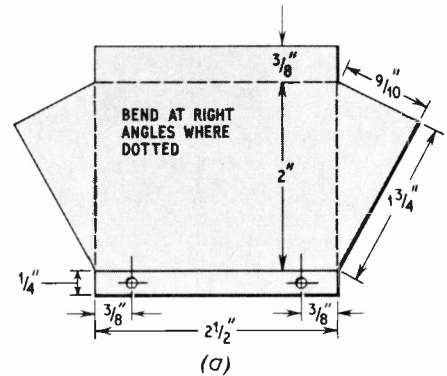

(a)

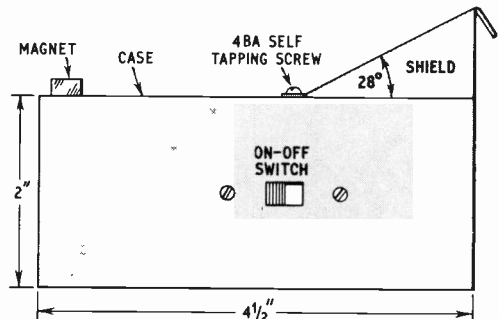

(b)

Fig. 4a (above right). Pattern for cutting and bending aluminium water shield

Fig. 4b (right). Profile of completed unit

NEWS BRIEFS


Cine to Television

HIGH quality T.V. pictures can be taken from cinefilm being shown on a normal large screen by a novel simultaneous projection unit, designed by Top Rank T.V. This replaces the ineffective technique of pointing a T.V. camera at the screen.

The unit can be mounted on most standard 35 mm cine projectors to deflect a proportion of the projected light, through a specially computed optical system, into a television camera (see photograph).

It is designed for professional 35 mm projectors but a variant for use with professional 16 mm machines is available to special order.

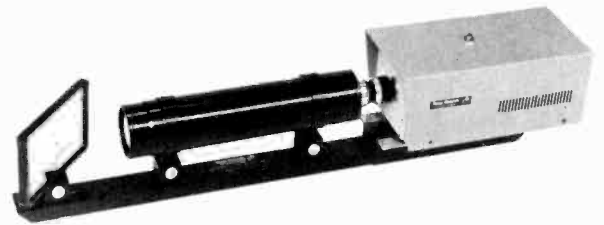The optical system provides matching to 1 inch vidicon or plumbicon picture formats, and has accommodation for balancing neutral density filters. It can be used with either mono-chrome or colour television cameras.





Portable Television

A NEW single standard (625 lines) 12-inch monochrome portable T.V. has been introduced by B.R.C. under the brand name Ferguson. Of its type the Courier—as the set is to be known—is the only portable on the U.K. market that is British made and has push-button selection. The set cost £58.60, less than any other comparable set.

The Courier shown below weighs only 16½ lbs. is mains operated, has an adjustable loop aerial and is enclosed in a plastics case.

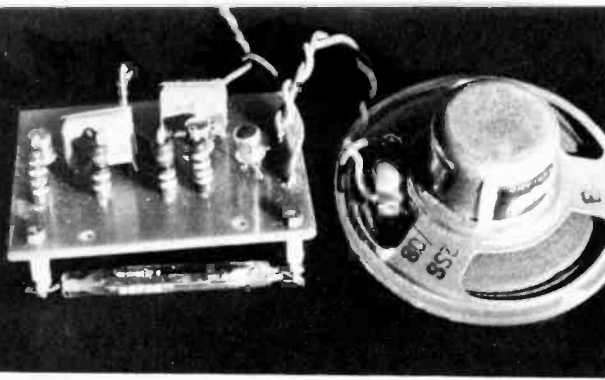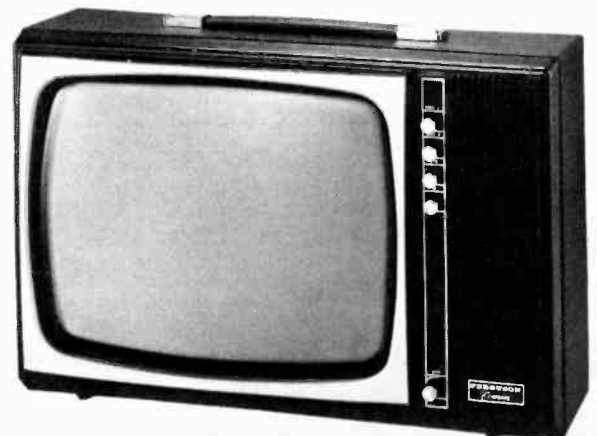Other unique aspects of the Ferguson 12-inch Courier include technical innovations not usual in small portables. There is a four-stage, transistorised, high gain I.F. amplifier with amplified AGC applied to the first two stages. The horizontal line timebase is flywheel controlled to avoid misregistration of lines under poor reception conditions.



Other small reed switches can be used if preferred, as the contact current rating requirement is extremely small.

LID MOUNTING

With the wiring of the printed circuit board completed, a 3½in by 4½in Bakelite sheet should be cut out and drilled as in Fig. 3. This will serve as a non-magnetic lid for mounting the board and loudspeaker.

Two ¼in, 6B.A. tapped pillars with ¼in countersunk screws are used for fixing the board. With this in position the area over the reed switch on the Bakelite lid should be scratched to provide a future marker for the magnet.

As the device will spend a good part of its life in the open air it is a good idea to fit some form of shield to protect the loudspeaker from the ingress of water. How this is achieved is given in Fig. 4 which provides constructional and mounting details of an aluminium water shield. Two 4B.A. self tapping screws are used to retain this to the lid.


Interwiring can now proceed according to Fig. 2. With this completed the unit should be functionally tested.

An Eddystone diecast box supports the lid assembly and contains the battery. This should be drilled for S1 and the switch mounted. The battery should now be connected and a final test carried out before securing the lid.

EASILY SEEN


When completed, the indicator should be painted in some bright, easily visible colour, so that it will not be accidentally trodden on or left behind when fishing is completed.

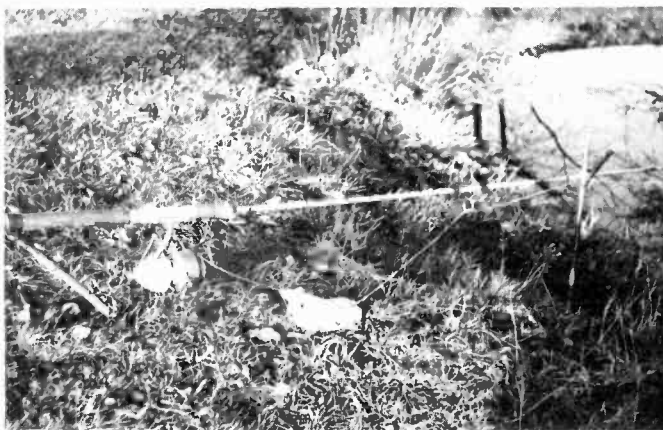The operating magnet should also be painted and a small piece of cloth glued to its base to supply the necessary friction between it and the fishing line. Green baize is an ideal choice here. ★



introducing the New SK2 KIT to the Antex range

£2.40 recommended retail price

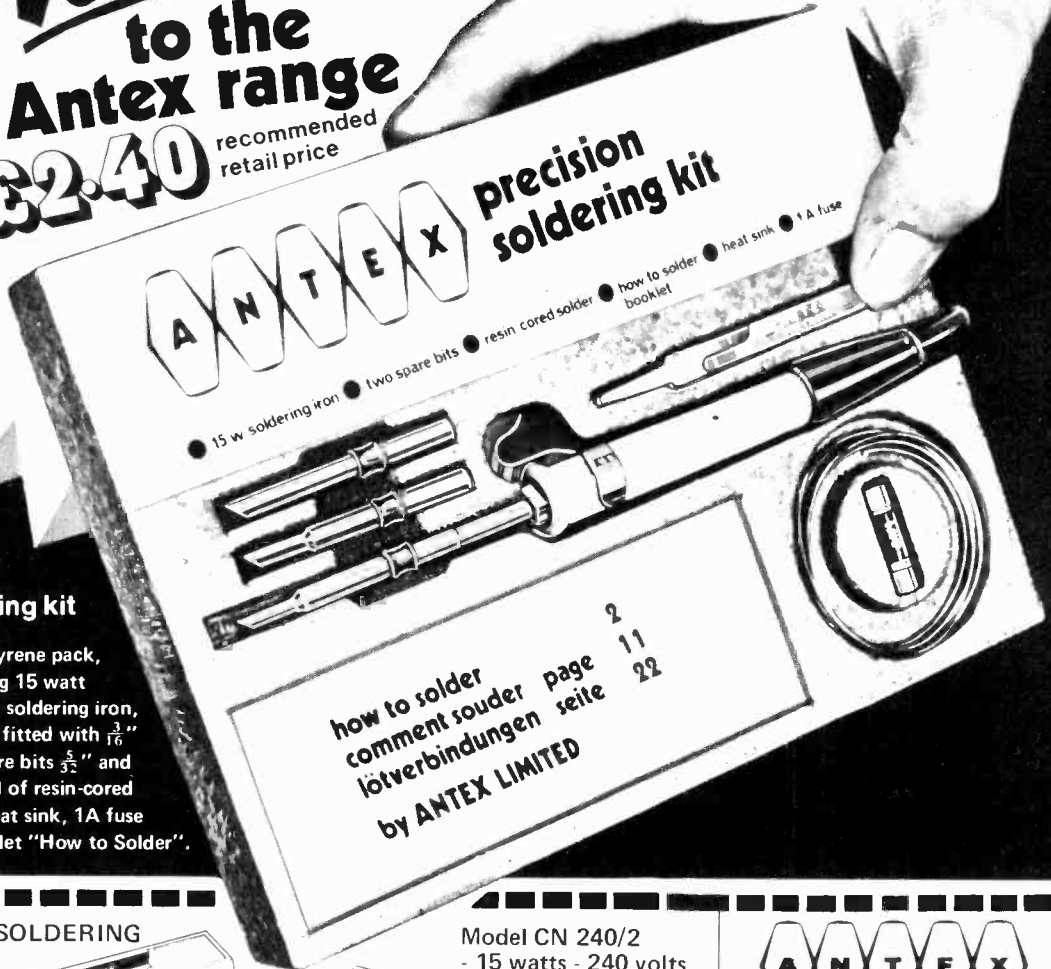


SK2 Soldering kit

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with $\frac{3}{16}$ " bit, 2 spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".

how to solder page 2
comment souder page 11
lötverbindungen seite 22
by ANTEX LIMITED


SK1 SOLDERING KIT

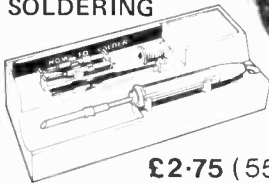

£2.75 (55/-)


In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted $\frac{3}{16}$ " bit. Spare bits $\frac{5}{32}$ " and $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder"

Model CN 240/2
- 15 watts - 240 volts

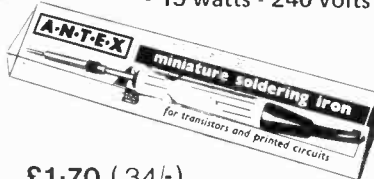

£1.70 (34/-)

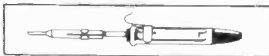Fitted with nickel plated $\frac{3}{32}$ " bit and packed in handy transparent box.



Model G - 18 watts. Fitted $\frac{3}{32}$ " bit. Spare bits $\frac{1}{8}$ ", $\frac{3}{16}$ " and $\frac{1}{4}$ " available. For 240 or 220 volts. £1.80 (36/-).



Model F - 40 watts. Fitted $\frac{5}{16}$ " bit. Spare bits $\frac{3}{32}$ ", $\frac{1}{8}$ ", $\frac{3}{16}$ " and $\frac{1}{4}$ " available. For 240, 220, 110, 20 volts. From £2.35 (47/-).

Model E - 20 watts. Fitted $\frac{1}{4}$ " bit. Spare bits $\frac{3}{32}$ ", $\frac{1}{8}$ " and $\frac{3}{16}$ " available. For 240, 220 or 110 volts. From £1.80 (36/-).

Model ES - 25 watts. Fitted $\frac{1}{4}$ " bit. Spare bits $\frac{3}{32}$ ", $\frac{3}{16}$ " and $\frac{1}{4}$ " available. For 240, 220 or 110 volts. From £1.80 (36/-).



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
Telephone Plymouth 67377/8.
Telex: 45296. Giro No 2581000.

- Please send me the Antex colour catalogue
 Please send me the following
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| | | | | |
| | | | | |


I enclose cheque/P.O./cash value

NAME

ADDRESS

PE5

DIGITAL

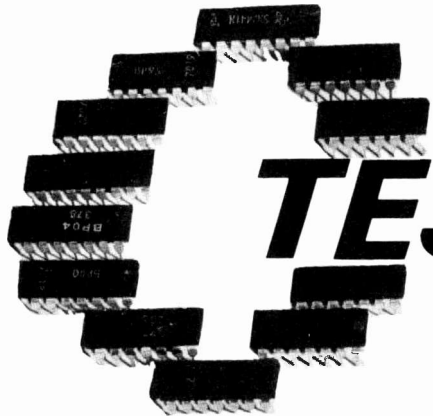

TESTER

By D. Burn Ph.D

Provides a rapid functional check-out for digital 'dual-in-line' integrated circuits

RECENT articles on digital integrated circuits in this magazine have stimulated a considerable interest in these fascinating devices. Added to the fact that they are now available to the amateur at low prices, many readers will doubtless wish to experiment with them.

When using transistors, particularly the low-cost bargain variety, the wise experimenter will have carried out a few simple tests on each one before incorporating it into his circuit. The same precaution is advisable to an even greater extent when using i.c.s, for trouble-shooting a complex system is difficult enough without the added complication of one or more dud i.c.s.

The tester to be described will carry out fairly simple go-no go tests on a wide variety of i.c.s., and is particularly aimed at the TTL dual-in-line series which is currently available with the largest choice of functions. However, both RTL and DTL can be checked, and simple adaptors could be devised for other types of i.c. package.

FLEXIBILITY

The major problem with an instrument of this type is to provide sufficient flexibility to enable any one of a very large range of possible logic functions to be checked, from a simple two input NAND gate to a complex four bit binary adder. The key to this problem lies in the use of patch-cords, which, although perhaps somewhat untidy, offers an economical solution.

The i.c. to be tested is plugged into a 16 pin socket, every pin of which is wired to a single pole, four-way switch. These switches enable each pin to be connected either to 0 volts, a logical 1 voltage, the supply voltage or, via a patch-cord socket, to some other input or output function.

The input is provided by a versatile pulse generator, while the output may be a voltmeter, an indicator lamp or an oscilloscope.

POWER SUPPLY


The circuit may conveniently be divided into two parts, a power supply with associated meter circuit, and a pulse generator with associated indicator lamps.

In the power supply circuit (Fig. 1) the output of transformer T1 is rectified by diodes D1 to D4, smoothed by C1 and fed to R1 and the Zener diode D5 to provide a fixed supply of 5.1 volts for the pulse generator and the indicator lamps.

Diode D6 provides a 12 volt source, part of which, selected by VR1, is fed to the base of the series transistor TR1.

The output from the emitter of TR1 is a voltage which may be varied from zero up to about 10V and forms the supply to the i.c. under test. In the prototype, a 2N3055 was used here, but it is probable that a transistor of a lower rating could be substituted.

Capacitor C3 further smooths the output, while C4 is a decoupling capacitor to prevent instability.

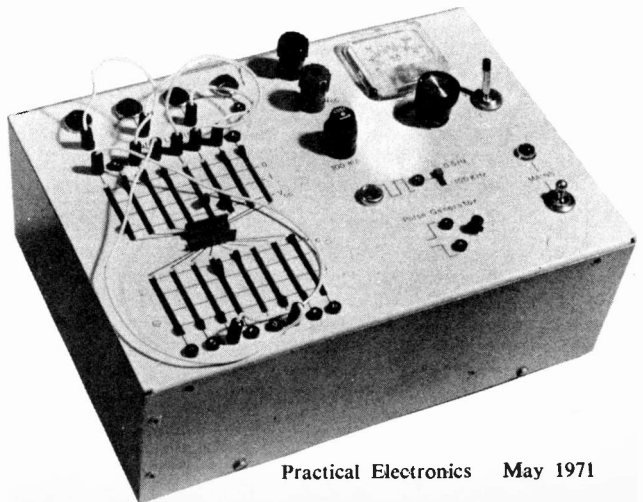


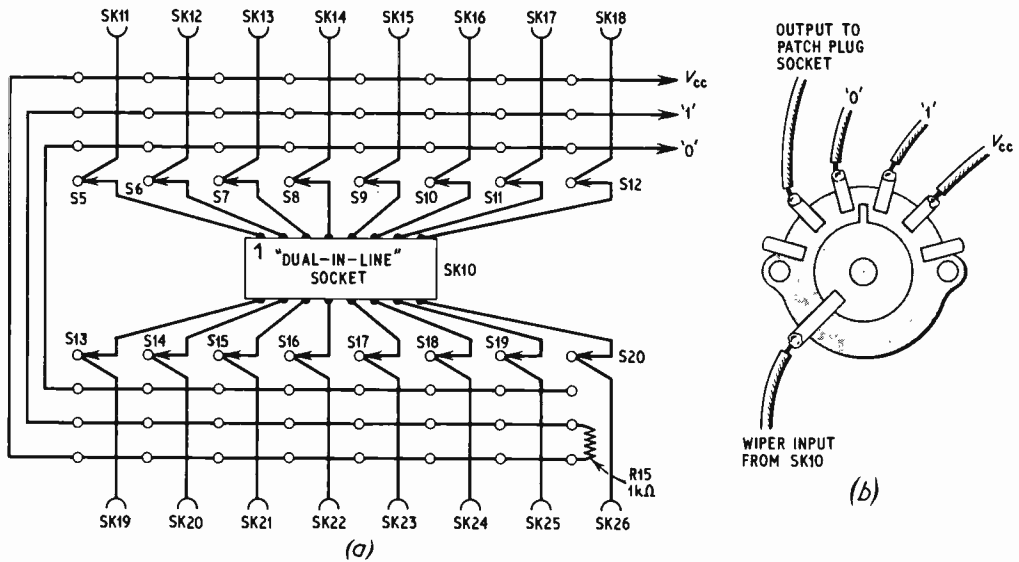


Fig. 4. (a) Wiring layout of i.c. test socket and pin switches. (b) Wiring pattern for all switch wafers. Note that only one half of the wafer is used. This figure should be consulted when assembling and wiring the switch banks

Fig. 5. Constructional details for assembling the aluminium case. Binder screws for fixing the side panels should be 2B.A. The upper and lower plates are fixed with 4B.A. screws

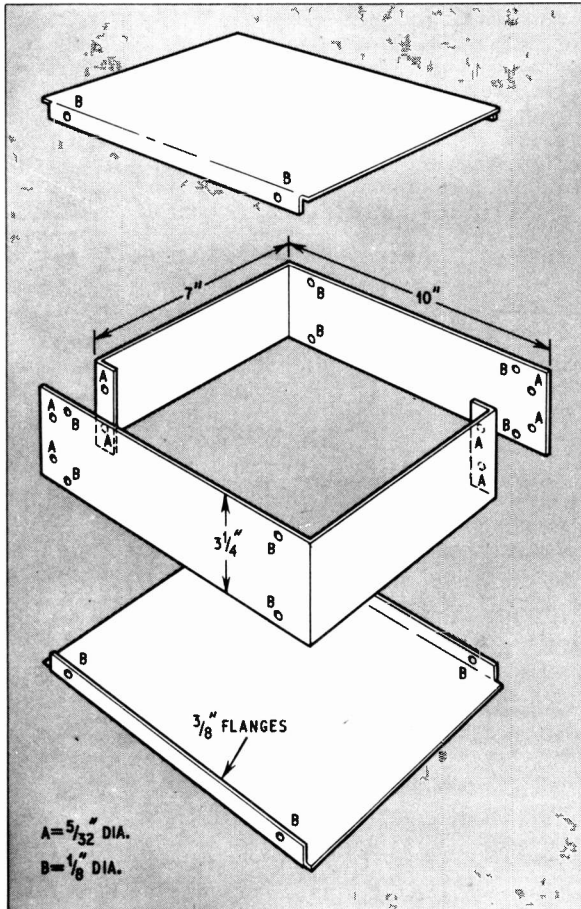

The wiring adopted for the pulse generator and its indicator lamp is such that the lamp LP2 follows the clock pulse, i.e. it is on when the clock is at a logical 1, but it does not load the output of the Schmitt and thus avoids possible degradation of the rise time.

The lower pulse rate allows the operation of an i.c. to be followed with the indicator lamps, while the fast pulse checks the operation of the i.c. at high speed, and is intended to be used with an oscilloscope.

The other two gates of IC1 are connected as a simple flip-flop which is used, in conjunction with the change-over switch S4, to provide single rising or falling waveforms for manual operation. This system is essential to avoid the multiple pulses that would otherwise be produced by the inevitable contact-bounce of the switch.

Four indicator lamps, LP3-LP6, and their associated amplifiers TR5-TR8, are provided for monitoring the operation of an i.c. under test. Resistors R11-R14 limit the current drawn from the i.c. output, and are wired to the patch-cord sockets SK6-SK9 so that any pin may be connected to any indicator.

The wiring of the i.c. 'dual-in-line', 16-way socket SK10, the 16 single-pole four-way switches S5-S20, and the associated patch-cord sockets SK11-SK25, is shown in Fig. 4a. Notice that the logical 1 level is derived from V_{CC} via a 1kΩ resistor R15. This ensures that the 1 level cannot exceed V_{CC}, a condition which would result in the instantaneous destruction of the i.c.

CONSTRUCTION

The instrument is built in a case measuring 10in by 7in by 3 1/4in. This may be constructed from 16s.w.g. aluminium following the dimensions of Fig. 5.

PHILIPS STEREO & MONO AUTOCHANGER

£8.75 Post 25p.

Precision hi-fi quality at bargain price. Silver and grey deck, enamelled finish. 10 1/2 in. dia. turntable. 4 speeds, 16, 33 1/3, 45 and 78 r.p.m. Plays 7, 10, 12 in. discs which can be mixed. Fitted renowned Philips plug-in Xial AG3800 with dual sapphire stylus for LP/EP/78. Sensitivity 100mV. Frequency response 30cps-16Kc/s. Lightweight stylus pressure 3-6 grammes. Board space required 14 x 12 1/2 in. Above 4 in. Below 2 1/2 in. 12 months guarantee.

Also available with GP310 diamond stylus LP Stereo/EP and Sapphire 78. £1 extra.

MATCHED TEAK PLINTH WITH PLASTIC COVER. Only 58 extra or Cut-out plywood base board 50p extra.



BSR 4-SPEED SUPERSLIM STEREO & MONO CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in.

Above motor board 3 1/2 in. below motor board 2 1/2 in.

with STEREO and MONO XTAL £7 Post 25p.

BSR Minichanger UA50 Stereo and Mono. Plays 12", 10" or 7" records. £8 Post 25p. Size 12 x 8 in. AC 200/250V.



GARRARD PLAYERS with Sonotone STA Cartridges.

Stereo Diamond and Mono Sapphire. SP25 Mk II £15. Model 8000 Stereo and Mono Autochanger £13. Post 25p. Model 8500 Stereo and Mono Autochanger £14. Post 25p.

RECORD PLAYER PORTABLE CABINET £3.75
Space for amplifier and autochanger. Post 25p.

RC8 DE-LUXE 3 WATT AMPLIFIER. Ready made tested. 2-stage with triode pentode valve. 3 watts output. Tone and volume controls. Isolated main transformer. Knobs, loudspeaker, valves ECL82, E230. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £4

RC8 2 WATT AMPLIFIER with loudspeaker and valves UCL82 and UY85. Post 25p. £3

R.C.S. TEAKWOOD BASE. Ready cut out £3.25 for mounting (state player make and model).

R.C.S. PLASTIC COVERS FOR ABOVE BASE. £3.25 Durable tinted plastic, attractive appearance.

EMI PICK-UP ARM. With mono rial and stylus £1.25.

EMI JUNIOR 4 SPEED RECORD PLAYER. Mains £3 operated motor, turntable and pick up. Post 25p.

HI-FI PICK UP CARTRIDGES. Diamond Stereo/Mono STA £2.90; GP94 £2.75; GP93 £2.25; Mono GP91 £1.60; GCS 11 £5; GP7 95p; ACOS L.P. only 50p.

All standard fixing complete with stylus.

WEYRAD P50 - TRANSISTOR COILS

RA5W Ferrite Aerial... 65p Spare Cores... 3p
Osc. P50/1AC... 30p Driver Trans. LFDT4... 50p
L.F. P50/2CC 470 kc/s... 33p Printed Circuit, PCA1... 50p
3rd L.F. P50/3CC... 33p J.B. Tuning Gans... 65p
P51/1 or P51/2... 33p Weyrad Booklet... 10p
P50/3V... 35p OPT... 55p
Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 25p.

VOLUME CONTROLS

Long spindle. Midgest size 5 K. Ohms to 2 Meg. LOG 8 L.N. L/S 15p. D.P. 25p. 40 yd. £1.40; 60 yd. £2.

STEREO L/S 55p. D.P. 75p. Edge 6K. S.P. Transistor 25p.

FRINGE LOW LOSS 10p. Ideal 625 and colour yd.

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 Ohm to 30 K. £2.5p

WIRE-WOUND 3-WATT STANDARD SIZE POTS. LONG SPINDLE £4.0p 10 OHMS to 100 K.

VEROBOARD 0.15 MATRIX

2 1/2 x 6 in. 19p. 3 1/2 x 3 in. 19p. 3 1/2 x 5 in. 26p.
EDGE CONNECTORS 16 way 25p; 24 way 38p.
PHS 36 per packet 17p. FACE CUTTERS 36p.

S.R.B.P. Board 0.15 MATRIX 2 1/2 in. wide 3p per lin., 3 1/2 in. wide 4p per lin., 4 in. wide 5p per lin. (up to 17 in.).

S.R.B.P. undrilled 4 in. Board 10 x 8 in. 15p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 in. sides, 7 x 4 in. 45p; 9 x 7 in. 50p; 11 x 7 in. 70p; 13 x 9 in. 75p; 14 x 11 in. 80p; 15 x 14 in. 85p; 11 x 8 in. 50p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 8p; 8 x 6 in. 15p; 10 x 7 in. 17p; 12 x 8 in. 23p; 14 x 9 in. 27p; 12 x 12 in. 32p.

1 1/2 inch DIAMETER WAVELENGTH SWITCHES.


2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 26p each.
1 p. 2-way, or 4 p. 2-way, or 4 p. 3-way 26p
1 1/2 inch DIAMETER WAVELENGTH SWITCHES 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 2-way, 6 p. 2-way, 1 water 60p, 2 water 95p. Extra water up to six 30p each.
TOGGLE SWITCHES, sp. 14p; dp. 18p; dp. dt. 23p.

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohm Super Sensitive... £1.75
LOW RESISTANCE HEADPHONES 2.5 ohm... £2
DE LUXE STEREO HEADPHONES 8 ohm... £3.25

"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER

200/250 v. A.C. Leaflet S.A.E. £2.35 Post 15p



GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

for Mike, Tape, P.U., Guitar, etc.

Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2". Response 25 cps. to 25 Kc/s, 26 db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. Guaranteed. Details S.A.E. 90p Post 10p

NEW TUBULAR ELECTROLYTICS

2/350V	14p	100/25V	10p	CAN TYPES	
4/350V	14p	250/25V	14p	50-16/500V	55p
8/450V	14p	500/25V	20p	50-50/350V	35p
16/450V	15p	8+3/450V	15p	60-1/100/350V	58p
32/450V	20p	8+16/450V	20p	32-32/350V	15p
25/25V	10p	16+16/450V	25p	32+32+32/350V	43p
50/50V	10p	32+32/350V	25p	100+50+50/350V	48p

SUB-MIN. ELECTROLYTICS.

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 12V 18p; 2000mF 25V 35p.

CERAMIC, 1pF to 0.01mF 4p. Silver Mica 2 to 5000pF, 4p.

PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p.

500V-0.001 to 0.05 4p; 0.1 0.25 8p; 0.47 25p.

1.000V-0.001, 0.0022, 0.0047, 0.01, 0.025 8p; 0.047, 0.1, 14p.

SILVER MICA. Close tolerance 1%, 2.2-500pF 8p; 560-2,200pF 10p; 2,700-5,600pF 20p; 6,900pF-0.01, mid 30p each.

TWIN GANG. "0-0" 208pF+176pF, 65p; Slow motion drive 386pF+386pF with 25pF+25pF, 55p; 500pF slow motion, standard 45p; small 3-gang 500 pF £1.10.

SHORT WAVE SINGLE 25pF, 50pF, 55p.

CHROME ELECTRIC AERIALS 29 50in. Swivel base 20p.

TUNING. Solid dielectric. 100pF, 500pF, 35p each.

TRIMMERS. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 5p; 250pF, 8p; 600pF, 70pF, 10p; 1000pF, 10p.

RECTIFIERS CONTACT COOLED half wave 60mA 38p; 85mA 48p. SILICON BY213 30p; BY100 50p.

Full wave Bridge Rectifiers 75mA 50p; 150mA 95p.

EX-OVT. RECTIFIER AERIALS 29 50in. Swivel base 20p.

NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p.

RESISTORS. 1 w. 1 w. 1 w. 20%; 1/2 w. 2 w. 5p.

HIGH STABILITY. 1 w. 2% 10 ohms to 10 meg., 10p. Ditto 5p. Preferred values 10 ohms to 10 meg., 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2 watt, 1 ohm to 8.2 ohms 10p.

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key £1.25


lin. 25p lin. 58p lin. 98p lin. £1.20 2 1/2 in. £2.21

lin. 83p lin. 1 1/2 in. £1.15 lin. 2 1/2 in. £2.86

lin. 84p 1 1/2 in. 88p lin. £1.08 2 in. £1.99 lin. sq. £1.83

AM - FM/VHF TUNING GANG

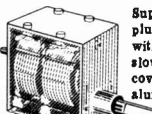Super quality small size 1 1/2 x 1 1/2 in. plus spindle 1 1/2 x 1/2 in. 385+385 pF with 25+25 pF British made. Geared slow motion drive 6.1. Plastic suit cover. 6BA tapped front fixing. Cast aluminium frame. 50p POST FREE



MAINS TRANSFORMERS

250-0-250 50 mA. 6.3 v. 2 amp. centre tapped	£1.10
250-0-250 80 mA. 6.3 v. 4 amp.	£1.40
250-0-250 80 mA. 6.3 v. 3.5 v. 6.3 v. 1 a. or 5 v. 2 a.	£2
300-0-300 80 mA. 6.3 v. 3.5 v. 6.3 v. 1 a. or 5 v. 2 a.	£2.30
300-0-300 v. 150 mA. 6.3 v. 4 a. C.T.	£2.50
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in.	75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in.	90p
HEATER TRANS. 6.3 v. 1 1/2 a.	70p

Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp. 80p

GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2

1 amp. 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, £2

2 amp. 8, 8.10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3

AUTO TRANSFORMERS 0-115-230 v. Input/Output, 150w. £2; 500w. 25; 1000w. £12

CHARGER TRANSFORMERS. Input 200/250V. For 6 or 12v., 1 1/2 amp. £1.20; 2 amp. £1.50; 4 amp. £1.90

FULL WAVE BRIDGE RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.


All Transformers Postage 25p each

E.M.I. 13 1/2 x 8 in. LOUSPEAKERS

With flared tweeter cone and ceramic magnet, 10 watt.
Bass res. 45-60 cps.
Flux 10,000 gauss.
3 or 8 or 15 ohm. Post 15p each

Also with twin tweeters. £4
With crossover, 10 watt.
State 3 or 8 or 15 ohm. Post 15p

Recommended Teak Cabinet Size 16 x 10 x 8 in. Post 25p. £5



10W MINI-MODULE £3.25 LOUSPEAKER KIT Post 25p

Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. x 8 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm.

TEAK VENEERED BOOKSHELF ENCLOSURE. 16 1/2 x 10 1/2 x 6 in. Modern design, dark grey Tegan covered baffle. £5 Post 25p

RADIO BOOKS - LISTS S.A.E. *

RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME

337 WHITEHORSE ROAD, CROYDON
Open 9.6 p.m. (Wednesdays 9.1 p.m., Saturdays 9.5 p.m.)
1333, 68 pass door. S.R. Stn. Selhurst. Tel. 01-884-1665

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12 in MAJOR £9

36-14,500 c.p.s., 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 cps. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50



BAKER "BIG-SOUND" SPEAKERS

Group 25'	Group 35'	Group 50'
12 inch £7	12 inch £9	15 inch £19
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 12 in. round Loudspeaker £9 Post 25p
For 13 x 8 in. Loudspeaker £4 Post 25p
For 10 x 6 in. Loudspeaker £4 Post 25p
LOUDSPEAKER CABINET WADDING 12 in. wide, 15p ft

THIS ELAC CONE TWEETER IS THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF PERFORMANCE THAN MORE EXPENSIVE UNITS

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt 3 ohm or 15 ohm models. £1.90 Post 10p



TWO-WAY OVER NETWORK 3000 c/s.

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5 1/2 in. x 4 in. with control knob, tweeter and woofer leads and 1 1/2 in. Post input terminals. Suitable for 3 or 8 ohm imp. £1.90 Post 10p

Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £1.50.
De Luxe Horn Tweeters 2-18 Kc/s, 15W, 8 ohm £2.
TWO-WAY 3,000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 95p.
SPECIAL OFFER! 90 ohm. 2 1/2 in. dia.; 85 ohm. 3 in. 25 ohm. 3 in. dia.; 8 x 4 in.; 8 x 5 in. 15 ohm. 3 1/2 in. dia.; 7 x 4 in.; 8 x 5 in. 3 ohm. 2 1/2 in. 3 in. 5 in. 5 x 5 in. 7 x 4 in.

90p EACH

LOUDSPEAKERS P.M. 3 OHMS. 6 in. £1.10; 8 x 5 in. £1.25; 8 x 2 1/2 in. 80p; 5 in. £1.75; 10 x 6 in. £1.90.
b/w WOOFER. 8 w. max. 20-10,000 cps. 8 or 15 ohm £1.90.
ELAC 8 in. De Luxe Ceramic. 3 ohm or 8 or 15 ohm £2.50.
RICHARD ALLAN TWIN CONE LOUSPEAKERS 8 in. dia. 4 watt; 10 in. dia. 5 watt; 12 in. dia. 6 watt. 3 or 8 or 15 ohm models £1.95 each. Post 15p.
OUTPUT TRANS. EL84, etc. 25p. MIKE TRANS. 50:1 25p.
SPEAKER COVERING MATERIALS. Samples Large S.A.E.
GOODMANS OUTPUT TRANSFORMERS 5 watt push pull for valves EL84, etc., 3, 8 and 15 ohm 85p. Post 20p.

100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Response 10-30,000 cps. Matches all loudspeakers. Weight only 12 lb. £36 Post A.C. 200/250V. Guaranteed. Details S.A.E. £36 Free

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES. ILLUSTRATED EAGLE CATALOGUE 20p. Post free

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4

BARGAIN 4 CHANNEL TRANSISTOR MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphones, records, tape and tuner with separate controls into single output. 9 volt. £3

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. £10

BARGAIN FM TUNER above. £7.50

Chassis only, less cabinet.

FM STEREO MULTIPLEX ADAPTOR for above or general use. Ready made with 4 transistors, 6 diodes £5


BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES. SURFACE OR FLUSH 25p.

BALANCED TWIN FEEDERS 6p. 8 or 30 ohms or 300 ohms. JACK SOCKET Std. open-circuit 14p. closed circuit 23p; Chrome Lead Socket 45p. Phone Plugs 6p. Phone Socket 5p. JACK PLUG Std. Chrome 19p; 3-5mm Chrome 19p. DIN SOCKETS Chassis 3-pin 9p; 5-pin 15p; DIN SOCKETS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 3p; CAN 5p.

E.M.I. TAPE MOTORS. 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA Spindle 0.187 x 0.76 in. Size 3 1/2 x 2 1/2 in. (Illustrated). Post 15p. £1.25

BALFOUR GRAM. MOTORS. 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 x 3/20. Size. 85p 2 1/2 x 2 1/2 in. Post 15p



LOW VOLTAGE AMPLIFIER Few only at **£1.75**

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.



plus 13p P. & P.

ACOS STETHOSET. 200 ohm d.c. Res. stethoet complete with 5ft of wire. Ideal for private listening on radio and tape recorder. These stethosets are made to very high standards, they are used but in good condition and are all guaranteed. Well below original Price at **39p** plus 8p P. & P.




CRESCENT RADIO LTD
11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL



EMI LOUDSPEAKER 450
10W 13in x 8in ± two 2.2in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. **£3.50** plus 38p P. & P. each.

PSYCHEDELIC LIGHT CONTROL UNIT

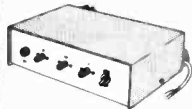

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18.50** plus 38p P. & P.

If you require more information please send S.A.E.

SHELF UNIT



Two teak finish shelves on a black frame (overall size: 28in x 25in x 12in). Ideal for hi fi equipment: amplifiers, speaker cabinets, etc. The perfect answer for housing unit audio and equipment. This unit is wall mounting. **£2.50** plus 38p P. & P.

EMI LOUDSPEAKER 150
10 watts. 13 x 8 base unit. Plus a flared centre cone. Designed to handle the higher frequencies. Please state imp required. 3.8-15 Ω. A bargain at **£2.50** plus 38p P. & P. each.

BATTERY ELIMINATOR



Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2 in x 2 in x 3 in approx. 4 1/2 V **£1.50**. 6V **£1.50**. 9V **£1.50**. 7 1/2 V complete with cable and plug for Philips Cassette. **£2** plus 8p P. & P. each.



CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 **38p**, C90 **63p**, C120 **88p** plus 5p P. & P.

HIGH QUALITY IMPORTED HEADPHONES

1,000 Ω per phone **80p** TTC
2,000 Ω per phone **88p** G1105
Plus 10p P. & P. per pair.



STEREO HEADSET

8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. **£2.50** plus 10p P. & P.




STEREO JUNCTION BOX

For stereo amplifiers without stereo jack socket. **£1.25** plus 8p P. & P.

MAINS KEYNECTOR

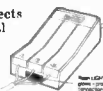Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage, demonstrations, etc. Multi connections can be made (max. load 13A fused). **ONLY £2.33** P. & P. Free on this item.



BARGAIN BOARDS

Component galore for the experimenter. Ex computer boards with: Resistors, Capacitors and useful Transistors—at least 4 transistors per board. BARGAIN PRICE 30p per board 5 BOARDS **£1.20**. P. & P. Free on this item.



BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price **£2.75** plus 5p P. & P. each.



CHROME TV STAND

28in x 8 1/2 in x 16in high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at: **£1.63** plus 25p P. & P.



WE HOLD THE LARGEST STOCK OF RETAIL COMPONENTS IN LONDON — SEND S.A.E. FOR FREE LISTS

Our new shop now open at **13 SOUTH MALL, EDMONTON, N.9** carries our complete stock of electronic components and hi-fi

It costs

ONLY 63p
post paid

for today's MOST USEFUL COMPONENTS CATALOGUE

Many radio and electronic enthusiasts say that our catalogue is "priceless"! Be that as it may, we charge you only 63 pence. What is more the catalogue contains 6 vouchers, each worth 5 pence when used as indicated. And for good measure, we throw in a useful Bookmark giving electronic abbreviations and a 30-page Price Supplement. *Why are you waiting?* By the way, if it suits you to call at our shop you save yourself another 20 pence—the post and packing costs.

POST THIS COUPON




Please write Name and Address in block capitals

Name
Address



with your cheque or P.O. for 63p

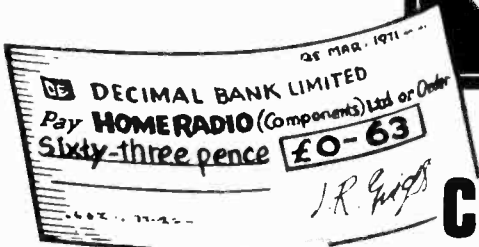HOME RADIO (Components) LTD.
Dept. PE, 234-240 London Road, Mitcham CR4 3HD



The price of 63p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

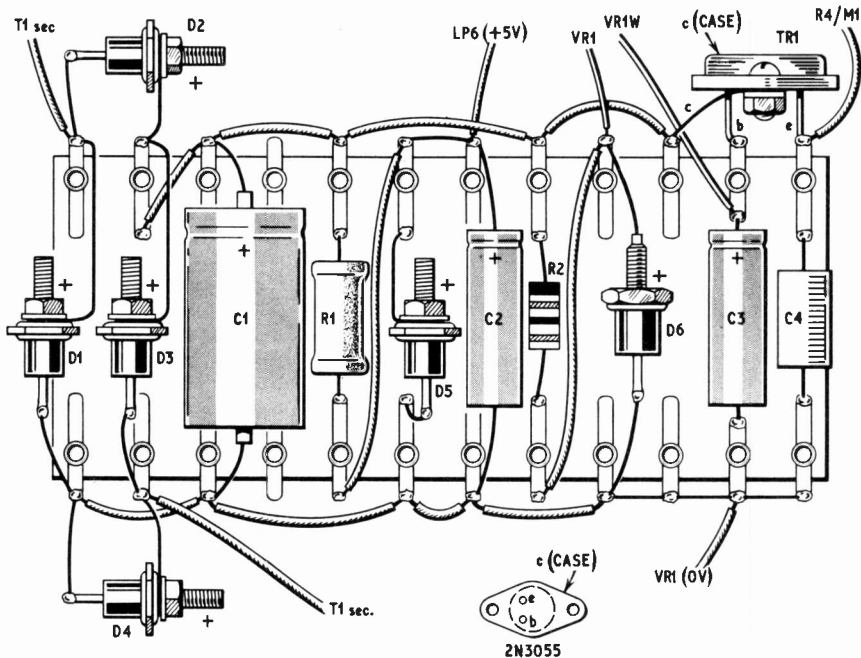


Fig. 6. Assembly and wiring details of power supply unit. Both this and the mains transformer are mounted on the chassis base plate (see photograph below)

The power unit is constructed on a 12-way piece of standard tag-board as in Fig. 6. Since TR1 is operating well within its capabilities, no heat sink is required, and it is soldered directly to the tags.

The unit is mounted on the chassis base by means of 6B.A. bolts and suitable spacers to ensure that all the components are isolated from the case. The mains transformer is also mounted on the base. The relative positioning of these units can be seen in the photograph.

The pulse generator (Fig. 7) and the lamp amplifiers (Fig. 8 and Fig. 9) are built on pieces of 0.1in matrix perforated board. Most of the wiring utilises the component leads which are passed through the board and soldered together as required.

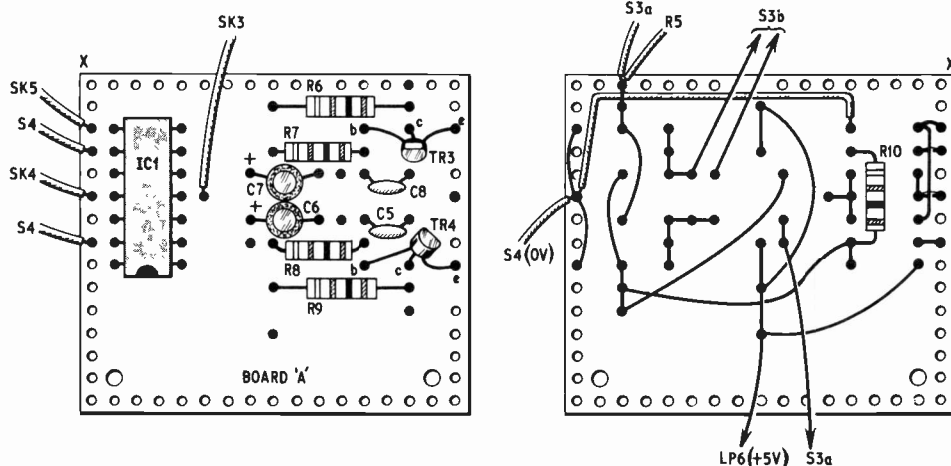
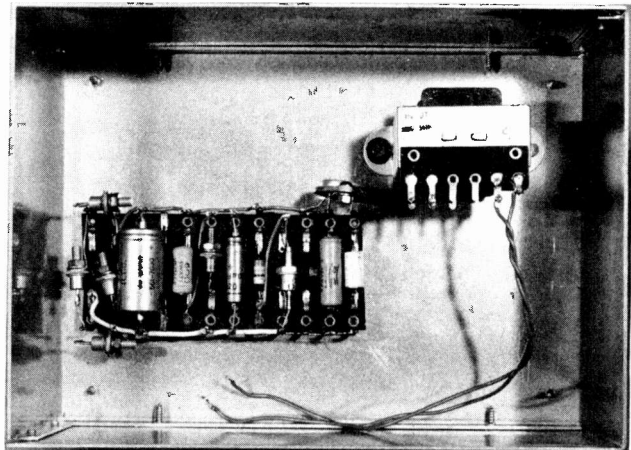


Fig. 7. Assembly and wiring details of pulse generator (Board 'A'). Verpins should be used where connecting flying leads

COMPONENTS . . .

Resistors

R1	60 Ω , 5W	R7	22k Ω
R2	68 Ω , $\frac{1}{2}$ W	R8	22k Ω
R3*	See text	R9	1k Ω
R4*	See text	R10	390 Ω
R5	4.7k Ω	R11-R14	4.7k Ω (4 off)
R6	1k Ω		

All 10%, $\frac{1}{4}$ watt carbon except where stated.

Capacitors

C1	1,000 μ F	elect.	25V
C2	250 μ F	elect.	10V
C3	100 μ F	elect.	15V
C4	0.22 μ F	polyester	
C5	470pF	polystyrene	
C6	16 μ F	elect.	10V
C7	16 μ F	elect.	10V
C8	470pF	polystyrene	

Potentiometers

VR1 470 Ω

Diodes

D1-D4	1N4001 or RS30AF (4 off)
D5	ZX5-1 5.1V, 10W, Zener
D6	ZL12 12V, 1.5W Zener

Transistors

TR1	2N3055
TR2-TR8	2N2926 (G) (7 off)

Integrated Circuit

IC1 SN7400N

Switches

S1	Double pole, mains on/off
S2	S.p.c.o., biased toggle
S3	D.p.c.o., slide
S4	S.p.c.o., biased toggle
S5-S20	Double-pole, 6 way, break-before-make 'Maka-switch' wafers (Radiospares) (16 off)

Miscellaneous

T1 Mains transformer, 12V 1A Secondary, M1—1mA moving coil meter $1\frac{1}{2}$ in square face, SK1, SK2 Insulated terminals, FS1—100mA fuse with panel fuseholder, LPI—Mains neon. LP2-LP6 Panel Mounting M.E.S. lamp holders with 6V, 0.06A bulbs (5 off). SK3-SK9 Miniature sockets with miniature single pin plugs to suit (9 off) (Radiospares). SK10-16 way, 'Dual-in-line' socket (Radiospares), Aluminium, 8B.A. threaded rod, washers, spacers. SK11-SK26 miniature sockets (16 off) (Radiospares).

The boards are mounted on the front panel with small brackets.

SWITCH ASSEMBLY

All the other components of the instrument are mounted on the front panel and present no great difficulty, except, that is, the 16 four-way switches S5 to S20 of Fig. 4.

In spite of considerable efforts, the author was unable to track down any suitable commercial items for this job. Ordinary wafer switches could perhaps have been used, but were rejected since a row of eight would require a panel space of some 10in. Finally, the two switch banks were constructed from 16 Radiospares 'Maka-Switch' wafers, each bank requiring only $3\frac{1}{2}$ in of panel space.

First, switch levers are cut from Paxolin or similar material, and a hole drilled at one end (Fig. 10). This hole should be countersunk deeply so that the screw head is flush with the surface of the material. Also, when the lever has been bolted to the wafer, the excess bolt length should be cut off and filed flush with the nut, because there is very little space between the wafers.

Next, the brackets should be made up (Fig. 11) and the wafers, together with the washers and spacers, should be assembled on threaded rods before finally bolting the whole lot firmly together to form a rigid unit. Note that the unused tags on the side of the wafers that are towards the front panel must be bent over otherwise they will foul it.

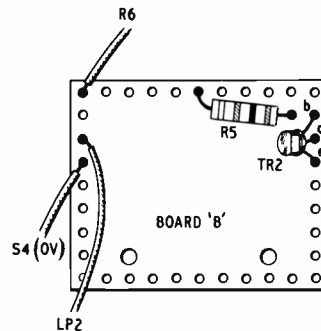


Fig. 9. Assembly and wiring detail of pulse generator lamp amplifier (Board 'B'). Clad Veroboard is used for this with none of the copper strips cut

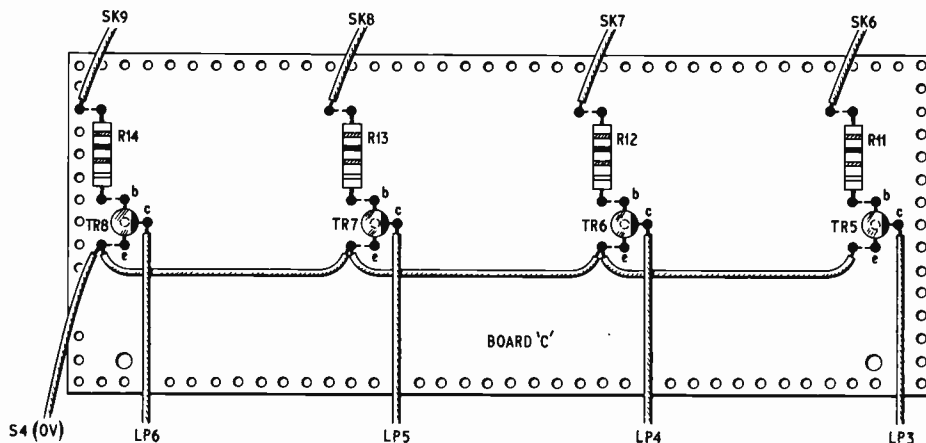


Fig. 8. Assembly and wiring details of function lamp amplifier (Board 'C')

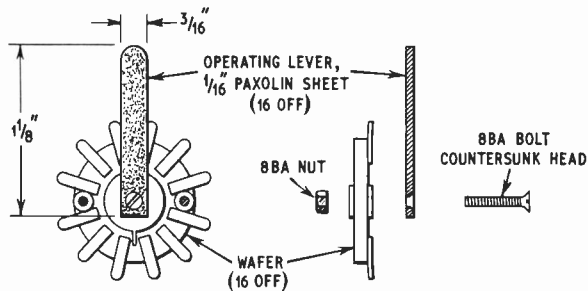


Fig. 10. Assembly details of switch levers

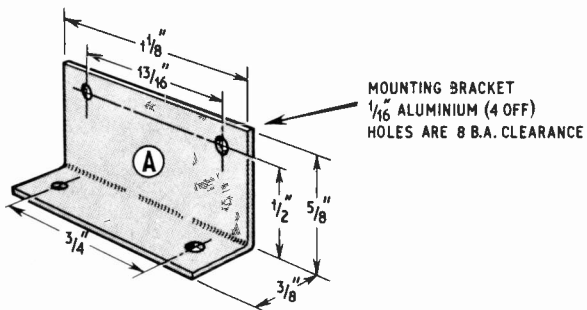
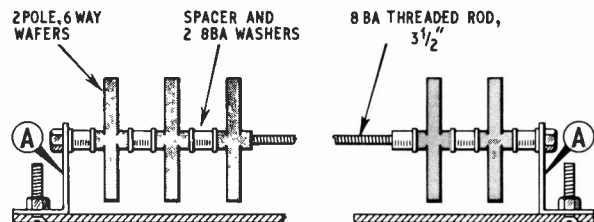


Fig. 11. Showing how eight switch wafers are assembled in a single unit. Two such banks are required


FRONT PANEL ASSEMBLY

The front panel of the case can now be cut and drilled. A suitable layout is illustrated in Fig. 12, but it is emphasised that this is not critical and may be modified to suit available components. For the same reason, drill sizes are not given, although it is recommended that the specified sockets are used for the patch-cords, in which case the holes should be 2B.A. clearance.


The only part that needs fairly accurate work is that concerned with the switch units, and the quoted dimensions should be followed closely or the switch levers may not pass freely through the slots. When the wafers are used in this way, the usual indexing employed in wafer switches is not present, and it may be thought that difficulty would be experienced in finding the correct positions. In fact, the wafer contacts are quite a tight fit on the moving contact and it is very easy to feel when the lever is in the correct position.

Before the components are finally mounted on the panel, it is a good idea to paint it and add the legends. The author used a matt white spray and added the lettering with Letraset, which gives a very neat appearance.

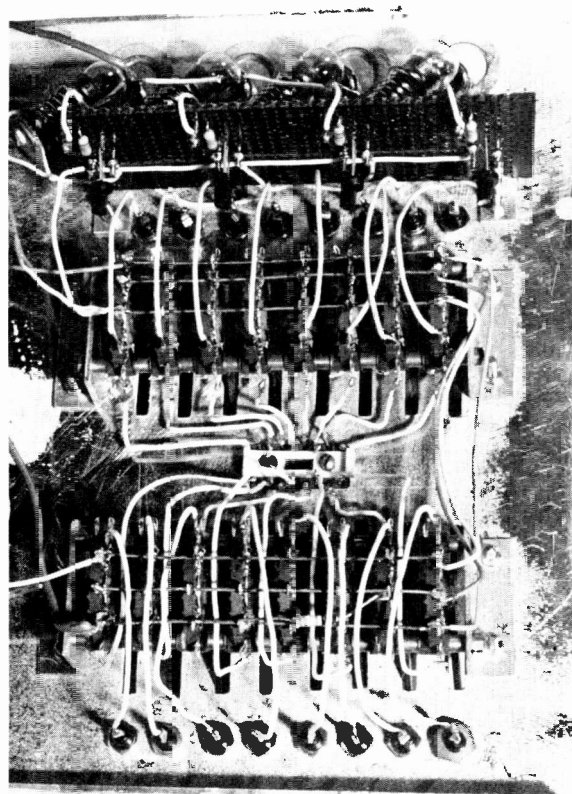A coat of Letraset protective lacquer will prevent the letters being rubbed off.



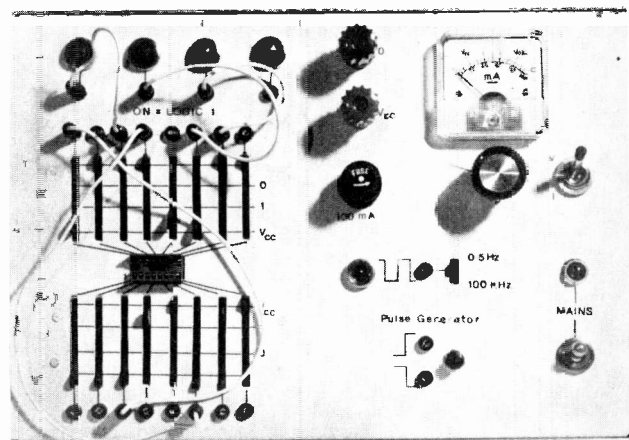Switch banks in position. Here and in Fig. 13 some of the wafers in the lower switch banks have been reversed which accounts for asymmetric wiring. Ideally all wiring should follow the pattern of Fig. 4b. The unused underside wafer tags should be bent back to prevent chassis fouling



The completed front panel with all the legends in position and fixed with a protective lacquer

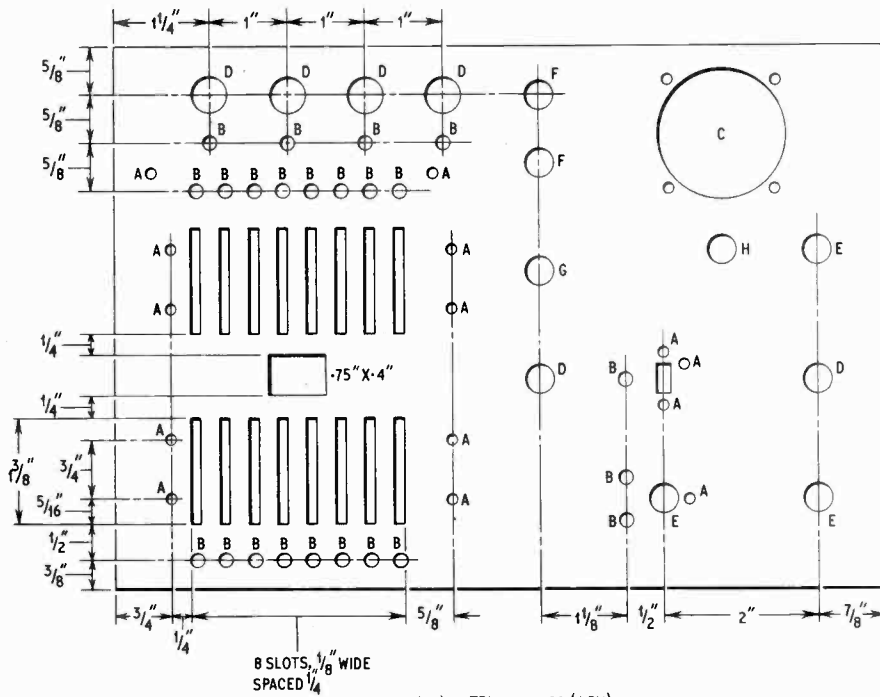


Fig. 12. Drilling details for the front panel of the tester

DRILLING DETAILS

- A — 8BA Clearance
 - B — 2BA Clearance
 - C — Panel Meter
 - D — Panel Lamps
 - E — Supply Switches
 - F — Supply Terminals
 - G — Fuseholder
 - H — Supply Potentiometer
- Holes C — H to suit components used


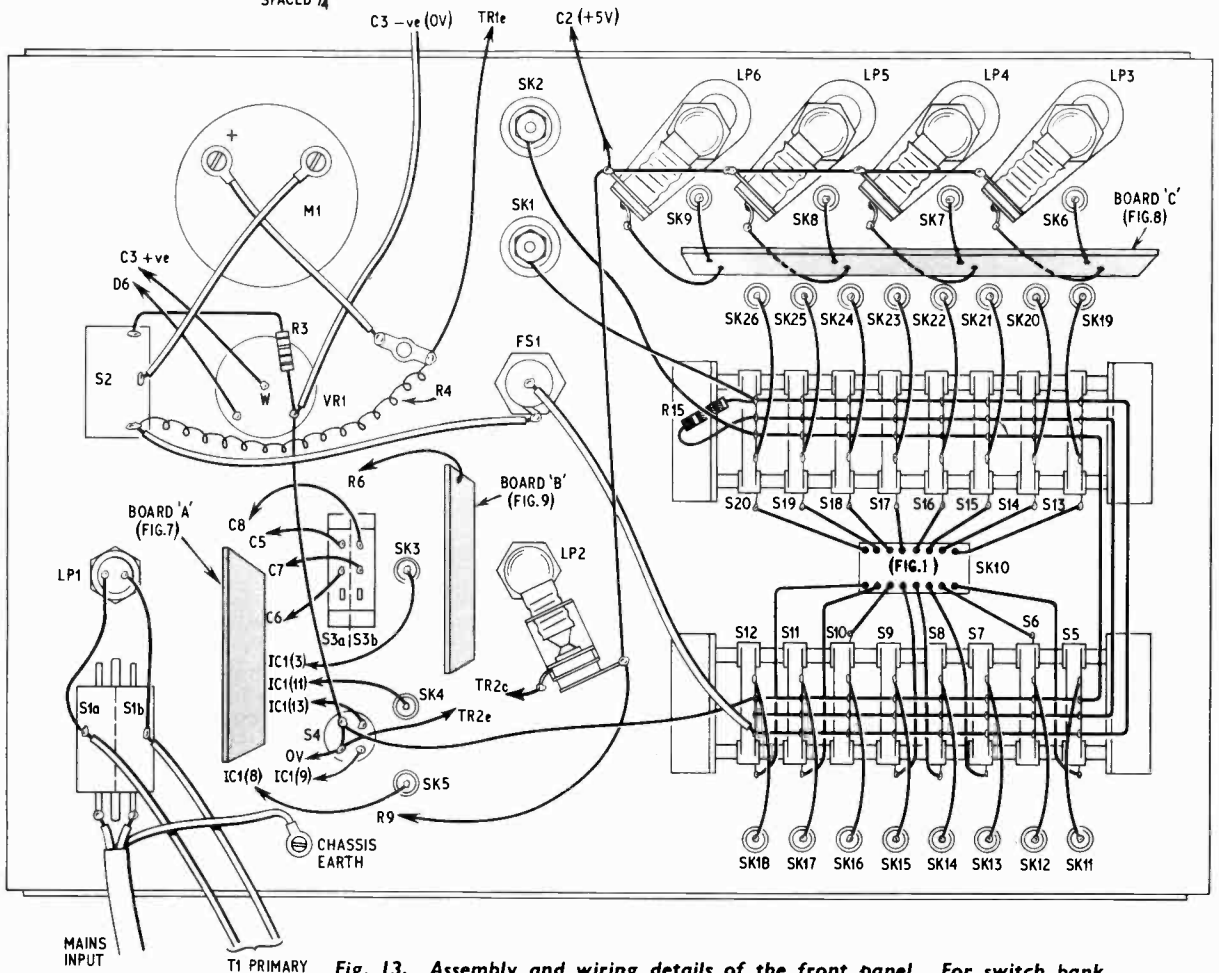


Fig. 13. Assembly and wiring details of the front panel. For switch bank wiring see also Fig. 4. Note that meter positive and shunt terminate at a stand-off insulator

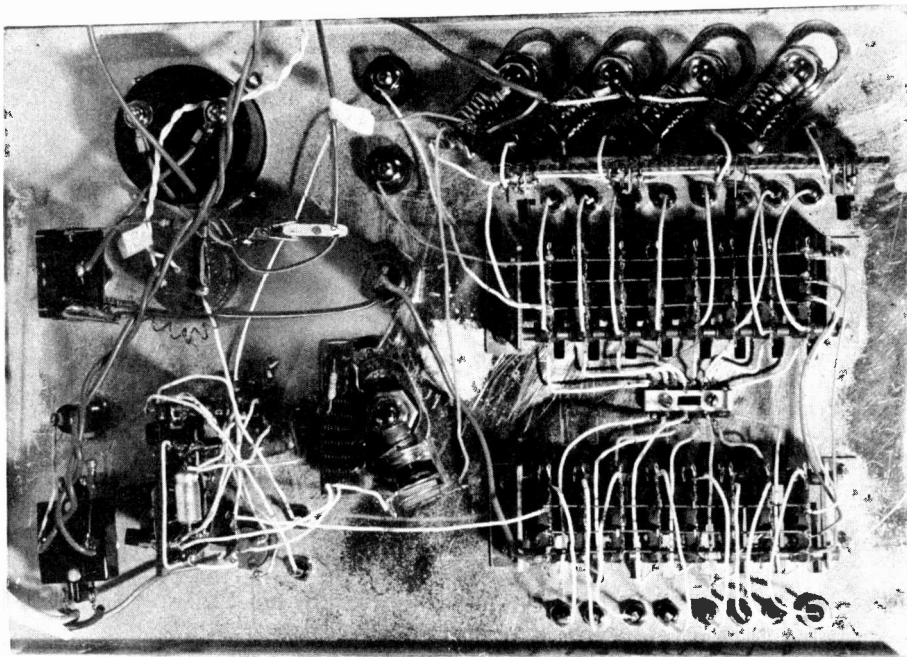

PANEL WIRING

The wiring of the panel is shown in Fig. 13. Reference should be made to Fig. 4b when wiring the switch banks as all connections should follow this pattern.

The mains cable is led in through a hole in the back of the case which should be fitted with a grommet to prevent damage to the insulation. This cable is wired directly to the mains switch S1, with the earth lead being anchored to the case by a solder tag fixed with a nut and bolt. Note that no other part of the circuit should be connected to the case.

The leads from the power unit are made longer than necessary so that it is possible to work on the panel wiring.

Values of the meter shunt and multiplier resistances must be found by experiment, for which a multimeter is required. First check that the power unit is working correctly before it is connected to the rest of the circuit. The potential at the junction of R1 and D5 is about +5 volts with respect to the 0 volt line. The potential at the emitter of TR1 should next be measured, and it should vary from 0 to a maximum of some +10 volts as VRI is turned from one extreme to the other.

Complete the wiring and connect the multimeter across V_{CC} and 0 volts. With a $10k\Omega$ resistor temporarily wired in for R3, check that the two meters give the same reading. If the meter reads low, reduce the multiplier and vice versa, until agreement between the two meters is obtained.

To find the value of the shunt resistor R4, the multimeter and a resistor of about 500 ohms should be connected in series across the V_{CC} and 0 volt lines with V_{CC} set at about 5 volts. A short piece of electric fire element resistance wire, say 2in, is temporarily connected across the meter. S2 is switched to the current position and the unit is

switched on. The multimeter should now read about 10mA, while the instrument meter will probably be giving a very low reading.

The length of the resistance wire should be gradually increased until the two meters give the same reading, then the shunt can be permanently wired into place.

CHECK OUT

Some patch-cords should be made up, say four about 3in long and six about 10in. Since it is occasionally necessary to make two connections to a socket, it is convenient to have two or three cords with a plug at one end and a loop, just large enough to fit over the plug pin, at the other.


The pulse generator and lamp amplifiers can now be checked. Switch on, and the slow speed operation of the pulse generator will be obvious by the indicator lamp LP2 pulsing. The high speed operation will require an oscilloscope, plugged into socket SK3, to follow its operation.

The manual pulse can be checked with the meter; a patch-cord from SK1 to either SK4 or SK5 will give a meter reading of about 2.5-3 volts, changing to 0 volts (or vice versa) as S4 is switched.

The lamps should turn on by connecting a patch-cord between SK1 and, one by one, the sockets SK6 to SK9.


THE INSTRUMENT IN USE

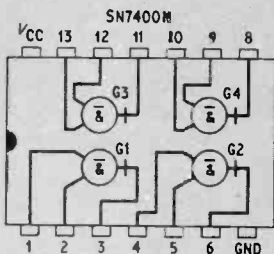It is not possible to lay down hard and fast rules for a tester of this type, since a test schedule must be devised for each type of i.c. to be examined. It follows that the type of i.c. must be known—unmarked devices are virtually useless. Once the type is known, its function, pin connections and truth table can be determined and appropriate tests worked out.




TRUTH TABLE EACH GATE		
INPUTS		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

Fig. 14. Pin diagram and truth table of a SN7400N quad two input gate. Note that this is a top view of the package

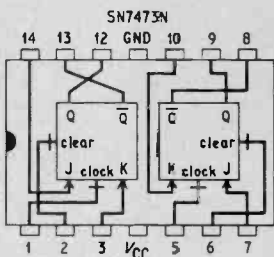

TRUTH TABLE EACH FLIP-FLOP		
J	K	Q
0	0	Qn
0	1	0
1	0	1
1	1	Qn

Fig. 15. Pin diagram (top view) and truth table for a SN7473N dual J-K flip-flop

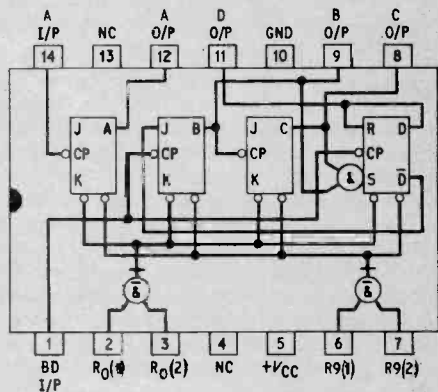

COUNT	OUTPUTS A B C D
0	0 0 0 0
1	1 0 0 0
2	0 1 0 0
3	1 1 0 0
4	0 0 1 0
5	1 0 1 0
6	0 1 1 0
7	1 1 1 0
8	0 0 0 1
9	1 0 0 1

(a)

COUNT	OUTPUTS B C D
0	0 0 0
1	1 0 0
2	0 1 0
3	1 1 0
4	0 0 1

(b)

COUNT	OUTPUTS A B C D
0	0 0 0 0
1	1 0 0 0
2	0 1 0 0
3	1 1 0 0
4	0 0 1 0
5	1 0 1 0
6	0 1 1 0
7	1 1 1 0
8	0 0 0 1
9	1 0 0 1

(c)

Fig. 16. Pin diagram (top view) and truth tables for an SN7490N decade counter

It is a wise precaution first to ensure that there is no internal short circuit across the supply pins. To do this, the device should be plugged into the test socket SK10, the appropriate pin switches set to 0 and V_{cc} , and the supply voltage increased slowly from 0 while monitoring the current. If all is well, the test can proceed.

To illustrate the method of use, detailed test procedures for three TTL devices from the currently available range will be given.

QUAD TWO-INPUT GATE

The pin diagram of a SN7400N quad two-input gate and truth table are shown in Fig. 14.

First set pin switch S11 (i.e. pin 7 of the i.c.) to 0 and S13 (pin 14) to V_{cc} . Check for a short circuit. Set all gate inputs to 0, that is, S5, 6, 8, 9, 14, 15, 17 and 18, and connect a patch-cord from the output of gate 1 (SK13) to one of the indicator lamps.

It is a wise precaution in this, and all other tests, to start with all the switches in the outside position, and only move those where a pin is to be connected to 0, logic 1, or V_{cc} . This will ensure that no pin will have the wrong voltage applied to it, and that when a patch-cord is used, it will automatically be connected to the corresponding i.c. pin.

To continue with the testing of gate 1, pin switches S5 and S6 should now be operated so as to apply 0/0, 0/1, 1/0 and 1/1 levels in turn to its inputs, pins 1 and 2. The truth table tells us that the lamp should remain on for the first three pairs of inputs, and turn off at the fourth. If any other response is observed, then the gate is faulty.

Now move the patch-cord to the outputs of the other three gates in turn and repeat the procedure with the appropriate input switches. Of course, should one or more of the gates prove to be faulty, it does not mean that the i.c. has to be discarded, for the other gates can still be used.

It is a good idea to cut off the pins of any faulty gates to make sure that they are not accidentally wired into a circuit.

The tester may also be used to demonstrate some possible applications of these gates. For example, if one of the inputs to a gate is connected by a patch-cord to SK3 of the pulse generator, it can be shown that the gate will pass the clock pulses when its other input is at 1, but will block them if it is at 0.

It will also be noticed that the clock pulses are inverted by this arrangement, and that by connecting the output of this gate by a patch-cord to both the inputs of another gate, the output of the second gate follows exactly the clock pulse.

DUAL J-K FLIP-FLOP

The pin diagram and truth table for an SN7473N, dual J-K flip-flop are shown in Fig. 15.

Set the pin switch S16 to 0 and S8 to V_{cc} and carry out the usual short circuit test. Before testing of this and related flip-flops can begin, it is important to note that the truth table only applies if the clear (and preset, if present) input is at a logical 1. The clear input overrides all others, and if it is at 0, the Q output will be forced to 0, irrespective of the states of any other input. Thus S6 and S10 should first be set to 1.

Set J and K (S13 and 7) to 0 and connect a patch cord from SK11 to SK4 of the pulse generator.

Line 1 of the truth table tells us that if J and K are both 0, the flip-flop does not change state on receipt of a clock pulse, so that operating S4 will simply leave the output in its initial form.

It is perhaps helpful to connect both the Q (SK21) and the \bar{Q} (SK20) outputs to the indicator lamps and verify that they are always in opposite states.

Moving to the second line of the truth table, set K to 1 and operate S4. Whatever its initial state, Q should now go to 0, and remain there for subsequent clock pulses. Set J to 1 and K to 0 and verify that Q now goes to 1 and stays there (line 3).

Finally, set both J and K to 1; line 4 tells us that after a clock pulse, Q will be in the state opposite to that before the clock pulse, in other words, the flip-flop will divide by two. The second flip-flop should now be checked in exactly the same way.

As with the SN7400N, we can also demonstrate a simple application of the SN7473N. Set J and K of both flip-flops to 1; connect a patch-cord from the Q output (SK21) of the first to the clock input of the second (SK15), and one from the pulse generator (SK3) to the clock input of the first (SK11). The combination will now divide by four, and an indicator connected to the Q output of the second flip-flop (SK24) will turn on once for every four clock pulses.

If a double beam oscilloscope is available, this can also be demonstrated at the fast pulse rate by connecting one beam to the pulse generator, and the other to the output of the second flip-flop. The 0 volt terminal should be used for the earth return to the oscilloscope.

DECADE COUNTER

The SN7490N decade counter is included as an example of medium scale integration, that is, a device containing several individual circuits interconnected so as to carry out a complex function, all in one package.

In the case of the SN7490N, four flip-flops and some additional gating are wired so as to provide a complete decade counter, with the full binary coded decimal count available at its outputs. In order to increase its versatility further, the counter is in two parts, a divide by two and a divide by five section, which may either be used separately or externally connected for use as a divide by ten unit.

The pin connections and truth tables are shown in Fig. 16, and each mode of operation will be checked in turn.

First, set S9 to V_{CC} , S17 to 0 and carry out the short circuit check. Install patch-cords from the four outputs to the indicator lamps so that the A output (SK21) goes to the left-hand lamp, the B output (SK24) goes to the next and so on—the lamps now correspond to the order shown in the truth tables.

The counter has two reset modes, each one having two AND-gated inputs. To reset the counter to 0, both the R_0 inputs must be at a logical 1, so if S6 and S7 are set to 1, none of the lamps should be on.

The counter may also be reset to binary nine, i.e. 1001, so if both S10 and S11 are set to 1, the first and last lamps should be on.

As in the case of the J-K flip-flop, these reset inputs override all others so that the truth tables will only be followed if at least one of each pair of reset inputs is at a logical 0. The two sections of the SN7490N will now be checked individually.

TWO SECTION CHECK

By connecting a patch-cord from SK5 of the pulse generator to the A input (SK19), the A output should change state once for every two input pulses. Change the input pulse to the BD input (SK11) and the B, C, and D lamps should now follow the truth table of Fig. 16b, that is, the D output gives one pulse for every five input pulses.

In order to check the full decade count, the A output must be connected to the BD input, and input pulses applied to the A input; the counter should now follow the truth table shown in Fig. 16a. It can be seen that the D output provides 1 output pulse for every ten input pulses.

The usefulness of the two-gated reset inputs may be demonstrated in the following way. Install patch-cords from the B and C outputs (SK24 and 25) to the R_0 inputs (SW12 and 13), the remaining connections being as for the decade count. Now when the count reaches six, i.e. binary 0110, both reset inputs will be at 1 and therefore force the counter to reset to 0, skipping the rest of the decade count sequence.

This is shown in the truth table of Fig. 16c, from which it can be seen that a divide by six function is available at the B or C outputs.

Other division ratios may also be obtained on the same way, providing the required ratio does not have more than two 1's in its binary number.

The above examples have shown how a test schedule may be devised for any one of three widely different types of TTL i.e. Using the same techniques, the reader may readily devise suitable tests for any of the currently available TTL devices, and with only minor modifications, devices of the RTL and DTL ranges. ★

PRACTICAL ELECTRONICS

● SUBSCRIPTION RATE

With effect from this issue (May 1971) the new Subscription Rate is £2.65 (£2 13s 0d) for 12 issues, including postage to any part of the world.

● INDEX

An index for volume six (January 1970 to December 1970) is now available price 7½p inclusive of postage.


Orders for copies of the Index *only* should be addressed to the Post Sales Department, IPC Magazines Ltd., Carlton House, 66 Gt. Queen Street, London, W.C.2.

● BINDERS

Easi-binders with a special pocket for storing booklets and data sheets, etc., are available price 73p inclusive of postage.

State required volume, e.g., Vol. 1, 2, . . . 7.

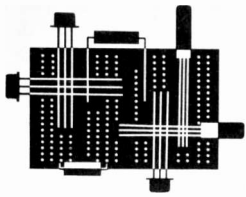Orders for Binders *and* Indexes should be addressed to the Binding Department.



F.E.T. VOX

A VOICE OPERATED SWITCH FOR THE BEGINNER

In this series every effort has been made to permit the continued use of the same semiconductor devices in the projects devised since the T-Dec, plug-in assembly method, makes for easy retrieval of parts if no permanent fabrication is intended.

This article is no exception as the entire semiconductor complement has previously been called up, one of these being the 2N3819 field effect transistor.

MATCHING

Designing a voice operated switch, or more commonly, a Vox, calls for a high input impedance preamplifier if a crystal microphone is to be used. In the circuit of Fig. 1 the 2N3819 *n*-channel f.e.t., TR1, is used in the first stage to match the high input impedance of the microphone X1.

This transducer has an output impedance of a few megohms and to connect this into a preamplifier of low input impedance would result in both a sacrifice of frequency response and an effective decrease in microphone sensitivity.

EQUIVALENT CIRCUIT

To understand why this should be look at Fig. 2. This gives the equivalent circuit of a crystal microphone which is, in effect, a voltage generator when excited, with internal resistance *R* and capacitance *C* which is typically a few hundred picofarads.

The load it is working into is indicated by the impedance *Z*.

With the arrival of sound waves the generator produces signal voltages which will divide according to the impedance proportions of the microphone and load. If *Z* is large compared to the microphone impedance most of the voltage developed appears across the load so the microphone can be said to be working efficiently.

At medium and high frequencies the capacitive element plays very little part in contributing to the microphone impedance, but at bass frequencies, because reactance varies inversely with frequency this addition becomes significant, so once again a high impedance load is important, but this time for a good low frequency response.

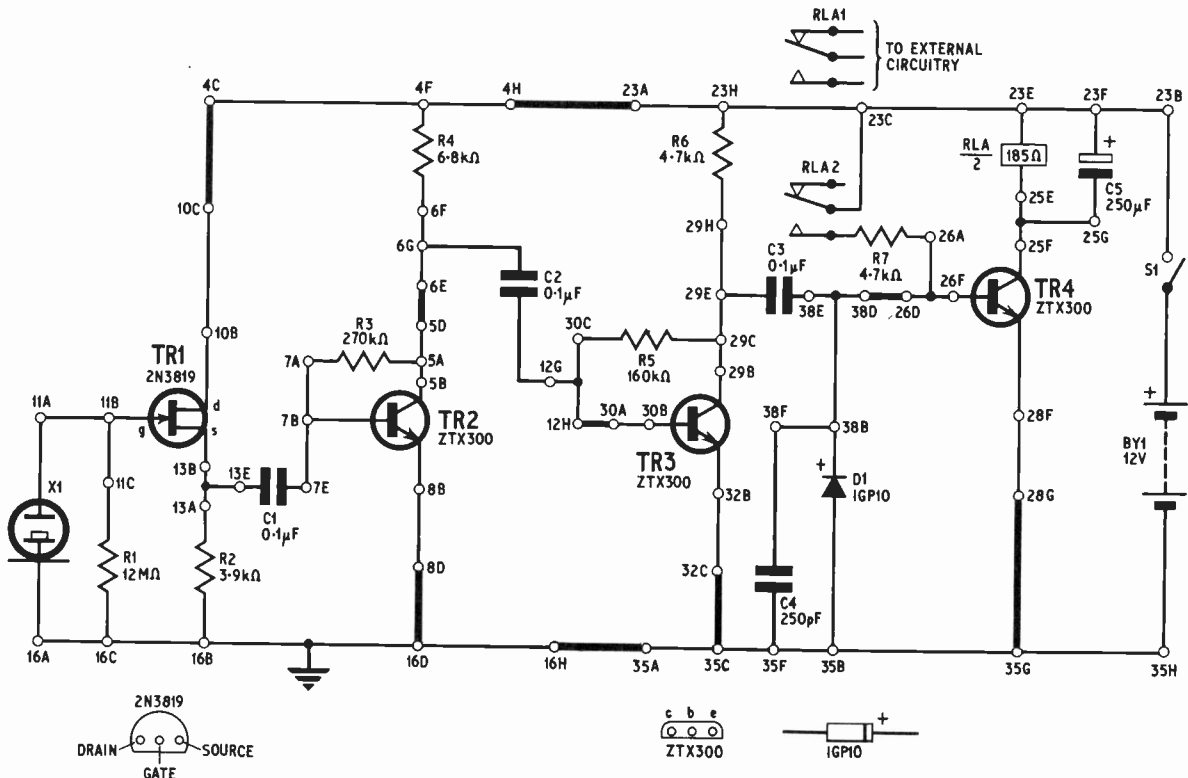


Fig. 1. Circuit diagram of the voice operated switch

SOURCE FOLLOWER

The gate resistor R1 (Fig. 1) provides the high input impedance requirement as the gate to source current of TR1 is exceedingly small, in the order of nanoamperes (10^{-9} A).

The function of the f.e.t. stage is to act as a transformer, impedance matching the microphone X1 with the low input impedance of TR2. This source follower, so called because the output at R2 "follows", in phase, the input, feeds TR2 the first of a pair of simple cascaded amplifiers.

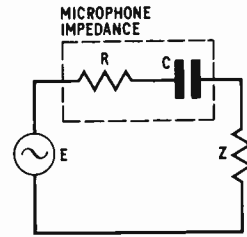


Fig. 2. Equivalent circuit of crystal microphone working into a load Z

Components . . .

Resistors

R1	12M Ω	R5	160k Ω
R2	3.9k Ω	R6	4.7k Ω
R3	270k Ω	R7	4.7k Ω
R4	6.8k Ω		
All 10% $\frac{1}{2}$ watt carbon			

Capacitors

C1	0.1 μ F polyester
C2	0.1 μ F polyester
C3	0.1 μ F polyester
C4	250pF mica
C5	250 μ F elect. 15V

Semiconductors

TR1	2N3819
TR2-TR4	ZTX300 (3 off)
D1	1GPI0

Microphone


X1 Crystal insert Type MCI (Henry's Radio)

Relay

RLA 2 Pole 2 way Type PC2 CBB/12 (Henry's Radio)

Miscellaneous

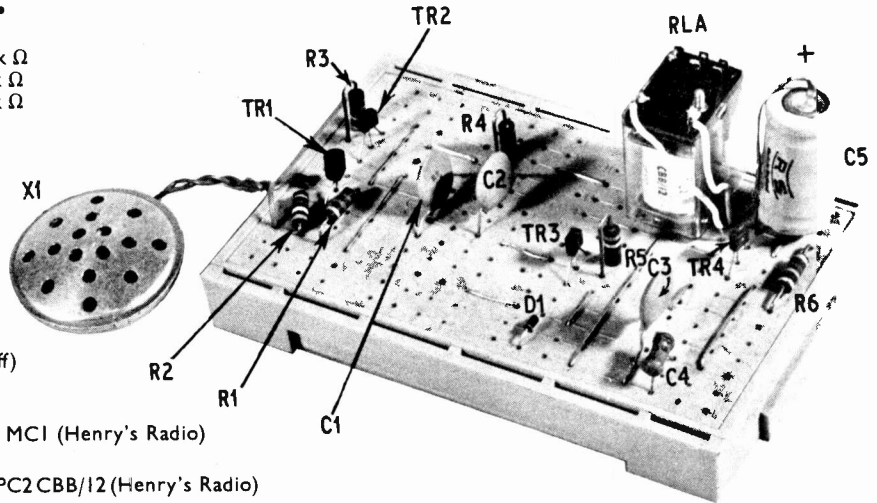BY1—12V (Two PPI 6V batteries). T-Dec, connecting wire, S1—on/off toggle switch



Overall gain over the three stages is about a 1,000 when TR3 is not loaded. The inclusion of the relay driver, TR4, does reduce this figure but the output is more than adequate to drive it.

CLAMPING DIODE

When a waveform is passed through a capacitor any d.c. level which might have been part of it is blocked. This means that signals passing across C3 are equally balanced about earth.

To get back a positive d.c. level necessary to switch TR4, diode D1 clamps the base of the alternating quantity to ground to provide a fluctuating d.c. quantity. The introduction of a reservoir capacitor before the base of TR4 for smoothing would, in fact, reduce this level, so instead an electrolytic capacitor is connected across the relay to provide a positive contact action.

With a high input sensitivity of less than 0.1mV r.m.s., and high input impedance it is inevitable that stray noise, produced by radiation influences, might well be troublesome.

In the prototype this problem was eliminated by the bypass capacitor C4. Under conditions of test, the Vox was surrounded by mains operated test equipment and not once was there any spurious activation.

If other construction methods are attempted the important thing is to keep all wiring short and direct to lessen the chance of stray noise pickup.

Ideally, the unit should be contained in a metal box screen with this properly earthed.

APPLICATIONS

Whilst many applications of the Vox may occur to the constructor, the most obvious is its use as a baby alarm or a voice command switch for the remote switching of lights or equipment.


The current consumption on standby is only 2mA so it is very economical. In terms of sensitivity, the relay will act when the microphone is four feet away from a low voiced conversation, so it is well suited to the aforementioned uses.

The relay specified is a two pole, two way type and for command switching it will be necessary to use a pair of these contacts for latching TR4 on. In Fig. 1, RLA2 is used for this with R7 as the biasing resistor. The other set of contacts, RLA1, should be routed to whatever alarm indicator is chosen, whether lamp or bell.

If this facility is used, switch S1 must be added so that the Vox can be restored to its quiescent state.

For impact photography, a flash-gun can be connected to RLA1 contacts. The Vox now takes the role of a flash trigger where action can be frozen photographically at the moment of impact.

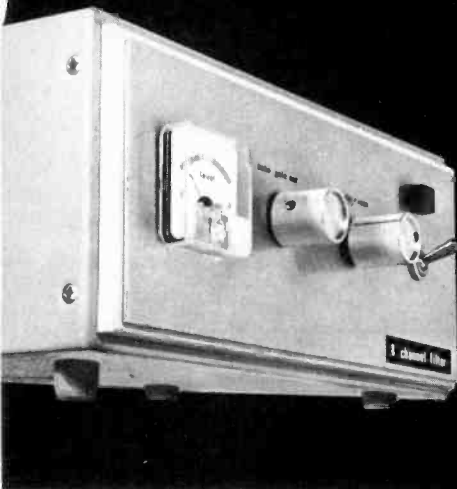In this last application it should be noted that the range of the Vox is very much increased with impulsive sounds such as bangs, whistles or horns which should point the way to some other uses.



P.E. AURORA



MUSIC INSPIRED LIGHT AND COLOUR PART 2 LAMP CONTROLLER

By M.J. HUGHES M.A.

THIS second part continues the description with construction and setting up details of the thyristor lamp controller. It was mentioned last month that either straight operation with eight lamps can be achieved with this design, or a more ambitious sixteen lamp matrix system using the same amount of electronic circuitry.

It is assumed that most constructors would like to experiment with the matrix, thus the constructional part of this article shows four thyristors mounted with common cathodes and four with common anodes. In-line operation of eight channels can still be effected although one has to be careful with the connections of mains line and neutral, see Fig. 10 later.

CONSTRUCTION

To facilitate stage-by-stage construction, and possible expansion of the system later, all circuits

are mounted on individual cards which are assembled together in a Contil cabinet. Layout presents no special problems as there are few parts of the system which interact. While it would be fairly straightforward to design printed circuit boards for the various stages, perforated s.r.b.p. board or Veroboard is quite suitable. Only three different circuit boards are required for the lamp controller.


- (a) Power supply and sync pulse generator, Fig. 8 (1 required);
- (b) Trigger circuits, Fig. 9—each board carries two channels (4 required);
- (c) Thyristor arrays, Fig. 10 (2 required).

Layout of the Veroboard has been arranged so that the minimum number of strips have to be cut. All the boards should be wired up except the flying lead interconnections (shown in Fig. 11 as looms); these will be added during the final assembly into the cabinet.

SYNC PULSE GENERATOR

It is suggested that this unit is built first as it can then be used to check the functioning of the other boards. Fig. 8 shows the layout; there are no special problems to be encountered with this part of the circuit except the general point about 0·1in matrix-board. It is imperative that care is taken to prevent solder running between strips as short circuits can be disastrous.

The unit can very quickly be checked out by wiring up to the mains transformer and making sure that +15V is present at point 39A. If the reader has an oscilloscope it is worth checking the waveforms at points 6J, 8C and 39P, which should be as shown in Fig. 4b, c, and d respectively, except that as the unit is not on load the waveform at the collector of TR1 will have a much faster rise time with an amplitude of approximately 10V. The unit should be left wired up to the transformer as it will form a useful power source for testing the trigger channels later.

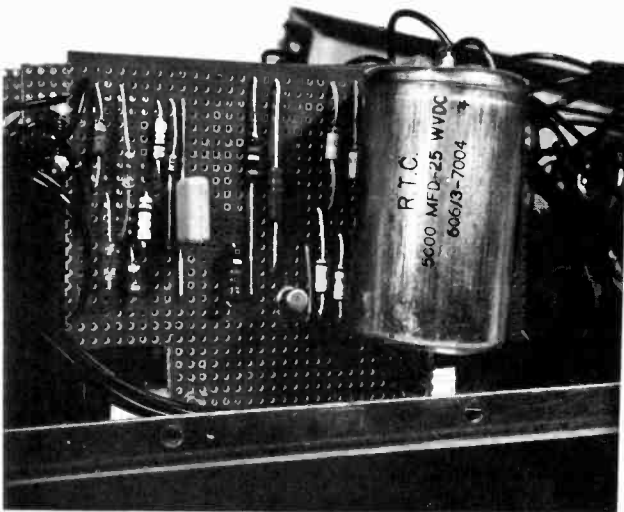

LAMP CONTROLLER

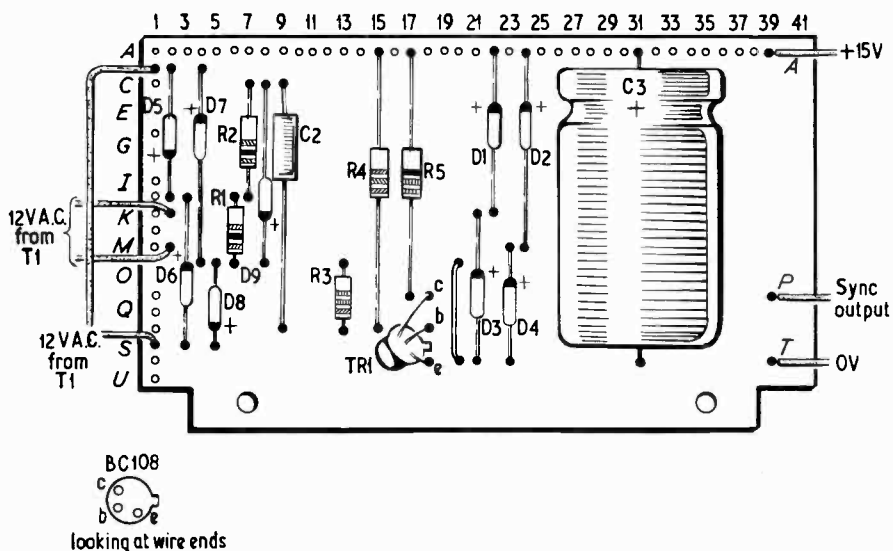


Fig. 8. Layout of components on 0-line matrix Veroboard for the power supply and sync pulse generator. No copper strips are cut. Do not connect the zero volts line to chassis.

COMPONENTS . . .

POWER SUPPLY AND SYNC PULSE GENERATOR

One of each of following except where stated

Resistors

- R1 1k Ω
- R2 1k Ω
- R3 5.6k Ω
- R4 100k Ω
- R5 2.7k Ω
- All $\pm 10\%$, $\frac{1}{4}$ watt carbon

Capacitors

- *C1 0.47 μ F polyester 1,000V
- C2 0.1 μ F polyester 125V
- C3 5,000 μ F elect. 25V

Transformer

- *T1 Mains transformer, Primary 230-250V; secondary 1 12V 500mA min; Secondary 2 12V 500mA min.

Inductors

- *L1, L2 Wound on Ferrite ring cores or pot cores —see text (2 off)

Transistor

- TR1 BC108 or any medium gain npn silicon transistor

Diodes

- D1 to D4 1N4004 (4 off) or 25V 1A min. rated bridge rectifier
- D5 to D 8 OA91 (4 off) or any small signal germanium diodes 25V min.
- D9 1N4148 or any small signal silicon diode 25V min.

Switch

- *S1 Double pole, on/off toggle switch

Lamp

- *LPI Neon indicator with ballast resistor for 250V a.c. mains


Fuse

- *FS1 5 amp cartridge fuse and fuseholder

Miscellaneous

- *Veroboard 0-line matrix $4\frac{1}{2}$ in \times $2\frac{3}{4}$ in
- *Component tag board for C1, L1, L2

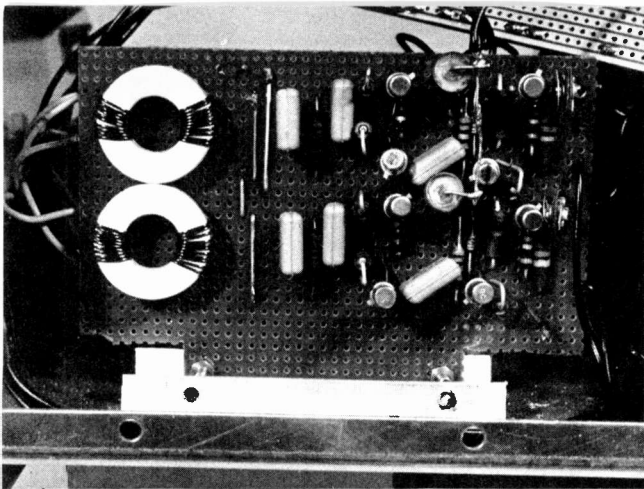All components above mounted on Veroboard A (Fig. 8) except those shown (*) which are mounted on chassis or case (Fig. 11)



TRIGGER UNITS

In this system, eight trigger channels are shown, but readers have the option of making the system smaller or larger. Fig. 9a shows the layout of a single board which carries two complete trigger channels (with the exception of the thyristor or triac). It is possible to split the circuitry into the two separate elements at the dotted line if a smaller system is wanted.

Before starting to wire up the components ensure that all the strips are cut in the correct places and take particular care that all the copper is removed between the primary and secondary connections of the pulse transformer (T2). Note that both *pnp* and *nnp* transistors are used on this board—both types specified are in TO-18 cans and it is easy to make an error by picking up the wrong device. There is quite a high packing density of components on this board so is it particularly important that all soldered joints are perfect and that there are no runs of solder. Remember that the transistor cans are connected to their collectors and should not be allowed to touch each other or any nearby wiring or components.

PULSE TRANSFORMERS

The pulse transformers (T2) are extremely simple to wind; it is worth making all these up at one time as an epoxy resin is used to hold the windings firm, and this will take some time to harden. Fig. 9b shows the winding details.

Ring cores were chosen owing to their low cost and high efficiency: some cores have a thick tough coating of insulating material which is adequate to give full protection. If during the course of winding this coating gets chipped or cracked (or if there is the slightest degree of doubt over the quality of the coating) at least two layers of good quality p.v.c. tape should be wound round the core before the windings are applied.

Adjacent turns of each winding should just touch but primary and secondary windings should be separated from each other by positioning them diametrically opposite. If any other form of ferrite core is used (see components list), ensure that the insulation between primary and secondary is adequate. Ferrite pot cores large enough to take the windings can be used, making sure that insulation is provided. The magnetic properties of the

cores are not critically important, so any type will probably suit.

It should be noted that one end of C4 is left floating. On final assembly this capacitor on each channel is commoned to the output of the sync pulse generator. On no account should the zero line be connected to chassis, otherwise problems may be experienced when connecting to audio equipment.

SETTING UP

Each circuit on this board can be tested by connecting the output of T2 across the gate and cathode of a thyristor; the cathode is also connected in series with a 40W lamp and the mains supply, the other mains connection going to the thyristor anode. Points 11B and 37U should be connected to points 39A and 39T of the sync pulse generator board (this is the power supply output) and the flying lead of C4 taken to point 39P of the sync board. VR1 should be set mid-way in its range and 15V d.c. applied to the boards and mains to the thyristor.

If all is well the lamp should light at medium intensity. By reducing VR1 to minimum resistance the lamp brightness should reach a maximum, showing that the dwell time of the monostable is being reduced. If the resistance of VR1 is increased the lamp brightness should fall to zero but, if the resistance is increased further, the lamp will suddenly start to fire again at medium intensity; this is due to the monostable "hanging on" into the next cycle.

To set VR1 correctly, slowly reduce its value from this latter condition until the lamp is off, then continue to reduce its value until the filament of the lamp can be seen just to glow. If an oscilloscope is handy this setting can be made more accurately by adjusting VR1 until the maximum dwell time of the monostable is 9ms.

CHECK VOLTAGE CONTROL

Having set VR1, now check that voltage control is working. This can be done simply by wiring a 10 kilohm potentiometer across a 1.5V cell. Connect the positive side of the cell to the +15V line and the wiper of the potentiometer to point 41I. When the wiper of the pot is hard against the positive end, the light should be extinguished. On advancing it in a negative direction, nothing should happen initially but on about one-third of a rotation the light should start to brighten and should reach full brightness at two-thirds of a complete turn.

These tests should be carried out to all eight channels before further assembly is attempted. Any intermittent or erratic flickering of the lamp should be investigated as it is almost certainly caused by a dry joint.

ASSEMBLY OF THE THYRISTOR BOARDS

In the prototype the thyristors were small IA devices which could be conveniently mounted on Veroboard. There are no real circuitry details for this assembly and no doubt readers will wish to use a variety of differing types of device, thus this description should be used mainly as a guide to a convenient layout. No heat sinks were used on the prototype, thus the current rating of the thyristors

LAMP CONTROLLER

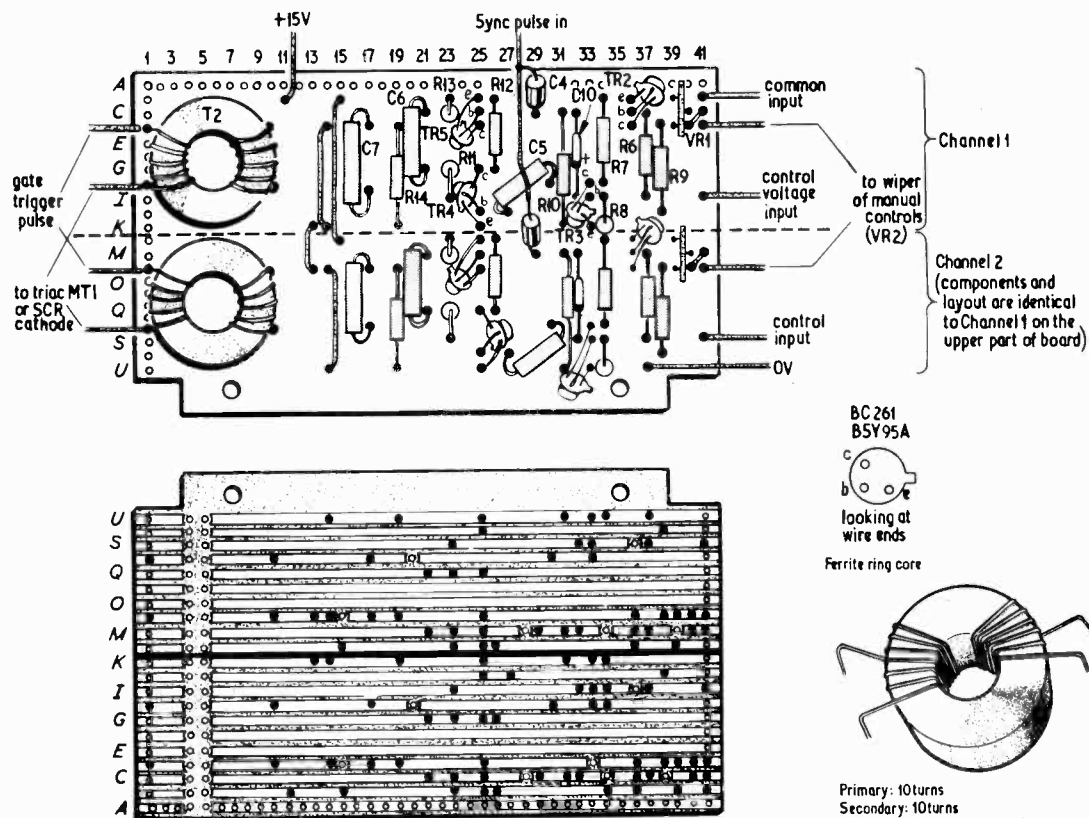


Fig. 9a. Layout of components on 0-1in matrix Veroboard for the trigger units of two control channels. The free end (top) of C4 on all channels are joined together and connected to the sync pulse generator. Do not connect the zero volts line to chassis

Fig. 9b. Winding details of the isolating transformers T2 on ferrite ring cores. Vinkor pot cores can be used if one large enough to accommodate windings is chosen. The core magnetic properties are not critical in this application. Primary 10 turns, secondary 10 turns, 20 s.w.g. enamelled copper wire

COMPONENTS . . .

PHASE CONTROL AND TRIGGER CIRCUIT

Eight of each of following except where stated

Resistors

R6	100k Ω	R11	10k Ω
R7	10k Ω	R12	5-6k Ω
R8	2.7k Ω	R13	56k Ω
R9	56k Ω	R14	1k Ω
R10	22k Ω		
All $\pm 10\%$, $\frac{1}{4}$ watt carbon			

Potentiometers

VR1	250k Ω linear skeleton preset
VR2	500k Ω linear control

Capacitors

C4	0.047 μ F polyester 125V	C6	0.1 μ F polyester 125V
C5	0.1 μ F polyester 125V	C7	0.1 μ F polyester 125V

Transformer

T2	20 s.w.g. enam. copper wire wound on ferrite ring cores or pot cores (see text)
----	---

Diode

D10	1N4148 or any small signal silicon type
-----	---

Transistors

TR2	BC261 or any medium gain pnp silicon (e.g. 2N3702)
TR3	BSY95A
TR4	BSY95A
TR5	BC261 or any medium gain pnp silicon (e.g. 2N3702)

Thyristors or Triacs* (see text and Fig. 10)

Two of each of the above mounted on Veroboards (B to E) $4\frac{1}{2}$ in \times $2\frac{3}{4}$ in 0-1in matrix (Fig. 9). Items shown (*) are mounted on Veroboards F and G (Fig. 10)

Other Items

- Case, Contil Mod-2 type C (West Hyde Developments)
- Sockets, 5-pin DIN type (2 off)
- Connector male 10 or 12 way rated at 250V 4A a.c. per pin, mounted on case. Female mate for light display

must take this into account, and should be considerably greater than the nominal operating current.

Only four connections are required to each device: two from the isolating transformer, one to the lamp channel and one as a return line to the mains. If we were not operating in the matrix mode (or did not require this facility) the polarity of the thyristors would not matter, but as explained previously, we shall need four devices with anodes commoned and taken to line and four whose cathodes are taken to neutral; these are mounted on separate boards and are shown in Figs. 10 and 11 as boards G and F.

Should higher power outputs be required it is

recommended that the thyristors be mounted on heatsinks outside the main cabinet—if this is done it is only necessary to route the trigger pulse lines from the switching circuits. Care must be taken to ensure that full protection from accidental contact with the thyristors or trigger lines is provided.

If constructors abide by the layout of the prototype it is necessary to route the output from the thyristor boards to the lamps. This was effected



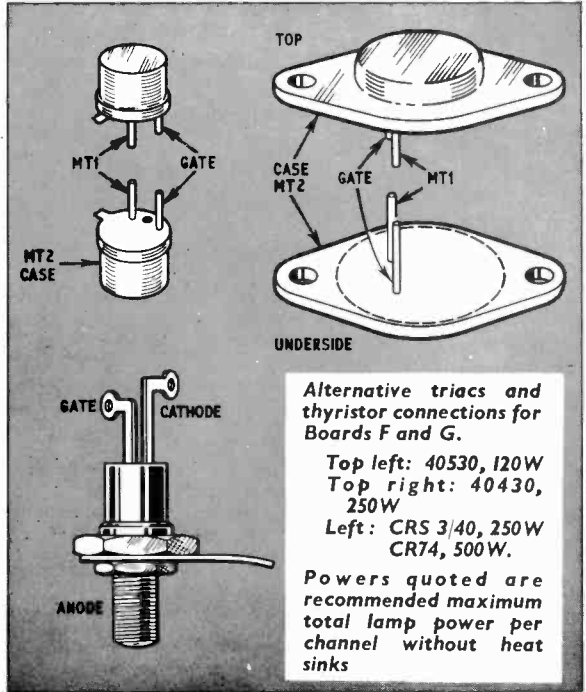
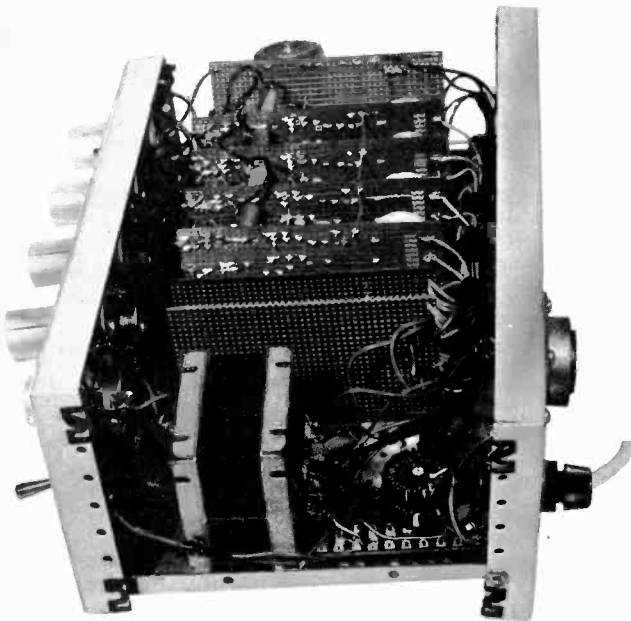


Fig. 10. A guide to the layout of the thyristors on two boards. Those shown are the CRS3/40. Other types of thyristors or triacs may appear different—follow the outline guide for connections

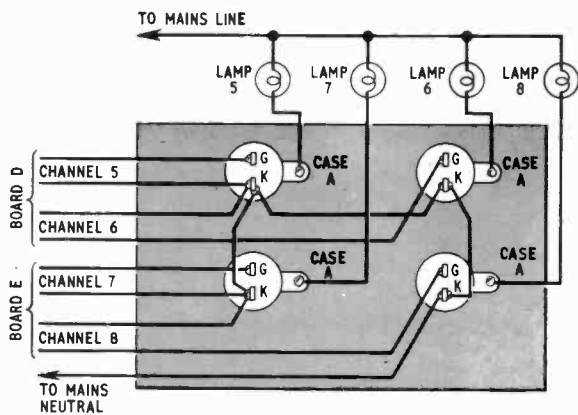

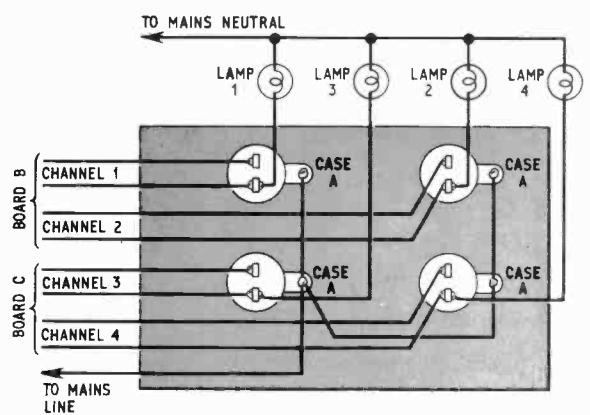(a) Board F—Common side of lamps 5, 6, 7, and 8 are connected to mains "line" for straight channel operation, but as in Fig. 7 if matrix operated. The cathodes of the thyristors (MT1 of triacs) are commoned and outputs to the individual lamp circuits are taken from the anodes of the thyristors (MT2 of triacs)



(b) Board G—Common sides of lamps 1, 2, 3, and 4 are connected to mains "neutral" for straight channel operation, but as in Fig. 7 if matrix operated. The anodes of the thyristors (MT2 of triacs) are commoned and outputs to the individual lamp circuits are taken from the cathodes of the thyristors (MT1 of triacs)

using a multi-pin plug and socket rated for mains operation and full load current. Ten pins are required: four connected to the cathodes on board G, four connected to the anodes on board F and common lines to mains neutral and line. If in-line operation of eight channels is required the external lighting circuits should be connected between mains neutral and the thyristor cathodes on board G and line and anodes on board F.

For matrix operation the circuit of Fig. 7 should be followed: the main matrix is connected between the respective thyristor anodes and cathodes, and the commoned ends of the holding current lamps to mains line and neutral.

Using this technique the two alternative methods of operating can be facilitated only by modifying the external lighting circuit and requires no internal modifications to the controller.

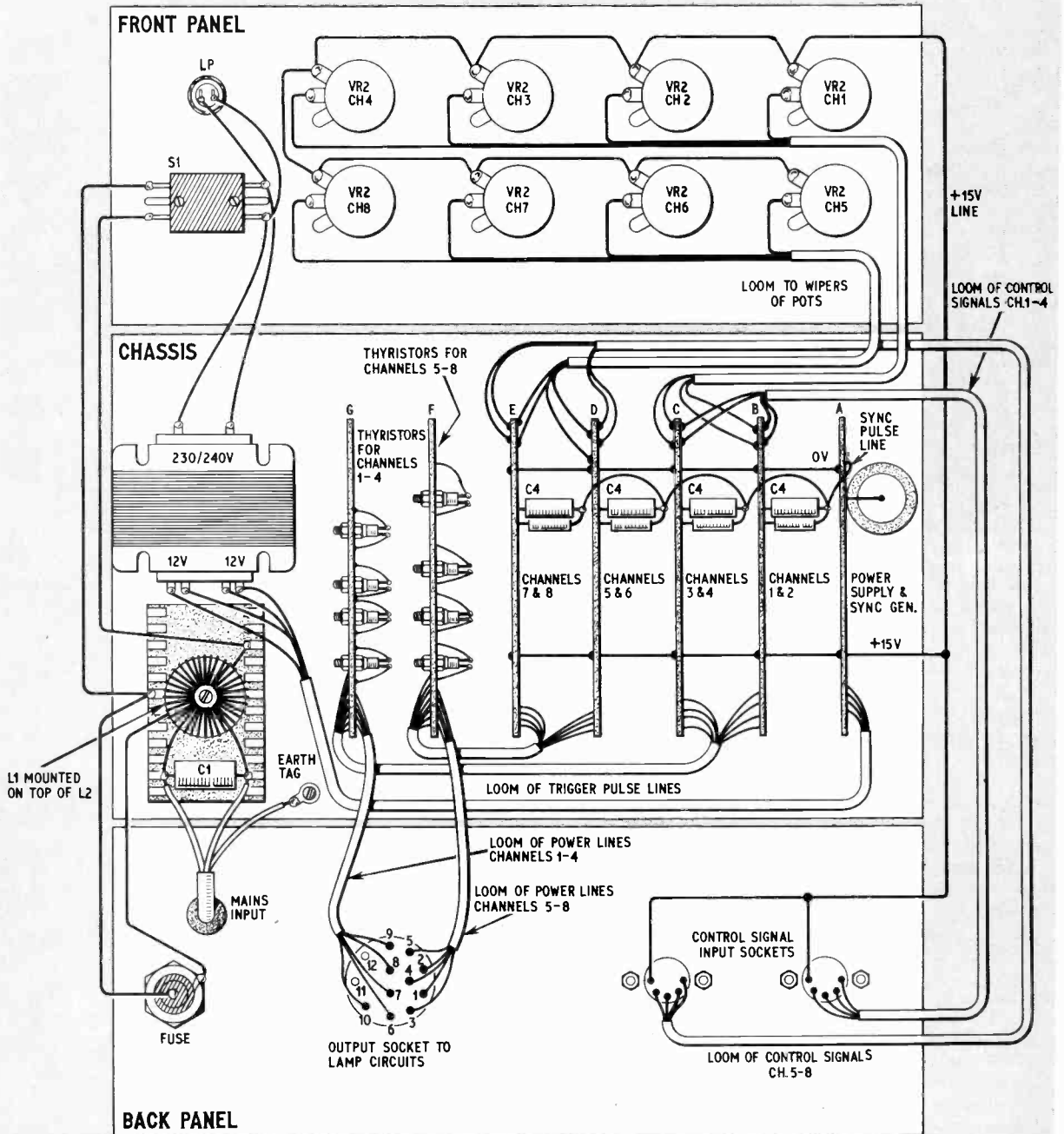


Fig. 11. Wiring looms for the boards mounted vertically on the chassis plate. Board identification is as follows:
A—Power supply and sync pulse generator B—Channels 1 and 2 C—Channels 3 and 4 D—Channels 5 and 6
E—Channels 7 and 8 F—Thyristor (or triac) channels 5 to 8 G—Thyristor (or triac) channels 1 to 4

FINAL ASSEMBLY

Readers will, no doubt, have their own ideas for the best technique of carrying out the final assembly. The author mounted the individual boards on the sub-chassis of the Contil cabinet, using $\frac{3}{8}$ in aluminium angle brackets. A tag board holds the suppression inductors and capacitor so that these can be connected into the mains leads as near the input to the cabinet as possible.

Inductors L1 and L2 are made by winding 40 turns of p.v.c. insulated connecting wire (of 5A rating) round ring cores of the same type as used for the isolating transformers, T2.

The eight manual controls are mounted on the front panel together with the mains switch and a neon. The rear panel carries two 5-pin DIN sockets (for control signal inputs), a panel mounted fuse holder (5A rating) and the multi-pin output socket. Once all the boards are in position, loop a pair of power supply lines to each board and back to the sync pulse board. Then parallel all the free ends of C4 (on each board) and take this to the output of the sync pulse generator.

One end of all the manual controls should be commoned and taken to the +15V rail and the individual wipers taken to their respective control channels. Keep this wiring as neat as possible and loom the wires together in bundles.

SEPARATE INPUTS

Separate input sockets were used for channels 1 to 4 and 5 to 8 so that completely separate control sources can be used simultaneously—this could be highly advantageous if it is desired to use matrix wiring of the lamps. Pin 1 on each input socket is commoned and taken to +15V, the remaining pins are connected to the respective control signal inputs (R6) on the individual channels. Once all these wires have been installed they should be neatly loomed together.

Pairs of wires should be taken from the output of each isolating transformer and connected between cathode and gate of each thyristor or triac. Finally, connections to mains neutral and line and outputs from the triacs or thyristors should be taken to the multi-pin output socket and the respective thyristor boards connected to mains line and neutral.

Care should be taken during this final wiring that some system of identifying individual channels is embodied—this will greatly simplify any trouble shooting that may occur at a later stage.

Before completely assembling the case it is worth giving the unit a final test and a trimming adjustment of VR1 made with VR2 set at maximum resistance. Be careful! Mains voltages are present on some boards.

The controller is now complete and will work as a manually controlled lamp dimmer. It is now necessary to start building input circuits which will provide various types of electronic control.

Note: On page 291 last month (ref. Fig. 6) the text stated that if y1 and x1 are triggered, lamp A will go on. This should read "lamp C."

Next month: The sound conversion unit with frequency band filters for the eight control channels.

NEWS BRIEFS

Machine-Tool Digital Readout System

AFTER evaluation of several digital readout systems offered for machine tool operation, Elliott Machine Tools Limited have selected the Venture design, on the basis of versatility, simplicity, ruggedness, compact transducer and display design. Elliott Machine Tools Limited will offer its range of centre lathes, milling machines, and other machine tools equipped with Venture readout systems.

The digital readout in two co-ordinates is one of the Venture systems type MSI manufactured by Smiths Industries.

Automatic Flight Control

A DIGITAL automatic flight control system designed to increase reliability tenfold and result in a weight saving of 75 pounds is being developed for the F-106 all weather jet interceptor aircraft by Hughes Aircraft Company of California.

The digital automatic flight control system, which will be the first of its kind, will consist of one small solid-state electronics unit weighing 15 pounds that will replace eight valve units currently in use in the F-106. The unit will serve as an interface between the aircraft's control surfaces and a new solid-state digital computer built by Hughes and recently installed in the interceptors.

Picture Enlarger

PICTURES from small T.V. cameras can be magnified up to 100,000 times for lecture-theatre audiences by the Swiss-made Eidophor electro-optical projector. It is shown below being used by Mr. Sebastian de Ferranti during the recent Faraday Lecture at Central Hall, Westminster, to illustrate fine detail in demonstrating the principle of magneto-electric generation during his lecture "Changes and the Future in Electrical Engineering". Made by Gretag AG in Switzerland, the Eidophor was lent for the series of lectures by Electronic Facilities Design Ltd.




LOOK!

PRACTICAL!

VISUAL!


EXCITING!

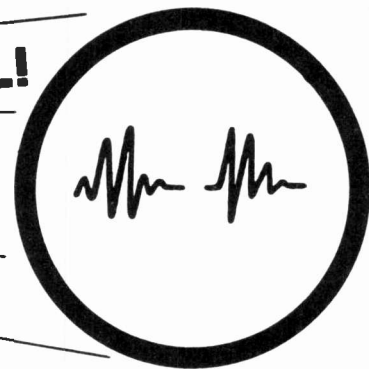

a new 4-way method of mastering
ELECTRONICS
 by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

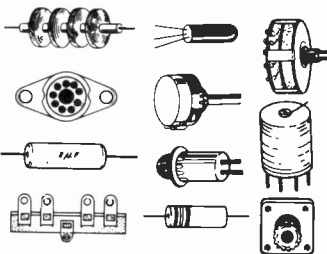complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

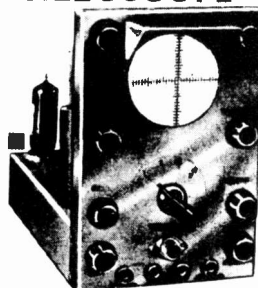a modern and professional **CATHODE RAY OSCILLOSCOPE**



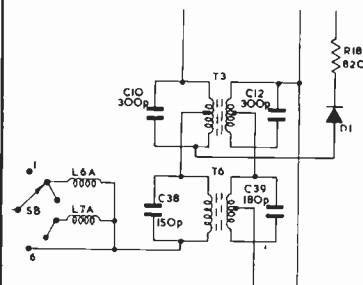3 ▶ READ and DRAW and UNDERSTAND CIRCUIT DIAGRAMS



4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
 for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.E. 5

VARIABLE VOLTAGE TRANSFORMERS

LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cadmium Sulphide PhotoCell, Relay, Transistor and Circuit, etc., 6-12 volt d.c. op. price £1.25 plus 12p P. & P. ORP12 including circuit. 63p each. Post Paid.

A.C. MAINS MODEL. Incorporates Mains Transformer, Rectifier and special relay with 1 make, 1 break H.D. contacts. Price inc. circuit £2.38 plus 20p P. & P.

LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP12 or similar cell. Both units are single hole fixing. Price per pair £2.75 P. & P. 18p.

SANWA MULTI RANGE METERS

New Model U-50DN Multi tester, 20,000 OPV, mirror scaled with overload protection. Ranges—d.c. volts: 100mV, 0.5V, 5V, 250V, 1,000V; a.c. volts: 2.5V, 10V, 50V, 250V, 1,000V; d.c. current: 5µA, 0.5mA, 5mA, 50MA, 250MA. Complete with battery and test probe. £8.00 post paid.

TEN OTHER MODELS. LEAFLET ON REQUEST.

230v AC SOLENOID

Extremely powerful with approx. 14lb. pull, 1" travel. Fitted with mounting feet. Size: 4" long, 2 3/4" wide, 3" high. £2.00 incl. P. & P.

INSULATED TERMINALS

Available in red, white, yellow, black, blue and green. New price 10p each.

12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of 125 RPM. Size: 4 1/2" x 2 1/2" dia. Price 95p inc. post.

200-230V 1/2 R.P.M. MOTOR

Manufactured by 5mth Price 75p inc. post.

12-28 VOLT DC BLOWER UNIT

Smooth running, precision made Blower Unit, 5,000 RPM, .54 amps. Size 3" diameter x 3 1/2" long overall. Price £2.00 post paid.

RECHARGEABLE BUTTON CELLS

2 x 1.2V, 250 MA HR Nickel Cad. Cells, connected to give 2.4V @ 25 milliamp 10 hour rate, complete with 200/250V a.c. charger. Fully tested and unused. Price 48p each plus 8p P. & P. or 2 units for £1.00 post paid.

UNISELECTOR SWITCHES

NEW 4 Bank 25 Way 24V d.c. operation. £5.88, P. & P. **22p. 6 Bank 25 Way 24V d.c.** £6.50, P. & P. **22p. 8 Bank 25 Way 24V d.c.** operation. £7.63 plus 22p P. & P.

VENNER Electric Time Switch

200/250V Ex. G.P.O. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £3.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.

INPUT 230/240V a.c. 50/60
OUTPUT VARIABLE 0-260V

BRAND NEW
Keenest prices in the country.
All Types (and Spares) from
1/2 to 50 amp from stock.

SHROUDED TYPE
1 amp, £5.50. 2.5 amp, £6.75. 5 amp, £9.75. 8 amp, £14.50. 10 amp, £18.50.
12 amp, £21.00. 15 amp, £25.00. 20 amp, £37.00. 37.5 amp, £72.00. 50 amp, £92.00.

OPEN TYPE (Panel Mounting) 1/2 amp, £3.93.
1 amp, £5.50. 2 1/2 amp, £6.63. Carr. 40p on open types.



50 AMPS



1/2 AMP

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard 5.C.R. Unijunction Xenon Tube and instructions £5.25 plus 25p P. & P.

NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil plastic thyristor. Speed adjustable 1-80 f.p.s. Price £9.45 50p P. & P.

HY-LIGHT STROBE
This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £10.88. P. & P. 50p.

7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230 mA; 2.5 kΩ, 2A; 5kΩ, 140 mA. Diameter 3 1/2 in. Shaft length 3/4 in, dia. 1/8 in. All at £1.50 each. P. & P. 5p.
50 WATT. 1/5/10/25/50/100/250/500/1/1.5/2.5/5kΩ. All at £1.12 each. P. & P. 11p.
25 WATT. 10/25/50/100/250/500/1/1.5/2.5/5kΩ. All at 78p each. P. & P. 15p.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS - COMPETITIVE PRICES

	1	2	3	4	1	2	3	4
45	6-9	2M HD	50p*	700	12-24	2 c/o	63p*	
180	6-12	2 c/o	50p*	700	16-24	6M	63p*	
185	6-12	2 c/o	60p*	1250	24-36	4 c/o	63p*	
230	6-12	2 c/o	63p*	250	36-45	6M	63p*	
280	6-12	2 c/o	73p*	2500	36-45	6M	63p*	
700	16-25	4M 2B	63p*	5800	80-85	4 c/o	63p*	
700	16-24	4 c/o	78p*	9000	40-70	2 c/o	50p*	
				15K	85-110	6M	50p*	

* Including Base
(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid.

MAINS RELAY
230V a.c. coil 3 c/o. 10 amp a.c. contacts, 50p plus 8p P. & P.


HOSIDEN DH-02-S Stereo Headphones
8 ohm impedance 20-12,000Hz. Adjustable head band. Price only £2.38. P. & P. 12p. Complete with lead and stereo jack plug.

MOTOROLA MAC 1/4 PLASTIC TRIAC 400 PIV. 8 AMP

Now available **EX STOCK**. Supplied with full data and applications sheet. Price £1.05, P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p., 50 cycle, .38 amp. (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible, 1/80th h.p., 50 cycle, .28 amp. The above two precision made U.S.A. motors are offered in "as new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p P. & P. or less transformer £2.13 plus 27p P. & P.

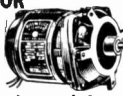

TRANSISTOR AUDIO AND RADIO CIRCUITS

for Radio Receivers, Radiograms, Record Players, Tape Recorders and Hi-Fi Equipment.

A Mullard Publication

£1-50 Postage 5p

ELECTRONIC DESIGNER'S HANDBOOK. A practical guide to transistor circuit design. T. K. Hemingway. £3.40. Postage 10p.

20 SOLID STATE PROJECTS FOR THE CAR & GARAGE. R. M. Marston. £1-20. Postage 5p.

COLOUR TELEVISION WITH PARTICULAR REFERENCE TO THE PAL SYSTEM. G. N. Patchett. £2-50. Postage 5p.

SECURITY ELECTRONICS. John E. Cunningham. £1-70. Postage 5p.

RADIO & AUDIO SERVICING HANDBOOK. Gordon J King. £3. Postage 10p.

TRANSISTOR POCKET BOOK. R. G. Hibberd. £1-40. Postage 5p.

1971 WORLD RADIO-TV HANDBOOK. J. M. Frost. £2-10. Postage 12p.

RADIO VALVE & TRANSISTOR DATA. A. M. Ball. 75p. Postage 9p.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET

LONDON, W.2

Phone: PADDINGTON 4185

Closed Saturday 1 p.m.

GUARANTEED FULL SPEC. COMPONENTS FROM LEADING MANUFACTURERS

Nixie tubes—1in clear end reading, similar to GNSA £3-00 £2-90 £2-80
TTL
SN74141N—BCD/decimal decoder driver £1-85 £1-15 £1-00
SN7490N, SN7492N—decade, ÷ by 12 counter £1-00 95p 82p
SN7483N—4 bit binary full adder £1-20 £1-10 £1-00
SN7415N—dual Schmidt trigger 40p 35p 30p
SN7470N, SN7472N—flip flops SN7473N, SN7474N, SN7476N—dual flip flops 40p 35p 30p
SN7475N—heavy bistable latch 45p 30p 28p
SN7400N, 01N, 02N, 03N, 04N, 10N—gates 60p 55p 50p
SN7420N, 30N, 40N, 50N, 53N, 60N—gates 30p 24p 18p
★ Free 74N wall chart with every TTL order
★ Full range 74N supplied—pro rata prices
★ Mix devices for quantity price.

LINEAR
1N4148/709N—14 pin diode op. £1-20, £1-10, £1-00, 80p, 70p, 60p
741F/709P—8 pin diode op. 95p, 85p, 75p, 60p, 50p, 40p
741L/709L—TO3 diode op. £2-20, £2-10, £2-00, 180p, 170p, 160p
709DN—Dual 709N £1-80 £1-20 £1-10

DISCRETES
1N4148/914—75V 75MA diode 4p 3p 2-5p
182000A—3% 400MW 3-30V zeners 15p 12p 10p
BC107/108/109—gen. purpose TO3 tran 12p 11p 10p
BC182L/183L/184L—Gen. purpose silicet tran. 12p 11p 10p

PRINTED CIRCUIT SERVICES

Graphiplan—artwork symbols and drafting aid
Dayplan—24-hour prototype P.C. service
Faciplan—adhesive backed stable film for dials, scales, labels
Terms: Cash with order. £1 min. order. P. & P. 10p U.K.; 20p Europe; 60p Overseas.
Overseas and large quantity semiconductor inquiries welcome. Delivery subject to stock levels.

ELMTEX LTD. (COMPONENTS DIVISION)


83 High Road, Dunmow, Essex

Tel.: Great Dunmow 2202

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. P.E. 57 BRIDGMAN ROAD, LONDON W4 5BB
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

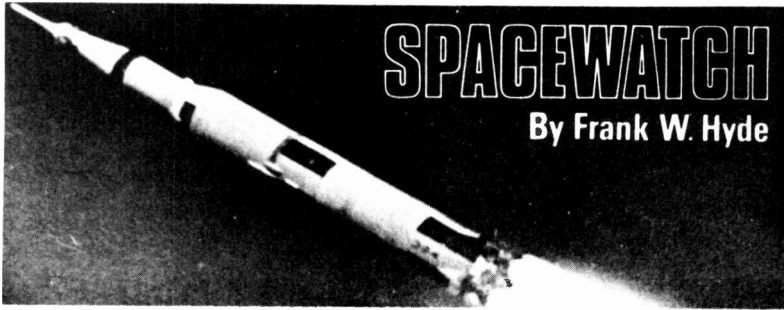Personal callers only. Open Sat.
9 LITTLE NEWPORT ST.
LONDON WC2H 7JJ 01-437 0576



GYROSCOPE ALTERNATIVE

The Aerospace Division of Honeywell at Minneapolis have developed an alternative system to the traditional type of gyroscope with a spinning rotor for the sensing of angular displacements. The new system consists of a vibrating wire of beryllium copper, stretched tightly between two magnetic fields. One of these drives the wire and the other generates the output signal.

To separate the two signals a second wire is set at right angles to the first. This is electrically earthed at the crossover point and the driving magnet is set with its poles in the same plane. The output magnet is set with its poles perpendicular to this plane.

The part of the tight wire which is in the drive field is caused to vibrate by an oscillator. This promotes sympathetic vibrations in the second half of the wire which is in the signal magnet field. Should there be any rotation along the longitudinal axis of the input side, "Coriolis forces" will appear as deflections of the wire which are proportional to the turning rate.

There are a number of advantages in this device, among them a short "warm up" time of only 100 milliseconds and a noise threshold of only 0.02 degrees per second in the output signal. For certain uses it has a possible lifetime of 75,000 hours.

CORIOLIS FORCE

The Coriolis force arises from the Earth's rotation and causes a horizontal force which is at right angles to the direction of the velocity of a body which may be clouds or, for example, a ship.

It has been suggested recently that these forces which are normally small can have an effect of some magnitude on large bodies such as the large oil tankers that are now coming into use. A nautical advisor to a Dutch firm, J. C. Annveld, has shown that the Coriolis force may be a source of danger which might lead to collisions between such vessels. It is possible that the *Torrey Canyon* disaster may have had this hazard to contend with.

In addition to the normal difficulties of manoeuvre, very large

vessels contemplated for the future are expected to need to take the Coriolis force into account.

SPACE SHUTTLE PROGRAMME

Investigations into structures, aerodynamics and flight test instrumentation for the space shuttle programme is to be carried out by the British Aircraft Corporation.

It is in these fields that BAC are particularly adept and they have already been engaged in space contracts including a large contract for the *Intelstat IV* communications satellites. They are at the present completing the work on *UK-4* which is due for launch in 1971.

SECOND BRITISH SATELLITE

The second wholly British satellite to be launched by NASA will also carry a United States experiment in addition to those designed for Britain, so helping to reduce the cost of the launch. Due to be launched in 1973 it will be named *UK-5* until successfully in orbit when its name will change to *Ariel 5*.

Coming at a time when very great interest is being shown in X-ray astronomy, the decision of the Science Research Council that *UK-5* is to be devoted to this study will be a very welcome one. It will enable the special data, in detailed form that is so badly needed, to be obtained for a better understanding of the high energy sources that have been observed.

X-RAY EXPERIMENTS

There will be a number of separate experiments and the Mullard Space Sciences Laboratory will supply a proportional counter for the purpose of studying individual sources of X-rays in the 2-30keV band. Higher energy sources will be dealt with by Imperial College, London, who have designed a detector for the study of known sources up to 2MeV and also to search for X-ray emission from pulsars.

The University of Leicester group, who have already contributed so much in this field, are responsible for two detectors. One of these will

scan the whole sky and the other will be designed to measure polarisation of the X-rays.

The Mullard group will also be responsible for another experiment at low energy levels from 0.3 to 30keV and for this several detectors will be used. In addition they will also be responsible for a special pointing detector which will have a photomultiplier to detect visible light.

The Goddard Spaceflight Centre will be adding an experiment to search for possible transient effects against the background X-radiation.

The satellite is a cylinder 37.75in in diameter and some 34in high. The sides will be almost entirely covered with solar cells to provide the necessary power. It has its own internal computer which will receive instructions from the ground. This means that most of the detectors on board can be pointed to specific sources as required, while the special detector mounted on one side will scan the whole sky as the satellite rotates in its search for new objects.

There is an interesting co-operative effort between Britain and America in the work of this satellite. Mount Palomar and Mount Wilson Observatories will carry out simultaneous optical measurements to correlate the X-ray observations.


At the Hale Observatories astronomers are planning to have a set of plates ready by the time the satellite is in operation. These have already been obtained by using their 48in Schmidt telescope. The uniqueness of the Hale survey is that it covers most of the galactic plane within which X-ray sources have been observed already.

SHIP TO SHORE CONTACT via SATELLITE

A very successful experiment has been carried out by the Post Office from their radio station at Burnham-on-Sea, Somerset. This was to communicate via an application technology satellite, in this case *ATS-3*, with the container ship of Cunard-Brocklebank called the *Atlantic Causeway*.

Simple multi-element crossed yagi aerials were used to provide a wide capture angle. Techniques tried out were the Lincompex and Compacon systems of speech processing. Traffic that was successfully passed was teleprinter, speech, facsimile, data and selective calls. The frequencies used were 135.6 and 149.22Mhz. The power at the shore station was 250W.

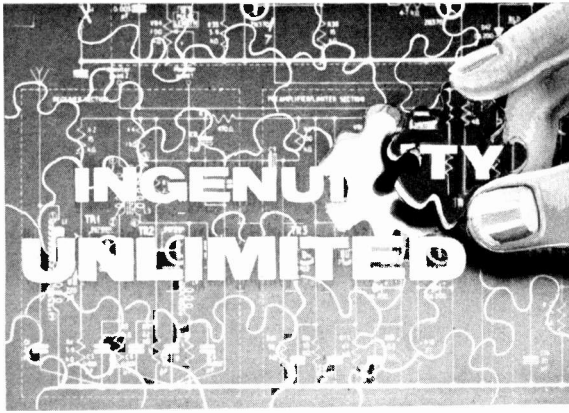The great advantage of this method of communication is that it avoids the changing ionospheric conditions which cause considerable difficulty with the conventional systems. It was found that transmission via satellite was only marginally affected.



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merit.

AUDIO CHOPPER OR EFFECTS UNIT

THE circuit in Fig. 2 may be of interest to some of your readers. It was developed primarily to produce extra effects on "pop" records, but can also be used to give voice effects.

Transistors TR1, TR2 and associated components form an astable multivibrator; TR3 is a buffer to prevent the frequency from changing when the output is loaded.

Transistor TR4 is connected across the audio line and severely attenuates the signal when conducting. This transistor (TR4) functions in a rather unusual mode, acting as an alternate high and low impedance across the audio line, and therefore, any attempt to use a collector resistor would result in a greatly amplified multi-vibrator "buzz" passing into the audio signal.

Potentiometer VR3 controls the level of chopping, while C3 provides bass cut. Capacitors C1 and C2, together with potentiometers VR1 and VR2 control the frequency of the multivibrator. The capacitors C1 and C2 could be several different value capacitors arranged

SIMPLE METRONOME/TUNING FORK

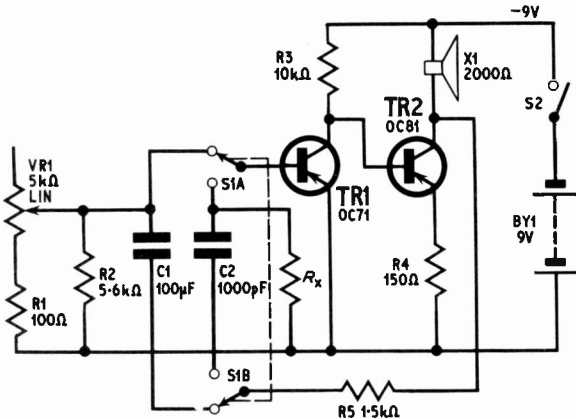


Fig. 1.


READERS with an interest in music may be interested in the circuit of a combined electronic metronome and tuning fork. The circuit, shown in Fig. 1, is an adaptation of a simple multivibrator circuit. A slide switch (S1) is used to change the circuit from the metronome to the tuning fork mode.

In order to give the metronome a loud "tick", a high gain output stage is used, the speaker (X1) being a balanced-armature type earpiece. The pitch of the tuning fork is governed by capacitor C2 and resistor R_x which, as a guide, is approximately 3.9 kilohms for a tone of $A = 440\text{Hz}$.

The device can easily be assembled in a small pocket-sized case and the layout of components is not critical.

Switched to the metronome mode, the control VR1 needs to be calibrated in beats per minute and the range of the metronome should be adequate: from about 30 to 240 beats per minute.

A. L. Dicks,
Wigston,
Leicester.

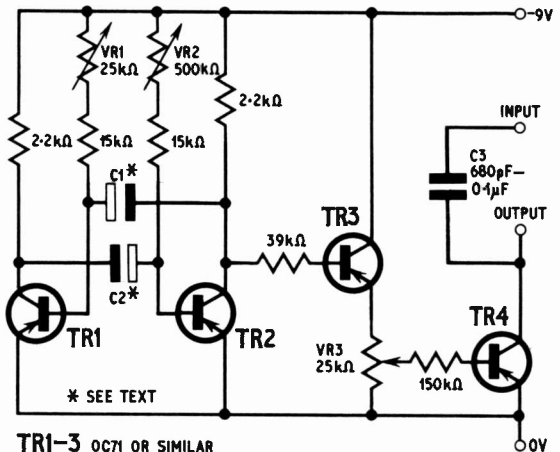

TRI-3 OC71 OR SIMILAR
TR4 OC200 OR SIMILAR SILICON

Fig. 2. Circuit diagram of the audio chopper or musical effects unit

so that they can be switched into the circuit depending on the required effect, i.e. $1.5\mu\text{F}$, $0.47\mu\text{F}$, $0.1\mu\text{F}$ or $0.02\mu\text{F}$.


The input/output impedances were found to be approximately 2 kilohms.

With regard to sensitivity, a crystal record pick-up can be connected straight to the input, the output going to an amplifier or tape recorder.

However, a preamplifier must be used with a microphone, otherwise the multivibrator noise is excessive.

P. Tyrell,
Ilford,
Essex.

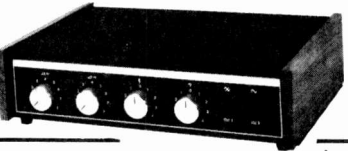HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response $\pm 3dB$ 20-20,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth $\pm 3dB$ 12-15,000Hz. Bass boost approx. to $\pm 12dB$. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Requirements: 23V at 1.0 amp. Overall size—12" wide x 8" deep x 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES AMPLIFIER KIT, £10.50 P. & P. 15p.
POWER PACK KIT, 23 P. & P. 25p.
CABINET, 23 P. & P. 25p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.50. Post Free.

Note: This above amplifier is suitable for feeding two mono sources into inputs (e.g. mixer, radio, turn record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.

FANTASTIC 'POLY PLANAR' WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size only 11" x 14" x 1 1/2" deep. Weight only 19 ozs. Can replace cone speakers in any application and is particularly useful for those with limited space. Extremely rugged and shockproof. Operating temperature -20°F to +175°F. Power handling 10 watts rms (20 watts peak). Impedance 8 ohm only. Response 40 Hz—20 KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

VYNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.
SINGLE HEADPHONE. With aluminium headband. Approx. 200 ohm. 25p. P. & P. 8p.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 85p. P. & P. 8p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1.05. P. & P. 8p.

HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity. £1.98. P. & P. 13p.

PIANO KEY TYPE SWITCHES. 8 press buttons plus 1 cancel button. Each of the 8 sections contains 6 s.p.c.o. (total 40 s.p.c.o.). Brand new—limited quantity only. Original manufacturing cost £1.37. OUR PRICE 75p. P. & P. 13p (3 or more post free).

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 145pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s. I.F. Size approx. 2 x 1 x 1/4 in. Only 43p. P. & P. 13p.

HONEYWELL MICROSWITCHES S/P, C/O. Push-button action. Rating 250V, AC at 15 amps. Size approx. 1 1/4 in. x 1/2 in. x 1/4 in. 25p each. P. & P. 5p (6 or more post free).

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to approx. 22 1/2 in. Maximum diameter 1/4 in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Offering 13 alternatives. Primary: 0.210-240V. Secondary combinations: 0.5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-10, 20-20, 30-30, at 2 amps full wave. Size 3in L x 3 1/2 in W x 3in D. Price £1.75. P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.35. P. & P. 18p. Tapped Primary 200-220-240V. Sec. 21-0V at 300mA. 65p. P. & P. 13p.

BATTERY CHARGER TRANSFORMERS. 200/240V, input. Nominal output for 6 or 12V batteries 0.5 amps. Size approx. 3 x 2 1/2 x 2 1/2 in. Brand New. Price £1.05. P. & P. 25p.

SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynal front. Size 16 1/2 in high x 10 1/2 in wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8.40 Carr. 50p.

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £6.50. Carr. 50p.

LOUDSPEAKER BARGAINS

3in 4 ohm 50p. P. & P. 13p. 3in 3 ohm 80p. P. & P. 15p. 7 x 4in 3 ohm £1.05. P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1.82. P. & P. 20p. E.M.I. 13 x 8in 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

BRAND NEW. 12in 15W H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hifux ceramic ferrobar magnet assembly £5.50. P. & P. 38p. Heavy duties: 25w £6.50, 35w £8.50.

E.M.I. 3 1/2 in GUITAR TUNING TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohm 85p each. P. & P. 13p.

12in "RA" TWIN CONE LOUDSPEAKER
10 watts peak handling. 3 or 15 ohm, £1.88. P. & P. 30p.
35 OHM SPEAKERS. 3in 70p. P. & P. 13p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 3 1/2 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE £2.95. P. & P. 15p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PREAMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/2 in. Brand new—complete with instructions. Price 85p. P. & P. 13p.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST. Fitted mono 1/8" stylus and cartridge for LP/78, ONLY £1. P. & P. 8p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 d. x 6 h. Ready built and tested. PRICE £3.75. P. & P. 30p. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4.88. P. & P. 35p.

DE LUXE QUALITY PORTABLE R/P CABINET MK II
Uncut motor board size 14 1/2 x 19in., clearance 2in. below, 5 1/2 in. above. Will take above amplifier and any S.B.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE £3.98. P. & P. 48p.

10/14 WATT HI-FI AMPLIFIER KIT


A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ20 rectifier. Simple instruction booklet 15p (Free with parts). All parts sold separately. ONLY £7.97. P. & P. 43p. Also available ready built and tested complete with std. input sockets, £9.97. P. & P. 43p.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V15/10p, 50p; OC71 25p; OC78 30p; AF17 18p; 2G339 (NPN) 15p. Set of Mullard 6 transistors OC44, 2—OC45, AC128D, matched pair AC128 £1.25; ORP12 Cadmium Sulphide Cell 55p. All post free.

VERY POWERFUL COMPACT MOTOR
For 12v. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" L x 1 1/2" dia. Free shaft 1/8" dia. x 1/4" L. Ideal for Model Makers, etc. ONLY 85p each. P. & P. 5p.
3 or more post free (A few 6v. versions also available).

HIGH GRADE COPPER LAMINATE BOARDS
8 x 6 x 1/4 in. FIVE for 85p. P. & P. 10p.

DE LUXE STEREO AMPLIFIER

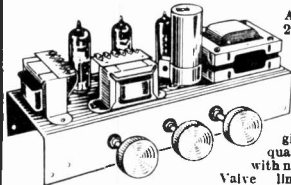

A.c. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2 x ECL86 Triode Pentodes.

1 x EZ80 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono) into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supply complete with knobs, chassis size 11 in. x 4 in. x. Overall height including valves 5 1/2 in. Ready built and tested to a high standard. Price £23.92. P. & P. 40p.

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing.
LATEST S.B.R. C109/A1 4-SPEED AUTOCLEANER. With latest mono compatible cartridge £6.97. Carr. 33p. With stereo cartridge £7.97. Carr. 33p.
SUITABLE PLINTH UNIT FOR ABOVE with rigid plastic cover. £5.75 complete. P. & P. 43p.

LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60, etc. S.A.E. for Latest Prices!
FLIGHT CUT OUT for Garrard Models 1025, 2025, 2000, 3000, 3500, etc. With lid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.75 complete. P. & P. 43p.

LATEST ACOS GP91/180 Mono Compatible Cartridge with 1/8" stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.
ACOS HI-G Single sided mono cartridge for LP & EP. ONLY 50p. Post Free.
SONOTONE STEREO COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.50. P. & P. 10p.
Also available fitted with twin Diamond T/O stylus for Stereo LP. ONLY £3. P. & P. 10p.
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1.68. P. & P. 10p.
LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. £1.50. P. & P. 10p.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TA1
Peak out-put in excess of 1 1/2 watts. All standard British components.
Built on printed circuit panel size 6 x 3in.
Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET14 or 81 Mullard AC 128D and matched pair of AC128 o/p), 9 volt operation. Everything supplied, including clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 15p (Free with Kit). All parts sold separately. SPECIAL PRICE £2.48. P. & P. 15p. Also ready built and tested, £2.75. P. & P. 15p.

3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 30p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 30p.

HARVERSON'S SUPER MONO AMPLIFIER
A stylish gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL84 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY.
OUR ROCK BOTTOM BARGAIN PRICE £2.75 P. & P. 30p.

Open 9.5-30 Monday
to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon
Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

£/Np		£/Np		£/Np		£/Np	
AC107	37	B5Y29	25	NKT80214	75	ZG302	19
AC126	25	B5Y94	15	NKT80215	75	ZG371	15
AC127	25	BY100	20	NKT80216	75	ZG374	25
AC128	20	BY100	15			ZN174	80
AC176	25	BY210	40	OA5	20	ZN385A/	
AC187	30	BY212	40	OA10	25	ZN386A/	
AC188	30	BY213	20	OA47	8	ZN404	73
AC17	29	BZ Y88 Series	15	OA70	8	ZN696	15
AC18	20	3.3V to 30V	15	OA73	8	ZN697	17
AC19	20			OA79	8	ZN698	30
AC20	19	D1371	45	OA81	8	ZN706	10
AC21	19	MJ520	75	OA85	8	ZN706A	10
AC22	19	M480	97	OA90	4	ZN708	16
AC40	15	MJ481	1.25	OA91	8		
AC41	15	M490	1.00	OA95	8	ZN711	37
AD140	55	MJ491	1.35	OA200	10	ZN711A	37
AD149	57	MPF102	43	OA202	10	ZN911	50
AD161	37	MPF103	37	OC19	37	ZN914	20
AD162	37	MPF104	37	OC20	97	ZN918	42
AF114	25	MPF105	40	OC22	47	ZN1090	30
AF115	25			OC23	60	ZN1091	33
AF116	25	NKT124	30	OC24	60	ZN1130	30
AF117	25	NKT125	40	OC25	37	ZN1132	30
AF118	44	NKT126	37	OC26	33	ZN1132	20
AF124	25	NKT128	25	OC26	25	ZN1303	25
AF126	17	NKT135	26	OC29	75	ZN1304	25
AF139	37	NKT137	32	OC35	50	ZN1305	25
		NKT210	25	OC36	63	ZN1306	30
AF186	40	NKT211	25	OC41	25	ZN1307	30
AF239	37	NKT212	25	OC42	30	ZN1308	34
AS526	25	NKT213	25			ZN1309	31
AS527	30	NKT219	23	OC44	15	ZN1507	23
AS528	22	NKT215	21	OC45	15	ZN1613	22
AS529	30	NKT216	46	OC71	15	ZN1711	25
AS521	37	NKT217	50	OC72	23	ZN2147	82
AU10	150	NKT218	25	OC75	23	ZN2148	63
BA115	8	NKT219	25	OC76	25	ZN2148	63
BC107	12	NKT223	27	OC77	40	ZN2268	17
BC108	12	NKT224	25	OC81	23	ZN2369	17
BC109	12	NKT225	21	OC81D	20		
BC147	15	NKT229	29	OC82	55	ZN2369A	20
BC148	15	NKT237	31	OC82	25	ZN2646	50
BC149	15	NKT239	19	OC82D	15	ZN2904	44
BC158	17	NKT239	23	OC83	23	ZN2904A	49
BC169C	19	NKT240	20	OC84	25	ZN2905	65
BC182	12	NKT241	21	OC139	25	ZN2905A	75
BC182L	10	NKT242	15	OC140	35	ZN2906	44
BC183	9	NKT243	56	OC170	25	ZN2906A	54
BC184	9			OC171	30	ZN2926	all
BC184L	15	NKT244	17	OC200	37	colours	10
BC184L	15	NKT245	17	OC201	47	ZN3053	25
BC212	17	NKT261	21	OC202	63	ZN3054	63
BC212L	12	NKT262	19	OC203	37	ZN3055	75
BCY30	25	NKT264	21	OC204	40	ZN3072	11
BCY31	48	NKT271	18	OC205	65	ZN3073	10
		NKT272	17	OC206	75	ZN3704	11
BCY32	50	NKT274	18	OC207	75	ZN3705	10
BCY33	20	NKT275	23	OCPT7/M	47	ZN3706	9
BCY34	25	NKT279A	12			ZN3707	11
BCY38	30	NKT281	29	ORP12	50	ZN3708	7
BCY70	19	NKT302	87	ORP60	40	ZN3709	9
BCY71	37	NKT304	79	ORP61	40	ZN3710	9
BCY72	16	NKT351	75	P346A	19	ZN3711	9
BD121	1.10	NKT401	71	ST140	15	ZN3819	35
BD123	1.10	NKT402	77	ST141	20	ZN3820	60
BD124	1.03	NKT403	65	TD716	60	ZN3826	30
BDY20	1.05	NKT404	60	TD716	62		
BF115	25	NKT405	79	TIP32A	74	ZN4058	17
BF163	40	NKT406	62	V405A	46	ZN4060	20
BF167	25	NKT420	1.83	ZTX108	11	ZN4061	20
BF173	30	NKT451	58	ZTX300	13	ZN4062	20
BF178	52	NKT452	54	ZTX302	18	ZN4284	15
BF180	37	NKT453	50	ZTX303	18	ZN4287	15
BF181	37	NKT603F	30	ZTX303	18	ZN4289	15
BF184	25	NKT613F	30	ZTX304	27	ZN4871	40
BF185	25	NKT674F	30	ZTX314	11	ZN84	1.30
BF194	17	NKT676F	30	ZTX320	30	ZN128	69
BF195	15			ZTX330	18	ZN140	76
BF196	15	NKT677F	28	ZTX500	16	ZN141	73
BF200	35	NKT713	29	ZTX501	16	ZN152	86
BFX13	25	NKT717	44	ZTX502	20	ZO250	55
BFX29	31	NKT734	32	ZTX503	17	ZO309	37
		NKT736	26	ZTX504	40	ZO310	45
BFX84	26	NKT773	25	IN6A	20	ZO312	48
BFX95	34	NKT781	29	IN60	20	ZO320	36
BFX96	25	NKT10339	25	IN64	20	ZO360	43
BFX97	30	NKT10419	19	IN82A	47	ZO361	48
BFX98	25	NKT10439	27	IN87A	23	ZO362	58
BFY50	23	NKT10519	22	IN91A	7	ZO406	56
BFY51	19	NKT20329	60	IN4001	7	ZO407	39
BFY52	20	0013	31	IN4002	7	ZO408	51
BFY53	16	NKT80111	67	IN4003	10	ZO409	54
BSX19	67	NKT80112	83	IN4004	10	ZO468A	35
BSX19	16	NKT80113	1.00	IN4005	12	ZO600	58
BSX20	16	NKT80211	75	IN4006	15	ZO601	55
BSX21	30	NKT80212	75	IN4007	20	ZO602	40
BSY27	27	NKT80213	75	IN4148	7	ZO603	49

TERMS: Cash with order please. Postage & packing - 10Np inland. 25Np Europe. 60Np elsewhere. All goods guaranteed. ALL ORDERS DESPATCHED WITHIN ONE WORKING DAY OF RECEIPT. 1971 Retail Catalogue now available. 5Np stamp for postage appreciated.

LST ELECTRONIC LTD
COMPONENTS
MAIL ORDER DEPT. (PE)
7 COPTFOLD ROAD
BRENTWOOD, ESSEX
Visitors welcome at our new retail shop - same address.

Components

RESISTORS
Carbon Film $\frac{1}{2}$ & $\frac{1}{4}$ Watt 5%
2Np each
Packs of 10 (of one value/voltage)
15 Np per pack

PRESETS
P.C. Type 0.3 Watt
Standard size 7Np
Sub-miniature 5Np
(Available vertical or horizontal mounting)
Usual values 100 ohms to 5 Meg.

POTENTIOMETERS
Log or Lin Less switch - 17 Np
Log or Lin DP switch - 27 Np
Log or Lin Stereo L/S - 50 Np
Values: 5k, 10k, 25k, 50k, 100k
250k, 500k, 1 Meg, 2 Meg.

CAPACITORS
Mullard Miniature Electrolytic
Mfd. Volt/Wtg. - C426 Series
2.5 16 8Np
10 16 6Np
20 16 6Np
40 16 6Np
80 16 6Np
1.6 25 8Np
6.4 25 6Np
12.5 25 6Np
25 25 6Np
50 25 6Np
90 25 6Np
1 40 8Np
4 40 6Np
8 40 6Np
16 40 6Np
32 40 6Np
50 40 6Np

Mullard Metallised Polyester 250v
Mfd. Mfd.
01 3Np 22 5Np
015 3Np 33 7Np
022 3Np 47 8Np
10 033 3Np 68 11Np
047 4Np 10 14Np
068 4Np 1.5 20Np
1 4Np 2.2 24Np
15 5Np

Mullard Electrolytic - C437 Series
Mfd. Volt/Wtg.
250 16 9Np
400 16 12Np
600 16 15Np
7 1000 16 18Np
9 160 25 9Np
25 250 25 12Np
9 400 25 15Np
640 25 18Np
100 40 9Np
160 40 12Np
250 40 15Np
400 40 18Np

Mullard Sub-Miniature Ceramic
Plate - C333 Series
63 volt working. Range 1.8pf to 220pf (usual pref values).
Packs of 6 (any values) - 30 Np

NEONS
Miniature neon bulbs: 0.6mA 65vac
90Vdc. Pack of 5 for 30Np
Panel neon indicators, mains voltage.
Red lenses - round, square or arrow-shaped faces. Each 20Np

VEROBOARD
2.5" x 17" x 15" 57 Np
4" x 17" x 15" 79 Np
2.5" x 5" x 15" 23 Np
2.5" x 3.75" x 15" 19 Np
3.75" x 17" x 15" 79 Np
3.75" x 5" x 15" 30 Np
3.75" x 3.75" x 15" 22 Np
2.5" x 5" x 1" 25 Np
2.5" x 3.75" x 1" 23 Np
Spot face cutters - 38 Np
Veropins: pack of 50 for 21 Np
Bargain Pack, 36 square inches of various sizes. 15" &/or 1 50Np

HEATSINKS
TO-5 (Clip-on) pack of 4 for 15 Np
FINNED type for 2 x TO-3 ready drilled at 43 Np
FINNED type undrilled for plastic power at 34 Np

BOOKS
G.E. Transistor Manual £1.47
R.C.A. Transistor Manual £1.47
Designers' Guide to British Transistors (data book) £1.25
R.C.A. Hobby Circuits Manual £1.25
110 Semiconductor Projects (Marston) £1.50
Zener Diode Handbook 84 Np
PhotoCell & SolarCell 84 Np
Handbook 84 Np
Thyristor (S.C.R.) Handbook £1.00



NEW! SN74N SERIES TTL LOGIC

NOW FROM L.S.T. - FULL SPECIFICATION TEXAS INDUSTRIAL INTEGRATED CIRCUITS AT ECONOMY PRICES

Part No.	Description	1-49	50-99	100
SN7400N	Quad 2-input NAND gate			
SN7401N	Quad 2-input NAND gate open collector	32	27	22
SN7402N	Quad 2-input NOR gate			
SN7403N	Quad 2-input NOR gate open collector	35	30	25
SN7404N	Hex Inverter	32	27	22
SN7405N	Triple 3-input NAND gate			
SN7413N	Schmidt Trigger	45	40	35
SN7420N	Dual 4-input NAND gate			
SN7430N	8-input NAND gate	32	27	22
SN7440N	Dual 4-input NAND Buffer			
SN7442N	BCD to decimal decoder TTL output	£1.12	£1.00	88
SN7450N	Expandable Dual 2-wide 2-input AND-OR-INVERT gate			
SN7453N	Expandable 4-wide 2-input AND-OR-INVERT gate	32	27	22
SN7460N	Dual 4-input flip-flop			
SN7472N	J-K Master-Slave Flip-flop	45	40	35
SN7473N	Dual J-K Master-Slave Flip-flop	50	45	40
SN7474N	Dual D-type Edge-Triggered Flip-flop			
SN7475N	Quadrate Bistable Latch	45	40	35
SN7476N	Dual J-K Master-Slave Flip-flop with Preset & Clear	55	50	45
SN7483N	Four-bit Binary Full-Adder	£1.30	£1.20	£1.10
SN7490N	Decade Counter			
SN7492N	Divide-by-12 Counter	£1.12	£1.00	87
SN7493N	Four-bit Binary Counter			
SN74141N	BCD to decimal Decoder/Driver (Replaces the obsolete SN7441AN)	£1.45	£1.30	£1.15


MIX PRICES: Devices may be mixed to qualify for quantity price. Larger quantities - prices on application.

LINEAR AND DIGITAL I/C's

R.C.A.	FAIRCHILD	Linear	Digital
CA3004	£1.80	1-11	12-24
CA3005	£1.20	40 Np	35 Np
CA3011	75	40 Np	35 Np
CA3013	£1.05	53 Np	50 Np
CA3014	£1.25	Devices may be mixed to qualify for quantity price.	
CA3018	85		
CA3020	£1.30		
CA3028A	75		
CA3035	£1.25		
CA3043	£1.40		
CA3044	£1.20		
CA3046	75		
CA3047	£1.48		
CA3048	£2.05		
CA3049	£1.40		
CA3052	£1.45		

BARTEK OP-AMPS!!	MISCELLANEOUS
LM709C	TA263
LD1L high gain	TA293
LM741CN	TA310
LM7421P	TA312
LM7431P	TA313
LM7432P	TA314
LM7433P	TA315
LM7434P	TA316
LM7435P	TA317
LM7436P	TA318
LM7437P	TA319
LM7438P	TA320
LM7439P	TA321
LM7440P	TA322
LM7441P	TA323
LM7442P	TA324
LM7443P	TA325
LM7444P	TA326
LM7445P	TA327
LM7446P	TA328
LM7447P	TA329
LM7448P	TA330
LM7449P	TA331
LM7450P	TA332
LM7451P	TA333
LM7452P	TA334
LM7453P	TA335
LM7454P	TA336
LM7455P	TA337
LM7456P	TA338
LM7457P	TA339
LM7458P	TA340
LM7459P	TA341
LM7460P	TA342
LM7461P	TA343
LM7462P	TA344
LM7463P	TA345
LM7464P	TA346
LM7465P	TA347
LM7466P	TA348
LM7467P	TA349
LM7468P	TA350
LM7469P	TA351
LM7470P	TA352
LM7471P	TA353
LM7472P	TA354
LM7473P	TA355
LM7474P	TA356
LM7475P	TA357
LM7476P	TA358
LM7477P	TA359
LM7478P	TA360
LM7479P	TA361
LM7480P	TA362
LM7481P	TA363

Gerry Brown . . . ON THE FRINGE

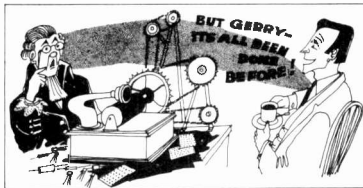

COUNTERPOINT

Isn't it quaint how, just when you think you've thought of a really good idea, it turns out to be one that someone else thought of, and probably patented, years ago! Just such an idea occurred to me last week.


For a long time now I have idly considered the possibility of designing a transistorised version of the early Regency musical box. Initially, as you may imagine, this was intended to be a relatively uncomplicated affair; but, like "Topsy", I got carried away and the thing just grew, and grew! It now comprises something approaching a cross between an Emmett automatic soup maker and a knitting machine that had mistakenly been programmed to fabricate a barbed wire vest!

After all this hard work (which, incidentally, was rewarded by it returning a fairly good rendering of Annie Laurie) my visions of untold fortunes accruing from this fantastic invention were dashed to the ground. "Oi!", said my old mate John over coffee, "did you know that 'Doom-watch' thing that's growing all over your study has already been invented?" I could hardly believe him, but there it was Patent Specification No. 1,173,747 . . . A Device for Composing and Playing Musical Motifs.

Since I had such a lot of fun making one of these machines I thought it would be interesting to include the basic design in this column. The electronics and associated mechanical principles are shown in Fig. 1.

The motor drives a rotary switch, via the reduction gearing, which sequentially connects pre-arranged wires from the oscillator to the positive supply rail. In this way it is possible to play short tunes of one's choice merely by running the motor.

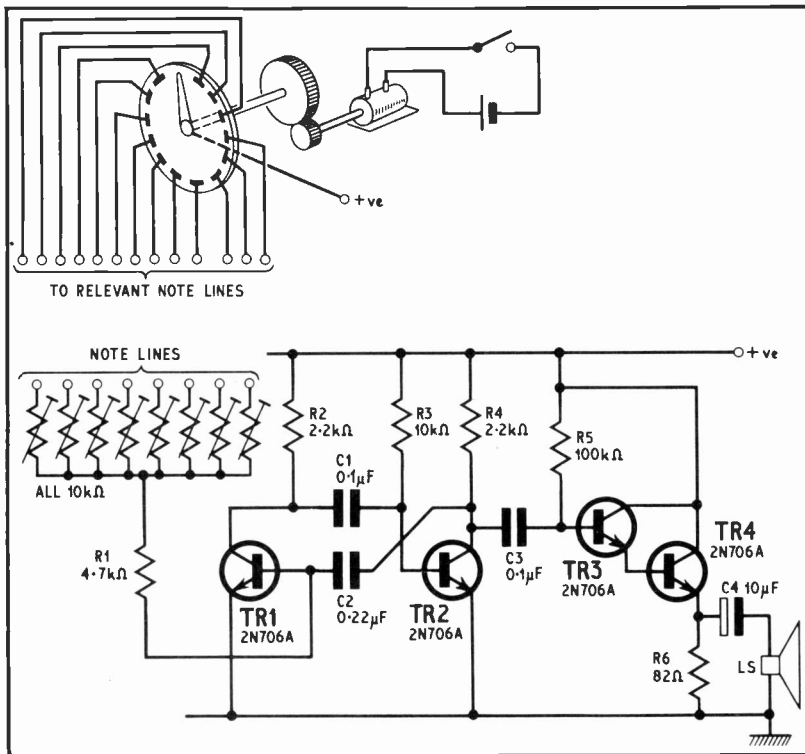Naturally, the set-up can be more sophisticated than this and have auto-switch off facilities as well, but this can be left to personal preferences. Certainly the device would make a rather novel door-annunciator, in fact, a solid-state version using a shift-register technique for selecting the notes would lend itself ideally to a composer-player machine.—What do you think?



SHELL-OUT

Just imagine how much must be lost to egg producers in uncooked omelets ever year! I am referring of course, to the "eggstra" cost involved in time, effort, and the replacement of busted produce



caused by "butter-fingered", and frequently rough, packaging machinery.

Apparently the cost to the U.S.A. alone each year for cracked or broken eggs due to this cause exceeds something to the tune of \$25 million. Not unnaturally, the U.S. Department of Agriculture has taken certain steps to reduce this high mortality rate and the result—the bringing into being of an electronic egg!

Having experimented with various materials for the "shell" of the gadget the research team finally settled on an acrylic plastic fashioned into the necessary shape, but hollowed out and having threaded halves so that the electronics embodied within could be serviced easily when required.

Incorporated inside the shell is a piezoelectric accelerometer coupled to a suitable amplifier which drives a telemetry transmitter so that the signals connected with the stresses undergone by the poor old crock can be monitored at a distance. A miniature mercury cell, also tucked away inside supplies all the power.

The electronic egg produces signals (as it goes through the routines connected with packaging) proportional to the degree of violence of its movement. To determine, in the case of a hen's egg, whether a crack or smash level has been exceeded requires the use of a pre-calibrated egg. The calibration, however, is a simple operation and it seems that such eggs have provided valuable data about critical areas in egg-handling machinery that could cause impacts severe enough to damage the cargo. Smashing!

TIME WARP

There was an error in the frequencies given for the two oscillators suggested for the long time-constant device outlined in the March issue. The frequencies should have been ten and six pulses per minute. Sorry about that.

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

METAL LOCATOR

Due to a recent television programme on buried treasure hunting, we have received numerous enquiries for information on metal locators. We would like to point out that we have in the past published three designs for metal locators (January 1969, January 1970 and October 1970 issues), but these are, unfortunately, now completely out of print and unobtainable—surely a good reason to place a regular order with your newsagent, as we will certainly publish another design as soon as practicable.

For those readers who are interested in metal locators, **Heath (Gloucester) Ltd.**, have just introduced a metal locator, in kit form, to their range of electronic audio/visual kits. Known as the Heathkit G.D.48, it comprises all components necessary to make an extremely sensitive metal locator.

It is claimed to be able to detect small coins up to 6in (15cm) below ground and very large pieces of buried metal up to a maximum 6ft (1.8m). The locator can be used to search for souvenirs, find buried treasure and hunt for lost jewellery or coins on beaches. The locator can also be used to trace buried pipes and conduits or detect under-surface hazards on farmland.

Powered by a 9V battery with a life of approximately 80 hours, the metal locator employs the induction balance method of detection. This ensures that no sound is emitted from the amplifier until such time as a metal object enters the search field.

When a metal object is located the amplifier gives off a piercing note, the intensity of this being somewhat relative to the proximity and size of the buried metal.

The locator is simple to operate, costs £32.80 and weighs 4lb, including battery. No specialised knowledge of electronics is needed to assemble the kit which takes approximately 6-8 hours to build and a step-by-step manual in pictorial form is supplied for this purpose.

A Post Office licence is required for use in the U.K. and an application form is included with the kit.

Full particulars of the G.D.48 Metal Locator is available from Heath (Gloucester) Ltd., Bristol Road, Gloucester.

PUBLIC ADDRESS AMPLIFIERS

Seen for the first time at the Sound '71 exhibition were the TA756 and TA757 professional P.A. Amplifiers from **Goldring Manufacturing Co. (GB) Ltd.**

The TA756 has an output of 30 watts, whilst the TA757 has an output of 60 watts. Both amplifiers have three microphone inputs plus one auxiliary input.

The amplifiers are fitted with 30 ohm plug-in internal transformers, but these can be changed for 200, 600 or 50 kilohm inputs. The outputs are 4, 8, and 16 ohms, and power supplies of 70 and 100V via a strip panel or octal plug are available.

Each microphone channel has a switched bass-cut filter, and other facilities include a remote control relay precedent switch.

Full technical information on the amplifiers and other public address equipment is obtainable from Goldring Manufacturing Co. (GB) Ltd., 10 Bayford Street, Hackney, London, E.8. 35E.

EQUIPMENT CASES

Instrument cases, type 1 and 2, finished in hammer blue with a contrasting grey front panel are the latest product from **Radiospares Ltd.** Available through dealers, the cases are supplied in flat-packed form complete with feet and assembly instructions.


The two types available are, type 1 which measures: width 10in (254mm), depth 7½in (197mm) and height 6¼in (159mm). Type 2 measures: width 16in (406mm), depth 7¼in (197mm) and height 6¼in (159mm).

BATTERIES


Seven new zinc carbon battery types are now being marketed by **Mallory Batteries** for general electrical and electronic apparatus.

The zinc carbon range covers all the standard types in common use at the moment, i.e. M1602 (PP6), M1603 (PP9), M1604 (PP3), M1605 (PP7), M13R (SP2), M14R (SP11) and M15R (H7). The numbers in brackets represent Ever Ready type numbers.

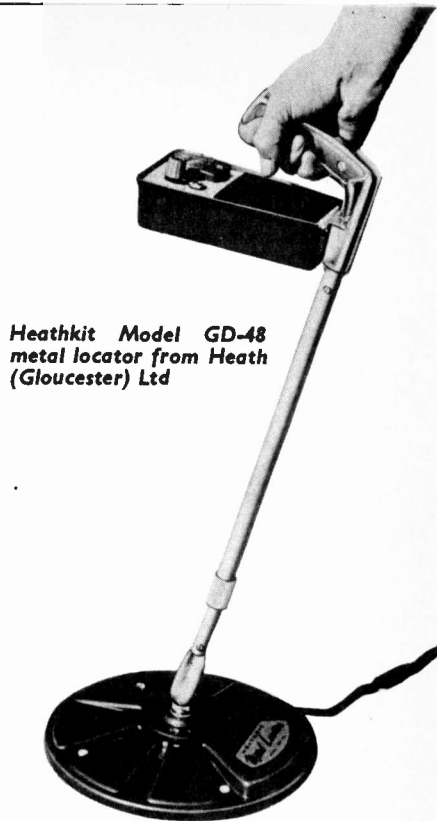Details of nearest stockists and prices can be obtained from Mallory Batteries Ltd., Gatwick Road, Crawley, Sussex.



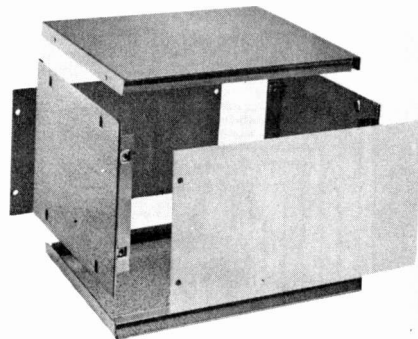Heathkit Model GD-48 metal locator from Heath (Gloucester) Ltd



Radiospares instrument case



Range of zinc carbon batteries now being marketed by Mallory Batteries

LOW COST ELECTRONIC & SCIENTIFIC EQUIPMENT & COMPONENTS

MOTORS

CONTINUOUS TAPE CASSETTE



Suitable for sleep-learning, teaching programmes, programming machines tools, telephone answering, etc. Complete with replay/record head and separate erase head; 1/4 in tape single track. Speed 3 1/2 in per sec. Length of tape 88ft, but will hold three times this amount. 230V 50Hz supply. £4.50. Post free.

DIGITAL INDICATORS KGM TYPE M3

A neat compact indicator providing selective display 0-9. Fig.Ht. 18mm. Panel mounting. 6mm tubular midjet flange lamps. Supplied with 28V bulbs. Finished matt black anodized. W. 1in, H. 2in, Wt. 4oz. £3.25. Post free.



SINGLE SPEED TAPE DECK



1/4 in single track on 7in spools. 1 1/2 in per sec. 3 motors. Capstan 240V, others 130V. Series operated. Facility for remote control operation. Record/replay heads with separate erase head. Ex equipment. Less spools. Bargain price: Deck only no plinth, £5.95. P. & P. 75p. Buy now while stock exists.

KEYNECTOR

Connects anything electrical in seconds without plugs or sockets. No more worries about dangerous live wires. Now you can make electrical connections safely, in seconds with the revolutionary new Keynector. Cuts out plugs, sockets and saves time. A hundred different uses in the home, and a must for the do-it-yourself enthusiast. Only £2.33 plus P. & P. 25p. Or send for a leaflet.



GRAMPHON AMPLIFIERS

Type 385B. 50W mains powered. 200 ohm O/P. Audio Power Amplifiers. Only a few available. Selling at well below list price: £15.50 each. Carriage £2.

TELEPHONE DIALS

Clear Perspex, very good condition. No markings. 75p each. P. & P. 25p.

LOW TORQUE HYSTERESIS MOTOR MA23

Extremely quiet running motor with high starting torque. Has many uses such as chart drives, disc-theque colour wheels, etc. 1/20 r.p.m., 1/12 r.p.m., 1 r.p.m., 120V 50Hz, 1/12, 1/18, 1/24, 1/240 r.p.m., 1/20, 1/60, 1/116, 1/15, 1 r.p.m., 20 r.p.m. £1.50 post free.



SYNCHRONOUS MOTORS

200/250V 50Hz. New condition, ex-equipment. 8.7 1 r.p.m. and 1 r.p.m. Self starting, complete with gearing shaft 1/4 in dia., 1/4 in long. £1.50.

ELECTRIC CLOCK MOTOR

NEW 200-250V, 50Hz, 2W. Synchronous induction motor. 2 revs. per hour. O/P shaft, 1/4 in dia. x 1/4 in long. Clockwise rotation. Three-hole mounting at 120° on 2in PCD. Price £1 post free.

GOOD QUALITY INSTRUMENTS TAKEN IN PART EXCHANGE OR PURCHASED FOR CASH!

BRAND NEW CAPACITOR REVERSIBLE SINGLE PHASE PARVALUX MOTORS
230/250V, 50Hz, 2,800 r.p.m.; 1/30 h.p. cont. rated; 1/4 dia. shaft; 3/16 in foot mounting; wt. 6lb. £5.75. Post free.

E.H.T. GENERATOR. BRAND NEW D.C. CONVERTER MULLARD TYPE 1049
Input 12V d.c., 0.3A. Output, 1,800V (min.) at 1mA, 2,000V (min.) on no load. Full spec. and circuit provided. Encapsulated module. L. 5in, W. 2 1/2 in, H. 1 1/2 in. £5.50. Post free.


DELAY LINE LEXOR MDN 2484D
Miniature resin encapsulated module. Total delay 50nsec to 10msec. Tapped at 10% intervals. Impedance 75 ohms to 10k Ω. 30V wkg. Attenuation 0.5 dB/msec. 2 1/2 in x 1 1/2 in x 1/2 in. £1.50. Post free.

BATTERY OPERATED TRANSISTOR TESTER

Battery powered for checking leakage current and gain of P.N.P. transistors, meter and audio indication. Siemens Ediswan Type R2285. W. 7 1/2 in, H. 4 1/2 in, D. 2in. £5.50. Post free.

MEMORY CORE STORES

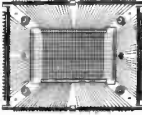42 x 52. 2k Ω bit ferrite core store. O/W quantity 0A10 load diodes. Ideal for building computer store, holding information, teaching experiments, demonstrations, etc. Price £2.25. P. & P. 35p.



NEW ENICRON SHADED POLE MOTORS
240/250V, 50Hz, 2,500 r.p.m. (no load). Shaft 3/16 in dia. x 1 1/2 in long. Suitable record player, blower motor, etc. 65p. Post free.

NEW FRACTIONAL H.P. CAPACITOR MAINS MOTORS
240/250V, 50Hz, 0.65A. 1/20 h.p., 2,850 r.p.m. Cont. rated. Shaft 3/16 in dia. x 1 1/2 in long. Circular clamp mounting. £3.50. Post free.

GENERAL PURPOSE RELAY

TMC Type GPR 300. Coil 700 ohm 12V. 4 x 1A changeover contacts. Plug in base. Price 5 for £1.75. Post free.



NEW MICROSWITCHES—HONEYWELL

1 PL 960 6 contacts. 15 Amp. 125/250 volts. Single pole. ON/OFF. Plunger operated. L. 1 7/8", W. 5/8", H. 3/4". Price 5 for £1.25. Post free.

RESET TIMERS — ACRO TIMER BY HAYDON

Synchronous motor driven timer providing manual adjusted delay. Delay time is set on graduated dial. Press button closes contact and drives motor which drives an arm until it actuates the load switch. The can then return to initial position for repeat action. Various ranges available. 230V 50Hz. Load contacts 15A 230V. £5.

WIDE RANGE OF PRECISION MULTI-TURN POTENTIOMETERS IN STOCK

EXTENSION TELEPHONES

Complete with dial. Suitable for numerous applications. Two for £2.70. Post free. Telephones less bells. Two for £2. Post free.



MEMORY PLANES

Ferrite core memory planes with wired Ferrite cores. Used for building your own computer or as an interesting exhibit in the demonstration of a computer. Mounted on plastic material, frame 5 x 3in. Consisting of matrices 40 x 25 x 4 cores each one individually addressable and divided into 2 halves with independent sense and inhibit wires. £6.50. P. & P. 15p.

LINEAR THYRISTOR CONTROLLED LIGHT DIMMER—BRAND NEW

High grade full wave bridge circuit gives linear control of light brightness. Ideal for controlling room lighting and a.c./d.c. commutator motors fitted to portable electric hand drills. Fits standard 2in conduit box. 240V, 50Hz, 400W. Price £2.99. P. & P. 13p.



MINIATURE MOVING COIL RELAY S115

By Sangamo Weston, suitable for D.C. circuit. A high sensitivity relay more sensitive than the electromagnetic type. Single Coil Resistance 310 micro amps. 315 Ω. List price £4.50. Our price £1.15.

6 DIGIT RESETTABLE COUNTER

Totalising 240V 50Hz. Viewing window 2in x 3/4 in. Ex-equipment. Price £2.75. P. & P. 25p.

6 DIGIT TOTALISING NON-RESETTABLE COUNTER

Mechanical operation. Chromium finish. Length 1 1/2 in x 3/4 in x 3/4 in with viewing window 2in x 3/4 in. Ex-equipment. Price 45p. P. & P. 13p.

BERKELEY DECIMAL COUNTING UNIT 0-9

Direct reading octal base plug in unit electronic counter. The number counts received is indicated by one of ten neon lamps behind acetate panel. The unit counts from 0-9 the tenth pulse resetting to zero and simultaneously generating an o/p signal. Circuits can be connected in cascade. Power supply 6.3V d.c. Cut on/Cut off 15V. Price £3.50 p. & p. free.



MINIATURE DIGITAL DISPLAY

Operates on a rear projection 6.3V pilot lamp. Character size 1/4 in high. 0-9 digits with degree symbol, i.e. (4°). Dimensions 1 1/2 in wide, 3/4 in deep, 1 1/4 in high. List price 6 pns. Our price £2.73.



1in characters £3.
4in characters £9. Post free.

EAC DIGIVISOR Mk. II DIGITAL READ-OUT DISPLAY

Uses a sensitive moving coil movement to project digits 0-9 on to a viewing screen via an optical lens system. Image height 1/4 in. Lamp 6.3V. Sensitivity 250 micro-amp. Dimensions L. 4 1/2 in, W. 2 1/4 in, H. 1 1/2 in. Price £3.50. P. & P. 25p.



OVERHAULLED AUTOMOTORS Models 40, 47A, 48A. (Models 47A and 48A are Admiralty pattern).

D.C. volts: 0-12, 1-2, 12, 120, 400, 1,200.
Amps: 0-12, 0-12, 1-2, 12, A.C. volts: 12, 120, 480, 1,200.
Amps: 0-0.12, 0-12, 1-2, 12.
Ohms: 1,000, 10,000, 1,000,000 (external voltage source).
Sensitivity: 166.6 Ohms/Volt, 333.3 Ohms/Volt when divided by two button is pressed on both a.c. and d.c. ranges.
£16. P. & P. 75p.
Complete with voltage multiplier for 480V and 3,600V. Current shunts for 120A and 480A. A.C. current transformer for 20A and 60A. In special wooden box. £18.50. P. & P. £1.
Due to demand it may not always be possible to supply a particular model, and a different type to that ordered may be dispatched. These models are electrically identical.



STOCK CLEARANCE

All items are sold in as seen condition.
CHEEK BOARD RECEIVERS. Model 7B. £15. Carriage £3.
OSCILLOSCOPE CO880R 1045. £10. Carriage £3.
OSCILLOSCOPE EMI TYPE WMS PORTABLE. £16. Carriage £2.
VALVE VOLTMETER. Arzhebi 378B/2. 1m 5 ranges. £2.50. Post free.
RF SIGNAL GENERATOR. RCA Type 710-A. I/P 117V, 60Hz, 50W. 370-560 MHz modulation. Carrier (metered) scaled O/P. £15. Carriage £1.50.
VALVE VOLTMETER. Marconi FT428. a.c./d.c. 5 ranges 1.5V. £3. Carriage £1.50.

WIDE RANGE OSCILLATOR. Dawes type 400C. 0.1Hz-1kHz. O/P control. C.R.T. monitor. £10. Carriage £2.50.
ONE ONLY—Type 400A. 20Hz-20kHz. O/P control (metered). O/P Z 500, 600, 2,000 ohm. £2. Carriage £2.50.
VALVE VOLTMETER CT54 MICROVAC. A.C./D.C. plus ohms. 6 ranges, 2-4-480V. 1kΩ-10MΩ in 5 ranges. Probe facility battery powered. Very good condition. £16. Carriage £1.
VOLTMETER "AS NEW". Ex GPO. Superior quality 2in moving coil 200 ohms/volt. A.C./D.C. 0-150V and 0-300V. Mirror scale. Ernest Turner Model 32 in leak carrying case. 10 1/2 in x 8 1/2 in x 4 1/2 in. £10. Post free.

MIDGET POWER RELAY ONHON Mk I
230V, 50Hz, 1PDT new. Faulty plating on frame. 5 for £1.50. Post free.

NUMICATOR PRICE LIST

End Reading	Quantity	Price each (less base)
1-3	1	£1.40
4-10	1	£1.35
11-25	1	£1.30
26-100	1	£1.20

Price Base. Bases 20p each.

Side Reading	38mm/m Lead	(Amber)
XN3/FA	38mm/m Lead	(Red)
XN3/F	38mm/m Lead	(Red)
XN3A/F	6mm/m Lead	(Clear)
XN3A	38mm/m Lead	(Red)
XN11/F	38mm/m Lead	(Amber)
XN23/FA	38mm/m Lead	(Amber)

1-3 £1.15 each
4-10 £1.10 each
11-25 £1.05 each
26-100 95p each

All Post Free

NEW LOW INERTIA INTEGRATING MOTORS

Electro-Methods Models 901 and 906PL. Permanent magnet d.c. motor. High sensitivity. Ideal for instrument-type servo-mechanisms, light loads, driving mechanical counters performing integration, or as small power generators. Will operate directly off a photo-cell or thermocouple, etc. Nominal typical parameter. Starting voltage (no load) 15mV at 0.375mA. Full load speed 1,845 r.p.m. (approx.). Moment of inertia of armature 1.8g cm/cm. Weight of Motor 300g. (approx.). £15. P. & P. included.

RAPID HEAT SOURCE . . .

from brand new Infra Red Tubular Quartz Lamps. Ideally suited as heat source for Drying Ovens, Egg Hatching, Incubators, etc. 240V, 1,440W, 20,000 Angstroms. Length 12in x 1/4 in dia. Price 75p. P. & P. 25p.

ELECTRONIC BROKERS LTD.
(Dept. PE), 49-53 PANCRAS RD · LONDON NW1
01-837 7781 · TELEX 247307
Open Mon.—Fri. 9—6 p.m.



LIND-AIR AUDIO

C.1001 MULTI-TESTER

Overload protection
20,000 per volt;
a.c. volts 10, 50,
250, 1,000V; d.c.
volts 0-25, 125, 500,
2,500V; d.c. current
0-50mA, 0-250mA;
Resistance 0-60kΩ
0-6MΩ; decibels
-20 to +22dB. Size
of meter 4 1/2 in x 3 1/2 in. Complete with
case. **£4.25**. P. & P. 17 1/2 p.

C.1050 MULTI-TESTER


Ranges:
D.C. Voltage: 0, 3,
15, 150, 600, 1,200V
(10,000Ω per V).
A.C. Voltage: 0, 6,
30, 300, 1,200V
(5,000Ω per Volt).
D.C. Current: 0-120mA
0-300mA.
Resistance: 0-50kΩ, 0-5
MΩ (R x 10)
(R x 1K). Decibels: -20 to +17dB.
£5.97 1/2. P. & P. 17 1/2 p.

C.1052 MULTI-TESTER

Ranges:
A.C. Voltage: 6, 30,
120, 300, 1,200
(15,000Ω/V).
D.C. Voltage: 0-6, 3,
15, 60, 300, 1,200
(30,000Ω/V). D.C. Current: 0, 0.03, 3, 30,
300mA. Resistance: 0, 6Ω, 60Ω, 600Ω,
6MΩ. Decibels: -20 to +63dB. **£7.35**.
P. & P. 17 1/2 p.

E.M.I. LOUDSPEAKERS

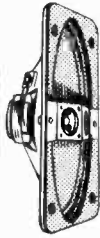MODEL 450, 13 1/2 in x 8 in
elliptical with twin tweeters.
8Ω impedance. 10 watts.
Brand new, guaranteed.



Lind-Air Price
£3.97 1/2
P. & P. 22 1/2 p each.

MODEL 150, 13 1/2 in x 8 in
elliptical, 3 and 15Ω
impedance. 10 watts.

Lind-Air Price
£2.97 1/2
P. & P. 22 1/2 p each.

SANYO 10F892 PORTABLE FM/AM RADIO

7 transistor plus one
integrated circuit for
excellent FM reception.
Covers FM 88-108 MHz,
AM 540-1605 KHz. Slide
rule tuning dial, rota-
table telescopic aerial.
Complete with case and
carphone. Size 3 1/2" x
4 1/2" x 1 1/2" (Batteries 4 x
HP7 not included). Rec.
Price **£10.35**
LIND-AIR PRICE **£9.25** P. & P. 30 p.



GARRARD HI-FI TURNTABLES




2025 T/C with stereo cartridge **£8.97 1/2**
3000 with Sonotone 9TAHCD stereo
cartridge **£10.97 1/2**
SP25 Mk. III **£11.97**
SL65B **£15.97 1/2**
Base and cover for above **£2.97 1/2**
AP76 **£19.50**
SL72B **£24.97 1/2**
SL75B **£28.35**
SL95B **£39.45**
Base and cover for above **£8.97 1/2**
401 **£28.50**
P. & P. Decks, 62 1/2 p; Base and Cover, 50p;
Deck/Base/Cover, 87 1/2 p.

THIS MONTH'S SPECIAL OFFERS!

SP25 Mk. III with base **£12.97 1/2**
P. & P. 75p.
SP25 Mk. III with Sonotone
9TAHCD cartridge and base **£15.77 1/2**
P. & P. 75p.

S-DeC BREADBOARD

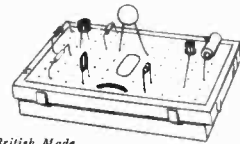

British Made
Solderless breadboard panels, for fast
reliable component connections.
Single DeCs. One S-DeC with Control
Panel, Jig and Accessories for solderless
connections to controls, etc., with booklet
"Projects on S-DeC" giving construction
details for a variety of circuits. **£1**.
P. & P. 17 1/2 p.
4-DeC KIT. Four S-DeCs with two Control
Panels, Jigs and Accessories and the book-
let "Projects on S-DeC" all contained in a
strong attractive plastic case. Ideal for
the professional user. **£3.95**. P. & P. 17 1/2 p.
T-DeC KIT **£2.50**. P. & P. 17 1/2 p.
S-DeC STOR **£2.50**. P. & P. 17 1/2 p.

WELLER "EXPERT" SOLDERING GUN

Comfortable and easy to use.
240V AC. Instant dual
heat 100/140 watt with
two position trigger
control. **£3.37 1/2**. P. & P. 27 1/2 p.



18/19, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.
Tel: 01-580 2225/7679
Open 9-6 Mon-Sat (Thurs until 7)

All Mail Orders and inquiries to Dept. PE5,
Kirkman House, 54a Tottenham Court Road,
London, W.1. Tel: 01-887 1801.

94-96, UPPER PARLIAMENT STREET, NOTTINGHAM
Tel: Nottingham 40403 (STD 0602)
Open 9-6 Mon-Sat (Weds until 7.30)

G. F. MILWARD

Mail Orders: DRAYTON BASSETT, TAMWORTH, STAFFS ELECTRONIC COMPONENTS

Wholesale/Retail: 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE ! ! ! !

RESISTORS, 1/4 watt
assorted 100 50p
Wire-wound 1 to 3 watt 20 50p
5 to 7 watt 15 50p
10 watts 10 50p
Multi-tapped 42 50p
PAPER CONDENSERS
TV types 50 50p
Miniature 100 50p
ELECTROLYTIC CONDENSERS
Suitable for Mains
Radio/TV 10 50p
Transistor types 20 50p
Mixed (both types) 15 50p
POLYSTYRENE CONDENSERS 100 50p
MULLARD POLYESTER COND. 100 50p
SILVER MICA WIRE-WOUND 3-Watt SLIDERS 15 50p
VOLUME CONTROLS.
Assorted 5 50p
NUTS AND BOLTS. Mixed length/type
8 B.A. 100 50p
6 B.A. 100 50p
4 B.A. 100 50p
2 B.A. 100 50p
METAL SPEAKER GRILLES 7 1/2 in. x 3 1/2 in.
EARPIECES, Magnetic
No Plug 6 50p
2.5mm Plug 4 50p
3.5mm Plug 4 50p
500 MICRO-AMP LEVEL METERS 1 50p
VEROBOARD, TRIAL PACK 5 BOARDS + CUTTER 50p

TRANSISTORS
P.N.P. Untested but mainly O.K. 50 50p
N.P.N. Untested but mainly O.K. 50 50p
OC71 equivalent 5 50p
Light-sensitive Diodes 10 50p
(These produce up to 1 ma from light)
OC44 Mullard 1st grade 4 50p
OC45 Mullard Boxed 4 50p
2G378 Output, Marked 4 50p
2G371 Driver, Marked 4 50p
ASY 22, Marked 5 50p
BY 127 Rectifiers 4 50p
IN4007 Rectifiers 4 50p
(1,200V peak)
STC 3/4 Rectifiers 6 50p
DIODES (0A 81 & 0A 91) 40 50p
WIRE:
Solid Core. Insulated 100yds. 50p
Stranded ditto 50yds. 50p
SOLAR CELLS.
Large Selenium 2 50p
Small 3 50p
(6 cells will power a Micromatic radio)
COAXIAL CABLE.
Semi Air-spaced 15yds. 50p
CRYSTAL TAPE RECORDER MIKES 1 50p
CRYSTAL EARPIECES 3.5mm Plug 2 50p
TRANSISTORISED Signal Injector 1 50p
TRANSISTORISED Signal Tracer 1 50p
TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 ma meter as indicator) 1 50p

SINCLAIR AMPLIFIERS AND SPEAKERS. Complete range in stock! All at 10% discount on list.

VEROBOARD
2 1/2 in x 1 in x 0.15 in 6p
5 in x 3 1/2 in x 0.15 in 28p
3 1/2 in x 2 1/2 in x 0.15 in 16p
17 in x 2 1/2 in x 0.15 in 55p
5 in x 3 1/2 in x 0.15 in 20p
17 in x 3 1/2 in x 0.15 in 74p
5 in x 2 1/2 in x 0.15 in 20p
3 1/2 in x 2 in x 0.15 in 21p
Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0.1 or 0.15) 36 for 18p. Special Offer Pack consisting of 5 2 1/2 in x 1 in boards and a Spot Face Cutter—50p.

TRANSISTORISED FLUORESCENT LIGHTS. 12 volt. All with reverse polarity protection. 8 watt type with reflector, suitable for tents etc., £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch. 22 in x 2 in x 1 in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.

MULLARD POLYESTER CONDENSERS
1,00pf, 1,200pf, 1,500pf, 1,800pf, 2,200pf, 15p per dozen (all 400V working).
0.15µf, 0.22µf, 0.27µf, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

RESISTORS
1/2 and 1 watt. Most values in stock. 50p per 100. 10p per dozen of any one value. WIRE WOUND MAINS DROPPERS. Hundreds of values from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS
Large range in stock, 75p per 100 of any one value. 15p per dozen.

RECORDING TAPE BARGAIN! The very best British Made low-noise high-quality Tape! 5in Standard 38p. Long-play 45p. 5 1/2 in Standard 45p. Long-play 60p. 7in Standard 60p. Long-play 82p. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock at these low prices?

NEW! PRODUCE YOUR OWN PRINTED CIRCUITS ! ! ! ! !
Our new aerosol sprays now make it possible to produce printed circuits either singly or by the hundred from one simple drawing!
Either photo-copy circuit or trace it on to clear plastic sheet.
Place same on copper laminate board which has been sprayed with our "Photo-lacquer" and expose to light.
Now spray with developer and circuit will appear ready for etching.
"Photo-lacquer" £1 per can. Developer 50p per can.

RECORD PLAYER CARTRIDGES. Well below normal prices!
G90 Magnetic Stereo Cartridges, Diamond Needle, 5mV output, £4. ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible, Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1.25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1.63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1.50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1.88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1.25.

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 10p.

WINDSCREEN WASHER TIMER

By P. HANCOCK B.Sc.

THE MAIN advantage of fitting an electric windscreen washer to a car is that a continuous jet of water is available as opposed to the intermittent jet from a manual pump. However, in practice, much of the advantage is lost since modern driving conditions do not leave a hand or foot free for more than an instant or two. A means for delivering a jet of selected duration at a momentary touch of the button, is desirable.

A "remnant" relay could be used to give a timed action but these are relatively expensive and, in any case, are non-adjustable. A resistance capacitance circuit suggests itself as a means of establishing the necessary time constant.

The standard washer pump circuit is shown in Fig. 1, and Fig. 2 shows a basic timing circuit which would work, but in order to achieve the necessary time constant would require much too large a capacitor; typically 16,000 μ F for a ten second hold using a 600 ohm relay.

FUNDAMENTAL IDEAS

The basic circuit of Fig. 2 functions in the following manner. When S1 is pressed for a moment, RLA1 contacts connect to the supply and allow current from the battery to charge C1 via the relay coil. At the same time, the pump motor is switched on by the second set of contacts RLA2. The relay continues to hold itself latched until capacitor C1 is sufficiently charged to cause the charging current to fall below the value necessary to hold the relay on. Contacts RLA1 then change back to the original state, shorting out C1 ready for the next cycle. The resistor R1 is necessary to prevent too great a surge of current through the relay contact points. Requiring such a large capacitor, the physical circuit is bulky and costly; we need to increase the effective impedance of the relay.

A useful increase of impedance can be obtained using a single transistor arranged in an "emitter-follower" type circuit. With most general purpose

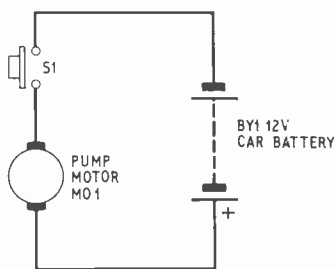


Fig. 1. Basic circuit diagram of an electric washer system


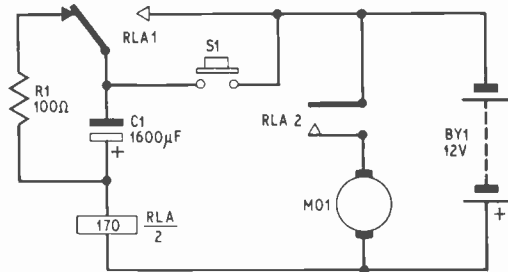


Fig. 2. Basic timing circuit

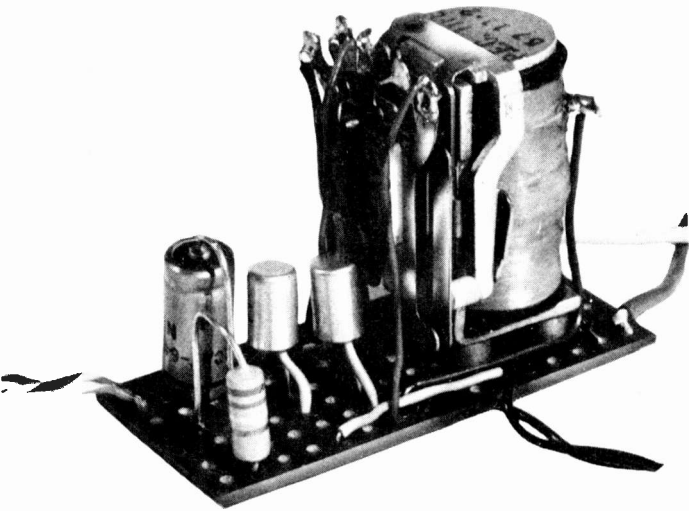

transistors, the input impedance can be raised by a factor of at least 30. However, a capacitor of $500\mu\text{F}$ is still needed.

FINAL CIRCUIT

A second transistor in a similar configuration will again raise the impedance by a similar figure, making the necessary capacitor (for a ten second "dwell" time) about $16\mu\text{F}$. We can now control the resistance of the time-constant circuit by putting a variable or a selected fixed resistor R1 in parallel with the input (see Fig. 3). Because of variations in components, especially cheap "reject" transistors, it may be necessary to experiment with values for R1 and C1. It was found in practice that a three second jet is adequate and using the transistors indicated, R1 is 22 kilohms and C1 $20\mu\text{F}$; these values provide a good starting point. Resistor R1 could be changed to a 500 kilohm potentiometer, which, set at maximum, would probably empty the bottle in a single continuous shot.

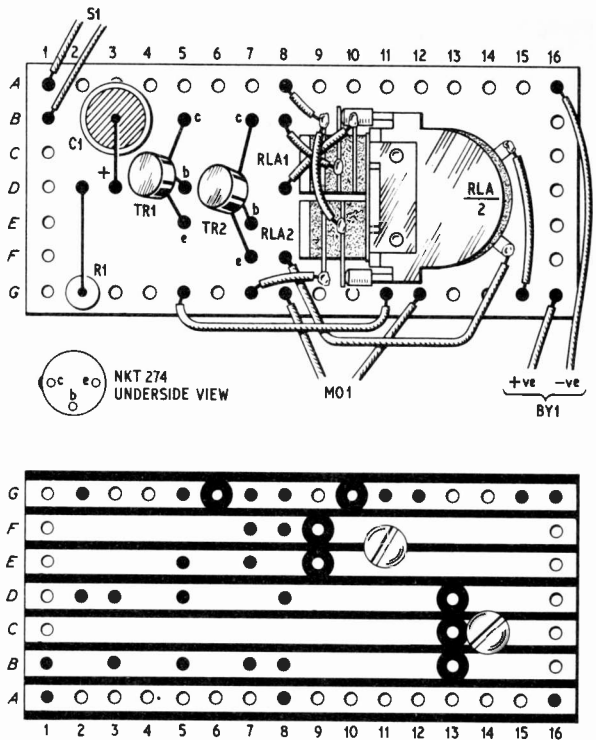



Fig. 4. Layout and wiring of the timer on Veroboard

CONSTRUCTION

The prototype was built on Veroboard and mounted in a plastic photographic slide box under the dash board. It has proved completely reliable in service over six months.

The layout on Veroboard is shown in Fig. 4, this is not at all critical. The relay specified is a miniature 170 ohm, 6 to 12V type, the contacts of which are rated at 2 amp. Any relay having a coil resistance of 150 ohms or more, with one set of changeover contacts and one pair of "normally-open" contacts, rated at 2 amp, will do, so long as it will operate on 12 volts. If the relay is mounted on the Veroboard as in the prototype, rather than separately, some

Fig. 3. Circuit diagram of the windscreen washer timer

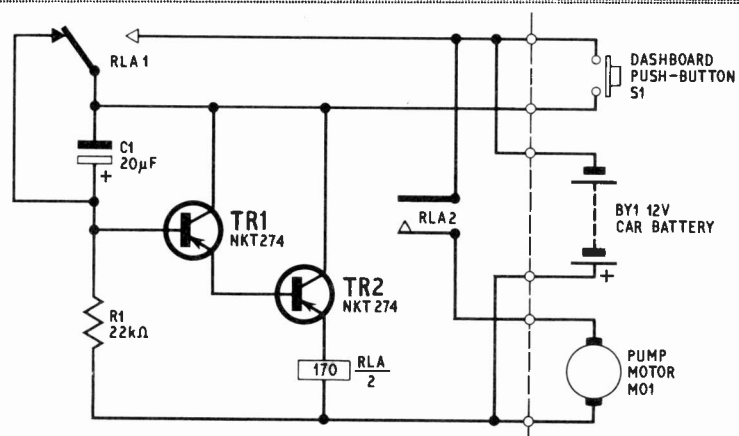

STEPHENS

ELECTRONICS
P.O. BOX 26
AYLESBURY
BUCKS.

SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded

The Diamond Tip is .007in radius, thus making it compatible to play stereo records on mono equipment without damage to the record; and of course full stereo.
BRITISH MADE
EXPORT ENQUIRIES WELCOME

CARTRIDGES

Inc. P.T. each		Inc. P.T. each	
AC08			
GP79	88p	SX5M	8/8
GP91-18c	£1.05	SX5H	8/8
2-11	89p	SX5M	D/8
12-49	77p	SX5H	D/8
50-500	57p	X4N	D/8
(FP91-28c)	As above		
(GP91-38c)	As above		
Suitable to replace TC9, etc.			
GP92	£1.32	GOLDRING	
GP93-1	£1.24	850	25-25
GP94-1	£1.55	908A	27-35
(GP94-5)	£1.80	G800E	£15
GP95	£1.24	G800E	£15
GP96	£1.24	G800 Super E	£19-50
Acos 104 1-10	£2.00	RONETTE	
11-25	£1.99	105	8/8 99p
26-50	£1.81	106	8/8 99p
51-499	£1.77	DC400	8/8 70p
		DC400SC	8/8 70p
		105	D/8 £1-12
		106	D/8 £1-12
		DC400	D/8 84p
		DC400SC	D/8 84p
		SONOTONE	
		8TA	D/8 £1-25
		8TA	D/8 £1-79
		8TAHC	D/8 £1-79

STYLII

Sapphire		Diamond		ELAC K8T9		Sapphire		Diamond	
AC08		GP59	15p	ELAC	(FE1B)	25p	47p		
		GP65	15p		ER5MB	25p	47p		
		GP67	15p		ER5MX	15p	37p		
		GP73-1	35p		ER5SB	35p	47p		
		GP73-2	35p		ER60 Stereo	35p	47p		
		GP79	15p						
		GP81-1	15p		DECCA				
		GP91-1	35p		Derram diamond only	£1.80			
		GP91-2	35p		GARRARD				
		GP91-3	35p		EV26 Stereo	15p	37p		
		GP91-18c	35p		GC2	15p	37p		
		GP91-38c	35p		GC8	15p	37p		
		GP93-1	35p		GC812	15p	37p		
		GP94-1	35p		GC810/1	15p	37p		
		GP95-1	35p		81-2-3	35p	47p		
		GP96	85p		T81	35p	47p		
		HGP37	15p		T82	35p	47p		
		104	35p		T83	35p	47p		
					GOLDRING				
B.S.R.		BSR CI (8T3)	35p	47p	CM50	15p	37p		
		BSR TC8H	15p	37p	CM60	15p	37p		
		BSR TC8M	15p	37p	MX1	15p	37p		
		BSR 8T8	35p	47p	MX2	15p	37p		
		BSR 8T9	35p	47p	Stereo C880	15p	37p		
		BSR 8T10	45p	57p	PERPETUUM EBER				
		BSR X1M	35p	47p	PE188	35p	47p		
		BSR X1H	35p	47p	PHILIPS				
		BSR X3M	35p	47p	AG3018	15p	37p		
		BSR X3H	35p	47p	AG3063	15p	37p		
		BSR X5H	35p	47p	AG3306	35p	47p		
		BSR X4H	35p	47p	AG3310/3306	35p	47p		
					AG3400	15p	37p		
COLLARO		Collaro Studio	15p	37p	RONETTE BIOMFLUID				
		Collaro-Ronett	15p	37p	BF40	15p	37p		
		TX88	15p	37p	DC284	15p	37p		
		Collet SK1	15p	37p	SONOTONE				
		Dual CDB2/CD83	35p	47p	2T	35p	47p		
		Dual CDS/320	35p	47p	3T	35p	47p		
		(DN3)	35p	47p	8T4A	35p	47p		
		ELAC K8T9	35p	47p	9TA	35p	47p		
		(PE10)	35p	47p	9TA/HC	35p	47p		
					19T	35p	47p		
					20T	15p	37p		

MAGNETIC RECORDING TAPES by a leading manufacturer

POLYESTER				POLYESTER			
Length	Spool Size in.	Price		Length	Spool Size in.	Price	
Standard Play				1200ft	5	70p	
600ft	5	50p		1800ft	7	£1.85p	
800ft	7	63p		Double Play			
1200ft	7	70p		1200ft	5	£1.70	
Long Play				1800ft	7	£1.80	
210ft	3	27p		2400ft	7	£1.80	
450ft	4	43p					

EMPTY TAPE REELS

3in	7p
4in	9p
5in	11p
7in	13p

CASSETTES

Boxed in Plastic Library Packs
 C60 55p
 C90 65p
 C120 87p
 P. & P. 7p on all orders.

SEMICONDUCTORS • BRAND NEW • MANUFACTURERS' MARKINGS • NO REMARKED DEVICES

2N388A	62p	2N2913	35p	2N3708	17p	2N5267	42-62p	AC128	20p	BC115	32p	BD132	97p	BFY41	50p	GET113	20p	NKT242	20p	OC20	75p
2N404	22p	2N2914	30p	2N3709	17p	2N5305	37p	AC154	22p	BC116	62p	BDY10	£1-37p	BFY43	62p	GET114	20p	NKT243	65p	OC22	50p
2N696	20p	2N2946	57p	2N3710	20p	2N5306	40p	AC176	20p	BC117	62p	BDY11	£1-87p	BFY50	22p	GET118	20p	NKT244	17p	OC23	50p
2N697	20p	2N2947	32p	2N3711	20p	2N5307	37p	AC187	62p	BC118	37p	BDY17	£1-87p	BFY51	22p	GET119	20p	NKT245	20p	OC24	57p
2N698	20p	2N2948	30p	2N3712	20p	2N5308	37p	AC188	37p	BC119	37p	BDY18	£2-47p	BFY52	22p	GET120	52p	NKT261	20p	OC25	50p
2N699	62p	2N2949	30p	2N3713	21-50p	2N5309	37p	AC189	27p	BC121	20p	BDY19	£2-12p	BFY53	22p	GET123	12p	NKT264	30p	OC26	35p
2N706	12p	2N2950	30p	2N3714	21-50p	2N5354	27p	ACY18	20p	BC122	20p	BDY20	£1-32p	BFY54	67p	GET126	85p	NKT271	20p	OC28	35p
2N708	16p	2N2951	30p	2N3715	21-50p	2N5355	27p	ACY19	25p	BC125	55p	BDY61	£1-80	BFY75	30p	GET128	20p	NKT272	20p	OC29	75p
2N709	16p	2N2952	30p	2N3716	21-50p	2N5356	27p	ACY20	25p	BC126	55p	BDY62	£1-80	BFY76	42p	GET129	22p	NKT274	20p	OC35	40p
2N718	20p	2N2953	40p	2N3717	21-50p	2N5357	27p	ACY21	25p	BC134	57p	BDY61	£1-80	BFY77	57p	GET130	22p	NKT275	20p	OC38	40p
2N718A	30p	2N2954	40p	2N3718	21-50p	2N5358	27p	ACY22	20p	BC140	37p	BDY62	£1-37p	BFY90	67p	GET136	22p	NKT281	20p	OC41	22p
2N726	20p	2N2955A	45p	2N3719	21-50p	2N5359	27p	ACY23	20p	BC147	17p	BF115	25p	BFW58	27p	GET137	22p	NKT401	67p	OC42	25p
2N727	30p	2N2956	30p	2N3720	21-50p	2N5360	27p	ACY28	30p	BC148	18p	BF117	47p	BFW69	28p	GET138	22p	NKT402	25p	OC44	25p
2N914	17p	2N2957	30p	2N3721	21-50p	2N5457	27p	ACY41	25p	BC149	17p	BF163	35p	BFW60	28p	MAT100	38p	NKT403	75p	OC45	18p
2N916	17p	2N2958	30p	2N3722	21-50p	2N8005	75p	ACY44	40p	BC152	17p	BF167	25p	BPX25	21-85p	MAT101	30p	NKT404	65p	OC46	18p
2N918	30p	2N2959	30p	2N3723	21-50p	2N8005	75p	AD140	40p	BC157	20p	BF172	32p	BPX29	21-80p	MAT120	30p	NKT405	75p	OC70	18p
2N929	22p	2N2962	17p	2N3724	21-50p	2N8102	32p	AD149	57p	BC158	17p	BF177	32p	BPY10	21-85p	MAT121	30p	NKT406	62p	OC71	12p
2N930	27p	2N2963	17p	2N3725	21-50p	2N8103	32p	AD150	57p	BC159	30p	BF178	35p	BSX18	17p	MJ406	21-77p	NKT451	62p	OC72	12p
2N987	52p	2N2964	17p	2N3726	21-50p	2N8104	32p	AD161	37p	BC160	62p	BF179	35p	BSX19	17p	MJ421	21-77p	NKT452	62p	OC74	25p
2N1121	27p	Green	14p	2N3727	21-50p	2N8105	27p	AD162	37p	BC167	18p	BF180	35p	BSX21	17p	MJ421	21-77p	NKT453	47p	OC75	25p
2N1132	32p	Yellow	12p	2N3728	21-50p	2N8106	27p	AD163	37p	BC168B	14p	BF181	32p	BSX22	47p	MJ430	21-62p	NKT603F		OC76	25p
2N1302	17p	Orange	12p	2N3729	21-50p	2N8107	27p	AD164	37p	BC182	15p	BF184	22p	BSX27	47p	MJ440	21-62p	NKT615F	32p	OC77	27p
2N1303	17p	2N3730	21-50p	2N3730A	40p	2N8108	92p	AD165	37p	BC189B	14p	BF185	42p	BSX28	32p	MJ481	21-25p	NKT615F	32p	OC81	25p
2N1304	22p	2N3731	21-50p	2N3731A	40p	2N8109	92p	AD166	37p	BC196	15p	BF186	42p	BSX29	32p	MJ481	21-25p	NKT674F	25p	OC81D	25p
2N1305	22p	2N3732	21-50p	2N3732A	40p	2N8110	92p	AD167	37p	BC171	17p	BF187	42p	BSX30	32p	MJ491	21-42p	NKT677F	30p	OC83	25p
2N1306	22p	2N3733	21-50p	2N3733A	40p	2N8111	92p	AD168	37p	BC172	17p	BF189	42p	BSX37	27p	MJ1800	42-17p	NKT713	25p	OC84	25p
2N1307	25p	2N3734	21-50p	2N3734A	40p	2N8112	92p	AD169	37p	BC175	22p	BF198									

ELECTROVALUE

SEMI-CONDUCTOR BARGAINS

ALL BRAND NEW AND TO SPEC. NO 'SECONDS'

All power types supplied with free insulation sets.

40361	55p	AF114	30p
40362	68p	AF115	30p
2N696	20p	AF117	20p
2N697	22p	AF124	30p
2N706	12p	AF127	28p
2N930	29p	AF139	48p
2N1131	36p	AF239	49p
2N1132	40p	ASY26	27p
2N1302	19p	ASY28	27p
2N1303	19p	BC107	14p
2N1304	23p	BC108	12p
2N1305	23p	BC109	14p
2N1306	33p	BC125	15p
2N1307	33p	BC126	22p
2N1308	36p	BC147	15p
2N1309	36p	BC148	14p
2N1613	23p	BC149	15p
2N1711	23p	BC153	19p
2N1893	54p	BC154	28p
2N2147	95p	BC157	19p
2N2218	34p	BC158	17p
2N2218A	43p	BC159	18p
2N2219	38p	BC167	13p
2N2219A	53p	BC168	11p
2N2270	62p	BC169	12p
2N2369A	19p	BC177	17p
2N2483	35p	BC178	15p
2N2484	42p	BC179	17p
2N2646	54p	BC182L	13p
2N2904A	42p	BC183L	11p
2N2905	44p	BC184L	13p
2N2905A	47p	BC212L	25p
2N2924	20p	BC213L	25p
2N2925	22p	BC214L	25p
2N2926	11p	BCY70	19p
2N3053	27p	BCY71	33p
2N3055	75p	BCY72	15p
2N3702	13p	BF115	23p
2N3703	13p	BF167	27p
2N3704	13p	BF173	31p
2N3705	13p	BF194	17p
2N3706	13p	BF195	18p
2N3707	13p	BFX29	31p
2N3708	13p	BFX84	25p
2N3709	13p	BFX85	34p
2N3710	13p	BFX87	29p
2N3711	13p	BFX88	26p
2N3819	35p	BFY50	23p
2N3904	35p	BFY51	20p
2N3906	35p	BFY52	23p
2N4058	20p	B5X20	16p
2N4059	20p	C407	17p
2N4060	20p	MC140	25p
2N4061	20p	MPS6531	35p
2N4062	20p	MPS6534	30p
2N4124	18p	NKT211	25p
2N4126	27p	NKT212	25p
2N4284	15p	NKT214	23p
2N4286	15p	NKT274	18p
2N4289	15p	NKT403	65p
2N4291	15p	NKT405	79p
2N4292	15p	OC71	19p
AC107	46p	OC81	25p
AC126	20p	OC81D	25p
AC127	20p	ZTX300	17p
AC128	20p	ZTX301	12p
AC153K	25p	ZTX302	22p
AC176	27p	ZTX303	22p
ACY20	20p	ZTX304	27p
ACY22	16p	ZTX500	18p
AD140	50p	ZTX501	21p
AD142	50p	ZTX502	25p
AD149	60p	ZTX503	22p
AD161	40p	ZTX504	52p
AD162	40p		

Appointed distributors and stockists for **SIEMENS (U.K.) LTD., NEWMARKET TRANSISTORS LTD., E. GRINSTEAD ELECTRONIC COMPONENTS LTD.**

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more. (No discount on nett items.)

POSTAGE AND PACKING

Free on orders over £2. Please add 10p if order is under £2. Overseas orders: carriage and insurance charged at cost.

ELECTROVALUE

DEPT. PE571, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY.

Phone: Egham 5533 (STD 0784-3) Telex 264475

Mullard

TECHNICAL BOOKS

Power Engineering using Thyristors

Part 1. Techniques of Thyristor Power Control

A new book to bridge the gap between electrical power engineering and electronics.

Including postage £1.60.

Data Book 1970

Gives Mullard abridged data on valves, picture tubes, semiconductors and components used in consumer electronics.

Paper bound. Including postage 24p.

Transistor Audio and Radio Circuits

For radio receivers, radiograms, record players, tape recorders, hi-fi equipment.

Over 200 pages packed with the most up to date information.

Bound in cloth. Including postage £1.60.

Electronic Counting Circuits. Techniques. Devices.

The increasing use of mechanization and automation in factories has given rise to an increased interest in counting. This present book is intended to help engineers to use electronics to solve their counting problems as simply or as cheaply as possible.

220 pages fully illustrated. With diagrams.

Including postage £1.50.

Semiconductor Devices

This book is an introduction to Semiconductor Electronics and its contents should be readily understood. The subject is treated non-mathematically. Numerous illustrations and diagrams.

Including postage 42p.

A programmed book on Semiconductor Devices

This book is an integral programme which is a form of self instructional text.

Size 12ins. x 8ins. Numerous illustrations and diagrams. Including postage 75p.

Electronic Experiments

The 20 experiments are intended as constructional projects, such as, an Oscilloscope, Logic Gates, Electronic Organ, Electronic Timer, etc. Containing numerous illustrations and diagrams.

Including postage 75p.

Post now to: Dept. M
SELRAY BOOK COMPANY
60 Hayes Hill Bromley BR2 7HP

COMPONENTS . . .

Resistor

R1 22k Ω $\frac{1}{4}$ W, $\pm 10\%$ carbon (or variable—see text)

Capacitor

C1 20 μ F elect. 25V

Transistors

TR1, 2 NKT274 or equivalent (2 off)

Relay

RLA 12V 170 Ω d.p.d.t. contacts rated at 2 amp (STC midget open type available from Henry's Radio Ltd)

Miscellaneous

Veroboard 2 $\frac{1}{2}$ in \times 1 $\frac{1}{2}$ in \times 0.15in matrix—or larger size to accommodate various relays. Connecting wire. Plastics box for case.

care must be taken to isolate the relay mounting screws from the copper strips. The completed unit can be mounted in the box by means of nuts, bolts and spacers or glued in using Araldite. The power supply can be derived from any convenient live line, e.g. from the ignition switch, and a chassis connection. Be absolutely certain to connect up with the correct polarity.

Note that no harm comes of holding the button down continuously; the relay merely drops out momentarily at the end of each completed cycle.

The two transistors do not have to be the same, but TR2 should be able to withstand a collector current of at least 100mA.

TESTING

To test the completed unit before installation in the car the supply should be connected to the leads indicated and the leads for the load (MO1) connected across a 12V bulb. The leads that are to be connected to S1 can then be momentarily touched together. This should cause the bulb to light and remain on for a few seconds. The dwell time can be adjusted to suit various requirements by varying R1 and C1 or as mentioned earlier, R1 may be replaced with a variable resistor to provide variable dwell times.

POSSIBLE APPLICATIONS

The unit can be used to time almost any operation of the car's electrical system over a limited period. The relay contacts must be able to switch the required current and it should be noted that the repeat time accuracy of the unit will not be exceptionally high.

If a relay with more than two sets of contacts is used, more than one operation can be actioned simultaneously, e.g. washers and wipers together for a set period. Other possible uses of the timer are: sounding the horn—in an alarm system; reversing light timer—to prevent it being left on; head light timer—to light the garage doors after parking the car; interior light timer—to keep the interior light on for a few seconds after closing the car door thus giving light for finding seat belts and controls.

Readers will probably find many other uses for this unit. ★



BOOK REVIEWS

F. M. RADIO SERVICING HANDBOOK (2nd edition)

By Gordon J. King

Published by Newnes-Butterworths

206 pages, 10in \times 6 $\frac{1}{2}$ in. Price £3.00

THE reliability of f.m. radio tuners and receivers is such that the amount of servicing or fault finding necessary on such modern equipment is minimal, particularly on those using semiconductors or integrated circuits. But when anything does go wrong it is essential to know what makes it tick if the serviceman is to restore it to full functional capabilities.

In particular, stereophony demands an understanding of some unusual radio propagation methods, and techniques for decoding to produce the optimum audio end-product.

It is not surprising therefore that actual servicing methods do not commence in this book until page 165. The preceding eight chapters, however, could have made up an excellent book on their own, being a fairly comprehensive down-to-earth description of the various principles involved in both valve and semiconductor f.m. tuners and stereo decoders.

The remaining chapters on servicing give a guide to analysis of breakdown symptoms with possible cures. Probably the most common faults are in the ageing of valves and capacitors which result in the tuned circuits drifting off frequency; a great deal is written on tuning procedures and the recommendations must be taken seriously to get the best results.

The final chapter explains the terminology used in specifications.

Overall this book is very well written, being largely new material that did not appear in the first edition. Some readers may even find it an improvement on the more general aspect found in "Radio and Audio Servicing Handbook" by the same author, and reviewed in our February issue.

M.A.C.

SEMICONDUCTORS — BASIC THEORY AND DEVICES

By I. J. Kampel

Published by Newnes-Butterworths

264 pages, 8 $\frac{1}{2}$ in \times 5 $\frac{1}{2}$ in

Price £2.50

WITH a title such as this, a mere 260 pages obviously imposes constraints upon its author. This accounts, one presumes, for the somewhat terse style of writing. In the main this makes for a most readable work, which provides a good general introduction to the properties of semiconductors and to specific devices employed in everyday electronics. But it does inevitably lead to certain generalisations and some superficial skating over deep and complexing matters. Although aimed at "readers with little knowledge of physical science who require an introduction to semiconducting devices and the theory associated with them", at times the book

appears to make certain assumptions about the reader's familiarity with physics: for example, on page 5 a bald statement "Pauli's principle states that the electrons in an atom must fill up the shells in order from the centre." That is the first and last we hear of Pauli and his principle. Maybe just a minor irritant. But, more seriously, on page 108 the author states that "the human being is particularly adept at sensing electromagnetic radiation in the region of 10^6 metres *with the ear*" (my italics). This confusion between e/m and sound compressional waves is by no means uncommon, but in the case of the author of a text book it is a bad and unexpected lapse.

Despite some shortcomings, this book has real worth, and its overall comprehensiveness will be attractive to those seeking to get to grips with solid state for the first time. The first ten chapters deal with the basic theory of semiconduction, from an outline of atomic structure through to p -type and n -type materials in contact, and so to the generic devices the diode and transistor, and how they are applied as active elements in circuits. After two chapters dealing with the somewhat abstruse subjects of Quantum Theory and Relativity, there are three devoted to photoelectric effects and semiconductors operating in the visible and infra-red regions respectively. Field effect semiconductors and switching devices are covered (but no mention of the triac), and then follow summary accounts of numerous other specialised solid state devices, including some advanced types not yet in common use. The manufacturing techniques for both discrete devices and integrated circuits are described with sectional views of typical devices. Strangely, the discussion on i.c.s is limited to linear devices.

F.E.B.

20 SOLID STATE PROJECTS FOR THE CAR AND GARAGE

By R. M. Marston
Published by The Butterworth Group
115 pages, 8½ in × 5½ in. Price £1.80

WHY OH WHY, must blurb writers make such amazing claims for the authors of books? I have been in trouble before because an introductory "sales" piece was so overwhelming that it was, in my opinion, a distortion of the facts, and now it has happened again. Most people read the cover blurb to get a quick synopsis of a book before buying, and so it is with me. The trouble is that when fantastic claims are made for a book or an author it is very annoying and can result in a bad book review. I hope I have learned to ignore such bumptious blurbs and try to give a fair appraisal of the book. However, publishers please do not print such things as; "R. M. Marston is probably five of the ten best-known electronics technical authors in the U.K. today." If you want to tell us how good he is, why not publish the pseudonyms and let the readers judge for themselves.

To get to the book itself, after the grouse the good points. All the projects would prove useful to most car owners, although I doubt if anyone would consider building them all. Circuit function is adequately described on all the circuits and this should help the novice building the simple circuits. The book is generally well written and the diagrams are good and easy to follow.

At a price of £1.80 the cost per project works out at 9p—even I can do it in my head with decimals—

admittedly some of the designs are worth more than this figure, but I would have expected them all to contain full constructional details and, in some cases, more information on wiring the devices to the car. The range of projects covered is great, from a suppressed-zero voltmeter (three components) right up to the complexities of a capacitor discharge ignition system.

It would be good to see the book better laid out so that the projects are arranged in some formal order—say relating to complexity—rather than in a random fashion. The ignition system, which was first published in *Wireless World* some time ago, has been placed first but will probably provide the most problems for the constructor both in layout and wiring, for which no diagrams are given, and in fault finding.

Not all projects are illustrated with photographs and those that are, show mainly the circuit boards and are generally of poor quality. Veroboard layouts are given for more than half the projects and these will enable most people to build them. M.K.

POINTS ARISING


P.E. GEMINI AMPLIFIER (November 70 to March 71)

Some constructors have reported difficulty with h.f. oscillation when setting up the amplifier as described in December 1970 issue. The trouble appears to be caused by the additional impedance of the meter together with feedback from meter leads to the open circuit input. This can be prevented by temporarily shorting the inputs whilst adjusting VR2 and VR102, i.e. link tags 1 to 2 and 3 to 4 on the main amplifier board.

Note that metal foil capacitors *must* be used for C17, C117, C25 and C125, although it is preferable to use metal foil types in the other positions indicated; electrolytic types may be substituted.

Components list p. 118: R69 and R169 should be 47k Ω . Switch S2, 2 pole, 5 way should be S3 and switch S5 is a d.p.d.t. toggle or slide. Fig. 34, p. 120, tag 102 has not been shown on either diagram; its position is indicated on Fig. 35. Fig. 3, p. 863 (November 1970) the voltage at R9 and R10 junction should be 26.2V as given in the check chart, not as shown on the diagram.

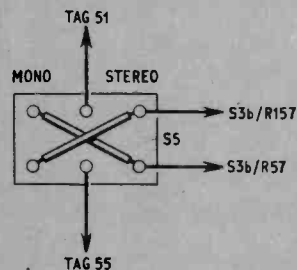We regret that the wiring of S5 was omitted, it is shown below:



SONY TFM-8030L

BARGAIN SCOOP

HIGH PERFORMANCE 11 TRANSISTOR THREE WAVEBAND PORTABLE BATTERY/MAINS RADIO

This is a really top performance, top quality solid state receiver packed with SONY know-how and backed by the outstanding reliability for which SONY are renowned. Now this outstanding set is available from Laskys at over 27% below the manufacturers list price making it without a doubt the NUMBER ONE SCOOP of 1971! Just look at these outstanding features. Covers MW, LW and FM (VHF). 11 transistor circuit for high sensitivity and stability. Powerful output to S' P.M. Dynamic speaker with rich clear tone quality. AFC for drift free VHF reception. Push button wavechange selectors and tone control.

Choice of three power sources—9V battery, household mains or car battery with suitable adaptors. Dial light for use in the dark. External jacks for earphone, tape recording, external power input and car aerial. Ultra modern styling and superb finish with padded leatherette covered cabinet for superior sound damping with chrome trim, strong carrying handle.

The SONY TFM 8030L will enliven your leisure hours anywhere, anytime with exciting sound, news, sport, music, etc. Technical specifications: Freq. range, FM 87-108MHz, LW 150-235kHz, MW 530-1,605kHz. Circuit: 11 transistors, 7 diodes and 2 thermistors. Aerial System: Directional telescopic for FM, internal ferrite bar for LW/MW. Power Output: 1.85W max. Speaker PM Dynamic—4Ωimp. Power Source: 9v power pack battery (Ever-Ready PP9 or equiv.), AC mains with adaptor, Car battery with adaptor. Size: 9½(W) x 8½(H) x 3½(D). Complete with earphone and battery and full instruction manual.

MANUFACTURERS LIST PRICE £29.75


LASKY'S SPECIAL OFFER PRICE **£21.50**

Optional Extras. SONY AC-90e AC adaptor £4.00 DCC-126 stabilised car battery cord £6.00. Both post FREE if purchased with radio.

Post 35p



EXCLUSIVE DIGITAL CLOCK SCOOP!

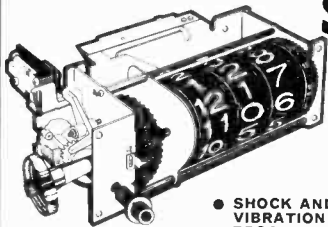

SPECIAL QUOTATIONS FOR QUANTITIES

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light, etc., at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4½W x 1½H x 3½D (overall from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS.

COMPLETE WITH KNOBS. LASKY'S PRICE **£6.95**

Post 18p

GARRARD SP25 Mk III

The SP 25 series record deck has proved to be one of the most popular of its type in the world. Styled in black and silver, this moderately priced three-speed unit complies with the Din 45-500 Hi-Fi performance standard. The tubular low resonance aluminium pick-up arm is counter-balanced by a resiliently mounted weight. Stylus force is adjusted by an optical-type knurled knob, finely calibrated from 0.5 grm. in steps of 1 grm. Bias compensation is set with a finger-tip adjustment, the scale being calibrated to correspond with the stylus force. The viscous damped cue control facilities raising and lowering the pick-up arm onto the track required without damage to either the record or stylus. The 10½in. aluminium turntable is driven by the well-proven Garrard 4-pole high and low voltage induction motor. Actual size including max. rear and side overhang of pick-up arm 15½in. wide x 12½in. front to rear x 2½in. above and 2½in. below edge of unit plate.



LASKY'S PRICE **£12.50**

or complete with 9TA Cart. £13.95 Post 35p

McDONALD

PROFESSIONAL SERIES FOUR-SPEED SINGLE PLAY UNIT

MP60

High-precision low-mass fully counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous curing device, slide-in cartridge carrier, four pole motor.



LASKY'S PRICE

£12.50

Post 35p

complete with plinth and cover **£15.75**

Post 40p

610 AUTOMATIC TURNTABLE

Same specifications as the MP60 but with synchronous four pole motor and full automatic change facilities.

LASKY'S PRICE **£15.45**

Post 35p

WITH PLINTH AND COVER **£18.75**

Post 40p

510 AUTOMATIC TURNTABLE

Counterbalanced pick-up arm, pressed steel turntable, bias compensator, viscous curing and synchronous four pole motor.

LASKY'S PRICE **£13.45**

Post 35p

WITH PLINTH AND COVER **£16.95**

Post 40p

310 AUTOMATIC TURNTABLE

Low-mass square section pick-up arm, cue and pause lever, visual stylus pressure indicator, slide-in cartridge carrier, four pole motor.

LASKY'S PRICE **£9.95**

Post 35p

WITH PLINTH AND COVER **£13.45**

Post 40p

NOW AVAILABLE LASKY'S EXCLUSIVE

LASKY-McDONALD plinth and cover available separately at

£4.75

Post 25p

Lasky's Radio Ltd

Branches

207 EDGWARE ROAD, LONDON, W.2

Tel: 01-723 3271

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centre

33 TOTTENHAM CT. RD., LONDON, W.1


Tel: 01-636 2605

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-583 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday

Open all day, 9 a.m.—6 p.m. Monday to Saturday

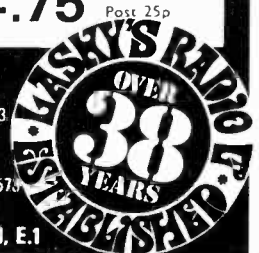ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1



BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	6p	OC170	6p
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-35
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15	Power	
BF274	0-15	Transistors	
BFY50	0-20	OC20	0-50
BSY25	0-57	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-15	OC36	0-37
OC41	0-13	AD149	0-30
OC44	0-13	AUY10	1-25
OC45	0-13	2S034	0-25
OC71	0-13	2N3055	0-63
OC72	0-13	Diodes	
OC73	0-17	AY42	0-10
OC81	0-13	OA95	0-10
OC81D	0-13	OA79	0-09
OC84	0-20	OA81	0-09
OC139	0-13	IN914	0-07
OC140	0-17		

FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER 64

CLEARANCE LINES

TO MAKE ROOM FOR NEW STOCK

OC71, OC72 transistors unmarked fully tested 5p.
TIC45 thyristors -6 amp 60V fully marked and tested Texas plastic type 15p.
CRS25/025 Thyristors 25 amp 25V 25p.
I.C.'s fully marked and tested by AEL. Gates 25p.
Flip flops 50p.
709C linear amp TO-5 can 50p.
1 watt zener diodes 7-5V, 6-8V, 24V, 27V, 30V and 43V 5p each.
OA47 gold bonded diodes 3p.

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each
post and packing 23p.

SPECIAL LINE

1 AMP Bridge rectifiers 2in Square
100 PIV. = 25p. 400 PIV. = 37p. 800 PIV. = 50p.

PAK F.3. 13p

Complementary Set. PAIR
NPN/PNP Germ. Trans.

BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1

Post and packing 25p.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	20	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

RETURN OF THE UNBEATABLE P.I PAK.

NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.1 ONLY 50p

10p P. & P. on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

FREE CATALOGUE AND LISTS for:-

ZENER DIODES
TRANSISTORS, RECTIFIERS
FULL PRE-PAK LISTS
& SUBSTITUTION CHART

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS 8 FOR

Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

£1

OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.

TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.

TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.

TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

ANNOUNCING THE OPENING OF OUR ENTIRELY NEW CASH AND CARRY DEPARTMENT, ON THE SPOT SALES OF ALL CATALOGUED ITEMS, PLUS MANY OTHER LINES OF INTEREST



Reductions for bulk buying manufactures welcome.

These are but a few examples. OC44, OC45, OC82, OC139, IN4007 all at 8p.

IN4001 at 4p, IN4004 at 5p, IN4006 at 6p, minimum quantity 500.

Semiconductor Supermarket of the South East.

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners. Top hat type	50p
H11	30	MAT Series "alloy" pnp Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

What about us!

Sir—May I make a strong plea to professional electronic components manufacturers to be a little more tolerant to amateurs, and at the same time suggest that we, the amateurs, take note of the specific problems that sometimes prevent the larger companies aiding us with the supply of specialised components.

Generally speaking we are able to obtain most day to day components through retail outlets and specialist companies advertising in your magazine. However, many of the projects that we might like to embark on require components of a highly specialised nature and it is only possible to obtain these directly from the manufacturers or their distributors.

Certain companies have attempted to satisfy this demand by setting up special divisions to deal specifically with the amateur but none seem to have been highly successful ventures—perhaps because the prices of components in question tend to be higher than average and that there are not sufficient of us to make the business worthwhile.

Professional distributors usually refuse to supply individuals because they are afraid that it will be the thin end of the wedge, but the thin end of what edge? Whenever I have challenged distributors to explain their fear it usually turns out that their impression is that individuals do not understand the usual conditions of business sales and present their orders in an un-intelligible way. Some have said that the “drips and drabs” of business they would get involved in would be uneconomic.

While I agree with the first two points I strongly disagree with the latter. The basis on which distributors operate is to provide a fast supply of small to medium quantities of components to user industries i.e., they take the business which is too small to be economic to the main factory. Most distributors are prepared to supply industrial concerns with remarkably low value orders—typically as low in

value as £2. Admittedly this is padded out by large orders but nevertheless the organisation must be tooled up to handle the small business as well. I would say that most projects that this magazine deals with involve the use of many times this value of components.

My feeling is that the first two points mentioned are the ones which frighten the distributors, e.g. sending off orders lower than the minimum order value that most companies now have, or telephoning repeatedly, chasing orders, which have only just been sent off, or even sending back goods after ordering the wrong devices in error; and perhaps the worst offender is the illegible order enclosing money for goods which obviously cannot be dispatched.

May I suggest that you approach such distributors on behalf of the amateur asking whether they would in future be prepared to supply

components against a formalised order form which really enthusiastic constructors can easily get printed for not much more than a pound or two (I enclose a simple example). Also that minimum order values are recognised.

If these conditions were laid down I seen no reason why the amateur should not receive exactly the same service as the professional and at the same time the distributors would find a none too small outlet for components.

M. J. Hughes,
Biggin Hill,
Kent.

Desirable scheme!

Sir—About a year ago we formed a buying group with about 15 other dealers in the London area which we provisionally call “Group One.” Its primary object was to buy components at the best prices in reasonable quantities. There are several secondary aims such as exchange of excess stock and exchange of information.

To some extent this has been forced on us because we wished to buy certain items that wholesalers don't wish to handle and the manufacturers will only sell in quantities that are beyond the pocket of one dealer to buy. But I would like to stress the fact that this is not aimed at distributors or wholesalers (I for one, have always believed that they do a useful job and earn their money) in fact any small wholesaler or manufacturer would be welcome to join. I feel sure you will agree that this is a desirable scheme, as ultimately it means we can offer your readers a greater range of goods at the lowest prices.

Initially we were going to limit the Group to about 20 dealers (not an account of any closed shop principle but because we thought (quite wrongly) that we could not handle the administration of a larger number). Now we would like to offer membership to any bona fide trader in the U.K. and I would be very grateful if you could make this generally known through the courtesy of your columns. At the moment there is no entrance fee or subscription. If anyone is interested please write to me at the following address.

A. Sproxtton,
Home Radio Ltd.,
234-240 London Road,
Mitcham, Surrey.

This magazine will give encouragement or support to any idea or scheme that seems mutually beneficial to all parties concerned. But our especial aim will always be to further the aspirations of the genuine enthusiast, which regretably are often held in check through want of desired components.

See this month's editorial comment.

U. R. BLOGGS Electronics Engineer
023-4367 34 Any Street Anywhere

To: Date:
Ref:

ORDER

Please supply

Item	Quantity	Description	Value
1			
2			
3			
4			
5			
6			
7			

Postage

TOTAL

Enclosed: Cheque to cover above total.

U R Bloggs

Sinclair Project 60



the world's most advanced high fidelity modules

Sinclair Project 60 presents high fidelity in such a way that it meets every requirement of performance, design, quality and value and now that the remarkable phase lock loop stereo FM tuner is available, it becomes the most versatile of high fidelity systems. With Project 60, it is possible to start with a

modest mono record reproducer and expand it to a sophisticated stereophonic radio and record reproducing system of fantastically good quality to hold its own with any other equipment, no matter how expensive. Project 60 is a unique high fidelity module system where compactness and ease of assembly are combined with

circuitry that is far in advance of any other manufacturer in the world. Thus it is extraordinarily easy to assemble any combination of modules using nothing more complicated than the simplest of tools, and you certainly do not have to be experienced to build with complete confidence. The 48 page manual free with Project 60 equipment makes everything easy and you can house your assembly in an existing cabinet, motor plinth, free standing cabinet or virtually any arrangement you wish. Once you have completed your assembly you will have superlatively good equipment to give you years of service and enjoyment. You will have obtained superb value for money because Project 60 is the best selling modular system in Europe and can therefore be produced at extremely competitive prices and with excellent quality control.


Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ.
Tel: St. Ives (048 06) 4311

sinclair

System	The Units to use	together with	Cost of Units
A Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
B Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
C 20+20 W. R.M.S. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., most dynamic speakers, F.M. tuner etc.	£23.90
D 20+20 W. R.M.S. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
E 40+40W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains trnsfrmr	As for D	£34.88
F Outdoor P.A. system	Z.50	Mic., up to 4 P.A. speakers controls, etc.	£5.48
G Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43
H High pass and low pass filters	A.F.U.	C, D or E	£5.98
J Radio	Stereo F. M. Tuner	C, D or E	£25.00

Sinclair Project 60

Z.30 & Z.50 power amplifiers

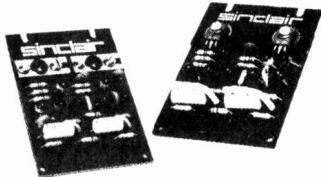

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts.

Frequency response: 30 to 300,000 Hz \pm 1dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$ in.

Z.30

Built, tested and guaranteed with circuits and instructions manual


£4.48

Z.50

Built, tested and guaranteed with circuits and instructions manual.

£5.48

Power Supply Units

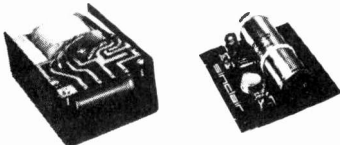

Designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ-5 30 volts un stabilised £4.98

PZ-6 35 volts stabilised £7.98

PZ-8 45 volts stabilised


(less mains transformer) £7.98

PZ-8 mains transformer £5.98

Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

Stereo 60 pre-amp/control unit

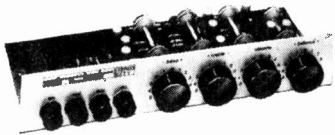

Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS

Input sensitivities: Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve \pm 1dB; 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; Aux—up to 3mV.

Output: 250mV

Signal-to-noise ratio: better than 70dB.

Channel matching: within 1dB.

Tone controls: TREBLE + 15 to -15dB at 10KHz; BASS + 15 to -15dB at 100Hz.


Front panel: brushed aluminium with black knobs and controls.

Size: $8\frac{1}{2} \times 1\frac{1}{2} \times 4$ in.

Built, tested and guaranteed.

£9.98

Active Filter Unit

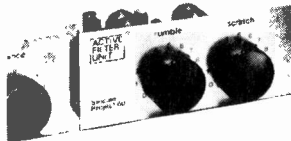


For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28kHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1kHz (35V. supply) 0.02% at rated output.

Built, tested and guaranteed

£5.98

Stereo FM Tuner

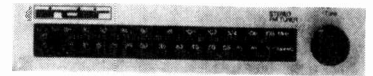

first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time, the principle has been applied to an FM tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Sensitivity is such that good reception becomes possible in difficult areas. Foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS:

Number of transistors: 16 plus 20 in I.C.

Tuning range: 87.5 to 108 MHz

Capture ratio: 1.5dB

Sensitivity: 2 μ V for 30dB quieting; 7 μ V for full limiting.

Squelch level: 20 μ V.

A.F.C. range: \pm 200 KHz

Signal to noise ratio: \geq 65dB

Audio frequency response: 10Hz—15KHz (\pm 1dB)

Total harmonic distortion: 0.15% for 30% modulation

Stereo decoder operating level: 2 μ V

Pilot tone suppression: 30dB

Cross talk: 40dB

I.F. frequency: 10.7 MHz


Output voltage: 2 x 150mV R.M.S.

Aerial Impedance: 75 Ohms

Indicators: Mains on; Stereo on; tuning indicator

Operating voltage: 25-30 VDC

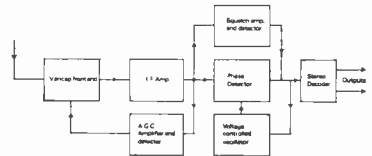Size: 3.6 x 1.6 x 8.15 inches; 91.5 x 40 x 207 mm



Price: **£25** built and tested. Post free

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

for which I enclose cash/cheque/money order.

Sinclair IC10/Q16/Micromatic

IC10



The world's most advanced high fidelity amplifier

This is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, having 5 watts RMS output (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, and is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is more rugged and has considerable performance advantages, including complete freedom from thermal runaway and a very low level of distortion. The IC10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. It may also be used in other applications including car radios, electronic organs, servo amplifiers (it is dc coupled throughout) etc.


Circuit Description

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. There is generous negative feedback round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory. Each IC10 is sold with a comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include oscillators, etc. The pre-amp section can be used as an RF or IF amplifier without any additional transistors.

Specifications:

Output: 10 watts peak, 5 watts RMS continuous.
 Frequency response: 5Hz to 100kHz $1 \pm$ dB.
 Total harmonic distortion: Less than 1% at full output.
 Load impedance: 3 to 15 ohms.
 Power gain: 110 dB (100,000,000,000 times) total
 Supply voltage: 8 to 18 volts. (A Sinclair power unit, PZ.7 is available for mains operation).
 Size: 1 x 0.4 x 0.2 in. plus heat sink and tags.
 Sensitivity 5 mV.
 Input impedance: Adjustable externally up to 2.5 Mohms.
 Price (with manual) **59/6** (£2.97 $\frac{1}{2}$) post free.

Q16

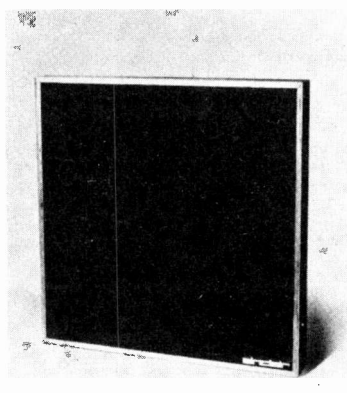

High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

Specifications:

Construction: Special sealed seamless sound or pressure chamber with internal baffle.
 Loading: up to 14 watts TMS.
 Input impedance: 8 ohms.
 Frequency response: From 60 to 16,000 Hz, confirmed by independently plotted B and K curve.
 Driver unit: Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and a special cone suspension for excellent transient response.
 Size and styling: $9\frac{1}{2}$ in square on face x 4 $\frac{1}{2}$ in. deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.
 Price **£8.19.6.** (£8.97 $\frac{1}{2}$).

Micromatic



Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute and attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

Specifications:

Size: 36 x 33 x 13 mm ($1\frac{4}{5}$ x $1\frac{3}{10}$ x $\frac{1}{2}$ in.)
 Weight: including batteries, 28.4 gm (1 oz.).
 Case: Black plastic with anodised aluminium front panel and spun aluminium dial.
 Tuning: medium wave band with bandspread at higher frequencies. (550 to 1,600 Hz).
 Earpiece: Magnetic type.
 On/off switching: By inserting and withdrawing earpiece plug.
 Kit in pack with earpiece, case, instructions and solder **49/6** (£2.47 $\frac{1}{2}$).
 Ready built, tested and guaranteed, with earpiece **59/6** (£2.97 $\frac{1}{2}$).
 Two Mallory Mercury batteries type RM675 required. From radio shops, chemists, etc.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____

Name _____

Address _____

for which I enclose cash/cheque/money order.

P.E. 5

Sinclair Radionics Ltd., London Road
 St. Ives, Huntingdonshire PE17 4HJ.
 Tel: St. Ives (046 06) 4311

sinclair

YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 vols.)** **BASIC ELECTRONICS (6 vols.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT



The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

"T.V. ENGINEER."

"So in two years I have come from a labourer on a building site to a T.V. Engineer, with the help of your books."

C.G., Sheppey.

"SIMPLE, CLEAR AND CONCISE."

"I would like to endorse the feelings of many purchasers that they are a simple, clear and concise introduction to the study of electronics."

E.P.Y., London, S.E.9.

"MONEY-WELL SPENT."

"I consider this as money well spent. Thank you."

F.A., Burton-on-Trent.

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/-. Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/-. Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY BASIC ELECTRONICS

Prices include Postage and Packing.

Signature

(If under 18 signature required of parent or guardian)

NAME

BLOCK LETTERS

FULL POSTAL ADDRESS

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG

Telephone: Bristol 421196 STD Code 0272

Your West Country shop for electronic components and solid state devices

TTL IC'S SERIES 74N

7400N	25p	7450N	25p	7483N	£1.50
7401N	25p	7453N	25p	7490N	£1.05
7404N	25p	7460N	25p	7492N	£1.05
7410N	25p	7470N	38p	7493N	£1.05
7420N	25p	7472N	38p	7494N	£1.05
7430N	25p	7473N	45p	7495N	£1.05
7440N	25p	7474N	45p	7496N	£1.05
7441N	£1.05	7475N	53p		
7442N	£1.05	7476N	53p		P. & P. 5p.

Full outs 5 of any one type ... 63p. P. & P. 5p

Series 74N Data Booklet ... 14p. post free

3 watt I.C. treble and bass data and components ... £25.25, P. & P. 5p

Stereo 2 3 watt I.C. treble and bass data and components ... £10, P. & P. 8p

Power supply for 3 watt I.C. £1.75. P. & P. 10p

Crystal Set components with earpiece (if headphones required add 80p) ... 78p. P. & P. 5p

Experimental I.C. with circuits for Morse code osc., variable timer, wiper speed control, etc. ... 50p. P. & P. 5p

Aircraft band converter circuit, instructions and components ... all you need is a tobacco tin ... £1.20. P. & P. 5p

Tap recorder level meters 500µA. Size lin x lin x 2in 50p. P. & P. 5p

3 Digit tap recorder counters 32p. P. & P. 5p

SEND 3p STAMP FOR FREE CATALOGUE

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 45/-; 11 element, 52/6; 14 element, 60/-; 18 element, 70/-
Wall Mounting with Cranked Arm, 7 element, 65/-; 11 element, 75/-; 14 element, 82/6; 18 element, 90/-
Chimney Mounting Arrays—Complete, 7 element, 80/-; 11 element, 87/6; 14 element, 95/-; 18 element, 105/-
Complete assembly instructions with every aerial. Low Loss Co-axial Cable, 18 yd. King Teleboosters—Labgear U.H.F. Boosters from 75/-
Belling Lee "Concord" all Band V.H.F. U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. Pre-amps from 75/-
Accessories 3/- C.W.O. or C.O.D.

BBC. ITV. FM AERIALS



H.R.C. (Band 1). Loft, 25/-
Wall S.D. 32/6. "H" array, 60/-
I.T.V. (Band 3). 5 element loft array, 45/-; 7 element, 55/-
Wall mounting 5 element, 65/-
Combined BBC ITV loft 1 + 5, 55/- + 1 + 7, 67/6. Wall mounting 1 + 5, 77/6. Chimney mounting 1 + 5, 90/-. Pre-amps from 75/-

Combined BBC ITV BBC2 Aerials, 1 + 5 + 9, 80/-; 1 + 5 + 14, 90/-; 1 + 7 + 14, 100/-. Available loft only.

F.M. Radio Loft S.D. 19 8. "H", 38/6. 3 element array, 57/6. Standard co-axial cable, 1-yd. Coax plugs, 1/8. Outlet boxes, 6/-
Diplexer crossover boxes, 17/6. p.p. Aerials, 8/-
accessories, 3/-
C.W.O. or C.O.D. (min. C.O.D. charge 3/6.) 1- for fully illustrated Lists.

CALLERS WELCOMED

OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)

40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

OSMABET LTD.

We make transformers amongst other things

MAINS TRANSFORMERS

Prim. 200/240V a.c. TX300. 425-0-425V. 500 mA. 6-3V. 6A CT. 0-5-6-3V. 3A. £19.75. TX1. 425-0-425V. 250mA. 6-3V 4A CT. 0-5-6-3V. 3A. £7.50; TX2. 250-0-250V. 150mA. 6-3V 4A CT. 0-5-6-3V. 3A. £4.05; TX5. 300-0-300V. 120mA. 6-3V 2A CT. 6-3V. 2A. 6-3V. 1A. £4.05; TX8. 250-0-250V. 65mA. 6-3V. 1.5A. £2.10; MT1. 200V. 30mA. 6-3V. 1A. £1.80; MT2. 230V. 45mA. 6-3V. 1.5A. £1.50; MT2A. 250V. 60mA. 6-3V. 2A. £1.95; MT3 Prim. 110/240V. Sec. 250V. 100mA. 6-3V. 2A. £2.25

MULTIVOLT TRANSFORMERS

Prim. 200/240V a.c. OMT4/1. One tapped sec. 5-20-30-40-60V giving 5-10-15-20-25-30-40-45-55-60. 10-0-10. 20-0-20. 30-0-30V a.c. 1A. £2.25; OMT4/2 ditto. 2A. £2.45; OMT5/1 one tapped sec. 40-50-60-80-90-100-110V a.c. 1A. £2.45

LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c. 6-3V. 1.5A. £2.5; 3A. £1.15; 6A CT. £1.80; 12V. 1.5A. £1.15; 3A CT. £1.80; 6A CT. £2.70; 18V. 1.5A CT. £1.80; 24V. 1.5A CT. £1.80; 3A CT. £2.70; 5A. £2.78; 8A. £2.12A. £2; 40V. 3A CT. £2.45; 50V. 6A CT. £2.75

MIDGET RECTIFIER TRANSFORMERS

For FW rect. size 1 1/2 x 2 1/4 in. Prim. 200/240V a.c. output. PPT1 9-0-9V. 0.3A. PPT2 12-0-12V. 0.25A. PPT3 20-0-20V. 0.15A. £1.80 each; ditto, size 2 x 2 1/4 x 1 1/4 in. MTV1 9-0-9V. 1A. 90p; MTV2 12-0-12V. 1A. MTV3 20-0-20V. 0.75A. £1.80 each.

O/P TRANSFORMERS

P.P. sec. tapped 3-7.5-15 ohms. A-A 6.6kΩ. 30W (KT86, etc.) £4.05; 50W. 3kΩ. A-A. £6.75; 100W. 3kΩ. A-A. EL34 (KT88, etc.) £11.40.

LOUDSPEAKERS

Ex equipment perfect. 3 ohms only. 5in at 40p each p.p. 10p min.

LOUDSPEAKERS. HI-FI. P.A. GUITAR. ETC.

New boxed famous makes. 25W. £2.60; 35W. £7.20; 50W. £9.45; 60W. £11.90; 100W. £19.90; E.M.I. 131 x 8in. 10W. 3. 8 and 15 ohms. £2; fitted two tweeter Hi-Fi, 3. 8 and 15 ohms. £4; Horn tweeters 2-16kHz. 8 or 15 ohms. 10W. £1.60.

P.E. AURORA LIGHT CONTROL UNIT

Mains trans. as specified. Prim. 200/240V. Secs. 12V 0.5A. £1.25 plus P. & P. 20p.

AIRCRAFT BAND CONVERTER

Covers entire aircraft band, 110-135MHz, fully tunable, works in proximity of any AM receiver, complete with battery, instructions. £4.85.

PRINTED CIRCUIT ETCHING KITS

Comprehensive outfit, to make your own P.C. boards. £1.25. Carriage extra all orders. S.A.E. INQUIRIES, LISTS PLEASE, MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Built Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it’s as fascinating as a hobby. Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of “OPPORTUNITIES IN TELECOMMUNICATIONS/TV AND RADIO”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.

FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 371B, ALDERMASTON COURT, READING RG7 4PF



POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. 371B, Aldermaston Court, Reading RG7 4PF
Please send books and full information — free and without obligation.

NAME AGE

ADDRESS

OCCUPATION

BIET
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

BI-PAK = LOW COST I.C.'s

NOW LOWER THAN EVER PRICES—GREATER RANGE

BI-PAK Semiconductors offer you the largest and most popular range of I.C.'s available at these **EXCLUSIVE LOW PRICES**. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.

BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24 \$p	25-99 \$p	100 up \$p
BP00 = 7400	Quadruple 2-input NAND gate	0-23	0-20	0-16
BP01 = 7401	Quadruple 2-input positive NAND gate (with open collector output)	0-23	0-20	0-16
BP02 = 7402	Quadruple 2-input positive NOR gates	0-23	0-20	0-16
BP03 = 7403	Quadruple 2-input positive NAND gates (with open-collector output)	0-23	0-20	0-16
BP04 = 7404	Hex Inverters	0-23	0-20	0-16
BP10 = 7410	Triple 3-input positive NAND gates	0-23	0-20	0-16
BP13 = 7413	Dual 4-input Schmitt trigger	0-35	0-32	0-29
BP20 = 7420	Dual 4-input positive NAND gates	0-23	0-20	0-16
BP30 = 7430	8-input positive NAND gates	0-23	0-20	0-16
BP40 = 7440	Dual 4-input positive NAND buffers	0-23	0-20	0-16
BP41 = 7441	BCD to decimal nixie driver	0-87	0-77	0-67
BP42 = 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	0-87	0-77	0-67
BP47 = 7447	BCD-seven-segment decoder/drivers (15V outputs)	1-40	1-30	1-20
BP50 = 7450	Expandable dual 2-input and-or-invert	0-23	0-20	0-16
BP51 = 7451	Dual 2-wide 2-input and-or-invert gates	0-23	0-20	0-16
BP53 = 7453	Quad 2-input expandable and-or-invert	0-23	0-20	0-16
BP54 = 7454	4-wide 2-input and-or-invert gates	0-23	0-20	0-16
BP60 = 7460	Dual 4-input expander	0-23	0-20	0-16
BP70 = 7470	Single-phase J-K flip-flop	0-85	0-82	0-79
BP72 = 7472	Master-slave J-K flip-flop	0-85	0-82	0-79
BP73 = 7473	Dual master-slave J-K flip-flop	0-43	0-40	0-37
BP74 = 7474	Dual D type flip-flop	0-43	0-40	0-37
BP75 = 7475	Quad latch	0-47	0-45	0-43
BP76 = 7476	Dual J-K with pre-set and clear	0-47	0-45	0-43
BP80 = 7480	Gated full adders	0-87	0-77	0-67
BP81 = 7481	16-bit read/write memory	1-85	1-85	1-15
BP82 = 7482	2-bit binary full adders	1-30	1-20	1-10
BP83 = 7483	Quad full adder	0-87	0-77	0-67
BP85 = 7485	Quad 2-input exclusive or gates	0-80	0-70	0-60
BP90 = 7490	BCD decade counter	0-87	0-77	0-67
BP91 = 7491	8-bit shift registers	1-21	1-00	0-87
BP92 = 7492	Divide-by-twelve counters	0-87	0-77	0-67
BP93 = 7493	4-bit binary counters	0-87	0-77	0-67
BP94 = 7494	Dual entry 4-bit shift register	0-87	0-77	0-67
BP95 = 7495	4-bit up-down shift register	0-87	0-77	0-67
BP96 = 7496	3-bit parallel in parallel out shift-register	1-10	1-00	0-90
BP100 = 74100	8-bit bistable latches	1-75	1-65	1-55
BP118 = 74118	Hex set-reset latches	1-30	1-20	1-10
BP121 = 74121	Monostable multivibrators	0-87	0-77	0-67
BP141 = 74141	BCD-to-decimal decoder/driver	0-87	0-77	0-67
BP145 = 74145	BCD-to-decimal decoder/drivers	1-80	1-70	1-60
BP151 = 74151	8-bit data selectors (with strobe)	1-40	1-30	1-20
BP153 = 74153	Dual 4-line-to-1-line data selectors/multiplexers	1-40	1-30	1-20
BP191 = 74191	Binary counter reversible	3-50	3-25	3-00

PRICE MIX. Devices may be mixed to qualify for quantity prices. **PRICES** for quantities in excess of 500 pieces mixed, on application. Data is available for the above Series of Integrated Circuits in booklet form, price 13p.

TTL INTEGRATED CIRCUITS

Manufacturers' "Full out"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N 50p	UIC42 = 5 x 7450N 50p	UIC80 = 5 x 7480N 50p
UIC01 = 12 x 7401N 50p	UIC60 = 12 x 7450N 50p	UIC82 = 5 x 7482N 50p
UIC02 = 12 x 7402N 50p	UIC51 = 12 x 7451N 50p	UIC83 = 5 x 7483N 50p
UIC03 = 12 x 7403N 50p	UIC60 = 12 x 7460N 50p	UIC86 = 5 x 7486N 50p
UIC04 = 12 x 7404N 50p	UIC70 = 8 x 7470N 50p	UIC90 = 5 x 7490N 50p
UIC05 = 12 x 7405N 50p	UIC72 = 8 x 7472N 50p	UIC92 = 5 x 7492N 50p
UIC10 = 12 x 7410N 50p	UIC73 = 8 x 7473N 50p	UIC93 = 5 x 7493N 50p
UIC20 = 12 x 7420N 50p	UIC74 = 8 x 7474N 50p	UIC94 = 5 x 7494N 50p
UIC40 = 12 x 7440N 50p	UIC75 = 8 x 7475N 50p	UIC95 = 5 x 7495N 50p
UIC41 = 5 x 7441AN 50p	UIC76 = 8 x 7476N 50p	UIC96 = 5 x 7496N 50p
	UICX1 = 25 x Asst'd 74's £1-50	

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1 Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	1-24	25-99	100 up
BP 201C—8L201C	TO-5	8	G.P. Amp	83p	53p	45p
BP 701C—8L701C	TO-5	8	OP Amp	83p	50p	45p
BP 702C—8L702C	TO-5	8	OP Amp Direct OP	83p	50p	45p
BP 702-72702	D.I.L.	14	G.P. OP Amp (Wide Band)		53p	45p 40p
BP 709 —72709	D.I.L.	14	High OP Amp		53p	45p 40p
BP 709P— μ A709C	TO-5	8	High Gain OP Amp		53p	45p 40p
BP 711— μ A711	TO-5	10	Dual comparator		58p	50p 45p
BP 741 —72741	D.I.L.	14	High Gain OP Amp (Protected)		75p	60p 50p
μ A 703C— μ A703C	TO-5	6	R.F.—I.F. Amp		43p	35p 27p
TAA 283—	TO-2	4	A.F. Amp		70p	60p 55p
TAA 293—	TO-74	10	G.P. Amp		90p	75p 70p

RTL MICROLOGIC CIRCUITS

	Price each
Epoxy TO-5 case	1-24 25-99 100 up
uL900 Buffer	35p 33p 27p
uL914 Dual 2/p gate	35p 33p 27p
uL923 J-K flip-flop	50p 47p 45p
Data and Circuits Booklet for I.C.'s	
Price 7p.	

Dual-in-Line Low Profile Sockets

14 and 16 Lead Sockets for use with Dual-in-Line Integrated Circuits.

	Price each
Order No.	1-24 25-99 100 up
T80 14 pin type	30p 27p 25p
T80 16 pin type	35p 32p 30p

BI-PAK SEMICONDUCTORS

P.O. BOX 6, WARE, HERTS.

Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please. Giro No. 388-7006.

VALUE ALL THE WAY

NEW LOW PRICE TESTED S.C.R.'s

PIV	3A		7A		10A		16A		30A	
	TO-5	TO-66	TO-5	TO-66	TO-48	TO-48	TO-48	TO-48	TO-48	TO-48
50	0-23	0-25	0-47	0-50	0-83	0-83	1-15			
100	0-25	0-33	0-53	0-58	0-63	0-63	1-40			
200	0-35	0-37	0-57	0-61	0-75	0-75	1-60			
400	0-43	0-47	0-67	0-75	0-83	0-83	1-75			
600	0-53	0-57	0-77	0-83	1-25	1-25				
800	0-63	0-70	0-90	1-20	1-50	1-50	4-00			

SIL. RECTS. TESTED

PIV	750mA		1A		1.5A		3A		10A		30A	
	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66
50	0-04	0-05	0-05	0-07	0-14	0-21	0-47					
100	0-04	0-06	0-05	0-13	0-16	0-23	0-75					
200	0-05	0-09	0-06	0-14	0-20	0-24	1-00					
400	0-06	0-13	0-07	0-20	0-27	0-37	1-25					
600	0-07	0-18	0-10	0-23	0-34	0-45	1-85					
800	0-10	0-17	0-13	0-25	0-37	0-55	2-00					
1000	0-11	0-25	0-15	0-30	0-46	0-83	2-50					
1200		0-53		0-58	0-87	0-75						

TRIACS

VBOM	2A		6A		10A	
	TO-1	TO-66	TO-18	TO-18	TO-18	TO-18
100	0-50	0-63	1-00			
200	0-70	0-90	1-25			
400	0-90	1-00	1-60			

SILICON HIGH VOLT-AGE RECTIFIERS

10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 80p each.

DIACS

FOR USE WITH TRIACS BR100 37p each

2A POTTED BRIDGE RECTIFIERS 200V 50p

UNIJUNCTION

UT48, Evt. 2N2646, Evt. T8143, BEN3000 27p each, 25-99 25p 100 UP 20p.

NPN SILICON PLANAR BC107/8/9, 10p each, 50-99, 9p; 100 up, 8p each; 1,000 off, 7p each. Fully tested and coded TO-18 case.

AD161 NPN

AD162 PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stage of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 65p PER PAIR

HIGH POWER SILICON PLANAR TRANSISTORS TO-3. FERRANTI ZT148:

VCB60 1c 6A PNP VCE40 Ptot. 75W VEB8 hFE15-45 PRICE 30p EACH

2N3055 115 WATT SIL. POWER NPN

OUR PRICE 65p EACH

FULL RANGE OF ZENER DIODES

2-33V 400mV (DO-7 Case) 13p ea. 1.5W (Top-Hat) 18p ea. 10W (SO-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed Pak No. EQVT
T1 8 2G371A OC71
T2 8 2G374 OC75
T3 8 2G374A OC81D
T4 8 2G381A OC81
T5 8 2G382T OC82
T6 8 2G344A OC44
T7 8 2G345A OC45
T8 8 2G378 OC78
T9 8 2G399A 2N1302
T10 8 2G417 AF117
All 50p each pack

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 25p each.

180 VCB NIXIE DRIVER TRANSISTOR. Sim. B8X21 & C407, 2N1893 FULLY TESTED AND CODED ND120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ Metal TO-18 Evt. ZTX300 5p each. Any Qty.

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	0-50
U2	60 Mixed germanium transistors AF/RF	0-50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0-50
U4	40 Germanium transistors like OC81, AC128	0-50
U5	60 200mA sub-min. Sil. diodes	0-50
U6	30 Silicon planar transistors NPN sim. B8Y95A, 2N706	0-50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0-50
U8	50 Sil. planar diodes 250mA, OA/200/202	0-50
U9	20 Mixed volts 1 watt Zener diodes	0-50
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132	0-50
U13	30 PNP-NPN sil. transistors OC200 & 28104	0-50
U14	150 Mixed silicon and germanium diodes	0-50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0-50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0-50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0-50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	0-50
U19	25 Silicon NPN transistors like BC108	0-50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0-50
U21	30 A.F. germanium alloy transistors 2G300 series & OC71	0-50
U23	30 Mad's like MAT series PNP transistors	0-50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0-50
U25	25 300Mc's NPN silicon transistors 2N708, B8Y27	0-50
U26	30 Fast switching silicon diodes like 1N914 micro-min	0-50
U28	Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc., 8 assorted pieces	1-00
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR51/25-600	1-00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0-50
U32	25 Zener diodes 400mW D07 case mixed volts, 3-18	0-50
U33	15 Plastic case 1 amp silicon rectifiers 1N4000 series	0-50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	0-50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0-50
U36	25 Sil. planar NPN trans. TO-5 BFY50/51/52	0-50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 28322	0-50
U38	20 Fast switching sil. trans. NPN, 400Mc's 2N3011	0-50
U39	30 RF germ. PNP trans. 2N1303/5 TO-5	0-50
U40	10 Dual trans. 6 lead TO-5 2N2060	0-50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0-50
U42	10 VHF germ. PNP trans. TO-1 NKT667 AF117	0-50

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

NEW QUALITY TESTED PAKS

Pack Description	Price
Q1 20 Red spot trans. PNP	0-50
Q2 16 White spot R.F. trans. PNP	0-50
Q3 4 OC77 type trans.	0-50
Q4 6 Matched trans. OC44/45/81/81D	0-50
Q5 4 OC75 transistors	0-50
Q6 4 OC72 transistors	0-50
Q7 4 AC128 trans. PNP high gain	0-50
Q8 4 AC128 trans. PNP	0-50
Q9 7 OC81 type trans.	0-50
Q10 7 OC71 type trans.	0-50
Q11 2 AC127/128 comp. pairs PNP/NPN	0-50
Q12 3 AF116 type trans.	0-50
Q13 3 AF117 type trans.	0-50
Q14 3 OC171 H.F. type trans.	0-50
Q15 2 2N2926 sil. epoxy trans.	0-50
Q16 2 GET890 low noise germ. trans.	0-50
Q17 3 NPN 1 BT141 & 2 BT140	0-50
Q18 4 Mad's 3 MAT 100 & 3 MAT 120	0-50
Q19 3 Mad's 2 MAT 101 & 1 MAT 121	0-50
Q20 4 OC44 germ. trans. A.F.	0-50
Q21 3 AC127 NPN germ. trans.	0-50
Q22 20 NKT trans. A.F. R.F. coded	0-50
Q23 10 OA292 sil. diodes sub-min.	0-50
Q24 8 OA81 diodes	0-50
Q25 10 NPN diodes 75PIV 75mA	0-50
Q26 8 OA85 germ. diodes sub-min. 1N69	0-50
Q27 2 10A 600PIV sil. rect. 1845R	0-50
Q28 2 Sil. power rect. ILYZ13	0-50
Q29 4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	0-50
Q30 7 Sil. switch trans. 2N706 NPN	0-50
Q31 6 Sil. switch trans. 2N708 NPN	0-50
Q32 3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0-50
Q33 3 Sil. NPN trans. 2N1711	0-50
Q34 7 Sil. NPN trans. 2N2369, 500MHZ.	0-50
Q35 3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0-50
Q36 7 2N3646 TO-18 plastic 300MHZ NPN	0-50
Q37 3 2N3053 NPN sil. trans.	0-50
Q38 7 PNP trans. 4 x 2N3703, 3 x 2N3702	0-50
Q39 7 NPN trans. 4 x 2N3704, 3 x 2N3705	0-50
Q40 7 NPN amp. 4 x 2N3707, 2 x 2N3708	0-50
Q41 3 Plastic NPN TO-18 2N3904	0-50
Q42 6 NPN trans. 2N5172	0-50
Q43 7 BC107 NPN trans.	0-50
Q44 7 NPN trans. 4 x BC108, 3 x BC109	0-50
Q45 3 BC113 NPN TO-18 trans.	0-50
Q46 3 BC115 NPN TO-5 trans.	0-50
Q47 6 NPN high gain 3 x BC167, 3 x BC168	0-50
Q48 4 BC170 NPN trans. TO-18	0-50
Q49 4 NPN trans. 2 x BFY51, 2 x BFY52	0-50
Q50 7 B8Y28 NPN switch TO-18	0-50
Q51 7 B8Y95A NPN trans. 300MHZ	0-50
Q52 8 BY100 type sil. rect.	1-00
Q53 25 Sil. & germ. trans. mixed all marked new	1-50

PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards 23, P. & P. 30p.

GENERAL PURPOSE GERM., PNP POWER TRANSISTORS

Code GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR—OC25-28-29-30-35-36. NKT401-403-404-405-406-450-451-452-453. T13027-3028, 2N2504, 2N456A-457A-458A, 2N511-511A & B. 2G220-222. ETC. SPECIFICATION VCB0 80V VCE0 50V IC 10A PT 30 WATTS HFE 30-170. PRICE 1-24 25-99 100 up 43p each 40p each 36p each

GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Code GP300. BRAND NEW TO-3 CASE. POSSIBLE REPLACEMENT FOR—2N3055, BDY20, BDY11. SPECIFICATION VCB0 100V, VCE0 60V, IC 15AMPS, PT. 115 WATTS. Hie 20-100. FT1 MHZ. PRICE 1-24 25-99 100 + 55p each 50p each 47p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, B8Y27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

	5p
20 For	0-50
50 For	1-00
100 For	1-75
500 For	7-50
1000 For	13-00

SURPLUS A.E.I. 40A GERM. JUNCTION RECTIFIERS. For Power Applications

Type GP6C20 400PIV 40p each GP6C30 600PIV 50p each

ALL PRICES QUOTED IN NEW PENCE.

Giro No. 388-7006.

Please send all orders direct to our warehouse and despatch department. BI-PAK SEMICONDUCTORS P.O. BOX 6, WARE, HERTS.

Postage and packing add 7p. Overseas add extra for Airmail. Minimum order. 50p. Cash with order please.

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 75p each.

GERM. POWER TRANS.

Type	Price each
OC20	50p
OC22	30p
OC23	33p
OC25	25p
OC26	25p
OC28	40p
OC29	40p
OC25	33p
OC36	40p
AD140	40p
AD142	40p
AD149	43p

OUR STOCKS of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Block at very competitive prices.

KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

G.E.C. INDUCTION MOTOR



Very powerful 1/40th h.p. 725 R.P.M. For normal 230/240V 50 c/s mains. Switch start, £2.50 including switch, plus post and insurance 62½p.

12 volt Car Battery Trickle Charger. Made in Japan, this is very small and neat. Regular use will keep your car battery in good trim throughout the winter. Silly price £1.25 plus 25p postage and insurance.

QUICK CUPPA

Mini Immersion Heater. 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12v. car model also available £1.



PLINTH AND COVER

Suitable for most auto changers, teak base with tinted perspex cover, £4.25 plus 35p postage. Special set for Balfour autochanger £4.25 plus 35p postage.



THYRISTOR LIGHT DIMMERS

Will dim incandescent lighting up to 600 w. from full brilliance to dim. Assembled and wired ready to install. £3.



AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v. positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.95 plus 25p post and ins.



COMPUTER TAPE

2,400 ft of the best magnetic tape money can buy. Made by E.M.I., 1in. wide almost unbreakable and on a 10 1/2in. metal computer spool. Users have claimed successful results with video as well as sound recordings £1 plus 33p post. Cassette to hold spool 50p extra.




HORSTMANN "TIME & SET" SWITCH

(A 30 Amp Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fire, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50. Post and ins. 23p.




1 HOUR MINUTE TIMER

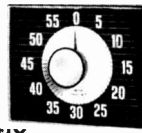Made by famous Smiths company, these have a large clear dial, size 4 1/2in. x 3 1/2in., which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch. £1.15.



THE FULL-FI STEREO SIX

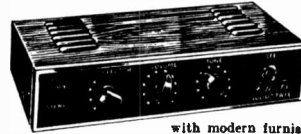

The amplifier sensation of the year You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled and teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. Price is £9 plus 35p post and insurance.

STANDARD WAFER SWITCHES

Standard size 1 1/2 water-silver-plated 5-amp contact, standard 1in spindle 2in long—with locking washer and nut.

No. of Poles 2 way 3 way 4 way 5 way 6 way 7 way 8 way 9 way 10 way 12 way

1 pole	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
2 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
3 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
4 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
5 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
6 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
7 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
8 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
9 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
10 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
11 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p
12 poles	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p	33p

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. S.A.E. with enquiries please.

SPARTAN RADIO

Long and medium wave. 7 transistor, size 6in. x 4in. x 1 1/2in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, earplug and case. £3.75 plus 25p post and ins.



MULTI-SPEED MOTOR

Replacement in many well known food mixers. Six speeds are available. 500, 860, and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. Very powerful and useful motor size approx. 2in. diameter 6in. long. Price £9p plus 25p post and ins.



MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. £1 each.



DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 50p each, plus 18p post and insurance, 8 or more post free.



0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits. 18p each, £1.20 doz.




ELECTRONICS (CROYDON) LTD
Dept. PE, 266 London Road, Croydon CR0 2TH
Also 102/3 Tamworth Road, Croydon

Your local component stockist

EAST ANGLIA
EAGLE
ELECTRONICS
EAGLE ST.
IPSWICH 50075

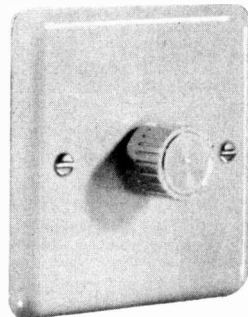Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescents at mains voltages from 200-250 V, 50 Hz. The DIMMASWITCH has built-in radio interference suppression. Price: £3.20 plus 10p post and packing. Kit Form: £2.70 plus 10p post and packing. Please send C.W.O. to:—

DEXTER & COMPANY
1 ULVÉR HOUSE, 19 KING STREET
CHESTER CH1 2AH Tel: 0244-25883
As supplied to H.M. Government Departments, Hospitals, Local Authorities, etc.

WAH-WAH PEDAL KIT

SELECTIVE AMPLIFIER MODULE. The basis of the Wah-Wah pedal. Kit contains all the components to build a 2-transistor circuit module, also the sockets, control, etc., required for the constructor to assemble his own design. £1.75. Assembled and tested module £2.13.

FOOT VOLUME CONTROL PEDAL. Foot pedal unit in very strong fawn plastic. Fitted with output lead and plug for connection to guitar amplifier. May be used for volume control or converted to Wah-Wah by adding the module. Pedal unit now only £5.13. Complete kit for Wah-Wah pedal now only £6.50.

All post free. Send 15p for our catalogue of components, testmeters, musical electronics and more details of the above items. Callers welcome.

WILSIC ELECTRONICS LIMITED
6 COPLEY ROAD, DONCASTER
YORKSHIRE

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) £2 each. P. & P. 15p. 9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) £2.50 each. P. & P. 15p. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety. R.C.S. PRODUCTS (RADIO) LTD. (Dept. P.E.), 31 Oliver Road, London, E.17

THE SOCIETY OF ENGINEERS

invites you to visit the
'ENGINEERING 71'
Exhibition at Earls Court, London (Cromwell Hall), 3.30 for 4 pm. on 29th APRIL, 1971, when a paper **HARRIER - FIRST OF THE NEW** will be presented by: **MR. J. W. FOZARD of HAWKER SIDDELEY AVIATION LTD.** Chief Designer (Harrier)
Complimentary tickets available from the Secretary **ABBAY HOUSE, VICTORIA STREET LONDON, S.W.1** Tel. 01-222 7244


ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is made of driver and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only £2. Less the value of the clock alone—post and insurance 14p.




20 AMP ELECTRICAL PROGRAMMER

Learn in your sleep: Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp Switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5 1/2 x 3 1/2 in. deep. Metal encased, glass fronted with chrome surround. Offered at £2-40 plus postage and insurance 23p.

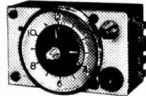

MAINS CONNECTOR

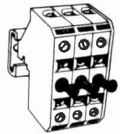A quick way to connect equipment to the mains safely and firmly; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7,029 cables. 65p each.



FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—10-20W, £1. Kit B—30-40W, £1. Kit C—50W, £1.20. Kit D—65W, £1.20. Kit E for 8ft 125W tube £1-75. Kit MF1 is for 6in, 9in and 12in miniature tubes, £1. Kit MF2 for 21in 13W miniature tube, £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23p on first kit then 18p for each kit ordered. Kit MF1 18p then 23p for each kit ordered. Kit MF2 18p on first kit then 18p on each two kits ordered.

BLANKET SWITCH

Double pole neon let into side so luminous in dark. Ideal for dark room light or for use with waterproof element—new plastic case 80p each. 3 heat model 40p.



BLANKET SIMMERSTAY

Although looking like, and fitted as an ordinary blanket, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1A. Listed at £1-40 each we offer these while our stocks last at only 65p each.

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1in long x approximately 1/4in diameter. Will fit into bread up to 1A up to 300 volts. Price 18p each, £1-20 dozen.
Standard. 2in long x 1/4in diameter. This will break currents of up to 1A, voltages up to 260 volts. Price 10p each, 80p per dozen.
Flat. Flat type, 2in long, just over 1/4in thick, flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 30p each, £2 per dozen.
Small ceramic magnets to operate these reed switches 8p each, 80p dozen.

HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-equipment.
100 mfd. 25V, 6p each 60p doz.
200 mfd. 25V, 6p each 75p doz.
250 mfd. 50V, 16p each £1-05 doz.
400 mfd. 40V, 25p each £2-30 doz.
500 mfd. 12V, 10p each £1-05 doz.
500 mfd. 25V, 18p each £1-80 doz.
500 mfd. 50V, 23p each £2-40 doz.
500 mfd. 350V, 45p each £4-50 doz.
1000 mfd. 12V, 12p each £1-40 doz.
1000 mfd. 18V, 17p each £1-70 doz.
1000 mfd. 64V, 37p each £4 doz.
2000 mfd. 25V, 34p each £3-95 doz.
5000 mfd. 12V, 24p each £2-40 doz.
10,000 mfd. 6V, 29p each £3 doz.
10,000 mfd. 15V, 30p each £4-00 doz.
15,000 mfd. 10V, 33p each £5 doz.
60,000 mfd. 8V, £1-10 each £20 doz.
70,000 mfd. 13V, £2 each £20 doz.

3 AMP 12V BATTERY CHARGER KIT—

comprising 230/40 mains transformer with 3 amp secondary and 3 amp rectifier £1-15 + 23p post. **12 VOLT 1 1/2 AMP POWER PACK.** This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mH/d/smoothing. Price £1-40. **SONOTONE STEREO CARTRIDGE.** Turnover type, ref. No. 19 T1. This fits most British pickups and is a really excellent reproducer. Limited quantity, £1.

5 AMP 3-PIN SOCKETS. These are always good stock, you never know when you will need some. Famous make, brown bakelite, standard size, 12 for 65p plus 23p post.

DITTO WIRE SWITCH. 12 for £1 plus 23p post. **13 AMP SOCKETS, WITH MOUNTING.** Bakelite, cream, less switch, 6 for £1.

BAKELITE PANELS, MANY THICKNESSES. We have just taken delivery of approximately 10 tons of bakelite in varying thicknesses from 2in. to a few thou. If you have a need for any of this then we would be glad to supply. The thickest is very heavy and could be used, for instance, as a bed for a motorised unit. Medium thickness is useful for front panels of instrument, etc., etc. Cut to your size price is 30p per lb. plus 30p cutting charge plus carriage. **2 AMP 3-PIN SWITCHED SOCKETS** for surface mounting, brown bakelite. Made by famous maker, 13p each or £1-20 dozen. **100 ASSORTED SILICON RECTIFIERS G.P. AND SWITCHING DIODES.** Small and very small sizes. A real snip for experimenters, 65p per 100.

HI-FI SPEAKERS (15, 30, 40 & 100W)

FULL FT 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwell—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—Specify 3 or 15 ohms—Mains resonance 80 c.p.s.—Chassis Diam. 12in.—12in. over mounting lugs—Baffle hole 11 in. diam.—Mounting holes 4, holes—1/2 in. diam. on pitch circle 1 1/2 in. diam.—Overall height 5 1/2 in. A £6 speaker offered for only £4, plus 37p p. & p. 12in. 40 watt £7 carr. 43p. 15in. 25 watt £8 carr. 63p. 18in. 100 watt £19.50 carr. £1-50.



CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions £1-50, plus 13p post and insurance.

BALANCED ARMATURE UNIT

500 ohm, operates speaker or micro phone, so useful in intercom or similar circuits, 33p each, £3-50 doz.




INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic MPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only £1 post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

THIS MONTH'S SNIP

ELECTRIC TIME SWITCH

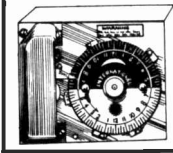Made by Smith's these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. £3-50, post and ins. 23p. Additional time contacts 50p pair.




DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to plug, £2 less plug; £2-25 with fitted 13 amp plug; £2-40 with fitted 15 amp plug, plus 23p P. & I.

BARGAIN OF THE YEAR

MICROSONIC KEYCHAIN RADIO

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/4 x 1 1/4 in.—complete with soft leather zippered bag. Specification— Circuit: 7 transistor superheterodyne. Frequency range: 830 to 1,600 Kc/s. Sensitivity: 5 mV/m. Intermediate frequency: 465Kc/s or 455Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only £1-25 plus 13p post and insurance, less batteries. 6 for £7, post free. Pair of rechargeable batteries and charger 85p.

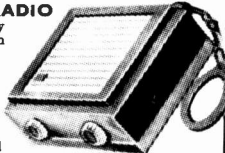

4 AMP VARIAC CONTROLLERS

With this you can vary the voltage applied to your circuit from zero to 270 volts without generating undue heat. One obvious application therefore is to dim lighting. Ex equipment but little used—as good as new offered at approx. half price—£5 plus 75p post and ins.



19-PIECE SOCKET SET

Complete with wall or bench rack. An ideal gift for the motorist. 80p + 23p; post and insurance. Most useful sizes from 1/4in to 1 1/2in.



HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which arc infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from Makers probably over £10 each. Special snip price £5-75 plus 25p post and insurance. Don't miss this terrific bargain.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semiconductors add 5p post. Over £1 post free. S.A.E. with enquiries please.


PROTECT VALUABLE DEVICES

FROM THERMAL RUN-AWAY OR OVERHEATING: Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg.F. or with the dial removed range setting is between 80 to 800deg.F. Price 50p.




THERMOSTAT WITH PROBE

This has a sensor attached to a 15A switch by a 14in length of flexible capillary tubing—control range is 20°F to 160°F so it is suitable to control acid heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heat subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddlington Co., we offer these at 65p each. Postage and insurance 14p.

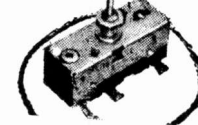

MAINS MOTOR

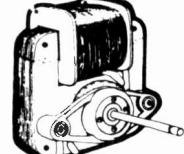Precision made — as used in record decks and tape recorders — ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.



NEED A SPECIAL SWITCH? Double Leaf Contact

Very slight pressure closes both contacts, 6p each, 60p doz. Plastic push-rod suitable for operating, 5p each, 45p doz.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 15p each. £1-00 dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

MICRO SWITCH

5 amp. changeover contacts, 5p each, £1 doz. 15 amp Model 10p each or £1-05 doz.



ELECTRONICS (CROYDON) LTD
Dept. PE, 266 London Road, Croydon CR0 2TH
Also 102/3 Tamworth Road, Croydon

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3, and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. 4 section 24in. retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7 x 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£6-98**

Post, packing and insurance 41p

Overseas
P. & P.
90p




roamer seven mk IV

7 FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (FREE with parts).

Total building costs
£5-98

Personal Earpiece with plug and switched socket for private listening, 30p extra.

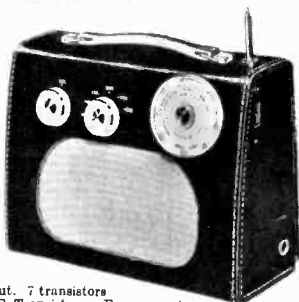Post, packing and insurance 41p
Overseas P. & P. 90p




NEW! transeight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

Total building costs
£4-48

Earpiece with plug and switched socket for private listening, 30p extra.

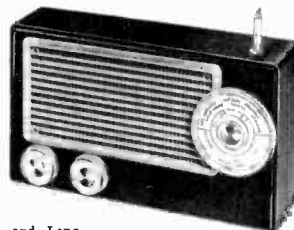
Post, packing and insurance 31p
Overseas P. & P. 70p



pocket five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND
PORTABLE
WITH SPEAKER

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2 in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Radio Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

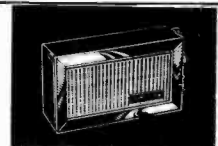

Total building costs
£2-23 Post, packing
and insurance 21p
Overseas P. & P. 55p

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND
PORTABLE
WITH SPEAKER


Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.



Total building costs
£2-38 Post, packing
and insurance 22p
Overseas P. & P. 55p

IMPROVED MODEL! roamer six SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

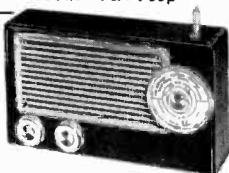

Total building costs
£3-98 Post, packing
and insurance 26p
Overseas P. & P. 70p

RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSEIGHT	<input type="checkbox"/>	POCKET FIVE	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for.....

Name.....

Address.....

PE 29

* Callers side entrance Barratts Shoe Shop

* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

Great new OFFER from DIOTRAN

TRANSISTORS

BRAND NEW FULLY GUARANTEED DEVICES

AC107	15p	AF115	17p	BC140	35p	BCY31	22p	BF272	80p	EC403	15p	ORP60	40p	2N918	30p	2N2714	25p	2N3704	15p
AC113	20p	AF116	17p	BC141	35p	BCY32	25p	BF273	30p	GET880	27p	ORP61	40p	2N929	22p	2N2904	25p	2N3705	12p
AC115	23p	AF117	17p	BC142	45p	BCY33	17p	BF274	30p	MAT100	15p	ST140	12p	2N1131	20p	2N2905	25p	2N3707	13p
AC125	17p	AF118	30p	BC143	40p	BCY34	20p	BF308	35p	MAT101	17p	ST141	17p	2N1132	20p	2N2905A	30p	2N3708	8p
AC129	17p	AF124	21p	BC145	45p	BCY70	17p	BF309	37p	MAT120	15p	TIS43	40p	2N1302	17p	2N2906	25p	2N3709	8p
AC127	17p	AF125	30p	BC147	17p	BCY71	30p	BF316	75p	MAT121	17p	UT46	27p	2N1303	17p	2N2906A	27p	2N3710	10p
AC128	17p	AF126	20p	BC148	12p	BCY72	15p	BFW10	55p	MPF102	43p	V405A	25p	2N1305	20p	2N2907	30p	2N3711	10p
AC141K	17p	AF127	20p	BC149	17p	BCZ11	20p	BFX29	27p	MPF105	43p	V410A	45p	2N1306	22p	2N2923	13p	2N3820	1p
AC142K	17p	AF139	33p	BC150	17p	BD121	85p	BFX84	20p	OC19	30p	ZG301	19p	2N1307	22p	2N2924	13p	2N3903	25p
AC151	15p	AF178	50p	BC151	20p	BD123	85p	BFX85	27p	OC20	50p	ZG302	19p	2N1308	27p	2N2925	13p	2N3904	27p
AC154	15p	AF179	50p	BC152	17p	BD124	75p	BFX86	22p	OC22	30p	ZG303	19p	2N1309	27p	2N2926	12p	2N3905	25p
AC155	17p	AF180	50p	BC153	30p	BD131	80p	BFX87	25p	OC23	33p	ZG304	19p	2N1613	17p	(G)		2N3906	27p
AC156	17p	AF191	50p	BC154	30p	BD132	80p	BFX88	22p	OC24	45p	ZG306	35p	2N1711	20p	2N2926(Y)11p		2N4058	15p
AC157	17p	AF186	45p	BC157	20p	BDY20	11p	BFY50	20p	OC25	25p	ZG308	35p	2N1889	35p	2N2926		2N4059	10p
AC165	17p	AF239	37p	BC158	17p	BF115	22p	BFY51	20p	OC26	25p	ZG309	35p	2N1890	45p	(O)	10p	2N4060	12p
AC166	17p	AFZ11	37p	BC159	20p	BF117	45p	BFY52	20p	OC28	40p	ZG339	17p	2N1893	37p	2N3010	80p	2N4061	12p
AC167	20p	AFZ12	45p	BC167	13p	BF118	60p	BFY53	17p	OC29	40p	ZG339A	15p	2N2169	60p	2N3011	20p	2N4062	12p
AC168	20p	AL102	85p	BC168	13p	BF119	70p	BSX19	15p	OC35	33p	ZG344	15p	2N2147	75p	2N3053	20p	2N5172	12p
AC169	14p	AL103	85p	BC169	13p	BF152	35p	BSX20	15p	OC36	40p	ZG345	15p	2N2148	60p	2N3054	50p	2N5459	43p
AC176	23p	ASV26	25p	BC170	12p	BF153	35p	BSY25	15p	OC41	20p	ZG371	13p	2N2192	30p	2N3055	63p	2N534	75p
AC177	20p	ASV27	30p	BC171	13p	BF154	35p	BSY26	15p	OC42	22p	ZG371B	10p	2N2193	30p	2N3391	17p	25301	50p
AC187	30p	ASV28	25p	BC172	13p	BF157	45p	BSY27	15p	OC44	15p	ZG374	17p	2N2194	27p	2N3391A	20p	25302A	45p
AC188	30p	ASV29	25p	BC173	13p	BF158	25p	BSY28	15p	OC45	12p	ZG377	27p	2N2217	20p	2N3392	17p	25302	45p
AC197	25p	ASV50	25p	BC174	13p	BF159	30p	BSY29	15p	OC70	15p	ZG378	15p	2N2218	25p	2N3393	15p	25303	60p
AC198	20p	ASV51	25p	BC175	22p	BF160	30p	BSY38	18p	OC71	9p	ZG382	15p	2N2219	15p	2N3414	15p	25304	45p
AC199	20p	ASV52	25p	BC177	17p	BF162	30p	BSY39	15p	OC72	12p	ZG401	30p	2N2220	22p	2N3395	20p	25305	1p
AC200	20p	ASV54	25p	BC178	17p	BF163	35p	BSY40	30p	OC74	12p	ZG414	30p	2N2221	22p	2N3402	22p	25306	1p
AC201	20p	ASV55	25p	BC179	17p	BF164	35p	BSY41	35p	OC75	15p	ZG417	25p	2N2222	27p	2N3403	22p	25307	1p
AC222	19p	ASV56	25p	BC180	20p	BF165	35p	BSY95	12p	OC76	15p	ZG418	25p	2N2368	30p	2N3404	32p	25321	60p
AC227	18p	ASV57	25p	BC181	22p	BF167	22p	BSY95A	12p	OC77	25p	ZN388A	50p	2N2369	15p	2N3405	45p	25322	50p
AC228	19p	ASV58	25p	BC182	10p	BF173	22p	BU105	£3.90	OC81	15p	ZN404	22p	2N2369A	15p	2N3414	15p	25322A	45p
AC229	30p	ASV58	25p	BC182L	10p	BF176	35p	CI11E	60p	OC81D	15p	ZN404A	30p	2N2411	50p	2N3415	20p	25323	60p
AC300	25p	BZ21	17p	BC183	10p	BF177	35p	C400	20p	OC82	15p	ZN524	55p	2N2412	50p	2N3417	37p	25324	1p
AC331	25p	BC107	10p	BC183L	10p	BF178	45p	C407	25p	OC82D	15p	ZN527	60p	2N2416	55p	2N3525	74p	25325	1p
AC334	18p	BC108	10p	BC184	13p	BF179	50p	C424	17p	OC83	20p	ZN696	12p	2N2711	22p	2N3702	12p	25326	1p
AC335	18p	BC109	11p	BC184L	13p	BF180	30p	C425	40p	OC84	20p	ZN697	15p	2N2712	22p	2N3703	12p	25327	1p
AC336	30p	BC113	25p	BC186	27p	BF181	30p	C426	30p	OC139	15p	ZN698	24p						
ACY40	15p	BC114	30p	BC187	27p	BF182	30p	C428	20p	OC140	17p	ZN699	55p						
AD141	18p	BC115	30p	BC207	11p	BF183	30p	C441	27p	OC170	15p	ZN706	7p						
AD144	35p	BC116	35p	BC209	11p	BF184	25p	C442	35p	OC171	15p	ZN706A	8p						
AD140	40p	BC117	35p	BC209	11p	BF185	30p	C444	37p	OC200	25p	ZN708	12p						
AD142	40p	BC118	25p	BC212L	11p	BF188	30p	C450	17p	OC201	27p	IN709	45p						
AD149	43p	BC119	45p	BC213L	11p	BF194	23p	C720	12p	OC202	27p	IN711	40p						
AD161	35p	BC125	35p	BC213L	11p	BF195	24p	C722	25p	OC203	25p	IN717	42p						
AD162	35p	BC126	35p	BC214L	12p	BF196	30p	C740	25p	OC204	25p	IN718	24p						
AD161/162(MP)	63p	BC132	35p	BC225	25p	BF197	35p	C742	17p	OC205	25p	IN718A	50p						
ADT140	50p	BC134	30p	BC226	35p	BF200	45p	C744	17p	OC309	35p	ZN726	27p						
ADZ11	42p	BC135	30p	BC217	12p	BF222	80p	C760	17p	P346A	17p	ZN727	27p						
ADZ12	42p	BC136	30p	BC218	12p	BF257	35p	C762	17p	P397	45p	ZN743	17p						
ADZ13	42p	BC137	35p	BC219	12p	BF270	25p	C764	60p	OCP71	43p	ZN744	17p						
AF114	17p	BC139	45p	BCY30	20p	BF271	17p	EC401	15p	ORP12	43p	ZN914	17p						

DIODES & RECTIFIERS

AA119	8p	BYZ11	32p	OAB1	7p
AA120	8p	BYZ12	30p	OAB5	7p
BA116	22p	BYZ13	25p	OA90	6p
BA126	22p	BYZ16	35p	OA91	7p
BY100	15p	BYZ17	35p	OA95	7p
BY101	12p	BYZ18	30p	OA200	6p
BY105	15p	BYZ19	25p	OA202	7p
BY114	12p	OA5	17p	SO10	4p
BY126	15p	OA10	22p	SO19	4p
BY127	17p	OA47	7p	IN914	6p
BY130	15p	OA70	7p	IN916	6p
BYZ10	35p	OA79	8p	IN4148	6p

1,000,000

NPN-PNP PLASTIC AND TRANSISTORS METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

TYPE STN18. Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77.

Price: 500 £9, 1,000 £15

TYPE STP18. Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18.

Price: 500 £9, 1,000 £15

TYPE STNL. Silicon Plastic Epitaxial Planar Transistors TO-92 case. I.C. 200mA, 300mV medium to high gain, available in npn or pnp and types similar to: NPN2N2926-2N2711-2N3391-2N3707-2N3711-BC167-8-9.

Price: 500 £7 50; 1,000 £13

TYPE STPL. As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL.

Price: 500 £7 50; 1,000 £13

TYPE STNK. Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration, I.C. 200mA, 300mV and similar to BC107-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8.

Price: 500 £9 50; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.

1,000,000

TRANSISTORS FOR SALE

Clearance of npn Silicon Transistors from the 2S300 (TO-5) and 2S320 (SO-2) range and similar to the GC200-205 and BCY30-34 series. Ideal for Amateur Electronics, Radio Hams and for experimental use in Schools, Colleges and Industry.

Approximate count by weight:

100 off—75p (plus p. & p. 10p)
300 off—£1.75 (plus p. & p. 15p)
500 off—£2.50 (plus p. & p. 17p)
1,000 off—£4 (plus p. & p. 25p)
10,000 off—£35 (plus p. & p. 55p)

Large quantities quoted for on request.

EXPORT INQUIRIES WELCOME

DIOTRAN

SALES PO BOX 5, WARE, HERTS

Full Money-Back
Guarantee

TRANSISTOR EQVT. BOOK

2,500 cross references of transistors—British, European, American and Japanese. A must for every transistor user. Distributed by DIOTRAN SALES. 75p EACH.

SIL. G.P. DIODES

300mV	30		50p
400V (Min.)	100		£1.50
Sub-Min.	500		£5
Fully Tested 1,000			£9

Ideal for Organ Builders.

BRAND NEW FULLY TESTED EPOXY CASE UNIONIUM TRANSISTORS. Type TIS43 and BEN 3000 and replacement for 2N2646. Full data available. LOWEST PRICE AVAILABLE ANYWHERE. 100 off 20p each = £20; 500 off 17p each = £87.50; 1,000 off 15p each = £150. Sample devices 35p each on request.

HIGH QUALITY SILICON PLANAR DIODES, SUB-MINIATURE DO-7 Glass Type, suitable replacements for OA200, OA202, BAY38, IS130, IS940, 200,000 to clear at £4 per 1,000 pieces. GUAR. 80% GD.

OA90 GERM. DIODES 30PW 45MA DO-7 GLASS. 30,000 Available. New and Coded. Price £3 per 100, £11 per 500, £17 per 1,000 pieces. Once sold cannot be repeated.

FULLY TESTED DEVICES AND QUALITY GUARANTEED—SURPLUS TO REQUIREMENTS

OA202 Silicon Diode. Fully Coded. 150 PIV 250mA Qty. Price £30 per 1,000 pieces.
OA200 Silicon Diode. Fully Coded. 50PIV 250mA Qty. Price £25 per 1,000.
IN100 Sil. RECT'S 800 PIV 550mA. 1-49 12p each; 50-99 11p each; 100-999 10p each; 1,000 up 9p each. Fully Coded. 1st Qty.

Practical Electronics Classified Advertisements

RATES: 7½p per word (minimum 12 words). Box No. 7½p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

MISCELLANEOUS

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: 'BOFFIN PROJECTS'
DEPT. K2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

FABRICA PANELS, hi-fi equipment, etc., etched aluminium to individual specifications, S.A.E. details. R. MARSH, 29 Shelbourne Road, Stratford on Avon, Warwicks.

MUSICAL MIRACLES

WAA-WAA Pedal. Complete kit of all parts, robust cabinet, mechanism and instructions. Huge sales, well proven design. Only £2.45 complete. Or built and tested £4.75 post free. **Rhythm Box**. Build your own from our pre-built electronic circuit modules, e.g. box giving waltz, foxtrost, etc., costs under £17.

Organ Percussion units £14. Bass pedal and other fascinating effects; fuzz, reverb, etc. Send 15p for list: D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset

12 VOLT FLUORESCENT LIGHTS

Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc., Fully Transistorised, Low Battery Drain, with ON/OFF Switch and 12V Socket to Run other Lights or 12V Equipment.

Unbeatable at **£3.30**
or in kit form **£2.90** post paid

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **£3.63** POST PAID


SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire S.A.E. for lists

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send 4 × 3p stamps NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 50p). No callers please, mail-order ONLY.

AUDIOSCAN Dept. P.E.5
4, PRINCES SQUARE
HARROGATE, YORKS.

BUILD IT IN A DEWBOX quality cabinet 2½n x 2½n x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

MISCELLANEOUS (continued)

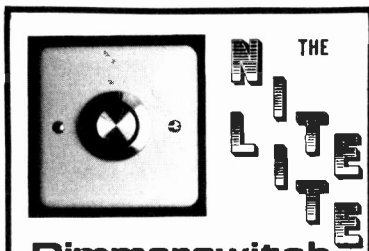

Dimmerswitch

Will dim up to 400 watts of Incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is fitted in a matter of minutes. An MK mounting frame is supplied, for use when more depth is required.

Complete Kit: **£2.85** (incl. P.
Built & tested: **£3.35** (incl. P.)

Diathane Ltd.

111, Sheffield Road, Wymondham, NORFOLK.
£0.10 postage & packing

NEW! NEW!! NEW!!!

The Sweetest Sound You Ever Heard

An exciting new, all silicon, power amplifier module to a completely NEW design. Minimum cross-over distortion, not dependent on supply voltage, eliminates unpleasant 'transistor sound'. Specially designed to work well from simple, unregulated power supply, 50-58 v. 11 transistors, short circuit proof, unconditionally stable, temperature stabilised. 400 mV input for 30 watts RMS (8 ohms). Output impedance 8-16 ohms. Completely built on 16 swg heatsink. Neat, space-saving, upright mounting. Fully tested and guaranteed with comprehensive instructions.

£8.75 each. P. & P. 15p. Stereo pair. Post free

Coming Soon! Matching Mono/Stereo Pre-amplifier designs to the same high standard. Available in Kit form. Telephone: Sheffield 365168

ELECTRONIC SUPPLIES
P.O. BOX 148, SHEFFIELD S17 3EX

PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use RF, SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM; YOUR FRIENDS WOULD BE AMAZED! If REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT: in a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"! DON'T PUT IT OFF! SEND 15p for your list—NOW

BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY
Designs by GERRY BROWN and JOHN SALMON
and presented on TV

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

MISCELLANEOUS (continued)

TOP TRANSISTORS

Unmarked but brand new and individually tested. We will refund your money and postage in full if any of our transistors are found to be faulty. All at 9p each or

Any 25 transistors for only £1.90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

MONEY BACK GUARANTEE. P. & P. 10p.

J. M. KING (D)

17 Buckridge, Portpool Lane, London E.C.1

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

MORSE MADE !!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring B.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:

G8EBC (Box 19), 45 GREEN LANE, PURLEY, SURREY

CATALOGUE NO. 18, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

PRACTICAL ELECTRONICS from No. 1 to current issue, with binders and indexes, accept best offer—Box No. 36.

WANTED

CASH PAID for New Valves. Payment by return. **WILLOW VALE ELECTRONICS**, 4 The Broadway, Hanwell, London. W.7. 01-567 5400/2971.

WE BUY NEW VALVES. Cash sent by return. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

TOP PRICES PAID

for new valves and components
Popular T.V. and Radio types
KENSINGTON SUPPLIES
(B) 367 Kensington Street
Bradford 8, Yorks.

HIGHEST CASH PRICES for tape recorders. 9.30-5. Immediate quotations. 01-472 2185.

MUSICAL INSTRUMENTS

ELECTRONIC ORGAN DIVIDER CIRCUITS

These i.c. divider circuits contain one master oscillator and six dividers. The output is square wave with a rise time of approximately 20 n secs. and size is only 2½" x 1½" x ½". Price £3.75 each or £42 per dozen. Edge Connectors are available at 22½p each. C.W.O. please, to:

AUDIONIC, 105 Anson Road
Great Wyrley, Walsall WS6 6JP



TELEVISION AND RADIO TRAINING

(DAY ATTENDANCE COURSES)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of one year's duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Radar and Radio Transmission are also available following the TV course. Write for prospectus to: London Electronics College, Dept. B/3, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373 8721.

EDUCATIONAL

HUNDREDS OF TOP PAID JOBS in engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful FREE book, B.I.E.T., Department 125K, Aldermaston Court, Reading, RG7 4PF.

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For free informative Guide, write CHAMBERS COLLEGE (Dept. 856K), Aldermaston Court, Reading, RG7 4PF.

A.M.S.E. (Elec.), City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio and TV, etc. Send for full details and illustrated book—FREE. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 124K Aldermaston Court, Reading, RG7 4PF.

MEN! You can earn £50 p.w. Learn Computer Operating. Send for FREE brochure—LONDON COMPUTER OPERATORS TRAINING CENTRE, C95 Oxford House, 9-15 Oxford Street, London, W.1.

SERVICE SHEETS

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6 (01-743 8441).

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, CAR RADIOS
25p EACH, MANUALS FROM 50p
PLEASE ENCLOSE LARGE S.A.E. WITH ALL INQUIRIES AND ORDERS.
OTHERWISE LETTERS NOT ATTENDED TO
(Uncrossed P.O.'s please, original returned if service sheets not available.)
FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER

C. CARANNA
71 BEAUFORT PARK, LONDON, N.W.11
MAIL ORDER ONLY

LADDERS

VARNISHED TIMBER LADDERS from manufacturer, LOWEST PRICES anywhere: 15ft ext., £6-20; 17ft extd., £6-50; 20ft extd., £7; 21ft extd., £7-75; 24ft extd., £8-90; 29ft extd., £10-25; 31ft triple extd., £12-25; 36ft. triple extd., £18. Carr. 80p. Free Lists. Also Aluminium Ext. and Loft Ladders. Callers welcome. Dept. PEE, HOME SALES, Baldwin Road, Stourport, Worcs. Phone: 0-2993 2574. Placing order on C.O.D.

RECEIVERS AND COMPONENTS

A CORNUCOPIA OF COMPONENTS! Scarce valves, selected TV components, speakers and cabinets. Computer panels—long leads, NOT printed circuits. Transistors, resistors—new and recovered. State your requirements. S.A.E. for details MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

HI-STAB RESISTORS mixed bag, 100, 50p; 250, £1. Please send cash with order to ELM-BRIDGE INSTRUMENTS LTD., Island Farm Avenue, West Molesey Trading Estate, Surrey.

8 WATT TRANSISTOR AMPLIFIERS £3-45 Intercoms Ohden 2 stations, £2-50; Capacitors Dubillier, 0.1µF 500V, 30p doz; Hunts 0.04µF 500V, 15p doz; Co-ax sockets on isolation panel, 6p, 60p doz; Jack plugs, standard, 9d; 3.5mm 5p; GP91-38C, 90p, 93-1, £1-22, 400-200-50-16µF 300V, 30p; £3 per doz. Switches rotary DP 2A 9d. S.A.E. for list. Post and Packing on orders under £5 add 10p — M. DZIUBAS, 158 Bradshawgate, Bolton, Lancs.

SITUATIONS VACANT

EAGLE INTERNATIONAL require Audio Engineers. Excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact MR. MORROW 01-636 0961.

RECEIVERS AND COMPONENTS

R & R RADIO

51 Burnley Road, Rawtenstall

Rossendale, Lancs

Tel.: Rossendale 3152

TESTED VALVES—3 MONTHS' GUARANTEE

EBF80	15p	PCC84	15p	PY800	17½p
EBF89	17½p	PCF80	15p	PY801	17½p
ECC82	15p	PCL82	20p	U191	22½p
ECL80	15p	PL36	25p	30C15	25p
EF80	10p	PY33	25p	PCF86	25p
EF85	15p	PY81	17½p	PCL85	25p
EY86	20p	PY82	15p	PCL84	25p

Copper Laminate Board, for etching, 1p per sq.in. Double sided 1½p per sq.in. Any size cut, min. order 50p plus 10% P. & P.

Postage on Valves: one valve 4p, up to 6 2½p, over 6 post paid.

HIGHEST GAIN low noise NPN, BC180C, hfe=450-900, mint, branded, 4 for 50p. U.K. post 5p. S.A.E. list—AMATRONIX LTD., 386 Seisdon Road, S. Croydon, Surrey CR2 0DE.

PRINTED CIRCUITS designed, produced, components assembled if required. Send details—JON TECHNICAL SERVICES, c/o Winchells, Ashford Road, Ashford, Middlesex.



Established 1891

TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- * C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- * C. & G. ELECTRONIC SERVICING.
- * R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- * RADIO AMATEURS' EXAMINATION.
- * RADIO OPERATOR CERTIFICATES.


Examination Students coached until successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

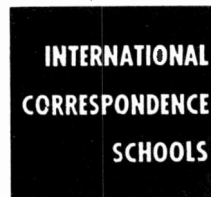MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES



A WHOLE WORLD OF KNOWLEDGE AWAITS YOU!

International Correspondence Schools
(Dept. 152), Intertext House, Stewarts Road,
London, S.W.8

NAME.....
Block Capitals Please

ADDRESS.....

AGE..... OCCUPATION...../5/71

RECEIVERS AND COMPONENTS

(continued)

Microcircuits:

709	47p	MEL11	47p
PA234	87p	7420	28p
SL402A	£1.00	PA230	92p
7410	28p	D40C1	67p
741	88p	DIL Conn.	30p
PA237	£1.57	7430	28p

Transistors:

ME402	21p	2N4059	15p
ME4102	12p	ME4101	11p
2N5172	28p	MP1811	35p
ME412	20p	2N3055	65p
ME6101	15p		

Rectifiers:

IN4001	7p	PL4003	11p
IN4002	8p	W02	40p
PL4002	10p	IN4005	12p
W005	37p	IN4006	14p
IN4003	9p	PL4004	12p
IN4004	10p	PD40	62p
40583 Diac Trigger Diode	26p		

JEF ELECTRONICS (P.E.5)

York House, 12 York Drive, Grappenhall Warrington, Lancs. Mail Order Only C.W.O. P. & P. 5p per order. Overseas 3p Money back if not satisfied

PRINTED CIRCUIT BOARDS for P.E. PROJECTS

All boards drilled and roller tinned complete with layout drawing.

EXAMPLES

Marine Tachometer (May 1970) 25p ea. Musical Stave (May 1970) 40p ea. Waa-Waa pedal Vol. 4 No. 7 14p ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 42p ea.

S.A.E. for List. Now available from:- HENRY'S RADIO LTD., Eborac Road, London, W.2 P.H. ELECTRONICS, Industrial Estate, Sandwich, Kent. Tel. 2517

TRANSFORMER KITS

Consisting of:- CLAMPS, WINDING BOBBIN AND LAMINATIONS

Max. Rating	Ref. No.	Price	P. & P.
5 VA	74163	45p	7½p
10 VA	3575	52½p	12½p
15 VA	14788	75p	17½p
25 VA	29/1	£1-02½	22½p
50 VA	78/125	£1-77½	27½p
75 VA	78/150	£2-37½	32½p
100 VA	120/125	£2-75	37½p

Transformer designs up to 100VA 50p ea., larger kits and designs available on request.

Supplied by:

WEST DIDSBURY TRANSFORMERS
Brooks Street, Higher Hillgate
Stockport, Cheshire SK1 3EU
Tel. 061-480 6479

C.T. ELECTRONICS

267 Acton Lane, W.4
Phone 01-994 6275

West London New Electronic Components Shop, wide range of Components in stock, including metal oxide resistors, relays from 50p each.

COMPUTER PANELS. 5-BC108 diodes, 15p (8/-), post 5p (1/-), 4-50p (10/-), post 15p (3/-). 8-OC76/OC72/OC42, 80A10 diodes, 40p (8/-), post 10p (2/-) per panel. 8-OC170 diodes, 40p (8/-), post 8p (1/7) per panel. 2-OC170, 2-GET875 or 4MD834, 5-100mfd 12V Electrolytics, pot core, etc., 30p (6/-), post 8p (1/7) per panel.

PANELS WITH VHF PNP AND/OR PNP SILICON TRANSISTORS, resistors, diodes, capacitors, etc. Panels with 4 transistors 10p (2/-), with 6-8, 15p (3/-). 10-12, 25p (5/-). 14-16, 30p (6/-). 24, 40p (8/-). 30-32, 50p (10/-). Post up to four 15p (3/-), five or over, 25p (5/-).

MIXED TRANSISTORS ON PANELS. 50 for 80p (16/-). 100 for £1.85 (27/-). C.P. panels with resistors, caps. and diodes, 6 for 25p (5/-). Post 15p (3/-) for six.

POLYSTYRENE CAPACITORS. 125V, 18, 22, 120, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 15p (3/-) dozen. Post free with other goods otherwise 10p (2/-).

ASSORTED COMPONENTS. 7lb. £1.10 (22/-) C.P. J.W.B. RADIO
75 Hayfield Road, Salford 6, Lancs.
MAIL ORDER ONLY

RECEIVERS AND COMPONENTS

(continued)

EX COMPUTER PRINTED CIRCUIT PANELS

2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 28 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1, P. & P. 25p.

LARGE CAPACITY ELECTROLYTICS

10,000MFD 30V } 40p each, P. & P. 6p.
16,000MFD 12V }
or £3-50 per doz. Carr. 50p.

250 MIXED RESISTORS 62p
½ & ¼ watt.

150 MIXED HI STABS 62p
½, ¼ & 1 watt 5% & better.

EXTRACTOR/BLOWER FANS (PAPST)

100 CFM 2,800 RPM 4½in x 4½in x 2½in. Ideal for kitchen extraction, instrument cooling, etc. etc. £2-50, P. & P. 25p. 240V a.c. 50 cycles

DIODES EX EQPT. SILICON

1 Amp 1,000 PIV 4 for 80p
20 Amp 150 PIV 4 for £1.
P. & P. 5p.

BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2-5kΩ coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
52 EARLS COURT ROAD
LONDON, W.8 01-478 8499

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62½p per doz.: £3-75 per 100; £37-50 per 1,000; £150 per 10,000. All carriage paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34887

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15 or 25V 1-10mfd, 3½p. 20-100 mfd, 4p. Mylar Film 100V 0-001, 0-002, 0-005, 0-01, 0-02, 2p. 0-04, 0-05, 0-1, 2½p. Mullard miniature Carbon Film Resistors E12 Series ¼W 1Ω-10MΩ, 8 for 5p. Postage 5p. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield S8 0RN.

NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio, 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.


Only 43-40. P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12p. P. & P. Free.


Cheques, Postal Orders, to:

Dept. PE
Gallean Trading Co., 25 Avelon Road
Romford, Essex

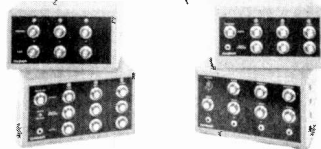P.E. AURORA. Component Kits. S.A.E. OPTELMEC LTD., 1, 2 & 3 Nelson Works, Back Road, Sidecup, Kent.



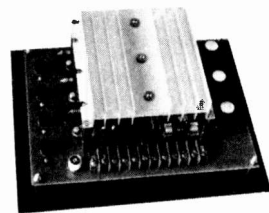Complete range of Kinetic Lighting Effects units and 100W Mixer-Amplifier. Send 5p in stamps for further details.



Still available—our ever-popular Mk.2 Psychodelic Lighting Unit, manufactured on professional fibre-glass printed-circuit board material.

Drive voltage is derived directly from amplifier output or across speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

Uses latest full-wave triac circuitry and incorporates signal input level and minimum ambient light level controls. Will drive up to 1-5KW per channel at 240V a.c. Complete printed-circuit board assembly built and tested. Size 8½in x 6½in x 3½in. £17.50 net plus 50p carriage

INSTRUMENTAL AUDIO EFFECTS

CREATE "PHASE" on your tape recordings, records, etc., unique electronic circuitry enables you to create "phase" at the turn of a knob. Just connect between pre-amp. and power-amp.

This is not waa-waa, white-noise or swish but genuine phase-shift created electronically. Input and output impedances match to 10-50kΩ. Operates from 9V battery. Complete printed-circuit assembly, built and tested. Size 4in. x 2½in. 1½in. £3.25 plus 10p carriage.

OR £2.50 plus 10p carriage in KIT FORM


SUPER "FUZZ" UNIT. Connects between guitar and amplifier. Operates from 9V battery. Complete printed-circuit board assembly, built and tested. Size 3½in. 2½in. ½in. £3.25 plus 10p carriage.

OR £2.50 plus 10p carriage in KIT FORM

MAIL ORDER ONLY
S.a.e. for all enquiries

Dabar Electronic Products
98a Lichfield Street, Walsall, Staffs.

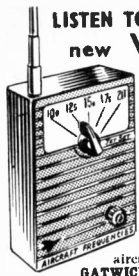LISTEN TO AIRCRAFT COMMUNICATIONS
new **V.H.F. AIRCRAFT**
BAND CONVERTER



ONLY **£2-37**

Listen in to AIRLINES, PRIVATE PLANES, JET PLANES. Eavesdrop on exciting cross-talk between pilots, ground approach.

(47/6) ground control, airport tower. Hear for yourself the disciplined voices when they have to take nerve-ripping decisions in emergencies—tune in to the international distress frequency. Covers aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2 in x 3 in x 1 1/2 in. All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny pocket radios). **NO CONNECTIONS WHATSOEVER NEEDED.** Use indoors or outdoors. **SEND NOW. ONLY £2-37 + 23p (4/6) P. & P.** for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately).

SHORTWAVE TRANSISTOR RADIO

ONLY **£2-25**


CAN BE BUILT IN ONE EVENING



At last! After trying countless circuits searching for easy built, work-first-time short wave. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 3 in. x 4 1/2 in. x 1 1/2 in. A tremendous demand anticipated price held to only £2-25 + 17p P. & P. (45/- + 3/6) for all parts incl. cabinet, screws, instr., etc. Parts available separately.

Examine at home for 7 days. Your money back if not delighted.

REAL WORKING ELECTRONIC ORGAN

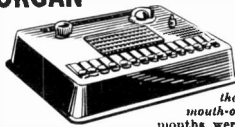

ONLY **£2-75**

(55/-)

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised, no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", "Silent Night", "Auld Lang Syne", and lots of similar tunes on this real working electronic organ. Size 13 1/2 in x 10 in x 2 1/2 in. Uses standard battery. Have the thrill and excitement of building it together with the pleasure of playing a real electronic organ. Play it anywhere. No soldering necessary. Easy as A.B.C. to make following the fully illustrated, step-by-step instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low price. **ONLY £2-75 + 23p P. & P.** (55/- + 4/6) for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformers, volume control, wire, nuts, screws, instructions, etc. (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

MAKE 5 PROJECTS

INCLUDING 3 TRANSISTOR LOUDSPEAKER RADIO



LIMITED QUANTITY **£1-97**

Amazing Radio Construction set for £1-97 (39/6). A complete Home Radio Course. No experience needed.

Parts including plans, all transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation box as illustrated 37p extra (7/6) if reqd. (parts avail. separately). Send only **£1-97 + 23p P. & P.** (39/6 + 4/6).

FIND BURIED TREASURE!
TREASURE LOCATOR—

NOW IT'S HERE AT LAST.



ONLY **£2-37**

(47/6)

after experimenting for four and a half months with a number of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location (no phones used—uses only transistor radio which fits inside—no connections needed). **FINDS GOLD, SILVER, LOB COINS, BULLION, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS, ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground. Can be built with ease in one short evening with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions. Fully transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2 in x 10 in x 2 1/2 in. **Great demand expected at this remarkably low price—All parts including detector head case, nuts, screws, wire, simple instructions, etc. Send now £2-37 + 33p P. & P.** (47/6 + 6/6) (Telescopic handle as illustrated £1-75 (35/-) extra). Parts available separately. Made up looks worth £15.

Examine at home for 7 days. Your money back if not delighted.

CONCORD ELECTRONICS LTD. (P.E.18) · 8 WESTBOURNE GROVE · LONDON · W.2
(Near Bayswater Tube) Callers welcome. 9-6 including Saturdays

ENAMELLED COPPER WIRE

S.W.G.	1/2 lb. Reel	1 lb. Reel
18-22	62 1/2 p	92 1/2 p
23-30	65 p	97 1/2 p
31-35	67 1/2 p	£1-02 1/2
36-40	82 1/2 p	£1-32 1/2
41-44	97 1/2 p	£1-62 1/2

Orders despatched by return of post.
Please add 12 1/2 p per item P. and P.

Supplied by:

BANNER TRANSFORMERS
(Dept. PE), Brooks Street
Higher Hillgate, Stockport, Cheshire

The most accurate pocket size CALCULATOR in the world



The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send £4-25 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

CARBIC LTD. (Dept. K2)
54 Dundonald Road, London, S.W.19



FREE
BOOKLET ON REQUEST


BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power 35 watts
Bass Resonance 35 c.p.s.
Flux Density 15,000 gauss
Voice coil impedance 8 or 15 ohms models
Useful response 20-14,000 c.p.s.
Nett weight 15 lbs.

£19
POST FREE

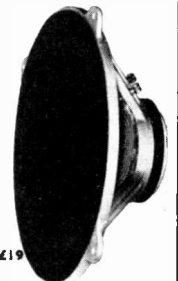GUITAR MODEL "GROUP 50" 50 watt rating £19
LATEST catalogue 5p with enclosure plans



Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical
A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology

B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D256, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)

POST THIS COUPON TODAY



To: B.I.E.T., Dept D256, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age

Address

Occupation

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/asia) Ltd.; South Africa - Central News Agency Ltd.; Rhodesia and Zambia - Kingstons Ltd.; East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.65 (£2.13.0.). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

HENRY'S RADIO LIMITED

HENRY'S RADIO


ENGLAND'S LEADING ELECTRONIC CENTRES

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

TRANSISTOR AMPLIFIERS NEW RANGES NOW IN STOCK

(Leaflets Ref. No.: 6 and 8).
Post, etc., 20p.

4-300 4TR 9V 300mW	£1-75
104 4TR 9V 1W	£2-12
304 4TR 9V 3W	£2-47
555 6TR 12V 3W	£2-75
PA7 6TR 16V 7W	£3-62
608 6TR 24V 10W	£4-12
410 4TR 28V 10W	£4-97
MPA12/3 6TR 18V 12W	£4-50
MPA12/15 6TR 36V 12W	£5-25
Z30 9TR 30V 20W	£3-75
PA25 10TR (Special) 25W	£7-50
Z50 30V 40W	£5-47
PA50 12TR 50W	£9-50
100 100W with power supply	£45

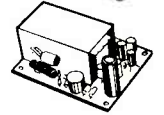

Post, etc., 20p

OPTIONAL POWER SUPPLIES

P500 (One or Two) for 104, 304	£2-62
P520 (One or Two) for PA7	£3-47
MU24/40 (One or Two) for MPA12/3 or MPA12/15	£4-50
PZ5 for Z30	£3-97
PZ8 for Z50	£5-97
P11 for 608	£2-87
P15 for 410	£2-62
MU442 for 1 or 2 PA25 or 1 only PA50	£6-50

PROJECT 60 PACKAGE DEALS


2 x Z30 amplifier, stereo 60 pre-amp. PZ5 power supply, £19. Carr. 40p. Or with PZ6 power supply, £21. Carr. 40p. 2 x Z50 amplifier, stereo 60 pre-amplifier PZ8 power supply, £21-50, p.p. 40p. Transformer for PZ8 £2-25 extra. Any of the above with Active Filter unit add £4-87 or with pair Q16 speakers add £16. Also VHF FM TUNER, £21.

BUILD THIS VHF FM TUNER



5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 and 7. TOTAL £6-97, p.p. 20p. Cabinet £1. Decoder Kit £5-97, Tuning meter £1-75. Mains unit (optional) Model PS900 £2-47. Mains unit for Tuner and Decoder PS1200 £2-62.

BUILD YOURSELF A QUALITY RADIO

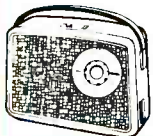

Excellent printed circuit design with full power output. Fully tunable on both MW/LW bands. 7 Mullard transistors. Fixed 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions. Total cost £6-98, p.p. 35p. All parts sold separately. Ask for Leaflet No. 1.

HI-FI TO SUIT EVERY POCKET



CHOOSE FROM 100 STEREO SYSTEMS

and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store. LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only). FREE—Stock Lists Nos. 16/17 on request—BEST VALUE IN U.K.

HENRY'S LATEST CATALOGUE



Now 350 pages
WHY NOT SEND AWAY TODAY?

• COMPONENTS, TEST GEAR

• EQUIPMENT, MODULES

• SPECIAL OFFERS, Etc., Etc.

Everything for the constructor. Complete with 50p value discount vouchers for use with purchase. Price 50p, post free.

FREE 8 page Transistor, IC, Diode lists No. 36

FREE 20 page Organs to Build brochure No. 9

FREE Decks and Hi-Fi Stocks Lists No. 16/17


FREE PA, Disco and Lighting List No. 18

FREE Quotations for all Electronics—send list and S.A.E.

TEST EQUIPMENT FOR HOME, SCHOOL & PROFESSIONAL USE



AF105 50k/V multimeter (illus.). Price £8-50, p.p. 20p. Leather case £1-42.
200H 20k/V. Price £3-87, p.p. 20p. Case £2.
500 30k/V multimeter. Price £8-87, p.p. 20p. Leather case £1-50.
THL33 2k/V. Price £4-12, p.p. 15p. Leather case £1-15.
TE65 Valve voltmeter (illus.). Price £17-50, p.p. 40p.
SE250B Pocket pencil signal injector £1-75 post paid.
SE500 Pocket pencil signal tracer £1-50 post paid.
TE20D RF generator. Price £15, p.p. 40p.

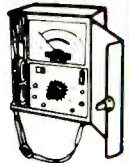

TE22D Matching audio generator. Price £17, p.p. 40p.


TE15 Grid dip meter. Price £12-50, p.p. 40p.

TO3 Scope 3 in. tube. Price £37-50, p.p. 50p.

TE22 Audio Generator. £17, p.p. 40p.

(Get a copy of our latest catalogue for full specifications and further ranges.)

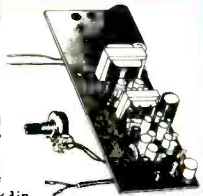NEW MINIATURE LOW COST AMPLIFIER MODEL 4-300



9V operated or mains unit optional transformer (MT98 70p, 1-10mV adjustable sensitivity. P/P output for 3-8 ohms. Fitted volume control and leads. Size 5 1/2 in x 1 1/2 in x 3/4 in. Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit.

Price £1-75
P.P. 15p. Complete with FREE leaflet No. 8.

STC TIME DELAY MODULE



Ideal for experimenters, educational projects as well as for practical uses. Delay adjustable 3-15 secs. Operates 9-12 volts. Heavy Duty Relay Contacts. Complete with suggested applications sheet. Price £1-75 post paid.

GARRARD TAPE DECK



Price £9-97

P.P. 33p (3 1/2 in. tape 300ft. and spool 40p.

9V operated 2-speed tape deck fitted Record/Replay 3 track and Erase/Bias Osc. Head. Complete with Oscillator/Record head circuit. Unit size 9 in x 6 1/2 in x 1 1/2 in and 2 1/2 in below motor board. Takes up to 4 in spools. Supplied Brand New.

HENELEC SELF-POWERED PREAMPLIFIERS

Designed for use with PA25 and PA50 Amplifiers.



SLIM MODERN DESIGNS USING THE LATEST SILICON TRANSISTORS, FET's and IC's, DIN SOCKETS, ETC., fitted. Self powered PUSH-BUTTON SELECTION. ±20dB BASS AND TREBLE BOOST AND CUT. All inputs provided plus TAPE RECORD and REPLAY.

GOLD AND SILVER FINISH. Mains operated. Supplied with all plugs, etc. ADJUSTABLE OUTPUT UP TO 1 VOLT.


• FET9/4. Mono with built-in mic. mixer. Accepts any ceramic or crystal cartridge. Plus tuner, tape, etc. Price £12-50, p.p. 20p.

• FET154 STEREO (illus.). Magnetic cart. input, tuner, tape, etc. Beautiful stereo sound. Price £16-50, p.p. 25p.

• Also suitable for use with any power amplifier. Suggested types PA25, PA50, MPA12/3, MPA12/15.

SIMPLICITY TO MOUNT EASY TO USE
All units no soldering—just edge connectors and plugs

25 WATT & 50 WATT SILICON AMPLIFIERS

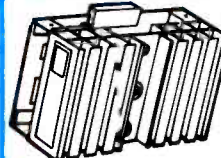

LOOK AT THE SPECIFICATIONS!

- At full power 0-3% distortion.
- At full power—1dB 11 c/s to 40 kc/s.
- Response—1dB 11 c/s to 100 kc/s.
- Rise time 2usec.
- Short circuit proof plus limiting cct.

FREE LEAFLET No. 25 on request

PA25 10 transistor all silicon differential input 400mV sensitivity. 25W Rms into 8 ohms. Supplied with edge connector harness size 5 in x 3 in x 2 in.
PA50 12 transistor version 50W Rms into 3 to 4 ohms. Size 5 in x 3 in x 4 in.
MU442. Power supply for one or two PA25 or one PA50.
PA25, £7-50. PA50, £9-50. MU442, £6. P.P. 20p each.

DESIGNED FOR QUALITY, PERFORMANCE AND PRICE
As specified for many "Practical Wireless" 1970 projects

Electronic Components & Test Gear Centre
356 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-402 5854

Electronic Organs, P.A. & Discotheque Centre
309 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 6963

Mail Orders, Special Bargain Shop, Industrial Sales
303 EDGWARE ROAD,
LONDON, W.2.
Tel: 01-723 1008/9

OPEN 9 a.m. to 6 p.m. MONDAY TO SATURDAY — 9 a.m. to 1 p.m. THURSDAYS — OPEN ALL DAY SATURDAY