

PRACTICAL

ELECTRONICS

FEBRUARY 1975

25p

Boat owners...
now's the time
to build our...

Electronic

MARINE SPEEDOMETER

Also in this issue...

- PROBABILITY ANOMALY DETECTOR
- AC/DC MILLIVOLTMETER

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN -PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio.
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

TOTAL BUILDING COSTS

£7-23 P.P. & INS. 44p
(Overseas P.P. £1-85p)
(+8% VAT 57p)

Components include:


- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 31" Loudspeaker ● Earpiece ● Mica Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 50p (free with parts)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9½in x 7in x 2½in approx. Parts price list and plans 40p (FREE with parts).

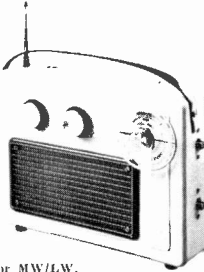TOTAL BUILDING COSTS **£6-95** P.P. & INS. 44p
(+8% VAT 55p) (OVERSEAS P. & P. £1-85)



NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9in x 5½in x 2½in approx. Parts price list and plans 20p (FREE with parts).

TOTAL BUILDING COSTS **£2-95** P.P. & INS. 30p
(+8% VAT 23p) (OVERSEAS P. & P. £1-25)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull Output. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£3-60** P.P. & INS. 30p
(+8% VAT 29p) (OVERSEAS P. & P. £1-25)

EV7 Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3" Loudspeaker. Parts price list and easy build plans 35p. Free with parts.


TOTAL BUILDING COSTS **£4-08** P.P. & INS. 31p
(+8% VAT 32p) (OVERSEAS P. & P. £1-85)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

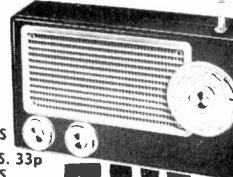
TOTAL BUILDING COSTS **£6-98** P.P. & INS. 47p
(+8% VAT 56p) (OVERSEAS P. & P. £1-85)



ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVE BANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

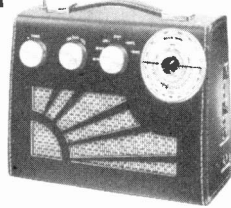TOTAL BUILDING COSTS **£8-50** P.P. & INS. 52p
(+8% VAT 68p) (OVERSEAS P. & P. £1-85)




POCKET FIVE

NOW WITH 3" LOUDSPEAKER

3 Tunable wavebands MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5½in x 1½in x 3½in approx. Plans and parts price list 20p (FREE with parts).

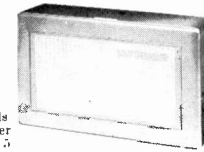Total Building Costs **£2-50** P.P. & Ins. 26p
(+8% VAT 20p) (Overseas P. & P. £1-25)




TRANSONA FIVE

NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 20p (FREE with parts).

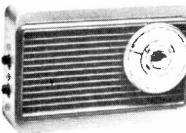
Total Building Costs **£2-75** P.P. & Ins. 26p
(+8% VAT 21p) (Overseas P. & P. £1-25)



TRANS EIGHT 8 TRANSISTORS AND 3 DIODES


6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW, and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker Parts. price list and plans 35p (FREE with parts).

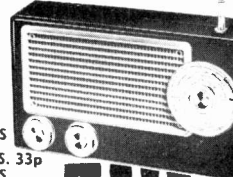TOTAL BUILDING COSTS **£4-48** P.P. & INS. 33p
(+8% VAT 36p) (OVERSEAS P. & P. £1-25)



ROAMER SIX CASE AND LOOKS AS TRANS EIGHT 6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Plans and parts price list 35p (FREE with parts).

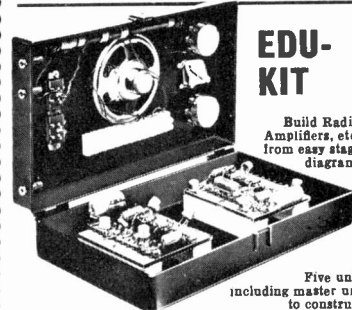TOTAL BUILDING COSTS **£3-98** P.P. & IN. 31p
(+8% VAT 32p) (OVERSEAS P. & P. £1-85)



Five units including master unit to construct.

Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine tone 3" moving coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three ½in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 40p (FREE with parts).

TOTAL BUILDING COSTS **£5-50** P.P. & INS. 39p
(+8% VAT 44p) (OVERSEAS P. & P. £1-85)

RADIO EXCHANGE LTD

*Gallers side entrance "Lavella" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52867 Reg. No. 788372

I enclose £..... for.....

Name

Address

PRACTICAL ELECTRONICS

VOLUME 11 No. 2 FEBRUARY 1975

CONSTRUCTIONAL PROJECTS

- MARINE SPEEDOMETER** *by C. Gammans*
"Tune" your boat with this simple instrument 120
- P.E. ORION—2** *by D. S. Gibbs & I. M. Shaw*
Construction, final testing and fault finding 124
- P.E. MINISONIC—4** *by G. D. Shaw*
Final wiring-up, alternative keyboards and optional extras 140
- AC/DC MILLIVOLTMETER** *by A. J. Woollard*
Op-amp design gives a useful and sensitive equipment 148
- PROBABILITY ANOMALY DETECTOR** *by A. Russell*
A novel unit for investigations into extra-sensory perception 152
- CAR CLOCK REPAIRS** *by D. L. Cooper*
A modification which puts new life into old car clocks 166

GENERAL FEATURES

- CEEFAX and ORACLE—1** *by J. Smith*
A look at the BBC and ITA systems for data transmission on TV signals 134
- INGENUITY UNLIMITED**
Patch Lead Sockets—In-circuit Power Detector—Making Printed Circuit Boards—
Voltage Controlled Amplifier—Schmitt Circuit Variations—Brake Light Detector 158

NEWS AND COMMENT

- EDITORIAL—A Healthy Market** 119
- SPACEWATCH** *by Frank W. Hyde*
Life Support Systems—Black Holes—Lunar Rocks 133
- BOOK REVIEWS**
Selected new books we have received 139
- NEWS BRIEFS**
Colour TV Certificate—Watch Displays—I.C. Price Cut 139
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 157
- PATENTS REVIEW**
Thought provoking ideas on file at the British Patent Office 165
- READOUT**
A selection of readers' letters 168

Our March issue will be published on Friday, February 14, 1975

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3.25, Overseas £4.10. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

ERSIN


Multicore

5 CORE SOLDER

for fast easy reliable soldering
EASY TO USE DISPENSERS AND REELS
IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser

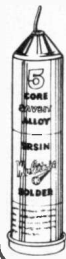

A coil of Ersin Multicore Solder in a dispenser 7 1/2 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy, 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-creed solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints




Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER

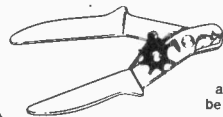

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B. 70p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,

Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP

Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 15p P&P. Prices and specifications subject to change without notice.

P. F. RALFE

10 CHAPEL ST. LONDON NW1

Phone 01-723 8753

MUFFIN INSTRUMENT FANS

Dimensions 4.5in x 4.5in x 1.5in. Very quiet running, precision fan specially designed for cooling electronic equipment, amplifiers, etc. For 110V, a.c. operation (practice is to run from split primary of mains transformer or unsuitable mains dropper). CC only 11 watts. List price over £10 each. Our price, in brand new condition, is £3.50.

MINIATURE SOLENOIDS

12-24V 140Ω. Coil size 1 1/2in x 1/2in x 1/2in. All brand new. Price 65p.

McMURDO 6-WAY EDGE CONNECTORS, PLUGS & SOCKETS
 C/W Covers. Brand new. Quantities are available at only 25p each.

DURATRAK VARIACS

Type 100L. 230V input. 0-230V a.c. output. 8 amps. Brand new minus control knobs. Price only £15, carriage £1.

AERIAL CHANGE-OVER RELAYS of current manufacture designed especially for mobile equipments, coil voltage 12V, frequency up to 250MHz at 50 watts. Small size only, 2in x 1/2in. Offered brand new, boxed. Price £1-50, Inc. P. & P.

TV WOBBLATOR Type '210'

Technical characteristics
 Frequency: 5 to 220Mc/s in one range.
 Accuracy: That of the marker generator (e.g. METRIX 936).

Output: Not less than 100mV attenuable in steps of 10 down to 10μV.
 Sweep width: 1-2-5-10-20Mc/s.
 Linearity: 10% at sweep width 10Mc/s.
 Amplitude modulation: Less than 10% at sweep width 10Mc/s.
 Power supply: 110-130-220V, 50-60c/s. 130V may be replaced by 160V, 220V may be replaced by 240V on demand.

Power Input: 35VA approx.
 Tubes used: 2 x EC81; 1 x 6J6; 1 x 6X4.
 Weight: 20lb 8oz (9.300kg).
 Dimensions: 20 x 11 1/2 x 7 1/2in. (510 x 195 x 195mm) overall. Price £48-50 inc. VAT.

Large selection of RF PLUGS AND SOCKETS


Available ex-stock: BNC plugs 50 30p; BNC sockets 50 25p; N. type plug 50 50p; Burndept plugs 40p; Burndept sockets 20p; All plugs and sockets are brand new. Please add appropriate amount for postage.

AVO VALVE TESTERS

Brief-case type 160. Full working condition throughout, £65.

PLEASE ADD 8% VAT TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH.

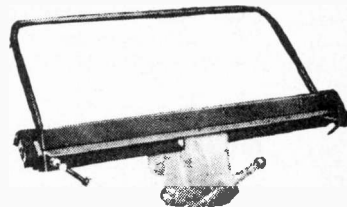PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

- No. 1. Capacity 18 gauge mild steel x 36in. wide ... £21 carr. free
- No. 2. Capacity 18 gauge mild steel x 24in. wide ... £15 carr. free
- No. 3. Capacity 16 gauge mild steel x 18in. wide ... £15 carr. free

Also new bench models. Capacities 36in. x 18 gauge £40. 24in. x 16 gauge £38. Carriage free. Add 8% VAT to total price of machine. End folding attachments for radio chassis. Tray and Box making. Steel Angle 36in. model, 40p per. ft. Other models 30p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper Boze St., Heckmondwike, Yorks. Telephone 403997

BALMAHA ELECTRONICS LIMITED

Balmaha House, 75/77 Sandy Lane, Melton Mowbray, Leics. LE13 0EN

ELECTRONIC COMPONENT STOCKISTS AND DISTRIBUTORS

I/Cs '74' series TTL. Full range.
 LINEAR I/Cs: 741, 709, 740, LM305, 723, 309K, 555V, etc.
 TRANSISTORS: BC107, 108, 109 Family ZTX, 2N3055 (50p), 2N2613, 2N2904, 2N3866, BCY34, BCY70, BC204 and many others.
 DIODES: General purpose and zeners 400mW to 1-SW, 50V-800V. Thyristor firing circuits in module form.
 Electronic plug-in timers. 8 pin and 11 pin
 Crelde relays and bases (PVE-TMC) 2 c/o and 4 c/o. B and R relays 2 c/o and 3 c/o all voltages.
 CERMET RECTILINEAR POTENTIOMETERS 8-75W and 1W.
 Other items to clear: new, not normally stocked. DEAC RE-CHARGEABLE BATTERIES: Capacity, 4ah/10hr rate. Physical

size as HP2 £1-50 each. KEYSWITCH RELAYS: Plug-in types KMK2P, KMK3P 110V a.c. 230V a.c. 5A contacts £0-90 each. 3 pole sockets for relays £0-10 each. DECIMAL THUMBWHEEL SWITCHES: 10-position, showing 0-9 by illuminated rotors. Only decimal output available (1 output per pos.) £0-80.
 End pieces for panel mounting of switches £0-40.
 VEROBOARD: 0-1in. 0-15in and 0-2in. Pitch 0-2in in regular size of 3 1/2in x 3 1/2in. Cards of 10, £0-80. PVE-TMC RELAYS: Crelde type, direct P.C. mount. 0-1in grid matrix. Suitable for 12V, 24V or 48V. 2 pole and single pole £0-50 each.
 MAGNETIC DEVICES RELAYS: Open type 1 pole and 2 pole c/o. 110V d.c. £0-50.

MANY OTHER ITEMS

Phone: Melton Mowbray (0664) 3669

SINCLAIR DM2 DIGITAL MULTIMETER



Will measure AC and DC volts, AC and DC current and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply.

RANGES:
DC VOLTS: 1v, 10v, 100v, 1000v.
AC VOLTS: 1v, 10v, 100v, 1000v.
DC CURRENT: 1mA, 10mA, 100mA, 1000mA.
AC CURRENT: 1mA, 10mA, 100mA, 1000mA.
RESISTANCE: 1k, 10k, 100k, 1000k.
OUR PRICE £59.95 P & P 50p

SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedance 52 Ω Indicator 100uA DC full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.
OUR PRICE £4.25 P & P 30p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25. HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-3000usec. Free running 20-200kHz in nine ranges. Calibrator pips: 220 x 360 x 430mm. 115-230V AC.
OUR PRICE £43.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2usec to 100 milli-sec. Free running time base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.
OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip. Oscillator. Absorption Wave Meter and Oscillating Detector. Frequency range 400Hz-280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.
OUR PRICE £17.50 P & P 30p

TRANSISTORISED I.C.R. A.C. BR/8 MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm + 1% Inductance: 6 ranges: 1 microhenry-111 henries + 2%. Capacity: 6 ranges: 10pF-1110 mfd + 2%. Turns Ratio: 6 ranges: 1:1-1000:1-11100:1. Bridge Voltage at 1.000cps. Operated from 9-volt battery. 100 microamp meter indication. Size 7 1/2 x 5 x 2".
OUR PRICE £25.00 P & P 30p

TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable RF attenuator audio output. X1el socket for calibration 220-240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.
OUR PRICE £17.50 P & P 50p

TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to 200kHz on 4 bands. Square 20 cps to 20 kHz. Output impedance 5000 Ohms. 220/240V AC operation. Supplied brand new guaranteed, with instruction manual and leads.
OUR PRICE £24.95 P & P 50p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.
OUR PRICE £37.50 P & P 50p

WALKIE TALKIES SKYFON CV7

Super low noise transmitter receivers. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna.
OUR PRICE £28.95 P & P 50p
NOT LICENSABLE IN THE UK

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19: 220,000Hz Sine Wave 19-100,000 Hz Square Wave. Output Sine or Square wave 10v. P to 220, 240V. A.C.
OUR PRICE £19.95 P & P 50p

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Sine hole fixing. 3/4" diameter shafts. Bulk quantities available.
25 WATT 1/25 50/100/500/1000 2500 ohms £1.15 P & P 10p
50 WATT 10/50/100/250/500/1500 5000 ohms £1.62 P & P 10p
100 WATT 1 1/5 10/25/50/250/500 2500 ohms £2.34 P & P 15p

SPECIAL PURCHASE LIMITED QUANTITY!

Tannoy 12" DR/8 Bass Speakers 8 ohms. 30 watt. Heavy duty, ideal for Hi-Fi P.A. Group.
OUR PRICE £12.50 P & P 50p

AUDIOTRONIC LE-102A INTERCOM

Beautifully made and finished in two-tone ivory buff, the LE-102A is useful in the home, office or shop alarm. Wall or desk mounting. 57mm speaker. mic gives clear 2 way communication with on/off and volume control on master unit. Operates on 9V batt. Approx. 60ft lead.
OUR PRICE £3.95 P & P 30p

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size 190 x 136 x 98mm.
OUR PRICE £19.95 P & P 50p

TRITON 4318 PORTABLE 8 TRACK CARTRIDGE PLAYER WITH MW/LW RADIO

Will play 8 track stereo cartridge manually. Channel selector switch. Covers medium and long wave bands. Volume and tone controls. Earphone socket. Battery. Mains operation.
OUR PRICE £11.95 P & P 50p

EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverberation control. Beautiful cabinet. 184 x 77 x 108mm.
OUR PRICE £7.50 P & P 30p

LH02S STEREO HEADPHONES

Light weight headphones with padded ear pieces. 4/16 ohms 20-20,000Hz. Complete with 6' lead and plug.
OUR PRICE £1.97 P & P 30p

DH02S STEREO HEADPHONES

Wonderful value and excellent performance. Comfortable adjustable head band. Impedance 8 ohms. 20-12,000Hz. Complete with lead and plug.
OUR PRICE £2.25 P & P 30p

TE1035 Stereo HEADPHONES

Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and ear jack.
OUR PRICE £2.60 P & P 30p

SDH8V MONO/STEREO HEADPHONES

Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Impedance 10H. Coiled lead and jack plug.
OUR PRICE £4.97 P & P 30p

BH001 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching. Complete with 10ft. Headphone impedance 16 ohms. Microphone impedance 200 ohms.
OUR PRICE £5.95 P & P 30p

HANIMEX HRC 3075 CASSETTE RADIO

Covers Medium and FM wave bands. Slider volume and tone controls. Battery Mains operation. Will record direct from radio or through built in condenser microphone. Complete with batteries, earphone, and cassette.
OUR PRICE £24.30 P & P 50p

SPECIAL OFFER! CONVERT YOUR STEREO SYSTEM TO 4D SOUND FOR UNDER £16

Exclusive offer of GOODWIN 4 CHANNEL CONVERTER and a pair of AD15 10 watt 8 ohm bookshelf speakers enables you to add 4D sound to your existing system. Complete with simple connection details. Normal retail value £25.50.
OUR PRICE £15.80 P & P £1
GOODWIN CONVERTER available separately £3.95 P & P 50p

SPECIAL BARGAIN !! STEREO SOUND SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size: 368 x 229 x 190mm. 8 ohms. 8 watts RMS. 16 watts peak. Complete with Din lead.
OUR PRICE £12.95 PAIR P & P 50p

FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Amps output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.
OUR PRICE £8.95 P & P 20p
Stereo Multiplex Adaptor £5.95 extra

Model A1018

6 transistor high quality unit. 3 IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.
OUR PRICE £13.50 P & P 30p
Stereo multiplex adapter £5.95 extra.

ELECTRONIC CALCULATORS

We carry a tremendous range of both pocket and desk calculators from as little as £8.90. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

MINIATURE ORGAN MUSIC MASTER AM100

Spanning nearly two octaves, including semi-tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket.
OUR PRICE £7.95 P & P 50p

BINATONE DIGITAL CLOCK

Attractive ivory case. Large clear numbers for hours, minutes and seconds. A.C. 240V operation. Size approx. 6 1/2 x 3 1/2 inches.
OUR PRICE £4.50 P & P 50p

SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER

complete with printed circuit mounting board.
OUR PRICE £1.50 P & P 15p

SINCLAIR Project 80 Modules

240 Power Amp £5.95 P & P 15p
A2 Pre-amplifier £7.45 P & P 15p
Stereo 80 Pre. Amp £13.95 P & P 15p
Active Filter Unit £7.45 P & P 15p
FM Tuner £13.95 P & P 15p
Stereo Decoder £8.95 P & P 15p
P25 Power Supply £5.95 P & P 30p
P26 Power Supply £8.95 P & P 30p
P28 Power Supply £8.45 P & P 30p
Transformer for P28 £4.05 P & P 30p
IC20 Stereo Amp Kit £7.95 P & P 15p
P20 Power Supply £5.45 P & P 30p
SINCLAIR Project 80 Packages
2x240 Stereo 80 P25 £28.60
2x240 Stereo 80 P26 £31.30
2x260 Stereo 80 P28 £33.55 each

TE1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facility for stereo headphones switching. Two gain controls, speakers on-off slide switch, stereo headphone socket.
OUR PRICE £2.25 P & P 15p

AUDIOTRONIC LOW NOISE CASSETTES

TYPE	5	10	25
C60	£1.57	£3.90	£7.08
C90	£2.24	£4.25	£10.00
C120	£2.73	£5.17	£12.24

P & P 3p each. 10 and over Post Free

MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 4mV 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k.
OUR PRICE £8.97 P & P 20p

AUDIOTRONIC AHA101 Stereo Headphone Amplifier

All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates on 9V D.C. battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.
OUR PRICE £8.50 P & P 30p

HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT
11302 Transistor Road, [42 & 34 Lisle Street, 152, Fleet Street, 311 Edgware Road, CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Packing 15p per kit.

AF20 Mono amplifier	£5.61
AF25 Mixer	£3.29
AF30 Mono pre-amplifier	£3.20
AF35 Emitter amplifier	£2.42
AF80 0.9V mic. amplifier	£4.86
AF305 Intercom	£7.67
AF310 2 Mono Amplifier	£7.55
M160 Multi vibrator	£2.18
M1302 Transistor tester	£8.33
M191 VU Meter	£5.37
M192 Stereo balance meter	£5.93
LF380 Quadraphonic device	£6.52
AT5 Automatic light control	£7.75
AT30 Photo cell switch unit	£6.68
AT50 400W track light	£5.18
AT52 200W track light	£5.75
AT60 1 channel light control	£10.82
AT65 3 channel light control	£16.52
GU330 Tremolo unit	£3.87
HF100 Edge detector	£3.87
HF65 FM transmitter	£3.21
HF75 FM receiver	£3.66
HF300 FM tuner	£16.32
HF325 Deluxe FM tuner	£26.33
HF330 Decoder (HF310/325)	£10.55
GP310 Stereo pre-amplifier	£22.98
GP2 Active board	£10.02
GP304 Circuit board	£5.33
HF380 lw/hf aerial amplifier	£6.02
HF395 broadband aerial supply	£2.10
NT10 Stabilised power supply	£6.27
NT300 Stabilised p. supply	£13.16
NT310 Power Supply 240 V AC	£5.54
NT305 Voltage converter	£5.64
NT315 Power supply 240V AC	£10.06
to 4,5/15V DC, 500mA	£12.06

Amateur Electronics by Josty-Kit

the professional book for the amateur covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.
OUR PRICE £3.30 (No VAT) P & P 25p plus VAT

AE1 100mW output stage	£1.55
AE2 Pre-amplifier	£1.32
AE3 Diode receiver	£2.05
AE4 Flasher	£1.26
AE5 Astable multi-vibrator	£1.10
AE6 Monostable multi-vibrator	£1.11
AE7 RC generator	£1.08
AE8 Bass filter	£1.05
AE9 Treble filter	£1.05
AE10 OCIR filter	£1.05

Also see previous page
ALL PRICES EXCLUDE VAT

SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR
3 LISLE ST., 311 EDGWARE RD., & 152 FLEET
ST., BRANCHES or order by post.

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.



CLEAR PLASTIC MODEL S0640

Size: 85 x 64mm

50uA	£3.90		
100uA	£3.85		
200uA	£3.80		
500uA	£3.75		
50.0-500uA	£3.85		
100.0-1000uA	£3.80		
1mA	£3.75		
5mA	£3.75		
10mA	£3.75		
50mA	£3.75	10V DC	£3.75
100mA	£3.75	20V DC	£3.75
500mA	£3.75	50V DC	£3.75
1A DC	£3.75	300V DC	£3.75
5A DC	£3.75	15V AC	£3.85
10A DC	£3.75	300V AC	£3.85
5V DC	£3.75	VU Meter	£4.00



*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL S0830

Size: 110 x 83mm

50uA	£4.40		
100uA	£4.35		
200uA	£4.30		
500uA	£4.25		
50.0-500uA	£4.35		
100.0-1000uA	£4.30		
1mA	£4.20		
5mA	£4.20		
10mA	£4.20		
50mA	£4.20	10V DC	£4.20
100mA	£4.20	20V DC	£4.20
500mA	£4.20	50V DC	£4.20
1A DC	£4.20	300V DC	£4.20
5A DC	£4.20	15V AC	£4.30
10A DC	£4.20	300V AC	£4.30
5V DC	£4.20	VU Meter	£4.50



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£4.05		
100uA	£3.95		
200uA	£3.90		
500uA	£3.85		
50.0-500uA	£3.95		
100.0-1000uA	£3.90		
500.0-5000uA	£3.80		
1mA	£3.80		
0-1mA	£3.80		
5mA	£3.80		
10mA	£3.80	300V DC	£3.80
50mA	£3.80	15V AC	£3.80
100mA	£3.80	50V AC	£3.90
500mA	£3.80	150V AC	£3.90
1A DC	£3.80	300V AC	£3.90
5A DC	£3.80	500V AC	£4.00
10A DC	£3.80	S Meter 1mA	£3.90
15A DC	£3.80	VU Meter	£4.20
20A DC	£3.80	1A AC	£3.80
30A DC	£3.80	30A AC	£3.80
50A DC	£4.15	10A AC	£3.80
5V DC	£3.80	20A AC	£3.80
10V DC	£3.80	30A AC	£3.80
15V DC	£3.80	50mA AC	£3.80
20V DC	£3.80	100mA AC	£3.80
50V DC	£3.80	200mA AC	£3.80
150V DC	£3.80	500mA AC	£3.80



CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.70		
100uA	£4.60		
500uA	£4.50		
50.0-500uA	£4.60		
100.0-1000uA	£4.55		
1mA	£4.40		
1A DC	£4.40		
5A DC	£4.40		
20V DC	£4.40	150V AC	£4.55
50V DC	£4.40	300V AC	£4.55
300V DC	£4.40	VU Meter	£5.00



CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3.30		
100uA	£3.25		
200uA	£3.20		
500uA	£3.10		
50.0-500uA	£3.25		
100.0-1000uA	£3.20		
500.0-5000uA	£3.05		
1mA	£3.05		
5mA	£3.05		
10mA	£3.05		
50mA	£3.05		
100mA	£3.05		
500mA	£3.05		
1A DC	£3.05		
5A DC	£3.05		
10V DC	£3.05		
20V DC	£3.05		
50V DC	£3.05		
300V DC	£3.05		
15V AC	£3.15		
30V AC	£3.15		
50V AC	£3.15		
100V AC	£3.15		
300V AC	£3.15		
500V AC	£3.15		
1mA	£3.05	300V AC	£3.15
5mA	£3.05	S Meter 1mA	£3.05
10mA	£3.05	VU Meter	£3.50
50mA	£3.05	1A AC	£3.05
100mA	£3.05	5A AC	£3.05
500mA	£3.05	10A AC	£3.05
1A DC	£3.05	20A AC	£3.05
5A DC	£3.05	30A AC	£3.05
10V DC	£3.05		
20V DC	£3.05		
50V DC	£3.05		
300V DC	£3.05		
15V AC	£3.15		
30V AC	£3.15		
50V AC	£3.15		
100V AC	£3.15		
300V AC	£3.15		
500V AC	£3.15		



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.60		
100uA	£4.55		
500uA	£4.30		
50.0-500uA	£4.65		
100.0-1000uA	£4.50		
1mA	£4.30		
1A DC	£4.30		
5A DC	£4.30		
20V DC	£4.30		
50V DC	£4.30		
300V DC	£4.30		
300V AC	£4.40		
VU Meter	£4.80		



EGGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.25		
100uA	£4.20		
200uA	£4.15		
500uA	£4.00		
50.0-500uA	£4.20		
100.0-1000uA	£4.15		
1mA	£3.95		
300V AC	£4.05		
VU Meter	£4.40		



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.




50uA	£8.70		
100uA	£8.10		
50.0-500uA	£8.10		
1mA	£7.80		
1.0-1mA	£7.80		
1A DC	£7.80		
5A DC	£7.80		
5V DC	£7.80		
10V DC	£7.80		
15V DC	£7.80		
20V DC	£7.80		
50V DC	£7.80		
300V DC	£7.80		
15V AC	£7.80		
30V AC	£7.80		
50V AC	£7.80		
100V AC	£7.80		
300V AC	£7.80		
500V AC	£7.80		
1mA	£7.80	20V DC	£7.80
5mA	£7.80	50V DC	£7.80
10mA	£7.80	300V DC	£7.80
50mA	£7.80	15V AC	£7.80
100mA	£7.80	5V/15V DC	£7.80
500mA	£7.80	1/5A DC	£7.80
1A DC	£7.80		
5A DC	£7.80		
10V DC	£7.80		
50V DC	£7.80		
300V DC	£7.80		
15V AC	£7.80		
30V AC	£7.80		
50V AC	£7.80		
100V AC	£7.80		
300V AC	£7.80		
500V AC	£7.80		

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£6.80		
100uA	£5.55		
200uA	£6.50		
500uA	£5.40		
50.0-500uA	£5.55		
100.0-1000uA	£5.80		
500.0-5000uA	£5.35		
1mA	£5.35		
1.0-1mA	£5.35		
5mA	£5.35		
10mA	£5.35		
50mA	£5.35		
100mA	£5.35		
500mA	£5.35		
1A DC	£5.35		
5A DC	£5.35		
15A DC	£5.35		
30A DC	£5.35		
10V DC	£5.35		
20V DC	£5.35		
50V DC	£5.35		
150V DC	£5.35		
300V DC	£5.40		
15V AC	£5.45		
30V AC	£5.45		
50V AC	£5.45		
100V AC	£5.45		
300V AC	£5.45		
500V AC	£5.45		
1mA	£5.35	S Meter 1mA	£5.35
5mA	£5.35	VU Meter	£5.70
10mA	£5.35	1A AC	£5.35
50mA	£5.35	5A AC	£5.35
100mA	£5.35	10A AC	£5.35
500mA	£5.35	20A AC	£5.35
1A DC	£5.35	30A AC	£5.35
5A DC	£5.35		
15A DC	£5.35		
30A DC	£5.35		
10V DC	£5.35		
20V DC	£5.35		
50V DC	£5.35		
150V DC	£5.35		
300V DC	£5.35		
15V AC	£5.45		
30V AC	£5.45		
50V AC	£5.45		
100V AC	£5.45		
300V AC	£5.45		
500V AC	£5.45		

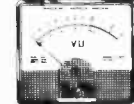

CLEAR PLASTIC MODEL S0460

Size: 59 x 46mm

50uA	£3.60		
100uA	£3.55		
200uA	£3.50		
500uA	£3.45		
50.0-500uA	£3.55		
100.0-1000uA	£3.50		
1mA	£3.40		
5mA	£3.40		
10mA	£3.40		
50mA	£3.40		
100mA	£3.40		
500mA	£3.40		
1A DC	£3.40		
5A DC	£3.40		
10A DC	£3.40		
5V DC	£3.40		
10V DC	£3.40		
15V DC	£3.40		
30V DC	£3.40		
50V DC	£3.40		
300V DC	£3.40		
15V AC	£3.40		
30V AC	£3.40		
50V AC	£3.40		
100V AC	£3.40		
300V AC	£3.40		
500V AC	£3.40		
1mA	£3.40	300V AC	£3.40
5mA	£3.40	S Meter 1mA	£2.85
10mA	£3.40	VU Meter	£3.30
50mA	£3.40	1A AC	£3.40
100mA	£3.40	5A AC	£3.40
500mA	£3.40	10A AC	£3.40
1A DC	£3.40	20A AC	£3.40
5A DC	£3.40	30A AC	£3.40
10A DC	£3.40		
5V DC	£3.40		
10V DC	£3.40		
15V DC	£3.40		
30V DC	£3.40		
50V DC	£3.40		
300V DC	£3.40		
15V AC	£3.40		
30V AC	£3.40		
50V AC	£3.40		
100V AC	£3.40		
300V AC	£3.40		
500V AC	£3.40		



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.80		
100uA	£3.60		
500uA	£3.60		
50.0-500uA	£3.60		
100.0-1000uA	£3.45		
1mA	£3.40		
5mA	£3.40		
10mA	£3.40		
50mA	£3.40		
100mA	£3.40		
500mA	£3.40		
1A DC	£3.40		
5A DC	£3.40		
10V DC	£3.40		
20V DC	£3.40		
50V DC	£3.40		
300V DC	£3.40		

RST

VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
 Express postage 5p for first transistor, 1p thereafter, over ten post free. INTEGRATED CIRCUITS 6p + 1p each added

1N21	5p	FAZ11	1-15	BY213	5p	0AZ205	0-45	Z8170	0-10
1N23	0-85	AFZ12	2-00	BY210	0-45	0AZ206	0-45	Z8271	0-18
1N25	0-85	ASY26	0-25	BY211	0-40	0AZ207	0-45	ZT21	0-25
1N263	0-85	AYZ27	0-30	BY212	0-40	0AZ208	0-40	ZT43	0-25
1N266	0-85	ASY28	0-25	BY213	0-35	0AZ209	0-40	ZTX107	0-12
1N265	0-16	ASY29	0-30	BY215	0-35	0AZ210	0-40	ZTX108	0-10
1N726A	0-20	ASY30	0-25	BY216	0-60	0AZ211	0-40	ZTX300	0-14
1N914	0-06	AY510	0-40	BZ788	0-10	0AZ222	0-45	ZTX304	0-84
1N4007	0-18	AY511	0-20	C111	0-55	0AZ224	0-45	ZTX503	0-18
18131	0-25	AY553	0-20	CR81/03	0-30	0AZ241	0-25	ZTX531	0-25
18202	0-23	AY562	0-25	CR81/40	0-35	0AZ242	0-15		
20271	0-40	AY566	0-23	CS4B	1-30	0AZ244	0-25		
20281	0-22	AY568	0-25	CS10B	0-60	0AZ246	0-15		
20414	0-30	AY569	0-25	DD000	0-15	0AZ290	0-28		
20417	0-35	AY570	0-25	DD003	0-15	OC16	1-00	7400	0-30
2N404	0-40	AYU10	1-00	DD006	0-25	OC16T	1-00	7401	0-30
2N697	0-15	BC107	0-12	DD007	0-40	OC19	0-50	7402	0-20
2N698	0-30	BC108	0-12	DD008	0-38	OC20	2-00	7403	0-20
2N706	0-10	BC109	0-12	GD3	0-38	OC21	1-25	7404	0-20
2N706A	0-12	BC110	0-20	GD4	1-10	OC23	1-25	7405	0-20
2N708	0-15	BC111	0-20	GD5	0-28	OC24	1-10	7406	0-20
2N709	0-40	BC116	0-20	GD6	0-25	OC25	0-40	7407	0-40
2N1091	0-55	BC116A	0-23	GD12	1-10	OC26	0-40	7408	0-25
2N1131	0-25	BC118	0-20	GET102	0-50	OC28	0-70	7409	0-33
2N1132	0-25	BC121	0-20	GET103	0-40	OC29	0-65	7410	0-28
2N1302	0-18	BC122	0-20	GET113	0-35	OC30	0-40	7411	0-28
2N1303	0-18	BC126	0-65	GET114	0-30	OC35	0-55	7412	0-28
2N1304	0-25	BC140	0-55	GET115	0-75	OC36	0-65	7413	0-20
2N1306	0-25	BC141	0-12	GET120	0-50	OC42	0-40	7420	0-20
2N1307	0-25	BC148	0-10	GET149	0-15	OC43	0-70	7422	0-28
2N1308	0-28	BC149	0-15	GET875	0-40	OC44	0-18	7423	0-40
2N1317	0-25	BC157	0-14	GET880	0-55	OC44M	0-17	7423	0-40
2N1318	0-25	BC158	0-12	GET881	0-55	OC45	0-18	7425	0-27
2N1319	0-25	BC160	0-63	GET882	0-35	OC45M	0-18	7427	0-27
2N2218	0-28	BC169	0-14	GET885	0-40	OC46	0-27	7428	0-20
2N2219	0-25	BCY31	0-45	EX344	0-05	OC57	0-60	7432	0-37
2N2369A	0-16	BCY32	0-20	EX451/1	0-45	OC58	0-60	7433	0-43
2N2444	1-50	BCY34	0-45	GJ3M	0-50	OC60	0-50	7437	0-43
2N2513	0-25	BCY35	0-55	GJ4M	0-50	OC70	0-18	7440	0-20
2N2546	0-60	BCY38	0-55	GJ5M	0-25	OC71	0-15	7441A	0-25
2N2904	0-20	BCY39	1-00	GJ7M	0-50	OC72	0-25	7442	0-85
2N2904A	0-25	BCY40	0-80	GJ8M	0-50	OC73	0-20	7450	0-20
2N2906	0-20	BCY42	0-30	H100A	0-20	OC74	0-30	7451	0-20
2N2907	0-23	BCY70	0-15	MA1100	0-20	OC75	0-30	7453	0-30
2N2924	0-18	BCY71	0-20	MA1101	0-25	OC76	0-30	7454	0-20
2N2925	0-15	BCZ10	0-60	MA1120	0-20	OC77	0-55	7460	0-20
2N2926	0-10	BCZ11	0-65	MA1721	0-25	OC78	0-25	7470	0-33
2N3054	0-50	BD121	1-00	MJ2950	0-85	OC79	0-50	7472	0-38
2N3055	0-60	BD123	1-00	MJ2955	1-10	OC81	0-28	7473	0-44
2N3702	0-11	BDY10	0-80	MF3055	0-75	OC81D	0-28	7474	0-48
2N3705	0-15	BDY11	1-45	MJ340	0-50	OC81M	0-20	7475	0-59
2N3706	0-11	BF115	0-22	MPF102	0-40	OC81DM	0-18	7476	0-45
2N3707	0-13	BF117	0-50	MPF103	0-38	OC81Z	0-45	7480	0-20
2N3709	0-10	BF167	0-25	MPF104	0-35	OC82	0-28	7482	0-87
2N3710	0-11	BF173	0-28	MPF105	0-45	OC82D	0-25	7483	1-20
2N3711	0-11	BF181	0-35	NKT128	0-48	OC83	0-25	7484	1-00
2N3819	0-20	BF185	0-22	NKT129	0-30	OC84	0-30	7486	0-40
2N4289	0-20	BF194	0-22	NKT211	0-25	OC114	0-38	7490	0-75
2N6027	0-23	BF195	0-13	NKT213	0-25	OC122	1-00	7491A	1-10
2N6088	0-23	BF196	0-15	NKT214	0-24	OC123	1-10	7492	0-75
2B301	0-60	BF197	0-15	NKT216	0-40	OC139	0-40	7493	0-75
2B304	1-15	BF198	0-15	NKT217	0-45	OC140	0-55	7494	0-85
2B301	0-75	BF199	0-25	NKT218	1-18	OC141	0-80	7495	0-85
2B303	1-00	BF200	0-20	NKT219	0-38	OC169	0-20	7496	1-00
AA129	0-30	BFX12	0-20	NKT222	0-30	OC170	0-25	7497	4-82
AAZ12	0-75	BFX13	0-25	NKT224	0-25	OC171	0-30	74100	2-16
AAZ13	0-10	BFX20	0-28	NKT225	0-25	OC200	0-55	74107	0-81
AC107	0-85	BFX29	0-28	NKT227	0-20	OC201	0-90	74110	0-87
AC126	0-25	BFX32	0-28	NKT271	0-20	OC202	0-90	74111	0-86
AC127	0-25	BFX63	0-60	NKT272	0-20	OC203	0-65	74118	1-00
AC128	0-30	BFX84	0-25	NKT273	0-20	OC204	0-65	74119	1-02
AC187	0-20	BFX85	0-28	NKT274	0-20	OC205	1-00	74121	0-97
AC188	0-20	BFX86	0-25	NKT275	0-25	OC206	1-10	74122	0-80
AOY17	0-35	BFX87	0-25	NKT277	0-20	OC207	1-00	74123	1-44
AOY18	0-27	BFX88	0-25	NKT278	0-25	OC460	0-20	74141	1-00
AOY19	0-27	BFY10	1-00	NKT301	0-85	OC470	0-30	74145	1-44
AOY20	0-22	BFY11	0-50	NKT304	0-75	OC771	1-00	74150	2-20
AOY21	0-22	BFY17	0-40	NKT403	0-70	ORP12	0-55	74151	1-15
AOY22	0-18	BFY18	0-45	NKT404	0-80	ORP60	0-45	74164	2-20
AOY27	0-25	BFY19	0-55	NKT678	0-30	ORP61	0-48	74165	1-15
AOY28	0-25	BFY24	0-45	NKT713	0-30	ORP61	0-48	74166	1-15
AOY39	0-85	BFY44	1-00	NKT773	0-25	OX68	0-20	74157	1-09
AOY40	0-22	BFY50	0-20	NKT777	0-38	OX631	0-45	74159	2-88
AOY41	0-22	BFY51	0-20	OR78B	0-38	OX635	0-65	74170	1-80
AOY44	0-22	BFY52	0-20	OA5	0-80	OX640	0-75	74171	1-80
AD140	0-50	BFY53	0-17	OA6	0-12	OX641	0-75	74172	1-29
AD149	0-60	BFY64	0-45	OA7	0-08	OX642	0-80	74173	1-44
AD161	0-39	BFY90	0-75	OA70	0-10	OX644	0-85	74176	2-20
AF106	0-30	BXK27	0-60	OA71	0-20	OX845	0-85	74190	2-20
AF114	0-25	BXK60	0-93	OA73	0-15	TIC44	0-29	74191	2-20
AF115	0-25	BXK76	0-18	OA74	0-18	V15/30P	0-75	74192	2-20
AF116	0-25	BXK78	0-17	OA79	0-10	V30/201P	0-75	74193	2-20
AF117	0-20	BXK81	0-20	OA81	0-10	V60/201P	0-50	74194	1-72
AF118	0-20	BXK82	0-20	OA85	0-15	XA101	0-10	74195	1-44
AF119	0-20	BXK83	0-20	OA86	0-15	XA102	0-18	74196	1-88
AF124	0-30	BT102/50R	0-12	OA90	0-07	XA151	0-15	74197	1-88
AF126	0-30	BT102/50R	0-12	OA91	0-07	XA152	0-15	74198	1-88
AF126	0-30	BTY42	0-92	OA92	0-07	XA181	0-25	74199	2-88
AF127	0-30	BTY79/100R	0-75	OA210	0-20	XB101	0-43		
AF139	0-33	BTY79/400R	0-75	OA211	0-25	XB102	0-30		
AF178	0-65	BY100	1-10	OAZ200	0-50	XB103	0-35		
AF179	0-65	BY101	0-15	OAZ201	0-45	XB108	0-35		
AF180	0-65	BY126	0-14	OAZ202	0-45	XB113	0-30		
AF181	0-60	BY127	0-15	OAZ203	0-45	XB121	0-43		
AF186	0-40	BY182	0-85	OAZ204	0-45				
AFY19	1-13	BY182	0-85	OAZ204	0-45				

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
 Valves, Tubes and Transistors Closed Sat. 1 p.m.-3 p.m.
 Terms C.V.O. only. Tel. 01-677 2424-7.
 All orders subject to V.A.T. at 8% rate. This must be added to the total order including postage.

Prices correct when going to press.

12in LONG PERSISTENCE CRT. Full spec. Price £8.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £8.25 P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBLULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 TV IF alignment, meters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £6.75 P. & P. 25p. (Not cased, not calibrated.)

20Hz to 200kHz WB. SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8.85 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of ELECTRONIC GOODIES for £1.50. Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 1 off 4 pole, 2 way, etc.), 50p, P. & P. 20p.

P.C.B. PACKS. S & D. Quantity 2 sq. ft.—no tiny pieces. 50p, P. & P. 20p.

CAPACITOR PACK—50 brand new components, only 50p, P. & P. 20p.

TRIMMER PACK. 2 twin 50/200pF ceramic; 2 twin 10/80pF ceramic; 2 min strip with 4 preset 50/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 10p.

MAPLIN ELECTRONIC SUPPLIES



Get your 1975 CATALOGUE!

Includes dozens of useful and interesting circuits you can build: data: hundreds of pictures: transistor equivalents list and hundreds of new lines. Packed with information. ONLY 35p.

SUPERSONIC SAME-DAY-SERVICE-MEANS QUALITY COMPONENTS-FAST!

● RESISTORS

CARBON FILM
 1/4W 1Ω to 1MΩ: 5%, 1MΩ to 10MΩ: 10% E12
 1/2W 1Ω to 10Ω: 5%, 1MΩ to 10MΩ: 10% E24
 1W 1Ω to 910kΩ: 5% E12 and E24 1p each.

METAL OXIDE WIREWOUND
 1/2W 10Ω to 1MΩ: 2% E12 and E24 4p each.
 3W 0.22Ω, 0.27Ω, 0.33Ω, 0.47Ω: 10% 7p each.
 1Ω to 270Ω: 5% E12 13p each.
 Other ranges stocked. See our catalogue for details.
 E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
 E24: 11, 13, 15, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

● POTENTIOMETERS

Rotary miniature carbon track 1in spindle. Values available 50kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ.
 Log. Single-gang 15p. Lin. Single-gang (+ 1kΩ) 16p.
 Log. or Lin. Single-gang with switch 33p.
 Log. or Lin. Dual-gang without switch 45p.
 Slider 60mm track. Metal-cased: overall length 85-15mm (knob 7p extra).
 Log. or Lin. Single-gang 1kΩ, 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 36p each.
 Log. or Lin. Dual-gang 1kΩ, 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ 45p each.
 Presets: 0.1W vertical or horizontal.
 100Ω, 220Ω, 470Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 10kΩ, 22kΩ, 47kΩ, 100kΩ, 220kΩ, 470kΩ, 1MΩ 7p each.

● CAPACITORS

Sub-miniature axial lead electrolytic

Mfd	V	Price	Mfd	V	Price	Mfd	V	Price
1	83	6p	47	63	6p	330	16	14p
1.5	83	6p	68	63	6p	330	63	25p
2.2	83	6p	68	16	6p	470	5.3	6p
3.3	83	6p	68	63	14p	470	10	14p
4.7	83	6p	100	63	6p	470	25	16p
6.8	40	6p	100	10	6p	470	40	25p
6.8	83	6p	100	25	6p	680	6.3	14p
10	25	6p	100	40	6p	680	15	25p
10	53	6p	100	63	16p	680	25	25p
15	16	6p	150	6.3	6p	680	40	25p
15	40	6p	150	10	6p	1000	4	14p
15	63	6p	150	25	6p	1000	10	16p
22	10	6p	150	40	14p	1000	16	25p
22	25	6p	150	63	6p	1000	25	25p
22	63	6p	220	4	6p	1500	6.3	18p
33	6.3	6p	220	10	6p	1500	10	25p
33	16	6p	220	15	6p	1500	15	25p
33	40	6p	220	25	14p	2200	6.3	25p
47	4	6p	220	40	16p	2200	10	24p
47	10	6p	220	63	25p	3300	6.3	25p
47	25	6p	330	4	6p	4700	4	28p
47	40	6p	330	10	6p			

● SWITCHES

Rotary adjustable stop. 1 pole, 2 to 12 way, 2 pole, 2 to 6 way, 3 pole, 2 to 4 way, 4 pole, 2 or 3 way 36p each. Slide Sub-min. DPDT 9p. Slide min. DPDT 19p. Push to make non-locking SPST 14p. Push-on, push-off locking DPDT 250V 4A 48p. Rocker white DPST 250V 10A 40p. Rotary mains DPST 250V 2A 20p. Toggle with on/off plate DPDT 250V 1.5A 25p.

● TRANSISTORS AND DIODES

AC127	18p	BY126	13p
AC128	16p	BY127	13p
AC176	17p	BY164	48p
AD161		BZV88	
162MP	93p	series	13p
BA100	9p	MPF102	36p
BA145	22p	OA91	6p
BC107	16p	OA200	7p
BC108	10p	OC71	20p
BC109	13p	SC146D	58p
BC109C	15p	TIS43	28p
BC142	23p	WO05	30p
BC143	26p	WO4	33p
BC147	10p	1N914	4p
BC148	16p	1N4001	6p
BC149	12p	1N4002	64p
BC168C	12p	1N4003	7p
BC169C	12p	1N4004	74p
BC178	17p	1N4005	8p
BC182L	20p	1N4006	84p
BC183L	12p	1N4007	9p
BC184L	12p	1N4148	4p
BC212L	14p	2N1302	20p
BC213L	15p	2N1303	20p
BC214L	18p	2N1304	30p
BCY71	22p	2N1711	24p
BD131	45p	2N2219	25p
BD132	54p	2N2646	45p
BD131/2MP		2N2905	33p
	£1.20	2N2926 Or.	
BD135	36p	Ye. or	
BD139	49p	Gn.	10p
BD140	65p	2N3053	18p
BF256	55p	1N4007	9p
BF259	25p	2N3819	22p
BFX29	30p	2N5459	51p
BFX30	33p	7400	16p
BFX84	30p	7413	39p
BFX85	36p	7447	£1.10
BFX87	30p	7473	54p
BFX88	25p	7474	45p
ZFY50	20p	7490	93p
BFY51	22p	7493	93p
BFY52	20p	£4121	37p
L.E.D. RED			
2mcd min only	15p		
Panel mtg. clip	5p		

(Other colours and 7-seg. displays in our catalogue)

● INTEGRATED CIRCUITS

CA3046 (14-pin DIL)	69p
LH0420H (TO9)	£4.25
MC1310P (14-pin DIL)	£2.50
MC1496 (14-pin DIL)	95p
MFC4000B	38p
MFC6040	83p
NE555V (8-pin DIL)	55p
SG1495 (14-pin DIL)	£2.70
SC3402 (14-pin DIL)	£1.89
µA741C (8-pin DIL)	36p
µA741C (14-pin DIL)	45p
µA747C (14-pin DIL)	£1.05
µA 748C (8-pin DIL)	39p
ZN414 (TO18)	£1.20

VOLTAGE REGULATORS
 µA7805 5V 1.5A (TO3) £1.75
 µA7815 15V 1.5A (TO3) £2.30
 MVR 5V, 12V, 15V, 500mA (TO3) £1.60
 µA78M05 5V 500mA £1.30
 µA78M15 15V 500mA £1.30
 µA78L05 5V 100mA (TO92) 60p
 µA78L15 15V 500mA (TO92) 60p
 µA723C Variable 2 to 37V (TO99 or 14-pin DIL) 75p

Our catalogue contains application circuits and data for all the above I.C.s and many more.

DISCOUNTS

Details in our catalogue. Start collecting MES Discount Vouchers NOW!

BCD OUTPUT SLIDE SWITCH
 Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue £1.38.

● PLUGS AND SOCKETS

Din	Plug	Chassis Socket
2-pin	8p	6p
3-pin	9p	7p
4-pin	10p	7p
5-pin A (180°)	10p	7p
5-pin B (240°)	10p	7p
5-pin B	10p	9p

JACK PLUGS

2.5mm Plastic Barrel	9p
2.5mm Metal Barrel	15p
3.5mm Plastic Barrel	9p
3.5mm Metal Barrel	15p
1/4in Std. Mono Plastic Barrel	13p
1/4in Std. Mono Metal Barrel	24p
1/4in Std. Stereo Plastic	18p
1/4in Std. Stereo Metal Barrel	30p

JACK CHASSIS SOCKETS

2.5mm open-type metal	9p
3.5mm open-type metal	9p
1/4in Std. Mono open-type metal	10p
1/4in Std. Mono moulded with 2 break contacts	14p
1/4in Std. Stereo open-type metal	15p
1/4in Std. Stereo moulded with 3 break contacts	18p

PHONO

Plastic-topped plug	5p
Screened plug	12p
Chassis socket single	4p
Chassis socket twin	6p

● MAINS CONNECTORS

P360 3-pin 1.5A Chassis plug with line socket	30p
SA2190 3-pin 5A Chassis plug	22p
SA1862 Line socket for SA2190	25p
P437 3-pin 5A Chassis socket with line plug	55p

● TRANSFORMERS

LT700 min. output. Pri. 1kΩ. Sec. 5V 200mA 50p; Sub-min mains. 6-0-6V 100mA 85p; 12-0-12V 50mA 95p (Size both approx. 30 × 27 × 25mm).
 Min. mains 0-6V 500mA, 0-6V 500mA £1.36; 0-12V 250mA, 0-12V 250mA £1.36; 0-20V 150mA, 0-20V 150mA £1.36; 0-24V 125mA, 0-25V 125mA £1.36.
 Mains MT3AT. Sec 12-15-20-24-30V 2A £3.60.
 Mains MT206AT. Sec 0-15-20V 1A, 0-15-20V 1A £3.98.

● ORGANS

A Full Scale Electronic Organ That You Can Build To Your Own Specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS.

Leaflet MESS1. Price 15p, describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.
 Leaflet MESS2. Price 5p - continues the description of the MESS5 series organs and shows you how to add a second keyboard with lots more stops.



● THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4kΩ to 8kΩ (highest) or 2kΩ to 4kΩ or 1kΩ to 2kΩ, etc. right down to 16Hz to 32Hz! And this new compatible design is even smaller: only 3.5in × 3.7in including gold-plated edge connector.
 DMO2T includes built in variable depth and rate frequency shift tremulant.
 DMO2 £12.25 DMO2T £14.25
 SAJ110 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.16.
 Keyboards high quality, fully sprung.
 Flat-front 48-note F to E £15.95
 Sloping-front 49-note C to C £15.95
 Sloping-front 61-note C to C £20.44
 Swell pedal with 10kΩ log pot £5.33
 *Spring Line Unit (short) £3.05
 *Spring Line Unit (long) £7.59
 *Reverberation Driver Module £5.34
 *S.A.E. please for full details. leaflet MES24.
 Gold-clad phosphor-bronze wire 39p per yd
 Palladium earth bar 15p per octave length
 Contact Blocks 2-make (GB2) 22p
 Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch 48p

SPECIAL OFFER

5W Audio Amp I.C. TBA810S with data and circuits.

Price £1.00

"ELECTRONICS TODAY INTERNATIONAL" 4600 SYNTHESISER


We stock all parts for this brilliantly designed synthesiser. This includes all the P.C.B. S. metalwork and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the E.T.I. International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. S.A.E. please for price list and specification. We also stock all parts for the P.E. Synthesiser, and Minisonic.




P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea (0702) 44101

VAT Please add 8% to the final total. Post and Packing FREE in U.K. (15p handling charge on orders under £1)

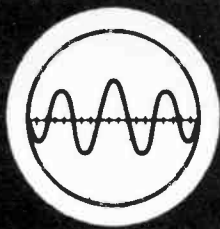First-class post pre-paid envelope supplied free with every order.



TUAC

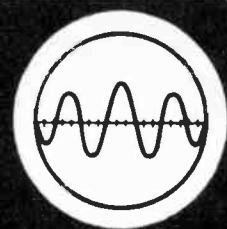

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD · LONDON SW17 9PG 01-672 3137/9080

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1M Ω ; Deck Tone Controls—treble + 20 - 10dB at 12kHz, Bass + 22 - 15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10k Ω ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47k Ω ; Power Requirements—30-45 volts at 100mA.

£26.50
PANEL SIZE
18 x 4½ in.
DEPTH 3 in.

HOW TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD (PE2)
or quote Access/Barclay Card No.
and post to TUAC LTD (PE2)

163 Mitcham Road, London, SW17 9PG


We accept phone orders against Access/Barclay Card Holders
Phone: 01-672 3137/9080

STOCKISTS—CALLERS ONLY

Bristol Disco Centre, 86 Stokes Croft, Bristol 1. Tel. 41666. Socodl, 9 The Friars, Canterbury. Tel. 60948. Calbarrie Audio, 88 Wellington Street, Luton. Tel. 411733. Damon Electronics, 99 Carrington Street, Nottingham. Tel. 53880. A1 Music Centre, 88 Oxford Street, Manchester. Tel. 236 0340. Mitchell Electronics, 64 Winchester Street, Salisbury. Tel. 23689. Wec Lighting, 35 Northam Road, Southampton. Tel. 28102.

NEW! 3 CHANNEL LIGHT MODULATOR

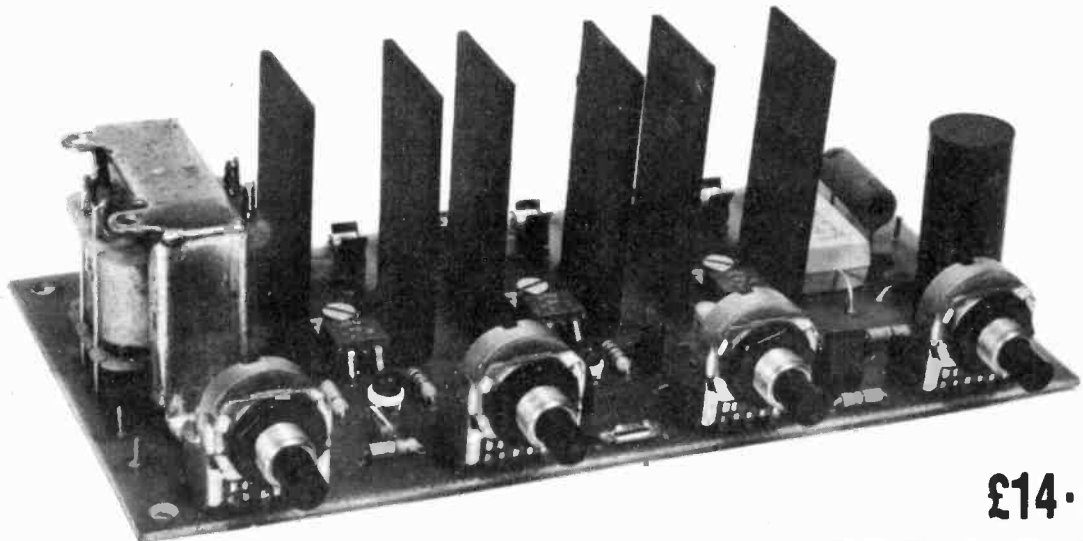
- R.C.A. 8 Amp Trlacs ● 1000W per channel ● Each channel fully suppressed and fused
- Master control to operate from 1W to 100W ● Full wave control—12 easy connections




£14.90

Single Channel Version £6.60

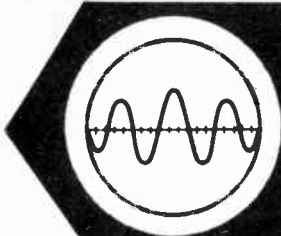MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT · OPEN 6 DAYS A WEEK 9.30am-6.00pm




TUAC

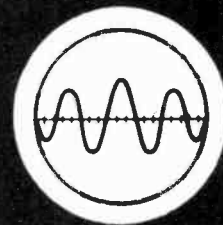

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

NEW TUAC POWER MODULES offering more power and quality than ever before.

Specification on all power modules:
All output power ratings ± 0.5 dB;
Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10k Ω ; Frequency response 20Hz-20kHz ± 2 dB; Hum and noise better than -70dB.

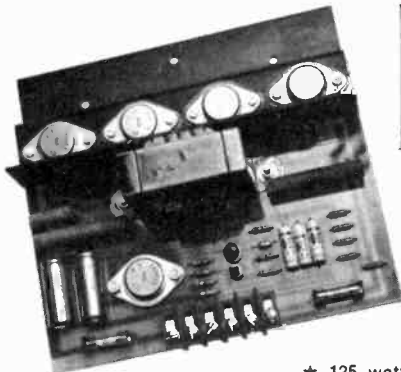


TP125

7 x 6 $\frac{1}{2}$ x 3in

£17.00

★ 125 watts RMS continuous sine wave output

★ 4 R.C.A. 150 watt 15 amp output transistors

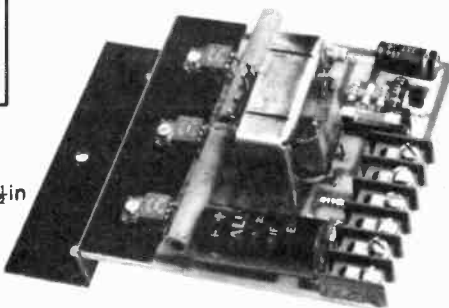

TL30


4 x 5 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in

~~£9.30~~

£7.90

★ 30 watts RMS continuous sine wave output
★ 2 R.C.A. 40 watt output transistors

★ Rugged layer wound driver transformer
★ Short—Open—and Thermal overload protection
★ Only 6 connections

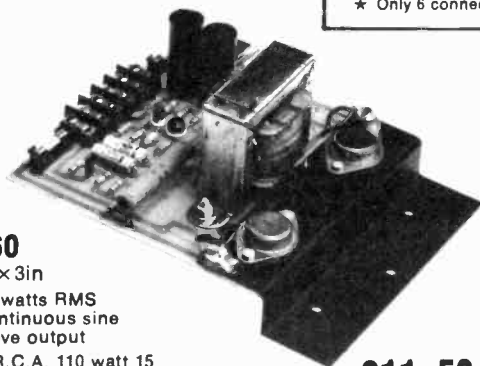

TL60

5 x 5 x 3in

★ 60 watts RMS continuous sine wave output

★ 2 R.C.A. 110 watt 15 amp transistors

£11.50


TL100

5 x 5 x 3in

★ 100 watts R.M.S. continuous sine wave output

★ 2 R.C.A. 150 watt 15 amp transistors

£13.20

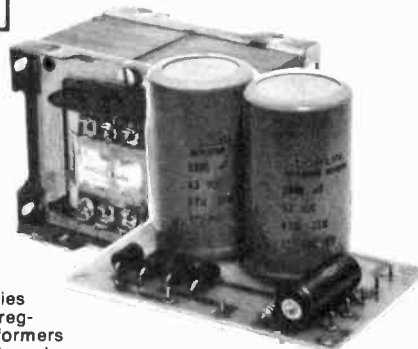

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 \pm 50 volts for one TP125	£11.50
PS 100 \pm 45 volts for one TL100	£10.50
PS 60 \pm 40 volts for one TL60	£9.30
PS 30 \pm 50 volts for one TL30	£5.90
PSU 2 for supplying disco mixer	£4.65

TUAC HIGH POWER AMPLIFICATION—ALL PURPOSE AMPLIFIER

built to high standards, and built to last
Suitable for Disco, PA, Guitar, 4 inputs, 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leathercloth covered case, short and open circuit protection. Tone control specification as VAO8 pre-amp. FULLY FUSED

MODEL 50	50 WATT	RMS CONTINUOUS SINE WAVE	£43.00
MODEL 100	125 WATT	RMS CONTINUOUS SINE WAVE	£64.50

Also available

100 WATT SLAVE AMPLIFIER
Spec as above. £48.50



ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED JUST SEND OR PHONE US YOUR NUMBER H.P. ARRANGED THROUGH PAYBONDS

A TECHNOLOGICAL MIRACLE DEVELOPED BY U.S. SPACE SCIENTISTS!

NOW YOU CAN JUDGE FOR YOURSELF WHETHER OR NOT THIS

MAKES VIRTUALLY EVERY OTHER TYPE OF WATCH IN THE WORLD OBSOLETE!

THE GREATEST HOROLOGICAL ADVANCE SINCE THE INVENTION OF THE CHRONOMETER

THE SYSTEM EXCELLED IN ACCURACY ONLY BY THE ATOMIC FREQUENCY STANDARD!



LIQUID CRYSTAL QUARTZ WRIST WATCH WITH CONTINUOUS 'COMPUTER DIGITAL READ OUT'

The space-age system **FEATURED ON TV!**

SAVE UP TO £140!

ELSEWHERE YOU COULD PAY UP TO £200 OR MORE FOR THIS INCREDIBLE NEW SPACE-AGE TYPE OF WATCH!

OUR WORLD SHATTERING PRICE **ONLY**

£57.95

REGISTERED POST PACK ETC. 50P

FROM WORLD FAMOUS MAKERS! The greatest Watch offer since time began! Everyone who sees it is fascinated by it! It's unbelievable! Continuous digital reading—hours and minutes AND second Pulsator miraculously transmits before your very eyes like a continuously changing TV Picture! A new "dimension" in time! Now YOU can join the elite few—the proud owners of a watch that is utterly different from any other timepiece you've ever known! **THEY'RE NEWS! THE WATCH OF TOMORROW-TODAY!** AND you buy at a price that's just a fraction of what you could have paid! But remember—you can only buy at this amazing price from Shopertunities. ★ **UNBELIEVABLY ACCURATE TO WITHIN SECONDS A YEAR!** The system excelled in accuracy only by the Atomic frequency standard! Now TIM can phone you for a time check! ★ **NO MOVING PARTS!** ★ **NO MAINTENANCE!** ★ **ABSOLUTELY SILENT!** ★ **BUILT TO GIVE A LIFE-TIME OF SERVICE!** ★ **18CT GOLD PLATED CASE!** ★ **BRAND SPANKING NEW ADVANCE 1975 MODEL! WRITTEN GUARANTEE.** Developed from the fantastic "space-age" techniques that first put men on the moon, this incredible watch is based on the natural action of Quartz Crystal, that vibrates approx. 32,768 times per second! A veritable miracle of micro-circuitry! An "electronic brain" with 1500 Transistors! You could even spend £400 or more for a Quartz Crystal watch! OUR fantastic cash price for this masterpiece is **ONLY £57.95, registered post, pack, etc. 50p ex, including expensive matching adjustable safety bracelet and presentation casket.** Send quickly and test for yourself on 7 days' mail order approval from receipt of goods. **REFUND IF NOT DELIGHTED.** Or send only £12.50 deposit, balance by 6 monthly payments of £9.47 (total credit price £69.32 plus post). Please hurry! Limited quantity! **THIS is the greatest investment you'll EVER make!** Or call at either store and see this fabulous watch for yourself! At this price you just can't lose!

Order by post to Uxbridge Road, or call at either store

Callers: ACCESS & BARCLAY CARDS ACCEPTED

Bargains galore at both stores—

COMMERCIAL TRAVELLERS NOTE: Merchandising office at Holborn.

SEND OR CALL

SHOPERTUNITIES LTD

Dept. PE/40, 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

PEMINISONIC

TRANSISTORS	VOLTAGE REGULATORS	POWER SLAVE P.C.B.'s
BC204 11p	ML7815 220p	Designers Layout Master Board £1.65
BC209C 11p	723 180p	Stabiliser £1.10
BC184 11p	ARRAYS	
BC212 14p	ML3046P 75p	
BC214 16p	CA3096AE 120p	
BC213 15p	OP. AMPS	
BC213L 15p	709/8 Dip 39p	
ZTX300 15p	710TOS 37p	
ZTX500 17p	748 48p	
2N2484 24p	FETMOPA 450p	
2N2904 30p	SPECIAL PURPOSE LINEARS	
2N2905 27p	SG3402N 174p	
2N2219 22p	SG3402T 174p	
2N3054 100p	SG1495D 290p	
High Voltage	MFC6040 100p	
MPSL01 39p	MFC4000B 70p	
MPSL51 41p	FETS	
MPSU07 69p	2N3819 46p	
MPSU57 85p	2N5459 60p	
SDT9203150p	DIODES	
T.T.L.	1N5401 21p	
7400J 29p	1N914 5p	
7402N 38p	BA148 25p	
7404N 24p	1SJ50 12p	
7410PC 24p	1G77 10p	
7420N 24p	NOISE DIODES	
7430PC 23p	Z11 53p	
7473N 48p	Z1M 120p	
7475N 75p	RECTIFIERS	
7476N 49p	REC41A 120p	
7489N 660p	REC46 255p	
7493PC 89p	REC70 40p	
74121J 85p	EA100/10 100p	
74122N 80p	MDA942A/1 210p	
74123N 144p	RESISTORS	
74150N 210p	2% METAL OXIDE 16p for 5	
V.A.T.	5% CARBON FILM 9p for 5	
Please add 8% to final total of order		
CONSTANTAN WIRE		
0.03 ohms/cm as specified for the POWER SLAVES. 20cm lengths 10p		
INTRODUCING THE MINISONIC C20 AUDIO CASSETTE		
£1.15 Inc. VAT P. & P.		

COMPONENT KITS NOW AVAILABLE. 4½p STAMP BRINGS DETAILS.

BARGAIN CORNER

2N3055 - 50p

Limited Stock to Clear

741 MINI DIP'S - 28p

Further Stocks Available

POTENTIO-METERS
MIN CARBON
24mm dia.

LINEAR 5kΩ; 10kΩ; 25kΩ; 50kΩ all at 21p each
GANGED. 100kΩ lin; 5kΩ log; 10kΩ log. all at 78p each

PRECISION TURN 10
1kΩ R.S. TYPE £3.40

CAPACITORS
Tubular Electro. 14p
25V, 25µF; 47µF
100µF 16p, 470µF 29p
1000µF 46p
50V, 1000µF 57p
63V, 10µF 22p
100µF 24p

PRINTED CIRCUIT ELECTROLYTIC
4.7/40V; 10/63V
22/40V; 47/40V
13p each
100/63V; 470/16V
23p each

HIGH RIPPLE TYPE
3300µF 63V £2.20
7100µF 40V 75p
10000µF 40V £1.44


TERMS: MAIL ORDER ONLY. C.W.O. Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P.&P. Otherwise please add 10p in the £1.



INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT! HANDY! TIDY!

DISCOUNT PRICES

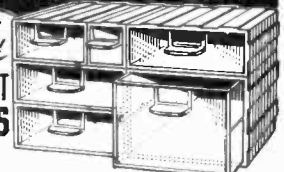

5 SIZES ALL INTERLOCK

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins × 2½ins × 2½ins). £2 DOZEN.

DOUBLE UNITS (2D) (5ins × 4½ins × 2½ins). £3.50 DOZEN.

TREBLE (3D) £3.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4.90 for 8.

EXTRA LARGE SIZE (6D1) £4.50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £ Orders £30 and over DEDUCT 7½% in the £

PACKING/POSTAGE/CARRIAGE: Add 40p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES Please add 8% V.A.T. to total remittance

FLAIR (Dept. PE2), 124 Cricklewold Broadway, London, N.W.2 Tel. 01-450 4844


CUSTOM CABINETS

331 High Street, Rochester, Kent. Tel: Medway (0634) 404199


SPEAKER CABINETS IN KIT FORM REPRESENT **HUGE SAVINGS**



2' x 12" Cabinet

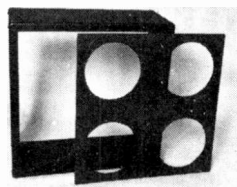

4' x 12" Cabinet

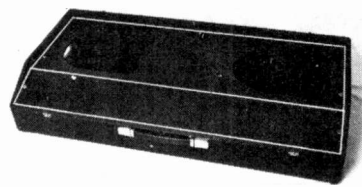

Disco Console (includes lid not shown)
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!


Kits are available in all specifications and all the kits contain everything you need as follows :-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!

PRICE & TYPE LIST

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4"	£21.45	£13.75
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4"	£26.95	£19.25
4 x 12" P.A. Column	48" x 27" x 13" x 3/4"	£33.00	£23.65
1 x 18"	31" x 31" x 13" x 3/4"	£26.95	£19.25
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4"	£23.10	£14.85
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 8" x 1/2"	£22.00	£14.30
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 1/2"	£27.50	£19.25

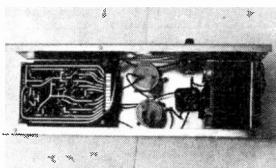Please ask for quotation on any other type or size of cabinet you may require.



- * 100w RMS slave amp for Disco
- * 100w RMS continuous sine wave output
- * Short and open circuit protection
- * Built to highest industrial spec.
- * Price £37.00 complete




- * Stereo studio disco mixer
- * Full PFL and Monitor facilities
- * As used by John Peel, Mark Wesley, Paul Burnett, DLT, Dave Christian, Tony Prince
- * Price £120.00



- ERC 100w power amplifier
- * Electrolytic capacitors and second generation ICs
- * Fully protected against short or open circuit
- * Less than 0.1% distortion at all powers
- * Rise time 4µs-stability- Unconditional Price £66.50

ALL OUR PRICES INCLUDE VAT AND UK DELIVERY

VALUE!!

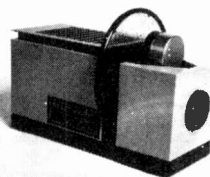

LOOK!!

Disco imp projector 150 watt tungsten
unbeatable price
Includes liquid wheel and postage
Normally sold between £24—£27.50

UNBEATABLE NOW ONLY £18

TRADE AND EXPORT ENQUIRIES WELCOME

R T V C FOR AUDIO AT A BUDGET

COMPLETE STEREO SYSTEM **System 1. £51.00**

*



40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.

System I includes:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within -1dB R.L.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble -12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 1/2" x 9" x 3 1/2".

Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 1/2" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. 10 watts handling.

Complete System £51.00

System 2. £69.00

Viscount III amplifier (As System I)

Garrard SP 25 Mk III deck (As System I)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2"

Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £69.00

PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge and hinged cover	£21.00 + £1.75 p & p
total:	£59.20

Available complete for only: **£51.00**
+ £3.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£84.20

Available complete for only: **£69.00**
+ £4.00 p & p



STEREO 21* QUALITY SOUND FOR LESS THAN £20.00

Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes:- BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.


Specifications: For the technically minded:-

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel.

Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only **£19.55 + £1.60 p & p**. Extras if required. Optional Diamond Stylus **£1.37**.

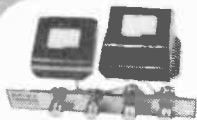Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



BUILD YOUR OWN* STEREO AMPLIFIER

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£7.64+55p p & p

8 TRACK HOME CARTRIDGE PLAYER*



Elegant self selector push button player

for use with your stereo system.

Compatible with Viscount III system,

Unisound module and the Stereo 21.

Technical specification Mains input,


240V. Output sensitivity 125mV

Comparable unit sold elsewhere at

£24.00 approx. Yours for only

£11.95 + 90p p & p.

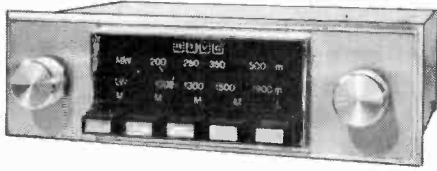PUSH BUTTON CAR RADIO KIT* - The Tourist II



NO SOLDERING REQUIRED!

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth. (2) **Integrated circuit** output stage, pre-built three stage IF Module. **Controls** volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4½" deep approx £7.70 + 55p. p & p. **Speaker** including baffle and fixing strip £1.65 + 23p. p & p.

Car Aerial Recommended—fully retractable £1.37 + 20p. p & p.

The Tourist I Kit For the experienced constructor If you can solder on a printed circuit board you can build this model.

Same technical specification as Tourist II

Price £6.60 + 55p p & p.

EMI SPEAKERS AT FANTASTIC REDUCTIONS



20 WATT SPEAKER SYSTEM*

System consists of a 13" x 8" (approx) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components.

Technical Specification:

Bass Unit
Flux density—100 K, speech coil—1½", Cone, Triple laminated paper with P.V.C. surround.
Mid Range Unit
Flux density—33K, speech coil—1" with parasitic tweeter.
Power Handling
20 watts R.M.S., impedance—8 ohms, frequency response—20 Hz to 18,000 Hz.


OUR PRICE
£6.60. Complete
+ 90p p & p.



15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz, flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

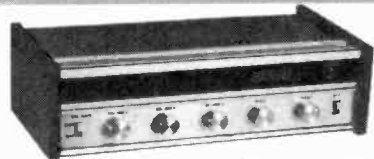Recommended retail price £40-80.
OUR PRICE £18-70
+ £1-50 p & p



DISCO AMPLIFIER*

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. **Outputs** 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls.



*Separate bass and treble controls common to all 4 inputs.

*Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES —Input—1.) Crystal mic, guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).

—Inputs—2), 3), 4). Medium output equipment—ceramic cartridge, tuner, tape recorder, organs, etc.—all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12½" x 6" x 3½". **£15.00 + 60p. p & p**

PORTABLE DISCO CONSOLE*

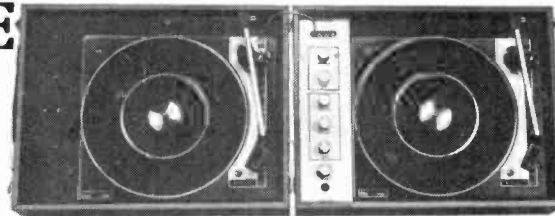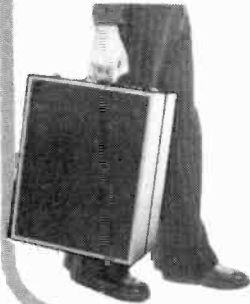

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

TECHNICAL SPECIFICATION:

Pre-amp—Output—200mV

Auxiliary inputs—200mV and 750mV into 1 meg.

Mic input—6mV into 100K. 240 volt operation.

Turntables capacity—7", 10" or 12" records.

Rumble, wow and flutter

Rumble Better than—35dB. Wow Better than 0.2%.

Flutter Better than 0.06% (Gaumont kalee meter).

Finish—Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size—

Unit Closed—17¼" x 13¼" x 8¼" (approx.)

Unit Open—35¼" x 13¼" x 4¼" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £45.00 + £3.50 P. & P.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Nov. 1974 and subject to change without notice. All prices include V.A.T. at 8% rate.

Personal Shoppers Edgware Road: 9a.m.—5.30p.m. Half day Thurs. Acton: 9.30a.m.—5p.m. Closed all day Wed.



Radio and TV
Components
(Acton) Ltd.

21d High Street, Acton, London W3 6NG
323 Edgware Road, London W2

SPARKRITE Mk II

Electronic Ignition... Better on all points



Because you keep your points!



The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly — with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of normal, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes.
- Up to 20% better fuel consumption.
- Instant all weather starting.
- Cleaner plugs — they last 5 times longer without attention.
- Faster acceleration.
- Faster top speeds.
- Coil and battery last longer.
- Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

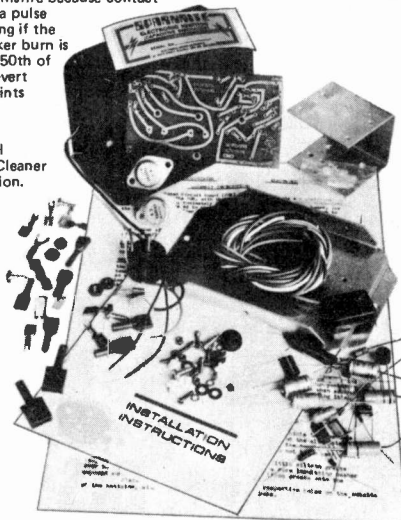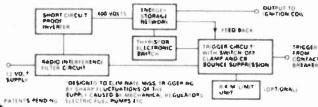WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!



Sparkrite MK II — full capacitive discharge electronic system — not just a transistorised inductive discharge booster.

PRICES

D.I.Y. Kit only £10.93 incl. VAT and P & P
 Ready Built Unit £13.86 incl. VAT and P & P
 (Both to fit all cars with coil/distributor ignition up to 8 cylinders).
 We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition. Details on request. Call in and see us for a demonstration.

ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES
 (Dept PE 2) 82 Bath Street
 Walsall WS1 3DE Phone 33652

Please supply

- Sparkrite Mk 2 D.I.Y. Kit(s) at £10.93 each incl VAT and P & P (Will make pos or neg earth)
- Sparkrite Ready Built Neg. Earth Unit(s) at £13.86 each incl. VAT and P & P
- Sparkrite Ready Built Positive Earth Unit(s) at £13.86 each incl. VAT and P & P

NAME _____
 ADDRESS _____

I enclose cheque/P.O. for £ _____
 Send SAE for brochure.

G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

We are glad to say that it is now possible to supply from stock the following integrated circuits. ALL ARE BRANDED, FULL SPECIFICATION devices offered at unbeatable prices!

	1/99	100/499	500/1000		1/99	100/499	500/1000		1/99	100/499	500/1000
7400	£0-15	£0-125	£0-10	7442	£0-645	£0-537	£0-43	7494	£0-495	£0-412	£0-33
7401	£0-15	£0-125	£0-10	7443	£1-275	£1-062	£0-85	7495	£0-63	£0-525	£0-42
7402	£0-15	£0-125	£0-10	7445	£0-855	£0-712	£0-57	7496	£0-72	£0-60	£0-48
7403	£0-15	£0-125	£0-10	7446	£1-05	£0-875	£0-70	74104	£0-315	£0-262	£0-21
7404	£0-18	£0-15	£0-12	7446A	£1-05	£0-875	£0-70	74105	£0-315	£0-262	£0-21
7405	£0-18	£0-15	£0-12	7447	£1-05	£0-875	£0-70	74107	£0-315	£0-262	£0-21
7406	£0-375	£0-312	£0-25	7447A	£1-05	£0-875	£0-70	74121	£0-315	£0-262	£0-21
7407	£0-375	£0-312	£0-25	7448	£0-855	£0-712	£0-57	74122	£0-45	£0-375	£0-30
7408	£0-15	£0-125	£0-10	7450	£0-15	£0-125	£0-10	74123	£0-63	£0-525	£0-42
7409	£0-15	£0-125	£0-10	7451	£0-15	£0-125	£0-10	74141	£0-75	£0-625	£0-50
7410	£0-15	£0-125	£0-10	7453	£0-15	£0-125	£0-10	74151	£0-69	£0-575	£0-46
7412	£0-195	£0-162	£0-13	7454	£0-15	£0-125	£0-10	74153	£0-69	£0-575	£0-46
7413	£0-345	£0-287	£0-23	7460	£0-15	£0-125	£0-10	74155	£0-69	£0-575	£0-46
7416	£0-345	£0-287	£0-23	7472	£0-255	£0-212	£0-17	74156	£0-69	£0-575	£0-46
7417	£0-345	£0-287	£0-23	7473	£0-153	£0-262	£0-21	74160	£1-005	£0-837	£0-67
7420	£0-15	£0-125	£0-10	7474	£0-315	£0-262	£0-21	74161	£1-005	£0-837	£0-67
7423	£0-27	£0-225	£0-18	7475	£0-465	£0-387	£0-31	74162	£1-005	£0-837	£0-67
7425	£0-27	£0-225	£0-18	7476	£0-315	£0-262	£0-21	74163	£1-005	£0-837	£0-67
7426	£0-27	£0-225	£0-18	7480	£0-435	£0-362	£0-29	74166	£1-425	£1-187	£0-95
7427	£0-27	£0-225	£0-18	7482	£0-75	£0-625	£0-50	74174	£1-20	£1-00	£0-80
7430	£0-15	£0-125	£0-10	7483	£0-825	£0-687	£0-55	74175	£0-975	£0-812	£0-65
7432	£0-25	£0-225	£0-18	7485	£1-275	£1-062	£0-85	74192	£1-275	£1-062	£0-85
7437	£0-27	£0-225	£0-18	7486	£0-315	£0-262	£0-21	74193	£1-275	£1-062	£0-85
7438	£0-27	£0-225	£0-18	7490	£0-465	£0-387	£0-31	74198	£2-10	£1-75	£1-40
7440	£0-15	£0-125	£0-10	7492	£0-465	£0-387	£0-31	74199	£2-10	£1-75	£1-40
7441A	£0-825	£0-687	£0-55	7493	£0-465	£0-387	£0-31				


To secure the above prices, all orders for these devices must exceed £25 in total value. Price rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made. For special quotations for large orders ring 021-327 2339 NOW!!!

NEW! NEW! NEW! NEW!
 An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
 Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet). Spray with developer, rinse and etch in normal manner.
 Light sensitive aerosol spray £1-00 plus
 Developer and Etchant 50p postage

FIBRE-GLASS COPPER LAMINATE
 Single sided 75p sq. ft
 Double sided £1 sq. ft
 Cut in any multiple of 6in to a maximum size of 3ft x 4ft


POSTAGE 25p NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS) POSTAGE 25p

SUPERSOUND 13 HI-FI MONO AMPLIFIER

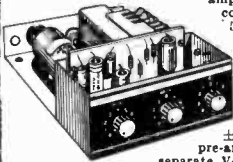

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz $\pm 3db$. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, eutechone panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £23.00. P. & P. 60p.

DE LUXE STEREO AMPLIFIER

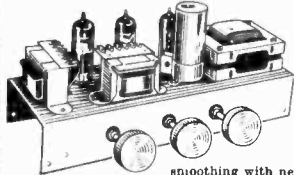

A.C. Mains 200-240 v. U.S.A. 110 v. Heavy duty fully isolated mains transformer with full wave rectification giving adequate r.f. smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes, 1 x E230 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4 1/2". Overall height including valves. Ready built and tested to a high standard. £10.75. P. & P. 50p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7.4v. and 9v. and 12v. at 1 amp on lead. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5.20. P. & P. 35p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS 35p 54 in. wide. Our price £1.30 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3 1/2" deep x 6 1/2" high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 40p. BARGAIN PRICE £4.20

FEW ONLY. High grade mains transformer with grain orientated lamination. Primary 200/240. Secondary 15-15 volts at 0-6 amps and 4-6 volts at 0-3 amps. Size 2in. long x 2 1/2in. wide x 2in. deep overall. £1.35 plus 25p. P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.60. P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Prio. 200/240V. Sec. 9-0-9 at 500 mA. £1.25. P. & P. 25p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.40. P. & P. 25p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.00. P. & P. 35p.

3 VOLT RELAY. 100 m/a single pole normally closed. 2 for 60p. P. & P. 10p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price £1.20. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVS. AND SUBS.

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between the transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents 90p. Transistor Equivalents £1. Transistor Characteristics £1.30. POST FREE. All three together £3.

NEW ISSUE

Thyratron, Triac, Diac etc. encyclopedias £1. Post Free. 8 pole 3 way 2 bank low loss Yaxley type switches 11" sections. Standard spindle. 2 switches 64p + 10p P. & P.

Open 9.30-5.30 Monday to Friday, 9.30-5 Saturday Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice


HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

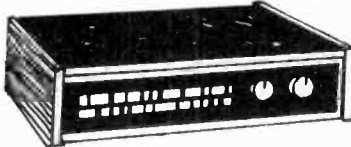HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to "lock on" station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2in wide x 8in deep by 2 1/2in high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). PRICE £23.00. Post and Packing 50p.

STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-18V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5 plus 10p P. & P. Stereo beacon light if required 40p extra.



LATEST HI SENSITIVITY UNI-DIRECTIONAL SLIM-LINE CONDENSER MICROPHONE as used by many professional hi-fi low acoustic feedback. Available Hi impedance or low impedance. State which required. £13.50. P. & P. 25p.

LATEST ACOS GP11/18C mono compatible cartridge with 1/0 stylus for LP/EP/78. Universal mounting bracket. £1.46. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY £1.75. P. & P. 15p.

SONOTONE TAPE COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphires 78. ONLY £2.27. P. & P. 10p.

Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.76. P. & P. 15p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £1.60. P. & P. 15p.

LATEST RONETTE T/O COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in wide x 3in deep x 6in high. Ready built and tested. PRICE £5.50. P. & P. 50p.

ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6.70. P. & P. 60p.

HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover (approx). AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which).

OUR PRICE £9.50 each. Carr. 90p.

Cabinet Available Separately £5.00. Carr. 90p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.00. Carr. 70p.

LOUDSPEAKER BARGAINS

5in. 3ohm £1.25. P. & P. 15p. 7 1/2in. 3ohm £1.40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 5in. 3ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3.50. P. & P. 30p. E.M.I. 13 x 8in 3, 8 or 15 ohm with inbuilt tweeter and crossover network £4.60. P. & P. 30p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. £1.25 + 20p. P. & P.


BRAND NEW. Bakers Loudspeakers at substantial discounts. 12in. 16w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with Hi Flux ceramic ferrobar magnet assembly £7.50. Guitar models: 25w. £7.50. 36w. £8.50. P. & P. 45p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3, 8, 15 ohm (state which) £3. P. & P. 36p. "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for details. Only £6.60 each. P. & P. 34p. NOW ALSO AVAILABLE: 8in. 10W rms 20W peak 40Hz-20,000Hz. Overall depth 1in. Ideal for Hi-Fi or for use in cars. £4.32. P. & P. 25p.

SPECIAL BARGAIN OFFER! Limited number of BSR C123 Auto Changer De Luxe with light weight tubular arm and stereo cartridge. Brand new. ONLY £8.00 + p. & p. 60p.

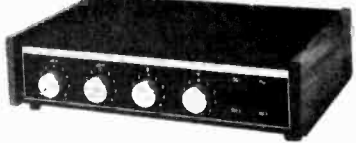HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




A really first-class HI-FI Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response $\pm 3db$ 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: $\pm 3db$ 12-15,000 Hz. Bass, boost approx. 10 $\pm 12db$. Treble cut approx. to -16db. Negative feedback 18db over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT £18.96 P. & P. 30p (Magnetic input components 33p extra)
POWER PACK KIT £4.32 P. & P. 40p
CABINET £4.32 P. & P. 40p
(Post Free if all units purchased at same time)

Also available ready built and tested £28.08. Post Free.

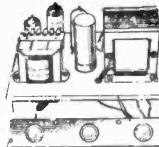Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discoteque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on detached heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2". Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £6.60. P. & P. 45p.

HBL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5.50. P. & P. 45p.

10 1/4 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP86 and E280 rectifier. Simple instruction booklet 15p x S.A.E. (Free with parts). All parts sold separately. ONLY £10.25. P. & P. 60p. Also available ready built and tested £14.00. P. & P. 70p.

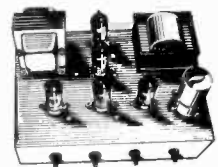

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £5.50. P. & P. 25p.

PRICES INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL

Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and 12V plus 25p Control Switch. **£7-50** P. & P.



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box approx. 4" x 3" x 2½" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at **£7-50** plus 10p.

MINIATURE RELAYS
Brand new range of British made relays, size: 1½in x 1in x 1½in. All two changeovers with 250V 1-5A contacts and suitable for fitting on 0-1in veroboard.
Type Volts Current Ohms
27/A 12V 17mA 700 All
21/A 12V 28mA/A 430 41-30
12/A 6V 33mA/A 185 each
200/250V Mains Relay
Heavy duty contacts 2,500 ohm coil. All new and unused D.P.D.T. mains relays 50p. Carr. free. Special quantity £40 per 100 off.

MIDGET MAINS TRANSFORMER
Varnish Impregnated
Size 45mm x 36mm x 31mm
PRI 240V
Sec 3-0-3 100mA
Sec 6-0-6 100mA
Sec 9-0-9 100mA
Sec 12-0-12 100mA
Sec 20-0-20 100mA
£1-23 10p P. & P.

CRESCENT BUBBLE LIGHT SHOW
This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—160W convection cooled. At 30ft the projected image is 18ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, **£15**; Wheel, **£5**; Total **£20**. Plus 75p carr.

7in x 4in LOUDSPEAKER
A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: **£1-60**. Free postage on this item.

U.K. CARRIAGE 15p UNLESS OTHERWISE STATED

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD. IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE**
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (80W into 16 ohm).

★ **THE PRE-AMP MODULE**
Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ **THE POWER SUPPLY**
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. **£25**, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

12-0-12V 500M/A
240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price **£1-20**.

18V 500M/A
240V primary. Approx. size: 60mm x 40mm x 50mm. Fixing centres: 75mm. Our Price **£1** each.

BARGAIN BOX
Loud buzzer mounted in a metal box complete with two U2 battery size holder. Designed and can be used as a fire alarm but is ideal as a door or Morse code practice buzzer. Approx. size: 2½in x 6½in x 1½in. **OUR PRICE 60p**

ABS PLASTIC BOXES
Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm x 73mm x 45mm 51p; 1006, 160mm x 75mm x 47mm 66p; 1007, 184mm x 124mm x 60mm 98p; 1021, 106mm x 74mm x 45mm (sloping front) 50p.


BARGAIN BOARDS
Components galore for the experimenter. Ex-Computer boards with resistors, capacitors and useful transistors—at least 4 transistors per board. Five boards **£1**.

2in. PANEL METERS

Size 59mm x 46mm
0-50µA—ME6 0-100mA—ME13
0-100µA—ME7 0-500mA—ME14
0-500µA—ME8 0-1A —ME15
0-1mA—ME9 0-50V a.c.—ME16
0-5mA—ME10 0-300V a.c.—ME17
0-10mA—ME11 S meter —ME18
0-50mA—ME12 V.U. meter—ME19
£3 each. 10p P. & P.

POWER PACKS
PP1 Switched 3-6-74-9V 400mA Transistor and Zener Stabilised On/Off switch and Polarity Reversal switch, in a black metal case, **£5-25** each.
PP2 Switched 6-74-9V Battery Eliminator. Approx. size 2½in x 2½in x 3½in. Ideal for cassette recorders, **£2-75** each (Philips type **£3-00**).
PP3 Car converter. From 12V Pos. or Neg. to = 6-74-9V. Easy to fit and transistor regulated, **£3-90**.

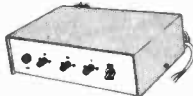3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18-50 plus 38p P. & P.

MINI LOUDSPEAKERS
2½in 80 ohm, 50p; 2½in 40 ohm, 50p. Please include 5p P. & P. on each L.B.

SEND 20p FOR A CRESCENT CATALOGUE



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, to become our famous courses go right up to City & Guilds levels.

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. AT NO EXTRA CHARGE! And this is a course anyone can afford. (You can even pay for it by easy instalments.)

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CPE 01
READING RG7 4PF

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME _____
ADDRESS _____
POSTCODE _____

BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

THE NEW NELSON-JONES FM TUNER



PUSH-BUTTON VARICAP DIODE TUNING (6 Position)

(‘WW’ JUNE ‘73)

Exclusive Designer Approved Kits

What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as:—

- MOSFET** front end for excellent cross modulation performance and low noise.
- 3 GANG** tuning for high selectivity.
- VARICAP** tuning diodes in back to back configuration for low distortion.
- CERAMIC** filters for defined IF response.
- INTEGRATED** circuit IF amplifiers for reliability and excellent limiting/AM rejection.

- PHASE LOCKED** Stereo decoder with Stereo mute, see below
- LED** fine tuning indicators.
- PUSH BUTTON** tuning (with AFC disable) over the FM band (88-104)
- IC STABILISED** and S/C protected power supply.
- CABINET** double veneered against warp.

The Nelson-Jones Tuner has all of these features and many more, and more importantly the design is fully proven not just with a few prototypes but with many thousands of working tuners spread across the world.


Typ. Specn: 20 dB quieting 0.75uV. Image rejection —70dB.I.F. Rejection —85 dB.

Basic tuner module prices start as low as £12.31, with complete kits starting at £26.95 (mono) + P.P. 65p, and of course all components are available separately.

Our low cost alignment service is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.


PORTUS and **HAYWOOD PHASE LOCKED DECODER** (W.W. Sept. ‘70). Still the lowest distortion P.L. decoder available. THD typically 0.05% (at Nelson-Jones Tuner O/P level)! Supplied complete with Red LED. Price £7.02 when bought with a complete N-J tuner kit or £8.29 if bought separately (P.P. 21p). **PLEASE NOTE.** Existing tuners are readily convertible and kits/parts are available for this purpose.

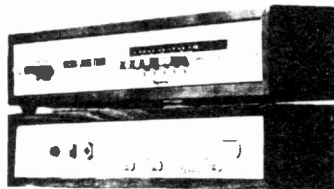TEXAN AMPLIFIER. We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at £30.78 plus P.P. 65p including Teak Sleeve.



NEW LOW COST STEREO TUNER Available as basic or complete kits

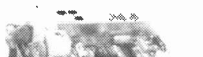Basic stereo tuner £15 post free.
Basic mono tuner £12 post free.
6 position push button units with integral pots £2.82.



No alignment required. Mullard LP1186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with Interstation Mute, restricted range AFC, single LED tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner.)

TYP. SPECIFICATION
2uV for 30dB S/N
Image rejection 40dB
IF rejection 65dB

VAT at 8% is included in all prices

PRICE Complete stereo kit £28.42
Complete mono kit £24.19
P. & P. 65p

Access

INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW Phone Swadlincote (023387) 5432 Telex 377106

PC ETCHING KIT

Contains 1lb ferric chloride, 100 sq ins copper clad board, DABO etch resist pen, abrasive cleaner, dish for etching and instructions. £3.30.

RESISTORS AND CAPACITORS
500 assd. resistors £1.40, 2500 £5, 15 different trimmers, air-spaced and compression up to 1250pF £1.

VEROBOARD

100 sq ins assorted sizes and pitches, about 8 bits £1.10.

3W TAPE AMPLIFIERS

Polished wooden cabinet 14x13x9" containing a ferric chloride 4 valve amplifier (20uV), with tone and volume controls. 3 watts output to 7 x 4" 30p speaker. Also a non-standard single motor tape deck. Supplied in good working condition with circuit. Standard mains operation. £4.50. Suitable cassette £1.10. Spare head 30p. Tape (ex-computer) 75p. Amplifier chassis only, complete and tested with speaker (uses 2 x ECC83, EL84, EZ80) £3.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb 90p, 3lb £1.65, 10lb £4.45, 100lb £35.

P.O. AMPLIFIER UNIT

Contained in steel case 5 1/2 x 5 x 3 1/2 are 2 x GET116 transistors on heat sinks, 3 pot cores, 2 30V zeners, 4 audio transformers, 1% R's & C's. With circuit £1.

SEMICONDUCTORS

All new full spec devices: AC127 AC128 AC176 AC177 AC187 AC188 all 20p; BC107, 8, 9 10p; 2N3 723C 75p; 741C 35p; IN914 4p; IN4001 6p; IN4004 8p; IN4007 12p; 800V 1 1/2A 10p; 499mW zeners 10p; 400V 6A triac £1.

715 BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches.

All prices include VAT and postage. SAE list, enquiries. Computers, equipment and components always wanted for cash.

GREENWELD ELECTRONICS (PE2)

Head office, mail-order dept. Wholesale/Retail shop: 51 SHIRLEY PARK RD., SOUTHAMPTON SO1 4FX. Tel. (0703) 772501. Also callers welcome at 21 Deptford Broadway SE8. Tel. 01-692 2009 and 38 Lower Addiscombe Rd., Croydon. Tel. 01-688 2950.

plus PC boards with transistors and diodes. Also loads of odds and ends. Contents always changing as new goods come in. Amazing value at £2.30.

COMPUTER PANELS

Always thousands in stock, all sizes, shapes and prices from 5p. 31b assorted £1.40, 71b £2.65, 561b £15. 12 high quality panels with power transistors, IC's, trim pots etc £2.50. Pack containing about 500 components including at least 50 transistors 95p. Pack of boards with 50 14 pin DIL DTL IC's £1.

TRANSFORMERS

All mains primary, 6-0-6V @ 100mA 85p; 9-0-9V @ 100mA 90p; 12-0-12V @ 100mA 95p; 16-0-16V with 9V tap @ 1 1/2A £2; 24-0-24V @ 500mA £1.85; 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V @ 1A £1.45; The following are ex-equip: 224-0-224V @ 1A £2; 12V @ 15A £3.50; 18V @ 5A £3; 55V @ 5A £4.

MULTIMETERS

LT101: 0-10-50-250-1000V AC & DC, 0-1-100mA DC, 0-150KΩ Only £3.60. IT12: 20,000 ΩV, 0-5-25-50-250-500-2500V DC, 0-10-50-100-500-1000V AC, 0-50µA-2.5-250mA, 0-60K-6MΩ, —20 to +22dB. Protected meter movement £6.20. Computer equipment: Ampex TM2 8 track 1/2" tape decks £27 (Callers only). Also paper tape punches, readers, etc.

POWER SUPPLIES

G101. Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1.7-10.5V output with 2 extra capacitors (provided) £1.20. G102. These are stabilized power supplies giving 7 1/2V @ 225mA. Voltage can be altered by changing zener. Not working, but only minor faults £1.

CJL PRICES INCLUDE P&P AND V.A.T.

- AERIAL**, telescopic, 15-120cm. £1.20
- AERIAL**, telescopic, h and v swivel, 15-80cm. . . £1.78
- EARPHONE**, stethoscope style, 8 ohm dynamic. . £1.00
- HAND DRILL**, (Leytool), Compact precision drill, 5/16" chuck. Gears totally enclosed, S/L bearings. . . £2.90
- INTEGRATED CIRCUITS**
- AUDIO POWER AMPLIFIER** (National) LM380 £1.00
- A.M. RADIO RECEIVER** (RCA) CA3123E £1.40
- F.M. STEREO DECODER** (Motorola) MC1310P £2.80
- I/C TIMER** (Signetics) NE555V £0.78
- D.I.L. SOCKETS** (pk of 3) 8 pin £0.50 14 pin £0.55
- KEYNECTOR**, rapid connect—single/multiple leads to mains. Built-in piano switches, neon & 13A fuse. . £3.20
- MICROPHONE**, lightweight dynamic, remote start/stop 200 ohms, 100-10,000Hz, 6mV average output. . £1.80
- MULTIMETER**, small and attractive, Vdc-10.50, 250, 1,000. Vac-10.50, 250, 1,000. Idc-100mA, R-150k. £4.95
- POWER SUPPLY COMPONENTS**
- SILICON BRIDGE RECTIFIER**, 100 P.I.V./2A £0.40
- ELECTROLYTIC CAPACITOR**, 2,200uF/50V £0.57
- ELECTROLYTIC CAPACITOR**, 5,000uF/25V £0.63
- SILICON POWER TRANSISTOR**, 2N3055 £0.60
- VOLTAGE REGULATOR** (Fairchild) uA7805 £1.70
- VOLTAGE REGULATOR** (Signetics) NE550A £0.80
- SIGNAL INJECTOR** produces audio through video signals, excellent—servicing amplifiers, radios, televisions, etc. £3.92
- SOLDERING IRON**, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable). . £1.85
- 3/32" bit £0.45 3/16" bit £0.45 Element £0.95
- STAND**, (Antex), ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits. . £0.95
- SPEAKER**, miniature, 8 ohms, 70mm dia. . . £0.80

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107	22	AD161 and	BC150	20	BD131	55	BF180	33	MAT120	21	T1843	33	2N1309	26	2N2926B	11	2N3806	30
AC113	20	AD162MP 76	BC151	22	BD132	66	BF181	33	MAT121	22	UT46	30	2N1813	22	2N3010	77	2N3808	13
AC115	22	ADT140 55	BC152	19	BD133	72	BF182	44	MJE2955	65	ZN414	£1.20	2N1711	22	2N3011	16	2N4059	11
AC117K	32	AF114 27	BC153	31	BD136	44	BF183	44	MJE3055	92	2G301	21	2N1889	35	2N3053	10	2N4060	13
AC122	13	AF115 27	BC154	38	BD136	44	BF184	28	MJE3440	55	2G302	21	2N1890	50	2N3054	51	2N4061	13
AC125	18	AF116 27	BC167	20	BD137	50	BF185	33	MPF102	48	2G303	21	2N1893	41	2N3055	45	2N4062	13
AC128	19	AF117 27	BC168	13	BD138	55	BF187	30	MPF104	41	2G304	27	2N2147	70	2N3391	16	2N4284	19
AC127	20	AF118 33	BC169	18	BD139	81	BF188	44	MPF105	41	2G306	44	2N2148	63	2N3391A	16	2N4285	19
AC128	20	AF124 33	BC160	50	BD140	68	BF194	13	OC19	39	2G309	39	2N2160	66	2N3392	16	2N4286	19
AC132	16	AF125 33	BC161	55	BD155	88	BF195	13	OC20	70	2G309	39	2N2192	39	2N3393	16	2N4287	19
AC134	16	AF126 31	BC167	13	BD175	66	BF196	16	OC22	52	2G339	22	2N2192	39	2N3394	16	2N4288	19
AC137	16	AF127 31	BC168	13	BD176	66	BF197	16	OC23	54	2G339A	18	2N2193	39	2N3395	16	2N4289	19
AC141	20	AF139 33	BC169	13	BD177	72	BF200	50	OC24	62	2G344	20	2N2194	39	2N3402	23	2N4290	19
AC142	20	AF178 55	BC170	13	BD178	72	BF222	£1.05	OC25	42	2G345	18	2N2217	24	2N3403	23	2N4291	19
AC142K	28	AF179 55	BC171	18	BD179	75	BF227	60	OC26	32	2G371	18	2N2218	22	2N3404	31	2N4292	19
AC154	22	AF180 55	BC172	16	BD180	77	BF256	66	OC28	55	2G371B	18	2N2219	22	2N3405	46	2N4293	19
AC154	22	AF186 55	BC173	16	BD186	72	BF259	94	OC29	55	2G373	19	2N2222	24	2N3415	17	2N4293	19
AC155	22	AF239 41	BC174	16	BD186	72	BF262	61	OC35	45	2G374	19	2N2221	22	2N3416	17	2N4294	19
AC156	22	AL102 72	BC175	24	BD187	77	BF263	61	OC36	55	2G377	33	2N2222	22	2N3416	31	2N4295	19
AC156	22	AL102 72	BC177	21	BD188	77	BF270	39	OC41	22	2G378	18	2N2268	19	2N3417	31	2N4296	19
AC157	27	AL103 72	BC178	21	BD189	83	BF271	33	OC42	27	2G381	18	2N2369	16	2N3525	85	2N4297	19
AC158	22	AS126 28	BC179	21	BD190	83	BF272	33	OC44	17	2G382	18	2N2369A	16	2N3526	85	2N4298	19
AC166	22	AS127 33	BC180	27	BD190	83	BF273	27	OC45	14	2G401	33	2N2411	27	2N3618	74	2N4299	19
AC167	22	AS128 28	BC181	27	BD196	94	BF274	39	OC70	11	2G411	27	2N2412	27	2N3619	74	2N4300	19
AC168	27	AS129 28	BC182	16	BD197	99	BF275	39	OC71	11	2G417	28	2N2413	27	2N3620	74	2N4301	19
AC169	16	AS150 28	BC182L	16	BD198	99	BF276	30	OC72	16	2N388	39	2N2711	23	2N3646	10	2N4302	19
AC176	22	AS151 28	BC183	16	BD199	£1.05	BF284	24	OC74	16	2N388A	61	2N2712	23	2N3702	13	2N4303	19
AC177	27	AS152 28	BC183L	16	BD199	£1.05	BF285	33	OC75	17	2N404	22	2N2714	23	2N3703	13	2N4304	19
AC178	27	AS153 28	BC184	22	BD199	£1.05	BF286	24	OC76	17	2N404A	31	2N2904	19	2N3704	14	2N4305	19
AC179	31	AS155 28	BC184L	22	BD205	88	BF287	27	OC77	28	2N404	31	2N2904A	23	2N3705	13	2N4306	19
AC180	22	AS156 28	BC186	31	BD206	88	BF288	24	OC81	17	2N404	31	2N2905	23	2N3706	13	2N4307	19
AC180K	22	AS157 28	BC187	31	BD207	£1.05	BF289	24	OC81D	17	2N404	31	2N2905A	23	2N3707	14	2N4308	19
AC181	22	AS158 28	BC207	12	BD208	£1.05	BF290	24	OC82	17	2N404	31	2N2906	17	2N3708	09	2N4309	19
AC181K	22	AS159 28	BC208	12	BDY20	£1.10	BFY52	22	OC82D	17	2N404	31	2N2906A	20	2N3709	10	2N4310	19
AC187	24	AS160 28	BC209	13	BDY20	£1.10	BFY53	19	OC83	22	2N404	31	2N2907	16	2N3710	10	2N4311	19
AC187K	25	BC101 44	BC212L	14	BF115	27	BSK19	17	OC139	22	2N404	31	2N2907A	24	2N3711	10	2N4312	19
AC188	24	BC108 9	BC213L	14	BF116	27	BSK20	17	OC140	22	2N404	31	2N2908	16	2N3712	10	2N4313	19
AC188K	25	BC109 9	BC214L	18	BF118	77	BSY25	17	OC169	28	2N404	31	2N2909	16	2N3713	10	2N4314	19
AC17	28	BC113 11	BC225	28	BF119	77	BSY26	17	OC170	28	2N404	31	2N2910	16	2N3714	10	2N4315	19
AC18	22	BC114 17	BC226	39	BF121	50	BSY27	17	OC171	28	2N404	31	2N2911	16	2N3715	10	2N4316	19
AC19	22	BC115 17	BC301	30	BF123	55	BSY28	17	OC200	28	2N404	31	2N2912	16	2N3716	10	2N4317	19
AC19	22	BC116 17	BC302	27	BF125	50	BSY29	17	OC201	31	2N404	31	2N2913	16	2N3717	10	2N4318	19
AC19	22	BC117 20	BC303	25	BF126	50	BSY30	17	OC202	31	2N404	31	2N2914	16	2N3718	10	2N4319	19
AOY22	18	BC118 11	BC304	40	BF152	61	BSY31	17	OC203	28	2N404	31	2N2915	16	2N3719	10	2N4320	19
AC127	20	BC119 33	BC440	34	BF153	50	HSY40	31	OC204	28	2N404	31	2N2916	16	2N3720	10	2N4321	19
AC28	21	BC120 38	BC460	40	BF154	50	HSY41	31	OC205	39	2N404	31	2N2917	16	2N3721	10	2N4322	19
AC29	39	BC125 13	BCY30	27	BF156	77	HSY42	31	OC206	39	2N404	31	2N2918	16	2N3722	10	2N4323	19
AC30	31	BC126 20	BCY31	29	BF156	53	HSY43	31	OC207	39	2N404	31	2N2919	16	2N3723	10	2N4324	19
AC31	31	BC132 13	BCY32	33	BF157	81	BSY95A	14	OC208	44	2N404	31	2N2920	16	2N3724	10	2N4325	19
AC32	31	BC133 20	BCY33	24	BF158	81	Bu105	20	ORP12	44	2N404	31	2N2921	16	2N3725	10	2N4326	19
AC33	23	BC134 20	BCY34	28	BF159	66	CI11E	55	ORP24	44	2N404	31	2N2922	16	2N3726	10	2N4327	19
AC34	23	BC135 13	BCY35	28	BF159	66	C400	30	ORP61	44	2N404	31	2N2923	16	2N3727	10	2N4328	19
AC35	23	BC136 13	BCY36	28	BF160	44	C401	28	P20	55	2N404	31	2N2924	16	2N3728	10	2N4329	19
AC36	31	BC137 17	BCY37	28	BF162	44	C424	28	P346A	22	2N404	31	2N2925	16	2N3729	10	2N4330	19
AC37	31	BC138 17	BCY38	28	BF163	44	C425	55	P397	46	2N404	31	2N2926	16	2N3730	10	2N4331	19
AC38	31	BC139 44	BCY39	28	BF164	44	C426	39	ST140	14	2N404	31	2N2927	16	2N3731	10	2N4332	19
AD130	42	BC141 33	BCZ11	28	BF167	24	C427	22	ST141	19	2N404	31	2N2928	16	2N3732	10	2N4333	19
AD140	53	BC142 33	BCZ12	28	BF167	24	C428	22	ST142	46	2N404	31	2N2929	16	2N3733	10	2N4334	19
AD142	53	BC143 33	BD115	28	BF178	24	C429	22	ST143	46	2N404	31	2N2930	16	2N3734	10	2N4335	19
AD143	42	BC144 50	BD116	28	BF176	39	C434	39	TIP31A	60	2N404	31	2N2931	16	2N3735	10	2N4336	19
AD149	55	BC147 11	BD121	66	BF177	39	C450	24	TIP32A	73	2N404	31	2N2932	16	2N3736	10	2N4337	19
AD161	39	BC148 11	BD123	72	BF148	33	MAT100	21	TIP41A	73	2N404	31	2N2933	16	2N3737	10	2N4338	19
AD162	39	BC149 13	BD124	76	BF179	33	MAT101	22	TIP42A	88	2N404	31	2N2934	16	2N3738	10	2N4339	19

DIODES AND RECTIFIERS

AA119	9	BY124	13	CG62	
AA120	9	BY126	16	(OA91Eq)	6
AA129	9	BY127	17	CG651	
AA130	10	BY128	17	(OA70-OA79)	
AA131	10	BY130	18	OA5	39
AA132	10	BY133	23	OA5 short	
AA133	10	BY136	23	OA5	23
AA134	10	BY138	23	OA10	15
AA135	10	BY142	24	OA47	8
AA136	10	BY145	24	OA70	8
AA137	10	BY148	24	OA79	8
AA138	10	BY151	24	OA81	8
AA139	10	BY154	24	OA85	10
AA140	10	BY157	24	OA90	7
AA141	10	BY160	24	OA91	7
AA142	10	BY163	24	OA95	8
AA143	10	BY166	24	OA98	8
AA144	10	BY169	24	OA99	7
AA145	10	BY172	24	OA99	7
AA146	10	BY175	24	OA99	7
AA147	10	BY178	24	OA99	7
AA148	10	BY181	24	OA99	7
AA149	10	BY184	24	OA99	7
AA150	10	BY187	24	OA99	7
AA151	10	BY190	24	OA99	7
AA152	10	BY193	24	OA99	7

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed
Pak No. EQVT
T1 8 2G3713 OC71
T2 8 D1374 OC75
T3 8 D1218 AF11D
T4 8 2G381T OC81
T5 8 2G382T OC82
T6 8 2G344B OC44
T7 8 2G345B OC45
T8 8 2G378 OC78
T9 8 2G399A 2N1302
T10 8 2G417 AF117
All 54p each pak

ND120 NIXIE DRIVER TRANSISTOR.
Suitable replacement for BSX21, CA07, 2N1893 120vdb.
0-19 0-25 100+
0-19 0-17 0-16

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqv. ZTX300 6p each. Any Quantity.

GP100 TO3 METAL CASE GERMANIUM
V_{be}=80V. V_{ceo}=60V. I.C.=10 amps. P_{tot}=30W. h_{fe}=30-170.
Replaces the majority of Germanium power transistors in the OC, AD and NKT range.
1 85 100+
0-48 0-44 0-40

GP300 TO3 METAL CASE SILICON
V_{be}=100V. V_{ceo}=60V I.C.=15 amps. P_{tot}=115W. h_{fe}=20-100T=1MHz. Suitable replacement for 2N3055, BDY11 or BDY20.
1 25 100+
0-55 0-53 0-51

NEW 8th EDITION
250 pages
TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK, £1.85 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18
81M. TO 2N708/8. BSX-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N3906, BCY70. When ordering please state preference NPN or PNP.
20 For 0-54
50 For 1-08
100 For 1-92
500 For 8-25
1000 For 14-30

SIL. G.P. DIODES 5p
300mV 30 0-55
401V(Min.) 100 1-65
Sub-Min. 500 5-50
Full Tested 1,000 9-80
Ideal for Organ Builders.

ADI61/162
M/P COMP. GERM. TRANS. OUR LOW-EST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO AND ELECTRONIC COMPONENTS ADVERTISEMENTS

PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-30V. 400mV (DO-7 Case) 9p ea. 11W (Top-Hat) 18p ea. 10W (80-10 Stud) 32p ea.

QUALITY TESTED SEMICONDUCTORS	Pak No.	Price 5p
Q 1 20 Red spot transistors pnp	Q 1	0-54
Q 2 16 White spot R.F. transistors pnp	Q 2	0-54
Q 3 4 OC77 type transistors	Q 3	0-54
Q 4 6 Matched transistors OC44/45/81/81D	Q 4	0-54
Q 5 4 OC75 transistors	Q 5	0-54
Q 6 5 OC72 transistors	Q 6	0-54
Q 7 4 AC128 transistors pnp high gain	Q 7	0-54
Q 8 4 AC126 transistors pnp	Q 8	0-54
Q 9 7 OC81 type transistors	Q 9	0-54
Q 10 7 OC71 type transistors	Q 10	0-54
Q 11 2 AC127/128 Complementary pairs pnp/pnp	Q 11	0-54
Q 12 3 AF116 type transistors	Q 12	0-54
Q 13 3 AF117 type transistors	Q 13	0-54
Q 14 3 OC171 H.F. type transistors	Q 14	0-54
Q 15 7 2N2926 Sil. Epoxy transistors mixed colours	Q 15	0-54
Q 17 5 pnp 2 x ST.141 & 3 x ST.140	Q 17	0-54
Q 18 4 MADDT*2 x MAT 100 & 2 x MAT 120.	Q 18	0-54
Q 19 3 MADDT*2 x MAT 101 & 2 x MAT 121.	Q 19	0-54
Q 20 4 OC44 Germanium transistors A.F.	Q 20	0-54
Q 21 4 AC127 pnp Germanium transistors	Q 21	0-54
Q 22 20 NKT transistors A.F. R.F. coded	Q 22	0-54
Q 23 10 OA202 Silicon diodes sub-min.	Q 23	0-54
Q 24 8 OA81 diodes.	Q 24	0-54
Q 25 15 IN914 Silicon diodes 75PIV 75mA	Q 25	0-54
Q 26 8 OA95 Germanium diodes sub-min IN69	Q 26	0-54
Q 27 2 10A 000 PIV Silicon rectifiers IS426R	Q 27	0-54
Q 28 2 Silicon power rectifiers BYZ13	Q 28	0-54
Q 29 4 Silicon transistors 2 x 2N695, 1 x 2N697, 1 x 2N698	Q 29	0-54
Q 30 7 Silicon switch transistors 2N706 pnp	Q 30	0-54
Q 31 6 Silicon switch transistors 2N708, npn	Q 31	0-54
Q 32 3 pnp Silicon transistors 2 x 2N1131, 1 x 2N1132	Q 32	0-54
Q 33 3 Silicon nnp transistors 2N1711	Q 33	0-54
Q 34 7 Silicon nnp transistors 2N2369, 300MHz (code P397)	Q 34	0-54
Q 35 3 Silicon pnp TO-5, 2 x 2N2904 & 1 x 2N2905	Q 35	0-54
Q 36 7 2N3646 TO-18 plastic 300MHz nnp	Q 36	0-54
Q 37 3 2N3053 nnp Silicon transistors	Q 37	0-54
Q 38 5 pnp transistors 3 x 2N3703, 2 x 2N3702	Q 38	0-54

555IC 65p each

ALL PRICES INCLUDE V.A.T.

MAMMOTH I.C. PAK

APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS' FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS. MANY CODED also SOME UNKNOWN TYPES—YOU TO IDENTIFY.

PAK NO. M.I.C. 200

PRICE £1.25 per PAK including P. & P. and VAT

INTEGRATED CIRCUIT PAKS

Manufacturers' "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0-54	UIC46	= 3 x 7446	0-54	UIC96	= 5 x 7496	0-54
UIC01	= 12 x 7401	0-54	UIC48	= 6 x 7448	0-54	UIC98	= 5 x 7498	0-54
UIC02	= 12 x 7402	0-54	UIC50	= 12 x 7450	0-54	UIC91	= 5 x 7491	0-54
UIC03	= 12 x 7403	0-54	UIC51	= 12 x 7451	0-54	UIC92	= 5 x 7492	0-54
UIC04	= 12 x 7404	0-54	UIC53	= 12 x 7453	0-54	UIC93	= 5 x 7493	0-54
UIC05	= 12 x 7405	0-54	UIC54	= 12 x 7454	0-54	UIC94	= 5 x 7494	0-54
UIC06	= 8 x 7406	0-54	UIC56	= 12 x 7456	0-54	UIC95	= 5 x 7495	0-54
UIC07	= 8 x 7407	0-54	UIC60	= 12 x 7460	0-54	UIC96	= 5 x 7496	0-54
UIC10	= 12 x 7410	0-54	UIC70	= 8 x 7470	0-54	UIC100	= 5 x 74100	0-54
UIC20	= 12 x 7420	0-54	UIC72	= 8 x 7472	0-54	UIC121	= 5 x 74121	0-54
UIC30	= 12 x 7430	0-54	UIC73	= 8 x 7473	0-54	UIC141	= 5 x 74141	0-54
UIC40	= 12 x 7440	0-54	UIC74	= 8 x 7474	0-54	UIC151	= 5 x 74151	0-54
UIC41	= 5 x 7441	0-54	UIC76	= 8 x 7476	0-54	UIC154	= 8 x 74154	0-54
UIC42	= 5 x 7442	0-54	UIC80	= 5 x 7480	0-54	UIC193	= 5 x 74193	0-54
UIC43	= 5 x 7443	0-54	UIC81	= 5 x 7481	0-54	UIC199	= 5 x 74199	0-54
UIC44	= 5 x 7444	0-54	UIC82	= 5 x 7482	0-54	UICXI	= 25 Assorted	
UIC45	= 5 x 7445	0-54	UIC83	= 5 x 7483	0-54			

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UICX1.

1975 CATALOGUE NOW READY 10p

NEW LOW PRICED TESTED S.C.R.'S

PIV	50	100	200	400	600	800
	5p	5p	5p	5p	5p	5p
1A TO5	0-22	0-27	0-32	0-32	0-42	0-63
3A TO66	0-27	0-27	0-32	0-42	0-52	0-70
5A TO66	0-38	0-52	0-54	0-59	0-75	0-88
7A TO48	0-52	0-55	0-82	0-87	0-84	0-99
10A TO48	0-55	0-63	0-67	0-83	1-07	1-32
16A TO48	0-58	0-62	0-67	0-77	0-97	1-50
30A TO48	1-27	1-54	1-76	1-93	—	4-40

2N3055

115 WATT SIL POWER NPN 45p EACH

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-54
U 2	60 Mixed Germanium Transistors AF/RF	0-54
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-54
U 4	40 Germanium Transistors like OC81, AC128	0-54
U 5	60 200mA Sub-Min. Silicon Diodes	0-54
U 6	30 Sil. Planar Trans. NPN like BS95A, 2N706	0-54
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0-54
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-54
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-54
U 10	20 BAY50 charge storage Diodes DO-7 Glass	0-54
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-54
U 13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0-54
U 14	150 Mixed Silicon and Germanium Diodes	0-54
U 15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-54
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-54
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-54
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-54
U 19	25 Silicon NPN Transistors like BC108	0-54
U 20	12 1 3 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-54
U 21	30 AF. Germanium Alloy Transistors 2F300 Series & OC71	0-54
U 23	30 MADDT's like MHz Series PNP Transistors	0-54
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-54
U 25	25 300MHz NPN Silicon Transistors 2N708, BSY27	0-54
U 26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-54
U 29	10 1 Amp SCR's TO-5 can, up to 600 PIV BR51/25-600	1-08
U 32	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0-54
U 33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-54
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0-54
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-54
U 36	25 Silicon Planar NPN Transistors TO-5 BEY50/51/52	0-54
U 37	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0-54
U 38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0-54
U 39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0-54
U 40	10 Dual Transistors 6 lead TO-5 2N2060	0-54
U 43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-54
U 44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-54
U 45	7 3A SCR. TO66 up to 600PIV	1-08
U 46	20 Unijunction transistors similar to TIS43	0-54
U 47	10 TO220AB plastic triacs 50V 6A	1-08
U 48	9 NPN Sil. power transistors like 2N3055	1-08
U 49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	1-08

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE

One 55p Pak of your own choice free with orders valued £4.00 or over

CADMIUM CELLS

ORP12 48p

SIL. RECTS. TESTED

PIV 300mA 750mA 1A 1.5A 3A 10A 30A (DO7)(8016) Plastic (8016) (8010) (8010) (TO48)

P	P	P	P	P	P	P		
100	05	06	1N4001	05	08	15	21	60
100	05	07	1N4002	06	10	17	23	75
200	06	10	1N4003	07	12	22	25	1-00
400	08	15	1N4004	08	15	30	38	1-35
600	09	17	1N4005	10	18	36	45	1-90
800	12	19	1N4006	11	20	38	55	2-10
1000	14	30	1N4007	12	25	48	65	2-50
1200	—	35	—	—	—	58	75	3-00

DIACS

FOR USE WITH TRIACS.

BR100 (D32) 25p each

10 amp POTTED BRIDGE RECTIFIER on heat sink.

100PIV. 99p each

TRIACS

VBOM 2A 6A 10A TO-5 TO-66 TO-48

p p p

100V 33 55 88

200V 55 88 99

400V 77 83 1-21

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 15p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back



TRAMPUS ELECTRONICS LTD

58-60 GROVE ROAD,
WINDSOR, BERKS.

FAST SERVICE.

SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.

CATALOGUE/LIST FREE SEND S.A.E.

Digital Displays



MINITRON 3015F
O-9DP £1.15 ea
LED 0.3" digit
O-9DP £1.49 ea
JUMBO LED 0.6"
O-9DP £2.25 ea
LIQUID CRYSTAL
6 digit £18

LEDS 14P.

MINI PIN SOURCE OR RED DIFFUSE
LEDS. 209 STYLE. NO CLIP. 14P ea
TIL209 RED LED & CLIP 17P ea
BIG 1" RED LED & CLIP 18P ea
ORANGE & GREEN LEDS:
MINI 25P ea. BIG & CLIP 33P ea
INFRA RED LED £1.2N5777 33P.
PS12 PHOTO IC/amp/switch £1.

DIGITAL CLOCK

MOS INTEGRATED CIRCUITS.
AYS1224 4 DIGIT CLOCK supplied
with 14pin socket & data £4.25
MMS311/14 6 DIGIT CLOCK with
28 pin socket & data £7.50
3j DIGIT DVM AY53500 £7.50
4DIGIT COUNTER/DRIVER £7.50

CASSETTE mechanics £12-50

STEREO CASSETTE MECHANISM.
As used in imported types
costing £100. Only requires
a case & electronics. Heads
supplied. Send for data 15p.

IC's & Semiconductors

702 OPA 69p
703 RF/IF 28p
709 7099 21p
709 DIL 14 29p
710 DIL 14 36p
720 Radio £1.39
723 Regulator 67p
741 T099 29p
741 D118 31p
741 D1L14 31p
747 Dual 741 89p
748 DIL 8 36p
1505 IC A/D
Converter £7
7805 1ASV £1.59
7808 1A8V £1.69
7812 1A12V £1.69
7815 1A15V £1.69
76009 1W AF 75p
8013 6W AF £1.39
8038 Sig Gen £3
CA3046 69p
LM301 OPA 49p
LM307 OPA 49p
LM308 HiPoPa 95p
LM309K Reg. £2.29
LM371 RF/IF £2
LM372N AF/IF £2
LM375 £3
LM380 2W AF 99p
LM381 2xpr. £2
LM382 amp £2
LM3900 4xOPA 69p
MCI1303 £1.20
MCI1306 49p
MCI1310 & LED £2.69
MCI1312 SQuamp £2.50
MCI1330 69p
MCI1339 £1
MCI1350 55p
MCI1351 71p
MCI1352 71p
MCI1357 £1
MCI1358 £1
MCI1375 £1.25
MFC4000 1W AF 35p
MFC4060 54p
MFC6030 52p
MFC6040 90p
MFC8010 £1.10
MFC8040 £1
NE531 35V/us £2
NE536 FET OPA £2
NE540 Driver £1
NE546 AM Rxf1.50
NE550 2v ref 79p
NE555 TIMER 67p
NE556 Dual £1.30
NE560 PLL £3.15
NE561 PLL £3.15
NE562 PLL £3.19
NE565 PLL £2.69
NE566 Gen £2.49
NE567 code £2.69
SN72709 709 29p
SN72741 741 31p
SN72748 748 36p
SN76131 £1.20
SN76660 FMIF £1
SN76611 IF £1.25
TAD low & IF £2
ZN400E £3
ZN402T £1.75
ZN405 Servo £2.50
ZN414 AM Rxf1.09
7400 etc gates 16p
7415 schmitt 31p
7447 driver £1.09
7470/72 32p
7475/74/76 39p
7475 48p
7490 Counter 63p
7492 Counter 69p
74121 mono 45p
74141 driver 83p
Full range in Cat.

SPECIAL OFFERS

741 29p MFC4009 35p
555 67p ZN414 11.09
BC107, BC108, BC109 9p ea
2N3055 39p Three for £1
115W/T03 or 90W plastic
2N3819E 16p 2N3053 17p
BFY50/51/52/53 all 18p
IASOVrect 4p ea IN914 4p

Price each:-

AC127/128 16p
AC187/188 19p
AD161/162 35p
BC107/8/9 9p
BC132/4/7 18p
BC147/8/9 10p
BC157/8/9 12p
BC167/8/9 12p
BC177/8/9 18p
BC182/3/4 11p
BC212/3/4 12p
*A or L
BCY70/1/2 15p
BD131/2 39p
BFY50/1/2 18p
BFY53 17p
BSX20 12p
MJE2955 95p
MJE3055 62p
MPU151put 42p
OAP1 8p
TIP29A 48p
TIP30A 57p
TIP31A 61p
TIP32A 73p
TIP41A 78p
TIP42A 89p
BZY88 400mW
ZENERs 9p
BRIDGE RECT
1A 50V 20p
GAS SENSOR £2
GAS " KIT £5
TIP2955 90p
TIP3055 55p
TIS43 UJT 25p
IN4001 4p
IN4004 6p
IN4148/914 4p
2N697 13p
2N706/8 10p
2N2646 49p
2N2904/5 20p
2N2926toys 9p
2N3053 17p
2N3055 39p
2N3614 49p
2N3702/3 9p
2N3704/5 10p
2N3706/7 9p
2N3708/9 8p
2N3710/11 9p
2N3563/64 16p
2N3566/67 16p
2N3658 16p
2N3641/2 16p
2N3819E 16p
2N3832E 17p
2N3904/6 14p
2N4249 16p
TAG 1/400 55p
C107D1 SCR
4A/400V 55p
SC146D TRIAC
10A 400V 75p

vero

VERO PINSx36 25p.
COPPER CLAD VEROBOARD 0.1"
21x5" 27p. 21x31" 24p. 31x31" 27p.
31x5" 29p. 31x17" £1.50
DIL IC's BOARDS 6x4" £1.50
24 way edge connector 60p
36way 90p. PLAIN 31x17 £1
FACE CUTTER 43p. FEC ETCHING

DALopen69p

PRINTED CIRCUIT BOARD KIT £1.69
COPPER BOARD 6x4" 40p
DESOLDER BRAID reel 59p
HEATSINKS
5E/T05 & 18E/T018 5p ea.
TV4 12p. TV3/T03 16p. 4Y1/T03 29p.
CAPACITORS
22pF to 0.1uf 4p ea. ELECTROLYTIC
25V 210/50/100uf 6p. 1000uf 10p
PRESETS VERT: 5p. RESISTORS 5p 11p

POTS AB or EGIN

ROTARY: 12p. SWITCH 13p. DUAL 38p.
SLIDERS: SINGLE 26p. DOUBLE 48p.
SWITCHES: SPST 18p. DPDT 25p.
MINI 1": SPST 39p. PUSH 39p.
BENCH POWER SUPPLY 3-12V £5.
DIN PLUGS all 13p ea. Sockets 9p
TRANSFORMERS 1A 6/12V £1.34
BHA 0002 MODULE 15WATT AMP £5
EA1000 4W AF MODULE £2.49
8W/12V FLUORESCENT LIGHT £3.

Oil sockets

PROFESSIONAL
GOLD PLATED
& GREY NYLON.
8, 14 or 16 PIN
ONLY 15p each.

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept. EB25, P.O. BOX 156, JERSEY

NAME: _____

ADDRESS: _____

BLOCK CAPS please

MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/volt High Sensitivity Meter
£14.40. 20p P. & P.

TAPE RECORDER LEVEL METER
500µA, 70p. 5p P. & P.

CARDIOID DYNAMIC MICROPHONE
Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £6.55. 11p P. & P.

3 WATT STEREO AMPLIFIER
£4.30. 10p P. & P.

4 1/2in x 3 1/2in METER. 30µA, 50µA or 100µA, £3.85. 11p P. & P.

MULTI-METER Model D62
20,000 ohm/volt, £7.65. 15p P. & P.

All above prices include 8% V.A.T. LARGE S.A.E. for List No. 10. Special prices for quantity quoted on request.

M. DZIUBAS
158 Bradshawgate • Bolton • Lancs. BL2 1BA



*COME AND JOIN THE ELECTRONIC ENTHUSIASTS CLUB!



240 pages
Over 6,000 items
Nearly 2,000 pictures

65p plus 33p POST AND PACKING

Send off the coupon today. It's your first step to solving your component buying problems.

The price of 98p applies only to customers in the U.K. and to B.F.P.O. addresses

I've been dealing with Home Radio Components for a number of years and I've never felt I was a *customer*; rather that I'd joined a bunch of enthusiasts who were out to help me every way they could. This shows itself in many ways. Take their catalogue for instance. Several pages are taken up with information such as useful formulae, how to choose a microphone, the meaning of conventional signs, resistor and capacitor codes. Every page in that catalogue must cost them a great deal of money, and these things can't show them a direct return. On the other hand it does show that they care! There is a whole page telling you the best way to order, plus carefully worked out order forms, and two pages showing how you can open a credit account. Then there is their philosophy with the catalogue. They are anxious that the good customer will get it for the minimum price, so they include 14 coupons each worth 5p if used as directed. Don't take my word for it, try it for yourself, join the merry band! Membership is automatic, once you buy a catalogue. Send off for it to day. It costs 65p plus 33p postage and packing but with the coupons you can get back 70p—the whole cost of the catalogue plus 5p towards the postage. Complete the coupon below and send it to the address shown, with your cheque or P.O. for 98p.

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. PE,
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No
912966 London

A HEALTHY MARKET

IN home constructor circles the component supply position has been a major bone of contention on many occasions in the past. It is pleasing, therefore, to comment upon the greatly improved situation we are currently enjoying. Part of this general improvement in the market is due to additional retail outlets which have come into existence to serve the private constructor. In recent times more industrial distributors have taken a close and quizzical look at the home constructor field; some, certainly, have liked what they have seen and have decided to extend their operations into this market, either through an extension of their existing business organisations, or through new companies launched to deal exclusively with small-order business.

Maybe the potential trade offered by the amateur market has assumed greater importance because the industrial business, on the other hand, has lost some of its former buoyancy under present difficult economic conditions. Cynics may indeed see this as the main reason for this late conversion of some suppliers to the home constructor market. But the cause matters infinitely less than the effect produced. All conversions are very welcome and we hope more will follow.

Whatever may in fact be the state of the industrial market, it is obvious that many component distributors have at last realised that the home constructor market represents rather more than peanuts. No sensible business man can afford to turn a blind eye to an area which still shows continuing growth during what is freely admitted to be a gloomy and rather stagnant period in trading affairs. So what could be more natural than a redirection of some of the accumulated components, especially the latest semiconductor devices, towards a market where demand persists and looks like growing even more.

As well as the opening up of additional retail outlets, significant changes have come about in the kind of components now made available to the amateur, both by the long established suppliers of this market, and the newcomers. Circuit modules, for example, originally intended for the exclusive use of set manufacturers have for some time now been featured in the advertisements and catalogues of component retailers. The range of i.c.'s listed has expanded, and devices which a few years ago would have been considered "too advanced" for the amateur are now commonplace lines.

This emancipation of components owes much to the revelation of their existence through designs published in magazines such as P.E. The brusque statement "not available to the amateur market" was frequently heard in the past from sales executives of some of the larger and important component makers. This discouraging and rather haughty kind of utterance is not so commonplace today, we are delighted to say.

F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

THE INCREASING interest in water sports, particularly sailing and power-boating, being shown these days has resulted in the development of a number of electronic devices for the boat owner. Not least amongst these is the marine speedometer with analogue readout, similar to the familiar car speedometer.

Such an instrument gives an immediate indication of the speed of water past the hull of a boat and is of use in both power and sail work for tuning and performance observations.

THE SYSTEM

In basis, a marine speedometer is made up of two parts, a transducer capable of sensing the speed of the water past the hull and a converter which changes the transducer signal into a visual indication of this speed.

Various methods have been used to sense the relative speed, including propellers, water wheels and even wands forced back against spring action. Of these the propeller type is generally favourite for a variety of reasons and the present case makes use of a commercially available skeg-mounted propeller unit manufactured by E.M.I. and readily available as a spare for the Emilog.

The pick-up system is shown in Fig. 1 from which it will be seen that the skeg mounting takes the propeller away from the hull of the boat. Whilst the distance is in fact small, only a matter of inches overall projection, it is sufficient to avoid problems due to "skin effect" adjacent to the hull where the water flow is not indicative of boat speed.

The transducer design is simple and thus reliable. A small magnet is cast in the hub of the propeller and the variation in magnetic field caused as this rotates is detected by the coil mounted inside the hull. Assuming a non-magnetic hull, this of course gives a distinct advantage to this system since the


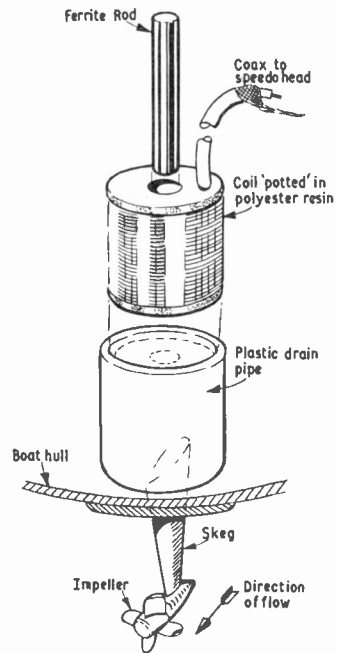


Fig. 1. The speedometer skeg and pick-up system

hull need not be broken at all, the skeg being mounted on the outside whilst the coil is located inboard.

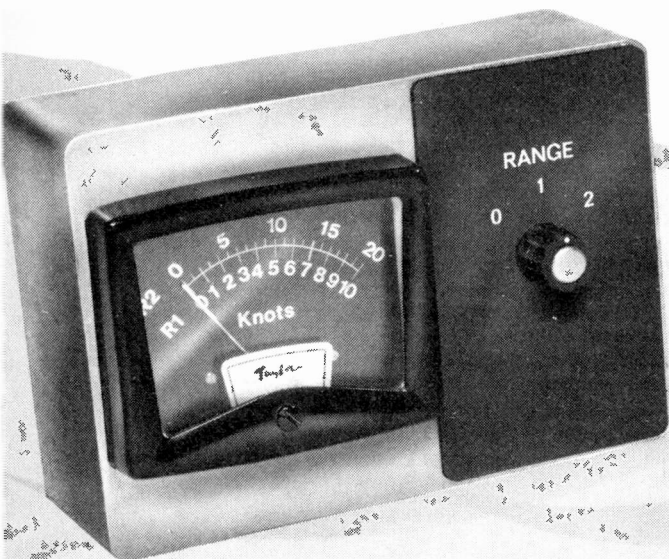The rate of pulses from the coil alters in a fairly linear fashion with the boat speed and thus it is possible to carry out calibration of the electronics and indicator on the bench if required. Of course, a final check over measured distances and times would be needed for optimum accuracy.



MARINE

PICKUP COIL

The coil is basically very simple, consisting of around 28g or 1oz of 40 s.w.g. copper wire wound round a 2in length of $\frac{1}{4}$ in ferrite rod. The finished coil can be potted in epoxy resin in a former made up from a 2in length of 1in diameter plastic drain pipe. In this way the unit is fully protected against the vagaries of boat bilge environments.

It is advisable to use co-ax for the lead to the indicator head as the signal from the coil is small ($\approx 150\text{mV}$ at 7 knots) and the input to the indicator sensitive.

The potting operation is fairly simple and should not require too much resin. Probably about 1oz of Araldite will suffice. As this is normally fairly stiff in consistency it is suggested that the tubes be warmed gently before use and, if still rather stiff, a few drops of methylated spirit will help the flow if mixed in during the 2-part mixing stage.

After casting, the setting process can be accelerated if this is allowed to take place in a warm environment and should take about 20 minutes to reach firmness. Twenty-four hours is required for real hardness.

Fig. 2 shows the circuit diagram of the electronics for the speedometer. The very small signal from the pickup coil is amplified by the operational amplifier IC1 and then fed to a Schmitt trigger TR1, TR2. This latter provides a square wave output with a fast rise time which is used to drive a monostable, TR3, TR4 which provides a chain of pulses of constant length and a repetition rate equal to the rotation rate of the propeller.

Finally, the pulse chain is fed to an output amplifier TR5 which drives an indicating meter ME1.

Ranges of 0 to 10 and 0 to 20 knots are obtained by selecting VR2 or VR3, R17, and S1 (not shown). S1 can be part of S2, giving off, range 1 and range 2 positions.

COMPONENTS . . .

Resistors

R1	1.5k Ω	R9	5.6k Ω
R2	12k Ω	R10	4.7k Ω
R3	3.3M Ω	R11	10k Ω
R4	3.3k Ω	R12	6.8k Ω
R5	33 Ω	R13	8.2k Ω
R6	2.7k Ω	R14	10k Ω
R7	12k Ω	R15	3.3k Ω
R8	1.5k Ω	R16	3.3k Ω
R17	390 Ω		

All $\frac{1}{4}$ W 5%

Capacitors

C1	15 μ F, 40VW elect.
C2	10nF, 160VW polyester
C3	0.22 μ F, 250VW polyester
C4	68 μ F, 16VW elect.

Potentiometers

VR1	2.2k Ω skeleton preset, 0.1in matrix
VR2, 3	470 Ω skeleton preset, 0.1in matrix (2 off)

Semiconductors

IC1	SN72741 (741 operational amplifier)
TR1 to 4	BC113 (4 off)
TR5	BC108
TR6	BFY51
TR7	2N1305
D1, 2	BZY88 C6V2 (2 off)

Miscellaneous

Material for pick-up coil, wire, 2in ferrite rod, Araldite etc.: Emilog impeller: suitable case or housing, preferably plastic: Veroboard, 0.1in matrix: Co-ax cable and plug/socket: 2 batteries, PP3 or PP6, 9V or alternately 2 \times 1k Ω , 1W resistors: 1mA meter suitably rescaled: S1, SPCO and S2, DPCO.



SPEEDOMETER *By C. GAMMONS*


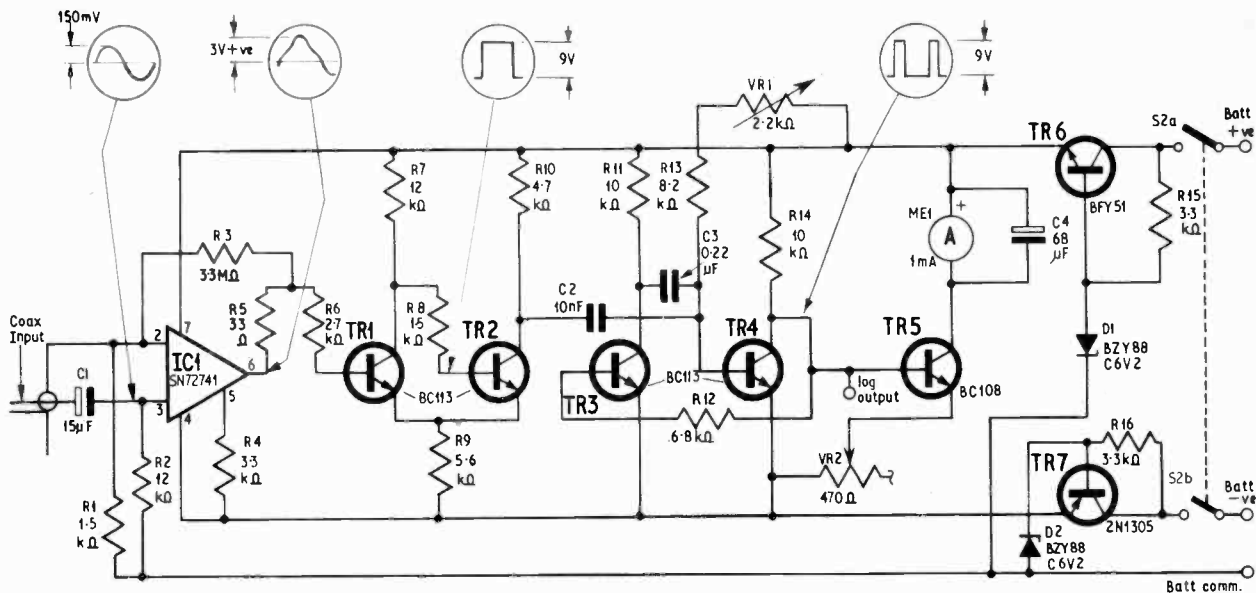


Fig. 2. Circuit diagram of the marine speedometer showing range switching

POWER SUPPLY

In the prototype the unit was powered by two PP6, 9V dry batteries, the input rails being stabilised using TR6, TR7, D1 and D2. The stabilisation circuitry should be retained with all forms of power supply for optimum results though the dry batteries may be replaced by the boat supply or some other source.

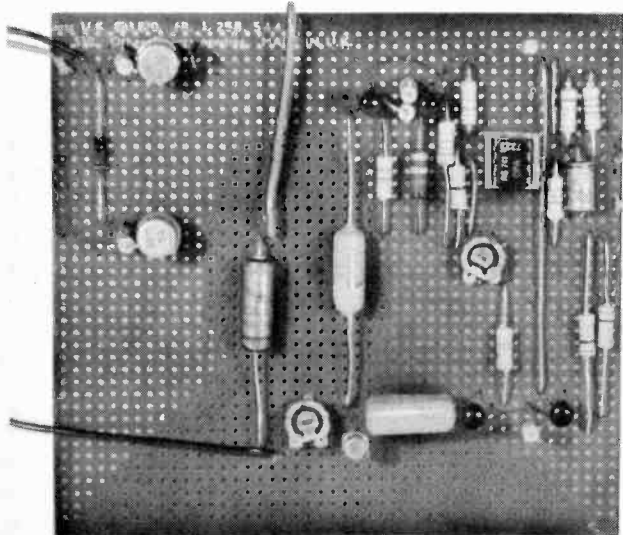Of course, if a 12V boat supply is used it will need to be wired to give 6, 0, 6V, just as a 24V supply would be tapped to give 12, 0, 12V if this is used. In fact the centre tap can be supplied by putting two, 1kΩ 1W resistors across the full supply in series and connecting 0V to the centre point thus formed.



Veroboard component layout for the marine speedometer

CONSTRUCTION

A Veroboard cutting and component layout diagram is shown in Fig. 3. Assembly follows normal practice and it is recommended that a holder be used for the i.c.

After assembly, the completed card can be tested by connecting suitable batteries or a bench supply and feeding about 215mV of 50Hz audio signal from an a.f. oscillator (or indeed a small mains transformer with a suitable attenuator network on the output) to the input.

With such an input the meter deflection should be between $\frac{1}{4}$ and f.s.d. It should be adjusted to give a reading of $\frac{1}{4}$ f.s.d. by suitably altering VR1. In the present circuit VR2 is set to mid-position.

An alternative method of supplying the 50Hz signal is to use the pickup coil itself. This is placed next to a mains transformer so that current is induced in the coil and this in turn is used to drive the indicator circuitry.

In this way both the coil and the electronics are tested at one time although one has to be careful with respective positioning of coil and transformer due to the presence of 100Hz pickup at certain distances.

If the circuit proves to be impossible to calibrate then a wiring and full circuit check is in order and it is recommended that a reasonable 20kΩ/V meter be used for this.

The final step in calibration involves the meter scale markings. If the meter carries a 0 to 10 or 0 to 100 scale then this will suit as it stands for a 0 to 10 knot scale. If the basic scale needs alteration then the scale plate should be carefully removed from the instrument and the unneeded numerals removed with an abrasive rubber, Vim or some similar gentle compound. If care is taken the face will not be damaged and the new figures and lettering required can be put on using pressure-adhesive lettering such as Letraset.

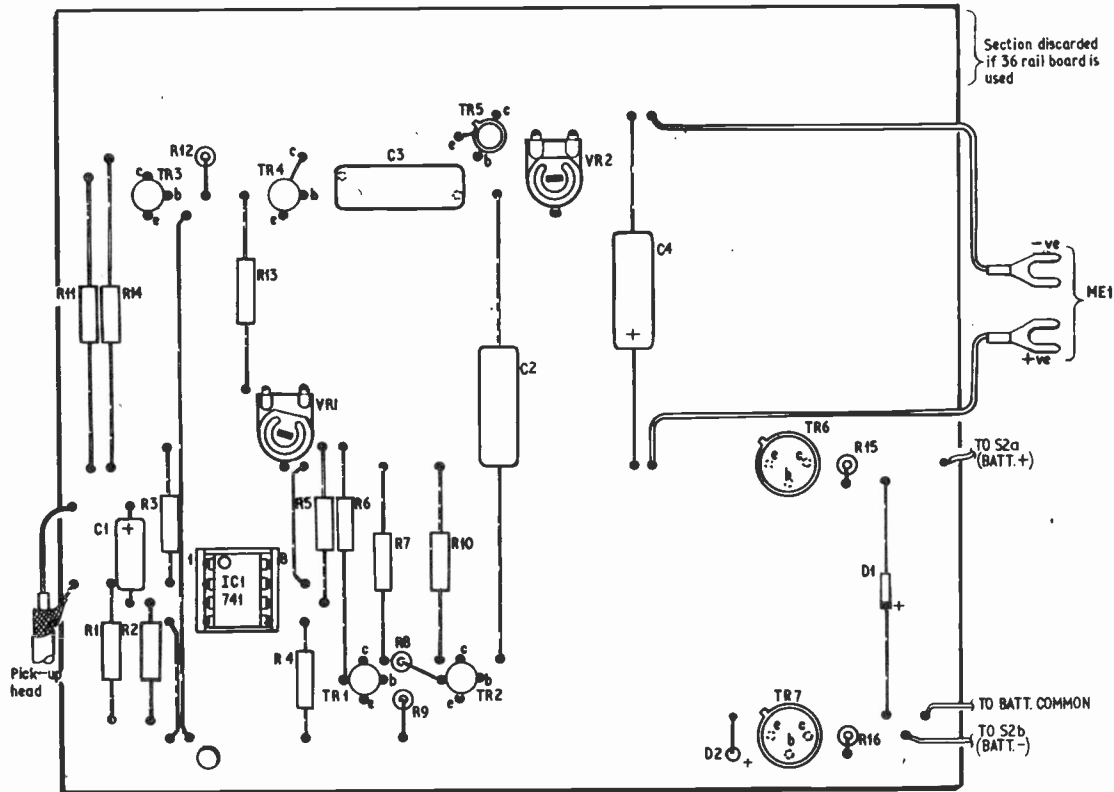


Fig. 3. Veroboard cutting and component layout for the marine speedometer of Fig. 2

The illustration of a prototype meter shows how both scales and an associated range switch may be arranged in a die-cast box.

HOUSING

There are a number of alternative methods of housing, extending from the die-cast box to some

rather well-made plastic cases now available. In any case, the housing chosen should be capable of protecting the circuit board from the usually unfriendly environment of a boat.

The Emilog impeller unit can be obtained from EMI agent chandlers but in the event of difficulty contact:—EMI Marine, Cramptons Road, Sevenoaks, Kent. ★



ATTENTION MUSIC LOVERS!

PE JOANNA

*This new piano will be demonstrated at the next meeting of the Electronic Organ Constructors Society**

2.30 p.m., SATURDAY, FEBRUARY 15

at St. DAVID'S CHURCH HALL, Lough Road, London, N.7
(Five minutes walk from Caledonian Road Tube Station—Piccadilly Line)

* The E.O.C.S. has extended an invitation to P.E. readers to attend this preview of our next exciting project

FOR SCINTILLATING SOUND



PE ORION

HI-FI STEREO AMPLIFIER

By D.S. GIBBS & I.M. SHAW* C.Eng., M.I.E.E.

THIS month full constructional detail for the Orion will be given together with test and fault finding procedures.

COMPONENTS

An effort has been made to use standard, easily obtainable components as far as possible, most of which can be obtained through firms advertising in this magazine.

Components which require special attention are the 0.33 ohm wirewound resistors. These should be low inductance types such as the 0.33 ohm, 2.5W from R.S. Components, the Welwyn W21 3W or C.G.S. C3A 3W. No other types should be used.

CONSTRUCTION

It is best to start by assembling the printed circuit board. The layout of this is shown in Fig. 2.1. The three push-button switches should be mounted first, followed by all the resistors and capacitors. Take care with the polarity of the electrolytic and tantalum bead types. Some tantalum capacitors are now marked with the polarity, but the colour coded type are not. The polarity of these can be deduced from Fig. 2.2.

All the semiconductors can now be soldered in place. Take care to connect the E-Line transistors the right way round.

The four fixing screws for the output transistors must be nylon, and these screws also hold the heatsink to the board. The heatsink is a six inch length of heavy gauge $1\text{in} \times 1\text{in} \times \frac{1}{8}\text{in}$ aluminium angle. Mica washers should be used under all the output transistors and a thin smear of silicone grease or heatsink compound is beneficial in reducing the thermal resistance.

The bias transistors TR7 and TR107 are held

down on to the heatsink by 6BA screws and a thin strip of metal to give good thermal contact. Care should be taken not to overtighten these screws or damage to the transistors may result. The screws should be just sufficiently tight to hold the bias transistors firmly against the heatsink, and can be locked with a blob of paint if desired. A small smear of silicone grease under the bias transistor helps in achieving good thermal contact.

Finally, all the connecting wires required should be soldered into the board, and the board checked carefully for mistakes and for solder "bridges" between adjacent tracks.

DRILLING

The main chassis should be drilled as shown in Fig. 2.3 and all the holes carefully deburred. Take special care with the three holes for the push-button switches as these need to be accurately placed and will remain visible after assembly. Errors or careless drilling will spoil the appearance of the finished amplifier.

A slight modification is necessary for the four DIN input sockets to be fitted to the back of the case. The left hand side of both the back panel and the back of the cover are removed and the hole created is filled with a 2in wide strip of aluminium sheet. This strip is clamped between the heatsink and the back of the case of the amplifier (Fig. 2.5).

LABELLING

If the drilling has been done carefully it may be possible to label the panels without any further preparation, but if scratches have appeared these should be removed by rubbing lightly with wire wool lubricated with soap and water. Rub in one direction along the length of the front and back panels until all the scratches have been removed.

The panel should then be dried and given one thin coat of protective lacquer, such as Letraset 101

* Ferranti Ltd.

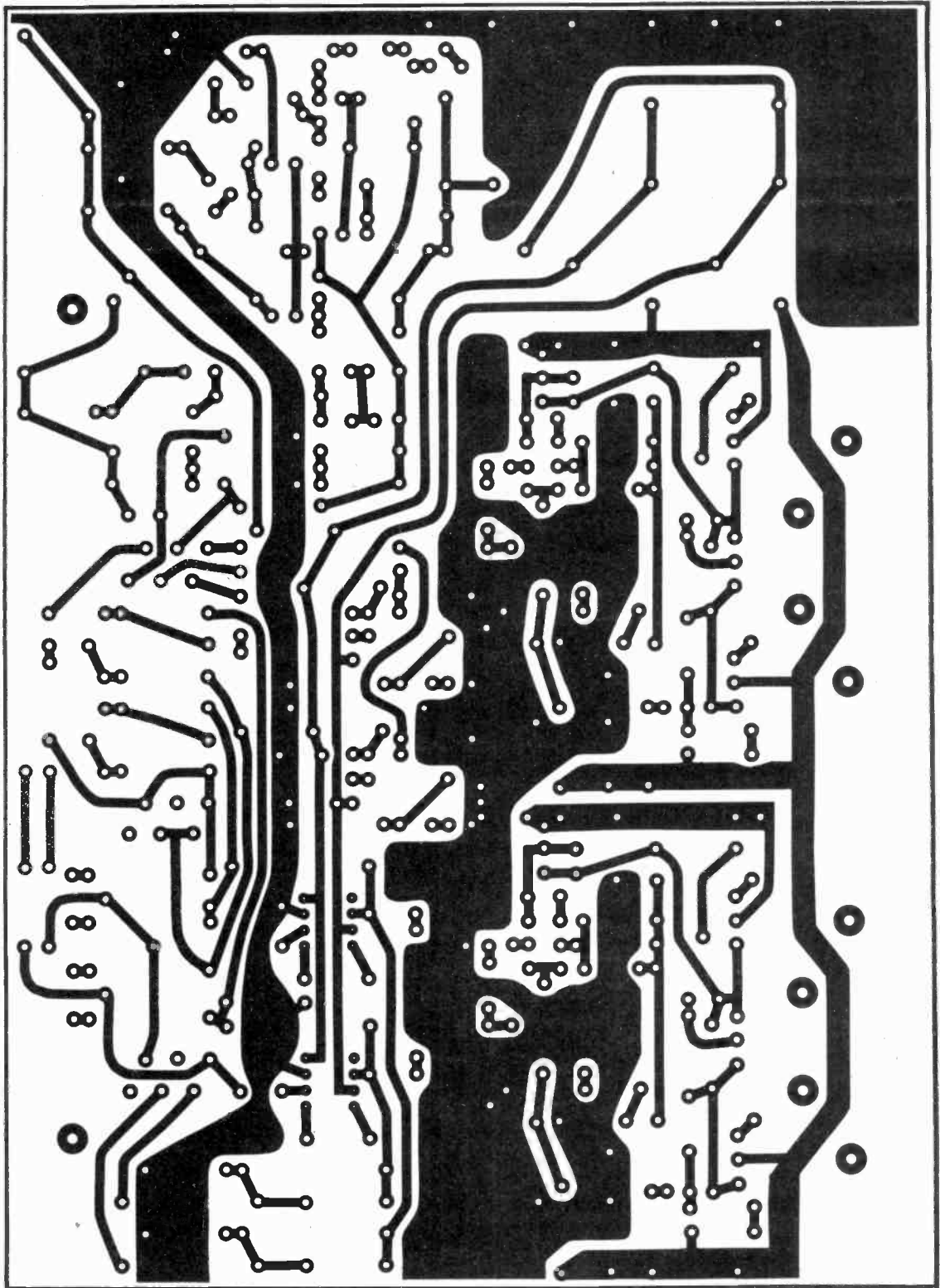


Fig. 2.1. Same size layout of printed circuit board

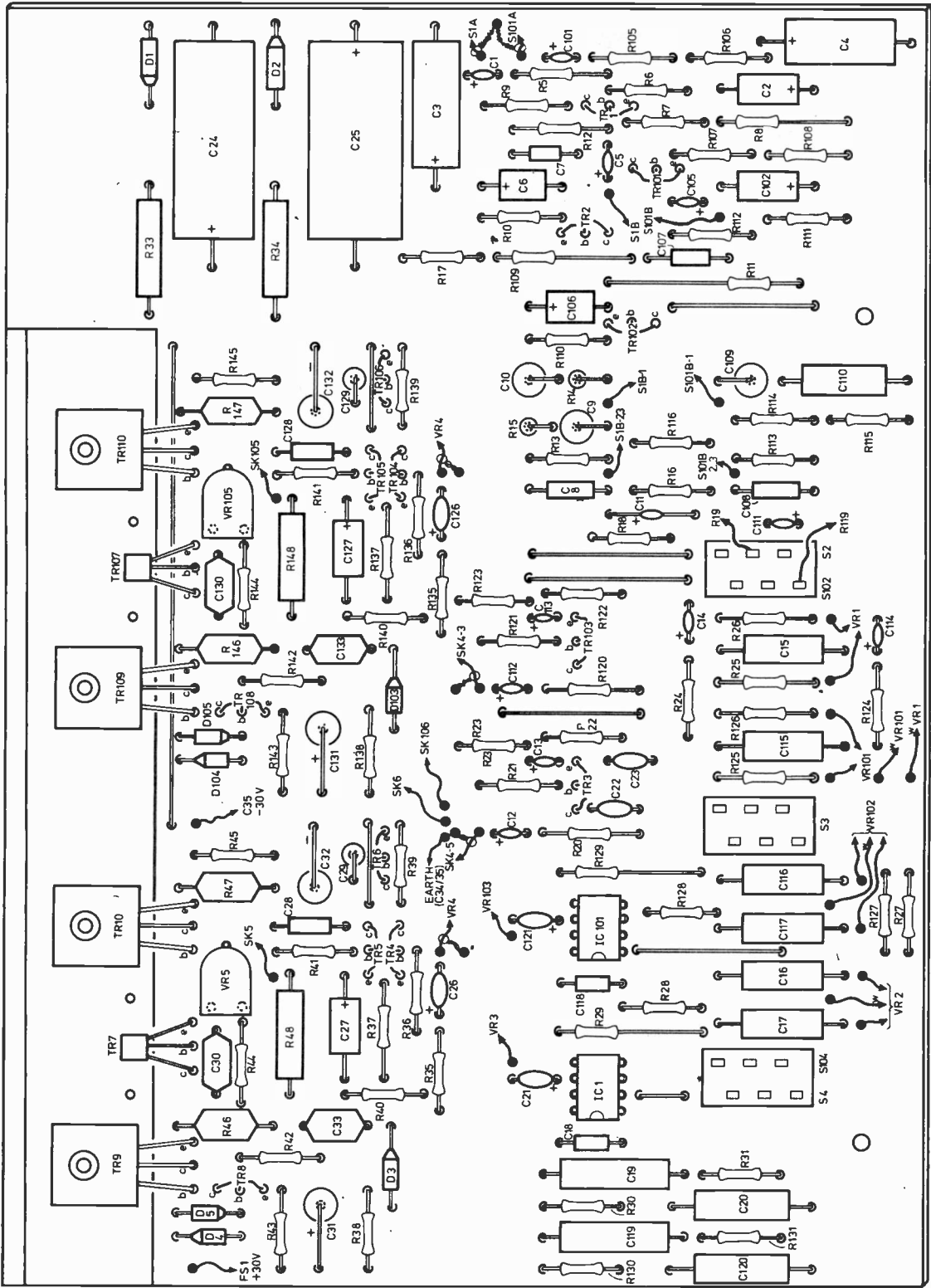


Fig. 2.2. Component layout of printed circuit board

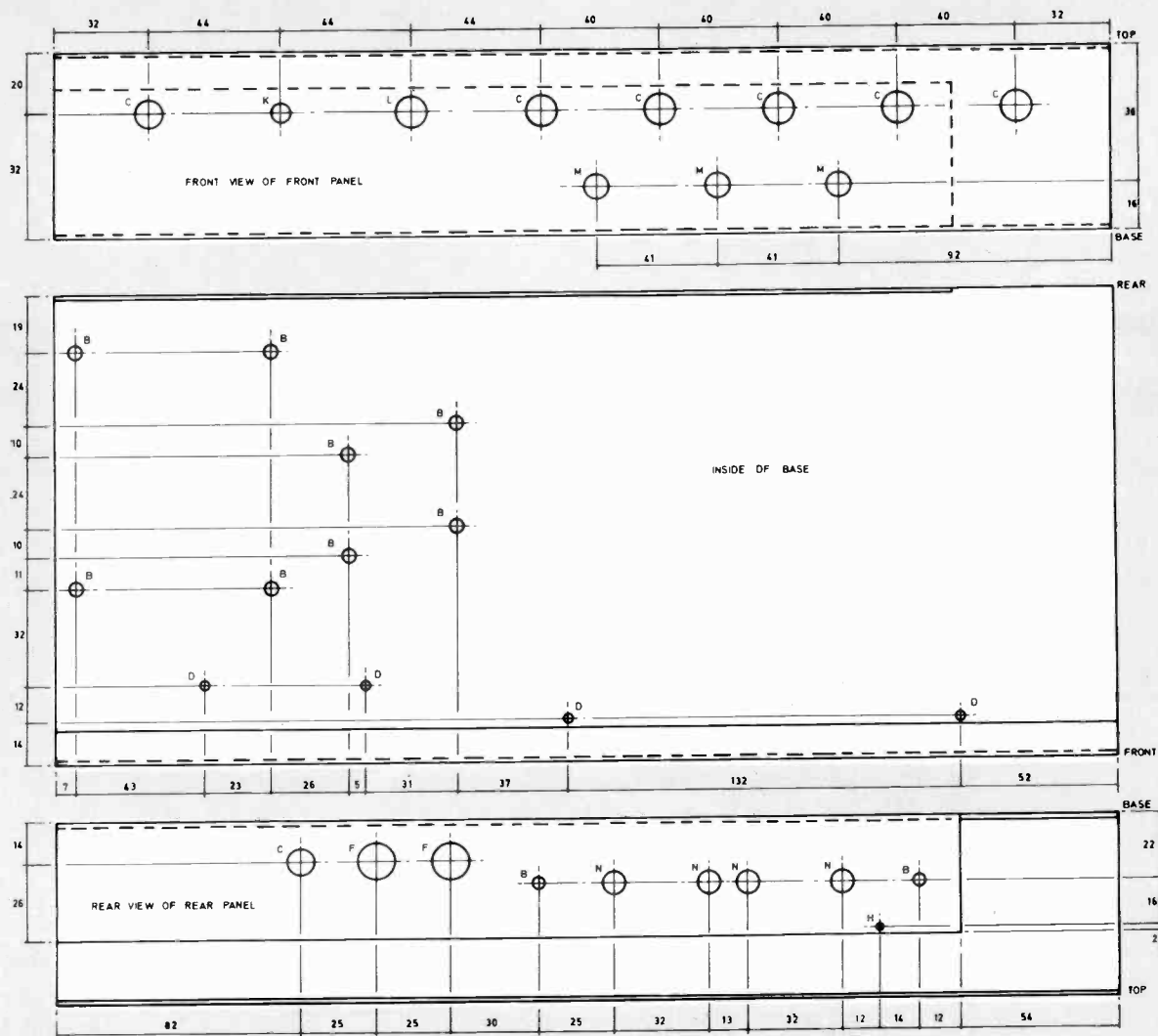


Fig. 2.3. Drilling details of main chassis

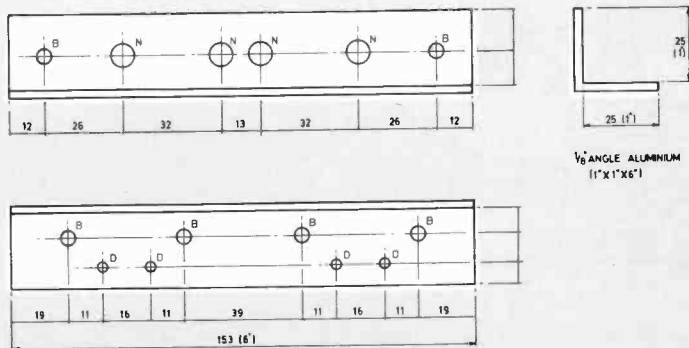


Fig. 2.4. Drilling details for the output transistor heatsink. "N" holes should be drilled using the mounting plate of Fig. 2.5 as a template

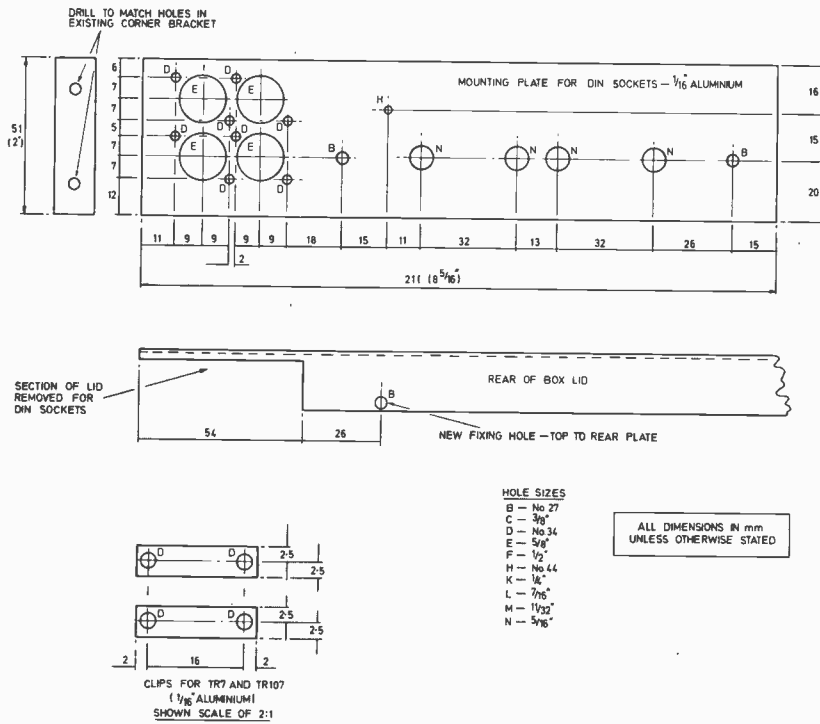


Fig. 2.5. Drilling details for DIN socket mounting plate, lid and small heat-sinks for TR7 and TR107

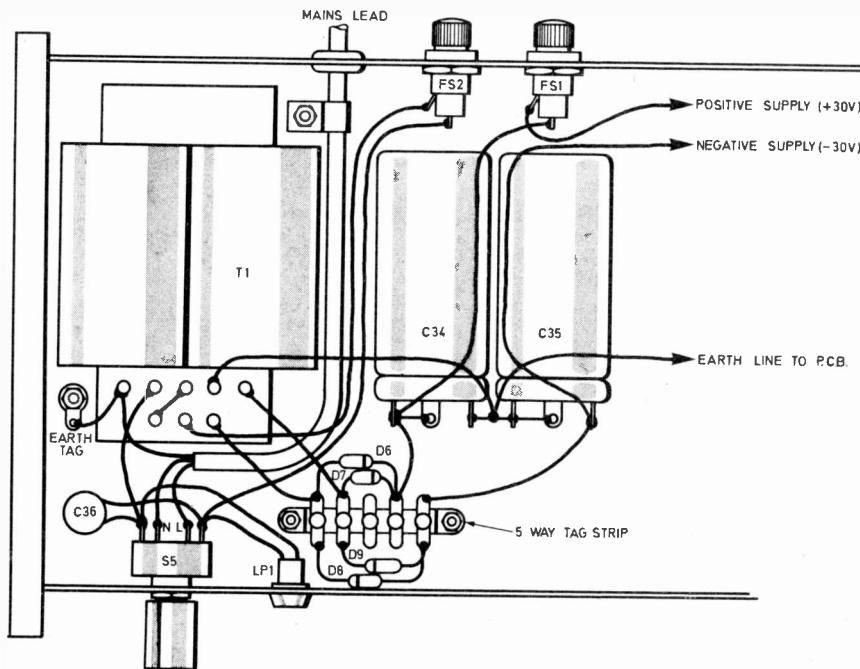


Fig. 2.6. Component layout for the power unit. The two hardwood end-cheeks are 7in x 2 1/4in x 3/8in


or Letracote. This gives the panel a smooth surface to which the instant lettering will adhere well. The panels can then be lettered using Letraset or some similar instant lettering. Take great care to get all the words level and evenly spaced as a little carelessness will spoil the appearance of the amplifier. After the lettering has been completed it should be sprayed with two further thin coats of protective lacquer.

CHASSIS ASSEMBLY

After the drilling has been completed and the panels lettered the wooden ends can be screwed back in place. The mains transformer should then be mounted, followed by the two fuseholders and the clamps for the smoothing capacitors.

The four rectifier diodes should be soldered to their tagstrip and mounted in place. Any suitable piece of tagstrip with five or more tags can be used and the case should be drilled to suit. The rotary mains switch and the headphone jack can then be fitted.

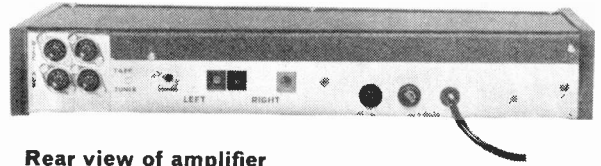The complete printed circuit board is fixed in place with two $\frac{1}{4}$ in spacers at the front, and by the four 4mm output sockets and two 4BA screws at the rear. Take care that the printed circuit board does not short against any of the screws in the corner of the case. If the push-button switches do not quite line up with their holes they can be bent slightly on their tags.



Rear view of amplifier

The potentiometers and the selector switch are next fitted and the wiring up commenced. Screened wire should be used between the DIN input sockets and the selector switch, between the selector switch and the input stage, to the tape inputs, and between the balance control and the main amplifier inputs, but ordinary connecting wire is satisfactory elsewhere. All leads should be as short as possible and the output and power supply leads should be kept well away from the preamplifier part of the circuit and all leads carrying low level signals.

A piece of thin insulating material should be glued inside the top cover over the terminals of the mains transformer to eliminate the possibility of the cover touching the terminals if anyone should lean on the top of the case.

TESTING

After all the constructional work has been completed, check the circuit carefully for errors, and turn the two bias potentiometers VR5 and VR105 fully anticlockwise.


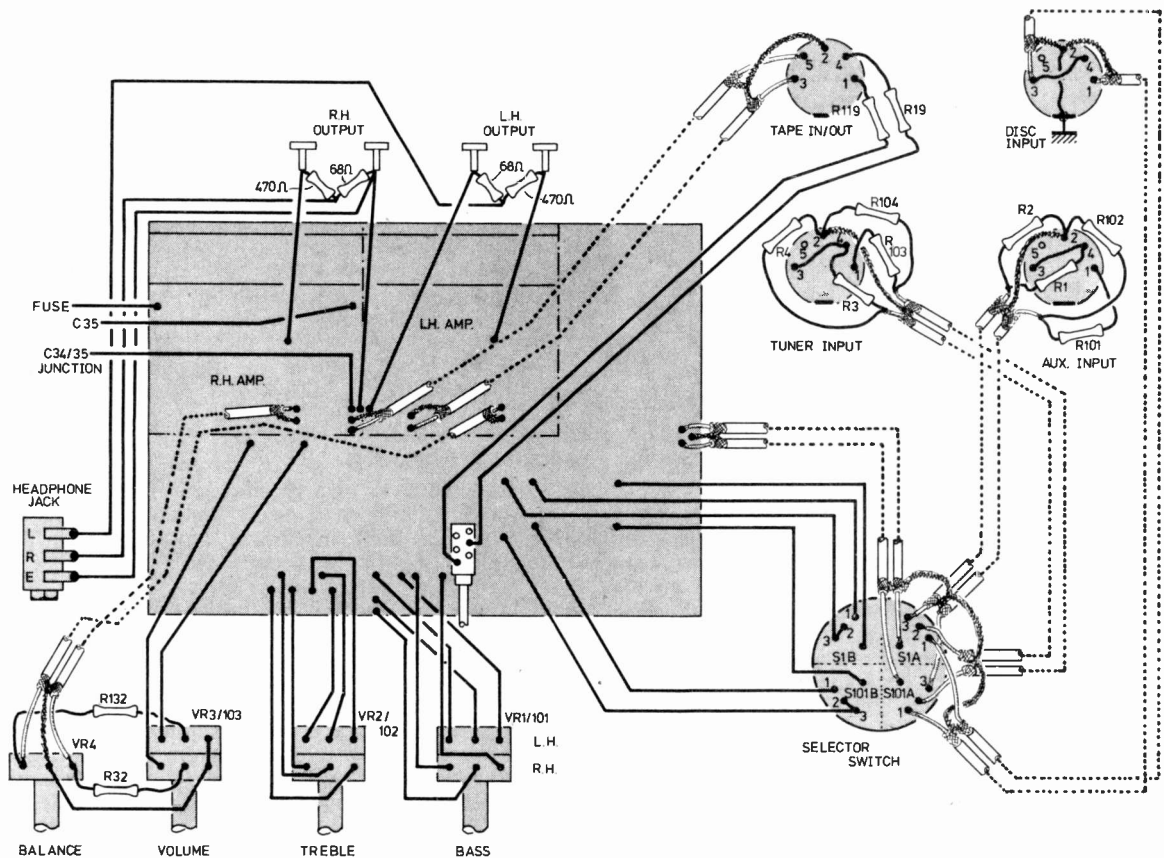


Fig. 2.7. External wiring to p.c.b.

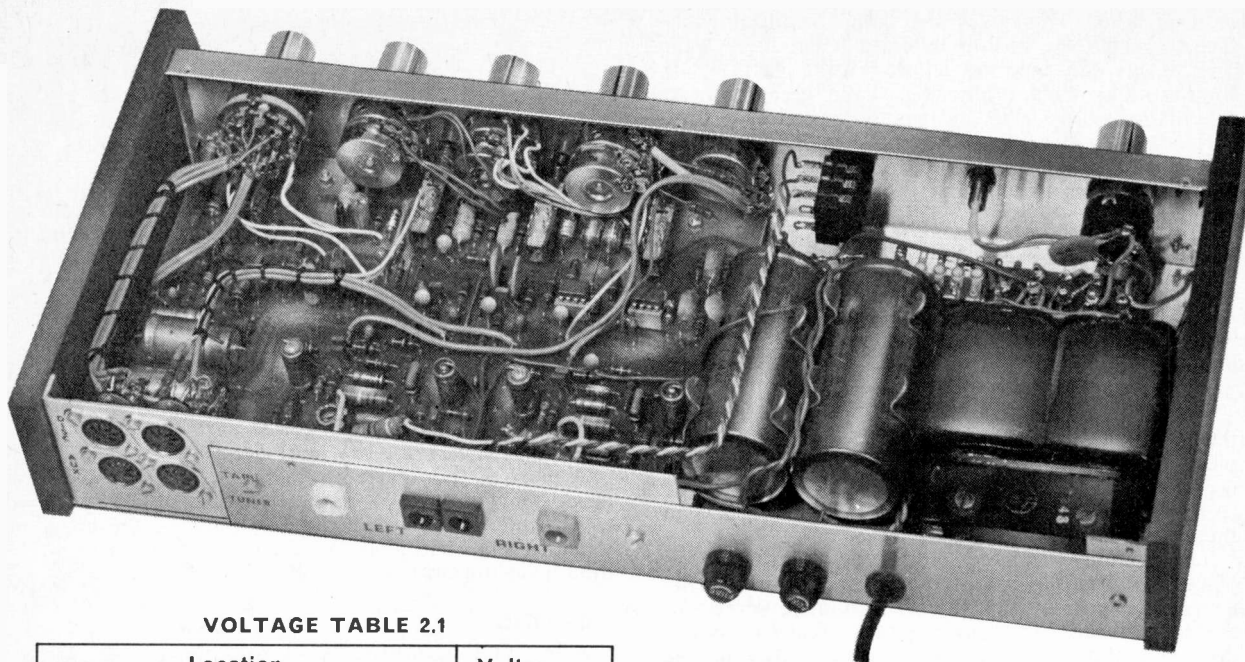

VOLTAGE TABLE 2.1

Location	Voltage
Across D4 and D5	1.3V
Across R43	0.6V
Across R39	0.6V
TR6 collector	- 1.2V
TR8 collector	1.2V
D3 anode	12V
TR4, TR5 emitters	0.7V
D1 anode	15V
D2 cathode	-15V
IC1 (pin 6)	0V
TR3 emitter	-1.2V
TR2 collector	1V
TR2 emitter	9.2V
TR1 emitter	-0.7V
C3	14V
C4	-14V
C34	30V
C35	-30V
All voltages are measured relative to chassis with no signal input.	

The initial testing should be done with a 1A fuse (FS1) and with the speakers disconnected and the volume control set at minimum.

Connect a meter reading 0-500mA or 0-1A in the positive rail, between C34 and FS1, and switch on. The meter should read about 80mA. Now turn either VR5 or VR105 until the reading on the meter increases by about 10mA.

Leave the amplifier running for about 10 minutes and then readjust if necessary. Repeat this procedure for the other channel. Check the voltage across the output terminals of each of the amplifiers. This should be less than 0.1V.

The loudspeakers and the record player deck or tuner can now be connected and the amplifier tested on music. Fuse FS1 can be left as 1 amp if only speech and music operation is required, but it should be increased to 2 A if the amplifier is to be driven at full power or if it is to be used with a transformer load (e.g. a Quad electrostatic loudspeaker).

VOLTAGES

A table of voltages (Table 2.1) is given to assist in fault finding. Due to the unregulated power supply there may be considerable variations in some voltages due to mains voltage variations and so differences of up to 20 per cent from the values given do not necessarily indicate a fault. Voltages are measured with the volume control at minimum using a meter of at least 20,000 ohms/volt.

EARTH LOOPS

Earth loops are a common problem with audio systems, usually evident as a loud hum on both channels. They arise when two pieces of equipment, such as an amplifier and a turntable, are both connected to a mains earth. Different voltages are induced in the earth leads of the two units and this causes a 50Hz current to flow in the braid of the screened cable connecting them. The fault can be cured by removing one of the earths, preferably not the amplifier, and the other equipment is then earthed via the amplifier.

FAULT FINDING

It is difficult to give specific advice as the number of possible faults in a newly built amplifier is very large and a fault in almost any component will affect the amplifier in some way. However the following general advice can be given:

Fault on Disc/Radio. Check Disc input stage.

Fault on Tape. Check Tape input and interconnecting leads between amplifier and tape deck.

Fault on all inputs. Check tone control, main amplifiers and power supply.

If you find any dud transistors do not assume that the transistor was the only fault. Transistors can easily be destroyed as a result of a fault elsewhere in the circuit and the circuit should be checked thoroughly for wiring errors or incorrect components before replacing. Failure to do this may result in blowing up the replacements as well! ★



Now there's Doram, you need never wait for electronic components.

7-day service.

Buy the new Doram catalogue and you could have your components within 7 days of our receipt of your order.

If you don't, you'll have your money back and no questions asked.

What you won't get is a tedious wait. Which goes on. And on. And on. And on. You know just where you are with Doram.

Millions of components.

Doram is a brand-new deal for serious amateurs. It's a complete door-to-door components service operated by mail order.

You buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint) and then you order from it.

We're big enough to offer you stocks of millions of components on over 4,000 product lines.

And so confident of our service that if we can't supply the part you want within 7 days of receiving your order, we'll give you your money back. Immediately.

No-quibble guarantee.

It's just about impossible to buy a defective part from us. Because our checking is so pains-taking.

But even if the unthinkable does happen—and you're unlucky—then we'll still make you happy quickly.

Because we offer a no-quibble replacement part service.

And our guarantee is guaranteed by the fact that we belong to the biggest electronics distribution Group in Britain.

All branded goods.

All goods supplied are branded goods. Made by big-name manufacturers like RS, Mullard, SGS-ATES, Ferranti, Siemens etc.

Doram brings the amateur the sort of service only professionals have enjoyed before.

So don't delay. Use the coupon. Send today for your first Doram catalogue. It can make your life a whole lot easier.

For 25p that can't be bad, can it?

I ENCLOSE 25p* PLEASE SEND ME THE NEW DORAM CATALOGUE.

Name

Address

Doram Electronics Limited,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

DORAM

PE/2/75



BY FRANK W. HYDE

LIFE SUPPORT SYSTEMS

The U.S.S.R. have always concentrated considerable thought on the value of life cycle support systems for space expeditions of the future. They have put such thinking to the test on a number of occasions, with remarkable success.

Two such experiments stand out from others. One of these was the experiment in which three astronauts were sealed in a chamber, which simulated a space cabin, for a year. This experiment added considerably to the data on reaction to such a closed environment.

The second outstanding piece of research was carried out, using four astronauts on a special recycling life support system, for six months. These men were again in a closed cabin simulating a space vehicle. For the duration of the experiment they were sealed in with an artificial atmosphere created by chlorella with some additional higher plants. Much was learned from this venture, all of it very much what future planners need to know when setting up missions for the future.

The latest experiment carried out at the Institute of Medical-Biological Problems, lasted for one month with one astronaut sealed in a small cabin containing 4.5 cubic metres of air. This is some 20 times less than the volume of air available to each astronaut in *Skylab*. The main supply for the support system came from a reactor in the form of a 30 litre cylinder. This reactor contained chlorella at a very high density, some 800 to 900 million cells per cubic centimetre of nutrient fluid. Ultra-violet light was used to illuminate the reactor.

During the experiment the chlorella, with the help of microbe mineralisers to break down the

urea, renewed both the oxygen and the water in the cabin. Total self regulation was not possible because the carbon dioxide and the oxygen have different gas exchange coefficients. The experimenters were a little apprehensive about the fact that two of the resultant impurities methane and carbon monoxide might reach a dangerous level in the cabin. However, this fear was not realised as the accumulation of the carbon monoxide lasted only three days and then ceased, while the methane reached an equilibrium level after some 12 days.

Because of the imbalance of the oxygen and carbon dioxide a chemical absorber to deal with excess of carbon dioxide was needed. The exchange between the human being and the chlorella production means that for every litre of carbon dioxide that the astronaut exhales, the system gives 1.2 litres of oxygen. Oxygen equilibrium if maintained gives rise to a surplus of carbon dioxide. Future systems will be arranged so that the equilibrium provided will make absorbers unnecessary.

An unpalatable part of the diet that Nikolai Mikhailov, the astronaut who was sealed in the cabin, had to suffer was to eat daily 50 grammes by weight of chlorella. However, it was laced with more palatable and homely food and no doubt this will be taken into account in future planning.

A BLACK HOLE OR NOT A BLACK HOLE

The *Uhuru* satellite discovered the X-ray source known as Cygnus X-1. The star, catalogue number HDE226868, is a bright hot star. The X-rays come from an invisible twin and not from the star itself. It was thought that matter was streaming from the bright star into the dark companion. On this supposition the dark companion was labelled a possible "black hole". This theory was tenable on the basis of the distance between the two bodies.

Now, however, new evidence has been put forward that this distance may not be as certain as was thought. A factor of two would be sufficient to reduce the candidate for black hole status to a possible red dwarf. The distance is uncertain because of the intervening dust. This is also patchy making it difficult to make a positive measurement. The further away the object is the more likely it is for the obscuring dust to make separation distance appear smaller than it is.

Support has now come for the possibility of the black hole being confirmed from three sources. These groups have results which correlate.

The data comes from the Copernicus satellite and the orbiting satellite *OSO-7*. There are three groups with K. Mason, F. Hawkins and P. Sandford of the Mullard Space Science Laboratory of University College, Paul Murdin and Ann Savage of the Royal Greenwich Observatory handling the Copernicus data and Fuk Kwok Li with G. Clark handling the *OSO-7* data.

They each confirm that the dips observed in the scans of the streams going towards the dark member of the binary are variations of the X-ray source and suggest that the variations are predictable as to time. If this is the case then it may well show "black hole or no black hole".

LUNAR ROCKS AND MAGNETISM

Most workers support the view that the remanent magnetism in the Lunar rocks implies that at some time in the past a global dipole magnetic field existed on the moon of at least a thousand gammas. What is still unresolved is where the field came from in the first instance.

Apart from the possibility of a solar field which no longer exists the source could be that there was a very large galactic field at the time when the solar system was born. The Moon could have had an enhanced magnetic field because of its close proximity to the earth during this time.

It is possible that there was a phase when the Sun ejected matter at a prodigious rate and created a cyclonic type of solar wind which heated and magnetised the lunar crust. Unfortunately a close examination of the solar wind particle tracks does not support this view. Indeed there was nothing to show that the solar wind was very different from what it is now.

Again there is a dissenting view of this attitude based on the fact that most rocks analysed have been on the surface for about five million years only; this is a short spell. However, if more rock from much lower levels could be checked there might be a more positive answer. So far the lunar regolith or top soil does show evidence of a higher intensity of solar wind in the past.

Some of the more exotic theories are challenged by the findings of *Mariner 10* in regard to Mercury. The instruments detected a bow shock wave similar to that of the Earth's magnetosphere when it encounters the solar wind. When *Mariner 10* made its closest approach of 730 kilometres it detected a magnetic field of 98 gammas. This certainly implies that the surface magnetism of Mercury is of the order of 100 to 2,000 gammas. This would be more than sufficient to divert the solar wind and cause the bow shock wave.

CEEFAX AND ORACLE

A PROPOSED
NEW BROADCASTING SERVICE

BY J. SMITH

MANY readers will no doubt have seen the press announcements that the BBC and IBA have agreed to a common standard for the transmission of data with the television picture. BBC's Ceefax (see the facts) and IBA's Oracle (Optical Reception of Announcements by Coded Line Electronics) are methods of transmitting written information simultaneously with the picture transmission. This written information can only be seen by viewers having special equipment to capture and decode the data.

THE PRESENT SITUATION

The idea of broadcasting data signals to send written information has been discussed by engineers since the 1930's. Unfortunately the cost of facsimile equipment, together with the need to load the machine with paper and ink, has prevented this idea from getting off the ground.

Today most people have television in their homes which, together with the broadcast signal, provide the means to receive and display written information. No messy inks or rolls of paper, just the familiar TV set and a new unit to receive and decode the data signals.

At the present time the decoding units are not cheap (they are not even available), but would cost well over a hundred pounds. A dedicated amateur

could build one for a hundred pounds or so, but remember the transmissions are experimental for the present. For the future, when one considers how the cost of an electronic calculator has fallen from over £1,000 to under £30, there is every hope that these decoder units can be brought down to the same level.

OVERALL SYSTEM

The system envisaged will allow the viewer to select up to 100 "pages" of information and display each page on his TV receiver. Each page will consist of 24 rows with 40 characters per row including spaces, about 150 to 200 words per page. This is of course a very low word density, four or five pages being necessary to give as much information as one page in PRACTICAL ELECTRONICS.

Obviously such a system cannot for a variety of reasons replace a daily newspaper, especially if you want to read it on the train, but it will be an additional public information service. For example, the TV pages will contain such information as an index, a list of programmes on television and radio, news flashes, weather forecasts, sub-titles for the deaf, sporting news, traffic conditions, financial news, statistics and graphs to supplement economic programmes and even local events of general interest in the service area.

In operation the viewer will have a small keyboard which will enable him to select any one of the 100 pages by pushing the appropriate buttons. He first selects the index page to see what information is available. Having decided he wishes to examine page 22 for example, he pushes buttons 22 and waits for up to 15 seconds, normally less, when the information is displayed on his television screen. The information is displayed for as long as the viewer wishes and only erased when he selects another page or returns to normal viewing.

DATA TRANSMISSION

The data are transmitted on two unused lines during the frame blanking period of the UHF (625 line) system. The data can be seen by adjusting picture height control until the frame blanking period is visible. The data consist of little black and white dots running along the top of the picture.

The service will not be available in fringe areas because it is in the nature of digital signals to suffer rapid impairment as the signal strength weakens.

A TV set displaying an Oracle index page. The small unit is the decoder



HOW DOES IT ALL WORK?

At the present time the system makes use of lines 17 and 18 (lines 330 and 331 on the interlace scan), that is two lines of data transmitted in every frame. Other lines could be used, 13 and 14 for instance, but these have been found to interfere with some existing receivers. In the future, alternative or additional lines may be brought into use.

Fig. 1.1 shows how the data is fitted into the line period. The data blocks contain synchronisation pulses, a starting code and the address of each line, in addition to the actual data. Each line contains a complete row of 40 characters.

As each "page" contains 24 rows, a page takes 12 fields or 12/50 seconds to transmit. This is four pages a second, so a "magazine" of 60 pages takes approximately 15 seconds.

The receiving equipment stores one page only, so this transmission rate determines that a wait of up to 15 seconds is necessary, with the initial 60 page service, before receiving a selected page.

One novel feature of the system is the use of command codes in the naturally occurring spaces between words. Whenever a command code is recognised it is automatically displayed as a space.

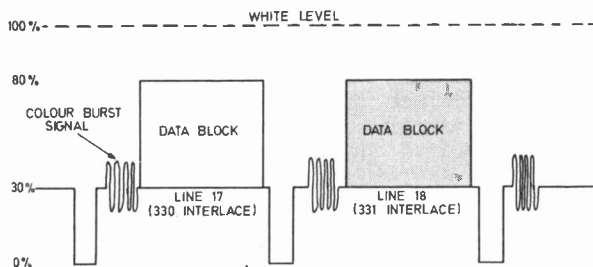


Fig. 1.1. Data is transmitted on lines 17, 18, 330, 331 and this diagram shows how the data is inserted into the video signal

INCORPORATION INTO EXISTING RECEIVERS

Fig. 1.2 shows how the overall system fits together with a unit incorporated into a television receiver.

The video and synchronisation signals are fed via a mixing unit which enables the viewer to select picture, text, or a mixture of the two. A page number is selected on the page selector and stored in a register. Signals fed into the data selector are compared with the register to find the page selected.

When the signals identical to the selected page occur they are fed to the RAM (Random Access Memory) where they are stored according to their line address. The RAM is filled under the control of the RAM control unit.

Once the RAM is full of data it is like any other memory unit and could be used to feed information to any suitable printer. For example, given the appropriate circuits the information could be fed to an electric typewriter.

The RAM can be visualised as a large matrix having rows and columns of data as shown in Fig. 1.3. Row A represents the first line of 40 characters. To obtain the first character in the line

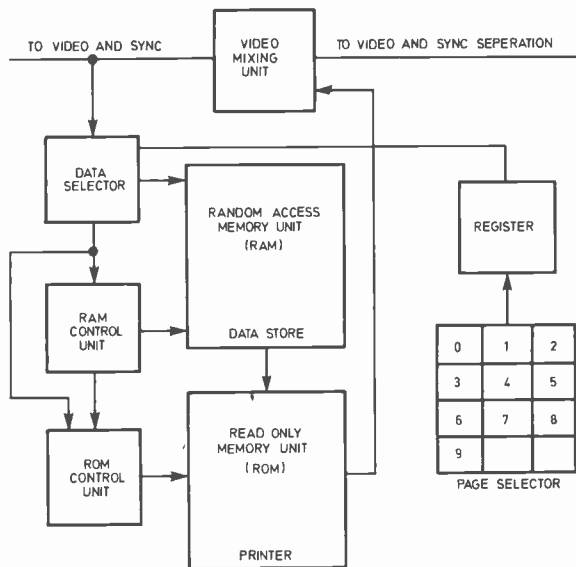



Fig. 1.2. The basic Ceefax/Oracle system

you address the memory A1 and get out the eight-bit character stored in box A1. The second character is in box A2 and so on. If the memory is addressed in sequence and each character fed to a typewriter, a line of print can be reproduced.

The memory unit has only sufficient capacity to store the contents of one page, which explains why you have to wait up to 15 seconds before you get the next page. This is the time which may elapse before receipt of the next full page of information.

If the television companies used more lines of data they could have a magazine larger than 60 pages and still take no longer than 15 seconds to produce another page. In practice it is most unlikely that a page selected will have just been transmitted; so on most occasions the RAM will be refilled with a new page in about 7.5 seconds.

An Oracle test card. Many of the characters are in colour

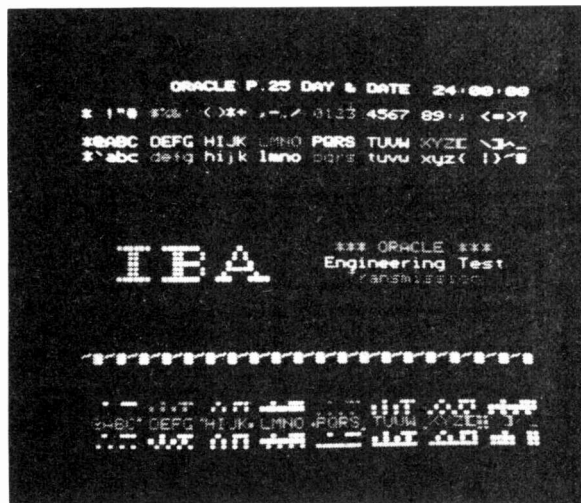


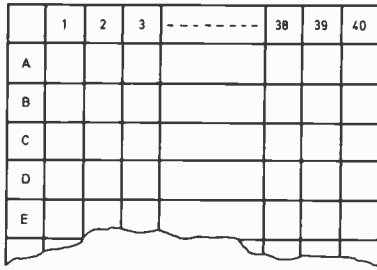


Fig. 1.3. Simplified RAM organisation. In the overall system the RAM is used to store a single page of data

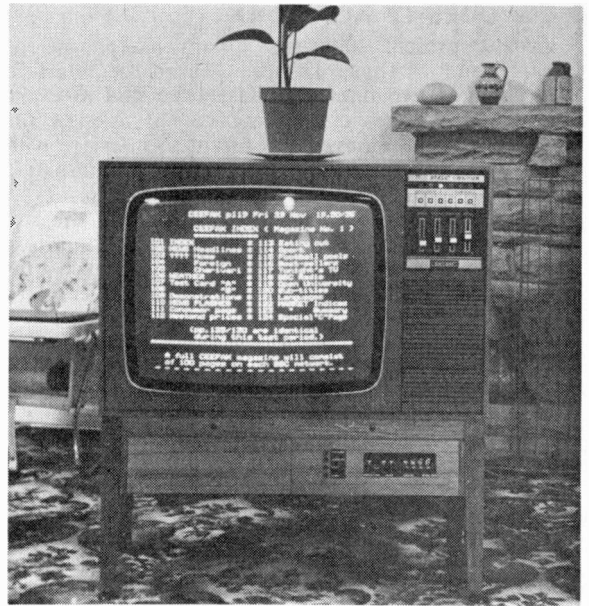

A TV set with an integral decoder
(Courtesy GEC Hirst Research Centre)

	000	001	010	011	100	101	110	111
0000	0	8		0	P	·	P	
0001	7	9	!	1	A	Q	a	9
0010	1	0	"	2	B	R	b	r
0011	J	0	#	3	C	S	c	3
0100	4	0	\$	4	O	T	d	t
0101	0	7	%	5	E	U	e	U
0110	✓	∩	&	6	F	V	f	v
0111	o	4	'	7	G	W	g	w
1000	7	8	<	8	H	X	h	x
1001	3	+)	9	I	Y	i	y
1010	≡	?	*	:	J	Z	j	z
1011	ψ	0	+	:	K	C	k	c
1100	ψ	0	,	<	L	\	l	!
1101	€	0	-	=	M	∩	m)
1110	0	0	.	>	N	∞	n	~
1111	0	0	/	?	O	_	o	⊗

Fig. 1.4. Characters contained in a Read Only Memory (ROM) designed by Mullard Ltd.

(Reproduced from Technical Note 7, Mullard Ltd., October 1974, TP1404)

CHARACTER GENERATOR

Of course Ceefax and Oracle do not employ an electric typewriter; they use the television screen, therefore a *character generator* is necessary. When the data are read out of the RAM the information is not lost; they can be read out repeatedly. This means that each frame of the TV can read the memory and display it on the screen giving an apparently "frozen" display of the page of data. All that is needed is a character generator to display characters on the TV screen. This is the function of the ROM (Read Only Memory). The characters are stored *permanently* in the ROM and organised into addresses in the same manner as data are stored in the RAM. Fig. 1.4 shows the characters contained in a ROM designed by Mullard Ltd. The addresses are given in binary notation.

To access capital A for example, the ROM is addressed with 0001 and 100. To display the characters the data in the RAM are accessed to find out which character is to be displayed. This character addresses the ROM which, together with the ROM control circuits, display the specified character on the TV screen.

This sequence of events occurs every frame so that characters are flashed onto the screen at a rate of 50 times per second for as long as the data are held in the memory. The characters are spread over a number of raster lines, the precise number being defined in the receiver design. It is expected that 20 lines will be used for each row, with characters 14 lines high and six lines between each row of characters. As the specification is still somewhat tentative, receiver manufacturers have been asked to make the ROM a plug-in unit on their experimental receivers.

In next month's article we shall look at the ROM organisation in a little more detail together with the means adopted to ensure accuracy in the received signals

INTRODUCING


SEAS

by Macel

The Elite of
Scandinavian
Loudspeakers

High Quality
High Fidelity
Loudspeaker Kits

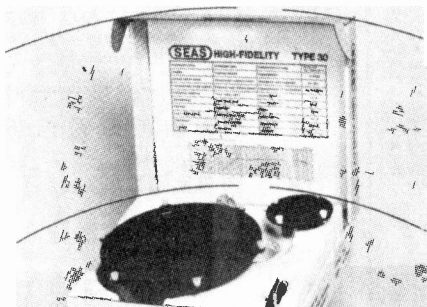INTRODUCTORY OFFER INCLUDES VAT AT 8% AND POSTAGE (UK ONLY)
(ALL KITS INCLUDE FULL WIRING DIAGRAM AND CABINET DRAWING)
(8 ohms impedance)



combine hobby with pleasure



PRICE LIST (Excl. VAT)

The following include High Compliance Bass Units and Cone Middle/Treble Units.

- Kit 91H:** 2 way and crossover (1 × 6½" plus 1 × 3½") (8-18 litre box) 10 watts 60-20,000 c/s. £7.35 each.
- KIT 94H:** 3 way and crossover (1 × 11" × 6½" plus 1 × 3½" plus 1 × 2") (25-40 litre box) 25 watts 45-20,000 c/s. £13.25 each.

The following include Neoprene Edge Bass Units and Dome Middle/Treble Units. Outer connecting lead and all internal wiring with mechanical push-on connectors.

- KIT 10-2:** 2 way and crossover (1 × 6½" plus 1" dome) (8-12 litre box) 20 watts 45-20,000 c/s. £15.35 each.
- KIT 18:** 2 way and crossover (1 × 8" plus 1½" dome) (15-20 litre box) 30 watts 35-20,000 c/s. £16.30 each.
- KIT 30:** 2 way and crossover (1 × 10" plus 1½" dome) (25-35 litre box) 35 watt 30-20,000 c/s. £16.95 each.
- KIT 35:** 3 speakers and crossover (2 × 8" plus 1½" dome) (30-40 litre box) 60 watts 30-20,000 c/s. £23.30 each.
- KIT 60:** 4 speakers and crossover (2 × 10" plus 1 × 6" × 4" plus 1½" dome) (50-70 litre box) 25-20,000 c/s. £34.95 each.

To MACEL ELECTRONICS LTD

P.O. Box 64, 14 High Street, Ipswich IP1 3LR.
Tel. 0473 215465

I enclose cheque/postal order


£..... for.....

NAME

ADDRESS

*Please debit my *Barclaycard/Access account. Account number

--	--	--	--	--	--	--	--	--	--

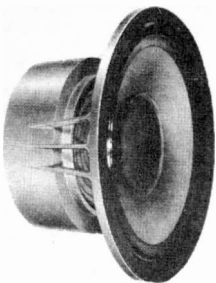

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm £7-75
 Baker Group 35 3, 8 or 15 ohm £8-50
 Baker Group 50/12 8 or 15 ohm £12-50
 Baker Deluxe 12in d/cone £10-75
 Baker Major 12in d/cone £8-50
 Baker Regent £7-75
 Baker Superb £14-50
 Baker Auditorium 12 £12-50
 Celestion MH1000, 8 or 15 ohm £10-85
 Celestion PST8 for Unilex £3-25
 Celestion G12M 8 or 15 ohm £12-00
 Celestion G12H 8 or 15 ohm £15-00
 Celestion G15C 8 or 15 ohm £3-00
 Celestion G16C 3 or 15 ohm £3-00
 Coral 8 1/2in d/cone roll surr. 8 ohm £3-25
 Coral 8in d/cone roll surr. 8 ohm £2-25
 EMI 13in x 8in 3, 8 or 15 ohm £2-50
 EMI 13in x 8in 150 d/c 8 ohm £3-75
 EMI 13in x 8in 450 Utw. 3, 8 or 15 ohm £2-25
 EMI 13in x 8in type 350 8 or 15 ohm £2-50
 EMI 13in x 8in 20W base £3-00
 EMI 6 1/2in 93850 4 or 8 ohm £2-50
 EMI 5in 14A/7030 mid range 8 ohm £2-50
 EMI 8 x 5 d/cone, roll surr. 10W £1-50
 EMI 2 1/2in tweeter 97492AT £1-50
 Eagle DT33 30W tweeter £3-00
 Eagle HT15 horn tweeter £1-75
 Eagle CT5 cone tweeter £2-55
 Eagle CT10 tweeter 8 or 16 ohm £3-80
 Eagle MHT10 horn tweeter £1-50
 Eagle crossover CN23, CN28, CN216 £5-30
 Eagle FR4 £8-35
 Eagle FR65 £10-65
 Eagle FR8 £2-80
 Elac 9 x 5 59RM109 15 ohm, 59RM114 8 ohm £3-50
 Elac 6 1/2in 6RM171 d/c roll surr. £2-65
 Elac 6 1/2in 6RM220 d/cone £1-50
 Elac 4in tweeter TW4 £2-85
 Elac 10in d/cone 10RM239 8 ohm £2-50
 Elac 8in 8CS175 3 ohm £5-25
 Fane Pop 15W 12in £7-25
 Fane Pop 25T 30W 12in £12-00
 Fane Pop 50W 12in £12-50
 Fane Pop 35 80W 12in £13-25
 Fane Pop 80W 15in £24-50
 Fane Pop 100W 18in £29-00
 Fane Crescendo 12A 100W 12in £29-00
 Fane Crescendo 12B bass £36-00
 Fane Crescendo 15in 100W £31-95
 Fane Crescendo 18in 150W £7-00
 Fane 801T 8in d/c roll surr. £3-85
 Fane 807T 8in d/c roll surr. £2-75
 Fane 808T 8in d/c £35-00
 Fane 701 twin ribbon horn £12-75
 Fane 910 horn £33-00
 Fane 920 horn £3-00
 Goodmans 6P 8 or 15 ohm

Goodmans 10P 8 or 15 ohm £5-30
 Goodmans 12P 8 or 15 ohm £12-85
 Goodmans 12P-D 8 or 15 ohm £18-75
 Goodmans 12P-G 8 or 15 ohm £15-75
 Goodmans Audiomax 12AX 100W £38-50
 Goodmans Audiomax 15AX £49-25
 Goodmans 15P 8 or 15 ohm £21-00
 Goodmans 18P 8 or 15 ohm £38-00
 Goodmans Midax 750 £18-00
 Goodmans Axeni 100 tweeter £7-25
 Goodmans Audiom 100 12in £12-00
 Goodmans Axiom 401 12in £17-25
 Goodmans Twinaxiom 8 £8-25
 Goodmans Twinaxiom 10 £9-00
 Kef T27 £5-25
 Kef T15 £6-00
 Kef B110 £7-25
 Kef B200 £9-25
 Kef B139 £9-25
 Kef DN8 £2-00
 Kef DN12 £4-95
 Kef DN13 £3-30
 STC401G3 super tweeter £8-19
 Richard Allan CG87 8in d/c r/surr. £8-35
 2 1/2in 64 ohm, 70mm 80 ohm, 70mm 8 ohm £9-85
 2 1/2in 75 ohm £9-50
 7in x 4in 3 or 8 ohm £1-40
 8in x 5in 3 or 8 ohm £1-50
 10in x 6in 3, 8 or 15 ohm £2-30

SPEAKER KITS

Baker Major Module each £10-75
 Fane Mode One each £9-90
 Goodmans DIN 20 each £9-75
 Helme XLK25 pair £22-00
 Helme XLK30 pair £14-85
 Helme XLK50 pair £39-95
 Kefkit 2 each £24-75
 Kefkit 3 each £36-75
 Richard Allan Twinkit each £8-95
 Richard Allan Triple 8 each £13-75
 Richard Allan Triple each £19-95
 Richard Allan Super Triple each £23-75
 Wharfedale Linton 2 kit pair £19-25
 Wharfedale Glendale 3 kit pair £34-50
 Wharfedale Dovedale 3 kit pair £52-50

PA/DISCO AMPLIFIERS

(carr. and ins. £1)
 Baker Major 100 watt £49-75
 Linear 30/40 £30-00
 Linear 40/60 £35-00
 Linear 80/100 £58-95
 Linear 100 watt slave £44-00

Eagle PA range in stock—ask for catalogue.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book.
 All units guaranteed new and perfect. Prompt despatch. Carriage and packing; speakers 38p each, speaker kits 75p each (£1-50 pair), tweeters and crossovers 20p.

Send stamp for free booklet "Choosing a Speaker"
 ALL PRICES QUOTED INCLUDE VAT

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.
 Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.



Cassettes The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!	C80	1	5	10
	C80	37p	£1-80	£3-90
	C90	50p	£2-48	£4-95
	C120	63p	£3-10	£8-20
AGFA HIGHDYNAMIC SUPER	C80 + 6	50p	5	10
	C80 + 6 <td>50p</td> <td>£2-40</td> <td>£4-70</td>	50p	£2-40	£4-70
	C120	63p	£3-35	£8-00
	C120	63p	£4-80	£9-90
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C80	1	5	10
	C80	55p	£4-20	£8-30
	C80	£1-08	£6-35	£10-80

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PE)
 10 SWAN STREET, WILMSLOW,
 CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

COLOUR TELEVISION WITH PARTICULAR REFERENCE TO THE PAL SYSTEM

by G. N. Patchett Price £5-10

ELEMENTS OF TRANSISTOR PULSE CIRCUITS by T. D. Towers. Price £3-70.

UNDERSTANDING IC OPERATIONAL AMPLIFIERS by R. Melen. Price £2-20.

BEGINNER'S GUIDE TO ELECTRONICS by T. L. Squires. Price £2-05.

ELECTRONIC EQUIPMENT RELIABILITY by J. C. Cluley. Price £2-65.

ELECTRONIC HOBBYIST'S IC PROJECTS HANDBOOK by B. Brown. Price £1-55.

DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS by N. M. Morris. Price £2-40.

RADIO CONTROL HANDBOOK by H. G. McEntee. Price £2-10.

DIGITAL LOGIC BASIC THEORY AND PRACTICE by J. H. Smith. Price £1-65.

UNDERSTANDING AND USING THE VOM AND EVM by J. Cunningham. Price £1-65.

GE TRANSISTOR MANUAL Price £1-30.

★ TOTAL PRICE INCLUDES POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185
 Closed Saturday 1 p.m.

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back-up service to ensure your success.

VHF and UHF Modulator Kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes, special mains transformers and focus/scan coils, also available P.W. tele-tennis game.

Send 5" x 7" S.A.E. for full details or come along for a demonstration and a chat with our technical staff.

CROFTON ELECTRONICS

124 Colne Road, Twickenham Middlesex TW2 6QS
 Telephone 01-898 1569
 Telex 934642 Cadanac LDN



BOOK REVIEWS

ELEMENTS OF TRANSISTOR PULSE CIRCUITS (2nd Edition)

By T. D. Towers
Published by Newnes-Butterworths
198 pages, 22cm x 13cm. Price £3.50

BASED on a series of articles which first appeared in *Wireless World* in 1964, this book provides the student or engineer with an excellent introduction to bipolar transistor switching circuits.

It could be thought that nowadays the logic designer simply needs to put together a number of integrated circuits and all his problems will be solved, but sooner or later, a situation arises where it becomes necessary to return to fundamentals, either because the integrated circuits do not fulfill all requirements, thus necessitating discrete component additions to the circuitry, or because a thorough understanding of the working of the integrated circuits themselves is needed to apply them efficiently to the job in hand.

Both the principles of transistor switching circuits and simple building blocks are described in terms suitable for the engineer or student who has a basic knowledge of electronics and the mathematics of tran-

sistor operation. Very basic logic systems are described but there is no attempt to delve deeply into this area.

It is a pity that the book could not be expanded to include integrated circuit logic systems such as TTL since these are the transistor pulse circuits the designer is most likely to encounter, but even so the book gives enough guidance for the engineer to cope with these circuits with little extra information.

S.R.L.

HOW THINGS WORK Vol. I & II

Published by Paladin. 13.5 x 19.5cm
Price, paperback £1.75 each volume

THESE two volumes, each over 500 pages in length, constitute a massive directory of answers to the age-old questions about machines and technology. Covering every possible facet of applied engineering from scientific measurement through the operation of T.V. to cars, tanks and guns, these volumes will provide an endless source of interest to the enquiring mind.

Hundreds of illustrations, many in two-colour, provide for ease of understanding and whilst it could be said that some are a little small or perhaps not quite as detailed as an expert in the subject might require, they provide ample clarification of each subject to give a clear understanding of the principles involved.

It is probably no exaggeration to say that these volumes will find a useful place in any home, office, workshop and school as a swift reference source to the answers for those difficult questions on operation which face us all in today's technological age.

R.D.R.

NEWS BRIEFS

Colour TV Certificate

IN response to demands from trade and industry a new Certificate of Competence in colour television servicing has been launched by the Radio, Television and Electronics Examination Board. Up until now there have been practical tests available in radio and TV servicing but nothing in colour.

The introduction of this certificate will, it is hoped, provide a national standard of practical ability which should reflect in good servicing for the consumer.

The examination is initially restricted to trained and experienced staff who hold a recognised technical qualification and who have had a minimum of one year's full time gainful experience.

Each examined candidate is required to trace a total of five faults in two hours on different chassis. An additional half-hour is allowed for adjustment of preset controls.

In addition to the practical assessment a short written test concerned with servicing matters is included.

First examinations are expected to start in March 1975. Besides the award of a certificate the Board will issue a personal identity card.

Further information can be obtained from RTEEB, Faraday House, 8-10 Charing Cross Road, London, WC2H 0HP.

Electronic Watch Displays

THE latest addition to the Litronix range of products for electronic watches is a group of four-digit displays using i.e.d.s. The complete displays are mounted on a tiny 0.75in x 0.21in ceramic substrate and all versions include a hyphen between the second and third digits.

Of the four versions available, three are full four-digit whilst one is a 3½-digit type. To reduce space requirements the packages are provided with solder bump contacts designed for reflow soldering attachment to watch modules.

Current pricing is only known for large quantities, 1,000 and upwards, at which it is £3.66 per item, but it seems clear that the costings on electronic watches are dropping fast.

Third Motorola Price Cut

YET again we are able to announce a further price cut in the Motorola CMOS range. This is the third cut in under twelve months and is said to be due to improved production techniques which have not only reduced costs but have also increased yields.

The new structure starts at 23.8 pence for a basic 14000-series quad NOR/NAND gate in quantities of 100 or more. The versatile 12-bit binary counter MC14040 has been reduced to £1.21.

It will be remembered that Motorola make most of the products for their European customers in Britain at East Kilbride. One of the factors said to be contributory in the price reductions is the fact that all production plant, including East Kilbride, use 3in diameter wafers, giving greater productivity.

PE MINISONIC


By G. D. SHAW

PART FOUR

- Final Wiring and Setting Up
- Alternative Keyboards
- Optional Extras

LAST month the electronics on the two Veroboard panels were described and so this month it only remains to connect the two boards with the controls on the front panel.

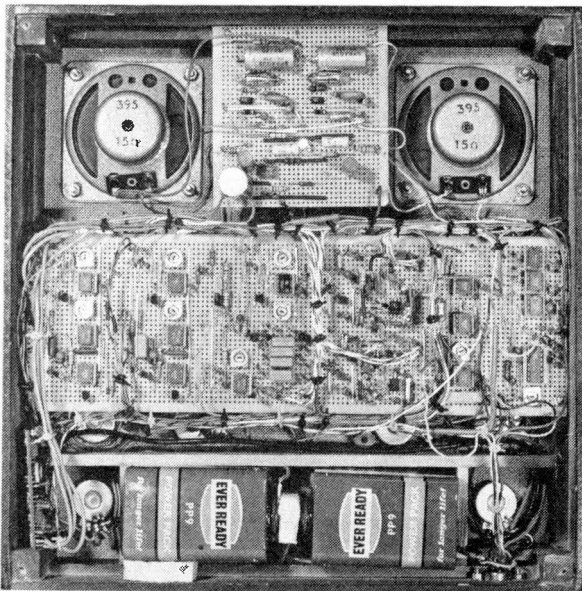Many of our more ambitious constructors may wish to add their own conventional keyboards to the Minisonic thus making it into a more "playable" musical instrument. Four different keyboard options are therefore described.



The upper board has been extended since the photo was taken so the large board must be mounted so that its lower edge is flush with the top of the battery compartment



WIRING UP

Fig. 4.1. shows a diagram of the reverse side of the front panel. Controls have been grouped together by labelled boxes so as to indicate which part of the main Veroboard panels they are connected with. All interwiring on the front panel has been shown; interconnections from the front panel to the Veroboards are indicated by lettered designations which correspond with the letters on the Veropins on the Veroboard panels.

When wiring the main circuit board to the front panel it is preferable that the front panel be fitted into the case with all leads, equal in length to the diagonal of the case, attached.

The leads, which should be suitably colour coded, are bunched tied in groups and, ideally, should be wired to the circuit board from one side only. This will enable access to the underside of the circuit board in the event of problems.

After trimming the various leads to length they can be soldered to their respective pins and then tied off to form a neat harness.

No problems of signal induction were experienced with the prototype despite the fact that both signal and control leads were included within the same harness. The NOISE GENERATOR may possibly give rise to induced noise and for this reason the output lead to its volume control should be kept as short as possible and routed clear of other signal leads. When the NOISE GENERATOR is not in use its volume control should be kept at zero.

A DIN socket was mentioned in passing in Part 3 without any detailed description of its function. In fact its purpose is to enable external keyboards to be plugged in to the Minisonic.

Wiring to the DIN socket is shown in Fig. 4.2. The DIN socket is in fact mounted on the front wooden panel at the lower left-hand side and can be seen in the photographs.

The two Veroboard panels are mounted on the Minisonic as shown in the photograph, though the smaller panel has been enlarged somewhat thus necessitating the lowering of the larger board so that its lower edge comes flush with the top of the battery compartment.

FRONT PANEL INTERWIRING

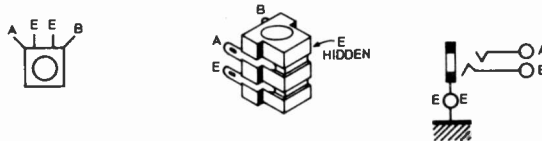
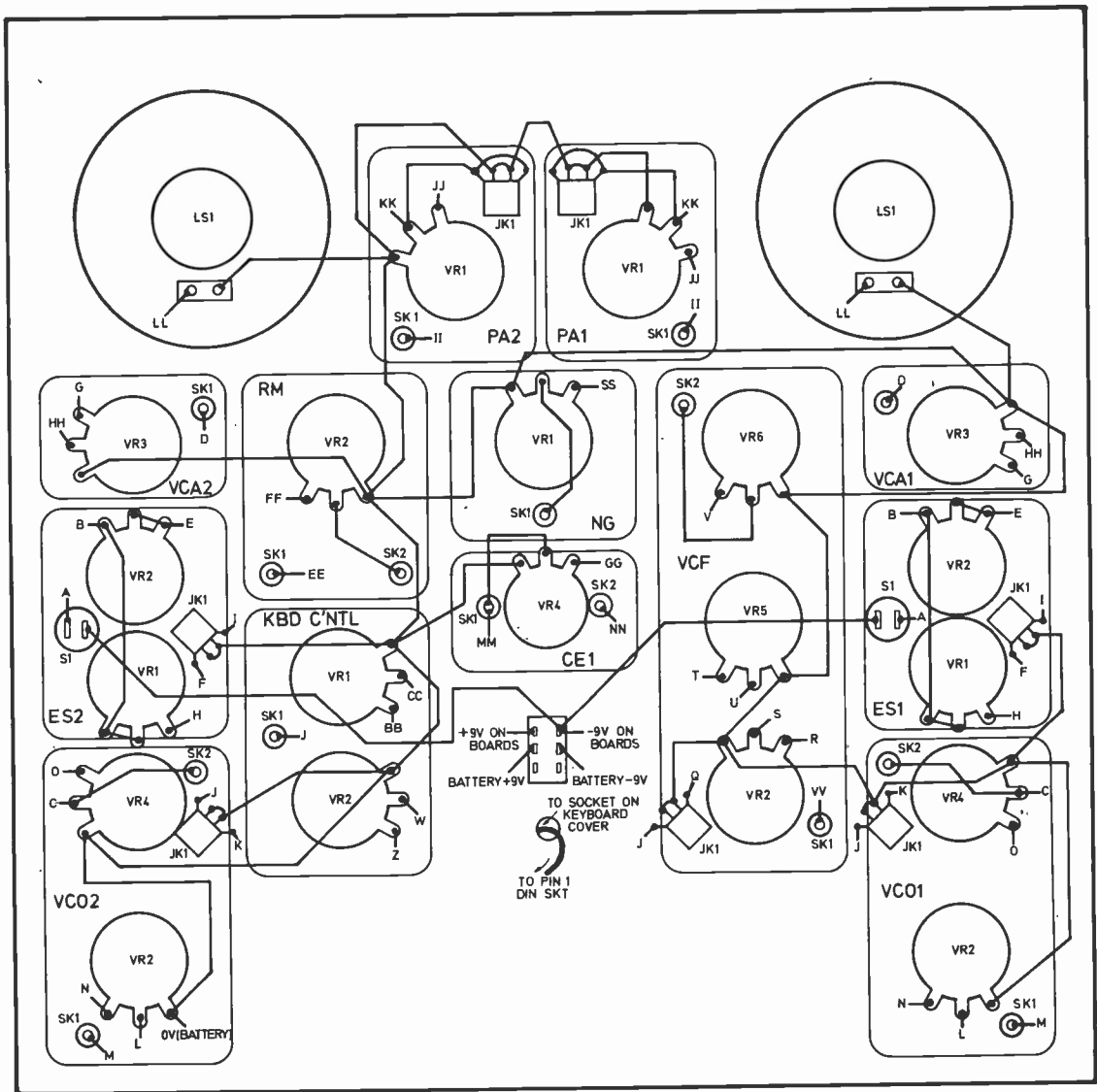


Fig. 4.1. The reverse side of the front panel. All interwiring on this panel has been shown; interconnections to the Veroboard panels are indicated by the lettered designations which correspond with letters on the Veroboards. The jack sockets are shown in detail to simplify wiring

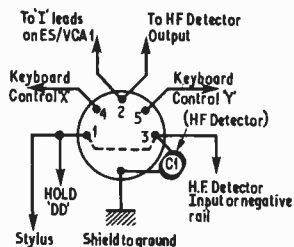


Fig. 4.2. Wiring of the DIN socket on the front panel. The link between pins 1 and 3 may not be necessary for some keyboard options—see text. The connection from pin 1 to the HOLD should go via a 20kΩ resistor (R7, Fig. 3.5)

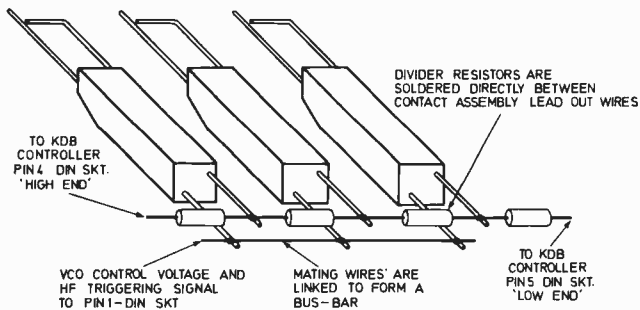


Fig. 4.3. The wiring of the single pole contact assemblies in a conventional keyboard. Only a three wire connection is necessary to the Minisonic. (Note: the normally closed contact wires have been omitted for clarity)

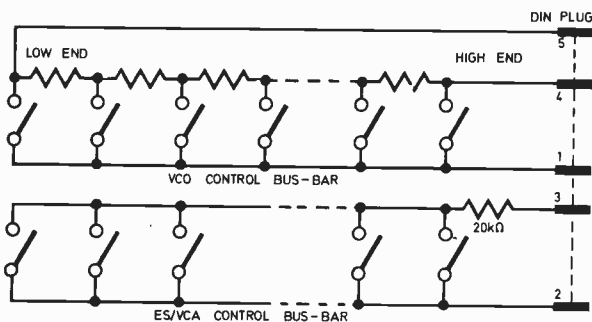


Fig. 4.4. Wiring arrangement for a conventional keyboard with double pole contact assemblies. In this case all five pins of the DIN plug and socket are necessary

KEYBOARD OPTIONS

1. Conventional Keyboard—single pole contact assemblies

The use of a keyboard of conventional style greatly improves the musical capabilities of the Minisonic and perhaps the simplest option here is to use a conventional style keyboard unit (the Kimber Allen type is recommended) which may be fitted with single pole changeover contacts of the Kimber-Allen G.J. type.

Wiring up is very easy and is illustrated in Fig. 4.3. After positioning the contacts such that the moving wires are central over their respective key actuators, connect up the moving wire lead-outs in the form of a busbar as shown. Divider resistors are now linked directly between the lead-outs on the normally-open contact wires.

Note that in Fig. 4.3 the normally-closed contact wires have been omitted for the sake of clarity.

Connection from the Minisonic to the keyboard unit in all cases is made via a DIN socket mounted on the front panel of the case. This has already been mentioned in the circuit diagrams of the HF DETECTOR last month. By simple changes in the wiring to this socket all the keyboard options to be described can be accommodated.

For this particular case a wire connection is made to each end of the divider chain and one to the busbar. All three wires are then taken to a DIN plug which mates with the DIN socket on the Minisonic. The "high" end of the divider chain goes to pin 4, the "low" end to pin 5, while the busbar goes to pin 1. The dotted link in Fig. 4.2 is required here.

If this option is adopted in addition to the printed circuit keyboard, then provision should be made to disconnect the latter keyboard divider when the external keyboard is in use.

2. Conventional Keyboard—double pole contact assemblies

With double pole contacts it is possible to trigger the Minisonic using the extra set of contacts rather than the HF OSCILLATOR signal superimposed on the vco voltage input.

Referring to the DIN socket wiring, Fig. 4.2, disconnect the HF DETECTOR input and output from pins 3 and 2 respectively. Remove the link between pins 1 and 3 (shown dotted) and couple pin 3 to -9V via a 20kΩ resistor. vco control voltages are brought to pin 1 as before while ES/vca trigger pulses from the second set of contacts are brought into pin 2.


Fig. 4.4 shows a diagrammatic wiring arrangement. When this option is used the HF OSCILLATOR and DETECTOR may be omitted from the overall scheme. In any event the HF OSCILLATOR should be disconnected from the KBD CONTROLLER.

3. Existing Keyboard System—single pole contact assemblies

This option requires that the existing keyboard should offer negative control voltages and also that there should be a facility whereby the HF OSCILLATOR output may be evenly superimposed on the keyboard divider system. If these requirements can be met by the external unit then the procedure is as follows.

In Fig. 4.2 link pins 1 and 3. Disconnect the keyboard control voltages from pins 4 and 5. Disconnect the HF OSCILLATOR from the Minisonic KBD CONTROLLER and reconnect through a 1,000pF capacitor to either pin 4 or 5.

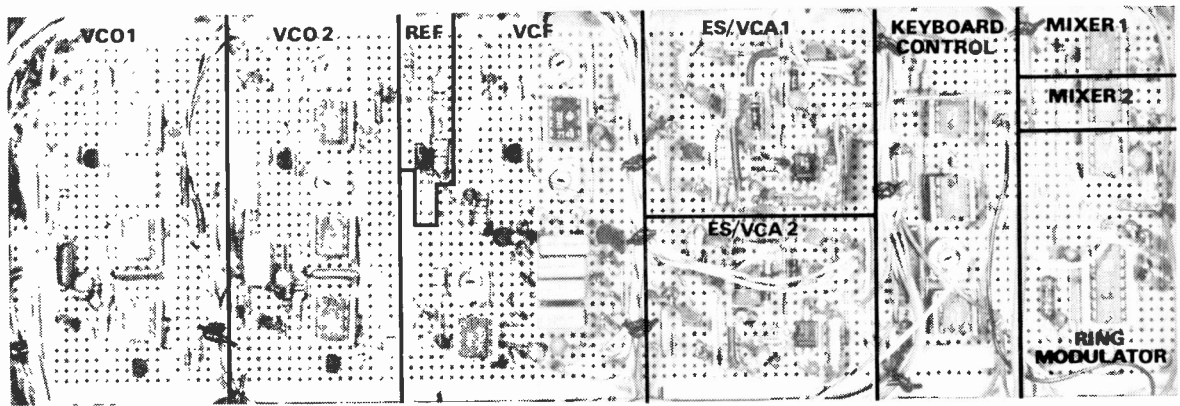The mating DIN plug from the external unit will in this case require only two connecting wires: one carrying the HF signal to the external KBD CONTROLLER; the other bringing the vco control voltage and the HF triggering signal to pin 1 as with the other options.



Photograph of complete board on which VCO's, VCF, Voltage Reference and ES/VCA's are mounted. (Note: some minor changes have been made to this layout)

4. Existing Keyboard System—double pole contact assemblies

With double pole contact assemblies the external unit will be supplying VCO and ES/VCA control voltages from its own resources. These voltages must be negative going. Pin 3 need not be connected to the negative rail.

It may possibly be necessary to include a resistor in series with pin 2 if the ES/VCA trigger pulse is in excess of $-3V$. For instance the *P.E. Sound Synthesiser* comes into this latter category, a $62k\Omega$ resistor being necessary to attenuate the trigger pulse sufficiently.

FINAL SETTING UP

Assuming that all circuits have been constructed, bench tested and linked to the front panel controls as described, it now remains to get the instrument into action.

VCO BALANCING

The front panel controls should be set as follows:
AT MINIMUM ENVELOPE SHAPER attack and decay.
 VCF frequency. CE inverter.

AT MID POSITION VCO frequency, tune, span and VCF "Q."

AT MAXIMUM All level controls.

Switch on the power and apply the stylus—in the case of a conventional keyboard, press a key—around the midpoint of the keyboard. Both channels should be heard (the frequency is unimportant) almost instantaneously with the application of the stylus, with the sound dying away equally quickly when the stylus is removed.

Apply the stylus again and hold it in position. Tune one or other of the oscillators so that there is a slow beat between them. Advance the decay control to maximum and remove the stylus. The audio signal from the oscillators should now begin to die away over a period of about 16 seconds.

At this point however there will almost certainly be a change in oscillator frequency as the sound decays away. The problem is that the hold circuit requires to be finally balanced by means of VR4, Fig. 3.2a.

Without an oscilloscope it is unlikely that a very fine balance can be achieved but perhaps what is more important is that the instrument "sounds" right.

Thus the stylus should be applied and removed with adjustment of VR4 being made during the decay period until finally there is no appreciable change in VCO frequency during the decay phase of the envelope. This operation requires some degree of patience since the closer the HOLD circuit is to balance the smaller will be the adjustments required.

SPAN CONTROL SETTING

Having balanced the HOLD circuit it now remains to set the KEYBOARD CONTROLLER span control such that the instrument can play an equal tempered scale. The situation is that the two VCO's are already tracking fairly closely with the tune and span controls in approximately their mid position. Tuning will be found easier however if only one oscillator is used.

Turn down the level control on one of the oscillators and advance the tune control to its maximum position. Run the stylus up and down the keyboard to ensure that the working oscillator frequency is within audible range at each extreme. If not adjust the oscillator frequency control accordingly. With the values given in the text of the series the equal temperament position will be found to be with the span control approximately in mid-rotation.

As with the HOLD circuit some patience may be required to get the tuning just right. Musicians with a sense of absolute pitch should not have too much difficulty in this respect but for the majority of constructors it will be a case of repeated adjustments and playing of octaves until the instrument sounds right.

An oscilloscope or frequency meter is a useful adjunct during these setting up procedures but is by no means essential. Having found the equal temperament position this should be carefully recorded since it is almost certain that the span control will be moved about again during the full evaluation phase of the instrument.

This completes the final setting up. Remaining checks on circuit performance may be made as follows:

VOLTAGE CONTROLLED FILTER

With the controls set as described, patch the output into a power amplifier external input. Turn both VCA level controls to minimum. Apply the stylus to

the keyboard in about mid-position and check that no signal is present in the channel carrying the vcf output.

Advance the vcf frequency control to maximum. As this is done the vco signal should become audible in the patched channel rising from a fairly bland sound to the full harsh bite of the sawtooth waveform as the frequency control of the vcf approaches its maximum setting.

Repeat this procedure with the Q control at both extremes. With Q at minimum the overall level of the sound should be somewhat greater than when it is at maximum but there will be less subjective change in the harmonic content of the resultant sound.

The next procedure is to check out the effect of automatically programming the vcf signal. Advance ES1 attack and decay controls to approximately one third of their rotation. Patch the output of the control envelope inverter into the control input of the VCF (jack socket). Set the CONTROL ENVELOPE level about halfway.

Application of the stylus to the keyboard will now result in a slow rise in audibility of the sound together with a distinct change in harmonic content as the sound becomes louder.

Try various settings of the attack, decay and envelope level controls to achieve a typical synthesiser "waa-waa" effect.

N.B. Remember that vco2 is permanently linked into the audio input of the filter. The level control of vco2 should therefore be at maximum for these latter checks.

RING MODULATOR

Remove the patch cords from the previous tests and patch the output of vco2 into the uncommitted input of the RING MODULATOR. Patch the output of the RING MODULATOR into one of the POWER AMPLIFIER inputs and with both vco level controls and the RING MODULATOR level control at maximum a resultant sound comprising the sum and difference of the input frequencies should be heard.

Try varying one or other of the vco frequencies and note how the composite signal from the RING MODULATOR contains both rising and falling frequencies at the same time.

Removal of the patch cord from vco2 should result in the complete loss of output signal from the RING MODULATOR. If this is not the case then VR1, Fig. 3.7, will require further adjustment.

NOISE GENERATOR

Patching the output of the NOISE GENERATOR into the POWER AMPLIFIER input should result in the immediate sound of white noise, a harsh, uneven rushing sound.

Having established that the main functions of the Minisonic are operating as described the constructor may now wish to make further investigation into the performance of the instrument.

Tracking of the oscillators at both extremes of the audio spectrum is a useful exercise particularly if the instrument is to be used for any kind of serious musical purpose. So far the checks on tracking have been limited to the measurement of current through the current generators. If this has been done with care there will be found to be very few problems

with the audible trackability. Any measurement with a meter however is liable to error if fundamental precautions, such as ensuring good contact between the probe and measuring point, are not taken.

AUDIO TRACKING

Audio tracking should be carried out using the keyboard to supply the reference voltages to both oscillators. With the stylus at about mid-position on the keyboard, set the vco's so that there is a slow beat between them, say around 2 to 3Hz. Now move the stylus to the top contact and, in this position, if the beat has increased so as to introduce a noticeable discord, then some adjustment will be necessary to VR3, Fig. 2.1, on one of the vco's.

It should be borne in mind that this latter adjustment should be very small and also that it will change the frequency setting at mid-keyboard. Consequently after such adjustment the stylus should be moved back to the original contact and the manual frequency controls on one or both vco's adjusted to achieve the slow beat again.

Do remember that with the law controls *exactly* matched any beat between vco's is as the result of differences in bias on the control node induced either by the manual frequency controls or by the bias preset or by a combination of the two.

Such a difference in bias will result in a minute variation between the currents through the constant current generators which will increase as the overall bias increases. Thus a slow beat at say 250Hz fundamental will be rather more rapid at 1kHz fundamental but should not be so rapid as to cause a discord.

The constructor should not therefore try to iron out the beats completely since although this is a theoretically possible exercise it is also one which is calculated to try one's patience to the limit.

Another useful check is to measure the timing of the attack and decay phases of the envelope shaper as far as is possible in order to gain some idea of the effects induced by various settings of the respective controls.

TEMPERATURE STABILITY

The greatest problem experienced with constant current generators utilising a single, uncompensated transistor is that the current is anything but constant. Minor variations in ambient temperature can cause quite significant changes in V_{be} and thus in current through the transistor.

For this reason it was decided to offer, as an optional extra, the possibility of incorporating temperature stabilisation to the vco's and vcf. The additional cost will be something under £2 (excluding Veroboard or PCB) and as such represents a good investment if the Minisonic is to be used for multi-tracking or more serious musical purposes.

During a twelve-hour soak test on a Minisonic vco the oscillator demonstrated a stability better than 0.2% per hour, a figure which would compare pretty favourably with most of the less expensive commercially available synthesisers.

STABILISER CIRCUIT

(Subject to Patent Application)

A full circuit of the stabiliser is given in Fig. 4.5.

TRA and TRB comprise part of a transistor array, the ML3046P. TRA is connected directly across the

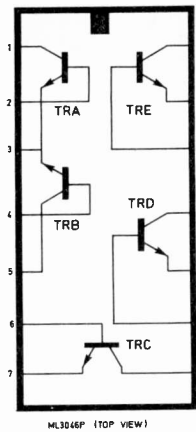


Fig. 4.5. Circuit of the optional stabiliser circuit

+9 and 0V rails and acts as a heater, the current through this transistor being limited by its own base current, which is, in turn, limited by R1. TRB is connected as a diode which is passing 1mA.

The V_{be} of TRB is compared by IC1 with a reference voltage set by R8, VR1, R9 which is nominally 660mV. IC1 is connected as a bounded integrator having a gain of about 10,000.

CIRCUIT ACTION

When power is first applied the transistor array is cold and thus the V_{be} of TRB will be greater than the reference voltage. The output of IC1 will therefore go rapidly positive turning on TRA which, with the output of IC1 at +8V, will pass about 7mA.

The effect is to heat up the transistor array which, in turn, causes the V_{be} of TRB to fall. The tendency will be for the V_{be} to fall to a point below the reference voltage at which time the output of the integrator will try to go negative. As soon as less current passes through TRA however the V_{be} of TRB will tend to rise again thereby signalling the requirement for more heating current to the integrator. In practice the circuit settles in about 30 seconds to a stable condition in which the V_{be} of TRB is maintained equal to the reference voltage.

In this situation the transistor array is kept at a constant temperature where the heat loss from the array is balanced by the heating effect of the current through TRA. Changes in ambient temperature will alter the heat balance of the system and thus cause a greater or lesser current to be passed through TRA. Similarly current passing through the other transistors on the array will also cause changes in the heat balance with the same effect.

SETTING UP

Setting up the so-called transistor oven is very simple. With a high impedance voltmeter connected

to the output of IC1 and switched to the 10V range, set VR1 so that the wiper voltage is 670mV and apply power.

The voltmeter will indicate that IC1 has an output of +8V although this will begin to fall almost immediately and will settle, depending on ambient temperature, to a point between +2 and +4V. Gradually adjust VR1 until its wiper potential reads 660mV and again check the output of IC1 which, at this time, should be about +6V.

The criterion here is that TRA must, under cold conditions, pass a current which is at least equal to the maximum combined currents of all the other transistors on the array. If this were not the case then stabilisation would fall off in a situation where the remaining transistors were all passing their maximum currents (not a common situation in practice).

USING THE OVEN IN THE MINISONIC

The oven may be incorporated into the Minisonic scheme by removing the current generating transistors from the VCO and VCF circuits and linking in TRC, TRD and TRE respectively using three wires per transistor in order to prevent any problems which might possibly arise due to a circuitous negative rail return.

The control voltage/current relationship will have altered in the sense that higher currents will be passed for a given control voltage due to the fact that the array temperature is significantly above ambient. This may be compensated for by a proportional adjustment to VR1 in all control nodes so that the current levels are similar to those shown in Fig. 2.2.

The actual "law" is unlikely to have changed significantly and thus it should not be necessary to reset VR3 in any of the control nodes.

The maximum current drain of the "oven" will be about 11mA with a mean drain of about 7mA.

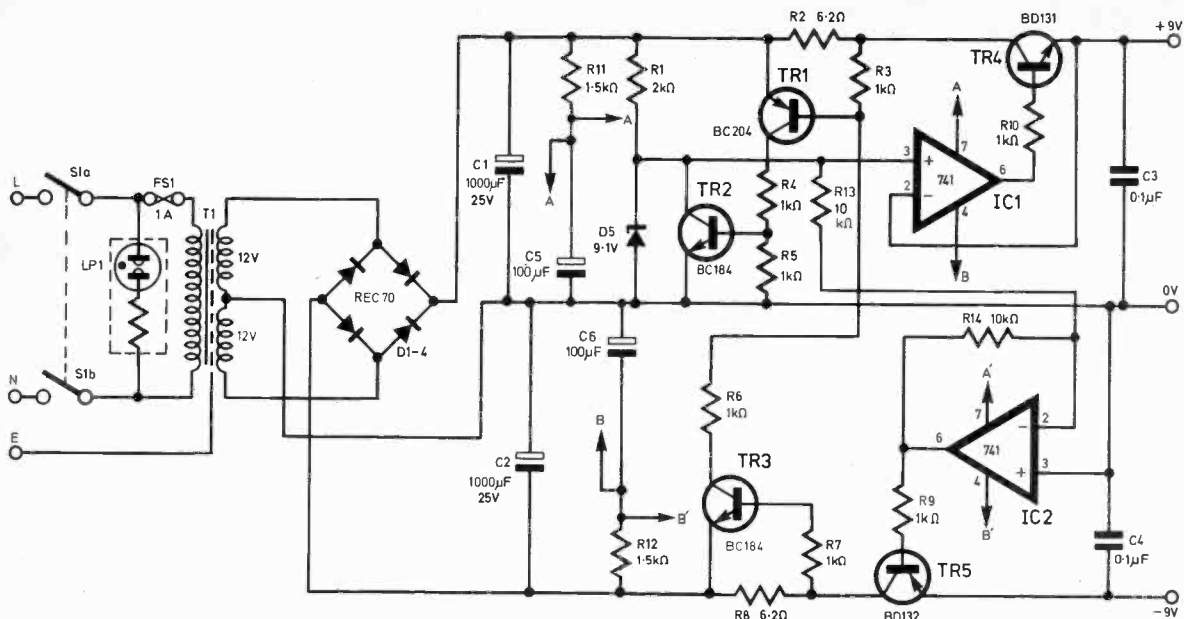


Fig. 4.6. Circuit of a battery eliminator for the Minisonic

POWER SUPPLY UNIT

The Minisonic was designed initially with the younger constructor in mind but it is a fact that, for the more serious experimenter, battery operation is not the ideal. Consequently a fairly simple stabilised power supply has been designed for incorporation into the instrument and is shown in Fig. 4.6.

CIRCUIT ACTION

Positive and negative rails are developed using a dual secondary or centre tapped transformer, a bridge rectifier and two electrolytic reservoir capacitors. D5 is a 9-1V Zener providing a reference voltage to the non-inverting input of IC1 which, in turn, provides drive to the series pass transistor TR4 which is operating as an emitter follower.

IC2 takes its reference from the same Zener diode as IC1 and provides drive to TR5, a complementary version of TR4. The arrangement of TR1, TR2 and TR3 provide short-circuit protection and current limiting.

Under normal conditions there is a minimal voltage drop across R2 and R8 and thus TR1 and TR3 are biased off. In this situation TR2 is also off.

If a short circuit occurs, say between the positive rail and ground, the voltage across R2 will rise rapidly thereby turning on TR1 and TR2.

The effect is to short out the Zener diode and pull down the outputs of IC1 and IC2 to zero volts. The power supply is thus effectively switched off. A similar action takes place if the short circuit occurs between the negative rail and ground or if the positive and negative rails are shorted together.

The values of R2 and R8 are chosen such that current limiting occurs when the demand is in excess of 100mA.

It should be pointed out that, at the time of writing, the performance of the power supply has not been fully evaluated and it may be necessary to make some adjustment to R2 and R8 in order that current limiting commences at the specified demand.

In general it is better to have R2 and R8 larger rather than smaller in relation to the specified value in order that limiting starts earlier. The specified series pass transistors are capable of handling up to 3A so it is unlikely that they would be too unhappy in the event of a short term overload particularly if the recommended transformer rated at 3VA per winding is employed.


PRINTED CIRCUIT BOARD

As mentioned last month, the author has now developed a printed circuit which carries all the Minisonic electronics thus replacing the two Veroboard panels.

This will be available through certain of the advertisers in P.E. including Eaton Audio.

Next month: Making the most of the Minisonic

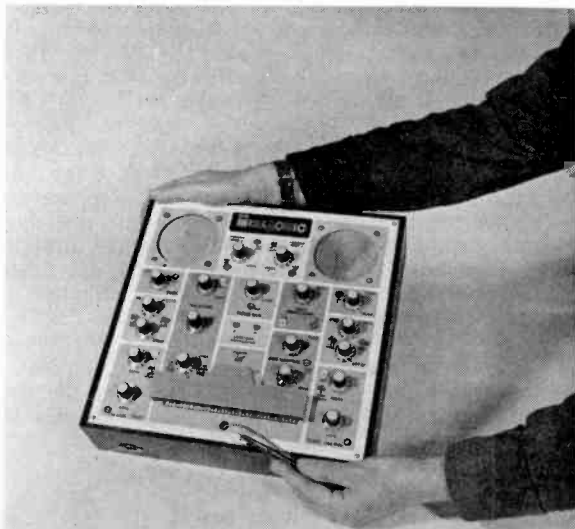The completed Minisonic showing the DIN socket mounted on the front wooden panel




**FREE! INSIDE NEXT
MONTH'S ISSUE**

I.C. IDENTICHART

An easy-to-read directory of popular i.c.s. Provides types and descriptions of hundreds of devices many of which are available through our advertisers.



ULTRASONIC DOPPLER SHIFT INTRUDER ALARM

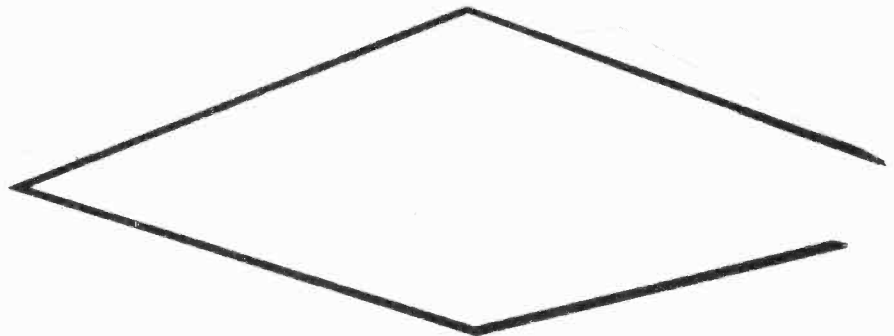

Remember—Prevention is better than cure. Protect a whole room and its contents with one security system using the principal of Doppler Shift to detect objects moving anywhere in an ultrasonic field. A complete system presented in one issue.


PRACTICAL

ELECTRONICS

MARCH 1975 ISSUE ON SALE FEBRUARY 14, 1975

AC/DC MILLI- VOLTMETER

By A.J. WOOLLARD

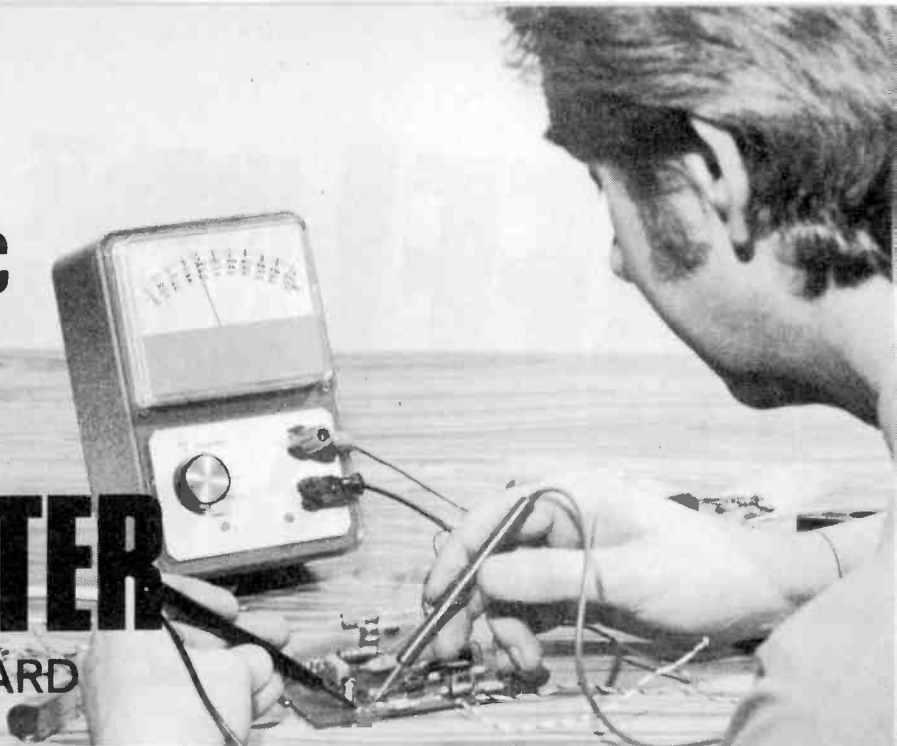

TO MEASURE low voltages across semiconductor junctions or switch contacts it is necessary to have a millivoltmeter with good overload characteristics. The unit described here can measure voltages down to 5mV and withstand 250V a.c. without harm.

SMALL VOLTAGES

The voltage dropped across a diode in the forward conducting mode, or a saturated transistor, is very much smaller than when the device is reverse biased. Also the voltage across a pair of relay contacts when closed varies with the current flowing through the contacts. The potentials for both these examples are almost invariably in the millivolt region and instruments capable of measuring such voltages are not always sufficiently well protected against very large input changes. Such changes occur when a transistor goes from on to off or a pair of relay contacts open. Careful use of integrated circuits and protection diodes allows an economic well protected unit to be constructed.

CIRCUIT THEORY

The instrument is designed around an operational amplifier with very high internal gain which is modified by the addition of external resistors. A.c. output for a.c. measurements is rectified by a bridge circuit to produce a unidirectional movement and indication on a moving coil meter.

OPERATIONAL AMPLIFIER THEORY

An ideal operational amplifier has an infinite voltage gain, infinite input resistance, zero output resistance, infinite bandwidth and zero offset voltage. A differential amplifier amplifies the difference between the voltages applied to its input terminals; a positive voltage at the inverting input produces a negative output, while a positive voltage at the non-inverting input produces a positive output.

Because of the infinite input resistance no current will flow into the amplifier and because of the

infinite gain the differential input voltage, when negative feedback is applied, is zero.

Take the case of Fig. 1, a simple inverting amplifier. Since the differential input is zero, the voltage at the inverting input equals that of the non-inverting input (earth) and therefore the two currents are

$$I_1 = \frac{V_{IN}}{R_1}$$

$$I_2 = \frac{V_{OUT}}{R_2}$$

If no current flows onto the amplifier: $I_1 = I_2$
and $\frac{V_{OUT}}{V_{IN}} = \frac{R_2}{R_1}$

i.e. the voltage gain is dependent only on the values of the external components. Variation of R_1 or R_2 will then vary the gain of the amplifier.

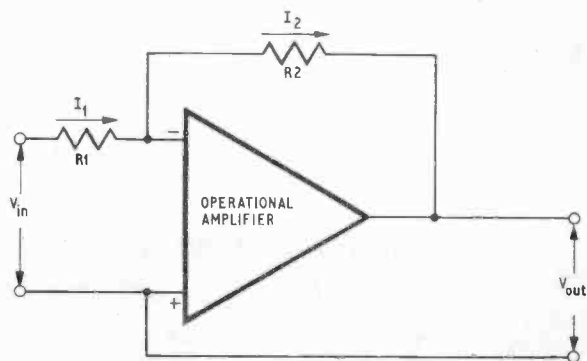


Fig. 1. Input/output relationships in a perfect operational amplifier

CIRCUIT OPERATION

The main gain setting elements in the full circuit, Fig. 2, are R8 and R10, corresponding in part to R1 and R2 of Fig. 1. These resistors should be precision types selected to 2 per cent or better where possible.

With switch S2 in the 100mV position the overall gain of the unit is determined by the ratio $\frac{R10}{R8} = \frac{10^7}{10^5} = 100$. Hence a 100mV signal at the input terminals will produce a 10V signal at the output of the amplifier.

To obtain different ranges, additional resistors R3, R4 and R5 are switched in, modifying the gain to 50, 25 and 10 respectively. These resistors should also be selected to better than 2 per cent. Indeed R4 and R5 are shown here as made up from selected components in series.

Components R11, C3 and C4 are compensation components chosen to keep the loop gain of the system below unity to prevent parasitic oscillation. These components limit the a.c. bandwidth of the meter so that signals up to 1MHz can be measured accurately.

OFFSET COMPENSATION

Although an ideal amplifier produces zero voltage at the output with both inputs earthed, in practice manufacturing tolerances cause an offset voltage to be produced, thus giving rise to an output voltage when both inputs are exactly equal in value.

The resistor chain R6, VR1 and R7 and R9 enable this offset to be compensated and the output set to zero voltage for zero input voltage.

PROTECTION

Diodes D5 and D6 are used to allow the input terminals to be connected to voltages in excess of 250V. By connecting them back to back both +ve and -ve half cycles of a.c. input waveforms are reduced to a safe level at the amplifier input.

To enable a.c. voltages to be read on a simple 1mA d.c. moving coil meter the bridge network D7-D10 is used. Resistor R13 (nominally 10kΩ) is used to obtain a 1mA signal from the maximum

10V output voltage. R13 can be adjusted as necessary to provide a suitable full scale deflection position by, for example, shunting with a large resistor.

POWER SUPPLY

To maintain the accuracy of the unit during periods of supply voltage and temperature variation, a stabilised power supply is necessary. A standard 12-0-12V transformer rated at 20mA is readily obtainable; diodes D1, D2 and Zener diodes D3, D4, together with R1, C1, R2 and C2 provide $\pm 12V$ to the amplifier.

CONSTRUCTION

The choice of mounting methods is largely personal and a die cast box or plastics box are equally suitable. The prototype was built in a commercially available plastics "lunch box".


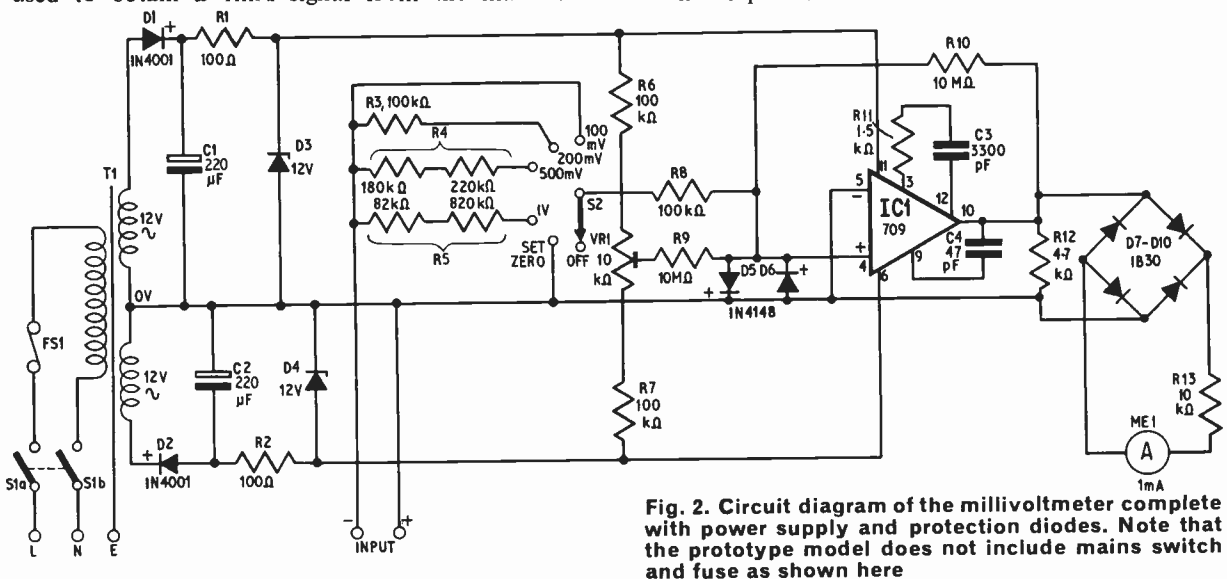


Fig. 2. Circuit diagram of the millivoltmeter complete with power supply and protection diodes. Note that the prototype model does not include mains switch and fuse as shown here

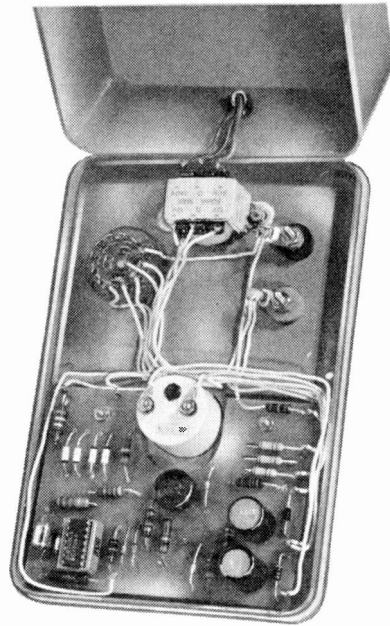

Fig. 3. Component layout for the p.c.b. of Fig. 4


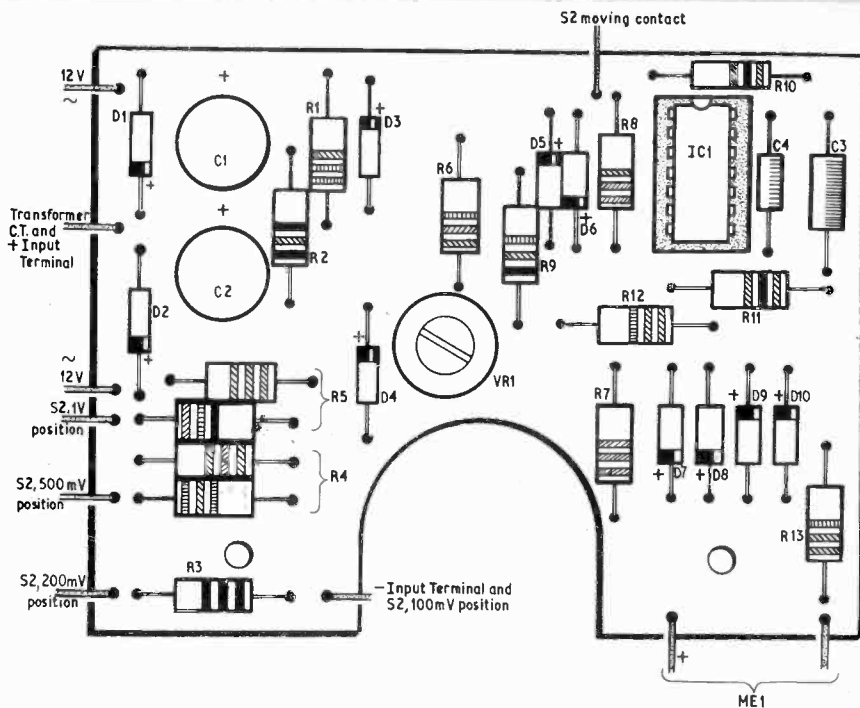


Fig. 4. Suggested p.c.b. layout as prepared for the prototype

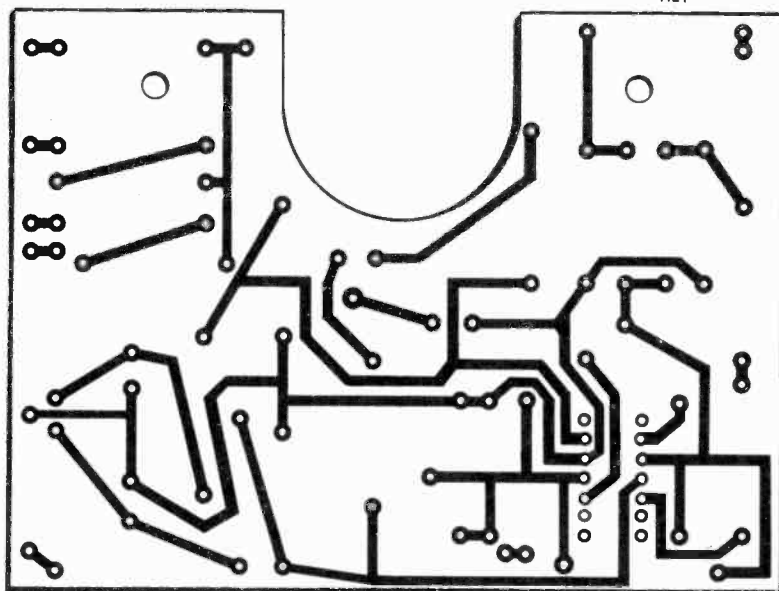

COMPONENTS . . .

Resistors

- R1 100 Ω
 - R2 100 Ω
 - R3 100k Ω
 - R4 180k Ω + 220k Ω \pm 2% $\frac{1}{4}$ W
 - R5 82k Ω + 820k Ω \pm 2% $\frac{1}{4}$ W
 - R6 100k Ω $\frac{1}{4}$ W
 - R7 100k Ω $\frac{1}{4}$ W
 - R8 100k Ω \pm 2% $\frac{1}{2}$ W
 - R9 10M Ω $\frac{1}{4}$ W
 - R10 10M Ω \pm 5% $\frac{1}{4}$ W
 - R11 1.5k Ω $\frac{1}{4}$ W
 - R12 4.7k Ω $\frac{1}{4}$ W
 - R13* 10k Ω $\frac{1}{4}$ W See text
- All 10% $\frac{1}{2}$ W unless otherwise noted

Potentiometers

- VR1 10k Ω min. pre-set

Capacitors

- C1 220 μ F 25V elect.
- C2 220 μ F 25V elect.
- C3 3,300pF \pm 10% 50V polysty.
- C4 47pF \pm 10% 50V polysty.

Semiconductors

- D1, D2 IN4001
- D3, D4 12V Zener 300mW
- D5, D6 IN4148
- D7 to D10 1B30 or OA91, should be germanium for minimum voltage drop
- IC1 709 operational amplifier

Switch

- S1 D.p.s.t. mains switch
- S2 Single pole 6-way

Transformer


- T1 Primary 240V, Secondary 12-0-12V, 20mA

Meter

- ME1 0-1mA f.s.d.

Miscellaneous

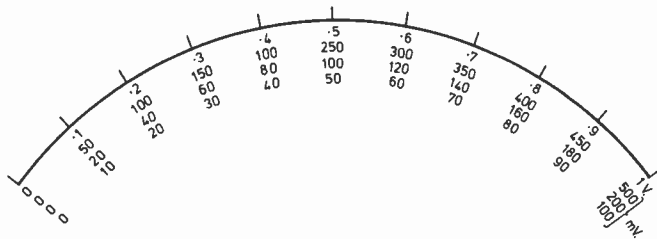- Case; knob; 2 insulated terminals; mains cable; miniature screened cable; copper clad board; cable retaining grommet; i.c. socket; solder tags: nuts and bolts. FS1, 2A



The scale used with a 1mA meter movement

COMPONENTS . . .

CALIBRATOR

Resistors

- R14 2.2k Ω \pm 5% $\frac{1}{4}$ W
- R15 2.2k Ω \pm 5% $\frac{1}{4}$ W
- R16 6.8k Ω \pm 2% or better, $\frac{1}{4}$ W
- R17, R18, R19 9 off 100 Ω \pm 2% or better, $\frac{1}{4}$ W
- R20 See text
- VR2 10k Ω min. pre-set

Semiconductors

- D11 5.1V Zener diode
- TR1 Any small signal p.n.p. transistor. See text

Meter

- ME2 0-1mA f.s.d.

Miscellaneous

- Board; wire etc.


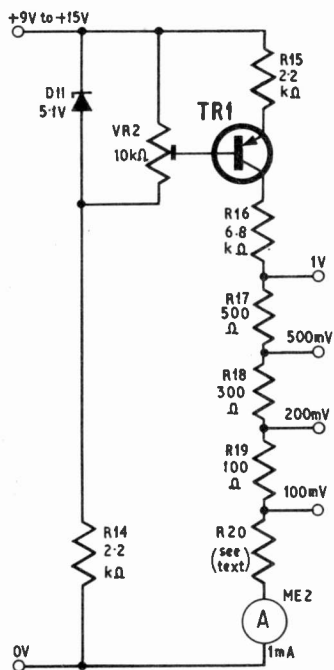
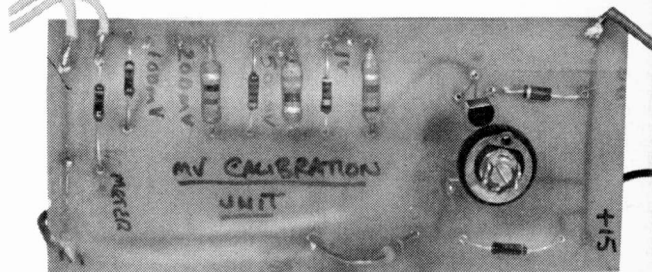


Fig. 5. A millivolt calibrator suited to checking the range f.s.d.s on the millivoltmeter

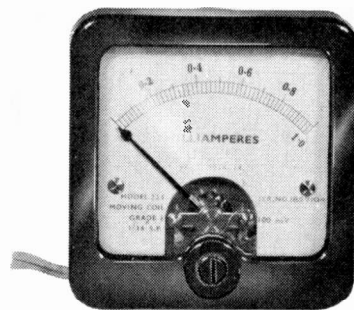

The millivolt calibrator with the circuit made-up on a small p.c.b.

The most consistent results will be obtained if a printed circuit board layout is used, and advantage was taken in the prototype to try out the new fibre pens with etch resisting ink. A suitable p.c.b. layout for the circuit board is shown in Fig. 4 and a component layout in Fig. 3. It is suggested that an i.c. socket is used.

The mains transformer is best mounted away from the meter to prevent stray magnetic fields from affecting the calibration.

CALIBRATION


One of the major problems in having made the millivoltmeter is to ensure that it reads correctly. If precision resistors have been used for gain selection then the meter will read to within \pm 5 per cent. However if the only resistors available are \pm 10 per cent then a calibration procedure will be necessary.

It is first necessary to find a source of 100mV, 200mV, 500mV and 1V to enable the full scale deflection points to be marked and one way of doing this is to use the circuit shown in Fig. 5. TR1 can be any small signal *pnp* type with a reasonable gain at 1mA. The meter shown can be the same as that used in the millivoltmeter. Resistor R20 should be selected such that R20 + meter resistance = 100 Ω . To obtain accurate calibration the chain of 100 Ω resistors should be as close a tolerance as possible.

Next, with S2 in the "set zero" position shorting the amplifier inverting input to 0V via R8, VR1 is adjustable so that 0 meter current flows. Now calibration of each range occurs, starting with the lowest.

Should the millivoltmeter not produce f.s.d. when the 100mV calibration voltage is applied with S2 in the 100mV position then resistor R8 should be modified by adding series or parallel resistors. Similarly R3, R4 and R5 can be adjusted to provide correct f.s.d. for their respective ranges.

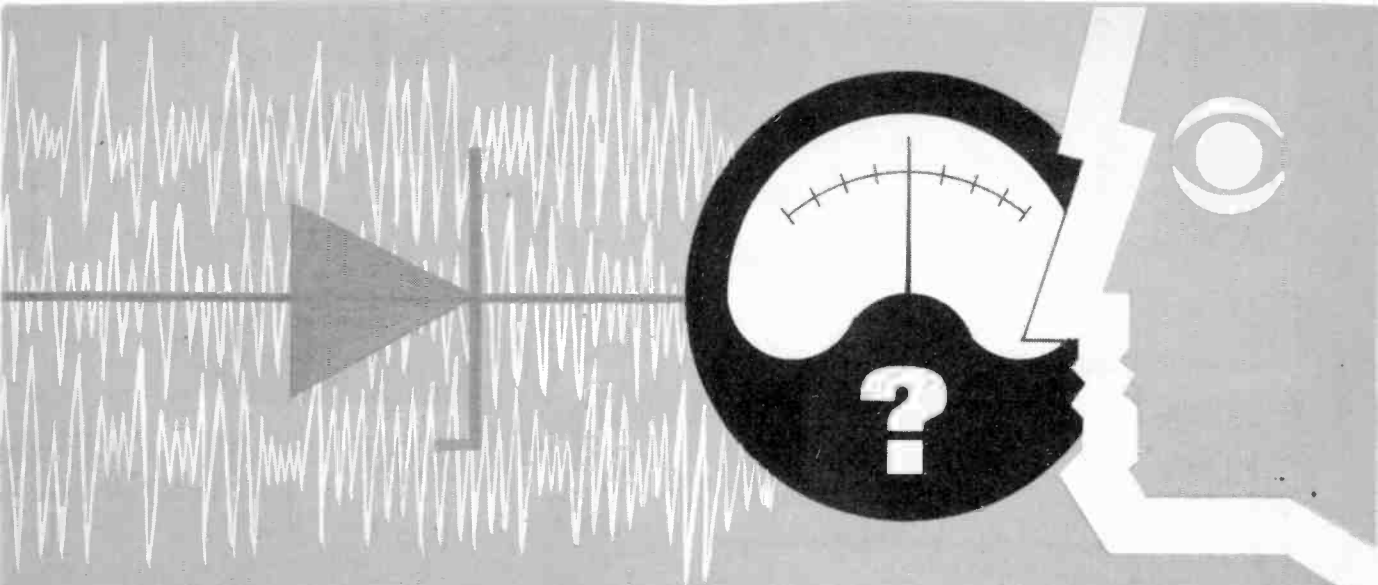The unit should always be zeroed in the "Set Zero" position before calibration is checked. ★



Probability Anomaly Detector

By A. RUSSELL

IS IT possible to influence physical things by the power of thought? Using the Probability Anomaly Detector described in this article, it may be possible to provide evidence that mind can affect matter.

ZENER NOISE

When a Zener diode is biased near to its breakdown voltage, microplasmas form within the diode. Microplasmas are small areas of high ionisation created by radiation such as light. These microplasmas occur at random and cause small fluctuations in the voltage appearing across the diode.

If the power of thought is capable of influencing the photons which cause the microplasmas, then the circuit of the Probability Anomaly Detector (P.A.D.) should be able to detect the effect.

The noise from a Zener diode is used to trigger a Schmitt trigger when it exceeds a certain voltage. The output of the Schmitt is sampled at regular intervals and used to trigger a bistable, the output being fed to an integrator.

If the output of the Schmitt is purely random, i.e. the probability of being in one state is exactly equal to that of being in the other, then the output of the integrator, monitored by a meter will be zero. However a sequence of one particular state will cause the meter reading to rise. A scale has been prepared indicating the probability of a particular meter reading so that the amount of influence a subject has can be estimated.

CIRCUIT DESCRIPTION

The complete circuit of the P.A.D. is shown in Fig. 1. A Zener diode D1 is biased by R1 so that a spiky voltage appears across it. These voltage variations show the creation and destruction of microplasmas within the diode.

COMPONENTS . . .

Resistors

R1	100k Ω (see text)	R9	2.7k Ω	R17	10M Ω
R2	15k Ω	R10	15k Ω	R18	10M Ω
R3	220k Ω	R11	100k Ω	R19	22k Ω
R4	1k Ω	R12	15k Ω	R20	100k Ω
R5	10k Ω	R13	39k Ω	R21	15k Ω
R6	15k Ω	R14	1M Ω	R22	22k Ω
R7	1.5k Ω	R15	1.5k Ω	R23	22k Ω
R8	10k Ω	R16	10M Ω	R24	100k Ω
All	$\pm 10\%$ $\frac{1}{4}$ W carbon	R25	12k Ω		

Potentiometers

VR1	50k Ω	} vertical skeleton preset
VR2	10k Ω	
VR3	100k Ω	

Capacitors


C1	0.1 μ F	C5	2.2 μ F 100V paper
C2	0.1 μ F	C6	0.047 μ F
C3	10 μ F 15V elect	C7	0.047 μ F
C4	0.47 μ F		

Semiconductors

D1	10V 400 mW Zener
D2, D3	EC403 (2 off)
D4, D5	TIL209 or similar light emitting diode (2 off)
D6-D9	EC403 (4 off)
TR1-TR3	BC108 (3 off)
TR4	ZTX500
TR5-TR8	BC108 (4 off)
IC1	Type 741 8-pin d.i.l.

Miscellaneous

ME1	50-0-50 μ A meter
S1	Momentary contact pushbutton
S2	Double pole on/off
B1, B2	9V battery PP3 (2 off)
	0.1in matrix Veroboard 5in x 2.7in
	Suitable case

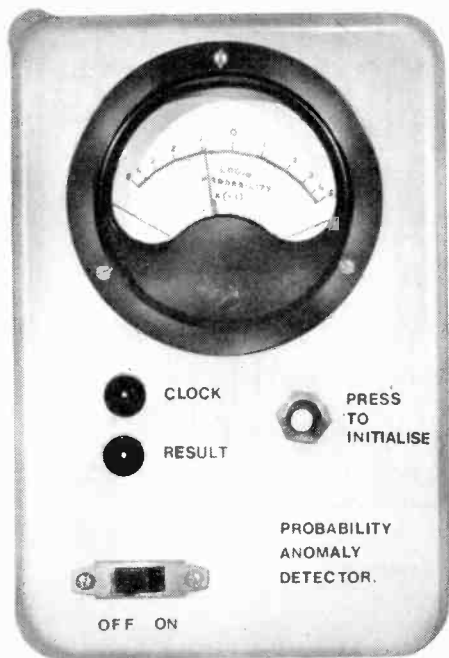

Front view of the prototype Probability Anomaly Detector

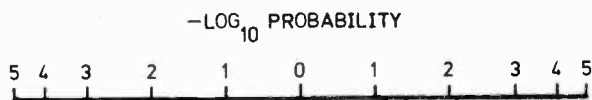


Fig. 2 Meter calibration

The diode voltage is amplified by TR1 and then used to fire the Schmitt trigger, the threshold at which it fires being adjustable by means of VR1.

Transistors TR5 and TR6 form an astable multivibrator which produces short pulses separated by about a second. Transistor TR4 acts as a gate which feeds the output of the Schmitt (controlled by the multivibrator) to the bistable TR7, TR8. After a burst of noise, suitably shaped by the Schmitt, the bistable takes up one of two states: either TR7 conducts and TR8 does not, or vice versa.

If no outside influence is operating the state of the bistable is determined at random. IC1 and C5 form an integrator. C5 charges or discharges depending on the state of the bistable so that a sequence of one state or another will cause a voltage to appear at the output of IC1 with a polarity depending on which state is repeated. The meter scale is suitably calibrated according to the passage of time (see Fig. 2).

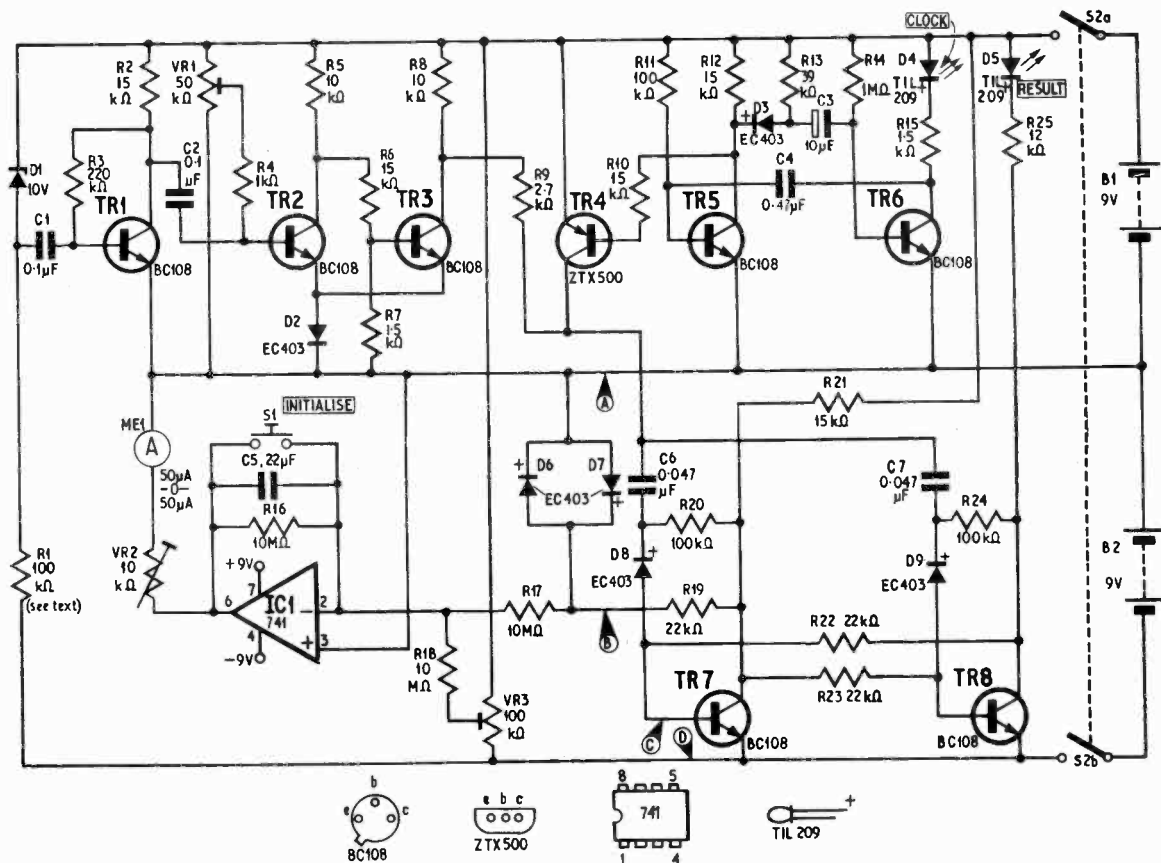


Fig. 1. Complete circuit of the Probability Anomaly Detector

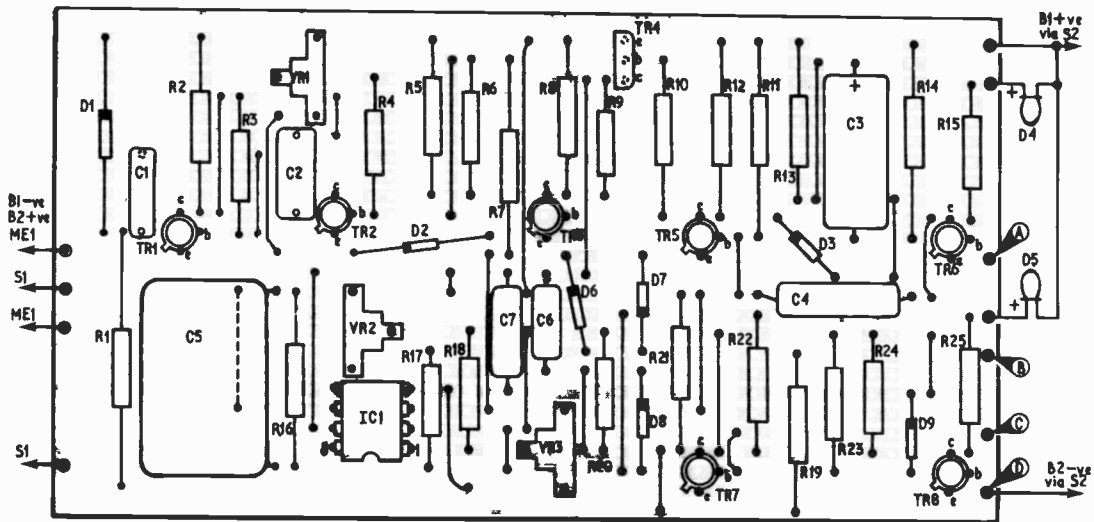


Fig. 3 Circuit layout on the Veroboard

To work out the calibration a computer simulation of the P.A.D. was created and after three days simulated operation figures were obtained as to how often certain sequences were likely to occur. The prototype used a $50\mu\text{A}$ - 0 - $50\mu\text{A}$ meter ME1 as the output indicator. For extra information as to the working of the circuit two l.e.d.s D4 and D5 were used to indicate the occurrence of the pulse from the multivibrator and the outcome of each trial, i.e. the state of the bistable after the gating period.

CONSTRUCTION

The circuit can be built on 0.1in matrix Veroboard as shown in Fig. 3. The front panel layout is shown in the photograph, but layout is not at all critical. For testing the circuit a crystal earpiece was found to be an invaluable aid.

SETTING UP

Once the circuit has been built the following procedure should be used for setting up. First the output of TR1 should be monitored with the earpiece and R1 adjusted until the noise is a maximum.

Next VR1 should be set so that the Schmitt triggers on the noise from TR1. This can be done by setting the wiper at 0V, connecting the earpiece between TR3 collector and 0V, and turning up VR1 until oscillation is heard.

Next points A and B should be shorted and VR3 adjusted until the meter ME1 reads zero.

Points A and B are disconnected and points C and D shorted. VR2 is then adjusted so that the meter reading rises from 0 to 2 in 10 clock pulses.

USING THE P.A.D.

After resetting the P.A.D. by pressing the INITIALISE switch S1 the experimenter should concentrate on the meter and try to force it to a high reading in a particular direction.

If a high reading does occur, the experimenter should then try to get a high reading in the opposite direction, thus eliminating the possibility of drift in the P.A.D.

If the state of the P.A.D. was purely random then it would be expected that the meter reading would be as follows:

- Above 0 almost always
- Above 1 1/10th of the time
- Above 2 1/100th of the time
- Above 3 1/1000th of the time, etc.

The higher the meter reading the more unlikely is the possibility that the cause is of a random nature.



**DO YOU KNOW SOMEONE
WHO IS INTERESTED IN
TAKING UP ELECTRONICS?**

Then why not introduce them to


**everyday
electronics**

— the ideal magazine for beginners

★ **REGULAR DOWN TO EARTH
FEATURES ON THEORY
AND CONSTRUCTION**

★ **MANY INEXPENSIVE, EASY
TO CONSTRUCT PROJECTS**

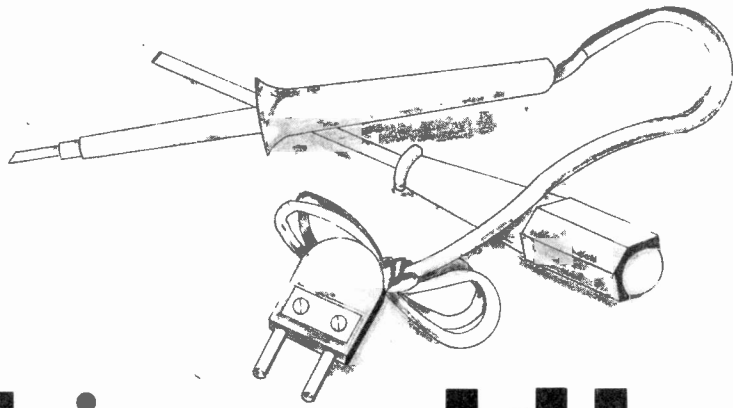**ON SALE THIRD FRIDAY OF
EACH MONTH. PRICE 25p.**



This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.


1

Build an oscilloscope.

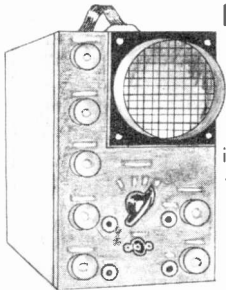

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2

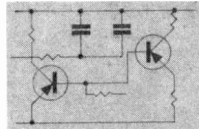

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.


3



Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS

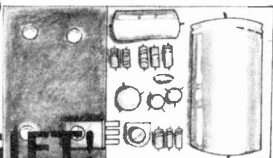

FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept EL25
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)

DISCO, SHOP, SOUND TO LIGHT, STAGE PHOTO-FLOOD LIGHT FITTINGS

TYPE B 3-BANK UNIT

Has two brackets to accept P/C Board. Transformers. Also has holes in ends for Potentiometers. Jack Socket. Cable, etc. Ideal for making Sound to Light and Strobes. Base Cover included. Less Lamps. only **£6.50**

inc. VAT. P. & P. 40p.

SOUND TO LIGHT

Three channel, using Type B unit. Ideal for small disco's and home entertainment. Complete with Lamps. Ready wired. **£25**

inc. VAT. P. & P. 40p.

STROBE UNIT

Using Type B unit. Adjustable frequency. Single knob control. Complete with Lamps. just plug into mains—that's it. **£25**

complete, inc. VAT. P. & P. 40p.

100 WATT SPOT LAMPS

Red. Pink. Green. Yellow. Blue. Violet. Clear. Only **80p**

each Minimum 3 Lamps = £2.40 inc. VAT, P. & P. 25p per 3.



ONLY **£1.50**
inc. VAT
Less Lamp
Plus 25p P. & P.
each

TRAFALGAR SUPPLIES

Dept H.T. · Standish Street · Burnley · Lancs

"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can

be applied to give DC. to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC (synchronous) operation at 120V 50Hz. Speed 60 rpm at 60Hz. 72 rpm. STEPPING Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions dia. 4" body length 4 1/2" spindle length 2 1/2" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. **OUR PRICE ONLY £15**

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant. Ideal for P.C.s. Size: 12" x 12" 24" x 12" 24" x 24" FULL SHEET 43" x 37" (11 sq ft.) Single-sided Copper with thickness of 3/64" Also double-sided 1/2" x 1/2" £1 per sq ft. Cut sizes (1-10 sq. ft.) 25p P. & P. Full Sheet £3 each. Carr. £1 for 1st sheet plus 25p each additional sheet.



SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging device, etc. Size (60 DB) 1/2" x 1/2" x 1/2" (80 DB) 1/2" x 1/2" x 1/2" Ex-equipment, all tested £1.20 each P. & P. FREE

Ultra PRECISION CENTRIFUGAL BLOWER by Air Control Ltd.



30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 V a.c. Very powerful and silent running. 5 1/2" dia. 3" inlet dia. Outlet flange 3" x 2 1/2". Limited number only £8.95. P. & P. 40p.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged elbow. Bracket incorporates 2 fixing screws. Length of arm 2 1/2". 240V AC Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

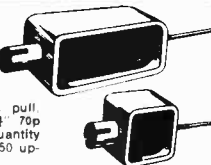240AC type MM6. 3lb pull. 2 1/2" x 1 1/2" x 1 1/2". Travel 1" 90p each P. & P. 10p. 240AC type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1 1/2". Travel 1" 70p each P. & P. 10p. Quantity discounts 10-50 10%, 50 upwards 25%.



OPEN FRAME SHADED POLE GEARED MOTORS

(Dural gear case) 240 AC. 28rpm. NEW HIGH TORQUE, approx. overall size 3 1/2" x 2 1/2" x spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but SLIGHTLY SMALLER) £2.70. P. & P. 30p.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1/2amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8; 100 for £15.50. FREE P. & P. over 10.

AMPEX 7.5V. D.C. MOTOR

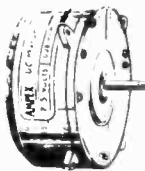


An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm = speed adjustment. Internal A/R/F suppression 1/2" dia. x 1" spindle. motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Quantities available. Mu metal enclosure available 75p each. FREE P. & P.

ALL PRICES INCLUDE V.A.T.
Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

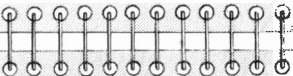315/317, EDGWARE ROAD, LONDON, W2.
Tel: 01-723 5667 01-402 5580



INDUSTRY NOTEBOOK

By Nexus



LOOK TO THE EAST

With what looks at best, a two-year period of stagnation ahead in Western Europe and North America the trade prospects in Eastern Europe suddenly look more attractive to businessmen.

I recently spent over a week in Hungary visiting the first ever all-electronics exhibition in Budapest. Previously, electronics had to take its place with other industries in general trade fairs so MIPEL 74, as it was called, was a great innovation. By Western standards it was a pretty small affair but this suited the eight British companies exhibiting because they then stood out prominently as the largest national group exhibiting except for the Hungarians themselves.

All the fringe countries of the Eastern bloc have growing markets and general expansion in an effort to catch up with the West in living standards. Budapest, for example, has its traffic jams morning and night, neon lights in abundance, plenty of goods in the shops and a general air of well-being. The great leap forward can be traced back to 1968 when the economic system switched emphasis to profitability. Experienced travellers in Eastern Europe tell me that Hungary is the exception rather than the rule but there is no question that the trend is upwards and the demand for Western technology is considerable.

Trading with the East is a laborious business. All orders have to go through state-controlled trading companies and this alone builds up frustration and needs the exercise of much patience. There are problems with the COMECON embargo which limits the level of

technology you can pass on to the East, and the Eastern states are all short of hard currency. But despite all these snags, plenty of companies are finding the effort worthwhile.

A favourite scheme is to set up a sales office in Vienna to serve Eastern Europe but many companies are still able to manage from their home bases or through local agents. What are the rewards? In three years Beckman Instruments have built up a business approaching £1 million a year, Mullard, operating from the UK is doing £100,000 and International Rectifier say they are doing a five-figure turnover in dollars in only two years.

CMOS PRICE DIP

It doesn't seem all that long ago that one of Motorola's gripes was the unrealistic pricing policy in the semiconductor industry. If I remember rightly it was Texas Instruments that was then supposed to be the villain. But 1974 saw Motorola slashing prices of CMOS logic not once, not twice, but three times so that by year-end you could buy Motorola CMOS at only one third the price you paid in January.

It's all to do with the learning curve, yields, volume production and market shares. At the beginning of the learning curve the product is hard to make and yield is low (i.e. rejects are high). Because volume is small, unit costs are high. But once engineers start designing the device into new products, demand rises and because volume is now higher the learning curve is accelerated and yields become greater leading to much lower unit costs. It's almost a predictable pattern which, eventually leads to the happy state of affairs that you can now buy a quad NOR/NAND gate in 100-off quantities for less than the price of a packet of cigarettes.

Motorola say that using three-inch slices has helped the price reductions and the time from design to production has been found to be less than predicted. And that's what the price reductions are all about. But these brave words are not stopping competitors growing fiercely and forecasting a bitter fight for the fast-developing CMOS world market which is expected to overtake TTL in popularity by 1978/79. As one old-timer in semiconductors told me, "you gotta be crazy to stay in this business".

NEW USE FOR DOPPLER

The hole in the road is one of the worst of the British diseases

and the automatically-timed temporary traffic lights to control single lane two-way traffic is one of the most powerful frustrations the motorist has to bear, especially when he can see that nothing is coming from the opposite direction. The temptation is to "jump" the light but frustration and temptation may both soon be a thing of the past if the temporary signals are fitted with a simple Doppler radar assembly.

The idea, put forward by Mullard applications engineers, is to fit the Doppler on top of the traffic lights to detect a moving vehicle approaching. The light will then switch immediately to green provided a similar Doppler radar at the other end of the obstruction detects no movement. It is quite simple to have a delay system and reversion to timed operation in cases of conflict or when traffic is heavy in both directions.

It's another example of expanding the market for electronics. The unit recommended by Mullard is a complete Doppler sub-assembly aimed primarily at the intruder-alarm market. It has an 8mW output and a range of 150ft and the whole transmitter/receiver is on a ferrite substrate only one centimetre square. You choose your own antenna which can be a waveguide, dielectric rod or printed circuit.

MONEY IN KNOW-HOW

Selling know-how is nice business if you can get it. A top performer is International Aeradio whose latest scoop is a contract extension worth £2.5 million for Saudi Arabia for operational and maintenance services for aviation communications at Saudi airports, civil and military.

Another of IAL's specialities is training air traffic controllers from all over the world. The base for this is now Kidlington Airport, Oxford, officially opened by Lord Boyd-Carpenter on November 22 last with the new name of the IAL College of Air Traffic Services. Fees are high, earning a lot of foreign currency and there are no raw materials to import.

Know-how of another kind goes into Britain's most successful avionics export, the range of head-up displays for combat and attack aircraft built by Marconi Elliott Avionics Systems. Latest score is over 2,000 systems exported, mainly to the United States.

QUOTE OF THE MONTH

"There are too many simple answers and not enough simple problems"—John Eger, director of the White House office of Telecommunications Policy, U.S.A.

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

ECONOMICAL TERMINATION FOR HOOK-UP WIRES

In building logic demonstration circuits a large number of terminal sockets are required to provide various interconnections by means of patching leads. The cost of these sockets as well as that of the corresponding plugs can become high enough to discourage would-be constructors.

To overcome this problem I have used a simpler and cheaper alternative.

Each of the sockets for termination is made up of an i.c. pin socket which are available in long strips at about £1 per 100 from a number of advertisers in P.E. These are soldered to the appropriate copper strip of the Veroboard and a piece of thick-walled sleeving about 4mm long, and with a diameter which is

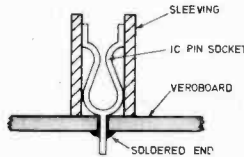


Fig. 1

a tight fit over the socket, slipped over it. (The outer sheath of a two-core cable used in telephone wiring was found most suitable.)

The combination of the i.c. pin socket and sleeving forms an effective termination which accepts single core hook-up wire and component

MAKING PRINTED CIRCUIT BOARDS

Most constructors will agree that the printed circuit method of construction for circuits is by far the most professional looking.

The constructor is faced with many ingenious methods of producing them, from gloss paint and brush to the special acid resistant pens now available. However, to draw or paint p.c.b. designs is a difficult task.

An admirable solution which I suggest is to use Letraset. Sheets of different thickness lines and patterns can be bought at good stationers.

The copper clad board is first cleaned and the design drawn lightly on the copper. Letraset lines are then rubbed over the pencil lines. Where connections are to be made full stops or dots are used for the termination points. When the design is complete the Letraset is rubbed firmly with the backing sheet provided. The p.c.b. is then immersed in a solution of ferric chloride until etched.

The result is a beautifully neat board that only needs cleaning and drilling.

F. Butterfield,
Leeds, Yorks.

leads directly, thus eliminating the need for costly plugs.

The sleeving acts as an insulator and at the same time protects the i.c. sockets from displacement as shown in Fig. 1.

C. S. Soh,
Singapore.

WHEN many devices are fed from a single mains supply it may be necessary to know that all of them are switched off. The circuit to be described illuminates a light emitting diode as long as power is being drawn from any source.

Diodes D2 and D3 are 10A 600V silicon diodes mounted on heatsinks. When current flows, 0.6V is developed across them. The germanium transistor TR1 conducts when 0.2V appears between base and emitter. R2 limits TR1 base current and R3 provides a low impedance path which prevents the induced e.m.f. in the neutral lead from switching on TR1.

The l.e.d. (D1) lights at a mains current of only 2mA and attains full brilliance at 7mA.

S. Beer,
West Byfleet, Surrey.

IN-CIRCUIT POWER DETECTOR


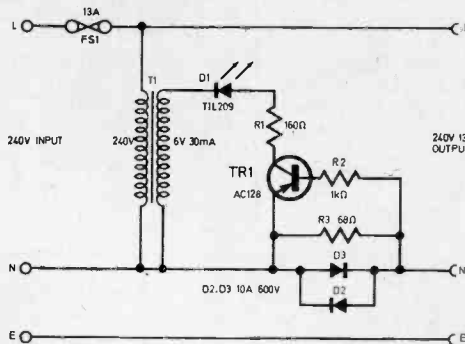


Fig. 1

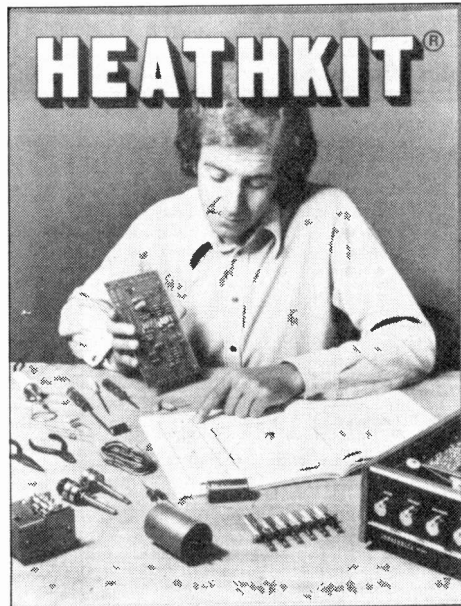Complete the coupon and we'll send you our new catalogue. Completely free.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now and we'll send you your free copy to browse through.


With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.


So, when you receive your catalogue you should have hours of pleasant reading. And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

At either one you'll be able to see for yourself the one thing the catalogue can't show you. Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. PE-25, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

AM/FM digital electronic clock-radio.

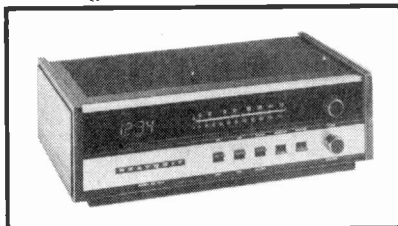

An oscilloscope from the Heathkit range.

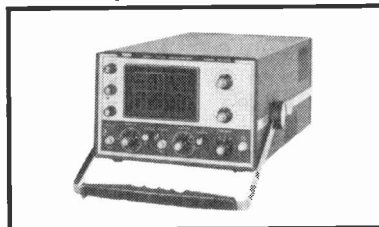

Digital electronic car clock/elapsed timer.




The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. PE-25, Gloucester, GL2 6EE. Please send me my free Heathkit catalogue.

Name _____ Address _____

Postcode _____

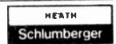Remember easy terms are available with the Heathkit Monthly Budget Plan.



ELECTROVALUE

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

Present

top quality electronic components for price-minded buyers

112p. CATALOGUE · FREE POSTAGE (U.K.) · ATTRACTIVE DISCOUNTS · SPECS. GUARANTEED

A 100 OF THE BEST From our transistor stock

2N1307	47p	BC149C	14p
2N2546	51p	BC158B	15p
2N3053	30p	BC159B	15p
2N3054	60p	BC167B	13p
2N3055	60p	BC168B	12p
2N3702	11p	BC169B	12p
2N3703	10p	BC169C	13p
2N3704	10p	BC179B	26p
2N3705	10p	BC182L	26p
2N3794	18p	BC184L	26p
2N3819	25p	BC212L	12p
2N4062	11p	BC214L	14p
2N4443	93p	BC257A	14p
2N5052	42p	BC259B	14p
2N5163	20p	BCY56	30p
2N5459	35p	BD130	70p
40361	48p	BD131	48p
40362	44p	BD132	52p
40602	46p	BD135	37p
40636	£1-38	BD136	39p
40669	£1-10	BDY20	83p
AC128	17p	BF194	15p
AC151R	36p	BFR39	23p
AC153	27p	BFR79	23p
AC153K	37p	BFX29	23p
AC176	24p	BFX84	37p
AC176K	38p	BFY51	23p
AC187K	21p	BRV39	50p
AC188K	39p	BY164	51p
AD133	£1-92	C106B1	42p
AD136	£1-11	C106D1	47p
AD149	52p	C1406	76p
AD161	42p	MJ481	£1-20
AD162	40p	MJ491	£1-35
AF200U	40p	MJ2955	80p
AF239	60p	MJE371	89p
B1906	36p	MJE521	81p
BA138	31p	MJE2955	£1-12
BB103	24p	MJE3055	68p
BB105	34p	OAS	6p
BB109	48p	SD4	6p
BC107A	16p	TIP31A	70p
BC107B	16p	TIP32A	80p
BC108B	15p	TIP41A	60p
BC108C	15p	TIP42A	£1-00
BC109B	18p	W02	30p
BC109C	18p	ZTX300	14p
BC147A	12p	ZTX304	23p
BC147B	13p	ZTX500	14p
BC148B	12p	ZTX504	45p

100s MORE IN CATALOGUE 7

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in 'Wireless World'. Simple to assemble, fantastically good results and a great money saver. Carries 10 watts RMS, 15 ohms impedance. Size 16in x 12in x 10in. Complete kit, including pack-flat cabinet. £16.90.

The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2.60. Loudspeaker Unit 59RM109, £2.85. Cabinet Kit (to Baxandall design), £11.95. Cross-over choke for additional woofer to above, £1.50.

DISCOUNTS

Available on all items except those shown with NETT PRICES. 5% on orders from £5 to £14.99, 10% on orders £15 and over.

FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders—carriage charged at cost. Giro A/C No.

38/871/4002

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
(see note below)					
C	1/3	4.7-470K	1-3	1-1	0-8 nett
C	1/2	4.7-10M	1-3	1-1	0-9 nett
C	3/4	4.7-10M	1-5	1-2	0-97 nett
C	1	4.7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0.56-3.9Ω	12	10	8 nett
WW	3	1-10K	9	8	6 nett
WW	1	0.22-0.47Ω	16	14	11 nett
WW	7	1-10K	11	10	8 nett

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide ElectroSil TR5 ultra low noise.
WW = wire wound, Plessey.

Values: All E12 except C 1/3, C 3/4 and MO 1/2 W.
E12, 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% ± 0.05Ω below 10Ω and MO 1/2 W 2%.
Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

POTENTIOMETERS

ROTARY, CARBON TRACK

Double wipers for good contact and long working life

P.20 SINGLE linear 100 ohms to 4.7 megohms. each 14p
P.20 SINGLE log. 4.7 Kohms to 2.2 megohms. each 14p
JP.20 DUAL GANG lin. 4.7 Kohms to 2.2 megohms. each 48p
JP.20 DUAL GANG log. 4.7 Kohms to 2.2 megohms. each 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only. each 48p
JP.20 DUAL GANG antilog 10K only 48p
2A DP mains switch for any of above 14p extra

Decades of 10, 22 and 47 only available in ranges above.
Skeleton Carbon Presets. Type PR, horizontal or vertical. each 8p

SLIDER

Linear or log mono 4.7K to 1 meg. in all popular values. each 30p

STEREO, matched tracks, lin. or log. in all popular values from 4.7K to 1 meg. 60p

Escutcheon plates, mono, black or grey. each 10p

Control knobs, blk/wht/red/yel/grn/blue/dk. grey. lt. grey. each 7p

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6.3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	11p	8p	8p
1.0	—	—	—	—	—	—	8p	8p
2.2	—	—	—	—	11p	—	8p	8p
4.7	—	—	—	11p	—	—	8p	8p
10	—	—	—	—	8p	8p	8p	8p
22	—	—	8p	—	—	8p	8p	10p
47	8p	—	8p	8p	8p	8p	10p	13p
100	8p	8p	8p	8p	8p	8p	10p	12p
220	8p	8p	8p	8p	8p	8p	10p	12p
470	8p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	17p	20p	25p	41p	—	—
2,200	15p	18p	23p	26p	37p	—	—	—
4,700	26p	30p	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point. 9mm characters in 16 lead DIL.
Suitable BCD decoder driver 7447 £1-15
3015G showing - or - & 1 & dec. pt. £1-20

LEDS (Light Emitting Diodes) 25p
Photo Cells cadmium sulphide each 40p

ANTEX Soldering Irons

CN240 £2-25 Spare bits 32p
CCN240 £2-65 Spare bits 42p

Order it from Electrovalue for dependable service.

DESOLDER BRAID

6ft strip 66p

WAVECHANGE SWITCHES

1 pole 12 way, 2 pole 5 way
3 pole 4 way, 4 pole 3 way each 33p
TAG STRIP 28 way 11p

NUTS, SCREWS, etc.

In lots of 100 each
4BA NUTS 24p
4BA NUTS 30p
4BA Screws 28p; 1/4" 6BA Screws 24p
Threaded pillars 6BA, 1/4" hexagonal £1-40

Plain spacers 1/4" round £1-12
Other sizes available

ENAMEL COPPER WIRE In 2 ounce reels

16, 18, 20, 22 SWG 34p
24, 26, 28, 30 SWG 40p
32, 34 SWG 46p. 36, 38, 40 SWG 54p

DIN CONNECTORS

2 way loudspeaker	Socket	Plug
3 way audio	10p	12p
5 way audio 180	10p	12p
5 way audio 240	12p	15p
6 way audio	13p	15p

EV CATALOGUE 7

2nd printing—Green and yellow Cover 112 pages, thousands of items—illustrations, diagrams; much useful technical information. The 2nd printing has been updated as much as possible on prices. It costs only 30p post free, including refund voucher for 25p for spending when ordering goods list value £5 or more.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, seconds or sub-standard merchandise is offered for sale. Prices quoted do not include V.A. for which 8% must be added to total net value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.

ELECTROVALUE LTD

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PE2. S.A.E. with enquiries requiring answers.
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone: Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-5.30 daily; Sat. 9-1 p.m.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

BRAKE LIGHT DETECTOR

THE IDEA of the circuit shown in Fig. 1 is to detect when one or both of the brake lights has failed and then turn on a failure warning indicator and to keep this lamp on even after the brake pedal has been released.

When the brake pedal is pressed current will flow through R1 to the lights. This resistor is chosen to drop 0.7V which hardly affects the brilliance of the lights. TR1 becomes forward biased and turns on, holding TR2 off and thus keeping the relay de-energised.

If either lamp fails insufficient current will flow through R1 to cause TR1 to conduct so TR2 will energise the relay. The contacts are wired in such a way as to keep


Fig. 1

LP1 on even after the pedal is released. The relay can be turned off by the ignition switch.

Relay contact RLA2 open circuits TR1 base to reduce TR2 collector current to around 70mA when one or both lamps have failed.

Resistor R1 must dissipate about 1.75W so four 1Ω 2.2W resistors in parallel are recommended. Relay RLA was an RS 12V low profile type, drawing 18mA.

R. Pravel,
Ascot, Berks.

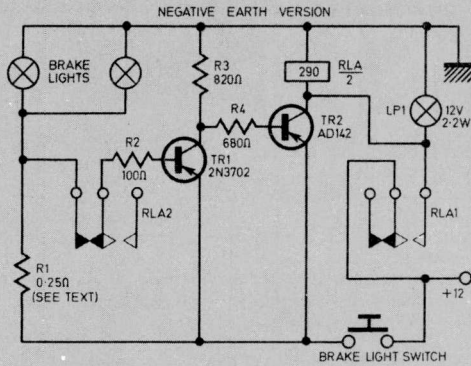

TOUCH TUNER

THE CIRCUIT shown in Fig. 1 was designed as a touch tuner for the P.E. Pushbutton Varicap Stereo Tuner but has not been tested and so is suitable only for the novelty experimenter.

Using skin resistance, two bistables are triggered to feed preset voltages to a Varicap f.m. tuner. By placing one finger on the common positive supply contact and another on one of the three inputs, either TR1, TR2 or TR3 will conduct and the appropriate diodes will direct current to one of the bistables. The

diodes are necessary to prevent interaction between the bistables.

With TR4 and TR7 on, and TR5 and TR6 off, the tuning voltage is set by VR2 as in the original tuner. When TR4 and TR6 are on, and TR5 and TR7 are off, VR3 and R10 are effectively connected in parallel across VR2 so that a lower tuning voltage is selected. Similarly with VR1 and R7, when TR5 and TR7 are on, and TR4 and TR6 off.

One disadvantage of the circuit is that if the radio is turned off the same station will not be returned when switching on again.

Also, it may be necessary to prevent TR5 and TR6 operating together by connecting a small capacitor (say 0.1μF) from their bases to the negative supply line so making sure that on switch-on TR4 or TR7 switch on first.

High gain silicon transistors such as BC109's should be used throughout.

Note that VR2 will always be set to bring in the station with the highest operating frequency. Touch inputs should be kept short and well away from electromagnetic fields such as mains transformers.

R. Keeling,
Loughborough, Leics.

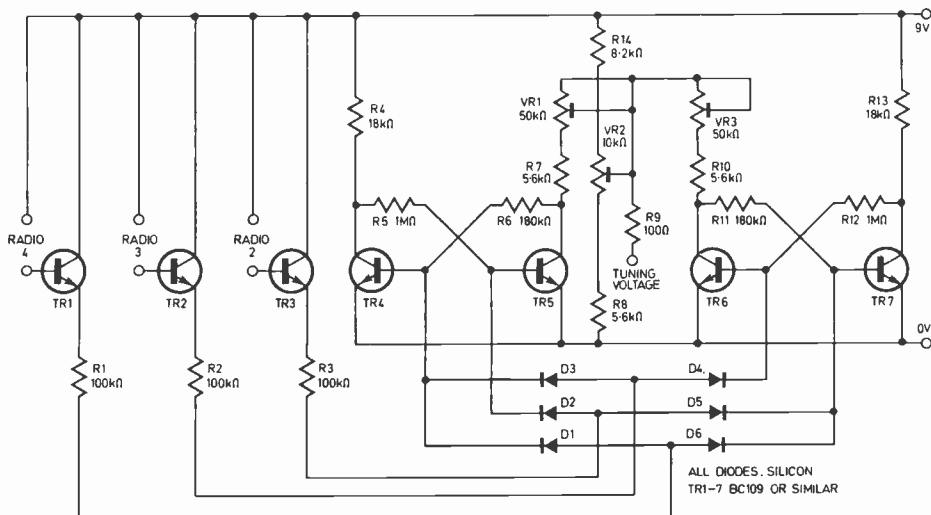


Fig. 1

VOLTAGE CONTROLLED AMPLIFIER

THE VOLTAGE controlled amplifier circuit of Fig. 1 may be of interest to readers as the basis of other control circuits. TR1 is an OC200 or equivalent and TR2 an OC71 or equivalent.

In the circuit, when TR1 base is near ground potential the transistor is held 'off' and thus acts as a resistance in the potential divider chain including R1. As the collector-emitter resistance of TR1 is large compared with the value of R1, the input signal will appear at the base of TR2 and be amplified by that device.

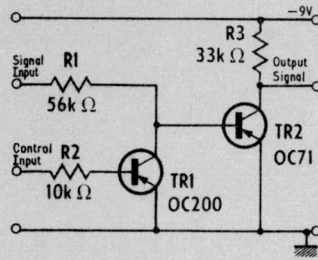


Fig. 1

As the base of TR1 is made positive and the device switched into the 'on' state the input signal will be effectively shorted to ground as

far as the input to TR2 is concerned and thus no output will appear.

Initially the circuit was developed for a synthesiser so decoupling was not important but ideally a capacitor should be used to decouple with the result that only a.c. signals can be passed. The control voltage input can be from such sources as an envelope shaper but it should be remembered that TR1 requires a positive (ground) signal for 'on' conditions. R2 can of course be part of the preceding circuitry if required.

Very little control signal if any at all will appear at the output and since TR2 is floating it will not switch on or off.

P. D. Maddison
Blackburn.

SCHMITT DOES EVERYTHING

FREQUENTLY the home experimenter encounters the need to produce a few circuits cheaply which involves casting around for ideas to minimise the number of components required to fulfil a given circuit function.

It isn't a bad thing to aim for simplicity anyway; you get your results quicker and systems tend to be cleaner and more reliable all round. Readers may find my solution to the need for three pulse type circuits based on a simple Schmitt circuit useful, particularly as the idea is capable of extension. The heart of the system is depicted in Fig. 1 and around this basic circuit it was possible to evolve a relaxation pulse generator, a pulse stretcher and a trigger circuit for a triggered oscilloscope time base.

The detailed circuits evolved appear in Figs. 2, 3 and 4 and from these it can be seen how simple each circuit has become and after a time the building of several systems around the central theme becomes almost second nature. Each can be guaranteed to work on switch on, the required operating conditions can easily be adjusted, and they are cheap.

The circuit of Fig. 2 is a pulse generator. This circuit has operated satisfactorily with $C = 470\text{pF}$ as a fast pulse generator, or $C = 4\mu\text{F}$ and R2 replaced by a relay coil giving a timed contact operation over some seconds. Excellent frequency stability with supply voltage changes is experienced. Transistors are all ZTX 330.

The pulse stretcher circuit of Fig. 3 can accept an input pulse of 1V, 1 μs and this gives an 8V, 30 μs output when $C = 47\text{pF}$. To stretch the pulse further, increase C. All transistors here are 2N3711.

The triggered timebase of Fig. 4 is quite simple. It can be seen from the circuit details that components

are kept to a minimum, and the transistors are a cheap plastic variety. There are endless possibilities by way of variations on the basic theme. The circuit easily converts to a set-reset bistable and the resulting circuits usually allow a marked degree of simplicity to be retained. Why not try a few variations to meet your requirements—it's fun.

A. P. Dixon,
Basingstoke.

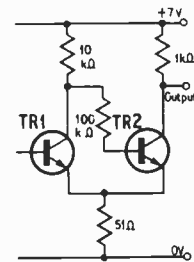


Fig. 1

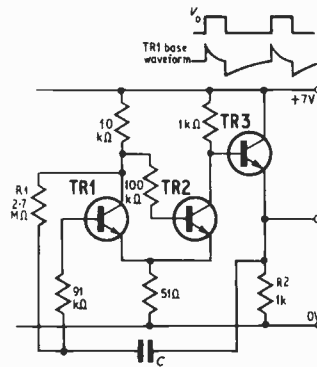


Fig. 2

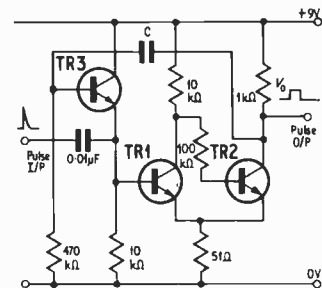


Fig. 3


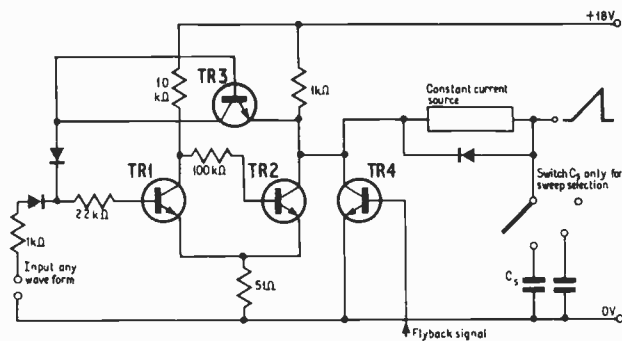


Fig. 4


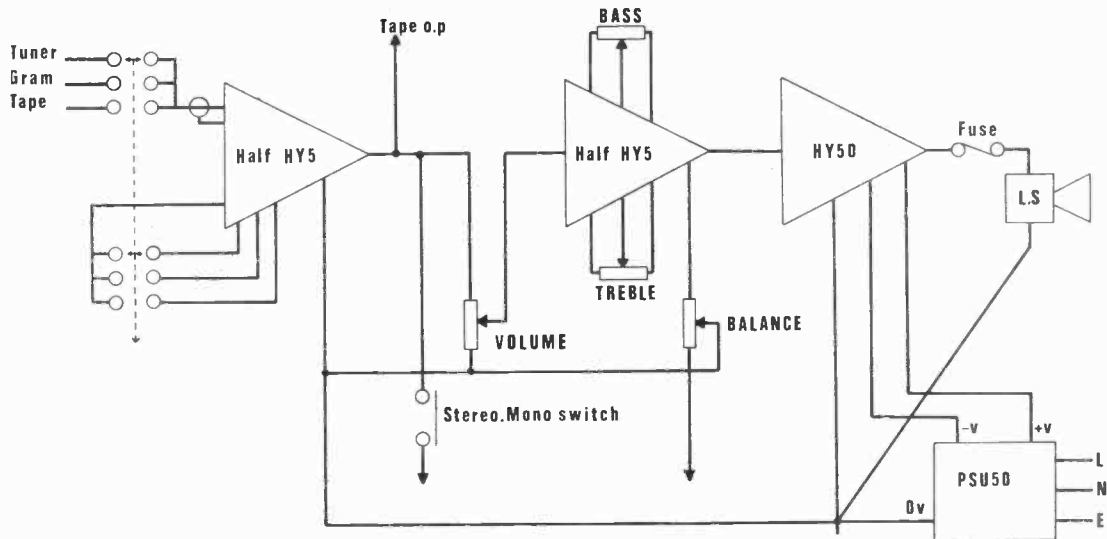


I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!



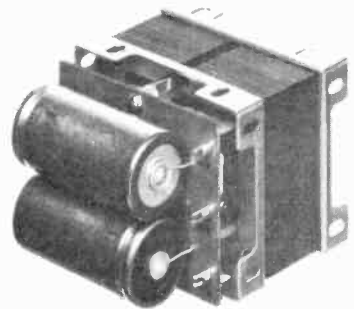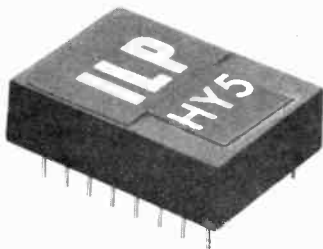MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION
Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input/impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS); Active Tone Controls: Treble = 12db at 10kHz; Bass = 12db at 100Hz; Distortion: 0.5% at 1kHz; Signal/Noise Ratio: 68db; Overload Capability: 40db on most sensitive input. Supply Voltage: ±16-25V.

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided. Input, output, power lines and earth.

TECHNICAL SPECIFICATION
Output Power: 25W RMS into 8 kΩ. Load Impedance: 4-16kΩ. Input Sensitivity: 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically. 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 x 50 x 25mm.

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS
Output voltage: ± 25V. Input voltage: 210-240V. Size: L 70, D.90, H.60mm.

PRICE £4.50

- 36p VAT
P. & P. free

PRICE £5.98

+ 48p VAT
P. & P. free

PRICE £6

+ 48p VAT
P. & P. FREE

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS


I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply
Total Purchase Price
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name and Address
Signature

BI-PRE-PAK

INTRODUCE STIRLING SOUND

Audio Modules

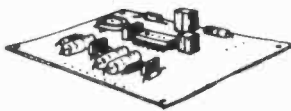


**SS. 203
STEREO
DECODER
£5.62**


Ready built unit, ready for connection to the I.F. stages of existing FM Radio or Tuner. A tell tale light can be connected. The unit is a small printed circuit, no further alignment necessary. An L.E.D. stereo indicating light may be added. Instructions included.
SS. 202 I.F. Unit **£5.25** SS. 201 Tuneable front end **£6.25**.

**SS. 103
I.C. POWER AMP
£1.75**

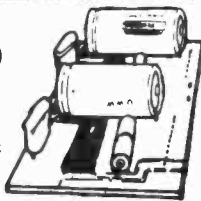These amps. are supplied with a free booklet on connecting up, specifications and easy-to-build projects. SS. 103-3 stereo version (using two I.C.s) **£3.25**.



5W & 10W POWER AMPS

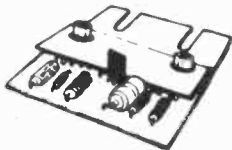

SS. 105 £1.95

SS. 110 £2.40

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/4 in x 1 1/4 in. The 5W Amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts available for quantity orders.

Other SS Modules

Pre-assembled printed circuit boards 2 in x 3 in available in stereo only, will fit 0-15 edge connector.

Stereo Pre-Amp SS. 101 for use with high output ceramic cartridges. **£1.60**

Stereo Pre-Amp SS. 102 for use with low output magnetic cartridges. **£2.25**

Stereo Tone Control SS. 100 active tone control board will give bass and treble boost and cut. **£1.60**

Instruction leaflet supplied with all units. Pots extra.

V.A.T.—Add 8% to total value of order including postage.

POSTAGE—Add 15p for postage and packing (U.K. orders).

B.P.P. Stirling Sound Modules are guaranteed, tested and individually boxed.

Please send

I enclose £..... inc. V.A.T at 8%.

Name

Address

BI-PRE-PAK

Co. Regn. No. 820919

Dept. D, 222/224 West Road,
Westcliff-on-Sea, Essex SS0 9DF.
Telephone: Southend (0702) 46344.

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System - with a big plus over all the other kits - the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy to follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.

Ready Made Unit £14.75 inc. VAT and p & p.

State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only **£28.50 inc. VAT and p & p.**

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from **£50 to £60 inc. VAT and p & p.**

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North

288 ECCLESALL RD., SHEFFIELD S11 8PE (D)

Tel: Sheffield (0742) 668888

PATENTS REVIEW...

COMBINED CCTV CAMERA AND RECEIVER UNIT

Anyone building the P.E. Monochrome CCTV Camera may well consider using it for closed-circuit communications. In BP 1 362 290, S.A. Engels Matra, of Paris, France, points out how CCTV communication, although electronically feasible, suffers from working problems.

The whole object of the exercise is, of course, that the correspondents at each end of the link should be able to both see and hear each other. But for one correspondent to watch the other on a monitor screen inevitably requires each to look at his screen and not at his camera. Hence neither can look the other in the eye! Also, although it is theoretically ideal to be able to illustrate a point with a diagram drawn for the camera, in practice this is easier said than done.

The French inventors propose a variety of mirror systems (of which one is shown in Fig. 1) which enable the camera and monitor at each end of the link to be effectively combined, together with a display surface for a diagram.

At each end of the link a light-tight box houses a receiver display tube and a camera. The optical axis of the camera and receiver are at right angles to each other, but a semi-reflecting plate (i.e. a

see-through mirror) is angled at 45 degrees relative to each. The plate is also similarly angled to a front window of the box, and a lens, which forms an image of a diagram drawn or laid out on a display surface.

A correspondent can look direct into the display tube while being photographed by the camera. So if a similar arrangement is provided at each end of the link, both correspondents will be continually looking each other straight in the eye. Simultaneously, any object laid out on the display surface can be superimposed on the transmitted picture.

Transmission of a reasonable TV picture of a correspondent requires good room lighting and such light can cause unwanted reflections on the display tubes of conventional set-ups. But any room light which passes through the window and is reflected back off the receiver screen to the viewer will be attenuated by its passage twice through the semi-reflecting plate.

IMPROVED PERSONAL RADIO AERIAL

In BP 1 354 710, Motorola Inc of Illinois, U.S.A., explain how there is a problem providing an aerial for a personal radio (e.g. police or paging type), which will operate

BP 1 354 710

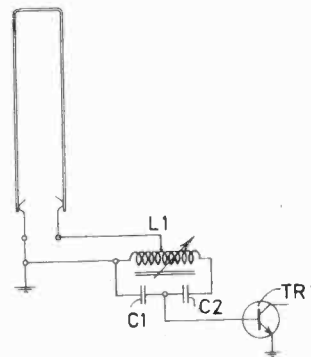


Fig. 1

on the range of 1-500MHz or more. Ferrite rods may be used but they claim that they take up too much space and are highly directional. Motorola suggest using part of the casing of the receiver as the aerial. Although this is not a new idea, the results are claimed to be an improvement over past achievements.

The circuit, Fig. 1, shows a U-shaped metal cover which slides over the moulded plastic casing of a miniature radio receiver. The arms of the U mate with gold plated contacts on the receiver, one contact being connected to earth potential of the receiver chassis and the other to a reactance circuit which includes inductor L1 and capacitors C1, C2. The reactance contact is connected to an intermediate tap on L1 which has a movable core for inductance adjustment.

The reactance or tuned circuit is adjusted to be capacitive at the frequency of operation so that the connections to the U-shaped cover in effect connect a capacitor across the open end. The signal received from the aerial is derived from the reactance network at the common connection between C1, C2 and coupled to the base of TR1 which functions as an r.f. amplifier. Usually the receiver will be carried in a pocket with the earth arm adjacent to the wearer's body.


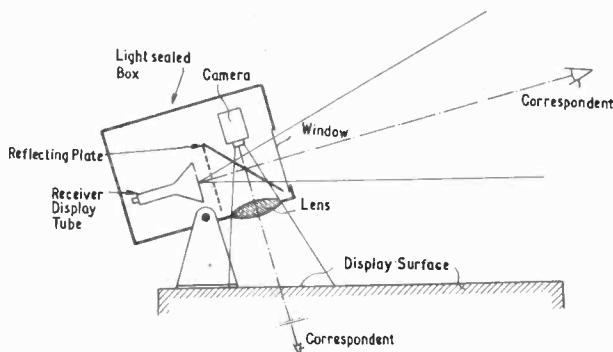


Fig. 1

BP 1 362 290

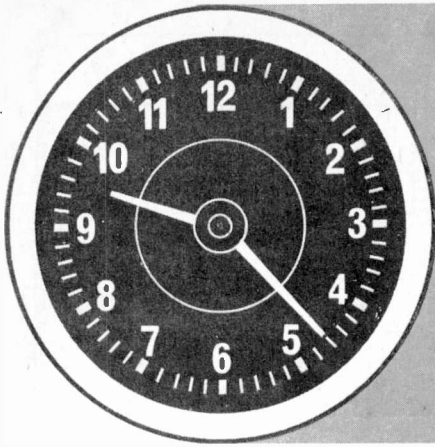Copies of Patents can be obtained from the Patent Office Safes, St. Mary Cray, Orpington, Kent. Price 25p each



CAR CLOCK REPAIRS

By D.L.COOPER

The modification described enables several years' additional life to be obtained from a clock which has failed due to contact wear.

THIS article describes a method of rejuvenating the type of electric clock used in a large number of cars up to about five years ago.

OPERATION OF THE CLOCK

The balance wheel of the clock drives the hands (through suitable gearing) in contrast with most other types of clock where the spring drives both the hands and the balance.

The balance is mounted between the poles of an electromagnet as shown in Fig. 1. When energised the balance rotates against its hairspring. The coil of the electromagnet is energised via a contact pin mounted on the balance, and a contact wiper in the form of a light spring arm.

When power is applied to the clock, current flows through the coil, along the spring arm to the balance wheel contact pin, and through the balance wheel hairspring to the clock frame. This causes the balance wheel to rotate until contact is broken.

The balance then swings back, makes contact, and is attracted in the opposite direction and the sequence is repeated.

WIPER ARM

When the clock is new the length of the wiper arm is set so that the balance wheel has to rotate a certain angle from its rest position before contact is broken. This is to ensure that the electromagnet is energised for long enough to give the balance a good push and keep it swinging vigorously.

However, as the contact wears (due mainly to arcing) the length of time for which the contacts are closed is reduced and the balance swings less vigorously.

In addition, if the contacts become dirty or pitted there may be intermittent contact.

Eventually the push from the electromagnet is not enough to overcome the friction in the bearings.

REPAIRING THE CLOCK

The ideal solution to the wear problem is to drive the electromagnet from a monostable circuit, triggered from the contact of the balance wheel. In this way wear on the contacts is greatly reduced as only transistor base current flows through them.

The period for which the contacts are closed is not important as the current flows for the full monostable "on" period. Dirty contacts have no effect since, once contact occurs to trigger the circuit, full current flows for the monostable "on" period.

CIRCUIT OPERATION

The circuit of the monostable is shown in Fig. 2.

The circuit is triggered when the contact closes, turning TR1 off and TR2 on. When the contact opens, TR2 is held on until the capacitor C1 charges via R1 and allows TR1 to conduct, whereupon TR2 turns off.

Diode D1 suppresses the reverse voltage transient in the coil after switch-off, protecting TR2. The values of C1 and R1 in Fig. 2 give an "on" time of about 20 milliseconds after the contacts open.

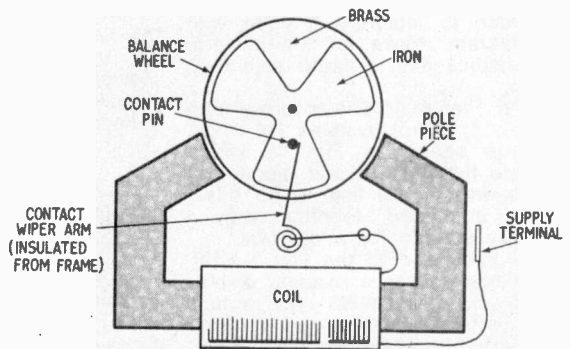


Fig. 1. Diagram showing the balance wheel mounted between the poles of the electromagnet in a typical car clock

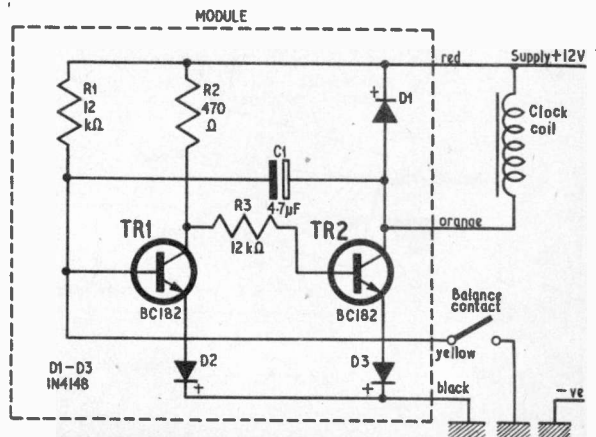


Fig. 2. Circuit of the car clock monostable

The circuit shown is for negative earth only and for positive earth cars all the diodes and C1 *must be reversed* and the transistors replaced by *pn*p types suggested in the components list.

All components must be miniature types to enable the finished circuit to fit inside the clock case.

The circuit is built up without a board for maximum compactness, component leads being soldered directly to each other. Thin coloured insulated wire should be used for the leadouts.

Once the module is completed it should be tested with the clock.

FITTING IN THE CLOCK

The clock must be removed from the car. The method of mounting varies but is usually a U-shaped clamp and two nuts accessible from behind the dashboard. Disconnect the supply leads to the clock, and the light if fitted.

Undo the four (or three) screws, washers, and rubber bushes on the back of the clock and remove small screw retaining the supply wire on the terminal post. Carefully prise off the chrome ring retaining the plastic face of the clock, sliding the face and clock mechanism out of the metal case.

The clock is very delicate and great care is needed if irreparable damage is not to be done, particularly to the balance wheel.

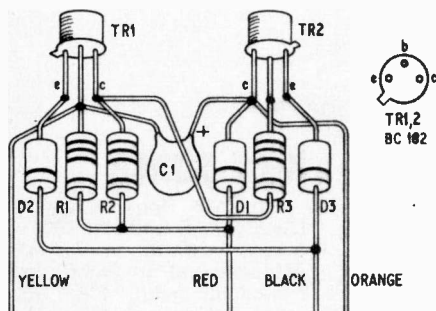


Fig. 3. Construction of the monostable module. After thorough testing this can be encapsulated in resin or insulating tape

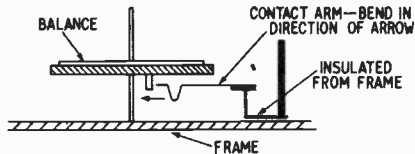


Fig. 4. Diagram showing the direction in which to bend the contact arm if the contact is at fault

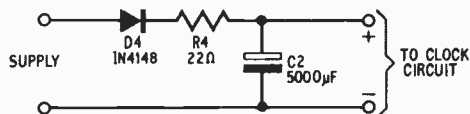


Fig. 5. Voltage regulator to keep the voltage constant while the starter is operated (Reverse D4 and C2 for the earth)

COMPONENTS . . .

Resistors

R1 12kΩ R2 470Ω R3 12kΩ R4 22Ω
All $\pm 10\%$ $\frac{1}{4}$ W carbon

Capacitors

C1 4.7 μ F 15V elect. (miniature or tantalum bead)
C2 5,000 μ F 15V elect.

Diodes

D1-D4 1N4148 (4 off)

Transistors

TR1, TR2 BC182 (-ve earth version) or
BC212 (+ve earth) (2 off)

Miscellaneous

Sleeving
Resin for encapsulation

Unsolder the coil lead from the contact pin connection and connect the four leads from the monostable: red to the supply side; orange to the coil lead unsoldered from the contact pin; yellow to the contact pin; and black to the clock frame. Leave the leads fairly long at this stage.

TESTING

Connect the 12V supply between the supply pin and the clock frame in the correct polarity and gently spin the balance wheel.

If the clock keeps running for a few minutes all is well; if it stops check the monostable connections. If they are all correct temporarily short circuit the contact pin to the frame which should cause the balance to be attracted to one extreme of its travel. If it is, then the contact is at fault. Using tweezers or long-nosed pliers, very carefully bend the spring contact arm slightly closer to the balance wheel contact pin (see Fig. 4).

Check by applying 12V again.

ENCAPSULATION

When the clock is running properly, disconnect the four leads from the clock and either encapsulate the module by dipping in polyester resin or Araldite.

The completed module should be small enough to fit inside the clock case. Cut the leads to length and reconnect as before.

Replace the clock in the case making sure that the module and wires do not foul the mechanism. Fit the screws in the back and replace the chrome ring retaining the face ensuring that the knobs for hand setting and regulating are properly fitted.

Check again that the clock is still working and replace in the car.

VOLTAGE REGULATOR

If any trouble is experienced when the starter is operated this may be due to the fact that operation of the starter causes the battery voltage to fall so much that the clock stops. A capacitor and diode can be used to keep the voltage at the required level.

Connections are shown in Fig. 5.

It will probably be found that the clock runs fast after modification but this can be corrected with adjustment provided on the clock. ★

Readout —

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

Stirring sounds

Sir,—I read with great interest the letter of your correspondent Mr. I. Stuart-Colwill in the December issue of P.E. There is nothing like a little controversy to get the blood stirring and whilst I would tend to go along with a number of Mr. Stuart-Colwill's comments I must say that I do not agree with all of his arguments.

As a starter I would agree that music is wallowing in the primeval mud—but no more so than any other art form. And I only agree with this sentiment in the sense that there are a great many musicians and composers who are struggling to express themselves in their chosen medium and in a way that can be understood by those of us who do not possess their gifts. That escape is possible from this "slough of despond" is clearly demonstrated by the works of such giants as Albinoni, Bach, Beethoven—yes, even Stravinsky and Schoenberg.

If one thinks about it at all, one comes to the inescapable conclusion that all acoustic instruments in use today are merely sophisticated versions of simple devices designed to imitate phenomena occurring in nature. Hence Malcolm Pointon's reference to natural sound, i.e. sound produced by physical processes such as a vibrating string—or column of air—or reed. This being the case one marvels all the more that with instruments of limited dynamic range and tone-colour, composers such as those cited above have managed to transcend all subjective aural boundaries and are still able to communicate emotionally with anyone who cares to listen.

The word "imitate" is a crucial one in reference to any art form. Thus there is no relevancy in the kind of fatuous remark made recently by one well-known critic on the BBC when he said that "All synthesisers sound alike." So too do all grand pianos—so what? It is not the instrument that matters so much as the performer's grasp of its potentiality and his ability to translate this into aural terms.

I agree wholeheartedly with Malcolm Pointon's view that the second half of the twentieth century is emancipated in a musical sense. Thanks to Robert Moog and his predecessors who pointed the way we now have musical instruments the like of which could not possibly have been imagined 20 years ago. With a dynamic range greater than a whole symphony orchestra, a frequency range encompassing the whole of the audio spectrum and a range of tone colour which defies classical description the synthesiser quite literally does make the aural universe boundless.

No, Mr. C, 1974 was not marked by your acquisition of a synthesiser. It was marked by the fact that hundreds of others like you also acquired one. Many will fall by the wayside, many will be content with imitative creations and many with cheap divider organs. But it only takes one composer with the imagination to transcend the current trend in synthesiser gimmickry and produce a work of any power at all for the synthesiser to find a firm place in the history of music.

G. D. Shaw,
Huntingdon.

Emancipated synthesiser

Sir,—How gratifying it was to read Mr Stuart-Colwill's letter "Discord" (*Readout* Dec '74). I wholeheartedly agree with his views of electronic pop. How many times must we hear facile popular ditties (thumped out by people who are mistakenly regarded by many as "musicians") performed in a pseudo organ tone and sickly tremelo, on instruments which could do so much to change the history of music?

Perhaps we are offended even more by the frequency with which people, when the synthesiser is mentioned say, "Oh! that thing that

plays all the Bach." Maybe I'm a musical snob, but I look on the pseudo-organ effect which is so often used with so little variation or modification in interpretations of Bach on synthesisers, as a detriment to the instrument and a slight to Bach. Would not Bach have fumed to see such an instrument shackled? We know that he was a keen experimenter and I personally doubt whether he would have forgiven the ravishes of the all too popular "Switched on Bach" records in which so little variation of effect is found.

Finally, I believe that the next 50 or more years will see a monumental battle for the emancipation of the synthesiser as an instrument in its own right. One only has to look at the influence of the old school of Gauthier and Co on the harpsicord style, to see that such a transfer of idioms is being attempted now, i.e. from organ to synthesiser.

Whilst some transfer is inevitable, total assumption of organ style cannot be allowed. The synthesiser must break away from the protection and influence of the organ and set up its own family.

P. Watson,
Bedfordshire.

New phase

Sir,—Mr Stuart-Colwill's letter (*Readout*, December 1974) is welcome; however in his attempted dampening of my enthusiasm he has missed the point of the article and let himself be carried away by quite a few red herrings.

Here in 1974 there is little doubt that we are in at the beginning of a new phase. Since Moog's musical application of voltage-controlled devices some ten years ago the market for synthesisers has widened considerably, and at this stage, thanks to PE and at least two other periodicals, interest in electronically produced sound has received an additional hefty boost.

Even Stockhausen in the early '50s could not have foreseen this enormous interest in electronic music. Many of his non-electronic works are still shunned by many people who can accept the medium of which, it would seem, only he knew the value. As for "primeval mud", my article implies that any new ideas in musical expression take time to settle and, having eventually settled, begin to develop towards the stage where it is felt that new ideas are needed; the process then starts all over again. Today's composers are still searching

for a distinguishable point of reference.

My apologies for any ambiguity in the phrase "seven modes were employed". I hereby correct this to "seven modes were available". The Locrian mode was, indeed, a rare bird, but without expert musicological evidence I would hesitate to refer to it as a "joke".

Mr Stuart-Colwill's thoughts now fall into rather hot water. With all the will in the world Beethoven could not have produced the aural universe inhabited by, say, Morton Subotnick's "Silver Apples of the Moon". As for dynamic level, even Webern's "pppp" could not, in the very nature of the instruments at his disposal, fall below a fixed minimum level; neither could Wagner or Stravinsky, for all their fortissimi, rise above a measurably fixed maximum level. Under normal concert conditions one does not sit with one's ear rammed into the bell of a brass instrument.

As for the comment about Liszt and Paganini, of course they were deemed "inhuman" a hundred years ago, but ninety-nine years ago people started acquiring the necessary skills; teenage virtuosi these days rattle the stuff off without much sweat-and-tears. I still cannot see men, within the next millennium or so acquiring independent brains within a single skull-case or multi-fingered hands capable of intense rhythmic complexity.*

Finally, I would not go far to hear anyone's lash-up of Ravel's or Stravinsky's exotic scores. I see little point in rehashing—at great expense of time and money—music which is better and more economically performed by acoustic instruments, but then: chacun a son goût. When requested I, too, dish up "synthesised classics", although I admit to treating this kind of work as a useful recreative exercise in exploring the potential of a synthesiser rather than an eminently more satisfying personal creative act.

Anyone who uses a £7,500 synthesiser to imitate a cheap divider organ is welcome to do so. I do not applaud his aural perception but I do envy his bank balance.

Malcolm Pointon

*Read Olaf Stapledon's fascinating look at the far distant future in his two novels: "Last and first men" and "Last men in London" (Penguin Books).

ITT

Sir,—In your issue of October 1974, page 905, under the heading "Big Bad Wolf?" you list the various locations which come under the control of ITT Components Group Europe. One of the locations listed is that at Foots Cray and I feel I

should point out that the Foots Cray site is not wholly directed by ITT Components Group Europe but contains other ITT Divisions such as ITT Semiconductors which is part of the world-wide activity of ITT, reporting directly to the ITT Headquarters in New York.

Roy Atterbury,
Publicity Manager

Our contributor Nexus, replies:

I was confining my comments to ITT Components Group Europe and the fact that ITT Semiconductors at Foots Cray reports direct to New York rather than to Brussels highlights, in my opinion, the different problems of manufacture and marketing of semiconductors as against other components. Semiconductor men need to think and co-ordinate strategy globally to stay in business.

ITT Components Group Europe, however, designs and manufactures quite a high proportion of components specifically for the European regional market and finds this economically successful. There are other factors, too, such as location of R and D facilities and general administration which have a bearing on the location of the control centre.

And although ITT Components Group Europe operates almost autonomously, the famous ITT technique of "business plans", even those originated in Brussels, still have to be ratified by ITT in the United States.

BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

April 1971 to March 1972

Mr. M. C. Knowles, 13 Cassiobury Road, Walthamstow, London, E.17.

March to December 1973

Mr. G. Kilfeather, 13 Woodstock Road South, St. Albans, Herts.

July and November 1969

Mr. M. Pearce, 29 Larmour Road, Grimsby, Lincs., DN37 9HH.

March, April, May, August and September 1973

Mr. S. A. F. Muirhead, 1 Marydene Drive, Kingston-upon-Hull, Yorks.

October 1973

Mr. J. G. McGonnell, The Lodge, Acol Road, London, NW6

January 1973

Mr. C. J. Swinnerton, 32 Bedford Street, Earlsdon, Coventry, Warcs.

July, September, November 1973, February 1971 and 1972

Mr. N. Anderson, P.O. Box 28917, Sandringham (2131) Johannesburg, South Africa.

November 1972

Mr. A. Jackson, c/o 2-7 Viewland Avenue, Royal Oak, Auckland 6, New Zealand.

September to December 1972, October 1973

Mr. C. C. Wood, Horseshoe Cottage, Thornton-in-Craven, Skipton, W. Yorks, BD23 3TJ.

December 1973

Mr. P. Daya, 19 Robson Street, Centrahil, Port Elizabeth, South Africa 6001.

September 1973

Mr. N. G. Bonello, "Magnolia", Thomas Dingli Street, Birkirkara, Malta.

April to August 1971

Mr. M. Duckmanton, 14 Carr Lane, Warsop, Mansfield, Notts., NG20 0BN.

November 1966

Mr. P. A. Hatton, 15 Greystoke Road, Caversham, Reading, Berks.

February 1973

Mr. H. P. Bailey, 45 Dalton Lane, Barrow-in-Furness, Lancs, LA14 4LE.

March, April 1969

Mr. R. C. K. Curzon, 24 Ivor Close, Holbury Hythe, Hants.

January to March 1974

Mr. R. Cooper, 21 Rookhill Drive, Pontefract, Yorks, WF8 2BY.

September to December 1973

Mr. A. C. Whitehead, 82 Cavendish Road, Eccles, Manchester.

December 1970 and February 1971

Mr. S. Cox, 21 Gwysfa Road, Ynystawe, Morriston, Swansea, S. Wales.

March 1969 and March 1970

Mr. C. C. Paise, Anson House, Royal Hospital School, Ipswich, Suffolk, IP9 2RX.

July 1968

Mr. P. A. Rawlins, 36 Alder Road, Coventry, Warcs, CV6 7DP.

May 1972

Mr. M. Shuaib, c/o Abdul Sattar Sons & Co. Ltd., O.P. Box 398, 47-48 Noor Chambers, Robson Road, Karachi-1, Pakistan.

August 1970

Mr. C. Ludricus, 10 Easter Drylaw Place, Edinburgh 4, EH4 2QD, Scotland.

February 1974

Mr. D. D. Wooster, The Flat, 4a Lodge Lane, Hassocks, Sussex, BN6 8NA.

January 1971

Mr. R. Chadwick, 8 St. Mary's Avenue, Altofts, Normanton, Yorkshire, WF6 2PU.

April 1970

Mr. C. R. Power, Moyes House, Boy's High School, New Plymouth, New Zealand.

July 1970

Mr. L. T. Roberts, 39 Willoughby Road, Liverpool, L14 6XA.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

February 1973

Carlos Raul Ron, Rua Baltazar Lisboa, 170-1 a Apto. 13, Vila Mariana, 04110—Sao Paulo—SP, Brasil.

June 1973

Mr. M. B. Wignall, 65 Mayles Road, Milton, Portsmouth, Hampshire, PO4 8NR.

October 1972

Mr. G. L. Price, 11 Pentland Avenue, Shoeburyness, Essex, SS3 9NE.

January and February 1973

Mr. K. M. Butcher, 5 Station Cottages, Retford, Nottinghamshire.

February and March 1973

Mr. A. J. Savery, 113 High Street, Ponders End, Enfield, Middlesex.

February 1968

Mr. A. McLean, Couston House, Aberdour, Fife, Scotland, KY3 0RX.

November 1973

Mr. J. Smith, 61 Pendrea Park, North Roskear, Camborne, Cornwall, TR14 8PF.

April and June 1971

Mr. N. C. Granger, 126 Eldred Avenue, Withden, Brighton, Sussex, BN1 5EH.

February 1969

Mr. G. Paine, 21 Estridge Way, Tunbridge, Kent, TN10 4JT.

January 1973

Mr. G. J. Lewis, 14 Ashleigh Road, Mayhull, Liverpool, L31 3EA.

November 1973, January, February and March 1974

Mr. P. Curtis, P.O. Box 1942, Riverside, Tasmania, Australia.

December 1971, January to March 1972


Mr. E. Nagela, San Nicolas 5187, Buenos Aires (S. 19), Republica Argentina.

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- SA35** £5.45 Carriage free
35W RMS 25-50V
7 transistors, 7 diodes
- SA50** £6.90 Carriage free
50W RMS 25-65V
7 transistors, 7 diodes
- SA100** £12.50 Carriage free
100W RMS 45-70V
10 transistors, 7 diodes
- 120 watt module complete with built-in supply—extra heavy duty £22.50 Carr. 60p**
- ★ 25Hz-25kHz
 - ★ 0.2% distortion
 - ★ Noise—80dB
 - ★ 500mV into 20K
 - ★ 4-16 ohms
 - ★ Simple wiring
 - ★ Short and open circuit proof
 - ★ Continuously rated
 - ★ Top-grade components

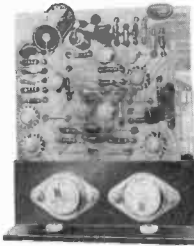

THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED	
PU45	Suits 2 SA35 or 1 SA50 (4 ohm) £5.45 Carriage 30p
PU70	Suits 2 SA50 or 2 SA100 (8 ohm) £8.45 Carriage 40p
STABILISED	
PS45	Suits 2 SA35 or 2 SA50 (4 ohm) £4.45 Carriage free
MT45	Transformer for above £3.50 Carriage 30p
PS70	Suits 2 SA100 £5.45 Carriage free
MT70	Transformer for above £4.90 Carriage 40p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £22.50 Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17 1/2 in x 3 in x 4 in deep.



DISCO MODULE £9.50 Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12 1/2 in x 3 in x 2 in deep.



3-CHANNEL SOUND-LITE £22.50 Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12 in x 3 in x 2 1/2 in deep. Professional standards at a price you can afford!




SINGLE CHANNEL VERSION £7.50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add 8% VAT to all orders

MULTI-PURPOSE MIXERS

M4HL £19.50 Carr. 50p
M6HL £29.50 Carr. 50p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfill the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

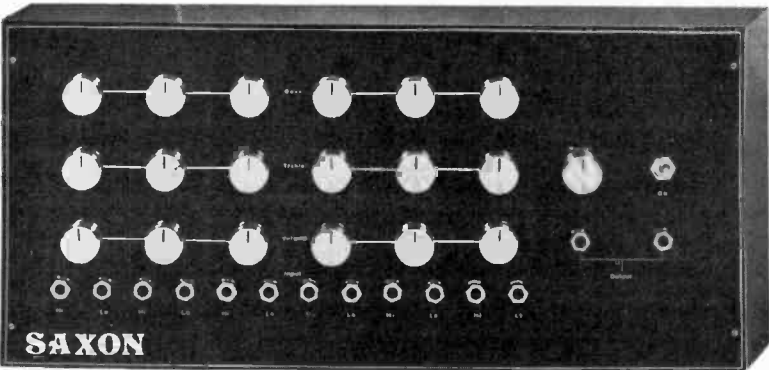

VA30 CHANNEL MODULE £3.50 Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)

SAXON CSE 100

COMPLETE AMPLIFIER

£39.90 Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive twin yvide case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29.50 Carr. free

NEW!!

SAXON MULTIMIX 100 £57 CARR. FREE

100W RMS SLIDER controls PLUS master slider. Wide range bass and treble controls—fantastic value. Ideal for complete Disco's, Groups, Clubs, etc.

SAXON MULTIMIX 50 EXACTLY AS ABOVE £45 BUT 50W RMS

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS


(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.-5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.-3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

SEND 10p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.
TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send 50p. for C.O.D.
Please include S.A.E. with all enquiries.
VAT at 8% must be added to all orders including carriage charges.

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO AND MONO

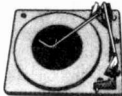

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V Size 13½ x 11½ in.

Above motor board 3½ in. below motor board 2½ in. with STEREO and MONO CARTRIDGE **£7.95** Post 45p

PORTABLE PLAYER CABINET

Modern design. Refine covered. Vynal front grille. Chrome fittings. Size 17 x 15 x 8 in approx. **£4.50** Post 45p

Motor board cut for BSR or Garrard deck.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13½ x 10 x 3½ in. Player unit clips to loudspeakers making it extremely compact, overall size only 13½ x 10 x 8½ in., 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls



240V a.c. mains. **£25** 35p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

0-60 MINUTES **£1.95** Post 25p. Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed.



TEAKWOOD LOUDSPEAKER GRILLES will easily fit to baffle board. Size 10½ x 10½ in—75p. 10½ x 7½ in—45p

WEYRAD P50 — TRANSISTOR COILS

RAZF Ferrite Aerial 85p
D.F. P50/2CC 470 kc/s 40p
3rd I.F. P50/3CC 40p
Spare Coils 3p
P50/1AC 60p
Mullard Ferrite Rod 8 x ½ in., 20p. 6 x ½ in., 20p. 3 x ½ in., 10p

Driver Trans. LF0T4...85p
Printed Circuit, PCA1 85p
J.B. Tuning Gang...£1.20
Weyrad Booklet...10p
OPT1...85p

VOLUME CONTROLS

5KΩ to 2MΩ. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. Edge 5KΩ. S.P. Transistor 25p

80 Ohm Coax 5p yd.

BRITISH AERIALITE
AERIAL-FLY SPACED
40 yd. £2.80 yd. £3
FRINGE LOSS LOSS
ideal 625 and colour **10p yd**

8 in. or 10 x 6 in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s, 8 ohm impedance, 10 watts. music power. **£3.75** Post 25p



E.M.I. 13½ x 8 in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 **£4.50** Post 25p

As Illustrated.

With flared tweeter cone and ceramic magnet. 10 watt. Bass resp. 45-60 c/s. Flux 10,000 gauss. Size 13½ x 8 in. **£3.25** Post 25p

State 3 or 8 or 15 ohm. Post 25p



Bookshelf Cabinet Teak finish 18 x 10 x 9 in.

13 in x 8 in. Bass Woofer, 20 watts, £5-50 **£6.60** Post 45p

SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK £1.50 Post 50p

BLANK ALUMINIUM CHASSIS. 18 a.w.g. 2½ in. slots 6 x 4 in 45p; 6 x 6 in 55p; 10 x 7 in 85p; 12 x 8 in 85p; 14 x 8 in 90p; 16 x 8 in 90p; 12 x 3 in 50p; 16 x 10 in £1.

ALUMINIUM BOXES. 3 x 3 in 60p; 4 x 4 in 70p; 6 x 4 x 4 in 80p; 9 x 4 x 4 in £1; 12 x 4 x 4 in £1.30.

ALUMINIUM PANELS 18 a.w.g. 6 x 4 in 12p; 6 x 6 in 19p; 14 x 3 in 20p; 10 x 7 in 24p; 12 x 5 in 25p; 12 x 8 in 34p; 16 x 6 in 34p; 14 x 8 in 40p; 12 x 12 in 47p; 16 x 10 in 60p. S.R.P.B. PAXOLIN PANEL 10 x 8 in 30p.

RADIO COMPONENT SPECIALISTS

Radio Books and Component Lists 10p. (Minimum posting charge 20p.)

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5 in HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.

Price **£2.95** Post 25p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Main Transformer. Input 200/240V a.c. Output voltages available 8 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. **£2.20** Post 25p

Details S.A.E. Size 3½ x 1½ x 1½ in.

RCS POWER PACK KIT

12 VOLT, 750mA. Complete with **£2.95** Post 25p

printed circuit board and assembly instructions.

12 VOLT 300mA KIT, £2.75. 9 VOLT 1 AMP KIT, £2.95.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or A.C. line 200-260V d.c. operation. Size: 1½ x 1½ x ½ in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. Details S.A.E. **£1.25** Post 20p

ELECTRO MAGNETIC PENDULUM MECHANISM

1-5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc. **95p** Post 20p

BRITISH FM/YHF TUNING HEART

88 to 108 M/Cs British made. 2 Transistors ready aligned requires 10-7 M/Cs I.F. Complete with tuning gang. Connections supplied but some technical experience essential.

Our price **£3.95** Post 20p

10-7 M/Cs I.F. strip £4.95 DECODER £4.95

MAINS TRANSFORMERS

ALL POST 25p each

250-0-250V 70mA, 6-3V 2A	£2.50
250-0-250 80 mA, 6-3V 3-5A 6-3V 1A or 5V 2A	£4.00
300-0-300V 120 mA, 6-3V 4A C.T. 6-3V 2A	£5.00
MINIATURE 200V 20mA, 6-3V 1A 2½ x 2½ x 2 in	95p
MIDGET 220V 45 mA, 6-3V 2A 2½ x 2½ x 2 in	£1.20
HEATER TRANS. 6-3V ½ amp 85p, 3 amp	£1.20
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 1 amp 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £2.00 2 amp 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £2.00 3 amp 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £2.50 5 amp 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £2.75 3, 5, 6, 8, 10, 13 or 5-0-5 amp. £1.50, 6-0-6 500mA 90p, 9V 1 amp 95p, 12V 300mA 75p, 12V 500 mA 85p, 12V 750 mA 85p, 12V 36V 48V, 2 amp, £2.30, 20V 3 amp, £2.20, 40V 3 amp, £2.50, 22-0-22V, 4 amp, £3.16V, ½ amp 95p, 16V, 2 amp, £1.85.	
AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W £4; 500W £7.50; 750W £15; 1000W £18.	
BATTERY CHARGERS. Ready built with leads and clips 1½ amp, £2.40; 4 amp, £3.40. 4 amp 40p, 5 amp 45p.	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1½ amp 40p; 2 amp 55p; 4 amp 85p.	

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3A 720W insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE **£12** Carr. Famous make. (Value £19). **95p**

Can be used as 800W auto transformers 240-110V.

IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V14p	250/25V14p	50 + 50/300V50p
4/350V14p	500/25V20p	800/350V95p
8/350V22p	1000/25V35p	32 + 32/250V20p
16/350V25p	1000/50V47p	32 + 32/450V60p
32/500V50p	6 + 6/450V22p	350 + 50/325V85p
25/25V10p	8 + 16/450V25p	100 + 50 + 50/350V 85p
50/50V10p	16 + 16/450V 40p	32 - 32 - 32/350V 65p
160/25V10p	32 - 32/350V 40p	4700/83V95p

LOW VOLTAGE ELECTROLYTICS.

1, 2, 4, 5, 6, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 15V 15p; 25V 20p; 50V 30p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 45p; 300mF 5V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

TRIMMERS 10pF, 30pF, 50pF, 100pF, 150pF, 15p. CERAMIC, 1pF to 0.01mF 4p. Silver Mica 2 to 5000pF 4p. PAPER 350V-0.1 7p; 0.5 15p; 1mF 50V 15p; 2mF 150V 15p. 500V-0.001 to 0.05 9p; 0.1 10p; 0.25 13p; 0.47 25p.

MICRO SWITCH LEVER ACTION 20p.

SUB-MIN MICRO SWITCH 25p. Single pole change over. TWIN GANG. "0-0" 208pF + 176pF £1.20; 500pF standard 75p.

385pF + 385pF with 25pF + 25pF. Slow motion drive 50p.

SHUNT WAVE SINGLE END. Imp. 50V 55p; 50V, 55p.

NEON PANEL INDICATORS 250V AC/DG. Amber 30p.

RESISTORS. ½ W, ¼ W, 20% 1p; 2W, 5p, 10p to 100W.

HIGH STABILITY. ½ W 2% 10 ohms to 8 meg. 10p.


Ditto 5%. Preferred values 10 ohms to 10 meg. 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each.

TAPE OSCILLATOR COIL Valve type 35p.

NEW MODEL "BAKER LOUDSPEAKER", 12IN 50 WATT.
GROUP 50/12, 8 OR 15 OHM HIGH POWER. **£12.95**
FULL RANGE PROFESSIONAL QUALITY.

BAKER MAJOR 12" £8.50

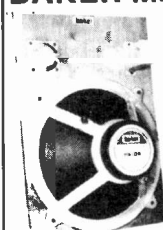

36-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000. 80 c/s. 12 in. 30mm bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with filter, crossover, baffle and instructions. **£10.95**

Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS

'Group 25' 12in. **£7.75** Post 25p
3 or 8 or 15 ohm

'Group 35' 12in. **£8.50** Post 25p
3 or 8 or 15 ohm

'Group 50/12' 12in. **£12.95** Post 25p
3 or 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER AND CABINETS
For 12in or 10in. dia. speaker 20 x 13 x 10in. £10.50 Post 75p
For 13 x 8 in or 8 in speaker 18 x 10 x 9 in, £8.60 Post 45p
For 8 x 5 in speaker 18 x 8 x 9 in, £5.60 Post 25p
For 8 in and Tweeter 18 x 8 x 9 in, £4.60 Post 25p

LOUDSPEAKER CABINET WADDING 18in wide, 20p ft

GOODMANS 6 1/2 in. HI-FI WOOFER

4 ohm or 8 ohm. 10W. Large ceramic magnet. Special Cambic cone surround. Twin cone. Frequency response, 30-12,000 c/s. **£4**

ideal P.A. Columns.
Hi-Fi Enclosure Systems, etc.
Suitable Cabinet 12x8x6 £4, Suitable Tweeter £2



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 2 1/2 in deep. Rating 10W, 3 ohm. Crossover £1.25 **£1.90**, Post 20p

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £2.25
De Luxe Horn Tweeters 2-18kc/s, 15W 15 ohm £4.
CROSSOVERS, TWO-WAY 3,000 c/s 3 or 8 or 15 ohm £1.25.
LOUDSPEAKERS P.N. 3 OHMS. 7x4 in., £1.25; 6 1/2 in. £1.50; 6x5 in. £1.60; 10 in., £2.00; 8 in., £1.75; 10x6 in., £1.50.
SPECIAL OFFER: 80 ohm, 2 in., 2 in., 3 in., 5 ohm, 5 in., 3 in., 25 ohm, 2 1/2 in. dia., 3 in. dia., 5 in. dia. **£1 each**

15 ohm, 3 1/2 in. dia., 7x4 in., 8x5 in., 12 in., 8 ohm, 10 ohm, 15 ohm, 15 ohm, £1.50.
3 ohm, 2 1/2 in., 3 in., 3 in., 3 in., 15 ohm, 15 ohm, £1.50.
RICHARD ALAN TWIN CONE LOUDSPEAKERS, 8 in. diameter 4W £2.95, 10 in. diameter 5W £2.95; 12 in. diameter 6W £3.50; 3/8/15 ohms, please state.
VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50t; 40p.
Mike trans. mu metal 100t £1.25.

Loudspeaker Volume Control 15 ohms 60W with one inch long threaded bush for wood panel mounting. 1 in spindle. 65p each, Post 15p.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER



All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music, 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. **£49** Carr. **£1.00**

NEW MODEL MAJOR—50 watt, 4 input, 2 vol. controls, treble and bass £39.95. Ideal disco amplifier.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 8V. TWO CHANNEL STEREO VERSION **£5.95**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor

Push-Pull Ready Built, with volume, Treble and bass controls. 18 volt d.c. **£3.95**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p.

OUTLET BOXES, SURFACE 25p. FLUSH 60p. TWIN 85p.
BALANCED TWIN RIBBON FEEDER 300 ohms. 7p yd.
JACK SOCKET STD. open-circuit 14p, closed circuit 23p; Chrom. Lead Socket 45p. Phone Plug 5p. Phone Socket 5p.
JACK PLUGS STD. Chrom. 20p; 3-5mm Chrom. 12p. DIN SOCKETS Chassis 3-pin 10p, 5-pin 10p. DIN SOCKETS lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMICS 10p; CANS 5p.

REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt. **£2.20**

1,200 r.p.m. 4 pole 105mA. Spindle 0-187x 0-75in. Size 3 1/2 x 2 1/2 in. (Illustrated). Post 25p.

EMI TAPE MOTOR

EMI TAPE MOTORS, 120V or 240V a.c. 1,200 r.p.m. 4 pole 105mA. Spindle 0-187x 0-75in. Size 3 1/2 x 2 1/2 in. (Illustrated). Post 25p. **£1.85**



337 WHITEHORSE ROAD, CROYDON
Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)
Buses 50, 68, 159. Rail Selhurst. Tel. 01-884 1665

ENGINEERS FREE YOURSELF FOR A BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

POST NOW

- Practical Radio and Electronics (Technatron)
- Electronic Engineering
- Television Maintenance and Servicing
- General Radio and TV Engineering
- Radio Servicing, Maintenance and Repairs

- C. & G. Radio, TV Electronics, Mechanics
- Radio Amateurs
- Practical TV
- Colour Television
- Computer Electronics
- C. & G. LI Radio TV Servicing cert.
- Post Master General 1st & 2nd class certs.
- C. & G. Electrical Engineering Practise

- C. & G. LI Installations and Wiring
- General Electrical Engineering
- Society of Engineers (Electrical Engineering)
- Electrical Installations and Wiring
- C. & G. Electrical Technicians (Primary)
- C. & G. Telecommunications

To ALDERMASTON COLLEGE

Dept EPEO2 Reading RG7 4PF

NAME (Block Capitals Please)

ADDRESS

Other subjects suggested by C.A.C.C.

Age Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

CALCULATOR OFFER!

SINCLAIR Cambridge	£17.25	TEXAS TI1500	£26.25
Cam. Memory	£24.00	TI2000	£13.95
Executive	£23.90	TI2550	£26.00
Exec. Memory	£28.45	TI3500	£35.00
Scientific	£25.00	SR10	£31.85

BUY IT WITH ACCESS, etc.

BC107 10p	BC184L 10p	TIP2655 85p	IN914 5p	7474 42p
BC108 10p	BC212L 12p	TIP3055 90p	IN916 5p	7475 80p
BC109 10p	BC213L 12p	TI843 18p	IN4148 8p	7476 48p
BC177 22p	BC214L 12p	TI874 80p	7400-5 20p	7483 £1.28
BC178 22p	BC182K 10p	ZTX304 25p	7410 20p	7486 48p
BC179 24p	BC183K 10p	ZTX304 35p	7413 30p	7490 65p
BC182 18p	BC184K 10p	OA10 30p	7420 20p	7492 70p
BC183 10p	BC212K 12p	OA47 7p	7430 20p	7483 65p
BC184 10p	BC213K 12p	OA73 6p	7440 20p	74107 45p
BC212 12p	BC214K 12p	OA81 5p	7442 80p	74121 51p
BC213 12p	TIP29A 85p	OA80 5p	7447 £1.30	74141 £1.00
BC214 12p	TIP30A 85p	OA81 5p	7470 34p	74151 £1.00
BC183L 10p	TIP41A 85p	OA200 6p	7472 34p	CA3028 90p
	TIP42A 85p	OA202 9p	7473 45p	CA3048 85p

702 14 pin DIL 45p	741 8 pin DIL 35p	2N3242 £1.45	BFY52 22p
708 8 pin DIL 35p	741 TO-9 35p	2N3216 20p	OC24 30p
709 TO-9 35p	748 8 pin DIL 35p	2N3820 45p	OC28 75p
708 14 pin DIL 35p	747 14 pin DIL 80p	2N4442 80p	OC29 75p
710 14 pin DIL 35p	8L301S 75p	BCY70 14p	OC30 80p
710 TO-9 35p	2N1302 12p	BCY71 14p	OC35 80p
733 14 pin DIL £1.35	2N1304 13p	BCY72 13p	OC44 20p
	2N3053 18p	BFY50 25p	OC45 20p
	2N3055 48p	BFY51 21p	OC78 20p

DIACAST BOXES: 4jinx2jinx1in. 80p; 4jinx2jinx2in. 90p; 7jinx4jinx2in. £1.80.
RESISTORS: TRS 2% £24, 24p; W.W. 2j W 10p, 8W 10p, 9W 12p, 12W 18p.
DALO PIN: 77p
DIBC CERAMICS, all values 10p. TANTALUMS 15p. I.C. SOCKETS 8 pin 15p; 14 pin 18p; 16 pin 18p. BOLDER, 18 S.W.G. £1.80 per 1/2 kg; 22 S.W.G. £1.90 per 1/2 kg.

No Lists. Prices too unstable. Phone for quotes.

VAT INCLUSIVE! POST FREE OVER £3!

P.E.C. 49-51 ST. MARY'S ROAD, OATLANDS VILLAGE
WEYBRIDGE, SURREY. TEL. WALTON 21324
Mail Order Only. C.W.O. P. & P. 15p



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR
100%
GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

WHAT READERS SAY

I am well pleased with the series. Everything is well set out in self-explanatory diagrams.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

D.D. West Ham

The manuals really open the door. D.C., Newbury

You can be assured that I will recommend your manuals to my friend. P.L., Lowestoft

These manuals are wonderful value for the prices asked. W.G., Bramhall

I find the manuals most enlightening and I am very grateful. A.C., Stratford

By far the easiest and simplest manuals I have ever studied. L.S., High Wycombe

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £6.50

BASIC ELECTRONICS 6 parts £7.50

BASIC TELEVISION 3 parts £4.25

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME

BLOCK LETTERS

FULL POSTAL

ADDRESS

POST NOW FOR THIS OFFER!

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT

The ever-popular P.E. AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A *must* for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors)	£11-49
8 channel component set (excl. thyristors)	£20-32
Power supply component set	£4-76
PCB for 4 frequency channels	£2-50
PCB for power supply and 8 lamp drivers	£1-25

P.E. CCTV CAMERA

Details in List

VOICE OPERATED FADER

For automatically reducing music volume during "talk-over"—particularly useful for Disco work, or for home-movie shows.

Component set, incl. PCB	£2-95
--------------------------	-------

P.E. GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system, specifications for which are shown in detail in our list, together with semiconductor requirements. While stocks last.

Main Amplifier:	
Set of resistors, capacitors and presets	£5-96
Stereo printed circuit board	£1-28
Pre-Amplifier:	
Sets of resistors, capacitors, potentiometers and switches—	
Standard Tolerance Set	£10-57
Superior Tolerance Set	£18-04
Stereo PCB (as Published)	£2-20
Regulated Power Supply:	
Set of resistors, capacitors and preset	£4-58
Printed circuit board	72p

HI-FI TAPE LINK

Designed for use with reasonable quality tape decks, this high performance pre-amp includes record, playback and metering circuits.

Stereo component set (excl. panel meter)	£22-05
Mono component set (excl. panel meter)	£13-31
Power supply component set	£3-72
Stereo main PCB	£2-50
Stereo sub-assembly PCB	86p

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB)	£2-30
Regulated power supply (including printed circuit board)	£3-71

PROJECT Q4

Multi-system Quadrasonic Decoder

Decoder component set	£13-74
Power supply components	£3-22
Printed circuit board	£2-60

SEMICONDUCTOR TESTER

Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and sub-assembly PCB (fuller details in list)	£6-06
--	-------

PHASING UNIT

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB)	£2-20
---------------------------	-------

P.E. SOUND SYNTHESISER


The well-acclaimed and highly versatile Synthesiser published in P.E. Feb 1973 to Feb. 1974

Component sets and printed circuit boards: Full details in list.

RHYTHM GENERATOR

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures.

Tempo, Timing and Logic Circuit	
Component set (excl. switches)	£17-25
Double-sided PCB for above	£2-30
Mixer, Pre-amp and Effects Circuits	
Component set	£12-70
PCB (illustrated)	£2-67
Monitor Amplifier	
Component set and PCB	£3-10
Power Supply	
Component set and PCB	£5-65

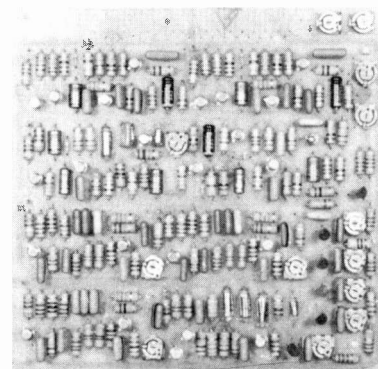

All PCB's are printed on professional quality fibre-glass, are drilled and roller-tinned

ULTRASONIC TRANSMITTER-RECEIVER

A highly sensitive and long range "invisible beam" detection circuit with numerous applications.

Component set with PCBs, but excluding transducers	£4-40
--	-------

P.E. RONDO

PCB details in List.

POWER SLAVES

PCB details in List.

P.E. ELECTRONIC PIANO

Details in List.

HOME INTERCOM

Details in List.

SOUND BENDER

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency doubler

Component set	£5-83
Printed circuit board	£1-44

REVERBERATION UNIT

A high-quality unit having microphone and line input pre-amps, and providing full control over reverberation level

Component set (excl. spring unit)	£8-44
Printed circuit board	£1-40

P.E. MINISONIC

Details in List

8W AMPLIFIER

A moderately powered amplifier of more than average performance. While stocks last

Main Amplifier	
Mono component set	£4-18
Stereo component set	£8-36
Mono printed circuit board	72p
Pre-Amplifier	
Mono component set	£2-50
Stereo component set	£6-46
Stereo PCB	£1-66
Power Supply	
Component set	£3-89

BIOLOGICAL AMPLIFIER

Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

Pre-Amplifier Module	
Component set and PCB	£3-48
Basic Output Circuits	
Combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feedback lamp driver circuits	£4-96
Audio Amplifier Module	
Type PC7	£5-50

PHOTOPRINT PROCESS CONTROL

For colour and B & W, an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

Component set (excl. meter)	£8-85
Printed circuit board	£1-80

ENLARGER EXPOSURE METER AND THERMOMETER

Dual-purpose dark-room unit with good accuracy

Component set with PCB, but excluding meter	£4-00
---	-------

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds

Component set incl. PCB	£2-40
-------------------------	-------

PCB LAYOUT AND CIRCUIT DIAGRAMS SUPPLIED WITH ALL PCBs DESIGNED BY PHONOSONICS	P. & P. Add 18p to all orders	VAT Add 8% (or current rate if different) to total order cost including P. & P.	LIST Send S.A.E. for free list giving fuller details of kits, PCBs, and other components.	OVERSEAS P. & P. will be charged at cost. VAT does not currently apply. List gives fuller details including kit weights. Charge for list: Europe 10p, other countries 20p.	COLOUR CODE IDENTIFICATION SUPPLIED WITH MOST KITS AND AS PART OF LIST
--	-------------------------------	---	---	--	--

Semiconductors		Integrated Circuits		Zeners		Electrolytic Capacitors (µF/V)		Polyester (µF)		Tantalum (µF/V)							
AC128	20p	MJE3055	75p	2N3823E	38p	709 TO5 or DIL	40p	0-47/63V	8p	47/40	7p	47/40	20p	0-015	3p	0-1/35	12p
AC176	20p	NKT0033	112p	2N4871	38p	723 TO5	95p	1-0/83V	8p	50/6-4	8p	500/64	46p	0-022	3p	0-22/35	12p
BC107	13p	OC28	85p	2N5777	45p	747 8-pin DIL	40p	1-5/63V	6p	100/10	6p	680-6-3	10p	0-033	3p	1-0/35	12p
BC108	13p	OC71	14p			748 TO5	63p	2-2/83V	6p	100/25	6p	680-25	20p	0-047	3p	2-2/35	12p
BC109	13p	OC84	25p			748 8-pin DIL	63p	6-7/63	6p	100/40	7p	680-40	25p	0-068	3p	2-2/35	12p
BC147	12p	2N107	12p	1N914	4p	748 14-pin DIL	63p	6-8/40	6p	100/63	13p	1000-10	14p	0-1	4p	4-7/35	12p
BC148	12p	ZTX102	12p	1N4001	6p	740	20p	6-8/40	6p	100/63	13p	1000-10	14p	0-15	5p	10/16	12p
BC149	12p	ZTX503	15p	1N4002	7p	7402	20p	10/25	6p	150/63	13p	1000/25	30p	0-22	5p	10/25	16p
BC157	13p	ZTX531	23p	1N4004	8p	7402	20p	15/40	6p	220/10	6p	1000/25	45p	0-33	7p	15-6-3	16p
BC158	13p	2N706	13p	1N4005	8p	7402	20p	22/10	6p	220/16	7p	2200/25	45p	0-47	9p	22/16	16p
BC159	13p	2N914	22p	1N4006	8p	7447	175p	22/25	6p	220/25	11p	2200/40	63p	1-0	14p	47/16V	25p
BC182L	12p	2N1304	22p	BA145	23p	7473	44p	6-8/40	6p	220/40	14p	2800/100	360p	0-68	11p	47/6-3	16p
BC204	14p	2N2219	27p	OA81	7p	7489	575p	10/25	6p	220/63	21p	3300/63	350p	0-8	11p	47/6-3	16p
BC209C	14p	2N2905	27p	OA200	7p	CA3046	89p	15/40	6p	4700-16	6p	4700-16	25p	1-0	14p	47/16V	25p
BC212L	15p	2N2907	12p	1G7	61p	µA7815 TO220	250p	20/10	6p	330/10	6p	3300/100	350p	2-2	24p	100/3-1	16p
BC478	20p	2N3054	66p	1SJ50	7p	MFC6040	95p	33-6-3	6p	220/40	14p	2800/100	360p	0-8	11p	47/6-3	16p
BCY71	22p	2N3055	50p	ZIL	61p	PA263	169p	33-50	6p	470-6-3	6p	4700-16	60p	0-8	11p	47/6-3	16p
BFY50	22p	2N3702	12p			SG3402N	169p	47/25	6p	470/10	10p	4700/25	75p	0-8	11p	47/6-3	16p
BFY52	24p	2N3703	12p					47/40	6p	470/25	16p	4700/40	93p				
BSY95A	22p	2N3704	12p														
ME2955	110p	2N3819	35p			Minitron 3015F	225p										

PHONOSONICS, DEPT. PE32, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY (P.S. DON'T FORGET VAT!)

CHROMASONIC electronics

Dept 2,
56, Fortis Green Road, London, N10 3HN.
telephone: 01 883 3705

OPTOELECTRONICS

Monsanto

Unitron

litronix



Common Anode



Common Cathode

Overflow

(±1)



DL 707
0.3" high character
14 pin DIL



DL 747
0.6" high character
L.H. Dec P.

Red

MAN 72 MAN 74 MAN 73

Green

MAN 52 MAN 54 MAN 53

Yellow

MAN 82 MAN 84 MAN 83

L/H Dec. Pt. R/H Dec. Pt.

OUR PRICE £1.82

£1.82

£2.42

LIGHT EMITTING DIODES

All supplied with retaining clip



Lens sizes

	0.125"	0.16"	0.2"
RED	18p	27p	19p
GREEN	27p	35p	30p
ORANGE	27p	35p	30p
YELLOW	34p	40p	35p

RED MLED500 TO92 size
17p each £1.39 for 10

LINEAR I.C.'s

709 (8 pin dip)	33p	LM377	£2.91	SL414	£1.723
709 (TO-99)	39p	LM380	£1.08	SL415	£2.243
709 (14 pin dip)	34p	LM381	£2.263	SL440	£2.84
710 (8 pin dip)	34p	LM382	£2.193	SN75491	£1.43
710 (TO-99)	39p	LM3900	73p	SN75492	£1.63
710 (14 pin dip)	38p			TAA263	80p
711 (TO-99)	44p	MC1303L	£1.853	TAA300	£1.76
711 (14 pin dip)	38p	MC1306P	54p	TAA310	£1.343
723 (TO-99)	74p	MC1310P	£3.05	TAA320	97p
723 (14 pin dip)	54p			TAA350	£2.51
741 (8 pin dip)	31p	MC 1312	£2.42	TAA370	£5.05
741 (TO-99)	44p	MC 1314	£4.05	TAA550	80p
741 (14 pin dip)	42p	MC 1315	£5.37	TAA570	£1.62
747 (14 pin dip)	90p			TAA700	£3.56
748 (8 pin dip)	41p	MC1330P	86p	TAD100	£1.53
748 (TO-99)	44p	MC1339P	£1.263	TBA231	88p
748 (14 pin dip)	42p	MC1350	81p	TBA500	£2.85
		MC1351	£1.08	TBA520	£2.66
AY-1-0212	£5.99	MC1352	£1.08	TBA530	£1.94
AY-5-1224	£4.59	MC1357	£1.56	TBA540	£1.96
AY-5-3507	£7.45	MC1358	£1.65	TBA560C	£2.92
AY-5-3510	£6.92	MC1375	£1.38	TBA625A	£1.03
		MC1456CG	£1.713	TBA625B	£1.03
		MC1458CP1	£2.37	TBA625C	£1.02
BHA0002	£3.87	MC1468G	£2.47	TBA800	95p
		MC1495	£5.54	TBA810S	£1.07
CA3046	95p	MC1496G	£1.46	TBA810AS	£1.07
CA3065	£1.53	MC3302	£1.30	TBA820	74p
CA3075	£1.62	MC3401	75p	TCA940	£1.94
CA3081	£1.61	MFC4000B	40p	TDA1200	£2.10
CA3082	£1.62	MFC4004A	76p	TDA1405	97p
LO05T1	£1.45	MFC6030A	81p	TDA1412	97p
LO36T1	£1.45	MFC6040	£1.08	TDA1415	97p
LO37T1	£1.45			ULN 2111A	1.56
L129	£1.39	MA5314	7.76	ZN402E	1.94
L130	£1.39	MA5316	£16.17	ZN414	1.293
L131	£1.39				

Back in stock again!

HC244R

The Stabilized Power supply
for which demand always exceeds supply
switched 3, 6, 7½ & 9 volts up to 400 mA

Polarity reversal switch; Neon Mains Indicator, on/off switch; 4ft Lead
Multi-Volt output plug adaptor; Metal Case; Rubber Feet
£4.89 + p & p 16p

74 SERIES TTL

1st. GRADE BRANDED PRODUCTS

7400	17p	7442	90p	7490	68p
7401	17p	7445	1.20	7491	1.10
7402	17p	7447	1.15	7492	80p
7403	17p	7447A	1.76	7493	70p
7404	25p	7448	1.47	74100	2.32
7409	29p	7470	33p	74121	50p
7410	17p	7473	33p	74122	85p
7419	29p	7474	40p	74141	1.07
7413	29p	7475	62p	74154	1.76
7420	17p	7476	42p	74192	2.11
7430	17p	7486	35p	74193	2.45
7441	90p	7489	4.65	74196	1.70

F.M. STEREO TUNERS

Transistor F.M. Tuner
Chassis, 9 volt
Operation.
A10055
£8.04



Stereo Decoder
to match A10055 MS £6.08



New Mini F.M. Tuner
* 12 volt supply
£6.76
Matching Stereo Decoder
£4.86

SIEMENS LCD's




LIQUID CRYSTAL DISPLAY complete with
socket and removable reflective backing;
Ref AN4132R 13mm character height. Can
be directly driven by National Semiconductor
Alarm Clock chip MM5316.

OUR PRICE £13.99

24 HOUR DESPATCH NOW IN OPERATION

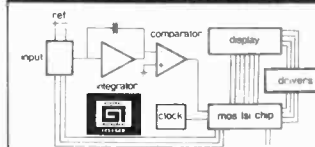3 1/2 DECADE DIGITAL VOLTMETER INTEGRATED CIRCUIT



This state-of-the-art MOS LSI chip contains
all the logic necessary for a 3½ decade, dual
slope integrating, automatic polarity detecting
DVM. Supplied with free data and circuit
booklet. AY-5-3507

OUR PRICE ONLY £7.46

(booklets alone 20p)

PHOTO-DARLINGTON




2N5777

Vceo: Vcbo 25v; Vcbo 8v
Vceo: Vcbo 25v; VEBO 8v
Ifc 2500; Ic 250 mA

MINITRON

Filament Indicators, 15 Pin DIL 10mm
Character Height
0-9 Digit Ref 3015F
- 1 Overflow/Polarity Ref 3015G

NEW PRICE £1.24

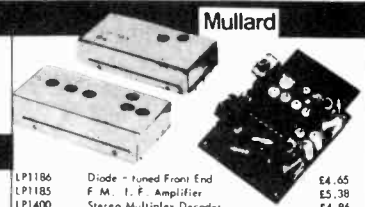

LP1186 Diode - Tuned Front End £4.65
LP1185 F.M. I. F. Amplifier £5.38
LP1400 Stereo Multiplex Decoder £4.86

This trio make one of the most fabulous F.M. tuners
of all time. Typical channel separation 50 db.

SPECIAL OFFERS

Left Hand Decimal Point

All Common Anode;
Character Height 0.3"

4 for £5.99
5 for £7.45
6 for £8.93

RED (Led 7)
GREEN (Led 18)
YELLOW (Led 21)



VAT INCLUDED AT 8%

OVERSEAS CUSTOMERS DEDUCT 2/27
VAT INVOICES ON REQUEST
P&P On U.K. Orders min. 15p.

CALLERS WELCOME

RESISTORS

The standard ranges of Resistors stocked are either E12 or E24 and the values are all in multiples of ten times the decade shown below. The E12 items are only those in bold type. The E24 items are both those in bold and light type.

10	18	33	56
11	20	36	62
12	22	39	68
13	24	43	75
15	27	47	82
16	30	51	91

CARBON FILM $\frac{1}{2}$ watt \pm 5% tol. 2p ea.
E12 Series 10 to 330K

CARBON FILM $\frac{1}{2}$ watt \pm 5% tol. 1p ea.
E24 Series 10 to 10M

CERMET THICK FILM $\frac{1}{2}$ watt \pm 2% tol. 8p ea.
E12 series 56 to 150K

METAL OXIDE FILM $\frac{1}{2}$ watt \pm 2% tol. 4p ea.
E12 series 10 to 1M

CARBON COMPOSITION $\frac{1}{2}$ watt 4p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; \pm 0.5 tol.
5.6 ; 6.8 ; 8.2 \pm 10% tol.

CARBON COMPOSITION 1 watt 5p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; \pm 0.5 tol.
5.6 ; 6.8 ; 8.2 \pm 10% tol.

CARBON FILM 1 watt \pm 5% tol. 3p ea.
E12 series 10 to 10M

CARBON FILM 2 watt \pm 5% tol. 6p ea.
E12 series 10 to 10M

WIREWOUND 2 $\frac{1}{2}$ watt \pm 5% tol. 0.2210 0.47 15p
E12 series \pm 10% tol. 11 to 270K 13p

WIRE WOUND 5 WATT 13p ea.

1	25	250	1.5K
1	30	270	1.8K
1.8	39	300	2K
2.2	50	330	2.2K
2.7	60	350	2.5K
3.3	68	400	2.7K
3.9	75	470	3K
4.7	82	500	3.3K
5	100	500	3.3K
5.8	125	600	3.9K
6.8	133	680	4.7K
8.2	150	750	5K
10	180	820	5.6K
15	200	1K	6.8K
21	220	1.2K	8.2K

WIRE WOUND 10 watt 14p ea.
All the values shown in bold in the 5 watt range

WIRE WOUND 10 watt \pm 5% tol. 20p ea.
10K ; 15K ; 20K ; 25K

WIRE WOUND 15 watt 13p ea.
All the values from 10 upward shown in bold in the 5 watt range.

POTENTIOMETERS



5K 250K Log or Lin Less Switch (and 1K Lin) 14p
10K 500K Log or Lin with Switch 29p
25K 1 Meg Dual Less Switch 46p
50K 2 Meg 1 Meg Log only 57p
100K 10K Log + 10K Anti Log Less Switch 46p

Sliders
10K Single 33p
25K
50K DUAL 55p
100K

Presets Vertical or Horizontal
.1 Watt 5p .25 Watt 7p
100 1K 10K 100K 1Meg
250 2.5 25K 250K 2.5 Meg
500 5K 50K 500K 5Meg

Cermets
100 2.5K 25K 250K
500 5K 50K 500K
1K 10K 100K 1Meg
40p

CAPACITORS

Ceramic Plate
Mullard C333 Series 63 Volts Wkg.
all at 5p each
1.8pF = 0.2pF 12pF = 2% 68pF = 2%
2.2pF 15pF 82pF
3.3pF 18pF 100pF
3.9pF 22pF 120pF
4.7pF 27pF 150pF
5.6pF 33pF 180pF
6.8pF 39pF 220pF
8.2pF 47pF 270pF
10 pF 56pF 330pF

Mullard 630 series 40 volts = 10% tol
629 series 100 volts
all at 5p each
390 pf 1000 pf 3300 pf
470 pf 1200 pf 3900 pf
560 pf 1500 pf 4700 pf
680 pf 1800 pf * 10 nf
820 pf 2200 pf * 22 nf
2700 pf

Erie Monolithic Ceramic 30 Volts Wkg.
27 nf 11p; 47 nf 13p; 100 nf 17p

Low Voltage Disc Ceramics
all at 5p each
0.01 uF 18v ; 0.1 uF 30v
0.022 uF 18v ; 0.22 uF 6v
0.047 uF 18v ; 0.47 uF 3v

Mylar Film 100 Volts Wkg.
1000 pf 2p ; 0.05 uF 3p
2000 pf 2p ; 0.068uF 3p
5000 pf 2p ; 0.1 uF 5p
0.01 uF 3p ; 0.2 uF 6p
0.02 uF 3p ; 0.47 uF 7p
0.04 uF 3p


Polystyrene
MULLARD C295 Series 63 volts
Tolerance = 1%
6.800pF (6.8nF) C295 AH/DEK8 11p
8.200pF (8.2nF) C295 AH/DBK2 11p
13.000pF (13nF) C295 AH/D18K 15p
18.000pF (18nF) C295 AH/D13K 15p
20nF (0.02uF) C295 AH/D20K 15p
30nF (0.03uF) C295 AH/D30K 18p
39nF (0.039uF) C295 AH/D39K 18p
51nF (0.051uF) C295 AH/D51K 25p

Polystyrene 160 volts Wkg
Tolerance = pF up to 33pF = 5% 47pF up
10 pf to 10,000 pf (0.01 uF) in multiples of:
10 ; 15 ; 22 ; 33 ; 47 ; 68.
all 5p each
Nimarks 0.22uF = 5% 1000 11p
Wima MKS 0.22uF 11p
= 5% 100V

Mullard C280 Series 250 Volts Wkg.
Metalised Polyester Film
0.01 uF 3p ; 0.22 uF 5p
0.015 uF 3p ; 0.33 uF 7p
0.022 uF 3p ; 0.47 uF 9p
0.033 uF 3p ; 0.68 uF 12p
0.047 uF 3p ; 1.0 uF 14p
0.068 uF 4 p ; 1.5 uF 22p
0.1 uF 4p ; 2.2 uF 26p
0.15 uF 4p

Mullard C281 series 400 volts Wkg.
Metalised Polycarbonate Film 10%
0.01 uF 5p ; 0.1 uF 8p
0.015 uF 5p ; 0.15 uF 9p
0.022 uF 5p ; 0.22 uF 11p
0.033 uF 6p ; 0.33 uF 15p
0.047 uF 6p ; 0.47 uF 16p
0.068 uF 6p


VDR's & Thermistors

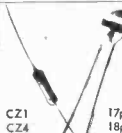

CZ1 17p
CZ4 18p
CZ13A 18p
CZ19 18p
E298CDAZ58 13p
E298EDA258 13p
E298EDA260 13p
E298EDA262 13p
E298EDA265 13p
E298EDP266 13p
E298ZD05 13p
E298ZD06 13p
E299DDP336 14p
E299DDP338 14p
E299DDP342 14p
E299DDP348 14p
GL16 E1.21
GL23 E1.21
R53 E1.49
R54 E1.61
VA1005 14p
VA1026 14p
VA1033 14p
VA1034 14p
VA1039 14p
VA1040 14p
VA1053 14p
VA1055S 14p
VA1056S 14p
VA1065S 17p

VA1067S 19p
VA1077 19p
VA1098 21p
VA1104 31p
VA1107 29p

CAPACITORS

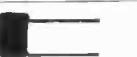

Silvered Mica 350V.
Tot. \pm 0.5pf 11p each
2.2 pf 18pf 30pf
3.3 pf 20pf 33pf
5 pf 22pf 39pf
10 pf 25pf 47pf

Tot. \pm 1% 11p each
50pf 150pf
56pf 82pf 180pf
68pf 100pf 200pf
75pf 120pf 220pf

250pf 330pf 560pf
270pf 390pf 680pf
300pf 470pf 820pf
500pf

1000 pf 1500pf 220pf
1800pf

2700pf 3600pf 5000pf
4700pf

6800pf 8200pf 10000pf

Mixed Dielectric 600 Volts Wkg.
0.01 uF 8p ; 0.1 uF 9 p
0.022 uF 8p ; 0.22 uF 17p
0.033 uF 8p ; 0.47 uF 26p
0.047 uF 8p ; 1 uF 36p
0.068 uF 9p

Mixed Dielectric 1000 Volts Wkg.
1000 pf 6p ; 0.022 uF 11p
2200 pf 6p ; 0.047 uF 13p
3300 pf 7p ; 0.1 uF 13p
4700 pf 7p ; 0.22 uF 24p
0.01 uF 10p ; 0.47 33p

Solid Tantalum Beads
all at 16p
0.1 uF 35v ; 10 uF 6.3v
0.22 uF 35v ; 10 uF 16v
0.47 uF 35v ; 10 uF 25v
1.0 uF 35v ; 22 uF 16v
2.2 uF 35v ; 47 uF 6.3v
4.7 uF 35v ; 100 uF 3v

Feed-through Ceramics
1000 pf 350v 6p

Disc Ceramics 750 Volt Wkg.
all at 5p each
470 pf; 1000 pf; 5000 pf; 0.01 uF

Tubular HI-K Ceramics 750 Volts Wkg.
1000 pf 5p 3000 pf 5p
1500 pf 5p 5000 pf 5p
2000 pf 5p 0.01 uF 5p

Pulse Ceramics all at 10p each
12 kv. D.C. Wkg. 8kv D.C.
10pf 120pf 200pf
22pf 140pf 220pf
68pf 150pf 250pf
82pf 100pf 270pf
100pf 200pf 300pf

VAT INCLUSIVE PRICES AT 8% OVERSEAS CUSTOMERS DEDUCT 2/27 VAT INVOICES ON REQUEST P&P On U.K. Orders 15p. Overseas Orders at Cost

TRANSISTORS

AC126 7	11p	BC177	18p	BFR41	26p
AC128	11p	BC178	17p	BFX29	30p
AC176	11p	BC179	18p	BFX30	30p
AC187	12p	BC182	10p	BFY50	15p
AC188	11p	BC183	10p	BFY51	15p
AD149	43p	BC184	11p	BFY52	15p
AD161	37p	BC212	11p	BRY39	34p
AD162	37p	BC213	10p	MJE2955	85p
AF114 5	13p	BC214	13p	MJE3055	65p
AF116 7	13p	BD115	55p	OC26	40p
AF139	41p	BD124	75p	OC28	55p
AF239	44p	BD131	42p	OC35	48p
BC107 8	9p	BD132	45p	OC36	52p
BC109	10p	BF115	22p	OC41 2	15p
BC147 8	7p	BF167	23p	OC44 5	11p
BC149	9p	BF173	25p	OC70 1/2	11p
BC157	13p	BF184	22p	OC73	80p
BC158	12p	BF194	11p	OC81 2	12p
BC159	14p	BFR39	28p	OC83 4	28p
BC169C	12p	BFR40	28p	TIP2955	70p

TIP41A	80p	2N2905	18p	FETS	
TIP42A	80p	2N2928RB	8p	BF244	38p
ZTX300	14p	2N2928	8p	MFF102	31p
ZTX304	24p	2N2928YG	9p	MFF103	31p
ZTX500	15p	2N3053	18p	MFF104	31p
ZTX504	30p	2N3855	40p	MFF105	31p
2N6896	15p	2N3442	140p	2N3819	20p
2N6897	13p	2N3702/3	11p	2N3820	20p
2N6898	30p	2N3704/5	11p	2N3823	60p
2N708	12p	2N3708/7	11p	2N5457	31p
2N708	18p	2N3708/9	9p	2N5458	31p
2N8930	18p	2N3772	181p	2N5459	31p
2N1131/2	18p	2N3773	240p		
2N1302/3	17p	2N3903/4	15p		
2N1304/5	21p	2N4058	15p		
2N1306/7	26p	2N4080	13p		
2N1308/9	26p	2N5191	95p		
2N1613	20p	2N5194	85p		

MOSFETS	
40803	58p
40673	80p
40841	75p
3N128	90p
3N140	85p
3N141	75p

SPECIAL OFFERS

555	50p	CA3046	55p
741	25p	ML723	50p
MC1310	245p	SN7447	95p
MC1312	220p	SN7490	52p

OPTO-ELECTRONICS

Photo- Light
Transistors Dependent
OCP70 50p Resistors
OCF71 65p
2N5777 60p ORP60 50p
LEDS TIL209 18p ORP61 55p
Red 18p Green 35p Yellow 35p
MINITRON 3015F 120p

LATEST ICs—
MANY APPLICATIONS
ICL8038 Voltage Controlled Oscillator 280p
NE567 Tone Decoder 250p
(Application Data 10p)

RECTIFIER DIODES

500mA	
BY100	15p
BY126	12p
BY127	12p
1N4001	5p
1N4004	6p
1N4007	7p
1.5 Amp	
PL4004	10p
3 Amp	
PL7004	20p
6 Amp	
BY210	50p
BY211	50p
BY212	50p
BY213	50p

SIGNAL DIODES

BA100	10p
OA47	7p
OA70	8p
OA79	7p
OA81	7p
OA85	9p
OA90	6p
OA91	6p
OA200	6p
OA202	7p
1N914	50p
1N916	4p
1N4148	4p

ZENER DIODES

3-3V to 33V	
400MW	9p
1-3W	18p
1-5W	25p
10W	55p

Other Diodes

TUNNEL	
AEY11	50p

VARICAP

BB103	15p
BB104	30p
BB105	30p

BRIDGE RECTIFIERS

250mA	18p	50V	100V	400V	600V
1 Amp	20p	21p	24p	25p	
2 Amp	30p	35p	45p	48p	
4 Amp	47p	48p	80p	70p	
6 Amp	55p	80p	78p	98p	

SCR—THYRISTORS

1 Amp	50V	100V	400V	600V
42p	48p	60p	78p	
3 Amp	43p	49p	78p	100p
7 Amp	—	80p	84p	115p
16 Amp	—	82p	98p	—

Other
C1060 45p, 2N3252 91p, 2N4444 185p

TRIACS

3 Amp	100V	400V	500V
85p	99p	120p	150p
6 Amp	88p	120p	150p
10 Amp	180p	154p	185p
18 Amp	145p	180p	200p

Other
40430 90p, 40486 85p, 40669 95p,
DIAC S12 for use with above triacs 21p.

VOLTAGE REGULATORS

ML723	95p	MFC4080	70p
1 Amp		Plastic	(TO220)
			(TO3)
		7805	5V 140p
		7812	12V 140p
		7815	15V 140p
		7818	18V 140p
		7824	24V 140p

LINEAR ICs

CA3046	Transistor Array	55p
CA3048	4 Independent Amps	230p
CA3089	FM, W/F Amp	250p
CA3090	FM Stereo Decoder	400p
LM301	OPA with ext comp	40p
LM307	OPA with int comp	50p
MC1303	Stereo Dec Amp	150p
MC1307	FM Stereo Decoder	120p
MC1310	Colless FM Stereo Dec	245p
MC1312	SQ Quadrasonic Disc	220p
MFC4000	1 Watt Audio Amp	40p
MFC6040	Electronic Attenuator	90p
MFC8070	Zero Voltage Switch	250p
TAA570	Limiter Amp	170p
TBA570	Am/FM Radio receiver	180p
TBA800	5 Watt Audio Amp	100p
TBA810	7 Watt Audio Amp	125p
TBA820	2 Watt Audio Amps	80p
TCA940	10 Watt Audio Amplifier	320p

ZN414	Radio receiver	110p
NE536	FET OPA	282p
NE555	Timer	90p
NE566	Quasi 555	120p
NE560	PLL	285p
NE561	PLL with AM Demod	285p
NE562	PLL with VCO	285p
NE565	Precision PLL	285p
NE568	Function Gen	200p
NE567	Tone Decoder	250p

Popular Op Amps

ML709	OPA with ext comp	28p
ML710	Diff comparator	35p
ML741	OPA with int comp (8 pin DIL)	25p
ML747	Dual 741	70p
ML748	OPA with ext comp	38p

TTL ICs

7400	14p	7441	75p	7478	37p
7401	18p	7442	70p	7480	65p
7402	16p	7448	120p	7488	43p
7404	18p	7450	22p	7490	52p
7408	20p	7454	22p	7492	68p
7410	18p	7460	22p	7493	55p
7413	20p	7470	30p	74107	45p
7414	72p	7472	30p	74121	34p
7416	33p	7473	38p	74122	76p
7420	18p	7474	34p	74123	110p
7430	18p	7475	52p	74141	85p

C-MOS ICs

CD4001AE	51p	CD4018AE	300p
CD4008AE	120p	CD4027AE	170p
CD4011AE	50p	CD4029AE	420p
CD4012AE	51p	CD4037AE	210p
CD4018AE	120p	CD4047AE	185p

We supply complete semiconductor parts including sockets for various projects in P.E., W.W., P.W., TELEVISION, etc.

TELETELEVISION

TRICOLOUR LIGHT UNIT
RHYTHM GENERATOR
MINISONIC SYNTHESIZER
TGS GAS DETECTOR

Minimum order £2.
All prices exclusive of VAT.
P. & P. 10p for orders under £5.

All goods brand new and guaranteed to manufacturers specification.
Money refunded if not satisfied.

Mail Order Only
01-204 4333


TECHNOMATIC LTD.
54 Sandhurst Road, London NW9

SCOOP!! CALCULATOR I.C.

XE 202 FULL 4 FUNCTION + CONSTANT CALCULATOR CHIP £2.95 + VAT

For only £2.95 you get a brand new, tested full four function calculator chip, with the following features:

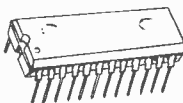
- 8 DIGIT DISPLAY CAPABILITY
- FULLY FLOATING DECIMAL POINT
- ALGEBRAIC LOGIC DATA ENTRY
- KEYED CONSTANT ON ALL FOUR FUNCTIONS
- TRAILING ZERO SUPPRESSION
- DIRECT SEGMENT DRIVE
- ENORMOUS EXPONENT RANGE: 10⁻²⁰ to 10⁺⁷⁹
- SINGLE 'STROBE' LINE FOR SIMPLE KEYBOARD CONSTRUCTION





By the addition of a display and a few discrete components you can construct a powerful machine capable of handling advanced calculations. The XE202 is supplied with full circuit diagrams and wiring details covering the use of different types of displays and keyboards (including a low cost single digit display and rapidly constructed stylus keyboard), and with instructions for realising the full computing powers of this chip to calculate advanced functions such as roots, sines, logs, etc.

ALSO AVAILABLE AT SPECIAL PRICES FOR PURCHASERS OF THE XE202 CHIP:

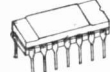Specially designed display driving interface chip at £0.75



8 digit magnified LED display at £3.95

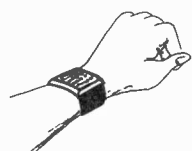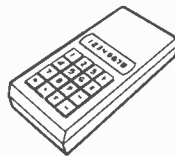

Full money back guarantee.
Cash with order. Postage and packing 20p per order.
Please add 8% VAT to total order value.

PLEASE SUPPLY _____

TO _____

THURLBY ELECTRONICS,

Church Farm House,
Church End,
Over,
Cambs. CB4 5NH

FOR WHICH I ENCLOSE CASH/CHEQUE/PO FOR

INCLUDING VAT & POSTAGE

NAME _____

ADDRESS _____

ALL MAIL ORDER BY RETURN. C.O.D. SERVICE WELCOME

C.T. ELECTRONICS

VAT
Unless otherwise stated all prices are EXCLUSIVE of VAT. Please add 8% to all orders. Carriage orders under £5 plus 20p. Over £5 post free.

All mail order and enquiries to 270 Acton Lane **Tel. 01-994 6275**

SEMICONDUCTORS

AC107 35p	BCY38 85p	MFP104			
AC125 25p	BCY39 £1-00	(2N5458)	35p		
AC126 25p	BCY55 £1-50	MFP105			
AC127 25p	BCY70 22p	(2N5459)	40p		
AC128 25p	BCY71 22p	0A4	10p		
AC176 25p	BCY72 22p	0A70	10p		
AC188 30p	BD121 75p	0A79	10p		
ACY17 25p	BD123 75p	0A81	10p		
ACY18 30p	BD124 75p	0A90	10p		
ACY19 30p	BD131 40p	0A91	10p		
ACY20 25p	BD140 25p	0A200	10p		
ACY21 30p	BD153 75p	0A202	10p		
AD140 60p	BD156 75p	0A210	35p		
AD142 50p	BDY11 £1-40	0A211	35p		
AD149 60p	BDY17 £1-60	0C16	90p		
AD161 44p	BDY19 £1-95	0C19	85p		
AD162 44p	BDY20 £1-40	0C22	55p		
AF114 25p	BF152 20p	0C26	85p		
AF115 25p	BF194 14p	0C28	60p		
AF116 25p	BF195 15p	0C35	60p		
AF117 25p	BF196 15p	0C36	85p		
AF118 60p	BF197 20p	0C42	40p		
AS221 80p	BF200 30p	0C44	20p		
ASV28 30p	BF24J 20p	0A200	10p		
BA102 35p	BFK29 30p	0C70	15p		
BA112 50p	BFK34 30p	0C71	12p		
BA114 16p	BFK85 30p	0C72	20p		
BA156 15p	BFK86 30p	0C75	25p		
BC107 12p	BFK86 30p	0C76	25p		
BC108 12p	BFY10 35p	0C77	40p		
BC109 14p	BFY44 50p	0C81	25p		
BC113 15p	BFY44 50p	0C83	25p		
BC115 15p	BFY51 25p	0C84	25p		
BC116 16p	BFY52 25p	0C139	30p		
BC117 20p	BFY53 25p	0C170	25p		
VC118 12p	BFY90 85p	0C200	80p		
BC147 11p	BSW63 65p	0C201	60p		
BC148 11p	BSW68 80p	0C202	75p		
BC149 12p	BY127 20p	TIP29A	45p		
BC153 15p	BY134 85p	TIP30	55p		
BC158 15p	IS100 15p	TIP31A	57p		
BC169 15p	IS103 15p	TIP32A	45p		
BC182 12p	MJ340 50p	TIP33A	£1-00		
BC183 12p	MJ481 85p	TIP34A	£1-40		
BC184 14p	MJ2801 £1-25	TIP35A	£3-20		
BC186 25p	MJ2901 £1-95	TIP36A	£3-50		
BC212 14p	MJE300 50p	TIP41A	70p		
BC212L 16p	MJE370 70p	TIP42A	85p		
BC213 14p	MJE371 50p	TIP29B	45p		
BC214 14p	MJE520 65p	TIP30B	80p		
BC301 25p	MJE2655 £1-20	TIP31B	65p		
BC302 25p	MJE3055 75p	TIP32B	77p		
BC303 40p	MM1613 45p	TIP33B	£1-06		
BC309 40p	MM1712 60p	TIP33C	£1-62		
BCY31 55p	MPE102 45p	TIP35B	£2-71		
BCY32 95p	MPE103 45p	TIP36B	£3-50		
BCY34 60p	(2N5457) 35p	TIP41B	78p		

TIP42B 85p	2N2907 25p
TIP50C 60p	2N2926 12p
TIP30C 72p	2N3053 25p
TIP31C 80p	2N3054 65p
TIP32C £1-00	2N3055 50p
TIP33C £1-20	2N3232 70p
TIP34C £1-60	2N3525 85p
TIP35C £3-00	2N3643 30p
TIP36C £3-75	2N3702 14p
TIP41C 90p	2N3703 12p
TIP42C £1-00	2N3704 12p
TIS50 40p	2N3705 12p
ZTX107 15p	2N3706 12p
ZTX300 10p	2N3707 12p
ZTX500 18p	2N3708 12p
ZTX501 20p	2N3709 12p
ZTX504 50p	2N3771 £1-70
ZTX531 30p	2N3772 £2-00
ZTX550 25p	2N3773 £2-50
IN659 4p	2N3819 35p
IN184 4p	2N3320 55p
IN1916 8p	2N3866 85p
IN4001 8p	2N3904 22p
IN4002 9p	2N3905 25p
IN4003 9p	2N4058 12p
IN4004 10p	2N4059 12p
IN4005 12p	2N4080 12p
IN4006 14p	2N4061 12p
IN4148 7p	2N4126 17p
2N696 15p	2N4286 15p
2N697 20p	2N4287 15p
2N698 20p	2N4288 15p
2N699 15p	2N4289 15p
2N705 12p	2N4290 15p
2N706A 15p	2N4444 £1-60
2N708 15p	2N4871 20p
2N930 20p	2N4903 £1-10
2N1132 25p	2N5069 £1-10
2N1302 16p	2N5191 90p
2N1303 16p	2N5194 £1-10
2N1304 25p	40360 50p
2N1305 25p	40361 50p
2N1306 25p	40362 50p
2N1307 25p	40679 90p
2N1308 25p	40683 70p
2N1309 25p	DS151 £1-60
2N1711 25p	Microwave Diode
2N2147 70p	
2N2160 65p	
2N2217 25p	
2N2218 25p	
2N2219 25p	
2N2220 20p	
2N2222A 25p	
2N2306 70p	
2N2477 30p	
2N2640 50p	
2N2846 £1-50	
2N2904 25p	
2N2906 25p	

S.C.R.s	
CRS1/05 40p	CRS1/10 50p
CRS1/20 60p	CRS1/40 65p
CRS1/60 90p	CRS3/10 62p
CRS3/20 82p	CRS3/40 90p
CRS7/400 £1-00	CRS16/100 85p
CRS16/200 90p	CRS16/800 £1-60
CRS16/800 £1-60	C106B 45p
C106D 70p	40669 90p
TIC44 35p	2N4444 £1-90
BT10/500A 90p	
BRIDGE RECTIFIERS	
W02 1A 20V 38p	BY164 1-4A 57p
MDA952 2 6A 100V 80p	
ZENER DIODES	
BZY98 Series 400mW	3-3V-33V, 5% 11p
	1-5W range 25p
	10W range 45p
L.E.D.	
HL209 38p	TIP5082 28p
MA2082R 20p	
L.D.R.	
ORP12 60p	
NE555 Timer 80p	

TRIACS	
TXL228B 8A 400V 85p	SC40D £1-40
SC40E £1-85	SC45D £1-60
SC45E £2-10	SC50D £2-42
SC50E £2-78	DIAC 25p
LINEAR I.C.s	
LM309K 5V IA	Voltage Reg. £2-10
LM723C 2-37V	150mA Voltage Reg. £1-05
789C Op Amp D.I.L.	799C Op Amp 8/14 D.I.L./7099 35p
741C Op Amp 8/14 D.I.L./7099 35p	748C Op Amp D.I.L. 75p
747C Dual OP Amp £1-20	ZN414 Radio I.C. £1-25
TAD100 Radio I.C.	inc. Filter £1-08
CA3014 £1-55	CA3018 £1-08
CA3028 £1-20	CA3038 £1-60
CA3046 85p	CA3048 £2-35
CA3075 £1-60	CA3090 £4-85
MC1303L £4-25	MC1310P £2-80

TO3 VOLTAGE REGULATORS	
L009 5V 650mA	L086 12V 500mA
L037 15V 450mA	£1-60 each

VEROBOARD	
2 1/2 x 3 1/2	0-15
2 1/2 x 5	23p
3 1/2 x 3	35p
3 1/2 x 5	40p
17 x 2 1/2	£1-05
17 x 3 1/2	£1-43
17 x 5	£1-84
PIN INS. TOOL	
S.P.F. CUTTER	72p
100 PINS DS	52p
100 PINS DS	30p
500 PINS DS	£1-20
500 PINS DS	£1-20

ALSO STOCKED
Electrolytic Capacitors Mullard, Sprague, Lorlin etc. Polyester, Polystyrene, Silver Mica Capacitors. etc. Resistors 1W-10Watt.
Potentiometers: carbon, wirewound, Preset, Rectilinear multiturn. Antex Soldering Irons, switches, rotary, slide, toggle, etc. Cable, veroboard.

Potentiometers		
Linear or Log	Single	Double
Rotary Pot	15p	42p
Rotary Switched	25p	—

★ ★ SPECIAL OFFERS ★ ★

MINIATURE MAINS TRANSFORMER. PRI 240V SEC. 12V 100MA Manuf.: Hinchley. Size: 36 x 45 x 40mm F.C. 53mm. Price 1—45p. 100—40p ea. 1,000—50p ea. 10,000—40p ea.

3 CORE PVC INSULATED MAINS CABLE. GREY ML6850. 3 x 7/0-2mm. Price 100m—£4.50, 1,000m—£35, 10,000m—£330. 0-47mfd. 50V MYLAR FILM CAPACITOR. Size 1in x 0-35in x 0-65in P.C. Mount. Price 100—4p ea. 1,000—3p ea.

240V A.C. SOLENOID. Reversible operation: twin coil. Size approx. 2 1/2in x 1 1/2in x 1 1/2in 80p ea.

30 unmarked OCT1 transistors £1-00
25 Unmarked 250mW Zenerdiode. 4-7V, 5-1V, 6-2V, 7-5V, 9-1V, 10V. Measured and tested £1-00

Please state voltage required £1-00

50 GE Diode 0A7 equivalent £1-00

TRANSFORMER: DOUGLAS PRI. 0, 115, 200, 220, 240 SEC. 25-0-25-0-6V, 2 1/2A, E4-50 x 50p p.p.

TRANSFORMER: DOUGLAS PRI. 0, 115, 200, 220, 240 SEC. 25-0-25-0-6V, 2 1/2A, E4-50 x 50p p.p.

748C Op Amp D.I.L. 75p

747C Dual OP Amp £1-20

ZN414 Radio I.C. £1-25

TAD100 Radio I.C. inc. Filter £1-08

CA3014 £1-55
CA3018 £1-08
CA3028 £1-20
CA3038 £1-60
CA3046 85p
CA3048 £2-35
CA3075 £1-60
CA3090 £4-85
MC1303L £4-25
MC1310P £2-80

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROBOARD WITH BASE AND P.K. screws

Length	Width	Height	
AB7 2 1/2in	5 1/2in	1 1/2in	55p
AB8 4in	4in	1 1/2in	55p
AB9 4in	2 1/2in	1 1/2in	55p
AB10 4in	5 1/2in	1 1/2in	55p
AB11 4in	2 1/2in	2in	65p
AB12 3in	2in	1in	50p
AB13 6in	4in	2in	77p
AB14 7in	5in	2 1/2in	90p
AB15 8in	6in	3in	£1-16
AB16 10in	7in	3in	£1-32
AB17 10in	4 1/2in	3in	£1-10
AB18 12in	5in	3in	£1-32
AB19 12in	8in	3in	£1-60

ALUMINIUM BOXES WITH SLOPING TOP PANEL—IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20 8in Long 9in Wide 3 1/2in High at back	£2-20
2in High at front 6in Slope to front With P.K. Screws	
AB21 As above but 10in long	£2-40
AB22 As above but 12in long	£2-60

ELECTRONIC COMPONENTS

BARGAIN COMPONENT PACKS
ALL COMPONENTS NEW AND UNUSED

- £1 plus 25p p.p. per pack. £5 for 5 packs p/free. Pack No.
- 1 500 Carbon resistors. 1, 2, 5, 10W.
- 2 100 Electrolytic Condensers.
- 3 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers.
- 4 250 Polyester, Polycarbonate, paper, etc., Condensers.
- 5 25 Potentiometers, assorted.
- 6 250 High-stab. 1%, 2%, 5% resistors.
- 7 50 Assorted Tagatrits.
- 8 1lb. Assorted nuts, bolts, washers, spacers, etc.
- 9 25 Assorted switches, rotary, lever, micro, toggled, etc.
- 10 50 Preset Potentiometers.
- 11 Trial mixed component pack £1.
- 12 Jumbo mixed pack £5.

DIGITAL INTEGRATED CIRCUITS

SN7400 18p	SN7428 50p	SN7473 40p	SN74107 55p	SN74167 £4-25
SN7401 18p	SN7430 20p	SN7474 40p	SN74110 80p	SN74170 £4-10
SN7402 20p	SN7432 42p	SN7475 55p	SN74118 £1-90	SN74174 £2-00
SN7403 20p	SN7433 70p	SN7476 45p	SN74119 £1-90	SN74175 £1-35
SN7404 20p	SN7437 50p	SN7480 80p	SN74121 £1-90	SN74176 £1-60
SN7405 20p	SN7438 50p	SN7481 £1-25	SN74122 £1-35	SN74177 £1-60
SN7406 20p	SN7440 50p	SN7482 80p	SN74123 £2-00	SN74180 £1-55
SN7407 30p	SN7448 75p	SN7483 £1-08	SN74141 £1-08	SN74181 £8-00
SN7408 20p	SN7442 75p	SN7484 90p	SN74145 £1-50	SN74182 £2-00
SN7409 40p	SN7443 £1-00	SN7486 45p	SN74146 £1-50	SN74183 £2-45
SN7410 16p	SN7445 £1-70	SN7490 75p	SN74153 £1-35	SN74184 £2-40
SN7411 25p	SN7446 £2-00	SN7491 AN £1-00	SN74155 £1-55	SN74185 £2-45
SN7412 22p	SN7447 £1-50	SN7492 75p	SN74156 £1-55	SN74192 £2-00
SN7413 40p	SN7448 £1-75	SN7493 80p	SN74157 £1-60	SN74193 £2-00
SN7416 30p	SN7450 20p	SN7494 80p	SN74158 £1-60	SN74194 £2-50
SN7417 30p	SN7451 20p	SN7495 80p	SN74161 £1-6	

COMPONENTS GALORE. Pack of 500 mixed components manufacturers' surplus plus fall out. Pack includes resistors, carbon and W.W., capacitors, various transistors, diodes, trimmers, potentiometers, etc.

Send £1 plus 15p P. & P. C.W.O. To:

CASCADE COMPONENTS COMPANY
Bankhead Farm, South Queensferry,
West Lothian

MISCELLANEOUS

12 VOLT 21in 13 watt FLUORESCENT LIGHTING (by THORN/AEI) with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc.



Guaranteed
£5.50 inc VAT and post.
List price £7.02 inc VAT.

SALOP ELECTRONICS Tel. 53206
23 Wyle Cop, Shrewsbury, Shropshire

Build the Mullard C.C.T.V. Camera Kits are now available with comprehensive construction manual (also available separately at 80p).
SEND 5" x 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
124 Colne Road, Twickenham
Middlesex TW2 6QS

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

LOW COST I.C. MOUNTING. 100 I.C. pin sockets 60p. Quantity rates. S.A.E. details and sample. 7 and 8 hole plastic supports 5p/pair. (P. & P. 5p/order). LED (MLED500) 20p each post free. Quantity rates. P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

SINTEL Add 10p P. & P. for orders under £2.
Data, and circuits where appropriate, supplied with orders, or available separately (4p stamp each).

3 Digit DIP LED calculator display £1-20 - VAT - £1 29
High Quality 8-3in LED 7 seg. display 85p - VAT - £1 02
MK50250N Alarm Clock IC £8-90 - VAT - £7 45
Send for our new simple MK50250N circuit diagrams
Soldercon IC socket pins — 1,000 pins for £1-60 - VAT - £1 82
MK50250N + 4 x DL704 0 3in LED 5 £10-20 - VAT - £11-01
Complete circuits and special prices for MK50250N with LED S.

SINTEL, 53B ASTON STREET, OXFORD. Tel (0865) 43203

FLUORESCENT LIGHT KIT

12 v
8 w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied: the tube, white enamelled metalwork, first quality components, P.C.B., instructions, etc.

Price only £3-19 inc VAT post & packing
Ready built £3-78
Diffuser only 55p extra

ALUMINIUM BOXES

	7 5/8"	10"	12 1/2"	15"	18"	21"	24"	30"
7 5/8"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	39p
8"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	39p
10"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	43p
10 1/2"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	39p
11"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	39p
12"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	39p
13"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	55p
15"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	by 4"	82p
16"	by 7"	by 7"	by 7"	by 7"	by 7"	by 7"	by 7"	82p

Order now to —

ELECTRONIC DESIGN ASSOCIATES
DEPT PE
82 Bath St., Walsall, WS1 3DE. Phone 33652

fibres optic suppliers

MARE'S TAILS. Build a decorative display with this professionally finished unit, 22in diameter with 7,000+ fibres. Looks immaculate, £8.70.
FIBROFLEX SIZE 1. Flexible 440 strand glass light conduit, bundle dia. 1.14mm. 48p per metre (£3 per 10m).
FIBROFLEX SIZE 4. 2.28mm bundle dia. £1.50 per metre (£12 per 10m).
CROFON 1810. 64-strand plastic light conduit, bundle dia. 1.8mm, O.D. 3.3mm. £1-20 per metre (£9-30 per 10m).

PLASTIC OPTICAL MONOFIBRE. For multiple illumination from one source, displays, internal illumination, effects, optical coupling, etc.
FP20 (0.5mm dia.)—50p per 10m. £4 per 100m.
FP40 (1mm dia.)—£2-20 per 10m; £14 per 100m.
FP80 (1.5mm dia.)—£4 per 10m; £38 per 100m.
OPTIKIT 183. Contains 2m Crofon 1810 plus 5m each FP20, FP40, FP80 plus polishing compound. A handy pack for the experimenter. £4.70.

LENSES AND REFLECTORS. We stock a range of 6 lenses and 5 reflectors for use in proximity detectors, intruder detectors, batch counters, tachometers, short range optical communications.
OPTIKIT LS. 1 each of 6 lenses. £2-50.
OPTIKIT RRS. 1 each of 5 reflectors. £1-50.

CIRCULAR POLARISERS. Cut that glare. Reduce specular reflection by up to 20x—enhance contrast on cr. LED displays, nixies, instruments, etc. Available in red/crim/ green/neutr. 50mm square 60p; 75mm £1-20; 150mm £4.

LINEAR POLARISERS. For light valves, stress analysis, type MH32. Type KM42 is for high temp. use in projectors. Use a pair to make a psychedelic light show. Price as for circular polarisers.

LIGHT SOURCES AND DETECTORS: MV54 Miniature (2mm) Red LED, 20p (10+ 18p). MLED500 T092 Red LED, 20p (10+ 18p). MLED92 Infra-Red Emitter, 30p (10+ 27p). XC209-R 3mm Red LED, 20p (10+ 18p); XC209-Y or -G Yellow/Green, 30p (10+ 27p); 2N5777 High Sensitivity Photodarlington Silicon Detector, gain x2,500, 50p (10+ 45p); MRD150 Photo-transistor—high speed, 4us good sensitivity, 79p (10+ 67p).

****NEW MLS203.** Latest Motorola Light Activated SCR. High sensitivity 10mW/cm²; high current 400mA (5A peak); 60V. Switch small motors or relay direct from optical control, up to 24V power. £1-20 (10+ £1-10).

SE055 ULTRASONIC TRANSDUCER. For remote control 40kHz. Tx/Rx pair, £3-50.

Please add 8% VAT to prices above
Send 9in x 6in S.A.E. for short form list.

FIBRE OPTIC SUPPLIERS

(Dept. PE), P.O. Box 702
London W10 6SL

PRINTED CIRCUIT MANUFACTURERS offer any P.E.E. Project P.C. ready drilled. One Price 65p. C.W.O. Also P.C. production, Design, Art-Work and Photography undertaken. Send basic circuit, P.C. layout or P.C. Master stating quantity required for estimate by return or phone: W.K.F. ELECTRONICS, Dept. P.C., Welbeck Street, Whitwell, Worsop, Not't., S80 4TW. Telephone Whitwell (Derbys) 695.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty P.V.C. faced steel. Hundreds of radio, electronic and hi-fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Prompt despatch. Free literature, BAZELI, Department No. 23, St. Wilfrid's, Foundry Lane, Hailton, Lancaster, LA2 6LT.

ENAMELLED COPPER WIRE

S.W.G.	1/1b Reel	1/2 Reel
10-14	£1-90	£1-05
15-19	£2-00	£1-10
20-24	£2-05	£1-15
25-29	£2-10	£1-20
30-34	£2-20	£1-28
35-40	£2-35	£1-35

All the above prices are inclusive in U.K.

COPPER SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone 061-224 3553

METER REPAIRS. Ammeters, voltmeters multi-range meters, etc. Send to METER, REPAIRS, 21 Mount Road, Thundersley, Benfleet, Essex, S87 1HA.

SLOW SPEED MOTORS required (about 1r.p.m.) any quantity considered. Phone Mr. SMITH, 061-633 3527.

YOUR OWN DESIGN FRONT PANELS in 280 micron aluminium. Details from PROJECTION AUDIOGRAPHICS, 9 Wilkins Road, Cowley, Oxford.

AUDIOSCAN, the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send 7p in stamps for bargain list to: AUDIOSCAN, Dept. PE9, 4 Princes Square, Harrogate, Yorkshire.


FANTASTIC NEW MICROTEST 80

MEASURES ONLY
90 x 70 x 18mm



Amazing Value at £11.95
8 fields of measurement and 40 ranges

Volts d.c. 6 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V (20kΩ/V)
Volts a.c. 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V (4kΩ/V)
Amp. d.c. 8 ranges: 50µA, 500µA, 5mA, 50mA, 500mA, 5A
Amp. a.c. 5 ranges: 250µA, 2.5mA, 25mA, 250mA, 2.5A
Ohms 4 ranges: Low Ω, Ω x 1, Ω x 10, Ω x 100 (da 1/10 Ω to 1MΩ)
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +82dB
Capacity 4 ranges: 25µF, 250µF, 2,500µF, 25,000µF.

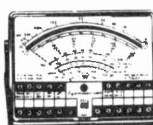

SUPERTESTER 680 R IC

20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields @ Scale width and small case dimensions (128 x 95 x 32mm) @ Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading @ Simplicity and ease of use and readability @ Full ranges of accessories


£18.50

Accessories Extra
Accessories (extra) available to convert Microtest 80 and SuperTester 680R into following SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLT METER, AMPER CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details.

MORE RANGES FOR LESS MONEY!


AC/DC Multimeter type U4324

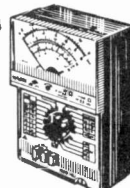A-DC 0-05-3A-6 Ranges.
A-AC 0-3-3A-5 Ranges.
V-DC 0-6-120V-9 Ranges.
V-AC 3-90V-8 Ranges.
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 15 Mohm—5 ranges. Decibel: -10 to +12dB. Accuracy: ±2.5%. DC ±4%. AC. Dimensions: 167 x 98 x 63mm. Only £8.85



ALPHANUMERIC NIXIE TUBES B7971

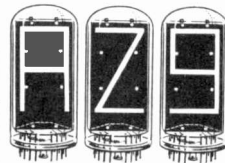The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alpha-



numeric NIXIE tube provides many unique benefits including * 17V-21mA * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light ... 200 footcandle brightness * Long life with no loss of brightness * Character height 2½in.

Bases for above 80p each
Price only 99p each plus 16p P./P.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES


Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V d.c. Current 14mA. Pulse duration 100µs. Character height 0.51, overall size 1-4.

Brand new, guaranteed. Surplus to manufacturer's requirements. Type 55853at

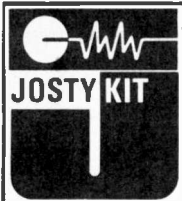1-25 £1-00; 25+ 90p; 100+ 80p; 1,000+ price on application.

Add 8% VAT to all Home - 35p P&P

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781



ONE OF
EUROPE'S
LEADING
ELECTRONIC KITS

Post free Mail Order
S.A.E. For Catalogue

TELEVIEW

414 CATCOTE ROAD
HARTLEPOOL
CLEVELAND

HARDWARE. Comprehensive range of screws, nuts washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-off's and small runs. Machine engraving in metals and plastics, contour milling. Send 2 4p stamps for catalogue. RAMAR CONSTRUCTOR SERVICES, Masons Road, Stratford on Avon. Warwick, CV37 9NF.

HOME SCIENTISTS

Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists DOZENS of HIGHLY UNUSUAL, LOW-COST BARGAINS, READY-BUILT MODULES.

Here are just a few examples, there are stocks more!

Dazzling MINI-STROBE (pocket size) £2.90
PEOPLE DETECTOR £3.20
Big-Ear SOUND-CATCHER £3.20
Mini DREAM LABORATORY £3.20

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and we'll RUSH YOU A COPY (YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!)

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey
(Mail Order U.K. only)

THE CHIPS ARE DOWN! AY-5-1224 digital clock chip now £3.95 inc. VAT, post free. (Circuit and details S.A.E. GREENBANK ELECTRONICS, Dept. 320, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

BUILD THE **TREASURE TRACER MK III** Metal Locator



- Vancap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send s.a.e. for leaflet

Complete kit **£9.80** Built, tested and guaranteed **£13.75**
P. & P. 45p + 78p VAT P. & P. 45p + £1.10 VAT

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order Only)

IC SOCKET PINS for low cost mounting of 8 to 40 pin DILs. 70p (+ 5p VAT) for strip of 100, £1.50 (+ 12p VAT), for 3 x 100, £4 (+ 32p VAT) for 1,000. Instructions supplied—send S.A.E. for sample. 10p P. & P. for orders under £2. S/NTEL, 53b Aston Street, Oxford. Tel. 0865 43203.

SITUATIONS VACANT

ELECTRONIC CRAFTSMEN

Is your present job routine and uninteresting?

We are a research establishment and our craftsmen are engaged on a wide variety of work in the fields of prototype and small batch wiring and assembly, test and inspection, maintenance fault finding and repair. Why not join us and enjoy working in first class conditions in the country.

You can expect gross earnings including overtime of £45 per week, and we can offer good housing at low rental (for applicants who reside outside the radius of our Assisted Travel Area) together with 3 weeks' paid holiday with holiday bonus, free pension and excellent sick benefit scheme.

Applicants who should have served a recognised apprenticeship or have had equivalent training together with experience in one of the fields detailed should phone Tadley 4111 (STD 073-56 4111) Ext. 5230, or write to:

Industrial Recruitment Officer
(PA/55/PE) Procurement Executive
Ministry of Defence
AWRE Aldermaston
Reading, Berks. RG7 4PR

MEN!
£70p.w.
can be yours

Jobs galore! Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. London Computer Operators Training Centre subscribes to the British Government backed National Computing Centre code of practice for Computer Training Schools so you know your training will be second to none.

After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators Training Centre Y32, Oxford Hse. 9-15 Oxford St., W.1. Tel. 01-734 2874

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

WANTED: P.E. Sound Synthesiser series, P.E. Feb.'73 to Feb.'74 inclusive, good condition. J. MERCHANT, 20 Mount Street, Aberdeen, AB2 4RB.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for service sheets, manuals, books on radios, T.V.s, etc. Service sheets 40p plus S.A.E. Free book lists on request. Back issues of P.W., P.E., E.E., TV available 25p plus 7p post. S.A.E. with enquiries: B.T.S. (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

SERVICE SHEETS for over 6000 models of Televisions, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only 30p, plus S.A.E. with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. S.A.E. enquiries. Catalogue 20p plus S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 20p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

FOR SALE

VALVES, VALVES AND MORE VALVES. Large stocks 1930-1974, many obsolete. Also available many types of transistors and styli. Price lists available 15p. COX RADIO, The Parade, East Wittering, Sussex. West Wittering 2023.

60 COPIES PRACTICAL ELECTRONICS March 1969 to date. Highest offer secures. Box No. 58.

LADDERS

LADDERS, timber and aluminium. Tel. Telford 586644 for brochure.

BOOKS AND PUBLICATIONS

ELECTRONICS MEN. You are worth more than a measly £40 or £50 a week. Last year I earned £3,600 for six months work, the other six I had off. You could do similar, my booklet explains how. It's 65p from ALBEN, 3 Church Street, 1 Diss, IP22 3DD.

PROFESSIONAL SERVICES

PATENTS AND TRADE MARKS. KINGS PATENT AGENCY LIMITED (Est. 1886). B. T. King, Director, M.I.Mech.E., Registered Patent Agent, 146a Queen Victoria Street, London, EC4V 5AT. Booklet on request. Tel. 01-248 6161. Telex 883805.

CALCULATORS

SAVE MONEY!
BUY DIRECT FROM
THE SPECIALISTS
VATMAN

£14.91 + VAT

45p P & P. and please add 8% VAT on all total prices.

Model	Our Price	Functions
Decimo Vatman	14.91	P. [A], R. G. 8D. E. F. K4. M. I. J. C. L5. B. N.
Decimo Vatman	16.91	P. [A], R. G. 8D. E. F. K4. H. I. J. C. L5. BM. N.
Decimo Memory	23.98	P. M. [A], R. G. 8D. E. F. K2. M. I. J. C. L5. BM. N. [W]
Decimo Slide rule	25.98	P. M. [A], R. G. 8D. E. F. K2. [H], [X], [J], I. C. L5. BM. N. S. M. [A], R. G. 8D. E. F. K2. H. I. J. L5. BM. N.
Decimo 9202	39.93	P. M. [A], R. G. 8D. E. F. K4. H. I. C. B. N.
Anita 911	39.95	T. M. [A], R. G. 8D. E. F. K2. K4. H. I. C. BM. N.
Bohn Omnitrex*	44.95	T. M. [A], R. G. 8D. E. F. K2. G. [H], [X], [J], I. C. M. V. U.
Bohn Omnitrex SO1*	50.95	
JUST OUT		
Bohn Metric*	69.22	T. W. [A], R. G. 8D. E. F. K2. H. I. M. C. V also 12 conversions in/ma, ft/metres, yds/metres, miles/km, ozs/ccs, qts/litres, gals/litres, F/C°, ozs/grams, lb/kg, area measurement, cubic measurement.
Bowmar MX75*	39.97	T. M. [A], R. 8D. E. F. K4. H. I. J. C. V.
Bowmar MX100*	65.99	T. M. 8D. E. F. K4. C. V. J. true scientific 20 functions for algebra, geometry, logs, calculus, integrals, etc.
Ricmac 121MD	44.16	OFFICE CALCULATORS S. 12D. [A], E. F. M. [W]. Ph. I. J. Item count.
Ricmac 1009P	81.97	2 colour print-out. A. 10D. F/S. K4. M. sub total. acc + X buffer
Ricmac 1220	121.19	Dhio. 12D. [A], 2M. rounding, [W] silent.

Code
A = percentage, B = battery (main adaptor extra), BM = battery (main adaptor incl.), C = carrying case, D = digit, E = - x ÷, F = floating decimal point, F/S = floating point and select, Fz = floating point and 2 places, Fz = floating point and 7 places, G = green display, H = x², I = x³, J = xⁿ, K² = constant X, K* = constant x + - , L5 = 50 hr. battery life, L10 = 100 hr. battery life, M = memory, N = negative entry, P = pocket, R = rotating, S = desk model, T = hand and desk, U = display blanking, V = rechargeable, W = exchange, X = √x, [] = extra separate keys, * = positive lead

BARCLAY ELECTRONICS
STANLEY HOUSE, 1115 FINCHLEY ROAD
LONDON, NW11



OSMABET LTD

We make transformers amongst other things

AUTO TRANSFORMERS 110-200/220/240V
30W. £2-10; 50W. £2-70; 75W. £3-45; 100W. £4; 500W. £12; 750W. £18-50; 1000W. £28-25, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V 1.5A. £1-45; 3A. £1-80; 6A. £3-80; 12V 1.5A. £1-90; 3A. £3-30; 6A. CT. £4-50; 18V 1.5A. CT. £3-30; 24V 1.5A. CT. £3-30; 5A. CT. £4-50; 5A. £6-75; 8A. £8-70; 12A. £12-40; 40V 3A. CT. £8; 50V 8A. CT. £15-75; 25V 2A + 25V 2A. £8-40; 12V 4A + 12V 4A. £8-40.

LT TRANSFORMERS TAPPED SEC. Prim 200/240V
0-10-12-14-16-18V 2A. £3-30; 4A. £4-50.
0-12-15-20-24-30V 2A. £4-50; 4A. £8.
0-5-20-30-40-60V 1A. £4-20; 2A. £8.
0-40-50-60-80-90-100-110V 1A. £8-40.

MIDGET RECTIFIER TRANSFORMERS
For FW rect. 200/240V a.c. 6.0-8V 1.5A or 9.0-9V 1A
£1-65 each; 12-0-12V 1A of 20-0-20V 0.75A or 3-0-3V 0.3A or 7-0-7V 0.75A or 20-0-20V 0.15A or 8V 0.5A + 8V 0.5A or 9V 0.35A + 8V 0.35A or 12V 0.25A + 12V 0.25A or 20V 0.15A + 20V 1.5A, all at £1-90 each.

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec. 425-0-425V 500 MA. 6.3V CT 6A. 6.3V CT 8A. 0-5-6.3V 3A. £18-75; TX1 425-0-425V 250 MA. 6.3V CT 4A. 6.3V CT 4A. 0-5-6.3V 3A. £11-25; MT3 Prim 0-110-240V, sec. 250V 100 MA. 6.3V 2A. E/S. £3-75.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec., tapped 3-8-15 ohms. A-A 6.6kΩ 30W £8-75; A-A 3kΩ 50W £18-15; 100W (EL34 KT88, etc.). £17-25; MRT/10, tapped multi O/P 10W £4.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 35p.

LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W. £7-80; 35W £8-40; Hi-Fi Major Module 20W w/wireless crossover. £11-80; Baker Speaker List. FANE 60W £13-50; EM1 13 x 8in. 8Ω, £2; 5in 8Ω, £1-15; 7 x 4in 15Ω, £1-60; 8 x 5in 3, 8, 15 or 80Ω, £1-75 each.

LOUDSPEAKERS
2½in 8 or 75Ω, 2½in 8 or 25Ω, 3in 3, 8, 25 or 35Ω, 3½in 8 or 80Ω, 85p each; 5in 3, 8 or 25Ω, 5 x 3in 3 or 8Ω, £1-15; 7 x 4in 3 or 15Ω, 6½in 3Ω, £1-30; 10 x 6in 3Ω, £1-50.

SPEAKER AUTO MATCHING TRANSFORMER
12W 3 to 8 or 15Ω up or down. £1-50.


"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter, tape spools, cassettes, demagnetise tape heads. 200/240V a.c. £3-75.

SYNCHRONOUS GEARED MOTORS 200/240V a.c.
Brand new, 5mths. Built-in gearbox. 7r. p.n., 75p each.
Carriage and VAT extra on all orders.
S.A.E. ENQUIRIES, LISTS. MAIL ORDER ONLY

48 Kenilworth Road, Edgware, Middx. HA8 8YJ
Tel 01-958 9314

Please mention
**PRACTICAL
ELECTRONICS**
when replying to
ADVERTISEMENTS

SYNTHESISER Modules by Dewtron®

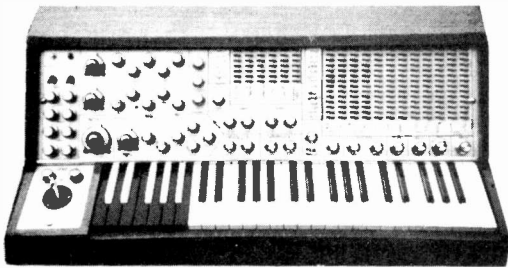

The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/p/s; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 15p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

P.E. ORION

Complete kit of semiconductor £9.95
High quality printed circuit £2.95

THIS GLASS FIBRE P.C.B. IS ROLLER TINNED AND
SCREEN PRINTED WITH COMPONENT LOCATIONS.

FERRANTI semiconductors

BFSS9	18p	ZTX304	29p	ZTX504	55p	ZS170	14p
BFSS0	21p	ZTX310	12p	ZTX510	25p	ZS171	16p
BFSS1	21p	ZTX311	14p	ZTX530	23p	ZS172	22p
BFSS6	19p	ZTX312	14p	ZTX531	34p	ZS174	26p
BFSS7	23p	ZTX313	16p	ZTX550	25p	ZS176	33p
BFSS8	23p	ZTX314	17p	ZTX551	27p	ZS178	58p
ZTX107	12p	ZTX330	21p	2N3055	76p	ZS270	15p
ZTX108	9p	ZTX331	23p			ZS271	22p
ZTX109	14p	ZTX382	15p	* DIODES *		ZS272	25p
ZTX212	14p	ZTX383	19p	ZS120	15p	ZS274	29p
ZTX213	15p	ZTX384	23p	ZS121	16p	ZS276	38p
ZTX214	19p	ZTX450	23p	ZS122	19p	ZS278	61p
ZTX239	16p	ZTX451	25p	ZS123	25p		
ZTX300	16p	ZTX500	16p	ZS124	29p	* ZENERS *	
ZTX301	17p	ZTX501	17p	ZS140	25p	KSO30A to	28p
ZTX302	23p	ZTX502	23p	ZS141	40p	KS180A	28p
ZTX303	18p	ZTX503	18p	ZS142	39p	BZV19 series	15p

MOTOROLA BD699 £1-10, BD700 £1-22, MJE2955 £1-30, MJE3055 75p.
SIGNETICS UA748CV operational amplifier 55p each.
RCA PRICES SLASHED! CA3090Q stereo decoder only £3-25 each.
ZN414 THE FAMOUS FERRANTI RADIO I.C. Only £1-32 with data.
SCORPIO Mk. II. Complete kit of semiconductors £5-65 (State 6V or 12V).
ALL DEVICES SOLD BY US ARE TOP GRADE. BRAND NEW AND TO FULL MANUFACTURER'S SPECIFICATION. We do not sell seconds or rejects. We are specialists in FERRANTI semiconductors and can supply any device to order. S.A.E. for quote. Send S.A.E. for our free data sheet and price list for FERRANTI semiconductors.

POSTAGE AND PACKING 10p. FREE ON ORDERS OVER £3
ALL OUR PRICES INCLUDE VAT

DAVIAN ELECTRONICS
PO BOX 38, OLOHAM, LANCOS, OL2 6XJ

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £
07	20	1 8	7.0 x 6.0 x 6.0	2.55 38
149	60	3 12	9.9 x 7.7 x 8.6	3.98 45
150	100	5 8	9.9 x 8.9 x 8.6	4.45 45
151	200	8 0	12.1 x 9.3 x 10.2	7.39 53
152	250	13 12	12.1 x 11.8 x 10.2	8.93 73
153	350	15 0	14.0 x 10.8 x 11.8	10.80 73
154	500	19 8	14.0 x 13.4 x 11.8	12.41 91
155	750	29 0	17.2 x 14.0 x 14.0	18.65 * *
156	1000	38 0	17.2 x 16.6 x 14.0	26.50 * *
157	1500	46 0	21.6 x 13.4 x 18.1	30.23 * *
158	2000	60 0	21.6 x 15.3 x 18.1	33.70 * *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.52 30
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.64 38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	3.75 45
66	300	6 4	9.9 x 9.6 x 8.6	" " " " " "	5.29 53
67	500	12 8	12.1 x 11.2 x 10.2	" " " " " "	8.02 67
84	1000	19 8	14.0 x 13.4 x 14.3	" " " " " "	12.44 91
93	1500	30 4	14.0 x 15.9 x 14.3	" " " " " "	16.65 * *
95	2000	32 0	17.2 x 16.6 x 14.0	" " " " " "	22.00 * *
73	3000	40 0	21.6 x 13.4 x 18.1	" " " " " "	31.90 * *

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets, 20VA £2.85, P & P 38p.
500VA £9.50, P & P 80p. 1000VA £15.92, via B.R.S.

LOW VOLTAGE SERIES (ISOLATED)

PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	P & P £
111	0.5	0-25	1 8	4.8 x 2.9 x 3.5 0-12V at 0.25A x 2	1.34 23
213	1.0	0-5	1 4	4.8 x 5.8 x 4.1 0-12V at 15A x 2	1.58 30
17	2	1 12	1 4	7.0 x 6.4 x 6.1 0-12V at 1A	2.09 38
18	4	2 12	1 8	8.3 x 7.7 x 7.0 0-12V at 2A x 2	2.60 38
70	6	3 3	8 8	8.9 x 8.0 x 7.7 0-12V at 3A x 2	3.75 45
108	8	4 5	8 8	9.9 x 8.9 x 8.6 0-12V at 4A x 2	4.15 45
72	10	5 6	4 8	9.9 x 9.6 x 8.6 0-12V at 5A x 2	4.67 53
116	12	6 12	6 12	9.9 x 10.2 x 8.6 0-12V at 5A x 2	5.02 53
17	16	8 12	8 12	12.1 x 9.9 x 10.2 0-12V at 8A x 2	6.62 60
115	20	11 8	14 0	9.6 x 11.8 0-12V at 10A x 2	9.45 73
187	30	15 15	8 14 0	12.1 x 11.8 0-12V at 15A x 2	12.29 85
226	60	32 0	32 0	17.2 x 15.3 x 14.0 0-12V at 30A x 2	15.30 * *

30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.65 30
79	1.0	2 4	7.0 x 6.7 x 6.1	" " " " "	2.18 38
3	2.0	3 4	8.9 x 7.7 x 7.7	" " " " "	3.18 38
20	3.0	4 8	9.9 x 8.3 x 8.6	" " " " "	4.12 45
21	4.0	6 4	9.9 x 9.6 x 8.6	" " " " "	4.67 53
51	5.0	6 12	12.1 x 8.6 x 10.2	" " " " "	5.83 53
117	6.0	8 0	12.1 x 9.3 x 10.2	" " " " "	6.51 60
88	8.0	12 0	12.1 x 11.8 x 10.2	" " " " "	9.00 67
89	10.0	13 12	14.0 x 10.2 x 11.8	" " " " "	8.97 73

50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.35 30
103	1.0	2 12	8.3 x 7.4 x 7.0	" " " " "	3.08 38
104	2.0	5 8	7.9 x 8.9 x 8.6	" " " " "	4.26 45
105	3.0	6 12	9.9 x 10.2 x 8.6	" " " " "	5.28 53
106	4.0	10 0	12.1 x 10.5 x 10.2	" " " " "	6.91 67
107	6.0	12 0	14.0 x 10.2 x 11.8	" " " " "	11.00 67
118	8.0	12 0	14.0 x 12.7 x 11.8	" " " " "	11.80 85
119	10.0	25 0	17.2 x 12.7 x 14.0	" " " " "	15.45 * *

60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60V	2.12 38
125	1.0	3 4	7.9 x 7.7 x 7.7	" " " " "	3.10 38
127	2.0	6 4	9.9 x 9.6 x 8.6	" " " " "	4.62 45
125	3.0	8 12	12.1 x 9.9 x 10.2	" " " " "	6.84 60
123	4.0	13 12	12.1 x 11.8 x 10.2	" " " " "	7.96 67
40	5.0	12 00	14.0 x 10.2 x 11.8	" " " " "	8.87 73
120	6.0	15 8	14.0 x 12.1 x 11.8	" " " " "	10.27 85
121	8.0	25 00	14.0 x 14.7 x 11.8	" " " " "	13.64 * *
122	10.0	2 0	17.2 x 12.7 x 14.0	" " " " "	15.93 * *
189	12.0	29 00	17.2 x 14.0 x 14.0	" " " " "	18.16 * *

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P £
238	200	2	2.8 x 2.6 x 2.0	3-0.3	1.40 10
212	1A, 1A	1	4 6.1 x 5.8 x 4.8	0.6, 0.6	1.67 30
13	100	4	3.9 x 2.6 x 2.9	0-0.9	1.28 13
235	330, 330	4	4.8 x 2.9 x 3.5	0.9, 0.9	1.42 19
207	500, 500	1	0 6.1 x 5.4 x 4.8	0.9, 0.8-9	1.75 30
208	1A, 1A	1	12 7.0 x 6.4 x 6.1	0.8-9, 0.8-9	3.00 38
236	200, 200	4	4 4.8 x 2.9 x 3.5	0.15, 0.15	1.30 19
214	300, 300	1	4 6.1 x 5.8 x 4.8	0.20, 0.20	1.76 30
221	700 (d.c.)	1	8 7.0 x 6.1 x 6.1	20-12.0-12-12.0	1.98 38
206	1A, 1A	2	12 8.3 x 7.7 x 7.0	0.15-20, 0.15-20	3.15 38
203	500, 500	2	4 8.3 x 7.0 x 7.0	0.15-27, 0.15-27	2.73 38
204	1A, 1A	3	4 8.9 x 7.7 x 7.7	0.15-27, 0.15-27	3.50 38

*Carriage via B.R.S.

PLEASE ADD 8% FOR V.A.T. INCLUDING P. & P.


BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST

DIG Discounts

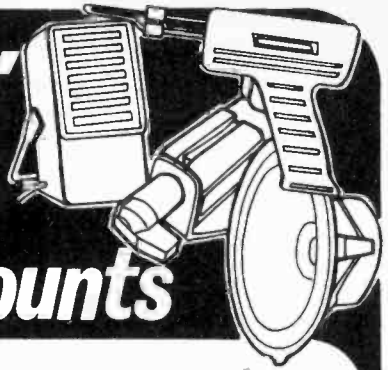

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS	£	ELAC 8in 8 ohm Dual cone	2-30
EMI 13in x 8in 3, 8 or 15 ohm		ELAC 10in 8 ohm Dual cone	3-50
Plain	2-05	GOODMANS 6in 8 ohm Dual cone	2-15
With Co-Axial Tweeter	2-20	FANE, 7in x 4in, 3 or 8 ohm	1-00
8 ohm only	4-10	ADASTRA 10in, 8 or 15 ohm, 10W	3-65
Type 350, 8 ohm, 20W	7-95	BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7-65
6in, 8 ohm, 10W	2-40	5in, 8 ohm, C/Mag.	P. & P. 0-85
8in, 8 ohm, 10W	3-75	8in x 5in, Dual cone 8 ohm, 10W	0-50
12in, 8 ohm, 20W	6-70	ELAC 6in 8 ohm Dual cone	P. & P. 0-15
8in x 5in, C/Mag. 5W	1-25		
8in x 5in, Dual cone 8 ohm, 10W	2-55		
ELAC 6in 8 ohm Dual cone	2-15		

TWEETER AND CROSSOVER	£	Dome Tweeter 8 ohm, 30W	5-40
EMI 3in, 3 or 8 ohm C/Mag.	1-25	Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-20
Cone Tweeter 8 or 15 ohm, 10W	2-80		
Cone Tweeter 8 ohm, 3W	1-45		P. & P. 0-15
Horn Tweeter 8 ohm, 20W	6-40		

KIT FORM CABINETS, TEAK VENEER.	£	13in x 8in cutout	3-80
12in x 12in x 6in with 8in, 8in x 5in or 6in and 3in cutout	3-30	18in x 11in x 9in with 13in x 8in cutout for EMI 350	4-25
17in x 10in x 9in with 8in or			P. & P. each 0-45

MICROPHONES	£	TW209	5-75
CM70 Planet stick metal, switch crystal	1-55	CONDENSER MIKE 600 ohm, uni-dir	9-35
DM100 Dynamic omni-dir, ball metal	4-75	Cassette Stick Mike with R. Control on/off switch (2.5 and 3.5mm J/Ply)	1-45
UD130 50K/600 ohm, uni-dir, ball metal	6-40		P. & P. 0-20

SOLDERING IRONS	£	spare Bib, etc.)	3-30
ANTEX CN240 15W	1-90	X25 25W (low leakage)	1-90
SK1 Kit (15 watt iron, 2)			P. & P. 0-10

CARTRIDGES AND STYLII	£	SONOTONE 9TACH or 9TACH/G diam.	1-80
AC08 GP91/28C or 38C Stereo comp.	1-00	3B09 Stereo ceramic diam.	1-90
GP93/1 or 95/1 Stereo crystal	1-35	GOLDRING G850	2-95
GP94/1 or 98/1 Stereo ceramic	1-75	G800	3-85
GP101 Crystal comp.	0-80	G800E	8-90
GP104 Stereo ceramic	1-65	D. Diamond Stylii for above	1-10
BSR X5M or SXH Crystal comp.	1-70	G800/G850	1-85
SX5M or SX6H Crystal comp.	1-90	G800E	3-85
SC5M Stereo ceramic	2-60		P. & P. 0-05

BATTERY ELIMINATORS	£	output 6, 7.5 or 9 d.c. output at 300mA	2-80
240V input 6, 7.5 or 9 300mA	2-95		P. & P. 0-15
12V d.c. input (please specify)			

TAPES	Stnd.	LP	DF	PLASTIC LIBRARY CASSES
5in	50p	65p	1-25p	5in Reels 18p. 5in. 22p. 7in. 25p.
5in	65p	80p	1-45p	P. & P. 1-3 9p each. 4 or more lot 30p
7in	80p	1-10p	1-80p	

LOW NOISE CASSETTES	£	Cassette Head Cleaner	0-85
C60	1-5	P. & P. 1-5 each	0-03
C90	35p	6-10 lot	0-15
C120	65p	11-20 post free	
	75p		

BIB ACCESSORIES	£	CALCULATORS	£
Tape Editing Kit, Ref. 23	1-35	SINCLAIR Cambridge Scientific	£19.95
Recording Tape Splicer, Ref. 20	1-15		
Cassette Tape, Editing, Ref. 24	1-50		
Cassette Salvage Kit, Ref. 29	0-45		

WHARFEDALE SPEAKER BARGAINS	£	P & P
Linton 2 Kit (pr.)	19-00	1-00
Glendale 3 Kit (pr.)	83-50	1-50
Dovedale 3 Kit (pr.)	52-00	1-50
Denton 2 Speaker (pr.)	80-00	2-00
Linton 2 Speaker (pr.)	39-50	2-00
Dovedale 3 Speaker (each)	42-00	2-00
Glendale 3 Speaker (pr.)	57-00	3-00
Kingsdale 3 Speaker (each)	59-85	3-00

Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics

Mail Order Department PE/2
P.O. Box 470, Manchester M60 4BU

BI-PRE-PAK

Bargains in Semi-Conductors, Components Modules and Equipment

Electronic Transistor Ignition £6.00

Complete kit p. & p. 11p

Now in kit form, we offer this "up-to-the-minute" electronic Ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

Extension Telephones

Ideal for toys 70p each P. & P. 25p.

New X Hatch Generator Mk.2

Essential for alignment of colour guns on all colour T.V. receivers. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3".

Ready built unit only **£9.95** Complete kit **£7.95**

(Includes p. & p. but no batteries)

LM 380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL80745.

This fantastic little 3watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00** ea complete with data and projects book

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can
TYPE "B" PNP Silicon, plastic encapsulation
TYPE "E" PNP Germanium AF or RF
TYPE "F" NPN Silicon plastic encapsulation
TYPE "G" NPN Silicon similar ZTX 300 range

8 RELAYS various types p & p 27p **£1.00** p

UHF TV Tuner Units

Brand new by a famous

manufacturer **£2.50**
Data supplied

B.P.P. CATALOGUE

20 pages packed with bargains. Size 11 1/2" x 8 1/2". Send large S.A.E. with 6p stamp.

Plastic Power Transistors

IN TWO RANGES



These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.
1-12 13-25 26-50
40 Watt 20p 18p 16p
90 Watt 24p 22p 20p

Range 2. VCE. Min. 40. HFE Min 40
1-12 13-25 26-50
40 Watt 30p 28p 26p
90 Watt 35p 33p 30p
Please state NPN or PNP on order.

High Speed Magnetic Counters 4 digit (non-reset) 24V or 48V 4 x 1 x 1 in 33p p & p 5p.

INTEGRATED CIRCUITS

We stock a large range of IC's at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 12p Wall Chart 18p

LOW COST DUEL IN LINE IC. SOCKETS

14 pin type at 15p each 1. Now new low profile 16 pin type at 17p each 1 type

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for IT TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Pak P.1. 50p

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. Please add 8% to total value of your order including postage. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 15p for postage & packing in U.K. Overseas—add £1., any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—50p You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

SPECIAL BPP PAKS Tested & Guaranteed

all at **50p** each



B79 4 IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic

B81 10 Reed Switches, 1" long 1/8" dia. Highspeed P.O. type

H35 100 Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked

H38 30 Short lead Transistors, NPN Silicon Planar types

H39 6 Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945

H41 2 BD131/BD132 Complementary Plastic Transistors

H85 4 40361 Type NPN Sil. transistors TO-5 can comp. to H66

H66 4 40362. Type PNP Sil. transistors TO-5 can comp. to H65

Special Bargain Paks (unmarked, untested)

all at **50p** each



B1 50 Germanium Transistors PNP, AF and RF

B66 150 Germanium Diodes Min. glass type

B83 200 Transistors, manufacturers' rejects, AF, RF, Sil. and Germ.

B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202

B86 100 Sil. Diodes sub. min. IN 914 and IN916 types

H20 20 BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts

H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can

H67 10 3819N Channel FET's plastic case type.

Sterling Sound Audio Modules

A new development by BI-PRE-PAK for enthusiasts who like building at keen prices.

SEE OUR SPECIAL AD. PAGE 164

A rev. counter for your car

The "Tacho Block" enables you to turn any 0.1 mA meter into an accurate linear rev. counter. The block is encapsulated and easily fitted into any car with conventional coil Ignition. Each **£1.00**

To BI-PRE-PAK 222 West Rd., Westcliff-on-Sea, Essex

Please send latest B.P.P. Catalogue. (I enclose large S.A.E. envelope with 6p stamp.)

Please send

.....

Enclosed £..... inc. V.A.T. cheque/money order (Write on more paper if necessary)

NAME

ADDRESS

BI-PRE-PAK LTD

Co Reg No 820919

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.



GIRO NO. 331 7056

C.W.O. only. P. & P. 10p on orders below £5
Discount: £10-10%, £20-15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS (Prices include Post and Packing).

10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.65 net
10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.35 net
25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.45 net
5E12 1W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £2.85 net
PLEASE NOTE: DUE TO CURRENT WORLD SHORTAGES THESE KITS MAY TEMPORARILY CONTAIN BOTH WATTAGE AND VALUE SUBSTITUTIONS.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3 1/2p. 0.068µF, 0.1µF, 4 1/2p. 0.15µF, 4 1/2p. 0.22µF, 5 1/2p. 0.33µF, 8p. 0.47µF, 9p. 0.68µF, 12p, 1µF, 13p. 1.5µF, 23p. 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 3 1/2p. 0.0047µF, 3p. 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3 1/2p. 0.047µF, 0.068µF, 0.1µF, 4 1/2p. 0.15µF, 6 1/2p. 0.22µF, 8 1/2p. 0.33µF, 12p. 0.47µF, 14p.
160V: 0.01µF, 0.015µF, 0.022µF, 3p. 0.047µF, 0.068µF, 3 1/2p. 0.1µF, 4 1/2p. 0.15µF, 5p. 0.22µF, 5 1/2p. 0.33µF, 6 1/2p. 0.47µF, 8 1/2p. 0.68µF, 12p. 1µF, 14p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.02, 0.033, 0.047, 2 1/2p each. 0.1, 30V, 41p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 10,000, 4 1/2p.

RESISTORS

CF—High Stab Carbon Film 5%, MF—High Stab Metal Film, 5%	W.	Type	Range	1-99	100-999	500-9999	1000+	Size mm
1/2	CF	22-1M	1	0.75	0.60	0.55	1000+	2.4 x 7.5
1/2	CF	22-2M2	1	0.75	0.60	0.55	1000+	3.9 x 10.5
1/2	CF	22-1M	1	0.75	0.60	0.55	1000+	5.5 x 16
1/2	MF	10-2M7	2	1.54	1.32	1.1	1000+	3 x 7
1/2	MF	10-2M2	2	1.43	1.21	0.99	1000+	4.2 x 10.8
1/2	MF	10-10M	3	1.98	1.81	1.65	1000+	6.6 x 18
2	MF	10-10M	4.5	3.52	3.08	2.75	1000+	8 x 17.5

For value mixing prices, please refer to our catalogue (price in pence each).
VALUES AVAILABLE—E12 Series only. Net prices above 100.

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 6p each
1K, 2K2, 4K7, 10K, etc. up to 1MΩ
SUB-MIN: 0.05W Vertical. 100Ω to 220KΩ 5p each

Wavechange Switches

1P, 4W; 1P, 12W; 2P, 2W; 2P, 4W; 2P, 6W; 3P, 3W; 4P, 2W; 3P, 4W; 4P, 3W, 30p

B. H. COMPONENT FACTORS LTD.

(P.E.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ
Tel.: Cheddington 668446 (Std. Code 0296)
CATALOGUE No. 3 20p.

Miniature Mullard Electrolytics

1.0µF 63V 6 1/2p	68µF 16V 6 1/2p
1.5µF 63V 6 1/2p	68µF 63V 12p
2.2µF 63V 6 1/2p	100µF 10V 6 1/2p
3.3µF 63V 6 1/2p	100µF 25V 6 1/2p
4.0µF 63V 6 1/2p	100µF 63V 14p
4.7µF 40V 6 1/2p	150µF 16V 6 1/2p
6.8µF 63V 6 1/2p	150µF 63V 15p
8.0µF 40V 6 1/2p	220µF 6.4V 6 1/2p
10µF 25V 6 1/2p	220µF 10V 6 1/2p
10µF 63V 6 1/2p	220µF 16V 8p
15µF 16V 6 1/2p	220µF 63V 21p
15µF 63V 6 1/2p	330µF 16V 12p
16µF 40V 6 1/2p	330µF 63V 25p
22µF 25V 6 1/2p	470µF 6.4V 9p
22µF 63V 6 1/2p	470µF 40V 20p
32µF 10V 6 1/2p	680µF 16V 15p
33µF 16V 6 1/2p	680µF 40V 25p
33µF 40V 6 1/2p	1000µF 16V 20p
32µF 63V 6 1/2p	1000µF 25V 25p
47µF 10V 6 1/2p	1500µF 6.4V 15p
47µF 25V 6 1/2p	1500µF 16V 25p
47µF 63V 6 1/2p	3300µF 6.4V 26p

VEROBOARD

0.1	0.15
2 1/2 x 5"	36p 36p
2 1/2 x 3 1/2"	33p 25p
3 1/2 x 5"	42p 46p
3 1/2 x 3 1/2"	36p 36p
2 1/2 x 1"	9p 9p
2 1/2 x 5" (Plain)	— 19p
2 1/2 x 3 1/2" (Plain)	— 16p
5 x 3 1/2" (Plain)	— 29p
Insertion tool	73p 73p
Track Cutter	56p 56p
Pins, Pkt. 50	22p 22p

TRANSISTORS

AC127	16 1/2p	BC212L	12p
AC128	22p	BC213L	12p
BC107	11p	BC214L	17p
BC108	12p	OC44	18p
BC109	13p	OC71	13p
BC148	12p	OC81	16p
BC149	12p	OC170	23p
BC182L	12p	T1543	33p
BC183L	12p	2N2926	11p
BC184L	13p	2N3702	11p

POTENTIOMETERS

Carbon Track 5KΩ to 2MΩ, log or lin. Single, 16 1/2p. Dual Gang 46p. Log Single with Slider Pots, 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001	6 1/2p
IN4002	7 1/2p
IN4003	9p
IN4004	9 1/2p
IN4005	12p
IN4006	14p
IN914	7p
IN916	7p
BA100	10p
OA5	42p
OA47	9p
OA81	11p
OA200	8p

PLUGS

DIN 2 Pin	12p
3 Pin	13p
5 Pin 180°	16p
Std. Jack	20p
2.5mm Jack	13p
Phono	6p

SOCKETS

DIN 2 Pin	10p
3 Pin	10p
5 Pin 180°	12p
Std. Jack	15p
2.5mm Jack	13p
Phono	6p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans

(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 300/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 90p, 2000/25, 30p, 2000/100, 95p, 2500/25, 38p, 2500/50, 62p, 3000/50, 80p, 5000/25, 66p, 5000/50, £1-10.
HI-VOLT: 8/350, 19p, 16/350, 22p, 32/350, 33p, 50/250, 20p, 100/100, 20p, 100/250, 30p, 4/450 14p, 16/450 23p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7 1/2p, 1µF, 9p.
500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7 1/2p, 0.5, 9p.
1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 28p.

STOP PRESS
OUR RETAIL SHOP
should now be open in
Leighton Buzzard
(59 North Street)

Screened Wire, Metre 6 1/2p
Twin Screened Wire, Metre 12p
Stereo Screened Wire, Metre 12p
Connecting Wire, All colours, Metre 2 1/2p
Neon Bulb, 90V Wire Ended 5 for 24p
Panel Neon, 240V, Red, Amber, Clear 16 1/2p

NEW KIT
5E12 1/2W Metal Film, 5 each value, 10Ω-1MΩ, total of 305. £3.25.



Phoenix Electronics (Portsmouth) Ltd.

139-141 Havant Road, Drayton, Portsmouth, Hants

PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

THIS MONTH'S BARGAIN OFFER!

74TTL Digital logic kit, 6 Gates, 2 flip-flops, decoder, decade counter, 8-bit shift register plus 5 D.I.L. sockets. Catalogue value £6.76 Bargain pack PEP/3A—£4.90


Please send your catalogue—free!

Name

Address

PEP/1A

NEW PE SCORPIO Mk. 2

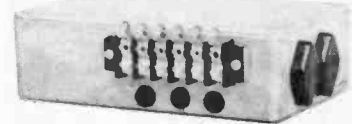

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- * Now with added R.F.I. suppression.
- * Fully machined and painted die-cast case with AMP termination connector block.
- * Custom wound transformer.
- * NOW AVAILABLE IN 6V, and 12V.
- * Suitable for all types of Cars, Boats, Go-Karts, etc.
- * Promotes easier starting—even under sub-zero conditions.
- * Improves acceleration, gives better high speed performance and quicker engine warm up.
- * Eliminates excessive contact breaker burning and pitting.
- * PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board.—Uses original plugs, points and coil.—No special parts or extras required. (Case size: 7 1/4in x 4 1/4in x 2in)

- * All components available separately.—S.A.E. with enquiries.
 - * Construction manual available separately 25p.
- Cost £11.78 incl. carr. and ins. or ready built and tested £14.49
Conversion kit from Mk. 1 to Mk. 2. For constructors already possessing Mk. 1 Kits.—Miniature P.C. assembly £1 incl. carr. and ins. With full conversion instructions.

PLEASE ADD VAT TO ALL U.K. ORDERS

(Carriage at cost outside U.K.—Export enquiries welcome.)

DABAR ELECTRONIC PRODUCTS


98 LICHFIELD STREET

WALSALL, Staffs WS1 1UZ



FREE!

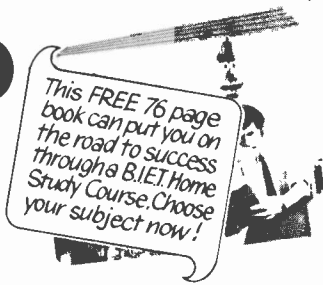Over 150 ways to engineer a better future



HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained *thousands* of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course."—Student D.I.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects."—Student J.A.O., Dublin.
 "My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold."—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters, and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to:

ALDERMASTON COLLEGE

Dept. TPE02, Reading RG7 4PF

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<p>MECHANICAL Society of Engineers— A.M.S.E. (Mech.) <input type="checkbox"/> Institute of Engineers & Technicians (A.M.I.F.) <input type="checkbox"/> CITY & GUILDS Gen. Mech. Eng. <input type="checkbox"/> Maintenance Eng. <input type="checkbox"/> Welding <input type="checkbox"/> Gen. Diesel Eng. <input type="checkbox"/> Sheet Metal Work <input type="checkbox"/> Eng. Inspection <input type="checkbox"/> Eng. Metallurgy <input type="checkbox"/></p> <p>ELECTRICAL & ELECTRONIC CITY & GUILDS Gen. Electrical Engineering <input type="checkbox"/> Electrical Installations <input type="checkbox"/> Electrical Maths <input type="checkbox"/> Computer Electronics <input type="checkbox"/> Electronic Eng. <input type="checkbox"/> Practical Radio & Electronics (with kit) <input type="checkbox"/></p> <p>MANAGEMENT & PRODUCTION Institute of Cost & Management Accntis. <input type="checkbox"/> Computer Programming <input type="checkbox"/> Works Management <input type="checkbox"/> Work Study <input type="checkbox"/> Gen. Production Eng. <input type="checkbox"/> Estimating & Planning <input type="checkbox"/> Storekeeping <input type="checkbox"/> Management Skills <input type="checkbox"/> Quality Control <input type="checkbox"/></p>	<p>DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) <input type="checkbox"/> General Draughtsmanship <input type="checkbox"/> Elec. Draughtsmanship <input type="checkbox"/> Architectural Draughtsmanship <input type="checkbox"/> Technical Drawing <input type="checkbox"/></p> <p>RADIO & TELECOMMUNICATIONS CITY & GUILDS Telecoms <input type="checkbox"/> Gen. Radio & TV Eng. <input type="checkbox"/> Radio Amateurs Exam <input type="checkbox"/> Radio Servicing <input type="checkbox"/></p> <p>AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I.I. <input type="checkbox"/> CITY & GUILDS Auto Eng. <input type="checkbox"/> Gen. Auto Eng. <input type="checkbox"/> Motor Mechanics <input type="checkbox"/> Auto Diesel Eng. <input type="checkbox"/> Garage Management <input type="checkbox"/> A.F.C. Aero Engineering <input type="checkbox"/> Exams <input type="checkbox"/> Gen. Aero Eng. <input type="checkbox"/></p> <p>CONSTRUCTIONAL Institute of Building I.I.O.B. <input type="checkbox"/> A.B.T. Clerk of Works <input type="checkbox"/></p>	<p>Construction Surveyors Institute I.C.S.I. <input type="checkbox"/> CITY & GUILDS General Building (all branches) <input type="checkbox"/> Heating & Vent. Inst. Clerk of Works <input type="checkbox"/> Site Surveying <input type="checkbox"/> Health Engineering <input type="checkbox"/> Road Construction <input type="checkbox"/> Quantities Estimates <input type="checkbox"/> Hydraulics <input type="checkbox"/> Structural Eng. <input type="checkbox"/></p> <p>GENERAL Agricultural Eng. <input type="checkbox"/> Council of Eng. Institutions <input type="checkbox"/> Farm Science <input type="checkbox"/> Plastics <input type="checkbox"/></p> <p><i>Supplementary courses for Nat. Certificates.</i></p> <p>G.C.E. — choose from 58 'O' & 'A' level subjects.</p> <p><i>Coaching for many exams, including C & G</i></p>
--	--	---

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, Dept. TPE02, Reading RG7 4PF TPE02

NAME
 Block Capitals Please

ADDRESS

POST CODE

OTHER SUBJECTS

AGE


Accredited by C.A.C.C. Member of A.B.C.C.

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (Asia) Ltd., South Africa—Central News Agency Ltd.
 Publisher's Subscription Rate including postage for one year: Inland £3.25 Overseas £4.10 International Giro facilities Account No. 5122007. Please state reason for payment message to payee.
 Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of trade at more than the recommended selling price shown on the cover, excluding Fire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

1301 LOVEFACE

Henry's

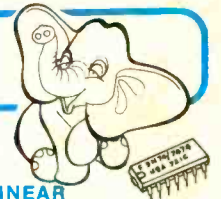LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES- MEAN LESS VAT.



You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board. Gardners low field transformer. 6-ICs, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2" x 2 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit.



£31·00 (GB post paid) (also built and tested £37·50)



(also built and tested £24·95)

STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8 1/2" x 2 1/2" x 6 1/2". Complete kit with teak sleeve

£21·00 (GB post paid)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

TRANSISTORISED MODULES

Tuners—Power Suppliers—Amplifiers

AMPLIFIERS (all single channel unless stated)

4-300	9 volt 300mW	1-75
2004	9 volt 250mW	2-70
104	9 volt 1 watt	3-10
304	9 volt 3 watt	3-95
555	12 volt 3 watt	4-10
555S2	12 volt 1 1/2 + 1 1/2 watt	5-95
E1208	12 volt 5 watt	5-10
506	24 volt 10 watt	4-95
410	28 volt 10 watt	4-95
620	45 volt 30 watt	9-95
Z40	30/35 volt 15 watt	5-45
260	45/50 volt 25 watt	6-95
SA6817	24 volt 6 - 6	10-20

Amplifiers with controls

E1210	12 volt 2 1/2 + 2 1/2 watts 8 ohms	8-25
R500	Mains 5 watts 4-16 ohms	6-30
SAC 14	Mains 7 + 7 watts 8 ohms	11-75
SAC30	Mains 15 + 15 watts 8 ohms	14-95
CAO38	9 volt 1 1/2 + 1 1/2 watts 8 ohms	6-95
CA068	12 volt 3 + 3 watts 8 ohms	10-50

FM MODULES

Mullard LP 1186 FM tuner (front end with data 10 7 MHz O/P)	4-85
Mullard LP 1185 10 7 MHz IF unit with data	4-50
Gorlier Permeability FM tuner (front end) 10-7 MHz O/P	4-20

FM AND AM TUNERS AND DECODERS

FM5231 (TU2) 6 volt FM tuner	7-95
TU3 12 volt version (FM use with Decoder)	7-95
SD4912 Stereo Decoder for TU3 12 volt	11-95
SP62H 6 volt Stereo FM tuner	4-80
A1007 9 volt MW-AM tuner	11-95
Sinclair 12 45 volt FM tuner stereo recorder for above	17-45
A1018 9 volt FM tuner in cabinet	13-95
A1005M (S) 9-12 volt Stereo decoder FM for above	7-50
106Z 12 volt Stereo decoder general purpose	6-50

PREAMPLIFIERS

Sinclair Stereo 60 Preamplifier	6-75
E1300 Car/Tape Mic inputs 9 volt	2-85
E1310 Stereo 3-30 mV mag cart 9 volt	4-75
FF3 Stereo 3 mV tape head 9 volt	4-95
3042 Stereo 5-20 mV Mag cart mains	5-95
EQ25 Mono 3-250 mV Tape/Cart/Play 9 volt	5-95

POWER SUPPLIES MAINS INPUT

(*chassis-rest cased) 470C 6.7V/9V 300MA with ad rs	2-25
P500 9V 500 MA	3-20
HC244R 3.6/7.9V, 400 MA stabilised	5-50
*P11 24V +A 3-30	3-30
*P15 28V +A	3-30
*P108 12V 1A 4-70	7-80
*P1081 45V 0.9A	7-80
P12 4-12V, 0-4-1A	7-15
SE101A 3.6/9/12V 1A stabilised	12-75
P1076 3.4/6/7.9/12V, 3A	4-20
SE800A 1-15 VOLT 0-3A stabilised	17-50

EMI SPEAKERS SPECIAL PURCHASE



13in x 8in chassis speakers (Carr/packing 36p each or 50p pr.)

- *150T 10 watts 8 ohms twin cone E2-20
- *450 10 watts 4, 8, 15 ohm with twin tweeters and crossover £3-85 each
- EW 15 watt 8 ohm with tweeter £5-25
- 350 20 watt 8, 15 ohm with tweeter £7-80 each.
- * Polished wood cabinet £4-80 carr., etc. 35p each or 50p pair.

UHF TV TUNERS

625 line receiver UHF transistorised tuners FM UK operation. Brand new (Packaging 25p each)

- TYPE C variable tuning £2-50
- TYPE B 4-button, push-button (adjustable) £3-50

PA DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc.

FREE stock lists (Ref No. 18) on request. CALL IN AND SEE FOR YOURSELF at HENRY'S DISCO CENTRE, 309 EDGWARE ROAD, TEL. 01-723 6963

1250-watt Light Dimmer

£3-50 pp 20p MANUFACTURED BY ULTRA LTD. SUPPLIED WITH PLATE KNOB AND INSTRUCTIONS.

Radionic Kits

X20-20 Projects	£6-20
X40-40 Projects	£13-65
X40A Add-on	£11-35

Denshi Board Kits

SR-2A-16 Projects	£7-70
SR-3A-100 Projects	£14-95
ST-4S-4S Projects	£10-50
ST-100-100 Projects	£13-20

Turner Kits

10 in 1-10 Projects	£6-80
50 in 1-50 Projects	£15-45
150 in 1-150 Projects	£23-65

TEST EQUIPMENT MULTIMETERS

U4324 20kΩ/V with case	9-25	£ p
U435 20kΩ/V with steel case	8-75	£ p
U4313 20kΩ/V with steel case	12-50	£ p
U4317 20kΩ/V with steel case	16-50	£ p
U4341 33kΩ/V plus transistor	10-50	£ p
U4323 20kΩ/V with 1kHz OSC with case	7-70	£ p
IT1-2 20kΩ/V slim type	5-95	£ p
TLH33D (L33DX) 2kΩ/V Robust	7-50	£ p
TP55N 20kΩ/V (Case E2)	8-25	£ p
TPW05 2kΩ/V	6-25	£ p
TW50K 50kΩ/V	10-00	£ p
EP10KN 10kΩ/V	9-95	£ p
SFN7413N	0-36	£ p
SFN7414N	0-72	£ p
SFN7415N	0-36	£ p
SFN7416N	0-36	£ p
SFN7417N	0-36	£ p
SFN7418N	0-36	£ p
SFN7419N	0-36	£ p
SFN7420N	0-36	£ p
SFN7421N	0-36	£ p
SFN7422N	0-36	£ p
SFN7423N	0-36	£ p
SFN7424N	0-36	£ p
SFN7425N	0-36	£ p
SFN7426N	0-36	£ p
SFN7427N	0-36	£ p
SFN7428N	0-40	£ p
SFN7429N	0-16	£ p
SFN7430N	0-37	£ p
SFN7431N	0-37	£ p
SFN7432N	0-37	£ p
SFN7433N	0-37	£ p
SFN7434N	0-37	£ p
SFN7435N	0-37	£ p
SFN7436N	0-37	£ p
SFN7437N	0-37	£ p
SFN7438N	0-37	£ p
SFN7439N	0-22	£ p
SFN7440N	0-37	£ p
SFN7441N	0-37	£ p
SFN7442N	0-79	£ p
SFN7443N	1-27	£ p
SFN7444N	1-27	£ p
SFN7445N	1-89	£ p
SFN7446N	1-89	£ p
SFN7447A	1-60	£ p
SFN7448N	1-27	£ p
SFN7449N	1-16	£ p
SFN7450N	0-16	£ p
SFN7451N	0-16	£ p
SFN7452N	0-16	£ p
SFN7453N	0-16	£ p
SFN7454N	0-16	£ p
SFN7455N	0-16	£ p
SFN7456N	0-38	£ p
SFN7457N	0-38	£ p
SFN7458N	0-41	£ p
SFN7459N	0-41	£ p
SFN7460N	0-59	£ p
SFN7461N	0-59	£ p
SFN7462N	0-59	£ p
SFN7463N	0-59	£ p
SFN7464N	0-59	£ p
SFN7465N	0-59	£ p
SFN7466N	0-59	£ p
SFN7467N	0-59	£ p
SFN7468N	0-59	£ p
SFN7469N	0-59	£ p
SFN7470N	0-59	£ p
SFN7471N	0-59	£ p
SFN7472N	0-59	£ p
SFN7473N	0-59	£ p
SFN7474N	0-59	£ p
SFN7475N	0-59	£ p
SFN7476N	0-59	£ p
SFN7477N	0-59	£ p
SFN7478N	0-59	£ p
SFN7479N	0-59	£ p
SFN7480N	0-59	£ p
SFN7481N	0-59	£ p
SFN7482N	0-59	£ p
SFN7483N	0-59	£ p
SFN7484N	0-59	£ p

NEW REVOLUTIONARY SUPERTESTER 690R

690R Multi-tester
 †TK40 AC Multivoltmeter
 †TK15 Grid dip meter 440kHz-28MHz
 †TK65 2B Range valve volt-meter
 †450 10 watts 4, 8, 15 ohm with twin tweeters and crossover £3-85 each
 †TK22Z AF Generator 20Hz-200kHz
 †TK205 Deluxe meter 1-300MHz
 †TK22Z AF Generator 20Hz-200kHz
 †HMS30 In circuit transistor tester
 †C3025 Deluxe meter 1-300MHz
 †TT145 Compact transistor tester
 †G3-36 R C osc. 20Hz-200kHz
 *C3042 SWR meter
 *SE350A Deluxe signal tracer
 *SC40 Mini-All in one tester
 C1-5 Scope 500,000kHz (carr. £1)
 *C3043 S CH F/A meter 1-300MHz
 Resistance sub box { Post etc 2.40
 Capacitor { 20p 2.10
 2A variable transformers (carr. £1)
 Radio activity counter 0-10r (carr. £1)
 Mains unit for above (carr. 50p) 3-75

TAPE HEADS

Marnot XRSP17; Track High	2-50
Marnot XRSP18; Track Med.	3-50
Marnot XRSP36; Track Med.	5-00
Marnot XRSP63; Track High	1-75
Marnot Erase Heads for XRSP 17/18/36 (XES11)	75
Marnot BX1ZE 343; Track Erase	75
R RPI Record/Play; Track	45
H/RP Single Track Rec/Play	35
Bogen Type UL290 Erase	1-50
Miniature Stereo Cassette Rec/Play	2-25

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load 30volt max. d.c. operation, complete with date Price £1-50 each or 2 for £2-85. Printed Circuit Panels 50p.

CALCULATORS

Sinclair Cambridge Kit, £13-50
 Sinclair Cambridge (BUILT), £17-50
 Sinclair Memory £22-50
 Sinclair Scientific, £25-95

INTEGRATED CIRCUITS

74 SERIES AND LINEAR

EXTRA DISCOUNTS
 Semiconductors—Any one type or mixed SN74 Series IC: 12—extra 10%; 25—extra 15%; 100—extra 20%.

SFN7400N	0-16	SFN7485N	1-63	SFN74191N	2-00
SFN7401N	0-16	SFN7486N	0-47	SFN74192N	2-00
SFN7402N	0-16	SFN7489N	0-37	SFN74193N	2-00
SFN7403N	0-16	SFN7490N	0-70	CA3014	1-80
SFN7404N	0-16	SFN7491N	1-00	CA3016	1-02
SFN7405N	0-16	SFN7492N	0-70	CA3019	1-12
SFN7406N	0-42	SFN7493N	0-70	CA3020	1-80
SFN7407N	0-42	SFN7494N	0-80	CA3022	1-73
SFN7408N	0-28	SFN7495N	0-80	CA3028A	1-03
SFN7409N	0-28	SFN7496N	0-95	CA3038	1-08
SFN7410N	0-16	SFN7497N	1-87	CA3046	1-03
SFN7411N	0-25	SFN74100N	0-89	CA3048	1-03
SFN7412N	0-30	SFN74104A	0-58	CA3051	1-03
SFN7413N	0-36	SFN74105N	0-53	CA3052	1-03
SFN7414N	0-72	SFN74107N	0-45	CA3059	1-82
SFN7415N	0-36	SFN74110N	0-58	CA3062	1-73
SFN7416N	0-36	SFN74111N	0-88	CA3068A	1-03
SFN7417N	0-36	SFN74116N	1-89	CA3038	1-08
SFN7418N	0-36	SFN74118N	0-89	CA3046	1-03
SFN7419N	0-36	SFN74119N	0-68	CA3092	1-03
SFN7420N	0-37	SFN74120N	0-85	CA3075	1-75
SFN7421N	0-37	SFN74121N	0-50	CA3081	1-80
SFN7422N	0-37	SFN74122N	0-50	CA3089E	2-94
SFN7423N	0-40	SFN74123N	1-00	CA3099	5-40
SFN7424N	0-16	SFN74124N	1-00	Signetics	
SFN7425N	0-16	SFN74125N	0-82	NE555	0-85
SFN7426N	0-32	SFN74126N	0-82	NE560B	5-00
SFN7427N	0-37	SFN74127N	1-00	NE561B	5-00
SFN7428N	0-16	SFN74128N	1-00	NE562B	5-00
SFN7429N	0-37	SFN74129N	0-82	NE567B	3-50
SFN7430N	0-37	SFN74130N	0-95	Motorola	
SFN7431N	0-37	SFN74131N	1-00	CA3014	1-80
SFN7432N	0-37	SFN74132N	1-00	MC1304P	1-79
SFN7433N	0-37	SFN74133N	1-00	MC1310P	2-91
SFN7434N	0-37	SFN74134N	1-00	MC1498CF	0-77
SFN7435N	0-37	SFN74135N	1-00	MC1700C	0-80
SFN7436N	0-37	SFN74136N	1-00	MFC4000P	0-45
SFN7437N	0-37	SFN74137N	1-00	MFC4010P	0-55
SFN7438N	0-37	SFN74138N	1-00	MFC6040P	1-00
SFN7439N	0-22	SFN74139N	1-00	TBA800	1-50
SFN7440N	0-37	SFN74140N	1-00	SN76003N	1-50
SFN7441N	0-37	SFN74141N	1-00	SN72741P	0-80
SFN7442N	0-79	SFN74142N	3-50	MC17248P	0-80
SFN7443N	1-27	SFN74143N	1-00	702C	0-75
SFN7444N	1-27	SFN74144N	1-00	709C	0-39
SFN7445N	1-89	SFN74145N	1-00	723C	0-90
SFN7446N	1-89	SFN74146N	1-00	726C	0-45
SFN7447A	1-60	SFN74147A	1-00	741C	0-50
SFN7448N	1-27	SFN74148N	1-38	747C	1-00
SFN7449N	1-16	SFN74149N	1-38	748C	0-61
SFN7450N	0-16	SFN74150N	1-38	TA093K	0-45
SFN7451N	0-16	SFN74151N	1-76	TA960	1-75
SFN7452N	0-16	SFN74152N	1-76	Sinclair	
SFN7453N	0-16	SFN74153N	1-76	IC12, 6W amp	2-20
SFN7454N	0-16	SFN74154N	3-50		
SFN7455N	0-16	SFN74155N	2-00		
SFN7456N	0-38	SFN74156N	1-57		
SFN7457N	0-41	S			