

PRACTICAL

ELECTRONICS

APRIL 1975

30p

... FULL EXPOSURE!!

with the
**PE
COMPENSATED
PHOTO
TIMER**



other projects include:

- MUSICAL DOORBELL
- ESP DETECTOR

Part ONE
of a NEW SERIES
TRANSDUCERS

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN - PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loud-speaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 31" Loudspeaker ● Earpiece ● Mica Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 55p (free with parts)

TOTAL BUILDING COSTS

£7-23 P.P. & Ins. 44p
(Overseas Seamail P. & P. £2-35)
(+8% VAT 57p)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors, 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9½in x 7in x 2½in approx. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6-95** P.P. & Ins. 44p
(Overseas Seamail P. & P. £2-35)
(+8% VAT 55p)

POCKET FIVE

NOW WITH 3" LOUDSPEAKER


3 Tunable wavebands, MW/LW and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5½in x 1½in x 3½in approx. Plans and parts price list free with parts.

Total Building Costs

£2-50

(+8% VAT 20p) P.P. & Ins. 36p

(Overseas Seamail P. & P. £1-70)

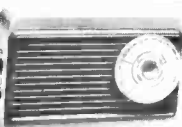

TRANSONA FIVE NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list free with parts.

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW, and LW. Telescopic aerial for short waves, 3in speaker, 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

TOTAL BUILDING COSTS

£4-48 P.P. & Ins. 40p

(Overseas Seamail P. & P. £2)

(+8% VAT 36p)

ROAMER SIX

CASE AND LOOKS AS TRANS EIGHT
6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND

FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves, 3in speaker, 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Plans and parts price list free with parts.

TOTAL BUILDING COSTS

£3-98 P.P. & Ins. 40p

(Overseas Seamail P. & P. £2-00)

(+8% VAT 32p)

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes, MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9in x 4½in x 2½in approx. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£2-95** P.P. & Ins. 36p
(Overseas Seamail P. & P. £1-70)
(+8% VAT 23p)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull Output. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£3-60** P.P. & Ins. 36p
(Overseas Seamail P. & P. £1-70)
(+8% VAT 29p)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves, 3" Loudspeaker. Parts price list and easy build plans free with parts.


TOTAL BUILDING COSTS **£4-08** P.P. & Ins. 38p
(Overseas Seamail P. & P. £2-00)
(+8% VAT 32p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch, 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

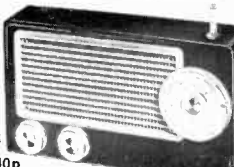TOTAL BUILDING COSTS **£6-98** P.P. & Ins. 47p
(Overseas Seamail P. & P. £2-50)
(+8% VAT 59p)



ROAMER TEN Mk. II

WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVE BANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 6 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

TOTAL BUILDING COSTS **£9-50** P.P. & Ins. 52p
(Overseas Seamail P. & P. £2-50)
(+8% VAT 76p)

Now with free earpiece and switched socket.



TOTAL BUILDING COSTS **£9-50** P.P. & Ins. 52p
(Overseas Seamail P. & P. £2-50)
(+8% VAT 76p)

EDU-KIT

Build Radios Amplifiers, etc., from easy stage, diagrams.



Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 3in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£5-50** P.P. & Ins. 40p
(Overseas Seamail P. & P. £2-35)
(+8% VAT 44p)

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52367 Reg. No. 788372

I enclose £ _____ for _____
Name _____
Address _____

PRACTICAL ELECTRONICS

VOLUME 11 No. 4 APRIL 1975

CONSTRUCTIONAL PROJECTS

- P.E. COMPENSATED PHOTO TIMER** *by K. Lenton-Smith* 292
For accurate colour and monochrome printing
- ESP DETECTOR** *by R. J. Johnson* 312
An aid to parapsychical exploration
- LOGIC INDICATOR PROBE** *by W. H. Davies* 318
Logic checking with visual readout
- MUSICAL DOORBELL** *by C. J. Allen* 328
Welcome your caller with "Beethoven's 9th"

GENERAL FEATURES

- TRANSDUCERS—1** *by P. R. Allcock* 300
An introduction to transducers, their operation, types and uses
- INGENUITY UNLIMITED** 320
Voltage Controlled Dimmer
- CEEFAX and ORACLE—2** *by J. Smith* 322
This concluding article examines some of the more detailed provisions of the system

NEWS AND COMMENT

- EDITORIAL—Vital Links** 291
- NEWS BRIEFS**
New Loudspeaker—DICE Conversion—Portable Heart Monitor—Another Component Source 299, 333
- SPACEWATCH** *by Frank W. Hyde* 307
The Potato Moon—Helios
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith* 308
Electronics and Music
- P.E. KIT REVIEW** 311
Building the Sinclair Scientific Calculator
- POINTS ARISING** 333
Marine Speedometer—P.E. Minisonic—Gas Detectors
- MARKET PLACE** 335
Digital Tutor, Pocket Multimeter and Professional Microphone
- INDUSTRY NOTEBOOK** *by Nexus* 336
What's happening inside industry
- PATENTS REVIEW** 339
Thought provoking ideas on file at the British Patents Office

Our May issue will be published on Friday, April 11, 1975


© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3.85, Overseas £4.70. USA and Canada \$13.00. International Giro facilities Account No. 5122007. State reason for payment, "message to payee".

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- | | | |
|--|---------------|---|
| SA35 £5-45 | Carriage free | <ul style="list-style-type: none"> ★ 25Hz-25kHz ★ 0.2% distortion ★ Noise—80dB ★ 500mV into 20K ★ 4-16 ohms ★ Simple wiring ★ Short and open circuit proof ★ Continuously rated ★ Top-grade components |
| 35W RMS 25-50V
7 transistors, 7 diodes | | |
| SA50 £6.90 | Carriage free | |
| 50W RMS 25-65V
7 transistors, 7 diodes | | |
| SA100 £12-50 | Carriage free | |
| 100W RMS 45-70V
10 transistors, 10 diodes | | |
- 120 watt module complete with built-in supply—extra heavy duty £22-50** Carr. 60p

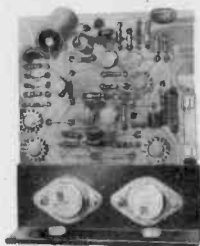

THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED			
PU45	Suits 2 SA35 or 1 SA50 (4 ohm)	£5-45	Carriage 30p
PU70	Suits 2 SA50 or 2 SA100 (8 ohm)	£8-45	Carriage 40p
STABILISED			
PS45	Suits 2 SA35 or 2 SA50 (4 ohm)	£4-45	Carriage free
MT45	Transformer for above	£3-50	Carriage 30p
PS70	Suits 2 SA100	£5-45	Carriage free
MT70	Transformer for above	£4-90	Carriage 40p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £22-50

This well tried Pre-Amp mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, hi/phone select, vol, Mains. Size 17½in x 3in x 4in deep. Carr. 30p



DISCO MODULE £9-50

Thousands sold of this extremely popular mono Pre-Amp. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: hi/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep. Carr. 20p



3-CHANNEL SOUND-LITE £22-50

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford! Carr. 30p




SINGLE CHANNEL VERSION £7-50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add 8% VAT to all orders


MULTI-PURPOSE MIXERS

M4HL £19-50 Carr. 50p
M6HL £29-50 Carr. 50p
Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

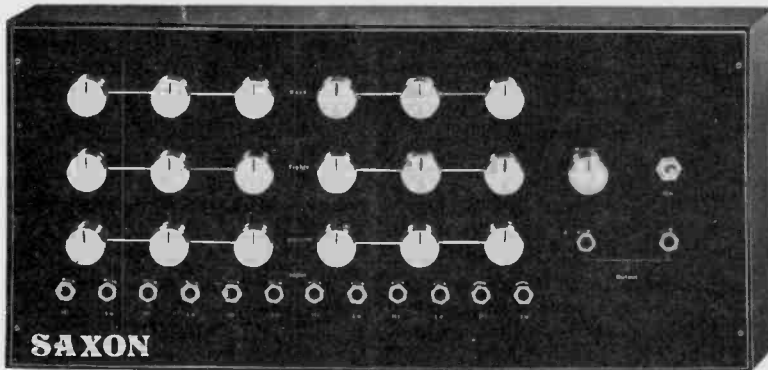

VA30 CHANNEL MODULE £3-50 Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)

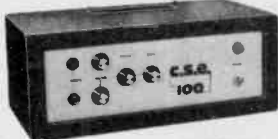SAXON CSE 100 £39-90 Carr. free
100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vynide case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29-50 Carr. free

NEW!!

SAXON MULTIMIX 100 £57 CARR. FREE

100W RMS SLIDER controls PLUS master slider. Wide range bass and treble controls—fantastic value. Ideal for complete Disco's, Groups, Clubs, etc.

SAXON MULTIMIX 50 EXACTLY AS ABOVE £45 BUT 50W RMS

CALLERS AND MAIL ORDER:
SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m. - 5 p.m. — LUNCH 12.30 - 1.30 p.m. MAIL ORDER DESK: 10 a.m. - 3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

SEND 10p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.
TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.
Please include S.A.E. with all enquiries.
VAT at 8% must be added to all orders including carriage charges.

Europe's Largest Hi-Fi Retailers



give you the greatest choice

TMK 200 MULTIMETER KIT

Build yourself a quality 20000 opv. multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test prods and instructions. Ranges: 0/0.6/6/30/120/600/1200V DC. 0/6/30/120/600/1200V AC. Current: 0/0.6/6/60/600mA. Resistance: 0/10/100k/1M Meg ohms. Decibels: -20 to +63dB. Size: 90 x 150 x 35mm.



OUR PRICE £7.95 P & P 30p.

AUDIOTRONIC MODEL ATM1

Top value 1,000 opv pocket multimeter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0/1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £3.25 P & P 15p

MODEL C1092

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0/3/15/150/300/1200V AC. (2500 opv). 0/6/30/300/600V DC. (5000 opv). 0/30/300/3000/1000V AC. Resistance: 0/100/1000/100k. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £3.95 P & P 20p

HIOKI 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0/50/500/250mA. 0/20k/2 Megohms.



OUR PRICE £5.97 P & P 30p

MODEL C7202EN

20,000 opv. DC. 10,000 opv. AC. Mirror scale. Ranges: 6/25/50/250/500/1000/2500V DC. 10/50/100/500/1000V AC. DC Resistance: 10/100/1000/100k/1M Meg. Current: 50mA. 2.5mA/250mA. -20 to +68dB.



OUR PRICE £6.95 P & P 30p

MODEL PL436

20,000 opv DC. 8000 opv AC. Mirror scale. Ranges: 6/3/12/30/120/600V DC. 3/30/120/600V AC. Current: 50/600mA/6/600mA. 10/100k/1 Meg/10 Meg Ohm. -20 to 46dB.



OUR PRICE £6.97 P & P 30p

HIOKI 730X


30,000 opv. Overload protection. Ranges: 6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 60/μA. 30mA/300mA. 2K/200K. 2 Meg Ohm. 10 to 63dB.



OUR PRICE £7.50 P & P 30p.

U4323 MULTIMETER

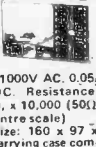20,000 opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: 10/100/1000/100k/1M Meg. Supplied in carrying case complete with test leads.



OUR PRICE £8.00 P & P 30p

U435 MULTIMETER

20,000 opv. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. Current: 50μA/1/5/25/100mA/0.5/2.5A DC. 5/25/100mA. 0.5/2.5A AC. Resistance: 0/3/30/300 ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.



OUR PRICE £8.75 P & P 30p

MODEL C7208FM

30,000 opv DC. 15,000 opv AC. Ranges: 6/3/15/60/300/600/1200V DC. 6/30/120/600/1200V AC. DC Resistance: 10/100/1000/100k/1M Meg. DC Current 300A. 3/30/800mA. -20 to +63dB.



OUR PRICE £8.95 P & P 30p

U4324 MULTIMETER


High sensitivity, overload protected. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



OUR PRICE £9.85 P & P 30p

U91 Clamp VOLT METER

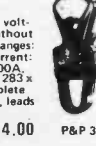For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 263 x 94 x 35mm. Complete with carrying case, leads and fuses.



OUR PRICE £14.00 P & P 30p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 667 opv. Ranges: 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/0.300A/1.5/15/150/600mA/1.5/6A. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £10.75 P & P 50p

HIOKI 750X VOLT-OHM-MILLIAMETER

43 ranges, mirror scale. Ranges: 0-0.3/0.6/1.2/3/6/15/30/60/150/300/600/1,200V DC. 0-3/6/15/30/60/120/300/600/1,200V AC. Current: 0-30/60/300mA/6/12A. Resistance: 0-3/30k/3/30k ohms. Decibels: 10 to +17dB. Output: 0-3/6/15/30/60/120/300V. Accuracy ±3% DC. ±4% AC. Sensitivity: 50,000 opv DC. 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.



OUR PRICE £11.95 P & P 40p

TMK MODEL TW50K

46 ranges, mirror scale. 50kV/V DC. 50kV/V AC. DC Volts: 0/25/125/250/500/1000. AC Volts: 1.5/3/15/30/250/500/1000. DC current: 25/50mA/2.5/5/25/50/250/500mA/5/10A. Resistance: 10k/100k/1 Meg/10 Meg ohms. -20 to +81.5dB.



OUR PRICE £12.50 P & P 20p

MODEL C7080EN


Giant 6" mirror scale. 20,000 opv. 0/25/125/500/1000/5000V AC. 0/50/500/1000/5000V DC. 0/25/100/500/250/1000/5000V AC. 0/50/500/1000/5000V DC. 20 Meg. -20 to +50dB.



OUR PRICE £19.95 P & P 35p

MODEL 500

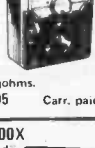
30,000 opv with overload protection. Mirror scale. Ranges: 0/0.6/1.2/1.5/3/6/12/30/60/120/300/600/1200V DC. 0/0.5/2.5/10/25/100/500/1000V AC. 0/50/500/500mA. 12A DC. 0/60k/6 meg/60 megohms.



OUR PRICE £13.95 Carr. paid

HIOKI MODEL 700X

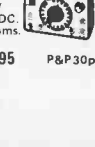100,000 opv. Overload protection. Mirror scale. Ranges: 0/3/6/12/15/30/60/120/300/600/1200V DC. 0/1.5/3/6/12/30/60/150/300/600/1200V AC. 0/15/30/300/600/600mA/6/12A DC. 1k/20k/2M/20M Ohms. -20 to +63dB.



OUR PRICE £14.95 P & P 30p

MODEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/100A/6/60/300mA. 12 Amp. 0/2K/200K/2M/200 Meg Ohm. -20 to 17dB.



OUR PRICE £17.50 P & P 30p.

KAMODEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: -0/25/125/50/100/1000V DC. 0/2.5/10/50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms



OUR PRICE £21.00 P & P 40p

KAMODEN 360 MULTIMETER


High sensitivity. DC 100ohm/V. AC 10k ohm/V. 5" mirror scale, overload protected. Ranges: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100M ohms. Decibels: -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc.



OUR PRICE £17.50 P & P 40p

Model HT1008A MULTIMETER

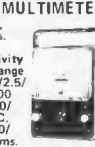Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV/V. Polarity change switch. Ranges: 0.5/2.5/10/50/250/1000V DC. 2.5/10/50/250/1000V AC. DC resistance: 0-20/200k/2/20 Meg. Ohms. DC current: 10/250uA/2.5/25/250 mA/100V AC current: 0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.



OUR PRICE £17.50 P & P 40p

370WR MULTIMETER


Features AC current ranges. 20,000 opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.



OUR PRICE £19.95 P & P 30p

U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer, 86mm mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.

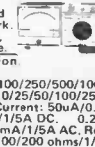

OUR PRICE £17.00 P & P 40p

KAMODEN 72.200 Multitester

High sensitivity tester. 200,000 opv. Overload protected. Mirror scale. Ranges: 0/0.6/3/30/120/600/1200V DC. 0/3/12/60/120/300/600/1200V AC. 0/6uA/1.2mA/120mA/600mA/12A DC. 0/12 AC. -20 to +63dB. 0/2k/200k/2 Meg/20 Megohms.



OUR PRICE £22.50 P & P 30p

MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter scale. Protection. Ranges: 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V AC. 0/30uA/6/60/300mA. 12 Amp. 0/10k/1m/100M Ohm. -20 to 17dB.



OUR PRICE £12.50 P & P 30p.

TMK MODEL 117 FET ELECTRONIC VOLTMETER

Battery operated. 11 Meg input, 26 ranges. Large 4 1/2" mirror scale. Size: 149 x 117 x 60mm. 0.3-12000V DC. 3-300V RMS AC. 8-800V P.P. DC current 0.12-12mA. Resistance up to 2000M Ohms. Decibels: -20 to +51dB. Supplied complete with leads and instructions.



OUR PRICE £18.50 P & P 20p

TMK 100K LAB TESTER

100,000 opv. 6 1/2" scale. Buzzer short circuit check. Sensitivity 100/500 opv DC. 5k/V AC. DC Volts: 0.5/2.5/10/50/250/1000V AC. 3/100/250/500/1000V DC. Current 10/100uA/100/2.5/10A. Resistance: 1k/10k/100k/1 Meg ohms. Decibels: -10 to +49dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.



OUR PRICE £19.95 P & P 30p

LBA TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.



OUR PRICE £4.50 P & P 20p

KAMODEN T335 TRANSISTOR TESTER


High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP, diodes, transistors, etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.



OUR PRICE £17.50 P & P 40p

U4341 Multimeter & Transistor Tester

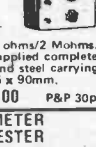
27 ranges. 16,700 opv. Overload protected. Ranges: 0.5/2.5/10/30/60/150/300/900V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.05/0.6/6/60/600mA DC. 0/3/30/300mA AC. Resistance: 0.5/25/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.



OUR PRICE £11.00 P & P 30p

S100TR MULTIMETER TRANSISTOR TESTER

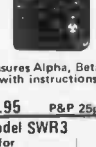100,000 opv. Mirror scale. Overload protection. Ranges: 0/0.12/0.6/3/12/60/300/600V DC. 0/6/30/120/600V AC. DC current: 0/12/30/60/120/300mA/6/12A DC. 0/10k/1 Meg/100 Meg. -20 to +50dB. Transistor tester measures Alpha, Beta and ICD. Complete with instructions, batteries and leads.



OUR PRICE £19.95 P & P 25p

SWR METER MODEL SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 50 Ohm. Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.



OUR PRICE £4.25 P & P 30p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic wave forms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 10kHz: VRMS/mm: 0.1-25; HOR. AMP. Bandwidth: 500kHz. Sensitivity by 100kHz: VRMS/mm: 0.3-25. Preset triggered sweep 1-3000/sec. Free running 200-2000 Hz in nine ranges. Calibrator pips 220 x 360 x 430mm. 115-230V AC.



OUR PRICE £44.00 Carr. paid

ALL PRICES EXCLUDE VAT

Also see following pages

SINCLAIR DM2 DIGITAL MULTIMETER



Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply.

RANGES:
DC VOLTS: 1v, 10v, 100v, 1000v
AC VOLTS: 1v, 10v, 100v, 1000v
DC CURRENT: 1mA, 10mA, 100mA, 1000mA
AC CURRENT: 1mA, 10mA, 100mA, 1000mA
RESISTANCE: 1k, 10k, 100k, 1000k

OUR PRICE £59.95 P & P 50p

RUSSIAN C116 Double Beam OSCILLOSCOPE

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2µsec. to 100 milli-sec/cm. Free running time base, 50Hz-1MHz. Built-in time base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.

OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz-260MHz. In six coils. 500µA meter. 9V battery operation. Size: 180 x 80 x 40mm.

OUR PRICE £17.50 P & P 30p

TRANSISTORISED L.C. A.C. BR/8 MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm ± 1% Inductance: 6 ranges: 1 millihenry-111 henries ± 2% Capacity: 6 ranges: 10pF-1110 mfd ± 2% Turns Ratio: 6 ranges: 1.1/1000-1.11100 ± 1% Bridge Voltage at 1.000cps. Operated from 9-volt battery. 100 micro-amp meter indication. Size 7 1/2" x 5" x 2"

OUR PRICE £27.50 P & P 30p

TE16A TRANSISTORISED SIGNAL GENERATOR

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale, 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.

OUR PRICE £8.97 P & P 30p

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 8 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.

OUR PRICE £19.95 P & P 50p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/Sine wave 10V. P.P. RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.

OUR PRICE £37.50 P & P 50p

MOEEL TE20 RF SIGNAL GENERATOR

Six bands. 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 155mm. Complete with test leads etc.

OUR PRICE £18.95 P & P 50p

TE22 SINE SQUARE WAVE AUDIO GENERATOR

Size 200cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.

OUR PRICE £24.95 P & P 50p

MODEL U4311 Sub-standard Multi-range Volt-Ammeter

Sensitive 330 Ohms/Volt AC and DC. Accuracy 0.5% DC 0.7% AC. Scale length: 165mm. 0/300/750mA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V DC. 0/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.

OUR PRICE £52.00 P & P 50p

OT 124 POWER UNIT

220-240V AC Input. Output 6, 7.5 or 9V DC 400 mA.

OUR PRICE £2.20 P & P 50p

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.

OUR PRICE £19.95 P & P 50p

BATTERY/LEVEL PANEL INDICATOR

150 mA 18mm 1.8mm Panel mounting.

OUR PRICE 75p P & P 15p Discounts for quantity.

NEW GOLDRING G102 KIT

Belt-drive 2-speed turntable in kit form complete with pick up arm and head shell.

OUR PRICE £16.95 P & P 75p

VU METER TYPE 3

Size: 33mm 20mm. £1.25 P & P 15p

SO8H MONO/STEREO HEADPHONES

Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.

OUR PRICE £4.97 P & P 30p

BH001 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.

OUR PRICE £5.95 P & P 30p

T.T.C. SPRITE STEREO HEADPHONES

Feather weight (5oz) Dynamic stereo headphones providing high quality reproduction at a budget price. Soft removable ear pads and adjustable headband. Speaker size: 28mm. Impedance: 8 ohms. Frequency response: 30-13000 Hz.

OUR PRICE £1.95 P & P 30p

UNIPEX NT100A

The unipex NT100A is a compact portable transistorised PA amplifier. This versatile unit has a maximum output of 10 watts RMS and operates on any 10-15V DC source, negative or positive ground and uses only 1.5A at rated output. Supplied complete with mounting brackets etc. plus full installation and operating instructions.

OUR PRICE £21.75 P & P 50p

EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverb control. Beaulieu cabinet. 184 x 77 x 108mm.

OUR PRICE £7.50 P & P 30p

RANK AUDIO RA 210T STEREO AMPLIFIER

75 75 watts rms. Inputs for magnetic phono, tuner, tape and aux. Separate base, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer.

OUR PRICE £17.50 P & P 50p

VHF 105

This unit will give instant reception of the ground-to-air, air-to-ground waveband. Simply place beside any AM or FM radio covering 535-1605 kHz. 88-108 MHz - no connection or connection required. This converter is self powered by one 9-volt (PP3 type) battery and comes complete with full set of instructions and battery.

OUR PRICE £3.50 P & P 50p

Just arrived - the sensational WIEN ET1008 CASSETTE! RECORDER

A highly recommended cassette recorder at this really low Laskys price. **ONLY £8.95** P & P 50p

SPECIAL OFFER! CONVERT YOUR STEREO SYSTEM TO 4D SOUND

This clever unit enables you to add 4D sound to your existing system. Complete with simple connection details. Use this converter (together with 2 extra speakers) to achieve the fantastic 4D quadrophonic sound! The effect of being immersed within the music becomes a thrilling new experience (2 year guarantee).

OUR PRICE £3.95 P & P 50p

FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 I F stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.

OUR PRICE £8.95 P & P 20p Stereo Multiplex Adaptor £5.95 extra

WALKIE TALKIES SKYFON NV7

Super low cost transmitter/receiver. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna.

OUR PRICE £31.50 per PAIR P & P 50p. NOT LICENSABLE IN THE U.K.

ELECTRONIC CALCULATORS

We carry a tremendous range of both pocket and desk calculators from as little as £8.90. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

MINIATURE ORGAN MUSIC MASTER AM100

Spanning nearly two octaves, including semitones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket.

OUR PRICE £7.95 P & P 50p

BINATONE DIGITAL CLOCK

Attractive ivory case. Large clear numbers for hours, minutes and seconds. A.C. 240V operation. Size approx. 6 1/2 x 3 1/2 inches.

OUR PRICE £4.50 P & P 50p

SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER

complete with printed circuit mounting board.

OUR PRICE £1.50 P & P 15p.

SINCLAIR Project 80 Modules

Z40 Power Amp. £5.95 P & P 15p
Z80 Power Amp. £7.45 P & P 15p
Stereo 80 Pre-Amp. £13.95 P & P 15p
Active Filter Unit £7.45 P & P 15p
FM Tuner £13.95 P & P 15p
Stereo Decoder £8.95 P & P 15p
P28 Power Supply £5.95 P & P 30p
P28 Power Supply £8.45 P & P 30p
Transformer for P28 £4.05 P & P 50p

SINCLAIR Project 80 Packages

2x240/Stereo 80/P28 £25.44 P & P 35p
2x240/Stereo 80/P28 £27.84 each
2x260/Stereo 80/P28 £29.84

TE1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. Two gain controls, speakers on-off side switch, stereo headphone socket.

OUR PRICE £2.25 P & P 15p

AUDIOTRONIC LOW NOISE CASSETTES

TYPE	5	10	25
C80	£1.57	£3.00	£7.08
C90	£2.24	£4.25	£10.00
C120	£2.73	£5.17	£12.24

P & P 3p each. 10 and over Post Free

MPT MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 4mV 50 ohms. Ceramic 100mV 1 Meg. Output 250mV 100k.

OUR PRICE £8.97 P & P 20p

AUDIOTRONIC AHA101 Stereo Headphone Amplifier

All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs: 5mV and 100mV. OUTPUT: 50mV per channel.

OUR PRICE £8.50 P & P 30p

HIGH QUALITY CONSTRUCTION KITS

WE ARE STOCKISTS AT Oxford Street, 42 & 257 Tottenham Court Road, 34 Lisle Street, 152, Fleet Street, 311 Edgware Road, CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Packing 15p per kit.

AF20 Mono amplifier	£5.61
AF25 Mixer	£3.29
AF30 Mono pre-amplifier	£3.20
AF35 FM transmitter	£2.42
AF80 0.5W mic. amplifier	£4.86
AF305 Intercom	£7.87
AF310 2 Mono Amplifier	£7.55
M160 Multi-vibrator	£2.18
M1302 Transistor tester	£8.33
M191 VU Meter	£5.37
M192 Stereo balance meter	£5.93
AT56 Quadrophonic device	£8.42
AT5 Automatic light control	£3.75
AT30 Photo cell switch unit	£6.68
AT50 400V triac light dimmer/speed control	£5.18
AT56 2,200V triac light dimmer/speed control	£6.75
AT60 1 channel light control	£10.82
AT65 5 channel light control	£16.52
GU330 Tremolo unit	£8.10
HF61 Diode detector	£3.87
HF65 FM transmitter	£3.21
HF75 FM receiver	£3.66
HF10 FM tuner	£16.32
HF325 Deluxe FM tuner	£26.33
HF330 Decoder (HF310/325)	£10.55
HF330 Stereo pre-amp	£22.98
for use with 2 x AF310	£22.98
GP312 Circuit board	£10.02
GP304 Circuit board	£5.33
HF380 lw/hf aerial amplifier	£6.02
HF395 broadband amplifier	£11.26
NT10 Stabilised power supply 100mA, 9V	£6.27
NT300 Stabilised p. supply	£13.16
NT310 Power supply 240 V AC or 2 x 18 V DC. at 2 amps	£5.64
NT305 Voltage converter	£5.64
NT315 Power supply 240V AC to 4.5/15V DC, 500mA	£12.06

Amateur Electronics by Josty-Kit, the professional book for the amateur - covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.

OUR PRICE £3.30 (No VAT) P & P 25p plus VAT.

AE1 100mW output stage	£1.55
AE2 Pre-amplifier	£1.32
AE3 Diode receiver	£2.05
AE4 Flasher	£1.26
AE5 Astable multi-vibrator	£1.14
AE6 Monostable multi-vibrator	£1.11
AE7 RC generator	£1.18
AE8 Bass filter	£1.05
AE9 Treble filter	£1.05
AE10 CCIR filter	£1.05

Also see previous page
ALL PRICES EXCLUDE VAT

SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR
3 LISLE ST., 311 EDGWARE RD. & 152 FLEET
ST., BRANCHES or order by post.



USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CALL INTO YOUR NEAREST
LASKYS BRANCH OR
SEND COUPON BELOW
FOR NEW 32 PAGE
HI-FI PRICE LIST

CENTRAL LONDON	
481 OXFORD ST	01-493 8641
3 LISLE ST. WC2	01-437 8204
34 LISLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-353 5812
152/3 FLEET ST. EC4	01-353 2833
10 TOTENHAM CT. RD.	01-637 2232
27 TOTENHAM CT. RD.	01-634 3715
33 TOTENHAM CT. RD.	01-634 2605
42/45 TOTENHAM CT. RD.	01-636 0845
257/8 TOTENHAM CT. RD.	01-580 0670

ESSEX	
86 SOUTH ST. ROMFORD	20210
205/206 CHURCHILL WEST, VICTORIA CROSS, SOUTHWEND 0702 612241	

GLOUCESTERSHIRE	
16/20, PENN ST. BRISTOL 0272-20421	

KENT	
53/57 CAMDEN RD., TUNBRIDGE WELLS	0892-23342

LEICESTERSHIRE	
45 MARKET PLACE, LEICESTER	0533-537678

NORTHAMPTONSHIRE	
73 ABINGTON STREET, NORTHAMPTON	0504-35753

NOTTINGHAMSHIRE	
57 LOWER PARLIAMENT STREET, NOTTINGHAM	

OXFORDSHIRE	
16 WESTGATE SHOPPING CENTRE, OXFORD	

STAFFORDSHIRE	
30 WULFRUM WAY, WOLVERHAMPTON	0902-23384

SURREY	
1046 WHITGIFT CENTRE, CROYDON	01-481 3027
38/40 EDEN ST., KINGSTON	01-546 1271
32 HILL ST. RICHMOND	01-948 1441

WARWICKSHIRE	
116 CORPORATION ST., BIRMINGHAM	021-236 3503

ALL BRANCHES OPEN FROM
9am to 6pm MON TO SAT

OUR CUSTOMER
SERVICES DIVISION at head office
will answer all your enquiries—
just ring 01-200 1321

EXPORT Personal exports
arranged for overseas visitors
Goods specially packed,
insured and despatched to all
parts of the world at minimum
cost exclusive of VAT.
Payment by bank transfer,
certified cheque, postal order
or money order in any
currency.

BARCLAYCARD & ACCESS

Phone your order to
01-200 0037 or
call into any branch

NO DEPOSIT TERMS
available on most goods
for personal callers

CHEQUES TO THE VALUE OF £20.
ACCEPTED FROM PERSONAL SHOPPERS
WITH BARRIERS CARD. IN OTHER CASES
AND FOR AMOUNTS IN EXCESS OF £20,
PLEASE ALLOW TIME FOR CLEARANCE.
BANKERS DRAFTS ACCEPTED.

All prices correct as 13/1/75 but
subject to change without notice E.B.O.E.
A member of the
Audiotronic Group of Companies

CLEAR PLASTIC MODEL SD640
Size: 85 x 84mm

50uA	£3.90
100uA	£3.85
200uA	£3.80
500uA	£3.75
50-0-500uA	£3.85
100-0-100uA	£3.80
1mA	£3.75
5mA	£3.75
10mA	£3.75
50mA	£3.75
100mA	£3.75
500mA	£3.75
1A DC	£3.75
5A DC	£3.75
10A DC	£3.75
5V DC	£3.75

10V DC .. £3.75
20V DC .. £3.75
50V DC .. £3.75
300V DC .. £3.75
15V AC .. £3.85
30V AC .. £3.85
300V AC .. £3.85
VU Meter .. £4.00

CLEAR PLASTIC MODEL SW100
Size: 100 x 80mm

50uA	£4.70
100uA	£4.60
500uA	£4.60
50-0-500uA	£4.80
100-0-100uA	£4.85
1mA	£4.80
5mA	£4.40
1A DC	£4.40
5A DC	£4.40
20V DC	£4.40
50V DC	£4.40
300V DC	£4.40

150V AC .. £4.55
300V AC .. £4.55
VU Meter .. £6.00

EDGWISSE MODEL PE70
Size: 90 x 34mm

50uA	£4.25
100uA	£4.20
200uA	£4.15
500uA	£4.00
50-0-500uA	£4.20
100-0-100uA	£4.15
1mA	£4.10
5mA	£4.05
10A DC	£4.05
50A DC	£4.05
300V AC	£4.05
VU Meter	£4.40

MODEL ED107 EDUCATIONAL METER
Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

50uA	£8.70
100uA	£8.10
50-0-500uA	£8.10
1mA	£7.80
1-0-1mA	£7.80
5A DC	£7.80
5V DC	£7.80
10V DC	£7.80
15V DC	£7.80

20V DC .. £7.80
50V DC .. £7.80
300V DC .. £7.80
500mA .. £7.80
1A DC .. £7.80
5A DC .. £7.80
5V/15V DC .. £8.80
1/5A DC .. £8.80

CLEAR PLASTIC MODEL MR 85P
Size: 120 x 110mm

50uA	£5.80
100uA	£5.55
200uA	£5.50
500uA	£5.40
50-0-500uA	£5.55
100-0-100uA	£5.50
500-0-500uA	£5.50
1mA	£5.35
1-0-1mA	£5.35
5mA	£5.35
10mA	£5.35
50mA	£5.35
100mA	£5.35
500mA	£5.35
1A DC	£5.35
5A DC	£5.35
15A DC	£5.35
30A DC	£5.35
10V DC	£5.35
20V DC	£5.35
50V DC	£5.35
150V DC	£5.35

300V DC .. £5.40
15V AC .. £5.45
30V AC .. £5.45
300V AC .. £5.35
S Meter 1mA .. £5.35
VU Meter .. £5.70
1A AC .. £5.35
5A AC .. £5.35
10A AC .. £5.35
20A AC .. £5.35
30A AC .. £5.35

240° Wide Angle
1mA METERS
MW1-8.60 x 60 mm
£6.50 P & P 15p
MW1-8.80 x 80 mm
£8.90 P&P 15p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS
Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V.
MODEL S280 BENCH MOUNTING

1A	£10.50
2.5A	£12.00
5A	£17.50
8A	£20.35
10A	£33.75
12A	£35.40
20A	£85.00
25A	£95.00
40A	£120.00

ALL PRICES EXCLUDE VAT

CLEAR PLASTIC MODEL MR 65P
Size: 86 x 78mm

50uA	£4.05
100uA	£3.95
200uA	£3.90
500uA	£3.85
50-0-500uA	£3.95
100-0-100uA	£3.90
500-0-500uA	£3.90
1mA	£3.80
1-0-1mA	£3.80
5mA	£3.80
10mA	£3.80
50mA	£3.80
100mA	£3.80
500mA	£3.80
1A DC	£3.80
5A DC	£3.80
10A DC	£3.80
15A DC	£3.80
20A DC	£3.80
30A DC	£3.80
50A DC	£3.80
10V DC	£3.80
20V DC	£3.80
50V DC	£3.80
150V DC	£3.80

300V DC .. £3.80
15V AC .. £3.90
30V AC .. £3.90
50V AC .. £3.90
100V AC .. £3.90
300V AC .. £3.90
500V AC .. £3.90
S Meter 1mA .. £3.90
VU Meter .. £3.80
1A AC .. £3.80
5A AC .. £3.80
10A AC .. £3.80
20A AC .. £3.80
30A AC .. £3.80
50A AC .. £3.80
100mA AC .. £3.80
200mA AC .. £3.80
500mA AC .. £3.80

CLEAR PLASTIC MODEL MR 45P
Size: 50 x 50mm

50uA	£3.30
100uA	£3.25
200uA	£3.20
500uA	£3.10
50-0-500uA	£3.25
100-0-100uA	£3.20
500-0-500uA	£3.05
1mA	£3.05
5mA	£3.05
10mA	£3.05
50mA	£3.05
100mA	£3.05
500mA	£3.05
1A DC	£3.05
5A DC	£3.05
10V DC	£3.05
20V DC	£3.05
50V DC	£3.05
150V DC	£3.05

300V AC .. £3.15
S Meter 1mA .. £3.05
VU Meter .. £3.30
1A AC .. £3.05
5A AC .. £3.05
10A AC .. £3.05
20A AC .. £3.05
30A AC .. £3.05

CLEAR PLASTIC MODEL MR 38P
Size: 42 x 42mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.20
50-0-500uA	£3.10
100-0-100uA	£3.10
500-0-500uA	£2.85
1mA	£2.85
1-0-1mA	£2.85
2mA	£2.85
5mA	£2.85
10mA	£2.85
50mA	£2.85
100mA	£2.85
150mA	£2.85
200mA	£2.85
300mA	£2.85
500mA	£2.85
750mA	£2.85
1A DC	£2.85
2A DC	£2.85
5A DC	£2.85
10A DC	£2.85
3V DC	£2.85
10V DC	£2.85
15V DC	£2.85

20V DC .. £2.85
50V DC .. £2.85
100V DC .. £2.85
150V DC .. £2.85
300V DC .. £2.90
500V DC .. £2.95
750V DC .. £2.95
15V AC .. £2.95
50V AC .. £2.95
100V AC .. £2.95
150V AC .. £2.95
300V AC .. £2.95
500V AC .. £3.10
S Meter 1mA .. £2.95
VU Meter .. £3.30

CLEAR PLASTIC MODEL SD460
Size: 58 x 46mm

50uA	£3.60
100uA	£3.55
200uA	£3.50
500uA	£3.45
50-0-500uA	£3.55
100-0-100uA	£3.50
500-0-500uA	£3.40
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10A DC	£3.40
15V DC	£3.40
50V DC	£3.40
300V DC	£3.40
500V DC	£3.40
15V AC	£3.40
50V AC	£3.40
300V AC	£3.40
500V AC	£3.40
15V AC	£3.40
50V AC	£3.40
300V AC	£3.40
500V AC	£3.40

BAKELITE MODEL S80 Enlarged Window
Size: 80 x 80mm

50uA	£4.80
100uA	£4.55
500uA	£4.30
50-0-500uA	£4.55
100-0-100uA	£4.50
500-0-500uA	£4.30
1mA	£4.30
5mA	£4.30
10mA	£4.30
50mA	£4.30
100mA	£4.30
500mA	£4.30
1A DC	£4.30
5A DC	£4.30
20V DC	£4.30
50V DC	£4.30
300V DC	£4.30
300V AC	£4.40
VU Meter	£4.80

S Meter 1mA .. £3.40
VU Meter .. £3.90
1A AC .. £3.40
5A AC .. £3.40
10A AC .. £3.40
20A AC .. £3.40
30A AC .. £3.40

CLEAR PLASTIC MODEL MR 52P
Size: 60 x 60mm

50uA	£3.80
100uA	£3.60
200uA	£3.55
500uA	£3.60
100-0-100uA	£3.45
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
20V DC	£3.40
50V DC	£3.40
15V AC	£3.50
30V AC	£3.50
300V AC	£3.50

S Meter 1mA .. £3.40
VU Meter .. £3.90
1A AC .. £3.40
5A AC .. £3.40
10A AC .. £3.40
20A AC .. £3.40
30A AC .. £3.40

BAKELITE MODEL MR 65 Size: 80 x 80mm

25uA	£5.40
50uA	£4.10
100uA	£4.05
500uA	£3.75
50-0-500uA	£4.05
100-0-100uA	£4.00
500-0-500uA	£3.70
1mA	£3.70
1-0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
2A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
30A DC	£3.70
50A DC	£3.70
100A DC	£3.70
15V DC	£3.70
30V DC	£3.70
50V DC	£3.70
150V DC	£3.70

300V DC .. £3.90
20V AC .. £3.70
50V AC .. £3.70
100V AC .. £3.70
150V AC .. £3.70
300V AC .. £3.70
500V AC .. £3.70
1A AC .. £3.70
5A AC .. £3.70
10A AC .. £3.70
20A AC .. £3.70
30A AC .. £3.70
50A AC .. £3.70
100mA AC .. £3.70
200mA AC .. £3.70
500mA AC .. £3.70
100mV DC .. £3.85
50mV DC .. £3.85
100mV DC .. £3.85

POSTAGE & PACKING 15p

ASK LASKYS

TO LASKYS CUSTOMER SERVICES DIVISION
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me the following items _____

TOTAL PURCHASE PRICE _____ (inc. P&P and VAT)

I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is _____

NAME _____


ADDRESS _____

Signature _____

Registered in England No. 347947 at 12 Lower Grosvenor Place London SW1 0EP

32 Page HI-FI PRICE LIST TICK HERE

BIG Discounts

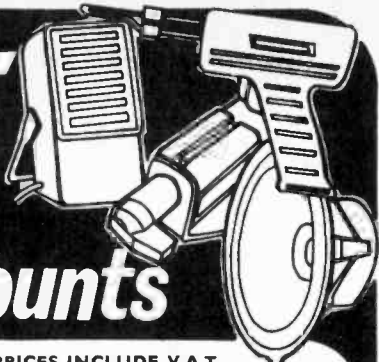

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£		
EMI 13in x 8in 3, 8 or 15 ohm			ELAC 8in 8 ohm Dual cone	2-30
Plain	2-05		ELAC 10in 8 ohm Dual cone	3-50
With Co-Axial Tweeter			GOODMANS 6in 8 ohm Dual cone	2-15
8 ohm only	2-20		7in x 4in, 3 or 8 ohm	1-00
Twin Tweeter 8 ohm only	3-95		ADASTRA 10in, 8 or 15 ohm,	3-65
Type 350, 8 ohm, 20W	7-95		10W	
6in, 8 ohm, 10W	2-60		BAKER GROUP 25 12in, 8 or	7-95
8in, 8 ohm, 10W	4-50		15 ohm, 25W	
12in, 8 ohm, 20W	6-70		P. & P 40p per speaker	
8in x 5in, C/Mag. 5W	1-40		5in, 8 ohm, C/Mag.	0-85
8in x 5in, Dual cone 8 ohm,			2in, 8 ohm or 64 ohm	0-55
10W	2-55		P. & P.	0-15
ELAC 6in 8 ohm Dual cone	2-15			

TWEETER AND CROSSOVER				
EMI 3in, 3 or 8 ohm C/Mag.	1-30		Dome Tweeter 8 ohm, 30W	5-60
Cone Tweeter 8 or 15 ohm, 10W	2-60		Crossovers CN23 (3 ohm), CN28	
Cone Tweeter 8 ohm, 3W	1-45		(8 ohm), CN216 (16 ohm)	1-30
Horn Tweeter 8 ohm, 20W	6-40		P. & P.	0-15

KIT FORM CABINETS, TEAK				
VEHEER, 12in x 12in x 6in with 8in,			13in x 8in cutout	4-25
8in x 5in or 6in and 3in			18in x 11in x 9in with 13in x	
cutout	3-40		8in cutout for EMI 350	4-75
17in x 10in x 9in with 8in or			P. & P. each	0-50

MICROPHONES				
CM70 Planet stick metal,			TW209	5-75
switch crystal	1-55		CONDENSER MIKE 600 ohm,	9-35
UD160 Dynamic omni-dir, ball			uni-dir	
metal	4-90		Cass. Stick Mike with R.	
UD130 50K/600 ohm, uni-dir,			Control on/off switch (2-5	1-50
ball metal	6-40		and 3-6mm J/Ply)	
			Cass. Stick Mike with R.	1-70
			Control (Philips type)	0-30

SOLDERING IRONS				
ANTEX CN240 15W	2-00		spare Bib, etc.)	3-40
SK1 Kit (15 watt iron, 2			X25 25W (low leakage)	2-00
			P. & P.	0-15

CARTRIDGES AND STYLII				
ACOS GP91/28C or 33C Stereo			SONOTONE 9TAHC or 9TAHC/G	1-80
comp.	1-00		diam.	
GP93/1 or 95/1 Stereo crystal	1-35		3509 Stereo ceramic diam.	1-90
GP94/1 or 96/1 Stereo ceramic	1-75		GOLDRING G850	2-95
GP101 Crystal comp.	0-80		G800	3-95
GP104 Stereo ceramic	1-65		G800E	6-90
BSR X5M or 5XH Crystal comp.	1-70		P. & P.	0-15
SX6M or SX6H Crystal comp.	1-90		D. Diamond Stylil for above	1-25
SC5M Stereo ceramic	2-60		G800/G850	1-85
			G800E	3-95
			P. & P.	0-05

BATTERY ELIMINATORS				
240V input 6, 7.5 or 9 300mA	2-95		12V (please specify output)	2-30
			300mA	0-15
			P. & P.	0-15

TAPES		Stnd.	LP	DP	PLASTIC LIBRARY CASES	
5in	50p	65p	1-25p		5in Reels 18p.	5in. 22p. 7in. 25p.
5in	85p	80p	1-45p		P. & P. 1-3 3p each. 4 or more lot 35p	
7in	80p	1-10p	1-80p			

LOW NOISE CASSETTES					
C60	35p	33p	30p	Cassette Head Cleaner	0-35
C90	85p	43p	40p	P. & P. 1-5 each	0-05
C120	75p	52p	50p	6-10 lot	0-20
				11-20 post free	

BIB ACCESSORIES				
Tape Editing Kit, Ref. 23	1-35		CALCULATORS	
Recording Tape Splicer, Ref. 20	1-15		SINCLAIR Cambridge	£12-95
Cassette Tape, Editing, Ref. 24	1-50		Scientific	£10-95
Cassette Salvage Kit, Ref. 29	0-45			

WHARFEDALE SPEAKER BARGAINS		P & P
Linton 2 Kit (pr.)	19-00	1-50
Glendale 3 Kit (pr.)	33-50	2-00
Dovedale 3 Kit (pr.)	52-00	2-00
Denton 2 Speaker (pr.)	30-00	2-50
Linton 2 Speaker (pr.)	39-50	2-50
Dovedale 3 Speaker (each)	45-00	2-50
Glendale 3 Speaker (pr.)	57-00	3-50
Kingsdale 3 Speaker (each)	59-95	4-00

Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
 Subject to manufacturers' increase and availability

Riversdale Electronics

Mail Order Department PE/4
 P.O. Box 470, Manchester M60 4BU



4in x 3in METER. 30µA, 50µA or 100µA, £3-85. 11p P. & P.

TAPE RECORDER LEVEL METER



500µA, 70p. 5p P. & P.



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £6-55. 11p P. & P.

42 x 42mm meters 100µA, 500µA, 1mA, 500mA, £2-76. 11p P. & P.
 60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £2-92. 11p P. & P.
 Edgewise meters 90mm x 34mm 1mA, £3-40. 11p P. & P.

MULTI-METER



Model D62
 20,000 ohm/volt, £7-65.
 15p P. & P.



3 WATT STEREO AMPLIFIER
 £4-30. 10p P. & P.


All above prices include 8% V.A.T. LARGE S.A.E. for List No. 11. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

Dimmit

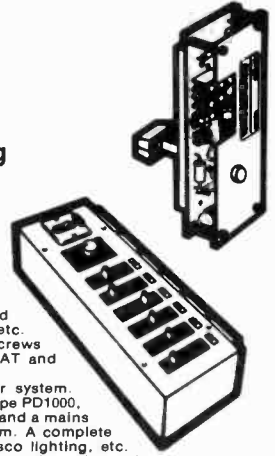range of light dimmers and lighting control systems



Illustrated is the popular PMSD1000 module. A 1kW slider control dimmer, interference suppressed, 60mm slider range size 12 x 5 x 4cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £7-25 inc. VAT and P. & P.

Illustrated is the DD61 dimmer system. Contains six 1kW slider dimmers type PD1000, six outlet sockets, a master control and a mains on/off switch. Size 59 x 22 x 12cm. A complete system in one unit for stage or disco lighting, etc. Also available DD261 dimmer system, as above, but with 2-preset arrangement. Future systems available with 2kW dimmers. Specials made DD61 £97-20 inc. VAT and P. & P. DD261 £117-72 inc. VAT and P. & P.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for industrial heating applications, etc. Rotary and slider control versions. Ratings: 1000W, 2000W, 3000W, 110V and 240V.

Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. No connections to speaker required. Simple wiring—similar to dimmer. Rating 800W.

All products are guaranteed and are supplied with full instructions and applications. Full after-sales service. Technical advice given.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Callers welcome, visit our showroom for a demonstration of any of the modules or systems. Mon-Fri. 9.30 to 6.0 p.m. Sat. by arrangement.

YOUNG ELECTRONICS LTD.

184 Royal College Street, London NW1 9NN. Tel. 01-267 0201

Sinclair Project 80



For elegant, versatile, stereo hi-fi systems designed and built by you!

Until recently, if you wanted a first-class hi-fi system you had two ways to get it.

You could buy the individual electronic components and build a system from scratch. If you were an electronics genius – fine.

Or you had to buy ready-made units. Expensive – and dull. About the only creative pleasure you'd get would be matching your amp and your speakers, or making your speaker enclosures.

So what's new?

A comprehensive hi-fi system, combining the enjoyment and satisfaction of build-it-yourself (without too much struggle)... a real value-for-money feeling... and results of the highest quality.

It's the new Sinclair Project 80.

How does Sinclair Project 80 work?

Project 80 is a comprehensive set of hi-fi modules, or sub-assemblies. Amps... pre-amps... FM tuners... stereo decoders... control units... everything you need to assemble hi-fi units. They're all designed to look alike and they're all completely compatible with each other. Simply decide on the specifications of the unit you want to build... buy the necessary modules... connect them... and house them.

No need to buy everything at once for your eventual set-up. All the modules are designed so that you can add to them as your system grows – whether or not it's based on Project 80.

This applies to refinements, like filters... to up-grading, adding a second set of amps, say, for greater output... or to real innovation, like quad. (Add a Project 80 quad decoder, a power supply, a pair of amps, and a pair of speakers – and your stereo's gone quad.)

Is it difficult to build?

Not at all. The modules are complete in themselves. All you do is connect them to your turntable... your speakers... or to each other. It's absorbing, but if you can solder wires to a 5-pin DIN plug, you can build a complete system with Project 80.

And if you're not so hot with a soldering iron? Use Project 805. Project 805 uses Project 80 modules, but provides special clip-on tagged wire connections – absolutely *no* soldering required.

And, of course, both Project 80 and Project 805 come complete with instructions for easy, step-by-step assembly. But if you do run into problems, just call our Consumer Advisory Service who are always happy to help.


OK. Where do I go from here?

Over the page! There you'll see for yourself the exacting specifications to which Sinclair Project 80 modules are made, and you'll see some suggested systems.

As you skim the suggestions, remember all Project 80 modules are backed by the remarkable no-quibble Sinclair guarantee. Should any defect arise from normal use within a year, we'll service the modules free of charge. What could be fairer than that?



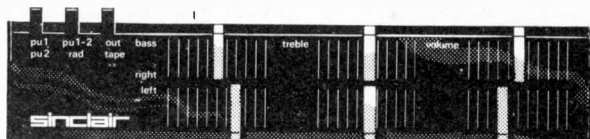Choose the Project 80 modules that are right for you.



Project 80 pre-amp/control unit

The control centre of Project 80. With its distinctive white-on-matt-black styling and plastic control sliders, it's a pleasure to look at, as well as to use.

Specification

(9 1/2 in x 2 in x 3/4 in.) Separate slider controls on each channel for treble, bass and volume. Inputs: PU magnetic - 3 mV (RIAA corrected), ceramic - 350 mV.

Radio 100 mV; Tape 30 mV. S/N ratio: 60 dB. Frequency range: 20 Hz to 15 kHz \pm 1 dB. Outputs: 100 mV and tape plus AB monitoring. Press buttons for PU, radio and tape. Operating voltage: 20 V - 35 V.

Price: £13.95 + VAT



Project 80 power amplifiers

Two different amplifiers, designed to be used separately or combined, with Project 80 modules or as add-ons to existing equipment. Protected against short circuits and damage from mis-use.

Z40 Specification

(2 1/4 in x 3 in x 3/4 in.) 8 transistors. Input sensitivity: 100 mV. Output: 12 W RMS continuous into 8 Ω (35 V). Frequency response: 30 Hz - 100 kHz \pm 3 dB. S/N ratio: 64 dB. Distortion: 0.1%


at 10 W into 8 Ω at 1 kHz. Voltage requirements: 12 V - 35 V. Load imp: 4 Ω - 15 Ω ; safe on open circuit. Protected against short circuit.

Price: £5.95 + VAT

Z60 Specification

(2 1/4 in x 3 3/4 in x 3/4 in.) 12 transistors. Input sensitivity: 100 mV - 250 mV. Output: 25 W RMS continuous into 8 Ω (50 V). Frequency response: 10 Hz to more than 200 kHz \pm 3 dB. S/N ratio: better than 70 dB. Distortion: 0.02% at 10 W into 8 Ω at 1 kHz. Voltage requirements: 12 V - 50 V. Load imp: 4 Ω min; max safe on open circuit. Protected against short circuit.

Price: £7.45 + VAT

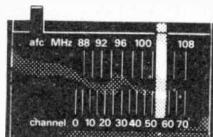

Project 80 FM tuner

Excellent reception from a tuner only 3 1/2 in long x 3/4 in deep! Styled to match Project 80 control unit.

Specification


(3 1/2 in x 2 in x 3/4 in.) Tunes 87.5 MHz to 108 MHz. Detector: IC balanced

coincidence (IC equivalent to 26 transistors) Distortion: 0.3% at 1 kHz for 30% modulation.

Sensitivity: 5 μ V for 30 dB signal to noise. Output: 100 mV for 30% modulation. Aerial imp: 75 Ω or 240-300 Ω . Features: dual Varicap tuning, 4-pole ceramic filter, switchable AFC.

Operating voltage: 23 V - 30 V

Price: £13.95 + VAT

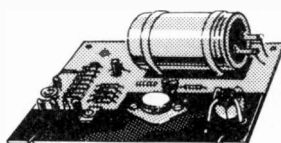

Power supply units

Range of power supply units to match desired specification of final system.

PZ5 Specification

Unstabilised. 30 V output. Including mains transformer.

Price: £5.95 + VAT

PZ6 Specification


Stabilised. 35 V output. Including mains transformer.

Price: £8.95 + VAT

PZ8 Specification

Stabilised. Output adjustable from 20 V to 60 V approx. Re-entrant current limiting makes damage from overload or even shorting virtually impossible. Without mains transformer.

Price: £8.45 + VAT

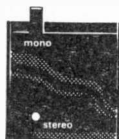

Project 80 stereo decoder


Designed for use with Project 80 FM tuner. Sold separately to

keep down the price of a mono FM system, but also to make the stereo decoder available for use with existing mono FM tuners.

Specification

(1 1/4 in x 2 in x 3/4 in.) 1 IC equivalent to 19 transistors. LED stereo indicator glows red.

Price: £8.95 + VAT

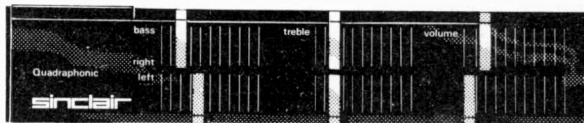

Project 80 SQ quadraphonic decoder

Combines with and exactly matches Project 80 control unit for true quadraphonics. This unit is based on the CBS SQ system and is a complete quadraphonic decoder, rear channel pre-amp and control unit.

Specification


(9 1/2 in x 2 in x 3/4 in.) Connects with tape socket on Project 80

control unit or similar facility on any stereo amplifier. Separate slider controls on each channel for treble, bass and volume.

Frequency response: 15 Hz to 25 kHz \pm 3 dB. Distortion: 0.1%. S/N ratio: 58 dB. Rated output: 100 mV. Phase shift network: 90 \pm 10 - 100 Hz to 10 kHz.

Operating voltage: 22 V - 35 V.

Price: £18.95 + VAT

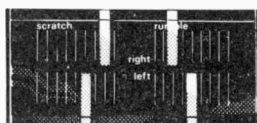

Project 80 active filter unit


Eliminates scratch and rumble (high and low-frequency noise).

Specification

(4 1/4 in x 2 in x 3/4 in.) Voltage gain: -0.2 dB. Frequency response: filter at zero: 36 Hz - 22 kHz; HF (scratch) out: variable 22 kHz to 5.5 kHz, 12 dB/octave slope; LF (rumble) out: -28 dB at 28 Hz, 9 dB/octave slope.

Price: £7.45 + VAT

Some system suggestions from Sinclair

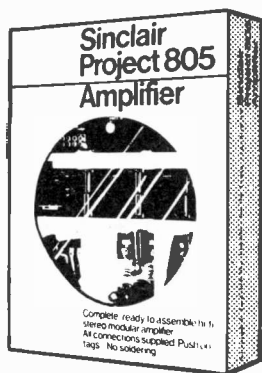

Project 805 amplifier kit

Contains following Project 80 units:

Project 80 control unit
2 x Z40 power amplifier modules
1 x PZ5 power supply unit
Masterlink unit
On/off switch
plus pre-cut wiring loom with clip-on tagged wire connections, nuts and bolts, instruction manual.

Price: £39.95 + VAT




Project 805Q quadraphonic add-on kit

Converts your existing stereo hi-fi system to quad using solderless connections.

Contains following Project 80 units:

Project 80 5Q quad decoder/rear channel pre-amp and control unit
2 x Z40 power amps
PZ5 power supply unit
Masterlink unit
On/off switch
plus pre-cut wiring loom with clip-on tagged wire connections, nuts and bolts, instruction manual.

Price: £44.95 + VAT

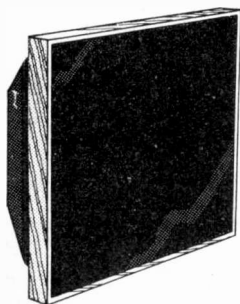

Sinclair Q16 speaker

Original and uniquely designed speaker of outstanding quality.

Specification

(9 $\frac{3}{8}$ in square x 4 $\frac{3}{4}$ in deep.)

Pedestal base. All-over black front. Teak surround. Balanced sealed sound chamber. Special driver assembly. Frequency response: 60 Hz to 16 kHz.

Power handling: up to 14 W RMS.

Impedance: 8 Ω .

Price: £8.95 + VAT

1. Quadraphonic system: 25 W per channel RMS
Pre-amp/control unit + quadraphonic decoder + 4 x Z60 amps + 2 x PZ8 mains power supplies + (2 x mains transformers) + (4 x equivalent speakers) + (turntable). Total Project 80 cost: £79.60 + VAT.

2. Stereo amplifier: 12 W per channel RMS
Pre-amp/control unit + 2 x Z40 amps + PZ6 power supply + 2 x Q16 speakers. Total Project 80 cost: £52.70 + VAT.

3. Stereo tuner/amplifier: 12 W per channel RMS
Pre-amp/control unit + FM tuner + stereo decoder + 2 x Z40 amps + PZ6 power supply + 2 x Q16 speakers. Total Project 80 cost: £75.60 + VAT.

Other applications

4. PA system
(MIC) + pre-amp/control unit + Z40 amp + PZ6 power supply + 2 x Q16 speakers. Total Project 80 cost: £46.75 + VAT.

5. Convert existing mono record-player to stereo
Pre-amp/control unit + Z40 amp + Q16 speaker. Total Project 80 cost: £28.25 + VAT.

What more can we tell you?

The basic facts are covered on these two pages. And you'll find Project 80 at stores like Laskys and Henry's.

But before you look, why not get really detailed information? Clip the FREEPOST coupon for the fully-illustrated Project 80 folder - today!

Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.
Telephone: St Ives (0480) 64646.

sinclair

Sinclair Project 80
a new concept in expandable hi-fi

Project 80 Stereo decoder Q16 Speaker Sinclair Micromatic

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me, by return post, a copy of the fully-illustrated Project 80 folder.

Name _____

Address _____

Please print FREEPOST - no stamp needed.

TO MAKE WAY FOR NEW ADDITIONS

★ AMTRON ★ SPECIAL OFFER AT UNREPEATABLE PRICES

UK160 I.C. Mono Amp. 8 Watt

Specifications:
Output power: 8 W, peak
AUX input sensitivity: 80 mV
PHONO input sensitivity: 300 mV
Output impedance: 5 Ω
Power supply: 12-15 V DC
Transistors: (1) AD161
(1) AD162
IC: TAA435



SALE PRICE £ 6.04 R.R.P. £ 11.46

	Sale Price	Rec. Retail
UK80 Oscilloscope Calibrator	£1.70	2.86
UK92 Telephone Amplifier	5.39	8.93
UK110 Stereo Amp. 5+5 Watt	7.55	12.48
UK115 Hi-Fi Mono Amp 8 Watt	2.94	4.86
UK135 High Impedance Pre-Amp	1.42	2.32
UK140 Low Impedance Pre-Amp	1.42	2.32
UK167 C.C.I.R. Stereo Pre-Amp	3.95	6.38
UK195 Miniature Amp 2 Watt	2.50	3.99
UK255 Level Indicator	4.20	5.91
UK270 I.C. Amp 6 Watt	4.95	7.85
UK275 Microphone Pre-Amp	4.50	7.38
UK375 27MHz Crystal Calibrator	5.45	9.94
UK415/C Resistor Substitution Unit	4.65	8.22
UK425/C Capacitor Sub Unit	4.65	8.17
UK435/C Stab. Power Supply 0=20V DC 1 Amp	13.75	19.16
UK445/C L.F. Watt Meter 5mV=15 Watt	6.55	10.36
UK465 Quartz Crystal Tester	5.50	9.06
UK470/C Crystal Calibration Marker Gen	8.75	14.99
UK555R/C 27MHz Field Strength Meter	5.90	7.25
UK610 Power Supply 24V DC 0.5A	3.75	7.38
UK615 Power Supply 24V DC 1 Amp	3.75	7.24
UK630 Stab. Power Supply 6V-7.5 9V-12V DC	4.95	6.72
UK640 Auto Light Dimmer 200 Watt	4.65	8.19
UK670 Buffer Batt. Charger 12-16V 200mA	4.25	9.45
UK710/C Four Channel A.F. Mixer	7.95	11.65
UK765 Multiple Stereo Junction Box 4x Standard Jack Output	1.98	2.85
UK835 Guitar Pre-Amp.	3.75	5.37
UK840 Car Burglar Alarm	4.65	7.59
UK 855 Electronic Fuzz Box	5.50	7.99
UK860/C Photo Timer	7.95	13.32
UK885 Capacitive Contact Alarm	5.50	7.99
UK900 R.F. Crystal Oscillator [20=60MHZ	1.60	2.86
UK905 R.F. Crystal Oscillator 3=20MHZ	1.60	2.86
UK910 R.F. Mixer 12=170MHZ	1.60	2.86
UK915 R.F. Amp. 12=170MHZ	1.60	2.86
UK920 R.F. Mixer 2-3=27MHZ	1.60	2.86
UK925 R.F. Amp. 2-3=27MHZ	1.60	2.86
UK930 R.F. Power Amp. 3=30MHZ	1.60	2.86
UK935 Wide Band Amp. 3=30MHZ	1.60	2.86

ALL PRICES INC. VAT. POST & PACKING 25p.



FOR ILLUSTRATED CATALOGUE OF FULL RANGE SEND/15p TO:

AMTRON UK LTD.
4 & 7 CASTLE ST.
HASTINGS, SUSSEX.
TEL (0424) 437875

TTL AT LOWEST PRICES!

Fast Delivery by 1st Class Post
All Prices include VAT (at 8%)

All Full Specification by Famous Manufacturers

Type	1/24	25/99	100+	Type	1/24	25/99	100+
	£	£	£		£	£	£
SN7400	0-14	0-13	0-12	SN7454	0-15	0-14	0-13
SN7401	0-15	0-14	0-13	SN7480	0-15	0-14	0-13
SN7402	0-15	0-14	0-13	SN7472	0-28	0-27	0-25
SN7403	0-15	0-14	0-13	SN7473	0-33	0-32	0-30
SN7404	0-18	0-16	0-15	SN7474	0-33	0-32	0-31
SN7405	0-18	0-16	0-15	SN7475	0-51	0-49	0-47
SN7408	0-18	0-16	0-15	SN7476	0-35	0-32	0-31
SN7410	0-15	0-14	0-13	SN7480	0-50	0-47	0-44
SN7412	0-23	0-21	0-19	SN7483	0-95	0-99	0-93
SN7413	0-33	0-32	0-31	SN7486	0-34	0-33	0-31
SN7417	0-30	0-29	0-28	SN7489	3-56	3-33	2-96
SN7420	0-15	0-14	0-13	SN7490	0-49	0-48	0-46
SN7427	0-29	0-28	0-27	SN7491	0-99	0-94	0-89
SN7430	0-15	0-14	0-13	SN7492	0-54	0-50	0-47
SN7432	0-31	0-29	0-27	SN7493	0-51	0-50	0-47
SN7437	0-31	0-29	0-27	SN7495	0-73	0-68	0-64
SN7440	0-15	0-14	0-13	SN7496	0-83	0-78	0-73
SN7442	0-70	0-68	0-64	SN74107	0-35	0-34	0-31
SN7445	0-99	0-92	0-86	SN74121	0-36	0-34	0-31
SN7447	0-98	0-96	0-87	SN74123	0-70	0-68	0-64
SN7450	0-15	0-14	0-13	SN74145	0-89	0-85	0-79
SN7451	0-15	0-14	0-13	SN74157	0-87	0-81	0-72
SN7453	0-15	0-14	0-13	SN74175	0-99	0-95	0-84

TTL may be mixed to qualify for quantity prices

DIODES/TRANSISTORS

1N4001	4p	ZTX107	10p	ZTX302	20p	ZTX313	14p
1N4002	5p	ZTX108	8p	ZTX303	16p	ZTX500	14p
1N4003	6p	ZTX109	11p	ZTX310	10p	ZTX501	15p
1N4004	6p	ZTX300	14p	ZTX311	12p	ZTX502	20p
1N4148	4p	ZTX301	15p	ZTX312	12p	ZTX503	16p

MULLARD C280 Polyester 250V Capacitors (radial leads for PCB mounting): 0-01µF, 0-015µF, 3µF, 0-047µF, 3µF, 0-1µF, 4µF, 0-22µF, 5µF, 0-022µF, 0-033µF, 3µF, 0-068µF, 4p, 0-15µF, 4µF, 0-33µF, 7µF.

Send S.A.E. for latest catalogue (includes hints for using TTL, etc.). 10p P. & P. on orders under £2, otherwise POST FREE ALL GOODS SENT FIRST CLASS POST. Discounts (excluding TTL): £5 to £14-99 10%, £15 and over 15%. ALL PRICES INCLUDE VAT.

J. C. JONES

Dept. PE4, 46 Burstallars,
St. Ives, Huntingdon PE17 4XX
(Mail Order only)

12In LONG PERSISTENCE CRT. Full spec. Price £8-50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED LOGIC STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £8-25, P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £6-75, P. & P. 25p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8-85 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of ELECTRONIC GOODIES for £1-50. Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 1 off 4 pole, 2 way, etc.), 50p, P. & P. 20p.

P.C.B. PACKS. S & D. Quantity 2 sq. ft.—no tiny pieces. 50p, P. & P. 20p.

CAPACITOR PACK—50 brand new components, only 50p, P. & P. 20p.

TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base ALL BRAND NEW. 25p the lot, P. & P. 10p.

PHOTOCELL equ. OCP71, 13p each. MULLARD OCP70, 10p each.

DELIVERED TO YOUR DOOR. 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY £4.

MODERN TELEPHONES. Type 706. Two-tone grey, £3-75 each. Two-tone green £3-75 each. Black £3-75 each, P. & P. 35p.

Ideal EXTENSION TELEPHONES with standard GPO type dial, bell and lead coding, £1-75 each, P. & P. 35p.

HANDSETS. Complete with 2 inserts and lead, 75p each, P. & P. 37p.

DIALS. ONLY 75p each, P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1-75, post paid.

BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each, P. & P. 15p; 10-99 10p each, P. & P. 25p; 100-999 7p each, P. & P. free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each, Carr. £2.

1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p, P. & P. 10p.

ALWAYS SOME CHEAP SCOPES AVAILABLE—or build your own. Send for our tube list with a S.A.E.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech College) Tel: Reading 528605/65916



CHINAGLIA DINO - ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

CHINAGLIA




PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS

One example from the big range of sophisticated instruments

CORTINA MINOR 33 RANGE POCKET MULTIMETER

- SENSITIVITY 20,000Ω/VOLT (D.C.), 4,000Ω/VOLT (A.C.).
- ROBUST DIODE PROTECTED PRECISION MOVEMENT.
- 33 RANGES D.C. VOLTS 0-100mV, 1-5V, 5V, 15V, 50V, 150V, 500V, 1,500V; D.C. CURRENT 0-50μA, 5mA, 50mA, 500mA, 2.5A; A.C. VOLTS, 0-7.5V, 25V, 75V, 250V, 750V, 1,500V; A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A; dB RANGES, -10 to +69; AF VOLTS RANGES 0-1,500V; RESISTANCE RANGES 10kΩ, 10MΩ F.S.D. CAPACITANCE RANGES 100μF, IF F.S.D.
- ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT, 2.5%; A.C. VOLTAGE AND CURRENT 3.5%.
- RESISTANCE RANGES POWERED BY INTERNAL BATTERIES.
- COMPACT SIZE: 150 x 85 x 40mm, 350gr.
- CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR.
- PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT.
- FULLY GUARANTEED FOR 12 MONTHS.
- AFTER SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET.
- SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

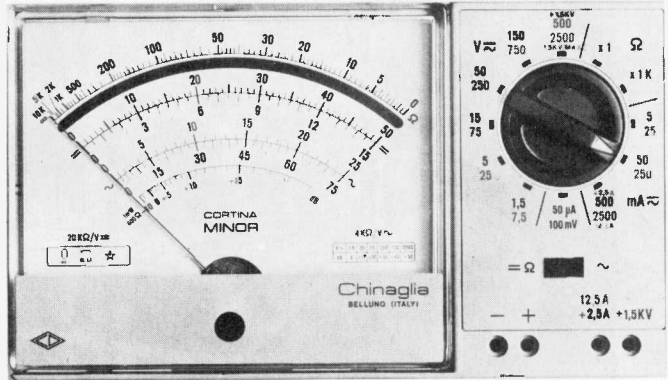

METER PRICE £16.30 (p & p 80p) PROBE £8.80 inclusive of V.A.T.

for further information on the "Cortina Minor" or other instruments from the exciting Chinaglia range write or telephone :-

CHINAGLIA (U.K.) LIMITED

19 Mulberry Walk, London S.W.3.

Telephone 01-352 1897

TRADE ENQUIRIES WELCOMED



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept. EB45, P.O. BOX 156, JERSEY

NAME : _____

ADDRESS : _____

_____ BLOCK CAPS please



Whether your project is electrical or electronic, SCS Components have a complete professional service for the non-professional. We are franchised distributors of Mullard components and Motorola, Ferranti, Signetics, G.I. and Monsanto, too. Our Trade Counter can supply you with all you need, including first-class technical advice. Or simply send cash with your order.

Never before have you been able to get top quality, guaranteed components so quickly, so inexpensively. Send for a free copy of our latest price list.

Try us; we think you'll notice the difference.



SCS Components,
Northfield Industrial Estate, Beresford Avenue,
Wembley, Middlesex HA0 1SD Tel: 01-903 3168

Even Better All Round Sound Reproduction!

Newly designed mat and trim.

Press button speed change.

Brushed Aluminium trim.



Perspex cover.

Easy "hinged-on, hinged-off" movement.

S.A.U.2 Arm with DAMPED lowering device.

Slim line Plinth.

New, Improved BD2 Turntable By *Connoisseur*

Manufactured by: A. R. Sugden & Co. (Engineers) Ltd.
Atlas Mill Road, BRIGHOUSE, Yorkshire HD6 1ER.
Telephone: Brighouse (04847) 2142. Telegrams & Cables: Connoisseur, Brighouse.



TRAMPUS

Electronics Ltd.

WINDSOR, BERKS.
58/60 GROVE RD;
SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 60p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL SPEC DEVICES. CALLERS WELCOME. CATALOGUE/LIST FREE SEND S.A.B. BARCLAYCARD & ACCESS * POST.

Digital Displays



SLA7 RED LED 0.3" DIGIT 0-9DP 89p ea
GREEN/YELLOW £1.40
JUMBO LED 0.6" 747 DISPLAY £2.25 ea.
3015F 0-9DP £1 ea.
ZENON FLASH TUBE £4. Data 15p.

LEDS red 13p

LEDS 209 STYLE ONLY 13p ea
TIL 209 WITH CLIP RED 15p ea
TIL 211 & CLIP GREEN 29p ea
LARGE 0.2" & CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR .2" ORANGE 29p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81p

TEC12 PHOTO AMP/SCMITT/RELAY DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK
8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
WM5311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 DIL14 29p	LM377 2x2Wt2.87
555 TIMER 54p	LM380 2W AF 89p
703 RF/IF 28p	LM381 2xPre £2
709 T099 23p	LM3900 4xOPA69p
709 DIL 14 28p	MC1303 £1.20
710 DIL 14 34p	MC1306 49p
723 Reg. 54p	MC1310&LED £2.65
741 DIL 8 27p	MC1312 SQ £2.10
741 DIL 14 29p	MC1330 89p
741 T099 29p	MC1339 2xPre £1
747 2x741 70p	MC1350 55p
748 DIL 8 33p	NE536 fetOPA £2
7805 5V £1.40	NE540 Driver £1
7812 & 15 £1.40	NE550 2vRef 79p
76013 6W AF £1	NE555 Timer 55p
8038 SIG GEN £3	NE556 2x" £1.20
CA3028 £1	NE560 PLL £3.15
CA3046 55p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.19
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM300 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN76660 IF £1
LM307 OPA 49p	SN76611 IP £1.25
LM308 HIRo 95p	TAD110 aIF £2
LM308K 5V £1.48	TDA810 7WAF 99p
LM372 IF £1.80	ZN414 RX £1.09

SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p. MFC4000B 33p
NE555 TIMER 55p. ZN414 RX £1.09
BC109 9p. 2N3819e 16p. BFY51 15p



79n TTL

7400 GATES 13p	7472/74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7490 52p
7413 SCMITT 31p	7491/2/3/4 59p
7440 BUFFER 14p	74100 74175 £1
7447 DRIVER 89p	74121 32p
7470 & 7472 29p	74123 59p
	74141 (&7441) 73p

TRANSISTORS & DIODES

Price each	MATCHING 16p
AC127 & 128 16p	INS. BUSH SET10p
AC187 & 188 19p	TIP 41 70p
AD149 43p	TIP 42 88p
AD161 & 162 33p	TIP 2955 90p
BC107 & 108 9p	TIP 3055 55p
BC109 10p	TIS43 2x2N2848
BC147/8/9 10p	ZTX109A301 13p
BC157/8/9 12p	1N4001 4p
BC167/8/9 12p	1N4004 & 7 7p
BC177/8/9 18p	1N4148 & 914 4p
BC182/3/4&4L10p	2N697 14p
BC212/3/4&4L11p	2N706&8 11p
BCY70/1/2 17p	2N2646 UJT 32p
BD131 & 132 39p	2N2904 & 5 20p
BFR51 23p	2N2926 roye 8p
BFR50/51 23p	2N3053 17p
BFR88 250V 29p	2N3055 115W 37p
BFY50/1/2 15p	2N3563 & 64 16p
BSX19/20/21 16p	2N3614 49p
MJE2955 90p	2N3702 & 3 9p
MJE3055 65p	2N3704 & 5 10p
MU131 PUT 49p	2N3706 & 7 9p
OA91 OA81 6p	2N3708 & 9 8p
OA81 & OA91 6p	2N3710 & 11 10p
TIP 29 & 30 52p	2N3819E FET 16p
TIP 31 & 32 69p	2N3823E FET 17p
	2N3904/5/6 15p

FULL SELECTION IN OUR FREE LISTS.

NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice £1	1A/50V SCR 36p
PAK B 4 741 OP AMP £1	TAG1/400 55p
PAK C 4 2N3055 £1. D 12 BC109 £1	C106 & 7 SCR D1
PAK E 10 BC182 £1. F 11 2N3704 £1	4A/400V 53p
PAK G 8 BFY51 £1. H 9 2N3819e £1	SC146B TRIAC
PAK J 9 2N3053 £1. K 40 1N914 £1	10A 400V 75p

vero

VERO PINS x36 28p.
COPPER CLAD VEROBOARD 0.1"
2 1/2" x 5" 29p 2 1/2" x 3 1/2" 26p 3 1/2" x 3 1/2" 31p.
3 1/2" x 5" 31p 3 1/2" x 17" £1.50

DIL IC'S BOARDS 6x4 1/2" £1.50
24 way edge connector 60p.
36 way 90P. PLAIN 3 1/2" x 17" £1.
FACE CUTTER 45p. FEC ETCH PAK 50p

DALopen 69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 59p

HEATSINKS

5F/T05 & 18F/T018 5p ea. TV4 15p.
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.

TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf in
10v 5p. 25v 6p. 50v 8p. 2uf/10v 5p.
100 uf/25v 18p. 200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LIN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6p. RESISTORS 14p

SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12p. SOCKETS 10p.
ALL CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v6v or 12v12v
Only £1.34. 100mA type CT 75p.

OIL sockets

TEXAS GOLD
LOW PROFILE ea
8, 14, & 16 PIN 13p

SOLDERCON STRIPS
100 PINS 50p. 1K £3.



BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

BARGAINS FROM OUR FREE CATALOGUE

6th edition. 20 large pages filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy by return. Meanwhile, for prompt delivery order from our ad. this month NOW.

B.P.P. TRANSISTOR PACKS ALL AT 50p EACH

TESTED AND GUARANTEED

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	H39	6	Integrated circuits 4 gates BMC 962. 2 flip flops BMC 945
B81	10	Reed Switches. 1in long 1/4in dia. Highspeed P.O. type	H41	2	BD131/BD132 Complementary Plastic Transistors
H35	100	Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked	H65	4	40361 Type NPN Sil. transistors TO-3 can comp. to H66
H38	30	Short lead Transistors. NPN Silicon Planar types Ex-equipment	H66	4	40362 Type PNP Sil. transistors TO-3 can comp. to H65

UNMARKED AND UNTESTED

B1	50	Germanium Transistors PNP. AF and RF	H34	15	Power Transistors, PNP. Germ. NPN Silicon TO-3 Can
B66	150	Germanium Diodes Min. glass type	H67	10	3819N Channel FET's plastic case type
B88	100	Sil. Diodes min. IN914 glass equivalent to IN4148			

OVER 1,000,000 TRANSISTORS

of all most-wanted types in stock—all at real bargain prices.

PLASTIC POWER TRANSISTORS—2 ranges

In NPN or PNP at shatteringly low prices under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15	Range 2. VCE. Min 40. HFE Min 40
1-12 13-25 26-50	1-12 13-25 26-50
40 watt 20p 18p 18p	40 watt 30p 28p 28p
90 watt 24p 22p 20p	90 watt 35p 33p 30p

Please state NPN or PNP on order.

X-HATCH GENERATOR MK.2



Rotary selector switch provides choice of four patterns—essential for colour TV alignment. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The reinforced fibre-glass case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3in x 5 1/2in x 3in. Operates from three U-2-type batteries (extra).

Ready built unit only **£9.93** Complete kit **£7.93**

MAINS TRANSFORMERS TO SUIT STIRLING SOUND MODULES

Type A—18V/1A (suit SS.103, etc.) £1.50.
Type B—25V/2A (suit SS.110, etc.) £2.00.
Type C—30V/2A (suit SS.140, etc.) £3.25.

SUNDRY

Metrication Pocket Charts 12p. 8 assorted relays £1. Rev. counter device (for cars) £1. UHF/TV Tuner Unit £2.50. LM380 Audio I.C. £1. Technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. Please add 8% to total value of your order including postage. No V.A.T. on overseas orders.
POSTAGE Except where stated, add 15p for postage and packing in U.K. Overseas—add £1. any difference being charged or refunded.
PAYMENT Cash with order. Cheque or money order. Minimum value—£1. You can also pay by ACCESS.
IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

Co Reg No R20719

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.


WRITE ORDER SEPARATELY AND ATTACH COUPON IF NECESSARY

CHALLENGING VALUES!



Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatch and include well printed instructions.

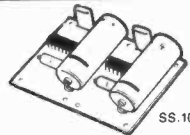

SS.103-3

AMPLIFIER MODULES

Pre-amplifiers; tone control

SS.100 Active tone control unit to provide bass, treble, balance and volume controls


SS.101 Pre-amp for ceramic cartridge, tape and radio

SS.102 Pre-amp for low output magnetic cartridge tape and radio. With R.I.A.A. correction ±1dB at 1kHz

£1.60

£1.60

£2.25

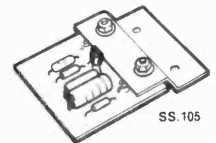

SS.105

POWER AMPLIFIERS

SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6-22. Size 3in x 2in.

SS.103-3 Stereo version of above using one I.C. on each channel

SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt run output, two make a good stereo amp. Size 2 1/2in x 1 1/2in.

SS.110 Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26-32V.

SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. T.H.D. better than 0.2%. Power requirements—45V d.c. With 0-15in centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms


£1.75

£3.25


£1.95

£2.40

£3.60

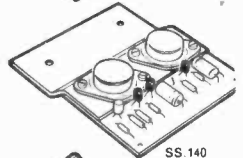

SS.140

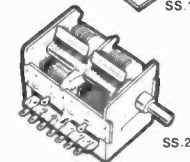

SS.201

TUNER MODULES

SS.201 Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V


SS.202 I.F. stage (with I.C.). Pre-tuned A.F.C. connection. Operates from 4.5-14V

SS.203 Stereo Decoder. Designed essentially for use with SS.201 and SS.202. This module can also be used on most mono F.M. tuners. A L.E.D. may be attached. Operating voltage 9-16V d.c.

£6.25

£5.25

£5.62

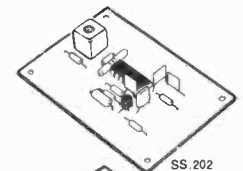


SS.202


POWER SUPPLY STABILISER

SS.300 Add this to an unregulated supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving and very reliable.

£3.25

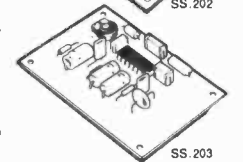

SS.203

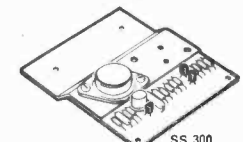

SS.300

- * ALL MODULES TESTED AND GUARANTEED
- * WITH WELL PRINTED INSTRUCTIONS
- * FULL RANGES OF ANCILLARY COMPONENTS AVAILABLE—SEE CATALOGUE

Have you had your FREE CATALOGUE?

To BI-PRE-PAK, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose

inc. V.A.T.

NAME

ADDRESS

PE4

A TECHNOLOGICAL MIRACLE DEVELOPED BY U.S. SPACE SCIENTISTS!

NOW YOU CAN JUDGE FOR YOURSELF WHETHER OR NOT THIS

MAKES VIRTUALLY EVERY OTHER TYPE OF WATCH IN THE WORLD OBSOLETE!

THE GREATEST HOROLOGICAL ADVANCE SINCE THE INVENTION OF THE CHRONOMETER

THE SYSTEM EXCELLED IN ACCURACY ONLY BY THE ATOMIC FREQUENCY STANDARD!



LIQUID CRYSTAL QUARTZ

WRIST WATCH WITH CONTINUOUS 'COMPUTER DIGITAL READ OUT'

The space-age system FEATURED ON TV!

SAVE UP TO £140!

ELSEWHERE YOU COULD PAY UP TO £200 OR MORE FOR THIS INCREDIBLE NEW SPACE-AGE TYPE OF WATCH!

OUR WORLD SHATTERING PRICE ONLY

£57.95

REGISTERED POST PACK ETC. 50p

FROM WORLD FAMOUS MAKERS! The greatest Watch offer since time began! Everyone who sees it is fascinated by it! It's unbelievable! Continuous digital reading—hours and minutes AND second Pulsator miraculously transmits before your very eyes like a continuously changing TV Picture! A new "dimension" in time! Now YOU can join the elite few—the proud owners of a watch that is utterly different from any other timepiece you've ever known! **THEY'RE NEWS! THE WATCH OF TOMORROW TODAY!** AND you buy at a price that's just a fraction of what you could have paid! But remember—you can only buy at this amazing price from Shopertunities. ★ **UNBELIEVABLY ACCURATE TO WITHIN SECONDS A YEAR!** The system excelled in accuracy only by the Atomic frequency standard! Now TIM can phone you for a time check! ★ **NO MOVING PARTS!** ★ **NO MAINTENANCE!** ★ **ABSOLUTELY SILENT!** ★ **BUILT TO GIVE A LIFE-TIME OF SERVICE!** ★ **18CT GOLD PLATED CASE!** ★ **BRAND SPANKING NEW ADVANCE 1975 MODEL!** WRITTEN GUARANTEE. Developed from the fantastic "space-age" techniques that first put men on the moon, this incredible watch is based on the natural action of Quartz Crystal, that vibrates approx. 32,768 times per second! A veritable miracle of micro-circuitry! An "electronic brain" with 1500 Transistors! You could even spend £400 or more for a Quartz Crystal watch! OUR fantastic cash price for this masterpiece is ONLY £57.95, registered post, pack, etc. 50p, including expensive matching adjustable safety bracelet and presentation casket. Send quickly and test for yourself on 7 days' mail order approval from receipt of goods. **REFUND IF NOT DELIGHTED.** Or send only £12.50 deposit, balance by 6 monthly payments of £9.47 (total credit price £69.32 plus post). Please hurry! Limited quantity! THIS is the greatest investment you'll EVER make! Or call at either store and see this fabulous watch for yourself! At this price you just can't lose!

Order by post to Uxbridge Road, or call at either store
Callers: ACCESS & BARCLAY CARDS ACCEPTED
Bargains galore at both stores—
COMMERCIAL TRAVELLERS NOTE: Merchandising office at Holborn.

SEND OR CALL

SHOPERTUNITIES LTD

Dept. PE/41, 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

PEMINISONIC

COMPONENT KITS NOW AVAILABLE. 4½p STAMP BRINGS DETAILS.

TRANSISTORS
BC204 11p
BC209C 11p
BC182 10p
BC184 11p
BC212 11p
BC214 15p
BC213 15p
BC213L 15p
ZTX300 15p
ZTX500 17p
2N2484 24p
2N2904 30p
2N2905 27p
2N2219 22p
2N3054 100p

VOLTAGE REGULATORS
µA7815 220p
723 180p

MINISONIC P.C.B.
118 x 295mm best quality epoxy-glass, roller tinned. Complete with overlay details and instructions.

MINISONIC COMPONENT KITS
V.C.O. (2 required) £3-85
V.C.F. (1 required) £4-98
ES/V.C.A. (2 required) £5-70
Voltage Ref. £0-57
Ring. Mod. (1 required) £4-14
Noise Gen. (1 required) £1-86
Kbd. Control (1 required) £4-16
HF Osc. and Det. £1-93
Power Amps £2-61

OP. AMPS
709/8 Dip 39p
710/TO5 39p
741 37p
748 48p
FETMOPA 450p

ARRAYS
ML3046P 75p
CA3096AE 120p

V.A.T.
Please add 8% to final total of order

All above prices are for single kits of each type and include VAT, P. & P. Full details are included in lists.

DIODES
IN5401 21p
IN914 5p
BA148 25p
1S150 10p
1GP7 12p

T.T.L.
7402N 38p
7410PC 24p
7420N 24p
7430PC 23p
7473N 48p
7475N 75p
7476N 49p
7489N 660p
7493PC 89p
74121J 85p
74122N 80p
74123N 144p
74150N 210p

CONSTANTAN WIRE
0.03 ohms/cm as specified for the POWER SLAVES. 20cm lengths 10p

Miscellaneous Items
5 way 180° DIN sockets 27p
5 way 180° DIN plugs 34p
Battery connectors 9p/pair
Hook up wire, 36 colours, ¼ metre of each 70p
Min. DPDT toggle switch £1.20

NOISE DIODES
Z1J 60p
Z1M 120p

RESISTORS
2% METAL
OXIDE 15p for 5
5% CARBON
FILM 9p for 5

INTRODUCING THE MINISONIC C20 AUDIO CASSETTE
£1.15 Inc. VAT, P. & P.

SAVE BY PURCHASING A COMPLETE SET OF KITS AS DETAILED TOGETHER WITH SWITCH, BATTERY CONNECTORS, HOOK-UP WIRE AND P.C.B.

Price inc. VAT & U.K. Postage £43

EATON AUDIO
P.O. BOX 3, ST. NEOTS HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P.&P. Otherwise please add 10p in the £1.



CALCULATORS

BUY FROM THE SPECIALISTS UP TO 45% OFF RRP



All guaranteed 1 year Money refunded on goods returned within 7 days.

VATMAN £14.91 + VAT

Model	Our Price	Functions
Decimo Vatman	14-91	P, [A], R, G, 8D, E, F, K4, H, I, J, C, L5, B, N
Decimo Vatman	16-91	P, [A], R, G, 8D, E, F, K4, H, I, J, C, L5, BM, N
Decimo Memory	23-88	P, M, [A], R, G, 8D, E, F, K4, H, I, J, C, L5, BM, N, [W]
Decimo Slide rule	25-88	P, M, [A], R, G, 8D, E, F, K4, H, I, J, I, I, C, L5, BM, N
Decimo Scientific	38-95	P, M, 8D, A, E, K4, C, BM, Integrals, etc.
Decimo 9202	39-83	S, M, [A], R, G, 8D, E, F, K2, H, I, J, L5, BM, N
Anite 811	39-95	P, M, [A], R, 8D, E, F, K4, H, I, C, B, N
Bohn Omnitrex*	44-95	T, M, [A], R, G, 8D, E, F2, K4, H, I, C, BM, M
Bohn Omnitrex SQ1*	50-95	T, M, [A], R, G, 8D, E, F2, K2, G, [H], [X], [I], C, M, V, U
Bohn Metric*	59-22	T, W, [A], R, G, 8D, E, F, K2, H, I, M, C, V also 12 conversions in/decim, ft/metres, yds/metres, miles/km, ozs/ccs, gis/litres, gals/ltres, F/°C, °ozs/grams, lbs/kg, area measurement, cubic measurement.
Bowmar MX75*	39-97	T, M, [A], R, 8D, E, F, K4, H, I, J, C, V, N
Bowmar MX100*	65-99	T, M, 8D, E, F, K4, C, V, J, true scientific 20 functions for algebra, trigonometry, logs, calculus, integrals, etc.
Special Import	19-90	P, M, [A], R, 8D, E, F2/4, K4, M, I, J, C, V, N Print-Outs
Ricomac 1000P	81-97	2 colour print-out, A, 10D, F15 K4, M, sub total, acc = X buffer

Code: A = percentage, B = battery (mains adaptor extra), BM = battery (mains adaptor incl.), C = carrying case, D = digits, E = +, -, x, ÷, F = floating decimal point, F/S = floating point and select, F2 = floating point and 2 places, F7 = floating point and 7 places, G = green display, H = x², I = x, J = x, K = constant X, L = constant x, M = L5 = 50 hr. battery life, L10 = 100 hr. battery life, M = memory, N = negative entry, P = pocket, R = prorating, S = desk model, T = hand and desk, U = display blanking, V = rechargeable, W = exchange, X = Vx, [] = extra separate keys, + = positive feel.
45p P. & P. and please add 8% VAT on all total prices.

BARCLAY ELECTRONICS
STANLEY HOUSE, 1115 FINCHLEY ROAD LONDON, NW11

INTERNATIONAL ELECTRONICS UNLIMITED

ORDER DIRECT FROM THE U.S. AND SAVE

SHIPMENT MADE WITHIN 3 DAYS FROM RECEIPT OF ORDER VIA AIR MAIL - POSTAGE PAID

TTL



7400	£ 0.11 p	7448	£ 0.80 p	74150	£ 0.75 p
7401	11	7450	12	74151	60
7402	11	7451	13	74153	71
7403	11	7453	13	74154	1.05
7404	13	7454	14	74155	95
7405	13	7460	11	74156	71
7406	22	7464	21	74157	71
7407	22	7465	21	74161	95
7408	14	7472	22	74163	1.05
7409	14	7473	26	74164	1.25
7410	11	7474	26	74165	1.25
7411	16	7475	41	74166	1.15
7413	35	7476	26	74173	95
7415	22	7483	70	74175	95
7416	22	7485	80	74176	95
7417	22	7486	24	74177	85
7420	11	7489	1.50	74180	80
7422	22	7490	44	74181	2.50
7423	22	7491	71	74182	80
7425	22	7492	44	74184	1.55
7426	23	7493	44	74185	1.45
7427	22	7494	49	74190	95
7430	12	7495	49	74191	95
7432	22	7496	55	74192	90
7437	25	74100	1.25	74193	85
7438	21	74105	60	74194	95
7440	11	74107	27	74195	80
7441	60	74112	32	74196	1.00
7422	55	74122	50	74197	75
7443	55	74123	55	74198	1.70
7444	60	74125	50	74199	1.70
7445	75	74126	50	74200	3.90
7446	85	74181	68		
7447	80	74145	75		

LOW POWER

74L00	£ 0.16 p	74L51	£ 0.16 p	74L90	£ 0.93 p
74L02	16	74L55	18	74L91	80
74L03	16	74L71	18	74L93	89
74L04	18	74L72	27	74L95	89
74L06	18	74L73	38	74L98	1.53
74L10	16	74L74	38	74L164	1.53
74L20	16	74L78	44	74L165	1.53
74L30	16	74L85	85		
74L42	89	74L86	38		

HIGH SPEED

74H00	£ 0.16 p	74H21	£ 0.16 p	74H55	£ 0.20 p
74H01	16	74H22	18	74H60	21
74H04	16	74H30	18	74H61	21
74H08	16	74H40	16	74H62	20
74H10	16	74H50	16	74H74	32
74H11	16	74H52	18		
74H20	16	74H53	20		

8000 SERIES

8091	£ 0.33 p	8214	£ 0.93 p	8811	£ 0.38 p
8092	33	8220	93	8812	60
8095	76	8230	1.42	8822	1.42
8121	49	8520	71	8830	1.42
8123	88	8551	91	8831	1.42
8130	1.20	8552	1.37	8836	27
8200	1.42	8554	1.37	8880	73
8210	1.92	8810	44		

9000 SERIES

9002	£ 0.21 p	9309	£ 0.49 p	9601	£ 0.54 p
9301	63	9312	49	9602	49

Data sheets supplied only on re-quest. Add 25p ea. for data sup-plied on items less than 50p ea.

CMOS

74C00	£ 0.21 p	74C74	£ 0.63 p	74C162	1.78 p
74C02	30	74C76	93	74C163	1.78
74C04	41	74C107	82	74C164	1.92
74C08	41	74C151	1.59	74C173	1.59
74C10	36	74C154	1.92	74C195	1.65
74C20	36	74C157	1.20	80C95	82
74C42	1.18	74C180	1.78	80C97	82
74C73	85	74C181	1.78		

INTRODUCTORY SPECIALS

5001	12 DIG 4 funct fix dec	Calculator	£ 1.61 p	1103	256 bit RAM MOS	Memory	£ 1.61 p
5002	Same as 5001 exc btry pwr		2.71	5260	1024 bit RAM		1.61
5005	12 DIG 4 funct w/mem		3.81	5261	1024 bit RAM		4.36
5725	8 DIG 4 funct chain & dec		1.23	5282	2048 bit RAM		3.81
5738	8 DIG 5 funct K & Mem		2.44	2102	1024 bit static RAM		10.88
5739	9 DIG 4 funct (btry sur)		2.71	5203	2048 bit UV Eras Prom		
5311	28 pin BCD 6 dig mux	Clock	2.71	HP50827414	4 digit common cathode	Led	1.51
5312	24 pin 1 pps BCD 4 dig mux		2.71		Flts 14 pin DIP - .11 bubble lens		54
5313	28 pin 1 pps BCD 6 dig mux		2.71	MAN 7	Red 7 seg 270"		1.92
5314	24 pin 6 dig mux		1.50	MAN 66	Red 6" spaced seg		2.47
5316	40 pin alarm 4 dig		3.26	MAN 6	Red 6" solid seg		35.36
				8008	8 bit CPU prime quality		

10% OFF ON ORDERS OVER £ 10

MEMORIES w/data

1101	256 bit RAM MOS	£ 0.96 p
1103	1024 bit RAM MOS	2.72
5203	2048 bit erasable PROM	13.68
5260	1024 bit RAM Low Power	2.16
7489	64 bit RAM TTL	1.50
8223	Programmable ROM	2.72

CALCULATOR & CLOCK CHIPS w/data

5001	12 DIG 4 funct fix dec	£ 2.17 p
5002	Same as 5001 exc btry pwr	4.26
5005	12 DIG 4 funct w/mem	4.63
MM5725	8 DIG 4 funct chain & dec	1.52
MM5738	18 pin 6 DIG 4 funct	2.72
MM5739	8 DIG 5 funct K & Mem	4.36
MM5738	9 DIG 4 funct (btry sur)	3.81
MM5311	28 pin BCD 6 dig mux	3.81
MM5312	24 pin 1 pps BCD 4 dig mux	3.81
MM5313	28 pin 1 pps BCD 6 dig mux	4.90
MM5314	24 pin 6 dig mux	4.90
MM5316	40 pin alarm 4 dig	4.90

LED & OPTO ISOLATOR

MV10B	Red TO 18	£ 0.14 p
MV150	Axial leads	8
MV5020	Jumbo Vis. Red (Red Dome)	18
	Jumbo Vis. Red (Clear Dome)	18
ME4	Infra red diff. dome	18
MAN 1	Red 7 seg. 270"	1.38
MAN 2	Red alpha num. 32"	2.72
MAN 4	Red 7 seg. 190"	1.18
MAN 5	Green 7 seg. 270"	1.62
MAN 6	6" high solid seg.	3.81
MAN 7	Red 7 seg. 270"	74
MAN 8	Yellow 7 seg. 270"	2.17
MAN 64	4" high solid seg.	2.45
MAN 66	6" high spaced seg.	2.55
DL 707	Red 7 seg. 3"	1.18
MCT2	Opto-iso transistor	38

DTL

930	10 p	937	10 p	949	10 p
932	10	944	10	962	10
936	10	946	10	963	10

4000 SERIES RCA EQUIVALENT

CD4001	£ 0.31 p	CD4013	£ 0.66 p	CD4023	£ 0.31 p
CD4009	47	CD4016	69	CD4025	31
CD4010	47	CD4017	62	CD4027	74
CD4011	31	CD4019	74	CD4030	52
CD4012	31	CD4022	1.50	CD4035	1.56

LINEAR CIRCUITS

300	Pos V Reg (super 723)	TO-5	£ 0.43 p
301	Hi Perf Op Amp	mDIP TO-5	18
302	Volt follower	TO-5	43
304	Neg V Reg	TO-5	49
305	Pos V Reg	TO-5	52
307	Op AMP (super 741)	mDIP TO-5	20
308	Micro Pwr Op Amp	mDIP TO-5	60
309K	5V 1A regulator	TO-3	3
310	V Follower Op Amp	TO-5 mDIP	65
311	Hi perf V Comp	mDIP TO-5	58
319	Hi Speed Dual Comp	DIP	71
320	Neg Reg 5.2, 12, 15	TO-3	74
322	Precision Timer	DIP	1.07
324	Quad Op Amp	DIP	92
339	Quad Comparator	DIP	92
340T	Pos Volt Reg (6V, 8V, 12V, 15V, 18V, 24V)	TO-220	1.07
		TO-5 or DIP	65
370	AGC/Squelch AMPL	DIP	44
372	AF-IF Strip detector	DIP	1.78
373	AM/FM/SSB Strip	mDIP	33
376	Pos. V. Reg	DIP	1.47
377	2w Stereo amp	mDIP	81
380	2w Audio amp	mDIP	89
380 8	Low Audio amp	DIP	98
381	Lo Noise Dual preamp	DIP	98
382	Lo Noise Dual preamp	DIP	98
550	Prec V Reg	DIP	44
555	Timer	mDIP	1.50
560	Phase Locked Loop	DIP	1.50
562	Phase Locked Loop	DIP	1.50
566	Phase Locked Loop	DIP TO-5	1.45
566	Function Gen	mDIP TO-5	1.50
567	Tone Decoder	mDIP	1.62
709	Operational AMPL	TO-5 or DIP	16
710	Hi Speed Volt Comp	DIP	21
711	Dual Difference Compar	DIP	16
723	V Reg	DIP	38
739	Dual Hi Perf Op Amp	DIP	85
741	Comp Op Amp	mDIP TO-5	20
747	Dual 741 Op Amp	DIP or TO-5	44
1304	Freq Adj 741	mDIP	21
1308	FM Mulx Stereo Demod	DIP	66
1307	FM Mulx Stereo Demod	DIP	45
1458	Dual Comp Op Amp	mDIP	38
LH2111	Dual LM 211 V Comp	DIP	1.07
3065	TV-FM Sound System	DIP	38
3075	FM Det LMTR & Audio preamp	DIP	44
3900	Quad Amplifier	DIP	33
7524	Core Mem Sense AMPL	DIP	1.04
7534	Core Mem Sense Amp	DIP	1.42
8864	9 DIG Led Cath Dvr	DIP	1.37
75451	Dual Peripheral Driver	mDIP	21
75452	Dual Peripheral Driver	mDIP	21
75453	(35 1) Dual Periph. Driver	mDIP	21
75491	Quad Seq Driver for LED	DIP	50
75492	Hex Digit Driver	DIP	55

Data sheets supplied only on re-quest. Add 25p ea. for data sup-plied on items less than 50p ea.

ALL ITEMS ARE NEW, MARKED, TESTED FUNCTIONAL - SATISFACTION GUARANTEED

The prices as listed are in British pounds and pence. Send bank cheque (U.S. funds) with order. If international postal money order is used, send receipt with order. Minimum order £2-50p.

INTERNATIONAL ELECTRONICS UNLIMITED
P.O. BOX 1708 MONTEREY, CA. 93940 USA
PHONE (408) 659-3171



The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107	22	AD161 and	BC150	20	BD131	55	BF180	33	MAT120	21	T1843	33	2N1309	26	2N2926B	11	2N3906	30
AC113	20	AD162MP 75	BC151	22	BD132	66	BF181	33	MAT121	22	UT46	30	2N1613	22	2N3010	77	2N4058	13
AC115	22	ADT140	BC152	19	BD133	72	BF182	44	MJE2955	95	ZN414	£1.20	2N1711	22	2N3011	16	2N4059	11
AC117K	32	AF114	BC153	31	BD134	44	BF183	44	MJE3055	62	2G301	21	2N1889	35	2N3053	19	2N4060	13
AC122	13	AF115	BC154	38	BD135	44	BF184	28	MJE3440	55	2G302	21	2N1890	50	2N3054	51	2N4061	13
AC125	19	AF116	BC157	20	BD136	50	BF185	30	MPE102	48	2G303	21	2N1893	40	2N3055	45	2N4062	13
AC126	19	AF117	BC158	13	BD138	55	BF187	30	MPE104	41	2G304	27	2N2147	79	2N3391	16	2N4284	19
AC127	20	AF118	BC159	13	BD139	61	BF188	44	MPE105	47	2G306	44	2N2148	63	2N3391A	18	2N4285	19
AC128	20	AF124	BC160	50	BD140	66	BF194	18	OC19	39	2G308	39	2N2149	39	2N3392	16	2N4286	19
AC132	16	AF125	BC161	55	BD155	88	BF195	15	OC20	70	2G309	39	2N2160	69	2N3392	16	2N4287	19
AC134	25	AF126	BC162	13	BD172	72	BF196	16	OC22	52	2G339	22	2N2192	39	2N3393	16	2N4288	19
AC137	16	AF127	BC163	13	BD173	66	BF197	16	OC23	54	2G339A	18	2N2193	39	2N3394	16	2N4289	19
AC141	20	AF128	BC169	13	BD174	72	BF198	16	OC24	62	2G344	18	2N2194	39	2N3395	19	2N4290	19
AC141K	32	AF128	BC170	13	BD178	72	BF199	16	OC25	42	2G345	18	2N2217	24	2N3402	23	2N4291	19
AC142	20	AF129	BC171	16	BD179	72	BF200	16	OC25	42	2G345	18	2N2218	24	2N3403	23	2N4292	19
AC142K	28	AF180	BC172	16	BD180	77	BF201	16	OC26	55	2G371B	13	2N2219	24	2N3404	31	2N4293	19
AC151	17	AF181	BC173	16	BD185	72	BF202	16	OC27	55	2G373	19	2N2220	24	2N3405	46	2N4294	19
AC154	22	AF186	BC174	16	BD186	72	BF203	16	OC30	46	2G374	19	2N2221	24	2N3414	17	2N5172	13
AC155	22	AF239	BC175	16	BD187	77	BF204	16	OC36	55	2G377	33	2N2222	22	2N3416	17	2N5294	60
AC156	22	AL102	BC176	21	BD187	77	BF205	16	OC41	22	2G378	18	2N2268	19	2N3417	31	2N5457	35
AC157	27	AL103	BC178	21	BD189	83	BF206	16	OC42	27	2G381	18	2N2369	16	2N3418	31	2N5458	35
AC158	22	AY26	BC179	21	BD190	83	BF207	16	OC42	27	2G382	18	2N2369A	16	2N3419	31	2N5459	35
AC166	22	AY27	BC180	27	BD195	94	BF208	16	OC45	14	2G401	19	2N2411	27	2N3614	74	2N6121	75
AC167	22	AY28	BC181	27	BD196	94	BF209	16	OC70	11	2G414	33	2N2412	27	2N3615	82	2830	55
AC168	22	AY29	BC182	16	BD197	99	BF210	16	OC71	11	2G417	28	2N2413	27	2N3616	82	2830a	46
AC169	16	AY50	BC182L	16	BD198	99	BF211	16	OC72	16	2N388	39	2N2711	23	2N3646	10	28302	46
AC176	22	AY51	BC183	16	BD199	99	BF212	16	OC74	16	2N388A	61	2N2712	23	2N3702	13	28303	61
AC177	27	AY52	BC183L	16	BD200	£1.05	BF213	16	OC75	17	2N404	22	2N2714	23	2N3703	13	28304	77
AC178	31	AY53	BC184	22	BD201	£1.05	BF214	16	OC75	17	2N404A	31	2N2904	19	2N3704	14	28305	86
AC179	31	AY54	BC184L	22	BD205	£1.05	BF215	16	OC77	28	2N524	22	2N2904A	19	2N3705	13	28306	86
AC180	22	AY55	BC186	31	BD206	£1.05	BF216	16	OC81	17	2N527	54	2N2905	23	2N3706	13	28307	86
AC180K	32	AY56	BC187	31	BD207	£1.05	BF217	16	OC81D	17	2N528	46	2N2905A	23	2N3707	14	28321	62
AC181	22	AY57	BC188	22	BD208	£1.05	BF218	16	OC82	17	2N529	50	2N2906	17	2N3708	09	28322	46
AC181K	32	AY58	BC189	12	BDY20	£1.10	BF219	16	OC82D	17	2N529	50	2N2906A	17	2N3709	10	28322A	46
AC182	24	AY59	BC212L	14	BF115	27	BF220	16	OC83	22	2N697	15	2N2907	22	2N3710	10	28323	62
AC187K	25	BC107	BC213L	14	BF117	50	BF221	16	OC83	22	2N698	27	2N2907A	24	2N3711	10	28324	77
AC188	24	BC108	BC214L	18	BF118	77	BF222	16	OC89	22	2N698	27	2N2908	39	2N3712	11	28325	77
AC188K	25	BC109	BC225	28	BF119	77	BF223	16	OC129	22	2N706	28	2N2924	16	2N3820	55	28326	77
AC197	28	BC113	BC226	32	BF121	50	BF224	16	OC129	22	2N706A	28	2N2925	16	2N3821	39	28327	77
AC198	22	BC114	BC301	30	BF122	55	BF225	16	OC171	28	2N708	13	2N2926G	14	2N3823	31	28327	77
AC199	22	BC115	BC302	30	BF123	55	BF226	16	OC200	28	2N711	33	2N2926H	14	2N3903	31	28327	77
AC200	22	BC116	BC303	35	BF125	61	BF227	16	OC201	31	2N713	39	2N2926I	11	2N3904	33	40364	44
AC201	22	BC117	BC304	40	BF127	55	BF228	16	OC203	28	2N718	27	2N2926J	11	2N3905	31	40362	50
AC202	22	BC118	BC340	34	BF153	50	BF229	16	OC204	28	2N718A	55						
AC203	22	BC119	BC450	40	BF155	77	BF230	16	OC205	39	2N727	31	A1119	9	BY124	13	CG62	
AC208	21	BC120	BCY30	27	BF157	61	BF231	16	OC209	44	2N743	22	A1120	9	BY126	18	(OA91Ea)	6
AC209	39	BC125	BCY31	29	BF158	61	BF232	16	OC210	48	2N744	22	A1121	9	BY127	17	CG61	
AC210	31	BC126	BCY32	24	BF159	61	BF233	16	OC211	48	2N744	22	A1122	9	BY128	17	(OA70-A70)	
AC231	31	BC132	BCY33	24	BF159	61	BF234	16	OC212	48	2N744	22	A1123	9	BY129	17		
AC232	23	BC133	BCY34	28	BF159	61	BF235	16	OC213	48	2N744	22	A1124	9	BY130	17		
AC233	23	BC134	BCY35	28	BF159	61	BF236	16	OC214	48	2N744	22	A1125	9	BY131	17	OA5	39
AC234	23	BC135	BCY36	28	BF159	61	BF237	16	OC215	48	2N744	22	A1126	9	BY132	17	OA5 short	
AC235	23	BC136	BCY37	28	BF159	61	BF238	16	OC216	48	2N744	22	A1127	9	BY133	17	leads	23
AC236	23	BC137	BCY38	28	BF159	61	BF239	16	OC217	48	2N744	22	A1128	9	BY134	17	OA10	15
AC237	23	BC138	BCY39	28	BF159	61	BF240	16	OC218	48	2N744	22	A1129	9	BY135	17	OA10	15
AC240	19	BC137	BCY40	28	BF159	61	BF241	16	OC219	48	2N744	22	A1130	9	BY136	17	OA10	15
AC241	20	BC139	BCY41	28	BF159	61	BF242	16	OC220	48	2N744	22	A1131	9	BY137	17	OA10	15
AC244	39	BC140	BCZ10	22	BF164	44	BF243	16	OC221	48	2N744	22	A1132	9	BY138	17	OA10	15
AD130	42	BC141	BCZ11	28	BF165	44	BF244	16	OC222	48	2N744	22	A1133	9	BY139	17	OA10	15
AD140	53	BC142	BCZ12	28	BF167	24	BF245	16	OC223	48	2N744	22	A1134	9	BY140	17	OA10	15
AD142	53	BC143	BCZ13	28	BF173	24	BF246	16	OC224	48	2N744	22	A1135	9	BY141	17	OA10	15
AD143	42	BC144	BCZ14	28	BF173	24	BF247	16	OC225	48	2N744	22	A1136	9	BY142	17	OA10	15
AD149	55	BC147	BD115	68	BF176	24	BF248	16	OC226	48	2N744	22	A1137	9	BY143	17	OA10	15
AD161	39	BC148	BD116	68	BF177	39	BF249	16	OC227	48	2N744	22	A1138	9	BY144	17	OA10	15
AD162	39	BC149	BD123	72	BF148	33	BF250	16	OC228	48	2N744	22	A1139	9	BY145	17	OA10	15
			BD124	76	BF179	33	BF251	16	OC229	48	2N744	22	A1140	9	BY146	17	OA10	15

DIODES AND RECTIFIERS

BY124	13	CG62	
BY126	18	(OA91Ea)	6
BY127	17	CG61	
BY128	17	(OA70-A70)	
BY130	17		
BY133	23	OA5	39
BY164	55	OA5 short	
BYX38/30		leads	23
BA148	16	OA10	15
BA154	13	OA10	15
BA155	16	OA10	15
BA156	16	OA10	15
BA173	28	OA10	15
BY100	17	OA10	15
BY101	13	OA10	15
BY102	13	OA10	15
BY103	13	OA10	15
BY104	13	OA10	15

LINEAR I.C.'s

Type No.	1	25	100+
72702	0.50	0.48	0.45
72705	0.25	0.23	0.20
72709F	0.20	0.19	0.20
72710	0.35	0.33	0.30
72741	0.30	0.29	0.28
72741C	0.28	0.27	0.26
72741P	0.30	0.29	0.28
72747	0.38	0.36	0.34
72748P	0.35	0.34	0.33
SL201C	0.59	0.45	0.40
SL701C	0.50	0.45	0.40
SL702C	0.50		

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2O417 AF117

All 64p each pak

ND120 NIXIE DRIVER TRANSISTOR.
Suitable replacement for BX821, C407, 2N1893 120vcb.

1	25	100+
0-19	0-17	0-18

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 6p each. Any Quantity.

GP100 TO3 METAL CASE SILICON GERMANIUM
V_{beo}=80V. V_{ceo}=50V. I_C=10 amps. P_{tot}=30W. h_{fe}=30-170. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0-48	0-44	0-40

GP300 TO3 METAL CASE SILICON GERMANIUM
V_{beo}=100V. V_{ceo}=80V. I_C=15 amps. P_{tot}=115W. h_{fe}=20. 100T=1MHz. Suitable replacement for 2N3055, BDY11 or BDY20.

1	25	100+
0-55	0-53	0-51

NEW 9th EDITION
over 300 pages

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. £2.30 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18
SIM. TO 2N708/8. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, DCV70. When ordering please state preference NPN or PNP.

20	For	0-54
60	For	1-08
100	For	1-92
500	For	8-25
1000	For	14-30

SIL. G.P. DIODES

300mW	30	0-54
40PIV(Min.)	100	1-08
Sub-Min.	500	5-50

Full Tested 1,000 9-90
Ideal for Organ Builders.

ADI61/162

PNP M/P COMP. GERM. TRANS. OUR LOWEST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO AND ELECTRONIC COMPONENTS ADVERTISEMENTS PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 9p ea. 11W (Top-Hat) 18p ea. 10W (SO-10 Stud) 32p ea.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q 1 20	Red spot transistors pnp	0-54
Q 2 16	White spot R.F. transistors pnp	0-54
Q 3 4	OC77 type transistors	0-54
Q 4 6	Matched transistors OC44/45/81/81D	0-54
Q 5 4	OC75 transistors	0-54
Q 6 5	OC72 transistors	0-54
Q 7 4	AC128 transistors pnp high gain	0-54
Q 8 4	AC126 transistors pnp	0-54
Q 9 7	OC81 type transistors	0-54
Q10 7	OC71 type transistors	0-54
Q11 2	AC127/128 Complementary pairs pnp/ppn	0-54
Q12 3	AF115 type transistors	0-54
Q13 3	AF117 type transistors	0-54
Q14 3	OC171 H.F. type transistors	0-54
Q15 7	2N2926 Sil. Epoxy transistors mixed colours	0-54
Q17 5	npn 2 x ST.141 & 3 x ST.140	0-54
Q18 4	MADT'82 x MAT 100 & 2 x MAT 121	0-54
Q19 3	MADT'82 x MAT 101 & 1 x MAT 121	0-54
Q20 4	OC44 Germanium transistors A.P.	0-54
Q21 4	AC127 npn Germanium transistors	0-54
Q22 20	NKT transistors A.F. R.F. coded.	0-54
Q23 10	OA202 Silicon diodes sub-min.	0-54
Q24 8	OA81 diodes	0-54
Q25 15	IN914 Silicon diodes 75PIV 75mA	0-54
Q26 8	OA95 Germanium diodes sub-min IN69	0-54
Q27 2	10A 600 PIV Silicon rectifiers 18425R	0-54
Q28 2	Silicon power rectifiers BYZ13	0-54
Q29 4	Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-54
Q30 7	Silicon switch transistors 2N706 npn	0-54
Q31 6	Silicon switch transistors 2N708, npn	0-54
Q32 3	nnp Silicon transistors 2 x 2N1131, 1 x 2N1132	0-54
Q33 3	Silicon npn transistors 2N1711	0-54
Q34 7	Silicon npn transistors 2N2369, 500MHz (code P397)	0-54
Q35 3	Silicon pnp TO-5. 2 x 2N2904 & 1 x 2N2905	0-54
Q36 7	2N3646 TO-18 plastic 300MHz npn	0-54
Q37 3	2N3055 npn Silicon transistors	0-54
Q38 5	nnp transistors 3 x 2N3703, 2 x 2N3702	0-54

555IC 65p each

ALL PRICES INCLUDE V.A.T.

MAMMOTH I.C. PAK

APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS' FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR AND AUDIO AMPLIFIERS. MANY CODED also SOME UNKNOWN TYPES—YOU TO IDENTIFY.

PAK NO. M.I.C. 200

PRICE £1-25 per PAK including P. & P. and VAT

INTEGRATED CIRCUIT PAKS

Manufacturers' "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0-54	UIC46	= 5 x 7446	0-54	UIC86	= 5 x 7486	0-54
UIC01	= 12 x 7401	0-54	UIC48	= 6 x 7448	0-54	UIC90	= 5 x 7490	0-54
UIC02	= 12 x 7402	0-54	UIC50	= 12 x 7450	0-54	UIC91	= 5 x 7491	0-54
UIC03	= 12 x 7403	0-54	UIC51	= 12 x 7451	0-54	UIC92	= 5 x 7492	0-54
UIC04	= 12 x 7404	0-54	UIC53	= 12 x 7453	0-54	UIC93	= 5 x 7493	0-54
UIC05	= 12 x 7405	0-54	UIC54	= 12 x 7454	0-54	UIC94	= 5 x 7494	0-54
UIC06	= 8 x 7406	0-54	UIC56	= 12 x 7456	0-54	UIC95	= 5 x 7495	0-54
UIC07	= 8 x 7407	0-54	UIC60	= 12 x 7460	0-54	UIC96	= 5 x 7496	0-54
UIC08	= 12 x 7410	0-54	UIC70	= 8 x 7470	0-54	UIC100	= 5 x 74100	0-54
UIC20	= 12 x 7420	0-54	UIC72	= 8 x 7472	0-54	UIC121	= 5 x 74121	0-54
UIC30	= 12 x 7430	0-54	UIC73	= 8 x 7473	0-54	UIC141	= 5 x 74141	0-54
UIC40	= 12 x 7440	0-54	UIC74	= 8 x 7474	0-54	UIC151	= 5 x 74151	0-54
UIC41	= 5 x 7441	0-54	UIC76	= 8 x 7476	0-54	UIC164	= 5 x 74164	0-54
UIC42	= 5 x 7442	0-54	UIC80	= 5 x 7480	0-54	UIC193	= 5 x 74193	0-54
UIC43	= 5 x 7443	0-54	UIC81	= 5 x 7481	0-54	UIC199	= 5 x 74199	0-54
UIC44	= 5 x 7444	0-54	UIC82	= 5 x 7482	0-54			
UIC45	= 5 x 7445	0-54	UIC83	= 5 x 7483	0-54	UICXI	= 25 Assorted	74's 1-85

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

2 Amp. BRIDGE RECTS.
50 v RMS 35p each
100 v RMS 40p ..
200 v RMS 45p ..
400 v RMS 50p ..
1,000 v RMS 55p ..
Size 16 mm x 16 mm.

D1899 NPN SILICON DUAL TRANSISTOR
(Similar to 2N2060)
1 25 100+
0-28 0-26 0-23

LINEAR INTEGRATED CIRCUIT PAKS
Manufacturers' fall-outs

Pak No.	Contents	Price
ULIC709	10 x 709	0-54
ULIC710	7 x 710	0-54
ULIC741	7 x 741	0-54
ULIC747	5 x 747	0-54
ULIC748	7 x 748	0-54

KIN OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-54
U 2	60 Mixed Germanium Transistors AF/RF	0-54
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-54
U 4	40 Germanium Transistors like OC81, AC128	0-54
U 5	60 200mA Sub-Min. Silicon Diodes	0-54
U 6	39 Sil. Planar Trans. NPN like B8V95A, 2N706	0-54
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0-84
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-54
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-54
U10	20 BA50 charge storage Diodes DO-7 Glass	0-54
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-54
U13	30 PNP-NPN Sil. Transistors OC200 & 2N104	0-54
U14	150 Mixed Silicon and Germanium Diodes	0-54
U15	25 NPN Sil. Planar Trans. TO-5 like BFY61, 2N697	0-54
U16	10 3 Amp Silicon Rectifiers 81u Type up to 1000PIV	0-54
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-54
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-54
U19	25 Silicon NPN Transistors like BC108	0-54
U20	12 5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-54
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	0-54
U23	30 MADT's like MHz Series PNP Transistors	0-54
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-54
U25	25 300MHz NPN Silicon Transistors 2N708, BSY27	0-54
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-54
U29	10 1 Amp SCR's TO-5 can. up to 600 PIV CR11/25-600	1-08
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-54
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-54
U34	30 Silicon PNT Alloy Trans. TO-5 BCY26 28302/4	0-54
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-54
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-54
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0-54
U38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0-54
U39	30 RF. Gern. PNP Transistors 2N1303/5 TO-5	0-54
U40	10 Dual Transistors 6 lead TO-5 2N3060	0-54
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-54
U44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-54
U45	7 3A SCR. TO56 up to 600PIV	1-08
U46	20 Unijunction transistors similar to T1843	0-54
U47	10 TO220AB plastic triacs 50V 6A	1-08
U48	9 NPN Sil. power transistors like 2N3055	1-08
U49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	1-08

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE	SIL. RECTS. TESTED
One 55p Pak of your own choice free with orders valued £4 or over	PIV 300mA 750mA 1A 1.5A 3A 10A 30A (DO7)(SO16) Plastic (SO16)(SO16)(SO10)(TO48)
	50 05 06 1N4001 05 08 15 21 60
	100 05 07 1N4002 06 10 17 23 75
	200 06 10 1N4003 07 12 22 25 1-00
	400 08 15 1N4004 08 15 30 38 1-35
	600 09 17 1N4005 10 18 36 45 1-90
	800 12 19 1N4006 11 20 38 55 2-10
	1000 14 30 1N4007 12 25 48 65 2-50
	1200 35

CADMIUM CELLS
ORP12 48p

NEW LOW PRICED TESTED S.C.R.'S

PIV	50	100	200	400	600	800
1A	TO5	0-22	0-27	0-32	0-42	0-53
3A	TO86	0-27	0-27	0-32	0-42	0-53
5A	TO86	0-32	0-32	0-32	0-42	0-53
7A	TO48	0-52	0-55	0-62	0-67	0-84
10A	TO48	0-55	0-63	0-67	0-83	1-07
16A	TO48	0-58	0-62	0-67	0-77	0-97
30A	TO48	1-27	1-54	1-78	1-93	4-40

2N3055

115 WATT SIL POWER NPN 45p EACH

DIACS	TRIACS
FOR USE WITH TRIACS. BR100 (D32) 25p each	V _{NOM} 2A 6A 10A TO-6 TO-66 TO-48
10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each	p p p p p p
	100V 33 55 88
	200V 55 66 99
	400V 77 83 1-21

Gira No. 388-7006


Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 15p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

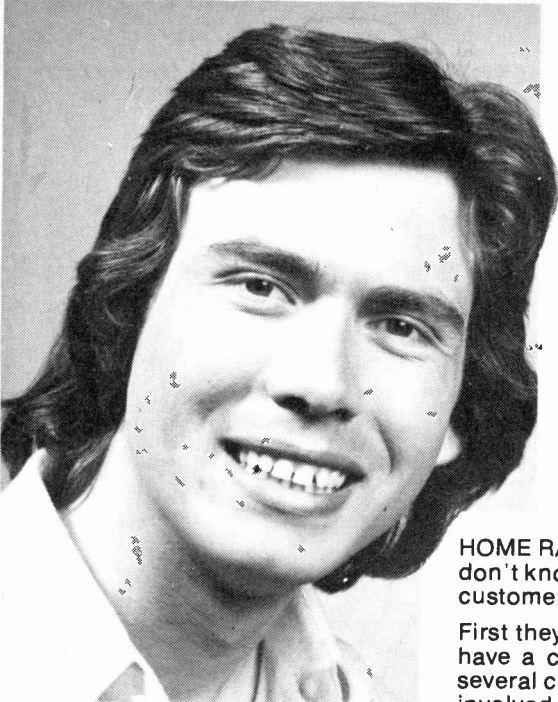


*I know ONE place
where Service
still means
something!*

HOME RADIO COMPONENTS LTD. of Mitcham are the people! I just don't know another firm that makes life so simple for their mail order customers.

First they devised a system whereby anybody who wanted to could have a credit account and pay monthly, thus saving the cost of several cheques or postal orders. Many credit account schemes are involved and awkward to join, but with Home Radio Components you simply have to complete a very simple form—not even references are called for. Then they send you a supply of order forms and pre-paid envelopes—another worthwhile saving. *Then they really pamper you!* They have installed an Answerphone system, so that you can phone orders through, any time of day or night—Sundays included! Very convenient—no wonder over 700 Credit Account customers use this service.

Of course, to order your components you first need the famous Home Radio Components Catalogue—just about the best catalogue of its kind you've ever seen. It costs 98p (65p plus 33p for post, packing and insurance). But Home Radio help you out even here—with the Catalogue they give you 14 vouchers each worth 5 pence when used against orders, so you can soon get the cost of the catalogue back, plus a bit towards postage! *Just send the coupon below with your cheque or P.O. for 98p.*

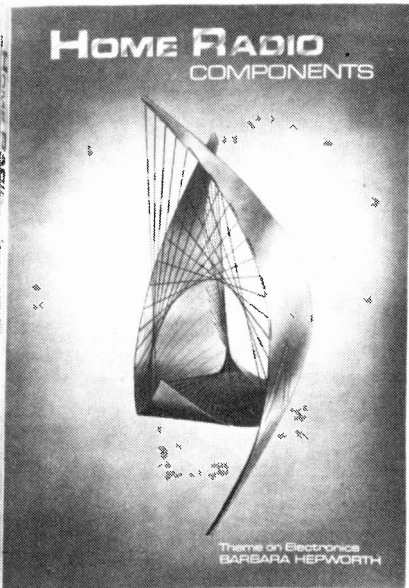By the way, you'll find full details of the Credit Account system inside the catalogue, together with the necessary form. And here's your bonus—once you've joined the scheme you'll receive a new catalogue FREE each year. Yes—Home Radio Components still know the meaning of SERVICE. *To prove it—send that coupon now.*



65p. plus 33p POST AND PACKING

Send off the coupon today. It's your first step to solving your component buying problems.

The price of 98p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. PE,
234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No.
London 912966)



VITAL LINKS

THE very successful infiltration by electronics into miscellaneous and apparently unrelated fields is based upon the ready ability to transform different forms of energy into electrical energy, and vice versa. Without those devices embraced by the term "transducers" electronic circuitry would be limited to purely electrical or electronic functions.

Many energy transforming devices used for industrial or scientific measuring and control purposes fall clearly into the class of precision instruments. They are usually designed for specific applications in association with hydraulic, pneumatic, or mechanical systems. These kind of applications are seldom encountered by the amateur. Apart from such highly specialised transducers, there are more commonplace devices and some—like the microphone and loudspeaker—have been around for a very long time and indeed antedate the introduction of the now generally used term transducer. There are also those simple home made devices which, in comparison with their elegant commercial counterparts, seem hardly to qualify for the rather impressive title of transducer. Yet they ably perform essential energy conversion roles in some electronic system or another.

The touch plate and the moisture sensor are examples of transducers of the most rudimentary form which can be fashioned from commonplace materials and work very successfully with standard electronic circuitry. Of course far more complex and intricate devices can also be made by the amateur who is adept in mechanical matters. For example, the electrodynamic type of instrument used in the Marine Speedometer (February issue).

There is also a good variety of semiconductor devices which are used for sensing or transducing purposes. The developments in this area have been of particular value and importance to amateurs, for they have opened up additional useful applications for circuitry without introducing undue mechanical problems. One of the more recent and notable innovations in solid state transducers is the gas or vapour detector. This device has now joined the ranks of other semiconductor devices which can sense atomic radiations, heat, light, sound and pressure. (Only taste appears to be lacking at present, but surely it can only be a matter of time before this sense is covered as well?)

As a matter of fact, this marked paralleling of human senses tempts us to indulge in a little whimsical speculation. Can we expect one day the arrival of the thought-responsive transducer, a device that will permit the control of electronic apparatus without the necessity of physical contact of any kind? Some extra-sensory perception devotees believe they really are on the track of this esoteric solution to some of life's little problems. And there has actually been a suggestion that the humble Zener diode could be a possible candidate for this post. Who knows, maybe some readers are currently engaged in pitting their wits against the undisciplined host of particles within that tiny component following the recent Probability Anomaly Detector article.

Frankly, though, we confess having doubts that any redundancy amongst orthodox transducers will result from this battle of mind over matter. So we return to wholly substantial and materialistic matters by drawing attention to the new series starting this month dealing with those important intermediaries—transducers.

F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

PE COMPENSATED PHOTO TIMER

By K. LENTON-SMITH



THE majority of photographic interval timers lack essential refinements where precision printing is concerned. The present design was specifically evolved for advanced photography students interested in colour printing and accurate monochrome work.

Layout of the controls takes into account the probability of working in total darkness, or something closely approaching this, due to the safelighting required with panchromatic papers. Exposure intervals may be continuously adjusted between 0.1 and 121 seconds, and these may either be exact or compensated for fluctuations in the a.c. mains voltage supplying the lamp. Controls which start, reset or a low focusing are conveniently placed on a bar at the front of the instrument, for easy location in darkness. A light emitting diode pilot may be switched on or off according to whether colour blind or colour sensitive material is being used. A foot switch may be run in parallel with the start switch so that both hands are available for "dodging" the print.

The circuitry is not particularly complicated, the basic timer being quite conventional. To obtain consistent exposures it is normally necessary to use a voltage stabiliser and, if both timer and stabiliser are commercially made, the parcel can be expensive. The present design dispenses with the voltage stabiliser by altering timing periods in inverse proportion to mains supply voltage. Constructors are warned that this involves mixing low tension d.c. supply for the timing circuit with a.c. mains potentials, thus more than usual care in construction is called for.

RECIPROcity LAW

Experienced photographers will be aware of the reciprocity law, on which all exposure measuring devices are based

$$T \times I \cong K$$

It expresses the fact that the product of time (T) and intensity (I) must be constant (K) for a given sensitised material (intensity being itself the product of subject brightness and the f stop used). Although it is well known that this law breaks down at extremes of shutter speeds and low light levels, it holds good over the normal ranges encountered in camera exposure. The photographer carefully measures light intensity and, with film speed (K) set, the (Reciprocity Law) calculator on the meter will compute the aperture/speed combinations for the material in question.

Having carefully measured camera exposure and accurately developed or reversed the material, the printing stage arrives. Here is where the Law goes out of the window!

Readers appreciate that there are small variations in mains voltage taking place the whole time, especially if a hospital or factory is nearby. More important, however, is that photographic high intensity enlarging lamps are slightly over-run, operating on a similar principle to the photoflood lamp. This means that their reaction to fluctuations is more highly-g geared than with household lamps. When voltage alters, so does intensity (I) and, if the timer gives precise intervals, "K" is meaningless.

To compensate for intensity changes, exposure time must be reciprocal. If the intensity falls, exposure time must be extended—and vice versa. Fig. 1 shows the percentage changes in the light output from an 150W enlarging lamp as voltage is decreased, the 75W lamp following much the same

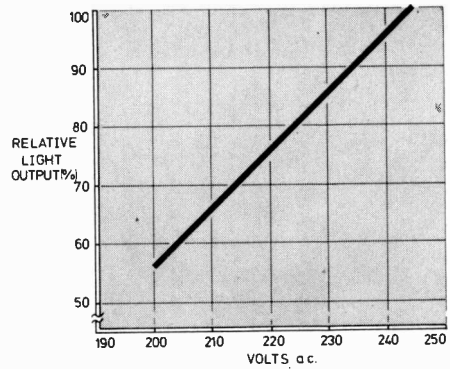


Fig. 1. Effect of mains voltage on enlarging lamps

pattern. A 10 per cent error in the exposure of papers such as Ektacolor 37RC will be most noticeable and really demand a reprint. Ideally, all mains supply fluctuations require compensation so that repeatable results are possible. When switched to the "Compensated" mode, this timer will give the same light dosage for a given setting of the interval switches, despite any unevenness in supply voltage.

CIRCUIT

The complete circuit is shown in Fig. 2. Pin 5 of IC1 is normally supplied with about half the rail voltage, this potential altering all intervals pro rata. When S6 is switched to "Exact", pin 5 is connected in this manner. With S6 set to "Compensated", pin 5 is supplied with an amplified version of small changes in a.c. mains voltage and thus makes the timed interval reciprocal. S3 and S2 are simple make switches, but the circuit is otherwise solid state.


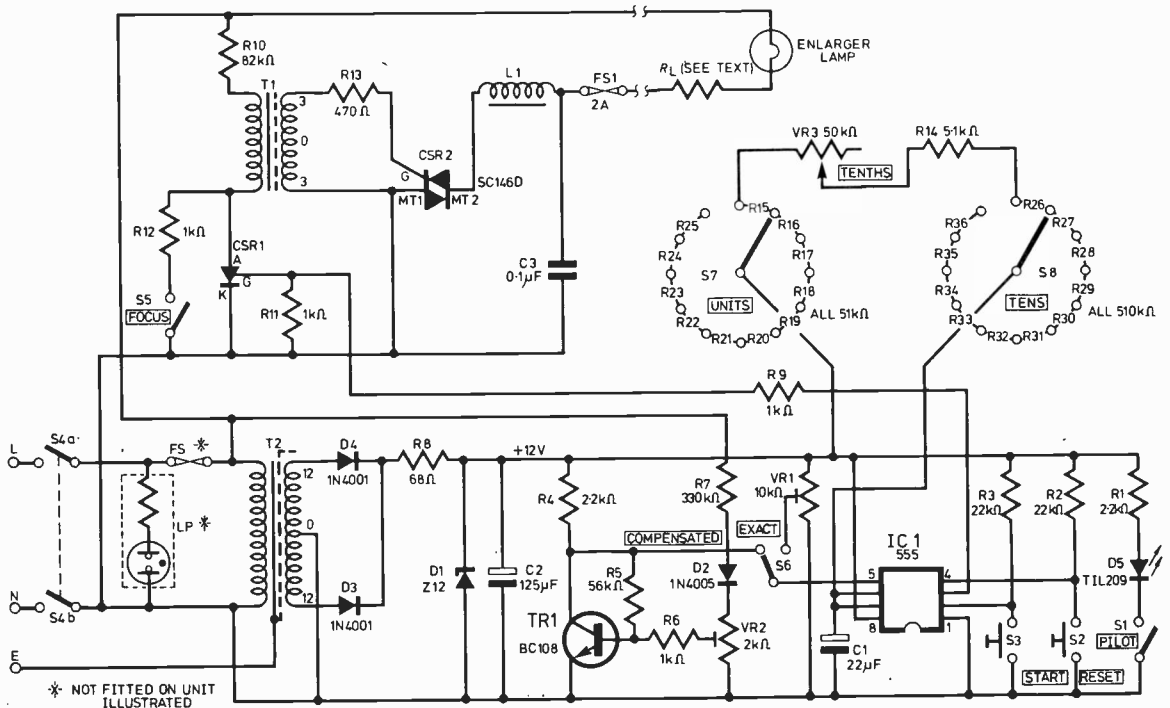


Fig. 2. Complete circuit of the timer

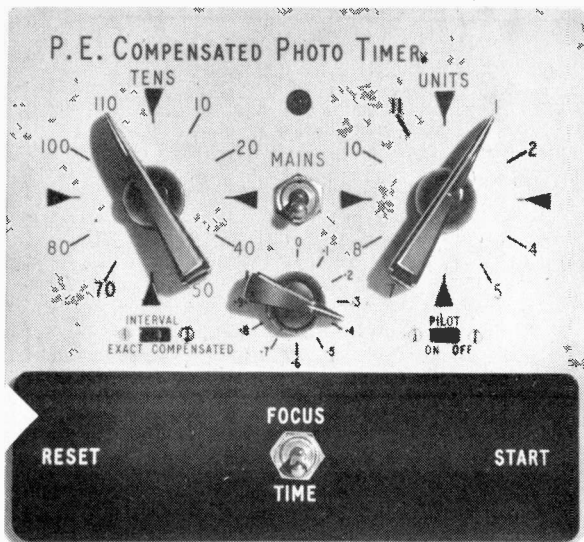

The completed front panel showing positioning of controls

Output from the timer i.c. is used to switch a thyristor in series with the primary winding of the transformer, whose secondary controls the gate of a triac and hence the lamp itself. Though a little more expensive than pure relay operation, this method is positive and reliable in obviating problems associated with relay points.

Supply voltage is nominally 12V, with 15V a safe upper limit. R8 may be adjusted upwards if D1 passes too much current. Reset switch S2 is connected to pin 4 of the i.c., and the start switch to pin 2. Both are held at positive potential by R3 and R2 to avoid spurious operation and are triggered by a negative going pulse when either switch is closed. The neutral side of the a.c. mains supply is ground with respect to the i.c. and its power supply. Threshold and discharge pins 6 and 7 are connected together in this application. From this point the charge on the timing capacitor C1, being fed through the timing chain, is sensed and the i.c. output switches off when the charge on C1 reaches two-thirds of the positive rail voltage. This capacitor should be either a bead tantalum or the closer tolerance tantalum specified.

RESISTOR CHAIN

Using the formula $t = 1 \cdot IRC$, any combination of resistor and capacitor may be used to arrive at the basic 1 second unit. However, it is best to keep the value of R as low as possible to avoid the risk of leakage currents. Mathematically, these produce just over 1 second, but capacitor tolerance and the ability to adjust VR1 and VR2 make these values ideal.

As the accuracy of the finished timer depends almost entirely on C1 and the timing chain, good quality components are essential—and the extra cost not exorbitant. Resistors should not be overheated when being fitted to S7 and S8 and the associated wiring must be kept clear of other components. New switches have better contacts than old ones.

Any "stops" should be removed from rotary switches S7 and S8 so that the pointers may be turned in any direction. Timing resistors must be used in the 11 o'clock positions (though R25 may be considered superfluous) to avoid an open circuit and consequent waste of expensive material. Though it would be simple to select a set of ordinary 20 per cent resistors using a bridge or meter, 2 per cent metal oxide types are more stable in use and are thus recommended.

COMPONENTS . . .

Resistors

R1	2.2k Ω
R2, R3	22k Ω (2 off)
R4	2.2k Ω 5%
R5	56k Ω
R6	1k Ω
R7	330k Ω 5%
R8	68 Ω 1W wirewound
R9	1k Ω
R10	82k Ω 1W
R11	1k Ω
R12	1k Ω
R13	470 Ω
R14	5.1k Ω 5%
R15–R25	51k Ω (11 off). All metal oxide 2%
R26–R36	510k Ω (11 off). All metal oxide 2%
All $\frac{1}{2}$ W 10% carbon except where stated	

Capacitors

C1	22 μ F tantalum elect. 16V
C2	125 μ F elec. 16V
C3	0.1 μ F 900V

Semiconductors

TR1	BC108
IC1	NE555V
CSR1	400V 1A Thyristor
CSR2	400V 10A Triac (Type SC146D)
D1	Z12 12V Zener diode, 600mW
D2	IN4005
D3, D4	IN4001 (2 off)
D5	TIL 209 l.e.d.

Potentiometers

VR1	10k Ω sub-miniature preset
VR2	2k Ω sub-miniature preset
VR3	50k Ω linear

Switches

S1	Miniature d.p.d.t. slide switches
S2, S3	Press-to-make switches (2 off) (see text)
S4	D.p.d.t. toggle 250V
S5	S.p.s.t. toggle 250V
S6	D.p.d.t. slide switch
S7–S8	12 way rotary (2 off)

Transformers

T1	Douglas type MT238C5. Pri. 240V, Sec. 3–0–3V, 200mA
T2	Brazenose 12012/1. Pri. 240V, Sec. 12–0–12V, 100mA

Miscellaneous

1 Pointer knob $1\frac{1}{2}$ in, 2 long pointer knobs $2\frac{1}{2}$ in, 4 way terminal block, 16 s.w.g. aluminium for small heat sink; Case (see text), 4 rubber feet, FS1 2A fuse and holder, L1 (see text)

PHOTOGRAPHIC TIMER WIRING

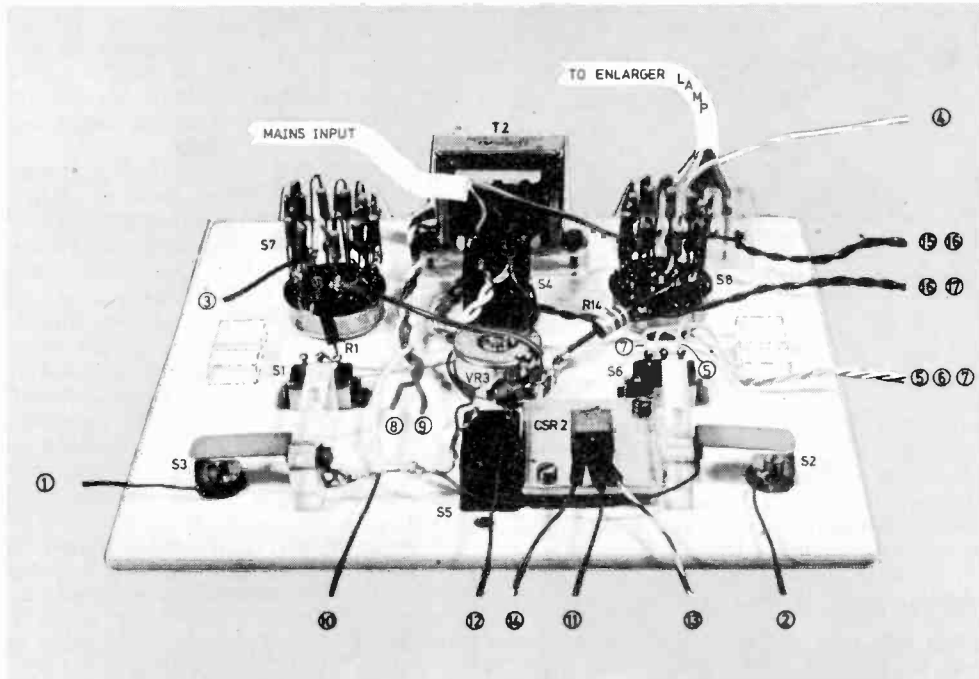


Fig. 3. Underside of control panel. Flying leads terminate at Veroboard sub-chassis (Fig. 4)


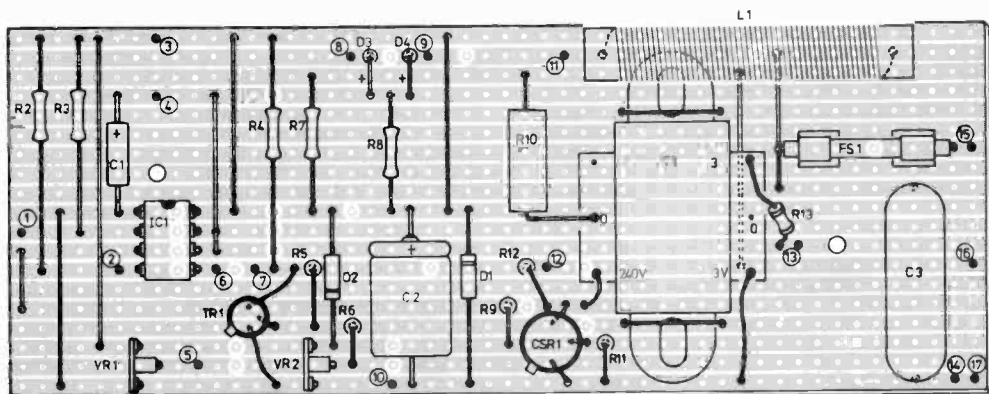


Fig. 4. Veroboard sub-chassis showing assembly and wiring

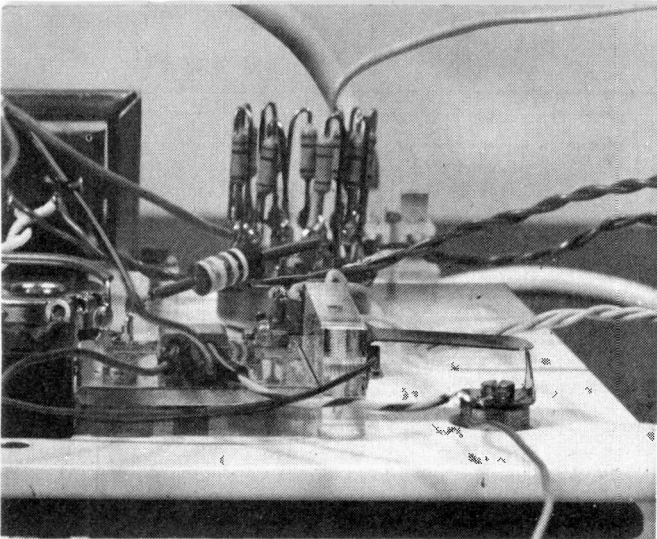

A close-up of the reset switch assembly and the 1 1/4 in x 1 1/4 in aluminium heat sink for CSR2

With S6 in the "Compensated" position, operation of the chip will be affected by mains voltage. R7 and VR2 form a potential divider, half rectified by D2. A small portion of this voltage is fed to the base of TR1 through R6. R5 provides automatic transistor stabilisation and the collector of TR1 reflects changes in mains voltage. A rise in voltage at the slider of VR2 will reduce collector voltage and shorten the interval, the opposite applying when voltage falls.

LAMP SWITCHING

Output from pin 3 of IC1 is fed to the gate of CSR1 through R9. The thyristor, primary winding of T1 and R10 are connected across the mains supply so that the transformer is energised by a positive signal on pin 3. The 6V secondary winding of T1 produces an a.c. signal, which is fed through R13 to the gate of the triac CSR2. The enlarger lamp is connected in series with the triac across the mains supply.

L1 and C3 form a transient suppression network which is necessary as triacs may easily be destroyed by high level pulses in the supply. In addition to fitting a 2A fuse in series with the lamp, it is advisable always to use a low resistance series limiter—because the triac could be destroyed before the fuse blows in the event of short-circuit lamp failure. It is suggested that a 5 ohm 100W wire-wound resistor (R_L) be fitted externally between timer and enlarger.

As this resistor gets hot, it is inadvisable to include it in the timer in view of the accuracy required of the timing components.

Focus switch S5 by-passes the thyristor so that the lamp may be turned on for an unlimited period.

CONSTRUCTION

This should commence with the Veroboard sub-chassis, cutting details being shown in Fig. 4. Because some copper strips carry mains voltage and others the 12V circuits, it is necessary to be even more careful than usual that the track is cut correctly and that solder bridges are not formed inadvertently. Veropins are best used where connections are made with inflexible flying leads.

L1 consists of 50 turns of 22 s.w.g. enamelled copper wire on a short piece of 1/8 in ferrite rod, but anything fairly similar will suffice. After winding the coil should be warmed up with a hair-dryer and Araldite applied. This will cut down any tendency to buzz when the timer is operating.

T1 is small enough to mount with an adhesive, reinforced by copper wire loops passed over the mounting tags and soldered into the track. Some versions of the Douglas MT238 CS transformer have theappings emerging from the underside of the coil (in the present case, they are brought out from the top) and could then be soldered into the board directly, with appropriate changes in the cutting pattern.

Timing resistors R15-R25 should be soldered round S7, bearing in mind that they progress anticlockwise when viewed from below. Even though 2 per cent resistors are being used, it is a wise precaution to measure the total value of R15-R24 by setting S7 to junction R24/R25. R26 should be chosen to match this value and VR3 and R14 must obviously be excluded in making this match. R14 itself is a limiting resistor (which adds 1/10 second to all timing intervals) and is included to prevent damage to the i.c. if the start switch is operated with all pointers set at zero.

S7, S8, VR3 and R14 wired in series form the timing resistor chain. These may be temporarily connected to the sub-chassis by thin, flexible wires to test the basic timer circuit. With S6 bridged to the "Exact" position and 12V applied to the i.c. supply rail, the constructor can ascertain that CSR1's gate is being supplied from pin 3 of the timer. S3 and S2 will have to be jury rigged for this test and the 12V may be supplied from a battery or from T2 alone connected to mains supply.

The Veroboard sub-chassis with all components mounted in position


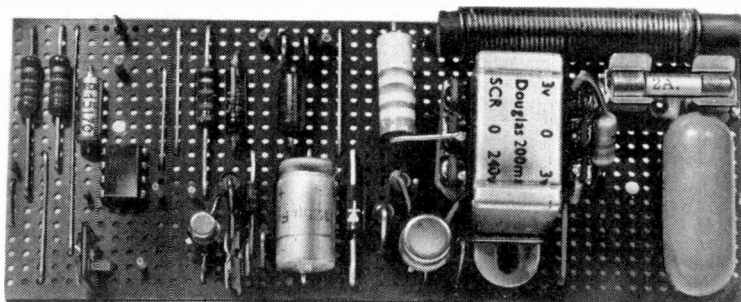


Fig. 5. Top panel dimensions and drilling details. The black Perspex operating bar shown unshaded stands proud of the panel by means of a spacer placed under the focus switch S5

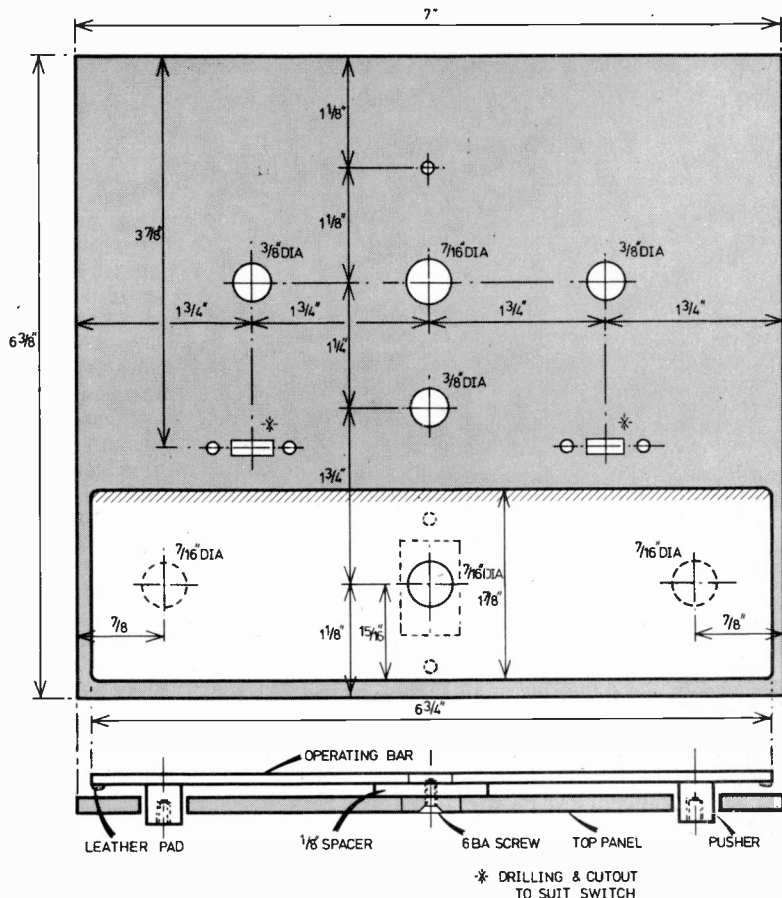

CASEWORK

Fig. 5 gives top panel dimensions and drilling data, whilst Fig. 3 shows the underside of this panel and connections of its components to the sub-chassis. The majority of the hardware is attached to the underside of the panel, the sub-chassis being slung on supports which ensure that it clears the switching associated with the operating bar. The Veroboard supports are tapped with 8 B.A. threads and two paxolin washers should be placed between board and supports before finally screwing down. A large hole must be drilled in the block used to mount T2 so that the light emitting diode pilot can be fitted through the panel underneath the transformer.

Where timers are concerned, a control panel of insulating material is to be preferred as it minimises the possibility of leakage between switches. Formica or Paxolin are suitable, but Perspex ($\frac{1}{8}$ in opaque white) has been used for this timer. Apart from being a fairly good insulator, Perspex is easy to work and neat in appearance. It may be sawn with a hacksaw, roughly finished with a metal file and finally finished with wet emery and metal polish. Screw-holes in the top of the panel may be minimised by attaching components T2 and the terminal block to pieces of tapped Perspex, then cementing to the underside. Holes may be tapped in the usual way, using white spirit as the lubricant and ensuring that the taper/plug is not allowed to clog.


The box covering the timer has also been made of Perspex, clear in this case, secured by screwing into

tapped blocks cemented to the underside of the panel. By rubbing down sawn edges on wet emery placed on a sheet of glass, good mating of the parts of the box can be achieved when cementing together.

The panel should overlap the box itself so that the timer may be free standing on four rubber feet or flush mounted into a darkroom control panel.

OPERATING BAR


The black Perspex operating bar ($\frac{1}{8}$ in thick) stands proud of the panel by means of a spacer placed under the focus switch S5. This bar is intended to flex so that pressure on either end will operate the associated switches. As one side of both S3 and S2 is at mains potential—and photographic workers are handling wet processes—these two switches are inside the timer, rather than simple contacts under the bar. "Pushers" cemented to the underside of each end of the bar protrude through holes in the panel to operate simple switches. Strips of phosphor-bronze have been used, though old relay contacts would probably be equally suitable. The spacer in the middle of the bar is cemented to it and the assembly held in place by countersunk screws through the underside of the panel. Focus switch S5 will probably have to be recessed into the panel to ensure that it clears the underside of the sub-chassis and that its retaining collar can be attached. Two small, thin leather pads on the underside of the extreme ends of the bar will prevent a click as S3 or S2 are operated.

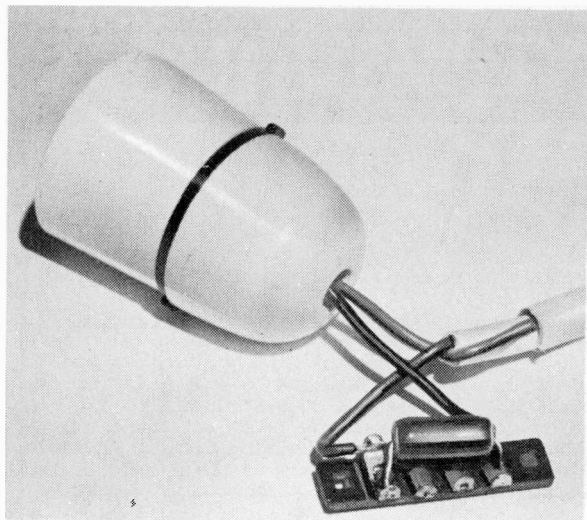

A tag-board mounted resistor (RL) is used as a series limiter

Triac CSR2 is mounted on a small heatsink attached to the panel by small tapped blocks. As the load will not normally exceed 150W, the size is not critical; 10 or 16 s.w.g. aluminium should be used—as large as will conveniently fit between S2 and sub-chassis mounting pillar. Main terminal 2 is electrically common to the heatsink, so the triacs connections should be sleeved and the sink should not touch other components.

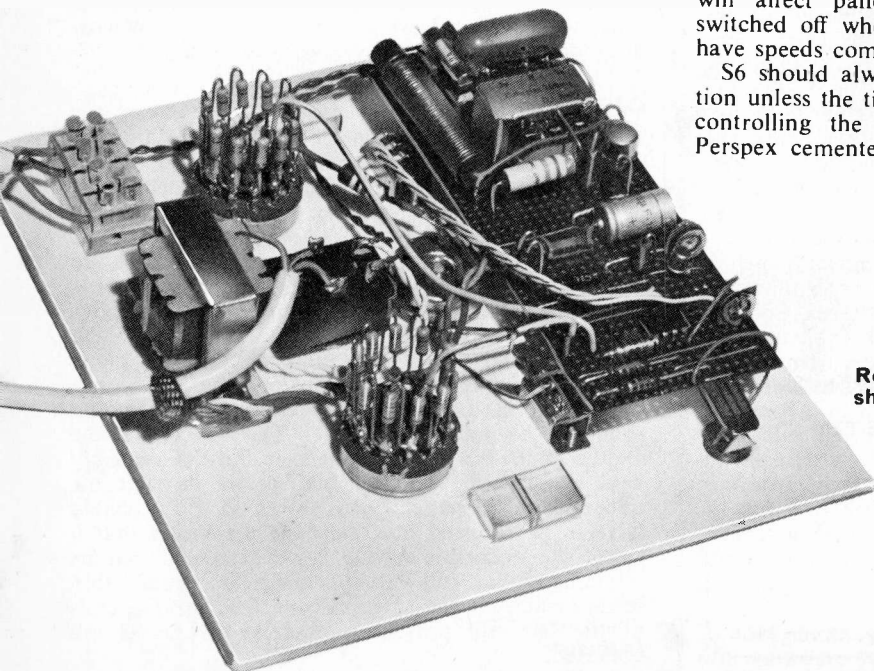A short busbar connects together one side of S2 and S3, one side of S5, centre tap of the secondary winding of T2 and one lead for the pilot. When finally assembled, this busbar is connected to the common neutral line at point 10 on the Veroboard.



Rear view of completed front panel showing the range resistors

The four-way output terminal block has provision for an earth connection, though many enlargers only require two-wire connection. Earthing the column is worthwhile as static in the enlarger head is reduced and dust in the negative carrier made less problematical.

SETTING UP

Assuming the basic timer has already been tested as described, the rest of the wiring should be completed and a 75W or 150W bulb connected to the terminal block with its limiting resistor. On test, the lamp should be of normal brilliance if the stated components have been adhered to. If not, R10 or R13 may have to be reduced slightly until full-wave operation is achieved.

Preset VR1 should first be accurately set, with S6 in the "Exact" position. Set the controls to 60 seconds (VR3 and S7 being at zero) and adjust VR1 until an interval as close to this as possible results. With S6 in this mode, the timer can be used, with an audible alarm, for developing prints for the usual 1½ or 2 minute period.

Preset VR2 is next adjusted, with S6 in the "Compensated" position. This setting should always be used for enlarging. This preset will need to be set somewhere near the "earthy" end of its track, the final setting being very critical. If the mains voltage is near to 245V, set the controls to 10 seconds and adjust VR2 minutely until this time is attained. If the mains voltage moves from this point, the timing will alter slightly—as it should. With a "Variac" transformer, it is possible to check time against voltage; the characteristic, when properly adjusted, will follow the pattern shown in Fig. 6.

USING THE TIMER

With monochrome materials, the pilot light may be switched on. The colour of the emission and value of R1 combine to produce a "safelight". As it will affect panchromatic materials, it should be switched off when using colour papers, which now have speeds comparable to bromide paper.

S6 should always be in the "Compensated" position unless the timer is used for purposes other than controlling the enlarger. Small triangles of $\frac{1}{8}$ in Perspex cemented at the 0, 3, 6 and 9 position of

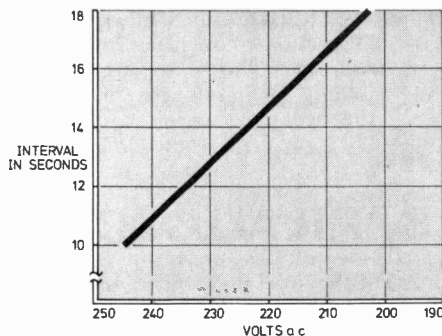


Fig. 6. Variations of a 10 second setting with changes in supply voltage produced by the timer with S6 in the compensating mode. This is close to the ideal implied in Fig. 1

S7 and S8 make it easy to set these in the dark by feel, whereas the less critical setting of VR3 can be closely estimated. In practice, the timer will be set immediately the test strip has been assessed, filtration changes made and before the lights are turned off ready for the next print to be made. It is reassuring to be able to check the setting in darkness to avoid wasting an expensive sheet of colour material!

The operating bar, carrying the most used controls, are nearest to the worker and easily operated in darkness. Positions of S3 and S2 may need to be reversed depending on the timer's position relative to the enlarger, dry bench layout and whether the user is left-handed. S3 nearest to the enlarger seems to be a natural choice. Any or all of the operating bar controls could be paralleled for foot operation, thus freeing the hands for shading and other manual control.

The timer will work comfortably at 210V or below, the author's own darkroom version having been in use during the power crisis. It will make for more consistent exposure, particularly where colour emulsions are concerned. Whilst falling mains voltage affects the colour temperature of the lamp to a small degree, the average variation will not have any practical effect, nor call for filtration changes of more than about 0.25Y—which can safely be ignored. Used with a filter Nomogram, this timer should enable the user to produce consistent prints of high quality with the minimum of wastage. ★

everyday electronics

- # CAR RALLY INTERCOM SYSTEM
- # TOUCH SWITCH
- # QUIZMASTER

For you to construct

PLUS—TWO NEW FEATURES:
CAREERS IN ELECTRONICS
WORKSHOP PRACTICE

All in the April issue on sale Friday, March 21

NEWS BRIEFS

Speakers In The Sun

How better to announce a new range of speakers than at a conference held in Malta? This clearly, is the view of the newly recreated Marsden Hall International company who recently held demonstrations in a luxury hotel in Malta of their latest range of quality loudspeakers.

Extending from a shelf-mounting 10W capacity unit up to a free standing 50W studio module, the range is split into two sections called respectively Annexe for powers up to 30W r.m.s. and Symphony for the two upper capacity modules of 35 and 50W rating.

The units are attractively styled in either Teak or Walnut, with detachable fronts either fabric or filter foam covered. Indeed, the foam-covered versions can be supplied in any of 26 different colours.

Of course, the critical test of a loudspeaker is not really the appearance, although this counts for a great deal in some circles, but the audio performance. Here, Marsden Hall went to some lengths to present their equipment as completely as possible.

They organised an audio demonstration of the various units in stereo pairs with the ability to switch from one pair to another at will. This allowed the listener to compare the six models one with another at ease. A selection of styles of music and types of orchestration was presented to show the ability of the equipments to cope with transients, bass and treble response, and so on.

Predictably, the larger studio units came out on top in all sections, but after all, the demonstration was given in a fairly large suite and it is under such circumstances that the full bass response can really benefit. However, all the units, including the smallest Annexe XL10 pair performed as well as one would expect, if not better.

It is quite educational to switch from a triple-driver system of 50W capacity to the smallest shelf-mounting model which uses only a six-inch base unit and a single three-inch tweeter. There is bound to be some colouration of response and a step-by-step run through the range shows this up as fairly minimal, often appearing with switching in one direction and not the other.

Prices are well in line with current ranges, running from £44.50 per pair for the smallest shelf-mounting model to £172.50 per pair for the Symphony 4522 studio units. The two smallest units are both shelf-mounting, the largest of the Annexe range can be used as a shelf-mounted or a freestanding unit whilst both the Symphony units are freestanding and can be optionally supplied with castor stands.

The prices mentioned are the recommended retail values and we understand that the units are to be available from specialist Hi-Fi dealers throughout the U.K.



The Annexe XL10 enclosure

TRANSDUCERS

Part 1 INTRODUCTION

By P.R. ALLCOCK*

INTRODUCTION TO SERIES

This series of articles is intended as an introduction to the vast range of transducers that exists today. Instrumentation engineers are constantly challenged to satisfy the increasing demands made by their colleagues in other areas of specialisation and may be called upon to measure an almost infinite variety of physical phenomena.

Broadly defined, a transducer is any device by means of which energy, available in one form, may be changed to energy in another form. Energy can exist in various forms such as electrical, mechanical, acoustical and thermal and often the output energy of a transducer is in the electrical form. Devices which convert electrical power into, say, mechanical force also come within our broad definition but are often classified into a separate group known as electrical machines. Some of these devices are very important to the electronic engineer and small rotary motors, stepping motors and related devices crop up very frequently, as, for example, in equipment using tape or paper as a recording medium. Often the input energy will be in mechanical form and the first section of the transducer may then perform a conversion from say applied force to displacement.

The subsequent conversion of displacement to electrical energy would take place in a second section and could employ one of the many principles available such as: piezo electric effect, differential transformer, capacitance resistance or inductance variation, photo electric effect, magnetostriction, etc. The nature of the electrical output from the transducer depends on the principle involved in the design and may be analogue, digital, frequency modulated or some form of pulse train. In fact a transducer may be based on almost any combination of the various mechanical and electrical arrangements available.

Some examples of commonplace transducers are listed below and these will be covered in the series.

Measurement Required	Possible Transducer
Shaft rotation or position	Coded optical disc
Linear displacement	Variable resistance element
Temperature	Thermistor or variable resistance devices
Ultrasonic sound waves	Piezo-electrical material
Mechanical strain	Resistive or semiconductor strain gauge
Liquid flow	Turbine type flow-meter

In general terms a transducer is a device which converts (or transduces) energy from one form to another. This definition is rather all-embracing since it includes devices such as electric motors, car engines and turbines whereas, at least through common usage, the term normally refers to devices of a somewhat more specialised nature.

In one category we have devices that can convert an electrical input stimulus into a mechanical output response, such as occurs in the moving coil loudspeaker, whilst in a second category we can group those devices that convert some physical quantity, property or condition to an electrical output signal as occurs for example with a pick-up cartridge.

It should be noted that transducers are not restricted to the use of an electrical signal at the input or output but such devices are by far the most common today due to the widespread use of electrical and electronic techniques in control, instrumentation, automation and measurement and the relative ease of processing or modifying such signals. For example, in many industrial processes the electrical output of a transducer is used, either directly or after processing, as a feedback signal in a servo-loop to control the output of the system in a specific manner.

In other applications a transducer might be connected to a readout device, such as a counter, tape printer or digital meter, and used to provide quantitative measurement information to an operator. Since it is not possible to control a process without measurement of one or more variables it is clear that transducers play an important part in a wide variety of modern engineering systems and measurement processes.

OPERATING PRINCIPLES

The operating principles of the majority of transducers in common use are straightforward, but in practice the utilization of these principles often involves very careful design and precision engineering in order that defects, which might otherwise limit the device accuracy, are kept to a low level. Even with careful manufacture, environmental factors such as temperature, vibration, shock and stray magnetic or electric fields, must be taken into account if the best accuracy is to be obtained.

Often several basic principles are used together to achieve the required output. The term measurand is often used to denote the quantity, condition or property which the transducer translates into the required output signal and in some cases the transducer does not respond directly to the measurand but to a related variable.

For example, transducers designed to measure acceleration are often activated by a displacement or force which is related in a known way to the acceleration.

* North Staffordshire Polytechnic

The "two-stage" principle is illustrated in Fig. 1.1. The first section translates the measurand into a displacement or stress and this in turn acts as the stimulus for the second stage which produces the requisite output. The second stage may generate the electrical output directly from the output energy of the mechanical transduction stage in which case it is known as self generating. The alternative form, which requires an external power source for excitation, is usually called a passive transducer.

TRANSDUCER CLASSIFICATION

It is an almost impossible task to classify the whole range of transducers now in use. However it is feasible to group them on the basis of their fundamental operating principles as in Table 1.1, even though they may be used in, or have evolved from, widely different applications.

Even with such grouping it may be difficult to classify a particular transducer uniquely because of overlap in the various selection parameters used. For example a thermistor might be classed as a variable resistance device or alternatively as a thermal device. Strictly speaking the thermal energy input is the measurand which can be related to temperature but two distinct modes of operation are possible.

If the electrical currents are kept sufficiently small the resistance will be dependent only on the heat input whereas if larger currents are permitted some self-heating will occur and the temperature will depend on two sources of heat.

VARIABLE RESISTANCE TRANSDUCERS

In the moving contact type, the measurand, either directly or indirectly, causes a change in the resistance of an electrical element. This change is usually caused by either a moving contact system or some physical or chemical action. The basic principle of a moving contact system is illustrated in Fig. 1.2 and here changes in liquid level are used to move a sliding contact along the resistance element BC.

Resistive	Electromagnetic
Capacitive	Thermo Electric (Voltaic)
Inductive	
Photo Resistive (Conductive)	Ionisation
Photo Electric (Emissive)	Electrolytic
Photo Voltaic	
Piezo Electric	Potentiometric
Piezo Resistive	Magneto Resistive

If we assume that the resistance between A and B is zero when the tank is empty the resistance R_{AB} for a liquid level of h will be $R_0 \cdot h$ where R_0 is the resistance change per unit height of liquid. If we assume also that R_0 is constant i.e. the resistance element is perfectly uniform over its whole length L we can express the output voltage as $V_o = E \left(\frac{h}{L} \right)$ volts providing no

current is drawn via the output terminals (Fig. 1.4).

In some application it may be desirable to use a resistance element that is not uniformly wound in which case the output voltage is no longer given by the above equation but by

$$V_o = E \left(\frac{R_{AB}}{R_{BC}} \right).$$

The way in which R_{AB} varies with height h determines the characteristic law of the transducer since E and R_{BC} are fixed. For example the resistance element R_{BC} could be wound on a thin wedge shaped sheet of insulating material as shown in Fig. 1.3. The resistance per unit length, R_0 , is not constant for this case and will in fact increase uniformly as the slider moves from B to C as long as the resistance wire is sufficiently fine

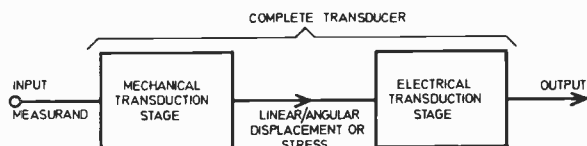


Fig. 1.1. Illustrating the "two-stage" principle of transducers

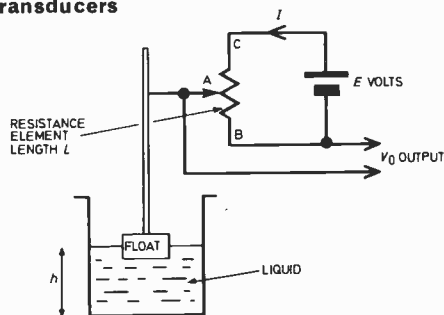


Fig. 1.2. A simple moving-contact system showing the basis of operation

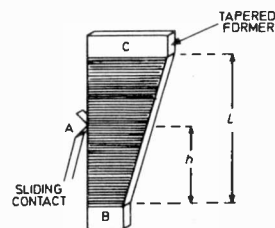


Fig. 1.3. A tapered or wedge-shaped element used in resistive transducers

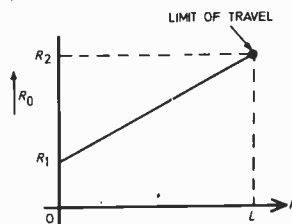


Fig. 1.4. Variation of resistance R_0 with height

and the element carefully wound so that the turns cannot move as the contact passes over their surface.

For the wedge profile shown in Fig. 1.3 the variation of R_0 with height h will be as indicated in Fig. 1.5. The resistance per unit length is obviously a function of h since as the slider moves along the resistance element the length of each turn of the resistance wire increases slightly. The variation of R_0 can be written as

$$R_0 = R_1 + \frac{h}{L}(R_2 - R_1).$$

If we put $h = 0$ we find $R_0 = R_1$ and for $h = L$ (the limit of slider travel) we find $R_0 = R_2$.

To determine the resistance between AB or BC we need to add together the resistance of all the turns of wire between the two points of interest. This is achieved mathematically by integration and for the section between A and B we have

$$R_{AB} = \int_0^h R_0 dh \\ = hR_1 + \frac{h^2}{2L}(R_2 - R_1).$$

At full height $h = L$ and substitution in the above equation then gives $R_{BC} = L \cdot \left(\frac{R_1 + R_2}{2}\right)$ which is simply the length of the element multiplied by the average resistance per unit length.

The variation of output voltage with height for this type of element is illustrated in Fig. 1.5 which also shows, for comparison, the output of a uniformly wound element operating from the same supply voltage.

The wedge element gives the greater rate of change of output voltage providing the tank is at least half full

($h > \frac{L}{2}$) whereas the uniform element gives the larger

output voltage for all heights except $h = L$ at which level both types give the same output voltage.

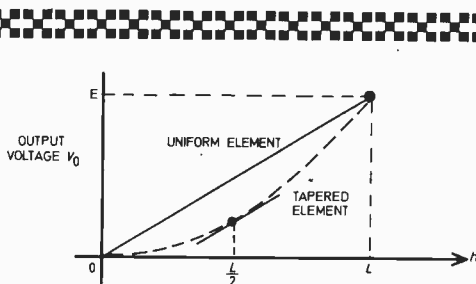


Fig. 1.5. Variation of output voltage with height

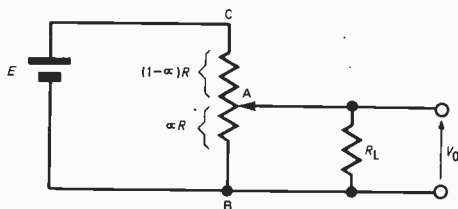


Fig. 1.6. Loading effects in transducer circuits

LAWS

The details discussed so far have shown that it is possible to control the characteristic law of the transducer by suitable choice of resistance variation with length of travel. In some applications it is the angular rotation of a shaft that activates the moving contact and in this case also it is possible, by choice of shape for the resistance wire former, to produce a given characteristic such as a sine or cosine variation of resistance against angular position.

Tapered resistance elements are sometimes used in bridge circuits to open out an otherwise cramped scale at the extremes of angular travel. The log and reverse-log audio volume controls use graded regions on the track with different resistance values per unit angle of rotation in an attempt to give a straight line piecewise approximation to the specified law.

Obviously mechanical friction has to be kept to a minimum in devices that have to operate with low forces and wear of contact and wire can limit the useful life. The wire used in some precision potentiometers is very fine to give good resolution and excessive currents can easily destroy the element, especially when the sliding contact is near to one end of the range of adjustment, due to the concentration of heat over a small region.

OUTPUT LOADING EFFECTS

No mention has been made of the loading that will occur if the transducer output is fed to a resistance which is not large relative to the element resistance. This form of loading is illustrated in Fig. 1.6 where the load on the output is represented by the inclusion of R_L . If α represents the fraction of the resistance element between A and B and R represents the total resistance of the element the circuit is simply that of a potentiometer having an upper portion of $(1-\alpha)R$ and a lower portion of αR in parallel with R_L .

Analysis of the circuit gives the output voltage V_0 as:—

$$V_0 = \frac{\alpha E}{1 + \alpha R(1 - \alpha)} = \frac{\text{(Ideal Unloaded Output Voltage)}}{1 + \alpha K(1 - \alpha)}$$

where K is the ratio of transducer element-resistance to loading resistance.

For a given value of K we see that the output voltage is correct for $\alpha = 0$ and $\alpha = 1$ (i.e. $V_0 = 0$ and $V_0 = E$ at the limits of travel) but at intermediate settings of α the output is in error and will always be less than the (ideal) true output.

In any reasonable system K should be considerably less than unity in which case the output is lower than the true value by approximately $[100\alpha(1-\alpha)K]$ per cent. The maximum error for a given K value occurs, as might be expected, when $\alpha = 0.5$ and is of the order $25K$ per cent low providing K is small. For $K = 0.1$ (i.e. $R_L = 10R$) the maximum error at mid-travel would be about 2.5 per cent low.

THERMISTORS

A thermistor is a heat-sensitive semiconductor resistor with a relatively large negative temperature coefficient of resistance, although thermistors having positive temperature coefficients are also available. A typical device will exhibit a resistance drop of about 4 per cent per degree temperature rise.

Unlike the p-n junction of a semiconductor diode or transistor, the thermistor does not depend on the effects that occur at a p-n interface and is not manufactured by doping silicon or germanium with impurities. Instead, a thermistor is made, using a sintering process, from mixtures of the oxides of metals such as manganese, nickel, cobalt, iron, copper, titanium and magnesium. Leads are attached to metallised areas on the thermistor body or connected during the controlled heating processes.

A very wide variety of shapes and sizes are now available ranging from small beads to large plates or rods.

A protective coating of epoxy or fused glass is often provided and some types are available in glass envelopes, either evacuated or gas filled. Resistance values at 25°C range from about 1Ω to several MΩ.

Early devices were very variable in characteristic and it was difficult to match the characteristics of two similar thermistors. Fortunately improvements in manufacturing techniques have virtually eliminated the shortcomings of the early devices and thermistors are now available which are stable with time, matched and interchangeable to within a fraction of a degree over wide temperature ranges.

Thermistors now rival thermocouples in many applications since stable amplification is invariably required with thermocouples due to their low output voltage (typically of the order of 50 μV/deg C). The main advantage of the thermistor over the thermocouple is sensitivity. The output of the thermocouple is determined by the choice of the two metals and cannot be changed.

Typical thermistor bridge or potentiometer circuits can give output voltage changes of 100 mV/deg C which is some 2,000 times that of an equivalent thermocouple. The useful temperature range of thermistors is considerably less than for the thermocouple, being limited to about -100°C to +400°C whereas thermocouples can operate over a range of thousands of degrees. The thermocouple also has a more linear output since its output voltage per unit temperature change is more nearly constant.

THERMISTOR POTENTIOMETER

A simple potentiometer using a thermistor is shown in Fig. 1.7. Obviously the same current flows through both the thermistor and the fixed resistor. If the current is sufficiently small the self-heating of the thermistor will be negligible and its resistance will therefore depend on the ambient temperature. If this temperature rises the thermistor resistance will fall (assuming a negative temperature coefficient) and the current will increase. The resulting increase in voltage across the fixed resistor can be used as an indication of temperature but the voltage-temperature characteristic will not be linear.

The resistance-temperature relationship for a thermistor is usually approximated by the equation


$$R = A e^{\beta/T}$$

where R is the resistance at temp. T° Kelvin, A and β are constants for the particular thermistor, T is the absolute temperature in Kelvin, and e is the base of natural logarithms, 2.7183. By taking logarithms of

both sides of this equation we see that $\text{Log}_e \left(\frac{R}{A} \right) = \frac{\beta}{T}$.

This inverse relationship is sketched in Fig. 1.8.

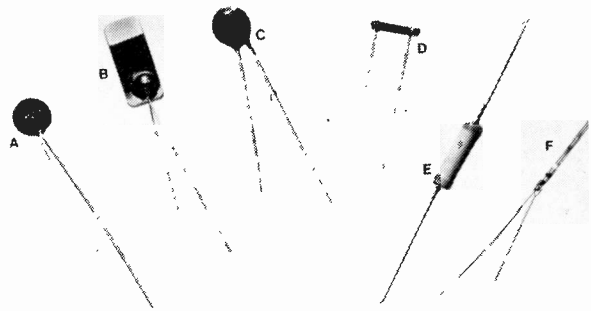For two temperatures T_1 and T_2 and corresponding



A selection of Mullard thermistors, (a) Diac NTC type, (b) Plate NTC type, (c) PTC type, (d) Rod NTC type, (e) Rod VDR type, (f) Bead in glass type

resistance values of R_1 and R_2 respectively we can write:

$$\frac{R_1}{R_2} = \frac{A e^{\beta/T_1}}{A e^{\beta/T_2}} = e^{\beta \left(\frac{1}{T_1} - \frac{1}{T_2} \right)}$$

which shows that the ratio of the two resistances depends only on β for given values of T_1 and T_2 . The value of β usually lies in the range 2,000° to 5,500° Kelvin and is specified by the manufacturer. Also it is usual to quote a typical resistance value at some specific temperature, often 25°C. If the variables with subscript 2 are taken as the given 25°C values, then

$$R_1 = R_{25} e^{\beta \left(\frac{1}{T_1} - \frac{1}{298} \right)}$$

which allows R_1 , the resistance at T_1 Kelvin, to be evaluated in terms of the resistance value at 25°C. For example if a particular thermistor has $R_{25} = 1\text{ k}\Omega$ and $\beta = 5,000$ the resistance at 0°C will be

$$R = 1,000 \left\{ e^{5,000 \left(\frac{1}{273} - \frac{1}{298} \right)} \right\} \Omega = 4,660 \Omega.$$

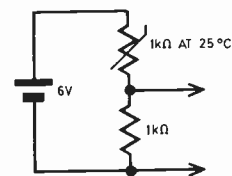


Fig. 1.7. A simple thermistor potentiometer circuit

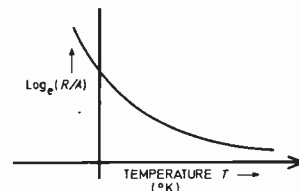


Fig. 1.8. The inverse relationship of temperature and voltage of Fig. 7

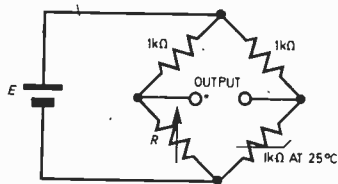


Fig. 1.9. A simple thermistor bridge circuit

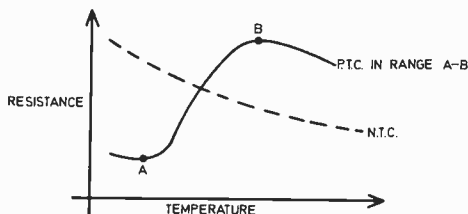


Fig. 1.10. The curves of a positive and a negative temperature coefficient thermistor

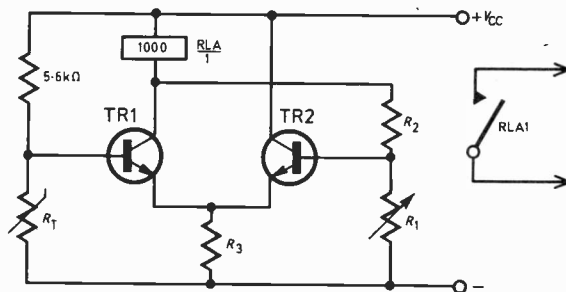


Fig. 1.11. A simple thermistor thermostat

The resistance has changed by nearly five times for a temperature change of 25 deg C.

One disadvantage of the simple circuit of Fig. 1.7 is that the output voltage (across the fixed 1kΩ) will vary with battery voltage which renders any calibration useless. This can be avoided by using a null method as shown in Fig. 1.9.

BRIDGE CIRCUITS

The bridge is balanced, by adjustment of R , to give zero output voltage. For this condition the resistance R and that of the thermistor must be equal and hence the temperature can be determined. Since the bridge circuit is always balanced when a reading is taken changes in the battery voltage have no effect on the null point providing current levels are sufficiently low to prevent self-heating.

When used at low current levels the thermistor responds to the ambient temperature as the measurand. However in some applications the most significant heating effect is due to power dissipated in the thermistor itself. As the current through the thermistor rises, from some initial low value, the voltage drop across the device rises. The onset of self heating eventually occurs and at a certain temperature the voltage stops increasing since the current increase is offset by the falling resistance.

Further increase in current (and power) causes the voltage to fall below this maximum value which is typically in the range 40° to 90°C. The temperature for maximum voltage drop depends on the β factor and ambient temperature. Another feature which is important in some applications is that of thermal time constant. An abrupt change of ambient temperature or power dissipation causes an exponential type change in the thermistor body temperature.

As mentioned earlier the temperature coefficient is large and can be shown to be equal to $-B/T^2$ per degree for negative temperature coefficient devices.

For positive temperature coefficient devices the coefficient is only positive over a finite temperature range as illustrated in Fig. 1.10 and it is usually difficult to express the resistance-temperature variation by a simple equation.


An interesting application of an n.t.c. thermistor is shown in Fig. 1.11 where the circuit behaves as a thermostat by operating the relay when the temperature falls to a predetermined level, say t_0 . Resistor R_1 is set equal to the resistance of the thermistor at the specified t_0 . At temperatures above t_0 the differential action of TR1 and TR2 is such that TR2 is passing current whilst TR1 is off due to the fact that the voltage across R_1 is greater than that across R_T .

As the temperature falls these two voltages become more nearly equal and eventually current starts to flow in TR1 at the expense of that in TR2. The current in TR1 flows via the relay coil and the resulting increase in voltage drop causes the base voltage of TR2 to fall. This further increases the current in TR1 and due to the regenerative action TR1 turns fully on and TR2 turns off.

The relay operates due to the flow of collector current in TR1 which aids the existing relay current that flows via R_1 and R_2 . Due to the positive feedback effect the turn-on is rapid but the temperature will have to rise well above t_0 before the circuit resets itself. This effect is known as hysteresis.

Ideally R_2 should be made 4.6kΩ so that the bridge formed by the four "resistance arms" is balanced at the trigger temperature. Under these conditions the circuit is relatively insensitive to variation of supply voltage V_{CC} . R_3 determines the current levels for TR1 and TR2 once V_{CC} and R_T are fixed. A thermistor, relay and battery in series can act in the same way but operation will be very dependent on supply voltage and the switch-on instant will be less well defined.

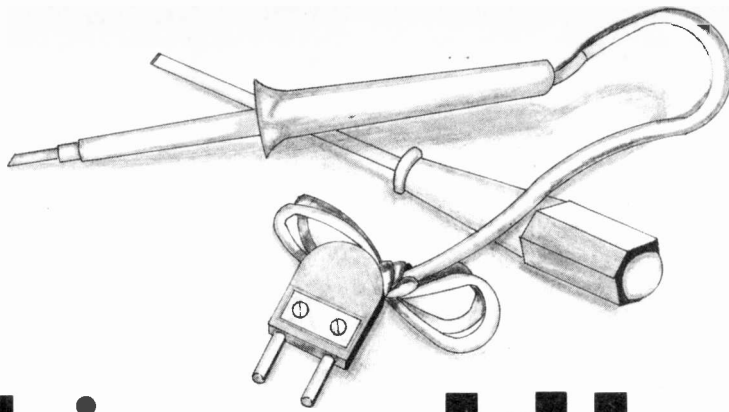Next month: Resistance thermometers, strain gauges, thermocouples and thermopiles.



This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1


Build an oscilloscope.

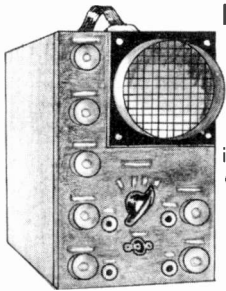

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2

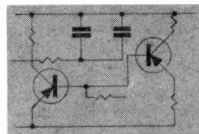
Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

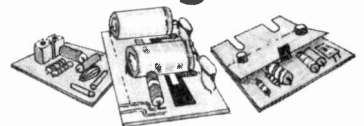
Carry out over 40 experiments on basic circuits.



We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

PLUS

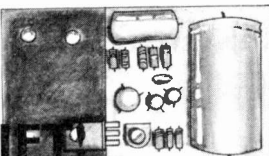

FREE GIFT

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept EL45
P.O. Box 156, Jersey, Channel Islands.

NAME.....
 ADDRESS.....

(Block caps please)

SPARKRITE MK2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

Sparkrite Mk. 2 is a high performance, high quality, capacitive discharge, electronic ignition system. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breaker for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and therefore eliminates the possibility of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)

Sparkrite can therefore give you: up to 20% better fuel consumption, instant all weather starting, cleaner plugs—they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

NOTE—FUEL CONSUMPTION:

The fitting of a Sparkrite Mk. 2 should reduce fuel consumption although the amount of the reduction will vary. A fair estimate of the savings which could be expected, based on reports by our customers and upon our own experience, are as follows:

- any 4-cylinder vehicle, 10% improvement
- any 6-cylinder vehicle, 15% improvement
- any 8-cylinder vehicle, 20% improvement


It is worth remembering that while fuel saving is important there are many other advantages to be gained from fitting a Sparkrite ignition system.

Voted best of 8 ignition systems tested by a leading Motoring Magazine



THE KIT COMPRISES EVERYTHING NEEDED: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5-year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

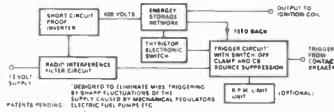WE SAY IT IS THE BEST SYSTEM AT ANY PRICE.



OPTIONAL EXTRAS

Electronic R.P.M. limitation
This can be included in the unit to prevent over revving, an advantage to most companies, hire firms, high performance drivers, etc.

Electronic/conventional ignition switch.

Gives instant changeover from Sparkrite ignition to conventional ignition for performance comparisons, static timing, etc., and will also switch the ignition off completely as a security device. Includes switch, connectors, mounting bracket and instructions. Cables excluded.

PRICES: D.I.Y. assembly kit £10-83*. Ready built unit £13-85* (both to fit all vehicles with coil/distributor ignition up to 8-cylinders).

Switch for instant changeover from Sparkrite ignition to conventional ignition £2-79*. R.P.M. limiting control £2-82* (fitted in case on ready built unit, dashboard mounting on kit).

*Including VAT, post and packing.

We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request. CALL IN AND SEE US FOR A DEMONSTRATION.

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES FLUORESCENT LIGHT KIT

These project boxes are manufactured from 18-gauge aluminium and come complete with lids and screws.

The prices shown include VAT (at 8%) but 18p should be added to the total order value for postage and packing.

Order No.	Length (in)	Width (in)	Height (in)	Price (inc. VAT)
7	5 1/2	2 1/2	1 1/2	47p
8	4	4	1 1/2	48p
9	4	2 1/2	1 1/2	48p
10	5 1/2	4	1 1/2	49p
11	4	2 1/2	2	48p
12	3	4	2	58p
13	6	4	2	58p
14	7	5	2 1/2	75p
15	8	6	3	83p
16	10	7	3	£1-14

Boxes can be made to any size but the minimum order for standard sizes is 500. General trade enquiries welcome.

You can build this reverse polarity protected 12V, 8W, fluorescent light. You will receive all of the necessary parts: white enamelled ready drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, end caps and cable, the fluorescent tube, nuts, bolts and washers, etc., and simple assembly instructions and operating instructions.

When complete the light has a wide variety of uses such as workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping, caravanning or boating, as an inspection lamp and many more.

If you can't spare 1/2 hr to put the light together then we will supply it ready built (for a few extra pence).

PRICES

Assembly kit £3-19 (inc. VAT, post and packing).

Ready built £3-78 (inc. VAT, post and packing).

Diffuser 59p extra (inc. VAT, post and packing).

ORDER NOW

To: ELECTRONICS DESIGN ASSOCIATES DEPT. P. E. 4
82 Bath Street, Walsall WS1 3DE. Phone 33652

From: Name _____

Address _____

Please Supply

Quantity	
	SPARKRITE Mk. 2 D.I.Y. assembly kits at £10-83
	SPARKRITE Mk. 2 ready built negative earth at £13-85
	SPARKRITE Mk. 2 ready built positive earth at £13-85
	Ignition changeover switches at £2-79
	R.P.M. Limit systems in the above units at £2-82
	Fluorescent light assembly kits at £2-19
	Fluorescent light built units at £2-78
	Diffusers for the above at 59p
	of number alum. boxes at _____
	of number alum. boxes at _____
	of number alum. boxes at _____

I enclose cheque/P.O. order for £ _____ Cheque No. _____
(Send S.A.E. if brochure only required)

'CUB' MINI-BLOWTORCH up to 2,500° F

Vest pocket size, yet will braze, silver-solder small jewellery items, etc. soft solder, strip paint, putty, burn-off oiled spark plugs, etc. Burns up to 1 hr on tiny gas cylinder. Complete with 2 cylinders and instruction book.

£2-92 inc. VAT, P. & P.
1010 Soft-solder bit for Cub 82p inc.



'No. 1000 BRAZING TORCH' up to 5,000° F

Combined gases give smaller but much hotter flame than Cub—perfect for all hobby-crafts. Complete with 2 Micronox cylinders, 1 butane, fine-wire silver solder and flux (extra cylinders 80p inc. per 2 of either)

£13-35 inc. VAT, P. & P.


De luxe set, inc. lighter, bench bracket, 6 Micronox, 3 butane, etc. £17-82 inc. VAT, P. & P.

1009 butane-only tip for low temperature work with No. 1000 torch

£1-03 Inc.



NEW! V.H.F. FRONT END/CONVERTOR

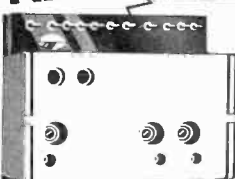

- ADVANCED DESIGN
- DUAL-GATE MOSFET FIRST STAGE

COVERS: AIRCRAFT WEATHER SATELLITES AMATEURS
VARICAP TUNED: INPUT 114-150 MHz
1:F OUTPUT 10-7 MHz

A high performance front-end combining high gain with low noise factor (8dB typ.). Each unit is fully tested and aligned before leaving the factory

PRICE £9-85 (includes VAT and P. & P.)

Sole Agents: REEDHAMPTON LTD., 182-184 Addington Road, Selsdon, Surrey, CR2 8LB

MICROFLAME (UK) LIMITED

'Freepost', Rickinghall, Diss, Norfolk, IP22 1BR. Tel. Botesdale (037-989) 555



BY FRANK W. HYDE

PHOBOS THE POTATO MOON

During the mission of *Mariner 9* to make a photographic survey of Mars, some 32 high resolution pictures were obtained of Phobos, the small Martian moon. These pictures were fortunately able to cover some 80 per cent of the satellite's surface and the first atlas of this small moon has now been published. These have been "cleaned up" using the special computer technique. The atlas was compiled by a group of scientists from Cornell, Stanford, Caltech and NASA, four very active establishments.

It is common practice, in setting up an atlas, to use a sphere on which the pictures can be placed and oriented. However, Phobos presents a special problem of its own for it is irregular in shape, more like a potato. It is thought that as the satellite has such a very small gravitational field it has not been pulled into a harmonious shape as it cooled. It is perhaps a quirk of cosmological humour that it so closely resembles the familiar potato.

Many models were tried out and T. Duxbury at Caltech finally arrived at a solution. The satellite radii are found to be 11.5, 15.5 and 9.5 kilometres. Duxbury settled on a triaxial ellipsoidal system of co-ordinates.

This reference grid was computer-fitted with the information and the results suggest that Phobos is in synchronous rotation around Mars. It keeps the same face to Mars and therefore behaves as the Earth's own satellite. The longest axis points toward Mars and the intermediate one of 11.5 kilometres is in the orbital plane, the shortest axis being normal to the plane.

Phobos is very heavily cratered and the surface density is close to saturation. The initial mapping reveals some 50 craters. Seven have been given names though one is only a partial crater. This is the Kepler Ridge. Others are named Roche, Wendell, Sharpless, D'Arrest, Stickney. The variations of the high to low points of the craters are as much as 20 per cent of the radius.

When compared with the Earth's Moon the feeling is that Phobos was formed as an independent unit very early in the life of the Solar System. Extensive fracturing seems to have taken place as a result of meteoritic impacts. The landscape appearance has been the result of meteor impacts. No doubt also the smallness of the body renders it liable to considerable geological change.

The structure generally suggests that Phobos is solid rock and the evidence is the manner of the cracks that can be seen. There is too little gravitation for it to be conglomerate. It is possible that the satellite is only part of a larger body that disintegrated a very long time ago.

As with all these "guestimations" alternatives are also offered. Whatever the conjectures may be there is now a good case to include a special programme to be set in operation at the time of the Mars *Viking* missions already planned.

HELIOS

In a past "Spacewatch" issue some details of a planned space probe were given. This or rather the first of two probes called *Helios* has been launched on behalf of West Germany by NASA.

The project was given the go-ahead in 1969. The probes weigh some 357 kilograms and will operate with a 192 day orbit. They will, at the apogee point, be within 45,000,000km of the sun, about one-third of an astronomical unit. Special thermal control will come into operation on these missions.

The first probe will steer into the ecliptic, the plane of the Earth's orbit, between Mercury and the Sun. Its final distance from the Earth will be some 300,000,000km. The primary mission will last 120 days. However, the life of the probes will be at least 18 to 20 months.

These two probes will also be supplementary, in the sense of data gathering, to that being obtained by *Explorer 47* and *50* and also that from *Pioneers 10* and *11*. The actual orbit of the probes will have a perihelion of 0.3 of an Astronomical Unit and an aphelion of

about 1.0 Astronomical Unit with respect to the Sun.

The tasks set are very extensive, the instruments will investigate the magnetic field, density, speed and direction of the Solar Wind particles (electrons, alpha particles and protons). It will be possible to evaluate the spatial gradients involved in those quantities. The study of the electron plasma oscillations will be made by radio which exhibits the characteristic Type III outbursts.

Other experiments will look at the interplanetary dust, its gradients, density and direction and its exact composition. X-ray examination of the surface of the Sun will be undertaken.

ODD BODY

Helios is an unusual shape for a probe with a 16-sided central body and truncated cones top and bottom, each with 16 facets. The solar cells are disposed over the surface of the probe.

Because of the extreme temperatures involved, some 370°C, nearly 90 per cent of the Sun's radiation must be reflected. This makes very stringent demands on the probe's thermal regulation system. The solar cells may not be subjected to a greater temperature than +165°C. The interior temperature must be kept within the limits of -10°C to +20°C.

This problem is partially solved by using special SSMs, second surface mirrors, developed by NASA. They are made from fused silica and covered on the underside by a thin film of silver which is further covered by a dielectric. These cells have a high emissivity and will prevent the central body from heating up to 800°C. This is the sort of temperature to which the aerial will be subjected when extended even though the probe is revolving at 60 r.p.m.

However, the mirrors alone are not sufficient to hold off the Sun's radiation which amounts to some 22,400 watts/sq.m. A special thermal insulation system consisting of layers of spaced metallised foil is also used. The foil is held apart by nylon mesh to avoid heat bridges. Other ingenious controls consist of bimetal levers which operate the louvres to allow the experiments to be carried out. They are also used to control the inside temperature.

Control of the mission is being carried out at the Command Station at Weilheim, Germany, with a 30 metre dish built specially for these missions. Also in use for transmission of commands and the reception of data is the Planck Institute 100 metre radio telescope at Eifel.

Strictly Instrumental

by K. Lenton-Smith

IN AN earlier article in this series, we mentioned that the roots of electronic music went back some 150 years. Two Americans, C. G. Page and C. E. L. Delezenne experimented with rotary generators and their findings were published in scientific journals of the time. However, it is probably more accurate to assume that 40 years is the life-span of electronic music as both L. E. A. Bourn and Laurens Hammond perfected their respective electrostatic and electromagnetic generators in 1935.

Among other inventions in this era, the Compton Electrone and the Hammond organ were soon to make the public aware that electronic musical instruments were a practical proposition and here to stay. Dr Robert Moog's voltage-controlled circuitry (circa 1960) gave this field a new fillip: it offered another method of musical self-expression, albeit the player had to be technically inclined, patient and equipped with special recording apparatus.

IMPERSONAL

Compared with this relatively short life, conventional musical instruments have been developed over the centuries by ingenious craftsmen: they have been improved to the point of near-perfection and in the main are capable of extreme expressiveness in the hands of a skilled performer.

I was recently asked to give a lecture on "Electronic Music" to students of an eminent classical pianist. Various forms of electronic music, previously edited on stereo tape, were played to the audience, including music concrete, the classical organ and light music. A bench demonstration was carried out to show various methods of tone-generation, waveforms, tone-forming, keying and synthesiser operation. Finally, this orthodox audience was asked to express views.

"You hug a cello", commented the eminent pianist, "kiss a flute and stroke a piano. You have a quasi-

erotic relationship with your instrument. Can this be so with electronic instruments? They sound too precise."

My reply was that, if you build your own instrument, you often go to bed with it! This remark was made with conviction, having built four organs over the years and burnt considerable midnight oil. Although it is literally true to say that electronic instruments certainly are "alive", his point was a valid one, as the reader will appreciate. Even so, the player can become equally attached or infatuated with his electronic instrument.

Perhaps we had invited the comment by playing tapes of both the "William Tell Overture" and part of the second movement of "Beethoven's Ninth," first by an orchestra then the Moog's imitation of it. The complexity of imitating an orchestral score on a synthesiser using multi-recording techniques is enormous, but the same performer adding line after line to his recording should be able to get timing closer than the many individual players of the concert orchestra. Indeed, the tape is often run at half speed and the parts played an octave lower than usual: when replayed at normal speed, the somewhat objectionable effect of mechanical precision is heightened.

ONE NOTE

The polyphonic synthesiser (the ability to play chords rather than single notes) is still rare, so perhaps the main objection to the instrument at present is that painstaking time and effort are involved in using it. Any solo acoustic instrument could be re-recorded in four-part harmony, provided its compass was great enough: a laborious process, but Les Paul was doing this 20 years ago with his guitar "orchestra". In its imitative capacity, at least eight tracks would be used with the synthesiser, the registration changing every few bars.

Until the polyphonic variety becomes commonplace and the cost economic, the majority of serious,

non-technical musicians will give the synthesiser a wide berth. Musical readers of P.E. are probably not typical as their interests will be technical: let's face it—the constructional articles by Douglas Shaw and Alan Boothman call for a high standard of technical ability and understanding if the correct results are to be obtained.

THE TREND

Our educational system should ensure that music has full rein in years to come. At the same time, the rising number of flat-dwellers makes the ordinary piano something of a problem in their homes. So the electric piano might well become more common, albeit the 5-octave manual imposes its limitations (an 8-octave instrument would present no technical problems, but would defeat the object by taking up the same space as an upright). The harassed parent could provide budding pianists with headphones through the five-finger exercise stage—surely a selling point!

Craftsmanship is rapidly becoming scarce. The special skills required in making violins, for instance, may become both expensive and hard to find as time passes. Woodwind, brass, pianos—indeed all acoustic instruments — are craftsman-made and inflation could make these difficult to afford for future generations.

CONTROL

Although electronic components are currently in short supply, they ought to remain relatively cheap in this age of technology. So there is a strong possibility that electronic musical instruments will progressively supplement—or even supplant—acoustic instruments in classical music.

Where money is to be earned in music, it is certainly not in the serious field. Pop groups have proved that they have money (and even instruments) to burn! Many of them use synthesisers and other sophisticated equipment, but the end-product is often hideous!

If the serious music fraternity looks with trepidation to the future, it will have to come to terms with electronics and start to lay down guidelines to manufacturers for the types of electronic instrument it would like to see made. Failing this, pop groups will continue to give the impression that cacophony is the only end-result, to the detriment of electronics and good musical taste.

CHROMASONIC electronics

Dept. 2. 56, Fortis Green Road,
Muswell Hill. London, N10 3HN.
telephone: 01-883 3705

RECTIFIERS				BRIDGES				TRIACS		SOLDERING		
V	1A	3A	6A	12A	V	1A	2A	6A	4A	Desolder Braid Reel 64p		
50	IN4001	63p	IN5400	153p	BYX61	-50	£3.21	50	25p	35p	75p	<p>Multicore 18 swg size 5 32p 22 swg size 15 36p carton size 1 50p " " 121.57</p> <p>Adcolia Invader L706 19Watt 1/8" bit £2.88 L646 23 Watt 3/16" bit £3.13</p>
100	IN4002	73p	IN5401	163p	BYX61	-100	£3.48	100	20p	40p	78p	
200	IN4003	9p	IN5402	173p	BYX61	-200	£3.76	200	22p	45p	90p	
400	IN4004	9p	IN5404	273p	BYX61	-400	£4.29	400	25p	50p	£1.05	
600	IN4005	11p	IN5406	28p	BYX62	-600	£4.29	600	25p	50p	£1.20	
800	IN4006	13p	IN5407	28p	BYZ10		65p	800	38p			
1000	IN4007	16p	IN5408	31p				1000	38p			

DIN CONNECTORS				4mm		HEAT SINKS	
	Pins	Plugs	Sockets	Line Couplers	Available in seven colours	Transistor covers	
	2	9p	7p	11p	Terminals 15p	TO 3 10p	TV2 (TO64) 15p
	3	10p	7p	11p	Plugs 13p	TO 66 10p	TV3 (TO 3) 16p
	4	11p	7p	11p			TV4 (TO 126) 14p
	5 (180)	11p	8p	11p			TV5 (TO 220) 14p
	5 (240)	11p	8p	11p			5F (TO 5) 7p
	6	11p	8p	11p			173 for SL414 SL415 183p
	7	13p	9p	11p			AY-1-4 35p

CO-AXIAL		I.C. SOCKETS	
Plug - Screened	11p	U1 (T8A800)	16p
Plug - Plastic	9p	U1 (T8A8105)	16p
Sockets		U2 (T8A810AS)	16p
Chassis	103p	U2 (TCA940)	16p
Surface	11p	U3 (TDA2020)	35p
Coupler	25p		

AUDIO I.C.'S

A brand New Audio I.C. Leaflet with Circuits and pin connections for ALL the I.C.'s listed below FREE with orders over £1.00 or 10p without

PHONO	
Sockets	
1 way	5p
2 way	7p
3 way	7p
4 way	8p
Plugs:	
Plastic Moulded	73p
Chrome Screened	123p
Coupler screened	13p

JACK	
Plugs	Sockets
2.5mm *	20p 12p
3.5mm *	20p 12p
standard *	25p 15p
stereo *	27p 21p
side entry standard	48p

* screened

SWITCHES	
High Quality 250v 1A	Rotary 2A Mains Switches
S.P.S.T 25p	35p
D.P.D.T. 45p	Bulgin
Render	push-to-make 25p
Subminiature Toggle S.P.D.T. 48p	Ergo D1 Switches
Slide D.P.D.T. 12p	1 pole 8 way 99p
	2 pole 4 way 85p
	4 pole 2 way £1.24
	LaFin Water Switches 27p
	1 pole 12 way; 4 pole 2 way
	3 pole 4 way; 4 pole 3 way

POWER OUTPUT WATTS	Supply Volts	Load Ohms	Style	Power I.C.	Price	Pre-Amplifiers	Simply Volt	
0.25	9	16	C	MFC4000B	78p	Dual Low Noise +24	A LM381	£2.16
0.5	9	8	E	MC1306P	68p	Dual Low Noise +24	A LM382	£2.19
1	9	8	F	TAA300	£1.76	Dual Pre-Amp +24	A MC1303L	£1.59
2	12	8	G	T8A820	74p	Dual Low Noise +12	A MC1339P	£1.31
2	18	8	A	LM380	£1.08	Dual Low Noise +15	A T8A231	88p
2 1/2 + 2 1/2	18	8	A	LM377	£2.91	General		
3	18	8	J	SL414	£1.72	D.C. Controlled attenuator	MFC6040	83p
5	24	16	J	SL415	£2.24	3 stage G.P. amp.	8 TAA263	90p
5	24	8	H	T8A800	99p	Type Pre-Amp	F TAA310	£1.34
7	16	4	H	T8A8105	£1.07	8i-Fat	8 TAA320	95p
7	16	4	K	T8A810AS	£1.07	Head/Aid Amp 1.3v	1 TAA370	£2.07
10	20	4	M	TCA940	£1.94	PPL stereo decoder(i)	A MC1310	£2.14
15	30	3	O	BHA0002	£2.60	4 channel SQ * (ii)	A MC1312	£2.42
35 driver	25	8	F	NE540L	£1.08	4 * pre-amp (ii)	16 MC1314	£4.05
20	+15	4	N	TDA2020	T8A	CBS SQ Logic (ii)	16 MC1315	£5.37

(i) & (ii) Separate leaflets available free only with purchases over £1

I.C. SOCKETS	
TO5 Style	Dual-In Line
8 pin	8 pin 13p
14 pin	14 pin 15p
16 pin	16 pin 15p
24 pin	24 pin 26p
28 pin	28 pin 30p
36 pin	36 pin 39p
40 pin	40 pin 44p

P.C. CONNECTORS	
0-1" pin centres 24 way + key	supplied with ends 64p

Etch resist from a pen. Draw your own printed circuit, then etch it. 84p

MAINS TRANSFORMERS			
6-0-6v, 100mA 97p	20-0-20v 1A £4.55	secondarys	
9-0-9v, 100mA 97p	24-0-24v 1A £2.48		
12-0-12v, 100mA 97p	28-0-28 1A £6.18		
18-0-18v, 200mA plus	0-24v 40mA 97p		
	1A 2A 4A		
0-9-17v	£1.95	£2.27	£2.64
0-12-15-20-24-30v	£2.48	£4.15	-
0-24-30-40-48-60v	£5.18	£7.02	-
	1A 1A 2A		
0-19-25-33-40-50	£2.70	£3.40	£4.53

RENDAR INSTA-POWER

safe, inexpensive, quick, A.C. mains connector. A 13 amp plug top containing snap connectors £1.75

VAT INCLUSIVE PRICES AT 8% OVERSEAS CUSTOMERS DEDUCT VAT INVOICES ON REQUEST! P&P On UK Order- 15p Overseas Orders at Cost

If you're interested in electronics You'll like the NEW LITESOLD SUPER IRONS

We've been supplying the electronics industry with soldering irons for many years and we have now put all our experience into an iron for the electronics enthusiast.

The new LITESOLD SUPER IRONS have all the features you have been looking for; a neon indicator which glows only when the supply is connected correctly and the iron is safely earthed, an unbreakable nylon handle, a burn-proof mains lead, a special oxydised binding, a long life element, a range of bit shapes to suit every job and a special bench stand.

There are three SUPER IRONS

- the S90
12 watts for miniature jobs
at £4.77
 - the S142
20 watts for medium jobs
at £4.85
 - the S187
24 watts for heavy jobs
at £4.89
- and the special spring stand at £2.24.

Get your LITESOLD SUPER IRON direct from

**Light Soldering
Developments Limited**
97-99 Gloucester Road
Croydon Surrey
Telephone 01-689 0574

All prices include postage, packing and VAT but not the diamond ring.



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**So fast, so easy,
this personalised course
will teach you even if
you don't know a thing
today!**

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

**Send now for FREE
76 page book—see how
easy it is—read what
others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**No soldering—yet you
learn faster than you
ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. AT NO EXTRA CHARGE! And this is a course anyone can afford. (You can even pay for it by easy instalments.)

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CPE 02
READING RG7 4PF


CPE02

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS

POSTCODE




BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

P.E. KIT REVIEW

SINCLAIR SCIENTIFIC CALCULATOR

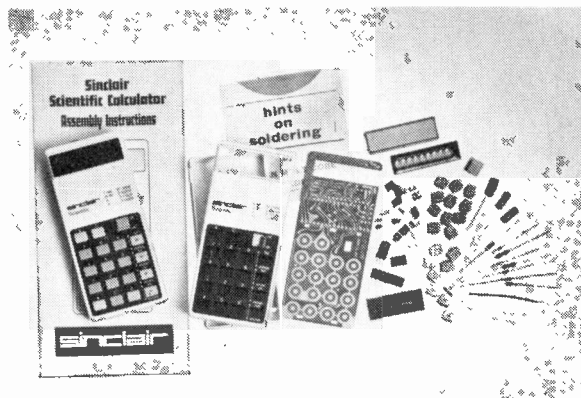

BUILDING THAT COUNTS

The pocket calculator is now firmly entrenched as a part of our way of life. It appears in almost every shop window alongside stationery, toys, cassette recorders and sweets. It comes in various forms extending from the simple four-function up to the sophisticated multi-function accountant's and engineer's dream, and can be acquired in the ready-made or even the kit style.

Recently just such an instrument became available, the Sinclair Scientific, which utilises Polish notation and logarithmic and trig functions to carry out calculations currently only available in far more complex machines.

THE KIT

The Scientific kit comes carefully wrapped and packaged in a compartmented foam plastic moulding complete with all parts, very comprehensive instructions and a variety of guarantee conditions suited to those who either fail or meet problems at the constructional stage.

Assembly is certainly simple if one has had prior experience with i.c.s, soldering and plastic models, but it should be stated that the job is not one for the totally inexperienced if they also have no tools. For example, a quality miniature soldering iron is a must and miniature sidecutters and snipe-nosed pliers a very useful adjunct.

The writer found a need for a model-maker's scalpel at one stage in gaining a tight fit of the keyboard assembly in the very nicely designed outer case. A small amount of mould flash was intruding on the area to be occupied by the keyboard.

In fact assembly went ahead smoothly and without any real hitch thanks to the clear and precise instructions. Indeed these are directed to all possible purchasers and take the uninitiated right through the various problems to be met such as tools, handling calculator chips, cleanliness and so on in a very helpful manner.

The only part of the assembly which might pose problems to some concerns the keyboard and here it would be wise for any first-timer to follow the instructions very carefully. Its not that one damages the unit in the process, more that one has to do the job several times to get it right.

In fact, the case and mechanical assembly tend to appear to be somewhat flimsy on first inspection but the design is quite interesting, making use of the inherent flexibility and strength of the plastic material to give at one and the same time a strong and attractive case. The external appearance is not marred by fixings of any sort and yet it is a simple matter to take apart and reassemble the case.

The only point of serious criticism which came to light concerns the battery connectors. In the Scientific as in most of the Sinclair range made to the same standard, use is made of small plated spring clips which are soldered to the circuit board. These at one and the same time form the connectors and retainer clips for the batteries. Whilst each clip has a projection which engages in a hole in the board, this effects location rather than mechanical retention, so only the soldered joint provides the necessary strength.

Under normal desk use this is no problem, but the vagaries of pocket use over a period of three months have caused one terminal to come loose twice. The first time the soldering was questionable and the second occurred within a few days of first use anyway, so the problem appears to be removed with due attention to one's soldering.

OPERATION

In use the Scientific takes some time to acclimatise to. Unlike its four-function associates such as the Cambridge, it makes use of so-called Polish notation for the normal four-function mathematics. Thus to add A and B one enters A+ and then B+. Take B from A one enters A+ and then B-.

Equally, it requires "programming" by way of pushing one of two extra buttons in order to carry out

the extra functions such as providing logs and trigonometric functions.

However, this is little hardship for the results obtained. The machine is sufficiently small to fit into the palm of the hand and be operable by the thumb of that hand if one wishes to show off just a little.

Clearly, at such a low cost and in such a small package, one cannot expect to get all the refinements of a £400 equipment or even, for that matter, of an £80 item. However, the Scientific gives results well in keeping with the job it is supposed to do. For example, taking the value of logs it gives. All those tried by the writer have matched four figures tables and, indeed, six figure tables most of the time. Of course, the machine only indicates to five figures, and to some this might be a disadvantage.

One or two simple tests indicate the value of the machine. Take 2^{64} up to that value and then back down again to 2, The result is 2.0001. Not bad.

Some of the Trig functions seem, in the face of accurate tables, to leave something to be desired, and it is wisest to learn just when one ought to bring a calculation out of the machine and make suitable notes in this area.


So far any errors of note on the Scientific have been clearly traceable to the user and not the equipment and the more one uses it the easier it becomes to replace the slide rule.



Rear view of the calculator showing the i.s.i. main chip and display driver

£14.95
INC.
VAT

ESP DETECTOR

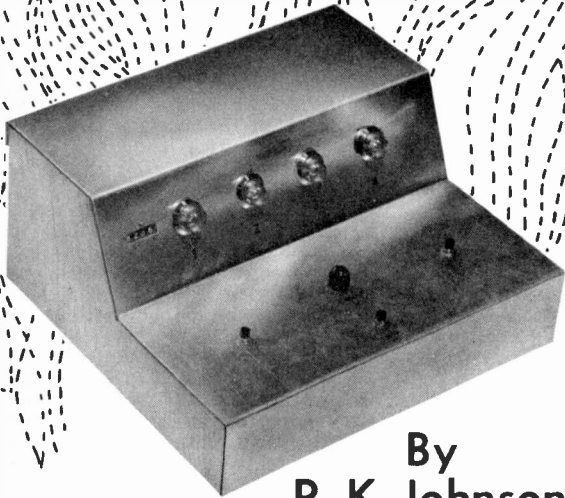

By
R. K. Johnson

EXPERIMENTS to detect the existence of Extra Sensory Perception (ESP) normally involve two people: the subject being tested and an operator to turn over cards and record their symbol or value. A common problem in these experiments is a gradual reduction in performance due to boredom and lack of interest.

The electronic apparatus described here was developed so that the subject alone could test himself and so that interest could be maintained by introducing a game element into the testing by using "biofeedback".

CONTROL LAYOUT

The layout of the detector and its controls are shown in the photographs. When the **SPIN** button is pressed the circuitry oscillates until the button is released when the circuit freezes at either "left" or "right".

The **CHOOSE** lamp lights to indicate that a choice must be made between left and right. The subject then presses either the **LEFT** button or the **RIGHT** button. If he has chosen correctly, lamp **LP1** lights, the **CORRECT** counter counts on by one digit and the **TOTALS** counter (at the rear) also counts on by one digit.

If he guesses wrongly, only the **TOTALS** counter is activated. The **SPIN** button is used again to spin left or right and the subject chooses again and so on. If the subject makes two successive correct guesses, then lamp **LP2** lights as well as lamp **LP1** (and both counters count on one).

As long as he makes more correct guesses, more lamps light until all four are illuminated and these stay illuminated so long as he guesses correctly. If he chooses the wrong button, all the lamps go out and he must begin again, trying to build up a row of lights. If required, the counters provide information for statistical analysis.

THE SYSTEM

The circuit is largely composed of cheap 74-series TTL integrated circuits. The block diagram is shown in Fig. 1 and the detailed logic in Fig. 2.

Block **MV1** is an astable multivibrator which alternates high and low or "left" and "right" at about five thousand times per second.

It may be made to oscillate at a higher frequency if required by reducing the values of two capacitors **C1** and **C2**. In any case these capacitors should have equal capacitance so that the multivibrator spends equal lengths of time in its "left" and "right" positions.

There is no possibility of the operator guessing the state of the circuit by the length of time he presses the **SPIN** button because the multivibrator is spinning all the time, not just when the **SPIN** button is pressed.

The output from the multivibrator is fed to the clock pulse input of a 7472 gated J-K flip-flop (**BS1**), which will not accept the pulses from **MV1** unless all **J** and **K** inputs are at logic 1. (Positive logic is used throughout, i.e. logic 0 equals zero volts and logic 1 equals about +4 volts). These **J**, **K** inputs are controlled by **SPIN** switch **S1** coupled to a "bistable latch" (**L1**).

The bistable latch is required to overcome problems of switch contact bounce and is formed from two of the **NAND** gates in a 7400 pack.

When **S1** (whose wiper is earthed) is in position "a" so that input "a" is at logic 0, input "b" is at logic 1. Output **C** is then at logic 1 and output \bar{C} , at logic 0, is connected to the **J**, **K** inputs of **BS1** (see Fig. 2). If **SPIN** switch **S1** is pushed so that contact "b" is earthed, the outputs **C** and \bar{C} of the bistable latch reverse, the **J**, **K** inputs of **BS1** are then at logic 1 and the output from multivibrator **MV1** is accepted into flip-flop **BS1**, causing the outputs (**Q** and \bar{Q}) to alternate at 5kHz.

If **S1** is released so that contact "a" is earthed, output \bar{C} goes to logic 0, thereby freezing flip-flop **BS1** in either a "left" (**Q** = 1, \bar{Q} = 0) or "right"

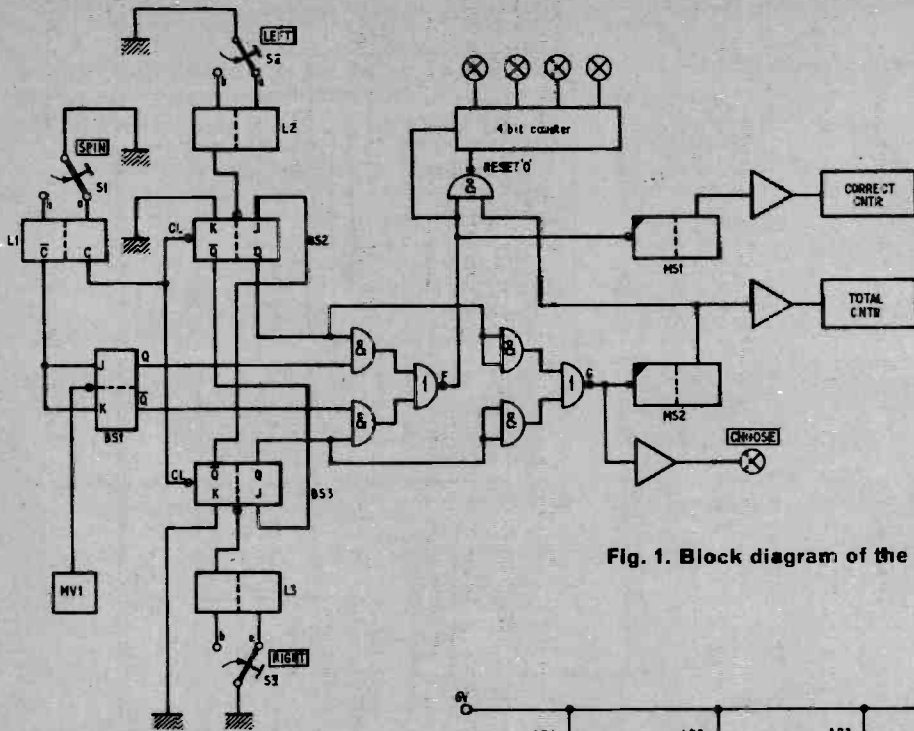


Fig. 1. Block diagram of the ESP Detector

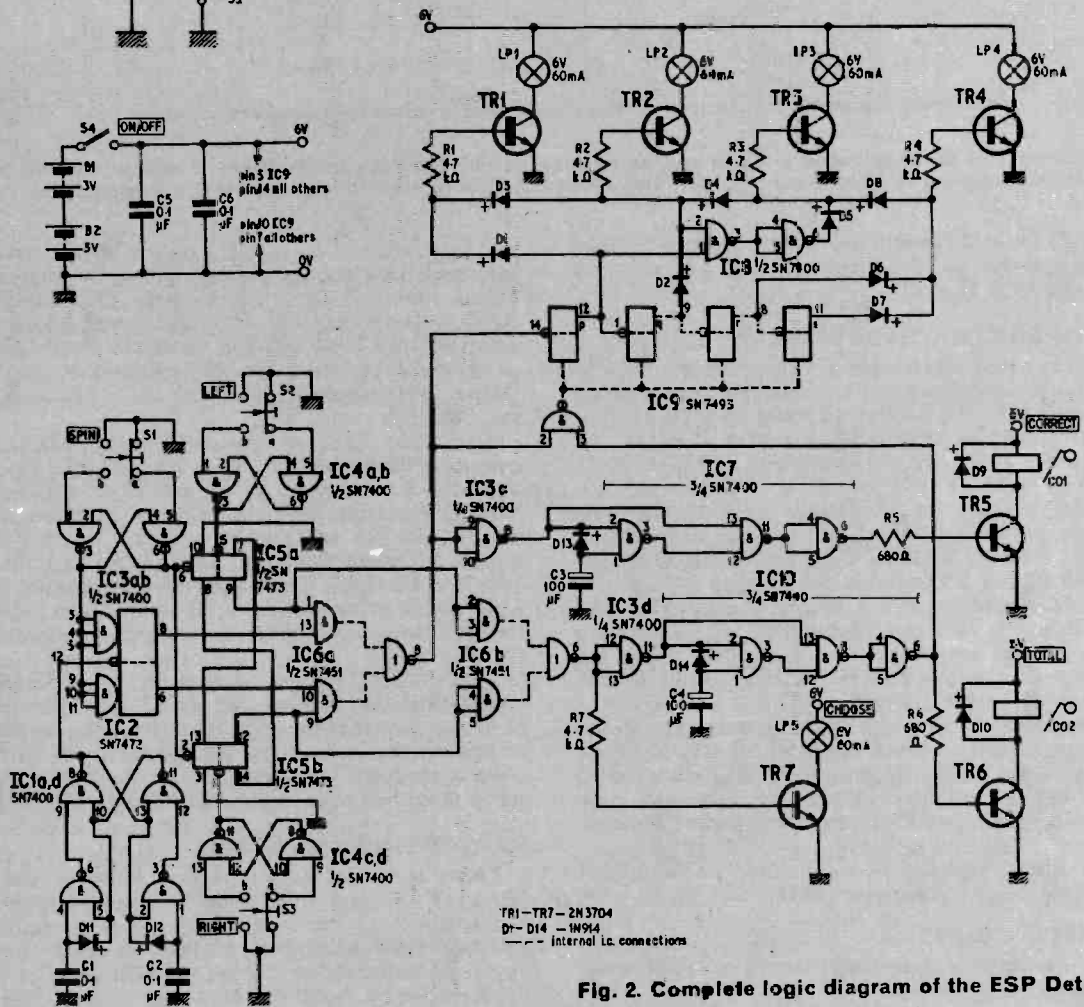


Fig. 2. Complete logic diagram of the ESP Detector

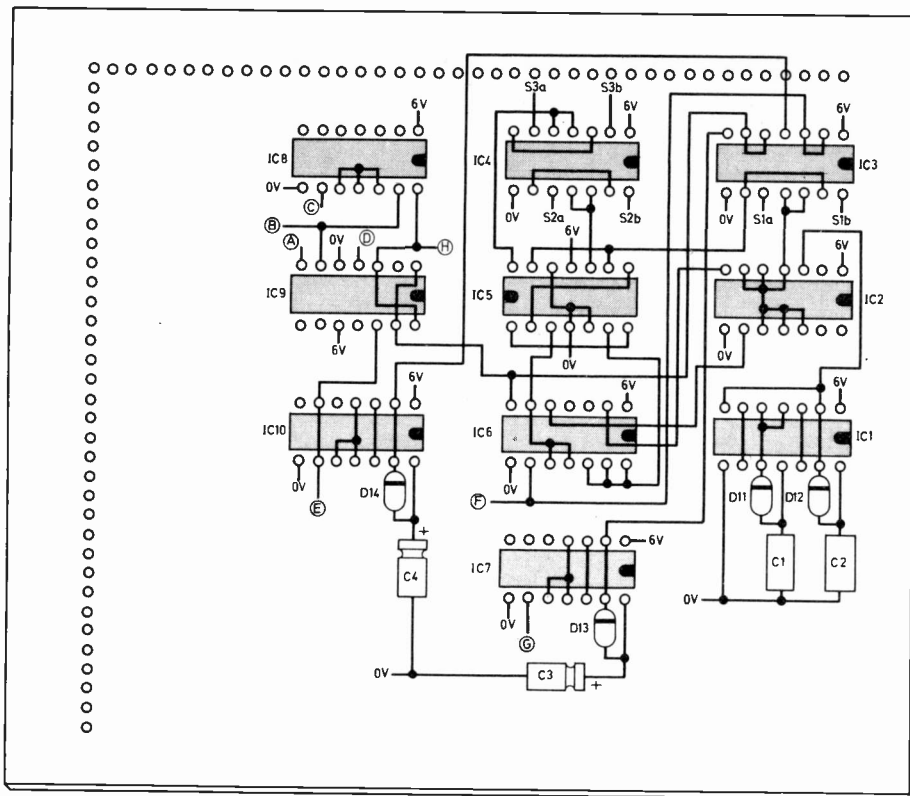


Fig. 3. Layout of the integrated circuits and associated components on the perforated board. Circled letters indicate connections to Veroboard (Fig. 4). This shows the board viewed from below (i.e. wiring side)

($Q = 0, \bar{Q} = 1$) condition. This condition is then to be guessed by the operator and his response compared with Q or \bar{Q} .

THE OPERATOR RESPONSE

The LEFT and RIGHT operator-response switches S2 and S3 are each connected to a bistable latch formed from each half of a 7400 quad NAND pack (IC4). The output from each bistable latch is fed to the clock pulse input of a JK flip-flop (BS2 or BS3), contained in pack IC5 which is a 7473 dual J-K flip-flop. Initially the Q outputs of both BS2 and BS3 are at logic 0, but after the operator's input from L1 with S2 or from L2 with S3, the Q output of either BS2 or BS3 will change to logic 1.

The Q output of BS2 with the Q output of BS1 is fed into one AND gate of one half of a 7451 dual 2-input AND/OR/INVERT pack IC6, while the Q output of flip-flop BS3 with the \bar{Q} output of BS1 is fed into the other AND gate of IC6a.

If the operator has guessed correctly (i.e. if the Q output of BS1 and the Q output of BS2 are both at logic 1, or if the Q output of BS3 and the Q output of BS1 are both at logic 1), then, and only then, will the output F change from logic 1 to logic 0.

This output F is fed to an inverter whose output is connected to a monostable (MS1).

CORRECT COUNTER

The monostable was built using a 7400 quad NAND pack.

When (after a correct guess) the signal from the inverter goes from logic 0 to logic 1, the monostable output rises to logic 1 for about 0.1 seconds. Passed through base resistor R5, this signal drives TR5 into an "on" condition for an equal length of time so that the CORRECT counter counts on one digit. Diode D9 protects TR5 from the back e.m.f. of the counter's coil.

The other half of AND/OR/INVERT pack IC6 is used to detect whether either BS2 or BS3 has been activated by switch S2 or S3 and if so, it then activates monostable MS2 (through an inverter), which drives TR6 to energise the TOTALS counter. The output G (changing from logic 1 to logic 0) also switches off TR7, to switch off the CHOOSE lamp. This lamp remains off until the circuit is reset through switch S1 when the output G again rises to logic 1.

The resetting of the activated flip-flop BS2 or BS3 (depending on whether S2 or S3 was pressed) is obtained at the same time that the SPIN switch S1 is pressed, by connecting the output from latch L1 (which changes from logic 1 to logic 0 as S1 is pressed) to the CLEAR inputs of both BS2 and BS3.

PREVENTING CHEATING

There is a further connection between the two flip-flops BS2 and BS3: the \bar{Q} output of each half is connected to the J input of the other half and each K input is earthed to logic 0. This ensures that once either S2 or S3 has activated one of these flip-flops, then both flip-flops are locked and are

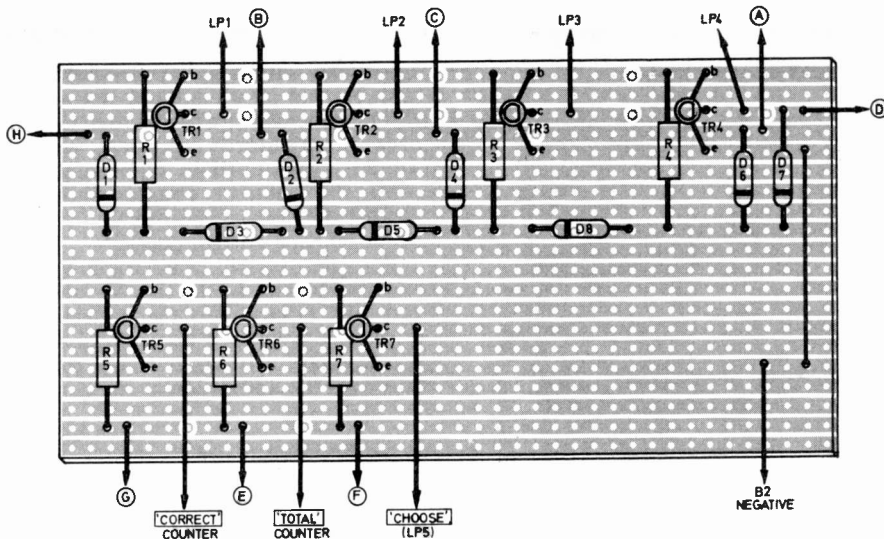


Fig. 4. Layout of the transistor circuits on the Veroboard panel

not affected by further operations of S2 and S3. This prevents the operator from trying one switch and then the other and from pressing one switch repeatedly to increase his score.

LAMP DECODING AND DRIVING

The remainder of the circuit consists of IC9 and IC8, the row of lamps LP1 to LP4 and their drivers (Fig. 2). Pack IC9 is a 7493 4-bit binary counter containing four flip-flops p, q, r, s and a NAND gated reset. The F output (which indicates correct guesses) is fed to the input of IC9. If only one pulse is fed into IC9, the output of p is at logic 1 while q, r, s are at logic 0. The p output is routed via diode D1 and R1 to TR1 which switches on lamp LP1.

If another pulse is received, p goes to logic 0 and q goes to logic 1 which is routed via diodes D2 and D3 to both TR1 and TR2 so that both lamps LP1 and LP2 light. Similarly for three pulses, both p and q are at logic 1 and their outputs are combined by gates (two of the NAND gates in 7400 pack IC8; the other two gates are not required).

Diodes D4, D5 and D3 ensure that three lamps light. For higher numbers of correct guesses (up to fifteen), the logic 1 outputs of r and s are routed via diodes D6, D7, D8, etc. so that all the lamps light. These lamps remain on so long as the two inputs to the reset are not both at logic 1. However, if the operator guesses wrongly, the output F will remain at logic 1 and the output of MS2 will rise to logic 1, thus operating the NAND reset and switching off the lamps.

While all this may seem rather complicated, the actual construction is straightforward.

CONSTRUCTION

In the prototype, the ten i.c.'s IC1 to IC10, the capacitors and the diodes D11 to D14 were mounted on 0.1in matrix plain s.r.b.p. board. See Fig. 3 and the photographs. Alternatively, 0.1 matrix Veroboard may be used providing the strips are cut away so that each i.c. is isolated from the others.


The connections for each of the i.c.'s (viewed from underneath) are also shown in Fig. 3.

The suggested order of construction is:

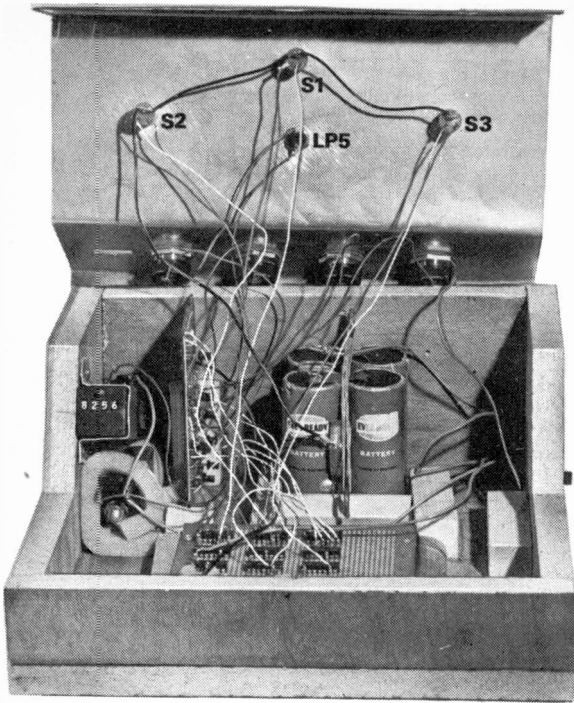1. After labelling each i.c. from beneath the board, make the common connections between pins on the same i.c., working from Fig. 3. Use a soldering iron with a small bit and low power, touching the pins on the i.c. for the least possible length of time.
2. Make the interconnections between the i.c. soldering as before and working methodically. These connections are most easily made with colour coded wire and as each connection is made, it should be ticked off on Fig. 3.
3. Connect diodes D11 and D12 to pack IC1. Connecting pins inserted in the matrix holes are useful here.
4. Similarly with diode D13 to pack IC7 and D14 to pack IC10, capacitors C1 and C2 to pack IC1, C3 to pack IC7 and C4 to pack IC10.
5. Connect the common earthed (negative) line to all the i.c.'s. This should go round all the i.c.'s like a ring main circuit.
6. Connect the common positive line round all the i.c.'s.
7. It is recommended that the supply line is decoupled every five packs by connecting capacitors C5, C6 between the positive and negative lines at two points on the board (see photograph).

All the lamp drivers and counter drivers are mounted on Veroboard. Fig. 4 shows the gaps to be cut in the copper strips and the component layout.

Rewind the coils of the two counters if they are not already six volt operating. In the prototype the counters were standard PO 4-digit non-resettable with an operating voltage of about 24V. These were dismantled to gain access to the solenoids from which all the turns of 40 s.w.g. wire were removed. The coils were then rewound with as many turns as possible (as neatly as possible) of 32 s.w.g. enamelled copper wire. The counters, when reassembled, should operate easily and firmly on 5V or less (drawing 150 to 200mA).



Photograph showing the internal layout of the ESP Detector

COMPONENTS . . .

Resistors

R1-R4 4.7k Ω (4 off)

R5, R6 680 Ω (2 off)

R7 4.7k Ω

All $\pm 10\%$ $\frac{1}{4}$ W carbon

Capacitors

C1, C2 0.1 μ F (2 off) (see text)

C3, C4 100 μ F 10V elect

C5, C6 0.1 μ F (2 off)

Transistors

TR1-TR7 2N3704 (7 off)

Diodes

D1-D14 1N914 or any general purpose silicon diodes (14 off)

Integrated circuits

IC1, 3, 4, 7, 8, 10 SN7400N (6 off)

IC2 SN7472N

IC5 SN7473N

IC6 SN7451N

IC9 SN7493N

Miscellaneous

CO1, CO2 PO type four-digit counters (2 off) (see text)

LP1-LP5 6V 60mA lamps with 4 amber and one green holder (5 off)

B1, B2 Type 800 3V batteries (2 off)

S1-S3 Single pole changeover pushbutton

S4 Single pole on/off

0.1in matrix Veroboard 4in \times 2in

0.1in matrix perforated board 12cm \times 10cm


32 s.w.g. enamelled copper wire

Case to suit

THE CASE

The prototype was housed in a box made from chipboard with an aluminium fascia. The counters may be held by aluminium straps to the walls of the case. Since we are using the principle of biofeedback to reinforce learning, the TOTALS counter should be wrapped in foam rubber to reduce noise while the CORRECT counter should be held firmly against the side of the box so as to give a satisfying clunk on each correct occasion.

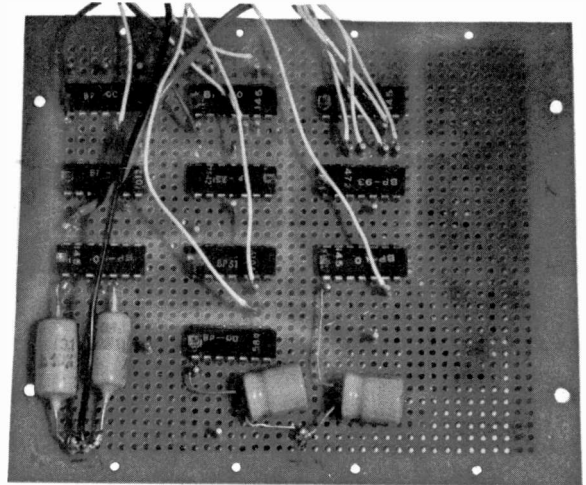The i.c. board was mounted horizontally on wooden blocks while the Veroboard was mounted vertically adjacent to the batteries which were held in place by wooden blocks and an elastic band (see photograph). Rub-on lettering for CHOOSE, SPIN, etc. improves the appearance of the completed detector.



Photograph of the integrated circuit board

TESTING

On first switching on, it may happen that all five lamps light. If so, press the switches until they all go off. On then pressing the SPIN switch, the CHOOSE lamp should light and remain on when the SPIN switch is released.

Pressing the left or the right switch should have no effect but releasing it should cause the TOTALS counter to be activated. Check that this is absolutely reliable, always counting on one digit when either the left or the right switch is pressed and released after the CHOOSE lamp is lit. Releasing the left or right switch may also have the effect of activating the CORRECT counter and lamp LP1.

Check that this counter is also reliable and always counts when another lamp lights or when the completed row remains on.

If the detector has been built for interest only, no further testing is necessary. However, any statistical analysis will rely on a 50/50 chance of the spinning circuit freezing in the left or the right condition. This can be tested in two ways:

(a) by taking the output of the astable multivibrator MV1 (pin 8, IC1) to the Y-plates of a cathode ray oscilloscope and running the X-timebase at about 5kHz. The trace should show a square


Table 1: Confidence Levels

	Excess over the mean (in standard deviations)									
	2.0	2.2	2.4	2.6	2.8	3.0	3.2	3.4	4.0	5.0
Odds (1in)	20	40	60	100	200	400	800	2,000	10,000	2,000,000
Confidence Level (%)	95.5	97.2	98.4	99.1	99.5	99.7	99.9	99.9	100	100

wave with an equal mark/space ratio. If not, it implies that the capacitors C1, C2 are not equal in value and should be changed or modified (by adding smaller capacitors in parallel with the lesser of C1 or C2) until the mark/space ratio is 1:1).

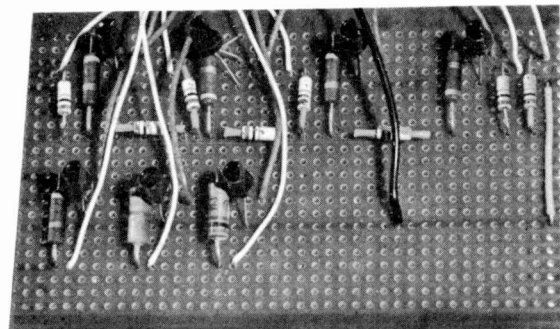(b) by pressing the SPIN and (say) the RIGHT button repeatedly for a large number of times (without touching the other button) and noting the scores on the CORRECT and TOTALS counters. Over a large number of results, the CORRECT number should tend towards one half of the total number of tries. Since we are testing a random process, the CORRECT number will not be exactly one half the TOTAL number even if the probability of left/right is exactly 50/50. However, almost all runs of 100 guesses should have 50 ± 10 correct results.

If, after repeating this several times, there is a clear bias, the value of one of the capacitors should be adjusted to reduce the bias. A small remaining bias will not affect the statistics providing the subject believes there is no bias.



Photograph of the transistor panel

STATISTICAL ANALYSIS

In deciding whether a result is due to ESP or purely to random chance, it is usual to calculate the odds against the event occurring by chance.

The odds against a run of x correct answers occurring by random chance is easily calculated by $\frac{1}{2^x}$. For example, the record run in the prototype was 14 correct in a row, which by pure chance would occur $\frac{1}{2^{14}} = \frac{1}{16,384}$ i.e. once in 16,384 guesses.

However, calculating the odds against getting x correct answers in a session of n guesses is rather

more complex. The formula is $\frac{n!}{x!(n-x)! 2^n}$ where $n!$ (pronounced "factorial n ") is calculated by multiplying n by all the whole numbers less than n . For example: $10! = 10 \times 9 \times 8 \times 7 \times 6 \times 5 \times 4 \times 3 \times 2 \times 1 = 3,628,800$. For small values of n , with a lot of cancelling, this is straightforward. For large values of n , the calculation becomes tedious, although using Stirling's approximation the formula becomes

$$\frac{(n/2)^n}{(n-x)^{n-x} x^x} \times \sqrt{\frac{n}{6x(n-x)}}$$

which, although it looks more complicated, is easier to evaluate (using logs to calculate the powers).

A simpler and sufficiently accurate way to decide whether a result is sufficiently unusual to be accepted as proof of ESP is to calculate the "standard deviation" of the results from the formula:

$$\text{standard deviation} = \frac{\sqrt{n}}{2}$$

CONFIDENCE LEVEL

Table 1 can then be used to determine the "confidence level" of the experiment. In psychology and biology experiments where similar methods are used, odds of 1 in 20 (5 per cent) are normally accepted as proof, providing similar or greater odds are indicated whenever the experiment is repeated. These 5 per cent odds are usually quoted as a "95 per cent confidence level". Naturally *all* results (for a particular individual) must be included for these calculations, not just good results or sessions with high scores.

EXAMPLE

A particular subject, in nine sessions (each of 100 guesses) obtained the following scores: 49, 52, 48, 54, 57, 55, 60, 56, 52.

(a) The total number of guesses, $n = 900$.

\therefore The standard deviation = $\frac{\sqrt{n}}{2} = \frac{\sqrt{900}}{2} = \frac{30}{2} = 15$

(b) The number of correct responses, $x = 483$.

The "mean" of the 900 guesses = $900 \times \frac{1}{2} = 450$
 \therefore The number of correct responses exceeds the mean by $483 - 450$.

- = 33 responses
- = $\frac{33}{15}$ standard deviations
- = 2.2 standard deviations

From Table 1, an excess of 2.2 standard deviations represents a 97.2 per cent confidence level (or odds of about 1 in 40) and, if repeatable, indicates the presence of ESP in the individual who is being tested. ★

THE requirement for a compact, lightweight and versatile logic tester for use with the current range of integrated circuits has long been recognised by many electronics hobbyists, particularly those who are not fortunate enough to possess an oscilloscope. The Logic Probe to be described not only fulfills this need, but has the added advantage of providing a facility for use in the field. It can be quickly assembled and the components purchased at relatively low cost.

CIRCUIT DESCRIPTION

The Logic Probe is basically comprised of two readily available integrated circuits which are the SN7413 dual 4-input NAND gate (Schmitt Trigger), and the 9601 retriggerable monostable multivibrator; the various logic outputs of the integrated circuits being fed, via suitable series resistors, to light emitting diodes to provide visual indication of the logic states of the circuit under test.

The two 4-input NAND gates are connected in series as shown at Fig. 1. A steady logic 1 at the probe will produce a logic 0 at the output of the first gate, a potential difference will exist between points 'C' and 'D' on the circuit diagram and LP2 will be illuminated. A steady logic '0' at the probe will produce logic '1' at the output of the gate and a logic '0' at the output of the second gate, a potential difference will now exist between points 'A' and 'B' and LP1 will be lit.

THREE L.E.D.s LIT

In the case where the logic under test consists of a stream of d.c. pulses having an equal mark/space

COMPONENTS . . .

Resistors

R1 470Ω
R2 470Ω
R3 33kΩ
R4 470Ω
All 10% $\frac{1}{8}$ watt carbon

Capacitor

C1 2.2μF elect. 10V

Semiconductors


IC1 SN7413
IC2 9601 (Fairchild)
D1 1N4001
D2 OA200
LP1—LP3 T1L209 l.e.d.s (3 off)

Miscellaneous

Veroboard (see text) and Veropins, plastic tubing, wooden dowels, wire, miniature crocodile clips

ratio, the monostable will trigger on the negative edge of the first pulse and LP3 will be illuminated and will remain lit for the period determined by the time constant provided by C1 and R3. Should further pulses occur during this period IC2 will retrigger. In addition LP1 and LP2 will follow the positive and negative logic, thus with a square wave all three l.e.d.s will be lit.

Consider now input logic which consists of negative going pulses where the pulse width is narrow (Fig. 2). As the d.c. state at the probe is predominantly positive (or logic '1') a predominant logic '0' will exist at the output of the first gate causing LP2 to light, also the monostable will trigger on the first negative edge and cause LP3 to light; thus, with a stream of negative going narrow pulses, LP2 and LP3 will be lit.

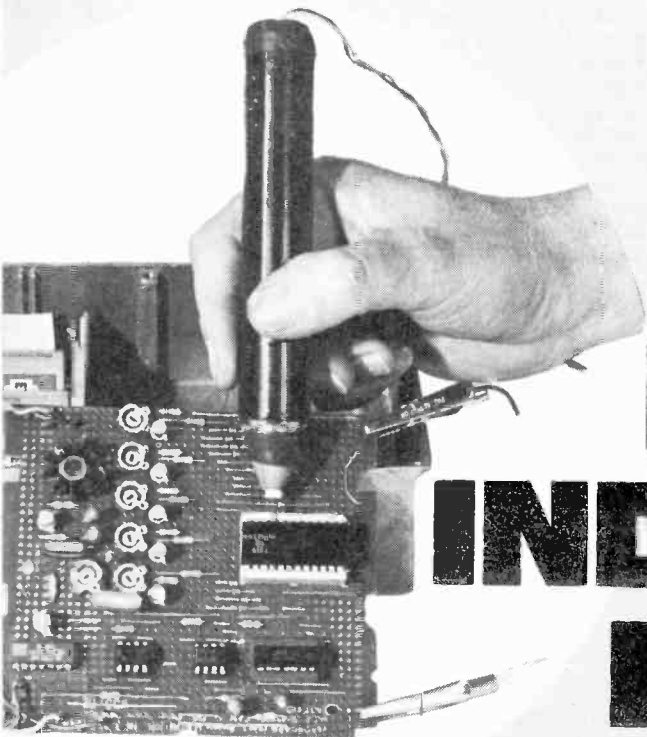

LOGIC INDICATOR PROBE

By W.H. DAVIES

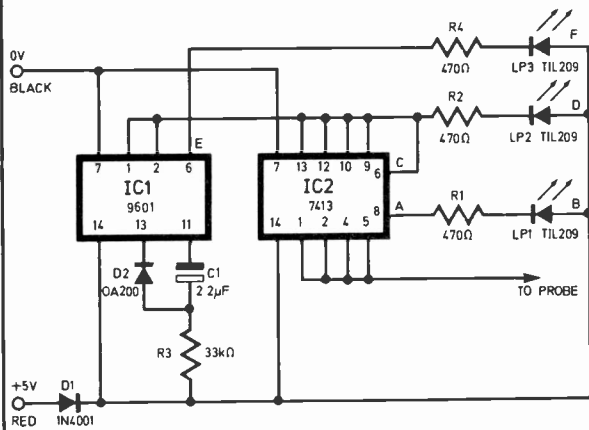


Fig. 1. Circuit of Indicator Probe

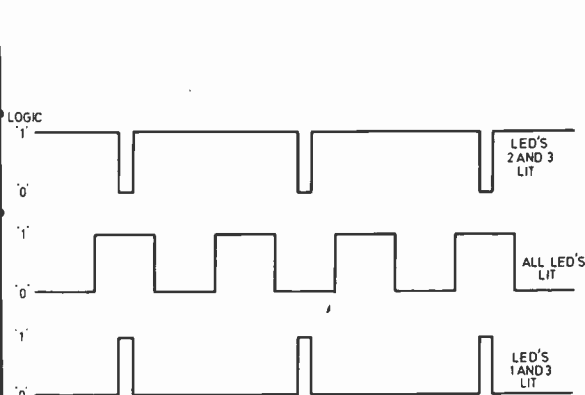


Fig. 2. Lamp switching for different pulse inputs

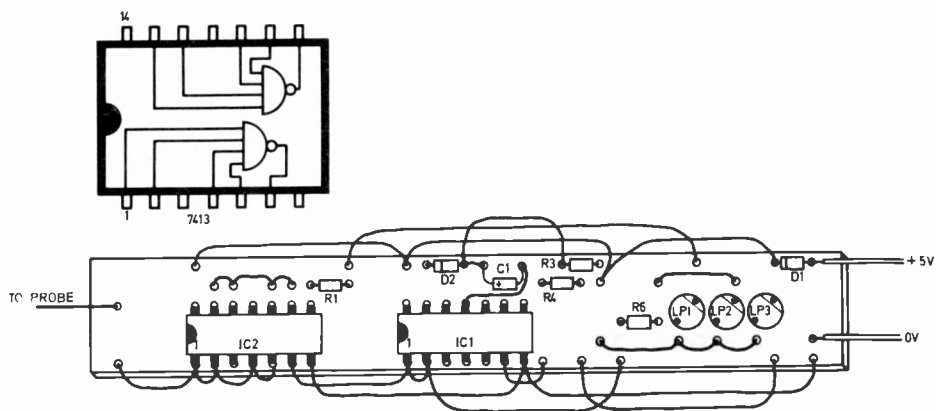


Fig. 3. Component layout and wiring details


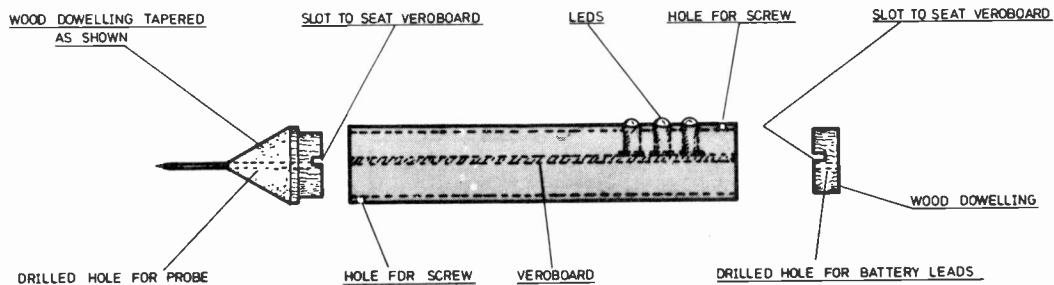


Fig. 4. Logic Probe housing details

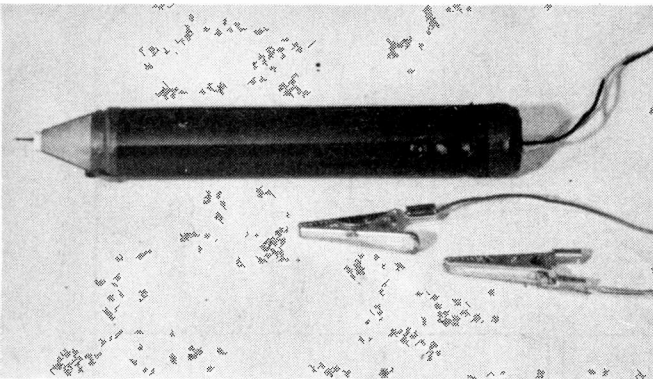

Completed logic indicator probe showing the three light emitting diodes and the supply leads with crocodile clips attached

In the reverse case (e.g. positive going pulses) LP1 and LP3 will be lit.

In either case, where the pulse repetition rate is low—say in the order of a few hertz—all three l.e.d.'s will flash on and off.

CHOICE OF I.C.s

The 7413 was chosen because it has a defined hysteresis and is capable of responding to input pulses having slow rising edges. The Fairchild 9601 is a reliable 'one shot' and will generate a wider pulse from a narrow input pulse when used in the

manner described. The probe will detect pulse widths of fractions of a micro-second. The diodes D1 and D2 are merely safety devices, D1 prevents damage to the i.c.s should the battery leads be inadvertently reversed, whilst D2 prevents a reversal of voltage reaching pin 13 of the monostable during the discharge of the electrolytic capacitor.

MATERIALS


The basic materials, excluding the electronic components, required for the construction are as follows—

- (a) One 4½in length of plastic tubing having an inside diameter of ½in (the author used plastic water piping purchased from the local building suppliers).
- (b) One piece of Veroboard (0.1in matrix) 4½in in length and ½in wide.
- (c) One suitable length of wooden dowelling having a diameter of ½in for the probe ends, an alternative would be to use suitable corks.
- (d) One metal probe. This can be made from a length of 16 swg wire or a pin.

CONSTRUCTION

Layout of the components on the Veroboard is given in Fig. 3. The Veroboard should be drilled—where indicated—to break continuity of the copper strips, and the i.c.s and the probe soldered to the appropriate strips. Fig. 4 shows the Logic Probe housing. ★

INGENUITY UNLIMITED

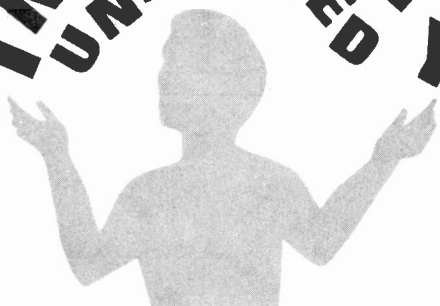

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

In fact the timing of the circuit can be synchronised to mains waveform by using unsmoothed 15V power.

On the prototype a 0V control voltage gives full power and reduction to zero occurs at about -12V. A smaller value of control voltage could be used by increasing the value of C1.

The transformer T1 was made up from two 40-turn windings of 30 s.w.g. enamelled copper wire on a length of ferrite rod. The CSR1 can be a triac or thyristor; in the prototype it was a SC45D.

M. Lawrance,
Helston,
Cornwall

VOLTAGE CONTROLLED DIMMER

THE circuit of Fig. 1 uses TR1 as a constant current source to charge the timing capacitor C1 at a rate determined by the applied control voltage at the base of TR1. At the correct level the charge voltage fires the unijunction TR2 to trigger CSR1 in turn via the trigger transformer T1.

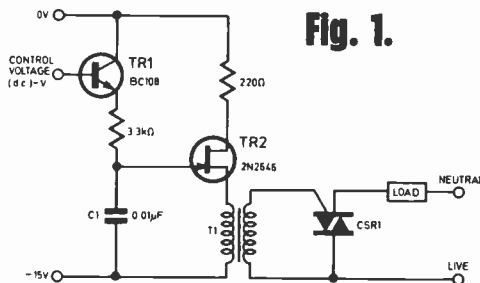


Fig. 1.

STARTING IN NEXT MONTH'S ISSUE...



The PE JOANNA

State-of-the-art piano design with additional choice of harpsichord or honky-tonk voicing. Keyboard is fully touch sensitive. Piano effect is further heightened with soft and sustain pedals. Other features include easy tuning, two speed vibrato and stool-integrated amplifier.

I.C. PULSE GENERATOR

A handy test instrument for analysing TTL circuits. Wide operating speeds covering 0.1Hz to 100kHz in six switched ranges. Pulse width is also variable from 1s to 1 μ s. An output reed relay enables it to be used with electromechanical systems.

ELECTRONIC DIRECTION INDICATOR

Electronic substitute for conventional thermal flasher. Advantages are: immediate indication when switched, long term reliability and an emergency flashing facility.

PRACTICAL ELECTRONICS

MAY 1975 ISSUE ON SALE APRIL 11, 1975

CEEFAX AND ORACLE

A PROPOSED
NEW BROADCASTING SERVICE

BY J. SMITH

SECOND AND CONCLUDING PART

In the previous article (February) we described the Ceefax and Oracle system in fairly general terms. This month we are going to examine some of the more detailed provisions of the system. A complete working unit is of little interest at this stage owing to the fact that the present system is still rather tentative and experimental.

SPECIFICATION

The main technical features given in the joint BBC, IBA, BREMA specification are as follows:

1. Data pulses are transmitted during the television field-blanking interval using a bit-rate of 6.9375 megabits per second.
2. Each page consists of 24 rows of 40 characters using both upper and lower-case characters, coded using the ISO-7 code. A special top row called the page-header carries information for control and display purposes.
3. All data-words are eight bits in length; parity protection is used for the character data words while Hamming Codes are used for addressing and control purposes.
4. News flashes and sub titles are provided.
5. Every page-header will carry clock-time information to provide a display and to permit the automatic time-selection of certain pages.
6. Control characters are used to provide colouring and flashing of selected words.
7. A simple graphics facility is provided.

This list is taken from the specification which goes into considerably more detail regarding the definition

of terms like "page", "magazine", etc. Readers interested in a full understanding of the system are recommended to read this publication*. In this article we shall confine our attention to the more interesting technical features of the system.

LINE ALLOCATION

Lines 17 and 18 are already allocated; they are in fact used internationally for insertion test signals. However, providing their use is restricted to this country they are available for data transmission.

Lines 13 and 14 are free, but research studies have shown that some receivers frame flyback times creep into this region. For this reason data pulses on lines 13 and 14 would be visible to some people. It is anticipated that, as the system develops, manufacturers will reduce flyback times to release these and possibly other lines to allow a better service.

RUN-IN AND FRAMING CODE

Fig. 2.1 shows how the data is fitted onto the television line scan. The clock run-in period of 16 bits is to synchronise the internal clock which determines the position of the data.

The clock run-in starts 1010 . . . for sixteen bits ending with a "0". This is followed by a framing (starting) code which identifies the start of the message. The clock run-in and starting code are the same on every line 10101010101010 11100100.

* Information transmission by digitally coded signals in the field-blanking interval of 625-line television systems. BBC, IBA, BREMA. Price 50p.

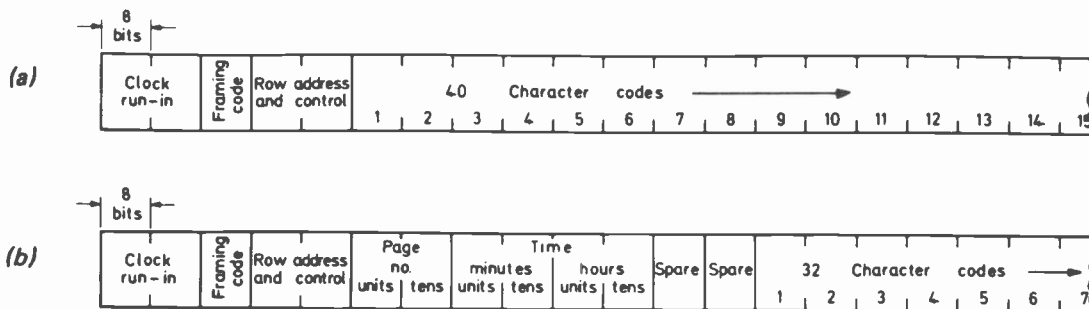


Fig. 2.1. Arrangement of data on TV lines. (a) shows a normal data line and (b) the page header line

This code has been carefully chosen for ease of recognition as it signifies the start of the data signal. From this point on, the clock, which has been previously synchronised determines the position of any eight bit character along the line scan period.

This clock is also vital when it comes to reading the data onto the TV screen because characters must be displayed in their *correct* positions along the line scan.

ROW ADDRESS GROUP

The framing or start code is followed by the row address group. It is very important to recognise the row address correctly, errors here could not only put a row in an incorrect position, but also interfere with another row. Consequently the row address is heavily protected by the Hamming Code, discussed later.

On most lines the framing code is immediately followed by the data bits, the exception being the occasional page-header line. Page-headers only occur on lines 18 or 331, but manufacturers are advised to organise receivers on a basis of code recognition, rather than line recognition, to allow for future developments.

Page-headers only occur on row 0 which must be recognised in order to deal with the page-header line correctly. The page numbers, tens and units, are also protected with the Hamming Code and must be dealt with in the appropriate manner.

PARITY CODE

The data are transmitted in blocks of eight, seven bits for the character; the eighth is a parity bit. The eight bits are transmitted in sequence the first bit being the least significant bit in binary encoded signals. Thus in binary notation we have;

Signal	1	2	3	4	5	6	7	8
Binary weight	2 ⁰	2 ¹	2 ²	2 ³	2 ⁴	2 ⁵	2 ⁶	0
	M	M	M	M	M	M	M	P

where M are the message bits and P is the parity bit.

The parity bit is "1" or "0" dependent upon odd or even message bits. The parity bit always makes an odd number of 1's. If an even number of 1's occurs, an extra (noise) pulse has been received and the signal is in error.

It is obvious that if two noise pulses occur the parity check will not reveal an error; however, some errors on the message signals can be tolerated.

HAMMING CODE

Signals protected by the Hamming Code are less liable to give errors because the Hamming Code employs four parity bits.

1	2	3	4	5	6	7	8
P	M	P	M	P	M	P	M

Again the bits are transmitted in numerical order beginning with number 1, the least significant bit. The four parity checks are carried out as follows:

- Parity check A is carried out over bits 1268
- Parity check B is carried out over bits 2348
- Parity check C is carried out over bits 2456
- Parity check D is carried out over all bits.

Table 2.1 shows the Hamming Code. A few minutes study of this code shows how the four parity checks can lead to information showing which bit is in error.

Table 2.2 shows how the various checks are used to correct some of the errors which may occur. Although Table 2.2 shows how parity bits may be complemented (1's changed to 0 or 0's changed to 1) it is only necessary to correct bits 2,4,6,8, the message bits.

Because the Hamming Code reduces the number of message bits available, four bits giving the sixteen different states shown on Table 2.1, *two blocks* of eight bits are allocated for control and row address as shown in Fig. 2.1. This arrangement gives a total of 16² (256) combinations of data which are protected by the Hamming Code.

Table 2.1: Hamming Code

Decimal Message Value	Bit Position Number							
	1	2	3	4	5	6	7	8
0	1	0	1	0	1	0	0	0
1	0	1	0	0	0	0	0	0
2	1	0	0	1	0	0	1	0
3	0	1	1	1	1	0	1	0
4	0	0	1	0	0	1	1	0
5	1	1	0	0	1	1	1	0
6	0	0	0	1	1	1	0	0
7	1	1	1	1	0	1	0	0
8	0	0	0	0	1	0	1	1
9	1	1	1	0	0	0	1	1
10	0	0	1	1	0	0	0	1
11	1	1	0	1	1	0	0	1
12	1	0	0	0	0	1	0	1
13	0	1	1	0	1	1	0	1
14	1	0	1	1	1	1	1	1
15	0	1	0	1	0	1	1	1

Bits 1, 3, 5, 7 = Protection bits
Bits 2, 4, 6, 8 = Message bits

Table 2.2: Error Correction Table

Parity Check				Action	
D	C	B	A		
0	0	0	0	Error free reception	
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0	Reject, even order error	
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0	Complement Bit 7	
1	0	0	1		Complement Bit 1
1	0	1	0		Complement Bit 3
1	0	1	1		Complement Bit 8
1	1	0	0	Complement Bit 5	
1	1	0	1		Complement Bit 6
1	1	1	0		Complement Bit 4
1	1	1	1		Complement Bit 2

NEW LOW PRICES!

Sinclair Scientific kit

(Was £19.95 - save £5!)

£14.95
(INC. VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range – features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £21.55 (including VAT).

And as a kit it costs under £15!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle directly

sin and arcsin,
cos and arccos,
tan and arctan,
automatic squaring and doubling,
log₁₀, antilog₁₀, giving quick access to x^Y (including square and other roots),

plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer – they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

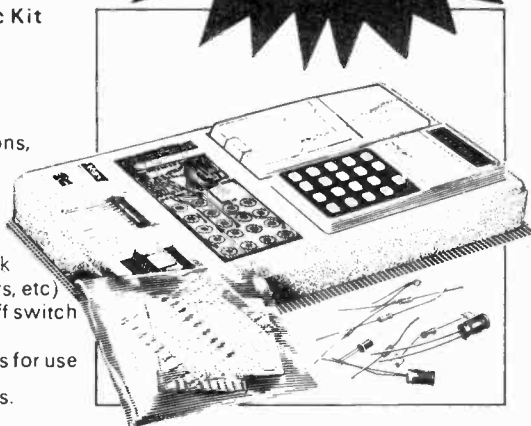

Features of the Sinclair Scientific

- 12 functions on simple keyboard
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.

- Scientific notation
Display shows 5-digit mantissa, 2-digit exponent, both signable.

- 200-decade range
10⁻⁹⁹ to 10⁺⁹⁹

- Reverse Polish logic
Post-fixed operators allow chain calculations of unlimited length – eliminate need for an = button.

- 25-hour battery life
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.

- Genuinely pocketable
4 1/3" x 2" x 1 1/16". Weight 4 oz. Attractively styled in grey, blue and white.



NEW LOW PRICES!

Sinclair Cambridge kit

Now only
£9.95
(INC. VAT)

(Was £14.95 - save £5!)

At its new low price, the original Sinclair Cambridge kit remains unbeatable value.

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below - then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

Take advantage of this

money-back, no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch - and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

Scientific

Price in kit form £14.95 inc. VAT

Price built £21.55 inc. VAT.

Cambridge

Price in kit form £9.95 inc. VAT.

Price built £13.99 inc. VAT.

Features of the Sinclair Cambridge



- Uniquely handy package. 4 1/3" x 2" x 1 1/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, -, ×, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £10.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,
FREEPOST St Ives,
Huntingdon, Cambs. PE17 4BR

Please send me

- Sinclair Scientific kit at £14.95
- Sinclair Scientific built at £21.55
- Sinclair Cambridge kit at £9.95
- Sinclair Cambridge built at £13.99

All prices include 8% VAT.

*I enclose a cheque for £....., made out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/ Access account. Account number

--	--	--	--	--	--	--	--	--	--	--	--

*Delete as required.

Signed _____

Name _____

Address _____

Please print. FREEPOST - no stamp needed.

PE/4/75

sinclair

Sinclair Radionics Ltd,
FREEPOST St. Ives,
Huntingdon, Cambs. PE17 4BR.

Reg. No: 699483 England. VAT Reg. No: 213 8170 88.

Bits		Column													
b7	b6	b4	b3	b2	b1										
Row		0	1	2	3	4	5	6	7						
0	0	0	0	0	0			SP	0	@	@	P	P	.	p
0	0	0	1	1	1	Graphics Red	I	1	A	A	Q	Q	a	q	
0	0	1	0	2	2	Graphics Green	"	2	B	B	R	R	b	r	
0	0	1	1	3	3	Graphics Yellow	£	3	C	C	S	S	c	s	
0	1	0	0	4	4	Graphics Blue	\$	4	D	D	T	T	d	t	
0	1	0	1	5	5	Graphics Magenta	%	5	E	E	U	U	e	u	
0	1	1	0	6	6	Graphics Cyan	&	6	F	F	V	V	f	v	
0	1	1	1	7	7	Graphics White	'	7	G	G	W	W	g	w	
1	0	0	0	8	8		(8	H	H	X	X	h	x	
1	0	0	1	9	9	Alpha ⁿ Red)	9	I	I	Y	Y	i	y	
1	0	1	0	10	10	Alpha ⁿ Green	*	10	J	J	Z	Z	j	z	
1	0	1	1	11	11	Alpha ⁿ Yellow	+	11	K	K	[]	k]	
1	1	0	0	12	12	Flash Alpha ⁿ Blue	v	<	L	L	\	/	l		
1	1	0	1	13	13	Steady Alpha ⁿ Magenta	-	=	M	M]]	m]	
1	1	1	0	14	14	End Box Alpha ⁿ Cyan	.	>	N	N	^	^	n	^	
1	1	1	1	15	15	Start Box Alpha ⁿ White	/	?	O	O	_	_	o	DEL	

control characters (columns 1 and 2) to be displayed as spaces

Notes

① This character code (position 0/3) is reserved for internal use by broadcasters

② UK version of national use character in the ISO 7 code

③ In the graphics mode when bit 6 = 0 the corresponding alphanumeric mode character should be displayed

④ All character rows start in the 'Steady', 'Alphanumeric White' and 'unboxed' condition, without control characters

character in alphanumeric mode

character in graphics mode

Graphics display rectangle showing the allocation of bit numbers to the individual calls

Fig. 2.2. Character code for data broadcasting. This table shows both alphanumeric and graphics information, the latter being selected by the appropriate control code in columns 1 and 2. (Reproduced from Joint Specification)


CHARACTER INFORMATION

The character information employs seven bits, 128 (2⁷) different combinations. Fig. 2.2 shows how these 128 combinations are used. A matrix of 8 × 16 is used to produce 128 different characters.

Rows are identified by bits 1, 2, 3, 4, whilst columns are identified by bits 5, 6, 7. Thus if we wish to display the "£" sign we will have a code 11000100. Similarly the "&" sign would be 0110010, the parity bit being "0" in each case to give odd parity. A "?" sign on the other hand would be coded 1111101, where the parity bit is "1".

The control instructions located in columns 0 and 1 (000 and 100) are reproduced as a blank space, but following characters are produced according to the instruction given. For example, a white number 1 coded 10001100 would be preceded by an instruction-space code 11111000. However, if the number was to be reproduced in red it would be preceded by the instruction-space code 1001 1000. In each case the last bit is the parity bit.

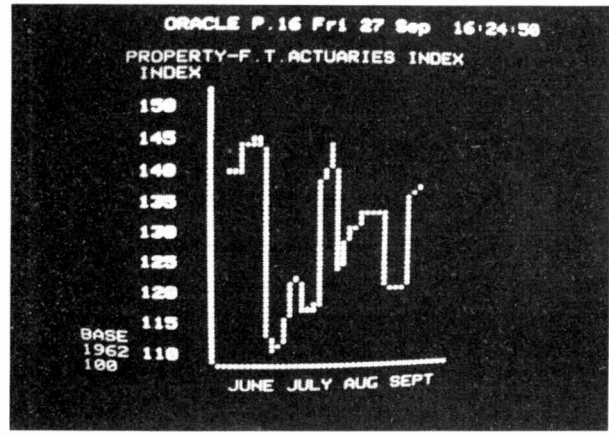An example of an ORACLE page using the graphics facility



GRAPHIC SYMBOLS

As the system has a graphics facility there are alternative graphic symbols given in each location which must be generated when called for. If instead of a red 1 the red graphic symbol was required the graphics space signal would be given. For example:

start 12345678 12345678 gives a red 1

10011000 followed by 10001100

10001001 followed by 10001100 gives red spots.

Thus the specification virtually dictates the design of the ROM unit discussed in last month's article. Before discussing the ROM organisation in more detail it will pay to re-examine how the RAM stores the transmitted data.

RAM ORGANISATION

The RAM can be organised in a variety of ways by receiver manufacturers, but from an operational point of view it is best to visualise a matrix 40 × 24, giving 960 locations, where each location can store seven bits of information. This then corresponds to the 40 characters and 24 rows of each page in the system.

Each row is identified by its row number (0 to 23), derived from the control and row-address group. The columns are numbered 1 to 40 and are derived from the synchronous clock.

The clock starts its division (by 40) on receipt of the framing (start) signal. Fig. 2.3 illustrates this arrangement. The row information is processed by the Hamming decoder logic which also determines if the row is "0" or not (i.e. the page header). If the row is "0", further Hamming logic is used on the next 16 characters which give the page numbers.

The synchronous clock ensures that the whole row is filled. After this nothing more happens until

ROW	CHARACTER COLUMN										
	1	2	3	4	5	6	7	8	9	39	40
0											
1											
2											
3											
4	6	.	4	0	p	m		P	L		
5	9	.	0	0	p	m		N	E		
6											
7											
23											
24											

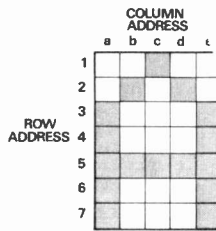


Fig. 2.3. (left) Diagram showing RAM visualisation. Each of the squares represents seven bits of data

Fig. 2.4. (right) A typical cell matrix. This particular character would be produced by the code 1000 001

another line of data appears complete with its clock run-in signals, framing code and row coding, then the next row in the RAM is filled with data.

Each row of the memory may be filled at random. The transmission of each row need not be sequential and in all probability will not be. Read, write, inhibit and reset logic is also required in association with the RAM in order to fully control its function.

When filled the RAM can be visualised as the representing page of information to be written on the television screen. This idea is shown in Fig. 2.3, line 4 illustrating a programme timetable: 6.40 pm PLAY, followed by line 5, 9 pm NEWS. Of course these characters are actually stored in a seven bit binary store.

ROM ORGANISATION

The ROM unit is rather more complicated than it appears from our preliminary examination. The character must be generated over 14 lines, so each line reproduces only a small part of the character. In addition, each line reproduces a small part of each of the 40 characters which appear along any particular row.

The ROM unit converts the parallel coded information from the RAM board to a serial output of dot information which modulates the CRT during scan. The ROM's themselves contain character information on a 7×5 dot matrix

Fig. 2.4 shows cell 1000001 (capital A) as given by the character codes in Fig. 2.2.

The sequence of operations is as follows:

1. The clock counter (synchronised with the clock run-in pulses) access the first letter stored in the RAM, in this case a capital A.
2. The ROM is addressed so that the cell containing A is activated. (Cell 1000001, Fig. 2.4.)
3. A television line scan counter has already activated the first line address input to every part of the ROM. (Line 1, Fig. 2.4.)
4. The contents of the ROM are transferred to a shift register of six bits. (The sixth bit is the space between characters.)
5. In this example the contents from line 1 of the ROM transferred to a shift register are white, white, black, white, white. (Line 1, Fig. 2.4.)
6. A 6MHz phase-locked counter shifts the information serially out of the shift register to



An operator entering data into the ORACLE system

modulate the CRT with a dot representing the top of the "A"

7. The clock counter addresses the RAM to find the next character, "B" for example.
8. The ROM cell containing "B" is addressed by the RAM (1000010 in Fig. 2.2). This cell already has its line 1 input activated.
9. The top of the "B" is transferred to the shift register and modulates the tube as described for the "A".

Proceeding thus, scan 1 moves from character to character of the row stored in the RAM, addressing the appropriate coordinates of the ROM for each character in the row. The ROM modulates the scan line with the top of each character in the row.

At the end of the row, scan line 2 on the ROM is activated to modulate the CRT with the dots required on the second line scan. The seven scan lines of character are reproduced by this means and followed by four blank lines of inter-row scan.

ADDITIONAL FEATURES

In the most simple systems reproduction of alphanumeric characters will be all there is to the ROM, but in more advanced receivers there will be provision for graphics and character rounding. These additional features will increase the complexity of the system considerably as will some of the other provisions of the specification.

To summarise the various systems in terms of increasing complexity, we have:

1. Alphanumeric display.
2. Upper and lower case alphanumeric characters.
3. Graphics display.
4. Flashing display.
5. News flash and sub titles superimposed on the picture.
6. Coloured displays. Red, green, yellow, blue, magenta, cyan and white.
7. Timed displays. Some data may only be transmitted once during the day. A time clock system can be incorporated to capture this signal.

We can look forward to the time when manufacturers put receivers onto the market and we can see the various ways in which they overcome the complexities of the system to provide the maximum of facilities at a minimum cost. ★



MUSICAL DOORBELL

By C. J. ALLEN

THE Electronic Doorbell was designed to replace any normal door-bell (other than the illuminated door-push type). It produces a novel sound with ample volume for an average house and a life of several months between battery changes with normal use.

OPERATION

The circuit, Fig. 1, uses an oscillator, IC1, capable of producing five different tones. The tune played includes up to fifteen time-slots of equal length, and during each of these time-slots the appropriate tone is selected, from IC1, using the pre-programmed diode matrix shown in detail in Fig. 2.

The oscillator's output is fed via a simple transistor amplifier to a loudspeaker LS1.

The time-slots are generated by a second oscillator, IC2, feeding a divide-by-sixteen binary counter, IC3, which in turn addresses a 4 to 16 line de-multiplexer, IC4.

IC4's seventeenth output is used to turn a latching relay RLA off, thereby removing power at the end of the tune.

tone GENERATION

By now the reader should be familiar with the '555' timer and its use as an astable multi-vibrator. The frequency of IC1 may be changed by altering any of the timing components identified in Fig. 1 as R1 to 5, R11 and C1. Here the five different tones are generated by switching in one of the pre-set resistors VR1 to VR5 via the transistors TR1 to TR5. This is achieved by switching the associated transistor base towards ground (0V) potential using a diode matrix.

AUDIO AMPLIFICATION

The amplifier is a very simple class A design which in fact introduces a great deal of distortion, but as the output waveform is unimportant this is ignored. Preset VR6 acts as a volume control.

Any small loudspeaker should suffice (3Ω to 50Ω); the prototype used a 2½in. speaker of unknown impedance removed from an old transistor radio.

CLOCK AND DE-MULTIPLEXING

This section of the circuit makes use of a second 555 timer IC2, running at about 4Hz to drive a binary counter IC3 (SN7493). The components C6 and R19 connected to IC3 set-zero input ensure that the counter is always started in the set-zero state such that the tune played starts from the chosen beginning.

The four output lines from IC3 (A, B, C and D) are then fed to a de-multiplexer IC4, which decodes the binary information into a selection of one of sixteen; that is, each of the sixteen outputs 1 to 16 is sequentially taken from logic 1 level to logic 0 for about 0.25s, only one output being at 0 at any one time.

The value for V_{out} in the logic 1 state of an SN74154 can be as low as 2.4V. As it was felt that the transistors TR1 to TR5 would not be held fully off by these voltages, the values of resistors R1 to R10 were made lower than would appear necessary to act as pull-up resistors for the IC4 outputs, thus avoiding problems of leakage currents through the transistors.

DIODE MATRIX

As the outputs from the SN74154 are so-called "totem-pole", each has to be diode or-gated and isolated from the others. Hence the use of a diode matrix.

If desired IC4 can be replaced with the pin-compatible, open-collector output version SN74159. This removes the need for the diodes which would then be replaced with wire links. The saving in cost of the diodes, however, does not offset the extra cost of the SN74159 and for this reason it was not used in the prototype.

The matrix of Fig. 2 is for a facsimile of the beginning of the Beethoven 9th symphony. Pauses may be introduced into the music by leaving the appropriate input to the matrix open circuit. This is demonstrated in Fig. 3 which gives the matrix for playing part of "Colonel Bogey".

LATCHING RELAY

As noted, the seventeenth output from IC4 goes to logic 1 on starting the machine. This holds TR8,

MUSICAL DOORBELL CIRCUIT DETAILS

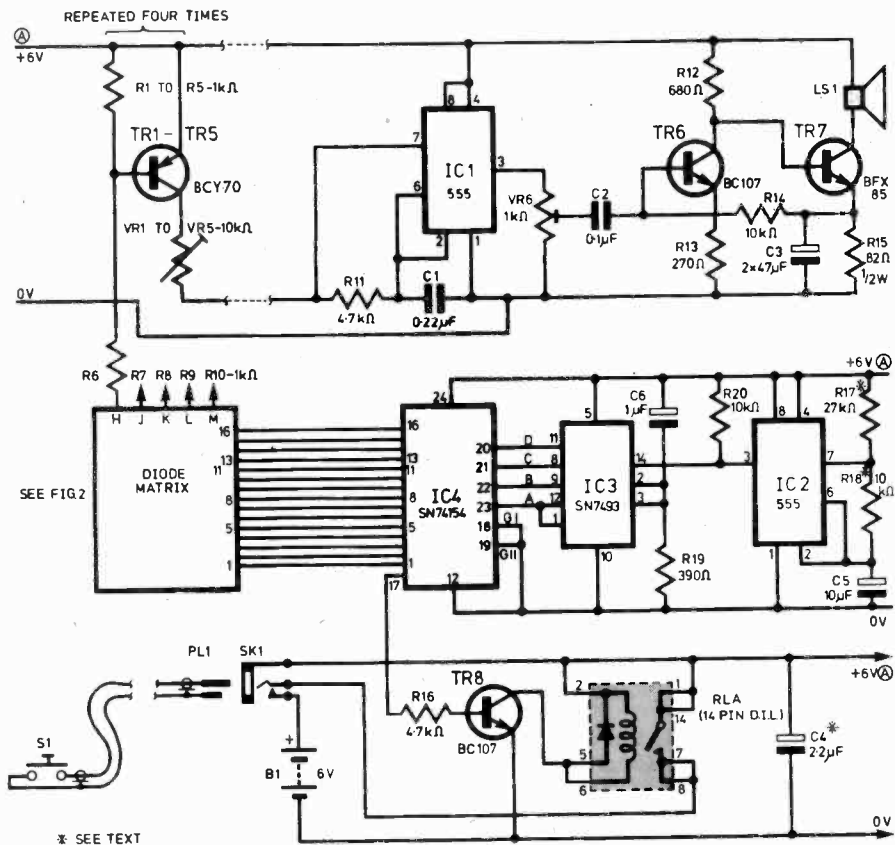


Fig. 1. General circuit diagram of the electronic doorbell

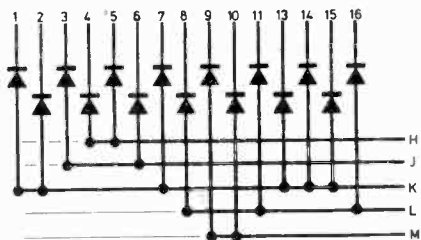


Fig. 2. The diode matrix used in the prototype to produce the first bars of the Beethoven 9th


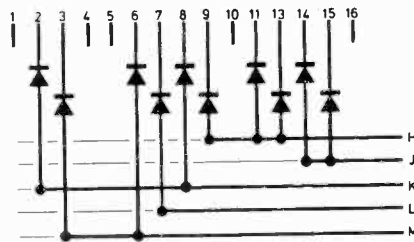


Fig. 3. Diode matrix alterations to produce Colonel Bogey

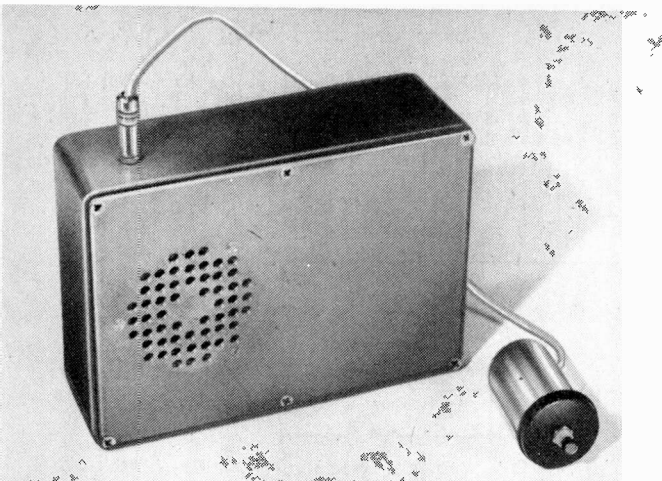

and hence the relay RLA on. Thus if the relay contacts are momentarily shorted (by the door-push) the circuit will latch and stay in that state until the tune has finished and the output of IC4 goes low, turning TR8 and the relay off. If the SN74159 is used for IC4 a 2.2k Ω resistor must be connected between this output and the +6V rail.

CONSTRUCTION

All the components, with the exception of batteries, loudspeaker and switch are soldered onto one piece of Veroboard, the size used being that made especially for mounting in a Lektrokit box. However, any piece of 0.1in Veroboard of 39 \times 41 or more holes will do.

The component layout for the Beethoven's Ninth version is given in Fig. 4, whilst the alterations necessary for playing Colonel Bogey are shown in Fig. 5.

The choice of box for mounting the circuit is left to the constructor. The prototype was built in a die-cast box 6 $\frac{1}{2}$ \times 4 $\frac{1}{2}$ \times 2in which also contains the speaker and four HP11 batteries required to power the machine.

If this method is used it is worthwhile cutting the Veroboard to fit in the box before mounting the components as shown in the photographs and Fig. 4. Make sure none of the copper strips short to any of the many protrusions in these boxes. As can be seen from the photographs, a miniature 3 $\frac{1}{2}$ mm jack-plug and socket were used to accept the wires from the door-push; the socket used was the type with a switch on the back, bent in such a manner that it closed when the plug was inserted. This switch turns the power to the electronics off when the plug is removed.

Holes, for mounting the board on pillars, if required, may be drilled in several places if some thought is given to not breaking any used strips and care is taken not to short any strips together or to earth. Further removal of copper with a spot face cutter may be needed.

The relay RLA used is a d.i.l. packaged device with its own protection diode. Fig. 8 shows how the batteries are mounted in the prototype but constructors may wish to use different batteries or a suitable holder for their particular requirements.

TESTING AND SETTING-UP

The tone adjusting pre-sets are, for convenience, numbered in ascending order of frequency: VR1 the lowest tone used and VR5 the highest. First of all remove IC4 from its socket, set VR6 to about $\frac{1}{4}$ of its travel clockwise, solder one end of a length of wire to earth (0V) and solder a temporary link across the terminals to the push switch. Touching the free end of the earthed wire to either end of any of the diodes should produce a tone from the speaker. By running the wire along the diodes corresponding to pins 1 to 16 respectively on IC4, the tune should be produced if the pre-sets have been correctly set. With a bit of practice and a good ear for pitch, the correct positions can soon be found.

If IC4 has been soldered in place then remove the end of the diode going to pin 1 on IC4, short

COMPONENTS . . .

Resistors

R1 to 10	1k Ω , 10 off
R11, 16	4.7k Ω , 2 off
R12	680 Ω
R13	270 Ω
R14, 18*, 20	10k Ω (see text ref. R18)
R15	82 Ω $\frac{1}{2}$ W
R17*	27k Ω (see text)
R19	390 Ω

All resistors $\frac{1}{4}$ W, 10% or better except where specified

Potentiometers

VR1 to VR5	10k Ω miniature preset (see text ref. VR4, VR5)
VR6	1k Ω miniature reset

Capacitors

C1*	0.22 μ F, 100VW polyester (see text)
C1	0.1 μ F 100VW polyester
C3	2 \times 47 μ F, 63VW Tant bead
C4	2.2 μ F, 35VW Tant bead
C5	10 μ F, 25VW Tant bead
C6	1 μ F, 35VW Tant bead

Transistors

TR1 to 5	BCY70
TR6, 8	BC107
TR7	BFX85

Diodes

D2 et al	Any general-purpose miniature silicon device such as OA200, 1N914, IS914, etc. (15 or 32 if required)
----------	---

Integrated Circuits

IC1, 2	NE555, MC1455G etc. (555 chip), 2 off
IC3	SN7493
IC4	SN74154, (A. Marshall)
IC5	SN7472 (if needed, see text)
IC6	SN74154 (if needed, see text)

Relay

RLA	D.I.L. mounting reed relay, Chromasonic Electronics
-----	---

Miscellaneous

Veroboard; suitable case; heat sink for TR7; i.c. sockets, particularly IC4 and IC6; loudspeaker, batteries or battery; wire; bell-push, etc.

* See text

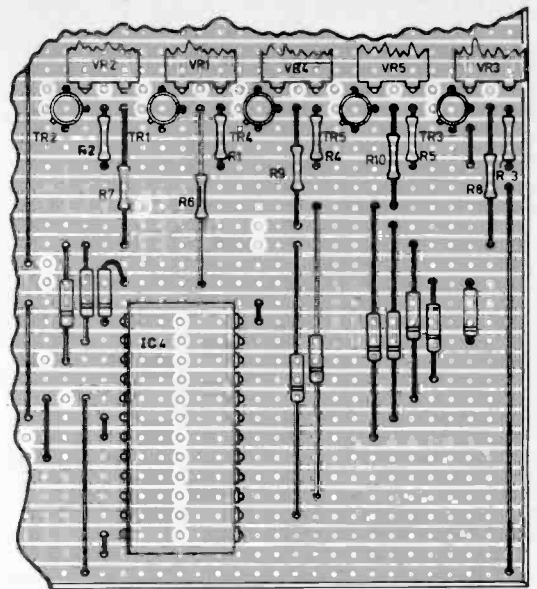
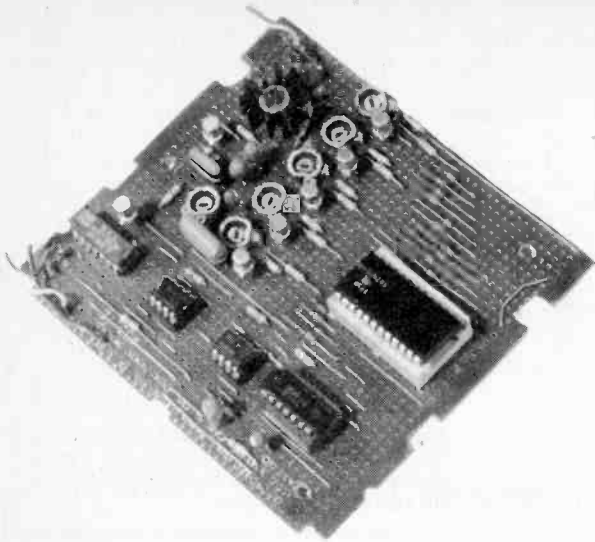


Fig. 5. Veroboard modifications for the Colonel Bogey version

out C5 to positive 6V. Now proceed with the steps from "set VR6" as above, making sure not to touch the wire on those ends of the diodes going directly to IC4 as this may be damaged. Always connect to the negative diode ends.

Remove the shorting link from the push (door) switch connections and either replace IC4, or remove the short from the capacitor and re-solder

the diode. On wiring in a door switch and pressing it the doorbell should now function properly.

If the tune is played too fast or too slow this can be remedied by increasing or decreasing the value of R18. If, however, it is made to run too fast the device will not turn itself off, in which case the smoothing capacitor C4 should be reduced in value.

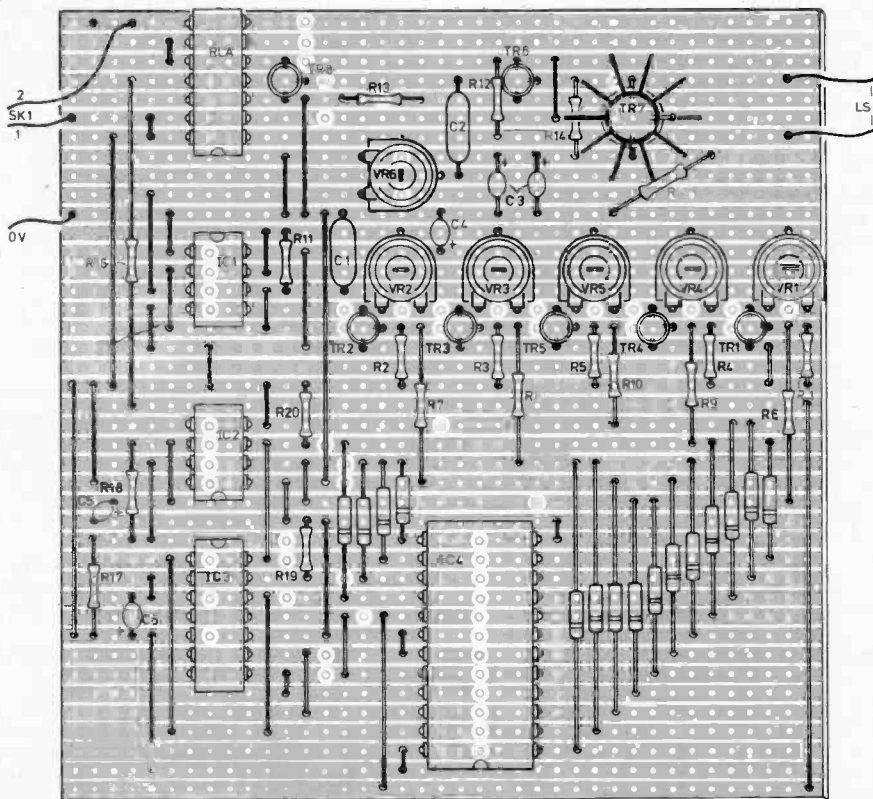


Fig. 4. Veroboard component layout and cutting details for the prototype electronic doorbell

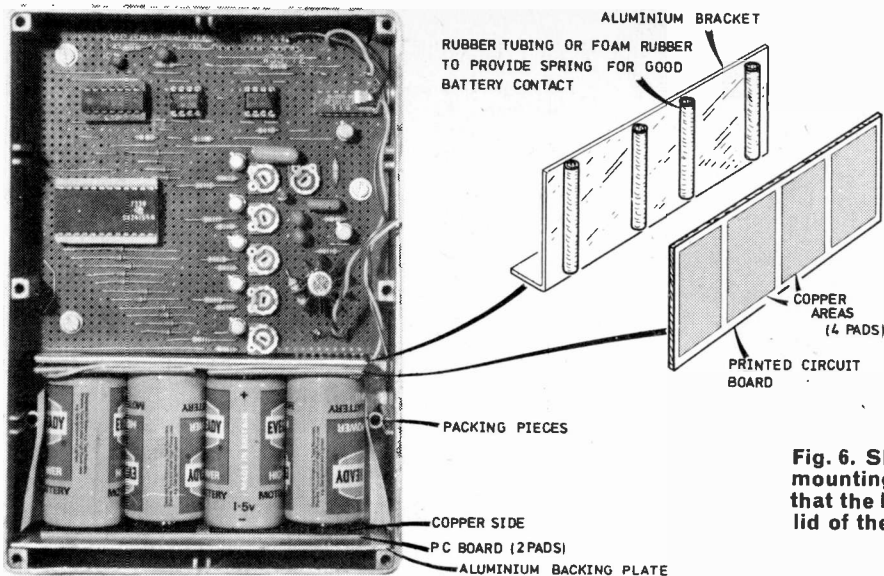


Fig. 6. Sketch of the board and battery mounting used in the prototype. Note that the loudspeaker is mounted on the lid of the diecast box.

WARNING

Do not allow any of the potentiometers VR1 to VR5 to be set fully anti-clockwise as this could damage IC1. If the Colonel Bogey version is built, note the changes marked with an asterisk in component values given in the parts list.

When the batteries start to run low the first part of the circuit to fail will be the counter IC3. This causes the device to emit a single tone that can only be stopped by removing the batteries. If you are at all tone-deaf get someone else to set the tones for you as even if it is set slightly off key it will sound very unpleasant, and can send connoisseurs of classical music mad at 100 yards.

ALTERNATIVES

The matrix could be wired on to a separate board which plugs into the main board via an edge-connector. Using this method a whole library of tunes could be built; one for each day of the week perhaps? The tunes would, of course, have to be made up of the

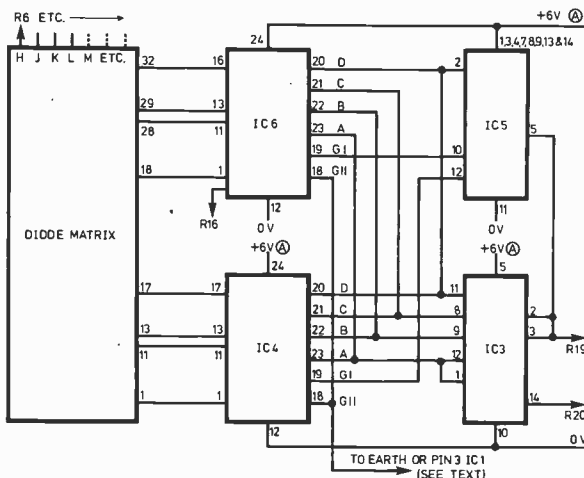


Fig. 7. Doubling the time-slot capacity to produce a longer melody requires this circuit

same five notes otherwise the pre-sets would have to be altered each time.

If this is done it becomes economical to use the SN74159 for IC4 as diodes would thus be saved.

The circuit can, if wished, be expanded to play thirty-one beats, as shown in Fig. 7. Here IC5 (SN7472) is used as a divide-by-two counter with complementary outputs such that, on starting the machine Q is low, enabling IC4 to decode the first sixteen time-slots, whilst the high \bar{Q} on the second strobe input of IC6 (SN74154) dis-enables this. On IC3's sixteenth count IC5 is toggled into its other state turning off IC4 and enabling IC6 to decode the second sixteen beats.

This modification will obviously necessitate the use of a larger diode matrix, but as this can be drawn to resemble a musical scale, working out the circuit is an easy matter.

It may be found that with or without the previous modification, more than five notes are required. This can be readily achieved by the addition of an extra output line in the matrix plus an extra transistor-switched pre-set resistor for each additional note.

Both these modifications will need a larger board and a re-designed layout for their construction.

As this circuit stands, each note follows on immediately from the preceding note. To make the tune sound more realistic short pauses between notes can be introduced by gating the output of the demultiplexer with the clock pulse such that notes are produced only when the clock's output is in the "low" state.

To do this, the output of IC1 (pin 3) should be taken to one of the strobe inputs of IC6 and/or IC4 (pin 18), the latter having first been disconnected from ground.

A sensible value for the pause-to-note ratio (mark:space ratio of the clock) is 1/10. To achieve this the clock circuit must be modified by the addition of a diode between pins 6 and 7, anode to pin 7, and suitable alteration of R17 and R18. These then become 3.6k Ω and 33k Ω respectively for the Beethoven 9th tune and 4.7k Ω and 47k Ω respectively for the Colonel Bogey version. Other melodies would obviously require experimentation. ★

NEWS BRIEFS

DICE Conversion

AN AGREEMENT, signed in February, gives Marconi Communication Systems Ltd. exclusive world-wide manufacturing and marketing rights of the Digital Intercontinental Conversion Equipment (DICE) developed by engineers of the Independent Broadcasting Authority.

The latest version of DICE can convert 525-line NTSC colour pictures, as used in the U.S.A. and Japan, into the 625-line PAL or SECAM pictures used in most other parts of the world, and vice-versa. DICE is, by a comfortable margin, the world's fastest computer.

Standards conversion is essential, not only for "live" relays via satellite, but also when programme material on video tape is exchanged between countries working to different television picture standards.

A number of different types of standards converters have been developed over the years, but IBA engineers were the first to develop a unit based on digital techniques to eliminate the need for careful alignment and adjustment and to provide conversion without perceptible picture impairment.

It is claimed that DICE solves the technically complex process of conversion between systems using 30 pictures a second, as in North America and Japan, and those using 25 pictures a second, as in Europe, entirely electronically and with negligible distortion and is capable of satisfying a global demand for high quality pictures by satellite. It also allows programme companies making television recordings for world-wide sale to offer high quality pictures no matter which standard was used during production.

Another Component Source?

ANOTHER American component distributor has decided to enter the U.K. market. Cramer Electronics of Newton, Mass., is one of the largest distributors of components in the U.S. They are "broad-line" distributors offering very wide range of components with particular emphasis on the less glamorous but vitally essential non-active components and hardware items, right down to the humble grommet.

The U.K. distribution centre to be set up in the London area will be under the control of David Griffin who has been appointed Managing Director of U.K. operations and also Marketing Manager/Europe for the Newton, Mass. (U.S.) based firm.

Although Cramer Electronics is an industrial distributor, the possibility of offering a "one-off" service to individuals is not entirely ruled out. David Griffin is aware of the needs of the constructor market and has indicated his willingness to examine this particular area.

Portable Heart Monitor

IN CLOSE co-operation with Danish doctors, Simonsen & Weel have developed a new portable, battery operated combined defibrillator/memory/scope. This unit is especially designed for the resuscitation of patients suffering from acute heart diseases.

The cardio-aid is very useful to on-the-spot ambulance staff. A feature of the unit is its capability to be linked to hospital staff from the ambulance by radio link. This enables the ECG, the heart activity of a patient in electrical form, to be sent to a qualified doctor at the hospital. The doctor can then instruct the ambulance staff, via the radio link, of any emergency treatment that needs to be carried out during the journey to the hospital.

POINTS ARISING

MARINE SPEEDOMETER (February 1975)

The last paragraph on page 121 should read: "Ranges of 0 to 10 and 0 to 20 knots are obtained by selecting either VR2 alone or VR3 and R17 in series to replace VR2. Selection can be by S1 (VR3, R17 and S1 are not shown) or S1 can be part of S2 which thus becomes a three-pole three-way switch with 'Range 1', 'Range 2' and 'off' positions."

The Zener diodes D1 and D2 in Figs. 1 and 3 should be reversed.

Further, the co-ax outer should be connected to the battery common line in Fig. 2.

P.E. MINISONIC (January 1975)

In Fig. 3.12 pin 4 of IC1, MIXER 2 should be shown connected to -9V line by means of connection at column 104, tenth strip down.

In Fig. 4.6, R14 should be disconnected from pin 6 and connected to TR5 emitter. Pins 2 and 6 should be bridged with a 100pF polystyrene capacitor.

GAS DETECTOR (September 1974)

Some readers have experienced trouble over the starting of oscillation after setting up has been carried out. It is suggested that the setting-up procedure be altered as follows.

Connect the "dummy" load as described but set VR1 to the fully anti-clockwise position and not the opposite as originally described. This places it in the position for producing the shortest mark-space ratio.

Now adjust VR1 till the load resistors are hot but not burning to the touch. Switch off and then on again to confirm the oscillator is indeed operating.

GUARANTEED 48hr SERVICE! SPECIAL OFFERS

SINCLAIR

Stereo 80 Pre-Amp	£11.35	Project 80 F.M. Tuner	£11.35
Z40 Amplifier	£5.10	Project 80 Decoder	£7.50
Z60 Amplifier	£6.60	Project 80 A.F.U.	£6.90
P25 Power Unit	£5.00	Cambridge Calc.	£11.25
P26 Power Unit	£7.50	Camb. Memory	£15.50
P28 Power Unit	£7.00	Scientific	£17.30
P220 Power Unit	£4.75	I.C. 20 Kit	£6.65

BC107	£ 0.12	BC212L	£ 0.13	2N3053	£ 0.17	1N4001	£ 0.07
BC108	£ 0.11	BC214L	£ 0.13	2N3055	£ 0.50	1N4002	£ 0.07
BC109	£ 0.13	BCY70	£ 0.17	2N3442	£ 1.50	1N4148	£ 0.05
BC182	£ 0.11	BCY71	£ 0.22	ZTX304	£ 0.26	OA91	£ 0.09
BC183	£ 0.11	BCY72	£ 0.13	ZTX504	£ 0.35	709	£ 0.38
BC184	£ 0.11	BFY50	£ 0.23	OC23	£ 0.50	741	£ 0.39
BC182L	£ 0.11	BFY51	£ 0.22	OC28	£ 0.70	747	£ 0.90
BC212	£ 0.13	BSX20	£ 0.22	OC35	£ 0.60	SL301B	£ 0.75
BC213	£ 0.13	TIP41A	£ 0.85	OC45	£ 0.30	CA3046	£ 0.75
BC214	£ 0.13	TIP42A	£ 0.95	OC170	£ 0.25	NE555	£ 0.85

7400	£ 0.19	7420	£ 0.20	7475	£ 0.60	7492	£ 0.70
7402	£ 0.20	7430	£ 0.20	7476	£ 0.42	7493	£ 0.67
7404	£ 0.20	7472	£ 0.34	7483	£ 1.25	74107	£ 0.45
7410	£ 0.20	7473	£ 0.48	7486	£ 0.46	74121	£ 0.51
7413	£ 0.38	7474	£ 0.42	7490	£ 0.66	74141	£ 1.00

DIECAST BOXES: 4½in × 2½in × 1in, 50p; 4½in × 2½in × 2in, 70p; 7in × 4½in × 2in, £1.50. DIL SOCKETS: 8, 14, 16 pin, 16p. RESISTORS: TR5, all values, 2.5p; TR6, 3.5p. SOLDER: 22 S.W.G., £1.90; 18 S.W.G., £1.80 ½ kilo.

VAT INCLUSIVE! POST FREE OVER £3!

P.E.C. 49-51 ST. MARY'S ROAD, OATLANDS VILLAGE
WEYBRIDGE, SURREY, KT13 9PX
Mail Order Only.

Marshall's

Everything you need is in our
New 1975 Catalogue
available now price 25p
(100 pages of prices and data)

A. Marshall (London) Ltd. Dept. PE
42 Cricklewood Broadway London NW2 3DH Telephone 01-452 0161/2 Telex 21492
& 85 West Regent Street Glasgow G2 2OD Telephone 041-332 4133

Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat
Trade and export enquiries welcome

Popular Semiconductors

2N456 0-80	2N2907 0-22	2N4061 0-11	AD150 1-15	BC171 0-13	BD135 0-43	BFY19 0-62	MJE2955 1-12
2N456A 0-85	2N2907A 0-24	2N4062 0-11	AD161 0-50	BC172 0-11	BD136 0-49	BFY20 0-50	MJE3059 0-68
2N457A 1-20	2N2924 0-14	2N4126 0-20	AD162 0-50	BC182 0-12	BD137 0-55	BFY29 0-20	MPB111 0-32
2N490 3-16	2N2925 0-17	2N4269 0-34	AD161 1-20	BC183 0-12	BD138 0-63	BFY50 0-23	MPB112 0-30
2N491 3-58	2N2926 0-17	2N4919 0-84	AD162 1-20	BC183L 0-12	BD139 0-71	BFY52 0-21	MPB113 0-47
2N492 3-99	Green 0-12	2N4920 0-99	AF109R 0-40	BC184 0-13	BD140 0-87	BFY53 0-18	MPB114 0-32
2N493 4-20	Yellow 0-11	2N4921 0-73	AF115 0-24	BC184L 0-13	BF115 0-25	BFY90 0-75	MPF102 0-39
2N696 0-22	Orange 0-11	2N4922 0-84	AF116 0-25	BC186 0-25	BF116 0-23	BFY99 0-48	MPSA05 0-26
2N697 0-16	2N3033 0-25	2N4923 0-83	AF117 0-20	BC186L 0-25	BF117 0-43	BU104 2-00	MPSA06 0-26
2N698 0-40	2N3034 0-60	2N5172 0-12	AF118 0-55	BC187 0-27	BF119 0-58	BU105 2-25	MPSA55 0-26
2N699 0-45	2N3055 0-75	2N5174 0-22	AF124 0-30	BC207 0-12	BF121 0-25	C106A 0-55	MPSA56 0-27
2N706 0-14	2N3390 0-26	2N5175 0-26	AF125 0-30	BC208 0-11	BF123 0-27	C106B 0-55	NE555V 0-70
2N706A 0-16	2N3391 0-23	2N5176 0-32	AF126 0-28	BC212K 0-16	BF125 0-25	C106D 0-65	NE560 4-48
2N708 0-17	2N3391A 0-29	2N5190 0-92	AF127 0-28	BC212L 0-16	BF152 0-20	C106E 0-43	NE561 4-80
2N709 0-42	2N3392 0-13	2N5191 0-95	AF139 0-39	BC214L 0-16	BF153 0-21	CA3020A 1-80	NE565A 4-48
2N711 0-50	2N3393 0-13	2N5192 1-24	AF170 0-25	BC237 0-13	BF154 0-20	CA3046 0-70	OC23 1-35
2N718 0-22	2N3414 0-60	2N5195 0-50	AF172 0-25	BC237 0-13	BF158 0-23	CA3048 2-11	OC28 0-76
2N718A 0-22	2N3402 0-18	2N5196 0-50	AF178 0-51	BC239 0-13	BF173 0-24	CA3089E 1-96	OC35 0-60
2N720 0-50	2N3403 0-19	2N5457 0-49	AF179 0-55	BC251 0-20	BF160 0-23	CA3090Q 4-23	OC42 0-50
2N721 0-55	2N3440 0-59	2N5458 0-46	AF180 0-68	BC252 0-18	BF161 0-42	CD4000 0-51	OC45 0-32
2N914 0-22	2N3441 0-59	2N5459 0-49	AF186 0-46	BC253 0-23	BF163 0-32	CD4001 0-51	OC71 0-20
2N916 0-28	2N3442 0-69	40361 0-48	AF200 0-35	BC257 0-14	BF166 0-32	CD4002 0-51	OC72 0-25
2N918 0-32	2N3414 0-60	40362 0-50	AF239 0-51	BC258 0-13	BF167 0-21	CD4009 1-07	OC81 0-25
2N929 0-22	2N3415 0-21	40363 0-88	AF245 0-72	BC259 0-13	BF173 0-24	CD4010 1-07	OC83 0-24
2N1302 0-19	2N3416 0-34	40389 0-46	AF279 0-54	BC261 0-20	BF177 0-29	CD4011 0-51	OC83D 0-55
2N1303 0-19	2N3417 0-24	40394 0-46	AF280 0-54	BC262 0-18	BF178 0-35	CD4015 2-66	R53 1-80
2N1304 0-24	2N3638 0-15	40395 0-65	AL102 1-00	BC263 0-23	BF179 0-43	CD4016 1-02	RL54 0-15
2N1305 0-24	2N3638A 0-15	40406 0-44	AL103 0-70	BC300 0-36	BF180 0-35	CD4017 2-66	SC35D 1-68
2N1306 0-31	2N3639 0-27	40407 0-33	BC107 0-16	BC301 0-34	BF181 0-34	CD4020 2-96	SC36D 1-46
2N1307 0-22	2N3641 0-17	40498 0-50	BC108 0-15	BC302 0-28	BF182 0-40	CD4023 0-51	SC40D 1-89
2N1308 0-40	2N3702 0-12	40409 0-52	BC109 0-19	BC303 0-54	BF183 0-40	CD4024 1-90	SC41D 1-32
2N1309 0-36	2N3703 0-13	40410 0-52	BC113 0-15	BC307 0-11	BF184 0-30	CD4027 1-56	SC45D 1-89
2N1671 1-44	2N3704 0-14	40411 2-00	BC115 0-17	BC307A 0-10	BF185 0-30	CD4028 2-34	SC45D 1-96
2N1671A 1-54	2N3705 0-12	40414 3-55	BC116 0-17	BC308 0-12	BF194 0-12	CD4029 3-79	SC50D 2-60
2N1671B 1-72	2N3706 0-12	40430 0-85	BC116A 0-18	BC308A 0-12	BF195 0-12	CD4041 2-11	SC51D 2-39
2N1671C 0-45	2N3707 0-13	40583 0-23	BC117 0-21	BC308B 0-09	BF196 0-13	CD4042 2-11	SL414A 1-80
2N1711 0-45	2N3708 0-10	40601 0-67	BC118 0-11	BC309 0-10	BF197 0-15	CD4047 0-65	SL62 4-59
2N1907 5-50	2N3709 0-11	40602 0-46	BC119 0-29	BC309A 0-10	BF198 0-18	CD4049 0-90	TAA263 1-00
2N2102 0-50	2N3710 0-12	40603 0-53	BC121 0-23	BC309B 0-10	BF199 0-18	CD4050 0-90	TAA350 2-10
2N2147 0-78	2N3711 0-11	40604 0-56	BC125 0-16	BC237 0-21	BF200 0-14	LM301A 0-48	TAA621 2-03
2N2148 0-94	2N3712 0-96	40636 1-10	BC126 0-23	BC238 0-19	BF252J 0-19	LM304A 2-03	TAA661B 1-80
2N2160 0-22	2N3713 1-20	40669 0-20	BC132 0-30	BC337 0-19	BF237 0-22	LM309K 1-88	TAD100 1-50
2N2192 0-40	2N3714 0-33	40673 0-73	BC134 0-13	BC338 0-22	BF238 0-22	LM709C 0-75	Filter 1-00
2N2192A 0-40	2N3715 1-50	AC107 0-51	BC135 0-13	BCY30 0-64	BF244 0-21	LM709 0-75	TBA271 0-64
2N2193 0-50	2N3716 1-80	AC113 0-16	BC136 0-17	BCY31 0-64	BF245 0-33	TO99 0-48	TBA710 0-64
2N2193A 0-61	2N3717 2-20	AC117 0-20	BC137 0-17	BCY32 1-15	BF246 0-58	BD18 0-38	TBA810 2-25
2N2194 0-73	2N3722 1-80	AC126 0-20	BC138 0-24	BCY33 0-45	BF247 0-49	14D1L 0-40	TBA810 1-50
2N2194A 0-30	2N3723 3-20	AC127 0-20	BC140 0-34	BCY34 0-49	BF254 6-16	LM723C 0-90	TBA810 1-50
2N2218A 0-22	2N3789 0-06	AC128 0-20	BC141 0-29	BCY36 0-55	BF255 0-17	LM741 1-00	TIP209 0-30
2N2219 0-40	2N3790 2-40	AC151V 0-25	BC142 0-23	BCY39 1-50	BF257 0-46	TO99 0-40	TIP29A 0-49
2N2219A 0-26	2N3791 2-35	AC152V 0-17	BC143 0-25	BCY40 0-87	BF258 0-59	BD18 0-40	TIP30A 0-58
2N2220 0-25	2N3792 2-69	AC153 0-25	BC145 0-21	BCY42 0-28	BF259 0-55	14D1L 0-38	TIP30A 0-58
2N2221 0-18	2N3794 0-24	AC153K 0-33	BC147 0-12	BCY58 0-21	BFS21A 2-20	LM747 1-00	TIP31A 0-82
2N2222 0-21	2N3819 0-37	AC154 0-20	BC148 0-13	BCY59 0-22	BFS28 0-92	LM748 0-74	TIP32A 0-74
2N2223 0-20	2N3820 0-64	AC176 0-23	BC149 0-12	BCY70 0-17	BF51 0-27	BD18 0-60	TIP33A 1-01
2N2224 0-25	2N3823 0-78	AC176K 0-33	BC153 0-16	BCY71 0-22	BF58 0-25	14D1L 0-73	TIP34A 1-51
2N2368 0-25	2N3900 0-28	AC187K 0-23	BC154 0-18	BCY72 0-13	BFX29 0-30	LM7805 2-00	TIP35A 2-09
2N2369 0-37	2N3901 0-32	AC188K 0-34	BC157 0-14	BCY87 3-54	BFX30 0-27	MC1303P 1-00	TIP36A 3-70
2N2369A 0-41	2N3903 0-24	ACV18 0-24	BC158 0-13	BCY88 2-42	BFX44 0-33	1-26	TIP41A 0-79
2N2646 0-55	2N3904 0-27	ACV19 0-27	BC159 0-14	BCY89 0-97	BFX63 0-24	MC1310 2-26	TIP42A 0-90
2N2647 1-12	2N3905 0-24	ACV20 0-22	BC160 0-37	BD115 0-75	BFX68 0-30	MC1458CP1 1-00	TIP2955 0-98
2N2904 0-24	2N4036 0-63	ACV28 0-20	BC167B 0-13	BD116 1-00	BFX84 0-24	MJ480 0-90	TIP3055 0-60
2N2905 0-24	2N4037 0-42	ACY30 0-58	BC168B 0-13	BD121 0-00	BFX85 0-30	MJ481 1-14	TIP300 0-13
2N2905A 0-26	2N4058 0-16	AD140 0-59	BC169B 0-11	BD123 0-82	BFX87 0-28	MJ481 1-14	ZTX302 0-20
2N2906 0-19	2N4059 0-09	AD143 0-60	BC169C 0-13	BD124 0-67	BFX88 0-25	MJ481 1-14	ZTX300 0-15
2N2906A 0-21	2N4060 0-11	AD149 1-20	BC170A 0-11	BD131 0-50	BFX89 0-45	MJ491 1-38	ZTX502 0-18
			BC171 0-13	BD132 0-40	BFY18 0-52	MJE340 0-45	ZTX500 0-21

10% Discount to Saturday callers

Bring this advertisement with you to our shops on a Saturday and you will get a 10% discount on our goods. This offer does not apply to kits.

P.C. Marker Pen Dalo 33PC

Price 87p
Zeners 400MW 2 7V-43V 11p. 1W 3.3V-120V 17p.
IC Sockets 8 DIL 16p. 14 DIL 17p. 16 DIL 20p.
Liquid Crystals—£13
Ex-stock S.A.E. for details of CMOS battery operated clock kit using LDC's
Scorpio Car Ignition Kit—£11.50 + VAT
IMF40V £1-10.
BSTB0246 £1-05. Transformer £2-75.
Minitrin £1-55.
DL707 £2-25 or 4 for £8.

Resistors Tant Beads

W	Tol	Price	Value	Price
1/2	5%	1p	0-1/35	14p
1/2	5%	1 1/2p	0-22/35	14p
1	5%	2p	0-47/35	14p
2	10%	2 1/2p	2-2/35	14p
2 1/2	5%	7p	10/16V	18p
5	5%	9p	47/6 3V	20p
10	5%	10p	100/3V	20p

Veroboard

	Copper	Plain
2.5 x 3 1/2in	0-1 0-15	0-1 0-15
2.5 x 5in	36p	26p
3 1/2 x 3 1/2in	40p	40p
3 1/2 x 5in	40p	42p
3 1/2 x 7 1/2in	£1-61	£1-26
£1-00	£1-26	£1-00
Plns x 36 30p	30p	
x 200 £1-16	£1-16	

Trade and Retail supplied.

Integrated Circuits—TTL Reductions!

SN7400 0-16	SN7409 0-33	SN7430 0-18	SN7450 0-16	SN7481 1-25	SN7496 1-00	SN74153 1-09	SN74175 1-29
SN7401 0-16	SN7410 0-18	SN7432 0-45	SN7451 0-16	SN7480 0-87	SN74100 2-18	SN74154 1-66	SN74176 1-44
SN7401AN 0-38	SN7411 0-25	SN7437 0-35	SN7453 0-16	SN7483 1-20	SN74107 0-43	SN74155 1-53	SN74177 1-18
SN7402 0-16	SN7412 0-28	SN7438 0-35	SN7454 0-16	SN7484 0-95	SN74118 1-00	SN74157 1-09	SN74190 1-95
SN7403 0-16	SN7413 0-50	SN7440 0-16	SN7456 0-16	SN7485 1-58	SN74119 1-92	SN74160 1-58	SN74191 1-95
SN7404 0-24	SN7414 0-45	SN7441 0-85	SN7457 0-30	SN7486 0-45	SN74121 0-57	SN74161 1-58	SN74192 2-05
SN7405 0-24	SN7420 0-30	SN7445 1-59	SN7458 0-38	SN7487 0-65	SN74122 0-80	SN74162 1-58	SN74193 2-30
SN7406 0-45	SN7423 0-27	SN7446 2-00	SN7459 0-44	SN7488 1-10	SN74123 0-72	SN74164 2-01	SN74196 1-58
SN7407 0-45	SN7425 0-37	SN7447 1-30	SN7475 0-59	SN7489 0-65	SN74124 1-00	SN74165 2-01	SN74197 1-58
SN7408 0-25	SN7427 0-45	SN7448 1-50	SN7476 0-45	SN7490 0-65	SN74145 1-44	SN74167 4-10	SN74198 3-18
					SN74150 1-44	SN74174 1-80	SN74200 2-88

Diodes and Rectifiers

PIV 50	100	200	400	600	800	1000
1-5	15p	17p	20p	22p		

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

ARITHMETIC TUTOR

To complement their range of computer educational aids, Limrose Electronics Ltd. have recently introduced a Digital Arithmetic Tutor.

This advanced logic trainer has been designed for teaching the principles of binary arithmetic and four-bit data word manipulation to senior students who have completed a basic course in combinational and sequential logic circuits.

The tutor consists of three general purpose 4-bit shift registers, two 4-bit synchronous binary counters, one 4-bit comparator, one 4-bit adder, a carry store, one J-K master-slave flip-flop, four 2-input NAND gates, four 2-input AND gates and three logic inverters. Two manual single pulse generators and one continuous clock pulse generator are also available.

Logic states are displayed on the front panel by means of red light emitting diodes and interconnections are made using a 1mm gold-plated terminal pin and patch lead system.

The equipment is accompanied by an illustrated instruction book containing numerous computer circuits which can be constructed on the equipment. These circuits include loading and shifting of registers, 1's and 2's complements, addition and subtraction of 4-bit numbers by serial and parallel methods and multiplication and division by the

shift-and-add-method. The instruction book also deals with the Octal Number System, binary fractional notation and overflow conditions in fixed point arithmetic.

Ideally suited for Universities and schools, prices of the tutor vary (approximately £150) and further information can be obtained from **Limrose Electronics Ltd., 8-10 Kingsway, Altrincham, Cheshire, WA14 1PJ.**

POCKET MULTIMETER

No bigger than a packet of cigarettes, the new ICE Microtest 80 multimeter combines several unique features in one compact and accurate instrument.

Covering 8 fields of measurement and 40 ranges, the meter has a 20,000 ohm per volt sensitivity, with 2 per cent accuracy on the a.c. and d.c. scales.

The design of the meter incorporates automatic electronic regulation for zero ohms, and the movement is protected against an overload of 1,000 times in the ohmic ranges before automatic cut-out.

The mirror scale of the meter enables clear and accurate reading. Each meter is supplied with a comprehensive instruction manual, a protective case and test leads.

A brief technical specification for the meter is as follows: volts d.c., in 6 switched ranges, 100mV to 1,000V (20k Ω /V); volts a.c., in 5 switched ranges, 1.5V to 1,000V (4k Ω /V). Current d.c., in 6 switched ranges, 50 μ A to 5A; current a.c., in 5 switched ranges, 250 μ A to 2.5A. Resistance, in 4 switched ranges, low ohms to ohms \times 100. Capacitance measurements are available from 25 μ F to 25,000 μ F.

The meter is powered by a 1.35V mercury battery which, in normal usage, will last up to 3 years, and a complete range of extra accessories is available. Amongst the accessories are a temperature probe (-50 to +200°C), gaussmeter and a luxmeter probe.

The Microtest 80 multimeter is priced at £11.95 ex. VAT, with special terms for quantity purchase, and is available direct from **Electronic Brokers Ltd., 49 Pancras Road, London, NW1 2QB.**

PROFESSIONAL MICROPHONE

A professional moving coil microphone with an excellent specification and features is announced by Beyer Dynamic (GB) Ltd.

Designated type M88, it has a hypercardioid polar pattern, a frequency response of 30Hz to 20,000Hz \pm 2.5dB, a high output, and is manufactured to a standard setting transient response and front-to-back ratio. This means that any two random units can be used as a stereo matched pair. Side attenuation at 120 degrees is approximately 23dB and the EIA sensitivity rating is -144dB/m.


The design and features of the M88 make it ideal for both indoor and outdoor applications and it will withstand the rigours of professional usage, being completely unaffected by humidity and extreme temperatures. The rated load of the microphone is greater than 1,000 ohms and the 200 ohm low impedance balanced output is at a level of -51dB/m at 1kHz.

The microphone is available in two versions: the M88N with standard DIN connector at £81.05 plus VAT and the M88N(C) with Cannon connector at £83.35 plus VAT. Each microphone is supplied with a protective carrying case. Optional extras include windscreens, stands and cable transformer.

Further information and nearest stockists can be obtained from **Beyer Dynamic (GB) Ltd., 1 Clair Road, Haywards Heath, Sussex, RH16 3DP.**

NOTE

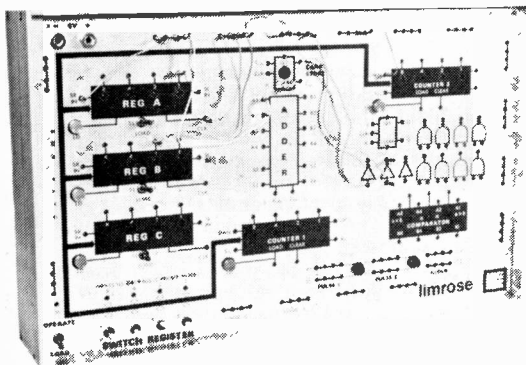
The SEAS loudspeaker kits, mentioned last month, are only available in 8 ohm versions.




Limrose Electronics Digital Tutor



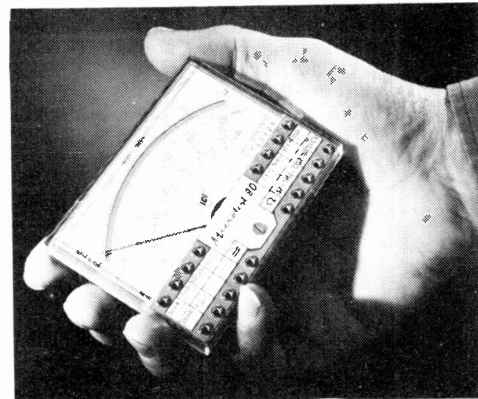M88 Professional Microphone from Beyer Dynamic



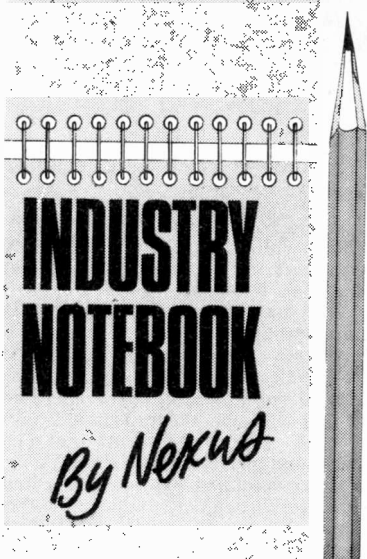Microtest 80 multimeter from Electronic Brokers



INDUSTRY NOTEBOOK

By Nexxa

EXPORTS HOLDING FIRM

Few in the electronics industry regretted the passing of 1974 with its succession of elections, budgets, industrial unrest, inflation and general economic stress. At least 1975 promises a higher level of stability and now we are well into the first quarter of the year there are already signs that whatever the depression in the home market, mainly in entertainments products, the world is still Britain's market and that trade remains at a substantial level.

The New Year saw a flurry of activity starting with confirmation from the British Overseas Trade Board that support for exhibitions at overseas trade fairs and for outward sales missions would be greater than ever before.

Few of these exhibitions, however, were specifically for electronics companies. Their turn comes a little later in the year with a major participation in a Communications Exhibition in Moscow at the end of May as just one of the high-lights in a full programme.

Quick off the mark in 1975 were Marconi-Elliott Avionics with a £1.25 million order for automatic test equipment for the US Navy and US Air Force. The equipment is for checking out head-up displays for A-7D and A-7E Corsair 2 aircraft. At the same time, sister company Marconi Communication Systems was announcing a £3 million contract for colour TV studio and OB equipment for switchover from monochrome to colour in the Egyptian TV service.

A few days later a contract worth £200,000 was announced for Marconi Mark 8 colour TV cameras for use in America.

But it's not only the truly exotic equipment that sells well. Few people are aware that Plessey, as well as being big in radar, electronic telephone exchanges and sophisticated sonar systems, have a thriving business in electronic igniters for gas stoves and boilers. In January, Plessey Windings expanded European activities by signing a contract with S.I.T., France, who will beef up markets in France, Belgium and Luxembourg.

This new agreement supplements existing arrangements in the Far East and North America. The North American breakthrough is regarded as significant because gas igniters is a cut-throat business over there. Plessey Windings is a major supplier to Caloric Corp., Pennsylvania, a principal cooker manufacturer.

Racal Group looks as vigorous as ever with Racal-Milgo high speed modems being ordered from Poland, Racal-Thermionic selling £220,000 worth of data recording equipment to French airports, and Redac Software selling computer-aided design software packages to Finland, bringing Redac customers in Scandinavia up to eight including names like Saab, Asea and Tandberg. These orders all came in early January.

Muirhead celebrated the New Year with a nice little order for 23 weather chart recorders for Kenya, Uganda and Tanzania. This brought Muirhead's export orders for this type of equipment to £325,000 in three months. Chairman Sir Raymond Brown commented that Muirhead will continue aggressive exploitation of the export potential of its products.

Smaller companies are also doing well. Membrain, for example, has installed an automatic tester for computer back-planes in West Germany. It will test over 2,000 points in less than a minute. The order was taken just before Christmas. The installation was operational by January 17. Nice work!

A heartening aspect of this brief survey is that so many of the orders, and they are only a short selection, are from countries such as the United States, France and West Germany which are themselves fully developed in the electronics industry. Another is the wide geographical spread.

WHIZZ KIDS

Gordon Pope, who led the Advance Electronics expansion programme from £800,000 turnover when he joined Advance as general manager in 1963 to today's £11 million, now rejoices in the title of Vice-President, Gould Instruments and Electronics, Europe. This follows the acquisition of Advance by

Gould last October. We may expect to hear of further vigorous developments in the months ahead.

You've got to move fast to keep up with Tom Jermyn who started making transistor pads in his garage as a part-time hobby and built up Jermyn Industries to a mini-multi-national operating in the USA and Europe as well as the UK. But Peter Smitham, who has become the top man in the Group, second only to Tom Jermyn, is no slouch. He leapt-frogged into the top spot only a little over a year after joining Jermyn to set up Mogul Electronics as Jermyn's second component distributor company. He came to Jermyn with a fine record behind him. He was the youngest divisional manager in ITT, Europe, and has a fine academic as well as business record.

Present plans are to expand Jermyn to £20 million turnover by 1980. Latest Jermyn company is Solek Ltd., manufacturing heat pipes, a product which Jermyn Industries has been pioneering in the UK for the past two years.

And how about Clive Sinclair, well known to our hobbyist readers through his electronic kits and, more recently, through pocket calculators? Predictions in some quarters that he would overtax his capacity last year were not realised and he bounced into 1975 with yet another round of price cuts on his established calculators, some new models, and a new electronic multi-meter.

On February 1 the standard Cambridge calculator came down to £12.95 (very near the £10 I was predicting in this column a year or so ago) and the Scientific came down to £19.95. His new range, announced at the same time, are equivalent to desk-top models though Sinclair prefers to call them "hand-held" indicating they will go in a brief-case, if not in the pocket. He claims to hold some 30 per cent of the calculator market in the UK, plus considerable exports with a production of some 70,000 units a month.

While majoring on calculators he is not neglecting his other product lines. His original electronic multi-meter, despite its low price, was a flop. It didn't sell at all well. Nobody liked the Nixie indicators. This year's model is very superior and has an 8mm 7-segment LED read-out on a front panel that looks and is highly professional although, at under £60, the instrument is at the low end of the price range. The old DM1 was not for me. But I'm now using the new DM2 very happily in my own workshop.

This year should also see Sinclair's long-awaited pocket TV set coming to the market place as well as an electronic digital watch.

Complete the coupon and we'll send you our new catalogue. Completely free.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.


And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.


Clip the coupon now and we'll send you your free copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

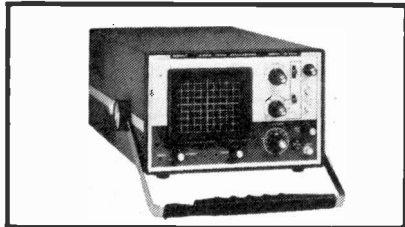
A new oscilloscope from the Heathkit range.



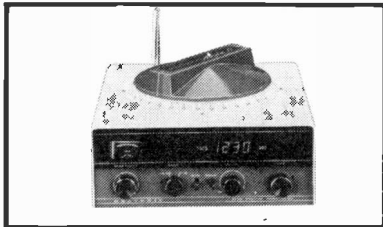Marine direction finder, with digital read-out.



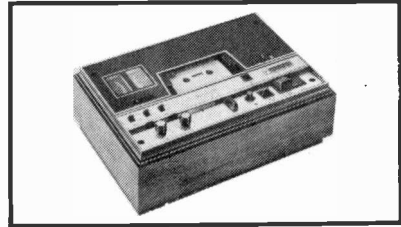Stereo cassette deck with built-in Dolby.



Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

So, when you receive your catalogue you should have hours of pleasant reading.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. PE-45, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. PE-45, Gloucester, GL2 6EE. Please send me my free Heathkit catalogue.

Name _____ Address _____ Postcode _____

Remember easy terms are available with the Heathkit Monthly Budget Plan.



MAPLIN

ELECTRONIC SUPPLIES

Get your 1975 CATALOGUE!



132 Big Pages
Includes dozens of
useful and interesting
circuits you can build:
data: hundreds of
pictures: transistor
equivalents list and
hundreds of new lines.
Packed with information.
ONLY 35p.

SUPERSONIC SAME-DAY-SERVICE-MEANS QUALITY COMPONENTS-FAST!

RESISTORS

CARBON FILM

½W 10-1MΩ 5%, 1MΩ-10MΩ 10% E12
½W 10 to 10Ω 5%, 1MΩ to 10MΩ 10% E12
1½W to 910Ω 5% E12 and E24 1p each

METAL OXIDE

½W 10Ω to 1MΩ, 2% E12 and E24 4p each

WIREWOUND

3W 0.22Ω, 0.27Ω, 0.33Ω, 0.47Ω, 10Ω,
1Ω, 5% 17p each.
1.2W to 270Ω 5% E12 13p each
Other ranges stocked. See our catalogue
for details.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68,
82 and decades E24: 11, 13, 16, 20, 24, 30,
36, 43, 51, 62, 75, 91 and decades

POTENTIOMETERS

Rotary miniature carbon track ½in spindle.
Values available: 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ.
Log Single-gang 18p, Lin Single-gang (+1kΩ) 18p.
Log or Lin Single-gang with switch 33p.
Log or Lin Dual-gang with out switch 48p.
Slider 60mm track Metal case overall length 86-15mm (knob 7p extra).
Values available: 1k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M, Lin Single Gang 36p, Log Single Gang 38p, Lin or Log Dual Gang 45p.
Presets: 0.1W vert. or hor 100Ω, 220Ω, 470Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 10kΩ, 22kΩ, 47kΩ, 100kΩ, 220kΩ, 470kΩ, 1MΩ 7p each

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd	V Price	Mfd	V Price	Mfd	V Price
1	83	6p	47	63	8p
1	5	83	68	63	330
2	2	83	68	16	6p
3	3	63	68	63	14p
4	7	63	100	4	6p
6	8	40	100	10	6p
6	8	63	100	25	6p
10	25	6p	100	40	5p
10	63	6p	100	63	15p
15	16	6p	150	63	6p
15	40	6p	150	5p	1000
15	63	6p	150	25	6p
22	10	6p	150	40	14p
22	25	6p	150	53	18p
22	63	6p	220	4	6p
33	6	3	220	10	6p
33	16	6p	220	16	6p
33	40	6p	220	25	14p
47	4	6p	220	40	16p
47	10	6p	220	63	25p
47	25	6p	220	63	25p
47	40	6p	330	4	6p
47	40	6p	330	10	6p

SWITCHES

Rotary adjustable stop, 1 pole, 2 to 12 way, 2 pole, 2 to 6 way, 3 pole, 2 to 4 way, 4 pole, 2 or 3 way 36p each. Slide Sub-min DPDT 9p, Slide min. DPDT 13p. Push to make non-locking SPST 14p. Push-on, push-off locking DPST 250V 4A 48p. Rocker white DPST 250V 10A 40p. Rotary mains DPST 250V 2A 20p. Toggle with on/off plate DPDT 250V 1-5A 25p.

TRANSISTORS AND DIODES

AC127	18p	BY126	13p
AC128	18p	BY127	13p
AC176	17p	BY164	49p
AD161		BZV88	
162MP	93p	series	13p
BA100	9p	MPP102	36p
BA145	22p	OA91	6p
BC107	10p	CA200	7p
BC108	10p	OC71	20p
BC109	13p	SC146D	88p
BC109C	15p	T1543	28p
BC142	23p	W005	30p
BC143	28p	W04	33p
BC147	10p	1N914	4p
BC148	10p	1N4001	6p
BC149	12p	1N4002	6p
BC168C	12p	1N4003	7p
BC169C	12p	1N4004	7p
BC178	17p	1N4005	8p
BC182L	10p	1N4006	8p
BC183L	12p	1N4007	8p
BC184L	12p	1N4148	4p
BC212L	14p	2N1302	20p
BC213L	15p	2N1303	20p
BC214L	18p	2N1304	30p
BCY71	22p	2N1711	24p
BD131	45p	2N2219	25p
BD132	54p	2N2646	45p
BD131/2MP	£1-20	2N2905	33p
		2N2926	
BD135	36p	Or	10p
BD139	49p	Ye	12p
BD140	89p	Gn	13p
BF256	35p	2N3053	18p
BF259	25p	2N3055	49p
BFX29	30p	2N3819	22p
BFX30	33p	2N5459	51p
BFX84	30p	7400	16p
BFX85	36p	7413	39p
BFX87	30p	7447	£1-10
BFX88	25p	7473	54p
BFY50	20p	7474	45p
BFY51	22p	7490	93p
BFY52	20p	7493	93p
		74121	39p

L.E.D. RED 2mcd 1in 15p.
Panel mtg. clip 5p.
(Other colours and 7-seg displays in our catalogue)

INTEGRATED CIRCUITS

CA3046 (14-pin DIL)	69p
LH042CH (TO99)	£4-25
MC1310P (14-pin DIL)	£2-50
MC1496 (14-pin DIL)	95p
MFC4000B	59p
MFC6040	83p
NE555V (8-pin DIL)	65p
SG1485 (14-pin DIL)	£2-70
SG3402 (14-pin DIL)	£1-69
µA741C (8-pin DIL)	36p
µA741C (14-pin DIL)	45p
µA747C (14-pin DIL)	£1-05
µA 748C (8-pin DIL)	39p
ZN414 (TO18)	£1-20

VOLTAGE REGULATORS
µA7805 5V 1-5A (TO3) £1-75
µA7815 15V 1-5A (TO3) £1-75
MVR 5V, 12V, 15V, 500mA (TO3) £1-60
µA78M05 5V 500mA £1-30
µA78M15 15V 500mA £1-30
µA78L05 5V 100mA (TO92) 60p
µA78L15 15V 500mA (TO92) 60p
µA723C Variable 2 to 37V (TO92) 75p
Our catalogue contains application circuits and data for all the above I.C.s and many more.

DISCOUNTS

Details in our catalogue. Start collecting MES Discount Vouchers NOW!

BCD OUTPUT SLIDE SWITCH
Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue £1-38.

PLUGS AND SOCKETS

Din	Plug	Chassis Socket
2-pin	8p	6p
3-pin	9p	7p
4-pin	10p	7p
5-pin A (180°)	10p	7p
5-pin B (240°)	10p	7p
6-pin	10p	9p

JACK PLUGS

2-5mm Plastic Barrel	9p
2-5mm Metal Barrel	15p
3-5mm Plastic Barrel	9p
3-5mm Metal Barrel	15p
½in Std. Mono Plastic Barrel	13p
½in Std. Mono Metal Barrel 24p	
½in Std. Stereo Plastic Barrel	18p
½in Std. Stereo Metal Barrel 30p	

JACK CHASSIS SOCKETS

2-5mm open-type metal	9p
3-5mm open-type metal	9p
½in Std. Mono open-type metal	10p
½in Std. Mono moulded with 2 break contacts	14p
½in Std. Stereo open-type metal	15p
½in Std. Stereo moulded with 3 break contacts	18p
In-line sockets of all above types stocked.	

PHONO

Plastic-topped plug	5p
Screened plug	12p
Chassis socket single	4p
Chassis socket twin	6p

MAINS CONNECTORS

P360 3-pin 1.5A Chassis plug with line socket	33p
SA2190 3-pin 5A Chassis	25p
SA1862 Line socket for SA190	28p
P437 3-pin 5A Chassis socket with line plug	66p

TRANSFORMERS

LT700 min. output. Pri. 1kΩ, Sec. 50 200mW 50p; Sub-min mains 6-0-6V 100mA 95p, 12-0-12V 50mA 95p (Size both approx. 30 x 27 x 25mm)
Min. mains 0-6V 500mA, 0-6V 500mA £1-36; 0-12V 250mA, 0-12V 250mA £1-36; 0-20V 100mA, 0-20V 150mA £1-36; 0-24V 125mA, 0-25V 125mA £1-36.
Mains MT3AT. Sec: 12-15-20-24-30V 2A £3-60.
Mains MT26AT. Sec: 0-15-20V 1A, 0-15-20V 1A £3-98.

ORGANS

A Full Scale Electronic Organ That You Can Build To Your Own Specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS.

Leaflet MES51 Price 15p, describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.
Leaflet MES52 Price 5p continues the description of the MES50 series organ and shows you how to add a second keyboard with lots more stops.



THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4kΩ to 8kΩ (highest) or 2kΩ to 4kΩ or 1kΩ to 2kΩ, etc. right down to 16Hz to 32Hz! And this to the new compatible design is even smaller, only 3.5in x 3.7in including gold-plated edge connection.
DMO2T includes built in variable depth and rate frequency shift tremulant.
DMO2 £12-25 DMO2T £14-25
SAJ110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1-80 each or 6 for £9-94 or 12 for £18-16.
Keyboards high quality, fully sprung.
Flat-front 48-note F to E £15-95
Sloping-front 49-note C to C £15-95
Sloping-front 61-note C to C £20-44
Swell pedal with 10kΩ log. pot £8-33
*Spring Line Unit (short) £3-05
*Spring Line Unit (long) £8-29
*Reverberation Driver Module £5-34
*S.A.E. please for full details: leaflet MES24
Gold-clad phosphor-bronze wire 30p per yd
Palladium earth bar 15p per octave length
Contact Blocks 2-make (GB2) 22p
Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch 59p

SPECIAL OFFER

5W Audio Amp I.C. TBA810S with data and circuits.

Price £1-00

"ELECTRONICS TODAY INTERNATIONAL" 4600 SYNTHESIZER

We stock all parts for this brilliantly designed synthesiser. This includes all the P.C.B.s, metalwork and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the E.T.I. International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. S.A.E. please for price list and specification. We also stock all parts for the P.E. Synthesiser, and Minisonic.



P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea (0702) 44101

VAT Please add 8% to the final total. Post and Packing FREE in U.K. (15p handling charge on orders under £1)

First-class post pre-paid envelope supplied free with every order.

PATENTS REVIEW...

TRANSDUCER IMPROVEMENTS

In BP1 364 669, STC Ltd. suggest some simple improvements to moving-iron transducers of the type used in some loudspeakers and telephone handsets. The basis of the technique described could be of interest to the experimenter.

Fig. 1 shows a conventional, rocking armature transducer (either a microphone or loudspeaker). A permanent magnet has pole pieces between which an armature is pivoted. The armature is coupled to a diaphragm and speech coils are wound on the pole pieces.

The passage of speech currents through the coils causes the armature to rock, or rocking of the armature induces currents through the coils. The arrangement works well until the armature is deflected too far and sticks or "freezes" against one pole of the magnet.

Diaphragm Fig. 2 shows the patented arrangement for preventing such freezing. The armature carries small magnets, one each side of its pivot point. The armature magnets lie between two end magnets and two front magnets. The polarity of the magnets is such that the armature floats freely in the central position as shown.

If currents are passed through the coil wound round the armature in such a direction as to make the left hand end of south polarity, then that end moves upwards towards the end magnet 1. Reversing the current direction causes an opposite movement, and the

passage of an alternating current through the coil produces a corresponding vibration of the diaphragm. Similarly, movement of diaphragm induces currents in the coil.

Because of the repulsive forces between the magnets there can be no freezing of the armature and relatively rough-and-ready constructional techniques will provide a floating armature of low stiffness.

SPARK-FREE SUPPLY OF A.C.

In BP 1 366 134, Victor Products (Wallsend) Ltd., of Northumberland, claim a simple electromagnetic coupling system for supplying a.c. supplies to loads in hazardous environments, such as inflammable gas atmospheres.

The obvious risk under such situations is that a spark will be generated when a connection is made or broken. It is not new to suggest using two separable halves of a transformer to provide spark-free connection and disconnection. The primary of a transformer is provided in a wall socket and the secondary is included in a plug. When the plug is pushed into the socket the flux from the primary induces current in the secondary. The problem is ensuring that the primary does not drain current and overheat when the plug is disconnected.

The inventors show in their patent a socket with a primary winding and a plug with a secondary winding. To prevent current drain from the primary when the secondary is removed, an inductor is connected in series with the primary and a capacitor is connected in parallel with the inductor and primary. This parallel circuit is in series with a further inductor.

When the plug (sec) is coupled with the socket (pri) the circuit is tuned to the supply frequency. When the secondary is separated the inductance of the circuit decreases to cause detuning. Thus the current flowing through the primary also decreases.

As an example of component values, where the effective inductance of the primary decreases from 100mH to 10mH on removal of the secondary, a 0.16 μ F capacitor was used to provide effective limiting for a supply frequency of 1kHz.

SPOT WELDING

In BP1 370 003, the Grumman Aerospace Corporation of Long Island, New York, explains how it is possible to spot weld by using a massive magnetic field. This creates a pressure on a metal workpiece and deforms it.

The Americans now suggest generating stress waves electromagnetically, to render the metal momentarily plastic. This they claim to have achieved with a device and circuit as shown in Fig. 1.

The power supply comprises a d.c. source, switch S1 and a capacitor bank. The capacitors are charged by the d.c. source when S1 is closed.

When charging is complete, switch S2 is closed to feed a high amperage current pulse of short duration to a pancake coil. The coil produces a high intensity magnetic field pulse which intersects a driver of aluminium or hardened copper. The driver acts as a one turn secondary winding of a transformer and the massive current which is induced in the driver sets up a high intensity magnetic field around it.

The electromagnetic repulsion created by the interaction of the two high intensity fields generates a stress wave in the driver, which is propagated through a focussing cone towards a tip. The combined effect of the backing mass and the stress from the tip deforms the workpiece and causes a spot weld.

The inventors claim success with voltages of between 4 and 7 kV, focusing cones of hardened steel, and a pancake coil of 18 turns of rectangular copper wire.

BP 1 364 669

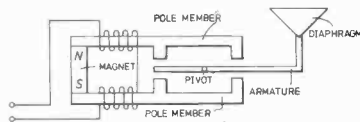


Fig. 1.

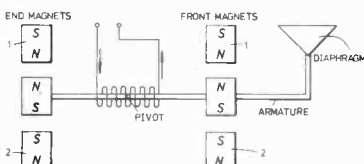


Fig. 2.

BP 1 370 003



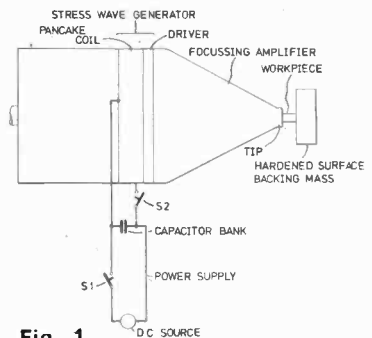


Fig. 1.

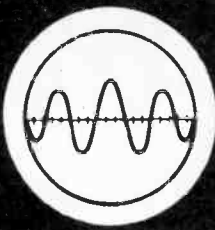

TUAC

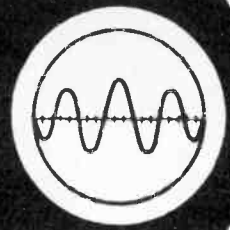

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD·LONDON SW17 9PG 01-672 3137/9080

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1M Ω ; Deck Tone Controls—treble + 20 - 10dB at 12kHz; Bass + 22 - 15dB at 40Hz; Mic Input—200 ohms upwards. 2mV into 10k Ω ; Mic Tone Control—Total Variation Treble 15dB. Total Variation Bass 10dB. Tape Input—30mV into 47k Ω ; Power Requirements—30-45 volts at 100mA.

£26·50
PANEL SIZE
18 x 4½ in.
DEPTH 3 in.

HOW TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD (PE2/3)
or quote Access/Barclay Card No.
and post to TUAC LTD (PE2/3)

163 Mitcham Road, London, SW17 9PG


We accept phone orders against Access/Barclay Card Holders
Phone: 01-672 3137/9080

STOCKISTS—CALLERS ONLY

Arthur Sallis Ltd., 28 Gardner Street, Brighton, Sussex. Tel 65806.
Bristol Disco Centre, 86 Stokes Croft, Bristol 1. Tel. 41666. Socodl, 9
The Friars, Canterbury. Tel. 60948. Cookies, 132 West Street, Crewe. Tel.
4739 or 581202. Calbarrie Audio, 88 Wellington Street, Luton. Tel. 411733.
A1 Music Centre, 88 Oxford Street, Manchester. Tel. 061-236 0340.
Damon Electronics, 99 Carrington Street, Nottingham. Tel 53880.
Mitchell Electronics, 64 Winchester Street, Salisbury. Tel 23689. Wec
Lighting, 10 Commercial Road, Southampton. Tel. 28102.

3 CHANNEL LIGHT MODULATOR

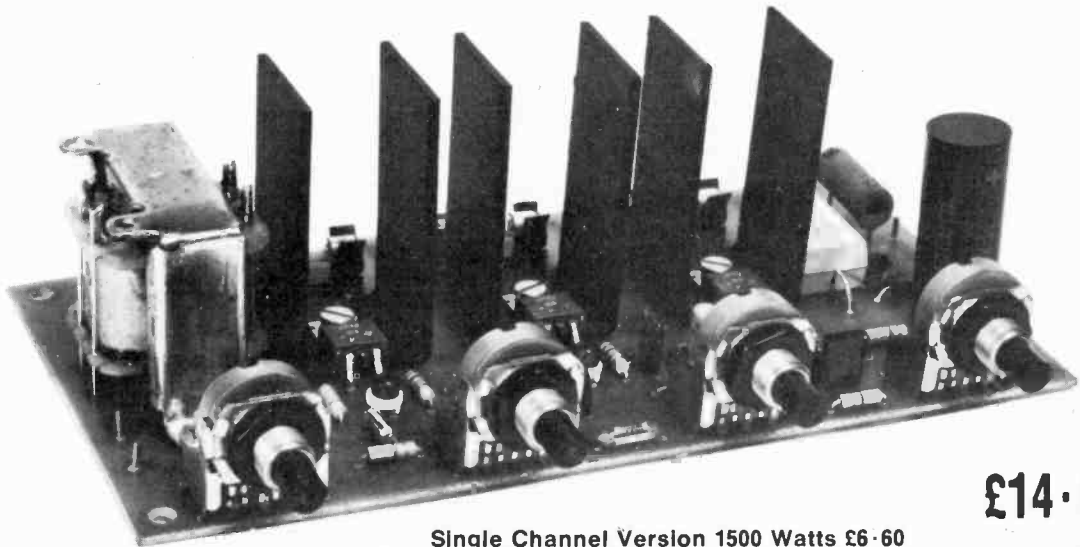
- R.C.A. 8 Amp Triacs ● 1000W per channel ● Each channel fully suppressed and fused
- Master control to operate from 1W to 100W ● Full wave control—12 easy connections




£14·90

Single Channel Version 1500 Watts £6·60

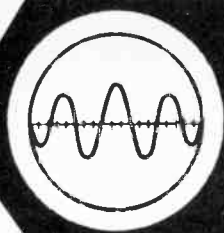MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT · OPEN 6 DAYS A WEEK 9·30am-6·00pm




TUAC

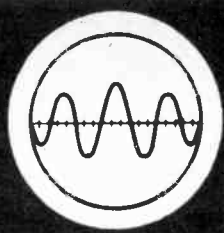

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

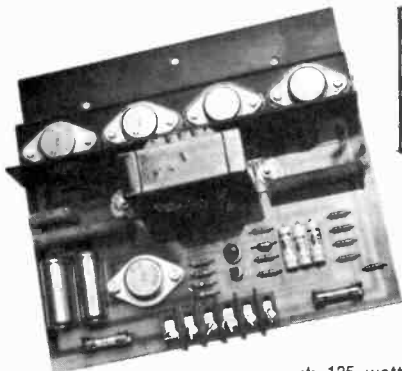NEW TUAC POWER MODULES offering more power and quality than ever before.




Specification on all power modules
All output power ratings ± 0.5 dB
Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10k Ω . Frequency response 20Hz-20kHz ± 2 dB. Hum and noise better than -70dB.

TP125
7 x 6 $\frac{1}{2}$ x 3in
£17.00

★ 125 watts RMS continuous sine wave output

★ 4 R.C.A. 150 watt 15 amp output transistors

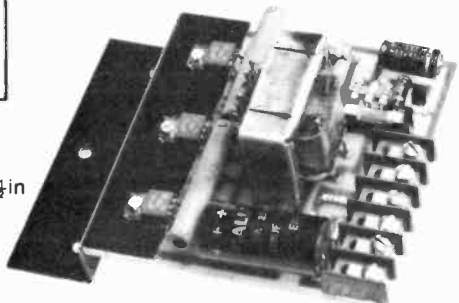


TL30
4 x 5 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in
£7.90

★ 30 watts RMS continuous sine wave output

★ 2 R.C.A. 40 watt output transistors

★ Rugged layer wound driver transformer
★ Short—Open—and Thermal overload protection
★ Only 6 connections

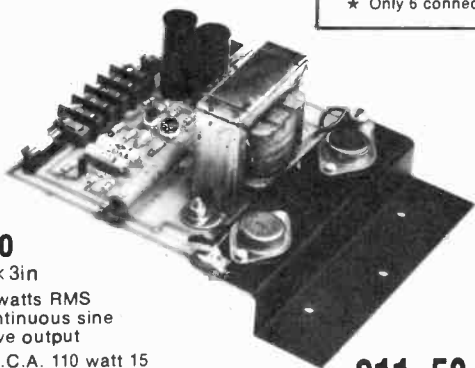

TL60
5 x 5 x 3in

★ 60 watts RMS continuous sine wave output

★ 2 R.C.A. 110 watt 15 amp transistors


£11.50

TL100
5 x 5 x 3in

★ 100 watts R.M.S. continuous sine wave output

★ 2 R.C.A. 150 watt 15 amp transistors

£13.20

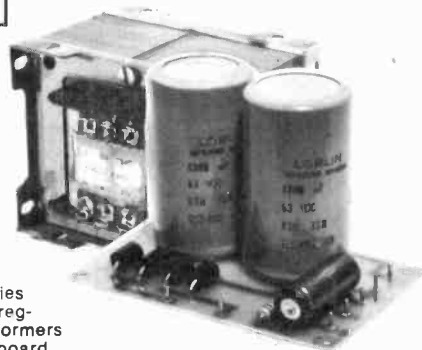

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 \pm 50 volts for one TP125	£11.50
PS 100 \pm 45 volts for one TL100	£10.50
PS 60 \pm 40 volts for one TL60	£9.30
PS 30 + 50 volts for one TL30	£5.90
PSU 2 for supplying disco mixer	£4.65


PREAMPLIFIERS

All TUAC audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into various wide range tone control circuits producing superb quality from any signal.

VAO8 Vol. Treble, Mid and Bass controls. Hi. IMP. FET I/P suitable Mid. Guitar, Radio. Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20-15dB at 1Hz Bass +20-10dB at 40Hz. **£4.90**

VAO6 Vol. Treble and Bass controls. Sensitivity 8mV at 40Hz. Treble +28-15dB at 12kHz. Bass +18dB **£4.15**

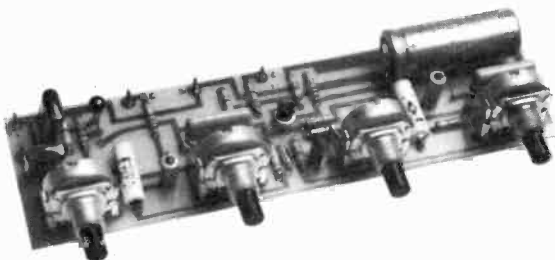SVAO1 Stereo Pre Amp Vol. Treble, Mid and Bass controls. Hi. IMP. FET, I/P suitable Mid, Guitar, Radio. Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20-15dB at 4kHz. Bass +20-10dB at 40Hz. Plus Full Balance Control **£10.00**



ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED—JUST SEND OR PHONE US YOUR NUMBER · H.P. ARRANGED THROUGH PAYBONDS

INSULATED TERMINALS

Available in Black, Red, White, Yellow, Blue, and Green. Brand New 12p each.



METERS NEW! 2 1/2 in. Flush round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20. Voltmeter 0-300V A.C. All types £2. Post 15p.



600 WATT DIMMER SWITCH Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1) Coil ohms	1	2	3	4	
	52	4-8	2 c/o		70p*
Col. (2)	58	5-9	6 c/o		80p*
Working d.c. volts	185	8-12	6M		80p*
Col. (3)	230	9-18	4 c/o		70p*
Contacts	430	15-24	2 c/o		80p*
Col. (4)	700	12-24	2 c/o		60p*
Price	700	16-24	4M 2B		60p*
	700	16-24	4 c/o		80p*
HD =	1,250	18-36	2 c/o		60p*
Heavy duty	2,500	31-43	2 c/o HD		60p*
	2,500	36-45	6M		60p*
	9,000	40-70	2 c/o		60p*
	15k	85-110	6M		60p*

*Incl. Base. All prices incl. P. & P.

OPEN TYPE RELAYS

6 VOLT D.C. 1 make contacts 35p. Post 10p.
9 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 10p.
12 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 10p.
24 VOLT D.C. 3 c/o 75p. Post 10p.
 2 HD c/o 700 ohm coil. 75p. Post 10p.
 4 c/o 300 ohm coil. 85p. Post 10p.
ENCLOSED TYPE RELAYS
24 VOLT A.C. Mfg. by ITT. 3 h.d. c/o contacts. 55p. Post 10p. Base 15p.
55 VOLT A.C. RELAY
 3 h.d. c/o contacts. Price 55p. Post 10p. Base 15p.
100 VOLT A.C. 2 c/o sealed type. 75p. Post 10p. Base 15p.

240 VOLT RELAY
 3 h.d. c/o contacts. Price 75p. Post 10p. Octal plug in base 15p extra.
230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d. 15 amp c/o contacts. Amp connectors. Price £1. Post 10p.
230/240 VOLT A.C. RELAY
 3 c/o 5 amp contacts. Sealed. Mfg. ISKRA. £1.25. Post 10p. Base 15p extra.
CLARE-ELLIOTT TYPE RP7641 G8
 Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 70p post paid.
 110V. 2 c/o. 20 amp contacts. £1.25. Post 10p. Many others from stock—phone for details.

VERY SPECIAL OFFER

MINIATURE ROLLER MICRO SWITCH. 5 amp. c/o contacts. NEW. Price 10 for £1.50. Post 10p. (Min. order 10). As above less roller/lever. 20 for £2. Post 10p. (Min. order 20). Ditto press to break. 20 for £1.50. Post 10p.



SUB-MINIATURE REED RELAY 3-9 volt d.c.

1 make, size 1 1/2 x 1 1/2 in. Outstanding Value only £1 for six, £1.50 for ten. Post 15p. (Min. order six.)



TRIACS GENERAL ELECTRIC POWER-GLA TRIACS 10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146E 10 amp. 500 PIV. £1.00. Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.

230/250 VOLT A.C. SOLENOID

Approximately 1 1/2 lb pull. Size of feet 1 1/2 x 1 1/2. Price £1.00. Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb pull 1 inch travel. Two x approx. 1lb pull 1/2 inch travel. 6 x approx. 4oz. pull 1/4 inch travel. One 24 volt d.c. 1 heavy duty single make relay. Price £2.50. Post 60p. **ABSOLUTE BARGAIN.**

CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd. Precision continuously rated, smooth running, 230/240V a.c. motor. £6.50. Post 50p.



All Mail Orders—Callers—Ample Parking
Dept. PE4, 57 BRIDGMAN ROAD CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE
 200 watt (1 amp) £9.00
 0.5 KVA (2 1/2 amp) (MAX) £10.00
 1 KVA (5 amp) (MAX) £14.70
 2 KVA (10 amp) (MAX) £28.10
 3 KVA (15 amp) (MAX) £31.25
 4 KVA (20 amp) (MAX) £72.50
 37.5 amp (MAX) £102.50



CARRIAGE AND PACKING EXTRA
OPEN TYPE 1 amp (panel mount) £9.00

L.T. TRANSFORMERS

0, 10, 17, 18 Volt at 10 amp. £7.90. Post 60p.
 0, 6, 12 Volt at 20 amp. £9. Post 60p.
 0, 12, 24 Volt at 10 amp. £9.20. Post 60p.
 0, 6, 12, 17, 18, 20 Volt at 20 amp. £10.40. Post 60p.
 Other types to order at short notice—Phone your enquiries.

AUTO TRANSFORMERS

Step up step down
 0-115/200/220/240 Volts. 75 watt £2.64. Post 36p.
 150 watt £3.18. Post 36p. 300 watt £6.20. Post 50p.
 500 watt £9.20. Post 65p. 1000 watt £12.00. Post 80p.

300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0-115V for 115 or 230 volt. Secondary two 115V at 150 VA each for 115 or 230 volt output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb.
SPECIAL OFFER PRICE £5. Carr. 80p.

230/240 VOLT A.C. MINIATURE MOTOR. 20 R.P.M. Price £1. Post 10p.

BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 0.38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle 0.28 amp. The above two precision made U.S.A. motors are offered in as new condition. Input voltage of motor 115V A.C. Supplied complete with transformer for 230/240V A.C. input. Price, either type £6.25. Post 50p or less transformer £3.75. Post 40p.



'FRACMO' 240 VOLT A.C.

50 cycle SINGLE PHASE GEARED MOTOR
 33 r.p.m. 30 lb. ins. Reversible. Fitted with mounting feet. Brand New. £14. Post 60p. (Total price incl. VAT £15.77).



9-12 VOLT D.C. GOVERNED REVERSIBLE MOTOR

Machine cut gear train, giving final speed of 2 r.p.m. with cam driving 3 sub-miniature micro-switches (removable). Spindle 12mm long 6mm dia. Built to PO spec. in heavy metal hinged case. £3.75. Post 25p.



POWER RHEOSTATS !!!

Superior Quality Precision Made **NEW POWER RHEOSTATS**

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
 25 WATT 10/25/50/100/150/250/500/1k/1.5k/2.5k ohm. £1.70. Post 10p.
 50 WATT 15/10/25/50/100/250/500/1k ohm £2.10. Post 10p.
 100 WATT 15/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £3.30. Post 15p.
 Black Silver, Skirted knob calibrated in Nos. 1-9 1/2 in. dia. brass bush. Ideal for above 22p each.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size 1.8in. W. 4in. H. 6in. weight 6lb. 1,000V, 1,000 megohms. £34. Post



All prices are subject to **8% VAT.** (8p in the £)
 To all orders add 8% VAT to total value of goods including carriage/packaging.


SERVICE TRADING CO.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. **RANGE OF FOUR STROBE KITS FROM STOCK. PRICES FROM £6.30 to £22. S.A.E. for details.**

COLOUR WHEEL PROJECTOR

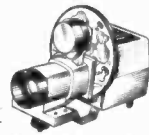Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £20.50. Post 50p. Extra colour effect wheels from stock. S.A.E. for details.



BIG BLACK LIGHT

400 Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. P.F. ballast is essential. Price of matched ballast and bulb £16. Post £1. Spare bulb £7. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES

2ft 20 watt, £4.25. Post 25p. (For use in standard bi-pin. MINI. 12in 8 watt, £1.60. Post 15p. 9in 6 watt, £1.30. Post 15p. Complete ballast units and holders for 9in and 12in tube. £1.70. Post 25p. (9in and 12in measures approx.)

U.D.I. SINGLE CHANNEL

750 WATT MANUAL AUTO DIMMER
 750W Solid State Fader, with three functions. Manual fade; Auto fade-up; Auto fade-down. Automatic cycling up and down. Functions selected with 'three-position' rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" x 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE £15. Post 30p.

50 IN 1 ELECTRONIC PROJECTOR KIT

50 easy to build projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 25p.

PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.
 2 cam model. £2.00 post 30p.
 4 cam model. £2.50 post 30p.
 8 cam model. £4.75 post 35p.
 8 cam model, each cam fully adjustable. 6 r.p.m. M.f.g. by Magnetic Devices. £7.50. Post 30p.



A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135mm x 130mm x 60mm. Price £2. Post 20p. (Total incl. VAT and Post £2.38).



VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp. contacts. Fitted diecast case. Tested and in perfect condition £4.75. Post 25p.



COIN MECHANISM (Ex London Transport)

Unit containing, selector mechanism for 1p, 2p and 5p coins. Micro switches, relays, solenoid operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only £2.50. Post 60p.

'STC' 6" RED ALARM BELL

24/48 volt DC. Brand New. Price £4. Post 50p.

'GENTS' 6" ALARM BELL

200/250V AC/DC. Brand New. Price £5. Post 60p.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET LONDON WC2H 7JJ
 Phone 01-437 0576

TRANSISTORS									
AC107	0-16	BC159	0-13	C111E	0-55	76217	0-30		
AC126	0-13	BC171	0-16	CY5441	0-27	V405A	0-25		
AC127	0-13	BC172	0-16	CY7464	0-10	V10-50	0-40		
AC128	0-12	BC173	0-16	CV7594	0-25	Y5	0-10		
AC138	0-20	BC184	0-18	CV7648	0-30	Z116	0-75		
AC141	0-20	BC208	0-12	CV8762	0-40	ZTX107	0-12		
AC142	0-20	BC209	0-13	MD533	0-30	ZTX302	0-17		
AC153	0-22	BC212L	0-14	ME4102	0-12	ZTX502	0-17		
AC176	0-15	BC301	0-30	NKT162	0-25	ZG106	0-21		
AC176	MP	BC306	0-15	NKT164	0-25	ZG306	0-44		
AC128	0-25	BC337	0-15	NKT212	0-20	ZG345	0-25		
AC178	0-25	BC211	0-28	NKT721	0-17	ZG402	0-15		
ACY17	0-28	BD131	0-40	NKT224	0-15	ZN526	0-46		
ACY19	0-22	BD132	0-40	NKT270	0-15	ZN897	0-15		
ACY20	0-22	BD131	MP	NKT278	0-15	ZN715	0-35		
ACY21	0-22	BD132	0-75	OC22	0-50	ZN726	0-25		
AD161	0-30	BD139	0-60	OC28	0-40	ZN730	0-19		
AD162	0-30	BD140	0-60	OC35	0-55	ZN1304	0-19		
AD161	MP	BF167	0-24	OC36	0-40	ZN1305	0-19		
AD162	0-75	BF194	0-12	OC45	0-14	ZN1309	0-25		
AF115	0-30	BF196	0-15	OC70	0-11	ZN1754	0-20		
AF116	0-30	BF197	0-16	OC71	0-11	ZN2484	0-30		
AF178	0-30	BF274	0-30	OC72	0-15	ZN2926	0-14		
ASYS2	0-22	BFX29	0-30	OC81	0-17	ZN3055	0-50		
BC107	0-09	BFX85	0-33	OC201	0-30	ZN3702	0-12		
BC108	0-09	BFY50	0-20	OC45K	0-25	ZN3703	0-12		
BC109	0-09	BFY51	0-20	SG526920	0-15	ZN3704	0-14		
BC142	0-30	BFY52	0-20	SG526942	0-14	ZN3710	0-10		
BC143	0-30	BFY81	0-65	SG526949	0-15	ZN3711	0-10		
BC147	0-18	BSY38	0-20	SG527022	0-18	ZN3713	0-20		
BC148	0-18	BSY39	0-20	SU203	0-65	ZN4047	0-25		
BC149	0-18	BSY40	0-31	TK100	0-75	Z5322	0-46		
BC157	0-11	BSY41	0-31	TIS90M	0-33	Z5712	0-46		
BC158	0-11	C111	0-50	TIS91M	0-33	Z5745	0-46		

DIODES									
AA119	0-06	BY100	0-16	IN34A	0-08	IN4003	0-05		
2AALL9	0-18	BY127	0-16	IN202	0-10	IN4005	0-07		
AAZ15	0-11	BY164	0-55	IN252	0-10	IN4006	0-06		
BA90	0-10	BYX38 300	0-46	IN984B	0-10	IN4007	0-09		
BA111	0-20	BZ123	0-28	IN1124	0-10	IN4151	0-04		
BA112	0-20	BZ195	0-15	IN3064	0-12	IN4148	0-06		
BAY31	0-15	OA81	0-06	IN4001	0-05	IN4244	0-07		
BAY74	0-18	OA200	0-07	IN4002	0-05	IS3036A	0-15		

ZENER DIODES									
40mW 2.33V	all	0-07	each	BZ91 C12 STUD TYPE	3-00				
1W 1.5-2.33V	all	0-16	each	BZ91 C33R STUD TYPE	3-00				
				BZ91 C43 STUD TYPE	3-00				

TESTED S.C.R.s		LOGIC I.C.s	
50 PIV 3A TO-66 CASE	0-25	TYPE	
100 PIV 3A TO-66 CASE	0-25	MC930	0-15
200 PIV 3A TO-66 CASE	0-30	MC932	0-15
400 PIV 3A TO-66 CASE	0-40	MC933	0-15
600 PIV 3A TO-66 CASE	0-50	MC934	0-15
800 PIV 3A TO-66 CASE	0-60	MC945	0-30
		MC9097	0-40

ZENER DIODES		74 SERIES I.C.s	
CV7204 11V STUD TYPE	0-60	SN741	0-45
		SN7400	0-18
		SN7401	0-18
		SN7402	0-18
		SN7490n	0-39
		SN7490n	0-74

THYRISTOR BT 109	
CON:BRI	0-75

OPTOELECTRONICS	
ORP 12	0-48
OCF 71	0-48

BONANZA

1/2 MILLION CAPACITORS

WE CANNOT NAME THE WELL KNOWN MAKER DUE TO THE LOW PRICE THEY ARE OF THE VERY LATEST DESIGN AND TYPE 100 MIXED VALUES AND TYPES VALUED AT OVER £5. YOURS FOR ONLY £1.50. NO MORE TO PAY (WHAT A BARGAIN)

Electrolytics 5 8uF at 40V, 100uF at 63V, 680uF at 16V, etc
Polyester 1500uF at 400V, 0.0015uF at 400V, 0.0068uF at 400V.
Miniature Metallized Film 0.22uF at 250V, 47nF at 250V, etc
Ceramic Plate 82pF at 100V, 22000pF at 40V, 4700pF at 40V, etc
etc etc etc etc etc etc etc etc etc

SPECIAL OFFER I.C.s	SPECIAL OFFER
BULK PURCHASE BRAND NEW 14 PIN DECADE COUNTER SN 7490 2 FOR ONLY £1-00	BULK PURCHASE BRAND NEW BC 337 TRANSISTORS NPN TO 84 case 20 FOR £1-00

SPECIAL OFFER	SPECIAL OFFER
RESISTORS CARBON FILM CR 25 TYPE 1m2 2m2 10% 10 120 470k 5% etc etc etc etc 200 MIXED FOR ONLY £1-00	BRAND NEW IN4148 BRAND NEW 40 FOR ONLY £1-00

SPECIAL OFFER	SPECIAL OFFER
MAINS TRANSFORMER 240V INPUT 12V 8A 25V 1-1A 30V 1-5A C CORE £2-50 P. & P. 25p. PAPST TAPE MOTOR 220V 50Hz £2-50 P. & P. 25p. AMPLIFIER 9V 500W 0-85p. P. & P. 5p. P. A. R. BISTABLE RELAY LATCHING 24V DC4 C/O CONTACTS 0-65p. RELAY KEYSWITCH 24V 1 POLE 2 WAY NEW AND BOXED 0-85p. RELAY T.M.C. MINIATURE 3.300 ohms 2 POLE 4 WAY 0-55p. TELEPHONE DIALS BRAND NEW £1-00 EACH P. & P. FREE. ELECTROLYTICS 0-1uF 250V 8p. 25uF 50V 8p. 40uF 16V 4p. 16-16uF 500V CAN TYPE 35p. 32-32uF 450V CAN TYPE 35p. CAPACITORS 0-047uF 400V 8p. 125uF 10V 7p. 100uF 10V 8p. FREE OFFER ONE J PACK OF YOUR OWN CHOICE WITH ALL ORDERS VALUED AT £5.00 AND OVER. PLEASE ADD 10% TO ALL TOTAL ORDERS FOR POST AND PACKAGE.	ONLY £3-00 TCA270b

MAIL ORDER DEPT. ONLY

(Callers by appointment)

J.E.T. ELECTRONICS

90a Mawney Road, Romford, Essex RM7 7DA
Telephone: Romford 61486
SPECIAL OFFERS ARE AVAILABLE ONLY WHILE STOCK LASTS

INTER-LOCKING PLASTIC STORAGE DRAWERS

**MEET
KAWNOY!
TWO!**



**DISCOUNT
PRICES**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins), £2 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins), £3-50 DOZEN.

TREBLE (3D) £3-50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D), £4-90 for 8.

EXTRA LARGE SIZE (6D1) £4-50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £
Orders £30 and over DEDUCT 7½% in the £
PACKING/POSTAGE/CARRIAGE: Add 40p to all orders under £10. Orders £10 and over, packing/postage/carrriage free.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

FLADLINE (Dept. PE4), 124 Cricklewood Roadway, London, N.W.2
Tel. 01-450 4844

OSMABET LTD

We make transformers amongst other things

AUTO TRANSFORMERS 110-200/220/240V
30W. £2-18; 50W. £2-78; 75W. £3-48; 100W. £4-50; 500W. £12-750W. £16-50; 1000W. £28-28, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V e.c. 8-3V 1-5A. £1-48; 3A. £1-80; 6A. £3-80; 12V 1-5A. £1-80; 3A. £2-30; 6A CT. £4-80; 18V 1-5A CT. £3-30; 24V 1-5A CT. £3-30; 3A CT. £4-80; 6A. £8-78; 8A. £8-78; 12A. £12-40; 40V 3A CT. £8-50V 6A CT. £16-78; 25V 2A + 25V 2A. £8-48; 12V 4A + 12V 4A. £8-48.

LT TRANSFORMERS TAPPED SEC. Prim 200/240V
0-10-12-14-16-18V 2A. £3-30; 4A. £4-80.
0-12-15-20-24-30V 2A. £4-20; 4A. £6.
0-2-20-30-40-60V 1A. £4-28; 2A. £8.
0-40-50-80-90-100-110V 1A. £8-40.

MIDGET RECTIFIER TRANSFORMERS
For FW rect. 200/240V e.c. 8-0-8V 1-5A or 0-0-8V 1A £1-88 each; 12-0-12V 1A or 20-0-20V 0.75A or 0-0-8V 0.3A or 12-0-12V 0.25A or 20-0-20V 0.15A or 8V 0-5A + 8V 0-5A or 9V 0.35A + 8V 0.35A or 12V 0.25A + 12V 0.25A or 20V 0.15A + 20V 1-5A, all at £1-98 each.

MAINS TRANSFORMERS
Prim. 200/240V e.c. TX8 sec. 425-0-425V 500 MA. 6-3V CT 6A. 6-3V CT 6A. 6-3-6-3V 3A £16-78; TX1 425-0-425V 250 MA. 6-3V CT 4A. 6-3V CT 4A. 0-5-6-3V 3A. £11-28; MT9 Prim. 0-110-240V. sec.. 250V 100 MA. 6-3V 2A. £78; £3-78.

OP TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec., tapped 0-4-15 ohms. A-A 8-8k 30W £8-78; A-A 3k 50W £10-18; 100W (E.L.3A KT88, etc.). £17-28; MRT/10, tapped multi OP 10W £4.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 35p.

LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W. £7-80; 35W £8-40; Hi-Fi Major Module 20W w/tweeter crossover, £11-00. Baker Speaker Lite. FANE 60W £13-80; EM1 12 x 8in. 8Ω. £2; 5in 8Ω. £1-18; 7 x 4in 15Ω. £1-88; 8 x 5in 3. 8. 15 or 8Ω. £1-78 each.

LOUDSPEAKERS
2½in 8 or 7.5Ω. 2½in 8 or 25Ω. 3in 3. 8. 25 or 35Ω. 3½in 8 or 8Ω. 85p each; 5in 3. 8 or 25Ω. 5 x 3in 3 or 8Ω. £1-18; 7 x 4in 3 or 15Ω. 8½in 3Ω. £1-38; 10 x 8in 3Ω. £1-80.

SPEAKER AUTO MATCHING TRANSFORMER
12W 3 to 8 or 15Ω up or down. £1-50.

"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads. 200/240V e.c. £3-78.

SYNCHRONOUS GEARED MOTORS, 200/240V e.c.
Brand new, Smiths. Built-in gearbox. 2r.p.h. 7½p each. Carriage and VAT extra on all orders.
S.A.E. ENQUIRIES, LISTS. MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HAS 8YG
Tel. 01-958 9314

VEROBOARD



VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK


0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER,
TRADE DISTRIBUTOR N. Ross (Electrical) Ltd., London, W.C.1.




VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford
SO5 3FR Tel: Chandler's Ford 2552

SUPERSOUND 13 HI-FI MONO AMPLIFIER

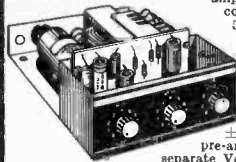

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz $\pm 3\text{db}$. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £12.50. P. & P. 30p.

DE LUXE STEREO AMPLIFIER

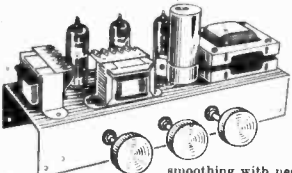

A.C. mains 200-240 v. Using 2 heavy duty fully insulated mains transformer with full wave rectification giving a d.c. smoothing with negligible hum. Valve line-up—2 x ECL86 Triode Pentodes, 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4 1/2" d. Overall height including valves 5". Ready built and tested to a high standard. £10.75. P. & P. 50p.

POWER SUPPLY UNIT 200/240V. A.C. input, four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp on lead. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/4". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. Price £5.20. P. & P. 35p.

VYNAIN & BEXINE SPEAKERS & CABINET FABRICS app. 64 in. wide. Our price £1.30 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-6 watts. Volume and tone controls. Chassis size only 7 1/2 in. wide x 3 in. deep x 6 in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 40p. BARGAIN PRICE £4.20

FEW ONLY. High grade mains transformer with grain orientated lamination. Primary 200/240. Secondary 18.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2 1/2 in. long x 2 1/2 in. wide x 2 in. deep overall. £1.35 plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-10-10-20-20-30-30-40-50v. at half wave at 1 amp, or 10-10-20-20-30-30-40v. at 2 amps full wave. Size 3 1/2 in. long x 3 1/2 in. wide x 3 in. deep. Price £2.60. P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pro. 200/240v. Sec. 9-9-9 at 500 mA. £1.25. P. & P. 25p. Pri. 200/240v. Sec. 12-12-12 at 1 amp. £1.40. P. & P. 25p. Pri. 200/240v. Sec. 10-10-10 at 2 amp. £2.00. P. & P. 35p.

3 VOLT RELAY. 100 mA single pole normally closed. 2 for 80p. P. & P. 15p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18V. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 28dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price £1.20. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVS. AND SUBS. A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.


3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristic, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents 90p. Transistor Equivalents 11p. Transistor Characteristics £1.30. POST FREE All three together £3.

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias £1. Post Free. 8 pole 3 way 2 bank low loss Varley type switches 11 1/2" sections. Standard spindle. 2 switches 64p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

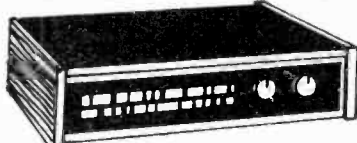HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to "lock on" station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2 in wide x 8 in deep by 2 1/2 in high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £23.00. Post and Packing 50p.

STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-18V neg. earth operation. Can be fitted to almost any FM VLF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5.40 plus 10p P. & P. Stereo beacon light if required 40p extra.



LATEST HI SENSITIVITY UNI-DIRECTIONAL SLIM-LINE CONDENSER MICROPHONE as used by many professionals. Very low acoustic feedback. Available Hi impedance or low impedance. State which required. £13.50. P. & P. 25p.

LATEST ACOS GP91/18C mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.46. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY £1.75. P. & P. 15p.

SOMOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.27. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.76. P. & P. 15p.

LATEST ROHETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/78/80. £1.60. P. & P. 15p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 in wide x 3 in deep x 6 in high. Ready built and tested. PRICE £6.50. P. & P. 50p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6.70. P. & P. 60p.

HI-FI LOUDSPEAKER SYSTEM Mk II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, E.P. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which).

OUR PRICE £9.50 each. Carr. 90p.

Cabinet Available Separately £6.00. Carr. 90p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.00. Carr. 75p.

LOUDSPEAKER BARGAINS

5 in. 3 ohm £1.25. P. & P. 15p. 7 x 4 in. 3 ohm £1.40. P. & P. 20p. 10 x 6 in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 5 in. 3 ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13 1/2 x 8 in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3.50. P. & P. 30p. E.M.I. 13 x 8 in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network £4.65. P. & P. 30p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £1.80 + 20p. P. & P.


BRAND NEW. Bakers Louzspeakers at substantial discounts. 12 in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiFiX ceramic ferrobear magnet assembly £7.50. Guitar models: 25w. £7.80. 35w. £8.50. P. & P. 45p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER Size 1 1/2" x 1 1/4" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for details. Only £6.60 each. P. & P. 34p.

NOW ALSO AVAILABLE. 8 in. 10W rms 20W peak 40Hz-20,000Hz. Overall depth 1 in. Ideal for Hi-Fi or for use in cars. £4.32. P. & P. 25p.

SPECIAL BARGAIN OFFER! Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £8.00 + p. & p. 60p.

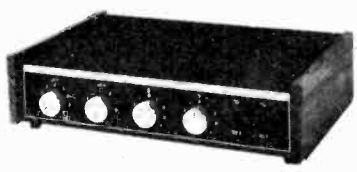
HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response $\pm 3\text{dB}$ 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: $\pm 3\text{dB}$ 12-15,000 Hz. Bass, boost approx. to $\pm 12\text{dB}$. Treble cut approx. to -16dB . Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall size 12 1/2" x 8 1/2" x 2 1/2".

Full detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. **AMPLIFIER KIT £12.96 P. & P. 30p** (Magnetic input components 33p extra) **POWER PACK KIT £4.32 P. & P. 40p** **CABINET £2.00 P. & P. 15p**

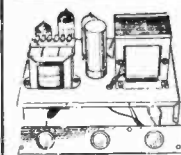(Post Free if all units purchased at same time) Full after sales service. Also available ready built and tested £28.08. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HK4 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2". Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm

speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £6.50. P. & P. 45p. **HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to Hk44 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5.50. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 15p x SAE (Free with parts). All parts sold separately. ONLY £10.25. P. & P. 60p. Also available ready built and tested £14.00. P. & P. 70p.

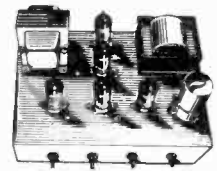

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexiform ear-cups. Wired and fitted with standard stereo 3/16 inch jack plugs. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.50. P. & P. 25p.

PRICES INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

ERSIN

Multicore

5 CORE SOLDER



for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7 1/2 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy, 63ft of 18 s.w.g. (19.2 metres of 1.22mm)



Size 12 £1.72

ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.



Size 4 £2.32

Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.



Size 10 £1.44

For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.




Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER

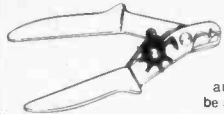

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B. 80p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,
Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP

Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 15p P&P. Prices and specifications subject to change without notice.

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

This 76 page FREE book shows how!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76-page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!


Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Practical Radio and Electronics (Technatron)	<input type="checkbox"/> Radio Amateurs	<input type="checkbox"/> Practical TV	<input type="checkbox"/> Colour Television	<input type="checkbox"/> Computer Electronics	<input type="checkbox"/> C. & G. LI Radio TV Servicing cert.	<input type="checkbox"/> Post Master General 1st & 2nd class certs.	<input type="checkbox"/> C. & G. Electrical Engineering Practice	<input type="checkbox"/> C. & G. LI Installations and Wiring	<input type="checkbox"/> General Electrical Engineering	<input type="checkbox"/> Society of Engineers (Electrical Engineering)	<input type="checkbox"/> Electrical Installations and Wiring	<input type="checkbox"/> C. & G. Electrical Technicians (Primary)	<input type="checkbox"/> C. & G. Telecommunications
---	---	---------------------------------------	--	---	--	---	--	--	---	--	--	---	---

To ALDERMASTON COLLEGE
Dept. EPE04, Reading RG7 4PF

NAME (Block Capitals Please) _____
ADDRESS _____
POSTCODE _____ Age _____
Other subjects Accredited by C.A.C.C. Member of A.B.C.C.

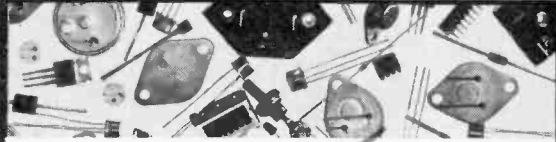BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



LINEAR 1/C'S		DIODES		ZENER DIODES	
709C	£ 0.24	IN4001	p 4	BZ788	400mW
710C	0.24	IN4002	4	Voltages 3v-30v	
741C (BP in Minidip)	0.20	IN4003	5	6p	
CA3046	0.50	IN4004	5		
LM309K	1.25	IN4005	6		
		IN4006	6		
COS/MOS		IN914	2	AUDIO 1/C'S	
CD4001	0.24	OA47	4	TAA661B	£ 1.0
CD4009	0.40	OA200	6	CA3089E	1.5
CD4011	0.20	IN4148	1.5	CA3090Q	3.0
CD4012	0.20			CA3028	1.0
CD4018	1.50			CA3048	2.0
CD4029	1.50				
TRANSISTORS					
BC107	£ 0.07	BFY50	£ 0.14	ZN696	£ 0.15
BC108	0.07	BFY51	0.12	ZN697	0.20
BC109	0.07	BFY52	0.15	ZN706	0.10
BCY70	0.09	BFY90	0.60	ZN930	0.18
BCY71	0.09	BSY95A	0.10	ZN1302	0.16
BCY72	0.09	C426	0.28	ZN1303	0.12
BFX29	0.16	40360	0.40	ZN1304	0.20
BFX84	0.16	40381	0.40	ZN1305	0.20
BFX85	0.16	40382	0.40	ZN2160	0.50
BFX86	0.16	40669	0.80	ZN2646	0.40
BFX87	0.16	40673	0.50	ZN3053	0.15
BFX88	0.16	40602	0.40	ZN3054	0.40
BC237	0.08			ZN3055	0.40

TERMS: CWO—ADD 8% VAT—10p POST & PACKING


ROWNSGEM LTD.
Rosebank Parade, Plough Road, Yateley, Camberley, Surrey.
Phone No. 0252 871717

THE PROFESSIONAL ORGANISATION FOR THE 'HOBBYIST'

R T V C FOR AUDIO AT A BUDGET

COMPLETE STEREO SYSTEM System 1a. £62.00

*

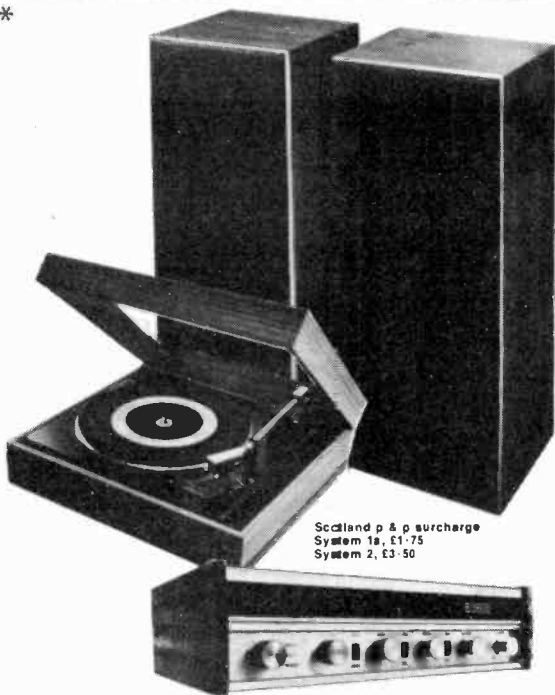

Scotland p & p surcharge
System 1a, £1.75
System 2, £3.50

System 1a. £62.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.

System I includes:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0.1% P.U.I. (for ceramic cartridges) 150mV into 3 Meg. P.U.I.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within -1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics:* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 1/2" x 9" x 3 1/2".

Garrard SP 25 deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type III matched speakers - Enclosure size approx. 19 1/2" x 9 1/2" x 7 1/2" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling.

Complete System £62.00 + £5.50 p & p.

System 2. £82.00

Viscount III amplifier (As system 1a).

Garrard SP 25 deck (As system 1a).

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2".

Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters.

20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £82.00 + £6.50 p & p.

PRICES: SYSTEM 1a

Viscount III R102 amplifier	£27.00 + £1 p & p
2 Duo Type III speakers	£26.00 + £5.50 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and cover	£21.00 + £1.75 p & p
total:	£74.00

Available complete for only: **£62.00**
+ £5.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier	£27.00 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and cover	£21.00 + £1.75 p & p
total:	£87.00

Available complete for only: **£82.00**
+ £6.50 p & p



STEREO 21* QUALITY SOUND FOR LESS THAN £20.00

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes: - BSR 3 speed deck, automatic, manual facilities together with stereo cartridge. Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.


Specifications: For the technically minded: -

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel.

Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only **£19.95** + **£2.60 p & p**. Extras if required. Optional Diamond Styli **£1.37**.

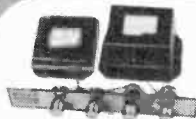Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£5.00**.



BUILD YOUR OWN * STEREO AMPLIFIER

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only. **£7.64 + 90p. p & p.**

Also available with 2 speakers (7" x 4") **£9 + £1.50 p & p.**

8 TRACK HOME CARTRIDGE PLAYER *



Elegant self selector push button player for use with your stereo system.

Compatible with Viscount III system, Unisound module and the Stereo 21.


Technical specification Mains input, 240V, Output sensitivity 125mV

Comparable unit sold elsewhere at

£24.00 approx. Yours for only

£12.95 + £1.45 p & p.

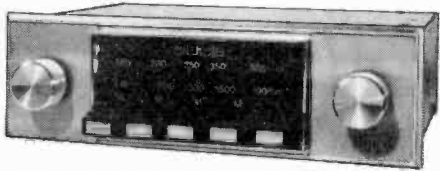PUSH BUTTON CAR RADIO KIT* - The Tourist TT



NO SOLDERING REQUIRED!

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) Output 4 watts R.M.S. output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4½" deep approx £8.00 + 90p. p & p.

Speaker including baffle and fixing strip £1.65 + 37p. p & p.

Car Aerial Recommended—fully retractable £1.37 + 32p. p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model.

Same technical specification as Tourist TT

Price £7.00 + 90p. p & p.

EMI SPEAKERS AT FANTASTIC REDUCTIONS

EASY BUILD SPEAKER KITS



These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3" tweeter and matching crossover. Easily put together with just a few basic tools. Specification (each speaker) Impedance 8 ohms. Power handling 15 watts r.m.s., (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£18.95 pair + £4.50 p & p.

20 WATT SPEAKER SYSTEM*

System consists of a 13" x 8" (approx) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components. Circuit diagram.

Technical Specification:

Bass Unit
Flux density—100 K, speech coil—1½"
Cone. Triple laminated paper with P.V.C. surround.
Mid Range Unit
Flux density—33K, speech coil—1" with parasitic tweeter.
Power Handling
20 watts R.M.S., impedance—8 ohms, frequency response—20 Hz to 18,000 Hz.

OUR PRICE
£7.50. Complete
+ £1.35 p & p.



DISCO AMPLIFIER*

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls.


*Separate bass and treble controls common to all 4 inputs.

*Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES -Input -1.) Crystal mic, guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).

-Inputs -2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12½" x 6" x 3½". **£17.00 + £1.15 p & p.**

PORTABLE DISCO CONSOLE*

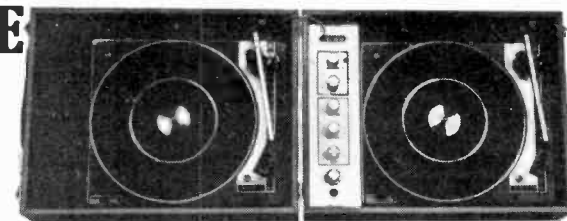

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

TECHNICAL SPECIFICATION:

Pre-amp - Output - 200mV.

Auxiliary inputs - 200mV and 750mV into 1 meg.

Mic input - 6mV into 100K. 240 volt operation.

Turntables capacity - 7", 10" or 12" records.

Rumble, wow and flutter

Rumble Better than -35dB. Wow Better than 0.2%.

Flutter Better than 0.06% (Gauont kallee meter).

Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size -

Unit Closed - 17½" x 13½" x 8½" (approx.)

Unit Open - 35½" x 13½" x 4½" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £49.00 + £5.60 p & p.



DO NOT SEND CARD


Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Feb. 1975 and subject to change without notice. All prices include V.A.T. at 8% rate.

Personal Shoppers Edgware Road: 9a.m.-5.30p.m. Half day Thurs. Acton: 9.30a.m.-5p.m. Closed all day Wed.



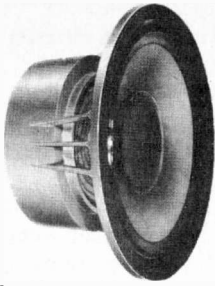21d High Street, Acton, London W3 6NG
323 Edgware Road, London W2



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7-75
Baker Group 35 3, 8 or 15 ohm	£8-50
Baker Group 50 12 8 or 15 ohm	£12-50
Baker Deluxe 12in d/cone	£10-75
Baker Major 12in d/cone	£8-50
Baker Regent	£7-75
Baker Superb	£14-50
Baker Auditorium 12	£12-50
Celestion MH1000, 8 or 15 ohm	£10-85
Celestion PS8 for Unilux	£3-25
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00
Coral 6 1/2in d/cone roll surr, 8 ohm	£2-50
Coral 8in d/cone roll surr, 8 ohm	£3-25
EMI 13in x 8in 3, 8 or 15 ohm	£2-25
EMI 13in x 8in 150 d/c 8 ohm	£2-50
EMI 13in x 8in 450 t/w, 3, 8 or 15 ohm	£3-75
EMI 13in x 8in type 350 8 or 15 ohm	£8-25
EMI 13in x 8in 20W bass	£8-00
EMI 6 1/2in 9350 4 or 8 ohm	£3-00
EMI 5in 14A/7030 mid range 8 ohm	£2-50
EMI 8 x 5 d/cone, roll surr, 10W	£2-50
EMI 2 1/2in tweeter 97492AT	£0-85
Eagle DT33 30W tweeter	£5-45
Eagle HT15 horn tweeter	£3-80
Eagle CT5 cone tweeter	£1-75
Eagle CT10 tweeter 8 or 16 ohm	£2-85
Eagle MHT10 horn tweeter	£3-80
Eagle crossover CN23, CN28, CN216	£1-50
Eagle FR4	£5-30
Eagle FR65	£8-35
Eagle FR8	£10-65
Elac 9 x 5 59RM109 15 ohm, 59RM114 8 ohm	£2-00
Elac 6 1/2in 6RM171 d/c roll surr.	£3-50
Elac 6 1/2in 6RM220 d/cone	£2-85
Elac 4in tweeter TW4	£1-50
Elac 10in d/cone 10RM239 8 ohm	£2-85
Elac 8in 8CS175 3 ohm	£2-50
Fane Pop 15W 12in	£5-25
Fane Pop 25T 30W 12in	£7-25
Fane Pop 50W 12in	£12-00
Fane Pop 55 60W 12in	£12-50
Fane Pop 60W 15in	£13-25
Fane Pop 100W 18in	£24-50
Fane Crescendo 12A 100W 12in	£29-00
Fane Crescendo 12B bass	£28-00
Fane Crescendo 15in 100W	£36-00
Fane Crescendo 18in 150W	£31-85
Fane 801T 8in d/c roll surr.	£7-00
Fane 807T 8in d/c roll surr.	£3-85
Fane 808T 8in d/c	£2-75
Fane 701 twin ribbon horn	£35-00
Fane 910 horn	£12-75
Fane 920 horn	£33-00
Goodmans 8P or 15 ohm	£5-00

Goodmans 10P 8 or 15 ohm	£5-30
Goodmans 12P 8 or 15 ohm	£12-85
Goodmans 12P-D 8 or 15 ohm	£16-75
Goodmans 12P-G 8 or 15 ohm	£15-75
Goodmans Audiomax 12AX 100W	£38-50
Goodmans Audiomax 15AX	£40-25
Goodmans 13P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£38-00
Goodmans Hifax 750	£16-00
Goodmans Axent 100 tweeter	£7-25
Goodmans Audiom 100 12in	£7-25
Goodmans Axiom 402 12in	£17-25
Goodmans Twinaxiom 8	£8-25
Goodmans Twinaxiom 10	£9-00
Kef 127	£5-25
Kef T15	£8-00
Kef B110	£7-25
Kef B200	£8-25
Kef B139	£14-25
Kef DNE	£2-00
Kef DN12	£4-85
Kef DN13	£3-30
STC4001G super tweeter	£5-70
Richard Allan CG8T d/c r/surr.	£8-35
2 1/2in 64 ohm, 70mm 80 ohm, 70mm 8 ohm	£0-85
2 1/2in 75 ohm	£0-50
7in x 4in 3 or 8 ohm	£1-48
8in x 5in 3 or 8 ohm	£1-50
10in x 6in 3, 8 or 15 ohm	£2-30

SPEAKER KITS

Baker Major Module	each	£10-75
Decca London Ribbon Horn		£28-00
Decca London Crossover		£8-50
Goodmans Mezzo Twinkit	pair	£38-50
Helme XLK25	pair	£22-00
Helme XLK30	pair	£14-95
Helme XLK50	pair	£30-95
Jordan Watts Module		£14-75
Kefkit 1	each	£20-95
Kefkit 3	each	£38-75
Pearless Dome tweeter		£8-95
Radford BD25		£14-75
Radford MD9		£8-95
Radford HD3		£8-75
Radford FN12		£8-95
Richard Allan Twinkit	each	£8-85
Richard Allan Triple 8	each	£13-75
Richard Allan Triple	each	£19-95
Richard Allan Super Triple	each	£23-75
Super 8 RS/DD		£8-95
Wharfedale Linton 2 kit	pair	£19-25
Wharfedale Glendale 3 kit	pair	£34-50
Wharfedale Doveclade 3 kit	pair	£52-50

Baker, Linear and Eagle PA disco amplifiers in stock. Send stamp for list.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing; speakers 38p each, speaker kits 75p each (£1-50 pair), tweeters and crossovers 20p. Send stamp for free booklet "Choosing a Speaker" ALL PRICES QUOTED INCLUDE VAT

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.



Cassettes

The best buy!

AGFA LOW NOISE CASSETTES AT LESS THAN HALF PRICE!	C60	1	37p	5	£1-80	10	£3-30
	C90	1	50p	5	£2-48	10	£4-95
	C120	1	63p	5	£3-10	10	£8-20
AGFA HIGH DYNAMIC SUPER	C60 + 5	1	50p	5	£2-40	10	£4-70
	C90 + 6	1	68p	5	£3-35	10	£6-60
	C120	1	99p	5	£4-90	10	£9-80
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C60	1	85p	5	£4-20	10	£8-30
	C90	1	£1-08	5	£3-38	10	£10-60

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO (DEPT. PE)

10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

INTERNATIONAL TRANSISTOR SELECTOR

Over 10,000 USA, EURO., JAP., BRITISH TRANSISTORS, ELECTRICAL, MECHANICAL SPECIFICATIONS, MANUFACTURERS AND AVAILABLE SUBSTITUTES by T. D. Towers, M.B.E. Price £3-15

1975 EDITION THE RADIO AMATEUR'S HANDBOOK

by A.R.R.L. Price £3-50

VIDEOTAPE RECORDING THEORY AND PRACTICE

by J. F. Robinson Price £4-80

RADIO CONTROL FOR MODELS

by R. H. Warring Price £5-80

DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS

by N. M. Morris Price £2-50

RADIO SERVICING POCKET BOOK

by V. Capel Price £2-15

★ PRICE INCLUDES POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185 Closed Saturday 1 p.m.

4-STATION INTERCOM



£16-15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft and other accessories. P. & P. 60p.

MAINS INTERCOM (new model) No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £28-75 per pair. P. & P. 60p extra.

INTERCOM/BABY ALARM



£6-50

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft connecting wire. Complete with battery. P. & P. 40p.

Transistor TELEPHONE AMPLIFIER




£6-45

Why not boost business efficiency with this incredible Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 30p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/4) 169 KENSINGTON HIGH STREET, LONDON, W.8

LOGIC LEISURE LTD

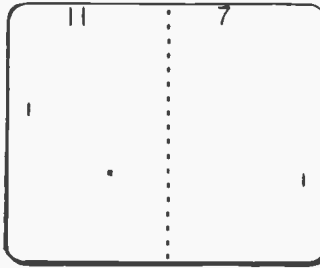KINGFISHER HOUSE
68 PARK ROAD
NEW BARNET, HERTS.
Tel. 01-440 9173/4



X-Y BAT CONTROL MODULE

ENABLING BATS TO
MOVE ALL OVER THE
SCREEN
PRICE: £6

JOY STICK CONTROLS
£12 PER PAIR

MODULATOR UHF OUTPUT

PRICE: £5.50

BUILT AND TESTED
CONVERTS ANY TV
INTO MONITOR FOR
CAMERAS OR TV
GAMES

COMPLETE TV TENNIS KIT

AS SEEN IN THE
AMUSEMENT
ARCADES

BUILD IT YOURSELF
FOR £68.50

PRINTED CIRCUIT BOARD

THIS IS FOR THE REAL
TV TENNIS GAME

OUR SPECIAL PRICE
£14.50 WITH FULL
INSTRUCTIONS

If you have any queries you are welcome to telephone us at
01-440 9173/4 or telex 264397 BROADTEC BARNET.
Callers are welcome at the above address for demonstration of
Teletennis.
Trade enquiries invited.

WE WELCOME YOUR
ORDERS WITH CARE

TTL I.C.s 7400 14p 7441 70p 7480 85p 7401 15p 7442 85p 7481 41p 7402 15p 7448 90p 7489 340p 7403 18p 7450 22p 7491 82p 7404 18p 7452 22p 7492 52p 7408 16p 7480 22p 7493 45p 7410 15p 7470 30p 74107 37p 7413 32p 7472 27p 74121 34p 7414 72p 7473 34p 74122 78p 7416 35p 7474 34p 74123 110p 7420 15p 7475 45p 74141 75p				5314 Clock Chip 24 pin DIL 650p. Alarm Clock Chip 40 pin DIL (similar MM5316) 750p. 5001 12 Digit Calculator Chip 28 pin DIL 485p. (All above supplied with full data; data separately 25p each + S.A.E.) PC Keyboard (0-9, decimal, 4 function, C, K, keys). Size: 2.36" x 3.76" x 0.45" 400p.				Popular Op Amps 709 OPA with ext. comp. 28p 710 Diff. comparator 35p 741 OPA with int. comp. (8 pin DIL) 25p 747 Dual 741 70p 748 OPA with ext. comp. 38p LINEAR I.C.s CA3046 Transistor Array 50p CA3048 4 Independent Amplifiers 230p LM301A Op. Amp. with ext. comp. 38p LM380 Audio Amplifier 80p LM381 Stereo Pre Amp. 150p LM3900 Quad Op. Amp. 70p MC1310 Coiles FM Stereo Dec. 225p MC1312 SQ Quadraphonic Dec. 220p MC1314 SQ Quadraphonic Dec. 360p MC1315 SQ Quadraphonic Dec. 430p MFC4000 iW Audio Amp. 50p				MFC6040 Electronic Attenuator 80p MFC8070 Zero Voltage Switch 250p NE536 FET Op. Amp. 192p NE555 Timer 8 pin DIL 50p NE556 Dual 555 14 Pin DIL 100p NE560 PLL 16 Pin DIL 325p NE561 PLL with AM Demod. 18 Pin 290p NE562 PLL with VCO 16 Pin 290p NE565 PLL 14 Pin DIL 290p NE566 Function Generator 8 Pin DIL 200p NE567 PLL Tone Decoder 8 Pin DIL 250p TBA570 AM/FM Radio receiver 160p TBA800 5 Watt Audio Amp. 100p TBA810 7 Watt Audio Amp. 125p TBA820 2 Watt Audio Amp. 90p ZN414 TRF Radio Receiver 110p ICL8038 Voltage Controlled Osc. 14 Pin DIL 285p Data sheets on above I.C.s 10p each.											
ACCESSORIES DIL SOCKETS (L.P.) 8 pin 12p, 14 pin 13p, 16 pin 14p. Mica + bushes for TO3 and TO66 6p.				BRIDGE RECTIFIERS 50V 100V 400V 600V 250mA 18p — — — 1 Amp 20p 24p 27p 28p 2 Amp 30p 35p 45p 48p 4 Amp — — — — 6 Amp 55p 60p 78p —				SCR—THYRISTORS 50V 100V 400V 600V 1 Amp 40p 45p 55p 72p 3 Amp 43p 48p 75p 100p 7 Amp — 80p 84p — 16 Amp — 82p 88p — Other C106D 45p, 2N3525 91p, 2N4444 185p				TRIACS 100V 400V 500V 600V 3 Amp 85p 95p 120p 6 Amp 88p 120p 150p 10 Amp 109p 154p 185p 16 Amp 145p 200p Other 40430 90p, 40466 85p, 40669 95p. DIAC for use with above triacs 21p.				VOLTAGE REGULATORS 723 7805 5V 140p .14 pin DIL 50p 7812 12V 140p 7815 15V 140p MFC4060 70p 7818 18V 140p 7824 24V 140p							
AC126/7 11p BC212 11p OC35 48p 2N1308/9 28p 2N4060 13p AC128 11p BC213 10p OC36 52p 2N1813 20p 40361 40p AC176 11p BC214 13p OC41/2 15p 2N1711 0p 40362 43p AC187 12p BD115 55p OC44/5 11p 2N2219 20p T1543 25p AC188 11p BD124 75p OC70/1/2 11p 2N2219 20p UJT8 25p AD149 43p BD131 42p OC73 80p 2N2369 14p 2N2160 70p AD161 36p BD132 45p OC81/2 12p 2N2484 30p 2N2646 35p AD162 36p BF115 22p OC83.4 28p 2N2904 20p 2N4871 31p AF114/5 13p BF167 23p TIP2955 75p 2N2905 18p FETS AF167/7 13p BF173 25p TIP41A 85p 2N2926RB 9p BF244 38p AF139 41p BF184 22p TIP42A 75p 2N2926D 8p 2N3820 57p AF239 44p BF194 11p ZTX300 12p 2N2926YG 9p MPF102/3 31p BC107/8 9p BF195 12p ZTX304 24p 2N3053 18p MPF104/5 31p BC109 7p BF196 14p ZTX500 15p 2N3054 45p 2N3819 20p BC147/8 10p BFR39/40 28p ZTX504 50p 2N3055 49p 2N3820 57p BC149 9p BFR41 28p 2N696 15p 2N3442 140p 2N3823 60p BC179 13p BFR42 30p 2N697 13p 2N3702/2 11p 2N5457 31p BC158 12p BFR50/1/2 15p 2N698 30p 2N3704/5 11p 2N5458 31p BC159 14p BFR39 34p 2N706 12p 2N3706/7 11p 2N5459 31p BC189C 12p MJE340 45p 2N708 18p 2N3708/9 9p MOSFETS BC177 18p MJE2955 95p 2N930 18p 2N3772 181p 40603 58p BC178 17p MJE3055 85p 2N1131/2 18p 2N3773 220p 40673 58p BC179 18p MFSU06 58p 2N1302/3 17p 2N3903/4 15p 3N128 75p BC182/3 10p OC28 47p 2N1304/5 21p 2N3905/6 15p 3N140 85p BC184 11p OC28 55p 2N1306/7 28p 2N4058 15p 3N141 75p				C-MOS I.C.s CD4001AE 37p CD4011AE 37p CD4012AE 37p CD4013AE 67p CD4016AE 37p CD4017AE 183p CD4023AE 148p CD4024AE 148p CD4025AE 37p CD4027AE 108p CD4030AE 82p CD4046AE 225p CD4047AE 154p				OPTO-ELECTRONICS LDR ORP12 50p, ORP60 60p; Trans OCP71 85p, 2N5777 40p. Leds TIL209 (Red) 18p, Green/ Yellow 35p. Seven Segment Displays Filament 3015F 0-354in DIL 120p All LED MAN-3M 0-127in PCB 100p MAN-4 0-19in DIL 180p Reflective Bar LED LIT 704 0-33in DIL 100p LIT 707 0-33in DIL 100p LIT 747 0-63in DIL 210p 3 Digit Readouts Blisdr Lens 0-127in DIL 250p Red Lens Filter 0-127in DIL 185p				RECTIFIER DIODES 500mA BY100 15p 1 Amp BY126 12p BY127 12p 1N4001 5p 1N4004 6p 1N4007 7p 1-5 Amp PL4004 10p 3 Amp PL7004 20p 6 Amp BYZ10 50p BYZ11 50p BYZ12 50p BYZ13 50p				SIGNAL DIODES BA100 10p OA47 7p OA70 8p OA79 7p OA85 9p OA90 6p OA91 6p OA95 7p OA200 6p OA202 7p 1N914 4p 1N916 6p 1N4148 4p				ZENER DIODES 3-3V to 33V 400MW 9p 1.3W 18p 1.5W 27p 10W 55p Other Diodes TUNNEL AEY11 50p VARICAP BB103 25p BB104 45p BB105 45p			
Minimum order £2. All prices exclusive of VAT. P. & P. 15p.				All goods brand new MAIL ORDER ONLY				TECHNOMATIC LTD. 54 Sandhurst Road, London NW9. Tel. 01-204 4333															

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL
Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and £7.50 P. & P.
Control Switch.



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box approx. 4" x 3" x 2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier.
A Bargain at £7.50 plus 10p.

MINIATURE RELAYS
Brand new range of British made relays, size: 1 1/2" x 1 1/2" x 3/4". All two changeovers with 250V 1.5A contacts and suitable for fitting on 0.1m veroboard.
Type Volts Current Ohms
27/A 12V 17mA 700 All
21/A 12V 283mA 420 £1.30
12/A 6V 33mA 185 each
200/250V Mains Relay
Heavy duty contacts 2,500 ohm coil. All new and unused D.P.D.T. mains relays 50p. Carr. free. Special quantity £40 per 100 off.

MIDGET MAINS TRANSFORMER
Varnish Impregnated
Size 45mm x 36mm x 31mm
PRI 240V
Sec 3.0-3 100mA
Sec 6.0-6 100mA
Sec 9.0-9 100mA
Sec 12.0-12 100mA
Sec 20.0-20 100mA
£1.28 10p P. & P.

CRESCENT BUBBLE LIGHT SHOW
This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—150W convection cooled. At 30ft the projected image is 16ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, £15; Wheel, £5; Total £20. Plus 75p carr.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"
* Completely portable.
* Solders up to 150 joints per charge.
* Recharges in its own stand.
* Fine tip for all types of soldering.
* Only 8in long and weighs just 6 ozs.
OUR PRICE £9.75
(Spare bits are available)

U.K. CARRIAGE 15p UNLESS OTHERWISE STATED

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ THE PRE-AMP MODULE
Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using P.E.T. first stage.

★ THE POWER SUPPLY
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. £25. carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

12 0-12V 500M/A
240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price £1.20.

18V 500M/A
240V primary. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our Price £1 each

LOW NOISE, LOW PRICE CASSETTES
Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C60 31p C90 42p C120 53p
10% discount on ten or more cassettes of one type.

ABS PLASTIC BOXES
Plianly boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm x 73mm x 40mm 51p; 1006, 150mm x 75mm x 47mm 66p; 1007, 184mm x 124mm x 60mm 96p; 1021, 106mm x 74mm x 45mm (sloping front) 50p.

BARGAIN BOARDS
Components gauge for the experimenter. Ex-Computer boards with resistors, capacitors and useful transistors—at least 4 transistors per board. Five boards £1.

2in. PANEL METERS
Size 59mm x 46mm
0.50µA—ME6 0.100mA—ME13
0.100µA—ME7 0.500mA—ME14
0.500µA—ME8 0.1A—ME15
0.1mA—ME9 0.50V—ME16
0.5mA—ME10 0.300V a.c.—ME17
0.10mA—ME11 S meter—ME18
0.50mA—ME12 V.U. meter—ME19
£3 each. 10p P. & P.

POWER PACKS
PP1 Switched 3-6-7.9V 400mA Transistor and Zener Stabilised On/Off switch and Polarity Reversal switch, in a black metal case, £5.25 each.
PP2 Switched 6-7.9V Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders, £3.25.
PP3 Car converter. From 12V Pos. or Neg. to = 6-7.9V. Easy to fit and transistor regulated, £3.80.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000V lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 38p P. & P.

MINI LOUSPEAKERS
2 1/2in 80 ohm, 50p; 2 1/4in 40 ohm, 50p. Please include 5p P. & P. on each L.S.

SEND 30p FOR A CRESCENT CATALOGUE

NEW PRACTICAL PAPERBACKS FROM FOULSHAM-TAB

TV SERVICING GUIDE-BOOK, by Art Margolis £1.55	WORKING WITH THE OSCILLOSCOPE, by A. C. W. Saunders £1.50
TAPE RECORDING FOR FUN AND PROFIT, by Walter G. Salm £1.70	WALKIE-TALKIE RADIO OPERATOR'S GUIDE, by Bob Brown and Paul Lawrence £1.70
HI-FI TROUBLES, by Herman Burstein £1.40	64 HOBBY PROJECTS FOR HOME AND CAR, by Bob Brown and Mark Olsen £1.80
BEGINNER'S GUIDE TO COMPUTER LOGIC, by Gerald F. Stapleton £1.60	PULSE AND SWITCHING CIRCUITS, by Harvey F. Swearer £1.95
FIRE AND THEFT SECURITY SYSTEMS, by Byron Wels £1.55	ELECTRONIC MUSICAL INSTRUMENTS, by Norman H. Crowhurst £1.80
HOME-CALL TV REPAIR GUIDE, by Jay Shane £1.35	MAJOR APPLIANCE REPAIR GUIDE, by Wayne Lemons and Billy L. Price £2.10
HOW TO USE TEST INSTRUMENTS IN ELECTRONIC SERVICING, by F. Shunaman £1.80	PRACTICAL TEST EQUIPMENT YOU CAN BUILD, edited by Wayne Green £1.80
POPULAR TUBE/TRANSISTOR SUBSTITUTION GUIDE £1.80	QUESTIONS AND ANSWERS ABOUT TAPE RECORDING, by Herman Burstein £2.05
ELECTRONICS SELF-TAUGHT WITH EXPERIMENTS AND PROJECTS, by James Ashe £1.85	
BASIC ELECTRONICS PROBLEMS SOLVED, by Donald A. Smith £1.60	

FOULSHAM-TAB LTD. YEOVIL ROAD, LEIGH, BERKS

VEROBOARD
Approx. 8 pieces, total 100sq.in. assorted sizes and pitches £1.15.

CAPACITORS
200 Mica, ceramic, poly. etc. £1, 15,000 £42. 15 diff. trimmers, air-spaced and compression up to 1250pF. Only £1.

8 PIN DIL 74i's FULL SPEC. OF COURSE
10+ 26p; 25+ 23p; 100+ 21p; 250+ 20p.

PC ETCHING KIT
Contains 1lb ferric chloride, 100sq.in. copper clad board, DALO etch resist pen, abrasive cleaner, etching dish and instructions £3.30.

FERRIC CHLORIDE
Anhydrous to Mill-spec in 1lb double sealed packs. 1lb 90p; 3lb £1.80; 10lb, £4.65.

COMPUTER PANELS
Large quantity always available. 3lb assorted £1.60; 71lb £2.85; 56lb £15.
12 high quality panels with IC's, trim pots, power transistors, etc. £2.65.
Pack with 50 14 pin DIL DTL IC's £1.20. Pack with 20 multi-turn trim pots plus other parts £1.10. Pack with 5 1A 200V SCR's plus 60 other parts 60p.

Price increases, which we regret, are due to higher postal, packaging and advertising costs. Prices include 8% VAT and inland postage. S.A.E. list. Computers, components and equipment always wanted for cash.

GREENWELD ELECTRONICS (PE4)
Mail order dept., retail/wholesale shop
51 SHIRLEY PARK ROAD, SOUTHAMPTON SO1 4FX. Tel. (0703) 772501
Also callers welcome at 21 Deptford Broadway, SE8. Tel. 01-692 2009, and 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.

71lb BARGAIN PARCELS
Hundreds of new components—resistors, capacitors, pots, switches plus PC boards with transistors and diodes, also loads of odds and ends. Contents always changing as new stocks arrive, £2.60.

TRANSFORMERS
All mains primary. 6-0-6V at 100mA 85p; 9-0-9 V at 100mA 90p; 12-0-12V at 100mA 95p; 24-0-24V at 500mA £2. Ex-equip: 22; 0-22V at 1A £2.10; 18V at 5A £3.40; 55V at 5A £4.50.

HEAT SINKS
6 x 5 x 3in. finned aluminium with 2 x OC29 or 2 x OC35. Only £1.20.

POWER SUPPLIES
G101: Mains transformer, 2A thermal cut-out, bridge rect. Will give 1.7V-10.5V output with 2 extra capacitors (provided). With data £1.30.
G102: stabilized supply giving 7V at 225mA (can be altered by changing zener). Not tested, probable minor fault. With circuit £1.10.
G103 ex-LEC III. Contains 55V 5A transformer, 6 x 5 x 3in. heat sink with 2 x OC35, stabilizer panel, 4 x 10,000µF 63V caps, 1 x 4,700µF 100V cap, etc. £12.50.

MICROPHONES
V996 dynamic microphone, 50k impedance, on/off switch, heavy desk stand. Very smart appearance £3.30. Crystal microphone insert 1in. dia. 35p.

555 TIMERS
1-9 60p; 10-24 50p; 25-99 46p; 100+ 43p.

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)
The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A *must* for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors) £11-49
8 channel component set (excl. thyristors) £20-32
Power supply component set £4-78
PCB for 4 frequency channels £2-50
PCB for power supply and 8 lamp drivers £1-25

P.E. SYNTHESIZER Details in List

VOICE OPERATED FADER (P.E. Dec. 73)
For automatically reducing music volume during "talk-over"—particularly useful for Disco work, or for home-movie shows.
Component set, incl. PCB £2-85

P.E. GEMINI 30W STEREO AMPLIFIER
An exceptionally high quality Stereo Amplifier system, specifications for which are shown in detail in our list, together with semiconductor requirements. While stocks last.

Main Amplifier:
Set of resistors, capacitors and presets £5-98
Stereo printed circuit board £1-28
Pre-Amplifier:
Sets of resistors, capacitors, potentiometers and switches—
Standard Tolerance Set £10-57
Superior Tolerance Set £13-04
Stereo PCB (as Published) £2-20
Regulated Power Supply:
Set of resistors, capacitors and preset £4-58
Printed circuit board 72p

HI-FI TAPE LINK (P.E. Mar./Apr. 73)
Designed for use with reasonable quality tape decks, this high performance pre-amp includes record, playback and metering circuits.

Stereo component set (excl. panel meter) £22-05
Mono component set (excl. panel meter) £13-31
Power supply component set £3-72
Stereo main PCB £2-50
Stereo sub-assembly PCB 86p

TAPE-NOISE LIMITER
Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB) £2-30
Regulated power supply (including PCB) £3-71

PROJECT Q4 (P.W. Oct. 73/Jan. 74)
Multi-system Quadraphonic Decoder.

Decoder component set £13-74
Power supply components £3-22
Printed circuit board £2-60

SEMICONDUCTOR TESTER (P.E. Oct. 73)
Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB £6-58

PHASING UNIT (P.E. Sept. 73)
A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £2-20

PHASING CONTROL UNIT (P.E. Oct. 74)
(for use with above Phasing Unit)
Component set (including PCB) £3-50

P.E. SOUND SYNTHESISER
The well-acclaimed and highly versatile Synthesiser published in P.E. Feb. 1973 to Feb. 1974.

Component sets and printed circuit boards. List shows full details including discounts.

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)
Component set £3-41
Printed circuit board £1-10

RHYTHM GENERATOR (P.E. Mar./Apr. 74)
Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures. See list for discount.

Tempo, Timing and Logic Circuit £17-25
Component set (excl. switches) £17-25
Double-sided PCB for above £2-30
Mixer, Pre-amp and Effects Circuits £2-30
Component set £12-70
Printed circuit board £2-67
Power Supply £5-65
Component set and PCB £5-65

ULTRASONIC TRANSMITTER-RECEIVER
A highly sensitive and long range "invisible beam" detection circuit with numerous applications.
(P.E. May 72)

Component set with PCBs, but excluding transducers £4-40

P.E. RONDO POWER SLAVES
PCB details in List PCB details in List.

P.E. ELECTRONIC PIANO HOME INTERCOM
Details in List. (While Stocks Last) Details in List.

SOUND BENDER (P.E. May 74)
A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency doubler.

Component set £5-86
Printed circuit board £1-44

REVERBERATION UNIT (P.W. Nov./Dec. 72)
A high-quality unit having microphone and line input pre-amps, and providing full control over reverberation level.

Component set (excl. spring unit) £6-44
Printed circuit board £1-40

P.E. MINISONIC Details in list (inc. discounts)

8W AMPLIFIER (P.W. Nov. 72)
A moderately powered amplifier of more than average performance. (While stocks last.)

Main Amplifier £4-18
Mono component set £8-36
Stereo component set £8-36
Pre-Amplifier £2-50
Mono component set £6-46
Stereo component set £3-90
Power Supply £3-90
Component set

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)
Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

Pre-Amplifier Module £3-48
Component set and PCB £3-48
Basic Output Circuits £4-96
Combined component set with PCBs, for alpha-
phone, cardiophone, frequency meter and visual
feed-back lamp driver circuits £4-96
Audio Amplifier Module £5-50
Type PC7

PHOTOPRINT PROCESS CONTROL
(P.E. Jan./Feb. 72)
For colour and B. & W. an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

Component set (excl. meter) £8-85
Printed circuit board £1-60

ENLARGER EXPOSURE METER AND THERMOMETER (P.E. Sept. 73)
Dual-purpose dark-room unit with good accuracy.

Component set with PCB, but excluding meter £4-00

WIND AND RAIN UNIT (P.E. Oct. 73)
A manually controlled unit for producing the above-named sounds.

Component set incl. PCB £2-40

PCB LAYOUT AND CIRCUIT DIAGRAMS SUPPLIED WITH ALL PCBs DESIGNED BY PHONOSONICS	LIST Send S.A.E. for free list giving fuller details of kits, PCBs, and other components.	VAT Add 8% (or current rate if different) to total order cost including P & P	OVERSEAS P & P will be charged extra. VAT does not currently apply. List gives fuller details including kit weights. Charge for list: Europe 10p, other countries 20p.	COLOUR CODE IDENTIFICATION SUPPLIED WITH MOST KITS AND AS PART OF LIST			
Semiconductors	BFY50 22p 2N3702 12p BFY51 22p 2N3703 12p BFY52 24p 2N3704 12p BSY95A 22p 2N3819 35p MJE2955 110p 2N4060 12p MJE3055 75p 2N4871 36p NKT9033 112p 2N5245 51p OC28 60p 2N5777 45p OC71 14p OC72 14p OC74 25p ORP12 60p ZTX107 12p ZTX503 15p ZTX531 23p 2N706 13p 2N914 22p 2N1304 22p 2N2219 27p 2N2805 27p 2N2807 22p 2N3054 66p	2N3702 12p 2N3703 12p 2N3704 12p 2N3819 35p 2N4060 12p 2N4871 36p 2N5245 51p 2N5777 45p Diodes 1N914 4p 1N4001 6p 1N4002 7p 1N4004 6p 1N4005 6p 1N4007 10p OA200 7p OA202 8p 1P67 12p 1S550 11p ZU (ZIL) 70p	Integrated Circuits 709 8-pin DIL 40p 709 T05 40p 723 T05 95p 741 8-pin DIL 40p 747 14-pin DIL 115p 748 T05 63p 748 8-pin DIL 63p 748 14-pin DIL 63p 7400 20p 7410 20p 7420 20p 7447 175p 7473 44p 7489 425p µ7815 TO220 250p CA3048 8p MFC6840 95p Su3402N 189p	Zeners 3.3V 400mW 12p 9V 400mW 15p 4.7V 1W 25p 5.1V 400mW 15p 5.6V 400mW 15p 6.2V 400mW 15p 9.1V 400mW 15p 11V 1W 25p 12V 400mW 15p 12V 1-3W 20p 18V 400mW 15p 18V 1W 25p 175p 20V 400mW 15p 20V 1-3W 20p 20V 1-3W 20p 27V 400mW 15p	Electrolytic Capacitors (µF/V) 0-47/63V 8p 1-0/63V 8p 1-5/63V 6p 2-2/63V 6p 6-8/40 6p 10/25 6p 10/63 6p 15/40 6p 15/63 6p 22/10 6p 22/10 6p 22/25 6p 33/6 3p 33/16 6p 33/50 6p 47/10 6p 47/25 6p 47/40 6p	Polyester (µF) 0.01 3p 0.015 3p 0.022 3p 0.033 3p 0.047 3p 0.068 3p 0.1 4p 0.15 5p 0.22 5p 0.33 7p 0.47 7p 0.68 11p 1.0 14p 2.2 24p	Tantalum (µF/V) 0.1/35 12p 0.22/35 12p 0.47/35 12p 1.0/35 12p 1.5/35 16p 2.2/35 12p 4.7/35 12p 10/16 12p 10/25 16p 15/6.3 16p 22/16 16p 47/8.3 25p 47/18V 16p 100/3 16p

PHONOSONICS, DEPT. PE34, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY DON'T FORGET VAT!

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System - with a big plus over all the other kits - the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy to follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £10.85 inc. VAT and p & p.
Ready Made Unit £13.65 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 9p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel: Sheffield (0742) 668888

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V, Sec 120/240V Centre Tapped and Screened
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P
07	20	1 8	7.0 x 6.0 x 6.0	2.80
149	60	1 12	9.9 x 7.7 x 8.6	4.37
150	100	5 8	9.9 x 8.9 x 8.6	4.89
151	200	8 0	12.1 x 9.3 x 10.2	8.13
152	250	13 12	12.1 x 11.8 x 10.2	9.83
153	350	15 0	14.0 x 10.8 x 11.8	11.88
154	500	19 8	14.0 x 13.4 x 11.8	13.65
155	750	29 0	17.2 x 14.0 x 11.8	20.51
156	1000	38 0	17.2 x 16.6 x 14.0	29.15
157	1500	46 0	21.6 x 13.4 x 18.1	33.23
158	2000	60 0	21.6 x 15.3 x 18.1	37.07

Ref. No.	VA (Watts)	Weight lb oz	Auto Taps		P & P
			Size cm.	Auto Taps	
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.67
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.90
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	4.12
66	300	6 4	9.9 x 9.6 x 8.6	"	5.82
67	500	12 8	12.1 x 11.2 x 10.2	"	8.82
84	1000	19 8	14.0 x 13.4 x 14.3	"	13.68
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.31
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.20
73	3000	40 0	21.6 x 13.4 x 18.1	"	35.09

CASED AUTO TRANSFORMERS
115V mains lead input and U.S.A. 2-pin outlets, 20VA £3.13, P & P 38p.
500VA £10.45, P & P 80p. 1000VA £17.51, via B.R.S.

LOW VOLTAGE SERIES (ISOLATED)
PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	P & P
111	0.5	0.25	8	4.8 x 2.9 x 3.5 0-12V at 0-25A x 2	1.47
213	1.0	0.5	1 4	6.1 x 5.8 x 4.8 0-12V at 0-5A x 2	1.74
71	2	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.29
18	4	2 12	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.86
70	6	3 8	8.9 x 8.0 x 7.7	0-12V at 3A x 2	4.12
108	8	4 5	8	9.9 x 8.9 x 8.6 0-12V at 4A x 2	4.56
72	10	5 6	4	9.9 x 9.6 x 8.6 0-12V at 5A x 2	5.14
116	12	6 12	9.9 x 10.2 x 8.6	0-12V at 5A x 2	5.52
17	16	8 12	12.1 x 9.9 x 10.2	0-12V at 8A x 2	7.28
115	20	10 11	8	14.0 x 11.8 x 11.8 0-12V at 10A x 2	10.39
187	30	15 15	8	14.0 x 12.1 x 11.8 0-12V at 15A x 2	13.59
226	60	30 32	0	17.2 x 15.3 x 14.0 0-12V at 30A x 2	16.83

30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.81
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.40
3	2.0	3 4	8.9 x 7.7 x 7.7	"	3.49
20	3.0	4 8	9.9 x 8.3 x 8.6	"	4.53
21	4.0	6 4	9.9 x 9.6 x 8.6	"	5.13
51	5.0	6 12	12.1 x 8.6 x 10.2	"	6.41
117	6.0	8 0	12.1 x 9.3 x 10.2	"	7.15
88	8.0	12 0	12.1 x 11.8 x 10.2	"	9.90
89	10.0	13 12	14.0 x 10.2 x 11.8	"	9.87

50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.58
103	1.0	2 12	8.3 x 7.4 x 7.0	"	3.38
104	2.0	5 8	7.9 x 8.9 x 8.6	"	4.68
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.81
106	4.0	10 0	12.1 x 10.5 x 10.2	"	7.60
107	6.0	12 0	14.0 x 10.2 x 11.8	"	12.10
118	8.0	18 0	14.0 x 12.7 x 11.8	"	12.98
119	10.0	25 0	17.2 x 12.7 x 14.0	"	16.99

60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60V	2.33
126	1.0	3 4	8.9 x 7.7 x 7.7	"	3.41
127	2.0	6 4	9.9 x 9.6 x 8.6	"	5.08
125	3.0	8 12	12.1 x 9.9 x 10.2	"	7.52
123	4.0	13 12	12.1 x 11.8 x 10.2	"	8.75
40	5.0	12.00	14.0 x 10.2 x 11.8	"	9.75
120	6.0	15 8	14.0 x 12.1 x 11.8	"	11.30
121	8.0	25 00	14.0 x 14.7 x 11.8	"	15.00
122	10.0	25 0	17.2 x 12.7 x 14.0	"	17.52
189	12.0	29 00	17.2 x 14.0 x 14.0	"	19.98

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P
238	200	2 00	2.8 x 2.6 x 2.0	3-0-3	1.54
212	1A, 1A	1 4	6.1 x 5.8 x 4.8	0-6, 0-6	1.84
13	100	4	3.9 x 2.6 x 2.9	9-0-9	1.41
235	330, 330	4	4.8 x 2.9 x 3.5	0-9, 0-9	1.56
207	500, 500	1 00	6.1 x 5.4 x 4.8	0-8-9, 0-8-9	1.92
208	1A, 1A	1 12	7.0 x 6.4 x 6.1	0-8-9, 0-8-9	3.30
236	200, 200	4	4.8 x 2.9 x 3.5	0-15, 0-15	1.43
214	300, 300	1 4	6.1 x 5.8 x 4.8	0-20, 0-20	1.93
221	700 (d.c.)	1 8	7.0 x 6.1 x 6.1	20-12-0-12-20	2.17
206	1A, 1A	2 12	8.3 x 7.7 x 7.0	0-15-20, 0-15-20	3.46
203	500, 500	2 4	8.3 x 7.0 x 7.0	0-15-27, 0-15-27	3.00
204	1A, 1A	3 4	8.9 x 7.7 x 7.7	0-15-27, 0-15-27	3.85


PLEASE ADD 8% FOR V.A.T. INCLUDING P & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

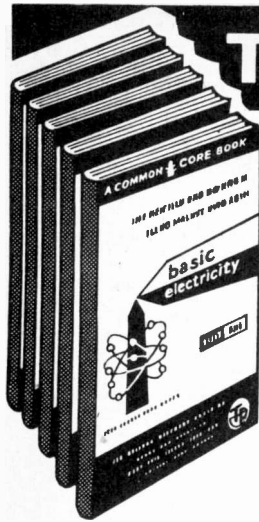NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

- I have made great use of the Basic Manuals.
B.C., Hendon
- I have found the Electronics volumes so interesting: please rush me Electricity.
C.A., Folkestone
- I would like to say I am completely satisfied with the wonderful manuals.
A.L.P., Buckingham
- I find these books are exactly what I have been looking for: they explain everything in perfect detail.
H.W.R., Pontefract
- These books make all other publications out of date with their simplicity and interest.
J.W.R., Newbury
- You can add my blessings to your already long list of praises about your Basic publications.
P.J.J., Rustington

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £6.50
BASIC ELECTRONICS 6 parts £7.50
BASIC TELEVISION 3 parts £4.25

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME

BLOCK LETTERS

FULL POSTAL

ADDRESS

POST NOW FOR THIS OFFER!

G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

We are glad to say that it is now possible to supply from stock the following integrated circuits. ALL ARE BRANDED, FULL SPECIFICATION devices offered at unbeatable prices!

	1/99	100/499	500/1000		1/99	100/499	500/1000		1/99	100/499	500/1000
7400	£0-15	£0-125	£0-10	7442	£0-645	£0-537	£0-43	7494	£0-495	£0-412	£0-33
7401	£0-15	£0-125	£0-10	7443	£1-275	£1-062	£0-85	7495	£0-63	£0-525	£0-42
7402	£0-15	£0-125	£0-10	7445	£0-855	£0-712	£0-57	7496	£0-72	£0-60	£0-48
7403	£0-15	£0-125	£0-10	7446	£1-05	£0-875	£0-70	74104	£0-315	£0-262	£0-21
7404	£0-18	£0-15	£0-12	7446A	£1-05	£0-875	£0-70	74105	£0-315	£0-262	£0-21
7405	£0-18	£0-15	£0-12	7447	£1-05	£0-875	£0-70	74107	£0-315	£0-262	£0-21
7406	£0-375	£0-312	£0-25	7447A	£1-05	£0-875	£0-70	74121	£0-315	£0-262	£0-21
7407	£0-375	£0-312	£0-25	7448	£0-855	£0-712	£0-57	74122	£0-45	£0-375	£0-30
7408	£0-15	£0-125	£0-10	7450	£0-15	£0-125	£0-10	74123	£0-63	£0-525	£0-42
7409	£0-15	£0-125	£0-10	7451	£0-15	£0-125	£0-10	74141	£0-75	£0-625	£0-50
7410	£0-15	£0-125	£0-10	7453	£0-15	£0-125	£0-10	74151	£0-69	£0-575	£0-46
7412	£0-195	£0-162	£0-13	7454	£0-15	£0-125	£0-10	74153	£0-69	£0-575	£0-46
7413	£0-345	£0-287	£0-23	7460	£0-15	£0-125	£0-10	74155	£0-69	£0-575	£0-46
7416	£0-345	£0-287	£0-23	7472	£0-255	£0-212	£0-17	74156	£0-69	£0-575	£0-46
7417	£0-345	£0-287	£0-23	7473	£0-315	£0-262	£0-21	74160	£1-005	£0-837	£0-67
7420	£0-15	£0-125	£0-10	7474	£0-315	£0-262	£0-21	74161	£1-005	£0-837	£0-67
7423	£0-27	£0-225	£0-18	7475	£0-465	£0-387	£0-31	74162	£1-005	£0-837	£0-67
7425	£0-27	£0-225	£0-18	7476	£0-315	£0-262	£0-21	74163	£1-005	£0-837	£0-67
7426	£0-27	£0-225	£0-18	7480	£0-435	£0-362	£0-29	74166	£1-425	£1-187	£0-95
7427	£0-27	£0-225	£0-18	7482	£0-75	£0-625	£0-50	74174	£1-20	£1-00	£0-80
7430	£0-15	£0-125	£0-10	7483	£0-825	£0-687	£0-55	74175	£0-975	£0-812	£0-65
7432	£0-27	£0-225	£0-18	7485	£1-275	£1-062	£0-85	74192	£1-275	£1-062	£0-85
7437	£0-27	£0-225	£0-18	7486	£0-315	£0-262	£0-21	74193	£1-275	£1-062	£0-85
7438	£0-27	£0-225	£0-18	7490	£0-465	£0-387	£0-31	74198	£2-10	£1-75	£1-40
7440	£0-15	£0-125	£0-10	7492	£0-465	£0-387	£0-31	74199	£2-10	£1-75	£1-40
7441A	£0-825	£0-687	£0-55	7493	£0-465	£0-387	£0-31				

BRAN TUB !!!

- * Resistors—wire-wound and carbon.
 - * Capacitors—silver-mica, paper, ceramic, polyester and electrolytic.
 - * Controls—volume, pre-set, carbon, wire.
 - * Diodes—silicon, germanium, zener.
 - * Transistors—silicon, germanium.
- All the above are new and unused stock.
- We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic, unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!
- To make things even more interesting—TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!
- And the price that we are asking? Only £1-50 including both postage and VAT!
- Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat!

To secure the above prices, all orders for these devices must exceed £10 in total value. Price rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made. For special quotations for large orders ring 021-327 2339 NOW! !!!

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.
Light sensitive aerosol spray Developer and Etchant

£1-00
50p
plus postage

FIBRE-GLASS COPPER LAMINATE

Single sided 75p sq.ft
Double sided £1 sq.ft
Cut in any multiple of 6in to a maximum size of 3ft x 4ft

POSTAGE 30p

NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)

POSTAGE 30p

Practical Electronics Classified Advertisements

RATES: 11p per word (minimum 12 words). Box No. 30p extra. Semi-Display £8.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House Farringdon Street, London EC4H 4AD

RECEIVERS AND COMPONENTS

BETA DEVICES FOR BETTER PRICES

TRANSISTORS	I.C.'s	DIODES & RECT.
AC187/188	709C TO 99	IN914 0-04
FR. 0-40	709C D.I.L. 0-80	IN4148 0-04
BC107/7	741C TO 99 0-80	BY127 0-14
BC108 0-09	741C D.I.L. 0-80	IN4001/2 0-06
BC109C 0-11	728C D.I.L. 0-80	1N4003/4/5 0-06
BC147/8/9 0-10	747C D.I.L. 0-80	IN4006/7 0-08
BCY70/71/720-13	748C D.I.L. 0-80	
BFX86/87/88		
	0-80 Watt Audio I.C.	BRIDGES
BFY50 0-18	TBA 800 £1.50	W01 1A 0-80
BFY51/52 0-12	Dca free with every order.	W06 1A 0-80
OC28 0-45		W06V 0-80
OC35 0-85		ZENERS
2N2846 0-80	D.I.L. SOCKETS	BZY88 3-3-
2N3053 0-14	8-Pin 0-12	33V 5% 0-09
2N3055 0-88	14-Pin 0-12	1 Watt 6-8-
2N3442 £1.40	16-Pin 0-14	200V 5% 0-15
2N3773 £2.20		L.E.D.
71F41A 0-74	All prices include V.A.T.	209-Red 0-17
40636 £1.00		L.E.D. Clip 0-08

C.W.O. PLUS P.P. 10p TO
Abbey Chmbrs, 4 Highbridge St, Waltham Abbey, Essex

VALVES, TRANSISTORS, STYLI. Valves 1930 to 1975, 1,500 types. Many obsolete. List 15p. Transistors list 15p. Styli list 10p. S.A.E. for quotation. (OX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. Tel.: West Wittering 2023.

ALLARD ELECTRONICS

Branded Components—Full Specification

TRANSISTORS	BCR's	Price each	LIN I.C.s	DIL Price each
AC125.6/7/8 0-13	CRS1/05 0-30	709C 0-80	741C SPECIAL PRICE 0-25	747C 1-10
AD143/149 0-48	CRS1/20 0-50	729C 0-80		748C 0-44
AD161/162 0-35	CRS1/40 0-45			309K 2-90
AF114/5/6/7 0-14	CRS3/40 0-55			
AF118 0-35				
BC107/8/9 0-09				
BC147.8/9 0-10	SPECIAL I.C. OFFER			
BC162.3/4 0-10	5 watt Radio Pair			
BC212.3/4 0-11	ZN14, TBA900			
BCY70/71/72 0-12	£2.15 pair FREE DATA			
BD131.132 0-35	Singly			
BF194/5/6 0-10	ZN £1-19			
BFY50/51/52 0-16	TBA £1-25			
BY127 0-25				
MJE370 0-82				
MJE371 0-73				
2N2218 0-19	IN914-IN4148 0-85			
2N2906 0-11	IN4001/8 0-90			
2N2926 all 0-13				
2N3053 0-15				
2N3054 0-15				
2N3055 0-44				
2N3702.3/4 0-10				
2N3705.6 0-10				
2N3707/8/9 0-08				
2N3819 0-20				
BZY88 0-10				
all volts 0-10				
BZX61 0-10				
series 1-3W 0-17				

299/301 BALLARDS LANE LONDON N12 8NP (01-445 5188) MAIL ORDER ONLY. Cash with order. Orders under £3 plus 15p P. & P. Add V.A.T. to total

AXIAL PRODUCTS DEPT. 24 23 AVERY AVENUE HIGH WYCOMBE BUCKS.

4 ELEMENT FM STEREO £3.80 + VAT and 3p P. & P.
16 ELEMENT TV £2 + VAT and 35p P. & P.
16 ELEMENT TV £1.75 + VAT and 35p P. & P.
New design, superior quality, includes mounting bracket, complete with instructions.

AC128 20p	BC148 8p	IN914 4p
BC107 9p	BCY70 16p	IN4004 6p
BC108 9p	BFY51 15p	BZY88C5V6 8p
BC109 10p	2N3055 45p	BZY88C15 8p
BC113 10p	NKT218 100p	LM301 37p
		LM741 28p

ADD 8% VAT + 10p P. & P. per £ under £5

C.W.O. MAIL ORDER ONLY

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate cash settlement.

LED S	dia.	0-125	0-2	D.I.L. SOCKET
RED	15p	19p		8 pin
GREEN	27p	33p		12 pin
YELLOW	27p	33p		14 pin
				13p

with Data clip 1p

INFRA-RED LEDs with Data 550µW axial lead, 49p 1.5 mW TO46, £1-10

OPTO-ISOLATORS with Data
IL74 1-5KV, 150kHz £1
4350 2-5KV, 5MHZ £2-25

OP. AMPS
709 all 25p
7418 pin 20p
748 D.I.L. 38p

THYRISTORS 50V 100V 400V
TO5 1A 25p 27p 40p
TO66 3A 25p 37p 50p

AC127 15p 2N2928(R) 7p
AC128 15p 2N2928(G) 12p
AF117 20p 2N3053 15p
BC107 10p 2N3055 41p
BC108 10p 2N3702 12p
BC109C 14p 2N3704 12p
BC189C 12p 7543 27p
BC182L 11p MPF102 48p
BC184L 11p 2N3819 25p
BC212L 12p 2N3823 30p
BC213L 11p
BCY70 15p
BCY71 22p 7827 Plastic
BCY72 12p 1-5A £1-80
BFY50/51 16p L129 Plastic 5V
OC71 10p 800mA £1-40
2N706 10p
2N2904 10p
2N2906 16p

NE555V 60p
2N414 £1-10
7400 18p
BHA 0002 15W
I.C. AMP £2-50

IN914 3p
IN4001 5p
IN4002 6p
IN4004 7p
IN4148 4p
OA47 6p
OA81 7p
OA81 5p
OA85 5p
OA200 6p
OA202 7p

BRIDGE RECTS.
2A 50V 30p
2A 100V 36p
2A 400V 46p

Used OC84 10 for 50p

PRICES INCLUSIVE + 10p P. & P. (1st class)

ISLAND DEVICES, P.O. Box 11, Margate, Kent

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—EXTREMELY LOW LEAKAGE
440V AC (±10%)
0.1µF (1% × 1%) 50p
0.22µF (1% × 1%) 80p
0.25µF (1% × 1%) 85p
0.47µF (1% × 1%) 75p
0.5µF (1% × 1%) 75p
0.68µF (2% × 1%) 80p
1.0µF (2% × 1%) 91p
2.0µF (2% × 1%) £1-25

63V Range
1.0µF ±1% 50p
2.2µF ±1% 50p
4.7µF ±1% 50p
6.8µF ±1% 50p
10µF ±1% 50p
15µF ±1% 50p
22µF ±1% 50p
33µF ±1% 50p
47µF ±1% 50p
68µF ±1% 50p
100µF ±1% 50p

TANTALUM BEAD CAPACITORS—Values available:
0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V;
10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V;
33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V.
ALL at 10p each. 10 for 95p, 50 for 24.

TRANSISTORS: BC183/183L 11p BFY50 20p
BC107/8/9 9p BC184/184L 12p BFY61 20p
BC114 15p BC212/212L 14p BFY62 20p
BC147/8/9 10p BC547/658A 15p AF178 30p
BC183/7/8 13p BF197 15p OC71 15p
BC182/182L 11p BF197 15p 2N3055 60p

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 90p; IN916 8p, 6 for 45p, 14 for 90p; 1844 5p, 11 for 50p, 24 for 81p; IN4148 5p, 6 for 27p, 12 for 48p; IN4001 6p; IN4002 6p; IN4003 6p; IN4004 7p; IN4005 7p; IN4008 8p; IN4007 8p.

LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 13V, 15V, 18.5V, 18V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. ALL at 7p each, 6 for 38p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.50.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C, 1/4W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 55.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO27: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 1/2 amp: 200V 40p; 350V 45p; 600V 45p.

SUBMINIATURE VERTICAL PRESETS—0-1W only: ALL at 6p each: 50 Ω, 100 Ω, 220 Ω, 470 Ω, 680 Ω, 1k Ω, 2.2k Ω, 4.7k Ω, 6.8k Ω, 10k Ω, 15k Ω, 22k Ω, 47k Ω, 100k Ω, 250 Ω, 680k Ω, 1M Ω, 2.5M Ω.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW 50p. ALL EXPORT ORDERS ADD COST OF SEAWAIGHT.

PLEASE ADD 8% V.A.T. TO ORDERS
Send S.A.E. for lists of additional ex-stock items.
Wholesale price lists available to bona fide companies.
MARCO TRADING
Dept. E.3, The Old School, Edinston,
Nr. Wem, Shropshire
Tel.: Whixall 464/465 (STD 0948 72)
(Proprs.: Minicost Trading Ltd.)

BRAND NEW COMPONENTS BY RETURN, Electrolytics, 16V, 25V, 50V, 0.47, 1.0, 2.2, 4.7, 10 mF. 4p; 22, 47, 100 (50V, 5p); 100, 0.7 (50V, 7p); 220, 7p (50V, 9p); 500, 9p (50V, 14p); 1000/25V, 15p. Subminiature bead-type tantalums, 0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V, 9p. Mylar Film 100V, 0-001, 0-002, 0-005, 0-01, 0-02, 2 1/2p; 0-04, 0-05, 3p. Mullard tubular polyester 400V E6 series, 0-001, 0-022, 3p; 0-033-0.1, 4p. Mullard polyester 160V tubular or 250V miniature for vertical mounting, E6 series, 0-01-0-047, 3p; 0-068, 0-1, 4p; 0-15, 0-22, 5p; 0-33, 6p; 0-47, 8p; 0-68, 10p; 1.0, 12p, 1.5/250V, 16p; 2.2/250V, 19p. Mullard miniature C333 ceramics 63V E12 series 2% 1.8 pF-47 pF, 2 1/2p; 56 pF-330 pF, 3p. Plate ceramics 50V E6 series 470 pF-47,000 pF, 2p. Polystyrene 63V, E12 series 10 pF-1,000 pF, 2 1/2p, 1,200 pF-10,000 pF, 3 1/2p. Miniature highstab. carbon film resistors 1/4W E12 series 5% (10% over 1MΩ) 1Ω-10 MΩ, 1p; IN4148, 3p; IN4002, 5p; IN4006, 7p. Postage 10p. Prices VAT inclusive. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

R.T. SERVICES (MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.
12 Volt 1 Amp Trickle Charger, £1.85 P.P.
FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 × 2 1/4 in with circuit, £1.37 inc. P.P.
Crouzet geared Motors, 30 r.p.m. New, £1.54 inc. P.P.
UHF TV Tuners. Transistorised, £1.85 inc. P.P.
Panels with I.C.'s on 7 1/2p per I.C. min. order 10 I.C.'s.
Transformers. 7.5V + 7.5V 1/2A, £1 inc. P.P.
12-0-12V, 100mA, £1-10 inc. P.P.
100mA, £1-10 inc. P.P.
29V 50mA, 85p inc. P.P.
6-0-6V, 100mA, £1-10 inc. P.P.
Transformer. 24 volt, approx. 1 amp + 6.3V CT approx. 500mA, £1-40 inc. P.P.
Transformer. 20-0-20 volt, approx. 2 amp + 6.3V, £3 inc. P.P.
Transformer. 20 volt, 1 amp, £1-25 P.P.
Transformer. 45 volt, 2 amp, £3 P.P.
P.C. Board S/S, 2 1/2 × 5 1/2 in, 10 for £1 inc. P.P.
3EG1 Scope Tubes with base and connections, £3-30 inc. P.P.
Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions. Brand new, £2 inc. P.P. Size 3" × 2" × 2".
Power Unit Components Transformer. 18 volt 1 amp F/W bridge rectifier, 2 1/2 mfd capacitors, all new £1-40 per kit. P.P.
Electrolytic Capacitors, 4,000 MF, 50VW, 4 1/2" × 1 1/2" 80p. inc. P.P.
Mixed Pack of C280 series Mullard capacitors. 100 for £1-15 inc. P.P.
4 Panels each with XN3 type Nixie tube ON £1-85 inc. P.P. Min. order 4.

COPPER CLAD FIBRE GLASS PANELS 12 1/2 in × 7 in, 60p; 18 in × 4 in, 70p. Double sided 12 1/2 in × 7 in, 90p; 11 in × 13 in, £1-30. All post paid. MC METERS, 3 assorted 2-3in, £1-30 (40p). LARGE COMPUTER PANELS, 35-50 Transistors. Lone leads, 85p (40p); 74 PANELS, 10 I.C.s ON PANELS, 10 for 80p (10p). COPPER CLAD PAX. PANELS, 8 in × 9 1/2 in, 3 for £1. 12 1/2 in × 9 in, 2 for 90p. 16 in × 9 1/2 in, 80p. Double sided 12 1/2 in × 12 1/2 in, 70p. All post paid. 22-WAY STEPPING SWITCH WITH RESET. A.C. mains operated, £1 (30p). THREE TRANSISTOR AUDIO AMP Transistors equip. to AC128, OC72, 40p (10p). 3 for £1, c.p. VALU-PACKS P9, 100 n/mica caps 55p, P3, 10 silicon diodes 650V 1 1/4, 50p. Post 12p for one, 20p any multiple. Send 12 stamps for full list plus computer panels, etc. Refund on purchase.

71b ASSORTED COMPONENTS £2 c.p.
31b COMPUTER PANELS £1-75 c.p.

J.W.B. RADIO
2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage in brackets Mail order only

LED's. Three colours, red, green, and yellow. Four sizes, 0.1 in 0.125 in, 0.16 in, 0.2 in. Mixtures all sizes and colours. 50-85, 100-85 including VAT and postage. C.W.O. Larger quantities by negotiation. INDUSTRIAL ELECTRONIC SUPPLIES (Stockport) Ltd., 151a Bramhall Lane, Davenport, Stockport, Cheshire.

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 69p per dozen; £4.12 per 100; £30.25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.
68/68 Portland Road, Worthing, Sussex BN13 3AB

SITUATIONS VACANT

MEN!
£70p.w.
can be yours

Jobs galore! Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. London Computer Operators Training Centre subscribes to the British Government backed National Computing Centre code of practice for Computer Training Schools so you know your training will be second to none.

After training, our exclusive appointments bureau — one of the world's leaders of its kind — introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators
Training Centre Y34, Oxford Hse.
9-15 Oxford St., W.1. Tel. 01-734 2874

EDUCATIONAL

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians, Radio/TV/Electronics Technicians Telecommunications Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

INTERNATIONAL
CORRESPONDENCE SCHOOLS
Dept. 730, Intertext House, London
SW8 4UJ
Or phone 01-622 9911 (All hours)

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 20p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

BELL'S TELEVISION SERVICES for service sheets, manuals, books on radios, T.V.s, etc. Service sheets 50p plus S.A.E. Free book lists on request. Back issues of P.W., P.E., E.E., TV available 25p plus 9p post. S.A.E. with enquiries: B.T.S. (Mail Order Dept.), 180 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

BOOKS AND PUBLICATIONS

UFO CHARTS: Daily Flight, 50p; Prediction, 54p; Map, 50p; Propulsion, 55p; "Anti-Gravity", 55p; TV UFO Detection (Reprint), 63p; Circuits: Transistor Optical Detector, 66p; Radiation/Optical, 44p; Microdetectors (Memory, LSI), 80p; Crystal Radiation/Counter-Timer/Stopclock, 85p; FET Multimeter, £1.70, R. & E., Highlands, Needham Market, Suffolk.

PROFESSIONAL SERVICES

PATENTS AND TRADE MARKS. KINGS PATENT AGENCY LIMITED (Est. 1886). B. T. King, Director, M.I. Mech. E., Registered Patent Agent, 146a Queen Victoria Street, London, EC4V 5AT. Booklet on request. Tel. 01-248 6161. Telex 883805.

LADDERS

LADDERS, timber and aluminium. Tel. Telford 586644 for brochure.

MISCELLANEOUS

EXPERIMENTERS and constructors. Hundreds of unusual items cheap. List 9, 8p. GRIMSBY ELECTRONICS, Lambert Road, Grimsby (callers Saturdays only).

SINTEL Add 10p P. & P. for orders under £2. Data, and circuits where appropriate, supplied with orders, or available separately (send 9in x 4in S.A.E.). ADD VAT at 8%

Economy DL784 0.3in LED 7 segment display	Only 85p
NBWS2 0.12in 3 Digit LED readout—only 55p/digit!	£1.85
MAN 3M type 0.12in 7 segment display	46p
MK92020N Alarm Clock I.C.	£3.99
P.C.B.s now available for clocks, drivers, displays (send 9in x 4in S.A.E.)	
CT7981 + 4 DL784 only £19.80: CT7981 + 8 DL784 for £12.78	
SOLDERCON I.C. Socket Pins	300 pins for £1.50
(Instructions supplied)	1,000 pins for £1.99
Send S.A.E. for sample	3,000 pins for £19.50

SINTEL, 53B ASTON STREET, OXFORD. Tel. (0865) 43203

IC SOCKET PINS for low cost mounting of 8 to 40 pin DILs. 70p (+ 5p VAT) for strip of 100, £1.50 (+ 12p VAT), for 3 x 100, £4 (+ 32p VAT) for 1,000. Instructions supplied—send S.A.E. for sample. 10p P. & P. for orders under £2. SINTEL, 53b Aston Street, Oxford. Tel. 0865 43203.

KIMBER — ALLEN

THE WORLD'S FINEST KEYBOARD

From the distributor:

**ALAN DOUGLAS, Leesbarn Road
Radcliffe on Trent, Notts. NG12 2DS**

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of radio, Electronics and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Largest choice at highly competitive prices, why pay more? Fast despatch. Free literature (stamp would be appreciated). BAZELLI, Department No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster, LA2 6LT.

LIGHTING MODULES AND KITS CHEAPER STILL!

SAVE POUNDS BY BUYING DIRECT!!

SOUND TO LIGHT: 3 x 1½ kW channels with SENSITIVITY, DIMMING and BYPASS controls. Designed to be robust and reliable and simple to build. KIT FORM: £13.99; PRE-BUILT: £15.99. THEATRE AND DISCO/CLUB DIMMERS OUR SPECIALTY!

Only written enquiries and Mail Order to:

**SELEKTRON
21 Priors Road, Windsor, Berks. SL4 4PD**

12 VOLT 21in 13 watt FLUORESCENT LIGHTING (by THORN/AEI) with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc. Guaranteed

£5.50 inc. VAT and post. List price £7.02 inc. VAT.

SALOP ELECTRONICS Tel. 53206
23 Wyle Cop, Shrewsbury, Shropshire

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-off's and small runs. Machine engraving in metals and plastics, contour milling. Send 2 44p stamps for catalogue. **RAMAR CONSTRUCTOR SERVICES,** Masons Road, Stratford on Avon, Warwick, CV37 9NF.

MINI ACCUMULATORS

2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.

Size L450—1'4" x 1'1" x 0'44". 3 for £1.85 inc. P. & P.

Size GA2—1'7" x 1'3" x 0'5". 3 for £2.35 inc. P. & P.

GARFIELDS, 269 Rye Lane, London, S.E.15

PRINTED CIRCUIT BOARDS. Manufacturers' offer: PCB's for ALL "P.E. and P.W." projects published after June, 1974, at ONE price, 70p each. Any 5 £2.85. PRODUCTION SPACE available for: PCB Production, PCB and Electronic Design to Spec.; electroplating, silk-screening, roller and electro tinning. All art-work and photography undertaken. Send basic circuit, P.C layout or R.C. master stating quantity required for estimate by return, or phone: W.K.F. ELECTRONICS, Dept. P.C., Welbeck Street, Whitwell, Worksop, Notts., S80 4TW. Tel.: Whitwell (Derbys.) 695.

fibres optic suppliers

MARE'S TAILS. Build a decorative display with this professionally finished unit, 22in diameter with 7,000+ fibres. Looks immaculate. £16.

FIBROFLEX SIZE 1. Flexible 440 strand glass light conduit. bundle dia. 1.14mm. 40p per metre (£3 per 10m).

FIBROFLEX SIZE 4. 2-28mm bundle dia. £1.50 per metre (£12 per 10m).

CROFON 1616. 84-strand plastic light conduit, bundle dia. 1.8mm. C.D. 3.3mm. £1.38 per metre (£9.38 per 10m).

PLASTIC OPTICAL MONOBEAMS. For multiple illumination from one source, displays, internal illumination, effects, optical coupling, etc.

FP20 (0.5mm dia.)—50p per 10m; £4 per 100m.

FP40 (1mm dia.)—£2.50 per 10m; £14 per 100m.

FP80 (1.5mm dia.)—£4 per 10m; £30 per 100m.

OPTIKIT 183. Contains 2m Crofon 1616 plus 5m each FP20, FP40, FP80 plus polishing compound. A handy pack for the experimenter. £4.78.

LENSES AND REFLECTORS. We stock a range of 6 lenses and 5 reflectors for use in proximity detectors, intruder detectors, batch counters, tachometers, short range optical communications.

OPTIKIT LS. 1 each of 6 lenses. £2.99.

OPTIKIT RRS. 1 each of 5 reflectors. £1.99.

CIRCULAR POLARISERS. Cut that glare. Reduce specular reflection by up to 20x—enhance contrast on crts. LED displays, nicols, instruments, etc. Available in red/amber/green/neutral. 50mm square 80p; 75mm £1.00; 150mm £4.

LINEAR POLARISERS. For light valves, stress analysis, type HN32. Type KN42 is for high temp. use in projectors. Use a pair to make a psychedelic light show. Price as for circular polarisers.

LIGHT SOURCES AND DETECTORS: MV54 Miniature (2mm) Red LED, 20p (10+ 18p); MLED507 T092 Red LED, 20p (10+ 18p); MLED82 Infra-Red Emitter, 30p (10+ 17p); XC209-R 3mm Red LED, 20p (10+ 18p); XC209-Y or -G Yellow/Green, 30p (10+ 27p); 2N5777 High Sensitivity Photodetector Silicon Detector, gain x2,500, 50p (10+ 48p); MFD150 Silicon Phototransistor—high speed, 4us good sensitivity, 70p (10+ 67p).

****NEW MLE263.** Latest Motorola Light Activated SCR. High sensitivity 10mW/cm²; high current 400mA (5A peak); 80V. Switch small motors or relay direct from optical control, up to 24W power. £1.50 (10+ £1.18).

SEOS8 ULTRASONIC TRANSDUCER. For remote control 40KHz. Tx/Rx pair, £3.50.

Please add 8% VAT to prices above

Send 9in x 6in S.A.E. for short form list.

FIBRE OPTIC SUPPLIERS

(Dept. PE), 2 Loudoun Road Mews

London NW8 0DN

(Please note change of address)

FANTASTIC NEW MICROTEST 80


MEASURES
ONLY

90 x 70 x 18mm



Amazing Value at £11.95
8 fields of measurement
and 40 ranges

Volts d.c. 6 ranges: 100mV, 2V, 10V, 50V, 200V, 1.000V (20kΩ/V)
Volts a.c. 5 ranges: 1.5V, 10V, 50V, 250V, 1.000V (4kΩ/V)
Amp. d.c. 6 ranges: 50μA, 500μA, 5mA, 50mA, 500mA, 5A
Amp. a.c. 5 ranges: 250μA, 2.5mA, 25mA, 250mA, 2.5A
Ohms 4 ranges: Low Ω, Ω x 1, Ω x 10, Ω x 100 (da 1/10 of Ω fino a 5MΩ)
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1.000V
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB
Capacity 4 ranges: 25-F, 250μF, 2.500μF, 25.000μF

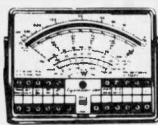

SUPERTESTER 680 R ICE

20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields
Scale width and small case dimensions (128 x 95 x 32mm)
Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading
Simplicity and ease of use and readability
Full ranges of accessories

£18.50

Accessories Extra

1,000 times overload
Printed circuit board is removable without de-soldering
More ranges than any other meter. Ask for free catalogue.
Accessories (extra) available to convert Microtest 80 and SuperTester 680R into following SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLT METER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details.

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0-06-3A-6 Ranges.
A-AC 0-3-3A-5 Ranges.
V-OC 0-6-1200 V-9 Ranges.
V-AC 3-900 V-8 Ranges.


Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm—5 ranges. Decibel: -1 to +12dB. Accuracy: ±2.5%. DC +4% AC. Dimensions: 167 x 98 x 63mm.

Only £8.85



ALPHANUMERIC NIXIE TUBES B7971

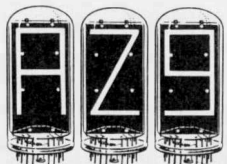The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube.



From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including * 170V, 21mA * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light . . . 200 footcandle brightness * Long life with no loss of brightness * Character height 2 1/2 in.

Bases for above 80p each.

Price only 99p each plus 16p P./P.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V d.c. Current 14mA. Pulse duration 100μs. Character height 0.51, overall size 1.4.
Brand new, guaranteed. Surplus to manufacturer's requirements. Type B5853at

1-25 £1.00; 25+ 90p; 100+ 80p; 1,000+ price on application.

Add 8% VAT to all items + 35p P. & P.

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

HOME SCIENTISTS

Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists DOZENS of HIGHLY UNUSUAL, LOW-COST BARGAINS, READY-BUILT MODULES.

Here are just a few examples, there are stocks more!

Dazzling MINI-STROBE (pocket size) £2.90
PEOPLE DETECTOR . . . £3.20
Big-Ear SOUND-CATCHER . . . £3.20
Mini DREAM LABORATORY . . . £3.20

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and we'll RUSH YOU A COPY (YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!)

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh

Ewell, Surrey

(Mail Order U.K. only)

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

ULTRASONIC TRANSDUCERS

Suitable for INTRUDER DETECTOR

Practical Electronics, March 1975

Tx/Rx Pair £3.50 + 28p VAT

FIBRE OPTIC SUPPLIES

2 LOUDOUN ROAD MEWS

LONDON NW8 0DN

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to: METER REPAIRS, 21 Mount Road, Thundersley, Benfleet, Essex, SS7 1HA.

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1/2lb Reel
10-14	£2.05	£1.15
15-19	£2.15	£1.20
20-24	£2.20	£1.25
25-29	£2.25	£1.30
30-34	£2.35	£1.38
35-40	£2.50	£1.45

All the above prices are inclusive in U.K.

COPPER SUPPLIES

102 Parrswood Rd., Wingham, Manchester 20
Telephone 061-224 3553

AERIAL BOOSTERS £3, P. & P. 10p. We make three types of boosters: L11-VHF radio; L12-VHF 405 TV. Please state channel numbers. L45-UHF-625 TV. S.A.E. leaflets: LANCASHIRE MAIL ORDER, 6 William Street, Stubbs, Ramsbottom, Bury, Lancs.

BUILD THE **TREASURE TRACER**
MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send s.a.s. for leaflet

Complete kit £9.80 Built, tested and guaranteed £13.75
P. & P. 60p + 78p VAT P. & P. 60p + £1.10 VAT

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD,
LONDON E16 2AN (Mail Order Only)

LOW COST I.C. MOUNTING. 100 I.C. pin sockets 60p. Quantity rates. S.A.E. details and sample. 7 and 8 hole plastic supports 5p/pair. (P. & P. 5p/order). LED (MLED500) 20p each post free. Quantity rates. P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

STEREO Pickup Pre-amp RIAA.

Suitable p.u.'s 2-10mv output. Features ultra low noise IC 70dB type. Max. output up to 1v. rms. (dep. on input). Frequency Response 20Hz-100KHz. Mains powered for easy installation.

£5.95 incl. VAT. P. & P. 15p.

S.A.E. for details of other modules.

P. F. STEVENS Electro-Acoustics
8A CLARENCE ROAD
SOUTH BENFLEET, ESSEX

FOR SALE

PARTLY BUILT ELECTRONIC ORGAN. 12 x 6 stage dividers, 12 x oscillators (less coils). Tone forming circuits, distribution panel and circuit details. £18. WESTELL. Tel. Whalley 3769 after 6 p.m.

PRACTICAL WIRELESS, Dec. 60-Sept. 71, 130 issues—cost £15.97. PRACTICAL TELEVISION, Oct. 60-Sept. 72, 143 issues, cost £17.39. Offers to Box No. 59.

MAGAZINES—Practical Electronics 1967-1974 and others. Offers to TREMLETT, 17 Radnor Road, Bristol, BS7 8QS.

GREENBANK ELECTRONICS new components. Digital clock chip AY-5-1224 plus data £3.66, data alone 16p (refundable on order). DL747 0.6 in. "Jumbo" LED display now only £2.04. 1/2W carbon film resistors 4.7 ohm to 4.7 MΩ 1p each. Triac TAG 250-400 8A, 69p. D32 diac 23p. 1N914/4148 3p. 2N3702/3704 9p. Post free, add standard VAT. 94 New Chester Road, Wirral, Merseyside. L62 5AG.

ELECTRONIC PIANO (five octave) with synthesised piano—honky tonk—plucked string bass and harpsichord effects. Complete with carrying case and service information. Perfect working order and condition. £100 o.n.o. Send S.A.E. for full details. FRANCIS MORTON, 65 Malmsey House, Vauxhall Street, London, SE11 6LU.

OSCILLOSCOPE Heathkit 10-18U for sale, £54 value, six months old: £40 o.n.o. COULSON, 39 St. Bedes Close, Durham.

"GEMINI"—PCBs with most components in place; offers, POWELL, 20 Rushington Avenue, Maidenhead, Berks.

WANTED

SERVICEABLE MAINS TRANSFORMER for Solartron CD1400 oscilloscope. State price. MURPHY, 185 Otley Road, Harrogate, HG2 0DA.

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

"RADIO & TV SERVICING" books wanted from 1961 onwards, any quantity. £2 paid per copy by return of post. BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, Yorks. Tel. (0423) 55885.

P.E. WANTED. Any 1971, Jan. to Oct. 72, and Feb. 73. HANNIS, Reading 882641.

SYNTHESISER Modules by Dewtron®



The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/ps; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 15p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

CJL PRICES INCLUDE P&P AND V.A.T.

BIB HI-FI ACCESSORIES

- CASSETTE TAPE RECORDER CARE KIT . . . £1.95
- CASSETTE SPLICING AND EDITING KIT . . . £1.50
- HI-FI STEREO TEST CASSETTE . . . £2.10
- 1/4" TAPE EDITING KIT . . . £1.35
- GROOV-KLEEN RECORD CLEANER . . . £1.85

COMPONENT PACKS

- CAPACITORS-Electrolytic-Tubular-Submin-Mixed £0.50
- CAPACITORS-P.C.B. Polyester-Mixed Preferred £0.50
- RESISTORS-Carbon Film-Mixed Preferred . . . £0.50
- POTENTIOMETERS-Midget Carbon Track-Mixed £0.50
- HEADPHONE, stethoscope style, 8 ohm dynamic £1.00
- HAND DRILL, (Laytool), compact precision drill, 5/16" chuck. Gears totally enclosed. S/L bearings . £2.99

INTEGRATED CIRCUITS

- AUDIO POWER AMPLIFIER (National) LM380 £1.00
- A.M. RADIO RECEIVER (RCA) CA3123E £1.40
- F.M. STEREO DECODER (Motorola) MC1310P £2.80
- TIMER (Signetics) NE555V £0.78
- VOLTAGE REGULATOR (Fairchild) uA7805 £1.70
- VOLTAGE REGULATOR (Signetics) NE550A £0.80
- D.I.L. SOCKETS (Pk of 3) 8 or 14 pin £0.50
- KEYNECTOR, rapid connect to mains-single/multiple leads. Built-in plano switches, neon & 13A fuse . £3.20
- LOCKFLEX RULE, (Rabone Chesterman), 3m/10ft precision pocket rule. Easy to read, 13mm/1/2" wide steel tape. Blade length lockable-power return. A superb rule . . . £0.93
- MICROPHONE, lightweight dynamic, remote start stop, 200 ohms, 100-10kHz, 6mV average output £1.80
- SIGNAL INJECTOR, audio through video signals, excellent for servicing amplifiers, radio & tv . £3.92
- SOLDERING IRON, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable) £1.85
- 3/32" bit £0.45 3/16" bit £0.45 Element £0.95
- STAND, ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits. £0.95



CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

SCIENTRONICS

greet constructors with EXCLUSIVE INTRODUCTORY MONEY-SAVING OFFERS

SCIENTRONICS

is a new company organised to develop and promote electronic designs of especial interest to constructors. We are privileged to offer, as our opening shot, a substantial quantity of selected items no longer part of the production programme of an internationally famous British manufacturer.

These include transistors by Ferranti, Texas, ITT and others made to stringent specifications, e.g., E5401 with a guaranteed gain at 1 micro amp. All these transistors are brand new and guaranteed within the terms of our published specifications.

S.A.E. brings full list by return. Leads on components are untrimmed

TRANSISTORS

General Purpose	NPN (N) PNP (P)	One off price in pence	VCE	HFE Min.	mA
FRB 771	P	7.5	*50	100	1
E5368A	N	7.5	25	100	1
E5368B	N	7.5	25	150	1
E5368C	N	8	25	250	1
E5369	P	7.5	20	70	1

Low Level

E5401	P	7.5	*30	50	1µA
E5403	P	7.5	*30	100	10µA
E5404	N	7.5	*30	100	100µA
E5405	P	7.5	*30	100	100µA

Drivers and Switching (tested for low Vce (sat))

FRB772	P	8	40	40	
E5370	N	5	20	{ 15	500
				{ 100	10
E5398	P	8	40	40	60
E5397	P	8	20	100	100

High Frequency (800MHz Ft)

E5395	N	7.5	30	20	3
E5400	N	8	10	10	1
XK6116	N	8	20	10	1

High Voltage

E5407	P	9	65	50	10
E5408	N	7.5	65	50	10

Quantity Discounts (prices in pence per device)

Single	10	100	1,000	Single	10	100	1,000
5	4.5	3.5	3.0	8	7.4	5.7	4.9
7	7.0	5.5	4.5	9	8	6.5	5.5
7.5	7.2	5.8	4.8				

*Intended for 10V working guaranteed but almost all would pass for higher voltage operation as indicated. Most can be selected for higher voltage working at an extra charge of 1p per device.

RESISTORS

Most values in E.12 series are available in 5% or 10% tolerances. Miniature types (1/4W). Quantity rates applicable to orders of same value.

0.8p each, 10 of same value 7p: in a range of useful values 100, 55p; 1,000 £4.50.

CAPACITORS

Ceramics from 1-1p to 2p each, 10p to 18p for 10, 77p to £1.45 for 100, £8.25 to £11.75 for 1,000.

Electrolytics from 10-50 Volts: 1 to 220mF, 3p each, 27p for 10, £2.20 for 100, £17.25 for 1,000.

NIXIE DISPLAYS/SWITCHES/TRANSFORMERS/KNOBS/NUTS/BOLTS etc.

Send S.A.E. for full lists and prices—REAL MONEY SAVERS THESE.

ENQUIRIES FROM TRADE AND BULK BUYERS INVITED SPECIAL QUANTITY DISCOUNTS

ORDERING AND GUARANTEE

All goods guaranteed within terms of specification and in stock at time of going to press. Send cheque or money order with order, or if cash, send reg. post. Please state your requirements clearly. Satisfaction guaranteed or your money refunded.

MIN. ORDER £1. All goods sent post paid in U.K. Overseas postage charged at cost. VAT—Add 8% total value of order in U.K.

SCIENTRONICS

Dept. PE4, 40 HIGH STREET, SOMERSHAM,
HUNTINGDON, CAMBS., PE17 3JA.

Telephone Somersham (04874) 321



"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give d.c. to winding for a maximum holding torque of 300oz/in with 35V at 0.35A through winding. For a.c. (synchronous) operation at 120v., 50Hz. Speed 60r.p.m. at 60Hz. 72r.p.m. STEPPING Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions dia. 4in. body length 4½in. spindle length 2½in x ¼in dia. Weight 6½lb. BRAND NEW in maker's packing. Offered at less than half maker's price.

OUR PRICE ONLY £15. P. & P. £1

MAGNETIC DEVICES SOLENOID

240V a.c. 50 P.C. rated 18lb pull. 1½in travel push or pull. Shackle both ends. length overall 4in plus 3in travel arm x 2½in x 3½in high. Brand new £5.25 plus 60p P. & P. or ex-equipment £3 plus 60p P. & P.

CARTER ELECTRIC

Similar to above with alloy gear case. 60r.p.m. This item is ex-equipment but perfect. £1.95. P. & P. 30p.

SHADED POLE MAINS MOTOR

A quality shaded pole motor. Open frame. 3in high x 2½in x 2in. Spindle 1in x ¼in. 1,420r.p.m. £1.95. P. & P. 20p.

"LABGEAR ELIMINAC"


P.S.U. 200-250V. 40/80Hz. Alternative outputs fully variable (variac incorporated). Output 1. 12V at 5A d.c. fully smoothed. Output 2. 12V at 8A d.c. with ripple content. Output 3. 20V at 10A a.c. 2½in x 2½in flush 0.20V d.c. m.c. motor. In attractive grey hammer finish case. In maker's carton. £27.50. Carr. & Pkg £1.50.

SPECIAL OFFER LIGHT DEPENDENT RESISTORS

Matched pairs Pioneer Type 174 similar to OPR 12. Resistance 1kΩ to 4kΩ. Dia. ½in with ½in flanges. £1.50 for two pair (minimum) 10 or more pairs 50p. per pair incl. P. & P.


MAINS SOLENOID

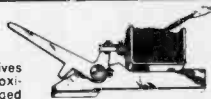This little unit gives vertical lift of approximately 1½in through hinged 'elbow'. Bracket incorporates 2 fixing screws. Length of arm. 2½in 240V a.c. Pull at coil is approximately 1½lb. £1. FREE P. & P. Special quote for quantities.



SOLENOIDS by WESTOOL

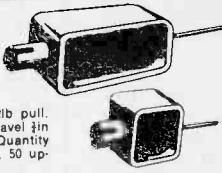240 a.c. type. MM6 3½lb pull, 2½in x 1½in x 1½in. Travel 1in 90p each. P. & P. 10p. 240 a.c. type MM4. 2½lb pull. 1½in x 1½in x 1in. Travel ½in 70p each. P. & P. 10p. Quantity discounts: 10-50 10%. 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 a.c. 28r.p.m. NEW HIGH TORQUE. approx. overall size: 3½in x 3½in x 2½in. spindle ½in dia. as illustrated. £2.70 plus 30p P. & P. 110r.p.m. with pressed steel gear case (similar to above but slightly smaller). £2.70 plus 30p P. & P.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!




A magnetically activated switch. vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3A at 120V. 1½A at 240V. Size: (approx.) 1½in long x ½in dia. Ideal for burglar alarms, security systems, etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8.80; 100 for £15.50. FREE P. & P. over 10.

AMPEX 7.5V D.C. MOTOR

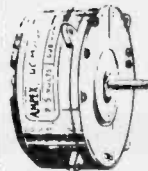

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500mA. Draws 60mA on run. 600r.p.m. — speed adjustment. Internal AF/RF suppression. ½in dia x 1in spindle motor 3in dia x 1½in. Original cost £16.50. OUR PRICE £4.25. P. & P. 25p. Quantity available. Mu-metal enclosure available 75p each. FREE P. & P.

FAN/BLOWER

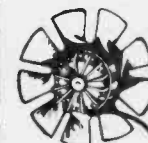

Precision built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60mA on run. Size: 5½in dia. x 2½in deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3 plus 40p P. & P.

ALL PRICES INCLUDE VAT

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317 EDGWARE ROAD
LONDON, W.2
Tel: 01-723 5667, 01-402 5580

ELECTROVALUE

IMPORTANT ANNOUNCEMENT ON PRICES

1975 is the year of challenge. Rather than sit back and wait for things to happen, we have produced our own policy to help stabilize price structure and maintain the services which have made ELECTROVALUE pre-eminent.

PRICES as shown in our latest catalogue (No. 7, issue 3) will be maintained at least until March 31st next (except in severe cases of market fluctuation) and then held after review for further 3-month periods instead of day to day price changes.

CATALOGUE No. 7, ISSUE 3 is now ready with 112 pages of bargains and information. Price—30p post paid, including 25p refund voucher for use on orders for £5 or more.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise. **SUPPLIERS OF QUALITY COMPONENTS AND SEMI-CONDUCTORS AT COMPETITIVE PRICES.**

ELECTROVALUE LTD

All communications to Dept. PE4, 28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB Telephone Egham 3603, Telex 264475 Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA Telephone (061) 432 4945 Shop hours: Daily 9-5.30 pm, 9-1 pm Sats.



Phoenix Electronics
(Portsmouth) Ltd.
139-141 Havant Road,
Drayton, Portsmouth, Hants
PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

COMPONENTS FOR I.C. APPLICATIONS BY MR. J. B. DANCE

SAJ110	£1.96	SAJ180	£1.96	SAK110/115	£1.23
TAA775G	£1.23	TAA930A	£1.23	TBA790KSD	£1.96
TBA800	£1.96	TBA950	£1.76	TCA250	£1.96

Please send your catalogue—free!

Name

Address

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course."—Student D.I.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects."—Student J.A.O., Dublin.
 "My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold."—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters, and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to:

ALDERMASTON COLLEGE

Dept. TPE04, Reading RG7 4PF

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T Home Study Course. Choose your subject now!



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL	<input type="checkbox"/> DRAUGHTSMANSHIP	<input type="checkbox"/> Construction Surveyors Institute
<input type="checkbox"/> Society of Engineers—	<input type="checkbox"/> Institute of Engineers	<input type="checkbox"/> I.C.S.I.
<input type="checkbox"/> A.M.S.E. (Mech)	<input type="checkbox"/> Designers (A.M.I.E.D.)	<input type="checkbox"/> CITY & GUILDS
<input type="checkbox"/> Institute of Engineers & Technicians (A.M.I.E.)	<input type="checkbox"/> Draughtsmanship	<input type="checkbox"/> General Building (all branches)
<input type="checkbox"/> CITY & GUILDS	<input type="checkbox"/> Elec. Draughtsmanship	<input type="checkbox"/> Heating & Vent
<input type="checkbox"/> Gen. Mech. Eng.	<input type="checkbox"/> Architectural	<input type="checkbox"/> Inst. Clerk of Works
<input type="checkbox"/> Maintenance Eng.	<input type="checkbox"/> Draughtsmanship	<input type="checkbox"/> Site Surveying
<input type="checkbox"/> Welding	<input type="checkbox"/> Technical Drawing	<input type="checkbox"/> Health Engineering
<input type="checkbox"/> Gen. Diesel Eng.		<input type="checkbox"/> Road Construction
<input type="checkbox"/> Sheet Metal Work		<input type="checkbox"/> Quantities
<input type="checkbox"/> Eng. Inspection	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS	<input type="checkbox"/> Estimates
<input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> Telecoms	<input type="checkbox"/> Hydraulics
	<input type="checkbox"/> Gen. Radio & TV	<input type="checkbox"/> Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC	<input type="checkbox"/> Eng. Radio Amateurs	<input type="checkbox"/> GENERAL
<input type="checkbox"/> CITY & GUILDS	<input type="checkbox"/> Exam Radio Servicing	<input type="checkbox"/> Agricultural Eng.
<input type="checkbox"/> Gen. Electrical Engineering		<input type="checkbox"/> Council of Eng. Institutions
<input type="checkbox"/> Electrical Installations	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL	<input type="checkbox"/> Farm Science
<input type="checkbox"/> Electrical Maths	<input type="checkbox"/> Institute of the Motor Industry	<input type="checkbox"/> Plastics
<input type="checkbox"/> Computer Electronics	<input type="checkbox"/> A.M.I.I.	
<input type="checkbox"/> Electronic Eng.	<input type="checkbox"/> CITY & GUILDS	
<input type="checkbox"/> Practical Radio & Electronics (with kit)	<input type="checkbox"/> Auto Eng.	
<input type="checkbox"/> MANAGEMENT & PRODUCTION	<input type="checkbox"/> Gen. Auto Eng.	
<input type="checkbox"/> Institute of Cost & Management Acctns.	<input type="checkbox"/> Motor Mechanics	
<input type="checkbox"/> Computer Programming	<input type="checkbox"/> Auto Diesel Eng.	
<input type="checkbox"/> Works M'nt	<input type="checkbox"/> Garage M'nt	
<input type="checkbox"/> Work Study	<input type="checkbox"/> AFC Aero Engineering	
<input type="checkbox"/> Gen. Production Eng.	<input type="checkbox"/> Exams	
<input type="checkbox"/> Estimating & Planning	<input type="checkbox"/> Gen. Aero Eng.	
<input type="checkbox"/> Storekeeping	<input type="checkbox"/> CONSTRUCTIONAL	
<input type="checkbox"/> Management Skills	<input type="checkbox"/> Institute of Building	
<input type="checkbox"/> Quality Control	<input type="checkbox"/> I.O.B.	
	<input type="checkbox"/> A.B.T. Clerk of Works	

Supplementary courses for Nat. Certificates.

G.C.E.
— choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, TPE04
Dept. TPE04, Reading RG7 4PF

NAME
Block Capitals Please
ADDRESS

POST CODE

OTHER SUBJECTS

AGE


Accredited by C.A.C.C.

Member of A.B.C.C.

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (Asia) Ltd. South Africa—Central News Agency Ltd. Publisher's Subscription Rate including postage for one year, Inland £3.85, Overseas £4.70 U.S.A. and Canada \$13.00 International Giro facilities Account No. 5122007. Please state reason for payment. "message to payee". Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's Radio

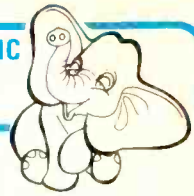LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES - MEAN LESS VAT.



You can build the Texan and Stereo FM Tuner

TEXAN 20 - 20 WATT IC STEREO AMPLIFIER

Features glass fibre PC board, Gardners low field transformer, 6-ICs, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15in x 2 1/2in x 6 1/2in mains operated. Free teak sleeve with every kit.



£31.00 (Carriage 50p) (also built and tested £37.50)



(also built and tested £24.95)

STEREO FM TUNER Features capacity stereo tuning, lead and tuning meter indicators, stabilised power supply - mains operated. High performance and sensitivity with unique station identification IC stereo decoder. Overall size in teak sleeve 8in x 2 1/2in x 6 1/2in. Complete kit with teak sleeve.

£21.00 (Carriage 50p)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

NEW SPECIAL PURCHASE



AM/FM tuner modules

Mullard type LP1179 and LP1171. These two modules together form a high quality AM/FM tuner covering the long, medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete. Supplied with circuits and spec data.

FM Coverage	87-108MHz
Bandwidth	300kHz
Selectivity	35 dB
Signal to noise at limiting threshold	40 dB
Audio output	75 mV
AM Bandwidth	6.5 kHz
Sensitivity	1 µV
Built-in AGC	

Supply 6V negative earth. LP1179 and LP1171 £7.50. Suitable Ferrite aerial 75p.

Amplifiers with controls

E1210	12 volt 2 $\frac{1}{2}$ + 2 $\frac{1}{2}$ watts 8 ohms	8.25
SAC 14	Mains 7 + 7 watts 8 ohms	11.75
SAC30	Mains 15 + 15 watts 8 ohms	14.85
CA038	9 volt 1 $\frac{1}{2}$ + 1 $\frac{1}{2}$ watts 8 ohms	6.95
CA068	12 volt 3 + 3 watts 8 ohms	10.50

AM/FM MODULES

Mullard LP 1186	FM tuner (front end) with data 10.7 MHz O/P	4.85
Mullard LP 1157	AM/module	4.50
Mullard LP 1171	AM/FM module	4.50
Mullard LP 1179	AM/FM front end	4.85
Mullard LP 1185	10.7 MHz IF unit with data	4.50

FM & AM TUNERS & DECODERS

FMS231 (TU2)	6 volt FM tuner	7.95
TU3	12 volt version (FM use with Decoder)	7.95
SD4912	Stereo Decoder for TU3 12 volt	7.95
SP62H	6 volt stereo FM tuner	11.95
A1007	9 volt MW-AM tuner	4.80
Sinclair	12/45 volt FM tuner stereo recorder for above	7.45
A1018	9 volt FM tuner in cabinet	13.95
A1005M (S)	9-12 volt Stereo decoder FM for above	7.50
1067	12V Stereo decoder gen. purpose	6.50
Garler	Permeability FM tuner (front end) 10.7 MHz O/P	4.20

PREAMPLIFIERS

Sinclair	Stereo 60 Preampifier	6.75
E1300	Cart/Tape Mic Inputs 9 volt	2.85
E1310	Stereo 3-30 mV Mag cart 9 volt	4.75
FF3	Stereo 3 mV tape head 9 volt	4.95
3402	Stereo 5-20 mV Mag cart mains	5.95
EQ25	Mono 3-250 mV Tape/Cart/Play 9 volt	5.95

POWER SUPPLIES MAINS INPUT

(*chassis-rest cased)		
470C	6.7/1.9V 300MA with adrs	2.25
PS50	9V 500 MA	3.20
HC24R	3/6/7/9V. 400 MA stabilised	5.50
*P11	24V 1A 3.30	3.30
*P15	28V 1A	3.30
*P1080	12V 1A 4.70	7.80
*P1081	45V 0.9A	7.80
P12	4-12V. 0.4-1A	7.15
SE101A	3/6/9/12V 1A stabilised	12.75
P1076	3/4/6/7/9/12V. 1A	4.20
SE800A	1-15 VOLT 0-1A stabilised	17.50

EMI SPEAKERS SPECIAL PURCHASE

13in x 8in chassis speakers (Carr packing 30p each or 50p per pair).
 *150TC 10 watts 8 ohms twin cone £2-20
 EW 15 watt 8 ohm with tweeter £5-25
 350 20 watt 8.15 ohm with tweeter £7-80 each
 * polished wood cabinet £4-80 carr. etc. 35p each or 50p pair.



UHF TV TUNERS

625 line receiver UHF transistorised tuners. UK operation. Brand new (Post packing 25p each).
 TYPE C variable tuning £2-50
 TYPE B 4-button push-button (adjustable) £3-50

PA DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses etc. etc.
 FREE stock lists (Ref. No. 18) on request. CALL IN AND SEE FOR YOURSELF AT HENRY'S DISCO CENTRE, 309 EDGWARE ROAD, TEL. 01-723 6963

TEST EQUIPMENT MULTIMETERS

(Carr. packing 35p)

U4324	20kΩ/V with case	9-25
U4325	20kΩ/V with steel case	8-75
U4313	20kΩ/V with steel case	12-50
U4317	20kΩ/V with case	16-50
U4341	33kΩ/V plus transistor steel case	10-50
U4323	20kΩ/V plus 1kHz OSC with case	7-70
IT1-2	20kΩ/V slim type	5-95
THL33D (L330V)	2kΩ/V Robust	7-50
TP55N	20kΩ/V (Case £2)	8-25
TP105	2kΩ/V	6-25
TW45	20kΩ/V	10-00
TW50K	50kΩ/V	11-25
EP10KN	10kΩ/V	9-95
S100TR	100kΩ/V plus transistor tester	22-50



NEW REVOLUTIONARY TESTER 880R

880R	Multi-tester	18-50
TE10	AC Multivoltmeter	19-75
TE15	Grid dip meter 40kHz-28MHz	19-50
TE65	28 Range valve volt-meter	22-50
TE20D	RF Generator 120kHz-500MHz	18-95
TE22D	AF Generator 20Hz-200kHz	19-95
*HM350	in circuit transistor tester	19-50
*C3025	Deluxe meter 1-300MHz	6-95
*T145	Compact transistor tester	14-75
TG3-36	R/C osc. 20Hz-200kHz	19-75
*C302	SWR Meter	5-75
*SE30A	Deluxe signal tracer	12-95
*SE400	Mini-lab. all in one tester	15-50
C1-5	Scope 500,000kHz (carr. £1)	43-00
*C3043	5 CH F/A meter 1-300MHz	5-75
Resistance sub box (Post. etc)		2-40
Capacitor	10p	2-10
2A variable transformers (carr. £1)		6-55
Radio activity counter 0-10r (carr. £1)		9-97
Mains unit for above (carr. 50p)		3-75

TAPE HEADS

Marriot XRSP/17	1 Track High	2.50
Marriot XRSP/18	1 Track Med.	3.50
Marriot XRSP/36	1 Track Med.	5.00
Marriot XRSP/63	1 Track High	1.75
Marriot Erase Heads for XRSP 17,18,36 (XES11)		75
Marriot BX12E 343	3 Track	75
R/RP1	Record/Play	45
H/RP	Single Track Rec/Play	35
Bogen Type UL290	Erase	1.50
Miniature Stereo Cassette Rec/Play (P.P. 15p)		2.25

EXCLUSIVE 5 WATT IC AMPLIFIERS



Special purchase 5 watt output 8-16 ohm load, 30 volt max. d.c. operation, complete with data. Price £1-50 each or 2 for £2-85. Printed Circuit Panels 50p.

CALCULATORS

Sinclair	Cambridge Kit	£9.95 (inc. VAT)
Sinclair	Cambridge (Built)	£12.95 (inc. VAT)
Sinclair	Memory	£17.95 (inc. VAT)
Sinclair	Scientific	£19.95 (inc. VAT)



VAT 8% EXTRA ON ALL ITEMS

SEND NOW FOR OUR NEW FREE LIST NO. 36 FOR OUR COMPLETE RANGE OF OVER 10,000 SEMI-CONDUCTOR DEVICES AT NEW LOW PRICES.

TTL '7400 series' I.C.'s from 16p each.
 Cosmos '4000 series' I.C.'s from 11p each.
 Linear op-amps from 40p each.
 Signonics phase lock I.C.'s.
 RCA linear I.C.'s.
 TO3 power devices in PNP and NPN.
 BC107 and 'BC range' from 12p.
 Range of 'OC' types.
 Plastic power devices, rectifiers, zener diodes up to 10W.
 Power regulator I.C.'s and many others.
 8-pin DIL sockets 14p
 14-pin DIL sockets 15p
 16-pin DIL sockets 17p
 705 I.C. sockets from 40p
 24-pin DIL sockets £1.15
 28-pin DIL sockets £1.25

NOMBREX TEST EQUIPMENT

Model 35 Stabilised Power Supply
 A short circuit proof power supply delivery up to 30V at 1A. Built-in Volts and ammeters. **£23.60**

Model 40 Wide Range Audio Signal Generator
 A high stability signal generator using the low distortion Wien bridge principle. Covering 10Hz to 100kHz in 4 ranges. Adjustable output from 1mV to 1V. Sine and square wave output. **£25.90**

Model 41 RF Signal Generator
 Covering 150kHz to 220MHz in 8 ranges. Built-in in AM mod. Output up to 50mV. Crystal calibration facilities. Large linear scale with slow motion drive. **£35.00**

Model 42 Wide Range RF Signal Generator
 Covering 150kHz to 300MHz in 8 ranges. Highest range in harmonic. Built-in AF mod. Output up to 50mV. Circular scale. **£17.50**

Model 43 RC Bridge
 Null indicating bridge for resistors and capacitors. Resistance range 10R to 10M ±2% at centre scale. Capacity range 10µF to 100µF ±2% centre scale except 1µF to 10µF range ±5%. Power factor measurement 0-70%. **£16.50**

Model 44 Inductance Bridge
 Measures 1µH to 100H in 4 ranges ±5% accuracy. Q measurement from 0.1-1,000 ±10%. **£27.50**

Model 45 Direct Reading Frequency Meter
 10Hz to 100kHz in 4 ranges. Input from 10MV to 5V. **£28.90**

All models except Model 35 are internally powered from 9V battery (extra). Carriage and packing all models 37p.

NOW OPEN SUPERMARKET

Come and browse round the new components supermarket at 404 Edgware Road. Bargains galore. Goodie bags. Components, etc.
 WATCH FOR FURTHER DEVELOPMENTS!

Henry's Radio

Electronic Centres
 404-406 Electronic Components & Equipment 01-402 8381
 309 PA-Disco-Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 303 Edgware Road London W2 1BW
 Prices correct at time of preparation. Subject to change without notice. E. & O. E

Hi Fi and Electronics Centres Open 9 am - 6 pm