

PRACTICAL

ELECTRONICS

NOVEMBER 1976

40p

PE ORION F.M. STEREO TUNER



HIGH PERFORMANCE STEREO RECEPTION
PRESET TUNING... INEXPENSIVE-EASY TO BUILD

**SPECIAL
OFFER!**




**Soldering
Kit**

Also inside...

**HAZARD
FLASHER**

and
DISCOSTROBE

NEW ELECTRONIC MASTER KIT

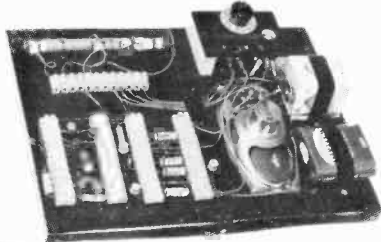

Another completely solderless Electronic Construction Kit with many more projects, including transistor radios of various types and wavebands. Amplifiers, metronome, sound amplifier, transistor tester, signal generator, quick check component tester, tuners, crystal set, morse code practice oscillator with morse key, AF oscillator, etc. Also a special project VHF aircraft receiver!

£14.99 Complete kit of parts including construction plans. Post, packing and insurance.

And all these components: 2 interchangeable control panels (ready drilled); 4 solderless construction boards (ready drilled); large 13 x 9 1/2 in. baseboard (ready drilled); ready-wound medium wave, long wave, short wave and VHF coils; 7 in. ferrite rod; quality 5 x 3 in. loudspeaker; crystal earpiece. Also: knobs, dial, wire, sleeving, capacitors, resistors, transistors, battery straps, connector clips, screws, nuts and bolts, potentiometers, tuning capacitors, instruction manual and pictorial diagrams.

V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the long wave band and operating as shown in the instructions supplied free with all parts.

Use a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. All parts including case and plans

£3.95 P.P. & Ins. 45p



NEW ROAMER TEN MODEL RK3

MULTIBAND V.H.F. AND A.M. RECEIVER.

13 TRANSISTORS AND FIVE DIODES. QUALITY 5' x 3' LOUSPEAKERS.


WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. And Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc.. Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P. P. 9 volt Battery.

Complete kit of parts including carrying strap, Building Instructions and **£13.99** Operating Manuals.

£13.99

Inc. P. & P.

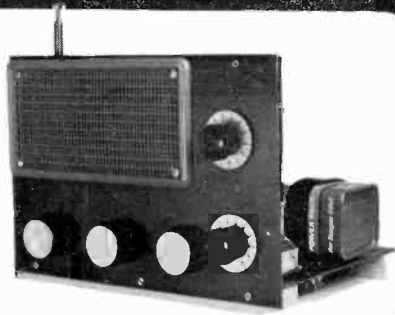Case enclosure kit (if required), £1.80 inc. P.P. and Ins.




POCKET FIVE

Now with 3in Loudspeaker

3 tunable wavebands: MW, LW and trawler band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2 in x 1 1/2 in x 3 1/2 in approx.

Complete kit of parts including construction plans.

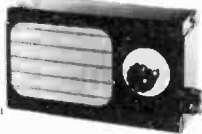Total P.P. and Building Costs: **£4.50** P.P. and Ins. 60p




TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 tunable wavebands: MW, LW, SW1, SW2, SW3 and trawler band. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker.

Complete kit of parts including construction plans

£7.50 P. & P. + Ins. 70p

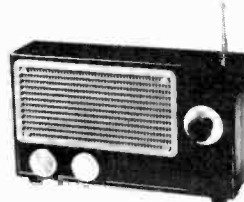


ELECTRONIC CONSTRUCTION KITS

E.C.K. 2 Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 3in loudspeaker, gain control, superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

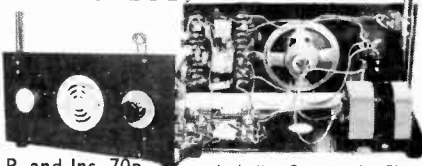Complete kit of parts **£7.95** P.P. and Ins. 70p




Including Construction Plans

E.C.K. 4

7 Transistors, 6 tunable wavebands, MW, LW, Trawler Band. 3 Short Wave Bands. Receiver Kit.

With 5in x 3in loudspeaker. Push pull output stage, gain control, and rotary switch. 7 transistors and 4 diodes. 6 section chrome-plated telescopic aerial. 5in sensitive ready wound ferrite rod aerial, tuning capacitor, resistors, capacitors, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

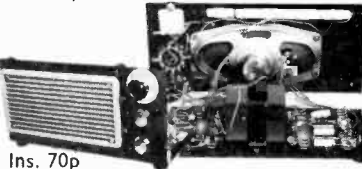Complete kit of parts **£7.25** P.P. and Ins. 70p



Including Construction Plans

ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT


6 tunable wavebands: MW, LW, SW1, SW2, trawler band plus an extra medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in approx.

Complete kit of parts including construction plans

£7.10 P. & P. + Ins. 70p

EDU-KIT MAJOR

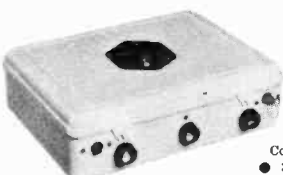COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN—PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One-Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier,

Components include: ● 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3 1/2" Loudspeaker ● Earpiece ● Mica Baseboard ● 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6 1/2 yards of wire ● 1 yard of sleeving, etc.

Complete kit of parts including construction plans

£9.00 Total building costs. P.P. and Ins. 85p

RADIO EXCHANGE LTD.,

61A HIGH STREET, BEDFORD MK40 1SA

Tel: 0234 52367

REG NO. 788372

- Callers side entrance "Lavells" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

I enclose £.....for.....

Name

Address

.....

..... PE11/76

PRACTICAL ELECTRONICS

VOLUME 12 No. 11 NOVEMBER 1976

CONSTRUCTIONAL PROJECTS

- P.E. ORION TUNER—1** *by D. S. Gibbs & I. M. Shaw*
Circuit details, specifications and components list for this high performance design 868
- HAZARD WARNING FLASHER** *by C. J. Coker*
A simple design suitable for fitting to any car 874
- DISCOSTROBE** *by A. Briar*
A four-channel light show controller offering a choice of three effects 888
- CINE/TAPE SYNCHRONISER—2** *by N. V. Davies*
Construction and operation, plus interface details for various projector types 896

GENERAL FEATURES

- SEMICONDUCTOR UPDATE** *by R. W. Coles & B. Cullen*
A look at some recently released devices 883
- INGENUITY UNLIMITED**
Accenting Metronome—Programmable Logic Generator—Touch Dimmer—15Hz Flasher—
"Pip" Tone Generator—Counter—Patch Panel—Phase Comparator—Traffic Light Controls—
Signal Injector/Tracer 902

NEWS AND COMMENT

- EDITORIAL**—How to succeed 867
- NEWS BRIEFS**
Transatlantic Microprocessor Link 873
- READOUT**
A selection of readers' letters 876
- BRITISH MUSICAL INSTRUMENT TRADE FAIR** *by G. Godbold*
A look at some of the latest trends from the music industry 878
- SPACEWATCH** *by Frank W. Hyde*
Return to the Moon—Drought and the Sun 880
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 884
- POINTS ARISING**
Cross-Hatch Generator—Digital Frequency Meter 887
- BOOK REVIEWS**
Selected books we have received 887
- VAT AND COMPONENTS**
The latest VAT information issued by H.M. Customs and Excise 914
- SPECIAL P.E. OFFER**
A pre-release introductory soldering kit offer including the new Adcola safety approved iron.
Exclusive to P.E. readers 877

Our December issue will be published on Friday, November 12, 1976
(for details of contents, see page 887)

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All mail orders and callers to this address please—callers only to 21 Deptford Broadway, SE8 (Tel. 01-692 2009) and 38 Lower Addiccombe Road, Croydon

NEW 44 PAGE CATALOGUE TOP + LARGE S.A.E.

Free with orders over £2

DIGITAL I.C.s

7400 12p	7450 15p	7495 73p
7401 14p	7451 14p	7496 85p
7402 14p	7453 14p	7407 37p
7404 17p	7454 14p	74121 36p
7405 23p	7460 14p	74122 51p
7406 28p	7472 28p	74123 64p
7408 14p	7473 28p	74132 58p
7410 13p	7474 28p	74150 173p
7413 28p	7475 51p	74154 144p
7414 62p	7476 28p	74155 73p
7420 14p	7483 81p	74157 66p
7430 14p	7486 40p	74159 280p
7432 18p	7490 40p	74174 118p
7437 18p	7491 75p	74179 120p
7440 15p	7492 52p	74180 120p
7447 64p	7493 52p	74367 120p

DIL. Sockets—8 pin 12p; 14 pin 13p; 16 pin 14p, 100 + less 25%.

LINEAR I.C.s

741 25p; 555 48p; 723 (T099) 50p
Plastic Voltage Regulators:
TO128 case 5V 600mA 80p, 12V 500mA 80p

TRANSISTORS

AC127 15p	BD131 38p
AC128 15p	BD132 40p
AC176 18p	BFY50 15p
AC187 18p	BFY51 15p
AC188 18p	BFY52 15p
AD161 35p	TIP41A 98p
AD162 35p	TIP42A 78p
BC107 10p	TIP2955 96p
BC108 10p	TIP3055 42p
BC109 10p	2N2219 22p
BC109C 15p	2N2369 28p
BC147 10p	2N2646 42p
BC148 10p	2N2928G 12p
BC149 10p	2N3053 18p
BC150 10p	2N3054 48p
BC151 10p	2N3055 38p
BC155 10p	2N3440 54p
BC159 10p	2N3442 £1.20
BC161 18p	2N3702 10p
BC182 12p	2N3703 18p
BC183 12p	2N3704 18p
BC184 12p	2N3705 10p
BC212 14p	2N3708 10p
BC213 14p	2N3819 22p
BC214 14p	2N4059 10p
BCY70 15p	2N4418 10p
BCY71 15p	2N5294 30p
BCY72 15p	40673 50p

DIODES AND LEDs AND SCR's

500V 5A SCR 45p; 400V 2A Triac 80p;
Diac BR100 25p; 400V 15A Triac £1.50;
ORP12 45p; MRD450 40p; TIL209 Red
LED 15p; 0.2in LED Red 22p; green,
Yellow or amber 24p
1N4002 5p; 1N4004 6p; 1N4007 8p;
1N4148 4p; BY127 12p; 100V 3A 12p;
400V 3A 18p; OA91 5p; OA91 5p
50V 1A bridge 22p; 800V 1A 40p;
250V 2 1/2A 40p; 200V 5A 70p; 500V 6A £1.60.
50V 30A rect. + or - stud 40p
Zeners—400mW BZY88. All voltages
from 3V to 30V 16p
1.3W plastic from 3V to 200V 28p

RESISTORS

Carbon film 5% 1/4W miniature. All values
in E12 series from 1Ω to 10MΩ (over
1MΩ 10%) 1 1/2p each.
Metal film 5% 1W. All values in E12
series from 27Ω to 10MΩ 2 1/2p.
Sub-min presets, vert. or horiz. all
values from 20Ω to 4MΩ, 7p.
Standard pots, lin or log, 22p.
Wirewound 2 1/2W 0.25, 0.33, 0.47 1Ω 8p.
Wirewound 5W all values from 1Ω to
47k 19p each.

TRANSFORMERS

0-0-30V 100mA 80p; 9-0-9V 100mA 85p;
12-0-12V 50mA 80p; 12-0-12V 100mA
£1; 12-0-12V 1A £2.80; 200V 55mA 90p;
22V 100mA £1; 28V 50mA 85p; 6-3V
1 1/2A £1.85; 0-0-6V 1 1/2A £2.30; 12V
150mA 80p; 17V 1A £1.80; 25V 1 1/2A
£2.30; 30-0-30V 1A £3.70.
Multitapped types to give 3, 4, 5, 6, 8,
10, 12, 15, 18, 20, 24 or 30V, or
12-0-12 or 15-0-15V, 1A version
£3.20, 2A version £4.50; 16V 20A
£8.50. Bell transformer in white
case, gives 4, 8 or 12V 1A £2.55-0.55V
5A £8.50.

See Practical Wireless for details of packs of components, surplus goods, etc. All prices quoted include VAT. Add 20p postage on orders under £2. Most orders despatched on day of receipt. SAE with enquiries. Send 10p for Multimeter catalogue—free on request on orders over £3. Official Orders accepted from Schools, etc. Export/wholesale enquiries welcome. Surplus components always wanted.

REEDS

1in Inserts, 5p; 10/40p; 100/£3.50. DIL relay, 3-7-10V, £2.28.

WIRE

Enamelled copper wire on 2oz reels
SWG/price: 18/32p, 18/34p, 20/36p,
22/38p, 24/40p, 26/42p, 28/44p, 30/46p,
32/48p, 34/50p, 36/52p, 38/54p, 40/56p.

RF CHOKES

0.75, 2-95, 6-6, 10, 22, 47μH, all 10p
each; 1.5, 2.5, 5-0, 7.5, 10mH, all
30p each.

CAPACITORS

Ceramic plate, 22pF to 1,000pF 2p;
polyester 1,000 to 6,800pF 5p; 0.01,
0.015, 0.022, 0.033, 0.047, 0.068, 0.1mF
4p; 0.15, 0.22mF 5p; 0.33 6p; 0.47 8p;
0.68 10p; 1mF 12p; 2.2mF 16p; 3.3mF
24p, 1,000pF feedthrough 5p.
1%: 1,000pF, 10,000pF 15p; 0.1μF, 0.2μF,
0.25μF 30p; 2.2μF 65p.
Polystyrene 10pF to 1,000pF 4p; 1,200pF
to 10,000pF 6p, All 2 1/2p.

Electrolytics:

All: 25V: 0.47, 1, 2.2, 4.7, 10, 22, 47mF
8p; 100mF 7p; 220mF 8p; 470mF 11p;
1,000mF 18p; 2,200mF 27p; 40V: 47mF
7p; 100mF 8p; 220mF 10p; 470mF 18p;
1,000mF 22p; 2,200mF 48p.
Tantalum bead, mF/V: 0.1/35; 0.22/35;
0.33/35; 0.47/35; 1/35; 2.2/16; 2.2/35;
3.3/35; 4.7/35; 6.8/35; 10/16; 10/25; 15/10;
22/6.3; 22/10; 22/16; 33/10; 47/6.3; 100/3.
12p each.

VEROBOARD

100 sq.in good size offcuts. Mixed, or
all 0-1 £1.30, £3.46/lb, 10lb £38; 17 x
3 1/2in x 0.1 sheets £1.96.

ALUMINIUM BOXES

Complete with base and PK Screws.
AB7 133 x 70 x 38mm 50p
AB8 102 x 102 x 38mm 50p
AB9 102 x 70 x 38mm 47p
AB10 102 x 133 x 38mm 50p
AB11 102 x 64 x 51mm 47p
AB12 76 x 51 x 25mm 44p
AB13 152 x 102 x 51mm 85p
AB14 178 x 127 x 64mm 85p
AB15 203 x 152 x 76mm £1.50
AB16 254 x 178 x 76mm £1.80
AB17 254 x 114 x 76mm £1.50
AB18 307 x 128 x 76mm £1.75
AB19 307 x 203 x 76mm £2.00
AB23 102 x 102 x 64mm 80p
AB24 133 x 102 x 64mm 90p
AB25 152 x 102 x 76mm £1.00

VEROBXES AND CASES


Professional 2 part boxes made of dark
and light grey high impact polystyrene.
2518 120 x 65 x 40mm £1.90
2520 150 x 80 x 50mm £2.15
2522 188 x 110 x 60mm £2.85
Sloping front version, ideal for mixers
2523 220 x 174 x 100/52mm £4.95
Cases, white plastic top and bottom,
front and back aluminium panels that
slot in. Type:
1410 205 x 140 x 40mm £2.80
1411 205 x 140 x 75mm £3.25
1412 205 x 140 x 110mm £4.20
1237 154 x 85 x 40mm £1.80
1238 154 x 85 x 80mm £2.25
1239 154 x 85 x 80mm £2.75
Small general purpose plastic boxes:
1413 7 1/2 x 40 x 24mm 32p
PB1 115 x 75 x 36mm 42p

DEVELOPMENT PACKS

Save ££££s by buying a full range of
components at one go! All full spec.
marked devices, no rejects or old stock.
50V ceramic plate capacitors 5% 10 of
each value, 22pF to 1,000pF. Total 210
capacitors £2.70.
CR25 carbon film resistors, 1/2 watt 5%
10 of each value 10Ω to 1MΩ, total
610 £8.00.
Extended range, 1 ohm to 10M 850
resistors £8.30.
Electrolytics, wire ended 25V working
10 each of: 1, 2, 4, 7, 10, 22, 47 and
100mF 70 capacitors for £3.20.
Zeners, 400mW 5% BZY88, 10 each
3V to 30V total 260 £14.00.
1/2 pack, 5 of each value £3.20.
Tantalum Bead caps, 14 values from
0.1/35 to 100/3, 10 of each total 140
caps £12.00.

Dimmit

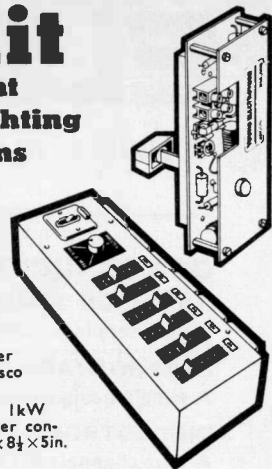range of light
dimmers and lighting
control systems



Illustrated is the popular
PMSD1000 module. A 1kW slider
control dimmer, interference sup-
pressed, 60mm slider range size
4 1/2 x 2 x 1 1/2in. Ideal for low cost
theatre and disco lighting. Used by
schools, theatres, studios, etc.
Complete with scale plate, fixing
screws and full instructions. £9.00
inc. VAT and postage and packing.

Complete compact light dimmer
systems for stage, club and disco
lighting, etc.

DD61M (illustrated). Six 1kW
channels, 15 outlet sockets, master con-
trol, mains on/off switch, size 23 x 8 1/2 x 5in.
Price £140-40 inc. VAT.

DD61-B. Six 1kW channels, using module
PMSD1000, lowest cost system. Size 16 1/2 x 8 x 5in. Price £64-50 inc. VAT.

DD62M. As DD61M but with six 2kW channels, size 25 x 10 1/2 x 6in.
Price £205-20 inc. VAT.

Add £2-20 postage and packing for all systems.

The Dimmit range includes rotary and slider control dimmers and
sound to light converters for home, entertainment and professional
applications. Ratings 1kW, 2kW, 3kW.

All products are guaranteed and are supplied with full instructions
and applications. Full after-sales service. Technical advice given.



For full information on all modules and lighting control systems send
for our FREE illustrated catalogue and price list. Callers welcome, visit our
showroom for a demonstration of any of the modules or systems. Mon.-Fri.
9.30 to 6.0 p.m. Sat. by arrangement.

YOUNG ELECTRONICS LTD.

184 Royal College Street, London NW1 9NN Tel. 01-267 0201

SINE WAVE OSCILLATOR

FROM THIS
S-DeC

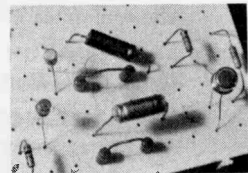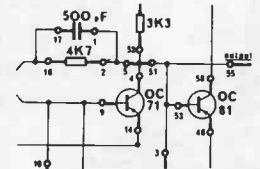

MAKE THIS

Simplify circuit design. Use S-DeC. Sockets in plastic frame are connected in
prearranged pattern. To build circuit, simply plug in components.
Afterwards, unplug components ready to build more circuits. Use same
components again and again.

Every S-DeC comes complete with step-by-step instructions, free control
panel, and booklet with nine circuits you can build. Sine wave oscillator,
radio receiver, binary counter, VHF radio microphone—they're all easy with
S-DeC (see free booklet for circuits and instructions).

Send cheque/P.O. now and start designing the easy way, with S-DeC. Each
S-DeC costs only £1.88 plus 37p post, packaging and VAT.

Please rush me.....S-DeCs so that I can start designing circuits the
easy way. I enclose a cheque/P.O. for £.....

Name

Address

PB Electronics (Scotland) Ltd

57 High Street, Saffron Walden, Essex CB10 1AA

Telephone: Saffron Walden (0799) 22876

BI-PAK **NEW** Order yours NOW!

OUR 1977 ILLUSTRATED CATALOGUE

The most comprehensive range of products and technical information ever, including **OVER 800 ADDITIONS** to our list of Semiconductors and Electronic Components. Fully illustrated and designed to be updated as we increase our range. This is **A MUST FOR ALL!** Order NOW. . . .

EVERY COPY CARRIES
A SPECIAL
DISCOUNT ORDER FORM!



GP300

115 WATT SILICON TO3 METAL
V_{ceo} 100V. V_{ceo} 80V. IC 15A.
replacement for 2N3055, BDY11
1-24 25-99
50p 48p

GP Switching

TO: 8 SIM. TO 2N106. 8 BS227 (285)
All usable devices. No open and short
AVAILABLE IN PNP similar to 2N2222
20 for *80p. 50 for *41. 100 for *41. 500
1,000 for *41.
When ordering please state NPN or PNP

WORLD SCOOP!!

APPROX. 200 PAGES
Assorted full-out integrated circuits
Logic, 74 series, Linear, Audio
Many coded devices but some un-
to identify.

OUR SPECIAL PRICE

P&P

Postage and Packing add 25p unless
otherwise shown. Add extra
airmail. Minimum order £1.

★ Indicators

3015F Mintron 7 Segment Indicator £1.10

L.E.D. DISPLAYS

DL707 Common anode 0.3" 85p. DL747
common anode 0.8" £1.70. DL727 Double
Display, common anode 0.5" £2.00

L.E.D.'s

Available in 0.125" and 0.2" dia lenses
RED 10p. GREEN 17p. YELLOW 17p.

★ 74 Series

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL
FAMOUS MANUFACTURERS

Type	1	25	100+	Type	1	25	100+	Type	1	25	100+
7400	0.09	0.09	0.08	7448	0.00	0.78	0.78	74122	0.50	0.48	0.48
7401	0.10	0.09	0.08	7450	0.12	0.11	0.10	74123	0.50	0.50	0.54
7402	0.11	0.10	0.09	7451	0.12	0.11	0.10	74141	0.60	0.58	0.58
7403	0.11	0.10	0.09	7453	0.12	0.11	0.10	74145	0.60	0.94	0.92
7404	0.13	0.12	0.11	7454	0.12	0.11	0.10	74150	£1.30	£1.25	£1.20
7405	0.13	0.12	0.11	7460	0.12	0.11	0.10	74151	0.78	0.74	0.72
7406	0.20	0.24	0.23	7470	0.25	0.24	0.23	74153	0.95	0.93	0.91
7407	0.25	0.24	0.23	7472	0.22	0.21	0.20	74154	£1.50	£1.45	£1.40
7408	0.15	0.14	0.13	7473	0.20	0.24	0.22	74155	0.80	0.78	0.76
7409	0.15	0.14	0.13	7474	0.27	0.25	0.23	74156	0.80	0.78	0.76
7410	0.09	0.09	0.08	7475	0.48	0.48	0.44	74157	0.95	0.93	0.91
7411	0.23	0.22	0.21	7476	0.25	0.24	0.23	74160	£1.00	0.98	0.96
7412	0.26	0.25	0.24	7480	0.50	0.48	0.46	74161	£1.00	0.98	0.96
7413	0.26	0.25	0.24	7481	£1.02	£1.00	0.98	74162	£1.00	0.98	0.96
7416	0.28	0.27	0.26	7482	0.50	0.51	0.50	74163	£1.00	0.98	0.96
7417	0.28	0.27	0.26	7483	0.60	0.96	0.94	74164	£1.25	£1.20	£1.15
7420	0.12	0.11	0.10	7484	0.00	0.98	0.96	74165	£1.25	£1.20	£1.15
7422	0.28	0.27	0.26	7485	£1.25	£1.20	£1.15	74166	£1.48	£1.44	£1.39
7423	0.30	0.28	0.26	7486	0.32	0.30	0.29	74174	£1.00	0.95	0.90
7425	0.30	0.28	0.26	7489	£2.00	£2.00	£2.70	74175	0.95	0.93	0.91
7426	0.30	0.28	0.26	7490	0.37	0.35	0.33	74176	£1.18	£1.11	£1.00
7427	0.30	0.28	0.26	7491	0.50	0.51	0.56	74177	£1.18	£1.11	£1.00
7428	0.42	0.38	0.36	7492	0.43	0.42	0.41	74180	£1.10	£1.11	£1.00
7430	0.12	0.11	0.10	7493	0.43	0.42	0.41	74181	£2.00	£1.00	£1.00
7432	0.30	0.28	0.26	7494	0.43	0.42	0.41	74182	0.90	0.88	0.86
7433	0.39	0.37	0.35	7495	0.70	0.60	0.60	74184	£1.07	£1.02	£1.58
7437	0.30	0.28	0.26	7496	0.60	0.60	0.64	74190	£1.50	£1.45	£1.40
7438	0.30	0.28	0.26	74100	£1.00	0.98	0.96	74191	£1.50	£1.45	£1.40
7440	0.12	0.11	0.10	74104	0.40	0.38	0.38	74192	£1.15	£1.10	£1.05

TRANSISTORS

AND NEW FULLY GUARANTEED

Type	Price	Type	Price	Type	Price
BF117	*0.40	BFY53	*0.13	OC75	*0.10
BF118	*0.71	BSY19	*0.10	OC76	*0.10
BF119	*0.71	BSX20	*0.10	OC77	*0.26
BF152	*0.36	BSY25	*0.10	OC81	*0.10
BF153	*0.46	BSY26	*0.10	OC81D	*0.10
BF154	*0.46	BSY27	*0.10	OC82	*0.10
BF155	*0.71	BSY28	*0.10	OC82D	*0.10
BF156	*0.40	BSY29	*0.10	OC83	*0.20
BF157	*0.36	BSY38	*0.10	OC139	*0.20
BF158	*0.36	BSY39	*0.10	OC140	*0.23
BF159	*0.01	BSY40	*0.20	OC169	*0.26
BF173	*0.15	BSY41	*0.20	OC170	*0.26
BF176	*0.30	BSY95	*0.13	OC171	*0.26
BF179	*0.31	BSY95A	*0.13	OC200	*0.26
BF180	*0.31	BU105	*1.00	OC201	*0.20
BF181	*0.31	MJE521	*0.50	OC202	*0.20
BF194	0.10	MJE2955	*0.88	OC203	*0.26
BF195	0.10	MJE3055	*0.57	OC204	*0.26
BF196	0.02	MJE3440	*0.51	OC205	*0.26
BF197	0.12	MPP102	*0.20	OC211	*0.44
BF198	0.12	MPP104	*0.20	ORP12/	
BF199	0.12	MPP105	*0.20	NSL4931	*0.48
F257	*0.20	OC19	*0.38	ORP80	*0.41
F258	*0.30	OC20	*0.00	ORP81	*0.41
F259	*0.46	OC22	*0.47	TIP29	*0.46
F262	*0.56	OC23	*0.49	TIP30	*0.45
F263	*0.50	OC24	*0.57	TIP31A	*0.52
F270	*0.36	OC25	*0.39	TIP32A	*0.60
F271	*0.31	OC26	*0.38	TIP41A	*0.65
F272	*0.01	OC28	*0.80	TIP42A	*0.75
F273	*0.30	OC29	*0.60	TIS43	*0.25
F274	*0.30	OC35	*0.65	UT46	*0.28
F275	*0.25	OC36	*0.57	ZTX107	*0.97
F276	*0.10	OC41	*0.20	ZTX108	*0.97
F277	*0.10	OC42	*0.25	ZTX109	*0.97
F278	*0.10	OC44	*0.18	ZTX300	*0.87
F279	*0.10	OC45	*0.13	ZTX500	*0.89
F280	*0.10	OC70	*0.10	2N696	*0.10
F281	*0.10	OC71	*0.10	2N697	*0.11
F282	*0.10	OC72	*0.15	2N698	*0.20
F283	*0.10	OC74	*0.15	2N699	*0.30

ONLY
50p
15p P+P

WORLD SCOOP!!

JUMBO SEMICONDUCTOR PAK
Transistors-Germ. and Silicon.
Rectifiers-Diodes. Triacs-Thyristors-I.C.'s and
Zeners. ALL NEW AND CODED.
Approx. 100 pieces only *1.85p.

ZENER DIODES
FULL RANGE IN STOCK, 2-33 Volts
400mW 8p 1.5W 17p 10W *38p

VAT CHAT

Please add 12½%
to prices marked*.
Remainder add 8%


VOLTAGE REGULATORS
TO 3 Plastic Encapsulation
µA.7805/L129 5V
(equiv. to MVR5V) £1.25
µA.7812/L130 12V
(equiv. to MVR12V) £1.25

BI-PAK
P.O. BOX 6, WARE · HERTS
SHOP 18 BALDOCK ST., WARE, HERTS.
AT OPEN 9 to 5.30 Mon/Sat. Tel: 61593

SYNTHESISERS, SOUND EFFECTS AND

PHONOSONICS

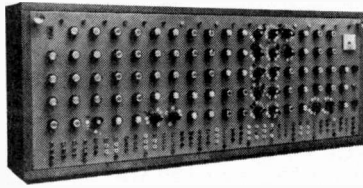MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.



COMPONENTS SETS include all necessary resistors, capacitors, semi-conductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs designed by Phonosonics.

PHOTOCOPIES of the P.E. texts for most of the kits are available—prices in our lists.

P.E. SYNTHESIZER

(P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesizer complete with keyboard circuits. All function circuits may be used independently, or interconnected. The greater the number of circuits, the greater the versatility. Other circuits in our lists may be used with the Synthesizer to good advantage (notably P.E. Minisonic, Phasing Unit, Wind and Rain, Rhythm Generator, Sound Bender, Voltage Controlled Filter, Guitar Effects Pedal).

THE MAIN SYNTHESIZER

- Stabilised power supply £12.05
- Two Linear Voltage Controlled Oscillators and one inverter—all 3 circuits £17.80
- PCB (2 are required) each £1.63
- Two Ramp Generators and Two Input Amplifiers all 4 circuits £5.92
- PCB (holds all 4 circuits) £1.51
- Sample-and-Hold and Noise Generator £7.95
- PCB (holds both circuits) £1.97
- Tone Control £2.68
- PCB 88p
- Reverberation Amplifier Sorine Line unit for Reverb. Amp. £5.50
- Ring Modulator £4.24
- Peak Level Meter Circuit £1.50
- 100µA Panel Meter £4.99
- PCB to hold Reverb, Ring Mod and Meter Circuits £2.14
- Envelope Shaper £6.04
- PCB £1.60
- Voltage Controlled Amplifier and Differential Amplifier £8.69
- PCB (holds both circuits) £1.45

THE SYNTHESIZER KEYBOARD CIRCUITS

- (Can be used without the Main Synthesizer to make an independent musical instrument)
- Two Logarithmic Voltage Controlled Oscillators Component set £15.28
 - PCB (holds both circuits) £2.86
 - Divider, 2 Hold Circuits, 2 Modulation Amplifiers, Mixer and 2 Envelope Shapers £21.88
 - PCB (holds the first 6 circuits) £1.98
 - PCB for both Envelope Shapers £1.70
 - Keyboard Stabilised Power Supply £7.61
 - Printed Circuit Board £1.04

GUITAR EFFECTS PEDAL (P.E. July 75)

- Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.
- Component Set with special foot operated switches £6.79
 - Alternative component set with panel mounting switches £4.90
 - Printed Circuit Board £1.43

SOUND BENDER (P.E. May 74)

- A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.
- Component Set for above functions (excl. SWs) £7.24
 - Printed circuit board £1.74
 - Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms. Component Set (incl. PCB) £2.76

PHASING UNIT (P.E. Sept. 73)

- A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.
- Component Set (incl. PCB) £2.85
- PHASING CONTROL UNIT (P.E. Oct. 74)**
For use with the above Phasing Unit to automatically control the rate of phasing.
- Component Set (incl. PCB) £4.25

WAH-WAH UNIT (P.E. Apr. 76)

- The Wah-wah effect produced by this unit can be controlled manually or by the integral automatic controller.
- Component Set incl. PCB £3.20

POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT.
Optional Insurance for compensation against loss or damage in post, add 35p in addition to above post and handling.
Ireland, C.I., B.F.P.O., and other countries are subject to Export postage rates.

P.E. JOANNA (P.E. May/Sept. 75)

A five-octave electronic piano that has switchable alternative voicing of Honky-Tonk piano, ordinary piano, harpsichord, or a mixture of any of the three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The power amplifier typically delivers 24 watts into 8 ohms. The PCBs have been redesigned by ourselves making improved use of the space available.

- Main Power Supply £10.09
- Tone Generator and Top C Envelope Shaper £10.61
- PCB for Main PSU, Tone Gen & Top C E.S. £2.31
- Envelope Shapers for all notes (except Top C) £37.68
- Set of PCBs for Envelope Shapers (except Top C) £11.88
- Voicing and Pre-Amp Circuits £10.53
- PCB for Voicing and Pre-amp £2.80
- Power Amplifier (incl. separate Power Supply) £15.06
- PCB for Power Amp and PSU 95p

RHYTHM GENERATOR (P.E. Mar./Apr. 74)

- Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, loud and short brushes, blocks and soft cymbal), and with variable time signatures and rhythm rates. Really fascinating and useful.
- Tempo, Timing and Logic circuits £12.68
 - PCB for above circuits (double-sided) £3.24
 - Component set for all 8 effects circuits £12.72
 - PCB for all 8 effects £3.70
 - Simple mixer (our design) incl. PCB £3.95
 - Alternative mixer with external volume controls, incl. PCB £10.94
 - Power Supply for T, T and L, and Effects, incl. PCB £7.10
- (See our list for Power Supplies for Mixers)

REVERBERATION UNIT (P.W. Nov./Dec. 72)

- A high quality unit having microphone and line input pre-amps, and providing full control over reverberation level.
- Component Set (excl. spring unit) £12.68
 - Printed Circuit Board £1.93
 - 9 in. Spring Unit £5.50
 - Panel Meter (50µA) (optional) £4.99

WIND AND RAIN UNIT

- A manually controlled unit for producing the above-named sounds.
- Component set incl. PCB £3.37

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

- Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.
- Component set using dual slider pot £6.57
 - Component set using dual rotary pot £5.80
 - Printed circuit board £1.37

FUZZ UNIT

- Simple Fuzz unit based upon P.E. 'Sound Design' circuit.
- Component set incl. PCB £1.98

TREMOLO UNIT

- Based upon P.E. 'Sound Design' circuit.
- Component set incl. PCB £3.19

TREBLE BOOST UNIT (P.E. Apr. 76)

- Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.
- Component Set incl. PCB £2.31

25 WATT MONO AMPLIFIER (P.E. Sept. 75)

- A good general purpose integrated circuit power amplifier typically delivering 25 watts into 8 ohms. Power bandwidth 20Hz to 20kHz, 3dB, input impedance 20kΩ. Distortion 0.2%. Suitable for use with any of our sound producing kits.
- Component Set incl. power supply £15.06
 - Printed Circuit Board 95p
- For stereo use two sets and PCBs are required.

DON'T FORGET YATI!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

P.E. MINISONIC MK 1

(P.E. Nov. 1974 to March 1975)

A portable, battery or mains operated, miniature sound synthesizer, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesizer, the functions offered by this design give it great scope and versatility. Like the large Synthesizer it too may be advantageously used with other circuits in our lists.

Oscillators and Voltage Controlled Filter now replaced by the Mk 2 version. Details in our list.

- Two Envelope Shapers and Two Voltage Controlled Amplifiers £9.07
- Keyboard Controller and Hold Circuits £2.84
- Keyboard Divider Resistors (select type to suit keyboard used) (all are 2% tolerance): 2 Octave £1; 3 Octave £1.48; 4 Octave £1.96; 5 Octave £2.44. £1.86
- H.F. Oscillator and Detector £1.86
- Ring Modulator, Noise Generator and Envelope Inverter £6.02
- Two Power Amplifiers and Two Mixers £4.28
- Battery Eliminator £6.69
- Temperature Stabiliser £1.54
- PCB to hold 2 ES, 2 VCAs, 2 Mixers, Ring Mod, Keyboard Control and Hold £2.42
- PCB to hold 2 Power Amps., Noise Gen., Envelope-Inverter, H.F. Osc and Detector £1.59
- PCB to hold Battery Eliminator and Temperature Stabiliser £1.48

P.E. MINISONIC MK 2

Conversion kits and PCBs for updating the MK 1 version are now available. Details in our list.

ENVELOPE SHAPERS

- Both of the kits below have manual control over their Attack, Decay, Sustain and Release functions. Both kits include PCB (VCA means Voltage Controlled Amplifier)
- Envelope Shaper and VCA (P.E. Apr. 76) £6.50
 - Envelope Shaper (without VCA) (P.E. Oct. 75) £4.62

VOICE OPERATED FADER (P.E. Dec. 73)

- For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.
- Component Set incl. PCB £3.74

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)

- An independently designed VCF that can be used with the P.E. Synthesizer.
- Component Set £3.67
 - Printed Circuit Board £1.38

P.E. TUNING FORK (P.E. Nov. 75)

- Produces 84 switch-selected frequency-accurate tones. An LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic and electronic musical instruments alike.
- Main Component Set incl. PCB £14.77
 - Power Supply set incl. PCB £6.95

P.E. SYNCHRONOME (P.E. Mar. 76)

- An accented-beat electronic metronome, providing duple, triple and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator. Includes power supply.
- Component Set incl. loudspeaker £10.68
 - Printed Circuit Board £1.70

PEAK LEVEL INDICATOR (P.E. Mar. 76)

- A twin-channel visual display unit for monitoring the peak level of audio signals. Well suited for use when inter-coupling our many sound producing kits to help avoid signal over-loading.
- Component Set incl. PCB (as published) £3.84

EXPORT ORDERS are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list for Europe send 20p, for other countries send 40p.

PHONOSONICS • DEPT. PE4N • 22 HIGH STREET • SIDCUP • KENT DA14 6EH MAIL ORDER AND C.W.O. ONLY SORRY BUT NO CALLERS PLEASE

OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.



LIST—Send Stamped Addressed Envelope with all U.K. requests for free list giving fuller details of PCBs, kits, and other components.

OVERSEAS enquiries for list: Europe—send 20p; Other Countries—send 40p.

KEYBOARDS AND CONTACTS

Kimbar-Allen Keyboards as required for many published circuits, including the P.E. Joanna, P.E. Minisonic, and P.E. Synthesiser. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C. The keys are plastic, spring-loaded and mounted on a robust aluminium frame.

3 Octave (37 notes) £23.10. 4 Oct (49 notes) £27.45. 5 Oct (61 notes) £32.10. Contact Assemblies for use with above keyboards: Single-pole change-over (type SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally open-make-break (type DP) as for P.E. Synthesiser. Special contact assembly (type 4PS) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables THE SAME KEYBOARD to be used with the P.E. Synthesiser, P.E. Minisonic and the P.E. Joanna simultaneously thus avoiding the cost of more than one keyboard.

Contact	Each	3 Octave Set	4 Octave Set	5 Octave Set
SP	22p	£8.14	£10.78	£13.42
DP	25p	£9.25	£12.25	£15.25
4PS	50p	£18.50	£24.50	£30.50

PRINTED CIRCUIT BOARDS for use with the above contacts and thus eliminating most of the inter-wiring required, are available. Details in our lists.

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)

The ever-popular Aurora—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A MUST for any Disco, and a fascinating visual display for the home.

4 Channel Component Set (excl. thyristors)	£14.42
8 Channel Component Set (excl. thyristors)	£25.75
Power Supply Component Set	£5.35
PCB for 4 frequency channels	£3.65
PCB for power supply and 8 lamp drivers	£1.70
1A 400V thyristors (1 per chan. req.) each	75p
Panel meter (1µA) (optional)	£4.99

3-CHANNEL SOUND-TO-LIGHT (P.E. Apr. 76)

A simple but effective sound-to-light controller capable of operating 3 lamps each of approximately 700 watts. Includes power supply, thyristors, and by-pass switches. Component Set incl. PCB

£11.18

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

Pre-Amp Module Component Set incl. PCB	£4.11
Basic Output Circuits—combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feed-back lamp-driver circuits	£5.95
Audio Amplifier Module Type PC7	£6.75

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs.

Standard Tolerance Set of Components	£2.85
Superior Tolerance Set of Components	£3.30
Regulated Power Supply (will drive 2 sets)	£4.69

SINE AND SQUARE WAVE GENERATOR (P.E. July 75)

Suitable for audio, digital, or general purpose. Controllable through 4 decade ranges 10Hz to 100kHz, switched attenuation through 10 ranges from 10V to 1mV peak-to-peak.

Component Set. While stocks last	£9.83
PCB for above components	£1.76
Power Supply	£6.21
PCB for Power Supply	£1.06

SEMI CONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor. While stocks last.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB	£8.86
Panel meter (500µA)	£4.99

P.E. MINIMIX 6 (P.E. Nov./Dec. 75)

Each of the 6 input channels has its own gain, volume and panning controls. The volume of the twin channel outputs are fully manually controllable, as are the headphone and pre-fade monitoring facilities. Twin VU meters provide visual display of channel audio levels. Ideal for use with effects and synthesiser kits. For details see our list. While stocks last.

8-INPUT MIXER

A simple mixer having 8 inputs each of which has a preset level control and which are combined into one output channel having a preset over-all level control and a master output volume control. Designed for inter-coupling our various sound effects and synthesiser kits. Component set incl. PCB

£3.95

PRICES ARE CORRECT AT TIME OF PRESS. E. & O.E. DELIVERY SUBJECT TO AVAILABILITY.

TRANSISTORS

AC128	20p
AC176	20p
BC107	14p
BC108	14p
BC109	14p
BC147	12p
BC148	12p
BC149	12p
BC157	13p
BC158	13p
BC159	13p
BC182L	12p
BC184	12p
BC187	25p
BC204	14p
BC209C	14p
BC212L	15p
BC213	15p
BC478	28p
BCY71	22p
BD131	44p
BD132	54p
BFY50	22p
BFY51	22p
BFY52	22p
BSY95A	22p
MJE295A	110p
OC28	60p
OC71	17p
OC72	25p
OC84	25p
ORP12	16p
ZTX107	12p
ZTX108	9p
ZTX501	13p
ZTX503	15p
ZTX531	23p
2N706	12p
2N914	22p
2N1304	22p
2N2219	27p
2N2905	35p
2N2905A	36p
2N2907	22p
2N3053	18p
2N3054	66p
2N3055	48p
2N3702	12p
2N3703	12p
2N3704	12p
2N3819	33p
2N3820	64p
2N3823E	39p
2N4060	12p
2N4871	36p
2N5245	51p
2N5777	45p

INTEGRATED CIRTS.

709 T05	40p
709 8-pin DIL	40p
723 T05	95p
741 8-pin DIL	32p
748 T05	63p
748 8-pin DIL	63p
µA7805 T0220	165p
µA7808 T0220	165p
µA7812 T0220	165p
µA7815 T0220	165p
µA7818 T0220	165p
AY-1-0212	622p
AY-1-6721/6	188p
CA3046	71p
MFC4000B	81p
SG3402N	220p

PHONOSONICS

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation. . .

Each of the 6 volumes of this self-instruction course measures 11½" x 8½" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers. Design of Digital Systems.



£6.20

plus 80p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic. Digital Computer Logic and Electronics

in 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4.20

plus 80p P. & P.

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises (Dept. ENG)
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR

*Please send me... set(s) of Design of Digital Systems at £7.00 each, p & p included

*or... set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included

*or... combined set(s) at £10.50 each, p & p included

Name

Address

*delete as applicable

No need to use a stamp—just print FREEPOST on the envelope. PE11

NOW-just when you need it most!

**BI-PRE PAK'S
ONCE-IN-A
LIFETIME**

SALE

**PACKS
COMPONENTS
MODULES
SUNDRIES
BOOKS**

**SEE
BELOW**

MANY ITEMS AT HALF PRICE AND LESS

PAKS DOWN FROM 60p TO 30p EACH

● **TESTED PAKS 30p each**

Pak No.	Contents
TP10	2 Light dependent resistors. 400 ohms light, 1 megohm dark. $\frac{1}{2}$ in dia.
TP11	10 Transistors XB102 & XB112 equiv. to AC126, AC156, OC812, OC72, etc.
TP13	5 OC771 Light sensitive transistors.
TP14	20 OC711 germanium PNP audio pre amp transistor, black glass type*
TP16	20 OC81 germanium PNP audio output transistor, white glass type*
TP17	20 1W zener diodes, mixed voltages, 6-8 to 43V*
TP20	10 Mullard OC45 transistors, I.F. amp PNP germanium.
TP21	30 Short lead ($\frac{1}{2}$ in approx) transistors. NPN silicon planer types. Ex radio manufacturer, all good but production line changes.
TP22	6 integrated circuits, 4 gates BMC962 and 2 flip flops BMC945
TP27	5 germanium PNP high frequency transistors, unmarked similar to OC170/171, AF115/6/7/3 lead TO-1.
TP28	5 2N918 UHF/VHF silicon transistors. NPN 4 lead TO-18 uncodded.
TP35	4 3B19E transistors, N channel FET's, these are 2N3819's in plastic cases.
TP38	8 integrated circuits, DTL data supplied. Mixed types flip flops*
TP40	15 Transistors, these are brand new manufacturers surplus items.

● **UNTESTED PAKS 30p each**

UT2	150 Germanium diodes, miniature glass type.*
UT3	100 Silicon diodes miniature glass type, similar to 1N4148.*
UT4	100 Silicon diodes, miniature glass type, similar to 1N9146.*
UT5	40 Zener diodes, 250mW OA2240 range, average 50% good.*
UT6	25 Zener diodes, 1- $\frac{1}{2}$ W top hat type, mixed voltages.*
UT7	30 Silicon rectifiers, 750mA BY100 type, top hat, mixed voltages.
UT10	15 Power transistors, PNP germanium and NPN silicon, mostly TO-3 but some plastic and some marked
UT11	30 OA47 gold bonded diodes, polarity marked.
UT12	10 2N3819 10 channel FET's plastic case type*
UT13	15 integrated circuits, experimenters pak, dual in line, 10-5 TTL, DTL, marked and unmarked, some definitely good but old types.
UT14	15 AC128 transistors, PNP germanium audio output.

● **COMPONENT PAKS at 30p each**

CP1	150 Capacitors, mixed bag of paper, silver mica electrolytics, etc. Approx quantity, counted by weight.
CP2	200 Resistors, mixed types and wattages, including H-stability. Approx. no. counted by weight*
CP5	5 Earphones, single low impedance for transistor radios, cassettes, etc. less plugs.*
CP7	25 Heat sinks, to fit SO-2 (OC72) and TO-1 (AC128) etc. 500 Cable clips for G.P.O. $\frac{1}{2}$ in dia. cable. Nylon with hardened steel pin (probably tungsten) per sealed box of 500
CP12	10 Reed relay inserts, $\frac{1}{2}$ in long $\frac{1}{2}$ in dia. These will operate from an external magnet or coil. For magnets see PAK CP13.
CP13	10 Magnets of various sizes for operating reed-switches in PAK CP12. Ideal for burglar alarms on doors and windows, etc.
CP16	5 P.C. boards each containing a BF180 UHF amplifier transistor. A good basis for building a T.V. aerial pre-amp as various parts inc.
CP17	25 Electrolytic Capacitors, various values and voltages, many useful types, from T.V. to transistor radio and Hi-Fi.
CP18	1 Light activated SCR 50V 1.6A type L9F. Ready mounted on P.C. board with gate resistor and leads fitted. Full data and circuit diagrams for 14 projects, includes slave photo flash unit, burglar alarm, etc.
CP19	3 Micro switches 1 pole change over, standard model $\frac{1}{2}$ in x $\frac{1}{2}$ in.
CP21	200 sq.in copper laminate P.C.B. in approx. 10 pieces.
CP23	4 miniature push-in to mike, single pole.

BUMPER I.C. PACK

50 I.C.s at one penny each!
50 assorted integrated circuits including many brand new marked devices

50p

MISCELLANEOUS—your chance to save pounds

PRINTED CIRCUIT PANELS (Ex Equipment)

TYPE L4, EX cash register board. Equipped with 8 x SN7490N decade counters, 11 x SN15849N quad 2 input NAND/NOR gate, 1 x SN7413 dual schmidt trigger
TYPE L5. A stabilised power supply board for I.C.'s equipped with 4 x SN7413N dual schmidt triggers, 1 x TVR2001 Zener I.C., 1 x 2N3738 power trans., various resistors and capacitors.

75p

UHF TUNER UNITS

We have sold thousands of these units brand new and made by a world famous manufacturer. Covers 625 line T.V. channels 21 to 65. Standard T.V. IF frequency output. Ideal for making a HI FI television sound receiver. **£1.50**

FIRST EVER! QUARTZ CRYSTAL PAK

Containing ten quartz crystals, 2-pin plug-in types. Easily dismantled from housing for regrinding to different frequencies. Add 10p per pack to postal charge.

50p

SUNDRY POST OFFICE (G.P.O.) ITEMS

EX G.P.O. telephone dials, as used in 700 and 300 type phones. Complete **35p**
EX G.P.O. telephone handsets with lead, black. (Additional P. & P. 25p) **40p**
EX G.P.O. buzzers, 12/24 volt operation, clean condition **20p**
EX G.P.O. push button key switches, 2 pole change over. Brand new **15p**
EX G.P.O. COUNTER UNITS 0000-9999. 10 per second (24-48v operation) **20p**

INSTRUMENT CASES

Beautifully finished in stove enamelled grey crackle, in heavy gauge aluminium with internal racking and heavy gauge panels (suitable as heatsinks). Ideal for P.A. systems, bench power supplies, oscilloscopes, metered instruments, etc. **BRAND NEW AND BOXED**
SIZE "A" 14" x 15" x 6" deep £5.50 + additional 75p for P/P
SIZE "B" 17" x 16" x 12" deep £8.50 + additional £1 for P/P

HIGH VOLTAGE (12KV) DIODES

Replacements for colour T.V. triplers, only 5 for 50p

ON-OFF ROCKER SWITCHES

2 pole 1 way push-fit mains type for hole size $\frac{1}{2}$ " x $\frac{1}{4}$ " each 15p

A FASCINATING AND UNUSUAL OFFER VARIABLE PRE-SET VOICE DECODERS

Brand new, but sold essentially for components 4 stages, 7 position control knobs. On 10" x 12" P.C.B. in plastic tray. Contains 35 I.C.s viz 8 x 7493, 5 x 7420, 7 x 7400, 4 x 7404, 2 x 7430, 2 x 7410, 2 x 7442, 2 x 7401, 1 x 7474 and 1 x 7490 (total 35) plus 35 transistors, 4 miniature rotary switches, voltage stabilizer and various other components. + additional 50p to Postal Charges

£4

+ additional 50p to Postal Charges

PUSH BUTTON SELECTOR ASSEMBLIES

for varicap tuning systems as used in VHF/FM radio receivers or UHF/TV tuners. With indicators on each stage.
4 button assemblies **£1.25***
4 button assemblies **£2.00***
7 button assemblies with A.F.C. switch.

STEREO DECODERS (FM)

I.C. operated units for use in negative earth systems. **£1.95***
Transistor operated unit for use in positive earth systems. **£1.75***
L.E.D.s can be added to the above.

12 RELAYS FOR ONLY £1

Ex G.P.O. and others, various voltages and coil impedances, non-specified. Add 35p per pack to postage charge.

9V D.C. MOTORS 75p

Speed stabilised, $\frac{1}{2}$ in. dia x $\frac{1}{2}$ in. plus spindle. Ideal for portable record or cassette players. Brand new, boxed.

TECHNICAL BOOKS

Dozens and dozens of titles by NEWNES-BUTTERWORTH, BARNES PRESS, BERNARD PUBLISHERS

All at **25%**

OFF PUBLISHERS PRICES
S.A.E. for list

VAT 8%

ON EVERYTHING EXCEPT ITEMS MARKED * AT 12 $\frac{1}{2}$ % Please add appropriate amount to total value of your order

MINIMUM ORDER for items sent by post £3 excluding VAT and postage

POSTAGE Please add 50p per P/P to all orders unless stated otherwise. Where additional postage and packing is quoted this is to be added to the basic 50p charge

ORDER WITHOUT DELAY—OFFERS CANNOT BE REPEATED—CALLERS WELCOME

BI-PRE-PAK

Originators of and first with component packs in U.K. and still leading

BI-PRE-PAK LTD

Dept PE/S

220-224 WEST ROAD, WESTCLIFF-ON-SEA
ESSEX SS0 9DF Telephone Southend (0702) 46344

SINTEL FOR KITS-CMOS-DISPLAYS-MEMORIES-BOOKS-MICROPROCESSORS

Components from leading manufacturers only

SINTEL

DATABOOKS and DATASHEETS (may be photocopies)

NEW 1976 RCA CMOS and Linear IC Combined Databook.....	£2-95
New 1976 RCA Databook on Power Transistors, SCR's, Thyristors, etc.....	£4-95
National Semiconductor 7400 series TTL Databook, c. 200 pages.....	£3-45
T.I. Pin-Out Card Index. Set of cards with pin-outs (top and bottom views) of T.I. TTL range and many other T.I. IC's.....	£2-95
Intel Memory Design Handbook, c. 280 pages.....	£4-75
Intel 8080 Microcomputer Systems Users Manual, c. 220 pages.....	£4-85
Motorola MC/MOS Databook, Vol. 3 Series A1 c. 500 pages.....	£2-77
Motorola M6800 Microprocessor Applications Manual, c. 650 pages.....	£12-45
Motorola M6800 Programming Manual, c. 200 pages.....	£8-85
Motorola Booklet introducing Microprocessors.....	£1-50
National SC/MP Introductory Users Manual.....	£0-75
National SC/MP Programming and Assembly Manual.....	£0-30
National SC/MP Technical Description.....	£1-85
2650 Microprocessor Manual 220 pp.....	£24-50
DATASHEETS on Microprocessors (usually Xerox Copies).....	£0-75
Intel 8080.....	£0-75
RCA CDP1802, 8 bit, CMOS.....	£0-35
National SC/MP, 8 bit, low cost.....	£0-75
Zilog Z80 (Enhanced 8080).....	£0-75
Signetics 2650, 8 bit, low cost.....	£0-75
Motorola MC6800.....	£0-75

FAST SERVICE We guarantee that telephone orders for goods in stock, received by 4.15 p.m. Mon.-Fri. will be despatched the same day First Class Post (books and kits by parcel post), and our stocking is good. Private customers should telephone order quoting their Access or Barclaycard number, with a minimum order value of £5. Official orders no minimum.

CMOS from the top manufacturers, mainly RCA and MOTOROLA

CD4000 0-18	CD4028 0-80	CD4053 0-87	CD4086 0-74	CLOCK CHIPS	
CD4001 1-16	CD4029 1-32	CD4054 0-89	CD4090 1-81	AY51202 2-89	
CD4002 0-18	CD4030 0-58	CD4055 1-37	CD4093 0-80	AY51224 3-50	
CD4006 1-22	CD4031 2-24	CD4056 1-37	CD4094 1-84	MK50250 5-00	
CD4007 0-17	CD4032 1-11	CD4057 27-95	CD4095 1-09	MK50253 5-80	
CD4008 0-85	CD4033 1-45	CD4059 4-88	CD4096 1-09		
CD4009 0-56	CD4034 1-22	CD4060 1-18	CD4097 3-87		
CD4010 0-56	CD4035 1-22	CD4062 0-87	CD4099 1-90	VEROCABS	
CD4011 0-17	CD4036 3-18	CD4063 1-14	CD4502 1-28	751610J 2-84	
CD4012 0-17	CD4037 3-06	CD4068 0-84	CD4510 1-41	751411D 3-04	
CD4013 0-58	CD4038 1-22	CD4067 3-87	CD4511 1-82	751237J 1-72	
CD4014 1-05	CD4039 3-09	CD4068 0-22	CD4514 2-85	751238D 2-15	
CD4015 1-05	CD4040 1-11	CD4069 0-22	CD4515 3-25		
CD4016 0-85	CD4041 0-87	CD4070 0-80	CD4516 1-41		
CD4017 0-80	CD4042 1-90	CD4071 0-22	CD4518 1-30	SUNDRY	
CD4018 0-99	CD4043 1-05	CD4072 0-22	CD4520 1-30	CA3130 1-14	
CD4019 0-86	CD4044 0-97	CD4073 0-22	CD4527 1-84	uA741 0-35	
CD4020 1-16	CD4045 1-45	CD4075 0-22	CD4532 1-90		
CD4021 0-85	CD4046 1-32	CD4076 0-22	CD4555 0-84		
CD4022 1-90	CD4047 0-94	CD4077 0-80	CD4556 0-84	SOLDERCON	
CD4023 0-17	CD4048 0-58	CD4078 0-22	MC14528 1-18	PINS	
CD4024 0-87	CD4049 0-56	CD4081 0-22	MC14553 5-24	100 0-50	
CD4025 0-17	CD4050 0-87	CD4082 0-22	IM6508 0-89	1,000 4-00	
CD4028 1-79	CD4051 0-87	CD4085 0-74			
CD4027 0-55	CD4052 0-97				

SINTEL

P.O. BOX 75B
OXFORD
Tel. 6965 49781



KITS

NEW



AUTOCLOCK "AUT-CK" £17-85

The SINTEL Autoclock is a four-digit car clock in an attractive mini white case. Features: large 0.5in red LED displays—High frequency quartz crystal timebase—an internal backup battery supplies power if the car battery voltage drops below nine volts when starting the engine, or if the clock is temporarily disconnected—only high quality components are used. Filter resistors, roller tinned fiberglass PCB's, etc. Full instructions included. Simple but sophisticated circuitry gives you good performance at low cost. You benefit from our experience in clock design.

- Complete kit/less battery—order as "AUT-CK"..... £17-85
- Also available less case—order as "AUT-MODULE KIT"..... £16-45
- Other Kits: For details see previous adds or Catalogue:.....
- "ACK" Advanced 6 digit alarm clock kit..... £26-90
- "GCK" 4 digit mini mantelclock (green displays)..... £12-90
- "XTK" 50Hz crystal timebase kit..... £8-28
- "ACK" + BBK + XTK..... £33-50
- "GCK" + GBBK + XTK..... £19-85

Send for **FREE CATALOGUE** giving details of our complete range of Clock kits, LED displays, Cases, and other components

memory ic's and microprocessors

Please: Microprocessors should only be bought by experienced constructors. Sorry, we cannot answer technical queries or supply data other than from our data selection.

IM6100CCDL.....	£58-00	6820.....	£17-87
8080A (2uS).....	£43-85	8224.....	£17-87
6803.....	£33-87	8224.....	£9-78
ISPA/500 (SC/MP).....	£18-75	8228.....	£12-16
2650.....	£27-00	8251.....	£17-87
		8255.....	£17-87

MPU'S

MEMORY IC'S
Intel 2102-8 (New version of 2102-2, 16 pin IC, TTL compatible. Single +5V supply. 6550mc. 1024 x 1 bit Static NMOS RAM..... £3-35
Intel 2112-2 6550mc. 256 x 4 bit Static NMOS RAM..... £4-78
Intel 6108 6550mc. 1024 x 1 bit Static RAM..... £8-05

SINTEL

Add 8% VAT + 25p P. & P. on all orders. Phone orders send "Fast service" for details. Export orders welcome, but you must contact us first for special order form and postage rates. OFFICIAL ORDERS WELCOME.

YES SIR 1st class post TONIGHT!
We specialise in high spec components with express service for phone customers



CRESCENT RADIO LTD.

164.166 HIGH ROAD, WOOD GREEN, N22
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4SJ
Phone: 888-4474

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Input connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound/light display. (All guaranteed.)

£18-50 plus 75p. P. & P. + 8%.

"C100" 100 WATT AMPLIFIER

All built and tested, mounted on a plain aluminium chassis which measures 18 x 9 1/2 x 4in, and which you can mount into a cabinet of your choice. Four controlled inputs, master volume, treble, middle and bass controls, S/C protected output. 100W clean into 8 ohm L/S. Ideal for disco, music groups, P.A. and clubs. A bargain at £42 + £1 carr. + 8% VAT.

TI MULTI-METER

Ideal tester for everybody interested in electronics. Weighing less than 100 grammes and only 60 x 24 x 90 mm. Ranges: A.c. volts: 0-10V, 50V, 250V, 1,000V. D.c. volts: 0-10V, 50V, 250V, 1,000V. D.c. current: 0-1mA, 0-100mA. Resistance: 0-150 kohm. Price £4-75 + 8% VAT.

TE-CLIP CONDENSER MICROPHONE

Omni-Directional 600 ohm 40-15,000Hz. Extra long lead. Ideal for stage work, conferences, etc. Price £8-50 + 12 1/2% VAT.

PPI POWER SUPPLY UNIT

Switched 3, 4, 6, 7, 9 and 12V at 500 mA. With on/off switch and pilot light. Size: 130 x 55 x 75 mm. Only £4-50 + 8% VAT.

CASSETTE MICROPHONE

On/off switch for remote control. Split lead with 2.5 mm and 3.5 mm plugs, standard cassette mics, to suit all types. Complete with desk rest. Please state which impedance required, 200 ohm/50 kohm. Price £1-80 + 12 1/2% VAT.

DUAL/IMP HAND MICROPHONE

The perfect hand/stand mic for stage, group, disco, etc. Finished in matt silver and black. Cardioid dynamic. Dual Imp: 600 ohm/50 kohm, 90-15,000Hz. With an on/off switch. Price £8-75 + 12 1/2% VAT.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

- ★ Completely portable.
- ★ Solders up to 150 joints per charge.
- ★ Recharges in its own stand.
- ★ Fine tip for all types of soldering.
- ★ Only 8in long and weighs just 6 ozs.

OUR PRICE £9-75 + 8%. (Spare bits are available)

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).

An ideal box to give a small project a professional finish. SIZE (internal) 81mm x 61mm x 28mm.

OUR PRICE 50p. + 8%.



U.K. CARRIAGE 50p UNLESS OTHERWISE STATED
VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

HIGH SPEC components FAST!

Agents for VERO - ANTEX - BIB MULTICORE SOLDER

- OPEN 9am-5pm, 6 days—Phone orders 9am-4pm.
- S.A.E. for stock list including pots, presets, I.C.'s 7400 & CMOS.
- capacitors, plugs, sockets, switches, cable, etc.
- Post free envelope included for your next order.
- SUPER EXPRESS phone service—ask for details.
- Shop at keen prices 6 days per week. Late night—Fri. 7-10pm.

TRANSISTORS + 200 OTHER TYPES IN STOCK

AC125 20p	BC109 11p	BC262A 15p	BFX29 26p	TIP41A 67p
126 20p	109B 12p	287 20p	84 22p	42A 89p
127 20p	109C 13p	300 27p	88 22p	TIS43 35p
128 20p	117 18p*	301 28p	BFY50 17p	ZTX300 15p*
151 35p	142 22p	303 30p	51 16p	302 18p*
153 35p	143 24p	338 16p*	52 18p	500 15p*
176 20p	147A 9p*	557 9p*	BY164 40p	502 18p*
187 20p	147B 10p*	BCY71 18p	ME0401 18p*	1N914 5p
188 20p	148 9p*	72 14p	041 18p*	4001 5p
AD149 68p	149B 10p*	BD123 6p	4001 10p	4002 5p
151 42p	149B 11p*	124 68p	4101 11p*	4005 9p
162 42p	149C 11p*	131 36p	MPF102 32p	4006 18p
MCH/PR 1.04	154 18p*	132 38p	OA47 8p	4148 5p
AF116 24p	157B 12p*	139 54p*	90 5p	2N2219 20p
117 24p	177 17p*	155 75p*	91 4p	2E46 40p
124 30p	178B 18p*	BF158 20p*	200 6p	2520G 15p*
239 37p	184B 12p*	185 28p*	OC29 9p	2982G 18p*
AU113 1.50*	184L 11p*	194 10p*	35 80p	3055 60p*
BC107 11p	187 26p	196 12p*	44 30p	3702 11p*
107A 12p	212A 13p*	197 12p*	71 25p	3703 10p*
108 10p	212L 15p*	199 15p*	ORP12 57p	3704 18p*
CL108 6p	213B 12p*	200 38p	TIP29A 47p*	3705 18p*
BC108B 11p	214 15p*	338 34p	30A 56p*	3707 12p*
108C 12p	214L 17p*	BFW11 68p	31A 57p	3819E 25p*


DIODES BRIDGES RESISTORS 1 1/2p each
50V 3A 13p 100V 1A 24p 1/2 WATT E12 (5%)
100V 3A 15p 200V 1A 25p 1 ohm - 10m ohm
200V 3A 18p 400V 1A 26p
400V 3A 21p

THYRISTORS
60V 1A 20p
600V 1A 60p TAG 1 600
700V 1A 1-20 BT106
400V 4A 56p C105D1
500V 6A 1-25 BT109
CLIPS for above 1p.

Post & Packing 25p per order. VAT please add to total * 12 1/2%, rest 8%

ORCHARD ELECTRONICS

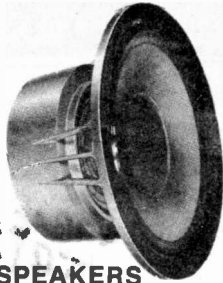FLINT HOUSE, HIGH STREET, WALLINGFORD, OXON, OX16 8DE
Telephone 0491 35529.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£9-00
Baker Group 35, 3, 8 or 15 ohm	£10-75
Baker Group 50/12 8 or 15 ohm	£14-00
Baker Group 50/15 8 or 15 ohm	£16-62
Baker Deluxe 124, 8 or 15 ohm	£12-38
Baker Major 3, 8 or 15 ohm	£10-98
Baker Superb 8 or 15 ohm	£16-31
Baker Regent 12in 8 or 15 ohm	£9-00
Baker Auditorium 12in 8 or 15 ohm	£14-65
Baker Auditorium 15in 8 or 15 ohm	£19-41
Castle 8RS/DD 4 or 8 ohm	£3-28
Celestion G12M 8 or 15 ohm	£13-50
Celestion G12H 8 or 15 ohm	£18-75
Celestion G12/50 8 or 15 ohm	£16-50
Celestion G12/50TC 8 or 15 ohm	£18-00
Celestion G12/50 2236 s/cone	£16-50
Celestion G12/50TC 2239 s/cone, alum. dome	£17-00
Celestion G15C 8 or 15 ohm	£26-95
Celestion G18C 8 or 15 ohm	£34-50
Celestion HF1300 8 or 15 ohm	£7-75
Celestion HF2000 8 ohm	£9-50
Celestion MH1000 8 or 15 ohm	£13-50
Celestion CO3K	£4-48
Decca London ribbon horn	£29-95
Decca London CO/1000/8 crossover	£8-95
Decca DK30 ribbon horn	£19-95
Decca CO/1/8 crossover (DK30)	£4-75
EMI 150 13 x 8in d/cone 8 ohm	£2-94
EMI 13 x 8in 20W bass 8 ohm	£9-00
EMI 14 x 9in bass 8 ohms, 14A770	£11-92
EMI 8 x 5in, 10W, d/cone, roll surr.	£3-56
EMI 6 1/2in d/cone, roll surr., 8 ohm	£3-93
EMI 8in roll surr. bass	£5-73
EMI 5in mid range	£3-50
EIac 59RM 109 (15 ohm), 59RM114 (8 ohm)	£3-38
EIac 6 1/2in d/cone, roll surr., 8 ohm	£3-83
EIac 10in 10RM239, 8 ohm	£3-83
Eagle Group 3000Hz 3, 8 or 15 ohm	£1-57
Eagle FR4	£5-51
Eagle FR65	£8-95
Eagle FR8	£11-95
Eagle FR10	£14-06
Eagle HT15	£3-96
Eagle HT21	£4-95
Eagle MHT10	£4-00
Eagle FF28 Multicell. horn	£5-95
Fane Pop 15, 8 or 16 ohm	£5-50
Fane Pop 33T, 8 or 16 ohm	£9-75
Fane Pop 50, 8 or 16 ohm	£12-50
Fane Pop 55, 8 or 16 ohm	£15-50
Fane Pop 60, 8 or 16 ohm	£17-95
Fane Pop 70, 8 or 16 ohm	£18-75
Fane Pop 100, 8 or 16 ohm	£27-95
Fane Crescendo 12, 8 or 16 ohm	£37-95
Fane Crescendo 12BL, 8 or 16 ohm	£39-95
Fane Crescendo 15/100A, 8 or 16 ohm	£49-95
Fane Crescendo 15/125, 8 or 16 ohm	£59-95
Fane Crescendo 18, 8 or 16 ohm	£87-95
Fane 910 Mk II horn	£15-75

SPEAKERS

Fane 920 Mk II horn	£39-95
Fane HPX1 crossover 200W	£2-50
Fane 13 x 8in, 15W dual cone	£5-50
Fane 801T 8in d/c, roll surr.	£8-96
Gauss 12in	£95-00
Gauss 15in	£110-00
Gauss 18in	£121-00
Goodmans Axent 100	£7-60
Goodmans Audiom 200 8 ohm	£13-46
Goodmans Axiom 402 8 or 15 ohm	£19-00
Goodmans Twinaxiom 8, 8 or 15 ohm	£9-50
Goodmans Twinaxiom 10, 8 or 15 ohm	£9-96
Goodmans 8P 8 or 15 ohm	£6-20
Goodmans 10P 8 or 15 ohm	£6-50
Goodmans 12P 8 or 15 ohm	£14-95
Goodmans 12PG 8 or 15 ohm	£16-50
Goodmans 12PD 8 or 15 ohm	£16-95
Goodmans 12AX 8 or 15 ohm	£39-00
Goodmans 15AX 8 or 15 ohm	£45-00
Goodmans 15P 8 or 15 ohm	£22-50
Goodmans 18P 8 or 15 ohm	£39-00
Goodmans Hifax 750P	£16-00
Goodmans 5in midrange 8 ohm	£4-05
Jordan Watts Module, 4, 8 or 15 ohm	£15-36
Kef T27	£5-18
Kef T15	£6-25
Kef B110	£6-75
Kef B200	£7-85
Kef B139	£15-08
Kef DN8	£2-08
Kef DN12	£5-39
Kef DN13 SP1015 or SP1017	£4-05
Lowther PM6	£30-60
Lowther PM6 Mk 1	£32-85
Lowther PM7	£48-60
Peerless KO10DT 4 or 8 ohm	£7-25
Peerless DT10HFC 8 ohm	£8-26
Peerless KO4DMRF 8 ohm	£9-50
Peerless MT225HCF 8 ohm	£2-95
Richard Allan CA12 12in bass	£19-80
Richard Allan HP8B	£11-93
Richard Allan LP8B	£8-33
Richard Allan DT20	£6-08
Richard Allan CN8280	£18-20
Richard Allan CN820	£3-15
Richard Allan Super Disco 60W 12in	£16-95
Richard Allen CG15 15in bass	£27-45
Richard Allan Super Disco 12in 80 watt	£16-95
Richard Allan Super Disco 10in 50 watt	£13-25
Richard Allan Super Disco 8in 50 watt	£12-85
Radford BD25	£23-40
Radford MD9	£11-50
Radford MD6	£12-50
Radford TD3	£7-25
Radford Cross Over Network	£14-75
Coles 4001 G & K	£5-96
Tannoy 10in Monitor HPD	£78-00
Tannoy 12in Monitor HPD	£88-00

Tannoy 15in Monitor HPD	£99-95
Wharfedale Super 10 RS/DD 8 ohm	£13-50

SPEAKER KITS

Baker Major Module 3, 8 or 15 ohm	each	£13-28
Fane Mode One Mk II 15W	each	£10-35
Fane D40 Disco Kit	each	£19-95
Goodmans DIN 20 4 or 8 ohm	each	£13-28
Goodmans Mezzo Twin kit	pair	£46-50
Helme XLK 30	pair	£21-95
Helme XLK 35	pair	£26-75
Helme XLK 40	pair	£38-50
Kefkit 1	pair	£51-00
Kefkit III	each	£46-00
Peerless 1060	pair	£54-00
Peerless 1070	each	£46-50
Peerless 1120	each	£54-00
Peerless 2050	pair	£39-50
Peerless 2060	pair	£53-00
Richard Allan Twin assembly	each	£13-46
Richard Allan Triple 8	each	£20-25
Richard Allan Triple 12	each	£25-16
Richard Allan Super Triple	each	£28-25
Richard Allan RA8 Kit	pair	£37-80
Richard Allan RA82 Kit	pair	£59-40
Richard Allan RA82L Kit	pair	£85-70
Wharfedale Linton II kit	pair	£21-50
Wharfedale Glendale 3XP kit	pair	£47-70
Wharfedale Dovedale III kit	pair	£59-40
Wharfedale Denton 2XP kit	pair	£23-25

HI-FI ON DEMONSTRATION in our showrooms:

Akal, Armstrong, Bowers & Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc.—ask for our Hi-Fi discount price list.

THIS MONTH'S SPECIALS! (Carr. £2)

Pioneer SX737	£179-00
Rotel RD20	£135-00
Rotel RA312	£56-00
Videotone Saphir 1	pair £52-00
Videotone Minimax 2	pair £43-00

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

ALL PRICES INCLUDE VAT (PRICES CORRECT AT 17/8/76)

Send stamp for free 32 page booklet "Choosing a Speaker"

ALL UNITS GUARANTEED NEW AND PERFECT
Carriage and insurance: Speakers 55p each (12in and up 85p each); Kits £1 each (£2 per pair); Tweeters and Crossovers 33p each.

WILMSLOW AUDIO

Dept PE

Loudspeakers, mail order and export:
Swan Works, Bank Square, Wilmslow.

Hi-Fi, Radio and TV: Swift of Wilmslow,
5 Swan Street, Wilmslow, Cheshire.

PA, Hi-Fi and Accessories: Wilmslow
Audio, 10 Swan Street, Wilmslow,
Cheshire.

Telephone: Loudspeakers, mail order and
export—Wilmslow 29599; Hi-Fi, Radio,
etc.—Wilmslow 26213.

Access and Barclaycard orders accepted by phone

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, Hi-Fi Answers Monitor (Rogers), Hi-Fi News No Compromise (Frisby), Hi-Fi News State of the Art, Wireless World Transmission Line (Bailey), Practical Hi-Fi and Audio Monitor (Giles), Practical Hi-Fi and Audio Triangle (Giles), Popular Hi-Fi (Colloms), etc.

On dem. Answers Monitor, State of Art, etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi Answers Monitor, free on request.

P.A. amplifiers, microphones, etc., by Shure, Linear, Eagle, Beyer, AKG, etc.

FREE with orders over £10—"Hi-Fi Loudspeaker Enclosures" book.

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

Colour T.V. Servicing
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. 772Z, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

TEXAS PNP DARLINGTON POWER TRANSISTORS TYPE T1P117, 35p.
NEW BOOKS. Constructing simple short wave receivers. Also building simple test gear, 75p.
1,000µF 40 VV ELECTROLYTICS. Size 1½ x ½in. 3 for 35p.
VHF POWER TRANSISTORS. Unmarked, good. 2N3866 40p 3 for £1.
SILICON SOLAR CELLS. 0.5V 5MA, 35p; 0.5V 50MA, 50p; 0.5V 100MA* 60p; 0.5V 200MA, £1; 0.5V 500MA, £2.25.
50 ASSORTED TRANSISTOR ELECTROLYTICS for 57p.
TEXAS TO3 PLASTIC POWER NPN TRANSISTORS TYPE R2880A. No information, 50p, 3 for £1-10.
50 PLASTIC NPN TRANSISTORS. 85% good, 57p.
50 PLASTIC PNP TRANSISTORS. 85% good, 57p.
GERMANIUM TRANSISTORS. AC141K, AC142K, AC153K, AC178K, AC187K, AC188K. All 25p each.
SILICON BRIDGES. 200PIV 2A, 30p; 400PIV 1A, 30p.
BF177 NPN TRANSISTORS. 100V 120 Mhz. 10p each, 6 for 50p.
12V DOUBLE CHANGE OVER SEALED RELAYS, 50p.
PLASTIC TRIACS. 50PIV 6A, 15p; 400PIV 6A, 60p.
PLASTIC SCRS. 50PIV 6A, 15p; 400PIV 6A, 60p.
AUDIO AMPLIFIER ICs. SN76001 55p; TAA611B 85p; TBA641 90p; SN76013ND £1; TBA800 85p.
GERMANIUM DIODES. OA85, IN34A. All 8p each.
BF224 RF 600MHz NPN TRANSISTORS, 6 for 50p.
20 SILICON PHOTO TRANSISTORS AND PHOTO DARLINGTONS. Assorted, untested, £1.
COMPRESSION TRIMMERS. 10pF, 30pF, 50pF, 150pF, 750pF, 1,000pF. All 8p each.
VHF DUAL GATE MOS FETs LIKE 40673, 33p, 4 for £1-10.
100 ASSORTED ½, ¼ WATT RESISTORS. 17 Different values, 57p.
50 AC128 TRANSISTORS. Branded but untested, 57p.
100 MULLARD C200 CAPACITORS. Assorted with chart, 57p.
TAG ENDED ELECTROLYTICS. 3,300µF 64VV, 50p; 4,700µF 40VV, 45p. Both size 2½ x 1½in.
STC CRYSTAL FILTERS 10.7MHz B.W. ± 6KHz, £4.
MULTI-TURN CERMET 20 TURN TRIMPOTS. 10Ω, 20Ω, 50Ω, 100Ω, 200Ω, 500Ω, 1kΩ, 2kΩ, 5kΩ, 10kΩ, 20kΩ, 50kΩ, 100kΩ, 200kΩ, 500kΩ, 1MΩ, 2MΩ. All 30p each.
MULTI-TURN WIRE WOUND 20 TURN TRIMPOTS. 10Ω, 20Ω, 50Ω, 100Ω, 200Ω, 500Ω, 1kΩ, 2kΩ, 5kΩ, 10kΩ, 20kΩ. All 25p each.
20 ASSORTED TUNING VARACTOR DIODES. Untested 45p.
500 x 500 + 17 + 17pF TUNING CAPACITORS. With SM drive, 38p.
250pF SOLID DIELECTRIC TUNING CAPACITORS, 33p.
BD167 4A NPN PLASTIC TRANSISTORS, 40p, 4 for £1-35.
CRYSTALS. 5MHz 75p; 8,040kHz 75p; 8,100kHz 75p; 28kHz 50p; 28.5kHz 50p; 7,620kHz 25p; 7,720kHz 45p; 7,985.7kHz 25p; 8,165.7kHz 25p; 8,233.3kHz 25p; 8,300kHz 25p; 8,365.7kHz 25p; 8,483.3kHz 25p; 8,583.3kHz 25p; 8,718.7kHz 25p; 8,036.25kHz 75p; 6,450kHz 60p; 6,221.11kHz 50p.

Please add 20p post and packing on U.K. orders under £2

J. BIRKETT
RADIO COMPONENT SUPPLIERS
25 The Strait, Lincoln LN2 1JF
Tel. 20767

TRAMPUS 

58-60 GROVE ROAD, WINDSOR, BERKS., SL4 1HS
Tel: 54525. For Industrial, Trade and Export

LOW PRICES TELEX 27950. REF 1617 FAST SERVICE
Add 6% to prices marked *. Add 12% VAT to all other prices or as current VAT legislation. Send C.W.O. except Government dept., etc. Post and packing 20p U.K. Barclay Card and Access by post or £5 min. by telephone. List free, send S.A.E. Money back if not satisfied.
ALL FULL SPEC. DEVICES. NORMALLY 24 HOUR TURNROUND ON STOCK ITEMS

IC's	All price each	TRANSISTORS	TTL	CMOS
555	35p*	AD181	50p*	7400 15p*
703 RF/IF	25p	AD182	50p*	7401 18p*
706 TO99	25p*	BC107	10p*	7402 18p*
723 Reg.	40p*	BC107B	13p*	7404 10p*
741 DIL 8	22p*	BC108	9p*	7410 10p*
741 TO99	35p*	BC108B	13p*	7413 20p*
741 DIL 14	35p*	BC109	9p*	7420 25p*
747 2 x 741	60p*	BC109C	15p*	7430 22p*
748 DIL 8	33p*	BC177/B/9	23p*	7440 10p*
7805 etc.	£1-50*	BC182/3/4	10p	7441 75p*
AY51224	£3-40*	BC212/3/4	12p	7442 85p*
CA3048	85p*	BCY70/2	16p*	7447 70p*
LM300	£1-50*	BC131	30p*	7470 25p*
LM301	30p*	BD132	30p*	7472 25p*
LM309K	£2-00*	BFY51	15p*	7474 31p*
LM380	80p*	MJ2955	85p*	7475 40p*
LM3900	80p*	MJE2955	85p*	7478 30p*
MC1310	£2-00	MJE3055	85p*	7490 42p*
MFC4000	75p	TIP29/30C	85p*	7491 75p*
NE538	£2-00*	TIP21/32C	£1-90*	7492 45p*
NE555	35p*	TIP41C	£1-35*	74121 32p*
NE556	90p*	TIP42C	£1-50*	4553 £4-00*
TBA800	80p	TIP2955		DIODES OA81/91 5p
TBA810	95p	TIP3055		IN4002 5p*
TBA820	90p	T1843	27p*	IN4148 and IN914
ZN414	£1-20	2N2646	40p*	silicon 4p*
		2N2905	20p*	BRIDGE 1A 50V 22p*
		2N2920	20p*	6A 100V 55p*
		2N3053	18p*	SCR and TRIACS
		2N3055	45p*	(BR100 25p*)
		2N3702/3	10p	C106 4A 400V SCR 55p*
		2N3704/5	10p	SC146 10A 400V TRIAC £1*
		2N3706/7	12p	DIL SOCKETS 8/14/18 ALL
		2N3708/9	12p	14p* SOLDERCON 10 65p*
		2N3819e	10p	1000 £4-00*
		2N3804/8	17p	VERO DIL BREADBOARD
		BUSH SETS	5p*	£2-25*, 2½" x 5" 40p*, 3½" x 5" 45p*, 2½" x 3½" 38p*
		DISPLAYS		
		0.3" DL704/7	£1-00	
		0.6" DL747	£1-25	
		DALO PEN	75p	


FABULOUS NEW KITS

EASY TO CONSTRUCT

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!



60W Guitar Amp

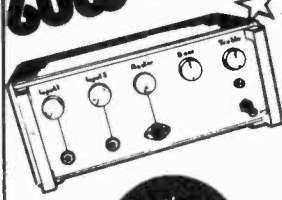


ONLY £29.95 +H

- ★ A fabulous easy-to-build Amp. that kicks out 50W R.M.S. into 8 ohms with 0.15% total harmonic distortion.
- ★ Rugged construction.
- ★ High sig/noise ratio
- ★ Output short circuit proof.
- ★ Two inputs allows mix Base and treble boost controls.

F M TUNER


£64.95 +H

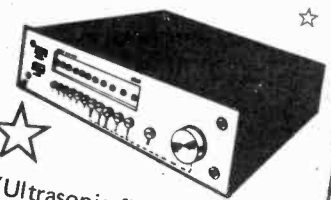

- ★ 'Varicap' Tuning.
- ★ Ultrasonic filter for pilot tone rejection to 65dB.
- ★ 'Mix' Control.
- ★ Sensitivity 1.2µV for 26dB quieting.
- ★ 6 pre-set station sel.

SIGNAL GENERATOR


£2.99 +S

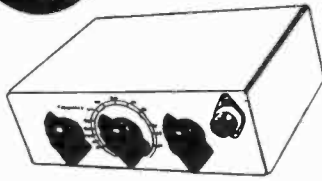

Gives audio signal from 20Hz - 20KHz with variable amplitude for system testing.

Available NOW!

CAR FLASHER UNIT

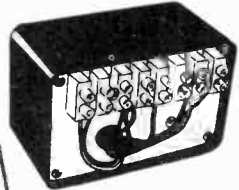

£6.25 +S

Electronic flash unit which gives constant indicator flashing rate independent of load.

TRANSISTOR TESTER

£9.95 +S



Measures Hfe, leakage for PNP, NPN, silicon or germanium transistors. Includes battery check facility.

- ★ New 16 page brochure contains complete details of kit range.
- ★ Big range of kits to interest Radio, Electronic and Hi-Fi enthusiasts.
- ★ Kits sent by return-of-post.
- ★ Each kit designed by specialists, only reliable and highest quality components included.

SEND FOR YOUR NEW KIT BROCHURE TODAY

Only **25p** inc. post and packaging.
S = 8%VAT. H = 12½%VAT.

DORAM

DORAM ELECTRONICS LTD
P.O.Box TR8,
Leeds LS12 2UF.

I enclose 25p please send me by return my new Doram kit brochure. Overseas orders except for N. Ireland, please add 10p for post and packing surface only. Customers who order this kit brochure together with Doram's new edition 3 component catalogue can save 15p, combined price 70p, on the individual purchase price for both and obtain two 25p vouchers.

PLEASE PRINT IN BLOCK CAPITALS
PE 11/76

Name _____
Address _____

Post Code _____
An Electrocomponents Group Company.

B. BAMBER ELECTRONICS

Dept PE, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

FREE WELLER 25W (SP25) SOLDERING IRON (worth £3.24 inc. VAT) with all orders over £20. Limited period only. Send now.

VARIABLE STABILISED POWER SUPPLY, mains input, 0-24V output, stabilised and current limiting at 500mA + 22V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 2 1/2 x 4 in. complete with external 5kΩ 3-turn pot for voltage control. Connection data supplied. £7.
50A (25-3-25A) EDGEWISE METERS, modern type by Sangamo Western, display area 1/2 x 1 1/2 with 2 mounting lugs. (Can be zeroed left or right hand). £1.50 each, while stocks last.

MAINS ISOLATION TRANSFORMERS, Tapped mains input, 240V at 3A + 12V at 500mA output. New, boxed, made by Gardners, £12.

FLEXIBLE HEATER STRIP, 240V a.c., 150W, approx. 1 metre long (insulated with fibreglass) with mains connector block. Many, many uses. 60p each.

HEAVY DUTY RELAYS, 24V d.c. operated (will work on 18V) 3 heavy duty make contacts (around 10A rating) + 4 change over contacts + 1 break contact. New, complete with mounting bracket (ideal for switching HT on Lincars). Many uses for this high quality unit. £1.50 each.

Good Quality Pressure Gauges, 2 1/2 in dia. flange mounting, 3 models avail. 0-60 lb/sq. in. 0-100 lb sq. in. 0-200 lb/sq. in. state which £1.25 each.
2N3055 type Transistors, O.K., but unmarked, 5 for £1.

110V NEONS, SCREW-IN-TYPE, 4 for 50p.
SLOW MOTION MOTORS (suitable for programmers, displays, etc.) 230-240V a.c. input, rotation between 1 and 2 revs per minute. £1.25 each.

MINIATURE PLIERS High quality "Crescent", made in USA. £4.35 + VAT (35p).
SIDE CUTTERS, high quality "Crescent", made in USA. £4.45 + VAT (44p).

MIXED COMPONENT PACKS, containing resistors, capacitors, switches, pots, etc. All new (random sample bag revealed approx. 700 items). £2 per pack, while stocks last.
TUNED COILS, 2 section coils, around 1MHz, with a black smart tuning knob, which moves an internal core to vary the inductance, many uses, easily re-wound, 3 for 50p.

HIGH QUALITY SPEAKERS, 8 1/2 x 6 in elliptical, only 2 in deep, inverse magnet, 4 ohms, rated up to 10W. £1.50 each or 2 for £2.75 (qty. discount available + 12% VAT).

TO3 transistor insulator sets, 10 for 50p.

MINIATURE 2 PIN PLUGS AND SOCKETS (fit into 1/8 in hole, pins enclosed, with covers for chassis mounting, or can be used for in-line connectors). Bargain pack of 3 plugs + 3 sockets + covers, 50p.

PROGRAMMERS (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable. Ideal for switching disco lights, displays, etc., or industrial machine programming. (Need slow motion motor to drive cams, not supplied) 9 switch version £1.50.

HEAVY DUTY HEATSINK BLOCKS, undrilled, base area 2 1/2 in x 2 in, with 6 fins, total height 2 1/2 in 50p each.

SPERRY 7-SEGMENT P.O.D. DISPLAYS, digit height 0.3 in red, with decimal points, 150V to 200V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new, AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one mount) £1 each. TYPE 333 (three digits in one mount) £1.50. (Sorry, no single digit available). Data Supplied.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC 108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type TOS Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
2N3819 Fet., 3 for 60p.
BA121 Varicap Diodes, 4 for 50p.
1N614 diodes, 10 for 25p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio Hi-Fi inputs, etc.) approx. 1/2 in x 1 1/2 in, 3 for 80p.
PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108 MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 6 1/2 in x 1 1/2 in, 2 for 35p.
Lead suppressors (10kohm) for mobile plug leads, 4 for 50p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

ALU-SOL ALUMINIUM SOLDER (made by Multi-core). Solders aluminium to itself or copper, brass, steel, nickel or tinplate. 16 a.w.g. with multiore flux, with instructions. Approx. 1 metre coil 30p pack. Large reel (approx. 12 metres) £2.75.

1 1/2 in polythene chassis mounting fuseholders, 6 for 30p.
I.C.'s, some coded, 14 DIL type, untested, mixed, 20 for 25p.

Mobile Converters, 24V DC input 13-8V at approx 3-4A DC output, fully stabilised, £3.50 each (ideal for running 12V car radio from 24V lorry battery).
R/S Midget 3 pole 4 way, rotary switches, 40p each.

We now stock Spirax Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

I.F. Cans, jin square, suitable for rewind, 6 for 30p + 12% VAT.
Miniature earphones with min. jack plug, 2 for 50p + 12% VAT.

TWIN I.F. CANS, approx. 1 in x 1/2 in x 1 in high, around 3-5-MHz. 2 separate transformers in 1 can, internally screened, 5 for 50p + 12% VAT.

Duobiler Electrolytics, 50uF, 450V, 2 for 50p.
Duobiler Electrolytics, 100uF, 275V, 2 for 50p.
Plessey Electrolytics, 470uF, 63V, 3 for 50p.
TCC Electrolytics, 1000uF, 30V, 3 for 60p.
Plessey Electrolytics, 1000uF, 180V, 40p each (3 for £1).
Duobiler Electrolytics, 5000uF, 35V, 50p each.
Duobiler Electrolytics, 5000uF, 50V, 60p each.
ITT Electrolytics, 680uF, 25V, high grade, screw terminals, with mounting clips, 50p each.
Plessey Electrolytics, 10,000uF at 6.3V, 75p each.
Plessey Cathodry Capacitors, 0-0-4uF at 12-5kV DC, screw terminals, £1.50 each.
PLEASE ADD 12% VAT TO ALL CAPACITORS

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

TV PLUGS AND SOCKETS
TV Plugs (metal type), 5 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 12% VAT.

PLUGS AND SOCKETS
N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
N-Type Sockets (4-hole chassis mounting), 50 ohms (a small coax lead type), 50p each.
PL259 Plugs (PTFE), brand new, packed with reducers, 65p or 5 for £3.
SO239 Sockets (PTFE), brand new (4-hole fixing type), 50p each or 5 for £3.25.
25-way ISEP Plugs and Sockets, 40p set (1 plug + 1 socket).
Plugs and sockets sold separately at 25p each.
Bulgin Round Free Suits, 3 pin, for mains input on test equipment, etc., 25p each.

WELDER SOLDERING IRONS
EXPERT, Built-in-spotlight illuminates work. Pencil grip with fingertip trigger. High efficiency copper soldering tip.

EXPERT SOLDER GUN, £8.80 + VAT (54p)
EXPERT SOLDER GUN KIT (spare bit case, etc.), £9.80 + VAT (78p)

SPARE BITS, PAIR, 80p + VAT (2p)
MARKSMAN SOLDERING IRONS
SP15D 15W £3 + VAT (24p)
SP25D 25W £3 + VAT (24p)
SP25CK 25W + bits, etc. kit £3.85 + VAT (31p)
SP40D 40W £3.44 + VAT (28p)
BENCH STAND with spring for Marksmen Irons, £2.22 + VAT (18p)

SPARE BITS
MT8 for 15W, 44p + VAT (4p).
MT4 for 25W, 38p + VAT (3p)
MT10 for 40W, 42p + VAT (3p)

TCPI TEMPERATURE CONTROLLED IRON, Temperature controlled iron + PSU, £20 + VAT (£1.80)

SPARE TIPS
Type CC single flat, Type K double flat fine tip, Type P very fine tip, £1 each + VAT (8p).
ALL SPARES AVAILABLE

MULTICORE SOLDER
Size 5 Savbit 16 a.w.g. in alloy dispenser, 32p + VAT (3p).
Size CISAV18 Savbit 18 a.w.g., 50p + VAT (4p).
Size 12 SAVBIT 18 a.w.g. on plastic reel £1.80 + VAT (15p)

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS SATURDAYS ONLY 9.30-12.00, 1.30-5.00.



Random FLASHER UNIT
Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random.
£18.95



TWIN BANK 6 LIGHT UNIT (less lamps)
LENGTH 14 1/2 inches
B.C. Fitting **£9.55**
E.S. Fitting **£10.35** EACH



Sound to Light MASTER UNIT
600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET



TYPE A SPOT (less lamp)
B.C. Fitting **£1.95** EACH
E.S. Fitting **£2.12** EACH



TYPE B 3 BANK UNIT (Less Lamps)
B.C. Fitting **£6.90** EACH
E.S. Fitting **£7.26** EACH



TWIN BANK 12 LIGHT UNIT (less lamps)
Length 31 1/2
B.C. Fitting **£15.60** EACH
E.S. Fitting **£17.00** EACH

100 WATT SPOT LAMPS RED, YELLOW, GREEN 3 lamps **£1.18** each
BLUE CLEAR **£1.18** each
B.C. or E.S. Fitting **£3.54**

ALL PRICES INCLUDE V.A.T. and POST & PACKING (These prices apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list

ALBEN ENGINEERING CO. LTD.
DEPT. PE THE CRESCENT, WORSTHORNE,
BURNLEY, LANCS. Tel Burnley 20940

Veroboards are available with 0.1" x 0.1" or 0.15" x 0.15" matrix with holes, in 15 sizes. A new catalogue describing Verostrip, DIP boards, Plastic x Metal cases, Veroboxes etc is available (price 10p + S.A.E.)

VARIABLE EASY TO USE RELIABLE ORIGINAL...



Vero Electronics Limited, Retail Dept.,
Industrial Estate, Chandler's Ford, Hants., SO5 3ZR
Telephone: Chandler's Ford 2956 (STD 04125)

CBM

- SR7919D ● 8-digit or 5-digit+2 Exp.
- Full trig and log functions ● Sq. root
- Reciprocals
- Yx, X², π
- Register exchange
- Memory plus
- Store recall
- Sign change
- Algebraic logic.



£11.70*

4148R—10-digits, 2 exponents, Full log and trig functions. X², Reciprocal, π, X root of Y, Polar rectangular coordinates, 2-store memory, Rechargeable. Mean and Standard deviation.

(R) £28.50

SR4190R. 10-digit, 2 Exp. 90 function pre-programmed, metric conversions. Extra functions to the 4148R:—Perms and combinations, Gamma, Poisson and Binomial distributions, factorial, complex numbers, hyperbolic functions, linear regression and integration of Y = f(x).

(R) £39.95

SR1800—Similar to the 4148R. Green display. Battery operated. £19.40*

SINCLAIR

CAMBRIDGE SCIENTIFIC

- 5-digit ● 2 Exp
- C & CE key ● sin ● cos ● tan ● arcsin ● arccos and tan ● reciprocal ● E to the X ● natural log ● antilog ● memory + ● memory - ● memory exchange ● memory cancel ● EE exponent ● change notation ● PLUS a degree radian switch.



£10.54

OXFORD 300—Larger version of above. £12.49*

DECIMO

VATMAN—SCIENTIFIC

Large green display, 8-digits, 2 exponents, 4 trig log functions 10⁻⁹⁹.

Radian degrees. Exchange. Memory, π, Reciprocal, X² etc. Single Function keyboard. 20 hr battery life. £23.50



SUPER-VATMAN—Similar to above but with full-function memory. X² Reciprocal. π. √. £11.50

ROCKWELL

44RD. 9-digit or 5-digit & 2 Exp. Green display. Store. Similar to the 63R less factorial. £17.55*



64RD. 12-digit or 8-digit+2 Exp. Additional to 44RD: Polar rec., coordinates, log, rad or grad. £22.20*

63R—8-digit, 2 exponent. 10⁻⁹⁹. Memory. 2-level parentheses. All trig and log functions. Degree radian. Factorial. Reciprocal. π. √ etc. Rechargeable. (R) £23.95

Including recharger. 61R—Green display. 8-digits. All trig and log functions. (R) £20.42

The ZYCON range of Quality Electronic Watches

L.C.D.

KLC3 L.C.D. Constant display Shows Hrs, Mins & pulsating secs. Chrome finish with Stainless Steel back and FREE Adjustable S/Steel bracelet. £22.68



KLC5 5-Functions. Shows Hrs, Mins, pulsating secs. Press button once for Mth & Date. Twice for Secs readout. Auto-set back to time! Plus 'Nite Lite' for viewing in dark. Stylish Chrome finish. S/Steel back. FREE matching S/Steel bracelet. £32.68



KLC6 SWISS MADE—Solid S/Steel throughout. Constant disp., shows Hrs, Mins, pulsating Secs. Single Command Button—Press once for Mth & Date, twice for Mins & Secs. Auto-reset back to time. 'Nite-Lite' FREE matching S/Steel bracelet. £36.98



Or In Heavy Gold Plate on Solid S/Steel with Gold Plated bracelet. £41.61

L.E.D.

KED5 5-Functions. Shows Hrs, Mins, Secs, Mth & Date. 4-Yr calendar. Beautifully finished with S/Steel back & FREE Leatherette Strap. £18.47



KED6 A fantastic 6-Functions—window display shows Hrs, Mins, Secs, Mth & Date. Day of week in letters. Single button. Auto-hold & fade-out. 4-Yr calendar. Case in Heavy Rhodium on Brass + S/Steel back. FREE matching S/Steel adjustable bracelet. £27.33



KED6 PLUS Month & Day of the Week in Letters! Shows Hrs, Mins, Secs, Date, Mth & Date, Day of Week, Auto 4-Yr calendar, A.M./P.M. Set/indicate. One of the most sophisticated watches at this price. Accurate to within a few secs a year. Finished in Satin Stainless Steel with FREE matching Steel bracelet. £34.62 ONLY



All come in FREE Presentation Box. All Zycon watches carry our 'NO QUIBBLE' 1 Year Guarantee!

NOVUS

4525—8-digit, 2 Exp. 100 step programmable. R.P.N. Full log, & trig functions. X Y Exchange, exponent key, change sign, memory, 4 roll stack, skip, delete, accessible additional programmes within the 100 step. (R) £39.55



4520—Non-programmable version of the 4525 Incl. mem + x², deg., & Rad. (R) £21.20

4510—8-digits, 3 level stack. All trig and log functions. √. π. Reciprocal. Memory etc. £13.50*

NEW 4640. 10-digit, 2 Exponent. 54 functions. 4-level Roll Stack. 3 fully addressable memories. Logs, Trips, Stat & Metric Conversions etc. (R) £47.10

4600—Same but Algebra IC (R) £47.10

4515—100-step programmable version. (R) £33.10

6010—Metric £17.80*

6020—Financier. £16.65*

6025—Rechargeable. Financier 100-step programmable. (R) £39.50

6030—Statistician. £16.50*

6035—100-step programmable Statistician. Rechargeable. (R) £39.50

CASIO

FX-20—Full trig and log functions. 8-digit mantissa or 6-digit mantissa and 2-digit exponents. 10⁹⁹ to 10⁻⁹⁹. Bright green display. Full sin, cos, tan, inverse sin, inverse cos, inverse tan. Log X and ln x, e^x, x^y, √, Reciprocal Degree Radian conversion. Memory and exponent key. ONLY £15.65*



FX-15—As above but larger and including a larger display. x² key. π key. Reciprocal key. ONLY £19.25*

FX-101—De Luxe model with similar functions to the FX-15 but 8-digits + 2 exponent 10⁹⁹ to 10⁻⁹⁹.

OUR PRICE £23.50*

ALL ITEMS CARRY A FULL YEARS GUARANTEE

*—Free B.S.I. approved adaptor. (R)—Free recharger.

ADD 8% VAT TO ALL PRICES

TEXAS

SR50A—10-digit. 2 exponent. Rechargeable. All trig and log functions. Hyperbolic. X to the root of Y. Radian and degree. Factorial. Memory etc. (R) £29.95



Including recharger

SR51A—As above but with 3 Independent memories. Linear regression. Mean. Variance. Standard deviation. Permutation. Random number generation + 20 basic conversions and their Inverse. Rechargeable. (R) £43.90

Including recharger

SR56—100 step Programmable. 10-digit, 2 Exp. 10 Independent memories, all log, trig and statistical functions. Can be programmed for mathematics, electronic engineering, statistical, financial and navigation.



£64.90 (R)

SR52—224 programme steps. 20 Independent memories. 9 level parentheses. Card programmable. Supplied with 20 blank magnetic cards and programme manual. FREE any one of the following pre-programme manuals: 1. Statistics. 2. Electrical Engineering. 3. Mathematics. 4. Finance. Each worth £25.

£208.33 (R)

THE ROCKWELL

STAINLESS STEEL 24K

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. ✓ Click-buttons. Rechargeable. Including recharger (R) £19.50



DECIMO DIGITAL CLOCK/RADIO

£32.95 OUR PRICE Incl. VAT plus £1 p&p



LARGE DIGITAL READOUT

This is the most unique clock/radio in the country today having a soft 11" high orange-glow digital readout which is completely silent and non-pulsating. In a beautiful teak style cabinet with up-to-date VHF/MW radio. You can awake to soft music or alarm—and if you want up to 10 minutes more—just press the 'Drowse' button. Automatic 80 minute 'sleep' button in case you drop off while the radio's on

ORDER FORM

PHONE CALLS AND PERSONAL CALLERS WELCOME MONS TO THURS BETWEEN 2 & 5 p.m. 01-458 4755. SUNDAYS 10 a.m. to 1 p.m. To: BARCLAY ELECTRONICS Dept. 10PE, 1115 FINCHLEY ROAD, TEMPLE FORTUNE, LONDON N.W.11

Please send me..... with/without optional mains adaptor. I enclose cheque/money order total value £..... Please add 55p to all items to cover p. & p.

NAME ADDRESS

barclay
ELECTRONICS

GOOD NEWS FROM



Connoisseur

THE NEW BD2/A

Based on the popular BD2, the new BD2/A offers the hi-fi enthusiast all the features usually associated with Connoisseur turntables, such as low rumble, wow and flutter, plus the addition of an automatic pick-up arm lift-off at the end of the record. This is achieved by an ingenious, though simple, electromagnetic system, which avoids having any physical contact with the pick-up arm. It is possible, therefore, to use top quality cartridges, tracking at less than one gram, without putting any extra side pressure on the stylus.

The BD2/A comes either as a chassis model, or mounted on a slimline plinth, standing on rubber anti-vibration feet, finished in genuine American walnut, and fitted with a bronze, hinged dust cover. For those with restricted space, a compact plinth measuring only 13½" x 15½" x 5½" is still available.

Specification

Rumble - 65dB when measured in accordance with DIN 45539 using weighting network, referred to 7cm/sec. at 330Hz.

Wow and flutter Less than 0.1%.

Hum level - 80dB.

The BD2/A sells for a recommended price of only £55.00 + VAT. Ask your local hi-fi dealer, or write to the factory, for further details.

Connoisseur

Manufactured by:- A. R. Sugden & Co (Engineers) Ltd., Atlas Mill Road, Brighouse, West Yorkshire, HD6 1ES. Telephone: Brighouse (04847) 2142. Telegrams & Cables: Connoisseur, Brighouse.

New to the UK from PRONTO

Battery operated LCD read out
CALENDAR CLOCK KIT - crystal accuracy -
Bold Digits - runs on two Penlight Cells.




Now is the time for the hobbyist to move into Advanced Technology with Pronto!
PRONTO MODEL 301 - The first completely portable liquid crystal display, digital CALENDAR CLOCK KIT offered in the United Kingdom.

- * Battery operation - two small alkaline cells give a minimum life of 12 months.
- * Superb accuracy through crystal control - of 3 minutes a year
- * Wide angle display with ½ inch digits
- * Push Buttons give choice of 3 display modes - hours minutes on 12 hour display with flashing colon, or seconds, or date.
- * PRONTO 301 comes complete with easy to follow

instructions AT **£29.50** including V.A.T. You save Pounds off the recommended retail price of a comparable made up clock.

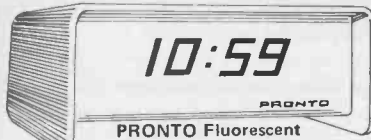TERMS: Cash with order - make a cheque and/or postal order payable to PRONTO ELECTRONIC SYSTEMS LIMITED. (P & P - U.K. £D.45 Overseas £1.50)



PRONTO Fluorescent Display Alarm Clock KIT

Wake up to the electronic age with the new PRONTO 304 Alarm Clock

- * Large Bright Green Display
- * Alarm with 10 minute 'snooze' feature
- * AM/PM indication and simple setting
- * Automatic brightness control on digits governed by room lighting

* Ingenious gravity alarm - time setting mode switch * Full assembly instructions

AT **£15.50** including V.A.T.

With all PRONTO products - enquiries from the Trade, as well as the Hobbyist, are welcome, and you can also buy individual components!

PRONTO CONSTRUCTOR'S CLUB
When you buy your first Pronto kit you're automatically a Member of the PRONTO CONSTRUCTOR'S CLUB. It will not only keep you in the picture on new ideas and kits... but gives you **FREE** a £2 Voucher against the purchase of your next kit!

Isn't it time you joined the Club?

Please send me -

PRONTO 301 KIT/S
AT £29.50 EACH (Plus P & P)

PRONTO 304 KIT/S
AT £15.50 EACH (Plus P & P)

My cheque/P.O. for _____ is enclosed

NAME _____

ADDRESS _____

Pronto Electronic Systems Ltd.
645/647 High Rd., Seven Kings,
Essex IG3 8RA. D1-599 3041

Reg. office No 1081707



DISCOUNTS

THESE DISCOUNTS APPLY TO TOTAL OF ORDER — SPECIALS INCLUDED

10% OFF ON ORDERS OVER £15
15% OFF ON ORDERS OVER £50

LARGE QUANTITY PRICING AVAILABLE ON REQUEST
 PLEASE SPECIFY ITEM AND QUANTITY

TTL	7400	7401	7402	7403	7404	7405	7406	7407	7408	7409	7410	7411	7412	7413	7416	7417	7420	7422	7423	7425	7426	7427	7430	7432	7437	7438	7440	7441	7442	7443	7444	7445	7446	7447	7448	7450			
10-10p	11	11	11	11	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	
10-13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	
10-13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13	13

LOW POWER	74100	74102	74103	74104	74106	74110	74120	74130	74142
10-16	16	16	16	16	16	16	16	16	16
10-16	16	16	16	16	16	16	16	16	16
10-16	16	16	16	16	16	16	16	16	16

LOW POWER SCHOTTKY	741500	741502	741504	741508	741510	741520
10-23	23	23	23	23	23	23
10-23	23	23	23	23	23	23
10-23	23	23	23	23	23	23

HIGH SPEED	74100	74101	74104	74108	74110	74111	74120	74121
10-16	16	16	16	16	16	16	16	16
10-16	16	16	16	16	16	16	16	16
10-16	16	16	16	16	16	16	16	16

SCHOTTKY	74500	74502	74503	74504
23	23	23	23	23
23	23	23	23	23
23	23	23	23	23

8000 (NATIONAL)	8041	8095	8121	8123	8130	8100	8110
10-33	33	33	33	33	33	33	33
10-33	33	33	33	33	33	33	33
10-33	33	33	33	33	33	33	33

8000 (SIGNETICS)	8263	9002	9301
3-79	79	79	79
3-79	79	79	79
3-79	79	79	79

IC SOCKETS	8 pin	14 pin	16 pin	18 pin
Solder tail - low profile	£-11	£-12	£-13	£-14
8 pin	£-11	£-12	£-13	£-14
14 pin	£-11	£-12	£-13	£-14
16 pin	£-11	£-12	£-13	£-14
18 pin	£-11	£-12	£-13	£-14
wire wrap - gold plate	£-30			

CMOS	4000A	4001A	4002A	4006A	4007A	4008A	4009A	4010A	4011A	4012A	4013A	4014A	4015A	4016A	4017A
21	21	21	21	21	21	21	21	21	21	21	21	21	21	21	21
21	21	21	21	21	21	21	21	21	21	21	21	21	21	21	21
21	21	21	21	21	21	21	21	21	21	21	21	21	21	21	21

CALCULATOR CHIPS	CT5002	CT5003	MM5725	MM5736	MM5738	MM5739	
12 digit, 4 function fixed decimal - battery operation	40 pin	12 digit, 4 function plus memory, fixed decimal	28 pin	8 digit, 4 function, floating decimal	28 pin	8 digit, 5 function plus memory and constant floating decimal, 9V battery operation	24 pin
12 digit, 4 function fixed decimal - battery operation	40 pin	12 digit, 4 function plus memory, fixed decimal	28 pin	8 digit, 4 function, 9V battery operation	18 pin	8 digit, 5 function plus memory and constant floating decimal, 9V battery operation	24 pin
12 digit, 4 function fixed decimal - battery operation	40 pin	12 digit, 4 function plus memory, fixed decimal	28 pin	8 digit, 4 function, 9V battery operation	18 pin	8 digit, 5 function plus memory and constant floating decimal, 9V battery operation	24 pin

MEMORIES	1101	1103	1702A	2102	2103-1	5203	5260	5261	5262	7489	82523	F93410	74187	74200	
256 bit RAM MOS	16 pin	1024 bit RAM MOS	18 pin	1024 bit static PROM elect. prog. - UV eras.	16 pin	1024 bit static RAM DTL/TTL comp. 1 ms	16 pin	1024 bit dynamic RAM MOS 16 pin	16 pin	1024 bit dynamic RAM MOS 16 pin	16 pin	256 bit RAM bi-polar	16 pin	256 bit RAM tri-state	16 pin
256 bit RAM MOS	16 pin	1024 bit RAM MOS	18 pin	1024 bit static PROM elect. prog. - UV eras.	16 pin	1024 bit static RAM DTL/TTL comp. 1 ms	16 pin	1024 bit dynamic RAM MOS 16 pin	16 pin	1024 bit dynamic RAM MOS 16 pin	16 pin	256 bit RAM bi-polar	16 pin	256 bit RAM tri-state	16 pin
256 bit RAM MOS	16 pin	1024 bit RAM MOS	18 pin	1024 bit static PROM elect. prog. - UV eras.	16 pin	1024 bit static RAM DTL/TTL comp. 1 ms	16 pin	1024 bit dynamic RAM MOS 16 pin	16 pin	1024 bit dynamic RAM MOS 16 pin	16 pin	256 bit RAM bi-polar	16 pin	256 bit RAM tri-state	16 pin

TANTALUM CAPACITORS SOLID-DIPPED ± 20%	1 ml	3.3 ml	1 ml	2.2 ml	4.7 ml	6.8 ml
35V	35V	35V	35V	35V	35V	35V
15p	15p	15p	15p	15p	15p	15p
10 mid	10 mid	10 mid	10 mid	10 mid	10 mid	10 mid
16V	16V	16V	16V	16V	16V	16V
21p	21p	21p	21p	21p	21p	21p

SHIFT REGISTERS	MM5013	MM5016	SLS-4025	2504
1024 bit accum. dyn.	8 pin	500/512 bit dyn.	8 pin	1024 bit multiplexed dyn
1024 bit accum. dyn.	8 pin	500/512 bit dyn.	8 pin	1024 bit multiplexed dyn
1024 bit accum. dyn.	8 pin	500/512 bit dyn.	8 pin	1024 bit multiplexed dyn

UNIVERSAL BREADBOARD
Silver plated copper circuit board 3-3/16" x 5-1/16". 2 rows of 27 holes for DIP IC's - space for transistors, resistors & capacitors. Versatile and simple for bread-boarding IC circuitry.

SHIPMENT MADE VIA AIR-POSTAGE PAID 3 DAYS FROM RECEIPT OF ORDER

CLOCK KIT
 6 Digits (NS71L)
 MM5314 Clock Circuit £9-50
 2 PC Boards Clock & Display
 All Transistors, Resistors
 Capacitors & 3 switches with Schematic & Instructions

4 Digits (NS74)
 MM5312 Clock Circuit £7-00
 1 PC Board
 All necessary transistors, resistors, capacitors, diodes & switches.
 With Schematic & Instructions

NOVEMBER SPECIALS

LINEARS	MEMORIES	TTL
311 £ 45	1103 £ 61	7410 .08
309K 61	1702 5-75	7438 .12
340T +5 82	5203 6-00	7454 .08
34T +15 82	5260 72	74151 .38
370 80	5261 72	74153 .36
555 29	5262 84	74154 .59
1310 1-25	F93410 97	74192 .68

2102 RAM
 1024 bit fully decoded static RAM
 DTL/TTL compatible - 16 pin DIP £1-50

7001 CLOCK CHIP
 4-6 digit, 12-24 hr. alarm, timer & date circuits with data £4-00

DVM CHIP 4% DIGIT
 MM 5330 - F channel device provides all logic for 4 1/2 digit voltmeter. 16 pin DIP with data £8

JUMBO LED
 Red 7 p
 Green 7
 Yellow 7
 8 digit multiplexed - live function - chain operation 2-lev memory - floating decimal - independent constant - interface with led with only digit driver - 9 V batt. oper. 24 pin £1-20

MISC DEVICES
 ULN 2208 FM gain block 34dB mDIP £1-03
 ULN2209 FM gain block 48dB mDIP 1-03
 2513 64 x 8 character generator 7-00
 CA 3046 Transistor array 14 pin DIP 55

LINEAR CIRCUITS
 300 Pos V Reg (super 723) 1U-5 £ 49
 301 Hi Perf Op Amp mDIP TO-5 21
 302 Volt follower TO-5 49
 304 Neg V Reg TO-5 56
 305 Pos V Reg TO-5 60
 307 Op AMP (super 741) mDIP TO-5 44
 308 Micro Per Op Amp mDIP TO-5 69
 309 5V IA regulator TO-3 1-25
 310 V Follower Op Amp mDIP 75
 311 Hi perf V Comp mDIP TO-5 67
 319 Hi Speed Dual Comp DIP 82
 320T Neg Reg 5, 12, TO-220 1-12
 320K Neg Reg 5.2, 12 TO-3 1-32
 322 Precision Timer DIP 69
 324 Quad Op Amp DIP 1-23
 339 Quad Comparator DIP 1-06
 340K Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-3 1-48
 340T Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220 1-23
 370 AGC/Squelch AMP DIP 92
 372 AF-Hi Strip detector DIP 51
 373 AM/FM/SSB Str TO-5 35
 376 Pos V Reg mDIP 38
 380 2w Audio Amp DIP 93
 380-8 6w Audio Amp mDIP 1-02
 381 Lo Noise Dual preamp DIP 1-13
 382 Lo Noise Dual preamp DIP 1-13
 531 High Slew rate Op Amp 2-07
 540 Power driver TO-5 1-38
 555 Prec V Reg DIP 62
 555 Timer mDIP 44
 556A Dual 555 Timer DIP 1-02
 560 Phase Locked Loop DIP 2-23
 562 Phase Locked Loop DIP 2-23
 565 Phase Locked Loop DIP TO-5 1-38
 566 Function Gen mDIP TO-5 1-38
 567 Tone Decoder mDIP 1-38
 569 Operational AMP TO-5 or DIP 31
 710 Hi Speed Volt Comp DIP 24
 711 Dual Difference Compar DIP 51
 723 V Reg DIP 44
 723 Diff. video AMPL TO-5 63
 739 Dual Hi Perf Op Amp DIP 75
 741 Comp Op Amp mDIP TO-5 29
 747 741 Dual Op Amp DIP or TO-5 51
 748 Freq Adj 741 mDIP 31
 1304 FM Mux Stereo Demod DIP 75
 1307 FM Mux Stereo Demod DIP 52
 1456 Op Amp mDIP 91
 1458 Dual Comp Op Amp mDIP 44
 1800 Stereo multiplexer DIP 1-73
 3900 Quad Amplifier DIP 38
 7524 Dual core memory sense Amp 1-20
 7525 Dual core memory sense Amp 92
 8038 Voltage contr. av. DIP 3-68
 8864 9 DIG Led Cath Drev DIP 1-58
 75150 Dual Line Driver DIP 1-27
 75451 Dual Peripheral Driver mDIP 24
 75452 Dual Peripheral Driver mDIP 24
 75453 (351) Dual Periph Driver mDIP 24
 75491 Quad Seg Driver for LED DIP 58
 75492 Hex Digit driver DIP 63

8038 FUNCTION GENERATOR
 Voltage controlled oscillator sine, square, triangular output 16 pin DIP with data £2-50

CLOCK CHIPS
 MM5311 6 digit multiplexed BCD, 7 seg 12-24 Hr, 50-60 Hz 28 pin £3-07
 MM5312 4 digit multiplexed BCD, 7 seg 1 pps, 12-23 Hr, 50-60 Hz 24 pin 2-23
 MM5313 6 digit multiplexed BCD, 7 seg 1 pps, 12-24 Hr, 50-60 Hz 28 pin 3-07
 MM5314 6 digit multiplexed 12-24 Hr, 50-60Hz 24 pin 3-07
 MM5316 4 digit, 12-24 Hr, 50-60 Hz, alarm, timer and date circuits 28 pin 4-80

LED'S
 ME4 Intra-red TO-18 29p
 MV50 Mini LED red emitting - axial 10p
 NS100 Mini red LED - point 10p
 NS102 Mini red LED - diffused 10p
 XC209-R Mini red LED - diffused 12p
 MV5020 Jumbo red - diffused 12p
 MV5020 Jumbo green - diffused 15p
 MV5020 Jumbo clear 12p
 MV5020 Jumbo amber 12p

LED DISPLAYS
 MAN1 Red .27" CA £1-50
 MAN2 Red .5x7 dot matrix .35" 2-95
 MAN3A Red .12" CC -15
 MAN5 Green .27" CA 2-03
 MAN6 Red .6" CA 2-03
 MAN7 Red .27" CA -97
 MAN8 Yellow .27" CA 2-03
 MAN66 Red .6" CA spaced seg 2-03
 DL10A Red .26" CA -89
 NSN71L Red .27" CA -89
 FND70 Red .25" CC -49

MULTIPLE DISPLAYS
 NSN33 3 digit .12" red LED £ -89
 HP5082-5 5 digit .11 red LED 1-80
 7405
 HP5082-4 4 digit .11 red LED 1-70
 7414
 SP-425-09 9 digit .25 gas disch. 1-50

Date sheets on request. Add 20p ea. item is priced below 50p each.

BANKAMERICA CARD MASTERCHARGE CHARGEX
 BARCLAYCARD ACCESS EUROCARD

Satisfaction guaranteed. Shipment will be made postage prepaid within 5 days from receipt of order. Payment may be made with personal check, charge card (include number and exp. date), international money order (include receipt) or bank cheque made payable in U.S.\$

Add 50p to cover shipping and handling if order is less than £5.
 The above prices do not include any taxes leviable by a purchasers country of residence.

INTERNATIONAL ELECTRONICS UNLIMITED
 P.O. BOX 3036 / MONTEREY, CA. 93940 USA
 PHONE (408) 659-3171

ambit international

Coils, ICs for RF&AF, Tuners, Modules for AM FM & TV.

complete tuner kits

Larholt Signalmaster Mark 8....the most stylish FM tuner kit that is available today. Suitable for even the relatively inexperienced in electronics construction, with clear and concise point-to-point details. Performance matches the excellent looks. £86.95

International Mark 2....A flexible system, with cabinet, chassis and panel designed to accommodate a variety of tuner electronics. The standard system is built around the Larholt 7253 tuner set, includes two meters 6 preset stations, manual tune, balanced LED tuning, PSU etc. £65.00

The above tuners are supplied with prealigned RF and IF stages.

AM/FM....a new low cost MW/LW and FM stereo tuner, with muting, mechanical drive, teak effect cabinet. £41.95

TV sound....the 7700 TV sound module in a chassis and cabinet that matches the AM/FM tuner. £36.95

Please remember to include an extra £3 carriage on complete tuner kits.

Radio ICs	Misc. regs etc.	Transistors
CA3089E FM IF 1.94†	7805UC 5v 1A 1.55*	ZTX107 0.14
CA3090AQ mpx 3.75†	78M12 12v ½A 1.20*	ZTX108 0.14
MC1310P mpx 2.20†	TDA1412 .. 0.95*	ZTX109 0.14
SN76660N FM IF 0.75	7815UC 15v 1A 1.55*	ZTX212 0.16
TBA120AS FM IF 1.00	78M20 20v ½A 1.20*	ZTX213 0.16
MC1350 AM/FM IF 0.70	78M24 24v ½A 1.20*	ZTX214 0.16
HA1197 AM system 1.40	uA723 5-35v 0.80*	ZTX413 0.18
TBA651 AM system 1.81	NE550A do. 0.80*	ZTX551 0.18
uA720 AM system 1.40	TAA550B 32v. 0.50*	ZTX451 0.18
	uA741 op amp 0.40*	BF224 0.22
	LM3900 quad amp 0.68*	BD165 0.50
	MC3401 do. 0.68*	BD166 0.54
	8038 wave gen. 3.10*	BD535 0.52
	NE555 timer 0.70*	BD536 0.53
	NE560B PLL 2.50	BD609 0.70
	NE561B PLL 3.50	BD610 1.20
	NE562B PLL 2.50	40673 0.50
	NE565A PLL 2.50	MEM680 0.75
	NE566V VCO 2.55*	BF256L 0.38
	NE567V tone trigger 2.50*	

Audio ICs

LM380N 2W scp 1.00
TBA810AS 7W scp 1.09
TCA940E 10w scp 1.80
TDA2020 20w scp 2.99
LM381N stereo pre 1.81

scp = short cct protection

† = includes coil

* = 8% VAT, others 12.5%

Tunerheads for VHF FM and UHF TV (All varicap types)

EF5800 6 circuit high quality 88-108MHz tunerhead	14.00
EF5600 5 circuit high quality 88-108MHz tunerhead	12.50
EC3302 3 circuit (same spec to LP1186) VHF tunerhead	5.50
5700 UHF TV tunerhead 38MHz IF with 4 way preset	8.00

Modules for IF, decoders etc. (Also available built & tested)

7020 kit 10.7MHz FM IF with mute, AFC, AGC, meter ops	5.25
7030 kit 10.7MHz linear phase low distortion FM IF	7.67
92310 kit Stereo decoder with full pilot tone filtering (PLL)	5.35
93090 kit Stereo decoder, low noise and distortion	6.40

7252 FM tuner set, built - 1uV in, Audio out with mute and all HiFi tuner features. Varicap tuned. (mono) 24.00

7253 FM tuner set, built 1.2uV in, stereo out, with mute and all Hi Fi tuner features. Varicap tuned. 24.00

71197 Varicap tuned MW radio module. The best AM kit tuner, with 75dB AGC, 0.3% THD. 9.65

8001 kit 55kHz low pass, birdy, filter for stereo radio 1.75

2020 kit TDA2020 stereo amplifier, with special heatsinks 9.35

Famous TOKO COILS, Mechanical filters, ceramic filters, chokes etc.

455/470kHz IF coils 0.30	M41T 4kHz/455kHz Mech filt. 1.65
(1st, 2nd & 3rd) IFTs 0.70	M71T 7kHz/455kHz Mech filter 1.65
10.7MHz IFTs 0.32	C455B 8kHz/455kHz ceramic filt 0.55
Variable signal chokes:	C455C 6kHz/455kHz ceramic filt 0.55
2mH, 23mH, 36mH, 7mH	C050D 6kHz/470kHz ceramic filt 0.60
11.75mH 0.33	CFS107 10.7MHz cer. FM filter 0.50
Fixed chokes: (uH)	SFE6.0 6MHz TV sound IF filter 0.80
1.0, 4.7, 10, 33, 47, 100,	3132A linear phase FM IF filter 2.25
22, 33, 470, 1000 0.16	SFD470B 470kHz ceramic filter 0.75

PLEASE REMEMBER TO INCLUDE VAT - thank you !!

If you have read this far, you probably appreciate that AMBIT tends to specialize in the areas of wireless and TV that most component sources do not include. Our catalogue and price list continue this theme with coils, linear ICs etc. Catalogue 40p, price list free with SAE. Post is 22p per order - unless otherwise stated.

**37a HIGH STREET,
BRENTWOOD ESSEX
telephone 0277 216029**

Complete the coupon and we'll send you our complete, new catalogue.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

Clip the coupon now (enclosing a 10p stamp for postage) and we'll send you your copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

Heath (Gloucester) Limited, Dept. PE-116, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

The new Heathkit catalogue. Out now FREE.

To: Heath (Gloucester) Limited, Dept. PE-116, Gloucester GL2 6EE. Please send me a Heathkit catalogue. I enclose a 10p stamp for postage.

HEATH

Schlumberger

Name _____

Address _____

FREE
SOLDERING IRON
WORTH
£3.50
with all orders over
£30

EASY TERMS AVAILABLE
WITH HEATHKIT MONTHLY
BUDGET 1 P/AN

SAXON for professional sound

BREAK THE SOUND PRICE BARRIER!



Delivered U.K.
+ 8% VAT

With sound-light converter, synchronous motor twin turntables, and features that give you professional levels of operation. Full-range heavy duty speakers.


- 4-channel sound/light converter, variable speed plus chaser
- X-fade and P.F.L.
- Tape and microphone inputs
- Strong wood cabinets, Vynide covered, 100W output



with **CENTAUR**
100W STEREO
sound-light
mobile disco
£199.00

INCLUDES CONDENSER MIC AND HEADPHONES
ABSOLUTELY NO MORE TO BUY!!

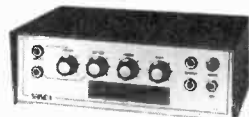Magnificent MINOTAUR 100 Professional 100W Amplifier



Compatible with all Saxon System 7000 units, this is a superb amplifier readily adaptable to a wide range of applications.

- 100 w.r.m.s into 8Ω
- Two mixed inputs, wide range bass and treble controls
- May be operated as a slave amplifier
- Extremely compact (27cm x 16cm x 10cm)
- Fully protected against all incorrect loads and short circuits
- Plug isolated terminals
- Silver anodised fascia

£49.50

PUT SYSTEM 7000 IN CONTROL NOW!

AUTOMATIC MIC OVERRIDE




- Ready to plug in—no soldering at all
- Stainless steel front panel
- Inputs for 2 ceramic cartridges/tape/microphone and autolafe
- Individual deck controls AND left/right fader
- Low noise (-80dB) 20Hz-50kHz ±1dB
- CONTROLS**—Master, Monitor, Volume, Selector, X-fade, etc.

BUILT
Mono £37.50
Stereo £53.50

MODULAR PCB ONLY
with all electronics
Mono £18.50
Stereo £27.50
Front panel £3.50

HIGH IN POWER—LOW IN COST! POWER AMPS 30-120 W.R.M.S.

(120W from £14.50)

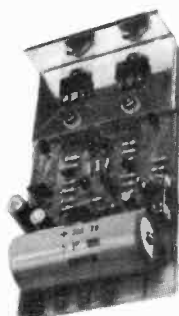

SA1208 (120 w.r.m.s./8Ω/95V) £21.00
SA1204* (120 w.r.m.s./4Ω/75V) £14.50
SA608 (60 w.r.m.s./8Ω/65V) £12.50
SA604* (60 w.r.m.s./4Ω/50V) £10.50
SA308 (30 w.r.m.s./8Ω/50V) £9.50

- Only 4 connections
- Distortion typically 0.4%
- Single supply rail
- Input—240mV
- Size—6in x 3in x 1in
- Individually tested and guaranteed

Power Supplies for

1 x SA1208—PM1201/8 £11.60; 2 x SA1208—PM1202/8 £15.30; 1 x SA1204—PM1201/4 £11.60; 2 x SA1204—PM1202/4 £15.30; 1 or 2 x SA608—PM601/8 £11.60; 1 or 2 x SA604—PM601/4 £11.60; 1 or 2 x SA308—PM301/8 £9.90.

SET ALIGHT WITH STROBE OR LIQUID WHEELS



- SUPERSTROBE**
- 1 flash/2 secs—up to 20/sec.
 - Compact black Bondone case
- PRO-STROBE**
- Giant 80 watt tube
 - Discharge energy up to 6 Joules
 - External trigger—audio up to 240V
 - 150 WATT LIQUID WHEEL PROJECTOR
 - Complete with wheel and 150 watt tungsten lamp
 - Wide range of extra effects may be attached

NOW ONLY
£19.75

NOW ONLY
£32.50

£31.50

NEW!! NEW!! NEW!!

SYSTEM 7000 LIGHTING CONTROL MK II

Successor to the LIGHTING CONTROL UNIT this new SYSTEM 7000 controller offers increased facilities and effects. Note these features:

- FOUR channels—up to 1000 watts each channel
- Twin sequencer—1 flash/2secs—20 flashes/sec
- INDEPENDENT DIMMERS ON EACH CHANNEL
- IC LOGIC circuitry PLUS RCA 8A Triacs
- STAINLESS STEEL PANEL TO MATCH OTHER SYSTEM 7000 UNITS

NOTE: SOUND/LITE PANEL SEQUENCER PLUS DIMMERS ALL IN THE SAME UNIT £42.50

QUADRAFFECT MODULE—same features as above but pcb only. Ready to connect and use £29

SYSTEM 7000 SOUND/LITE

THE tried and tested soundlite now in module form AND COMPLETE ON FRONT PANEL. THREE CHANNELS—THREE KW—INDIVIDUAL CONTROLS PLUS MASTER.

COMPLETE ON PANEL £24.75 MODULE ONLY £16.50


Mix it perfectly with modular SYSTEM 7000 MIXERS

Automatic Mic override

UP TO 20 CHANNELS MONO/STEREO/MIXED

- Inputs for all sources inc. mag. cartridge
- Wide range bass and treble controls
- ½W monitor power outlet
- Echo send/return facility
- Feeds most amplifiers
- With front panels, ready to use
- Individual monitor buttons

INPUT	£8-50	MIXER	£8-50
Mono	£8-50	Mono	£8-50
Stereo	£12-00	Stereo	£12-00
PCB Modules only		PCB Modules only	
Mono	£5-50	Mono	£5-50
Stereo	£9-00	Stereo	£9-00

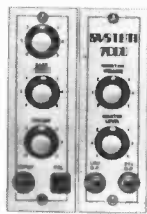

Power Supply
£7.50

NOW ALSO AT WALLINGFORD (BETWEEN READING and OXFORD) WITH SALES 7 SERVICE 6 DAYS A WEEK

FLINT HOUSE HIGH ST
WALLINGFORD OXON OX10 0DE
Phone (0491) 35529

SAXON EQUIPMENT IS
DESIGNED AND MADE
IN OUR OWN CROYDON
FACTORY



PRICES include carr. and packing. VAT must be added to all orders at 8%. C.O.D. 65p extra. S.A.E. all enquiries please

Orders by post—Please make cheques or crossed P.O.s payable to

SAXON ENTERTAINMENTS LTD.

327-333 WHITEHORSE ROAD, CROYDON, SURREY CR0 2HS

Telephone: 01-684 6385/0098

Shop Hours 9am-5pm (Lunch 12.30-1.30) Sat 9.30am-5pm Prices and specifications subject to alteration without notice Mail Order desk 10am-4pm Mon-Fri

TRADE ENQUIRIES
NORMAN ROSE
(ELECTRICAL) LTD.

London 01-837 9111 Birmingham
021 236 4710 Manchester 051 273
1598 Bradford Works 0274 26104

Send or phone your
ACCESS or
BARCLAYCARD
No for prompt attention
After 5.0 p.m. leave your
message on our answer-
phone 01-684 6385

HOW TO SUCCEED

ARE you unpopular at home? Do you wish to extend your circle of friends? Do you suffer from a guilt complex? If the answer to any of these is "yes", maybe you should try the PRACTICAL ELECTRONICS recipe. It's a dependable cure for any electronics addict who feels in danger of becoming branded as an anti-social type.

First of all, one important fact must be acknowledged. Constructing activities isolate one from the family circle for long or longish periods. Such absences may be warmly approved, resignedly accepted, or vehemently resented, according to the individuals involved! Be this as it may, there are ample compensations for family and friends, no less than for the constructor himself, to be derived from such hermit-like activities.

To prove this let us set down a three-part recipe for preserving harmony in the home, for establishing a good reputation in local society, and finally for looking after number one. What is more, all the essential ingredients are to be found within this month's issue.

To maintain good family relations, to demonstrate that all those hours spent closeted in den or workshop are not just wasted, we recommend the PE Orion Tuner. As fine an instrument as you could wish to grace chiffonier, sideboard or music centre. It will be a permanent testimony to the constructor's skill; an object for all to admire and to enjoy.

To further one's reputation outside the home, we recommend the Discostrobe. It's bound to be a winner, a real wow at the club or church hall on Friday night. Only trouble is the inevitable demand for the donor's services on this, that, and every other evening of the week. Firmness is required here. Fame may bring in its train demands upon valuable spare time that could severely restrict building activities. However gratifying public acclaim may be, don't let it upset your sense of proportion. One simply has to be selfish at times.

And thinking of number one, how about that Hazard Flasher for the car. It won't take long to make and what a blessing it might prove to be one day. (Non-motorists substitute any other "shorty" project from past, present, or future PE's, according to fancy.)

Other interesting recipes to suit particular occasions can be concocted from the great variety of designs offered in PE, month by month. With careful choice of ingredients, one is certain to achieve success at home and away. So don't feel guilty about it when you retreat to workshop or den with PE under your arm. Walk to your hobby head high, as befits one whose altruism is not at all in doubt.

F.E.B.

Editor
F. E. BENNETT

Editorial
G. C. ARNOLD *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4504

P. J. MEW
Phone: 01-634 4181

C. R. BROWN *Classified*
Phone: 01-261 5762

Make-up and Copy Dept.
Phone: 01-634 4372

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4504



F.M. STEREO TUNER

By D.S. GIBBS & I.M. SHAW

THE Orion Stereo Tuner was designed to complement the P.E. Orion Amplifier, which was published in PRACTICAL ELECTRONICS in January/February 1975. (See Advertisement on page 913.)

The same design philosophy has been used in that this tuner has been designed to give a very high standard of performance at modest cost and with easy construction. The overall cost of parts is in the region of £25-30 at the time of writing.

The circuit is very simple and can be aligned without any instruments, although it is advantageous if a voltmeter is available.

TUNER HEAD

Whilst it is possible to construct one's own tuner head, a high degree of constructional skill is required and optimum results cannot be obtained without the use of elaborate and expensive test equipment. To overcome this problem we have used a ready-made tuner head in this design. The tuner head used is a Mullard LP1186, which is readily available from various firms advertising in PRACTICAL ELECTRONICS.

With a tuning voltage supply of 13.5 volts the LP1186 (Fig. 1.1) will tune from 87.5 to 105MHz and it provides a gain of 30dB with input and output impedances of 75 ohms. A particularly useful feature is the built-in 10.7MHz bandpass filter. This provides a useful amount of selectivity at 10.7MHz and permits the use of only one ceramic filter element in the i.f. amplifier, which reduces costs and eliminates the need for matched ceramic filters.

I.F. AMPLIFIER

Transistor TR1 provides a voltage gain of about 20dB, with an output impedance of 330 ohms to match the Vernitron FM4 ceramic filter. There are some cheaper 10.7MHz ceramic filters available but we have found that these tend to have inferior selectivity to the Vernitron type.

SPECIFICATION

Sensitivity: 1.5 μ V for 20dB quieting, 2 μ V for 30dB quieting

Tuning Range: 87.5 to 105MHz

Signal to Noise Ratio: 60dB unweighted for inputs over 50 μ V

Distortion: Less than 0.5% at 100% modulation, 1kHz

Output: 200mV r.m.s. at 100% modulation

Selectivity: 3dB down at \pm 100kHz bandwidth
30dB down at \pm 200kHz bandwidth

Image Rejection: 40dB

I.F. Rejection: 65dB

Stereo Separation: 30dB at 1kHz

Aerial Impedance: 75 ohms

The selectivity curve of the tuner head and i.f. amplifier is shown in Fig. 1.2 and it can be seen that the output remains relatively constant over a bandwidth of \pm 100kHz, but falls off rapidly outside this band. At \pm 200kHz the attenuation is 30dB to give good rejection of adjacent channels.

Fig. 1.3 shows the output level and signal-to-noise ratio of the tuner against aerial voltage. The tuner has a sensitivity of 1.5 μ V for 20dB signal-to-noise ratio and 2.0 μ V for 30dB, for mono reception. On stereo operation signal levels some 20dB higher are necessary to obtain the same signal-to-noise ratio because of the very much greater bandwidth of the stereo signal.

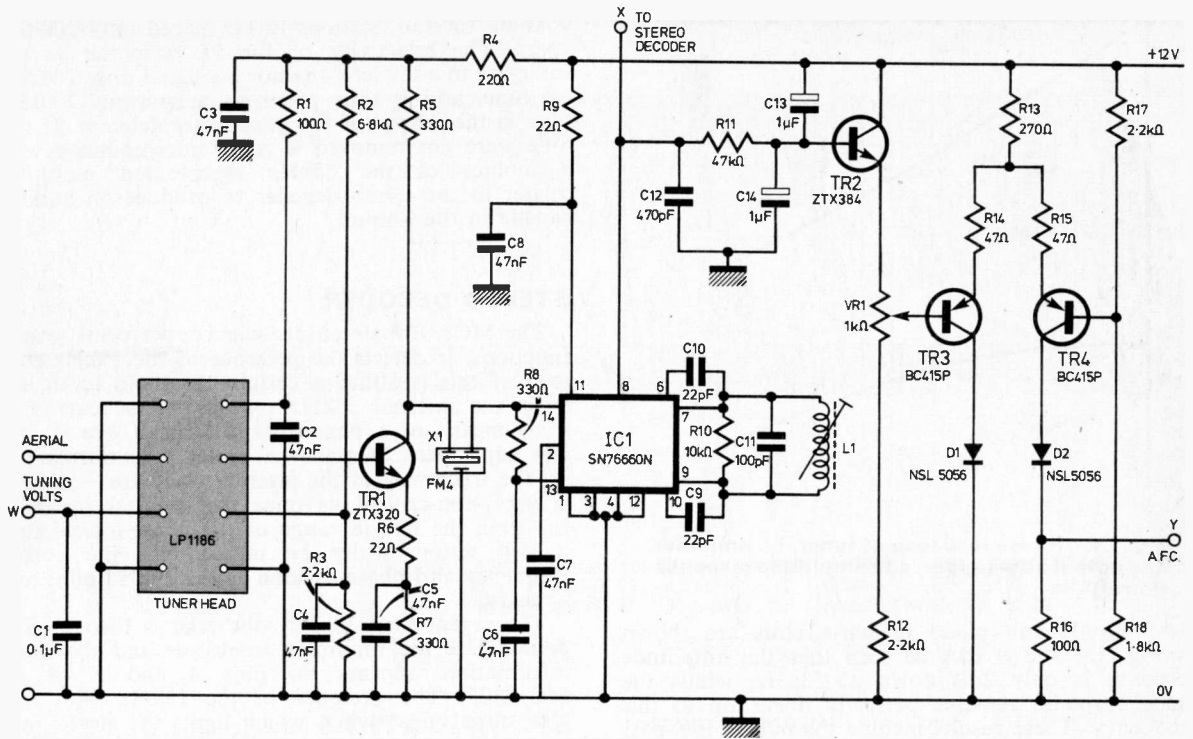


Fig. 1.1. R.F. and discriminator circuits

LIMITER/DISCRIMINATOR

The output from the ceramic filter drives the SN76660N limiter/discriminator i.c., which provides six stages of amplification and limiting followed by a quadrature detector (Fig. 1.1).

The component values in the quadrature detector have been chosen to give a distortion level of less than 0.5 per cent (typically 0.3 per cent) at 100 per cent modulation level. The distortion is of low order—mainly second and third harmonics—and is imperceptible to most listeners. It is possible to obtain lower distortion than this by the use of two coupled resonant circuits in the quadrature detector but this unfortunately introduces alignment problems

that would be beyond the resources of most amateur constructors.

For stereo reception it is equally important for the detector to have a flat amplitude response and a linear phase response for modulation frequencies up to 53kHz, as failure in these requirements will lead to poor stereo separation. A linear phase/frequency response means, in effect, that the time delay through the whole tuner is constant regardless of the modulation frequency. Thus a complex waveform will come out of the system with all the harmonic components in exactly the same phase relationship to each other as when they went in. This keeps the pilot tone in the correct phase with the multiplex sidebands and gives good separation.

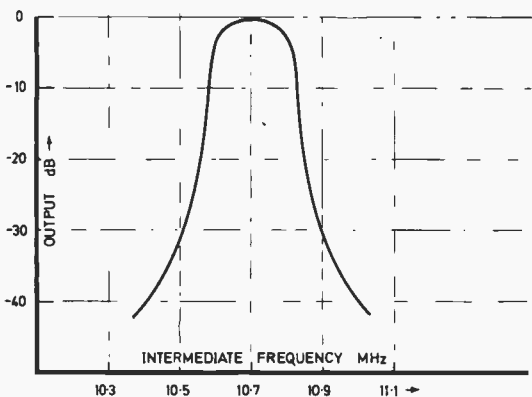


Fig. 1.2. Selectivity curve

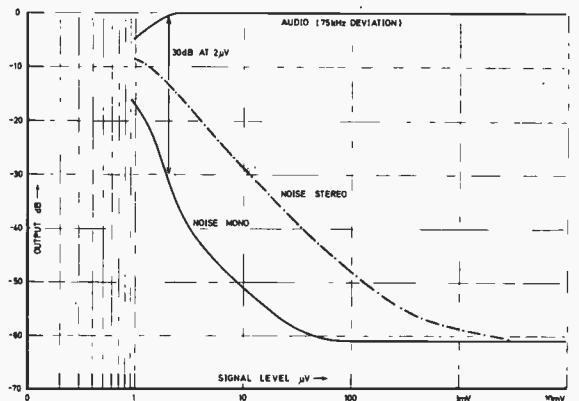


Fig. 1.3. Signal/noise graph for tuner

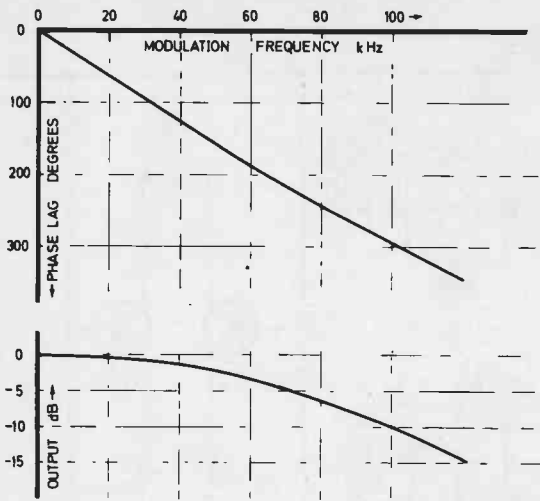


Fig. 1.4. Phase response of tuner, i.f. amplifier and output filter (upper) and amplitude response (lower)

Amplitude and phase response plots are shown in Fig. 1.4 and it can be seen that the amplitude response is only 2dB down at 53kHz, whilst the phase response remains perfectly linear up to this frequency. These results include the 60kHz low-pass filter included in the stereo decoder to remove "birdies".

BIRDIE FILTER

TR5 is an emitter follower and provides a low impedance drive for the MC1310P stereo decoder (Fig. 1.5). At the same time it acts as an active filter with capacitors C12, C15, and C16 giving a 3-pole low pass response. The response curve is -3dB at about 60kHz and approximately -37dB at 200kHz.

This filter is desirable because in some areas it is possible for f.m. stations to be spaced only 200kHz apart. The selectivity of the i.f. amplifier is not sufficient to completely remove a signal only 200kHz off tune, and it thus produces a spurious 200kHz tone in the output of the quadrature detector. If this tone were not removed it could intermodulate with harmonics of the 38kHz regenerated multiplex carrier in the stereo decoder to produce an audible whistle in the output.

STEREO DECODER

The MC1310P stereo decoder i.c. performs several functions. It detects the presence of the 19kHz pilot tone, if this is above a certain threshold level, and locks the internal 38kHz regenerated subcarrier to it by means of a phase-locked loop. There is only one adjustment to make—a preset potentiometer to set the frequency of the internal oscillator—and this is very non-critical as once the internal oscillator is within the pull-in range of the phase-locked loop it will automatically be pulled into the correct frequency and phase as soon as the 19kHz pilot tone appears.

The regenerated 38kHz subcarrier is then used to demodulate the multiplex sidebands and the audio information appears on pins 4 and 5 of the MC1310P. The presence of the 19kHz pilot tone also turns on a switch which lights the stereo indicator lamp.

The distortion generated by the MC1310P is very low, typically 0.1 per cent at the signal level used in this tuner.

The output from the stereo decoder contains a certain amount of 19kHz pilot tone and 38kHz subcarrier. These spurious signals are attenuated by the 50μs de-emphasis network on the output of the decoder, comprising components R25, C23, and R26, C24. Further attenuation is provided by a simple 16kHz low pass filter comprising R30, C27, and R31, C28.

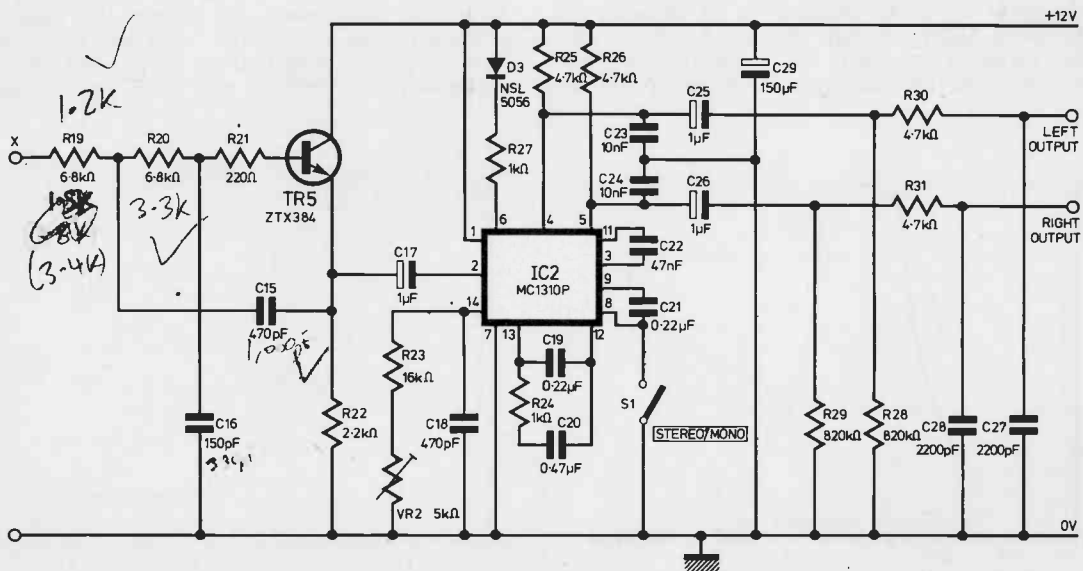


Fig. 1.5. Stereo decoder

COMPONENTS . . .

Resistors

R1	100 Ω
R2	6.8k Ω
R3	2.2k Ω
R4	220 Ω
R5	330 Ω
R6	22 Ω
R7-R8	330 Ω (2 off)
R9	22 Ω
R10	10k Ω
R11	47k Ω
R12	2.2k Ω
R13	270 Ω
R14-R15	47 Ω (2 off)
R16	100 Ω
R17	2.2k Ω
R18	1.8k Ω
R19	6.8k Ω
R20	6.8k Ω
R21	220 Ω
R22	2.2k Ω
R23	16k Ω
R24	1k Ω
R25-R26	4.7k Ω (2 off)
R27	1k Ω
R28-R29	820k Ω (2 off)
R30-R31	4.7k Ω (2 off)
R32	220 Ω
R33	1k Ω
R34	5.6k Ω
R35	6.8k Ω
R36	150 Ω
R37	68 Ω
R38	47k Ω
R39	220 Ω
R40	47 Ω
R41	4.7k Ω
R42	470 Ω
R43	4.7k Ω
R44	22 Ω

All 0.5W 5% carbon film

Capacitors

C1	0.1 μ F Mullard C280 polyester
C2	47nF 12V disc ceramic
C3	47nF 12V disc ceramic
C4	47nF 12V disc ceramic
C5	47nF 12V disc ceramic
C6	47nF 12V disc ceramic
C7	47nF 12V disc ceramic
C8	47nF 12V disc ceramic
C9	22pF polystyrene
C10	22pF polystyrene
C11	100pF polystyrene
C12	470pF polystyrene
C13	1 μ F 35V tantalum bead
C14	1 μ F 35V tantalum bead
C15	470pF polystyrene
C16	150pF polystyrene
C17	1 μ F 35V tantalum bead
C18	470pF polystyrene
C19	0.22 μ F Mullard C280 polyester
C20	0.47 μ F Mullard C280 polyester
C21	0.22 μ F Mullard C280 polyester
C22	0.047 μ F Mullard C280 polyester
C23	0.01 μ F Mullard C280 polyester
C24	0.01 μ F Mullard C280 polyester
C25	1 μ F 35V tantalum bead

C26	1 μ F 35V tantalum bead
C27	2,200pF polystyrene or polyester
C28	2,200pF polystyrene or polyester
C29	150 μ F 16V electrolytic
C30	10 μ F 35V tantalum bead
C31	0.01 μ F Mullard C280 polyester
C32	1,000 μ F 25V electrolytic
C33	0.01 μ F 750V disc ceramic

Potentiometers

VR1	1k Ω preset
VR2	5k Ω or 4.7k Ω preset

Switches

S1	S.p.d.t. miniature toggle or slide
S2	S.p.d.t. miniature toggle or slide
S3	Rotary mains

Semiconductors

TR1	ZTX320 Ferranti
TR2	ZTX384 Ferranti
TR3	BC415P Ferranti
TR4	BC415P Ferranti
TR5	ZTX384 Ferranti
TR6	ZTX384 Ferranti
TR7	ZTXA20 Ferranti
TR8	ZTXA20 Ferranti
TR9	ZTX108 Ferranti
TR10	ZTX550 Ferranti
TR11	ZTXA20 Ferranti
D1	NSL5056 National
D2	NSL5056 National
D3	NSL5056 National
D4	BZV19 C6V2 Ferranti
D5	BZV19 C11 Ferranti
D6	ZS170 Ferranti
D7	ZS170 Ferranti
IC1	SN76660N Texas, or TBA120A (ITT)
IC2	MC1310P Motorola

} All I.e.d.s

Tuner Head

Mullard LP1186

Inductor


L1-24 turns of 30 s.w.g. enamelled wire close-wound on a Neosid 6mm coil former type 722/1, with core type 4 x .5 x 10/900SL screening can type 7100 and base plate type 5027/4PLD. The whole coil former assembly is available from Neosid under type No. A6.

Miscellaneous

- 1 Printed circuit board (Davian Electronics)
- 1 Case type GB1 (H.M. Electronics)
- 1 Vernitron ceramic filter type FM4 (Home Radio)
- 1 Push button tuner unit
- 1 15-0-15 volt mains transformer (R.S. Components type 207-217)
- 1 20mm fuseholder and 1A fuse
- 1 DIN 5 pin 180° socket
- 1 Belling Lee insulated co-ax aerial socket
- 1 Control knob (Eagle type K30/3)

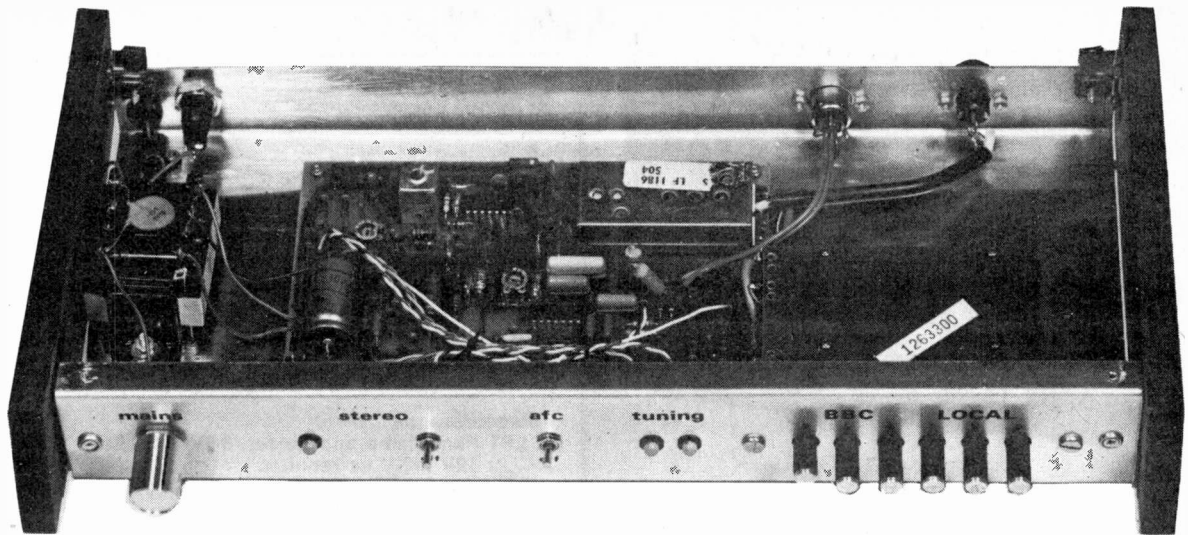Screws, spacers, grommet, connecting wire, solder





The design of an a.f.c. system presents certain problems in that for good stability a strong a.f.c. action is desirable—but this in turn introduces a tendency for the tuner to lock on to the wrong station when it is first switched on.

This problem has been overcome in the Orion Tuner by the use of an a.f.c. amplifier which provides strong a.f.c. action over a limited range of about $\pm 100\text{kHz}$, but which saturates beyond this range. Thus if the tuning is within 100kHz of the station the a.f.c. will come into action and pull the tuning in to the correct frequency, but if the error is more than 100kHz there will be no effect.

The amplifier also has ideal characteristics for use as a fine tuning indicator and the tuning is indicated by two l.e.d.s in series with the collectors of TR3 and TR4. The tuning is adjusted so that both lamps glow with equal brightness.

TUNING VOLTAGE REGULATOR

The Mullard LP1186 tuner head and the push-button tuner unit require a supply voltage of 13.5 volts at about 1mA. This is provided by transistor TR6 and Zener diode D4 (Fig. 1.7). The circuit operates as follows. As the supply current rises, the voltage across the Zener diode also increases because of its finite slope resistance. However, the increase in current through the transistor causes an increase in the voltage drop across resistor R37. This reduces the output voltage, and for a limited range of supply current the reduction in output voltage caused by R37 can be made to compensate for the increase in Zener voltage, by suitably choosing the value of R37.

Good thermal stability is also achieved because the positive temperature coefficient of the Zener diode is approximately matched by the negative temperature coefficient of the transistor base-emitter junction. This keeps the output voltage stable with variations in ambient temperature.

To further increase stability and ensure low ripple the regulator circuit is fed from a constant current source comprising TR7 and TR8.

A.f.c. action is provided by connecting the output of the a.f.c. amplifier to the top of R33. Thus any deviation in the output voltage of the a.f.c. amplifier

from its nominal value of 1 volt causes a corresponding variation in the tuning voltage to compensate for the tuning error.

POWER SUPPLY

The power supply for the tuner is 11.7 volts at about 60mA, which is provided by TR9, TR10, and TR11. The circuit used has the advantage of providing very low ripple (approximately $50\mu\text{V}$). This is desirable because the output of the stereo decoder appears in series with the h.t. rail and so any ripple on this rail would appear in the audio output.

Next Month: Constructional details and test procedures

NEWS BRIEFS

Transatlantic Microprocessor Link

ONE of Britain's largest i.c. manufacturers, G.E.C. Semiconductors Ltd., has decided to market the American Intel microprocessors, rather than develop yet another design of their own. G.E.C. believe that it makes sense to devote its own research and development capacity to strong support activity for the proven range of Intel products, and in this connection have just announced details of what is claimed to be a world leadership in MPU software development, the RCC80 Coral 66 Compiler. This compiler, available ex stock for £1,500, is designed for use with the Intel 8080A microprocessor, it runs on an MDS800 development system, and is designed to reduce the cost of producing reliable microprocessor software.

Coral 66 is the British Government Standard high level language for real time and process control applications, and is widely used in defence and research establishments and in nationalised and other large industries. G.E.C. Semiconductors Ltd. chose Coral 66 because of its universal acceptability as an independently defined real-time language, and its particular relevance to microprocessor development in many of its current fields of application.



COMPONENTS . . .

Resistors

R1, R2 47k Ω

Capacitor

C1 10 μ F tantalum 35V

Semiconductors

IC1 NE555 timer

D1 1GP10 or similar germanium diode

Relay

RLA 3 pole changeover with 5A contacts, 6V or 12V coil as required, see text (Pigmy mains relay-Electrovalve)

Miscellaneous

LP1 Panel lamp and holder, 6.5V 0.3A or 12V 2.2W as required

S1 S.p.s.t. switch (car accessory type)

Printed circuit board

8-pin DIL i.c. socket (optional)

4-way connector block; 10A cable for external connections; Case, 100 x 65 x 50mm approximately; 2 "Scotchlok" connectors

WITH so many cars on the roads these days, a breakdown can lead to a very hazardous situation. It was with this thought in mind that the unit to be described was constructed. It can be used on both 6V and 12V electrical systems with either positive or negative earth, and is connected to the car electrics with only four wires. The flashing rate, as required by law, is approximately one per second.

CIRCUIT DESCRIPTION

The hazard flasher uses the now common NE555 timer i.c. connected in the astable mode to give a continuous pulse output. The circuit diagram and connection details are given in Fig. 1.

Capacitor C1 charges through R1 and R2 from a potential of one-third of the supply voltage up to a potential of two-thirds of the supply voltage, and then discharges again to one third of the supply voltage when the internal comparator in the NE555 causes the potential at pin 7 to go low.


The charging time is approximately $0.7(R1 + R2)C$ and the discharging time $0.7R2.C$. The frequency of operation is approximately

$$\frac{1.44}{(R1 + 2R2)C}$$

HAZARD WARNING

FLASHER

By C. J. COKER

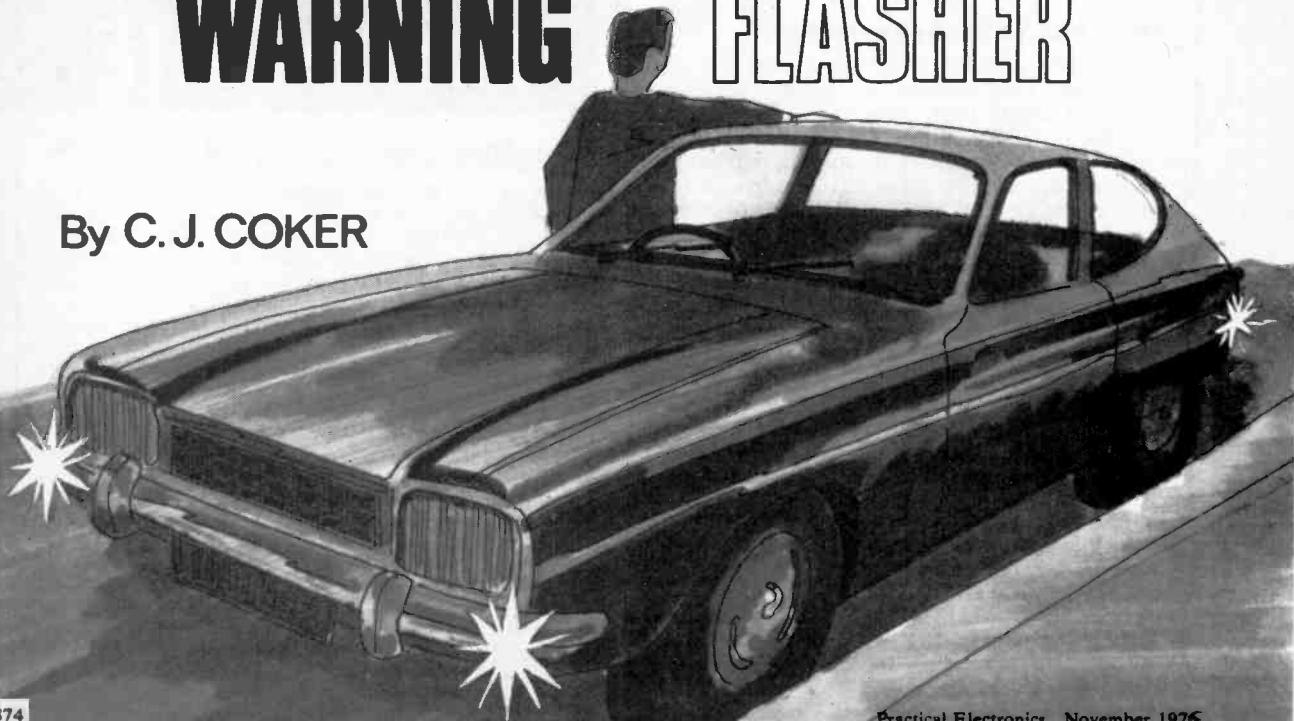

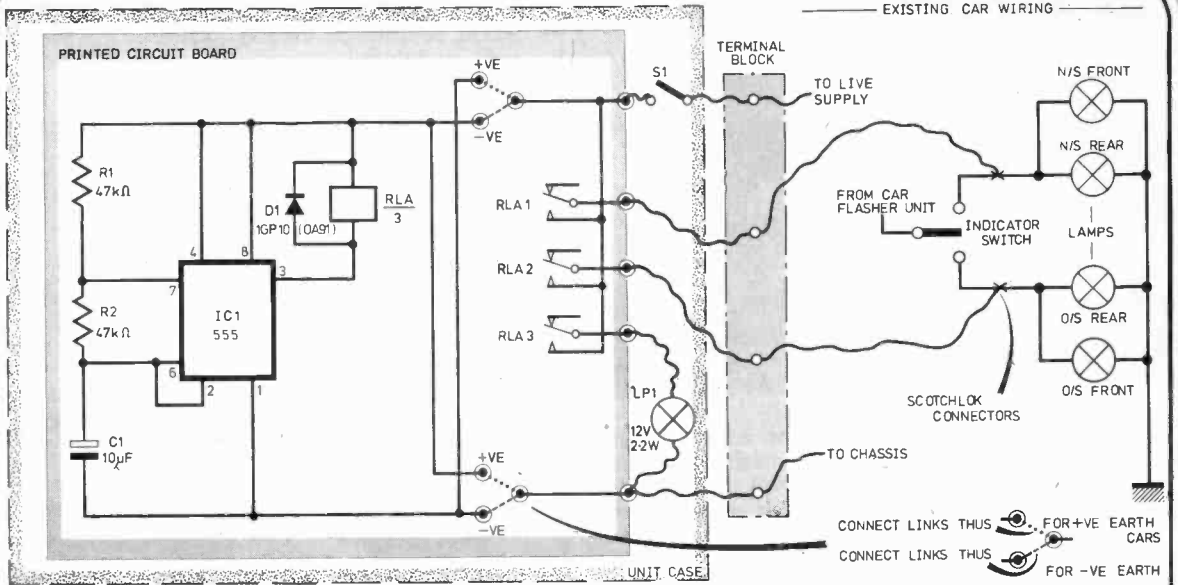


Fig. 1. Circuit diagram and connection details


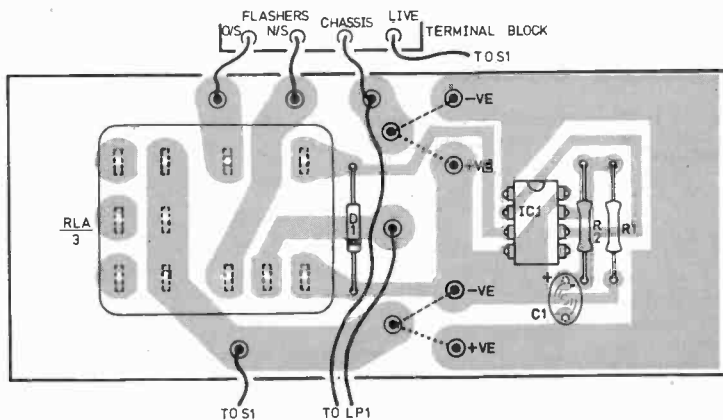
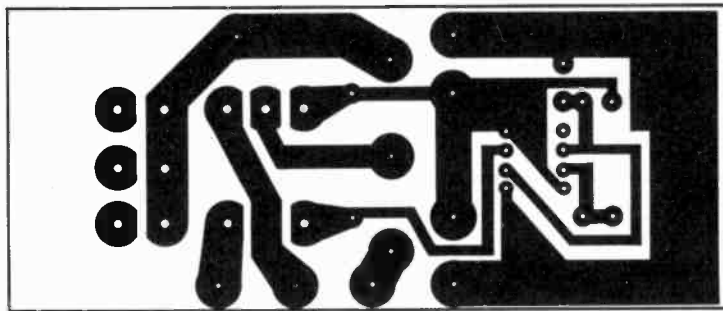


Fig. 2. Printed circuit board pattern and component layout

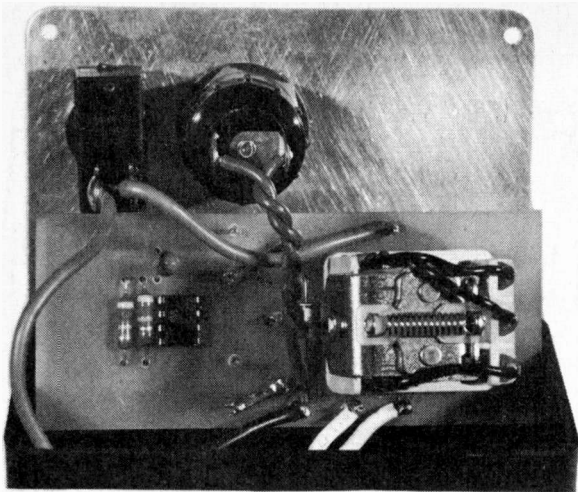

The output at pin 3 is a square wave which is high whilst C1 is charging and low when discharging. The diode D1 serves to suppress voltage spikes, generated when the relay is de-energised, which might otherwise damage the i.c. The lamp LPI indicates that the unit is functioning correctly.

CONSTRUCTION

The circuit is constructed on a small printed circuit board. Fig. 2 shows the component layout and track pattern. Care should be taken when soldering the 555, as damage can easily be done. An i.c. socket can be used if desired. The relay can be any miniature type with 5A contacts, provided it does not take more than about 150mA from the supply. It can be mounted on or off the board, depending on its shape and size.


The unit can be housed in any suitable small metal or plastics box, and mounted underneath the dashboard. The on/off switch and warning lamp should, of course, be fitted on the front panel of the box.

INSTALLATION

The live supply connection is taken from the fuse box of the car, or if it has no fuse box, via a line fuseholder with a 10A fuse in circuit. The supply must be on when the ignition is turned off. The earth connection should be taken to a convenient car chassis point.

The existing wires going to the indicator lights can be located at the back of the turn indicator switch, and the two output wires tapped in using "Scotchlok" connectors, available at motor accessory shops.

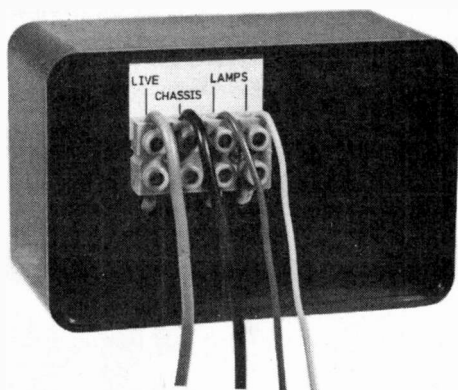The two links on the printed circuit board must be wired accordingly for a positive or negative earth supply, as shown in Fig. 2. ★



Readout —

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

Karnaugh Map

Sir,—May we draw your attention to page 652 PRACTICAL ELECTRONICS, August 1976, "Karnaugh Map Display" where Mr Cartledge mentions how the idea of constructing a "real time" Karnaugh map display occurred to him.

We wish to claim the design as our manufactured product which has been available and sold for a number of years to a great many establishments, colleges, universities, etc. Enclosed herewith you will find

an illustration, together with a booklet written by Professor Reeves of Keele University and available from us free upon payment of 15p for postage and packing.

It would be very much appreciated if you feel you could make these facts known in a future publication to your readers.

We wish your journal long success.

J. Fairhurst,
Managing Director,
Fairhurst Instruments Ltd.,
Wilmslow, Cheshire.

Our Contributor replies

Until I saw the above letter I had not heard of Fairhurst Instruments Ltd., but I must admit that their product is very similar in principle to the unit described in my article. However, how many ways can one display a four-function variable on sixteen l.e.d.s!


It was after a class in which mappings were done on paper and, during which, as an exercise a mapping unit was being built on Farnell Logikit, its display being on an oscilloscope, I thought to myself that it would be nice to have some self-contained Karnaugh Mapping Units displaying their outputs on light-emitting diodes. From that thought or "idea", myself and my lecturer friend designed the circuitry and I built the units and submitted the design for publication.

I am sorry that the phrase in the second paragraph of my article has, perhaps, been misinterpreted, and I can only say that had I known about Fairhurst's product I may have saved myself a great deal of hard work.

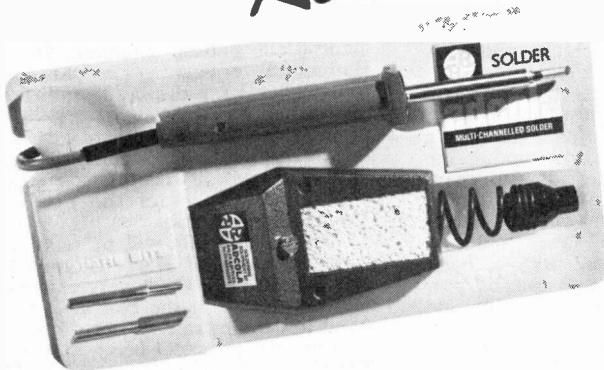C. Cartledge,
Stafford.

SPECIAL PRE RELEASE INTRODUCTORY OFFER!

Exclusive to
PRACTICAL ELECTRONICS
Readers!



ADCOLA SOLDERING KIT

WITH SAFETY APPROVED IRON

£5.95

INCLUSIVE OF POSTAGE AND PACKING

MANUFACTURER'S RECOMMENDED RETAIL PRICE £6.75

A new soldering instrument is the star feature of this Adcola Products soldering kit. It has been developed to conform generally to British Standard BS 3456, 2:14 and to world-wide safety precautions. Known as the Invader "S" 646—the "S" stands for "safety"—it is flash tested at 2,000 V (far in excess of most safety standards) and the accent is on complete user safety without sacrificing efficiency or ease of use. The iron is thermally controlled to provide a constant level of the correct heat for soldering at 400 degrees C. Each model weighs less than 2 oz, and two metres of cable, fitted with a cable protector, are provided. The standard soldering tip provided is $\frac{3}{16}$ in. (4.7 mm) diameter but two alternative bits of $\frac{1}{8}$ in. (3.2 mm) and $\frac{1}{4}$ in. (6.3 mm) diameter are included to provide complete versatility in use. These bits are easily inserted in the hexagonal shim at the end of the tool as required.

An Invader stand is also contained in the kit to provide the user with a mobile and safe receptacle for the hot soldering instrument. The stand features an integral sponge for cleaning excess solder from the soldering bits and two holders to contain the spare bits. A wide angle spring holder is mounted on the base of the stand at an angle of about 45 degrees and the soldering tool is simply inserted into the holder when not in use.

To complete the kit a packet dispenser of Adcola solder wire—which contains its own flux—and a guide to soldering are also included.

The kit is presented in an eye-catching pack consisting of a lemon coloured plastic tray which incorporates recessed areas to locate each part. This base is covered by a crystal clear plastic lid to display the components in an effective manner.

Remittances must be by postal order or cheque (name and address on back of cheque please), crossed, and made payable to Adcola Products Ltd.

Please complete both parts of the coupon below in **BLOCK CAPITALS**.

To: Adcola Products Ltd. (P.E. Offer)
 Adcola House, Gauden Road, London SW4 6LH
 Please send me the Soldering Kit(s) as indicated
 at £5.95 each.

I enclose P.O./Cheque No. Value

No. of kits required

Name

Address

Tel. No. (Home or Work)

No. of kits required

Name

Address

From: Adcola Products Ltd. (P.E. Offer)
 Adcola House, Gauden Road, London SW4 6LH

Cut Round Dotted Line



THIS year's Musical Instrument Trade Fair (August 15-19) was spread about last year's venues, namely the Bloomsbury Centre, Russel Hotel, etc., with the exception that pianos and organs shared the Connaught Rooms.

SYNTHESISERS

Boosey and Hawkes featured a sound booth with the impressive ARP family of synthesisers; the single oscillator Axxe and multi-voiced Odyssey and 2600 and of course Little Brother which provides a lot to expand the versatility of these instruments making possible string orchestra and other instrumental ensemble effects.

Notable newcomers was the ARP Sequencer and the Omni. In principle a sequencer can be thought of as a versatile function generator. Unlike the normal function generator that provides a time-varying voltage that cycles about this can prove a complete sequence of output voltages—which are immediately programmable—for control of a synthesiser.

The ARP Sequencer in demonstration proved an extremely creative tool, providing arpeggios, "walking eight" accompaniments and melody lines. Programming is done through sixteen switches. Pitch levels can be rapidly set up and a musical pattern set which can be easily varied. Accent patterns, harmonies and rhythms can also be arranged. In conjunction with the synthesiser this is a powerful composing aid.

The ARP Omni in contrast is an outstanding keyboard for live performance. Completely polyphonic it allows one to call up string choruses in the right hand with all those gorgeous harmonic products of phasing which one associates with string ensembles, and in the left hand, brass synthesis. Since you can mix the stereo image at will and contour the sounds this is a very potent entertainment outrider to an organist.

MICRO-MOOG

Latest of Moog products is the Micro-Moog T.M. This is a single oscillator synthesiser but artfully augmented with a continuous mix of a square waveform either one or two octaves lower which overall provides a doubling effect. Square, sawtooth, variable rectangular and a mixture of variable and rectangular waveforms are available. A feature is that both the oscillator and filter control circuits are thermostated and heated which apparently makes for total pitch stability.

This is a live performance instrument which will allow you to compete with a guitarist as it includes a pitch bend ribbon and modulation wheel for those specially expressive sounds.

Brodr Jorgensen offered in its synthesiser range the modular System 100. Starting with a basic synthesiser other units can be purchased, as circumstances allow, to culminate in a studio sound synthesiser. The additions include an expander, sequencer and mixer.

ORGANS


This year the general emphasis for organs was towards full specification models in the middle price range. There were quite a few new models but very few new features.

Some sales blurb even tried to capitalise out of the single primary tone oscillator found in their instruments. This Lowrey patent has been around now for seven years.

Once again the fun machines were very much in evidence with Baldwin perhaps stealing the edge with their "FunMachine". This has two in-line keyboards—the left of one octave the right of three. A one fingered rhythmic accompaniment is played on the left from a choice of seventeen. Likewise a one fingered solo line can be picked out on the right. Once again one of those awful acronyms ASR (Automatic Solo Registration) is available to choose the correct voices (?) to go with the rhythms for those tots who are confused in selecting a registration. Major and minor chords are automatically available in the left hand with rhythm on touch or continuously available.

It's well known that repeated rhythm patterns become very wearisome and many manufacturers now incorporate pattern changes. Some Hammond organs cycle through four with a lamp display to indicate the sequencing. However, there are devices that help to mitigate such as the magic strums, arpeggios and "walking-bass" figures that are such an exciting feature of the Lowrey "Magic Genie" series.

Most organ buffs will be familiar with the name of Harry Stoneham and Jerry Allen. These very capable musicians were at the Norlin Music stand to demonstrate various Lowrey instruments, principal being the new Symphonic Citation Theatre Spinnet organ. This includes a Bass Symphoniser that simulates the attack and timbre of brass instruments and an Orchestral Symphoniser which provides authentic piano and guitar yet I have still to hear anything to beat the jazz violin sounds conjured up by Bill Skidmore playing an

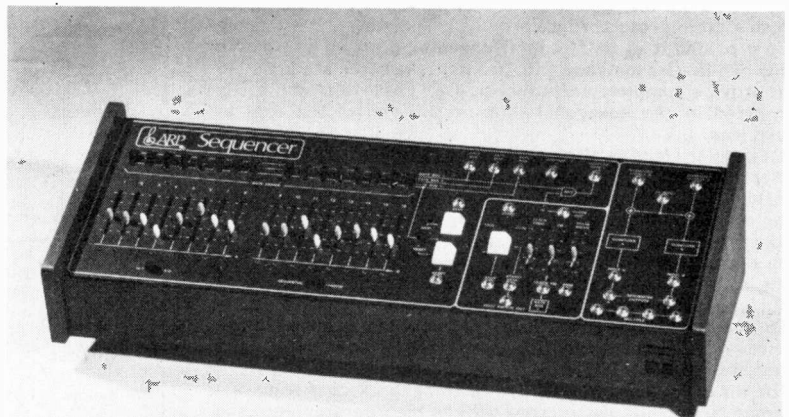

The ARP Sequencer

Orbit III keyboard on an 805 model Wurlitzer—real vintage Grappelli. At £3,300 this versatile instrument represents good value as its character can be readily swung from liturgical through theatrical to jazz.

M.C.H. Manufacturer's Centres Ltd., a British subsidiary of the Dutch parent company displayed the Eminent 2000 Grand Theatre organ with a specification that would fill this page and costing £4,500. At nearly half this price you can get the Eminent 310 with ARP Pro-Soloist synthesiser (preset voices).

AMPLIFIERS

Many musicians favour a valve amplifier with its "heavy" harmonically rich sound produced through the large proportion of third harmonic distortion as it approaches its rated output. Comparatively, a transistor amplifier is distortion free and provides a guitarist with a musically "thin" sound which appears sterile.

H.H. Electronics have seemingly solved this in their V-S range of instrument amplifiers, here they've invested solid state with a foot-switch controllable "valve sound". The secret is a harmonic generator which creates an overtone character identical to a pentode valve output stage.

Obviously this is a useful innovation as the footswitch can immediately remotely control the amplifier for a muddy guitar solo followed by clear solid state amplification, say for a keyboard.

Among new items displayed by Omece was a voice box which will be recognised by many as used by Stevie Wonder. The box connects

between instrumental amplifier and speakers; when a switch is pressed the instrument output suitably attenuated and diverted to the box transducer, usually a horn driver, then via a tube to the performer's mouth which he shapes to the instrument sound (very effective when the instrument is a synthesiser). The new sound is then passed to the microphone and P.A. system.

The Omece Digital Amplifier is certainly different with futuristic push buttons and not a knob in sight.

This is a 130W solid state unit which is designed to take a lot of the headaches away from the performer as it is possible to recall any one of four preset combinations of tonal equalisation (i.e., bass, middle or treble with volume control) complete with reverb, sustain or fuzz by pushing control buttons. Here pots and switches have been substituted by digital methods. Adjustments can be made to the selected channel while playing, any alteration being automatically transferred to the memory for that channel when a new one is selected.

The unique plus about the amp is that particular sounds can be precisely repeated at every performance by simply punching buttons.

OTHER UNITS

I suppose it had to come; the "rotating sound" or Leslie effect has gone solid state so Roland (Brodr Jorgensen) announces with their Revo (120W) and Revo 120 (70W). These are three channel units which make clever use of electronic phasing techniques and numbers of speakers, to beguile the ear with amplitude and frequency modulations normally associated with the

genuine article. Both units include reverb, bass balance and an effective "rotor" speed selection. Since the price nearly equates with the Leslie and Sharma organ-speakers I don't expect the status-quo to be very much disturbed.

Another area which has genuflected the knee to electronics (this time "bucket-brigade" techniques) is tape-echo. Carlsbro presented an excellently engineered electronic echo—the Mantis—which is claimed to create a wide range of clean echo, reverb and phasing effects.


For the record Brodr Jorgensen have also come out with such a machine with "digital chorus" whilst I have no information on this it seems obvious that either unit could duplicate as rotary speakers but without the sophistication of the Revo units.

From Hornby Skewes comes a whole range of effects units—briefly—the Jen Motorphaser, a rotating sound footswitch which has chorus and tremolo speeds with simulated motor acceleration and deceleration; and the Systech range of pedals. These included a Harmonic Energiser with gain boosts, of up to 100 times for harmonics. An Envelope Computer for harmonic shaping and rate changing and a Flanger which effectively augments keyboards, vocals, drums, cymbals and all P.A. effects.

A demand for a modular sound effect system that could be mains powered and enable the player to have several units interconnected, all switchable with preset controls has resulted in the Black Box models by Eurotec. Fuzz, phase, sustain, octivide and a v.c.f. are available and these effects can be varied with the pedal that completes the system.



Eminent 2000

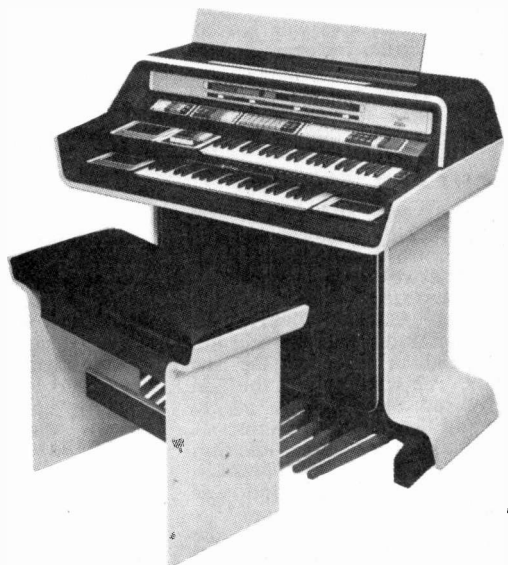

Thomas 2001

THE RETURN TO THE MOON

The next lunar mission, planned by NASA, will be accomplished with a pair of satellites orbiting the Moon. The present plan sets a date in 1980. NASA have already announced the outline plan and the experimenters.

The principal satellite will remain on station for about a year. This station will be in a polar orbit and will therefore make the first global survey of a body in the solar system other than the Earth. It is expected that the whole of the surface of the Moon will be observed. Continuous survey will be made of the gravitational variations, changes of magnetic field and the heat flow in the Moon.

It will also be possible to extend the experiments to determine the chemical and mineral composition of the surface. Since there has been very extensive examination of the lunar rocks, brought back by the *Apollo* missions, some anomalies have caused concern. For example, only two pieces of rock were identified conclusively as being part of the original crust of the Moon. The time scales were so at variance with those of the Earth that it seemed possible that the Moon was derived from a different source.

However, because of the *Apollo* manned observations together with the observatories left by each mission, to continue operations on the Moon itself, a number of the doubts have been resolved. It is established that the crust on the far side of the Moon is much thicker and more mountainous than the side facing the Earth. The Moon then shows today what the Earth, Venus and Mars once were.

It was thought that all debris would have been swept up within 700 million years of the original formation. Clearly this was not so. The Mare Imbrium for example was probably caused by a body the size of Cyprus. These are some of the problems that this new lunar mission may solve.

DROUGHT AND THE SUN

In recent years and particularly since the *Skylab* missions the Sun has been shown to be anything but a stable and well behaved body. It has been suggested by John A. Eddy of the High Altitude Observatory, Boulder, Colorado, that the Sun has been anomalous twice in the last 900 years. The condition of the Sun is partly indicated by the aurora activity and the number of sunspots. A very notable period when the Sun went "anomalous" was between 1645 and 1715. This period was called the "Maunder Minimum".

The records from all over the world for this period show that the Sun behaved in a most strange way.



BY FRANK W. HYDE

There were very few sunspots in some years in this "Maunder Minimum" and in others none at all. Aurorae were almost non-existent and it is interesting to remember that this was a period when Edmund Halley the great astronomer watched the skies almost nightly. Yet he was nearly 60 before he observed aurorae in London. During the "Maunder Minimum" the corona was faint with little structure compared with that expected now.

During such times the galactic cosmic ray particles penetrate the solar system to a much greater degree. The particles follow the magnetic field lines and enter the atmosphere destroying ozone. They also produce carbon 14 which is later absorbed by rocks, plants and trees.

Another consequence during that period was the change of climatic conditions. Europe had its coldest period for centuries. Tree rings in the USA showed erratic patterns indicative of drought.

There are signs that an anomalous state is occurring now. At the moment a drought period is beginning.

The Soviet Union is also finding agreement on these points. They have recently reported that the Arctic areas are getting colder. The north pole has already entered upon a new phase of harsh conditions. In Leningrad a survey of the North Sea covering the last 50 years has shown that the warming up period began to lessen in the 1940s and is getting progressively less. This means that the warming period which enabled the development of transport beyond the Arctic circle is reducing again. The ice is thickening and the icefields are extending southwards. Also the areas in Russia's Arctic coastline have suffered a shortening of the summer

period by a month. Soviet observers believe that these conditions will continue till the year 2000.

It is clear from space observations that the Sun is a much more complicated body than was supposed. In the present, researches into the harnessing of solar energy space techniques are likely to have great demand. From the knowledge gained in solar space observation will come the leads to a better understanding, not only of the Sun itself, but also its more intimate effect on the Earth. Thus it appears that there is an interdependence between the Sun and the Earth and that the Earth, Moon and Sun must be considered together.

SALYUT 5

Some of the specialised experiments carried out by the cosmonauts were directed to surveying the terrestrial atmosphere in infra-red rays.

Previous work done with *Salyut 4* led to the conclusion that the basic source of infra-red emission from the upper layers of the atmosphere, was nitrogen oxide. A greatly improved infra-red telescope on *Salyut 5* has enabled this work to be extended.

This telescope has a system of mirrors which enables the focusing of the emission in a way that can be recorded on tape. The operation of this technique involved keeping the spacecraft and telescope directed to the disk of the setting Sun.

Another experiment is with the growth of crystals in the absence of gravity. One of the crystals produced in the crystalliser was put into a sealed container and brought back to Earth. The cosmonauts also repeated earlier experiments in soldering in weightless conditions. A cycle of studies was made to determine the changes in taste sensations under spaceflight conditions. During the period of working on the guidance of *Salyut 5*, some 17 hours continuous navigating was undertaken using an optical sight and manual control. Although the period spent aboard *Salyut 5* was shortened there is every reason to believe that the whole mission was a complete success.

SATELLITE DISCOVERY

An unusual side issue from satellite remote sensing activities comes from sensing experiments by the Indian Space Research group for the development of indigenous capabilities. Success in the location of minerals has already shown promise. A bonus came from the agricultural and forestry areas. It was shown that many areas where forests are supposed to exist have no trees at all. In the reports to the authorities false information had been recorded. So a literal eye from the sky brings truth.

RETURN OF POST MAIL ORDER SERVICE

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. A mono kit or a stereo kit. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors with printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms, 7W into 15 ohms. Response 20c/s to 30kc/s, input 100M.V. high imp. Size 9 1/2 in x 3 in x 2 in.

Mono kit **£11.25** Stereo kit **£18** post 45p
Easy to build. Full instructions supplied.



ELAC 10 inch

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 10W. 9 x 5 in. model **£3.25**. **£4.95**

MAINS TRANSFORMERS

ALL POST 50p each.
250-0-250V 80mA, 6-3, 2A **£2-85**
250-0-250 80mA, 6-3V 3-5A, 6-3V 1A or 5V 2A **£4-60**
350-0-350 80mA, 6-3V 3-5A, 6-3V 1A or 5V 2A **£5-80**
300-0-300 120mA, 6-3V 4A C.T., 6-3V 2A **£7-00**
MIDGET 220V 45mA, 6-3V 2A, 2 1/2 x 2 1/2 in **£1-75p**
HEATER TRANS. 6-3V 3A, **£1-45** 1 amp. 95p
GENERAL PURPOSE LOW VOLTAGE.
Tapped outputs at 2A 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V **£4-60**
1A 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£4-60**
2A 6, 8, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£7-00**
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8-70**
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11-25**
5A, 6, 8, 10, 18V 1A **£2**. 6-0-6V 500mA **£1**. 9V 1A **£1**
12V 300mA **£1**. 12V 500mA **£1**. 12V 750mA **£1**
40V 2A tapped 10V or 30V **£2-50**. 20V 3A **£2**
40V 3A **£2-50**. 30V 5A + 34V 2A ct. **£3-75**
20-0-20V 1A **£3**. 30V 1A **£1-75**. 20V 1A **£1-80**
60V, 40V, 20V or 20-0-20V, 1A **£3-50**
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W **£5**; 250W **£6**; 400W **£7**; 500W **£8**.
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V 1A **£2-75**; 4A **£4-60**.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs 1A 40p; 2A 55p; 4A 85p.

R.C.S. STABILISED POWER PACK KIT

All parts including printed circuit and instructions to build this unit. Voltages available: 6V, 7.5V, 9V, 12V. Up to 100mA output. **£2-95** post 45p.
Please state voltage required.

R.C.S. STEREO FM TUNER



This completely cased mains powered Hi-Fi Tuner with brushed aluminium face is British made using the latest circuitry. Bargain. **£27-50** post 45p
Stereo Tuner/Amplifier Chassis. Brand new **£38-50**.

BARGAIN 3W AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£3-95**

WAFER HEATING ELEMENTS

Size 10 1/2 x 8 1/2 x 1/8 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.

ONLY **40p** EACH (FOUR FOR **£1-50**)
ALL POST PAID—Discounts for quantity.

E.M.I. 13 1/2 x 8 in SPEAKER SALE!


With tweeter. And crossover. 10W. **£5-25**
State 8 or 8 ohm. As illustrated. Post 45p

15W model **£7-95** Post 50p

8 or 15 ohms.

20W model **£8-95** Post 50p

8 or 15 ohms.

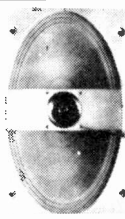

BAKER MAJOR 12 £10-35



Post 50p
30-14,500 c/s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£13**
As illustrated.

Please state 3 or 8 or 15 ohms. Post 80p

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response 30-13,000 c/s. Bass Resonance 55 c/s.

GROUP "25" **£8-95**
12in 30W
3, 8 or 15 ohms. Post 50p

GROUP "35" **£10-50**
12in 40W
3, 8 or 15 ohms. Post 50p

GROUP 50/12in **£14-50**
60W 8 or 15 ohms with aluminum presence dome. Post 90p

GROUP "50" **£19-50**
16in 75W
8 or 15 ohms. Post 90p

Disco, Group + PA Cabinets in stock. Send for Leaflet. Cabinet Fittings, Handles, Corners, Feet, Covering Material all in stock.



BAKER 150 WATT

ALL PURPOSE TRANSISTOR MIXER AMPLIFIER

Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music. 4 way mixing. Output 4/8/15 ohm. a.c. Mains. Separate treble and bass controls. **£68** Carr. 21-60
50 watt model **£49**.

NEW 'DISCO 100 WATT' £52

ALL TRANSISTOR AMPLIFIER CHASSIS 2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. **£52** Carr. 21-60
BLACK CARRYING CABINET AVAILABLE **£9**.

PW SOUND TO LIGHT DISPLAY Complete kit of parts with R.C.S. printed circuit. Three 1,000W channels. As featured in December Practical Wireless. **£12-50** CABINET extra **£3**.

GOODMANS CONE TWEETER

18,000 c/s. 25W 8 ohm. Price **£3-25**
8in Woofer **£6-75**.

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS



Professional model. Four inputs. Treble, Bass, Master Volume Controls. Ideal disco, P.A. or groups. S.A.E. for details. 5 speaker outputs. 3 or 8 or 15 ohm. 100V line to order. Suitable carrying case **£16-50**. plus **£2-50** carr.

E.M.I. GRAM MOTOR 120V or 240V a.c. 2,400 r.p.m. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. **£1-25** Post 30p

E.M.I. TAPE MOTOR 4 pole, 240V 185 mA 1,400 r.p.m. Spindle 1/8 in dia. 75V version **£1** (illustrated). Size 3 1/2 x 2 1/2 in. **£2-00** Post 30p

COLLARO GRAM MOTOR 120V GEAR BOX 25:1 95p. **75p**




NEW BSR HI-FI AUTOCHANGER

Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.c. 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 2 1/2 in. Below motor board 2 1/2 in. With STEREO/MONO CARTRIDGE. **£10-95**
Single Player version **£15-50**. All Post 75p
GARRARD AUTOCHANGER Model 6300 **£14-95**.

PORTABLE PLAYER CABINET £4-50

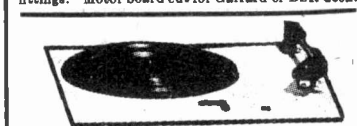Modern design. Size 16in x 15in x 7in rexine covered. Large front grille. Hinged lid. Chrome fittings. Motor board cut for Garrard or BSR deck. Post 50p.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/compat. cartridge. Baseplate. Size 11in x 9 1/2 in. Turntable. Size 7in diameter. A.c. mains. **£20/250V**. 3 speeds plays all size records. **£6-25** Post 45p
Two for **£12**. Post 75p.

HEAVY METAL PLINTHS

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A". Size 12 1/2 x 14 1/2 x 7 1/2 in. **£5-95** Post 75p.
Model "B". Size 16 x 18 1/2 x 7 in. **£6-95**.

TINTED PLASTIC COVERS ONLY

Sizes: 'A'—14 1/2 in x 12 1/2 in x 4 1/2 in, **£2-50**. 'B'—20 1/2 in x 12 1/2 in x 4 1/2 in, **£3**. 'C'—17 1/2 in x 13 1/2 in x 3 1/2 in, **£3-25**. 'D'—16 1/2 in x 14 in x 4 in, **£3-50**.
Ideal for record decks, tape decks, etc. Post 75p.

BAKER HI-FI SPEAKERS HIGH QUALITY—BRITISH MADE SUPERB

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25 c/s Flux Density 16,500 gauss Useful response 20-17,000 c/s 8 or 15 ohms models. **£16-30** Post 80p.

AUDITORIUM 12in 35 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Disco-theques. Bass Resonance 35 c/s Flux Density 16,500 gauss Useful response 20-18,000 c/s 8 or 15 ohms models. **£15-50** Post 80p.
15in model 45 watts **£17-50**. Post 90p.

BLANK ALUMINIUM CHASSIS 18 s.w.g. 2 1/2 in sides

6in x 4in, 70p; 8in x 6in, 90p; 10in x 7in, **£1-15**; 14in x 9in, **£1-60**; 16in x 6in, **£1-45**; 12in x 3in, **87p**; 16in x 10in, **£1-70**.


ALUMINIUM PANELS, 18 s.w.g. 6in x 4in, 15p; 8in x 6in, 25p; 10in x 7in, 30p; 12in x 5in, 30p; 12in x 8in, 40p; 16in x 6in, 45p; 14in x 9in, 50p; 12in x 12in, 55p; 16in x 10in, 75p.

ALUMINIUM ANGLE BRACKET, 6in x 3 1/2 in x 1 1/2 in, 20p.
ALUMINIUM BOXES MANY SIZES IN STOCK.




RADIO COMPONENT SPECIALISTS

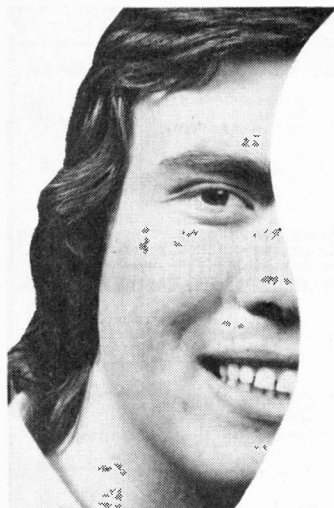337 WHITEHORSE ROAD, CROYDON
Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)
Minimum post 30p. Access and Barclaycard Welcome. Radio Books and Components Lists 10p. Rail Selhurst. Tel. 01-684 1665



Are you only **HALF** a Constructor?

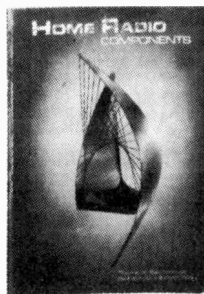

For a year or two I was only half a constructor—struggling along trying to find the right components by tramping from shop to shop. Then I discovered Home Radio and their marvellous Components Catalogue! It's made life so much simpler for me—I can soon locate just what I need and then order by phone. I really feel that now I can claim to be a *complete* constructor.

The Home Radio Components Catalogue consists of 200 pages containing some 5,000 items, nearly 2,000 of them illustrated. Everything is set out so clearly the catalogue is a pleasure to use. When you buy one you also receive *free* a mini catalogue filled with super bargains. The saving on some of your purchases from this bargain list alone can more than pay for your catalogue. The catalogue costs £1 plus 40p for postage and packing. Why hesitate? Send off your cheque or P.O. for £1.40 now, and discover the satisfaction of being a *complete* constructor!

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD. Dept. PE
234-240 London Road, Mitcham, Surrey CR4 3HD Regd No. 912966 London



POST THIS COUPON
with cheque or p.o. for
£1.40

HOME RADIO (Components) LTD. Dept. PE 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

PRECISION PETITE LTD.

119a High Street, Teddington, Middlesex TW11 8HG


Tel. 01-977 0878 (24 hr. Telephone enquiry service)

S.A.E. please for leaflet and order form

- Super 30 Kit (30 Tools) (incl. drill without stand)
£17.62 plus P. & P. 85p
- Super 10 Kit (10 Tools) (incl. drill without stand)
£13.74 plus P. & P. 65p
- Mk. II Drill Stand
£4.40 plus P. & P. 35p
- Mk. II Drill only
£8.79 plus P. & P. 35p
- Flexible Drive Shaft
£5.46 plus P. & P. 25p
- Transformer 240V a.c./12V d.c.
£6 plus P. & P. 70p

Replacement drills, stones, burrs, etc. 40p each. Circular saw blades 50p each. £2 per set of 4 sizes. P. & P. any quantity 20p.

All VAT inclusive

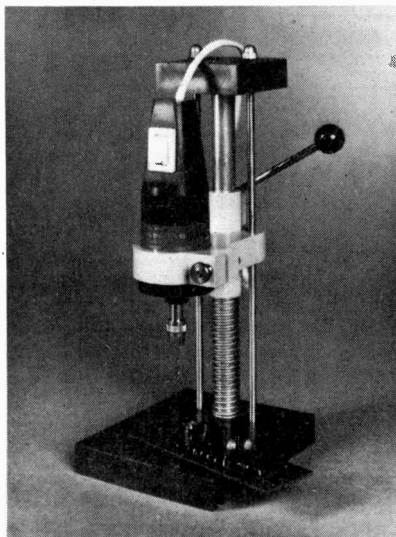

Still some of the following Low Cost Items available:

MARCONI OSCILLATOR TF885A/1 in superb condition covering 25Hz to 12MHz sine wave in 3 ranges and 50 Hz to 150KHz square wave. High output 31.6V. Meter scaled in volts and dB.

AVO VALVE TESTER CT160—"The Suitcase". Size approx 15in. wide x 10in. high x 11in. deep.

FURZEHILL VALVE VOLTMETER V200A Audio to 10MHz with probe 1mV FSD. As new condition.

MARCONI TF1026/11 Absorption Frequency meter 100MHz to 160MHz. Very fine condition.

ALL ITEMS £22.50 each or ANY THREE ITEMS FOR £60. Carriage £2.50 each or £5 for 3.

COME AND LOOK ON OUR SHELVES—HUNDREDS OF OTHER ITEMS TO INTEREST YOU. TOO FAR AWAY—THEN SEND FOR LISTS.

Low cost peripherals

5 Level Printers, Punches, Readers all with ASCII interface.

8 Level items also available at higher cost.

Various KEYBOARDS available.

CHILTMead LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel. Reading 582805



SEMICONDUCTOR UPDATE

By R.W. COLES

SC/MP
MC904

SCAMP

"Scamp" is the way you say SC/MP, and SC/MP stands for Simple, Cost-effective, Micro-Processor, and really, I couldn't have put it better myself, because this really is the most simple and cost effective microprocessor to come along, and probably the first which will break into the amateur market in a significant way.

As we have all heard by now, microprocessors are "binary computers on a chip" which can be used to replace almost any array of hard-wired logic gates and flip-flops if an appropriate programme is written and stored in a ROM (Read Only Memory). These devices really are powerful, and can be used to build sophisticated control systems and a host of others. "Micro-madness" is currently gripping the professional electronic industry and microprocessors from various manufacturers are being used for just about every job which used to be done with a board full of TTL or CMOS logic.

You may be wondering why, if they are so wonderful, we haven't seen more of them in the amateur magazines, and the answer is that they have been, up to now, rather complicated things to use, requiring substantial peripheral components during the programme development phase of a project. The new National SC/MP is an attempt to minimise this initial complexity, and to make using a microprocessor a possibility for everyone, even amateurs.

The SC/MP instruction set is easy to learn and consists of only 46 instructions which are, nevertheless, very powerful and able to cope with a variety of memory and input/output situations. A separate clock generator circuit is not necessary, all you need is a single capacitor or perhaps a crystal, and you are in business. SC/MP also uses the tried and trusted P.M.O.S. technology and has a versatile 8-bit word length, both features which make for easy application.

To bring home the simplicity of the new chip, National sell an "Intro-kit" which consists of an SC/MP

chip, a PROM containing a programme called Kitbug, a few peripheral chips and a small printed circuit board, which can be quickly hooked up and then used to develop programmes with the aid of just a power supply and a teletype.

The teletype is, of course, a king-sized snag if you don't happen to have one kicking around in the workshop, but don't despair! National have also produced a companion to Introkit called "Telekit" which uses a cheap calculator keyboard and display as a teletype replacement!

The SC/MP and the kits are available from National distributors.

ALL BRITISH

Not long ago the analogue of logic circuitry to make a $3\frac{1}{2}$ digit, digital voltmeter, would have occupied a couple of shoe boxes and would have cost the earth. Thanks to MOS l.s.i. technology and the ingenuity of the all British semiconductor firm, Integrated Photomatrix Ltd., you can now buy the whole shooting match in a 28-pin DIP package for just a few pounds.

The I.P.L. MC904 is a complete $3\frac{1}{2}$ digit, dual ramp, autopolarity,

analogue to digital converter with basic voltage ranges of $\pm 200\text{mV}$ or $\pm 2\text{V}$, depending on the value of a single external resistor. The chip contains the integration and comparison amplifiers as well as all the control and counting logic, and even has "range up" and "range down" outputs so that an autoranging meter can be designed with the minimum of external components.

A wide variety of display devices can be interfaced with the MC904, including the simple and inexpensive 7-segment l.e.d. types, a combination which will be cheap enough and small enough to compete directly with moving coil meters of the traditional variety. Possible applications are varied and include comprehensive digital multimeters using the new chip as the measuring system, and requiring only the addition of suitable range switching circuits to convert a.c. and d.c. amps and volts, or resistance, into an equivalent d.c. voltage to drive the MC904 and display.

Power requirements are modest at plus and minus 14V and this new chip is likely to find its way into many amateur projects in the near future.

The MC904 is available from: Integrated Photomatrix Ltd., The Grove Trading Estate, Dorchester, Dorset.


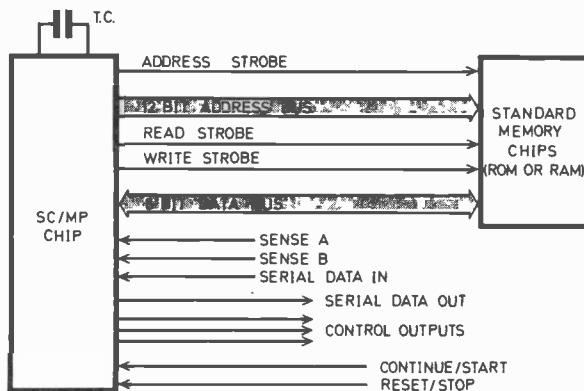


Fig. 1. A basic SC/MP system using the minimum of components and suitable for TV games and simple automatic control systems

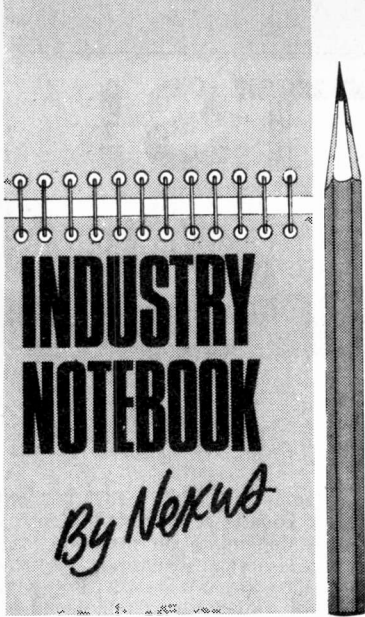

INDUSTRY NOTEBOOK

By Nexus

INCENTIVE

When Sir Jules Thorn retired at the end of August he could look back on a lifetime of achievement. He may have been small in stature but he was big in vision—literally so considering his companies' interests in TV.

He was such a well known figure in British electrical and electronics business circles and he has been around so long that it is hard to imagine him as a diminutive immigrant arriving from Vienna during the depths of the depression in the mid-20s. The company he founded went public in 1936 with a profit of £42,000. His last address to shareholders announced a profit of £74 million from sales at home and overseas of £957 million.

He started in business in the UK by importing electric light bulbs, trading them cheaply against a "ring" of suppliers then controlling prices and markets. He subsequently started manufacturing and broadened his interests to include radio and, later, TV and a whole range of household appliances. Today, Thorn companies hold 40 per cent of the lamp market, about the same in TV manufacturing, and in TV rentals Thorn is dominant.

Sir Jules always kept a tight rein on his companies through his own personal shareholdings and those of his family. His shareholding at the time of his retirement was valued at £1.5 million and as a first-named trustee in family and charitable trusts holding almost £15 million of shares he had and retains a huge personal stake in the success of Thorn Electrical Industries.

Sir Arnold Weinstock's personal shareholding in GEC is currently

worth about £4 million. I am inclined to agree with one analyst who recently observed that he would far sooner invest in companies with bosses heavily involved financially, such as Thorn and GEC, than in those where the bosses' interest is confined to basic salary and fringe benefits. It is a fact of life that people tend to be more prudent when risking their own money than other people's. Not to mention the in-built incentive to succeed.

And with a new wave of public interest in early retirement it is interesting to note that Sir Jules Thorn celebrated his 77th birthday this year and was, I suspect, still thoroughly enjoying his work to the end. We wish him well in his new and less demanding role as Thorn's president.

THREAT

People like Sir Jules Thorn and Sir Arnold Weinstock are by nature self-reliant and this is reflected in the companies they lead which are nothing if not thrusting, vigorous and as keen on penetrating overseas markets as anyone. In fact, it is nothing less than their duty to do so on behalf of their employees, shareholders and Great Britain Ltd.

However, we still find Thorn and GEC, together with Philips, petitioning the Departments of Trade and Industry, not with the begging bowl, thank heaven, but its near relation which is a plea to curb imports of electronic consumer products from Japanese manufacturers in Japan, or from low-cost labour areas in the Far East where many Japanese-controlled factories are situated.

The managing director of Mullard, the U.K. component manufacturing arm of Philips, Jack Akerman, has already sounded off on the threat to British component manufacturers before the new initiative of the big three in consumer electronics which, it should be noted, was on behalf of the whole industry.

The case for import restriction is based firmly on allegations of unfair competition. That the pricing of Japanese products in the U.K. market place is neither reflecting inflation in manufacturing costs nor the devaluation of the pound sterling against the Japanese yen. In fact that Japanese prices remain stable whereas they ought to have advanced considerably. It is implied that prices are being deliberately manipulated to damage the British industry.

Following Jack Akerman's earlier statement, a thoughtful leading article "Tapping the Glass" was published in the September issue of PE so I won't cover the same

ground again except to observe that I am in agreement with our Editor when he writes that "the average person will not take kindly to any restriction on his access to cheaper goods".

I would only add that the British company BSR dominates the Japanese market for record players because BSR is clever at making them and the Japanese aren't. That GEC colour TV is selling rather well in Europe. Good sets in their own right but built with relatively cheap British labour compared with labour costs in Germany or France. That Philips, while complaining of low-cost imports from Taiwan, has a semiconductor assembly plant there because it is cheap and convenient. That GEC employs black and coloured labour in South Africa and pays well above the official Household Subsistence Level, but this is still substantially lower than that enjoyed by Europeans.

The name of the game is competition as Sir Jules Thorn demonstrated when he started out in business with cut-price imported lamps and the buying public responded. Was this unfair? The established suppliers certainly thought so. Whether the present Japanese onslaught on the U.K. consumer market is unfair trading in the sense of landing goods at less than production cost may or may not be true—without hard evidence we can only guess. Perhaps it's just that the Japanese are cleverer at making and marketing electronic consumer products than the British, just as they are so clearly better at building and marketing motorcycles.

The big multinational corporations decide what they are going to make, and where to make it, for a complex variety of reasons of which labour cost is only one. Sony is already manufacturing in the U.K., National Panasonic is to start soon and Hitachi is said to be thinking about it. On level terms with established British manufacturers how will they fare? If they can make better sets more cheaply for the U.K. and European market, then we shall all be rejoicing on the further buoyancy of British electronics and British-built exports, just as we do now for other great British-based exporters like Hewlett-Packard (US owned), ITT (US owned), and not forgetting Philips (Dutch owned).

It is easy to forget the fact that we in electronics are all in a world-trading environment and that it is natural for various products to be manufactured in different locations for world markets. All the big companies play the multinational game and none more keenly than the British.

15-240 WATTS!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.


FEATURES: complete pre-amplifier in single pack; multi-function equalisation; low noise; low distortion; high overload; two simply combined for stereo.

APPLICATIONS: hi-fi; mixers, disco; guitar and organ; public address.

SPECIFICATION: input—magnetic pick-up 3mV; ceramic pick-up 30mV; tuner 100mV; microphone 10mV; auxiliary 3-100mV; input impedance 47k Ω at 1kHz; Outputs—tape 100mV; main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz; bass \pm 12dB at 100Hz. Distortion—0.1% at 1kHz; signal/noise ratio 68dB. Overload—36dB on magnetic pick-up. Supply Voltage— \pm 16-50V.

Price \pounds 4.75 + 59p VAT. P. & P. free

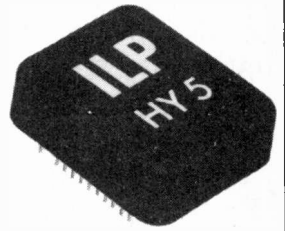HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit; low distortion; short, open and thermal protection; easy to build.

APPLICATIONS: updating audio equipment; guitar practice amplifier; test amplifier; audio oscillator.

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω . Distortion—0.1% at 15W. Input Sensitivity—500mV. Frequency Response—10Hz-16kHz -3dB.

Price \pounds 4.75 + 59p VAT. P. & P. free

AVAILABLE
JUNE 1976

HY50 25W into 8 Ω


The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion; integral heatsink; only five connections; 7 amp output transistors; no external components.

APPLICATIONS: medium power hi-fi systems; low power disco; guitar amplifier.

SPECIFICATION: Input Sensitivity—500mV. Output Power—25W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 25W at 1kHz. Signal/Noise Ratio—75dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 25V. Size—105 x 50 x 25mm.

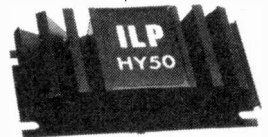Price \pounds 6.20 + 77p VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion; integral heatsink; load line protection; thermal protection; five connections; no external components.

APPLICATIONS: hi-fi; high quality disco; public address; monitor amplifier; guitar and organ.

SPECIFICATION: Input Sensitivity—500mV. Output Power—60W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.04% at 60W at 1kHz. Signal/Noise Ratio—90dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 35V. Size—114 x 50 x 85mm.

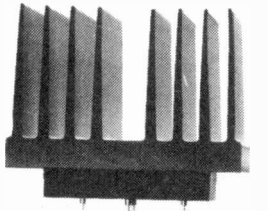Price \pounds 14.40 + \pounds 1.16 VAT. P. & P. free



HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown; very low distortion; load line protection; integral heatsink; no external components.

APPLICATIONS: hi-fi; disco; monitor; power slave; industrial; public address.

SPECIFICATION: Input Sensitivity—500mV. Output Power—120W R.M.S. into 8 Ω . Load Impedance—4-16 Ω . Distortion—0.05% at 100W at 1kHz. Signal/Noise Ratio—96dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Size—114 x 100 x 85mm.

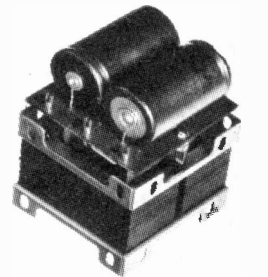Price \pounds 21.20 + \pounds 1.70 VAT. P. & P. free



HY400 240W into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown; very low distortion; load line protection; no external components.

APPLICATIONS: public address; disco; power slave; industrial.

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω . Load Impedance—4-16 Ω . Distortion—0.1% at 240W at 1kHz. Signal/Noise Ratio—94dB. Frequency Response—10Hz-45kHz -3dB. Supply Voltage— \pm 45V. Input Sensitivity—500mV. Size—114 x 100 x 85mm.

Price \pounds 29.25 + \pounds 2.34 VAT. P. & P. free

POWER SUPPLIES: PSU36—suitable for two HY30s \pounds 4.75 + 59p VAT. P. & P. free. PSU50—suitable for two HY50s \pounds 6.20 + 77p VAT. P. & P. free. PSU70—suitable for two HY120s \pounds 12.50 + \pounds 1.00 VAT. P. & P. free. PSU90—suitable for one HY200 \pounds 11.50 + 92p VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400 \pounds 21 + \pounds 1.68 VAT. P. & P. free.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

.....

Signature

Registered office No. 1032630

TAMBA ELECTRONICS

QUALITY PRODUCTS
FOR HI-FI, DISCO,
P.A. GROUP AND CLUB USE

A BRAND NEW RANGE OF AMPLIFIER MODULES 5 to 100 WATT/RMS

Choose the power *you* need from these five pure complementary amplifiers
Two-year guarantee

All amplifiers feature a pure complementary symmetry output stage for low distortion and high reliability—the highest grade components (by Mullard—Texas; Plessey—RCA etc.) used throughout



TAM50 5W RMS 25V supply	£3.20
TAM100 10W RMS 35V supply	£3.75
TAM250 25W RMS 45V supply	£4.25
TAM500 50W RMS 45V supply	£6.95
TAM1000 100W RMS 65V supply	£9.80
(all modules carriage free)	

- Suits loads 4–16 ohms (optimum load 8 ohms, TAM50/100/250, 4 ohms TAM500/1000)
- Low distortion (0.1%)
- 20–20,000 Hz \pm 1dB
- Silicon circuitry throughout
- Inherently open circuit proof
- Four simple connections

- High sensitivity—100mV
- Low profile (1in high 3½in \times 3in)
- 75% efficient
- Glass fibre printed circuit board
- Accepts most mixers/pre-amplifiers

POWER SUPPLIES

For 1 or 2 TAM50/100	£4.25 (carr 50p)
For 1 or 2 TAM250/500	£6.95 (carr 50p)
For 1 or 2 TAM1000	£9.80 (carr 50p)

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc) C.O.D. (50p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50–100W units and at 12½% for 5–25W units

Hours, 9.30a.m.–5p.m.
Mon.–Sat. Callers
welcome.
Tel: (01) 684 0098

TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

An exciting **NEW** series from ...



Newnes Technical Books

Each of the books in this series is written by an expert in his own particular field. The books are authoritative yet easily understood by those with no technical knowledge whatsoever, and the texts are supplemented by many highly informative illustrations.

MASTER ELECTRONICS IN MUSIC

T. D. Towers

Contents: Creating Musical Sounds by Electricity — Making Musical Instruments Louder — Musical Special Effects by Electronics — Electronic Keyboard Instruments — Electric Guitars — Magnetic Tape Music — The Robot Drummer — Music Synthesisers — Music by Computer — Index.

130 pages 0 408 00262 X £2.50

MASTER HI-FI INSTALLATION

Gordon J. King

Contents: How it Works — The Amplifier — Programme Signal Sources — Importance of a Good F.M. Signal — The Loudspeaker — Mono, Stereo and Quadrophonic Sound — Four-channel Techniques — Room Effects — Best Use of Controls — Terminology — Index.

150 pages 0 408 00237 9 £2.50

MASTER STEREO CASSETTE RECORDING


I. R. Sinclair

Contents: Stereo Systems — Signal Sources — Controls and Facilities — Making the Recording — Replaying and Monitoring — Essential Maintenance — Aids to Better Recording — Noise Reduction Systems — Cassette Recorder and Hi-Fi.

140 pages 0 408 00238 7 £2.50



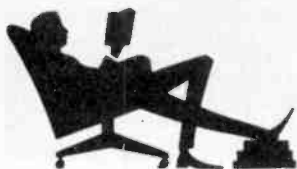NEWNES TECHNICAL BOOKS, Newnes-Butterworths, Borough Green, Sevenoaks, Kent



BOOK REVIEWS

ELECTRONICS FOR WORKS ELECTRICIANS

By Noel M. Morris
Published by McGraw Hill
268 pages, 230×150mm. Price £6.00

THIS is one of those all too rare books pitched at a level between the elementary introduction and the advanced mathematical treatment. Although, as its title implies, it is intended to help electricians in industry to cope with the growth of electronic controls, etc., it is written in such a way as to form a useful introduction to electronics in general.

More than half the book is devoted to basic theory and a description of components and their properties, including semiconductors and opto-electronic devices. The remainder deals with amplifiers and basic logic circuits, feedback amplifiers and oscillators, operational amplifiers, stabilised power supplies and power electronics, and finally test equipment.

G.C.A.

QUESTIONS AND ANSWERS ON RADIO AND TELEVISION (4th Edition)

By H. W. Hellyer and I. R. Sinclair
Published by Newnes Technical Books
120 pages, 165×110mm. Price £1.25

A USEFUL little book for the enquiring beginner in radio or television. The treatment is essentially basic and non-mathematical.

G.C.A.

TWO TRANSISTOR ELECTRONIC PROJECTS

By F. G. Rayer
Published by Babani Press
90 pages, 180×108mm. Price 85p

A SELECTION of simple circuits using two transistors, ranging from the astable multivibrator in various applications, through audio amplifiers, games and controls of various types to radio receivers.

G.C.A.

POINTS ARISING

CROSS-HATCH GENERATOR (September 1976)

In Fig. 3b, page 712, the pad for pin 1 of IC2 appears to be joined to the adjacent pad connected to R5, D5, etc. This is, of course, incorrect. Constructors should ensure that the two pads are isolated from each other on their p.c.b.

DIGITAL FREQUENCY METER (May/June 1976)

In Fig. 6, page 379, the leads from S1a to pins 17 and 19 on the main board should be transposed. The wiring shown in Fig. 12, page 503, is correct.

NEXT MONTH

Have fun with our
Gamesmachine

ROULETTE POOLS
RANDOM NUMBER

DICE

This design uses TTL circuitry to produce Random Numbers up to 99, Dice scores up to 6 + 6, Roulette wheel numbers up to 60 or Pools numbers up to 59.

46

METAL LOCATOR

Designed with the "D.J.Y.-Man" in mind, this simple unit will warn of the presence of pipes or wiring buried in a house wall. A boon to anyone engaged in home improvements, or even just hanging a picture.

Plus

Part 2 ORION TUNER

Also in this issue...

INDEX for 1976

PRACTICAL
ELECTRONICS

DECEMBER ISSUE ON SALE NOVEMBER 12

DISCO STROBE DISCOSTROBE

By A. BRIAR

FOUR CHANNELS — THREE MODES

THIS article describes the circuit and construction of a discotheque lighting and strobe unit. The system is completely self-contained and all controls are simple to understand and operate.

Designed using TTL integrated circuits, the unit may be constructed for about one fifth the cost of a comparable commercial unit.

In addition to the main strobe unit, details are given for construction of the lamp display units compatible with the system.

DESIGN FEATURES

There are four channel outputs, each channel being connected to two 100W lamps. The layout of the lamps is in two portable banks of four.

Each channel has an override switch to permanently enable or inhibit selected channels.

A variable speed control for the strobe effect is incorporated.

The design allows synchronised strobing (to the beat of the music) to be added, and the number of lamps per channel to be increased.

Three modes of operation of the unit are provided:

1. **Sequential**—each channel strobos in turn, only one channel at a time being enabled.
2. **Random**—the channels flash in a purely random sequence.
3. **Full Strobe**—all channels flash simultaneously.

Provision is made for the operator (disc jockey) to monitor the selected mode of operation by means of small i.e.d. slave lamps on the top of the unit.

BLOCK DIAGRAM

The full block diagram is shown in Fig. 1.

The main timing source is an oscillator whose frequency is variable between about 2Hz and 20Hz, the control being mounted on top of the unit for the operator to use.

The output of the oscillator feeds a four-bit register where, in conjunction with the MODE switch and appropriate gates, the three modes of operation described above can be selected. The resultant four-channel selected output is routed along the four "highway" lines to an intermediate gating stage. It is to these highway lines that the slave monitor i.e.d.s are connected (the lamps being mounted on top of the unit). Also, at this point, the override facility for each channel is incorporated.



The ultimate switching of the mains on each channel is achieved with triacs. For these devices to operate correctly a triggering source must be provided and this is achieved by using another oscillator which is at a fixed frequency of about 800Hz.

The oscillator is followed by a monostable circuit so that very narrow pulses are formed and these pulses are gated with each highway such that if any highway is at its high state then these trigger pulses are allowed through to operate the appropriate triac drive circuit.

Two power supplies are necessary: a 5V rail for the TTL circuits and a -6V rail for the triac drive circuits.

The complete circuit diagram is shown in Fig. 2.

The main timing source uses a 7413 Schmitt trigger IC1a which is connected as an oscillator, variable in speed between 2Hz and 20Hz.

To use the 7413 as a square wave oscillator, a feedback resistor (R1 and VR1 in series) is connected from the output back to the commoned input pins and a capacitor (C1) connected between input and earth.

The oscillator output is fed to the register as a common clock pulse. The register consists of two 7474 dual D-type latches (IC2 and IC3) to give the required four stages.

For simplicity the three modes of operation will be described individually.

SEQUENTIAL MODE

In the SEQUENTIAL (S) mode, only the first two stages of the register are used. The output of the second stage (B) is fed back to the input of the first stage forming what is known as a Johnson Counter. This has four states which are decoded by the four three-input gates IC4a to c and IC5a. In fact only two of the three inputs to each gate are actually used for decoding, the third input being used as an inhibit.

When SEQUENTIAL mode is selected by setting S1 to "S," an enabling input is put on gates IC4a to c and IC5a by S1c such that the individual outputs are routed to the main channel highways via gates IC8a to IC8d. Also, at this time, gates IC5b and IC6a to c are inhibited by S1c giving an earth to their inputs so the outputs of these four gates are all at a constant logic 1.

RANDOM MODE

For the RANDOM (R) mode, all four stages of the register are used. The configuration is known as a pseudo-random generator and the random sequence is established by feeding the last two stages of the register through an equivalence circuit formed from gates IC7a to IC7c.

The equivalence circuit will feed a logic 1 back to the input if the outputs from the last two stages are the same and a logic 0 if they are different.

No decoding is necessary for this mode so the outputs of the four stages of the register are taken to the appropriate gate from IC5b to IC6c. When RANDOM (OR FULL STROBE) mode is selected S1c provides an enabling input to gates IC5b to IC6c and inhibits gates IC4a to IC5a such that the outputs can be routed via gates IC8a to IC8d to the main channel highways.

FULL STROBE MODE

In the FULL STROBE (F) mode, the output of the oscillator is fed to gates IC5b to IC6c directly via S1a. However, to ensure that there is no interaction from the register, each stage is either reset or set by means of S1d such that the register outputs to gates IC5b to IC6c are all held at a high level.

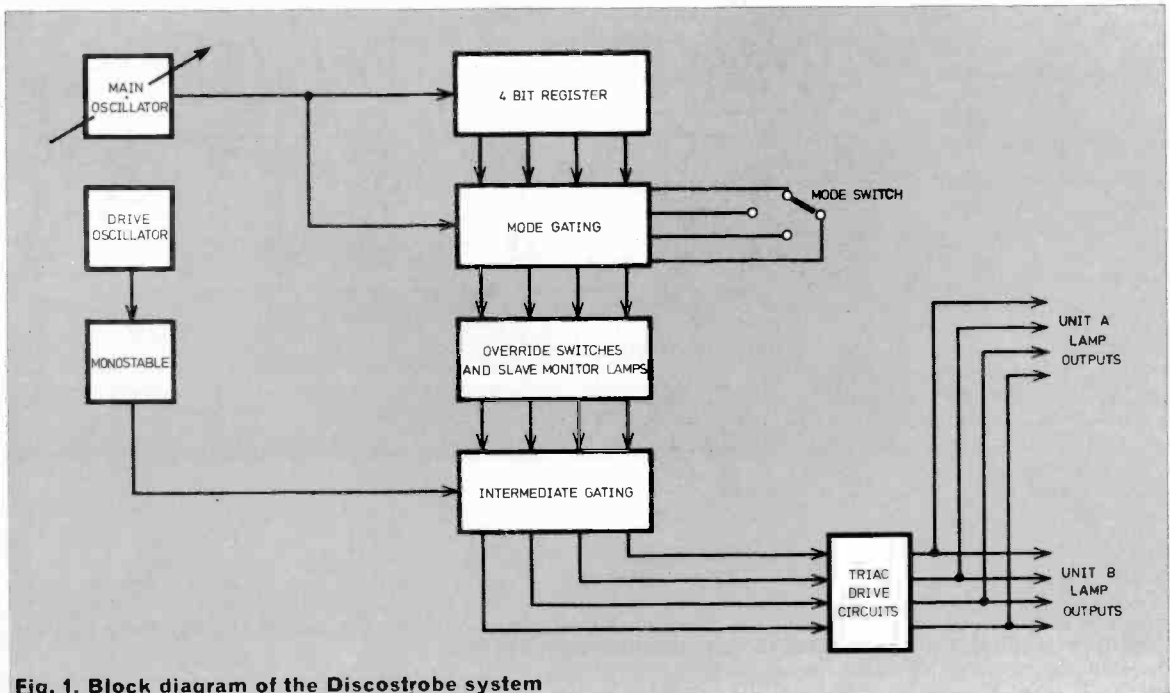


Fig. 1. Block diagram of the Discostrobe system

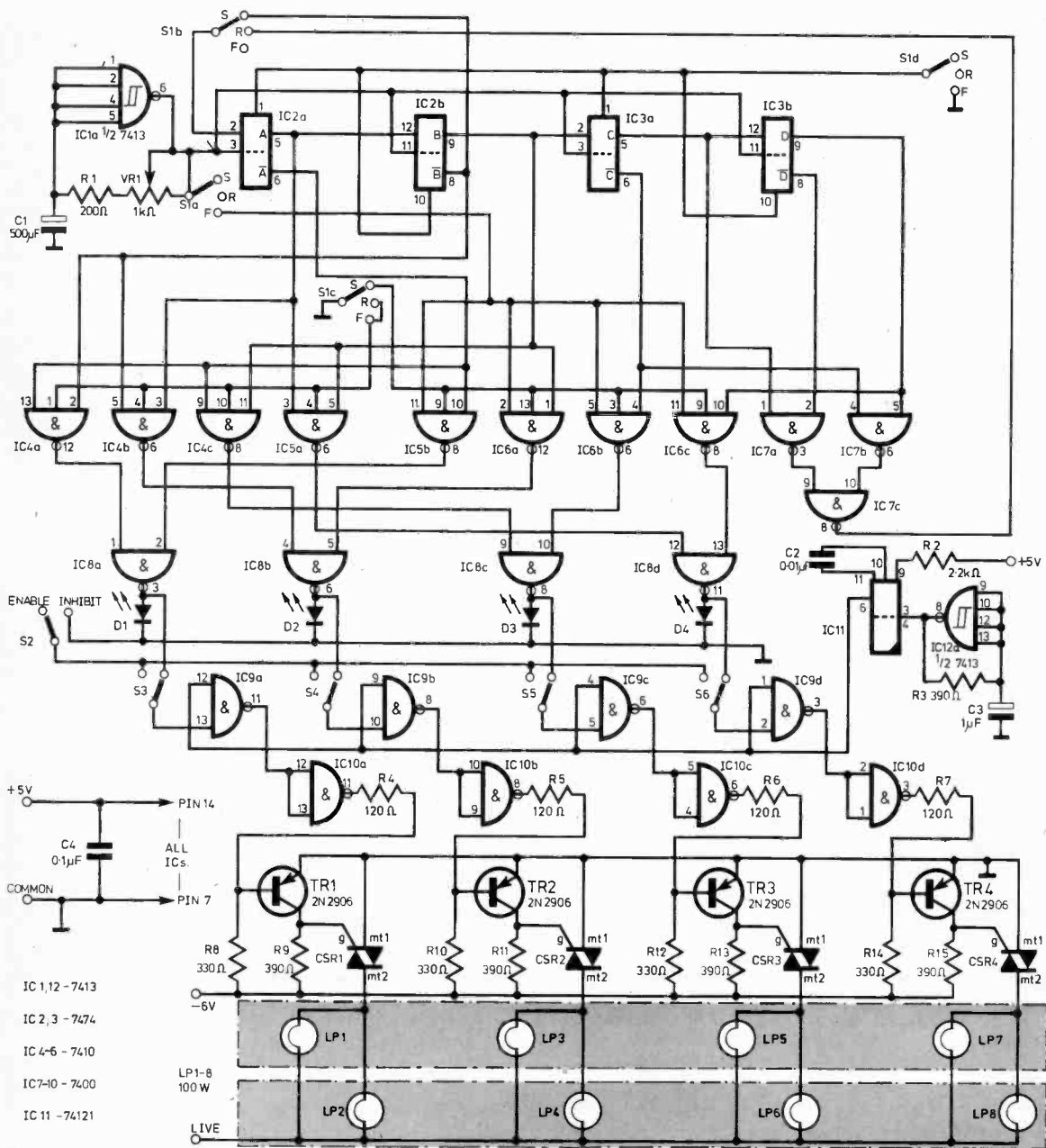


Fig. 2. Complete circuit diagram of the Discostrobe system excluding the power supply. Note that the common terminal is not connected to earth but to the neutral line

VERRIDE

The main channel highways are the outputs of gates IC8a to IC8d and these drive the l.e.d. indicators D1 to D4 located on top of the unit. These give the operator an indication of the sequence in use.

The highways are also routed via the channel override switches S3 to S6. The INHIBIT/ENABLE switch S2 determines the function of the override switches.

With S2 in the INHIBIT position, switching on any of the override switches will permanently inhibit that channel. With S2 in the ENABLE position, the override switches will cause the selected channels to be permanently on.

TRIAC TRIGGERING

The pulses for triggering the triacs are produced by an oscillator with a frequency of 800Hz coupled to a monostable which gives pulses about 20 μ s duration.

The oscillator is formed from half of the dual Schmitt trigger IC12. The monostable, IC11, is a 74121 i.c. which is triggered by the negative-going transitions of the output of IC12a.

The output of the monostable is fed to all four gates IC9a to IC9d. Should any of these gates have an enabling high level from its associated highway (or should the highway be open circuit) then the trigger pulses will pass through to the triac drive circuit via the appropriate inverter gate (IC10a to IC10d) to re-establish them as positive pulses.

Table 1: Resistor Values for Triacs

Type	Current (A)	Voltage	Values of R9, 11, 13, 15 (Ω)
NAS 0164X	1.6	400	470 to 560
NAS 0304X	3.0	400	390 to 470
NAS 0354X	3.5	400	330 to 390
NAS 0654X	6.5	400	220 to 330
NAS 0854X	8.5	400	180 to 220
NAS 1004X	10.0	400	100 to 180

The triac is a bi-directional switch and belongs to the thyristor family of devices, i.e. devices which are four-layer *pnpn* type with a gate connection.

The triac will conduct current in either direction i.e. from mt1 to mt2 or vice versa. It is triggered into conduction by either a positive or negative signal on the gate. Once the triac is triggered it will stay on, regardless of the gate voltage, until the main current drops below a threshold value. Therefore, if used for passing an a.c. voltage, the device will switch off every half cycle as the voltage passes through zero.

Bearing these points in mind, the device must be triggered every half cycle during the period that conduction is to take place: removing the trigger will allow the triac to automatically turn off.

Rather than build a complicated circuit to detect the start of each half cycle of mains voltage for triggering the triac, the Discostrobe uses the method

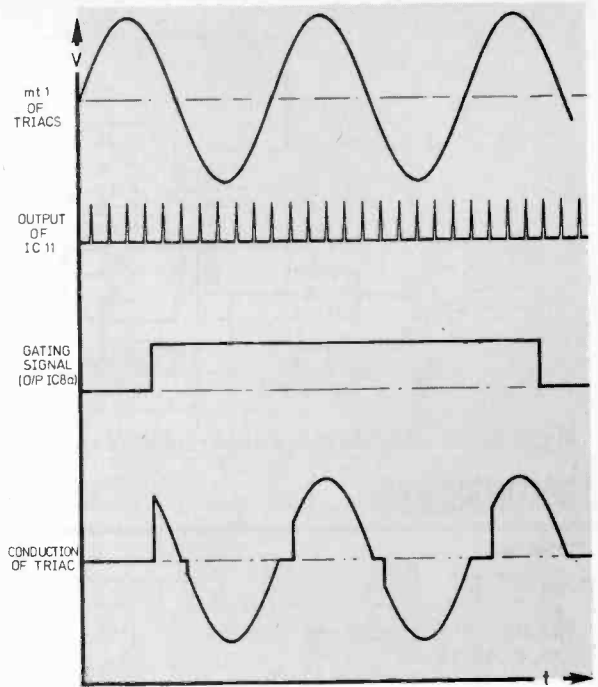


Fig. 3. Waveforms at various parts of the circuit of Fig. 2

of triggering at a much higher frequency than the mains supply such that the triac conducts shortly after the start of each half cycle.

The operation of the triac drive circuit is such that when a positive-going pulse is present at the base of the transistor the transistor cuts off and current is allowed to flow from the -6V rail into the gate of the triac. When the trigger pulse is removed, the transistor conducts providing effectively zero volts at the gate of the triac which causes the device to cut off when the a.c. mains once again passes through zero volts.

The waveforms at various parts of the circuit are shown in Fig. 3. Note that the common point of all the supply lines and the common terminals of the triacs must be returned to the neutral line of the mains supply.

If a higher output power rating is required the triac types and the values of resistors R9, R11, R13 and R15 will have to be changed. A list of the various triacs available along with suggested values of resistors is given in Table 1.

POWER SUPPLIES

Although TTL logic usually requires a highly stable power rail, in this application all that was necessary was the simple smoothed supply as shown in Fig. 4. This circuit is quite adequate provided that the number of TTL circuits is not going to be increased too dramatically.

In constructing the power supply, the common rail of the two supplies should be connected to the **neutral** of the mains supply and **not earth**.

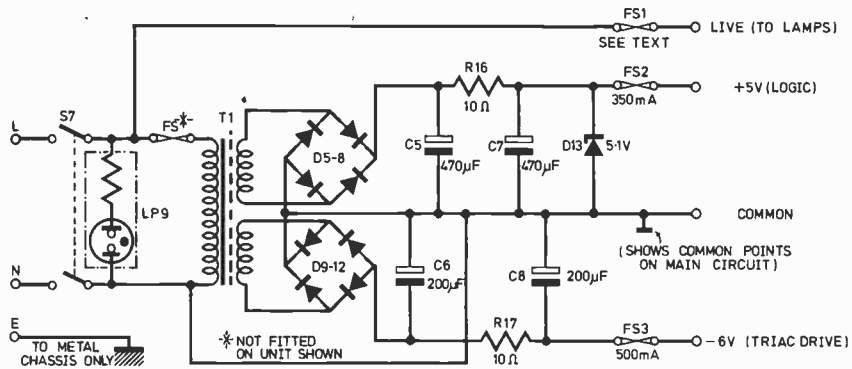


Fig. 4. Circuit diagram of the power supply to give the 5V and -6V lines required by the Discostrobe system

COMPONENTS . . .

Resistors

R1	200Ω
R2	2.2kΩ
R3	390Ω
R4-R7	120Ω (4 off)
R8, 10, 12, 14	330Ω (4 off)
R9, 11, 13, 15	390Ω 1W (4 off)
R16, R17	10Ω 5W (2 off)

All ±10% ½W except where stated

Potentiometer

VR1 1kΩ linear

Capacitors

C1	470μF 12V elect.
C2	0.01μF
C3	1μF 12V
C4	0.1μF
C5, C7	470μF 10V elect (2 off)
C6, C8	200μF 10V elect (2 off)

Transistors and diodes

TR1-4	2N2906 (4 off)
D1-4	TIL209 or similar i.e.d. (4 off)
D5-8	50V 1A bridge rectifier
D9-12	50V 1A bridge rectifier
D13	5.1V 400mW Zener diode

Integrated Circuits

IC1	7413	IC7-10	7400 (4 off)
IC2, 3	7474 (2 off)	IC11	74121
IC4-6	7410 (3 off)	IC12	7413

Triacs

CSR1-4 NAS0354X 400V 3.5A triac (4 off) (Available from The Radio Shop, 16 Cherry Lane, Bristol BS1 3NG) (For more than 2×100W per channel see Table 1)

Miscellaneous

S1	4 pole 3 way rotary switch
S2-6	S.p.d.t. toggle switch (5 off)
S7	D.p.d.t. mains switch
T1	Mains primary, 0-6V, 0-6V ½A secondaries
FS1	5A fuse and holder
FS2	350mA fuse and holder
FS3	500mA fuse and holder
LP1-8	100W, bayonet type mains spot lamps (various colours) (8 off)
LP9	Mains neon indicator
0.1in matrix Veroboard, case to suit, edge connectors (if used)	
5-way mains sockets and plugs (2 off) (if required use Bulgin P551 and P552)	

CONSTRUCTION

The logic is divided between two main boards as shown in Figs. 5 and 6. In the prototype the two boards were 0.1in matrix stripboard which plugged into an edge connector so that the boards were easily removable from the unit. However, this expense is not essential.

Board A (Fig. 5) is mounted in the bottom of the case and carries the main oscillator (IC1), the register (IC2 and 3), and mode selection gates (IC4 to IC8). Two 200μF capacitors in parallel have been used for C1 but these can be replaced by a single 470μF.

Capacitor C4 serves to decouple the supply lines.

Board B is shown in Fig. 6. This board is fed with 6V a.c., the bridge rectifier and smoothing components sharing this board with the logic i.c.s. Also mounted on this board are the triac drivers (TR1 to TR4 and associated components). The triac oscillator IC12, monostable IC11 and gates IC9 and IC10 complete this board.

Because of the complexity of the wiring it is not possible to give point to point wiring diagrams for these two boards. However, layout of the components is in no way critical and by laying out the i.c.s and using the circuit diagram as a wiring guide, no difficulties should occur.

The four triacs are bolted on to the side of the case as shown in Fig. 7. Their leads are inserted into a piece of stripboard which carries wires from the triac drivers (Board B). This small piece of board also carries the smoothing components for the -6V supply.

The lid of the case has been turned back in Fig. 8 to show the components it carries. Also seen in this photo are the two output sockets which carry the signals to the two banks of lights. The type used in the prototype were Plessey types but a suitable alternative is the Bulgin P551 and P552 plug and socket.

Note carefully that the earth input from the mains is used only to earth the metal chassis; the neutral wire is connected to the common terminal of the power supply.

The layout of the controls on the top panel is shown in the photographs.

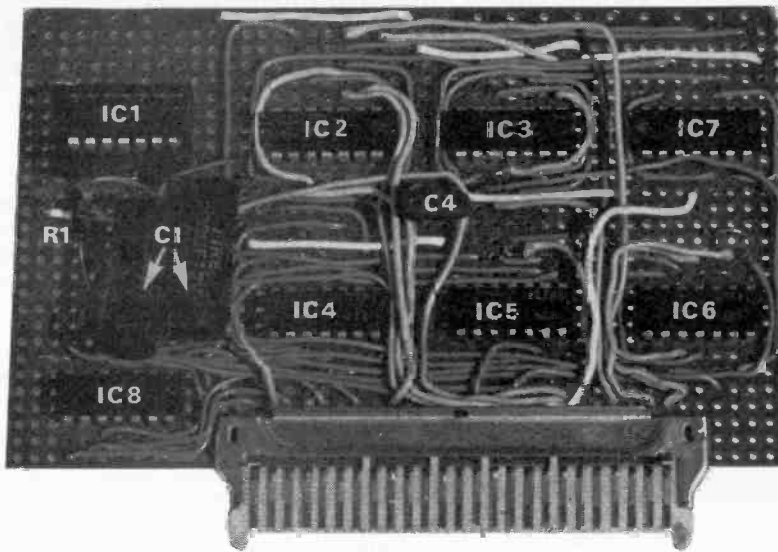


Fig. 5. Board A carries the main oscillator, register and mode selection gates. Though two capacitors in parallel have been used for C1, a single 470 μ F type should be used

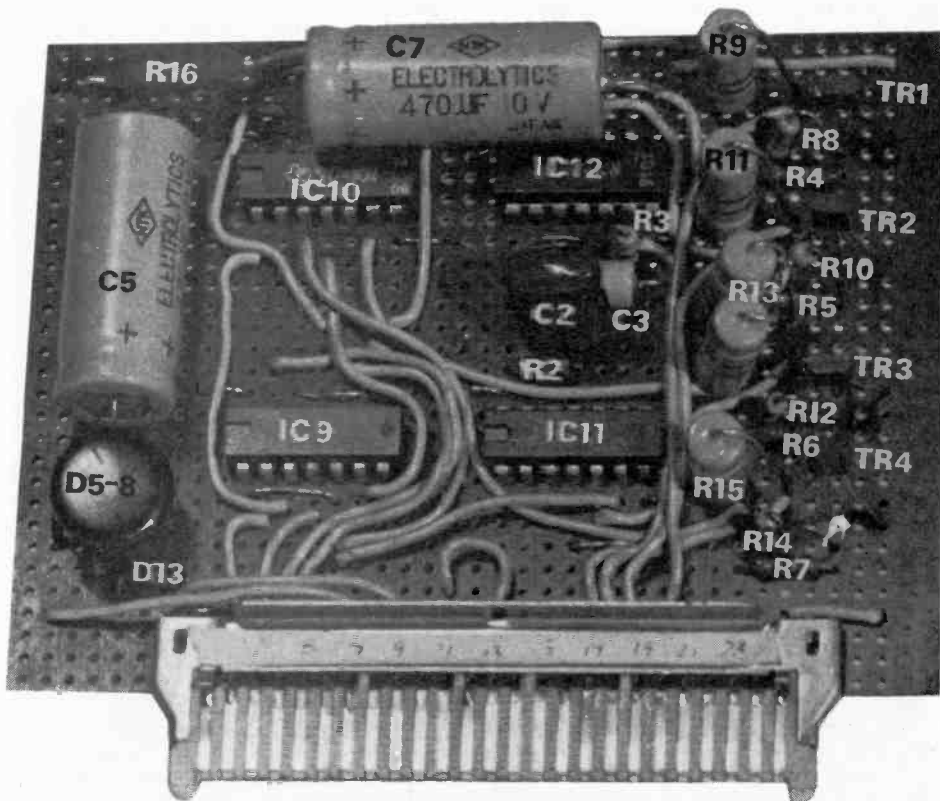


Fig. 6. Board B carries the 5V power supply components, triac drivers, and output gating circuits

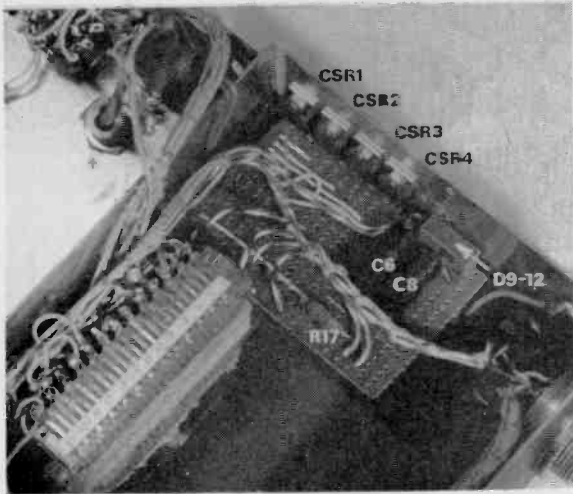


Fig. 7. The triacs CSR1 to 4 are bolted to the side of the case as shown with their leads in the piece of stripboard. Also on the stripboard are the -6V power supply components

CONSTRUCTION OF THE LAMP DISPLAYS

The construction of the light display boxes is shown in Fig. 9.

The unit is made from five-ply hardboard to make it sturdy. The units used with the Discostrobe were finished in matt black paint and the effect was very pleasing.

More of these units may be constructed but ensure that the rating of the triacs is not exceeded when there are a number of lamps per channel.

Ideally, four different colour lamps should be used: these should be mains spotlight types with bayonet fittings to match the connectors.

TESTING

No adjustments are necessary when the unit is complete. Before connecting the lamp display to the unit, the logic circuitry may easily be checked by observing the four l.e.d.s on the front panel. If the three modes operate correctly on monitoring these lamps then the light display boxes may be connected.

If the logic circuitry does not operate correctly and no suitable test equipment is available, then a useful tool for fault finding is a simple logic probe which is easily constructed and will be useful in other logic applications.

Details of a suitable probe are shown in Fig. 10.

To use the probe, connect the flying lead to the common rail (in this case the neutral of the mains supply). The probe can then be moved around the integrated circuit pins. A logic 1 is indicated by the l.e.d. lighting.

INCORRECT TRIGGERING

It is possible that when the lamp displays are connected a channel may not trigger correctly. This will be indicated by the lamp(s) on that channel becoming half-lit or pulsating with, possibly, false logic switching.

The effect is due to small variations in the characteristics between triacs and can be overcome by reducing the values of resistors R9, 11, 13 or 15. The fault is that insufficient gate current is getting to the triac with the component values specified.

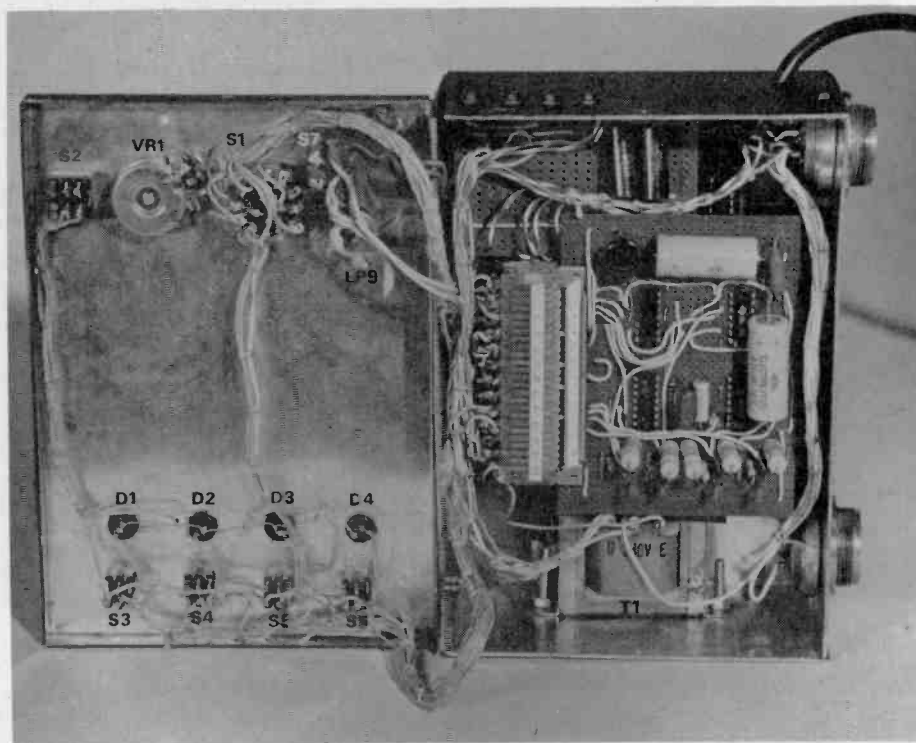


Fig. 8. The switches, potentiometer and l.e.d.s are mounted on the lid of the case as shown

Fig. 9. Construction of the light display boxes (2 off required). The boxes are constructed from 5-ply hardboard

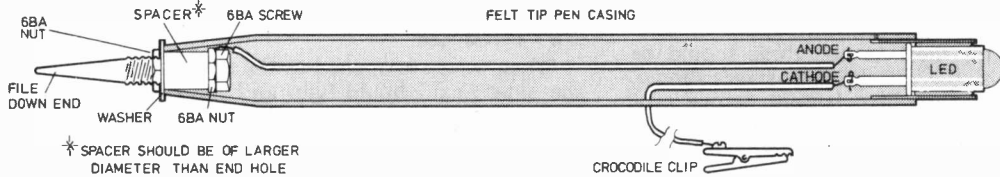
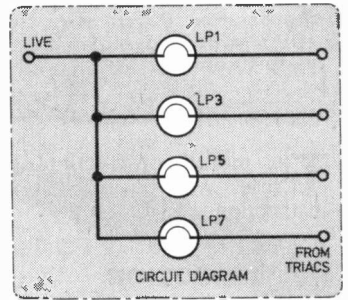
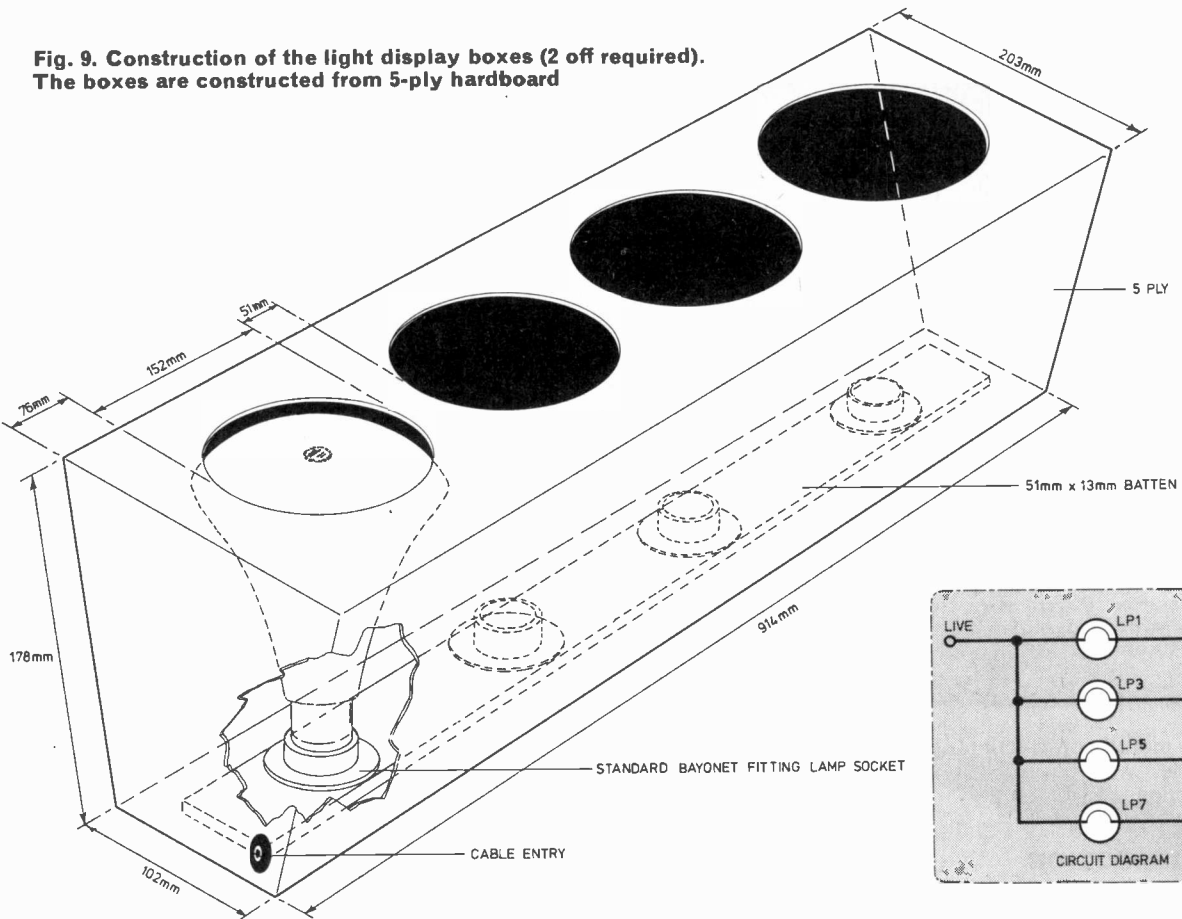


Fig. 10 A simple logic probe useful for fault finding

The fault is possible since the gate current with these values is very near to the minimum limit in an attempt to keep the drain on the $-6V$ line as low as possible.

Provided the rating of the transformer T1 is over $\frac{1}{4}A$ the values R9, 11, 13 or 15 can be reduced to about 100 ohms quite satisfactorily.

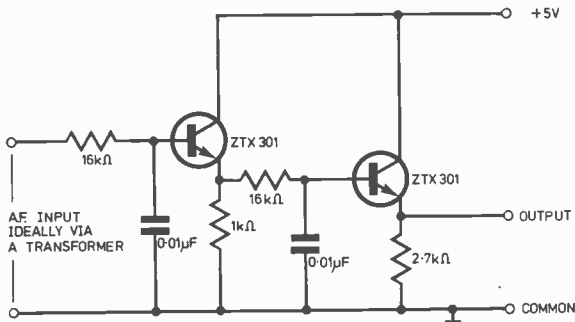


Fig. 11. This circuit may be used to replace the main oscillator in the Discostrobe system. It gives a 12dB per octave roll off above 1kHz

EXPANSION

Provision has been made in the circuit design for expansion in a number of areas.

The strobe effect may be synchronised to the beat of the disco music rather than the internal oscillator by connecting a suitable circuit to the input to IC2a (pin 3). Either the internal oscillator (IC1, C1, R1 and VR1) may be eliminated or a switch may be used to give the two alternatives. A circuit to detect the beat of the music need not be complicated, a suggested configuration being shown in Fig. 11.

The number of lamps per channel may be increased as explained earlier. Always allow an adequate margin between expected current and triac current rating. For example, if six 100W lamps are to be driven the current per channel is about 3A so use a triac with a 4A capability. ★

CINE/TAPE SYNCHRONISER

PART 2

By N.V. DAVIES

... featuring a CMOS 12-bit magnitude comparator

THIS month construction of the Cine/Tape Synchroniser will be detailed together with setting-up instructions.

CONSTRUCTION

The Sync Indicator is constructed on a d.i.l. Breadboard. Due to the complexity of the interconnecting wiring between the i.c.s, this is shown in two stages in Fig. 4.

Sockets are used for the i.c.s and these should be fitted first, followed by the wiring in the stages shown. Each stage should be carefully checked before proceeding to the next, paying particular attention to the possibility of shorts between the copper conductors or socket pins.

As many different colours of connecting wire as possible should be used to make checking easier.

On completion of the wiring the i.c.s can be inserted, the normal precautions for handling CMOS i.c.s being taken.

No details of mechanical construction or housing are given as the requirements depend on whether a battery or mains power supply is incorporated, so this is left to the individual constructor.

Plugs and sockets will be required for connections to the tape recorder and these should match the constructor's existing equipment.

Suitable cases are available from many advertisers in this magazine.

If space is available, the unit can, of course, be built into the projector (as was the prototype, see Fig. 5), or into the tape recorder. The circuit layout is not critical and can be split over a number of smaller boards to fit the space available.

If the unit is built into the projector, the photodiode D1 may be placed inside the projector case using the opposite side of the shutter, and if insufficient light is available from the projector lamp in this position, a separate small panel-type lamp can be used. An i.e.d. could be used, but in this case a more sensitive photodetector such as the 2N5777 would be necessary. In the


prototype the photodiode mounting was as shown in Fig. 6.

The i.e.d. indicators are shown mounted on the circuit board for convenience. They can, of course, be mounted in any convenient position and connected to the board by suitable leads.

SETTING UP

When power is applied to the Sync Indicator board, the SYNC i.e.d. should light and the remaining i.e.d.s remain unlit. If this is not the case, a fault must exist and the power supply must be switched off (and disconnected from the mains if a mains power supply is being used) and the fault located and rectified.

Fig. 5. Side view of the prototype modified projector. Here the fully automatic synchronisation facility has been built in

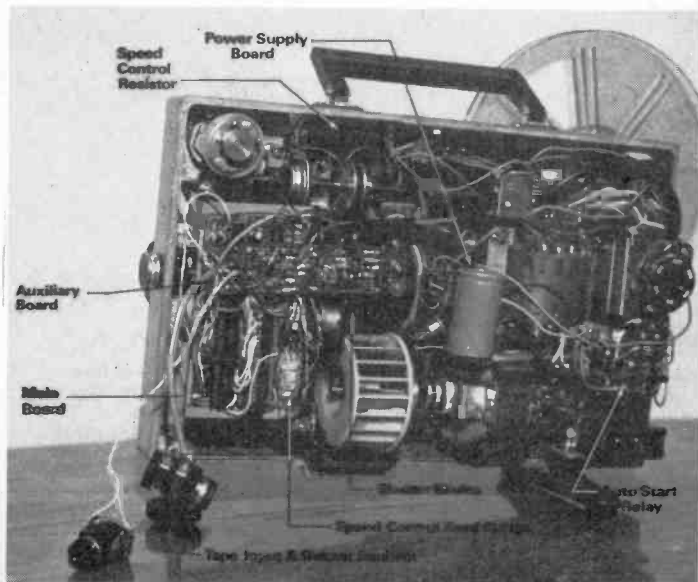

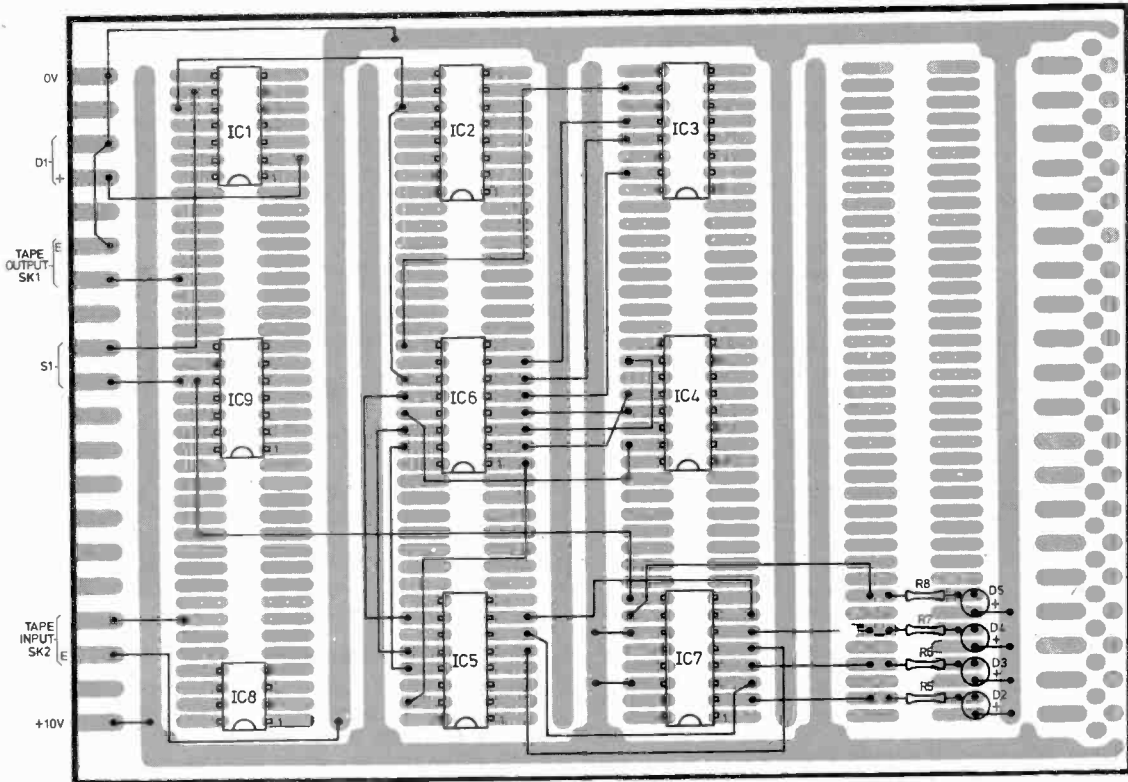
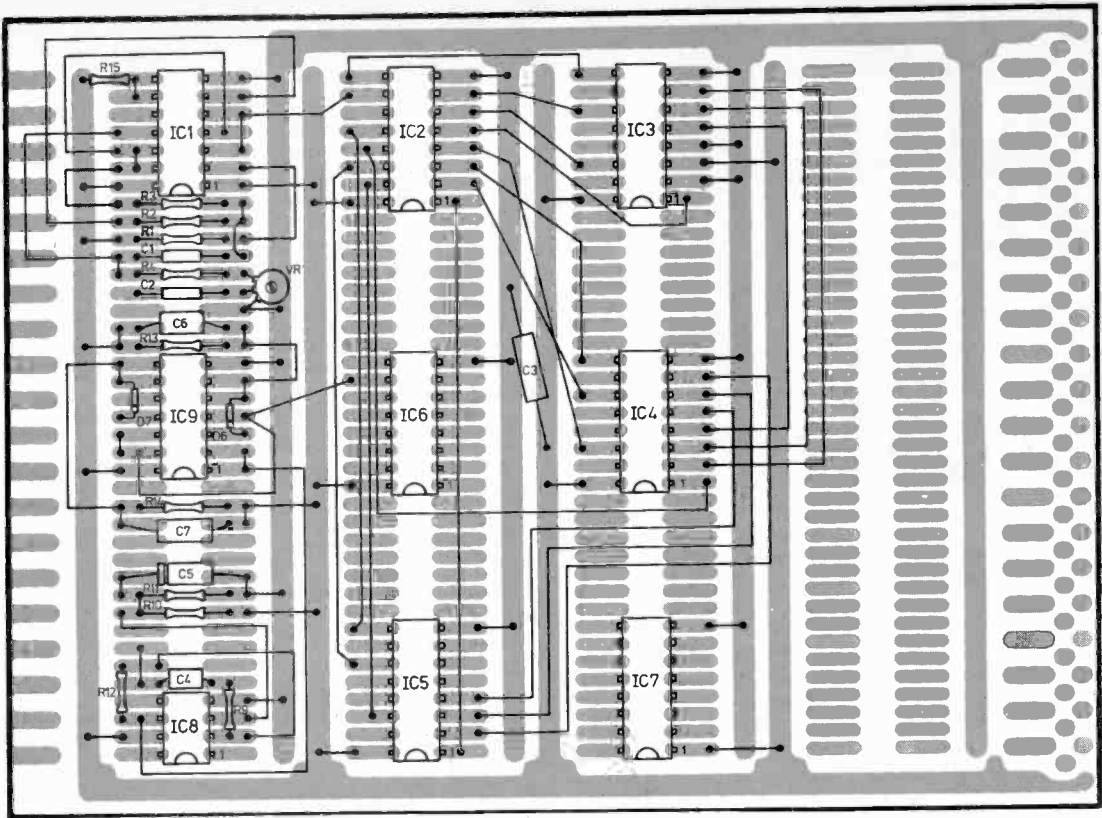


Fig. 4. Layout of components and interwiring on the DIP Breadboard. To simplify matters the wiring is shown in two stages

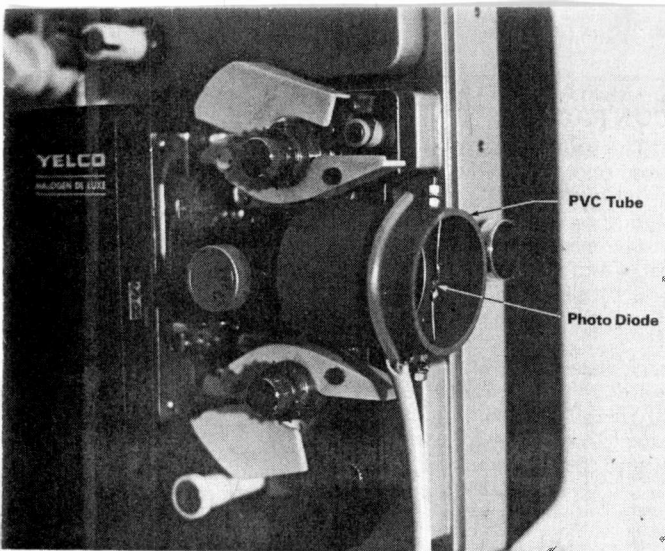


Fig. 6. The photodiode is mounted in a p.v.c. tube which fits over the lens mounting

Assuming that all is well, which it should be if reasonable care is taken during construction and reliable components used, the photodetector assembly should be placed over the projector lens and the projector started. It is not necessary to have any film in the projector during this test run.

The projector speed control may be at its normal setting provided this allows a small speed variation either up or down to allow sync errors to be corrected. The eye is extremely tolerant of small variations in projection speed so even if the speed has to be set slightly above or below its normal setting to allow this tolerance for synchronising, this will not be noticeable.

The output from the synchroniser should now be connected to the tape recorder high-level input and, with the recording level control set at a suitable level, VRI should be adjusted for full modulation of the tape as indicated on the recording level indicator.

A recording of the sync pulses of at least five minutes duration should now be made. On completion of the recording, the tape should be rewound back to the start and the projector stopped.

The line or external amplifier output of the tape recorder should now be connected to the Sync Indicator input and the tape played back.

The SYNC l.e.d. should go out as soon as the pulses are received from the tape and the START and SLOW l.e.d.s light.

The projector should now be started and its speed control set to a slightly higher speed than that used for the recording. After a few seconds, the projector counter will catch up with the tape counter, the SLOW l.e.d. will go out, the SYNC l.e.d. flash briefly, and the FAST l.e.d. light.

The projector should now be slowed down until the opposite process occurs and this should be repeated making smaller adjustments to the speed control on each occasion until the SYNC l.e.d. stays alight at full brilliance and the FAST and SLOW l.e.d.s either go out completely or one or the other just glows dimly.

This process sounds complicated but it takes longer to describe than it does to carry out, and after a little practice it will be performed almost automatically each time the projector is started.

IN USE

The first indication that tape and film are beginning to drift out of sync will be the dimming of the SYNC l.e.d., and brightening of either the FAST or SLOW l.e.d. depending on the direction of the sync error.

If no correction is made and the sync error continues to increase the SYNC l.e.d. will go out and either the FAST or SLOW l.e.d. come up to full brightness. At this stage the sync error is only one third of a frame and this would have to increase to four frames or more (depending upon the type of sound) before it became noticeable. Even if this amount of error or even more was allowed to occur, it would only be necessary to adjust the projector speed as indicated by the l.e.d. which is alight and the Sync Indicator will show when sync has been restored.

RECORDING A SOUND TRACK

When recording an actual sound track the film should be loaded on the projector and stopped when the first frame is in the gate.

The Sync Indicator is set up for recording the sync pulses on one track of the tape, while the other track is used for the film sound track. The tape recorder is started, followed by the projector.

It is not necessary to record the whole of the film sound track in one go as, provided the tape recorder can be switched to record on the track used for the film sound while replaying the sync pulse track, once the complete pulse track has been recorded, the tape and film can be rewound and the sound track re-recorded as necessary to obtain the desired result, using the Sync Indicator to keep the film and tape in sync.

The process can be repeated as many times as is necessary. If S1 is opened once the projector has started at the beginning of the film, it will be possible to stop the projector and tape recorder at any point during the film without the loss of tape pulses resetting the counters and sync being lost. This enables the recorder to be stopped to switch from record to playback or vice versa to alter and re-record part of the sound track. The tape recorder and projector must, of course, be stopped or restarted within a few seconds of each other.

Each time the film and tape are rewound it is necessary to load the film so that the first frame is in the gate before starting the tape recorder, and the projector must not be started until the START l.e.d. lights. This rule must be observed on each subsequent showing of the film and sound track.

AUTOMATIC PROJECTOR START

Automatic projector start controlled by the tape pulses is easy to arrange as the power supplies to the projector can be switched by a relay operated by a transistor connected to the START l.e.d. driver. The relay used must be suitable for switching mains voltage and the full load current of the projector, a suitable circuit being shown in Fig. 7.

MONO TAPE RECORDERS

Two methods of using the Sync Indicator with mono tape recorders are possible. An additional pulse replay head operating on the lower track can be fitted. No additional record or erase head is necessary as the sync pulses may be recorded first using the existing heads and the tape then reversed to record the sound track, using the sync pulses to keep the film and tape in sync.

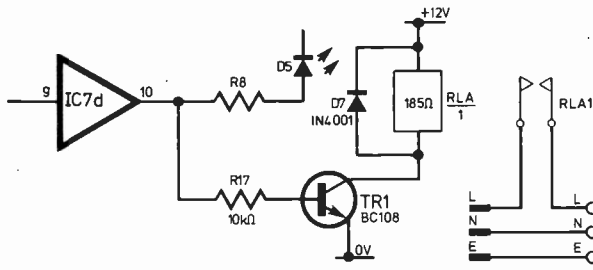


Fig. 7. To produce automatic start and stop the start driver IC7d is used to drive a relay via the transistor TR1. The relay controls the supply to the projector and should have contacts rated at 240V 5A a.c.

CAMERAS WITH SOUND SYNC CONTACTS

The sound sync contacts in cameras fitted with such close once per frame and a small battery powered unit using one CD4011 can be built to produce a burst of square waves each time the contacts close.

The circuit is similar to that used in the Sync Indicator and is shown in Fig. 10.

Because the pulse bursts will be at frame frequency, it will be necessary to fit a divide-by-three counter in the Sync Indicator circuit as was done for use with the perforated tape but, as in this case it may also be required to produce sync pulses for recording, the original circuit of IC1 must be retained and a further CD4011 used. The alterations necessary to the Sync Indicator circuit are shown in Fig. 11.

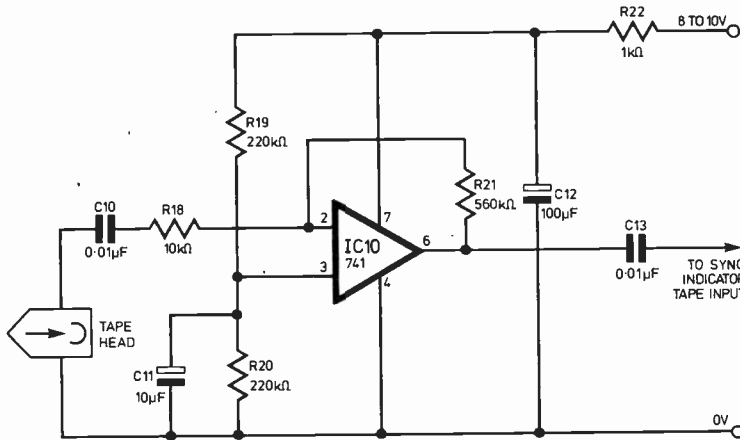


Fig. 8. When using mono tape recorders fitted with an extra head, this preamplifier circuit is necessary

If the recorder is fitted with $\frac{1}{2}$ track heads, the unused half of the existing head can be used.

A replay preamplifier for the pulse head will be required and a suitable circuit is shown in Fig. 8. As pulses only are to be amplified, no replay equalisation is required.

The second alternative is to use perforated tape which is available from various advertisers in photographic magazines and can be obtained with either 16 or 18 perforations per $3\frac{1}{2}$ or $7\frac{1}{2}$ inches. The correct type for the projection and tape speed to be used should be obtained.

The passage of the perforations is sensed by a photo-detector and l.e.d. placed on either side of the tape in line with the perforations and mounted in a suitable housing to exclude light.

Because the pulses produced from the perforations will be at frame rather than shutter frequency, it will be necessary to fit a divide-by-three counter between the output of IC1a and the input to the projector pulse counter.

The circuit used is a CD4018 presetable divide-by-n counter connected to divide by three by connecting the Q1 and Q2 outputs back to the data input via a NAND gate and inverter.

As the circuit to produce the bursts of square waves for recording is no longer required, the spare gates in IC1 can be used. The alterations necessary to the Sync Indicator are shown in Fig. 9.

FULLY AUTOMATIC SYNCHRONISATION

Whilst not wishing to discourage anyone from attempting fully automatic synchronisation, it must be understood that mains voltages are being dealt with and

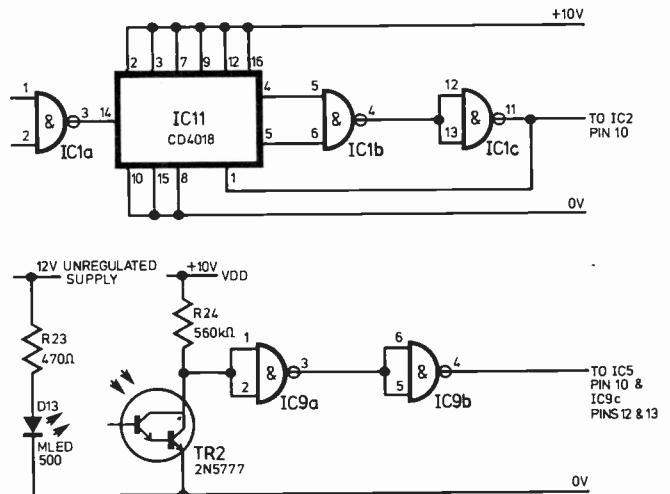


Fig. 9. Modifications to enable the synchroniser to be used with a mono tape recorder using perforated tape

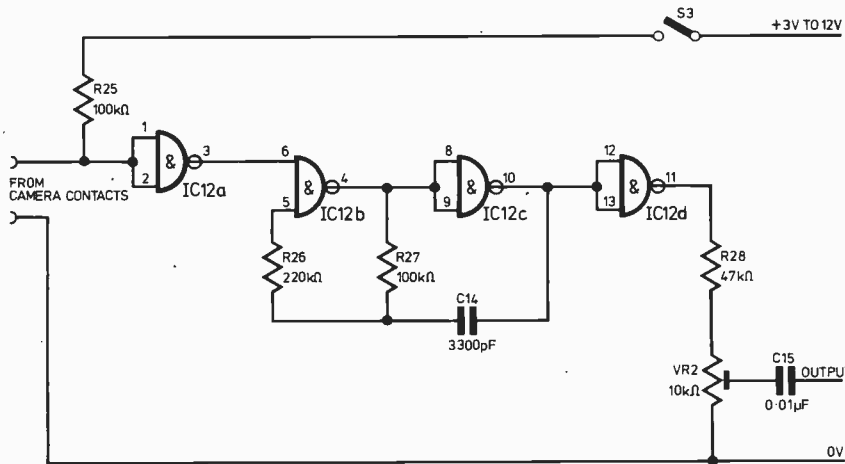


Fig. 10. A pulse generator circuit suitable for use with cameras fitted with sound sync contacts

all the necessary precautions must be observed: the projector must be disconnected from the mains before carrying out any work on the internal circuitry.

The actual modification to the projector will, in most cases, only involve fitting a mains socket which is connected in the projector motor circuit to enable this to be brought out to the synchroniser.

It will be essential to determine the type of motor fitted and, if necessary, the manufacturer's data should be consulted.

Because of the wide variety of projectors in use and the different types of motor fitted, only general guidance and suggested circuits which may be adapted for use with a particular type of motor can be given.

A.C. COMMUTATOR MOTORS AND RHEOSTAT SPEED CONTROL

Projectors fitted with a.c. commutator motors and rheostat variable speed control were, until recently, the most common. The projector speed is continuously variable from under 16 f.p.s. up to 24 f.p.s. by means of a variable resistor in series with the motor.

Automatic speed control and synchronisation can be achieved by connecting additional resistors in series with the speed control rheostat and arranging for these resistors to be shorted out in sequence by relays controlled by the SYNC and SLOW i.e.d. driver outputs.

This was the method adopted by the author for his Yelco P111Q projector and the circuit used is shown in Fig. 12.

The miniature reed relays RLB and RLC have 12V, 1,040 ohm coils but will operate from as little as six volts so could be driven directly by the two spare buffers in the CD4050 package IC7.

The author was rather dubious about using this arrangement as no information was available on the performance of CMOS buffers into an inductive load. The prototype synchroniser has, however, been in extensive use for a number of months and no problems have occurred. Separate driver transistors could be used and would be required in any case if heavier duty relays had to be used to carry the projector motor load.

The circuit shown for the auto-start relay would be suitable but high speed relays would be necessary as they have to operate at over 50Hz on occasions.

The value of the speed control resistors has to be determined experimentally—about ten per cent of the value of the speed control rheostat would be a good starting point. The resistors must be wirewound types rated to carry the full motor current.

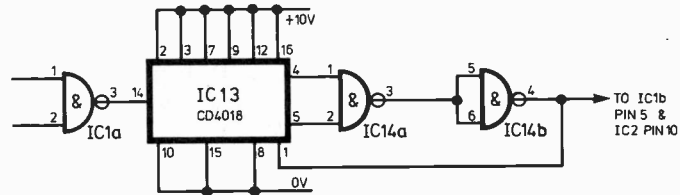


Fig. 11. Modifications to Sync Indicator circuit to operate at frame frequency for use with sync pulses recorded from camera sound sync contacts. IC14c and d are unused and their inputs should be connected to 10V line

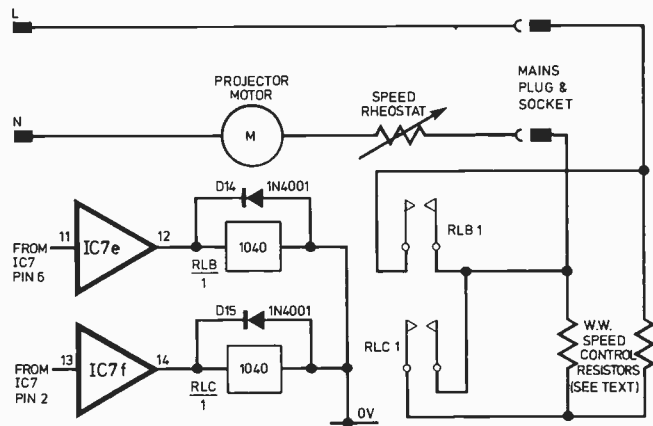


Fig. 12. Auto synchroniser circuit for use with projectors having rheostat speed control. The relays are reed types with 250V 0.5A contacts

If the resistors are too low in value insufficient speed variation will be obtained for reliable synchronisation and if they are too high in value the projector motor will tend to hunt instead of running at a steady speed.

SOLID STATE SPEED CONTROL

An alternative all solid state method of speed control is shown in Fig. 13. This uses an opto-isolator made by cementing an i.e.d. to an ORP12 photoresistor using epoxy glue and giving the whole assembly a liberal coating of black paint to exclude external light.

The opto-isolator is used to isolate the Sync Indicator from the mains part of the circuit which uses a power transistor connected across a bridge rectifier as a variable speed control resistor.

The power transistor will have to dissipate a number of watts so must be fitted with an adequate heatsink from which it must be isolated as the transistor casing will be at mains voltage.

The three preset resistors must be adjusted to obtain correct speed control, starting at a minimum value to avoid excessive dissipation in the power transistor.

The fixed series resistors prevent excessive current being drawn from the drivers.

As no thermal stabilisation is incorporated, the projector will tend to speed up as the temperature of the power transistor rises but once a stable temperature is reached the circuit will operate satisfactorily.

ELECTRONICALLY GOVERNED D.C. MOTORS

In projectors with electronically governed d.c. motors, it may be possible to identify a preset resistor which is used during manufacture to set up the projector speed, or resistors which are switched into circuit by the projector speed control.

If this is so, the circuit of Fig. 12 using suitable value resistors or the circuit of Fig. 13 with the rectifier removed may be connected in series or possibly in parallel with one of these resistors in order to control the projector speed by the synchroniser.

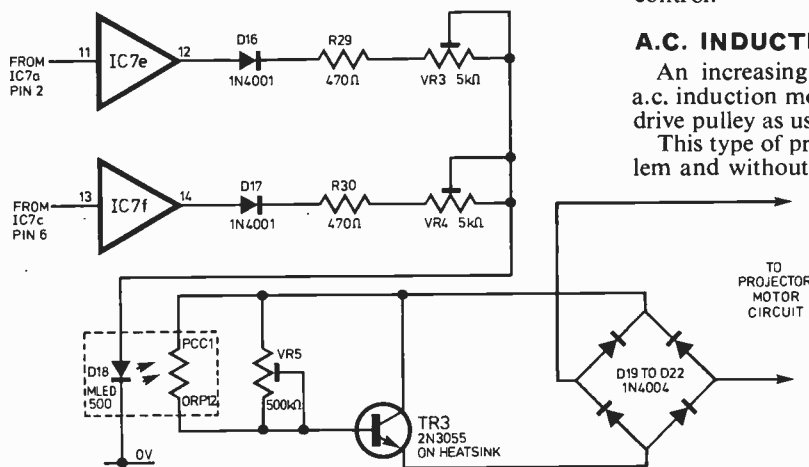


Fig. 13. All solid state auto synchroniser. D18 and PCC1 form an opto-isolator to isolate the synchroniser circuit from the mains. TR3 must be fitted with a heatsink from which it is insulated as its case will be at mains potential

If a circuit diagram of the projector speed control can be obtained or traced from the wiring this will of course make it much easier to identify a suitable point to connect the synchroniser.

PROJECTORS WITH COARSE SPEED CONTROLS

Constructors whose projectors have rather coarse speed controls may have difficulty in adjusting the projector speed to maintain sync within plus or minus one third of a frame for any length of time. In this case a simple modification to the sync indicator circuit will give a better indication of the magnitude of sync error over a much wider range, and also indicate within this range whether the sync error is increasing or decreasing.

The modification is to disconnect the cascading outputs of the first CD4063 (IC3) from the cascading inputs of the second CD4063 (IC4), and connect the cascading inputs of IC4 as follows: Pin 3 to +10V, Pins 2 and 4 to 0V. Constructors who have used sockets for the i.c.s. can remove IC3 as it no longer serves any purpose in the circuit. As a result of this modification, the first four stages of the CD4040 counters act simply as dividers and the comparator and sync indicator will now operate at one sixteenth of shutter frequency.

With the modified circuit, when a sync error occurs the SYNC l.e.d. and (depending upon the direction of error) either the FAST or SLOW l.e.d. will begin to flash on and off due to the phase difference at the comparator inputs. At small sync errors the phase difference will be small and the SYNC l.e.d. will be on for longer than it is off, while the appropriate error l.e.d. will be off for longer than it is on. If the sync error increases, the phase difference will increase and this will be indicated by an increase in the off period of the SYNC l.e.d. and the on period of the error l.e.d. until the sync error reaches $5\frac{1}{2}$ frames. At this point the phase difference will be 360° and the SYNC l.e.d. will extinguish and the error l.e.d. remain on.

This modification gives a good indication of the magnitude as well as the direction of sync error over the range of plus or minus $5\frac{1}{2}$ frames, which should be sufficient for all practical purposes. The modification is not however recommended if it is intended to use the circuit for automatic speed control.

A.C. INDUCTION MOTORS

An increasing number of manufacturers are using a.c. induction motors with speed selection by a stepped drive pulley as used on tape recorders.

This type of projector presents the most serious problem and without resorting to drastic measures such as

changing the motor, very little can be done. The only possible approach appears to be to supply the motor or indeed the entire projector from a transistor inverter, the frequency of which can be controlled by the synchroniser.

This solution, although complicated, is extremely attractive as it would enable modern projectors such as the Eumig 610D to be synchronised and no modifications to the projector would be necessary, as the projector would simply be plugged into the inverter instead of the mains. ★

NOTE

The MRD150 photo-diode, the MLED500 l.e.d.s and the 2N5777 Darlington pair are available from Fibre Optic Supplies, 2 Loudoun Road Mews, London, NW8 0DN.

INGENUITY UNLIMITED



A selection of readers suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

Please Note

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

A SIMPLÉ ACCENTING METRONOME

THE circuit shows a means of using the 2N2646 unijunction transistors for providing audible beats, with bar accents, directly in a loudspeaker. This arrangement is far simpler and cheaper than has been described with the use of a number of integrated circuits.

Two unijunction transistors are used, with their b1 bases returned to negative supply via the loudspeaker coil. TR1 generates the tempo beat rate, adjustable by VR1, while TR3 generates the bar accent beats adjustable by VR2.

The tempo beat generator is a conventional relaxation oscillator circuit. The sudden discharges of C1

occurs at each discharge of C1 during the tempo beats. Differentiation by C2, R2 limits these negative excursions to uniform negative "spikes". C3, therefore, receives a uniform length pulse on each tempo beat at a charging rate determined by the setting of VR2. Diode D1 ensures that the charge does not leak back between pulses. During one of the tempo beats the stepped charge on C3 will be sufficient to fire TR3. The discharge of C3 via the emitter and loudspeaker coil will then augment (or accent) the tempo beat. The setting of VR2 determines the number of beats per each accent.

It has been found that wirewound variable resistors are suitable for VR1 and VR2 which may be calibrated for tempo and beats in the bar. By tapping off the loudspeaker coil via a capacitor and feeding into an

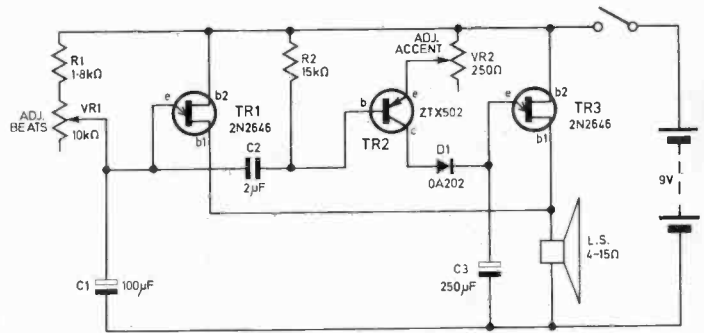


Fig. 1

via the emitter and the loudspeaker coil produce clearly audible beats.

Switching transistor TR2 is a npn type which is rendered conductive between emitter and collector only when the base goes negative. This

amplifier and loudspeaker some interesting drum effects may be obtained.

F. Hayes,
Southall,
Middlesex.

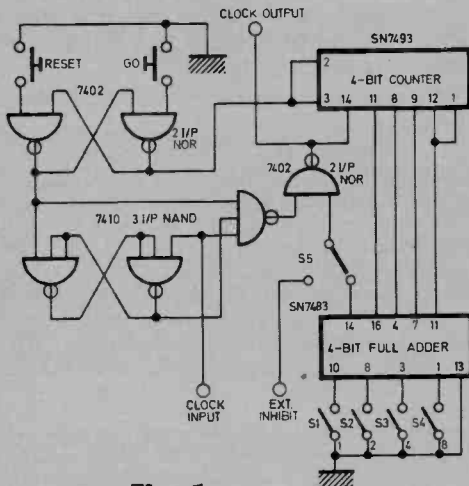



Fig. 1

PROGRAMMABLE LOGIC GENERATOR

WHEN checking static logic levels, or complete logic circuits, it is useful to have available a programmable source of clock pulses, so that the circuit can be "frozen" after a finite number of pulses have been input. Ideally, the source should provide pulse trains either of a fixed number of pulses, or which can be terminated by a logic level within the unit under test.

This circuit (Fig. 1) will give fixed length pulse trains of between 1 and 15 pulses as set by switches S1 to S4, initiated by pressing the RESET and GO switches in sequence. Alternatively the train can be terminated by a signal on the EXT INHIBIT input.

J. R. Keneally,
Weymouth,
Dorset.

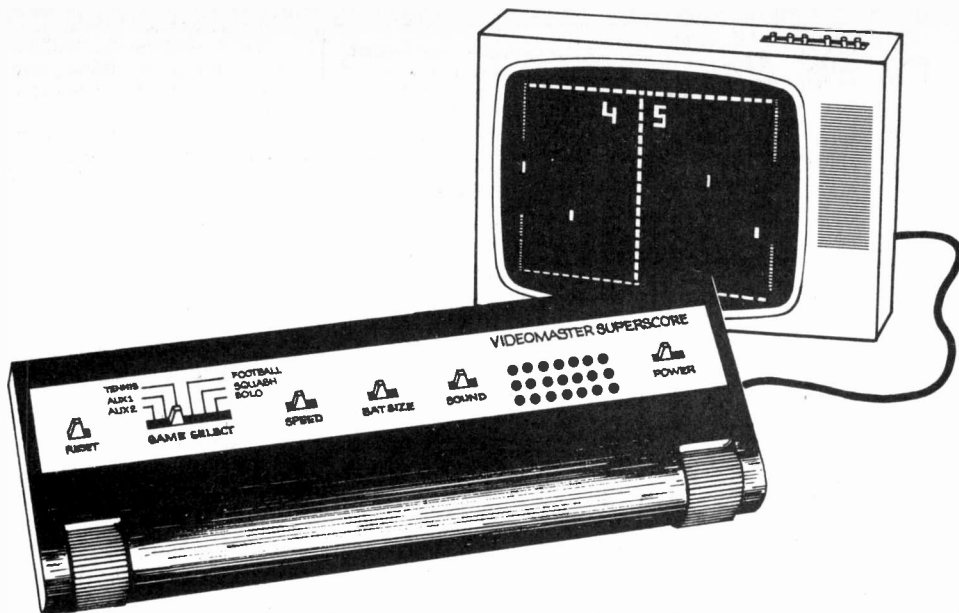

Here's the remarkable new **VIDEOMASTER™** Superscore Home TV Game Get it together for only £24.95

Available to you in kit form at the same moment as its national launch, the brilliant new Videomaster Superscore contains the latest product of MOS technology: a TV game chip.

The logic contained in it had previously to be generated by 100 TTL devices. Now it is condensed into one 28-pin chip.

This all-new Videomaster plugs into your 625-line UHF TV set (for overseas customers having VHF sets we can supply the necessary VHF modulator) to give you four exciting games (including tennis and football) and two future game options. It features on-screen digital scoring, realistic hit sounds, two bat sizes, two

ball speeds, automatic serving and much more. It runs on six 1½ volt SP11 type batteries (not supplied).

The Videomaster Superscore kit costs only £24.95 including VAT (recommended retail price of the ready built model is over £40.00) and comes complete with ready-tuned UHF or VHF modulator, circuit board with printed legend, all resistors, transistors and diodes, built-in loudspeaker, socket for mains adaptor, and, of course, the TV game chip itself.

Easy to put together the Superscore has full assembly instructions, circuit diagram and circuit description. Don't miss this chance to own the newest electronic game at such low cost.

POST TODAY TO:

Videomaster Ltd 14/20 Headfort Place, London SW1X 7HN



Please send me (insert No. requ'd).....Videomaster Superscore Kits at £24.95 (inc. VAT & P&P in UK) or £23.10+£4.00 for P&P overseas)

I enclose my cheque/money order* for £.....

VHF modulator required YES/NO*

PE71

NAME _____

ADDRESS _____

ALLOW 21 DAYS FOR DELIVERY

* delete as necessary

RST VALVE MAIL ORDER CO.

Climax House
159 Fallsbrook Road, London SW16 6ED
SPECIAL EXPRESS MAIL ORDER SERVICE

Sp	AF181	0-50	BY213	0-25	OAZ204	0-45	XB121	0-48	
1N21	0-17	AF181	0-50	BY213	0-25	OAZ204	0-45	XB121	0-48
1N23	0-85	AF186	0-48	BY210	0-45	OAZ205	0-45	ZB170	0-12
1N45	0-88	AF211	1-15	BY211	0-40	OAZ206	0-45	ZB271	0-30
1N253	0-50	AF212	2-00	BY212	0-40	OAZ207	0-45	ZT21	0-85
1N256	0-50	AS326	0-25	BY213	0-42	OAZ208	0-40	ZT43	0-85
1N455	0-16	AS329	0-45	BY215	1-35	OAZ209	0-40	ZTX107	0-12
1N725A	0-20	AS330	0-20	BY216	0-60	OAZ210	0-40	ZTX300	0-13
1N914	0-06	AS351	0-40	BZY88	0-10	OAZ211	0-40	ZTX304	0-24
1N4007	0-12	AS353	0-20	CI111	0-55	OAZ222	0-45	ZTX500	0-13
1B113	0-85	AS355	0-20	CR81/05	0-45	OAZ223	0-45	ZTX531	0-85
1B202	0-88	AS356	0-88	CR81/40	0-65	OAZ224	0-45		
2G371	0-75	AS357	1-00	CR84B	1-90	OAZ241	0-85		
2G381	0-82	AS358	0-75	CR1015	3-50	OAZ242	0-85		
2G414	0-80	AU104	1-00	DD000	0-15	OAZ246	0-15	7400	0-16
2G417	0-25	AUY10	1-50	DD003	0-15	OAZ290	0-38	7401	0-16
2N404	0-85	BC107	0-14	DD006	0-25	OC16	1-00	7402	0-16
2N497	0-16	BC108	0-12	DD007	0-40	OC16T	1-00	7403	0-16
2N688	0-80	BC109	0-14	DD008	0-88	OC22	1-00	7404	0-86
2N706	0-12	BC113	0-15	GE3	0-33	OC23	1-25	7405	0-82
2N706A	0-12	BC115	0-20	GD4	0-10	OC24	1-10	7406	0-42
2N708	0-15	BC116	0-20	GD5	0-33	OC25	0-40	7407	0-42
2N709	0-40	BC118A	0-23	GD8	0-25	OC26	0-40	7408	0-28
2N709	0-40	BC118	0-20	GD12	0-10	OC28	0-75	7409	0-28
2N1081	0-55	BC121	0-20	GET102	0-50	OC29	0-65	7410	0-18
2N1131	0-25	BC122	0-20	GET103	0-40	OC30	0-40	7411	0-30
2N1132	0-24	BC125	0-68	GET113	0-85	OC35	0-75	7412	0-30
2N1302	0-18	BC126	0-45	GET114	0-30	OC36	0-68	7413	0-86
2N1303	0-18	BC140	0-65	GET115	0-90	OC41	0-35	7416	0-86
2N1304	0-28	BC147	0-10	GET116	0-85	OC42	0-40	7417	0-86
2N1305	0-28	BC148	0-08	GET120	0-50	OC43	0-70	7420	0-18
2N1306	0-28	BC149	0-10	GET872	0-30	OC44	0-20	7422	0-25
2N1307	0-28	BC157	0-14	GET875	0-40	OC44M	0-17	7423	0-27
2N2147	1-25	BC158	0-12	GET880	0-60	OC45	0-20	7425	0-37
2N2148	0-80	BC160	0-63	GET881	0-25	OC45M	0-18	7427	0-87
2N2180	0-78	BC169	0-14	GET882	0-35	OC46	0-87	7428	0-40
2N2180	0-78	BC169	0-14	GET885	0-40	OC57	0-60	7430	0-18
2N2218	0-28	BCY31	0-45	GEX44	0-08	OC58	0-60	7432	0-37
2N2219	0-28	BCY32	0-85	GEX45/1	0-45	OC59	0-80	7433	0-27
2N2389A	0-16	BCY33	0-38	GEX941	0-45	OC66	0-80	7437	0-87
2N2444	1-09	BCY38	0-38	GJ3M	0-50	OC70	0-13	7438	0-37
2N2613	0-75	BCY38	1-00	GJ4M	0-60	OC71	0-25	7440	0-82
2N2646	0-60	BCY39	1-50	GJ5M	0-25	OC72	0-28	7441AN	0-92
2N2904	0-20	BCY40	0-80	GJ7M	0-50	OC73	0-50	7442	0-78
2N2906	0-80	BCY42	0-80	HG1005	0-50	OC74	0-30	7450	0-18
2N2907	0-88	BCY70	0-13	HS100A	0-20	OC75	0-30	7451	0-18
2N2924	0-13	BCY71	0-22	MAT100	0-20	OC76	0-30	7453	0-18
2N2925	0-15	BCZ10	0-48	MAT101	0-20	OC77	0-30	7454	0-16
2N2926	0-12	BD121	1-00	MAT120	0-90	OC78	0-25	7460	0-18
2N3054	0-43	BD123	1-00	MAT121	0-25	OC79	0-30	7470	0-38
2N3055	0-65	BD124	0-65	MJE340	0-47	OC81	0-29	7472	0-38
2N3702	0-11	BDY11	1-45	MJE320	0-38	OC81M	0-20	7473	0-41
2N3705	0-15	BF115	0-20	MJE2955	1-27	OC81DM	0-18	7474	0-59
2N3706	0-11	BF167	0-25	MJE3055	0-77	OC81Z	0-75	7475	0-59
2N3707	0-13	BF192	0-48	MPF102	0-40	OC82	0-20	7476	0-45
2N3709	0-10	BF181	0-85	MPF103	0-38	OC82M	0-25	7477	0-80
2N3710	0-11	BF184	0-22	MPF104	0-35	OC83	0-60	7482	0-87
2N3711	0-11	BF185	0-22	MPF105	0-38	OC84	0-30	7483	1-10
2N3618	0-28	BF194	0-10	NE555	0-42	OC114	0-38	7484	1-00
2N4259	0-80	BF196	0-13	NKT128	0-45	OC122	1-00	7486	0-47
2N5027	0-53	BF196	0-15	NKT129	0-80	OC123	1-10	7490	0-55
2N5088	0-83	BF197	0-15	NKT129	0-80	OC129	1-00	7491AN	1-00
2S801	0-59	BF861	0-25	NKT211	0-25	OC130	1-40	7492	0-70
2S804	1-15	BF898	0-25	NKT214	0-24	OC141	0-80	7493	0-70
2S801	0-76	BFX12	0-20	NKT216	0-40	OC169	0-20	7494	0-80
2S793	1-00	BFX13	0-26	NKT217	0-45	OC170	0-30	7495	0-80
40250	0-54	BFX29	0-28	NKT218	0-45	OC171	0-80	7496	0-95
40251	0-81	BFX50	0-28	NKT219	0-58	OC200	1-00	7497	0-87
AA129	0-70	BFX35	0-98	NKT222	0-30	OC201	1-60	74100	1-89
AAZ12	0-26	BFX63	0-60	NKT224	0-25	OC202	1-50	74107	0-45
AAZ13	0-12	BFX84	0-25	NKT251	0-24	OC203	1-25	74110	0-68
AAZ17	0-13	BFX85	0-28	NKT271	0-20	OC204	1-60	74111	0-86
AC107	0-21	BFX86	0-25	NKT272	0-80	OC205	1-75	74115	0-90
AC126	0-25	BFX87	0-25	NKT273	0-20	OC206	1-10	74119	1-88
AC127	0-25	BFX88	0-24	NKT275	0-60	OC206	1-10	74121	0-60
AC128	0-15	BFY10	0-50	NKT277	0-20	OC207	1-00	74122	0-70
AC187	0-21	BFY11	0-60	NKT278	0-25	OC460	0-20	74123	1-00
AC188	0-20	BFY17	0-40	NKT301	1-00	OC470	0-20	74141	0-80
ACY17	0-75	BFY18	0-45	NKT304	1-00	OC71	1-20	74145	1-20
ACY18	0-85	BFY19	0-55	NKT403	1-00	ORP12	0-80	74150	1-75
ACY19	0-25	BFY24	0-45	NKT404	1-00	ORP60	0-85	74151	1-00
ACY20	0-35	BFY44	1-00	NKT678	0-30	ORP61	0-48	74154	2-00
ACY21	0-35	BFY50	0-21	NKT713	0-30	SX68	0-20	74155	1-00
ACY22	0-35	BFY51	0-20	NKT718	0-25	SX68	0-20	74156	1-00
ACY27	0-25	BFY52	0-20	NKT777	0-88	SX631	0-45	74157	0-95
ACY28	0-28	BFY53	0-17	OA5	0-72	SX635	0-55	74170	2-52
ACY39	0-78	BFY64	0-38	OA6	0-18	SX640	0-75	74174	1-87
ACY40	0-22	BR100	0-40	OA7	0-08	SX641	0-75	74175	1-10
ACY41	0-22	BR100	0-40	OA7	0-10	SX642	0-80	74176	1-26
ACY44	0-32	BRX27	0-20	OA71	0-26	SX644	0-85	74190	2-00
AD140	0-60	BRX60	0-93	OA73	0-15	SX645	0-85	74191	3-00
AD149	0-78	BSX76	0-18	OA74	0-15	TC144	0-29	74192	2-00
AD191	0-44	BSY26	0-17	OA79	0-10	V15/30P	0-75	74193	2-00
AD192	0-44	BSY27	0-20	OA81	0-18	V30/201P	0-75	74194	1-80
AF106	0-30	BSY61	0-60	OA85	0-15	V60/201	0-60	74195	1-10
AF114	0-25	BSY95A	1-12	OA86	0-15	V60/201P	0-75	74196	1-20
AF115	0-25	BT102/500R	0-12	OA90	0-07	XA101	0-10	74197	2-70
AF117	0-54	BT102/500R	0-12	OA90	0-07	XA102	0-10	74198	2-77
AF118	0-57	BTY42	0-75	OA95	0-07	XA102	0-10	74199	2-52
AF119	0-20	BTY79/100R	0-20	OA200	0-08	XA102	0-10		
AF124	0-30	BTY79/100R	0-20	OA200	0-08	XA151	0-15		
AF125	0-30	BTY79/400R	0-20	OA202	0-06	XA152	0-15		
AF126	0-30	BY100	0-27	OAZ200	0-60	XA192	0-25		
AF127	0-30	BY100	0-27	OAZ200	0-60	XB101	0-43		
AF139	0-41	BY126	0-14	OAZ201	0-45	XB102	0-30		
AF178	0-55	BY127	0-12	OAZ202	0-45	XB103	0-35		
AF179	0-65	BY182	0-85	OAZ203	0-45	XB113	0-30		
AF180	0-55	BY182	0-85	OAZ203	0-45				

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7
Quotations for any types not listed.
Post and Packing 15% per order.
V.A.T. to be added. Plastic Transistors 12 1/2%.
Metal Can Transistors 8%. Integrated Circuits 8%.

Prices correct when going to press.

Sound ideas

HI-FI FOR THE ENTHUSIAST

Sixth, Revised Edition M L Gayford
Cased £5.50

THE ELECTRONIC MUSICAL INSTRUMENT MANUAL

Sixth, Revised Edition Alan Douglas
Cased £7.50

RADIO CONSTRUCTION FOR AMATEURS

R H Warring
Paperback £2.50

Pitman Publishing Ltd (C)

39, Parker Street,
London WC2B 5PB

from Pitman

FEATURED IN "SOUND DESIGN"

READY-MADE INSTRUMENTS AVAILABLE



THE MINISONIC 2

probably represents the best value for money in electronic music today.
Kits are available for complete instruments or individual sections, or for the conversion of Mk. 1 Minisonics to Mk. 2 specification. (Conversion details apply to Eaton Audio P.C.B.s, but may be adapted to suit others.)
In order to ensure that the appearance of the complete instrument enhances its performance, a complete cabinet kit is available, incorporating a fully finished black enamelled, silk-screened front panel, with matching back and base, and solid Afrormosa end-cheeks. This kit also includes all switches, knobs, sockets, screws and panel indicators. Suitable keyboards and contact assemblies are also in stock.

Kit Description	Price	Kit Description	Price
Cabinet Kit (Inc. Keyboard, etc.) MS/2-1 & 2	£192-84	CONVERSION KITS	
Keyboard Controller MS/2-3	£8-67	Ancillary Functions Kit MS/2-14C	£11-87
Voltage Controlled Oscillator MS/2-4	£16-96	Power Supply—EAO15	£1-00
(Note—2 off MS/2-4 required)		Dual Transistor MD9001	£1-00
Sync. Kit MS/2-4 sync Envelope Shaper/VCA MS/2-5	£8-98	Operational Amplifier LM318N	£2-40
(Note—2 off MS/2-5 required)		Hind Modulator MS/2-9	£3-75
H.F. Oscillator/Detector MS/2-6	£1-94	Noise Generator MS/2-10	£2-00
Hold Isolator MS/2-7	£3-24	Output Amplifiers MS/2-11	£8-33
Voltage Controlled Filter MS/2-8	£7-54	Control Envelope Inverter MS/2-12	£3-51
Ring Modulator MS/2-9	£3-75	Stabilised Power Supply MS/2-13	£3-00
16 pin DIL	0-17		

EATON AUDIO

DEPT PE, P.O. BOX 3
ST. NEOTS, CAMBS
PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. MINIMUM ORDER £1. VAT: Please add 12 1/2% to value of order inc. P. & P. unless otherwise stated. Cheques or P.O.s payable to Eaton Audio. Orders over £5 free of P. & P., otherwise please add 10p in the £1.

SIMPLE TOUCH DIMMER

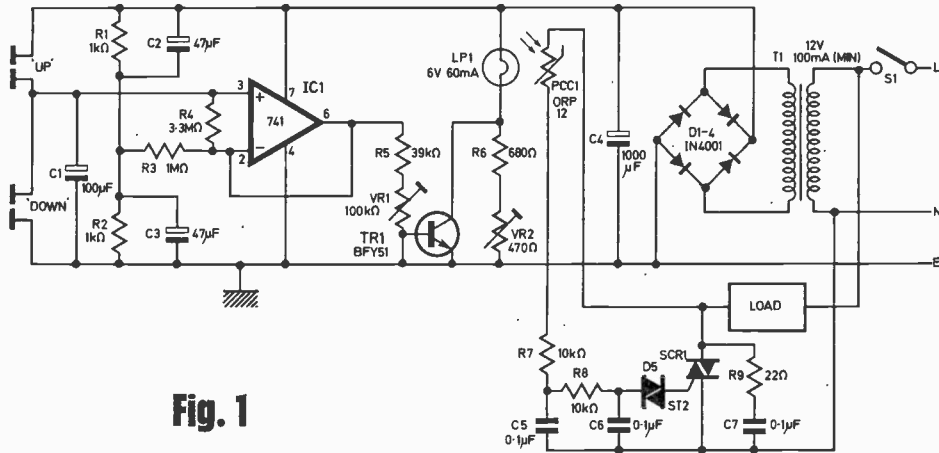


Fig. 1

THE two touch pads, which may consist of copper clad Veroboard with alternate tracks linked, are used to charge and discharge the $100\mu\text{F}$ capacitor C1 which acts as an analogue memory. The capacitor is connected to a d.c. buffer built around a 741 operational amplifier. This circuit is bootstrapped and displays an input impedance in the region of 400 megohms, giving a theoretical time constant in excess of 10 hours for the circuit. In practice, however, it was found that the capacitor had a tendency to drift towards the voltage at the junction of R1 and R2 over a period of about three hours. Since the dimmer was designed to be a novelty, this was not found to cause any real inconvenience as the same lighting level was rarely set for more than an hour at a time.

The output of the 741 is applied to TR1 which drives a small lamp—i.e.s. or m.e.s. 6V 0.06A—placed in close proximity to an ORP12 photocell, which replaces the potentiometer in a standard phase control dimmer circuit. The photocell and lamp should be taped together to exclude external light, with two layers of tissue paper between them. This helps to diffuse the light from the bulb and provide a more linear dimming effect. Great care should be taken that the two components are completely isolated from one another electrically. A heatsink clip is advisable for TR1. The low voltage electronics must be earthed. If they are not, static voltages can build up on the floating circuit and cause alarming though harmless shocks when the touch pads are touched.

Any large signal *npn* transistor is suitable for TR1. The type of triac used is not critical as the circuit will fire any rating up to 25 amps. A quadrac (triac with internal diac) can be used if D5 is omitted.

This circuit also has other applications. Since the unit is basically a voltage controlled dimmer, it could be operated from a great variety of sources. If the two touch plates and C1 are omitted, pin 3 of the i.c. can be connected to a voltage source so that an input varying between 0V and +15V can control the load over its full range of brightness.

N. Valentine,
Forfar,
Angus.

15Hz FLASHER

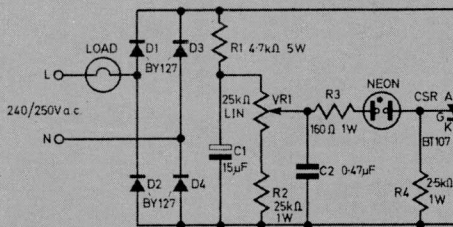


Fig. 1

THIS circuit (Fig. 1) consists of a bridge rectifier and a neon oscillator firing a thyristor. The flash rate is adjusted by means of VR1, which should have an insulated spindle since all components are at mains potential. Changing R2 will alter the range of frequency available by VR1.

The resistors used should be one watt types, except for R1 which runs quite hot and should be rated at five watts. The capacitors should be 350 volt working. The unit has been used to drive a 100 watt reflector spotlight in a disco strobe application, and has proved to be quite satisfactory.

D. White,
Paisley,
Renfrewshire.

PIP TONE GENERATOR

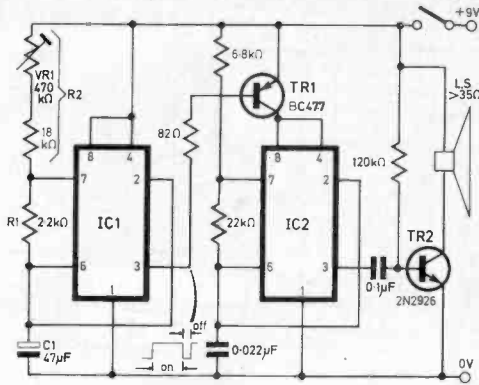


Fig. 1

THIS circuit provides a "pip" (BBC News type) at regular intervals in the range 3 to 20 seconds, the delay being adjusted by means of VR1. Two 555 integrated circuit timers are

used, both in the astable mode. The first, IC1, produces a squarewave voltage at pin 3 which is adjusted to have a short zero-voltage pulse length (about one second—the length of the

"pip"), and a long positive-voltage pulse length equal to the delay between pips. For the 555 operating as an astable, it is not possible to have the "on" time at pin 3 (given by $0.7(R1+R2)C1$) shorter than the "off" time, given by $0.7R1C1$.

Timer IC2 is wired as an astable operating at a frequency of about 1.2kHz, and is driven by the "off" pulse at pin 3 of IC1. This off pulse pulls down the voltage at the base of the *pnp* transistor TR1, thereby switching it on and allowing current to pass into the positive supply pin of IC2. During the delay period, controlled by VR1, the base of TR1 is at too high a voltage for it to conduct.

In order to obtain adequate output amplitude, a single transistor audio amplifier based on TR2 is used, driving a miniature loudspeaker. Capacitor C1 should be a tantalum type for reliable long period delays between successive pips. Even longer delays may be obtained by increasing VR1 to 1 megohm, and C1 may be increased to, say 100µF or more.

M. Plant,
Nottingham.

SELF-STOPPING COUNTER

A 9310 decade counter can be arranged to stop at its terminal count simply by connecting the TC (Carry) output to the CEP (Enable P) input via an inverter, see Fig. 1. It should NOT, however, be connected to the CET input since TC is a function of CET: such a connection causes oscillation.

N. V. Smith,
Shenfield,
Essex.

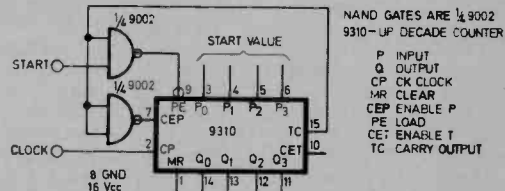


Fig. 1

COUNTER WITH BUILT-IN BOUNCE ELIMINATOR

THE first stage of a 9305 variable modulo counter can be used as a debouncing latch. It is a master/slave flip-flop, but when the clock input CP₀ is low, the master is isolated from the slave and Q₀ and Q̄₀ can be used as latch outputs.

This circuit will accept bouncing contacts and counts modulo 5, 6, 7 or 8 depending on the S₀ and S₁ connections to the Q₁, Q₂ and Q₃ outputs. The steady state contact current is negligible (less than 2mA), a momentary current of about 50mA is drawn for less than 20ns.

N. V. Smith,
Shenfield,
Essex.


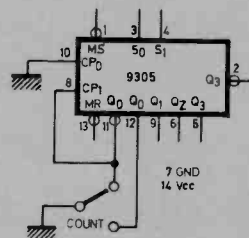


Fig. 1

CALCULATOR DISPLAYS

1" digit height, bright red LED 7 segment displays for calculators, digital watches, miniature clocks, DVMs, timers etc.
 * Fairchild FND-10, single digit common cathode £1.00 (+vat 8p) 6 for £5.00 (+vat 40p)
 * HP 7414 4 digit, common cathode 12 pin d.i.l. pin out 99p (+vat 8p) 6 for £5.00 (+vat 40p)
 * Bowmar 8 $\frac{1}{2}$ digit, common cathode with pc connector, and red bezel £1.85 (+vat 15p) 6 for £10 (+vat 80p)
 * Texas 3 digit common cathode 12 pin d.i.l. pin out 85p (+vat 7p) 6 for £4.00 (+vat 32p)
 * Texas 4+5 digit, common cathode 2x14 pin d.i.l. £1.85 pair (+vat 15p)
 * 30 pin termination board for all types except FND-10 20p (+vat 2p)
 * Texas calculator keyboards, 19 gold plated 'snap' type key contacts on gold plated pcb. 75p (+vat 6p) p & p on all the above 25p.

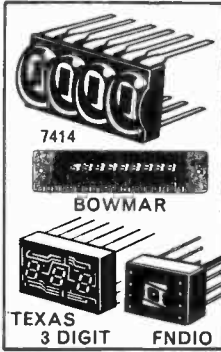


TAPE HEADS

BX12E343 TRACK ERASE HEAD - £1.25 (+vat 15p)
 BX12RP63 WITH BX12E343 - £2.95 (+vat 36p)
 STEREO CASSETTE R/R/P HEAD (200 ohm) - £2.25 (+vat 28p)
 TWIN STAGGERED MARRIOTT HEADS R/R/P1 - £1.50 (+vat 18p)
 MARRIOTT RECORD/REPLAY & ERASE HEAD - £1.75 (+vat 21p)
 MINIFLUX R9N ERASE - £2.25 (+vat 28p)
 GX11 E388 ERASE 675 ohms 2mA - £0.88 (+vat 11p)
 GX12 E387 ERASE 675 ohms 2mA - £0.88 (+vat 11p)
 GX20 E362 ERASE 90 ohms 90 mA - £0.95 (+vat 11p)
 R/R/P13 TAPE HEAD TRACK - £0.85 (+vat 8p)

MULLARD TUNER MODULES

LP1171 combined AM/FM IF strip - £4.29 (+vat 53p) * LP1179 FM front end with AM tuning gang, used with LP1171 - £4.29 (+vat 53p) * LP1171 & 79 pair - £8.00 (+vat 110p) * LP1157 complete AM strip - £2.05 (+vat 26p) * Ferrite Aerial - 95p (+vat 7p)
 p & p all modules 25p each
 HR-RP TAPE HEAD SINGLE TRACK £0.55 (+vat 6p)
 XRPS1 TRACK - £3.25 (+vat 40p)
 XRPS18 TRACK RED - £3.25 (+vat 40p)
 XRPS36 TRACK - £0.75 (+vat 7p)
 XES11 TRACK ERASE - £1.25 (+vat 15p)
 BX/RP63 TRACK - £2.25 (+vat 28p)

HENELEC RADIO CONTROL SYSTEM

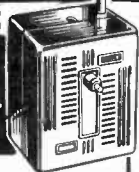

Specially designed to provide aircraft and boat model makers with a low-cost, easy-to-use radio control. The Henelec system gives you everything from single channel, up to sophisticated 7-channel Digital Proportional System! Buy the components you want. Ideal for any radio control application.
 * Simple transmitter - £2.95

* INCLUDING PROPORTIONALLY CONTROLLED SWITCH
 * FEATURING COSMOS DIGITAL LOGIC to minimise power consumption and extend battery life.
 (+vat 37p) * Single-ch. add-on for receiver - £11.78 (+vat £1.47p)
 * PC board for above - 75p (+vat 8p) * Case for transmitter - £1.25 (+vat 16p) * Basic receiver - £8.95 (+vat 87p) Send now for leaflet No. 8 (35p) for full details. Post etc. 50p each.

HENRY'S GREAT NEW CATALOGUE

For this latest edition, we have made hundreds of changes and additions. Containing virtually everything for amateurs and professionals, Henry's Radio Catalogue is also a "must" for manufacturers.
 Again, we have included a complete alphabetical index, as well as a sectional index, so that you'll have no trouble at all in finding what you need.

IT'S THE BEST EVER!



- ★ OVER 5,000 ITEMS
- ★ OVER 200 PAGES
- ★ DISCOUNT VOUCHERS
- ★ QUANTITY DISCOUNTS ON MOST ITEMS


ONLY 85p PLUS 14p p&p

FREE - to educational establishments and manufacturers when ordered on official headed notepaper.

BULK PURCHASE - EXCLUSIVE TO HENRY'S
ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!

QUALITY ITEMS
 Compare performance and specification with units costing 3 times as much!

DIGITAL CLOCK

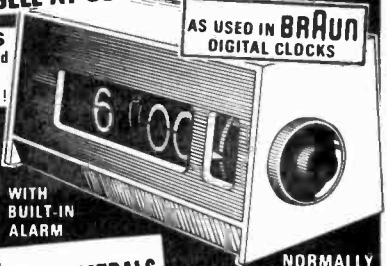


WITH BUILT-IN ALARM

AS USED IN BRAUN DIGITAL CLOCKS

NORMALLY £24 WITH CASE

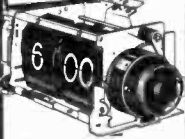- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS ● SIZE 6 $\frac{3}{8}$ x 2 $\frac{3}{8}$ x 2 $\frac{3}{8}$



MECHANISM ONLY

£6.00 +VAT 48p P&P 25p



MECHANISM AND CASE

£7.99 +VAT 64p P&P 25p



COMPLETE UNIT

£8.99 +VAT 72p P&P 25p

THREE FOR £16.50 +VAT £1.32 POST FREE

THREE FOR £22.00 +VAT £1.76 POST FREE

THREE FOR £25.00 +VAT £2.00 POST FREE

TEXAN AMPLIFIER
 featured by PRACTICAL WIRELESS
 still the best selling amp in the UK.

Build it yourself
£29.95 +VAT £3.74 P&P £1 Built £39.95 +VAT £4.93

Build the Texan stereo amplifier, and be doubly proud! You'll own a superb home entertainment unit. And the pleasure of doing it yourself.
 Look at the Texan specification:
 Fully integrated stereo preamp and power amp, 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fibre pcb; Gardners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 $\frac{1}{2}$ " x 6" x 2" overall. 20 watts per channel RMS.

The natural follow on!



TEXAN FM TUNER KIT £20.95 +VAT £2.62
 Built and tested £25.95 +VAT £3.24

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

NEW HENELEC Mullard AM/FM TUNER MODULE £21.95 +VAT £2.74 O&P £1.00



MAY BE ASSEMBLED IN AN EVENING. FEATURES * Built-in AM Ferrite aerial * LW coverage 150KHz-250KHz * MW coverage 530KHz-1.6MHz * FM coverage 87-104MHz * 75 Ohm aerial for FM * 150mV output * Size 8 $\frac{1}{2}$ "(L) x 6 $\frac{1}{2}$ "(W) x 2 $\frac{1}{2}$ "(H)

This new AM/FM tuner kit incorporates 2 Mullard modules. Supplied as a pre-aligned and tested printed circuit, the constructor only has to build the PCB into the chassis, connect the power, aerial and output loads. Styled to match the Texan amp, mains operated. Price £8.75 +VAT £1.02 p&p 50p.

We will be pleased to quote for parts for circuits in this magazine. Send your list for quotation in S.A.E. Ask for FREE leaflets and lists on our kits projects.

Henry's RADIO All mail to: Henry's Radio 303 Edgware Rd. London W2

LONDON W2: 404/6 Edgware Road. Tel: 01-402 8381
 LONDON W1: 231 Tottenham Ct Rd. (lower sales floor) Tel: 01-636 6681

Sparkrite mk2

Capacitive discharge
electronic ignition kit

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service — phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept. PE11,
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

Mk. 2 DIY Ass. Kit @ £11.80	I enclose cheque/PO's for £ Cheque No. Send SAE if brochure only required.
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.3D	
R.P.M. Limit systems in above units @ £2.42	

PE ORION STEREO TUNER

Complete set of semiconductors £4.99
Mullard LP186 tuner head £6.88
High quality glass fibre P.C.B. £2.45

STEREO AMPLIFIER

Complete set of semiconductors £9.40
High quality glass fibre P.C.B. £2.75

FERRANTI semiconductors

BC107P	11p	ZTX108	9p	ZTX330	17p	ZTX530	18p	ZS176	33p
BC108P	9p	ZTX109	11p	ZTX331	18p	ZTX531	19p	ZS178	54p
BC109P	11p	ZTX212	15p	ZTX382	16p	ZTX550	16p	ZS270*	14p
BC415P	17p	ZTX213	15p	ZTX383	15p	ZTX551	17p	ZS271*	23p
BFS59	14p	ZTX214	17p	ZTX384	17p	ZN3055*	70p	ZS272*	24p
BFS60	15p	ZTX239	10p	ZTX450	16p			ZS274*	29p
BFS61	15p	ZTX300	12p	ZTX451	16p	DIODES		ZS276*	36p
BFS96	14p	ZTX301	13p	ZTX500	13p	ZS142*	38p	ZS278*	57p
BFS97	15p	ZTX302	15p	ZTX501	14p	ZS170	13p		
BFS98	16p	ZTX303	18p	ZTX502	16p	ZS171	16p	ZENERS	
ZTXA20	10p	ZTX304	19p	ZTX503	17p	ZS172	23p	BZV19 series	
ZTX107	11p	ZTX320	16p	ZTX504	20p	ZS174	25p	4.7 to 47V	10p

FERRANTI CDI INTEGRATED CIRCUITS. All with circuits and data.
ZN414 radio microphone i.c. £1.00
ZN425E* D to A converter £3.50, High quality glass fibre p.c.b. £1.00
ZN1034E* precision timer i.c. £1.80
ZN1040E* universal Count/display i.c. £7.50

PE TV SOUND SEPARATOR

Complete kit of semiconductors £2.30 High quality glass fibre p.c.b. £1.00
Murata ceramic filters — SFE6.0MA 35p, CDA6.0MG 35p each.

PHASE LOCKED STEREO DECODER

To Motorola specification. COMPLETE KIT ONLY £3.50, including MC1310P, glass fibre p.c.b., all resistors & capacitors. LED indicator and full instructions.

MOTOROLA: MC1357PQ £1.65, MC1310P £1.80, BD699* £1.14, BD700* £1.28,
MJ4032* £5.17, MJ4035* £4.95.

PE OPTO REV COUNTER. MS4A photocells £1.35

PE JOANNA. 77 ZTX108 for £5.00, 163 ZS170 diodes for £15.00.

POSTAGE AND PACKING: 15p per order. Orders over £5.00 post free. All devices top grade, brand new and to full manufacturers spec. We do not sell seconds or rejects. Send SAE for our data sheet and price list. We can supply any Ferranti semiconductor device to order.

PRICES DO NOT INCLUDE VAT — ADD 8% TO ITEMS MARKED * AND 12½% TO ALL OTHERS.

DAVIAN ELECTRONICS

PO BOX 38 OLDHAM LANCs. OL2 6XJ

CMOS WITH DISCOUNTS!

Any mix: Discount 10% for 25+, 25% for 100+, 33½% for 1,000 —



**C US
4 CMOS!**

4000	1-20	4037	1-00	4075	0-24	14175	1-04	14528	1-22	'E' LED DISPLAYS	
4001	0-20	4038	1-20	4076	1-71	14184	1-17	14529	1-72	DL-704E 0-3"	79p
4002	0-20	4039	3-90	4077	0-85	14410	0-70	14530	0-95	DL-707E 0-3"	79p
4008	1-31	4040	0-18	4078	0-26	14411	0-54	14531	1-74	DL-728E 2 x 0-5"	£1-00
4009	1-29	4041	0-93	4081	0-24	14412	17-87	14532	1-30	DL-727E 2 x 0-5"	£1-00
4008	1-87	4042	0-93	4082	0-24	14415	7-35	14534	0-15	DL-750E 0-6"	£1-00
4009	0-80	4043	1-12	4085	0-00	14419	2-87	14536	4-00	DL-747E 0-6"	£1-00
4010	0-80	4044	0-84	4086	0-00	14422	4-00	14537	19-17		
4011	0-20	4045	1-58	4089	1-74	14435	7-93	14539	1-24	RED LEDS	
4012	0-20	4046	1-40	4093	0-00	14440	11-58	14541	1-82	0-1"	15p
4013	0-00	4047	1-91	4094	2-00	14450	2-87	14543	1-82	0-2"	15p
4014	1-12	4048	0-80	4095	1-18	14451	2-87	14549	4-18		
4015	1-12	4049	0-80	4096	1-18	14480	0-91	14552	1-00	CLOCK CHIPÉ	
4016	0-00	4050	0-00	4097	4-13	14501	0-20	14553	4-00	AY-5-1224A	£3-00
4017	1-12	4051	1-04	4098	1-22	14502	1-38	14554	1-87	MK 50253	£5-50
4018	1-12	4052	1-04	4099	2-02	14503	0-70	14555	1-01		
4019	0-00	4053	1-04	4101	1-78	14505	4-38	14556	1-91	SOLDERCON PINS	
4020	1-24	4054	1-29	4102	2-16	14506	0-87	14557	4-85	1000	80p
4021	1-12	4055	1-46	4103	2-16	14507	0-00	14558	1-25	1000	£4-00
4022	1-87	4056	4-00	4104	2-28	14508	3-00	14559	4-18	2500	£8-78
4023	0-20	4057	2-18	4107	0-85	14510	1-51	14560	1-10		
4024	0-67	4059	0-20	4108	0-18	14511	1-74	14561	0-78	DIL SOCKETS 14/16 PIN 15p	
4025	0-20	4060	1-24	4109	2-21	14512	1-03	14562	5-50		
4026	1-82	4061	25-00	4111	4-38	14514	3-47	14566	1-87	RED ACRYLIC FILTER	
4027	0-80	4062	10-18	4112	1-72	14515	3-47	14568	3-18	For L.E.D. displays	
4028	1-00	4063	1-22	4114	2-20	14516	1-81	14569	3-72	157 x 92 x 3mm	79p
4029	1-27	4066	0-00	40257	2-20	14517	4-82	14572	0-27	PUSH SWITCHES	
4030	0-00	4067	4-13	4700	1-79	14518	1-20	14580	0-36	Type SW9	15p
4031	2-48	4068	0-24	7083	4-25	14519	0-87	14581	1-10		
4032	1-18	4069	0-24	14180	1-18	14520	1-30	14582	1-84		
4033	1-88	4070	0-85	14181	1-18	14521	2-77	14583	0-84	OP-AMPS	
4034	2-11	4071	0-24	14182	1-18	14522	2-18	14585	1-18	CA 3130 (COS.MOS)	£1-00
4035	1-91	4072	0-24	14183	1-18	14526	2-18	14586	2-18	CA 314 (S1MOS)	85p
4036	3-08	4073	0-24	14174	1-00	14527	1-78			741 Minidip	25p

Terms: C.W.O. Add VAT to all prices at 8%. Post, etc. U.K. 25p (+ 2p = 27p) per order. All orders processed same day. Official Govt. Varsity, Poly., etc. orders (written or telephoned) welcome.

GREENBANK ELECTRONICS (Dept. E11P)

94 New Chester Road, New Ferry, Wirral, Merseyside, L62 5AG, England.
Tel: 051-645 3391

PATCH PANEL

Fig. 1


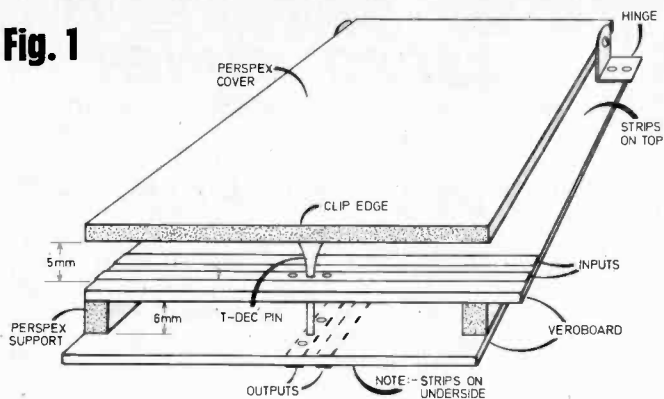


Fig. 2

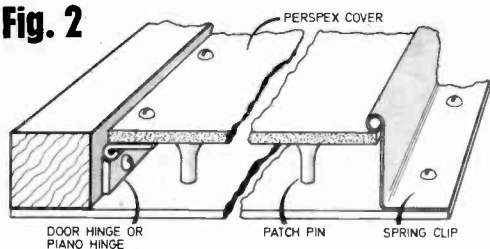

This is an idea for a simple, cheap and reliable patch panel for use with synthesisers etc. The copper strips of a "stiff quality" 0.1 or 0.15in pitch Veroboard are coated along their length liberally with solder so as to cover all the holes but not to short adjacent strips. On to the upper surface of this board two parallel perspex supports (6mm thick) are stuck with impact adhesive. The 6mm allows for 1mm Veroboard thickness. A second board is placed with strips at right angles to the first and with an overhanging edge across the supports as shown in Fig. 1. The

holes are carefully aligned using "T-Dec" pins and the top board is stuck to the supports (clamps are recommended).

The patch pins are simply "T-Dec" pins which have a shoulder to butt against the top Vero strips. To hold the strips in position a piece of Perspex is used which is hinged at one end to allow easy access to the pins. The hinge can be either a "piano-hinge" or end brackets with a bolt into either edge acting as a hinge (see Figs. 2 and 3). The other edge of the perspex is held down by a spring clip made of beryllium copper or spring

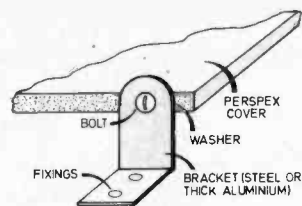


Fig. 3

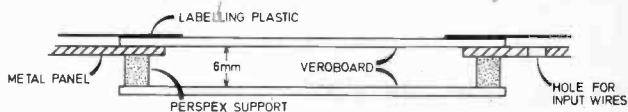


Fig. 4

steel, and bent round a rod at the top and into a suitable right angle at the bottom (Fig. 2).

The unit was originally sunk into wood but it could be fitted to a metal panel (Fig. 4).

To finish the patch panel a suitable square hole is cut into a piece of a thin p.v.c. plastic or card and labelled with Letraset along the "X" and "Y" axes. Also to aid in line recognition the space between every fifth copper strip can be inked.

R. A. Curtis,
Worthing.

PHASE COMPARATOR

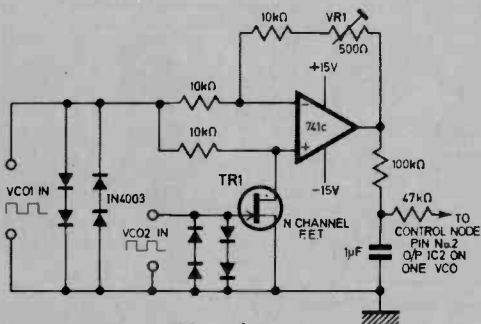


Fig. 1

This circuit (Fig. 1) was constructed for use with the *P.E. Sound Synthesiser* (February, 1973—February, 1974), and provides an easy method of phase-locking the v.c.o.s in the keyboard. The circuit consists of a phase comparator followed by a low-pass filter.

The potentiometer VR1 is adjusted to cancel out the effect of the r_{ds} of TR1 when it is on. Any general purpose *n*-channel f.e.t. should be suitable. The diodes on the inputs limit the amplitude of the input signals to about 1.4V peak to peak.

P. Gopakumar,
Cochin,
India.

SIGNAL INJECTOR/TRACER

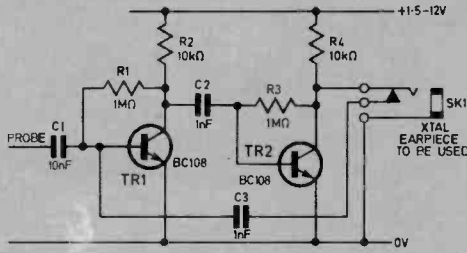


Fig. 1

THE circuit shown in Fig. 1 makes an excellent signal injector with harmonics going well above 5MHz, and also a crude but effective signal tracer.

Without the earpiece connected, the circuit acts as an astable multivibrator, feedback being provided via C3. When the earpiece is plugged in, C3 is disconnected and the unit becomes a simple two-stage audio amplifier.

The prototype unit was built into a small plastic box with four Mallory batteries, current consumption being less than 0.5mA.


P. Dow,
Sunderland.

TRAFFIC LIGHT CONTROLS

THIS simple circuit controls a set of traffic lights for a cross roads and can perhaps also be used as a party lights display.

If the sequence for a set of traffic lights is drawn out as shown in

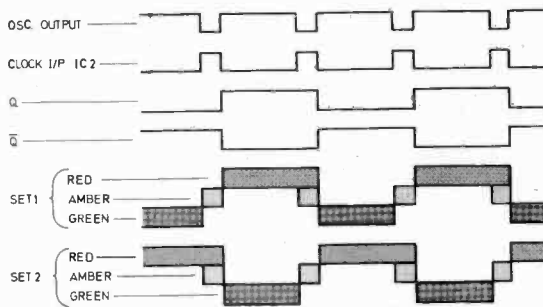- Fig. 1, three facts become apparent:
- Both sets of amber are always on together.
 - One set of red or other is always on.
 - When one red is on, the other green is on, except when the amber lights are on.



The circuit to achieve this is shown also in Fig. 1. IC1 is the ubiquitous 555 connected as an oscillator with 1 second in its low state and 5 seconds in its high state.

The output of IC1 drives the amber lights direct (max. load 200mA) turning them on when it goes low. The output of IC1 also feeds IC2, a single binary counter. The Q and Q outputs drive the two reds via the transistors TR2 and TR3.

The positive supply for the green lights is provided by IC1 (i.e. it is removed when the waveform goes low and the ambers are on). The negative return for the green is connected to the red on the other set giving the correct sequence.

Diodes D1 and D2 prevent the sneak paths that would occur between red and green when IC1 output goes low. D3 provides the 5V supply for IC2 and TR1.

E. A. Parr,
Carlisle.

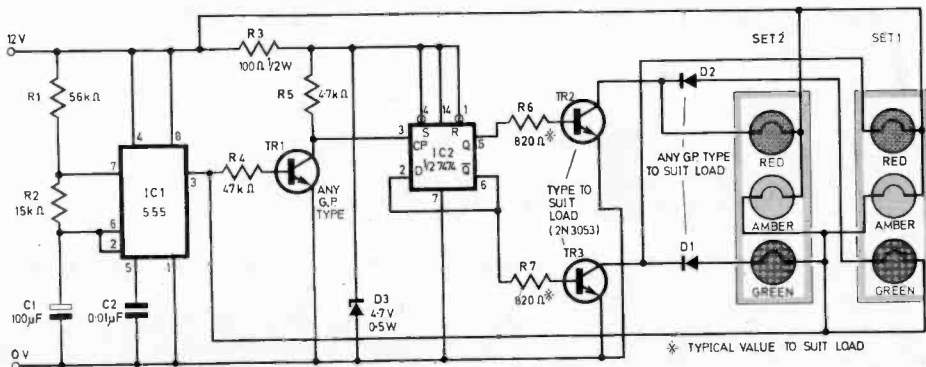


Fig. 1

20x20 Watt STEREO AMPLIFIER

Superb Viscount IV unit in teak-finished cabinet. Black fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20+20 watts rms, 40+40 watts peak.



£2990
+ p & p £210

HOW YOU CAN SAVE

SYSTEM 1B

For only £80, you get the 20+20 watt Viscount IV amplifier; a pair of our 12-watt-rms Duo Type IIb matched speakers; a BSR MP 60 type deck complete with magnetic cartridge, de luxe plinth and cover.

£8000
+ p & p £6.50

SYSTEM 2

Comprising our 20+20 watt Viscount IV amplifier; a pair of our large Duo Type III matching speakers which handle 20 watts rms each; and a BSR MP 60 type deck with magnetic cartridge, de luxe plinth and cover.

£9200
+ p & p £7.60


Carriage surcharge to Scotland: System 1b £2.50, System 2 £5

SPEAKERS Two models—Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/4" approx.

£34 + p & p £6.50
PER PAIR

Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2"

£48 + p & p £7.50
PER PAIR

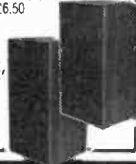

TURNTABLE Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover.

£2400
+ p & p £3.50

VALUE



DIY 30x30 AMPLIFIER KIT

Specially designed by RT-VC for the experience constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched, drilled and formed. Cabinet is finished in teak veneer. Black fascia and easy-to-handle aluminium knobs. Output 30+30 watts rms, 60+60 peak.

£2900
+ p & p £210

STEREO CASSETTE DECK KIT

Again, this kit is specially designed for the experienced constructor — for mounting into his own cabinet. Features include solenoid-assisted AUTO-STOP, 3-digit counter, record/replay PC board, mains transformer and input and output controls. AC BIAS AND ERASE

£3250
+ p & p £150

DELUXE ACCESSORY KIT

Comprises of a matched pair of dynamic mics and two replacement slider level controls.

£3.95 + p & p £1
P. & P. FREE WHEN PURCHASED TOGETHER WITH ITEM BELOW.

DIY STEREO SYSTEM

COMPLETE WITH SPEAKERS
Here's real value in DIY! Comprises ready-built amplifier module, 3-speed Garrard auto-return deck, and teak-veneered simulate cabinets with clear plastic top. Easily built by hobbyists.

£2695
+ p & p £4.05

TURNTABLES BY BSR

Big value from RT-VC! Two units COMPLETE WITH PLINTHS. First, the popular MP 60 type semi-professional deck. Second, the lower-cost C141 automatic unit, fitted with a stereo ceramic cartridge.

£1750 + p & p £2.50
£1195 + p & p £2.55

Both units have plinths finished in superb teak veneer. Either way, you're on to a bargain from RT-VC

STEREO AMPLIFIER KIT

Build up a 4-watts rms per channel stereo amplifier with Unisound MK2 modules. For only £9.95 you get pre-amp, power amp, and all the control panel parts. Features include IC power chips for low distortion. For the experienced constructor only.

£995
+ p & p £1.55

35-WATT DISCO AMP

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges; tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

£2750 - p & p £1.50

PORTABLE DISCO CONSOLE with built-in pre-amplifiers

Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single-play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier.

£5500
+ p & p £6.50

70 and 100 WATT DISCO AMPLIFIERS

Brilliantly styled for easy disco performance! Sliding fascia so that you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth acting, vertically mounted slide controls — master volume, tape level, mic level, track level.

PLUS INTER DECK FAULT for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. 70 watts rms, 140 watts peak output.

£4900 + p & p £3.00

All the big features as on the 70-watt disco amplifier, but with a massive 100 watts rms, 200 watts peak output power.

£6500 p & p £4.00

EASY-TO-BUILD, WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two 3 1/4" (approx.) tweeters and a pair of matching crossovers. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms, 30 watts peak, each unit. Cabinet size 20" x 11" x 9 1/2" (approx.).

£2550 + p & p £5.50
PER PAIR

DIY SPEAKER KITS

'COMPACT' FOR TOP VALUE
How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 — just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready milled and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is finished in simulated teak. Complete with two 8" (approx.) speakers for max. power handling of 7 watts.

£750
p & p £1.70 per pair

15-WATT KIT IN CHASSIS FORM

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the above enclosures. Size 13" x 8" (approx.) EMI woofer, 3 1/4" (approx.) tweeter, and matching crossover. Power handling capacity 15 watts rms, 30 watts peak.

£750 + p & p PER SET

YOU CAN'T DO BETTER

20-WATT HI-FI KIT IN CHASSIS FORM

For extra power, choose this super RT-VC kit! EMI 13" x 8" (approx.) triple-laminated-coned woofer with massive 5" (approx.) magnet, plus 5" (approx.) mid-range unit with concentric 2" parasitic tweeter and 2 1/4" (approx.) magnet. Complete with circuit diagram and crossover components.

£1050 + p & p £2 PER SET

ELECTROLYTIC CAPACITORS AT BARGAIN PRICES

all brand new from reputable international manufacturers.

PACK 1—Containing 30 mixed Electrolytics, values from 4.7mF to 47mF. Minimum 16 volt working. 35p + 20p p & p.

PACK 2—Containing 17 mixed Electrolytic values from 100mF to 2200mF. Minimum 16 volt working. Majority 40 volt working. 75p + 20p p & p.

ALL PRICES INC. VAT AT CURRENT RATES

GOODS NOT DESPATCHED OUTSIDE UK
All items subject to availability
Price correct at 1st September 1976 and subject to change without notice

For further information, please send stamped addressed envelope


RTVC

212 HIGH STREET, ACTON, LONDON W3 8NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE ROAD 9 a.m.—5.30 p.m.
Half day Thurs
ACTON 9.30a.m.—5p.m. Closed all day Wed.

Minimum order on Access and Barclaycards £15

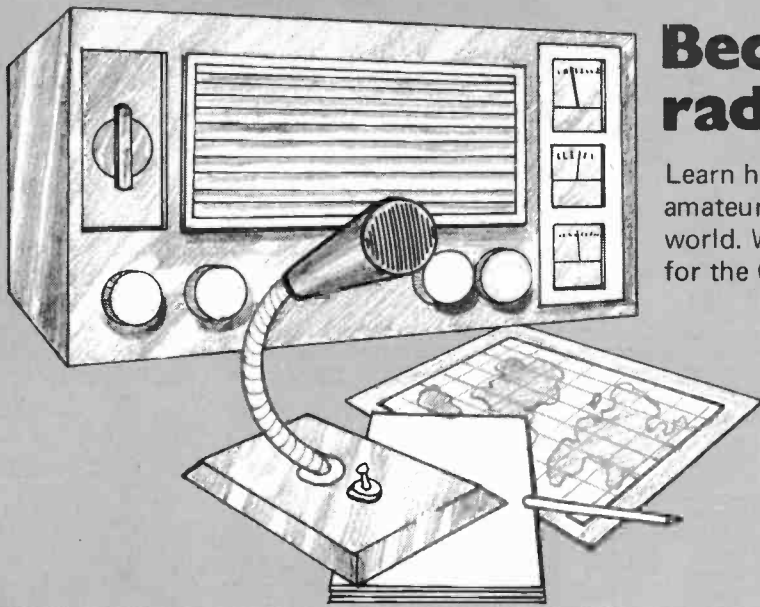DO NOT SEND CARD
Just write your order giving your credit card number



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. PEE 11/6
 P.O. Box 156, Jersey, Channel Islands.

NAME _____
 ADDRESS _____ Block caps please

JOIN THE TREASURE HUNTERS

NEW! MONEY SAVING BFO METAL DETECTOR KIT!

Enjoy the world's most exciting hobby with this high quality metal detector. Search for old silver, coins, jewellery, antiques and many more valuable articles. Simple to make, the detector embodies the latest circuitry and design features and its performance is comparable to detectors costing twice as much. Circuit incorporates varicap tuning, Loud-speaker, Faraday Screen gives excellent sensitivity and stability.

Complete kit includes all parts, components, printed CCT Board, aluminium frame, incorporating search head, all hardware and full instructions.

Circuit diagram and instructions available separately, price £1—refunded with kit.

COMPLETE KIT £11-95 85p p+p	BUILT & TESTED £15-75 85p p+p
--	--

ACCESS & BARCLAYCARD ORDERS ACCEPTED

SILHILL PRODUCTS (Dept. PE1)
 (226 Mary Street, Birmingham B12 9RJ. Tel. 021-440 3600)

Suppliers to the trade of:

- * **KEYBOARDS** (Agents for 4 ranges)
- * **CONTACT SYSTEMS**
- * **STOPS, DRAWBARS**
- * **VOLUME PEDALS**
- * **PEDAL BOARDS**
- * **REVERBS, etc.**

Harmonics* OAKLEY GRANGE
 KIRDFOUR, SUSSEX
 RH14 0JY
 (Bromley) Ltd. Tel: (040 377) 455

OVER 2,000 ELECTRONIC COMPONENTS IN A

BIG NEW FREE

100 PAGE CATALOGUE

YOURS BY POSTING TODAY

Please send me the 100 page Tandy catalogue

Name _____

Address _____

TANDY PE/3
 Nationwide supermarket of sound!

Tandy Corporation (Branch UK), Bilston Road, Wednesbury, W. Midlands WS10 7JN

40 PAGES IN COLOUR

PLEASE CONTACT SILHILL

READY WIRED LEADS SOCKETS & PLUGS

TURN 48 hr ROUND

The answer to your connecting problems. Now you can connect that new tape recorder to your present amplifier! Any plug to any plug or any plug to its matching socket all with 5ft leads. In the case of Speaker leads we offer you a choice of either 16ft or 33ft—please state preference.


ANY CONNECTION
ONLY £1.25 incl. VAT

POST FREE

Adaptor leads 9in long for correcting non-matching plugs and sockets
£1 incl. VAT POST FREE

No.		PLUGS
8/4P		3 DIN Plug
8/8P		5 DIN Stereo Plug
8/7P		4 Phono Plugs
9/6P		1/2 In Stereo Jack
9/0P		Wander Plugs 1/2 In
9/1P		2 Banana Plugs 4mm
9/3P		2.5mm Jack
9/4P		3.5mm Jack
9/5P		1/2 In Standard Jack
9/6P		2 Round and 1 Flat Pin Plug
9/7P		Loudspeaker Plug
9/20P		Coaxial Plug
10/1P		Phono Plug
10/9P		2 Phono Plugs
11/4P		7 pin DIN Stereo Plug
12/6P		Loudspeaker Plugs
12/9P		Loudspeaker Plugs
		SOCKETS
13/4S		Loudspeaker Socket
13/7S		Twin Phono Socket
13/9S		1/2 In Standard Socket
13/0S		1/2 In Stereo Socket
15/2S		3.5mm Jack Socket.
15/0S		Phone Socket
16/8S		5 pin Din Stereo Socket
16/4S		3 pin DIN Stereo Socket

TELEPHONE PICK-UP LEADS

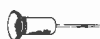

Phone Sucker to either 3 DIN, 1/2 Jack, 3.5 Jack Phono or Philips EL3581/3582/84 or other Philips models.
Please state which one

ONLY £1.99 incl. VAT

ALL LEADS WILL BE WIRED UP IN THE STANDARD WAY UNLESS OTHERWISE STATED

barclay **ELECTRONICS**

1115 Finchley Road, Temple Fortune, London NW11.
Tel. 01-458 4755

SOUND DESIGN

A PRACTICAL ELECTRONICS PUBLICATION

A SPECIAL SELECTION OF MUSICAL PROJECTS FROM PE

THE MINISONIC MK2 SOUND SYNTHESISER

An up-dated version of the published Mk 1, the Mk 2 has an integral keyboard, two 250 mW monitoring channels and loudspeakers, and facilities for amplitude, frequency and harmonic modulation.

THE JOANNA ELECTRONIC PIANO

has realistic piano effect with touch-sensitive keyboard and additional choice of harpsichord or honky-tonk voicing.

THE ORION STEREO AMPLIFIER

A hi-fi amplifier with output of over 20 + 20 watts. Compact and complete in one unit, it measures only 14" x 6" x 2".

PLUS

Some great sound effects units for guitars, keyboard instruments and general recording.

Available
Now

£1.20

POST PAID

(Please allow at least 2 weeks for delivery)

If you do not wish to mutilate your copy of the magazine, please send your order on a separate sheet.

To: Practical Electronics
IPC Magazines Ltd., Receiving Cashiers Dept.,
King's Reach Tower, Stamford Street, London SE1 9LS

Please send me copy(ies) of "Sound Design". I enclose a Postal Order/Cheque for £1.20 (post paid) or (state amount for more than one copy) (£2.35 post paid for 2 copies)

PLEASE WRITE IN BLOCK LETTERS

Name

Address

..... Post code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only.
PE 810

Company registered in England. Regd. No. 53626.
A subsidiary of Reed International Limited.

V.A.T.

THE NEW AND REVISED VAT LEAFLET No. VLA/8/76 ISSUED BY CUSTOMS AND EXCISE

VAT and Components

To help unravel some of the confusion still existing regarding VAT, a new and revised VAT leaflet, No. VLA/8/76, covering electrical and electronic components has been issued by H.M. Customs and Excise. This leaflet gives recent alterations of rate and changes of interpretation as they affect components.

For those Advertisers and readers who do not receive a copy we give below the full text of the VAT leaflet No. VLA/8/76. Any Traders interested in obtaining their own copy should note that the leaflet is available from their local VAT Office.

HIGHER RATE OF VAT: ELECTRICAL AND ELECTRONIC COMPONENTS

1—Introduction The following guidelines, which have been agreed with representatives of the component manufacturing industry are to be used to determine the liability to VAT of various product categories of electronic components. It should be noted that, in certain cases, these guidelines have been revised with effect from 1 July 1976; this leaflet incorporates all such changes.

2—Determination of liability The product categories of electronic components which are chargeable at the higher rate of VAT under the provisions of Schedule 7 of the Finance (No. 2) Act 1975 are listed in paragraph 4 below. Where the higher rate is not specified as applying, the standard rate is normally chargeable. However, while the list in paragraph 4 is intended to be as complete as possible, it cannot be exhaustive, particularly in view of the continuing technological developments in the industry. Any trader who is in doubt about the liability of a component not covered by the list, or who requires additional guidance, should therefore consult his local Customs and Excise VAT Office.

3—Components manufactured to a specification Special rules apply where parts and components are manufactured solely to the specification of a particular customer (or group of customers) for use in standard-rated or zero-rated goods and are not made available for use for any other purpose. In such cases the list in paragraph 4 need not be followed and such parts and components may be regarded as chargeable at the standard rate. This special treatment extends to those parts and components which both have a specification higher than the upper end of the standard components specification range and are sold at a higher price than standard components.

4—Product categories to be charged at the higher rate of VAT

- (A) Cathode ray tubes for television sets or radio receiver/monitors.
- (B) Tuners for radio and television sets, including tuners featuring touch button controls and/or remote control units for audio equipment and television sets, video tape recorders with a built-in tuner, and video receiver/monitors.
- (C) Delay lines and networks for television sets and audio equipment.
- (D) Transformers, chokes and coils for television and audio equipment, and domestic appliances.
- (E) All valves for higher-rated goods.
- (F) Voltage multipliers (triplers, etc.) for higher-rated goods.
- (G) Modules (assemblies and sub-assemblies) for higher-rated goods.
- (H) Printed circuit boards and micro circuits (including hybrid and passive) for higher-rated goods.
- (J) Digital and linear integrated circuits suitable for higher-rated goods.
- (K) Discrete semiconductors:
 - (1) Transistors, triacs and thyristors, plastic encapsulated and less than 3A rating.
 - (2) Power transistors for TV deflection applications.
 - (3) All plastic diodes and diacs of less than 1A rating, except light emitting diodes.
 - (4) All Zener diodes which have plastic encapsulation and a power rating of less than 3W.
 - (5) Rectifiers of a kind suitable for use in low voltage battery charger equipment having a current rating of less than 5A.

(L) Capacitors excluding:

- (1) Any capacitor supplied against a Government department approval, e.g., R.R.E., R.A.E., S.R.D.E., A.S.W.E., G.P.O.
- (2) Paper and plastic film capacitors of greater than 0.5 μ F and/or metal cased and/or rated above 500V d.c. and/or meeting I.E.C. Specification 68.2 or equivalent—21 days humidity rating.
- (3) Sintered tantalum capacitors of greater than 300 microcoulombs and/or metal cased.
- (4) Tantalum capacitors with liquid electrolyte.
- (5) Aluminium electrolyte capacitors meeting I.E.C. Specification 103, Type 1—85°C or equivalent specification or operating in excess of 110V a.c.
- (6) Mica (other than rivetted and bonded types) and Polystyrene capacitors.
- (7) Ceramic and porcelain capacitors of multilayer construction.
- (8) Vacuum and pressure gas capacitors.
- (9) Variable capacitors having a precious metal deposit on rotor or stator and/or rated at or above 2,000V d.c.

(M) Resistors.

- (1) Fixed resistors:
 - Carbon composition, up to and including 2W rating, excluding hot moulded types.
 - Carbon film, up to and including 2W rating.
 - Wirewound, excluding (i) vitreous and silicone protected types, (ii) precision types and (iii) types using heat sink methods of power dissipation.
 - Pluggable metal oxide.
 - Pluggable thick film.
- (2) Variable resistors:
 - Wirewound convergence controls.
 - Focus control for colour TV.
 - Potentiometers and presets using carbon composition elements, excluding hot moulded track type.
- (3) Other resistors:
 - Non-linear voltage or temperature dependent, except directly and indirectly heated bead thermistors.
 - Modules specifically designed for TV applications.

(N) Transducers suitable for higher-rated goods.

(O) Filters (electronic) suitable for higher-rated goods.

(P) Connectors excluding:

- (1) Edge connectors;
- (2) Connectors used solely with goods which are not subject to the higher rate;
- (3) Connectors for a wire size area exceeding 3.3mm²;
- (4) Connectors plated with a precious noble metal; and
- (5) Connectors with integral insulation.

(Q) Electromechanical components and assemblies (holders and sockets, control knobs, dials, relays, switches, heat-sinks) for higher-rated goods.

(R) Quartz crystals and quartz crystal filters for higher-rated goods.

(S) Insulators for higher-rated goods.

RELAYS

SIEMENS, PLESSEY, Etc.
MINIATURE RELAYS

Col. (1) Coil ohms	1	2	3	4
Col. (2)	52	4-8	2 c/o	85p*
Working	58	5-9	6 c/o	95p*
d.c. volts	185	8-12	6M	85p*
	230	9-18	2 c/o HD	95p*
	430	12-24	2 c/o HD	85p*
	430	15-24	4 c/o	95p*
	600	10-20	6M	95p*
Col. (3)	600	10-24	2 c/o	85p*
Contacts	600	14-24	4 c/o	95p*
	700	12-24	2 c/o	85p*
	700	16-24	4 c/o	95p*
Price	1,250	18-36	2 c/o	85p*
	2,500	31-43	2 c/o HD	85p*
	2,500	30-45	6M	85p*
	15k	85-110	6M	85p*

*Incl. Base. All prices incl. P. & P.

OPEN TYPE RELAYS


9 VOLT D.C. RELAY
3 c/o 5 amp contacts. 70 ohm coil. 85p. Post 15p.
12 VOLT D.C. RELAY
12 c/o 5 amp contacts. 120 ohm coil. 85p. Post 15p.
6 VOLT D.C. 1 make contacts 45p. Post 15p.
100 VOLT A.C. 2 c/o 75p. 3 c/o 85p. Post 15p.

ENCLOSED TYPE RELAYS

24 VOLT D.C. 3 c/o 85p. Post 20p. Base 15p extra.
24 VOLT A.C. Mfg. by I.T.T. 3 h.d. c/o contacts. 85p. Post 20p. Base 15p.
33 VOLT A.C. RELAY
3 h.d. c/o contacts. Price 65p. Post 20p. Base 15p.
230/240 VOLT A.C. RELAY. 3 h.d. c/o contacts. Price 85p.
Post 20p. Octal plug in base 15p extra.
230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d. 15 amp c/o contacts. Amp connectors. Price £11.10. Post 20p.
230/240 VOLT A.C. RELAY
3 c/o 5 amp contacts. Sealed. Mfg. ISKRA. £1.35. Post 20p. Base 15p extra.
CLARE-ELLIOTT TYPE RP7641 G8
Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 80p post paid.

UNISELECTOR SWITCHES

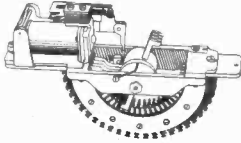4 bank, 25 way
75 ohm. Coil
36-48V d.c.
operation. Ex.
New equip-
ment £4.25, P.
& P. 75p. Total
price incl. VAT
£5.40.



MINIATURE C/O ROLLER

MICRO SWITCH

OMRON Type V15 FL22/IC. 10 for
£2. Post 50p. (Min. order 10).
Sub miniature Burgess Type V.4.T.1. 10 for £2.50.
50 for £10. Post paid.



MINIATURE UNISELECTOR

12 volt 11-way, 4 bank (3 non-bridging, 1 homing),
£2.50, p.p. 35p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb
pull 1 inch travel. Two x approx. 1lb pull x inch
travel. 6 x approx. 4oz. pull x inch travel. One
24 volt d.c. 1 heavy duty single make relay. Price
£3.00. Post £1. **ABSOLUTE BARGAIN.**

600 WATT DIMMER SWITCH
Easily fitted. Fully guaranteed by makers.
Will control up to 600W of lighting
except fluorescent at mains voltage.
Complete with simple instructions.
£3.15. Post 25p.
1,000 watt model, £4.50. Post 25p.
2,000 watt model, £9. Post 40p.

CENTRIFUGAL BLOWER

Mfg by Smiths Industries. 230/240V
a.c. Miniature Model. Series SE/200.
Size 95mm x 82mm x 82mm.
Aperture 38mm x 31mm. 12
c.f.m., £2.75. Post 50p.
Mfg. by Sracmo 115/230V a.c. 2800/3400 r.p.m. Fan
type aperture 3" x 2 1/2" VBL425/L. Mfg. Aircontrol
Installations Ltd. Price £12. Post £1.



INSULATION TESTERS

NEW!

Test to I.E.E. Spec. Rugged metal
construction, suitable for bench or
field work, constant speed clutch.
Size L.8in. W.4in. H.6in, weight 6lb.
500V, 500 megohms. £40. Post 80p.
1,000V, 1,000MΩ, £46. Post 80p.



BLOWER UNIT

200/240V a.c. precision German
built. Dynamically balanced, quiet,
con rated, reversible. Consumption
60mA. Size 120mm dia. x 60mm deep.
Price £3.50. Post 50p.



All Mail Orders—Callers—Ample Parking
Dept. PE11, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE

200 watt (1 amp) inc. AC voltmeter

£11.50

0.5 KVA (2 1/2 amp) (MAX) £11.50

1 KVA (5 amp) (MAX) £18.00

2 KVA (10 amp) (MAX) £30.00

3 KVA (15 amp) (MAX) £38.00

4 KVA (20 amp) (MAX) £60.00

CARRIAGE AND PACKING EXTRA



L.T. TRANSFORMERS

0, 10, 17, 18 Volt at 10 amp. £10.45. Post £1.00

0, 4, 6, 24, 32 Volt at 12 amp. £13.00. Post £1.00

0, 6, 12 Volt at 20 amp. £11.85. Post £1.00

0, 6, 12, 17, 18, 20 Volt at 20 amp. £14.15. Post £1.00

Other types to order at short notice—Phone your enquiries.

AUTO TRANSFORMERS

Step up, step down, 0-115/200/220/240 volts at 75
watt £3.60. Post 40p. 150 watt £5.15. Post 50p. 300
watt £7.45. Post 60p. 500 watt £11.00. Post 75p.
1000 watt £16.20. Post 90p.


STROBE! STROBE! STROBE!

HY-LIGHT STROBE MK IV

Build a Strobe Unit, using the latest type Xenon
white light flash tube. Solid state timing and
triggering circuit. 230/250V a.c. operation.
For use in large rooms, halls and utilises a silica
tube, printed circuit. Speed adjustable 0-20 f.p.s.
Light output greater than many (so called 4
Joule) strobes £15.40. Post 75p. Specially de-
signed case and reflector £8.25. P. & P. £1.
Super high light approx. 4 times more output.
S.A.E. for leaflet.

XENON FLASHGUN TUBES

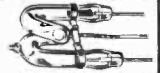Range available from stock.
S.A.E. for details.



ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt, £6.00 (callers only).
2ft 20 watt, £4.60. Post 60p. (For use in
standard bi-pin). MINI, 12in 8 watt, £1.75.
Post 25p. 9in 6 watt, £1.40. Post 25p.
6in 4 watt, £1.40. Post 25p. Complete ballast
unit and holders for 9in and 12in tube, £2.50.
Post 30p. (9in and 12in measures approx.)

SQUAD LIGHT

A new conception in
light control. Four
channels each capable
of handling 750 watts
of spot lights, flood lights or dozens of small
mains lamps. Seven programs all speed
controlled plus flash modulation, effectively
giving 14 different positions. Makes sound-to-
light obsolete. Completely electrically and
mechanically noise free. Price only £60. Post
75p. S.A.E. (Footscap) for further details.




WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (Footscap) for details.

COLOUR WHEEL PROJECTOR TYPE P150 INTACHANGE

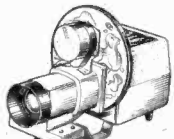200/240V a.c. 50Hz
150W lamp, com-
plete with oil filled
colour wheel and
motor plate. Takes
intachange acces-
sories and full range
of lenses. £29.95.
Post £1.35. (Total
inc. VAT & Post,
£33.70.)



BIG BLACK LIGHT

400W Mercury Vapor Ultra Violet Lamp. Powerful
source of UV P.F. ballast unit is essential with this
lamp. Price of bulb and matched ballast unit. £28.
Post £2. Spare bulb only £10. Post 80p.

VAT

VAT AT 8% MUST BE ADDED TO
ALL ORDERS FOR THE TOTAL VALUE
OF GOODS INCLUDING POSTAGE
UNLESS OTHERWISE STATED.

SERVICE TRADING CO.

GEARED MOTORS


100 r.p.m. 115lb. in. 110V,
50Hz. 2.8A, single phase, split
capacitor motor. Immense
power. Continuously rated.
Totally enclosed. Fan cooled in-line gearbox.
Length 250 mm. Dia. 135 mm. Spindle dia. 15.5 mm.
Length 145 mm. Ex-equipment tested £12. Post
£1.50. Suitable transformer 230/240V operation
£8. Post 75p.



DRAYTON MOTOR

Type RQR

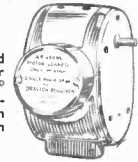230/250V 50c. Continuously rated
1 r.p.m. 90lb. in. Reversible Motor
is fitted with limit switch for 160°
angular reversible rotation if re-
quired. Twin spindle size 100mm
by 140mm by 125mm. Shaft 50mm
by 8mm. Weight 2 kg.
New Price £16.50, P. & P. £1.



BODINE TYPE N.C.I.

(Type J) 71 r.p.m. torque 10 lb. in.
Reversible 1/70th h.p. 50Hz.
The above precision made U.S.A. motor is
offered in 'as new' condition. Input voltage of motor
115V A.C. Supplied complete with transformer for
230/240V A.C. input.
Price, either type £6.25. Post 75p or less trans-
former £3.75. Post 65p.
(Type 3) 71 r.p.m. 4 lb. ins. 230V a.c. Continuously
rated. Non-reversible. £6.50. Post 75p.



15 R.P.M.

Type SD48 80 lb. in. Input 100/200 volt A.C. Length
incl. gearbox 270 mm. Height 135 mm. Width 150
mm. drive shaft 16 mm. Weight 8.5 Kilos. BRAND
NEW. Price £10. Carr. £1.
Suitable transformer for use on 220/240 volt A.C.
£3.85. Post 50p.

24 R.P.M. 230V a.c. Continuously rated. Mfg. My-
calex. Ex-equip. Fully tested. £3.85. Post 75p.

1 R.P.M. 230/240V A.C. SYNCHRONOUS!

Ex-equipment. Thoroughly tested and guaranteed.
ONLY £1.50. Post 20p.

20 R.P.M. 230/240 volt a.c. miniature motor. Price
£1. Post 20p.

PROGRAMME TIMERS

230V operation a.c. 15 or 20 r.p.m.
6 cam model £5. Post 60p.
9 cam model £6.50. Post 60p.
12 cam model £7.50. Post 60p.
Also available for 50V operation. Prices as above.




METERS NEW—90 mm Diameter

Type: 65CS D.C. M/C 2, 5, 10, 20, 50 amp.
£2.75. Post 20p. 100 amp £3.25. Post
20p.
Type: 62T A.C. M/I 1, 2, 50, 50 amp. £2.50. Post 20p.
100 volt A.C. M/I £2.75 and 300 volt A.C. R/M/C.
£3. Post 30p.



WHY PAY MORE?!

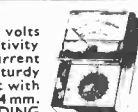MULTI RANGE METER. A.C. volts 2-5-500. D.C. volts 2-5-500 (Sensitivity
2000Ω/V D.C. and A.C.) D.C. current
0/1/10/100 mA. Ohms range. Sturdy
compact moving coil instrument with
21 ranges, dimensions 120x80x44 mm.
Weight 32 kg. SERVICE TRADING
CO. Price £5.50. Incl. leads and battery.
Post 50p. (Total price incl. VAT and Post £6.48).



TIME SWITCH

'Horstmann' Type V Mk. II Time
switch. 200/250 volt A.C. Two on/Two
off every 24 hours, at any manually pre-
set time. 30 amp contacts. 36 hour
spring reserve in case of power failure.
Day omitting device. Fitted in heavy
high impact case, with glass observa-
tion window. Built to highest Electricity
Board Spec. individually tested. Price
£7.75. Post 50p. (Total inc. VAT £8.91)



Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous
enamel embedded winding, heavy
duty brush assembly, continuously
rated.
25 WATT 10/25/50/100/150/250/500/1k/1.5k ohm.
£1.90. Post 20p.
50 WATT 1/5/10/25/50/100/250/500/1k ohm.
£2.40. Post 25p.
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/
3.5k/5k ohm £3.70. Post 35p.
Black Silver, Skirted knob calibrated in Nos. 1-9
1/4in. dia. brass bush. Ideal for above 22p each.




Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

KIT

KABS

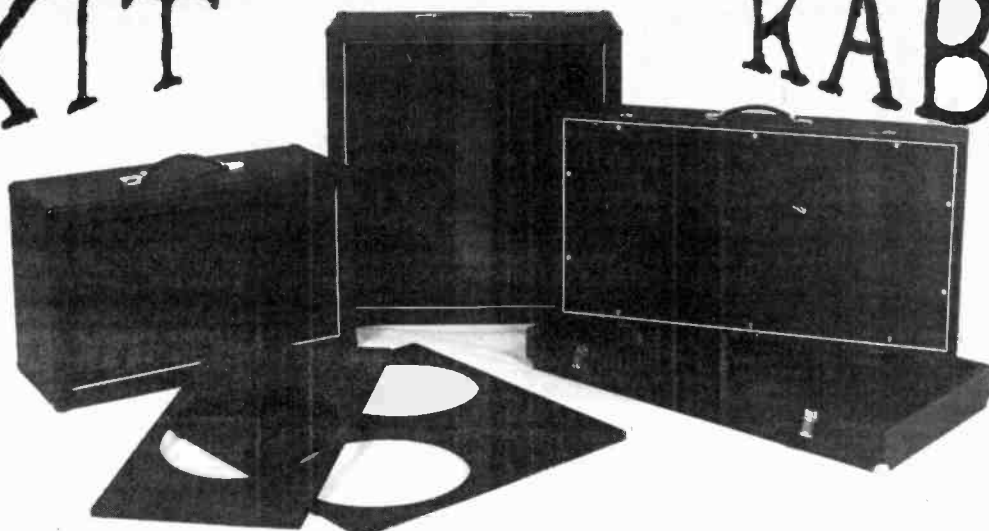

A RANGE OF STURDY, PRE-FABRICATED WOODEN CABINETS

All these cabinets are accurately machined, rebated and radiused, with all baffle holes cut out and fixing holes drilled. All the cabinet covering, fretcloth and fittings are included, along with detailed assembly instructions.

ALL YOU PROVIDE IS GLUE AND MANPOWER!

2 x 12" (or 1 x 15") Cabinet Kit—28" x 17½" x 11⅞"	£15·40	(¾" board)	} All prices inc. V.A.T. and carriage
4 x 12" (or 2 x 15") Cabinet Kit—29" x 28" x 11⅞"	£18·40	(¾" board)	
Disco Console Kit—36" x 19" x 9"	£17·40	(¾" and ½" board)	

Cheque or Postal Order to: KITKABS, P.O. Box 41, Stadium Works, Grainger Road, Southend-on-Sea, Essex



CAMERA KITS AND READY BUILT MODULES

Whether professional,
student, teacher or amateur,
a CROFTON module is the answer



Apart from our popular C.C.T.V. Camera Kits we are launching a range of ready built, tested, and guaranteed electronic modules both for trade and end user.

The ultimate range will be extensive. Some of the existing modules available are:

- E.T.I. Master Mixer ● E.T.I. Electronic Ignition
- Wide range R.F. Wobulator ● E.T.I. Digital Voltmeter ● E.T.I. Frequency Meter ● Video Amplifier ● Video Mixer ● Sound/Video Modulator
- Guitar Amplifier ● As well as all E.T.I. P.C.B.s, V.L.F. Transmitters and Receivers ● Send S.A.E. for information.

Secondhand cameras and monitors always available

CROFTON ELECTRONICS LTD

Dept. E, 35 Grosvenor Road, Twickenham, Middx. Tel. 01-891 1923

110 Electronic Alarm Projects for the Home Constructor

R. M. Marston

This is the latest addition to the author's popular series of electronic project books. It brings together 110 useful alarm circuits of a variety of types to intrigue the amateur, the student and the engineer.

Contents: Contact-operated alarm circuits; Burglar alarm circuits; Temperature-operated alarm circuits; Light-sensitive alarm circuits; Miscellaneous alarm circuits; Automobile alarm circuits; Instrumentation alarm circuits; Appendix; Index.

120 pages 0 408 00269 7 £2·95

Order from



Newnes Technical Books

NEWNES-BUTTERWORTHS

Borough Green, Sevenoaks, Kent TN15 8PH

Get a great deal from

Marshall's

A Marshall (London) Ltd Dept: PE
40/42 Cricklewood Broadway London NW2 3ET
Tel: 01-452 0161/2 Telex: 21492
& 85 West Regent St Glasgow G2 2QD
Tel: 041-332 4133
& 1 Straits Parade Fishponds Bristol BS16 2LX
Tel: 0272-654201/2
& 27 Rue Canton Issy Les Moulineaux
Paris 92

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome

CATALOGUE PRICE 40p (30p TO CALLERS)

TOP 500 SEMICONDUCTORS FROM THE LARGEST RANGE IN THE U.K.

All devices manufacturer's branded stock

2N456	1-40	2N4926	0-65	2N4922	0-65	AD161	PR	BC183	0-11	BF152	0-25	CA3130	0-68	NE561	4-48
2N456A	1-54	Green	0-13	2N4923	0-70	AD162	1-70	BC183L	0-14	BF153	0-25	LM301A	0-47	NE565A	1-30
2N457A	1-70	Yellow	0-13	2N5190	0-70	AF106	0-45	BC184	0-12	BF154	0-25	LM308N	1-32	OC35	1-50
2N490	4-60	Orange	0-13	2N5191	0-80	AF114	0-65	BC207	0-11	BF159	0-35	LM309K	1-80	OC42	0-50
2N491	5-00	2N3053	0-25	2N5192	1-00	AF115	0-65	BC208	0-10	BF160	0-30	LM381AN	0-07	OC71	0-45
2N492	5-75	2N3054	0-50	2N5195	1-10	AF116	0-65	BC212	0-14	BF166	0-40	LM702C	0-75	OC72	0-45
2N493	5-88	2N3055	0-65	2N5245	-29	AF117	0-65	BC212L	0-17	BF167	0-33	TO99	0-40	OC83	0-50
2N596	0-25	2N3391	0-34	2N5245	-29	AF117	0-65	BC214L	0-17	BF173	0-33	8D1L	0-40	ORP12	1-80
2N697	0-12	2N3390	0-37	2N5294	0-35	AF118	0-65	BC237	0-17	BF177	0-38	14D1L	0-40	SL414A	2-35
2N698	0-82	2N3392	0-14	2N5295	-40	AF124	0-65	BC238	0-12	BF178	0-45	LM710	0-45	SL810C	2-35
2N699	0-55	2N3393	0-15	2N5296	-40	AF125	0-65	BC239	0-16	BF179	0-48	LM723C	0-60	SL811C	2-35
2N706	0-12	2N3394	0-15	2N5297	-40	AF126	0-65	BC251	0-15	BF180	0-45	LM741	0-47	SL812C	2-35
2N706A	0-12	2N3402	0-30	2N5457	-29	AF127	0-65	BC253	0-22	BF181	0-45	TO99	0-38	SL820C	3-50
2N708	0-21	2N3414	0-15	2N5458	-29	AF139	0-69	BC257	0-17	BF182	0-45	8D1L	0-35	SL821C	3-50
2N709	0-20	2N3415	0-17	2N5459	-29	AF186	0-50	BC258	0-17	BF183	0-45	14D1L	0-40	SL823C	5-75
2N711	0-22	2N3416	0-17	2N5482	0-42	AF200	0-70	BC259	0-18	BF184	0-35	LM747CN	0-78	SL840C	4-00
2N718	0-55	2N3418	0-27	2N5484	0-45	AF239	0-74	BC262	0-19	BF185	0-36	LM748	0-48	SL841C	4-00
2N718A	0-40	2N3440	0-57	2N5777	0-45	AF279	0-80	BC263	0-30	BF195	0-11	8D1L	0-44	SN7603N	2-38
2N720	0-69	2N3441	0-78	2N6022	0-45	AF280	0-85	BC300	0-45	BF196	0-13	LM3900N	0-55	SN7603N	1-50
2N914	0-22	2N3442	1-20	3N128	0-80	AL102	1-50	BC301	0-45	BF197	0-14	LM7805P	1-39	SN7603N	2-50
2N916	0-43	2N3638	0-16	3N139	1-45	AL103	1-50	BC302	0-40	BF198	0-15	LM7812P	1-39	ST2	2-20
2N918	0-34	2N3638A	0-16	3N140	1-00	BC108	0-12	BC303	0-60	BF200	0-31	LM7815P	1-39	TA263	1-25
2N929	0-25	2N3639	0-30	3N141	0-85	BC107	0-14	BC307	0-20	BF225J	0-25	LM7824P	1-39	TA300	2-67
2N930	0-26	2N3641	0-20	3N200	2-60	BC108	0-15	BC308	0-15	BF244	0-48	LOC0511	1-60	TA350	2-48
2N1302	0-37	2N3702	0-17	40361	-15	BC113	0-15	BC309C	0-25	BF245	0-34	MC1303	0-75	TA550	2-25
2N1303	0-37	2N3703	0-15	40382	-48	BC115	0-19	BC317	0-14	BF246	0-75	MC1310	1-06	TA6611C	2-60
2N1304	0-40	2N3704	0-15	40383	-1-00	BC116	0-19	BC318	0-13	BF254	0-20	MC1330P	0-75	TA6621	2-15
2N1305	0-40	2N3705	0-15	40389	-1-00	BC116A	0-20	BC337	0-19	BF255	0-20	MC1351P	0-87	TA6611B	1-32
2N1306	0-45	2N3706	0-14	40384	-0-80	BC117	0-22	BC338	0-21	BF257	0-37	MC1352P	0-87	TBA641B	2-50
2N1307	0-45	2N3707	0-18	40395	-1-20	BC118	0-18	BC547	0-12	BF258	0-49	MC1466L	3-95	TA6651	1-80
2N1308	0-60	2N3708	0-14	40406	-0-48	BC119	0-30	BC548	0-10	BF259	0-49	MC1469R	2-50	TBA800	1-20
2N1309	0-80	2N3709	0-15	40407	-0-38	BC121	0-15	BC549	0-43	BF259	0-49	MC1469R	2-50	TBA810	1-18
2N1671	1-80	2N3710	0-14	40408	-0-50	BC125	0-18	BCY30	1-03	BF279	0-24	ME040	0-15	TBA820	1-10
2N1671A	1-82	2N3711	0-15	40409	-0-55	BC126	0-25	BCY31	1-06	BFS21A	2-60	ME0412	0-20	TBA920	1-79
2N1671B	1-92	2N3712	1-20	40410	-0-55	BC132	0-30	BCY32	1-18	BFS28	1-04	ME4102	0-10	TIL209	0-30
2N1711	0-22	2N3713	0-20	40411	-2-30	BC134	0-15	BCY33	0-90	BFS61	0-30	ME4104	0-10	TIP29A	0-50
2N1907	5-50	2N3714	2-45	40554	-0-80	BC135	0-18	BCY34	0-98	BFS98	0-27	MJ480	1-05	TIP29C	0-50
2N2102	0-60	2N3715	2-45	40595	-0-85	BC136	0-19	BCY38	2-00	BFX89	0-95	MJE3055	0-75	TIP30A	0-80
2N2147	1-40	2N3716	2-60	40601	-0-70	BC137	0-14	BCY42	0-60	BFX30	0-38	MJ490	1-05	TIP30C	0-85
2N2148	1-85	2N3717	1-60	40602	-0-50	BC140	0-60	BCY58	0-55	BFX84	0-38	MJ491	1-55	TIP31A	0-82
2N2160	1-10	2N3772	1-70	40603	-0-60	BC141	0-65	BCY59	0-32	BFX85	0-41	MJ2955	1-21	TIP31C	0-85
2N218A	0-47	2N3773	2-65	40604	-0-60	BC142	0-30	BCY70	0-25	BFX87	0-35	MJE340	0-58	TIP32A	0-75
2N2219	0-42	2N3789	2-60	40636	-0-60	BC143	0-30	BCY71	0-26	BFX88	0-32	MJE2955	1-25	TIP32C	1-00
2N2219A	0-52	2N3790	2-75	40673	-0-73	BC147	0-10	BCY72	0-24	BFX89	0-95	MJE3055	0-75	TIP33A	1-00
2N2220	0-35	2N3791	2-75	40673	-0-73	BC148	0-10	BD115	1-20	BFY50	0-30	MJE370	0-68	TIP33C	1-45
2N2221	0-22	2N3792	2-90	AC127	-44	BC149	0-13	BD116	1-20	BFY51	0-36	MJE371	0-81	TIP34A	1-20
2N2221A	0-28	2N3794	0-20	AC128	-37	BC153	0-27	BD121	2-00	BFY52	0-38	MJE520	0-65	TIP34C	1-70
2N2222	0-25	2N3820	0-29	AC129	-50	BC154	0-27	BD123	2-00	BFY53	0-34	MJE521	0-75	TIP35A	2-50
2N2368	0-17	2N3823	0-61	AC153	-40	BC157	0-12	BD124	2-00	BFY90	1-27	MP8111	0-35	TIP36A	3-36
2N2369	0-25	2N3904	0-21	AC153K	-42	BC160	0-78	BD132	0-54	BSX20	0-31	MP8112	0-40	TIP41C	1-00
2N2369A	0-21	2N3906	0-22	AC154	-45	BC167	0-12	BD135	0-42	BSX21	0-32	MPF103	0-45	TIP42A	0-80
2N2646	0-55	2N4036	0-67	AC178	-48	BC168	0-12	BD136	0-42	BU105	3-05	MPSA05	0-20	TIP42C	1-20
2N2647	1-10	2N4037	0-55	AC178K	-48	BC168	0-12	BD137	0-45	BU205	2-40	MPSA06	0-20	TIP2955	1-50
2N2904	0-38	2N4056	0-20	AC187K	-48	BC169	0-12	BD138	0-48	C106D	0-65	MPSA12	0-35	TIP3055	0-50
2N2904A	0-37	2N4059	0-15	AC187	-48	BC170	0-16	BD140	0-50	CA3020A	1-50	MPSA55	0-20	TIS43	0-30
2N2905	0-37	2N4060	0-20	AC187	-48	BC170	0-16	BD140	0-50	CA3020B	1-50	MP8112	0-40	ZTX300	0-15
2N2905A	0-38	2N4061	0-17	AD188	-42	BC171	0-14	BD529	0-35	CA3035	1-35	MPSU05	0-40	ZTX301	0-15
2N2906	0-28	2N4062	0-18	AD142	-85	BC172	0-12	BD530	0-35	CA3046	0-73	MPSU06	0-40	ZTX302	0-20
2N2906A	0-25	2N4216	0-17	AD143	-78	BC177	0-19	BDY20	1-10	CA3048	2-15	MPSU55	0-45	ZTX500	0-15
2N2907	0-21	2N4289	0-30	AD148	-74	BC178	0-18	BF115	0-36	CA3052	1-62	MPSU56	0-45	ZTX501	0-15
2N2907A	0-22	2N4319	0-80	AD150	-78	BC179	0-19	BF117	0-70	CA3080A	1-10	NE555V	0-48	ZTX502	0-18
2N2924	0-15	2N4920	0-80	AD161	-75	BC182	0-11	BF121	0-55	CA3089E	2-00	NE561	3-70	ZTX503	0-23
2N2925	0-17	2N4921	0-80	AD162	-75	BC182L	0-14	BF123	0-55	CA309AO	4-25	NE560D	4-48	ZTX531	0-22

NEW RANGE TOOLS—HIGH QUALITY
MINIATURE ELECTRONIC PLIERS
AND CUTTERS INSULATED HANDLES

- Round nose box joint 4in long £2-50
- Diagonal cutters box joint 4in long £2-80
- Flat nose box joint 4in long £2-40
- Snipe nose box joint 4in long £2-40

DESOLDERING TOOL £5-00

P.C. MARKER PEN DALO 33PC 87p
ZENER DIODES 400MW 11p, 1W 17p, 2-5W 35p.
IC SOCKETS 8 DIL 14p, 14 DIL 15p, 16 DIL 16p.
RESISTORS $\pm 2\%$ (100 per value £1-30)
 $\pm 5\%$ 3p (100 per value £2-00)
SCORPIO CAR IGNITION KIT £12-95.
JUMBO 7 SEGMENT DISPLAYS £2-16.
DL 707 £1-60.
MINITRON £1-50.
LEDs Red, green and yellow, 0.2in dia, 24p.

SEE MARSHALL'S FOR CMOS




CD4000	0-20	CD4018	0-01	CD4042	0-83
CD4001	0-20	CD4019	1-10	CD4043	0-50
CD4002	0-20	CD4020	1-12	CD4044	0-84
CD4008	1-18	CD4021	1-01	CD4045	1-43
CD4007	0-20	CD4022	0-87	CD4046	1-32
CD4008	0-87	CD4023	0-87	CD4047	1-15
CD4009	0-87	CD4024	0-78	CD4048	0-88
CD4010	0-87	CD4025	0-20	CD4049	0-88
CD4011	0-20	CD4027	0-86	CD4050	1-54
CD4012	0-20	CD4028	0-81	CD4510	1-40
CD4013	0-87	CD4029	1-17	CD4511	1-84
CD4014	1-01	CD4030	0-87	CD4518	1-26
CD4015	1-01	CD4031	2-28	CD4520	1-25
CD4016	0-56	CD4037	0-87	CD4553	4-00
CD4017	0-01	CD4041	0-83		

MICROPROCESSORS FROM MARSHALL'S

WATCH THIS SPACE FOR NATIONAL SEMICONDUCTOR MICROPROCESSORS — AVAILABLE EXCLUSIVELY FROM MARSHALL'S. WE'LL STOCK THE HARDWARE — YOU CAN SEE HOW SIMPLE IT IS STARTING NEXT MONTH IN PRACTICAL ELECTRONICS.

TTL FROM NATIONAL, ITT, TEXAS, SIGNETICS, ETC.

SN7400	0-16	SN7412	0-25	SN7438	0-35	SN7454	0-16	SN7483	0-92	SN74100	1-15	SN74153	0-73	SN74175	0-84
SN7401	0-16	SN7413	0-25	SN7											

<p>JC12 AMPLIFIER 6W IC audio amp. with free data and printed circuit. £2-25*</p>  <p>DELUXE KIT FOR JC12 Contains extra parts for the pcb and volume and tone controls. Mono version £2-33. Stereo £4-95.</p> <p>JC12 POWER KIT Supplies 25V 1A. £3-55.</p> <p>JC12 PREAMP KITS Type 1 for magnetic pickups, mics and tuners. Mono £1-50, Stereo £3. Type 2 for ceramic or crystal pickups. Mono 88p, Stereo £1-75.</p> <p>LOUDSPEAKERS FOR JC12 8 x 5in 8 ohms 5W £2-48. Send S.A.E. for free leaflet on kits.</p>	<p>JC40 AMPLIFIER New integrated circuit 20W amplifier kit complete with chip, printed circuit and data £4-45. Send S.A.E. for free leaflet.</p> <p>PRINTED CIRCUIT KIT £3-95* Make your own printed circuits. Contains etching dish, 100sq.in of pc board, 1lb ferric chloride, etch resist pen, small drill bit, laminate cutter.</p> <p>SINCLAIR BLACK WATCH Fully assembled with free stainless steel bracelet £20-95.</p> <p>S-DECS AND T-DECS* S-DeC £2-24 T-DeC £4-05 µ-DeCA £4-45 µ-DeCB £7-85 IC carriers— 16 dit: plain £1-07, with socket £2-21. 10TOS: plain 99p, with socket £1-95.</p>  	<p>Battery Eliminator Bargains STABILIZED POWER UNITS* Millenia series. Switched 1 to 30V in 0.1V steps. 1A output: Kit £11-45; Kit + case £14-40; Bullt £18-40. 2A output: Kit £13-95; Kit + case £16-90; Bullt £20-95.</p> <p>6-WAY SPECIAL £5-20 Switched output of 3/4V/6/7/9/12V at 500mA.</p> <p>6-WAY DOUBLE RADIO MODEL £6-20 Switched output 3 + 3/4V + 4/6 + 6V/7 + 7/9 + 9/12 + 12V at 250mA. Also 15/18/24V single.</p> <p>3-WAY MODEL Switched output of 6/7/9V at 250mA with 4-way multi-jack plug £2-95*.</p> <p>RADIO MODELS 50mA with press-stud battery connectors. 9V £3-25. 6V £3-45. 9 + 9V £4-95. 6 + 6V £4-95. 4 + 4V £4-95. Also 9V 300mA £3-95.</p> <p>CASSETTE MAINS UNITS 7/9V output with 5 pin DIN plug. 50mA £3-45. 300mA £3-95.</p> <p>CAR CONVERTORS Input 12V d.c. Output 6/7/9V d.c. 1A regulated. £4-75*.</p>
<p>SINCLAIR IC20 IC20 10W + 10W stereo IC amplifier kit with free printed circuit and data £4-95. PZ20 Power supply kit for the above. £3-95. VP20 Volume, tone-control and preamp kit. £7-95. SP20 10W 4 ohm speaker for IC20 £2-95. CS20 11 x 6 x 3in. attractive case for IC20 £2-95* Send S.A.E. for free leaflet.</p>	<p>SINCLAIR CALCULATORS* Cambridge Univ £6-60. Cambridge Scientific £11-45. Oxford 300 £13-30. Programmable Scientific with free mains unit £24-95. Mains adaptors are available for all models (state model) £3-20.</p> <p>CBM CALCULATORS* 887D 8 digit %/4 function memory £4-95. SR7819D 8 digit or 5 + 2 memory/trig/log/pi/powers £10-95. SR1800 10 digit scientific £17-95. Mains adaptors £3-20.</p> <p>NOVUS CALCULATORS* 835 Model 8 digit %/sq. root/const/4 function memory £4-95. Mains adaptors £4-20.</p>	<p>BATTERY ELIMINATOR KITS Send S.A.E. for free leaflet on range. 100mA radio types with press-stud battery terminals. 4V £1-95. 6V £1-95. 9V £1-95. 4V + 4V £2-60. 6V + 6V £2-60. 9V + 9V £2-60. 100mA cassette type with 5 pin DIN plug. 7/9V £1-95. Transformer stabilized 8-way type for low hum 3/4/6/7/9/12/15/18V 50mA £3-15; 1A £6-50. Heavy duty 13-way type 4/6/7/8/11/13/14/17/21/25/28/34/42V. 1 amp model £4-40. 2 amp model £8-95. Car converter kit. Input 12V d.c. Output 6/7/9V d.c. 1A regulated £1-95.</p>
<p>FERRANTI ZN414 IC radio chip £1-44. Extra parts and pcb for radio £3-65. Case 99p. Send S.A.E. for free data.</p>	<p>MISTRAL DIGITAL CLOCK KITS* Includes pcb, power supply, case, 7in display, chip and all parts. Kit £10-95. Bullt £11-95. Also Mistral 2, de luxe assembled version with alarm and tilt sleep-over facility £13-95. Send S.A.E. for our Digital Clock leaflet</p>	<p>MAINS TRANSFORMERS 6-0-6V 100mA £1. 9-0-9V 100mA £1. 18V 1A £1-95. 0. 12. 15. 20. 24. 30V 1A £3-60. 12-0-12V 100mA £1. 0. 12. 15. 20. 24. 30V 2A £4-95. 20V 2 1/2A £2-25. 6-0-6V 1 1/2A £2-16. 9-0-9V 1A £2-45. 12-0-12V 1A £2-95. 15-0-15V 1A £3-20. 30-0-30V 1A £4-15. 6-3V 1 1/2A £2-45. 0-24V twice 100mA £1-65.</p>
<p>SINCLAIR PROJECT 80 AUDIO MODULES FM tuner £13-25. Q16 £9-50. PZ5 £4-95. PZ6 £8-70. Z40 £5-75. Stereo 80 £11-95. Project 80SQ £18-95.</p> <p>BI-PAK AUDIO MODULES S450 Tuner £18-95. AL60 £4-33. PA100 £13-45. MK60 audio kit £27-20. Teak 60 £10-95. Stereo 30 £15-95. TC30 £4-60. AL250 £18-15. Send S.A.E. for free data.</p> <p>SAXON ENTERTAINMENTS AUDIO MODULES SA1208 £18-95. SA1204 £13-30. SA608 £11-95. SA604 £10-30. PM1201/8 £11-45. PM1202/8 £14-95. PM1202/4 £14-95. PM1201/4 £11-45. PM601/8 £8-95. PM301/8 £8-70. Send S.A.E. for free leaflet.</p>	<p>SWANLEY ELECTRONICS Dept. PE, PO Box 68, Swanley, Kent</p> <p>Post 30p on orders under £2, otherwise free. Prices include VAT (Overseas customers deduct 7% on items marked *, otherwise 11%). Official orders welcome.</p>	



THE "Manta" Capacitive Discharge Electronic Ignition

IMPORTANT NEWS:

We are pleased to announce that the "Manta"—one of the highest quality ignition units available—is now supplied in Kit Form.

Construct this top performance electronic ignition unit and benefit from improved petrol consumption, smoother running and instant starting for your vehicle. **ONLY £16-50**

Kit price (including postage and packing, VAT, full assembly and installation instructions): (Ready-made unit available at £19-85, including VAT, postage and packing)

Please send S.A.E. today for full details of this top quality unit and our illustrated brochure "Electronic Ignition—How it Works"

ELECTRO SPARES
Dept. P.E., 187a Sheffield Road, Chesterfield, Derbyshire S41 7JQ. Tel. (0246) 36638



This fine Super Touch-Sensitive Piano can be built in just 12 hours. All component parts are brand new and guaranteed, and sold at wholesale prices. Visit our showroom and see how simple and professional the end product is.

For further details on our complete range including Organ kits and components for musical instruments, telephone 01-986-8455/5063, 01-870-4949, 01-249-5624.

Elvino Electronic Musical Instruments
Showroom: 12 Brett Road, Hackney, London, E8 1JP.

CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT
ALL PRICES INCLUDE P&P AND V.A.T.

AUDIO MODULES		SOLDERING IRONS (ANTEX)	
AMPLIFIERS	5W RMS £ 3-15	15W "C" Miniature Irons	£ 3-20
10W RMS £3-50	25W RMS £ 4-60	15W "CCN" Low Leakage Irons	£ 3-45
35W RMS £7-70	125W RMS £17-40	18W "G" Miniature Irons	£ 3-25
PRE-AMPLIFIERS Microphone	£ 2-75	25W "X25" Low Leakage Irons	£ 2-90
Stereo for 5/10W	£ 7-50	"SK1" Soldering Kits	£ 4-40
Stereo for 25W, PB Selector	£15-35	"MLX" 12V Kits	£ 4-10
STEREO FM TUNER		Elements, "C" £1-50	"CCN" £ 1-85
Decoder, PB Selector	£22-70	"G" £1-85	"X25" £ 1-60
POWER SUPPLY 10W £1-50, 25W £ 3-55		each £ 0-50	
TRANSFORMERS			
10W £2-95,	25W £ 3-35		
EARPHONES/HEADPHONES			
Crystal £0-65,	Stethoscope £ 1-35		
2,000Ω £3-85	Stereo £ 4-15		
INTERCOMS 2 station	£ 6-75		
MICROPHONES Dynamic	£ 2-15		
SPEAKERS 75mm dia. 8Ω	£ 1-00		
TAPE HEAD DEMAGNETISERS	£ 3-65		
TEST CASSETTES	£ 2-30		



4 1/2 in x 3 1/2 in **METER.** 30µA, 50µA or 100µA, £4.29. 16p P. & P.

TAPE RECORDER LEVEL METER



500µA, 80p. 10p P. & P.



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £7.50. 26p P. & P.


42 x 42mm meters 1mA, 500mA, £2.76. 16p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £3.70. 11p P. & P.

Edgewise meters 90mm x 34mm, 500µA, and 1mA, £3.40. 16p P. & P.

MULTI-METER

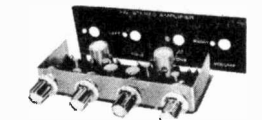Model ITI-2
20,000 ohm/volt, £8.87.
26p P. & P.



3 WATT STEREO (1 1/2 + 1 1/2) PER CHANNEL AMPLIFIER
£4.30. 16p P. & P.

All above prices include V.A.T. LARGE S.A.E. for New List. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

complete DIGITAL CLOCK KITS TEAK CASES



"DELTA"

GENUINE TEAK OR PERSPEX CASE

prompt order despatch
NON-ALARM
£10.65
+ 85p VAT
ALARM
£13.43
+ £1.07 VAT
(Prices include P. & P.)

DELTA DATA: 4 Radiant Red 1/2 in high LEDs. 12hr display with a.m./p.m. indication. Beautiful Burma Teak Case or Pretty Perspex in white, black, blue, red, green. Power failure is indicated by flashing display.

MODULES: Kits can be bought without case—Non-Alarm £9; Alarm £12.50 inclusive.

READY BUILT: Buy a working tested module and fit your own case—Non-Alarm £9.50; Alarm £13; or put it with our case parts (£4.32) and save on complete clock price. Complete clock ready built. 2yr guarantee—Non-Alarm £13.50; Alarm £18.50.

ALARM FEATURES: Pulsed tone. Tilt operated 10 minute "Snooze" period. Single switch setting. Optional extra mercury switch (45p) allows alarm reset by tilting clock. Digit brightness is automatically controlled to suit lighting level.

"ALPHA" CHRISTMAS OFFER 4 Glowing Green 1/2 in high digits | Built and Tested Module plus Perspex Case | **£11 incl.**
12 or 24 hour. Non-Alarm

NOVUS CALCULATORS 650 £5.40 4510 £16.20
850 £8.75 6030 £21.60



Send payment with order. S.A.E. for complete range of clocks, calculators and components

Pulse Electronics Ltd

Dept. PE5, 202 Shefford Road, Clifton Shefford, Beds.
Telephone: Hitchin (0462) 814477



One of these could make a new man of you

Take a look at the labels. Each one a formula for making you forget the stresses and strains of modern living. The message of each name is: make something. Make a digital clock . . . make a coffee table . . . make some new sounds. The sheer concentration involved in constructional projects like these smooths away the tensions. Any one of these "Practical" magazines packs so many hours of creative satisfaction that it could make a new man of you.

PRACTICAL HI-FI & AUDIO

November issue:
Special 12 page supplement: Getting the best from your Hi-Fi system. A comparison of ten receivers plus five moving coil pick-up cartridges. There is also a £900 Hi-Fi system to be won. OUT OCTOBER 15TH.

Television

November issue:
This month we show you how to build a Remote Control Channel Selector requiring a minimum of connections and modifications to the television set. There are also features on the Sony VO 1810 Video Cassette Recorder and Video Cassettes for the Experimenter. OUT OCTOBER 18TH.

PRACTICAL ELECTRONICS

November issue:
Build our Orion Stereo Tuner - it has been designed to complement the Orion amplifier but can also be used satisfactorily with others. Other features this month are a Disco Strobe 4-channel light show controller and a Hazard Flasher for your car. OUT OCTOBER 8TH.

everyday electronics

November issue:
In this issue there are three easy projects for three different hobbies - for amateur astronomers there is the Clear Sky Indicator; for photographers, the Enlarger Timer; and for hi-fi enthusiasts, a Scratch and Rumble Filter. OUT OCTOBER 15TH.

PRACTICAL WIRELESS

November issue:
Our 8 page supplement shows you how to equip your car with electronic gadgets to make it safer, cheaper to run, and less prone to breakdowns - there is a Burglar Alarm, and Electronic Thermostat. OUT OCTOBER 15TH.

PRACTICAL WOOD WORKING

November issue:
Extra 8 page booklet on portable power tools. Construction details for a nest of tables, a wardrobe plus bookshelves and cupboards. OUT OCTOBER 15th

Pick up a 'Practical' and be a new man



Handy size Reels & Dispensers

**OF THE WORLD'S FINEST CORED SOLDER TO DO
A PROFESSIONAL JOB AT HOME**

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

SAVBIT
handy solder dispenser



Contains 2.3 metres approx. of 1.22 mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.
Size 5 39p


For soldering fine joints

NEW handy size reels of **SAVBIT, 40/60, 60/40 & ALU-SOL** solder alloys



These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

BIB WIRE STRIPPER & CUTTER



Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds. **Model 8B 86p**

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits.
PC115 50p
Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.
Size 19A 43p

Ref.	Alloy	Diam. mm	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£1.49
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£1.99
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£1.49
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£1.49

SOLDER-WICK



Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 Watt soldering iron. Quick and easy to use. Non-corrosive.
Size 18 97p

Sole U.K. Sales Concessionaires:

Bib Hi-Fi Accessories Limited,
Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ.

Prices shown are recommended retail, inc. VAT From Electrical and Hardware Shops. In difficulty send direct, plus 15p P&P. Prices and specifications subject to change without notice.

ARROW ELECTRONICS LTD.

NEW EXTENDED COSMOS RANGE

CD4000	20p	CD4030	58p
CD4001	20p	CD4035	£1-18
CD4002	20p	CD4040	£1-08
CD4006	£1-06	CD4042	88p
CD4007	20p	CD4043	£1-08
CD4008	98p	CD4044	98p
CD4009	58p	CD4049	58p
CD4010	58p	CD4050	58p
CD4011	20p	CD4052	98p
CD4012	20p	CD4056	£1-38
CD4013	58p	CD4060	£1-38
CD4014	£1-08	CD4066	98p
CD4015	£1-08	CD4068	24p
CD4016	58p	CD4069	24p
CD4017	£1-08	CD4070	50p
CD4018	£1-08	CD4071	24p
CD4019	58p	CD4073	24p
CD4020	£1-18	CD4077	24p
CD4021	£1-08	CD4081	24p
CD4022	98p	CD4082	24p
CD4023	20p	CD4085	75p
CD4024	60p	CD4086	75p
CD4025	20p	CD4093	85p
CD4026	£1-80	CD4099	£1-85
CD4027	58p	CD4511	£1-85
CD4028	98p	CD4528	£1-45
CD4029	£1-18		

74 SERIES TTL VEROBOARD TRANSISTORS SWITCHES

LM380
2 watt IC £1-10

IC SOCKETS
8 Pin 14p
14 Pin 18p
16 Pin 17p

NATIONAL CLOCK CHIP
MM5314 £4-20
(Basic clock chip)

Other components
Zener diode 400mW 3-3V to 30V 12p
Resistors, carbon film ½W 5 E12, 2p; ½W 2p.

THE GREEN GIANT
Jumbo-sized Green LED-5mm 28p

TRANSDUCERS

40kHz Ultrasonic transducers as used in many Mag. articles complete with suggested circuits: Order type: RL400PP £4-54 pair

741 OP-AMP MINIDIP 35p
301A OP-AMP, 8 PIN DIL 45p
3900 14 PIN DIL 70p
558 14 PIN DIL £1-10
100 VOLT 7 AMP SCR 55p

7 WATT AUDIO CHIP
TBA810S with data £1-05

TIMER CHIP NE555V. 60p

SOLDERING EQUIPMENT AND TOOLS

DST Mk. 1 "Solder Sucker" a truly indispensable tool £4-66
Spare Nozzle 50p
CCN-15W Miniature Iron 240V £3-74
X25-240 25 Watt Iron 240V £3-47
MLX12 12V Battery Iron £4-29
ST3 Soldering Iron Stand £1-53
For all models
S167 Thermal shunt for delicate components 43p

3 WATT ZENERS

Axial lead, miniature plastic case full 3 Watt Diac. Following voltages only: 6-8, 8-2, 10, 11, 12, 15, 16, 18, 22, 24, 27, 32, 33, 62, 68, 91, 100.
ALL ONE PRICE 43p

TDA2020 20W Audio Amp. £3-36
ZN414 TRF Radio Receiver £1-40

SENSATIONAL STOCK CLEARANCE

PAK: AA1 25 assorted transistors. Our choice £1-90
PAK: AA2 Ten TAA243 Op Amps (high gain) 70c £1-90
PAK: AA3 Ten BCW54 300mW 300mHz 64V Transistor NPN £1-00

GREAT TRIAC CLEARANCE

SC35A 3A 100V 55p
SC35B 3A 200V 65p
SC40B 6A 200V 70p
SC40E 6A 400V 85p
SC40E 6A 500V 90p
SC45A 10A 100V 75p
SC45B 10A 200V 90p
SC45E 10A 500V £1-00
SC50D 15A 400V £1-10

4-TRACK TAPE HEADS

record/pb £3-25

SEMICONDUCTORS AND ICs

Our huge availability of transistors, diodes, Triacs, SCRs, Zeners, etc., is too large to list. For price and availability Telephone Alan Green on 0277 219435 (Ex. 7).

VISIT OUR **NEW**

RETAIL SHOP
open six days per week—
FOR A WIDE RANGE
OF INTERESTING ITEMS!

**COPTFOLD ROAD
BRENTWOOD ESSEX**
(Thurs. early closing)

ALL PRICES INCLUDE V.A.T.

Trade Enquiries Welcome. Ex. 9

POSTAGE: 25p, over £5 free

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

MAINS ISOLATING
PRI. 120/240V
SEC. 120/240V

CENTRE TAP WITH SCREEN

Ref.	VA	(Watts)	£
07*	20	4-57	
149	60	8-68	
150	100	7-65	
151	200	11-95	
152	250	14-47	
153	350	17-14	
154	500	19-73	
155	750	27-25†	
156	1000	37-87†	
157	1500	43-33†	
158	2000	48-34†	
159	3000	76-36†	

*115V or 240V Sec. only.

30 VOLT RANGE
Prim. 200-240V
Sec. 0-12-15-20-24-20V

Ref.	Amps	£
112	0-5	3-15
79	1-0	4-00
3	2-0	5-55
20	3-0	6-87
21	4-0	7-83
51	5-0	9-55
117	6-0	10-88
88	8-0	14-15
89	10-0	14-51

60 VOLT RANGE
Prim. 200-240V
Sec. 0-24-30-40-48-60V

Ref.	Amps	£
124	0-5	3-84
126	1-0	5-43
127	2-0	7-85
125	3-0	11-00
123	4-0	13-07
120	5-0	14-20
120	6-0	16-64
121	8-0	19-58†
122	10-0	24-09†
189	12-0	25-18†

12 and or 24 Volt PRIMARY 240-250 VOLTS

Ref.	12v	24v	£
111	0-5	0-25	2-30
213	1-0	0-5	3-01
71	2	—	3-99
68	3	—	5-10
18	4	2	4-56
85	5	—	5-81
70	6	3	6-36
108	8	4	7-34
72	10	5	7-88
116	12	6	8-39
17	16	8	10-48
115	20	10	15-42
187	30	15	19-50
226	60	30	21-84†

HIGH VOLTAGE
Mains Isolating
Prim. 200/220 or 400/440
Sec. 100/120 or 200/240

VA	Ref.	£
60	243	6-82
350	247	15-23
1000	250	32-88†
2000	252	54-80†

AUTO TRANSFORMERS
Ref VA Auto Taps

Ref	VA	£
113	20 0-115-210-240	2-81
64	75 0-115-210-240	4-85
4	150 0-115-200-220-240	6-24
66	300 0-115-200-220-240	8-82
67	500 0-115-200-220-240	13-10
84	1000 0-115-200-220-240	19-79
93	1500 0-115-200-220-240	23-82†
95	2000 0-115-200-220-240	31-56†
73	3000 0-115-200-220-240	45-78†

CASED AUTO TRANSFORMERS
240V mains lead input & USA 2 pin outlets.

Ref	VA	£
20VA	E4-85	
150VA	E8-84	
500VA	E15-11	
1000VA	E22-84†	
2000VA	E35-86†	

ELECTRONIC CONSTRUCTION KIT
10 projects (including Electronic Organ).
Ideal gift at £8-63

50 VOLT RANGE
Prim. 200-240V
Sec. 0-19-25-33-40-50V

Ref.	No.	Amps	£
102	0-5	4-07	
103	1-0	5-27	
104	2-0	7-17	
105	3-0	8-77	
106	4-0	11-26	
107	6-0	17-28	
118	8-0	18-82	
119	10-0	22-04†	

SCREENED MINIATURES

Ref mA	Volts	£
238 200	3-0-3	2-50
212 1A, 1A	0-6, 0-6	2-87
13 100	9-0-9	2-28
235 330, 330	0-9, 0-9	2-39
207 500, 500	0-9-9, 0-9-9	3-14
208 1A, 1A	0-9-9, 0-9-9	4-51
236 200, 200	0-15, 0-15	2-28
214 300, 300	0-20, 0-20	3-22
221 700 (DC)	20-12-0-12-20	3-86
206 1A, 1A	0-15-20, 0-15-20	5-37
203 500, 500	0-15-27, 0-15-27	4-77
204 1A, 1A	0-15-27, 0-15-27	6-00
S112 500	12, 15, 20, 24, 30	3-15

TRANS CASES
Combined wall and floor mounting.
Send for details.

BRIDGE RECTIFIERS

Ref	VA	£
200V	2A	0-87
400V	2A	0-72
200V	4A	0-89
500V 10A (PM 7A6)		2-70

TEST METERS

Ref	£
AVO 8 MK5	£87-33
AVO 72	£28-86
AVO TT 169	£27-34
AVO MM5	£23-48
U4315 (USSR) inc. steel carry case	£13-93

POWER UNIT
CC12-05 Output Switched
3-4, 5-6-7, 5-9-12V at 500mA £5-18

NO HIDDEN EXTRAS—Prices include VAT and P & P. EXCEPT † WHERE CARRIAGE WILL BE ACCORDING TO WEIGHT AND DISTANCE—BRS. Electroshare Audio accessories, semiconductors, panel meters and multi-meters.

C1000 MINI-MULTIMETER
D.C.—1,000V, A.C.—1,000V, 1,000Ω/V.
D.C.1—100mA, Res.—150kΩ.
BARGAIN AT £4-50

ANTEX SOLDERING IRONS
15W £3-57 18W £3-31 25W £2-99
SOLDERING IRON KIT £4-48
STAND FOR ABOVE £1-49

MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR
OPERATING VOLTAGE 20-45V only
£3-17.

CALLERS WELCOME (MON.-FRI.) OR SEND STAMP FOR LISTS.

COMPONENT PAKS

- 200 Mixed value resistors (count by weight)
- 150 Mixed value capacitors (count by weight)
- 30 Mixed value precision resistors ½w 2%
- 15 Assorted pots & pre-sets
- 10 Reed switches
- 3 Micro switches
- 20 Assorted tag strips

PLEASE STATE PAK REQUIRED
90p PER PAK

AUDIO KIT 25W

- 2 + 25W Amplifiers
- 1 + Per-Amp
- 1 + Power supply
- 1 + Transformer
- 1 + Front Panel
- 1 + Kit of parts to include on/off switch, neon ind. Stereo head-phone socket. Plus instructions book £32-18.

TEAK AUDIO KIT 25W

Teak veneered cabinet
16½ + 11½ + 3½" aluminium chassis.
Heat sink and front panel brackets plus back panel and sockets etc.
£11-21

CARTRIDGES

Ref	£
Magnetic Sonotone 100	£5-31
Ceramic E. I. CS 2000	£2-72
ALOS GP93-1	£2-11
TCC AT55	£4-42

STEREO FM TUNER WITH PHASE-LOCK LOOP
4 Pre-selected stations supply 20-35V, 90mA Max. £22-72

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS ALDGATE & LIVERPOOL ST

Test Equipment

Multimeters

The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment.

NAME _____

ADDRESS _____

Eagle International, Precision Centre, Heather Park Drive, Wembley HA0 1SU Tel: (01)-902 8832



W:K:F ELECTRONICS

THE P.C.B. SPECIALISTS

PRACTICAL ELECTRONICS "PRINTED CIRCUIT BOARDS"
NOW AVAILABLE

TYPE 'A'—Made in 1.6mm Epoxy/Glass-fibre, supplied Roll-tinned & drilled.
TYPE 'B'—Made in 1.6mm S.R.B.P., supplied Roll-tinned & drilled:

All units available Ex. Stock by return. All prices INCLUDE Post—Pack, and V.A.T.
TERMS: Cash with order. Cheques & P.O.s payable to W.K.F. Electronics.

ISSUE	PROJECT	QTY OF TYPE 'A'	TYPE 'B'	P.C.B.s PRICE	PRICE
Sept. 1976	Cross-Hatch Generator	1	3.75	—	—
Sept. 1976	Gas—Smoke Detector	1	2.25	1.65	—
Sept. 1974	Gas & Smoke Detector	1	—	1.75	—
JAN. 1975	ORION STEREO 20W AMPLIFIER	1	3.60	2.20	—
May 1975	I.C. Pulse Generator	1	—	1.40	—
DEC.-JAN 1976	50 + 50W GUITAR AMPLIFIER	3	3.25	2.00	—
JUNE 1976	DIGITAL FREQUENCY METER	4	4.25	3.50	—
June 1976	Audio Millivolt Meter	2	—	1.60	—
JUNE-AUG. 1976	RADIO CONTROL SYSTEM	8	5.70	4.30	—

PRODUCTION SPACE ALWAYS AVAILABLE FOR:

P.C.B. PRODUCTION—ELECTROPLATING—SCREEN PRINTING—TINNING
CONTRACT DRILLING—ANY PHOTOGRAPHIC ART PROCESS

SERVICE FOR:

P.C.B. MASTER PREPARATION + ANY GRAPHIC ARTS PROCESS

FROM:

ROUGH COPIES—EXISTING UNITS—CIRCUIT DIAGRAM
EVEN FELT TIP PEN ON OLD FISH & CHIP PAPER!!

QUOTATIONS FREE OF CHARGE BY RETURN


Large discounts given for long runs. Run-on's and repeat orders. Also call-off orders accepted

FOR OUTLINE QUOTATIONS PHONE:
WHITWELL (DERBY'S) 695 (STD 090974)

ALL ORDERS & MAIL TO:
W.K.F. Electronics,
Welbeck Street,
Whitwell, Near Worksop,
Notts.



INVERTORS

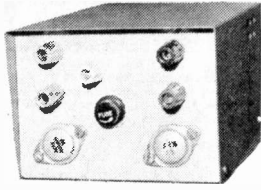

240v-50Hz from your 12v car battery.

25 watt—£4.75 300 watt (24v)—£26.45
 40 watt—£8.27 400 watt (12v)—£39.05
 75 watt—£12.03 500 watt (24v)—£48.18
 150 watt—£21.27 1kW (50v)—£127.00
 300watt (12v)—£33.03 1.5kW (110v)—£140.80

All above invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24.50 + £1.70p. & p.

FLUORESCENT LIGHT INVERTOR KIT
 8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats & secondary lighting for factories, hotels, etc.

12"-8 watt—£3.90 + 35p p. & p. Built up—£4.90 + 35p p. & p.
 21"-13 watt—£4.20 + 52p p. & p. Built up—£5.80 + 52p p. & p.

TRANSFORMERS & COILS

Both high volume & small order capacity available.
 Special offer. Miniature mains transformer 6-0-6v-6V.A.—85p plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

P.E. ORION STEREO AMPLIFIER



20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response \pm 1dB 20 Hz to 20 kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.


Complete kit of parts including slim line bookend case, silk screened front panel & knobs. £47.30 incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

INSTRUMENT CASES

Bookend Amplifier and attractive styled Instrument Cases available. Send S. and A. envelope for Price List.

ASTRO IGNITION

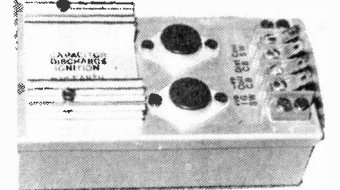

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10.45 incl. VAT. Ready built with only two connections to alter £13.75 incl. VAT. Thousands have used this system both home and abroad. Consider these *advantages* more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

ASTRO ELECTRONICS

Spring Bank Road, West Park
 Chesterfield.

MINICOMPUTERS AND MICROPROCESSORS

by M. Healey Price £6.80

SOLID STATE COLOUR TELEVISION CIRCUITS by G. R. Wilding. Price £6.25

PRACTICAL SOLID STATE D.C. SUPPLIES by T. D. Towers. Price £5.85

FOUNDATIONS OF WIRELESS AND ELECTRONICS by M. G. Scroggie. Price £4.25

SERVICING WITH THE OSCILLOSCOPE by G. J. King. Price £4.85

COLOUR TELEVISION by G. N. Patchett. Price £3.50

TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR by A. Douglas and S. Astley. Price £4.75

SEMICONDUCTOR CIRCUIT ELEMENTS by T. D. Towers. £6.00

110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston. Price £3.00

FET PRINCIPLES, EXPERIMENTS AND PROJECTS by E. M. Noll. Price £6.00

HOW TO BUILD ELECTRONIC KITS by V. Capel. Price £2.00

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
 of British and American Technical Books
**19-21 PRAED STREET
 LONDON W2 1NP**
 Phone 01-723 4185
 Closed! Saturday 1 p.m.

P.E. JOANNA Electronic Piano



ALL PARTS CAN BE SUPPLIED

Keyboard, Keyswitch, P.C.B.s, Hardware, Semiconductors, Resistors, Capacitors, Cabinets
 Complete kits or easy stages

Send S.A.E. for details

Clef Products
 31 Mountfield Road, Bramhall
 Stockport, Cheshire SK7 1LY

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c., 5V 1A 80p; 6.3V 1.5A £1.65; 3A £2.10; 6A CT £3.75; 12V 1.5A £2.10; 3A £3.75; 6A CT £5.25; 18V 1.5A CT £3.48; 24V 1.5A CT £3.75; 3A CT £5.25; 5A £5; 8A £11.25; 12A £18.80; 40V 3A CT £7.85; 50V 6A CT £18.75; 25V 2A + 25V 2A £7; 12V 4A + 12V 4A £7.

LT TRANSFORMERS TAPPED SEC. Prim 200/240V 0-10-12-14-16-18V 2A, £4; 4A, £5.25. 0-12-15-20-24-30V 2A, £4.50; 4A, £5.75. 0-5-20-30-40-60V 1A, £4.85; 2A, £5.75. 0-40-50-60-80-100-110V 1A, £7.

MIDGET RECTIFIER TRANSFORMERS
 For FW rect. 200/240V a.c., 5-0-8V 1.5A or 9-0-9V 1A £1.80 each; 12-0-12V 1A, or 20-0-20V 0.75A, or 9-0-9V 0.3A, or 12-0-12V 0.25A, or 20-0-20V 0.15A, or 6V 0.5A + 6V 0.5A, or 9V 0.35A + 9V 0.35A, or 12V 0.25A + 12V 0.25A, or 20V 0.15A + 20V 0.15A, all at £2 each.

LOUDSPEAKERS
 2 1/2" 8 or 75Ω, 2 1/2" 8 or 25Ω, 3 1/2" 8 or 35Ω, 3 1/2" 15Ω, £1 each; 5 x 5 1/2" 3, 8 or 25Ω, £1.75; Goodmans 8 1/2" twin cone, hi-fi, 4Ω, £2.80; 7 x 4 1/2", 3-8, 15 or 25Ω, £1.80.

"INSTANT" BULK TAPE/CASSETTE ERASER
 Instant erasure any diameter tape spool or cassette, demagnetises tape heads. 200/240V a.c., £3.75.

SYNCHRONOUS GEARED MOTORS 200/240V a.c.
 Brand new Smiths, built in gearbox, 6 r.p.m., £1.25 each.

PAPER TUBULAR CONDENSERS
 4.7mF, 180V, 30 x 20mm, 20p (100 for £10).

SPEAKER MATCHING AUTO TRANSFORMER
 12W, 3 to 8 or 15Ω, up or down, £1.85.

G.E.C. MANUAL OF POWER AMPLIFIER COVERING VALVE AMPLIFIERS OF 30W TO 400W 3sp.

CABLES — CABLES — CABLES

MICROPHONE TWIN H/DUTY, BRAIDED SCREEN
 Professional cable for stage, studio, outdoor. PVC covered, grey, 20p per metre. Grey: Single cable, black, 10p per metre.

MULTI WAY SCREENED, PVC COVERED
 36 way £1; 25 way 75p; 14 way 25p; 6 way 25p; 4 way 14p; 2 way 10p; 1 way 8p per metre.

LOW LOSS CO-AXIAL CABLE 75Ω
 UHF, white, 12p per metre; VHF, white, 9p per metre.

FLEXIBLE PVC MINI 3-CORE CABLE, 19/8-16MM
 100 metres £2.80. Ideal for speakers, intercoms, etc.

TWIN FIG. 8 CABLE
 Polarised, £2.50/100m. Screened stereo £1/15m.

ALL TYPES DOMESTIC AND COMMERCIAL CABLES.
 ALL SIZES AND COLOURS CONNECTING WIRES.
 MULTI SCREENED AND UNSCREENED CABLE.

TRADE ENQUIRIES INVITED
 Carriage and VAT extra on all orders
 S.A.E. ENQUIRIES. LISTS. MAIL ORDER ONLY
 46 Kenilworth Road, Edgware, Middx. HA8 8YG

Tel. 01-958 9314

GIRO NO 331 7056 Access and Barclay card accepted
 C W O only Terms of business as in our Catalogue
 Export Order enquiries welcome (€5 min.)
E & O E
 Official Orders accepted from Educational and Government Departments
 ALL PRICES include VAT and P. & P.
 SHOP HOURS 9-12.30, 1.30-5.00 5 DAYS
 CLOSED WEDNESDAY

1976 ISSUE 66 PAGES—3,000 ITEMS
 FULLY ILLUSTRATED
 *20p CREDIT VOUCHERS
 *ALL NEW STOCK
 *SATISFACTION GUARANTEED
 *DISCOUNTS

- 20p plus 10p postage
- Boxes — Cases —
 - Kits — PC Materials —
 - Tools — Resistors — Test
 - Meters — Capacitors —
 - Hardware — Semiconductors
 - Books — Pots — Coils
 - Audio Accessories — Screws
 - Connectors — Audio — Modules
 - Veroboard — Transformers
 - Knobs — Calculators — Audio Leads
 - Batteries — 5 sec Storage Units —
 - Heatsinks, etc., etc.

SPECIAL CAPACITOR KITS
 C280 Kit—PC Mounting polyester 250V 5 of each value 0.01, 0.022, 0.047, 0.1, 0.22 μ F, 2 of 0.47, 1 μ F, £1.81 net.
 C296 Kit—Tubular polyester, 400V, 5 of each value 0.01, 0.022, 0.047, 0.1, 0.22 μ F, 2 of 0.47 μ F, £2.43 net.
 Ceramic Kit—square plaque, 50V 5 of each value, 22, 33, 47, 100, 220, 330, 470, 1000pF, 220, 4700pF, 0.01 μ F, £1.71 net.

SPECIAL RESISTOR KITS (CARBON FILM 5%) (Prices include post & packing) 10E12 μ W or μ W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 E5-04 net 25E12 μ W or μ W KIT: 25 of each E12 value, 22ohms—1M, a total of 1425 E11-70 net

B. H. COMPONENT FACTORS LTD.

MULTIMETER U4323
 22 Ranges plus AF/IF Oscillator 20,000 Ω /Volt.
 Vdc—0.5—1000V in 7 ranges
 Vac—2.5—1000V in 6 ranges
 Idc—0.05—500mA in 5 ranges
 Resistance—5 Ω —1M Ω in 4 ranges.
 Accuracy—5% of F.S.D.
 OSCILLATOR—1KHz and 465KHz (A.M.) at approx. 1 Volt.
 Size—160 x 97 x 40mm.
 Supplied complete with carrying case, test leads and battery.
 PRICE £9.95 net P. & P. 75p



U4323

MULTIMETER U4324
 34 Ranges. High sensitivity, 20,000 Ω /Volt.
 Vdc—0.6—1200V in 9 ranges.
 Vac—3—900V in 8 ranges.
 Idc—0.06—3A in 6 ranges.
 Iac—0.3—3A in 5 ranges.
 Resistance—25 Ω —5M Ω in 5 ranges.
 Accuracy—dc and ac—2% of F.S.D.
 Size—187 x 98 x 63mm.
 Supplied complete with storage case, test leads, spare diode and battery.
 PRICE £11.72 net P. & P. 75p



U4324

MULTIMETER U4341
 27 Ranges plus Transistor Tester, 16,700 Ω /Volt.
 Vdc—0.3—900V in 8 ranges.
 Vac—1.5—750V in 6 ranges.
 Idc—0.06—600mA in 5 ranges.
 Iac—0.3—300mA in 4 ranges.
 Resistance—2K Ω —2M Ω in 4 ranges. Accuracy—dc—2%.
 ac—4% of F.S.D.
 I μ —10—350 in 2 ranges.
 Size—115 x 215 x 90mm.
 Complete with carrying case, test leads, and battery.
 PRICE £12.10 net P. & P. 75p



U4341


MULTIMETER U4313
 33 ranges. Knife edge with mirror scale, 20,000 Ω /Volt. High accuracy, mVdc—75mV.
 Vdc—1.5—600V in 9 ranges.
 Vac—60—120 microamps in 2.
 Idc—0.8—1500mA in 6 ranges.
 Iac—0.8—1500mA in 6 ranges.
 Resistance—1K Ω —1M Ω in 4 ranges db scale—10 to +12db.
 Accuracy—dc—1% ac—2%.
 Size—115 x 215 x 90mm.
 Complete with carrying case, test leads, and battery.
 PRICE £16.09 net P. & P. 75p



U4313

(P.E.), LEIGHTON ELECTRONICS CENTRE, 59 NORTH STREET, LEIGHTON BUZZARD, LU7 7EG. Tel. Leighton Buzzard 2316 (Std. Code 05253)

G8CZW DIGITAL FREQUENCY METER

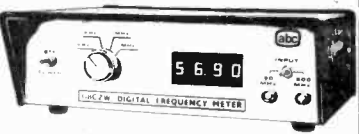

COMPLETE 50MHz KIT £54 inc. VAT and Post (U.K.)

ZN 1040E Count/Display I.C.	8.90
Integrated Circuit Pack	9.25
Displays and Filter	7.28
Semiconductor and Diode Pack	2.38
Resistor and Capacitor Pack	2.98
Logic and Display P.C.B.'s	4.84
5 MHz Crystal	3.45
Transformer 8-0-8V (+ 60p P. & P.)	2.48
I.C. Sockets Pack	2.30
Switches, Knob, BNC Sockets, etc.	4.15
Hardware and Wire Pack	1.45
Case—Two-tone PVC-faced steel punched and lettered (+ 75p P. & P.)	5.75
Spare min. BNC Sockets (50 ohm)	0.65
Spare min. BNC Plugs (50 ohm)	0.70
Complete kit of parts for High Impedance Buffer (includes PCB)	3.62
High Impedance Buffer P.C.B. only	0.80
Complete kit for VHF pre-scaler (includes PCB but less I.C.)	1.78
VHF Pre-scaler printed circuit board only	0.80
SP8631B 500MHz Pre-scaler I.C.	8.96
ZN1034E Precision Timer I.C.	2.97
ZNA118E 3 $\frac{1}{2}$ digit digi-voltmeter I.C.	6.48
Digital Voltmeter P.C.B.'s and Circuits	3.78
NE592 Wideband video amplifier I.C.	1.43
Reprint of full G8CZW article (post free)	0.50

All prices inc. VAT at the standard rate. Please add 20p P. & P. for packs. S.A.E. for full lists.
 Overseas—Deduct 8% off these prices

abc ELECTRONICS (OLDHAM) LTD.
 83 Lees Road, Oldham OL4 1JW
 Tel. 061-624 8812

4-STATION INTERCOM



£16.95 + VAT £1.36
 Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft and other accessories. P. & P. 85p.

MAINS INTERCOM NEW MODEL
 No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £89.24 per pair. P. & P. 85p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £12.95 + VAT £1.04
 Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates on/off switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. Volume. Direct tape recording model at £13.95 + VAT £1.12 P. & P. 75p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PE11)
 169 KENSINGTON HIGH STREET, LONDON, W.8

TANDY
START 'EM RIGHT WITH SCIENCE FAIR P-BOX KITS

IC MW RADIO KIT
 Like all Tandy P-Box kits, they build the 'pro' way—by 'bread-boarding'. Easy to follow instructions aid in building a great MW sound from speaker or plug-in earphone.



3-TRANSISTOR SW RADIO KIT
 Brings you the world on 4.5-50 MHz.
NEW LOW £6.99 PRICE

MORE EXCITING P-BOX KITS

MORSE CODE KIT (28-105)	£3.29	NIGHT LIGHT KIT. (28-126)	£1.99
SIREN KIT (28-107)	£3.99	BURGLAR ALARM KIT. (28-128)	£4.69
PHONE BOOSTER KIT (28-116)	£4.99	ELECTRONIC ORGAN KIT. (28-101)	£4.95
ELECTRONIC METRONOME (28-118)	£2.95	METAL LOCATOR KIT. (28-134)	£4.99
"GOOPY LITE" FLASHER KIT (28-130)	£3.99		

Batteries necessary for all kits are extra. All offers subject to availability.

P-BOX-KIT VOUCHER
 (as advertised)

Name _____
 Address _____

£1 OFF

FOR TANDY
Pat. Powell

Fill in your name and address and take this voucher to any Tandy store. It's worth £1 off any P. Box Kit advertised above. 1 per customer. Offer ends 30.11.76

Available from any of our 150 stores,

TANDY
 Nationwide supermarket of sound!



RECEIVERS AND COMPONENTS

250 WATT AMPLIFIERS

250 W into 4 ohms (300 V peak), 140 W into 8 ohms. 0.1% distortion. 130 dB signal to noise ratio. Very reliable. Single +140 V power supply.

Circuit board and instructions £2.25
Components and heatsink kit £18.50
120 W Power Amplifier. 120 W into 8 ohms. 0.1% distortion. 130 dB signal to noise ratio. Single 140 V power supply.
Circuit board and instructions £2.00
Components and heatsink £14.50

Electric Guitar preamp. 7 Transistors. Two inputs, Volume, Bass, Treble and treble boost controls.
Circuit board and instructions £1.20
Components kit £6.50

Microphone preamp for microphones of 200 ohms to 50k. Very low noise. Will take overloads of up to 300mV without distortion. Ideal for stage use or for mixers.
Circuit board and instructions £1.00
Components kit £2.90

GRAPHIC EQUALIZER

21 Transistors. Distortion 0.05%. Boost and cut ± 15 dB. Input 500mV — Output 1V (up to 3V). Components, circuit board and slider controls for 5 bands £9.50 9 bands £15.20 27 bands £40.50
Prices include taxes and postage in UK. Note — the kits do not include cabinets.

For more details on these kits and tone controls, power supplies, HiFi preamps, etc., send two 8p stamps or 17p for catalogue. (Outside UK free)

ALFA ELECTRONICS

(Mail Order Only)

96a Glengall Road, London, N.W.6

VALVES, RADIO, TV, TRANSMITTING, INDUSTRIAL. 1930 to 1975. 2,200 types in stock, many obsolete. List 20p. Quotation S.A.E. Postal export service. We wish to purchase new and boxed valves. Dealers, wholesalers, etc., stocks purchased. COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. Tel. West Wittering 2023.

R. T. SERVICES

(MAIL ORDER ONLY)

75 Hayfield Road, Salford 6 Lancs.

FM TUNER with R.F. Stage and A.G.C. 3 transistors, neg. earth $2\frac{1}{2} \times 2 \times 1\frac{1}{2}$ inch with circuit, £1.75.

Memory Array Panel. £1.50 inc. VAT, P. & P.

P.C. Board S/S, $5\frac{1}{2} \times 5\frac{1}{2}$ inch 10 for £1.25, P. & P.
Mixed Pack of C280 series Mullard capacitors, 100 for £1.15 inc., P. & P. Send S.A.E. for our list prices.

Tel. 061-236 1541

All prices include VAT and P. & P.

COMPONENTS BRAND NEW, fully marked, full spec. BC107/109 9p, IN4002 5p, IN4005 6p, 1600/10 15p, 2200/16 18p, 1000/25 15p, 250/64 12p, prices inclusive of VAT. Send for free list to—THOMPSON ELECTRONICS, 105 Park Road, Adlington, Chorley, Lancs. PR7 4JW.

SMALL ADS

The prepaid rate for classified advertisements is 15 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £12.00 per single column inch (2.5cm). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

SOUTH AFRICAN HOBBYISTS

FOR ALL YOUR COMPONENT REQUIREMENTS WRITE TO
SEFRA TV & ELECTRONICS
P.O. BOX 415 SILVERTON 0127
FOR QUOTE BY RETURN POST

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate cash settlement.

Precision Polycarbonate Capacitors

All High Stability—extremely Low Leakage				80V D.C. RANGE			
Value	Dimens-	Price		Value	Dimens-	Price	
(μ F)	(mm)	each		(μ F)	(mm)	each	
L	D			L	D		
0-1	27	12-7	88p	0-01-0-2	11-28	75p	50p
0-15	27	12-7	80p	0-22-0-47	11-32	77p	51p
0-22	33	16	88p	0-68	11-44	84p	56p
0-25	33	16	88p	1-0	11-56	91p	60p
0-33	33	16	99p	1-5	11-68	1-18	67p
0-47	33	19	11-10	2-2	11-98	1-32	75p
0-5	33	19	11-10	3-3	12-40	1-60	99p
0-68	50-8	19	11-25	4-7	12-88	1-88	1-25
1-0	50-8	19	11-27	10	14-98	2-32	2-01
1-5	50-8	25-4	11-64	15	17-14	2-76	2-88
2-0	50-8	25-4	11-95	22	19-66	3-44	3-90

TANTALUM BEAD CAPACITORS—Value available: 0-1, 0-22, 0-33, 0-47, 0-68, 1-0, 2-2, 3-3, 4-7, 6-8 μ F at 16V/26V or 35V; 10-0 μ F at 16V/20V or 26V; 22-0 μ F at 6V/10V or 16V; 33-0 μ F at 6V or 10V; 47-0 μ F at 3V or 6V; 100-0 μ F at 3V. All at 12p each, 10 for £1-10, 50 for 45, 100 for 49p.

TRANSISTORS & I.C.'s

BC107/8/9	8p	BC212/212L 18p	2N3055	50p
*BC114	12p	*BC213/213L 11p	OC71/2	90p
*BC147/8/9	10p	*BC214/214L 11p	*NE555/Timer 61p	
*BC153	18p	*BF194/5	12p	*741C 8pin DIL
*BC154/7/8/9	12p	BFY60/1/2	20p	32p
*BC182/182L 11p	AFY178	40p	ZN414	11-16
*BC183/183L 11p	AF235	38p	BN76013ND	
*BC194/184L 18p	*2N3079/4	11p		11-60

POPULAR DIODES—IN414 8p, 6 for 45p, 18 for 90p; IN916 8p, 6 for 45p, 14 for 90p; 1844 5p, 11 for 60p, 26 for £1-00, IN414S 5p, 6 for 27p, 12 for 45p; 1N4001 5p; 002 6p; 003 5p; 004 7p; 005 7p; 006 8p; 007 8p.
LOW PRICE ZENER DIODES—400mV, Tol. $\pm 5\%$ at 5mA. 3V; 3V3; 3V6; 4V; 5V; 5V6; 6V; 6V8; 7V6; 8V; 8V; 10V; 11V; 12V; 13V; 13V5; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each, 6 for 38p, 10 for 65p, 50 for 23-12. SPECIAL OFFER: 100 Zeners (may be mixed) for 26-00.

RESISTORS—High stability, low noise carbon film 5% \pm W at 40°C, \pm W at 70°C. E12 series only—from 2-20 to 2-2M Ω . ALL at 1p each, 8p* for 10 of any one value, 70p* for 100 of any one value. SPECIAL PACK: 10 of each value 2-20 to 2-2M (750 resistors) 65p.

SILICON PLASTIC RECTIFIERS—1.5 amp, wire-ended DO27: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).
BRIDGE RECTIFIERS—24 amp; 200V 40p; 350V 45p; 600V 65p.

SUBMINIATURE VERTICAL PRESETS—0-1W only: All at 8p each; 50; 100; 220; 470; 680 ohm; 1k; 2k; 4k; 7k; 10k; 15k; 22k; 47k; 100k; 320k; 680k; 1M; 2M; 5M.
PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with * which are 12 $\frac{1}{2}$ %.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. P.3)

The Old School, Edgaston, Wem, Shropshire
Tel: Whitchell 464/465 (STD 094 572)
(Propra. Minicost Trading Ltd.)

MINIATURE RESISTORS CARBON FILM.

5% E12 Series \pm W, \pm W, \pm W. Mixed values and wattages to your choice. 100 for 90p, P. & P. 15p. CANDAR, Freepost, Reading RG1 1BR.

PANEL WITH 10 SCRs 200V 1A, 12 Trans., 12 Ferrite Cores, etc. £1 (25p). T.V. CONVERGENCE PANEL 2 x AC 128, 3 Slugged Coils, 3 Slide Switches, 11 W.W. Pots, 3 Carbon Presets, 2 Ferrit Chokes, etc. £1 (50p). 5 FIGURE RESETTABLE COUNTER 1822M, works on 12V. £2.50 (50p). COPPER CLAD P.A.C. PANELS 17 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ " 90p, 5 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " 6 for 85p, 12 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ " 60p. FIBRE GLASS 13 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " 80p, 13 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ " £1.50. D.S. + 10%. All C.P. List 15p. Refund on purchase. 71b Assorted Components £2.60 C.P.

J. W. B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage In Brackets Mail Order Only

SOLARTRON CD7118 dual beam oscilloscope, incl. circuit, £25 plus carriage. Part-built CT 436, 10MHz dual beam, with circuits, parts to complete, offers 3kV isolating transformer, 120/240V in, 120/240V out, offers 25 computer panels (250 transistors) £3. DIL ICs, ex-computer, 90% good, 20 for 40p, data available —J. PAWSON, 4 Koim Crescent, Bathgate, W. Lothian.

RELAYS ENCLOSED PLUG-IN TYPE, 220/240V

a.c. 3 c/o contacts, complete with 11-pin base. 75p each, plus 20p post.

FLATPACK, for p/c mounting 24V d.c. 1 c/o contact, 50p each, plus 10p post.

OPEN TYPE, 220/240V a.c. 3 c/o contacts. Single hole fixing, 35p each, plus 15p post.

REED SWITCHES, one n/o plated contact. Approx 1in. long, 50p per 25, plus 10p post.

PACKS OF P/C PANELS, containing in excess of 700 usable components, transistors, SCRs, diodes, etc., and including encapsulated relays, also transistor stabilizer for power supply, £5-80 per pack, plus £1 post.

CONSTRUCTOR'S KIT, comprising components, hardware, relays, etc. Numerous new and part used items, £5-40 per pack, plus £1 post.

MICRO SWITCHES, button, roller, low torque, latching, etc., mixed lot, 10 for £1-50, plus 50p post.

PROCESS TIMERS, adjustable 1-100 seconds, 24V operation, includes triac switch with reset facility, £1 each plus 35p post.

PROGRAM TIMERS, suitable for lighting displays, etc., compete with C/O micro switches, are fully adjustable operating range, 50V a.c. operation. 6 cam model, £2-50 each. 12 cam model, £4 each. Plus 60p post.

All prices inclusive of VAT; all items tested ex-equipment except where stated. Cash with order, minimum order value £3.

B. A. JONES (ELECTRONICS)

39 Ashgate Valley Road, Brockwell

Chesterfield, Derbyshire

SPECIAL OFFER

1-ZN1040E inc. data £6

2-ZN1040E inc. data £11

1-1040E(R) unmarked reject of above

Counts/Displays/Reset OK £2-75

7489 fully functional 64 bit. Read/write

memory-speed failures 1 @ 75p; 2 @ £1-30;

3 @ £1-65; 4+ @ 50p each.

All prices inclusive (mail order only)

GJD ELECTRONICS, 105 Harper Fold Rd.,

Radcliffe, Manchester M26 0RQ

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 85V, 50V—0.47, 1.0, 2.2, 4.7 and 10mF 5p; 22, 47 5p (50V 6p); 100 7p (50V 8p); 220 8p (50V 10p); 500 11p (50V 16p); 1,000 (16V) 15p, 1,000 (25V) 18p, 1,000 (50V) 22p.

Subminiature Tantalum Bead Electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 at 35V, 4.7/25V 11p; 10/25V, 22/16V, 47/16V and 100/16V 15p.

Mullard Min. Ceramic E12 Series 63V 2%—10-47F 8p; 66-330pF 4p. Ceramic plate 60V E12 series 22-1,000pF and E6 series 1,500-47,000pF 5p.

Polystyrene E12 Series 63V Horizontal Mounting—10-1,000pF 3p; 1,200-10,000pF 4p.

Mullard Polyester 250V Vertical Mounting E6 Series—0.01-0.1 4p; 0.15, 0.22 5p; 0.33, 0.47 5p; 0.68 11p; 1.0 15p; 1.5 20p; 2.2 22p.

Mylar (Polyester) Film 100V Vertical Mounting—0.001, 0.002, 0.005 3p; 0.01, 0.02 3p; 0.04, 0.05 4p.

Miniature Resistors Highstab. E12 Series 5%—Carbon Film 1/4W 1Ω-10MΩ (10% 1M up) 1p; Metal Film 1/4W 10Ω-2MΩ 1.5p; Metal Film 1/4W 10Ω-2MΩ 1.5p; Metal Film 1W 27Ω-10MΩ 1.75p.

1N4148 8p; 1N4002 5p; 1N4006 7p; 1N4007 8p; BC107/8/9, 147/18/9, 157/18/9, BF194/7 9p.

Fuses 20mm glass, 1 1/2in glass, 1in ceramic 2p. Post 10p (free over £4). Prices inclusive of VAT.

THE C.R. SUPPLY CO.
127 Chesterfield Road, Sheffield S8 0RN

7413 TTL 19p
741 OP AMP 19p
1μF Poly 8p

Single Pole 12 way wafer switch 25p

Please add 8% VAT. P. + P. 15p on all orders

NORTH WALES ALARMS LIMITED
Parc House, Llidiart-y-Parc
Corwen, Clwyd LL21 9EL

LED S

	0-125	0-2	INFRA RED 550uW Axial lead 40p
RED	15p	19p	6mW E1-55 OPTO Data free
G/Y	27p	33p	
OR	27p	33p	ORP12 55p

panel clip 1p

OPTO-ISOLATORS

TIL111 1-5kV, 150kHz 11	SCR's 50V 100V 400V Diac	
4350 2-5kV, 5MHz 12-25	TOS 1A 25p 27p 40p BR100	
Avdelbond 2gm 8p	TO66 3A 27p 35p 50p 21p	
	400V TRIACS 2A 40p 10A 11-90	

VOLTAGE RES.

AC125/6/7/8 15p	2N2926(G) 12p	5V 7805 Plastic
AD161/162 40p	2N3053 15p	12V 7812 1 Amp
AF117 20p	2N3054 45p	15V 7815 all
AF124/5/6/7 34p	2N3055 41p	18V 7818 1.5
BC107/8/9 9p	2N3702/3/4 12p	723 DIP14 50p
BC108/7 12p	2N3930/3/4/5/6 16p	
BC147/8/9 10p	2N2846 35p	
BC157/8/9 11p	TI543 25p	BRIDGE RECTS.
BC167/8/9 11p	MPF102 40p	2A 50V 30p
BC169C 12p	2N3819 25p	2A 100V 36p
BC177/8/9 17p	2N3823 30p	2A 200V 41p
BC182/3/4/L 11p		2A 400V 46p
BC212/3/4/L 12p	IN914 3p	555 Timer 60p
BCY70/71/72 13p	IN4001 5p	556 2 x 555 11-10
BF194/5 12p	IN4002/3 6p	LM380 11-00
BF198/7 14p	IN4004/5 7p	7400 16p
BFY50/51 16p	IN4006/7 8p	
BFY29 30p	IN4148 4p	OP. AMPS
BFX84 24p	BA100 9p	709 all 25p
BSX19/20 16p	BY127 16p	741 8-pin 29p
OC71 10p	OA47 6p	748 D.I.L. 36p
2N706 10p	OA70 OA79 8p	
2N1711 20p	OA81 OA90 7p	D.I.L. SOCKETS
2N2219 20p	OA91 OA95 6p	9-pin 12p
2N2904/5/6/7 16p	OA200 6p	14-pin 13p
2N2904/5/6A 18p	OA202 7p	16-pin 14p
2N2926(R) 7p	ZENERs 2-7-33V	Mica + bushes
	BZY88 or sim 8p	TC3 TO88 5p
		Dalo Pen 70p

PRICES INCLUSIVE + 15p P. & P. (1st class)

ISLAND DEVICES, P.O. Box 11, Margate, Kent

Each of the following Packs of Manufacturers' Supplies, £1 inc. post, 3 1/2 toy motors; 3 of 4,700μF 10V; 10 red, black or yellow 500 ohm terminals; 10 of 100μF 35V; 10 of 250 or 500 ohm 8W; 10 BZ785e 3V; 10 1N4001s; 2 DPDT toggles; 3 SPST toggles; 1 transformer to 6 + 6V 3 + 3W; 10 of 1N4733; 10 black pointer knobs; 15 of 1μF 63V; 20 mixed banana plugs—yellow, black, red; 1 tough black PVC box 9 x 8 x 3in with lid and screws; 10 of BFY51; 10 mixed 4mm sockets—red, black, blue and yellow; 5 plastic 5V stabiliser ICs; 3 ORP93 photo cells; 5 bridge recs., 1A 400V; 3 three-pole thin tip jack sockets; 4 MVR 5V stabilisers; 5 500kΩ twin slider pots; 2 plastic cases with lid and screws 4 1/2 x 2 1/2 in.

Larger Items: 1mA meter movements scaled 0-10 22p; 7 x 5 x 2in socket boxes containing partly completed "halo" music modules, 22; Complete "top-boost" modules 25; Wahwah modules optical control 26; 4-input mixer modules 25; Akai reel-to-reel and cartridge recorder-player with reel to cartridge transfer facility, 290; 3 stereo channel mike mixer, prototype, 23; 70cm transmitter amplifier with knockup heater and HT supply, 25; 35mm camera 24; 110 camera 24; electronic flashgun 22. Crystals: 17.5 to 18MHz HC25U, 50p; 53-275MHz HC18U, 50p.

TRISAGION LTD., Dall, Rannoch, Perth PH17 9QH
State second choice or cash returned when sold out

Silicon Solar Power Cells: 1/8c typ. 500mA £1-25; 250mA 80p; 100mA 40p; 5mA 20p. Blue Response Cells: 1 sq.cm 80p. Photo-Diodes: MS1AE £1-20, MS4B £1-20, MS9AE £1-20. Photo-Switches: 5V 4 pin ext. R-C, ZNPF08/109 21. Photo Trans: ZMX141 55p, BPX25 21, BPX29 21. Photo-Dart: ZMX140 60p.

10 off ZTX108 50p; 10 off ZTX212A 50p; 10 off BC307L 50p.

10W Zeners Branded 18V, 27V, 56V, 20p each.

Bargain Packs: tested and g'teed, 50p each. 8 off 50V 8A rect.; 8 off 100V 8A rect.; 6 off 200V 8A rect.; 10 off 50V 1.5A rect.; 10 off 200V 1.5A rect.; 20 off n.p.n. gen. purp. trans.; 20 off p.n.p. silicon trans.; 4 off 2kV diodes; 12 off assorted voltage DO-7 diodes 400mV; 15 off 400mV zeners, 5 voltages; 10 off double diodes; 7 off photo trans; 5 off photo lead; 7 off I.R. L.E.D.; 20 off 50V 1.5A metal rect.; 15 off 200V 1.5A metal rect.; 10 off 800V 1.5A metal rect.

Photo-Switches: Manufacturers' downgrades, 40p each, 3 for £1.

C.W.O. P. & P. 20p. All prices inclusive of VAT.

P. A. ELECTRONICS
21 Kendal Drive, Shaw, Oldham, Lancs.

COMPONENTS AND HARDWARE—FAST.
Free catalogue and samples. Send 2 x 6p stamps—MAGENTA ELECTRONICS LTD., PE10, 61 Newton Leys, Burton on Trent, Staffs. DE15 0DW.

SITUATIONS WANTED

MRC NEUROLOGICAL PROSTHESES UNIT TECHNICIAN

to help develop and maintain Neurological Prostheses (i.e. electronic therapeutic systems, parts of which are surgically implanted). The work is carried out both in the laboratory and in patients' homes. The successful applicant will have initiative, an enthusiasm for electronics and an ability to get on with people. Any specialist training necessary will be given.

Candidates should possess an HNC or University degree or City and Guilds Full Technological Certificate in a relevant subject. Salary on a scale rising to £3738 p.a.

Apply in writing to:

The Director,
MRC Neurological Prostheses Unit, Institute of Psychiatry, De Crespigny Park, London SE5
marking the envelope M.T.

EDUCATIONAL

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 771Z, Intertex House, London SW8 4UJ
Tel. 01-622 9911 (all hours)

RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination, and obtain your G8 licence, with an R.R.C. Home Study Course. For details of this, and other courses (G.C.E., Professional Examinations, etc.) write or phone: **THE RAPID RESULTS COLLEGE**, Dept. J31, Tulliton House, London, SW19 4DS. Tel. 01-947 7272 (Careers Advisory Service) or for a prospectus only ring 01-946 1102 (24 hr. recording service).

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 771Z, Intertex House, London SW8 4UJ
Tel. 01-622 9911 (all hours)

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners, with GCE (or equivalent) in Maths & English.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on January 3rd.

Prospectus from **London Electronics College, Dept. A11, 20 Penywern Road, London SW5 9SU.** Tel. 01-373 8721.

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 771Z, Intertex House, London SW8 4UJ
Tel. 01-622 9911 (all hours)

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc., 50p and S.A.E. Catalogue 20p and S.A.E. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, radio, TV, etc., 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. **TELRAY**, 154 Brook Street, Preston, PR1 7HP.

BELL'S TELEVISION SERVICES for service sheets on radio, TV, etc., 75p plus S.A.E. Colour TV service manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

FOR SALE

NEW HEATHKIT Oscilloscope, Model 10-4540. Six months of guarantee left, complete with manual £100—Box 65.

P.W. 1949-76, P.E. 1964-76 15p each plus P. P. S.A.E. to—**RUTHERFORD**, 41 Anzio Close, Aldershot, Hants.

ENTHUSIAST DISPOSING £100 WORTH unused assorted components for £30—01-998 9799.

SYNTHESIZER: Minisonic Mark II. Fully built to spec. with 4-octave Kimber Allen Keyboard and Eaton Audio p.e.b., 200p o.n.o. Tel. 01-458 2106 evenings.

DISCOLIGHTS: 3-chan soundlights £17.50! Strobes £22! Full catalogue from—AARVAK ELECTRONICS, 12a (L) Bruce Grove, London N17. (01-808 8923).

WANTED

WANTED PRACTICAL ELECTRONICS. Complete set, volumes 1 to 11 inclusive, bound volumes preferred—Box 66.

WANTED, NEW VALVES, TRANSISTORS, top prices, popular types—KENSINGTON SUPPLIES (B), 387 Kensington Street, Bradford 8, Yorkshire.

WANTED, MINISONIC or similar small working synthesiser less keyboard—061-764 6591 evenings, Mr. Howard.

BOOKS AND PUBLICATIONS

START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc., etc. A goldmine of information and knowledge. Only £3.90 plus 26p P. & P. From:

MAGNUM PUBLICATIONS, Dept. PE5
Brinkway Trading Estate, Brinkway
Stockport SK3 0BZ
Overseas Distributors wanted.

Theory and practice of MODEL RADIO CONTROL

2nd edition with latest circuitry Development of proportional digital systems explained. Gives practical examples of a modern digital system transmitter-receiver-decoder and servo's.

£2.25 plus 35p P. & P. C.W.O.

SAE for lists to:

D. J. & D. MODEL GEAR
58 Lowther Grove, Garforth,
Leeds LS25 1EN

FREE T.V. CIRCUIT DIAGRAMS

All main British T.V. sets (plus many foreign) comprehensively covered in our easy-to-follow T.V. Repair Manuals—4 mono and 3 colour. Just send model no., if colour (mfrs. chassis type helps) with £4.50 and receive the manual covering your set—plus your set's circuit diagram on request free. Set of 7 only £27.

British T.V. Circuit Diagram Manuals—the main mono (over 37 series) for £9.90 and virtually every colour for £17.50. Full details of these and other publications from:

T.V. TECHNIC

76 Church Street, Larkhall, Lanarks, ML9 1HE
Tel. (0698) 883334

LADDERS

LADDERS, varnished, 20ft. 9in. extd., £20.50. Carr. £1.90. Leaflet, Alloy ext. and loft ladders. **Immed. despatch. THE LADDER CENTRE (PRE)**, Halesfield (1), Telford, Salop. Tel. 686644. Order C.O.D.

MISCELLANEOUS

LIGHTING CONTROL UNITS

Sound to Light, Quality 3 channel display control (1&W per channel) is designed for ruggedness, safety and simplicity of construction. The kit includes individual sensitivity controls and the unique 1/2 intensity dimming control. **KIT PRICE £18.90** (incl.). Bypass switches, 25p each (3 required).

Strobe/Flasher Control Unit. KIT £7.50. Pre-built £9.90. Flash rate. 20 ft/sec. to 2 ft/min. Flash on time variable.

Other kits and modules for discos, shops & theatres available. Order or write for details from:
SELEKTRON, 21 Priors Rd., Windsor, Berks. SL4 4PD

COIL WINDING SERVICE. Contact—EMS, 21 Mount Road, Benfleet, Essex SS7 1HA.

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Recess Handles, Strap
Handles, Feet, Castors, Locks and Hinges,
Corners, Trim, Speaker Bolts, etc., etc.
Send 2 x 8ip Stamps for samples and list.


ADAM HALL (P.E. SUPPLIES)

Unit G, Starline Works, Grainger Road
Southend-on-Sea, Essex.

RECHARGEABLE NICAD BATTERIES. Pencil, AA 94p; Sub. "C" £1.16; "C" £1.92; "D" £2.59; PP3 £4.48. Chargers: £4.48, £4.48, £4.98, £4.98, £3.98 respectively. Others available. All prices include VAT. Add 10% P. & P. S.A.E. for price list plus 25p for information booklet. **SANDWELL PLANT LTD.**, 1 Denholm Road, Sutton Coldfield, West Midlands. Tel. 021-854 9764.

BUILD THE TREASURE TRACER

MK III Metal Locator

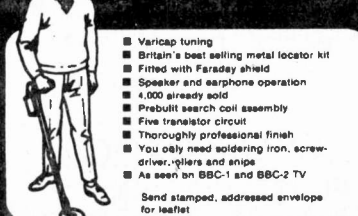

- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete Kit Post 85p = £12.50 (incl. 8% VAT) Built and tested Post 85p = £17.50 (incl. 8% VAT)

MINIKITS ELECTRONICS, 69 CLEVELAND ROAD LONDON E18 2AN (Mail Order Only)

ENAMELLED COPPER WIRE

S.W.G.	1lb reel	1/2lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All the above prices are inclusive of postage and packing in the U.K.

COPPER SUPPLIES

102 Parrswood Road, Winton,
Manchester 20
Telephone 061-445 8753

LOW COST I.C. MOUNTING for any size DIL package. 100 Soldercon sockets 65p. 7 and 8 hole plastic supports 5p/pair. Quantity rates. S.A.E. details and sample. Trial pack 65p (P. & P. 10p/order). **PKG ELECTRONICS**, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

Musical Miracles!

by Dewtron®

Build your own synthesiser or musical effects using some of the huge range of DEWTRON modules. Or, build fuzz or wah-wah at budget prices using special kits.

Send 20p for Catalogue from:

D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AR.

PUBLIC ADDRESS ENGINEERING!

Find out more, join the Association of Public Address Engineers—Details from:

**The Secretariat
APAE
47 Windsor Road
Slough, Berks.**

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy-duty pvc faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 82p. Examples: width, depth, height, 8in. x 5in x 3in, £1.70; 10in x 6in x 3in, £2.42; 10in x 8in x 3in, £3.02; 12in x 10in x 3in, £3.96; 8in x 4in x 4in, £1.98; 10in x 6in x 4in, £2.97; 12in x 8in x 4in, £3.98; 7in x 7in x 5in, £2.91; 8in x 10in x 6in, £3.96; 12in x 8in x 7in, £4.40; 12in x 12in x 7in, £4.84. Plus 85p carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated): **BAZELLI**, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

TRANSMIT!

★ **Unique TRANSMITTER RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £7.95 plus 20p P. & P.

★ **Psychedelic MINI-STROBE** Kit. Take a pocket-sized lightning storm to Discos and parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £3.50 plus 20p P. & P.

(All prices include V.A.T.)

Send remittance to:

**BOFFIN PROJECTS
4 CUNLIFF ROAD
STONELEIGH, EWELL, SURREY**
(Mail order U.K. only)

Or for more details, send 20p for lists

PRINTED CIRCUIT BOARDS in Glass Fibre, drilled with a soldering varnish finish (6p per sq. in.) or tinned (8p per sq. in.) P. & P. 30p—**R. F. DARLISON**, 1 Valentine Drive, Oadby, Leicester.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs.

Prompt service.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
Masons Road, Stratford on Avon
Warwicks. Tel. 4879

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

H.M. ELECTRONICS

275a Fulwood Road, Broomhill, Sheffield S10 3BD



Give your project that professional looking finish. Build it in a BEC.

Dry transfer lettering now available...

BEC CABINETS

ORION cabinet still available punched or unpunched. Send 15p (refundable) for leaflets.

KNOCKDOWN PRICE TO CLEAR: £2 inc. pots for a partly completed Electronic Music Module in strong metal box 17 x 12 x 6cm, with printed circuit, pots, jack sockets, IC's, transistors, etc. Clear Plastic Sheet, stiff, 1mm thick, any rectangle up to 35 x 50cm, 30 sq.cm for 1p. plus post 11p. Oscar Satellite Predictor, pins to shack wall and shows time and longitude of 7 successive equator crossings, 70p inc., post. S.A.E. for lists please. **TRISAGION LIMITED**, Dall, Rannoch, Perth (08822 379 most evenings.)

MORSE IMPROVEMENT

C90 Cassettes

1-12 wpm with simple exercises.
12-24 wpm Computer produced professional level operator material including international symbols.

Price: complete with instruction and exercise booklets £4 each including postage. Overseas £1 extra.

Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation. Price £3 including postage. Overseas £1 extra.

MHEL Electronics

12 Longshore Way, Milton
Portsmouth, (UK) PO4 8LS

12 VOLT FLUORESCENTS

35% OFF
RRP

MADE BY THORN LIGHTING. Ideal for Caravan, Boat, Tent, Emergency Lighting etc. All lamps guaranteed for 12 months.

21 watt
13 watt
£4.90



12 watt
8 watt
£4.00

All lamps have On/Off Switch, Wrong Polarity Protection Device and Diffuser.

C60 CASSETTES 22p
C90 CASSETTES 45p

All Cassettes in Plastic Case with Index and Screwed Assembly.

All prices include VAT. Add Postage 5p in £1.
Quantity Discounts:
10 Units 5%
50 Units 7%
100 Units 10%

SALOP ELECTRONICS
23 WYLE COP
SHREWSBURY
Tel. 53208

COLCHESTER'S COMPONENT SHOP open
Sunday-Friday, 12-6 p.m. J. K. ELECTRONICS, 11 Mersea Road, Tel. 64433.

WERSI ORGAN KITS

BUILD YOUR OWN WERSI ELECTRONIC ORGAN
as played by KLAUS WUNDERLICH

These superb German WERSI kits for ORGANS, PIANOS, TONE CABINETS and PROFESSIONAL AUDIO equipment, now available for D.I.Y. assembly and CUSTOM BUILT, direct from U.K. WERSI agents.

Electronic Services (Stroud) Ltd.
21 Mount Hill Rd., Hanham, Bristol BS15 2QU
0272 671312

I.C. EXPERIMENTER'S KITS

Learn about modern electronics with our new series of Kits on digital logic techniques. Each Kit contains specially selected I.C.s, Holders, Veroboard, L.E.D.s, and Instructions. Available at £3.50 each (including P. & P.)
Kit One—Gates Kit Two—Flip-Flops
Kit Three—Shift Registers
Kit Four—Counters Kit Five—Displays
S.A.E. for further details to:
AUTOMATED HOMES
69 High Street, Ryton, Coventry CV8 3FJ
(Mail Order Only)

GLASS FIBRE P.C.B.'s

From your own tape, film or ink master.
Send S.A.E. for quotation.

PRACTICAL ELECTRONICS printed circuit boards in glass fibre, drilled and tinned.
June 76 Transmitter 93p., Coder 84p.
July 76 Receiver 90p., Decoder 73p.,
Interface 56p., August 76 Servo Drive 69p.,
Servo Amp 54p., Relay Driver 62p.
Complete set of above boards £5.30.
Sept. 76 Tone Generator 66p., Tone Decoder 72p.
May-June 76 Digital Frequency Meter.
Complete set of 4 boards £4.20 C.W.O. please.

PROTO DESIGN

4 Highcliffe Way, Wickford, Essex SS11 8LA

AN INVALUABLE COMPANION FOR ANY CALCULATOR

ELECTRONIC CALCULATOR USER'S HANDBOOK

by M. H. Babani, B.Sc.(Eng.)

No. BP33 208 pages 4½ × 7½. **95p**

Provides instant reference formulae, data, methods of calculating conversion factors, also how to calculate trig and hyperbolic functions, logs, power and sq. roots using only four function calculators. (ISBN 0 85934 036 8)

HOW TO BUILD YOUR OWN METAL & TREASURE LOCATOR

by F. G. Rayer, T.Eng.(CEI), Assoc.I.E.R.E.

No. BP32 96 pages 4½ × 7½. **85p**

A most fascinating electronics application. Shows stage by stage how to make your own locator efficiently and inexpensively (0 85934 035 X)

OBTAINABLE FROM most large branches of W. H. Smith, good bookshops, component dealers, mail order houses, etc. S.A.E. brings complete list.

BABANI PRESS

The Grampians, Shepherds Bush Rd., London W6 7NF
01-403 7296/2581

LOW COST — HIGH EFFICIENCY AUDIO TEST OSCILLATOR £20



RANGE: 10Hz to 100kHz. OUTPUT: 1V, sine/sq. DISTORTION: less than 0.02%. 9V battery. Also available in Kit form at £16.50. Add 8% VAT. P. & P. and ins. 75p. Leaflet available. Also F.M. Signal Generator, Millivoltmeter, freq. meter, THD analyser, P.S. Units and high quality amplifiers.


TELERADIO ELECTRONICS
325 Fore Street, London, N9 0PE
Tel. 01-807 3719

LIMITED OFFER MM5314 full spec. with data, £2.65. Submin, toggle, SP, change over, 38p; miniature 5-way toggle 14.8 square, £1.75. 10p. P. & P.—L.B. 43 Westacott, Hayes, Middx. UB4 8AH.

ELECTRONIC KIT

Build, Dismantle and Rebuild Over 100 Different Projects and Design New Circuits too

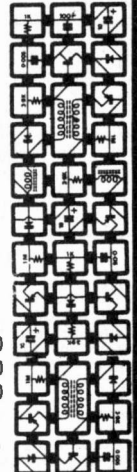Radio Receivers and Transmitters, Telephone Amplifiers, Time Buzzers, Battery Checkers, Computer Circuits, Amplifiers, Directional Transmitters, Metal Detectors, Continuity Testers, Electronics Birds, Guns, Metronomes, Sirens, Roulette, etc. All in one kit



"... educational kits of exceptional quality"

(Audio mag.)

"... worthwhile... good value for money"

(Everyday Electronics mag.)

Educational manuals included with each kit. No previous experience required. Suitable for beginners and experts too.

100 project kit £19.60

45 project kit £15.60

25 project kit £12.10

(Add-on kits available too)

Prices include manuals, batteries, VAT and P. & P.

Cheque/P.O. (or 11p for illustrated literature) to Dept. PE

Satisfaction guaranteed

ELECTRONIC-KIT LTD. 408 St. John's Street, London, E.C.1. (01-278 4579)

THE OPEN DOOR TO QUALITY



This catalogue—Electrovalue Catalogue No. 8 (Issue 2, up-dated)—offers items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts are allowed on many purchases; Access and Barclaycard orders are accepted.

* FREE POSTAGE on all C.W.O. mail orders over £2 list value (excluding VAT) in U.K. If under, add 15p handling charge.

144 pages
post paid


40p
inc. refund voucher worth 40p

All communications to Head Office, Dept. PE11/2, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 6WB. Phone Egham 3803. Telex 264475. Hours 9-5.30 daily; 1 pm Sat.
NORTHERN BRANCH: 608 Burnage Lane, Burnage, Manchester M19 1NA. Phone 061-432 4945. Hours 9-5.30 pm; 1 pm Sat.

ELECTROVALUE LTD


TTLs by TEXAS			C-MOS ICs			OP AMPS			Linear ICs			TRIACS			VOLTAGE REGULATORS (Plastic) Fixed			OPTO DEVICES			SCR-THYRISTORS			BRIDGE RECTIFIERS			DIODES			ZENERS			OTHER											
7400	17p	7494	80p	4000	18p	1458	75p	AC125	18p	BF198/7	18p	TIS43	40p	2N3806	18p	OC771	120p	1Amp +ve	1Amp -ve	OC770	33p	TIL209	Red	18p	1A 50V TOS	43p	1A 100V TOS	48p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p				
7400	30p	7495	75p	4001	19p	301A	40p	AC126/7	18p	BF200	40p	TIS93	38p	2N4080	12p	OC771	120p	5V 7805	150p	5V 7805	200p	OC771	120p	TIL211	Green	30p	1A 400V TOS	56p	1A 400V TOS	56p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
74LS00	32p	7496	85p	4002	19p	3130	100p	AC128	18p	BF244/B	40p	ZTX108	12p	2N4123/4	22p	OC771	120p	12V 7812	150p	12V 7812	250p	OC771	120p	TIL212	Infrared	75p	1A 400V Stud	81p	1A 400V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
74S00	48p	7497	250p	4003	19p	3140	100p	AC141/2	20p	BF257/8	36p	ZTX300	16p	2N4125/6	22p	OC771	120p	15V 7815	150p	15V 7815	250p	OC771	120p	TIL213	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
7401	18p	74100	110p	4007	19p	3800	110p	AC178	18p	BF39/40	34p	ZTX500	20p	2N4401/3	34p	OC771	120p	18V 7818	150p	18V 7818	200p	OC771	120p	TIL214	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
7402	18p	74104	80p	4009	87p	53E7	300p	AC187/8	20p	BFR79/80	34p	2N687	25p	2N4427	85p	OC771	120p	24V 7824	150p	24V 7824	200p	OC771	120p	TIL215	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
7403	18p	74105	80p	4011	19p	709	30p	AC187K	25p	BFR88	40p	2N688	34p	2N4487	85p	OC771	120p	LM309K (TO3)	5V 1A 150p	LM309K (TO3)	5V 1A 150p	OC771	120p	TIL216	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
7404	24p	74107	30p	4012	19p	741	25p	AC188K	25p	BFX29/30	34p	2N706/8	22p	2N5296	85p	OC771	120p	5V 3A 7809	150p	5V 3A 7809	150p	OC771	120p	TIL217	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
74H04	40p	74109	70p	4013	85p	747	70p	AD149	48p	BFX84/85	36p	2N918	43p	2N5296	85p	OC771	120p	7805 (TO3)	150p	7805 (TO3)	150p	OC771	120p	TIL218	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
7405	25p	74110	50p	4014	110p	748	40p	-AD181/2	30p	BFX86/7/8	30p	2N930	18p	2N5457/8	40p	OC771	120p	16 pin DIL	300p	16 pin DIL	300p	OC771	120p	TIL219	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p		
7406	45p	74111	80p	4015	120p	776	153p	AF114/5	20p	BFY50	18p	2N930	18p	2N5457/8	40p	OC771	120p	VARIABLE: 723	14 pin DIL	48p	VARIABLE: 723	14 pin DIL	48p	OC771	120p	TIL220	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7407	30p	74112	220p	4016	54p			AF116/7	20p	BFY51	18p	2N930	18p	2N5457/8	40p	OC771	120p							OC771	120p	TIL221	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7408	22p	74118	90p	4017	90p			AF124	27p	BFY52	18p	2N1131/2	25p	2N6027	60p	OC771	120p							OC771	120p	TIL222	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7409	22p	74120	95p	4018	120p			AF127	27p	BFY53	18p	2N1304/5	40p	2N6107	70p	OC771	120p							OC771	120p	TIL223	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7410	18p	74121	32p	4019	54p			AF127	27p	BFY54	18p	2N1306/7	40p	2N6247	200p	OC771	120p							OC771	120p	TIL224	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
74H10	30p	74122	53p	4020	120p			AF127	27p	BFY55	18p	2N1613	22p	2N6254	140p	OC771	120p							OC771	120p	TIL225	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7411	28p	74123	70p	4021	100p			AF127	27p	BFY56	18p	2N1711	22p	2N6292	70p	OC771	120p							OC771	120p	TIL226	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7412	28p	74125	70p	4022	18p			AF130	43p	BFY57	18p	2N1993	32p	2N6328	81p	OC771	120p							OC771	120p	TIL227	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7413	36p	74126	70p	4023	18p			AF130	43p	BFY58	18p	2N2160	80p	2N6328	81p	OC771	120p							OC771	120p	TIL228	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7414	85p	74128	90p	4024	75p			AF130	43p	BFY59	18p	2N2160	80p	2N6328	81p	OC771	120p							OC771	120p	TIL229	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7416	35p	74132	70p	4025	19p			AF130	43p	BFY60	18p	2N2219	22p	2N6328	81p	OC771	120p							OC771	120p	TIL230	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7417	36p	74136	81p	4026	200p			AF130	43p	BFY61	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL231	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7420	18p	74141	85p	4027	81p			AF130	43p	BFY62	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL232	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7421	43p	74142	300p	4028	152p			AF130	43p	BFY63	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL233	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7422	20p	74145	90p	4029	120p			AF130	43p	BFY64	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL234	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7423	36p	74148	170p	4030	50p			AF130	43p	BFY65	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL235	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7425	33p	74150	135p	4031	80p			AF130	43p	BFY66	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL236	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7427	48p	74151	77p	4032	80p			AF130	43p	BFY67	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL237	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7430	18p	74153	82p	4033	100p			AF130	43p	BFY68	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL238	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7432	30p	74154	180p	4034	100p			AF130	43p	BFY69	18p	2N2222	22p	2N6328	81p	OC771	120p							OC771	120p	TIL239	Infrared	75p	1A 50V Stud	81p	1A 50V Stud	81p	1N4001	4p	1N4002	8p	1N4003	8p	1N4004	7p	1N4007	8p	1N4148	4p
7437	33p	74155	87p	4035	54p			AF130	43p</																																			

SUPERSOUND 13 HI-FI MONO AMPLIFIER

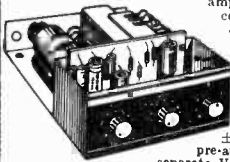

A superb solid state audio amplifier. Brand new components throughout. 3 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz $\pm 3dB$. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-16 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, esutchon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £13-75. P. & P. £1-00.

DE LUXE STEREO AMPLIFIER

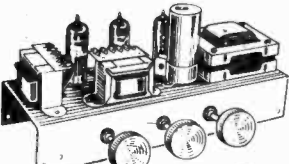

A.C. mains 200-240 v. Using heavy duty fully insulated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes, 1 x E230 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4 1/2". Overall height including valves 5". Ready built and tested to a high standard. £12-40. P. & P. £1-30.

HARVERSON STEREO 44



A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speaker. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier, smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" x 2 1/2" x 1" max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way esutchon (to allow the amplifier to be mounted horizontally or vertically), at only £7-50 plus 50p P. & P. Mains transformer with an output of 17V a/c at 500 mA can be supplied at £1-50 plus 40p P. & P. if required. Full connection details supplied.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-50V. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2-90. P. & P. 90p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240V. Sec. 0-0-3 at 500 mA. £1-50. P. & P. 60p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1-65. P. & P. 60p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2-35. P. & P. 90p. Pri. 200/240V. Sec. 23v. at 1.5 amp, 6v. at 6 amp, 8v. at 50 mA. £2-00 + 65p P. & P.

ALL PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested. Price £5-75. P. & P. 85p.


STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-500mV for 9-16V n.c. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5-62 plus 20p P. & P. Stereo beacon light if required 40p extra.



QUALITY RECORD PLAYER AMPLIFIER MK II A top quality record player amplifier employing heavy duty double wound mains transformer, EOC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in wide x 3in deep x 6in high. Ready built and tested. PRICE £6-20. P. & P. 90p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £7-30. P. & P. £1-00.

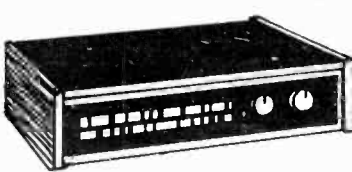HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER




Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to "lock on" station and prevent drift. IC stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2in wide x 9in deep by 2 1/2in high. Supplied ready built, fully tested and fully guaranteed. AC mains 200/240V (not available in kit form).

Special Offer £22-50 + £1-40 P. & P.

SPECIAL OFFERS

Mullard LPI169 RF-IF Double Tuned Amplifier Module for nominal 470kHz. Size approx. 2 1/2" x 1 1/2" x 1 1/2" 7-6V + earth. Brand new pre-aligned. Full specification and connection details supplied. £2-25 + P. & P. 12p.

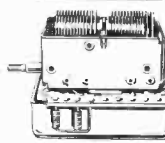Pye VHF/FM Tuner Head covering 88-108MHz 107MHz IF output 7-8V + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-gear FM Gang and 323 P1 + 323 P1 AM Tuning Gang only £3-15 + P. & P. 35p.



PRECISION MADE Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" x 2 1/2" x 1". Supplied complete with chrome finished switch buttons 2 for £1-60 + 20p. P. & P.

HI-FI LOUSPEAKER SYSTEM Mk II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which).

OUR PRICE £12-00 each. Carr. £1-90

Cabinet Available Separately £7-25. Carr. £1-40. Also available in 8 ohms with EM1 13" x 8" bass speaker with parasitic tweeter £10-25. Carr. £1-90

LOUDSPEAKER BARGAINS

5in. 3 ohm £1-45, P. & P. 35p. 7 x 4in. 3 ohm £1-69, P. & P. 48p. 10 x 6in. 3 or 15 ohm £2-50, P. & P. 75p. E.M.I. 8 x 6in. 3 ohm with high flux magnet £2-00, P. & P. 50p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £2-00 + 25p. P. & P.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS ap. 54 in. wide. Our price £1-50 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceiling, walls, etc. and used with or without baffle. Send S.A.E. for details. Only £2-40 each. P. & P. 75p for one, 90p for two.


Now also available 6"-8 ohm, 10 watt r.m.s., 20-watt peak 40 Hz-20,000 Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cars. £5-10 + P. & P. (one 35p, two 60p)

SPECIAL LINES OFFERED SUBJECT TO STOCK AVAILABILITY

Hi-Fidelity stereo cassette tape deck transport mechanisms as used in Hi-Fi Music Centres. Electronically speed controlled motor, belt-driven flywheel capstan, three digit resettable counter. Record/Play pre-amps. Bias oscillator. Record/Play and erase heads, etc. Power supply required 12V D.C. Circuit diagrams, etc. supplied. These units are brand new, but un-tested and are only offered to the more advanced constructor enthusiast. PRICE £16-87 + £1-25 P. & P. WE REGRET THAT WE ARE UNABLE TO ENTER INTO CORRESPONDENCE ON THESE UNITS.

New but very slightly marked 'GLENBURN' BSR automatic record changer decks fitted with cueing lever, lightweight arm and ceramic Hi-Fi stereo/compatible cartridge. Can be used for automatic or manual play. PRICE £9-56 + £1-20 P. & P.

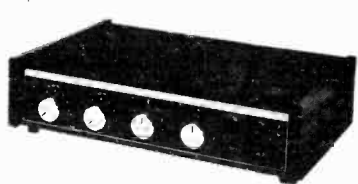
HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response $\pm 3dB$ 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: $\pm 3dB$ 12-15,000 Hz. Bass, boost approx. to $\pm 12dB$. Treble cut approx. to $-16dB$. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall size 12" w. x 8" d. x 2 1/4" h. Fully detailed 7 page construction manual and parts list with kit or send 25p plus large S.A.E. **AMPLIFIER KIT** £18-50. P. & P. 65p (Magnetic input components 33p extra) **POWER PACK KIT** £4-85. P. & P. 85p **CABINET** £4-85. P. & P. 85p

Special offer—only £22-50 if all 3 units ordered at one time plus £1-00 P. & P.

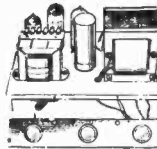Full after sales service Also available ready built and tested £29-25. P. & P. £1-00.




3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates EOC83, EL84, PZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7-80. P. & P. £1-00. **HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £7-00. P. & P. £1-00.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. SR Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EOC83, EFS8 and E230 rectifier. Simple instruction booklet 25p x SAE (Free with parts). All parts sold separately. ONLY £11-25. P. & P. £1-35. Also available ready built and tested £16-20. P. & P. £1-35.

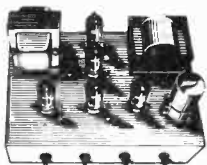

SPECIAL OFFER

Latest model Garrard 6300 Auto/Manual changer de luxe with cueing lever, bias compensator, counter-balanced low resonance arm and fitted with Acos 104 diamond ceramic stereo cartridge. PRICE ONLY £14-50 + £1-50 P. & P.

Limited number of the latest BSR C141R1 Auto/Manual changer de-luxe. Lightweight tubular arm cueing lever, bias compensator. PRICE £12-60 + £1-40 P. & P. ALSO similar but without cueing lever or bias compensator. ONLY £11-00 + £1-40 P. & P.

OUR PRICES INCLUDE VAT AT CURRENT RATES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9.30-5.30 Monday to Friday, 9.30-5 Saturday Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

HARVERSON SURPLUS CO. LTD.


(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

OPEN SESAME

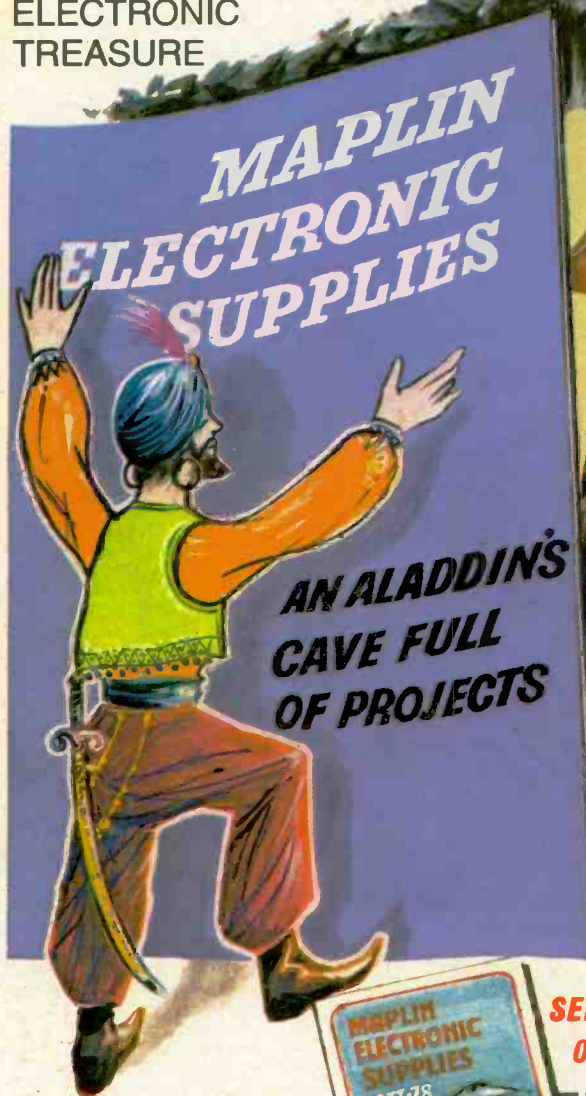THE MAGIC WORDS TO A HUGE CACHE OF
ELECTRONIC
TREASURE



**SEND THIS COUPON FOR YOUR COPY OF
OUR CATALOGUE ON APPROVAL!**

Publication date October 28th, 1976



For full details of the
projects shown above

**LOOK FOR THE
GENIE ON PAGE 854
OF THIS ISSUE.**

All new Completely re-written Hundreds of new lines.
Lots of exciting new projects to build—PRICE 50p.
SEND NO MONEY NOW. Overseas send 8 International reply coupons.

P.E.

Please rush me a copy of your brand new 1977/78 catalogue the instant it is published (October 28th, 1976) Only if I am completely satisfied that it is worth every penny will I send 50p within 14 days of receipt. If I am not satisfied I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____

ADDRESS _____

MAPLIN ELECTRONIC SUPPLIES, P.O. BOX 3, RAYLEIGH, ESSEX