

PRACTICAL

ELECTRONICS

APRIL 1978

45p

FUMBLE MUDGE *Game*



FREE! MARSHALL'S
40 PAGE
CATALOGUE
IN THIS ISSUE

EXTRA DESIGN
IDEAS

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS. CASH/CHEQUE/P.O. or BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 30p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

MINIMUM ORDER £2.00 PLEASE.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12½%. We stock many more items. Send S.A.E. for our free list. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am - 6.00 pm. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in µF)
400V. 0.001 0.0015 0.0022 0.0033 8p. 0.0047 0.0058 0.01 0.015 0.018 9p. 0.022 0.033 10p. 0.047 0.068 14p. 0.10 15p. 0.15 0.22 22p. 0.33 0.47 39p. 0.68 45p. 1.00V. 0.039 0.15 0.22 13p. 0.33 0.47 22p. 0.68 1.0 29p. 2.2 39p. 4.7 47p. **DUBILIER:** 1000V. 0.01 0.015 16p. 0.022 18p. 0.047 16p. 0.1 34p. 0.15 43p.

POLYESTER RADIAL LEAD (Values in µF) 250V
0.01 0.015 6p. 0.022 0.027 7p. 0.033 0.047 0.068 0.1 8p. 0.15 12p. 0.22 0.33 14p. 0.47 16p. 0.68 20p. 1.0 24p. 1.5 27p. 2.2 31p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF)
63V 0.47 1.0 1.5 2.2 2.5 3.3 4.7 6.8 8.0 10.0 15.0 22.0 29p. 47 32 50 12p. 63 100 27p. 50V 0.1 0.7p. 50 100 220 25p. 470 50p. 1000 2200 68p. 40V 0.22 33 9p. 100 12p. 3300 62p. 4700 64p. 35V 10 33 7p. 330 470 32p. 1000 49p. 25V 10 22 47 6p. 80 100 160 8p. 220 250 13p. 470 640 25p. 1000 27p. 1500 30p. 2200 41p. 3300 52p. 4700 54p. 16V: 10 40 47 68 7p. 100 125 8p. 470 16p. 1000 150 20p. 2200 34p. 10V: 4 100 6p. 640 10p. 1000 14p.

TAG-END TYPE: 70V: 2000 98p. 4700 121p. 50V: 3000 75p. 40V: 4000 70p. 2500 65p. 25V: 4700 48p. 2000 37p. 40V: 2000 - 2000 95p. 325V: 200 - 100 - 50 - 100 190p.

TANTALUM BEAD CAPACITORS
35V 0.1µF 0.22 0.33 0.47 0.68 1.0 2.2 3.3 4.7 6.8 25V 1.5 10 20V 1.5 16V 100µF 13p each 47 100 64p. 35V 10 33 7p. 47 6V: 47 100 3V: 68 100µF 20p each

MYLAR FILM CAPACITORS
100V 0.001 0.002 0.005 0.01µF 5p 0.015 0.02 0.04 0.05 0.06µF 6p 0.1µF 0.15 0.2 7p. 50V: 0.47µF 10p

CERAMIC CAPACITORS 50V
0.5pF to 10nF 3p each 15nF 22nF 33nF 47nF 4p each 0.1µF 6p

POLYSTYRENE CAPACITORS
100pF to 1nF 6p. 1.5nF to 47nF 10p. 0.1µF 20p each

SILVER MICA (Values in pF) 3: 4.7 6.8 10 12 18 22 33 47 50 68 75 82 85 100 120 150 220 250 300 330 360 390 600 820 18p each 1000 1800 2000 2200 20p each

CERAMIC TRIMMER CAPACITORS
2 7pF 4 15pF 6 25pF 8 30pF 20p

MINIATURE TYPE TRIMMERS
2.5 5pF 3 10pF 10 40pF 22p 2.5 5pF 5 45pF 60pF 88pF 30p

COMPRESSION TRIMMERS
3 40pF to 80pF 25 190pF 100 500pF 1250pF 25p 38p

JACK PLUGS Screened chrome 12p Plastic body 8p open metal 11p moulded with break 11p in line couplers 12p 15p 20p 22p 24p

SOCKETS 2 Pin 13p 3 Pin 8p 4 Pin 8p 5 Pin Audio 8p

CO-AXIAL (TV) 14p 14p 14p

PHONO assorted colours 9p Metal Screened 12p 5p single 8p 8p double 10p 3-way 12p

BANANA 4mm 10p 2mm 10p 1mm 10p 3mm 9p


WANDER 3mm 9p

FIGARO Gas and Smoke Detectors
Types: 109, 308, 812 or 813. 355p each
Sockets for above 25p*

TV GAMES ICs.
AY-3-8500 450p*
AY-3-8550 650p*
AY-3-8600 900p*
"JOY STICK" 175p*

We stock thousands more items, Capacitors, Coils, Bridge Rectifiers, Diodes, ICs, Lamps, Neons, Solder, Irons, S Dec, Thyristors, Triacs, Transformers etc., etc., ... It pays to visit us.

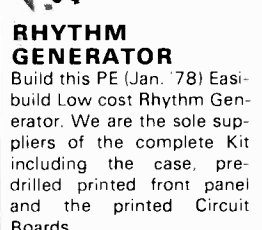(TV Games & Rhythm Gen. Demonstration on at our shop!)



RHYTHM GENERATOR
Build this PE (Jan. '78) Easy-build Low cost Rhythm Generator. We are the sole suppliers of the complete Kit including the case, pre-drilled printed front panel and the printed Circuit Boards.

Complete Kit price incl. VAT £49.95 only. P & P £1.10 insured. Ready Built Units available in limited quantities at £65.00 plus P & P. Send S.A.E. for descriptive leaflet.

DALO Resist. Pen Spare Tip 75p*

COPPER BOARDS
Fibre Glass Single Sided 6 x 6 1.30p 6 x 12 1.30p 8 x 10 70p

VOLTAGE REGULATORS
723C 45p TB6258 95p TO3 Cen -ve 1A 5V 220p 1A 12V 140p 1A 15V 145p 1A 18V 150p LM323K 626p 1A 5V 220p 1A -12V 220p Plastic -ve 1A 5V 99p 1A 12V 99p 1A 15V 99p 1A 18V 99p 0.1A 24V 99p 0.1A 5V 51p 0.1A 6V 51p 0.1A 8V 51p 0.1A 12V 51p 0.1A 15V 51p 0.1A 18V 51p

TTL 74★		7494 85		74194 140		4056 134		4513 206		4518 102		4526 199	
7400	14	7495	70	74195	95	4057	2570	4514	265	4519	59	4527	152
7401	14	7496	82	74196	118	4058	118	4515	188	4520	100	4528	99
7402	16	74100	125	74198	250	4060	115	4516	25	4521	268	4529	165
7403	16	74105	62	75150	110	4062	2380	4517	382	4522	199	4530	85
7404	20	74107	33	75491	75	4063	110						
7405	22	74109	54	75492	80	4066	58						
7406	22	74110	54			4067	380						
7407	38	74111	70			4068	22						
7408	20	74112	90			4069	15						
7409	20	74116	198			4070	32						
7410	15	74118	90			4071	21						
7411	24	74119	90			4072	21						
7412	23	74120	115			4073	23						
7413	37	74121	28			4074	25						
7414	74	74122	48			4076	129						
7416	35	74123	70			4077	40						
7417	39	74125	65			4078	21						
7420	16	74126	60			4081	22						
7421	33	74128	75			4082	21						
7422	24	74132	73			4083	19						
7423	32	74136	73			4086	74						
7425	30	74141	72			4089	150						
7426	36	74142	280			4092	85						
7427	36	74143	314			4094	190						
7428	38	74144	314			4095	105						
7430	18	74145	85			4098	15						
7432	32	74147	175			4097	372						
7433	40	74148	143			4098	110						
7437	30	74150	118			4099	190						
7438	33	74151	75			4100	22						
7440	17	74159	56			4102	52						
7441	74	74154	140			4103	330						
7442	68	74155	82			4104	99						
7443	115	74156	80			4105	93						
7444	112	74157	80			4106	52						
7445	94	74159	225			4107	108						
7446	74	74160	56			4108	58						
7447	82	74161	116			4109	720						
7448	78	74162	116			4110	720						
7450	17	74163	116			4111	995						
7451	17	74164	121			4112	126						
7453	17	74165	130			4113	130						
7454	17	74166	141			4114	130						
7456	17	74167	198			4115	130						
7470	30	74170	240			4116	250						
7472	28	74172	625			4117	625						
7473	32	74173	175			4118	105						
7474	32	74174	113			4119	86						
7475	42	74175	90			4120	86						
7476	40	74176	120			4121	120						
7480	50	74177	116			4122	96						
7481	97	74178	102			4123	96						
7482	82	74180	142			4124	130						
7483	95	74181	299			4125	99						
7484	195	74182	265			4126	58						
7486	36	74185	146			4127	52						
7489	320	74188	65			4128	89						
7490	36	74190	140			4129	89						
7491	80	74191	140			4130	89						
7492	53	74192	140			4131	140						
7493	35	74193	140			4132	140						

CMOS★		4068BE 22		702		709C 14 pin		710*		741C* 8 pin		748C		8038CC*		AV-1-0212		AV-1-1313		AV-1-5051		AV-1-672/1		AV-3-8500*		AV-3-8550*		AV-5-1224*		AV-5-1230*		CA3011*		CA3018*		CA3020		CA3021		CA3022		CA3023		CA3028A*		CA3030		CA3036		CA3040		CA3048		CA3075		CA3080E		CA3081		CA3089E		CA3090A*		CA3120*		CA3130*		CA3140		ICL7106Ev*		ICM7205*		LM3008		LM301A		LM308		LM318		LM324		LM339		LM348		LM379		LM381		LM381A		LM382		LM3900		LM3909		LM391		M252AA*		M253AA*																																																																																																									
4056	134	4057	2570	4058	118	4060	115	4062	2380	4063	110	4066	58	4067	380	4068	22	4069	15	4070	32	4071	21	4072	21	4073	23	4074	25	4076	129	4077	40	4078	21	4081	22	4082	21	4083	19	4086	74	4089	150	4092	85	4094	190	4095	105	4098	15	4097	372	4098	110	4099	190	4100	22	4102	52	4103	330	4104	99	4105	93	4106	52	4107	108	4108	58	4109	720	4110	720	4111	995	4112	126	4113	130	4114	130	4115	130	4116	250	4117	625	4118	105	4119	86	4120	86	4121	120	4122	96	4123	96	4124	130	4125	99	4126	58	4127	52	4128	89	4129	89	4130	89	4131	140	4132	140	4134	140	4135	140	4136	140	4137	140	4138	140	4139	140	4140	140	4141	140	4142	140	4143	140	4144	140	4145	140	4146	140	4147	140	4148	140	4149	140	4150	140	4151	140	4152	140	4153	140	4154	140	4155	140	4156	140	4157	140	4158	140	4159	140	4160	140	4161	140	4162	140	4163	140	4164	140	4165	140	4166	140	4167	140	4168	140	4169	140	4170	140	4171	140	4172	140	4173	140	4174	140	4175	140	4176	1

PRACTICAL ELECTRONICS

VOLUME 14 No. 8 APRIL 1978

CONSTRUCTIONAL PROJECTS

- FUMBLE NUDGE GAME** *by A. R. Cuff*
A contest of speed and manual dexterity for two players 564
- P.E. CHAMP—8** *by R. W. Coles and B. Cullen*
CHAMP-PROG—A PROM programming attachment for Champ 582
- P.E. STRING ENSEMBLE—2** *by A. J. Boothman*
Keyboard, keyswitch and diode gating assemblies 592
- ELECTRONIC KEYSWITCH** *by S. V. Essex*
An electronic lock using CMOS 601

GENERAL FEATURES

- EXTRA DESIGN IDEAS—INGENUITY UNLIMITED**
Fast Ni-Cad Battery Charger—Versatile V.C.O.—741 Tester—Double Tremolo Unit—Quiz Master—
Magnetic Tape Speedometer—Helipot Substitute—Car Lights On Indicator—Simple Car Tachometer 568
- FAULT FINDING—4** *by G. Loveday*
Handling and testing i.c.s. 577
- SEMICONDUCTOR UPDATE** *by R. W. Coles*
A look at some recently released devices 591
- MICRO-BUS** *by D.J.D.*
A bi-monthly focus on micro's for the home constructor 605

NEWS AND COMMENT

- EDITORIAL** 561
- MARKET PLACE**
Interesting new products 562
- BOOK REVIEWS** 581
- NEWS BRIEFS**
Ring A Ring—Traffic Computer 589
- PATENTS REVIEW**
Thought provoking ideas on file at the British Patents Office 590
- SPACEWATCH** *by Frank W. Hyde*
Forthcoming missions, new hot line systems, Soviet cargoship 608
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 609

Our May issue will be on sale Friday, 14 April 1978
(for details of contents see page 604)

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

BD 103 - The Connoisseur's Professional Choice



An exceptional transcription unit that performs to truly professional standards. Fitted with a new specially designed arm, the BD 103 will form the start, or an integral part, of a system for those who never believed they could achieve this level of quality at a reasonable price, simply compare specifications. *Low voltage DC servo controlled motor with electronic speed variation on all 3 speeds - 33 $\frac{1}{3}$, 45 and 78 rpm. *Externally housed power source, thereby eliminating hum fields, convertible for 120 or 230v mains supply. *Belt drive with precision ground natural rubber moulded belt of round cross section. *Neon illuminated stroboscope underneath 12" aluminium turntable is viewed through a mirror in the platform; available with either 50 or 60Hz stroboscope. *Pick-up arm automatically raises at the end of the playing section of the record. *Automatic lift-off can be overridden for non-standard records. *Low friction pick-up bearings - unipivot for horizontal motion, knife edges for vertical motion - with a unique system of magnetic stabilization on the unipivot bearings. *Playing weight adjusted by sliding weight on arm tube, which is calibrated. *Additional counter weights provided for accommodation of a full range of cartridges. Adjustable magnetic bias, calibrated for varying playing weights. *Inter-changeable lightweight plug in head shell accepts cartridges with 1" mounting centres. The turntable unit is solidly mounted on to a walnut plinth, which stands on a sprung and damped anti-vibration suspension system, thereby using maximum mass to improve performance, and fitted with a hinged acrylic dust cover with lid stay.

Dimensions: 15" x 18" x 5 $\frac{1}{2}$ ".

An alternative version is available without the pick-up arm and lifting device, incorporating a larger walnut/plastic cover, enabling most high quality pick-up arms to be used.

Dimensions: 15" x 18" x 7".

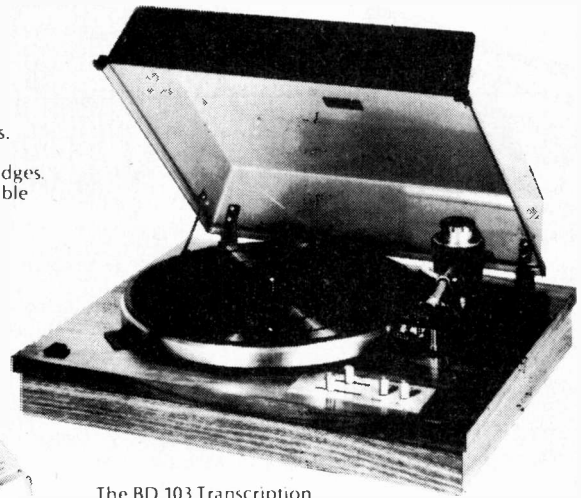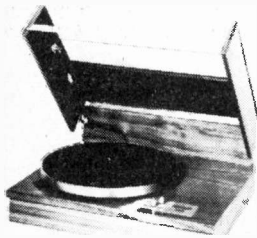BD 103 Alternative unit without arm and lifting device.



The BD 103 Transcription turntable and External Power unit

Connoisseur

Write for further details to:
A. R. Sugden & Co. (Engineers) Ltd.
 Manufacturers of Connoisseur Sound Equipment, Connoisseur Works, Atlas Mill Road, Brighouse, West Yorkshire HD6 1ES
 Telephone: Brighouse (0484) 712 142, Telex: 517144 Sugden G,
 Telegrams & Cables: Connoisseur Brighouse.

ELECTROVALUE

COMPONENTS FOR ALL WHO MUST HAVE ACCURACY, WITH QUALITY, SERVICE AND KEENEST PRICES

★ All the many types of components we sell are **BRAND NEW**, conform completely to manufacturers' specifications. **NO SURPLUS OR SECONDS**

★ **AMONGST THE MANY RANGES WE CARRY WE ARE PLEASED TO RECOMMEND**

SIEMENS Capacitors for quality and dependability.

SIEMENS silicon pnp & npn transistors from 8p.

POTS - wide range always available inc. W and W/O switch; mono & stereo slide etc.

RESISTORS

LEDS

CMOs BE types + & - Regulators 7805, 7905 etc.

MAGNETO RESISTORS and HE devices.

TEMP. CONTROLLED SOLDER IRONS, solder suckers.

★ **PRICE LIST** - for latest up-to-date and complete price list, please send 9p S.A.E. (large). Good discounts on orders £10 and upwards. Goods over £5 sent post paid in UK.

★ **MONTHLY BARGAIN LIST** Thanks to computer controlled stocks, we are able to offer a monthly bargains list. This month it's germanium & small power transistors; ceramic & electrolytic capacitors, polyesters. Please send S.A.E. for your copy.

ELECTROVALUE LTD

Dept PE4, 28 St Judes Rd. Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 3603; Telex 264475

Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA Phone (061) 432 4945.

T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD etc

7400 14p	7426 25p	7473 30p	74121 30p	74151 65p	74179 140p
7401 14p	7427 25p	7474 30p	74122 40p	74153 65p	74180 100p
7402 14p	7428 40p	7475 30p	74123 60p	74154 120p	74181 200p
7403 14p	7430 15p	7476 30p	74125 50p	74155 70p	74182 75p
7404 14p	7432 25p	7483 85p	74126 50p	74156 70p	74184 150p
7405 14p	7437 25p	7485 100p	74130 130p	74157 70p	74185 150p
7406 40p	7438 25p	7486 30p	74131 100p	74160 80p	74188 350p
7407 40p	7440 15p	7489 250p	74132 65p	74161 90p	74189 350p
7408 20p	7441 65p	7490 35p	74135 100p	74162 90p	74190 140p
7409 20p	7442 65p	7491 75p	74136 80p	74163 90p	74191 140p
7410 15p	7445 80p	7492 45p	74137 100p	74164 125p	74192 120p
7411 20p	7446 85p	7493 40p	74138 125p	74165 125p	74193 120p
7412 20p	7447 75p	7495 60p	74139 100p	74166 125p	74194 100p
7413 30p	7448 70p	7496 70p	74141 60p	74167 325p	74195 100p
7414 80p	7450 15p	74100 95p	74142 270p	74170 200p	74196 100p
7416 30p	7451 15p	74104 40p	74143 270p	74173 150p	74197 100p
7417 30p	7453 15p	74105 40p	74144 270p	74174 100p	74198 185p
7420 15p	7454 15p	74107 30p	74145 75p	74175 75p	74199 185p
7422 20p	7460 15p	74109 50p	74147 230p	74176 100p	
7423 25p	7470 30p	74116 90p	74148 180p	74177 100p	
7425 25p	7472 25p	74120 90p	74150 120p	74178 140p	

CMOS

4000 20p	4030 60p
4001 20p	4032 150p
4002 20p	4043 220p
4006 120p	4046 150p
4007 20p	4047 115p
4009 70p	4049 70p
4011 20p	4050 50p
4012 20p	4054 130p
4013 55p	4055 140p
4015 90p	4056 145p
4016 55p	4060 130p
4017 110p	4066 55p
4018 250p	4069 30p
4020 140p	4071 30p
4022 180p	4072 30p
4023 20p	4081 20p
4024 100p	4082 30p
4025 20p	4510 145p
4026 200p	4511 200p
4027 85p	4516 140p
4028 155p	4518 110p
4029 130p	4528 130p

IN4148 BY ITT/TEXAS

100 for £1.50.

TEXAS TIS88A VHF FET
 10 for £2.30, 100 for £20.00.

555 Timer, 10 for £2.80.

741 Op. amp. 10 for £2.00.

RCA SCR TO3 case
 100V 12.5A £2.50.

BTY 87-100R SCR
 100V 8-5A £1.00 each.

ALL PRICES INCLUDE
 POSTAGE AND V.A.T. AT
 8 or 12 $\frac{1}{2}$ % AS
 APPROPRIATE.

1200 μ F 63V, 2 for £1.00.
 2200 μ F 63V, 2 for £1.50.
 3300 μ F 63V, 2 for £1.60.

BD607/608 COMP.
 POWER £1.50 pair.

BF257 10 for £1.50.

7410 10 for £1.00
 7420 10 for £1.00
 7430 10 for £1.00
 7442 10 for £3.50
 7483 10 for £7.00
 7496 10 for £4.50
 74107 10 for £2.00
 74161 10 for £8.00

XEROZA RADIO


306 ST. PAUL'S ROAD,
 HIGHBURY CORNER, LONDON N.1

Telephone: 01-226 1489

Easy access to Highbury via Victoria Line (London Transport) British Rail

Understanding Digital Electronics

New teach-yourself courses

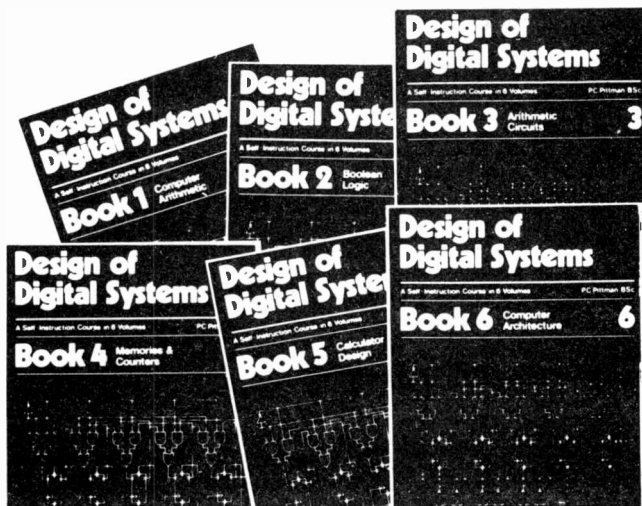

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes – each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes – each A4 size – and serves as an introduction to the subject of digital electronics. Everyone can learn from it – designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, Unit 2, Freepost, RIVERMILL LODGE, ST. IVES, HUNTINGDON, CAMBS, PE17 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446. PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES. Giro Ac. No. 278 9159. REGD. IN ENGLAND NO. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only:

£7.10

And the four volumes of Digital Computer Logic and Electronics cost only:

£4.60

But if you buy both courses, the total cost is only:

£11.10

. 90p post & packing by surface mail anywhere in the world. Airmail extra.

Flow Charts & Algorithms

HELP YOU PRESENT:

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

THE ALGORITHM WRITER'S GUIDE explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

£2.95

+ 45p post and packing by surface mail anywhere in the world. Airmail extra.

GUARANTEE

If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, Unit 2, Freepost, Rivermill Lodge, St. Ives, Huntingdon, Cambs, PE17 4BR, England.

Please send me the following books:

.....sets Digital Computer Logic & Electronics @ £5.50, p & p included
sets Design of Digital Systems @ £8.00, p & p included
Combined sets @ £12.00, p & p included
The Algorithm Writer's guide @ £3.40, p & p included (PE4)

Name

Address

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number


Signature *delete as appropriate

Telephone orders from credit card holders accepted on 0480-67446 (ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank.



ELECTRONIC KITS

TO MAKE WAY FOR OUR EXCITING NEW RANGE OF KITS, WE ARE OFFERING OUR OBSOLETE MODELS AT TRADE PRICE!

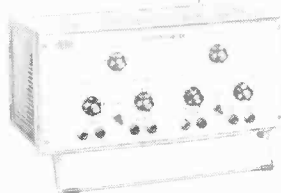

UK 585
(Electronic Beam Switch for Oscilloscopes)


REC. PRICE
INC. VAT

SALE PRICE
£12.45
INC. VAT

UK 302
(4 Channel Radio Control Transmitter)

REC. PRICE
INC. VAT

SALE PRICE
£9.50
INC. VAT

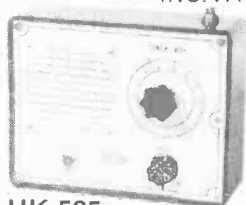

UK 525
VHF Tuner
120-160 MHz

INC. VAT

SALE PRICE
£7.65 INC. VAT

UK 167
Stereo Preamplifier R.I.A.A.

REC. PRICE
INC. VAT

SALE PRICE
£4.95 ★ (Please add 50p. post and packing on all orders)


We have on offer POWER SUPPLIES, AMPLIFIERS, (Stereo and Mono) ULTRA-SONIC BURGLAR ALARMS, MIXERS, TEST EQUIPMENT KITS and many others. Send large SAE for list, and our NEW RANGE catalogue.

NEW RANGE OF KITS

RHYTHM GENERATORS—6 channel STEREO MIXERS, AMPLIFIERS, STEREO TUNERS, V.H.F. RECEIVERS & TEST EQUIPMENT.

AMTRON (UK) LTD.
7, HUGHENDEN ROAD, HASTINGS,
SUSSEX, TN34 3TG
Telephone: (0424) 436004

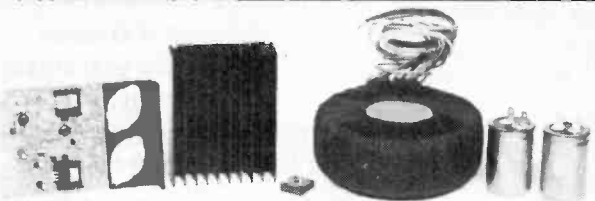TWO NEW SUPERMODULES: 170W INTO 4 OR 8 OHMS



By popular demand we have designed higher powered versions of our well known modules. The CE 1704 which gives 170W into 4 ohms and the CE 1708 which gives 170W into 8 ohms are physically similar to the original types and have the same combination of compatible performance features which makes CRIMSON amplification audibly superior to the competition and the only choice if you have an ear for music. We have also produced suitable power supplies which again use our superb TOROIDAL TRANSFORMERS, only 50mm high, with a 120-240 primary and single bolt fixing. Write or phone for more information and biased opinions.

POWER AMPLIFIER MODULES	Home	Europe
CE 608 60W/8 ohms 35-0-35V	£16.30	£16.60
CE 1004 100W/4 ohms 35-0-35V	£19.22	£19.30
CE 1008 100W/8 ohms 45-0-45V	£23.22	£23.00
CE 1704 170W/4 ohms 45-0-45V	£29.12	£28.46
CE 1708 170W/8 ohms 60-0-60V	£31.90	£31.04

TOROIDAL POWER SUPPLIES	Home	Europe
CPS 1 for 2 x CE 608 or 1 x CE 1004	£14.47	£18.40
CPS 2 for 2 x CE 1004 or 2/4 x CE 608	£16.82	£20.57
CPS 3 for 2 x CE 1008 or 1 x CE 1704	£17.66	£21.35
CPS 4 for 1 x CE 1008	£15.31	£19.18
CPS 5 for 1 x CE 1708	£22.68	£26.50
CPS 6 for 2 x CE 1704 or 2 x CE 1708	£23.98	£27.70

HEATSINKS	Home	Europe
LIGHT DUTY 50mm 2°C/W	£0.90	£1.30
MEDIUM POWER 100mm 1.4°C/W	£1.60	£2.40
DISCO/GROUP 150mm 1.1°C/W	£2.30	£3.65

THERMAL CUT-OUTS	Home	Europe
Recommended for improved reliability		
70°C for use with Free Air Heatsink	£1.60	£1.90
40°C for use with Fan Cooled Heatsink	£1.60	£1.90

T.H.D.	TYPICALLY <0.2% ANY POWER, 1kHz, 8 OHMS
T.I.D.	INSIGNIFICANT
SLEW RATE LIMIT:	20V/μS
S/N RATIO	: 110dB
FREQ. RESPONSE:	10Hz - 35kHz, -3dB
STABILITY	: UNCONDITIONAL
PROTECTION	: DRIVES ANY LOAD SAFELY
SENSITIVITY	: 775mV (250mV or 100mV ON REQUEST)
SIZE	: 120 x 30 x 25mm

CRIMSON ELEKTRIK
Please note our new address and telephone number:
**1A STAMFORD STREET,
LEICESTER LE1 6NL**
Telephone: (0533) 537722

Home prices include V.A.T. and postage. C.O.D. 90p extra, £100 limit. Export no problem. European prices include carriage, insurance and handling, payment in Sterling by bank draft, P.O., International Giro or Money Order. Outside Europe, please write for specific quote by return. Send SAE or two International Reply Coupons for full literature. Favourable trade quantity price list on request. High quality pre-amp circuit 20p.

CRESCENT RADIO LTD. MAIL ORDER DEPT. 1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4SJ PHONE: 888-4474

MULTIMETER BARGAINS

A special bulk purchase of Eagle Multimeters enables us to offer two from their range at up to 15% off Eagle's own Recommended Retail Price.


KEW 7 POCKET MULTIMETER

Handy pocket-size (3½" x 2½" x 1") 1000 opv meter with 'off' damping. Includes all basic ranges: DC volts 0 to 10, 50, 250, 1000. AC volts: 0 to 10, 50, 250, 1000. DC amps: 0 to 100 mA. Resistance: 0 to 150K ohms. Decibels: -10 to -22dB. £5.97. 8% VAT with leads and battery.



C1095 20,000 OPV MULTIMETER

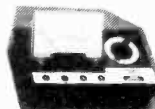with hinged 4-position scale for easy reading bench use. Anti-parallax mirror, 3-colour scale, overload protection. Ranges: DC volts: 5, 25, 50, 250, 500, 2,500 (20,000 opv). AC volts: 10, 50, 100, 500, 1,000 (10,000 opv). DC amps: 50μA, 2.5mA, 250mA. Resistance: 50K ohms, 5 megohms. Decibels: 20 to 22dB. £14.31. 8% VAT.



EFFECTS PROJECTOR "150"

(150 watt)
Ideal for disco work, this versatile machine takes a range of accessories and is of a sturdy metal construction. Comes complete with bulb and 6in. Liquid Wheel. Ready to use.



A bargain at £34 + 8% V.A.T.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT (1000 Watt per channel)

Three channel: Bass, Middle, Treble. The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display. Full instructions supplied or S.A.E. for details.
Fantastic Value at £20.00 + 8% V.A.T.

LOUDSPEAKER SELECTION

+ 12½% V.A.T.
2½in. 8, 40, and 75 ohm at £1.10 (please state which impedance is required)
5in. 8 ohm Ceramic at £1.70
8in. Goodmans "Audiom 8PA" 8 ohm 15W £5.26.
10in. "ELAC" Dual Cone 8 ohm 10 watt at £4.75

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED ALL PRICES INCLUDE POSTAGE—PLEASE ADD V.A.T. AS SHOWN—S.A.E. WITH ALL ENQUIRIES PLEASE

Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N13. Phone: 888 3206 and 13 SOUTH MALL, EDMONTON N9. Phone: 803 1685



KONTAKT 60 FOR INACCESSIBLE CONTACTS

—More than just a cleaner.

KONTAKT 60 guarantees perfect cleaning of contacts chemically in accordance with today's technology.

KONTAKT offers the following advantages:

1. Dissolves oxides and sulphides the safe way without attacking contact substances.
 2. Contains carefully selected solvents which do not attack plastics whereas they do dissolve resinified contact greases and dirt.
 3. Contains no silicone.
 4. Contains a light lubricant in order to avoid the contact paths being corroded.
 5. Prevents further oxidation setting in.
 6. Prevents 'creep' currents.
- Because of these outstanding properties Kontakt 60 is one of the best and most popular contact cleansing agents in the world.

Used by major industrial companies

OTHER KONTAKT PRODUCTS ARE:

- | | |
|-----------------------------------|------------------------------------|
| 70 Protective Lacquer. | 80 Special Siliconized Polish. |
| 72 Insulating Spray. | 100 Antistatic Agent for Plastics. |
| 75 Cold Spray for Fault Location. | 101 Dehydration Fluid. |

Write for full details of above complete range of Kontakt products to:

SPECIAL PRODUCTS DISTRIBUTERS LIMITED

81 Piccadilly, London, W1V 0HL. 01-629 9556.

The latest kit inovation!

from **Sparkrite**

the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM

Introductory
SPECIAL OFFER
£2 OFF Kit



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing. Electronic Design Associates, 82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791.

**Electronics Design Associates, Dept. PE4,
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791.**

Name

Address

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D.

X4 KIT	£14.95	£12.95
TACHS PULSE SLAVE UNIT	£3.35	
Access or Barclaycard No.		

I enclose cheque/PO's for

£


Cheque No.

Send SAE if brochure only required.

COIL FORMERS $\frac{1}{2}$ " dia. with core at 5p ea or 6 for 25p.
SPECIAL STRIPLINE 2 GHz NPN LOW NOISE TRANSISTOR at £1 each.
50 VARI-CAP DIODES Untested for 57p.
WIRE WOUND VARIABLE RESISTORS 1.2K 6 Watt @ 22p.
VERNITRON FM4 10.7 MHz CERAMIC FILTERS at 50p each.
BAW 62 HIGH SPEED SILICON DIODES at 12 for 35p.
NUT FIXING 1000pf FEED THRU's 500v.w. at 15p each.
100 MULLARD C280 CAPACITORS assorted for 57p.
BF 451 SILICON PNP 300 MHz TRANSISTORS 6 for 35p.
50 BC 107-8-9 TRANSISTORS assorted untested @ 57p.
ELECTRET MICROPHONE INSERT with FET PRE-AMP @ £1.85.
UNIJUNCTIONS TIS 43 Type @ 20p, MEU 21 @ 22p, MU 4894 @ 22p, 2N 4871 @ 25p, GE4JD5E29 @ 22p, D13T1 @ 25p, 2N 6028 @ 30p.
BELLING LEE CO-AX PLUGS @ 15p, CO-AX SOCKETS @ 15p.
TEXAS SCR TIC47 200 PIV 300mA @ 18p each.
TO39 NPN 5 WATT DARLINGTON TRANSISTORS @ 20p.
100 ASSORTED DISC CERAMIC CAPACITORS @ 57p.
12 BRANDED VHF FETS Assorted for £1.
500yd Reel of PVC CABLE 25 Strand .004 for £3.
20 0-100uA TUNING METER $1\frac{1}{2}$ " x $1\frac{1}{2}$ " at 90p.
100 PHOTO DARLINGTONS and PHOTO TRANSISTOR assorted untested for £1.
BD 187 4 AMP PLASTIC POWER NPN TRANSISTORS @ 25p each.
30 ASSORTED 10XAJ CRYSTALS 5100 To 7900 KHz for £1.10
DIE CAST ALLOY BOXES 4 x 2 x 1" @ 55p, 4 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " @ 65p, 4 $\frac{1}{2}$ " x $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " @ 85p, 6 x 3 $\frac{1}{2}$ " x 2" @ £1.15.
MAINS TRANSFORMERS 240V A.C. Input. Type 2. 22v 300mA, 7.5v 1 amp @ 99p (20p P & P). Type 4. 9v 500mA @ 88p (20p P & P). Type 5. 12v 500mA @ 88p (20p P & P). Type 6. 50v 2 amp, 50v 500mA @ £3.50 (85p P & P). Type 7. 20v 1 amp Twice. 10v 1 amp Twice @ £4.50 (95p P & P). Type 8. 16v 500mA @ 88p (20p P & P). Type 9. 14v 2 amp @ £1.60 (25p P & P). Type 10. 20v 1.5 amp 6v 1 amp @ £1.60 (25p P & P). Type 11. 25v Tapped 14v 1 amp @ £1.25 (25p P & P).
50 ASSORTED TRANSISTOR ELECTROLYTIC CAPACITORS @ 57p.
200 ASSORTED $\frac{1}{4}$, $\frac{1}{2}$ watt RESISTORS for 75p.
NKT 214 equivalent to OC 71 TRANSISTORS at 10p, 6 for 50p.
10 AMP S.C.R.'s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
400mW UNMARKED GOOD ZENERS 3.3v, 6.8v, 10v, 11v, 12v, 13v, 16v, 24v, 30v, 33v, 36v all at 10 for 40p.
TBA 120S FM IC.'s Untested with data 6 for 60p.
F.M. FRONT ENDS 88 To 108 MHz with conversion data to Aircraft Band or 144 MHz £3.20.
5 TURN POTENTIOMETERS 5K, 10K, 20K @ £1 each.
2N 706 UNMARKED GOOD TRANSISTORS at 12 for 50p.
MINIATURE ROTARY SWITCHES 2 Pole 4 way @ 20p, 3 Pole 3 Way @ 40p, 1 Pole 11 way @ 40p.

Please add 20p for post and packing on UK orders under £2. Overseas orders at cost.

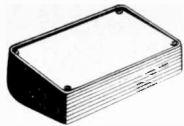J. BIRKETT
RADIO COMPONENT SUPPLIERS
25 The Strait, Lincoln LN2 1JF
Tel. 20767.



MINI CONSOLES

Ideal for small desk control panels and consoles. Moulded in orange, blue, black and grey ABS. Incorporates slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of console and held by screws running into integral brass bushes.

MC 161 x 96 x 58mm £2.12 (1-9) (Includes VAT)
MC 215 x 130 x 75mm £2.94 (1-9) (Includes VAT)
(Prices include VAT & P.P.)

ECONOMY QUALITY LED'S

50 for only £5 - 100 for only £9
Mixed bags, all sizes, various colours



Full specification LED's also available
Red (specify size) 75p per pack
Green, Yellow, Orange (specify size) £1.20 per pack
Packs contain 5 LED's, mounting clips and data

TYPE A NEON INDICATORS


Supplied with resistor for 240 Volts operation
Held in 8mm hole by plastic bezel
150mm wire leads




Red, Amber, Clear, Opal 19p each
Green 28p each

12 VOLTS MINI HAND DRILL

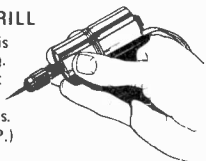Ideal for drilling pcb, chassis etc as well as model making. Supplied with 2 collets that accept tools and drills with 3/32" and 0.50" dia shanks. £7.56 (Includes VAT & P.P.)



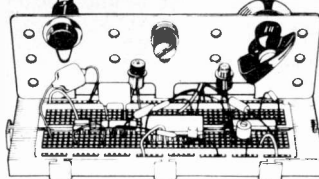Stop wasting time soldering
The NEW MW BREADBOARD accepts
Transistors, LED's, Diodes, Resistors, Capacitors and all DIL packages with 6 to 40 pins



Includes slot-in Component Support Bracket and has 470 individual sockets, plus Vcc and Ground Bus Strips
Price £9.72 (includes VAT & P.P.)

TYPE MP NEON INDICATOR

Supplied with resistor for 240 Volts operation
150mm leads, held in 6.4mm hole by nut



Red, Amber, Clear, Opal 20p each

SEVEN SEGMENT DISPLAYS

Economy quality
Red, yellow and green
Only 45p each
Common Anode - 0.3" Left Decimal
Full specification displays also available as above
Red @ 98p each
Green and Yellow @ £1.35 each.
Data supplied with full spec. displays only.



Quantity quotations on request

P.P. Note Unless included in price add 25p Post & Packing for orders totalling under £10. All prices include VAT and are valid in UK only for 2 months from journal issue date

Michael Williams Electronics

47 Vicarage Av. Cheadle Hulme, Cheshire SK8 7JP

SC BOXES

Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of the box and held by screws running into integral brass bushes.




SC 85 x 56 x 35mm 97p (1-9) (Includes VAT)
SC 111 x 71 x 48mm £1.29 (1-9) (Includes VAT)
SC 161 x 96 x 59mm £1.81 (1-9) (Includes VAT)

Add 25p per £1 order value for Post & Packing

240 VOLTS MINI HAND DRILLS

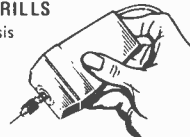
Ideal for drilling pcb's, chassis etc as well as model making. Supplied with 3 collets that accept tools and drills with 1mm, 2mm and 1/8" dia shanks.



£9.72 (includes VAT & P.P.)
Accessory tools... 5 Burrs, 1mm, 2mm, 1/8th Drills, 3/32" Collet Price £1.75 (Includes VAT & P.P.)

RC BOXES ABS and DIECAST

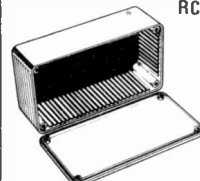1.5mm pcb slots and close fitting flanged lids. ABS in orange, blue, black or grey colours. Diecast in natural or grey hammetone colour. Lid held by screws running into integral brass bushes.



	ABS	Natural Diecast	Hammetone Diecast
RC 100x62x25mm	68p	70p	93p
RC 112x62x31mm	79p	94p	1.23
RC 120x65x40mm	88p	1.22	1.59
RC 150x80x50mm	1.03	1.64	2.11
RC 190x110x60mm	1.77	2.53	3.08

Polystyrene version

in grey only, no slots, no integral brass bushes
RC(P) 112 x 61 x 31mm 61p
All prices are 1-9 off, include VAT, but please add 25p per £1 order value for Post & Packing

BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs - £4.95; 14lbs - £7.95; 28 lbs - £12.00; 56lbs - £20.00; 112 lbs - £30.00.

BARGAIN PACKS

Handy Packs

4 aluminium boxes 128 x 44 x 38 mm ideal for signal injectors, etc. £1.00
100 miniature reed switches ideal for burglar alarms, model railways, etc. £3.30
15 x 2-pole reed relays on board operate at 12 volts £2.45.
6 x 6-pole 12 volt reed relays on board £2.45
High quality computer panels smothered in top grade components: 5 lbs £4.75; 10 lbs £8.95
Miniature edgewise panel meters 200 va. & sd £1.

Miniature transistorised f.m. front end with integral tuning gang 88-108MHz £2.50.
New U.H.F. transistor TV tuners 4 pushbutton type £2.50
Rotary type with slow motion drive £2.50
Aluminium TV coax plugs 10 for £1.00
Miniature 5K log pots with s/p switch. 4 for £1.
Hardware Packs each containing 100's of items including: BA nuts and bolts, Nylon, Self-tapping, Posidrive, "P" clips, Cable clamps, Fuse holders, Spare nuts etc. £1 per pound. 100 assorted "P" clips £1.

DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad 1/8 board, 1 lb ferric chloride, 1 dolo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions / only £5.30

150 sq. in. fibre glass board £2
Dolo pen 90p
1 lb ferric chloride to mil spec £1.25

Miniature mains transformers, fully shrouded. 240v. in 6-0-6v at 100MA, out. Ex. New equipment, complete with mains lead and plug on input and short leads on output £1.20.

Ultrasonic transceiver units. Each contains transmit and receive transducers (1/2" diam.), transistor circuit board, range control, connection chart and temper proof switch. Mounted in smart aluminium cases with grille. Brand new and boxed £5.25.

Semiconductor Bargains


TH3 Thermistors, 10 for £1.
100 new & marked silicon and germanium transistors including BC148, BF194, BC183, etc. £3.95
200 new & marked transistors, including 2N3055, AC128, BFY50, BD131, etc. £6.95
100 mixed diodes IN4148, etc. £1.20
100 mixed diodes including zener, power and bridge types £3.30
Bridge rectifier 100v 2.5 amp. 4 for £1.
Brand new ITT 25kv T.V. triplers for Decca Bradford chassis £2.50. 5 for £10.

5 lbs ferric chloride to mil spec £5.00
Instruction sheet 20p
50 Germanium diodes ideal for crystal sets etc. £1.
200 unmarked mixed transistors, lots of interesting types including power. Send 60p for samples £4.50
25 New & marked integrated circuits including 555, 741, 7400, 7490, TBA 800, CD4001, etc. £4.70
BR 101 full spec. 5 for £1.00
TBA 120A 50p each
20 mm anti-surge fuses your selection 800mA to 3.15A 12 for £1.00

Component Bargains

300 mixed resistors 1/2 & 1 watt £1.50
300 modern mixed cops most types £3.30
125 mixed resistors, mostly 1/2 & 2 watt £1.
100 mixed polyester caps £2.20
100 mixed modern miniature ceramic plate caps, £1.50.
100 mixed electrolytics £2.20
100 mixed wirewounds £2.20
300 printed circuit resistors £1.00.
25 mixed pots & presets £1.00

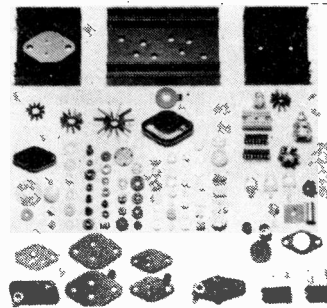40p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PE, 149A BROOKMILL ROAD, DEPTFORD SE8.



LOW PROFILE DIL SOCKETS - TIN PLATED

PRICE PER	1	5	10	25
8 PIN	10p	45p	85p	£2.00
14 PIN	12p	55p	£1.05	£2.50
16 PIN	13p	60p	£1.15	£2.75
28 PIN	25p	£1.20	£2.30	£5.50
40 PIN	40p	£1.80	£3.50	£8.25
STANDARD PROFILE DOUBLE-SIDED DIL - SOCKETS				
14 PIN	14p	65p	£1.25	£3.00
16 PIN	15p	70p	£1.35	£3.25

MOUNTING PADS

	10/PACK	50/PACK
TO 5 4 HOLE	9p	40p
TO 18 4 HOLE	9p	40p
CONVERTERS		
TO 99 TO DIL	55p	£2.50
TO 100 TO DIL	55p	£2.50
TO 92/98 TO TOS	9p	40p
TO 18 TO TOS	9p	40p
TO 98 TO TOS	9p	40p
DIODE CRADLES	10p	45p

READY DRILLED BLACK ANODISED HEAT SINKS

TO 3	1 @ 40p	5 @ £1.80
TO 66	1 @ 40p	5 @ £1.80
TO 3 x 2	1 @ 70p	5 @ £3.20

HEAT SINK COOLERS. FITTING TO 5.

NF 204	1 @ 14p	5 @ 65p
NF 205	1 @ 12p	5 @ 55p
NF 207	1 @ 13p	5 @ 60p
NF 209	1 @ 15p	5 @ 75p

INSULATING KITS. 5 WASHERS 10 BUSHES.

	MELINEX	MICA
TO 3	28p/KIT	30p/KIT
TO 66	28p/KIT	30p/KIT
BUSH SHANK LENGTH REQ:		
-.125, -.05, -.025	125, -.05, -.025.	For TO 3 only.

TRANSISTOR INSULATION COVERS

TO 3	5 @ 35p	10 @ 70p
TO 5	5 @ 15p	10 @ 25p
TO 66	5 @ 35p	10 @ 70p

POWER SOCKETS

TO 3	1 @ 14p	5 @ 65p
TO 66	1 @ 16p	5 @ 75p


LARGER RANGE OF TRANSISTOR PADS AND INSULATING BUSHES IN CATALOGUE. ALL PRICES INCLUDE V.A.T.

POST AND PACKING 15p KITS/PADS/SOCKETS/COOLERS. 45p FOR ANODISED HEAT SINKS

FULL ILLUSTRATED CATALOGUE - SEND 30p FOR POST AND PACKING.

FROM

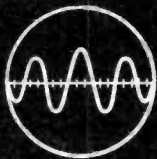MOULDED ELECTRONIC COMPONENTS INT. LTD.
34d QUARRY HILL ROAD
TONBRIDGE, KENT.
Telephone: 0732 365910



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS

PRICES INCLUDE VAT. P & P FREE
correct at 1.2.78

TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. (PE48) or quote
Access/Barclaycard No. and post to TUAC LTD. (PE48) 119
Charlmont Road, London Sw17 9AB. We accept phone orders
from Access/Barclaycard Holders. Phone 01-672 9080.

PRE AMPLIFIERS

Designed for use with TUAC power amplifier modules.



VA08

Vol. Treb. Mid. and Bass controls. HI. IMP. FET. I/P suitable Mid. Guitar, Radio Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 1kHz. Bass +20 -10dB at 40Hz.

VA06

Vol. Treb. and Bass controls. Sensitivity 8mV. Treb +28 -15dB at 12kHz. Bass -18dB at 40Hz.

SVA08 STEREO PRE AMP


Vol. Treb. Mid. and Bass controls. I/P suitable Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -7dB at 4kHz. Bass +20 -18dB at 30Hz. Plus Full Balance Control. Fully I/C operation supply voltage ±25VDC.

£9.00

£7.75

£15.00

POWER SUPPLIES

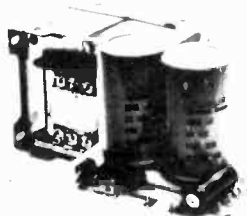

Vacuum varnish impregnated. Transformers with supply board incorporating pre-amp supply.

PS250 for supplying 2 TP125s £28.50

PS200 for supply to TL100 £28.50

PS60/60 for supplying 2 TL60s £17.75

PS125 ±45 volts for TP125 £16.25


PS100 ±43 volts for TL100 £16.25

PS60 ±38 volts for TL60 £15.25

PS30 ±25 volts for TL30 £11.75

PSU 2 for supplying disco mixer £7.50

AMPLIFIER MODULES

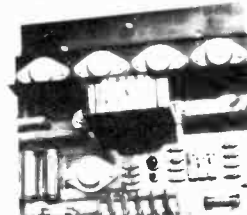

TL30 D.C. COUPLED 5 × 5 × 1 1/2 in.

• 30 watt R.M.S. continuous sine wave output
• 8 transistors 4 diodes

£12.75

TL60 5 × 5 × 3 in.

• 60 watt R.M.S. continuous sine wave output
• 2 R.C.A. 110 watt 15 amp transistors

£18.75

TL100 5 × 5 × 3 in.

• 100 watt R.M.S. continuous sine wave output
• 2 R.C.A. 150 watt 15 amp transistors

£20.75

TP125 7 × 6 1/2 × 3 in.

• 125 watt R.M.S. continuous sine wave output
• 4 R.C.A. 150 watt 15 amp output transistors

£25.75


4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSMI

- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£20.75

Model 501 500W per channel as above without sound triggering

£12.25

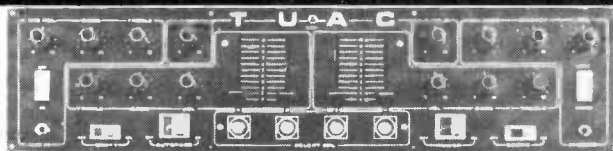

STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A.A. comp.). Flat 50mV at 1kHz. Bass controls ±18dB at 60Hz. Treble controls ±18dB at 15kHz.

OUTPUT: Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz ± dB

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions. Size: 25in long × 6in high × 3in deep.

Mono Disco Mixer with autofade £45.00

£129.00

3 CHANNEL LIGHT MODULATOR SILMB

- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£20.25

Single Channel Version 1500 Watts

£9.75



FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs) as illustrated




For S1LMB £6.50
Size 8" × 4 1/2"



4LSM1 £5.50
Size 6 1/2" × 4 1/2"



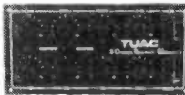FUZZ LIGHTS
Red, Green, Blue,
Amber. £23.50



S1LMB £7.50
Size 9" × 4 1/2"
Combined with 3SDM1

new from TUAC... ULTRA QUALITY HIGH POWER TD 500 POWER AMPLIFIER New DC coupled design

Output power using PS250

300w into 2 Ohms

220w into 4 Ohms

140w into 8 Ohms

75w into 15 Ohms

RMS continuous sine wave

output


INPUT Sensitivity 0.775V

RMS (ODB) at 25 KOHMS

Hum and Noise - 100dB

Relative full output

THD = at Full Power 0.1%

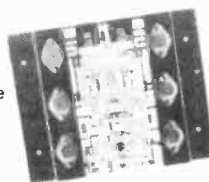


7" × 9" × 1 3/4" £45

PIEZO SUPER HORN £10.95

STOCKISTS - CALLERS ONLY

A1 Music, 88 Oxford Street, Manchester (Tel. 061-236 0340)
Geo Mathews, 85/87 Hurst Street, Birmingham (Tel. 021-622 1941)
Bristol Disco Centre, 25 The Promenade, Gloucester Road (Tel. Bristol 41666).
Soccodi, 9 The Friars (Tel. Canterbury 60948)
Cookies Disco Centre, 132 West Street (Tel. Crews 4739).
Garland Bros. Ltd., Deptford Broadway, London 01-892 4412
Luton Disco Centre, 88 Wellington Street, Luton (Tel. Luton 411733)
Mitchell Electronics, 7 Queen Street (Tel. Salisbury 23689).
Session Music, 183 Mitcham Road, Tooting (Tel. 01-872 3413).
Mon-Sat 9.30 a.m. - 5.30 p.m. Half Day Wed. 9.30 a.m. - 1 p.m.

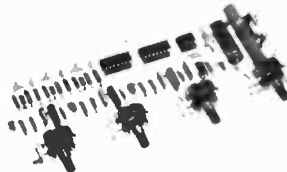ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR




- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDM1

£14.50

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 20 PAGE ILLUSTRATED CATALOGUE S.A.E. STAMPED PLEASE

KITS FOR SYNTHESISERS, SOUND EFFECTS

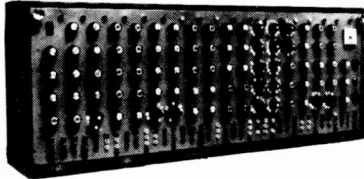

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware, such as cases, sockets, knobs, etc are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs designed by Phonosonics

PHOTOCOPIES of the P.E. texts for most of the kits are available—prices in our lists

P.E. MINISONIC Mk. 2 SYNTHESISER

A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the functions offered by this design give it great scope and versatility. Consists of 2 log VCOs, VCF, 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits, HF oscillator and detector, ring modulator, noise generator, output amp and mixer, power supply

Set of basic component kits £64.25
Set of printed circuit boards £9.71

P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage, notably P.E. Minisonic Phasing Unit, Wind and Rain, Rhythm Generator, Sound Bender, Voltage Controlled Filter, Guitar Effects Pedal and Overdrive, Fuzz, Tremolo and Wah-Wah units.

The Main Synthesiser: PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp. Full details in lists.

Set of basic component kits £83.03
Set of printed circuit boards £13.20

The Synthesiser Keyboard Circuits (can be used without the Main Synthesiser to make an independent musical instrument) 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, mixer, 2 envelope shapers and additional PSU. Full details in our lists.

Set of basic component kits £48.18
Set of printed circuit boards £7.66

GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches £7.59
Alternative component set with panel mounting switches £4.96
Printed circuit board £1.43

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl SWs) £7.84
Printed circuit board £1.81

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce 'jungle-drum' rhythms.

Component set (incl. PCB) £2.88

PHASING UNIT (P.E. Sept 73)

A simple but effective manually controlled unit for introducing the phasing sound into live or recorded music.

Component set (incl. PCB) £2.87

PHASING CONTROL UNIT (P.E. Oct 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4.48

SOPHISTICATED PHASING AND VIBRATO UNIT

A slightly modified version of the circuit published in Elektor, December 1976, and includes manual and automatic control over the rate of phasing and vibrato.

Component set £17.69
Printed circuit board £2.33

WAH-WAH UNIT (P.E. Apr. 76)

The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.

Component set (incl. PCB) £3.55

AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7.27
Component set and PCB, with panel switches £4.83

P.E. JOANNA (P.E. May/Sept. 75)

A five-octave electronic piano that has switchable alternative voicing of Honky-Tonk piano, ordinary piano, harpsichord, or a mixture of any of the three, together with facilities including fast and slow tremolo, loud and soft pedal switching and sustain pedal switching. The power amplifier typically delivers 24 watts into 8 ohms. The PCBs have been redesigned by ourselves making improved use of the space available.

Main power supply, tone generator, 61 envelope shapers, voicing and pre-amp circuits

Set of basic component kits for above £75.29
Set of printed circuit boards for above £20.35
Power amplifier £15.97
Printed circuit board for power amp 95p

ELECTRONIC ORGAN

5-octave electronic organ with 5 basic voices that can be used individually or together, 5 pitches (21, 41, 81, 161, 321), variable attack, tremolo, vibrato, phasing, and variable sustain. Details in our list.

ORGAN CONVERSION KIT

Converts the P.E. Joanna electronic piano to also provide most of the facilities offered by the above electronic organ.

Basic component set and PCB £12.34

SYNTHESISER TUNING INDICATOR (P.E. July 77)

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl sw.) £7.45

GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)

A modified and extended version of the circuit published. Details in list

SEE OTHER PAGE FOR KEYBOARDS, AND OUR LISTS FOR OTHER COMPONENTS AND ACCESSORIES STOCKED

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set (incl. PCB) £3.72

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.

Component set using dual slider pot £6.86
Component set using dual rotary pot £6.20
Printed circuit board £1.62

FUZZ UNIT

Simple Fuzz unit based upon P.E. Sound Design circuit

Component set (incl. PCB) £2.03

TREMOLO UNIT

Based upon P.E. Sound Design circuit

Component set (incl. PCB) £3.64

TREBLE BOOST UNIT (P.E. Apr. 76)

Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable.

Component set (incl. PCB) £2.40

P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments. Ideal for tuning acoustic and electronic musical instruments alike.

Main component set (incl. PCB) £15.59
Power supply set (incl. PCB) £7.03

P.E. SYNCHRONOME (P.E. Mar. 76)

An accented-beat electronic metronome, providing duple, triple and quadruple times with full control over the beat rate. Can also be used as a simple drum-beat rhythm generator. Includes power supply.

Component set (incl. loudspeaker) £11.62
Printed circuit board £2.04

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings. All kits include PCBs.

Standard tolerance set of components £2.96
Superior tolerance set of components £3.76
Regulated power supply (will drive 2 sets) £4.89

ENVELOPE SHAPER WITHOUT VCA (P.E. Oct 75)

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB) £4.66

ENVELOPE SHAPER WITH VCA (P.E. Apr 76)

This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions.

Component set (incl. PCB) £6.68

TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA, having the usual attack, decay, sustain and release functions, and in addition it also provides a Repeat Effect enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set £4.52
Printed circuit board £1.82

WAVEFORM CONVERTER

Slightly modified from a circuit published in a German edition of Elektor. Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio.

Component set (incl. PCB but excl sws) £8.19

VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 65-1) £8.22

RING MODULATOR (P.E. Jan 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 59-1) £5.50

NOISE GENERATOR (P.E. Jan. 75)

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 60-1) £3.35

SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists

MICROPHONE PRE-AMP (P.E. Apr. 77)

Component set (incl. PCB) £3.78

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during talk-over—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3.97

DYNAMIC RANGE LIMITER (P.E. Apr. 77)

Automatically controls sound output to within a preset level.

Component set (incl. PCB) £4.58

POST AND HANDLING

U.K. orders—under £15 add 25p plus VAT, over £15 add 50p plus VAT. Keyboards £2.00 plus VAT.

Optional Insurance for compensation against loss or damage in post, add 35p in addition to above post and handling.

Eire, C.I., B.F.P.O., and other countries are subject to Export postage rates.

DON'T FORGET VAT!

Add 12½% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

EXPORT ORDERS are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 40p.

PHONOSONICS · DEPT. PE63 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

MAIL ORDER AND C.W.O. ONLY
SORRY BUT NO CALLERS PLEASE

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 20p other countries—send 40p



KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits, including the P.E. Joanna, P.E. Minisonic, and P.E. Synthesiser. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C. The keys are plastic, spring-loaded and mounted on a robust aluminium frame.

3 Octave (37 notes) £25.50. 4 Oct (49 notes) £32.25. 5 Oct (61 notes) £39.75.

Contact Assemblies for use with above keyboards. Single-pole change-over (type SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally-open make-break (type DP) as for P.E. Synthesiser. Special contact assembly (type 4PS) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables THE SAME KEYBOARD to be used with the P.E. Synthesiser P.E. Minisonic and the P.E. Joanna simultaneously thus avoiding the cost of more than one keyboard. See our list for other contacts.

Contact	Each	3 Octave Set	4 Octave Set	5 Octave Set
SP	24p	£ 8.88	£11.76	£14.64
2P	27p	£ 9.99	£13.23	£16.47
4PS	53p	£19.61	£25.97	£32.33

PRINTED CIRCUIT BOARDS for use with the above contacts and thus eliminating most of the inter-wiring required, are available. Details in our lists.

MORE KITS!

NEW RHYTHM GENERATOR

Redesigned, improved and extended version of the PE 1974 design and including new automatic rhythm programme selector.

TUNE-PROGRAMMABLE SEQUENCER

(PE Nov. 77) The new music unit currently being published.

FORMANT SYNTHESISER

(Elektron Magazine 1977). Very sophisticated music synthesiser for the advanced constructor and for whom cost is secondary to performance.

GUITAR SUSTAIN UNIT

(PE Oct. 77). Details in lists. Please send S.A.E.

SOUND-TO-LIGHT (P.E. Aurora) (P.E. Apr.-Aug. 71)

Four channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities.

Basic component set (excl. thyristors)	£15.92
Printed circuit board for above	£3.90
Power supply	£5.78
PCB for power supply	£1.79

3-CHANNEL SOUND-TO-LIGHT (P.E. Apr. 76)

A simple but effective sound-to-light controller capable of operating 3 lamps each of approximately 700 watts. Includes power supply, thyristors, and by-pass switches.

Component set (incl. PCB)	£11.95
---------------------------	--------

DISCOSTROBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic component set	£18.19
Printed circuit board	£3.45

BIOLOGICAL AMPLIFIER (P.E. Jan. Feb. 73)

Multi-function circuits that with the use of other external equipment can serve as lie-detector, alphaphone, cardiophone etc.

Pre-Amp Module Component set (incl. PCB)	£4.22
Basic Output Circuits—combined component set with PCBs for alphaphone, cardiophone frequency meter and visual feedback lampdriver circuits	£6.59
Audio Amplifier Module Type PC7	£7.35

SEMI CONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor. While stocks last.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB	£9.63
Panel meter (500µA)	£5.70

TRANSISTORS

AC128	26p
AC176	26p
BC107	14p
BC108	14p
BC109	14p
BC147	12p
BC148	12p
BC149	12p
BC157	13p
BC158	13p
BC159	13p
BC182L	12p
BC184	12p
BC187	25p
BC204	14p
BC209C	14p
BC212L	15p
BC213	15p
BC478	29p
BCY71	22p
BD131	44p
BD132	54p
BFY50	22p
BFY51	22p
BFY52	24p
BSY95A	22p
MD8001	172p
OC28	60p
OC71	20p
OC72	25p
OC84	25p
ORP12	70p
ZTX107	12p
ZTX108	9p
ZTX501	13p
ZTX503	15p
ZTX531	23p
2N706	13p
2N914	22p
2N1304	22p
2N2219	27p
2N2905	35p
2N2905A	36p
2N2907	22p
2N3053	18p
2N3054	66p
2N3055	48p
2N3702	12p
2N3703	12p
2N3704	12p
2N3819	35p
2N3820	64p
2N3823E	39p
2N4060	12p
2N5245	51p
2N5459	33p
2N5777	45p

INTEGRATED CIRTS.

318	230p
709 T05	40p
709 8-pin DIL	48p
723 T05	105p
741 8-pin DIL	32p
748 T05	63p
748 8-pin DIL	63p
µA7805 TO220	205p
µA7808 TO220	205p
µA7812 TO220	205p
µA7815 TO220	205p
µA7818 TO220	205p
AY-1-0212	650p
AY-1-6721/6	195p
CA3046	90p
MC3340	150p
SG3402N	262p

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

Colour T.V. Servicing
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. 273 S, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONOSONICS

NEW SEASON'S COMPONENTS

BRIDGE RECTIFIERS

SILICON 1 amp		
Type	Order No.	Price
50V RMS	BR1/50	£0.20
100V RMS	BR1/100	£0.22
200V RMS	BR1/200	£0.25
400V RMS	BR1/400	£0.36
SILICON 2 amp		
50V RMS	BR2/50	£0.45
100V RMS	BR2/100	£0.48
200V RMS	BR2/200	£0.52
400V RMS	BR2/400	£0.58
1000V RMS	BR2/1000	£0.68

BOOKS BY BABANI

Purchase books to the value of £5.00 from the list below and choose any 60p pak from this page FREE.

BP2	Handbook of Radio, TV & Industrial & Transmuting Tube & Valve Equivalents	160p
BP3	Handbook of Tested Transistor Circuits	140p
BP6	Engineers and Machinists Reference Tables	140p
BP7	Radio & Electronic Colour Codes and Data Chart	115p
BP10	Modern Crystal and Transistor Set Circuits for Beginners	135p
BP14	Second Book of Transistor Equivalents	195p
BP15	Constructors Manual of Electronic Circuits for the Home	150p
BP16	Handbook of Electronic Circuits for the Amateur Photographer	160p
BP18	Boys and Beginners Book of Practical Radio and Electronics	160p
BP22	79 Electronic Novelty Circuits	175p
BP23	First Book of Practical Electronic Projects	175p
BP24	52 Projects Using IC741 (or equivalents)	175p
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	185p
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	160p
BP29	Major Solid State Audio Hi-Fi Construction Projects	185p
BP32	How to Build Your Own Metal & Treasure Locators	185p
BP34	Practical Repair & Renovation of Colour TVs	195p
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	195p
BP36	50 Circuits Using Germanium, Silicon & Zener Diodes	175p
BP37	50 Projects Using Relays, SCR's and TRIACS	11.10
BP39	50 (FET) Field Effect Transistor Projects	11.25
129	Universal Gram-motor Speed Indicator	18p
160	Coil Design and Construction Manual	175p
161	Radio, TV and Electronics Data Book	160p
196	AF-RF Reactance Frequency Chart for Constructors	115p
202	Handbook of Integrated Circuits (ICs) Equivalents and Substitutes	175p
205	First Book of Hi-Fi Loudspeaker Enclosures	175p
213	Electronic Circuits for Model Railways	185p
214	Audio Enthusiasts Handbook	185p
216	Electronic Gadgets and Games	185p
217	Solid State Power Supply Handbook	185p
219	Solid State Novelty Projects	185p
220	Build Your Own Solid State Hi-Fi and Audio Accessories	185p
222	Solid State Short Wave Receivers for Beginners	195p
223	50 Projects Using IC CA3130	195p
224	50 CMOS IC Projects	195p
225	A Practical Introduction to Digital IC's	195p
226	How to Build Advanced Short Wave Receivers	11.20
RCC	Resistor Colour Code Disc Calculator	110p

BOOKS BY NEWNES

No. 229	Beginners Guide to Electronics.	Price £2.25†
No. 230	Beginners Guide to Television.	Price £2.25†
No. 231	Beginners Guide to Transistors.	Price £2.25†
No. 233	Beginners Guide to Radio.	Price £2.75†
No. 234	Beginners Guide to Colour Television.	Price £2.25†
No. 235	Electronic Diagrams.	Price £1.80†
No. 236	Electronic Components.	Price £1.08†
No. 237	Printed Circuit Assembly.	Price £1.08†
No. 238	Transistor Pocket Book.	Price £3.90†
No. 225	110 Thyristor Projects Using SCRs & Triacs.	Price £2.50†
No. 227	110 COS/MOS Digital IC Projects For the Home Constructor.	Price £2.25†
No. 226	110 Operational Amplifier Projects for the Home Constructor.	Price £2.50†
No. 242	Electronics Pocket Book.	Price £3.75†
No. 239	30 Photoelectric Circuits & Systems.	Price £1.80†

CASES

ALUMINIUM BOXES. Made from bright ali., folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	62p*
160	4in	4in	1 1/2in	62p*
161	4in	2 1/2in	1 1/2in	62p*
162	5 1/2in	4in	1 1/2in	74p*
163	4in	2 1/2in	2in	64p*
164	3in	2in	1in	44p*
165	7in	5in	2 1/2in	£1.04*
166	8in	6in	3in	£1.32*
167	6in	4in	2in	86p*

INSTRUMENT CASES. In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	6in	2in	£1.40*
156	11in	6in	3in	£1.80*
157	6in	4 1/2in	1 1/2in	£1.25*
158	6in	5 1/2in	2 1/2in	£1.60*

SPECIAL OFFER

AGFA CASSETTES STEREOCROM

307	C60	RRP £2.05	Our price £1.60
308	C90	RRP £2.54	Our price £1.80
309	C120	RRP £3.49	Our price £2.60

SFD - Super Ferro Dynamic			
310	C60	RRP £1.48	Our price £1.00
311	C90	RRP £1.89	Our price £1.50
312	C120	RRP £2.82	Our price £2.00

DIODES SIL G.P.

300 mW 40 PIV (min) SUB-MIN FULLY-TESTED
Ideal for Organ builders
30 for 50p, 100 for £1.50, 500 for £5, 1,000 for £8

INTEGRATED CIRCUITS CMOS

Type	Price	Type	Price	Type	Price
CD4000	£0.15	CD4022	£0.90	CD4046	£1.30
CD4001	£0.18	CD4023	£0.20	CD4047	£1.10
CD4002	£0.18	CD4024	£0.80	CD4048	£0.55
CD4006	£0.98	CD4025	£0.20	CD4050	£0.55
CD4007	£0.18	CD4026	£1.70	CD4054	£1.10
CD4008	£0.98	CD4027	£0.60	CD4055	£1.40
CD4009	£0.58	CD4028	£0.98	CD4056	£1.35
CD4010	£0.58	CD4029	£1.15	CD4069	£0.40
CD4011	£0.20	CD4030	£0.55	CD4070	£0.40
CD4012	£0.20	CD4031	£2.20	CD4071	£0.23
CD4013	£0.52	CD4035	£1.30	CD4072	£0.23
CD4015	£0.98	CD4037	£0.95	CD4081	£0.20
CD4016	£0.50	CD4040	£0.95	CD4082	£0.23
CD4017	£0.98	CD4041	£0.82	CD4510	£1.30
CD4018	£1.00	CD4042	£0.82	CD4511	£1.60
CD4019	£0.55	CD4043	£0.98	CD4512	£1.40
CD4020	£1.10	CD4044	£0.94	CD4518	£1.25
CD4021	£0.98	CD4045	£1.40	CD4520	£1.25

LINEAR

Type	Price	Type	Price	Type	Price
CA3011	£1.05*	MC1303L	£1.48*	7270P	£0.25*
CA3014	£1.70*	MC1304P	£1.90*	UA710C	£0.40*
CA3018	£0.75*	MC1310PQ	£0.90*	727110	£0.30*
CA3020	£1.70*	MC1312PQ	£0.90*	UA711C	£0.32*
CA3028	£1.02*	MC1330P	£1.90*	727111	£0.32*
CA3035	£1.70*	MC1350P	£1.20*	UA723C	£0.45
CA3036	£1.35*	MC1351P	£1.20*	72723	£0.46
CA3024	£1.85*	MC1352P	£1.40*	UA741C	£0.24*
CA3046	£0.80*	MC1456G	£1.40*	741P	£0.20*
CA3052	£1.60*	MC1466L	£4.50*	UA747C	£0.70*
CA3054	£1.35*	MC1469R	£2.95	7274	£0.79*
CA3075	£1.50*	MC1496G	£2.95	UA748	£0.35*
CA3081	£1.50*	NE536	£0.98*	72748	£0.35*
CA3089	£2.10*	NE540	£1.50*	748P	£0.35*
CA3090	£4.25*	NE550	£0.95	SN76013N	£1.75*
CA3123	£1.90*	NE555	£0.32	SN76023N	£1.75*
CA3130	£0.93*	NE562B	£3.95*	SN76110	£1.50*
CA3140	£0.90*	NE565A	£3.50*	SN76115	£1.90*
LM301	£0.39*	NE567	£1.80*	SN76660	£0.75*
LM304	£1.60	NE568	£0.82	SL414A	£1.95*
LM308	£1.40*	NE569	£0.46*	TA4550B	£0.35
LM309K	£1.50	NE570	£0.46*	TAA621A	£2.00*
LM320.5V	£1.50	NE571	£0.46*	TAA661A	£1.65*
LM320-12V	£1.50	NE572	£0.46*	TAD100	£1.30*
LM320-15V	£1.50	NE573	£0.46*	TBA540Q	£2.20*
LM320-24V	£1.50	NE574	£0.46*	TBA6418	£2.25*
LM380-14p	£0.85*	NE575	£0.46*	TBA800	£0.90*
LM381	£1.55*	NE576	£0.46*	TBA810S	£1.05*
LM390N	£0.65*	NE577	£0.46*	TBA820	£0.80*
		NE578	£0.46*	TBA920Q	£3.40*
		NE579	£0.46*	TCA270S	£2.20*

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER AND YOUR NAME AND ADDRESS IN CAPS.

VAT

ADD 12 1/2% TO PRICES MARKED *. ADD 8% TO OTHERS EXCEPTING THOSE MARKED †. THESE ARE ZERO RATED.

POSTAGE AND PACKING

Please add postage as follows:
Small orders Medium orders Large orders
25p 50p 75p
Minimum order £1.00.

PANEL METERS

4" RANGE

Value	No.	Price
0-50U	1302	£6.70
0-100UA	1303	£6.70
0-500UA	1304	£6.70
0-1MA	1305	£8.40
0-50V	1306	£8.40

2" RANGE

Value	No.	Price
0-50UA	1307	£5.50
0-100UA	1308	£5.50
0-500UA	1309	£5.50
0-1MA	1310	£5.50
0-50V	1311	£5.50

MR2P TYPE

Value	No.	Price
0-50UA	1313	£5.40
0-1MA	1315	£5.40

MIN. LEVEL METER

No.	Price
1320	£2.80

BALANCE/TUNING

No.	Price
1319	£2.00

Vu METER

No.	Price
1321	£2.00

MINIATURE BALANCE/TUNING METER

No.	Price
1318	£1.95

MINI MULTI-METER

No.	Price
1322	£7.50

TRANSFORMERS

No.	Type	Price
2024	MT280 0-6V, 0.6V RMS	£1.50*
2025	MT150 0-12V, 0-12V RMS	£1.50*

No.	Secondary	Price
2021	6V-0-6V 100mA	90p*
2022	9V-0-9V 100mA	90p*
2023	12V-0-12V 100mA	95p*

No.	Secondary	Price	P & P
2026	6V-0-6V 1 amp	£2.80*	P & P 45p
2027	9V-0-9V 1 amp	£2.00*	P & P 45p
2028	12V-0-12V 1 amp	£2.60*	P & P 55p
2029	15V-0-15V 1 amp	£2.75*	P & P 60p
2030	30V-0-30V 1 amp	£3.45*	P & P 80p

STANDARD MAINS Primary 240V
Multi-tapped secondary mains transformers available in 1/2 amp, 1 amp and 2 amp current ratings. Secondary taps are 0-19-25-33-40-50V.

Voltagages available by use of taps:
4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 25-0-25V.

No.	Rating	Price	P & P
2031	1/2 amp	£5.50*	P & P 86p
2032	1 amp	£6.60*	P & P 86p
2033	2 amp	£8.40*	P & P £11.10

G.P. SWITCHING TRANS.

T018 SIM, T02N706/8
BSY27/28/95A. All usable devices. No open and shorts.
ALSO AVAILABLE IN PNP similar to 2N2906, BCY 70.
20 for 50p, 50 for £1, 100 for £1.80, 500 for £8, 1,000 for £14.
When ordering please state NPN or PNP

JUST OUT - NEW EDITION BI-PAK CATALOGUE

SEND FOR YOUR COPY NOW! ENCLOSING 65p† TO COVER POSTAGE AND PACKING.

WORLD SCOOP! JUMBO SEMICONDUCTOR PAK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, ICs and Zeners.

ALL NEW AND CODED
Approx. 100 pieces. Offering the amateur a fantastic bargain PAK and an enormous saving.
ORDER No. 16

High quality audio modules for Stereo and mono

S450 STEREO FM TUNER

Fitted with
phase lock-loop

£22.30

+ 40p p&p




The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the pre-set controls. Features include FET input stage, Vari-Cap diode tuning, Switched AFC LED Stereo Indicator.

FREQUENCY RANGE	88 - 108 Mhz
SENSITIVITY	3.0 uV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 kHz	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	20 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm x 110mm x 32mm

Stereo 30

COMPLETE
AUDIO
CHASSIS
£18.95

+ 40p p&p

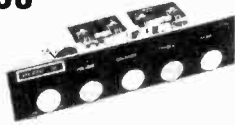

7 + 7w R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, main switch, fuse and fuse holder and universal mounting brackets.

OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than .5% (Typically .3%)
FREQUENCY RESPONSE	50 Hz to 20 kHz ± 3dBs
TONE CONTROL RANGE	± 12 dBs at 100Hz and 10kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V.A.C. rated at 1A
DIMENSIONS (Less controls and panel)	200mm x 130mm x 33mm

AL60

AUDIO
AMPLIFIER
MODULE
25 Watts RMS
£4.55

+ 25p p&p



25w
R.M.S.

This high quality audio amplifier module is for use in audio equipment and provides output powers up to 25 RMS with distortion levels below 0.1%.

OUTPUT POWER	25 Watts RMS
SUPPLY	30 - 50 V
LOAD IMPEDANCE	8 - 16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

AL80

AUDIO
AMPLIFIER
MODULE
£7.15*

+ 25p p&p



35w
R.M.S.

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.

OUTPUT POWER	35 Watts RMS
SUPPLY	40 - 60 V
LOAD IMPEDANCE	8 - 16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

AL250

POWER
AMPLIFIER

£17.25*

+ 40p p&p



125w R.M.S.

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50 - 80 V
LOADS	4 - 16 ohms
FREQUENCY RESPONSE	25 Hz - 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS O/P AT 1 kHz	450 mV
INPUT IMPEDANCE	33 K ohms
TOTAL HARMONIC DISTORTION	50 WATTS into 4 ohms 0.1%
	50 WATTS into 8 ohms 0.06%

AL30A

AUDIO
AMPLIFIER
MODULES

£3.75

+ 25p p&p



10w R.M.S.

This low cost 10 watt module offers the utmost in reliability and performance, whilst being compact in size.

MAXIMUM SUPPLY VOLTAGE	30 V
POWER OUTPUT for 5% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than .5% (Typically .03%)
LOAD IMPEDANCE	8 - 16 ohms
INPUT IMPEDANCE	50 K ohms
FREQUENCY RESPONSE	50 Hz - 25 kHz ± 3 dBs
SENSITIVITY	90 mV for full output
DIMENSIONS	90 x 64 x 30mm approx.

SPM80

STABILISED
POWER SUPPLY

£4.25

+ 25p p&p



Designed to power two AL60's at 15 Watts per channel simultaneously. Circuit Techniques include full short circuit protection.

INPUT A.C. VOLTAGE	33 - 40V
OUTPUT D.C. VOLTAGE	33 V nominal
OUTPUT CURRENT	1.0 mA - 1.5 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	105mm x 63mm x 30mm

PA100

STEREO
PRE-AMPLIFIER

£15.80

+ 40p p&p



A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution for the front end requirements of stereo amplifiers or audio units. The six push button selector switch gives a choice of inputs together with two filters for high and low frequencies.

FREQUENCY RESPONSE	20 Hz to 20 kHz x 1dB
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .07%)
SENSITIVITY	1 TAPE 100 mV/100 K ohms For an 100mV/100 K ohms output
INPUTS	2. RADIO TUNER 3. MAGNETIC P.U. 3.5 mV/50 K ohms) 250 mV.
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dBs at 75 Hz
TREBLE CONTROL RANGE	+ 10 - 20 dBs at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dBs (All inputs)
INPUT OVERLOAD	Better than 26 dBs (All inputs)
SUPPLY	20 to 40V
DIMENSIONS	300 x 90 x 33mm (less controls)

TRANSFORMERS

T538 For use with S.450 AL30A MPA30	Price: £3.20 + 55p p&p
Order No. 2036	
T2050 For use with Stereo 30	Price: £3.25 + 55p p&p
Order No. 2050	
BMT80 For use with AL60 SPM80	Price: £5.40 + 86p p&p
Order No. 2034	
BMT250 For use with AL250	Price: £6.35 + £1.10 p&p
Order No. 2035	

PS12 POWER SUPPLY

Designed for use with the AL30A S.450 and MPA30 in conjunction with transformer T538

INPUT VOLTAGE 17-20v AC	£1.30
OUTPUT VOLTAGE 27-30v DC	
OUTPUT CURRENT 800mA	
SIZE 60mm x 43mm x 26mm	25p p&p

MK60 AUDIO KIT

This kit enables you to build a complete 30w RMS stereo amplifier comprising of 2 x AL60 amplifiers - 1 x SPM80 stabilised power supply - 1 x BMT80 transformer - 1 x PA1000 pre-amplifier and a kit of parts to include front panel - knobs - head-phone socket on/off switch, neon indicator, together with complete instructions for construction.

Price: **£36.75** + 12½% V.A.T. + 62p p&p

TEAK 60 AUDIO KIT

This kit contains everything you require to put the finishing touches to your MK60 and give your amplifier that professional touch - contents: Teak veneered cabinet size: 16½" x 11½" x 3½" - aluminium chassis heatsink - front panel - bracket - back panel also sockets - nuts - bolts - fuse holders - solder tags etc.

Price: **£13.25** + 12½% V.A.T. + 86p p&p

TEAK 60 CABINET

Teak veneered cabinet only, measuring 425mm x 290mm x 95mm as supplied in the above mentioned Teak 60 kit. Ideal for use with our PA100 pre-amplifier and one of the complimentary modules. The ideal amplifier sleeve has not front or back panel.

Order No. 140. Price: **£7.00** + 12½% V.A.T. + 86p p&p.

TEAK 30 CABINET

Teak veneered cabinet designed mainly for use with our Stereo 30 chassis but had proved very useful to home constructors measuring 320mm x 235mm x 80mm comes complete with solid uncut front and back.

Order No. 139 Price: **£5.45** + 12½% V.A.T. + 70p p&p

MPA30 MAGNETIC CARTRIDGE PRE-AMPLIFIER



£2.95
25p p&p

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

SENSITIVITY	3.5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V - re earth
DIMENSIONS	110x50x25mm (inc DIN socket)

PA12

STEREO
PRE-AMPLIFIER



£7.10
30p p&p

The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL 20/30 Audio Amplifier Modules, the PS12 power supply and the T538 Transformer. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

FREQUENCY RESPONSE	20 Hz - 20 kHz (-3dB)
BASS CONTROL	± 12 dB at 60 Hz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	- 60 dB
SIGNAL/NOISE RATIO	- 65 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm x 84mm x 35mm

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER.

VAT

ADD VAT AT 12½% EXCEPT TO THOSE MARKED * WHICH ARE 8%.

BI-PAK

DEPT. PE4, P.O. Box 6, Ware, Herts

SAXON ENTERTAINMENTS LTD

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT
NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY,
TWIN SPEAKERS & LEADS

Standard 100W

£225 or Deposit **£28.80**
12 Months @ £21.18 or 24 Months @ £11.81

Super 200W

£275 or Deposit **£32.80**
12 Months @ £25.89 or 24 Months @ £14.44

GXL 200W (with twin 200 watt cabinets)

£349 or Deposit **£42.72**
12 Months @ £32.49 or 24 Months @ £18.11

BSR Decks - 17,000 Line Loudspeakers - Rugged Aluminium Trimmed Cabinets - Cue Light And Phones Output - Slave Output - Deck Lights/Motor Starts (GXL)

COMPLETE STEREO
ROADSHOWS - BUILT IN
SOUND TO LIGHT/SEQUENCER
& DISPLAY
TWO YEAR GUARANTEE

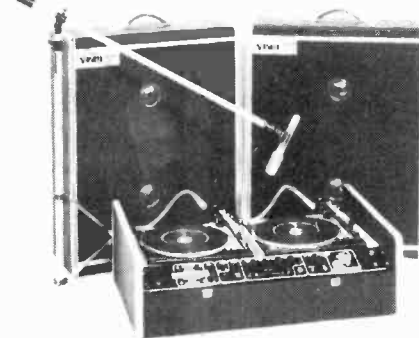


illustration shows GXL Centaur System
These systems feature full mixing for two decks tape & mic with monitoring facilities - override and are supplied complete with sound to light sequencer, display, speaker leads etc.

JUST PLUG IN AND GO!

MINI DISCO 100 WATT MONO SYSTEM

£179.50 Deposit **£24.66**
12 Months @ **£16.95**
or 24 Months @ **£9.45**

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system **£7.50**
EM507 Electret Mic **£15.00**
ECM 81 Electret Mic **£19.95**
Boom Stand **£15.50**
Carriage on all disco and PA systems **£10.00**
(Included in H.P. Prices)

**10% Deposit Terms
On All Orders
Over £150 - 12 or 24
Months - Low Interest**

D.I.Y. MODULES FOR ALL DISCO/P.A. AMPLIFIERS


SA308 30W 8 ohms 45V	£9.95*	SUPPLY FOR TWO MODULES	£10.90*
SA604 60W 4 ohms 50V	£13.25	SUPPLY FOR TWO MODULES	£13.50
SA608 60W 8 ohms 65V	£14.25	SUPPLY FOR TWO MODULES	
SA1204 120W 4 ohms 75V	£15.95	SUPPLY FOR ONE MODULE	£22.50
SA1208 120W 8 ohms 95V	£21.00	SUPPLY FOR TWO MODULES	
SA2404 240W 4 ohms 95V	£29.50	SUPPLY FOR ONE MODULE	

0.2% Distortion, 30Hz-20, KHz - 2dB, Fully Short/Open Circuit proof input sensitivity 240 mV to suit most mixers - D.C. & Output Fuses fitted.

TOP QUALITY COMPONENTS THROUGHOUT



DISCO MIXERS - COMPLETE OR MODULAR

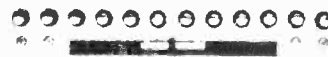

MONO OR STEREO
WITH AUTOFADE

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted - full instructions supplied.

FEATURES INCLUDE:

Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls - Full headphone monitoring - Crossfade - Professional standard performance.


MODULES	£22.50
Mono module	£33.50
Stereo module	£3.95
Panel	£5.50
Kit of knobs/sockets etc	£39.50
COMPLETE MIXERS (with case)	
Mono 18V	£57.50
Stereo 18V	£45.75
Mono mains	£63.75
Stereo mains	

COMPLETE LIGHTING CONTROL AT YOUR FINGERTIPS!



Lighting Control Unit Mk II	£44.50
4kW Sequencer - Sound Light Dimmers	
- Automatic Level Integrated Logic	Module £32.50
Circuitry	Panel £2.95
Three Channel Sound to Light	£26.75
3kW 1-240W input - master	Module £19.75
Plus channel controls	Panel £2.95

STROBE UNITS

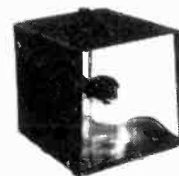

Pro-Strobe 4-6 Joules **£37.50**
Super Strobe 2-3 Joules **£22.50**
(Pro-Strobe has external trigger facility).

SPARES & ACCESSORIES - LOUDSPEAKERS & CABINETS

Rope Lights - Red or Multicolour	£22.00	Melos Echo Chamber	£59.00
per 12 ft.		Headphones	£7.50*
Rope Light Controller for up to 120 ft	£30.00	Sirens: English Police, USA Police,	
Fuzz Lights-Red/Blue/Yellow/Green	£22.80	Destroyer, Alien Voice Simulator	£7.50
Magnetic Cartridge Equalisers	£3.50*	Bulgin 8 way lighting plug/socket	£1.90

PROJECTORS - PLUTO - NEW LOW PRICES!!! CHOICE OF WHEEL/CASSETTE

P150 150W Tungsten	£34.00	Liquid wheels	£7.50
P500 100W Q.I.	£69.50	Cassettes	£8.00
P500 250W Q.I.	£79.50	Picture wheels from	£4.75
		(Wide choice available)	


100 Watt Chassis Loudspeakers 12"	£23.50	18"	£47.50	(Add £1.50 carr.)
Empty Loudspeaker Cabinets: Small 12"	£15.50	Large 12"	£21.50	Small 2 x 12"
	£15.50	Large 2 x 12"	£28	£22.50

PIEZO HORNS only **£7.50** **YES! - only £7.50**

(As fitted to our package PA system)

Direct from Motorola Inc., USA at an
UNBEATABLE PRICE

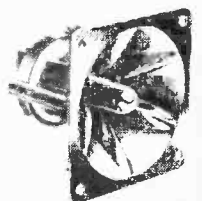No crossover required 4kHz - 30kHz rated
75W/8 ohms 150W/4 ohms use two per 100W
amplifier - Full instructions supplied.



Projector lamps: A1167 **£2.90**. M6 **£5.65**.
100W Spot lamps Red/Blue/Yellow/Green
£1.50 ea **£13.50** for 10
MD Spot Banks: 3-way 300W **£19.50**,
4-way 400W **£22.50**.
Bubble machines (optokinetics) **£36.50**

Strobe tubes 80W **£8.50**
ICI Vynide 50" wide **£3.50** Metre
Kickproof Grille 24" wide **£3.25** Metre
Kick Resistant Grill 50" wide **£3.25** Metre.
FULL RANGE OF RE-AN PRODUCTS IN STOCK
SEND FOR OUR BROCHURE NOW!!



PACKAGE P.A. SYSTEMS (2 Year Guarantee)

Complete with PIEZO horn columns fitted with 100 watt units (100 watt system illustrated)

100 Watt £149.50

Deposit £17.26

12 Months @ £14.60 or 24 Months @ £8.14


Includes 4 Channel 100 Watt Amplifier with Treble, Bass and Master Controls plus Leads and Twin Piezo Horn Columns (shown on right).

200 Watt £225.00

Deposit £28.80

12 Months @ £21.18 or 24 Months @ £11.81

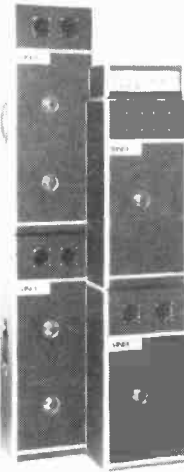zSix Mixed Inputs plus Three Sets of Bass and Treble Controls plus Slave Output and Master Control.



ACCESSORIES


Melos Echo Unit £59.00

A high quality Cassette Tape Echo Unit giving long tape life, infinitely variable echo depth and speed control. Suitable for all mics. and instruments.

High quality Boom Stand £15.50. Floor Stand £9.90. ECM81 Condenser Mic. - Removable Lead - Good Anti-Feedback £19.95.* EM507 Condenser Mic. - Good Value £15.00. Phasers £19.80.

D.I.Y. MODULES FOR P.A. SYSTEMS Mono or Stereo

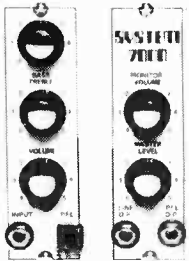Make your own mixer - Mono/Stereo - up to 20 channels with these, easy to wire modules - Available as PCB's or assembled on panels.



Input Stages Up to 20	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Mixer/Monitor (One only per system)	Mono PCB	£5.95	Mono C/W panel etc.	£8.95
	Stereo PCB	£9.50	Stereo C/W panel etc.	£12.50
Power supply for up to 20 channels		£9.50	Blank panel	£1.00


Send for free brochure for complete specification

Saxon AP100 Amplifier £45

Four mixing inputs - 100W into 4 ohms
Wide range bass & treble controls
+ master - Twin outputs

Saxon 150 Amplifier £59

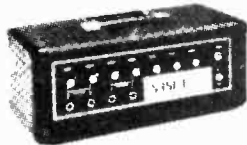Four mixing inputs - 100W into 8 ohms
150W into 4 ohms - wide range bass
& treble controls + master



All prices subject to 8% VAT except where asterisked (12 1/2%)
Shop premises open Mon to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm
Mail order dept open Mon to Fri 10 am - 4 pm - Ring 01-684 6385

TO ORDER

By Post Send your requirements with cheque crossed P.O. or 60p COD charge to address below - or just send your Access or Barclay Card Number - NOT THE CARD.

By Phone You may order COD, Access or Barclay Card.

Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS LTD.

327 Whitehorse Road, Croydon, Surrey.

All Enquiries Large SAE Please Brochures on request

AITKEN BROS.

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729

S-DEC

This, the most popular Board is designed solely for the use of discrete components and is particularly useful for basic educational purposes. (No. of Contacts: 70)
PRICE £2.43 inc. VAT.

T-DEC

This Board allows 2 T05 or 1 DIL IC Station to be used and so is primarily intended for discrete work or for linear IC application where considerable numbers of discrete components may be required. (No. of Contacts: 208)
PRICE £4.30 inc. VAT.

μ-DEC 'A'

The μ-Dec 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 T05 stations to be used but will accommodate discrete components with equal facility. (No. of Contacts: 208)
PRICE £4.31 inc. VAT.


μ-DEC 'B'

The μ-DEC 'B' is for similar uses as μ-DEC 'A', but has two 16 lead IC sockets as part of the Board. (No. of Contacts: 208)
PRICE £7.55 inc. VAT.

PANEL METERS

Dims 60mm x 45mm.
50μ amp, 100μ amp, 500μ amp, 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 1 amp, 2 amp, 25v dc, 30v dc, 50v ac, 300v ac, "S", "VU", 50-0-50μa, 100-0-100μa, 500-0-500μa.
PRICE £4.13 inc. VAT.

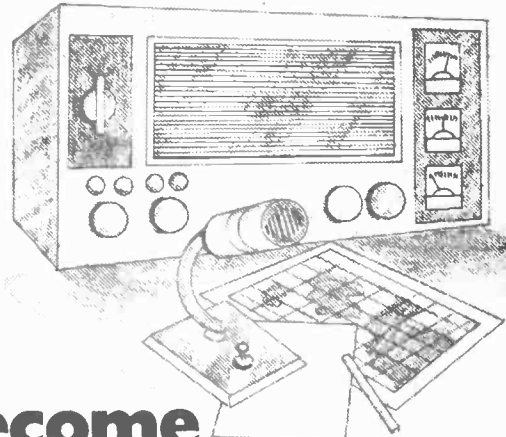POTS* CAPACITORS, BOXES, INST. CASES, DIN PLUGS, RESISTORS, ETC., ALWAYS IN STOCK. POSTAGE AND PACKING 20p EXTRA. CATALOGUE AVAILABLE PLEASE SEND 40p.



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA

PEK 4

Free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,

P.O.Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

(Block caps please)

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- * **SAVE ON TIME** - No delays in waiting for parts to come or shops to open!
- * **SAVE ON MONEY** - Bulk buying means lowest prices - just compare with others!
- * **HAVE THE RIGHT PART** - No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES - SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5% .10 of each value 22pF to 100pF. Total 210, £3.35

K002 Extended range, 22pF to 0.1µF, 330 values £4.90

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75
K004 Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. £12 series 5% 160V. Total 370 for £12.30

K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2, 2.3, 4, 7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/8 100/3. Total 170 tan for £14.20

K007 Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2, 2, 4, 7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M. £12 series. Total 610 resistors, £6.00

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes, 400mW 5%, BZ88 etc. 10 of each value from 27V to 36V, E24 series. Total 280 for £15.30

K042 As above but 5 of each value £8.70

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.15.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs, 1lb £1.00; 3lb £2.18; 10lb £5.60; 100lb £39.00

SIRENS

Work off 4 x HP7 batteries, emit very loud noise. Overall size 110 x 75 x 60mm. Use as Burglar Alarm in car, house, workshop etc. ONLY £1.95.

VERO OFFCUTS

Pack A, All 0.1"; Pack B, All 0.15"; Pack C, Mixed; Pack D, All 0.1" plain Each pack contains 7 or 8 pieces with a total area of 100 sq in. Each pack is £1.50. Also available by weight, 1lb £4.20, 10lb £32.50.

17 x 3 1/2" strips: 0.1" 2.20, 10 for £15; 0.15" £1.98; 0.1" plain £1.83.

TEXAS 741

8 PIN DIL
FULL SPEC.
100 off £19.50
25 off £5.50

TRANSFORMERS

Special - 12V 8A for only £4.00. 6-0-6V 100mA 85p; 9-0-9V 75mA 85p; 12-0-12V 50mA 85p; 100mA 95p; 12-0-12V 1A £2.90; 20-0-20V 2A £4.70; 20V 2.75A £4.

VERO PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.

Type
2518 120 x 65 x 40mm £2.24
2520 150 x 80 x 50mm £2.68
2522 188 x 110 x 60mm £3.72

Stopping front versions:

Type
2523 220 x 174 x 100/52mm £6.90
1798 171 x 121 x 75/37.5mm £4.65
Gen. purpose plastic potting box 71 x 49 x 24. In black or white 40p.
Hand controller box, shaped for ease of use in the hand, 94 x 61 x 23mm 64p.

S-DECS & T-DECS

S-DEC Breadboard £2.25
T-DEC Breadboard £3.95

RELAYS AND SOLENOIDS

Open construction relay with 2 10A c/o contacts, coil rated 24V AC, but works well on 6V DC 60p
240V AC enclosed, 11 pin plug in base, 3 10A c/o contacts. £1.20
240V AC open, 2 15A c/o contacts £1.50
Solenoid, rated 48V DC, but work on 24V. 10mm push or pull action. Single hole fixing. Size 27 x 18 x 15mm. Made by Varley. Only 40p.

1977/8 CATALOGUE NOW AVAILABLE - MUCH BIGGER AND BETTER, WITH 50p DISCOUNT VOUCHERS. ONLY 30p plus 15p POST.

WIRE AND FLEX

Flex pack - 5m of 5 diff colours, thick or thin. 25m for 30p.

POWER PACK

Wood grained metal case 90 x 80 x 75mm containing mains transformer giving 6V at 200mA, 2 co-ax sockets, PC board with 1 1/2 fuseholder R's C's etc. Only £1.

EDGE CONNECTORS

Special purchase of these 0.1 pitch double-sided gold plated connectors enables us to offer them at less than 1/3rd their original list price! 18 way 41p 21 way 47p 32 way 72p 40 way 90p 49 way 111p.

SOLAR CELLS

As used on space labs etc., these tiny cells give 50µA at 0.5V in sunlight. Ideal for powering small C-MOS projects etc. Can be banked for greater power output. Size 19 6.5mm. 3 for £1; 10 for £3; 25 for £7; 100 for £25.

CALCULATOR CHIP

Type C500 by GI - 8 digit 4 function + constant. Multiplexed for simple keyboard interfacing. Supplied with comprehensive data and 24 pin IC socket. Only £1.50.

DARLINGTON COMP. PAIR

Motorola type BD695A and BD696A 45V 8A 70W - gain 750 @ 4A PNP-NPN pair. Only £1.50.

MISCELLANEOUS IC's

All supplied with data.
MC3302 Quad comparator £1.20.
ITT7105 LED Digit driver, 8 for £1.
710 TO99 case Diff. comparator 40p.
MC1469R Voltage reg. £1.50.
ZN1304E Precision timer £2.25.
LM1303 Dual stereo preamp £1.40.
733 Diff. video amp £1.20. LM301 Op amp 40p. ITT326 2 x 2 & 2 x 3 1/2 TTL NAND gate, 10 for £1. SLD2128 Dual 128 bit static shift reg. £1.50.

Our retail shops at 21 Deptford Broadway, London, SE8 (01-692 2009) and 38 Lower Addiscombe Road, Croydon (01-688 2950) stock some of the advertised goods for personal callers only. Ring them for details.

All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

PE SUSTAIN UNIT

(OCT. 1977 PRACTICAL ELECTRONICS)




BUILD A SUSTAIN UNIT EQUAL TO THE BEST COMMERCIAL MODELS.

COMPLETE KIT - £7.95

ALL HIGH QUALITY COMPONENTS AS SPECIFIED.

DESIGNER APPROVED.

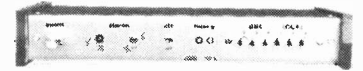

ORION
tuner

Complete set of semiconductors £4.99
LP1186 Tuner Head £9.60
Glass fibre PCB, printed with component locations £2.45

ORION
amplifier

Complete set of semiconductors £9.40
Glass fibre PCB, printed with component locations £3.50

FERRANTI SEMICONDUCTORS

BZV19	BFS98	16p	ZTX108	9p	ZTX320	16p	MOTOROLA
all values	ZS170	13p	ZTX109	11p	ZTX384	17p	BD699* £1.14
BC415	ZS178	54p	ZTX212	15p	ZTX384W	24p	BD700* £1.28
BFS60	ZS271*	23p	ZTX213	15p	ZTX450	16p	MC1310P £1.80
BFS61	ZTXA20	10p	ZTX214	17p	ZTX550	16p	MC1357PD £1.65
BFS97	ZTX107	11p	ZTX239	10p	ZTX4403	16p	SN76660N 75p

WE ARE THE EXPERTS!

We can supply any FERRANTI semiconductor device. SAE for quotation.
ZNA116E* £6.00 ZN1040E* £7.50 ZN1034E* £1.80 ZN424E £1.20
PE DIGITAL VOLTMETER (April 77) Send SAE for our special prices.

PE TV SOUND SEPARATOR

Complete set of semiconductors £2.30. High quality glass fibre p.c.b. £1 POSTAGE AND PACKING 15p per order. Orders over £5 post free. All devices are top grade, brand new and to full manufacturer's spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list. Prices do not include VAT—add 8% to items marked*, and 12 1/2% to all others

DAVIAN ELECTRONICS (MAIL ORDER ONLY)
13 Deepdale Avenue, Royton, Oldham OL2 6XD

24 HR. CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1kW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display/drivers, switches, LEDs, triac, complete with PCBs and full instructions. £14.85
Special white box (56 x 131 x 71mm) with red Acrylic window - undrilled £2.38
drilled £2.70

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated touch plates. Complete with easy to follow instructions.
TSD300K - TOUCHSWITCH and DIMER combined. ONE touchplate to switch light on or off. Brightness controlled by small knob. £5.62
TS300K - TOUCHSWITCH. TWO touch plates. One for ON one for OFF. £4.32
TSA300K - AUTOMATIC TOUCHSWITCH. ONE touch plate. Touch for ON and light stays on for preset time (variable from 2 secs. to 3 1/2 mins.). Ideal for stairs and hall. £4.32

LD300K - 300W LIGHT DIMMER KIT. Replaces conventional light switches. £3.02

AY-5-1230 Clock/Appliance Timer I.C. £5.24
LM3911 Thermometer/Temperature Control IC (with data) £1.08
NE555 Timer I.C. 8 pin dil 39p (3 for £1.08)
741 Op. Amp. I.C. 8 pin dil 26p (5 for £1.08)

TRIAC BARGAINS					
BC147	9p	BFY50	16p	2N6027 PUT	37p
BC148	9p	2N3055	43p	TIS43 UJT	26p
BC158	11p	TIP31A	54p	1N4148	5p
BC182L	9p	TIP32	54p	1N4004	5p

CMOS LOW PRICES

4000	19p	4012	19p	4023	19p	4077	49p
4001	19p	4013	55p	4025	19p	4501	22p
4002	19p	4015	98p	4040	105p	4510	162p
4007	19p	4016	55p	4049	54p	4516	162p
4011	19p	4017	98p	4050	54p	4519	61p

MINI MAINS TRANSFORMERS

6-0-6V 100mA	92p
12-0-12V 100mA	103p

OPTO ELECTRONICS

0.2" Red LED	11p	C280 Polyester Capacitors 250V d.c. (values in µF)
0.2" Green LED	23p	01 5p; 022, 033, 047, 068 6p; 01 7p; 5 8p; .22 9p;
0.2" Yellow LED	27p	33 12p; 47 13p; 68 19p; 1.0 22p; 2.2 39p.
DL727 Dual 0.5" Display	£1.62	RESISTORS 33W 5% 22 ohm to 10M ohm
		Push Button, push to make

QUANTITY DISCOUNTS ON REQUEST
PRICES VAT INCLUSIVE. ADD 25p P&P. MAIL ORDER ONLY TO:
T.K. ELECTRONICS (PE)
106 STUDLEY GRANGE ROAD, LONDON, W7 2LX.

HF 7948 FRONT END



£13.12
Inc. VAT P&P


TECHNICAL CHARACTERISTICS:

Output terminal for digital frequency meter; Antenna impedance - 75 to 300 Ohms; Frequency ranges 87.5 to 104 MHz or to 108 MHz; Sensitivity - 0.9 μ V 26dB signal to noise ratio + 75 kHz deviation; Inter-modulation 80dB Image rejection - 60dB; Tuning voltage - 1V to 11V; Total gain - 33dB; Intermediate frequency - 10.7 MHz; Power supply voltage + 15V; Power consumption 15mA; Dimensions 104 x 50 mm.

TECHNOLOGY:

Double sided epoxy printed circuit board with plated through holes. Dual gate effect transistors; Silvered coils.

**FI 2846
IF AMP AND DECODER**

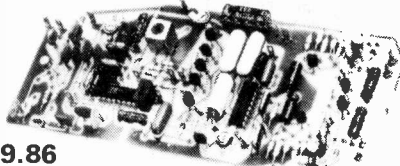

£9.86
Inc. VAT P&P

TECHNICAL CHARACTERISTICS:

Intermediate frequency - 10.7MHz. IF Bandwidth - 280kHz; Signal to noise ratio - 70dB with 1mV input; Distortion - mono 0.1%, stereo 0.3%; Sensitivity - 30 μ V up to the 3dB limit; Channel separation - 40dB at 1kHz; Pass band - 20 to 15,000Hz; Rejection at 38kHz greater than 55dB; Am rejection - 45dB; De-emphasis - 50 to 75 μ s; Pilot capture at 19kHz + 4%; Channel matching within less than 0.3dB; Output impedance - 100 Ohms; Output voltage - 500mV; Phase locked loop stereo decoder; Output for LED VU-meter; Null indicator; Outputs for AGC AFC and inter-station muting; Consumption - 55mA LEDs extinguished; 100mA LEDs illuminated; Power supply - 15V; Dimensions 195 x 76mm.

CIRCUIT TECHNOLOGY

Epoxy printed circuit board; Monolithic integrated circuits; ceramic filter.

**ALS 1500
STABILISED POWER SUPPLY**



£2.53
Inc. VAT P&P

TECHNICAL CHARACTERISTICS:


Output voltage - 15V; Max. output current - 500mA; Thermal coefficient less than 1mV/C; 15V power supply for modules HF 7948 and FI 2846; Supply protected against short circuit (power and current protection); Dimensions - 65 x 55mm.

TECHNOLOGY:

Double sided epoxy circuit board; Monolithic integrated circuit.

OPTOELECTRONIC OPTIONS



£8.06
Inc. VAT P&P

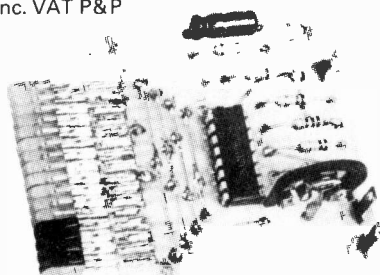

LED VU-METER
Station strength indicator


£8.77
Inc. VAT P&P

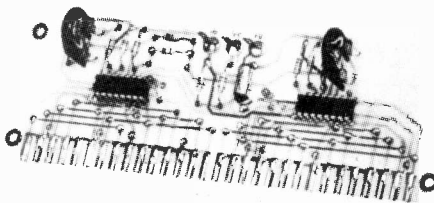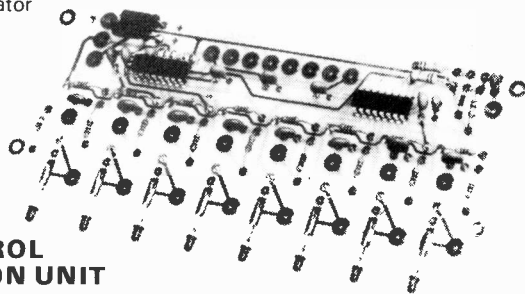**TOUCH CONTROL
PRE-SELECTION UNIT**
LED channel indication




£13.50
Inc. VAT P&P

ILLUMINATED POINTER
Station finder

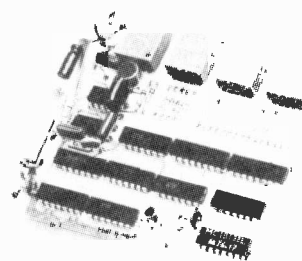

£22.74
Inc. VAT P&P

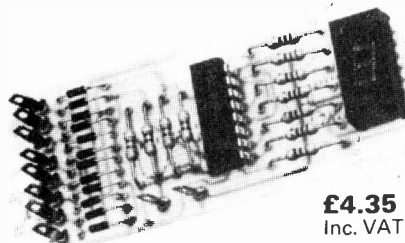FREQUENCY METER
Digital display of received station frequency.



£4.35
Inc. VAT P&P

NUMERICAL DISPLAY
Pre-selected channel number

CROSSLAND HOUSE
Telephone (0227) 63218

NACKINGTON

CANTERBURY · KENT

Telex 965780

DESIGN IDEAS

THE STRENGTH of P.E. is mainly based on the readers and this point is amply demonstrated by the *Extra Design Ideas* contained in this issue, in the form of seven pages of *Ingenuity Unlimited*. We make no apologies for presenting a product you have partly made yourselves—and of course charging 45p for it! Don't forget that we pay, quite handsomely some may say, for every original idea published.

We feel that the I.U. section of P.E. is outstanding in the quality and, yes, ingenuity of the submissions. We must hasten to add that we do not put them to the test of actual construction and they are presented as design ideas for you—the ever inventive readers—to build upon or modify for your own ends.

However when you have modified and incorporated why not give others a chance to benefit from your further experiments by returning the design to us for further inclusion? We get many, many I.U.'s submitted and a good proportion of them are published, but if one of yours is, or has been, rejected do not despair—it may only have been

because we already had similar ideas on file—by all means have another bash!

Very often we find that good and unusual projects come from I.U. ideas and we're always on the lookout for those too, so keep that in mind when you've built the latest "computer controlled egg timer" or "golf ball finder"!

READOUT

Even if you have no ideas to send we always like to see readers' comments on projects, features, the magazine in general and any other topical "electronic" subjects. Our *Readout* page appears irregularly but with some lively correspondence and comment from you we could improve on the regularity and present an interesting, topical and possibly controversial page for and from you each month. Such subjects as C.B. in Britain, hobby computers, electronic games, even the front cover of P.E. must at one time or another have aroused interest or disgust in some of you, so why not send us your views, get them aired in public and see how others feel.

If you want to start a computer club or arrange electronics evening classes

in your area we can help by publicising that too. Take the trouble to write and say what you feel, we can't promise we will publish your letter but we will try and air as many views as possible, even if we don't agree with them. *Readout* could be such an interesting feature and we are sure most of you enjoy reading it when it does appear; **if you don't, let us know!**

CATALOGUES

The presentation of another catalogue within P.E. will no doubt meet with the approval of all readers. It is interesting to note the vast range of items stocked by many companies that are, and can, never be advertised; they only appear in the catalogue. For this reason we recommend you to investigate, not just those presented with P.E., but the catalogues of all our advertisers. We are sure you will find it worthwhile.

For those regular readers who did not read this page last month the colour is here to stay. We hope you like it, we feel it will improve our presentation. It is, in fact, just one of a number of moves to improve the product.

Mike Kenward

EDITORIAL

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland TECHNICAL SUB EDITOR

Jack Pountney ART EDITOR

Keith Woodruff SENIOR ARTIST

George Dilkes SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Editorial Offices:
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

ADVERTISEMENTS

ADVERTISEMENT MANAGER

D. W. B. Tilleard

P. J. Mew REPRESENTATIVE

C. R. Brown CLASSIFIED MANAGER

Make Up and Copy Dept.
Phone: 01-261 5000

Advertising Offices:
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Phone: Advertisements 01-261 5000
Telex: 915748 MAGDIV-G

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Back Numbers and Binders

Copies of most of our recent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 65p each including Inland/Overseas p & p.

Binders for PE are available from the same address at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Cheques and postal orders should be made payable to IPC Magazines Limited.

Letters

Queries regarding articles published in PE should be addressed to the Editor, at the Editorial Offices, and a stamped, addressed envelope enclosed. We cannot undertake to answer questions regarding other items, nor to answer technical queries over the telephone.

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

PCB PRODUCTION KIT

An easy way to produce a number of p.c.b.s is to use master artwork and expose the circuit design onto the copper clad board using an ultraviolet exposure unit. All the necessary materials for this method of p.c.b. production have been available for sometime. Now a company called **Mega Electronics Limited** have introduced a complete p.c.b. kit. This kit enables the user to produce his own printed circuit boards, right from the preparation of the artwork to the finished circuit board.

The kit, which is called **Photolab**, consists of the ultraviolet exposure unit, drafting aid and film, positive resist coated epoxy glass laminate sheets, developing and etching trays, labels, a high-speed drill and all the necessary developers.

This unit can handle boards up to 9 x 6in and is priced at £44.50 complete.

For further information contact **Mega Electronics Ltd.**, 9 Radwinter Road, Saffron Walden, Essex CB11 3HU.

ELECTRONIC MULTIMETER

The Miselco "Tester Electronic" from **Alcon Instruments** is a 48 range instrument constructed with "Self Service" in mind. This facility allows a damaged board or movement to be quickly and easily replaced by the user.

The instrument offers a 1M Ω /V sensitivity for both a.c. and d.c. except on the 300V and 1kV ranges where it is 100k Ω /V.

Accuracy is 2.5 per cent on a.c., 1.5 per cent on the d.c. and resistance ranges. The very clear scaleplate includes an anti-parallax mirror and a centre zero scale for galvanometric and null detection applications.

Maximum current measurement is 1 amp f.s.d. on a.c. and d.c. whilst there are optional high voltage probes which extend the voltage range to 3kV on both a.c. and d.c. or 30kV on d.c. only. Five resistance ranges cover 10k Ω f.s.d. to 100M Ω f.s.d. and power measurements can be made from -70dB to +51dB.

An optional built in signal injector is capable of providing a 1kHz modulated 500kHz signal at 20V peak-to-peak, so rich in harmonics, as to be detectable up to 500MHz.

The **Tester Electronic**, complete with carrying case and leads costs £48.20 exclusive of VAT.

For further information contact **Alcon Instruments Limited**, 19 Mulberry Walk, London SW3 6DZ.

LOGIC ANALYSER

A new modular instrumentation system available from **Tektronix UK Limited** enables any oscilloscope or X-Y monitor with more than 500kHz bandwidth to be converted into a versatile logic analyser or word recogniser.

The LA501 logic analyser system incorporates 4096 bits of storage, which may be used as four channels of 1024 bits, eight channels of 512 bits or 16 channels of 256 bits according to the required application.

On the oscilloscope screen, stored data is displayed in the form of a timing diagram, in groups of four. Each trace displays high and low logic states and a magnifier provides the capability to zoom in on any segment of the timing diagram. Channel to channel timing comparisons are simple because any trace can be moved vertically and positioned next to any other.

The WR501 16 bit parallel word recogniser with digital delay produces trigger pulses when a preselected parallel word occurs, giving fast access to almost any unique word in the data stream.

For further information contact **Tektronix UK Ltd.**, Beaverton House, P.O. Box 69, Harpenden, Herts.

NEW CASSETTE TAPE

An iron oxide tape, **Ferro Super LH1**, has been developed by **BASF** in Germany to give the optimum performance on the widest possible range of Japanese recorders using high bias currents in the record head.

Cassette recorder manufacturers in Japan have moved away from the DIN standard to a high bias situation. The standard was established by the DIN Committee with Philips, the inventors of the compact cassette. However, manufacturers have not adhered to the standard, each one preferring to choose his own personal bias setting.


The majority of high bias recorders have bias settings in the range of 1.5dB to 2dB. Using this range as its datum, **BASF** developed **Ferro Super LH1**. The bias settings are midway between 1.5dB and 2.0dB making it suitable for a wide range of high bias recorders.

The tape is available in C60, C90 and C120 cassettes, with a suggested retail price of £1.66, £2.22 and £2.90 (exc. VAT at 8 per cent) respectively.

ALARM CALCULATOR

The latest calculator in the **Casio** range is the **AQ810** alarm computer. This versatile unit has the normal range of calculating functions plus an alarm clock and two count down timers. It can be used as a calculator whenever required, irrespective of the timing mode it is in.

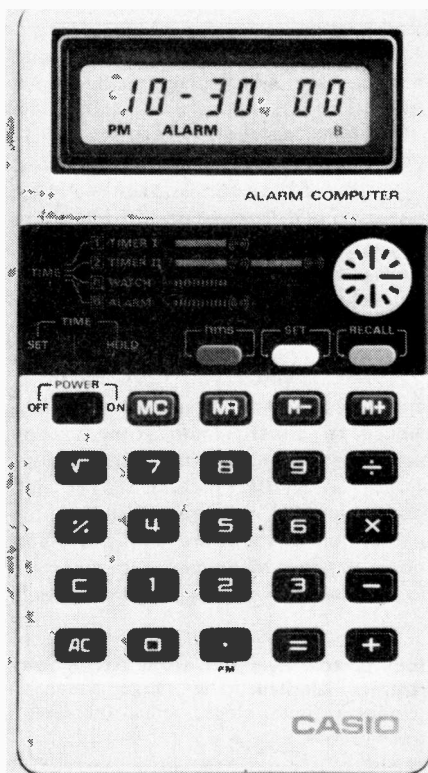The calculator covers the four basic functions, square/powers, square roots, automatic access to memory, percentage and time calculations. The capacity of the unit for time calculations is 99 hours 59 mins 59 secs.



The clock can be used in the 12 or 24 hour mode and the alarm will sound for 10 secs after which it will automatically clear itself.

The two count down timers sound the alarm after a predetermined time period has elapsed, timer I automatically clears itself and timer II will repeat itself everytime the preset period has elapsed.

The accuracy of the clock is within ± 3 secs per day, it has a liquid crystal display and the unit gives approximately 3000 hours continuous operation on two silver oxide batteries.

The calculator is housed in an attractive carry case and really is just the right size for the pocket. The flip top case allows rapid operation of the unit.

The calculator costs £19.95 inclusive of VAT, post and packing and further details can be obtained from **Tempus, Talk of the Town**, 19-21 Fitzroy Street, Cambridge CB1 1EH.

PULSE GENERATOR AND P.S.U.


The setting up of different types of power supply units for operating t.t.l., CMOS and op amps can be both time consuming and awkward.

The latest development of **Mechtric Engineering Ltd.** overcomes this problem by combining the essential power supplies necessary for CMOS, t.t.l. and op amps together with a pulse generator. The power supplies and generator outputs are all protected against short circuits.

The CMOS supply is variable from 4-16V d.c., the t.t.l. is 5V d.c. and the balanced op amp supply is variable from 6-21V d.c.

The instrument has two square wave outputs one leading the other by 90 degrees with a frequency range of 0-45Hz to 500kHz.

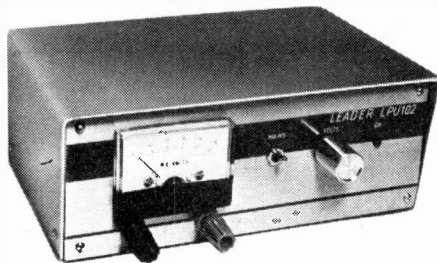The price of the instrument is £198-00 excluding VAT and further details can be obtained from **Mechtric Engineering Ltd.**, 12 Brunel Road, Manor Trading Estate, Benfleet, Essex SS7 4PS.



Bench Power Supply LPU102

ELECTRONIC KITS

A new range of **Leader** electronic kits is now available from **Arrow Electronics Limited**. The range which includes a digital clock, bench and laboratory power supply and a test bench oscillator have been extensively tested and are of guaranteed "bug proof" design.

With each kit is a comprehensive manual of building instructions, fully finished case/chassis including all the necessary nuts and bolts. The front panel is lettered and has a distinctive horizontal red stripe.

For further information contact **Arrow Electronics Limited, Leader House, Coptfold Road, Brentwood, Essex.**



Laboratory Power Supply LPU 103

P.E. will shortly be assembling and reviewing the **Leader kit LPU103, Laboratory Power Supply.**

CABINET

No more hole cutting! That's the theme behind the Instrument Case Type PDS by **Amatek**.


The moulded plastics front panel of this box is designed to take a wide combination of push buttons (including RS and Doram types), toggle switches, 4mm terminals, indicator lamps, and also has a location for a rotary switch. By laying on the table plate and cutting with an art knife to expose the holes which are to be used, a piece of equipment can acquire an instant and effortless professional finish.

The case measures 178mm x 80mm x 152mm, is made of p.v.c. coated aluminium, and has a frontal display aperture of 70mm x 29mm.

Various accessories are available, including display modules, 4mm terminals, and fuse-holder and cable clamp kits.

The basic case costs £8-50 complete. For further details contact:

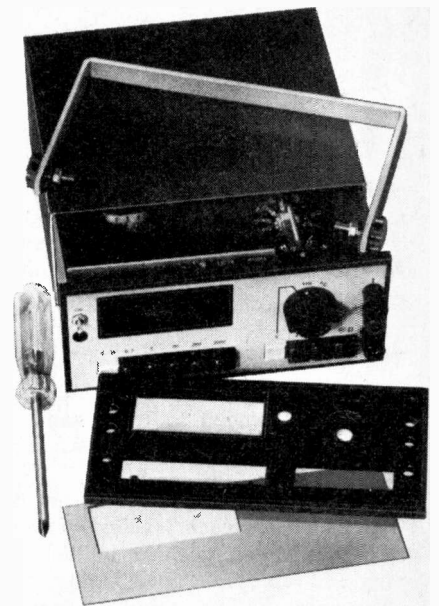Amatek, 22 Bardsley Lane, Greenwich, London, SE10 9RF.



DIGITAL WATCHES

Pulse, pulse, digital time is 10:58 and 50 seconds; press a button, digital month, date and day is 4:12 MO; press another button for Paris time, Kuwait time, Hong Kong time, Tokyo time, Honolulu time, San Francisco time, Chicago time, New York time, São Paulo time.

This all seems a long way from three chickens past Mickey Mouse but if you commute by Concorde then Casio's World Time LCD digital watch could well save you many frustrating synchronizations to local times. For the traveller interested in minimum "lift off" to "touch down" times the Casio Chronograph has a one hundredth second stopwatch which can be started then left to count away unobserved while normal time read out resumes display. For sports activity measurers the Chronograph can

give normal time, net time, lap time and first and second place times.

The liquid crystal display is quick to change and easily viewed if the face of the watch is nearly at right angles to line of sight. At more than 45 degrees from vertical the structure of the LCD causes a faint, shadowed image. At dusk a third button supplies a bright white light across the display.

Time keeping is better than half a minute per month and with only the 29th February to be coped with (fourth and final button) the days of winding and setting to GMT appear to be past.

Chronograph, £64-95. World Time—Price and availability to be announced shortly.

Further information is available from: **Tempus, 19-21 Fitzroy Street, Cambridge.**



THIS project should appeal to those constructors who already have a taste for electronic games, and those who are looking for an interesting application of a logic circuit on which to try their skill.

The game itself is essentially a contest of speed and manual dexterity between two players, and it has proved to have almost instant appeal to gamesmen of all ages. This attraction seems to be based on the fact that while beginners are quick to grasp the idea, the game is at all levels limited only by the players' dexterity; not by the circuitry. Thus there is never a point at which the game can be mastered and hence devoid of any further challenge.

THE GAME


Fumble-Nudge is an easy game to play, and only a few minutes are needed to understand the basic details, and reference to Fig. 1 will help while reading the following explanation.

The playfield consists of a row of 16 l.e.d.s, the inner 14 of which are each labelled with a four bit binary code representing their position in the row, while the l.e.d.s at either end represent "goals" and are unmarked.

The game begins with D15 (code 1000) being illuminated, and this l.e.d. represents the "ball" during play. The object of the game is for both players simultaneously to try to force the ball into the goal at their opponent's end of the field by a series of "fumble" and "nudge" sequences, which operate as follows:


Each player has in front of him four "Fumble" switches and a "Nudge" button, and in order to move the ball towards his opponent his four "Fumble" switches must first be set to equal the binary code directly alongside the ball (in this case 1000). Having done this the Nudge button becomes effective and when pressed it advances the ball a random one, two or three positions along the playfield.

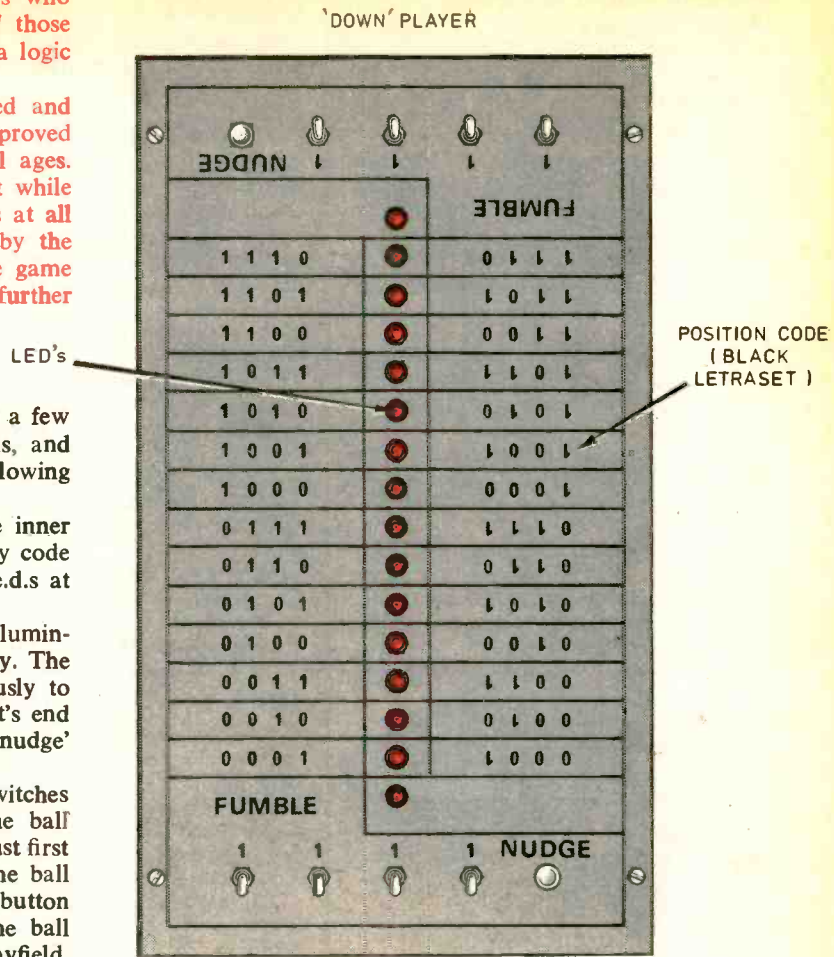Only the first valid Nudge signal is accepted by the circuitry so that the quicker of the two players succeeds in moving the ball towards his opponent. If, for example, the "Down" player wins the first exchange, the ball may



'UP' PLAYER
Fig. 1. Playfield

FUMBLE

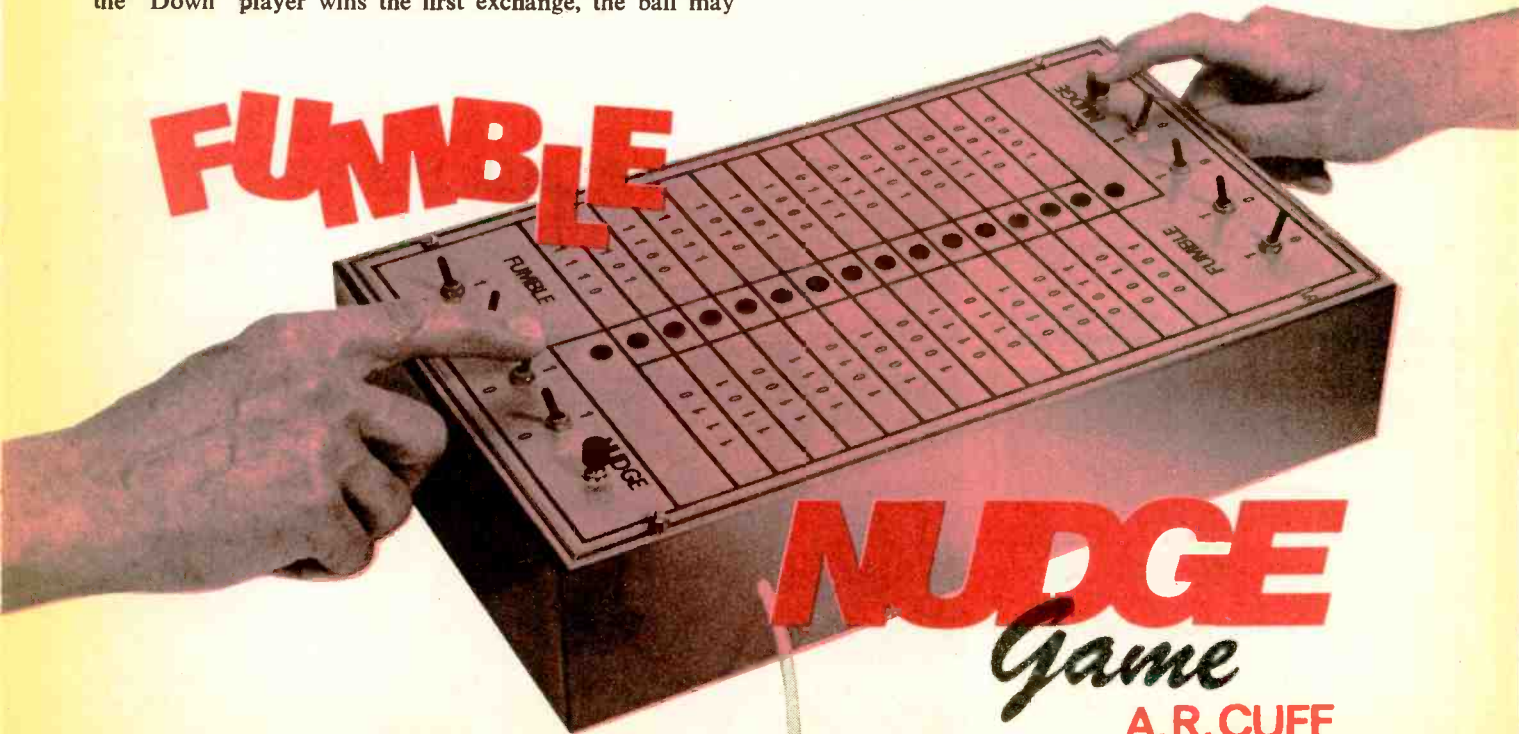

NUDGE
Game
A.R. CUFF

have advanced two positions and D13 (code 0110) is then lit.

To nudge the ball again both players must race to set up the new code (0110) on their "Fumble" switches before a second nudge is accepted. Thus the play continues until one player succeeds in nudging the ball into his opponent's goal to win the game.

CIRCUIT DETAILS

A block diagram illustrating the operation of the circuit is shown in Fig. 2. At the start of each game, the 74193 is preset to the 1000 position and D15 lights up. Each of the 4 output bits of the 74193 is also fed to one input of an EXCLUSIVE-OR gate (7486), the other input of

Fig. 3. Circuit diagram

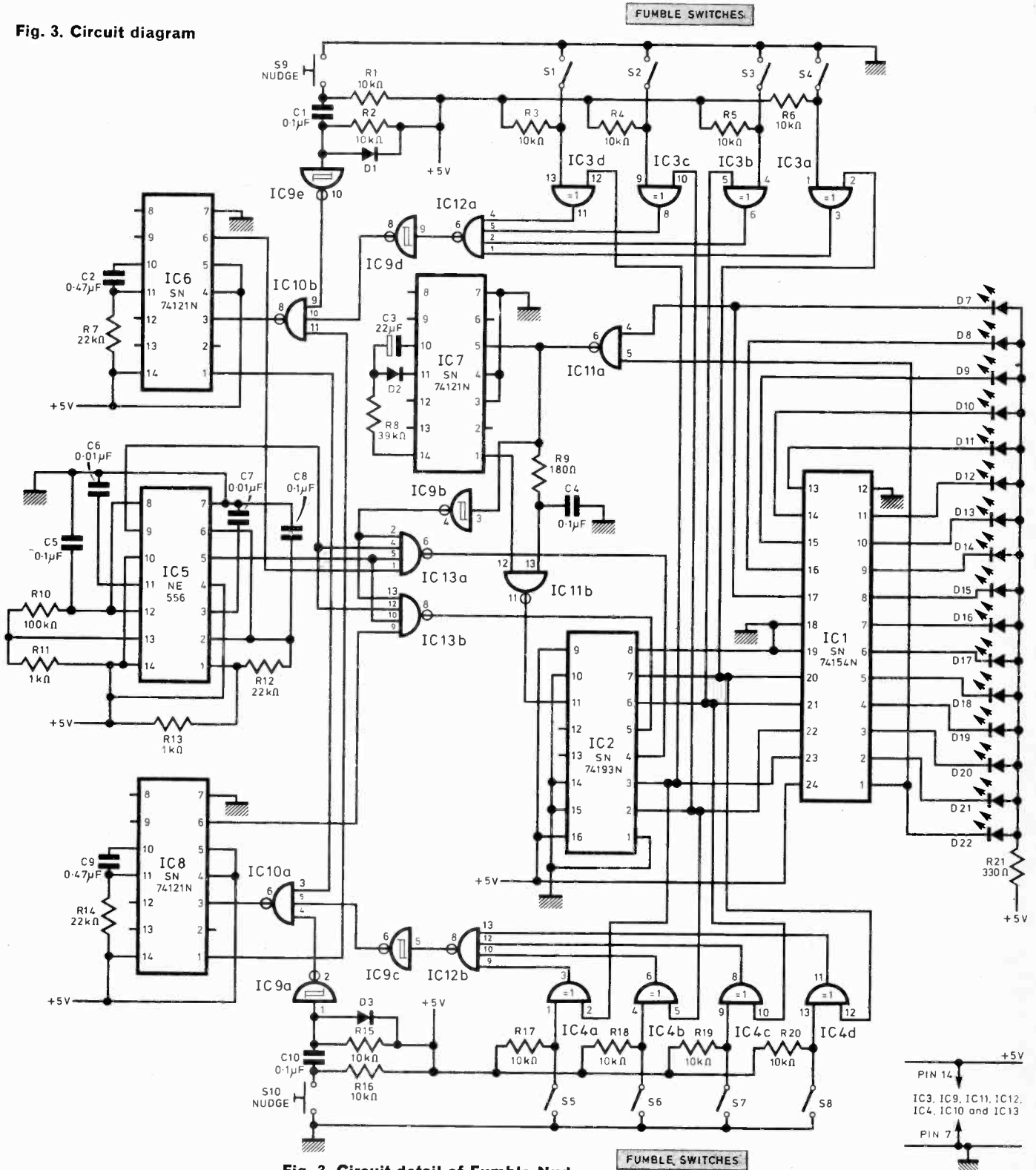


Fig. 3. Circuit detail of Fumble Nudge

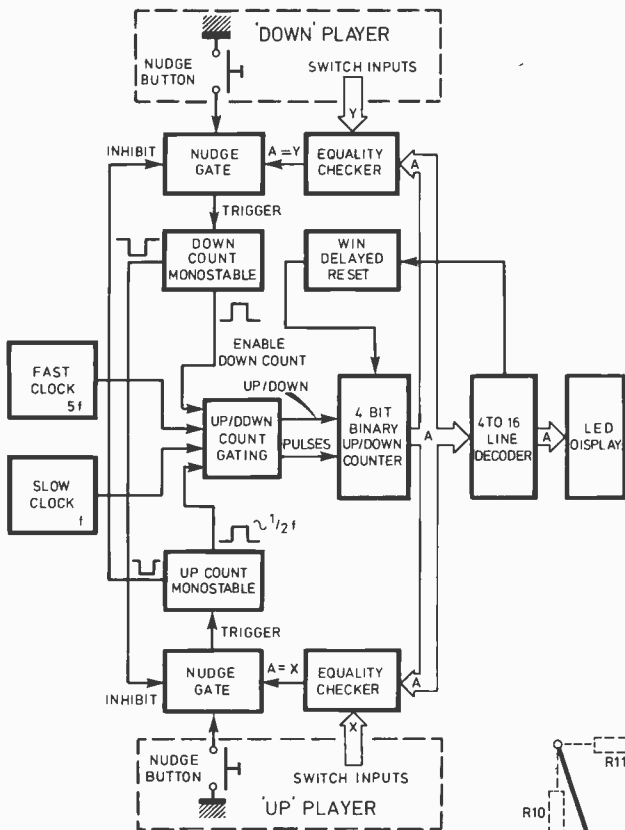


Fig. 2. Block diagram of Fumble Nudge

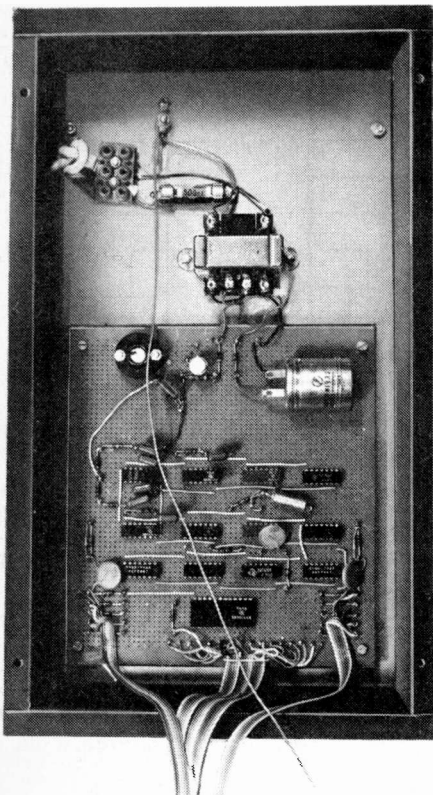


Fig. 7. Layout of power supply, i.c.s. and ribbon cabling

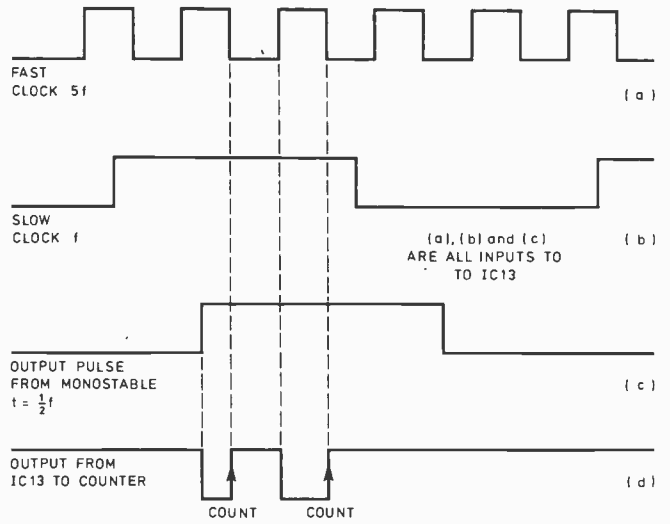


Fig. 4. Timing diagram

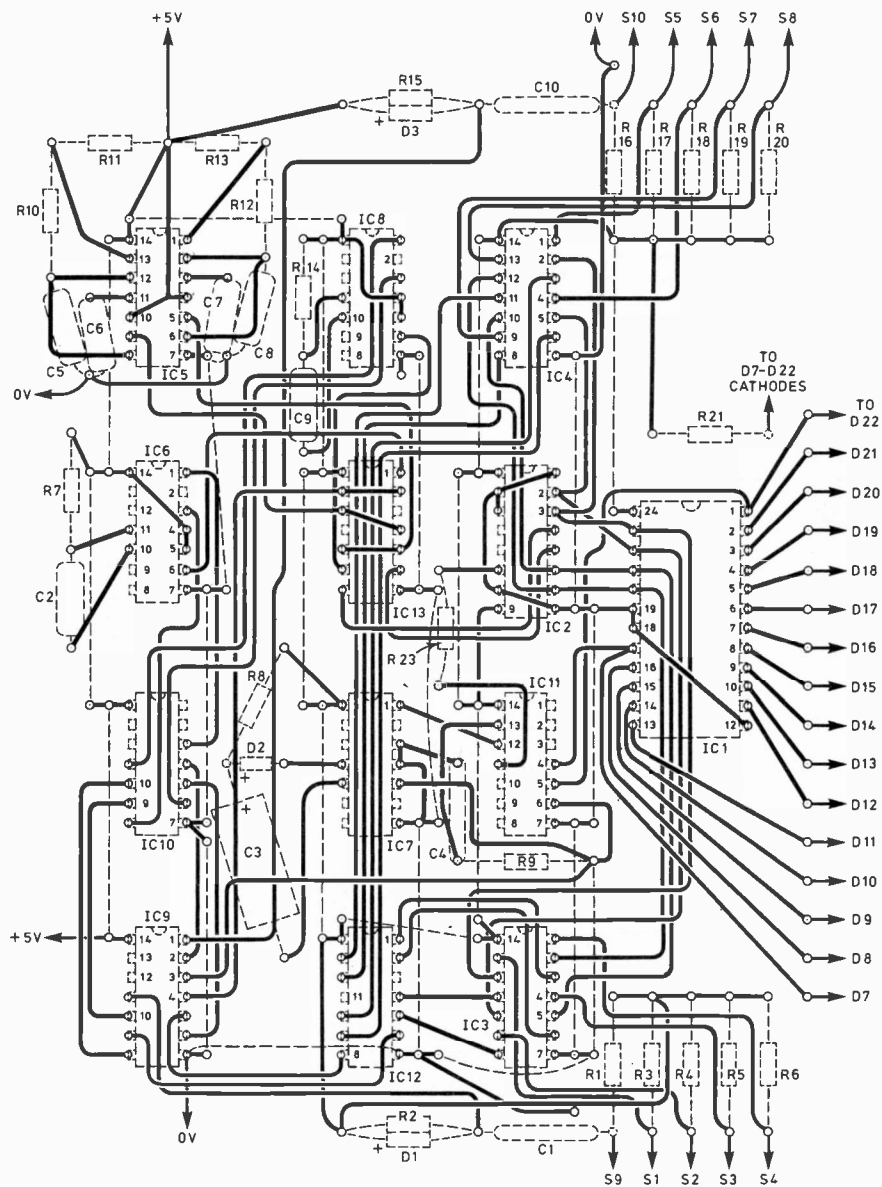


Fig. 6. i.c. layout and wiring

which is derived from one of the player's "Fumble" switches. Only when a player has set the correct code on his switches are the outputs from the EXCLUSIVE-OR gates all at logical 1. The occurrence of this condition is detected for each player by the NAND gate IC12 (7420), and is used to open the appropriate "Nudge" gate. Pressing the "Nudge" button gives a short pulse which, when passed through the "Nudge" gate, triggers a monostable (74121). Only the first player to nudge at this time gains access to his monostable since the UP COUNT inhibits the DOWN NUDGE gate, and vice versa.

If, for example, the "Up" player has been successful then the UP COUNT line of the 74193 is enabled for a time of approximately $1/2f$ seconds. During this period, the FAST- and SLOW-CLOCKS are also gated to the UP COUNT line via IC13. Their frequencies of f Hz and approximately $5f$ Hz are designed to give a random one, two or three counts for each nudge. (The operation of this can be seen in the timing diagram, Fig. 4).

The frequency f can be any convenient value. (In the prototype it is about 70 Hz).

After each nudge, the output from the EQUALITY CHECKERS are no longer "true" and the NUDGE buttons are inhibited until the new input code is set up. When the illuminated l.e.d. eventually reaches one end of the playfield this state is detected by IC11 and the WIN DELAYED RESET mono is triggered. This provides a short pause

to enable the win to be noted before presetting the 74193 with the starting code for a new game.

Power for the game is provided from the mains via a simple series regulator (Fig. 5), and current consumption is 200-250 mA. Only one decoupling capacitor is used as this was found to be adequate, but for some layouts it may be necessary to fit one further $0.1\mu\text{F}$ capacitor for every three i.c.s to ensure freedom from supply noise problems.

CONSTRUCTION

A suggested layout of the logic i.c.s is shown in Fig. 6. All the components together with the power supply can be accommodated on a single piece of Veroboard approximately 150mm square, and the arrangement is not critical.

The circuit board and the mains transformer are mounted on an aluminium sheet which then forms the base of the game box. The l.e.d.s and switches are fitted on a further aluminium panel which is painted and lettered to provide the playfield. The construction of the box and front panel are detailed in Figs. 1 and 7. ★

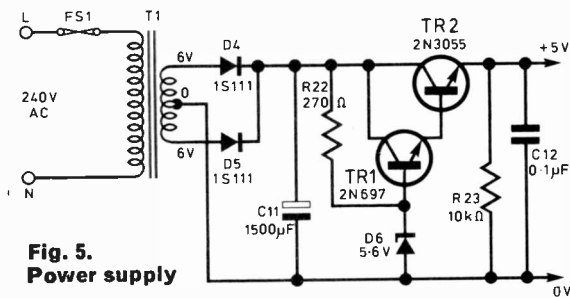


Fig. 5. Power supply

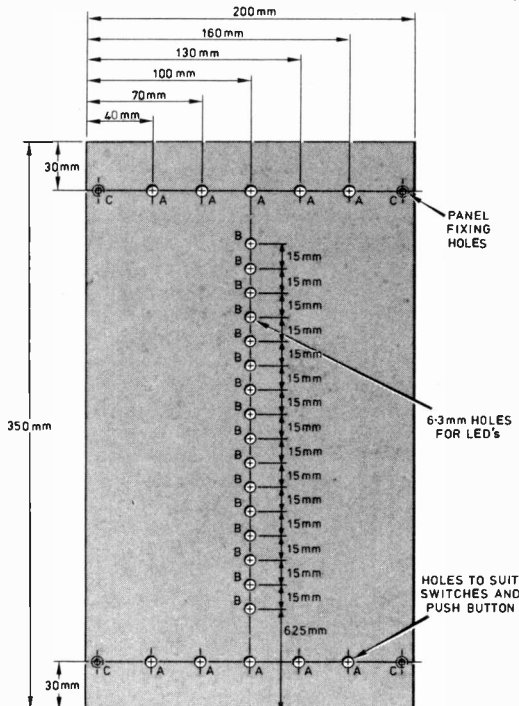


Fig. 8. Hole positions

COMPONENTS . . .

Resistors

R1-R6, R15-R20, R23	10kΩ (13 off)
R7, R14, R12	22kΩ (3 off)
R8	39kΩ
R9	180Ω
R10	100Ω
R11, R13	1kΩ (2 off)
R21	330Ω
R22	270Ω
All resistors $\frac{1}{4}$ W 10%	

Capacitors

C1, C4, C5, C8, C10, C12	0.1µF (6 off)
C2, C9	0.47µF (2 off)
C6, C7	0.01µF (2 off)
C11	1,500µF elect.
C3	22µF elect.

Diodes

D1-D5	1N4004 or similar
D6	5.6V Zener (400 mW)
D7-D22	T1L 209 or similar

Transistors

TR1	2N697
TR2	2N3055 or 2N697 with heatsink


Integrated Circuits

IC1	SN 74154N	4 to 16 line decoder
IC2	SN 74193N	Up/down counter
IC3, IC4	SN 7486N	Quad EXCLUSIVE OR
IC5	NE 556	Dual timer
IC6, IC7, IC8	SN 74121N	Monostable
IC9	SN 7414N	Hex Schmitt Inverter
IC10	SN 7410N	Triple 3 input NAND
IC11	SN 7400N	Quad 2 input NAND
IC12, IC13	SN 7420N	Dual 4 input NAND

Miscellaneous

S1 to S8	S.P.S.T. Toggle Switches (8 off)
S9, S10	S.P.S.T. Pushbuttons (2 off)
T1	Mains Transformer 6-0-6V at 300 mA
FS1	500mA
0.1 inch matrix Veroboard and pins, fuseholder, 2A terminal block, lettering for playfield	

EXTRA DESIGN IDEAS

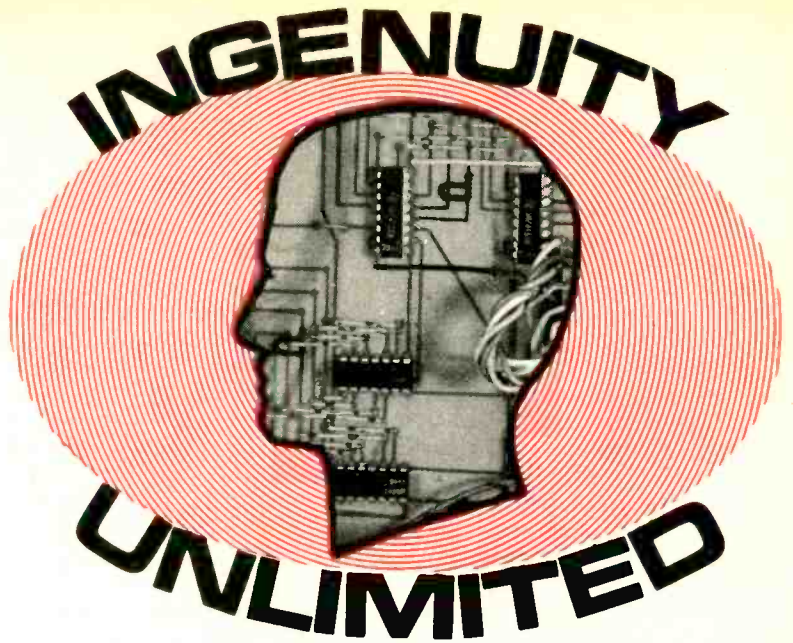

FAST NI-CAD BATTERY CHARGER

THE usual form of constant current nickel cadmium charger is designed to charge a battery of cells fully in 12-14 hours. However, it is often necessary to be able to charge a battery in a shorter time. This circuit is capable of charging 1-8 1.25V cells in 8 hours.

A flat battery is connected to the output terminals and the "Boost" button S1 depressed momentarily. The l.e.d. will then extinguish whilst a constant high charge current is delivered to the battery.

When the terminal voltage exceeds a preset level, the l.e.d. comes on and the battery is trickle charged until disconnected. The trickle charge cur-


rent is approximately $\frac{1}{3}$ of the high charge current. With the l.e.d. on, the battery can be left charging indefinitely without causing any damage.

A level about 10 per cent greater than the nominal battery voltage is set on the preset potentiometer. The charge current is set by the value of the emitter resistor of TR1. 16Ω gives a charge current of about 130mA which is satisfactory for charging HP7 size (AA) cells.

Both TR1 and TR4 should be mounted on adequate heatsinks.

R. Dudley,
Berkhampstead,
Herts.

Fig. 1

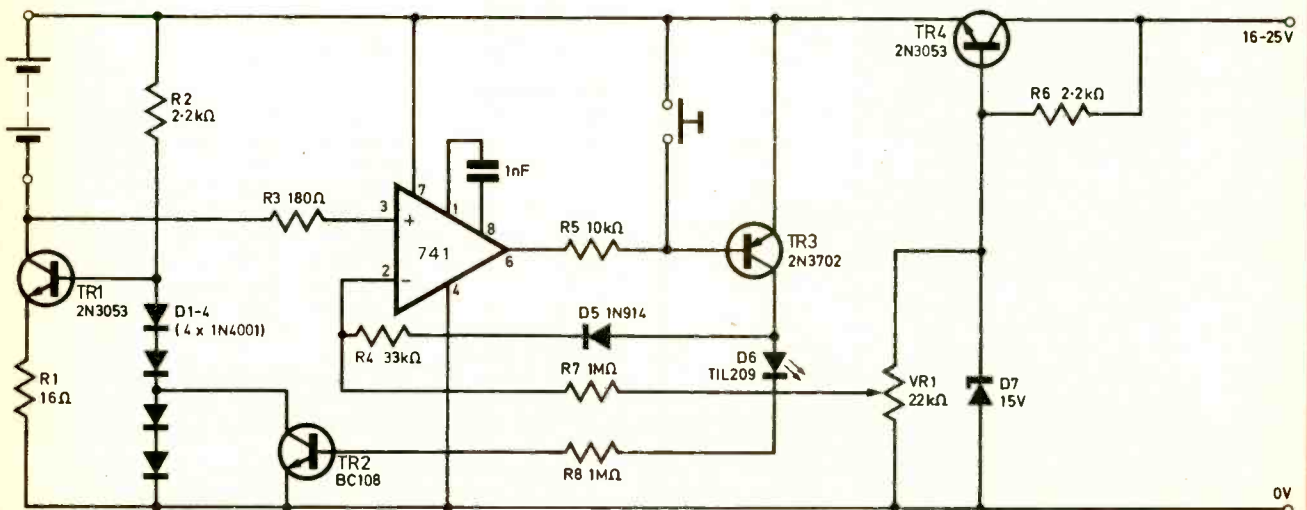

MAGNETIC TAPE SPEEDOMETER

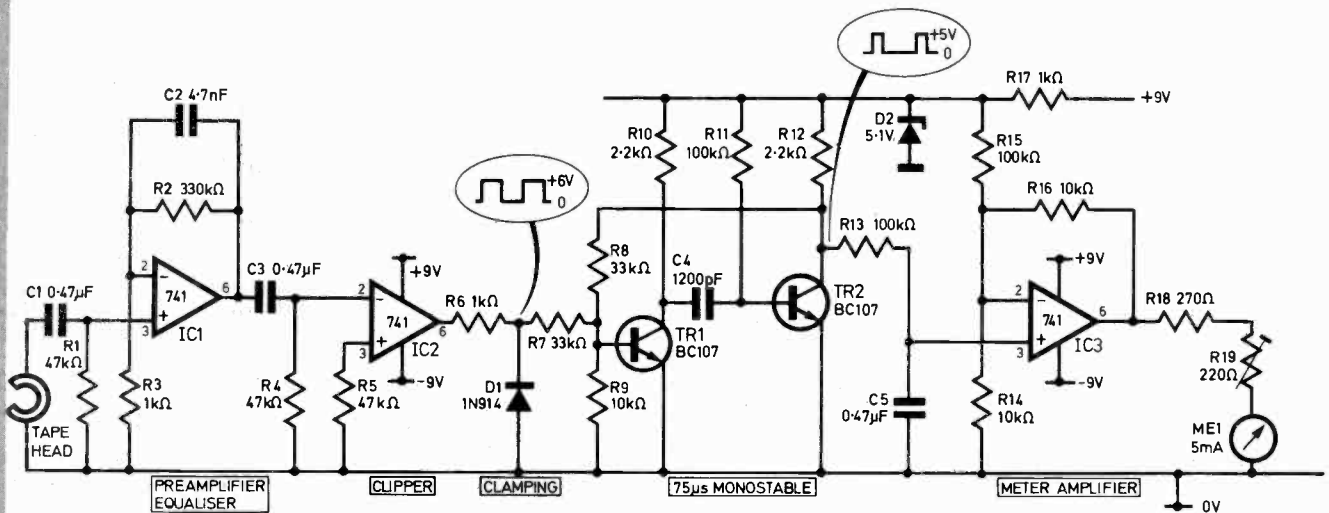


Fig. 1

Sq. wave recorded at $3\frac{1}{2}$ i.p.s.	F.s.d. of meter
5kHz	5cm/s
1kHz	25cm/s
500Hz	50cm/s
250Hz	1m/s

THIS circuit (Fig. 1) was designed as an aid to teaching about motion and collisions, as an alternative to the more usual "ticker-tape". No doubt readers could think of many other applications.

A square wave tone is recorded on an ordinary piece of recording tape (open reel), so that a fixed number of pulses is recorded on the tape per cm. The tape is attached to the trolley used in the motion experiment, and drawn past a playback head. The frequency of the signal from the playback head is proportional to the speed at which the tape is travelling. The circuit converts this frequency into a meter reading.

The circuit is designed to work under all sorts of adverse conditions, including mild tape "drop out", and ailing batteries. IC1 is a tape head preamplifier and equaliser. The output from most tape heads increases with frequency, and this is compensated by the capacitor C2 in the feedback network. The stage has a gain of about 50dB at low frequency, falling off at 20dB per decade above 100Hz.

The second stage, IC2, is a clipper, producing a square wave of the same frequency as the signal from the tape head, and this square wave trig-

gers a monostable consisting of TR1 and TR2. The monostable produces pulses, each 75µs wide and 5.1V high, at the frequency of the incoming signal. It is worth mentioning the function of the Zener diode, D2, here. It is often not realised that during the action of a monostable (or for that matter an astable), the base of one of the transistors (TR2) goes negative by an amount equal to the supply rail. Now most modern small-signal transistors cannot sustain more than about 5V reverse bias across their base-emitter junctions before they avalanche, which would give a rather shorter pulse than expected. The Zener diode has been included for two reasons; to keep the supply rail down to 5V, and to stabilise the amplitude of the output pulse from the monostable.

The pulses from the monostable are then smoothed and amplified by IC3 to drive the meter. The waveform on the collector of TR2 does not actually go down to 0V, but to about 0.2V depending on the transistor. R15 has been included to offset this effect. If the meter gives a positive reading with no tape passing the head, R15 may need to be reduced (or increased if a negative reading is obtained).


The prototype was built into a small box with a tape head, rescued from a defunct tape recorder, on the side. One of the biggest problems was friction at the head; for reliable operation a felt pressure pad had to be used. One way to overcome the effect of this friction would be to perform the motion experiment on a sloping runway. However, with a little experimentation with the position of the tape head and the path of the tape, it may be possible to do away with the pressure pad altogether.

A table of the square wave tones recorded on the tape is given.

Once the tapes have been made up they can be used for many experiments. R19 should be adjusted to give the correct full scale deflection on the meter with one of the tapes. One way to do this would be to use the 25cm/s tape, and arrange for it to be pulled past the head by a tape recorder movement running at $7\frac{1}{2}$ i.p.s. (19cm/s). Once R19 has been adjusted for one tape, the other tapes will give their correct f.s.d., provided, of course, that the frequencies of the recorded tones were reasonably accurate.

K. J. Dorrell,
Southampton, Hants.

741 TESTER

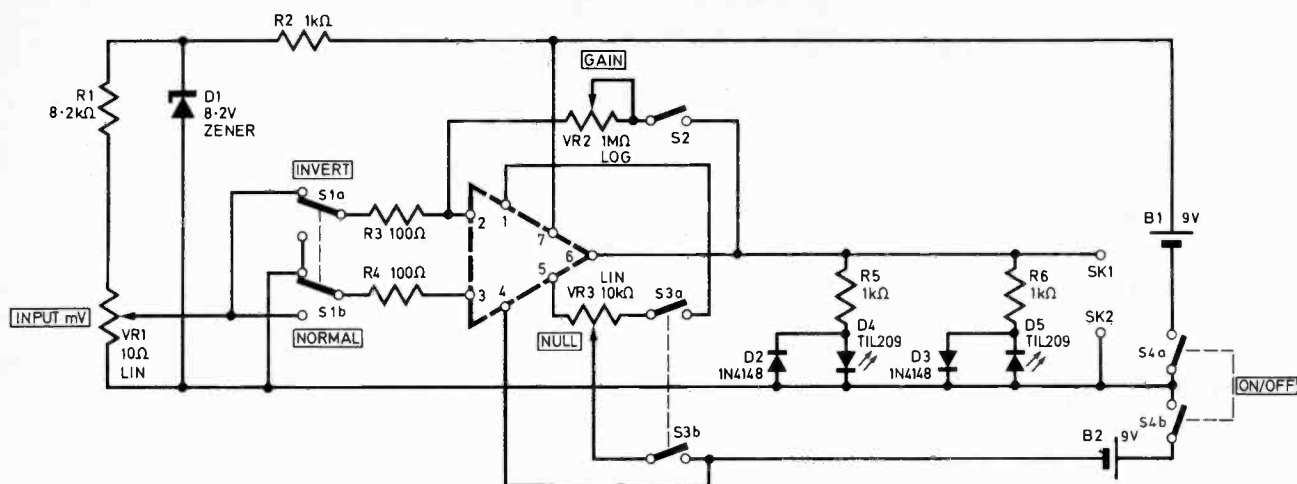

RECENTLY acquired a bulk purchase of i.c.s which contained many 741 series op-amps said to be untested. Looking through articles for the past couple of years failed to give any circuits for this purpose (although digital i.c. testers and transistor testers were fairly numerous). I therefore built the tester illustrated in Fig. 1, a simple circuit which has proved quick and easy to use as well as being relatively cheap.

The input is tapped off a low impedance source, VR1 which can supply 0-10mV, and this was read off by using a knob with a skirt labelled 0-10 directly. This is supplied via switch S1 to either the inverting or normal input of the 8 pin d.i.l. socket and the gain set using VR2. With the values used for VR2, R3 and R4, the gain is continuously variable from around unity to 10,000,

and the use of a log potentiometer enable gains up to 1,000 to be read off with fairly good resolution. The gain scale was in fact calibrated by using an ohmmeter, marking off the 10kΩ, 50kΩ, 100kΩ, 500kΩ and 1MΩ points and then labelling these points directly with the gain figures 100 to 10,000.

The output from pin 6 of the socket is taken across two l.e.d.s which on the panel are labelled normal for D4 and invert for D5, and this gives instant indication of the correct mode of operation of the i.c. under test. The diodes D2 and D3 limit the reverse voltage across the l.e.d.s to 0.6V.

The brightness of the l.e.d.s also should vary as both VR1 and VR2 are changed, and sockets are provided so that the output can be measured directly with a multimeter if more

accurate data is required.

Finally S3 is used to switch in the offset null potentiometer VR3 which should cause the l.e.d.s to change over as it is slowly rotated.

When a "good" 741 i.c. was used to test the device, it was found that the open loop gain, i.e. with S2 open, gave a voltage saving of ±7.5V whereas the rails were ±9V, but this is probably due to the combined effect of R5 and R6 which give a load of about 500Ω compared to the output impedance of the i.c. of around 150Ω. However, this should not prove a problem during testing.

Using the 741 tester, it was possible to very quickly check all the main parameters on over forty 741 op-amps. It was unfortunate for me that only two proved fully functional!

T. Smales,
Wrexham,
Clwyd.

VERSATILE V.C.O.

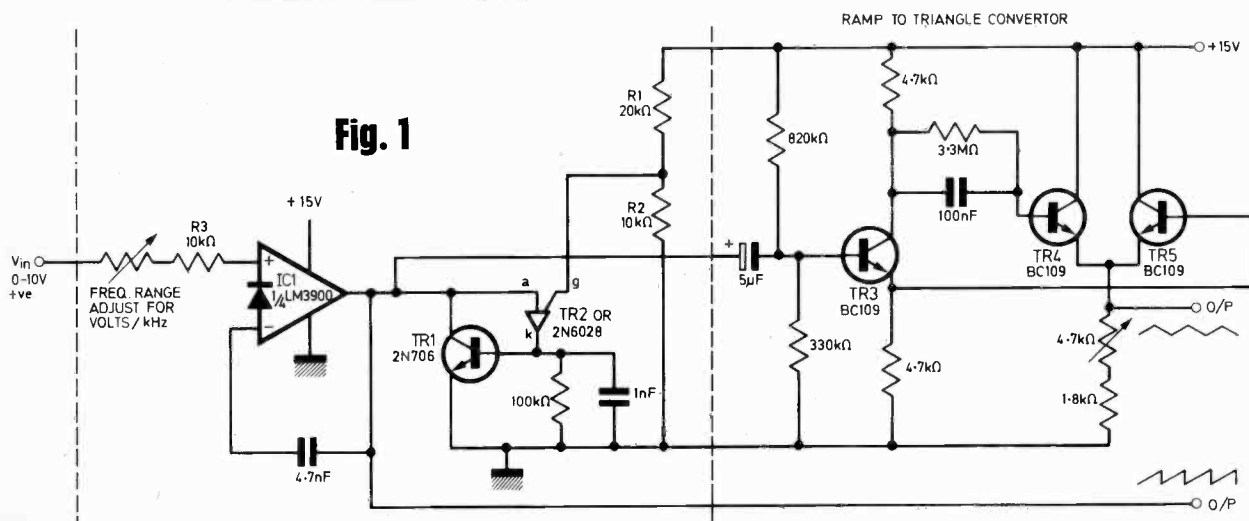


Fig. 1

"DOUBLE TREMOLO UNIT"

At present there are available a large number of both ready built tremolo units and plans for building them. Whilst providing a useful effect for guitars, they nearly all just regularly vary the amplitude of the signal and, if used a lot, they can become monotonous. This unit produces an effect totally different from normal tremolo or any other effect available at present.

Most electric guitars have two pick-ups, the idea behind this being that due to their different positions they give different tones, the guitar having a selector switch allowing both or either one of the pick-ups to be used. The novelty in this unit is that it regularly switches from one pick-up to the other, thus giving a regular change in the tone quality produced, however the effect is totally different from Wah-Wah and is very distinctive.

The circuit below is fairly simple, consisting of a multi-vibrator which alternatively switches on TR3 and TR4. Whichever transistor is "on" shorts out the pick-up which is in effect wired across it.

The value of VR1a/b depends upon the internal resistance of the guitar's pick-ups, and can easily be found by finding the lowest value of resistor which, when put in place of the variable resistors will just produce a noticeable effect with the unit on. This value should be under 1 kilohm.


As the outputs of the pick-ups are mixed together then fed to the guitar output socket it will be necessary to remove the mixing (usually the final) stage from the internal circuitry of the guitar and fit a stereo jack socket in place of the mono output socket, with one pick-up wired to each channel of the socket, the output of the guitar then being fed to the unit by

a stereo lead, with the output of the unit going to the amplifier.

Alternatively (and preferably) the unit can be built into the guitar, with its controls mounted alongside the guitar controls on the scratchboard, with the output of the unit connected to the guitar's output socket. This method is preferable as it allows the unit's controls to be altered more quickly and a normal lead to be used to connect the guitar to the amplifier.

With a few minor alterations to the unit's input/output connections it could be used to tremolo in and out another effect such as Fuzz or even between two instruments alternatively, but by far the most effective use of the unit is in its original form.

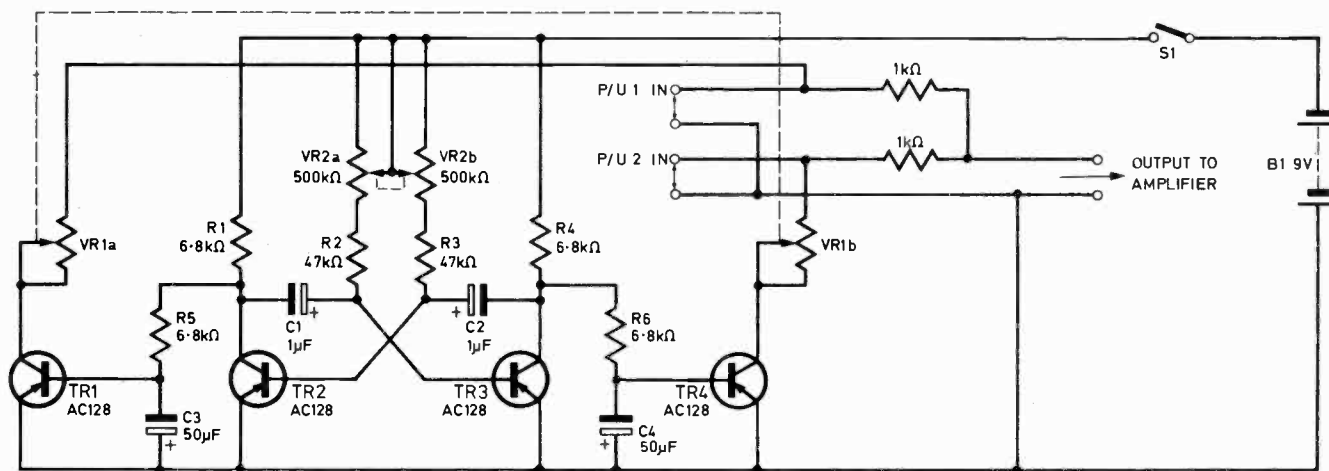S. J. Baxendale,
South Shields,
Tyne & Wear



The circuit to be described is the outcome of many months' experimenting in search for an accurate, versatile and cheap voltage controlled oscillator.

In Fig. 1, positive value of V_{in} produces a positive going ramp of about 5V peak. The ratio of R1/R2 controls the output voltage. The slightly unconventional configuration of the p.u.t. (TR2) is necessary as when using the standard u.j.t. replacement circuit the p.u.t. is liable to latch on and if a current limited power supply is not used, excessive current drain can result in the destruction of IC1 and the p.u.t. The circuit as shown produces a fool-proof stable circuit with a very fast reset time. A u.j.t. shows slower reset and this spoils the triangle wave symmetry at high frequencies. The ramp shows a small (10µs) reset pulse caused by the internal circuit of the

LM3900. No way has been found to overcome it, however, it is of no consequence if the oscillator is used for audio work.

The maximum usable frequency is about 25kHz.

The ramp to triangle wave converter consists of a phase splitter and a form of linear OR gate. The former produces two equal but opposite output which are fed into the differential pair. The b/e junctions of these "select" the highest possible voltage at any instant and combine the two ramps to produce a perfect triangle waveform, the symmetry of which is adjustable from ramp to triangle using the 4.7 kilohm potentiometer.

TR4/5 also act as emitter followers and produce a low impedance output.

Four v.c.o.s can be made with one LM3900 and if attention is paid to decoupling there is only very small interaction between each.

The best way of adjusting the frequency range over wide limits is by altering the integrator capacitor. For the value given the range is 1Hz-25kHz.

The resistor R3 can also be altered over a very wide range as IC1 input current requirements are low.

Some interesting and unusual effects can be obtained by driving one fast v.c.o. with a slow one (integrator capacitor about 1µF).

If a 1nF capacitor in series with a 500 kilohm potentiometer is wired between two p.u.t. anode gates the two v.c.o.s can be made to lock onto each others harmonics. With the reduction of potentiometer resistance to zero the slower running v.c.o. will speed up to the fast one in harmonic "jumps" until finally both run at the same speed.

J. A. Oliver,
Wellington,
New Zealand

CAR LIGHTS-ON INDICATOR

WITH the new laws calling for car lights to be used during daylight hours, when the visibility is poor, the great problem is in remembering to turn them off at the end of a journey. When motoring in daylight, if rain, sleet or snow begins to fall, the head lights are switched on. The panel illumination is too dim to see and if, at the end of the journey, the lights are left on a flat battery may result.

With this unit, if the engine is switched on, no warning tone will be generated during the day or night. If the engine is switched off during daylight, this will start a warning tone. This will stop when the driver switches off the lights.

Should the driver stop at night and leave the lights on, again no warning will be generated as leaving lights on at night is still necessary in poorly lit areas.

The unit is dormant until the lights are switched on, then power is applied to an audio oscillator. TR2 and TR3 form part of this with C2 and R6 in the feedback loop. These values can be adjusted to set the pitch of the tone (Fig. 1).

TR1 and surrounding components make up a NAND gate, where TR1 will be switched off as long as a positive d.c. potential is applied to its base. If the potential is removed TR1 will become biased through R3 and turn on, biasing TR2 and switching the audio oscillator on.

A d.c. positive potential is applied through D1 (from light sensor) or D2 from the ignition switch so that when the engine is running, 12V is continually holding TR1 off. Once the engine is switched off, this potential is removed leaving D1 holding the oscillator off.

In darkness R7 resistance will be very high, making pin 3 of IC1 positive and providing a positive output to TR1 through D2.


In daylight when the lights are on and ignition off, R7 resistance will be very low, making pin 2 drop in voltage to almost zero, and causing the output to drop to zero volts. The ignition is off, therefore D2 is off, it is daylight therefore pin 6 is at zero volts and so D1 is off, hence TR1 will turn on through R3, activating the oscillator.

The tone will be cancelled by turning off the lights (or switching off the device).

The unit was mounted behind the dashboard, out of view, with R7 in a position where it can best sense the general illumination level.

G. Luck,
Gosport, Hants

Fig. 1

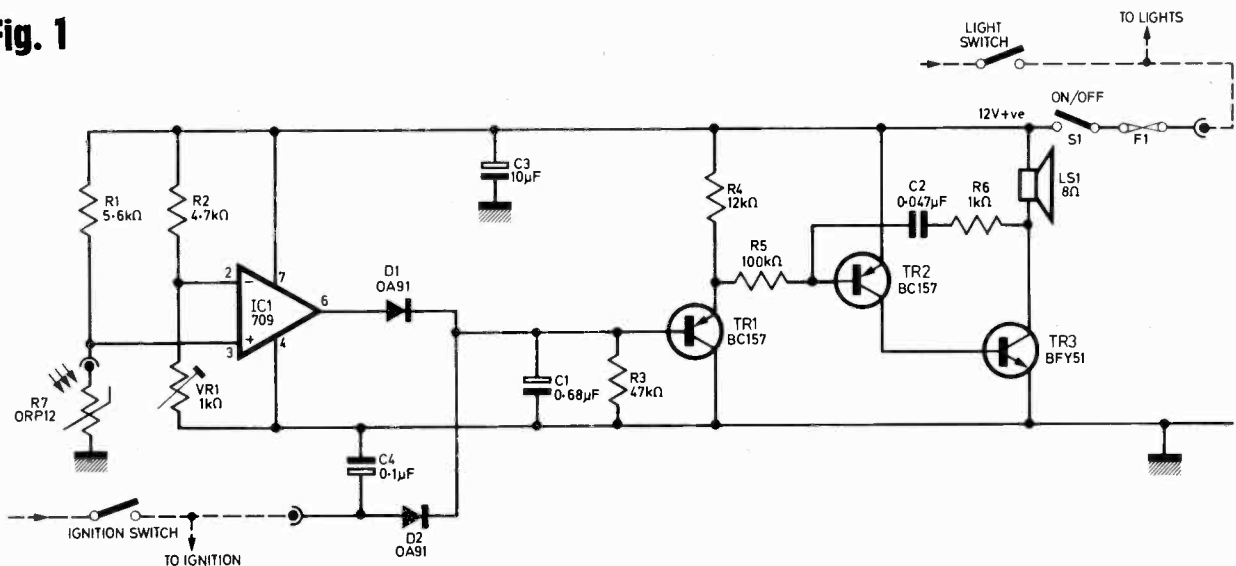

QUIZ MASTER

PREVIOUSLY published circuits for multi-station "Quiz Masters" have relied on circuits similar to that shown in Fig. 1. If S1 is closed when all the inhibit lines are at "1", gate G1 output will go to 0, thus inhibiting all other stations. (All stations except No. 1 will have one of their inputs connected to G1's inhibit line).

As soon as S1 is released, G1's output will go high and the other stations will no longer be inhibited.

This circuit can be adapted for different numbers of stations and can also use NOR gates (interchange resistor and switch—this arrangement uses less quiescent current), however, it does have the following disadvantages:

- (a) Limited by the number of inputs on each gate (8 usually, unless additional circuitry is used).
- (b) Limited by the fan-out of each gate (10 usually).
- (c) Stations grow more complex as total number of stations increase.


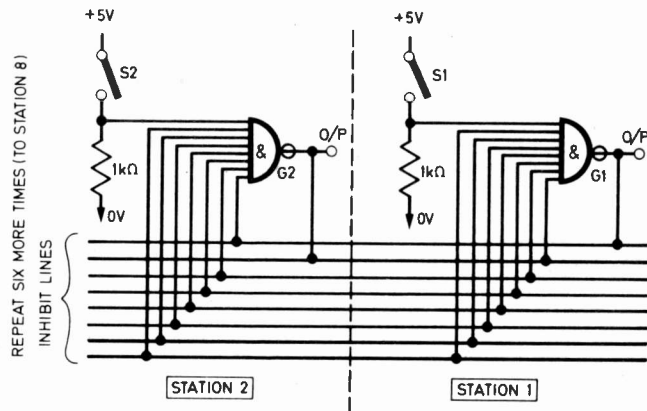


Fig. 1

Fig. 2

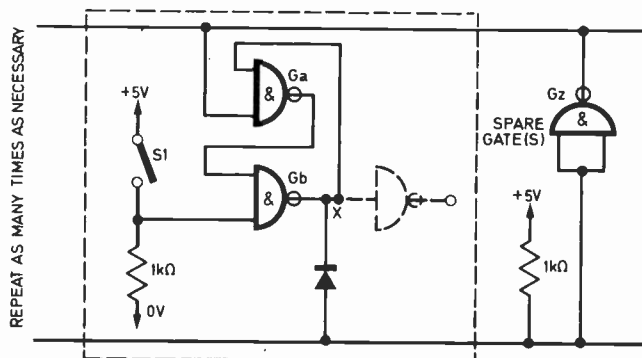

The circuit shown in Fig. 2 solves all these problems, using only two inhibit lines, one the inverse of the other.

If S1 is closed when Gz's output is low, Gb will go low, sending Gz's output high via the diode. All other stations will now be inhibited but because S1 was closed before the inhibit line was activated, Gb will remain low until S1 is released. At this point the inhibit line will be deactivated and other stations will no longer be inhibited.


The prototype used silicon diodes and worked satisfactorily; however, germanium types are preferable. Gz uses any spare gates wired as invertors.

If the number of stations exceeds 10 (the normal fan-out) several gates can be wired in parallel or a power gate used (e.g. 7437 with fan-out of 30). An inverted (normally positive) low current output can be taken from point X (remembering it also has to sink current for Ga and Gz). Alternatively, this output can be inverted by a further gate as shown to give a non-inverted output with a fan-out of 10.

This circuit has several other applications. For example, the control of a vending machine selling several different brands or types of goods with a select button for each.

T. Turner,
Stockport,
Cheshire

SIMPLE CAR TACHOMETER

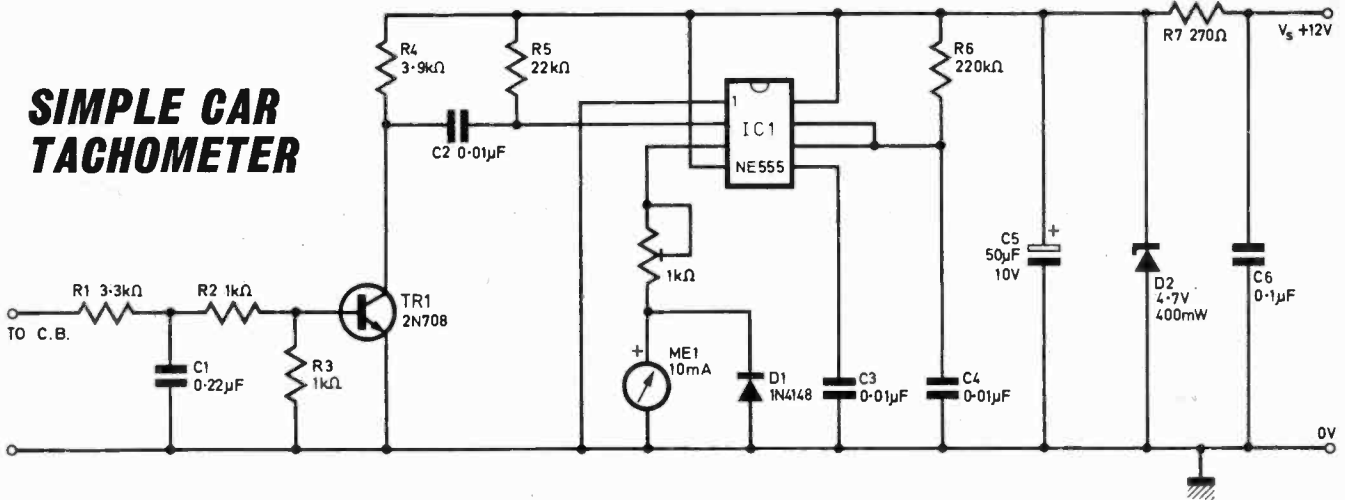

I WAS recently asked to repair a car tachometer which had "self destructed". Research into back issues of *Practical Electronics* produced a suitable circuit which used an SN74121 monostable integrated circuit. However, I did not have a SN74121, but I did have a NE555 timer i.c. This was duly pressed into service as a monostable and the circuit shown is the result.

The circuit is designed to operate from a 12V supply, but other voltages may be used provided that R7 is altered using the following formula:

$$R7 = \frac{V_s - 4.7}{0.025} \Omega$$

The meter may be any type up to 10mA f.s.d. However, the value of

the resistance in series with the meter may need to be altered to give the correct r.p.m. range.

Input pulses from the contact breaker drive TR1 into saturation which triggers the monostable via C2 producing pulses of fixed width at pin 3 of IC1 which are, in turn, used to drive the meter. The timing components R6 and C4 give a pulse width of approximately 2.5ms.

As the engine r.p.m. is increased, the monostable is triggered more frequently and therefore the average voltage seen by the meter is also increased.

The reverse biased diode D1 connected across the meter prevents spurious operation of the circuit due to the back e.m.f. generated by the meter with its pulsed operation.

The tachometer may be calibrated via VR1 using a signal generator. The corresponding meter readings for 4-stroke engines are given in Table 1; these should be halved for 2-stroke engines.

J. R. Shield,
Blaydon,
Tyne & Wear.

Table 1

No. of cylinders	R.p.m. corresponding to 50Hz input
2	3,000
4	1,500
6	1,000
8	750

HELIPOT SUBSTITUTE

WHEN there is a requirement for a variable resistor with a broad span and finely realisable accuracy one is generally recommended to a multi-turn helipot with suitable apologies for the high expense involved in such a purchase. Such occasions can arise when "setting-zero" on an operational amplifier.

The circuit shown in Fig. 1 achieves that of a "10-turn" potentiometer in sensitivity for the price of two common potentiometers.

Zero can be set by moving R2 to mid scale—zeroing as best possible with the "coarse" R1 and finally trimming with R2.

Although there are two knobs to twiddle, the 100kΩ potentiometer does give a ×10 resolution whilst the ganged potentiometer gives a full range coarse control.

O. Ormrod,
Auckland,
New Zealand


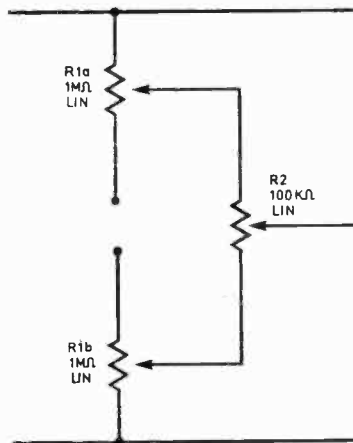


Fig. 1

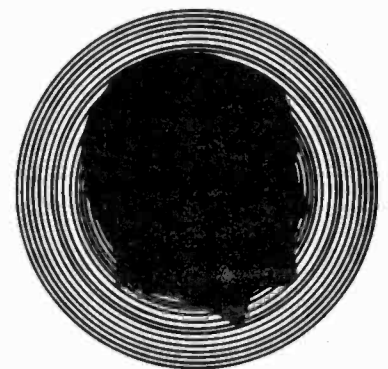

**INGENUITY
UNLIMITED**

The amazing, automatic Logic Monitor LM-1.


Just clip it over your IC.
It instantly and accurately shows both static and dynamic logic states, on a bright, 16-LED display. It finds its own power.

It cuts out guesswork, saves time, and eliminates the risk of short-circuits.

LM-1 is suitable for all dual-in-line logic ICs; DTL, TTL, HTL, CMOS; up to 16 pins.

LED on = logic state 1 (high), LED off = logic state 0 (low), and each LED is clearly numbered 1 to 16 in the conventional IC pattern.

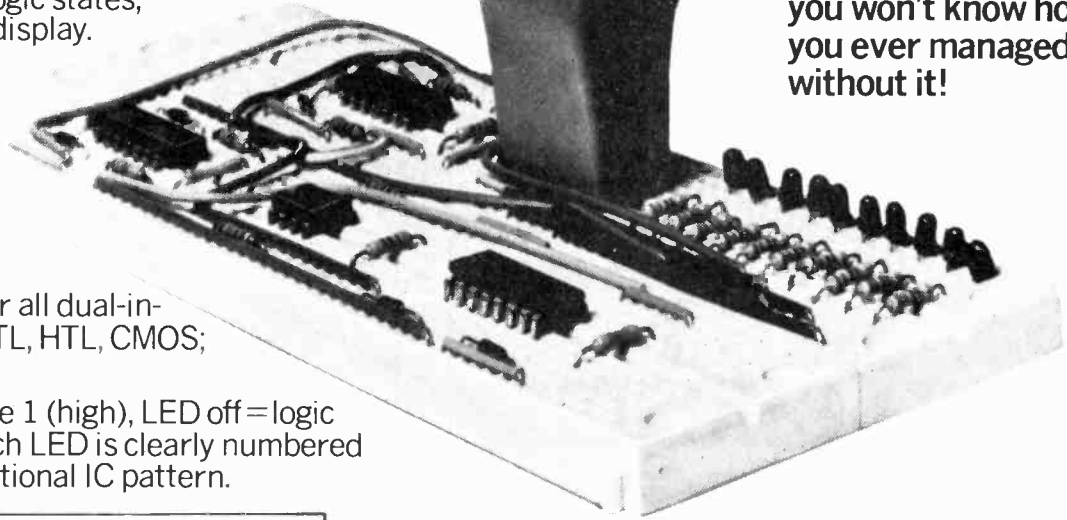Try the LM-1 and you won't know how you ever managed without it!



Brief specification

Input Threshold	2V ± 0.2 volts.
Input Impedance	100,000 Ohms
Input Voltage Range	4 volts minimum 15 volts maximum across any two or more input leads
Maximum Current Drain	200 mA @ 10 volts
Maximum Input Frequency*	10,000 Hz 50% duty cycle
Operating Temperature Range	0°C to 50°C
Weight	3 ounces (85 grams)
Maximum Dimensions	4.0 x 2.0 x 1.8" 102 x 51 x 45 mm

*LM-1 will respond to signals up to 0.1MHz when the input signal swing exceeds the threshold voltage by more than 0.5 volts.

Applications

Design, breadboarding, testing and checking new logic systems. Direct real-time monitoring of logic function in operating equipment. Long-term testing of individual ICs. Identification of unused elements, to find room for an extra gate, clock etc. Observing relationships between ICs on different boards of multiple board systems (you need more than one LM-1 to observe simultaneously, of course). Plus dozens of other uses. You'll find them.

It's Easy to Order


Ring us (01-890 0782) with your Access, Barclaycard or American Express number and your order will be in the post that night. Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days. Otherwise ask for our complete catalogue.

CONTINENTAL SPECIALTIES CORPORATION



ONLY £28.70

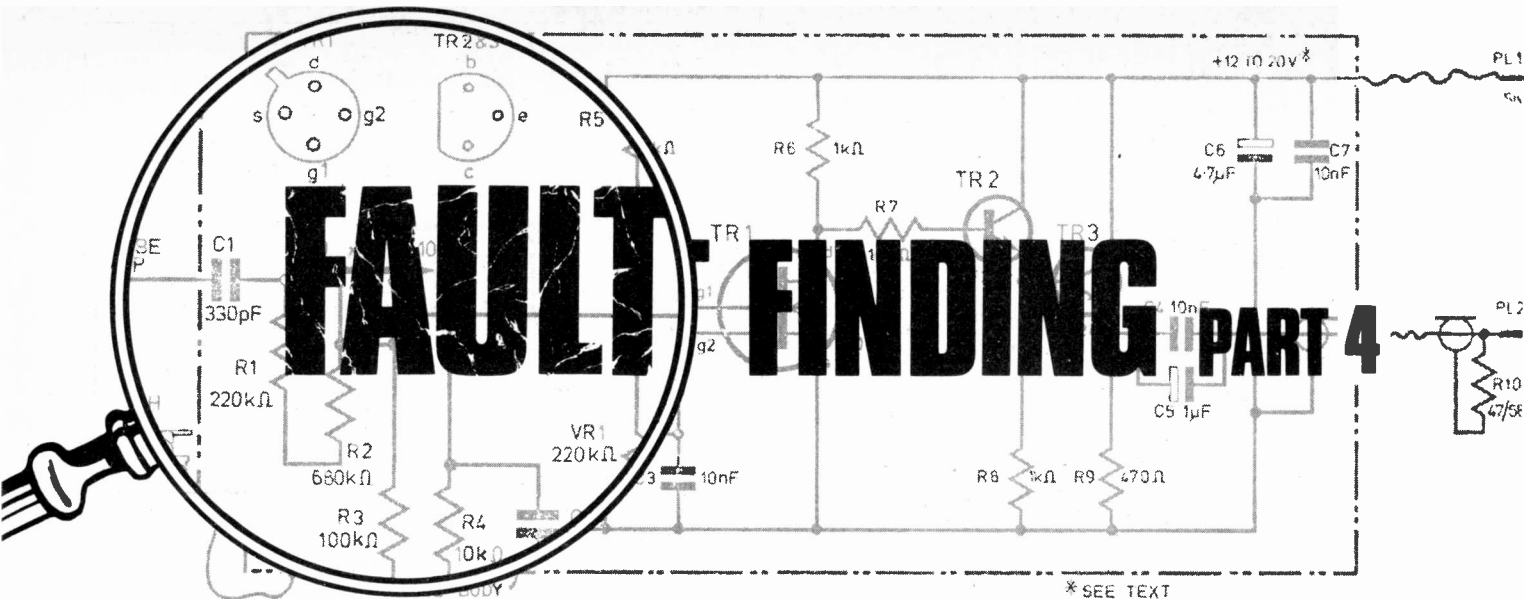Plus 8% VAT, plus post and packaging total £32.34, including box and instruction manual.



G. LOVEDAY

So far in this series we have introduced the basic concepts for fault finding in transistor and thyristor circuits, and methods used to locate faults in systems. Now we turn to perhaps the most important area of modern electronics, that of integrated circuits.

Most experimenters will have already used a few types of i.c. since most projects nowadays are built round either an analogue or digital type. The variety of i.c.s available for project work is very large and prices are really very modest.

I.C. BASICS

With this device the whole of a circuit function is contained inside one encapsulation. All the necessary diodes, transistors and resistors for a particular circuit function are diffused and interconnected in one piece of silicon. For example the popular 741 contains twenty transistors and eleven resistors and functions as a high gain differential amplifier. It's termed an analogue i.c. since it responds linearly to small changes of input signals.

A TTL i.c. on the other hand such as the SN7400N has four identical two input NAND gates so it contains sixteen transistors, four diodes and twenty resistors. Such an i.c. is termed digital since it switches between two logic states—its output being either high or low.

These two examples are of comparatively simple i.c.s. There are now several others available that contain many circuit functions inside the encapsulation making the whole i.c. almost a self contained system. The simpler circuits are grouped under the general heading of small scale integration, and as circuits become more complex they are termed Medium Scale Integration (MSI) typically between 15 and 100 equivalent gates per package, and finally Large Scale Integration (LSI) typically above the level of 100 equivalent gates per package.

DEVICE FAILURE

It follows from the preceding paragraph that a failure of one part of the i.c. renders the whole device useless, with a consequent complete loss of performance. It then has to be replaced.

I.c.s are designed to give very high reliability, in fact this is one of the benefits obtained by diffusing all the components into one piece of silicon, but failures will occur. Failures can result from any natural environmental stresses. Temperature cycling for example weakening an internal connecting lead and finally causing an open circuit. But more often the failures are caused by misuse such as exceeding the rated value of current, voltage and power.

High voltage 'spikes' on the supply leads will damage i.c.s in just the same way as other semiconductor devices. If relay coils are being switched ensure that they are properly suppressed.

It is also wise to keep in mind the maximum rated voltages for the type of i.c. you are using. TTL, for example, requires a regulated power supply of between 4.75V and 5.25V, and the absolute maximum voltage must not exceed 7.0 volts. Overvoltage would cause the i.c. to overheat and lead to possible damage.

Most i.c. power supplies are fitted with an overvoltage protection circuit—called a crowbar—which automatically switches the power off if the voltage rises above a preset value.

HANDLING AND TESTING

Apart from observing the maximum values of power supply voltages and input signal levels there are one or two other points worth noting when servicing units with i.c.s.

When making measurements don't use large test probes as these may short some of the i.c. pins together. If the i.c.s are mounted in sockets, never remove or plug them in while the power supply is switched on. Under these conditions large current surges can be taken by the i.c. which could destroy it like a fuse. It's also wise not to apply test signals while the power is off.

When fault finding, always check the power supply voltage at the actual pins of the i.c., not between board connections or on the printed circuit wiring. If, for example, you leave the -ve prod of the meter on chassis and put the +ve prod to the i.c. pin, a break in the ground line to the i.c. will not be indicated.

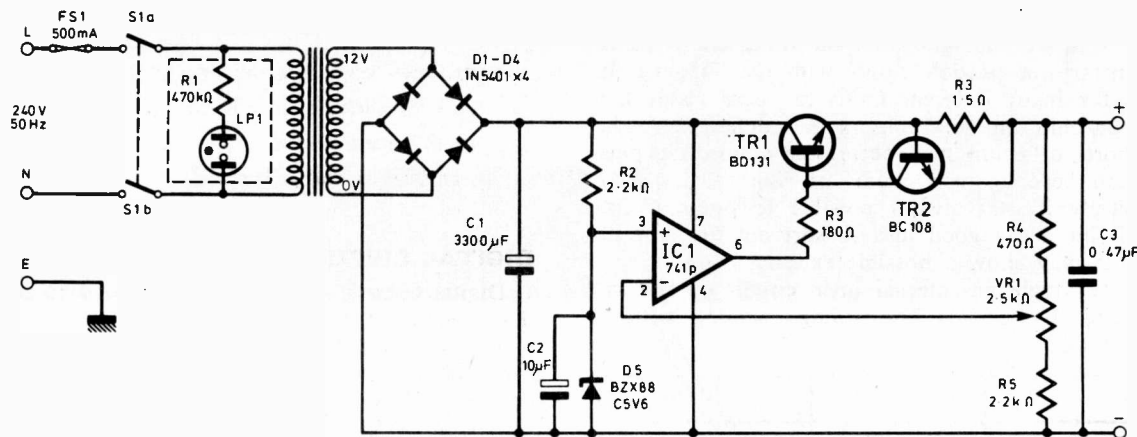


Fig. 4.1 Simple stabilised power unit

Having checked that power is present at the correct i.c. pins, next make sure that the required input signals are present, then finally test for the correct output. Since i.c.s are very reliable a lot of faults are caused by dry joints and breaks in copper tracks so always check visually and with a meter for any open or shorted connections.

If you are using an i.c. for the first time, before you switch on your project, double check the wiring and ensure that the i.c. is connected the right way round. A pin connection diagram of the i.c. is a must.

The best way to learn fault diagnosis is to practice on a few circuits so as an introduction we shall start with a project using a 741p op-amp.

STABILISED POWER UNIT

Since the 741p is a differential amplifier with very high gain it makes an ideal comparator and error amplifier for a linear series stabiliser. This gives a relatively simple circuit with quite a good performance. A circuit example is given in Fig. 4.1. The specification is as follows:

Output voltage range	7V to 12V
Max. output current	0.4A (current limited)
Ripple	2.5mV pk-pk.
Load regulation	Better than 0.02 per cent zero to full load
Line regulation	±10 per cent change in mains gives less than ±0.05 per cent change in output

The circuit is a conventional stabiliser, the non-inverting input (+) of the 741p amplifier being held at a constant voltage by the Zener diode (5.6V). The inverting input (-) is taken to a potentiometer. Since the 741 has such a high gain (100,000) it only requires a difference of a millivolt or so between the (+) and (-) input terminals for the output to be driven positive or negative by a large amount. If for example the input difference is 1mV negative the output would try to move several volts positive. The output therefore assumes a voltage which will cause the difference between the Zener voltage and the voltage on VR1 slider to be as small as possible.

Take the example when VR1 is set so that its slider is at the same point as the top of R5 (Fig.4.2). The voltage across R5 must be nearly 5.6 volts. This means that the voltage across R4 and VR1 is about 7 volts so that the total output voltage is just over 12 volts. By moving the slider of VR1 towards R4 the output voltage must reduce, giving an output of about 7V when the slider is at R4.

Neglecting the action of the current limit we can see how the circuit operates to hold the output constant by imagining a fall in output caused by an increased load. This would provide at IC1's inverting input a net negative input. The output will go positive causing TR1 (the series element) to conduct more, thus forcing the output back to very nearly its initial value. The opposite will occur if the output rises for any reason.

The changes in output voltage from zero to full load current are very small because of the very high gain of the 741. Thus one i.c. gives this relatively simple power supply very good performance.

The maximum output current is limited to about 0.4A. If the current increases beyond this the voltage across R3 causes TR2 to conduct and the output voltage falls. Thus, if TR1 is mounted on a small heat sink no damage occurs if the output is accidentally short circuited.

We have to understand how a circuit operates before we can do some fault diagnosis so having grasped the operation let's turn to some faults.

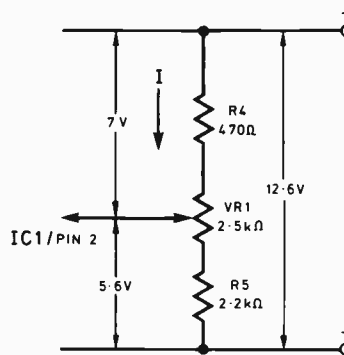


Fig. 4.2 Illustrating voltage control at IC1

SOME FAULTS

To start with we will ignore all the other components and concentrate on possible faults with the 741p i.c. It is possible for many different faults to occur inside the actual silicon chip and for faults in the connecting leads. Internal shorts or opens may occur, the connecting pins or track can become open circuit or short to adjacent pins. Naturally it isn't always possible to pinpoint the actual fault but it's a good idea to sort out the type of fault since it may show a possible external cause.

Take for example an internal open circuit on the inverting input of the 741. The voltage reading with a 100mA load are:

Pin No.	2	3	7	6	Output
Voltage	+9.3V	5.7V	16.2V	15.1V	12.5V

Symptom is no control and poor regulation.

Since the inverting lead is open circuit the output of the 741 has been driven hard positive forcing the output to rise. VR1 will have no control. Note that there is an excessive positive difference signal between 2 and 3 which should drive the output down, not up.

If the output going high is a symptom for an open circuit pin 2 then we must expect the reverse effect if pin 3 were open circuit. This is in fact the case as indicated:

Pin No.	2	3	7	6	Output
Voltage	1.7V	5.7V	16.2V	3.5V	No control

It's important to note that similar symptoms would be produced if the Zener or C2 became short circuit, or if R1 went open, except for the fact that pin 3 would then read zero volts. We have to sort out the difference between possible i.c. faults and those of external components.

(a) What would be the fault on the i.c. that gives the following?

Pin No.	2	3	7	6	Output
Voltage	0V	5.7V	16.2V	0V	0V

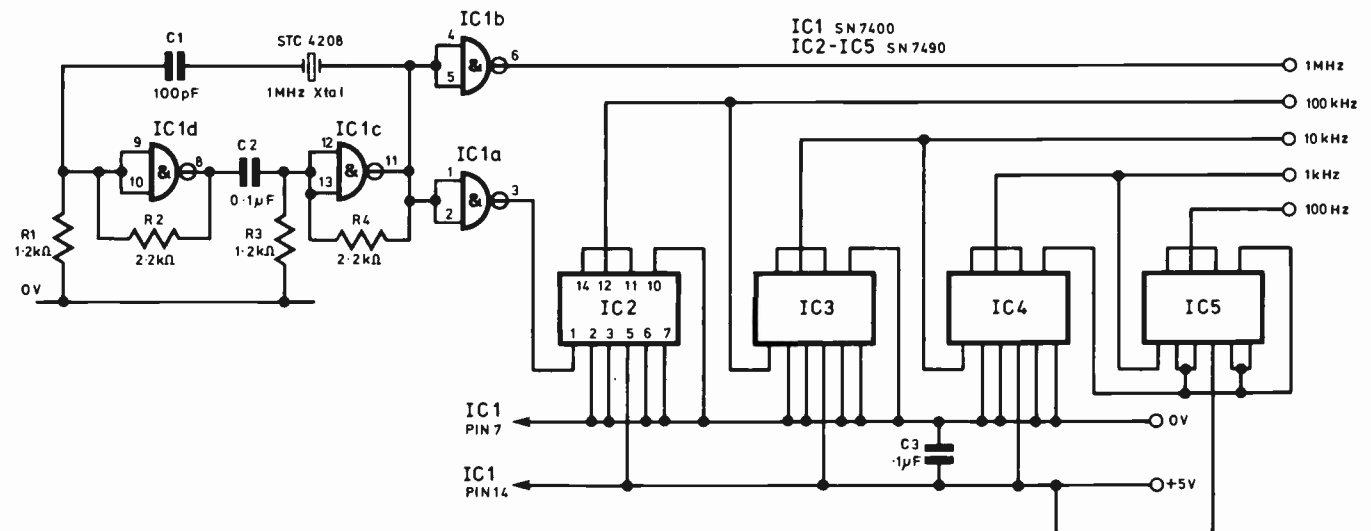


Fig. 4.3 Frequency standard unit

Can you work out the symptoms for the following faults?

- (b) Open circuit connecting lead to pin 7
- (c) VR1 slider open circuit
- (d) R5 open circuit.

(Answers at end of article.)

DIGITAL CIRCUITS

Digital circuits are those that respond to logic signals. The outputs being switched between two well defined states. With TTL logic '0' is typically 200mV (not greater than 400mV) and '1' is typically 3.3V (not less than 2.4V). Faults in digital circuits can then be stated as output "stuck at 1" or "stuck at 0". However, if an output is stuck, don't necessarily assume that the fault is with that particular i.c., since the required inputs signals also have to be present.

LOGIC GROUPS

In general, digital logic circuits can be grouped into combinational and sequential types. With combinational logic various input conditions have to be met simultaneously to give an output. Whereas in sequential logic the elements are in series, the output of one feeding the input of the next and so on. A frequency standard unit with divider chain is a good example of this (Fig. 4.3). A 1MHz crystal is used to provide the stable frequency and SN7490 decade dividers the various lower frequencies.

This can be a handy unit to have since the spot frequencies can be used to calibrate oscilloscopes, signal generators and frequency meters.

Now fault diagnosis on sequential circuits is relatively straightforward since a failure of one i.c. or its connections can easily be checked using the beginning to end method, or if the divider chain is long, the half split.

In the example imagine that there is a fault such that there is no 100Hz output although the 10kHz signal is present. The fault can only lie with IC4 or IC5 or their connections.

First check the input of IC5 on pin 1, this should be

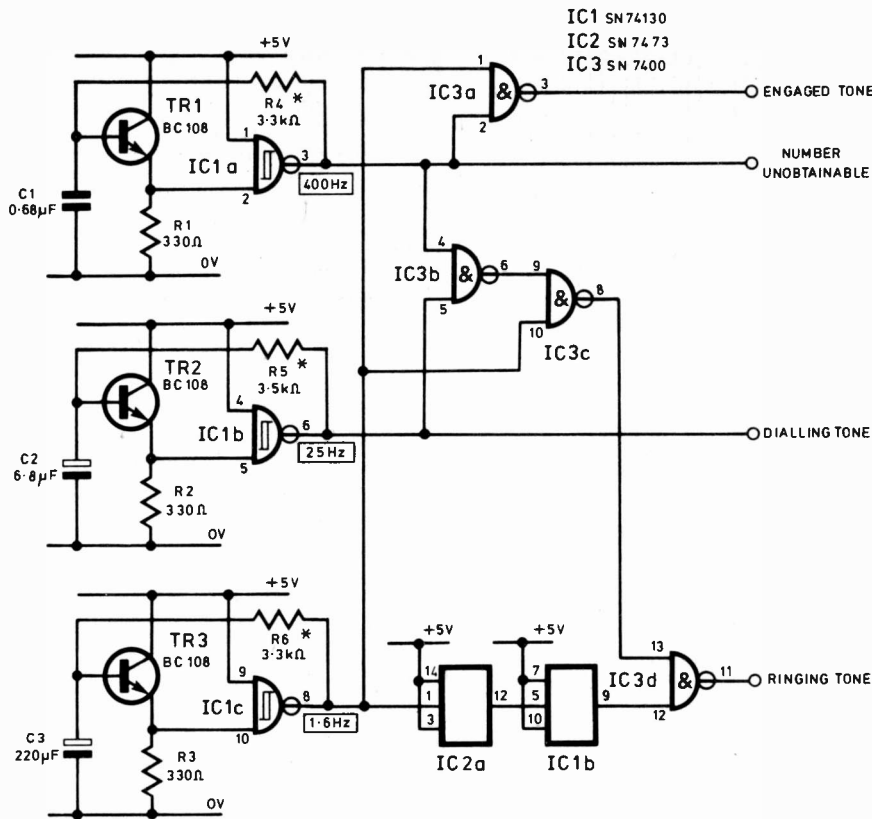


Fig. 4.4 Telephone tone generator

a 1kHz square wave. If this signal is present the fault must lie in this chip. Measure the power supply between pins 5 and 3, check all connections and then if necessary replace it.

What would be the symptoms for the following faults?

- (a) IC3 open circuit track from +5V line to pin 5
- (b) IC1b output stuck at 1
- (c) C2 open circuit

TELEPHONE TONE GENERATOR

This generator (Fig. 4.4) was developed as a simulator of the four tones and as part of a demonstration telephone system. It is also a useful unit for learning about logic and fault diagnosis.

Three TTL i.c.s are used. A 74132 Quad Schmitt to generate three frequencies of approximately 400Hz, 25Hz, and 1.6Hz. The other two i.c.s are a 7400, used for gating the signals and a 7473 dual JK bistable, wired to divide by 4, so generating a 0.4Hz square wave from the 1.6Hz output.

The simultaneous outputs are:

- Dialling tone 25Hz approx.
- Number unobtainable 400Hz
- Engaged 400Hz gated with 1.6Hz
- Ringling tone 400Hz modulated at 25Hz gated first with 1.6Hz then with 0.4Hz.

The outputs can readily be checked by a small speaker via an emitter follower as shown (Fig. 4.5) so no special test gear is required.

The circuit is really a mixture of combinational and sequential logic. The Nand gates of the SN7400 being the combinational portion. With Nand gates both inputs must be at logic 1 (high) for the output to be at logic '0'

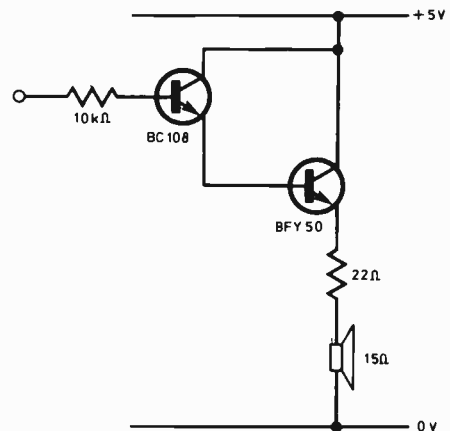


Fig. 4.5 Audio amplifier for tone generator

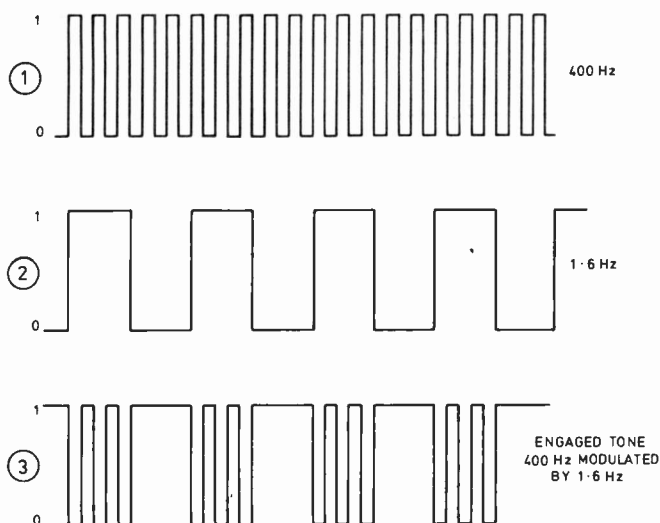


Fig. 4.6 Output waveforms at IC3

(low). Take IC3a for example, the waveforms at pins 1 and 2 will be as shown in Fig. 4.6. If the 1.6Hz oscillator failed with its output stuck at 0 the symptoms would be no outputs on the "Engaged" or "Ringing" tones (since IC3a and IC3c gates would be closed). On the other hand if this oscillator failed with its output stuck at 1, the output on the engaged tone would be 400Hz. A fault such as this last one would occur if C3 became short.

Consider fault symptoms of the ringing tone being almost the same as the engaged tone. Obviously all the oscillators are functioning correctly, and also the four gates of the 7400 are working. The fault can only be that the output (pin 9) of the 7473 bistable is stuck at 1. Verify this for yourself.

Now try and diagnose the component faults from the following symptoms. Assume outputs are correct unless stated otherwise.

(a) No ringing tone available—although an engaged tone is present on pin 13 of the 7400

(b) No dialling tone available

(c) No engaged tone available.

What would be the symptoms for the following faults?

(d) TR1 base emitter open

(e) IC3c output stuck at 1

(f) Open circuit connection 1.6Hz o/p to pin 1 IC3a.

CONCLUSION

This series is only intended as an introduction to fault diagnosis. We haven't explored the more troublesome faults such as intermittent shorts and opens, these can really be frustrating. It's hoped that the articles have given some encouragement to newcomers, and shown that successful fault diagnosis is mostly combining an understanding of circuit operation with logical investigations and measurements.

My thanks to Pitmans for permission to use some of the material from my book on Electronic Fault Diagnosis. ★

ANSWERS

Power supply

(a) Open circuit output or internal supply lead of 741.

Symptom	2	3	7	6	Output
(b)	0V	5.7V	0V	0V	0V
(c)	0V	5.7V	16.2V	14V	13.3V
(d)	5.7V	5.7V	16.2V	6.5V	5.8V

Frequency standard

(a) No 10kHz, 1kHz or 100Hz output. No +5V to pin 5 on IC3.

(b) No 1MHz output, although rest of output frequencies will be present.

(c) No outputs. Since oscillator will not function.

Tone generator

(a) Output from bistable (pin 9) stuck at 0.

(b) 25Hz oscillator circuit failed, output high.

(c) IC3a failure or open circuit connections.

(d) 400Hz oscillator fails output high.

Therefore engaged tone will be 1.6Hz

'Number unobtainable' will be dead.

Dialling tone will be o.k.

Ringing tone will be 1.6Hz gated with 0.4Hz.

(e) Ringing tone will be 0.4Hz.

(f) With an open circuit on a TTL Nand gate the gate will be open. Therefore the engaged tone will be 400Hz only.



BOOK REVIEWS

TELEVISION & RADIO 1978

Editor Eric Croston

Published by Independent Broadcasting Authority

224 pages, 230mm x 190mm. Price £1.85

IBA's prestigiously published year book is thoughtfully designed and well endowed with colour photographs. The bulk of the book is concerned with interesting details about programmes; News, Current Affairs, Documentary, Children's Television, Science, Drama, Arts, Sport, Educational TV, Religion and Light Entertainment.

Independent Local Radio has a large mention and station coverage is mapped out, as are the television areas. An engineering section on better viewing and listening heralds the possibilities of the 'all digital studio', 'digital VTR', the 'suitcase transposer', 'surround-sound', ORACLE, adaptive aerials, and the studio caption machine which has become a 'character generator' programmed by a 'video typographer'. This section also explains some studio jargon which inevitably creeps into the TV programme magazines.

For a producer's approach to developing a major drama series an article on 'Love for Lydia' gives the low down on how a special atmosphere can be created for a story set in the Midlands in the 1930's.



PE CHAMP

R.W. COLES B. CULLEN

PART EIGHT

CHAMP-PROG

THOSE readers who have successfully completed the construction of CHAMP can now look forward to many interesting and rewarding hours of programming and experimentation. Their systems can be used as learning aids to gain practical experience of the exciting new microprocessor technology, and as development aid to encourage the fulfillment of a multitude of software and hardware ambitions. When CHAMP is used in the latter mode, as a proving ground for hardware circuits and software programs which perform some useful function, there will come a time when programs tried out in CHAMP program RAM will need to be committed to a more permanent kind of storage for eventual use in some other small, dedicated, 4040 based system. This is when CHAMP-PROG and CHAMP-U.V. become very useful, if not essential, as additions to the CHAMP family. CHAMP-PROG is a PROM programming attachment which allows the user to copy a program stored in CHAMP program RAM into a 4702A device mounted in a "zero insertion force" (z.i.f.) front panel socket. CHAMP-U.V. is a simple erase light unit for 4702A and similar PROMS which allows a single device to be programmed and re-programmed many times over.

These facilities make for extremely low cost program amendment or enhancement when it is required, and represent a big improvement over the one-shot fusible-link PROM techniques sometimes used in m.p.u. system development.

This month we shall be looking at the operating principles and circuit of CHAMP-PROG, and how this unit is integrated with CHAMP itself.

CHAMP-PROG

As you can see from the title picture, CHAMP-PROG is built using the same system principles which were developed for CHAMP itself. The circuitry is carried on a fairly large sheet of Veroboard, which is mounted above a stylish low profile plinth made of wood and aluminium. The front panel carries a mains ON/OFF rocker switch in addition to the special 24 pin programming socket for the PROM being programmed. CHAMP-PROG has its own separate mains connector, and housed inside

the plinth is a special +80V programming supply. The standard +5V and -10V supplies also required are provided by the main CHAMP power source over the same 16 way connector that is used to transmit and receive programming data. In accordance with standard CHAMP techniques, the 16 way umbilical link terminates at low cost 16 pin d.i.l. sockets, the link itself being made from d.i.l. header plugs, and ribbon or multiway cable.

The programming operation requires the application of voltage pulses with an amplitude considerably in excess of the 15 Volts used during normal operation, and the level and timing of these pulses must be kept within tight limits. The CHAMP-PROG board carries all the voltage regulation, switching, and timing functions required for successful programming of 4702A type PROMS, together with the necessary data and address drivers which are driven in their turn by two 4265 programmable interface chips.

PROMPT

The programming operation is carried out under the control of a program called PROMPT (PROM Programming Technique) which is housed in a 4702A PROM plugged into the second socket on the CHAMP main board (Chip-One). PROMPT is an interactive program which uses the keyboard interrupt routine and display driver subroutine of the CHOMP program, which *must* also be present in the Chip-Zero socket (as usual) before programming can take place. PROMPT is entered via CHOMP on the depression of the TEST button on the CHAMP front panel. (You may recall that when TEST is detected, CHOMP carries out a JUN to 100H, which is the start of PROMPT when it is resident in the Chip-One socket). After the depression of TEST, the 7 segment display will show "Adr 1" which is a cue to the user that a three digit hexadecimal address is required which corresponds with the *start* of the source data block in CHAMP program memory. After entering a suitable address, which will appear as usual on the left of the display, the ENTER DATA button is pressed to confirm that entry is complete. The display will now change to show "Adr 2", and a similar procedure is followed to enter an address which indicates the *end* of the source data block in CHAMP program memory. A display of "Adr 3" is next, and on this cue an address is entered which represents the *start* of the destination area in the PROM to be programmed. Although the last address need only be a two digit hexadecimal quantity (because there are only 256 locations in a 4702A PROM), a three digit address is nevertheless expected by PROMPT since this makes the initialisation procedure as uniform as possible. The most significant digit, or chip-select hexadecimal digit, is in fact ignored, and so you can enter anything you like in this position; but usually a zero of course to prevent confusion!

After the entry of Adr 3, but *before* depression of the ENTER DATA key, the PROGRAM POWER switch adjacent to the programming socket is turned ON. Subsequent depression of the ENTER DATA key starts the programming sequence which takes about 2.5 minutes for 256 locations. Completion is signalled by a display of "done", but if any location was not erased properly, or failed to program at any point in the sequence, programming will stop prematurely and a display of "Fail" will result.

THREE ADDRESS SYSTEM

The fact that PROMPT uses a three address system makes CHAMP-PROG extremely versatile since blocks of data from CHAMP program memory can be moved to new locations in the PROM being programmed, and a PROM can be loaded with blocks of data from several sources if necessary. For example:

- (i) To duplicate Chip-Zero, (CHOMP), Adr 1 is entered as 000H, Adr 2 as OFFH, and Adr 3 as 000H.
- (ii) To put the first half of Chip-Two into the second half of the PROM being programmed, Adr 1 = 200H, Adr 2 = 27FH, Adr 3 = 080H.
- (iii) To put the single line of data at address 300H into address 020H of the PROM Adr 1 = 300H, Adr 2 = 300H, Adr 3 = 020H.

Of course, when relocating blocks of data in this way, account must be taken of the label destinations of any JUN, JMS, JCN, or ISZ instructions in the source block because these will probably be incorrect when loaded into the PROM. In the usual case the source block will be in program RAM, Chip-Two or Chip-Three, and so these label destination addresses can be temporarily changed (using CHOMP), to those applicable in the new PROM and its intended hardware system. (Obviously the 12 bit JUN and JMS addresses must also refer to the correct *chips* in the new system).

FAMOS PROMS

The 4702A is an MOS device using the FAMOS (Floating gate, Avalanche injection, Metal, Oxide, Semiconductor) technology to store data in the form of isolated charges on the gates of an array of MOSFET transistors. Each of the 2,048 memory cells (Fig. 8.1) consists of a single MOSFET with its gate electrode unconnected and isolated by means of a silicon dioxide insulating layer. When a cell is unprogrammed or erased there is no charge on the gate, and the source-to-drain resistance, R_{SD} , is very high. To program a logic one into a cell, a drain to source voltage of about 47 volts is applied for a short period of time and this causes an avalanche breakdown between the drain and the substrate material. Electrons are swept across the junction, and some are energetic enough to penetrate the silicon dioxide insulator to become trapped on the buried gate electrode. A negative charge builds up on the gate and this opens a low resistance channel between source and drain in normal enhancement mode MOSFET fashion. The charge accumulated on the buried gate is proportional to both the programming voltage and to the length of time that the voltage is applied, and so these must be carefully controlled by the programmer circuitry.

In addition, the avalanche action generates considerable heat, and so the programming must be carried out not with one long pulse but with a succession of narrow pulses with a "cooling-off" period between each one.

Fortunately the 4702A data sheet (Page 5-153, MCS40 manual) contains full details of the voltages and duty cycles which must be used to provide reliable programming without overheating.

BLOCK DIAGRAM

The CHAMP-PROG design is based on an original circuit supplied by Intel and used in their "Inteltec" development systems. The circuit has been simplified and in many cases components have been changed to make them easier to obtain in this country. The full circuit (Fig. 8.2) is still quite complex, and contains facilities such as current limiting and crowbar overvoltage protection to protect the PROM being programmed.

The best way to appreciate the way it works is to first study the block diagram Fig. 8.3. The voltage regulator block is required to generate the programming waveforms, and it actually contains two separate regulators, one a high current +47V circuit from which the VCCS, CS, Vgg, Vdd and Program pulses are derived, and the other a +60V low current circuit which supplies Vbb. The outputs from the regulator block are not continuous d.c. voltages, but pulses of accurately determined amplitude, and the switching which generates these pulses is carried out in the regulator block under the control of the timing circuit. This consists of a chain of t.t.l. monostables

Fig. 8.1. Memory cell used in the 1702A PROM. The cell is an f.e.t. whose gate has no lead. Source to drain resistance is a function of gate charge


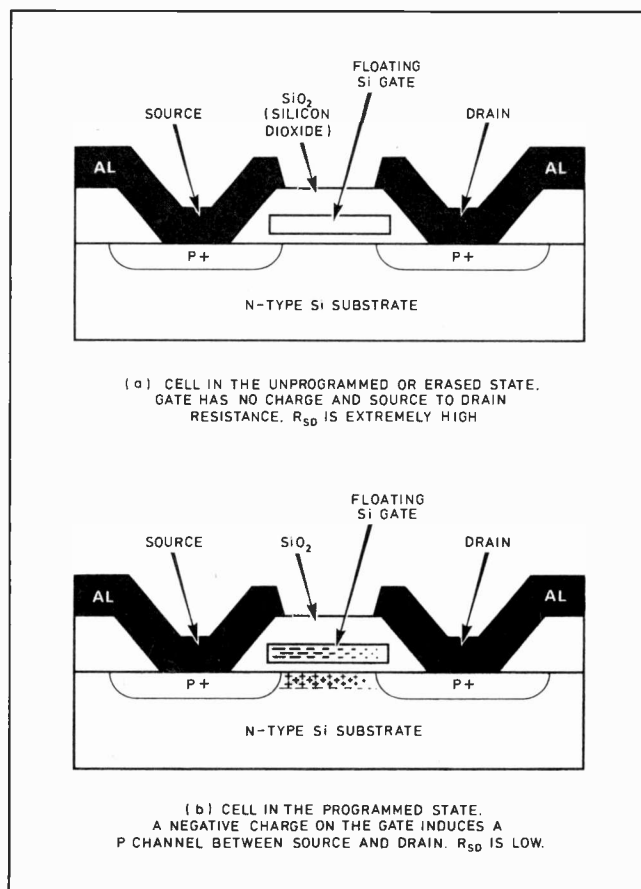


Fig. 8.2. CHAMP-PROG circuit diagram

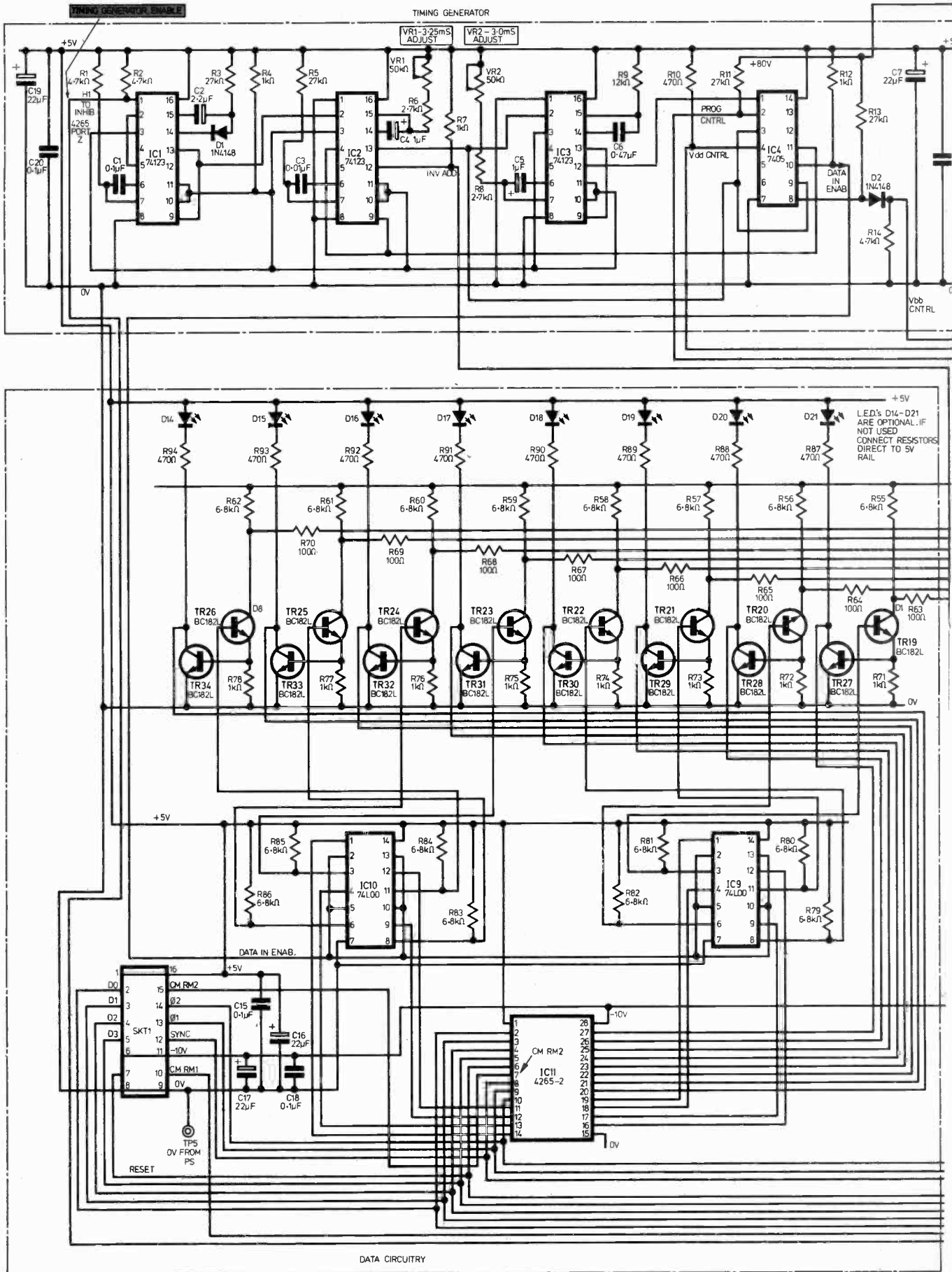

Get a great deal from
Marshall's


London - NW2 · 40-42 Cricklewood Broadway, NW2 3ET 01-452 0161

- **W2** · 325 Edgware Road, London, W2 01-723 4242

Glasgow · 85 West Regent Street, G2 2QD 041-332 4133

Bristol · 1 Straits Parade, Fishponds Road, B316 2LX 0272 654201

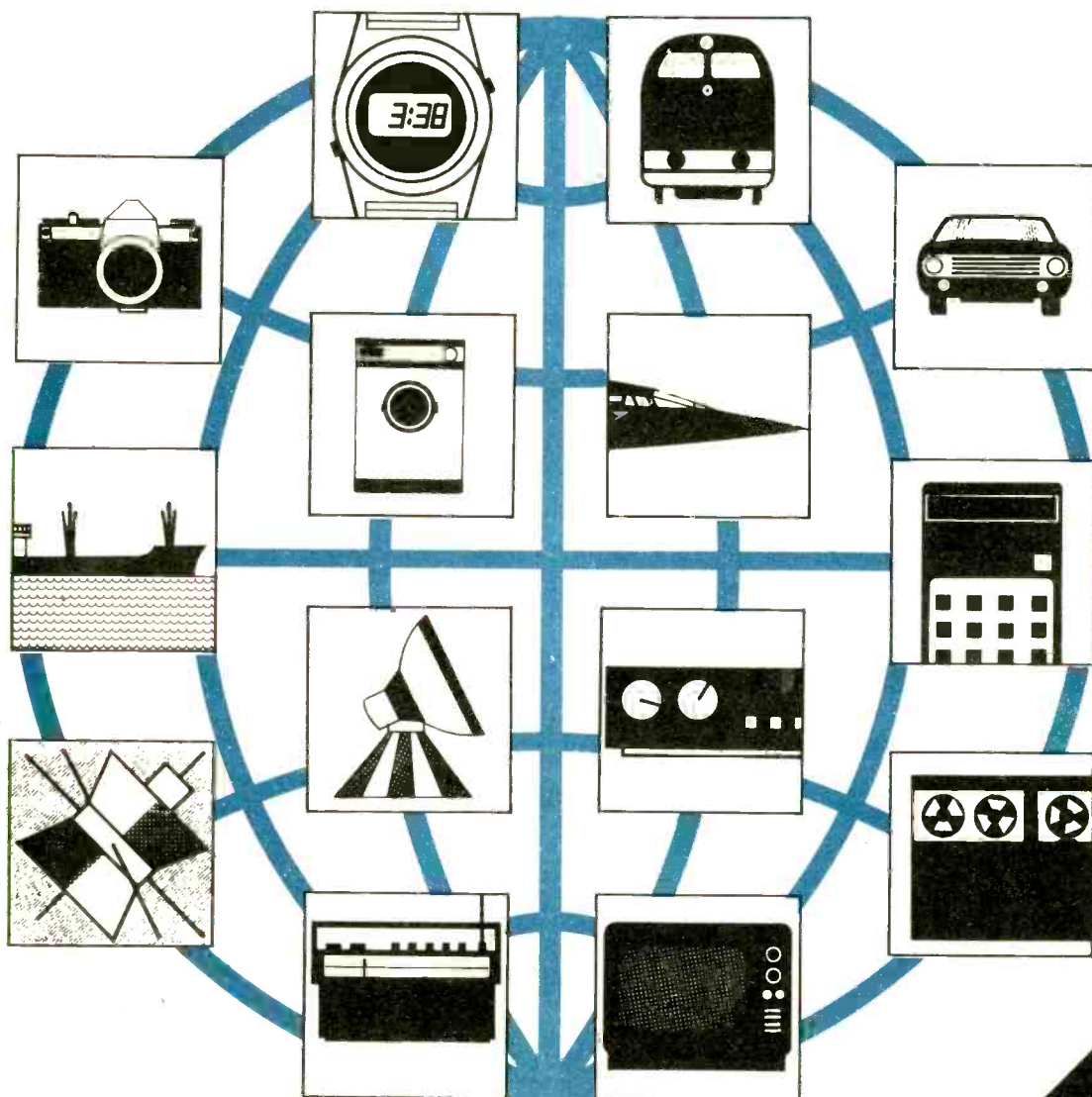Electronic components distributors TELEX 21492



**New
Catalogue**

JUDGE US BY THE COMPANIES WE KEEP

TO ALL OUR CUSTOMERS – ALL PRICES NOW INCLUDE VAT

IF YOU HAVE NEVER HAD A MARSHALL'S CATALOGUE BEFORE, YOU'VE PROBABLY ONLY SEEN OUR ADVERTS AND NEVER REALLY APPRECIATED THE VAST RANGE OF PRODUCTS WE CAN OFFER. WELL, HERE'S AN OPPORTUNITY TO CHANGE ALL THAT! IN THIS 40 PAGE CATALOGUE, WE HAVE SET OUT TO MAKE YOUR COMPONENT BUYING EASY. YOU WILL FIND OVER 8000 LINE ITEMS LISTED AND PRICED AND FOR THOSE OF YOU WHO BUY COMPONENTS IN QUANTITY WE CAN OFFER ATTRACTIVE DISCOUNTS; WE CARRY STOCK IN ALL OUR FOUR U.K. BRANCHES SO PLEASE DO NOT HESITATE TO CONTACT US.

WE ARE AN OFFICIALLY APPOINTED DISTRIBUTOR FOR THE COMPANIES LISTED ON THE RIGHT AND AS SUCH CAN SUPPLY QUALITY COMPONENTS AT REASONABLE PRICES – WHATEVER YOUR NEEDS MAY BE.

IF, ON THE OTHER HAND, YOU HAVE ALREADY GOT ONE OF OUR CATALOGUES, YOU'LL ALREADY KNOW THE RANGE OF COMPONENTS WE KEEP, AND THE SPECIALIST SERVICES WE PROVIDE IN ALL OUR LOCATIONS, BUT WE TRUST THAT THE NEW LINES WE HAVE INCLUDED MEET WITH YOUR APPROVAL... READ ON.

A. MARSHALL (LON.) LTD.

SPECIALIST
CONSUMER DISTRIBUTOR

- NATIONAL
- TEXAS
- MULLARD
- SIEMENS
- THOMSON CSF
- VERO
- ANTEX
- ARROW HART
- SIFAM
- BAHCO
- DOUGLAS
- REDPOINT
- ERMA
- ELECTROLUBE

TERMS AND CONDITIONS OF SALE

Our Retail and Trade Counters are open 9.00-5.30 Monday to Friday and 9.00-5.00 on Saturday. Cheques accepted only with Bankers Card. Barclay Card, Access and American Express welcome.

CASH WITH ORDER

No minimum order charge if cash or cheque is sent. Post & Packing charge is 40 pence. All postal orders, money orders and cheques must be crossed and made payable to A. Marshall (London) Ltd. Please use our mail order forms to speed the processing of your order.

CREDIT ACCOUNTS

Minimum order charge £10. Credit facilities will be provided subject to the submission of two satisfactory trade references and a Bank reference, Government Departments and Government Sponsored Organisations, H.M. Forces, Educational Establishments and Nationalised Industries automatically qualify for a credit account. Accounts are granted solely on the understanding that payment is made 30 days from date of invoice. All credit sales are subject to a minimum invoice value of £10. The post & packing charge is 50 pence.

DESPATCH

All items in stock are despatched the same day as receipt of order and are sent by first class parcel post. Exceptions to our same day turn round service are where matched transistors are required or when we are out of stock of a particular item. In the latter case the balance of your order will be sent as soon as possible.

NON-DELIVERY

All complaints should be made in writing giving exact details of the items ordered, the remittance sent if applicable and the date the order was posted to us.

CARRIAGE & PACKING CHARGES

Minimum 40p, balance will be charged at cost.

ENQUIRIES

Requests for quotations and details of the items offered for sale by this company should be sent separate from any orders, and we would appreciate the enclosure of a stamped addressed envelope to facilitate prompt attention.

ORDERS

These should be worded exactly as per description in our catalogue and confirmation orders must be clearly marked confirmation, otherwise we cannot be held responsible for duplication.

PRICES

All goods will be supplied as per prices quoted in our latest catalogue, subject to no special quotation having been made, but we do reserve the right to change prices without prior notification and would point out that all prices quoted are inclusive of VAT.

As we are distributors for a large number of British, Continental and American semiconductor and component manufacturers, we can offer attractive quantity prices for all devices in this and our other product lists.

Please note that one of the main factors affecting prices is the parity of the £ to other currencies, particularly the \$ (U.S.)

RETURNS/SHORT DELIVERIES/DAMAGED GOODS

No goods may be returned without our prior consent. There will be a 10% handling charge on goods returned other than for replacement due to fault or damage as described below, e.g. goods wrongly ordered.

1. Marshall's liability is limited to goods lost or damaged in transit and claims must be made within 7 days of delivery.
2. Goods which can be proved to be of faulty manufacture or below manufacturer's specification should be returned to us accompanied by a full statement specifying the fault and the application, and will be returned by us to the original supplier for checking. Claims of this kind must be made within 14 days of despatch and returned to us in the original condition and packing material. Please note no claims can be accepted for goods which have been soldered.
3. We must emphasise that we cannot replace components that have been soldered, and recommend the use of sockets, or if in doubt, prior testing.

EXPORT & DOCUMENTATION

For customers requiring details on export procedures with any necessary documentation, please apply to our Sales Department.

CONSEQUENTIAL DAMAGE

We cannot accept responsibility for damage to persons or equipment as a result of failure of product supplied by us.

DATA

All data in this catalogue is believed to be correct but Marshall's cannot accept responsibility if errors or omissions occur.

TELEPHONE ORDERS

Orders for prompt delivery can be accepted from account customers subject to our standard minimum order charge.

Credit Card telephone orders are subject to the same £10 min. — goods can only be sent to the cardholders home address.


MAIL ORDER FACILITIES

Our Company offers a return-of-post service on all stock items.


Marshall's mail order forms should be used whenever possible in order to reduce errors and save time. The prices shown in this catalogue are those valid at the date of publication and are subject to change without notice, but every effort will be made to ensure you a swift return service. In the event of a price change, or an item being out of stock, you will be notified immediately of the problem. Items ordered which are out of stock will be sent on at a later date as soon as we receive fresh stocks. We can only ask you to be patient as *in some cases deliveries are very extended.*

When writing out an order to us, we would appreciate a **complete** description of the items being ordered, including the various type numbers where available.

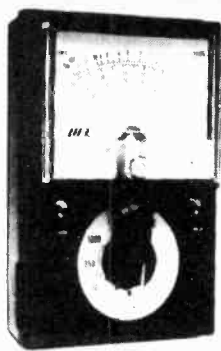
All goods are guaranteed brand new and to makers' specification. Faulty goods will be replaced under guarantee providing they are returned within 14 days from date of purchase, unused and with full information on the fault. Subject only to our technical agreement. Note: We cannot exchange soldered devices.



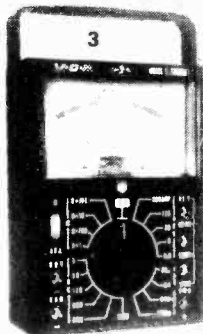1 MM1-LT101 1000 ohms/volt
 AC volts 0 to 10, 50, 250, 1000
 DC volts 0 to 10, 50, 250, 1000
 DC current 0 to 1mA, 0-100mA
 Resistance 0-3000 ohms
 0-150 Kohms
 Size 2 x 3½ x 1 inch
 Price £6.75



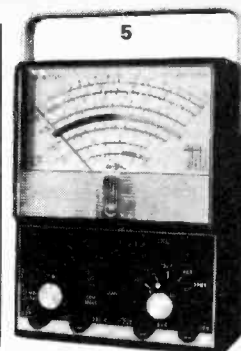3 MM7-C7200EM
 20,000 ohms/volt
 Ranges
 AC volts 0-6, 30, 120, 600, 1200
 DC volts 0-6, 30, 120, 600, 1200,
 3000, 6000
 DC current 0-60uA, 6mA, 60mA,
 600mA
 Resistance 0-6k, 600k, 6meg,
 30meg, 60meg
 Decibels -20dB to +63dB
 Size 6 x 4¼ x 2 inch
 Price £17.00



5 MMB-PROE 20,000 ohms/volt
 Ranges
 AC volts 0-2.5 to 0-5000 in six
 ranges
 DC volts 0-0.25 to 0-5000 in eight
 ranges
 DC current 0-50uA to 0-10A in six
 ranges
 Resistance 0-12 to 0-20megohms in
 six ranges
 Decibels -20 to +50dB
 Size 7½ x 6½ x 2½ inch
 Price £30.00

2 MM-2-LT22 20,000 ohms/volt
 Ranges
 AC volts 0-10, 50, 250, 1000
 DC volts 0-0.5, 2.5, 10, 50, 250,
 1000
 DC current 0-0.05, .25, 250mA
 Resistance 0-300, 3k, 30, 50k,
 500k, 5meg ohms
 -20 to +62dB
 Size 5 x 3½ x 1¼ inch
 Price £13.95



4 MM11-7081GN
 50,000 ohms/volt
 Ranges
 AC volts 0-1.5 to 0-500 in ten ranges
 DC volts 0-0.5 to 0-500 in twelve
 ranges
 DC current 0-25 uA to 0-10A in ten
 ranges
 Resistance 0-100 to 0-16megohms
 in four ranges
 Decibels -20 to + 62db in ten
 ranges
 Size 6½ x 4½ x 2¼ inch
 Price £24.95



DIGITAL MULTITESTERS-PORTABLE

COMPLETE WITH CHARGER

THREE DIGIT
 Accuracy 1% reading



Model: LM-3A £88.56

MAINS/BATTERY OPERATED — COMPLETE WITH RECHARGEABLE NiCad BATTERIES & CHARGER UNIT

Features

- ★ Measures DC volts, AC volts, ohms and current
- ★ Automatic polarity, decimal and overload indication
- ★ No zero adjustment and no full scale ohms adjust
- ★ Battery operated — NiCad batteries; also AC line operation
- ★ Large LED display for easy reading without interpolation
- ★ Size 1-9"H x 2-7"W x 4" deep
- ★ Parts and labour guaranteed for one year
- ★ Input voltage protection in ohms and current range

Ranges

Volts DC — 0-1, 10, 100, 1000 volts
 Volts AC — 0-1, 10, 100, 1000 volts
 Resistance — 0-1k, 10k, 100k, 1meg, 10megohms
 Current — 0-1mA, 10mA, 100mA, 1A

NEW

IDEAL FOR
 SERVICEMEN

THREE & A HALF DIGITS
 Accuracy 0.5% reading



Model: LM-3.5A £102.60

Complete with tilt stand for benchwork or optional case £8.75


MICROTESTERS

MICROTEST 80

The smallest precision tester available with 8 fields of measurement and 40 ranges features 20,000 ohms/volt, fully screened, dimensions 90 x 70 x 18mm. Electronic zero ohms complete with case and instructions.


Volts DC	6 ranges	100mV-1000V
Volts AC	5 ranges	1.5V-1000V
Amps DC	6 ranges	50uA-5A
Amps AC	5 ranges	250uA-2.5A
Ohms	4 ranges	1Ω-5megΩ
V output	5 ranges	1.5V-1000V
Decibels	5 ranges	+6dB +62dB
Capacitance	4 ranges	25uF to 25,000uF

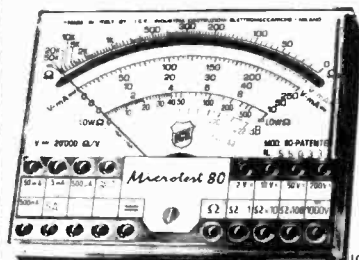Accuracy and stability (2% of FSD AC & DC)
 Size 90 x 70 x 18mm
 Price (inc case) £16.15



ICE MILANO

SUPERTEST 680R

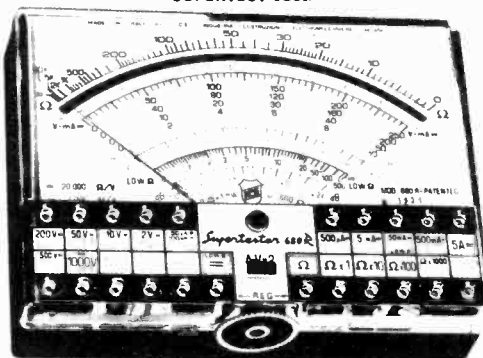

The revolutionary supertester to beat them all, 10 fields of measurement and 80 ranges, 20,000 ohms/volt mirror scale — complete with case and instructions.

Volts AC	11 ranges	2-2500V
Volts DC	13 ranges	100mV-2000V
Amp DC	12 ranges	50uA-10A
Amp AC	10 ranges	250uA-5A
Ohms	6 ranges	1Ω-10megΩ
Freq out	2 ranges	0.500 and 0-5kHz
Volt out	9 ranges	10-2500V
Decibels	10 ranges	-24 to +70dB
Capacity	6 ranges	0-20,000uF


Accuracy & stability 1% in DC 2% in AC
 Size 128 x 95 x 32mm
 Price (inc case) £27.27

SUPERTESTER 680G

New supertester 680G — shockproof, mirror scale, magnetically screened 20,000 ohms/volt, 10 fields of measurement and 48 ranges

Volts DC	7 ranges	100mV-1000V
Volts AC	6 ranges	2V-2500V
Amps DC	6 ranges	50uA-5A
Amps AC	5 ranges	250uA-2.5A
Ohms	6 ranges	1Ω-100megΩ
Capacity	4 ranges	0-200uF
Freq out	2 ranges	0.500 & 0.5000Hz
Volt out	6 ranges	2-2500V
Decibels	5 ranges	-10dB to +62dB

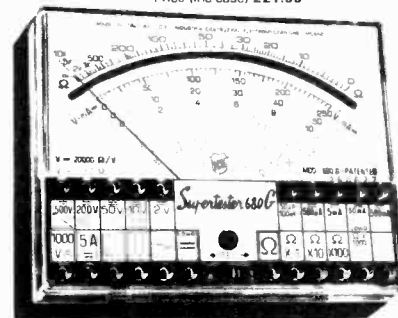Accuracy and stability 2% AC & DC
 Size 105 x 84 x 32mm
 Price (inc case) £21.55



0.84" High LED Digits



MA 1002 & MA1010 Series Electronic Clock Modules

The MA1002 & MA1010 Series Electronic Clock Modules are assembled and pretested modules which combine a monolithic MOS-LSI integrated clock circuit, 4-digit LED display, power supply and other associated discrete components on a single printed circuit board to form a complete electronic clock movement. The user need add only a transformer and switches to construct a digital clock for application in clock-radios, alarm or instrument panel clocks. Timekeeping may be from 50 or 60 Hz inputs and 12- or 24-hour display formats may be chosen. Direct LED drive eliminates RF interference. Time setting is made easy through use of Fast and Slow scanning controls.

For 50Hz operation connect pin 16 & 17 on MA1010

The MA1002F and MA1010E have a 12-hour display with an AM and PM indicator. The MA1002H and MA1010G have a 24-hour display.

Features include alarm on and PM indicators, sleep and snooze timers and variable brightness control capability. The modules are extremely compact: the MA1002 measuring 1.375" by 3.05" the MA1010 measuring 1.75" by 3.75". This small size is achieved by bonding the IC to the back of the circuit board.

It is highly recommended that the transformer be obtained with the clock module as it is a special dual secondary type not otherwise readily available.

NEW DIGITAL ALARM CLOCK MODULES

MA1002F 12-hr £10.45
MA1002H 24-hr £10.45
MA1010E 12-hr. £13.75
MA1010G 24-hr. £13.75

0.5" High LED Digits



Special transformer £1.65

PHOTO TRANSISTORS

2N5777	Darlington Amplifier
2N5778	Darlington Amplifier
2N5779	Darlington Amplifier
BPX25	General Purpose Silicon
BPX29	General Purpose Silicon
BPX80	General Purpose Silicon Array (10)
BPX81	General Purpose Silicon
BPX86	General Purpose Silicon (5)
TIL63	General Purpose Silicon
TIL64	General Purpose Silicon
TIL65	General Purpose Silicon
TIL66	General Purpose Silicon
TIL67	General Purpose Silicon
OCP71	Germanium Photo Transistor
TIL78	Photo Transistor



PRICE
£0.88
£0.99
£1.30
£1.80
£1.80
£7.20
£0.86
£5.75
£1.60
£1.87
£2.15
£2.20
£2.20
£2.30
£2.20
£0.75

PHOTO DIODES

BPW32	Low Dark Current Silicon
TIL32	I/R Diode
BPX48	Differential (Precision)
BPX60	High Output Voltage
BPX61	10 MH _z
BPX63	Ultra Sensitive Silicon
BPX65	High Speed Silicon
BPX97	General Purpose Silicon
BPX68	General Purpose Silicon



PRICE
£2.87
£1.10
£4.28
£4.75
£3.95
£2.20
£5.17
£1.78
£2.00


SOLAR CELLS

BP100	Miniature Solar Cell
BPX79	Miniature Solar Cell Blue Sensitive
BPY64	General Purpose Solar Cell

PRICE
£0.93
£4.17
£4.17

OPTO COUPLERS

4N25	Opto Couplers
CNY17	Opto Couplers
TIL116	Opto Coupler

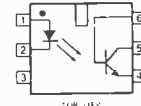

PRICE
£2.36
£2.36
£1.55

4N25 8 PIN DIL
2500V Isolation

LIGHT SWITCHES

TIL138	Transmissive Source & Sensor
TIL139	Reflective Source & Sensor




PRICE
£2.20
£2.20

MISCELLANEOUS

ORP12	Photo Conductive Cell Cad Sulph
ORP61	Photo Conductive Cell Cad Sulph
FW9802	Photo Conductive Cell Cad Sulph
RPY60	Photo Conductive Cell Cad Sulphoselen
RPY63	Photo Conductive Cell Cad Sulphoselen

PRICE
£0.90
£0.77
£0.82
£3.96
£3.96

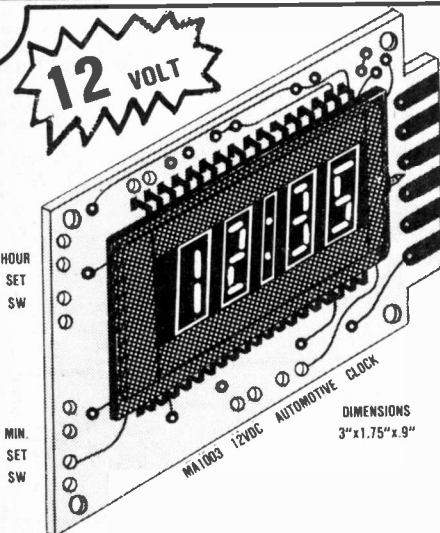

- 6 GROUND
- 5 NC
- 4 PARK LIGHTS
- 3 BATT. 12v
- 2 DASH LAMPS
- 1 IGNITION

HOUR SET SW

MIN. SET SW

DIMENSIONS
3"x1.75"x.9"

NEW DIGITAL CAR CLOCK MODULE



THE MA1003 ready-built module was specially built and designed for the American market, with the luxury car, aircraft and boat in mind. Unlike conventional quartz clocks, this unit operates from a very high frequency crystal resonating at over 2MHz for extra accuracy and stability. Stringent safety regulations dictate that this module is completely suitable for use in hostile environments and "shake, rattle and roll" conditions. Automatic display blanking is included when ignition is turned off, to consume a miserly 3mA.

THE BRIGHT GREEN DISPLAY, fluorescent, can be filtered from green to blue to give that personalised look. The compact and rugged design enables the module to be mounted anywhere, easily and with the minimum of effort. Works from any 12 volt supply. First time in Europe.

DEVELOPED BY NATIONAL SEMICONDUCTORS, A name known worldwide and respected. RECOMMENDED TO RETAIL AT £29.95+VAT

- INTERNAL CRYSTAL TIMEBASE ± 5 SEC/DAY
- COMPLETE, TESTED MODULE. JUST ADD SWITCHES
- BRIGHT 0.3" DISPLAY — GREEN FOR SAFETY.
- TRANSIENT PROTECTED, TIMEKEEPING DOWN TO 9V.
- EASILY INSTALLED, COMPACT AND RUGGED DESIGN

- DIMS TO 50% BRIGHTNESS WHEN CAR LIGHTS ON
- LOW POWER CONSUMPTION — FOR PORTABLE USE
- IDEAL FOR CARS, BOATS, AIRCRAFT OR CARAVAN

PRICE £14.95 INC. VAT

ALSO AVAILABLE

Specially designed case, with cut out centre front, black rexine finish for dash mounting.

Price £1.35

CRICKLEWOOD
01-452 0161

VAT INCLUSIVE
PRICES

EDGWARE ROAD
01-723 4242

OPTOELECTRONICS

LED LAMPS

LARGE STANDARD

Part No.	Color	LUMINOUS INT. MCD	PRICE
LD52	Red	1.2-2.4	£0.20
LD55	Yellow	3-6	£0.20
LD57	Green	2-4	£0.20

LARGE EXTRA BRIGHT

LD52C	Bright Red	15-30	£0.40
LD56C	Bright Yellow	10-20	£0.40
LD57C	Bright Green	20-40	£0.40

MEDIUM WIDE ANGLE

CQX23	Red	2-4	£0.28
CQX33	Yellow	1.6-3.2	£0.28
CQX13	Green	2.5-5	£0.28

SMALL

LD30A	Red	0.8	£0.18
LD35A	Yellow	1.5	£0.19
LD37A	Green	0.8	£0.19
TIL209	Red	0.8	£0.18
TIL211	Green	0.8	£0.19


MICRO

LD461A	Red	1.0	£0.25
LD466	Red Array (5 LEDs)		£1.85
LD469	Red Array (9 LEDs)		£3.00
LD471A	Green	0.8	£0.38
LD476	Green Array (5 LEDs)		£2.20
LD479	Green Array (9 LEDs)		£4.00
LD481A	Yellow	1.0	£0.33
LD486	Yellow Array (5 LEDs)		£2.45
LD489	Yellow Array (9 LEDs)		£4.00

INFRA RED

LD242	Micro IR LED Transmitter		£1.10
BPW34	I.R. Photo Diode Receiver		£2.10
LD271	Large I.R. LED Transmitter		£0.55
BP104	I.R. Photo Receiver for above		£1.45

THE BRIGHT ONES
"SIEMENS"

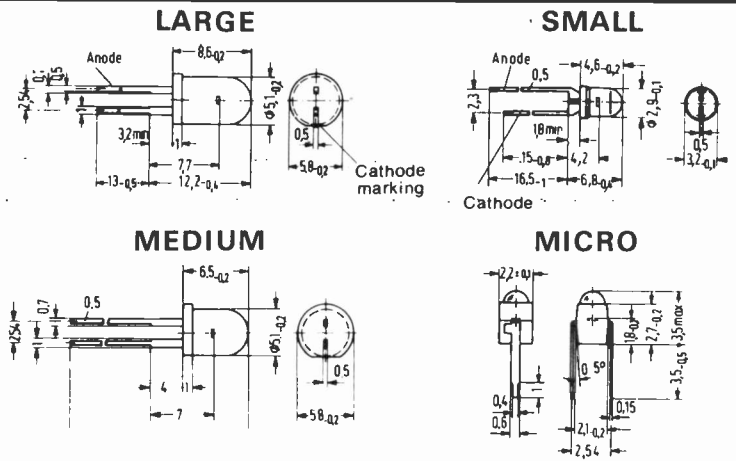


National

SEVEN SEGMENT DISPLAYS FOUR DIGIT MULTIPLEXED

Specially designed four digit multiplexed seven segment LED displays from National semiconductors. Many applications - smart in presentation and can be banked end to end to produce as many digits as required. Available in common anode or common cathode in .5" digit height.

NSB5881	COM CATHODE	Pin con are given for com cathode type. For com anode read anode for cathode and vice versa.	£5.95
NSB5882	COM ANODE		£5.95

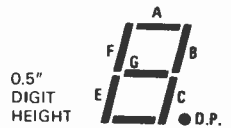

SEGMENT IDENTITY
(See Pinning)



PINNING

- 1 - ANODE A
- 2 - NC
- 3 - ANODE D
- 4 - COM CATH DIGIT 1
- 5 - NC
- 6 - NC
- 7 - COM CATH DIGIT 2
- 8 - ANODE C
- 9 - NC
- 10 - COM CATH DIGIT 3
- 11 - ANODE B
- 12 - ANODE F
- 13 - ANODE E
- 14 - COM CATH DIGIT 4
- 15 - ANODE D.P.
- 16 - ANODE G


FOR COMMON ANODE TYPE, ANODE & CATHODE ARE INTERCHANGED.

SEVEN SEGMENT LED DISPLAYS - SIEMENS

A unique, high quality range of displays to suit all applications. Extra bright red display. Sizes quoted are in mm.

Current per segment	20mA
Luminous intensity segment	.3 mcd
Forward voltage at 20mA	2.0 volts

PIN CONNECTIONS - TOP VIEW

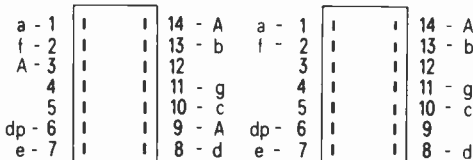


A = common anode

A = common anode

HA 1081

HA 1101

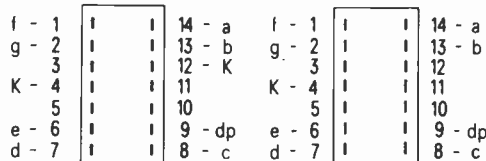

K = common cathode

K = common cathode

HA 1083

HA 1103

DESCRIPTION PRICE

8mm CHARACTERS		
HA1081	C An	£1.50
HA1083	C Cath	£1.50

10mm CHARACTERS		
HA1101	C An	£1.55
HA1103	C Cath	£1.55


14mm CHARACTERS		
HA1141	C An	£1.57
HA1143	C Cath	£1.57

18mm CHARACTERS		
HA1181	C An	£1.85
HA1183	C Cath	£1.85

NB.
DL707 replaced by HA1081
DL704 replaced by HA1083




Single Digit Displays

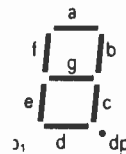


SIEMENS
QUALITY

HA 1181

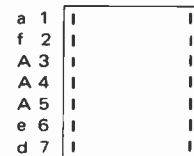


A = common anode

HA 1183

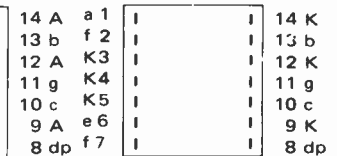


K = common cathode

HA 1141

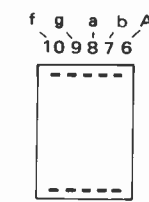

A = common anode

HA 1143

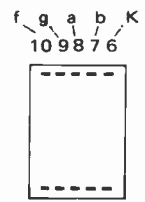

K = common cathode

Thomson-CSF... a European second source for the 6800 microprocessor

MPU SFF 96800

We haven't missed the 'bus'!

CLOCK

SFF 96870A
SFF 96871A
SFF 96971B

PROGRAMME MEMORY ROM

SFC 70324 512 x 8
U.V. REpROM
SFF 71702A 256 x 8

COMING SOON

16K RAM
8K U.V. REpROM
SFF 96802 SFF 96844
SFF 96821 SFF 96846
SFF 96840 SFF 96854
SFF 96843 SFF 96875

RAM

SFF 96810 128 x 8 static
SFF 80112 256 x 4 static
SFF 81104 4096 x 1
dynamic
SFF 81107B 4096 x 1
dynamic
SFF 80102 1024 x 1 static

IN STOCK NOW AT MARSHALL'S

6800 DII	EVALUATION KIT SEE PAGE 21 SUPPORT CHIPS	PRICE
6800 A	8 BIT 1.5MHz CLOCK MICRO	£16.99
6820 A	PIA CHIP	£ 9.20
6821 A	INCREASED O/P PIA CHIP	£10.50
6850 A	ACIA 1.5MHz CLOCK	£10.99
MEMORY		
6810 A	128 x 8 STATIC RAM	£ 4.95

Write or phone for full technical data



P.I.A.

SFF 96820

A.C.I.A.

SFF 96850

S.S.D.A.

SFF 96852

London · 40-42 Cricklewood Broadway, NW2 3ET

01-452 0161

Glasgow · 85 West Regent Street, G2 2QD

041-332 4133

Great value, superb quality.


That's the wonder of Texas. We have all you need for your next design project and at prices that are unbeatable all the way down the High Street.

Take our new 16K Dynamic Ram TMS4116. Hundred off price is just £22.84 each 16-pin, 300 mm ceramic DIL package, fully TTL compatible, address and data inputs latched for system simplicity, data output unlatched for flexibility. Low power dissipation and even lower standby consumption. Ideal for high-density memory applications where system costs are critical.

And we've a new line up of four 4K Static RAMs and a new EPROM, the TMS2716, which doubles the capacity of the TMS2708. Great range, great value!

For further information, contact:

TEXAS INSTRUMENTS

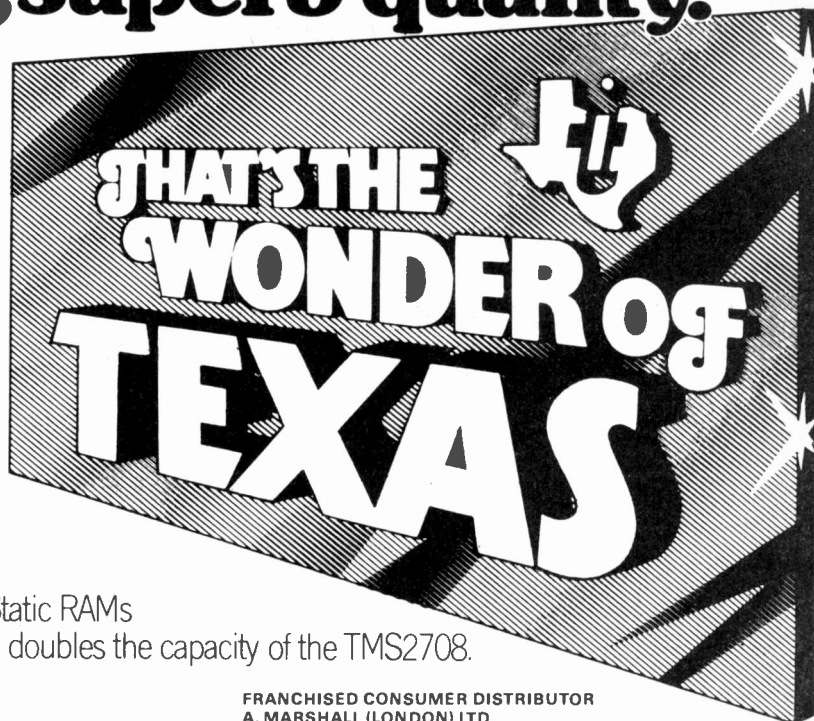

FRANCHISED CONSUMER DISTRIBUTOR
A. MARSHALL (LONDON) LTD.
40/42 CRICKLEWOOD BROADWAY
LONDON NW2 3ET
TEL: 01-452 0161

SILICON POWER TRANSISTOR SELECTION CHART

* NB. COMPLEMENTARY PAIRS SHOW NPN TRANSISTOR FIRST (AT TOP). IF NO PAIR IS SHOWN TRANSISTOR IS NPN.

V A	1A	2A	3A	4A	5A	6A	7A	10A	12A	15A	16A	20A	25A	30A	40A	50A
40V	BD135 BD136	BFR41 BFR81	BD131 BD132	2N6121 2N6124	2N4913 2N4901	BD233 BD234	BD201 BD202	BD181	40514	BD142				2N3771		
60V	BD137 BD138	BFR40 BFR80	TIP31A TIP32A	2N6122 2N6125	2N4914 2N4902	TIP41A TIP42A	BD203 BD204	TIP33A TIP34A		2N3055 MJ2955		2N3772	TIP35A TIP36A			
80V	BD139 BD140	40594 40595	2N4923 2N4920	2N6123 2N6126	2N4915 2N4903	BDY24		2N3715 2N3790		BD183			BDY57	40411		
100V	TIP29C TIP30C	BD237 BD238	TIP31C TIP32C			TIP41C TIP42C	40871 40872	TIP33C TIP34C					TIP35C TIP36C	MJ802 MJ4502		
120V			2N3441	40373	2N4347	BDY25		2N3442	BDY54	BDY56	2N3773		BDY58			BUX20
150V	40412				40374		25025									
200V			2N3738		2N5239											BUX21
250V	2N3440 2N5415	2N3584														BUX22
300V	2N3439 2N5416	2N3585	2N3902													BUX23
400V							BU104					BUX24				
500V										BUX25						
700V			BU205			BU126	BU208									
800V			BU206													
1kV				BDX32												
A. MARSHALL (LON) LTD 01-452 0161																

THIS TABLE IS ONLY INTENDED AS A GENERAL GUIDE; COST EFFECTIVENESS, PACKAGE DETAILS, FREQUENCY RESPONSE AND OTHER FACTORS ARE NOT TAKEN INTO ACCOUNT - CONSULT MANUFACTURERS DATA SHEET FOR DETAILED APPLICATIONS.

Type	Data	Price	Type	Data	Price	Type	Data	Price	Type	Data	Price	Type	Data	Price	Type	Data	Price	Type	Data	Price			
2C111	N73	5.20	2N2219	N70	.38	2N3446	N66	10.00	2N3962	P70	.95	2N4926	N70	1.70	*2N5486	NF86	.40	40313	N28	1.38	AF172	P98	.70
2G301	P70	.70	2N2219A	N70	.39	2N3447	N66	10.50	2N3993	PF80	3.65	2N4927	N70	1.70	2N5490	N37	.64	40315	N70	.60	AF178	P64	1.30
2G303	P70	.80	2N2220	N70	.39	2N3448	N66	12.00	2N4030	P70	.53	2N4928	P70	2.20	2N5492	N37	.64	40316	N28	.95	AF186	P65	.55
2G309	P70	.70	2N2221	N70	.25	2N3468	P70	1.32	2N4031	P70	.55	2N4944	N54	.30	2N5494	N37	.65	40317	N70	.60	AF200	P20	1.30
2G339A	P70	.70	2N2221A	N70	.25	2N3507	N70	10.00	2N4032	P70	.65	2N4945	N54	.30	2N5496	N37	.67	40324	N66	.95	AF201	P20	1.30
2G344A	P54	.70	2N2222	N70	.25	2N3512	N70	10.10	2N4033	P70	.65	2N4964	P70	.28	2N5543	NF76	7.50	40325	N66	1.35	AF239	P65	.70
2G345A	P54	.70	2N2222A	N70	.25	2N3553	N70	3.25	2N4036	P70	.72	2N4965	P70	.28	2N5550	N57	.38	40326	N70	.60	AF240	P65	1.25
2G371	P54	.70	2N2223	N73	3.99	*2N3563	N54	.25	2N4037	P70	.60	2N4966	N54	.28	2N5551	N57	.44	40327	N70	.73	AF279	P99	.88
2G374	P54	.70	2N2223A	N73	4.99	*2N3564	N54	.25	*2N4058	P50	.22	2N4967	N54	.28	2N5555	NF86	.65	40348	N70	1.10	AF280	P99	.95
2G374B	P54	.70	2N2224	N70	.49	*2N3565	N54	.25	*2N4059	P50	.17	2N4968	N54	.28	2N5538	NF86	.45	40349	N70	1.45	AFY42	P65	1.65
2G381A	P54	.85	2N2227	N70	.49	*2N3566	N70	.25	*2N4060	P50	.22	2N4969	N54	.28	2N5640	NF86	.45	40360	N70	.55	AS278	N70	1.30
2G417	P70	.95	2N2303	P70	.50	*2N3567	N70	.25	*2N4061	P50	.18	2N5010	N70	5.75	2N5654	NF86	.55	40361	N70	.55	AS280	N70	1.10
2N335	N70	3.00	2N2368	N70	.27	2N3570	N65	4.50	*2N4062	P50	.20	2N5011	N70	8.25	2N5655	N37	.55	40362	P70	.55	AS282	N54	.82
2N388	N70	.80	2N2369	N70	.27	2N3571	N65	1.90	2N4064	N81	1.35	2N5030	N50	.22	2N5656	N37	.65	40363	N66	1.45	AS284	P54	.82
2N388A	N70	.77	2N2369A	N70	.27	2N3572	N65	1.75	2N4074	N70	2.65	*2N5033	PF83	.65	2N5657	N37	.75	40364	N27	1.45	AS285	P54	.82
2N456	P66	2.20	2N2405	N70	.66	2N3583	N66	1.25	2N4091	NF79	1.35	2N5035	N84	1.10	2N5661	N66	17.00	40372	N66	1.15	AAU10	P66	2.70
2N489	U71	4.90	2N2410	N70	1.40	2N3584	N66	1.35	2N4092	NF79	.82	2N5036	N84	1.20	2N5662	N70	.98	40373	N66	1.65	AAU11	P66	2.70
2N489A	U71	5.40	2N2411	P70	.80	*2N3585	N66	1.55	2N4093	NF79	1.10	2N5086	P57	.30	2N5613	N70	.55	40374	N66	1.65	BC107	N70	.16
2N489B	U71	5.90	2N2412	P70	.80	*2N3605	N50	.18	*2N4121	P54	.27	*2N5087	P57	.30	*2N6027	PUB84	.64	40388	N70	.70	BC107A	N70	.16
2N490	U71	4.95	2N2417	N70	1.10	*2N3606	N50	.18	*2N4122	P54	.27	*2N5088	N57	.30	2N6099	N37	.62	40390	N70	1.05	BC107B	N70	.16
2N490B	U71	6.50	2N2483	N70	.30	*2N3607	N50	.18	*2N4123	N57	.19	2N5089	N57	.30	2N6107	P37	.45	40391	N70	.90	BC108	N70	.16
2N490C	U71	6.90	2N2484	N70	.30	*2N3608	N50	.18	*2N4124	N57	.19	2N5126	N59	.44	2N6108	P37	.55	40392	N27	.70	BC108A	N70	.16
2N491A	U71	5.75	2N2491	P58	2.40	2N3632	N10	12.75	*2N4125	P57	.19	2N5127	N54	.22	2N6109	P37	.55	40394	P27	.90	BC108B	N70	.16
2N491B	U71	6.25	2N2613	P59	.90	*2N3638	N70	.17	*2N4126	N57	.19	2N5128	N54	.22	2N6111	P37	.49	40395	P59	1.45	BC108C	N70	.16
2N491	U71	7.50	2N2614	P59	.70	*2N3638A	P70	.17	2N4220	NF82	.87	2N5129	N54	.22	2N6121	N37	.41	40396	P8N59	1.45	BC109	N70	.16
2N492	U71	6.25	2N2646	U71	.80	*2N3639	P70	.33	2N4221	NF82	.80	2N5130	N54	.22	2N6122	N37	.44	40406	P70	.73	BC109B	N70	.16
2N492A	U71	6.75	2N2647	U71	1.55	*2N3640	P70	.25	2N4222	NF82	.78	2N5131	N54	.22	2N6123	P37	.48	40408	N70	.82	BC109C	N70	.16
2N492B	U71	7.75	2N2696	P70	1.35	*2N3641	N70	.25	2N4223	NF82	.78	2N5133	N54	.22	2N6124	P37	.45	40409	N70	.82	BC113	N54	.22
2N492C	U71	10.00	*2N2711	N50	.30	*2N3642	N70	.22	2N4224	NF82	.78	2N5137	N54	.22	2N6125	P37	.47	40410	P70	.82	BC114	N54	.22
2N493A	U71	7.99	*2N2712	N50	.18	*2N3643	N70	.38	2N4234	P70	1.35	*2N5138	P54	.22	2N6126	N37	.48	40411	N66	3.10	BC115	N66	.22
2N493B	U71	8.75	*2N2713	N50	.25	*2N3644	P70	.40	2N4235	P70	1.65	*2N5139	P54	.22	2N6129	N37	.60	40412	N66	3.10	BC116	P59	.21
2N494	U71	6.90	*2N2714	N50	.22	*2N3645	P70	.38	2N4236	P70	1.65	*2N5140	P54	.22	2N6130	N37	.65	40413	N66	3.10	BC117	P59	.21
2N494A	U71	7.65	2N2848	N70	1.10	*2N3646	N54	.26	2N4237	P70	.99	2N5142	P70	.22	2N6131	N37	.70	40422	N66	2.20	BC118	N54	.22
2N494B	U71	8.40	2N2865	N75	2.20	*2N3662	N50	.29	2N4238	N70	1.28	*2N5143	P70	.22	2N6132	P37	.70	40440	P66	.70	BC119	N70	.33
2N494C	U71	9.35	2N2890	N70	2.50	*2N3663	N50	.29	2N4239	N70	1.55	*2N5172	NF83	.24	2N6133	P37	.70	40447	P70	3.30	BC123	N100	.65
2N549	N70	3.25	2N2891	N70	2.50	*2N3690	N59	.45	2N4240	N66	1.70	2N5179	N50	1.50	2N6134	P37	.70	40462	P66	.90	BC125	N70	.22
2N681	THY	72.20	2N2892	N70	10.00	*2N3691	N54	.45	2N4248	P54	.22	2N5180	N65	.58	2N6179	N36	.77	40467A	NF82	1.05	BC132	N54	.33
2N696	N70	.39	2N2894	P70	.50	*2N3692	N54	.45	*2N4249	P54	.20	2N5181	N20	.55	2N6180	P36	1.05	40468A	NF82	.70	BC134	N54	.22
2N697	N70	.31	2N2903	N73	1.60	*2N3693	N54	.50	2N4250	P54	.26	2N5182	N20	.70	2N6181	P36	.88	40512	N95	1.70	BC135	N54	.22
2N698	N70	.49	2N2904	P70	.31	*2N3694	N54	.50	*2N4254	P54	.83	2N5183	N20	1.20	2N6253	N66	1.00	40513	N84	1.60	BC136	N54	.21
2N699	N70	.58	2N2904A	P70	.31	*2N3702	P50	.14	*2N4258	P54	.50	2N5188	N70	.44	2N6254	N66	1.45	40514	N84	1.60	BC137	P70	.22
2N706	N70	.30	2N2905	P70	.31	*2N3703	P50	.14	*2N4266	N57	.22	2N5189	N70	.49	2N6288	N67	.50	40537	P70	.66	BC138	N70	.44
2N706A	N70	.30	2N2905A	P70	.31	*2N3705	N50	.14	*2N4274	P54	.27	2N5190	N2	.65	2N6289	N38	.50	40543	N84	1.50	BC140	N70	.30
2N708	N70	.30	2N2906	P70	.25	*2N3706	N50	.14	*2N4275	N54	.33	2N5192	N2	.80	2N6290	N37	.50	40576	TR193	2.20	BC142	N70	.32
2N718	N70	.30	2N2906A	P70	.25	*2N3707	N50	.14	*2N4284	P77	.38	2N5193	P2	.75	2N6291	N37	.50	40594	N70	.82	BC143	P70	.32
2N718A	N70	.54	2N2907	P70	.25	*2N3708	N50	.12	*2N4286	N77	.22	2N5194	P2	.80	2N6292	N37	.50	40595	P70	.98	BC147	N61	.13
2N721	P70	1.05	2N2907A	P70	.25	*2N3709	N50	.12	*2N4287	N77	.22	2N5195	P2	.97	2S002	N70	6.00	40600	NF92	.82	BC148	N61	.13
2N722	P70	.45	2N2920	N73	3.30	*2N3710	N50	.12	*2N4288	P77	.22	*2N5209	N57	.35	2S005	N70	8.25	40601	NF92	.82	BC149	N61	.13
2N727	P70	.50	*2N2923	N50	.17	*2N3711	N50	.12	*2N4289	P77	.22	2N5210	N57	.38	2S018	N70	9.75	40602	NF92	.60	BC149A	N61	.13
2N744	N70	.35	*2N2924	N50	.17	2N3712	N70	1.35	2N4290	P77	.22	2N5212	N57	.38	2S019	N70	9.75	40603	NF92	.60	BC152	N61	.13
2N753	N70	.35	*2N2925	N50	.19	2N3713	N66	1.50	2N4291	P77	.22	2N5220	N57	.16	2S024	N89	13.00	40604	NF92	.70	BC153	N54	.30
2N760	N70	.35	*2N2926	N50	.19	2N3714	N66	1.55	2N4292	N77	.22	2N5221	P57	.16	2S025	N89	15.50	40605	NF92	.70	BC154	N54	.30
2N869	P70	.35	2N3010	N70	1.10	2N3715	N66	1.55	2N4293	N77	.22	2N5222	N57	.16	2S095A	N70	3.25	40606	NF92	.70	BC155	N54	.30
2N914	N70	.38	2N3011	N70	.37	2N3716	N66	1.70	2N4294	N77	.22	2N5223	N57	.16	2S102	N70	1.28	40607	NF92	.70	BC156	N61	.15
2N916	N70	.33	2N3012	P70	.37	2N3717	N66	1.70	2N4297	N66	.33	2N5224	N57	.16	2S103	N70	.83	40608	N70	1.65	BC157	N54	.30
2N917	N65	.38	2N3013	N70	.37	2N3724	N70	.65	2N4302	NF83	.31	2N5225	N57	.16	2S104	N70	.55	40609	N66	.6			

PRICE LIST AND DATA

MARSHALL'S

Type	Data	Price	Type	Data	Price	Type	Data	Price	Type	Data	Price	Type	Data	Price
BC182LA	N50	.15	*BC383	N57	.19	BD246C	P37	.93	BF255	N52	.26	BSY7B	N70	1.00
BC182LB	N50	.15	*BC383L	N50	.19	BD249A	N37	2.40	BF257	N70	.35	BSY79	N70	1.42
*BC183	N51	.12	*BC384	N57	.21	BD249C	N37	3.00	BF258	N70	.35	BSY95A	N70	.37
BC183A	N51	.12	*BC384L	N50	.21	BD250A	P37	2.75	BF259	N70	.35	*BU104	N66	1.80
BC183B	N51	.13	*BC407B	N54	.27	BD250C	P37	3.40	BF262	N99	.66	*BU105	N66	1.55
BC183C	N51	.13	*BC408B	N54	.27	BDX32	N66	2.70	BF263	N99	.75	*BU126	N66	2.08
*BC183L	N50	.15	*BC409B	N54	.27	BDY54	N66	1.55	BF270	N65	.55	*BU204	N66	2.20
BC183LA	N50	.15	*BC413	N57	.16	BUX20	N66	15.25	BF271	N65	.27	*BU205	N66	2.40
BC183LB	N50	.15	*BC414	N57	.17	BUX21	N66	17.50	BF273	N53	.55	*BU206	N66	2.70
BC183LC	N50	.15	*BC415	P57	.16	BUX22	N66	19.50	BF274	N53	.55	*BU208	N66	2.70
*BC184	N51	.12	*BC416	P57	.17	BUX23	N66	24.00	*BF324	N51	.35	*ME0401	P54	.22
BC184B	N51	.13	*BC427	N51	.13	BUX24	N66	26.00	*BF336	P70	.42	*ME0402	P54	.22
BC184C	N51	.13	*BC547A	N51	.13	BUX25	N66	28.00	*BF337	N70	.49	*ME0404	P54	.17
*BC184L	N50	.15	*BC547B	N51	.13	BD433	N2	.44	*BF338	N70	.52	*ME0411	P54	.22
BC184LB	N50	.15	*BC549	N51	.14	BD434	P2	.46	*BF355	N70	.53	*ME0412	P54	.22
BC184LC	N50	.15	*BC549B	N51	.14	BD435	N2	.46	*BF362	N104	.53	*ME0413	P54	.17
*BC204	P54	.17	*BC549C	N51	.15	BD436	P2	.46	*BF363	N104	.53	*ME0414	P54	.22
*BC205	P54	.17	*BC549E	N51	.15	BD437	N2	.55	*BF450	P52	.24	*ME0461	P54	.27
*BC206	P54	.17	*BC557	P51	.13	BD438	P2	.55	*BF451	P52	.22	*ME0462	P54	.27
*BC207	N54	.17	*BC558	P51	.14	BD441	N2	.44	*BF452	N2	.44	*ME1001	N54	.17
*BC208	N54	.17	*BC559	P51	.15	BD442	P2	.44	*BF458	N2	.49	*ME1002	N54	.17
*BC209	N54	.17	BCY10	P6B	1.10	*BD529	N36	.49	*BF459	N2	.55	*ME1075	N54	.22
*BC212	P51	.15	BCY30	P70	1.10	*BD530	P36	.55	*BFR39	N50	.30	*ME1100	N54	.22
*BC212A	P51	.15	*BCY31	P70	1.10	BD535	N37	.70	*BFR40	N50	.30	*ME1120	N54	.27
BC212B	P51	.15	BCY32	P70	1.10	BD536	P37	.70	*BFR41	N50	.30	*ME3001	N54	.27
*BC212L	N50	.18	*BCY33	P70	1.10	BD537	N37	.74	*BFR79	P50	.30	*ME4002	N54	.16
*BC212LA	P50	.18	BCY34	P70	1.10	BD538	P37	.77	*BFR80	P50	.30	*ME4003	N54	.16
BC212LB	P50	.18	*BCY3B	P70	2.20	BD539	P37	.60	*BFR81	P50	.30	*ME4004	N54	.16
*BC213	P51	.15	BCY40	P70	1.05	BD540	P37	.60	BFS21A	NF79	2.90	*ME4101	N54	.11
BC213A	P51	.15	*BCY42	N70	.65	BD581	N37	1.10	BFS2B	NF79	1.50	*ME4102	N54	.11
BC213B	P51	.15	*BCY43	N70	.76	BD582	P37	1.30	*BFS61	N48	.33	*ME4103	N54	.11
BC213C	P51	.15	BCY54	P70	2.40	BD675	N02	.60	*BFS98	P48	.33	*ME4104	N54	.11
*BC213L	P50	.17	BCY58	N70	.27	BD676	P02	.65	BFW10	NF79	.83	*ME6001	N54	.16
*BC213LA	P50	.17	*BCY59	N70	.27	BD677	NP2	.70	BFW11	NF79	.83	*ME6002	N54	.16
BC213LB	P50	.17	BCY66	N70	2.20	BD678	P02	.82	BFW30	N65	2.45	*ME6003	N54	.16
BC213LC	P50	.17	*BCY67	P70	2.70	BDX14	P2B	1.32	BFW43	P70	1.65	*ME6101	N54	.22
*BC214	P51	.17	BCY70	P70	.21	BDX18	P66	1.90	BFW59	N61	1.75	*ME6102	N54	.22
*BC214B	P51	.17	*BCY71	P70	.26	BDY11	N66	3.30	BFW87	P61	1.75	*ME8001	N70	.22
BC214C	P51	.17	BCY72	P70	.18	BDY12	N66	3.30	BFW90	P61	1.75	*ME8002	N70	.22
*BC214L	P50	.18	*BCY77	P70	.70	BDY18	N66	3.80	BFX12	P70	.35	*ME8003	N70	.22
*BC214LB	P50	.18	BCY78	P70	.43	BDY20	N66	1.10	BFX13	P70	.33	*ME9001	N54	.22
BC214LC	P50	.18	*BCY79	P70	.41	BDY23	N66	2.45	BFX19	N65	.49	*ME9002	N54	.22
*BC237B	N51	.15	BCY87	N101	5.35	BDY24	N66	2.65	BFX20	P70	.34	MJ400	N66	1.45
*BC238A	N51	.13	*BCY8B	N101	3.99	BDY25	N66	2.85	BFX30	P70	.34	MJ430	P70	1.45
*BC238B	N51	.13	BCY89	N101	3.80	BDY38	N66	1.10	BFX34	N70	.66	MJ481	N66	1.70
*BC238C	N51	.13	BCY10	P6B	1.65	BDY55	N66	1.90	BFX37	P70	.49	MJ490	P66	1.49
*BC239B	N51	.16	BD115	N70	.88	BDY56	N66	2.10	BFX68	P70	1.10	MJ491	P66	2.10
*BC239C	N51	.17	BD116	N66	1.35	BDY57	N66	5.90	BFX84	N70	.30	MJ901	PD66	2.45
*BC250A	P51	.17	BD121	N66	2.20	BDY58	N66	6.50	BFX85	N70	.38	MJ1001	ND66	2.10
*BC250C	P51	.17	BD124	N66	2.20	BDY60	N66	1.65	BFX86	N70	.30	MJ2500	PD66	2.70
*BC251	P51	.17	BD131	N67	.55	BDY61	N66	2.75	BFX87	P70	.35	MJ2501	PD66	2.70
*BC251A	P51	.17	BD132	P67	.75	BDY62	N66	2.75	BFX88	P70	.30	MJ2505	P66	1.35
*BC251C	P51	.17	*BD135	N67	.40	BDY92	N66	2.75	BFX89	N70	1.37	MJ3000	ND66	2.15
*BC252	P51	.20	*BD136	P67	.40	BF115	N20	.39	BFY10	N70	1.10	MJ3001	ND66	2.35
*BC252C	P51	.22	*BD137	N67	.41	BF119	N70	1.10	BFY18	N70	1.10	MJ4502	P66	4.90
*BC253	P51	.24	*BD138	P67	.41	BF121	N19	.60	BFY19	N70	1.10	*MJ5340	N2	.62
*BC253B	N51	.24	*BD139	N67	.43	BF123	N19	.60	BFY37	N70	1.10	MJ5370	P2	.62
*BC253C	P51	.24	*BD140	P67	.43	BF134	N59	.60	BFY39	N70	.38	MJ5371	P2	.66
*BC256A	P51	.29	BD142	N66	.70	BF137	N70	.60	BFY41	N70	.88	*MJ5520	N2	.50
*BC257A	P57	.18	BD153	N67	1.05	BF152	N54	.27	BFY50	N70	.27	MJ5521	N2	.70
*BC258A	P57	.18	BD155	N67	1.10	BF153	N54	.27	BFY51	N70	.27	MJ2955	P2	1.65
*BC258B	P57	.19	BD157	N67	.70	BF154	N54	.27	BFY52	N70	.27	MJ3055	N2	1.05
*BC259B	P57	.19	BD158	N67	.70	BF157	N70	.48	BFY53	N70	.37	*MPB111	N111	.40
BC260B	P70	.17	BD159	N67	.70	BF159	N54	.37	BFY72	N70	.99	*MPB112	N111	.45
BC260C	P70	.18	BD160	N66	3.40	BF160	N54	.33	BFY75	N70	.77	*MPB113	N111	.50
BC261A	P70	.25	BD181	N66	1.90	BF161	N65	.65	BFY76	N70	1.10	*MPB121	N111	.45
BC261B	P70	.27	BD182	N66	2.20	BF166	N65	.44	BFY90	N65	1.35	*MPB122	N111	.45
BC261C	P70	.26	BD183	N66	2.35	BF167	N20	.37	BR101		.55	*MPB123	N111	.50
BC262A	P70	.26	BD187	N67	.95	BF170	N70	.76	BRY30	THY106.55		*MPB131	N111	.50
BC262B	P70	.26	BD201	N37	1.10	BF173	N20	.37	BRY39	SCS90	.55	*MPF102	NF86	.33
BC262C	P70	.27	BD202	P37	1.25	BF177	N70	.27	BRV56	THY106.38		*MPF103	NF86	.44
BC263B	P70	.26	BD203	N37	1.28	BF178	N70	.27	BSW41	N70	1.65	*MPF104	NF86	.44
BC263	P70	.32	BD204	P37	1.35	BF179	N70	.33	BSW66	N70	.90	*MPF105	NF86	.44
BC264B	P70	.65	BD220	N37	.66	BF180	N65	.37	BSW67	N70	1.09	*MPF111	NF86	.30
BC266A	P70	.34	BD221	N37	.66	BF181	N65	.37	BSX19	N70	.35	*MPF112	NF86	.30
BC266B	P70	.35	BD222	N37	.66	BF182	N65	.37	BSX20	N70	.35	MPS005	N57	1.10
BC300	N70	.43	BD223	P37	.75	BF183	N65	.44	BSX21	N70	.35	MPS3563	N57	.20
BC301	N70	.43	BD224	P37	.75	BF184	N20	.41	BSX22	N70	.35	MPS3638	P57	.22
BC302	N70	.37	BD232	N2	.75	BF185	N20	.37	BSX26	N70	.88	MPS3640	P57	.22
BC303	P70	.54	BD233	N2	.45	*BF194	N60	.16	BSX27	N70	.82	MPSA05	N57	.27
BC304	P70	.60	BD234	P2	.46	*BF195	N60	.16	BSX29	P70	.53	MPSA06	N57	.27
*BC307	P51	.16	BD235	N2	.46	*BF196	N60	.16	BSX39	N70	1.20	MPSA10	N57	.22
*BC307A	P51	.16	BD236	P2	.44	*BF197	N60	.18	BSX60	N70	.71	MPSA12	ND57	.33
*BC307B	P51	.16	BD237	N2	.44	*BF198	N52	.19	BSX61	N70	.53	*MPSA16	N57	.22
*BC308	P51	.16	BD238	P2	.44	*BF199	N52	.19	BSX76	N70	.60	*MPSA18	N57	.22
*BC308B	P51	.16	BD239A	N37	.44	BF200	N65	.38	BSX77	N70	.60	MPSA55	P57	.27
*BC309A	P51	.16	BD239C	N37	.59	*BF224J	N18	.22	BSY10	N70	1.10	MPSA56	P57	.27
*BC309B	P51	.16	BD240A	P37	.49	*BF225J	N18	.27	BSY24	N70	.52	MPSL01	N57	.32
*BC309C	P51	.16	BD240C	P37	.59	BF238	N18	.55	BSY25	N70	.65	MPSL51	P57	.32
*BC317	N57	.15	BD241A	N37	.49	BF240	N52	.24	BSY26	N70	.55	MPSU01	N36	.49
*BC318	N57	.14	BD241C	N37	.65	BF241	N52	.24	BSY27	N70	.55	MPSU05	N36	.55
*BC321	P57	.19	BD242A	P37	.55	*BF244A	NF78	.38	BSY28	N70	.44	MPSU06	N36	.60
*BC322	P57	.19	BD242C	P37	.62	BF244B	NF78	.33	BSY29	N70	1.10	MPSU07	N36	.60
*BC323	N70	.41	BD243A	N37	.65	*BF245A	NF103	.44	BSY38	N70	.33	MPSU13	N36	.55
*BC327	P51	.22	BD243C	N37	.87	*BF245B	NF103	.44	BSY39	N70	.33	MPSU51	P36	.55
*BC328	P51	.20	BD244A	P37	.70	*BF246A	NF78	.82	BSY51	N70	.33	MPSU55	P36	.60
*BC337	N51	.20	BD244C	P37	.87	BF246B	NF78	.82	BSY52	N70	.33	MPSU56	P36	.65
*BC338	N51	.23	BD245A	N37	.69	BF247A	NF78	.49	BSY53	N70	.33	MPSU57	P36	.70

CAPACITORS

SIEMENS—MULLARD
THOMSON CSF

ELECTROLYTIC — AXIAL



Miniature electrolytics
By SIEMENS and
MULLARD
Types B41313 B412B3
B41010, 015 - 016

UF	Volts	Size mm	Price 1-99	UF	Volts	Size mm	Price 1-99
47	100	4.5 x 11	£0.14	47	40	8.5 x 15	£0.12
1.0	40	3.2 x 11	£0.14	47	63	8.5 x 20	£0.15
1.0	100	4.5 x 11	£0.14	68	16	6.7 x 18.5	£0.10
1.5	63	6.1 x 12.5	£0.10	100	16	8.5 x 15	£0.13
2.2	25	3.2 x 11	£0.14	100	25	8.5 x 17.5	£0.14
2.2	63	4.5 x 11	£0.14	100	40	10 x 20	£0.16
2.2	100	5.8 x 11	£0.15	100	63	10 x 25	£0.22
3.3	63	6.1 x 12.5	£0.10	100	100	14 x 30	£0.30
4.7	16	3.2 x 11	£0.14	150	16	8.3 x 18.5	£0.13
4.7	40	4.5 x 11	£0.14	150	25	10.3 x 18.5	£0.15
4.7	63	5.8 x 11	£0.15	220	16	8.5 x 20	£0.15
4.7	100	6.5 x 17.5	£0.11	220	25	10 x 20	£0.18
6.8	40	4.8 x 12.5	£0.09	220	40	10 x 25	£0.22
6.8	63	6.1 x 12.5	£0.09	220	63	14 x 30	£0.31
10	25	4.5 x 11	£0.14	220	100	18 x 30	£0.42
10	40	5.8 x 11	£0.15	470	16	10 x 25	£0.20
10	63	6.5 x 17.5	£0.12	470	25	12 x 30	£0.23
10	100	8.5 x 15	£0.13	470	40	14 x 30	£0.28
15	16	4.8 x 12.5	£0.09	470	63	18 x 30	£0.44
15	40	6.1 x 12.5	£0.09	470	100	21 x 40	£0.66
15	63	6.7 x 18.5	£0.09	1000	16	14 x 30	£0.27
22	25	5.8 x 11	£0.15	1000	25	16 x 30	£0.38
22	40	6.5 x 17.5	£0.12	1000	40	18 x 35	£0.47
22	63	8.5 x 15	£0.12	1000	63	21 x 40	£0.66
22	100	8.5 x 20	£0.15	2200	16	18 x 35	£0.46
33	16	6.1 x 12.5	£0.09	2200	25	21 x 40	£0.55
33	40	6.7 x 18.5	£0.10	2200	40	25 x 40	£0.60
47	16	6.5 x 20	£0.12	4700	16	21 x 40	£0.66
47	25	6.5 x 17.5	£0.12	4700	25	25 x 40	£0.90

ELECTROLYTIC — RADIAL

HIGH RIPPLE

UF	Volts DC	Size mm	Price 1-99
1000	40	25 x 35	£1.02
1000	63	25 x 45	£1.15
2200	25	25 x 45	£1.10
2000	40	30 x 45	£1.18
2200	63	30 x 55	£1.43
2200	100	30 x 55	£1.65
4700	25	30 x 45	£1.26
4700	40	35 x 55	£1.50
4700	63	40 x 74	£2.20
10000	25	35 x 55	£1.98

Tol
+50%
-10%



SIEMENS B41070

ELECTROLYTIC — PLUGGABLE

TYPE B41316/7
SIEMENS

UF	Volts DC	Size mm	PRICE 1-99
1.0	63	8.7 x 12.6	£0.13
2.2	63	8.7 x 12.5	£0.13
4.7	63	8.7 x 12.5	£0.13
10	63	8.7 x 12.5	£0.13
22	63	10.7 x 12.5	£0.13
47	63	12.7 x 16.5	£0.16
100	63	15 x 20	£0.21
220	15	12.7 x 16.5	£0.15
470	16	15 x 20	£0.20
1000	16	15 x 30	£0.30

Tol
+100%
-10%



TANTALUM BEAD

UF	Volt DC	Size mm	Price 1-99	UF	Volts	Size mm	Price
0.1	35	9 x 5	£0.17	10	6.3	10 x 5.5	£0.17
0.22	35	9 x 5	£0.17	10	16	11 x 6	£0.21
0.47	35	9 x 5	£0.17	15	15	12 x 7	£0.23
1.0	35	9 x 5	£0.17	15	25	12 x 7.5	£0.25
2.2	16	9 x 5	£0.17	22	6.3	11 x 6	£0.21
2.2	35	10 x 5.5	£0.17	33	10	11 x 6	£0.23
4.7	16	10 x 15	£0.17	47	6.3	12 x 7.5	£0.23
4.7	35	11 x 6	£0.21	100	3	12 x 7.5	£0.23

TYPE B45134 SIEMENS
Radial lead Tol ± 20%
MINIATURE TANTALUM BEAD



CERAMIC DISC 63V

SIEMENS
B37448/9

Flat Ceramic Capacitors from a New Material
with Dielectric Constant of 50,000


The development of a new titanate ceramic material represents a step towards reducing capacitor size which is significant for capacitors used for coupling and decoupling in AF circuits.



UF	VDC	Size mm	Price
.01	63	4 x 2.5 x 4	£0.07
.022	63	4 x 2.5 x 4	£0.07
.033	63	4 x 2.5 x 6	£0.07
.047	63	4 x 2.5 x 8	£0.07
.068	63	4 x 2.5 x 10	£0.09
.1	63	4 x 2.5 x 9	£0.09
.22	63	6 x 2.5 x 18	£0.19

HIGH VOLTAGE CERAMIC DISC

Capacitance VDC	Price	Capacitance VDC	Price
100pf 1kv	£0.08	2,200pf 2kv	£0.10
100pf 2kv	£0.10	2,200pf 4kv	£0.13
100pf 3kv	£0.10	2,200pf 5kv	£0.19
100pf 4kv	£0.10	3,300pf 2kv	£0.12
220pf 6kv	£0.08	3,300pf 4kv	£0.16
470pf 2kv	£0.08	4,700pf 2kv	£0.12
470pf 6kv	£0.11	4,700pf 4kv	£0.20
1,000 2kv	£0.08	10,000pf 2kv	£0.14
1,000pf 4kv	£0.10	10,000pf 3kv	£0.19
1,000pf 6kv	£0.17		

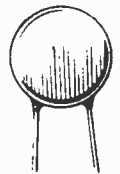

HIGH VOLTAGE

CERAMIC PLATE

MULLARD

ALL 63 VDC WORKING 6p EACH
Values available pF
Quantity Price on request

Tolerance
1-10pF + 25%
10-330pF + 2%
390-1000pF + 5%
1000pF-10kP + 10%

Capacitance	Price	Capacitance	Price
1pF	10	100	1000
1.2	12	120	1200
1.5	15	150	1500
1.8	18	180	1800
2.2	22	220	2200
2.7	27	270	2700
3.3	33	330	3300
3.9	39	390	3900
4.7	47	470	4700
5.6	56	560	5600
6.8	68	680	6800
8.2	82	820	10000

VERY NEAT AND
COMPAT 1" PIN
SPACING

pF	Price	Size	Dims
1.8-22		1	3.5 x 4.5mm
27-47		2	4.5 x 5.5mm
56-68		3	5.5 x 6.5mm
82-100		4	6.5 x 7.5mm
120-150		5	6.5 x 10.5mm
180-220		4	6.5 x 7.5mm
270-330		5	6.5 x 10.5mm

POLYSTYRENE

Close tolerance Polystyrene capacitors from Siemens B31110/B31310

5% Tolerance. 160v working



Values available
10pf, 15pf, 22pf, 33pf, 47pf, 68pf, 100pf, 150pf,
220pf, 330pf, 470pf, 680pf, 1000pf

Price 1-99

6p each


1500pf, 2200pf, 3300pf, 4700pf, 6800pf,
10000pf

10p each

POLYESTER

MULLARD C280 SERIES
AN INEXPENSIVE WIDELY USED
CAPACITOR - DIMENSIONS IN MM

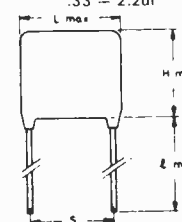250 VDC-RADIAL LEADS
Metallized film capacitors
Tol .01 - .22 + 20%
.33 - 2.2uf + 10%



MULLARD


UF	Price	S	T	L	H
0.01	£0.06	10.2	4	12.5	9
0.015	£0.06	10.2	4	12.5	9
.033	£0.06	10.2	4	12.5	9
0.022	£0.06	10.2	4	12.5	9
0.033	£0.06	10.2	4	12.5	9
0.047	£0.06	10.2	4	12.5	9
0.068	£0.06	10.2	5	12.5	10
0.1	£0.06	10.2	6	12.5	11
0.15	£0.08	15.3	6	17.5	11
0.22	£0.09	15.3	7	17.5	12
0.33	£0.12	20.3	6.5	22.5	11.5
0.47	£0.14	20.3	7.5	22.5	12.5
0.68	£0.20	20.3	9.5	22.5	14.5
1	£0.24	27.9	9.5	30	14.5
1.5	£0.36	27.9	10.5	30	18
2.2	£0.37	27.9	12.5	30	20.5

ATTRACTIVE QUANTITY DISCOUNTS

CAPACITORS

POLYCARBONATE

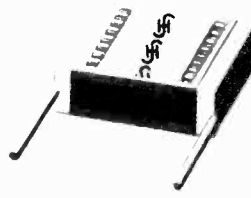Polycarbonate— **B32540/60**
Polyester **SIEMENS**



7.5mm lead spacing tinned

1—99	Price
250 Volt working	
001 9 x 2.6 x 7.3	£0.07
0022 9 x 2.6 x 7.3	£0.07
0033 9 x 2.3 x 7.3	£0.07
.0047 9 x 2.3 x 7.3	£0.07
.0068 9 x 2.7 x 7.3	£0.07
.0082 9 x 2.7 x 7.3	£0.07
.01 9 x 2.3 x 7.3	£0.07
.012 9 x 2.5 x 7.3	£0.07
.015 9 x 2.9 x 7.3	£0.07
.022 9 x 2.6 x 7.3	£0.07
.027 9 x 2.4 x 7.3	£0.07
.033 9 x 2.6 x 7.3	£0.07
.039 9 x 2.9 x 7.3	£0.07
.047 9 x 3.2 x 7.3	£0.07
.056 9 x 3.5 x 7.5	£0.07
.068 9 x 3.5 x 7.5	£0.09
.082 9 x 3.5 x 11	£0.11
.1 9 x 3.9 x 11	£0.11
100 Volt DC	
.12 9 x 3.5 x 8.3	£0.10
.15 9 x 3.6 x 10	£0.10
.18 9 x 4.1 x 10	£0.12
.22 9 x 4.7 x 10	£0.12
.27 9 x 5.0 x 11	£0.16
.33 9 x 5.5 x 11.5	£0.16
.39 9 x 6.6 x 11.5	£0.20
.47 9 x 7.2 x 12.5	£0.20
.56 9 x 8.4 x 12.5	£0.25
.68 9 x 8 x 13	£0.25

Self-healing layer capacitor with polycarbonate as dielectric. In accordance with DIN 41379 these types are designated MKC capacitors

B32541/61 Polycarbonate/Polyester as B32540/60 but 10mm lead spacing — also available in 100 and 250 volt DC working

1—99	Price
250 Volt working	
UF Dimensions mm	
.01 11.5 x 3.2 x 6.6	£0.07
.015 11.5 x 3.2 x 6.6	£0.07
.022 11.5 x 3.2 x 6.6	£0.07
.047 11.5 x 3.2 x 6.6	£0.07
.068 11.5 x 3.2 x 6.6	£0.07
100 Volt working	
.22 11.5 x 3.9 x 9.5	£0.11
.47 11.5 x 5.3 x 11.5	£0.17
1.0 11.5 x 9.8 x 11.5	£0.31
.22	£0.60

POLYESTER

SIEMENS B32234 MKH 20% Tol
Self healing flat capacitor winding with polyethelene-terephthalene dielectric to DIN 41379 spec. Encapsulated and epoxy resin sealed. The case is provided with spacers to improve solderability in solder bath, parallel leads, plug in, suitable for printed circuits



1—99	Price
100Vot DC	
uF Dimensions mm	
.1 4 x 9.5 x 13	£0.14
.15 5 x 10.5 x 13	£0.16
.22 6 x 11.5 x 13	£0.17
.33 5.5 x 11 x 18	£0.20
.47 5.5 x 11 x 18	£0.25
.68 7 x 13 x 18	£0.30
1.0 9 x 14.5 x 18	£0.36
1.5 7 x 16.5 x 27	£0.47
2.2 8.5 x 18.5 x 27	£0.54
3.3 10.5 x 19 x 27	£0.70
4.7 11 x 20 x 32	£0.82
6.8 13 x 22.5 x 32	£1.11
250Vot DC	
uF Dimensions	
.047 4 x 9.5 x 13	£0.13
.1 5.5 x 11 x 18	£0.14
.22 7 x 13 x 18	£0.15
1.0 8.5 x 18.5 x 27	£0.35
400 Volt DC	
.01 4 x 9.5 x 13	£0.11
.015 4 x 9.5 x 13	£0.11
.022 4 x 9.5 x 13	£0.11
.047 5.5 x 11 x 18	£0.15

PLASTIC FOIL—HIGH RELIABILITY

SIEMENS B32110
High reliability plastic foil
Axial lead 20% Tol MKL



1—99	Price
63 Volt working	
uF Dimensions	
.15 5.4 x 18.5	£0.53
.22 5.4 x 18.5	£0.56
.33 6.4 x 18.5	£0.59
.47 7.4 x 18.5	£0.66
.68 7.4 x 18.5	£0.70
1.0 7.4 x 21	£0.78
1.5 8.4 x 21	£0.80
2.2 10.7 x 21	£1.37
100 Volt Working	
.1 5.4 x 18.5	£0.61
1.0 9.4 x 21	£1.16

Self-healing tubular capacitor winding with cellulose acetate as dielectric. In accordance with DIN 41379 these types are designated MKU capacitors.

Enclosed in tubular metal case, shrunk sleeve insulated, epoxy resin sealed face ends. Central axial leads.

TRIMMERS

MINIATURE FILM DIELECTRIC

Type	Capacitance swing pF	Minimum capacitance pF	£. p
808 00005	8	2	£0.20
808 00006	20	2	£0.22
808 01001	59.5	5.5	£0.27



MULLARD

METALLISED POLYESTER

up to 630 volt

B32231 metallised Polyester from SIEMENS

Axial leads
Tolerance 20%
Type MKH similar to Mullard C281 range available in three voltages 250, 400 and 630 VDC



1—99	Price	400 Volt DC	Price	1—99	Price
250 Volt DC				400 Volt DC	
uF Dimensions mm		022 4.5 x 7.5 x 14	£0.14	047 4.5 x 8 x 19	£0.15
.047 4.5 x 8.5 x 14	£0.14	1 5.5 x 8.5 x 19	£0.16	630 Volt DC	
.068 5.5 x 9 x 14	£0.15	.01 4.5 x 8 x 14	£0.13	.015 4.5 x 8 x 14	£0.14
.1 6 x 9 x 14	£0.15	.022 5 x 8.5 x 14	£0.15	.047 5 x 10.5 x 19	£0.16
.22 4.5 x 10.5 x 19	£0.16	.01 5 x 12.5 x 26.5	£0.30	15 6.5 x 14 x 26.5	£0.31
.33 7 x 11 x 19	£0.19	22 7.5 x 16.5 x 26.5	£0.32	47 10 x 22 x 29	£0.53
.47 4.5 x 13.5 x 26.5	£0.22				
.68 6 x 15 x 26.5	£0.26				
1.0 8 x 17 x 26.5	£0.35				
1.5 8.5 x 20.5 x 29	£0.42				
2.2 10.5 x 22.5 x 29	£0.54				
4.7 12 x 27.5 x 44	£1.16				
10 19.5 x 34.5 x 44	£1.94				

NB 630 V.d.c. rating equivalent 250V rms.

Self-heating flat capacitor winding with polyethylene-terephthalate as dielectric. In accordance with DIN 41379 these types are designated MKT capacitors.

Capacitor winding coated with insulating material. epoxy resin sealed face ends.

METALLISED POLYESTER EXTENDED FOIL-MULLARD

MULLARD C296 SERIES
400 VDC WORKING
±10% Tolerance
Temp range — 40 to +80 C

0.47µF
±10%

uF	Dimensions	Price	uF	Dimensions	Price
0.001	21 7.5	£0.11	0.033	21 10	£0.14
0.0015	21 7.5	£0.11	0.047	21 11.5	£0.16
0.0022	21 7.5	£0.11	0.068	35 9.5	£0.17
0.0033	21 7.5	£0.11	0.1	35 11	£0.20
0.0047	21 7.5	£0.11	0.15	35 12.5	£0.25
0.0068	21 7.5	£0.11	0.22	35 14.5	£0.33
0.01	21 7.5	£0.12	0.33	35 17	£0.47
0.015	21 7.5	£0.12	0.47	35 19.5	£0.56
0.022	21 8.5	£0.12			

Radial leads

MICA

Close tolerance — suitable for pulse operation
Tol + 5pF below 50pF - 1% for 50pF and higher

SILVERED MICA CAPS
500 VDC WORKING

Values available in pF	Price
2.2, 3.3, 5, 10, 18, 20, 22	10p
25, 27, 30, 33, 39, 47, 50	10p
56, 68, 75, 82, 100, 120, 150	10p
180, 200, 220pF	10p
250, 270, 300, 390, 470	13p
500, 560, 580, 820.F	13p
1,000	18p



DIODES AND RECTIFIERS

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
AA116	£0.13	BA243	£0.38	BY206	£0.22	DK110	£0.36	Z344	£0.28	IN4009	£0.27
AA118	£0.13	BA244	£0.55	BY207	£0.22	GEX23A	£0.08	IN345	£0.17	IN4148	£0.08
AA119	£0.14	BA316	£0.07	BYW11-600	ITT33	£0.08	IN461	£0.15	IN4150	£0.20	
AA129	£0.10	BA317	£0.07	BYW11-800	ITT44	£0.08	IN659	£0.08	IN4154	£0.22	
AA144	£0.11	BA318	£0.07	BYW11-1000	ITT210	£0.75	IN821	£0.35	IN4446	£0.15	
AA130	£0.18	*BAV10	£0.09	BYW11-1000	ITT920	£0.11	IN823	£0.55	IN4448	£0.09	
AA132	£0.18	*BAV19	£0.11	BYW11-1000	ITT921	£0.12	IN825	£0.65	IN4517	£0.12	
AA133	£0.20	*BAV20	£0.12	BYW12-100	ITT922	£0.13	IN914	£0.08	IN5172	£0.19	
AA134	£0.20	*BAV49	£0.17	BYW12-100	ITT923	£0.20	IN916	£0.08	IN5176	£0.30	
AA135	£0.35	*BAX13	£0.07	BYW12-200	ITT2001	£0.12	IN1183R	£1.00	IN5233A	£0.30	
AA136	£0.25	*BAX16	£0.08	BYW12-200	ITT2002	£0.13	IN1188	£2.50	IN5400	£0.15	
AA137	£0.20	BAY31	£0.17	BYW12-200	ITT2003	£0.25	IN1190	£2.75	IN5401	£0.17	
BA100	£0.20	BAY36	£0.28	BYW12-400	OA10	£0.60	IN1194	£1.25	IN5402	£0.18	
BA102	£0.20	BAY38	£0.28	BYX10	OA47	£0.15	IN1194A	£1.30	IN5404	£0.19	
BA111	£0.30	BAY44	£0.17	BYX10	OA85	£0.20	IN1196	£1.80	IN5406	£0.25	
BA115	£0.17	BAY71	£0.18	BYX97-600	OA90	£0.09	IN1198A	£2.75	IN5407	£0.30	
BA127	£0.22	BAY72	£0.22	BYX97-1200	OA91	£0.09	IN1201A	£0.80	IN5408	£0.45	
BA130	£0.11	BAY74	£0.19	BYX99-600	OA95	£0.11	IN3492	£0.88	IS44	£0.08	
BA133	£0.28	BB103	£0.35	BYX99-1200	OA200	£0.11	IN3493	£0.95	IS120	£0.16	
BA138	£0.25	*BB104	£0.44	BYX99-1200	OA202	£0.15	IN3595	£0.33	IS121	£0.16	
BA142	£0.19	*BB105A	£0.33	CL1506	OA211	£0.27	IN3602	£0.17	IS130	£0.11	
BA144	£0.14	*BB105B	£0.33	CL1507	OAZ200	£0.30	IN3604	£0.17	IS131	£0.11	
BA145	£0.20	*BB105G	£0.40	CL1507	OAZ201	£0.30	IN3766	£3.95	IS132	£0.25	
BA154	£0.11	*BB109	£0.40	CV7047	OAZ202	£0.30	IN3766R	£4.00	IS134	£0.25	
BA155	£0.13	*BB139	£1.25	CV7047	OAZ206	£0.30	IN3768R	£4.75	IS136	£0.45	
BA156	£0.16	BY103	£0.55	CV7071	OAZ209	£0.30	IN3826	£1.35	IS420	£0.80	
BA157	£0.32	BY126	£0.32	CV7130	OAZ212	£0.30	IN4001	£0.07	IS421	£0.85	
BA158	£0.42	BY127	£0.39	CV7130	OAZ237	£0.30	IN4002	£0.08	IS423	£0.90	
BA159	£0.55	BY133	£0.35	CV7641	OAZ241	£0.30	IN4003	£0.09	IS425	£0.95	
BA182	£0.22	BY134	£0.33	*DD000	OAZ244	£0.20	IN4004	£0.09	IS427	£1.10	
BA201	£0.10	BY182	£1.65	D1300A	OAZ245	£0.20	IN4005	£0.11	IS429	£1.45	
BA202	£0.10	BY189	£3.75	DK13	OAZ270	£0.20	IN4006	£0.12	IS940	£0.07	
BA203	£0.13	BY190	£3.70	DK14	TV12	£0.17	IN4007	£0.13	IS941	£0.08	
								IS961	£0.18		

RECTIFIER DIODE FINDER CHART

P.I.V.	50V	100V	200V	400V	600V	800V	1000V	1200V
1 AMP	IN4001	IN4002	IN4003	IN4004	IN4005	IN4006	IN4007	BY127
3 AMPS	IN5400	IN5401	IN5402	IN5404	IN5406	IN5407	IN5408	—
6 AMPS	—	—	—	—	BYW11-600	BYW11-800	BYW11-1000	—
10 AMPS	—	IS420	IS421	IS423	IS425	IS427	IS429	—
15 AMPS	—	BYW12-100	BYW12-200	BYW12-400	BYX99-600	—	—	BYX99-1200
47 AMPS	—	—	—	—	BYX97-600	—	—	BYX97-1200

* NB. BYW11 & BYW12 ARE FAST RECOVERY RECTIFIERS.





ZENERS

ZENERS-400mW - 12p		ZENERS-2.5W - 65p	
BZX83	C2.7	BZX70	C7V5
BZX83	C3.0	BZX70	C8V2
BZX83	C3.3	BZX70	C9V1
BZX83	C3.6	BZX70	C10
BZX83	C3.9	BZX70	C11
BZX83	C4.3	BZX70	C12
BZX83	C4.7	BZX70	C13
BZX83	C5.1	BZX70	C15
BZX83	C5.6	BZX70	C16
BZX83	C6V2	BZX70	C18
BZX83	C6V8	BZX70	C20
BZX83	C7V5	BZX70	C22
BZX83	C8V2	BZX70	C24
BZX83	C9V1	BZX70	C27
BZX83	C10	BZX70	C30
BZX83	C11	BZX70	C33
BZX83	C12	BZX70	C36
BZX83	C13	BZX70	C39
BZX83	C15	BZX70	C43
BZX83	C16	BZX70	C47
BZX83	C18	BZX70	C51
BZX83	C20	BZX70	C56
BZX83	C22	BZX70	C62
BZX83	C24	BZX70	C68
BZX83	C27	BZX70	C75
BZX83	C30		
BZX83	C33		
BZX83	C36		
BZX83	C39	ZENERS-5W - 76p	
BZX83	C43	BZV40	C3V3
BZX83	C47	BZV40	C3V6
		BZV40	C4V0
		BZV40	C4V3
		BZV40	C4V7
		BZV40	C5V1
		BZV40	C5V6
		BZV40	C6V2
		BZV40	C6V8
		BZV40	C7V5
		BZV40	C8V2
		BZV40	C8V7
		BZV40	C9V1
		BZV40	C10V
		BZV40	C11V
		BZV40	C12V
		BZV40	C15V
		BZV40	C33V
		BZV40	C68V
		BZV40	C120V
		ZENERS-20W - 95p	
		BZY93	C6V8
		BZY93	C7V5
		BZY93	BV2
		BZY93	9V1
		BZY93	10
		BZY93	11
		BZY93	12
		BZY93	C13V
		BZY93	15
		BZY93	16
		BZY93	18
		BZY93	20
		BZY93	22
		BZY93	24
		BZY93	27
		BZY93	30
		BZY93	33
		BZY93	36
		BZY93	39
		BZY93	43
		BZY93	47
		BZY93	51
		BZY93	56
		BZY93	62
		BZY93	68
		BZY93	75

MULLARD SIEMENS
AND
SESCOEM


BRIDGE RECTIFIERS

TYPE	RATING	CASE	PRICE	TYPE	RATING	CASE	PRICE	TYPE	RATING	CASE	PRICE
W005/1T1005	1A	50v	£0.28	SO2	2A	200v	£0.48	PW01	6A	100v	£0.95
W01	1A	100v	£0.30	SO4	2A	400v	£0.60	PW02	6A	200v	£0.97
W02	1A	200v	£0.32	SO6	2A	600v	£0.70	PW04	6A	400v	£1.08
W04	1A	400v	£0.40	SO8	2A	800v	£0.84	PW06	6A	600v	£1.18
W06	1A	600v	£0.50	6A600	6A	600v	£1.35	PW08	6A	800v	£1.28
VM18	1A	100v	£0.44	BY164	1.4A	120v	£0.75				
VM28	1A	200v	£0.48	840C1500	1.5A	100v	£0.53	K005	25A	50v	£2.20
VM48	1A	400v	£0.50	840C3200	3.2A	100v	£1.20	K01	25A	100v	£2.37
SO05	2A	50v	£0.39	880C1500	1.5A	200v	£0.82	K02	25A	200v	£2.75
SO1	2A	100v	£0.44	880C3200	3.2A	200v	£1.25	K04	25A	400v	£3.40
BY179			£0.90	PW005	6A	50v	£0.90	K06	25A	600v	£3.99

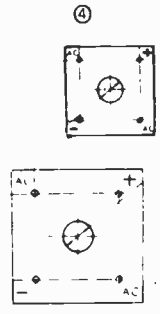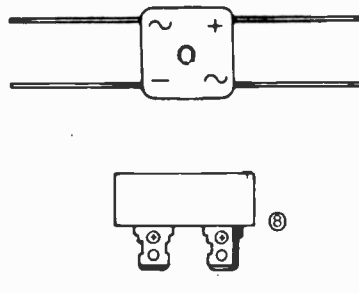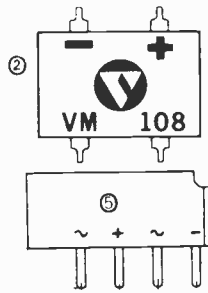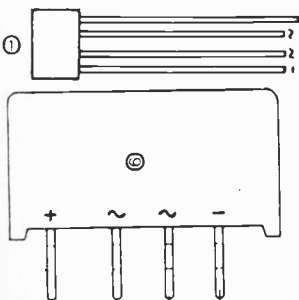


THYRISTORS

TYPE	RATING	CASE	PRICE
*TIC44†	0.6A 30v	TO18	£0.35
*TIC46†	0.6A 100v	TO18	£0.50
*TIC47†	0.6A 200v	TO18	£0.73
*2N5060	0.5A 25v	TO18	£0.32
*2N5061	0.5A 50v	TO18	£0.33
*2N5062	0.5A 100v	TO18	£0.40
*2N5063	0.5A 150v	TO18	£0.43
*2N5064	0.5A 200v	TO18	£0.45



*BstB0126	1.2A 400v	Plastic	£0.74
*BstB0140	1.2A 600v	Plastic	£1.05
*BstB0146	1.2A 700v	Plastic	£1.37
BstB0206	4.7A 100v	M478	£0.72
BstB0213	4.7A 200v	Plastic	£0.82
BstB0226	4.7A 400v	Plastic	£0.92
BstB0240	4.7A 600v	Plastic	£1.25
BstB0246	4.7A 700v	Plastic	£1.48
BT106		Stud Mounting	£1.10

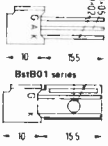


POWER THYRISTORS

C106A†	4A	100v	Plastic	£0.38
C106B†	4A	200v	Plastic	£0.44
C106C†	4A	300v	Plastic	£0.48
C106D†	4A	400v	Plastic	£0.54
C116A	8A	100v	Plastic	£0.47
C116B	8A	200v	Plastic	£0.54
C116C	8A	300v	Plastic	£0.61
C116D	8A	400v	Plastic	£0.68
C116M	8A	600v	Plastic	£0.80
C126A	12A	100v	Plastic	£0.63
C126B	12A	200v	Plastic	£0.70
C126C	12A	300v	Plastic	£0.80
C126D	12A	400v	Plastic	£0.90
C126M	12A	600v	Plastic	£1.07


PLASTIC POWER

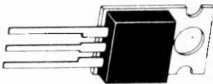PLASTIC TO66 FROM TEXAS INST. QUALITY AND RELIABILITY




LOW COST HIGH STANDARDS

THIS PORTION OF LEADS FREE OF FLASH

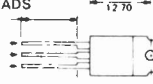

MECHANICAL INTERCHANGEABILITY OF THE PLASTIC PACKAGE WITH TO66 OUTLINE




TRIACS-DIACS QUADRACS

TYPE	DIAC	Mullard	PRICE
ST2	DIAC		£0.22
BR100	DIAC	Mullard	£0.55

TRIACS


SC35D	3A	400v	Stud Mounting	£1.55
TC4/40	4A	400v	Press Fitting	£1.48
SC40D	6A	400v	Stud Mounting	£1.56
SC45D	10A	400v	Stud Mounting	£2.09
BTW37-600	12A	600v	TO64	£3.63
BTW37-1	12A	1000v	TO64	£4.75
BT123	14A	500v	TO127	£2.75
BTX94-200	25A	200v	TO48	£6.90
BTX94-400	25A	400v	TO48	£9.50
BTX94-600	25A	600v	TO48	£12.50
40512			Quadrac	£1.70




POWER TRIACS AT UNBEATABLE PRICES FROM TEXAS INSTRUMENTS

TIC206D	Plastic TO66	400v 4A	£0.72
TIC225D	Plastic TO66	400v 6A	£0.77
TIC226D	Plastic TO66	400v 8A	£0.82
TIC236D	Plastic TO66	400v 12A	£0.93
TIC246D	Plastic TO66	400v 16A	£1.21
TIC253D	Plastic TO3	400v 20A	£1.87
TIC263D	Plastic TO3	400v 25A	£2.20


PLASTIC TO66

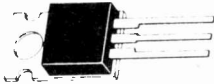

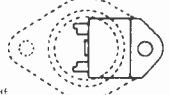
MECHANICAL INTERCHANGEABILITY OF PLASTIC PACKAGE WITH TO66 OUTLINE




PLASTIC TO3



MECHANICAL INTERCHANGEABILITY OF THE PLASTIC PACKAGE WITH TO66 OUTLINE



THIS PORTION OF LEADS FREE OF FLASH

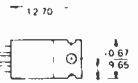


VOLTAGE REGULATORS

TYPE	DESCRIPTION	PRICE
LM309KC	1A 5v Reg Pos TO3	£1.95
LM317MP	500mA variable TO202	£1.35
LM317T	1.5A variable TO220	£2.20
LM317K	1.5A variable TO3	£3.35
LM320T-5	1A 5v-ve TO220	£2.15
LM320T-12	1A 12v-ve TO220	£2.15
LM320T-15	1A 15v-ve TO220	£2.15
LM320T-24	1A 24v-ve TO220	£2.15
LM320MP-5	0.5A 5v-ve TO202	£1.15
LM320MP-12	0.5A 12v-ve TO202	£1.15
LM320MP-15	0.5A 15v-ve TO202	£1.15
LM320MP-24	0.5A 24v-ve TO202	£1.15
LM323K	3A 5v+ve TO3	£6.95
LM337T	1.5A negative variable	£2.99
LM350K	3A version LM317K	£6.45
LM340T-5	1A 5v+ve TO220	£0.88
LM340T-12	1A 12v+ve TO220	£0.88
LM340T-15	1A 15v+ve TO220	£0.88
LM340T-24	1A 24v+ve TO220	£0.88
LM341P-5	5A 5v+ve TO202	£0.80
LM341P-12	5A 12v+ve TO202	£0.80
LM341P-15	5A 15v+ve TO202	£0.80
LM341P-24	5A 24v+ve TO202	£0.80
LM78L05CH	100mA 5v+ve TO5	£0.85
LM78L12CH	100mA 12v+ve TO5	£0.85
LM78L15CH	100mA 15v+ve TO5	£0.85
LM78L24CH	100mA 24v+ve TO5	£0.85
LM7805KC	1A 5v+ve TO3	£1.75
LM7812KC	1A 12v+ve TO3	£1.75
LM7815KC	1A 15v+ve TO3	£1.75
LM7824KC	1A 24v+ve TO3	£1.75
LM78L05CZ	100mA 5v+ve TO92	£0.30
LM78L12CZ	100mA 12v+ve TO92	£0.30
LM78L15CZ	100mA 15v+ve TO92	£0.30
LM78L24CZ	100mA 24v+ve TO92	£0.30


National

VOLTAGE REGULATOR SELECTOR GUIDE

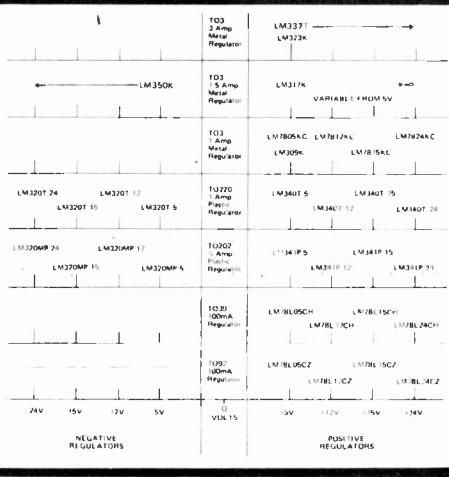


A SELECTED RANGE FROM NATIONAL SEMICONDUCTORS MAKERS OF QUALITY COMPONENTS

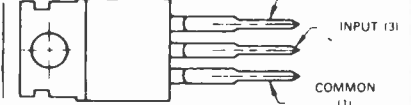In cases of supply difficulty, we reserve the right to supply an equivalent device from another manufacturer at our own discretion.




TO220/202 NEGATIVE REGS ONLY

THE SELECTOR GUIDE INDICATES THE RANGE OF REGULATORS NORMALLY KEPT IN STOCK, AND LISTS THEM IN ORDER OF THEIR RATINGS FOR QUICK REFERENCE



BOTTOM VIEW
TO-5 Metal Can Package (H)

VIEWED FROM ABOVE

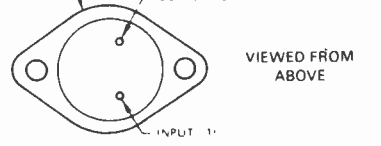

TO220/202 POSITIVE REGS ONLY

N.B. THESE PIN CONNECTIONS DO NOT APPLY TO THE ADJUSTABLE REGS LM317, 337, 350 REFER TO VOLTAGE REGULATOR HANDBOOK AVAILABLE SEE P.18

INTEGRATED CIRCUITS

AV-3-8500 AV-3-8710	B/W TV Games Chip G.I. Tank Battle 2-Game	\$3.50 \$3.30	CD4095	Gated J-K Flip-Flop	\$1.30	LM7812KC	Positive 3 Terminal 12 Volt. Reg. 1A TO3	\$1.75
CA3000	Temp. Comp. Diff. Amp. DC to 30MHz	\$3.30	CD4096	Gated D Flip-Flop	\$1.30	LM7815KC	Positive 3 Terminal 15 Volt. Reg. 1A TO3	\$1.75
CA3001	Temp. Comp. Diff. Amp. LOZ out DC to 30MHz	\$3.25	CD4097	Dual 8-1 Multiplexer	\$1.60	LM7818CZ	Positive 3 Terminal 24 Volt. Reg. 1A TO3	\$1.75
CA3002	Temp. Comp. Diff. Amp.	\$3.30	CD4098	8 Bit Addressable Latch	\$1.20	LM78L05CZ	Positive 3 Terminal 5 Volt. Reg. 100mA TO92	\$0.30
CA3005	RF Amplifier	\$2.50	CD4510B	Prestable Up/Down Counter (BCD)	\$1.60	LM78L15CZ	Positive 3 Terminal 15 Volt. Reg. 100mA TO92	\$0.30
CA3006	RF Amplifier	\$4.00	CD4511	Decade Counter/Driver 7 Segment	\$1.75	LM78L24CZ	Positive 3 Terminal 24 Volt. Reg. 100mA TO92	\$0.30
CA3007	Aud. Driver for Class B C/P	\$4.18	CD4516	Prestable Binary Up/Down Counter	\$2.10	MC667P	DTL Delay Line - Variable	\$2.75
CA3008	Wide Band Op. Amp., Univ. GN, at 50MHz	\$2.85	CD4518B	Dual BCD Up Counters	\$1.20	MC671P	Triple 3-Input NAND/NOR Gate - ACTIVE Output	\$1.25
CA3012	5 Lig. Amp. 100KHz to 20MHz	\$2.95	CD4520B	Dual Binary Up Counters	\$1.20	MC672P	Quad 3-Input NAND/NOR Gate - ACTIVE Output	\$1.75
CA3013	If Lig. Amp. with Discrim. 100KHz to 20MHz	\$1.85	DM131Z	Hex. Comparator	\$2.70	MC724P	Quad 2-Input NOR Gate	\$2.10
CA3014	If Lig. Amp. with Discrim. 100KHz to 20MHz	\$2.20	DM8281	Prestable Binary Counter	\$1.85	MC789P	Hex. Inverter	\$1.80
*CA3018	Transistor Array	\$0.75	DM8288	Prestable Divide by Twelve Counter	\$1.85	MC790P	Dual J-K Flip-Flop	\$3.10
*CA3018A	Transistor Array	\$1.10	DM8300	4-Bit Parallel-In-Out Shift Register	\$1.85	MC798P	Dual 2-Input Buffer	\$2.20
*CA3020	Wide Band Pwr. Amp. 8MHz/0.5W	\$2.20	DM8601	Reintegrable Monostable Multivibrator	\$1.75	MC799P	Dual Buffer	\$2.20
*CA3020A	Wide Band Pwr. Amp. 8MHz/1.0W	\$2.40	DM9601	Reintegrable Monostable Multivibrator	\$1.75	MC832P	Dual 4-Input NAND/NOR Buffer	\$0.70
*CA3021	Lo. Pwr. Video 4MW/2MHz 8W	\$2.40	DM9097	Dual J-K Flip-Flop Common Clock (2x)	\$0.87	MC835P	Dual 4-Input Expander	\$0.70
*CA3022	Lo. Pwr. Video 12.5MW/7.5MHz 8W	\$2.20	DM9099	Dual J-K Flip-Flop Common Clock (6x)	\$0.87	MC836P	Hex. Inverter	\$0.82
*CA3023	Lo. Pwr. Video 35MW/16MHz 8W	\$2.20	FH101	8-Input NAND Gate without CRC	\$2.75	MC837P	Hex. Inverter with Fast Rise Time	\$0.82
*CA3026	Dual Differential Amplifier	\$0.80	FJL151	BCD-Decimal Decoder	\$1.85	MC838P	Synchronous 4 Bit Decade Counter	\$1.85
CA3028A	Diff/Cascade Amp. DC to 120MHz	\$0.90	FJ101	Dual 4-Input Expander	\$1.85	MC840P	Hex. Inverter without Input Diodes	\$1.65
CA3028B	Premium Diff/Cascade Amp. DC to 120MHz	\$1.25	FJH111	TV. Volt. 4In NAND	\$2.75	MC844P	Dual 4-Input NAND/NOR Power Gate	\$0.70
CA3029	Wide Band Op. Amp. FT at 60MHz	\$0.75	JO0511	5-Unit Signal Reg. TO3 SGS	\$2.25	MC846P	Quad 2-Input NAND/NOR Gate	\$0.70
CA3029A	5 V. Trans. Arr. DC Op. Amp. FT at 60MHz	\$2.40	LM1	High Gain Amplifier TO3 Case	\$2.75	MC848P	Flip-Flop with Set and Clear	\$1.25
CA3030	Wide Band Op. Amp. FT at 60MHz	\$1.50	*LM301AN	Improved Operational Amplifier TO99	\$0.50	MC849P	Quad 2-Input NAND/NOR - Fast Rise Time	\$0.70
CA3030A	Premium Wide Band Op. Amp. FT at 60MHz	\$2.20	*LM301-B	Improved Operational Amp. 8 Pin D.I.L.	\$0.30	MC857P	Quad 2-Input NAND Buffer Gate	\$0.85
CA3033	High Pwr. O/P Op. Amp. 1.2W	\$3.70	LM304	Negative Voltage Regulator	\$2.50	MC861P	Dual 4-Input NAND/NOR Fast Rise Time	\$0.85
CA3034	Phase Detector	\$2.75	LM307N	General Purpose Compensated Op. Amp.	\$0.60	MC1035P	Triple Line Receiver	\$1.90
CA3035	Ultra. Hi. Gain 3 Amp. ARR. 129DB at 40KHz	\$1.95	*LM308H	Super Gain Op. Amp. TO5 Multi-Lead	\$0.20	*MC1327P	Dual Chroma Demodulator	\$1.70
*CA3036	Dual Darlington Array	\$1.21	*LM308N	Super Gain Op. Amp. 8 Pin D.I.L.	\$1.95	MC1330P	3rd I/O Video Detector	\$1.10
CA3037	Operational Amplifier	\$1.65	LM309KC	5 Volt. Regulator TO3 Case	\$2.35	*MC1357P	Dual Vid. IF Amp.	\$1.25
*CA3038A	Operational Amplifier	\$4.10	LM317K	Also available in other cases. See p.13	\$3.35	*MC1433G	Operational Amp. Non-Comp.	\$3.65
CA3039	Diode Array	\$0.77	LM318N	High Speed Reg. Op. Amp.	\$2.45	*MC1435G	Operational Amp. Non-Comp.	\$2.20
CA3040	Wide Band Amp. DC to 200MHz	\$3.75	LM320T-5	1.00 Amp. Negative 5 Volt. Reg. TO220	\$2.15	*MC1439G	Power Booster/Drivers	\$1.75
*CA3041	TV Sound Section/Driver - Tubes	\$1.65	LM320T-12	1.00 Amp. Negative 12 Volt. Reg. TO220	\$2.15	MC1440G	Operational Amplifier	\$1.65
*CA3042	TV Sound Section Drv. Trans.	\$1.85	LM320T-15	1.00 Amp. Negative 15 Volt. Reg. TO220	\$2.15	*MC1456G	Op. Amp. Internally Compensated	\$2.75
*CA3043	FM Receiver System to 20MHz	\$2.20	LM320T-24	1.00 Amp. Negative 24 Volt. Reg. TO220	\$2.15	MC1463R	Reg. Voltage Reg. 1/4 to 40V	\$3.90
*CA3045	5 V. Trans. Arr. DC Op. Amp. FT at 60MHz	\$2.40	LM320MP-5	0.5 Amp. Negative 5 Volt. Reg. TO202	\$1.15	MC1468R	Dual 1.5V. Tractor 24 Hr. or 6 Digits	\$3.80
*CA3046	T Transistor Array Inpt	\$0.77	LM320MP-12	0.5 Amp. Negative 12 Volt. Reg. TO202	\$1.15	MC1469R	Positive Voltage Reg. 1/4 to 2.5V. 37V	\$3.10
CA3047	Medium Pwr. Op. Amp. 0.75W	\$2.20	LM320MP-15	0.5 Amp. Negative 15 Volt. Reg. TO202	\$1.15	MC1488L	Quad Line Driver	\$4.25
CA3047A	Premium Medium Pwr. Op. Amp. 0.75W	\$3.70	LM320MP-24	0.5 Amp. Negative 24 Volt. Reg. TO202	\$1.15	*MC1495L	Linear Four-Quadrant Multiplier Chip	\$6.50
*CA3048	Quad-Low Noise Amp. NF 0.60B	\$2.45	LM323K	5 Volt. 3 Pin. Amp. Regulator	\$6.95	*MC1529G	Diff. Video Amplifier	\$7.10
CA3049	Dual Differential Amp.	\$1.98	LM324	Quad Op Amp	\$0.60	MC4024P	Dual Voltage Controlled Multivibrator	\$2.20
CA3050	Dual Differential Amp.	\$2.86	LM339N	Quad Comparator	\$0.75	*MC14000AE	See CD4000 Series CMOS	
CA3051	Dual Differential Amp.	\$1.65	LM340T-5	Positive 3 Terminal 5 Volt. Reg. 1A TO220	\$0.85	MM5314	MC1468R	\$4.60
*CA3052	Quad-And-Inverting 300KHz BW	\$1.78	LM340T-12	Positive 3 Terminal 12 Volt. Reg. 1A TO220	\$0.85	MM5316	Digital Clock IC as a Bus and Alarm (40 Pin)	\$4.60
CA3053	Diff/Cascade Amp.	\$0.77	LM340T-15	Positive 3 Terminal 15 Volt. Reg. 1A TO220	\$0.85	MM5330N	4 1/2 Digit Digital Voltmeter Chip	\$4.20
CA3054	Dual Differential Amp.	\$1.10	LM340T-24	Positive 3 Terminal 24 Volt. Reg. 1A TO220	\$0.85	NE555	Precision Timer	\$0.33
CA3059	Zero Voltage Trigger S.C.R., Triac	\$2.10	LM341P-5	Positive 3 Terminal 5 Volt. Reg. 5A TO202	\$0.80	NE556	Dual Precision Timer	\$0.85
CA3062	Photo Det. and Pwr. Amp. 100MA O/P	\$3.75	LM341P-15	Positive 3 Terminal 15 Volt. Reg. 5A TO202	\$0.80	NE558N	Quad Timer	\$1.98
*CA3064	AF System. Gen. Purpose and TV	\$1.10	LM341P-15	Positive 3 Terminal 15 Volt. Reg. 5A TO202	\$0.80	NE600	Phase Locked Loop	\$4.50
*CA3065	AF Amp. Det. DC Volt. Cont.	\$1.10	LM341P-24	Positive 3 Terminal 24 Volt. Reg. 5A TO202	\$0.80	NE611	Phase Locked Loop	\$4.50
*CA3068	TV Video IF System	\$3.80	LM348N	Quad 741 Operational Amplifier	\$0.95	NE582	Phase Locked Loop	\$4.50
*CA3070	TV Chroma Sig. Proc	\$1.90	LM358N	Low Power Dual Operational Amplifier	\$0.60	NE585	Phase Locked Loop	\$1.39
*CA3071	TV Chroma Amp.	\$1.90	LM360N	High Speed Comparator	\$3.00	NE586	Voltage Controlled Oscillator	\$1.75
*CA3072	TV Chroma Demod.	\$1.90	*LM370N	AGC/Squelch Amplifier 14 Pin	\$3.00	NE567	Tone Decoder Phase Locked Loop	\$1.90
*CA3075	FM-IF Amp/Limited Det.	\$1.70	*LM371H	Integrated RF/IF Amplifier	\$2.35	NE571N	Comparator	\$4.95
*CA3076	Hi-Gain IF Amp/Limiter	\$2.12	*LM350K	3 Amp. Version LM317. See p.13	\$6.45	SAS560	Switching Amp. for 4 Ch. Touch Switch	\$2.70
CA3080	Op. Transconductance Amp.	\$1.65	*LM373N	AMP/SSB Strip (14 Pin)	\$3.35	SAS565	Switching Amp. for 4 Ch. Touch Switch	\$2.70
CA3080A	Op. Transconductance Amp.	\$2.10	*LM374N	AM/FM/SSB IF Video Amp.	\$3.35	*SAS580	Touch tuner amplifier	\$2.40
*CA3086	Transistor Array (N-P-N)	\$0.80	*LM377N	Dual 2W Power Amp.	\$1.80	SAS590	Touch tuner amplifier	\$2.40
*CA3088F	AM Receiver Sub. Sys. Network	\$1.87	*LM378N	Dual 4W Audio Amp.	\$2.40	SN7400N	Quad 2 Input NAND	\$0.17
*CA3089E	FM-IF System	\$2.90	*LM379S	Dual 6W Audio Amp.	\$2.45	SN7401N	Quad 2 Input NAND O/C	\$0.17
*CA3090Q	FM stereo Multiplex Decoder	\$4.40	*LM380N-8	0.6 Watt Audio Amplifier 8 Pin D.I.L.	\$0.70	SN7402N	Quad 2 Input NOR	\$0.17
CA3130	FET Operational Amplifier	\$1.06	*LM380N-14	2 Watt Audio Power Amp. 14 Pin D.I.L.	\$2.90	SN7403N	Quad 2 Input NAND O/C	\$0.17
CA3141	FET Operational Amplifier	\$1.04	*LM381AN	Low Noise Audio Pre-Amp. D.I.L. Package	\$1.08	SN7404N	Hex. Inverter	\$0.17
CD4000	Quad 2-Input NOR gate plus Inverter	\$0.22	*LM381N	Low Noise Dual Pre-Amp.	\$1.69	SN7405N	Hex. Inverter O/C	\$0.22
CD4001B	Quad 2-Input NOR Gate	\$0.22	*LM382N	Low Noise Dual Pre-Amp.	\$1.32	SN7406N	Hex. Inverter/Buffer 30V. O/P	\$0.55
CD4002	Dual 4-Input NOR Gate	\$0.22	*LM384N	5 Watt Audio Amp.	\$1.55	SN7407N	Hex. Buffer 30V. O/P	\$0.55
CD4006	10-Stage Static Shift Register	\$1.25	*LM386N	Low Voltage Audio Amp.	\$0.88	SN7408N	Quad 2 Input and Gate	\$0.22
CD4007	Dual Complementary Pair Plus Inverter	\$0.22	*LM387N	Low Noise Dual Pre-Amp.	\$1.10	SN7409N	Quad 2 Input and Gate	\$0.22
CD4008B	4-Bit Full Adder with Parallel Carry	\$0.89	*LM388N	1.5 Watt Audio Amp.	\$0.80	SN7410N	Triple 3 Input NAND	\$0.26
CD4009	4-Bit Parallel Inverter	\$0.88	*LM389N	Low Volt. Aud. pwr. amp. with NPN tran array	\$0.90	SN7411N	Triple 3 Input NAND	\$0.22
CD4010	Hex. Buffer/Converter (Non-Inverting)	\$0.88	*LM555CN	See NE555 timer	\$0.33	SN7412N	Triple 3 Input NAND O/Circuit	\$0.20
CD4011B	Quad 2-Input NAND Gate	\$0.22	*LM555CN	See NE555	\$1.39	SN7413N	Quad 4 Input NAND Schmitt	\$0.36
CD4012	Dual 4-Input NAND Gate	\$0.22	*LM701B	Operational Amplifier TO99	\$2.99	SN7414N	Hex. Schmitt Trigger	\$0.60
CD4013B	Dual "D" Flip-Flop with Set/Reset	\$0.52	*LM701C	Operational Amplifier TC99	\$2.99	SN7416N	Hex. Inverter/Buffer 15V O/C	\$0.36
CD4014	8-Stage Static Shift Register	\$1.00	*LM702C	Wide Band D.C. Amp. Commercial TO99	\$0.81	SN7417N	Hex. Buffer 15V O/C	\$0.36
CD4015	Dual 4-Stage Static Shift Register	\$1.05	*LM703LN	1/2 Limiting Amplifier	\$1.15	SN7420N	Dual 4-Input NAND	\$0.36
CD4016	10-Stage Static Shift Register	\$0.52	*LM709	Operational Amplifier TO5 Multi-Lead	\$0.70	SN7422N	Expandable Dual 4 Input NOR Gate	\$0.32
CD4017B	Decade Counter/Divider	\$1.05	*LM709-B	Operational Amplifier 8 Pin D.I.L.	\$0.50	SN7425N	Dual 4 Input NOR-Strobe	\$0.32
CD4018B	Prestable Divide-By "N" Counter	\$1.05	*LM709-14	Operational Amplifier 14 Pin D.I.L.	\$0.49	SN7427N	Triple 3 Input NOR	\$0.32
CD4019B	Quad AND/OR Select Gate	\$0.82	LM710	Differential Comparator TO5	\$0.67	SN7430N	8 Input NAND	\$0.22
CD4020B	14-Stage Binary Ripple Counter	\$1.15	LM710-10	Differential Comparator 14 Pin D.I.L.	\$0.64	SN7432N	Quad 2 Input OR	\$0.30
CD4021	8-Stage Static Shift Register	\$1.05	*LM711CN	Differential Comparator - Dual 14 D.I.L.	\$0.72	SN7437N	Quad 2 Input NAND Buffer	\$0.38
CD4022B	Divide-by-8 Counter/Divider	\$0.77	LM723C	Precision Voltage Reg. TO5	\$0.78	SN7438N	Quad 2 Input NAND Buffer O/C	\$0.30
CD4023B	Triple 2-Input NAND Gate	\$0.22	*LM723C-14	Operational Voltage Reg. 14 Pin D.I.L.	\$0.45	SN7440N	Quad 4-Input NAND Buffer	\$0.22
CD4024B	7-Stage Binary Counter	\$0.76	*LM726	Temp. Controlled Diff. Pair TO99	\$5.80	SN7441AN	BCD to Decimal Decoder/Driver	\$0.84
CD4025B	Triple 3-Input NOR Gate	\$0.22	*LM741C	Compensated Op. Amp. TO5	\$0.70	SN7442N	BCD-Decimal Decoder	\$0.78
CD4027B	Dual J-K Master Slave Flip-Flop	\$0.85	*LM741C-8	Compensated Op. Amp. 8 D.I.L.	\$0.30	SN7445N	BCD-Decimal Decoder 30V O/C	\$1.40
CD4028B	BCD-TO-Decimal Decoder	\$0.92	*LM741C-14	Compensated Op. Amp. 14 D.I.L.	\$0.30	SN7446AN	BCD-Seven Segment Decoder 30V	\$0.90
CD4029B	Prestable Up/Down Counter	\$1.10	*LM747CN	14 Pin D.I.L. Dual Comp. Op. Amp	\$0.95	SN7447AN	BCD-Seven Segment Decoder/Driver	\$0.80
CD4030	Quad Exclusive-OR Gate	\$0.88	*LM748-B	Operational Amp. 8 Pin D.I.L.	\$0.50	SN7448N	BCD to 7 Segment Decoder/Driver	\$0.80
CD4031B	64-Stage Static Shift Register	\$2.25	*LM748-14	Operational Amp. 14 D.I.L.	\$0.50	SN7450N	Dual 2-Wide-2-Input A/O/Inv	\$0.22
CD4035B	4-Stage Parallel IN/OUT Shift Register	\$1.30	LM716	Nonlinear Semiconductor I/C Op. Amp.	\$1.00	SN7451N	Dual 2-Wide-2-Input A/O/Inv	\$0.22
CD4037	Triple AND/OR Bi-Phase Pairs	\$0.80	LM900	Buffer	\$0.50	SN7453N	4-wide A/O/1	\$0.22
CD4041B	Quad True/Complement Buffer	\$0.86	LM911	4-Input or NOR Gate	\$0.50	SN7454N	4-wide A/O/1	\$0.22
CD4042B	Quad Clocked "D" Latch	\$0.86	LM921	Dual 2-Input Gate Expander	\$0.50	SN7460N	Dual 4-Input Expander	\$0.22
CD4043	Quad 3-State NOR R/S Latch	\$1.08	LM923	J-K Flip-Flop	\$0.50	SN7470N	J-K Flip-Flop Edge Trig and Gate	\$0.45
CD4044	Quad 3-State NAND R/S Latch	\$1.15	*LM1303N	3-F.M. Multiplexer Stereo Demodulator	\$1.52	SN7472N	J-K Flip-Flop and Gated M.S. FF P/S/CL	\$0.30
CD4045	21-Stage Counter	\$1.75	*LM1304N	F.M. Multiplexer Stereo Demodulator	\$1.52	SN7473N	Dual J-K Flip-Flop	\$0.44
CD4046B	Micropower Phase-Locked Loop	\$1.50	*LM1305N	F.M. Multiplexer Stereo Demodulator	\$1.52	SN7474N	Dual D-Type Flip-Flop	\$0.32
CD4047B	Monostable/Instable Multivibrator	\$0.95	*LM1307N	F.M. Multiplexer Stereo Demodulator	\$1.22	SN7475N	Quad Latch	\$0.60
CD4049	Hex. Buf./Con. (Invig.)	\$0.55	*LM1310N	F.M. Multiplexer Stereo Demodulator	\$2.10	SN7476N	Dual J-K Flip-Flop	\$0.45
CD4050B	Hex. Buf./Con. Non-Inverting	\$0.85	*LM1351N	F.M. Detector Limiter and Audio Pre-Amp.	\$1.30	SN7480N	Gated Full Adder	\$0.60
CD4051B	Single 8-Channel Multiplexer	\$0.85	*LM1458N	Dual Comp. Op. Amp. (0-70°) 8 Pin D.I.L.	\$0.45	SN7481N	16 Bit Memory	\$1.00
CD4052B	Dual 4-Channel Multiplexer	\$0.85	*LM1496D	Balanced Diff/Demodulator (0-70°)	\$0.97	SN7482N	2 Bit Binary Full Adder	\$0.80
CD4053B	Triple 2-Channel Multiplexer	\$0.85	*LM1800N	PLL Demodulator	\$1.94	SN748		

INTEGRATED CIRCUITS

SN74153N	Dual 4-to-1-Line Selector	£0.76
SN74154N	4-16 Line Decoder	£1.20
SN74155N	Dual 2 and 4 Demultiplexer	£0.70
SN74157N	Quad 2 Input Data Selector	£0.78
SN74160AN	Synchronous Decade Counter	£1.10
SN74161AN	Synchronous Binary Counter	£1.10
SN74162AN	Synchronous Decade Counter	£1.10
SN74163AN	Synchronous Binary Counter	£1.10
SN74164AN	8 Bit Shift Register S/PD	£1.35
SN74165N	8 Bit Shift Register P/SO	£1.35
SN74167N	Synchronous Decade Decimal Rate Multiplier	£2.50
SN74174N	Hex D-Type Flip-Flop Quad	£1.00
SN74175N	Quad D-Type Flip-Flop Hex	£1.00
SN74176N	Decade Counter	£0.90
SN74177N	Binary Counter	£0.90
SN74180N	8 Bit Parity Generator	£1.00
SN74181N	4 Bit Arithmetic Logic Unit	£2.00
SN74182N	Carry Look Ahead	£0.80
SN74184N	BCD to Binary Converter	£1.50
SN74185AN	BCD to Binary Converter	£1.50
SN74188AN	256 Bit Field Prog Rom	£3.26
SN74189N	TR1 State 64 Bit Ram (DM8599)	£2.80
SN74190N	Synch. Decade Up/Down Counter	£1.20
SN74191N	Synchronous Binary Up/Down Counter	£1.20
SN74192N	Reversible Decade Counter	£1.20
SN74193N	Reversible Binary Counter	£1.20
SN74196N	Decade Counter	£1.20
SN74197N	Binary Counter	£1.00
SN74198N	Parallel In and Out 8 Bit Shift Reg.	£2.00
SN74199N	Parallel In and Out 8 Bit Shift Reg.	£2.00
SAJ110	Frequency divider for electronic organs	£2.10
SO41P	FM IF amplifier & demodulator	£1.35
SO42P	Mixer to 200MHz	£1.35
SN74H00N	High Speed TTL	£0.55
SN74H01N	High Speed TTL	£0.60
SN74H04N	High Speed TTL	£0.60
SN74H10N	High Speed TTL	£0.55
SN74H11N	High Speed TTL	£0.65
SN74H20N	High Speed TTL	£0.55
SN74H21N	High Speed TTL	£0.65
SN74H30N	High Speed TTL	£0.55
SN75H40N	High Speed TTL	£0.55
SN74H51N	High Speed TTL	£0.55
SN74H53N	High Speed TTL	£0.55
SN74H54N	High Speed TTL	£0.55
SN74H55N	High Speed TTL	£0.65
SN74H60N	High Speed TTL	£0.55
SN74H62N	High Speed TTL	£0.55
SN74S00	Schottky TTL	£0.77
SN74S03	Schottky TTL	£0.77
SN74S04	Schottky TTL	£0.77
SN74S10	Schottky TTL	£0.77
SN74S20	Schottky TTL	£0.77
SN74S40	Schottky TTL	£0.77
SN74S64	Schottky TTL	£0.77
SN74S65	Schottky TTL	£0.77
SN74S112	Schottky TTL	£1.70
SN74S114	Schottky TTL	£1.70
SN74S140	Schottky TTL	£1.30
SN74S262	Schottky TTL	£12.50
SN74L00	Low Power TTL	£0.55
SN74L02	Low Power TTL	£0.55
SN74L04	Low Power TTL	£0.60
SN74L07	Low Power TTL	£0.90
SN74L74	Low Power TTL	£3.50
SN74L85	Low Power TTL	£2.75
SN74L93	Low Power TTL	£0.70
SN75451BP	Dual Peripheral Drivers	£0.70
SN75452BP	Dual Peripheral Drivers	£0.70

74CMOS - 74LS See Page 19

*SN76001N	1 Watt Power Amplifier	£1.30
*SN76003N	Audio Amp & HT Sink 4W 35V 15R	£2.38
*SN76008KE	10 Watt Audio Amp 5 Pin	£1.60
*SN76013N	Audio Amp and HT Sink 4W, 24V 8R	£1.50
*SN76012ND	As above, no HT Sink	£1.30
*SN76013ND	10 Watt Audio Amp, 5 Pin	£1.60
*SN76023N	Audio Amp, and HT Sink 4W, 24V, 8R	£1.50
*SN76023ND	As above, without HT Sink	£1.30
*SN76033N	Audio Amp and HT Sink	£2.35
*SN76110N	Stereo Demodulator	£1.30
*SN76115N	Stereo Demodulator	£1.65
*SN76116M	Stereo Decoder (Radiogram)	£1.80
*SN76131N	Dual Preamplifier	£1.30
*SN76226N	Colour (PAL) Decoder	£1.68
*SN76227N	Colour (PAL) Decoder	£1.30
*SN76228N	Colour (PAL) Decoder	£1.55
*SN76530N	Video IF	£0.82
*SN76532N	Line Frame Processor (Spares Only)	£1.55
*SN76533N	Line Frame Processor (Spares Only)	£1.30
*SN76544N	Line Frame Processor	£1.60
*SN76545N	Line Frame Processor	£1.80
*SN76546N	Line Frame Processor	£1.58
*SN76550-2	Tuner Control Voltage Stabiliser	£0.38
*SN76552-2	Tuner Control Voltage Stabiliser	£0.57
*SN76570N	Video IF	£1.80
*SN76620AN	Sound IF	£0.99
*SN76650N	Video IF	£1.20
*SN76660N	Sound IF	£0.66
*SN76666N	Sound IF	£0.99

*SL610C	RF Amplifier	£2.75
*SL611C	RF Amplifier	£2.75
*SL612C	IF Amplifier	£2.75
*SL620C	Vogel	£3.85
*SL621C	AGC Generator	£3.75
*SL623C	AM Det. & AGC Amp. + SSB Demod	£6.25
*SL630C	AF Amplifier	£2.50
*SL640C	Double Balanced Modulator	£4.40
*SL641C	Receiver Mixer	£4.40
*SL701C	Operational Amplifier	£2.50
*TAA263	100mW.A.F. Amp 8V	£1.35
*TAA300	1WAF Amplifier 4.5 - 9V	£3.70
*TAA320A	MOS IF Preamplifier	£1.15
*TAA350A	Wide Band Differential Amp	£3.00
*TAA521	Operational Amplifier	£1.10
*TAA522	Operational Amplifier	£2.10
*TAA550	Voltage Stabiliser 31-35V	£0.48
*TAA560	Level Control Amplifier	£2.10
*TAA570	4 Stage Limiter Amp FM Detector	£2.20
TAA370A	Hearing aid amplifier	£6.45
TAA630	Synchronous demodulator (PAL)	£2.40
TAA960	Triple amp for active filters	£3.90
TAA970	Microphone amp TO74	£4.20
*TAA611B	3 Watt Audio Amplifier	£2.50
*TAA621	4 Watt 24V Audio Amplifier	£2.50
*TAA661A	Limiting IF Amp/FM Detector	£1.65
*TAA661B	Limiting IF Amps FM Detector	£1.45
*TAA700	TV Signal Processing Circuit	£4.50
*TAA930A	IF Amp-Limiter FM Demod	£1.45
*TAA930B	IF Amp-Limiter FM Demod	£1.45

*TAD100	Pre-amp. Stages of AM Receiver	£2.00
	Filter for FM Reception - Filter Price	£0.90
*TBA120	Limiting IF Amp/FM Detector	£0.80
*TBA400	Adjustable Broadband Amplifier	£2.20
*TBA500	Colour Processing-TV Luminance Combination	£2.24
*TBA500Q	Quad-In-Line Version of above	£2.35
*TBA510	Colour Processing - Chrominance Comb	£2.48
*TBA510Q	Quad-in-Line Version of above	£2.48
*TBA520	Colour Modulation Circuit	£2.60
*TBA520Q	Q1.1 Version of above	£2.70
*TBA530	R G B. Matrix Preamplifier	£2.35
*TBA530Q	Q1.1 Version of above	£2.45
*TBA540	Reference Oscillator Circuit	£2.60
*TBA540Q	Q1.1. Version of above	£2.70
*TBA550	Signal Processing - TV Receivers	£3.80
*TBA550Q	Q1.1. Version of above	£3.80
*TBA560CQ	Luminance & Chromo Control	£3.00
*TBA570	AM/FM Radio Receiver Circuit 6V	£2.10
*TBA570Q	Q1.1. Version of above	£2.20
*TBA841B	Audio Power Amp 4.5W (1Kv-4R)	£3.00
*TBA851	Tuner and Matrix Amplifier	£2.50
*TBA700Q	AM/FM Radio Receiver 1W Output	£2.20

*TBA720AQ	Line Oscillator combination for TV	£2.06
*TBA750	Limiter Amp. & FM Det. D.C. Vol. Control and Preamp	£2.35
*TBA750Q	Q1.1. Version of above	£2.45
*TBA810S	5 Watt Audio Amp 24V 16R	£1.30
*TBA810T	7 Watt Audio Amp 16V 4R	£1.30
*TBA820	2 Watt Audio Amp 12V 8R	£0.80
*TBA920	Line Oscillator Combination (Mullard)	£2.99
*TBA920Q	Line Oscillator Combination (Mullard)	£3.09
*TBA990Q	I.C. Colour Demodulator for TV	£2.75
*TCA160C	Audio Amp. 2 Watt battery op 5 16V and Ht. Sink	£2.66
*TCA160B	Audio Amp. 2 Watt Battery Op. 5-16V D.I.L.	£2.55
*TCA270	Synchronous Demodulator & Processing	£2.99
*TCA280A	Trigger I.C. for Thyristors & Tracs	£2.42
*TCA290A	Stereo Decoder for F.M. 15V Supply	£2.84
*TCA420A	10.7MHz Limiter I.F. Amp for F.M. Receipt	£2.60
*TCA730	D.C. Stereo Audio Vol & Balance Circuit	£4.50
*TCA740	D.C. Stereo Audio tone Control Circuit	£4.50
*TCA750	Multi-Stabilizer for Elec. Tuning	£3.00
*TCA760	Audio Amp Battery Op. 4-14V 1 Watt 16DIL	£2.00
*TCA800	I.C. Colour Oemod. with Feed Back Clamps for TV	£3.75

TCA105	Threshold switch	£1.49
TCA440	AM receiver circuit	£1.65
TCA640	Chroma amp for Pal/Secam receivers	£4.40
TCA650	Chroma demodulator Pal/Secam receivers	£4.40
TCA660	Contrast saturation control receivers	£4.40
TCA980	Microphone amp (TO12)	£3.19
TDA1022	Bucket Brigade delay line	£7.50
TDA1024	Trac control I.C.	£1.24
TDA1034	High performance op amp	£4.75
TDA2540	VID IF amp & detector	£3.84
TDA1002	I.C. Tape Recorder Circuit Preamp & Record	£2.10
TDA2020AD	20 Watt Audio Power Amp	£4.50
*TDA1003	I.C. Tape Recorder Motor Regulator Bias Erase and Phase	£2.30
*TDA1004	Sho	£3.33
*TDA1005	Phase locked loop Stereo Decoder F.M.	£3.58
*TDA2610	4 7 Watt Sound Output Circuit for TV Rec.	£3.10
*TDA2640	Switched Mode Power Supply Control Circuit	£2.70
UAA170	I.C. for Driving Led Display Line (Up to 16)	£2.15
UAA180	I.C. for Driving Led Display Line	£2.15

BIFET OP-AMPS

TEXAS		
TL080CP	JFET Op-Amp Equiv to 301, 748	£1.25
TL081CP	JFET Op-Amp Equiv to 741, 3140	£0.60
TL082CP	Dual JFET Amp Equiv to 1458	£1.10
TL083CN	Dual JFET Amp Equiv to 747	£1.40
TL084CN	Quad JFET Amp Equiv to 324	£1.45
Texas JFETs are pin compatible to popular Op-Amps and offer dramatic improvements in I/O characteristics, slew rates and noise spec.		
NATIONAL		
LF355N	Low power JFET Op-Amp	£0.80
LF356N	Gen purpose JFET Op-Amp	£0.80
LF357N	High speed JFET Op-Amp	£0.80
LF13201N	Quad SPST JFET analog switch - closed	£3.00
LF13331N	Quad SPST JFET analog switch normal open	£3.00
LF13741H	FET Input 741 8 Pin DIL	£0.80
LF13741N	FET Input 741 14 Pin DIL	£0.55

TRY THEM! - YOU'LL BE AMAZED!
QUANTITY PRICES AVAILABLE

NATIONAL COLOUR TV GAMES KIT

Four Chip Set SK1122 - six games, full sound and full colour - all the super features you would expect from National - as featured in T.V. magazines. Now priced at - £18.75 inc. VAT. MM57105 TV GAME

ELEKTOR PROJECT BOARDS

We can supply board and back issues:-


PROJECT	BOARD	£	ISSUE
LM317K	Variable Power Supply	9456	£1.65 22
AY-8500	TV Games PCB. B/W	77084	£2.05 27
UHF	Modulator PCB Kit	9864	£1.35 32
5 Volt	TTL Power Supply	92188	7

We stock all components to build these projects. Back issues are only available when ordered with boards priced at 50p/copy. Prices above are for PCB's only.

AUDIO ICS



RADIO & TV SPARES

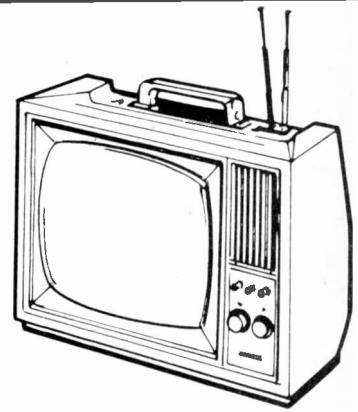

A full range of IC's for the designer, serviceman, hobbyist or experimenter. Top quality semiconductors.

QUANTITY DISCOUNTS

CONSUMER CIRCUITS

- NATIONAL
 - TEXAS INSTR.
 - MULLARD
 - SIEMENS
 - SESCOSEM
 - RCA, SGS
 - MOTOROLA
 - SIGNETICS
 - PLESSEY
- DATA
AVAILABLE ON MOST DEVICES
SEND 30p + S.A.E.
(30p per data sheet)

MAIL ORDER

LONDON 01-452 0161
BRISTOL 0272 654301
GLASGOW 041-332 4133

£10 MINIMUM ORDER FOR TELEPHONED CREDIT CARD No.

Texas Instruments manufacture a wide range of MOS and Bipolar memory devices to complement the leadership T.T.L. products. Listed below, you will see the complete range of memory products with a cross reference list of the major 2nd sources and our highly competitive 100 up pricing. If you have not already – try Texas Instruments and get ex-stock delivery of high quality memory products from Marshalls.

Mos Memories

INTEL	TEXAS ORDER CODE	£	£
		1-99	100+
	TMS4027NL	6.10	3.81
2101-1	TMS4033NL	2.04	1.27
2102-2	TMS4034NL	1.94	1.22
2102	TMS4035NL	1.88	1.17
—	TMS4036	3.11	1.94
2101	TMS4039NL	3.37	2.11
2101-2	TMS4039-1NL	3.63	2.27
2101-1	TMS4039-2NL	4.20	2.62
2111	TMS4042NL	3.37	2.11
2111-2	TMS4042-1NL	3.63	2.27
2111-1	TMS4042-2NL	4.20	2.62
2112	TMS4043NL	3.37	2.11
2112-2	TMS4043-1NL	3.63	2.27
2112-1	TMS4043-2NL	4.20	2.62
—	TMS4044NL-45	15.88	9.92
2114	TMS4045NL-45	15.88	9.92
2107A/B	TMS4060NL	7.69	4.81
2107A/B	TMS4060-1NL	8.47	5.29
2107A/B	TMS4060-2NL	9.31	5.82
5270* NS	TMS4050NL	7.43	4.30
5270* NS	TMS4050-1NL	7.58	4.74
5270* NS	TMS4050-2NL	8.35	5.22
2116*	TMS4116JL	36.55	22.84

Bipolar Memories


NSC (DM)	INTEL (—) OR HARRIS	ORDER CODE T.I.	£	£
			1-99	100+
8577	7602	SN74S188N	2.70	1.67
8578	7603	SN74S288N	2.70	1.67
—	NPROM 512	SN74186N	10.71	6.70
8574	3621	SN74S287N	4.32	2.70
8573	3601	SN74S387N	4.32	2.70
74S470	—	SN74S470N	8.53	5.33
74S471	—	SN74S471N	8.53	5.33
74S472	—	SN74S472N	13.48	8.42
74S473	—	SN74S473N	13.48	8.42
87S296	3624	SN74S474N	13.48	8.42
87S295	3604	SN74S475N	13.48	8.42
FSC (—)				
93403	3101A	SN74S189N	1.81	1.13
93404	—	SN74S289N	1.81	1.13
93411	3106	SN74S201N	3.71	2.32
93410	3107	SN74S301N	3.71	2.32
93411	3106A	SN74S200AN	5.06	3.16
93410A	3107A	SN74S300N	5.06	3.16
—	*27LS01	SN74LS200AN	5.89	3.48
—	*27LS00	SN74LS300N	5.89	3.48

Static Random-Access Memories

DEVICE	ORGANIZATION	MAX. ACCESS/ MIN. CYCLE	TYPICAL POWER DISS.	PACKAGE	
				TYPE	PINS
TMS 2101 /4039	256 × 4	1000 ns	175 mW	CDIP/Plas	22
TMS 2101-2/4039-1	256 × 4	650 ns	175 mW	CDIP/Plas	22
TMS 2101-1/4039-2	256 × 4	450 ns	175 mW	CDIP/Plas	22
TMS 2102-1/4033	1024 × 1	450 ns	225 mW	CDIP/Plas	16
TMS 2102-2/4034	1024 × 1	650 ns	225 mW	CDIP/Plas	16
TMS 2102 /4035	1024 × 1	1000 ns	225 mW	CDIP/Plas	16
TMS 2111 /4042	256 × 4	1000 ns	175 mW	CDIP/Plas	18
TMS 2111-2/4042-1	256 × 4	650 ns	175 mW	CDIP/Plas	18
TMS 2111-1/4042-2	256 × 4	450 ns	175 mW	CDIP/Plas	18
TMS 2112 /4043	256 × 4	1000 ns	175 mW	CDIP/Plas	16
TMS 2112-2/4043-1	256 × 4	650 ns	175 mW	CDIP/Plas	16
TMS 4043-2	256 × 4	450 ns	175 mW	CDIP/Plas	16
TMS 4036	64 × 8	1000 ns	250 mW	Plas	20
TMS 4036-1	64 × 8	650 ns	250 mW	Plas	20
TMS 4036-2	64 × 8	450 ns	250 mW	Plas	20
TMS 4044	4096 × 1	200 ns	450 mW	CDIP/Plas	18
TMS 4045	1024 × 4	200 ns	450 mW	CDIP/Plas	18


MARSHALL'S – THE LEADING CONSUMER DISTRIBUTOR FOR TEXAS

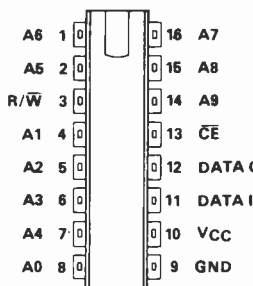16-PIN CERAMIC AND PLASTIC DUAL-IN-LINE PACKAGES (TOP VIEW)




TMS 4033/34/35

20-PIN CERAMIC AND PLASTIC DUAL-IN-LINE PACKAGES (TOP VIEW)

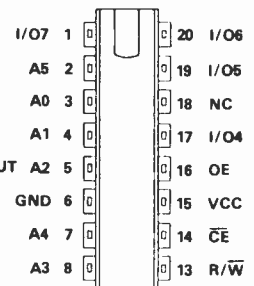


TMS 4036

22-PIN CERAMIC AND PLASTIC DUAL-IN-LINE PACKAGES (TOP VIEW)

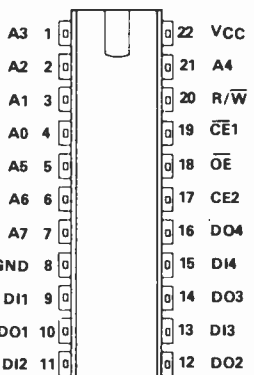


TMS 4039

18-PIN CERAMIC AND PLASTIC DUAL-IN-LINE PACKAGES (TOP VIEW)

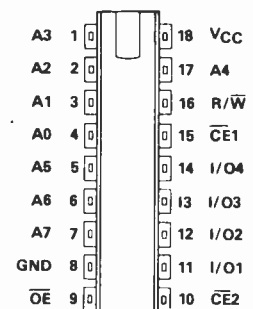


TMS 4042

16-PIN CERAMIC AND PLASTIC DUAL-IN-LINE PACKAGES (TOP VIEW)

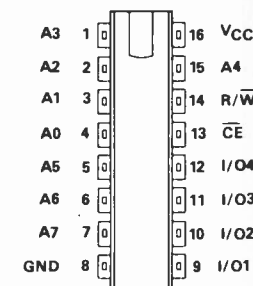


TMS 4043

18-PIN CERAMIC AND PLASTIC DUAL-IN-LINE PACKAGES (TOP VIEW)

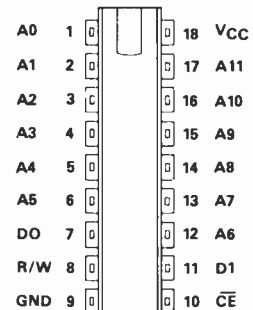

TMS 4044

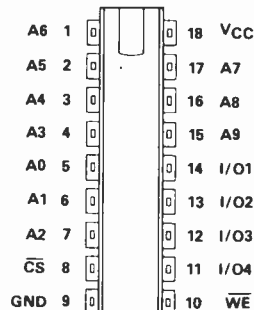18-PIN CERAMIC AND PLASTIC DUAL-IN-LINE PACKAGES (TOP VIEW)



TMS 4045/2114

TI Static RAM's feature:


- Reliability, same process as TI's industry standard 4K RAM's
- Economy, high volume production techniques and choice of plastic or ceramic packaging
- Extremely low standby power (typically 2-3 mW) due to TI's enhancement mode design
- Complete range of speeds for design optimization
- Easy to use 8-bit byte organization (64 x 8) along with industry-standard 256 x 4 and 1024 x 1 organizations

All TI Static RAM's are easy to use:


- No clocks — no refresh
- I/O fully TTL compatible
- 3-state output for OR-time capability
- Single +5V supply
- Simple, fully decoded addressing

Dynamic Random-Access Memories

DEVICE	ORGANIZATION	NO. CLOCKS	MAX ACCESS (ns)	MIN CYCLE (ns)	NOMINAL SUPPLY VOLTAGES				TYP. POWER DISS (mW)		PACKAGE	
					V _{CC}	V _{DD}	V _{SS}	V _{BB}	STANDBY	ACTIVE	TYPE	PINS
TMS 4050 JR, JL, NL	4096 x 1	1	300	470	N/A	12	0	-5	0.1	420	CDIP/Plas	18
TMS 4050-1 JR, JL, NL	4096 x 1	1	250	430	N/A	12	0	-5	0.1	420	CDIP/Plas	18
TMS 4050-2 JR, JL, NL	4096 x 1	1	200	400	N/A	12	0	-5	0.1	420	CDIP/Plas	18
TMS 4051 JL, NL	4096 x 1	1	300	470	N/A	12	0	-5	60	460	CDIP/Plas	18
TMS 4051-1 JL, NL	4096 x 1	1	250	430	N/A	12	0	-5	60	460	CDIP/Plas	18
TMS 4060 JR, JL, NL	4096 x 1	1	300	470	5	12	0	-5	0.2	400	CDIP/Plas	22
TMS 4060-1 JR, JL, NL	4096 x 1	1	250	430	5	12	0	-5	0.2	400	CDIP/Plas	22
TMS 4060-2 JR, JL, NL	4096 x 1	1	200	400	5	12	0	-5	0.2	400	CDIP/Plas	22
SMC 4050 JR	4099 x 1	1	(same as TMS 4050s)	N/A	12	0	-5	0.1	420	CDIP	18	
SMC 4060 JR	4096 x 1	1	(same as TMS 4060s)	5	12	0	-5	0.2	400	CDIP	22	
TMS 4116 JL	16384 x 1	2	350	500	5	12	0	-5	10	600	CDIP	16
TMS 4027 NL	4096 x 1	1	250	430	N/A	12	0	-5	0.1	420	CDIP	16

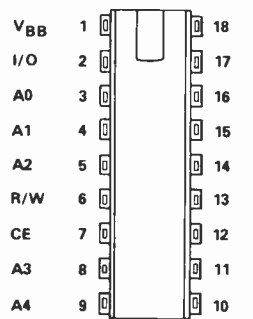


TMS 4050/51

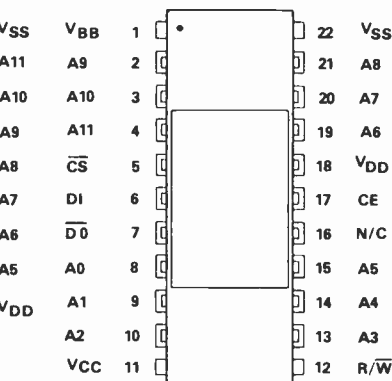

TMS 4060/30

16-PIN CERAMIC DUAL-IN-LINE PACKAGE (TOP VIEW)

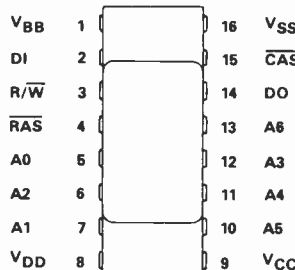

TMS 4070

T.I. DYNAMIC RAM FEATURES

- Low cost per bit storage
- Low power on stand by combined with high performance
- Fully TTL compatible I/Os
- Standard N channel Silicon gate process

READ ONLY MEMORIES

8 BIT ERASABLE-PROGRAMMABLE READ ONLY MEMORIES

MM1702AQ.....	256x8	EPROM	£8.10
MM5204Q.....	512x8	EPROM	£11.00
MM2708Q.....	1024x8	EPROM	£13.00
TMS2716.....	2048x8	EPROM	£40.00


- 1024 x 8 Organization
- All Inputs and Outputs Fully TTL-Compatible
- Static Operation (No Clocks, No Refresh)
- Maximum Access Time . . . 450 ns
- Minimum Cycle Time . . . 450 ns
- 3-State Outputs for OR-Ties
- N-Channel Silicon-Gate Technology
- 8-Bit Output for Use in Microprocessor Based Systems

UV ERASABLE PROMS

1024-WORD BY 8-BIT ERASABLE PROGRAMMABLE READ-ONLY MEMORIES


- MM2708 Features
 - Power Diss. 800 mW(max)
 - 5% Power Supply Tolerance
 - T.T.L. Compatible I/Os
 - 2 standard TTL loads drive capability

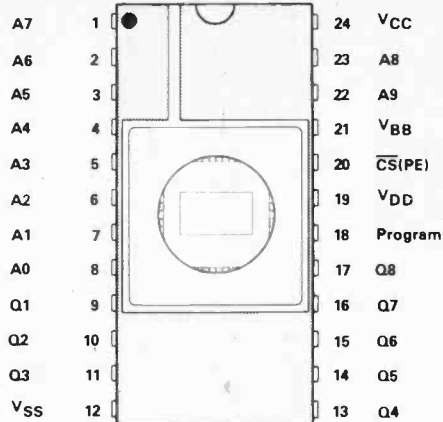24-PIN CERAMIC DUAL-IN-LINE PACKAGE (TOP VIEW)



SC/MP POWER SUPPLY

POWER SUPPLY FOR SC/MP INTROKIT

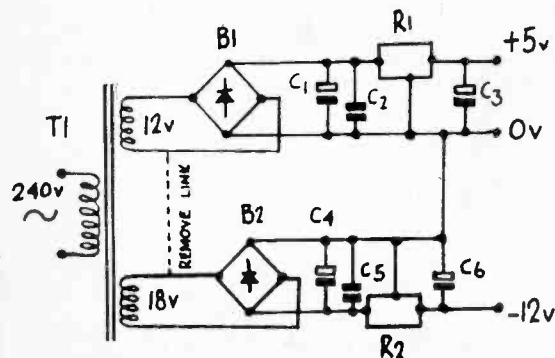

Note: Disconnect common secondary winding

Parts list:	C1 1000µF 25v B41010
TI MT 79AT	C2 0.22µF B37449
R1 LM309K	C3 2.2µF TANT B45134
R2 LM 320-12	C4 220µF 40v B41283
B1, B2 W005	C5 0.22µF B37449
	C6 2.2µF TANT B45134



First-choice for linear and digital circuits

National, currently the second-largest manufacturer of integrated circuits in the world, can offer an unparalleled range of products in all semiconductor technologies. Many are made in the UK.

NATIONAL DATA PUBLICATIONS

SC/MP	Programming and assembler manual	£3.00
SC/MP	Technical description	£2.40
SC/MP	Applications manual	£3.00
National	Linear IC data book	£3.00
National	TTL data book	£2.50
National	Interface data book	£2.50
National	Special function data book	£2.00
National	CMOS data book	£2.50
National	Memory data book	£2.50
National	Audio handbook	£2.00
National	Voltage regulator handbook	£1.25
National	Data acquisition handbook	£2.00
National	F.E.T. handbook	£1.50
National	MOS/LSI data book	£2.75

TEXAS DATA BOOKS

Texas/	TTL data book (hardback)	£5.75
Texas	Memory and microprocessor data book	£4.75

PRICES ARE EXCLUSIVE OF POST/PACKING 50p PER BOOK

That's why it pays to
BE NATIONAL
in semiconductors.



National Semiconductor (UK) Ltd.
19 Goldington Road
Bedford
Tel. 0234-211262
Telex 826209

74LS SERIES TTL

— LOW POWER SCHOTTKY —

TYPE	1 + £	100 + £
DM74LS00N	0.26	0.16
DM74LS01N	0.26	0.16
DM74LS02N	0.26	0.16
DM74LS03N	0.26	0.16
DM74LS04N	0.29	0.18
DM74LS05N	0.29	0.18
DM74LS08N	0.26	0.16
DM74LS09N	0.26	0.16
DM74LS10N	0.26	0.16
DM74LS11N	0.27	0.16
DM74LS12N	0.26	0.16
DM74LS13N	0.58	0.39
DM74LS14N	1.43	1.05
DM74LS15N	0.26	0.16
DM74LS20N	0.26	0.16
DM74LS21N	0.27	0.16
DM74LS22N	0.26	0.16
DM74LS26N	0.39	0.21
DM74LS27N	0.50	0.38
DM74LS28N	0.42	0.32
DM74LS30N	0.26	0.16
DM74LS32N	0.27	0.23
DM74LS33N	0.35	0.27
DM74LS37N	0.32	0.23
DM74LS38N	0.32	0.23
DM74LS40N	0.29	0.16
DM74LS42N	1.07	0.43
DM74LS47N	1.09	0.80
DM74LS48N	1.09	0.80
DM74LS49N	1.09	0.80
DM74LS51N	0.26	0.16
DM74LS54N	0.26	0.16
DM74LS55N	0.26	0.16
DM74LS73N	0.42	0.25
DM74LS74N	0.42	0.28
DM74LS75N	0.58	0.38
DM74LS76N	0.42	0.25
DM74LS78N	0.42	0.25
DM74LS83AN	1.20	0.64
DM74LS85N	1.10	0.73
DM74LS86N	0.44	0.28
DM74LS90N	1.10	0.80
DM74LS91N	1.20	0.86
DM74LS92N	0.86	0.63
DM74LS93N	1.10	0.80
DM74LS95AN	1.10	0.80
DM74LS96N	1.35	1.00
DM74LS107N	0.42	0.29
DM74LS109N	0.42	0.29
DM74LS112N	0.42	0.39
DM74LS113N	0.42	0.29
DM74LS114N	0.42	0.29
DM74LS122N	0.80	0.62
DM74LS123N	0.83	0.65
DM74LS124N	2.70	2.15
DM74LS125N	0.50	0.36
DM74LS126N	0.50	0.36
DM74LS132N	0.85	0.56
DM74LS136N	0.44	0.33
DM74LS138N	0.65	0.43

TYPE	1 + £	100 + £
DM74LS139N	0.65	0.43
DM74LS145N	1.30	0.99
DM74LS151N	1.07	1.00
DM74LS153N	0.58	0.39
DM74LS154N	1.45	0.98
DM74LS155N	1.20	0.71
DM74LS156N	1.20	0.71
DM74LS157N	0.60	0.39
DM74LS158N	0.65	0.43
DM74LS160N	1.43	1.02
DM74LS161N	0.85	0.56
DM74LS162N	1.43	1.02
DM74LS163N	0.85	0.56
DM74LS164N	1.43	0.98
DM74LS168N	2.43	1.68
DM74LS169N	2.43	1.68
DM74LS170N	2.20	1.47
DM74LS173N	1.30	0.87
DM74LS174N	1.33	0.98
DM74LS175N	1.26	0.91
DM74LS181N	3.95	3.00
DM74LS189N	3.74	2.34
DM74LS190N	1.00	0.66
DM74LS191N	1.00	0.66
DM74LS192N	1.98	1.54
DM74LS193N	1.98	1.54
DM74LS196N	1.28	1.00
DM74LS197N	1.28	1.00
DM74LS221N	1.20	0.92
DM74LS247N	1.09	0.80
DM74LS248N	1.09	0.80
DM74LS249N	1.09	0.80
DM74LS251N	1.00	0.75
DM74LS253N	1.20	0.87
DM74LS257N	1.26	0.91
DM74LS258N	1.26	0.91
DM74LS261N	3.25	2.45
DM74LS266N	0.44	0.32
DM74LS279N	0.58	0.41
DM74LS283N	1.20	0.82
DM74LS289N	3.74	2.34
DM74LS290N	1.00	0.75
DM74LS293N	1.00	0.75
DM74LS295N	1.35	1.02
DM74LS298N	1.75	1.40
DM74LS352N	1.07	0.80
DM74LS353N	1.20	0.87
DM74LS365N	0.55	0.41
DM74LS366N	0.55	0.41
DM74LS367N	0.55	0.41
DM74LS368N	0.55	0.41
DM74LS386N	0.44	0.31
DM74LS670N	2.45	1.66
DM81LS95N	1.36	0.94
DM81LS96N	1.36	0.94
DM81LS97N	1.36	0.94
DM81LS98N	1.36	0.94
DM86LS52N	2.60	1.90

74C SERIES CMOS

TYPE	1 + £	100 + £
MM74C00N	0.24	0.175
MM74C02N	0.24	0.175
MM74C04N	0.24	0.175
MM74C08N	0.24	0.175
MM74C10N	0.24	0.175
MM74C14N	1.41	1.00
MM74C20N	0.24	0.175
MM74C30N	0.24	0.175
MM74C32N	0.24	0.175
MM74C42N	0.92	0.70
MM74C48N	1.38	1.00
MM74C73N	0.54	0.50
MM74C74N	0.56	0.43
MM74C76N	0.54	0.50
MM74C83N	1.30	0.96
MM74C85N	1.30	0.96
MM74C86N	0.64	0.49
MM74C89N	4.39	3.35
MM74C90N	0.85	0.61
MM74C93N	0.85	0.61
MM74C95N	1.04	0.78
MM74C107N	1.22	0.88
MM74C150N	4.14	2.98
MM74C151N	2.47	1.80
MM74C154N	3.68	2.67
MM74C157N	2.21	1.60
MM74C160N	1.11	0.82
MM74C161N	1.11	0.82
MM74C162N	1.11	0.82
MM74C163N	1.11	0.82
MM74C164N	1.04	0.78
MM74C165N	1.04	0.78
MM74C173N	0.90	0.82
MM74C174N	0.90	0.82
MM74C175N	0.90	0.82
MM74C192N	1.11	0.82
MM74C193N	1.11	0.82
MM74C195N	1.04	0.78
MM74C200N	6.70	4.99
MM74C221N	1.36	1.05
MM74C901N	0.54	0.50
MM74C902N	0.54	0.50
MM74C903N	0.54	0.50
MM74C904N	0.54	0.50
MM74C905N	7.28	5.25
MM74C906N	0.54	0.50
MM74C907N	0.54	0.50
MM74C908N	0.96	0.71
MM74C909N	1.63	1.18
MM74C910N	6.79	4.88
MM74C914N	1.41	1.01
MM74C915N	1.11	0.82
MM74C918N	2.72	1.85
MM74C920D	11.83	8.65
MM74C921D	11.83	8.65
MM74C922N	3.90	2.70
MM74C923N	3.74	2.83
MM74C925N	5.36	3.87
MM74C926N	5.36	3.87
MM74C927N	5.36	3.87
MM74C928N	5.36	3.87
MM74C929D	11.83	8.65
MM74C930D	11.83	8.65
MM74C935N	12.60	9.85
MM74C935N-1	10.20	7.00
MM80C95N	0.54	0.50
MM80C96N	0.61	0.55
MM80C97N	0.54	0.50
MM80C98N	0.61	0.55
MM82C19N	4.14	2.85
MM88C29N	1.93	1.40
MM88C30N	1.93	1.40

THE ADVANTAGES OF LS OVERALL

With the new reduced cost, low power Schottky is becoming the leading logic family - eliminates the need for large power supplies + no loss of speed over standard TTL.

Family Type	Delay Per Gate	Average Power Per Gate
74LS series	10 nano seconds	2 milliwatts
74 series	10 nano seconds	10 milliwatts
74S series	3 nano seconds	20 milliwatts
74H series	6 nano seconds	23 milliwatts
74L series	33 nano seconds	1 milliwatt

TV-CRT CONTROLLER — SF.F 96364 £17.20

GENERAL DESCRIPTION

A 1024 six bit word size (at least) static or dynamic memory and a character generator (7 x 5) used with the SF.F 96364 allows to change any TV set into a visual display for computing system.

This processor performs text refreshment, characters writing and cursor management on TV screen.

Line erasing, line end erasing and other special functions capabilities make it strictly compatible with any computing system (computer or microprocessor).

An internal top generator, CCIR compatible, ensures control of any TV set.

The SF.F 96364 is manufactured in MOS N channel silicon gate technology.

PRINCIPAL FEATURES

- Single power supply +5 V
- TTL-LS compatible
- 250 mW typical power
- 1,6 MHz typical clock freq.
- Dual in line 28 pins pack
- 16 lines 64 characters disp.
- Text shifts up when index reaches the end of a page
- Pages linking capability
- Variable display size
- Character flickering
- Brilliancy increasement
- Automatic line erase
- Automatic end of line erasing
- Read cursor address
- Read refresh memory
- Flickering cursor (2 Hz)
- Mobile in the 4 directions
- "Hard copy coupling"
- Static or dynamic memory
- Memory refresh
- Light pen capability

NEW FROM SESCOSEM SEND 30p FOR DATA NOW

INS 8080A

The National 8080 direct plug in replacement for Intel 8080A - 8 bit micro now at a fantastic price!

SEND 30p FOR DATA **£7.42**

INS 8900D

The latest addition to the family of National micro's - 16 bit system and equal in price to many 8 bits. Low power schottky compatible and capable of interfacing with all 8080A memory and peripheral chips.

SEND 30p FOR DATA **£15.00**

TMS 9900

The powerful and now famous TMS 9900 micro from Texas Instruments. 16 bit system - now available.

SEND 30p FOR DATA **£61.50**


SEE PAGE 6 Mc 6800P

Made famous by Motorola now 2nd sourced from Thomson CSF

£16.99

SC-MP

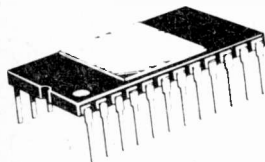Very popular 8 bit from National
SC-MP I **£12.96** SC-MP II **£10.80**



MICROPROCESSOR SUPPORT DEVICES

LISTED BELOW IS OUR COMPREHENSIVE RANGE OF MICRO SUPPORT DEVICES TOTAL SYSTEM SUPPORT

AT
COMPETITIVE PRICES



PART No.	DESCRIPTION	PRICE/EQUIV.
8080A	8 Bit CPU 2µs Cycle	£7.42
8060N	SC-MP II 8 Bit CPU (ISP 8A-600N)	£10.80
8900D	16 Bit CPU	£15.00
8224N	Clock Generator	£4.58
8228N	System Controller	£5.85
8238N	System Controller	£5.85
DIGITAL I/O		
8202	Tri State 8 Bit Bus Driver/Buffer	DM81LS95
8203	Tri State 8 Bit Bus Driver Inverting	DM81LS96
82LS05	1 out of 8 Binary Decoder	74LS138
82C06	8 Bit I/O Latch	£1.99
8208	8 Bit Bi-directional Bus Driver	£6.41
8212	8 Bit Input/Output Port	£3.10
8213	Bi-directional 8 Bit I/O Port	£15.00
8216	4 Bit Bi-directional Bus Driver	£2.60
8226	4 Bit Bi-directional Bus Inverting	£2.60

PERIPHERAL CONTROL CHIPS

8244	90-Key Keyboard Encoder	£7.23
8245	16-Key Keyboard Encoder	MM74C922
8246	20-Key Keyboard Encoder	MM74C923
8247	4 Digit Display Control	£7.50
8248	6 Digit Display Control	£7.50
8253	Programmable Interval Timer	£11.38
8254	Bit Programmable Peripheral Interface	£4.50
8255	Programmable Peripheral Interface	£6.27
8257	Programmable DMA Controller	£11.93
8259	Programmable Interrupt Controller	£11.37
8272	Floppy Disk Formatter/Control	£22.00
8276	CRT Controller	£12.95
8285	Character Generator	DM8678CABN
8292	8 Bit A/D Converter + 16CH ANA MUX	£20.00
8298	LLL 80BAA "Basic" Interp. + HEX DEBUG	£72.75

PART No.	DESCRIPTION	PRICE/EQUIV.
COMMUNICATIONS		
8250	Async. Communications Element (ACE)	£8.99
8251	Program. Communications Interface	£8.18
8252	Advanced Communications Interface	£17.80
8261	Program. Communications Subsystem	£15.75
8274	Multi-Protocol Communications	£13.90
Memory (See Page 16, 17 & 18)		
8154	128 x 8 Static Ram with 16-Bit I/O Ram I/O Chip ISP-8A/650D	£8.83
MM74C920	256 x 4 Stat Ram + Separate I/O CMOS	£11.83
MM74C921	256 x 4 CMOS Static Ram + Comm. I/O	£11.83
MM74C929	1024 x 1 CMOS Static Ram	£11.83
TEXAS THS9900		
TMS9900	16 Bit Microprocessor	£61.50
TMS9980NL	16 Bit Microprocessor	£29.89
TMS9901NL	Program. Interrupt and I/O Interface	£10.65
TMS9902NL	Async. Communications Controller	£9.15
TMS9903NL	Binary Synch Interface	TBA
TIM9904N	Four Phase Clock Driver	£7.56
TIM9905N	Data Selector/Multiplex	74LS251

CALCULATOR ORIENTED PROCESSOR SYSTEMS - COPS

MM57109N	Number Cruncher	£12.75
MM57160N	"Stac" Standard Timer and Controller	£10.25
MM57161N	"Sit" Standard Interval Timer	£10.25

EXTRAS

MM5307AA/N	Baud Rate Generator	£13.69
MM5303N	UART	£6.85
AY-3-1013	UART Replaced Pin for Pin BY	TMS6011NC
TMS6011NC	UART 5-8 Bit 200 kHz	£5.35
DMB678CABN	CRT Character Generator 5 x 7 UC	£15.40
AY-2513	CRT Character Generator 5 x 7 UC	£8.75

— THE "ONE-STOP" SHOP FOR ALL YOUR MICROPROCESSOR COMPONENTS —

NEW FROM MOTOROLA


MEK 6800 DII

A SELF-CONTAINED MICROCOMPUTER KIT

The kit, when assembled, is a fully functional microcomputer. The integral keyboard/display module can be used in conjunction with monitor program. For entering and debugging of user programs, a second P.I.A. allows operation via TTY or other input/outputs

FEATURES

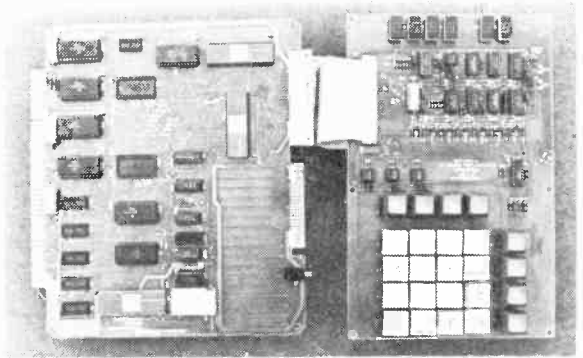- 72 basic instructions
- 7 addressing modes
- On board monitor program
- On board cassette interface — connecting direct to cassette mike and earphone socket
- Spare prewired sockets for additional ROM/RAM, etc.. + space for user's extra circuitry
- Expandable via data bus to 65k words using inbuilt motherboard techniques
- 256 words of RAM + monitor program
- Comprehensive literature / fact pack




A FULL RANGE OF SUPPORT DEVICES WILL BE AVAILABLE SHORTLY

PRICE £205 INCL. VAT DATA 30p + Sae

Now second sourced from Thomson-CSF
See page 6 for details of chips

SC/MP MICROPROCESSOR

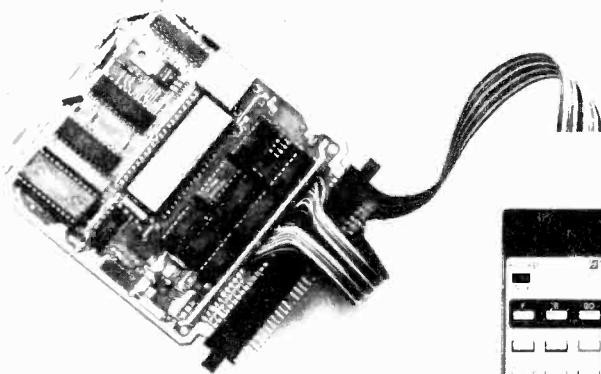

INTROKIT — NATIONAL

Price £71.63 INCL. VAT

SC/MP, the Microprocessor kit from National Semiconductor includes everything you need to build a completely functional microprocessor system — featuring the National SC/MP microprocessor — the low cost microprocessor for every application. Test Systems, Instrument Control, Machine Tool Control, Small Business Machines, Word Processing Systems, Educational Systems, Multiprocessors Systems, Process Controllers, Terminal Control, Laboratory Instrumentation, Sophisticated Games, Automotive Controller and Appliance Controllers.

The kit, neatly packaged with all the components and literature you need, in a looseleaf binder, includes The SC/MP Microprocessor — a single-chip Central Processing Unit in a 40-pin, dual in-line package. Features static operations, forty-six instruction types, single-byte and double-byte, software controlled interrupt structure, built in serial input/output ports, bidirectional 8-bit TRI-STATE bus, parallel data port and latched 12-bit TRI-STATE address port. ROM — 512 bytes (8-bits/byte) of pre-programmed Read-Only-memory containing KITBUG—a monitor and debugging program to assist in the development of your application programs. KITBUG provides teletypewriter input/output routines and allows examination, modification and controlled execution of your programs. RAM—256 bytes of static read/write memory for storage of your application programs. Transfers of data to and from RAM are controlled by SC/MP and KITBUG Teletypewriter Interface including buffer and drive capability for 20 MA current loop interface. Voltage Regulator. Data Buffer-providing interface between memory and bidirectional data lines. All the literature you need, including schematics and programming manuals. Timing Crystal—providing 1.000 MHz timing signal. Plus all the passive components and circuit board with 72 pin edge connector required to build and interconnect your microprocessor system with external hardware.

KEYBOARD KIT — National Semiconductors £68.74 INCL. VAT

Replaces the need for a conventional teletype terminal for input/output data. The calculator type keyboard provides manual input commands to the SC/MP and a six digit hex display provides visual output. An umbilical cord connects it to the Introkit P.C.B. Using the keyboard, programmes can be entered in hexadecimal (easier to use than binary). As well as the 16 hexadecimal keys (0-9, A, B, C, D, E and F) there are 4 control keys, which allow the contents of any RAM address to be examined or modified.

COMPLETE TEACH YOURSELF MICRO COURSE AVAILABLE ON TAPE. SEE BELOW
SC/MP MICROPROCESSOR FAMILY

- 1SP-8A/500D SC/MP CPU chip
- 1SP-8A/600N N-channel CPU chip (NEW N² INS 8060N)



£12.96
£10.80

ISP 8K-400

NEW DATA ACQUISITION CHIP

SINGLE CHIP 8-BIT DATA ACQUISITION SYSTEM

The ADC0816, ADC0817 (MM74C948) data acquisition components are monolithic CMOS devices with an 8-bit analog-to-digital converter, a 16-channel multiplexer and microprocessor compatible control logic. The 8-bit A/D converter uses successive approximation as the conversion technique. The converter features a high impedance chopper stabilized comparator, a 256R voltage divider with analog switch tree and a successive approximation register. The 16-channel multiplexer can directly access any one of 16 single-ended analog signals and provides the logic for additional channel expansion. Signal conditioning of any analog input signal is eased by direct access to the input of the 8-bit A/D converter.

The device eliminates the need for external zero and full-scale adjustments and features an absolute accuracy ≤ 1 LSB including quantizing error. Easy interfacing to microprocessors is provided by the latched and decoded address inputs and latched TTL TRI-STATE[®] outputs.

★ ADC0817CCN STOCKED. PRICE £18.92 INCL. VAT
DATA SHEET AVAILABLE PRICE 30p + SAE

SC/MP RETROFIT

★ KIT ★

£13.38

ISP 8K-205 Kit National

- Kit contains all the components including the CPU & Crystal etc. To convert existing SC/MP users over to the new N channel SC/MP complete with literature.

ELEKTOR SC/MP

"EXPERIMENTING WITH SC/MP"

ELEKTOR PROJECTS WORK!

A series of articles and constructional projects using SC/MP Micro to build into a hexadecimal — 7-segment Micro computer with cassette interface. (Video/TV interface + full keyboard — to come). Build as much or as little as your budget allows. All components available.

+ PCB + Back Issues etc. + 4k RAM CARD

★ SEND S.A.E. FOR FULL DETAILS ★

AUDIO VISUAL

CASSETTES PLUS BROCHURES

"TEACH YOURSELF"

"WHAT IS A MICROPROCESSOR?"

COMPLETE TEACH YOURSELF COURSE

The amazing response we experienced at our last two microprocessor forums in London — and the tremendous interest shown by individuals in microprocessor technology, has prompted us to release an edited recording of the lecture on cassette accompanied by a 72-page booklet keyed to the tapes — the forum was arranged by National Semiconductors. Practical Electronics and ourselves in an effort to remove the problems and uncertainties arising for anyone not familiar with this new and increasingly important subject. The lecture (on 1 x C90 and 1 x C60 cassettes) was given by two of National Semiconductors' leading microprocessor engineers.

£9.95 incl. VAT & P/P

RESISTORS

CARBON

FIXED

0.25 watt ± 5% Tol. Available in E12 range 10Ω to 1 meg	PRICE
0.5 watt ± 5% Tol. Available in E12 range 10Ω to 10 meg	2p each
1.0 watt ± 10% Tol. Available in E12 range 10Ω to 10 meg	3p each
2.0 watt ± 10% Tol. Available in E12 range 10Ω to 10 meg	5p each
	9p each

WIRE WOUND

2.5 watt ± 5% Tol. Available in the following values only	10p each
Ohms 1, 22, 33, 5, 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330.	

5 watt ± 5% Tol. Available in the following values only	12p each
5, 1, 2.2, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 25, 33, 39, 47, 60, 75, 82, 100, 120, 130, 150, 180, 220, 250, 270, 300, 330, 470, 500, 560, 680, 820, 1k, 1k2, 1k5, 2k, 2k2, 2k5, 3k3, 4k7, 5k6, 6k8, 7k5, 8k2, 10k, 12k.	


10 watt ± 5% Tol. Available in the following values only	14p each
1, 2.2, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 25, 33, 39, 47, 70, 82, 100, 120, 150, 200, 250, 330, 470, 560, 680, 750, 1k, 1k2, 1k5, 1k8, 2k, 2k2, 2k7, 3k, 3k5, 4k7, 5k, 5k6, 6k8, 10k, 15k, 18k, 20k, 25k.	

METAL OXIDE

MULLARD MR25 SERIES

0.5 watt ± 2% Tol. Available in E24 range 10Ω to 1 meg	4p each
--	----------------


RESISTOR COLOUR CODES

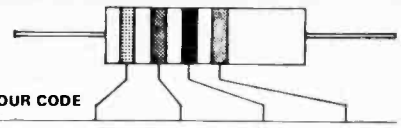

Color	1st Digit	2nd Digit	Multiplier	Tolerance
Black	—	0	1	—
Brown	1	1	10	1%
Red	2	2	100	2%
Orange	3	3	1000	—
Yellow	3	4	10000	—
Green	5	5	100000	—
Blue	6	6	1000.000	—
Violet	7	7	—	—
Grey	8	8	—	—
White	9	9	—	—
Gold	—	—	0.1	5%
Silver	—	—	0.01	10%

E24 series = 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91, 100 PLUS DECADES
E12 Series = 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100 PLUS DECADES


PRESET POTENTIOMETERS-TRIMMERS

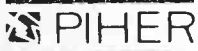

FOR THE PROFESSIONAL FINISH

PT10 SERIES (FULLY ENCLOSED) **13p**
PT10h (2.5) vertical mounting 0.15 watt at 40°C.
PT10V horizontal mounting 0.15 watt at 40°C.
Tol. 20%.
Price **13p** each. Please specify horizontal or vertical.

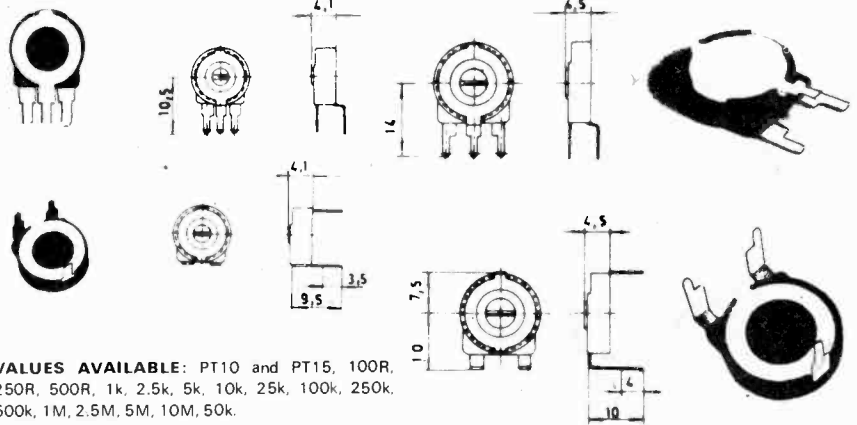PT15 SERIES (FULLY ENCLOSED) **15p**
PT15 Nh vertical mounting 0.3 watt at 40°C.
PT15 Nv horizontal mounting 0.3 watt at 40°C.
Tol. 20%.
Price **15p** each. Please specify horizontal or vertical.
The PT15 range has the extra facility of clip in thumb wheels or spindles for easy adjustment without a screwdriver.
Thumb wheels **5p** each
Spindles **5p** each



VALUES AVAILABLE: PT10 and PT15, 100R, 250R, 500R, 1k, 2.5k, 5k, 10k, 25k, 100k, 250k, 500k, 1M, 2.5M, 5M, 10M, 50k.


POTENTIOMETER-VOLUME CONTROLS

ROTARY POTENTIOMETERS. All standard 1/4" spindles

35p	1) SINGLE LESS SWITCH Long spindle, double wiper, available in following values	5k 25k 250k	10k 50k 500k	LIN or LOG
75p	2) SINGLE SWITCHED As above but with 2 Pole Switch 2 Amp 250V AC	5k 50k 500k	10k 100k 1Meg	LIN or LOG
95p	3) DUAL GANGED-STEREO As above, but dual <i>No Switch</i>	5k 50k 500k	10k 100k 1Meg	LIN or LOG

SLIDER POTENTIOMETERS

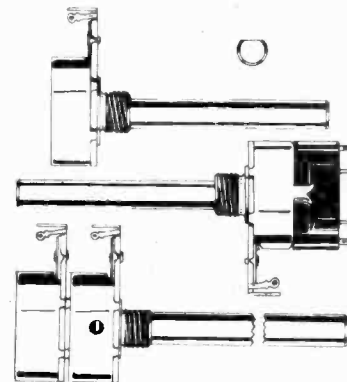- 1) SINGLE—LOG OR LINEAR in following values 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M. Price **55p** includes Knob.
- 2) DUAL GANGED-STEREO—LOG OR LINEAR, matched to 2dB. 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M. Price **95p** includes Knob.



NON LINEAR RESISTORS

Thermistors R at 25° C. Price

1) Rod type 0.6w Dissipation	VA10665	4.7k	£0.22
	VA10555	15k	£0.22
	VA10565	47k	£0.22
	VA10655	150k	£0.22
2) Disc Type 0.6w Dissipation	VA1096	150	£0.20
	VA1097	470	£0.20
	VA1098	1.5k	£0.20
	VA1109	4.7k	£0.24
	VA1108	15k	£0.24
	VA1112	22k	£0.24

3) Disc Types 1w Dissipation	VA1111	33k	£0.24
	VA1086	2.2	£0.18
	VA1033	4	£0.18
	VA1074	6	£0.18
	VA1053	8	£0.18
	VA1110	10	£0.18
	VA1100	15	£0.18
	VA1077	32	—
	VA1034	50	£0.18
	VA1040	130	£0.20
	VA1039	500	£0.22

VOLTAGE DEPENDENT

1) Rod Types	E298ED/A258	1500	£0.22
	E298ED/A260	1800	£0.22
	E298ED/A262	2200	£0.22
	E298ED/A265	2400	£0.22
	E298ED/P268	3000	£0.22
	E298ZZ/06	3020	£0.22
2) Disc Types	E299DD/P116	14	£0.20
	E299DD/P118	18	£0.20
	E299DD/P120	21	£0.20
	E299DD/P216	25	£0.20
	E299DD/P218	32	£0.20
	E299DD/P220	40	£0.20

E299DD/P224	57	£0.20
E299DD/P226	60	£0.20
E299DD/P228	70	£0.20
E299DD/P230	85	£0.20
E299DD/P232	100	£0.20
E299DD/P336	190	£0.20
E299DD/P338	230	£0.20
E299DD/P340	300	£0.20
E299DD/P342	350	£0.20
E299DD/P344	400	£0.20
E299DD/P346	500	£0.20
E299DD/P348	600	£0.20
E299DD/P350	750	£0.20
E299DD/P352	900	£0.20
E299DD/P354	1100	£0.20

TRANSFORMERS DOUGLAS AND REPANCO

12 7

TYPE No	SECONDARY VOLTAGES	CURRENT	WEIGHT	P/P	PRICE
MT111CS	0-12+0-12 (24 volt)	250mA	275g	60p	£2.50
MT213CT	0-12+0-12 (24 volt)	500mA	450g	60p	£3.15
MT71AT	0-12+0-12 (24 volt)	1 amp	825g	90p	£4.90
MT68AT	0-12+0-12 (24 volt)	1.5 amp	1.05kg	£1.00	£5.50
MT18AT	0-12+0-12 (24 volt)	2 amps	980g	90p	£6.00
MT85AT	0-12+0-12 (24 volt)	2.5 amps	1.3kg	£1.00	£6.50

MT111CT - MT85AT may have their secondaries parallel to give 0-12v at twice the secondary current ratings; i.e. MT71AT to give 0-12v at 2A or 0-24v at 1A.

TYPE No	SECONDARY VOLTAGES	CURRENT	WEIGHT	P/P	PRICE
MT112CT	0, 12, 15, 20, 24, 30v	500mA	575g	60p	£3.30
MT79AT	0, 12, 15, 20, 24, 30v	1 amp	725g	60p	£4.50
MT3AT	0, 12, 15, 20, 24, 30v	2 amp	1.35kg	£1.00	£6.20
MT20AT	0, 12, 15, 20, 24, 30v	3 amp	1.95kg	£1.00	£7.25
MT21AT	0, 12, 15, 20, 24, 30v	4 amp	2.73kg	£1.25	£8.70
MT51AT	0, 12, 15, 20, 24, 30v	5 amp	3.025kg	£1.50	£11.00

Secondary output of MT112CT to MT51AT may be taken from between any of the following voltages 2, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30v or 15-0-15v

TYPE No	SECONDARY VOLTAGES	CURRENT	WEIGHT	P/P	PRICE
MT102AT	0, 19, 25, 33, 40, 50v	500mA	800g	90p	£4.90
MT103AT	0, 19, 25, 33, 40, 50v	1A	1.3kg	£1.00	£5.50
MT104AT	0, 19, 25, 33, 40, 50v	2A	2.35kg	£1.25	£8.25
MT105AT	0, 19, 25, 33, 40, 50v	3A	2.9kg	£1.25	£9.90
MT107AT	0, 19, 25, 33, 40, 50v	4A	5.25kg	£2.00	£16.50

The secondary output of MT102AT to MT107AT may be taken from between any of the above tapings to give the voltages: 6, 7, 8, 10, 14, 15, 17, 19, 21, 25, 31, 33, 40, 50v or 25-0-25v.

TYPE No	SECONDARY VOLTAGES	CURRENT	WEIGHT	P/P	PRICE
MT124AT	0, 24, 30, 40, 48, 60v	500mA	700gm	60p	£4.90
MT126AT	0, 24, 30, 40, 48, 60v	1A	1.4 kgm	£1.00	£6.75
MT127AT	0, 24, 30, 40, 48, 60v	2A	2.4 kgm	£1.25	£8.80
MT123AT	0, 24, 30, 40, 48, 60v	4A	5.25 kgm	£2.00	£14.50

Following voltages available from secondary tapings. MT124AT to MT123AT 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60v or 30-0-30v


MINIATURE MAINS TRANSFORMERS					
TYPE No.	SECONDARY VOLTAGES	CURRENT	WEIGHT	P/P	PRICE
MT6	6-0-6v	500mA	200g	40p	£1.65
MT12	12-0-12v	250mA	200g	40p	£1.65
MT20	20-0-20v	150mA	200g	40p	£1.65

SUB MINIATURE MAINS TRANSFORMERS					
TYPE No	SECONDARY VOLTAGES	CURRENT	WEIGHT	P/P	PRICE
TR1	6-0-6	100mA	75.9	40p	£1.10
TR2	9-0-9	75mA	75.9	40p	£1.10
TR3	12-0-12	50mA	75.9	40p	£1.20
TR4	12-0-12	100mA	75.9	40p	£1.35

TYPE No	SECONDARY VOLTAGES	CURRENT	WEIGHT	PRICE
MT207CT	0, 8, 9v	500mA	510g	£3.75

SIZES IN MM OF TRANSFORMERS

MT6	60x40x45	MT79AT	70x60x70
MT12	60x40x45	MT85AT	95x70x70
MT20	60x40x45	MT102AT	75x75x65
TR1	45x25x27	MT103AT	80x60x65
TR2	45x25x27	MT104AT	80x70x100
TR3	45x25x27	MT105AT	100x90x90
TR4	50x27x30	MT107AT	140x105x120
MT3AT	75x55x90	MT112CT	70x65x60
MT18AT	95x60x70	MT124AT	125x100x100
MT20AT	100x75x85	MT126AT	75x75x65
MT21AT	100x90x85	MT127AT	100x70x85
MT51AT	120x80x110	MT127AT	
MT68AT	85x80x75	MT207CT	75x50x60
MT71AT	75x75x75	MT213CA	81x45x45

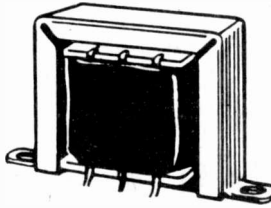


DON'T FORGET POSTAGE

HEATSINKS-REDPOINT




Y-TYPE POWERSINKS				PRICE
2Y1	Undrilled	6.2 C/W	55gms	£0.55
2Y2	1 x TO3	6.2 C/W	55gms	£0.60
4Y1	Undrilled	3.9 C/W	110gms	£0.85
4Y4	2 x TO3	3.9 C/W	110gms	£1.10
4Y5	2 x TO66	3.9 C/W	110gms	£1.32

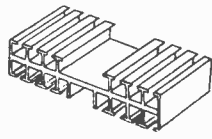Compact design stocked in 2 lengths 2" and 4". For moderate power involvement.



W-TYPE POWERSINKS				PRICE
ORDER CODE	RATING	WEIGHT		
2W1	Undrilled	1.9 C/W	150gms	£0.90
4W1	Undrilled	1.3 C/W	280gms	£1.37
4W4	2 x TO3	1.3 C/W	280gms	£1.65
6W1	Undrilled	1.1 C/W	425gms	£1.98
6W4	2 x TO3	1.1 C/W	425gms	£2.35

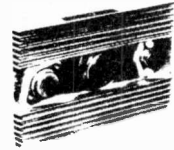Stocked as Standard HT-Sink in three lengths 2", 4" and 6" with Transistor Drillings as shown.



M-TYPE POWERSINKS				PRICE
2M1	Undrilled	4.2° C/W	90gms	£0.60
2M2	1 x TO3	4.2 C/W	90gms	£0.71
2M3	1 x TO66	4.2 C/W	90gms	£0.90
4M1	Undrilled	2.8 C/W	170gms	£1.05
4M2	1 x TO3	2.8 C/W	170gms	£1.10
4M3	1 x TO66	2.8 C/W	170gms	£1.25


Stocked in 2" and 4" lengths Transistor Mountings as shown.



PRICE	CH-TYPE HEATSINK	
35p	CH77	23 C/Watt for TO126 Plastic and Motorola Case 77 19 x 8 x 25mm
35p	CH90	18 C/Watt for TO127 Plastic and Motorola Case 90 19 x 8 x 32mm
35p	CH106	18 C/Watt for C106D etc 19 x 8 x 32mm



F-TYPE HEATSINK	
12p	18F 50 C/Watt Clip on for TO-5 Case
12p	5F 50 C/Watt clip on for TO-18 Case

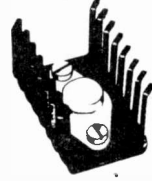

TV-TYPE HEATSINK	
35p	TV-2 10.5 C/Watt for TO66 Power
35p	TV-3 10.5 C/Watt for TO3 Power
35p	TV-4 10.5 C/Watt for Plastic Power

CABLE

AUDIO-SCREENED CABLE

Z.1-MICROPHONE, SINGLE (STANDARD)	12p
Z.2-MICROPHONE SINGLE HEAVY DUTY	17p
Z.3-MICROPHONE, TWIN	19p
Z.8-MULTICORE, STANDARD, 8-WAY	45p
Z.12-MULTICORE STANDARD, 12-WAY	55p
Z.14-MULTICORE, MINIATURE, 4-WAY	30p
Z.19-MULTICORE, MINIATURE, 9-WAY	45p

Z.20-MULTISCREENED 4 WAY	28p
Z.21-PICK-UP, SINGLE SUB MINIATURE	12p
Z.22-PICK-UP, TWIN SUB MINIATURE	14p
Z.23-STEREO SCREENED LEAD	18p

Z.33-3 CORE ROUND, STANDARD 2% AMPS	18p
Z.34-3 CORE ROUND, HEAVY DUTY, RIBBED	28p

COAXIAL CABLES

Z.41-U.H.F. (BANDS I-V) 75 OHMS	24p
Z.45-V.H.F. (BANDS I-III) 75 OHMS	18p

MAINS CABLE

Z.25-FIGURE 8-RIB POLARISED	10p
Z.31-2 CORE OVAL - 2% AMPS	12p

V.H.F. FEEDER CABLES

Z.50-V.H.F./F.M. TWIN RIBBON FEEDER	12p
-------------------------------------	-----

INSTRUMENT CASE

THE PROFESSIONAL TOUCH!

CASE—A housing unit for plug in Eurocards (100x160) and/or modules. Can be used free standing or in 19" racking. Consists of aluminium frame, 34 prs. of guides and separate mounting rail for 31-way connectors — top, rear and base removable — blue PVC clad aluminium — base and rear are ventilated — inside width is 17" — to take a combination of modules and front panels.

4" MODULE—Consists of 4" front panel, 4 guide rails with fixing holes, a rear and base plate — rigid construction.

FRONT PANELS available 1" or 2" wide made of anodised aluminium — easily attached to Eurocards with mounting angles and screws — economic way of building control units.


CARDS—Standard Eurocards — designed to slide in and out easily

CONNECTORS—A 31-way plug and socket array — designed to work quickly and efficiently — accurately guided together when cards are inserted.

Description:	Price
● CASE (including guides)	71-3841-L £23.00
● 4" MODULE	71-3844G £3.50
● 2" F	71-3845-G £1.10
● 1" FRONT PANEL	71-3846-H £1.05
● VEROBOARD	09-1034F £1.32
● DIP BOARD	10-1041J £3.60
● 31-WAY PLUG	17-0267H £1.40
● 31-WAY SOCKET	17-0268C £1.65

POSTAGE

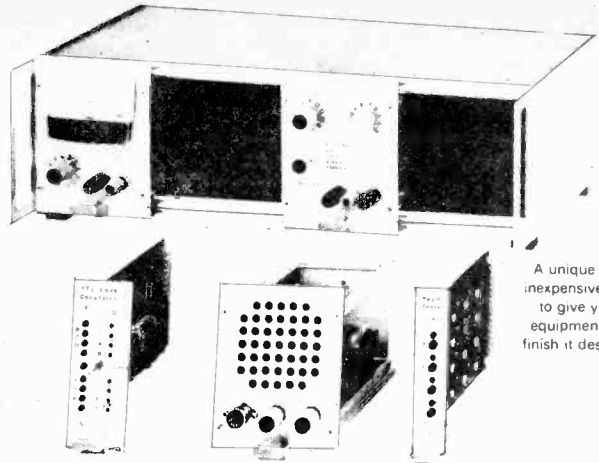Although the case comes flat, please allow an extra £1.20 for postage. Many thanks.



A unique and inexpensive way to give your equipment the finish it deserves

A wide range of combinations for the amateur and electronics lab



19" CARD FRAME/CASE SYSTEM FOR YOUR ELECTRONIC EQUIPMENT

* THE SYSTEM

verowire

Verowire is basically a new kind of interconnecting system for P.C. Boards enabling maximum density to be achieved using integrated and/or discrete components.

The Verowire wiring system is ideal for prototypes, bread boards and limited production runs. Finished results are of a high standard with a neat and orderly appearance achieved in significantly less time than required by more conventional methods previously available.



Spare Pen
Plus 1 Spool £2.75

KIT CONTAINS	
Wiring Pen	1
Circuit Board	1
Reels of Wire, 38 AWG (Red) (one reel fitted to wiring pen)	3
Reels of Wire, 34 AWG (Green)	2
Half pins	100
Shouldered Terminal Pins	100
Plastic Wiring Comb	20
Lead deformation tool	1
Pin insertions tool	1
Cutters	1
Inspection magnifier	1
PRICE £19.00 FULL KIT	

4 spare spools
8 SWG for £2.55

WIRE WRAPPING / UNWRAPPING TOOL

PRICE £6.50

This tool does the job of two at less cost and with less weight. It is quick, convenient and easy-to-use.
TYPE 5B-1908K


WIRE WRAPPING WIRE

Standard packs of 500 x 4" lengths of Kynar insulated wire — Silver plated soft copper wire — pre-stripped ready for use.
59-1766L PACK OF 500 4" £6.00

WIRE WRAPPING SOCKETS

8 PIN DIL	£35p
14 PIN DIL	45p
16 PIN DIL	50p
24 PIN DIL	75p

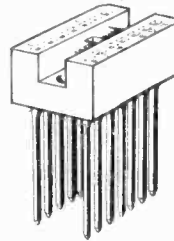High quality sockets designed to provide max. reliability at a most economical cost.
Excellent performance.



NEW



VEROBOARDS

● .1 MATRIX COPPER BACKED

10345/P16	2.5" x 5"	£0.55
10346/P16	2.5" x 3.75"	£0.46
13236/P16	2.5" x 1.7"	£1.69
10347/P16	3.75" x 5"	£0.62
10348/P16	3.75" x 3.75"	£0.55
13237/P16	3.75" x 1.7"	£2.18
Packets of 5pcs	2.5" x 1"	£0.67
126/P16	4.7" x 1.7 5"	£2.81
14354/P16	2.5" x 1"	£0.15

● PLAIN BOARD .1

520	2.5" x 3.75"	£0.31
521	3.75" x 5"	£0.50
522	3.75" x 1.7"	£1.41

● INDUSTRIAL BOARD .1

VB111001	9.95" x 4.4"	£2.50
VB111004	6.95" x 7.9"	£3.25
VB111005	9.95" x 7.9"	£4.20
VB1124	7.05" x 17.9"	£4.40

● .15 PLAIN BOARD

441/4501	2.5" x 1.7"	£0.92
442/4505	3.75" x 1.7"	£1.20
444/8023	4.95" x 1.7"	£1.83
14352	3.75" x 5"	£0.43
11990	2.5" x 5"	£0.31
11991	2.5" x 1.75"	£0.24

.15 STANDARD COPPER BACKED

41/P16	2.5" x 1.7"	£1.35
42/P16	2.5" x 5"	£0.50
43/P16	2.5" x 3.75"	£0.36
44/P16	3.75" x 1.7"	£1.80
45/P16	3.75" x 5"	£0.67
46/P16	3.75" x 3.75"	£0.50
Pkts. of 5 pcs	2.5" x 1"	£0.62
14353/P16	2.5" x 1"	£0.15

.2 PITCH

4/1101/P16	4.80" x 18"	£2.30
------------	-------------	-------

GROUP BOARDS

11986 (0 15)	8.4" x 1.5"	£0.53
13897 (0 1)	8.4" x 1.5"	£0.53
Spot Face Lutter		£0.80




Pin Insertion
Tools £1.10



PINS

Available in		.1	.15
1 & 15	36 Pins	£0.39	£0.39
Price per	200 Pins	£1.42	£1.39
bag	1000 Pins	£5.26	£4.90

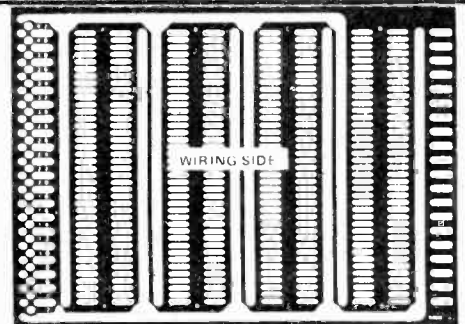


IC BREADBOARD (DIP)

VERO TYPE 13401, 4.15" x 6.15"

Most popular integrated circuit Breadboard

£2.68

VERO V-Q BOARD

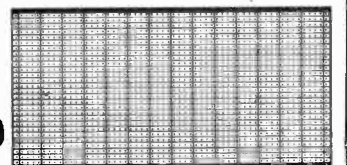

150 x 75mm
SPECIAL DESIGN FOR DIL ICs — 14 x 4 hole SEGMENTS
ELIMINATES TRACK CUTTING — 28 STRIPS

£0.90

STANDARD KNOBS


M14		M1	
M10		M4	
M15		M5	
M16		M7	
M6		M8	
M11		M10	
M12		M12	
M13		M13	
M14		M14	
M15		M15	
M16		M16	

ALL KNOBS ARE FOR 1/4" SPINDLEX EXCEPT M14

BOXES AND CASES

ALUMINIUM BOXES


BA1	2 3/4 x 5 1/4 x 1 1/2"	72p
BA2	4 x 4 x 1 1/2"	77p
BA3	4 x 2 3/4 x 1 1/2"	72p
BA4	4 x 5 1/4 x 1 1/2"	93p
BA5	4 x 2 1/2 x 2"	83p
BA6	3 x 1 x 2"	55p
BA7	6 x 4 x 2"	£1.10
BA8	7 x 5 x 2 1/2"	£1.32
BA9	8 x 6 x 3"	£1.65
BA10	10 x 7 x 3"	£2.20
BA11	10 x 4 1/2 x 3"	£1.98
BA12	12 x 5 x 3"	£2.15
BA13	12 x 8 x 3"	£2.58

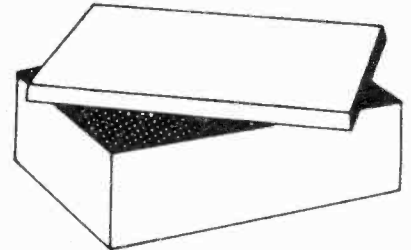

REXINE COVERED

RB1	6 x 4 1/2 x 1 3/4"	£1.55
RB2	8 x 5 x 2"	£1.80
RB3	9 x 5 x 2 1/2"	£2.10
RB4	11 x 6 x 3"	£2.55
RB5	11 x 7 1/2 x 3 1/2"	£3.20
RB6	13 x 8 x 4 1/2"	£4.40
RB7	15 x 8 x 4"	£4.65

Complete with screws and feet

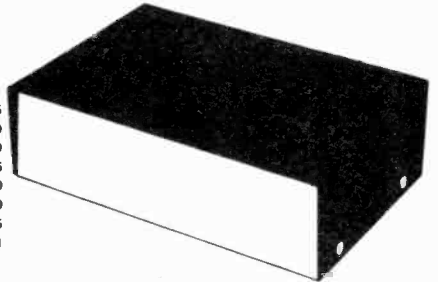

VERO POTTING BOXES

VPB1	2x3x1 Black	50p
VPB2	2x3x1 White	50p

A small high quality ABS plastic box supplied complete with lid and screws — 75-1413E.


HAND HELD CONTROL BOX

The new Vero Hand Held Control Box — ideal for remote control uses — specially designed for the purpose. White ABS plastic. Measures 94x61x22.6mm. Price 68p

VERO CASES

1 PLASTIC BOXES

VB1	—65x120x40mm	£2.50
	CODE 65-251BH	
VB2	—80x150x50mm	£2.80
	CODE 65-2520J	
VB3	—110x188x160mm	£3.75
	CODE 65-2522K	

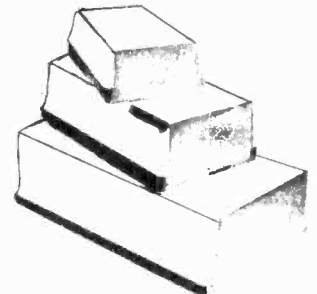


Moulded in 2 tone high impact polystyrene — screw fixing — very strong — ideal for wall mounting or bench use — threaded brass inserts for P.C. mounting

2 PLASTIC CASES

a) illustrated


VC1	—205x140x40mm	£3.20
	CODE 75-1410J	
VC2	—205x140x75mm	£3.60
	CODE 75-1411D	
VC3	—205x140x110mm	£4.70
	CODE 75-1412K	

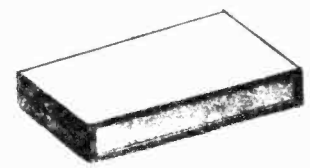

Moulded in light grey high impact ABS — includes internal P.C.B. fixing screws and anodised aluminium front panel held in place by the two halves of the case — screw fixing plus rubber feet.

3 PLASTIC CLIP CASES


VCC1	—85x40x154mm	£2.27
	CODE 75-1237J	
VCC2	—85x60x154mm	£2.85
	CODE 75-1238D	
VCC3	—85x80x154mm	£3.40
	CODE 75-1239K	

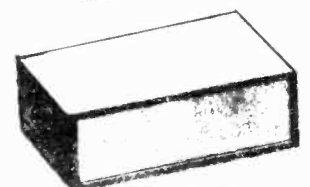


Similar to plastic boxes (1) but with anodised aluminium front panel, two tone halves clip together solidly without screws for ease of access. P.C.B. fixings inside

4 PLASTIC SLOPING CASE

VSC1	—220x174x100/50mm	£6.95
	CODE 65-2523E	
VSC2	—171x121x75/37.5mm	£4.20
	CODE 75-1798K	

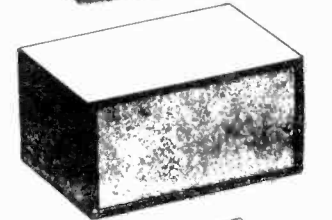


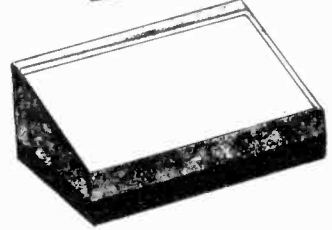Two tone case — removable anodised ali. front panel and recess at rear for cable entry, ideal instrument case.



INSTRUMENT KNOBS

SIFAM COLLET KNOBS

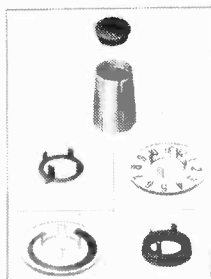

Function, styling, handling & simplicity of assembly are the main features of this new range of collet knobs. The various accessories — caps, pointers & nut covers — are simply plugged into basic knobs to form a vibration proof unit. Full size illustrations shown here indicate the possible combinations of colours available

Two basic ranges are stocked along with related accessories, these are a 15mm diameter range and a 21mm diameter range

KNOBS available in black or grey

S150	— 15mm short knob, plain	£0.30
S151	— 15mm short knob and line pointer	£0.33
K150	— 15mm standard knob and plain	£0.33
K151	— 15mm standard knob and line pointer	£0.36
W151	— 15mm wing knob and line pointer	£0.38
K210	— 21mm standard knob, plain	£0.38
K11	— 21mm standard knob and line pointer	£0.42
W211	— 21mm wing knob and line pointer	£0.44

CAPS available in black, red, grey, green, blue or yellow

C150	— cap for 15mm knob, specify colour	£0.02
C210	— cap for 21mm knob, specify colour	£0.02

POINTERS available in same colours as caps

P150	— pointer for 15mm knobs	£0.03
P210	— pointer for 21mm knobs	£0.03

NUT COVERS available black, red, grey

N150	— nut cover for 15mm knobs	£0.03
------	----------------------------	-------

Nut covers not needed on 21mm knobs

FIGURE DIALS available as shown

Black with white pointer	15mm 12p	21mm 15p	each
Grey with black pointer	15mm 12p	21mm 15p	each
Clear with black taper	15mm 12p	21mm 15p	each
Figure dial 1-10 clear	15mm 13p	21mm 15p	each

ALL KNOBS ARE FOR 1/4" SPINDLES
DON'T FORGET TO SPECIFY COLOUR REQD



MODEL C15 — 15 watt

Miniature soldering iron. Bits slide on and off stainless steel shaft. Efficient heat transfer. Length 16cm. **£3.69**

Spare Elements **£1.58**

**SPARE BITS AVAILABLE**

(2)		2.3	3/32	All Bits are Nickel Plated Price 50p
(3)		4	1/8	
(4)		4.7	3/16	
(6)		1	1/16	

MODEL CCN15 — 15 watt

Unique Ceramic shaft—no measurable leakage. Capacitance 30pf. Tested at 2kV A.C. Length 16 cm. **£3.96**

Elements **£2.06**

**CCN**

15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation

SPARE BITS AVAILABLE

1100		2.3	3/32	All Bits are Iron Coated Price 50p
1101		3	1/8	
1102		4.7	3/16	

MODEL X25 — 25 watt

Near perfect insulation. Breakdown voltage 1.500v A.C. Leakage 3.5uA. Stainless steel shaft and phenolic handle. Length 22cms. weight 50g. **£3.69**
Element **£1.74**



25 watt 240 volts soldering iron

X25 Soldering Iron

with ceramic shaft to ensure perfect insulation.

Element X25E

SPARE BITS AVAILABLE IRON COATED

No. 50		2.4	3/32	Price 54p
No. 51		3.2	1/8	
No. 52		4.7	3/16	

THE 17 WATT MODEL CX

NEW PRICE £3.69

Model CX is manufactured on the same principle as the model X.25 which has proved such success since its introduction.

The *double shaft* principle of the X.25 has now been applied to a miniature iron, giving it the strength of the model C and the superb insulation of the CCN and the X.25. It is virtually *free of current leakage*, like model CCN, but it is not so delicate as that model. The addition of a steel shaft has of course meant that it has an *earth contact* and it is supplied with 3-core flexible cable.

Specification

Voltage range:	220-250 volts A.C. / D.C.
Power consumption:	17 watts at maximum voltage
Breakdown voltage:	4000 volts A.C.
Current leakage:	3.5 uA.
Lead:	3-core
Length:	19cm (7 1/2")
Weight:	40 grams (without lead)

Spare Elements available Price **£1.58**

Uses same tips as Model CCN i.e. No. 1100, 1101 & 1102


PRICE 50p

**ST3 Stand**

Price **£1.53**

This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands.

The two sponges at the side which are easily replaceable, serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration.

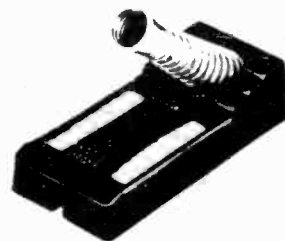**DESOLDERING TOOL. £5.94**


SPARE TIPS 65p

A new and improved model to deal with solder removal where components are tightly grouped or otherwise inaccessible. Instantly removes all unwanted solder from printed circuits and all other solder joints. Simple, reliable, speedy and accurate.

CORDLESS SOLDERING IRONS

7500 — "Iso-Tip" Soldering Iron Kit (Standard). Price **£17.28**

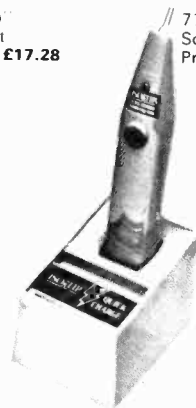7700 — Quick Charge Soldering Iron Kit Price **£19.98**



NEW AND EASY TO USE

No. 7645—FINE TIP #2

No. 7535—REGULAR TIP #5

No. 7588—MICRO SOLDERING TIP

Quick charge iron comes complete with one spare tip.

£2.50

The Oryx Super 30 £3.78

The Oryx Super 30 gives you these features as standard.


- A long life screw-on iron coated tip.
- Extended element life through current phase control built into the handle.
- Neon light in handle – a unique safety feature.
- Robust – very rigid construction.
- Stainless steel shaft and clip-on hook.
- Beautifully styled handle designed.

The Oryx Super 50 £9.61 TEMPERATURE-CONTROLLED

Temperature controlled iron so small, light and because it runs at an even temperature, it can be set to a lower heat than conventional uncontrolled irons. This is an important advantage when dealing with P.C. boards, I.C.s etc. 50 watts, 210/250 volts, Heating: 45 secs., Length 8"/200mm. Weight 2½ ozs/77 grms. Safety. Range of tips as for Oryx 75.

- ☆ Temperature range from 200°C to 400°C ± 2°C.
- ☆ Long life iron coated tip fitted as standard
- ☆ Built-in indicator lamp operates with thermostat
- ☆ Aluminium heat sink keep handle cooler

SPARE TIPS £0.95


LL/SF/16		LL/SF/32	
LL/SF/24		LL/SF/48	
		LL/SF/64	

COOLING FANS

The new 'Mule' fan represents a breakthrough in slim axial fan design. It reverses the drive principle in normal use with this type of fan by employing an outer stator/inner rotor design. The result is up to 20% more output than other fans of its size (up to 60cfm) and a large saving in production costs. The impeller is glass re-inforced nylon with a specially-developed aerofoil section for maximum performance. The fan is designed to be mounted either way round to enable induction or extraction and can be positioned inside or outside the cabinet. Built to the highest standards of safety, the unit incorporates a thermal cut-out to eliminate overheating problems should the fan be jammed. It will be of great use in electronics, vending machines, refrigeration, air conditioning, and other fields.

New design means

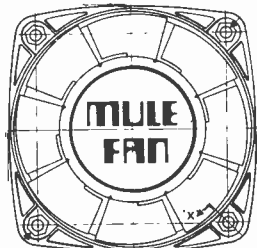- Lower price
- Up to 20% more output than other fans of its size
- Easily mounted for either induction or extraction
- High performance g r n impellers
- Thermal cut-out to protect unit and installation.



It's 95mm x 50mm thick at the Slim Price £9.70

**STAY
COOL!**

**USE
MULE**


**THE NEW
LOW COST
FAN**

ERSIN



HANDY SOLDER DISPENSER Size 5 £0.50

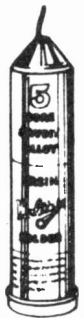Contains 2.3 metres of
SAVBIT SOLDER
Postage/Packing 45p
on Size 10 & 12



Ref.	Alloy	Daim. mm	Length metres approx	Use	Price
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits	£1.84
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold	£1.84

PRINTED CIRCUIT KIT

ideal PCB kit for the enthusiastic printed circuit board designer.

Contains

- Printed Circuit Board
- Circuit Marker Pen
- Etching Crystals
- Solvent

Kit. Price £3.50



PCB
KIT

SOCKETS & HOLDERS


			Price
TO18	4 pin holder	A1236/4L	£0.18p
TO5	3 pin holder	A1192	£0.19p
TO18	3 pin holder	A1236	£0.16p
TO99	8 pin holder	A23 2013	£0.44p
TO99	10 pin holder	A23 A2014	£0.49p
TO99	12 pin holder	A1200	£1.30p



DUAL-IN LINE SOCKETS

8 pin D I L	£0.15p
14 pin D I L	£0.16p
16 pin D I L	£0.18p
18 pin D I L	£0.27p
22 pin D I L	£0.30p
24 pin D I L	£0.35p
28 pin D I L	£0.45p
40 pin D I L	£0.55p

**NEW
LOW PROFILE**

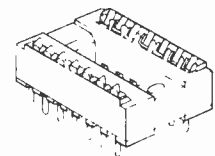

TRANSISTOR COVERS


TO3C	Plastic cover	£0.11p
TO66C	Plastic cover	£0.11p

SOLDERCON PINS

FOR LOW COST

IC SOCKETS £0.55/100 STRIP

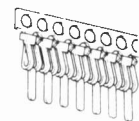Strip of 100 pins for those odd moments you find yourself without a socket



ENAMELLED COPPERWIRE

Available on 2oz Reels in the following gauges

20z REELS	SWG	Price	SWG	Price
	16	£0.44	28	£0.55
	18	£0.44	30	£0.60
	20	£0.44	32	£0.60
	22	£0.50	34	£0.65
	24	£0.50	36	£0.65
	26	£0.55	38	£0.70


























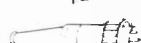
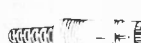









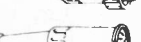

















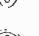

ETCH RESIST PEN











Etch Resist Pen for Printed Circuit Boards—Simple and Efficient

£1.08



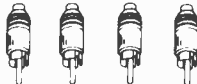





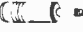

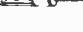





DIN PLUGS & SOCKETS

		2 PIN LOUDSPEAKER PLUG	11p
		2 PIN LOUDSPEAKER CHASSIS SOCKET	8p
		2 PIN LOUDSPEAKER SNAP-IN SOCKET	11p
		2 PIN LOUDSPEAKER LINE SOCKET	11p
		3 PIN PLUG FULLY SCREENED	16p
		3 PIN CHASSIS SOCKET	13p
		3 PIN CHASSIS SNAP-IN SOCKET	13p
		3 PIN SCREENED LOCKING PLUG	75p
		3 PIN LOCKING LINE SOCKET	66p
		3 PIN LINE SOCKET	16p
		4 PIN PLUG	16p
		4 PIN SOCKET CHASSIS MOUNTING	13p
		5 PIN 180° PLUG FULLY SCREENED	16p
		5 PIN 180 CHASSIS SOCKET	13p
		5 PIN 180 CHASSIS SNAP-IN SOCKET	13p
		5 PIN 180 LINE SOCKET	16p
		5 PIN 180 LOCKING PLUG	85p
		5 PIN 180 LOCKING LINE SOCKET	85p
		5 PIN 240° PLUG FULLY SCREENED	16p
		5 PIN 240 CHASSIS SOCKET	13p
		5 PIN 240° LINE SOCKET	16p
		6 PIN PLUG FULLY SCREENED	16p
		6 PIN CHASSIS SOCKET	13p
		7 PIN PLUG FULLY SCREENED	16p
		7 PIN PLUG FULLY SCREENED	16p
		7 PIN PLUG FULLY SCREENED	13p
		ADAPTOR 2 PIN SPEAKER PLUG TO TWO 2 PIN SOCKETS	66p






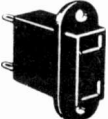






PHONO PLUGS & SOCKETS

	PHONO PLUG—METAL FULLY SCREENED	16p
	PHONO LINE SOCKET FULLY SCREENED	16p
	PHONO PLUGS & LINE SOCKETS—SCREW TOP PLASTIC	11p
	PHONO SINGLE CHASSIS SOCKET ON PAXOLIN	8p
	DOUBLE PHONO SOCKET	11p
	FOUR-WAY PHONO SOCKET	22p
	SIX-WAY PHONO SOCKET	27p
	EIGHT-WAY PHONO SOCKET ON PAXOLIN	38p

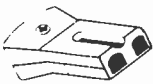
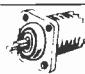


JACK PLUGS & SOCKETS

MONO		
	1/4" STANDARD JACK PLUG — FULLY SCREENED	29p
	1/4" STANDARD JACK PLUG — UNSCREENED	17p
	1/4" STANDARD JACK CHASSIS SOCKET SWITCHED	22p
	1/4" STANDARD LINE SOCKET PLASTIC or METAL	22p 33p
STEREO		
	1/4" STEREO JACK PLUG FULLY SCREENED	38p
	1/4" STEREO JACK PLUG UNSCREENED	27p
	1/4" STEREO JACK CHASSIS SOCKET— SWITCHED	27p
	1/4" STEREO LINE SOCKET 1) METAL 2) PLASTIC	49p 27p
	3.5mm JACK PLUG FULLY SCREENED PLUG	17p
	3.5mm JACK PLUG FULLY SCREENED LINE SOCKET	17p
	3.5mm JACK PLUG PLASTIC— UNSCREENED LINE SOCKET	11p 11p
	3.5mm JACK SOCKET CHASSIS—PLASTIC	13p
	3.5mm JACK SOCKET CHASSIS—METAL	11p
	2.5mm JACK PLUG PLASTIC	11p
	2.5mm JACK PLUG METAL	16p
	2.5mm JACK SOCKET CHASSIS, SWITCHED PLASTIC	11p




POWER CONNECTORS

- | | | |
|------------|--|---|
| 33p | 12 WAY FLEXIBLE CONNECTOR BLOCK
2 AMPS |  |
| 10p | BANANA PLUGS
RED OR BLACK |  |
| 7p | BANANA SOCKET
RED OR BLACK |  |
| 16p | POWER PLUG
USA 2 PIN MAINS
CONNECTOR
PLASTIC |  |
| 16p | USA MAINS POWER
LINE SOCKET
PLASTIC |  |
| 16p | USA MAINS POWER
CHASSIS SOCKET
PLASTIC |  |
| 11p | PP3 BATTERY SNAPS |  |
| 15p | PP9 BATTERY SNAPS |  |
| 20p | MAINS CONNECTOR
NON-REVERSIBLE
2 PIN CALCULATOR PLUG |  |
| 35p | NON-REVERSIBLE
CHASSIS MOUNTING
CALCULATOR SOCKET |  |
| 15p | ROCA PLUG—
BATTERY USE,
SLIDING SLEEVE |  |
| 13p | ROCA SOCKET
SWITCHED FOR
BATTERY CONNECTION |  |






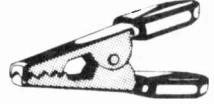







U.S.A. COAXIAL CONNECTORS

- | | | | |
|--------------|---|---------|---|
| £0.65 | UHF Plug suits Uniradio 67 | PL259 |  |
| £0.55 | UHF Chassis Mounting
Square Socket
18 x 18 x 3.2 Fixing | S0239 |  |
| £0.55 | UHF Round Socket
Panel Mounting | S0239SH |  |
| £0.70 | UHF Double Ended
Female Coupler | PL258 |  |








BNC CONNECTORS (75R)

- | | | |
|---|---|---|
|  |  |  |
| TYPE FS75
£0.82 | TYPE FP75
£0.82 | TYPE CP75
£0.82 |
| 75Ω COAXIAL CONNECTORS BY GREENPAR | | |

TERMINALS & CLIPS

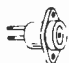- | | | |
|--------------|--|---|
| 21p | TWO POLARISED
SCREWS &/OR
PHONO SOCKET
2-3/8" x 3/4" |  |
| 37p | DOUBLE, SPRING
LOADED PUSH TO
RELEASE CABLE
TERMINAL ONE RED
ONE BLACK |  |
| 55p | DOUBLE SPRING
LOADED TRIGGER
TERMINALS ONE
RED ONE BLACK |  |
| £1.00 | FOUR WAY SPRING
LOADED TRIGGER
TERMINALS 2 RED &
2 BLACK |  |
| 80p | FOUR WAY SPRING
LOADED PUSH TO
RELEASE CABLE
TERMINAL |  |
| 7p | CROCODILE CLIPS
1 1/2" long Red or Black
PLASTIC HANDLES |  |
| 15p | 2mm METER PLUG
4mm METER PLUG
Red or Black |  |
| 11p | 2mm CHASSIS SOCKET
4mm CHASSIS SOCKET
Red or Black. Not insulated |  |
| 16p | SPADE TERMINALS
Red or Black |  |
| 22p | TERMINAL POST—Will
accept 4mm Meter Plug
Red or Black |  |
| 11p | 4mm LINE COUPLER
Red or Black |  |
| 27p | CROC CLIP 4mm
PLASTIC—Red or
Black—
Takes 4mm plug |  |
| 7p | CROC CLIP MINIATURE
FULLY INSULATED
Red or Black |  |


COAXIAL CONNECTORS

- | | | |
|------------|---|---|
| 16p | COAXIAL TV AERIAL
ALUMINIUM PLUG |  |
| 11p | COAXIAL PLASTIC
PLUG |  |
| 15p | COAXIAL CHASSIS
SOCKET Plastic or
metal |  |
| 17p | COAXIAL SNAP-IN
CHASSIS SOCKET |  |
| 60p | COAXIAL LINE SOCKET
METAL |  |
| 11p | COAXIAL IN LINE
ALUMINIUM COUPLER |  |
| 17p | CAR AERIAL PLUG |  |

SWITCHES

QUANTITY DISCOUNTS
CONTACT US NOW


STANDARD TOGGLES

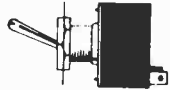

STANDARD
SPST (2 tags) 2A 250V
Chrome toggle—on/off plate
DIMS 25x14x14mm


PRICE

39p

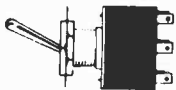

DPDT (6 tags) 2A 250V
Extra long toggle + plate
DIMS 29x18x17mm

48p

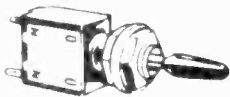

SUB MINIATURE 2A 250V
SPST (2 tags) 12x6x9mm
Red toggle
SPDT (3 tags) 12x6x9mm
Red toggle
DPDT (6 tags) 12x11x9mm
Red toggle
DPDT (6 tags) 12x11x9mm
Centre off Red toggle

70p

77p

85p

95p



MICRO MINIATURE 2A 250V
SPST (2 tags) 8x5x7mm
Chrome toggle
SPDT (3 tags) 8x5x7mm
Chrome toggle
DPDT (6 tags) 8x7x7mm
Chrome toggle

60p

65p

70p



STANDARD
SPST (2 tags) 24x16x17mm
6A 250 extra long paddle
shaped chrome toggle

45p



250v, 15 amp, SPST (2 tags)
Body dims 24x13x14mm
Black plastic toggle

40p



FLAT TOGGLE
250V, 3 amp SPST (2 tags)
Flat toggle, two screw fixing
eschitcheon covers screws
As above but SPCO (3 tags)

88p

95p

QUALITY TOGGLES

ARROW

CT SERIES

Approved to BS3955 Spec.
2A 250V AC, 5A 29V DC

Low cost subminiature toggle switches, designed for applications where compact size, low weight and rugged construction are required. Fitted with solder lug terminals of silver alloy, moving contacts of silver alloy and fixed contacts of silver alloy.

Initial Contact Resistance	10M Max (at 4Vd.c. 1A)
Proof Voltage	2000V r.m.s. at sea level
Insulation Resistance	1000M Min
Electrical Life	50,000 cycles Min.
Mechanical Life	100,000 cycles Min.
Operational Force	150-200 grms
Temp. Range	-40 C to +80 C
Angular Movement	24 - 3


1 POLE, 2 AND 3 POSITIONS — 3 TAGS



BODY DIMS
14x6x16mm

		Price
CTS3	S.P. Change Over	£1.00
CTM3	S.P. Biased C/Over	£1.10
CTC3	S.P. Centre Off	£1.00
CTE3	S.P. Centre Off ½ Biased	£1.10
CTG3	S.P. Biased Centre Off	£1.10

2 POLE, 2 AND 3 POSITIONS — 6 TAGS

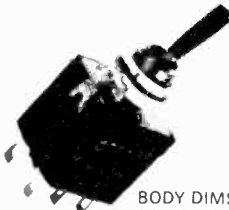

BODY DIMS
14x13x16mm

		Price
CTS6	D.P. Change Over	£1.35
CTM6	D.P. Biased C/Over	£1.45
CTC6	D.P. Centre Off	£1.42
CTE6	D.P. Centre Off ½ Biased	£1.45
CTG6	D.P. Biased Centre Off	£1.45

ROCKER SWITCHES

SPECIFICATION: 16A, 250 Volts A.C. Contact Rating

Dimensions
1600 Series Cutout 27.4 x 12.3 mm
2600 Series Cutout 27.4 x 22x3mm

FEATURES:

- Low cost
- Compact design with popular snap-in fixing.
- Choice of colour and termination.
- Complementary pilot lights and illuminated switches.
- Slow, make and break action providing Class B disconnections as defined in BS. 3955 Part 3, 1972.
- Overseas approved.
- Choice of single pole 1600 Series or double pole 2600.



1 POLE 2 AND 3 POSITION

		PRICE
1600-22E	1 Pole On-Off (2 tags)	£0.45
1602-22E	1P2W Changeover 3 tags	£0.51
1603-22E	1P2W Changeover biased one way 3 tags	£0.53
1604-22E	1P2W Changeover 3 position centre off 3 tags	£0.54
1622-R22E	1 Pole On/Off with 250v red neon	£1.10

2 POLE 2 AND 3 POSITION

2600-22E	2 Pole On-Off (4 tags)	£0.53
2602-22E	2P2W Changeover 6 tags	£0.67
2603-22E	2P2W Changeover biased one way 6 tags	£0.68
2604-22E	2P2W Changeover 3 position centre off	£0.71
2600-R22E	2 Pole On/Off with red mains neon 4 tags	£1.07
2600-R52E	As above but for 12v filament indicator	£1.02

PILOT LIGHTS/INDICATORS

1609-R22E	250v Red mains neon indicator	£0.53
1609-G22E	250v Green mains neon indicator	£0.78
1609-R52E	12v Filament indicator red	£0.48
1609-G52E	12v Filament indicator green	£0.48


SIEMENS MINIATURE PCB SWITCHES

A new range of miniature quality switches specifically designed for the professional


- Extremely reliable
- Break before make
- Double pole double throw
- P.C.B. mounting

Available in push buttons or slide version

Side slide versions	A60-A2	£1.70
Push button	A60-A3	£1.70
Slide switch top	A60-A1	£1.70

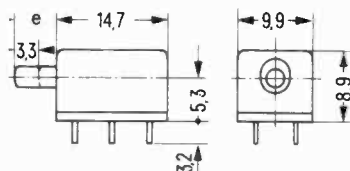

push button switch

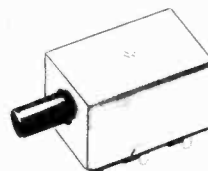

C42315-A60-A3

Side Slide switch



C42315-A60-A2

SIEMENS

SIEMENS MICRO MINI SLIDE SWITCH




The new slide switch (smallest version*) for P.C.B. mounting break before make contacts. The contact parts are gold-plated, 2 double-throw contacts. Further information available.

Part number C42315-A68-A1

£1.45 EACH.

QUALITY & RELIABILITY

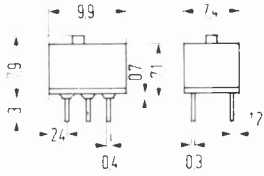

ROTARY SWITCHES


Available in four types all having adjustable rotation limit stop (Located under fixing nut and washer)

RSW12	1 Pole—Adjustable from 2 to 12 Way	£0.54
RSW6	2 Pole—Adjustable from 2 to 6 Way	£0.54
RSW4	3 Pole—Adjustable from 2 to 4 Way	£0.54
RSW3	4 Pole—Adjustable from 2 to 3 Way	£0.54

STANDARD 1/4" SPINDLE

MAKE BEFORE BREAK

See Page 25
for knobs to suit.

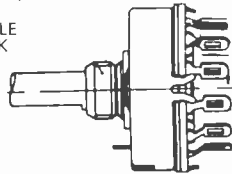

MICROSWITCHES

Miniature Microswitches—10A 250v AV Changeover type
BODY DIMS 28 x 16 x 10mm. Available as standard (S160) Or with free action lever-roller 17mm long (S162)




S.160



S.162

Price
54p

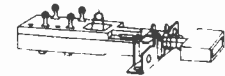

MAINS SWITCH **£0.50**



4 POLE BUSH-BUTTON **£0.45**



8-WAY MOUNTING FRAME **£0.15**


Both the push-button and the mains switch are supplied with a single mounting frame, which can be removed enabling them to be mounted on the mounting frame—up to 8 Way. The push-button is a latching action. Push-on, Push-off but can be converted to momentary contact by removal of the locating pin. All switches include knobs. Independent action.

FOOT SWITCH

2 Pole Change Over
Alternate Action
(Latching)

A Professional Switch—sturdy and rugged construction with strong metal or plastic button
Body DIMS
17 x 32 x 18mm
Rated 3A 250 AC

ARROW

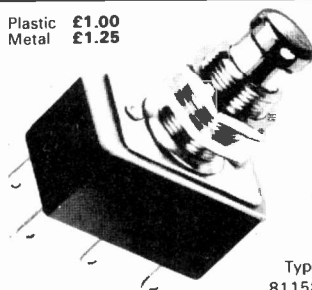


Type
81158

Plastic **£1.00**
Metal **£1.25**

SLIDE SWITCHES

STANDARD PRICE

DPDT 1A 250V Small 15 x 8 x 12	17p
DPDT 1A 250V Medium 16 x 11 x 9	17p
DPDT 1A 250V Large 22 x 13 x 8	17p
DPDT 1A 250V Large 22 x 13 x 8 Centre off	17p

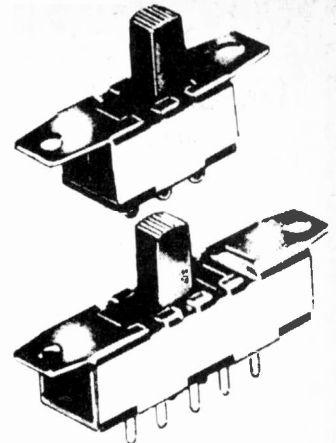


MULTIPOSITION
2 POLE-3 POSITION

5295CS **25p**

2 POLE-4 POSITION

5295CS **25p**

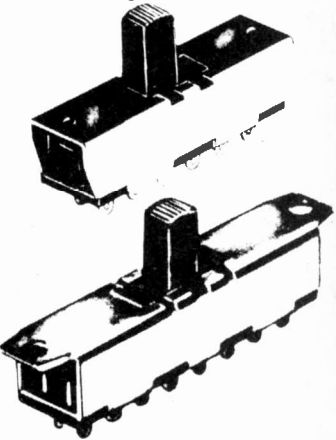

MULTIPOLE
4 POLE-2 POSITION

5289CS **30p**

4 POLE-3 POSITION
5293CS **30p**

PUSH BUTTONS

16p Push to make—Spring off
1A 250V Red, Yellow, Green
DIMS 16 x 6mm (dia)

25p Push to break—as above—Black


50p Push On/ Push Off DPDT (6 tags)
DIMS 20 x 12 x 13mm
Red or Black

85p SPST (2 tags) DIMS 11 x 7 x 17mm
Spring loaded Red top

90p SPDT (3 tags) DIMS 11 x 7 x 17mm
Spring loaded Red top

£1.08 DPDT (6 tags) DIMS 11 x 11 x 17mm
Spring loaded Red top latching
Push to make—Spring off
1A 250V

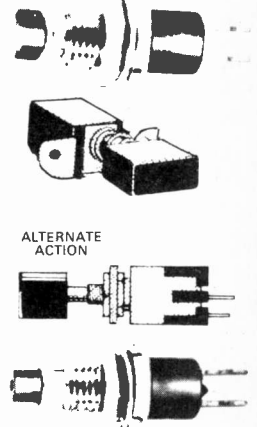15p DIMS 14 x 6mm Diameter
Red, Yellow, Green, Blue and Black Top



ALTERNATE
ACTION


ROCKERS

PRICE EACH


75p SP On-Off (3 tags) 3A 250V
White, See Saw
When on, Neon Lights
DIMS: 29 x 11 x 21

45p On-Off-On 10A 250V
British made, Rocks on-
Off-On
DIMS. 29 x 11 x 18

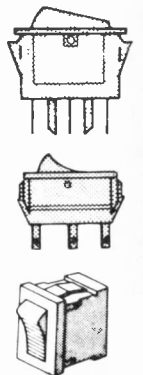
22p SPST (2 tags) 6A 250V
White, miniature
BODY DIMS: 21 x 15 x 13mm



SIEMENS TURN-SLIDE SWITCHES NEW

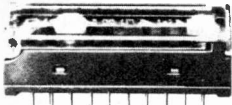


TYPE V42264-V1503-D13

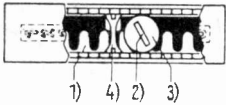

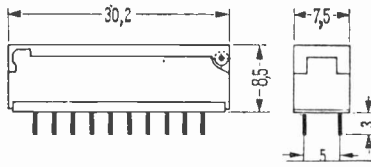- 1) Rack
- 2) Screwdriver slot
- 3) Switching element
- 4) Stop

This new version of the rotary switch is especially suitable for setting programs. The rotary switch is of a 3 elements 3 stops

Voltage rating $\leq 60 V \approx$
 Current rating $\leq 0.5 A \approx$
 fixed contacts gold-plated **£4.40**




SIEMENS DIL SWITCHES

The new dual-in-line switch of printed circuits.

The transparent cover protects the contacts against dust.



Voltage rating $\leq 24 V \approx$
 Current rating $\leq 0.5 A$

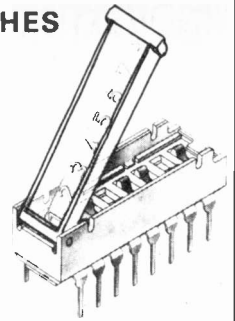All contact parts are nickel plated and gold plated.



TYPE C42315-A1341-A4

8 WAY
 D.I.L.
£2.75

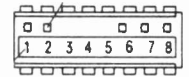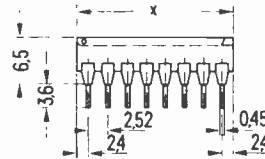

RELAYS—DIL


D.I.L. REED RELAYS

Low power drive -- 35 mW -- for operation direct from TTL
 5, 12 and 24 V nominal coils available
 Contact rating 10 VA switched to carry 1 A
 Optional internal diode and electrostatic screen
 Isolation between coil and contacts.
 10,000 M-ohms -- proof tested to 500 V min
 At present available with 1 form A contact configuration

Coil	VOLTAGE DC				Max	Nom	PRICE
	Operate	Release	FROM	TTL O/P			
15002	530	8	2	18	12	£2.55	
15003	2000	16	4	32	24	£2.55	
15005	360	3.5	1	15	5	£2.55	
15005AB	360	3.5	1	15	5	£3.25	
15005B	360	3.5	1	15	5	£2.75	
15015AB	2000	11.5	4	32	15	£3.35	

Modification 'A' -- Electrostatic shield connected to pin 2.
 Modification 'B' -- Diode connected between pin 6 and 9.

PIN CONNECTIONS

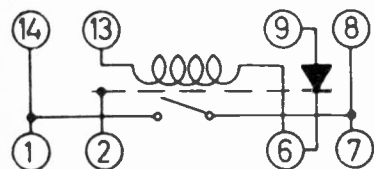


DIL PACKAGE



PICOREED

SIEMENS

Maximum quality.
 Minimum size.

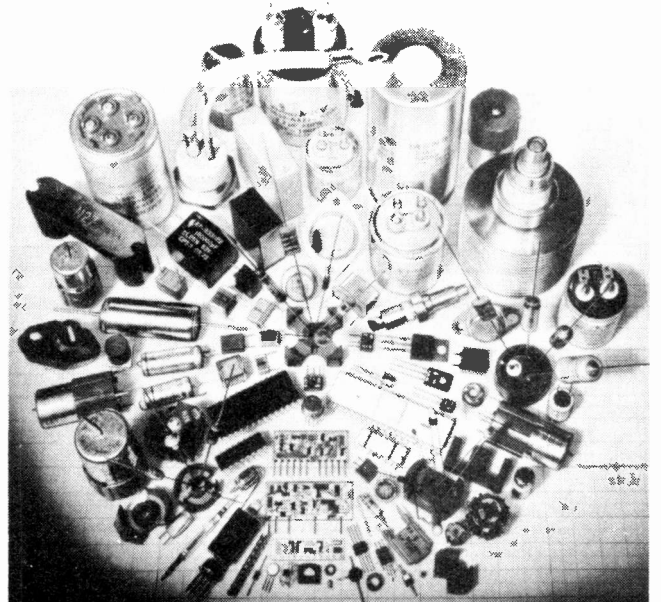


Examples from a range of thousands. Siemens.

Siemens Limited, Great West House,
 Great West Road, Brentford, Middx. TW8. 9DG.
 Telephone: 01-568 9133

64 WAY PCB PLUG AND SOCKET PCB SOCKET




£6.00

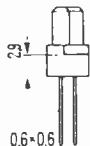

PCB PLUG

£3.95

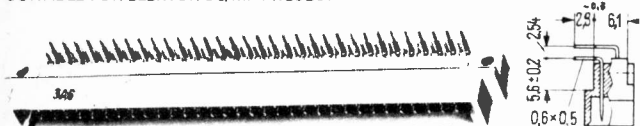BOTH PLUG & SOCKET FIT STANDARD EUROCARD AND ARE SUITABLE FOR ELEKTOR SC/MP PROJECT



INDICATORS & LAMPS

IN1	M575	RED		Price
IN2	M575	BLUE	10mm HOLE	24p
IN3	M575	GREEN		
IN4	M575	YELLOW		
IN5	M575	WHITE		



IN6	B215	RED		28p
IN7	B215	GREEN	11mm HOLE	
IN8	B215	BLUE		
IN9	B215	YELLOW		



IN10	B218	RED		30p
IN11	B218	GREEN	11mm HOLE	
IN12	B218	BLUE		



IN17	TB31S	GREEN	Neon 240v.	35p
------	-------	-------	------------	-----



IN18	JH12R	RED	Neon 240v.	30p
IN19	JH12R	AMBER	Neon 240v.	



IN20	JH12S	RED	Neon 240v.	30p
IN21	JH12S	AMBER	Neon 240v.	



BULBS

To fit Indicators M575, B215 and B218


BU1	12v	12 volt, 0.1 amp, Lilliput screw	10p
BU2	6v	6 volt, 0.2 amp, Lilliput screw	

BATTERY HOLDERS

B1	B205	Moulded. To take four SP11 HP11 batteries in line. Tag terminals	32p
----	------	--	-----



B2	B203	Moulded. To take four SP11, HP11 batteries Two by two. Snap terminals	32p
----	------	---	-----

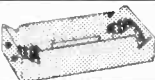

B3	A302	Moulded. To take four penlight batteries Two by two. Snap terminals	20p
----	------	---	-----



B4	A303	Moulded. To take four penlight batteries. Side by side. Snap terminals	20p
----	------	--	-----



B4A	A304	Moulded. To take six penlight batteries. Three by three. Side by side. Snap terminals	28p
-----	------	---	-----



SERVICE AIDS

ELECTROLUBE — SERVICE AIDS

Product Description		Price
Electro-mechanical lubricant	340g	£1.00
Electronic cleaning solvent	340g	£1.00
Freezer	340g	95
Contact treatment oil	170g	£1.00
Contact treatment grease	170g	£1.15
Anti-static foam cleanser	397g	.80
Clear protective lacquer	397g	£1.70
Electro-mechanical lubricant	5cc pen	.55
Contact cleaning strips	(20 strips)	.50

Postage 50p per can
Reliable and safe to use

ELECTROLUBE



AUDIO CONNECTORS

SWITCHCRAFT®

Compatible with Cannon XLR Series

A()F CORD PLUGS



Fresh, streamlined design includes rugged, diecast zinc body, satin nickel finish, high-impact resistant thermosetting plastic socket insert, moulded latchlock, dual pressure plates, keyed neoprene relief bushing. Features "Ground Terminal" and "Ground Contactors" offers 4-, 5-, 6-, and 7-contact versatility. Mates with Switchcraft

A()M and other connectors with similar contact arrangements. Overall length 3 7/32"; diameter 3/4"

Has "Captive Design" insert screw, one-piece pin insert assembly easily removable for fast soldering. Polarizing groove. Die-cast zinc shell, satin nickel finish. Mates with Switchcraft A()F and other connectors with similar contact arrangements. Brass, silver plated chromate dipped pins to resist tarnishing. Overall length 2 25/32"; dia 3/4"




RIGHT-ANGLE CORD PLUGS



Newly styled right angle cord plugs with rugged die-cast housings in two types. A()R()F female and B()R()M male. Ideal for equipment with limited space for connectors. Satin nickel finish, high-impact resistant thermosetting plastic insert, moulded latch-lock, dual pressure plates. Features "Ground Terminal" and "Ground Contactors". Mates with Switchcraft A()M, R()M, S()FM and other connectors and receptacles with similar contact arrangements.

D()F RECEPTACLES

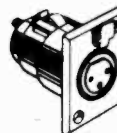

Rectangular flange design receptacle permits close mounting on crowded panel or chassis. Features "Captive Design" loss-proof insert screw, positive latch locking device and high impact thermosetting socket insert. Mates with Switchcraft A()M and other connectors with similar contact arrangements. Dimensions: Flange 1 1/16" x 1 7/16"; Barrel 1 13/64" overall, pin extension 1/4"

D()M RECEPTACLES



Narrow, rectangular flange design receptacle for mounting on compact panel or chassis. Mates with Switchcraft A()F and other connectors with similar contact arrangements. Dimensions: Flange 7/8" x 1 7/16"; Barrel 13/16" overall; pin extension 9/32"

THE ABOVE ARE AVAILABLE IN 3 & 5 PIN VERSIONS

A3F	— 3 Pin	— £1.90	R3M	— 3 Pin	— £4.10
A5F	— 5 Pin	— £3.85	D3F	— 3 Pin	— £2.75
A3M	— 3 Pin	— £1.65	D5F	— 5 Pin	— £4.10
A5M	— 5 Pin	— £3.30	D3M	— 3 Pin	— £1.60
R3F	— 3 Pin	— £4.50	D5M	— 5 Pin	— £2.85

15% DISCOUNT for 50-piece Mix

THE PROFESSIONAL CONNECTION

SILICON GREASE


Thermpath 167 — When mounting semiconductors this material improves thermal resistance by up to 40%. The compound is stable over a wide temp. range and maintains insulation

12gm vial (not illustrated) £0.40
20ml. syringe (46gms) £1.20




QUARTZ CRYSTALS

— 100 kHz	— HC13/μ	— £3.75
— 200 kHz	— HC6/μ	— £4.75
— 1 MHz	— HC6/μ	— £3.75
— 2 MHz	— HC33/μ	— £2.00
— 3-2768 MHz	— HC33/μ	— £2.75
— 4 MHz	— HC18/μ	— £2.75
— 4.194304 MHz	— HC18/μ	— £2.75
— 4.433619 MHz	— HC33/μ	— £1.10
— 10 MHz	— HC18/μ	— £2.50
— 10.7 MHz	— HC6/μ	— £2.75
— 18 MHz	— HC13/μ	— £2.75
— 100 MHz	— HC18/μ	— £3.95

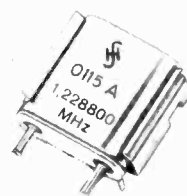

FOR MICROPROCESSORS — CLOCKS — TV & GENERAL APPLICATIONS.

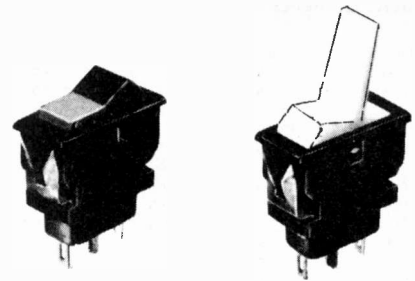
C SERIES SNAP-IN ROCKER & PADDLE LEVER SUBMINIATURE SWITCHES



ARROW

- Robust ■ Positive action ■ Light weight ■ Long operational life
- Lever choice ■ Special requirements by enquiry


CP (Paddle lever)

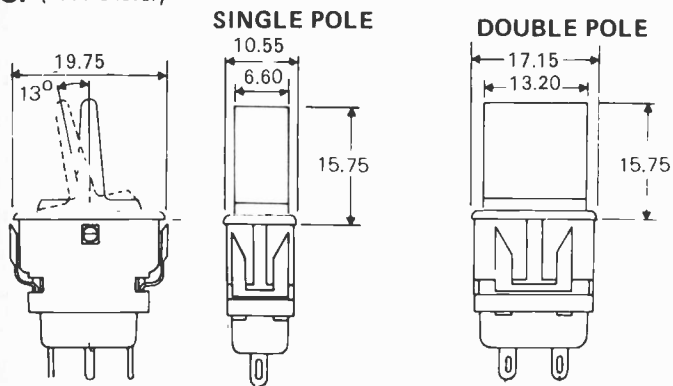

CR (alternative rocker lever)



other dimensions as for CP switch

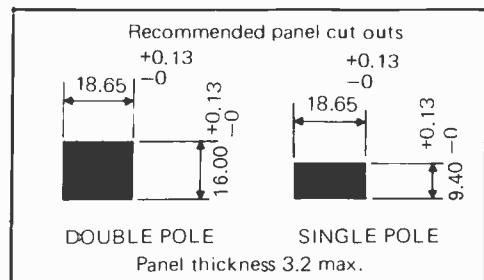

TYPE NUMBERS

1 POLE 2 & 3 POSITION

Single Pole Change over
" " Biased C/off
" " Centre Off
" " C/off 1/2 Biased
" " Biased C/off

ROCKER PADDLE

CRS3	CPS3
CRM3	CPM3
CRC3	CPC3
CRE3	CPE3
CRG3	CPG3

2 POLE 2 & 3 POSITIONS – 6 TAGS

Double Pole Change over
" " Biased C/off
" " Centre off
" " C/off 1/2 Biased
" " Biased C/off

CRS6	CPS6
CRM6	CPM6
CRC6	CPC6
CRE6	CPE6
CRG6	CPG6

Specification 2 Amps 250 Volts

Base Moulding	glass filled phenolic
Contacts	silver and silver/ copper alloy (gold plated to order)
Weight	4 grms. approx. 1 pole 6 grms. approx. 2 pole
Contact Resistance	10 milliohms maximum at 4v DC 1 amp.
Proof Voltage	2000v RMS
Insulation Resistance	100 megohms
Electrical Life	50,000 operations
Mechanical Life	100,000 operations (50,000 momentary action)
Temperature Range	-40°C to +80°C

OUR PRICES INCLUDE VAT

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
CRS3	£0.90	CRS6	£1.25	CPS3	£0.90	CPS6	£1.25
CRM3	£1.10	CRM6	£1.40	CPM3	£1.10	CPM6	£1.35
CRC3	£0.95	CRC6	£1.35	CPC3	£0.95	CPC6	£1.35
CRE3	£1.10	CRE6	£1.45	CPE3	£1.10	CPE6	£1.45
CRG3	£1.10	CRG6	£1.40	CPG3	£1.10	CPG6	£1.40

WHEN QUALITY, RELIABILITY AND STYLE REALLY COUNTS USE ARROW

MULLARD VALVES

QUALITY VALVES BY MULLARD

Type	Price	Type	Price	Type	Price
DY87/802	£1.05	GY501	£2.55	PCL805/8S	£1.55
ECC82	£1.15	GZ34	£1.90	PD500	£3.90
ECC83	£1.15	PC86	£2.05	PFL200	£1.97
ECC84	£1.35	PC88	£2.05	PL36	£2.05
ECC88	£1.90	PC97	£1.15	PL83	£2.55
ECF80	£1.35	PC900	£1.27	PL84	£1.55
ECH84	£2.45	PC84	£1.37	PL95	£1.27
ECL80	£1.52	PCC85	£1.52	PL504	£2.15
ECL82	£1.52	PCC89	£1.55	PL508	£2.55
ECL86	£1.55	PCC189	£1.90	PL509	£3.65
EF80	£1.05	PCF80	£1.37	PL519	£5.20
EF85	£1.05	PCF86	£1.55	PL802	£3.45
EF86	£2.62	PCF200	£2.45	PY800	£1.27
EF183	£1.35	PCF201	£2.45	PY88	£1.40
EF184	£1.45	PCF801	£1.55	PY500A	£2.20
EL34	£2.25	PCF802	£1.55	UCH81	£2.67
EL36	£2.25	PCF806	£1.55	UCH82	£1.65
EL84	£1.15	PCH200	£2.58	UCL83	£1.65
EL86	£2.15	PCL82	£1.37	UL84	£1.85
EL95	£1.52	PCL84	£1.45		
EY86/802	£1.05	PCL86	£1.55		

WHY SETTLE FOR ANYTHING LESS - ASK FOR MULLARD

MULLARD AUDIO MODULES

TYPE	FUNCTION	PRICE
LP1173	Audio Amplifier Module 10 watts	£10.50
LP1181	AM, IF Amplifier Module	£6.30
LP1183/2	Stereo Pre-Amplifier Module	£7.70
LP1184/2	Stereo Pre-Amplifier Module	£11.90
LP1186	FM Tuner Module with Diode Tuning	£11.20
LP1400	Stereo Decoder Module	£11.90




All modules built and factory tested.
Full data with each module or send 5p + S.A.E.

MAINS KEYNECTOR

Ideal for high speed bench testing, shop demonstrations etc. It can take connections up to 13 amp maximum.

Connects electrical equipment to a mains supply in seconds. No plugs or sockets needed. No dangers from touching a live-wire circuit.

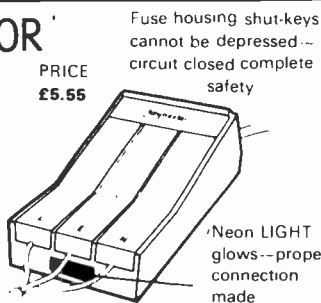● Built-in safety switch with 13 amp fuse.





PRICE
£5.55

SOLDERLESS TERMINALS



RING TONGUE

Red	Blue
15715 £1.65	15735 £1.65
15714 £1.45	15734 £1.45
15713 £1.35	15733 £1.35

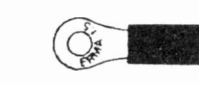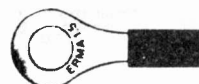


FORK TONGUE

15607 £1.90	15617 £1.90
15606 £1.60	15616 £1.60

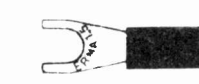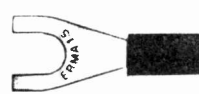


PIGGY-BACK ADAPTOR

15652 £2.75	15653 £2.75
----------------	----------------

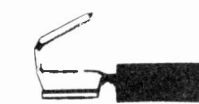

SLIDE-ON SOCKET

15671 £1.60	15673 £1.60
----------------	----------------

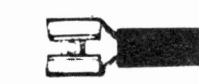

BUTT CONNECTOR

15666 £1.45	15667 £1.45
----------------	----------------



WIRE PIN

15661 £1.85	15662 £1.85
----------------	----------------



SLIDE-ON PLUG

15681 £1.80	15683 £1.80
----------------	----------------



CRIMPING TOOL/ WIRE STRIPPER

Prices are per pack of 50 Terminals

£4.10

RED for Cable 5mm -- 1.5mm BLUE for 1.5mm to 2.5mm

TOOLS & CUTTERS

GENERAL PURPOSE 100mm (4 1/2")

DIAGONAL CUTTERS	£3.40
ROUND NOSE PLIERS	£3.25
FLAT NOSE PLIERS	£3.20
SNIFE NOSE PLIERS	£3.20
END/TOP CUTTERS	£3.80

A quality range of tools for the service man and enthusiast. Box joint construction for strength. Small compact and reliable, insulated handles and smart individual wallet.

20% DISCOUNT

If all five tools are bought at the same time, deduct 20%.

PROFESSIONAL TOOLS/CUTTERS

DIAGONAL CUTTERS TYPE 2111-4 with bevel on outer edge	£9.75
DIAGONAL CUTTERS, TYPE 2112-4 with no bevel -- cuts flush	£9.75
SNIFE NOSE PLIERS TYPE 2411-4	£7.00

A high quality range of Swedish electronic pliers and cutters from Bahco -- combine highest cutting accuracy with precision at reasonable cost. Spring loaded, insulated handles 115mm.


QUALITY FROM BAHCO

FROM BAHCO & BRINDLEY


NEW CUTTERS

Type	Price
2131-4 with bevel	£6.90
2132-4 without bevel	£6.90

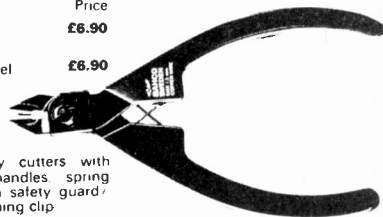
New safety cutters with insulated handles, spring loaded with safety guard, offset retaining clip.




DIAGONAL

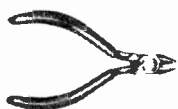


ROUND NOSE

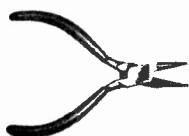


FLAT NOSE

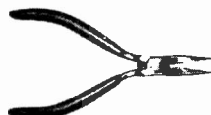

SNIFE NOSE

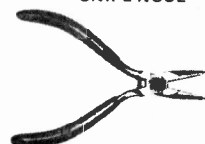

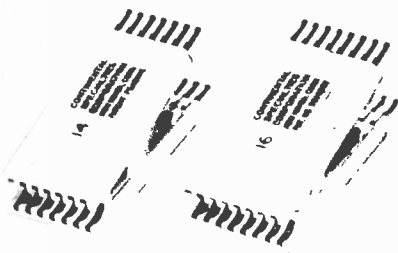PROTO CLIPS Foolproof-power-on incurcuit IC testing. IC test clips. Test clips pay for themselves within weeks. Available in 14 and 16 DIL versions - short proof.



14 PIN DIL PC14 £2.80 16 PIN DIL PC14 £2.97


LOGIC PROBES AND MONITORS

LP2 - LOGIC PROBE (ILLUSTRATED ON RIGHT)

Hand held design/test tool gives instant overview of circuit conditions. Just clip power leads to circuit supply rail - switch to TTL or CMOS and trace logic. Logic levels and pulses through digital circuits. Instant LED readout "Hi" "Lo" and blinking pulse detector.

LM1 - LOGIC MONITOR

(Illustrated below) with the speed of light, you can check all digital IC'S and get foolproof readouts - self powered tests TTL, COS, DTL and HTL up to 16 Pin DIL. Versatile, fast and accurate. You can even watch your circuits spring to life as signals work effortlessly through.

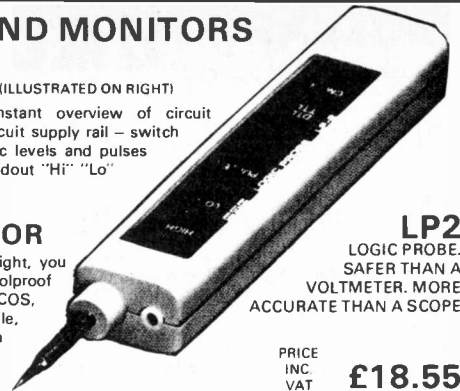


LP2
LOGIC PROBE.
SAFER THAN A
VOLTMETER. MORE
ACCURATE THAN A SCOPE

PRICE
INC.
VAT **£18.55**

PROTO BOARD TEST SOCKETS & BUS STRIPS

Design and build circuits as fast as you can think using the CSC Proto Board solderless-Bread Boards. Unique exclusive snaplock allows expansion to any size. DIP compatible, accepts all standard components. Can be mounted on any flat surface to form a permanent design station. All boards are .33" thick.

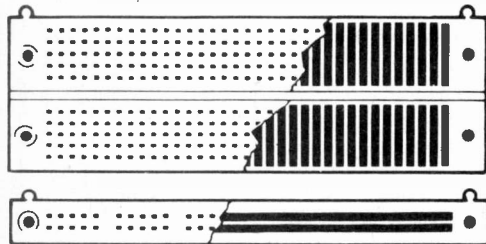
Sockets: Groups of 5 Connected Tie Points



QT-59S
6.5" x 1.3" Socket
£7.75


QT-59B
6.5" x .36" Bus
£1.56

USE YOUR COMPONENTS OVER & OVER AGAIN - NO SOLDERING

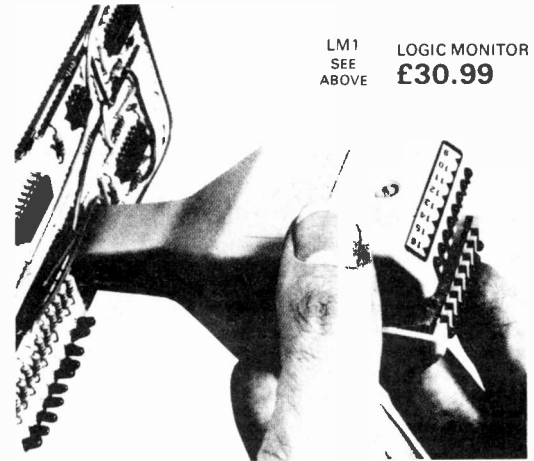

LM1
SEE
ABOVE **£30.99** LOGIC MONITOR

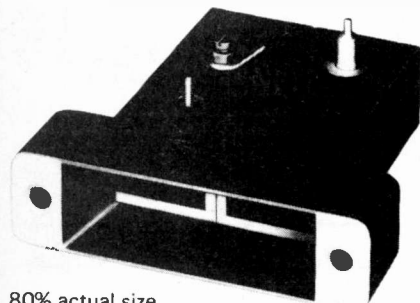MULLARD CL8960 X-BAND DOPPLER RADAR MODULE



80% actual size

TYPICAL APPL.

- INTRUDER ALARM
- MICROWAVE FENCE
- COUNTING
- DETECTION
- INDEXING
- MANY MORE

£25.92
DATA ON
REQUEST

The X-Band doppler module CL8960 is a device designed specifically for detecting movement of a remote target by detecting doppler-shift in microwave radiation reflected from the target. The CL8960 contains a fixed frequency gunn oscillator, which produces the energy to be radiated, and a mixer cavity which mixes the reflected energy with a sample of the oscillator signal.

* Range-feet Man detection (typical)	Supply Voltage (typical)	Running Supply Current (typical)	Output Power (typical)	Centre Frequency
30 to 100	7V (±0.1V)	140mA	8mW	10.687 GHz


PCB MOUNTING KEYBOARD SWITCHES

Digitast is a remarkable new modular electronic switch input component for use with dual in-line packages (DIP). The inner construction, in connection with standard TTL-ICs, eliminates more costly and troublesome conductor plate sandwiched switches.

The contact arrangement also lends itself to economical PC board designs, and assembly techniques of sophisticated electronic equipment.


The single pole, double throw momentary contact element is made of gold-plated over nickel-plated brass. Included in the contact arrangement is a unique bussing contact precluding the need for double-sided printed circuit boards in most cases.

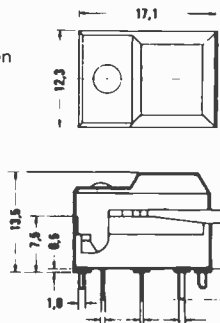SUITABLE FOR MOUNTING ON .1" MATRIX BOARD AND AS USED IN THE **ELEKTOR** SC-MP PROJECT



Standard SPST-SR **£0.95**
or with LED TYPE SRL **£1.65**

SCREW KITS

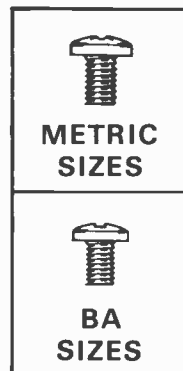

METRIC
SIZES

BA
SIZES

2.5mm Slotted Pan Head Kit **£0.45**

12 Screws 4 x 6mm + 4 x 12mm
+ 4 x 20mm
+ 12 Nuts, Washers and Shakeproof Washers

3mm Slotted Pan Head Kit **£0.45**

12 Screws 4 x 8mm, 4 x 12mm, 4 x 20mm
+ 12 each - Nuts, Washers and Shakeproof Washers

4BA Slotted Round Head Kit **£0.55**

12 Screws 4 each 1/4", 1/2", 1"
+ 12 Nuts, Washers and Shakeproofs

6BA Slotted Round Head Kit **£0.50**

12 Screws 4 each 1/4", 1/2", 1"
+ 12 Nuts, Washers and Shakeproofs

NOW YOU NEED NEVER BE WITHOUT!

3½ DIGIT LCD PANEL METER KITS

these low-cost, easy-to-assemble kits using the new Intersil 7106 A/D converters

Intersil's 7106 is the first single-chip CMOS A/D for driving LCD displays – including backplane – directly. The 7107 is the first single-chip CMOS A/D for driving instrument-size LED displays directly without buffering. Each provides parallel seven segment outputs, ideal for DVMs, DPMs and anywhere modern digital displays are needed. Both new devices provide cost advantages over multi-chip designs, because they require no additional active components. Both have internal reference and clock, and both are CMOS so you get low noise (12 to 15 μ V) comparable with the finest bipolar devices, and low power (10 mW max. @ 10V). A few more features:

- ± 1 -count accuracy over the entire ± 2000 -count range.
- Guaranteed to read Zero for 0 Volts input.
- Provides true polarity at Zero count for precise null detection.
- Differential input from 200 mV to 2.000V full scale.


Kits provide all materials . . .

Including PC board, for a functioning panel meter. **Assembly time is only ½ hour.**

ONLY LCD KIT AVAILABLE. ICL 7106EV(LCD) £26.99.



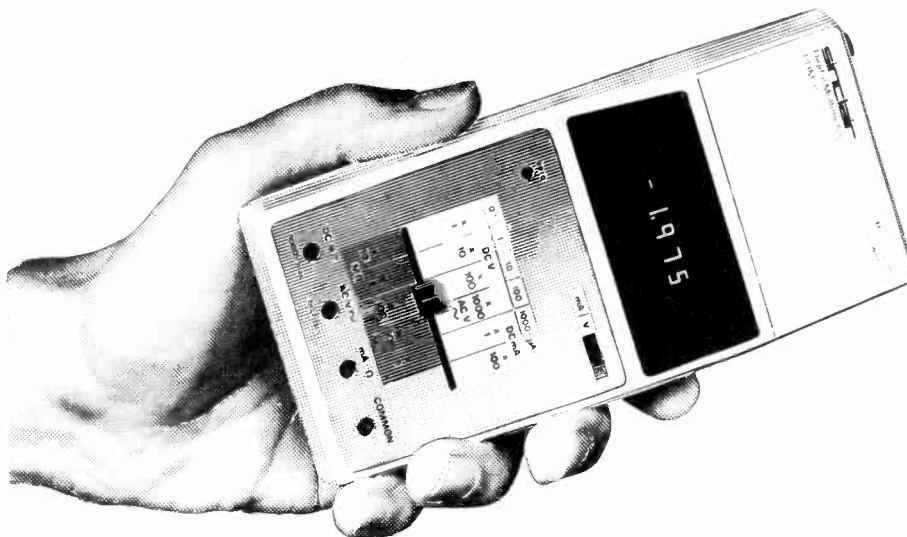The Sinclair PDM35. A personal digital multimeter for only £32.35



Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

What you get with a PDM35

- 3½ digit resolution.
- Sharp, bright, easily read LED display, reading to ± 1.999 .
- Automatic polarity selection.
- Resolution of 1 mV and 0.1 nA (0.0001 μ A).
- Direct reading of semiconductor forward voltages at 5 different currents.
- Resistance measured up to 20 M Ω .
- 1% of reading accuracy.


PDM35 – Meter	£32.35
Padded Carrying Case	£3.00
A.C. Adaptor 240V 50Hz	£3.00

Operation from replaceable battery or AC adaptor.
Industry standard 10 M Ω input impedance.

THE MINI-BLEPTONE 525 £4.05


is an electronic warning device that doubles as a fault indicator or localised warning of fire or intruders. Developed for panel mounting its solid state electronics gives reliability whilst its small size and low current consumption of 3-15mA produce a choice of two signals up to 80dBA. Its wide voltage range ensures operation from almost any transistorised equipment, completing the flexibility of this unit.

Requires 12.7mm (0.5") fixing hole

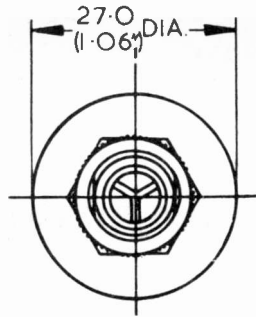

BUZZERS

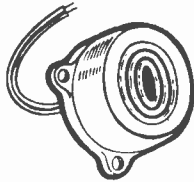VERY LOUD NOTE!
CREAM PLASTIC CASE, 50mm DIAMETER BY 30mm HIGH. THREE FIXING FEET WITH HOLES SPACED AT 50mm AVAILABLE IN



6 VOLTS - PRICE **£0.70**
12 VOLTS - PRICE **£0.83**

CHOKES

- CH1 RF Choke 2.5 mH **48p**
- CH2 RF Choke 5.0 mH **55p**
- CH3 RF Choke 7.5 mH **55p**
- CH4 RF Choke 10 mH **55p**
- CH5 RF Choke 1.5 mH **48p**



COIL FORMERS
1/4" Coil Formers complete
Price **£0.16** each

4mm Coil Formers **15p** each



FUSES & FUSEHOLDERS

1) PANEL MOUNTING

For 1 1/4" (32mm) fuse
Coloured spring-off safety top **£0.38**
Colours available: Red, Blue, White, Yellow



2) PANEL MOUNTING

With see-through cover
For 32mm fuse **£0.20**



3) CAR IN LINE (not illustrated)

Fuse holder takes 1 1/4" fuses **£0.15**

4) PANEL MOUNTING

Fuse Holders for 20mm or 1 1/4" fuses
20mm **£0.32**
1 1/4" **£0.35**




5) PRINTED CIRCUIT MOUNTING FUSE CLIPS for 20mm fuses only £0.05 pair

6) CHASSIS MOUNTING FUSE HOLDERS for 20mm fuses on paxoline £0.10 each

VALUE	FUSES 1 1/4"	
	QUICK BLOW	ANTI-SURGE
100mA	£.06	£.22
150mA	.06	.22
250mA	.06	.13
500mA	.06	.13
750mA	.06	.13
1 AMP	.06	.13
1.5A	.06	.13
2 AMP	.06	.13
3 AMP	.06	.13
5 AMP	.06	.13
7 AMP	.06	.13
10 AMP	.06	.13
15 AMP	.06	—
20 AMP	.06	—
25 AMP	.06	—


VALUE	FUSES 20mm	
	QUICK BLOW	ANTI-SURGE
100mA	£.06	£.22
125mA	.06	—
160mA	.06	.22
200mA	.06	—
250mA	.06	.13
315mA	.06	.13
400mA	.06	.13
500mA	.06	.13
630mA	.06	.13
800mA	.06	.13
1 AMP	.06	.13
1.25A	.06	.13
1.6A	.06	.13
2 AMP	.06	.13
3.15	.06	.13
4A	.06	.13
5A	.06	.13
6.3A	.06	.13

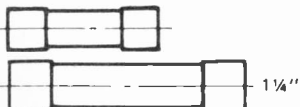

Both 20mm and 1 1/4" fuses are available in quick blow or anti-surge Please specify

PANEL METERS

REF	CAT	F.S.D.
ME1	T21	0-50 UA
ME2	T22	0-100 UA
ME3	T23	0-500 UA
ME4	T24	0-1 MA
ME5	T25	0-5 MA
ME6	T26	0-10 MA
ME7	T27	0-50 MA
ME8	T28	0-100 MA
ME9	T29	0-500 MA
ME10	T30	0-1 AMP
ME11	T33	0-50v.AC
ME12	T34	0-300v.AC
ME13	T35	"S"
ME14	T36	"VU"
ME15	T40	50-0-50 UA
ME16	T41	100-0-100 UA
ME17	T42	500-0-500 UA

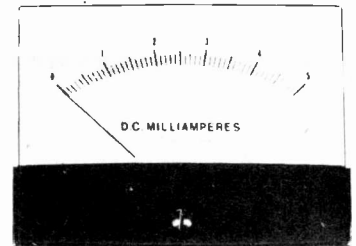


Illuminating Kit
For Above **90p**

PRICE **£4.90** P&P **40p**

DIMS -- 2 3/8" x 1 7/8" x 1 3/8"
REQUIRE 1 1/2" DIA CUT OUT

AVO TEST LEADS

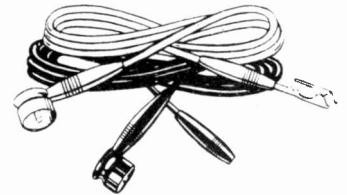AVO TEST LEADS REPLACEMENT. MANUFACTURED FROM HIGHEST GRADE MATERIALS TO GIVE IDENTICAL SPECIFICATION TO ORIGINAL AVO LEADS. ONE CROCODILE CLIP SUPPLIED.



PRICE **£3.75/PAIR**


EXTRAS

TELEPHONE PICK UP
suction action to phone enables conversation to be recorded (3.5mm plug)



EAR PIECE (each) **40p**
EAR PIECE Magnetic **25p**

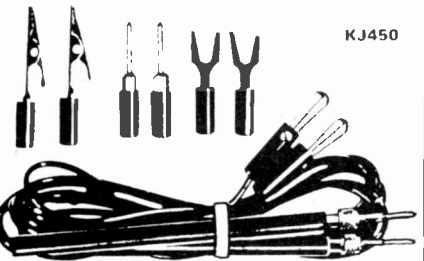
3.5mm PLUGS
TEST LEAD KIT KJ450
Complete with long reach prods - banana plugs, pin plugs, spades and crocodile clips - all push on fittings



PRICE **£1.75** Set

SIGNAL INJECTOR
Model SE250B

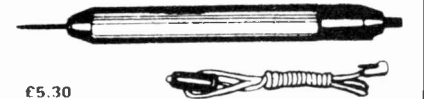
Unusually stable trouble-shooter - for checking TV, Radio, amp. etc. One hand operation - penlight battery. Output approx. 1.4v RP. at nom. 1kc/s + harmonics up to VHF measures 7" x 6"



£5.30

TEST LEADS KIT PN90

Complete luxury kit - curly leads, long reach prods - supplied with quality alternative ends, banana plug, pin plug, Spade terminal and croc clip. PRICE **£3.50/SET**

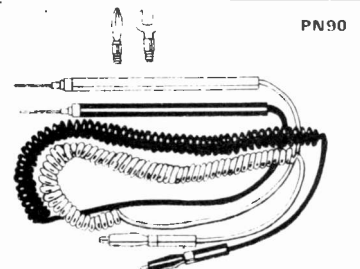

PN90

TEST PRODS

IDEAL EXTRA FOR ANY ENTHUSIAST



SET OF 1 RED 1 BLACK PRICE **£1.55/SET**

A. MARSHALL is your MAN OF MANY PARTS

with components
it pays you to use -



Mullard components

He can give a fast supply from large stocks of all the electronic components you need – the very best components for TV, Radio, Audio and Domestic Appliance servicing. Mullard Components.

It pays to fit a Mullard quality component because its reliability and long service life will save time, trouble, and money. By giving real customer satisfaction Mullard quality is always cheaper in the long run!

Keep up-to-date on all Mullard components with Mullard Component News.

Mullard quality components
- cheaper in the long run

Mullard

Renewal Sales Department
Mullard Limited, Mullard House,
Torrington Place, London WC1E 7HD




Mullard manufacture and market electronic components under the Mullard, Philips and Signetics brands.



INDEX

DESCRIPTION	PAGE	DESCRIPTION	PAGE	DESCRIPTION	PAGE	DESCRIPTION	PAGE	DESCRIPTION	PAGE
Aerial Plugs	29	Coil Formers	38	Indicators – Numerical	5	Pliers	35	Sockets Wire Wrapp	24
Aerosols	33	Conditions of Sale	2	Panel Mounting	5	Plugs & Sockets	28, 29	Solder	27
Audio Connectors	28, 33	Cordless Iron	26	Instrument Cases	24, 25	Portable Digital Meters	3, 37	Soldering Irons	26, 27
Audio Modules	35	Clock Module	4	Isotip Irons	26	Potentiometers	22	Sprays	33
Battery Holders	33	Crimping Tool	35	Jack Plugs & Sockets	28	Presets	22	Switches	30-32, 34
Connectors	29	Crystals	33	Keyboard Switches	36	Printed Circuit Pen	27	Terminals	28, 29, 35
BNC Connectors	29	Dalo Marker Pen	27	Keystector	35	Board	24	Terms & Conditions	2
Boards – Printed Circuit	24	Data Books	18	Knobs	25	Protoboard	36	Test Leads	38
Boxes	25	Desolder Tool	26	Lamps	33	Push Button Switches	13	Meters	3, 37
Breadboards	36	Diacs	13	L.D.R.s	4	Quick Charge Irons	26	Thermistor	22
Bridge Rectifiers	12	Digital Multitesters	3, 37	L.E.D.s	4, 5	Radar Module	36	Thyristor	13
Bulbs	33	D.I.L Sockets	27	Logic Monitor	36	Rams	16, 17	Toggle Switches	30
Buzzers	38	D.I.L. Relays	32	Logic Probe	36	Rectifiers	12	Tools	35
Cabinets	24, 25	Din Plugs & Sockets	28	Mail Order Facilities	2	Regulators – Voltage	13	Tool Wire Wrapp	24
Cases	24, 25	Diodes	12	Mains Plugs	29	Relays D.I.L.	32	Transformers	23
Cable	23	Displays – Digital	5	Memories	16, 17	Resistors	22	Transistors	8, 9
Capacitors	10-11	Ear Pieces	38	Meters	3, 37, 38	Rotary Variable	22	Triacs	13
Electrolytic	10	Electrolytic Capacitors	10	Mica Capacitors	11	Slider Variable	22	Trimmers	11
Tantalum	10	Enamelled Wire	27	Microprocessors	6, 16-21	Carbon Fixed	22	UHF Connectors	29
Ceramic	10	Eth Resist Pen	27	Microswitches	27	Metal Oxide	22	Unijunctions	8, 9
Polycarbonate	11	Etching Kit	27	Microster	3	Preset Skeleton	22	Valves	35
Metal Film	10, 11	Fans	27	Modules – Audio	35	Neon Linear	22	Veroboard	24
Silvered Mica	11	Fets – Field Effect Trans	8, 9	Modules – Clock	4	Wirewound	22	Verowire	24
Plastic Foil	10, 11	Foot Switch	31	Multimeters	3, 37	Rocker Switches	30, 34	Voltage Regulators	13
Polyester	10, 11	Fuses & Holders	38	Neons	33	Roms	18	Data	13
Polystyrene	10	Heat Sinks	23	Opto Electronics	4, 5	Rotary Switches	31	Volume Controls	22
Variable	11	Compound	33	Coupler	4	Screws	36	Wire	23
Card Frame 19"	24	High Stability Resistors	22	Panel Meters	38	SRC's	13	Wire Wrap Pen	24
Car Clock	4	Illuminated Switch	30	PCB Switches	30-32	Signal Injector	38	Wire Wrap Sockets	24
Chokes	38	Integrated Circuits	16-20	Phono Plugs & Sockets	28	Silicon Grease	33	Zener Diodes	12
Coaxial Cable	23	Sockets	24, 27	Photo Devices	4, 5	Slide Switches	31		
Connectors	29			Pick-up Coil – telephone	38	Sockets	28, 29		

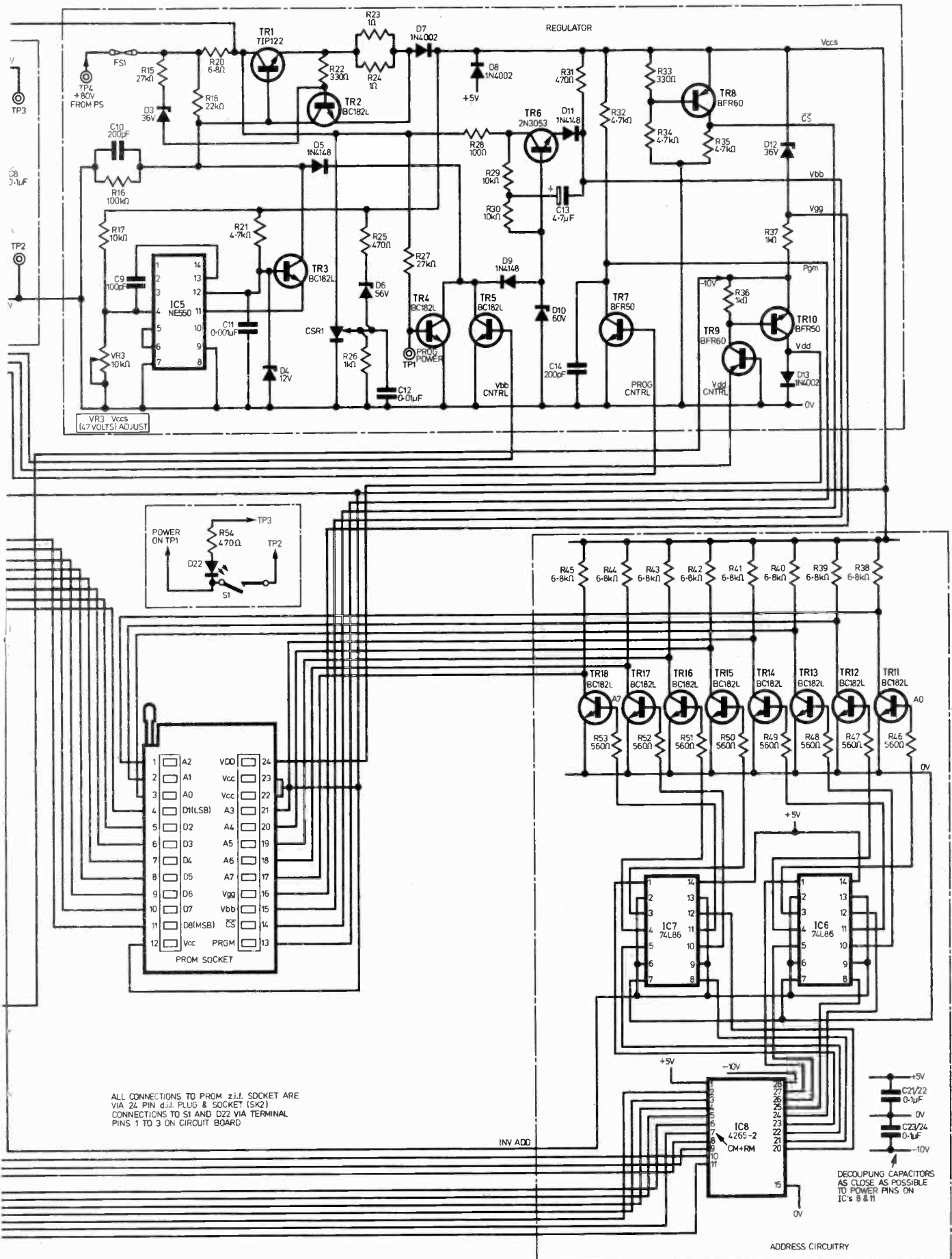

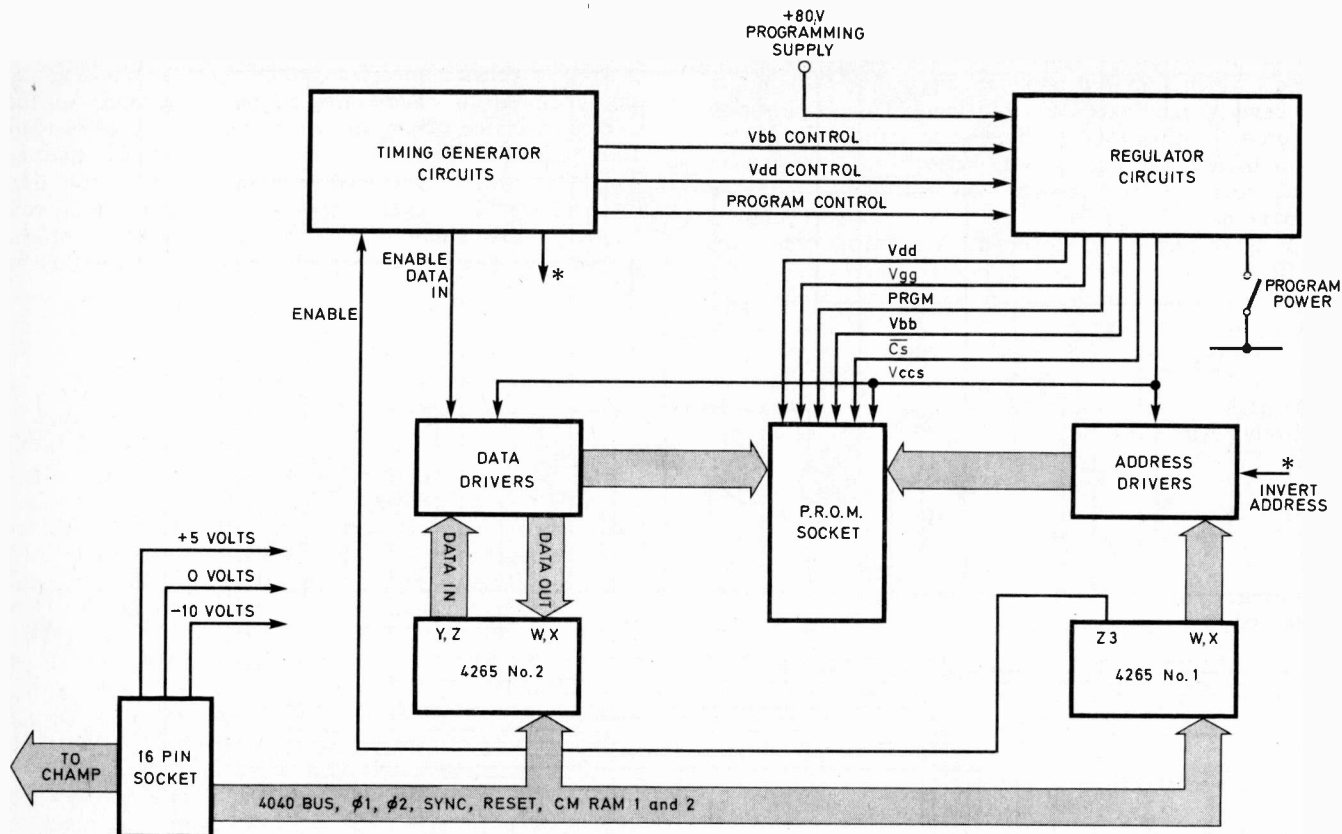


Fig. 8.3. CHAMP-PROG block diagram

that trigger each other continuously in the presence of a logic zero on the output of 4265 Number 1 port Z3. The timing generator produces a 3ms program pulse every 15ms, to give a 5:1 duty cycle, and also provides pulses to enable the program data input, and to invert the address information while Vdd and Vgg are in transition.

Because of the need to control the pulse timings to within tens of microseconds the timing function could not be carried out effectively by the 4040 itself, and so it has to be content with merely controlling the total number of 3ms pulses applied by means of port Z3 of 4265 Number 1. At present about thirty five consecutive pulses are applied, and this is determined by a 540ms software delay controlled by PROMPT. Some commercial PROM programmers operate in a slightly different way in that they provide four times the number of program pulses initially required to program a particular location, and thus adjust themselves to the needs of individual locations, using *less* pulses than CHAMP-PROG for most locations, but *more* for the stubborn ones. This latter technique has the advantage of faster (and some say more reliable) programming, but needs more complicated software. We mention it here in case anyone would care to modify the PROMPT software and try it, but there's no need to worry about this since we have never had a programming failure, and none of our PROMS ever forget! Intel themselves use the fixed duration programming techniques.

CHAMP INTERFACE

As mentioned earlier, all data, address, and control information is passed to and from the CHAMP-PROG circuit over the four-bit 4040 main data bus which is interfaced to two 4265 chips on the programmer circuit

board. Up to four 4265's (including the one on the CHAMP main board) can be used with the basic CHAMP system, one to each CM-RAM line where it will respond to the RAM Chip-Two SRC address, 80H. 4265 Number 1 (IC8) is controlled by CM RAM 1 and is set to mode 4 (four four-bit output ports) as soon as PROMPT is initialised. This chip provides an eight bit address to select a PROM location on ports W and X, and uses output Z3 to control the timing generator. The other outputs are unused. 4265 number two (IC11) is set to mode 6 (two four-bit input ports, two four-bit output ports) and provides the data to be programmed on ports Y and Z, and monitors the data from the PROM between program pulses, using ports W and X. Monitoring the results of a programming sequence is necessary because after programming a location PROMPT checks the data output against the data sent earlier to ports Y and Z, to ensure that they are the same. Any discrepancy results in a program abort and a FAIL message. During programming, the data and address inputs to the PROM must take up voltage levels commensurate with the programming supplies, and so the outputs of the 4265 chips are connected to the PROM via discrete transistor drive circuits and low power t.t.l. gates. The address drivers are fed by 74L86 EXCLUSIVE OR gates which are controlled by the timing generator and used to invert the address information from 4265 number one during the transition period of 60 microseconds.

If you are wondering how the input data is presented to the 4702A when these devices do not have any inputs, the answer is that the data *outputs* are used as inputs during programming.

LED DISPLAY

On the prototype of CHAMP-PROG, an in-line array of l.e.d.s which provided a binary display of data in the PROM being programmed, was provided. This display was very pretty but was later thought to provide little information that was not available elsewhere, and so was deleted from the final version, with the happy result of a gain in noise immunity at the inputs to 4265 number two ports W and X. These l.e.d.s are shown dotted on the circuit and can be used if desired, they do at least provide helpful data during circuit debugging operations!

The output data from the PROM is monitored in a rather unusual way. The emitters of the PROM data line drivers (i.e. TR19) have a resistor in series, and in between program pulses the collector of this driver transistor is effectively "wire-ored" with the PROM output driver. If the stored data is a logic 1, the collector voltage of the driver becomes +5V, and a voltage is developed across the emitter resistor due to the current through the transistor. If a logic 0 is stored however, the driver transistor collector is clamped to zero volts and it turns OFF, therefore no voltage is developed across the emitter resistor. Thus, the emitter resistor voltage is an indicator of the stored data, and this voltage is used to control another transistor (TR27) which provides a 5 Volt logic level at its collector to drive the 4265 inputs and the l.e.d.s if fitted.

TIMING GENERATOR CIRCUIT

The timing generator and voltage regulator sections of Fig. 8.2 are complicated enough to deserve a more complete explanation. IC's 1, 2 and 3 form the heart of the timing generator, and are 74123 (or 74L123 if you can get them) dual monostable circuits. IC1 provides the basic 15 millisecond P.R.F. and is a free running multivibrator which produces narrow negative going pulses at the pin 13 Q output. These pulses trigger IC2a which provides an accurately timed pulse of 3.25ms, its length being adjustable by means of VR1. The leading edge of this pulse triggers IC3a which provides a 155 μ s delay before triggering the actual program pulse monostable (IC3b). IC3b is set to 3.0ms by VR2. IC2b is triggered at the same time as IC3a, and this mono provides a pulse of about 60 μ s to invert the 4702A addresses while the supplies move to their programming levels. Four separate control outputs are produced by the timing generator, and these are buffered by means of 7405 (not low power) open collector inverters before distribution. The timing of these outputs is summarised in Fig. 8.4.

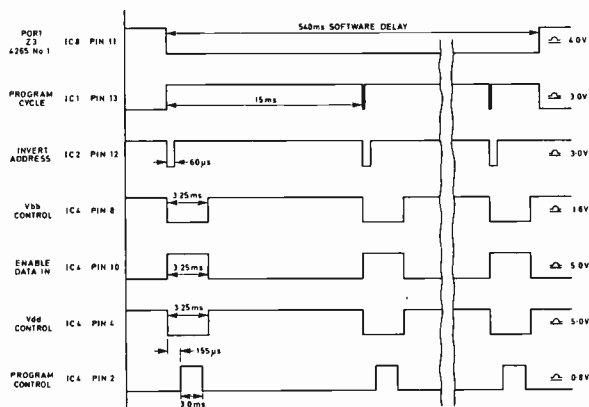


Fig. 8.4. Timing generator waveforms (not to scale)

You may have noticed that two of the 7405 outputs are returned, via 27 k Ω resistors to the +80V rail. This is done to provide superfast switching by minimising the time required to charge the wiring capacitance to the voltage regulator switch transistors, but the use of 80 volts does mean that these outputs should *never* be disconnected from their following transistor stage (during circuit testing for example), because the 7405 would be destroyed. Under normal circumstances the clamping effect of the base-emitter diode of the switch transistors makes the use of an 80V supply quite safe.

VOLTAGE REGULATOR CIRCUIT

The heart of the +47V regulator circuit is formed with IC5, TR3 and TR1. IC5 is a 14-pin 200mA regulator chip type NE550, similar to the more common LM123, and this device is used to provide the basic voltage reference and error amplifier functions required by any regulator circuit. The output of this chip controls the collector current of TR3, which has its base clamped to +12V by D4 and operates in the unusual "common base" mode. The collector load of TR3 is returned to the +80V supply rail, and the collector itself drives the base of TR1, which is the device which forms the "business end" of the regulator. TR1 has 80V at its collector, and during programming provides a +47V output at its emitter whilst passing current pulses of up to 0.5A. Obviously this is a demanding job, and the transistor chosen is a Texas TIP 122 monolithic darlington with a 100V 5A specification, and a current gain of at least 1,000 at 3A. The output voltage of the regulator is sensed at the cathode of D7 via a resistive divider, R17 and VR3, and is fed to the non-inverting input of the error amplifier in IC5. VR3 is of course used to set the output voltage to the required 47.0V.

PROTECTION

A double measure of protection is provided by the regulator circuit. TR2 acts as a current limiter when turned on by a voltage drop across R23||24 (0.5 ohms) which exceeds its Vbe threshold, thus diverting TR1 base current which clamps the output current to a level low enough to prevent destruction of the regulator during short-circuits. CSR1 and D6 act as a crowbar over-voltage protection circuit to prevent damage to other regulator components on the PROM being programmed should TR1 ever fail. On the appearance of a potential in excess of about 56V at the cathode of D7, D6 turns on and triggers CSR1 causing it to short out the 80V supply via R20 and blow FS1 (1A). A ruthless procedure perhaps, but without doubt the simplest and neatest way to disconnect supplies in an emergency!

Transistor TR6 and D10 form the other 60V regulator circuit, and in this case a simple Zener/emitter follower combination is all that is necessary.

SWITCHING CIRCUITS

Up to now I have referred to the regulators as though they were standard d.c. circuits, but of course they are not, because pulsed operation is necessary for proper programming. Both regulators are turned off by means of the clamp transistor TR5 which when not turned off itself by means of the 3.25ms Vbb CNTRL pulse from the timing generator, conducts to clamp the bases of TR1 and TR6 to a low voltage so that they cease to function.

COMPONENTS . . .

Resistors

2 off 1Ω 1W 5%	R23, R24
1 off 6.8Ω 5W 5%	R20
1 off 100Ω 1W	R28
8 off 100Ω	R63-R70
2 off 330Ω	R22, R33
11 off 470Ω	R10, R25, R31, R87-R94
8 off 560Ω	R46-R53
14 off 1kΩ	R4, R7, R12, R26, R36, R37, R71-R78
2 off 2.7kΩ	R6, R8
7 off 4.7kΩ	R1, R2, R14, R21, R32, R34, R35
24 off 6.8Ω	R38-R45, R55-R62, R79-R86
3 off 10kΩ	R17, R29, R30
1 off 12kΩ	R9
1 off 22kΩ	R18
6 off 27kΩ	R3, R5, R11, R13, R15, R27
1 off 100kΩ	R16

All resistors $\frac{1}{2}$ W 2% unless otherwise stated, R87-R94 are optional i.e.d. resistors

Potentiometers

1 off 10kΩ 20 turn min preset	VR3
2 off 50kΩ 20 turn min preset (Doram)	VR1, VR2

Capacitors

1 off 100pF polyester	C9
2 off 200pF polyester	C10, C14
1 off 0.001μF ceramic	C11
2 off 0.01μF	C3, C12
9 off 0.1μF disc ceramic (2 for IC8 and 2 for IC11)	C1, C8, C15, C18, C20-C24
1 off 0.47μF ceramic	C6
2 off 1μF	C4, C5
1 off 2.2μF/35V tant bead	C2
1 off 4.7μF/35V tant bead	C13
4 off 22μF/25V tant bead	C7, C16, C17, C19

Diodes and Rectifiers

5 off 1N4148	D1, D2, D5, D9, D11
3 off 1N4002	D7, D8, D13
1 off 12V zener 1W	D4
2 off 36V zener 1W	D3, D12
1 off 56V zener 1W	D6
1 off 60V zener 1W	D10
8 off Min red i.e.d. (optional)	D14-D21
1 off Front panel red i.e.d.	D22
1 off Thyristor 400V/4A	CSR1

Constructor's Note

The zero insertion force 24-pin PROM socket (Type 2, part No. 224-3344-00-0602) is available from:
B.F.I. Electronics, Sinclair House, The Avenue, West Ealing, London W13.

In parallel with TR5 is TR4, and this transistor is capable of the same clamping action, but in this case it is controlled manually by means of the PROGRAM POWER switch on the front panel.

PROGRAMMING SUPPLIES

The other active components, TR7, TR8, TR9 and TR10 are used to generate the required PRGM, Cs, Vgg and Vdd voltage pulses from the "raw material" provided by the 47V Vccs line, the +5V line and the -10V line. The full complement of program voltage waveforms is shown in Fig. 8.5, and no doubt most readers will be able to see for themselves just how these are generated by the circuit. The Vccs line actually switches between +5V and +47V, and D8 provides the clamping action to maintain the +5V level in the absence of program pulses. Notice also that the 3.0ms PRGM pulse itself is actually a negative going waveform (+47V to 0V).

Transistors


1 off TIP122	TR1
28 off BC182L	TR2-TR5, TR11-TR34
1 off ZN3053	TR6
2 off BFR50	TR7, TR10
2 off BFR60	TR8, TR9

Integrated Circuits

3 off 74123 or 74L123	IC1-IC3
1 off 7405	IC4
1 off Signetics NE550	IC5
2 off 74L86	IC6-IC7
2 off 4265-2	IC8, IC11
2 off 74L00	IC9, IC10

Miscellaneous

PROM socket 2, which is a 24-pin d.i.l. low profile p.c.b. type. Also a 24-pin d.i.l. header plug and suitable miniature flexible wire to form a loom.
Zero insertion force 24-pin PROM socket.
Fuse holder (p.c.b. type) and 1A fuse.
Reel of Kynar wire or similar
Piece of VB24 Veroboard cut to 88 holes × 160mm.
Soldercon pins (approx 200).
Terminal pins (0.1 inch).
One single sided 16-way d.i.l. low profile p.c.b. socket, complete with two 16-way d.i.l. header plugs joined by a 16-way ribbon cable to form a link between CHAMP and CHAMP-PROG, approx. 300mm long.
Fine 4BA plastics pillars cut to 20mm and glued to p.c.b.
Thin clear perspex sheet 650 × 220mm (to be fastened to pillars).

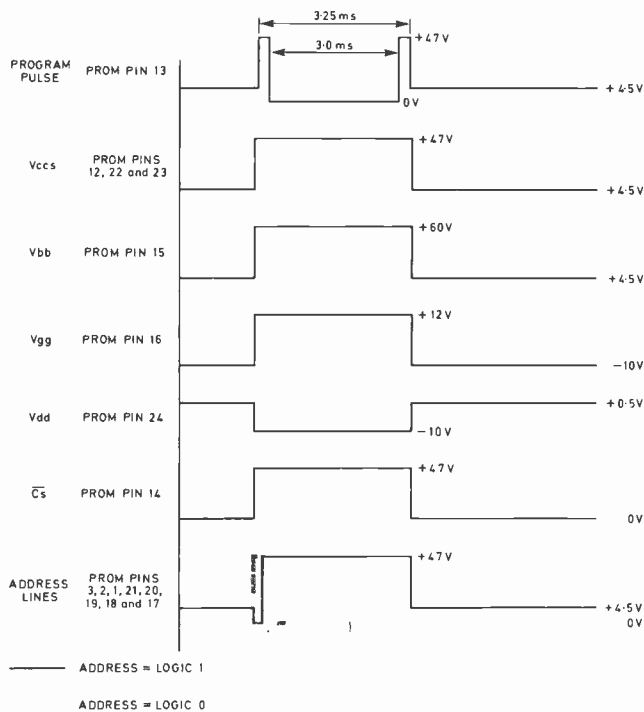

SUCCESSFUL

CHAMP-PROG has proved to be a really useful addition to the CHAMP system, and the prototype has been used to program a total of more than 50 PROMS of mixed origin without a failure.

Intel 4702A and 1702A devices have been tried together with low cost surplus devices of unknown origin, and CHAMP-PROG has coped with them all. Anyone who has tried to develop their own software while using the CHAMP "postal programming service" will know just how expensive and unsatisfactory this can be. CHAMP-PROG will enable CHAMP programmers to be completely independent in their activities, and consequently very productive! ★

NEXT MONTH: CHAMP-PROG construction and PROMPT

A number of Intel MCS-40 User's Manuals and 4004/4040 Programming Manuals are held by P.E. at Poole, which we are willing to give away in sets on a "first come first serve" basis to anyone supplying a strong 11 x 13 inch s.a.e. with 54p stamp (67p 1st class).

Fig. 8.5. Address lines and regulator circuit outputs during program pulse

NEWS BRIEFS

Ring A Rig

COULD a worker on a North Sea oil rig 150 miles north-east of the Shetlands, pick up a normal telephone and dial directly to anywhere on the mainland? The answer is yes! Thanks to a £5 million top priority Post Office project, even the most distant oil platform, Thistle "A", came into the telephone network last November, giving workers there a telephone dial capable of calling 355 million phones in 67 different countries, just like subscribers on the mainland!

Over the next 15 months there are a number of platforms still to be linked into the system, known as the technique of trans-horizon radio, and which has never before been used by the PO. It all relies on the tropospheric scattering of microwave frequencies normally used for line-of-sight communication, but which are still visible to aerials far beyond the horizon. Turbulence in the troposphere (Earth's lower atmosphere) will cause this "fringe" of radio signals in much the same way as the glow from a distant searchlight might be seen, even when the beam itself is out of sight.

A powerful signal is beamed in the direction of the production platform, and a signal reduced in strength by something in the order of $1/10^{10}$ will reach the directional aerial waiting for it.

The control station is located near Fraserburgh, Aberdeenshire, and two relay stations are sited on South Shetland. Two separate troposcatter paths link land to a pair of platforms up to 30 miles apart, which are linked to each

other by line-of-sight microwave. This completes the triangle for alternative path operation, giving high service reliability.

Traffic Computer

NOT all drivers in the Leicester area will realise that they are being told what to do by a computer, and have been since the Leicester Area Traffic Control Scheme became operational in October 1974.

The traffic plan swung into action with 96 traffic signals and Pelican crossings linked to a central computer via Telecommand/5 remote control systems, built by Plessey Controls Ltd of Poole, Dorset. As additional urban area signals were installed, they too were connected to the computer, bringing the total to 128 signals with expansion capability to 192.

Some of that spare capacity is now being used with an extension of the traffic control system to Loughborough, 11 miles away. Fourteen extra signals, including 7 on the A6, will spread the improved traffic flow situation, which was found in Leicester to give a 12 per cent decrease in delays to general traffic, and save travel time to buses of about 6 per cent during peak periods. There are now also 53 special detectors continuously relaying traffic information.

The Leicester Control Centre monitors both cities, where consoles comprising VDUs, closed circuit television, and a large mosaic map showing the condition at each intersection can be used to call up reserve plans for relieving congestion. Be it caused by a breakdown, an accident or any other unexpected event, the use of a reserve plan will activate a warning light at the appropriate point on the mosaic map. Any predictable problems such as the rush hour or football matches, will be dealt with by one of the computerised traffic plans.

A side-benefit of this system is immediate location of the majority of traffic light faults, and the computer even runs a special program during the night to check out all the signal timings and report any errors.



PATENTS REVIEW

Copies of Patents can be obtained from :
 the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each

NAVIGATION AID

BP 1 484 183

In BP 1 484 183, Shell Internationale of the Hague, describes an interesting electronic movement sensing system for a ship. The need for a ship's captain to know exactly where he is, at exactly what speed, and in what direction he is travelling is obvious. Previous systems have used fixed master radars on a jetty with transponders on board the ship, or acoustic transducers underneath the ship's hull to set a fix on the sea bed. But transponders are only useful where there is a pair of master radars close by, and operation of the acoustic transducers is often upset by aeration effects under the ship created by the propeller during manoeuvring. The Shell plan is to use a series of sensors along the ship and correlate the information they produce. At the ship's stern, where there is no aeration, a crossed pair of acoustic transducers or laser logs, working on the doppler principle, are mounted.

Element (5) provides a longitudinal speed signal and element (7), lateral velocity. At the side, amidships, there is mounted a rate of turn transducer, which can work on the tuning fork, gyroscope or laser principle.

A processor (12), has three inputs, one for the longitudinal speed signal, one for the rate of turn, and one for the lateral speed. The first signal, longitudinal speed, is amplified, and fed to a servo system to provide direct readout of forward/aft velocity. The rate of turn signal is amplified and fed both to a servosystem for direct read-out, and also to an operational amplifier 20, with three preset potentiometer positions. These represent the stern, midship and bow of the ship, and serve to introduce into the rate of turn signal the three longitudinal components of the distance between the positions on board ship and the location of the velocity transducer. The selected output signal is summed at (32) with the lateral speed signal.

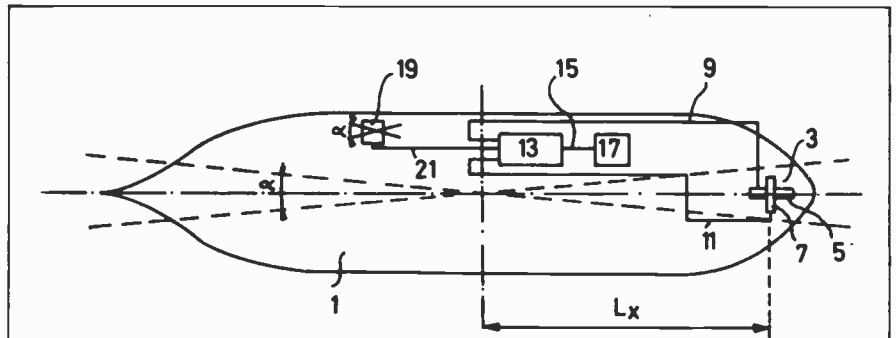


Fig. 1

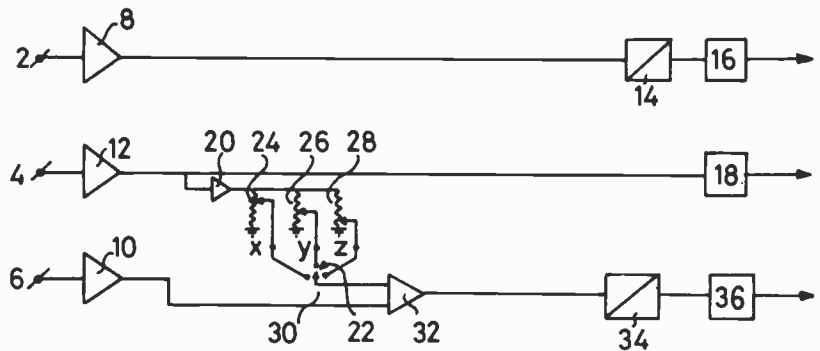


Fig. 2

The captain switches the presets to provide a signal representative of the absolute lateral velocity at the stern, midship or bow station. The claim is that this signal summation technique will, when the midship station is selected, cause any unwanted oscillatory rate of turn signal to cancel any unwanted oscillatory lateral velocity signal. This clever approach permits absolute velocity of the ship to be displayed,

without any need for the signal damping techniques which are normally necessary to obviate high seas motion and so preserve readability of the data display. Damping is of course undesirable because it reduces accuracy of the display. The algebraic theory behind the invention is detailed by Shell, and it is likely that it would be applicable to private yachts.

Semiconductor UPDATE...


FEATURING : HDSP 6504/6508 MC6875 1435

R. W. Coles

SHOWING THE FLAG


When you are desperate, it is possible to display a sort of Alphabet on cheap seven segment indicators, but be warned that the resulting mixture of upper and lower case, with a few inverted letters like M and W, is usually quite unintelligible to the uninitiated! There can of course be excellent reasons for using this revolutionary new kind of script, and you will discover the most important of these when you examine the cost of buying and driving a multi-character, true alphanumeric, i.e.d. dot matrix type of display. A very sobering experience indeed! At this point you either have to resign yourself to that weird new alphabet that you invented or, if you need a lot of characters, you can deprive the family of "Kojak" and rewire the family T.V. set as a V.D.U. (This solution will cost you about £50 and a couple of front teeth.)

Before you pursue either of these alternatives, cast an eye in the direction of two new displays from Hewlett Packard, the HDSP 6504 and the HDSP 6508, because these may be offering you a compromise too good to miss. The new displays are i.e.d. segment units, but they boast not seven but sixteen segments arranged as a sort of "upended Union Jack" which can handle not just the alphabet, but the full 64 character ASCII set which includes punctuation marks and arithmetical signs.

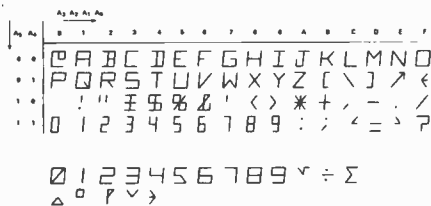

"Union Jack" display fount of the HDSP6504/6508 display

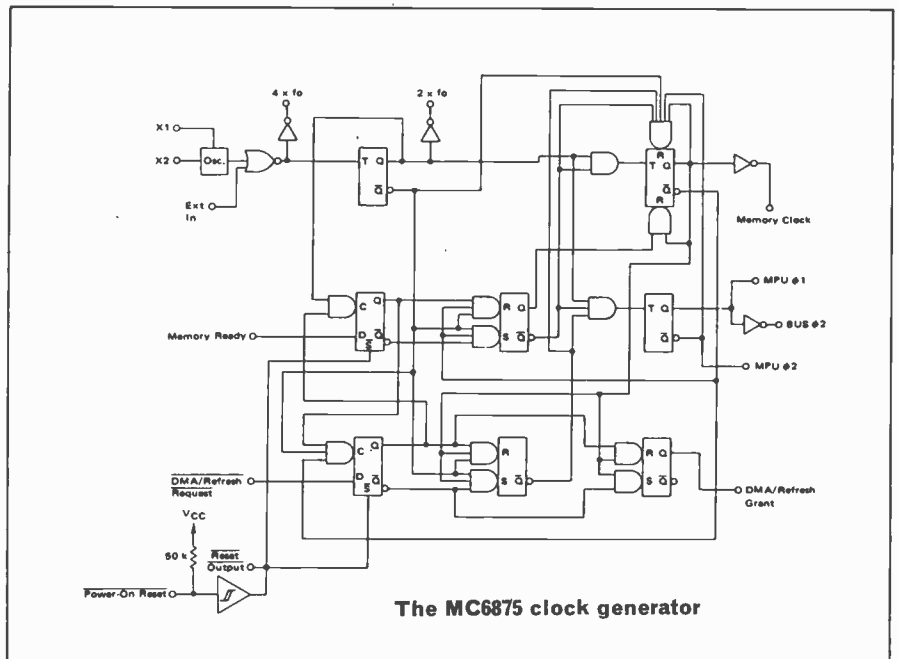Driving these displays is just like driving the seven segment types only more so, a job easily handled by your pet micro-processor using a 128 byte look-up table and a few I/O ports. The "Union Jack" format is not new, and was available in the older gas discharge type of display families, but what Hewlett Packard have



The MC6875 clock generator

done is to put together potentially cheap, multi character display "sticks" of 0.15 inch character height, which are almost as easy to drive as any other multiplexed i.e.d. display. The 6504 has four characters, and the 6508 has eight, and these may be used together and stacked end to end to give a line of any reasonable length. The availability of these displays gives us a viable alternative to the v.d.u. where only a single line of data is really needed, or where space is a problem.

CHEAPER CLOCKS

Anyone who uses the 6800 micro from Motorola is probably very pleased about the easy-to-use, 5 volt operation of their system, but perhaps not so pleased about the requirement for an external clock generator in not-so-cheap hybrid form. This requirement probably wouldn't bother anyone using a ready made system, but when you want to put together a dedicated system, like an electronic door bell, low cost is vital and an on-chip clock can save a lot of money. Well, I can't offer a new 6800 with an on-chip clock, but Motorola

have made it possible to build a cheap off-chip clock, by introducing the MC6875 monolithic clock generator. This chip can be used instead of the existing hybrid module designs MC6870A, MC6871A, and MC6871B, and offers other advantages like a built in power-on reset circuit and logic for implementing various DMA (Direct Memory Access) schemes. The hybrid modules did have the unique advantage of an internal crystal, whereas the MC6875 requires a separate crystal, but the new device is more flexible because it can be used over a wide range of frequencies, and for ultra low cost designs the crystal can be replaced by a simple RC network.

The new chip makes possible the use of sophisticated DMA schemes and dynamic RAM refresh systems with a 6800 processor, because in addition to the clock and reset logic the MC6875 contains circuitry to stretch clock cycles on demand. For this purpose a DMA/REFRESH REQUEST input and a DMA/REFRESH GRANT output are provided. The chip uses high speed Shottky t.t.l. logic and is housed in a 16 pin ceramic d.i.p.



PE STRING ENSEMBLE

A. J. BOOTHMAN B.Sc.

Part 2

entire compass of a piano keyboard. The bottom note (C_2) is approximately 130Hz whilst the top note (C_7) is approximately 2.1kHz.

This register is available in string voicing only and is called "String II".

Returning to the theory of organ registers, the use of a longer open pipe, approximately 16ft in length, produces an octave lower at 33Hz, which from Fig. 2.1(a) can be seen to be the bottom C (C_1) on a piano. Again using a shorter 49 note keyboard, the range produced from a 16ft register is C_2 at approximately 65Hz to C_6 at approximately 1.05kHz with middle C (C_4) exactly half-way up the keyboard. This 16ft register shown in Fig. 2.1(c) is available in string, woodwind, and brass voicing and is the fundamental orchestral register (I) used in the String Ensemble.

LOWER KEYBOARD SPLIT

With the "Couple" push button control depressed all 49 notes give a continuous range, at either 16ft (I) or 8ft (II), for the voices selected on the Upper Voice sliders. However three further push buttons allow the keyboard to be split such that the lower 16 notes are independent of the upper 33 notes.

Fig. 2.1(d) indicates the "String I" button depressed, and under these conditions the upper 33 notes remain under the control of the sliders, whilst the lower 16 notes convert to 16ft (I) strings only.

The lower range is C_2 to E^b_3 at approximate frequencies between 65Hz and 156Hz. Depression of "String" (II) converts the lower section to 8ft, ranging from approximately 130Hz to 311Hz (C_3 to E^b_4), Fig. 2.1(e), now converting middle C (C_4) into the left hand, in addition to remaining within the compass of the 16ft (I) setting, Fig. 2.1(c), of the upper section of the keyboard which is played by the right hand.

The "String III" push button converts the lower section to 4ft pitch (C_4 to E^b_5), which as shown in Fig. 2.1(f) commences at middle C on the piano compass and it can now be seen that the lower section clearly rises in register above the middle of the upper keyboard section, with a fundamental range of approximately 261Hz to 622Hz.

THE Tone Generator system described last month provides up to 96 square wave frequencies, 85 of which are used in the String Ensemble to facilitate a number of combinations of register for both hands, and up to three even harmonics above the fundamental over the entire keyboard range.

For simple reference in playing the instrument I, II and III indicate the register of the fundamental range of each control, and equate to the organ terminology of 16ft, 8ft and 4ft respectively.

FOOTAGES

The use of the term "footage" arose in organ parlance due to the length of pipe required to produce a particular fundamental frequency. An open pipe approximately eight feet long produces 65Hz, which is two octaves below middle C on a piano, and on a classical organ with a 61 note manual the range would extend for five octaves to three octaves above middle C (261Hz) up to approximately 2.1kHz, and this would be known as the 8ft pitch, normal pitch, or 8ft register. A spinet type of organ, which is the format normally employed in entertainment type organs uses either 49 note or 44 note keyboards, and in the 8ft register of the upper manual maintains the same number of octaves above middle C, with a reduced number of notes below middle C.

The String Ensemble follows the recognised practice for the latter type of organ and it can be seen from Figs. 2.1(a) and 2.1(b) how the 8ft register relates to the

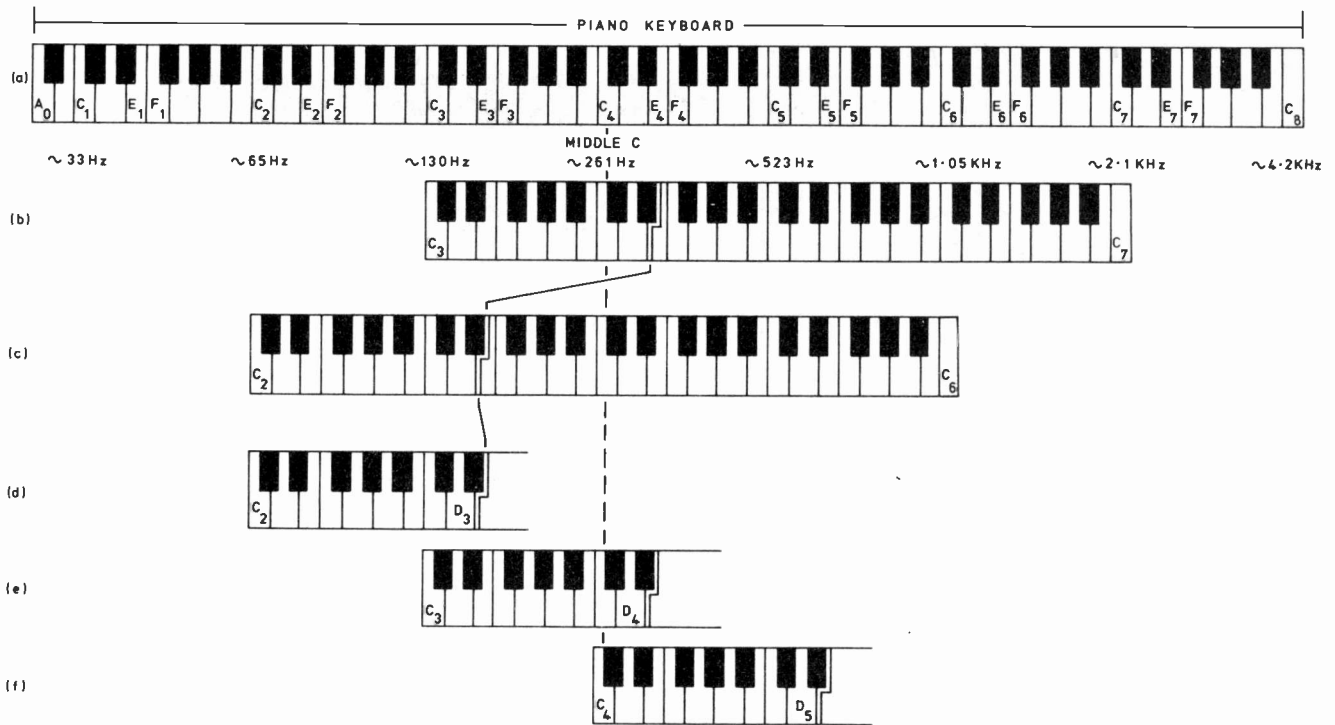


Fig. 2.1. Keyboard registers of the String Ensemble relative to a piano compass (a) Piano compass (b) Ensemble 8ft register—"String II" (c) 16ft register (String I, woodwind and brass) (d) Lower keyboard split—16ft "String I" depressed (e) Lower keyboard split 8ft String II depressed

ADDITIONAL FREQUENCIES

The highest fundamental frequency shown for the instrument is indicated in Fig. 2.1(b) as approximately 2.1kHz (C₇). Frequencies up to approximately 8.4kHz are available from the Tone Generator system and these are used to give additional even harmonics to be described later in association with the voice circuitry.

FREQUENCY SWITCHING

The switching of the large number of frequencies, including harmonics, described above is complex by traditional means in which direct signal keying by multi-

mechanical contacts has been used. Many modern electronic organs simplify this problem by the use of electronic keying utilising diode, transistor, or integrated circuit elements with single mechanical contacts.


Diode keyswitching has been adopted in the String Ensemble.

DIODE KEYING

Switching of the Tone Generator frequencies through to the voice circuits is accomplished by diode gating circuits shown in Fig. 2.2. One circuit within the shaded area is required for each note of the keyboard such that whilst that key is down four octave related square waves corresponding to the note concerned, are switched independently onto busbars identified as 16ft, 8ft, 4ft and 2ft.

SHAPING FOR ATTACK

On depression of the key the moving keyswitch makes contact with a keyswitch rod which is at a positive potential thus charging C13 via R5 with a relatively slow time constant to simulate the slow attack of a string section. The keyswitch rod receives its potential via a slider potentiometer VR6 which further slows the charging rate of C13, and the optimum string attack rate is chosen to coincide with VR6 in its mid position.

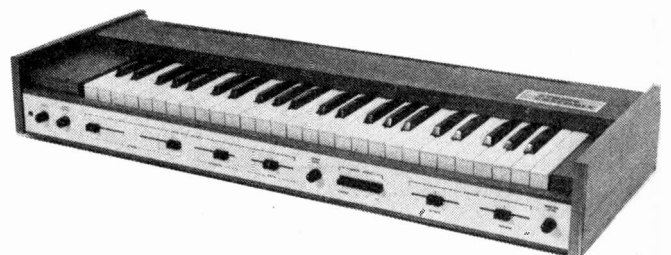

COMPONENTS . . .

DIODE GATES (49 required)

Resistors

- R5 3.3k Ω (49 off)
- R6-R13 120k Ω (392 off)
- R14 10k Ω (49 off)
- ¼W 5% carbon film

Capacitors

- C13 4.7μF elect. 25V (49 off)

Potentiometers

- VR6 10k Ω linear slider
- VR7 4.7k Ω log slider

Diodes

- D14-D22 1N4148 (441 off)
- D23-D30 1N4148 (8 off)

Miscellaneous

- 3 printed circuit boards
- 49 note keyboard (Italian style) with set of keyswitch components—(Clef Products)

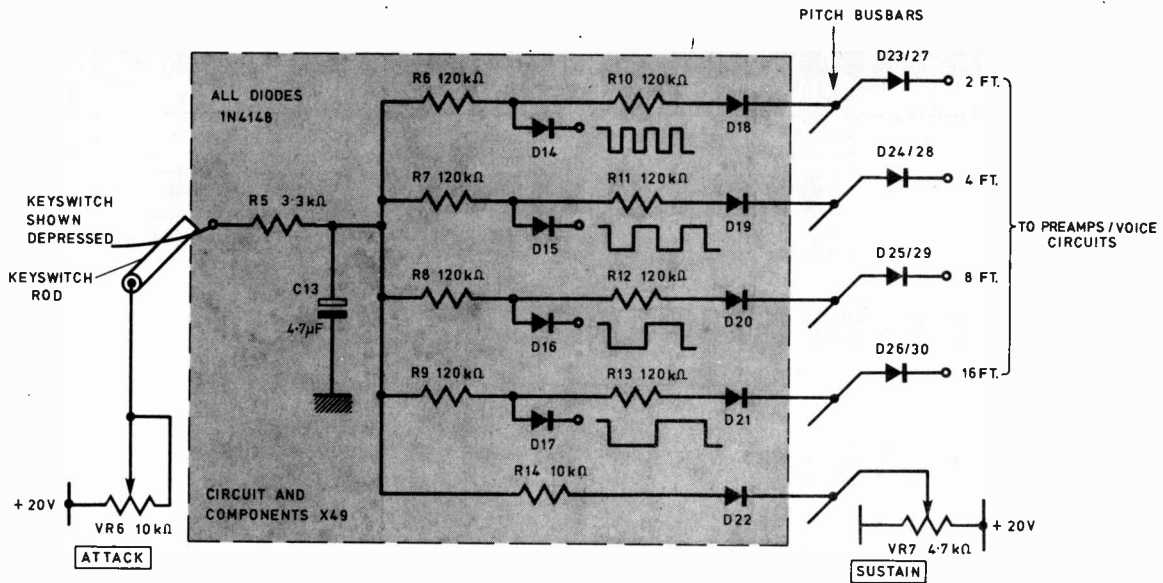


Fig. 2.2. Diode gating circuits

This simple "Attack Control" produces a degree of automatic levelling of the overall output as the number of notes depressed changes which is useful in simulating the smooth flow of the string section, but the slowest attack position can introduce the effect to an excessive degree, whilst in the fastest attack position the keyboard section is fully additive.

SUSTAIN

When the key is released the capacitor C13 is discharged at a rate dependent on the time constant of C13 coupled with the combined effect of resistors R6-13, which are eventually grounded via terminating resistors on the busbars, but modified by the effect of R14 which is returned via D22 to a potential set on slider potentiometer VR7. When the potential is high it is isolated from C13 by D22, but when VR7 is at minimum potential (0V) the low value of R14 dominates over the R6-13 combination to produce a short sustain. As the potential from VR7 is set at an increased level, the domination of R14 ceases when the falling potential on C13 approaches that on VR7 such that the longer time constant associated with R6-13 comes in earlier giving an overall increased length of sustain.

The resulting envelope shapes available are shown in Fig. 2.3, indicating the variations possible from the mid position each of the slider potentiometer controls.

TONE SWITCHING

The required octave related square waves for a particular note are connected to the cathodes of D14-17, and have amplitudes of approximately 14 volts. Assuming the key is at rest with the keyswitch in the open circuit condition then C13 will be discharged and the junction of R5 and C13 at zero potential. Thus the anodes of D14-17 will also be at zero potential and the reverse characteristics of the diodes will block the Tone Generator signals.

Whilst a positive potential is present on C13 during the envelope generation process, the signals will pull down the voltages on R6-9 via D14-17 allowing signals to pass through R10-13 which are proportional to the envelope amplitude.

BEEHIVE REDUCTION

"Beehive" is the term used to describe the effect of all frequencies in the Tone Generator breaking through into the amplifier circuits in chorus, producing a background level of sound which gives considerable annoyance. There are many routes in a polyphonic instrument by which this can occur, related to screening, cable looming and earthing of the various sub-assemblies, but the first route to consider is the direct transmission of low level tones through the keyswitch system when it is supposedly in its quiescent state.

Diodes D18-22 first isolate each gate from the other 48 such that from the point of view of one signal it does not see the 120 kilohm resistors in all other notes of the same pitch, only considering the terminating resistor at the end of the busbar in determining its final level at the preamplifier. Secondly the diodes block the sum total of signals from the keys depressed feeding back to C13 and providing a small positive potential for the signal to modulate in a supposedly quiescent note. The diodes also

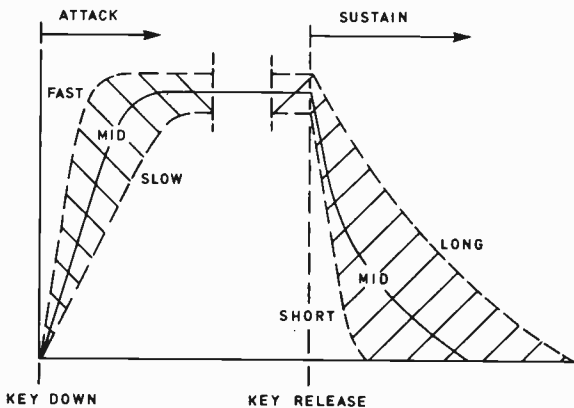


Fig. 2.3. Envelope shapes produced by the Diode Gate circuits

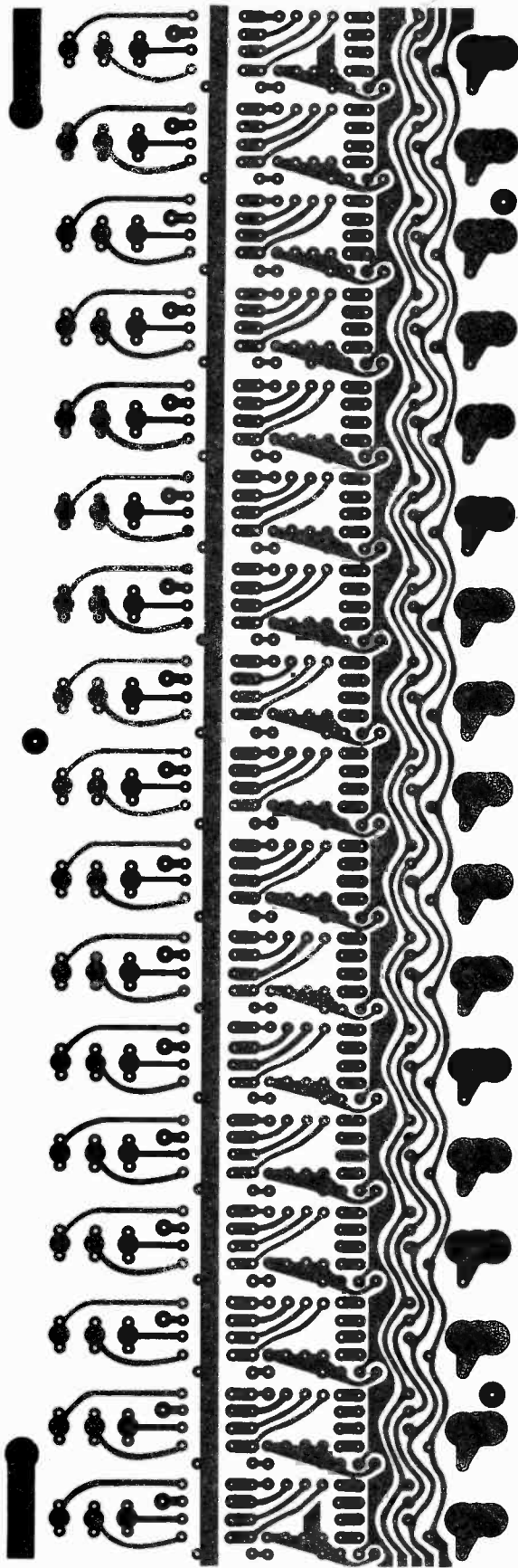


Fig. 2.4. Track layout of Diode Gate p.c.b.


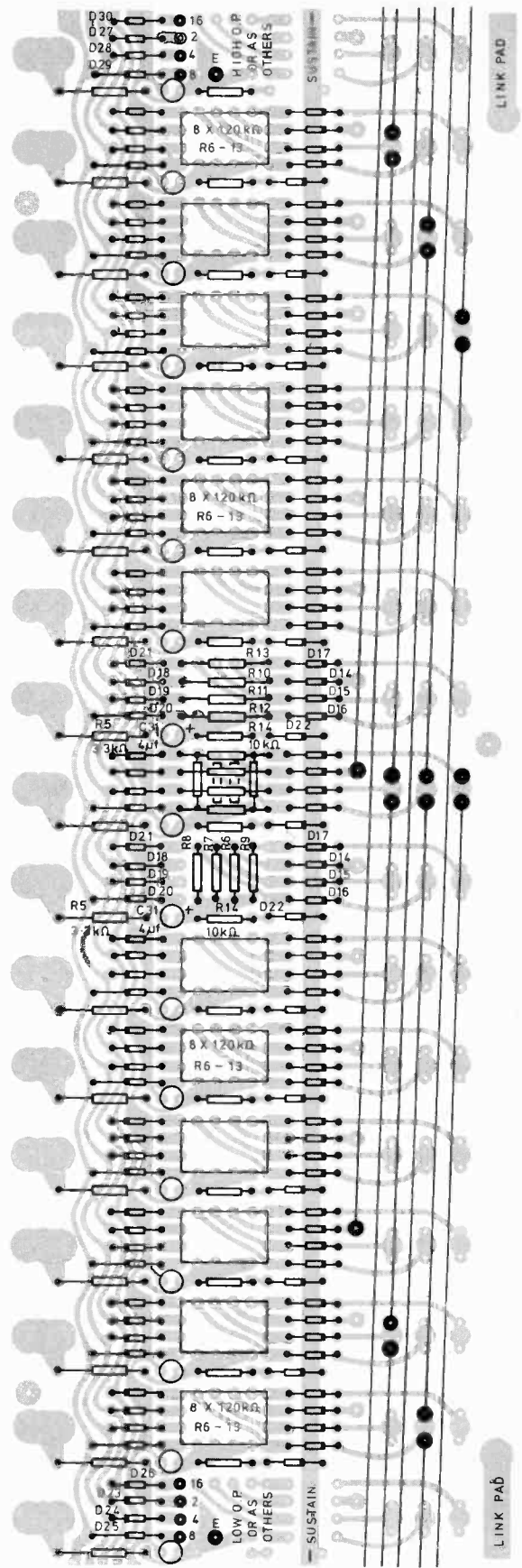


Fig. 2.5. P.c.b. component layout

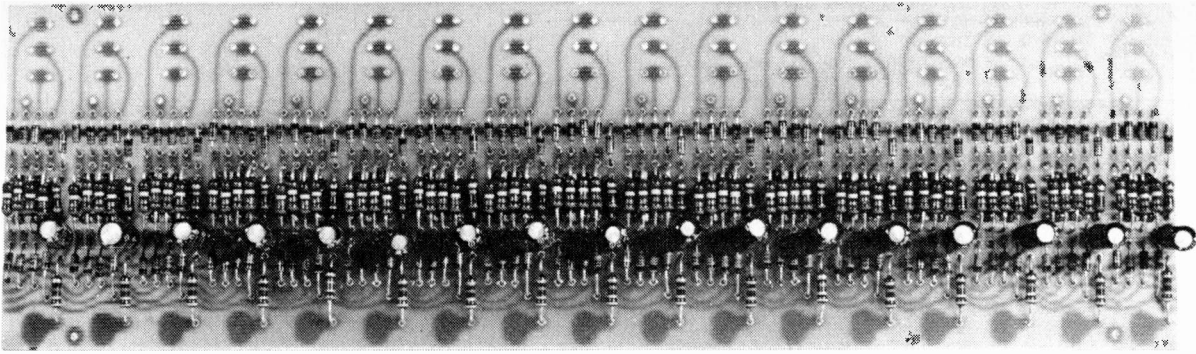

have a high impedance in the forward direction at low voltages to assist the blocking of any small residual voltage on C13, and effectively increase the values of D18-22 in this condition.

Finally it has to be accepted that even when reversed biased D14-17 allow low level spike signals to pass due to internal capacitance, and the small finite stray capacitance of D18-22 further reduces to a small degree the onward transmission of signals from this source.

THRESHOLD DIODES

Even at this stage beehive signals are present on the pitch busbars in the quiescent state and diodes D23-30 are used to further block the breakthrough from reaching the preamplifiers. Since the keyboard is split with two independent sets of outputs from the keyswitch circuits, two sets of threshold diodes are required, D23-26 for the lower section of the keyboard and D27-30 for the upper end of the keyboard.

The overall result is negligible beehive due to transmission through the Diode Gate circuits, and since all signals are in square wave form, with a common baseline potential, the signal harmonic content or distortion level is not modified.

DIODE GATE P.C.B. CONSTRUCTION

All Diode Gate circuits are mounted on three printed circuit boards, the etching and drilling details of which are given in Fig. 2.4, with the component assembly details in Fig. 2.5. The boards are designed to accommodate 49

identical circuits of the type previously described within the shaded area of Fig. 2.2. Since each board has a pattern to cover 17 notes, two are omitted, one at each end of the final three board assembly, and the remaining spaces are used to accommodate the threshold diodes D23-30. Thus in Fig. 2.6 it can be seen that PCB1 is at the lower end of the keyboard and contains 16 notes plus threshold diodes D23-26 on the left hand end, PCB2 contains 17 notes, whilst PCB3 contains 16 notes plus threshold diodes D27-30 at its right hand end at the upper end of the keyboard.

To assemble the Diode Gate p.c.b.s resistors R5, R14 and R6-9 should first be fitted to the board, omitting R10-13 at this stage. All diodes, including D23-30, should then be soldered followed by R10-13, and finally C13. Care should be taken when fitting R10-13, which are mounted across R6-9, that none of the resistor lead ends are positioned such that shorting can occur.

CLOSE INSPECTION

Experience has shown that whilst repetitive soldering of the type involved in this project is easy, ninety per cent of problems occurring in similar projects can be eliminated by *close* physical inspection of the completed p.c.b. The most common fault is to completely miss a solder connection, such that after cropping the waste leads a superficial check on the board indicates that all connections are made. On closer more careful inspection it can then be seen that a component wire is simply passing through a hole without any solder present.

A second possible fault is the creation of a solder bridge

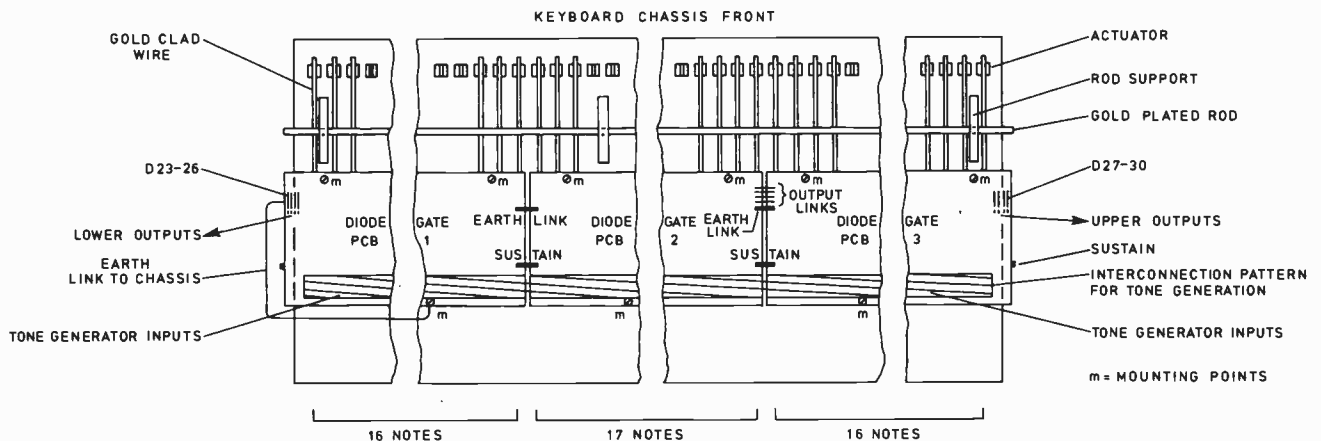


Fig. 2.6. Assembly of Diode Gate p.c.b.s under Veroboard

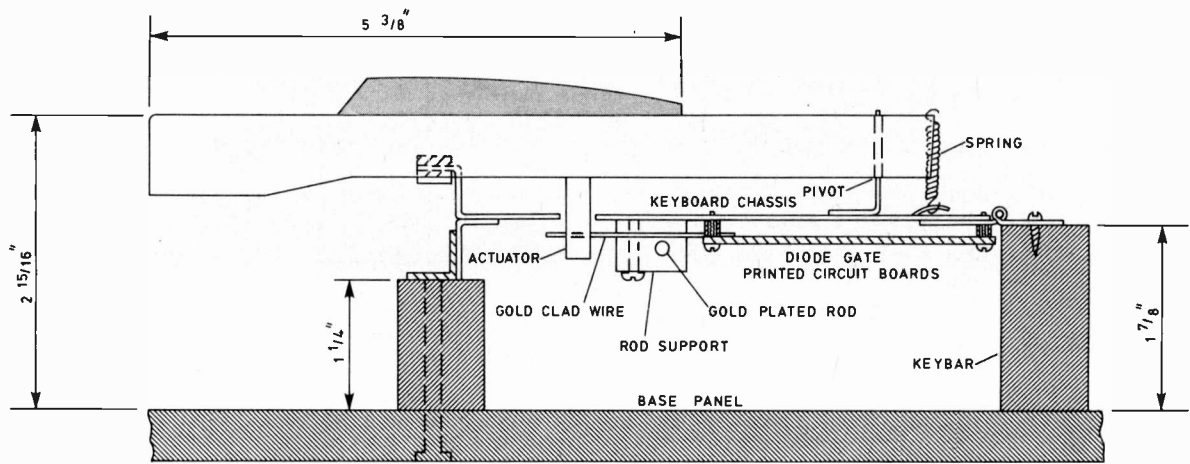


Fig. 2.7. Keyswitch and Diode Gate p.c.b. mounting detail

between two adjacent lands or tracks which again requires careful inspection to detect.

Whilst on the subject of faults the one other error which does occur is the incorrect reading of resistor or capacitor values by factors of ten. Careful attention to these three points in a positive manner leads to a very high degree of complete project success first time when using modern reliable components.

GATE CONTROLS AND P.C.B. MOUNTING

The "Attack" and "Sustain" controls, VR6 and VR7 respectively, are mounted on the front panel at a later stage, and are unnecessary in any tests carried out after assembly of the Diode Gate p.c.b.s and keyswitch.

Referring back to Fig. 2.6 the position of the Gate p.c.b.'s can be seen and before any interwiring is carried out the mounting points (m) for the p.c.b.s can be marked on the keyboard chassis using both Figs. 2.6 and 2.7. Fig. 2.6 also indicates connections between each of the diode gate p.c.b.s.

The interconnection pattern to distribute the signals from the Tone Generator is given in detail later, but it should be noted that earth and sustain links are required both between PCB1 and 2 and between PCB2 and 3. A link should also be made from an earth track to the keyboard chassis to provide an additional screening effect. A further four output links are required between PCBs 2 and 3 which together constitute the 33 notes of the upper section of the keyboard. Outputs for this section are taken from diodes D27-30 and for the lower section from diodes D23-26.

Output footages are marked in Fig. 2.5, with a point E for connecting the four-core cable screen.

KEYBOARD AND KEYSWITCH

The keyswitch action is integrated with the Diode Gate p.c.b.s and consists of gold clad springy wires approximately 2 inches long soldered onto lands provided on the p.c.b.s. Details are shown in Fig. 2.7.


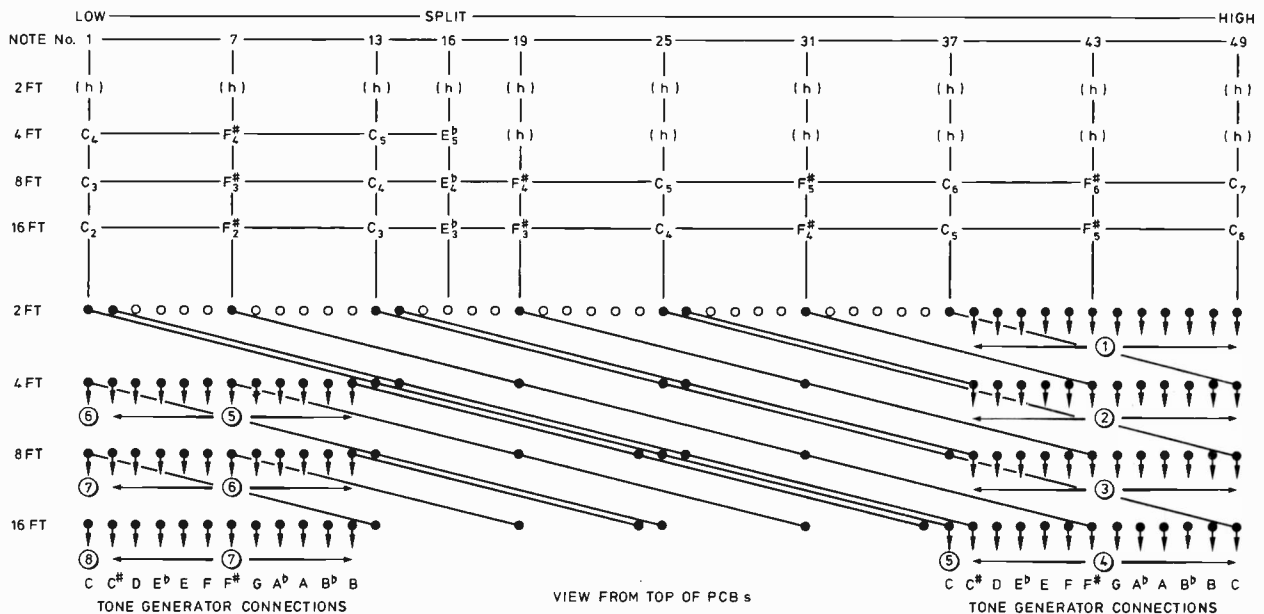


Fig. 2.8. Interconnection pattern for Diode Gate p.c.b. and connections to Tone Generator

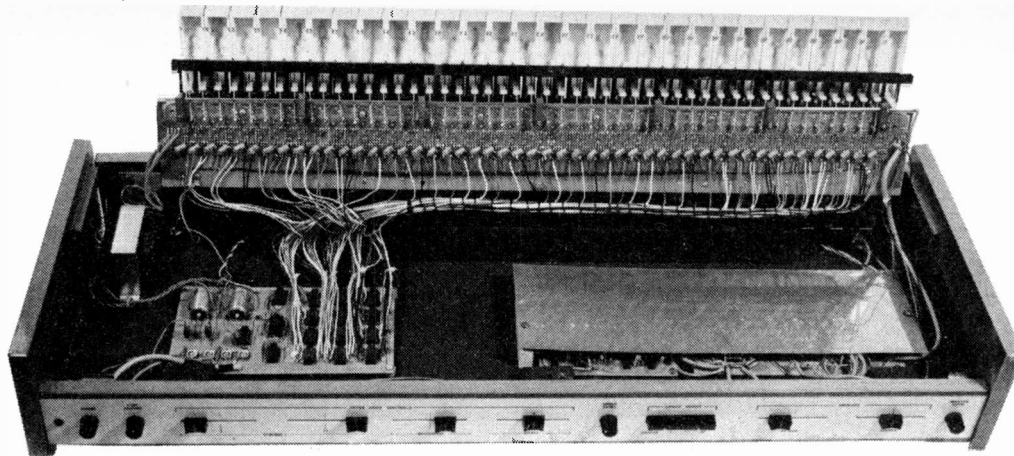

The Diode Gate p.c.b.s are shown fixed to the underside of the keyboard with stand off insulated washers.

INTERCONNECTION PATTERN

In order to distribute signals at the four pitches 16ft, 8ft, 4ft and 2ft from the Tone Generator to each note on the keyboard an interconnection process to the pattern shown in Fig. 2.8 is required. This is carried out on the Diode Gate p.c.b.s, a continuous wire linking for example the 2ft gate input for note No. 7 with the 4ft gate input for note No. 19, the 8ft gate input for note No. 31, and the 16ft gate input for note No. 43, then continuing as the interconnecting lead to the Tone Generator board output F#(4).

All notes in this example are F#s and it can be seen from Fig. 2.8 how the same F#(4) tone generator frequency acts as the fundamental where F#5 in the piano keyboard, shown in Fig. 2.1(a), occurs, i.e. at 16ft and 8ft in notes 43 and 31 respectively, whilst in note 19 it acts as the fourth harmonic for F#3 at 16ft and the second harmonic for F#4 at 8ft, and in note 7 as the eighth harmonic for F#2 at 16ft, the fourth harmonic for F#3 at 8ft and the second harmonic for F#4 at 4ft.

This pattern is repeated for every pitch of every note until a complete matrix is made up with 85 interconnecting leads to the Tone Generator board.

MATRIX CONSTRUCTION

The three Diode Gate board assembly is constructed before it is fixed to the keyboard. The three boards should be temporarily clamped in line using nuts, bolts and washers at the front and rear of each junction, or in a temporary timber frame which allows the boards to sit in slots during assembly.

The first process is to solder the earth and output linkages previously described and shown in Fig. 2.6. Two extra link pads are also provided on the p.c.b.

Copper wire of approximately 28 s.w.g. with a solderable insulated coating is used to build the matrix. A few

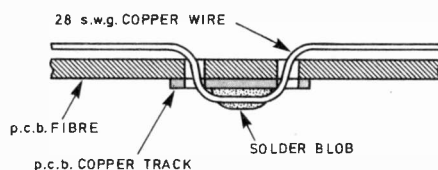


Fig. 2.9. Cross section of solder joint and method of threading copper wire through Diode Gate p.c.b.s

guidelines for the pattern are given on the p.c.b. component identification diagram in Fig. 2.5. A continuous wire both interconnects the relevant pitch on each note and acts as a lead between the Diode Gate p.c.b.s and the Tone Generator. A solder land is provided on the Gate board for each pitch of each note and has two holes one on each side of the land.

The copper wire is threaded through one hole from the top of the board and then returned through the remaining hole. All interconnect wires can be "knitted" in this way prior to soldering and then as a final process a hot iron is used to melt the insulation providing the solder connection to each land. A cross section of the joint is shown in Fig. 2.9.

TONE GENERATOR CONNECTION

The points at which interconnect wires are taken from the Diode Gate boards to the Tone Generator are shown in Fig. 2.8. The corresponding Tone Generator frequency reference numbers are also given in this diagram, i.e. C(1) to C(8).

When threading the wires to construct the matrix, an extra length should be allowed to reach the Tone Generator. For connections taken from the left hand group in Fig. 2.8 an extra 16 inches should be allowed, and for connections taken from the right hand group an extra 30 inches should be allowed.

As each wire is fitted to the matrix, labels can be attached to the tone generator end of the lead identifying the tone generator reference numbers, or alternatively identification can be ignored whilst interwiring and a multi-meter used to locate the leads at a later stage.

TESTING THE GATE/KEYSWITCH ASSEMBLY


A test of the system can be carried out at this stage by terminating each of the output busbars with 10 kilohm resistors to ground giving simple square wave outputs at 16ft, 8ft, 4ft and 2ft, from lower and upper parts of the keyboard. The Keyswitch rod should be fed direct from the +20 Volt supply on the Tone Generator board, and the sustain line may be fed from either +20 Volts or ground to give maximum and minimum sustain respectively.

Note: In Fig. 1.6 the copper track between pins 1 and 14 should be broken.

Next Month: Cabinet assembly and Chorus System description.

Electronic KEYSWITCH

S.V. ESSEX

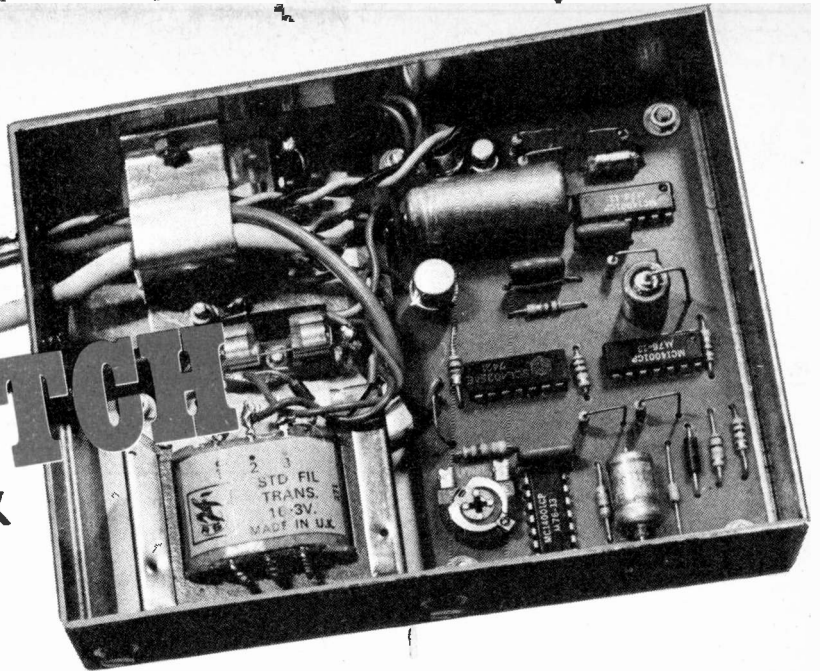

ELECTRONIC locks have always held a strange fascination for electronics constructors; they are primarily novelties, although one can always think of many more serious applications; for instance the "keyswitch" can be used as a safety device to isolate the power to a piece of equipment unless someone authorised to use it is available to insert the key.

The basic design is very flexible, since the keyswitch can be considered in terms of building blocks, which can be altered to fulfil the requirements of most applications. The basic version of the design uses four CMOS logic integrated circuits, which are readily available, easy to use, and inexpensive. The key is in fact a jack plug, the two terminals of which are connected to a resistor housed in its body.

CIRCUIT DESCRIPTION

The complete circuit diagram of the keyswitch is shown in Fig. 1 with the four CMOS i.c.s. enclosed within the dotted lines.

The operation of the circuit can first be considered without a key inserted in the socket. In this quiescent state the diode (D1) is reverse biased and the output of the comparator (IC1) is low. The 'inhibit 1' input to the gating circuit (IC3) is high, holding off the monostable and alarm circuits. When the output of IC1 is low the outputs of the schmitt trigger (IC2) and the gating circuit remain low with the transistor (TR1) reverse biased and the relay de-energised.

When a key is inserted into the socket its resistance is measured by the comparator and if its value is within an acceptable range, D1 is forward biased and the 'inhibit 1' input is switched to a low state. At the same time the schmitt trigger receives a positive pulse from IC1; before the gating circuit can use this pulse without error it must be modified into a square wave by the schmitt trigger. On receiving a correct signal from the schmitt trigger, output (a) of the gating circuit switches

to its high state turning on TR1 and energising the relay.

The schmitt trigger output holds the monostable and alarm circuits off in place of the inhibit 1 input which is switched low.

If an incorrect input is applied to the circuit the comparator, schmitt trigger and gating outputs all remain in their low state with TR1 switched off and the relay de-energised. The diode D1 will be forward biased, the 'inhibit 1' input to IC3 will be switched low and the monostable IC4 triggered. The output of the monostable will remain high for a time period determined by the values of C3 and R9. The inhibit 2 input to IC3 ensures that any input applied to the keyswitch is disregarded until the monostable returns to its quiescent state and turns off the alarm.

CONSTRUCTION

Nearly all the components can be mounted on one printed circuit board: the p.c.b. layout is shown in Fig. 2. Fig. 3 shows the component locations on the board. The cable connecting the keyswitch input socket to the main circuit should be screened, with the braiding connected to the 0V supply rail; this can be earthed for safety. Microphone cable is quite satisfactory for this.

The prototype keyswitch was housed in an aluminium box, type AB10, with dimensions 101mm × 133mm × 38mm, which is probably the smallest size that the circuit can be fitted into, if it is powered from the mains.

The mains transformer was bolted to one side of the box: and to save space, the two rectifier diodes were soldered direct to the transformer secondary connections.

The output device in the prototype was controlled by a relay, which was held in place by an aluminium clamp which also held the input and output cables. The diode, D4, was connected directly across the relay coil connections, and D5 was connected directly across the speaker coil.

When assembling the components on the printed circuit

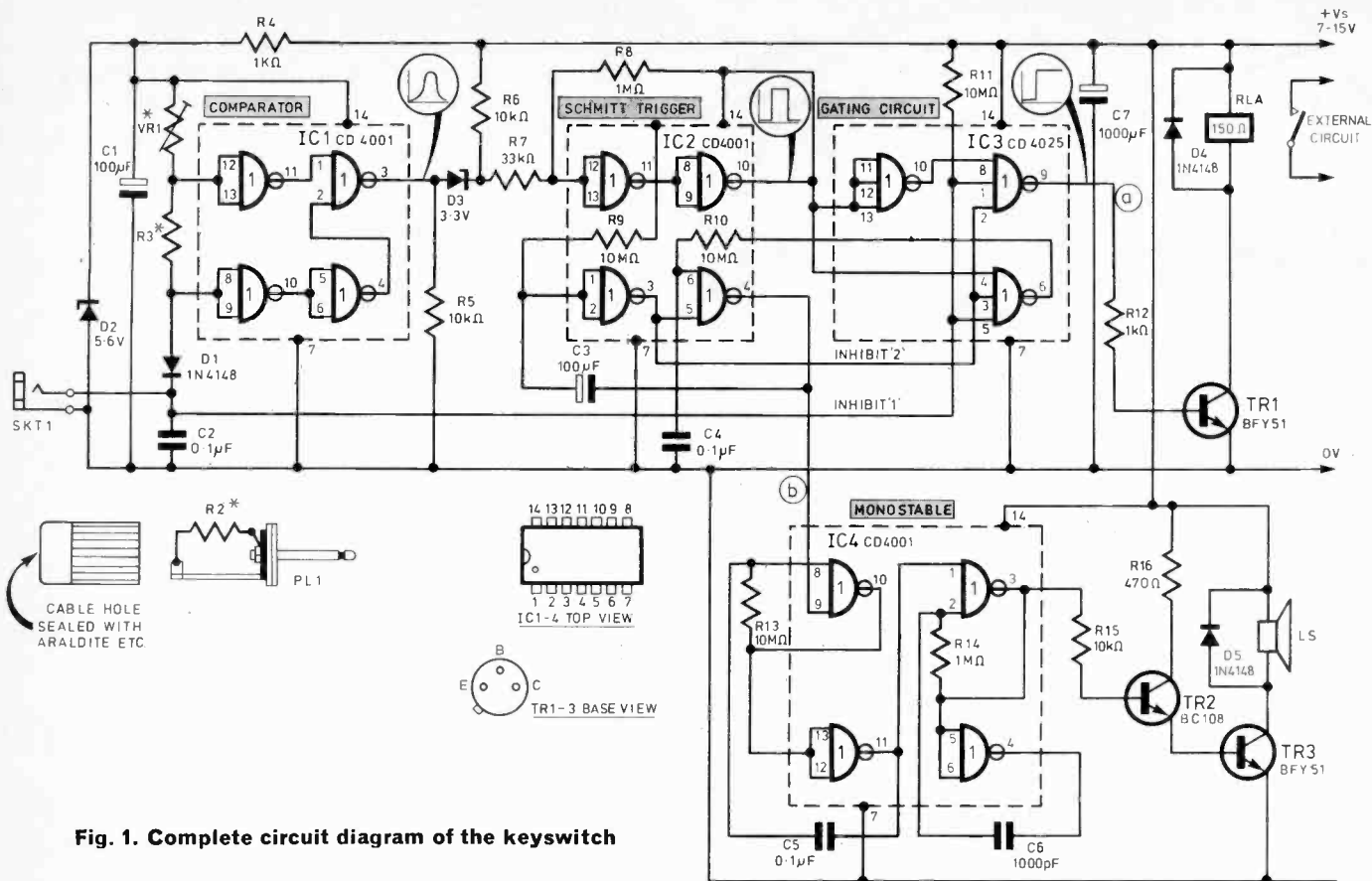


Fig. 1. Complete circuit diagram of the keyswitch

COMPONENTS . . .

Resistors

R1, R2, R3	See text
R4, R12	1kΩ (2 off)
R5, R6, R15	10kΩ (3 off)
R7	33kΩ
R8, R14	1MΩ (2 off)
R9, R10, R11, R13	10MΩ (4 off)
R16	470Ω ½W 10% carbon
All resistors ¼W 10% carbon except where stated	

Capacitors

C1	100μF 10V elect.
C2, C4, C5	0.1μF polyester (3 off)
C3	100μF 16V elect.
C6	1,000pf polystyrene
C7	1,000μF 25V elect.

Semiconductors

TR1, TR3	BFY 51 (2 off)
TR2	BC108
D1, D4, D5	1N4148 (3 off)
D2	5.6V 400mW Zener
D3	3.3V 400mW Zener

Integrated Circuits

IC1, IC2, IC4	CD4001 (3 off)
IC3	CD4025

Miscellaneous

PL1	2-pole 0.25in jack plug and socket
SKTA	
RLA	12V/150Ω relay
LS1	35Ω loudspeaker

board, the insertion of the four CMOS i.c.s should be left to last and they should be handled as little as possible, to avoid any static discharges damaging them.

CHOOSING R1, R2 AND R3

The key resistance R2 can be given any value between 4.7kΩ and 1MΩ. R1 should be a linear preset with a value twice that of R2 and if R3 has a resistance of R2/10, the circuit will have a sensitivity of ±10 per cent, this figure can be improved to ±3 per cent if a preset is used for R3.

POWER SUPPLIES

The circuit draws only a modest current from the supply in its quiescent state—around 6mA at 12V—and will work on any voltage in the range 7–15V; battery operation is therefore possible, although of course mains operation is desirable if the circuit is to be operated for any long period of time.

A simple full wave or bridge rectifier is all that is required for mains operation. Fig. 4 shows the arrangement used in the prototype. It must be borne in mind that transformer manufacturers usually use more windings for the secondary than is strictly necessary, to allow for the voltage drop in the secondary winding resistance; hence off-load rectifier voltage outputs can be at least 10 per cent higher than expected. It is important that the supply voltage to the CMOS i.c.s is never allowed to exceed 15V. D6 and D7 are shown as 1N4001's; these are suitable for output currents of up to 1A.

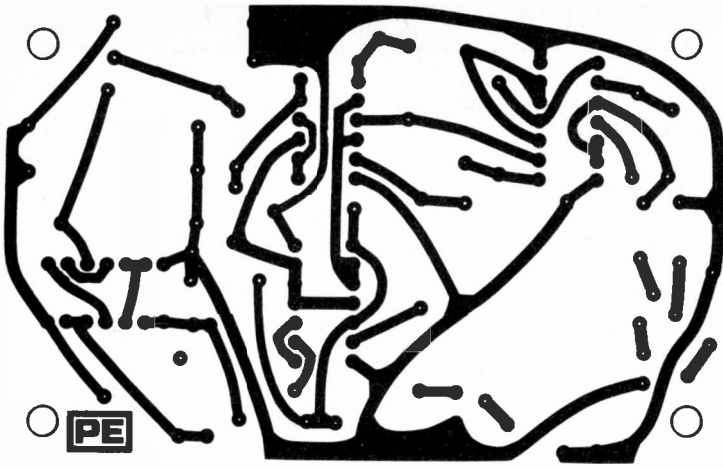


Fig. 2. Printed circuit board layout

INPUT PROTECTION

If a high voltage is applied to the input socket, the effect on the circuitry is rather unpredictable; although it is unlikely that such an action would result in the

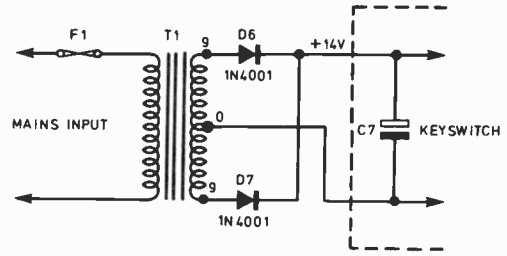


Fig. 4. Power supply

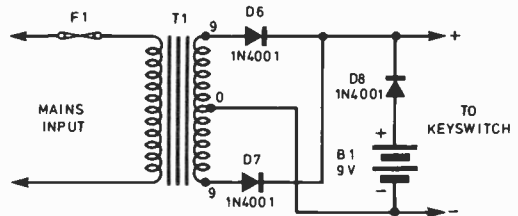


Fig. 5. Standby battery supply

external circuit being activated, the possibility of it doing so is still present.

The CMOS gates would probably be the first casualties if this should happen, but damage can be prevented by wiring 1 Megohm resistors in series with the gate inputs; these will not affect the circuit operation in any way (since the input impedance of a CMOS gate is typically 10^{12} ohms), but will limit the input currents to very low values.

SETTING UP

Because of the long monostable time constant, setting up would be extremely time-consuming and tedious, unless a 470 kilohms resistor is temporarily connected in parallel with R9; the alarm circuit then only operates for a few seconds, rather than the usual 12 minutes. The setting-up procedure for the basic circuit is as follows:

With the circuit operating from its normal supply voltage, connect a multimeter across the output of the schmitt triggered and the 0V line: with the key inserted, adjust R1 for a high output voltage. It will be found that this voltage is high for variations in R1 over a small range: R1 should be set to the middle of this range. No further setting up should be necessary.

If a preset is used for R3, the following procedure should be followed:

Set R3 to maximum, and adjust R1 in the same way as for the basic circuit: it will be found that the possible variation of R1 is quite large. Now R3 should be reduced in value until the schmitt trigger voltage drops, when R1 should be readjusted. R3 and R1 should be adjusted in turn until no further adjustment is possible. Although in this state the circuit is very sensitive, R3 should be increased in value by a small amount, to give some allowance for supply voltage and temperature changes.

The keyswitch is then ready for use. ★

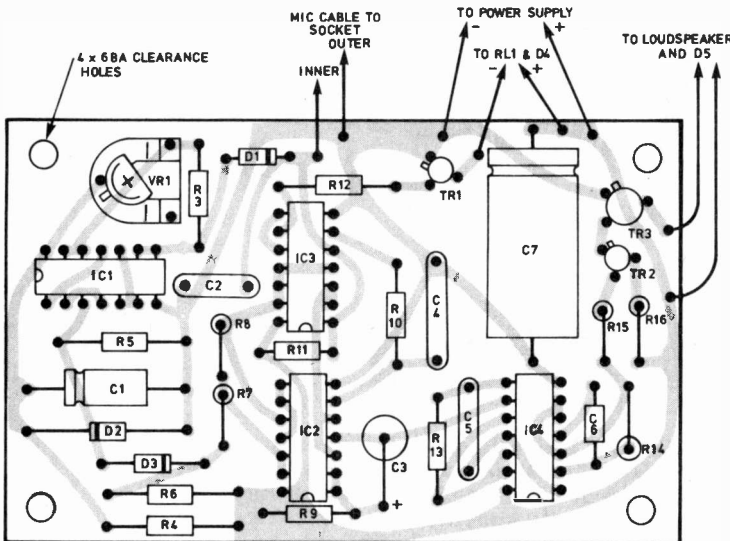


Fig. 3. Component layout for p.c.b.

BATTERY OPERATION

It is possible to incorporate automatic battery switch-over in the event of a mains failure, using the circuit shown in Fig. 5. When the mains supply fails, D8 conducts (it is normally revers-biased), and the 9V battery powers the circuit until the mains voltage is re-established. The voltage drop from 14V to 9V should not affect the circuit, unless R3 (if it is made preset) is set too close to the limit (i.e. to give a very small acceptance range).

If the circuit is to be permanently battery powered, some form of battery voltage check will be required to ensure that the batteries are changed before their voltage drops below 7V.

ALARM OPTIONS

There are several alternatives to using an alarm tone generator and loudspeaker; an electric bell or any other load (e.g. a light mounted above the doorway) can be controlled in the same way, using a relay or transistor.

Next Month... this 24 Page Booklet **FREE!**

The literature of the computer world is riddled with its own brand of mystifying esoteric jargon which can make the understanding of this vital technology a hard slog. This handy reference offers to simplify such endeavours with explanations of the basic vocabulary.

PRESENTED FREE WITH PRACTICAL ELECTRONICS MAY 1978

A Guide to the Language of **MICROCOMPUTERS**

TTL TEST CLIP

A compact unit which is capable of testing all 74 series 14 and 16 pin packages. It has a clip on action and l.e.d.'s are used to indicate the logic states '1' and '0'. Its specification matches many of the more expensive ready built types.



WORKSHOP POWER SUPPLY UNIT

This p.s.u. has an adjustable output up to 25 volts with over voltage protection. The current is variable to a maximum of 1.5 amps.



PRACTICAL ELECTRONICS

OUR MAY ISSUE WILL BE ON SALE FRIDAY, 14 APRIL, 1978

MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus will present ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas will probably come from readers working on their own microcomputer systems, and payment will be made for any contribution featured here. This is also the place to air your views, in general, on this new technology, so let's be hearing from you!

FOUR MICROS COMPARED

THIS month's Micro-Bus looks at and compares the four microprocessors which have so far proved most popular with home programmers: SC/MP, M6800, MCS6502, and Z80. Obviously it would be possible to devote several pages of detailed description to each one, but since such data is available from the manufacturer or a distributor this article will concentrate on the differences between them from a programming point of view.

This should help people familiar with one micro to understand programs intended for another. To this end each of these micros' approaches to solving the same simple problem will be presented. The choice of a suitable "benchmark" problem is tricky because a particular micro may handle certain operations with an ease that does not reflect its general capability; for example, the Z80 can move blocks of data with a single instruction, and SC/MP has a delay instruction.

The task chosen does not favour any particular micro: the sorting of an array of numbers in memory using an "exchange sort". Although for large amounts of data a more efficient algorithm could certainly be found, this was chosen for its simplicity. It involves scanning through the array exchanging pairs of elements which are out of order; this is repeated until a complete scan has been done without any exchanges, when the array must be in correct order and the program stops.

Additionally it was specified that the length of the array should be less than 256 bytes and passed to the routine in a suitable register, and that the array could reside anywhere in memory, its address being also passed to the routine.

The programs for each micro are given in Fig. 1. These are assembler listings, and the formats are similar in that the addresses and machine code are in hexadecimal on the left, and the symbolic form of each instruction appears to their right. Assembler is a symbolic language

which makes it possible to think about and write programs in terms of mnemonic words rather than numbers, and without having to calculate details inessential to the logic of the program (such as addresses and relative jumps). A program called "the assembler" takes the program in symbolic form—the right-hand side of the listings—and calculates the corresponding addresses and opcodes. In addition the assembler can be told to perform other operations, such as reserving storage for variables and positioning the program in memory. Such "assembler directives" tend to differ between manufacturers; for example, the symbol for the current address is `.`, `*`, or `$` for these four micros.

The programs are believed to be the shortest possible, but we would be pleased to hear from anyone who feels that a particular micro has had an unfair presentation.

NATIONAL'S SC/MP

SC/MP (pronounced "scamp") is one of the cheapest micros available, and it has a very simple and symmetrical instruction set. There are three 16-bit pointer registers, P1, P2, and P3, and all memory addressing (apart from immediate) is indexed either using one of these, or relative to the program counter—effectively a fourth pointer P0. Jumps are similarly either PC-relative or pointer-relative. There is one 8-bit accumulator, AC, which is used in all operations, and an 8-bit "extension" register which can be specified instead of a memory address in most dual-operand instructions, or used as a temporary store.

In SC/MP's version of the sort routine, Fig. 1 (a), P1 is used to point to the pair of elements being compared. The dual-operand instructions may also auto-increment/decrement the pointer register; for example, the instruction `LD @1 (1)` in the program increments the pointer by 1 after loading the AC with the value it addressed. Besides saving instructions, this facility makes it possible to implement stacks quite neatly.

Subroutine calls are performed by the XPPC instruction which exchanges the specified pointer register with the program counter, causing a jump. The current value of the program counter is thus saved in the register, and a second XPPC will return control to the calling program. The subroutine address must first have been loaded into the register, and this unfortunately takes four instructions—a fact which tends to discourage the liberal use of subroutines. The other three micros all automatically stack the program counter on a subroutine call and restore it on a return, so nested or recursive subroutine calls are no problem.

SC/MP's instruction set has been pared down to the essentials, and its version of the sort routine is longer than for the other micros. It also seems to be harder to understand programs written for it due to the need for non-obvious tricks; for example, there is no "jump if carry clear" instruction; instead one must first copy the status word to the AC and then, since the carry is the top bit of the status word, a "jump if positive" achieves the required result. Nevertheless its three index registers, auto increment/decrement, and the ability to write relocatable programs, all make it an attractive micro once such tricks have been mastered.

MOTOROLA'S M6800

The sort routine for the M6800 is shown in Fig. 1 (b). The M6800 differs from the other micros considered here in having two primary accumulators, A and B, either of which can be specified as an operand in the majority of instructions. This saves instructions where otherwise temporary variables would be needed, as for example in the section of the routine which swaps the two adjacent elements.

All the memory reference instructions use either direct or indexed addressing. With direct addressing the address is given in the instruction and the single-operand instructions such as increment, decrement, or clear, can therefore operate

```

(a) ; SORT ROUTINE FOR SC/MP
; ON ENTRY: P1 POINTS TO DATA
; AC CONTAINS LENGTH
0000 ; -OF18
OF18 COUNT: ; -,+1
OF1C LEN: ; -,+1
OF1D FLAG: ; -,+1
OF1E PTR: ; -,+2

OF20 C8F8 SORT: ST LEN
OF22 88F9 DLD LEN ;SUBTRACT 1
OF24 35 XPAH 1
OF25 C8F8 ST PTR
OF27 31 ST PTR+1
OF28 C8F6 ST PTR+1 ;SAVE P1
OF2A C4FF NEW: LDI -1
OF2C C8F0 ST FLAG ;CLEAR FLAG
OF2E C0E7 LD PTR
OF30 35 XPAH 1
OF31 C0E0 LD PTR+1
OF33 31 XPAL 1 ;RESTORE P1
OF34 C0E7 LD LEN
OF36 C8E4 ST COUNT ;RESET COUNTER
OF38 C501 NOEX: LD 8+(1) ;AUTO INCREMENT
OF3A 32 CCL (1) ;COMPLEMENT & ADD
OF3B F500 CND (1) ;COPY STATUS TO AC
OF3D 06 CSA ;JUMP IF POSITIVE
OF3E 840C JP NOEX
OF40 C100 EXCH: LD (1)
OF42 01 XAE (1) ;SAVE IN EXTENSION
OF43 C1FF LD -1(1)
OF45 C900 ST (1)
OF47 01 XAE (1) ;BRING IT BACK
OF48 C9FF ST -1(1)
OF4A A8D2 ILD FLAG
OF4C B8CE NOEX: DLD COUNT
OF4E 9CE8 JNE ;FINISHED 1 PASS?
OF50 A8CC ILD FLAG ;FLAG UNCHANGED?
OF52 9CD6 JNE ;IF SO, DO AGAIN
OF54 3F XPRC 1 ;RETURN

```

```

(b) * SORT ROUTINE FOR M6800
* ON ENTRY: X CONTAINS ADDRESS OF DATA
* A CONTAINS NUMBER OF ELEMENTS
0000 0002 PTR RMB 2
0002 0003 LEN RMB 1
0003 0004 FLAG RMB 1
0004 0005 COUNT RMB 1
*
0005 DF 00 SORT STX PTR
0007 4A DEC A
0008 97 02 STA A LEN
000A 7F 0003 CLR FLAG
000D 96 02 AGAIN LDA A LEN
000F 97 04 STA A COUNT
0011 DE 00 LDX PTR
0013 A6 00 NEXT LDA A 0,X
0015 A1 01 CMP A 1,X
0017 23 08 BLS NOSWAP
0019 E6 01 SWAP LDA B 1,X
001B A7 01 STA A 1,X
001D 27 00 STA B 0,X
001F 7C 0003 INC FLAG
0022 08 NOSWAP INX
0023 7A 0004 DEC COUNT
0026 2B EB SNE NEXT
0028 7D 0003 TST FLAG
002B 26 DD BNE AGAIN
002D 39 RTS ;RETURN

```

```

(c) ; ON ENTRY: X CONTAINS HIGH BYTE OF ADDRESS
; Y CONTAINS LOW BYTE OF ADDRESS
; A CONTAINS LENGTH OF ARRAY
0000 ; PTR
0002 ; LEN
*
0003 86 01 SORT STX PTR+1
0005 84 00 STY PTR
0007 85 02 STA LEN
0009 A4 02 LDY LEN
000B A2 00 LDX 00
000D 81 00 NEXT LDA (PTR),Y
000F 88 DEY
0010 81 00 CND (PTR),Y
0012 80 0C BCS NOSWAP
0014 AA SWAP LDA ;SAVE IT
0015 81 00 TDX (PTR),Y
0017 87 INY
0018 91 00 STA (PTR),Y
001A 88 DEY
001B 8A TBA
001C 91 03 STA (PTR),Y
001E A2 FF LDX 8FFF
0020 C0 00 NOSWAP CPY 00
0022 D0 E9 BNE NEXT
0024 E8 INX
0025 F0 E2 BEQ AGAIN
0027 60 RTS ;ANY EXCHANGES?
; IF NOT - RETURN

```

```

(d) ; ON ENTRY: HL CONTAINS ADDRESS OF DATA
; C CONTAINS NUMBER OF ELEMENTS
0000 222600 SORT: LD (DATA),HL ;SAVE DATA ADDRESS
0003 C884 LOOP: RES 0,H ;INITIALIZE FLAG
0005 41 LD B,C ;INITIALIZE LENGTH
0006 05 DEC B ;COUNTER
0007 DD2A2600 LD IX,(DATA) ;INITIALIZE POINTER
0008 DD7E00 NEXT: LD A,(IX)
000E 57 LD D,A ;TEMPORARY STORE
000F D05E01 LD E,(IX+1)
0012 93 SUB E ;COMPARE
0013 3008 JR NC,NOEX-8
0015 DD7300 LD (IX),D ;EXCHANGE ELEMENTS
0018 DD7201 LD (IX+1),D
001B C8C4 SET 0,H ;SET FLAG
001D DD23 INC IX ;POINT TO NEXT ONE
001F 10E4 DJNZ NEXT-8 ;REPEAT IF MORE
0021 C844 BIT 0,H ;EXCHANGES?
0023 20DE JR NZ,LOOP-8 ;IF SO CONTINUE
0025 C9 RET ;OTHERWISE EXIT.
*
0026 ; DATA: DEFS 2 ;STORAGE FOR ADDS.

```

Fig. 1. Four microprocessors approaching the same programming problem of sorting an array of numbers into ascending order using an "exchange sort" algorithm. (a) SC/MP. (b) M6800. (c) MCS6502. (d) Z80.

directly on memory without using an accumulator. Indexed addressing adds the contents of the 16-bit index register to the second byte of the instruction to give the effective address, thus making it possible to service arrays of any length and positioned anywhere in memory.

The orderliness of the instruction set and the variety of branch-on-condition instructions available make it possible to implement most problems directly and in a comprehensible way. The only real limitation is in the provision of only one index register which makes it necessary, when processing two independent arrays of data as in multibyte arithmetic, to save and load its value to and from memory between operations on each array. The other three micros are more fortunate in this respect.

An upward-compatible addition to the family due out later this year, the 6809, will overcome this by providing an extra 16-bit index register together with several new addressing modes.

MOS TECHNOLOGY'S MCS6502

The MCS6502 is a member of the MCS5600 range of micros, all with different hardware options but the same instruction set. They were designed with the same basic philosophy as the M6800 and at first sight programs for them look similar. However, MOS Technology have made a number of simplifications and improvements to the M6800 instruction set resulting in a machine which tends to execute programs faster, and which solves certain types of problems more efficiently.

The M6800's 16-bit index register has been replaced by two 8-bit index registers, X and Y, and there is only one

accumulator, A. As well as normal indexed addressing, which can use either of the index registers, two addressing modes are provided which are not found in the M6800 or indeed in either of the other two micros; pre-indexed and post-indexed indirect addressing.

THE MODES DESCRIBED

With pre-indexed indirect addressing the contents of the X register and the second instruction byte are added to give an address in the first 256 bytes of memory—page zero—and the two bytes of data at that address are taken as the indirect address for the operation. This mode of addressing is useful for servicing a set of independent locations whose addresses are kept in a table in page zero.

With post-indexed indirect addressing, the mode used in the MCS6502's version of the sort routine in Fig. 1 (c), the second byte of the instruction specifies an address in page zero where an indirect address is found. The contents of the Y register are added to this to give the effective address.

Post-indexed indirect addressing makes it possible to index arrays whose positions could be anywhere in memory, as in the sort program. The address of the array in this program is stored in page zero at PTR, and this indirect address is indexed by Y to select elements of the array. Note that this makes the SWAP part of the routine rather inelegant; this could be improved if the address of the array were known in advance. The array is scanned backwards from the end in this version because the program works out shorter this way.

ZILOG'S Z80

The Z80 is an improved version of the popular 8080A and contains all its codes as a subset of its instruction set. To it have been added an additional set of seven 8-bit registers, a large number of new instructions, program-relative jumps, and indexed addressing. The indexed addressing uses one of the two 16-bit index registers, IX or IY, and the codes have been obtained by prefixing the existing indirect addressing code, which takes the address from the register pair HL, by one of two modifiers which were unassigned codes on the 8080A, "DD" or "FD". The displacement, where applicable, is the last byte of the instruction, resulting in lengths of four bytes for the indexed addressing operations.

The Z80's version of the sort routine is taken from the Z80-CPU Technical Manual and it illustrates several of the additions to the 8080A instruction set: the "decrement and jump if non-zero" uses the B register as a counter to provide very neat loop control, and the bit clear (RES), set (SET), and test (BIT) instructions each achieve what would otherwise take two or three instructions.

The question arises: is it worth paying the price of a messy instruction set for the advantage of upward compatibility with the 8080A? Firms with 8080A software already written are one matter, but as far as amateurs intending to program in machine code are concerned the answer seems to be no. Instruction set design has come some way since the 8080A and yet the Z80 has retained its basic design philosophy resulting in a confusing mixture of low-level and high-level operations.

SYSTEMS AND PRICES	RAM (bytes)	Monitor (bytes)	Available from	Price (ex. VAT)
SC/MP MPU chip (N channel) SCRUMPI 1 kit. Binary programmed (Reviewed P.E. Aug. 77) SCRUMPI 3 kit. Hex programmed from keyboard, TV, cassette, TTY interfaces	256	—	Marshalls	£10.00
Introkrit. Hex programmed from TTY	128	1 K	Bywood	£46.30
Keyboard kit. Converts Introkrit for programming from hex keyboard. (Reviewed P.E. April 77)	256	½K KITBUG	Bywood	£154.92
MK14 kit. Hex programmed from keyboard	256	½K SCMPKB	Marshalls	£68.61
	256	½K SCMPKB	Marshalls	£65.84
	256	½K SCMPKB	Science of Cambridge	£39.95
M6800 MPU chip D2 kit. Hex programmed from keyboard Cassette interface. (Reviewed P.E. July 77) 77-68 kit. Binary programmed from MP-68 kit. Hex programmed from TTY	256	1K JBUG	Newbear	£14.00
	256	—	Cramer	£175.00
	256	—	Newbear	£102.77
	4K	1K MIKBUG	Computer Workshop	£275.00
MCS6502 MPU chip KIM-1 built. Hex programmed from keyboard. Cassette, TTY interfaces. (Reviewed P.E. Feb. 78)	1½K	2K	Newbear	£14.93
	1½K	2K	G.R. Electronics	£199.00
Z80 MPU chip (2.5 MHz) 280Z. TTY interface NASCOM 1. Qwerty keyboard, TV, cassette, TTY interfaces. KONTRON kit. Hex programmed from keyboard. Cassette, TTY interfaces	4K	2K	Newbear Sintel	£15.50 £398.00
	2K	1K	Lynx	£197.50
	256	1K	Cramer	£215.00

Low cost systems currently known to be available for the four popular microprocessors discussed in this article.

RANDOM NOISE

Electronics constructors with no computing background should not despair at the thought of programming microprocessor systems; in many cases programs can be derived directly from a consideration of how the same task is carried out in hardware. To illustrate this a circuit to generate random noise is given together with an analogous program written for a M6800 micro. There should be no problems in converting this for other micros.

The circuit in Fig. 2 shows how a 23-stage shift register can be arranged to produce a maximal-length sequence of bits by connecting the outputs from stages 18 and 23 back to the input by an exclusive-OR gate.

ANALOGOUS PROGRAM

In the analogous program, shown in Fig. 2, the shift registers are replaced by three 8-bit memory locations designated LAST, LAST+1, and PIAREG. The third of these is contained in a versatile

input/output chip, Motorola's MC6802 Peripheral Interface Adapter, and the first two lines of the program are for configuring this so that the contents of the location PIAREG are available at the PIA's eight output pins PA0-PA7. The first of these locations is ANDed with binary 01000010 to isolate bits 23 and 18, and adding 00111110 then sets bit 23 to the exclusive-OR of these two bits. This is then shifted into the carry bit, and from there into the bottom bit of the three locations.

The sequence is $2^{23}-1$ or 8,388,607 bits long and with the program as it stands the output, which can be taken from any stage, is a white noise with a power spectrum substantially flat over the audible frequency region. With a delay inserted into the loop the sequence of bits can be used as random-coin tosses for use in games, modelling, or psychological experiments. If the bits are generated at a rate of 1 per second the sequence will repeat itself only after 97 days; for most practical purposes it is random!

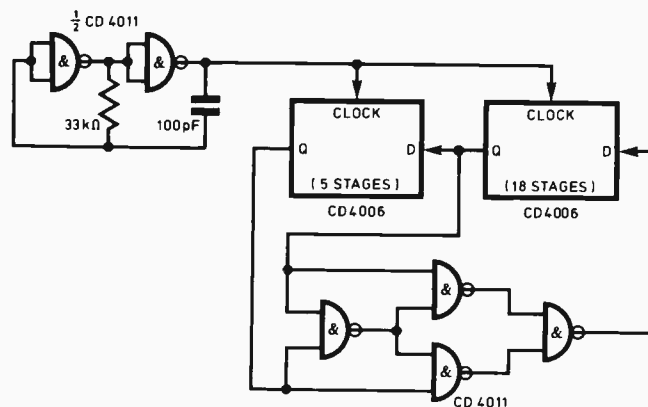


Fig. 2. Maximal-length sequence generator using CMOS gates and shift registers. The output, taken from any stage, is a random noise.

NAM PRN		* PSEUDO-RANDOM NOISE		*	
0000	0002	LAST	RMB	2	
	8004	PIAREG	EQU	\$8004	
0002	CE FFO4	ENTER	LDX	E\$FFO4	
0005	FF 8004		STX	PIAREG	CONFIGURE PIA
0008	96 00	NOISE	LDA	A LAST	
000A	84 42		AND	A E%01000010	
000C	8B 3E		ADD	A E%00111110	
000E	48		ASL	A	
000F	48		ASL	A	
0010	79 8004		ROL	PIAREG	
0013	79 0001		ROL	LAST+1	
0016	79 0000		ROL	LAST	
0019	20 ED		BRA	NOISE	

Fig. 3. Complete program for the M6800 which generates a pseudo-random sequence of bits in a way analogous to the circuit of Fig. 2.

Addresses for Firms in table

Bywood Electronics, 68 Ebbens Road, Hemel Hempstead, Herts HP3 9QRC.

Cramer Electronics, 16 Uxbridge Road, London W5 2BP.

Computer Workshop, 174 Ifield Road, London SW10 9AG.

G. R. Electronics Ltd., 80 Church Road, Newport, Gwent.

Lynx Electronics (London) Ltd., 92 Broad Street, Chesham, Bucks.

A. Marshall (London) Ltd., 40-42 Cricklewood Broadway, London NW2 3ET.

The Newbear Computing Store, 7 Bone Lane, Newbury.

Science of Cambridge Ltd., 6 King's Parade, Cambridge CB2 1SN.

Sintel, P.O. Box 75A, Oxford.



FRANK W. HYDE

THE NEXT FEW MONTHS

During the next few months the American space programme is a full one. One of the major events is the mission of two probes to Venus for an extensive investigation of that planet's atmosphere and surface. This mission has already been specially described in *Spacewatch* for March.

A new Earth spacecraft called 'Seasat' will be launched in May. This vehicle will be of particular value to meteorologists. Seasat will measure the dynamics of the Earth. In particular it will measure the changing shape of ocean surfaces, the heights of waves and the movements of the many ocean currents. It will track icebergs and locate oil slicks using radar. In addition there will be a special watch on eddies and tides.

The extent of these activities is another step forward in this technology. The benefits will be felt in many other areas apart from meteorology. Oceanography will have access to valuable data and the world shipping and fishing industries will also benefit from the knowledge of the daily conditions.

Another mission, HOMM (Heat Capacity Mapping Mission), is devoted to the measurement of land temperatures. Special sensors on the spacecraft will monitor land surface temperatures at daytime maximum and night time minimum. From the changes that are noted in the way that solar heat is retained in trees, in surface rocks and soil it is hoped that the types of rock may be deduced, plant temperatures indicating stress of disease, water cycles and soil moisture.

Some success in this area has already

been achieved with previous Earth Resources Satellites. The wider activities of the HCMM mission will make soundings in temperature over snow covered areas, hot springs and detect man made pollution.

Another new programme is an astronomical observatory; the IUE, International Ultraviolet Explorer. This mission is a joint activity involving science and industry. The European Space Agency and the American National Agency for Space Administration (NASA) are joining to study objects which generate, reflect or re-radiate ultraviolet light. Some young hot stars radiate mostly in the ultraviolet region of the spectrum. In consequence they are almost invisible at other wavelengths. There are also other targets for this mission and among these are studies of the Seyfert Galaxies and observation of the gas and dust between stars where absorption and re-emission of ultraviolet takes place.

Another mission launched in July; this is the third ISEE spacecraft (International Sun-Earth Explorer) which will join the two that were launched in 1977. Each of these craft will be stationed at a different point between the Earth and the Sun. They will be observing the relationships between solar events and magnetic phenomena in the outer environment of the Earth. Recent work has indicated a relationship between magnetic storms and the weather. This co-operative venture involves all the nations of ESA.

The launch schedules in addition to those already mentioned include a third Landsat Earth Resources satellite and the second HEAO. This latter will deal with High-Energy Astronomy. It is an observatory mainly for the study of X-rays and Gamma rays. HEAO 1 launched in August 1977 has observed a dense star which seems to be a good candidate for the title of Black Hole.

THE HOT LINE

The Hot Line between Washington and the USSR has now entered the space age; two independent systems of communication via two satellites. The new line, officially known as Direct Communications Link (DCL), will be more efficient and less liable to failure during times of emergency. The link is less vulnerable than the old system since it depends to a much lesser degree on the extensive microwave links. It also makes it possible for direct communication without a third country being involved. Like its predecessor DCL, contrary to popular belief, makes possible the exchange of printed messages and not telephone calls. The advantage of the printed message is that the language barrier is overcome. It avoids the misunderstanding by translators and provides a written record of the communication. The main purpose of this link is to provide direct communication between the President of the United States and the President of the Soviet Union.

SOVIET CARGO SPACESHIP

Work on the Soviet Cargo Spaceship Progress 1 was put in hand when the space station proper was commenced. According to Konstatin Feoktistov, speaking on this subject, it was realised that there were a number of items which could not be kept in space over long periods of time. Also there were items which might need replacement because of malfunction, replenishment of such things as fuel for control and gas stocks for the atmosphere within the spacecraft. There was also the question of water for showers and washing of linen etc.


It is estimated that each cosmonaut requires about 30 kilogrammes of materials per day. The cargo ship is similar in basic design to the Soyuz spacecraft. The unit module has remained unchanged but the size of the instrument module has been increased. Special tanks for liquid cargoes and a compartment for dry cargo were added. The freight compartment is hermetically sealed so that, after docking, the cosmonauts can work in it to transfer cargo to Salyut-6. Because the power circuit and the layout of the spacecraft were substantially changed, a new set of intensive tests for rigidity, strength, vibration and heat cycles, was made. Since the movement of even small things takes time in space, the design changes were for making such work by the cosmonauts easier and more comfortable.

Progress 1 docked after two days instead of one, as would be normal. This was because the cargo ship was unmanned and the ground commands by radio take longer. Also it was considered that it was better not to hurry the operation.

The cosmonauts aboard Salyut-6 performed the role of a standby system for the automatic control during docking. During the approach phase, data on the speed of Progress 1 and its orientation were transmitted to Salyut-6. The crew watched the approach and would have, if malfunction had occurred, aborted the docking, or, if the craft was approaching dangerously fast, started the motors and escaped from impact. None of this was necessary as the whole operation was carried out according to plan.

PUTTING THE RECORD STRAIGHT

In the January issue of *Spacewatch* reference was made to the Kettering School Station. Unfortunately the name of the master who is its director was given as Mr. Cooper. This error on the writer's part is regretted. The more so because in the early days of the space scene we were in close contact. G. E. Perry MBE, FInstP is famous for his activities in the field of monitoring, particularly in the case of Soviet launchings. On a number of occasions launches were detected and announced from Kettering before official news was given. On a number of occasions *Spacewatch* has mentioned Mr. Perry and the school.

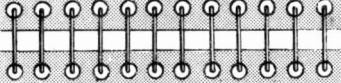

INDUSTRY NOTEBOOK

By *Nexus*



OUTLOOK

All indicators suggest this will be a good year for the European electronics industry and not least for the UK. Even the depressed consumer sector can take heart from the pre-election sweetener of big tax concessions which will encourage consumer spending.

An interesting point is that taking Western Europe as a whole the balance of trade with the rest of the world is only just favourable, with total imports only marginally lower than total exports. But this has to be accepted in a world industry like electronics. The time to worry is when the balance is wholly and consistently unfavourable.

Meantime, the structural shake-up of the British electronics industry, a big talking point in the latter half of 1977, is only barely being kept alive. Plessey, one of the favourites for chopping up and merging with others in a huge group, turned in a reasonable if not sparkling performance last year. Decca, another candidate according to industry gossip, still has founder Sir Edward Lewis in the chair who is said not to be in favour. Some recent 'kite-flying' suggests that STC, at present wholly owned by the US giant ITT, might be a catalyst but only if STC shares were made available to British buyers so that the company could claim to be 'British', or partly so. There is talk of government intervention. But my own thought, shared by a large part of what is a very successful industry, is that this would be the kiss of death.

The proposed government support for microelectronics development in the UK is, however, welcome. The idea is that £25 million invested by the industry itself should be matched by an equal amount from the taxpayers. It

sounds generous until you compare it with the reported £135 million which the Japanese government is spending on similar projects. And when you compare £25 million with the hundreds of millions spent supporting loss-making industries like steel and shipbuilding it looks downright mean. A sound business maxim is to back your winners and shed your losers. But logic counts little in an election year.

ATE

The final round-up of Automatic Test 77, held late last year at Brighton, reveals an even higher level of interest as well as increased attendance. Membrain, as usual, had one of the biggest stands. There had been industry rumours for some time that the six-year-young dynamic company was on the market but it was only after the exhibition that a terse announcement came that Membrain had been acquired by Schlumberger Measurement and Control (UK) Ltd, who already have Solartron and Sangamo Weston under their belt. Membrain, however, will continue to operate as a separate company. Among its recent successes is a contract connected with development of the British Army Ptarmigan communications system.

Because of the huge international interest in automatic test equipment, this year's show and conference will be staged by the British organisers in Paris.

ATE is now showing through as a great money-saver. It is super-efficient. But for ATE, according to one company, they would have to employ 250 test engineers instead of only 50. Looked at in another way, ATE throws people out of work. Which illustrates the difference between wealth-creation and job-creation.

RAILWAY SIMULATOR

Redifon Simulation Ltd, world leaders in flight simulators, are firmly on the ground with their latest project, an order for three railway cab simulators for training drivers on the new underground system in Hong Kong. As in flight simulators, the trainees will have a lively and realistic experience with vision and sound effects while the instructors will be able to introduce various faults which, in real life, could be catastrophic.

MIDDLE EAST

The £1.6 billion sale-of-the-century telecommunications contract for Saudi-Arabia left Britain out in the cold. The winning consortium was Philips/Ericsson/Bell (Canada).

Philips and Ericsson will build the equipment and Bell (Canada) will

operate and maintain it. The contracts will solve many problems for Ericsson in Sweden and Philips in Holland, both of whom had been shedding labour in their telecommunications factories but are now recruiting again.

A consolation prize for Britain is a £40 million contract with Egypt for the Swingfire anti-tank guided weapon. Britain has now supplanted the Soviet Union as a major weapons supplier to Egypt but the long-term penalty is that eventually Egypt will, with British assistance, build up her own independent industry. A purpose-built factory is being erected near Cairo where the missiles will be assembled from UK-made components. Ultimately the whole project will move to Egypt.

This pattern is already being followed in Egypt by at least one British electronics company. A British executive tells me there is now no alternative to this type of agreement. If you turn it down you get no business at all. Such arrangements are not confined to the Middle East. The £128 million contract for Hawk trainer aircraft for Finland gives the Finns the opportunity of assembling the aircraft from piece parts, many of them being also manufactured in that country. We thus not only train overseas customers in what, to them, is advanced technology but also transfer the know-how. It is therefore more than ever important to stay one stage ahead in advanced technology.

ENGINEERING INQUIRY

Of the chairman and 17 members serving on the Committee of Inquiry into the Engineering Profession only one member is identifiable as having deep practical knowledge of the electronics industry. He is Dr. John A. Powell, managing director of EMI Ltd.

The IEE was among the first to make a submission to the Inquiry. Calling for tougher entry qualifications and more demanding degree courses the IEE stated that entry standards have fallen and this has encouraged students to undertake theoretical studies that are beyond their intellectual capacity. The implication is that the weaker students should go for HNC or diploma courses and emerge as first-class technician engineers rather than third-rate graduates.

DIGITAL BROADCASTING

Two sessions on digital techniques in broadcasting were held at the IEE recently. It was a joint presentation by the BBC, IBA, ITCA and the Post Office and as well as the usual propagation methods there was a demonstration of digital techniques transmitted through fibre-optics. We shall be hearing a great deal more on this topic in the future.

BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:

DOES IT HAVE


- ★ 30A power transistors
- ★ 2-year guarantee
- ★ 3A drivers (100W unit)
- ★ Integral output capacitor

Then compare with the Tamba range—excellent value—25, 50 and 100W R.M.S

TAM1000 100W 4 ohms 65V	£9.80
TAM500 50W 4 ohms 45V	£7.50
TAM250 25W 8 ohms 45V	£5.75

POWER SUPPLIES

For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.80
(Carriage 50p on supplies)	

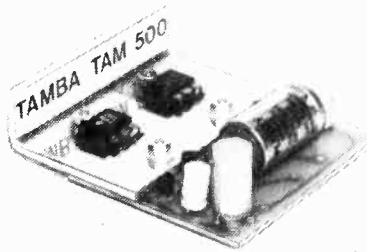

ALL PURPOSE MIXER/PRE-AMP.

(with 60mm slider volume)

- Suitable for multiple input systems
- High and low impedance inputs
- High sensitivity
- Built-in supply smoothing
- 20–20,000 Hz ± 1dB
- –80dB noise level
- Accepts a wide variety of inputs
- Wide range bass and treble controls

Use up to 10 PRE-AMPS with 1 power supply

Printed circuit board assembly with treble and bass controls plus slider volume control

£6.50

- Suits loads 4–16 ohms
- 20–20,000 Hz ± 1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)

- Low distortion (0.1%)
- Low profile (1in high 3½in x 3in)
- 75% efficient
- Accepts most mixer/pre-amplifiers
- Four simple connections

High grade components used throughout: Texas. Mullard, R.C.A., Plessey, etc.

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s etc)—C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50 and 100W systems and at 12½% for 25W systems (including preamp if ordered at same time).

Hours, 9.30 a.m.–5 p.m.
Monday — Saturday.
Callers welcome. Tel.
(01) 684 0098

TAMBA ELECTRONICS

Bensham Manor Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

NEW FROM CASIO NEW

All watches display hours, minutes, seconds, AM/PM, with day, date and month at a touch of the calendar button.

CHRONOGRAPH: Times from 1/100 second to 59 minutes, 59.99 seconds then restarts from zero. Measures normal time, net time, lap time and first and second place times. ±15 seconds/month accuracy. **31QS-12B**, Stopwatch, Dual Time Zone. **31QR-17B**, Stopwatch. All stainless steel, mineral glass. Shock resistant. Water resistant (100 feet). Night light. Automatic calendar. One battery lasts 12 months or more.



31QR-17B
8.4mm thick
£26.95
(RRP £34.95)



31QS-12B
7.7mm
£39.95
(RRP £49.95)



38CS-14B
7.9mm
£49.95
(RRP £64.95)

MQ-2 LCD Clock, Calendar, Alarm, Alarm Timer, Time Memory, Calculator. Two daily alarms or countdown alarm timer (10 second duration). 24 hour Time Memory. Time, Date and % calculations. ½ x 4½ x 1½". 1.6 oz. ±15 seconds accuracy. 18 months battery.

RRP £39.95. Our price **£34.95**

Casio Mini Card. 4 x 55 x 91mm, 3 key memory, %, LCD, 1000 hours **£16.95**. New powerful scientifics with (I) and permutations/combinations. Numerous Sci. functions, Fractions, %, SD etc. FX 120 **£19.95**. FX 3000 (LCD) **£25.95**. OPTIM Battery LCD travel/alarm clock. Stopwatch feature. 1 x 1½ x 5" **£19.50**.

Send 25p (refundable on purchase) for our illustrated catalogue.

Prices include VAT, P&P. Send cheque, P.O., or phone your credit card number to:

TEMPUS

Dept. P.E.
19/21 Fitzroy Street
Cambridge CB1 1EH
Tel. 0223 312866

TRAMPUS



BARGAIN MONTH! POST FREE £5+

FREE 1978 CATALOGUE SALE LIST. MANY SURPLUS & CLEARANCE LINES. SEND S.A.E. DO YOURSELF A FAVOUR A SEMICONDUCTOR POWER HOUSE.

TRAMPUS ELECTRONICS LTD. 58-60 GROVE ROAD, WINDSOR, BERKS. SL4 1HS. TELEPHONE WINDSOR (07535) 54525.

Fast service on ex stock product. Normally 24 hour turn around. Quality devices to manufacturers specifications. No minimum order charge except Barclaycard or Access by post or telephone £5 minimum. Send C.W.O. post free over £5, except invoiced or credit card orders, otherwise add 20p post & packing. Add 8% VAT to items marked * 12% VAT to unmarked items.

LEDs ½" & 0.2" dia.
Red no clip 9p
0.2" or 209 & clip 12p
Colour LEDs all 16p

DISPLAY
0.3" DL704/2 & 707/2 59p
0.6" DL747/2 £1.50
TGS Gas Detectors £5

CAPACITORS
Ceramic 22pf to 0.5 5p
Electrolytic 1µf to 200µf 7p
1000µf/25v 20p
Tantalums only 16p ea

RESISTORS ¼w 2p ea
Presets 10p Pots 25p

VERO 0.1 MATRIX
2½ x 3½ 42p
3½ x 5 42p
3½ x 17 £2.50
DIL Board 6" x 4" £2.50
Dalo PCB Pen 65p
Nylon Board Copper 6 x 4 60p
Tub FEC Etch ½kg £1
RS Bleeder 12v £1.50
Knobs: Cheap 10p
Relay: Multi Pole 12v 10p
Silicon Grease Satchet 25p
Digital Clock IC £2

BULK BUY BARGAINS FULL SPEC PAKS.

All £1 each

PAK A: 12 x Red LEDs £1
PAK B: 5 x 741 8 PIN £1
PAK C: 4 x 2N3055 90W £1

PAK D: 12 x BC109 £1
PAK E: 13 x BC182 £1
PAK F: 13 x 2N3704 £1
PAK G: 7 x BFY51 £1
PAK H: 7 x 2N3819E £1
PAK J: 6 x 2N3053 £1
PAK K: 40 x 1N4148 £1
PAK M: 4xPair NPN/PNPZA £1

PAK N: 50 x OA81/91 £1
PAK P: 20 x Plastic 109 £1
PAK R: 14 x BC107 £1
PAK S: 14 x BC108 £1
PAK T: 10xNPN 2A 60v £1
PAK U: 4x1A 50VSLR £1
PAK V: 40x5MFD 10v £1
PAK W: 20 Electrolytics £1
PAK Y: 4 x LM301/14 £1
PAK Z: 20x2N3702 £1

NEW PAK X: 4 x 555 £1
TRIAC: 10A 400v £1
SCR: 4A 400v (106) £1
DIAC: BR100/STZ 25p
SCR: TAG 1A/600v 60p

DIL Sockets: Lo Profile 8 pin 12p
14 or 16 pin 15p

REDUCED LINES IC's & TRANSISTORS

BC107 8p MJE2955 £1
BC108 8p MJE3055 55p
BC109 8p ORP12 50p
BC109C 15p TIP2955 65p
BC177/8/9 20p 2N3055 45p
BC182/3/4 7p 2N3702/4 8p
BC212/3/4 7p 2N3819E 18p
BCY70/1/2 20p 2N3820 38p
BD131/132 eq 20p 2N2646 50p
BD131/132 eq 20p 2N5457 50p

MJ2955 39p Matching -20p
Ins Bush Sets AOD 10p

ZENERS 400MW 9p
DIODES: 1N4148/914 5p
1N4001 5p 4004 7p

LINEARS: IC's 7812 £1
301/14pin 29p 7815 75p
3080PA £1 76013 £1.49
555 29p LM309K £1
741/8 21p LM380 89p
747 89p LM381 £1.55
748/14 29p LM3900 69p
748/8 39p MC1310 £1
7805 £1 2N4148X 75p

7400TTL 12p 7480 45p
7401 8p 7490 33p
7405 8p 74121 27p
7413 27p 74123 50p
7420 8p 74157 50p
7430 8p CMOS etc
7445 50p 4001 18p
7447 79p 4011 18p


FREE: 1978 CATALOGUE SALE LIST. SEND S.A.E. BARGAIN OFFERS!

THIS MONTH'S SNIPS. LIMITED STOCKS.
TUNER MODULE. BRAND NEW EXPENSIVE. EX MUSIC CENTRE MW, LW, FM, MPX PUSH BUTTON £22.50
7 wait STEREO AMPLIFIER MODULE £31.69

TUNING GANG AIR SPACED 0-360/395 PC HALF PRICE £1 ea.

LOOK! Here's how you master electronics




... the practical way

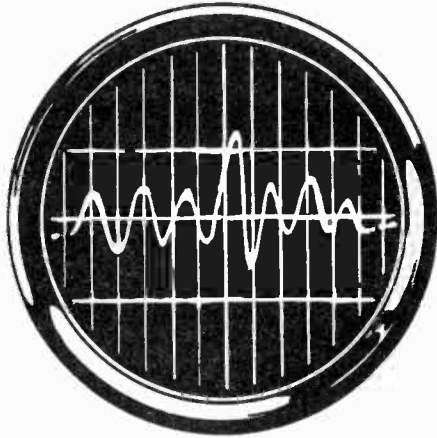

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

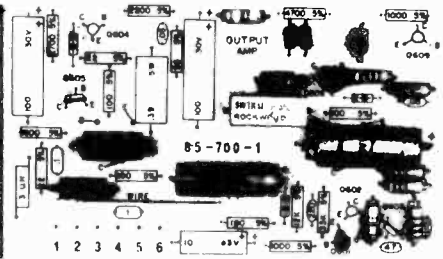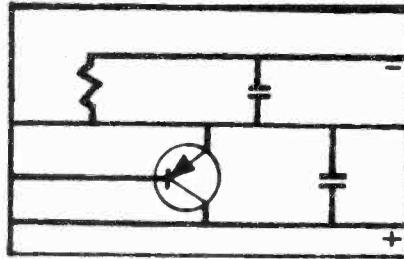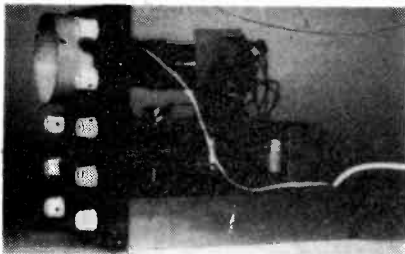All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


2 Read, draw and understand circuit diagrams

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

FREE GIFT

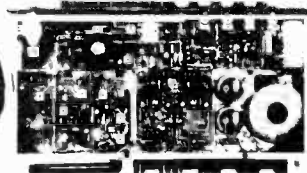

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free!

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.


NAME

ADDRESS

PEB4

Block caps please

VERO

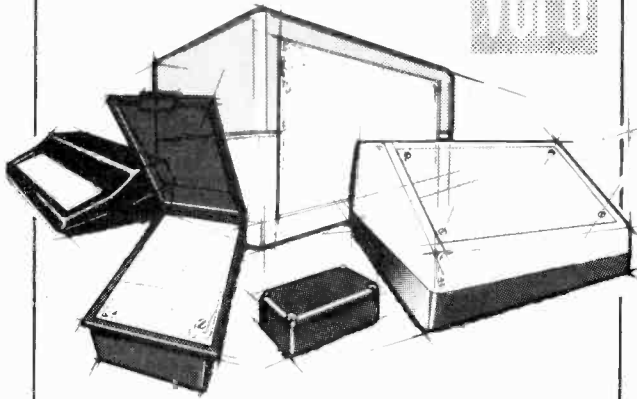

Our new 1978 catalogue lists a whole range of plastic boxes to house all your projects. And we've got circuit boards, accessories, module systems, and metal cases — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

IT'S EASY WHEN YOU KNOW!

To avoid missing your copy of **PRACTICAL ELECTRONICS** — simply complete this order form and hand it to your newsagent.

ORDER FORM

To:
(name of newsagent)

Address

Please reserve/deliver every month one copy of **PRACTICAL ELECTRONICS** until further notice.

My Name

Address

WHAT'S NEW?

ME, semiconductor
teaching kit



the most MODERN, RAPID,
ECONOMIC way to master
space age electronics.
Starting even from ZERO,
by performing over,

100 EXPERIMENTS
and creating more than 20 practical
applications

You learn all about the most up to date electronic circuits: how to calculate, repair, and design them, while pursuing your favorite hobby. Start from scratch, or improve your present knowledge. Train and earn money in your spare time turn your pastime into valuable job opportunities. Compare our price you receive the entire course, "mini laboratory" and components for LESS than the price of the components alone.

COMPLETE KIT: nothing else to buy*

you get:

- instruction manual : over 200 pages of detailed step-by-step instructions -starting from scratch, explains basic laws and physics of Electricity, semiconductor principles and operation electronic circuits : from diodes (including diac, zener) transistors, triacs to integrated circuits (C.MOS, operational amplifiers) etc...
- Over 200 Electronic components : aerospace technologie printed circuit experiment board, phototransistor, triac, thyristor I.C.S Transistors (including FET, MOSFET) LEDs + résistors , capacitors, speaker, milliameter, potentiometers, variable capacitor, etc... etc... etc...
- measuring instruments (you assemble yourself from among componens furnished in kit.)
ELECTRONIC VOLTMEIER, LOW FREQUENCY MEASURING AMPLIFIER, LOGIC INDICATORS, REGULATED POWER SUPPLY, MILLIAMMETER.

you perform:

- over 100 DIFFERENT EXPERIMENTS : from the most basic voltage measurements to radio transmitter circuits and including HI FI, Flip Flops, Ic applications, triac use, etc... etc... etc...

you construct

- more than 20 complete fonctional systems : light modulator, high fidelity amplifier, radio control set, radio receiver and transmitter, electronic gadgets and games and many, many more.

* Hand tools not furnished.



SAVE £10 - mail coupon today - SAVE £10

SAGA ENGLAND: P.O. Box 401
Kingsmead, Kings Lane, Chipperfield,
Nr. King's Langley, Herts. WD4 9PB

Please send me (QTY) IK2 teaching Kit(s)
I enclose Cheque/Postal order for £

NAME

ADRESS


SAGA FRANCE : 11 rue Prosper HELFAD POST CODE
92100 BOULOGNE FRANCE.

THERMOSTATS




Refrigeration as illustrated with 36" capillary **£1.62**.
Limit Stat must be mounted in close contact calibrated 90°-190°F 15 amp contacts **£1.62**.
Appliance Stat fix like a volume control—15 amp contact 30°-80°F **85p**. ditto but for high temps **£1.25**.
 Over Stat—with Serson and capillary **85p**

MAINS OPERATED SOLENOIDS

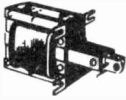

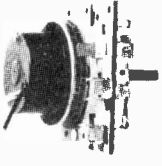Model TT2—small but powerful 1in. pull approx. size $1\frac{1}{2} \times 1\frac{1}{2} \times 1\frac{1}{2}$ in. **£2.00**
Model 4001/1— $\frac{1}{2}$ in. pull. Size $2\frac{1}{2} \times 2 \times 1\frac{1}{4}$ in. **£2.50**
Model TT10— $\frac{1}{2}$ in. pull. Size $3 \times 2\frac{1}{2} \times 2$ in. **£4.50**
 Prices include VAT & postage.




DELAY SWITCH


Mains operated—delay can be accurately set with pointers knob for periods of up to 2½ hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact 95p.

MOTORIZED DISCO SWITCH

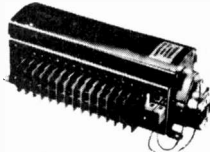With six 10 amp change-over switches. Multi adjustable switches are rated at 10 amp each so a total of 200w's can be controlled and this would provide a magnificent display. For mains operating. 8 switch model **£5.25**. 10 switch model **£6.75**. 12 switch model **£8.75**.




SMITHS CENTRAL HEATING CONTROLLER

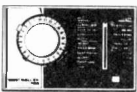


Push button gives 10 variations as follows: (1) continuous hot water and continuous central heating (2) continuous hot water but central heating off at night (3) continuous hot water but central heating only for 2 periods during the day (4) hot water and central heating both on but day time only (5) hot water all day but central heating only for 2 periods during the day (6) hot water and central heating on for 2 periods during the day time only—then for summer time use central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off. A handsome looking unit with 24 hour movement and the switches and other parts necessary to select the desired programme of heating. Supplied complete with wiring diagram. Originally sold we believe at over **£15**. We offer these while stocks last at **£6.95** each INCLUDING VAT and Postage.

LOW R.P.M. MOTORS

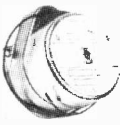

5 rpm 15 rpm 20 rpm 25 rpm 30 rpm

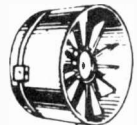
Made by Crouzet—Smiths—SAIWA—Venner and similar famous companies—all supplied ready for 230/240v 50hz mains working at £2.75 each. Following speeds in stock when preparing this advert.
 1 rev per day 6 rev per day
 1 rev per hour 12 revs per hour
 ½ rev per min 1 rev per min
 2 rpm
 1½ rpm



EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic feet per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5½in. casing comprises motor, fan blades, sheet-steel casing, pull switch, mains connector and fixing brackets. **£5.25** including post and VAT. Monthly list available free send long stamped envelope.

FLUORESCENT TUBE INVERTOR

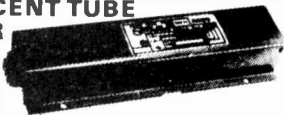

For camping—car repairing—emergency lighting from a 12v battery you can't beat fluorescent lighting, it will offer plenty of well distributed light and is economical. We offer invertor for 21" and 13 watt miniature tube for only **£3.75** with tube and tube holders as well.

MINI-MULTI TESTER



Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—1000opv—11 instant ranges measure—
 DC volts 10, 50, 250, 1000
 AC volts 10, 50, 150, 1000
 DC amps 0-1 mA and 0-100 mA
 Continuity and resistance 0-150k ohms.
 Complete with insulated probes, leads, battery, circuit diagram and instructions.


Unbelievable value only **£5.50** + 50p post and insurance.

FREE

Amps ranges kit enable you to read DC current from 0-10 amps directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one send **£1.50**.

MULLARD UNILEX


A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Plessey speakers this should sell at about **£30**—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only **£15** including VAT and postage.

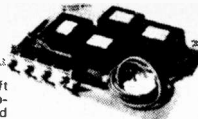

UNISELECTORS

These are pulse operated switches as used in automatic telephone switchboards etc. The pulse moves the switch arm through one position. Except where indicated the selector arm has 25 position types and 50v Coil is standard, 24v or 12v operation extra at **£2** per switch.

3 pole	£4.80	4 pole	£5.94
5 pole	£7.02	8 pole	£9.72
10 pole	£10.10	12 pole	£12.96
3 pole 50 way	£10.68	4 pole 50 way	£12.74

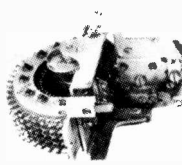

24 HOUR TIMERS

The one illustrated is 'E' controls this uses the Smiths mechanism as in their autostat. 2 On/off's per 24 hours. 13 amp contacts. Override switch **£6.50**. Smiths 100 amp model one on/off per 24 hours **£10.50**, extra contacts **£1.00** per set. AEG 60 amp model with clockwork standby, one on/off per 24 hours **£9.50**, extra contacts **£1.00** per set.



INDUCTION MOTORS

One illustrated is our reference MM11 made for ITT $\frac{3}{4}$ " stack 1½" spindle **£2.25**. $\frac{1}{2}$ " stack model **£1.75**. 1" stack **£2.75**. 1½" stack **£3.25**.



MAINS TRANSFORMERS

20v ½ amp 20w auto 230v **£1.50**.
 18v ½ amp **£1.75**. 6.3v 2 amp **£1.75**. 25v 1½" **£2.25**.
 24v 2 amp **£2.50**. 50v 2 amp **£4.50**. 9v 1 amp **£1.50**. 8.5v-0.85v ½ amp **£1.50**. 100v auto 230-115v **£2.00**. 8-5kv **£9.50**.
 Many more, send for list.



WAFER SWITCHES



6 pole 2 way	12 pole 2 way	18 pole 2 way
5 pole 3 way	10 pole 3 way	15 pole 3 way
4 pole 4 way	8 pole 4 way	12 pole 4 way
3 pole 5 way	6 pole 5 way	9 pole 5 way
2 pole 6 way	4 pole 6 way	6 pole 6 way
2 pole 8 way	4 pole 8 way	6 pole 8 way
1 pole 10 way	4 pole 9 way	6 pole 9 way
1 pole 12 way	2 pole 10 way	3 pole 10 way
all £1.32 each	all £2.41 each	all £3.12 each

Multi bank switches up to 72 pole 2 way—to 12 pole 12 way quickly made to special order.


THIS MONTH'S SNIP

Japanese made FM tuner and matching decoder. Two items for less than average price of the tuner only **£11.20** the two. Don't miss this—stocks will not last long.




RELAYS

12 volts, two 10 amp changeover plug in **95p**. 12v three 10 amp changeover plug in **£1.28**. 12v two changeover miniature wire ended **95p**. 12v open single screw fixing two 10 amp changeovers **85p**. 12v open three 10 amp changeovers **£1.25**. Latching relay mains operated 2 c/o contacts **£2.11**. Mains operated three 10 amp changeovers open type one screw fixing **£1.25**. Many other types, with different coil voltages and contact arrangements are in stock, enquiries invited.

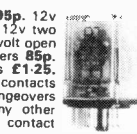

TANGENTIAL HEATER UNIT

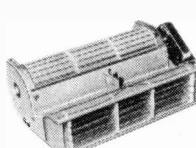

A most efficient and quiet running blower-heater by Solatron same type as is fitted to many famous name heaters—Comprises mains induction motor—long turbo fan—split 2 kw heating element and thermostatic safety trip—simply connect to the mains for immediate heat—mount in a simple wooden or metal case or mount direct onto base of say kitchen unit—price **£4.95** post **£1.50** control switch to give 2kw, 1kw, cold blow or off available **60** extra.

3KW MODEL **£5.95** + **£1.50** P & P

Terms. Prices include Post & VAT. But orders under **£6.00** please add 50p to offset packing. Bulk enquiries—Please Phone for Generous Discounts **688 1833**.

J. BULL (ELECTRICAL) LTD

(Dept. PE), 103 TAMWORTH RD. CROYDON CR9 1SG

IT'S FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear.—It's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lists.

FM Tuner and decoder, 2 very well made (Japan) units, nice clear dial, excellent reproduction, **£11.20** the pair.
12 Volt Heavy Duty Relay, plug in type has three pairs of 10 amp changeover contacts. A transparent dust cover, price **£1.08** suitable 1 pin base 45.
4 Changeover Relay, upright mounting 4 sets of 10 amps changeover contacts, mains voltage coil **£1.72**
12 Volt Pump. Designed we believe as a bilge pump, this is 12 volt AC/DC motor coupled by a long enclosed shaft to a submersible pump. Suitable for water or most any fluids. Price **£12.50**.

Just arrived. Fruit machines, working order, very impressive choice of several but very heavy so you must collect. **£50**.
High Load 24 Hour Clock Switch, made by the famous AEG Company for normal mains but with clockwork reserve has load capacity of 80 amps at 240V 50HZ. Therefore suitable for dealing with large loads of say shop lighting, water heating, storage heaters etc. Has triggers for on and off once per 24 hours but extra triggers will be available. Price **£1.50** per pair. Size of clock approximately 8" x 5" x 5", totally enclosed but has lift up flap for ease of altering switching times. Price **£7.50**.

Enclosed 24 Hour Clock, with contacts for breaking 10-12 amps at 240 volts. This one has two sets of on/off per 24 hours, price **£7.00**.

Light Dimmer, our timer module with small mods makes an excellent light dimmer. Contains a 4 amp 400V-SCR so it should be suitable for loads approaching 1KW. Price of module and instructions **£2.25**.

Push Fit Solenoids, mains operated solenoids which will push as well as pull or instead of pull. Very heavy duty, estimate this at 20lbs push or pull. 1½" x 3½" x 4" made Magnetic Devices Co. **£7.50**

Fleshing Lights, chasing lights, random flashes, strobe devices etc. can easily be achieved using our disco switches. These switches are ex-equipment but guaranteed perfect and supplied suitable for mains working. To get some idea of the loading suitable for the light pipe or Catherine Wheel effect order the 12 switch model with light pipe data model, interconnecting the switches to give fastest speed. 6 Switch model **£5.9** Switch Model **£9.75**. 12 Switch model **£6.25**

Reed Switches, standard 60 watt glass type. Normal open contacts glass lengths 2" diameter $\frac{1}{16}$ " 10 for **£1**. 100 for **£8**. 1000 for **£70**.
Flat Reed Switches, for stacking, greater quantity in confined space. Price **50p**.

Single Ended Types for jobs where it is not easy to bring a lead to each end. **75p** each. In these switches are normally open but can be biased to a normally closed position by fitting a magnet adjacent. The reed switch would then be opened by a magnet of opposite polarity being brought up to it.
Ceramic Magnets suitable for operating reed switches, central fixing hole. 10 for **£1**.

Music Centre Transformer 12-0-12 at 1 amp and 9 volt at ½ amp. Normal primary, uprighting, impregnated and varnished for quiet operation. Price **£3.50**.

W Shaped Fluorescent Tubes for porch light, box signs or where you want light evenly spaced over a confined area of approx. 10" x 10". 30 watts, made by Philips price **£2.24**.
Extension Speakers 8 ohm 4-5 watts handling power. We have 5 or 6 different models in stock, cheapest being the Partytime at **£3.95** each, again only really a bargain for callers as postage is **£1.50** per speaker.

T.V. Monitors, an item for callers, believed to be in good working order, switchable thro' 405-525 & 625, 21" tube line systems, normal controls, volume, brightness, contrast, width etc. Price **£16.20**, 12" model **£18**, suitable for conversion to special purpose scope, etc.

Auto Transformers for working American tools and equipment, completely enclosed in sheet metal case with American type flat output socket made for computer so obviously first class 500 watts. With cang handle, offered at about half price only **£15**. These may be a bit soiled but are fully guaranteed. Similar but 1000 watt **£25.50**.

Car Starter Charger Kit. New version. We supply two 10 amp rectifiers. 250V transformer and the start charge switch with instructions, price **£9.75**. This is probably one of the most useful pieces of equipment you can have in your garage. Sooner or later you or someone will leave something on and you will have a flat battery, this starter will get you away usually in less than 5 minutes.

Resistor Counter by Veederroot Company, 230/240V mains operated. Intended for surface mounting has a fixing flange at the bottom. Price **£2.16**.

12V Drip proof Relay, Specially designed for going under the bonnet of a car, made by one of our big manufacturers, this really has a removable semi-hard rubber cover. Contacts look suitable for up to 10 amps so this could be the right one if you are thinking about making an anti-theft device. Price **£1** + 8p.

High Speed Uniselectors. As many customers know, we have a very comprehensive stock of uniselectors as used in automatic telephone exchanges, light flashing device etc. etc. Just arrived, however, is a high speed model made by famous Plessey, this is 2 pole 32 way with make before break wipers, overall size approx. 4" x 3" x 2½", price **£3.50** + 28p.

Pneumatic Ram for lifting, thrusting, pulling etc., etc. has 2½" travel, looks large enough to open doors, lift, staircase, ventilators etc. Price **£7.00**.

Solder Gun Bargain. The ETP, this is 100 watt solder gun, a very well made tool with lamp to illuminate work, has double insulated mains transformer and is built into the shockproof thermoplastic case. Comes complete with spare tips. Mains operated of course. Price **£4.50**.


Interested in Tape Control. American made tape punches, really beautiful units full of sophisticated parts, designed we believe to automatically operate typewriters, and they can of course be used to operate other punch tape controlled machines. Reference number is NCR Class 461-2 reference 205 H8 R56. We believe these are 8 bit paper tape punches, powered from 115V 50Hz in very good condition with tape **£16.00**, carriage is **£3.20**.

Memories. The memory units which work with these tape punches, again by NCR, are in very good condition and we believe in working order. Price and details on request.

Tangential Blowers. 12" long with powerful induction motor ideal for blowing heaters or general air extraction or circulation, offered at low price of **£2.70**. The motors are 110V so you will have to work them in pairs or through a dropper or mains transformer. Post **£1.08** for one or two.

Digital Panel made for the G.P.O. for incorporation, we understand, in push button dialling units, this has the usual 10 digits, each of which when depressed operated a two pole changeover switch. Really a beautifully made size approximately 4" square. Price **£3.78**.

INTER-LOCKING PLASTIC STORAGE DRAWERS

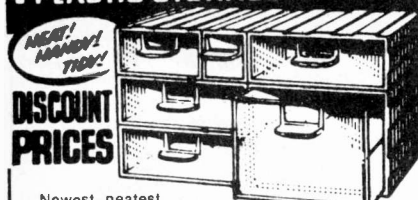

Neatest, newest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2½in x 2½in). £2.90 DOZEN.

DOUBLE UNITS (2D) (5in x 4½in x 2½in). £4.90 DOZEN.

TREBLE (3D) £4.90 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £7.25 for 8.

EXTRA LARGE SIZE (6D1) £6.25 for 8.

PLUS QUANTITY DISCOUNTS

Orders over £20, less 5%.
Orders over £60, less 7½%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES Please add 8% V.A.T. to total remittance. All prices correct at time of going to press.


FLAIRLINE SUPPLIES

(Dept. PE4)


124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

NEW for electronic design engineers!

FIX-PRINT JIG for printed circuits

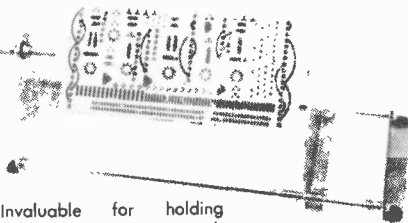

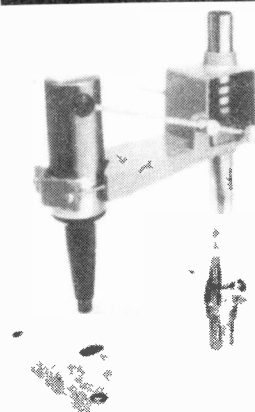Invaluable for holding P.C.B.s and other panels when inserting and soldering components. Can be adjusted to suit work up to 280mm, rotated to gain access to reverse side and locks in any position. All metal. Price £10 inc. VAT. p. & p. £1.



S2

Drill Stand

Robust, all metal with ample throat dimensions. Adjustable height cantilever with lever actuated feed. Spring return. Will accept both P1 and P2 Mk 2 drills. Price £18.50 inc. VAT. p. & p. 106p.

P2 Mk 2 Drill £18.00 p. & p. 86p
In case, room for transformer £19.50 p. & p. 86p
In case with vari/transformer £29.00 p. & p. 86p

S1 Drill Stand

Constructed to take the popular P1 drill and ensure a high degree of accuracy in all types of electrical precision work.

Price £5.13 inc. VAT. p. & p. 38p

P1 Drill £9.67 inc. VAT.

p. & p. 38p.

Write or phone for details.

Sole UK Distributors

PRECISION PETITE LTD

119a HIGH STREET
TEDDINGTON MIDDLESEX TW11 8HG

TEL: 01-977 0878

AN INTRODUCTION TO MICROCOMPUTERS

VOL 0 - BEGINNERS BOOK Price: £5.30
written for the complete beginner explains what a computer system consists of - its component parts and what they can do for you.

VOL I - BASIC CONCEPTS Price: £5.30
takes you by the hand from elementary logic and simple binary arithmetic, every aspect of microcomputers is covered.

VOL II - SOME REAL PRODUCTS Price: £10.80
covers real microcomputers in considerable detail. Every major microcomputer 4 bit, 8 bit or 16 bit is described. More than 20 microcomputers in all.

8080 PROGRAMMING Price: £5.30
for logic design.

SOME COMMON BASIC PROGRAMS Price: £6.30
describes 76 short programs.

6800 PROGRAMMING Price: £5.30
for logic design.

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.


BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

'COMPUTER CHESS CHALLENGER'

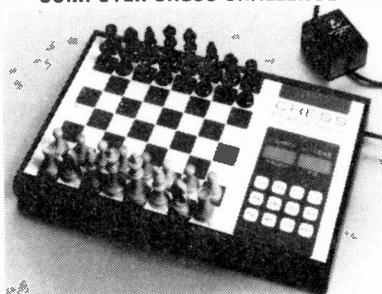

IT'S YOU AGAINST THE COMPUTER (IN YOUR OWN HOME!)

A Microcomputer, programmed to challenge you at one of THREE levels to match and improve your game. With this unique game, there is no need to find an opponent! You simply enter your moves, then 5-40 seconds later, after analysing the new position, the computer will respond!

This amazing microprocessor computer is supplied complete with Chessmen, comprehensive instructions, and mains adaptor; and is fully guaranteed. You can now play chess when you are ready, day or night, without the bother of finding a chess partner.

The 'COMPUTER CHESS CHALLENGER' has many other features to intrigue and excite the chess enthusiast, whether young or old, including: Castling and en passant, position verification by computer memory recall. You can even set up chess problems on the board! Available by mail order post free. Price: £185.00 (SINGLE level model available at £135.00).

Write or telephone now for full colour literature and data sheets.

COMPUTER BACKGAMMON GAME NOW AVAILABLE - Write or 'phone for full details. Sinclair Microvision Pocket Television - Write or 'phone for full details.

We offer SEIKO watches at discount prices - SAE. We accept company purchase orders by telephone. Scientific calculators - all brands - supplied at discount prices - SAE. We accept payment by Access - just send your number.

GEMINI ELECTRONICS

3 Branksome Avenue, Prestwich,
Manchester M25 5AG.

Tel: 061-773 4467.

EXPORT ORDERS WELCOME

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.
6.3V 1.5A £2.45; 3A £2.85; 6A CT £5.30; 12V 1.5A £2.85; 3A CT £5.30; 6A CT £6.85; 18V 1.5A CT £5.30; 24V 1.5A CT £5.30; 3A CT £6.85; 6A CT £14.00; 8A CT £23.75; 12A CT £30.00; 40V 3A CT £9.75.

TWIN SEC TRANSFORMERS: Prim 240V ac.
6V 0.6A + 6V 0.6A, 9V 0.4A + 9V 0.4A; 12V 0.25A + 12V 0.25A, 20V 0.15A + 20V 0.15A; all at £3.25 each; 15V 0.75A + 15V 0.75A £4.85; 18V 1.5A + 15V 1.5A £6.85; 18V 1A + 18V 1A £6.10; 18V 1.5A + 18V 1.5A £7.30; 20V 1.5A + 20V 1.5A £7.30; 12V 4A + 12V 4A £8.10; 25V 2A + 25V 2A £8.10.

MIDGET RECTIFIER TRANSFORMERS: 240V ac.
6.0-6V 1.5A or 9.0-9V 1A £2.45 each; 12.0-12V 1A or 20.0-20V 0.75A £2.95 each; 9.0-9V 0.3A or 12.0-12V 0.25A or 20.0-20V 0.15A £2.95 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.
0-10-12-14-16-18V 2A £4.85; 4A £6.50; 0-12-15-20-24-30V 2A £5.65; 4A £8.90; 0-5-20-30-60V 1A £6.75; 2A £9.75; 0-40-50-60-80-100-110V 1A £9.70.

MAINS TRANSFORMERS SPECIAL OFFER: Prim 240V ac.
250-0-250V 60Ma 6.3V 1A £1.50; 250V 100Ma 6.3V 2A £2; 9V 3A £2; 23V 0.5A 85p; 20W Auto, 110/240V £1.75.

SPEAKER AUTO MATCHING TRANSFORMERS
12W, 3 to 8 or 15 up or down; £2.50.

LOUDSPEAKERS

35 or 45mm 2½in 8Ω, 2½in 8 or 25Ω, 2½in 8 or 80Ω, 3in 35Ω, 3½in 3, 16 or 80Ω, all at £1.10 each; 7 x 4in 3, 8, 16, 25 or 80Ω, £1.75; 8 x 5in 4, 8, or 25Ω, £2.50; 8in 8Ω, £2.50.

"INSTANT" BULK CASSETTE TAPE ERASER

Instant erasure of cassettes and tape spools, any diameter, demagnetises tape heads, 200/240V ac £5.50.

POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.
New, British manufacture, smoothed d.c. output 20V 1.5A, plus stabilised output of 15V 100Ma, plus 12V ac 0.5A output, complete with diagram, £3.00.

CONDENSERS

Electrolytic 1000/50V 30p; 2000/30V 30p; 1200/75V 50p; 3900/100V £1.25; Paper tubular W/E 0.47/600V, 2.2/400V, 4.7/160V all at 25p each, £10 per 100.

EDGEWISE LEVEL METER FSD 200 µA

Size 19 x 18 x 20mm 800Ω, £1.10.

SYNCHRONOUS GEARED MOTORS, 240V ac.

Brand new, built in gearbox, 1, 6, 8, or 20 RPH all at £1.20 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS

P.P. sec. tapped 3-8-15, A-A 6K 30W £9.00; A-A 3K 50W £12.00; 100W (EL34, KT88, etc) £18.75.

G.E.C. MANUAL OF POWER AMPLIFIERS

Covers valve amplifiers 30W to 400W 75p.

MULTI WAY CABLE, SCREENED PVC COVERED

36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; fig 8 stereo 15p per metre, 4 way individually screened 20p per metre.

TWIN FIG 8 CABLE

Polarised, 100 metre £4.50.

MINI 3 CORE CIRCULAR CABLE, 19 x .10mm

Ideal for speakers, intercoms, telephones, etc £4.50 100m.

ALL PRICES INCLUDE V.A.T.

CARRIAGE EXTRA ON ALL ORDERS

Callers by appointment only

S.A.E. enquiries, lists

46 Kenilworth Road, Edgware, Middx H8 8YG

Tel: 01-958 9314

15-240 WATTS!

HY5 Pre-amplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack, multi-function equalisation low noise, low distortion, high overload, two simply combined for stereo

APPLICATIONS: hi-fi, mixers, disco, guitar and organ, public address

SPECIFICATION: Inputs—magnetic pick-up 3mV, ceramic pick-up 30mV, tuner 100mV, microphone 10mV, auxiliary 3-100mV, input impedance 47k Ω at 1kHz Outputs—tape 100mV, main output 500mV R.M.S. Active Tone Controls—treble \pm 12dB at 10kHz bass \pm 12dB at 100Hz Distortion—0.1% at 1kHz, signal/noise ratio 68dB Overload—38dB on magnetic pick-up Supply Voltage— \pm 16-50V

Price £5.22 + 65p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



HY30 15W into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available.

FEATURES: complete kit, low distortion, short, open and thermal protection, easy to build

APPLICATIONS: updating audio equipment, guitar practice amplifier, test amplifier, audio oscillator

SPECIFICATION: Output Power—15W R.M.S. into 8 Ω Distortion—0.1% at 15W Input Sensitivity—500mV Frequency Response—10Hz-16kHz -3dB

Price £5.22 + 65p VAT. P. & P. free

HY50 25W into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: low distortion, integral heatsink, only five connections, 7 amp output transistors, no external components

APPLICATIONS: medium power hi-fi systems, low power disco, guitar amplifier

SPECIFICATION: Input Sensitivity—500mV Output Power—25W R.M.S. into 8 Ω Load Impedance—4-16 Ω Distortion—0.04% at 25W at 1kHz Signal Noise Ratio—75dB Frequency Response—10Hz-45kHz -3dB Supply Voltage— \pm 25V Size—105 x 50 x 25mm

Price £6.82 + 85p VAT. P. & P. free



HY120 60W into 8 Ω


The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion, integral heatsink, load line protection, thermal protection, five connections, no external components

APPLICATIONS: hi-fi, high quality disco, public address, monitor amplifier, guitar and organ

SPECIFICATION: Input Sensitivity—500mV Output Power—60W R.M.S. into 8 Ω Load Impedance—4-16 Ω Distortion—0.04% at 60W at 1kHz Signal Noise Ratio—90dB Frequency Response—10Hz-45kHz -3dB Supply Voltage— \pm 35V Size—114 x 50 x 85mm

Price £15.84 + £1.27 VAT. P. & P. free

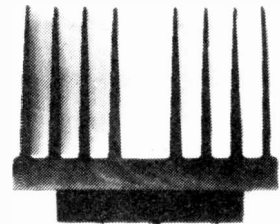

HY200 120W into 8 Ω


The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown, very low distortion, load line protection, integral heatsink, no external components

APPLICATIONS: hi-fi, disco, monitor, power slave, industrial, public address

SPECIFICATION: Input Sensitivity—500mV Output Power—120W R.M.S. into 8 Ω Load Impedance—4-16 Ω Distortion—0.05% at 100W at 1kHz Signal Noise Ratio—96dB Frequency Response—10Hz-45kHz -3dB Supply Voltage— \pm 45V Size—114 x 50 x 85mm

Price £23.32 + £1.87 VAT. P. & P. free

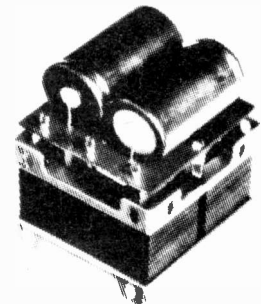

HY400 240W into 4 Ω

The HY400 is I.L.P.'s Big Daddy of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown, very low distortion, load line protection, no external components

APPLICATIONS: public address, disco, power slave, industrial

SPECIFICATION: Output Power—240W R.M.S. into 4 Ω Load Impedance—4-16 Ω Distortion—0.1% at 240W at 1kHz Signal Noise Ratio—94dB Frequency Response—10Hz-45kHz -3dB Supply Voltage— \pm 45V Input Sensitivity—500mV Size—114 x 100 x 85mm

Price £32.17 + £2.75 VAT. P. & P. free

POWER SUPPLIES: PSU36—suitable for two HY30s £5.22 + 65p VAT. P. & P. free. PSU50—suitable for two HY50s £6.82 + 85p VAT. P. & P. free. PSU70—suitable for two HY120s £13.75 + 1.10 VAT. P. & P. free. PSU90—suitable for one HY200 £12.85 + £1.01 VAT. P. & P. free. PSU100—suitable for two HY200s or one HY400 £23.10 + £1.85 VAT. P. & P. free.

I.L.P. Electronics Ltd., Crossland House, Nackington, Canterbury, Kent CT4 7AD

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply

Total Purchase price

I Enclose: Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

Registered office No. 1032630

GREAT SOUND – GREAT VALUE!

Stirling Sound Disco 2 Mixer Control unit + power supply



£39.95
inc V.A.T. & post
free in U.K.

By designing and manufacturing in our own Essex factory, with strict material control and stage by stage checking and then selling direct to YOU, the customer, we can save you pounds, offer better service and guarantee satisfaction. Our latest modular assembly, Disco 2, has already been thoroughly field tested and is ready for immediate service under the toughest working conditions.

- INPUTS – Left deck, right deck, mic. and aux.
- INPUT IMPEDANCE – 47K ohms
- POWER SOURCE – 220-240V. A.C. Mains
- CONTROLS – Mains on-off, master volume, bass ± 15 db, treble ± 15 db, L and R mixing, L and R motor switches, selector switch for P.F.L. (Pre-Fade Listening), headphone volume; mic. vol., aux. vol., LED indicators on mains and decks on/off switches.
- HEADPHONE AMPLIFIER – Powerful 2 watts into 8 ohms; separate vol. control.
- TERMINATIONS – Five $\frac{1}{4}$ " jack sockets – 2 input; 2 output, headphones.
- SIZE – $23\frac{1}{2}$ " x $3\frac{3}{4}$ " x $2\frac{1}{2}$ " max. depth to rear (plus separate power unit). Panel in matt black with controls sensibly grouped for easy handling.

■ PRICE – Post free, with power unit and inc. V.A.T. **£39.95**

Delivery ex-stock, built, tested and guaranteed.
Suitable Stirling Sound power amps with heat sinks and power supply units – 140PH (40 watts RMS) £18. 160PH (60 watts RMS) £22. 1100PH (100 watts RMS) £26.75.

Mail Orders to Dept. PE4

STIRLING SOUND, 37 VANGUARD WAY, SHOEBURNESS, ESSEX (03708) 5543. Shop & Showroom 220/224 West Rd., Westcliff-on-Sea (0372) 351048

OTHER STIRLING SOUND DISCO/P.A. ITEMS

■ BASIC CONSTRUCTIONAL MODULES

SS 104/2 Two channel mixer stage **£3.75**
SS 104/4 Four channel mixer stage **£7.00**
SS DTM Output control stage 30db variation on both treble and bass. Master vol. control. 3mV in for 2V out. 18V working voltage. **£6.75**

■ INTEGRATED POWER AMPLIFIERS

Ready built in cases, tested and guaranteed – 60 watts R.M.S. into 4 ohms.
POWER AMP 60 – with two channel mixer **£48.00**
POWER AMP 40 – watts R.M.S. into 4 ohms with two channel mixer **£43.00**
POWER AMP 100 – 100 watts R.M.S. into 4 ohms with 4 channel mixer **£85.00**
100 watt SLAVE AMP **£50.00**

■ READY BUILT ITEMS TESTED AND GUARANTEED

SSTL 3/250B Sound to light unit 3 channels, 250 w. each **£23.95**
SSTL3/1000B Sound to light unit 3 channels, 1000 w. each **£25.95**
Also loudspeakers, twin T/T consoles, etc.

■ STIRLING SOUND-LIGHT MODULES


SSTL3/250 Three channels, each 250 watts output **£9.25**
SSTL3/1000 Three channels, each 1000 watts **£11.50**

TO ORDER BY ACCESS OR BARCLAYCARD JUST WRITE OR PHONE IN YOUR NUMBER. AUDIO CONSTRUCTORS, HAVE YOU HAD YOUR LATEST STIRLING SOUND CATALOGUE SHEETS YET? FREE ON REQUEST.

ALL PRICES QUOTED INCLUDE VAT.
GOODS SENT POST FREE IN U.K. with C.W.O. orders except some heavy ready built items. Prices are subject to amendment without notice.

Stirling
Sound

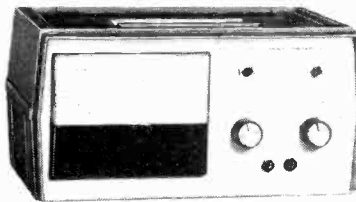
Over 200 kits in the free Heathkit Catalogue



NEW 4 Function
Solid State Multimeter
— One of a whole range
of test equipment




NEW Digital Clock
with repeater alarm

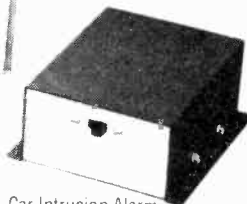

Car Intrusion Alarm
Gives a distinctive
yelping sound signal
the moment your car
is tampered with

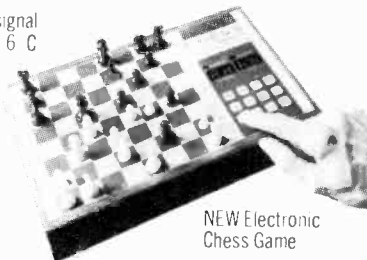Freezer Alarm Gives audible signal
if freezer temperature rises to 6°C
for any reason



NEW Electronic
Chess Game

The Heathkit catalogue is packed with top quality kits — hundreds of practical and fascinating items which you can build yourself.

Send for
your copy now!

To Heath (Gloucester) Ltd.
Department PE 48
Bristol Road, Gloucester, GL2 6EE.

Please send a copy of the Heathkit Catalogue.
I enclose 11p in stamps to cover postage only.

Name _____

Address _____

Soldering
iron offer
FREE

When you receive
your catalogue
you'll get details of
this free offer worth
approximately £4.75

HEATH
Schlumberger

The world's
biggest producers
of electronic kits.

ACCESS AND
BARCLAYCARD
WELCOMED

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (Gloucester 29451).



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

CHIPS AND THINGS

I.C.s at give-away prices! — you test you save!
Untested devices (NDT manufacturers rejects, fallouts etc.)

- PACK E1** (80% guaranteed good). 5 × MAN3 0.127" 7 segment LED displays **£1.00**
- PACK E2** (100% good). 1 × 8 digit (plus overflow) 0.33" 7 segment Liquid Crystal calculator style display **£3.95**
- PACK M1** (100% guaranteed good). 2 × Calculator keyboards **£0.00**
- PACK O1** (80% guaranteed good). 15 × Logic I.C.s mainly dual J-K DTL flip-flops, compatible with TTL. Could replace those costly TTL flip-flops in most projects **£1.25**
- PACK D2**. 25 × SN7400 type I.C.s 100 two ip NAND gates. We guarantee 50 good **£1.25**
- PACK L1** (marked and unmarked). 20 × Assorted Op-Amps. Could include LM301, 741, 709, 555 etc. **£1.25**
- PACK L2**. 20 × LM709 Op-Amps (8 lead TO5) **£1.50**

Could be they are all O.K., but as they're untested — we don't know. For packs with no stated guarantee we will guarantee it works out much cheaper than average mail order prices buying this way. Satisfaction guaranteed or return complete pack for replacement or refund.

MAIL ORDER ONLY — NO CALLERS
POSTAGE & PACKING add 20p.

CODESPEED, P.O. Box 23, 34 Seafield Road, Copnor,
Portsmouth, Hants. PO3 5BJ.

L.B. ELECTRONICS, BF195 9p, BC213 9p, BC108C 10p, OCP70 16p, BXY49 38p, IN4148 4p, 3-3V, 24V, zeners 5p, 2102 (500NS) + data £1.50, 8080A £16, 1702A £7.50, CD4250 70p, 741 20p, 741 TO99 (DIL) 30p, 555 45p, 74H00 20p, 7 way DIL switches 60p, min push button switches (change over) 40p, 75450 38p, Penwell Thermistors, pair potted + lead-plug 20p, PCB 1 watt amplifier LM 380 etc £1.20, ITT 5870ST nixi + data 50p, Sperry SP425-09 (9 digit 7 seg) + data £1, 747 6" (Red) £1.35, D.P.M. Display 44 digit (LED) with bezel £2.50. P & P 10p. L.B. ELECTRONICS, 43 Westcott, Hayes, Middx. UB4 8AH.

New Stereo Modules by Famous Manufacturer

Stereo amplifier, 10w × 10w inc. rect **£4.90 each**
AS above plus pre-amp with 4 slider controls, 6 push buttons **£11.90 each**

Speakers to suit 8" elec 8Q 15wpk **£4.25 each**
Stereo gram amplifiers 3w × 3w with pre-amp 64 controls **£5.90 each**

Mono VHF-FM rec. module varicap tuner, I.F. filter & IC, demod. O.P. 300mV **£4.65**
Prices inc. P&P & VAT. Cash with order.

ELECTRONICAL SUPPLIES, CROYDON
40 Lower Addiscombe Road, Croydon, Surrey CR0 6AA

SMALL ADS

The prepaid rate for classified advertisements is 18 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

VALVES — Radios, T.V., industrial, transmitting, and projector lamps many types. We dispatch to any part of the world by return of post. Air or Sea Mail. 4000 types in stock. 1930 to 1976 obsolete types a speciality. List 30p. Projector Lamps. Quotation S.A.E. Open to callers. Mon. to Sat. 9.30-5.00, closed Wed. 1.00. We purchase all types of new and boxed valves. And projector lamps. COX RADIO (Sussex) Ltd., Dept P.E., The Parade, East Wittering, Sussex PO20 8BN. West Wittering 2023. (STD code 024366).

SOLAR CELLS

- 57mm dia 255mW **£4.90**
 25mm dia 35mW **£3.80**
 4.7mm × 9.00mm 2.5mW **£0.55**
 Booklet "SOLAR CELLS" **£0.75**
 Data Sheets on 255 & 35mW cells **£0.20**

Prices include VAT and postage. Large SAE for lists. Mail order only. Speedy service. IC's books, capacitors, solar batteries, half price bargains and surplus PCBs resistors, semiconductors etc etc

Edencombe Ltd.,

34 NATHANS ROAD, N. WEMBLEY, MIDDX HA9 3RX

COMPONENTS FOR P.E. PROJECTS. Components lists with prices available for P.E. Projects from November 1977 onwards. Send SAE stating project and month of publication (Maximum four projects per SAE). Lists sent by return together with ACE order form/catalogue. ACE MAILTRONIX, Tootal Street, Wakefield, W. Yorks. WF1 5JR.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V — 0.47, 1-0, 2-2, 4-7 and 10µF 5p; 22, 47, 51p (50V 8p); 100 7p (50V 8p); 220 8p (50V 10p); 470 11p (50V 16p); 1,000 (16V) 15p, 1,000 (25V) 18p, 1,000 (50V) 22p.

Subminiature Bead Tantalum Electrolytics — 0.1, 0.22, 0.47, 1-0, 2-2 at 35V, 4-7/25V 11p; 10/25V 13p; 22/16V, 47/6V and 100/3V 15p.

Mullard Min. Ceramic E12 Series 63V 2% — 10pF to 47pF — 3p; 56pF to 330pF 4p.

Vertical Mounting Ceramic Plate 50V — E12 series 22-1,000pF 3p and E6 series 1,500-47,000pF 2p.

Polystyrene E12 Series 63V Horizontal Mounting — 10-1,000pF 3p; 1,200-10,000pF 4p.

Mullard Polyester 250V Vertical Mounting E6 Series — 0.01-0.1 4p; 0.15, 0.22 5p; 0.33, 0.47 8p; 0.68 11p; 1-0 13p; 15 20p; 2-2 22p.

Mylar (Polyester) Film 100V Vertical Mounting — 0.001, 0.002, 0.005 3p; 0.01, 0.02 4p; 0.04, 0.05 4p.

Miniature Resistors Highest E12 Series 5%. Carbon Film 0.25W 1Ω to 10M Ω. (10% over 1M) 1p. Metal Film 0.125W, 0.25W and 0.5W 10 Ω to 2M Ω 1 1/2p. Metal Film 1W 25 Ω to 10M Ω 2p.

1N4148 3p; 1N4001 5p; 1N4007 7p; 1N4007 8p; BC107/8/9, BC147/8/9, BC157/8/9, BF194, 197 9p.

Fuses 20mm glass, 1in glass, 1in ceramic 2 1/2p.
Post 10p (free over £4). Prices inclusive of VAT.

THE C.R. SUPPLY CO.

127 Chesterfield Road, Sheffield S8 0RM

240/12-0-12V. 100mA transformers with power supply P.C.B. 4 for £1.99. T03 metal power transistors 35 for £1.99. Push to make switches Red/Y/Blue 12 for £1.99. Please add 30p P&P, VAT included. JONES SUPPLIES, 588 Ashton Road, Oldham, Lancs. 061 652 9879.

PCBs PAXOLIN 91"×8" 55p, 12"×9" 70p, 17 1/2"×9 1/2" £1.15. FIBRE GLASS DOUBLE SIDED 13" × 6" £1.30. 12"×10 1/2" £2.10. UNIT WITH 8 SILICON DIODES 600V 20A, 8 SCRS 3 or 400V/6A 6 VINITORS V.W. RES. ETC. £6.75. 300 SMALL COMPONENTS, TRANS, DIODES £1.30. 715 ASSORTED COMPONENTS £2.95. LIST 15p REFUNDABLE POST 20p UNDER £1. INSURANCE ADD 15p.

J.W.B. RADIO
 2 BARNFIELD CRESCENT, SALE,
 CHESHIRE M33 1NL

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs, 0945-4188. Immediate settlement.

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.



SPECIAL OFFERS.

Buy NOW while stocks last. PRICES INCLUDE V.A.T.

RESISTORS 1/4W 5% carbon film E24 range 10R-1M.	3p each, 100 of one value £1.05, 1000 of mixed 100g	£8.95	
E12 series pack 10R-1M, 10 of each value (610 resistors)		£6.40	
E24 series pack 10R-1M, 10 of each value (1210 resistors)		£12.70	
E12-E24 expansion packs 10 of each value (600 resistors)		£6.30	
TRANSISTORS			
BC107/8/9C	10p	BC182/184L	12p
BC171	15p	BC212L	12p
2N2926Y	10p	2N2926G	11p
2N3054	48p	2N3055	48p
INTEGRATED CIRCUITS			
CA3089E IF System	£1.99	CA3090AQ Ster. Decoder	£3.99
741 8 pin DIL Op Amp	26p	748 LM Op Amp	38p
709 8 pin DIL Op Amp	27p	723 Voltage Regulator	54p
LM3900 Quad Amp	76p	LM380 2W Amp	99p
LED's Red 3 or 5mm	13p	Pack 10 LED's (seconds)	89p
RECTIFIERS 1N4001	5p	1A/50V Bridge	29p
POLYESTER CAPACITORS (250V)			
0 1µF 3p.	0 22µF 4p.	0 47µF 7p.	1 0µF 12p.

Please add 15p for Postage. Send 2 stamps for Catalogue. BARCLAYCARD phone service available. Tel. 0473 50975.

FRASER-MANNING LTD.,
 26 HERVEY STREET, IPSWICH, IP4 2ES.

ELECTRONIC, T.V. AND AUDIO COMPONENTS AND ACCESSORIES. New, surplus and ex-equipment. Write to us for your requirements. S.A.E. Please. Lists 15p. We always do our best to help. J. P. S. 9 East Street, Colne, Huntingdon, Cambs.

LADDERS

LADDERS. Varished 25ft. Extd. £35.70. Carr. £2.40. Leaflet. Callers welcome. Open Sat. Ladder Centre. (PEE4) Halesfield (1) Telford, Salop, Tel: 586644.

FOR SALE

SEEN MY CAT? 5000 Odds and ends. Mechanical Electrical. Cat free. Whiston, Dept. PRE. New Mills, Stockport.

MICROPROCESSOR introk. SC/MP, never been assembled, only board removed from shrink-wrap. Reason for sale — purchaser blind. £55 n.o.o. Phone 078-16 3957.

550' of Triple play tape (Ex-Recording Studio) on 3" unbreakable reel. Ideal for messages. Bargain at 25p each. P&P 30p, 10 1/2" Metal Spool (NAB) in sturdy Box 80p, p/p 30p. R. Southern. 551 Chester Old Road, Bolton, Lancs. BL1 6AE.

PRACTICAL ELECTRONICS Sports Centre new chip £12, or nearest offer. Needs attention. Mark Andrews, Bank View, Parson Drive, Wisbech, Cambs.

MINISONIC Synthesiser plus many extras, needs attention. £125 n.o.o. Tel: Banbury 51534.

P.E. MULTIMETER

ANTI-LOCK-UP KIT £1.20 inc.

FULL SPEC DL704s NOW £1.50 each

P.C. BOARDS £2.65. All Parts Available

S.A.E. for details:

SPARKS DEVELOPMENTS

53 North Street, Melbourne, Derby.

NEW ISSUES of "Practical Electronics" available from April 1974 edition up to date. Price 65p each. Post Free. BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. (Tel: 0423) 55885.

PRACTICAL ELECTRONICS 1967-1977 FOR SALE. Mainstone, Chandlersford 4882. Evenings — Weekends.

ORGAN PARTS. abandoned project. C-C 49 note Keyboard. Plastic £14 wood £7. Reverb & Valve driver £7. Metal Pedal Board £12. 43 stops £4. S.A.E. please. 31 Steele Road, Wellingborough.

WANTED

WANTED - NEW VALVES. Transistors. Top Prices, popular types. Kensington Supplies, (B) 367 Kensington Street, Bradford 8, Yorkshire.

"RADIO AND TELEVISION Servicing". Books wanted from 1964-1965 edition up to date. £3.00 plus postage paid per copy by return of post. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Telephone (0423) 55885.

WANTED. Synthesisers, modules, etc. Cash or part exchange with Farisa Organ. Phone Wolverhampton 732306. After 5pm.

BOOKS AND PUBLICATIONS

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £1.50, request free circuit diagram. Stamp brings details unique. TV Publications, (AUSEPE) 76 Church Street, Larkhall, Lanarkshire.

ELECTRONIC TIMESAVER Learning Program. 30-stage easy-learn electronics program including boards, terminals, plans and circuit know-how. Ideal for beginners, students, schools and colleges. Special intro-offer £4.75. Money back if not delighted. TECHNOCENTRE (PE), PO Box 33, 54 Adroit Road, Middlesbrough.

PERSONAL

ELECTRONICS SERVICE Engineer required to give part-time tuition. Please Ring 599-1403.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc. 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

ELECTRICAL

LIST No. 28 now ready. Styli illustrated equivalents also Cartridges, Leads, etc., free for long S.A.E. Felstead Electronics, (PE), Longley Lane, Gatley, Cheadle, Cheshire. SK8 1EE.

EDUCATIONAL

WHY NOT BE A PROFESSIONAL? New T.E.C. Higher certificate in Marine Electronics. Apply Maritime Studies Department, Lowestoft College of Further Education, Lowestoft, Suffolk.

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272S Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272S Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272S Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

SITUATIONS VACANT

Radio Technicians

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over.

STANDARDS required call for a sound knowledge of the principles of electricity and radio, together with 2 years' experience of using and maintaining radio and electronic test gear.

DUTIES cover highly skilled telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer and analytic machinery.

QUALIFICATIONS: Candidates must hold either the City and Guilds Telecommunications Part 1 (Intermediate) Certificate or equivalent HM Forces qualifications.

SALARY (inc. supps.) from £2,673 at 19 to £3,379 at 25 (highest pay on entry) rising to £3,883 with opportunity for advancement to higher grades up to £4,297 with a few posts carrying still higher salaries.

Opportunities for service overseas.

Further particulars and application forms available from:

GCHQ

Recruitment Officer,
Government Communications,
GCHQ, Oakley, Priors Road,
Cheltenham, GL52 5AJ.
Cheltenham (0242) 21491 Ext 2270



BBC


REPAIR AND CALIBRATION TECHNICIAN

The BBC has a vacancy for a technician to look after the repair and calibration of a wide range of test equipment used in its Test Laboratory in Chiswick. The work is interesting and varied and the instruments in use include d.v.m.'s, oscilloscopes, sweep generators, spectrum analysers, signal generators, used over the frequency spectrum from d.c. to 1GHz.

A suitable technician, male or female, will have a good basic knowledge of electronics and the techniques used in test equipment, and will have had considerable experience of repair and calibration or similar testing work.

Starting salary depending on experience will be in the range of £3535 to £3835 rising by increments to £4285.

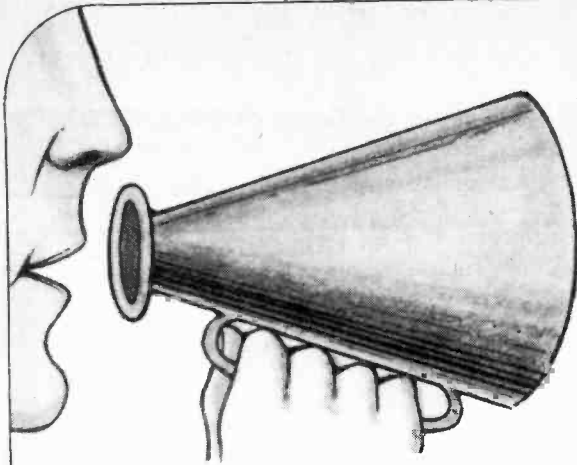For further details please ring Mr. P. Green, No: 01-994 8541 Ext: 232, or write for an application form to the Engineering Recruitment Officer, BBC, Broadcasting House, London W1A 1AA, quoting reference 78. E. 2033/PE and enclosing a foolscap envelope. Closing date for completed application forms is fourteen days after publication.



Calling all professional electronics engineers and amateur electronics enthusiasts

The Electronics Industry has always been a breeding ground of professional talent, particularly within the specialist areas. At EMI, we have always attracted talented people, graduates and specialist engineers with valuable experience to contribute.

We're a flexible company, which is undoubtedly one of the attractions to professional people. We're also an acknowledged major force in the industry. Our training is excellent, our products ahead of the field. Our expertise has changed the face of electronics time and time again.

People joining us at any level rapidly acquire a great deal of knowledge and experience which puts them on a steady path to promotion. And right now, we have a very special need for a limited number of men and women as Semi-Conductor Consultant Engineers within our Engineering Standards Group.

We are extending our invitation to both experienced Electronics Engineers and men and women who have a particular interest, though not necessarily experience, in electronics as a hobby.

Your role with EMI Electronics will be to advise engineers, production personnel, buyers and Q.A. staff on various aspects of semi-

conductor and micro-processor products, to liaise with suppliers and initiate/draft standards. You will also be expected to undertake laboratory testing, evaluate devices and be responsible for seeking out new products.

These varied duties require people with at least HNC qualifications but probably more important for this work, is the right personality. You must enjoy resolving technical problems and yet be capable of confident and effective communication with a wide and varied range of people. Knowledge of passive components, the foreign components markets and a working fluency in a European language, would be very useful though is not absolutely essential.

The men and women we envisage joining us will be aged between 20 and 35 and will be looking for a challenging and rewarding career with one of the major forces in international electronics.

For further information, please contact Neil Robotham, Personnel Department, EMI Limited, 135 Blyth Road, Hayes, Middlesex. Telephone 01-573 3888 or Record-a-call anytime on 01-573 5524.

EMI Electronics Ltd

A member of the EMI Group. International leaders in music, electronics and leisure

MISCELLANEOUS

ARMATURE AND COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied. All orders despatched within 24 hours.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices inclusive of P. & P. in U.K.

COPPER SUPPLIES

102 Parrswood Road, Withington, Manchester 20 Telephone 061-445 8753

CLEARING LABORATORY. Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

RECHARGEABLE BATTERIES

'AA' pencil (HP7) £1.32; sub 'C' £1.64; 'C' (HP11) £2.43; 'D' (HP2) £3.56; PP3 £4.98. Matching chargers £6.98 each except PP3 charger £5.82. Charging holders for 2, 3, 4, 5 or 6 pencils 50p. 'C' and 'D' size holders, 4 cell only, 80p. 250/12 volt inverters now available.

Prices include VAT. Add 10% post, package and insurance orders under £20. 5% over £20. S.A.E. for full details plus 75p for 'Nickel Cadmium Power' booklet. Mail orders to:

SANDWELL PLANT LTD. DEPT. P.E.

201 Monmouth Drive, Sutton Coldfield, West Midlands. Tel. 021-354 9764
Callers to T.L.C., 32 Craven Street, Charing Cross, London, WC2.

MANUFACTURERS SURPLUS Teletext Display P.C.B.'s; COLOUR. Upper/Lower case ASCII, Graphics, Flash etc. Ideal start MPU O/P onto T.V's. With cct, notes £5.94. Requires TTL, ROM. Char Gen I.C. Only £12.96. Post Free. TECHNOLOGICS, 8 Egerton St., Liverpool L8 7LY.

SPECIAL OFFER FAMOUS CARTERS

SIRENS


12V DC only 5.25
240V AC only 8.99
inclusive of VAT & P.P.
Send cheque, P.O. to

CWAS ALARM

11, Denbrook Walk
Bradford BD4 0QS
SAE for Price List



240V AC

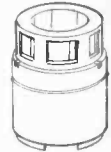

12V DC

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
Fretcloths, Coverings, Strap & Recess Handles, Feet, Castors,
Jacks & Sockets, Cannons, Bulgin 8 ways, Reverb Trays,
Locks & Hinges, Corners, Trim, Speaker Bolts etc.
Send 2 x 9p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)
Unit G, Starline Works, Grainger Road
Southend-on-Sea, Essex.

OUTSTANDING 2200 Hi-Fi FM Tuner. Full Coverage 88-102MHz. Varicap tuning. Latest silicon superhet design. Ideal for push button/manual tuning only £9.95. Unique 3300 stereo class A Amplifier, power 32 watts peak, complete stereo pre-amplifier 2 power amplifiers, all inputs accepted only £10.95. 5500 Tuner amplifier + specification as above 2 only £19.95. All equipment built, tested and guaranteed with full instructions (P&P 50p). GREGG ELECTRONICS, 86-88 Parchmore Road, Thornton Heath, Surrey.

MAKE YOUR OWN PRINTED CIRCUITS

RUB-ON TRANSFERS - Starter pack (5 sheets, lines, pads, I.C. pads) £1.30. Single Sheets 27p. **FERRIC CHLORIDE** - 1 lb bags 70p (P. & P. 40p)*. **SOLDERCON SOCKETS** - 100 65p. (quantity rates). **PLASTIC SUPPORTS** - 7 or 8 hole 6p./pair. S.A.E. lists sample. P. & P. 15p/order except*. P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE

SINTEL FOR BOOKS, CMOS AND COMPONENTS

6800 Booklet 1.80, MOT CMOS Databk 3.50, 6800 Appl Man 12.95, 6800 Prog Man 5.35, SC/MP Introkit Man 0.75 NS TTL Databk 2.10, RCA CMOS Databk 5.45, 8085 User's Man 5.15, Z80 Ass Lang Prog Man 7.50, Z80 CPU Man 5.60, Z80 CTC Spec 0.80, Z80 PIO Man 3.30. Also a full range of CMOS - send for free catalogue. MPUs: MEK6800D2 205.20, MC6820 8.66, Z80 30.72, Z80A 39.94, Z80CTC 13.82, Z80PIO 13.82, Memories: 2102-A 2.55, 2112A-4 3.13. Displays: Type FND500 C.C. 1.40, Type TIL321 C.A. 1.61, 51T01 5.29. Crystals: 32.768KHz 3.78, 5.12MHz 3.89. Clock ICs: AY51202 4.35, AY51224 3.78, MK50253 6.05. Soldercon Pins: 100 0.54, 1000 4.32, 3000 11.34. Free catalogue by return. All items C.W.O. Prices inclusive of VAT. Add 35p p&p. SINTEL, P.O. Box 75B, 209 Cowley Road, Oxford. Tel. (0865) 49791

We would like you to know that we make -

- BEC Cabinets
- Special cabinets
- Prototype printed circuits
- Instrument panels



We also have a quantity punching service, and undertake artwork

GB3/AT Cabinet

H.M. ELECTRONICS

275a Fulwood Rd : Sheffield S10 3BD TEL: (0742) 669676
Send 15p (refundable) for leaflets

AUTOMATIC ELECTRONIC Time Delays, 1KW Output, Kit £6.10, PCB/Details £1.20. Information - SAE. L. O. Green, 4 Gurney Road, Costessey, Norwich, NR5 0HA.

SPEAKER CONSTRUCTORS

Acoustically Transparent
Reticulated Polyurethane Foam

Special Dense Black Colour - $\frac{1}{2}$ " thick
Cut to size 3p per sq. inch
(includes VAT & P. & P.)

Acoustic Wadding - Mixture of synthetic and superfine glass fibre media
Ideal for packing cabinets
1 Kg. Bag £1 inc. VAT + 66p post.

AUTOMET ACOUSTICS

CHARLES LANE MILL
HASLINGDEN, ROSSDALE, LANCs.

100 WATT GUITAR/PA/MUSIC AMPLIFIER

With superb treble, bass. Overdrive, slimline. 12 months guarantee. Unbeatable offer at £39. Also twin channel with separate treble/bass per channel £48. Money returned if not absolutely delighted within 7 days. Also fuzz boxes great sound robust construction £6.60. Also 100 watt 12 in. speakers £22.50.

All inclusive of P.P. Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION
62, THORNCLIFFE AVENUE, DUKINFIELD,
CHESHIRE. TEL: 061-344 5007

BUILD YOUR OWN TV CAMERA



ONLY KNOWN HIGH PERFORMANCE SOLID STATE CAMERA IN KIT FORM. Also available factory assembled. Ideal for experimenters, industry security, education etc. *Will work with most other CCTV equipment. *Fully guaranteed. *Completely self-contained. With our modulator will connect to any domestic TV set. Model C1 complete with Vidicon £99. Less Vidicon £82.35. (Lens available as optional extra). SAE for info or phone your order through using your Barclay or Access Card.

CROFTON ELECTRONICS LIMITED
35 Grosvenor Road, Twickenham, Middlesex. 01 - 891 1923

PRACTICAL ELECTRONICS P.C.B.'s

in glass fibre tinned and drilled
Dec. 77 Car Burglar Alarm 1412-1 88p.
Feb. 78 Auto Ranging Volt Meter incl. power £3.10.
C.W.O. Please.

For full list and current boards please send S.A.E. P.C.B.'s also produced from customer's own master - please send for quote.

PROTO DESIGN

4 Highcliffe Way, Wickford, Essex, SS11 8LA

PRINTED CIRCUIT BOARD LAYOUTS from 60p per component. S.A.E. to Consultant Design Service, The Galleon, Porlock, Somerset. 862567.

THE FABULOUS D2 MICROPROCESSOR EVALUATION KIT FROM MOTOROLA.

Featuring *24 key keyboard *Seven segment display *Cassette interface *Erom & Ram Expandable *Interface Capability *Full Documentation *5 Volt power supply Required *One years FREE membership of The Amateur Computer Club with every purchase*. £176 + £1.50 P & P + 8% VAT.

ENAMELLED COPPER WIRE

	1 lb	8 oz	4 oz	2 oz
10-19	2.60	1.40	.66	.55
20-29	2.80	1.60	.85	.65
30-34	3.00	1.70	.95	.70
35-40	3.35	1.90	1.10	.79
40-43	4.50	2.50	1.90	1.25
44-46	8.00	5.00	3.00	1.65
47	8.00	5.00	3.00	1.76
48	15.00	9.00	6.00	3.30

Tinned Copper, Even Gauges 14-30 £3 per lb.
Multicore 60/40 Solder 18SWG £3.24 per lb.
Prices include P & P and VAT.
SAE brings list of copper and resistance Wires.

THE SCIENTIFIC WIRE COMPANY

PO Box 30 London E.4.
Reg. Office, 22 Coningsby Gdns.

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). BAZELLI. Dept. No. 23, St. Wilfred's, Foundry Lane, Halton, Lancaster. LA2 6LT.

BUILD THE TREASURE TRACER

- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- 4,000 already sold
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron screwdriver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped addressed envelope for leaflet

Complete Kit	£15.95	Built and tested	£20.95
Post £1.20 - £1.37 VAT		Post £1.20 - £1.77 VAT	

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD, LONDON E18 2AN (Mail Order Only)

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4.30 plus 20p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 20p P. & P.

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS

Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue. From:

RAMAR CONSTRUCTOR SERVICES,
Masons Road, Stratford upon Avon, Warwick.
Tel. 4879.

SOWTER TRANSFORMERS

FOR SOUND RECORDING AND
REPRODUCING EQUIPMENT

We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large or small quantities. Let us quote.

SOWTER TYPE 3678

A recent release
MULTITAP MICROPHONE TRANSFORMER

Primary windings for 600 ohm, 200 ohm and 60 ohm with Secondary loadings from 2K ohm to 10K ohm. Frequency response plus/minus ± 8 dB 20 Hz to 25 KHz. Contained in well finished Mumetal box. 33mm diameter by 22mm high, with colour coded end leads, low distortion. DELIVERY (small quantities) EX-STOCK. HIGHLY COMPETITIVE PRICE. FULL DETAILS ON REQUEST.

E. A. SOWTER LTD.

Transformer Manufacturers and Designers
The Boat Yard, Cullingham Road
Ipswich, Tel. 0473 219390 & 52794

SCOPE CALIBRATOR, portable, battery operated, s.a.e. details. Ramar Constructor Services, Masons Rd, Stratford on Avon, Warwickshire.

MICROJET WELDER

A TINY FLAME UP TO
5000°F!
WELDS BRASSES
SOLDERS

£22.50

INC. FLAME TIPS

INC. FLAME TIPS
Precision tool using combination of butane and compressed oxygen or micronox. A pencil lead thin flame size. Adjustable to 5,000 F. Cuts metals, welds, brazes and solders gold, silver. Ideal electricians, clockmakers, electronic and computer servicing. Up to 30 minutes use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder. £2.10 extra including post. £22.50 + £1.25 P. & P. Send £23.75.

JOHN DUDLEY & CO. LTD.

Dept. PE16, 301 Cricklewood Lane
Finchley Rd., London, NW2. Tel. 01-458 5917
Callers welcome. Access accepted

PLACE YOUR ORDER BY PHONING
SANDY GATES SERVICES
SHEFFIELD 665950
PRINTED CIRCUIT BOARD CUT TO YOUR REQUIREMENTS


$\frac{1}{16}$ " Thk x 6"-12" wide - single/double side 80p/sq. ft.
 $\frac{1}{16}$ " Thk x 5" max. width - single/double side 55p/sq. ft.
Mixed P.C. Board - 3"-4" wide (Approx 4 sq. ft.) £1.00
Terms - as above + P & P - C.O.D. - Money back undertaking.

TTLs by TEXAS		CMOS I.C.s.	OP. AMPS.	NE531V	MEMORY I.C.s.	LOW PROFILE DIL SOCKETS BY TEXAS		TRANSISTORS		TRIACS		SCR THYRISTORS	
7400	14p	74112	90p	108p	709	8 pin	12p	BDY56	225p	P1A	50p	1A 50V T05	85p
7401	14p	74116	210p	108p	733	14 pin	13p	BF115	24p	TIP31A	70p	1A 400V T05	85p
7402	18p	74118	180p	120p	741	18 pin	14p	BF179	35p	TIP32C	85p	3A 400V STUD	97p
7403	18p	74120	180p	120p	747	18 pin	16p	BF179	35p	TIP33A	97p	12A 400V Plastic	180p
7404	24p	74120	130p	120p	747	18 pin	20p	BF179	35p	TIP33C	120p	16A 600V Plastic	220p
7405	25p	74121	32p	130p	748	18 pin	20p	BF179	35p	TIP34A	124p	16A 600V Plastic	220p
7406	43p	74122	52p	127p	748	18 pin	20p	BF179	35p	TIP34C	160p	BT106 1A 700V STUD	130p
7407	43p	74123	52p	127p	748	18 pin	20p	BF179	35p	TIP34C	160p	MC1901 4A 400V Plastic	61p
7408	22p	74125	70p	100p	850p	18 pin	30p	BF179	35p	TIP35A	160p	2N5459 40p	200p
7409	22p	74126	85p	100p	850p	18 pin	30p	BF179	35p	TIP35C	200p	2N5485 45p	40430
7410	18p	74128	85p	100p	850p	18 pin	30p	BF179	35p	TIP36A	287p	2N6027 70p	40669
7411	20p	74132	81p	100p	850p	18 pin	30p	BF179	35p	TIP36C	360p	2N6247 200p	40p
7412	20p	74136	81p	100p	850p	18 pin	30p	BF179	35p	TIP41A	75p	2N6254 140p	30p
7413	40p	74141	85p	100p	850p	18 pin	30p	BF179	35p	TIP41C	80p	2N6292 75p	30p
7414	85p	74142	30p	100p	850p	18 pin	30p	BF179	35p	TIP42A	78p	3N128	30p
7416	40p	74145	95p	100p	850p	18 pin	30p	BF179	35p	TIP42C	96p	3N140	97p
7417	40p	74148	100p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	3N141	97p
7420	18p	74150	130p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40360	43p
7421	43p	74153	81p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40361 2	43p
7422	20p	74151	81p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40409 10	75p
7423	30p	74154	100p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40411	32p
7425	33p	74155	97p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40454	97p
7426	43p	74156	97p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40459	97p
7427	40p	74157	81p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40463	90p
7428	40p	74159	250p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40473	90p
7430	18p	74160	90p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40481	90p
7432	37p	74161	130p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7433	13p	74162	110p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7437	37p	74163	130p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7438	37p	74164	120p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7440	18p	74165	150p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7441	85p	74167	81p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7442	75p	74167	320p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7443	120p	74170	20p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7444	120p	74172	75p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7445	100p	74173	190p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7446	100p	74174	130p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7447	75p	74175	97p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7448	85p	74176	130p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7450	18p	74177	100p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7451	18p	74180	160p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7453	18p	74181	324p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7454	18p	74182	150p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7460	18p	74184	250p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7470	38p	74185	190p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7472	32p	74186	90p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7473	38p	74190	140p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7474	37p	74191	140p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7475	43p	74192	120p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7476	37p	74193	120p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7480	54p	74194	180p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7481	18p	74195	110p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7482	90p	74196	130p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7483	90p	74197	130p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7484	100p	74198	270p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7485	120p	74199	270p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7486	36p	74201	175p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7489	340p	74251	150p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7490	36p	74265	87p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7491	90p	74278	320p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7492	90p	74279	150p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7493	36p	74283	220p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7494	90p	74284	475p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7495	75p	74285	475p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7496	90p	74290	85p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
7497	200p	74293	180p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
74100	180p	74298	220p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
74104	75p	74365	180p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
74105	75p	74366	180p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
74107	38p	74367	180p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
74109	80p	74390	220p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
74110	80p	74393	215p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p
74111	75p	74390	250p	100p	850p	18 pin	30p	BF179	35p	TIP295	75p	40487	85p

INDEX TO ADVERTISERS

Adam Hall (P.E. Supplies).....	623	Flairline Supplies.....	616	Radio Component Specialists.....	Cover 11
Advanced Electromusic Application.....	600	Fraser-Manning Ltd.....	620	Radio & T.V. Components.....	599
Aitken Bros.....	557	Gemini Electronics.....	616	Ramar Constructor Service.....	623
Alben Engineering.....	612	Government Communications.....		R.S.T. Valve Mail Order.....	618
Amtron.....	548	Headquarters.....	621	Saga.....	613
Astra-Pak.....	600	Greenwell Electronics.....	558, 620	Sandwell Plant.....	622
Aura Sounds.....	612	H.M. Electronics.....	623	Sandygate Supplies.....	623
Automet Acoustics.....	623	Harversons.....	600	Saxon Entertainments.....	556-557
B.B.C. Engineers.....	621	Heathkit Ltd.....	619	Scientific Wire Co.....	623
Baron.....	614	Home Radio.....	599	Sentinel Supply.....	550
Barrie Electronics.....	576	I.C.S. Intertex.....	553, 621	Sinclair.....	560
Bi-Pak.....	554-555	I.L.P. Electronics.....	559, 617	Sintel Limited.....	623
Birkett J.....	549	J.W.B. Radio.....	620	Sowter E.A. Ltd.....	623
Boffin Projects.....	623	Lynx Electronics.....	614	Sparks Developments.....	620
British National Radio & Electronics.....		Maplin Electronic Supplies.....	Cover IV	Special Products.....	549
School.....	557, 611	M.E.C.I. (Moulded Electronic Components Int. Ltd.).....	550	Stirling Sound.....	619
Bull J.....	615	Minikits Electronics.....	623	Sugden A.R.....	546
Cambridge Learning.....	547	Modern Book Co.....	616	Swanley Electronics.....	618
Clef Products.....	600	Orchard Limited.....	614	Tamba Electronics.....	610
Component Centre, The.....	612	Osmabet.....	616	Technomatic Ltd.....	624
Continental Specialities.....	575	P.K.G. Electronics.....	623	Tempus.....	610
Copespeed.....	620	Phonosonics.....	552-553	Tirro Electronics.....	599
Copper Supplies.....	622	Pitman.....	576	T.K. Electronics.....	558
Crescent Radio Ltd.....	548	Precision Petite.....	616	Trampus Electronics.....	610
Crimson Elektrik.....	548	Progressive Radio.....	576	T.U.A.C.....	551
Crofton Electronics.....	623	Proto Design.....	623	Vero Electronics.....	613
C.R. Supply Co.....	620	Radio Component Specialists.....	Cover 11	Watford Electronics.....	Cover II
C.W.A.S. Alarm.....	622	Williams, Michael.....	550	Williams Amplification.....	623
Davian Electronics.....	558	Williamson Amplification.....	623	Wimslow Audio.....	618
Dudley, John Co. Ltd.....	623	Xeroza Radio.....	546		
E.D.A.....	549				
E.M.I. Electronics Ltd.....	622				
Edencombe Ltd.....	620				
Electrovalue Ltd.....	546				

R.C.S. 10 WATT AMPLIFIER KIT

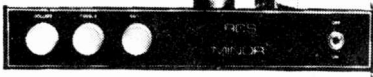

This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec 10W output into 8 ohms, 7W into 15 ohms. Response 20c/s to 30kc/s input 100M V high imp. Size 9 1/2 x 3 x 2 1/2. A.C. mains operated.

Mono kit **£11.25** Stereo kit **£18** post 45p
Easy to build Full instructions supplied

MONO PRE-AMPLIFIER

A mains operated solid state pre-amplifier unit designed to complement amplifiers without low level phono and tape input stages. This free standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Power ON/OFF, PHONO/TAPE switches and pilot lamp are on the front panel; phono socket input and output are rear located. AC mains 240V.



Size 6 x 3 1/2 x 2in.
£4.50 ea. - 2 for £8. Post 50p.

ROBUST BLACK PLASTIC BOX
Size 6 1/2 x 3 1/2 x 2in with brushed aluminium fascia. Ideal for constructional projects. **£1.50** Post 30p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE **£1.45**

Ideal for Mike Tape P.U. Guitar Battery 9 12V or H.T. line 200-300V d.c. operation. Size 1 1/2 x 1 1/2 x 1in. 25 c/s to 25kc/s 26 dB gain. For valve or transistor equipment. Instructions supplied.

ELECTRO MAGNETIC PENDULUM MECHANISM **95p** Post 30p

1.5V d.c. operation over 300 hours continuous on SP2 battery fully adjustable swing and speed. Ideal displays teaching electro magnetism or for metronome strobe etc.

BSR HI-FI AUTOCHANGER
Plays 12in, 10in or 7in records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. a.c. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in. With STEREO/MONO CARTRIDGE. **£12.95** All Post 75p




Single Player version £15.50.
BSR P128 with Magnetic Cartridge **£24.50**
GARRARD MINICHANGER plays all records **£9.95**
BSR P163 BELT DRIVE DECK, less cartridge **£27.50**
GARRARD AP76 **£27.50**

BSR DE LUXE AUTOCHANGER
Features balanced arm. Cueing device, stylus pressure gauge, 3 speed plays all size records. Fitted with stereo ceramic cartridge. Size 13 x 12in. Post £11.
Or with Sonotone V100 magnetic cartridge **£21.50**



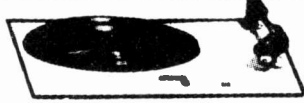R.C.S. DISCO DECK SINGLE RECORD PLAYER
Fitted with auto stop, stereo compatible cartridge. Baseplate Size 11 x 8 1/2in. Turntable Size 7in diameter a.c. mains 220 250V. 3 speeds plays all size records. **£7.95** Post 75p



ELAC 10 inch **£4.50**
Ribbed cone. Large ceramic magnet 50-16,000 c/s. Bass resonance 55 c/s. 10W. 15 ohm impedance.



RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp. per channel, with volume control and P.C. Board. Can be ganged to make multi-way mixers. **£2.95** Post 35p

- MAINS TRANSFORMERS**
- 250-0-250V 70mA, 6.3, 2A **£3.45**
 - 250-0-250 80mA, 6.3V 3 5A 6.3V 1A or 5V 2A **£4.60**
 - 300-0-300 120mA, 2 x 6.3V 2A C.T. 6.3V 2A **£8.50**
 - 220V 45mA, 6.3V 2A **£1.75**
 - HEATER TRANS. 6.3V 3A **£1.45**, 7 amp **£1.00**
 - GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2A 3 4 5 6 8 9 10 12 15 18 24 and 30V **£5.30**
 - 1A, 6.8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£5.30**
 - 2A, 6.8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8.50**
 - 3A, 6.8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11.00**
 - 5A, 6.8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£14.50**
 - 5, 8, 10, 16V 1A **£2.12** 12V 100mA **£1.12** 12V 750mA **£1.30** 24V 2A tapped 10V or 30V **£2.95** 70V 2A **£2.40** 2A **£2.95** 230V 2A **£2.95** 20V 2A **£2.95** 200V 2A **£2.95** 30V 1A **£2.75** 20V 1A **£2.20** 9V 3 amp **£2.75** 60V 40V 20V or 20-0-20V 1A **£3.50**. **£3.00** 30 2A 27.
- AUTO TRANSFORMERS. 115V to 230V or 230V to 115V **150W £5; 250W £6; 400W £7; 500W £8.**
CHARGER TRANSFORMERS Input 200/250V for 6 or 12V 1 1/2A **£2.75; 4A £5.20.**
FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs 1 1/4A 40p; 2A 55p; 4A 95p. HALF WAVE 12V 1 1/2A 25p.

BAKER MAJOR 12 INCH **£15** Post £1 00
30-14,500 c/s 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W.
NOTE 4 or 8 or 16 ohms available.
Module kit 30-17,000 c/s with tweeter, crossover baffle, 19 x 12 1/2in. **£19**
Please state 4 or 8 or 16 ohms. Post £1 60

"BIG SOUND" BAKER SPEAKERS
Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response 30-13,000 c/s. Bass Resonance 55 c/s

- GROUP "25"**
12in 30W 4, 8 or 16 ohms **£12** Post £1
- GROUP "35"**
12in 40W 4, 8 or 16 ohms **£14** Post: £1
- GROUP 50/12in**
12in 60W 4 or 8 or 16 ohms with aluminium presence dome **£21** Post £1 60
- GROUP 50/15in**
15in 75W 8 or 16 ohms **£26** Post £1 60

Disco Group - PA Cabinets in stock. Send for Leaflet, Cabinet Fittings, Handles, Corners, Feet. Covering Material all in stock.



BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER
Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music 4 way mixing. Output 4/8/16 ohm. a.c. Mains 240V. Separate treble and bass controls. **£75** Carr 11 50

NEW "DISCO 100 WATT" **£59** Carr £1
ALL TRANSISTOR AMPLIFIER 2 inputs 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis. Made by Jennings.

R.C.S. SOUND TO LIGHT DISPLAY MK II
Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 20mV signal source. CABINET extra £4. **£17.00** plus £2 50 carr

GOODMANS CONE TWEETER
18,000 c/s 25W 8 ohm **£3.25**
E.M.I. 5in mid range 25W **£4.95**.
E.M.I. 13 x 8in 25W Bass Unit **£10.50**

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS



Professional model. Four inputs Treble, Bass, Master Volume Controls. Ideal disco, P.A. or groups. SAE for details. 5 speaker outputs 3 or 8 or 15 ohm 100V line to order. Suitable carrying case **£16.50** Post £2 50 carr

LOW VOLTAGE ELECTROLYTICS
1 2 4 5 8 16 25 30 50 100 200mF 15V 10p. 500mF 12V 15p; 25V 20p; 50V 30p; 100mF 12V 17p; 25V 35p; 50V 47p; 100V 70p; 200mF 6V 25p; 25V 42p; 2500mF 50V 62p; 3000mF 25V 47p; 50V 85p; 3000mF 100V £1.60; 4700mF 53V £1.20; 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 5600mF 76V £1.60; 1200V 76V 80p.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS
All parts and instructions with Zener diode printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2in. Please state voltage required. **£2.95** Post 45p

GOODMAN'S COMPACT 12in BASS WOOMER
Standard 12in diameter fixing with cut sides 10in square 14,000 gauss magnet. 30 watt 4 ohm impedance. Bass resonance 30 cps. Frequency response 30-8,000 cps. **£10.95** each. Post £1.00 20 Watt model **£9.95**.



10 WATT PER CHANNEL STEREO AMPLIFIER
In chassis form. A.C. mains operated. Volume, balance, treble and bass slider controls. Pick up and tape inputs. Recording output. Front panel size: 16 1/2 x 1 1/2in. **£18.50** Post 50p

HEATING ELEMENTS WAFER THIN
Size 10 1/2 x 8 1/2 x 1 1/2in Operating voltage 200 250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters etc. Must be clamped between two sheets of metal or asbestos. **ONLY 40p EACH (FOUR FOR £1.50)**
ALL POST PAID—Discounts for quantity

E.M.I. 13 1/2 x 8in SPEAKER SALE!
With tweeter. And crossover. State 4 or 8 ohm

- 10W Model **£7.95** Post 45p
- 15W Model **£10.50** Post 65p
- 20W Model **£11.50** Post 75p



TEAK VENEER HI-FI SPEAKER CABINETS
MODEL "A" 20 x 13 x 12in. For 12in. dia. or 10in. speaker. Illustrated **£14.50** Post £1.60
MODEL "B" BOOKSHELF
For 13 x 8in. EMI Loudspeakers. **£8.50** Post £1
R.C.S. BOOKSHELF complete with speakers. Size 14 x 9.6in. approx. Response 50 to 14,000 cps. 6 watt rms 8 ohms **£16 pair** Post £1.30
ACOUSTIC WADDING 18in. wide, 20p ft.


HEAVY METAL PLINTHS
With P.V.C. Cover. Cut out for most BSR or Garrard decks. Silver grey finish. Model A Size 12 1/2 x 14 1/2 x 7 1/2in. **£6.50** Post £1 30
Model B Size 16 x 13 1/2 x 7in **£7.50**
Extra Large Plinth and Cover. For transcription decks. Size 20 x 17 1/2 x 9in. uncut board. Callers only **£18 50**

TINTED PLASTIC COVERS ONLY
Sizes: 14 1/2 x 12 1/2 x 4 1/2in, £3. 14 x 12 1/2 x 2 1/2in, £3.50. 16 1/2 x 14 1/2 x 3in, £3.75. 16 1/2 x 14 x 4in, £4. 19 x 14 1/2 x 4 1/2in, £4. 15 x 13 1/2 x 3in, £3.50. 17 1/2 x 9 1/2 x 3 1/2in, £3. 14 1/2 x 14 1/2 x 2 1/2in, £4. Ideal for record decks, tape decks, etc. Post 75p.

BAKER HI-FI SPEAKERS
HIGH QUALITY—BRITISH MADE

SUPERB 12in 25 watt **£22** Post £1 60

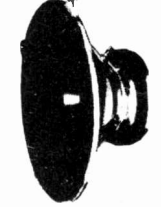Quality loudspeaker: low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register.
Bass Resonance 25 c/s
Flux Density 16 500 gauss
Useful response 20 17 000 c/s
8 or 16 ohms models



AUDITORIUM 12in 35 watt **£21** Post £1 60

A full range reproducer for high power Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.
Bass Resonance 35 c/s
Flux Density 15 000 gauss
Useful response 25 16 000 c/s
8 or 16 ohms models



AUDITORIUM 15in 45 watt **£26** Post £1 60

BLANK ALUMINIUM CHASSIS, 18 s.w.g 2 1/2in sides, 6 x 4in 95p; 8 x 6in £1.40; 10 x 7in £1.55; 14 x 8in £1.90; 16 x 6in £1.85; 12 x 3in £1.20; 16 x 10in £2.20; 12 x 8in £1.70.
ALUMINIUM PANELS, 18 s.w.g 6 x 4in 20p; 8 x 6in 40p; 10 x 7in 50p; 12 x 5in 50p; 12 x 8in 50p; 16 x 6in 75p; 14 x 9in 80p; 12 x 10in 80p; 16 x 10in 95p.

ALUMINIUM ANGLE BRACKET, 6 x 1/2 x 1in 15p
ALUMINIUM BOXES, MANY SIZES IN STOCK
4 x 2 x 2in, 55p; 3 x 2 x 1in, 55p; 6 x 4 x 2in, 65p; 8 x 6 x 3in, £1; 9 x 4 x 4in, £1.20; 12 x 4 x 4in, £1.50

THE "INSTANT" BULK TAPE ERASER & HEADS DEMAGNETISER.
Suitable for cassette and all sizes of tape reels. a.c. mains 200 240V. Leaflet S A E **£4.95** Post 50p



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K. Tel. 01-684 1665

Minimum post 30p. Access/Eurocard and Barclaycard/Visa. Same day despatch. Radio Books and Components Lists 20p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)

Published approximately on the 15th of each month by IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel Hill Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (Asia) Ltd., South Africa—Central News Agency Ltd. Subscriptions INLAND and OVERSEAS £10.60 payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

MAPLIN

everything for the modern D.I.Y. electronics enthusiast and more.




100W RMS STEREO DISCO

A genuine 100W RMS per channel (both channels driven) stereo disco with auto fade on microphone, VU meters, full monitoring and cueing facilities and a very high quality light show. Complete construction booklet MES41, price 25p. Cabinet comes complete with lid and carrying handles.




VERY LOW-DISTORTION AUDIO OSCILLATOR

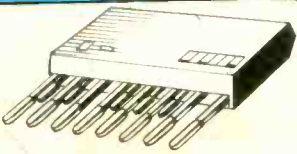The very low distortion sine wave (<0.01% output is suitable for testing very high quality hi-fi audio equipment. Also includes square wave output. Range 20Hz to 26kHz. Output 0V to 1V in three continuously variable steps. Total cost around £21. Full construction details in our catalogue. Send the coupon below, now! (All prices include V.A.T. and p & p)




PEDAL UNIT

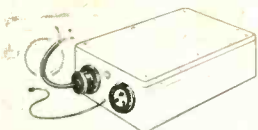A completely self-contained pedal unit. 13-note, 2-Octave range. 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue - post the coupon below, now!



ELECTRONIC IGNITION SYSTEM

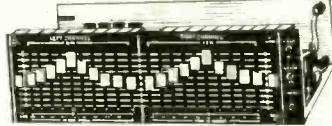A high performance electronic ignition system that saves fuel, cuts points wear, gives strong spark and easy start even with very low battery, improves engine power at high revs. Change back to conventional system in seconds. Total cost around £14. Full construction details in our catalogue. Send the coupon below, now! (All prices include V.A.T. and p & p)




10 CHANNEL STEREO GRAPHIC EQUALISER

A new design with no difficult coils to wind, but a specification that puts it in the top-flight hi-fi class. All this for around £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 25p. (All prices include V.A.T. and p & p)




INTEGRATED CIRCUITS

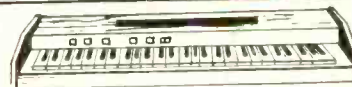Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applications circuits and projects to build. Post the coupon now!




TOUCH-SENSITIVE PIANO

The revolutionary new IC AY-1-1320 first seen on 'Tomorrow's World' is now available. Complete kit of IC's to build a 60-note piano (18 x IC's) order as HQ53H price £36.86. Preliminary circuit details in our October newsletter. Complete design, pcb's attractive veneered wooden cabinet available soon. It's the most realistic-sounding electronic piano we've ever heard and includes simulated damping, loud and soft pedals. Full details in our newsletters. (All prices include V.A.T. and p & p)

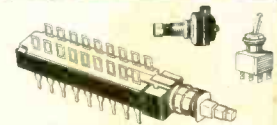

SWITCHES

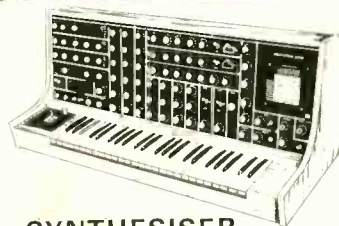We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches - there are dozens to choose from, but it's only a tiny part of our fantastic range.



SYNTHESISER

The International 4600 Synthesiser. A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart teak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request. Full construction details in our construction book £1.50. (All prices include V.A.T. and p & p)



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated!

No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR
Telephone: Southend (0702) 715155
Shop: 284, London Road, Westcliff-on-Sea, Essex
(Closed on Monday) Telephone: Southend (0702) 715155



POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME _____

ADDRESS _____