

Whitney

THE MILLER TIMEBASE

PRACTICAL TELEVISION

AND TELEVISION TIMES

1/6

**EDITOR
F. J. GAMM**

A NEWNES PUBLICATION

Vol. 5 No. 60

MAY, 1955



A useful
TEST UNIT

FEATURED IN THIS ISSUE

Radio Component Manufacturers
Exhibition Reviewed
Corona Discharge
Flyback Suppression

The RF 24 & 26 Units
Servicing The Ekco EK
Your Problems Solved
A TV Engineer

PREMIER RADIO COMPANY


(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone :
AMBASSADOR 4033
FADDINGTON 3271

OPEN TILL
 6 P.M. SATURDAYS

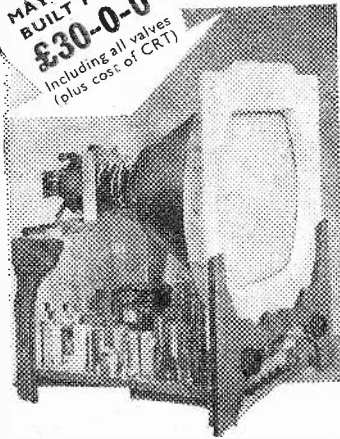MAY BE
 BUILT FOR
£30-0-0
 Including all valves
 (plus cost of CRT)



**MULTI-CHANNEL TUNER
 AVAILABLE SHORTLY**
 WATCH FOR ANNOUNCEMENT

The NEW PREMIER TELEVISOR

SUITABLE FOR USE WITH THE ENGLISH ELECTRIC CATHODE RAY TUBE T901 OR ANY POPULAR WIDE ANGLE TUBE

20 valves (plus tube) Superhet Receiver, tunable from 40-68 Mc/s without coil or core changing. Wide angle scanning Flyback EHT giving 14 kV. Duomag Focalsiser, permanent magnet focussing with simple picture centring adjustments, suitable for any wide angle Tube, may also be used with a 12 in. Tube with very minor modifications.

VISION CIRCUIT. Common RF Amplifier, single valve frequency changer, two IF stages, Video Detector and Noise Limiter followed by special type of Video Output Valve. ALL COILS PRE-TUNED ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.

SOUND CIRCUIT. Coupling from anode of frequency changer, two IF stages, Double Diode Triode detector and first LF Amplifier, Diode Noise Limiter and Beam type Output Valve, feeding a 10in. Speaker. ALL COILS PRE-TUNED.

TIME BASES. 2 valve sync. Separator, giving very firm lock and excellent interlace.

LINE TIME BASE. Blocking Oscillator using a pentode driving a high efficiency output stage comprising Ferroxcube Cored Output Transformer with Booster Diode.

FRAME TIME BASE. Blocking Oscillator driving a Beam Output Valve coupled through a Transformer to the high efficiency FERROXCUBE Cored Scanning Coils.

POWER PACK. Double wound Mains Transformer supplying all L.T. and H.T. using two full-wave Rectifiers.

The Televisor may be constructed in 5 easy stages: (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced. All preset controls can be adjusted from the front, making setting up very simple.

Instruction book 3/6, Post Free. *Send Stamp For Latest Catalogue*
 Console Cabinets in figured walnut can be supplied for the above receiver at a cost of £13/10/-, plus 21/- pkg. & carr. H.P. Terms for cabinet on request.

BUILDING THE "SIMPLEX"?

Thousands of enthusiasts are building the "Simplex" Television, now being featured in "Practical Television". WHY NOT YOU? CONSTRUCTOR'S ENVELOPE containing full constructional details and Blue Print, additional notes and suggestions, and Query Service form, sent for ONLY 5/-. All components available ex stock as follows:

ALUMINIUM CHASSIS. — 18 s.w.g. DRILLED, for VCR97 version with screens and tube holder bracket. 22/6.

TRANSFORMER. — 350-0-350 v. 150 ma. 6.3 v. 5 a., 5 v. 3 a., tapped at 4 v., ONLY 37/6. (Postage 2/-).

CHOKE. — 10 h. 120 ma., 10/8. (Post 1/-).

RECTIFIERS. — RM3 5/- ea., K340 6/- ea. VALVES. — EP50 6/8, SP61 4/-, 6SN7 9/-, 6A5 5/6, EB34 3/6, EA50 3/6.

VALVE HOLDERS. — B9C/(EP50) 10d., I.O. and M.O. 6d., Diode (EA50) 6d., VCR97 2/6.

VCR97 TUBE. — Tested full screen. 42/8.

CONDENSERS. — Electrolytics 25 mfd. 25 v. 1/10, 16 x 8 mfd. 450 v. 5/6, 32 x 32 mfd. 450 v. 6/-, Mica, silver mica, and tubulars, 350 v. 6d. each.

POTENTIOMETERS. — All values, pre-set 1/9 each, long spindle 3/-, with switch, 4/6.

RESISTORS. — 1 watt 4d., 1/2 watt 5d., 1 watt 6d., 1.5 k. 5 watt 1/6.

COIL FORMERS. — 1in. 8d., tin. 10d.

SPEAKER. — 8 in. P.M. less trans. 16/6 (postage 2/-).

O.P. TRANSFORMER. 5/-.

All Components Brand New and Unused. Full Price List available on request.

VALVES

1G6	6/6	7A7	8/6	5Z4	10/-
1E7	6/6	7C5	8/6	5U4	10/-
1LH4	8/-	7F7	8/6	6AC7	6/6
1LN5	8/-	7W7	8/6	6K7GT	5/6
1L4	7/6	12H6	8/6	807	7/6
2B7	8/6	12J5	6/-	ECH35	12/6
3A4	9/-	12A7	12/6	EA50	3/6
3B7	8/6	12SG7	7/6	EBC33	8/6
6AG5	7/6	12SK7	8/6	EB34	3/6
6AK7	9/6	12SR7	7/6	EF33	6/6
6B4	7/6	28D7	7/6	EF39	6/6
6B8	7/6	32	7/6	EF50	6/6
6C9	8/-	5Y6	8/6	Red	
6G6	6/6	50Y6	8/6	Sylvania	8/6
6H6	5/-	58	5/6	EP91	12/6
6K6	9/-	1622	11/-	EY51	15/-
6L7	7/6	1626	4/-	EK32	6/6
6N7	7/6	129A	7/6	EL32	7/6
6R6	8/6	VR150/30	8/6	SP61	4/-
6U5	8/6	VR137	5/9	SP61	7/6
6V6	8/6	KT44	8/6	MU14	10/6
6V6GT	7/6	KT52	5/-	RL37	6/6
6SA7	8/6	VP23	6/6	VS70	7/6
6SG7	7/6	HL23DD	6/6	934	6/6
6SH7	7/6	TP25	8/-	953	6/6
6SJ7	8/6	1S5	8/-	9031	6/-
6SK7	7/6	1L74	8/-	9031	6/-
6SL7	9/-	1R5	8/-	931A	50/-
6SS7	7/6				

R.F. UNITS TYPE 26 and 27. For use with the R.1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves EF54 and 1 of EC52. Type 26 covers 65-50 Mc/s (5-6 metres) and Type 27 covers 65-85 Mc/s (3.5-5.0 metres). Complete with valves, and BRAND NEW IN MAKER'S CARTONS. ONLY 29/6 each.

GLASS OF INDICATOR 233. — Contains VCR97 C.R.T. holder, 11 valve holders, resistors, condensers, etc. etc. BRAND NEW. ONLY 10/- (carr. etc., 5/-).

E.H.T. TRANSFORMER. — Normal 230 v. Primary, with Secondary of 2,000 v. r.m.s. (approx. 2,800 v. D.C.). A special offer of interest to all using the VCR97 or similar tube. Size 2 1/2in. W. x 2 1/2in. D. x 3 1/2in. H. + 3in. for tag panel. AN UNREPEATABLE SNIP, and well worth buying as an insurance against failure of existing E.H.T. supplies. ONLY 15/- (postage, etc., 2/-).

TRANSFORMERS. — Manufactured to our specifications and fully guaranteed. Normal Primaries. 425-0-425 v. 200 ma. 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., ONLY 65/-; 350 v. 0-350 v. 160 ma., 6.3 v. 5 a., 6.3 v. 3 a., 5 v. 3 a., ONLY 47/6; 250 v. 0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., ONLY 37/6; 350 v. 0-350 v. 150 ma., 6.3 v. 5 a., 5 v. 3 a., ONLY 37/6; 250-0-250 v. 60 ma., 6.3 v. 3 a., 5 v. 2 a., ONLY 21/-. The above are fully shrouded, upright mounting, 5.5 kV. E.H.T. with 2 windings of 2 v. 1 a., ONLY 79/6; 7 kV. E.H.T. with 4 v. 1 a., ONLY 89/6. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

PYE 45 mcs. I.F. STRIPS. — The strip that is ready made for the London Vision Channel. Complete with 6 valves EP50 and 1 of EA50. BRAND NEW. ONLY 59/6.

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station), 5 mins. by bus from King's Cross. Cash with order, please, and print names and address clearly, include postage as specified and on Component Orders under £2.

THE RADIO CORNER, 133, GRAY'S INN ROAD, LONDON, W.C.1. (Phone TERMINUS 7937.)

U.E.I. CORPN.

HENRY'S

(RADIO LTD.)

SPECIAL OFFER '38' WALKIE TALKIE SETS

We have purchased large quantity of the above '38' Sets, and can now offer same complete with 5 valves: 4-VP23 and ATP4. Throat microphone, headphones, junction

box and collapsible aerial. Freq. range 74 to 9 mc/s. Range approx. 5 miles. In absolutely new condition and Guaranteed Air Tested at 59/6 carriage 5/-.

"R.F. 26" F.M. CONVERTER UNIT 88/100 Mc/s

We can now offer this self-contained unit comprising 6 valves: 2-6BA6, EB91, VR137, EF54, EF54. Two I.F. stages and separate local oscillator, also Muirhead Graduated Vernier Drive ensuring easy tuning.

Components Offered to Complete F.M. Unit

New RF "26" Unit with 3 valves, VR137, EF54, EF54. Chassis stamped out for easy conversion £1.15.0

Complete set of all components for conversion including 2-6BA6 and EB91, tuning condenser, I.F.T.'s and Osc. coils, resistors and fixed condensers, plugs, wire and tag strips£4.12.6

Instruction Book with technical circuit and complete lay-out diagrams 2.0

Special offer of all above items and RF26, including circuit, postage 3/-£6. 5.0

Charge for alignment when completed 7.6

Assembled, aligned and ready for use £8.10.0
All items sold separately.

We have over 20,000 American and B.V.A. valves in stock.

ALL VALVES NEW AND GUARANTEED.

1D8GT	10/-	6AM6	9/-	12SA7GT	8/6	EF36	6/6	SP41	4/-
1A7GT	12/6	42	8/6	12SQ7GT	8/6	EF39	6/6	D41	5/-
1H5GT	10/-	43	8/6	12SJ7GT	8/6	EK32	6/6	VP23	8/6
1N5GT	10/-	75	8/6	12SK7GT	8/6	EL32	7/6	HL23DD	
1L4	7/6	30	8/6	12SR7	7/6	EF50 (Red)	6/6		
1Q5GT	10/-	8L8G	10/-	6D9	6/6	Syl.)	10/-	TP25	8/-
13GT	10/-	6Q7GT	8/6	6C6	6/6	HL2	3/6	PEN25	6/6
185	7/6	6SQTGT	8/6	6A7G	8/6	LP2	4/-	QP25	6/6
1S4	7/6	6SG7GT	6/6	6A8G	8/6	KT2	5/-	QP21	8/-
1T4	7/6	6SJ7GT	8/6	1T40	35/-	VP2	8/6	TP22	8/6
1R5	7/6	6SK7GT	8/6	0Z4	7/-	SP2	8/6	ATP4	4/-
3S1	7/6	6SN7GT	9/-	25Z5G	8/6	TDD2A	8/6	MS/PENB	7/6
3V4	7/6	6SL7GT	9/-	25Z5G	8/6	VP2B	8/6	MS/PEN	7/6
1LN5	8/-	6SC7	10/-	35Z4GT	8/6	215SG	4/-	PS/PEN	7/6
1LD5	8/-	6V8G	7/6	35Z5GT	8/6	866A	15/-	PX25	12/6
5U4G	8/6	6V8GT	7/6	35L6GT	8/6	354V	5/-	6A3	10/-
5Z4G	8/6	6F8G	7/6	50L6GT	8/6	4D1	4/-	46	10/-
526G	8/6	6AC7	6/6	25A6G	8/6	8D2	4/-	AC/PEN	10/-
MU11	8/6	6AG7	12/6	KT39C	10/-	8D2	4/-	FC13C	10/-
6B8	7/6	6CSGT	5/-	KT66	12/6	PEN46	7/6	FC13s/c	10/-
6K8G	9/-	6J5GT	5/-	EBC33	8/6	AC6PEN	6/6	42SP2	6/-
6K7G	6/6	12A6	7/6	EF54	6/-	VP41	7/6	PENDD	40.00
6T7G	6/6	12K7GT	8/6	EB34	3/6	TR23	10/-		12/6
8N7GT	7/6	12K9GT	8/6	EA50	2/-	41MP	7/6	VT501	7/6
6L7	7/6	12Q7GT	8/6	DL	2/-	SP61	4/-	U19	10/-

EY51	12/-	UL41	11/-	EF80	10/6	PL81	12/6	12AT6	8/-
EP41	11/-	UY41	11/-	EABCO10	10/-	PL82	10/-	12AT7	9/-
EL41	11/-	UF41	11/-	ECC85	10/-	PY81	10/-	12AU6	9/-
EP40	10/-	DK40	10/-	EZ80	9/-	PY82	10/-	12BA6	9/-
EM34	10/-	50B5	10/-	EN80	10/-	PCQ94	12/6	12B8G	10/-
55W4	8/-	150C5	10/-	ECL80	12/6	PCF82	12/6	6X4	8/6

22-page Catalogue, 3d. Open Mon-Sat. 9-6. Thurs. 1 p.m.

HARROW ROAD, PADDINGTON, LONDON, W.2

TEL.: PADDINGTON 1008/9, 6401.

CRYSTAL MICROPHONE INSERTS



Ideal for tape recording and amplifiers. No matching transformer required.

SPECIAL REDUCTION

1A7GT, 1N6GT	
1H5GT, 1A5GT	
10 EF50 (Ex-Brand New Units) 5/-	
6A8G, 6K7G, 6Q7G, 5Z4G, 6V6G	...45/-
1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4)	...27/3
TP25, HL23/DD, VP23, PEN25 (or QP25)	...25/-
6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 (or 25Z6G)	...37/6
12K6GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50L6GT)	...37/6
12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 55L6GT (or 50L6GT)	...37/6

PACKARD BELL AMPLIFIER

Brand new complete with 2BD7 and 6SL7GT and instruction book 12/6. P. & P. 2/-.

Specially useful for Television Work ...

The AVO WIDE-RANGE SIGNAL GENERATOR

A Signal Generator of wide range and accuracy of performance, designed to cope with modern radio and television work. Turret coil switching provides six frequency ranges covering 50 Kc/s—80 Mc/s.

- 50 Kc/s—150 Kc/s
- 150 Kc/s—500 Kc/s
- 500 Kc/s—1.5 Mc/s
- 1.5 Mc/s—5.5 Mc/s
- 5.5 Mc/s—20 Mc/s
- 20 Mc/s—80 Mc/s

Stray field less than 1μV per metre at a distance of 1 metre from instrument. General level of R.F. harmonic content of order of 1%.

Direct calibration upon fundamental frequencies throughout range, accuracy being better than 1% of scale reading. 45 inches of directly calibrated frequency scales with unique illuminated band selection, giving particularly good discrimination when tuning television "staggered" circuits.

Of pleasing external appearance with robust internal mechanical construction

using cast aluminium screening, careful attention having been devoted to layout of components with subsidiary screening to reduce the minimum signal to negligible level even at 80 Mc/s.

Four continuously attenuated ranges using well-designed double attenuator system.

Force output 0.5 volts.

Internal modulation at 400 c/s, modulation depth 30% with variable L.F. signal available for external use.

Mains input, 100-130 V. and 200-260 V. 50-60 c/s. A.C.





MAINS MODEL, as specified, or BATTERY MODEL, covering 50 Kc/s to 70 Mc/s, powered by easily obtainable batteries £30

Fully descriptive Pamphlet available on application to the Sole Proprietors and Manufacturers

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD
WINDER HOUSE · DOUGLAS STREET · LONDON · S.W.1 Telephone: VICTORIA 34

SPEED UP your SOLDERING

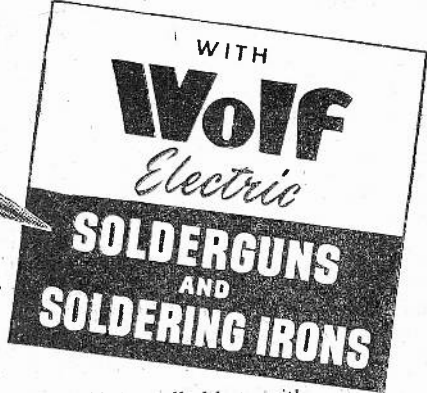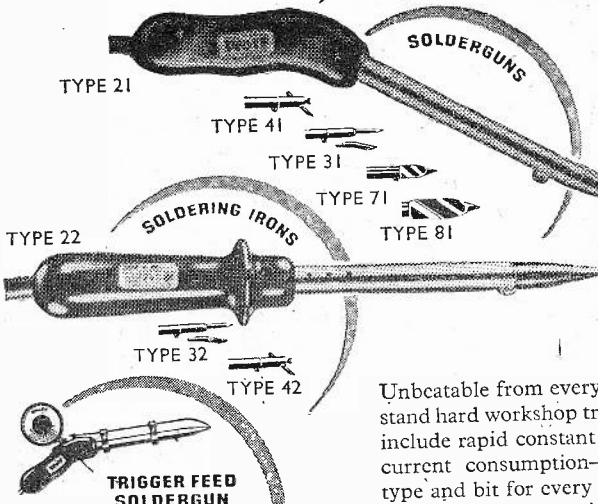

Unbeatable from every point of view, well able to withstand hard workshop treatment and ideal for continuous use. Features include rapid constant localised heat—solid sturdy construction—low current consumption—perfect balance—absolute dependability. A type and bit for every purpose from fine instrument to heavy industrial work. Each tool includes 5 feet tough rubber 3-core cable.

Obtainable from all leading tool merchants and factors. Fully descriptive Brochure on request

WOLF ELECTRIC TOOLS LTD · PIONEER WORKS · HANGER LANE · LONDON · W.5
 Tel: PERIVALE 5631-4 Branches: BIRMINGHAM · MANCHESTER · LEEDS · BRISTOL · NEWCASTLE · GLASGOW

TRIGGER FEED SOLDERGUN
 Type No. 51 is designed specially for all assembly operations. Solder is fed automatically with trigger-action and two reels are supplied—one 15 ft. acid-cored and one 15 ft. resin-cored.

Space-saving suggestion

CHASSIS MOUNTING DRY ELECTROLYTIC CONDENSERS


The saving of space resulting from the use of these condensers is one of the chief reasons for their popularity. Type 928 is of particular interest to designers of rectifier units as a small and efficient substitute for a large 800 v. paper condenser.

Except where indicated, these condensers use plain foil electrodes. The can is negative, but when this connection is not required via the chassis, insulating washers and terminal tags are available upon request.


Capacity tolerance; -20% to +50%. Voltage range; 250 v. to 800 v. Peak Working.

Capacity in μ F.	Peak Work'g Volts	Surge Volts	Dimensions in Inches			T.C.C. Type No.	List Price Each
			H.	D.	Screwed Boss		
*32	350	400	2½	1	½	312	9/-
4	500	600	2½	1	½	512	7/-
8	500	600	4½	1	½	512	8/-
16	500	600	4½	1½	½	512	11/6
32	500	600	4½	1½	½	512	17/6
*8	800	900	4½	1½	½	928	18/-


*Etched Foil.

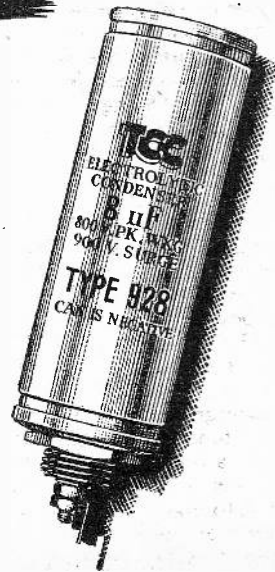

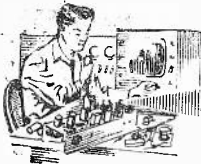THE TELEGRAPH CONDENSER CO. LTD
 RADIO DIVISION: NORTH ACTON · LONDON · W.3 Telephone: ACOrn 0061



Practical Television

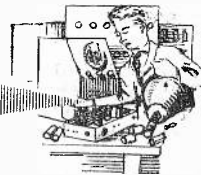

& TELEVISION TIMES

Editor : F. J. CANN

Editorial and Advertisement Offices : "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone : Temple Bar 4383. Telegrams : Newnes, Rand, London. Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 5 No. 60

EVERY MONTH

MAY, 1955

Televiews

INTERFERENCE STATISTICS

THE Post Office Engineering Department has recently published an interesting analysis of interference complaints which it has received and investigated. These figures may not, however, show the magnitude of the interference problem, because the number of viewers or listeners whose reception is affected by interference is usually much greater than the number of complaints received, and also more than one source of a given kind may be concerned in some complaints, and more than one complaint may be made about a common source. The statistics are presented in the form of two tables, the first dealing with the number of complaints attributed to specific sources, and the second with the number arising from defective receiving conditions.

Thus, in the first table there were 578 complaints about bedwarmers interfering with sound broadcasting, and 1,183 with television; 342 complaints concerning calculating machines with sound broadcasting and 818 with television. Comparable figures for other sources of interference are: drills, 1,177, 2,792; external cross-modulation, 1,177, 2,492; faulty electrical wiring of premises, 2,194, 494; hairdriers, 598, 6,954; ignition systems of petrol engines, 49, 1,313; industrial and medical R.F. equipment (valve), 91, 736; industrial and medical R.F. equipment (spark), 105, 151; lighting, filament type lamps, 66, 2,569; lighting, fluorescent tubes, 1,676, 233; street lighting, all types, 712, 113; neon signs, 416, 1,444; power lines, overhead, less than 650 volts, 260, 230; 650 volts to 11 kV, 200, 2,052; more than 11 kV., 222, 1,447; underground, faulty, 132, 60; radiation from TV timebase circuits, 6,805, 3; superhet, local oscillators, 62, 1,604; radio transmitters, amateurs, 125, 303; others sited in U.K., 142, 476, foreign, 533, 146; refrigerators (compressor, fan, or thermostat), 1,228, 1,587; sewing machines, 1,577, 8,956; smoothing irons, 399, 198; vacuum-cleaners, 1,043, 3,269; unknown, 12,206, 21,877. All other identified sources amount to 6,376, 12,404 respectively.

These figures are illuminating. They show that

with the exception of external cross-modulation, faulty electrical wiring, fluorescent tubes, street-lighting, and power lines, radiation from timebase circuits, smoothing irons, the majority of interference relates to television.


The number of complaints arising from defective conditions at the receiving site amounted to 10,335 (sound) and 2,456 (television) respectively under the heading of inefficient aerial or earth installations: 5,290 (sound) and 5,375 (television) due to faulty receivers, 227 (sound) and 666 (television) due to maladjustment of receivers, and 3,168 (sound) and 2,998 (television) due to other conditions.

These figures show the enormity and the complexity of the interference problem, which was recently discussed in Parliament, when the Assistant Postmaster-General was asked what steps he is taking to ensure that television sets are adequately suppressed or screened to prevent their causing interference with sound radio reception.

The reply was that where a television set causes interference with sound receivers, which are themselves in proper order and condition, the owner of the television set is liable to have his licence withdrawn.

TV AND EDUCATION

MORE than 30 educational television stations with a covering of 40 million Americans will be operating this year in the United States of America. Commercial stations are co-operating with local schools, and indeed at present 800 Philadelphia schools receive TV instruction from three commercial stations. In New York crippled children are able to complete their high-school education by TV, and results of TV education are promising. One university reported a 30 per cent. higher performance by students taught by TV than by those who received standard class-room instruction. Educational television in the U.S.A. is about to expand considerably, and is far ahead of any similar effort in this country.—F. J. C.

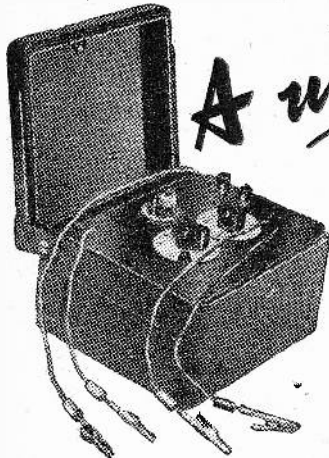

A useful TEST UNIT

A SIMPLE INSTRUMENT FOR TESTING CONDENSERS,
INCLUDING ELECTROLYTICS, MEASURING E.H.T. AND
SUPPLYING AN AUDIO OUTPUT

By F. W. Austin

the 1 megohm potentiometer. This limits the current at 16 kV. to 500 microamps., and gives 500 volts across the potentiometer at that reading.

Calibration

As few readers are likely to have a 500 volts D.C. supply readily available other means must be found for marking the scale. We can, therefore, connect the top end of potentiometer to a 250 volts source and mark the position at which the neon "strikes." This will then be the position for 8 kV. reading.

The resistance of the potentiometer arm across the neon should then be measured. Assuming it is 500 k Ω a mark can then be made against 250 k Ω on the scale. This becomes the 16 kV. reading. All other scale markings can be made by multiplication or division, thus:

16 kV. \times 250 k Ω = 4,000, also 8 kV. \times 500 k Ω = 4,000
 \therefore 10 kV. = 4,000 \div 10 = 400 k Ω , also 6 kV. = 4,000 \div 6 = 666 k Ω , etc.

These figures are arbitrary, depending on the

THIS simple piece of test gear was designed to make as much use as possible of a small neon tube having a minimum of switching arrangements. The results have been, for the small outlay involved, pleasing enough to merit further investigation.

Functions

The apparatus will measure E.H.T. voltage, give a reasonable indication of leakage in paper condensers, give indication of capacity of electrolytic smoothing condensers and supply a signal for injection into both the audio and video detector stages.

Power Requirements

The only power required is obtained by making use of the high tension supply of the receiver under test. When measuring E.H.T. a switched potentiometer isolates the normal H.T. lead and prevents shock to the user from this source, as can be seen from the circuit diagram.

Basic Unit

The basic unit consists of a 1 megohm potentiometer having a 150-volt neon (surplus CV71) shunted between the slider and "earthy" end. This is shown in the circuit as a chassis connection.

E.H.T. Voltage

This is developed across a chain of 32 megohms consisting of 14 resistors (2.2 M Ω -1 watt each) and 1 resistor (200 k-1 watt) with the remainder across


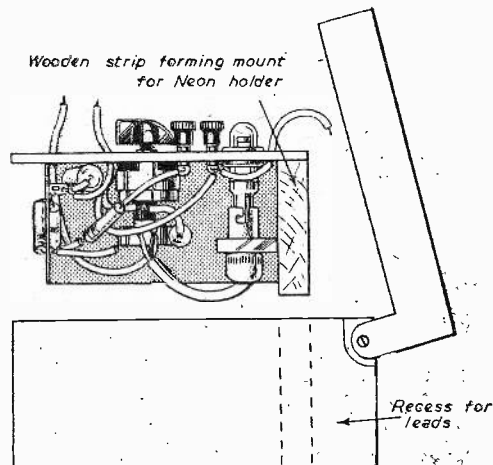


Fig. 1.—Details of case, method of assembly and part of the E.H.T. bleeder panel.

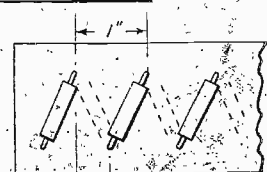

Resistor chain arrangement

PARTS LIST

RESISTORS	CONDENSERS	SUNDRIES
14 \times 2.2 M Ω (1 watt)	1 \times .05 μ F paper (350 v.v.)	1 neon (surplus CV71)
1 \times 200 k Ω (1 watt)	1 \times .02 μ F paper (350 v.v.)	2 Insulated terminals
1 \times 47 k Ω (1 watt)		1 neon holder
1 \times 1 M Ω potentiometer (less switch).		4 wander plugs
1 \times 1/2 M Ω potentiometer (s/p. switch)		4 crocodile clips
		Box, panels, etc.

neon. In my own case the neon struck at 150 volts and the following resistances applied for the various settings:

- 5 kV. = 960 k Ω
- 6 kV. = 800 k Ω
- 7 kV. = 686 k Ω
- 8 kV. = 600 k Ω
- 9 kV. = 533 k Ω
- 10 kV. = 480 k Ω
- 12 kV. = 400 k Ω
- 14 kV. = 343 k Ω
- 16 kV. = 300 k Ω


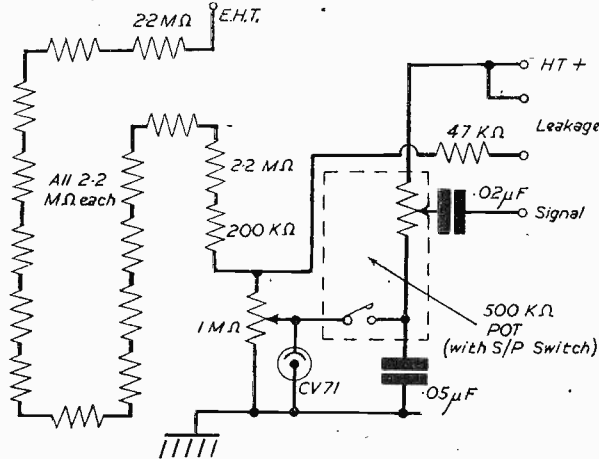


Fig. 2.—Theoretical circuit of the unit.

Construction

A study of the circuit diagram and layout of components should give a good idea of the methods to adopt. The only critical arrangement is the setting out of the resistor chain, which was made up on two thin paxolin panels and mounted on the left-hand side and along the bottom of the layout diagram. All other components should be kept well clear. These resistors were of the type having wires coming directly out of the body and their use is strongly advised. My own unit, as may be seen from the illustration, was enclosed in a plastic box complete with lid, bought cheaply as surplus, but as they are not generally available a wooden box will suffice. The panel holding the controls should be rather shorter than the box to give space at the back for packing away reads when not in use. A strip of wood is fixed at right-angles at the rear of the panel, and besides forming the recess for leads it also

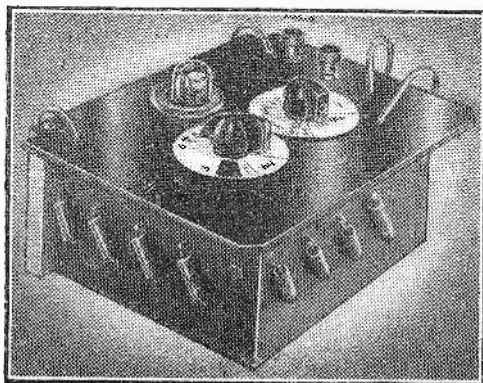

Another view of the finished instrument.

supports a bracket on which the neon holder is mounted. See Fig. 1.

E.H.T. Operation

When measuring E.H.T., the signal control should be turned off (switched off). With the negative lead connected to the chassis the striking point of the neon then indicates potential.

Signal Operation

With H.T. leads connected between H.T.+ and chassis the signal amplitude control is turned to maximum, and the kV pointer reduced slowly from maximum kV setting towards minimum (it will be noted that this control is connected in "reverse sense" to give maximum kV reading in a clockwise direction). The signal will not be variable and can be set as desired.

Paper Condensers

These are tested by having the kV control set to CAP and the signal control switched off. The capacitor is then applied to leakage terminals and quickly reversed. A short, sharp flash should be the reward. A constant glow shows either bad insulation or a short-circuit.

Testing Electrolytics

For fairly full information about these a potential of 250 volts is desirable, although similar results are obtainable at 230 volts. This is, of course, limited by

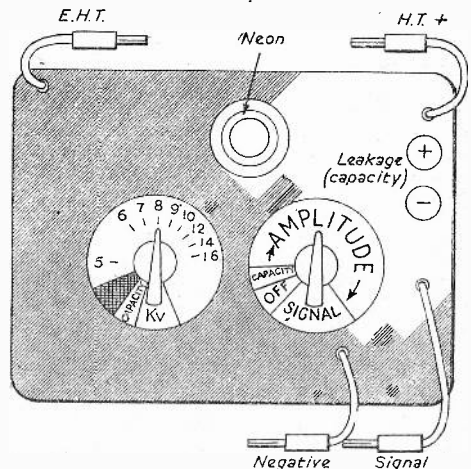


Fig. 3.—Details of panel, controls and connections.

the striking voltage of the neon and the various high resistances in the circuit. The kV control should be set to CAP and the signal amp. control switched off. The condenser is connected to plus and minus leakage terminals, when the neon should glow for a time before going out. The signal control is then switched on and left at the CAP setting. After a short period the neon will commence to flash at regular intervals, the capacity being ascertained by the interval between flashes. With 250 volts applied

to the H.T. terminals, times should be roughly as follows:

$8\mu\text{F} = \frac{1}{2}$ second off; $16\mu\text{F} = 1$ second off; $32\mu\text{F} = 2$ seconds off.

Larger condensers than these should not be attempted, although they may be measurable with a lower applied potential. In any case, their normal leakage current grows greater and modification of the unit to suit would result in spoiling the other amenities of the apparatus.

If the leakage is excessive, the neon will remain

alight. If condenser is open-circuited, neon will oscillate.

Important Note

The particular neon used (CV71) has a tendency to oscillate better one way round than the other in the holder. This position will be found by observing when a glow surrounds the ring in the lamp and extends right down the supporting wires. Three different neons of the same type have been tried with similar results.

BBC Television Transcription Service

WAR IN THE AIR, the series of BBC films recently seen by millions of viewers throughout Britain, will soon be shown on Canadian television screens. The Canadian Broadcasting Corporation have taken the whole series of 15, which trace the development of air power in our lifetime, and, by using film from official sources, present a graphic picture of the struggle for air mastery in the second World War. The films have been described as one of the achievements of BBC television.

Their sale in Canada also underlines one of the achievements of the BBC's Television Transcription Service, which is responsible for sending such films and tele recordings to other countries. This three-man unit (which, like the long-established transcription service for sound radio, is part of the BBC External Services) has just completed its second year of operations, and in that time it has given an international flavour to BBC Television. Films or tele recordings have been sent from the BBC to appear on television screens in Canada, the U.S.A., Holland, France, Germany, Belgium, Switzerland, Italy, Denmark and Japan.

Two Years Old

This two-year-old service grew out of the demand from other countries for tele recordings of the Coronation. It was clear that these countries were interested in what the BBC was doing; and none more than Canada, who is to-day the Transcription Unit's best customer. In 1953, nine films and 41 tele recordings were dispatched to Canada; and before the end of 1954 six films and 41 tele recordings had been sent.

What kind of BBC programmes have the Canadian viewers been seeing this year? They have seen Emyln Williams and Lord Beaverbrook in the Speaking Personally series, and the archaeological stories of the Buried Treasure programmes. They have watched the animal and bird features by George Cansdale and Peter Scott; and have seen something of Britain's stately homes. And the Canadians, like viewers in other countries, have taken many tele recordings of outside events, among them the Queen's return from her tour, Trooping the Colour, Sir Winston Churchill's speech at the Lord Mayor's Banquet, and on his 80th birthday. The round of British sport was covered in tele recordings of Rugby Union at Twickenham, the Boat Race, the F.A. Cup Final, racing at Ascot, Chataway's victory in the 5,000 metres, and the table tennis championships.

The U.S.A. took a number of tele recordings. Both N.B.C. and C.B.S. networks showed the Mansion House lunch while N.B.C. has given its viewers Sir

Anthony Eden's party political broadcast and racing at Ascot.

Europe has shown an interest not only in films specially made for BBC television, such as that about the artist Graham Sutherland, but in tele recordings of national and sporting events. Germany, for instance, showed viewers the Trooping the Colour, a full version of Sir Winston Churchill's 80th birthday presentation, and the England v. Germany soccer match. In Holland the Queen's return was among the programmes seen during the year. Switzerland, France, Holland, Belgium and Italy all took the Trooping ceremony; and Belgium particularly asked for library material about Christmas in England. And a tele recording of the table tennis championships, in which some of their expert players took part, was requested by Japan.

Speed Essential

In sending tele recordings of outside events to overseas television stations speed is essential. Some idea of the way the transcription unit works can be gauged from the fact that the tele recording of the Prime Minister's birthday presentation was received in Hamburg shortly after noon the next day. An edited version reached Canada within two days.

The European television networks are making an increasing demand for tele recordings of international football matches, particularly where their own national teams are concerned. In some studio programmes the language is a barrier. But this obstacle has been overcome with the Art Films made by the documentary department of the Television Service in association with the Educational Television and Radio Centre of the United States and the Arts Council of Great Britain. A separate music and effects track is provided, but no English commentary. The European television stations can then add their own commentary in the native language. This commentary is a translation of the English script.

Not only does the transcription unit send to countries with television but to those without a service. Films have gone to Malaya, Australia and Norway, for non-theatrical distribution. They are issued to film societies, Government film libraries and so on; but not to cinemas.

Tele recordings and films are sold to overseas television networks at prices which make the transcription unit fully self-supporting. In two years of work the unit has laid the foundation of a service which not only gives viewers in other countries a picture of British life, but which enables millions of people abroad to share with the viewer at home some of the pleasures and excitements of BBC television programmes.

NEW SERIES



Serviceing TELEVISION RECEIVERS

No. 9.—EKCO EK10, TS105 AND SERIES

By L. Lawry-Johns

THESE notes may be used in conjunction with many Ekco receivers which employed a basically similar chassis. Models may be found with or without radio, 9in. or 12in., table or console. Some employed SP41 valves instead of the more usual SP61 as used in the receiver about to be described. As is well known, the service equivalent of the SP61 is the VR65 and of the SP41 the VR65A. The receiver is of the TRF type and the circuit is quite straightforward. The radio unit is of the superhet type with four preset stations, and consists of a three-valve unit which will be described in detail later. The audio circuit of this receiver is different in many respects from other models in the series which are not fitted with radio. A point to bear in mind is that although a transformer is fitted and the receiver therefore is for A.C. mains only the chassis is connected to the mains, and caution is to be used as in the case of an A.C./D.C. receiver.

The aerial input is by 75 ohm coaxial cable through isolating condensers to the coils L3 and L4, a separate feed being taken to the radio section from the outer contact of the aerial socket via L1 which is the coil mounted at the rear of the socket. From L3-L4 the signal is taken to the grid of the first R.F. amplifier V1, which, with V2, is common to both sound and vision. The contrast control is fitted in the cathode circuit of V1. V3 is the vision only R.F., the sound signal being tapped off of the anode coil of V2. The coil L19 is the sound rejector, and is fitted in the grid circuit of V10, the first sound R.F. amplifier.

From the anode of V3 the signal is coupled by L9, L10 to the video detector V4, which is a double diode, the second section being used as the vision interference limiter. The video signal is taken from the cathode of the detector diode via a system of peaking chokes and a resistor to the grid of the video amplifier V5. The anode of V5 is D.C., coupled to the C.R.T. cathode via a choke resistor combination. The interference limiter is also fed from this point. A lead is taken from here to the cathode of the V4B diode. The anode of this section is connected to the cathode through a resistor; a second resistor is wired across this, but can be disconnected by operation

of the screw marked interference limiter at the rear of the chassis. A $.1\mu\text{F}$ condenser is taken from the diode anode to chassis. Operation of the screw changes the time constant of the circuit and thus V4B conducts just before peak white. This increases the effectiveness of the limiter, but affects the picture content.

Sound Channel

The sound signal is amplified with the vision by V1 and V2 and then passed to the grid of V10. A preset gain control is fitted in the cathode circuit of this valve to enable an approximate level to be obtained between TV sound and radio as the volume control is common to both. V11 is used as the second R.F. sound amplifier and also as the audio amplifier.

The TV sound signal is taken via a set of coils from the anode of V10 to the grid of V11. The anode of this valve is coupled through a further set of band-pass coils to one section of V12 which is a double diode. The rectified signal is then coupled to the cathode of the second section which is used as a series noise limiter. From the anode of this diode the signal is then taken back to the grid of V11 for A.F. amplification. The cathode of V11 is decoupled by two condensers, one, a $.001\mu\text{F}$, is for R.F. and the other, a $20\mu\text{F}$ 12 volt electrolytic, for A.F. bypass. The amplified A.F. signal is taken from the screen of V11 to one contact of the four-pin radio chassis plug. It is then passed to the radio-TV selector switch, and then to the volume control. Both the TV and radio signals are then passed back to the main chassis to the grid of the sound output valve, V13. A negative feed-back circuit is fitted from the anode of this valve through a $.001\mu\text{F}$ condenser and resistor to the control grid. This point should be borne in mind when severe distortion of sound is experienced.

The video signal at the anode of the video amplifier V5 is passed by a condenser and resistor to the grid of V14. This acts as the usual grid current type of sync separator. The sync pulses drive the valve into grid current which produces a steady negative bias across its grid leak resistor. Thus the negative video signals are placed beyond cut off and are not passed. The sync pulses alone are present at the anode of V14, which has two resistors and a choke in its anode circuit. The first resistor is decoupled to chassis by a $4\mu\text{F}$ electrolytic. This is another point to remember when unsteady synchronism is experienced.

Line Time Base

The frame pulses are taken from the junction of the second resistor and the choke. The line pulses

are taken from the junction of the choke and the anode of V14, and are fed by a condenser to the suppressor grid of the line oscillator V15. This valve is used as a combined miller and transition oscillator and no blocking oscillator transformer is therefore used. The scan voltage is developed across the cathode load resistor and is fed via a resistance-capacitor network to the control grid of the line output beam-tetrode V16. Line hold is by a variable control feeding H.T. to the grid of V15 through a 2.2 MΩ resistor. Should the control be at the end of its travel and still not locking this resistor should be suspect. V18 is the efficiency diode and is connected with its cathode to chassis. The anode is connected through the secondary of the line output transformer to the cathode and grid of the line output V16. The E.H.T. rectifier V17 is fed from the overwind on the line output transformer.

Frame Timebase

The frame oscillator is a thyatron marked V7 in Fig. 1, and is a 6K25. A fault very often met with is a "jittery" raster. That is, the picture rapidly vibrates up and down although the synchronism is still held. Almost invariably a replacement 6K25 will provide a cure. The valve base is sunk below chassis level and the valve is often difficult to remove. It is often necessary to help matters by pushing up the centre spigot of the valve from beneath. The blunt end of a pencil is often a help as a screwdriver may damage the surrounding components. The Frame Hold control is in the cathode circuit of V7 and operates purely by altering the cathode bias. The charging components are a 100Ω resistor and a .5μF condenser from the anode to

cathode. The load resistor is a 100 KΩ and the scan waveform is taken from the junction of the 100Ω resistor and the .5μF. It is fed through a .1μF condenser to the top of the height control, the centre slider of which feeds the grid of the frame output valve V8.

The cathode resistor of V8 is not taken directly to chassis. The secondary of the output transformer and the frame scan coils both have one side directly returned to chassis. The cathode resistor is connected to junction of the other two sides. As secondary winding has a low resistance of only 1Ω as opposed to the scan coils' 14Ω the cathode may be thought of as being in series with the secondary winding of the frame output transformer.

H.T. Supplies

H.T. is supplied by two half-wave rectifiers, the main television PZ30 and the UY41 in the radio unit. On television both are used, but on radio the PZ30 is switched out of the circuit and the UY41 carries the smaller load alone. Although both these rectifiers have a common cathode output, to the smoothing circuit, they are supplied independently from the primary of the mains transformer. The surge limiting resistors to the anodes of the PZ30 often go open circuit, and their location and replacement is very simple. They are wired to a tag strip at the base of the coated type, and lower wattage should not be used. If one should go open circuit it would leave one half of the PZ30 to take the increased load, the current drain would be excessive and one anode of the PZ30 and that of the UY41 would be seen to be red hot. In addition, the remaining resistor would be passing the excess current, and this would very soon cause it to become defective. This, of course, leaves the UY41 totally inadequate to cope with the situation. Under these circumstances the UY41 may flash over and blow the fuses. If, therefore, the fuses are found to be blown it is very necessary to check the UY41 for internal shorts, also the PZ30, which can well be responsible for the whole trouble, and ensure that the surge limiting resistors are in order.

Another common cause of trouble from an H.T. and blown fuse point of view is the power plug connecting the radio and TV chassis. This may well be found to have a leak between pins and should be given priority attention should trouble of this nature persist after the PZ30 and UY41 have been checked. Note that the video amplifier V5 has its H.T. supply to its anode maintained when the receiver is switched to radio. This is to keep the C.R.T. cathode biased so as to prevent the tube from being burned by a spot when switching from TV to radio. Therefore, the anode of V5 is supplied direct from the smoothing circuit and not via the connecting plug and TV radio switch, as is the remainder of the TV section. Of course, this also applies to the sound output valve V13, which is common to both TV and radio. The heaters of the TV valves are fed from

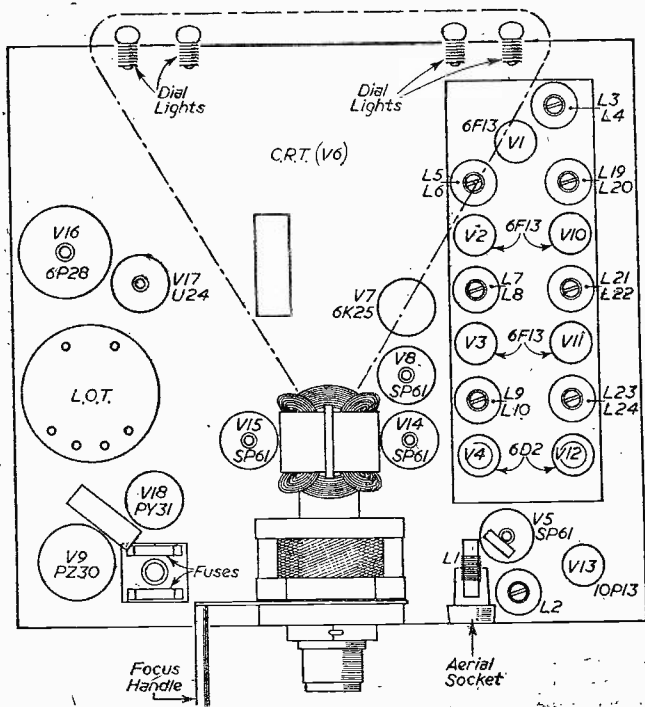


Fig. 1.—Top view of chassis.

various secondary windings on the mains transformer, again with the exception of V13, which is in series with the A.C./D.C. chain of the radio valves. The fuses should be rated at 1.5 amp.

Radio Section

The radio receiver consists of a triode-hexode frequency changer, UCH42. The I.F. amplifier is a UAF42 with its diode section used for detection. The output valve is, as stated, common to TV and radio and is a 10P13. The outer screening of the coaxial TV aerial cable is used as the radio aerial, as stated earlier. The I.F. is 455 kc/s and A.V.C. is fed from the detector circuit to the grids of the UCH42 and the UAF42. The station indicator lamps are switched by the selector switch, and the bulb in use is put in series with the heater chain and is shunted by a 100Ω 2-watt resistor wired from the radio selector switch to chassis.

Picture Troubles

Faults likely to be encountered are fading, weak reception, unsteady picture, weak or no synchronisation, partly collapsed raster, weak and poorly defined picture coupled with poor or no sync, and no raster at all.

Fading of vision only is often due to a poor contact on the valve bases of the vision valves. A varying emission video amplifier may be responsible, and it may be changed with another SP61, the sync-separator, for instance, to prove the point.

Weak reception may be caused by a large number of factors. Assuming the sound to be unaffected, however, the valves should be changed with reference to the diagram indicating their positions and purpose. If no improvement is effected a voltage check on the valve bases should be made, and the decoupling capacitors bridged in turn by a known good component. The decoupling condensers are of the .001μF tubular ceramic type, and can quite easily go open circuited with consequent loss of gain. V4 (the vision double diode) should be checked, and if no vision signals are being received do not forget to ensure that *both* sections are lighting up. A glow from inside the valve does not indicate that the detector section is being heated, and both heaters should be observed.

Open-circuited anode and screen decoupling resistors are a common cause of "no signals." These are of the 4.7 KΩ ½-watt type, and a voltage check on the valve bases will soon locate the faulty component.

Weak synchronism, assuming the contrast to be well up, usually points to the SP61 sync separator, V14, being low on emission. If this valve is changed with V5, that is, the video amplifier, and it is in fact low, the picture will now be darker, necessitating increased brilliance and contrast adjustment, depending upon just how low the emission has fallen. If the valve is not at fault attention should be directed to the 4μF 275-volt anode and screen decoupling condenser. This is one section of a double unit can, located under the chassis near the vision limiter plug. The other half of the unit is the 8μF anode and screen decoupler of V11 (sound R.F. and A.F. amplifier).

If the poor sync is accompanied by a smeared picture, poorly defined and inclined to tear, a cathode to heater leak in the C.R.T. should be suspected. If this is the case a heater isolating transformer may be fitted and should be of the 2-volt secondary type.

If one of these transformers is fitted the cathode should be joined to one of the heater leads so as to prevent variations if the defect is of an intermittent nature.

As described previously, a jittery raster is nearly always due to a defective 6K25 (V7 frame oscillator). Also a partly collapsed raster can often be caused by this valve. Usually, if this is the case, the bottom half of the raster will be almost normal, but the top

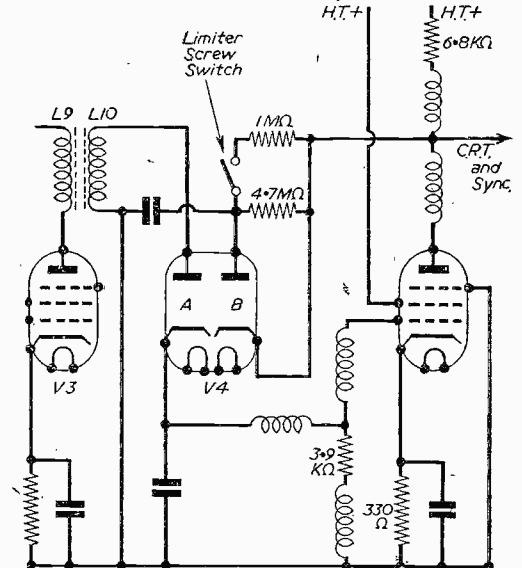


Fig. 2.—Vision limiter, detector and video circuit. Anode and screen separate the supply source.

half will be compressed to the middle, leaving a large blank area at the top of the tube.

The frame output valve (V8, SP61) may also be the cause of a small or reduced frame scan and can easily be checked by substitution.

If no raster can be resolved and the line time base whistle is absent the line oscillator (V15, SP61) should be suspected and changed as described previously. If a change of valve does not start the time base working normally the series resistor associated with the line hold control should be investigated. It is a 2.2 MΩ ¼-watt (red, red, green) and can go open circuited or high. This resistor should be suspected also when the picture cannot be locked in a horizontal direction and the control is fully over. The line output valve (V16, 6P28) could, of course, also be responsible for the non-operation of line transformer, E.H.T., etc. This is not so often the case, however, and the SP61 should be suspected first. If the time base is working, but there is no E.H.T., the U24 (V17) rectifier will often be found to be glowing blue inside. This indicates that it is soft and should be replaced. On later Ekco models, such as the 162 series, such a blue glow often indicates a defective line output transformer; the valve in this case is a wire-ended U25. However, in the receiver being dealt with, the line transformer is rarely the cause of the trouble and another U24 is usually all that is required.

By way of explanation, a blue glow in a valve indicates excess current; this does not apply to the

line output valve, which normally operates in this way. An excess current may be caused by a heavy load, as in the case of a leak in the line output transformer, or by the presence of gas (air) in the valve as in the set being described.

Sound Defects

Weak volume which is not distorted can usually be traced to a low emission V10 or V11, or these valves may be improperly seated. The electrolytic decoupling condensers used to by-pass the cathodes of V11 and V13 may be open circuited. These are separate condensers mounted near the respective valve bases and are rated at $20\mu\text{F}$ 12-volt for V11 and $50\mu\text{F}$ 12-volt for V13. These condensers, however, even if one is completely open circuited, do not cause a drastic drop in volume. Low volume on TV sound with marked distortion is often the result of the load resistor of the sound noise limiter going high or open circuited. This is rated at $2.2\text{ M}\Omega$ on this model, but may be found to be $4.7\text{ M}\Omega$ on some models which are "near relatives."

It will be found near the valve base of V12. It is hoped that the voltage table given will enable fault location to be speeded up and doubts as to whether this or that voltage is correct to be overcome.

A few final notes which may be of help:

The dial lamps are rated at 6 volts, .06 amp. The E.H.T. should be approx. 7 kV. The tube in this particular model is a Mazda CRM92 or CRM121 for the 12in. model. The cathode voltage should

read 185 volts. The sound output valve used on models without radio is a 6P25 in the same position as the 10P13.

TV VOLTAGE CHART

Valve	Anode	Screen	Cathode
1—6F13	195	195	1.9
2—6F13	195	195	1.9
3—6F13	195	195	1.9
4—6D2	—	—	—
5—SP61	185	242	2.4
6—Tube	7 kV	—	185
7—6K25	Pulsating		—
8—SP61	235	242	3.0
9—PZ30	225	—	—
10—6F13	195	195	1.8
11—6F13	185	185	1.8
12—6D2	—	—	—
13—10P13	225	242	13
14—SP61	Pulsating		—
15—SP61	190	142	30
16—6P28	—	210	.27
17—U24	7 kV	—	7 kV
18—PY31	—	—	—

RADIO VOLTAGE CHART

Valve	Anode	Screen	Cathode
UCH42	223	87	—
OSC	123	—	—
UAF42	150	87	—
UY41	—	—	226
V1310P13	210	223	11.5

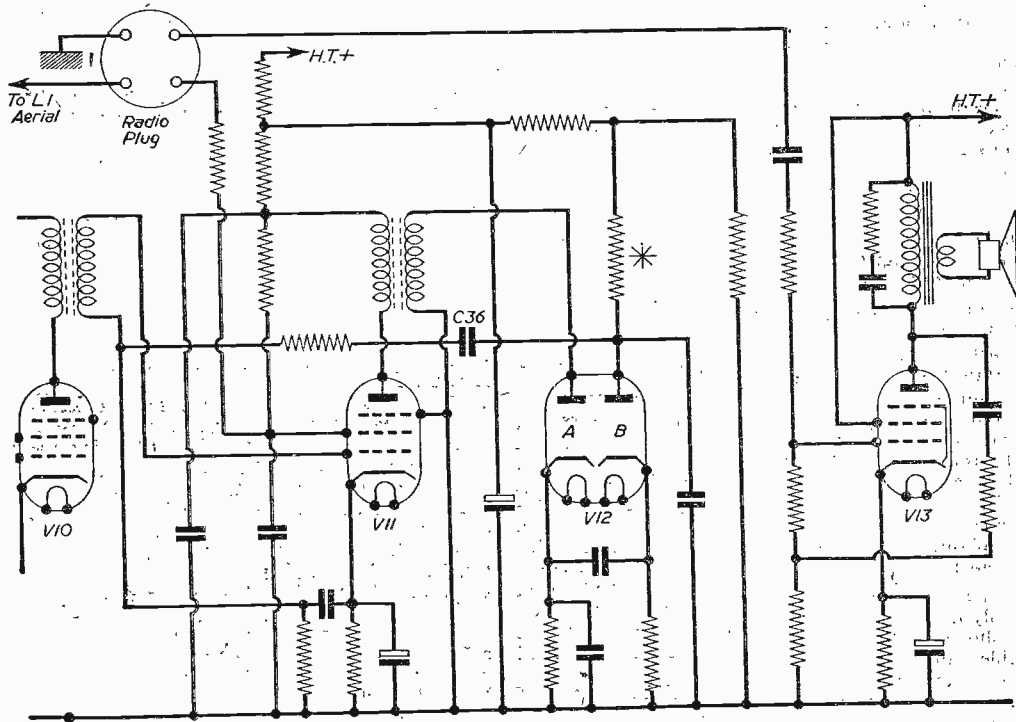


Fig. 3.—Television sound amplifier. C36 feeds back A.F. to the grid of V11 from the noise limiter anode. The resistor marked * is the limiter anode load and is rated at $2.2\text{ M}\Omega$ in this model.

The Radio Components Show

DETAILS OF SOME OF THE EXHIBITS AT THE R.E.C.M.F. EXHIBITION IN LONDON

ONCE again the component manufacturers have been able to show, under one roof, the vast collection of special items which they have produced for radio and television, and this year's exhibition, held as usual at Grosvenor House on April 19th to 21st, was even more interesting than previous shows. Naturally, with the advent of transmissions on Band III by the ITA there was a very wide selection of tuners and adaptors, but these were almost entirely of types designed for commercial receivers. They all appeared to consist of an R.F. stage, utilising a double-triode connected as an earthed-grid cascode amplifier followed by a triode-pentode as frequency changer. The output was generally at 34 Mc/s and intended for connection to the I.F. stages, and some had a special heater connection to provide the necessary 15 or 17 volts, whilst others were complete with power unit. Details of these will be given in a later issue. A general impression of the remaining exhibits would be that there is otherwise very little actually new, most of the items being improved versions of existing components, but one outstanding new development is the printed circuit technique which is being produced by the T.C.C. and other firms. One interesting component incorporating this principle is illustrated below and is a Belling-Lee circuit connector. These are designed for easy installation, and can be mounted side-by-side in multiples of four connector strips to produce a practically unlimited number of contacts. They can be "stacked" with spacers between for component mounting. They can be mounted direct to plates, printed or otherwise, and are suitable for mounting on ceramic and laminated plastic printed circuits.

T.C.C. Printed Circuits

On the T.C.C. stand was a vast range of samples of the types of apparatus which are available in this new technique. These included:

- Several high quality amplifiers.
- Radio receivers of the A.C./D.C. and battery types.
- Portables with contained battery.
- TV tuners for Band I and Band III.
- Aerial filters for TV receivers.
- Cross-over networks.
- I.F. transformers for TV.
- I.F. transformers and amplifiers for TV.
- Transistor computer panels.
- Telephone distribution panels.
- Flexible circuits, etc., etc.

In addition, various types of electrolytic and paper condensers were shown which were particularly suitable for assembly in printed circuit panels. There were, of course, also the many electrolytic, ceramic and plastic film condensers already well-known under such names as "Metalmite," "Micro-pack," etc.

Potted Chokes

Another type of component which is coming into increasing use is the "C" core potted transformer and choke. Illustrative of these is the W/B component shown on page 540. This has a "C" core moulded in Aroldite, and is fitted with waterproof plugs and sockets. Other W/B exhibits included the complete range of Stentorian high fidelity loudspeakers, now incorporating the patented Cambric cone from 2½ in. to 18 in. in diameter, including 8 in., 9 in. and 10 in. models fitted with universal impedance speech coils, providing instant matching at 3, 7.5 and 15 ohms.


The television components series shown included numerous items suitable for wide angle C.R.T.

The radio sonde transmitter as supplied to the British Meteorological Office and several foreign governments will also be seen at this company's stand.

Ion Traps

As one of the largest manufacturers to the trade, the Plessey exhibit was particularly interesting. Many set makers use ready-made Plessey parts and among the new television items which Plessey had on view was a new ion-trap magnet specially designed to reduce astigmatism in picture tubes. This ion trap gives an approximately linear field distribution and a small decrease in field strength along the axis. This is achieved by means of new style pole pieces in which the usual half-circle pole pieces have been replaced by soft-iron strips bent twice along their lengths.

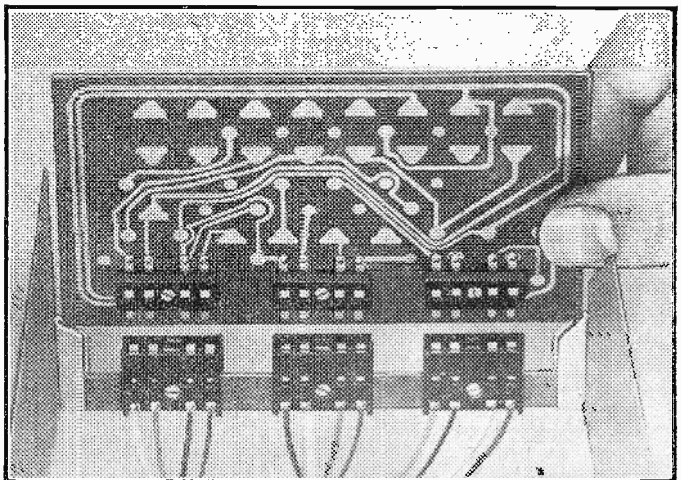Standard focus units on display consisted of two Ferrite magnet rings exactly aligned, the rear magnet being capable of axial positional adjustment with respect to the front magnet, which is fixed to the main assembly. Varying sizes of magnet are made, with or without a shift ring clamp.



A Belling-Lee printed circuit component.


A combined focus and scan unit was shown, consisting of a mounting which has a scanning coil in a screening cover on the front portion, and a double-ring focus unit on the rear part. Adequate mechanical shift is provided by a steel ring fitted in front of the forward magnet; its position is such that it introduces the minimum of spot distortion. The screening coil can be moved axially over $\frac{1}{2}$ in. total within its screen. An important feature of this unit is

with the same screen diagonal. This enables the front-to-back cabinet measurement of a television receiver to be kept reasonably small (21 in.), a factor of special importance in table models.

A new range of Mullard cores has been developed for line output transformers and scanning coils for use with the 90 degree tubes.

For line output transformers, the new cores give closer coupling between coils and core, leading to higher inductance for a given number of turns and lower leakage inductance. The resulting circuits have less tendency to "ring."

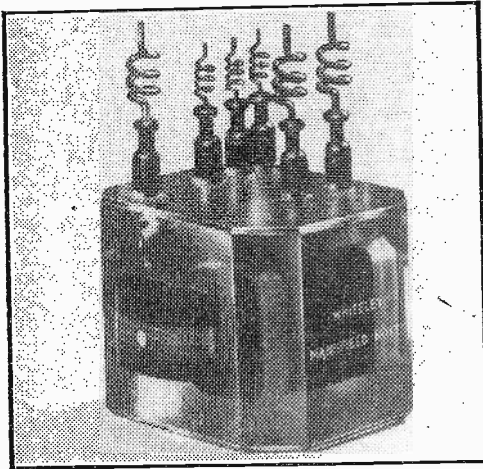The cores for scanning coils have been produced in the form of 16-slot castellated yokes, specially shaped to allow them to be fitted close to the flare of a tube, thus avoiding corner cutting. An advantage of the use of 16 slots is a more uniform magnetic field, and therefore a reasonably undistorted raster.



A potted "C" core transformer by Whitley Electrical.


that the picture tube is supported by resilient means within the neck of the assembly. A number of different handles for the focus unit are available and the shift ring is provided with a clamp at the top of the unit. The leads from the scanning coils are brought out from a slot provided at the front end of the cylinder.

Aerials

Several firms had television aerials on show and although generally these are unchanged (that is, they still consist of single, "H" and "X" units) some of the models shown had the new Band III units added. These Band III aerials were seen in various types, from single to folded units, and with and without directors and reflectors. The illustration on the right shows a folded dipole and director adaptor, intended for assembly on a standard Band I dipole, in which case it offers a substantially correct impedance match to the feeder, and the Band I dipole acts as a partial reflector on Band III, giving an overall gain of about 4 db. This kit is intended to sell at £1 16s. The "Addex" is an antiference Band III aerial, also arranged to assemble on a standard Band I, "X" type aerial. This may be added in different ways to provide the equivalent of a Band III, "H" aerial and give equal reception from stations in opposite directions—a most important point, as some receiving sites may be in a position mid-way between two transmitters.

Solders

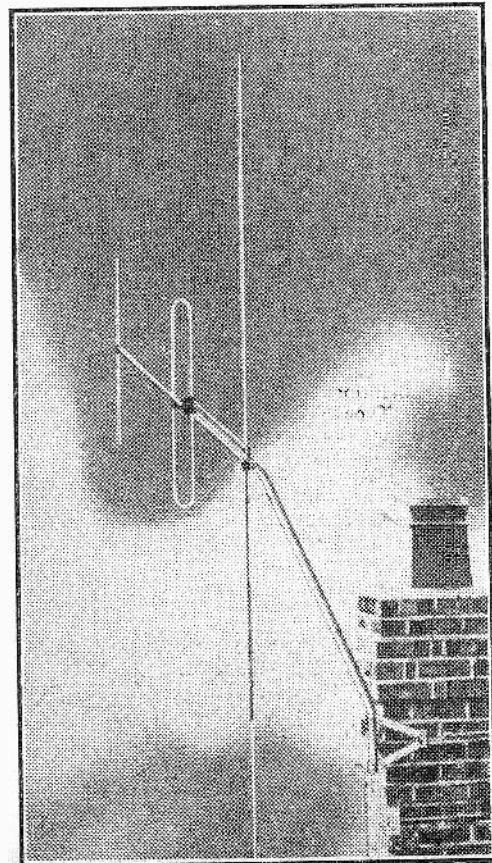The well-known Ersin Multicore Solder, containing five cores of extra fast non-corrosive type 362 flux specially formulated for extreme soldering speed, was an important feature of the Multicore stand: A new type of Ersin Multicore Solder which was shown, also containing five cores of the extra fast non-corrosive




A Band III aerial mounted on a standard Band I dipole. This is a Belling-Lee kit assembly.

Valves and Tubes

Several new picture tubes were to be seen, amongst them being a new Mullard 21 in. tube for 90 degree scanning, the MW53-80. This is of particular interest in that it is about 3 in. shorter than 70 degree tubes

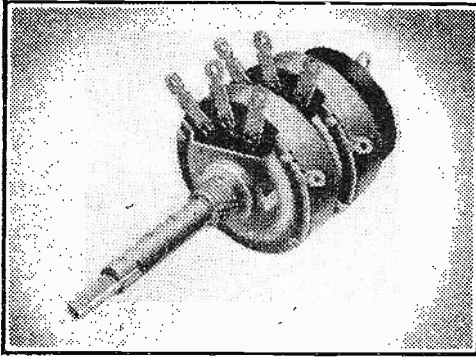type 362 flux, is known as Savbit alloy and contains approximately 2 per cent. copper and is claimed to increase the useful life of a soldering bit by 10 times. This special alloy which is made under sole British Licence of Patent No. 721,881 is already in production and can be supplied in nominal tin content alloys of 50 per cent., 50 per cent. and 40 per cent. There is no



One of the new dual controls with concentric spindles, by Egen Electric.

appreciable difference in melting points between Savbit alloys and conventional tin/lead alloys.


Steps are being taken to obtain A.I.D. approval for Savbit alloy and for any new edition of B.S.S. 219 to be amended for such copper-loaded alloys.

Among the other special solder products exhibited was solder tape, solder rings and washers, preforms and a complete soldering and fluxing process for printed circuits. (The attention of component manufacturers is drawn to Multicore Activated Surface Preservative, P.C.10. This material, which is already being used by manufacturers of printed circuits, ensures that wires and tags will not become oxidised during storage.)

Among the many other items seen were a wide range of components displayed by Egen Electric, Ltd.

Designed for application in the television and electronic engineering fields, the new range of Egen dual potentiometers with concentric operating spindles (Types 136, 137 and 138) incorporate all the features which have contributed to the success of the Egen potentiometers, including multiple contact rotors, smooth, easy movement and freedom from wear and noise. The component is designed to ensure thorough screening between sections, and spindles can be machined to customers' particular requirements.

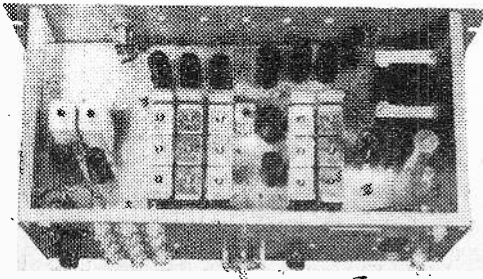Type 138 has a double-pole, single-throw mains switch; Type 137 is of similar design but incorporates



a single-pole, single-throw switch; and Type 136 is exactly similar but has no mains switch.

The new Egen concentric switch potentiometer range (Types 154 and 155) offers the outstanding advantage of an independently operated switch, and this component when applied to a typical modern television receiver reduces day-to-day operation to simply switching on and off, while the potentiometer can remain pre-set in its optimum position.

Type 154 is fitted with a single-pole, single-throw mains switch, while Type 155 is an identical component, but with a double-pole, single-throw switch.

On both types the switch is operated by the inner spindle and the potentiometer by the outer spindle.

The Egen Types 126 and 127 pre-set potentiometers are widely specified by television and electronic equipment manufacturers. Type 126 incorporates an efficient wire-wound element, while Type 127, of identical external appearance and dimensions, has a carbon element.

Also shown were the Types 105 and 115 miniature carbon potentiometers, co-axial plug and socket, Type 104 special wire-wound pre-set resistor, Types 123 and 125 sub-miniature carbon pre-set resistors, a number of interesting special inductance mechanism assemblies, a sub-miniature volume control, and several components designed for incorporation into printed circuits.


Messrs. James Neil & Co. (Sheffield) showed a wide range of magnets for loudspeakers and for ion traps, focusing and picture shifting in television.

At the 1954 Radio Components Show this company exhibited prototypes of the remarkable new Radial Focalizer, then emerging from experimental stages. The Radial Focalizer is now in bulk production. It is highly efficient magnetically, it is non-astigmatic, and it has no significant external field.

Rectifiers

A comprehensive display of Westalite rectifier units included a number of new miniature assemblies in various types of sealed housings. All of the new miniature rectifiers contain either double or quadruple voltage elements capable of withstanding peak inverse voltages of 42 and 85 volts respectively. Although many of these midget rectifiers were developed primarily for Service and Ministry requirements, they have also found a ready commercial market.

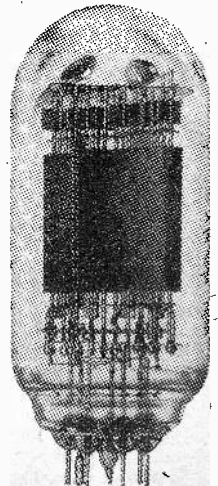Westalite rectifiers for radio and television anode supplies include both the usual spindle types and the newly developed contact cooled rectifiers for chassis mounting. The latter rectifiers dissipate their losses through the chassis and therefore effect a considerable saving in space, and increased efficiency.



Left: A 5-channel pre-selector, by Plessey. Right: a new Mazda Beam Tetrode D.C. control valve, type 13E1, suitable for use in stabilised power supplies.

CORONA DISCHARGE

THE CAUSES AND CURE OF A COMMON FAULT

By W. J. Delaney

A VERY common defect in many home-constructed and serviced commercial receivers often causes difficulty due to its similarity to other faults. We refer to that trouble known as "corona discharge." It is a form of arcing which occurs in the E.H.T. circuits and which, in an extreme case, is apparent on visual inspection of the chassis and also by the peculiar smell which arises shortly after the discharge commences. Before going into this fault further it would be as well to try and explain how the trouble arises. To put it non-technically it may be stated that E.H.T. may be considered as travelling at high speed (pressure), and is thus comparable with a car or train travelling at high speed. Any change in direction of the latter must be carried out over a curve, the higher the speed (pressure) the more gradual the curve. If a railway track has a curve designed for slow speeds, and is accordingly fairly sharp, a train arriving at the bend at high speed will shoot off the rails in the direction it was already travelling, and the E.H.T. current does exactly the same thing. If there is, for instance, a terminal on the E.H.T. transformer and a lead has to go from this to the anode cap on the C.R.T., the lead from the terminal should come away in a gradual curve to the anode cap, and if it is soldered and taken at right angles a corona discharge is almost certain to take place at the angle. Similarly, the solder surrounding the point should also be put on in such a manner that it has no points.

Corona Points

One of the main effects of a corona discharge is to generate ozone, a smell peculiar to the seaside, and which can readily be identified when once it has been noticed. Therefore, if corona is suspected it would be quite a good way of confirming it to *switch off*, and then smell inside the set. The smell will hang about for some while before dispersing. Similarly, if the chassis is inspected in a darkened room, the source of the discharge will be located as a faint blue—either halo or thin pencil beam. The extent of the corona depends upon the value of the E.H.T., the sharpness of the bend, or the acuteness of the point from which it takes place. The sharper the point, or the higher the E.H.T., the greater the corona. Accordingly, by flattening the point the discharge will be reduced, and if the point is finally removed or rounded off the discharge will cease. Similarly, if the E.H.T. is reduced so will the discharge, until at a certain value it will cease.

It might be thought that the trouble will not matter, but the reason for this article is that many occasions have been investigated where a constructor or viewer thought he was suffering from some other trouble when the real trouble was simply corona discharge. The most obvious effect of the arcing which takes place under this condition is the production of white spots on the raster. These are very similar to those experienced in fringe areas from radiated interference, but can be identified in that they usually cover the entire raster evenly. Car interference, or interference from other types of electric motor usually take the form of lines of dots,

generally dividing the screen into three equal parts, and sometimes these lines travel up and down the screen. Local interference from, say, a hair dryer or vacuum cleaner, will again be in more or less band form, although if very close to the receiver these may cover the entire raster. It will be found, however, that there is a distinct regularity in the formation of the spots. Atmospheric disturbances in fringe areas, or noise from over-driven valves on the R.F. side, will be of haphazard formation and cover the screen, but the spots will generally be more widely spaced and more erratic than those produced by corona. Service men who are not familiar with the trouble can easily create it by drawing off some solder to a point on the E.H.T. feed and making this very prominent so that corona takes place and then noting the effect on the screen. Unfortunately the point at which the discharge takes place may be under the chassis or otherwise obscured, so that it is not readily visible. It may be of such a character that it produces no spots on the screen, and the viewer may thus be unaware of the fact that it is taking place, other than that the E.H.T. will be reduced. If the receiver has a separate volume control this may be turned right off, and if the set is reasonably quiet it should then be possible to hear the discharge in the form of a sizzling or frying noise, fairly high in pitch, and regular, as distinct from that produced by noisy resistors, etc. Again, if the point is below the chassis the noise may be masked. Removing the aerial lead is not a definite test, as noise caused in the early stages may give rise to a trouble which may not readily be distinguished from corona by the inexperienced, and it may not be possible to remove valves as a check if the heaters are wired in series.


If the frying noise can be heard, and it is doubtful whether it is corona or a noisy component; one test is to reduce brilliancy, or otherwise adjust the tube controls so as to vary the beam current and thereby modify the E.H.T. flow. Alternatively, in the case of flyback E.H.T. the drive may be reduced to lower the E.H.T., and if the noise ceases with lowered E.H.T. then it is fairly certain that it is corona.

Soldered Connections

It is a good plan, to make sure that corona will not occur in a home-made receiver, to solder all connections which are in any way connected with the E.H.T. supply with round beads of solder and to run all leads in curves rather than direct from point to point. For instance, in the case of a flyback E.H.T. arrangement, similar to that used in the Super-Visor, from the anode of the line output stage every lead should be regarded as critical. This includes the leads to the recovery diode, the E.H.T. transformer, the heater leads for the E.H.T. rectifier and the smoothing capacitor. In addition, the actual connections to the anode of the tube must also be kept free from points and sharp angles. It will be remembered, for instance, that in the Super-Visor the E.H.T. connections were made by means of metal clips mounted on the tops of smoothing condensers, and the front edge of the metal tube rests in the clips.

(Continued on page 571.)

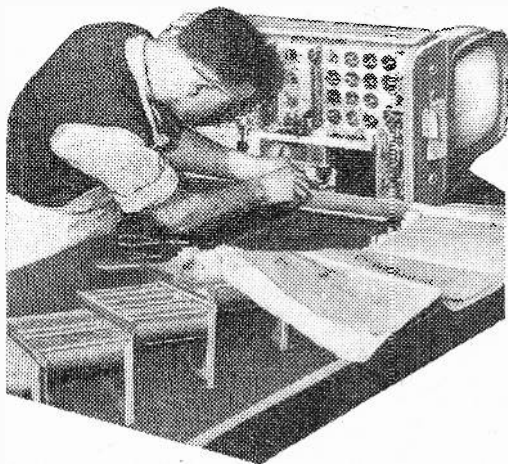PAGES FROM A TELEVISION ENGINEER'S NOTEBOOK



THE CATHODE FOLLOWER CIRCUIT

potential at the cathode will cause changes in the anode voltage V_a and the grid voltage V_g equal to the change in voltage across R_k , say, V_k . V_a is diminished and the grid is effectively more negative than it was before with respect to the cathode.

It is not very difficult to see that the gain will always be less than unity because any change in the input voltage must appear, in part, as a change in bias, in order to produce a change in the valve current. Only the balance of the input voltage appears as output. It is simple to show that the gain of the circuit is given by

$$\frac{\mu R_k}{R_a + R_k(1 + \mu)}$$

where R_a is the valve impedance and μ the amplification factor. For the gain to be as near to unity as possible, μ must be much greater than 1, and R_k must be much greater than R_a . There is no difficulty about the first of these conditions, but the second is often impracticable.

Unlike the anode loaded amplifier, a positive input to the cathode follower produces a positive output, and a negative input produces a negative output, that is, there is no reversal of phase.

In the true cathode follower there is no anode load, but in practical circuits one is often included. The circuit is then basically a phase-splitter, but the theory of the cathode-follower still stands. The outputs are both less than unity in gain, and the output at the anode is of reversed polarity to the input.

Input and Output Impedances

It can be shown that the input impedance of a cathode follower is very high due to its very low input capacity; in fact for a triode the input capacity is given by

$$C_{in} = C_{ag} + C_{gc}/\mu$$

where C_{ag} and C_{gc} are the anode-grid and grid-cathode capacities respectively.

THE cathode follower is often found in the home-constructed television where it is nearly always used as an impedance matching device for feeding into a capacitive load such as a picture tube.

Basically, the cathode follower is a negative-feedback type of valve circuit with the output taken from across an unby-passed cathode load; or, as it is sometimes looked on, an amplifier circuit in which the load is common to both anode and grid circuits.

It is characterised by a very high input impedance and a low output impedance, so that a direct output coupling can be taken into a low-impedance cable or highly capacitive load. Since the output of an ordinary amplifier with the load in the anode circuit is high impedance, such a system cannot be used for direct coupling in this way unless some impedance matching device such as the transformer is interposed. This is all right at audio and low frequencies, but at television video frequencies extending to some 4 Mc/s or so a transformer is not a practicable solution. The cathode follower, on the other hand, can readily be adapted as such a device for its high input impedance permits feeding from the output of a preceding amplifier of normal design, and the frequency response is not limited over the range mentioned above.

Basic Circuit

A basic cathode follower is shown in Fig. 1, where the cathode load is R_k , and the input signal is applied between grid and earth. The presence of a signal causes an A.C. component of voltage to be developed between cathode and earth, and so R_k may be considered as an A.C. generator as far as its feedback function is concerned. A change in the

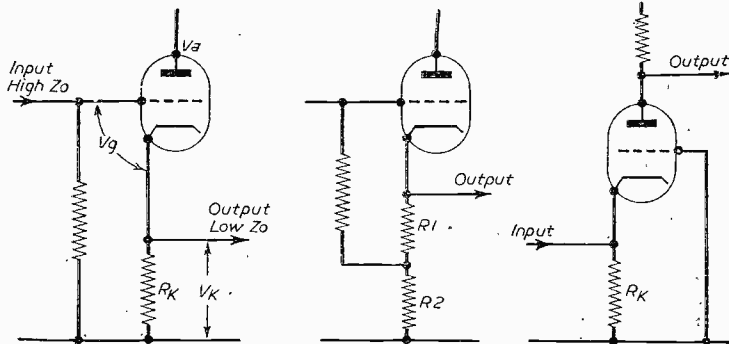


Fig. 1 (left).—A basic cathode follower circuit. Fig. 2 (centre).—Modified circuit. Fig. 3 (right).—Cathode input stage.

The valve works with its grid always negative with respect to cathode, and a high amplitude positive input is, therefore, permissible without the danger of grid current flow. This is due to the degenerative effect of the cathode load, the high impedance being maintained essentially constant throughout the input cycle.

The cathode impedance of the stage can be shown to be equal to $R_a/(\mu+1)$; as μ is always very large compared with 1, this reduces to R_a/μ which is, of course, effectively $1/g_m$. The output impedance of the cathode follower is, therefore, this cathode impedance in parallel with R_k , which is $R_k/(1+R_k/g_m)$. The output impedance is consequently very low and can be matched quite easily into 70 ohms type cable by the use of a high slope valve and the proper value of R_k .

It should be noted that whereas the output impedance of an anode loaded amplifier is constant, the output impedance of a cathode follower may not remain so. The mutual conductance g_m varies with anode current and is subject to variation with changes in the instantaneous input voltage amplitude. For example, if the input swing is sufficiently negative to cut the valve off, g_m becomes zero and the output impedance is then simply R_k .

The output from a cathode follower is distortionless if it is operated within its normal range, but it will distort in the same way as any other type of amplifier

if the input swing is excessive. When very large negative inputs have to be handled, the circuit may be modified as shown in Fig. 2. R_k is now split into two parts and the grid is returned to the centre point of them. The valve bias is consequently reduced to the voltage present across R_1 , and a greater negative swing can be handled as input.

The Cathode Input Stage

A modification of the basic follower circuit is shown in Fig. 3, where the input is applied to the cathode and the output is taken from the anode, the grid being earthed. The input impedance of this arrangement is low, but the output polarity is in phase with that of the input as it is in the cathode follower. The gain this time is not less than unity, but is, in fact, rather greater than the gain of an ordinary anode-loaded amplifier using similar components.

The application of such a system as this is restricted because of the low input impedance, but it can be used to match a low impedance line into a high impedance circuit. It is, in fact, the opposite number of the cathode follower in that it represents a step-up transformer as compared to the step-down effect of the latter system.

Its main application in modern television is found in the R.F. side of the set as the earthed grid input amplifier for V.H.F. working.

New Mullard Cathode Ray Tube Tester

AT Mullard Valve Service Depot, Glasgow, a new equipment designed to test television picture tubes to laboratory standards has been brought into operation.


The equipment is capable of testing to the laboratory test specification all direct-viewing tubes whether fitted with straight or ion trap guns and the design is based on tube testing equipment used in the Mullard tube factories. The design of the tester makes for ease of handling by the operator. For example, the tube can be turned from the vertical to the horizontal position for screen inspection by means of a low geared motor on pressing a button. Faults can be quickly located, however obscure, and an accurate technical assessment of the trouble can be easily obtained which is invaluable to the central service organisation for statistical records and quality control.

The test procedure begins with a check on the insulation between electrodes, including a measurement of heater-cathode insulation, the voltages applied being in excess of those which occur under normal operating conditions in a television set. Next, operating voltages are applied, and a raster is put on the screen. Adjustments are made to focus controls and, if necessary, to the ion trap magnet, and under normal brightness conditions the tube face is examined for screen-uniformity and brightness under focused and de-focused conditions.


Characteristics of the tube, including emission, cut-off, stray emission, and gas current are now measured, and the tube is subjected to overload conditions to investigate arcing, brushing and insulation breakdown. Readings are taken on 16-voltage current meters of the wide scale type.

Elaborate safety precautions include the fitting of armour plate glass to the front of the tube screen, and automatic disconnection and short circuiting

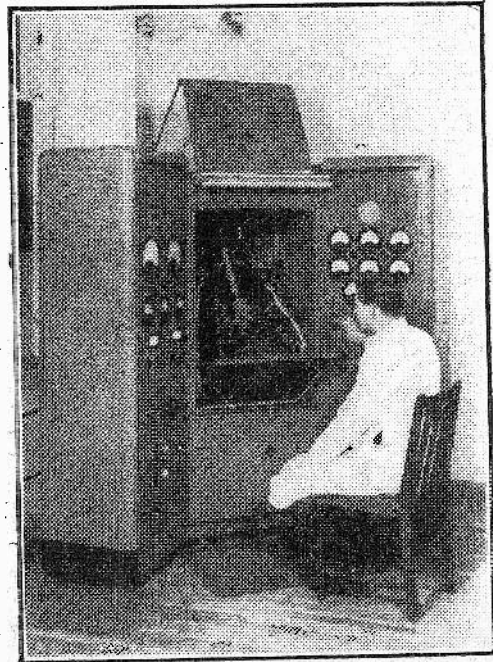of the E.H.T. voltage when the tube is in a position to be handled by the operator. Safety switches automatically disconnect the mains when the rear doors of the tester are opened for servicing.



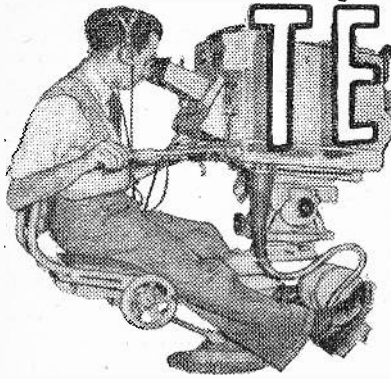The new television picture tube tester at the Mullard Valve Service Depot, Glasgow.



TELENEWS



Televising the Olympic Games

SIR GEORGE BARNES, director of television to the BBC, told the Radio Industries Club of the Midlands recently that it may be possible for the Olympic Games to be televised to Europe from Melbourne, Australia, next year.

This could be done, he said, by passing the TV link on from country to country just as programmes are sent to this country from Europe. He added that there was no technical reason why this could not be done.

I.T.A.'s Croydon Station

WORK on the I.T.A.'s temporary transmitter is now well in progress.

The contract for the station, complete with 200ft. tower and a special high gain aerial, has been awarded to Marconi's Wireless Telegraph Co. Ltd., who are also supplying the vision and sound transmitters.

The Cup Final

IT is almost certain that the Cup Final on May 7th will be televised to large screens in several cinemas throughout the country.

TV Network by July

THE Austrian postal authorities have been told to have ready by July 24th a complete television network with stations at Linz, Salzburg, Vienna and Graz.

This order comes from Herr Waldbrunner, Austrian Minister of Communications.

Wrong Ratio

THE extra width of films made in CinemaScope makes it almost impossible for them to be shown to best advantage on the narrower television screen. This is one form of spectacle that can be seen only in the cinema.

Television Licences

THE following statement shows the approximate number of television licences issued during the year ended February, 1955. The grand total of sound and television licences was 13,916,246.

Region	Number
London Postal	1,108,493
Home Counties	475,796
Midland	811,781
North Eastern	636,365
North Western	638,867
South Western	236,505
Wales and Border Counties	239,379
Total England and Wales	4,147,186
Scotland	237,512
Northern Ireland	22,695
Grand total	4,407,393

Commercial Appointment

IT is announced that Mr. R. H. Hammans has left the BBC to take up duties as chief engineer with Granada Television. He will supervise the building of Granada's TV centre in Manchester.

Staff Shortage

SIR IAN JACOB, BBC Director-General, has stated that the shortage of qualified television engineers in this country will soon become acute.

"The new era of competition means a problem of staff to be faced," he forecasts. "Top-grade TV producers are at a premium and it will be a pretty good fight as to who gets them."

Scottish Stations

THE Independent Television Authority hope that one or possibly two commercial television stations will commence operation in Scotland next year.


Suppressors for Fire Brigade

VIEWERS in Worcestershire will not be bothered by television interference when fire engines rush past their houses on alarm calls.

All fire brigade vehicles in that county have now been fitted with suppressors.



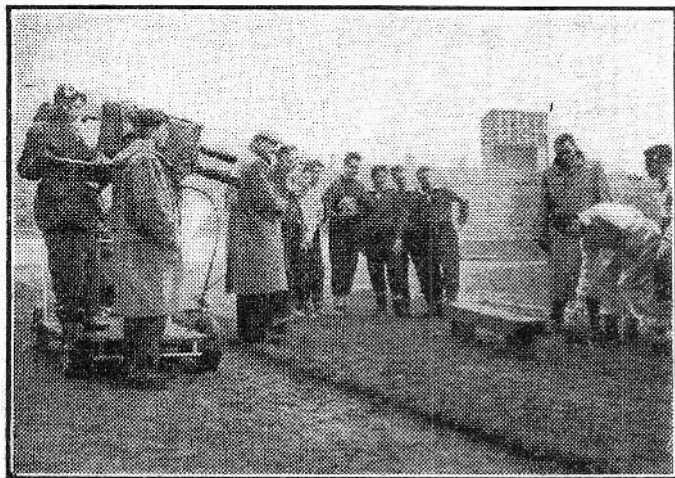Left to right: Beryl Reid, Jeremy Hawke and Benny Hill in a recent edition of the popular "Benny-Hill Show."



The camera spotlights Roy Paul, Manchester City captain, as he rehearses schoolboy footballers for a Children's Television broadcast at Maine Road, Manchester.

No H Aerials at Tower

FOLLOWING a Ministry of Works decision that they were not in keeping with the character and dignity of the building, the individual TV aerials on the living quarters of the Tower of London have been removed and replaced by one central aerial.

The new installation is invisible from the ground and has been carried out by E.M.I. Sales and Service, Ltd.

Cameras For Tests

BBRITISH aeroplane manufacturers are using special television cameras for testing new aircraft engines.

The cameras give the designers close-ups of the power units in operation and any fault in performance or behaviour is instantly noticed.

Play Telerecording

WHEN a telerecording of the play "For Dear Life" was shown to viewers on April 7th it was the first to be seen under the recent agreement between the BBC and Equity.

Light Entertainment

THE pattern of light entertainment during the coming months is now taking shape. On Sundays the panel show "Guess My Story" will be augmented with a fortnightly half-hour show televised from Blackpool, starting in May or June. Mondays will carry Henry Hall's "Face the Music," "Café Continental", and "Show Case" with Dave King.

"Find the Link," "Top Town" and "Garrison Theatre" shows will be placed on Tuesdays, and Wednesdays will bring two new shows to the screen—"Off the Record," a disc programme starting on May 11th and "The Lyon Family" on June 15th.

Where Honesty Pays

ARENO, Nevada, club manager has installed a television camera above his gambling tables, with a cable connection to a receiving screen in his office.

The camera is constantly trained on the players trying their luck; any signs of cheating are easily observed from the manager's office and the appropriate steps taken.

Ocean Cable

A HIGH power telephone cable will be laid across the Atlantic next year.

3-D TV

TELEVISION in three dimensions is being employed by the United States Argonne National Laboratory of the Atomic Energy Commission to control at a distance the operation of radio-active materials.

A twin lens is used on the camera and a normal set has been modified to receive pictures in 3-D.

Miss Jean Metcalfe

MISS JEAN METCALFE, who is now a member of the Outside Broadcasts Department (Sound), Entertainment Division, will take part in "Special Inquiry Into Cosmetics" on television on May 16th.

Norwich Transmitting Station

THE BBC has placed a contract with J. L. Eve Construction Co. Ltd., 17, Hillside, London, S.W.19, for the design, supply and erection of the 560 ft. stayed mast for the Norwich television station.

Design work has started and it is hoped that the mast, with its aerials, will be completed so that the station can be ready for service about the middle of 1956.

£1,500,000 a year

FOR the use of the three commercial TV stations which will operate from London, Birmingham and Manchester the ITA is charging its four programme contractors £1,500,000 a year.

The Treasury loan to the IFA of £2 million has to be repaid within ten years.

The Long Wait

MR. P. H. SPAGNOLETTI, of Kolster-Brandes, has forecast that colour TV will not be seen in Scotland until about 1959-60. He told this recently to members of the Radio Industries Club of Scotland at a meeting in Edinburgh.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berné Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

ALPHA FOR VALVES

GUARANTEED NEW AND BOXED

AC/P	6/9	PV30	8/-	5Z4G	8/6	6W2	15/-
AC6/PEN	5/8	PY80	11/-	6A7	7/6	6X4	8/-
ATP4	6/6	PY81	11/6	6AG5	10/6	6X5GT	7/9
B56	16/-	PX25	15/-	6AG7	6/8	786	9/6
DDL4	4/-	S180	8/6	6AGS	7/8	7B7	8/6
DH7M	10/-	SP220	6/9	6AJ5	9/-	7C6	8/6
DH81	10/-	SP61	3/9	6AK3	9/-	7H7	8/6
E A50	2/-	SP41	3/8	6AL5	7/-	797	8/-
EB34	9/-	TP26	9/6	6AM5	7/8	787	8/6
EB41	11/-	U16	9/-	6AM6	7/8	787	8/6
EBRC3	7/8	U16	12/8	6AQ5	8/6	7Y4	8/6
EBRC41	11/-	U22	8/-	6AT6	8/-	75	10/-
ERF80	11/8	U25	14/8	6B4	6/-	77	8/-
EC32	6/3	U35	15/-	6B8G	4/-	80	8/6
EC91	9/-	U281	10/8	6BA6	8/-	84	8/6
ECH35	12/-	U404	10/8	6B8	8/-	807	7/8
ECH42	10/8	UAF42	12/8	6BR7	9/6	8D2	2/9
ECL20	14/6	UB41	9/-	6BW6	8/6	9001	5/6
EP8	6/6	UBC41	11/-	6BX6	14/6	9002	5/6
EP36	6/6	UCH42	13/8	6C4	8/-	9003	6/6
EP39	6/8	UF41	11/-	6CG5GT	7/8	9004	5/6
EP41	10/-	UG41	11/8	6C6	6/8	9006	5/6
EP50S1	8/-	UY41	10/6	6C9	8/-	954	2/9
EP50	6/-	Y23	8/-	6CDBG	13/6	955	4/-
EP80	11/6	VR105/30	5/8	6D3	7/8	958	3/6
ER32	8/-	VR116	4/-	6D6	7/8	10C2	13/8
ET2	12/6	VR150/309	9/-	6F6G	7/8	10P1	10/-
EL33	12/-	U41	11/8	6FM1	8/8	10F9	11/-
EL41	11/8	U48	8/-	6FR8	7/-	10F,D11	13/-
EL42	13/8	VT75 (KT4)	7/8	6F13	13/8	10P13	11/8
EL84	12/3	VT105	7/8	6F14	12/8	10P14	11/8
EM31	9/-	VT501 (TF11)	11/8	6F15	11/8	12A6	8/9
EY51	14/6	U39 (MU12)	8/-	6G6G	6/6	12A8B	11/8
EZ39	12/6	V48	3/8	6H3	3/8	12AT7	9/-
EZ41	11/-	V41	8/8	6J5G	5/-	12AU7	9/-
E1148	2/-	VU111	3/8	6J6GT	5/8	12AX7	10/-
H30	5/-	VU120A	3/8	6J5M	6/8	12C8	3/-
H63	7/8	WB1	9/-	6J6	8/-	12H6	5/8
HLL230	5/8	W77	8/6	6J7	6/8	12L5	6/8
HL23DD	7/8	WB81	10/-	6K6GT	6/8	12J7GT	9/8
HP21C	7/8	OZ4	6/-	6K7G	6/8	12K7	9/8
KT2	5/-	IA3	9/-	6K7GT	6/8	12K8GT	9/-
KT32	10/-	IA5GT	6/8	6K7M	6/8	12Q7GT	9/-
KT38C	11/6	IA7	11/8	6K8G	8/-	12R6T	7/8
KT66	11/6	IG5GT	5/-	6K3GT	9/8	12S47	5/8
KT74	8/-	IB4	7/8	6L1	11/8	12S7	7/8
KTW61	7/9	ILD5	8/8	6L19	12/6	12SK7	6/8
KTW68	7/9	IR5	7/8	6L6G	9/-	12SL7	6/8
KTZ41	6/9	IR4	7/8	6L7M	7/8	12R07	8/8
LD210	6/9	IR5	7/8	6N7	7/8	12SR7	7/8
LP220	6/9	IR4	7/8	6O7G	9/-	20D1	10/8
MS/PEN	5/-	I15	8/-	6Q7GT	8/-	20F2	12/6
P61	3/9	220VSG	6/9	6R7G	8/-	20P1	10/-
PA20	14/-	2A3	6/9	6SA7GT	8/-	20P1	15/-
PCC84	12/6	2X2	5/8	68GT	7/8	20P3	11/-
PCF80	12/6	3A4	8/-	68H7	6/-	20P4	9/-
PCF82	12/6	3D6	5/-	68J7GT	9/-	25A8G	11/-
PEN25	8/-	3Q4	9/-	68K7	6/8	25L6GT	8/6
PEN44	12/6	3Q5	10/-	68L7	8/-	25U4GT	12/-
PEN46	8/6	3A4	8/8	68N7GT	9/-	25Z4G	9/-
PL81	14/6	3V4	8/-	68Q7	9/-	35L6GT	8/8
PL82	11/6	4D1	3/-	68S7	3/-	35W4	10/-
PL85	13/-	42	8/8	68T7	7/8	35Z4GT	8/8
PM12M	10/-	5U4 (U32)	8/8	6L5G	8/8	50L6GT	8/8
PM2B	5/8	5Y3GT	8/6	6V6G	7/8	117Z6GT	8/-
PM22B	5/8	5Z3	8/6	6V6GT	7/8	215SG	7/-

CHASSIS
Aluminium Cradled with Reinforced Corners. Available in the following sizes.

6in. x 4in. x 2 1/2in. 4/6 ea.
8in. x 6in. x 2 1/2in. 6/3 ea.
10in. x 8in. x 2 1/2in. 7/8 ea.
12in. x 8in. x 2 1/2in. 9/6 ea.
14in. x 8in. x 2 1/2in. 9/6 ea.
16in. x 9in. x 2 1/2in. 12/- ea.

All are four sided—ideal for radio receivers—amplifiers—powerpacks, etc.

SENERCEL RECTIFIERS
RM1, 3/9 ea.; RM2, 4/2 ea.; RM3 5/- ea.; RM4, 16/- ea.

WHEN ORDERING PLEASE QUOTE "DEPT. P.T."

METAL RECTIFIERS
12 v. 4 amp., 1/6 ea.; 12 v. 1 amp. 4/6 ea.; 2 v. 1 amp., 3/- ea.; 250 v. 45 mA., 6/3 ea.; 250 v. 75 mA., 7/6 ea.; 300 v. 60 mA., 7/6 ea.

GOLDRING PICK-UP HEADS. Pick-up head type No. 112 (2,000 ohms), complete with lead. Price 17/6 each.

NYLON DRIVE CORD
25 yard reel nylon drive cord on wooden reel, 2/9 ea.

BI CONDENSERS
Waxed cartons, with flying leads. 500 mfd., 500 v., 1/6 ea.; 4 x 4 mfd., 500 v., 3/4 ea.

MAINS TRANSFORMERS

3-WAY MOUNTING TYPE
MT1
Primary: 200-220-240 v.
Secondaries: 275-0-275 v., 80 mA. 0-6.3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. 17/6 ea.
MT2
Primary: 200-220-240 v.
Secondaries: 350-0-350 v., 80 mA. 0-6.3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. 17/6 ea.

LOUDSPEAKER UNITS
Rola 5in. Speaker with transformer..... 16/- ea.
Plessey 6in. lightweight unit 16/6 ea.
Rola 6in. standard type..... 17/6 ea.
Electrona 6in. with transformer..... 18/- ea.
Trustox 6in. water type..... 20/- ea.
Plessey 8in. lightweight unit 17/6 ea.
Mains energised 8in. unit, 1,000 Ω..... 21/- ea.
Mains energised 6in. unit, 600 Ω..... 17/6 ea.

CRYSTAL DIODES
Plastic case, wire ends, 2 for 2/1.
BAKELITE CASED BI CONDENSERS
0 mfd., 1,000 v.; .01 mfd., 4 kV.; .001 mfd., 4 kV.; .03 mfd., 500 v. All 1/8 ea.

DUBILIER NITROGOL CONDENSER
12 mfd., 350 v., 5/6 ea.
OSMOR COIL PACKS
Type H.O., 48/- ea. Type LM, 40/- ea. Type T.B., 20/- ea. Type TIF, 40/- ea.

SPRAGUE CONDENSERS
.05 mfd., 500 v.; .01 mfd., 1,000 v.; .1 mfd., 350 v.; .02 mfd., 750 v. All 9/- doz.

TCC VISCONOL CATHODAY CONDENSERS
Type CP370, .002 mfd., 18 kV., 7/6 ea. Type CP350Q, .001 mfd., 6 kV., 5/- ea. Type CP55T0, 500 pF., 10 kV., 5/- ea.

VIBRATORS, ETC.
Vibrator unit for 6 v. operation, 14/6 ea. Post 1/6. 6 v. and 12 v. Vibrators, 4-pin UX types, 6/6 ea.

DOUBLE TRIMMERS
250/250 pF., 100/100; 100/50. All 6d. each.

YAXLEY SWITCHES
3 pole, 3 way, 1 bank, 1/8 ea.
3 pole, 3 way, 3 bank, 1/8 ea.
Outlet Plug and Socket (screened), 1/- ea.

GOLDTRONS BAKELITE CASED BUZZERS 2/3 ea.

TRANSFORMERS FOR BATTERY CHARGERS
230 v. Input Tapped 6/-
12 v. 1 amp. 13/6 ea.
250 v. Input Tapped 6/-
12 v. 3 amp. 18/- ea.
Both with tap on Primary for 2.5 v. Pilot light.

HEATER TRANSFORMERS
250 v. Input 2 volt 5 amp. 4/6
230 v. Input 2 volt 3.0 amp. 7/9
230 v. Input 4 volt 1.5 amp. 5/-
230 v. Input 4 volt 3.0 amp. 10/-
230 v. Input 5 volt 2.0 amp. 10/-
230 v. Input 6.3 volt 5 amp. 5/-
230 v. Input 6.3 volt 1.5 amp. 6/-
230 v. Input 6.3 volt 3.0 amp. 9/-
230 v. Input 12 volt 7.5 amp. 5/-

PRE-SET CONTROLS (CARROW)

50 k Ω, 1 Meg Ω, 1 Meg Ω, 2 Meg Ω, 1/9 ea.
RESISTORS 2 WATT
2.2 k Ω, 470 Ω, 7.5 k Ω, 22 Ω
150 Ω, 5.6 k Ω, 390 Ω, 150 k Ω
1 meg Ω, .29 Ω, 1.5 meg Ω, 56 k Ω.
All 4d. ea.

★ ★ ★ ★ ★
EX GOVERNMENT AND SURPLUS CONTROLS
This popular range is suitable for all Television constructors, etc. Keep your costs down when building the "Argus" or "Simplex" receivers. Available: 500 Ω, 600 Ω, 1,500 Ω double type, 2 k Ω, 5 k Ω, 10 k Ω, 20 k Ω, 25 k Ω, 50 k Ω, 200 k Ω, 100 k Ω, 1 meg Ω, 2 meg Ω, 1 meg Ω double type. All 1/2 each.

COLVERN PRE SET CONTROLS
Type CLR 1106/85, 1,000 Ω ... 1/9 ea.
Type CLR 1126/78 250 Ω ... 1/9 ea.

★ ★ ★ ★ ★
RESISTORS
The following range of Resistors is available in 1/2 watt and 1 watt. Prices 1/2 watt 3d. ea. 1 watt 6d. ea.
10 Ω 120 Ω 1.5 k Ω 18 k Ω
12 Ω 150 Ω 1.8 k Ω 22 k Ω
15 Ω 180 Ω 2.2 k Ω 27 k Ω
18 Ω 220 Ω 2.7 k Ω 33 k Ω
22 Ω 270 Ω 3.3 k Ω 39 k Ω
27 Ω 330 Ω 3.9 k Ω 47 k Ω
33 Ω 390 Ω 4.7 k Ω 56 k Ω
39 Ω 470 Ω 5.6 k Ω 68 k Ω
47 Ω 560 Ω 6.8 k Ω 82 k Ω
56 Ω 680 Ω 8.2 k Ω 100 k Ω
68 Ω 820 Ω 10 k Ω 120 k Ω
82 Ω 1 k Ω 12 k Ω 150 k Ω
100 Ω 1.2 k Ω 15 k Ω 180 k Ω

SOLDERING IRONS
Solen type 964 fitted oval bit 19/11 ea.
Solen type 968 fitted pencil bit 19/11 ea.
Both types are complete with approx. 6ft. of Henley 3 core cable and are suitable for 230/250 v.

SOLDERING PASTE
Large tin soldering paste by Tyne Chemical Co., approx. 1 lb. 1/9 per tin

CONDENSERS
The following is a selection of our stocks of manufacturers' surplus condensers all by well-known makers—DUBILIER, B.F., BEC (EDISWAL), SPRAGUE, etc. Aluminium Can Types Clip Fixing:

STILL A FEW LEFT "THE COMPACT" TV AERIAL TYPE CD4 BY ANTIFERRE, LTD.
Full instructions with each one. Listed 50/-. Our price, 14/6, plus 1/6 packing and post.

ENAMELLED COPPER WIRE—All 4 pin Reels.

S.W.G.	Price	S.W.G.	Price
16	1/11	30	3/1
18	2/1	32	3/3
19	2/3	34	3/5
22	2/5	36	3/7
24	2/7	38	3/11
26	2/9	40	4/2
28	2/11		

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; £5 add 2/- unless otherwise stated. Minimum C.O.D. fee and postage 2/3.

MAIL ORDER ONLY

ALPHA RADIO SUPPLY CO

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

More About the RF26 Unit

SOME FURTHER DETAILS OF THIS USEFUL R.F. UNIT

By B. L. Morley

A LOT of interest has been aroused on this class of unit since my article in the February issue of PRACTICAL TELEVISION and in response to requests it is hoped that some further details may be of interest to constructors.

The circuit of the unit was given in the March issue of PRACTICAL TELEVISION. It comprises an R.F. amplifier using an EF54, a mixer also using an EF54 and an oscillator using an EC52. The service equivalents are VR136 for the EF54 and VR137 for the EC52.

The unit is in a self-contained chassis which is silver-plated, and is an excellent buy at the modest price of 35s. A power supply of 6.3 v. at 1 amp and 250 v. at 30 mA is needed additional to the unit itself.

Tuning is effected by a dial on the front of the chassis and the range covered is 65—50 Mc/s. The unit will tune Kirk o' Shotts and Sutton Coldfield (Channels 3 and 4) direct; Holme Moss and London (Channels 1 and 2) by the insertion of iron-dust cores in the tuning coils; Wenvoe (Channel 5) by the insertion of brass cores in the coils.

The output is delivered at about 7.5 Mc/s.

It was intended originally to feed into an I.F. strip—the well-known RJ355, which has I.F.s tuned to 7.5 Mc/s, but it is possible to use it with other I.F. strips provided that the oscillator frequency is altered.

Another feature is its possible use on Band III, and the writer will be giving data for this when it is available, should it prove practicable.

Tuning-in the Vision Signal

One important point with this unit which some constructors seem to miss is that when tuning the unit for single sideband reception (i.e., all transmitters except London) special precautions must be taken.

When used with an I.F. strip the following procedure should be adopted to ensure accurate tuning.

First tune the dial for maximum vision, adjusting the trimmers above the chassis, fitted across the tuning condensers, for absolute maximum. The trimmer on the front panel should be adjusted for maximum response.

Now adjust the small oscillator trimmer so that the "volume" of the vision signal is reduced by half. This is a small postage stamp trimmer fitted under the chassis, directly underneath the oscillator section. It will be found to be very sensitive and requires careful adjustment.

The adjustment should be made by turning the trimmer towards the sound channel. If it is not clear in which direction this lies so far as the trimmer is concerned, then note the dial reading giving maximum vision and then turn the dial to reduce the vision a little by increasing the capacity. For example, supposing the vision comes in at dial reading 100, then turn the dial to 110.

At this point you may get the sound coming in. Note the position of the marker on the oscillator

trimmer and adjust it so that sound is at maximum. This will show the direction in which the oscillator must be trimmed for optimum vision.

Now restore the trimming as it was originally for maximum vision and carry out the process given above.

The "volume" of the vision signal will be reduced by half and must be compensated for by operation of the contrast control. It will be noted that the picture quality is greatly improved.

When cores are being used in the coils for obtaining the requisite channel, then the cores should be set level with the tops of the coil forms and the separate ganging trimmers adjusted as given.

If brass cores are difficult to obtain then one turn can be taken from each tuning coil so as to get Channel 5.

It is also possible to avoid the use of cores for Channels 1 and 2 by adding one turn to each tuning coil.

The final adjustment for picture quality should be to adjust the small trimmer on the front panel.

Fitting a Wavetrap

One snag with the unit is that it is liable to let signals through at intermediate frequency. As the 7.5 Mc/s band is well occupied with high-powered transmitters, it is possible to get severe interference from this source.

To avoid break-through a simple wavetrap can be fitted directly in the aerial system.

Using a $\frac{3}{16}$ in. diameter coil former wind on 26 turns of about 34 s.w.g. enamelled wire, close-wound. Connect a 10 pF condenser across the ends and insert an iron-dust core. Break the wire from the aerial socket to the first coil and insert the rejector coil. The coil former can be mounted on the inside of the front panel. (Fig. 1.)

To trim it, connect an ordinary aerial to the aerial socket and adjust the coil for minimum sound. If this is done at night-time there are plenty of signals in the band which will break through.

It is possible to get sharper tuning if the 10 pF condenser is replaced by one at 0—30 pF.

Using a Pre-amplifier

The unit is extremely stable and a one-, two- or even three-valve pre-amplifier can be fitted. It has been the writer's experience that little is gained beyond a two-valve pre-amplifier.

When a pre-amplifier is fitted it will be found that there is no need for a wavetrap at intermediate frequency.

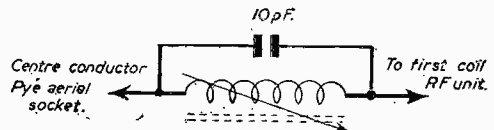


Fig. 1.—A rejector coil for 7.5 Mc/s.

Range of Unit

When used with the R1355 unit the RF26, with the aid of a two-valve pre-amplifier, can bring in the signals at what may be considered impossible ranges. I have received signals at over 180 miles which would provide a reasonable picture, and if the path of the signal is over water there is no reason why the range cannot be extended.

Of course, local conditions come into operation at these extreme distances and reception could not be guaranteed.

Here is a thought for those who live near the south coast. Why not try the transmissions from Paris using a really good directional aerial of high gain? If any reader has tried this the results would be interesting to hear.

Altering the I.F.

The intermediate frequency given by the unit can be altered by modifying the oscillator section.

Before we deal with the actual method, however, it would be as well to review the underlying principles as otherwise the phenomenon produced may be confusing to the novice, especially when trying to use the unit for producing sound and vision simultaneously.

The intermediate frequency is produced by beating a locally generated frequency against the incoming frequency. The R.F. valve picks up and amplifies the incoming signal at its transmitted frequency. The local oscillator generates a separate frequency and the two are introduced to the mixer valve, which by a process of detection (it is known as the first detector) produces the signal at a frequency which is the difference between the two.

The setting of the oscillator frequency can provide two intermediate frequencies. Further, two separate oscillator frequencies can produce a single intermediate frequency.

Let us choose some easy figures for the purpose of comparison.

Supposing the signal is coming in at 50 Mc/s and our oscillator is working at 40 Mc/s; then we shall have two intermediate frequencies from which to choose. The first is the oscillator frequency plus the signal frequency ($40+50=90$ Mc/s) and the second is the difference between the oscillator frequency and the signal frequency ($50-40=10$ Mc/s). Thus we have two possible frequencies available at the output of the mixer, and we choose which one we desire simply by arranging a tuned circuit at the output of the oscillator to resonate to the desired frequency.

Supposing that we decide to have an I.F. of 10 Mc/s, then we can see that our oscillator can be tuned to 40 Mc/s as $50-40=10$. But note that the signal frequency is 50 Mc/s and we could use an oscillator at 60 Mc/s as $60-50$ also = 10.

Generally, it is desirable to have the oscillator frequency above the signal frequency, but the production of harmonics and possible interference decides the final arrangement.

So far so good. The snag arises when we are tuning an oscillator if we are not quite certain of its actual frequency and we wish to produce sound and vision.

In order to study the problem let us use some simple arithmetic.

Channel 1 transmits vision on 45 Mc/s and sound on 41.5 Mc/s. Supposing we are receiving these signals and have arranged for the vision intermediate frequency to be 13 Mc/s; then we could use a frequency of $45-13=32$ Mc/s for our oscillator as $45-32=13$.

Now, if the oscillator is working at 32 Mc/s, then the sound signal coming in at 41.5 Mc/s will be converted to a frequency of $41.5-32=9.5$ Mc/s.

Again so far so good. Our vision is at 13 Mc/s and sound 9.5 Mc/s which is quite common in commercial practice. Supposing we are dealing with an oscillator whose exact frequency is not known and that it will oscillate not only at 32 Mc/s but also at 58 Mc/s and all points in between. One setting of the oscillator will produce 13 Mc/s when the oscillator is working at 32 Mc/s, and the same signal will be produced at another setting of the oscillator when it is working at 58 Mc/s. We shall thus receive the vision signal at two settings of the oscillator.

It does not matter which setting is used for the vision, but if we are receiving

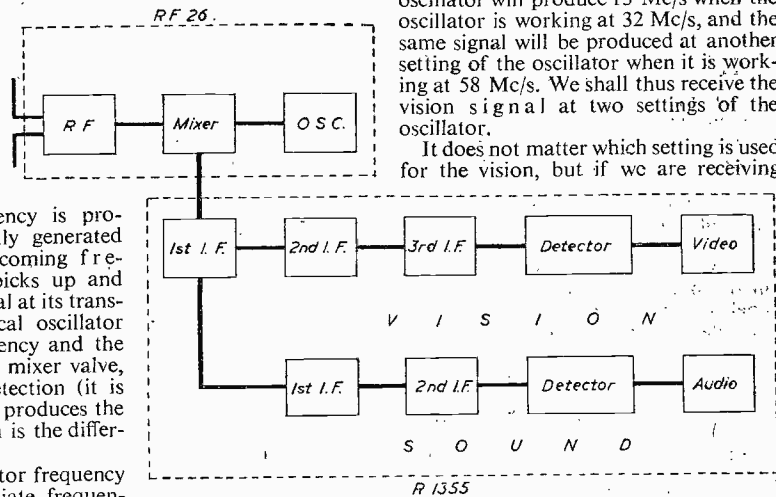


Fig. 2.—Block schematic of the R1355.

sound as well at 9.5 Mc/s we shall not receive sound at the second setting of the oscillator. This is because the oscillator working at 58 Mc/s will produce the sound signal at $58-41.5=16.5$ Mc/s, which is a long way from our intermediate frequency of 9.5 Mc/s.

The principle holds good for the sound, and it is possible for the corresponding conditions to arise: (a) First position of oscillator sound but no vision; (b) Second position of oscillator sound and vision; (c) Third position of oscillator vision no sound. All this without touching the I.F. coils!

The golden rule when altering the oscillator frequency and endeavouring to receive sound and vision is to tune in the vision first and adjust the oscillator to see if the sound is nearby. If this is not the case find the second position of the oscillator and try again.

Sound and Vision on R1355

The I.F. strip of the R1355 contains five stages. It is an easy matter to divide these stages, using two for sound and three for vision in areas of average

MUCH has been written in the past on the conversion of the R.F. units of the 1355 receiver, and the subject was clearly summarised by B. L. Morley in the February issue. Almost all conversion instructions presuppose that the R.F. units will be used as a superheterodyne either with a 1355 or other I.F. unit working at 7 Mc/s.

The R.F.24 and R.F.25 units can, however, be quite simply converted into straight sound units in far less time than it would take to make up a receiver from a design. There have been a number of straight television receivers described in the past and these usually employ an R.F. stage common to both sound and vision. The sound is taken off by a pick-up loop on the anode coil of the first valve and the sound section consists of two R.F. stages followed by detector and output stages. The R.F.24 may be converted into such a complete sound section with comparatively little alteration. The shallow chassis and the neat and accessible wiring of these units make the conversion particularly easy.

The following instructions relate to the R.F.24, but readers will have little difficulty in applying them to the R.F.25, which differs only in minor details.

Fig. 1 shows the original circuit using three SP61 (VR65) valves. The first is a radio-frequency amplifier, the second a frequency changer, and the third is the local oscillator. It is convenient for the conversion that the three valves are the same type. Fig. 2 shows the final circuit in which V1 remains an R.F. stage with only minor alterations. V2 is converted into a second R.F. stage again with few circuit changes. The oscillator stage, however, is completely scrapped and in its place is wired a germanium detector and the output valve V3.

The output stage V3 uses the original SP61 valve, and some readers may be surprised at this. However, provided a high-ratio output transformer is employed, sufficient volume with reasonable quality can be obtained, particularly if a 15-ohm loudspeaker is used. This arrangement is satisfactory with VCR97 and other small-screen receivers. The writer uses this sound section, in place of the one specified, in his Argus receiver. If greater sound output is desired, then a normal short grid-base L.F. pentode could be substituted after suitable adjustment of the bias resistor.

AN RF24 SOUND UNIT

USING AN EX-GOVERNMENT UNIT FOR A SOUND ONLY RECEIVER

By J. Stebbings

The First Stage

The first stage of the conversion is to remove from the top of the chassis the five-way switch, and all coils and trimmers. Having cleared the top of all wiring, remove the steel end panels and the longitudinal screen. This will leave only an H-shaped screen across the middle of the chassis. The coil formers, valve top-cap connectors, and three of the 30 pF trimmers should be saved for re-use.

The next stage is to re-wind the coils, leaving plenty of spare wire at the ends. The original unit was used on channel 2 with coils having the number of turns shown below. Figures are given, however, for other channels, and these should be used as a guide in arriving at the required inductance. The ceramic former is used for L1 and the two ebonite formers for L2 and L3.

L1 and T1 are mounted vertically close to V1. It

will be found impossible to drill a hole in the required position for fixing L1, so it should be mounted on a piece of strip steel which is secured at a convenient bolt hole. L2 and T2 are mounted horizontally on the centre part of the H-screen on the opposite side to the valve. L3 and T3 are mounted vertically next to V3, but before doing this it will be necessary to remove the tag strip underneath. This strip will not be required in any case.

That completes the mechanical work on top of the chassis. Unwanted components should now be removed from the three compartments underneath. In the middle V2 compartment remove the coil in the anode circuit, C4, and the screened output lead. In V3 compartment remove all components except the heater by-pass capacitor.

Re-wiring

Re-wiring may now be started with V1 stage. L1, T1, and the valve-top connector are all dealt with above the chassis and, below, the anode load resistor R3 should be changed to 6,800 ohms. L2 and T2 may now be wired connecting up with C3 below the chassis. The bias resistor (R11) of V2 should be changed to 100 ohms, a 10,000-ohm resistor connected in parallel with the screen feed R7, and a 6,800-ohm resistor wired as a new anode load. A 100 pF capacitor should be connected to the anode of V2 and a lead taken into the third compartment. L3 and T3 are wired above the chassis and a lead through to the underside will be necessary. It remains only to complete the detector and output wiring in the third compartment as shown in Fig. 2. In the original model the volume-control was mounted externally and connected by two screen leads. The loudspeaker was likewise external, and the primary of the output transformer was connected with twisted flex.

The power required is 240 v. at 30 mA and 6.3 v. at 2A. when the SP61 output valve is employed.

Results

The original is giving excellent results in an Argus receiver fed from a dipole at 25 miles from Holme Moss.

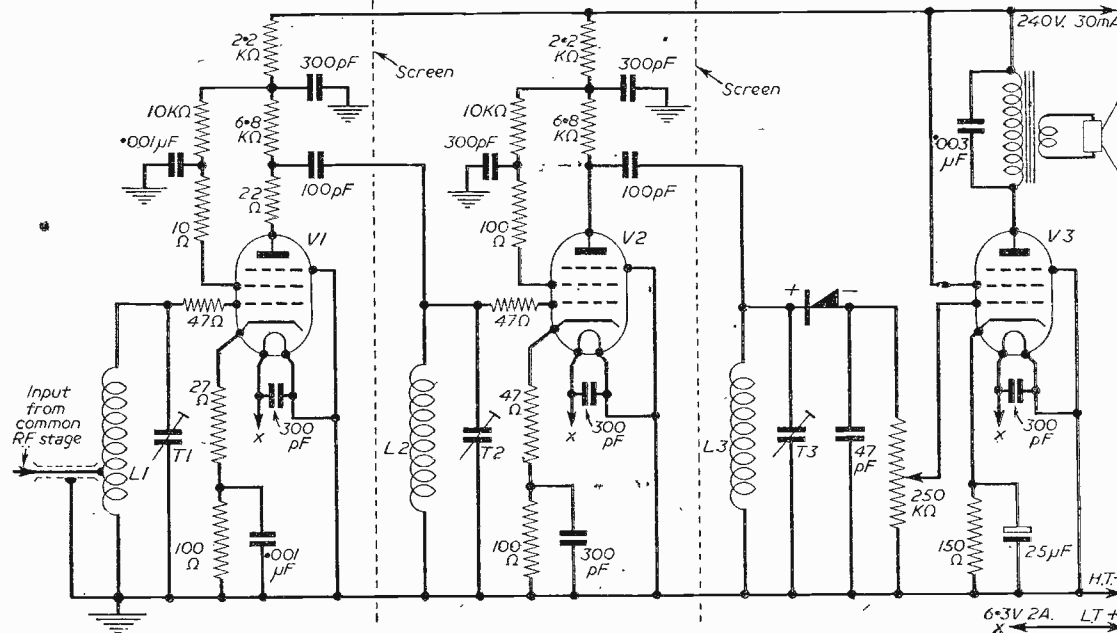


Fig. 2.—The sound unit modification.

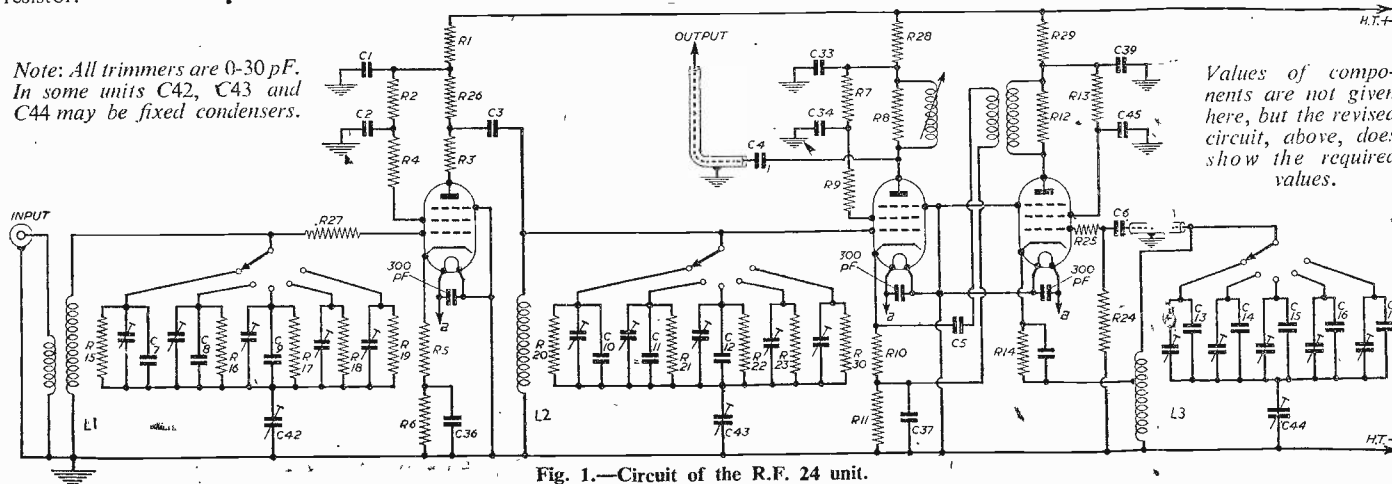


Fig. 1.—Circuit of the R.F. 24 unit.

Note: All trimmers are 0-30 pF. In some units C42, C43 and C44 may be fixed condensers.

Values of components are not given here, but the revised circuit, above, does show the required values.

COIL TURNS

Channel	L1	L1 tap	L2	L3
1	4½	1	4½	5½
2	4	1	4	5
3	3½	1	3½	4
4	3	1	3	3½
5	3	1	.3	3

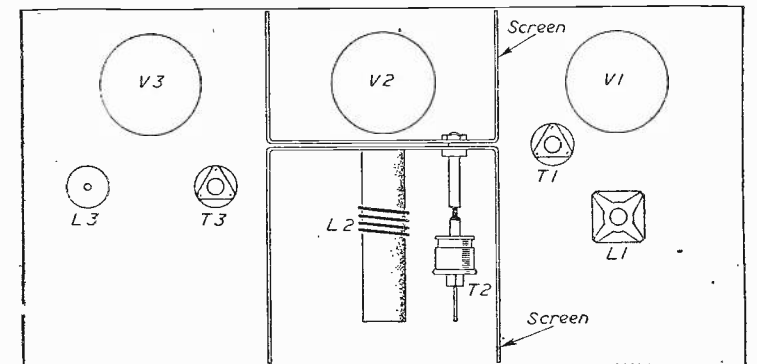


Fig. 3.—Layout showing coil positions.

The Miller Timebase

BASIC THEORY AND PRACTICAL OPERATION

By "Engineer"

THE Miller Timebase is, perhaps, the type which is most widely used in home-constructed receivers—particularly those employing electrostatic tubes. There is no doubt that it is capable of a fine performance with practically perfect linearity and these features, coupled with its simplicity and cheapness, have given it a deserved popularity.

Unfortunately not all constructors are getting the best out of this class of circuit and this is probably due to a lack of a full understanding of the basic principles, and of the effects of varying the values of the components, not only in the timebase itself, but also in the associated coupling networks. It is possible, for example, to have a Miller timebase which is itself performing perfectly yet which is producing a non-linear scan by reason of faulty choice of coupling components.

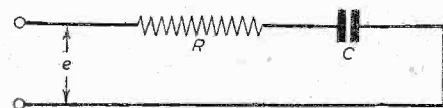


Fig. 1.—A charging condenser.

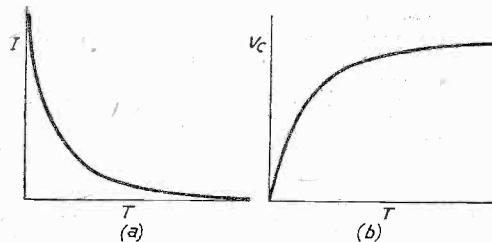


Fig. 2.—Current and voltage curves.

Time Constants

Most television timebases rely for their operation upon a condenser which is charging or discharging via a resistance. The object of the valve in the circuit in most cases is merely to trigger the circuit so that it operates at the correct time.

When a condenser is connected in series with a resistor across a voltage source, then the condenser will commence to charge up (Fig. 1). It will be appreciated that when the circuit is first connected, the full voltage "e" from the supply is directly across the condenser and a heavy current will flow from the supply to charge up the condenser.

However, as soon as the current starts to flow through the resistance "R" it will cause a potential difference across the resistance, the value of the P.D. depending upon the value of the resistance. The resistance therefore acts as a sort of limiter to the current, and instead of a sudden surge of current flowing to charge up the condenser, the current will flow in a more or less steady manner.

At the commencement of the charging period the current will be fairly heavy, but as the condenser

becomes charged the voltage across it becomes higher, and gradually becomes more equal to the voltage of the supply. The current flow will gradually tail off; the voltage drop across R decreases, the voltage across C becomes more nearly that of the supply, the current reduces and thereby reduces the voltage drop across R, and so on.

If the current through the resistance is plotted against time, it will be found to appear something like that shown in Fig. 2a. Similarly, the voltage built up across C will be as given in the curve in Fig. 2b.

In each case it will be seen that the curve has an almost straight portion and then dwindles off into a very shallow bend in a

non-linear fashion.

This type of curve is called an exponential curve.

Consider Fig. 2b. It will be noted that after the initial drive the curvature becomes less and less, the condenser voltage rising more and more slowly. In fact, it would take an infinite time for the condenser to become exactly the same as the potential of the supply. Most of the work of charging is done within the first few microseconds.

For practical purposes the circuit loses its usefulness when the voltage across the condenser reaches 0.632 of that of the supply.

The actual time taken for this to occur is termed the *Time Constant* of the network. Its value is given in seconds when the capacity of the condenser in Farads is multiplied by the resistance in ohms (this is also when microfarads are multiplied by megohms).

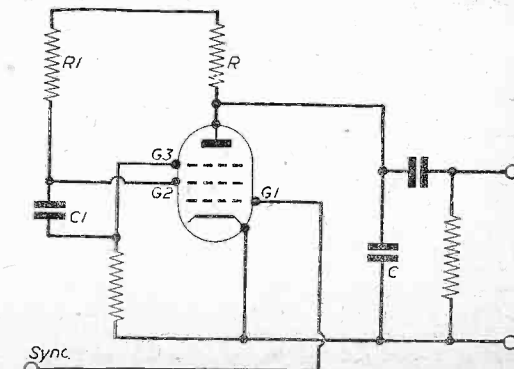


Fig. 4.—The basic transitron circuit.

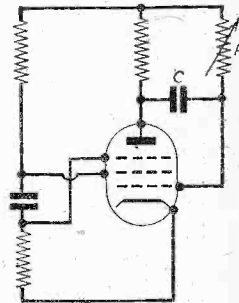


Fig. 3.—The basic Miller circuit.

signal strength. It is not proposed to give the details here as that has been given elsewhere, but what we are concerned with is the tuning.

Two methods can be employed. First, the vision can be arranged to be at 7.5 Mc/s and the sound at 11 Mc/s, or the vision at 11 Mc/s and the sound at 7.5 Mc/s, according to whether the oscillator frequency is above or below the signal frequency.

(Proof is: Oscillator at 52.5 Mc/s produces vision at $52.5 - 45 = 7.5$. Sound at $52.5 - 41.5 = 11$, or oscillator at 34 Mc/s gives vision at $45 - 34 = 11$ and sound at $41.5 - 34 = 7.5$.)

Whichever is used is mostly one of personal choice. All that is required to alter the existing 7.5 coils to 11 Mc/s is to insert brass cores in place of the iron-dust cores.

Tuning

Whichever is chosen, the difficulty remains of arriving at the correct oscillator frequency, as it is possible to make the oscillator tune to both 52.5 and 34 Mc/s.

Supposing vision is chosen to be 7.5 Mc/s and sound at 11 Mc/s, then the tuning should proceed in the following manner.

Tune in the RF26 for maximum vision "volume" and adjust all the ganging trimmers for maximum. Now adjust the small oscillator trimmer underneath the oscillator section until the vision strength is reduced by half. Note the dial readings and also the position of the oscillator. Tune in the sound on the dial. It doesn't matter what the dial position is, but make a note of it and go back to the vision. Once again off-tune the dial from the vision towards the channel used for sound (about 10 degrees) and turn the oscillator until sound is heard in the sound section.

Band III Test Transmissions

THE call sign allocated to the Band III experimental transmitter operated by "Belling-Lee" at Beulah Hill is G9AED. Through the helpful co-operation of the Independent Television Authority the transmitter and mast is located on the same piece of ground as their temporary mast and transmitter.

The test card is primarily intended for the investigation of ghost images and provides the following features.

(a) A wavy line in black and white, followed by white, grey and black. This line is wavy to differentiate from the vertical range marks. With ghost signals the wavy-line predominates, and positive or negative ghosts can be identified.

(b) Vertical lines numbered 1, 2, 3 and 4 indicating the additional path in miles that the ghost has travelled, i.e., if the reflecting object is situated directly behind the receiving aerial, in line with the transmitter, the distance of the reflecting object is exactly half the extra distance travelled by the delayed image.

(c) A circle to enable approxi-

This should be somewhere near the optimum oscillator position for the vision. All that is necessary now is to turn the trimmer towards the optimum vision position retuning the sound I.F. stages as the trimmer is altered until eventually maximum sound is obtained with the oscillator set at optimum vision position and the vision is received as well.

A slight adjustment of the tuning dial may be necessary, and the trimmer on the front panel should be set at maximum quality of picture.

Where the optimum oscillator position and maximum sound oscillator position do not come fairly close (as given in the paragraph before the last), then it is possible that the oscillator is working at the incorrect frequency and a second position where vision can be received should be found.

I.F.s Other Than 7.5 Mc/s

A popular I.F. for vision is 13 Mc/s with 9.5 for sound, and it should be possible to tune this in simply by altering the oscillator trimmer or adding an iron-dust core.

The unit should be trimmed, adopting the method given in the previous paragraph.


There are quite a few I.F. strips which operate at 12 Mc/s, and the RF26 can be used with these by modifying as for a 13 Mc/s strip.

It seems that with the advent of Band III an intermediate frequency in the region of 35 Mc/s will be used and to cater for this the oscillator can be tuned to 80 Mc/s.

To do this take one turn from the oscillator coil and, if this is found insufficient, then a brass core can be added, though this was not found necessary in the prototype.

At an oscillator frequency of 80 Mc/s the vision is 35 Mc/s and the sound is 38.8 Mc/s.

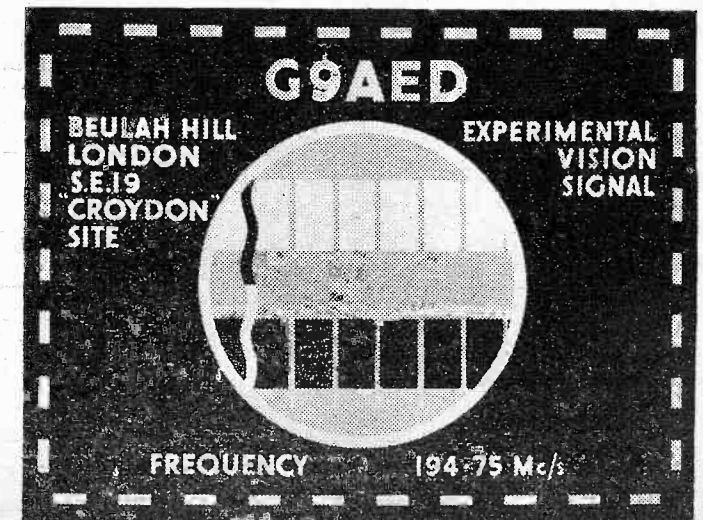mate linearity adjustments to be made to the receiver. (d) The black and white border to the card corresponds to the similar design on test card C and indicates the edge of the picture.



The Band III Test Card.

In TV work we are more concerned with very short periods of time of the order of millionths of a second (microseconds), and to simplify calculations we find the time constant in microseconds by multiplying capacity in picofarads (pF) by resistance in megohms.

The same sort of process takes place when a condenser is discharged through a resistance; there is, at first, a rapid fall in voltage which then gradually fades out more and more slowly.

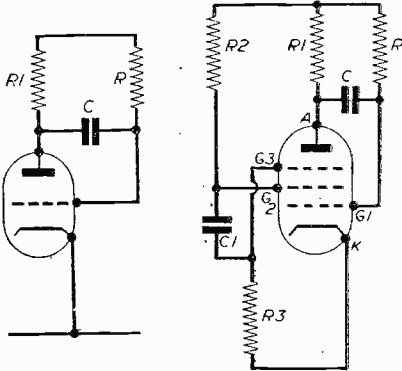


Fig. 5 (left).—The basic Miller integrator circuit. Fig. 6 (right).—The Miller integrator and transition circuit.

Some television timebases use a charging condenser while others (like the Miller) use a discharging condenser. In the first case a condenser is steadily charged to a certain point and then rapidly discharged, while in the second case the fully charged condenser is discharged to a certain point and then rapidly recharged. The result is the production of the well-known saw-tooth waveform necessary in the scanning process.

The Miller Circuit

Fig. 3 shows the basic Miller circuit and the condenser C with its resistance R is used in a discharging circuit brought about by operation of the valve.

The Miller circuit is actually a combination of two circuits—the transitron and the integrator. Its full title is the Miller Integrator and Transitron Circuit.

In Fig. 4 will be found the basic transitron circuit; its operation follows.

Assume that C is charged and the suppressor grid G3 is sufficiently negative to cut off the anode current: the screened grid G2 is drawing full current and is, therefore, at its most negative.

When a positive sync pulse is applied to the grid anode current will commence to flow and the anode will draw current away from G2. G2 will, therefore, start to move in the positive direction, and the positive movement is communicated to G3 via C1, and still more anode current flows. The increased current causes an increase in the voltage drop across R and the anode will move in a negative direction; C will therefore commence to discharge.

A point is soon reached where the anode potential is too low to maintain anode current, and the current from the cathode will therefore start to move more and more to the screen. There will, therefore, be an increasing voltage drop across R1 and the screen will move in the negative direction. The negative movement is communicated to the suppressor which

therefore cuts off more anode current. The effect is cumulative and anode current is rapidly cut off. Lack of anode current via R causes the potential drop across this resistor to decrease and hence C will charge from the increasing positive potential appearing at the anode. C is therefore rapidly charged up and the process recommenced.

The grid of the valve is used only for the application of the sync pulse.

The output of the circuit is not strictly linear and can be vastly improved by inclusion of the Miller integrator.

The Miller Integrator

The basic circuit is shown in Fig. 5. Assume that C is fully charged and the valve is drawing current. Because of the voltage drop across R1 the anode is negative with respect to HT+. This negative voltage is communicated to the grid via C.

C discharges via R1 and R and, hence, as its voltage falls the grid becomes less negative and the anode draws more current. The falling voltage across C1 is almost equalled by the steadily increasing potential difference across R1. The change of voltage at the anode is much greater than that across the grid due to the voltage magnification of the valve. In fact the voltage change at the anode is the integral of the change of grid voltage and the miller effect between grid and anode gives rise to the term miller integrator for this class of circuit.

The interaction between anode and grid means that the discharge of C is very linear.

The Complete Circuit

The complete circuit is shown in Fig. 6. Starting with C fully charged, G3 is at zero potential and G2 at its most positive. R1 and R2 are about the same value but the voltage drop across R1 is greater than that across R2 as the anode current is greater than the screen current.

C commences to discharge and the voltage across it

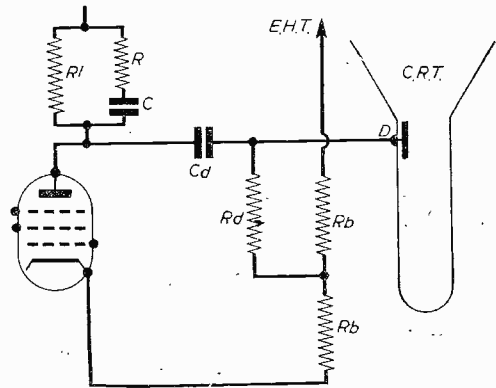


Fig. 7.—The coupling circuit.

will fall until a point is reached where the anode voltage is too low to hold the main stream of electrons from the cathode. They are therefore diverted to the screen and the consequent increase of current through R2 causes G2 to move in the negative direction; the negative movement is communicated to the suppressor grid G3 via C1 which reduces the current flow to the anode still further and the anode is rapidly cut off. At this point C is almost fully discharged.

As no current is being drawn via R1 the potential at the anode will rise and the rise in the positive direction is communicated to the grid. Another way of looking at it is that as the anode moves more positive, the negative on the grid communicated via the condenser is reduced and the grid becomes very positive (it is connected to the positive line via R). The result is that C is very rapidly charged up and the current is thereby drawn from the cathode and diverted away from the screen; G2 will therefore move in the positive direction and the movement communicated to G2 via C1 returns G3 to zero.

When C is fully charged the grid becomes negative, anode current commences to flow, and the process is repeated.

There are two important points to note. First, although the grid is returned to H.T. positive, grid current does not flow continually because of the charge on C. If C were removed the grid would draw a heavy current. The second point is that the discharge of C takes place via R and R1. The time taken for the discharge to take place depends upon the value of the condenser C and the value of R and R1 which form the discharge path. R is usually made variable so that the timing of the circuit can be accurately adjusted.

The synchronising pulses are usually applied to the suppressor grid so that the anode is cut off and the charging of C initiated. C is charged, of course, during the flyback period.

The negative charge accumulated on the suppressor grid via C1 must be rapidly extinguished during the flyback period or the flyback will be delayed. The charge on C1 leaks away via R2 and R3; the amount of the charge will depend upon the capacity of the condenser, and the discharge period will depend upon the total capacity of C1 plus the resistance of the discharge path.

The run-down of C takes place in an extremely linear manner due to the inherent properties of the circuit. The majority of the causes for non-linearity lie in the associated coupling networks; in this particular circuit about the only real causes of non-linearity are a faulty valve, leaky condensers (a common cause in ex-Government equipment and particularly noticeable in the frame circuit), or bad choice of components in the screen circuit.

In order to obtain the very best out of the circuit R3 and R2 can be made variable.

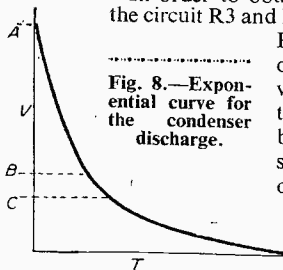


Fig. 8.—Exponential curve for the condenser discharge.

R will, of course, consist of a fixed resistor plus variable resistor to enable the range of the sweep to be varied, the fixed resistor limiting the range of the variation and thereby avoiding making the grid a direct connection to H.T.+

Causes of Non-linearity

The most likely cause of non-linearity is in the coupling network, provided the values of the Miller circuit itself are as specified.

A typical example of the coupling network is shown in Fig. 7. The output from the oscillator is taken via Cd to the deflector plate "D." The latter is biased from the E.H.T. network and the associated resistor arrangement is shown as Rd (the decoupler) and Rb the bleeder.

It will be seen that Cd plus Rd, Rb form a condenser and resistance network and will, therefore, have a certain time-constant. The time-constant of this section must be rather larger than that of the

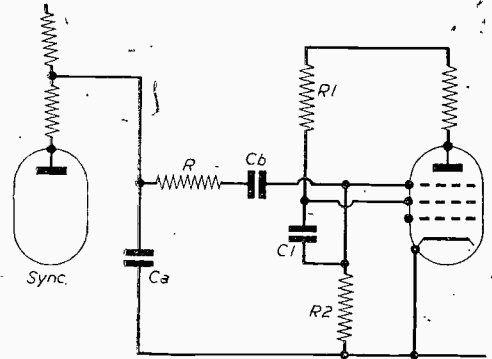


Fig. 9.—The sync coupling circuit.

valve circuit. If the condenser Cd is too small, for example, then the resultant waveform at the deflector plate will be distorted.

In Fig. 8 we show the exponential curve for the condenser discharge. It will be observed that from A to B the discharge is linear, but from B to C the discharge becomes non-linear the degree of non-linearity rapidly increasing.

Supposing C in Fig. 7 is too small, then the condenser will barely hold the charge, and the discharging of it will take place right through to the curved portion. On one side we could have a linear waveform but on the other the waveform would be non-linear.

For optimum results the time constant of Cd, Rd, Rb should be 50 times that of the duration of the saw-tooth. This figure is generally the case in line circuits but often is not attained in the frame circuit. For the frame typical values are 0.5 μ F and 2 M Ω .


Another possible cause of non-linearity closely associated with the above is the method of feeding the output of the oscillator into a low-impedance circuit. Ideally, the output should be fed into a circuit of infinite impedance. If the circuit is of low impedance, a load will be placed upon the oscillator which will materially affect the linearity of the scan.

When the oscillator output is fed directly to the C.R.T. network, high-impedance circuits are usually attained, but when fed into an amplifier it is possible, by error, to have the input circuit at a rather lower impedance than is desirable.


A point which is quite often overlooked is the input from the sync separator. The usual method is to integrate the pulses in a standard integrating network, and to inject the integrated wave-form into the suppressor circuit. The circuit must be carefully designed or the R2, R3, C1 characteristics may be modified, with consequent non-linearity.

When investigating the cause of non-linearity the coupling circuit from the sync must not be forgotten. Fig. 9 shows a typical coupling network for a frame oscillator, R, Ca and Cb forming part of the differentiator. It will be seen that these components are practically in parallel with R2, which is in the flyback circuit. Incorrect values, leaky condensers or high value resistances will obviously modify the operation of the oscillator.

(To be continued.)

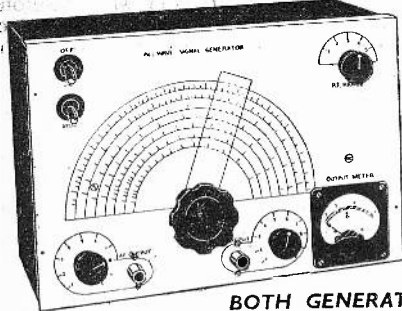

Used A.C. mains 5 valve, 3 wave-band superhet chassis, size 11 1/2 x 8 1/2 x 3 1/2 in., complete with 3 wave-band scale size 10 1/2 x 5 1/2 in., pair of 465 Kc/s IF's, tuning condenser, mains transformer, volume control with switch, tone control 3 wave-band coil pack (this is a completely detachable coil-pack on separate small chassis) various small condensers and resistors and biasing condensers, 19/6. Post & packing 3/6. As above two-waveband, 15/- Post & packing, 3/6.

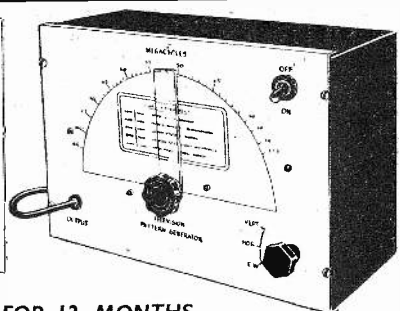

BOTH GENERATORS GUARANTEED FOR 12 MONTHS

COMPLETELY BUILT SIGNAL GENERATOR

Coverage 120 Kc/s-320 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8.5 Mc/s-25 Mc/s, 17 Mc/s-50 Mc/s, 25.5 Mc/s-75 Mc/s. Metal case 10 x 8 1/2 x 4 1/2 in. Size of scale 8 1/2 x 3 1/2 in., 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated, R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%. £4/19/6, or 34/- deposit and 3 monthly payments 25/- P. & P. 4/- extra.

PATTERN GENERATOR

40-70 Mc/s direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits and vision channel band width. Silver plated coils, black crackle finished case 10 x 8 1/2 x 4 1/2 in. and white front panel. A.C. mains 200/250 volts. This instrument will align any T.V. receiver, accuracy plus or minus 1%. Cash price £3/19/6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/- extra.

USED MULLARD TUBES GUARANTEED 3 MONTHS
with heater cathode short.

- M.W. 31/74 12in. bent gun ... £3.17.6. P. & P. 7/6 extra
 - M.W. 31/16 9in. bent gun ... £3.17.6. P. & P. 7/6 extra
 - M.W. 32/16 9in. bent gun ... £1.17.6. P. & P. 7/6 extra
- Any of the above complete with Line E.H.T. trans. 9 KV. Ferrocart core. Line and width control scan coils and frame O/P trans. 35/- extra.

Used Mazda C.R.M. 123 Cathode heater short aluminiumised. Complete with rubber mask, Elac P.M. focus unit, scan coils, low line, low frame and frame O/P trans. 45.10.0. P. & P. 7/6.

Used 9in. TUBE 22/14C with ion burn, 17/6. Post paid.
Used Mullard 12in. with ion burn, 50/- P. & P. 7/6.

Line and E.H.T. Transformer, 9KVA using Ferrocart core complete with built-in line and width control. Mounted on Ali-chassis. Overall size 4 1/2 in. x 1 1/2 in., EY51 Rec. winding. 27/6. P. & P. 2/6.

Scan Coils, low line, low frame, complete with frame O/P trans. to match above line and E.H.T., 27/6. P. & P. 2/6.

Heater Transformer, Pri: 230-250 v. 6v. 1 1/2 amp., 6/-; 2 v. 2 1/2 amp., 5/- P. & P. each 1/-.

T.V. Converter for the new commercial stations complete with 2 valves. Frequency can be set to any channel within the 186-196 Mc/s band. I.F.: will work into any existing T.V. receiver designed to work between 42-68 Mc/s. Sensitivity 10 MuV with any normal T.V. set. Input: arranged for 300 ohm feeder. 80 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF90 as local oscillator. ECC81 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier 10 db. Required power supply of 200 v. D.C. at 25 mA., 6.3 v. A.C. at 0.6 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2-10.0. P. & P. 2/6.

Line and E.H.T. Transformer, 9KVA using Ferrocart core. EY51 heater winding, complete with scan coils and frame output transformer and line and width control. £2-5.0. P. & P. 3/-.

As above but complete with line and frame blocking transformers, 5 henry 250 mA. choke, 100 mfd. and 150 mfd. 350 wkg., 380 mA. A.C. ripple. £2-19.6. P. & P. 3/-.

Standard wave-change Switches, 4-pole 3-way, 1/9; 5-pole 3-way, 1/9; 3-pole, 3-way, 1/9; 9-pole 3-way, 3/6; Miniature type, long spindle 3-pole 4-way, 4-pole 3-way and 4-pole 2-way, 2/6 each. 2-pole 11-way twin wafer, 5/-; 1-pole 12-way single wafer, 5/- P. & P. 3/4.

T.V. Filter in lightly tinted perspex, size 1 3/4 x 1 1/2 x 3 1/16 in., 4/6.

USED metal rectifier, 250 v. 150 mA., 6/6.

R. and A.T.V. energised 6in. Speaker with O/P Trans., field coil 175 ohms. Requires minimum 150 mA. to energise maximum current 250 mA., 9/6. P. & P. 2/6.

R. and A.M.E. 6in. with O/P Trans., 440 ohms field, 10/6 plus 2/6 P. & P.

Combined 12in. Mask and Escutcheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet. 12/6. As above for 4 1/2 in. tube, 17/6.

Frame Oscillator Blocking Trans., 4/6.
Line Oscillator Blocking Trans., 4/6.

Smoothing Choke, 250 mA., 5 henry, 8/6; 250 mA., 10 henry, 10/6; 250 mA., 8 henry, 8/6.

P.M. Focus Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15/- P.M. Focus Unit for Mazda 12in., without Vernier adjustment, 15/- Wide Angle P.M. Focus Unit, Vernier adj., state tube, 25/-.

Energised Focus Coil, low resistance mounting bracket, 17/6.
Ion Traps for Mullard or English Electric tubes, 5/- Post paid.
T.V. Coils, moulded former, iron core, wound for rewinding purposes only. Ali-can 1 1/2 in., 1/- each; 2 iron-core Ali-can, 2 1/2 in. x 1 1/2 in., 1/6 each.
Dubilier .001 10kV. working, 3/6.
Cydion 5 channel T.V. tuner, 12/6. Post paid.

MAINS TRANSFORMERS

- Primary, 200-250 v. P. & P. 2/-.
- 300-0-300, 100 mA., 6 v. 3 amp., 5 v. 2 amp., 22/6.
- Drop thro' 350-0-350 v. 70 mA., 6 v. 2 amp., 5 v. 2 amp., 12/6.
- Drop thro' 250-0-250 v. 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.
- 280-0-280, drop through, 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.
- 250-0-250 80 mA., 6 v. 4 amp., 14/-.
- Drop thro' 270-0-270, 80 mA., 6 v. 3 amp., 4 v. 1.5 amp., 13/6.
- Drop thro' 270-0-270 60 mA., 6 v. 3 amp., 11/6.
- 250 v. 350 mA., 6.3 v. 4 a., twice 2 v. 2 a., 19/6.
- Auto Trans. Input 200/250, H.T. 500 v., 250 mA., 6 v. 4 a., twice 2 v. 2 a., 19/6.
- 250-0-250, 60 mA., 6.3 v. 1.5 a., 0.5-6.3 v. 1.5 a., 10/6
- Auto Trans. Input 200/250, H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 1 1/2 amp., 5 v. 3 amp., 25/- P. & P. 3/-.
- Heater Transformer, Pri. 230/250v. 6v. 1 1/2 amp., 6/-; 2v. 2 1/2 amp., 5/- Pri. 200/250. Secondary 9 v. 3.5 amp., 6.3 v. 3 amp., 12/6.
- Pri. 230 v. Sec. 500-0-500 and 500-0-500 250 mA., both windings. 4 v. 3 amp., 4 v. 3 amp., 39/6. P. & P. 5/-.

Mains Transformer, fully impregnated, input 210, 220, 230 and 240. Sec. 600-0-600, 275 mA., and 250 v. at 30 mA., complete with separate heater transformer, Input 210, 220, 230, 240. Sec. 6.3 v. 2 amp. three times, 0, 4, 6.3 v. at 3 amp. and 5 v. 3 amp., 45/- P. & P. 5/-.

Mains Transformer fully impregnated. Input 210, 220, 230, 240. Sec. 350-0-350 100 mA, with separate heater transformer. Pri. 210, 220, 230, 240. Sec. 6.3 v. 2 amp., 6.3 v. 3 amp., 4 v. 6 amp., and 5 v. 2 amp., 30/- P. & P. 5/-.

Mains Transformers, chassis, mounting, feet and voltage panel. Primaries 230/250.
350-0-350 75 mA., 6.3 v. 8 a. tap 4 v. 6.3 v. 1 a., 13/6.
500-0-500 125 mA., 4 v. C.T. 4 a., 4 v. C.T. 4 a., 4 v. C.T. 2.5 a., 27/6.
500-0-500 250 mA., 4 v. C.T. 5 a., 4 v. C.T. 5 a., 4 v. C.T. 4 a., 39/6.

Valve Holders, moulded octal Mazda and loctal, 7d. each	8 mfd., 500v. wkg., wire ends	2/6
Paxolin, octal Mazda and loctal, 4d. each	8 mfd., 350 v. wkg., tag ends	1/6
B7G, B8A and B9A, 7d. each	50 mfd., 25 v. wkg., wire ends	1/9
B7G moulded with screening can, 1/6 each	100 mfd., 350 v. wkg. ...	4/-
32 mfd., 350 wkg. ...	100 mfd., 450 v. wkg., 280 mA. A.C. ripple ...	3/11
16 x 24, 350 wkg. ...	150 mfd., 350 v. wkg., 280 mA. A.C. ripple ...	4/6
4 mfd., 200 wkg. ...	100 x 200 mfd., 350 wkg. ...	9/6
40 mfd., 400 wkg. ...	16 x 16 mfd., 350 wkg. ...	3/3
16 x 8 mfd., 500 wkg. ...	50 mfd., 180 wkg. ...	1/9
10 x 16 mfd., 500 wkg. ...	35 mfd., 220 wkg. ...	1/6
16 x 16 mfd., 450 wkg. ...	8 mfd., 150 wkg. ...	1/6
32 x 32 mfd., 350 wkg. ...	60 x 100 mfd., 280 wkg. ...	7/6
32 x 32 mfd., 350 wkg., and 25 mfd., 25 wkg. ...	50 mfd., 12 wkg. ...	11d.
25 mfd., 25 wkg. ...	32 x 32 mfd. min. 275 wkg. ...	4/-
250 mfd., 12 v. wkg. ...	50 mfd., 50 wkg. ...	1/9
16 mfd., 500 wkg., wire ends	Miniature wire ends	3/3
4 and 001. ea. ...	100 pf., 500 pf. ...	7d.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

R. AND T.V. COMPONENTS (ACTON) LTD. 23 HIGH STREET, ACTON, W.3
Telephone: ACOrn 5901
(Opposite Granada Cinema)

(LATE D. COHEN)

RADIO SUPPLY CO. (LEEDS) LTD.

Post Terms C.V.O. or C.O.D. NO C.O.D. under £1. Postage 1/- extra under 10/- 1/6 extra under £1. 2/- under £3. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d.; Trade List 6d.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s Screened.

TOP SHROUDED, DROP THROUGH

250-0-250 v 70 ma, 6.3 v 2.5 a ...	13/9
250-0-250 v 70 ma, 6.3 v 2 a, 5 v 2 a ...	16/9
350-0-350 v 60 ma, 6.3 v 2 a, 5 v 2 a ...	18/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ...	23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ...	23/9
350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ...	23/9

FULLY SHROUDED UPRIGHT

250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a	17/6
Midget type, 2 1/2-3 in. ...	17/6
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ...	26/9
250-0-250 v 100 ma, 6.3 v 6 a, 5 v 3 a, for R1335 Conversion ...	31/9
300-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ...	27/9
350-0-350 v 70 ma, 6.3 v 2 a, 5 v 2 a ...	19/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ...	27/9
350-0-350 v 150 ma, 6.3 v 4 a, 0.4-5 v 3 a	31/6
425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a ...	49/9
450-0-450 v 250 ma, 6.3 v 6 a, 6.3 v 6 a, 5 v 3 a ...	69/9

FILAMENT TRANSFORMERS

All with 200-250 v 50 c/s Primaries: 6.3 v 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0.4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/9.

CHARGER TRANSFORMERS

200-250 v 0.4-15 v 1 a, 11/9; 0.4-15 v 3 a, 16/9; 0.9-15 v 4 a, 19/9; 0.9-15 v 6 a, 22/9.

OUTPUT TRANSFORMERS

Standard Pentode 5,000 to 3 ohms ... 4/9
Standard Pentode 7/8,000 to 3 ohms 4/9
Battery Pentode 10,000 to 3 ohms 4/9
Small Pentode 5,000 to 3 ohms ... 3/9

E.H.T. TRANSFORMERS 200-230-250 v

2,500 v 5 ma, 2.0-2 v 1.1 a, 2.0-2 v 1.1 a for VCR97, VCR517 ... 37/6

ELECTROLYTICS.—Tubular 8 mfd 450 v,

1/9; 16 mfd 450 v, 2/11; Can 8-8 mfd 450 v, 3/11; 8-16 mfd 450 v, 3/11; 16-16 mfd 450 v, 4/11; 32 mfd 350 v, 2/11; 32 mfd 450 v, 4/11; 32-32 mfd 350 v, 5/6; 32-32 mfd 450 v, 5/11; 64 mfd 450 v, 3/9; 60-100 mfd 350 v, 7/6; 100 mfd 450 v, 4/9.

SMOOTHING CHOKES

250 ma 3 h 100 ohms ...	11/9
100 ma 10 h 200 ohms Potted ...	8/9
80 ma 10 h 350 ohms ...	5/6
60 ma 10 h 450 ohms ...	4/11

CO-AXIAL CABLE 1/4 in.

75 ohms 14/36 ...	7d yd
Twln-Screened Feeder ...	10d yd

TV. PREAMPLIFIER.—For Fringe Areas. Brand New. Complete with 6F13 valve. Only 22/6.

SELENIUM METAL RECTIFIERS

RM4 250 v 250 ma, 11/9; G.E.C. 300 v 250 ma, 12/9; 120 v 40 ma 3/9; 6/12 v 1 a F.W., 5/9; 240 v 50 ma, 6/9; 6/12 v 2 a F.W., 9/9; 250 v 80 ma, 7/9; 250 v 150 ma, 11/9.

BATTERY SET CONVERTER KIT

All parts for converting any type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplied 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 v at 0.4 a to 1 a. Price including circuit 48/9. Or ready for use 8/9 extra.

ALL DRY RECEIVER BATTERY SUPERSEDER KIT.—All parts for the construction of a unit (metal case 5.4-4 1/2 in.) to supply 4-valve Battery receivers requiring 90 v 10 ma, and 1.5 v 250 ma. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 35/9. Or assembled and tested at 42/6.

SILVER MICA CONDENSERS. Most values 5d. ea. 3/9 doz. one type.

VOL. CONTROLS (standard long spindles). All values, less switch, 2/9; with S.P. switch, 3/9; with D.P. switch, 4/6.

SPECIAL OFFERS.—Midget Mains Trans. Primary 220/240 v 50 c/s. Secs. 220-0-220 v 70 ma, 6.3 v 3 a, 11/9. Output Trans. 5,000 to 3 ohms, 2/9. Goodman's P.M. speaker 3/4 in. Ex-equip. with matching trans. for battery pentode, 12/9.

Dept. N., 32, THE GALLS, LEEDS, 2.

EX-GOVT. SMOOTHING CHOKES.—

50 ma 5-10 h ...	2/9
100 ma 10 h 500 ohms Tropicalised ...	6/9
150 ma 10 h 150 ohms ...	11/9
250 ma 10 h 150 ohms ...	14/9
250 ma 10 h 50 ohms ...	14/9

EX-GOVT. MAINS TRANSFORMERS

Primaries 230/250 v 50 c/s 4 v 2.5, 4/9; 4 v 6 a (High Ins.), 7/9; 48 v 1 a, 9/9; 400 v C.T. 150 ma 4 v 6 a, 6.3 v 6 a, 6.3 v 0.6 a, 4 v 8 a, 4 v 3 a, 5 v 3 a, 4 v 3 a, 5 v 2 a, 22/9; 300-0-300 v 120 ma 4 v 1 a, 17/6; 610-0-610 v 150 ma, 300-0-300 v 150 ma, 1220 v 350 ma, 29/6; 460 v 200 ma, 6.3 v 5 a, 29/6; 460 v 200 ma, 6.3 v 5 a, 29/6. Add 5/- carr. to types at 29/6.

EX-GOVT. E.H.T. SMOOTHERS

.02 mfd 4,000 v, L11; .05 mfd 4,000 v (Block), 4/9; .5 mfd 3,500 v 3/6.
R.F. UNIT TYPE 26.—Brand new. Cartoned, 39/6, plus carr., 2/6.

BATTERY CHARGER KITS.—Consisting of attractive Green Crackle Case, Transformer, F.W. Rectifier, Fuse, Fuseholder, Tag strip, Grommets, and Circuit.

For mains input 200-230-250 v 50 c/s 6.2 a, 25/9; 6 v or 12 v, 2 a, 31/6; 6 v or 12 v, 4 a, 49/9; Any type assembled and tested for 6/9 extra.

R.S.C. 6v or 12v BATTERY CHARGER

For normal A.C. mains input 200-230-250 v, 50 c/s. Selector panel for 6 v or 12 v charging. Variable charge rate of up to 4 AMPS. Fused, and with 5 amp meter. Well ventilated metal case with attractive crackle finish. Guaranteed for 12 months, 69/6. Carr. 2/6.

BATTERY CHARGERS.—For mains 200-250 v 50 c/s. Outputs for charging 6 v or 12 v at 1 amp. In strong metal case. Only 19/9. Above can also be used for electric train power supply.



NEW!

EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY

Specially prepared sets of television parts (which you receive upon enrolment) with which we teach you, in your own home, the working of circuits and bring you easily to the point when you can construct and service a television set. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business—this Practical Course is intended for YOU—and may be yours at very moderate cost.

EASY TERMS FROM 15/- A MONTH

A tutor is available to give individual help and guidance throughout the Course.



EXPERIMENTAL OUTFITS:

TELEVISION—Instruction and equipment for building a Television Receiver.

BEGINNER'S RADIO OUTFITS—A course in basic principles.

ADVANCED RADIO OUTFITS—Instruction and equipment from which you build a Radio Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S. W. Radio, Languages.

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation


POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:
To: E.M.I. INSTITUTES, Dept. 138X, Grove Park Road, London, W.4.

NAME.....

ADDRESS.....

SUBJECT(S)..... MAY

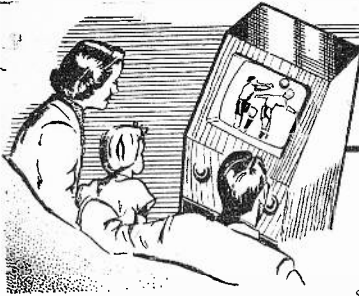

UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

PUBLIC DEMAND

NEWSPAPER critics are not easy to please, whether they specialise in plays, films, books or television, and the growing importance of television can be measured by the steady increase of space allocated to TV critics.

Some newspapers now devote even more columns to television critiques, news and gossip than they do for films; in fact, a Sunday newspaper recently gave 28in. of space to TV matters and only 10in. to films. This indicates current public demand. There is, of course, the support of the publicity world which must also be taken into account—large amounts of advertising space are taken in newspapers, by radio, television and film products. However, this commercial consideration in no way affects the opinions of the professional critics concerned. It merely ensures that there is adequate space for their writings.

BLASÉ CRITICS

IT is only natural that the TV critics tend to become a trifle blasé. They, like their colleagues in the other fields of entertainment and art, are apt to become a little satiated with their own particular medium. It must be somewhat discouraging for the hard-worked BBC producers to read a succession of "panning" notices about their efforts—but, all the same, they do read them avidly and with benefit. I have noted lately that the critics are realising more fully the magnitude of the task of the BBC play-producers whose greatest handicap is the shortage of suitable material and the time to put it into the best possible shape.

SCRIPT PREPARATION

CONSIDER what happens before a stage play or a film is put into production. The subject is selected from large numbers of

so-called original scripts, from books that have already been published or seen in an alternative medium. Quite a few good films and plays have been adapted from material first seen on TV, "Ten Minute Alibi" being an excellent example. Public appeal, suitability of the material for contract stars, topicality, breadth (or lack of breadth) of background, all influence the decision of the producer as to whether he should venture to the next step—the preparation of a treatment or master-scene script which sets out the main highlights of the story and characterisation in the manner required. For a stage play, the story must fall naturally into the theatrical convention of time and place which limits the number of sets, for obvious reasons. For a film, the canvas is much broader and the emphasis is on various settings, including exteriors, together with plenty of movement rather than on dialogue. A television play comes somewhere in between these two extremes.

From the first "treatment" or master scene scenario, there is progress through various draft scripts until the stage or shooting script has been finalised. This takes time. Amendments are made for various reasons, principally to mould the characters in the story to fit specific actors or actresses. Then, at last, the preparations of set design, wardrobe, special effects, music and casting are put in hand. This complex procedure sometimes takes weeks or months in the case of plays and films but has to be compressed into the shortest possible time for TV plays. All the time the preparations are going on, the production cost is mounting and the BBC is strictly limited in its budgets. The theatrical repertory companies' ideal of a single stage setting and five or six characters would be convenient and inexpensive but would be very dreary as a staple diet on TV. Altogether, considering these fac-

tors, I think that the boys at Lime Grove are doing a first-class job. Their chief difficulty lies in the availability of suitable material in large enough quantities.

"FANTASTIC SUMMER"

HAVING thus praised the back-room drama boys of Lime Grove as a whole, I will now refer to one of them, Barry Learoyd, in particular.

Mr. Learoyd has given us many smooth and gripping TV plays in his capacity of producer, but for "Fantastic Summer" he was also the TV playwright, founding his script upon the novel of that name by Dorothy Macardle. It was the story of a widow who had strange glimpses of the future and, forewarned of disaster, tried to prevent the betrothal of her daughter to a man she imagines will be her daughter's murderer. Fay Compton gave a beautifully sensitive performance and made the most of dialogue and material which was very ordinary indeed. Nan Wilde was attractive and convincing in the equally gloomy part of the daughter, while that fine old actor, Ian Fleming, brought a little brightness and authority to the play as Dr. Franks, the psychiatrist.

Maybe I am prejudiced against plays which feature psychiatrists, but their professional jargon which figures in so many modern plays has now become cliché. It seems to me that very brilliant dialogue is now required to put this kind of story over and Mr. Learoyd is less good as a dialogue writer than he is as producer.

THE COMEDIANS

IT is the comedians who have been registering the best with viewers lately. "Before Your Very Eyes" has become very popular with the masses and once more demonstrates the complete mastery that fine little comedian Arthur Askey has over the technique of television. The dumb

blonde of the show, Sabrina, was an attractive gimmick and stooge, in spite of her extraordinary Robey-ish eyebrow make-up, and the sketches were amusing and well-written. Another comedian who has scored with viewers is Jimmy James, and the Benny Hill shows—a little uneven at first—have become some of the slickest and most hilarious productions on the air. Peter Ustinov and Peter Jones, whose specialised type of humour has scored heavily with some, but not all, sections of the sound radio listeners, make a much broader appeal on TV.

BRITISH KINEMATOGRAPH SOCIETY'S RECOMMENDATIONS

THE B.K.S. has once more been doing good work in the television field, especially since the special Television Division has been established under the chairmanship of Mr. L. C. Jesty.

A special Television Standards Committee has been considering recommendations for producers making films for television, with particular references to standards for the use of magnetic sound and the density and contrast factor of prints of the picture side: 35 mm. film is still favoured on this side of the Atlantic. In the U.S.A. 16 mm. film is widely used, but not exclusively. A lecture on making films for television was given by Harold Huth, producer

at the Douglas Fairbanks Studio at Elstree, where upwards of two hundred features for American TV have been made. Apart from explaining various technical problems, Mr. Huth outlined the many restrictions on types of material acceptable to the American viewer which also conformed to the code laid down by the authorities. Unlike the British viewers, the Americans, especially those living in the mid-West, were allergic to dialects and strong accents, especially to Cockney, "Kensington" or "Oxford" English and to certain Scottish accents. Strangely enough, Lancashire, Yorkshire, Irish or Somerset accents, if moderate, were accepted. The English drawing-room type comedy did not appeal at all, but stories set in familiar London tourist spots, such as Trafalgar Square, the Tower of London or Limehouse, and those about Scotland Yard, scored heavily. As for characters—the London "Bobby" is extremely popular via TV in all parts of the States.

"WHAT'S MY LINE?"

"WHAT'S MY LINE?" has had a long run, but the fact that it is being "rested" for a few months before its reappearance in commercial TV, will not be regretted. "Find The Link" is an entertaining parlour game which has now settled into fine

shape, though it suffered a severe loss in the death of the brilliant young chairman, Peter Martyn. That veteran young man of TV interviewers, Leslie Mitchell, has taken over the chair with great tact and skill, and it bids fair to eclipse the success of "What's My Line?"

FOR BALLETOMANES

DANCING figures increasingly in BBC programmes. The standard of dancing has always been high, but it is not easy to put over in an entertaining manner. The comedy shows now regularly feature ballet scenes as well as the tap and soft-shoe routines, and the dance arrangements are more akin to the choreography of American ballet as seen in American musical films. "Dancers of Tomorrow" was a charming feature about the training of young dancers at the Sadler's Wells School and the Spanish Ballet programme presented by Antonio and soloists from his Palace Theatre Company was excellent. In the latter case, the entire company were not seen on TV and only about eight were seen on the screen at the same time, and then only for the finale. This is a sensible way of putting ballet over on television. Massed lines of dancers are rather wasted, except when filling the ultra-wide screen of a CinemaScope picture. The Antonio presentation was extremely well done from the technical point of view, with novel camera angles and lively cutting from shot to shot which made the most of the gifted dancers.


CONJURORS

RALPH READER has a good reputation as a dance arranger and producer of musical shows, but I found him less good as a comper and comedian's stooge in "It's A Great Life." The highlight of this show was the smooth performance of David Berglas, whose conjuring on a "drink" theme was highly entertaining. A magician has to be good to get by the very close close-ups captured by TV cameras with long-focus lenses. Berglas did it all right—better than some of the magicians who competed in the programme visit to the Magic Circle. Of course, though the tricks are important, it is the patter that goes with them which sells the act.



Viewers recently said goodbye to "What's My Line?" for a while. The show is planned to return when the commercial programmes begin. Left to right: David Nixon, Lady Barnett, Barbara Kelly and Gilbert Harding.

A FEW REMAIN

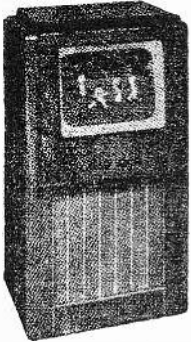

This cabinet is offered below cost. It is suitable for a television using tube sizes varying from 12in. to 17in., its overall dimensions being 3ft. 5in. high, 1ft. 4in. deep, 1ft. 10in. wide. It is complete with plywood back and "Bowler Hat." Originally made for a very expensive television and really good quality. Unrepeatable. Offered at £6/10/6 carriage, packing, etc., 12/6.

BATTERY 3-VALVER



Good reception on both medium and long waves. All parts including three valves, resistors, tuning condensers, in fact, everything except loud speaker, cabinet and chassis (available if you haven't something suitable) costs only 19/6; data available sep. price 1/6.

COMPONENT BARGAINS

(all new and unused)
Blac focus magnet type No. R25-7D—price, 12/6, plus 9d. post. Output transformers standard pentode matching ordinary. 2/6; push-pull, centre tapped. 3/6. Coils suitable for F.M. and T.V. with dust cores and fixing lugs. 12 assorted, 5/6. I.F. transformers, medium, small size, exceptional high Q potted construction, tuning over 450-470 Kc/s. 5/6 per pair. 2-gang tuning condenser—midget, .0005. 5/6. 1/2 meg. pots. with switch, 1/9; less switch, 1/3. double pole switch, 2/-.

SPEAKERS

5 in. p.m. 19/6 | 8 in. p.m. 19/6
6 1/2 in. p.m. 17/6 | 10 in. p.m. 25/-
12 in. p.m. ... 35/-


GENUINE HALF-PRICE OFFER

BEETHOVEN CHASSIS

Extremely well built on chassis size approx. 9 1/2 x 7 1/2 x 8 1/2, using only first-class components, fully aligned and tested, 110-240-volt A.C. mains operation. Three wave bands covering medium and two shorts. Complete with five valves, frequency changer, double diode triode, pentode output and full wave rectifier. Special cash-with-order price this month, £5/19/6, carr. and insurance 7/6.

THE CLEVELAND OCTAVIAN

In this instrument is combined the exceptional qualities of the G.E.C. metal cone loudspeaker in its ideal cabinet and a most modern 3-valve amplifier. This combination will give a realism of musical reproduction not easily obtained even at twice or three times its price and is definitely the reproducer for bringing out the full frequency now available in long-playing microgroove recordings. If you can, please come to one of our branches and hear this fine instrument—failing this, then take our word that it is really good—and send an order today. Price 27 guineas or £4/10/0 deposit, balance by 12 monthly payments of £2/5/9, carriage and insurance 10/-. Amplifier available separately at £10/10/-.

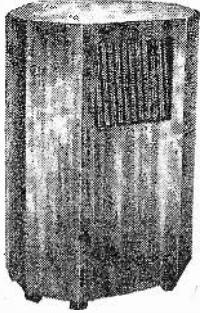

OCTAGONAL SPEAKER CABINET

Conforming exactly to the designer's specifications, suitable for G.E.C. metal cone speaker—price £12/10/- or 37/6 deposit, balance by 12 monthly payments of £1/0/6, carriage and insurance, 5/- extra.

A NEW APPROACH TO AN ALMOST UNIVERSAL PROBLEM

An electronic computer to indicate football results is described in our latest publication. The computer uses 3-valves and information is fed into 12 ratio arms. The result "home," "draw," or "away" is indicated on a centre zero-meter, suitably scaled. The information fed into the ratio arms can be derived from the operator's own pet methods, or alternatively the data freely available in newspapers and popular magazines can be used. The circuit is quite an interesting one but it is not difficult to operate. When complete the unit is entirely self-contained and mains operated. The price of all components needed, excluding metal front plate and chassis, is £3/10/-. Our Publication "A New Approach" is provided free with orders, alternatively will be supplied separately at 2/6, post free.


THE BENDIX RA-1B COMMUNICATIONS RECEIVER

Originally intended for the American Forces this fine receiver, a small quantity of which has been released by the Ministry of Supply, is available to you if you act promptly. Designed to receive C.W. or R.T. it uses probably the finest band spreading arrangement possible, and covers the following bands:

Band 1	.15	to	.315	mc/s	} i.e., 20 to 200 metres
Band 2	.315	to	.680	mc/s	
Band 3	.680	to	1.5	mc/s	
Band 4	1.5	to	3.7	mc/s	
Band 5	3.7	to	7.5	mc/s	
Band 6	7.5	to	15.0	mc/s	

The Sensitivity is 4 micro valves for full output. It uses 8 valves and operates from batteries (12 or 24 volt) or from the mains through a power pack. It has built in output stage with a jack socket for Controls, all of which are brought to the front panel, include aerial switch comparative condenser, main tuning condenser, band selector, C.W. switch, power on/off switch, and volume control.

Very compactly built in crackle finished case, these sets are brand new, having never been used and guaranteed in perfect working order—special price this month is £14/10/- each, or 45/- deposit, balance by 12 monthly payments of £1/3/6, carriage and insurance 10/-. Order now to avoid disappointment. Circuit diagram and component data given free-with sets, or available separately price 2/6, post free.

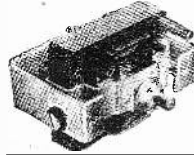

FRICTON DRIVE MOTOR

Operates from standard 50 cycle mains—a thoroughly good job with dozens of applications—limited quantity only—17/6 each, post and packing, 1/6.

THIS MONTH'S SNIP

Mains transformer and choke by Haines Radio, Ltd., Standard 50 cycle input with 10 volts tappings. Secondaries: 500-0-500 volt at 500 millamp and 6.3 volt at 6 amps., also choke to match 10 henrys at 500 millamps. Limited quantity only at 45/- the pair. Carriage and packing 5/- extra.



COMMUNICATIONS RECEIVER R1155 YOURS FOR 30/-



The R1155 is considered to be one of the finest communication receivers available to-day. Its frequency range is 75 kc/s to 18 Mc/s. It is complete with 10 valves and is fitted in a black metal case. Made for the R.A.F. so obviously a robust receiver which will give years of service. Completely overhauled and guaranteed in perfect working order. Price £9/19/6, or will be sent on receipt of deposit of £3/- Balance by 12 monthly payments of 16/3. Carriage and Transit Case 15/- extra. Mains Power Pack, £5/10/-.

CABINETS FOR ALL

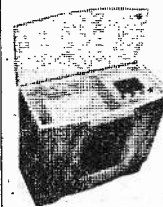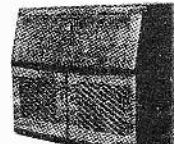We undoubtedly hold the largest stock of cabinets in the country. All are made of the finest plywood, veneered and polished, and all radio and motor boards are left uncut to suit your own equipment. The top one



is The Bureau, walnut finished and highly polished, size approximately 30in. high, 32in. wide, and 16in. deep. Price 16 guineas, carriage 12/6. The centre one is The Empress, our most popular

lar cabinet, size 32in. high, 36in. wide, and 16in. deep, walnut finished, lined sycamore. Price 15 guineas, carriage 12/6. The lower one is The Contemporary, size 29in. high, 30in. wide and 15in. deep. Oak finished with contrasting mouldings. Price £8/15/-, H.P. deposit 19/-, carriage 12/6. H.P. terms available.



MULLARD AMPLIFIER "510"

A High Quality Amplifier designed by Mullard engineers. Robust high fidelity with a power output exceeding 10 watts and a harmonic distortion less than .4% at 10 watts. Its frequency response is extremely wide and level being almost flat from 10 to 20,000 C.P.S.—three controls are provided and the whole unit is very suitable for use with the Goliath Studio and most other good pick-ups. The price of the unit completely made up and ready to work is £12/10/- or 25/- deposit, plus 10/- carriage and insurance.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 7, RUISLIP.


42-46, Windmill Hill, 152-3, Fleet Street, 29, Stroud Green Rd., 249, Kilburn
Ruislip, Middx. E.C.4. Finsbury Park, N.4. High Road, Kilburn.
Phone: RUISLIP 5780 Phone: CENTRAL 2833 Phone: ARCHWAY 1049
Half day, Wednesday. Half day, Saturday. Half day, Thursday. MAIDA VALE 4921

LASKY'S RADIO

CRYSTAL DIODES
Glass type, wire ends. 1/6 each. Higher Grades, 12 Assorted for 30/- Post free.

CO-AXIAL CABLE
75-90 ohms impedance. Single core, yd. 8d. Twin, 1/- Twin-Balanced Feeder, 6d.

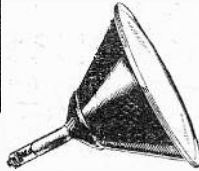SPECIAL PURCHASE OF 16in. C.R. TUBES. Famous make offered at nearly Half-Price. Metal cone, 3 amp. heater, e.h.t. required 10-14 Kv. Limited quantity only.
LASKY'S PRICE £12.19.6
Carr. & Ins. 22/6 ex




THE HANDSOME "ROTHESAY" CABINET

Absolutely rigid construction throughout with the finest laminated woods, veneered in walnut, polished light, medium or dark shade. Fitted with gold anodised speaker grille. The C.R.T. aperture frame is detachable, supplied to suit any size tube to order.

NOTE THESE GENEROUS SIZES
Outside dim. 34in. high, 21in. wide, 21in. deep. Inside dim. 18in. wide, 19in. deep. Size of top 22in. x 21in. Thickness 1in.

Lasky's Price ... £9.19.6
Carriage 15/- extra.

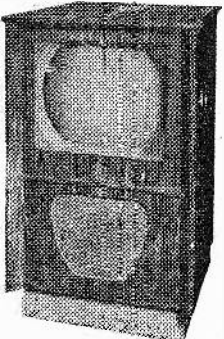Available on H.P. terms. Details on request.




ALL MAIL ORDERS TO HARROW ROAD, Please.
Please add reasonable amount for postage unless specified.

CONVERT YOUR "VIEW MASTER" TO 14, 16 or 18in. SCREEN

Wide Angle Conversion Kit using only W/B components as specified, viz., line trans., filament trans., frame trans., scanning coils, width and linearity controls, focus magnet, ion trap, 1-K3/100, 1-K3/40 metal rectifiers, 1-6CD6, 1-6U4GT valves, 3 resistors, 9 condensers. Complete parcel including valves and data book.

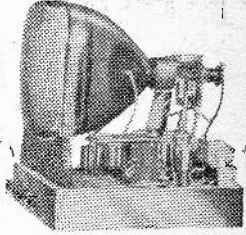£7.19.6 Post & Pkg. 3/6 extra.
BOOKLET 3/6 post free.



MAKERS' SURPLUS COMPONENT BARGAINS

WIDE ANGLE 38 mm.	STANDARD 35 mm.
Line E.H.T. trans. ferro-cube core, 9.16 kv. ... 25/-	Line Output Transformers No. E.H.T. 19/6 Line Output Transformers 8.9 kv. E.H.T. and 6.3 v. winding. Ferro-cube 19/6
Scanning Coils, low imp. line and frame ... 25/-	Scanning coils. Low imp. line and frame, by Igranic ... 12/6
Frame Output Transformer ... 10/6	Scanning Coils. Low imp. line and frame, by Igranic ... 14/6
Scanning Coils, low imp. line and frame ... 17/6	Line blocking oscillator transformer ... 4/6
Frame blocking osc. transformer ... 4/6	Frame blocking oscillator transformer ... 4/6
Line Blocking osc. transformer, caslam cored ... 4/6	Frame blocking oscillator transformer ... 4/6
Focus Magnets Ferro-dure ... 25/-	Frame output transformer ... 7/6
P.M. Focus Magnets, Iron Cored ... 19/6	former ... 4/6
Duomag Focalsisers ... 29/6	Focus Magnets: Without Vernier ... 12/6
300 m.a. Smoothing chokes ... 15/-	With Vernier ... 17/6
Electromagnetic focus coil, with combined scan coils ... 25/-	Focus Coils. Electro-magnetic ... 12/6
	200 m.a. Smoothing chokes ... 10/6

Open all day SAT. Half day Thurs.

LASKY'S (HARROW ROAD) LTD.,
370, HARROW ROAD, PADDINGTON, W.9.
Telephone: CUNningham 1979-7214.
42, TOTTENHAM COURT ROAD, W.1.
Telephone: MUSeum 2605.

LOW LOSS COAX 9d. Yd.

Especially in fringe areas, it is important to cut losses to a minimum. We can offer low loss semi-rigid coax at only 9d. yd. standard coax, stranded core, 8 1/2 yd. Both types 75 ohms, approx. 1in. dia.

COAX FITTINGS.—Universal plug, 11d.; solderless plug, 1/2; socket, 1/3; outlet box, 4/6. Coupler (double socket), 1/3.

BAND 3 CONVERTERS.—We are now booking orders for forward delivery of these. Self-contained types involving no alteration to set are available. Send for details now, and avoid disappointment, there will be a big rush later.

BARGAIN BASEMENT!

VALVES.—A. Maker's cartons. B. Unseal, boxed.
Type A B Type A B Type A B
6P6G 7/- — 6K3G — 8/- 80 — 8/-
6J5GT 3/9 — 6Q7CT 8/- 7/6 EB34 — 1/9
6J7 — 6/8 68H7 5/6 — EC31 — 3/6
6K6GT 6/- — 6SK7 5/9 — KT263 — 6/-
6K7 6/6 — 6V04 — 6/9 RK24 2/3 —
6K7GT 4/9 3/9 12H6 — 2/9 SP41 — 2/6

CONDENSERS.—Micas: 20, 50, 75, 200 pF, .001, .002, .003, .005 mfd., 2/6 doz. Metal boxes 5+ 5 (400 v.), 4d. 6 mfd. 2,000 v. test, 3/8, post 1/-.

MIDGET TUBULARS (tested), .01, .04, 3/6 doz.
RESISTORS.—5 w. carbon, 500, 700, 8 K, 4 K, 5.6 K, 12 K, 20 K, 30 K, 200 K, 8d., 6 for 3/-.

WIRE WOUND RESISTORS, SILICONE COATED.—25, 50, 68, 100, 150, 200, 250, 350, 500, 680, 1 K, 1.5 K, 2 K, 2.5 K, 3.5 K, 5 K, 8 K, 10 K, 5 w. 1/-, 10 w. 1/3, 15 w. 1/9; 1/2 K, 1/8 K, 20 K, 25 K, 33 K, 5 w. 1/9, 10 w. 2/9; 47 K, 50 K, 5 w. 2/3, 10 w. 2/6.

POTENTIOMETERS (Carbon) 500 K, 1in. dia., 1in. spindle; 5 K, 100 K, 1 1/2in. dia., 1in. spindle; Boxed 500 K, 1 1/2in. dia., 1in. spindle; all 1/6 (6 for 6/-).

BARGAIN ASSORTMENTS (all goods unused).—Our choice, 50 micas, 3/9; 100 micas, tantalum, metal blocks, etc., 17/6; 50 resistors from 1 w. to 2 w. 8/-; 12 potentiometers, 10/-.

VALVEHOLDERS (Amphenol).—Octals (U.S.A. or British), 8/6, 9d.; B8A, B8H, B9A, 1/-.

PLUGS FOR VALVEHOLDERS.—B7G and B9A (very neat), 1/6. International octal, 2/3.

Orders over £1 post free! List 3d.

REED & FORD
2A BURNLEY ROAD, AINSDALE, SOUTHPORT

OPPORTUNITIES IN TELEVISION

144 pages
Free!



Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS—NO FEE"

If you are earning less than £15 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

— WRITE TODAY! —

British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane,
Kensington, W.8. **BIET**

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH
CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE

(DEPT. B)

72-76 Leather Lane, Holborn, E.C.1
Phone: CHAncery 6791/2

NEW VALVES — 24 HOUR SERVICE

1R5	7/6	6C4	5/-	CV287	7/6	EL55	8/6
1R5	7/6	6C16	6/6	CB11	10/-	EL91	7/6
1T4	6/6	6P7	7/6	EB3	10/-	EL84	11/6
1L4	4/6	6J7	5/-	EB91	5/-	EL75	11/6
2D21	9/-	6B6	5/-	EC130	11/6	PC354	12/-
2X2	3/6	6K7G	5/6	ECC81	10/6	PL81	11/6
3A4	7/6	6K7GT	6/6	ECC82	10/6	PL82	10/-
3D6	5/-	6K7M	6/6	ECH35	10/-	UVJ1	9/-
6V3RT	7/6	6K8G	8/6	ECH42	10/-	UCH42	10/-
6U4G	8/6	6N7GT	7/6	EP97	7/6	VS110A	4/6
6Z4G	8/6	6N7GT	6/6	EP29	6/-	VR10630	7/6
6AG7M	10/-	6SL7M	7/6	EP30 (5y)	7/6	VR150/30	7/6
6AK5	6/6	6X5GT	7/6	EP54	8/-	VR150/30	7/6
6AM6	5/-	6Z4G	5/-	EP50	10/-	W77	5/6
6BE6	7/6	12B26	7/6	EP92	5/-	XP (1.5)	3/6
6BA6	7/6	12B26	7/6	EP91	5/-	Z77	5/6
6BW6	7/6	CV286	7/6	EP91	5/-	Z77	5/6

Please add 6d. postage.

JOHN ANGLIN (Dept. P.T.)
180, Cleethorpe Road, Grimsby, Lincs.
Tel. 56315.

Frame Flyback Suppression—2

SOME CIRCUITS FOR THE EXPERIMENTER

By "Erg"

(Continued from page 488, April issue)

A TYPICAL method of applying the principles in a practical way is shown in Fig. 4. This shows the scheme applied to the Electronic Engineering television which employs grid modulation of the tube.

V16 is the thyratron-frame oscillator and provides an output which is positive-going on scan. The output of the frame output valve is therefore positive

in the diagram; the cathode is then connected to the anode of the output valve via the resistor R3 and the condenser C.

It should be noted that the performance of the circuit depends upon the time constants of the coupling components, and if difficulty with linearity is experienced, then some variation of the condenser C may be called for. This applies to all the circuits mentioned.

The Simplex Magnetic Television

Another example of a grid modulated television is the Simplex. The position here is further complicated by the fact that the input to the frame output valve is negative-going on scan, which means that the output has a negative flyback and obviously cannot be applied to the cathode circuit.

The problem can be overcome by tapping the pulse, from the frame coils themselves, the correct polarity being obtained by earthing one or other side of the coil, the tap being taken from the other side. Fig. 5 shows the scheme.

The cathode circuit of the C.R.T. must be modified in the manner given previously.

The "Practical Television" Television

This television uses cathode modulation of the C.R.T. and the output of the frame amplifier is positive-going on scan. The flyback is therefore negative and a suggested circuit for flyback suppression applied to the grid of the tube is given in Fig. 6.

The Lynx

Like the previous model, this television also uses cathode modulation of the C.R.T. The flyback at the frame output valve is negative-going and a method of adapting the circuit is given in Fig. 7.

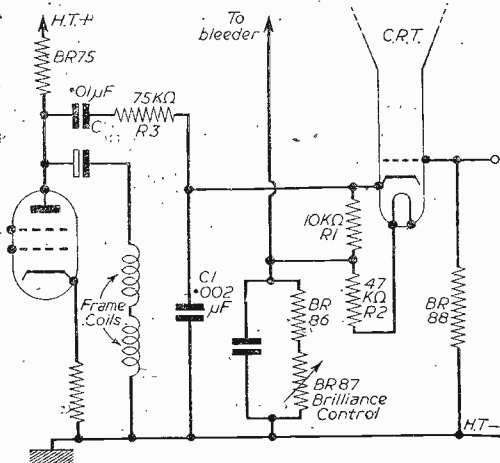


Fig. 4.—E.E. circuit modified. Here R1, R2, R3, C and C1 should be inserted.

on the flyback, and this can be applied directly to the cathode of the C.R.T.

The first step is to modify the existing cathode circuit by the insertion of the resistor R1 as shown

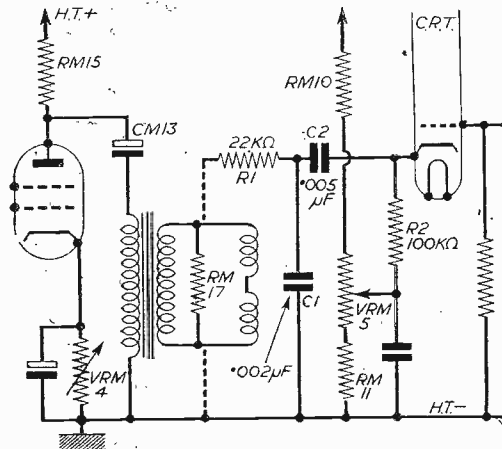


Fig. 5.—"Simplex" M circuit modified. R1, R2, C1 and C2 should be inserted.

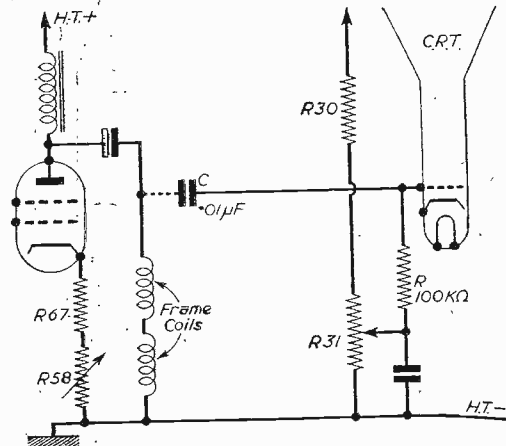


Fig. 6.—The "Practical Television" receiver modified. C and R are inserted in the existing circuit.

The Viewmaster

The Viewmaster is another circuit which uses cathode modulation. A suggested circuit for modifying the flyback is given in Fig. 8. In this case the flyback is obtained from the frame coils themselves; one side of the coils must be connected to chassis and the other taken to the cathode of the C.R.T. If correct polarity for suppression is not obtained, simply change the earth and the 27K. connections round on the frame coil.

Other Models

It has not been possible to mention the variations required for all the television receivers designed for the home constructor in a short article of this nature, but the principles given should enable the constructor to adapt the designs to his own particular needs.

Miller Timebases

There are very many receivers built by the amateur which employ the Miller transistor and integrator type of timebase. It has not been favoured a great deal by the manufacturer because, in spite of its excellent properties in providing a linear scan, its output is the reverse to the usual timebase oscillator—i.e., it is negative-going on scan.

The modern type of timebase amplifier precludes the use of a negative input for the line circuit, not only because of the difficult biasing arrangements for the output valve, but also because of the extremely high voltages produced during the flyback. If the amplifier input is negative, then the flyback at the anode is negative, and when it is realised that a peak voltage in excess of 2,000 volts can be reached by the flyback it is plain to see that severe damage may be done to the output valve.

It is possible to employ the Miller circuit in a magnetic televisor, but steps must be taken to reverse the polarity of the output. This is not difficult and circuits employing this principle have been published in this journal.

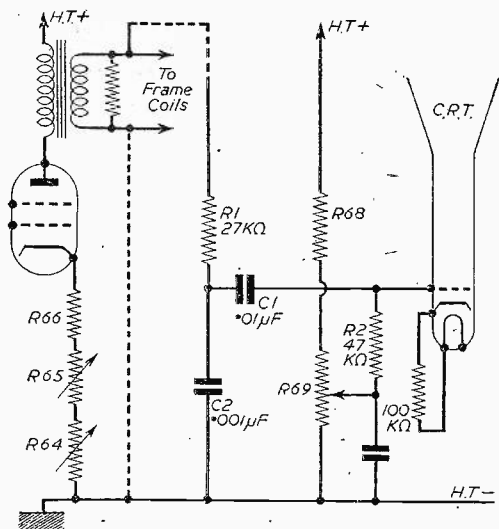


Fig. 8.—The "Viewmaster" modification. R1, R2, C1 and C2 should be inserted.

The suppression of the flyback can be accomplished in this class of circuit quite easily, provided the fact that the output is negative-going on scan and positive-going on flyback is kept in mind. We have already dealt with one case of this kind—the Simplex

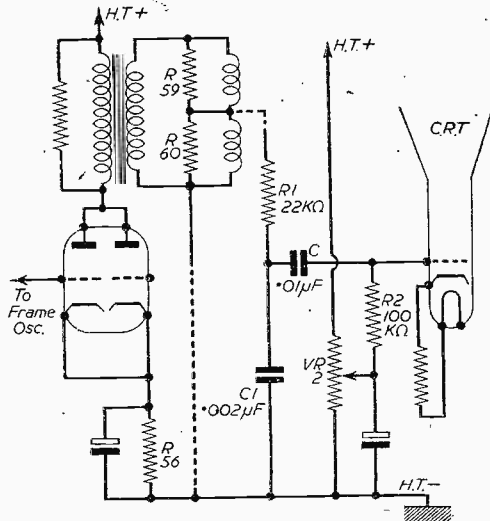


Fig. 7.—The "Lynx" modification. R1, R2, C and C1 should be inserted.

magnetic model which uses a Miller oscillator followed by a phase reversal stage before the line amplifier proper.

Simplex Electromagnetic Model

This televisor is a recent example of a circuit employing the Miller oscillator for the frame circuit, and the method of adapting it for suppression of flyback is quite simple. Fig. 9 shows the adapted circuit.

A resistance of 100 kΩ is inserted between the
(Continued on page 567)

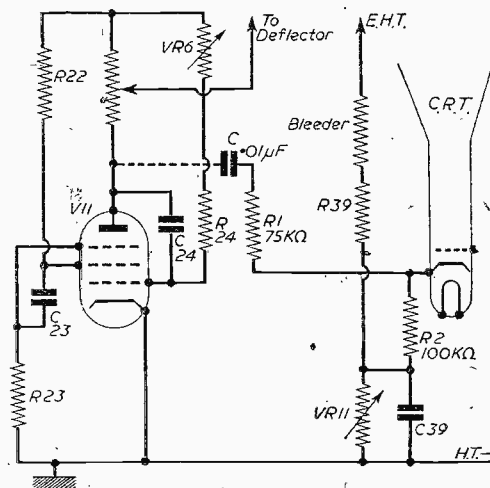


Fig. 9.—The "Simplex Electromagnetic" modification. C, R1 and R2 should be inserted.



E.H.T. TESTER

Don't guess E.H.T.—test it. 3-16 kV. A.C. and D.C. for line fly-back or transformer E.H.T. Boxed with full instructions. 52/6 post paid.

"A Practical TV Aerial Manual for Bands I and III."

Describes almost every type of TV aerial of practical use with full details for their construction and erection. Deals with the latest developments in Band III aerials and the construction of tested and tried types. This booklet is an essential for every engineer and home constructor.

PRICE 4/9d. post paid

HOME RADIO OF MITCHAM
187, London Road, Mitcham, Surrey. MIT 3282

SOLDERING - SAFE - SIMPLE - SPEEDY
with the sensational



70/-
post free

PRIMAX—★
BALANCED GRIP SOLDERING GUN

★ NOW IN A NEW UNBREAKABLE CASE

WITH HOOK ATTACHED FOR HANGING OVER WORKBENCH

The PRIMAX-SOLDERER is the ideal tool for any RADIO-TV-TELEPHONE mechanic or amateur. Just the tool for service calls and small jobs on the bench. For semi-continuous soldering. Available for 110, 200/220 and 220/250v. A.C., 50/60 cycles (60w.). One year guarantee. Specially designed for easy soldering on hard-to-reach jobs.

- ★ TRIGGER CONTROL for semi-continuous use.
- ★ EXCLUSIVE ALLOY TIP—never needs re-tinning or filing, lasts indefinitely under normal use and care.
- ★ INSTANT HEATING—Ready for soldering in 6 seconds.
- ★ COMPACT LIGHTWEIGHT—slips into pocket or tool-kit, weighs only 24 ounces.

Sole Distributors :—

S. KEMPNER, Ltd. 29, Paddington Street, W.1
Tel. HUNTER 0755. Through wholesalers and retailers

IT'S 60% CHEAPER!!

to construct your own aerial, whether
TELEVISION or YAGI


Write for our catalogue, illustrating all fittings, prices, etc. Included in the range we offer Alloy Masts, Insulators, Reflector and Director rod holders, Mast head fittings, together with formulae, useful construction hints for designing your own aerial, etc.

Send 9d. in stamps to cover the cost of postage and catalogue to :—

Fringevision Ltd.

MARLBOROUGH, WILTS.

Phone 605.

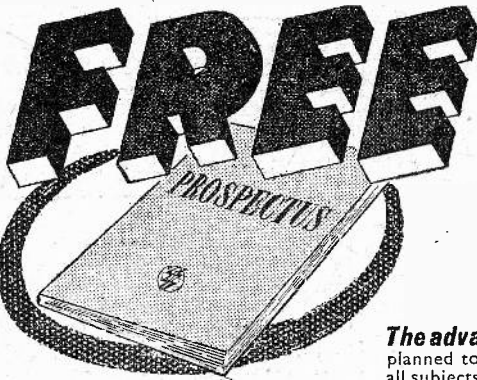

POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M.Brit.I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

Equipment supplied upon enrolment and remains your property.

Courses from 15/- per month

POST THIS COUPON TODAY

Send without obligation your FREE book.
E.M.I. INSTITUTES, Dept. 138K,
43 Grove Park Road, London, W.4.

NAME _____

ADDRESS _____

5/55
SUBJECT(S) OF INTEREST _____

NEW LEARN THE PRACTICAL WAY, COURSES WITH EQUIPMENT

With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

EMI INSTITUTES
The only Postal College which is part of a world-wide Industrial Organisation.

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

ADJACENT CHANNEL INTERFERENCE

SIR—Re your answer to W. A. Henderson (Whitehaven), "Your Problems Answered," "Adjacent Channel Interference," January, 1955.

The "venetian blind" effect mentioned is not only suffered by Mr. Henderson, but is received on all makes of receivers not only in this area but also by residents of the Isle of Man.

This seems to point to the interference being transmitted from the Isle of Man.

It might be noted that on the original opening of the Isle of Man station this interference was not present.

It is possible that adjacent channel interference may be in the radio link to the Isle of Man.

We of one of the forgotten TV areas would much appreciate any reliable information about the permanent high-power transmitter which is supposed to be installed on the Isle of Man.—J. COLEBROOK (Whitehaven, Cumb).

THE P.T. "SUPERVISOR"

SIR—I have yet seen no correspondence concerning the above receiver and it was the February issue with modifications article which has prompted me to write this.

When I completed this receiver some four months ago I encountered trouble with the vertical hold. In fact it was through your query department I learned about the error re R37. Although I changed this to a 100K with some improvement the picture still rolled. After much "tearing of hair" I decided to try a different value for the frame hold control VR6. This was increased to 1 meg. and now the picture locks solid even with the contrast a quarter of the way up.

A few further points which may be of interest. In order to cut costs I took the risks of using all "surplus market" valves except the 6CD6 and I used an RM4 and a GEX35 in place of the Westinghouse types.

The C.R.T. is a T901A with heater coupled to an isolating transformer as suggested.

The set is used with a home-made "H" aerial receiving Sutton Coldfield some 70 to 80 miles away.

I found it quite simple to align and the advantages of refinements such as A.P.C. have gone towards giving reception superior to a T.R.F. receiver which I had previously. Wishing your journal continued success.—E. ANDREWS (Oxford).

FADING OUT PROGRAMMES

SIR—I really cannot agree with the remarks made by "Iconos" about the fading-out of some television programmes as an indignity. The fact is that both cases he mentions were followed during the evening by a Continental exchange and we cannot expect these other countries concerned to alter the whole of their time-tables just because British TV producers and comics cannot work to an allotted time. They were over-running their time and there's an end of the matter. Why should the pianist or the author sacrifice their programmes because of the long-winded efforts of some comics who don't know when to stop? Let those who like their comedy (and

I am one of them) have it by all means but don't drop down like a sack of bricks on the "cultural" items which happen to follow.

"Iconos" needn't appeal to Sir George Barnes for examples of "culture" giving way to comedy or other programmes of similar vein—I can recall dozens of occasions when this has happened, usually during symphony concerts and classical recitals on the Home Services, though I agree that the tendency is much less on television.—S. A. KNIGHT (Chelmsford).

BIG SCREEN CINEMA TV

SIR—I was interested to read in the February issue of PRACTICAL TELEVISION Iconos's note of the London Coliseum and Television.

Actually it was in 1929 that the Coliseum first was associated with television in conjunction with the late J. L. Baird. In that year a large screen was placed on the Coliseum stage and the picture of the late Sir George Robey live, also from a film, was transmitted from the Baird studios in Long Acre. The presentation of the act was when Sir George Robey first appeared on the Coliseum stage in person, then while he travelled up to Long Acre, a distance of some 300 yards, a film of him was projected on to the screen from Long Acre and then arriving in the studio he did the same act again by live television. I forget exactly for how long this was done—it was certainly a week and may have been a fortnight.

It might interest a younger generation to know that the screen used 2,100 bulbs of the "torch" variety, the scanning being arranged by rotary commutator of the same number of segments, and the actual screen was (if my memory is correct) some 30in. x 70in., the exact definition being 30-line.—D. R. CAMPBELL (Weybridge).

SOUND QUALITY

SIR—In last August's issue you published a letter of mine in which I criticised the quality of film sound tracks when shown on television.

Now, having seen the "Fabian of the Yard" series, I take back what I said. The quality that the recording engineers have obtained for this series of films is excellent, almost like "live" broadcasts.—J. BARWELL (Haywards Heath).

TELEVISION HEARING AID

SIR—I read with interest your note in the March edition of PRACTICAL TELEVISION under the heading "News from the Trade."

I would like to point out that such an attachment has been on the market to my knowledge for a considerable time, and during the course of my business I have run across dozens of them. I refer to the product known as the "Adaphone," measuring only 2in. by 1½in., and manufactured by a firm well known for its work in hearing aids and the needs of the deaf.

The Adaphone is marketed in three distinct forms, each fitted with a miniature earpiece, and, indeed, includes a standard mould which fits into the ear.

For those desiring a tailored mould, one is supplied at a slight extra cost, moulded to suit the individual

(Continued on page 571.)

THE *Radar* KILOVOLT for E.H.T. MEASUREMENT


RANGE 3-30KV.

Designed for use with Line-Flyback, R.F. and Pulse E.H.T. systems.

The Kilovolt consists essentially of a calibrated spark gap and no load is presented at the correct setting.

Safe, reliable and fully guaranteed. Order now from your usual wholesaler or direct from:

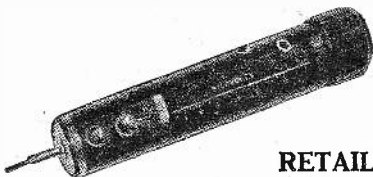WAVEFORMS LTD., Radar Works, Truro Road, London, N.22. Telephone: Bowes Park 6641-2-3.



**RETAIL
PRICE
£3. 17. 6.**



QUALITY TELEVISION COMPONENTS

SCANNING COILS
6/10 kV. R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS
LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

For study or daily reference—a work that records achievement to date and anticipates new developments:

TELEVISION PRINCIPLES AND PRACTICE

(2nd Edition).

by **F. J. CAMM.**

Some of the Contents: The B.B.C. Television System—The Television Camera—From Transmitter to Receiver—Projection Receivers—Stereoscopic and Colour Television—Time Bases—D.C. Receivers—Aerials—London-Birmingham Converter—Servicing—Interference—A Pattern Generator—Choosing a Receiver—Dictionary of Television Terms.

25/- NET

or 25/6 post free from

**GEORGE NEWNES, Ltd., Tower House,
Southampton Street, W.C.2.**

From all booksellers.

NEWNES

BUILD ONE OF THESE SETS!

CAN BE BUILT FOR ONLY
49/6



Build this exceptionally sensitive twin-triode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes.

Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 5 in. Covers all medium and long waves, uses one only all-dry battery which lasts many months as H.T. Consumption

is only 1 to 1.5 m.a. Ideal for bedroom, garden, holidays, etc. Complete kit only 49/6. Post Free (sent by return with full set of clear, easy-to-follow plans). For headphone operation (speaker and extra stage 34/-). All parts sold separately.


MAINS VERSION WITH SPEAKER 89/6 Post Free
A.C. Mains only. Twin-triode mains version with speaker, completely hum-free, with exceptional tone, optional negative feedback. Very low consumption. Complete kit with speaker, etc., 89/6 Post Free (with full set of clear, easy-to-follow plans). All parts sold separately.

CAN BE BUILT FOR ONLY **97/6**

AMAZING VALUE!... Complete kit of 3 valves, plus metal rectifier, A.C. Mains set, only 97/6. Terrific new circuit, with optional negative feedback circuit giving beautiful tone. Covers all Medium and Long Waves. Ready to use chassis (Punched, etc.). Every component tested before packing. Cabinet size 12 in. x 6 in. x 5 in. For A.C. Mains 200/250 volts. Complete kit with valves, speaker, cabinet, etc., only 97/6, plus 2/6 Post and Packing. (Sent with full set of clear, easy-to-follow plans). All parts, cabinet, speaker, etc., sold separately.

READ THESE TESTIMONIALS.
Mr. Carter, of Worcester, writes: "Just a few lines to let you know how pleased I am with the midget portable radio. I was surprised at the number of stations I could get with a clear performance. The price was a real bargain." Mr. Norton, of Oxted, writes: "Yesterday evening on the medium wavelength, I counted 32 separate stations: I am very pleased with the set, which is well worth the money."

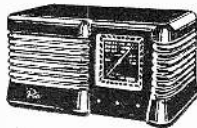BRIGHTON RADIO & TELEVISION CO., D. Dept. P.T.7) 69, PRESTON STREET, BRIGHTON, I.



SIMPLEX 12" MAGNETIC MODEL COMPLETE (LESS TUBE & SPEAKER)

£23

STAGE I, £3 STAGE II, £3 STAGE III, £4/18/-
STAGE IV, £2/7/- STAGE V, £6/19/- (Less Speaker & Tube)
STAGE VI £3/5/-

6" MODEL

STAGE I, £3 STAGE II, £3 STAGE III, £4/18/-
STAGE IV, 57/- STAGE V, 33/- PRE-AMP STAGE, 7/6
(Less Speaker)

VALVES

EF50	4/-	6B4	4/-	RK34	2/6	SP61	2/6
EF50(Syl)		EF36	4/6	EA50	2/-	SP41	2/6
	6/3	EF39	7/6	EB34	2/-	Pen43	5/-
EF54	5/-	EF91	7/6	D1	2/-	3A4	7/6
1T4	7/-	1R5	7/6	1S5	7/6	6SL7	7/6
3S4	8/6	3V4	8/6	3Q4	8/6	6SA7	7/6
6SN7	9/-	6SK7	4/-	6SJ7	4/6	EBC33	8/-
6K7	6/-	6V6	8/6	6Q7	8/6	ECC31	8/-
6K8	11/-	5Z4	8/6	5Y4G	8/6	6AT6	7/6
EL50	9/-	EL32	7/-	6U5	5/-	AR8	6/6
9BW7	9/-	R19	13/-	6N7	8/-	50L6	9/-
VU133	3/-	VU111	3/-	2X2	2/6	VU120	4/6
954	3/-	955	5/-	VU39	8/6	ARP12	6/-

CONDENSERS.—Elect. DUBILIER. 500 volt wkg. 20 mfd., 3/-; 32 mfd., 5/-; B.E.C. 450 volt wkg. 8 mfd., 2/-; 8+8 mfd., 3/9; 8+16 mfd., 4/-; 16+16 mfd., 4/6; 32+32 mfd., 6/-; Bias 25/25, 2/-; 50/50, 2/-.

RECTIFIERS.—RMS, 5/9; RM4, 16/-; K3/40, 6/9; K3/45, 8/-.


POTENTIOMETERS.—All values to 2 Meg., less switch, 2/6 each. 100k 1, 1, 1.2 Meg., with switch, 4/- each.

RESISTORS (Carbon).—1, 1, 1.2 watt, 12/6 per 100. Our Selection, CRACKED CARBON, 1/-, 1/6; 2/-, 1/-; 5/-, 9d. each. VITREOUS, 5 watt, 1/3 each.

COAX (CABLE).—in. 80 ohm, any length, 8d. per yd.

GERMANIUM-CRYSTAL.—1/8 each, 15/- per dozen.

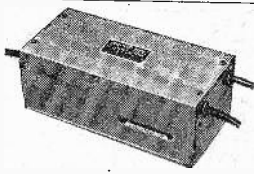VINER'S (Middlesbrough)
Radio Government Surplus Electrical
26, EAST STREET, MIDDLESBROUGH
Telephone: MID 3418.



CONVERTOR TYPE 26.
For conversion from channel 3 to channel 1, complete with self contained power supply unit and totally enclosed in a handsome, well finished steel case. Price complete£11-17-0

Also available in chassis form less H.T. supply but including mains operated heater supply for inclusion in receivers. Price complete£8-0-0

CONVERTOR TYPE AC/4
For weak signal areas. Price complete£15-15-0

(Leaflets on request)

**SPENCER-WEST
QUAY WORKS,
Gt. YARMOUTH.**

Tel. : 3009. Grams : Spencer-West,
Gt. Yarmouth.

VALVES

SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. miniatures. 1R5, 1S5, 1T4, 3S4, DAF91	DF91, DK91, DL92, 7/3 ; any 4 for 27/6.
1A7GT	6LD20 9/6, 50L6GT8 6/EY51 12/-
1C5GT	11/6 6P25 14/6 80 8/6 E240 8/6 6E28 18/6 B36 18/6 E241 9/-
1D5	11/6 6S7GT 9/- CL33 12/6 FC2 9/6
1H5GT	8/6 6D7 8/6 6R33 7/6 11/6 6U4GT DAC32 MU14 8/6
1N5GT	11/6 6V8G 17/- DF33 11/6 Pen15 15/- 7/3 6V8GT 7/6 DH77 8/6 PCF80
1R5	7/3 6X4 7/6 DK32 11/6
1S5	7/3 6X4 7/6 DK32 11/6
1T4	7/3 6X5GT 6/9 DK32 7/6 PCC04 10/6
3Q5GT11/6	7/6 DL33 11/6
3S4	7/3 7C5 8/6 DL35 11/6 PL81 11/6
3U4G	8/6 7C8 8/6 RA50 1/9 PL82 9/6
5Y3GT	7/9 757 7/6 EB91 8/9 PL83 12/6
5Z4C	9/- 7Y4 8/6 EBC41 10/- PY81 9/6
6AL5	6/9 10C1 12/6 EBF80 PY82 7/9
6AM5	6/6 10F1 10/- 10/6 PZ30 17/-
6AM6	7/6 10P13 10/- ECC91 10/6 T41 13/-
6AT5	8/6 10P14 13/6 EC91 7/6 U14 8/6
6BA6	8/6 12AT 9/- EC301 9/- U22 7/6
6BB6	6/6 12AU6 7/6 ECC83 U22 7/6
6BH6	6/6 12AU7 10/6 11/6 U25 12/-
6BJ6	6/6 12J7GT ECH35 U50 7/9
6BW6	7/6 10/6 11/9 U78 8/6
6B7	9/6 12KTG 19/6 ECH42 10/- U404 9/-
6C1	7/6 12K6GT ECL80 9/6 UB49 14/6
6C9	8/6 10/6 EP37A UBC41 9/-
6F1	19/6 12Q7GT 14/6 UBF80 10/6
6FG6	7/6 9/6 EFX9 6/8 10/6
6F12	7/6 12SK7 6/- EF41 9/- UCH42 9/9
6F13	19/6 20P2 11/6 EFX50 UF41 8/6
6F14	13/6 20P1 15/- (Sylvania) UF42 13/6
6J7GT	7/6 25Z4G 8/- 8/6 UL41 9/9
6KTG	6/- 25Z5 8/6 EFX80 10/- UUR 17/-
6KTGT	6/- 25Z6G 8/6 EFX91 7/6 UY41 9/-
6K8C	8/6 35L6GT 8/6 EFX92 5/6 W77 5/6
6K8GT	9/- 35Z4GT 8/6 EL41 11/6 Y63 7/6
6K25	11/9 35Z5GT 8/6 EL51 6/6 Z77 7/6

Postage 4d. per valve extra.

READERS RADIO
24, COLBERG PLACE, STAMFORD
HILL, LONDON, N.16. STA. 4587

**NEW-MAX
ELECTRONICS LTD.**

307, EDGWARE ROAD

(Just past the Met.)

Tel. : PAD 5607

London's Best T.V. and Radio
Bargain Store

We have just completed a large purchase of used and H.P. reprocessed T.V. sets—all types and all sizes—to be sold at knock-out prices. Special item : 1807 H.M.V. 10in. chassis adapted to be used with Mazda 12in. tube, £19/10/-, including tube. Also large selection of used radios, gram chassis, instruments, amplifiers,

TAPE RECORDERS, ETC.

STOP PRESS !—Special offer : T.V. Tubes
All Sizes : 9in., £4 ; 12in., from £4/10/- ;
14in., £6 15in., £7.

Every tube guaranteed.

Callers can see picture before purchase.

BENDIX RECEIVERS, TYPE RA1B.—Brand New, ultra sensitive, 15 metres to 166 metres, and 200 to 2,000 metres in 6 Bands. Very neat and compact. Dia's : 9 1/2in. x 6 1/2in. x 14 1/2in. All controls on front panel. An excellent receiver for Ham Bands. 20, 40, 80, 160 metres, for Trawler Band and Long and Medium Waves. Size makes it suitable for a superb Car Radio. Only £15, P.P. 10/-.

INDICATOR UNIT TYPE 233. with VCR57 and 8 valves. Ideal for Simplex, etc., only 42/6.

MICROAMP METERS.—100 uA, 2 1/2in. Prof. Min.-Max. scale, but a standard 100 uA. movement, 27/6. 500 uA, 1 1/2in. Rd., Fl. 0-10 scale, 8/6. 50 mA., Mic., 2in. Sq., 6/-.

MAINS TRANSFORMERS.—350-0-350 v., 80 mA., 6.3 v. 3.5 a., 5 v. 2 a., new, D.T. covered, 17/6. P.P. 1/-.

NEONS.—Strike on 80 v. Supplied with series res. for mains, 1in. x 1/2in. dia., 2/- at 7 kv., T.C.C. 7/- 1A., 1. 500 v. 1 in. Tropical Cartons, 1952. 3 for 1/-, Aladdin Coils, 1in. with Core, 6d. Polyester 4 in. with Core, 9d. Bulgin Panel Lamps, Red or Green, 2/-.

RESISTORS.—1 w., 3d., 1 w., 4d.; 1 w., 6d. VALVES.—AR12, 4/- ; SP41, 1/3. EF50 Bases, Ex. Equip. Cap., 3 for 1/-, Metal Recs., 300 v. 80 mA., 5/6. Pots., 100 K., 3 K., Sp., 1/- ea. 1 Meg., 1/6. H/R Headsets, 3,000 ohm, 7/6. 100 pF. Mica, 500 pF. Mica, 2,000 pF. and 5,800 pF. Silver Mica, 3 for 1/-.

PILOTS HELMET MIKES 2/- each. Post extra. Ex. Equip. only if stated S.A.E. for Lists.

Bates Surplus Store

49, IVY ST., BIRKENHEAD, CHESHIRE

**HIGH GRADE
TRANSFORMERS**

FOR ALL PURPOSES
SINGLY OR IN QUANTITIES
TO YOUR SPECIFICATION

VARNISH IMPREGNATED
BAKED WINDINGS
WITH OR WITHOUT TAG PANELS
GOOD DELIVERIES

Our rewind dept. will handle your repairs promptly and efficiently.

S.A.E. with enquiries please.

P. HOWORTH

(Dept. P.T.)

51 POLLARD LANE BRADFORD

Tel. : 37030

LYONS RADIO Ltd.

3, GOLDHAWK ROAD, Dept. M.T.
SHEPHERDS BUSH, LONDON, W.12.

Telephone : SHEPHERDS Bush 1729

BRIDGE MEGGERS.—An invaluable testing set comprising a Meg. insulation tester and a complete Wheatstone bridge for the accurate measurement of resistance. Incorporating a constant pressure hand generator, a direct reading ohmmeter which also serves as the galvanometer for the Wheatstone bridge, a direct reading adjustable resistance and the necessary ratio and change-over switches. Testing volts 250 v. Insulation range 0/100 megohms. Resistance measuring range 0.01 ohms to 1 Megohm. In good condition and supplied in leather case. PRICE £21.

AMPLIFIER UNITS, TYPE A.1134.—These are two valve audio amplifiers and can be used without any modification as a mike preamp or as a gramophone amplifier. Also for intercom purposes. Valves fitted are VR21 and VR35. Operate from 2 v. L.T. and 90 or 120 v. H.T. and 9 v. G.B. Housed in neat metal cases, 7 x 5 x 4 ins. In good condition and with connection details provided. PRICE ONLY 12/6, post 2/6.

INDICATOR UNITS, TYPE 182.—Fitted with cathode ray tube, type VCR517 (TV picture tested), 3-VR91's, 4-VR65's, 1-5U4, Mu metal screen, wire wound pots, and a mass of other useful components. In good condition. PRICE ONLY 65/-, or less valves. PRICE ONLY 37/6. Carriage 6/-.

VALVE BARGAINS.—All as new and guaranteed. 1T4, 1R5, 1S5, EP91, 6AM6, 6L34, 6K7metal, 6B8metal, all at 7/6 each. 6SH7metal, 5/-, 6H6metal, 3/-.

0/1A AMMETERS, A.C. or D.C.—First-grade meters as new, in maker's cartons. Moving iron type, 4 1/2in. dia. SPECIAL PRICE ONLY 12/6, post 1/3.

COVENTRY RADIO

189, DUNSTABLE ROAD,
LUTON, BEDS.

Phone : Luton 2677

The Quality Component
Specialists offer you Kits of
Parts for the following :—

Osram "912" Amplifier	... 3/6	Manual
Mullard 10-watt Amplifier	... 3/6	
The Coventry		
2-watt Amplifier	...	} 1/-
4-watt Amplifier	...	
6-watt Quality Amplifier	...	
The Coventry A.M. Tuner Unit	1/-	
Denco F.M. Tuner Unit	... 1/6	

Complete Component Price Lists will be supplied with each Manual.

Have you had a copy of our 1954/5 60-page illustrated Component Catalogue, price 1/- plus 3d. postage?

requirements. It is fitted with weighted straps for holding the instrument securely to the arms of a chair, and it is finished in an attractive grey colour. One model I have seen, used by a friend of mine, even incorporates A.V.C., and my friend has been using it for some years.

So you see, sir, the article you mentioned in the April edition is not a new item, for I saw them at least two years ago.—C. R. JONES (Barry).

SIR,—We were very interested to read in your April issue an article on the radio and television attachment for use by the hard of hearing. We would like to say how, as manufacturers of hearing aids and attachments for the deaf for over 20 years, we entirely agree with the opinions expressed in this article, and we thought that it might be of interest to your readers, or to yourself, to know that we have been marketing a special device for television and radio listening, since May, 1953, and that the attachment in question, the Adaphone, was a modernised version of an attachment, bearing the same name, which we introduced in 1936. This was written-up in *Practical Wireless* on October 3rd, 1936, some of these attachments still being in use.

I thought this bit of history might amuse you. You will see, however, from our leaflet that the modern version which still incorporates automatic volume control is very similar and neater than the original.—B. MONTAGU (Hearing Aid Department, Multitone Electric Co., Ltd.).

PICTURE TUBE FAULT

SIR,—With reference to the problem published in the April issue of PRACTICAL TELEVISION of Mr. M. Gibson, of London.

It may be of considerable interest to him and perhaps others to learn of my experience with a picture tube fault which was almost identical with the failure he experienced. Like him, I had a C.R.T. in my set which developed an inter-electrode short, which on first sight appeared to be a cathode-heater short. As in his case, I fitted an isolating transformer with no improvement. The emission of the tube was quite good, however, and in order to reduce to some extent the strain between electrodes I tried reducing the heater voltage on the tube. This did

CORONA DISCHARGE

(Continued from page 542)

These may be cut from 1in.-wide strips of brass, but the edges should be rounded and the ends also should be clipped and rounded. Similarly, if a glass tube is used, and the lead is soldered on to a top-cap connector, the lead should not be soldered flat to the side of the connector but placed end on and surrounded by a large round blob of solder. For a similar reason the valveholder used for the line output valve and the recovery diode should also be chosen with care, as the discharge may take place between adjacent pins, and cases have been known where the actual material between certain pins has been charred, giving rise to a conducting surface (carbon) which has eventually resulted in ordinary electrical flash-over and the ruin of a valve. It should be emphasised that all the above precautions are not essential, but to avoid any possibility of later trouble it is worthwhile taking every precaution to prevent corona in every part of the E.H.T. circuit.

the trick, although the focus was slightly impaired. It was necessary to move the focus magnets forward. There still remained, however, a severe disturbance in the background on dark scenes. This I eventually cured by decoupling the accelerating anode to earth via a 0.1 μ F condenser.

The tube in my set is a Mullard MW31-16, and I reduced the heaters to about 5 volts.

Trusting this will be of some value and interest.—R. G. JAMES (Stoneycroft).

PRICE OF HOME-CONSTRUCTED TELEVISION SETS

SIR,—I should like the opportunity of answering the points raised by Mr. Simpkins and Mr. Sanders in their letters to you which appeared in the March issue of PRACTICAL TELEVISION.

We have, in fact, taken much care to produce a 15in. high-quality television kit, specially for the television student and constructor, which we feel is offered at a reasonable price. All the parts are of brand new manufacture and, to assist in one of the main difficulties, we can supply the R.F. unit ready assembled and aligned. The total price, without tube, of approximately £40 represents the one-third decrease on the equivalent retail figure, as mentioned by Mr. Simpkins.


We also sell this kit on the instalment system which should make it fully comparable to the purchase methods employed by the retail trade.

Students who have constructed this receiver, under our guidance, have all commented on its excellence and suitability for home construction.—P. T. V. PAGE (Director of Studies, E.M.I. Institutes, Ltd.).

BAND III RECEPTION

SIR,—In your comments in the March issue you state that the second aerial will cost £15 to £20. Pye are supplying their agents with aerials that cost £2. Also you state that you can only convert 25 sets a week. I have fitted tuners to Pam sets 954, 952, 953 and Invicta 118, 120. These have been 13 channel units and I have not hurried over them and they took on average two hours, so on the assumption that I worked on converters all day the number will be far above the one that you state.—DAVID D. MALYON (Branch Manager, Arion Television).

A case of corona recently investigated arose from a projecting ceramic pillar terminal on a commercial transformer. This was situated near the line output valve, and the lead had fractured just beyond the connecting point. The corona discharge in this case was in the form of a thin pencil about $\frac{3}{8}$ in. long aiming at the line output valve. A sheet of glass was placed between the terminal and the valve, and the pencil pierced the glass as though it were not there. A sheet of a plastic material was then placed in the way, and this melted after some time in the shape of a jagged hole. A special wax material was then placed round the joint and effectively stopped the discharge. This material is commercially available, but should not normally be necessary if the precautions mentioned above are taken. Ordinary petroleum jelly will stop the discharge, but unfortunately will melt and run from the point due to the normal temperature rise inside the average set. Hard wax removed from an ex-Government transformer, for instance, will also keep it down, but in some cases it may not prevent it entirely.

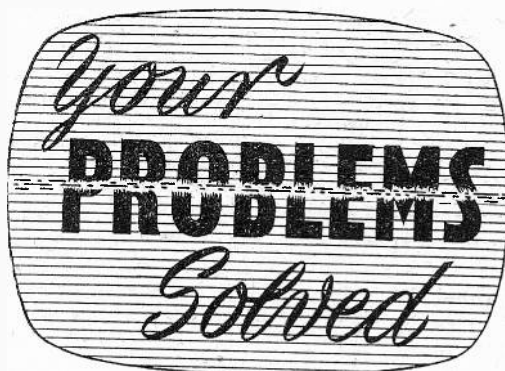

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 575 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

MURPHY V200

My Murphy V200 TV has developed a fault in vision. Sound is in order, and tube heater is lighting up as normal. E.H.T. whistle is normal, too.

The fault was preceded by black lines flashing across the screen, and a crackle on sound that was similar to interference from an electric motor. Then it got very intense, and the screen went black. I can't get the screen to light up at all, by means of the brightness, contrast or sensitivity controls. Could the fault be in the vision interference limiter circuit? This has not seemed too good for a while, the adjustment being at position giving maximum interference. This had to be adjusted like this or flattening of the highlights was present. Even on this position the contrast couldn't be turned up too much or the highlights would become flattened.—A. Gwilym Davies (Flintshire).

The effects which preceded the final black-out are symptomatic of a collapse of insulation in the picture-tube. A fault of this nature would cause the tube beam current to rise considerably and show as intense illumination on the screen. Moreover, the final fade out may have been caused by failure of a weak component in the E.H.T. circuit, which could not stand up to the strain of the heavy beam current.

We would, therefore, advise that you first of all ensure that the picture-tube is up to standard, and then go on to investigate the E.H.T. section.

We would point out that the progressive alteration in the characteristics of the vision interference limiter might well have been aggravated by a gradual reduction in tube emission.

MARCONI VT53A

I have a Marconi Model VT53A, London only, T.R.F. I would like to use a converter or modify to receive Channel 3, i.e., Norwich transmitter.

Would the Cyldon 5 Channel tuner suit? If not, do you know of any that would, or details to modify?—C. R. Woodard (Norwich).

The Cyldon 5 Channel tuner is totally unsuitable for the modification you have in mind. Channel converter units for this purpose can be obtained from

Spencer West, of Quay Works, Great Yarmouth, Norfolk.

BUSH 24A

My Bush receiver has developed the following faults, which no doubt can all be attributable to one cause.

(a) Kinks in the lines and fly-back lines on the left of the picture.

(b) White vertical bars about half an inch wide, pronounced in the top left-hand corner, gradually decreasing in intensity towards the middle of the picture.

(c) A kind of halo effect on the right-hand side of the picture subject, giving letters and figures the appearance of depth.—E. E. Butcher (Leigh-on-Sea).

These symptoms are probably caused by a fault in the damping diode circuit PY81 (V10 Trader Service-sheet). You should have the condition of this valve checked, and replace it if necessary. You should also check the condition of the associated 0.1 μ F reservoir capacitor in the anode circuit of the PY81. Also ascertain that the line amplifier valve PL81 (V8) is well up to standard.

PYE FV1

I shall be most grateful if you will advise me on a fault with my Pye FV1. E.H.T. at the tube anode is non-existent. I have had EY51 tested also PL38 (line output) and proved O.K. I have also discovered that V14 (line oscillator) is overheating and also that a blue glow is present on the PL38.

I suspect the line output transformer as being the cause of the E.H.T. fault and, if this is so, could you inform me as to where I can obtain a replacement.—J. Ward (Rotherham).

The symptoms mentioned are consistent with line output transformer trouble. It will be necessary to install a correct replacement component, which can be obtained only through a Pye agent.

ULTRA T22

When I switch on all I get is a bright spot about 3in. in diameter.

I do not know a great deal about them but I am willing to learn. I would also like to know if it is possible to change it to a larger tube. It now has a CRM92 9in.—T. Dodkin (Edgware).

Your trouble is almost certainly due to the absence of H.T. on the timebase H.T. rail (terminal N8). You should check along this line from the H.T. point in an endeavour to discover where the fault lies. Check C6 for insulation.

You could use a CRM121 12in. tube in the receiver, but this would probably give a slightly less brilliant picture than a new CRM92.

BUSH TV22

My picture has developed a distinct slant from the horizontal. Whilst the screen can be filled by stretching the picture, any writing on the screen has a definite slope down to the left of the screen. Can you please tell me how to correct this fault?—A. Cudmore (Colchester).

The alignment of the picture on the screen is controlled by the position of the scanning coils. These are situated on the neck of the picture-tube, behind the focus unit. The coils should be very carefully twisted to correspond to alignment of the picture;

BRAND-NEW: R.F. Units, types 26 or 27 27/6, 24 12/6, postage 2/4 each; Receiver 161; Valves, 1/CV66, 1/VFR37, 2/VVR136; VHF Tuning Unit, 17/6; Dipole Aerial Insulators for 3in. rods, flat fixing, 5/6; Co-axial c/o Relays, 12/24v, 8/6; Wire-wound Pots, range 1k to 100k, each 2/6; carbon, 1/6; Condensers, bak. tub., 0.25mf, 1.5kV, 2/-; Hunts .001, .01, .1mf, 500Vv, 5/- doz.; Metal Recs. HW, 600v 30ma, 350v 80ma, each 6/-; cash with order; post extra. S.A.E. for lists/enquiries. W. A. BENSON, 308, Rathbone Rd., Liverpool, 13.

R.F. UNITS, Types 26 at 27/6, 25 at 12/6, 24 at 11/-; brand new with valves; post 2/6. E.W.S. CO., 69, Church Road, Moseley, Birmingham.

JIM'S RADIO COMPONENTS, 23, Alexandra Rd., Sleaford, Lincs. Send s.a.c. for free price lists and order forms.

CONDENSERS, .1mf, 2,500v, d.c. wkg., 4 1/2in. x 2 1/2in. x 1in., 5/6 ea.; .1mf, 1,500v, 2/6; 4mf, 2,000v, wkg., 7/6 (4 1/2in. x 3 1/2in. x 3in.); tubular metal-cased wire ends, .002mf, 350v, 6d.; 005/500v, 8d.; .05/500v, 1/-; .1mf, 150v, 1/-; dark screen, 14 1/2in. x 1 1/2in. x 1in., 6/-; chimney mounting Aerials with lashings, "H" 55/-; "X" 55/-; Dublex 88/6; single dipole, 40/-; single dipole for fascia board or window mounting, 20/-; indoor roof type, 15/-; co-axial, 9d. yard. **GLADSTONE RADIO**, Gladstone Place, Newton Abbot, Devon.

SERVICE SHEETS, T.V. and Radio, over 2,000 models, sale or hire, Valves and Components. S.A.E. with enquiries W. J. GILBERT, 24, Friehville Gardens, London, W.12.

TV WITHOUT MAINS.—Absolutely first-class picture, plus DC circuit for lighting; as supplied to the B.B.C. Special AC/DC "Chorehorse" Generators, self-starting, compact, and complete. AC 220/250 volts, 50/60 cycles, 250/350 watts AVC. Will run radios, vacuum cleaners, small tools, etc. £47/10/-, plus 10/- delivery. Below:—

STORAGE BATTERIES, 12v, 75Ah heavy duty, 19 plates, separate cells in hardwood cases; finest possible specification. £5/17/6, 9/6 delivery; 12v, 22Ah almost similar specification, surprisingly powerful. £2/14/-, delivery 5/6. **TEDDINGTON ENGINEERING CO. LTD.**, Dept. "C", High St., Teddington, Middx. (Kingston 1193-4.)

VIEWMASTER TV Soundmaster Tape Recorder. Ostram 912 amp. All specified components in stock. Stamp details. **FRANKLIN & HALL**, 371, Havant Rd., Farnlington, Portsmouth.

TV SIMPLEX COILS, 21/-; TV 3in. Canned Formers, 2/3 ea. BEL, Marlborough Yard, Archway, N.19. (ARC 5078.)

THE CHEAPEST BLANK All Chassis. Made in bright 18g. All with sides and narrow end turned in and down 1in. for maximum strength and rigidity. 7 x 4 x 2 3/4, 9 x 5 x 2 1/2, 10 x 6 x 2 1/2, 4/6, 10 x 8 x 2 1/2, 5/-, 12 x 8 x 2 1/2, 5/6, 12 x 9 x 2 1/2, 6/-, 14 x 9 x 2 1/2, 6/6, 15 x 9 x 2 1/2, 6/9, 16 x 8 x 2 1/2, 6/9, 16 x 10 x 2 1/2, 7/3, 17 x 9 x 2 1/2, 7/3, 17 x 12 x 2 1/2, 8/6. Other sizes made to specification. Any length up to 17in., any width up to 12in., any depth up to 3in. Price: 1d. per sq. in. of the top surface only, ignoring depth. Fractional sizes should be taken to the next whole No., e.g., 10 x 6 1/2 x 2 = 10 x 7 = 7d. in. = 70d. = 5/10. **SERVIO RADIO**, 156/8, Merton Rd., Wimbledon, S.W.19. (LIBerty 6525.)

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1, extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

RADIO UNLIMITED offer guaranteed new Valves: 1L4, 3A4, DF92, EB91, CV875, CV286, EF36, 6K7G, 1T4, 1S5, 6J5M, 6K7M, all at 5/- each, post free: U329, 6V6M, 6SL7, 6SN7, EB333, 5U4G, 6BE6, 7/- each; 1A7 and 807, 8/- each; 9D2, 8D2, 3/6 each; 17,000, Valves in stock. Lists free. Iso/trans., 1-to-1, 25% boost, 2v, 4v or 6v types, 6/3 each; door-rod Aerial, with co-ax lead, 17/6; Co-ax Cable, 70/80 ohms, 8/6 doz. yds.; 3-wave Coilpacks, 1. in. and s., 21/-.

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Bullington Rd., Oxford.

VALVES, 6 months' guarantee, discount on orders over £1. Well-known maker. Send 5d. for list of over 70 types, including operating "gen." pin connections, prices, etc. **BLANCHARDS** (PT1), 13, Gainford Gardens, Manchester, 10.

2-VCR 97 CRT-EHT Chassis, mag. mask, glass, working order, £8, offers. **BURT**, LAB 2377.

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempt from the provisions of the Notification of Vacancies Order, 1952.

TELEVISION TECHNICIANS—all districts. Big money for you in your spare time. Opportunity to establish your own business. Write, giving fullest particulars of training, experience, whether owner of test equipment, age. All replies treated in strictest confidence. Apply to **TELEPATROL LTD.**, Federation House, Epsom.

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or in fact, anything that needs lenses. Then get our booklets "How to Use Ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D With Viewers," price 7/6. Comprehensive lists of lenses, optical, radio and scientific gear free for s.a.c. H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.

"VIEWMASTER" valves, exact to specification, guaranteed new and boxed, set of 12 £5/15/-; "Tele-King," complete set of 17, £8/19/6; 14v miniatures: 1S5, DAF91, 1R5, DK91, 1T4, DF91, 5S4, DL92, DK92, any 4 for 27/6, post 1/-, all new and boxed. For individual prices and other types see displayed advert., page 570. **READERS RADIO**, 24, Colberg Place, Stamford Hill, London, N.16. (STA 4587.)

SIMPLEX T.V. 18 swg Chassis, with screens and valve punched, 17/6, post 1/6; fully wound Coil Sets, 15/-, post 1/-; Simplex Mains Transformer, 27/6, post 2/-; Magnetic Chassis and Screens, 22/6; 0.1 µf 2.5 kv wkg., 7/6; Rectifiers, RM5, 5/9; 3K/40, 6/-; 14-way Tag Boards, 2/-; List for other items. **LYNX** wound Coil Sets, 35/-, post 1/-; **C.O.P.Y. WINDINGS**, Healey Lane, Batley, Yorks.

DIRECT T/V REPLACEMENTS offer the most complete Handbook of T/V Components and Rewinds, price 1/-; T/V Components for all kit sets in stock. "Nuray" heater booster isolator for 2-volt C.R.T.s, just plugs in, 27/6, plus 2/- packing and postage. 134-136, Lewisham Way, S.E.14. (TIDeway 3696-2330.)

WINWOOD for Value. New Valves, 6V6, 6K7, 6K8, 6Q7, 5Z4, 31/- set; 1T4, 1S5, 1R5, 35A, 29/- set; ECL80, 8/6; EF39, EBC33, 6SL7, 6SN7, 6V6M, 5U4, 1A7, 7/6 each. W.V. Contrs., 5K, 3-watt, 3/-; Fresh stock 16 x 16mf-500v, 3/9; 32 x 32-450v, 4/6; 0.1-500v, 7/6 doz.; 0.05-500, 7/6 doz. Lists. **WINWOOD**, 12, Carnarvon Road, Leyton, E.10. (Mail only.)

VALVES

VALVES WANTED, all types, state quantity, condition and prices asked. **R.H.S. LTD.**, 155, Swan Arcade, Bradford, 1.

WANTED VALVES, 5Z4, ECL80, EY51, EF90, KT66, 6U4GT, KT61, and all T.V. types, also P.M. Speaker Units, 3 1/2in., 5in., 6 1/2in., 8in., 10in.; prompt cash. **WM. CARVIS LTD.**, 103, North Street, Leeds, 7.

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcot Road, N.W.1. (PRImrose 9090.)

EDUCATIONAL

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest electronic organisation; moderate fees. Write to Dept. PT28, E.M.I. INSTITUTES, London, W.4.

I.P.R.E. Data for constructing TV Aerial-strength Meter, 7/6; 5,500 Alignment Peaks for superhets, 5/9; sample copy "Practical Radio Engineer," 2/-; Membership-examination particulars, 1/-; Syllabus of seven postal courses free and post free. **SECRETARY**, I.P.R.E., 20, Fairfield Road, London, N.8.



PULLIN
SERIES 100
TEST METER

AC/DC 10,000 v/v
21 RANGES
100µA to 1000V

COMPLETE IN DIE-CAST CASE WITH TEST LEADS
CLIPS AND PRODS
FULLY GUARANTEED

SENT POST FREE FOR **£2.10s.**
DEPOSIT AND TEN FURTHER MONTHLY PAYMENTS OF £1. CASH PRICE 11GNS

Frith
RADIOCRAFT Ltd
69-71 CHURCH GATE LEICESTER

RADIO AND TELEVISION COMPONENTS

All parts in stock for: **VIEWMASTER, SOUNDMASTER, TELEKING, ETC.**

Easy Terms Available.
Stamp for list, NOT S.A.E.

JAMES H. MARTIN & CO.
Finsthwaite, Newby Bridge,
Ulverston, Lancs.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British & American Technical Books

Television Engineers' Pocket Book, edited by E. Molloy & J. P. Hawker. 10s. 6d., postage 4d.

Electronic Musical Instruments, by R. H. Dorf. 55s. 0d., postage 1s. 0d.

The Radio Amateur's Handbook: 1955, by "A.R.R.L." 30s. 0d., postage 1s. 0d.

Basic Television: Principles & Servicing, by B. Grob. 45s. 0d., postage 1s. 0d.

Radar Pocket Book, by R. S. H. Boulding. 15s. 0d., postage 4d.

The "Lodestar" Tape Recorder, by A. S. Torrance. 3s. 6d., postage 3d.

Practical TV Aerial Manual for Bands I & III, by R. Laidlaw. 4s. 6d., postage 3d.

The A.R.R.L. Antenna Book. 14s. 0d., postage 9d.

Transistors & Crystal Diodes, by B. R. Bettridge. 5s. 0d., postage 3d.

RC A Receiving Tube Manual. 8s. 6d., postage 4d.

Television Explained, by W. E. Miller. 5s. 0d., postage 6d.

Radio Valve Data: 4th edn., compiled by "Wireless World." 3s. 6d., postage 3d.

Please write or call for our catalogue.

**19-23 PRAED STREET
(Dept. T.5) LONDON, W.2.**
*Phone: PADDington 4185
Open 6 days 9-6 p.m.

MAIL ORDER DEPT.

TELEKIT SUPPLY

Chantry Lane, Bromley, Kent.

Please mention P.T.V. and enclose 6d. postage
VALVES, NEW & SURPLUS, GUARANTEED.

OZ4	4/-	6B8	7/-	11D9	6/-
11A	5/6	6B126	6/-	12BE5	6/-
11N5(soft)	6/-	6BR7	8/6	12AS 1299	5/6
IS5	6/-	6BS7	7/-		
1T4	6/6	6BW6	6/6	15D2	4/-
1U5	6/-	6C5	5/-	EP50	5/-
3V4	6/6	6X4	6/6	6AK6	6/6
5703	3/-	6X5	7/-	6AQ5	8/-
6A3	3/-	6D5	6/-	6U5	6/-
7T11	8/-	6D6	6/-	12AT6	7/6
GAM5	6/-	6D7	6/-	13D1	7/-
6AT6	7/6	6D2	3/-	60C5	3/-

BECKENHAM, KENT
THE SHOP FOR THE CONSTRUCTOR
NOW OPEN AT 104, HIGH STREET,
BECKENHAM 3720

TELEVISION COMPONENTS

always in stock for the
**P.T. LYNX, TELE-KING
P.T. SUPER-VISOR
THE E.E. TELEVISOR
VIEWMASTER
AND WIDE ANGLE
MODIFICATIONS**

Separate price lists available free on request to

J. T. FILMER,
Maypole Estate, Bexley, Kent
Tel.: Bexleyheath 7267

Bentley Acoustic Corp. Ltd.

38, CHALGOT ROAD, N.W.1.

PR11mrose 9090

BUDGET REDUCTIONS

0Z4	6/-	6SH7	6/-	210LP	3/-	KP35	9/-
1A5	6/-	6SJ7	8/-	213SG	4/-	KL35	9/-
1B7	8/6	6AK7	6/-	311SU	9/-	KT2	5/-
6/6	6SL7	8/-	451PT	9/6	KT4	7/6	
1G6	6/6	6S87	8/6	71TA	8/6	KT71	12/-
11A	6/-	6S87	7/6	807	7/6	KT74	12/-
11A4	9/6	6U5(UX)	7/-	813	7/6	KT76	12/-
11LD5	4/6	6U5(TO)	7/6	832	25/-	KTW62	5/-
11LN5	4/6	6U7G	8/6	866A	12/6	KTZ4	6/6
1M1	12/6	6V6GT	7/6	885	7/6	LP2	4/6
1R5	7/-	6X4	7/6	1203	3/6	MP4	5/6
1S3	7/-	6X5	7/6	5763	9/-	ML5	6/6
1T4	4/-	6Y6	8/-	7193	2/6	N77	7/6
2D13C	8/6	6Y7	15/-	9601	5/8	N142	9/6
2D21	4/6	6Z4	10/6	9902	5/8	N150	10/6
3A4	7/6	7A7	8/6	9003	5/8	OC2	9/6
3B7	8/6	7B7	7/6	9006	6/-	OD3	8/6
3D6	2/6	7C5	7/6	AC/HL	6/6	OM3	7/6
3S4	7/-	7C6	7/6	AC/P	7/6	OM5A	10/6
3V4	8/-	7D3	8/-	AC/P4	8/-	OM5B	10/6
4D1	3/-	7E7	7/6	AR3(A)	5/-	PC24	10/6
5U4	8/-	7Q7	8/6	ATP3	3/-	Pen 25	9/6
5X4	8/6	7R7	8/6	ATP4	3/-	Pen 48	7/6
5Y3	7/6	7V7	8/6	BL63	7/6	Pen 46	7/6
5Z3	8/6	7Y7	9/-	B52	9/-	Pen 1340	6/6
6B3	8/6	8A8	13/-	R309	9/-	PL1	10/-
6A3	10/6	8D2	9/6	R319	10/6	PL2	9/6
6A7	8/6	8D3	6/6	CB11	17/6	PL3	11/6
6AB7	6/-	10C1	9/6	D77	6/-	PM12	4/6
6AB8	10/-	10D1	4/6	DAPF1	7/-	PM12M	7/6
6AC7	6/6	10F9	8/6	DPF1	7/-	PY80	9/6
6AG5	6/6	10LD3	9/-	DP93	6/-	PY81	10/6
6AG7	10/-	10LD11	10/-	DE30	15/6	PY82	7/6
6AK5	7/6	10P13	9/6	DH77	8/-	QP21	7/6
6AL5	6/-	12A6	6/6	DH142	9/-	Q895/1010/6	
6AM5	6/6	12AH7	12/6	DH150	10/-	Q875/2010/6	
6AM6	6/6	12AT6	10/6	DK92	7/-	Q8150/13	
6AQ5	9/-	12AT7	7/-	DL2	8/6	QVO47	10/6
6AT6	8/-	12AU7	9/-	DL33	8/-	OK37	2/6
6B4	6/-	12AX7	7/-	DL94	7/-	RK31	9/6
6B7	7/6	12BA6	9/6	DL810	10/6	RL7	2/-
6B8G	4/-	12BE5	6/6	EL148	2/-	RM4	12/-
6B8M	4/6	12BH7	12/6	EA50	2/-	S130	5/6
6BE5	6/6	12E1	30	EA75	3/6	SP47	2/6
6BOG	12/6	12E6	3/-	EAC91	9/-	SP61	2/6
6B76	6/6	12J5	6/-	EB34	2/-	SU61	11/-
6BQ5	10/6	12K8	8/6	EB41	11/-	TP22	8/6
6B77	9/-	12SCT	7/6	EB91	6/-	V25	12/-
6BW6	7/6	12SG7	8/6	EB95	10/6	U31	8/6
6BW7	9/6	12SJ7	7/-	EB9C3	9/-	U30	7/6
6BX6	10/-	12SK7	6/-	EB41	10/-	U52	3/6
6C4	7/6	12SQ7	8/6	EC91	7/-	U78	7/6
6C6	6/6	12SR7	7/6	EC82	5/6	U142	9/6
6C8	3/6	12U4	6/6	EC93	9/-	U30	8/6
6C10	10/-	14H7	10/6	EC93	9/-	U30	10/6
6CH6	6/6	14R7	10/6	ECC81	9/-	U154	10/6
6D6	6/6	16A5	9/6	ECC82	10/6	U319	8/6
6F6M	7/6	17J23	10/-	ECC91	7/6	U320	10/6
6F8	7/-	18	8/-	ECH42	10/-	U404	9/-
6F11	6/6	19H1	10/-	ECL89	10/-	UAF42	12/6
6F12	6/6	19Y3	7/6	EF22	9/-	UBC41	9/6
6F16	9/-	25L6	8/6	EF36	4/6	UCH42	9/6
6F17	9/6	30	7/6	EF37	10/6	UP41	8/6
6F22	6/6	35L6	8/-	EF57A	10/6	UL41	9/6
6F23	6/6	35W4	7/6	EF59	6/6	UL44	20/-
6G5(PX)	7/-	35Z1	8/6	EF41	9/-	UL46	7/6
6G6	6/6	35Z5	8/6	EF50(A)	8/-	UO9	9/6
6H6G	2/6	42	8/-	EF50(B)	5/-	UX41	9/6
6H6M	3/6	32MPT	15/-	EP4	5/-	VL8492A	
6H74	5/-	50C5	10/-	EP7	10/6		£30/0
6J5M	6/-	50L6	8/6	EP9	10/-	VP27	7/6
6J6	7/6	50Y6	8/6	EP91	6/6	VP40	8/6
6J7G	5/-	57	8/6	EP95	7/6	VP18K	7/6
6K6	7/-	58	8/6	FL32	6/6	VP23	6/6
6K7G	5/-	62DDT1	10/-	EL41	10/6	VR33	5/6
6K7M	6/6	62TH	10/-	EL50	20/-	VT501	6/6
6K8G	6/6	62VP	9/-	EL84	10/6	VU111	6/6
6K8GT	8/6	64ME	10/6	EL91	6/6	VU120A	3/6
6K8M	9/-	66KU	8/6	EM34	10/-	VU133	4/6
6L6	7/6	67PT	10/6	EY31	11/-	W142	8/6
6L6G	9/-	74	4/6	EY91	7/6	W145	8/6
6L7	7/6	75	8/6	EZ40	8/6	W150	9/6
6LDR	10/-	76	7/-	EZ41	9/-	X36	7/6
6N7G	7/6	77	8/6	H30	7/6	X142	9/6
6N7M	8/-	78	8/6	H12	3/-	X150	10/-
6P4	8/6	80	8/-	HLL3C	7/6	XH(1.5)	4/6
6R7	8/6	83A2	10/6	HLL3DD	6/6	Y32	7/6
68A7	8/-	121VP	8/6	HL41	7/6	Z27	7/6
68CT	10/-	141DDT	9/-	HLL320	6/6	Z710	10/-
68G7	6/6	141TH	9/6	KBC32	8/6		

Shop hours 8.30 to 5.30, Sats. 1 p.m.
Phone or wire that urgent order for immediate despatch C.G.D.

FIRST-CLASS TELEVISION and RADIO COURSES

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.C. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.S., (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc.,** together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

CASCADE TYPE T/V PRE-AMPS

NOW PROVING VERY POPULAR

Manufactured specially to suit fringe and ultra-fringe conditions. In use 140 miles north of Kirk O'Shotts, check our position and in many other distant locations and difficult reception areas. Complete in cracked steel case with built-in power-pack 200-250 A.C., 255V-. Also available, less powerpack, for inclusion in 15 or 3 amp heater chains.

£2.17.6

State heater current and channel used, or send 6d. stamp for illustrated details and some interesting fringe data.

ELECTRO-A COUSTIC LABS., TAIN—ROSS-SHIRE—SCOTLAND

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.
6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:
36, ROSEBERY AVE., LONDON, E.C.1.
Branches at Liverpool, Manchester, Birmingham, Leeds.
"No Quantity too Small!"

It is best to perform this adjustment directly after the receiver is switched off, while the inside is still warm.

PYE VT4

I have a Pye VT4 and have noticed the following faults.

(1) When the vernier fine tuner is adjusted to give maximum definition it introduces severe ringing and sound on vision. Is this due to misalignment of the tuned circuits, or is this an inherent fault with this receiver?

(2) After being in operation for approximately 30 minutes a convex gap is noticeable at bottom of frame. Your help and advice in these matters will be greatly appreciated.—N. D. Healey (Bristol).

(1) This is quite a normal occurrence; the fine tuning should be adjusted for maximum sound, consistent with minimum sound interference on vision and optimum definition. A compromise between definition and "ringing" is generally necessary. If this condition cannot be achieved the vision I.F. stages may be in need of re-alignment.

(2) This effect is probably caused by an alteration in the characteristics of the frame timebase valve as it increases in temperature. It is sometimes aggravated by the receiver's mains adjustment not corresponding closely to the local mains voltage. You should check these points.

G.E.C. BT4542

Could you please help me with a fault which has developed in my G.E.C. BT4542 television receiver, Holme Moss frequency?

The set was switched off after working normally, and on switching on the following evening there was a complete loss of picture.

The raster is quite normal and I have had all the valves in the video strip tested, and they are O.K. The vision detector and noise-limiter in the above section are crystal diodes. What effect would either of these diodes have if faulty? And is there any test which I could apply to them? At times it is possible to see a very faint picture on the raster.—F. Bowman (Knutsford).

We presume that the sound channel is unaffected by the fault on vision. If this is the case then the trouble lies somewhere in the vision I.F. detector stages. It is unlikely that the video amplifier is at fault, as you are able to obtain a raster. Your best plan of action would be first to check the potential on the electrodes of the vision I.F. valves, making sure that the voltages are more or less normal. Assuming that they are, and that the valves are up to standard, the vision detector stage should come under suspicion.

The crystal diode becoming defective would give rise to the symptom, and this does sometimes happen on your receiver. There is no really satisfactory test for this component; by far the best is by substituting with a component of known goodness.

SIMPLE TV 'SCOPE

I am starting to build the 'scope shown in the August, 1954, issue of "Practical Television" (page 119), but using a different C.R.T.—a VCR517B (10E/818). I have completed the E.H.T. exactly as shown in

Fig. 1, except that I have reversed the polarity of MR4 and MR5, which surely are drawn wrongly.

I could not get the tube to emit, although I used the brilliance and focus controls throughout their range, so I replaced R7, R17 and R16 with variables of 1 m., $\frac{1}{2}$ m. and 2 m. respectively. The tube did then emit, but only when R17 was zero (then R7 had no control). I obtained better results when I interchanged pin 1 and pin 2 connections on the tube, but even then the best "picture" I got was about $\frac{1}{4}$ in. diameter. Can you please give me the C.R.T. circuit for my tube, and can I expect to get a pin-point?—E. Jones (Gosport).

You should be able to get a pin-sharp trace with the VCR517. It is possible that you have a fault in the E.H.T. network, or a resistor has changed its value in this network. Try varying the values and check very carefully for possible leakage, especially via spindles of the shift controls.

FERGUSON 983T

Could you please tell me how to reduce picture width on my Ferguson Model 983T?

I have the plug in minimum position, but the picture overfills the screen—by how much I cannot say—and this has only been so since a service engineer replaced the line-output transformer with a new one which, incidentally, was obtained from Ferguson, and to outward appearances at least looks to be the same as the old one.—E. Walker (York).

This symptom almost certainly means that the replacement transformer's tolerance is outside that stipulated by the manufacturers for optimum performance. If you are certain that the E.H.T. rectifier valve is up to standard and that the width adjustment is correctly positioned, then we feel that it would be to your advantage to have your dealer rectify the trouble for you.

A "K" AERIAL

I wish to construct a type of aerial which I have sometimes seen made in the form of a capital K. Can you please tell me whether the reflector should be insulated from the mounting bracket, or is it permissible for the lower arm of reflector to be longer than the upper and be made part of the mounting bracket? Can you also suggest the best angle between dipole and reflector arms and suitable lengths of both for Channel 5.—W. Prewett (Salisbury).

Theoretically, it is desirable to insulate the reflector from the chimney bracket. In practice this is not very often done, however, and the performance would appear to be little affected.


There is no critical angle between dipole and reflector, though a satisfactory figure is something like 45 deg.

The dipole should have an overall length of 7ft. 1in. and the reflector 7ft. 7in.

QUERIES COUPON

This coupon is available until MAY 21st, 1955, and must accompany all Queries.

PRACTICAL TELEVISION, MAY, 1955.

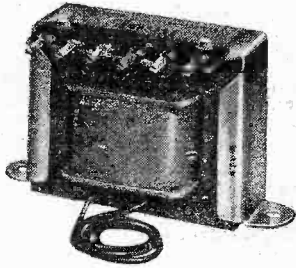

Forrest COMBINED BOOSTER AND ISOLATING TRANSFORMERS

Cheap and easy to fit to any Receiver, they enable Tubes with low emission or with Cathode-Heater short to be used again. Supplied in any voltage from 2v.—13.3v.

OPTIONAL BOOST (12½% and 25%).

Price 21/- (Retail)

H. W. FORREST

349 HASLUCKS GREEN ROAD
SHIRLEY, BIRMINGHAM. SHI. 2483

WE SPECIALISE ONLY

IN

RADIO COMPONENTS—

LET US QUOTE YOU BY
RETURN FOR ANY RADIO
VALVES OR PARTS YOU
REQUIRE

HIRE PURCHASE TERMS ON KITS,
INSTRUMENTS, ETC.

Osram "912" and Mullard "510"
Amplifier Parts in Stock.

NEW CATALOGUE WITH H.P. TERMS 6d.
QUOTES S.A.E.

RADIO SERVICING COMPANY

82 SOUTH EALING ROAD
LONDON W.5 EAL. 5737

NEXT DOOR SOUTH EALING TUBE STATION (TURN LEFT)

Telex: GRA 6677
DUKE & CO
CWOI
COD
621 ROMFORD RD. LONDON. E.12.

RADIO-GRAM CHASSIS 29/9. Including Speaker.

5 valve s/het., 3 w/band, A.C. mains, complete, but less valves and dial. All used, tested guaranteed. P. & P. 4/6. Drawings 2/6 or free with order. Knobs, 1/6 set extra. Complete with valves, 97/6.

RADIO CHASSIS, 7/9. A.C. or universal s/het. receivers. Less valves, dial and electrolytics. Otherwise believed to be in working order. Note:—our 8in. M.E. speaker fits some of these sets. We match on request with order. P. & P. 3/6.

RADIO CHASSIS, 14/9. As above, with 3-band coil packs, 485 I.F.s. All used bargains. P. & P. 3/6.

SPEAKERS, 12/9. 8in., 6in., 5in. or 3½in. std.: P.M. 3-5 ohms, or with O.P. trans. 14/9. Used, tested guaranteed. Post 1/3.

SPEAKERS, 2/9. 8in. M.P. field lk. 2k. 5k ohms. With O.P. trans., 4/9. Post 1/3. Used, tested guaranteed.

V.H.F. RECEIVER, 1124. 17/6, with 6 valves, X.W.D. New condition. 6 channel switching. Receives T.V. sound, police, fire and amateurs. 30.5 to 40 mc/s. I.F. 7 mc/s. Post 2/6. Drawings and conversion data free with each set.

V.H.F. 1125 SET, 7/9. New and boxed. This little set is a V.H.F. receiver. Requires modification to put it into service. Complete with valves. Post 2/-.

R.F. UNIT 24. 12/6. New and packed. tuning 20-33 mc/s.

Including valves. Post 2/6.

T.V. TUBES AND P. CHASSIS. We hope to accept your further orders this month, after we have completed your overwhelming response to previous ads. We are sorry for the past delay in despatch.

(O.P.) TRANSFORMERS, 1/9. Used, tested, guaranteed. Std. size. Post 9d.

2 GANG CONDENSERS, 2/9. Std. size .0005, used, tested guaranteed. Also 3 gang, 2/9; post 9d.

T.V. CONDENSERS, 12/6. Electrolytic. 123 mfd., +64 mfd. 350 volt. Post 1/-.

MAINS TRANSFORMERS, 5/9. 350-0-350 v., 12 v., +4 v. Primary, 100, 120, 200, 250. Make ideal auto trans. Post 2/-.

AMPLIFIERS, 57/6. 3 valve, 4 watt output, A.C. or universal. Post 2/6.

AMPLIFIERS, 77/6. 4 valve, 7 watt output, A.C. or universal. Post 3/6.

AMPLIFIERS, 97/6. 5 valve, 10 watt output, A.C. only, with extra pre-amp. stage, 3 controls. Post 3/6.

2d. stamp only for complete catalogue.

HANNEY of BATH offers:—

VIEWMASTER.—Constructor's Envelope, 7/6. Stage 1, 62/3; two, 43/3; three, 25/1/8; four, 9/10; five, 1/0/4/-; six, 27/7/3; seven, 64/-. Complete pre-amp kit (less valve), 32/2.

Complete pre-amp kit (less valve), 32/2.
WB100 (sound and vision chassis), 15/6. WB101, 6/-; WB102, 13/6. WB103, 42/-; WB103A, 52/6; WB104, 15/6; WB105, 47/2; WB106, 25/6; WB107, 32/6; WB108, 33/3; WB109, 1, 2 or 3 (state tube type), 22/6; WB110, 7/6; WB112, 21/6; WB Console conversion kit, 35/-; WB300 pre-amp chassis, 17/6; Westinghouse Rectifiers, 14A86, 20/4; 14D36, 11/7; WX3 and WX6, 2/5 each; 35EHT100, 29/5; 36EHT30, 26/1; 36EHT45, 23/8; K3/100, 14/5; K3/50, 9/9; E3/45, 8/2. T.C.C. Condensers, 47/10/- (any condenser supplied separately). Post 3/6.
Morganite pots, 5/- each; Morganite resistors, 35/3. Colvern pots, 22/6; or CLR901, 3/3 each and CLR4089/22, 6/4. Belling-Lee 1707, 3/3. Fuses 6d. each. Wearite Coils (with L9), L'don and Belfast, 22/-; Wenvoe and Pontop Pike, 28/-; H. Moss, K.O.S., B'ham and Brighton, 30/-; Pre-amp coils, 4/- pr. (any channel).

TELEKING.—Constructor's Envelope, 6/-; Coils, 44/6; Chassis kit, 50/-; T.C.C. kit, 47/4/3; RMA rectifier, 21/-; Allen Components, LO308, 40/-; FO305, 21/-; DC300C, 39/6; FC302, 31/-; GL16 and GL18, 7/6 each; BT314, 15/-; SC312, 21/-; AT310, 30/-; OP117, 9/-; Dubilier Resistor/pot, kit, 81/6.

P.T. SUPER VISOR.—T.C.C. Condenser kit, 28/6/4; Erie resistor kit, 54/4; 4 w/w pots, 28/-; 7 Erie carbon pots, 35/-; Allen coils, 44/6; Allen DC/300C, 39/6; GL16 and GL18, 7/6 each; SC312, 21/-; FC302, 31/-; OP117 output trans., 9/-; Denco WA/FMAL, 21/-; WA/LOT1, 49/-; Denco chassis kit, 51/6; Westinghouse WX6, 3/10; WG4A, 7/6; L.W.7, 28/8; English Electric polystyrene mask, 45/8; perspex filter, 32/8; anti-corona ring, 6/8; Tube sheath, 6/2; T.901 tube, inc. carriage and insurance, 222/14/10; Elac T18 ion trap, 5/-.

OSRAM 912 Erie resistor-pot. kit with ceramic tube resistors, very highly recommended, 29/8; Lab. resistor kit, 32/4; T.C.C. condensers, 55/-; PARTRIDGE Components, with loose lead terminations, Mains trans., 44/-; Smoothing Choke, 29/6; Output trans., 76/9. Price includes Partridge carriage/packing charge. Printed panel, 14/6. W.B. chassis, 28/6. Send for complete list.

MULLARD 5 VALVE 10 WATT AMPLIFIER. T.C.C. Condensers, 45/-; Erie resistor-pot. kit, 37/6; Elstone Mains trans., 36/-; Elstone Output trans., 45/- (both types); Denco chassis, 14/6. Small parts as per our list. Matched pairs of valves are available for both the above designs.

Send 6d. in stamps for our complete list

L. F. HANNEY, 77 Lower Bristol Road, Bath.

Tel: 3811

Free ★ ★ ★ ★ ★

No. 9 CATALOGUE

- Illustrated on fine art paper
- 58 pages, with up-to-date list
- Orders dealt with day received
- A square deal

Post Free. U.K., Forces and Eire only

OVER 2,000 ITEMS LISTED WITH OVER 100 PHOTOGRAPHIC ILLUSTRATIONS

VIEWMASTER.—Constructional Envelope, 7/6. Big Picture Conversion Envelope, 3/6. Pre-amplifier Folder, 1/-. Complete Pre-amp kit, less valve, 32/2. WB200 Sound/Vision Chassis, 18/6. WB101 Chassis Support, 6/-. WB102 Timebase Chassis, 18/6. WB103, 32/6. WB103A, 52/6. WB104, 15/6. WB105, 47/2. WB106, 25/6. WB107, 32/6. WB108, 33/3. WB109/1, 2 or 3 (state which tube), 22/6. WB110, 7/6. WB112, 21/6. WB Console Conversion Kit, 35/-. WB300 Pre-amp Chassis, 17/6. Westinghouse Rectifiers: 14A86, 20/4; 14D36, 11/7; WX3 or WX6, 3/9; 36EHT100, 29/5; 36EHT45, 23/8; 36EHT50, 26/1. Morganite Type T resistors: 20%, 6d.; 10%, 9d.; Type R, 20%, 8d.; 10%, 1/-. All T.C.C. Condensers sold separately. CLR901 pots., 3/3; CLR4089/22, 6/4. Wearrite Coil Sets: London and Belfast, 20/-; Wenvoe & Pontop Pike, 26/-; Holme Moss, Rowridge, Kirk-o-Shotts, Sutton Coldfield, Brighton, 28/-. Pre-amp. Coils, 4/- pair. All other items available, including Wide-angle ype.

Please include Postage on orders under £2. Minimum 6d. Established 21 Years—Our Technical Help at Your Disposal.


SOUTHERN RADIO & ELECTRICAL SUPPLIES

SORAD WORKS

REDLYNCH : SALISBURY : WILTSHIRE

Telephone : Downton 207


LAFCO "E. PAYMENT" CORNER

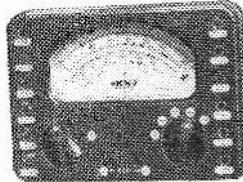

THE "METRIX" MULTIMETER 460

with 28 ranges. Internal resistance 10,000 ohms per volt A.C. and D.C. Volts: 3-7.5-30-75-150-300-750 v. A.C. and D.C. Resistance from 0 to 2 megohms in two ranges. Dimensions: 5 1/2 in. x 4 in. x 1 1/2 in. Weight: 1 lb. 5 ozs. Cash Price £14.6.4 or 35/- deposit and 8 monthly payments of 35/-.

THE "METRIX" MODEL 410

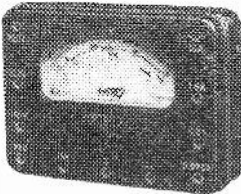

—19 ranges with a sensitivity of 100 ohms per volt from 75-750 volts. A.C. and D.C. Volts 15-75-150-300-750. Resistance 0-100 ohms. Weight: 1 lb. 2 ozs. Cash Price £9.2.11 or 22/5 deposit and 8 monthly payments of 22/5.

There is a "Metrix" Meter for YOUR needs

MODEL 400 TRANSLIP.—Currents can be measured without any volts drop. All voltages (A.C.) up to 600 v. may be measured. A.C. currents 0-10, 30, 100, 300 A. Accuracy 1.5%. F.S.D. £17.8.0 cash or 42/7 deposit and 8 by 42/7.

MODEL 422E.—Sensitivity 5,000 ohms per volt. A.C. and D.C. volts 1.5-5-15-50-150-500-1,500. A.C. and D.C. currents 1.5-5-15-50-150-300 mA., 1-5 amps. resistance 0-2 meg. in 2 ranges. Accuracy 1.5% on D.C., 2.5% on A.C. Weighs 2 lbs., £22.14.10 cash or 55/7 deposit and 8 by 55/7. Send stamp for leaflets of the Metrix range, all of which are available on easy terms.

LAFCO COMPOUNDS, LTD. (Desk 451)
3, Corbetts Passage, Rotherhithe New Road, London, S.E.16. Telephone: BRMonitsey 4341. Est. 1

VIEWMASTER AND SIMPLEX KITS

ON EXTENDED PAYMENTS

Only 3/- in the £ Deposit

★ SIMPLEX ★

- Six-inch kit, less tube. Deposit £2.11.0 and 12 monthly payments of £1.5.9.
- Conversion to Twelve-inch kit, less tube. Deposit £2.6.0 and 12 monthly payments of £1.4.1.
- Twelve-inch kit, less tube. Deposit £4.10.0 and 12 monthly payments of £2.5.10.

★ VIEWMASTER ★

- Nine- or Twelve-inch kit, less tube. Deposit £5.8.6 and 12 monthly payments of £2.15.10.
- Wide Angle Model, less tube. Deposit £6.6.0 and 12 monthly payments of £3.5.6.

Full details of these Kits are given in our lists which will be sent free upon request.

WATTS RADIO

8, Apple Market, Kingston-on-Thames, Surrey.

Telephone : KINGston 4099.

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.s.

AVO METERS IN STOCK

Avo Model 7	—	—	—	—	£19 10 0
Avo Model 8	—	—	—	—	23 10 0
Electronic Test Unit	—	—	—	—	27 10 0
Electronic Test Meter	—	—	—	—	40 0 0
Valve Characteristics Meter	—	—	—	—	60 0 0
★ Cossor Oscilloscopes Model 1052	—	—	—	—	104 0 0
					1049 — 132 0 0

Full range Taylors Meters. List on request.

- Leak—TL/10 Amplifier and "Point One" Pre-Amplifier — Complete 28 7 0
- F.M. Kit of parts £5 less valves. Ref. Radio Constructor July, 1954.
- Jayson F.M. Tuner Unit — — — 15 17 0
- Chapman Tuning Units — — — from 16 0 0

LATEST VALVE MANUALS

MULLARD, OSRAM, & BRIMAR No. 5, 5/- each, MAZDA 2/- each.

SCOPE SOLDERING IRON A.C./D.C. HEATING TIME: 4 v. 6 sec. 6 v. 4 sec. 39/6.

Postage 6d. each extra.

Terms C.O.D. OR CASH with order and subject to price alterations and being unsold.

Arthur's


Est. 1919

PROPS: ARTHUR GRAY, LTD. OUR ONLY ADDRESS: Gray House,

150-152 Charing Cross Road, London, W.C.2

Temple Bar 5833/4 and 4765.

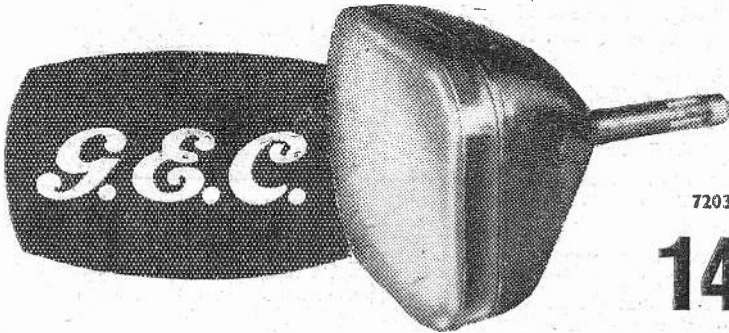
TELEGRAMS—"TELEGRAY, WESTCENT, LONDON." CABLES—"TELEGRAY, LONDON."



7203A

14 INCH

RECTANGULAR Television CATHODE RAY TUBES

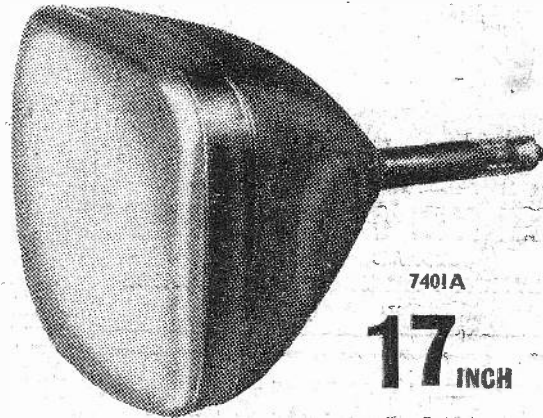

7401A

17 INCH

These G.E.C. Television tubes combine all the requirements for perfect viewing. ALUMINISED SCREENS for brighter and more contrasty pictures with long life and freedom from screen burn. GREY FILTER GLASS face-plates with high light transmission efficiency permitting viewing under normal lighting conditions without loss of contrast and without need of separate viewing filters.

BRIEF DATA

7203A	7401A
Vh 6.3V	Vh 6.3V
Ih 0.3A	Ih 0.3A
Va (min) 10.8kV	Va (min) 11kV
Va (max) 14.0kV	Va (max) 16kV

Both tubes are provided with an external graphite coating, and have a scanning angle of 70°.

The heaters are suitable for both series or parallel operation.

For further information write to the Osram Valve and Electronics Dept.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2