


# Practical TELEVISION DECEMBER 1961 1'9

## PREPARING FOR UHF - A Band V Aerial


Interference  
suppression

Phase distortion

Safety precautions

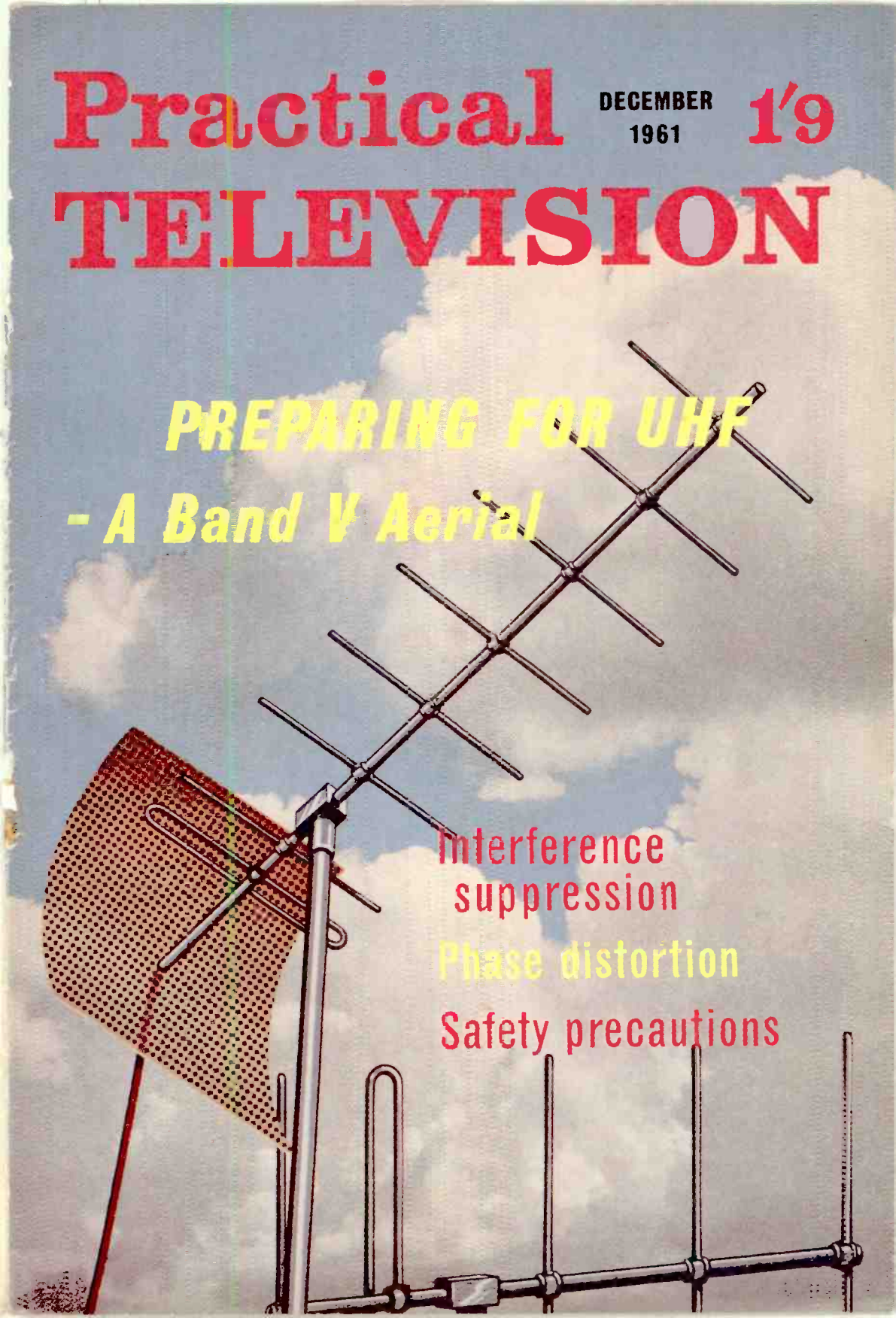

# Build your own Aerials...

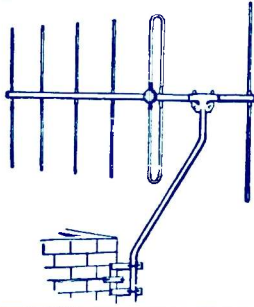

## AT HOME

**AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.** Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:—

# Fringelevision Ltd.

MARLBOROUGH, WILTS. Phone: 657/8



## SPECIAL FOR THE "HAMS" RADIO STATION

*Illustrated*

$\frac{1}{8}$  inch detachable bit soldering instrument  
List No. 70

Combined Protective Unit with Wiper Abrasion Pad and Solder Reel  
List No. 700

Apply **SALES & SERVICE**

# ADCOLA

(Regd. Trade Mark)

**ADCOLA HOUSE  
GAUDEN ROAD,  
LONDON, S.W.4**

Telephones:  
MACauley 4272-3101  
Telegrams:  
"SOLJOINT, LONDON S.W.4"



British & Foreign  
Patents, Registered  
Designs, etc.

## THOUSANDS

OF SATISFIED PEOPLE

VIEW ON **E.M.S.**

### REBUILT TELEVISION TUBES

- ★ A NEW GUN IN EVERY TUBE
- ★ BUY DIRECT FROM THE FACTORY
- ★ 18 MONTHS' GUARANTEE

**12 inch £5.0.0 14 inch £5.10.0**  
**17 inch £6.10.0**

Immediate dispatch on receipt of Remittance  
Carriage and insurance 12/6 extra  
**£1 Refunded on receipt of your old Tube**

For the benefit of South Coast customers we have an agent in **BRIGHTON**. See our classified advertisement for further details.

**SPECIAL TERMS TO THE TRADE**

**MARSHALL'S for TELEVISION LTD.**

131 St. Ann's Road, Tottenham, London, N.15  
STAMFORD HILL 3267 & 5555

**NOW**  
**YOU can MASTER ELECTRONICS!**

**BRITAIN'S MOST COMPREHENSIVE PRACTICAL COURSE IN RADIO • ELECTRONICS TELEVISION!**

**THESE SPECIAL TRAINING KITS — YOURS TO KEEP**

**Multi-Range TEST METER**

**CATHODE RAY OSCILLOSCOPE**

**AM and VHF/FM LUXURY RECEIVER**

**SIGNAL GENERATOR**

**Complete set of Picture Way books and Experimental Manuals**

**LEARN BY BUILDING NOW for your CAREER • HOBBY • OWN BUSINESS**

**YOU RECEIVE**

- Complete kits of equipment as illustrated.
- Complete set of experimental manuals.
- Complete set of "picture-way" theory books.
- Modern test-yourself examination sheets.
- Study programme.
- Unlimited consultation with Tutors.

**FREE BROCHURE NOW**

**RADIOSTRUCTOR**

TO RADIOSTRUCTOR (DEPT. M102) READING, BERKS.

Name \_\_\_\_\_ **BLOCK**


Address \_\_\_\_\_ **CAPS**

\_\_\_\_\_ **PLEASE**


(We do not employ representatives) 12/61
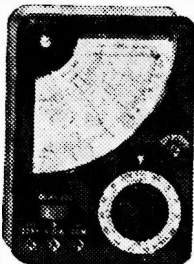
# MULTI-METER BARGAINS!

**MODEL 200H** (illus. on right). 20,000-ohms per volt, 20 ranges comprising AC volts, 5 ranges up to 1,000V DC volts, 8 ranges up to 2.5KV, DC current, 3 ranges up to 25 ohms, resistance, 2 ranges up to 6 meg, capacity, 2 ranges up to .1. decibels -20 to +22. Scale cornerwise to the equivalent of 4in. movement is a pocket size instrument measuring 4 1/2 x 3 1/2 x 1 1/2. Complete with test prods, battery and operating instructions, price **£6.19.6**. Post free.



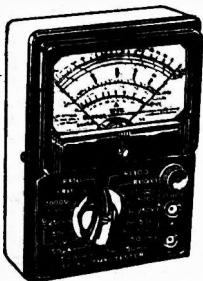**MODEL TE10**. Similar in size and appearance to 200H except that this is 10,000 ohms per volt and maximum DC volts 1,200 instead of 2.5K, also no capacity range. Price **£5.19.6**. Post free.




**MODEL TPS5**. (illus. on left). 20,000 ohms per volt, DC volts, 5 ranges up to 1,000, AC volts, 5 ranges up to 1,000, resistance, 2 ranges up to 10 meg., capacity 2 ranges up to .1, decibels -20 to +26. One switch control, really beautifully made precision instrument, size only 3 1/2 x 5 1/2 x 1 1/2in., price only **£5.19.6**. Post free.

**MODEL TP10**. Similar in size and appearance to TPS5, but sensitivity 2,000 ohms per volt, price **£3.19.6**. Post free.

**MODEL U1**. A robust instrument of 1,000 ohms per volt sensitivity, AC/DC volts up to 1,000, DC current up to 500, resistance up to 200K, size 5 1/2 x 3 1/2 x 2 1/2in., complete with test prods, single switch control, large easily read scale, price only **£2.19.6**. Post free.

# A READY BUILT TRANSISTOR RADIO FOR ONLY **£5.10.0**

Post & Ins. 2/6  
Battery 2/-

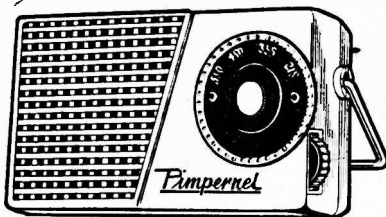

## THE "PIMPERNEL"

Our amazing pocket size transistor set uses five transistors and is an all British product. There is nothing on the market to compare with it and it is many times better than any Japanese set at similar price. Uses only the best and latest components including 3in. Moving Coil Speaker, air spaced tuning condenser two-tone cabinet, etc.

### SEVEN DAYS' FREE TRIAL

Send today, you can keep the set for seven days and if you are not 100 per cent satisfied return it and your cash will be refunded in full.

Demonstrations at all branches. You'll hear it here... You'll hear it there... You'll hear our "Pimpernel" everywhere!!

## ELECTRONIC PRECISION EQUIPMENT LTD

★ Orders received by post are despatched from our warehouse, Dept. 5, 66 Grove Road, Eastbourne, and to save time, please post your order to this address. Please include enough for postage. Callers, however, should use one of the following addresses:

520 High Street North 42-46 Windmill Hill 266 London Road 29 Stroud Green Road 246 High Street  
Manor Park, E.12 Ruislip, Mdx. Croydon Finsbury Park, N.4 Harlesden, N.W.10

## AERIALS

BAND I BAND II BAND III

**Combined Arrays I and III**  
1+3 Element Loft Mounting .. 38/3  
1+5 Element Loft Mounting .. 46/9  
1+3 Element Wall Mounting .. 45/3  
1+5 Element Wall Mounting .. 61/-  
1+3 Element Chimney M'ting. .. 57/10  
1+5 Element Chimney M'ting. .. 66/9

**Band I**  
Single Dipole Wall Mounting .. 24/7  
Single Dipole Chimney M'ting. .. 40/2  
X Aerial Chimney Mounting .. 62/3  
H Aerial Chimney Mounting .. 67/7

**Band III**  
3 Element Yagi Wall Mounting 33/-  
6 Element Yagi Wall Mounting 43/-  
9 Element Yagi Wall Mounting 56/-  
Chimney Lashing Mounting add 10/-  
Double 6 Array, only with clamp 83/-

**Band II**  
Single Dipole Wall Mounting .. 20/5  
Single Dipole Chimney M'ting. .. 29/9  
H Array Chimney Mounting .. 52/4

### REPAIR KITS

Band III Folded Dipole With Insulator, Complete .. 9/3  
Band I Insulator With Two 1/2 inch Dipoles For 1 or 1/2 inch Booms, Complete .. 19/5  
6 inch Lashing Kit, 12/11. 7 1/2 inch Lashing Kit .. 14/8  
6 inch Wall Bracket With U Bolts .. 7/10  
1 1/2-1 1/2 inch Clamps, 3/10. 1-2 inch Clamps Universal 5/4  
Bracket Repair Kit, J Bolts, U Bolts, 20ft Lashing Wire; Thimbles; Corner Plates .. 6/-  
Insulators, All Types .. .. .. (Enquire)  
Co-Ax. Semi Air Spaced, 7ft. vd. .. .. .. Plugs 1/2  
Send 6d. for Lists. Please state Channel when ordering.  
Cash with Order. Post and Packing 3/- extra.

SATISFACTION OR MONEY BACK GUARANTEE

## WALKER & SQUIRES

PINNOX STREET, TUNSTALL, STOKE-ON-TRENT

Phone: Stoke-on-Trent 88767

**WORTH LOOKING INTO!**

**OUTSTANDING OFFER!**

While stocks last

### GUARANTEED REBUILT CATHODE RAY TUBES

12" & 14". Types MW 31-74 : MW 36-24 : SE 14-70 : 4/14 : C14 FM each Carriage Paid CASH WITH ORDER Your old tube not required.

**59/6**

## TATES ELECTRONIC SERVICES LTD

3 Waterloo Road, Stockport, Cheshire. Tel. : Sto. 7301.



# REPLACEMENT TUBES

**REBUILT CATHODE RAY TUBES ARE NOW USED BY  
OVER 80% OF RETAIL SERVICE DEPARTMENTS  
AND RENTAL ORGANISATIONS**

**FOR QUALITY, RELIABILITY AND SERVICE BUY FROM BRITAIN'S  
LEADING GROUP OF INDEPENDENT MANUFACTURERS OF REBUILT  
CATHODE RAY TUBES**

**SUFFOLK TUBES LIMITED**  
1/3 UPPER RICHMOND ROAD  
PUTNEY, S.W.15.  
Tel: Vandyke 4304/5267

**MIDLAND TUBES LIMITED**  
37 GEORGE STREET  
MANCHESTER, 1.  
Tel: Central 4568/9

**VIDEO REPLACEMENTS LIMITED**  
25 ADDINGTON SQUARE  
CAMBERWELL, S.E.5.  
Tel: Rodney 7550/7559

ALL TYPES

KEEN PRICES

PROMPT DELIVERY

WRITE FOR BROCHURE

**Scotts Radio Ltd.**  
4 Church Street  
Brighton  
Tel: Brighton 26891

**Weston Hart Ltd.**  
236/8 Fratton Road  
Portsmouth  
Tel: Portsmouth 24125

**Lawsons Ltd.**  
36 Cornhill  
Bury St. Edmunds, Suffolk  
Tel: Bury St. Edmunds 3304

**J. H. Sunder'and**  
11 Clements Street  
Rochdale. Lancs.  
Tel: Rochdale 48484

**Wizard Productions**  
16 Withy Grove  
Manchester  
Tel: Dea 2772

**J. Charlesworth & Son**  
14 Hightown  
Crewe, Cheshire  
Tel: Crewe 2535

**Taylor's**  
162 Eastney Road  
Milton, Portsmouth  
Tel: Portsmouth 35000

**Millards Southern Rentals**  
3 High Street  
Aldershot, Hants.  
Tel: Aldershot 20408

**Lucketts of Banbury**  
57a/58a High Street  
Banbury, Oxon  
Tel: Banbury 2813

**Snell & Sons Ltd.**  
204 High St.  
Swansea  
Tel: Swansea 50518/9

**H. Knowles**  
54/56 Chester Road  
Manchester  
Tel: BLa 9031

**Radio Services Ltd.**  
30 Mona Street  
Amlwch, Anglesey  
Tel: Amlwch 594

**Hi-Lite Ltd.**  
89 Southbourne Grove  
Southbourne, Bournemouth  
Tel: Bournemouth 44344

**R. Watson**  
Leathern Bottel  
Wavenden, Woburn Sands, Bucks  
Tel: Woburn Sands 2027

**R.E.S. Ltd.**  
17/19 Paynes Lane  
Coventry  
Tel: Coventry 28781

**Radiovision of Glamorgan Ltd.**  
Nolton St. Bridgend  
Glam.  
Tel: Bridgend 2727

**J. Wildbore Ltd.**  
6-12 Peter Street  
Oldham  
Tel: Mai 4475

**R. L. Television Services Ltd.**  
33 Charles Street  
Cardiff  
Tel: Cardiff 26337/8

# Practical Television

AND TELEVISION TIMES

VOL. 12, No. 135, DECEMBER, 1961

Editorial and Advertisement  
Offices:

**PRACTICAL TELEVISION**

George Newnes Ltd., Tower House  
Southampton Street, W.C.2.

© George Newnes Ltd., 1961

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

Inland . . . . £1.5.0 per annum  
Abroad . . . . £1.3.6 per annum  
Canada . . . . £1.2.0 per annum

## Contents

	Page
Editorial ... ..	117
Telenews ... ..	118
The "Lines" Battle ... ..	120
Television Filters ... ..	121
TV Safety Precautions ... ..	123
Servicing Television Receivers	125
Phase Distortion ... ..	129
A Precision Wobblulator ... ..	133
A Band V Aerial... ..	136
Interference Suppression ... ..	140
Underneath the Dipole ... ..	143
Letters to the Editor ... ..	147
Your Problems Solved... ..	148

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television", George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

## Bands IV and V

IT seems safe to assume that any extensions or developments in television techniques or programmes will take place on frequencies other than those at present in use, in order that existing receivers will not be rendered obsolete. This, of course, takes into account colour or any line definition modification which may be advised when the report of the Pilkington Committee is published. As readers will know, two frequency bands may come into use when any such changes are made; these are Bands IV and V. The former extends from 470Mc/s to 585Mc/s and the latter from 610Mc/s to 960Mc/s. These two bands are part of what is now known as the ultra high frequency band which covers from 300Mc/s to 3,000Mc/s, and, from these figures, it is obvious that special techniques will have to be employed in receiver construction. Those readers who saw the introduction of the ITV transmission on Band III will remember how great was the change from the Band I transmissions which were then standard, but the advent of transmissions on Band IV and Band V may introduce much greater difficulties, and those who are anxious to build equipment for receiving new transmissions will no doubt wish to start carrying out experiments and thus follow developments as they are made. We have already published constructional details of a Band V Signal Generator (in the October 1959 issue), but, now, reception of actual transmissions or experimental tests will be necessary. First a reliable aerial must be constructed and full details of a high gain array are given on pages 136-139.

We shall, of course, be introducing designs and details of apparatus from time to time as the UHF bands come into general use, and, next month, we shall be describing the construction of a Band V sound receiver in great detail; this design has been developed to enable circuit changes to be made easily so that future changes in transmission standards may be accommodated.

## OUR QUERY SERVICE

ONCE again we must remind our readers of the rules of our Free Query Service. The following points should be carefully noted:

- (i) We cannot undertake to answer technical queries over the telephone
- (ii) All queries must be accompanied by the query coupon from the current issue
- (iii) If a postal reply is required a stamped and addressed envelope must be enclosed with the query.

We must also point out that we cannot design circuits to readers' specific requirements. Nevertheless we shall continue to help readers as far as possible but it should be remembered that all information necessary for answering the query should be sent to us.

Our next issue, dated January, will be published on December 22nd.

# Telenews

## Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of September, 1961, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London .. .. .	1,949,253
Home Counties .. .. .	1,806,605
Midland .. .. .	1,738,266
North Eastern .. .. .	1,849,785
North Western .. .. .	1,510,904
South Western .. .. .	985,352
Wales and Border Counties .. .. .	697,859
<b>Total England and Wales .. .. .</b>	<b>10,338,394</b>
Scotland .. .. .	1,044,636
Northern Ireland .. .. .	168,425
<b>Grand Total .. .. .</b>	<b>11,552,655</b>

## A New Transmitter

THE Independent Television Authority's new transmitter at Caldbeck, near Carlisle, commenced programme transmissions on Friday, September 1st, 1961.

This transmitter broadcasts the programmes provided to the Authority by Border Television Ltd. It stands on a site 940ft above sea level and has a mast 1,000ft high.

The station is equipped with two 5kW Marconi vision transmitters and two 1.25kW Marconi sound transmitters.


## A New Ultra-Violet TV Camera Tube

THE direct observation of fundamental processes in living cells has been the aim of biologists for many years. This has been brought a step nearer by the development of an ultra-violet-sensitive vidicon television camera tube. Experiments in ultra-violet microscopy have recently been carried out by Dr. R. Barer, at the Department of Human Anatomy, Oxford University, using an EMI Electronics

closed-circuit TV camera fitted with this new-type EMI tube.

Normally, the method of using an ultra-violet microscope—which can observe details in cells of animals or plants not visible to the human eye—is to take a large number of photographs for different settings of the controls, in order to ensure that some of them will be in focus. But high intensity ultra-violet radiation quickly kills the cells. Another disadvantage is that it takes time to develop and print the photographs, and some of those taken at vital stages of the activity may be so much out of focus as to be unusable.

The new EMI ultra-violet tube is so sensitive that the amount of ultra-violet radiation can be reduced to a level which does not kill the cells for a considerable time. And the observation is immediate and continuous. So a specimen can be examined for interesting features in breadth, width and depth by moving the specimen stage and by focusing the microscope through the depth of the specimen as easily as in ordinary light microscopy. Using the EMI television camera, a large number of specimens were thus inspected in one hour which would otherwise have taken several months.

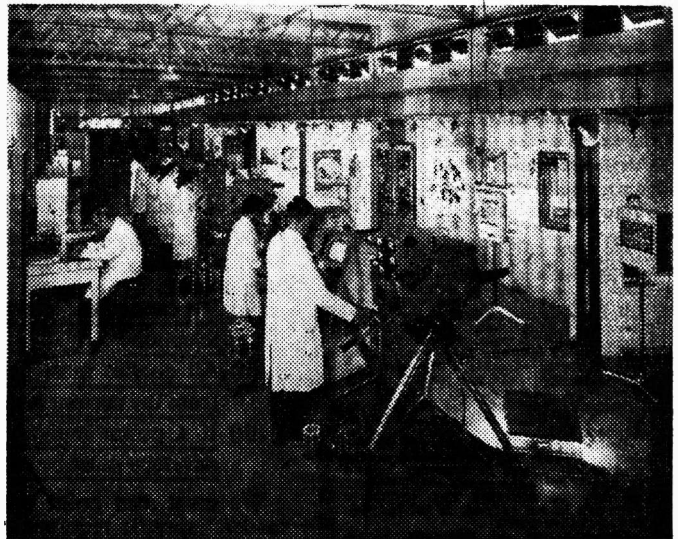

The test studio of the Photoelectric Tubes Division, English Electric Valve Co., Ltd., where Image Orthicon and Vidicon television pick-up tubes are tested. The pick-up tubes receive a thorough electrical test to stringent specifications and an optical test under studio conditions in a television camera.



Observation of cell division on a television microscope is a very stringent test as the cells are very sensitive to ultra-violet radiation. If there is sufficient sensitivity in the tube, the ultra-violet intensity can be kept low enough for the cell division to be observed.

There is reason to believe that the cost of an ultra-violet microscope installation can be considerably reduced by the use of a closed-circuit television camera equipped with this tube.

#### **Closed-Circuit TV at Computer Exhibition**

SO many executives have applied to attend the Electronic Data Processing Symposium—to be held in conjunction with the Electronic Computer Exhibition in the National Hall, Olympia, next week—that EMI Electronics Ltd. have been asked to supply a closed-circuit television system to bring a close-up view of the speakers to those sitting at the back of the room.


The Symposium will be held in the Apex Restaurant—adjoining the National Hall—where several large pillars limit the size of audience which can have a direct view of the speakers' platform. But six closed-circuit TV receivers, placed behind the pillars, will enable the whole audience to see the speakers and any diagrams shown.

Closed-circuit television will also be used on the EMI stand in the National Hall, where a picture of the printed output from the EMIDEC 1100 computer will be displayed on a TV screen mounted high up on the stand.
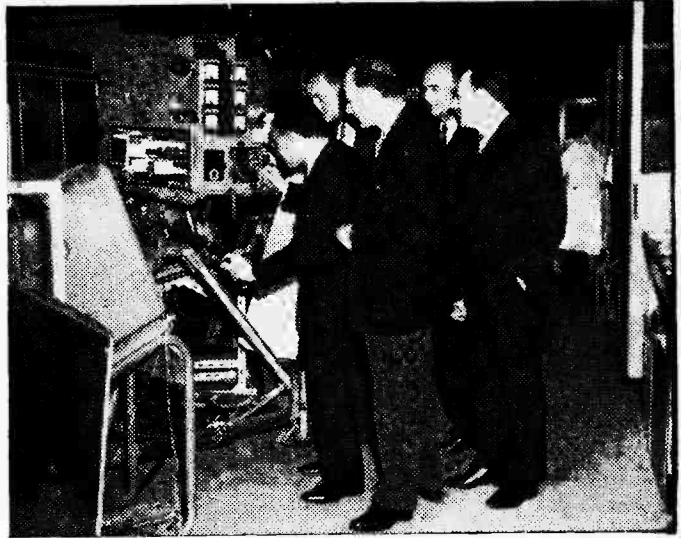
#### **TV for Nigerian Schools**

OVER 150 schools in Western Nigeria and the Federal territory of Lagos began watching WNTV television for schools this month when the third term of Schools TV got under way.

WNTV is the first commercial and educational television network in Africa, launched in October 1959 as a partnership project between the Western Nigerian Government and Overseas Rediffusion Ltd of London. Transmitters are located in Ibadan, capital of Western Nigeria, and at Abafon, some 18 miles from Lagos. Since its inception the television service has provided schools programmes.



At a recent visit to the English Electric Valve Company Limited, representatives from leading French television and electronic organisations, who for a considerable time have been users of the Company's image orthicons, gathered to discuss and evaluate the award-winning English Electric 4½in. and the 3in. image orthicons.

Live shows to be seen this term include an experimental programme on Infant Nutrition; Nature Study; and the popular "News and You", in which a team of experts from the Western Nigerian Ministry of Education discuss current events and their background.

#### **Television at USA University**

EXPERIMENTS with a Marconi 4½in. image orthicon TV camera have been so successful at the University of California at Berkeley, USA, that the College has planned large-scale television facilities for the coming academic year.

An 80-seat classroom has been set aside as a television teaching laboratory; in addition, a number of lecture courses at the college will be video-taped for subsequent playback. These are two of the facilities being made available through the use of television as a teaching aid.

#### **Fair in Yugoslavia**

AN Image Orthicon Camera channel, type 203/6, was the highlight of EMI Electronics Ltd's exhibits at the Ljubljana Fair, Yugoslavia (October 21st to 29th). Although in the past EMI has had a number of busi-

ness dealings in Yugoslavia this was the first time that EMI Electronics Ltd. equipment has been exhibited at a Yugoslav Trade Fair.

A scale model layout of an EMIDEC 1100 computing system illustrated one of their range of fully-transistorised electronic computers.


Other units shown included a display of the company's special electronic valves; tape recorders; electronic instruments, including a range of nuclear health equipment; and a wide selection of the company's industrial electronic products.

#### **Television Cameras for Poland and Denmark**

FOLLOWING a successful demonstration of equipment in Warsaw earlier this year, two EMI vidicon camera channels have been ordered on behalf of Polskie Radio, Poland.

These channels comprise camera, camera control unit, remote control panel and four-position lens turret. Also Denmark's Radio—the Danish State broadcasting service—has placed an order with EMI Electronics Ltd. to supply four 4½in. image orthicon camera channels for use in the Copenhagen studios.

# 405 or 625?

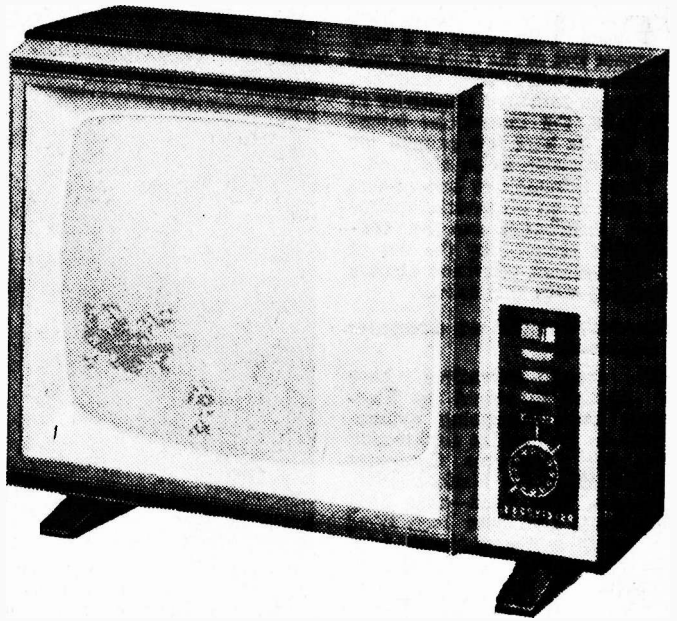

(Above)—This receiver may be used on the 405-line standard, but may be adapted for 625-line transmission should this become necessary.

## The "Lines" Battle

### THE TRUTH BEHIND THE PRESENT CONTROVERSY

(Continued from page 69 of the November issue)

By J. Harwood

EVERY new requirement of a new system brings added complications. All these added complications and the lack of material information on future standards make it impossible for any manufacturer to produce a set with a switched conversion system which he would be sure would be suitable for the future while satisfying today's requirements. There are, nevertheless, designs and prototypes of dual standard television receivers for the British and CCIR systems.

#### Towards Conversion

Manufacturers have tackled the problem in such a way that their new receivers are designed towards conversion at some future date. This does not necessarily mean that the receivers will be able to be switched over the two systems although, on the other hand, it may mean that a future conversion may, in fact, change an existing new model to a truly dual standard model. Whether or not this would be economically and technically feasible will

depend mainly on two factors: firstly, the extent of change over to the new standard as governed by the type of system eventually adopted, and secondly, when the new system becomes available. There is, of course, the possibility that even today's new models will be worn out before a new system is launched.

It would appear that truly dual standard models will not be produced until some definite ruling has been given by the Government, but in the meantime manufacturers must satisfy the demands of their customers—and their customers demand that any new receiver that they may buy today will also be suitable for tomorrow. There is no doubt about this, of course!

The "convertibility" features of the new models range from switched timebases and a UHF position on the tuner to elaborate "plug-on" conversion units. Most models now have a UHF position which simply opens up the tuner to the I.F. channel. A separate UHF tuner would thus be plugged in and this would be brought into operation by switching the ordinary tuner to UHF. The Cydon PC80 tuner, for example, has a switched injection point at the grid of the mixer for the introduction of the output for a separate UHF tuner.

(Continued on page 147)

# Television Filters

By T. Kemp

THE FIRST OF A SERIES OF ARTICLES ON THIS SUBJECT

**T**ELEVISION filters serve two basic requirements. One, they either block or short out unwanted signals; or two, they produce a specific passband allowing signals of certain frequencies to pass with very little attenuation while signals (outside the passband) are heavily attenuated.

Such filters are built either in the receiver circuits or in units external to the receiver. In the former case, typical examples are adjacent

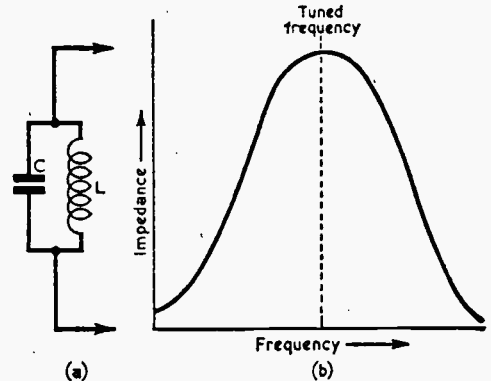


Fig. 2—The parallel-tuned circuit (a), has maximum impedance at resonance (b).

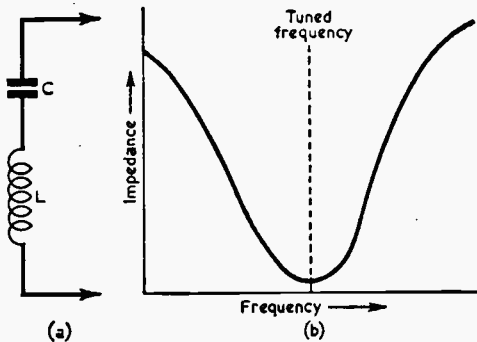


Fig. 1 (above)—The series-tuned circuit (a), has minimum impedance at resonance (b).

channel and sound rejectors, while falling in the latter category are low-pass, high-pass and band-pass filters, duplexers and triplexers and certain kinds of frequency-selective attenuators, all of which may be connected in the aerial downlead.

In this short series of articles it is proposed to describe the various types solely from a practical plane with the minimum of mathematics. However, as filters are essentially mathematical in their conception, one or two slight ambiguities may be observed by those well versed in the arts, but it is hoped that these will be overlooked by the purist in the interests of simplicity of presentation.

### Classification of Filters

The simplest filters consist of either a series or parallel resonant circuit. With the series arrangement, the impedance offered to signals at the frequency to which the filter is tuned is at a minimum, while either side of resonance the impedance increases, as shown in Fig. 1. With the

Fig. 3 (right)—Examples of four-terminal filters.

- (a) low-pass T-section;
- (b) low-pass  $\pi$ -section;
- (c) low-pass series-derived T-section;
- (d) low-pass shunt-derived  $\pi$ -section;
- (e) high-pass T-section;
- (f) high-pass  $\pi$ -section;
- (g) high-pass series-derived T-section;
- (h) band-pass;
- (i) band elimination.

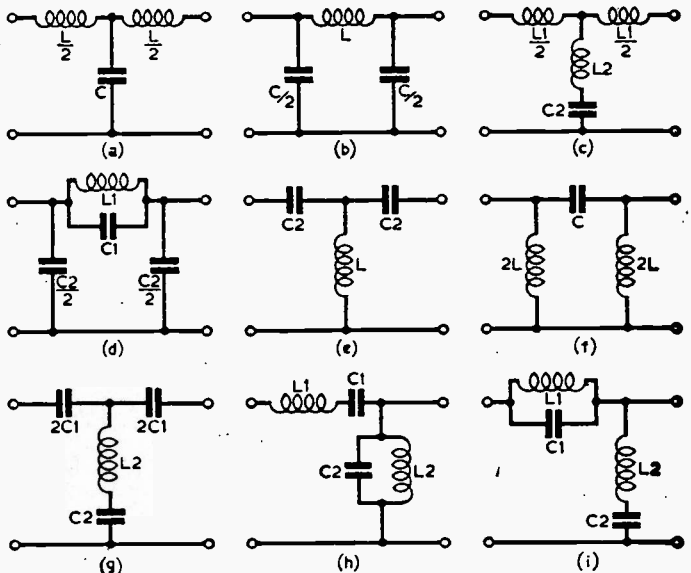


Fig. 4 (right)—A Parallel-tuned rejector. The resonant frequency is equal to  $\frac{1}{2\pi}\sqrt{L.C}$  where L is the inductance and C is the total capacitance.


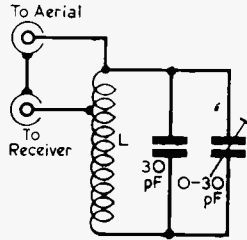


Fig. 5 (below)—The construction of the rejector in Fig. 4.

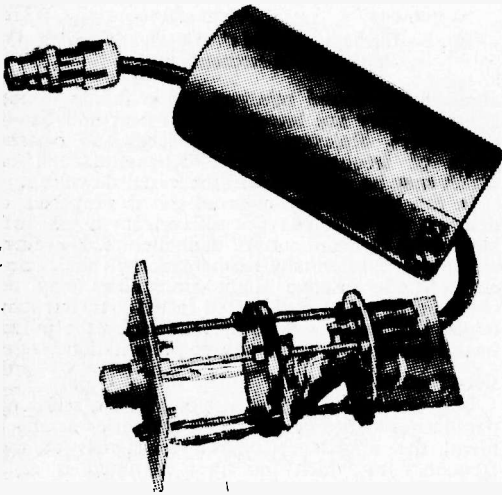

computed to provide the required critical frequency and terminal impedance, for in the latter respect it must be remembered that a filter has to work into and out of impedances governed by the circuit in which it is connected. For example, a filter which is required to be connected in series with an aerial download must have an impedance on the input side equal to the aerial and an impedance on the output side equal to the aerial input of the set. In this particular case, of course, the input and output impedances would have similar or identical values.

**Tuned Rejector Circuit**

The simple tuned rejector circuit can be very useful for certain external applications, especially

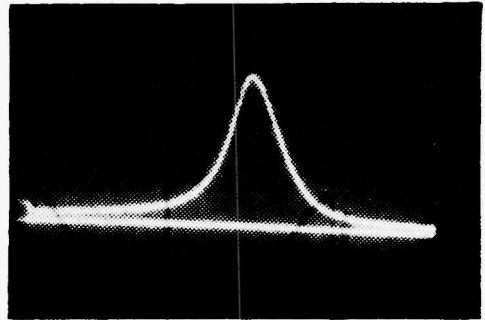


Fig. 6—The response curve of the parallel-tuned rejector as displayed on the screen of an oscilloscope.

parallel arrangement the impedance is at a maximum at resonance, as shown in Fig. 2. These are known as "resonant circuits" and in some applications are called "rejectors" or "traps".

**Four Terminal Filters**

Of slightly more complicated structure are the four-terminal filters, so-called because they have two input terminals and two output terminals. These come under four primary classifications: "low-pass", which pass all frequencies below a critical frequency; "high-pass", which pass all frequencies above a critical frequency; "bandpass", which pass all frequencies between two critical frequencies; and "band-elimination", which pass all frequencies outside two critical frequencies.

Examples of such filters are given in Fig. 3. It will be seen that they are all composed of inductance and capacitance. The values of these elements are

in cases where an interfering R.F. signal falls towards the edge of the vision passband. A typical example in this respect is when it is required to receive a distant station on a channel adjacent to that used by a powerful local station.

Although the set itself is designed to possess reasonable adjacent channel selectivity, the aerial signal of the adjacent channel station may be of sufficient strength to force its way into the set and cause breakthrough and pattern interference.

When that happens a parallel-tuned rejector can  
(Continued on page 152)

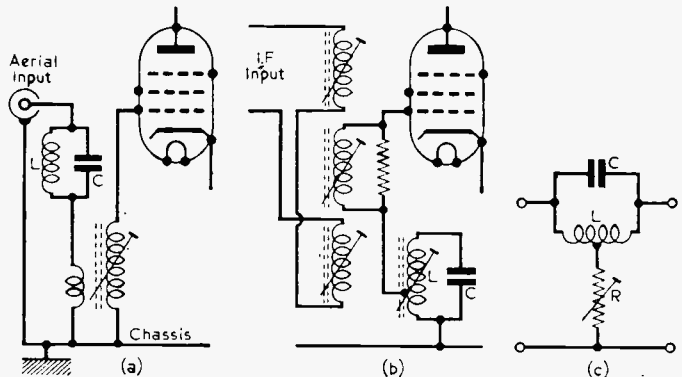


Fig. 7—Simple parallel rejectors; (a) the rejector is inserted in the signal input circuit, (b) the circuit forms an "absorption" sound rejector, (c) is a "bridged-T" rejector.

*" . . . a television receiver, by virtue of the fact that it is permanently connected to the public power supply is a potentially dangerous device, if handled incorrectly".*

# TV Safety Precautions

By F. C. Adams

**T**HIS article relates mainly to the safety aspect of television receivers not only from the experimenters' and service technicians' points of view but also so far as the viewer himself is concerned.

## Dangers

Modern sets are not dangerous from the EHT angle, as were old sets in which the EHT was derived from the mains transformer, though, nevertheless, a severe electric shock can be experienced

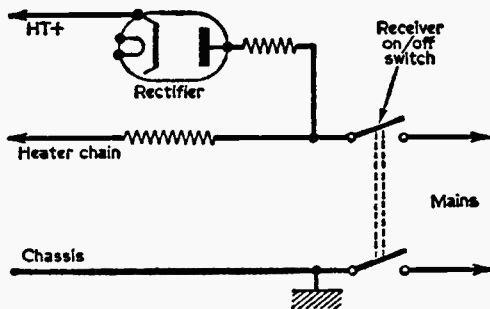


Fig. 1—A connection between one side of the power supply and chassis is made on all A.C./D.C. equipment; the chassis being connected to neutral.

by touching the final anode connection of the CRT or the EHT feed circuit, even after the set has been switched off for a while. Under normal conditions, there is not enough power in a line flyback EHT system to feed a lethal current to anyone who contacts the wiring, but sets with large tubes are particularly dangerous especially to anyone with a weak heart. A very unpleasant burn is, however, possible by touching the high pulse voltage points, in particular the anode of the EHT rectifier valve, the anode of the line output valve and the cathode of the efficiency diode. Indeed, the power at these points is sufficient to set fire to the set. An ideal condition for this to happen is set up by a collapse of the insulation at the high pulse voltage points, such as on the line output transformer. Severe arcing begins and the insulation progressively becomes more conductive, resulting in an even greater arc and finally fire.

## Dangers from the Mains

On most modern sets, one side of the mains supply is fed straight to the chassis and the other

to the anode of the H.T. rectifier and the heater chain, as shown in Fig. 1. This can represent the greatest danger to both the viewer and the experimenter or technician, because the side of the mains connected direct to chassis may be the "live" side. At the generator or sub-station the neutral side of the supply is connected very efficiently to earth and the live side is highly insulated from earth. If, at the receiver, the live side is connected to chassis, and contact is made with a hand or other part of the body to the chassis, an electric current will flow from the earth at the generator back through the body and via the chassis to the live side. There is, in fact, a complete circuit.

How much current flows will depend on how good the connections are at the body. If, for example, the hand is slightly moist and pressed hard against the chassis and there is very little insulation between the feet and a good earth, then a large current will flow, possibly with fatal results. If, on the other hand, one is standing on a dry, wooden floor, or is wearing rubber shoes, there will only be a very small current and it may not even be felt. An extremely dangerous condition exists if one happens to be leaning against an earthed object, such as an electric radiator, while touching a live chassis with the other hand and similarly, if one is standing on a concrete or stone floor and wearing leather shoes.

## Testing for Live Chassis

Conditions for an electric shock of this nature only exist, of course, when the chassis or object being touched is connected to the live side of the mains supply. If it is connected to neutral, all is well, as there is very little potential difference between the neutral side of the mains and a local earth.

There are several ways of determining which mains wire is the live one. A small neon tester of the type found in some screwdrivers will glow when the blade is connected to the live terminal. An ordinary household bulb can be used by connecting one side to a good earth and the other side in turn to the two terminals. The bulb will light — though possibly not at full brilliance — when connected to the live terminal. The largest diameter socket on three-point outlets is itself connected to a local earth (or should be). When looking at the rear of the plug or the front of the socket with the earth point at the top, the neutral side, labelled N, is on the left and the live side, labelled L, is on the right. It often pays to check

this on the outlet points fitted in new houses! However, do not keep a bulb operating between the live wire and earth for any length of time.

### Correct Connection Always Advisable

When servicing a set or making internal adjustments the precaution of checking for a live chassis is highly recommended. Indeed, it is advisable always to ensure that the chassis is connected to the neutral and not the live wire, even when the set is operating normally in its cabinet. There are several reasons for this; on some older sets the control knobs are secured by grub screws against the metal spindles of the controls and a chassis connection may thus be accessible from the outside of the cabinet and an electric shock may be sustained by a viewer operating the controls. This type of control knob is no longer allowed, but they still exist on certain old sets. The grub screw hole should be filled with wax after the screw is tightened. Secondly, the metal speaker grille may become bent after years of use and touch the chassis. This is highly dangerous if the chassis is live, for then there is a large live area on the front of the set. A child was killed some years ago due to a defect of a smaller nature. He was touching an earthed electric fire with one hand when the other hand made contact with the metal speaker grille. Regulations prevent this from happening on modern sets, but it is as well to bear in mind when dealing with old sets and home constructed models.

### Live Aerial Danger

Another danger of a live chassis is that the aerial itself may become live. Theoretically, the braid of a coaxial downlead should be earthed and on some sets an earthed terminal is provided for this purpose. It is rarely used, however, and the downlead is nearly always isolated from earth. The downlead must be in R.F. connection with the receiver chassis and this is accomplished by a capacitor, shown by C in Fig. 2.

This effectively isolates the aerial from the chassis so far as the mains frequency is concerned but connects it to chassis at VHF. The value is around  $0.001\mu\text{F}$  so it lets through very little current at 50c/s. However, if the chassis is live, almost the full mains voltage develops across the capacitor, especially when the aerial is partially earthed as it usually is, particularly when it is raining. The capacitor may eventually become short-circuited. This will not affect the performance and will blow neither the set fuse (if fitted) nor the household fuse because the aerial and downlead are not properly earthed. There is usually not the slightest indication that the isolation has failed.

We now have a very dangerous condition where the aerial and downlead are connected to the live side of the mains. This may go on for quite a long time without anyone being aware of the condition. If the aerial is removed from the set and reconnected there would be a tell-tale spark—quite a big one if it were raining. Even with isolation there would be a small spark with a live chassis because the capacitor lets through a little of the 50c/s current. This symptom, therefore, should lead to a thorough investigation of the isolating capacitor and a reversal of the mains leads. An aerial rigger was killed recently because of a live aerial—not so much as the direct result of electric

shock, but because the shock caused him to fall off his ladder.

All receivers should be installed with the chassis connected to the neutral of the mains—this stipulation is sometimes made in the instruction booklet issued by the manufacturer. If a dealer makes the

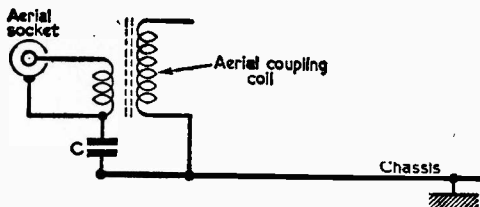


Fig. 2—Capacitor C isolates the aerial from the chassis. If this breaks down on a live chassis the aerial will become live.

installation then he should attend to this, also when re-installing after a repair. If the viewer makes the installation, then it is his full responsibility to ensure that all is correct. With modern receivers, it is almost impossible to receive an electric shock, even when the chassis is connected to the live side of the mains.

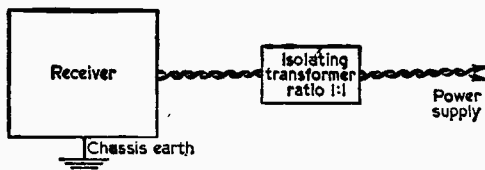



Fig. 3—If external equipment is to be connected to an A.C./D.C. receiver, a 1 : 1 ratio isolating transformer should be used.

### External Connections

Manufacturers do not recommend that any external equipment should be connected to their receivers, apart from that which they themselves authorise. If, for example, an extension speaker, tape recorder or pair of headphones, is connected, then this must be at the owner's own risk. Such connections are highly dangerous on A.C./D.C. equipment of the type under discussion. There is only one really safe way that this can be accomplished and that is to connect the set to the power supply through a 1-to-1 ratio isolating transformer, as shown in Fig. 3. The receiver chassis may then be connected to an efficient earth point and external equipment may be connected without danger of electric shock from the mains supply. If running a tape recorder or pick-up, this "earthed" arrangement makes it relatively easy to remove hum, which is virtually impossible to achieve on A.C./D.C. equipment with capacitor isolation. *On no account, however, should an earth be connected to a receiver of this type without transformer isolation.*

Isolating transformers can be obtained from most dealers at various wattage ratings. A very substantial 200W transformer costs about £6. The transformer must have a 1-to-1 ratio so that the output voltage is the same as the voltage applied from the power supply.

# Servicing Television Receivers

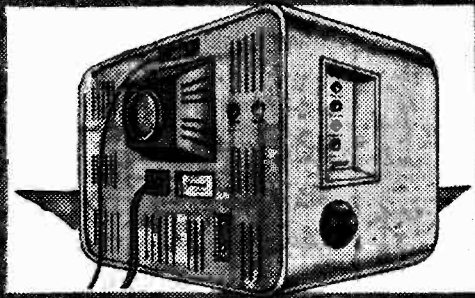

No. 74—THE ENGLISH ELECTRIC 16T11D AND SERIES

By L. Lawry-Johns

(Continued from page 67 of the November Issue.)

**H**AVING considered the EHT system and its usual faults (last month), we now discuss the line timebase in greater detail.

### Line Hold

Quite a common complaint is loss of line hold, the control being at one end of its travel. A 1W resistor of 220k (red, red, yellow) is connected from pin 2 of V13 to the hold control and this (R251) sometimes goes a little high, sufficiently to put the control out of range. The resistor R250, 470k does not often change in value but when it does go high in value, lack of line drive results producing insufficient width, poor EHT regulation and (owing to underdriving the output stage) early failure of the PL81.

Complete loss of EHT, line whistle etc., is often caused by R255 4.7k 3W becoming o.c. This is a wire-wound resistor and the element fails on occasions, resulting of course in no screen voltage

on pin 8 of the PL81 and consequently rendering the valve inoperative. If the timebase is dead, the thermal overload is not tripped and the valves are in order, a glance at the PL81 will show whether it is overheating or not. If it is not overheating check the pin 8 voltage and R255. If the PL81 is overheating check C251 (0.1μF) and the V13 stage.

### Oscillator

Overheating may well be caused by an overload, in the EHT circuit for example, and it should be remembered that V13 cannot oscillate on its own. It depends upon a feedback waveform from the output transformer. Thus if an overload is present the oscillations will fail and the PL81 will be overheated. Such conditions will also obtain if C259 is leaky.

If the timebase starts operating soon after switch-on but fails after a few seconds, C254 (0.5μF-500VW) should be suspected after the essential preliminary valve check. Valve V15 (PY81) is occasionally responsible for an inoperative line timebase.

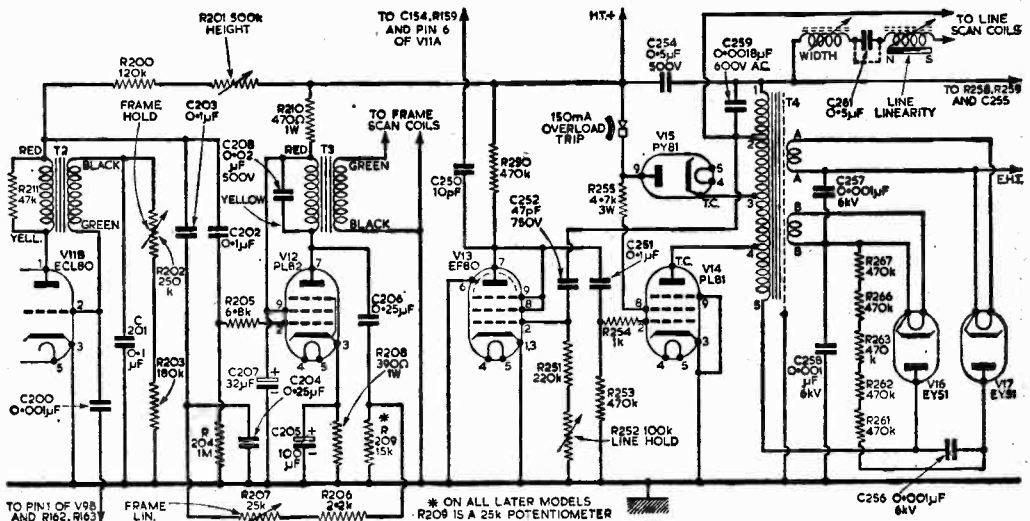


Fig. 4—Circuit of the frame and line timebases.

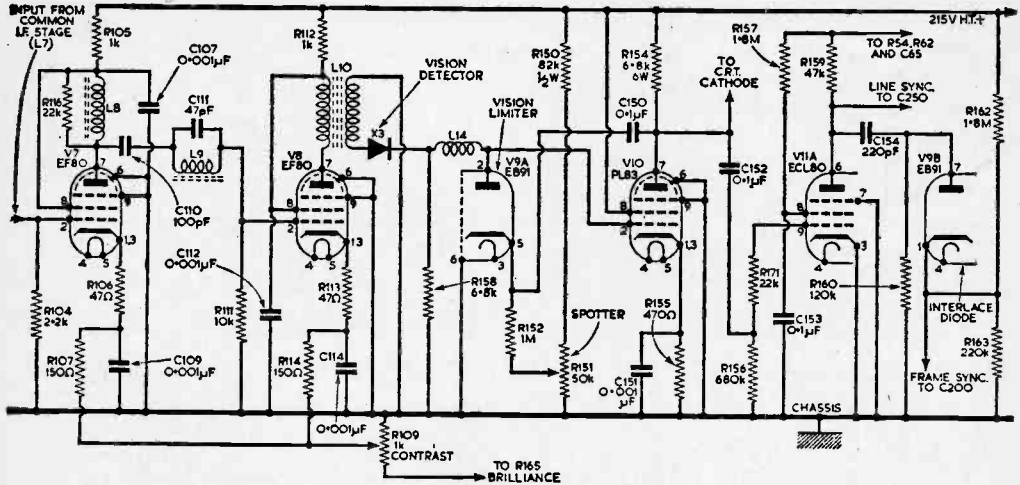


Fig. 5—The vision I.F., detector and sync separator circuits.

**The Frame Timebase**

A blocking oscillator (V11B) is used to drive an output pentode V12. The oscillator which is the triode section of an ECL80 is conventional, the

driving waveform being developed across R200 (120k) and R201 (500k height). This is coupled to the control grid of the PL82 via C202 (0.1μF). Linearity of the frame scan is obtained by a feed-

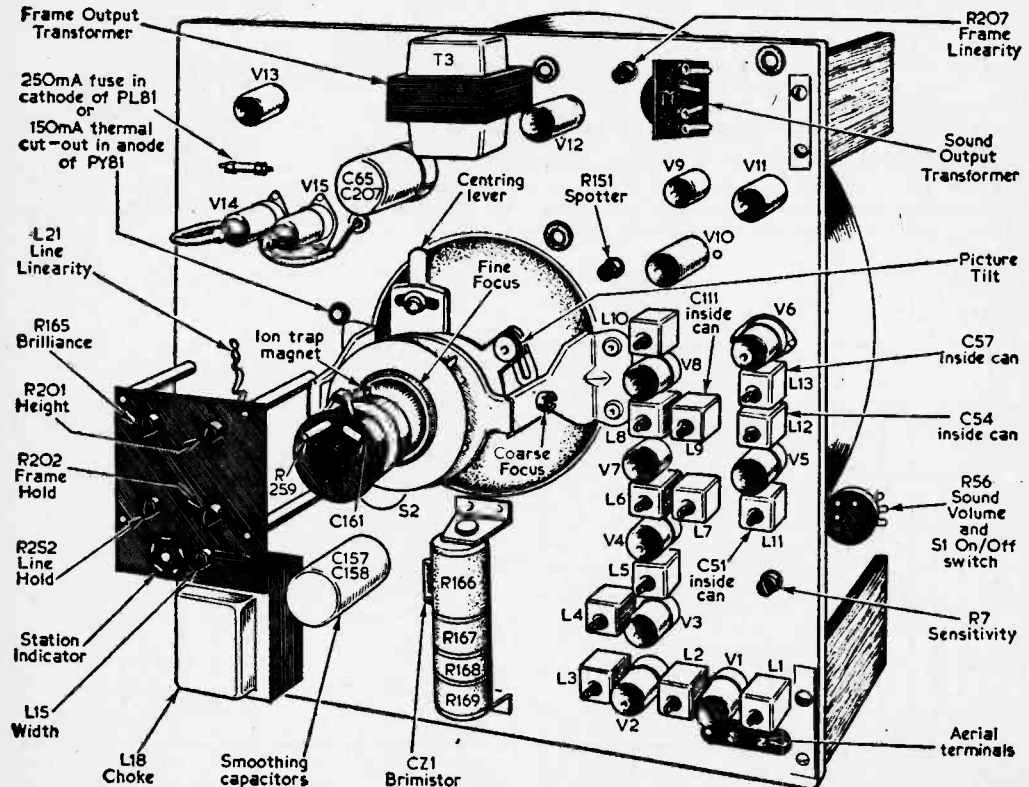


Fig. 6—Rear view of the chassis.



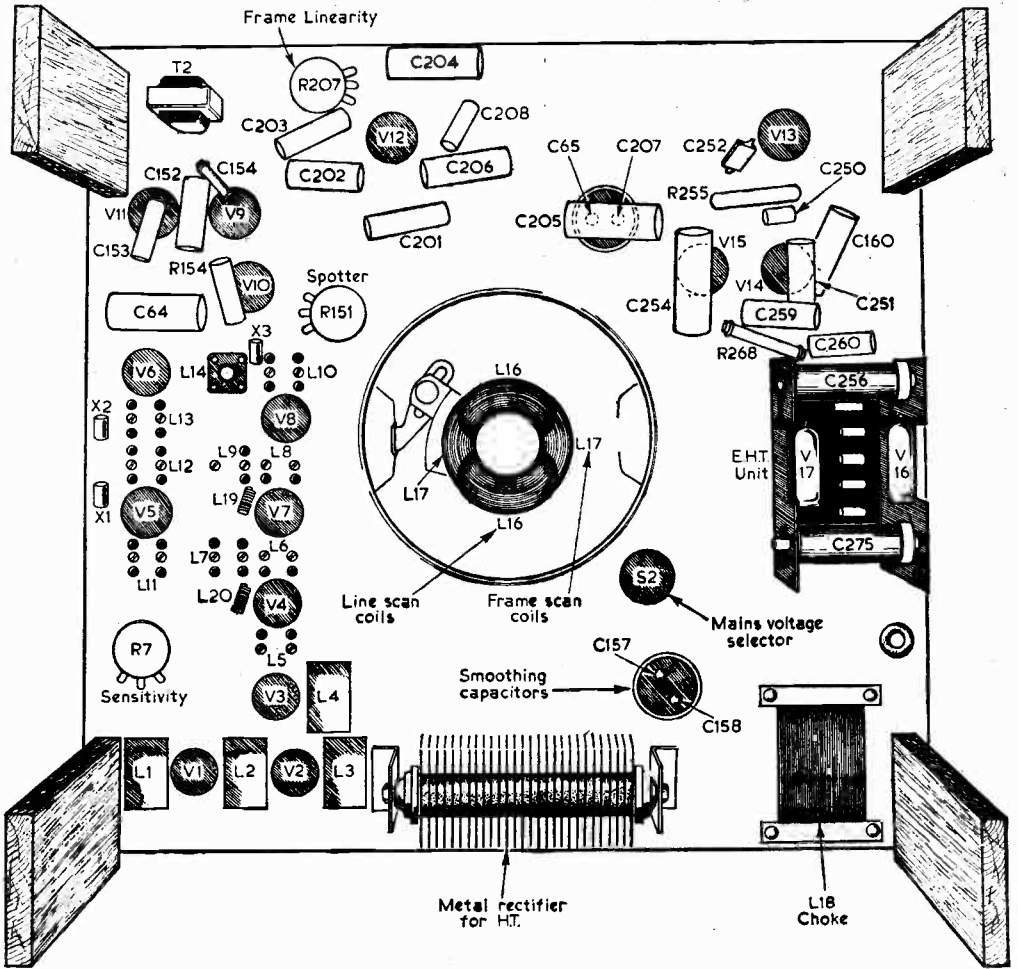


Fig. 7—A simplified front view of the chassis.

back loop using rather high valued capacitors (C206-C203-C204).

**No Frame Scan**

A white line across the centre of the screen denotes trouble in the V11B-V12 stages. The output stage (V12) is easily checked by connecting a small capacitor (say 0.01µF) from pin 4 of the PL82 to pin 2. If this results in some sort of raster being obtained the V11B stage should be checked. V11 could be defective, but, if a replacement fails to cure the fault, check the voltages at pins 1 and 2. Over 80V should be present at pin 1 and about (-40)V at pin 2 when the stage is working correctly. Check T2 by disconnecting R211 (47k) and noting the effect upon a voltage reading at pin 1 or make a "cold" continuity check between the red and yellow leads. If the stage is oscillating, bridge C202 with a known good 0.1µF capacitor as this can go o.c.

If the V12 stage is inoperative, check the voltages at pins 7 and 9 of the PL82 base. If the voltage is absent from both, suspect R210 (470Ω)—probably o.c. and check C207 (32µF) which may be shorted. If H.T. is present at pin 9 but not at pin 7 check the continuity of T3, red-yellow winding.

If the picture revolves and the hold control is at one end of its travel check R203 (180k) and if necessary C201; R202 (hold control 250k).

**Reduced Height**

Even gap top and bottom; check R200 which sometimes goes high. If the bottom is compressed, and the top stretched; check V12 (PL82), C205 (100µF) and linearity capacitors (C203, 204, 206).

If both timebases are difficult to lock perhaps one more than the other, for example, the line hold may be critical, but the frame hold just rolls up or down with no locking point, check V11 and R157 (1.8M). If these are in order, check C152 (0.1µF). If the

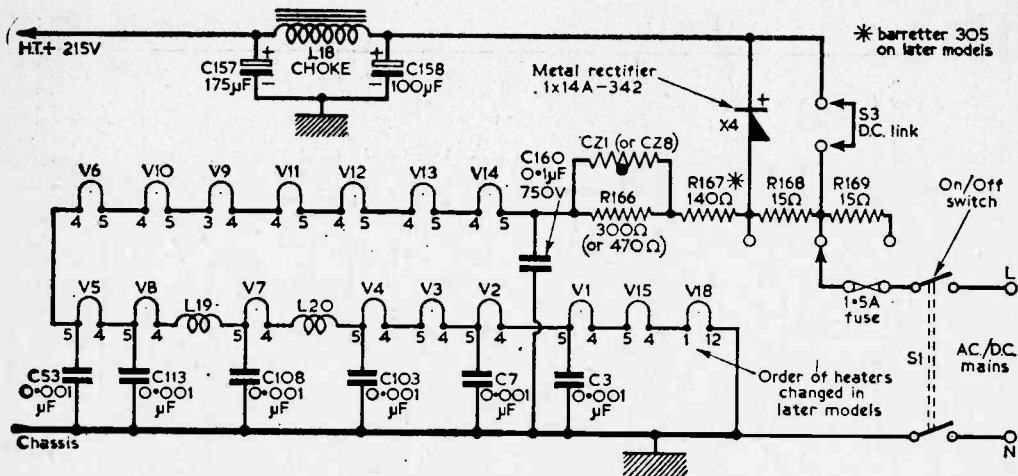


Fig. 8—Circuit of the heater chain and power pack.

line hold is not impaired at all, check V9 and the components connected with pins 7 and 1 e.g., C154, R160, R162, R163, 200. If the line sync is poor although the frame locks well, check C152 but bear in mind the effect of reflected signals on the aerial. As well as producing "ghosts", these can cause severe line displacement whereby sections of the picture move horizontally on black and white picture content, particularly as the white content

nears the right-hand side (see page 505, July issue).

**Sound Stages**

Low and distorted sound, check V5 and V6. If in order check R54 (10M), X1 and X2. A loud howl may be caused by C64 becoming o.c. thus promoting positive feedback from V6 output pentode to the triode section.

(To be continued)

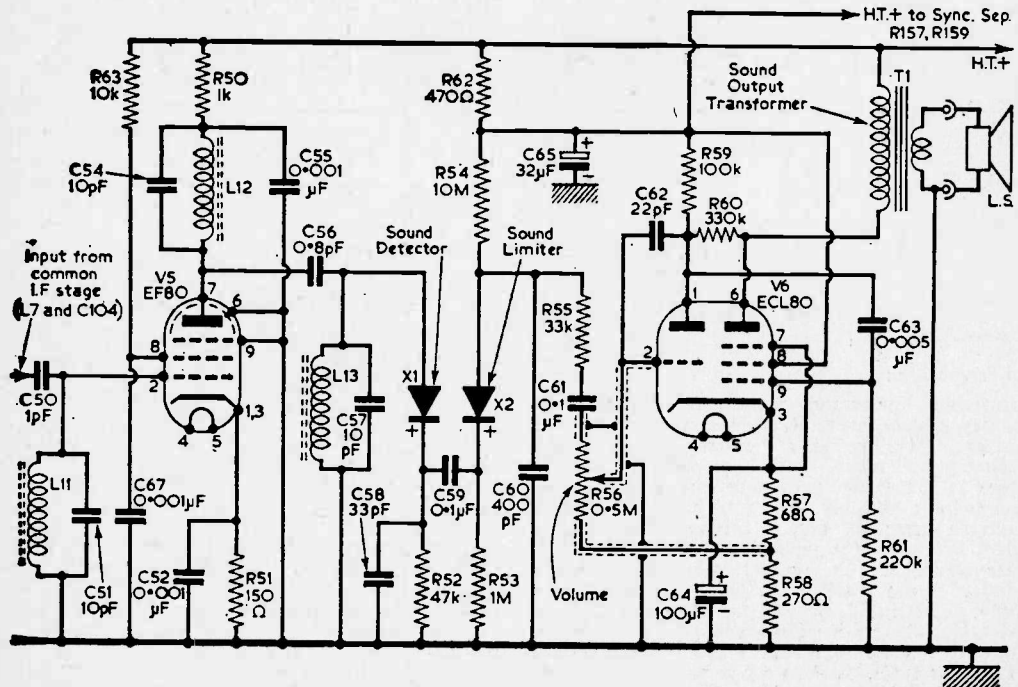


Fig. 9—The sound I.F., detector and output stages.

# phase DISTORTION

By T. W. Carreyett

A KNOWLEDGE OF PHASE SHIFT AND PHASE DISTORTION IS ESSENTIAL FOR ALL TV ENTHUSIASTS

**M**AINLY because of developments during the last ten years in wide band equipment, pulse techniques, television equipment, wide band recording equipment and the like, interest in phase shift, and the correction of phase distortions has become necessary. By means of a square wave, phase distortion can quickly and easily be found. In an ideally perfect amplifier, the response would be linear and would possess a phase shift characteristic proportional to frequency and the output therefore could produce a perfect square wave.

## A.F. Testing by Square Wave and Sine Wave

When applied to A.F. amplifier testing, it should be mentioned that the square wave test has one big disadvantage—a square wave output expresses the combined output of the phase and frequency response at all frequencies incorporated in the square wave. At low frequencies in an A.F. amplifier, the phase response may be poor, so producing a poor square wave output and this may, to an inexperienced eye, be thought

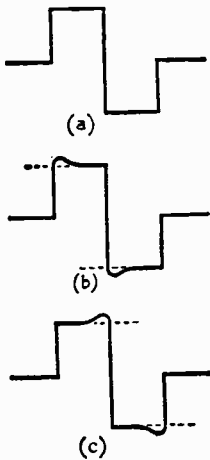


Fig. 1 (a)—A square waveform for testing; (b) an example of phase advance, generally known as "overshoot"; (c) an example of phase lag, known as "undershoot".

to represent a poor amplifier. Fortunately, since the ear can tolerate a large quantity of phase distortion at low frequencies, this does not matter, so the distorted low frequency square wave, although telling a true story, tells one that may be neglected. Because of this, it is not on the whole advisable to test A.F. amplifiers with a square wave frequency below 1kc/s.

In testing of an audio system, it is often sufficient to "squeak" the equipment with an oscillator with reference to a zero level frequency point (zero dB or 1mW developed in 600Ω at 1kc/s). Providing that the losses at the top and the bottom of the audio frequency spectrum are within some specified tolerance, all may be assumed to be well. It is found, however, that when wider

bands of frequencies are involved, a spot frequency test of a system does not represent a true picture, for although the frequency response can sometimes be adjusted to a satisfactory result, trouble may now be encountered with the phase response. Within an audio system, the phase response can, on the whole, be neglected, although for the enthusiast "hi-fi" this would never do, for he would quickly explain that a poor phase response would ruin the transient response and would give a lack of "presence". Let us now consider the lack of "presence".

## Wide Band Response

In a wide band system, with careful design, phase distortion in equipment can be kept to a small value. One thing that cannot be controlled so easily is the number of links or lines connecting equipment in the system, and it is here, by equalisation with frequency correction that one may run into phase distortion. One typical example of phase distortion which most people with a television set will have experienced at some time or another, is the effect on the picture when an aeroplane flies around the district. The bright, fuzzy picture illustrates phase distortion owing to the sum and difference paths introduced by the original signal path and the new path from the aeroplane.

Let us now see how this effect can be caused by circuitry instead of the aeroplane. Apart from

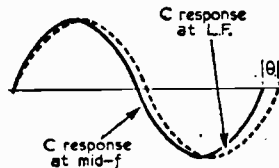


Fig. 2—How phase distortion will affect an L.F. signal.

valves the main circuit elements are resistance, capacitance and inductance. If these three components are connected in series it will be found that the current across the resistance will be in phase with the applied current; across the capacitance it will have a 90° phase lead, and across the inductance it will have a 90° phase lag. Now, since all circuitry can be broken down by network theorems to an equivalent circuit of L, C, and R, it seems reasonable to suppose that phase distortion will be introduced only by the reactive components XL and XC. So, from this deduction it appears that in order to control the phase response of a system a very careful control of XL and XC must be maintained. From a general inspection of equipment, and a little thought, it can be seen that the values of XL on the whole can be fairly well controlled, but values of XC cannot be. Here, XL and XC are total values including all stray sources.

## Stray Sources

Stray inductances likely to take effect are mainly such things as long leads, induction and the effects

of cans around transformers, and some screening and shielding—all these effects can be taken into account in design.

Stray capacitance however cannot always be compensated in a design; for example, the disturbance of a grid lead, or the use of a non-standard high capacity coaxial cable for a link. It appears, therefore, that the main culprit involving phase distortion is capacitance, stray or otherwise.

### Waveforms

In Fig. 1(a) is shown the square wave test waveform, in (b) is seen an example of phase advance, known generally as "overshoot" and in (c) is shown an example of phase lag, or phase retard, which is known as "undershoot". Now, if these distortions are mainly the work of the condenser, it would be worth while to look at its physical properties and see how they will affect a wide band signal. Let the signal be split into three bands one of medium frequency for minimum distortion as a reference, one of high frequency, and one of low frequency.

### The Low Frequency Case

A condenser is basically formed by two plates separated by an insulator, and in most signal paths, the function of the condenser is mainly one of charging and discharging. From basic theory it is found that the capacity seen by the signal is dictated by  $C=Q/V$  and since  $Q=It$ ,  $C=(I/V)t$ . Therefore, the charging of a condenser is governed by time, and this can also be read as meaning that in order for the plates of the condenser to reach the value of the applied EMF, the dielectric must have been charged to a value of  $It$  or must have accepted a current for a given time  $t$ . From this reasoning, we can see how phase delay can be introduced, because in order for the condenser to pass the low frequency signal without distortion, its plates must rise to a voltage equal to the source EMF, and since it will take a given time to acquire this voltage, a delay will be introduced. Fig. 2 shows how this phase distortion will affect an L.F. wave. The delay is shown as  $\theta$ . This is a rather exaggerated case, but it does serve to show the effect of phase distortion at L.F. The cause of this type of distortion is also known as dielectric hysteresis, because of the time required to "soak" the dielectric with a charge. A distortionless output calls for a phase shift proportional to frequency as shown in Fig. 3(a), at low frequencies; for the case considered, a shape of Fig. 3(b) would be likely.

### The High Frequency Case

At high frequencies another state of affairs is added to that existing in the L.F. case. Let us consider a very high frequency charge applied to a condenser. This time the charge varies so quickly that it is impossible for the dielectric to derive any form of soak charge. This can be imagined, for no sooner has a positive charge been applied when a negative charge follows very quickly after it. The dielectric can therefore never be fully charged, and only the surface layer of the dielectric can be working at all. This means that at H.F., the dielectric constant has been lowered with respect to its mid-frequency value, thus lowering

the effective capacity. However, at H.F., stray capacities will start to take effect, working in parallel with the signal source to produce additive phase losses. The net result will therefore produce frequency and phase distortion. As frequency is raised still higher, so the phase losses will increase because of the dielectric hysteresis, as more time is going to be demanded to charge the more predominant stray capacities. The H.F. phase response will therefore be similar to that shown in Fig. 3(b).

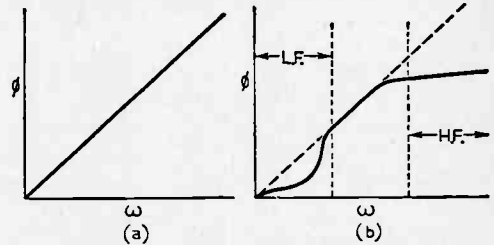


Fig. 3 (a)—A distortionless output needs a phase shift proportional to frequency; (b) shows the distortions considered.

### Analogy of Low and High Frequency Cases

At low frequencies an analogy of the condenser charging can be found in filling a container with a gas. For the container to possess the same pressure as the applied pressure, then it must firstly have stored a full quantity of gas. At high frequencies the effect on the dielectric can be simulated to a deep fast flowing river, where the surface layer may move very quickly but the bottom layer has relatively no movement. This action at H.F. in the condenser is therefore known as dielectric viscosity.

### Conclusions and Cures

This discussion has presented in a very general way the causes of phase distortion. It can however be reduced by means of phase equalisers and special techniques such as derivative amplifiers, or in some cases coaxial chokes. But, the correction of phase distortion is a rather delicate and gentle matter, because, in its correction, no other non-linearities must be introduced which may upset the frequency or amplitude response. For example, the introduction of phase equalisers may at a given point correct phase distortion, but also result in severe ringing on the square wave output. This in effect is only trading one evil for another and is still leaving trouble. However, introduced in the right place, successful correction can occur, the right place being one where impedance uniformity can be obtained between source and phase equaliser. As this uniformity is likely to be disturbed over a wide frequency range, it may have to be obtained by masking the phase corrector into a valve amplifier stage as is found in derivative amplifiers. This method of correction will work, but, unfortunately, it is not very economical, but at times this form of correction may be favoured instead of using many small corrections. It can therefore be seen that phase distortion over a wide band system is something that must be reckoned with, but with thoughtful design it can be kept down to quite small values. ■

COMPLETE RECORD PLAYERS

B.S.R. UAR, 4 Speed Autochanger ... \$6 16 0
B.S.R. UA14, 4 Speed Autochanger ... \$7 19 0
B.S.R. UAD20, 4 Speed Autochanger ... \$8 19 0
Garrard 210/209 ... \$9 19 0
EMI 4 Speed Single Player ... \$4 12 6

4-SPD. RECORD PLAYERS

Latest B.S.R. TU9 Turntable, together with light-weight Starr Galaxy dual sapphire crystal turnover pick-up head. Truly amazing value at \$3.10.0 Carr. 3/4.

PORTABLE RECORD PLAYERS

Takes all sizes, all speeds of Records. Auto-change Unit. Complete in attractive dual-tone Cabinet. Ideal for Gift. Approx. Value \$20. Our price \$14.15.0

RENEW YOUR PICK-UP

With the following CARTRIDGES. ACOS G.P. 65.3, 22/6; SONOTONE 17/-; STEIG and REUTER 17/-; POWER POINT, 17/-. All the above complete with "STARR-GALAXY" Tone Arm, 3/4 extra.

MAINS AMPLIFIERS

3 valve (10F3, 10F14, UO9), 3 watt, 8 in. loudspeaker in two tone case with controls. Ideal for record players, etc.. 19/-. P. & P. 5/6.

100 RESISTORS 6/6

100 CONDENSERS 10/-

Miniature Ceramic and Silver Mica Condensers. 3 pf to 10,000 pf. LIST VALUE OVER £5.

LOUDSPEAKERS

Top Make manufacture fresh. 24in. 13/-; 5in. 10/-; 8in. 19/-; 10in. 22/6; 7 x 4 18/-; 8 x 3, 19/-; 8 x 6, 21/-; 8 x 13, 29/-.

PM SPEAKERS

3 ohms, top makes performance guaranteed: 8in. 5in. 10in. 6in. 8/- 7 x 4 11/- 10 x 6 13/-

UNIVERSAL VOLT OHM MULTIMETER

Reads A.C. and D.C. Volts to 1000. 5 Ranges at 1000 Ohm per Volt. D.C. Current, 3 Ranges to 500 Milliamps Resistance reading to 200K in 2 Ranges. Complete with Prods. 59/6. P. & P. 1/6.

SILICONE DIODES

125 V. 500 M.A., 2 in series make superior replacement for R.M.4 and R.M.5, etc., 8/- each.

VALVES ALL GUARANTEED 3 MONTHS PL81 SOLED. AMAZING VALUE AT ONLY 4/6

EY51 SHORT ENDS 4/6 U25 SHORT ENDS 8/-

PORTABLE TAPE-RECORDER CASES

10 1/2 x 14 1/2 x 3 1/4, 14 1/2 x 12 x 7, 20 1/2. Covered Attractive Resine. P. & P. 3/-. We are always pleased to answer your enquiries, S.A.E. essential.

Latest! Ideal Extension Speakers. Very attractive Resine covered case, size 8 x 5 1/2 x 3 1/2 with 7 x 4 speaker, complete. Our Price 19/6
Baffle Type, with Polished Wood front P.P. 1/6. 19/6

GO-AX standard and low loss, 25 yds. 12/6, 50 yds. 22/6, 100 yds. 42/6, Co-ax. Plugs 1/8. Wall outlet boxes 3/6.

PRE-SET CONTROLS 1K to 2 Meg. 3/3 P.P. 6d.

BLOCKING TRANSFORMERS A wide variety. Suitable for all Sets, from 9/6 up.

ION TRAP MAGNETS Suitable for all Tubes, adjustable, 3/9 P.P. 6d.

Anti-Static Screen Clearances ... 4/3 Tube Switch Cleaner ... 3/8 Tin Silicone Grease ... 13/6 Tube Cellulose Cement ... 4/6 Tin

RESISTORS 6 Watt, wire wound, from 15 Ohm to 6.8K 1/9

MAINS DROPPERS Adjustable: 1 amp to 2K to 3 amps at 800 Ohm 7/9

TUBES

DIRECT FROM OUR FACTORY Carr. & Ins. 12/6. GUARANTEED 6 Months

COMPARE OUR PRICES

Table with columns for tube types (Most Mullard, Mazda, Emiscope, Brimar types) and prices. Includes 'NEW TYPES' column with prices like MW 31/74 \$3.10.0.

13 CHANNEL TV'S

Table models, complete with all valves and tubes. They are untested, and not guaranteed to be in working order

Table with 2 columns: TV model (12in., 14in.) and price (e.g., \$2.19.0, \$4.19.0).

★ VALVES BY RETURN OF POST ★ THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozen). Post: 1 valve, 6d., 2-11, 1/-.

NEW LOW PRICES GUARANTEED 3 MONTHS

FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-military origin. Satisfaction or Money back Guarantee on goods if returned unused within 14 days.

Large grid of valve types and prices. Columns include valve type (e.g., 02A, 1A5GT, 1D6), price, and other specifications. Includes 'NEW LOW PRICES' and 'FREE TRANSIT INSURANCE' headers.

Post: 2 lbs. 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6, etc. No C.O.D.


ALL ITEMS 5% & POST FREE IN DOZENS (Callers always welcome). LIST OF 1000 SNIPS 6d. P.O. BOX 21 (W) 350-352 FRATTON ROAD, PORTSMOUTH.

TECHNICAL TRADING CO.

**ALL TUBES  
GUARANTEED 12 MONTHS  
Carriage Free**  
Speedy Passenger Train despatch.

**NEW**

12"	MW 31-74 etc.	£5.5.0
14"	MW 36-24/44 Limited quantity	£6.6.0
17"	MW 43-69 (limited) CRM 171, 172	£7.7.0

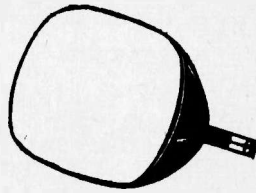

**COMPLETELY REPROCESSED**

TO MAKERS' SPECIFICATIONS!

**REBUILT, RESCREENED, REALIMINISED TUBES OF  
THE HIGHEST QUALITY**

14"	.. .. .	£5.5.0
15"-17"	.. .. .	£5.10.0
21"	.. .. .	£8.0.0

**ASTOUNDING BARGAIN!**

The "Clarion" Transistor Battery Tape Recorder. Push-button controls, 3 1/2 i.p.s. Portable. Durable plastic case. List price 25 gns. Complete with Mike and Tape. **16 GNS.** Carr. 7/6.



**TRADE ENQUIRIES INVITED**

**WESTWAY RADIO**

**LINE OUTPUT TRANSFORMERS**

Direct Replacements for 500 sets.

Beird. T2, T13	.. .. .	53/-
T184, T187, T192, 2014, 1712	.. .. .	60/-
Bush. TV 11A, B; 12A, B; TVF 12A, TUG12A, B; TRG 12A, B	.. .. .	45/-
TV12AM, TV22, 24; TRG24, TUG24	.. .. .	60/-
Cossor, 830, 831, 933, 934, 948, etc.	.. .. .	58/-
Ekco, TS149; TS113-114; T161	.. .. .	47/8
T221, 231; TSC311	.. .. .	55/-
Ferguson, 841, 2, 3; 941 to 945	.. .. .	55/-
900T-908F; 103-146T; 203-246T	.. .. .	66/8
Ferranti, 1413, 1474, 17K3, 17T3-4	.. .. .	45/-
1472, T1205, T1215, T1225, T1325, T1405, T1415, T1425, T1505, T1825	.. .. .	65/-
G.E.C. and H.M.V. mostly 55/- to	.. .. .	60/-
Invicta, T101-104; T108-110	.. .. .	52/-
T114-126; T133-142	.. .. .	60/-
Murphy, V114C, V118C, V118C	.. .. .	45/-
V123C, V180, V173, V200, V202C, V240, 250	.. .. .	57/8
Philips, 114 UFUM, 1115 U, 1437 U, 1448 U, 1726 U, 1746 U, 1747 U	.. .. .	85/-
353A, 463A, 553, 563A	.. .. .	60/-
Pye, LV30, 1ET, CA, VT17	.. .. .	60/-
CTM4, V4, V74, V7, V77	.. .. .	52/8
Ultra, 814, 815, 817, 915, 917, VWS0, Y/YA730, Y/VW84, V/WY720, V710	.. .. .	85/-
(Complete assembly with U35)	.. .. .	14/63, 15/60, 17/63, 17/53, 17/63, 17/63-4, 17/70-1-2, 21/50, 21/60, 21/70-1-2
All Ultra Frame O.P.T.'s	.. .. .	60/-
Add post 2/6	.. .. .	26/8

100 mixed resistors, 1W-2W-7/8 post 1s.

**SKANTEST**

Tests Line Output Transformers—Deflector Coils—Blocking Oscillator Transformers, etc. for shorting turns and open circuit. SKANTEST is a fraction of the cost of any similar tester available in this country. SKANTEST • Saves hours of work. • Is portable. • Easy to use. • Increases good will. No TV Serviceman should be without SKANTEST. SAVE TIME! SAVE MONEY! Free Leaflet available. £7.10.0. post etc. 5/-.

S.A.E. with enquiries please.  
5 Westward Way  
Preston Road, Harrow, Middx.  
Tel: WOR 2663

**Better, Brighter  
Picture Tubes**

**BRAND NEW THROUGHOUT  
excepting glass.**

12in.	... £4.10.0	14in.	... £5. 5.0
15-17in.	... £5.15.0	21in.	... £7.15.0

New Silver Screen and Aluminising. All makes Mullard, Mazda, Emiscope, Cossor, Brifmar, Emitron, etc.

**REBUILT MULLARD AND MAZDA  
TUBES**

12in.	... £3. 0.0	14in.	... £4. 0.0
15-17in.	... £4.10.0	21in.	... £6.10.0

All Tubes Fully GUARANTEED 12 MONTHS. Dispatch same day. C.W.O. or C.O.D. Carriage and Insurance 10/-.

**S.T.S. Ltd.**

35 POUND STREET, CARSHALTON,  
SURREY.

Telephone: WALLINGTON 9665

**EXPRESS ELECTRONICS**

**ROSEDENE LABORATORIES  
KINGSWOOD WAY, SELSDON, SURREY**

**VALVES NEW TESTED AND GUARANTEED  
FOR THREE MONTHS**

1C1	7/6	8BA4	6/-	8D3	4/-	DF98	5/-	EF41	9/-	PCL84	7/-
1C3	8/-	8BE6	7/-	12AB5	10/-	DH76	6/-	EF90	8/-	PL81	12/8
1P1	8/-	8BH6	5/0	12AT7	6/-	DH77	6/-	EP96	8/-	PL82	7/-
1P3	7/6	8BJ6	5/0	12AU7	5/6	DH142	8/6	EP91	4/-	PL83	7/6
1PD1	8/-	8BR7	8/0	12AX7	6/-	DH150	10/-	EP92	5/6	PY81	6/0
1PD9	7/6	8B7	10/6	12BE6	8/6	DK91	7/6	L41	9/6	FX82	7/6
1L4	6/0	8BW6	7/6	12BH7	10/6	DK92	7/6	EL84	7/-	FX83	7/6
1P1	8/-	8BW7	7/-	12K9GT11K	11/-	DK96	8/-	EM84	10/-	R19	11/6
1P10	7/6	8C10	9/-	12Q7GT	7/6	D192	7/6	EM85	10/-	U28	9/6
1P11	7/6	8D2	4/-	18A5	9/-	D194	6/6	EY81	7/6	U32	7/6
1B5	8/-	8F12	4/-	25A80	8/6	D196	8/-	EY81	10/-	U78	7/6
1B3	6/-	8H9GT	8/-	25L44T	7/6	E991	4/-	EZ40	7/6	U78	8/-
1T4	7/6	8J7GT	7/6	25T40	9/-	EB4C1	10/-	EZ80	6/-	UBC41	8/6
1U3	5/6	8K7G	5/6	30C1	6/6	EBF90	8/8	EZ81	6/0	UCH42	9/6
3Q4	8/-	8K90	6/0	30L1	7/-	EC081	6/-	KT330	6/-	UF41	8/6
3E4	7/6	8Q7G	6/6	35L6GT	8/-	EC092	5/6	KT98	11/6	UL41	8/6
3V4	8/6	8LGT	6/-	35W4	8/6	EC093	6/-	N17	7/6	UY41	7/6
5U4G	7/6	8N7GT	6/-	35Z4GT	8/-	EC484	7/6	N18	8/-	W76	6/6
5Y3GT	5/-	6V8G	7/6	53KU	10/6	ECF90	8/6	N19	7/6	W142	8/6
5Z4G	9/6	8X4	5/-	57B3	7/6	ECF92	8/-	N709	7/-	X17	7/6
6AL5	9/6	8X5GT	6/-	50	6/-	ECH42	9/-	PCC84	6/0	X142	8/-
6AM6	4/-	8X8GT	7/6	DAF91	7/6	ECM81	10/-	PCF90	6/0	X150	8/-
6AT8	6/-	7B7	8/6	DAF96	8/-	ECL90	5/6	PCF82	7/-	Z77	4/6
		787	9/6	DF91	7/6	ECL82	9/-	PL82	8/-	ZD17	5/6

High Stability Resistors 1W 5% 50 Q to 1M. 5d. Migot Ceramics 500 v. 2d. Coax. Super quality 1in., 3d. yd. Plug 9d. Booklets 9d. Silicone H.T. Beets. 250v. 300 MA 1in. x 1in. 17/6. Contact Cooled 250v. 50 MA 6/6. 85 MA 8/6.

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES. D. P. switch 4/- Less switch 2/6. Values 10K to 2M, B9A B7G v. holders 9d., Screens 9d.

**VALVES MATCHED IN PAIRS**

EL84 17/-, N709 17/-, 6V6G 17/-, 6BW6 18/- per pair. Push Button O.P. Transformers for above 3-15 Q 14/6, P. & P. 1/6. 12in. P.M. Speakers 3 Q 94/6. Baker's "seibsters" 12in. 15 Q 15W, 90/-, 12in. Stereo Model, £7.7.0.

**SETS OF VALVES**

DK91, DF91, DAF91, DL92 or DL941, 18/6 ECH42, EF41, EBC41, DK96, DF96, DAF96, DL96, 27/8 EL41, EY40, 27/8 EL41, EY40, 27/8 IC3, 1P1, 1PD1, 1P1, 27/8 UCH42, UF41, UBC41, 1R5, 1T4, 1B5, 3R4, or 3V4, 27/8 UL41, UY41, 35/- Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

# A Precision Wobbulator

By N. Mears

(Continued from page 83 of the November issue)

## USING THE INSTRUMENT

**L**AST month the 200c/s multivibrator and the 20c/s multivibrator and sawtooth generator were aligned; the sawtooth linearity must now be adjusted and the oscillator aligned before the method of using the wobbulator can be explained.

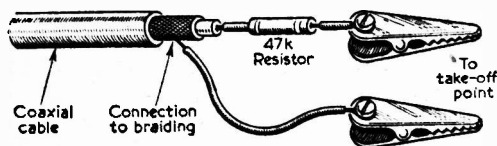


Fig. 16—Terminating the cable for attachment to the receiver take-off point.

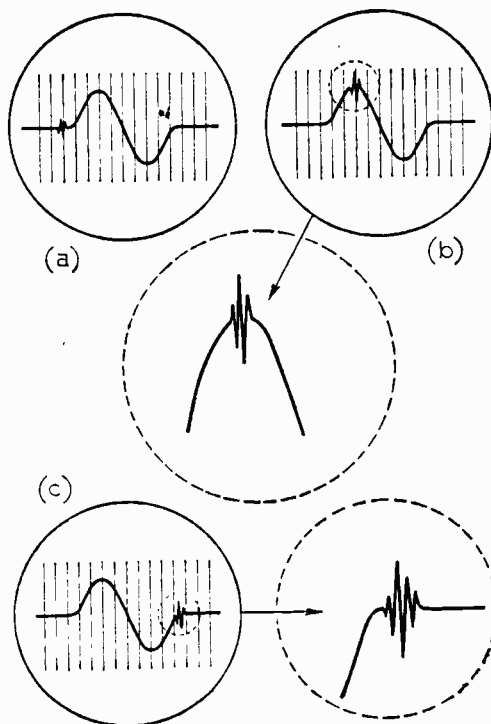
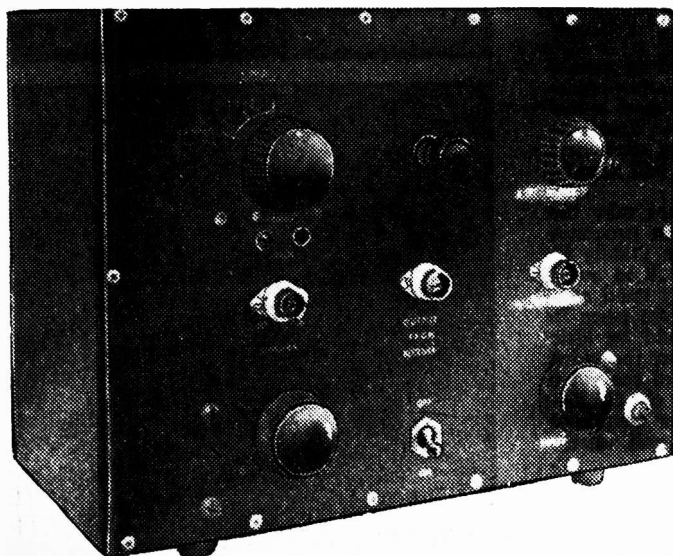


Fig. 17—The calibration of the sweep (see text).

### 3. Adjustment of sawtooth linearity

- (a) Connect the Y-amplifier lead of the 'scope to the cathode of the ECC82 and R29.
- (b) Set VR4 at its maximum setting.
- (c) Check the shape of the sawtooth wave.

If it is still too linear, increase the value of R29 a little, say to 2.2k.

The linearity should be such that the exponential shape of the wave is just noticeable—a linear sweep is not wanted, but too distorted a wave is not required either. The ideal shape is such that the sloping portion—the sweep—becomes nearly horizontal just at the very end of the sweep. The shape is not very critical, as long as extremes are avoided.

### 4. Alignment of Oscillator

- (a) Attach 6in. of wire to the R.F. output socket to act as a short aerial. Set the R.F. control (VR6) to maximum.
- (b) Tune the receiver well away from any station, and turn up the volume control.
- (c) Set the "sweep" control (VR4) to about  $\frac{1}{5}$  of its range.

(d) Rotate the core of the coil until reception is obtained.

(e) Check that I.F. is now generated by reducing VR4 setting to zero, and test for a heterodyne whistle on all stations.

It may well be that the R.F. output gives too little output, even at maximum, for a

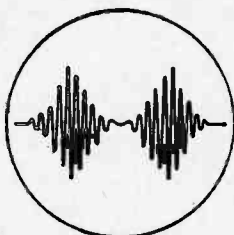


Fig. 18—If an amplitude modulated signal is used to produce a marker pip, the pip is of the form shown above.

**(A)—Discriminator curve for a VHF F.M. transistor portable.**

well-screened receiver, when stray pick-up is used. If so, connect the R.F. socket direct to the aerial terminal of the receiver via the usual coaxial lead, and adjust the R.F. control for a suitable output. If this fails, connect the coaxial cable direct to the grid of the frequency changer.

The wobblulator is now ready for use.

**Method of Use**




To avoid any instability, an audio point in the receiver would be best for connecting to the "output from receiver" socket of the wobblulator. To avoid hum pick-up the signal should be taken from as early a point as possible, best of all from the detector load resistor; this however tends to cause instability by introducing unwanted feedback. To avoid this, a coaxial lead should be terminated by a resistor of value 47k, as shown in Fig. 16.

**(B)—Response curve for an M.W. transistor portable.**


Crocodile clips afford a secure method of attachment; for VHF and TV use, the miniature crocodile clips are best, and the writer has used ladies' hair clips (cut-down) with good effect. Since the detector output is not very great, the usefulness of the built-in pre-amplifier mixer V4 will now be apparent.

If hum pick-up is found to interfere with the displayed response curve, the waveform generator can be made to run at 250c/s (flat on middle C) and 25c/s respectively. Hum is difficult to avoid with mains receivers, but if thoroughly good connections are ensured, and precautions are taken in layout during construction, there should be little interference found. With a TV receiver the video output should be taken from the grid of the video valve, *not from the cathode or grid of the CRT*—the latter is more accessible, but the extra trouble of reaching the earlier take-off point is well worthwhile.

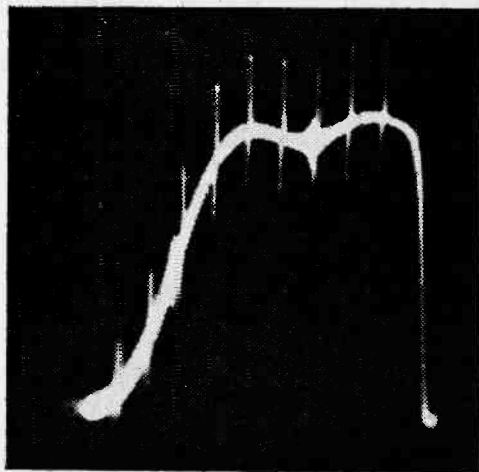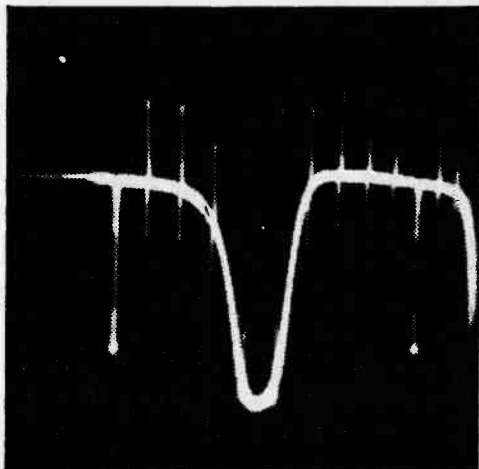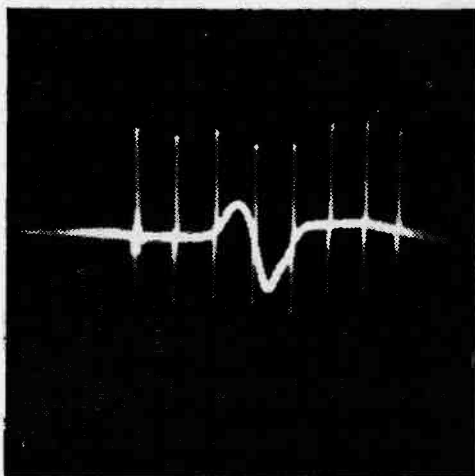**(C)—Response curve of a TV receiver—note the calibration pip.**





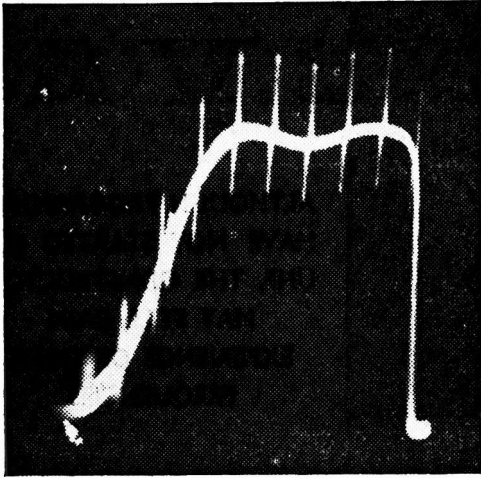

**Calibration of Sweep (Fig. 17)**

For this process, an external calibrated signal generator is required. The connections are made between wobulator, oscilloscope and TV receiver, and the signal generator is provided with a short "aerial" at its "high-output" socket. When the response curve is displayed, set VR4 for maximum sweep and centralise the response curve by adjusting the D.C. control VR5. Adjust so that a recognisable point on the curve coincides with a marker.

**Marker Pips**

Using an unmodulated output, tune the signal generator slowly through the I.F. listening for the sound output (unless the TV vision curve is being displayed!) and watch the response curve closely. A small "pip" will become visible when the receiver begins to respond to the signal generator output (see Fig. 17(a)).

As the pip approaches the I.F. its amplitude will become larger; when it passes through the peak response position it may well obscure the response curve altogether, and as it passes out of the I.F. range it will become smaller and finally disappear. It should be clearly visible for several markers. Note the number of markers covering the range of the pip's visibility. From this, the total sweep can be calculated, because the signal generator frequency difference between the pip's appearance and final disappearance is known.

**A.M. Signal**

When an "amplitude-modulated" signal is displayed, at the central point the "pip" will appear similar to that shown in Fig. 18—the "pip" splits into two halves. If the pip blots out the curve altogether, the signal generator output is too high; reduce it by the control provided or by shortening the "aerial".

Owing to lack of space, it has been found necessary to hold over until next month "How TV Sets Work" and "Tracing TV Faults"

The calibrations are not the same on all ranges, but once found, they are quite stable and the markers thus have a definite meaning although the meaning is different for each range. The writer's instrument has the following calibrations:

- 465kc/s—the markers are at 8kc/s intervals.
- 10.7Mc/s—the markers are at 200kc/s intervals.
- 34-38Mc/s—the markers are at 500kc/s intervals.

The accompanying illustrations show the response of the following receivers:

- (A) A VHF transistor portable, with interfering I.F. signal from a short-wave transmitter.
- (B) Transistor receiver for broadcast wavelengths. The long markers represent the ends of the sweep. This came out the "wrong way up" because of the particular diode connection in the detector stage.

◀ (D)—The same response curve as in (C) without the calibration pip.

- (C) A commercial television receiver—the calibration pip is in the centre of the response curve.

- (D) The same as (B) above without the calibration pip.

In using the wobulator care must be taken not to arrange matters so that the D.C. control sets the standing bias on the diode at less than two volts or so. The optimum setting is about 6 or 7V, corresponding to about 3/4 maximum, when full sweep is used. The best setting can readily be found by experiment, and the control can then be used to shift the trace a little each way as needed. This is about the only precaution needed in use; the operation of the instrument is very simple and has proved to be virtually trouble-free. ■

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

☆ CHOOSE A "PRACTICAL" PRESENT ☆  
THIS CHRISTMAS

☆ A gift subscription for PRACTICAL ☆  
TELEVISION will bring your friends a ☆  
reminder of your good wishes every month ☆  
throughout 1962... and all through the ☆  
year they'll thank you for the practical ☆  
help it contains.

☆ Either send your friends' names and ☆  
addresses, together with your own and ☆  
remittance\* to cover each subscription, ☆  
to The Subscription Manager (G.2), ☆  
PRACTICAL TELEVISION, Tower House, ☆  
Southampton Street, London, W.C.2., or ☆  
you may place your instructions with one ☆  
of the leading newsagents or bookstalls, ☆  
who will be pleased to make the necessary ☆  
arrangements.

☆ Whichever way you choose, your friends ☆  
will receive a Christmas Greetings Card ☆  
announcing each gift.

☆ \* RATES (INCLUDING POSTAGE) FOR ☆  
ONE YEAR (12 ISSUES):—U.K. £1.5.0, ☆  
OVERSEAS £1.3.6, CANADA £1.2.0. ☆

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

# A Band V Aerial

ALTHOUGH PROGRAMMES  
HAVE NOT STARTED ON  
UHF, THE CONSTRUCTOR  
MAY STILL GAIN  
EXPERIENCE OF THESE  
FREQUENCIES

FROM time to time during the past two years the writer has passed on to the home constructor some of his results in experimenting with frequencies in the region of 650Mc/s. In June 1959 an experimental Band V converter was described, and in October and November 1959 a signal generator circuit was published in this journal. The exhibition by the BBC of colour

television at the Radio Show this year has no doubt stimulated the interest of many. If the Pilkington Committee does eventually recommend to the Government that colour transmission should be started it will doubtless go out on Band V. The BBC intends to radiate high-power transmissions in 1962 and is currently operating low-power experimental broadcasts from Crystal Palace.

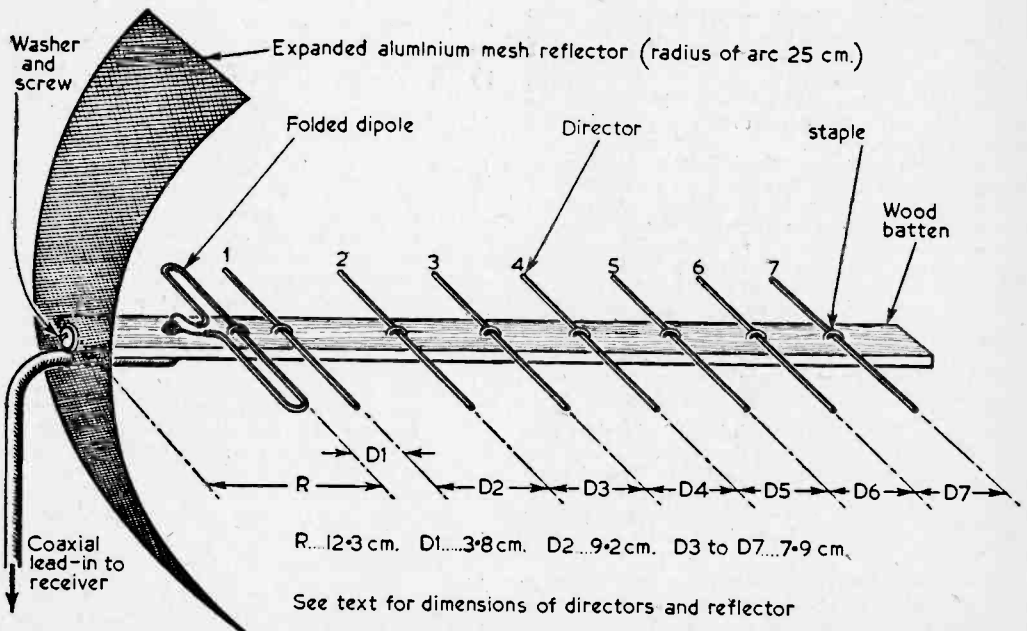


Fig. 1—The Band V aerial—the distances between the elements are indicated above while the dimensions of the elements themselves are given in the table.

### Preparation

Those living within range will doubtless be interested to attempt reception of these experimental broadcasts, and others who would be able to receive the high-powered transmissions in due course will wish to prepare their equipment in good time. In this article a suitable aerial array is described, while in future issues details of a fully tunable receiver will be given.

### Design Considerations

At such frequencies it is important to consider the type of aerial in relation to the type of receiver likely to be used. Until valves or transistors definitely designed for the UHF bands are generally available the experimenter will tend to

#### TABLE OF TUBULAR LENGTHS (See Fig. 1)

##### Directors:

No. 1 20.5cm	No. 5 19.7cm
No. 2 20.3cm	No. 6 19.5cm
No. 3 20.1cm	No. 7 19.3cm
No. 4 19.9cm	

Dipole according to the bending diagram.  
Reflector 12.3cm behind.

#### TABLE OF DIRECTOR DISTANCES

(measured from the reference member of the folded dipole)

No. 1 3.8cm	No. 2 13cm
-------------	------------

and the rest spaced 7.9 cm apart.


Note.—The smaller the dimensions of an aerial the poorer is its reproducibility. An effort should therefore be made to work to the nearest millimetre.

The normal Yagi array suffers from the disadvantage of having an appreciable response if facing directly away from the transmitter. This defect can be removed by replacing the conventional rod reflector by a parabolic cylindrical reflector—which in practice can be a plain cylindrical reflector, since the difference between circular and parabolic sections is not large for the portion of the cylinder actually used. At lower frequencies this is not practicable for home installations because of its size and weight—and in any case is much less necessary.
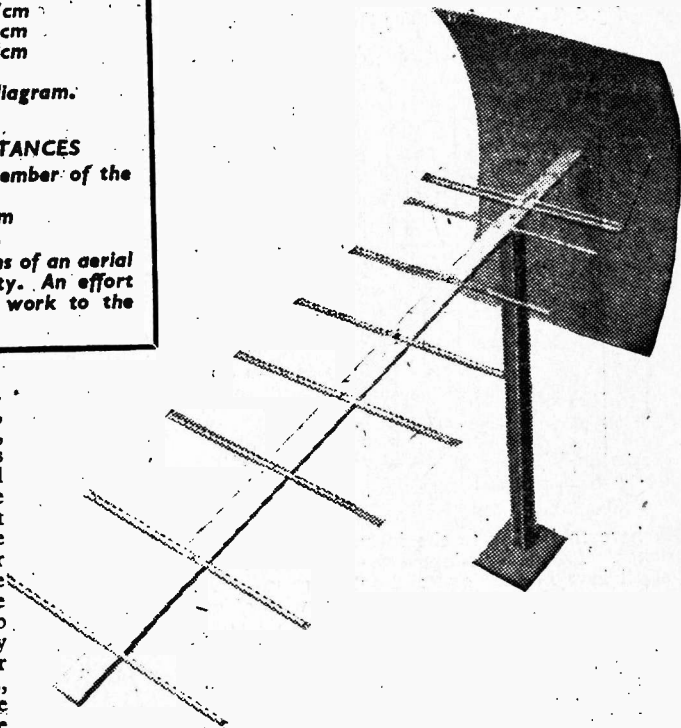
### Construction

The materials required for this aerial are very modest — they are as follows: one piece of expanded aluminium, similar to that used for loudspeaker grilles; measuring 40cm x 23cm, is required for the reflector. The dipole and directors

use what devices can be obtained. This requirement will, in general, rule out an R.F. stage in the receiver, and the "front end" will thus consist of a silicon crystal and local oscillator. These will be associated with a band-pass input filter, partly because there will be little protection against oscillator radiation. To minimise further the nuisance of oscillator radiation the aerial must have not only sharp directional properties but a very high "back-to-front ratio," together with an absence of side lobes. Thus, any oscillator radiation will be directed chiefly back toward the transmitter, where it does negligible harm.



The completed aerial

are all of  $\frac{1}{4}$  in o.d. copper tubing (from a garage), and 6ft of this will be needed or a little over. A wooden batten 1 in. x  $\frac{1}{4}$  in. and 2ft 6 in. long is also needed, together with enough wood to make a stand about 2ft high on a firm base. Small galvanized iron staples are also needed and brass screws as necessary.

As bought the copper tubing is unrolled from a coil and cut off by the garage storekeeper. It is never straight enough for use and the first thing to do is to straighten it out. This is done by pulling it until it stretches, and here something

thought to the robustness of the garage structure, to say nothing of the strength of the bumper of the car, and to do nothing rashly.

### Preparing the Elements

When the tubing has been stretched it is laid flat on a bench and cut into the required lengths. Each piece is carefully cleaned with metal polish and is dropped into really hot detergent solution and scrubbed clean ready for silver-plating.

In the past the writer has found that the silver-plating is rendered much more durable and the surface much less likely to lift or "blister" if, before putting it into the electrolyte bath, the copper is given a very light coating of mercury. This is applied in the following way:

### Mercury Layer

The least possible quantity of mercuric chloride is bought from the local chemists. (Not remembering anything from his schooldays about penny-weights or grains, the writer persuaded the local chemist to sell him five grams, which proved to represent about five years' needs.) Mercuric chloride is very poisonous and the usual precautions must be taken with it, both in solid state and in solution. It is dissolved in

a good quantity of water and some sodium cyanide solution added to it. The mixture is then applied to a clean swab of cotton wool and, holding the copper tubing with a rag soaked in detergent solution (to keep away any grease from the fingers), the tube is rubbed briskly until it assumes a uniform silvery appearance. After treatment the tube is then silver-plated in the usual way. If any appreciable time is to elapse between mercury treatment and silver-plating the tube can be kept under cold water. However, the exposed mercury surface deteriorates in time and the aim should be to plate straight away; no more than ten to 15 minutes' delay should be allowed.

After plating heavily, the surface of the tubes should be polished with plate polish (not metal polish, which removes too much silver).

### Effects of Constructional Change

If silverplating is not carried out the aerial will require different design. At the frequencies concerned the material and type of surface has a noticeable effect on the spacing of the directors as well as on the properties of the finished aerial. The reason for this is not obvious and it has not been investigated theoretically by the writer, who records his findings without attempting an explanation.

The reflector is next made up by cutting the expanded metal to size and bending to the necessary radius. This may be done well by using a cake tin from the pantry as a bending bar. Such tins often have a diameter of about 15 in, so one can hardly wrap the metal round the tin and leave it at that. However, by judicious pulling a creditable bend can be made and the reflector can easily


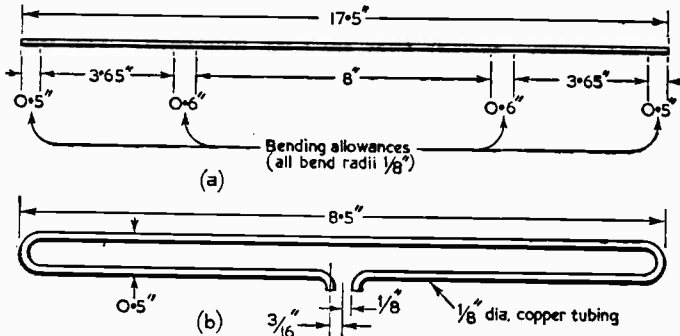


Fig. 2a—The dimensions of the copper tube from which the folded dipole is formed.

Fig. 2b—The completed folded dipole.

Fig. 3 (below).—Positioning the folded dipole.

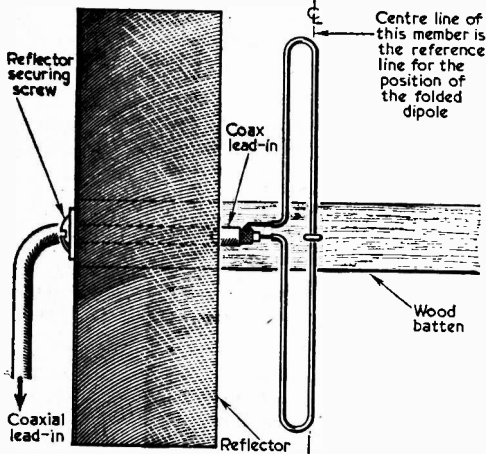

will have to be left to the ingenuity of the constructor. The writer adopted the device of making a small loop in each end and soldering up. One loop was attached by a stout fencing wire of galvanized iron—about  $\frac{1}{4}$  in in diameter—to a main roof beam of his garage. The other loop was similarly attached to the front bumper of his car, which had been run into position and jacked up 6 in. When the jack was lowered the tubing stretched very nicely and controllably. However, with such methods one needs to give careful

be checked against a circle of 10in radius chalked out on a suitable surface. Fortunately, the accuracy required here is not especially high.

A dead central hole will already have been marked out to take the retaining screw, together with a  $\frac{1}{4}$ in. diameter hole through which the coaxial cable will be led.

#### Folded Dipole

All that now remains to be done is to mark out and bend the folded dipole. Actually this is probably best done before silver-plating; although polishing the bends is not too easy, the ready-made dipole is easier to handle in the plating bath than the straight tube from which it is fashioned.

The wooden batten is now marked with the positions which the rods will occupy, and it should be noted that the position of the folded dipole is referred to the centre line of its continuous member. The sides connected to the coaxial cable are turned inwards toward the reflector. Fine holes are drilled in the wood each side of these positions so that when the staples are knocked in, securing the aerial elements, the wood does not split.

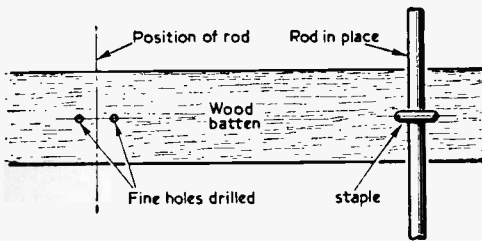


Fig. 4—The method of securing the elements of the aerial.

#### Connecting the Cable

When all the elements have been secured to the batten, the coaxial cable (which should be of the low-loss type) is pushed through the hole in the reflector, along the underside of the batten, through a hole drilled in the batten, and is brought up so that the conductors can be connected to the free ends of the aerial. The outer insulating layer of the cable should have been removed as far back as the reflector so that the reflector can make contact with the outer braiding. The edges of the hole are now pushed down hard upon the braiding so as to make a good contact. Finally the aerial is mounted on its stand and the job is done.

#### Outdoor Aerial

It will be seen that this construction is not intended for out-of-doors use. If it is intended to work it permanently on a mast additional precautions must be taken as follows . . . The reflector will have to be supported in some way. This can be done by adding bracing across the aperture with strips of polystyrene or Perspex secured to the batten. The batten itself will preferably be made of Perspex or paxolin as wood may warp badly in wet weather and acquire a permanent set. Two staples instead of only one should be used to secure the directors, or preferably the rods should be made a force fit with holes drilled through the batten. All conducting surfaces should be coated

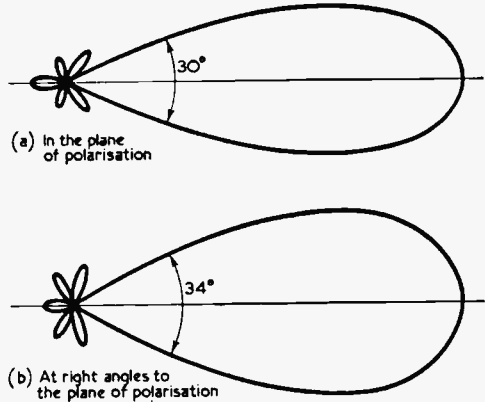


Fig. 5—Polar diagrams of the Band V aerial in the plane of polarisation and at right-angles to it.

thinly with polystyrene varnish or epoxy resin to avoid atmospheric contamination of the polished silver surfaces. Paint is, of course, no use, and probably the best protective coating would be a few millionths of an inch of gold, plated direct on to the silver.

#### Performance

The performance of the aerial is as follows: Centre frequency, 660Mc/s; power gain, greater than 100; back-to-front ratio, about 1/60; band width, 14Mc/s; beam-width in the plane of the elements, 30° approximately; beam width at right-angles to the elements, 34° approximately. The polar diagrams for this aerial are shown in Figs. 5(a) and 5(b).

#### Transmission Schedule

The BBC has kindly afforded the following information about the transmissions now being made.

Times: Daily (including Sundays), 9 a.m. to 10 p.m. (except when the channel is required for outside broadcast links). Carrier frequency: 659.75Mc/s. Power: Peak 2.8kW, mean 1.4kW. Modulation: Square wave, pulse repetition frequency 1,000c/s (amplitude modulation). Identification: 3sec silence every 60sec. Polarisation: Horizontal.

It is probable that when high-power transmissions are resumed the frequency will be close to the above, since major retuning of the transmitting klystrons would otherwise be necessary. Meanwhile the experimenter can obtain experience either with these transmissions or with the signal generator referred to at the beginning of this article.

There is one practical point of importance in the setting up of the aerial for use with transmissions. That is, care should be taken to erect the aerial with accuracy. Since the beam width is quite narrow, alignment on a compass bearing alone may result in poor reception. The need to apply corrections for magnetic variation and local compass deviation is stressed if the compass is used. It is probable that the most accurate method is to use the sun, which is always due south at noon GMT, or the Pole star as the reference. ■

# INTERFERENCE

## SUPPRESSION


By T. S. Ferriers

### CAUSES AND CURES OF TVI

**T**HE best way of proving whether or not an electric tool or other domestic electrical appliance is a source of radio or television interference is to set up the appliance as it would normally be used and observe the effect on one's own receiver. Before the appliance is switched on, however, the receiver should be tried to ensure that it is free from interference and then it will be conclusively evident that any interference from the speaker or on the screen is caused entirely by the appliance under test.

#### Wear and Vibration

Almost all recently made tools and electric motors are suppressed for both radio and television, but, even with this type of equipment, there is always the possibility that wear on the motor brushes or commutator rotor will eventually cause interference. Continuous vibration may also loosen the internal suppression components causing random bursts of very heavy interference when the appliance is in use.

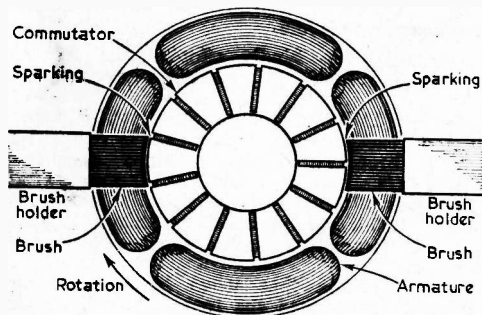

**Fig. 1**—Interference can be caused by sparking occurring between the brushes and commutator of armature type electric motors. The trouble is aggravated by wear on the brushes or commutator. Induction motors, which do not use brushes, are free from interference.


#### What is Reasonable Suppression?

It should be understood that perfect interference suppression is virtually impossible to achieve. This would necessitate costly anti-interference precautions at both the receiver and source of interference. Interference precautions at the source are, therefore, based on the assumption that the receiver itself is installed with due regard to interference pick-up.

For example, if "reasonable" suppression is undertaken on the appliance and yet a nearby neighbour suffers interference because his aerial is mounted, say, in the roof-space close to the mains wiring, then it becomes the responsibility of the neighbour—viewer or listener—to improve his installation before making a complaint to the Post Office. A radio dealer would advise on such a problem and, if necessary, the dealer himself may consult the Post Office.

#### The Effect of Signal Strength

How much interference is seen on a picture or heard from a loudspeaker depends not only on how much interference the appliance is radiating but also on how much signal the set is receiving. If the wanted signal is weak, the interference will be equal to or above the wanted signal, in which case it would override the picture and sound and cause extremely disturbing noises and flashes. On the

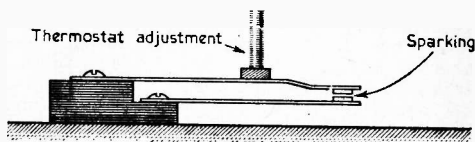

**Fig. 2**—Interference can also be caused by sparking and arcing between the contacts of thermostats. The arcing may be prolonged on 'switch-off' if the thermostat tension springs are weak.

other hand, if the wanted signal is much stronger than the interference, then it may be almost totally masked by the wanted signal and hardly show up at all.

Clearly, then, in areas where the signals are strong (close to a transmitter), a far greater level of radiated interference can be tolerated than in areas where the wanted signals are weak. This means that "reasonable" suppression in a strong signal area may be looked upon as "poor" suppression in a weak signal area.

Manufacturers of electrical appliances usually design their suppression circuits on the assumption that there will be an average signal level at the receiver, of a level, for instance, that would work a television set adequately from an H-type aerial. Such suppression would, therefore, be almost perfect in areas close to a powerful station, but may be below "reasonable" in areas where the signal strength is very weak.

#### Radiation from Appliance

Interference to television reception is almost entirely radiated direct from the appliance and

connecting cable. The appliance and cable, in fact, act rather like a transmitting aerial and, the closer the appliance to the receiver, the stronger will be the interference. Thus, when an appliance is checked on one's own receiver some small interference effect will almost certainly be observed. This test should, of course, be made with the set receiving a signal, for in the event of there being no programme, the receiver would be highly sensitive to even the smallest amount of interference.

If the interference effect appears to be excessive on the nearby receiver, it often pays to visit neighbours to see whether their reception is being affected. If the interference is highly disturbing, steps should be taken to improve the suppression of the appliance.

**Cause of Interference**

Interference of the nature under discussion is caused entirely by sparking taking place within the appliance. Whenever there is a make or break in an electrical circuit, sparking takes place. This happens even when an ordinary electric light switch is operated and may cause a small click on sound and an instantaneous flash on vision. Such interference is so short-lived that it is not troublesome. However, when sparking is prolonged the resulting interference can be very disturbing.

**Prolonged Sparking**

Prolonged sparking takes place between the brushes and the commutator of electric motors having armatures as shown in Fig. 1. As the armature and commutator rotate, so the current is disconnected and connected very rapidly and the sparking is almost continuous. This produces a continuous buzz on sound and bright, horizontal lines across the picture. The amount of interference radiated is almost proportional to the size of the spark, which means that on a motor with worn brushes or commutator the interference is likely to be very high indeed.

Similar sparking occurs between the contacts of a thermostat, as shown in Fig. 2. This happens only when the control comes into or goes out of operation. With a faulty thermostat, however, the sparking on disconnection can be prolonged due to arcing between the contacts, so instead of short-lived interference, prolonged buzzing and flashing may well be produced. Electric irons and electric blankets cause this type of interference, but immersion heater thermostats are often sufficiently well screened by the earthed water jacket which surrounds them, although they also may cause interference.

**The Cure**

If the appliance is obviously defective in itself, then this should be attended to before suppression or additional suppression is contemplated. It should be noted that there are two basic suppression arrangements—one for radio and the other for television—and it does not necessarily follow that radio suppression will have been achieved after dealing with an appliance for television, and vice versa. Where an appliance is affecting both radio and television sets, it is necessary to combine the suppression arrangements recommended for each.

**Suppressing TV Interference**

When suppressing a motor for television interference, it is essential that the suppression components be mounted as close as possible to the part of the motor concerned. For example, if a choke is to be connected to the brushes, then it *must* be mounted inside the motor housing adjacent to the terminal of the brush holder. This does not follow to such an extent with radio suppression, for such interference is mostly mains-borne, and the principle in this case is to prevent the interfering currents from travelling out of the appliance into the mains wiring. We have already seen that with television interference, direct radiation is the important factor.

**Suppressing Radio Interference**

Small chokes and capacitors have been developed by various firms specialising in suppression equipment, for inclusion inside the motor housing, but, even so, ingenuity is often necessary in order to


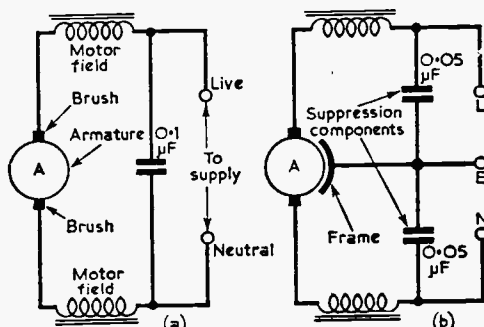


Fig. 3—These suppression circuits are designed for use on small appliances in areas of reasonably good signal strength and moderate interference: (a) and (b) (above) are for radio and (c) and (d) (below) are for television.

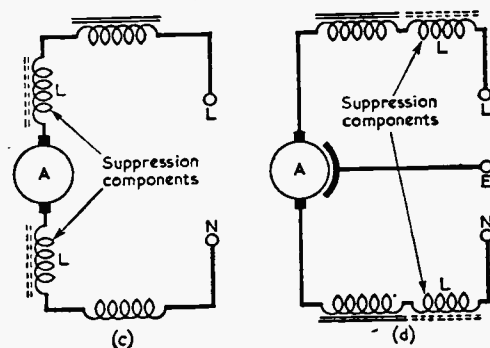

accommodate a complex suppression arrangement inside a portable appliance. If radio as well as television suppression is required, it may be necessary to fix the radio suppression components outside the housing.

With this in mind, Belling & Lee have designed a series of suppression units that can quickly be fitted to the flex lead within about 12in. of the appliance. Similar arrangements in the form of adaptors for plugging in at the power output sockets are also available from radio dealers. The

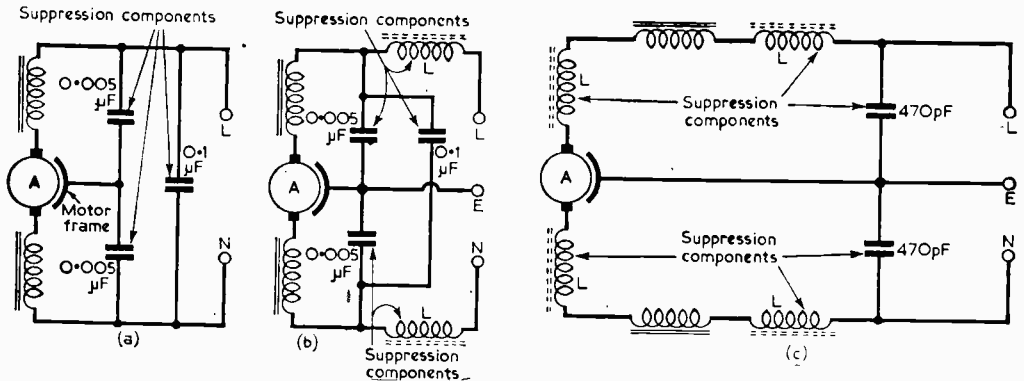


Fig. 4—These circuits are also for small appliances but have a better performance than those of Fig. 3 (a) and (b) (above) are for radio and (c) (top-right) is for television.

latter type are ineffective on television, but the flex lead type are also suitable for television when moderate suppression is required provided they are connected close up to the offending appliance.

#### Moderate Suppression

In Fig. 3 are given four circuits for moderate suppression of portable appliances. At (a) is the simplest of radio suppression circuits and takes the form of a capacitor across the mains input terminals. If the appliance uses three-core cable (e.g., with a green earth wire), the arrangement at (b) should be used. Special capacitors for this purpose are available.

Similarly, at (c) is shown the simplest of television suppression circuits which uses a pair of television chokes connected close to the brushes. At (d) is the arrangement for a three-cored appliance, but here it may be better to include the chokes *L* as in (b), depending on results. When checking the success of suppression, it is essential to reassemble the motor housing and run the unit in the normal way with all the screws properly tightened.

#### Excessive Suppression

In weak signal areas, suppression circuits after the style of those in Fig. 4 (a), (b) and (c) are often called for. Fig. 4 (a) is for radio and could be used on a two or three terminal appliance, but if only two conductors are used, it is still necessary to take the junction of the two  $0.005\mu\text{F}$  capacitors to the motor frame. Connection should be made to a soldering tag clamp beneath one of the motor securing screws.

The circuit at (b) is also for radio and gives even better performance than (a). This is due mainly to the two R.F. chokes *L*, which in this circuit should have an inductance of about 1.5mH.

The arrangement at (c) is for television only, and the improved performance is given by the use of four television chokes and the two 470pF capacitors. As already pointed out, it is essential that all these components are mounted as close as possible to the motor unit, preferably in the housing.

#### Suppression Components

For television suppression of small appliances there are two basic components, small chokes wound

on dust-iron cores and small 470pF ceramic capacitors. The chokes are rated at 1A or 2A, according to the current requirements of the appliances, and the capacitors must be rated at 300VW A.C., at least.

Capacitors for radio suppression should have a rating of 250VW A.C. and delta-connected units containing three capacitor elements, as in Fig. 4(b) are available in values of  $0.1\mu\text{F} + 0.005\mu\text{F} + 0.005\mu\text{F}$  and  $0.1\mu\text{F} + 0.01\mu\text{F} + 0.01\mu\text{F}$ . Chokes for radio suppression are somewhat larger than their television counterparts, depending upon inductance and power rating, but are also available in 1A and 2A ratings.

#### Fitting Suppressors

When fitting, extreme care should be taken to avoid the possibility of internal short-circuits and adequate insulation should be adopted throughout. The components should be mechanically rigid and wired in a sound electrical manner. Capacitors greater than  $0.05\mu\text{F}$  should never be connected to the frame of an unearthed appliance, but this should not be taken to mean that it is safe to run an appliance without an earth. All appliances featuring an earth conductor *must for safety reasons be connected to an efficient earth point*, such as to the earth pin of a three-pin plug. ■

FRIDAY, FEBRUARY 2nd, 1962

## A FILM SHOW

(in collaboration with Mullard Ltd.)

CAXTON HALL, WESTMINSTER  
at 7-30 p.m.

Send for your free tickets now, marking your envelope "Caxton Hall" in the top left-hand corner and enclosing a stamped addressed envelope (at least  $3\frac{1}{2}\text{in.} \times 6\text{in.}$ ) for the tickets.

The films to be shown will be announced later, but, as in previous years, the programme will be arranged to appeal to all who are interested in radio.

The demand for tickets will be great; order yours NOW.



# Underneath the Dipole

A MONTHLY  
COMMENTARY

By Iconos

**F**EATURE cinema films, especially old ones, are said to be unpopular with viewers these days. Maybe some of them are rather bad and dated, but just now and again we see on television a film from the cinemas which is neither ancient nor bad. The ITV programme companies have had a few good vintage films but recently it has been the BBC which has scored the successes. One of these was "Cast A Dark Shadow", a modern mystery starring Dirk Bogarde and Margaret Lockwood, which had been adapted from a stage play "Murder Mistaken" which I had seen performed by a West-end company in London and also by a repertory company at Aldershot several years ago. "Cast A Dark Shadow" was a "who-done-it", with light comedy and strong drama mixed in the usual two-to-three proportions but, in this case, including a few novel twists. The story concerned the activities of a plausible young man who made a habit of marrying wealthy women and then murdering them, in order to inherit their riches.

This basic plot sounds bald enough, but the initial script characterisation had been elaborated by London and repertory interpretations and additional "business" by the players, all of which contributed to the meatiness of the film.

The first wife-victim in the film story, a weak drink-sodden woman (who was assumed to have gassed herself) was followed by an ex-barmaid, of the hard and brassy type, who had inherited a fortune and was all set to be the next victim.

In the repertory version, the parts of both wives was played by Hermione Baddeley, whose appearance in both parts was effectively changed by make-up, wig, clothes, and, of course, expert character acting. This, perhaps was the best performance of both parts!

The BBC film cast Margaret Lockwood in the part of the brassy barmaid wife who was nearly murdered, which role she played with great skill, especially in the production of an authentic Cockney accent.

This was the type of film in which television reaped the benefit of prior stage production and yet was not restricted by limitations of two or three settings and no exteriors.

I remember it as a good, but not great, stage play and a gripping film; but on television it seemed to gain something in presentation. Perhaps this was by comparison with some of the puzzling modern kitchen-sink epics recently put before us on television. If it wasn't vintage drama, it was first-class entertainment with Dirk Bogarde and Margaret Lockwood at their best, and with Robert Fleming as the solicitor who solves the mystery. Since he played in this film he has become a reliable solicitor-character on many TV features.

## Vintage Tapes

Dramatic, comedy and documentary films are not the only vintage entertainment put before viewers. Now we are able to see vintage video tape shows, and there are no pieces of old tape more welcome to our screens than those which record the diverting adventures of Tony Hancock. The earlier series in which Sidney James was foil to Tony is ever welcome; and now the BBC has reissued, after only four months, the later series in which Tony Hancock is the central figure. Alan Simpson and Ray Galton evolved a new formula for displaying the virtuosity of Hancock, and a second viewing confirms that it is first-class, and suitable for many more showings.

The episode in which he considers matrimony in turn with June Whitfield, Myrtle Reed and Gwenda Ewen, three young women with highly differing characteristics, provided even



This is an interior view, looking upwards, of the 250ft mast at Llandrindod Wells, central Wales, for which EMI Electronics Ltd. have supplied a turnstile aerial array to the British Broadcasting Corporation. This is one of five new stations which the BBC is building to extend its television and sound services and to improve reception in the fringe areas.

more laughs on its second viewing. Let us hope that the BBC repeat these Hancock video tapes regularly, just as they do the five-year-old Hancock sound tapes on radio—they are all classics.

### Comedy Classics

Comedy classics of the cinema are not very often seen on television. I can't remember having seen a Chaplin film though I hear that this great comedian has permitted a section of one of his last films, "Limelight" to be shown by Scottish Television.

The antics of Laurel and Hardy used to be regularly shown on BBC TV at one time, and might once more be brought out of the film vaults and given an airing on television. A new generation of viewers has grown up and may never have seen these amusing buffoons.

Other comedy classics which might (or might not) make the grade, are the real vintage silent comedies of Harold Lloyd, and the slapstick adventures of Will Hay and George Formby jr.

### Sound Levels

One of the advantages BBC television has over the ITV programme companies is its unified policy as regards sound quality and volume. The result is that in all regions the BBC programmes keep reasonably even in volume and quality, uninterrupted by fortissimo commercials. The ITV companies, on the other hand, are not all of the same mind on policies which may affect the uniformity of sound. Advertisers who feel that their wares are best pushed home by sheer force of volume, have their actors declaim the merits of the product loudly and the recording reinforced by electronic compression of sound. Occasionally, this bangs the "message" home to viewers and also to the people living next door, if the volume knob is not turned down quickly! But it often makes the next item on the programme sound rather thin and feeble by comparison.

There is now a tendency for ITV companies to make use of electronic sound compression on various items which depend upon clarity of diction—so often missing these days in so-called plays of realism.

I.T. News uses compression, for instance, without losing quality and certainly with a gain in

intelligibility. Electronic sound compression mainly affects the peaks of modulation, reducing the top 15 or 20dB into 10dB, thus allowing a higher level of volume without overshooting. By its use, whispered or throw-away lines become audible instead of being lost. This is an important factor when the viewer has a television set with a loudspeaker at the side, operating towards the wall or curtains in a room.

### Programme Papers

The BBC also has uniform presentation of its programmes in its weekly journal in all regions. ITV companies have very different ideas from one another on the right and proper way of producing a television programme journal.

The London companies, Southern, Midland and Anglia have their own regional versions of the 'TV Times', a magazine publication somewhat like the BBC's journal in shape, but a little easier in which to find the night's programme. Ulster, Scottish Television and TWW have 'The TV Post', 'TV Guide' and 'Television Weekly' respectively, which are all large-page publications, more like newspapers. Tyne-Tees and Westward produce 'The Viewer' and 'Look Westward' for their respective regions, very fully illustrated with photographs and cartoons, but otherwise, in the

rather more handy size and shape of the 'Radio Times'.

All of these publications line up with the style of the film-fan magazines of twenty years ago, but with the benefit of more modern printing techniques. None of them carry technical information of any weight but all are bright and informative in a popular picture paper style, with readable articles. British viewers are better served with their regional programme magazines than any other country in the world.

### The Roaring Twenties

It—or rather—they, had to come. First the gay nineties, then the plushy 1900's, and now the roaring twenties. I don't know whether the new craze was triggered off by the authentic jazzy sounds of the Temperance Seven, but the days of the Charleston, the Black Bottom, the Savoy Orpheans and Red Nicholls are with us again.

The Warner Brothers television series, "The Roaring Twenties" seems to have appeared at just the right moment with American speakeasies, straw-boaters and tuxedos as a background to gangster melodrama in its most elementary and—it must be admitted—entertaining form. At any rate, the TAM rating indicates that it kept quite a lot of people awake at a late Saturday night spot on several of the ITA network stations.

## PRACTICAL WIRELESS

**Chief Contents of the December Issue (Including FREE 'Citizen' blueprint)**

**Now on Sale 2/-**

HIGH SENSITIVITY BRIDGE  
TRANSISTOR TRF RECEIVER  
CHECKING TEST INSTRUMENTS  
AN IMPROVED VALVE-VOLTMETER  
UNDERSTANDING POWER SUPPLIES  
R.F., I.F. AND A.F. SIGNAL GENERATOR  
PERSONAL PHONE FOR TRANSISTOR RECEIVERS  
A PORTABLE GRAMOPHONE AMPLIFIER  
HOW TO MEASURE INDUCTANCES  
A DRY-BATTERY RECHARGER  
SHORT-WAVE SECTION  
CLUB NEWS  
ETC., ETC., ETC.

# RADIO BARGAINS

## SIGNAL GENERATOR




£6.19.6 or 25/- deposit and 6 monthly payments of £1.6. P. & P. 5/6 extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 x 3 1/4 x 5 1/2 in. grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 800 milli-volts. O.W. and mod. switch

variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6. Plus Postage and Packing 5/6.


Coverage 120 Kc/s-84 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30% modulated or unmodulated R.F. output continuously variable. 100 milli-volts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

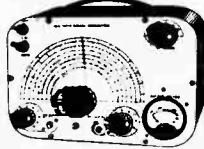
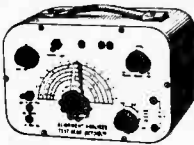
## ALIGNMENT ANALYSER


TYPE MC12

A.C. mains 200/250 v. Provides: "Wobbling" (Sweep Frequency) Operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s-80 Mc/s. Capacitance Measurement. Two ranges provided 0-80pF and 0-12pF. Special Facility enables true resonant frequency of any tuned oct. I.F. transformer, etc., to be rapidly determined. Cash price £6.19.6 plus 5/6 P. & P. H.P. terms 25/- deposit, plus 5/6 P. & P. and six monthly payments of 21/6.



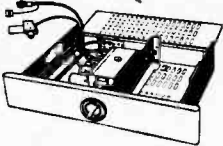
## CHANNEL TUNER

Will tune to all Band 1 and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series). I.F. 16-19 or 38-88. Also can be modified as an aerial converter (instructions supplied). Complete with knobs. 32/6 plus 4/6 P. & P.



HEATER TRANSFORMER To suit the above, 200-250 v., 6/-, plus 2/- P. & P.

## LINE E.H.T. TRANSFORMERS

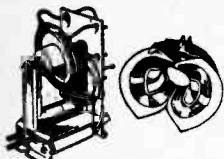


With built-in line and width control. 1417 Scan coil, 90in. deflection on ferrite yokes. Frame O.P. transformer pl. 19 KV smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.

29/6 Plus 4/6 P. & P.

As above, but for 825 lines, £2.10.0, plus 4/6 P. & P.

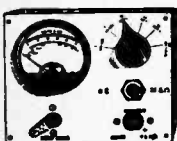Focus Magnet suitable for the above (state tube), 10/- plus 3/- P. & P.



## A.C./D.C. POCKET MULTIMETER KIT

2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wirewound pot (for ohms zero setting), toggle switch resistor and rectifier. 19/6. P. & P. 2/- Wiring diagram 1/-, free with kit.

## RADIO & T.V. COMPONENTS (Acton) LTD.

23c HIGH STREET, ACTON, LONDON, W.3

All enquiries S.A.E. Goods Not Despatched Outside U.K.

## REBUILT REPLACEMENTS TV TUBES



12 months Guarantee

21 in. . . . . 99/6  
17 in. . . . . 90/-  
15, 14, 12 in. . . . . 70/-  
Ins. and Carr. 15/6

£1 extra without old bowl, refundable if same received within 14 days.

36/24 and 14KP4 TV TUBES. Due to purchase of 35/- Rental replacement stocks. Carr. 5/-.

TRANSISTORS per set 47/6 post free Mullard  
1 OC8ID 6/9, 2 OC8I 6/9, 1 OC44 9/9, 2 OC45 8/9. Diode 1/9

GEC Ediswan  
114 6/9, XC121 8/9, 873 8/9, XB113 8/9, 2-874 9/9

## ELLIPTICAL SPEAKERS


15/9 Brand new, slot type. 8 x 3in. and 7 x 4in. P.P. 3/3.

## SCOTCH BOY TAPES

19/9 5 1/2in. Limited quantity. Post FREE

## EX-RENTAL SETS

17 in. £11.10.0

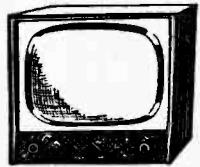

Excellent Table models. ITA/BBC. Famous manufacturer. 12 months' guarantee. Personal collection advised. INS: Carr. 25/-.

14 in. £7.10.0

ITA/BBC. Identical to 17in. TV. Ideal for Caravans, Weekend Bungalows. Chalets. etc. 12 months' guarantee. Carriage 20/-.

## RECORD PLAYER AMPLIFIERS

12 months' guarantee

MK. D.2. 79/6. Latest design incorporating negative feedback, giving 4 watts undistorted output. Valves: ECL82 and metal rectifier. Tone and volume control panel on flying leads. P. & P. 4/-.



MK. D3. 89/6. As above de luxe model, with separate tone controls for treble and base boost. P. & P. 4/-.

MK. D5. 39/6. New circuit employing ECL80 triode pentode output valve giving 3 watts output. A.C. only. Mains isolated. Single control for volume and on/off switch with knob. P. & P. 4/-.

## DE LUXE RECORDER CABINET



79/6

Beautifully styled, rexine covered cabinet in Red or Beige. Size 14 1/2 x 13 x 9 1/2 in. Storage compartment in lid for Tapes and microphone. Easily adapted to Record Player Cabinet. Ins: Carr: 5/-.

## VALVES

Salvage	7/6 Doz.	2/9 each	30/- Doz.
4D1, 6AL5, 6D1, 6D2, 9D2, 12Y4, 15D2, 78, 210VPT, 2050, 7193, C2C, CV66, D1, D152, EA50, EB91, EF50, SP61, T41, VR35, VR51.	1/9d each	5/9 each	60/- Doz.
6AM6, 6AT6, 6F1, 6F12, 6F13, 6F14, 6F15, 6K7, 6P25, 6P28, 8D3, D77, DH77, EB41, EF91, Z77	1/76 Doz.	5/9 each	60/- Doz.
		6F6, 6V6, 7AN7, 9BW6, 12AX7, 20F2, 20L1, 20P1, 21A6, 30C1, 30L1, 30PL13, PCF80, PL81, PL83.	

Postage: 1 valve—7d., 6—1/6d., 12—2/6d.

## DUKE & CO. (London) LTD.

621/3 ROMFORD RD. MANOR PARK E12 ILFord 6001/3 Send for Free List

**SPECIAL BARGAIN OFFER!**

**RECORD PLAYER KITS**

**AUTOCHANGER KIT**  
Comprising three Units, Contemp. styled Cabinet, size 17 x 14½ x 8½in. 2 valve, 2 watt amp. and 7 x 4in. Quality Speaker. Variable tone and volume controls with feedback circuit and B.S.R. 4-speed 12-record Mixer Autochanger Unit.  
BGN. PRICE only £12.10.0 Carr. 7/6.

**SINGLE PLAYER KIT**  
Similar spec. to Autochanger Kit except Player is 4-speed B.S.R. T.U.9 Single Record Player Unit. Attractive Contemp. Styled Cabinet. Size 13½ x 14 x 6in. with splendid volume and reproduction.  
BGN. PRICE only £8.19.6 Carr. 5/-

— ALL UNITS READY WIRED —

SIMPLE SCREWDRIVER ASSEMBLY ONLY

**FULL SATISFACTION — REFUND GUARANTEED**

NEW VALVES	ALL GUARANTEED	TRANSISTOR BARGAINS!
1T4	6/- EP86	12/8
1R5, 1R5	7/6 EY81	8/6
3A4, 3V4	7/6 EY81	9/6
DAF96	9/- EY86	10/-
DP98	9/- EZ80/81	7/6
DK96	9/- PCC84	9/6
DL96	9/- PCF60	9/6
ECL80	10/6 PCL83	12/8
ECL92	10/6 PL18	12/8
EF80	8/- U25	12/8

BRAND NEW—BVA 1st Grade	
0C44	10/6 874 9/6
0C45	9/6 873 9/-
0C81D	7/6 0FT114 6/6
240C81	15/6 0C72 7/6
XA102	10/- 0C70 5/6
XA101	9/6 0C71 6/-
XB103	7/6 0EX34 2/9
XC101	8/6 0A70 2/9
8B305	9/6 0A81 2/9

**SPEAKER FRET.** Expanded Bronze anodised metal 8 x 8in. 2/8; 12 x 8in. 3/-; 12x12in. 4/6; 12x16in. 6/-, etc.

**TYGAN FRET** (Contemp. pattern) 12 x 12in. 2/-; 12 x 18in. 3/-, etc.

**SPEAKERS P.M.** 8 ohms 2½in. Elac. 17/6. 3½in. Goodmans, 18/6. 5in. Eola, 17/6. 6in. Elac., 18/6. 7 x 4in. Goodmans, 18/6. 8in. Eola, 20/-.

**CONDENSERS—Silver Mica.** All values, 2 pF to 1,000 pF, 6d. each. Ditto, ceramics 8d. Tub. 450 v. T.C.C., etc., .001 mfd., .01 and 1/350 v., 9d.; 0.2-1/500 v., 1/-; .25 Hunts 1/8; .5 T.C.C. 1/8, etc., etc.

**RESISTORS—FULL RANGE** 10 ohms—10 megohms 20% ± w. and 1 w., 3d.; 1 w., 6d.; (Midget type modern ratings), 1 w., 6d.; 2 w., 9d.; 10% Hi-Stab, 1 w., 5d.; 4 w., 7d.; 5% ± w., 9d.; 1% Hi-Stab, 1 w., 1/8.

**W/W RESISTORS.** 25 ohms to 10K, 5 w., 1/8; 10 w., 1/6; 15 w., 2/-.

**PRE-SET T/V POTS.** Full range 25 ohms—2 meg., 2/-.  
**VOLUME CONTROLS—5K—2 Meg.** ohms. 3in. SPINDLES MORGANITE MIDGET TYPE, 1½in. diam. Guar. 1 year. LOG or LIN ratios less Sw., 3/-. D.P. Sw. 4/6. Twin Stereo less Sw., 6/6. D.P. Sw., 8/-.

**TURRET TUNER — BAND 1/BAND 2.** Ex. mfrs. current production offer—std. type 13-channel unit. 35-38 Mc/s I.F. (complete with PCC84 and P4780 Valves and coils for channels 1-3-9. No knobs or circuit diagram, but connection data supplied. Clearance Bargain Only 38/6. Carr. 2/6. Worth 5 kns.

Transistor Midget Electrolytics—all values 1 mfd. to 100 mfd. 1/8 ea.  
Transistor Condensers—.01 mfd., .05 mfd., 9d.; .05 mfd., 1 mfd., 1/-; .25 mfd., 1/3; .5 mfd., 1/8.

**RECORDING TAPE—Special Offer**

American COLUMBIA (C.B.S.) 1st Grade P.V.C. TAPE. Fitted leader and auto stop folia. Brand New, boxed, and fully guaranteed. Standard Long Play

5in., 600ft. ... ..	15/-	900ft. ... ..	19/6
5½in., 900ft. ... ..	18/6	1,200ft. ... ..	22/6
7in., 1,200ft. ... ..	21/-	1,800ft. ... ..	32/-

P. & P. per reel 1/-, 6d. on o.v. additional reel.  
**SPECIAL BARGAIN:** 3in. mfrs. Tape 226ft. 5/6. P. & P. 6d.  
Plastic Tape Reels ... .. 3in. 2/8. 5in. 3/-; 5½in. 3/8. 7in. 3/6.

**TAPE RECORDER KIT ONLY £16 10s.**

Latest 5-valve circuit based on Millard's design. Magic eye and tone controls. Printed circuit already wired. A sensitive quality recorder. B.S.R. Amp. Kit 96/-, B.S.R. Tape Deck £8.10.0. Collaro Amp. Kit £5.5.0. Collaro Tape Deck £12.10.0. Set of 5 valves 45/-.  
**Special Unit Kit Prices—**Send stamp for detailed list. Handbook (full details) 2/6.



Jason Tuners—Approved Kits—comprehensive range in stock. Model FMT1 5 kns, etc., 48-hour Alignment Service. Send for complete bargain list.




**RADIO COMPONENT SPECIALISTS**

76 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Est. 1946. Telephone THO 2188  
Terms C.W.O. or C.U.D. Post and Packing up to 1 lb. 2s. 1 lb. 1/4, 3 lb., 1/8, 5 lb., 2/-, 10 lb., 2/6. Hours: 9 a.m.—6 p.m.; 1 p.m.—4 p.m.

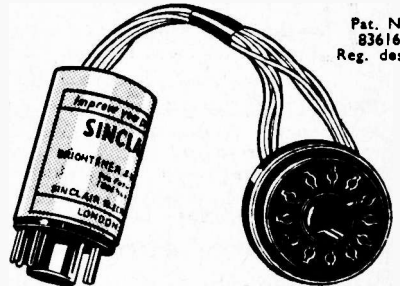**RESTORE TV TUBE PICTURE QUALITY & BRIGHTNESS**



Pat. No. 836161  
Reg. design.

**JUST PLUG IN!**  
No technical knowledge required.

Lengthen the life of tubes suffering from low emission. This Unit removes the cathode contamination, restores low emission on all sets operating off A.C. mains. **IMPORTANT.** State name and address, make and model No. of set and tube in block capitals, please.

**STANDARD MODEL .. .. 22/6**


**DE LUXE MODEL .. .. 30/-**

Postage 2/6 either model.

**SINCLAIR ELECTRONICS**

Dept. P.T.4, 18 NEWPORT COURT  
CHARING CROSS RD., LONDON, W.C.2

Terms: C.W.O. C.O.D.

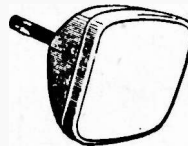

**“SABRINA”**  
STILL WELL IN FRONT

Make your TV set 100% again before Prices rise. (You have been warned!)

**COMPLETELY REBUILT C.R. TUBES ALL TYPES** (including electrostatics)

12" now ... ..	£5. 0.0	} For Single Tubes
14" to 17" now ... ..	£5.10.0	
21" now ... ..	£8. 0.0	

ALL C.W.O. Trade supplied

**Special Bonus Scheme for Service Engineers** (reducing to: 12"—87/6, 14/17"—97/6, 21"—147/6)

**FREE** Pass. transit & Ins. anywhere in British Isles or N. Ireland (12 months guarantee).

**SABRINA C.R. TUBE CO.**

Electron Works, North Bar

BANBURY, OXON

Telephone 2390

# Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

**SPECIAL NOTE:** Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

## ANTI-FLUTTER CIRCUITS

**SIR,**—I have tried most of the commercial circuits of the above type but cannot yet completely remove the flutter caused by aircraft passing overhead. Surely it is not beyond the bounds of possibility that a very efficient type of AVC circuit could be developed which would hold a picture steady except perhaps under the most extreme conditions. Living on a "run" to London Airport, I think we have about the worst position in the country, and I would like to avoid the very intense fade and glare which results from the big planes passing over the house.—E. LEESON (Kenton).

## AN EKCO FAULT

**SIR,**—In your September issue in a reply to a Mr. A. Phillips concerning a fault in his Ekco T161, you have hit the right nail on the head. You suggest that his trouble may be due to a weak signal. I recently had two sets giving a similar trouble and after much searching found that the decoupling condenser in the I.F. stage had gone open circuit. This occurred on both sets and after only a short period of use. The voltage rating is correct, but presumably the condenser had developed a fault and although replaced by similar components the trouble has not recurred.—G. BRETTENDEN (Harringay).

## LINE SLIP

**SIR,**—I would suggest to Mr Humberstone that the washers were not originally in his set

(September issue). They must have been dropped there after the set had been installed, as they were presumably of steel and had been magnetised. The magnetic field on the coils is negligible, and they were probably lodged where they were found as a result of the pull of the focussing magnet, and when the set had cooled down they should have fallen away. Is he sure they were not part of the actual scanning yoke assembly and had not in fact become loose and if they are not replaced the coil assembly may later give trouble.—D. GROVES (Leamington).

## RE-GUNNED TUBES

**SIR,**—I wonder if anyone has had experience with the remade tubes to the extent that they could suggest a possible cause for the trouble which I have experienced with these items. I have had several tubes from time to time, and from different firms, but in nearly every case the tubes have become erratic after a period of use. The fault does not take the form of the standard failing tube symptom, but rather resembles that found in an area of weak signal strength, where the signal fades. The picture *suddenly* drops in intensity, to return after a few minutes in a rather dim manner. Full black and white are not obtained, but in other respects the results are normal. No adjustment of controls has any effect on the screen, and when the tube is next used it appears perfectly normal. The sudden drop in brightness (contrast?) does not occur every night and only after an hour's use or so. I feel convinced that it is the tube and that in some manner the re-gunning process has this effect. I did once try a replacement, but it takes so long to change the tube that a comparison is not practicable, and by the time the new tube is in, if there has been any fault in the circuit itself, it would have cleared itself.—G. BORHAM (Kidderminster).

## THE "LINES" BATTLE

(Continued from page 120)


### UHF Tuners

There are several UHF tuners and typical in this respect is the Cyldon Type UT. This has continuous tuning over Bands IV and V through a 5-to-1 gear drive which may be further modified through the manual tuning and indicator drive built into the set. An earthed grid self oscillating mixer is used and tuning is accomplished by Lecher lines and a three-ganged capacitor.

Another idea, adopted by Ferguson and others, is simply an additional segment clipped into the existing tuner. This produces double mixing and multiples of the oscillator frequency (usually the third or fourth) are generated by a crystal circuit, as shown in Fig. 1 (last month). The harmonics are mixed with the incoming UHF signal by a second crystal and so produce a first I.F., which is fed into

the mixer section of the standard tuner in the ordinary way and changed into the I.F. of the receiver.

Ferguson also have available a comprehensive conversion unit that is designed for the Senator Phase II models. This is in the form of a sub-chassis and contains the I.F. stages, video amplifier and flywheel sync circuits. When the unit is installed it can be brought into operation by a 405/625 control knob which, although fitted on some models, is at the present time disconnected. It would, of course, be linked to the conversion chassis and, with the addition of a UHF tuner or adaptor, the receiver would be a switchable dual standard model. The design of the conversion chassis cannot be finalised until the standards are fixed, but a completely converted model has been demonstrated on the true CCIR system.

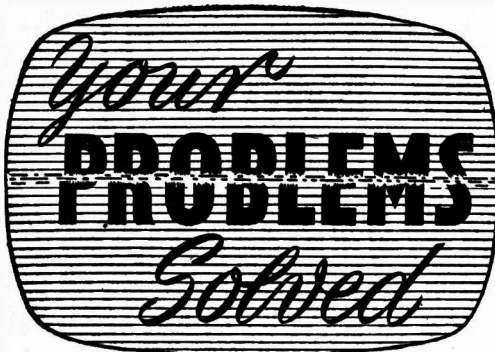

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p. 152 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

#### FERGUSON 406T

I have a Ferguson 406T which has been used for two years on 250V without the voltage adjustment link for 200V being removed. A number of condensers have been replaced and the remainder checked by shunting. Valves 6, 5, 11, 12 and 13 have been replaced. When switched on the picture is short top and bottom, split into two parts and the screen is covered by numerous white lines. After approximately 15 minutes the picture flickers and fills the screen, but it remains divided into two parts. Movement of the frame hold then produces a normal picture. I have just replaced the OAB1 interlace filter and would appreciate any suggestions as to what to do next. C. Violet (Hemel Hempstead).

Carefully check the printed wiring associated with V5 and V12. Check the height, vertical lock and frame linearity control are in good order. It would seem from your description that there is a minute crack in one of the printed wires.

#### K.B. OV30

My receiver is a 17in. K.B. New Queen Special OV30. Could you please help me with two faults? Firstly, when the brightness control is altered the picture blows up and goes out of focus. The second fault appears to be with the vertical hold control. The picture is subject to intermittent rolling. Once the picture starts rolling it takes very careful handling of the vertical control to stop it.—W. Gregg (Belfast).

You should first ensure that ion trap magnet on the rear of the tube neck (if fitted) is adjusted for maximum brilliance. If the effect continues, change the R19 EHT rectifier, mounted on the front of the line output transformer, inside the screened section. With reference to the frame hold fault, check the 12AX7 valve situated on the right side near printed panel.

#### RGD Deep 17

Perhaps you would be able to help me on the following points regarding the above receiver. On

replacement of V11 (EF80 sound I.F. amplifier), which developed a fault, the sound kept clicking on and off after about five minutes warming up. I found the sound, particularly on ITV, was not as loud as it had been. I have since tried two more EF80's in this position, but with no better results. Could you please suggest a possible solution? With regard to your July 1961 issue—Servicing Television Receivers, page 519, about PY32 failure—I have recently fitted a new PY32 and am puzzled about the paragraph stating that pins 3 and 5 should be strapped together. Should the resistors 90A and B be taken out of circuit when you do this, or left as they are? Also if the above modification is not done, what detriment is there to the set—will the PY32 function properly, or will it have a shorter life, etc.—J. Wormald (Leeds).

Original valves of the PY32 type, used a twin anode construction, each anode brought out to a separate pin i.e. one to 3, one to 5. Recent PY32 valves have a single anode brought out to pin 5. As this passes the whole H.T. current, not half as before, the series resistor will drop twice the voltage. To avoid this it is only necessary to connect pin 3 and pin 5 together to place both resistors in parallel, thus halving the voltage drop which would occur across one. Check the 0.001 $\mu$ F capacitor from pin 8 to chassis and that from pins 1 and 3 to chassis by replacement. Check the alignment of L22-23-24, and, if necessary, the feed resistor R88. If sound is intermittent, restored by a pulse, check C70 (0.1 $\mu$ F), C72 (0.01 $\mu$ F) and C74 (0.005 $\mu$ F).

#### MARCONI VT53

Could you please help me with the following fault. Adjustment of the contrast control gives a picture at one end of its travel with no sound, and sound with no picture at the other end. Also the picture will not lock. R40 is correct. I did disconnect C32 from pin 3 of V10, but it made no difference to the picture. I would have thought that disconnection at this point would remove the picture and so I reconnected again as it was before. Also V5—the vision amplifier—has 70V on the anode, the control grid, pin 1, has 12V D.C. and the cathode 10V. The current through this valve is from 30 to 40mA. The cathode voltage on the CRT is only 30 because of the heavy fault current through V5. Could you tell me how a 12V positive appears on the control grid at all?—T. M. Lloyd (London, S.E.17).

The video section is in a state of oscillation, possibly due to L14 being partially open circuited (note the effect of replacing this with another choke) or to incorrect vision R.F. alignment. Check security of screening cans and realign L10-L7, etc. Maladjustment of T.C. (sound rejector) could cause the effect but this should not be altered unless absolutely necessary. If the fault persists, check V6 and the decoupling capacitors C11, C9 and C13.

#### SOBELL T192

Although I live within 20 miles of both BBC and ITV transmitters, owing to surrounding hills, reception is reduced to fringe area conditions. The

(Continued on page 151)

# LASKY'S RADIO

## MAKER'S SURPLUS COMPONENT BARGAINS

- WIDE ANGLE 38 m.m.**  
Line E.H.T. Trans. Ferroxcube core, 9-18 kV ..... 19/6  
Scanning Coils, Low imp. line and frame ..... 19/6  
Ferrox-cube cored Scanning Coils and Line Output Trans., 10-15 kV EY51 winding Line Trans. with width and linearity controls, circuit dia., pair ..... 50/-  
Frame Output Transformer, Frame or line block osc. Transformer ..... 6/6  
Focus Magnets Ferroxcube ..... 4/6  
P.M. Focus Magnets, iron-cored ..... 12/6  
Duomag Focallisers ..... 15/-  
300 m/a Smoothing Chokes.. 10/6
- STANDARD 35 m.m.**  
Line Output Transformers 6.9 kV E.H.T. and 6.3 v. winding, Ferroxcube ..... 17/6  
Scanning Coils, Low imp. line and frame ..... 7/6  
Frame or line blocking oscillator Transformer ... 4/6  
Frame Output Transformer.. 7/6  
Focus Magnets:  
Without Vernier ..... 9/6  
With Vernier ..... 12/6  
200 m/a Smoothing Chokes.. 7/6

# GREAT TV OFFER

Don't neglect this final offer of well-known television products, all brand new, at clearance prices. Full data and instructions supplied. Call or post your order without delay.

## 110° SLIMLINE 17" TV CHASSIS

Complete with 14 valves and 12-channel turret covering all Bands I and III. Valves: 2 PY82, 2 PL81, EY52, 2 PCL82, 2 PCF80, PCL84, 3 BW6, PCL89. Uses 17in. C.R. tube type C17A7. Overall dim.: 19 x 12 x 6in.

**LASKY'S PRICE 19 Gns.** Carr. & Ins. 7/6 less C.R. Tube

Complete with C.R. tube, £24.19.6. Carr. & Ins. 19/6.

Above Chassis less valves, C.R. tube and Line Output Transformer, 99/6, Carr. 7/6.

**C.R. TUBE type C17A7, separately, £6.19.6.** Carr. & Ins. 19/6.

Line Output Transformers with EY51, 29/6. Post 2/6.

**Sound & Vision Chassis.** Printed circuit, all components wired, complete with valves: 3 6BW7, PCL84, 2 PCL82, PCF80. Overall size 4 x 16 x 5in. (including valves), £5.19.6. Carr. 7/6. Less valves, 59/6. Carr. 5/-.

## PRESS BUTTON TURRET TUNER

Covers all channels Band I and III also VHF/FM. I.F. 33-38 Mc/s. Operated by 5 press buttons. Complete with valves 30L15 and 30C15. Overall measures: 5 x 4 x 2in.

**LASKY'S PRICE 49/6** Post 2/6

207 EDGWARE ROAD, LONDON, W.2.

PADDington 3271/2.

33 TOTTENHAM COURT ROAD, W.1.

MUSEUM 2805.

BOTH OPEN ALL DAY SAT. Early Closing, Thurs. Mail Orders to Dept. P.T., Edgware Road.

## 90° 17 in. TV CHASSIS

Complete with 13 valves and latest Fireball turret covering all Bands I and III channels. Valves: 3 PCF80, PC84, 3 6BW7, PCL84, PCL82, PY82, PL81, PY83, EY51. Overall dim: 6 x 16 1/2 x 6in.

**LASKY'S PRICE £18.19.6** less C.R. Tube

Carr. & Ins. 7/6.

Complete with new Brimar C17SM 17in. tube, £23.19.6. Carr. & Ins. 19/6.

Above Chassis less valves, C.R. tube and Line Output Transformer, 77/6. Post 7/6.

## LASKY'S FOR NEW C.R. TUBES

All sizes in stock at lowest prices. 17in. from 79/6. Send for list.

**FERRANTI 17in. type TR17/10,** 6.3 v., 0.3 amp. heater. Now and unused £6.16.6. Carr. & Ins., 12/6.

## REGUNNED C.R. TUBES

GUARANTEED FOR 12 MONTHS

Type	Carr. & Ins.
12in. round .....	25 10 0 12/6
14in. rect. ....	25 10 0 12/6
15in. & 18 round	25 19 6 12/6
17in. rect. ....	25 19 6 12/6
21in. rect. ....	27 19 6 21/-

# "TELFAC"

## Regunned TV Tubes

Supplied from stock and despatched per British Railways SAME DAY. COMPLETE NEW GUANS fitted in every tube and fully guaranteed for TWELVE MONTHS.

	Mullard	Mazda
12 in. ....	£4. 0.0	£4.10.0
14 in. MW .....	£4.10.0	£5. 0.0
14 in. AW .....	£5. 0.0	£5. 0.0
15 in. 2 Volt .....	£5.10.0	£5.10.0
15 in. 12 Volt .....	£5. 0.0	£5. 0.0
16 in. ....	£5.10.0	£5. 0.0
17 in. MW .....	£5. 0.0	£5. 0.0
17 in. AW .....	£5.10.0	£5.10.0
21 in. MW .....	£6.10.0	£6.10.0
21 in. AW .....	£7. 0.0	£7. 0.0

MW = Magnetic Focus  
AW = Electrostatic Focus  
Plus 10/- for Carr. & Ins.

Other types not listed available, Please contact:-

**J. P. WRIGHT**

Television Factors

103 Carr House Road, Doncaster  
Sole Distribution Agent  
Phone: DON 2636

# VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

## SETS

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL82, DL84 ... Set 4 for 19/6  
DAF98, DF98, DK98, DL96 ... 4 for 27/6  
6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 6Y3G' .. .. 5 for 24/6

1A7GT 11/-	6L19 12/-	30FL1 10/-	EBL21 13/6	EZ80 6/3	U50 6/-
ID5 8/-	6LD20 8/-	30L15 11/-	ECC40 15/-	EZ81 6/8	U52 4/6
1H5GT 9/-	6P1 10/-	30PL1 10/6	ECC81 5/-	KT33C 6/8	U78 4/9
1N5GT 8/-	6P25 8/-	35A5 14/-	ECC82 6/8	KT41 11/6	U81 14/6
1R1 8/-	6Q7G 8/-	35L6GT 8/3	ECC83 7/-	KT44 5/8	U281 16/6
1S4 8/-	6Q7GT 8/6	35Z4GT 6/9	ECC84 8/3	KT61 9/-	UABC80 6/6
1S5 5/3	6SL7GT 5/9	35Z5GT 8/3	ECC85 7/9	KT63 6/6	UAF42 8/3
1T4 3/6	6SN7GT 4/9	50L6GT 8/3	ECCF80 7/6	MU14 11/6	UB41 8/6
1U5 5/9	6U4GT 9/9	AC/TH1 16/9	ECCF82 8/6	MX40 9/6	UBC41 7/9
3A5 9/-	6V6G 4/6	AZ31 9/6	ECH31 13/6	N18 7/-	UBF80 8/3
3Q4 7/-	6V6GT 6/6	B98 8/6	ECH35 6/3	PC85 10/6	UBF89 7/-
3S4 4/-	6X4 4/9	CL33 12/3	ECH42 8/9	PCC84 7/6	UCC84 13/3
3V4 7/-	6X5GT 4/9	DAC32 9/-	ECH81 7/9	PCC89 9/3	UCC85 7/-
5U4G 4/6	7B6 9/-	DAF91 5/3	ECL80 7/6	PCF80 7/9	UCH80 14/6
5V4G 7/6	7B7 7/6	DAF96 7/6	ECL82 9/-	PCF82 8/-	UCH21 13/6
5Y3GT 8/-	7C5 7/6	DCC90 9/-	EF39 7/6	PCF86 14/-	UCH42 8/-
5Z4G 7/9	7C8 7/6	DF33 9/-	EF40 12/6	PCL82 9/-	UCH81 7/6
6AL5 3/9	7H7 7/6	DF91 3/6	EF41 7/9	PCL83 11/6	UCL82 9/9
6AM6 3/6	7S7 9/-	DF96 7/6	EF42 10/6	PCL84 7/6	UCL83 13/3
6AQ5 6/6	7X4 7/-	DH76 4/9	EF50 4/9	PCL85 13/6	UF41 7/-
6AT5 6/9	10C2 17/-	DH77 6/9	EF85 4/9	PEN14 11/-	UF42 6/6
6BA5 5/9	10P13 14/6	DK32 11/-	EF86 9/9	PEN36C 8/-	UF85 7/-
6BE6 5/9	12A26 7/-	DK91 6/-	EF89 7/-	PL36 11/6	UF89 7/-
6BH6 5/9	12A27 5/-	DK92 7/6	EF91 3/6	PL81 9/8	UL41 8/6
6BU6 5/9	12A2U 6/3	DK96 7/6	EF92 3/9	FL82 7/9	UL84 6/6
6BR7 12/6	12AX7 17/-	DL33 9/6	EL33 9/6	FL83 7/6	UM4 14/-
6BW6 7/-	12K7GT 9/6	DL35 9/6	EL41 9/6	PL84 8/6	UR10 8/-
6CD6G 27/3	12K8GT 8/6	DL92 6/-	EL42 9/-	PY32 11/6	UU6 13/6
6F1 10/-	12Q7GT 4/9	DL94 7/-	EL84 6/6	PY80 7/6	UY21 13/6
6F6G 6/6	12Z3 7/6	DL96 7/6	EM34 6/9	Y81 7/9	UY41 6/6
6F13 10/-	14S7 19/6	EABC80 5/6	EM80 9/6	Y82 6/6	UY35 6/6
6F14 10/-	20F2 17/-	EAF42 8/6	EM81 9/-	Y83 7/9	VP4B 9/6
6K7G 1/11	20L1 17/-	EB91 3/9	EM84 9/-	T41 6/6	VP41 5/-
6K7GT 5/-	20P4 20/-	EBC33 5/-	EY51 7/6	U22 7/3	VP1321 16/6
6K8G 5/-	25A6G 8/-	EBC41 8/-	EY96 7/9	U24 17/6	W76 4/9
6K8GT 9/-	25L6GT 7/9	EBF80 8/-	EZ40 6/9	U25 18/-	W77 3/9
6L18 10/-	25Z4G 7/3	EBF89 8/9	EZ41 7/-	U26 12/-	Z77 3/6

# READERS RADIO

24 COLBERG PLACE STAMFORD HILL

LONDON, N.16

STA. 4587

Post 6d. per valve extra.  
Any Parcel Insured Against Damage in Transit 6d. extra.  
Any C.O.D. Parcel 3/- extra.

# 18/9 SOLDERING IRON

30-watt 230-volts A.C. Portable, for light-weight applications. High stable heat characteristics assure long life and safety in use. Features a removable handle that may be used to cover the tip and barrel to permit the iron to be carried safely even while hot. Complete with vinyl bag, mains lead and plug. Size: overall length 10 1/2 in. (6 1/2 in. when not in use). Carriage free.

# TUBES 15/-

31/74, 124, 153 Ex-RENTAL Working Guaranteed. Carriage 5/-.


14" 36/24-14K4 EX-RENTAL REPLACEMENT STOCK Carriage 3/6 35/-



# SPEAKERS 8/9

5 inch—6 inch—8 inch—7 x 4 inch. Ex. manufacture salvage. P. & P. 3/3.

# 12/6 SOLO SOLDERING TOOL

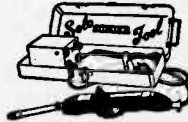

110 v., 6 v. or 12 v. (special adaptor for 200/250 v., 10/- extra). Automatic solder feed including reel solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Cannot burn. In light metal case with full instructions for use. Post 4/-.

## MISCELLANEOUS

Insulating Tape. 75ft. by 1/2 in. Sealed in metal tin, 1/6, post 9d. Rectifiers. 250 v. 100mA. Salvage, 2/9, post 1/3. Co-Ax Cable 6d. per yard. Cut to any length. Post on 20 yards 2/6. Vol./Tone Controls 2/6 per dozen. Assorted volume and tone controls, stripped from working chassis, post 2/6.

# 9d. SALVAGE VALVES GUARANTEED

4D1, 6D1, 6D2, 9D2, 15D2, 6F12, 6F13, 6F14, 6F15, D77, D1, D152, EA50, EB91, U151, ECC31, EF50, EF91, L63, PM202, UB41, SP61, T41, UF42, Z77, U281.

1/9 AND 2/9

6AM6, 6AT6, 6F1, U22, U31, 6P25, 6P28, 7C5, KT33C, KT63, LN152, LN309, LZ319, B36, 8D3, DH77, EB41, UBF80, PEN46, W77, N152, N309, N339, W76, KTW61.

6L18, 6SN7, 10F1, 10P13, 12A77, 12AU7, 20D1, 20P3, DH76, EBF80, ECC81, ECC82, ECC31, ECC34, ECC91, EY51, KT36, EF80, EF92, PL33.

Post 1—9d. 6—2/-, 12—3/-.

★ ★ ★ ★ ★ ★ ★ ★ ★ ★



COMPONENTS LTD.

623 ROMFORD RD., MANOR PARK, E.12

Stamp for FREE Catalogue

Phone: ILF 6003

# D. & B. TELEVISION

Phone Cherrywood 3665

131 & 131a KINGSTON ROAD,

SOUTH WIMBLEDON, LONDON S.W.19

FOR THE FINEST, FASTEST SERVICE IN THE COUNTRY. We are Open from 10 a.m. Until Midnight. For any information or problems you have Call or Phone, we are always pleased to help.

## NEW!

SEND FOR OUR COMPREHENSIVE L.O.P.T. SCAN COIL L.B.O., F.B.O., F.O.P.T. LIST Prices of nearly all makes and models, 2/6, post 6d. Invaluable as a service aid. The finest list ever compiled. Special quotations for the trade.

## TRANSISTORS

Geniue Mullard Transistors in sets of Six: 1, OC4; 2, OC45; 1, OC81D; 2, OC81's in matched pair. Including OA81, Diode, for ONLY 22.2.6.

Geniue G.E.C. Transistors in Sets of Six: 1, GET874; 2, GET 873, GET114; 2, GET114's in matched pair; plus 1, GEX34 for ONLY 11.18.8.

## SINGLE TRANSISTORS PRICE LIST

Mullard: OC44, 10/-; OC45, 9/-; OC70, 5/-; OC71, 6/-; \*OC72, 7/-; OC76, 7/-; OC78, 7/-; \*OC81, 7/-; OC81D, 6/-; G.E.C.: GET874, 9/-; GET873, 8/6; \*GET114, 5/9.

\* Available in matched pairs at 1/- extra. Mullard Diodes: OA70, 2/9; OA79, 2/9; OA81, 2/9; OA91, 3/6; G.E.C.: GEX34, 3/6.

All above are genuine manufacturers new 1st grade.

## SURPLUS TRANSISTORS

Red Spot, A, F, OC71 and 72. Equivalent .. .. 4/3 each  
White Spot, R, F, OC44 and 45. Equivalent .. .. 5/- each  
Diodes, general purpose .. .. 1/- each

Various other types in stock. Please ask for prices of types not listed.

TURRET TUNERS, Various Makes: 10, 16, 38 M/cs, 40/-.

## EXAMPLE OF TRANSFORMER LIST

		L.O.T.	SCAN COILS
FERGUSON:	(New)	(Used)	(Used)
103T, 105T	.. ..	69/9	60/-
292/4/6/8	.. ..	89/9	35/-
P.Y.E.	(New)	(Used)	(Used)
V4, VT4, V7	.. ..	52/6	55/-
V7, CTM4	.. ..	52/6	55/-
MURPHY:	(New)	(Used)	(Used)
V214, V240, V250	.. ..	60/6	45/-
E.K.O.:	(New)	(Used)	(Used)
221, 283	.. ..	47/3	40/-
231, 284, 288	.. ..	54/-	40/6

## REGUNDED CATHODE RAY TUBES

all with 12-month Guarantee  
ALL MAKES: 12in., £3.15.0; 14in., £4.5.0; 17in., £4.15.0.  
ADD: 10s. for 90° tubes; 15s. for 110° tubes; 5/- for Electrostatic types.

SECONDS, with 12-month Guarantee—ALL MAKES: 12in., £2.15.0; 14in., £3.5.0 (when available); 17in., £3.15.0.  
SECONDS, No Guarantee—ALL MAKES: 12in., £1.5.0; 14in., £1.15.0 (when available); 17in., £2.15.0.

NOT APPLICABLE TO NO GUARANTEE SECONDS;  
10/- allowance on old tube if in good condition.

## THE FABULOUS R.T.D. TRANSISTOR SIX

LATEST ON THE KIT MARKET  
Spec.: Six transistor plus diode, printed circuit, superhet. ferrite rod aerial. Automatic gain control to stop overloading. Output 450mW in push pull. All components brand new and guaranteed. Neat, small, two-tone grey cabinet. Two radios in one, portable and car radio. Incorporates car aerial input socket. Everything to build this superb Transistor Radio. Only £3.9.6

## VALVES—GUARANTEED 90 DAYS

AZ31	8/6	ECL80	6/9	PCF80	7/-	U26	12/-	UU9	6/6	6V6	5/-
B36	5/6	EF39	5/-	PCL82	10/9	U31	9/6	8P41	2/3	10F1	4/6
D77	7/6	EF50	3/9	PCL83	11/9	U50	8/6	8P61	2/3	10C1	10/-
DH77	4/6	EF80	4/6	PCL84	8/6	U52	7/6	W77	5/6	10E2	13/-
DK91	6/9	EF91	5/6	PL3	8/6	U191	9/-	Z77	3/6	10F13	9/6
DK92	8/6	EL92	5/6	PL36	10/9	U281	9/6	6U4	5/6	10P14	9/6
DL92	6/9	EL34	8/6	PL38	14/6	U282	20/-	6V4	9/6	12A77	8/6
DL94	6/9	EL38	14/6	PL81	8/6	U301	20/-	5Y3	10/6	12A7U7	5/9
DL96	7/6	EL84	7/-	PL83	7/-	U329	20/6	6Z4	10/-	20D1	8/6
EB91	3/6	EY518K	6/6	PY31	7/-	UBC41	7/9	6AM6	3/6	20L1	12/6
EBU35	5/6	EY51	7/9	PY32	10/-	UCH42	7/9	6CD6	27/6	20P1	10/6
EBF80	9/6	EY80	7/6	PY80	6/6	UF41	8/6	8D2	3/6	20P3	12/6
EC81	5/6	EZ40	6/6	PY81	6/6	UF42	8/6	8P1	5/6	20P4	12/6
ECX82	9/9	KT33C	6/6	PY82	6/6	UL41	7/9	6F12	3/6	27B5	14/-
ECC84	8/6	KT36	6/6	PZ30	10/-	UL46	7/9	6F13	7/6	30C1	7/6
ECP80	8/6	KT66	15/-	U22	9/6	UL44	11/6	6F14	9/6	30L1	7/6
ECH35	9/6	PCC84	7/-	U24	10/-	UY1	6/6	6F15	9/6	30P4	10/9
ECH81	6/6	PCC89	8/6	U25	12/-	UY8	14/6	6L1	12/6	185BT	14/6

These are only examples of our valves: if you do not see what you require send stamped addressed envelope for special quotation.

We pride ourselves that we can obtain and supply any TV spare OUR GIGANTIC STOCKS INCLUDE: Line Output, Frame Output, Sound Output, Line and Frame Blocking, Osc. Trans. and Scan Coils for any make or model Television. Please ask us for ANY components you require we are almost certain to have them.

TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra. Postage on Valves, 6d. each. C.R.T.'s 12/6 inc. insurance. SATISFACTION ASSURED. RETURN POST SERVICE.



(Continued from page 148)

ITV transmitter (Band III, Channel 11, Caldbeck) has only recently commenced and at present is on daily test transmission. I have tried receiving this station, using a BBC aerial only, but the picture obtained is extremely indistinct. Do you think a proper Band III aerial would improve reception to any great extent? The BBC picture received is quite good, but with a certain amount of horizontal "tearing" which is quite noticeable on the test card, but not so noticeable on an actual programme transmission. Also the background, especially when light, flickers a great deal. I was wondering if a pre-amplifier would be worthwhile for this Band. The advertisement I obtained re pre-amplifiers also refers to diplexers and triplexers. Can you advise me about diplexers and triplexers please?—J. Hornbrook (Keswick).

If you are receiving an indistinct picture from the ITV transmitter using a BBC aerial, we think it is quite likely that a good picture will be received using an efficient Band III aerial, such as a double 4 or double 5 array. The interference on BBC is not due to a weak signal but to reflected "ghost" signals. A diplexer is necessary to combine two aerial leads to a common downlead. A triplexer takes three inputs—Band I, Band III and VHF radio on Band II—to a common downlead. In your situation efficient aerials are the correct solution.

#### AMBASSADOR TV 15CC

There are three faults on this set: no raster, no whistle from the line timebase, and no white flashes when the channel switch is rotated. Upon switching the set on there is immediately a flash in the neck of the tube, and thereafter it lights up normally. The sound is perfect. The valves line-up in the set is U301, 20P4, 6K25, 10P14, 10LD11 and 10F1. The U301, 20P4 and 10LD11 are faulty, but before replacing them I wish to be assured that the flash in the tube is nothing serious, which may result in the new valves being blown.—G. Harrison (Swinton).

Either or both the 20P4 and the V301 may be causing the trouble referred to. The flash in the tube neck is of little or no importance. The 6K25 is the frame generator and this affects the height and vertical hold aspects of the picture only. Being a gas-filled triode with a "flash point", a valve tester cannot apply a satisfactory set of conditions to make a worthwhile test.

#### FERRANTI 14T6

I would like some information on the following fault on a Ferranti 14T6. On advancing the brightness control, the picture swells. I suspect low EHT so the EY86 was changed, to no avail. The same effect occurs if the contrast is advanced, and also if the iron trap is moved carefully. The PL81 and PY82 were changed without improving things. The grid voltage on the tube is 0.50V, and the video anode voltage is 140V. The CRT tube is an electrostatic type. Do you think it is the tube? The H.T. D.C. voltage seems correct, as does the sound.—T. V. Byrne (Farnborough).

You do not say whether the EY86 heater is glowing normally or not at low brilliance. If the heater glow is clearly visible and remains so while the brilliance is advanced and the picture

swells and fades, the new EY86 is at fault. If the glow is subdued or hardly visible at all times, the line timebase circuit must be carefully checked. If the glow is clear when brilliance is low but fades as the brilliance is advanced, although the picture does not come in from the sides, the ion trap magnet is inefficient or wrongly positioned, or the tube is passing excess current. Try wiring a 1M resistor from pin 10 to pin 1 of the tube base socket.

#### INVICTA 126

I am having trouble with this receiver, the difficulty being that the valve heaters do not light up. I have checked all the valves, fuses and switches, but have made no progress, and would be pleased if you could help me in this matter.—Frank M. Lever, R.M.R. (Netherfield).

You will almost certainly find that one section of the left side mains dropper has fractured. Observe the position of the voltage selector plugs; connecting to these are the sections of the mains dropper. Carefully check these windings. If a break is found, repair it or clean the end, unwind a turn or two and wrap firmly around the nearest connecting post. If the receiver does not have two PY82 valves on the upper right side, remove the chassis and check the single wire-wound resistor, mounted on the lower part. A black mark on the body normally denotes a fracture which necessitates a new resistor—130Ω 10W.

#### ALBA T644

The following fault has occurred on this set. There is no picture or sound. All the valves light up except the EY86, which I have changed with no results. Also there is no spark at the EHT clip on the side of the tube. The set was working all right when switched off the previous night but would not work when switched on again. Could you please explain how to boost a fading tube?—M. Evans (Gateshead-on-Tyne).

It would appear that the A.C. supply to pin 9 of the PY82 is absent. Check the three sections of the dropper—35Ω-30Ω-30Ω—which supply pin 9 according to the setting of the mains plug. The PY82 itself could of course be defective. To boost the tube wire a 5k 10W resistor from the mains dropper to pin 12 of the base. If the emission is not improved, remove it from pin 12 and connect to pin 1. This applies to the T644 only.

#### EKCO T221

I have an Ekco T221 television which does not give full volume. I have changed all the valves and checked the voltages. I have found that connecting the AVC line to earth increases the volume.—J. Bullock (Horley).

Your trouble is likely to be caused by an unstable sound I.F. strip and this is frequently caused by defective 0.003μF decoupling condensers. If replacement of these does not improve matters, a 47k damping resistor across the grid winding of the middle sound I.F.T. will stabilise the strip.

#### PYE V.T.4

The frame on above receiver collapsed to a single horizontal line. The frame oscillator and

frame output valves were replaced, as was the frame output transformer. Can you suggest what else I can try to cure the fault, as the above changes have not had any effect at all.—F. Crowley (Hatch End, Middlesex).

We suggest that you isolate your fault to either the oscillator or output stage. This can be done by applying 6.3V A.C., from a suitable source (CRT "live" heater pin), via a 0.1 $\mu$ F condenser to the grid of the PL82. This should produce a distorted picture some 6in. tall if the stage is satisfactory. Frequent causes of your symptoms are: an open circuit frame hold control, broken scancoil leads, and faulty coupling condensers in the ECC82 stage.

#### DECCA DM4/C

My receiver has recently developed the following faults. The picture is quite good but is spoilt

by very predominant scan lines, also the picture flickers. The volume is quite loud, but on ITV and VHF it has rather a rasping quality whilst on BBC it emits a high pitched hum. I should be very grateful for any assistance you can give me in curing these faults.—W Gibson (Pudsey).

On the right of the centre screened section, as viewed from the rear, are three valves (all ECL80). We would advise you to check the second and third by replacement. The harsh quality of the sound seems to suggest incorrect sound I.F. alignment whilst the hum could be due to incorrect BBC oscillator core adjustment or possibly excessive input signal. The oscillator coil core is adjusted from the front; the channel selected, the fine tuner set to midway, the knobs removed, and a long non-metallic tool is inserted to the right of the spindle to adjust the coil core.

## Television Filters

(Continued from page 122)

be fitted in the aerial downlead and tuned to the frequency of the offending station. Fig. 2 reveals how the arrangement works. At the frequency of the unwanted transmission, a high impedance is offered by the rejector, while at frequencies either side the impedance is relatively small and so the wanted signals pass through without trouble while the unwanted signal is considerably reduced in strength at the set input.

The success of this method depends very much on the "efficiency" of the rejector. The circuit should have a high Q so that the sloping sides of the response are as steep as possible to prevent them from embracing the frequency of the wanted signals and to provide maximum rejection.

A circuit which has been proved for this work is shown in Fig. 4 and its construction is shown in Fig. 5. The coil is self-supporting in 18 s.w.g. wire and is tapped at a quarter turn to provide the correct impedance match and to avoid damping the tuned circuit by the low impedance of the coaxial cable. Tuning is by means of a low-loss air-dielectric trimmer. For Band I operation, the coil consists of two turns with a  $\frac{1}{4}$ in. diameter and the turns spaced by the diameter of the wire. A fixed 30pF capacitor puts the circuit on Band I and the 0.30pF trimmer allows tuning from Channel 1 to Channel 5. A picture of the response of such a circuit is shown in Fig. 6, from which it will be seen that the insertion loss is quite small (compared with the datum line) while the rejection is quite high and peaky.

This arrangement is suitable for suppressing interfering R.F. signals at almost any frequency, but, with very high frequencies, difficulty is encountered in maintaining a sufficiently high Q.

#### Internal Rejectors

The circuits in Fig. 7 (a) and (b) show how simple parallel rejectors are used in the circuits of a receiver. At (a), L and C form the rejector in series with the aerial input. In this application, the rejector is usually tuned to the I.F. of the set or to the image frequency.

At (b) is shown a similar type of rejector comprising L and C, but when this is found in the vision I.F. channel, as shown, it usually serves as a sound rejector or adjacent channel sound rejector. A similar arrangement may sometimes be found in the cathode circuit of the vision I.F. amplifier valve. At the tuned frequency, the circuit impedance is largest and purely resistive so that heavy negative feedback occurs and reduces the gain of the stage at the rejection frequency. Off frequency the feedback falls and thus restores the stage gain to normal. The cathode lead is usually tapped into the rejector coil to reduce the load on the circuit by the valve cathode.

At Fig. 7 (c) is shown a four-terminal filter network which is sometimes incorporated as a sound rejector or adjacent channel rejector. This is called a "bridged-T" rejector because the action of the circuit is rather like that of a bridge. In effect, when R is adjusted for maximum attenuation the bridge is in balance and the "resistive" losses of the tuned circuit are cancelled out. In this way the circuit exhibits a very high Q resulting in extremely high rejection ratios.

(To be continued)


### QUERIES COUPON

This coupon is available until DECEMBER 22nd, 1961, and must accompany all Queries sent in accordance with the notice on page 148.

PRACTICAL TELEVISION, DECEMBER, 1961.

# LAWSON


## DIRECT REPLACEMENT Reprocessed TUBES

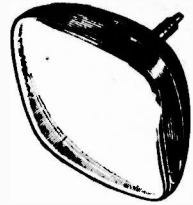

LAWSON TUBE WITH NEW SILVER ACTIVATED SCREEN AND "MICRO FINE" ALUMINISED

12 MONTHS FULL REPLACEMENT GUARANTEE

### ENGINEERS WITH EXPERIENCE

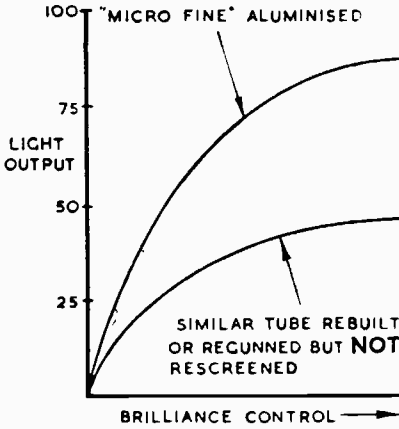

know that as a tube gets old, not only does it become Low emission but the light efficiency of the Phosphor Screen also deteriorates (up to 10% per year). This deterioration of the Screen obviously continues if the tube is only rebuilt or regunned.

Don't risk a "DEAD SCREEN", enjoy the brilliant crisp high definition of a LAWSON TUBE. Tubes which are absolutely BRAND NEW throughout (excepting the glass), and which incorporate the very latest CRT developments. New silver activated screens, "micro fine" aluminising, high efficiency gettering, plus Brand New electron guns by Britain's premier manufacturers, Mullard, Mazda, Eniscope, Cossor, Brimar, Emulon, English Electric, G.E.C., etc.

ALL MAKES AND TYPES FROM STOCK

LAWSON. The ONLY replacement tubes, for which all types are guaranteed, correct and direct plug-in replacements.

EXPRESS PASSENGER SERVICE—Orders received by 3 p.m. are dispatched same day. Special direct services to Scotland & Ireland inc. Eire.

TRADE AND QUANTITY DISCOUNTS  
**LAWSON TUBES LTD.**

156. PICKERSLEIGH RD. MALVERN. Worcs.  
TEL. 3798

12" - £4.10.0

14" - £5.5.0

15-17" - £5.15.0

CARR. and INS. 7/6

C.O.D. or C.W.O.

10/-

Gladly refunded if you wish to return your old tube (excepting 12")

VACUUM ELECTRONIC LIMITED

## KEEPS YOU IN THE PICTURE

WITH THE FINEST REBUILT CATHODE RAY TUBES

12 MONTHS GUARANTEE

12"-14" £4-15-0

15"-17" £5-5-0

21" £7-15-0

CASH WITH ORDER OR PRO FORMA, ADD 12/6 FOR CARRIAGE AND INSURANCE.

DELIVERY FREE IN LONDON AREA

15/-

ALLOWED ON RECEIPT OF OLD TUBE

**VACUUM ELECTRONIC LTD.**


WRITE PHONE OR CALL  
35, SACKVILLE STREET  
LONDON, W.1  
REGENT 6404

## HARVERSON SURPLUS CO. LTD.

83 HIGH ST., MERTON, S.W.19. Cherrywood 3985/6/7

### HARVERSON'S F.M. TUNER KIT

£4.19.6 Plus 8/6 P.P. & Ins.

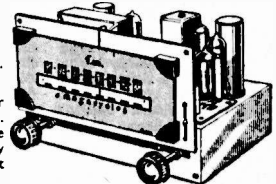

At last a quality F.M. Tuner Kit at a price you can afford. Just look at these fine features, which are usually associated with equipment at twice the price.

★ F.M. Tuning Head by famous maker. ★ Guaranteed Non-drift. ★ Permeability Tuning. ★ Frequency coverage 88-100 Mc/s. ★ OAB1 Balanced Diode Output. ★ Two I.F. Stages and Discriminator. ★ Attractive maroon and gold dial (7 x 3in. glass). ★ Self powered, using a good quality mains transformer and valve rectifier. ★ Valves used ECC85, two EF80's and EZ80 (rectifier). ★ Fully drilled chassis. ★ Everything supplied, down to the last nut and bolt. ★ Size of completed tuner 8 x 6 x 5 1/4in. ★ All parts sold separately. Circuit diagram and illustrations, 1/6, post free. (Free with kit.) Magic Eye 8/6 extra.

★ SMART METAL CABINET. Specially designed to house the above F.M. Tuner, now available. Robust yet attractive design in heavy gauge metal. Beautifully finished in a choice of Hammer Green, Hammer Grey, or Black Crackle. Front panel has apertures for dial, control knobs, and magic eye. Price Complete 25/-; P. & P. 2/6. Front Panel only 10/6. P. & P. 9d.

### TELEVISION TUBE BARGAINS

**COSSOR** 108K 10-in. New & boxed, 15/-, plus 6/- P. & P. 75K 10-in. New & Boxed, 15/-, plus 6/- P. & P.

Ion trap magnets to suit the above, 2/9, 3d. P. & P. **REBUILT TV TUBES.** We can supply all types and all sizes of quality rebuilt tubes at very competitive prices. Write, call or phone for your requirements.

**SETS & COMPONENTS**

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD., Dept. PT/22/11. 138 Lewisham Way, S.E.14. Tideway 6666.

**COMPLETELY REBUILT  
C.R.T.s**

Fully Guaranteed

14in. .. .. .	£6. 0. 0
17in. .. .. .	£8. 10. 0
21in. .. .. .	£8. 10. 0

10/- Old Tube Allowance. C.W.O.  
Free Carr. and Ins. Passenger.  
All types and sizes. S.A.E.  
Enquiries.

**TRADE SUPPLIED**

**BROADBENT, Canal Bridge,  
Birmingham Road, Stratford-  
on-Avon.**

**B.V.A. NEW and rebuilt TV tubes.  
S.A.E.: REDWATT TUBE DISTRI-  
BUTORS, 41 Denmark St., Wakefield,  
Yorks.**

**VALVES EX-TV sets 10/- doz. Lists  
free. 14 Cricklade Road. Swindon.**

**Television Tube Shop**

now stock

**Tubes for every make of set  
OVER 600 TUBES IN STOCK**

12 inch Mullard type ...	£4. 5. 0
12 inch Mazda type ...	£4.15. 0
14 inch Mullard type ...	£5. 5. 0
14 inch Mazda type ...	£5.10. 0
15 inch Mazda type ...	£5.15. 0
16 inch G.E.C. & Mullard type	£6.12. 6
17 inch Mazda & Mullard type	£6.10. 0
17 inch G.E.C. & Brimar type	£6.15. 0
21 inch Mullard type ....	£8. 0. 0

Add 10/- for insured carriage to your door within 48 hours, or 5/- via B.R.S.

**Terms £2 down (plus carriage).**  
All tubes tested before despatch and guaranteed for 12 months. Guarantee cards enclosed with each tube.

**Special Purchase of 110", 17 inch tubes—**

Slight mark. Guaranteed for 12 months.  
Mazda CME 1703 j replace AW43-88,  
GEC 7405A £6.

**Shop Soiled Tubes.**

(Slight scratches or marks) Guaranteed 12 months. Ideal for second set. 12in. 3/18, 3/31 37/6. MW31-74 50/-, 14in. MW 36-44 52/6. CRM141 55/-, 17in. CRM171, MW 43-64 60/-.  
Others available from time to time. Please enquire.

**Service Engineers**  
Our Rebate Scheme shows real savings—send for details.

**Television Tube Shop**

**48 Battersea Bridge Road, S.W.11**  
BAT 6859  
Just South of the Bridge. Open Saturdays.

**RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television" Tower House, Southampton St., London, W.C.2.**

**SETS & COMPONENTS  
(continued)**

**SURPLUS, AND NEW VALVES, guaranteed. S.A.E. for list. Also reclaimed Valves, tested perfect; 5/- maximum plus 6d. postage each. Genuine Valve bargains. Valves bought. Lewis, 46 Woodford Avenue, Iford, Essex.**

**TV SPARES  
LINE OUTPUT  
TRANSFORMERS**

A few examples from our extensive range.

TELEPHONE ORDERS SENT SAME DAY C.O.D.

- Alba T301, 304, 394, 484, 494, 421/6.
- Alba T321, 324, 424, 524, 39/6.
- Baird 164/5/7, 172/5, 1812/15, 62/6.
- Baird P2014/7, P2114/7, 58/6.
- Banner B112/4/7, 124, 412, 436, 65/-.
- Beethoven B77, 80, 94-9, 106-9, 65/-.
- Bush TV53, 69/6; TV24C, 89/6; TUG34, 5 gns.
- Cossor 930-9, 58/6; (new), 30/- (used).
- Decca D14/17, 58/6; DM14/17, 55/-.
- Ekco T221, 231, 311, 284, 330, 55/-.
- Ekco T161, TC162, TC166, TU169, 30/- (used).

- Ferguson 992/6/8 66/9; (new) 30/- (used).
- Ferguson 205-246; 66/9; 306/8, 58/6.
- Ferranti 14T3/4/5, 47/6; 14T2/T1225, 62/6.
- Ferranti T1002/5, 55/-0 T129-138, 47/6.
- G.E.C. BT, 1251/2 1746/8, 2250, 50/-.
- H.M.V. 1824/9, 1840-8, 2805-5902, 69/6.
- K.B. NF 70/FM, MV/OF 100, PVP20, 75/-.
- Masteradio T917, TETT, T409/12, etc. 58/6.
- McMichael TM/C/CR 51-2, 55/-; C/R 53 75/-.
- Murphy V 240/250/280, 65/-; V200, 49/6.
- Pye/Pam/Invicta V4/7, VT4/7, LV30, FV1 908-958, T118-120, 55/-, CS17, etc., 75/-.
- New Scan Coils on all above 65/-.
- Peto-Scott TV123/4/6, 67/6; TV14, 72/6.
- Philco 1457-67, 1717-47, 753-77, 87/6.
- Philco 1114U, 1115, 1437, 1446, 89/6.
- Philco CV76, 77, 84, 87, etc. 65/-, TV94, 89/6.
- Portadyne TA 17, T237, T417, used, 39/6.
- R.G.D. C55, 1455/6, 1755/6/7, etc. 89/6.
- Ultra VT9/17, etc. with U25 5 gns.
- Vidor CN4206-12, 59/6; CN4217-31, 65/-.

We stock or can obtain most L.O.T.'s Scan Coils, Frame O.P.'s and spares.  
**PLEASE SEND S.A.E. FOR IMMEDIATE QUOTE.**

Callers welcome. Open all day Saturday. Terms C.W.O. or C.O.D. Add 2/6 P. & P.

**NEW TV BARGAINS**

We have a limited number of 1962, Slim-line Television Receivers by Famous Makers at special prices. For example 17 inch. List 57 gns. Our Price 44 gns., plus 25/- Carr. & Ins., 110 Tube, Printed Circuit. Contemporary Styling. All Channels. Full guarantee. All in sealed boxes. Immediate despatch on your order.

**TELEVISION CONSUMER SERVICES LTD.**

**112 CAMBERWELL RD., S.E.5.**  
RODney 7917

**SETS & COMPONENTS  
(continued)**

**DARLING . . .** I could sit and admire it all day long now I've a Prime Electrics TV tube. Carriage free. year's guarantee. 12in., 14in. 85/-; 15in., 17in. £8; 21in. £7/10/0. S.A.E. 38 Queensdale Road, London, W11.

**TV TUBES**

**12 MONTHS' GUARANTEE**

12in. and 14in.	£5.0.0
15in. and 17in.	£5.10.0
21in.	£7.10.0

7/6 allowance on old glass  
All fitted new American Guns.  
Phone or Call only NUN 3946

**FELMARC LTD.**

**15 Kingsway, Nuneaton, Works.**

Callers to Works:

**R/O 15 Marlborough Road**

**13 CHANNEL Turret Tuners less valves 17/6. P. & P. 2/6. CAPITAL TELEVISION, 382 Brockley Road, Crofton Park. S.E.4.**

**ELECTRICAL . . . .  
FACTORS**

**OFFER THE FOLLOWING  
UNREPEATABLE BARGAINS**

**Brand New Television 12in. Tubes, Type M.W. 31-74. £2.19.6 (Carr. & Ins. 12/6)**

**Salvaged TV Chassis, 30/-, 5/- carr. Ultra 814, 815, 817, H.M.V. 1824, 1825, 1829, 1840, Philips 1746U, 1748U/45, 1726U/15, 1446U, 1115UF/45, 1115U/15. K.B. KF50, F.V. 30L, H.F. 40L, J.F. 40. Ferguson 993, 998. McMichael T.M.54. Ambassador T.V.11T.M. G.E.C. 6542 Sobell. T.S.14. T174. Master-Radio, T.D.7T, T917. Many others. Salvaged guaranteed 2/9 each. 30/- dozen. 10F1, EF80, EF91, EB91.**

**Short List New Valves**

EF183	7/6	6F19	8/6	30P4	12/-
EF184	7/6	6F23	10/-	30F5	6/-
U26	9/6	10LD12	8/6	30PL1	10/6
U193	8/6	10F18	9/6	30PL13	12/6
PCB89	11/6	30C1	8/-	30FL1	9/6
6D2	5/-	30L1	8/-	30L15	10/6

**Fantastic clearance of Stereo Amplifiers, including two Mullard ECL82 and EZ80, pilot lights, knobs, one speaker circuit diagram, etc. £2.19.6 (carriage 3/6).**

**TELEVISION COMPONENTS AT BARGAIN PRICES**

Please write for your individual requirements.

S.A.E. for Free Lists

**4 HENDERSON ROAD  
EASTNEY : PORTSMOUTH**

SETS & COMPONENTS (continued)

Television Picture Tubes

Twelve Months Manufacturers' Guarantee

- 12 inch ALL Types £5. 0. 0
14 inch " " £5. 10. 0
15 inch " " £7. 0. 0
16 inch " " £7. 0. 0
17 inch " " £7. 0. 0
21 inch " " £8. 15. 0

Deposit 20/- plus 12/6 carriage. Tubes for ALL H.M.V. and Marconi sets at reduced prices. A few shop-soiled tubes at £4.

Cathode Ray Tube Service

35 Broomwood Road St. Paul's Cray, Kent Orpington 21285

REBUILT TUBES, 18 months' guarantee; free advice. S.A.E. to G. HURST, 3 Coniston Road, Sheffield 8.

In Scotland . . . . .

RENVUE

for Better Value

COMPLETELY REPROCESSED TUBE (NEW GUN, RESCREENED, ALUMINISED)

- 12.6v. and 6.3v., 0.3 amp., 17 and 15in. Types ... £6.10.0
12.6v. and 6.3v., 0.3 amp., 14in. Types ... £6. 0. 0
12v., 15in. Types ... £7. 0. 0
2v., 12 and 15in. Types ... £6. 0. 0
Electrostatic 90 degree and 110 degree tubes 10/- extra. Carr. paid.

17in. BBC and STV Receivers ... £19.0.0 COMPLETELY OVERHAULED AND FITTED WITH PROCESSED TUBE STV and BBC 14in. Receivers ... £2.10.0 COMPLETE WITH VALVES AND TUBE. CALLERS ONLY. CARRIAGE EXTRA. OPEN SATURDAY AFTERNOON

Renfrew Electronics Ltd. Anderson Drive Renfrew : Scotland

Tel.: Renfrew 2642

SALVAGED VALVES TESTED ON A MULLARD HIGH SPEED VALVE

TESTER

EXAMPLES FULL CATALOGUE 9d.

VALVE HOLDERS American Octal ... 5/- doz. Novak ... 8d. ea.

RESISTORS Card of 1W Resistors, 72 valves covering complete 10% range 24/- per card. Full range of separate Resistors, Condensers, etc.

VARIABLE CONDENSERS 3-50pf concentric trimmers 3/- doz. Banks of six compression trimmers, 3-30pf... 8d. ea.

GEC CRT's (SALVAGED) SPECIAL OFFER

16in. G.E.C. 6901 ... 30/- ea. 12in. G.E.C. 7102 ... 10/- ea. Personal Callers Only

35M/secs and 10M/secs TURRET TUNERS, less valves (ex receivers) ... 12/6 We can often supply for the actual set you want to fit the tuner in.

TRANSFORMERS

CRT Boost Transformers. 2V, 4V, 6V, 10V, 15V State which required ... 12/6 ea. Heavy Duty Output Transformers. 6 ratios from 13:1 to 43:1 ... 25/- ea. Miniature Output Trans. ... 3/9 ea. Standard Output Transformers, Multi-match ... 10/- ea. Transistor Drivers: 1-1 CT 10/- ea. 3-0-1 CT 12/6 ea. Transistor Output: 6-6-1 CT 10/- ea. 9-2-1 CT 10/- ea. Microphone Transformers, ratio 65:1 ... 35/- ea.

I.F. TRANSFORMERS

Standard 465kc/s ... 12/6 per pair Midget 465 kc/s ... 16/- per pair

AUTO TRANSFORMERS

250W ... 67/8 ea. 100W ... 27/8 ea. 50W ... 20/- ea.

TRANSISTORISED FAULT FINDER

Enables faults to be located quickly. Consists of a two-transistor multi-vibrator in a box. Complete with battery. 32/6

CRYSTALS

GENUINE MULLARD. Boxed OA5 6/- OA41 3/- OA70 3/- OA85 3/- OA79 8/- OA91 8/6

TRANSISTORS

OC16W 48/- OC75 8/- OC19 48/- OC72 8/- OC26 25/- OC76 8/- OC44 11/- OC78 8/- OC45 10/- OC81 8/- OC70 6/6 OC82 18/- OC71 6/6 OC170 17/6

TERMS: C.W.O. or C.O.D. Orders under £1, P. & P. 1/3. Open till 11 p.m. most days.

3d. stamp for list or 9d. for full catalogue.

ARION TELEVISION

4 Macted Road, S.E.15 NEWX 7152

SETS & COMPONENTS (continued)

C. EDWARDS

1070 Harrow Rd., London N.W.10 Ladbroke 1734

500 S/H TV Sets must be cleared as taken part exchange. Condition unknown.

ALL SETS COMPLETE

- 12in. BBC 25/- 13 Channel 50/- 14in. " 50/- " " 75/- 17in. " 85/- " " 125/- Plus 15/- carriage

Guaranteed Valves

- 10C2 10/-, 20D1 6/-, 6K25 8/-, PL38 10/-, PL81 8/-, PY81 8/6, PY80 7/6, PL30 10/-.

1/6 TESTED VALVES?

YES! All popular TV types, fully tested -only 1/6 each. Minimum order: four (post free) One dozen, your choice -only 16/- (post free). Clive Middleton, 11 Hazelwood Road, Hale, Altrincham, Cheshire, Altrincham 5025

RECLAIMED TELEVISION VALVES. 10F1, EF80, EB91, ECL80 2/- each; PCF80, PCC84, PL81, PY81, PY80, PCL83 4/2 each. Postage 3d. per valve. THOMAS, 30 Heolcrodde, Tomma, Neath.

TUBES-AERIALS-VALVES

Regunned tubes, guaranteed one year, full range of aerials and fittings, I.T.V. boosters, valves, braided tuners, T.V. sets, transistor radios and all electrical appliances. Co-axial cables and house wiring cables, fluorescent fittings. All quotations without obligation. Special terms to the trade and Home Engineers. S.A.E. for Catalogue.

G. A. STRANGE

BROADFIELD, NORTH WRAXHALL. Nr. Chippenham, Wilts. Tel. Marshfield 236

IMPORTANT NOTICE !!

"LUMENAR" The Finest Replacement Tube now available with low new price

- 12in. ... £5.10.0
14in. ... £7. 8. 6
17in. ... £8.10.0
21in. ... £11. 0. 0

Carr./Ins. 10/-

"LUMENAR" Tubes are made by MULLARD, The Original Manufacturers and are Fully Guaranteed.

C.W.O. to:

REDWATT TUBE DISTRIBUTORS (BVA Specialists)

41 Denmark Street, Wakefield, Yorks.

(Continued on next page)

## LINE OUTPUT TRANSFORMERS

### SCAN COILS SPECIALISTS

Make: Models Prices  
**ACE:** Spares available.  
**ALBA:** T301, T304, T394, T484, T494, etc. ... 89/6

**AMBASSADOR:** Spares supplied.

**ARGOSY:** Most models available.

**ARMSTRONG:** Spares supplied.

**BAIRD, BANNER, BEEHOVEN:** Spares supplied.

**BUSH:** TV11A, 11B, 12A, 12B, TVG12A, 12B, TRG12A, 12B ... 45/-  
 TVG26, TV32, TV33, TVG34, TVG34A, T36, TV36, TVG36, TV36C, VVG36C, TV43 ... 89/6  
 TV53, TV56, T57, TV57, ... Row'd  
 TVG58, TV62, TV63, TV66, only  
 TV67, etc. ... 69/6

**COSSOR:** 930 & T, 931, 933-4-5, 937, 938A & F, 939 & A & F ... 59/6  
 943T, 940-946, 945, 945B, 949 ... 69/6

**CHAMPION COLUMBIA:** Spares supplied.

**DECCA:** DI7 & C ... 69/6  
 DM1, DM2C, DM3, DM4/C, DM5, DM14, DM17, 444, 555 ... 65/-

**DEFIANT:** TR1453, TR1753 ... 59/6

**DYNATON:** Spares supplied.

**EKCO:** TS93, TC8102, TS105, TS114, TRC124, TC138, TS188, TS193 ... 55/-  
 TRC139, TC140, T141, TV142 ... 79/6  
 T161, TC162, T164, T165, etc. ... 79/6  
 TC208, TV209, T231, T221, T231F, T248, T283, T284, T293, etc. ... 55/-

**ENGLISH ELECTRIC/ELECTRONIC:** Spares supplied.

**FERGUSON:** 103T, 105T, 113T, 135T, 145T ... 64/6  
 941T-953T inclusive ... 59/6  
 991T-997T inclusive ... 64/6  
 203T-246T inclusive ... 69/6  
 306T, 308T ... 65/-

**FERRANTI:** 14T3, 14T3F, 14T4 ... 45/-  
 17K3 & F, 17T3 & F ... 45/-  
 17K4 & F, 17K4 & F ... 45/-  
 17T4 & F ... 45/-  
 14T5, 17SK5, 17K5 ... 45/-

Scancoils, Osc. and Output Txs. for all above makes available.

Post and Packing 2/6. C.O.D. 3/6 extra. All Enquiries S.A.E.

(Continued End Column)

## WYNDSOR TELEVISION

Dept. P.T.  
 ST. ALBANS RD., BARNET, HERTS  
 BAR 1769

## SETS & COMPONENTS (continued)

### H.P. on Regunned C.R.T.s

At No Extra Charge  
 12 Months' guarantee  
 12" & 14" .. £3.10.0  
 17" .. £4.10.0  
 21" .. £5.10.0

Phone or Call only:  
 Rod 7778

**P. J. F. Andrews**  
 61-63 ROSEMARY RD.  
 LONDON, S.E.15

### BRAND NEW and BOXED VALVES GOV. & MANUFACTURERS' SURPLUS

IL4 2/8	PL81 10/-	EY51 7/6
EB91 3/-	PCF80 8/-	EY88 7/6
EF91 3/-	PCC84 7/6	ECL80 8/6
ECC81 5/-	PCL82 10/-	ECC82 7/6
964 8/-	PCL83 12/-	ECC83 7/6
1B48 3/6	PCL84 10/-	EM86 7/6
12AH7 3/6	PCC89 14/6	EL42 8/6
6K7G 1/3	PCC89 11/6	EL41 8/6
6Q7G 5/-	PCC85 8/6	EL84 8/6

S. Woodward, 58 Wiverton Road, Forest Fields, Nottingham.

### TUBES—VALVES—SPARES

TUBES 6 mon. Guar. FITTED FREE  
 8-10-12in. 30/-. 14in. 40/-. 17in. 50/-  
 VALVES, 50,000 in stock, 1,000 types.  
 All set tested before despatch.

Examples:

SUA 4/6	EBC41 8/-	N37 4/6
5V4 4/6	EB30 8/-	N108 10/-
5Z4 4/6	EBF80 6/-	PCC84 4/6
6AU6 4/6	EBL31 12/6	PCF80 4/6
6AQ5 4/6	ECC81 3/-	PCL82 4/6
6BA8 4/6	ECC82 3/-	PenA4 5/-
6BD8 4/6	ECC83 3/-	PI38 4/6
6BG6 10/-	ECC84 4/6	PL42 4/6
6BW8 4/6	ECC85 4/6	PL82 4/6
6DB6 17/6	ECC91 4/6	PL83 4/6
6CH8 4/6	ECH35 6/-	PY31 4/6
6C9 8/-	ECH42 6/-	PY80 4/6
6K25 4/6	ECP30 4/6	PY81 4/6
6L18 4/6	ECL80 4/6	PY82 4/6
6P25 4/-	ECL82 6/-	PZ30 4/6
6V6 4/6	EP80 2/-	R19 7/6
8X4 4/6	EP88 4/6	MU14 5/-
7S7 4/6	EP92 4/6	T41 2/-
7Y4 4/6	EL38 4/6	U22 4/6
10C2 4/6	EL81 4/6	U24 7/6
10F1 3/-	EL90 4/6	U25 10/-
10P13 6/-	EL91 4/6	U37 12/6
12BH7 6/-	EX81 4/6	U31 4/6
20L1 6/-	EY88 4/6	U35 4/6
20P1 4/6	FC4 5/-	U191 7/6
20P3 6/-	KT36 4/6	U281 6/-
185BT 12/6	KT66 7/6	U403 7/6
B36 4/6	ET81 4/6	UL41 4/6
DDT4 5/-	KT88 7/6	UL44 6/-

Most Pre-war 4, 5, 7 and 9 pin valves of British, European and American manufacture, 5/- each. Postage and packing 6d. per valve. Orders over £1—free.  
 NEW TRANSISTORS. Red Spot 8/6. OC45, OC72, OC76, 7/6, OC36 (1 watt power), OC201 (Silicon) 20/-. Postage 3d. each.  
 SPEAKERS: 6in. 5/-. Postage 2/-.  
 VALVE PARCEL. 12 valves, all different.  
 CONSTRUCTOR'S PARCEL. 2lbs. assorted components from TV Sets, resistors, condensers, pots, electrolytics, valveholders, etc. 7/6. Postage 2/6.  
 VALVE PARCEL. 12 valves, all different, as taken out of TV sets. Ideal spares. 3/6. Post and Packing 1/6.  
 Send stamp with enquiries or for full list of 100 valves, tubes, transistors, etc. to: "ST. JOHN'S RADIO", 3 Jews Row, London SW18. Phone: VAN 8822

## LINE OUTPUT TRANSFORMERS

### SCAN COILS SPECIALISTS

Make: Models Prices  
**G.E.C.:** BT1251, BT1252, BT1746, BT1748, BT4743 ... 49/6  
 BT4643, BT5147, BT5246-48 ... 89/6  
 BT5348-BT5643R inclusive ... 49/6 and 89/6

**H.M.V.:** 1824 & A to 1831 inclusive 67/6  
 1840, 1841, 1842-1848 ... 67/6

**INVICTA:** T118, T119, T120 ... 55/-  
 All other models available.

**K.B.:** LFT50, LVT50, LFT60, MV60 ... 107/6  
 All models available, etc.

**MARCONI:** All models available.

**MASTERADIO:** All models available.

**McMICHAEL:** All models available.

**MURPHY:** V200, V202C ... 57/6  
 V240, V250 ... 95/-

**PAM, PETO SCOTT PHILCO:** All models available.

**PHILIPS:** 1768U, 2168U ... 105/-  
 All models available.

**PILOT:** All models available.

**PORTADYNE:** All models available.

**PYE:** CTM4, FV4C, FV4COL ... 55/-  
 V4, VT4, V7, VT7 ... 55/-  
 LV30, FV1, FV1C ... 69/6  
 CB17F, CTM17F, CW17 ... 69/6  
 CW17C, CW17CF, CW17F, etc. ... 69/6  
 All models available.

**RAYMOND:** All models available.

**REGENTONE:** All models available.

**R.G.D.:** 6017T, 7017, C54, etc. ... 59/6  
 All models available.

**SOBELL:** TS17, T346 ... 65/-  
 All models available.

**STELLA:** ST5721U ... 105/-  
 ST8617U, ST8621U, ... 105/-  
 ST8917U ... 105/-

**STRAD, TELEVOICE, TRUIVUE:** Available.

**ULTRA:** 86 series, 815 series, with U25 etc., complete ... 79/6  
 All models available.

**VALRADIO:** Spares available.

**VIDOR:** CN4217-CN4231 inclusive 65/-

**WESTMINSTER:** Spares available.

**WHITE-IBBOTSON:** Spares available.

Scancoils, Osc. and Output Txs. for all above makes available.

Post and Packing 2/6. C.O.D. 3/6d. extra. All Enquiries S.A.E.

## WYNDSOR TELEVISION

Dept. P.T.  
 ST. ALBANS RD., BARNET, HERTS.  
 BAR 1769

**FOR SALE**

**1,000 TELEVISIONS**, all makes, from £3 working, 10/- not. Callers only, 9 till 6 including Sats. 39 Whitehorse Lane, Stepney, London.

## TV AERIALS POST FREE UNBEATABLE QUALITY AND PRICES.

**LOW LOSS CO-AX CABLE**  
6d. YD.

CATALOGUE AND CABLE SAMPLE FROM  
**A.E.S.**

**13 ST. THOMAS STREET, WEYMOUTH**

**VALVE CARTONS** at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a Godwin Street, Bradford 1.

**TV's FOR SALE**

PRICES REDUCED

BBC/ITA in good working order:	C.R.T. Good Rebuilt
14in. Ultra V1815: KB LVT30	£13    £17
14in. Ekco T221 or T283	..    £18    £21
14in. Ferguson 982	..    £29    £13
17in. Plessey: RGD	..    £17    £21

Send for Lists                      Carr. Paid

**CADMAN'S**

Bryan Street, Hanley  
Phone: Stoke-on-Trent 2357

**GARRARD 210 29/8/6**; B.S.R. UA14 27/15/6; T.U.9 24/2/6; B.S.R. Tape Deck 27/10/6. Set of 7 Transistors, standard quality. 32/6. Full list from—H F. JAMES, 21 Claremont Road, Twickenham, Mdx.

**Star TV Tubes**

70/-

all sizes up to and including 17in. includes old glass or plus 7/6 without C.W.O. Carriage 7/6.

**WHY PAY MORE**

new guns, 12 months' guarantee.

also 20/- each

12in. 14in., Part Exchange Televisions. Callers only.

**ARTHUR SLARK**

43-45 Thicketford Road, Tonge Moor, Bolton.  
Phone: 26684.

**110° LINE OUTPUT Transformers.** 17in. and 21in. 12/6 post free. WEBB, 649 London Road, Hadleigh, Essex.

Television Tubes Rebuilt. Please note we have appointed M/S E. S. Stradwick, 17 Hollingdean Road, Brighton 7, as Sole Agent for our Genuine Rebuilt Television Tubes for the South Coast. For details of prices, etc., please refer to our advertisement in the inside front cover.

**MARSHALL'S**

for TELEVISION LIMITED

181 St. Ann's Road, Tottenham, London, N.15.  
Stamford Hill 3267 & 5855

**FOR SALE**

(continued)

**ALUMINIUM LADDERS/STEPS.** Gigantic offer, 400 models. SANCO LTD., 17 (P.T.) Boundary Rd., Hove.

**METAL RECTIFIERS**

RECTIFIERS—CONTACT COOLED.

14KA1282 (FCU10) type 250 v., 250 mA, 13/6;  
14KA1283 (FCU11) type 250 v., 300 mA, 17/6;  
350 mA, 19/6.

RECTIFIERS—FIN TYPES

Equivs. for RM1 250 v., 250 mA, 13/6; RM5 250 v., 300 mA, 17/6; 11A989 300 mA, 15/6;  
14A46 16/8; 14A87 19/6; 14A100 22/6; 14A124 19/6; LW7 17/6.

**CABY MULTIMETERS**

A11 - 16 ranges, 25, 12.5, 12.5 - 20 ranges, 25, 10, S.A.E. for full details.

**ARMCHAIR EXTENSION VOLUME CONTROL** unit for TV Radio Amplifiers, etc. Easily fitted, perfectly safe, 19/6.

**TRANSISTORS**

ALL 1st GRADE  
OC1 6/-, OC41 9/6, OC45 8/6. Set of 6 + Diode, 40/-, OC170 9/6, OC28 16/-, Under 41 P. & P. 6d. over 41 Post Free. C.O.D. 2/6.

**DURHAM SUPPLIES**

175 Durham Road, Bradford 8, Yorkshire.

**100 BAYS** of brand new adjustable Steel Shelving, 72in. high by 34in. wide by 12in. deep, stove enamelled dark green. Sent unassembled. Six shelf bay—£3/15/0. Sample delivered free. Quality discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel: 69018.

**WANTED**

**WANTED NEW VALVES** and transistors, any quantity. S. N. WILLETTS, 43 Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

**NEW VALVES WANTED** — EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. DURHAM SUPPLIES, 175 Durham Rd., Bradford 8, Yorkshire.

**A PROMPT CASH OFFER** for your surplus brand new Valves, Speakers, Components Test Instruments, etc. R.H.S. Beverley House, Manville, Terrace, Bradford 7.

**SERVICE SHEETS**

**SERVICE SHEETS.** Television 4/3; Radio 2/9. DARWINS, 19 George St., St. Helens, Lancs.

**SERVICE SHEETS.** Radio, TV, 5,000 models. List 1/-. S.A.E. enquiries: TELRAY, 11 Maudland Bk., Preston.

**FAULTFINDER FILES (TV)** showing common faults that each receiver is prone to and other useful servicing information, 2/- each. List 9d., plus postage S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

**SERVICE SHEETS.** Radio and TV 4/- each. List 1/-. All orders dispatched on day received. Also manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

**FOR SALE**

(continued)

**SERVICE SHEETS.** We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- each, old type receivers a speciality. Guaranteed return of post service. Service Sheet list 1/-, manufacturers' Manuals for sale and hire, list 1/-. S.A.E. please. Mail orders only to: S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

**SERVICE SHEETS;** also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20 Extension, Shepherd's Bush Market, London W.12 (Phone: SHE 3052).

**SERVICE SHEETS.** Radio and Television 4/- each, list 1/-. All old and modern receiver sheets available. Faultfinder files 2/- each. List now available 1/-. KAYBRO PUBLICATIONS, 44 Old Bond Street, London W.1.

**SERVICE SHEETS**

For all makes of Radio and Television—1930-1962. Prices from 1/-. Free fault-finding guide with all Service Sheets. Please send S.A.E. with enquiries.

Catalogue of 6000 models, 1/6.

Special offer of 125 Radio/TV Sheets covering 870 popular models, 20/-.

Hamilton Radio, Western Road, St. Leonards, St.

**BOOKS & PUBLICATIONS**

**FIND TV SET TROUBLES** in minutes from that great book, "The Principles of TV Receiver Servicing," 10/6 all book houses and radio wholesalers. If not in stock, from Secretary I.P.R.E., 20 Fairfield Rd., London, N8.

**SITUATIONS VACANT**

**TV FIELD ENGINEERS.** Permanent, pensionable vacancies are available in many parts of England and Scotland. Due to continued expansion promotion prospects are good in this National Rental Organisation. Apply to: Service Executive ROBINSON RENTALS LTD., 43-45 St. Peters St., Bedford or call at any local Branch.

**EDUCATIONAL**

## Radio Television & Electronics

Learn at home with the world's largest home study organisation, Brit. I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for FREE prospectus stating subject to

**I.C.S.**

Dept. 516  
Intertext House, Parkgate Road,  
London, S.W.11.

(Continued on next page)

**EDUCATIONAL**  
(continued)

**THE INCORPORATED Practitioners in Radio and Electronics (I.P.R.E.) Ltd.** Membership Conditions booklet 1/-. Sample copy of I.P.R.E. official journal 2/- post free.—Secretary, 20 Fairfield Road, London, N.8.

**"HOW AND WHY"** of Radio and Electronics made easy by a new, non-maths practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment, as well as knowledge of this fascinating subject. Free brochure from Dept 12, P.T. RADIO-STRUCTOR, Reading.

**ELECTRONICS**

Key to YOUR Future?



An exciting career—  
A new Hobby—Your  
own spare- or full-  
time BUSINESS?

New experimental course includes big kits for building test gear and a complete AM/VHF receiver.



**FREE**

brochure from

**RADIOSTRUCTOR**  
DEPT. E78, READING, BERKS.

**NEW VALVES!**

Guaranteed Set Tested  
24-HOUR SERVICE

1R5, 1R5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6.

DAF96, DF96, DK96, DL96, SET of 4 26/-

1D5	7/-	DL92	5/11	PCF80	7/9
1R5	6/-	DL94	6/9	PCF82	7/8
1S5	4/6	DL96	6/9	PCL82	8/3
1T4	3/8	EB91	3/-	PCL83	11/6
3R4	5/11	EBC41	7/6	PCL84	7/6
3V4	6/9	EBF90	7/9	PL36	10/9
5U4G	4/3	EBL21	12/6	PL81	8/6
5Y3GT	5/6	ECC40	14/6	PL82	6/6
5Z4G	7/3	ECC81	4/9	PL83	6/6
8AM6	2/9	ECC82	5/9	PL84	8/-
6K7G	1/8	ECC83	6/3	PY32	11/-
6K8G	4/9	ECC84	8/-	PY80	7/-
6Q7G	5/6	ECC85	7/6	PY81	7/-
6V8G	4/-	ECP80	7/3	PY82	6/6
6V8GT	6/6	ECP81	8/3	PY83	7/3
6X5GT	4/3	ECH21	12/6	U25	11/6
12K7GT	4/3	ECH42	7/9	UABC90	8/-
12K8GT	9/-	ECL80	6/9	UAF42	6/6
12Q7GT	4/6	EF40	12/3	UBC41	7/-
35L9GT	5/-	EF41	7/6	UBC42	6/6
35Z4GT	5/9	EF80	4/3	UC85	6/6
AZ31	8/9	EF85	4/6	UCH21	12/6
CL33	11/9	EF98	8/9	UCH42	7/6
DAC32	8/6	EF99	9/9	UCH81	7/-
DAF91	4/6	EF91	2/9	UC82	9/9
DAF96	6/9	EL41	9/9	UCL83	13/-
DF33	8/6	EL84	6/3	UF41	6/6
DF91	3/3	EY51	7/3	UF85	6/6
DF96	6/9	EY96	7/6	UF89	6/9
DH77	5/-	EZ40	6/-	UL41	7/-
DK32	10/6	EZ41	6/9	UL84	6/6
DK91	6/-	EZ80	5/9	UY21	13/-
DK92	7/3	EZ81	6/-	UY41	5/6
DK96	7/3	MU14	6/-	UY85	6/3
DL33	7/6	PC84	6/9	P4B	8/6
DL36	8/6	PC89	9/-	Z77	2/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 3/- extra. Office address, no callers.

**GERALD BERNARD**

(Note new address—formerly of Leeds)  
83 OSBALDESTON ROAD,  
STOKE NEWINGTON, LONDON, N.16

**NEW EDITION OF THE Mullard MAINTENANCE MANUAL**

This is a completely new and up-to-date edition including all current replacement types. It contains valuable new material and is an essential source of reference for every Service Engineer. 16/-. Postage 1/-.

**TELEVISION SERVICING** by G. N. Patchett, 25/-. Postage 1/-.

**COLOUR TELEVISION** by P. S. Carnit & G.B. Townsend, 85/-. Postage 1/-.

**RADIO CONTROL MANUAL** by E. L. Safford Jr., 25/-. Postage 1/-.

**SOUND & TELEVISION BROADCASTING**. General Principles by K. R. Sturley, 45/-. Postage 1/-.

**TV FAULT FINDING** a Data Pub: 5/-. Postage 6d.

**RADIO VALVE DATA**. Compiled by "WV" 7th Ed. 6/-. Postage 10d.

**TELEVISION SERVICING HANDBOOK**, by G. J. King, 30/-. Postage 1/-.

**COMPLETE CATALOGUE** 1/-.

**THE MODERN BOOK CO.**

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books  
19-21 PRAED STREET LONDON, W.2  
Phone: PADdington 4185  
Open 6 days 9-6 p.m.

**BBC - ITV - F.M. AERIALS**



**B.B.C. (BAND 1)**. Telescopic loft, 19/6. External, S/D 28/3.  
**I.T.V. (BAND 3)**. 3 Element loft array, 24/-. 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.  
**COMBINED B.B.C. + I.T.V.** Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting, 63/9 also available.  
**F.M. (BAND 2)**. Loft "H", 28/-. 3 Element loft, 52/6. S/D loft, 12/6. External S/D, 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept. P.T.)**  
3<sup>rd</sup> Godstone Road, Kenley, Surrey

**TUBES**

All types  
**12"-17" ONLY 30/-**  
Also a few 21" at only 50/-  
**WHY PAY MORE ?**

These tubes are ex rental stocks, each one fully tested before despatch. Guaranteed to give excellent results, and complete satisfaction, or money refunded. Please state type required, or Model No. of set.

Carr. up to 17in. 10/-; 21in. 12/6.  
**SEND NOW WHILE STOCKS LAST TO**  
**REGENT SUPPLIES Dept. P.T.**  
124 Athelstan Rd., Southampton

**REBUILT TV TUBES**

FULLY GUARANTEED  
12 MONTHS  
Complete New Gun Fitted  
In Every Tube

12in. ... ..	£4.00
14-15in. ... ..	£4.10.0
17in. ... ..	£5.00
21in. ... ..	£7.00

Immediate Delivery. Carriage and Insurance 10/- extra.  
**ALLOWANCE ON OLD TUBE**

**NU-GUN TELETUBES LTD.**

3 THE MEWS  
Duckett Road, Harringay, London, N.4  
Telephone: MOUntview 2903

**RES/CAP. BRIDGE 38/-**

p. & p. 2/6  
Checks all types of resistors, condensers & RANGES  
Built in 1 hour. Direct reading.  
**READY CALIBRATED**  
Stamp for details of this and other kits.  
**RADIO MAIL (DEPT. 5P)**  
Raleigh Mews, Raleigh Street, Nottingham

**FIRST-CLASS TELEVISION and RADIO COURSES**

**GET A CERTIFICATE!**

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification or learn Servicing and Theory. Let us show you how.

**FREE GUIDE**

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ. London, B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career

**FOUNDED 1885—OVER 150,000 SUCCESSSES**

**NATIONAL INSTITUTE OF ENGINEERING**  
(Dept. 462), 148 HOLBORN LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.  
Australia: P.O. Box 4570, Melbourne.



# CLARKSON'S TUBE CHANGE

6A DENISON ROAD, LEEDS 2  
Tel. Leeds 24576.

We are now able to offer SUPER SCREEN TV TUBES with 12 months' guarantee at the keenest exchange price ever.

Example:

Tubes all types	Cash allowance on return of old tube	Actual cost of Tube
12"-14" £5	15/-	£4. 5.0
15"-17" £6	25/-	£4.15.0
21" £8	30/-	£6.10.0

Carriage and Insurance 10/- extra

These tubes are COMPLETELY REBUILT by experts, with the most up-to-date electronic equipment, and are fitted with the famous American Golden Grid Electron Gun. Many thousands of these tubes are in service today. Our factory is open to inspection to readers of "Practical TV". Technical advice and queries are answered free of obligation. All tubes are dispatched with adhesive paper and return labels. Cash allowance is sent on receipt of old tube.



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Post Free 15/- per pair.

**AVO LTD** . AVOCET HOUSE,  
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.

Victoria 3404 (12 lines)



A Member of the Metal Industries Group of Companies

# "THREE STAR"

RE-BUILT TELEVISION TUBES

- ★ Manufacturer's Own Make of Gun
- ★ Re-screened for Greater Contrast
- ★ Aluminised for Better Brightness

## TWO WAY TESTED

Free carriage and insurance.

ALL TYPES AND SIZES

12" - £4.10      14" - £4.15

15" - £5. 0      17" - £5.10

21" - £7. 0

C.O.D. or Cash with order.

## DARLING ELECTRONICS

Dept. TV, 62 High Street, Croydon, Surrey

MAIL ORDER ONLY—NO CALLERS

## RST

MAIL ORDER DEPARTMENT  
211 Streatham Road, Mitcham, Surrey  
ALL VALVES LISTED ARE NEW STOCK  
& Terms C.W.O. or C.O.D. Postage 3d. per valve.  
MITCHAM 8201

AZ1 15/-	EF92 4/-	PCF82 7/-	UY76 7/-	6K9G 7/6
B65 3/6	EL42 10/-	PCL82 9/6	VP4B 17/6	6K8GT 7/6
DAF91 7/6	EL84 6/9		W81M 6/-	6L1 9/6
DAF96 8/9	EL90 8/6		W142 8/6	6L18 13/-
	EM80 8/6		W719 7/6	6L8G 7/6
DF91 4/-	EM81 8/6		W727 7/6	6L18 10/-
DH19 6/-	EY81 8/6	PENAA 4	X78 21/-	6L19 17/6
DK91 8/-	EY84 10/-		X79 21/-	6N7G/GT 6/6
EABC80 8/-	EY86 3/6	PEN4VA 17/6	Z21 12/6	6SL7GT 6/6
	EY91 4/-		Z77 4/-	
EAF42 9/6	EZ35 6/-	PL36 15/-	Z152 5/-	6SN7GT 5/6
EB91 4/-	EZ40 7/-	PL81 12/-	Z179 5/-	6V6G 5/6
EB41 9/-	EZ41 7/-	PL82 8/-	1R5 7/6	6X5GT 5/-
EBF80 8/6	EZ42 7/6	PL83 10/6	1R5 7/6	7S7 10/-
EBF89 8/6	EZ81 7/-	PY80 7/6	SU4G 4/6	7Y4 7/6
EC91 9/6	FC2 21/-	PY81 7/6	SV4G 9/6	8D3 4/-
ECC83 5/-	FC4 15/-	PY82 7/6	SY3GT 8/6	
ECC81 5/9	FC13 21/-	PY83 8/6	SZ4G 10/-	
ECC83 7/6	FC13C 21/-	R10 10/-	6A8GT 13/6	10LD11 15/-
ECC84 8/6	GZ32 10/6	R19 10/-	6AL5 6/-	12AH8 9/-
ECC85 8/-	H30 5/-	TF22 15/-	6AM6 4/-	12AT6 7/6
ECF80 8/6	H33 9/-	U147 7/6	6AN5 7/6	12AT7 5/6
	H83 9/-	U153 8/6	6AQ5 6/6	12AU7 9/6
ECF82 8/6	HBC90 9/6	UABC80 7/-	6BA6 6/-	12AX7 7/6
	HL22 8/6		6BE8 7/-	12BA6 7/6
ECH42 9/6	HL133D 10/-	UAF42 8/6	6BJ6 6/-	12BE6 7/6
ECH91 8/-	KT33C 8/-	UBC41 9/6	6BR7 12/6	12BH7 10/-
ECL90 9/-	KT66 15/-	UBF80 8/6	6BW6 7/-	12J7G/GT 8/6
	LZ319 12/6	UCH42 8/6	6BW7 5/-	12K7GT 8/6
ECL82 9/6	MKT4(5) 15/-	UCH81 9/6	6X85 8/-	
EF37A 5/-	(or 7) 17/6	UCH81 9/6	6D2 4/-	12K8GT 5/-
EF40 15/-	ML4 8/6	UCH83 8/-	6F1 10/6	12K8GT 8/6
EF41 8/-	MSP4 17/6	UCL83 13/6	6F12 4/-	12Q7 10/-
EF42 10/-	MU14 9/-	UF41 7/6	6F13 10/-	12Q7GT 8/6
EF50(A) 4/-	MX40 15/-	UF89 8/6	6FGC 4/6	12Q7GT 6/6
EF90 5/-	N142 9/6	UF93 8/6	6FOT 7/6	35Z4GT 7/6
EF65 8/6	N153 10/-	UL41 8/6	6K7 2/-	60L6GT 7/6
EF86 10/6	PCC84 9/-	UL84 7/-	6K7G 3/-	
EF89 9/-	PCF80 9/6	UY41 7/6	6K7GT 8/6	
EF91 4/-				

SEND FOR LISTS.

Quotations given for any types not listed. Obsolete and old types a speciality.

FREE TRIAL OFFER!

SIMTECH

## BOOKS ON FREE TRIAL, EASY PAYMENT PLAN!

Put Money-Making Time  
Saving know how at your  
fingertips!

### TRY ANY THREE BOOKS ON NO RISK FREE TRIAL

Look over the list of books and select the first three books you would like to examine. Note the book numbers on the coupon. Additional books you would like to see may be entered separately, and will be sent to you after completion of the first transaction.

#### SPECIAL OFFER COYNE ELEMENTARY PRACTICAL RADIO-TELEVISION SET OF THREE VOLUMES, total 1,038 pages, sturdy Vinyl washable covers. £3.12.6d. the set!

These three volumes present the principles of construction, operation and testing of radio and television equipment in a SIMPLE, EASY TO FOLLOW manner.

By using NEW & DIFFERENT methods of explanation these books clearly explain the direct relation between the various parts of sets. This information is especially helpful in repair work where many times a burned out valve, resistor or transformer is actually caused by some other defective part of a circuit. Until the cause of the trouble is removed the parts would continue to burn out. For this reason each part of the radio or television unit is explained, thus, making the material especially helpful to the experienced radioman, as well as the amateur.

One very important way in which these books differ from many other radio and television books is that the publishers did not try to assume the "extent of technical knowledge" of the reader. Every subject is explained COMPLETELY—while at the same time keeping it brief and to the point.

You will find hundreds of photos, charts, diagrams, etc., in these books. These have been provided to make it easier to understand the explanations. To set this special offer, send no money now, then 12/6d. after free examination, and 20/- per month.



#### No. 9 *Pin-Point* Transistor troubles in 12 minutes (Coyno)

Trouble-Shoot every type of circuit in ALL transistorized equipments! 525 pages; hundreds of illustrations; 120 check charts; includes portable Transistor Wireless Sets, Preamplifiers, Heating Aids, Amplifiers, Car Radio, TV sets, and special types of equipment. Test procedures, trouble shooting charts and much useful reference data. Price 47/6.

#### No. 4. LATEST INSTRUMENTS FOR SERVICING RADIO AND TELEVISION. (Coyno).

This up-to-the minute book tells all about modern radio, TV and electrical testing equipment and how to use it. Money-making short cuts on trouble-shooting, servicing, construction, and other jobs. Over 530 pages, 250 photos and diagrams. Covers Multimeters, Resistors, Ohmmeters, Oscilloscopes and many others. All data has been pretested in the Coyne radio shops. Vinyl cloth covers. 28/-.

#### No. 3. PRACTICAL TELEVISION SERVICING AND TROUBLE SHOOTING MANUAL. (Coyno).

A book of fast time saving methods for servicing TV receivers. Includes dozens of new testing ideas all of which have been proven on the job. Contents include TV Servicing methods, TV Servicing Instruments, Tuners, Video I.F., Amplifiers, alignment, etc., with 200 crystal clear photos and diagrams. 137 pages. Washable vinyl cloth covers. Price 54/-.

#### No. 22. PIN POINT COLOUR TV TROUBLES IN 15 MINUTES. Edited by Robert G. Middleton. (Coyno).


This book deals with 150 types of faulty pictures and sound with over 1000 troubles which may be the cause. Some of the subjects covered are: Antennae, Tuner, Video and Luminance Amplifiers, Matrices, Picture Tubes (Black and White, and Colour), One-Gun Tubes, Set up of Colour Tubes, Colour Killer and Automatic Chroma Control, Low Voltage, Power Supply, TV Sound, etc. Picture Pattern Section - 362 Check Charts, Diagrams and Photos. 548 pages. Price 47/6.

#### No. 18. REFERENCE MANUAL OF TRANSISTOR CIRCUITS. Mullard.

Features 60 circuits you can build, 241 diagrams. 308 pages. 12/6.
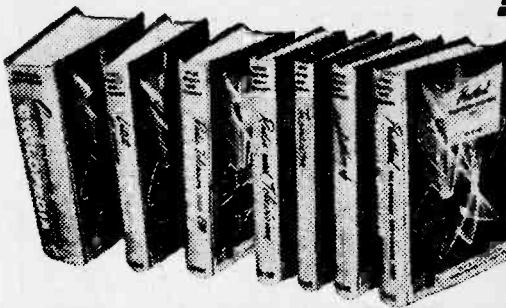
#### No. 6. COYNE TELEVISION SERVICING CYCLOPEDIA. Harold P. Manly. (Coyno).

Quick and concise answers to TV problems in alphabetical order, cross indexed, fully illustrated, covers hundreds of questions involving radio, TV, electronics operation and repair. 450 illustrations; photos, diagrams, charts, test patterns, etc., 860 pages. Vinyl cloth covers. Price 47/6.



#### No. 19. REFRIGERATION SERVICE MANUAL. H. P. Manly.

Learn Refrigeration! This manual is a course in itself. Packed with information to enable you to do that repair job yourself. Used by many leading refrigeration firms as a standard reference. Features 364 pages together with 187 illustrations bound in cloth. An excellent buy at only 24/- plus postage.

#### No. 7. TRANSISTOR CIRCUIT HANDBOOK. Louis E. Garner. (Coyno).

39/6.

#### No. 8. PIN POINT TV TROUBLES IN 10 MINUTES. Your most useful on-the-job "tool"! Quickly and easily pin-points the exact trouble in any TV set. Covers 50 symptoms, 700 trouble spots. Over 540 cross-indexed pages; 60 time-saving Check-Charts; 290 diagrams and photos; explanation of circuits and designs. 31/8.

#### No. 12. RADIO DESIGNER'S HANDBOOK. F. Langford-Smith. Ilife.

55/-.

#### No. 16. PRINCIPLES OF FREQUENCY MODULATION. R. S. Camies. Ilife.

21/-.

#### No. 11. PRINCIPLES OF TRANSISTOR CIRCUITS. S. W. Amos. Ilife.

21/-.

#### No. 20. PRINCIPLES OF SEMICONDUCTORS. M. G. Serrogie. Ilife.

21/-.

#### No. 10. TELEVISION RECEIVER SERVICING, Vol. 1. Spreadbury. Ilife.

26/-.

#### No. 17. ELECTRONIC COMPUTERS. Principles and Applications. Ilife. T. E. Ival, 2nd Edition. 25/-.

#### No. 15. WIRELESS SERVICING MANUAL. W. T. Cocking. Ilife. 17/6.

#### No. 38. COLOUR TELEVISION, NTSC System, Principles and Practice. P. A. Carr, G. E. Townsend. Ilife. 25/-.

#### No. 21. BASIC MATHEMATICS FOR RADIO AND ELECTRONICS. Ilife. 17/6.

#### No. 23. INTRODUCTION TO LAPLACE TRANSFORMS. For radio and electronic engineers. W. D. Day. Ilife. 32/6.

#### No. 84. RADIO VALVE DATA. Compiled by "Wireless World". Ilife. 6/-.

#### No. 25. THE OSCILLOSCOPE AT WORK. A. Haas and R. W. Hollows. Ilife. 18/-.

#### No. 28. NUMERICAL METHODS FOR HIGH SPEED COMPUTERS. G. N. Lance. Ilife. 42/-.

#### No. 27. SECOND THOUGHTS ON RADIO THEORY. "Cathode Ray" of "Wireless World". Ilife. 25/-.

#### No. 23. FOUNDATIONS OF WIRELESS. M. G. Serrogie. Ilife. 15/-.

## LIMITED OFFER! ACT NOW!

Just mail coupon for free trial. After 7 days send only low price or return books and pay nothing. If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum three books value not exceeding £5.0.0). To buy one book send one-half in 7 days, and one-half in 30 days.

#### To SIM-TECH BOOK COMPANY (U.K.)

Mail Order Division, DEPT. PTV16, Gaters Mill, West-End, Southampton, Hants.

Please send me the Elementary Radio TV Set as per special offer.

RUSH (Insert Book number here) ( ) ( ) ( )

Tick here if enclosing full price, we pay postage (Coyno Books only). Same 7 day money-back guarantee.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

City \_\_\_\_\_ County \_\_\_\_\_

Postage charges: Orders up to 23 allow 1/6, 25 or over allow 2/-. OVERSEAS ORDERS PROMPTLY SHIPPED on receipt of full amount. Same guaranteed satisfaction.

# TELEVISION TUBES RE-BUILT BY "RE-VIEW"

	PRICE:		
12in. ... ..	...	...	£4.10.0
14in. ... ..	...	...	£4.15.0
15in. ... ..	...	...	£5. 0.0
17in. ... ..	...	...	£5. 0.0
21in. ... ..	...	...	£7. 0.0

**SAVE £££s**

Correct voltage heaters  
All types



**TWELVE MONTHS' GUARANTEE**

Free carriage and insurance

Cash with order or C.O.D.

Be one of our satisfied customers. Call and see our TUBES REBUILT and TESTED  
**RE-VIEW (London) LTD., 385 London Road, West Croydon, Surrey**

Terms to the Trade

Tel.: THORNTON HEATH 7735

## FREE TO AMBITIOUS ENGINEERS — THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

### Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee  
"NO PASS—NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

### WHICH IS YOUR PET SUBJECT ?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

**GET SOME  
LETTERS AFTER  
YOUR NAME!**

A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.Prod.E.  
A.M.I.M.I.  
A.I.O.B.  
A.F.R.A.S.  
B.Sc.  
A.M.Brit.I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.  
SCHOOL OF  
ELECTRONICS**



### POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"  
 (Write if you prefer not to cut page)  
 **NAME**.....  
 **ADDRESS**.....  
 .....  
 **SUBJECT OR EXAM THAT INTERESTS ME**..... (SE/20).

**BRITISH INSTITUTE OF ENGINEERING  
TECHNOLOGY (Incorporating E.M.I. Institutes)**  
(Dept. SE/20), 29 Wright's Lane, London, W.8

**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**

**CRT BOOSTER TRANSFORMERS**  
 TYPE A. OPTIONAL 25%, and 50%. BOOST.  
 2 V. OR 4 V. OR 6.3 V. OR 10.8 V. OR  
 13.8 V. MAINS INPUT. 12/6

**TYPE A2. HIGH QUALITY. LOW CAPACITANCE.**  
 10/15 pF. OPTIONAL BOOST 25%, 50%,  
 75%. MAINS INPUT. 16/6

**TYPE B. H. MAINS INPUT. MULTI OUTPUT.**  
 4, 8.5, 7.3, 10 and 13 VOLTS. BOOST 25%,  
 AND 50%. LOW CAPACITY. 21/-

Full instructions supplied.

**TRIMMERS.** Ceramic. 30, 50, 70 pF. 9d.; 100 pF.  
 150 pF. 1/2s; 200 pF. 1/6; 500 pF. 750 pF. 1/0.

**RESISTORS.** Preferred values. 10 ohms, 10 meg.,  
 1 w.; 4d.; 1 w.; 6d.; 1 w.; 8d.; 2 w.; 1/-.

**HIGH STABILITY.** 1 w. 1%, 2/- Preferred values.  
 10 ohm to 10 meg. Ditto, 5 ohm, 100 ohm to 10 meg. 9d.

**WIRE-WOUND RESISTORS** 1/3  
 15 watt 25 ohms—10,000 ohms 2/-  
 12.5K to 50K 10 w. 3/-

**AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE**

Double Play	7in. reel, 2,400ft	60/-	Spare Plastic Reels
	5in. reel, 1,200ft	37/6	
Long Play	7in. reel, 1,800ft	35/-	
	5in. reel, 1,200ft	23/6	5in. 1/6
	5in. reel, 900ft	18/6	5in. 2/-
Standard	7in. reel, 1,200ft	25/-	5in. 2/-
	5in. reel, 600ft	16/-	7in. 2/6

"Instant" Bulk Tape Eraser and Head Defuser, 200/250 v. A.C., 27/6. Leaflet, S.A.E.

**O.P. TRANSFORMERS.** Heavy Duty 50 mA, 4/6. Mid-ratio, push-pull. 7/6. Ditto, 10w, 15/6. Miniature, 384, etc., 4/6. L.F. CHOKES 15/10 H, 60 Hz, 5 mA, 5/-; 10 H, 85 mA, 10/6; 10 H., 150 mA, 14/-.

**MAINS TRANSFORMERS 200/250 v. A.C.**  
 Postage 2/- each transformer.

STANDARD, 250-0-250, 60 mA, 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350	22/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a.	10/6
MIDGET, 220 v. 45 mA, 6.3 v. 2 a.	15/6
SMALL, 220-0-220, 65 mA, 6.3 v. 2 a.	17/6
STD., 250-0-250, 65 mA, 6.3 v. 3 a.	17/6
HEATER TRANS. 6.3 v. 14 amp.	7/6
Ditto, tapped sec. 2.4, 6.3 v., 14 amp.	8/6
Ditto, sec. 6.3 v. 3 amp.	10/6
GENERAL PURPOSE LOW VOLTAGE, 2a., 3.4, 5.6, 8, 9, 10, 12, 15, 18, 24, 30w.	22/6
AUTO TRANSFORMERS, 150 w.	22/6
0, 120, 200, 230, 250 v., 500 w.	22/6

**ALADDIN FORMERS** and core, 4in., 8d.; 4in., 50c. 0.3in. FORMERS 6987/8 and Cans TV/2. 4in. sq. 4/6 and 4in. 1/2in. 1/6.

**SOLENOID Soldering Iron,** 200 or 240 v., 25 w. 24/-.

**MAINS DROPPERS,** 8in. x 14in. Adj. Sliders, 0.3 amp., 1,000 ohms, 4/3. 0.2 amp., 1,000 ohms, 4/3.

**LINE CORD,** 0.3 amp., 60 ohms per ft., 0.2 amp., 40 ohms per ft., 2 way, 1/2 per ft., 3 way, 1/2 per ft.

**LOUDSPEAKERS** 8" 30/6, 9" 21/6, 10" 4in. 19/6, 10in. 17/6. 8in. Plesey, 19/6. 7in. x 4in. Rola, 18/6. 4in. Rola, 18/6, 10 x 6in., 27/6. 10in. 30/-.

4in. Hi-Fi Tweeter, 25/-; 12 in. R.A., 30/-.

**STENOPIAN HF012,** 10in. 3 to 15 ohms, 10w., 95/-.

2in. Baker 15 watt 3 ohms, 15 ohms, 9/6.

**CRYSTAL DIODE G.E.C., 2/-.** GEX34 J., OA81, 3/-.

**HIGH RESISTANCE PHONES,** 4,000 ohms, 15/- per pair.

**MIKE TRANSF.** 50 : 1, 3/6 ea.; 100 : 1, Potted, 10/6.

**SWITCH CLEANER,** Fluid spirit, approx. 4/3 tin.

**TWIN GANG TUNING CONDENSERS,** 355 pF. miniature 1in. x 1 1/2in., 11in., 500pF standard with trimmers, 9/-; midget, 7/6 with trimmers, 9/-.

**SINGLE,** 50 pF., 75 pF., 100 pF., 160 pF., 5/6. 100 ohm electric 100, 300, 500 pF. 9/6.

**New and Boxed VALVES 90-day Guarantee.**

1B5	7/6	6K8	7/6	6AR5	8/6	HARCO	8/6
5A	7/6	6L6G	10/6	6BR1	8/6	12/6	
1T4	6/-	6N7M	6/6	6EB33	8/6	14V2A	6/6
2X2	3/6	6Q6G	6/6	6BC41	8/6	MU14	9/-
384	7/6	68A7	8/6	6BF80	10/6	6P1	8/6
5V4	7/6	6X4	7/6	6CX54	9/6	6PC84	9/6
5L4	7/6	68N7	6/6	6CF80	9/6	6PC80	9/6
5Y3	7/6	6V6G	6/6	6CH42	10/6	6PC82	11/6
5Z4	9/6	6X4	7/6	6CH42	10/6	6PC82	11/6
6A6	5/-	6N5	6/6	6EP39	5/6	PL22	10/6
6BE6	5/6	12A7	8/6	12A1	9/6	PY50	7/6
6BE7	7/6	12A7	8/6	6EP50	5/6	PY81	9/6
6BE6	9/6	12A7	8/6	6EP80	8/6	PY82	7/6
6BW6	9/6	12BF6	8/6	6EP86	12/6	8P61	3/6
6D6	8/6	12K7	6/6	6EP91	5/6	PC41	9/6
6F6	7/6	12K7	6/6	6EP99	5/6	PC142	9/6
6H6	3/6	6X4	7/6	6EL32	6/6	6E142	9/6
6J5	5/6	65Z4	7/6	6EL84	8/6	CU41	9/6
6L6	5/6	80	9/6	6EM1	9/6	UY41	9/6
6KT6	8/6	807	5/6	6E240	7/6	U22	8/6
6KGT	8/6	854	1/6	6E280	7/6	VR105	9/6
6KGT	5/6	EA30	1/6	6E145	1/6	VR150	9/6

**"REGENT" 4 VALVE "96" RANGE VALVES KIT PRICE £6. 6. 0. carr. 4/-**

**PRINTED CIRCUIT BATTERY PORTABLE KIT**  
 Medium and long wave. Powerful 7 x 4in. high Flux Speaker. T.C.C. Printed Circuit and condensers. Components of finest quality clearly identified with assembly instructions. Osamor Ferrite Aerial Coils. Resin covered attache case cabinet. Size 12in. x 8in. x 4in. Batteries used B126 (L5512) and AD35 (L5040), 10/- extra. Instructions 9d. (Free with kit). Mains Unit ready made for above, 39/6. Sold separately.

**TV REPLACEMENT LINE OUTPUT TRANSFORMERS**  
 FROM 45/- ea. Most makes available. S.A.E. with all enquiries.

**LINE BLOCKING TRANSFORMERS,** from 10/6.  
**FRAME BLOCKING TRANSFORMERS,** from 13/6.  
**FRAME OUTPUT TRANSFORMERS,** from 27/6.

**NEW MULLARD TRANSISTORS**  
 Audio OC71 8/6 RF OC44 10/6  
 OC72 7/6 OC45 9/6  
 Sub Miniature Condensers. 0.1mF, 30v. 1 1/3, 1.2, 4.5, 8, 25, 50, 100 mfd. 15 volt. 2/8 each.  
 Weyrad Printed Circuit Components in Stock.  
 Hook 2/- 7 x 4 in. Speaker 35/0 25/-.

**HIGH GAIN TV PRE-AMP KITS**  
**BAND I BBC**  
 Tunable channels 1 to 5. Gain 18dB. EC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PC084 valves if preferred).

**BAND III ITA—Same prices**  
 Tunable channels 8 to 13. Gain 17dB. EC84 valve. (PC084 valves if preferred).

**CRYSTAL MIKE INSERT** by Acos, precision engineered. Size only 1 1/2in. by 1in., 8/6.

**ALUMINIUM CHASSIS.** 18 s.w.g. undrilled. With 4 sides, riveted corners and lattice fixing holes. 2 1/2in. sides, 7 x 4in., 4/8; 9 x 7in., 5/8; 11 x 7in., 6/8; 13 x 9in., 8/8; 14 x 11in., 10/8; 15 x 14in., 12/8; 18 x 16 x 3in., 16/8.

**ALUMINIUM PANELS.** 18 s.w.g. 12in. x 12in., 4/8; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/6.

**JASON F.M. TUNER COIL SET, 29/-.** H.F. coil, aerial coil, Oscillator coil. Two I.F. trans. 10.7 Mcw Ratio Detector and heater choke. Circuit book using four 6AK6. 2/6.

**COMPLETE JASON P.M. KIT, PMT1.** with set of 4 valves, etc., £6.5.0.

**BBC TRANSISTOR RADIO.** Med. and Long Wave. Two transistors and diode. Complete kit, 32/6, phone 7/6 extra or Deaf Aid Earpiece 7/6. Details 6d.

**465 Kcs. SIGNAL GENERATOR.** Total cost 15/-, Use H.P.O. Unit ZA 30038 ready made. POCKET SIZE 2 1/4 x 4 1/4 in. Eight modifications required, full instructions supplied. Battery 7.6 extra 69 v. 1 1/2 v.

**I.F. TRANSFORMERS 7/6 pair**  
 465 Kcs. Slug Tuning Miniature Can. 1 1/2 x 1 1/2 in. High Q and good bandwidth. Data sheet supplied.

**RECORD PLAYER BARGAINS**  
 Postage 2/- each.

**4 Speed Auto-changers, B.S.R., U.A.14** £7.10  
 Collaro Auto-changer £7.10  
 Garrard Model 210, GC8 Head £10.10  
 4 speed Single Players, EMI £6.50  
 Garrard TA Mk.II, GC8 Head £8.00  
 Garrard Model 45P GC8 £8.17.6  
 Garrard Stereo Head, 22 extra  
 Suitable player cabinets (except 4 H.F.) 49/6  
 Amplifier player cabinets (except 4 H.F.) 63/-  
 2-valve amplifier and 4in. speaker 79/6  
 3-valve amplifier and 4in. speaker 95/-

Wired and tested ready for use with above.  
 All apparatus still available from 6/-.

**Volume Controls 80 ohm COAX CABLE**  
 Long spindles. Guaranteed. Semi-air spaced. Insulated 1 year. Midget Losses out 50%.  
 5K ohms to 2 Meg. 40 yds. 17/6 6d. 3/6.  
 No Sw. D.P.Sw. 60 yds. 25/-.  
 3/- Fringe Quality 1/- 3/4.  
 Linear or Log Tracks. Air Spaced.

**COAX PLUGS 1/- LEAD SOCKET 2/-**  
**PANEL SOCKETS 1/- OUTLET BOXES 4/6**  
**BRACED TWIN FEEDER 9d. 50 or 300 ohms**  
**DITTO SCREENED PER YD. 1/6.** 50 ohms only.  
**WIRE-WOUND POTS, 3 WATT.** Pre-set Min. TV Type. All valve 25 ohms to 25 K., 3/- ea. 30 K., 50 K., 4/-; Carbon 30 K. to 2 meg., 3/- ea.  
**WIRE-WOUND 4 WATT 30 K.** Long Spindles. Values 50 ohms to 50 K., 4/6; 100 K., 7/6.  
**CONDENSERS.** New Stock. 0.001 mfd. 7 kV. T.C.C., 5/6; Ditto, 20 kV., 9/6; 0.01 mfd. 7 kV., 9/6; 0.05 mfd. 1/9; 0.1 mfd. 9d.; 0.1, 1/-; 0.1, 1.000 v., 1/9; 0.1 mfd., 2,000 volts, 3/6.  
**CERAMIC CONDS.** 500 v., 0.3 pF to 0.01 mfd., 9d. SILVER MICA CONDENSERS. 10% 5 pF to 500 pF, 1/-; 600 pF to 3,000 pF, 1/8. Close tolerance (± 1 pF) 1.5 pF to 47 pF, 1/6. Ditto 1%, 50 pF to 815 pF, 1/9; 1,000 pF to 3,000 pF, 2/6.

**NEW ELECTROLYTICS, FAMOUS MAKES**  
**TUBULAR TUBULAR CAN TYPES**  
 1.550v. 2/- 50/350v. 5/6 16.450v. 5/-  
 2.450v. 2/8 100/25v. 2/8 32.350v. 4/8  
 4.450v. 2/8 250/25v. 2/8 100.270v. 5/8  
 8.450v. 2/8 500/12v. 3/- 2.500.30v. 4/-  
 8.500v. 2/8 8.450v. 3/6 5,000.6v. 5/-  
 16.450v. 3/8 16/450v. 3/8 32.34.450v. 6/-  
 16.500v. 4/- 16.500v. 5/8 32.32.32/350v. 7/-  
 32.450v. 3/8 16.16.450v. 4/8 50.30.350v. 7/-  
 25.25v. 1/8 16.16.300v. 4/8 125.25v. 11/8  
 50.50v. 2/8 32.32.450v. 4/8 100.2.200.27v. 12/8

**RECTIFIERS** Cooled 250 v., 50 mA, 7/6. 50 mA, 8/6; 200 mA, 21in.; 300 mA, 27/6.  
**COILS** Wearite "P" type, 3/- each. Osamor Midget "Q" type, adj. dust core from 4/-, All ranges.  
**TELETRON, J & Med. T.R.F.** with reaction, 3/6.  
**FERRITE ROD AERIAL, M.W.** 8/8; 10 in. 12/6.  
**T.P. COILS A/H/P, 2 pair, 11/-** CH10K88, 2/6.  
**FERRITE ROD, 8in. x 1in. dia., 2/6.**  
**FULL WAVE BRIDGE SELENIUM RECTIFIER.** 2, 6 or 12 v. 11 amp., 8/8; 2 a., 11/3; 4 a., 17/6.  
**CHARGER TRANSFORMER.** Tapped 1 input 200 v. for charging at 2.6 or 12 v., 14 amps., 15/6. 2 amps., 17/6; 3 amps., 22/6. Circuit included.  
**VALVE and TV TUBE equivalent books, 9/6.**  
**WAGGE SWITCHES, S.P. 2/-, 1-P. 3/6, D.P.D.T. 4/6.**  
**TOGGLE SWITCHES**  
 8 p. 4-way 2 water long spindle 8/6  
 2 p. 2-way, or 3 p. 2-way short spindle 2/6  
 2 p. 6-way, 4 or 1 p. 12-way long spindle 3/6  
 3 p. 4-way, or 1 p. 12-way long spindle 3/6  
**VALVE HOLDERS.** Pax Int. Oct. 4d. EF50, EA60, 6d. B12A, CRT 1/3. Eng. and Amp. 4, 5, 6 and 7 pin. 1/4. MOULDED MAZDA and Int. Oct. 6d. 6d. BG, BSA, BSU, B9A, 9d. B7C with can., 1/6. B9A with can., 1/8. CERAMIC EF50, B7C, B9A. Int. Oct. 1/4. 8/CANS B7G, B9A, 1/4 ea.  
**SPINNER FRET GOLD CLOTH.** 7in., 25in., 5/-; 25in. x 35in., 10/-; Tapes 25in. wide, 10/- ft., 20in. wide, 5/-; Greater lengths, etc. Samples S.A.E.

**RADIO COMPONENT SPECIALISTS**

Fast 1/- unless otherwise stated.

C.O.D. 2/- extra. (Export post Extra.) (Wed. 1 p.m.)

**OUR ONLY ADDRESS**  
 337 WHITEHORSE RD.,  
 WEST CROYDON