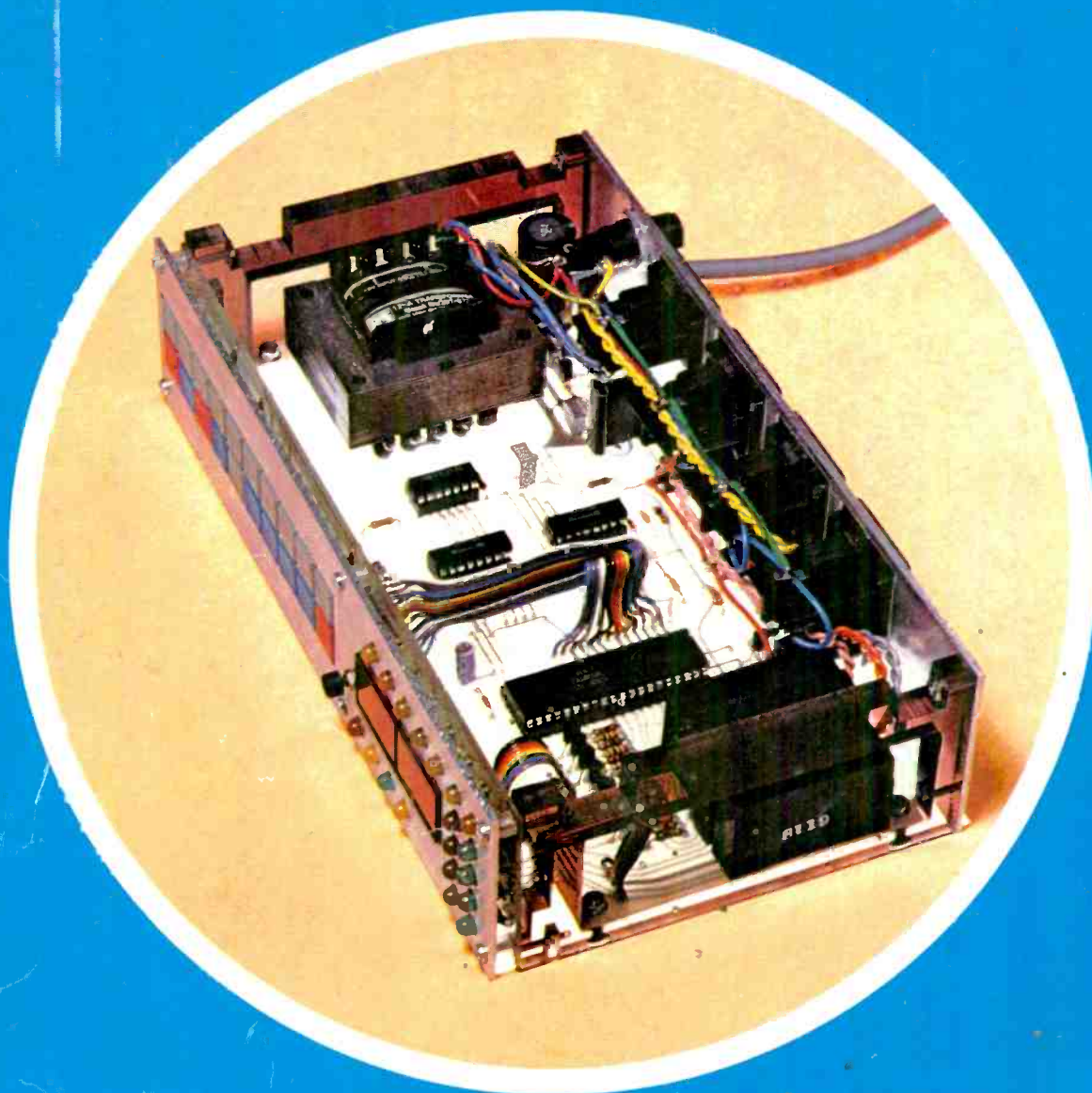


DECEMBER 1981

\$2.80
70p

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS



**MICROCOMPUTER
CLOCK-TIMER**

**GUIDE TO THE PHILIPS
K12 CHASSIS**

**LINEAR OHMMETER
COMB FILTERS**

PHD COMPONENTS
RADIO & TV COMPONENT DISTRIBUTORS
UNIT 7 CENTENARY ESTATE
JEFFRIES RD ENFIELD MIDDX
SHOP NOW OPEN TELEX 261295

ALL COMPONENTS OFFERED SUBJECT TO AVAILABILITY. WE RESERVE THE RIGHT TO SUBSTITUTE REPLACEMENTS SHOULD THE ORIGINAL PART BE OUT OF STOCK OR UNAVAILABLE!
PLEASE ADD 50p per parcel post and packing.

SEMICONDUCTORS

AA113	0.16	AU113	3.00
AA116	0.16	AL103	3.00
AA117	0.16	AY102	3.00
AA119	0.16	BC107	0.20
0A91	0.12	BC108	0.20
0A95	0.12	BC109	0.20
0A202	0.18	BC113	0.15
BA100	0.18	BC114	0.15
BA102	0.10	BC115	0.20
BA130	0.15	BC117	0.20
BA154	0.10	BC118	0.20
BA155	0.20	BC119	0.50
BA164	0.12	BC125	0.50
BAX13	0.16	BC126	0.50
BAX16	0.08	BC136	0.50
BA38	0.16	BC137	0.50
BY206	0.20	BC138	0.40
IN4148	0.04	BC139	0.40
BY126	0.20	BC140	0.40
BY127	0.15	BC142	0.40
BY133	0.22	BC143	0.40
BY164	0.50	BC147	0.15
SKB2/08	1.00	BC148	0.10
BY238	0.15	BC149	0.15
BYX10	0.10	BC153	0.15
IN4001	0.10	BC154	0.15
IN4002	0.10	BC157	0.15
IN4003	0.12	BC158	0.15
IN4004	0.12	BC159	0.15
IN4005	0.12	BC160	0.40
IN4006	0.14	BC161	0.40
IN4007	0.16	BC170	0.15
IN5407	0.33	BC171	0.15
BR100	0.30	BC172	0.20
BR101	0.60	BC177	0.20
BRY39	0.60	BC178	0.20
TIC1160N	1.50	BC179	0.20
BI119	2.00	BC182L	0.20
BI120	2.00	BC183L	0.15
BYX/71/600	0.80	BC184L	0.15
2N444	1.50	BC184LC	0.15
TV106/2	1.50	BC186	0.30
BYX88 2V7	0.10	BC187	0.30
BZY88 3V3	0.10	BC203	0.15
BZY88 3V6	0.10	BC204	0.15
BZY88 3V9	0.10	BC205	0.15
BZY88 4V3	0.10	BC206	0.15
BZY88 4V7	0.10	BC207	0.15
BZY88 5V1	0.10	BC208	0.15
BZY88 5V6	0.10	BC209	0.15
BZY88 6V2	0.10	BC212L	0.15
BZY88 6V8	0.10	BC213L	0.15
BZY88 7V5	0.10	BC214L	0.15
BZY88 8V2	0.10	BC225	0.40
BZY88 9V1	0.10	BC237	0.15
BZY88 10V	0.10	BC238	0.15
BZY88 11V	0.10	BC251A	0.15
BZY88 12V	0.10	BC301	0.40
BZY88 13V	0.10	BC303	0.40
BZY88 15V	0.10	BC307	0.40
BZY88 18V	0.10	BC308	0.15
BZY88 20V	0.10	BC327	0.15
BZY88 22V	0.10	BC328	0.15
BZY88 27V	0.10	BC337	0.15
BZY88 33V	0.10	BC338	0.15
BZX61 7V5	0.20	BC547	0.15
BZX61 8V2	0.20	BC141-10	0.80
BZX61 9V1	0.20	BD115	0.50
BZX61 10V	0.20	BD124	1.80
BZX61 11V	0.20	BD131	0.70
BZX61 12V	0.20	BD132	0.60
BZX61 13V	0.20	BD133	0.70
BZX61 15V	0.20	BD134	0.70
BZX61 16V	0.20	BD144	2.50
BZX61 18V	0.20	BD159	0.80
BZX61 20V	0.20	BD238	0.50
BZX61 22V	0.20	BD380	0.70
BZX61 24V	0.20	BD441	0.70
BZX61 27V	0.20	BD537	0.70
BZX61 30V	0.20	BD538	0.70
BZX61 33V	0.20	BD539	0.70
BZX61 36V	0.20	BD508	0.75
BZX61 39V	0.20	16182	1.20
BZX61 47V	0.20	BD709	1.00
BZX61 72V	0.20	BD710	1.00
AC107	0.35	BD442	0.70
AC127	0.50	BD379	0.50
AC127/01	0.60	BF115	0.60
AC128	0.60	BF118	0.60
AC128/01	0.60	BF152	0.40
AC141	0.50	BF154	0.20
AC141K	0.60	BF157	0.70
AC142	0.40	BF158	0.70
AC142K	0.60	BF160	0.60
AC176	0.60	BF163	0.60
AC176/01	0.60	BF167	0.60
AC186	0.40	BF173	0.50
AC187	0.40	BF177	0.50
AC187K	0.60	BF179	0.50
AC188	0.40	BF180	0.50
AC188K	0.60	BF181	0.50
AD140	1.50	BF182	0.60
AD142	1.50	BF183	0.50
AD143	1.50	BF184	0.50
AD145	1.50	BF185	0.50
AD149	1.00	BF194	0.20
AD161/2	1.50	BF195	0.20
AD162	0.70	BF196	0.20
AD262	1.50	BF197	0.20
AF121	0.80	BF198	0.15
AF124	0.80	BF199	0.15
AF125	0.60	BF200	0.45
AF126	0.60	BF224	0.15
AF127	0.60	BF240	0.15
AF139	0.60	BF241	0.20
AF239	1.00	BF256LC	0.50
AL102	3.00	BF257	0.50
AU107	3.00	BF258	0.50
AU110	3.00	BF271	0.60

BF273	0.20
BF274	0.25
BF336	0.50
BF337	0.50
BF338	0.50
BF355	0.50
BF458	1.00
BF459	1.00
BF473	0.50
BF429	0.50
BFX84	0.50
BFX88	0.50
BFX89	0.50
BFY50	0.50
BFY51	0.50
BFY52	0.50
BFY90	1.20
BF381	0.30
BF389	0.30
BF259	0.25
BFX89	0.25
BFX88	2.50
BFX87	1.60
BFX86	2.80
BFX85	1.00
BFX84	2.00
BFX83	2.50
BFX82	1.70
BFX81	2.50
BFX80	2.50
BFX79	2.50
BFX1	2.50

TBA396Q	2.00
TDA440	2.50
SN76001N	1.50
TBA520	2.00
TBA120S	1.00
TBA396	2.00
TCA2705Q	2.00
TDA2030	8.00
TDA2140	6.00
TDA2150	6.00
TDA2160	6.00
TDA1230	3.00
TDA3089	2.00
TDA1054M	2.00
MC1349P	1.50
SAA66T	0.60
SAS560S	2.00
SAS57CS	2.00
SN7400N	0.40
SN7413N	0.90
SN74122N	1.00
SN74141N	1.00
TBA395	1.80
TBA395Q	1.80
TBA950	4.00
TCA800	4.00
TCA800C	4.00
TDA1180	3.00
TDA1190	3.30
TDA2002H	3.60
TDA2590Q	5.00
TDA2600	5.00
TDA2640	1.20
TDA3950	3.30
TAA621 AX1	3.30
TBA625X5	2.00
TCA830S	2.00
TDA2020/A2	5.00
TDA2020P	5.00
TDA2030V	3.60
TDA2010/BD2	4.50
TDA2002V	5.00
TCA940E	3.00

We can often supply equivalents to transistors & I.C.s not listed. Free list on request with any order.

VALVES

DY86/37	1.30
DY902	1.80
ECC82	1.40
ECC84	1.20
ECH83	0.60
ECH84	0.80
ECL80	0.50
ECL82	1.80
ECL86	1.10
EF80	1.10
EF95	1.50
EF183	1.70
EF184	1.60
EL34	3.00
ELB4	2.00
GY501	3.00
PC97	1.50
PC900	1.50
PCF80	1.74
PCF802	1.60
PCF805	1.10
PCL82	1.70
PCL84	1.80
PCL85/805	1.90
PCL86	1.90
PD500/510	5.00
PFL200	2.60
PL36	2.60
PL81	4.00
PL504	1.50
PL508	2.50
PL519	4.00
PL519	5.00
PL802	3.00
PY88	1.70
PY500A	2.80
PY800/801	1.70
UCL82	1.70
30FL21	1.40
PCF805	1.20
PCF808	1.20
PL519 PY500A	5.00

VALVES NOT SHOWN HERE MAY BE IN STOCK. PLEASE WRITE FOR QUOTE.

DIRECT REPLACEMENT PARTS

Decca 30 Series Lopt	8.00
173 Trimer (Repl Eic 1043/05)	8.00
4.443MHz Crystals	2.00
Cut Out TCE 3500	2.50
Cut Out GEC	2.50
Cut Out TCE 8500	2.00
TV18 Rectifier Stick	2.00
TV20 Rectifier Stick	2.00
VA 1104 Thermistor	0.80
Transductor TCE 3000	1.50
VEG Tuner (Repl Eic 1043/06)	9.00
Philips G8 Lopt	12.00
Aeriel Isolator Kit	1.60
Philips G8 Lopt	12.00
PYE 691/697 Lopt	11.00
Bush A 774 Lopt	18.00
Bush 0823 Lopt	5.00
Pye 731 IF Gain	10.00
AB23 Bush Power Panel	20.00
PL 802T Transistorised	4.00

BAHCO TOOLS Come and see the full range at our shop or send for full catalogue free, on request, with any order

EHT MULTIPLIERS

TCE950 Doubler	2.00
TCE950/1400 Tripler	5.04
TCE1400 (Piped System Only)	4.56
TCE1500 Doubler	4.16
TCE1500 Tripler	4.64
TCE1600 1/2 Wave	3.95
DECCA CS 1730/1830 Doubler	4.23
DECCA CS 1910/2213 Tripler	6.67
DECCA 30 Series Tripler	6.01
DECCA 80 Series Tripler	6.43
DECCA 100 Series Tripler	6.68
GEC Hybrid 2028 Tripler	6.43
GEC 2110 Tripler Pre JAN77	7.21
GEC 2110 Tripler Post JAN77	6.43
ITT CVC 5/8/9 Tripler	6.51
ITT CVC 20/25/30	6.45
Philips 520 Tripler	6.51
Philips 550 Tripler	6.42
Philips G9 Tripler	6.63
PYE 691/693/697 Tripler	6.68
RRI 823 Tripler	5.68
RRI 2179/823	6.68
TCE 3000/3500 Tripler	5.51
TCE 4000 Tripler	8.00
TCE 8000 Doubler	3.53
TCE 8500 Tripler	5.60
TCE 9000 Tripler	7.28
TVK 76/13 Continental Sets	5.50
TVK 52 ITT Replacement	6.68
Korting 90% Tripler	6.50
Autovox Tripler	6.50
Rediffusion MK 1 Tripler	6.00
RRI TV 25 Quadrupler	4.00
RRI T20	7.04

MULTISECTION CAPACITORS

DECCA 400 400/350	3.72
DECCA 80/100 400/350	4.00
800/250	4.00
GEC 200 200 150 50/350	3.00
GEC 100 2000/35	1.10
GEC Philips G8 600/250	2.10
GEC Philips G8 600/300	2.50
ITT KB 200 200 75 25/350	3.00
ITT CVC 20 200 400	2.20
Philips G11 470 250	1.90
PYE 691 200 300 350	2.80
PYE 1000 1000/40	0.90
PYE 731 800/250	2.50
RRI 2500-2500/40	1.30
RRI 600-300	2.50
RRI 300 - 300/300	2.50
TCE 950 100 300 100 16	1.00
TCE 1400 150 100 100	3.70
100 150	



TELEVISION

December
1981

Vol. 32, No. 2
Issue 374

COPYRIGHT

©IPC Magazines Limited, 1981. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

SUBSCRIPTIONS

An annual subscription costs £10 in the UK, £11 overseas (\$24.20 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£4.40) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 85p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").


this month

- 65 **Leader**
66 **Teletopics**
News, comment and developments.
- 71 **Letter from America: Comb Filters** *by Jim Edwards*
Comb filters – the delay-line type of filter, but this time in solid-state form – are being used in the latest US colour chassis to separate the luminance and chrominance signals and provide improved definition.
- 72 **Desolate Dan** *by Les Lawry-Johns*
Strange customers with strange sets. This time a Bush set that gave a cosy picture, a Teleton that wouldn't tune, and Mr. Bore-Crashing's EW modulator trouble.
- 74 **Microcomputer Clock-Timer, Part 1** *by Luke Theodossiou*
Originally intended for up-dating early VCRs, this versatile design can be used for many purposes in the home and workshop.
- 76 **Fidelity's Monochrome Portables** *by S. George*
Fidelity entered the TV market late last year with a state-of-the-art monochrome portable. An account of the circuitry and in particular the interesting remote control system used on some versions.
- 77 **Guide to the Philips K12 Chassis** *by Derek Snelling*
The K12 is of continental origin and has some unusual circuitry and features, including a hi-fi sound system. A guide to servicing problems.
- 80 **VCR Servicing, Part 4** *by Mike Phelan*
A detailed look at some of the luminance playback signal processing in the basic JVC machine.
- 82 **Readers' PCB Service**
83 **Linear Ohmmeter** *by William E. Harrison*
A neat design using operational amplifiers to obtain linear resistance readings. Ranges from 0-10 Ω to 0-20MΩ.
- 84 **TV Receiver Design: The Decca 120 Series, Part 2** *by Ray Wilkinson*
The decoder and video circuits, and the method of coupling the tuner to the SAWF.
- 87 **Next Month in Television**
88 **Servicing Luxor 110° Hybrid CTVs, Part 2** *by Mike Phelan*
The luminance and colour-difference amplifiers, the timebases and convergence.
- 90 **Service Notebook** *by George Wilding*
TV faults and how to tackle them.
- 91 **Reusing Heads** *by Steve Beeching, T.Eng. (C.E.I.)*
A warning, following our article on the N1700 head drum last month, on the problems of head replacement.
- 92 **Long-distance Television** *by Roger Bunney*
European satellite TV transmissions from a redundant OTS transponder are due to start at any time. Plus DX conditions and reception etc.
- 95 **VCR Clinic** *by Steve Beeching, T.Eng. (C.E.I.)*
Many of the faults this time relate to defective microprocessor i.c.s – a new source of concern...
- 97 **Letters**
98 **Service Bureau**
100 **Test Case 228**

OUR NEXT ISSUE DATED JANUARY WILL
BE PUBLISHED ON DECEMBER 23

MANOR SUPPLIES

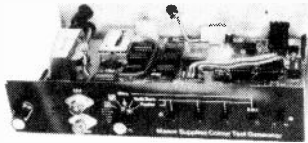NEW MKV CHEQUERBOARD & PAL COLOUR TEST GENERATOR FOR TV & VCR.



- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.


PRICE OF KIT £80.50.
DE LUXE CASE (10" x 6 1/4" x 2 1/4") £8.50
Post/Packing £2.00.

ALL ABOVE PRICE INCLUDE VAT 15%.

PAL COLOUR BAR GENERATOR (Mk 4)



4TH SUCCESSFUL YEAR

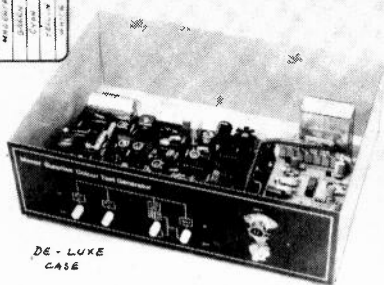

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £40.25 P&P £1.20. DE-LUXE CASE £5.95.
ALUMINIUM CASE £3.30, P&P £1.20, BATT HOLDERS £1.70 P&P 85p, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.55 (Combined P&P £1.80).

MK 4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.80 P & P.
 MK 4 DE LUXE (MAINS) BUILT & TESTED £80.50 + £1.80 P & P.
 VHF MODULATOR (CHI to 4) FOR OVERSEAS £4.60.
 EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

(ALL PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETXT ADAPTOR KITS

Remote control of stations & teletext.

MK1 (Texas XMII) £170.20.

Further details on request P/P £2.80.

TELEVISION PROJECTS & SERVICE SPARES

"TELEVISION" NEW COLOUR PORTABLE PROJECT (Parts available)
 SWITCH MODE POWER SUPPLY KIT £26.00 p.p. £1.60. SIG BOARD KIT (Incl. ALT. SAW IF) £70.00 p.p. £1.60. TIME BASE £44.80 p.p. £1.60. CRT BASE £2.60 p.p. 60p.
 (PHONE, CALL, SEND FOR LIST). FULL TECHNICAL ADVICE & PANEL TEST SERVICE FOR OUR CUSTOMERS.
 "TELEVISION" TV PATTERN GEN. PARTS AVAILABLE.
 "TELEVISION" MONITOR PARTS AVAILABLE.
 "TELEVISION" MONO PORTABLE RECEIVER PARTS AVAILABLE. WORKING MODELS & PANEL TEST SERVICE.
 "TELEVISION" COLOUR RECEIVER (LARGE SCREEN) PROJECT ALL PARTS AVAILABLE. SEND OR PHONE FOR LIST. WORKING MODEL ON SHOW WITH TELETXT. (PANEL TEST SERVICE) NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.80 p.p. £1.20 (SUITABLE FOR USE WITH TELEVISION SIGNAL BOARDS).
 SPECIAL OFFER TEXAS XMII TELETXT MODULE NEW & TESTED, LIMITED QUANTITY AT HALF PRICE £69.00 p.p. £1.60. TELETXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE £7.80 p.p. £1.20. XMII INTERFACE PANEL (THORN) £2.10 p.p. 75p. CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £12.65 p.p. 60p. (ALUM CASE £2.60 DE LUXE CASE £5.50 p.p. £1.00.) ADDITIONAL GREY SCALE KIT £3.35 p.p. 45p.
 UHF SIGNAL STRENGTH METER KIT £20.00 (VHF VERSION £21.60). ALUM CASE £2.00 DE LUXE CASE £5.95 p.p. £1.80.
 CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO £28.00 p.p. £2.00.
 BUSH Z718 BC6100 SERIES IF PANEL £5.75 p.p. 90p.
 BUSH A816 IF PANEL (SURPLUS) £1.90 p.p. 90p.
 BUSH 161 TIMEBASE PANEL A634 £3.25 p.p. £1.40.
 DECCA "Bradford" IF T.B. POWER ex rental £5.75 each p.p. £1.40.
 DECCA 80, SERIES, IF FRAME TB £7.90 each p.p. £1.40.
 GEC SERIES I MONO PANELS £2.10 p.p. £1.30.
 GEC 2110 Decoder, RGB panels (ex rental) £5.75 each p.p. £1.00.
 GEC 2010 SERIES TIMEBASE PANEL £1.15 p.p. £1.00.
 GEC 2040 (TYPE) CDA PANEL £2.88 p.p. £1.25.
 PYE 713/715 Convergence £5.75 each p.p. £1.40.
 PYE 697 Line T.B. P.C.B. type salvaged £4.80 p.p. £1.50.
 THORN 3000 LINE TB PCB £5.75 each p.p. 85p.
 THORN 3000 VID, IF, DEC. Ex Rental £5.75 each p.p. £1.30.
 THORN 8500 Series channel selector & front control unit £4.37 p.p. £1.80.
 THORN 8000/8500 IF/DECODER PANELS salvaged £5.52 p.p. £1.60.
 THORN 8000/8500 FRAME T.B. PANELS salvaged £5.52 p.p. £1.40.
 THORN 8000/8500 POWER/SALV. SPARES £2.88 p.p. 60p.
 THORN 9000 LINE T.B. (incl. Lopt etc.), Salv., spares £8.62 p.p. £1.60.
 THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET £19.32 p.p. £1.84.
 THORN 9000 IF/DECODER PANELS Salvaged £8.90 p.p. £1.60.
 PHILIPS 210, 300 Series Frame T.B. Panels £1.15 p.p. 80p.
 PHILIPS G8/G9 IF/DECODER Panels for small spares £4.80 p.p. £1.30.
 G8 IF Panels for small spares £1.75 p.p. 95p.
 G8 Decoder panels salvaged £4.25. Decoder panels for spares £2.00 p.p. £1.35.
 VARICAP, U321, U322, ELC 1043/06 £7.82, ELC 1043/05 £6.35 p.p. 60p; G.I. type (equiv. 1043/05) £4.00 p.p. 60p. Control units, 3PSN £1.40, 4PSN £1.75, 5PSN £2.00, 6PSN £2.88 p.p. 60p.
 BUSH "Touch Tune" and Varicap Control Unit £4.40 p.p. 95p.
 VARICAP UHF-VHF ELC 2000S £9.80. BUSH TYPE £8.60 p.p. 85p.
 VARICAP VHF MULLARD ELC 1042 £7.95 p.p. 60p.
 UHF/625 Tuners, many different types in stock. UHF tuners transisted. incl. s/m drive. Mullard 4 position push button £4.80 p.p. £1.30.
 TRANSISTORISED 625 IF for T.V., sound, tested. £7.82 p.p. 95p.
 MULLARD EP9000 Audio Unit incl. LP1162 Module £4.38 p.p. 85p.
 LINE OUTPUT TRANSFORMERS. New guar. p.p. £1.25.

BUSH 145 to 186SS series £9.20
 BUSH, MURPHY A816 series £9.80
 DECCA 20/24, 1700, 2000, 2401. £8.80
 FERG., HMV, MARCONI, ULTRA 850 to 1580 £6.80
 THORN 169, 1691 £10.15
 GEC 2000 to 2038 series £7.80
 GEC series 1 & 2 £9.20
 INDESIT 20/24ECB £8.80
 ITT/KB VC 1 200, 300 £8.80
 MURPHY 1910 to 2417 series £8.80
 PHILIPS 19TG 170, 210, 300 £8.80
 PYE, INVICTA, EKO, FERR. 368, 169, 569, 769 series £8.80

COLOUR LOPTS p.p. £1.30 (BOBBINS 80p)

R.B.M. A823 £5.60
 R.B.M. Z179 £6.70
 R.B.M. T20, T22 Bobbin £6.44
 DECCA Bradford (state Model No.) £10.15
 DECCA 80, 100 £9.50
 GEC 2028 £7.82
 GEC 2040 £11.30
 GEC 2110 Series £12.20
 ITT CVC 5 to 9 £10.15
 ITT CVC 30 Series £10.15
 PYE 691-697 £14.80
 PYE 713-715 £7.85
 PYE 731 to 741 £7.85
 PHILIPS G8, G9 £10.15
 PHILIPS 570 £7.85
 THORN 3000/3500 SCAN, EHT £7.85
 THORN 8000/8500 £14.80
 THORN 9000 £10.15

SPECIAL OFFER

GEC 2114J/FINELINE £5.50
 PYE 40, 67 £5.50
 THORN 1590/1591 £5.50
 KB VC ELEVEN (003) £3.25

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.T.S.

TRANSDUCTORS Suitable for G8, A823, Bradford etc. £1.72 p.p. 60p.
 THORN 950 3 Stick Tray £1.15 p.p. 55p. Most others available.
 THORN 3000/3500, 8000, 8500, MAINS TRANSF. £10.15 p.p. £1.80
 6-3V CRT Boost Transformers £5.80, Auto Type £3.20, p.p. £1.20.

CALLERS WELCOME AT SHOP PREMISES Telephone 01-794 8751/7346
 THOUSANDS OF ADDITIONAL ITEMS AVAILABLE, ENQUIRIES INVITED
 LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
 W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

ALL PRICES INCLUDE VAT AT 15%



BT

There's never been a better time to buy from Briarwood TV.



Any 5 British Makes
GOOD WORKING
Including: Thorn 3500 + 8500 — PYE Solid State G8 — ITT/KB — GEC 2100 ETC.
£55.00 EACH + VAT



Any 5 Foreign Makes
GOOD WORKING
Including: Hitachi — Grundig — Luxors Saba — ASA — Mitsubishi — Etc.
£55.00 EACH + VAT

Colour TVs with tested tubes... Guaranteed 100% complete!

	In 10's	In 20's	Good Working in 10's
PYE 691	£18.00 each	£15.00	£33.00
PYE 697	£21.00 each	£18.00	£38.00
GEC 2040	£18.00 each	£15.00	£33.00
BUSH 184	£23.00 each	£20.00	£38.00
THORN 3000 19"	£28.00 each	£25.00	£43.00
THORN 3500 26"	£28.50 each	£25.00	£43.00
DECCA BFD - 30's	£28.00 each	£25.00	£43.00
KORTING	£25.00 each	£22.00	£45.00
TELPRO	£28.00 each	£25.00	£43.00

Please note — 15% VAT on all above prices.

100's OF SINGLE/STANDARD MONO
- 100% COMPLETE
I.E. THORN 1300 - PYE 169 - PHILIPS 300 -
GEC FINELINE - BUSH/MURPHY -
INDESIT - ITT/KB ETC.
£7.00 each + VAT

100's OF COLOUR
TV'S 100% COMPLETE
AS THEY ARRIVE — IN
BATCHES OF TEN
BRIARWOOD SPECIAL CLEARANCE
PRICE **£15.00**
per set! + VAT

TUNE IN TO THESE BRIARWOOD BARGAINS
ALL SETS IN BATCHES OF FIVE
— ALL GOOD WORKING

5 · 25" 3000 THORN OR
5 · 26" PYE WITH DOORS!
@ £40.00 each + VAT

5 · 25" BUSH WITH DOORS
OR 5 · 26" GEC 2040
@ £40.00 each + VAT

5 · 26" THORN WITH DOORS
OR 5 · 26" KORTING WITH DOORS
@ £40.00 each + VAT



**RING BRADFORD (0274) 306018 FOR DETAILS OF
SPECIAL PRICES FOR SINGLE SETS!**

BRIARWOOD TELEVISION LIMITED



BRIARWOOD

QUALITY SELECTED EX EQUIPMENT SPARES

MISC S/Output Trans. £1 + VAT + P&P F/Output Trans. £1.25 + BAT + £1 P&P Scancoils £1.50 + VAT + £1 PIP. Other spares available, please write or phone for details.	MONO TUNERS 6 button integrated all at £4.00 U.H.F. P/Button D/S £3.50. U.H.F. P/Button S/S £4.00. Rotary £3.00 + £1 P&P	MONO TUBES (tested) 19" Rimguard £3.00 23" Rimguard £4.00 20" Rimguard £5.00 24" Rimguard £6.00 + £5.00 P & P	MONO LOPTS All D/Standard Lopts at £4.00 + £1 P&P. All S/Standard at £4.00 + £1 P&P.	MONO PANELS i.e. Philips, Bush, etc. £3.50 + £1 P&P. Quotations for complete S/hand chassis if required. (Diff. prices)
---	---	---	---	--

PLEASE ADD 15% V.A.T. TO ALL ITEMS AND OVERSEAS AT COST. CASH WITH ALL ORDERS.

VALVES (MONO & COLOUR)

PCL82 0.10	30C1 0.10	PCC189 0.10	EF183 0.10	PL504 0.25	ECL80 0.10
PCL83 0.25	30C17 0.10	30C15 0.10	EF184 0.10	6/30L2 0.10	PL509 1.00
PCL84 0.10	PCF802 0.10	30C18 0.25	6BW7 0.10	30PL1 0.25	PY500 1.00
PCL85 0.10	PCF805 0.25	PC97 0.20	EH90 0.10	30PL13/4 0.10	GY501 1.00
PCL86 0.10	PCF806 0.10	PC900 0.10	DY802 0.10	30FL1/2 0.25	PL508 0.50
PFL200 0.10	PCF808 0.25	EF80 0.10	PY800/1 0.10	ECC82 0.10	PCF200 0.50
PCF801 0.10	PCF80 0.10	EF85 0.10	PL36 0.25	ECC81 0.10	EY51 0.15

Please note there is 50p Postage and Packing per order.

BRIARWOOD TV LTD (Export Division)

TEL: 0274-306018 FOR PRICES & FREIGHT DETAILS

COLOUR & MONO TV'S ALWAYS AVAILABLE FOR WORLDWIDE USE

Briarwood T.V. Ltd., have international experience in quality used T.V. supply. Fully tested & converted where necessary – by our experienced Export Division.

WE DO NOT SELL RUBBISH AT BRIARWOOD TV

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	12.00	—	6.00	6.00	12.00	—
GEC Hybrid	6.00	6.50	9.00	—	5.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	5.00	—	—	6.00
Thorn 3000	6.00	6.00	6.00	—	5.00	15.00	15.00	6.00
Pye 691/693	6.00	6.00	8.00	—	5.00	—	15.00	5.00
Thorn 3500	6.00	6.00	6.00	6.50	12.00	15.00	15.00	6.00

Korting and other foreign panels available on request.

Postage & Packing £1.25

COLOUR TUBES

17"	£15.00
18"	£15.00
19"	£15.00
19" A49/192	£18.00
20"	£18.00
22"	£20.00
25"	£15.00
26"	£22.00

Plus P&P £6.00
New rebuilt tubes available on request.

COLOUR TUNERS

Bush	£5.00
GEC	£5.00
Philips G6 S/S	£5.00
Pye 691	£5.00
Thorn 3000	£5.00

Some new tuners in stock, can supply on request. Many Foreign Tuners also available on request. Plus P&P £1.

COLOUR LOPTS

Most Lopts available from £5.00. Both British & Foreign makers. Please ring or write. P&P per Lopt £1.00

MISC.

S/Output transformer from £1.50.
F/Output from £1.25.
Scancoils from £5.00.
P&P £1.00
Other spares available on request.


THORN 1500 TUNERS

NEW SPECIAL OFFER AT £8.00

Postage & Packing £1.00

NEW PRODUCTS!

£2.50 each
£1.00 p&p

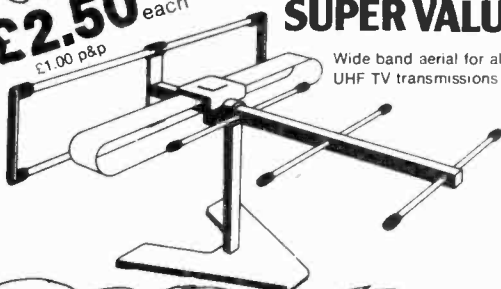


Wide band aerial for all UHF TV transmissions

SUPER VALUE - SUPER QUALITY

£5.95 each
£1.75 p&p

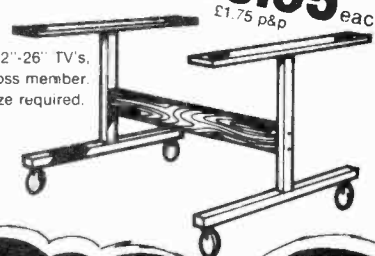Fits 22"-26" TV's, wood finished cross member. State size required.



TV scores with quality

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED

NEW SPARE SELECTION

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £
AC107	0.24	AF181	1.00	BC179	0.12	BD137	0.30	BF218	0.12	OC36	0.90	2N3053	0.21
AC113	0.22	AF186	0.90	BC182L	0.09	BD138	0.31	BF219	0.12	OC38	0.90	2N3054	0.60
AC115	0.23	AF239	0.46	BC183L	0.09	BD139	0.40	BF220	0.12	OC42	0.45	2N3055	0.60
AC117	0.30	AU113	1.40	BC183LA	0.10	BD140	0.37	BF221	0.21	OC44	0.60	2N3442	1.00
AC125	0.23	BA130	0.08	BC183LB	0.10	BD144	1.39	BF222	0.12	OC45	0.50	2N3702	0.15
AC126	0.23	BA145	0.14	BC184L	0.09	BD145	0.50	BF224	0.18	OC46	0.39	2N3703	0.12
AC127	0.22	BA148	0.21	BC186	0.21	BD177	0.50	BF256	0.37	OC70	0.39	2N3704	0.18
AC128	0.22	BA155	0.08	BC187	0.21	BD178	0.50	BF258	0.30	OC71	0.39	2N3705	0.18
AC131	0.13	BAX13	0.05	BC209	0.11	BD203	0.40	BF259	0.30	OC72	0.39	2N3706	0.14
AC141	0.24	BAX16	0.08	BC212	0.09	BD204	0.70	BF260	0.25	OC74	0.39	2N3707	0.14
AC142	0.24	BC107	0.11	BC212L	0.09	BD222	0.73	BF262	0.28	OC75	0.39	2N3708	0.14
AC141K	0.31	BC108	0.11	BC213L	0.09	BD233	0.36	BF263	0.25	OC76	0.39	2N3772	2.00
AC142K	0.31	BC109	0.11	BC214L	0.09	BD234	0.34	BF271	0.27	OC77	0.50	2N3773	2.50
AC151	0.21	BC113	0.11	BC237	0.09	BD237	0.44	BF272	0.27	OC78	0.23	2N3619	0.30
AC165	0.21	BC114	0.11	BC238	0.09	BD238	0.44	BF273	0.16	OC81	0.26		
AC166	0.21	BC115	0.11	BC240	0.31	BDX22	0.73	BF336	0.30	OC810	0.14		
AC168	0.22	BC116	0.11	BC249	0.35	BDX32	1.98	BF337	0.29	OC82	0.26		
AC176	0.22	BC117	0.12	BC251	0.22	BDY18	0.80	BF338	0.29	OC820	0.20		
AC176K	0.28	BC119	0.24	BC257	0.20	BDY60	0.80	BF479	—	OC83	0.30		
AC178	0.23	BC125	0.15	BC262	0.18	BF115	0.30	BFT	0.27	OC84	0.30		
AC186	0.26	BC126	0.15	BC263B	0.20	BF121	0.29	BFT	0.27	OC85	0.28		
AC187	0.23	BC136	0.15	BC267	0.19	BF154	0.12	BFX84	0.27	OC123	0.25		
AC188	0.23	BC137	0.17	BC281	0.24	BF158	0.19	BFX85	0.27	OC169	1.20		
AC187K	0.30	BC137	0.23	BC300	0.27	BF159	0.24	BFX	0.30	OC170	1.20		
AC188K	0.30	BC139	0.23	BC301	0.27	BF160	0.23	BFY37	0.22	OC171	0.92		
AD130	0.58	BC140	0.24	BC302	0.30	BF163	0.30	BFY50	0.21	OA91	0.07		
AD140	0.68	BC141	0.27	BC303	0.27	BF164	0.30	BFY51	0.21	BRC4443	0.65		
AD142	0.80	BC142	0.27	BC307	0.11	BF167	0.30	BFY52	0.21	R2008B	1.50		
AD143	0.70	BC143	0.27	BC307A	0.11	BF173	0.21	BFY53	0.27	R2009	1.30		
AD145	0.70	BC147	0.10	BC308A	0.12	BF177	0.26	BFY55	0.33	R2010B	1.50		
AD149	0.64	BC148	0.10	BC309	0.14	BF178	0.24	BFX	—	R2265	1.50		
AD161	0.42	BC149	0.10	BC337	0.12	BF179	0.28	BHA0002	1.90	R2305	0.38		
AD162	0.42	BC153	0.12	BC338	0.15	BF180	0.30	BSX20	0.23	R2305	0.38		
AD161)	—	BC154	0.12	BC487	0.20	BF181	0.34	BSX76	0.23	BD222	0.37		
AD162)	1.00	BC157	0.12	BC547	0.10	BF182	0.30	BSY84	0.36	R2540	2.50		
AF106	0.42	BC158	0.12	BC548	0.11	BF183	0.29	BU105	1.00	S2802	—		
AF114	0.37	BC159	0.12	BC549	0.11	BF184	0.27	BU105 02	1.50	SCR957	0.55		
AF118	0.45	BC160	0.26	BC557	0.12	BF185	0.29	BU105 04	2.00	TIP31A	0.38		
AF121	0.37	BC161	0.26	BCX33	0.10	BF186	0.32	BU126	1.40	TIP32A	0.36		
AF125	0.30	BC167	0.11	BD112	0.39	BF192	—	BU205	1.20	TIP3055	0.53		
AF126	0.30	BC168	0.11	BD113	0.65	BF194	0.15	BU206	1.63	TIP31B	0.39		
AF127	0.30	BC169	0.11	BD115	0.32	BF195	0.13	BU208	1.60	TIS90	0.23		
AF139	0.40	BC171	0.10	BD116	0.47	BF196	0.13	CO22	1.10	TIS91	0.25		
AF150	0.27	BC171A	0.10	BD124	1.30	BF197	0.13	OC23	1.30	TV106	1.09		
AF151	0.30	BC172	0.10	BD131	0.36	BF198	0.12	OC24	1.30	MJE340	0.50		
AF170	0.92	BC173	0.12	BD132	0.36	BF199	0.14	OC25	1.00	MJE520	0.45		
AF172	1.00	BC177	0.12	BD133	0.37	BF200	0.28	OC26	1.00	2N2219	0.40		
AF178	1.00	BC178	0.12	BD135	0.30	BF216	0.12	OC28	1.30	2N2646	0.40		
AF180	1.00	BC178A	0.12	BD136	0.30	BF217	0.12	OC35	1.00	2N2926	0.15		

E.H.T. Trays Colour

TYPE	PRICE £
Pye 691 693	4.50
Pye 715/731/735	5.50
Pye 737	5.40
Decca (Large Screen)	—
CS2030/2232/2630/2632/2230/2631	5.00
Decca 80	5.30
Decca 100	5.30
Philips G8	—
520/540	5.30
Philips G9	5.50
Philips 550	5.30
GEC C2110	5.50
GEC Hybrid	—
CTV	5.10
Thorn 3000	—
3500	5.00
ECC82	0.60
EF80	0.55
EF183	0.70
EF184	0.70
EH90	0.75
PC86	0.85
PCC89	0.65
PCC189	0.80
ITB KB CVC	5.10
ITT KB CVC	—
20/25	—
30/32	5.50
Bush CTB25	—
MK3	—
Quadrupler	8.00
Bush X179	4.50
RRI (RBM)	—
A823	5.00
Bang & Olufsen	—
4/5000 Grundig	—
5010/5011/5012/6011/6012/7200/2052/2210/2252R	—
Tandberg (radionette)	—
Autovox	6.60
Grundig	—
3000/3010	—
Saba 2705/3715	—
Telefunken	—
709/710/717/2000	6.80
Korting	6.80

VALVES

DY87	0.60
DY302	0.64
ECC82	0.60
EF80	0.55
EF183	0.70
EF184	0.70
EH90	0.75
PC86	0.85
PCC89	0.65
PCC189	0.80
ITB KB CVC	5.10
ITT KB CVC	—
20/25	—
30/32	5.50
Bush CTB25	—
MK3	—
Quadrupler	8.00
Bush X179	4.50
RRI (RBM)	—
A823	5.00
Bang & Olufsen	—
4/5000 Grundig	—
5010/5011/5012/6011/6012/7200/2052/2210/2252R	—
Tandberg (radionette)	—
Autovox	6.60
Grundig	—
3000/3010	—
Saba 2705/3715	—
Telefunken	—
709/710/717/2000	6.80
Korting	6.80

All transistors, IC's offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc. Please add 15% VAT to all items and overseas at cost. P & P UK, 50p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

MAIL ORDER TV BARGAINS

PYE 691	22" @ £55.00
PYE 691	26" @ £55.00
PYE 697	22" @ £65.00
PYE 697	26" @ £65.00
BUSH 184	19" @ £70.00
BUSH 184	22" @ £70.00
BUSH 184	26" @ £70.00
GEC 2040	19" @ £55.00
GEC2040	22" @ £55.00
GEC 2040	25" @ £55.00
GEC 2040	26" @ £65.00
KORTING	22" @ £70.00
KORTING	26" @ £80.00
THORN 3000	19" @ £70.00
THORN 3000	25" @ £60.00
Good working mono's Pye, GEC, Bush etc.	
20" & 24" S/S	£20.00
20" & 24" D/S	£18.00
19" & 23" D/S P/Button	£15.00
19" & 23" D/S Rotary	£12.00

Cheques, P.O. or Cash with orders Please. Please note there is 15% VAT on all the above prices. Plus £10.00 p & p for colour TV. £5.00 for mono. ENGLAND, WALES and SCOTLAND Inland N & S IRELAND £15.00 for colour. £7.00 for mono.

TYPE PRICE £

IC's	TYPE	PRICE £
BTT6018	1.00	
CA3605	1.20	
MC7/c		
MC14016	0.50	
SN76005N	1.40	
SN76023N	1.20	
SN76110N	1.00	
SN76226DN	1.50	
SN76227N	1.20	
SN76532N	1.30	
SN76550N	0.30	
SN76666N	0.70	
TAA570	1.38	
TBA120AS	1.00	
TBA120S	0.75	
TBA120SQ	0.75	
TBA395	2.20	
TBA341	0.97	
TBA520	1.40	
TBA520Q	1.10	
TBA530Q	1.10	
TBA540	1.30	
TBA540Q	1.45	

TBA550Q	1.40	BAX13	0.08
TBA560C	1.50	BAX16	0.10
TBA560CQ	1.50	BY126	0.10
TBA570	1.00	BY127	0.10
TBA570Q	1.00	BY164	0.40
TBA800	1.00	BY179	0.57
TBA810	1.50	BY226	—
TBA920	2.00	BY227	0.12
TBA920Q	1.50	BYF206	0.14
TBA990Q	1.50	1N4001	0.04
TCA270SQ	1.45	1N4002	0.05
TCA270SA	1.45	1N4003	0.06
TCA270Q	—	1N4004	0.07
TCA1327B	1.00	1N4005	0.07
TCA800	2.00	1N4006	0.08
TDA1010	—	1N4007	0.08
TDA1327B	1.00	1N4148	0.05
SBA750	1.75	1N4751	0.14
SC9503P	1.20	1N5401	0.12
SC9504P	1.20	1N5403	0.12
SL901B	5.00	1N5404	0.14
SL917B	7.00	1N5405	0.14
		1N5406	0.14
		1N5408	0.25
		BR100	0.22
		BR101	0.28
		BT106	1.19
		BT108	1.23
		BT109	1.09
		BT116	1.60
		BT120	1.60
		2N4444	0.90

E.H.T. TRAYS MONO

950 MK2	—
Single Stick	—
Thorn TV	—
11.16K 70V	0.75
TV 20 2 MT	0.75
TV 2016K	—
18V	0.75
Bush 718	1.30

BRIARWOOD TELEVISION LTD

Briarwood House, Preston Street, Bradford West Yorkshire BD7 1LU
Tel: (0274) 306018

P. V. TUBES

Telephone: Accrington (0254) 36521

38A WATER STREET, ACCRINGTON, LANCBS BB5 6PX. WHOLESALE SUPPLIERS OF TELEVISION COMPONENTS

TRADE COUNTER OPEN MON-FRI 9 a.m.-4.30 p.m. SAT MORN. 9.30 a.m.-12 noon.

INTEGRATED CIRCUITS

MC1307	1.00	ML922	3.29	SN76131N	1.30	TAA350A	60	TBA1208	1.30	TBA570	1.00	TCA800	1.99	TDA2540	3.84
MC1327	1.00	ML928	2.18	SN76226(DIN)	1.55	TAA300	58	TBA1208B	1.30	TBA641-811	2.40	TCA940	1.80	TDA2541	2.85
MC1330P	90	ML928	2.18	SN76227N	1.10	TAA310	2.83	TBA120U	1.00	TBA641 8X1	2.00	TDA440	2.20	TDA2560	1.90
MC1349	1.20	SA5560S	1.80	SN76532N	1.50	TAA320	59	TBA395	2.20	TBA690	1.50	TDA1004A	2.95	TDA2561	2.25
MC1350	96	SA5570S	1.80	SN76533N	1.30	TAA550	28	TBA395	80	TBA673	1.10	TDA2540	3.15	TDA2580	1.25
MC1351	1.00	SA5580S	2.90	SN76033N	1.53	TAA570	1.00	TBA440N/TBA1441		TBA700	2.12	TDA1170	1.99	TDA2591	2.75
MC1352	1.00	SA5590S	2.90	SN76544N	1.35	TAA630	2.50		2.75	TBA7200	2.12	TDA1190	2.80	TDA2593	2.50
MC1358PD	1.50	SL9018	4.45	SN76850M	85	TAA630S	2.50	TBA440	2.50	TBA750	2.05	TDA1270	3.73	TDA2600	3.25
MC1495L	1.00	SL9170	6.25	SN76860N	60	TAA621 AX1	3.00	TBA480	1.20	TBA800	99	TDA1327	1.00	TDA2603	1.95
MC140118CP	42	SL1310	1.80	SN76866N	70	TAA840/S1	1.80	TBA4800	1.20	TBA813AS	1.35	TDA1352B	1.80	TDA2611A	1.95
MC140498CP	43	SL13270	1.20	SW153	2.74	TAA700B	1.70	TBA500P	1.58	TBA820	1.70	TDA1412	1.20	TDA2640	2.25
ML2318ETTR6016	2.20	SN76544	2.00	TA7141P	95	TAA700	1.70	TBA510	3.00	TBA890	3.94	TDA2020	4.88	TDA2680	1.00
ML2322ETTR6016		SN76003N	1.75	TA7050P	95	TAA616B	1.20	TBA5200	1.20	TBA920	1.80	TDA2030	2.80	TDA3950	2.98
CA3065	2.20	SN76013N	1.50	TA7051P	95	TAA840		TBA530	1.28	TBA9200	1.80	TDA2521	4.17	UPC566H	2.35
ML236	5.35	SN76013ND	1.50	TA7171P	1.80	TBA120A	70	TBA530	1.20	TBA950I(2X)	2.40	TDA2522	2.40	UPC575C2	3.40
ML237	1.95	SN76023N	1.45	TA7172P	1.80	TBA120S	70	TBA540	1.49	TCA160	1.49	TDA2523	2.20	UPC1025HI	4.50
ML238	4.20	SN76023ND	95	TA7173P	1.45	TBA120SA	70	TBA550	1.58	TCA760	1.20	TDA2530	1.95		
ML239	2.50	SN76110N	89	TA7074P	1.80	TBA120AS	70	TBA550Q	1.58	TCA760	2.30	TDA2532	2.45		
ML920	4.12	SN76115N	2.27	TA7176P	75	TBA120AS	70	TBA560Q	1.59	TCA70S0	1.25	TDA2524	2.25		

SOCKETS IC
8 pin 24 16 pin 20
14 pin 18 14 pin DII/DUI28

WE NOW HAVE THESE SPECIAL CB INTEGRATED CIRCUITS

TA7205AP	3.72	MSN5807	7.87	PLLO2AG	9.89	LC7120	5.87	Please enquire for others	
25C1909	1.41	AN7150	3.97	MC1351P	1.00	TA7204P	3.77		
25C495	1.10	TA7222	4.07	AN214Q	3.91	TA7130P	1.93		
LC7130	5.93	TA7310P	2.78	LA4031P	3.21	UPC1156H	4.28		
AN240	3.84								

NEW VALVES

30FL2	1.41	EY500A	1.33	PCL85/805	79
DY802	72	EZ80/1	56	PCL86	81
DY86/7	66	GY501	1.45	PD500	2.93
ECC81	60	GZ34	1.56	PFL200	1.35
ECC82	58	KT66	5.00	PLK36	1.15
ECC83	80	KT88	6.00	PL81	94
ECC84	80	PC86	81	PL82	46
ECC85	80	PC88	81	PL83	1.43
ECC88	1.35	PC92	80	PL84	84
ECC89	80	PC97	1.14	PL95	1.00
ECC82	80	PC900	80	PL504	1.32
ECC81	1.04	PCCR4	70	PL508	1.43
ECC84	1.13	PCCR5	85	PL509	2.78
ECC80	84	PCCR8	82	PL519	2.78
ECC82	77	PCCR9	79	PL802	2.45
ECC86	84	PCCR189	1.02	PY33	81
ECC86	78	PCCR805	1.40	PY88	81
EF80	68	PCF80	75	PY500A	1.40
EF85	68	PCF86	1.13	PY800/1	69
EF86	1.19	PCF200	1.23	UCF80	87
EF89	1.83	PCF800	1.38	UCH81	1.43
EF183	68	PCF801	1.13	UCL82	84
EF184	68	PCF802	86	UCL83	94
EH90	1.02	PCF805	1.63	UL84	1.02
EL34	1.63	PCF806	1.30	U26	1.30
EL81	86	PCF808	1.63	U191	95
EL84	86	PCH200	1.45	UF23	85
EL90	82	PCL82	78	UY85	80
ES09	2.22	PCL83	2.00	PL802T	2.50
EY86/7	68	PCL84	81		

All valves are new - boxed - guaranteed.

Please add 15% VAT to ALL items.

SEMICONDUCTORS

AC126	22	AU110	2.00	BC171	9	BC261B	15	BD138	23	BF155	35	BF259	24	BFY90	75	OC79	20	2N3706	10
AC127	22	AU113	1.40	BC171A	10	BC262A	15	BD139	28	BF117	36	BF262	84	BR100	17	R20D88	180	2N3708	17
AC128	20	BC107	20	BC172	10	BC262B	15	BD140	31	BF125	26	BF263	50	BR101	30	R2108	180	2N2904	30
AC128K	32	BC107A	20	BC172	9	BC300	33	BD144	1.20	BF127	26	BF271	24	BR4443	80	R2265	1.40	2N5294	48
AC141K	34	BC107B	20	BC172B	10	BC301	28	BD159	65	BF154	12	BF273	12	BRX46	40	R2322	58	2N5296	48
AC142K	30	BC108	20	BC172C	10	BC303	28	BD160	1.30	BF158	18	BF310	30	BRX39	30	R2323	67	2N5298	69
AC176	25	BC108A	20	BC173C	12	BC307	10	BD166	52	BF160	27	BF311	30	BRX56	57	R2461	1.50	2N5496	53
AC176K	32	BC108B	20	BC174A/B	10	BC308A/B	17	BD179	52	BF167	24	BF336	36	BT105	1.00	R2540	2.30	2N6107	75
AC187	26	BC108C	20	BC182	9	BC327	11	BD182	72	BF173	22	BF337	30	BT108	1.24	RC18334	90	2SC643A	1.50
AC187K	28	BC109	20	BC182B	10	BC328	9	BD183	75	BF177	35	BF338	34	BT116	1.21	RC18335	80	2SC1172Y	2.20
AC188	25	BC109B	20	BC183B	10	BC337	11	BD201	85	BF178	26	BF355	37	BU104	2.00	TIP29C	43	2N5498	53
AC188K	37	BC109C	20	BC184	9	BC338	9	BD202	80	BF179	28	BF362	37	BU105	1.25	TIP30C	43	2N5499	53
AD143	82	BC114	12	BC184	10	BC461	30	BD203	80	BF180	36	BF363	33	BU108	1.80	TIP31C	41	VA1104	75
AD149	79	BC116A	12	BC204	10	BC547	10	BD204	84	BF181	36	BF371	30	BU124	1.30	TIP32C	42	VAB650	55
AD161	42	BC117	20	BC208	13	BC548	10	BD222	46	BF182	30	BF457	35	BU126	1.49	TIP33B	75	VA1039	35
AD161/2	1.15	BC119	24	BC209	10	BC549	8	BD223	56	BF184	30	BF458	28	BU204	1.50	TIP41C	46	GECC Qual	
AD162	42	BC140	32	BC212	9	BC550	7	BD225	47	BF185	30	BF459	35	BU205	1.34	TIP42C	47	Posistor	1.50
AF114	40	BC141	26	BC212L	9	BC557	8	BD232	45	BF194	11	BF639	28	BU206	1.80	TIP47	70	GECC Qual	
AF118	62	BC142	21	BC213	9	BC558	9	BD233	35	BF195	11	BF742	28	BU208	1.80	TIP2955	90	2040	1.50
AF121	56	BC143	24	BC2138	10	BCY72	13	BD234	37	BF196	10	BF743	28	BU208A	1.85	TIP3055	63		
AF124	34	BC147	9	BC213L	9	BD115	32	BD235	33	BF197	11	BFW10	60	BU208/02	2.10	TIS91	21		
AF125	35	BC148	9	BC214	9	BD116A	65	BD236	40	BF198	18	BFX29	30	BU326A	1.42	TV105/02	1.55		
AF126	34	BC149	10	BC214L	10	BD124P	60	BD237	33	BF199	15	BFX84	27	BU407	1.25	2N696	21		
AF127	32	BC157	11	BC2378	12	BD131	33	BD238	35	BF200	30	BFX85	28	BU500	1.95	2N2905	28		
AF139	42	BC158	10	BC238A/B/C	8	BD132	35	BD410	55	BF241	15	BFX86	30	EI222	28	2N3054	60		
AF239	45	BC159	10	BC251A	12	BD133	40	BD434	56	BF256LC	28	BFX88	25	MJE340	40	2N3055	60		
AL102	2.00	BC160	25	BC252A	12	BD135	26	BD517	60	BF256	28	BFY50	28	MJE500	44	2N3702	11		
AU106	2.50	BC161	28	BC252B	12	BD136	27	BD520	75	BF257	28	BFY51	22	MJ3900	2.36	2N3703	10		
AU107	2.00	BC170B	15	BC261A	18	BD137	26	BDX32	1.50	BF258	25	BFY52	20	OC71	27	2N3705	10		

DIODES

AA119	9	BY210/800	33	IN5401	12
BA102	17	BY298	22	IN5402	14
BA115	13	BY299	22	IN5403	12
BA145	17	BYX10	20	IN5404	12
BA148	17	BYX36/10	30	IN5405	13
BA154	6	BYX36/600	35	IN5406	16
BA155	14	BYX55/600	30	IN5407	16
BA156	15	BYX71/600	90	IN5408	16
BA317	25	0A47	9	ITT44	4
BAX13	4	0A90	5	ITT2002	11
BAX16	8	0A91	6	Y969	89
BB105B	30	0A95	6		
BB105G	30	0A202	11		
BY126	12	IN914	4		
BY127	11	IN4001	4		
BY133	15	IN4002	4		
BY164	45	IN4003	4		
BY176	85	IN4004	5		
BY182	87	IN4005	5		
BY184	55	IN4006	5		
BY223	90	IN4007	8		
BY199	28	IN4148	2		
BY206	14	IN4448	10		

RECTIFIER TRAYS

THORN 950 Mk II	4.25
THORN 1400 3 Stick	4.25
THORN 1500 3 Stick	3.85
THORN 1500 5 Stick	4.25
THORN 1600	3.45
THORN 1600	8.80
THORN 2000	8.89
THORN 3000/3500	3.56
THORN 8000	5.35
THORN 8500/8800	5.40
THORN 9000	7.43
DECCA CTV 19/25	5.35

P. V. TUBES

Telephone: Accrington (0254) 36521

REPLACEMENT ELECTROLYTICS

DECCA 30 (400/400/350V)	2.96
DECCA 80 (400/350V)	3.15
DECCA 100 (800/250V)	3.15
DECCA 1700 (200/200/400/350V)	4.83
PHILIPS G8 (600/300V)	2.21
PHILIPS G9 (600/300V)	2.21
PHILIPS G11 (470/250V)	4.50
PYE 691/7 (200/300/350V)	2.39
PYE 731 (600/300V)	2.31
RBM A823 (2500/2500/300V)	1.26
(2500/2500/25V)	1.15
RBM A823 (600/300V)	2.30
RBM Z146 (300/300/350V)	3.15
ITT CVC5/9 (200/200/75/25)	2.47
ITT CVC 20 (220/400V)	2.00
GEC 2110 (600/250V)	1.94
GEC 2040 (1000/2000/35V)	1.19
GEC 2040 (300/300/150/100/50)	4.10
THORN 3500 (400/40V)	30
THORN 950 (100/300/100/16/275V)	1.83
THORN 1400 (150/100/100/100/150/320V)	2.79
THORN 1500 (150/150/100/300V)	2.01
THORN 1500 (12/300V)	31
THORN 3500 (175/100/100/400/350V)	2.46
THORN 3500 (1000/63V)	65
THORN 3500 (1000/70V)	84
THORN 8000/8500 (2500/2500/63V)	1.54
THORN 8000/8500 (700/250V)	2.31
THORN 8000/8500 (400/350V)	2.56
THORN 9000 (400/400V)	3.05

WIREWOUND RESISTORS

PREFERRED VALUES	
4W/5W	price each
1R 1K5	20
2K2-3K3	20
4K7-6K8	20
10K	25
7W	
1R-4K7	21
5K6-12K	21
15K 22K	21
11W	
1R-6K8	24
10K-15K	24
22K	24
17W	
1R-10K0	28
15K-22K	28

RESISTORS

A range of the following at Preferred Values

	Price per 10 pack
0.25W	20p
0.5W	20p
1W	36p
2W	62p
2W	62p
10M	62p

MIXED DIELECTRIC CAPACITORS

Volts DC			
600V	0.1 mFd	38	
1000V	0.01 mFd	20	
	0.047 mFd	29	
	0.1 mFd	32	
	0.22 mFd	48	
	0.47 mFd	75	
1250V	0.1 mFd	45	
1500V	0.0022 mFd	19	
	0.0047 mFd	20	
	0.022 mFd	24	
	0.033 mFd	59	

CAPACITORS

AXIAL TYPE

Volt	MF	Price	Volt	MF	Price
10	22	7	47	7	7
	47	7	100	10	19
	100	8	220	30	30
	220	11	470	38	38
	470	18	1000	53	53
16	1000	20	2200	85	85
25	10	7	100	10	12
	22	7	22	14	14
	47	9	47	19	19
	100	10	100	29	29
	220	17	220	36	36
	470	22	300	12	30
	1000	36	450	1	23
	2200	46	4.7	28	28
	4700	80	10	28	28
40	22	9	22	56	56
	500	36	33	62	62
50	1	7	500V	1	30
63	2.2	7			

DISC CERAMIC CAPACITORS

8KV d.c. - 12KV d.c.	High Voltage		
39 pF	180pF	30	
140pF	200pF	30	
150pF	220pF	30	
	250pF	30	

TEST EQUIPMENT

Portable Oscilloscope	150.00
Probes x 10	£10.90
TF200 Frequency Metre	155.00
CRT Tester/Rejuvenator	172.00
LABGEAR Colour Bar/Cross Hatch	215.00
LABGEAR Pattern Generator (Pocket Size)	97.50

EAGLE PRODUCTS

SE500 Headphones	3.75
SE540 Headphones with Volume Control	5.50
SE600 Lightweight Headphones	7.95

SKELETON PRESET POTENTIOMETER HORIZONTAL and VERTICAL

MINIATURE		price each 14
100R-220R-470R-1K0-2K2-4K7-10K-22K-47K-100K		
220K-470K-1M0		
STANDARD		price each 14
100R-220R-470R-1K0-2K2-4K7-10K-22K-47K		
100K-220K-470K-1M0-2M2-4M7		

'MIDGET' CONTROLS

Insulated spindle length 44mm.

LESS SWITCH	39p
Log or Lin	
5K-10K-25K-50K-100K-250K-500K-1M	
WITH D.P.S.T. SWITCH	81p
Log: 5K-10K-25K-50K-100K	
250K, 500K, 1M, 2M	

SLIDER POTENTIOMETERS

Lin or Log			
470R	55p	4K7	55p
1K	55p	10K	55p
2K2	55p	47K	55p

MULTITURN POTENTIOMETERS

100K	55p
GEC/TCE	55p
PHILIPS G8	55p
OECCA/RANK	55p

THICK FILM RESISTOR NETWORKS

THORN 3500 (5 pin connection)	1.98
PYE 731 (6 pin connection)	2.20
THORN 9000 (Circuit Ref R704/7)	1.98

CONVERGENCE PRE-SET POTS

3 Watt complete with knob	each
5R0-6R8-10R-15R-20R	35
50R-100R-200R-500R	35

METRIC CONVERGENCE POTS

Philips G8	
5R-10R-20R-50R	35

EAGLE PRODUCTS

Please send large SAE for full EAGLE Catalogue.

Multimeters

KEW 7N	2,000 opv	5.25
EM5	5,900 opv	9.95
EM10	10,000 opv	11.50
EM50	50,000 opv	19.95
EMC321 Carrying Case for above		2.25
Digital Meter TS1000		44.50
KHP 30N Measuring Probe (30kV) (E.H.T.)		29.95
T1206 2 Station Intercom.		6.95

ELECTRONIC TUNERS AND ASSEMBLIES

Mullard ELC1043/05	7.60
Mullard ELC1043/06	7.60
4 P/B OECCA/GEC/ITT	5.80
6 P/B OECCA/GEC/ITT	7.00
4 P/B PYE	9.00
6 P/B PYE	16.00
PHILIPS G8 Tuner	10.50
PHILIPS G8 Ass (Square/Early)	13.50
PHILIPS G8 Ass. (Sloping/Late)	13.90
PHILIPS G9 Tuner	10.50
PHILIPS G11 Tuner	9.00
ITT/PYE/GEC 7 Button P/B	13.95
GEC 2110 6 way P/B	7.75
U321 UHF Tuner	7.50
THORN 8800 SELECTOR	7.50
THORN 9000 SELECTOR	11.40

SUNDRY TUNER ACCESSORIES

RANK Tuner Push Button 1 1/2" x 1/4" dia.	30p
RANK Tuner Push Button 2" long x 1/4" dia.	30p
RANK Tuner Push Button 2" long x 1/2" dia	30p
GEC Tuner Neons 2110 chassis	14p
Drive Cams	10p each

SWITCHES

4A Double Pole On/Off Switch General Purpose Push/push	62
Philips G8 Push On/Off Switch	1.38
4A Double Pole Rotary On/off	62
A1 Beam Switch (THORN 3500)	50
A1 Controls 5m (THORN 3500)	69
GEC 2110 A1 Control IMS (Red, Blue, Green)	each 58p
GEC 2040 On/Off Switch	each 86p

THERMAL CUT OUT

THORN 3000 2A Metal	1.60
THORN 8500 2.5 Plastic	1.60
GEC 2040 Metal	2.50

PYE LABGEAR

CMS040/WB UHF Masthead (ch21-68)	18.08
CM7025 UHF High Gain M.H.A. 24V (specify group A, B or CD)	14.81
CM7061 Power Unit (12V)	10.84
CM7065/WB VHF/UHF M.H.Amp (12V)	12.80
CM7073 VHF/UHF Dist Amp (8+1)	37.00
CM7053 'Behind the set' UHF Amp. (mains)	10.73
CM7043 'Behind the set' 2nd Set Amp (UHF-2 outputs)	10.72
CM6006 UHF 6 way Passive Splitter	10.72
CM7042 TV Games Combiner	3.31
CM9003 Flush Mount Single Outlet Isolated	1.76
CM9009 Flush TV/FM Duplex Outlet Isolated	3.00
CM7069 Tri Star Amplified Set Top Aerial (ch21-68) UHF	17.50
CM6038 VHF/UHF 625 TV Patt Generator	97.50
CM6052 UHF/VHF Pal Colour Bar Generator	215.00
7056 TELETEXT ADAPTOR (Converts any set to remote)	208.00
AMPLIFIED CARAVAN AERIAL (All Channels)	18.50

FUSES

	Pack of 10
1 1/2" QUICK BLOW	48
100ma	48
250ma-500ma-750ma-1A	49
1.5A-2A-2.5A-3A-5A	40
1 1/2" ANTISURGE	
250ma, 500ma, 600ma, 630ma, 750ma, 850ma, 1A, 1.25A	
1.5A, 2A	1.41
2.5A, 3A, 5A	2.18
20m ANTISURGE	
80ma	3.11
100ma, 160ma, 200ma	2.08
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.6A, 2A	1.07
2.5A, 3.15A	1.43
20mm QUICK BLOW	
100ma	45
250ma, 500ma, 630ma, 800ma.	37
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	37
1" MAINS	
2A, 3A, 5A, 10A, 13A	84

MAINS DROPPERS

DECCA 20	2.20
R.B.M. A823	77
R.B.M. 161	85
GEC 2000/2018	70
GEC27840	84
PYE 713/15 3R5/15/45R	1.45
PYE 725/31 3R0/56R/27R	94
PYE 725 56R/27R	82
PHILIPS 50501	88
PHILIPS 210/50511/LINK	64
PHILIPS G8/50832	85
PHILIPS G8 47R section	39
THORN 1500	95
THORN 3500	75
THORN 8000	96
THORN 8500	86

SUNDRIES

ANTIFERENCE Super Set Top	6.80
ANTIFERENCE Car antenna	7.80
ANTIFERENCE Xtra Boost UHF Amp.	15.40
ANTIFERENCE SB11 Splitter	2.40
Surface Mounting Aerial Outlets	80
Cable Clips	per 100 1.18
Transductor 90°	2.08
EHT Final Anode Cap	53
Delay Line CTAV 82/DL50/50L141	2.20
EHT Cable 30kV	25p per mtr.
Coax Plugs	pack of 10 1.80
Focus control GEC/THORN	1.83
PVC Tape	35
FM Plugs	25
PL259 Plugs	40
DECCA 30 Series width control	50
DECCA 3.9R Modulohm	60
Line Connectors	35
6.3V CRT boost trans	4.35
ANTIFERENCE XGB High Gain Aerial (State Channel)	18.00
Reducers for PL259	16
N.B. We have a full range of aerials and accessories available from the trade counter	

SOLDERING EQUIPMENT

WELLER Iron Kit 15W	3.80
WELLER Iron Kit 25W (inc tips)	4.89
WELLER Iron 25W	3.80
WELLER 3/16" Single Flat Tips	51
MIN Soldering Iron	5.00
WELLER Heat Gun Kit	14.00
WELLER Heat Gun	11.00
(Pair) Tips for Gun	36
WELLER Cordless Iron	24.78
ANTEX Soldering Iron 25W	6.50
Solder Remover Sucker	70
Solids Map	7.00
500G Reel Solder	43
Oily Type Solder	43
250G Solder	3.50

DATA BOOKS NO VAT

Transistor Equivalent	
TVT 80 A-Z only	3.75
TVT 80 2N/2S series only	4.00
TVT 80/80 A-Z and 2N/2S together	7.50
LIN IC Books LIN 1	5.95
LIN 2	5.95

SERVICE AIDS

SERVISOL Freeze-It	80
SUPER SERVISOL	75
SERVISOL Foam Cleanser	70
SERVISOL Plastic Seal	68
SERVISOL Silicone Grease	78
SERVISOL Tubes Silicone Grease	1.60
SERVISOL Aero Klene	63
SERVISOL Aero Duster	72
SERVISOL Excel Polish	58
Penetrating Fluid	70
Fire Extinguisher 640G	1.88
Heat Sink Compound 25G	1.00
Silicone Rubber Tube 1108	2.98

ELECTROLUBE PRODUCTS

Electro-Mech lubricant	1.39
Elect cleaning solvent	1.50
Freezer	1.39
Foam cleanser	1.00
Heat transfer compound	1.07
Silicone compound	1.81
Special contact fluid (Snorkel)	2.07
Permagard	1.43
Elec mech lubricant pen	89

HOW TO ORDER

Add 15% VAT to all Prices.
Add 75p per order P&P - First Class Mail is used whenever possible.



Goods for U.K. supply only.

For orders of very small odd items, i.e. IC's, Trans. diodes - Customers need send only 30p

For Aerosol's please add 30p per can (These are very heavy!)

Orders over £25 before VAT are Post Free except when the order contains AEROSOLS

Carriage on Tubes is as stated on list

ALL ENDURIES SAE PLEASE

VAT invoice on request

We do regret any postal increases but we try our best to give a speedy, and efficient service, at a fair price


Same day dispatch

TRANSISTORS, ETC.		Type Price (£)		Type Price (£)		Type Price (£)		Type Price (£)		Type Price (£)		Type Price (£)		Type Price (£)		Type Price (£)			
AC107	0.48	AU103	2.40	BC192	0.56	BC377	0.29	BD234	0.68	BF222	0.51	BPX29	1.62	MPSU05	0.66	ZTX500	0.18	2N3819	0.47
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.39	BD235	0.63	BF224 & J	0.22	BR101	0.53	MPSU06	0.76	ZTX502	0.22	2N3820	0.72
AC126	0.36	AU110	2.40	BC205*	0.39	BC440	0.52	BD236	0.63	BF240	0.32	BR103	0.64	MPSU55	1.26	ZTX504	0.28	2N3866	1.08
AC127	0.54	AU113	2.60	BC206*	0.37	BC441	0.59	BD237	0.68	BF241	0.31	BR303	1.06	MPSU56	1.32	2N4004	1.30	2N3904	2.00
AC128	0.48	BC107*	0.16	BC207*	0.39	BC461	0.78	BD238	0.68	BF244*	0.51	8RC4443	1.76	MPSU60	0.82	2N6956	0.46	2N3905	0.20
AC128K	0.55	BC108*	0.16	BC208*	0.37	BC477	0.38	BD253	1.58	BF245*	0.43	BR399	0.60	MPU131	0.59	2N697	0.46	2N3906	0.20
AC141	0.65	BC109*	0.16	BC209*	0.39	BC478	0.25	BD410	1.65	BF254	0.48	BR556	0.44	OC26	1.90	2N706A	0.33	2N4036	0.94
AC141K	0.70	BC110*	0.22	BC211*	0.36	BC479	0.33	BD433	0.65	BF255*	0.58	BSS27	0.92	OC28	1.49	2N708	0.29	2N4123	0.17
AC142	0.60	BC114	0.22	BC212*	0.17	BC547*	0.17	BD435	0.70	BF256*	0.49	BT106	1.50	OC29	1.80	2N914	0.32	2N4124	0.17
AC142K	0.65	BC115	0.24	BC212L*	0.17	BC548*	0.13	BD436	0.74	BF258*	0.44	BT109	1.99	OC35	1.25	2N916	0.48	2N4126	0.17
AC151	0.31	BC116*	0.26	BC213*	0.16	BC549*	0.15	BD437	0.74	BF259	0.52	BT116	1.45	OC36	1.25	2N918	0.54	2N4236	2.20
AC152	0.36	BC117	0.30	BC213L*	0.16	BC550	0.24	BD438	0.76	BF259	0.52	BT119	5.18	OC42	0.90	2N930	0.28	2N4289	0.32
AC153	0.42	BC118	0.24	BC214*	0.18	BC556	0.23	BD519	0.88	BF262	0.73	BU102	3.36	OC44	0.68	2N1164	10.29	2N4292	0.32
AC153K	0.52	BC119	0.34	BC214L*	0.18	BC557*	0.16	BD520	0.88	BF263	0.88	BU105	1.80	OC45	0.63	2N1304	1.40	2N4416	0.85
AC154	0.41	BC125*	0.30	BC225	0.42	BC558*	0.16	BD599	0.87	BF270	0.47	BU105/02	1.95	OC70	0.65	2N1305	1.29	2N4444	1.90
AC176	0.45	BC126	0.30	BC237*	0.16	BC559*	0.17	BD600	1.23	BF271	0.42	BU108	2.98	OC71	0.73	2N1306	1.49	2N4921	0.80
AC178	0.51	BC132	0.20	BC238*	0.15	BCY10	0.30	BD663BR	0.86	BF272A	0.80	BU126	2.91	OC72	0.73	2N1307	1.32	2N5042	1.65
AC179	0.55	BC134	0.22	BC239*	0.15	BCY30A	1.06	BDX18	1.55	BF273	0.33	BU204	2.50	OC81	0.83	2N1308	1.53	2N5060	0.28
AC187	0.56	BC135	0.21	BC251*	0.25	BCY32A	1.19	BDX32	2.95	BF274	0.34	BU205	2.88	OC81D	0.96	2N1311	0.47	2N5061	0.30
AC187K	0.65	BC136	0.22	BC252*	0.26	BCY34A	1.02	BDY16A	0.63	BF275	0.63	BU206	2.59	OC139	1.30	2N1893	0.52	2N5084	0.63
AC188	0.52	BC137	0.30	BC253*	0.38	BCY72	0.27	BDY18	0.72	BF336	0.63	BU208	2.71	OC140	1.30	2N2102	0.71	2N5086	0.49
AC188K	0.61	BC138	0.35	BC254*	0.28	BD115	1.35	BDY20	2.29	BF338	0.68	BU407	1.38	OC170	0.80	2N2118	0.38	2N5207	0.50
AC193K	0.70	BC140	0.36	BC262A*	0.28	BD123	1.50	BDY38	1.38	BF355	0.72	BU477	2.50	OC171	0.82	2N2218	0.38	2N5208	0.50
AC194K	0.74	BC141	0.44	BC263*	0.26	BD124	1.85	BDY38	1.48	BF362	0.49	CI06D	0.80	OC200	3.90	2N2219	0.42	2N5294	0.66
ACV17	1.20	BC142	0.35	BC267*	0.20	BD130Y	1.56	BF117	0.45	BF363	0.49	CI06F	0.43	OC201	3.95	2N2221A	0.26	2N5296	0.68
ACV19	0.95	BC143	0.38	BC268*	0.28	BD131	0.58	BF120	0.55	BF367	0.29	CI11E	0.46	OC202	2.40	2N2222A	0.41	2N5298	0.71
ACV28	0.98	BC147*	0.12	BC286	0.40	BD132	0.68	BF121	0.85	BF451	0.43	D40N1	0.64	OC205	3.95	2N2369A	0.40	2N5322	1.16
ACV39	2.02	BC148*	0.12	BC287	0.49	BD133	0.70	BF123	0.48	BF457	0.48	E300	0.42	OC207	1.98	2N2401	0.80	2N5449	0.18
AD140	1.75	BC149*	0.28	BC291	0.47	BD134	0.38	BF125	0.55	BF458	0.58	E1222	0.47	ON236A	0.94	2N2484	0.35	2N5457	0.46
AD142	1.90	BC152	0.42	BC294	0.37	BD136	0.38	BF127	0.55	BF459	0.49	E5024	0.19	R2008B	2.72	2N2570	0.74	2N5458	0.40
AD143	1.78	BC153	0.38	BC297	0.36	BD137	0.40	BF137F	0.27	BF459	0.16	GE7872	0.48	T210B	2.79	2N2646	0.82	2N5459	0.58
AD149	1.42	BC154	0.41	BC300	0.62	BD138	0.42	BF152	0.19	BF459	0.16	ME6042	0.18	R2323	0.85	2N2669	0.18	2N5466	0.85
AD161	0.66	BC157*	0.13	BC301	0.38	BD139	0.46	BF158	0.25	BF597	0.27	MF040A/02	0.18	R2323	0.85	2N2669	0.18	2N5466	0.85
AD161/162	1.22	BC158*	0.12	BC302	0.86	BD140	0.50	BF159	0.27	BF639	0.30	ME6001	0.18	ST2110	0.49	2N2894	0.45	2N6027	0.55
AD162	0.71	BC159*	0.14	BC303	0.64	BD144	2.24	BF160	0.20	BF640	0.29	ME6002	0.18	ST6120	0.48	2N2904*	0.40	2N6107	0.71
AF114	1.32	BC160	0.52	BC304	0.44	BD145	0.75	BF161	0.64	BF641	0.40	MJ2955	1.30	TC44	0.25	2N2905*	0.39	2N6122	0.60
AF115	1.26	BC161	0.58	BC307*	0.17	BD150A*	0.51	BF163	0.65	BF650	0.29	MJ3000	1.58	TC46	0.35	2N2906*	0.36	2N6178	1.07
AF116	1.28	BC162	0.15	BC308*	0.14	BD155	0.50	BF166	0.95	BF652	0.23	MJE340	0.68	TC47	0.45	2N2926G	0.15	2N6180	1.39
AF117	1.32	BC163	0.16	BC309*	0.16	BD157	0.51	BF166	0.95	BF652	0.23	MJE341	0.72	TC29A	0.47	2N2926G	0.15	2N6181	2.74
AF118	0.95	BC169*	0.14	BC317*	0.15	BD158	0.75	BF167	0.38	BF662	0.28	MJE370	0.74	TC29A	0.47	2N2926G	0.15	2N6181	2.74
AF121	0.68	BC170*	0.15	BC318*	0.15	BD159	0.59	BF167	0.38	BF662	0.28	MJE371	0.79	TIP31A	0.81	2N2955	1.12	2N5458	0.78
AF124	0.38	BC171*	0.15	BC319*	0.19	BD160	2.69	BF177	0.35	BF680	0.20	MJE520	0.67	TIP31A	0.81	2N2955	1.12	2N5458	0.78
AF125	0.38	BC172*	0.14	BC320	0.17	BD163	0.67	BF178	0.46	BF681	0.30	MJE521	0.95	TIP32A	0.87	2N3053	0.48	2N5459	2.26
AF126	0.36	BC173*	0.22	BC321A & B	0.18	BD165	0.66	BF179	0.58	BF688	0.42	MJE2955	1.20	TIP32C	0.72	2N3055	0.72	2N5459	2.26
AF127	0.86	BC174A & B	0.26	BC322	0.28	BD166	0.88	BF180	0.53	BF741	0.45	MJE3000	1.95	TIP33A	0.77	2N3250	0.52	2N5459	2.26
AF139	0.58	BC176	0.22	BC323	1.15	BD175	0.90	BF181	0.53	BF743	0.58	MJE3055	1.22	TIP34A	0.84	2N3254	0.58	2N5459	2.26
AF147	0.52	BC177	0.22	BC327	0.16	BD177	0.58	BF182	0.44	BFW11	1.02	MPP102	0.40	TIP41A	0.72	2N3391A	0.38	3N128	1.60
AF149	0.45	BC177*	0.20	BC328	0.18	BD178	0.92	BF183	0.52	BFW30	2.58	MPS3702	0.33	TIP42A	0.80	2N3633	0.60	40250	0.98
AF179	1.36	BC179*	0.22	BC337	0.17	BD181	1.94	BF184	0.44	BFW59	0.19	MPS3705	0.36	TIP2955	0.77	2N3703	0.17	40251	1.14
AF179	1.36	BC179*	0.22	BC337	0.17	BD182	1.34	BF186	0.42	BFW60	0.19	MPS6521	0.30	TIP3055	0.68	2N3704	0.19	40257	0.67
AF180	1.35	BC182*	0.15	BC340	0.19	BD183	0.57	BF185	0.42	BFW60	0.19	MPS6523	0.36	TIS43	0.44	2N3705	0.17	40361	0.48
AF181	1.33	BC182*	0.15	BC347*	0.17	BD184	2.30	BF184*	0.42	BFV90	0.65	MPS6523	0.36	TIS73	1.38	2N3706	0.16	40362	0.50
AF186	1.46	BC183*	0.14	BC348A & B	0.17	BD187	1.20	BF195*	0.13	BFX29	0.48	MPSA05	0.30	TIP300	0.23	2N3707	0.18	40410	0.88
AF202	0.27	BC183L*	0.14	BC349	0.17	BD188	1.25	BF196	0.14	BFY50	0.38	MPSA06	0.32	TIS91	0.28	2N3708	0.17	40429	0.94
AF239	0.73	BC184*	0.15	BC349B	0.17	BD189	0.71	BF197	0.15	BFY51	0.37	MPSA55	0.43	ZTX108	0.14	2N3715	1.70	40520	0.88
AF240	0.90	BC184L*	0.15	BC350*	0.24	BD222	0.91	BF198	0.29	BFY52	0.36	MPSA56	0.45	ZTX109	0.16	2N3717	2.09	40595	1.39
AF279S	1.41	BC185	0.36	BC351*	0.22	BD225	0.91	BF199	0.29	BFY53	0.36	MPSA93	0.56	ZTX123	0.23	2N3772	2.08	40603	1.13
AL100	1.30	BC186	0.25	BC352A*	0.24	BD232	0.91	BF200	0.25	BFY90	1.98	MPSL01	0.33	ZTX300	0.16	2N3773	2.90	40636	1.25
AL103	1.50	BC187	0.27	BC360*	0.59	BD233	0.62	BF218	0.42	BPX25	1.62	MPSU01	0.61	ZTX304	0.26	2N3794	0.40	40654	0.89

Alternative gain versions available on items marked*.

For matched pairs add 20p per pair.

LINEAR IC's		Type Price (£)		Type Price (£)		DIODES		Type Price (£)		VDR's, etc.		Type Price (£)		Type Price (£)		RESISTORS	
BRCC1300	0.93	SN76003N	3.32	TBA240A													

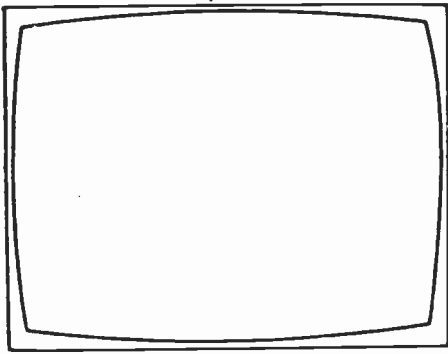

TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Colin R. Brown
01-261 5762

ACKNOWLEDGEMENT

We have been asked by the BBC to point out that the maps shown in our article on Satellite TV (October, page 639) were based on ones originally produced by the BBC Research Department. We apologise for our discourtesy in failing to mention this.

HELD OVER

Due to production difficulties with the present issue, the Simon column and Part 8 of the Colour Portable Project have had to be held over. They will appear next month.

In Praise of Profit

At a time when consumer organisations seem to feel that the public is entitled to get the earth for next to nothing, left-wing parties regard it as anathema, and right-wing parties believe in applying monetary pressure to just about everything in sight in an effort to restore stable economic conditions, the subject of profit seems to be rather out of fashion. It's also a fact that the fall of profits as a percentage of the country's annual income has been a feature of our economy for many years. Since our economy has not been exactly a success story, maybe it's time that greater consideration was given to profits. But who would take up the theme? One has only to ask which political party might be prepared to campaign for increased profits to realise just how unfashionable the subject has become.

Profits have had a bad image for a very long time – the image of the greedy capitalist exploiting the public. The first industrial revolution occurred in the UK, which for a time became the workshop of the world – rather long ago now. Large profits were made by many early industrialists, and there's no doubt that exploitation of the workforce often went hand in hand with high profits. But not all industrialists achieved success, and high profits more often came from exploitation of one sort or another in the remoter parts of the empire. These profits were all too often sunk in unsound, badly managed enterprises, with the net result that the rich got wise and tended to put their money into the things they knew better – property, land, livestock and so on. Manufacturing industry came to be neglected, and it was certainly not fashionable to become involved in it. Perhaps this is the reason why so many of the firms at the forefront of the gentle economic resurgence that occurred in the thirties were of US parentage – Ford, Hoover and so on. Nowadays it seems that Japanese manufacturers are the only ones with the confidence to invest in manufacturing activity in the UK.

The UK has many technological achievements to its credit. But we don't follow through. The failure is not in marketing but in between, in an inability to instal and operate the productive capacity that can generate the profits required for sound industrial development. When this topic comes up for consideration, it's usual to place a large portion of the blame on the educational system. As long ago as 1869, Herbert Spencer wrote that British schools ignore "what most nearly concerns the business of life. Our industries would cease were it not for the information men acquire as best they may after their education is said to have finished." The situation may be better today, but still leaves much to be desired. And those who've "made it" still by and large prefer their children to enter the professions – any profession other than engineering! Unfortunately for us however, those in other nations don't share this attitude. Hence the growing difficulty in finding goods with "UK made" stamped on them.

A recent visitor to Toshiba's Plymouth TV plant reports that there's a notice above the production line reading "let us together provide many other people with good and inexpensive products – smoothly." It's not only the rather odd cultural aspect of this message that strikes one, it's also the harsh realisation that this simple idea doesn't seem to find ready acceptance in the UK. It's as if our industrialists are suffering from some sort of collective loss of nerve, which is hardly surprising. Successful manufacturing requires sustained investment, which in turn is possible only in the context of profitable operation. When profits dry up, the economy can only get weaker and weaker. What inducement is there to investment in manufacturing when money can earn a better return elsewhere – in building societies, on deposit and so on? When it costs more to borrow from the bank than you can make out of running a business, then business activity must decline. This situation really is appalling. Manufacturing investment in the UK fell by 15% this year, from an already low level. It's expected to decline by a further 5-10% next year. The UK's industrial base has shrunk by 20% over the past two years.

The inescapable conclusion is that the idea of profit must come in from the cold. It is after all simply a measure of whether an organisation is producing/providing a product/service for which there is a need, and doing so efficiently. Merely to say that profit is a good thing, vital to economic well-being, won't produce it from a hat of course. But removing its bad image can only help. An overriding factor to bear in mind is that lack of productivity is a prime cause of inflationary pressure: you can't increase productivity without investment, and you can't increase investment in a profitless situation. Perhaps we need a profit party.

Teletopics

W. GERMANY STARTS TWO-CHANNEL TV SOUND SERVICE

Two-channel TV sound is now being regularly transmitted by the W. German ZDF network via its 29 main transmitters which cover some 60% of the W. German population. The start of the new service was timed to coincide with the opening of the Berlin Radio Show on September 4th. The system uses the two-carrier technique developed by the Institut für Rundfunktechnik in Munich. Patents have been taken out by IGR, the W. German equivalent of BREMA, and it's expected that this will have a dampening effect on imports, which have risen substantially over the last couple of years. Most W. German setmakers exhibited dual-channel sound receivers at the Berlin show, the additional cost working out at around 12-20%. By 1983, 45% of W. German TV set production is expected to feature dual-channel sound.

The technical details are as follows. The two carriers are spaced at 5.5MHz and 5.742MHz from the vision carrier, both being frequency modulated at up to 30kHz. The separation between the two carriers (242.1875kHz to be exact) is an odd multiple of half the line frequency. The 5.5MHz carrier is transmitted at -13dB with respect to the vision carrier, the second sound carrier being at -20dB. The 5.742MHz channel also contains a 54.6875kHz subcarrier for signal identification. The subcarrier is amplitude modulated at 117.5Hz to indicate a stereo transmission and at 274Hz to indicate a dual-sound (e.g. bilingual) transmission - zero modulation indicates a mono transmission.

£50 PRIZE WINNER

A questionnaire was included in 5,000 copies of our September issue, the aim being to find out a bit more about our readers and their interests. Over 1,000 questionnaires were returned to us - many thanks to all those who waded through the thing. The results are at present being analysed (not by us, or we'd never get this issue out on time!), and we'll let you know the outcome in a later issue. The winner of the £50 prize was John L. Saunders of West Sussex.

WIND-SOLAR POWERED TRANSMITTERS

The first television transmitting station in the UK to be powered by the wind and sun has been built by the IBA at Bossiney, Cornwall. The experimental station will provide ITV, BBC and TV4 programmes to just under 300 people, and marks an important development in the design of low-cost relay stations. The experimental use of the wind and solar generators combination is intended to continue for several years, during which data will be taken daily for analysis on a computer at the IBA Engineering Centre. The results will be compared with the performance predicted on the basis of a study of the Meteorological Office's daily sun and wind records over the past ten years.

The Bossiney station's power will normally come either directly from the wind or solar generators or from a bank of 36 large lead-acid batteries (about 1,000Ah capacity) that will be kept charged by the generators. The wind generator

has an output of 150W at a wind speed of 7m/sec, while the array of 24 solar panels, comprising 864 silicon solar cells, can provide a maximum output of 780W in peak sunlight. The transmitting equipment has a consumption of about 150W. The attraction of a wind-solar system in the UK is that the weather conditions will usually favour one or the other of these energy sources - only in long periods of still fog (unusual in Cornwall) is there thought to be any risk of the batteries becoming fully discharged. The solar panels, wind generator and four-channel transposer have been supplied by Laboratoire Général des Télécommunications (LGT).

Meanwhile the BBC has brought into operation a wind and solar powered link station at Dychliemore, Argyllshire, using all-British equipment. The link is at an intermediate site between the main Torosay transmitter on the Isle of Mull and the Dalmailly relay station - it's a mile and a half south of the relay station and nearly 200ft. farther up the mountain, acting as an "active deflector". The booster amplifier is supplied by a wind-driven generator or an array of four solar panels, with storage batteries to supply power during windless, sunless periods - the battery capacity is sufficient to provide power for over three weeks without recharging.

The use of wind and solar power saves little energy since the power consumption of these transmitters is small. The advantage lies in the saving of the considerable capital cost of taking mains supplies to remote sites (the Bossiney station is linked to the mains, though this power source will normally be used only to operate the sophisticated data recording system).

ZOOM MIKES

One of the problems with using a video camera is getting the sound right - in particular when a zoom for a close-up is accompanied by an almost inaudible voice.

To overcome the problem JVC have introduced two microphones for use with their GX77/88 colour cameras. The idea is to be able to "focus" the sound to match the image. The simpler microphone is type MZ250, which incorporates a manual switch for selection of two settings, unidirectional and super-directional. In the super-directional setting the sensitivity is increased four times and the directivity is narrowed. The price is £40.95. The more expensive (£82.70) type MZ500 changes automatically from an almost omnidirectional response with the camera lens at a wide angle to a super-directional effect as the lens zooms in, being linked to the powered zoom system. This microphone employs three unidirectional elements (see Fig. 1), with the third element reversed in relation to the other two. All three units have the same sensitivity and are mounted on the same axis. For super high directivity elements one and two are used; for moderate directivity element two only is used; while for an omnidirectional response elements two and three are used. Intermediate

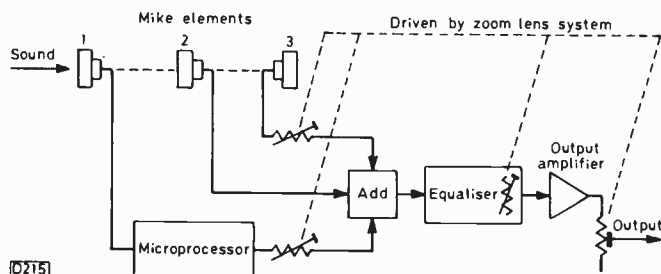


Fig. 1: The JVC MZ500 zoom microphone system.

effects are obtained since all four controls are ganged and driven from the zoom lens angle control circuit.

IC CHOPPER

Each new TV chassis that comes along seems to include something different and a bit unexpected. The latest circuit to come our way covers the GEC Models C2065H and C2265H, which are fitted with Hitachi 90° pincushion-distortion free tube assemblies. The completely new circuit features are the line output transistor, type 2SD898B, which has a common encapsulation with the shunt efficiency diode, and the extraordinarily simple switch-mode power supply – simple because nearly everything, including the chopper transistor itself, is incorporated within a single i.c. (type STR441). The over-voltage protection circuit places a short across the h.t. line in the event of excessive h.t./e.h.t.: the result is no sound or raster, with a high-pitched note to indicate that the safety circuit is operating.

MURPHY BACK

A welcome return by a well-known name in TV – Murphy. The brand is now being handled by Murphy Electronics, a subsidiary of J. J. Silber. The range will comprise sets with 20-26in. screen sizes and models with teletext facilities and remote control with frequency-synthesis tuning. The chassis used is the Rediffusion Mk. IV, which is produced at Rediffusion's Bishop Auckland factory in Co. Durham.

TRANSMITTER OPENINGS

The following relay transmitters are now in operation:

Avening (Gloucestershire) HTV West ch. 41, BBC-2 ch. 44, TV4 (future) ch. 47, BBC-1 ch. 51.

Braemar (Deeside) BBC-1 ch. 39, Grampian Television ch. 42, BBC-2 ch. 45, TV4 (future) ch. 49. The BBC transmitters are of a new BBC design nicknamed "Silver Streak": the central module of these units remains the same regardless of channel, making the transmitters cheaper and simpler to maintain.

Burnham (Norfolk) BBC-1 (East) ch. 40, Anglia Television ch. 46. BBC-1 (North) and Yorkshire Television can be received in the area from the Belmont transmitter.

Cane Hill (Coulston, Surrey) BBC-2 ch. 54, Thames TV/London Weekend TV ch. 58, BBC-1 ch. 61, TV4 (future) ch. 68.

Dalmally (Argyllshire) Scottish Television ch. 41, BBC-2 ch. 44, TV4 (future) ch. 47, BBC-1 ch. 51 (see note on wind-solar powered transmitters above).

Glynn (County Antrim) TV4 (future) ch. 54, BBC-1 ch. 58, Ulster Television ch. 61, BBC-2 ch. 64.

King's Lynn (Norfolk) BBC-1 (East) ch. 48, Anglia Television ch. 52. This is a two-channel relay – see note under Burnham above.

Newtownards (County Down) TV4 (future) ch. 54, BBC-1 ch. 58, Ulster Television ch. 61, BBC-2 ch. 64.

Wells-next-the-Sea (Norfolk) BBC-1 (East) ch. 43, Anglia Television ch. 50. This is a two-channel relay – see note under Burnham above.

The above transmissions are all vertically polarised.

UP-DATING VHS MACHINES

Michael Selman Ltd. (12 Newlyn Close, Bricket Wood, Herts AL2 3UP) have introduced a VHS machine modification system that brings earlier models up to more recent standards. The modification replaces the earlier



A JVC VCR incorporating the Selman up-dating modification with remote control.


timer, adds infra-red remote control and rapid rewind, and extends the recording time to six hours.

The new timer is a state-of-the-art microcomputer arrangement which enables the machine to be programmed for up to ten separate recordings on any channel. The timer can remember the sequence of programmes and repeat it the following week, or erase the sequence on completion. This is called "week repeat" and is something not found on other timers. Everyday repeat is retained. Something else that's new is the way in which the information is entered into the timer – no need now for three hands! A key pad is used, with the functions selected simply by momentarily pressing the appropriate key and then typing in the times and days. Entry errors can be erased at the touch of a key.


The remote control system gives remote control of pause/freeze frame, fast picture search and slow motion playback. A tri-colour LED is added to the front panel to indicate the mode selected – red for pause/freeze, green for picture search and yellow for slow motion. The additional rapid rewind mode enables the rewind time to be reduced by approximately two-thirds, and is switchable from the remote control handset.

The six-hour option is switch selected to retain normal operation. Selman claim that the quality of the sound and picture remain totally acceptable in the six-hour mode, which enables full use to be made of the advanced timer.

The modification can be carried out on most older models in the JVC, Akai, Ferguson and NordMende ranges. The additional electronics and hardware are all contained within the machine (no boxes bolted on the side!), while the electronic components mainly bridge across existing ones. The modification is available complete or in part to meet particular requirements, and after modification the entire machine is guaranteed for three months. If a

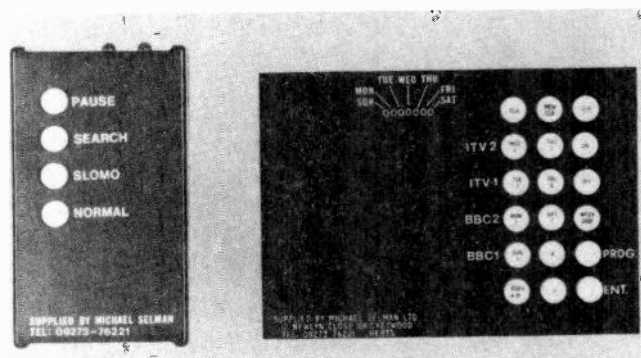

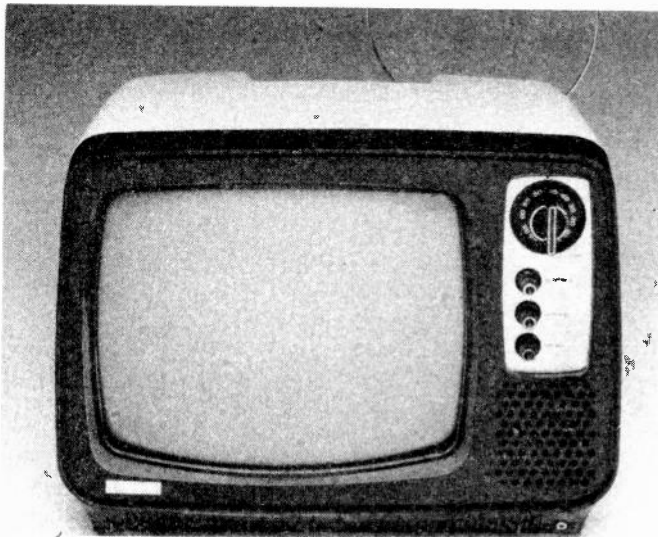The Selman VCR modification units – remote control handset left, timer etc. right.



This smart monochrome portable is produced by the UK's newest setmaker – Network Industries.

module fails, it can be removed complete and returned for repair without affecting the normal operation of the machine. For further details write to the address given above or phone Garston 76221.

SERVICE NOTES – PHILIPS

The latest issue of *Service Link* contains a fault survey on the G11 chassis. Amongst the conditions not mentioned previously in these pages are:

- (1) Hum bar on both sides of the scan with slight ripple on the picture due to transistor T4033 (BCX32) in the active filter circuit.
- (2) High volume/brightness or buzz on sound due to the 12V stabiliser i.c. (TDA1412).
- (3) A dark vertical bar on the right-hand side of the screen due to the sync/line oscillator i.c.
- (4) Trapezium distortion/bending in from the sides due to faulty transistor(s) in the EW raster correction circuit – check T2119 (BC148C), T2140 (BC158) and T2150 (BD238).

Here's an interesting one on the G7000 video games unit: in the event of loss of picture or picture break up, check the clock oscillator circuit – if in doubt, replace the crystal and C3 (crystals covered with a grey plastic sleeve are most suspect).

THE LEGAL ASPECT

The legal aspect of video recording has never been clearly defined. One suspects that the proverbial blind eye has been turned on it. Not in California however, where the Federal Court of Appeals, in the case of Universal Studios and Walt Disney versus Sony, has ruled that VCR manufacturers are liable for damages if users of the machines infringe the laws of copyright. The case against Sony had been brought as a test because Sony's advertisements emphasized the use of their VCRs for taping TV programmes at home, and certainly won't end with the California Federal Court of Appeals. Just where it will end is another matter . . .

HITACHI LASER FOR DISC PLAYERS

Hitachi have introduced a solid-state laser diode, type HL7801, whose relatively short wavelength (780 nanometres) gives excellent reproduction when used to scan

optical audio or video discs. The short wavelength reduces the size of the scanning unit and improves the signal-to-noise ratio. Whilst reliability has been a problem in the past with short wavelength laser diodes, the expected service life of the HL7801 diode is at least 100,000 hours at room temperature – equivalent to that of a typical 830 nanometre diode. The maximum output is 5mW, and a pin photodiode is incorporated in the encapsulation for convenience in assembling an automatic tracking control circuit. The availability of a suitable solid-state laser diode is likely to have a significant effect on the cost of an optical disc system.

HIGH-SPEED TELETEXT

The BBC and ITV are both now using four lines per field for teletext transmissions. In the case of Ceefax the waiting time for a page to appear has been halved – to an average 7 seconds, maximum 14 seconds. With Oracle the waiting time may be longer since the fourth text line is to be used for regional teletext.

Regional Oracle has already come to the Scottish Television area. STV's teletext service carries 60 pages of local information – news, sport, weather, travel, farming and a local "What's On".

The Oracle service throughout the UK now starts at 8.30 a.m., an hour before ITV weekday programme transmissions start.

PRESTEL FOR THE BLIND AND DEAF

At the recent National Aids for the Disabled Exhibition British Telecom demonstrated the world's first braille reader for use with Prestel. The reader has been developed by Clarke and Smith Ltd., in collaboration with British Telecom's Research Laboratories, and consists of a flat box about the size of an attache case. An array of tiny flat-topped pins is recessed into the surface of the box, selected pins being raised by the electronic equipment to create in braille the information being called up from the Prestel computer. As with an ordinary Prestel set, the braille version has a push-button control pad for page selection.

Also on show was a telephone terminal for the deaf (DCT). This consists of a small typewriter keyboard and moving strip visual display. The unit is linked to an ordinary telephone by means of two rubber acoustic cups into which the handset fits: users "converse" by using their typewriter keyboards. DCT is compatible with Prestel, and deaf people can use it to communicate with hearing people having Prestel sets with an alphanumeric keyboard.

NEW HITACHI VCR

Hitachi have introduced a new VCR, Model VT8300, to replace their successful VT8000. The new machine has a similar specification and look to its predecessor, but incorporates many circuit changes to achieve greater efficiency and reliability – much of the previous discrete circuitry is replaced by i.c.s. There's a four-digit tape counter to cater for four-hour tapes, and a ten-mode, full-function wired remote control keypad. The compact design is achieved by reducing the size of the motor system – a direct drive capstan is used, with a built-in high-precision quartz motor. The head cylinder also uses a built-in direct-drive motor with i.c. servo control. The capstan flywheel has been eliminated, the rotor performing this function. A microcomputer circuit controls the timed recordings, giving selection up to ten days in advance. To help with setting up, a test signal generator has been built in.

POST-A-PART-ELECTRONICS

SEMICONDUCTORS

AC 128	24p
BC 107	25p
BC 108	25p
BC 109	25p
BC 153	12p
BC 154	12p
BC 171	7p
BC 172	7p
BC 208	7p
BC 237	10p
BC 238	7p
BC 251A	7p
BC 307	10p
BC 308	7p
BC 347	7p
BC 455	7p
BC 456	7p
BC 546	7p
BC 549	7p
BC 556	7p
BC 559	7p
BC 595	10p
BCX34	10p
BD 131	25p
BD 183	£1.00
BF 137	20p
BF 197	20p
BF 240	8p
BF 255	10p
BF 256C	50p
BF 256LC	50p
BF 257	30p
BF 259	40p
BF 274	10p
BF 337	20p
BF 394	8p
BF 459	8p
BFR 87	30p
BU 105	60p
BU 108	£1.00
BU 207	£1.00
BU 208	£1.00
BU 126	£1.00
ME0404	7p
ME0412	7p
ME6002	7p
NKT241 (ACY21)	24p
NKT276 (AC128)	7p
PN107 (BC107)	£1.00
R2010B	£1.00
R2443	20p
R2540	£1.30
R2781	30p
RC A16446	7p
TIC 126	7p
TIS91	20p
2N2193	7p
2N3703	20p
2SA473	7p
2SC 734 (BC107)	7p
2SC 388	7p

DIODES

AA112	8p
AA119	8p
AA143	8p
BA115	8p
BA131	8p
BA154	8p
BA157	8p
BB103	8p
BY127	12p
BY133	10p
BZU15C12R	14p
BY204	8p
BYX22/400	8p
BZY79C 20V	8p
DA002	8p
SCR957	30p
IM102255	8p
IN60	8p
IN5349	8p
IN2070	8p
IN5254B	8p
IN4742A	8p
IS025	8p
IS451	8p
IS1554	8p
IS1658	8p
ITT638 CV9	6p
ZX6.2	8p
ZX150	8p

INTEGRATED CIRCUITS

BAV40	50p
BRC/M/200	£1.00
BRC/M/300	£1.00
DM74123N	50p

SN15846N	40p
SN7123N	40p
SN74154N	£1.40
SN74110N	40p
SN6622N	40p
TA7109AP	£1.00
TA7117P	£1.40
TAA570	£1.00
TBA480	£1.00
TBA1440C	£1.00
TDA2680	40p
TDA2690A	40p

E.H.T. TRAYS

PYE 731	£4.00
THORN 3000	£5.00
THORN 8500	£5.00
THORN 9000	£5.00
THORN 4000	£5.00

EHT STICK FOR THORN

950/1400/1500	
TRIPLERS E.C.T. TYPE	
80/150	5p

TRANSFORMERS/LOPT

MAINS TX 3000/3500	£10.00
MAINS TX 8000/8500	£10.00
S.O.P.T. 8000/8500	£3.50
3000/3500 SCAN TX	£6.00
3000/3500 EHT TX	£6.00
8000 LOPT	£9.35
8500 LOPT	£10.65
9000 LOPT	£10.15

DROPPERS

PYE-78+161	40p
PYE 147+260	40p
THORN 6+1+100 3K	50p
THORN 56+1K+47+12	£1.00
THORN 350+20+128+1K	
5+317	£1.00
THORN 50+40+1K5	50p
RBM 250+14+58TV161	50p
185+185 28W	40p
190+190 28W	40p
140+140 28W	40p

UHF AERIAL SOCKET & LEAD	25p
PYE. ITT, THORN	

UHF AERIAL SOCKET & LEAD GEC	25p
------------------------------	-----

UHF AERIAL SOCKET & LONG LEAD GEC	35p
-----------------------------------	-----

MAINS ON/OFF SWITCH ROTARY	20p
----------------------------	-----

MAINS ON/OFF SWITCH PUSH	20p
--------------------------	-----

A1 SWITCH THORN 3000/3500	50p
---------------------------	-----

A1 POT 5M 3000/3500	70p
---------------------	-----

100K 40 TURN POTS FOR V/CAP TUNERS	25p
------------------------------------	-----

UHF TV AERIAL FOR PORTABLE	50p
----------------------------	-----

MAINS NEON ON TAG STRIP WITH SERIES RESISTORS + LEADS THORN	25p
---	-----

DOUBLE FUSE HOLDER ON SMALL PAX. BOARD	10p
ITT BRIDGE REC FXS 244/2A	15p

BELLING & LEE SWITCHED FLUSH FITTING AERIAL OUTLET (WHITE)	£1.20 each
--	------------

MIXED PACKS

300 MIXED RESISTORS	£1.50
---------------------	-------

300 MIXED CAPACITORS	£1.50
----------------------	-------

150 MIXED ELECTROLYTICS	£2.00
-------------------------	-------

100 W/W RESISTORS	£1.00
-------------------	-------

20 MIXED CONV POTS	£1.00
--------------------	-------

40 MIXED POTENTIOMETERS	£1.50
-------------------------	-------

20 MIXED SLIDERS	£1.00
------------------	-------

40 MIXED PRESETS	60p
------------------	-----

20 MIXED VDR & THERMISTOR	£1.00
---------------------------	-------

20 MIXED FERRITE CORES	50p
------------------------	-----

20 MIXED VALVE BASES	£1.00
----------------------	-------

10 SPARK GAPS	£1.00
---------------	-------

10-16 PIN QUIL. IC SOCKET	90p
---------------------------	-----

20 ASSORTED TV KNOBS	£1.00
----------------------	-------

10-16 PIN QUIL. TO DIL IC SOCKET	90p
----------------------------------	-----

100 MIXED DIODES	£1.00
------------------	-------

FUSES 20mm

50ma	10 for 70p
315ma	10 for 50p
500ma	10 for 40p
1.25ma	10 for 40p
2.5ma	10 for 40p
3.15ma	10 for 40p

Thorn 3000 metal 2A cut out	£1.25
-----------------------------	-------

Thorn 8500 plastic 2.5A cut out	£1.25
---------------------------------	-------

SLIDERS

470R	
1KR	
2K5	any 6 £2.80
4K7	
10K	
47K	

3000, 8500, 9000, Thorn focus pots	£1.25
------------------------------------	-------

IC INSERTERS	50p
16 pin	

Large IC Extractor	50p
--------------------	-----

Crystals +433619 MHZ	50p
----------------------	-----

Degauss Thermistor PT37P ITT/GEC	25p
+ Fits some PYE/Bush etc.	

Degauss VDR Type E299D/H P230, 3000/8000	25p
--	-----

EX-EQUIPMENT UNTESTED 3000/3500 PANELS ANY SPECIFIED PANEL	£3.75
PRICE INCLUDES P&P	

8500 IF/DECODER PANEL EX-EQUIPMENT UNTESTED	£4.75
P&P INCLUDED	

LEATHER BOUND VIDEO CASSETTE CASE'S AVAILABLE IN FOUR COLOURS RED, BLUE, BROWN, GREEN	10 for £25.00
---	---------------

COAX PLUGS	12p
------------	-----

R2265	£1.35
-------	-------

MULTI SECTION CAPACITORS

200+32+300+100/350V	50p
200+200+100/350V	70p

2500+2500/63V Thorn	£1.20
---------------------	-------

200+100+100+50/350V	40p
---------------------	-----

32+32+16/350V	40p
---------------	-----

200+100+50/300V	40p
-----------------	-----

100+150+50/350V	50p
-----------------	-----

32+32/350V	30p
------------	-----

400+400+/350V	£1.30
---------------	-------

175+100+100/350 Thorn 3K	£2.00
--------------------------	-------

150+150+100/Thorn 1500	£1.90
------------------------	-------

CAN TYPES

2MF 250V	50p
----------	-----

22MF 375V	50p
-----------	-----

50MF 350V	50p
-----------	-----

400MF 350V Thorn 8K	90p
---------------------	-----

800MF 2V PRINT TYPE	80p
---------------------	-----

800MF 250V	70p
------------	-----

1250MF 50V	50p
------------	-----

1500MF 70V Thorn 3K	£1.00
---------------------	-------

2000MF 30V	50p
------------	-----

2500MF 35V	50p
------------	-----

2500MF 40V	50p
------------	-----

3000MF 40V	50p
------------	-----

ELECTROLYTICS

1MF 63V	20 for £1.00
---------	--------------

4MF 350V	10 for £1.00
----------	--------------

10MF 160V	10 for £1.20
-----------	--------------

15MF 16V	20 for £1.00
----------	--------------

15MF 63V	20 for £1.00
----------	--------------

22MF 40V	20 for £1.00
----------	--------------

22MF 63V	20 for £1.00
----------	--------------

22MF 160V	10 for £1.00
-----------	--------------

22MF 400V	10 for £1.00
-----------	--------------

33MF 40V	20 for £1.00
----------	--------------

33MF 50V	20 for £1.00
----------	--------------

47MF 250V	10 for £1.00
-----------	--------------

50MF 25V	20 for £1.00
----------	--------------

100MF 150V	10 for £1.00
------------	--------------

100MF 160V	10 for £1.00
------------	--------------

100MF 350V	10 for £1.00
------------	--------------

125MF 16V	10 for £1.00
-----------	--------------

150MF 25V	20 for £1.00
-----------	--------------

160MF 25V	20 for £1.00
-----------	--------------

160MF 40V	10 for £1.00
-----------	--------------

220MF 40V	10 for £1.00
-----------	--------------

330MF 10V	20 for £1.00
-----------	--------------

330MF 35V	10 for £1.00
-----------	--------------

330MF 63V	10 for £1.00
-----------	--------------

470MF 10V	10 for £1.00
-----------	--------------

470MF 25V	10 for £1.00
-----------	--------------

680MF 16V	20 for £1.00
-----------	--------------

680MF 40V	10 for £1.00
-----------	--------------

1000MF 10V	10 for £1.00
------------	--------------

1000MF 70V (Thorn)	80p
--------------------	-----

1500MF 16V	10 for £1.00
------------	--------------

2200MF 25V	6 for £1.00
------------	-------------

2200MF 40V	6 for £1.00
------------	-------------

THORN 8000 EHT DOUBLER	£3.12
------------------------	-------

10R 20W SPECIAL RESISTOR FOR 3500 CONVERGENCE BOARD (R751)	50p
--	-----

PANEL MOUNTING FUSE HOLDER 20MM	25p
---------------------------------	-----

MOST VALUES OF PRESETS AVAILABLE HORIZONTAL OR VERTICAL MINIATURE OR STANDARD 10 OF ANY VALUE	£1.00
---	-------

350G 6 PUSH BUTTON UNIT PLUS KNOBS, THORN V/CAP	£1.00
---	-------

625 AERIALS + FITTINGS AVAILABLE. PRICE LIST ON REQUEST	
---	--

EHT LEAD FOR SPLIT DIODES LOPT	£1.00
--------------------------------	-------

LITESOLD 20 WATT 240V SOLDERING IRON ELEMENT	65p each or 4 for £2.00
--	-------------------------

RECLAIMED 8000/8500 FOUR PUSH BUTTON MECH/ TUNERS	£3.75 each Plus P&P £1.00
---	---------------------------

WIREWOUND RESISTORS

Interested in Television Servicing?

Try a ZED Pack. Effect Repairs at Minimum Cost.

Z1	300 mixed 1/2 and 1/4 watt and miniature resistors	£1.95	Z20	10 Assorted switches including: Pushbutton, Slide, Multipole, Miniature etc. Fantastic Value	£1.20	Z44	TO3 Mounting kits (BU208)	8 for 60p
Z2	150 mixed 1 and 2 watt resistors	£1.95	Z21	100 Assorted Silver Mica caps	£2.20	Z45	TO220 Mounting kits (TIP33)	10 for 60p
Z3	300 mixed capacitors, most types amazing value	£3.95	Z22	10 Mixed TV convergence Pots	£1.00	Z46	TO126 Mounting kits (BD131)	12 for 60p
Z4	100 mixed electrolytics	£2.20	Z23	20 Assorted TV Knobs including: Push Button, Aluminium and Control types	£1.20	Z47	Pack of each Mounting kit. All include insulators and washers	£1.50
Z5	100 mixed Polystyrene Capacitors	£2.20	Z24	10 Assorted Valve bases B9A, EHT, etc.	£1.00	Z48	3a 1000v Diodes (IN5408 type)	8 for £1.00
Z6	300 mixed Printed Circuit Components	£1.95	Z25	10 Spark Gaps	£1.00	Z49	Brushed Aluminium Push Button Knobs, 15mm long x 11mm Diam. Fit standard 3 1/4mm square shafts	10 for £1.00
Z7	300 mixed Printed Circuit resistors	£1.45	Z26	20 Assorted Sync Diode Blocks	£1.00	Z50	Chrome finish 10mm x 10mm Diam as above	10 for £1.00
Z8	100 mixed High Wattage Resistors, wirewounds etc.	£2.95	Z27	12 Assorted IC Sockets	£1.00	Z51	Aluminium Finish, Standard Fitting Slider Knobs (Decca)	10 for £1.00
Z9	100 mixed Miniature Ceramic and Plate caps	£1.50	Z28	20 General Purpose Germanium Diodes	£1.00	Z52	Decca "Bradford" Control Knobs Black and Chrome. 1/4" Shaft	8 for £1.00
Z10	25 Assorted Potentiometers	£1.50	Z29	20 Assorted Miniature Tantalum Capacitors. Superb Buy at	£1.20	Z53	Tuner P/B Knobs, Black and Chrome. Fit most small Diam Shafts, ITT, THORN, GEC etc.	8 for £1.00
Z11	25 Assorted Presets, Skeleton etc.	£1.00	Z30	40 Miniature Terry clips, ideal for small Tools etc.	£1.00	Z54	Spun Aluminium Control Knobs (ITT) 1/4" Shaft, suitable for most sets with recessed spindles	8 for £1.00
Z12	20 Assorted VDR's and Thermistors	£1.20	Z31	5 CTV Tube Bases	£1.00	Z55	14 Pin DIL I.C. Sockets	12 for £1.00
Z13	1 lb Mixed Hardware, Nuts, Bolts, Selftappers, "P" clips etc.	£1.20	Z32	10 EY87/DY87 EHT bases	£1.00	Z56	16 Pin Quil I.C. Sockets	12 for £1.00
Z14	100 mixed New and marked transistors, all full spec. includes: PBC108, BC148, BF154, BF274, BC121L, BC238, BC184L and/or Lots of similar types	ONLY £4.95	Z33	20x PP3 Battery Connectors	£1.00	Z57	16 Pin DIL TO QUIL I.C. Sockets	10 for £1.00
(Z14A)	200 Transistors as above but including power types like BD131, 2N3055, AC128, BFY50 etc.	£9.95	Z34	6x Miniature "Press to Make" Switches, Red Knob	£1.00	Z58	22 Pin DIL I.C. Sockets	10 for £1.00
Z15	100 Mixed Diodes including: Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec.	£4.95	Z35	12 Sub Min S.P.C.O. Slide Switches	£1.00	Z59	B9A Valve Bases P.C. Type	20 for £1.00
Z16	20 IN4148 Gen Purpose Diodes	£1.00	Z36	12 Min D.P.C.O. Slide Switches	£1.00	Z60	0.47Ω 1/2 Watt Emitter Resistors	40 for £1.00
Z17	20 IN4003/10D2	£1.00	Z37	8 Standard 2 Pole 3 Pos Switches	£1.00	Z61	Chassis Coax. Socket	6 for £1.00
Z18	20 Assorted Zeners. 1 watt and 400 mw	£1.50	Z38	4x HP11 Batt Holders (2x2 Flat type)	4 for £1.00	Z62	Chassis 5 Pin Din Socket	8 for £1.00

ELECTROLYTIC

1µf 63v	20 for £1.00
1µf 350v	10 for £1.00
2.2µf 63v	20 for £1.00
4.7µf 63v	20 for £1.00
4µf 350v*	10 for £1.00
10µf 400v	8 for £1.00
22µf 16v	20 for £1.00
100µf 25v	20 for £1.20
160µf 25v*	20 for £1.50
330µf 25v	10 for £1.00
400µf 40v*	8 for £1.00
470µf 25v	10 for £1.00
470µf 35v	8 for £1.00
1000µf 16v	10 for £1.00
1000µf 25v*	8 for £1.00
1000µf 35v	6 for £1.00

*Axial. All others are Radial.

CAN TYPES

100+200 350v	£1.00
2000µf 100v	£1.00
1000µf 100v	60p
2.200µf 40v	60p
2.200µf 63v	70p
3.500µf 35v	50p
220µf 400v ITT/RBM	£1.00
10,000µf 35v 2 1/2" x 1 1/2" with fixing stud and nut.	£1.00 6 for £5.00

THYRISTOR

SS106 (BT106)	65p each
3 for £1.50, 10 for £4.50	

33v REGULATOR

Equivalent to TAA550, SN76550, ZTK33 etc.	8 for £1.00
---	-------------

EHT STICKS

TV18 KV	50p each, 3 for £1.00
Replacement Tripler Sticks (Thorn)	10 for £1.00

EHT DIODES

Very small. 20kV 2.5ma. 30ma peak	50p ea. 3 for £1.00
-----------------------------------	---------------------

TANTALUM

0.15µf 40v	12 for £1.00
0.22µf 10v	12 for £1.00
0.33µf 40v	12 for £1.00
0.47µf 40v	12 for £1.00
0.68µf 40v	12 for £1.00
2.2µf 40v	12 for £1.00
3.3µf 16v	12 for £1.00
12 of each value	£6.00
Pack of 20 Assorted. our selection	£1.20

SPECIAL OFFERS

100 Assorted Polyester Capacitors. Mullard C296's and others	
160v-400v only	£2.00
100 Assorted Mullard C280's	
Cosmetic imperfects etc.	£2.00
200 Mullard Miniature Electrolytics Cosmetic imperfects etc.	£2.00
PACK OF EACH	£5.00

TRANSISTORS

BC154, BC149, BC157, BF195, BF495, PBC108, BF393S	
12 of one type	£1.00
12 of each	£6.00
2N3055H	60p each
BD181	50p each
BD131	4 for £1.00
BD132	4 for £1.00

CONVERGENCE POTS

5Ω, 10Ω, 20Ω, 30Ω, 50Ω, 100Ω, 200Ω. 1K. 8 of one type	£1.00, 8 of each type £6.00.
---	------------------------------

ZENER DIODES

0v7, 2v7, 4v3, 4v7, 5v6, 6v2, 6v8, 7v5, 27v, 30v. ALL 400mw.	
10 of one value	80p
10 of each	£6.60
1.3 watt, 12v, 13v, 18v	
10 of one value	£1.00
10 of each	£2.50

DIODES

25 x IN4002	£1.00
10 x SKE 4F2/06 (600v 2a fast switching)	£1.00
12 x BY127	£1.00
10 x BA 158 (600v 400ma)	£1.00
IN5402 3a 1,750v	8 for £1.00
BY142 3a 1,750v	5 for £1.00
6A. 100V. Bridge Rectifier. Very small.	80p ea. 3 for £2.00

I.C.'s

CA270AE	£1.00
MC1327P	£1.00
TBA810P	£1.00
555 Timer	30p

LEDS

3mm Crystal Clear, very pretty. Red, Green, Yellow.	
10 of one colour	£1.00
10 of each	£2.50
TIL209 3mm Red	12 for £1.00
5mm Red	10 for £1.00
Red Triangle	8 for £1.00
Green Rectangle	8 for £1.00
Infra Red. LED Transmitter, Til 38. Hi-Power.	50p each. 3 for £1.00

THORN SPARES

"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly, Rotary type	£1.50, 3 for £4.00
"8500".0022 2000v Line Capacitor	10 for £1.00
"1590/91" Portable metal boost. Diode (W11)	5 for £1.00
"1500" Bias Caps 160µf 25v	20 for £1.50
"1500" Jellypot. L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"1600" Dropper 18 + 320 + 70 + 39Ω	3 for £1.50
"950" Can. 100 + 300 + 100 + 16µf	£1.00

MISCELLANEOUS

Line output transformer for RBM 823A	£4.25 each, 3 for £10.00
ITT VC200 4P/B Transistor Tuner. Suitable for some Pye and Philips sets. 3 hole fitting	£2.75 each
Decca Bradford Tuners. 5 button type	£3.00 each, 5 for £12.50
Decca Bradford Triplers	£3.00 each
UHF Modulator UHF out Video in. Ch. 36. 2 1/2" x 2" x 1 1/2" complete with 9 foot coaxial lead and plug. With connection data	£3.00 each, 2 for £5.00
Video Game Boards. All new but incomplete. Hundreds of useful components. C.M.O.S. I.C.'s, transistors, diodes, sockets, switches etc. Pack of five assorted boards	£2.50
GEC Hybrid 2040 series Focus Assembly with lead and VDR rod	£2.00 each, 3 for £5.00
Convergence Panel for above. Brand new leads and plug.	£3.00 each
GEC 2010 Transistor Rotary Tuner with AE, SKT, and leads	£1.95 each, 3 for £5.00
Bush CTV 25 Quadrupler type Q25B equivalent to ITT TU25 3QK	£3.00 each, 2 for £5.00
PYE 697 Line and power panel, damaged with some components missing but ideal for spares	£2.20 each, 3 for £6.00
Grundig UHF/VHF Varicap Tuner for 1500 GB, 3010 GB	£12.50 each, 3 for £30.00
EHT Lead with Anode cap (CTV) suitable for split Diodes sets 1m long	60p each, 3 for £1.50
EHT Cable	30p per metre, 10 metres £2.50
Anti Corona Caps	3 for £1.00
4.433 Mhz CTV Crystals	£1.00 each, 3 for £2.50
Cassette Mains Leads. 7ft with fig 8 plug	60p each, 3 for £1.50
6 MHz sound filters, ceramic 3 pin "TAIYO" type	50p each, 3 for £1.00
10.7 MHz Ceramic Filters "Veritron" FM4	50p each, 3 for £1.00
PYE CT200 Control Knobs	8 for £1.00
High quality Metal Coax Plug. Grub screw fixing	5 for £1.00, 100 for £12.50
Cassette/Calc Leads. 2m long, figure 8 skt. to flat pin. American plug	60p each, 3 for £1.50
3.5mm Jack Plug on 2m of screened lead	5 for £1.00
T.V. Game Remote Controls. Contains 22k thumbwheel pot on 2m of screened lead with 3.5mm plug	2 for £1.00
Mains Neons	10 for £1.00
Mini Grundig Motors. Regulated, variable.	
9/16" x 1 1/2" 1-6V	
2k2 Screened Resistors.	60p each, 3 for £1.50
White ceramic, 9 watt, with fusible link.	8 for £1.00
Phillips G8 Transductor.	£1.20 each, 3 for £3.00
Mullard LPI173, 10 watt.	
Amplifier module with circuit diagram.	£3.50 each, 2 for £6.00
E.H.T. Discharge probe, with heavily insulated handle, with lead and chassis connector.	60p each, 3 for £1.50

GEMINI ELECTRONIC COMPONENTS

Dept. TV, The Warehouse, Speedwell Street, London S.E.8.

Please quote ZED code where shown. Send cheque* or Postal Order. Add 60p P&P and 15% VAT.

*Schools etc. SEND OFFICIAL ORDER

ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8.

Send Large S.A.E. for list of Quantity, Prices and Clearance Lines etc.

Letter from America: Comb Filters

Jim Edwards

BEING badly in need of a haircut (even the editor looked surprised during a recent quick return visit to the UK, and his hair is never exactly short!), my mind has been drifting to thoughts of scissors and combs, which brings us immediately to the topic this month – comb filters. Since comb filters are probably not a subject that readers will have come across in reading *The Sporting Life* and other popular papers, we'd better perhaps start by saying what they do as well as how they do it.

Every PAL colour decoder (unless of the "simple PAL" variety, and those haven't been produced in many a year) employs a form of comb filter – the chroma delay line and its associated circuitry. It's not needed in an NTSC decoder of course, but something similar has come on the scene here recently – for a somewhat different purpose.

With system M, as used in the USA, Japan and one or two other countries, the maximum vision bandwidth is 4.2MHz, the colour subcarrier sitting at 3.58MHz. As a result, if a conventional LC filter is used to remove the chroma information from the luminance channel, the luminance bandwidth is severely restricted. Result: loss of detail. Similarly, filtering to reduce the luminance signal in the chroma channel (to eliminate cross-colour effects) severely reduces the lower sidebands of the chroma signal.

The results obtained using conventional filtering are thus poor. The effects are not so bad with the European systems B, G and I because of the wider channel bandwidth and higher subcarrier frequency. So what's the solution? Enter some high technology in the form of a type of comb filter to separate the luminance and chrominance components of the composite video signal without the problems of bandwidth limiting.

A bit of theory is required before we go further. If you examine the nature of the NTSC signal in detail you find that the luminance and chrominance signals, together with their 30Hz and 60Hz sidebands, are arranged so that they interleave, being separated by half the line frequency ($f_h/2$). This is shown in Fig. 1 – the colour subcarrier frequency is chosen to get this effect.

This frequency spectrum, together with the relative similarity of successive lines of the transmitted picture, means that near perfect separation of the luminance and chrominance components of the signal is possible, at the expense of vertical resolution, using a transverse filter – one operating on a time delay basis rather than by bandwidth limiting. Transverse filtering brings us back to the comb filter. The idea is that, in the same way as we add and subtract the signals on successive lines in a PAL decoder to separate out the U and V components of the chrominance signal, we can use addition and subtraction of successive lines of an NTSC signal to separate out the luminance and chrominance components of the composite video signal. This is possible because with an NTSC transmission there's a 180° phase change in the colour signal on alternate lines (done to minimize subcarrier patterning on a monochrome display).

The simplest comb filter arrangement for our purpose is shown in Fig. 2. It feeds the response peaks of the

luminance spectrum and the troughs of the chrominance signal spectrum into the luminance channel and vice versa. The circuit can be realised by using a glass delay line plus adder networks, an inverting amplifier and some rather critical balancing components. It operates only around the colour subcarrier frequency however, and may not eliminate the lowest colour signal sidebands. Difficulties also occur due to the fixed delay and the variable conditions when using a VCR – which is just where the system is most needed!

More recently semiconductor technology has come into use instead – employing a CCD delay line. This type of delay line has the advantages that it can operate down to the lowest video frequencies (rather than just around the colour subcarrier), and that the delay can be adjusted accurately in real time by locking the CCD clock to the colour subcarrier. Operating the filter down to the video base band has the disadvantage of destroying much of the vertical resolution however, so it's necessary to add back some of the low-frequency input to restore the vertical signals. It's possible to use vertical peaking comparable to the peaking frequently used in a video circuit to improve the picture definition.

The net result of all this applied high technology is a 40dB separation between the luminance and the chroma channels, with some 30dB attenuation of the chroma signal in the region 3.08-4.08MHz. This gives picture quality as good as that provided by continental European systems, albeit at a large add-on cost. The basic disadvantage of the NTSC system – the effect of phase shifts on colour – remains of course, but any improvement is a big help.

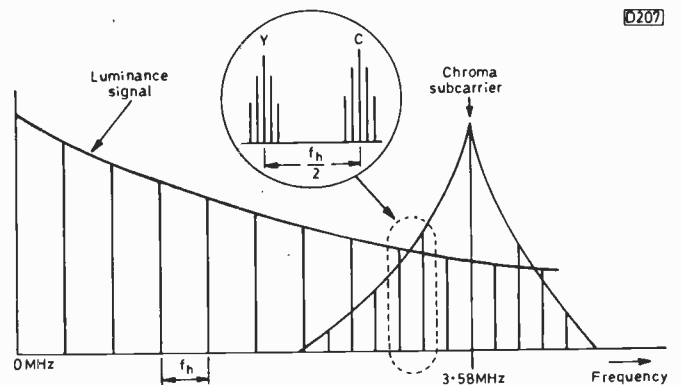


Fig. 1: NTSC signal spectrum, showing interleaved luminance and colour components.

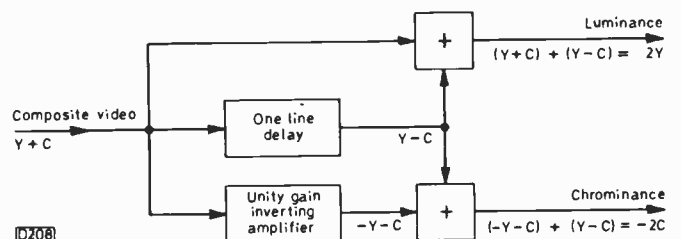


Fig. 2: Use of a delay line comb filter circuit to separate the luminance and chrominance signals.

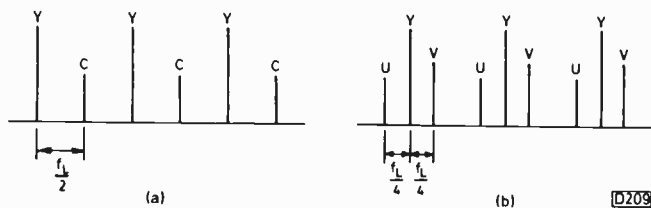


Fig. 3: Comparison between NTSC (a) and PAL (b) video signal spectra in the vicinity of the colour subcarrier.

Now you'll probably be asking why not apply the idea to the PAL system to get an even better picture? The answer unfortunately is that it won't work, not easily anyway. The problem is that when Dr. W. Bruch developed PAL he put a quarter-line offset on the subcarrier frequency (see Fig. 3). This means that the 180° relationship between the

luminance and chrominance signals doesn't hold, making life difficult to say the least. You can still do this type of filtering, and in fact an allied technique is used in the latest digital standards converter units, but you need at least one frame in store and a lot of computing power, which is not economical for the domestic telly! TV is going digital however, and memory is dropping in price, so who knows what may be possible in a few years' time?

Well that about wraps it up for now. All I've got to do is to think up a subject for my next report! Maybe you'd like to make some suggestions on what you'd like to know about the US TV scene? Just drop a line, care of the editor.

Finally a tip for drinkers who are "Hitch Hicker" fans: the pangalactic gargleblaster is alive and well and living in the USA under the name of Long Island Iced Tea... Freew!

Desolate Dan

Les Lawry-Johns

WE get a strange assortment of customers here. One of the strangest is probably Dan, whose vocation in life is the cleaning of outside pub toilets – which is why he's known as Dan the lavatory man. During his off-duty periods he goes around with an odd character called No Nose, who pushes a barrow around for a living. What's in the barrow no one seems to know, since he keeps it covered up. The two are probably friends because No Nose has difficulty smelling anything, and if there's one thing Dan has it's a smell. The principle is akin to working in a fish and chip shop – the smell follows you home. The aroma around Dan is a trifle offensive unfortunately. Even the cat, tolerant though she is about most things, beats a hasty retreat whenever Dan comes in. I can't beat a hasty retreat, so I keep a fixed smile on my face while I shake my head at whatever he asks for in the hope that he'll beat it quicker than if I nod. Honey Bunch does her disappearing act even quicker than usual when Dan is about.

Anyway, Dan brought his old Bush CTV184 (A823 chassis) in the other day with the complaint that the sound was o.k. but there was no picture.

"I've a couple of jobs to do" said Dan, "so I'll be back in about half an hour. You might have found out what's wrong by then".

"I might" I agreed, "but on the other hand I might not. But do call back. We're always pleased to see you Dan."

So off he went to slosh his toilets around a bit or whatever it is he does with them, and I turned to the set to check whether the top h.t. fuse was intact. It was, and a quick check at the tube base socket revealed that the first anode voltages were also present. The cathode voltages were a bit high, so attention was turned to the RGB output transistors which were found to be without any forward base bias. The preceding driver transistors had a negative voltage at their bases.

"Clamp pulses" I muttered, as though I knew what I was on about. There's a feedback clamp system you see, the clamp pulses coming from the line output transformer. Oh dear, all this complication. I looked at the circuit for a bit of help. Ah yes, the pulses come via the power supply panel. Let's take a look here. Two diodes near the h.t. smoothing resistors provide pulse clipping, so the bench lamp was directed on them. Glory be, one was away from its tag. Checks proved that the diodes were in order, so we soldered

the diode back on and the voltages returned to normal.

Which is more than the picture did. It was plain red. The green and blue tube base voltages were right, so we thought we'd check the tube's emission. Red good, nothing on the blue, nothing on the green. Patient reactivation brought them up to scratch, but it took a time and Dan's return would not be delayed much longer. Now that the emission of the three guns was about equal, we could set up the picture for natural colours. I was quite pleased with the result.

Dan came back, accompanied by No Nose. I turned the set round so that Dan could see the results of my good work. The reaction was not what I expected.

"What have you done to my picture? It was a lovely red, now it looks like anyone else's."

"It looks all right to me" said No Nose.

"Yes, but you didn't see it the way it was" said Dan. "It was a sort of cosy colour. Made you feel comfortable just looking at it. Now it looks... ordinary."

"Don't worry Dan" I said. "It'll soon be all nice and red again. If not this week then next, or possibly next month. It'll go back to red sooner or later, and then you'll be happy and it'll be worth waiting for."

Dan looked dubious, but I had to get rid of him somehow as it was getting a bit thick and I didn't care to think what other customers would say when they came in and sniffed the local air.

So Dan and No Nose carried the set out, leaving us to coax some breeze through the shop.

Teleton Touch Tuner

We then turned our attention to a Teleton set which had been waiting for us to summon up enough patience to find

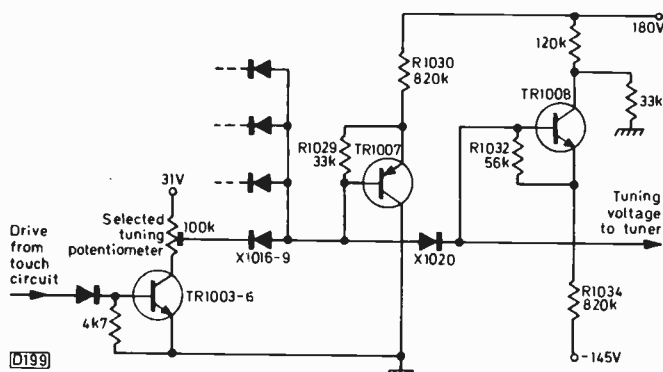


Fig. 1: Tuning voltage selection arrangement used in the Teleton Model C18BS.

out why the tuner wasn't tuning. A touch-tuner type, Model C18BS. We located the lead which should have carried the tuning voltage to the varicap tuner, but there was nothing there at all. Over to the selectors. The situation that confronted us here was as follows: about 30V at the supply end of the tuning potentiometers, but no tuning voltage output to the tuner unit – if anything there was a slight negative voltage, which was rather upsetting. We then received a distinct h.t. kick on the hand, which we'd carelessly rested on the end of the panel. Fancy that we thought, and decided to check the voltage. 180V. It feeds a couple of resistors, one of which (R1030) has the fairly high value of 820k. It seemed reasonable to see what the voltage at the other end of this resistor was. Nothing, because the resistor was open-circuit. Correct tuning was restored on fitting a replacement.

Fancy that we thought, Mrs. Crabbe will be pleased.

We then took a closer look at the circuit (see Fig. 1) to see what had been going on. As usual, there's an isolating diode in series with the slider of each of the tuning potentiometers. The idea is that only the diode connected to the selected potentiometer conducts, the others being reverse biased by the 30V supply. For the selected diode to be held conductive, there has to be a hold-on current path. This is provided by TR1007 and R1030, the transistor acting as a shunt stabiliser to hold the voltage at the junction of R1029/R1030 constant at some 1.2V above the voltage at the slider of the selected tuning potentiometer. So with R1030 open-circuit, the diode in series with the slider of the selected potentiometer won't conduct and there will be no tuning voltage output.

What does the rest of the circuit do? X1020 provides temperature compensation for X1016-9 (whichever is conductive). It too requires a hold-on current path, which this time is provided by TR1008 and R1034. The fact that the emitter of TR1008 is returned to a -145V rail explains the slight negative voltage we found on the tuning line.

And Then

Our peace was shattered by the arrival of Mr. Bore-Crashing, who claims to be an authority on all matters electrical. We'd crossed swords over his hi-fi equipment in the past, and he still claims that if he records a cassette here and sends it to a relative in the USA it will play at a different speed due to their 60Hz mains supply. This time he brought in his Ferguson colour receiver (Thorn 9600 chassis) and announced that the h.t. was low. As he was busy, he didn't feel like tracing the circuit through to find out where the h.t. was being dropped. I've learnt not to ask questions of him, because you get only a load of "I think" and "I know" but no description of the fault. So I plugged the thing in and connected it to an aerial. A picture appeared, with a gap at each side and a bit of a kink right down the centre.

"There you are" said Mr. Bore. "Not enough h.t. to fill the picture out. Now tell me I'm wrong!"

"You're wrong" I said, having had a similar case the previous week. "Your E-W modulator isn't modulating."

"There you are" he said, "it's not modulating because it's not got enough h.t. to modulate it." Too late, I realised I'd given him a new term to play with. He caught sight of Honey Bunch mucking about with the window display.

"My modulator's not working properly" he confided to her.

"You poor man" she replied, "I do hope it gets better soon."

So he gave that up and returned to watch me shining a

light into the right side of the main panel to see whether W810 – one of the modulator diodes – was feeling sorry for itself. It was a bit charred, and came out in pieces. It's a BY298, but I generally fit a BYX71 as a replacement since these seem to last longer and anyway I keep these and BY223s in stock for use in this position.

"Ah, the h.t. rectifier" proclaimed Mr. Bore.

"You could call it that, but it isn't" I said wearily, not wishing to go into the niceties of 110° scanning as I lazily soldered the replacement on the underside of the panel and checked with an ohmmeter to see that I'd got it the right way round.

"We'll soon see if it works" said the impossible Mr. Bore.

It did, for about a minute or so. The picture then sort of shuddered in and out and a cloud of grey smoke came from the approximate area of the tripler. Triplers don't give off grey smoke however, and they don't smell like that. It was like what you get from a hybrid ITT set when the mains filter capacitor starts steaming off whilst leaving the set working, thereby spreading consternation throughout the household (you know what I mean – those yellow ones). So it appeared to be a defective capacitor, and the circuit suggested that it might be C815 (1 μ F) which provides filtering between the driver transistor and the two modulator diodes. It didn't look an easy matter to get at it, so I suggested to Mr. Bore that he might like to call back later.

He seemed to hesitate, as though loath to leave the set in the hands of an incompetent idiot who couldn't even replace an h.t. rectifier without blowing up something else, but he eventually wandered off. So I called for coffee and had to make it myself as Honey Bunch was busy playing with a radio which was getting CB, with an interesting conversation about a Teddy Bear or something.

When I'd got up enough courage to tackle the suspect, which was hiding away at the front of the scan panel, I had to remove the tripler to reach it. I then found that I didn't have a 1 μ F capacitor with the correct voltage rating, so I ended up with two 2 μ F capacitors in series. This seemed to work all right, and I'd hardly replaced the back when the horror returned. Not the smoke or anything wrong with the set, but Mr. Bore himself.

"I thought I'd better not stay away too long in case you might need a bit of help."

Repeat Performance

Hardly had he gone than a Rank Z718 was brought in with a no-go symptom. The h.t. feed was o.k., but something was preventing the line output stage from working. Unhooking the top retainers enabled us to get at the front of the right side panel, where just for fun we checked the same circuit (the EW modulator – not quite the same, but you know what I mean). The two diodes here are 5D5 and 5D6. 5D6 was faulty, and turned out to be an SKE something or other. Anyway we stuck in a BYX71, which is what the circuit actually said, and order was restored. Funny how things seem to go in cycles, isn't it?

If you get one Thorn 1500 in with poor sync for example, you can bet your life that there'll be at least two others close behind waiting to have their 47k Ω sync separator screen grid feed resistors replaced.

We've also had a run of solid-state GEC colour sets in recently (C2100 series), all with line output stage trouble where the 40V rectifier diode D601 (fed from a winding on the line output transformer) goes short-circuit. In goes another BYX71, underneath instead of on top. I wonder what it'll be next?

Microcomputer Clock-Timer

Part 1

Luke Theodossiou

The idea for a comprehensive timer project originates from a colleague who owns a Philips N1500 VCR with its rather inadequate built-in timer. We had a look at several design approaches and eventually settled for a rather "inflated" unit, partly because we didn't think that there are many readers with these now old Philips machines and also, since we were going to produce a timer, it may as well be as versatile as possible to cater for a wide range of uses.

The unit may be used to switch four totally independent devices on and off on an hourly, daily or weekly schedule. It may be used for a variety of applications around the home and workshop, for example in crime prevention by periodically switching *different* lights on and off around the house; controlling the central heating; switching on the TV, radio, electric blanket, kettle for morning tea; greenhouse heating etc.

Circuitry

The circuit is shown in Fig. 1. It is designed around a Texas Instruments microcomputer, the TMS1601. The device requires a 50Hz input and this is conveniently taken from the secondary of the mains transformer and injected to the i.c. via a buffer/pulse shaper comprising Tr102 and

its associated components.

Data entry is from a twenty-switch matrix keyboard. The memory uses two 2102 i.c.s and data is loaded into the memory via a shift register, IC101. The display used is a 4-digit multiplexed common cathode type, whilst l.e.d.s are used to show status and days of the week. The display devices are driven by buffer transistors with the current limited by resistors in the collector leads. The cathodes are switched on via a Darlington driver i.c. (IC1) from the row outputs R1-R10 of the timer i.c.

The switch outputs from the timer i.c. are used to trigger solid state relays. These devices offer opto-coupled mains isolation, eliminate failure due to contact wear and are totally silent in operation. The ones we have chosen are able to switch 2.5A r.m.s. each but larger types are available which can switch 10A r.m.s. These are larger than the ones we are using, therefore they will need to be accommodated outside the case. Heatsinking is also required by these larger devices, so it may be as well to use mechanical types if very large loads are to be switched.

Next month we shall provide constructional notes, the complete programming guide, the circuit diagram of the power supply section and the component overlay diagrams.

★ Components List

Resistors: all 0.25W carbon film, $\pm 5\%$, except where stated.

R1	470R	R110	4k7	R122	24k $\pm 1\%$
R2	470R	R111	1k8	R123	22R
R3	470R	R112	22k	R124	22R
R101	2k2	R113	18k	R125	22R
R102	2k2	R114	10k	R126	22R
R103	10k	R115	10k	R127	22R
R104	10k	R116	10k	R128	22R
R105	10k	R117	10k	R129	22R
R106	10k	R118	10k	R130	22R
R107	10k	R119	10k	R131	5k6
R108	4k7	R120	10k	R132	3k3
R109	2k2	R121	10k		

Capacitors:

C101	47p	ceramic plate
C102	4 μ 7	50V radial electrolytic
C103	2200 μ F	25V radial electrolytic
C104	220n	100V Siemens B32560
C105	470n	100V Siemens B32560
C106	220n	100V Siemens B32560
C107	470n	100V Siemens B32560

Miscellaneous:

20 p.c.b. keyboard switches 12.7mm square
S1 RS Components 339-241
T1 RS Components 207-677
Heatsinks for IC105 and IC106: Staver F9-4-220

Semiconductors:

D1-D2	1N4148
D101-D106	1N4148
Tr101--Tr110	2N3904
Tr111	BC182L
LED1-4	0.2" green l.e.d.s
LED5-LED11	0.2" yellow l.e.d.s
LED12	0.2" green l.e.d.
LED13	0.2" yellow l.e.d.
LED14	0.2" red l.e.d.
LED15	0.2" yellow l.e.d.
LED16-LED19	0.2" red l.e.d.s
4-digit display:	RS Components 587-507
IC1	RS Components 307-109
IC101	74LS164
IC102	2102
IC103	2102
IC104	TMS1601
IC105	7905
IC106	7905
RLA1-RLA4	RS Components 348-431

F101 1A antisurge fuse with p.c.b. fuse clips
Output sockets: RS Components 488-797
Mating plugs: RS Components 488-781
Output fuses: 2.5A antisurge with chassis-mounting fuse holders.

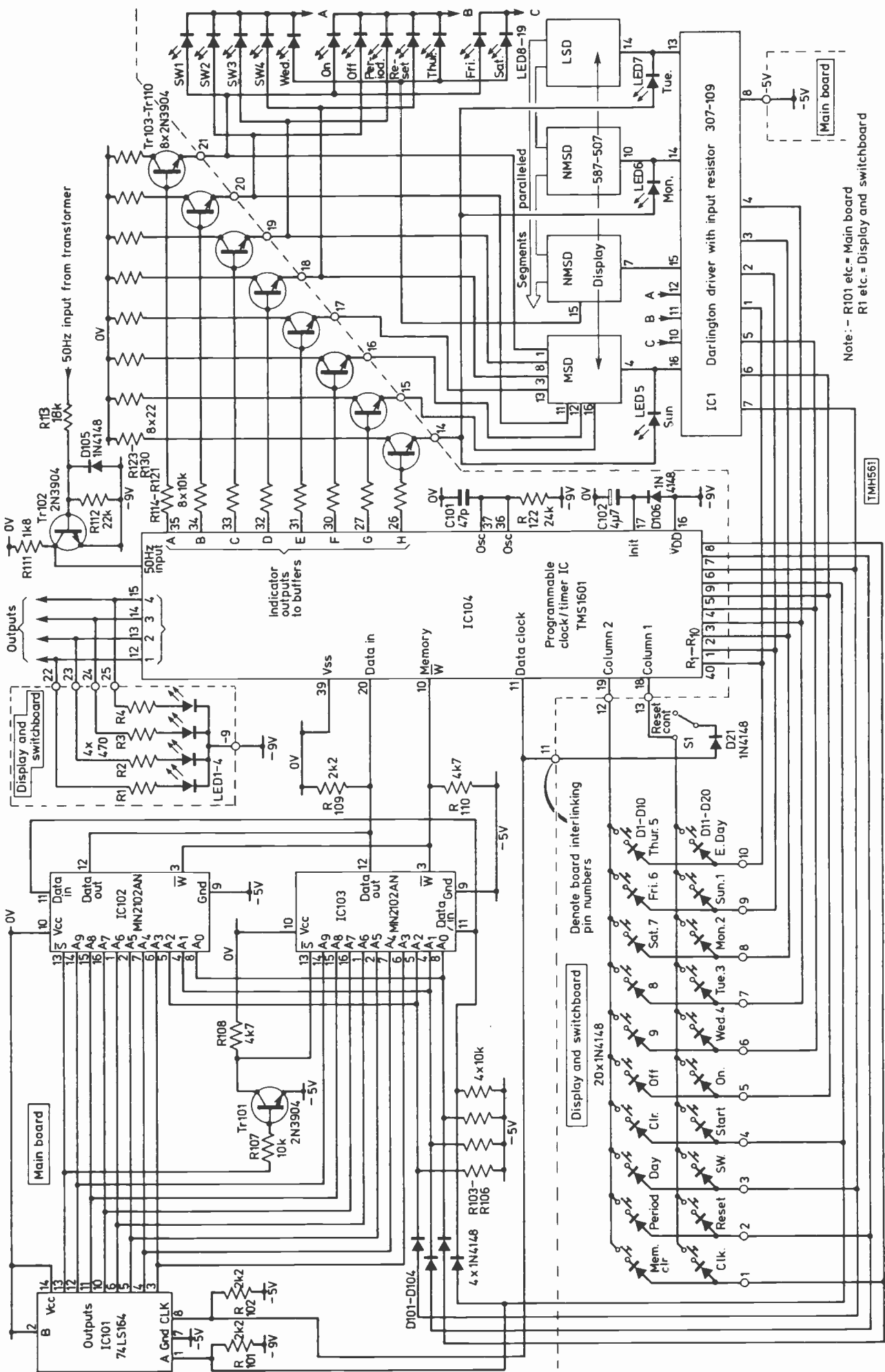


Fig. 1: Circuit diagram of the microcomputer clock-timer unit, with the exception of the power supply section and the output interface. These will be shown next month - they are all mounted on the main printed panel.

Fidelity's Monochrome Portables

S. George

FIDELITY Radio entered the TV field for the first time late last year, with a neat 12in. monochrome portable (Model FTV12). The use of six i.c.s means that the component count is low: apart from the loudspeaker, the c.r.t. assembly and the user controls, all the components are on a compact, horizontally mounted panel. Subsequently a version with remote control was added, Model TVR120, the infra-red remote control system providing on/off from a stand-by mode and stepping through six preselected channels. Tuning on the basic model is by means of a rotary potentiometer. Emboldened by the success of these sets, Fidelity entered the colour TV market earlier this year. We'll be taking a look at the colour chassis in a subsequent article: for the moment the subject is the monochrome portables.

Circuitry

On the signals side there are just two transistors, the BC148 video emitter-follower and BF257 video output transistor. Everything else is done by four i.c.s, two in the i.f. department and two on the sound side. The varicap tuner is followed by an SL1432 which provides i.f. preamplification and a.g.c. for the tuner unit. The SL1432 drives an SW153 SAWF, the i.f. strip being contained within a TDA440 i.c. The 6MHz intercarrier signal is selected by a ceramic filter and passed to a TBA120S i.c., audio amplification (1W output) being provided by a TBA820M i.c. All very straightforward, with only three tunable coils – one each for the vision and sound detectors and a sound trap in the feed to the video circuit.

On the timebase side, field deflection is taken care of by a TDA1170 i.c. while a TDA1180 acts as the sync separator and line generator, providing a pulse to drive the line output stage. Since the latter uses a BU807 Darlington line output device (see Fig. 1), no driver stage is necessary. This makes things simple indeed. The line drive pulse from pin 2 of the TDA1180 i.c. is capacitively coupled to the base of the

BU807 by C306, the d.c. restorer network D306/R304 setting the pulse at the correct d.c. level. The shunt efficiency diode is encapsulated within the BU807, while the series boost diode D306 produces some 24V across C312.

The power supply uses a bridge rectifier followed by a

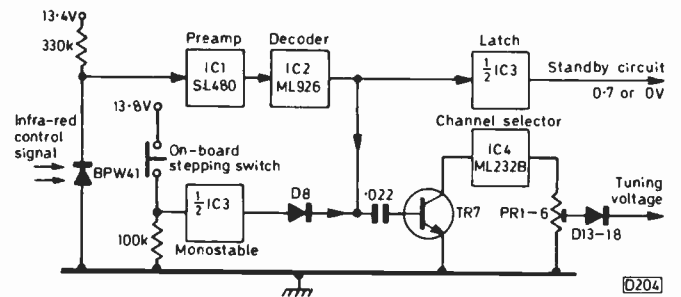


Fig. 2: Block diagram of the remote control receiver.

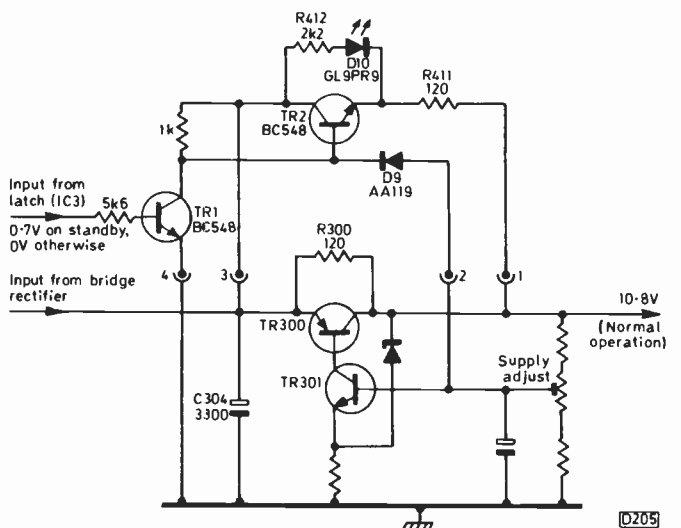


Fig. 3: The stand-by arrangement – when TR1 is switched on, the base of TR301 is shorted to chassis via D9. The regulator then turns off, its output voltage falling from 10.8V to a very low figure.

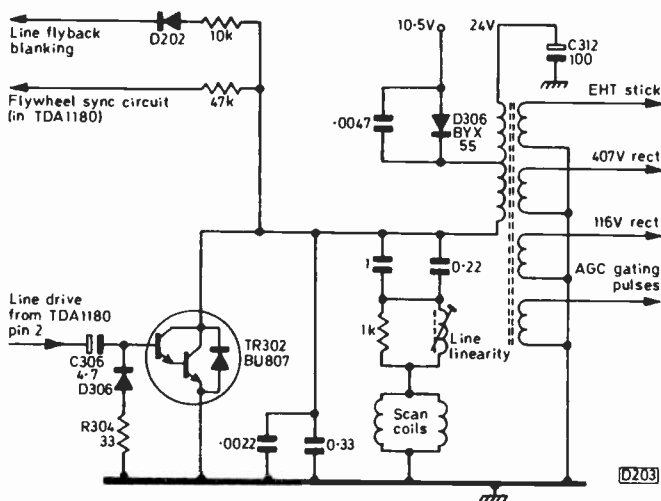


Fig. 1: The simple line output stage, with the BU807 Darlington output transistor driven directly from the sync processor/line oscillator i.c.

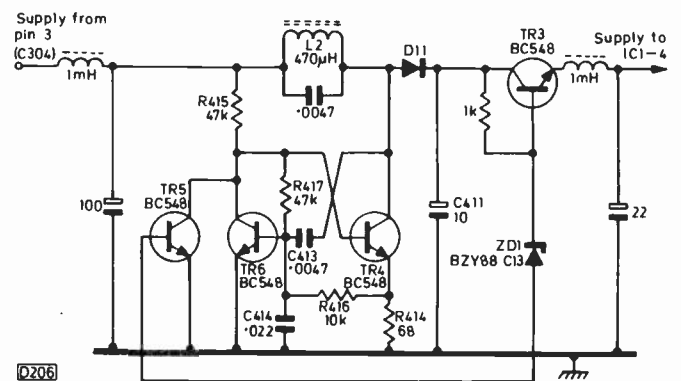


Fig. 4: The remote control receiver unit's power supply, with TR3 providing regulation. With a low input voltage the inverter comes into operation, the circuit then operating as a step-up regulator.

conventional two-transistor series regulator circuit, the regulator transistor TR300 being a pnp device (type BD534).

Remote Control Version

The infra-red remote control system has several interesting features. The transmitter unit uses an SL490 i.c. to produce the control pulse signal; this is followed by a three-transistor amplifier to drive the CQY99 infra-red emitting diode. The receiver unit (see Fig. 2) employs four i.c.s and seven transistors. The first i.c., type SL480, is simply a preamplifier. This is followed by an ML926 to decode the received control signal. Its output drives, via TR7, the ML232B channel selector i.c. (IC4). It also drives a two-gate latch in IC3 to give the stand-by action. The other two gates in IC3 are connected as a monostable which, with a front-panel switch, gives channel stepping at the set itself.

Now to the stand-by arrangement – see Fig. 3. TR300 is the conventional series regulator transistor and C304 the bridge rectifier's reservoir capacitor. The output from the latch, 0.7V on stand-by and 0V at all other times, is applied to the base of TR1. TR1 is thus normally switched off: its collector voltage will then be at some 13V, so diode D9 will be reverse biased. TR2 on the other hand will be

conductive, shorting out the stand-by LED D10 and its series resistor R412.

When a stand-by command signal is received, the latching circuit raises the voltage at the base of TR1 to 0.7V. TR1 switches on, and since its collector voltage is now almost zero diode D9 is forward biased. As a result, the base of the error detector transistor TR301 is shorted to chassis – via D9 and TR1. TR301 switches off, removing the drive to TR300 which also switches off. The 10.8V line falls to a very low voltage, since the only current feed is via the start-up resistor R300 and the parallel LED path. The rest of the set is now virtually without power, and since TR2 switches off the stand-by LED D10 lights up. The voltage across C304 rises to something like 20V on stand-by mains operation, since the rectifier circuit is unloaded.

An ingenious arrangement is used to power the four i.c.s on the remote control receiver panel – see Fig. 4. TR3 with zener diode ZD1 form a conventional voltage stabiliser circuit, with the anode of ZD1 returned to chassis via TR5. Since TR5 is saturated, TR6 is shorted out. On battery operation or a low mains supply, ZD1 will cut off, switching TR5 off. The inverter circuit consisting of L2, TR6/4 and the feedback components C413/R416 then comes into operation to boost the voltage across the reservoir capacitor C411 to the point at which ZD1 again conducts. The action continues intermittently. ■

Guide to the Philips K12 Chassis

Derek Snelling

THE Philips K12 chassis is of continental manufacture and is not seen in great quantities in the UK. It's used principally in a Philips and a Pye 26in. model featuring hi-fi sound – there are two speakers and a built-in bass reflex enclosure. Features include: 10W audio output with separate bass and treble controls; a LED to indicate that the VCR channel is selected; a LED to indicate optimum tuning; variable channel indicator brightness; headphone socket; speaker on-off switch; tape socket; and full infra-red remote control. The tube is of the 20AX type.

Plug-in Boards/Modules

Like many continental chassis, the design is based on the mother/daughter board principle, which in this case seems to have been carried to the extreme – there are no fewer than 15 plug-in panels/modules (16 if a v.h.f. tuner is fitted), three of which are mounted on the tube base! Looking at the chassis from the back, starting at the top left-hand corner and going round the chassis in a clockwise direction, the panels are as follows:

- (1) U555 EW correction panel. Rectifiers on the panel provide 225V and two separate 30V rails.
- (2) U590 field timebase panel.
- (3)* U410 luminance/chrominance matrixing panel. Also black-level clamping etc.
- (4) U405 decoder panel.
- (5) U585 sound panel.
- (6)* U450 i.f. detector module. Contains part of the a.f.c. circuit.

(7)* U455 sync module. Sync circuits plus VCR switching.

(8)* U440 i.f. amplifier/a.g.c. module.

(9)* U431 u.h.f. tuner. Also U430 v.h.f. tuner if fitted.

(10) U535 stabiliser panel. Contains part of the a.f.c. circuit and provides stabilised 32V, 12.7V and 12V supplies plus the 28-31V tuning voltage supply.

(11) U540 mains rectifier panel. Mains bridge rectifier (OF432) etc. plus degaussing components.

(12) U548 supply panel. Contains the BU426 chopper transistor, its BSX21 driver transistor and the TDA2581Q control i.c. The driver and chopper transformers (T549 and T525) are on the main panel. The chopper transformer has a tapped primary winding and provides a 145V output; the two secondary windings drive the 2SD350A line output transistor and feed a 30V supply rectifier on the EW panel.

(13-15) The red, green and blue output stage modules. These are mounted on the tube base panel. The RGB drives are applied to the c.r.t.'s grids, the cathodes being held at 200V by the regulator transistor TS617 (see Fig. 1).

Unfortunately the manual provides no information other than block diagrams and voltage check points for the items marked *. Philips presumably consider that these should be replaced as complete units. Fortunately they don't seem to cause trouble.

Circuit Notes

The TDA2581Q i.c. on the U548 power supply panel provides over-voltage and overload protection, plus switching to stand-by when a voltage arrives from the

remote control panel. The chopper transistor (TS204) is the one on the heatsink on this panel.

The line output stage is conventional, with a diode-split line output transformer which also supplies 7.5kV to the focus control – this is part of another little module, with the first anode controls, beside the line output transformer at the bottom left.

The field timebase employs a TDA2780Q i.c. as generator and for linearity correction. It feeds a BD327/BC337 (TS362/TS351) driver stage and in turn the BD291/BD292 (TS363/TS357) output stage – the output transistors are mounted on heatsinks on the panel. There are four 1Ω resistors in parallel providing feedback to the i.c.

The sound department is certainly elaborate by TV standards. There are two chips, a TDA2790Q which contains the intercarrier sound channel plus audio preamplifier and tone control circuitry, and a TDA2010Q which provides up to 10W of audio. Transistor TS294 provides buffering for the tape recorder output while TS293 provides a regulated 12V supply for the TDA2790Q i.c.

The decoder panel uses two i.c.s, a TDA2560 luminance/chrominance amplifier/processor and a TDA2523 reference oscillator/demodulator i.c. The panel provides separate luminance and colour-difference signal outputs.

The supply rails are complex, and the guide given in Fig. 2 should help.

Control Panels

The control panels are situated at the front of the set, near the speaker. U800 is the panel with the tuning potentiometers and channel selector i.c.s; panel U655 contains the customer controls. The panel in the can is the infra-red receiver unit – it also contains the preset brightness and colour controls. Also situated at the front are two small panels, one with the mains fuses and the other with the channel number indicator and driver. A preset next to the stand-by light adjusts the brightness of the channel number display.

Servicing

The chassis can be hinged out for servicing by releasing the catches at the top and bottom on the right-hand side.

The location of the adjustments – and panels – is shown in Fig. 3. Two controls affect the line synchronisation, R11 on the sync module and R209 on the supply module. To adjust, short-circuit pins 14 and 15 of IC201 (the TDA2581Q) and adjust R209 for an upright, stationary picture; remove short, then short-circuit points 15 and 16 on the sync module and adjust R11.

To set up the supplies, connect a voltmeter between test point M2 (adjacent to the chopper transformer) and chassis and adjust R223 on the supply panel for 145V. Then connect the voltmeter between pin 19 of the stabiliser module and chassis and adjust R198 for 12V.

If the over-voltage circuit needs setting up due to tripping or component replacements, proceed as follows: set the brightness and contrast to minimum and turn R228 (on the supply module) fully clockwise; connect meter between M2 and chassis; adjust R223 for 155V, then adjust R228 until the supply just starts to trip; switch off, turn R223 down slightly, switch on and readjust R223 for 145V.

To adjust the grey scale, connect a meter between pin 17 of the green drive module on the tube base and chassis and adjust the green first anode potentiometer (in housing next

to line output transformer) for 44V, then repeat similarly for red and blue. Finally adjust R413 and R414 (next to the chroma module) for correct whites.

If the brightness or colour is incorrect at switch on, adjust the preset R056 or R066 on the infra-red receiver module. If the volume is incorrect, adjust the preset in the control drawer.

To switch off the green, or green and blue, guns to assist with convergence, use SK2 at the top centre of the main board (next to the matrix board). This switch is rather unusual: it earths either the G – Y or the G – Y and B – Y signal inputs to the matrix board rather than switching the first anodes.

Handling the RGB Modules

Note that particular care should be exercised when handling the thick-film RGB modules on the c.r.t. base panel – rough treatment can cause intermittent contacts or breaks in the print, resulting in intermittent wrong colours etc. Philips Service recommend the following procedure when removing or refitting one of these modules: (1) bend both retaining arms slightly outwards; (2) lean the module towards the bevelled edge of the retaining arms, then lift out; (3) refit by placing the module into the edge connector at an angle, with the plain side against the bevels of the retaining arms, then gently press the module into the grooves of the retaining arms by pressing on both sides of the module – *not the centre*.

Faults

When it comes to repairing the K12, it's usually spoken of in hushed tones – basically because loud noises seem to start it tripping! Requests for help from Philips are inclined to be met by maniacal laughter at the other end of the phone... We've had the following faults on several sets however, and they seem to form something of a "stock fault" pattern. My thanks to colleague John Bourne, the one who gets lumbered with K12s in our service department.

Dead set with mains fuse(s) blown: Line output transistor TS488 short-circuit. Alternatively the chopper transistor TS204 could be short-circuit.

Dead set – tripping: D551 (BYX71-600) in the chopper

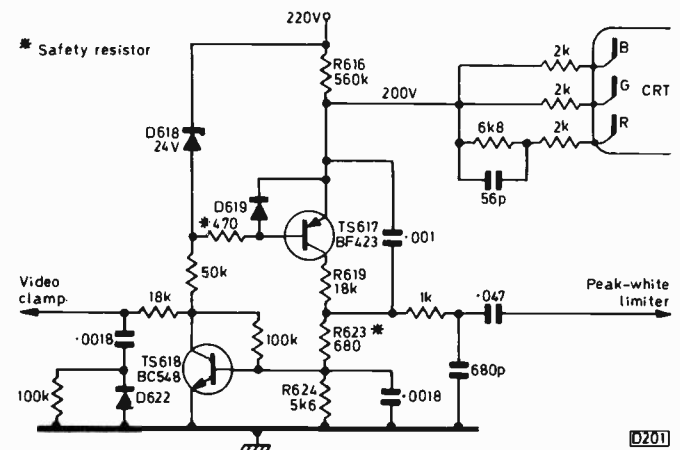


Fig. 1: The unusual c.r.t. cathode circuitry – the RGB signals drive the grids. Transistor TS617 acts as a voltage-regulating emitter-follower, holding the cathodes at about 200V since its base is biased by the 24V zener diode D618. The c.r.t. cathode currents flow via R624, R623, R619 and TS617, the voltages at various points in the chain being used to operate the peak-white limiter and to provide a video clamp reference source.

VCR Servicing

Part 4

Mike Phelan

In following the luminance signal path through the JVC HR3330 machine in the record mode last month, we reached the point where the signal has been used to frequency modulate a 3.8MHz carrier. The resultant f.m. signal next goes to the record current amplifier on the pre-rec board, and we'll examine this month the way in which the signals are recorded on the tape and how they are amplified on playback. The relevant circuitry is shown, in simplified form, in Figs. 23 and 24.

On the pre-rec board, the signal passes first to the f.m. record level preset. The purpose of this is to enable the amplitude of the signal to be adjusted so that the extreme edges of the f.m. signal fall within the linear part of the tape's BH characteristic (see Fig. 2, Part 1). This is necessary, if you recall what we said in Part 1, to ensure that the chroma signal is recorded linearly – the latter is an amplitude modulated signal, the f.m. luminance also acting as the bias for the chroma signal. The chroma signal is added to the luminance signal via the chroma record level preset, the combined signal then going to a class AB amplifier consisting of X3-X7 in a configuration that will be familiar enough to anyone acquainted with audio circuitry and equipment, i.e. an emitter-follower (X3), a complementary-symmetry driver stage (X4/5) and a complementary-symmetry output stage (X6/7).

The signal then goes two ways (because there are two video heads), each branch going to one winding of the rotary transformer that couples the signal to the rotating heads. A preset is included in one branch to provide compensation for differences in transformer and head characteristics. The signal at this point is around 2-3V peak-to-peak, the chroma signal being about 100-200mV peak-to-peak and just visible at the edges of the luminance f.m. waveform.

Record/playback switching on this particular machine is carried out by using opposite ends of the transformer windings for record and playback, transistors X8-X11 earthing the ends not in use. These transistors are switched

on by the Rec 12V and PB 12V rails. Some machines use mechanical switches and some small relays for this purpose, but we digress.

Playback Operation

Next to playback – we'll deal with the chroma side of things later, since most of the chroma circuitry is common to the record and playback modes.

As can be imagined, the signal coming from the heads on playback is minute. The initial circuitry is enclosed in a screening can therefore. X10/11 will be off, due to lack of forward bias from the Rec 12V supply, while X8/9 are turned on by the PB 12V supply, earthing the record ends of the transformer windings.

Each channel (see Fig. 24) has a trimmer capacitor and a potentiometer across the input to adjust the frequency response of the signal – to make up for differences in the Q and inductance of the heads. The trimmer is adjusted to peak the response at 4.5-5MHz, the potentiometer being adjusted for a fairly level response below this frequency. To do this, a special tape with a sweep recorded on it is required.

The signals are next amplified by IC1/X12 and IC2/X13 respectively. Even after this, the level is only about 5mV peak-to-peak! We now come to X14/15. We mentioned in a previous instalment the use of a squarewave derived from the drum servo to switch off the head not being used. This is what X14/15 do, being driven by the squarewave so that one or other is always switched on, depending on which head is in contact with the tape.

The two signal paths converge at the playback f.m. balance potentiometer, which is present to equalize the luminance signals from the two channels. From here the luminance signal goes via another preset to adjust the overall level. This is followed by several stages of amplification in IC3 (18V103). The signal can be checked at TP7 before it goes to the Y-C board: don't forget TP7 –

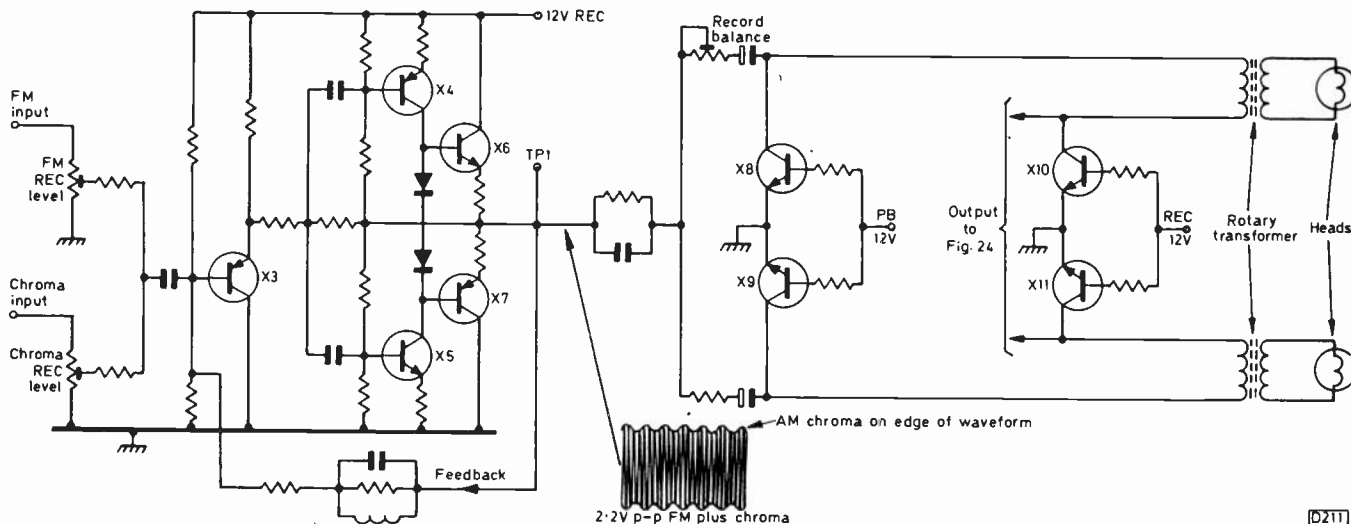


Fig. 23: The recording amplifier (X3-X7) and the video feeds to and from the heads.

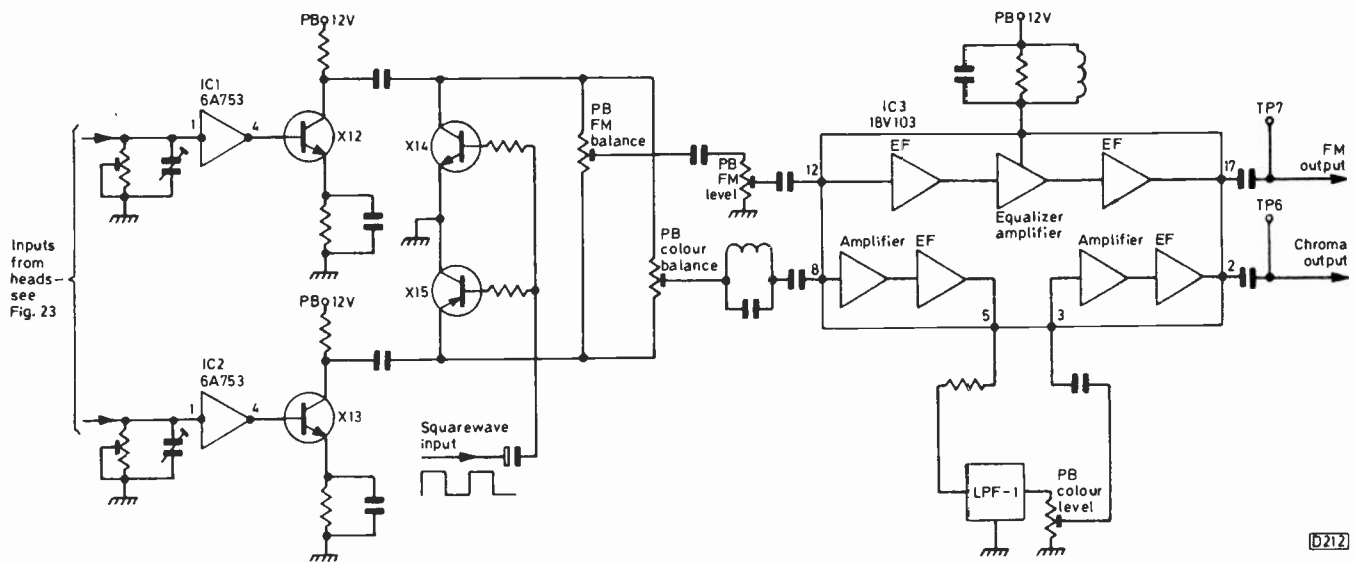


Fig. 24: Playback signal amplification on the pre-rec board.

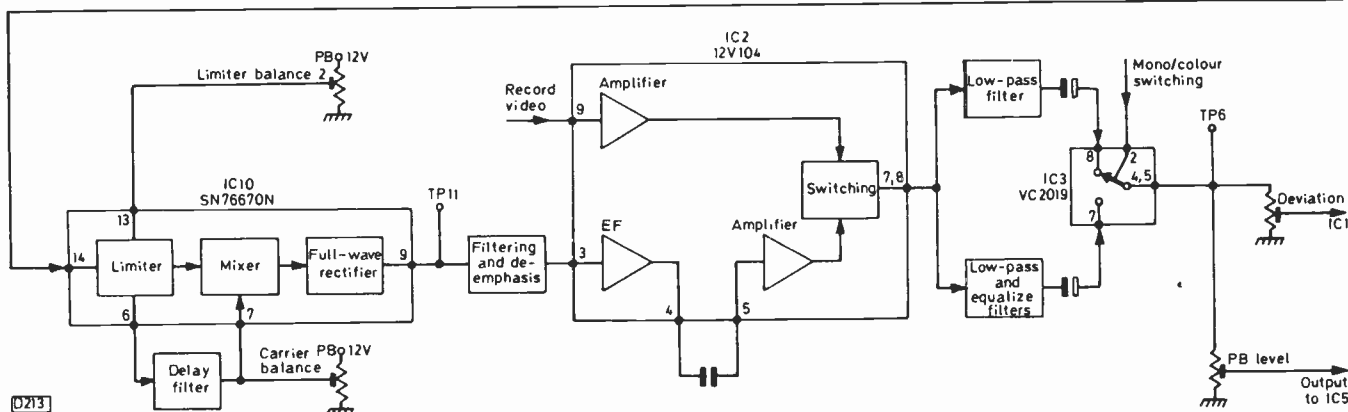
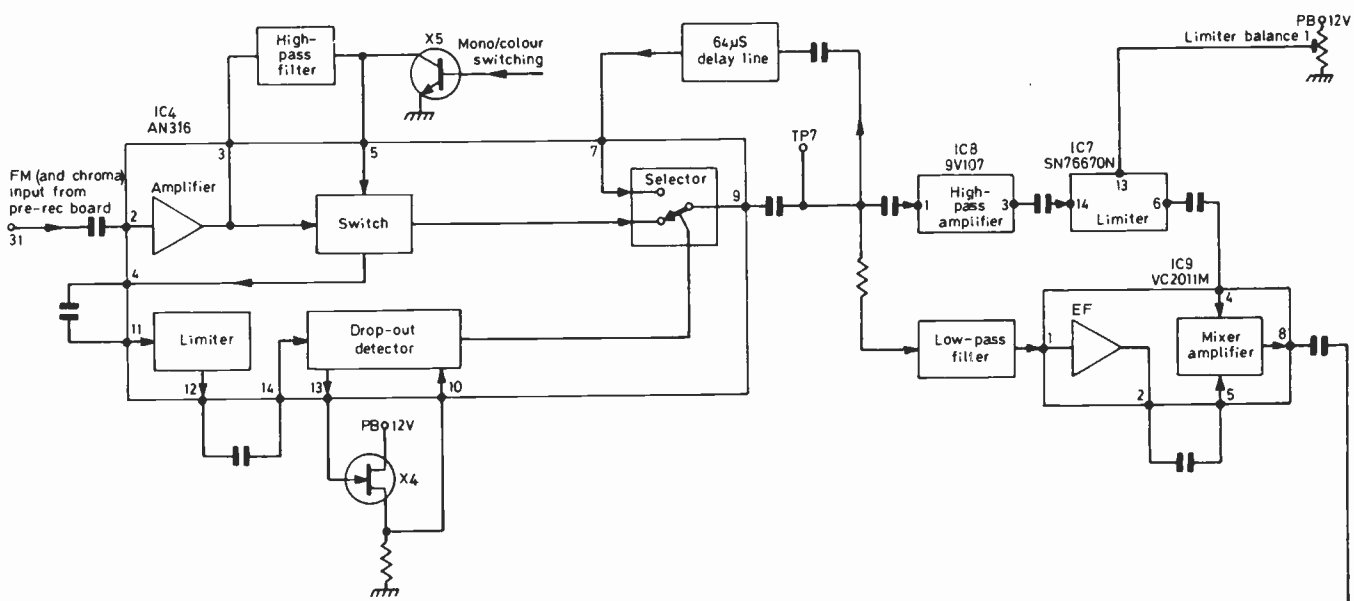


Fig. 25: Luminance signal processing on the Y-C board.

it will later be seen to be one of the most useful test points in the machine.

Another potentiometer, the playback colour balance control, is connected in parallel with the f.m. balance preset. The signal from the slider of this control goes through a similar chain to the other one, using the rest of IC3, but a low-pass filter in the circuit passes only the chrominance signal, eliminating the f.m. carrier. The filtered chroma signal goes to the Y-C board via TP6, where we'll leave it

for now to concentrate on the luminance channel.

The luminance signal enters the Y-C board at connector 31 (see Fig. 25) and goes to IC4 (AN316) which contains a stage of amplification and in addition the drop-out compensator circuit: a discrete high-pass filter between pins 3 and 5 removes the chroma component of the signal. This is shorted out by X5 in the monochrome mode to allow more of the lower sidebands of the f.m. signal through for better reproduction. Then follows drop-out compensation.


This operates in conjunction with the one-line delay line. Normally the signal passes directly from pin 9 to the following circuitry. If the f.m. signal falls to zero however, due to a portion of oxide being absent from the tape, this fact is detected and the selector switches in the signal from the previous line, via the delay line, instead.

Limiting

The next step is limiting. The problem here is that the use of a simple limiter can result in low-amplitude, high-frequency signal components being lost (see Fig. 26). So the signal is first separated by means of high- and low-pass filters, the high-frequency component only being limited to start with. The limited h.f. and the l.f. components are then added in IC9 and passed to IC10 which provides further


limiting followed by demodulation. The latter process is carried out in conjunction with a delay filter: the basic idea is that the mixer adds direct and delayed signals to produce a symmetrical signal whose pulse width depends on frequency. After full-wave rectification the carrier is filtered out and the signal de-emphasized: we are now left with video.

The following section of the circuit, around IC2 and IC3, is also used in the record mode and was described last month. The processes involved consist of amplification and frequency response limiting. From the playback level control the signal goes to IC5, which enhances the h.f. component to make up for the loss of definition above 3MHz and also adds the chroma to the luminance signal. Exactly how this is done, and other exciting things, will be our subject next month. Fig. 26 will appear next month.

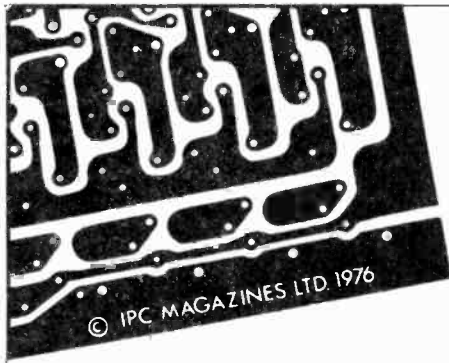

All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

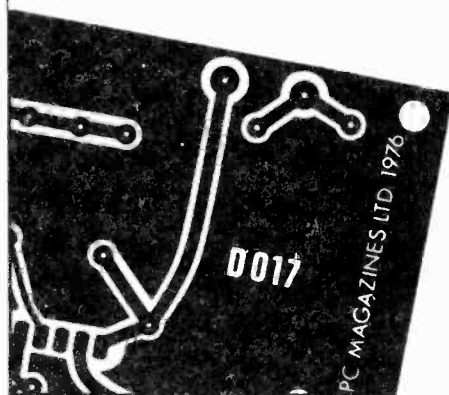Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.



TELEVISION READERS PCB SERVICE

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£3.85 per set
March 1977	Teletext Decoder Power Supply	D022	£3.75
May 1977	Teletext Decoder Input Logic	D011	£12.50
June 1977	Wideband Signal Injector	D031	£1.00
June 1977	Teletext Decoder Memory	D012	£10.50
July/Aug 1977	Teletext Decoder Display	D013	£11.00
September 1977	Teletext Decoder Switch Board	D021	£1.75
April/May 1978	CRT Rejuvenator	D046	£3.00
October 1978	Colour Receiver PSU Board	D052	£4.00
January 1979	Colour Receiver Signals Board	D053	£10.75
February 1979	Commander-8 Remote Control System	D054/5	£6.00 per set
March 1979	Colour Receiver Timebase Board	D049	£17.13
July 1979	Colour Pattern Generator	D062	£14.50
		D063	£9.15
September 1979	Teletext Decoder Options Board	D064	£8.50
August 1979	Teletext Decoder New Mother Board	D065	£6.00
August 1979	Simple Sync Pulse Generator	D067	£4.00
September 1979	New Teletext Signal Panel	11331	£8.00
October 1979	Teletext Keyboard	D057	£3.50
October 1979	Teletext Interface Board	D058	£5.00
November 1979	Colour Receiver Remote Control	D066	£5.00
January 1980	Remote Control Preamplifier	D061	£3.75
February 1980	Teletext/Remote Control Interface	D070	£9.50
February 1980	LED Channel Display	D071	£4.00
March 1980	Improved Sound Channel	D072	£3.25
May 1980	Monochrome Portable Signals Board	D074	£6.25
June 1980	Monochrome Portable Timebase Board	D075	£7.75
July 1980	Monochrome Portable CRT Base Board	D076	£1.00
Sept/Oct 1980	New CTV Signals Panel	D077	£9.50
January 1981	Small-screen Monitor Board	D078	£8.50
December 1980	Video Camera Pulse Generator Board	D079	£4.50
December 1980	Video Camera Video/Field Timebase Board	D080	£5.50
January 1981	Video Camera Power Supply Board	D082	£2.00
January 1981	Video Camera Line Timebase/H.T. Board	D083	£4.00
Feb/March 1981	Video Mixer	D086	£4.50
May 1981	Switch-mode Power Supply	D089	£6.75
June 1981	Simplified Signals Board	D088	£10.00
August 1981	Timebase board	D091	£9.00
August 1981	CRT base board	D087	£2.00
September 1981	Remote Control Preamplifier	D085	£1.00
September 1981	Remote Control Interface	D090	£7.00
September 1981	Channel Display Module	D095	£1.00
October 1981	Remote Control Transmitter	D084	£4.00
October 1981	TV Pattern Generator	D094	£6.50

To:— Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____

ADDRESS _____

Post Code _____

Linear Ohmmeter

William E. Harrison

IF your's is digital, read no further: this design is for analogue meter types – those suffering from cramp in the Ohms scales. Making resistance checks accounts for a great deal of time in servicing work, so anything that makes life easier must be of value. The design uses a junction-f.e.t. operational amplifier as an inverting amplifier and a meter with decade scaling to read ohms like volts.

Circuit

The circuit is shown in Fig. 1: in this type of arrangement, the value of the operational amplifier's input resistor, i.e. the resistor connected to pin 2, is the meter's full-scale resistance reading. The resistor being tested is connected in position X: since it provides feedback, its value determines the gain of the amplifier. When the values of the input and feedback resistors are equal, the operational amplifier's gain is unity and the meter reads full scale.

To prevent operational amplifier overloading, the minimum input resistor value is 1k Ω . In most circuits of this type, 0-1k Ω is the lowest range. This disadvantage is overcome by using a second operational amplifier to boost the gain on the lowest ranges by ten and a hundred. The meter has ranges in decades from 0-10 Ω to 0-10M Ω , plus 0-20M Ω for TV work. As the absence of a test resistor in position X would give full gain due to the open-circuit feedback loop, a push-to-read push-button switch is connected across the test resistor terminals. This prevents

meter activity until the reading is made.

The 1V stabilised line obtained at the emitter of Tr1 supplies a reference input for the amplifier, the buffer transistor coping with current variations as the meter ranges are switched.

The circuit includes the meter and its associated resistors – the values of these must be selected to suit the meter movement used. The values shown are suitable for use with a 100 μ A meter.

Construction

Construction is not critical and is left to individual choice. Every care must be taken to avoid possible leakage paths however, since high-resistance ranges are included. The accuracy of the meter depends on the ranging resistors used – they should be close-tolerance types, wired directly to the switch wafers. The 10M Ω resistor may have to be an ordinary one, as high-stability types of this value are rare. The operational amplifier may be the single TL081 type, or alternatively the dual TL082 type can be used (RS stock numbers 304-223 and 304-217 respectively).

To set up the meter, short-circuit the input pins (pin 2) of the operational amplifiers and adjust the 22k Ω offset trimmers for a null reading. Then switch to the 100k Ω range, connect a known accurate 100k Ω resistor in the test position, and adjust the meter's series trimmer for full-scale deflection.

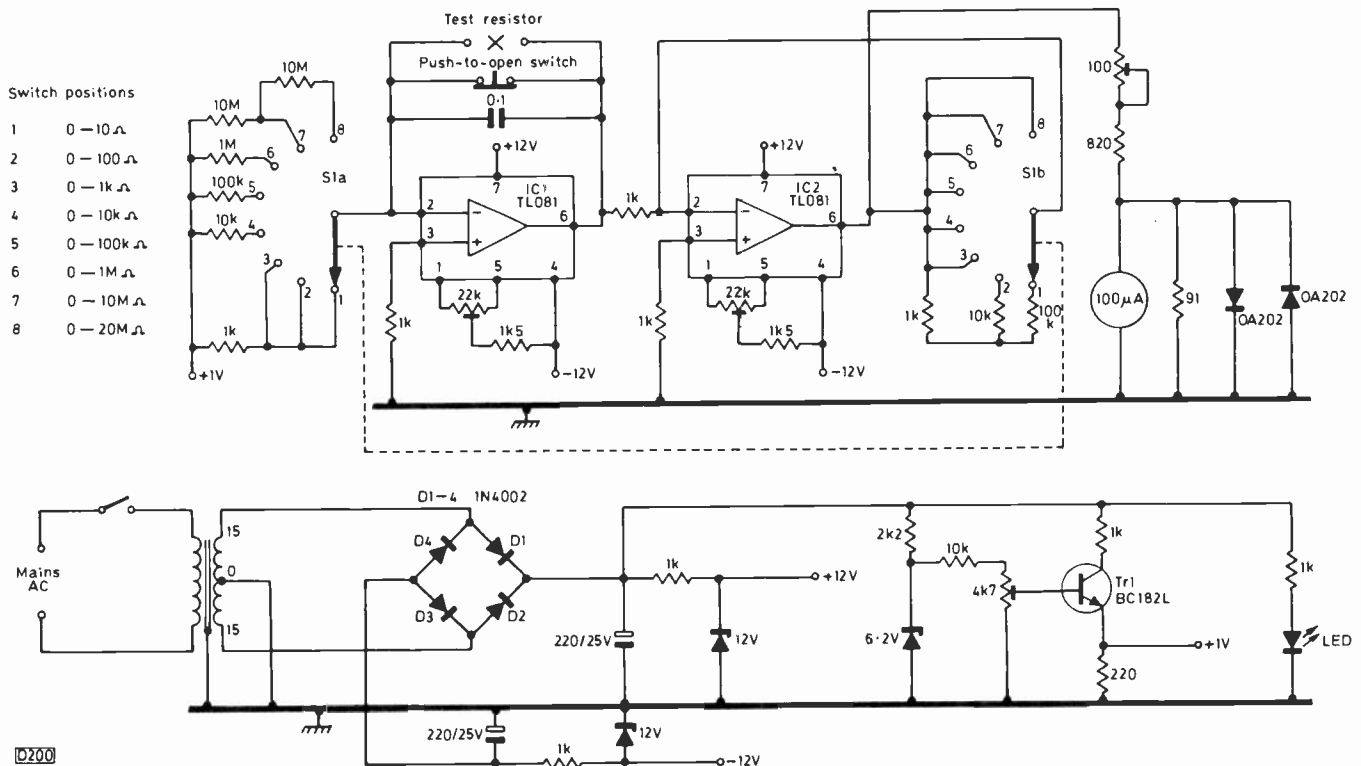


Fig. 1: Circuit diagram of the linear ohmmeter. The mains transformer is rated at 3VA, e.g. the RS 207-841 with the secondary windings connected in series. The wafer switches are of the make-before-break type. Use metal-film H.S. resistors for range selection. The values of the resistors in the meter circuit depend on the movement used. Those shown are suitable for use with a 100 μ A meter – any 0-10 meter can be used, up to say 1mA f.s.d. The diodes in parallel with the meter provide protection against overloading.

TV Receiver Design: The Decca/Tatung 120 Series

Part 2

Ray Wilkinson

IN Part 1 last month the basic considerations behind the design of the Decca/Tatung 120/130 series chassis, also the circuitry used, were outlined. The subject this month is the colour decoder and the RGB output stages.

The Decoder

Most of the PAL decoder circuitry is incorporated within a μ PC1365C integrated circuit, which was initially produced by NEC and is now also available from Plessey. Several setmakers use it. The resulting decoder is economical, the i.c. itself has a good reliability record, text signals can be added, and a Secam add-on i.c. is available.

The full circuit of our version of this decoder is given in the service manual. For the present purposes, block diagrams are the most suitable means of illustrating the decoder's operation.

A simplified block diagram of the i.c. is shown in Fig. 5. Let's follow the chrominance signal path first. From the bandpass tuned circuit, the chroma enters the i.c. at pin 11. The initial processing consists of a.c.c. (automatic chrominance control) and burst gating. The latter extracts the burst signal for application to the subcarrier regenerator, at the same time removing the burst from the chroma signal feed to the following colour control amplifier. The colour and contrast controls track together to avoid

saturation changes when the contrast control is adjusted. The amplified chroma signal emerges at pin 9 and passes via Q501 to the usual PAL delay line circuit. This separates the U and V components of the chroma signal, driving the appropriate synchronous demodulators at pins 24 and 25. Proportions of the R - Y and B - Y colour-difference signals are matrixed to form the G - Y signal, the three colour-difference signals then being matrixed with the luminance signal to obtain RGB outputs at pins 26, 28 and 27 respectively. Line and field flyback blanking is also carried out in the RGB matrix circuitry, using pulses stripped from the sandcastle pulse (see Fig. 6).

The subcarrier regenerator and PAL ident/switch blocks produce the reference subcarriers required by the synchronous chroma demodulators. A signal is also produced in this section to disable the colour killer when acceptable chrominance is present.

The black-level feedback clamp is shown in greater detail in Fig. 7. The luminance signal enters the i.c. at pin 5, passing to an amplifier whose d.c. operating point is controlled by the voltage at pin 3. The voltage from the contrast control is fed in at pin 7, adjusting the amplitude of the luminance signal. The output from the contrast control amplifier is sampled during the back porch period by a sampling circuit which is switched on by the burst gate pulse. The level of the sample is compared with the d.c.

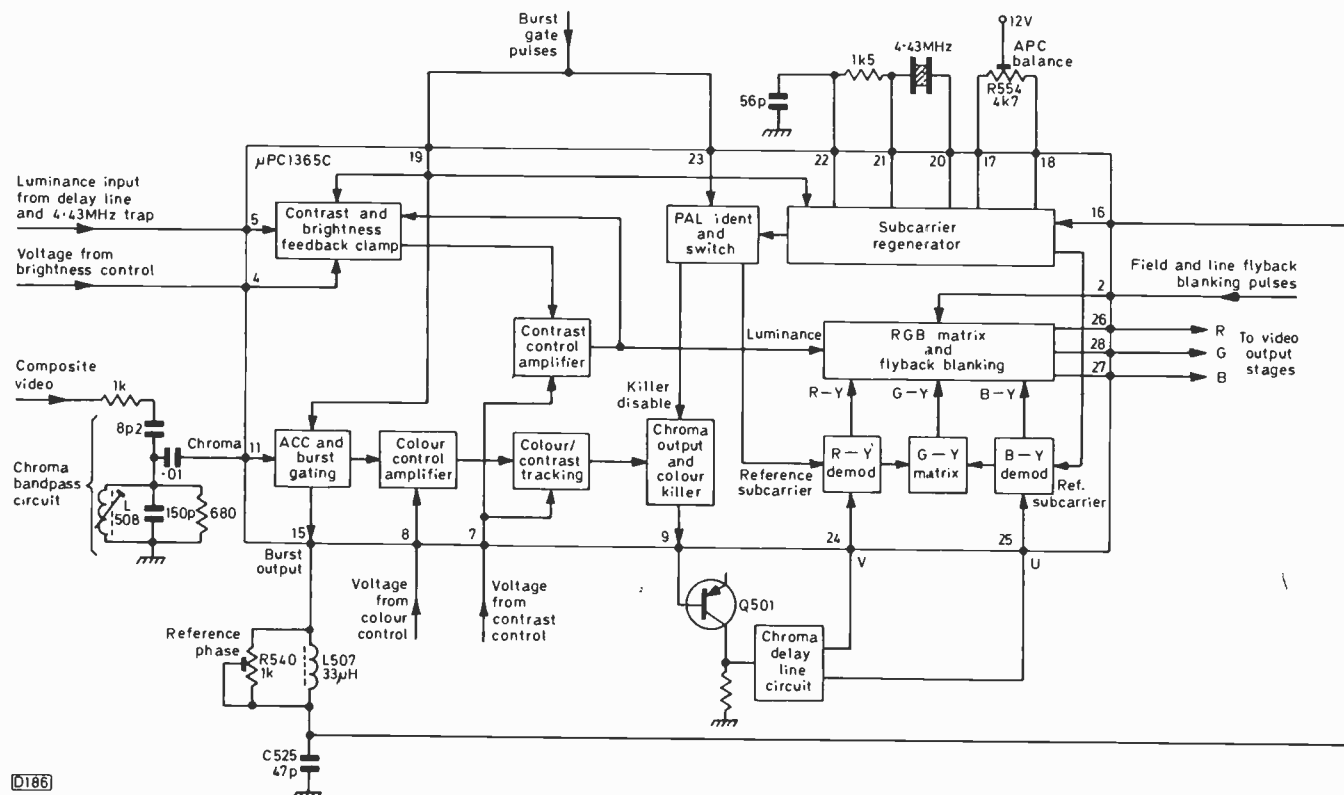


Fig. 5: Simplified block diagram of the decoder.

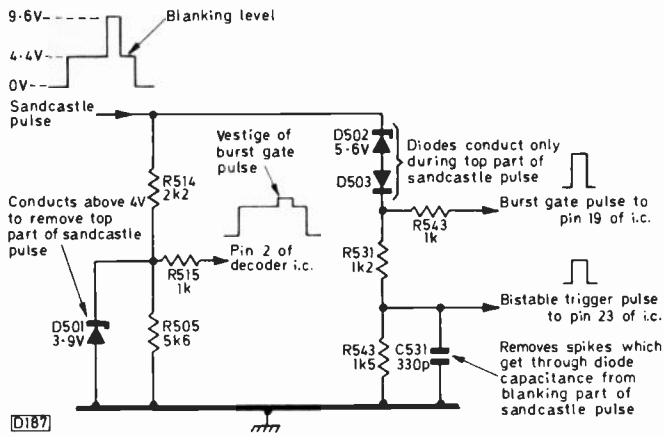


Fig. 6: Sandcastle pulse separating circuit.

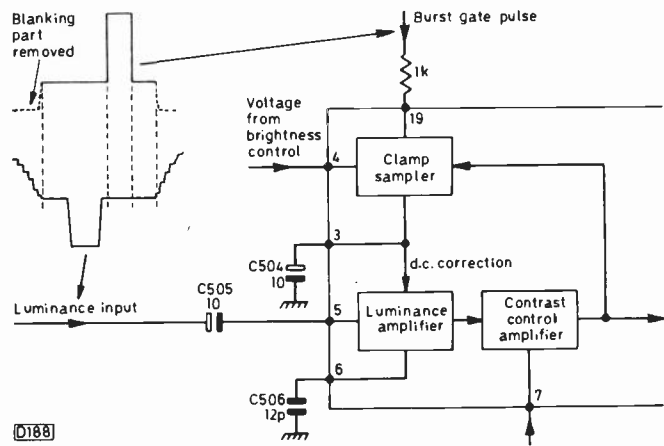


Fig. 7: Black-level clamping. C506 provides frequency response correction.

voltage from the brightness control, the resulting voltage produced across C504 being used to correct the luminance amplifier's d.c. conditions. The output from this section of the i.c. thus consists of a luminance signal whose black level has been clamped to a voltage determined by the setting of the brightness control and whose amplitude is determined by the setting of the contrast control.

Fig. 8 shows the operation of the a.c.c. circuit. The idea is

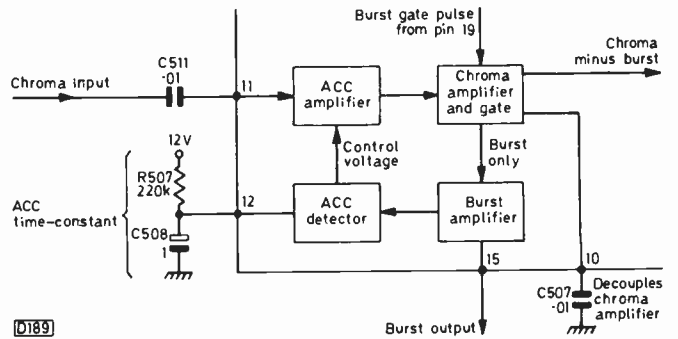


Fig. 8: The a.c.c. loop.

to keep the amplitude of the burst signal at pin 15 and the chroma signal fed to the colour control amplifier constant. For this purpose the a.c.c. detector produces from the bursts a d.c. voltage to control the a.c.c. amplifier.

Reference Oscillator and Ident

The subcarrier regenerator (4.43MHz reference oscillator plus its phase-locked loop) and PAL ident/switch sections are shown in greater detail in Fig. 9. This is all conventional, the crystal oscillator being phase-locked by a d.c. voltage from the a.p.c. (burst) detector. The a.p.c. balance potentiometer does the initial setting up.

The R - Y reference signal must be switched through 180° on alternate lines, and this switching must be in the correct phase. The H/2 detector compares the 7.8kHz ident signal ("swinging burst") from the a.p.c. detector with the output from the H/2 bistable (the bistable is triggered by the burst gate pulses). If the two signals applied to the H/2 detector are in phase, the d.c. voltage at pin 13 falls below 6.2V. The level detector uses this fact to recognise that the amplitude of the chrominance/burst signal is adequate and that the bistable is operating in the correct phase. It then sends out a signal to disable the colour killer, allowing the chroma signal output to appear at pin 9. If the amplitude of the burst signal is poor or the bistable is operating in the wrong phase condition, the d.c. voltage at pin 13 rises to about 7.2V. The killer then blocks the chroma signal and the bistable is inhibited until it comes back into phase.


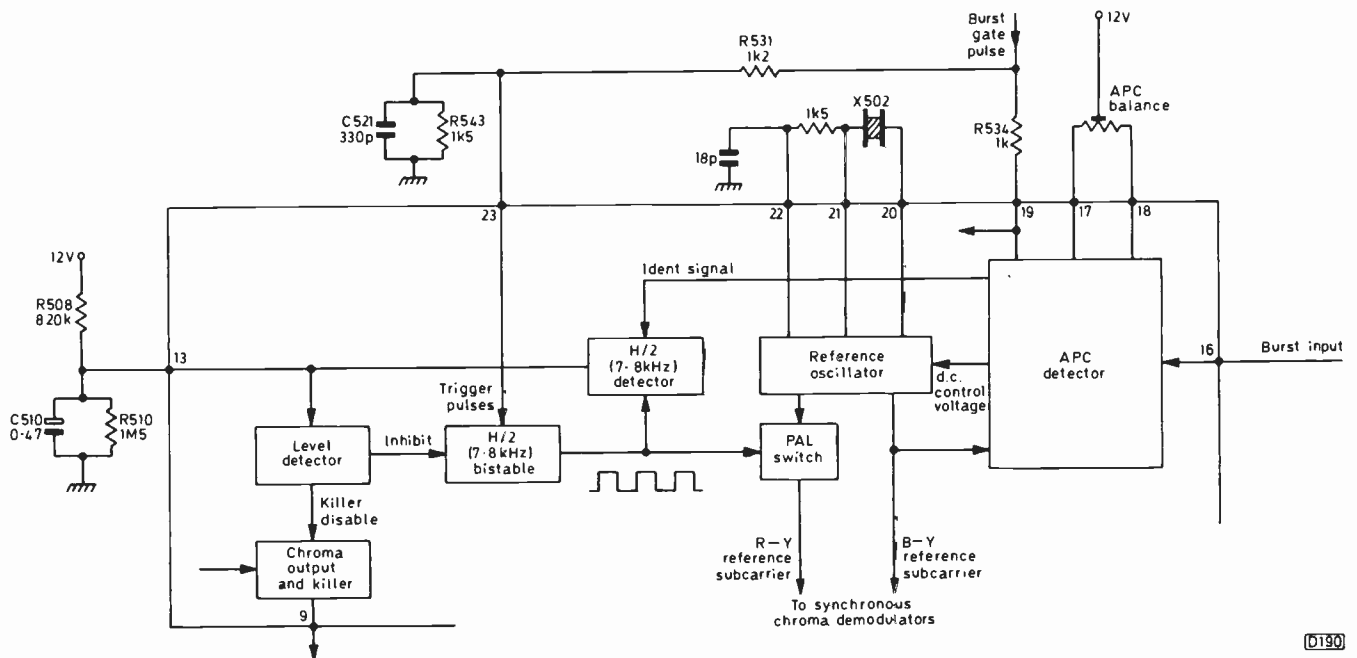


Fig. 9: The reference oscillator and ident system.

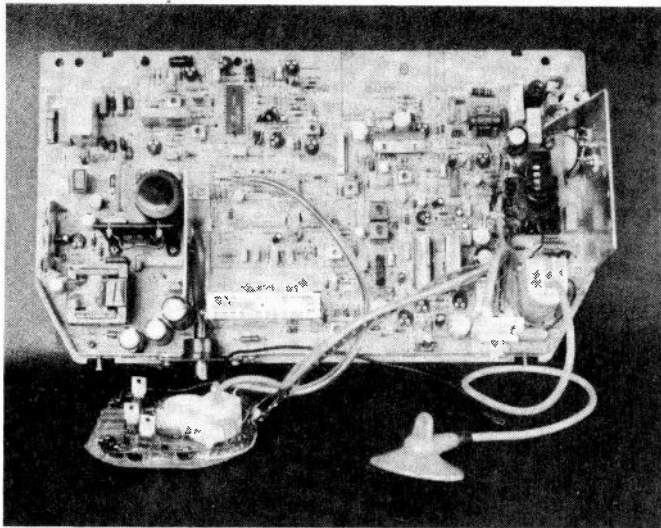

The Decca/Tatung 120 chassis.


To disable the colour killer externally, you simply dab a resistor of about 47kΩ across R510 to reduce the voltage at pin 13 below 6.2V.

RGB Output Stages

Now to the RGB output stages. During the development of the chassis we carried out an investigation into video output circuits, looking particularly at the display of text information. We wanted to establish what was important in getting the best text display. We found that due to the limitations of the tube, i.e. spot defocusing at high beam currents, there was no advantage to be obtained from maintaining the video amplifier bandwidth beyond about 4.5MHz. What was important, as you might expect, was a good phase response which, together with the frequency response, needed to be maintained over the full black-to-white range. This meant a smooth roll-off to the frequency response, with no fancy peaking circuits at the output – these tend to cause nasty overshoots and ringing, which the tube can't resolve and displays as a smear.

The choice of video output stage load resistor value is always a compromise, bearing in mind the c.r.t.'s input capacitance. A low-value resistor gives a wider frequency response but higher dissipation. If the resistor's value is increased to reduce the dissipation, the frequency response goes for a chop. We chose 12kΩ as a reasonable value.

Fig. 10 shows most of the components in the circuit we finally developed. We decided upon a cascode arrangement for a number of reasons, the most important being: (1) No input fringing is needed to compensate for the output transistor's collector-base capacitance, since this transistor is within the feedback loop (R226). (2) In some earlier circuits we tried, the compensation had to be varied according to the drive setting in order to keep the frequency response constant. (3) No temperature compensation is needed for the output transistor, again because it's within the feedback loop. With a single transistor output stage, the variation in the base-emitter voltage with temperature can cause noticeable changes in the black level at the tube's cathodes. (4) Temperature compensation for the low-voltage transistor is easily done using low-voltage, low-power devices. (5) Since the output transistor's collector-base capacitance is within the feedback loop, variations in this characteristic from one device to another are unimportant and the choice of output transistor type is not so restricted. With a single-transistor output stage, we found that

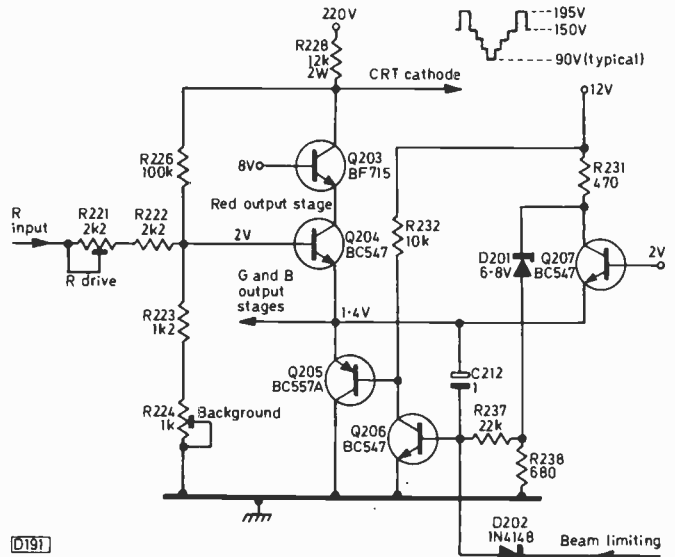


D191

Fig. 10: Video output stage – simplified circuit. Q205/6/7 and their associated components are common to all three (RGB) output stages.

fractions of a pF difference caused noticeable changes in the frequency response.


The cascode configuration is widely used and should be familiar to most readers. Taking the red output stage as our example, Q204 is connected in the common-emitter mode to provide current gain, driving Q203 which is connected in the common-base mode to provide voltage gain. The stage gain is the ratio of the value of the feedback resistor R226 to R221 and R222, with R221 made variable to provide amplitude (drive) adjustment. Output d.c. level adjustment is provided by R224, which is set up for a black-level output voltage of 150V. Q203's base is held at about 8V by means of a decoupled potential divider fed from the 12V rail.

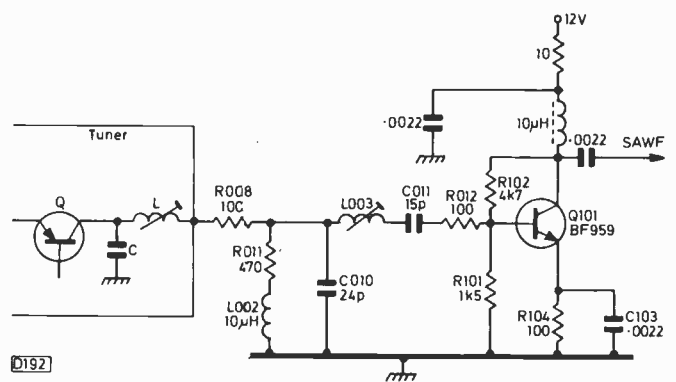The rest of the circuit provides temperature stabilisation and d.c. compensation for Q204 (and the corresponding transistors in the other two channels). Q207's emitter matches these three and as the temperature varies they all track fairly closely. The feedback via D201, R237, Q206



D192

Fig. 11: Coupling the tuner to the SAWF.

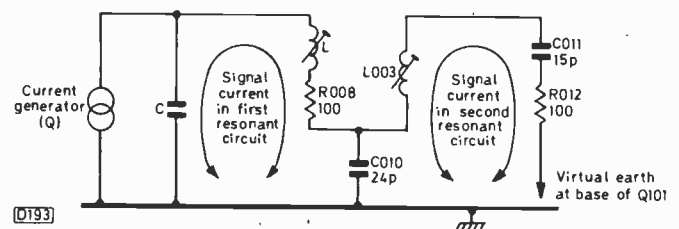

D193

Fig. 12: Principle of the coupling circuit.

and Q205 provides a stable d.c. at low impedance for the emitter of Q204 and the corresponding transistors in the other two channels. C212 maintains the h.f. stability of the loop.

The chassis has a conventional beam-limiter circuit acting on the contrast control. If a fault occurs however, or the first anode voltages are wrongly set, this circuit can run out of range. It's common practice therefore to add a beam-quenching circuit which cuts off the tube cathodes to avoid potential damage to the tube. As the beam current rises, the voltage at the cathode of D202 falls until, at a predetermined level, D202 conducts, turning Q206 off. Q205 and Q204 (also the corresponding transistors in the other two channels of course) quickly follow suit. The voltages at the collector of Q203 etc. then rise to h.t., taking the c.r.t. cathodes up into the blanked region. When the cathodes are cut off there's no beam current, and unless something is done about this the whole system will rapidly come on again. D202 charges C212 to hold the circuit in the cut-off state.

The video output stage d.c. levels are accurately set at the chassis test point, only small background adjustments being necessary at final test to take into account tube tolerances. We recommend adjusting only two of the background presets - in the direction away from blanking. (The first anode controls provide a third degree of freedom.) This avoids reducing the blanking capability with the brightness control range.

Although the collector-base capacitance of the output transistors is not significant, since the capacitance is within each output stage's feedback loop, the capacitance of the feedback resistor itself is important. It was necessary to choose a component that has low capacitance, and to take care with the board layout in the vicinity of this resistor. For the same reason, the dressing of the leads also has to be carefully controlled in production.

Tuner Coupling

A recent article in *Television* (September 1981) went into the subject of tuner coupling, so it might be of interest to explain the system we use. Fig. 11 shows the relevant circuit (UK version), with part of the tuner's output circuit included. In Fig. 12 the circuit is redrawn to make the action clearer.

Transistor Q in the tuner forms a current source, the d.c. return for its collector being via R011 and L002. You can see that from the a.c. point of view the set up consists of two resonant circuits. Both are tuned to the same frequency, with bottom-capacitance coupling by means of C010. L and C, with R008 to determine the circuit Q, form the first tuned circuit. L003, C011 and R012 form the second tuned circuit. The currents in both circuits flow via C010, whose value is selected to get critical coupling between the resonant circuits for a broad-topped bandpass response.

So how do we get the signal out? Since the emitter of Q101 is decoupled and there's feedback between the collector and base, the transistor's base is at "virtual earth". The signal current flowing through R012, i.e. the current in the second resonant circuit, thus flows into this low impedance. Q101 drives the bandpass shaping SAWF from its collector, the stage gain being set by the ratio of R102 to R012.

Next Month

In the concluding instalment next month we'll be dealing with the switch-mode power supply.

next month in

TELEVISION

● SERVICING FEATURES

The emphasis next month will be on servicing matters. John Brown deals with the power supply arrangements used in the Skantic 20AX chassis. This employs the now famed Siemens self-oscillating chopper to generate the stabilised h.t. supply, so the notes should prove helpful with several other chassis that use this system.

Bob Walker reports on his experiences with the Thorn 2000 chassis. Conversion to single-standard operation simplified matters and removed many possible sources of trouble. The set seems to be going so well that the addition of remote control is contemplate.

S. Simon is back the *Practical TV Servicing*, this time giving advice on tripler troubles and what to look for.

Plus fault reports, VCR servicing and so on.

● DEVELOPMENTS

MAVICA for a start. That stands for Magnetic Visual Camera, and is the latest development to come from Sony. The idea is to integrate yet another activity with TV, this time photography.

Also a look at some of the developments that have been taking place in the field of high-definition TV systems.

● VIDEO

Why not make your own programmes? Malcolm Burrell decided on a space theme, and gives a vivid account of how various effects, both sound and visual, were produced.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the January issue of TELEVISION (70p), on sale December 23rd, and continue every month until further notice.

NAME.....

ADDRESS.....

.....
.....

Servicing Luxor 110° Hybrid CTVs

Part 2

Mike Phelan

LAST month we dealt with the power supplies and the signal circuits up to the decoder. Time next to take a look at the colour-difference amplifier panel, which also houses the luminance output stage and two transistor luminance amplifier stages (Q401/2 – see Fig. 3).

The CDA Panel

Q401 is the luminance delay line driver. After passing through the delay line, the luminance signal is fed to the emitter-follower Q402 which provides matching to the low-impedance contrast control. An interesting little network (D413/R416/R426) is included here to cancel the line sync pulses at the emitter of Q402 so that adjustment of the contrast control doesn't affect the black level. The luminance signal is then a.c. coupled by C410 (0.1 μ F) to the control grid of the PL802 luminance output valve. A two-diode driven clamp is used in the control grid circuit, while a conventional transistor flyback blanking arrangement is included in the cathode circuit. Between the anode of the PL802 and the c.r.t. cathodes there's a simple diode beam limiter network (D404/C429/R446). It's non-adjustable – probably the best sort, being simple and immune from itchy screwdrivers. There are no cathode drive presets.

Faults in this area are usually straightforward. No luminance with a very dark raster normally means that either Q401 or the delay line is short-circuit or the flyback blanking transistor Q403 is open-circuit. A faulty delay line can also produce a multiple-ghost effect on the picture. When Q402 develops an emitter-base short-circuit, the contrast is reduced and the definition impaired. The PL802's anode load resistor R444 (2.7k Ω) goes open-circuit to give a bright, blank raster.

The colour-difference signals are amplified by three

EF184 valves which, surprisingly enough, rarely fail. The signals are then a.c. coupled to the c.r.t. grids, with more two-diode driven clamps in each feed. The clamp diodes (D406, D407, D408, D409, D411 and D412) give a fair amount of trouble, the symptoms ranging from shading or coloured bands down one side to complete loss of clamping on one colour – this is best seen on a test card, the monochrome part of the picture altering in colour when the saturation is advanced. The BY206 is a suitable replacement, and the diodes should be renewed in pairs.

Grey Scale

The CDA panel also carries the c.r.t. first anode controls – on a subpanel mounted at one end – but alas there are no switches, and you can't pull off the c.r.t. cathode leads as in a set with RGB drive. Turning the appropriate potentiometers to minimum is the only convenient way of turning the guns off. The two potentiometers at the other end of the board, R458 and R461, provide a fine, albeit limited, adjustment for the highlights. They set the green and blue clamp voltages. Inability to set up the grey scale within the range of these adjustments usually means that the c.r.t. is faulty. Either an A66-140 or an A66-410 can be used as a replacement – the "quick heat" facility of the latter is no advantage however, and a 33 Ω 2W resistor must be connected across pins 1 and 14 if the A66-410 is used.

Field Timebase

The field timebase employs a PC92 triode in a blocking oscillator circuit and a PL508 output pentode. There are also a couple of transistors – the sync pulse amplifier Q752 (BC147B) and Q753 (BFR39) in the output stage automatic bias stabilisation circuit (see Fig. 4). A

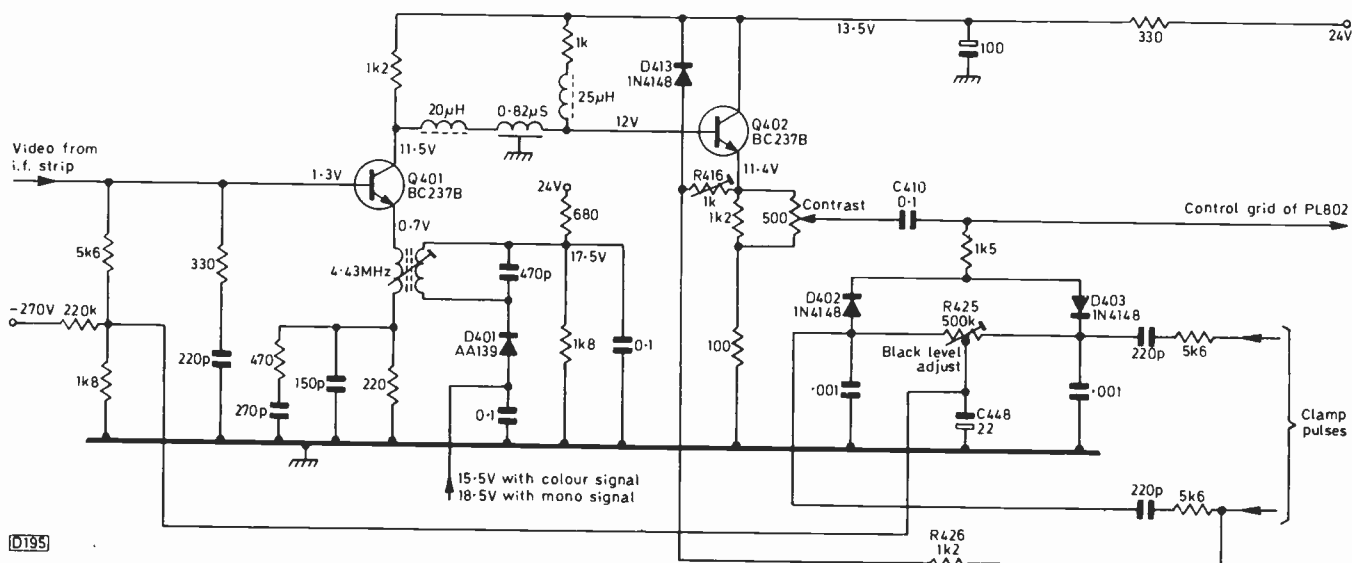


Fig. 3: The luminance delay line driver and emitter-follower circuits. D402/3 form a two-diode driven clamp in the PL802 luminance output pentode's control grid circuit. One of the clamp pulses is also used to switch D413 on to remove the sync pulses from the feed to the contrast control – when D413 switches on, Q402 switches off.

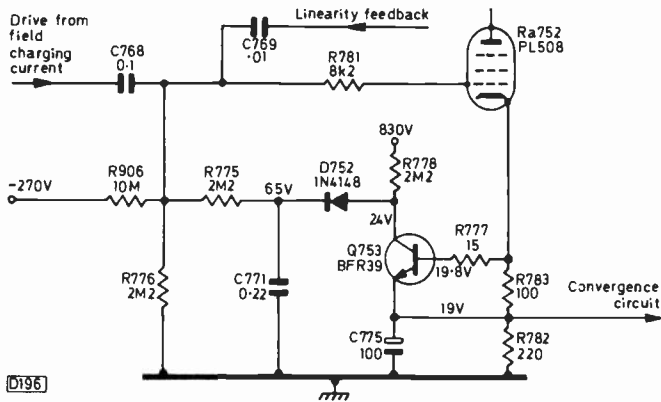


Fig. 4: The auto-bias circuit used in the field output stage. During the forward scan Q753 is conductive and D752 is cut off. When the PL508 field output pentode switches off during the flyback period, there is no voltage across R783 and Q753 switches off. D752 is then forward biased via R778, and C771 charges to 65V.

characteristic of the latter arrangement is the tendency for the whole thing to go into oscillation if the height control is increased slightly above the normal setting – this produces a violent field bounce. Cures are to connect a 390kΩ (1W) resistor and a 1μF paper capacitor between pin 1 (anode) of the PC92 and chassis, or a 250-500μF 25V electrolytic from the cathode of the PL508 to chassis.

No field sync usually means failure of Q752 – the SN76532 sync separator/line oscillator i.c. rarely gives any trouble. The PC92 is occasionally responsible for no field scan, but more often the culprit is the PL508. Lack of height or very poor linearity should lead one to suspect the bias switch transistor Q753 and the associated diode D752.

Sometimes the printed board becomes conductive between the height control and chassis, quickly leading to the formation of a large hole. R771 (2.2MΩ), which is in series with the height control, also increases in value with age, causing lack of height.

Line Scan

The line output stage (see Fig. 5) is similar to those used in several other continental chassis of the time, e.g. the Kuba 110° hybrid chassis, and it must be stated at the outset that the line output valve must be a PL519, not a PL509, and one of reputable make at that. The genuine PL519 has its cathode and suppressor grid brought out on separate pins – the same pins are used on the PL509, but the electrodes are connected together internally. This also applies to some valves we've come across marked PL509/519. If one of these is fitted, R901 (10kΩ) between the suppressor grid and the 24V rail will burn out.

The high-value resistors in the width circuit cause little trouble – lack of width is more often due to R901 or the screen grid stopper resistor R908 having increased in value.

There's a secondary, rapid-acting width/e.h.t. feedback loop, D904/R912/C903/C902/R907, which has a much shorter time-constant than the main control loop and keeps the e.h.t. constant during rapid changes in scene brightness. In cases of poor e.h.t. regulation, check D904 (BYX10) and the clipper diode D902 (E800 C5), either of which may be open-circuit. Failure of either the tripler or the line output transformer in this chassis is very rare indeed.

Focus troubles can be caused R951 (27MΩ) or R952 (39MΩ) – these resistors are in series with the focus control, at either end – or by the screened cable being short-circuit

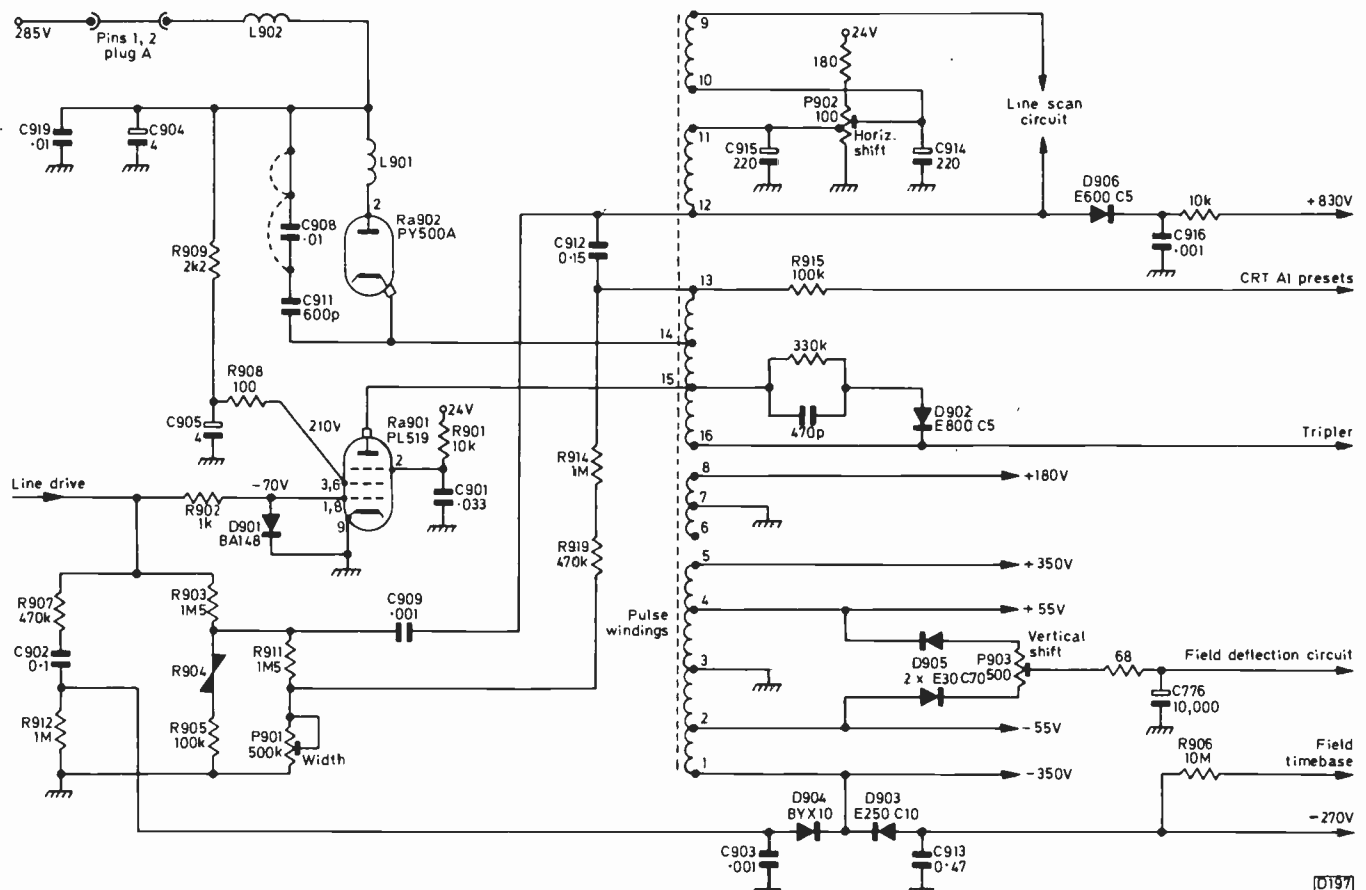


Fig. 5: The line output stage. There are two feedback loops in the PL519 line output valve's control grid circuit – via C909 and via D904 (the latter loop is fast acting). C912 is the boost reservoir capacitor.

because someone has not replaced it in its clip, the result of this being that it has cooked against the PL508.

A fairly common fault on this chassis is heavy loading on the line output stage, with a very small raster and low e.h.t. Before starting to disconnect things from the line output transformer, examine the corner correction transducers L852 and L853 on the raster correction panel for signs of burning. An occasional culprit is the EW correction transducer L858 (the blue one), which runs very hot if faulty. Variations in raster shape (the corners folding in) or corner convergence with changes in brightness can be cured by replacing C852 (220 μ F), C855 (220 μ F) and C853 (25 μ F) on this panel. If the line linearity coil (L851) burns out frequently, see the note last month on the l.t. supply.

Failure of one half or the line scan (i.e. a keystone-shaped raster) is often due to the fact that one of the windings on L852, L853 or L858 is dry-jointed. The first two can be repaired but L858 is encapsulated in resin.

That summarises the line scan department. Between the line oscillator i.c. and the line output stage there's a transistor (Q751, BF292C) line driver stage on the field timebase panel.

Convergence

The convergence circuitry is rather complicated, as you'd expect with a 110° delta-gun tube, a control being provided to remove almost every sort of error. Stock faults are few, the most common being failure of the static blue lateral convergence control P803 (470 Ω). Breaks in printed tracks, and absence of red/green corner convergence on either the right- or left-hand side due to Q805 or Q804 (both BC147) being defective, are other fairly frequent faults. Most faults however require the standard approach of noting which controls work and which ones don't or have reduced effect, followed by cold checks on the relevant passive components.

The functions of the convergence controls are shown on

a diagram inside the back cover, but the controls on the raster correction panel may require some explanation. There are four small presets in a row, one large preset, one small coil, one large coil, a transducer with a movable magnet and a coil with two magnets – this one is for line linearity. The adjustable transducer should be set for the straightest horizontal centre lines consistent with parallel sides to the raster; the large coil is the NS phase and the large potentiometer the NS amplitude control; the small potentiometer below it is the EW amplitude control – adjust for straight sides.

The remaining four controls are for convergence and should be adjusted as follows. Connect pins 5/6 to 7/8 on the raster correction panel and remove the plug nearest the raster correction panel on the convergence board. Adjust the balance coil (on top of the scan coils) for best R/G horizontal convergence in the centre, then remove the short on the raster correction panel and adjust P852 (next one down from the EW potentiometer) for the same effect. Replace the plug and carry out the convergence procedure, then adjust the remaining two potentiometers for best horizontal corner convergence at the top and bottom. Both these controls provide differential adjustment between the right- and left-hand corners. The small coil (L857) provides a fine adjustment of the top and bottom corners.

P751 on the field timebase board provides adjustment to straighten the centre verticals. It may be necessary to carry out the convergence and raster correction adjustments several times for best results, but these should then be very good.

Audio Department

Finally, a brief note about the audio department. The only trouble we've had here, apart from noisy sliders, has been intermittent or permanent failure of the audio driver transistor Q272 (BC161). The audio quality from the two large speakers is quite good. ■

Service Notebook

George Wilding

Field Collapse

Two monochrome sets fitted with the Thorn 1500 chassis came our way recently with almost identical fault symptoms. The causes turned out to be rather different however. The first had complete field collapse, so as a first step a new PCL805 was fitted. As this made no difference we checked the voltages around the valve. The pentode's anode and screen grid voltages were about normal, but the triode's anode voltage was lower than normal. This is usually the case, since failure to oscillate leaves the triode conducting continuously. Touching various points in the circuit with the test prod instigated slight movement of the horizontal white line, confirming that the fault was lack of oscillation rather than failure of the pentode section to drive the scan coils. The oscillator cross-coupling networks came under suspicion therefore, and as a first step we tried shunting the coupling capacitors with equivalents. This failed to restore the scan, and as all the resistors had the original unblemished paint coding it seemed certain that the trouble was due to a dry-joint – resoldering that often

troublesome 18k Ω resistor R102 cured the problem.

In the second set the symptoms were misleading. When the set was switched on from cold a raster of about half the normal height would present itself, quickly reducing to a horizontal white line. This is often due to a defective PCL805, and tapping the glass may then momentarily produce at least a partial scan. In this case a new valve once again made no difference, and we discovered that there was zero voltage across the pentode's cathode resistor R103, i.e. the pentode was not conducting. Touching the pentode's control grid (pin 9) with a test prod produced a restricted scan, so it was clear that the trouble was due to the absence of a d.c. path between the control grid and chassis. The d.c. path is via four fixed resistors and the two linearity presets R104/6, the fault being due to R106's track being open-circuit.

Broken Oscillator Core

The fault we had recently with a Decca hybrid colour set was sound but no picture. The set had apparently slipped off a make-do stand, and on removing the battered back we discovered that the line output stage valves were running hot due to lack of drive – the line oscillator coil unit was broken. Unfortunately I didn't have a spare, and the set was wanted urgently. An exact replacement was found in a Pye set however, so this was pressed into service.

When we switched the set on the line frequency was well out, as expected. There were also some ominous crackling

noises from the back of the chassis, around the line output stage. It seemed as if the line frequency was so far out that excessive e.h.t. was being developed. We switched off, turned the core well away from its initial position, then tried again. This time there was an excellent picture, with just a suggestion of line trembling at the top – a little further adjustment cured that. The moral is to position the core similarly to the one in the original coil if you ever have to change a line oscillator coil – and to be careful with large sets unsecured on incorrect stands!

Similar Symptoms – Different Faults

You sometimes find similar symptoms produced by very different causes. For example, not long since the owner of a Pye hybrid colour set phoned to say that the picture was too large and the brightness was poor. On inspection we found that the picture was oversized in both directions, dark and with poor e.h.t. regulation. Clearly the e.h.t. voltage was low. The PL509 and PY500 were both running hotter than they normally do, and the next thing we noticed was a large, raised semicircle on the tripler, clearly indicating that a severe leak in it was pulling down the e.h.t.

A few days after replacing the tripler and obtaining a good picture, the owner phoned to say that the symptoms had returned. This time the two line output stage valves were much cooler than they usually are, the basic fault being low h.t., due to a big loss of capacitance in the h.t. reservoir capacitor C306 (200 μ F). This is encased in the same can as the smoother (C315), which seems to fare much better. We always replace the dual canister however – whenever in fact there's the slightest indication of rounding and slight swelling of the insulating end cap.

Tuning Trouble

The owner of a hybrid ITT colour set phoned to say that he could get only ITV. The set was one of the earlier ones, with a five push-button selector and common tuning knob, with no visual indication of the tuning position unless the back and convergence box are removed, when red plastic "travellers" can be seen. After some retuning, we managed to get BBC-1 and BBC-2, but they would drift off at the slightest provocation, giving the impression that the sliders were making poor electrical contact with the tracks.

Now we do get occasional complaints of intermittent colour drop-out and mistuning due to faulty tracks on this

selector unit and the later seven-button version, and ITT have a repair/exchange service for them. Sometimes only two or three buttons may be affected, the owners still being able to get all the channels they want, but the trouble invariably progresses until they end up with only one or two good selectors.

On this occasion there was no sign of the usual flickering tuning variation, and we found that acceptable stability could be obtained if we tuned each selector to a channel other than the one to which it had previously been tuned. So we thought it would be worth applying a little switch cleaner to the tracks, running the sliders repeatedly over the new tuning positions. This gave a big improvement, and no further trouble has been reported. It was an unusual case however: generally the only cure is to use the ITT repair/exchange service.

No Results

A Bush monochrome set fitted with the Rank A774 chassis was brought in with the complaint "no results". So naturally our first move was to check for continuity across the mains plug. Ignoring the initial charging current taken by the reservoir/smoothing capacitors, we found that there was no continuity in either direction across the plug. On lowering the chassis we found that the PL504 line output valve's fusible screen feed resistor 3R56 was open-circuit. This rather suggested that a fault in the line timebase had resulted in the PL504 drawing excessive current, either the PL504 or the PY88 boost diode developing a heater-cathode short with its heater then going open-circuit. The valve heaters were intact however, the lack of heater continuity being due to a dry-joint at the top end of the heater chain. But on repairing this the heater circuit was still open-circuit. The second break was found to be where the earth lead from the tube heater is soldered to the chassis – the lead is the outer braid of a piece of coaxial cable.

Resoldering this and the fusible resistor restored normal results, but within a few minutes there was sparking in the PY88 and 3R56 went open-circuit again. A new PY88 put that right, and the set worked happily during a long soak test. As to the heater circuit dry-joints, we can only assume that they'd been present for some time and had been healing up at switch on when the full mains voltage would be present momentarily across them – the tiniest of sparks would be sufficient to bridge the high-resistance soldered joint.

Reusing Heads

It's been some time since there's been criticism of any of the articles we've published – other than mine... More than a couple of VCR manufacturers have contacted me on the hot line however since the appearance of "Reusing Heads" last month. Special concern has been expressed by Pete of big G – they give credit on returned video head drums, and have received head assemblies that have obviously had a screwdriver applied to the video head fixing screw.

Some years ago I used to service Shibaden (Hitachi actually) reel-to-reel monochrome machines. If a video head failed, both could be changed – they were supplied in pairs. Each head had to be changed individually, and this involved the use of a large micro jig which was fitted on to the VCR chassis by means of big bolts. It had two eyepieces (one for each eye) so that each head could be critically adjusted using the calibrated microscope – each head had to be

aligned three-dimensionally, for height, overlap and angular position, to an accuracy of five microns. Since the adjustments were interdependent, they were done on a rotation basis.

So, before you decide to start messing about with the heads, consider the following points. (1) If you proceed as outlined in the article, you cannot guarantee that each head is even on the same track, let alone correctly displaced. (2) Can you measure the overlap to two-three thousandths of an inch? (3) For colour crosstalk purposes, the heads are not 180° apart but are displaced by one video line. Can you align two heads exactly 180° apart and then move one of them in the correct direction by one line?

Otherwise, you'll end up with a machine that's miles out of tolerance, able to record and replay only its own tapes, not to mention the wiggle at the top of the picture. Take my advice: leave the video heads alone – fit a new head drum complete.

Steve Beeching, T.Eng. (C.E.I.)

Long-distance Television

Roger Bunney

A STARTLING development in the broadcasting field – it looks as if the UK, along with the rest of Europe, could be enjoying satellite TV before the end of the year, though you'll need a three-metre dish for reception. Brian Haynes, director of Satellite TV Ltd., a London-based company, has obtained permission from the thirteen national PTT bodies in the Eutelsat organisation (and also the blessings of the Home Office and British Telecom) to use a redundant transponder aboard the OTS satellite for transmitting back to Europe, with a footprint ranging from Tunisia in the south to Finland in the north. The transmissions will consist of a commercial TV service with a single English language track. There will initially be two hours of programme material nightly, based around a first run movie, increasing to six hours during the week and ten hours at weekends as things develop. Advertising agencies have already booked time for such well known items as Coca Cola, Levis, Esso, Schweppes and so on.

The venture is regarded as being an incentive to aerial manufacturers and an experiment through which the advertising world can gauge the reaction from an international audience to a commercial service using the English language. Due to the low transmitter power, the use of a three-metre dish will be necessary to obtain satisfactory reception and it's assumed that cable operators and perhaps hotels and such like will be the main users. The signals may be scrambled.

Programme origination will be in London, with the service linked by British Telecom to Goonhilly for uplinking to the satellite. The down transmissions will be at approximately 11.6GHz, just below the allocated satellite broadcast band. The use of this redundant transponder means that there are no back-up facilities – so if a fault develops, the service will come to an end.



The BRT (Belgium) teletext index page 100, photographed by Jeff May (Colchester) on the screen of his unmodified Philips colour receiver (KT3 chassis). The transmission was on ch. 43, using an aerial directed at Dover.

If the project gets going quickly, the closing months of the year could be an exciting time – the service should be in operation by the time these words are read. I've been making a few enquiries as to the availability of 12GHz equipment – it can certainly be obtained, but in one-off quantities and matching prices. It seems likely however that domestic equipment will become available within a year or so, either from Western Europe or the Far East – rumours suggest that at least two UK firms are taking active steps. Now if someone reading this column can design a simple terminal that's easy to duplicate, I'm sure we shall all be pleased to hear . . . And now to DX matters.

Conditions during September

September was unusually active, with Sporadic E propagation continuing, a period of enhanced tropospheric propagation early in the month and the first signs here of F2/TE reception. First the SpE log.

- 1/9/81 TSS (USSR) ch. R1.
- 2/9/81 TSS R1, 2; TVP (Poland) R1, 2, 3; RAI (Italy) IA, B; RTVE (Spain) E2, 3, 4; RTP (Portugal) E3; JRT (Yugoslavia) E3; ARD (W. Germany) E2; plus unidentified signals.
- 5/9/81 RTVE E2, 3, 4; NCT-Italy E3/IA; ORF (Austria) ch. E2 – a new one!
- 6/9/81 TSS R1, 2; unidentified ch. R1, 2 signals.
- 8/9/81 RAI IA, B; JRT E3.
- 9/9/81 CST (Czechoslovakia) R1, 2 – using the EZO pattern with RS-KH identification; SR (Sweden) E3.
- 13/9/81 TSS R1, 2; RTVE E3.
- 14/9/81 TVP R1, 2; TSS R1; SR E2; Switzerland E2, 3.
- 16/9/81 NRK (Norway) E2, 3; RTVE E2, 3, 4.
- 17/9/81 RTVE E2, 3, 4; RTP E3.
- 18/9/81 NRK E3.
- 19/9/81 TSS R1, 2; MTV (Hungary) R2; RTVE E4.
- 20/9/81 RAI IA, B; RTVE E2, 3, 4.
- 21-22/9/81 RAI IA.
- 23/9/81 RTVE-1 E2, 3, 4; RTVE-2 E2.
- 27/9/81 TSS R1, 2; unidentified signal on ch. R1.

The above SpE log is based on reception by Cyril Willis (Ely), Arthur Milliken (Wigan), Ray Davies (Norwich) and myself at Romsey.

Tropospheric conditions improved from the end of August, giving enhanced Band III/u.h.f. reception. August 28/29 produced noiseless French u.h.f. signals on many channels, and the ATV G8RYC station at Ely. Conditions then veered to give reception from a more easterly/NE direction, with NRK signals in Band III and DR (Denmark) ch. E7, plus lots of W. German stations on all channels! Early morning openings continued over the next few days, with similar signals, but the peak occurred over the 5-7th. This produced the above signals, plus further NRK stations, SR up to chs. 30, 33 and 42, very strong signals from DR on chs. E5, 7, 10 and several ATV stations – Cyril Willis apparently had G8SUY from London producing overloading! Reception was subsiding rapidly by the 8th, with only W. Germany on chs. 35/48.

Ionospheric activity in the F2 layer commenced early in the month, with US paging stations on 35-22 and 35-58MHz from about the second week. On the 12th I could resolve them using an indoor Tandy portable! Conditions continued to improve, with the MUF rising into the low 40MHz region, and on the 20th I received both GBC (Ghana) and ZTV (Zimbabwe), fighting over ch. E2, from 1720-1810 BST (via TE). Hugh Cocks also logged

ZTV/GBC between 1600-1800 on the 21st and 22nd. During the afternoon on the 26th I heard harbour control at a Florida resort discussing the berthing of a large cabin cruiser with a patrol officer (the latter was on the stern of the ship, using a hand-held unit). This is indicative of the low powers that can be propagated via F2 when active – the signals were at 37.9MHz.

My thanks to Cyril Willis, Arthur Milliken, Ray Davies, Hugh Cocks and Jeff May (Colchester) who all contributed to this tropospheric/F2 report.

MS (Meteor Scatter) reception has also been present throughout the month, with the usual signal pings.

News Items

Fire: Further news from Trevor Plowman (Dublin) about the independent TV station operating in the city. The station identifies itself as "Channel 3 – Independent Television Dublin" and transmits on ch. D in Band III (not ch. C as earlier suggested). The test pattern consists of colour bars with the lower part of the screen carrying the identification mentioned above (moving across from left to right): it comes on air at 0000, followed by advertisements at 0010 and a film at 0015 until close down at around 0145. The station is at the former State cinema in the Phibsboro district and has two reserve transmitters and a large supply of feature films on video. There's no information on transmitter power or polarisation to date, but the signals can be seen at a distance of some 35 miles (this report from Mike Pettigrew, Church Hill, Wicklow).

India: Plans for an Indian TV broadcasting satellite (INSAT-3) suggest a launch in early 1982, with two channels. The INSAT-1 satellite already in orbit at 102°E may be used for TV, relaying at 4.17GHz. India has adopted the PAL colour system. The Russian Stat-T craft (99°E, 714MHz) continues to provide the Moscow-1 TV service from 0615-1515GMT.

Sri Lanka: A full TV service will start in January, with PAL colour, from Colombo ch. E5, Kokuvil (Jaffna) ch. E7 and Kandy ch. E10. Report from Bindu Padaki (Madras).

Mozambique: The first scheduled TV service starts in January, using system I, initially in monochrome only.

Saudi Arabia: Transmitters are now in operation on chs. 22, 23, 24, 25, 26, 27, 30, 39, 42, 45 and 47. Our correspondent mentions that European (particularly UK) football matches are commonly transmitted in full, with the original commentary and an occasional Arabic commentary laid "over the top". This is quite usual in fact in the Middle East and certain African countries.

New Transmitters

Two new pirates in Holland, one at Duivendrech (south of Amsterdam) on ch. 43 and the other at Monnikendom on ch. 27. Two new TVR (Rumania) transmitters have been received in Holland – simultaneously, on ch. R2. The RTM (Morocco) Band I transmitter operates on ch. E4. An HR (W. Germany) transmitter has opened at Rhon for the HR-3 service, on ch. 37 with 364kW. The GDR (E. Germany) Helpterberg station now operates on chs. E22 and E37 – it's thought that the E3 outlet may close.

Mysteries

Westward TV is reported as having been received recently in northern France on ch. E3! The 1956 RETMA test card has been received in Holland on ch. E2, via SpE, from a south-easterly direction. The identification "RTA

GOLDEN ANODISED AERIALS: SUPERB ECONOMY AMPLIFIERS; ALL PRICES INCLUDE VAT.

EST. 26 YRS.

EST. 26 YRS.

Masthead Amps	Type	Gain	Price
Astrax 1441	VHF/UHF	21dB	£12.82
Astrax 1450 LN	Bands 4&5 (TV)	28dB	£15.49
Astrax 1455	Bands 1&3 (TV)	25dB	£16.81
Astrax 1520	power unit for above amps		£9.15

SPECIAL OFFER HIRSCHMANN ROTATOR £42.95

IMPORTANT Quote TVM

For highly graphic lists and Brochure Send 52p. Refund of 30p on 1st purchase over £5.

ESTABLISHED 26 YEARS



Stockists of the finest aerials available in Britain:

OPTIMAX (Malta)
FUBA TV & FM aerials (W.Ger.)
MARGON TV aerials (Hol.)
UKW FM aerials (E.Ger.)
ANTIFERENCE TV & FM aerials (U.K.)

The fabulous golden anodised FUBA XC391

We specialise in Rotator & DX work. Bands I & III stocked.

ASTRA (GOLDEN D.I.Y.) AERIALS

SOME OF OUR SUPERB TV & FM AERIALS.

Name	Group & W/Band	Gain dB	Price	After discount
Margon 103 (TV)	both stocked	19.5/21.5	£61.41	£52.19
Margon 91 (TV)	both stocked	18.5/20.5	£44.16	£37.53
Fuba 91 (TV)	both stocked	18.5/20.5	£48.61	£43.75
Optimax 14 (FM)	Band 11 W/B	14	£57.50	£48.88
Optimax 8 (FM)	Band 11 W/B	9.5/10.5	£32.54	£29.29
Fuba 8 (FM)	Band 11 W/B	10.5	£40.85	£36.77
Fuba 9 (FM)	Band 11 W/B	11.0	£45.85	£41.27


Over 3,000 aerials stocked; all transmitters; poles; lashings; rotators; clamps; wall brackets; amplifiers; duplexers; triplexers; notch filters; coax white or brown

Many of our customers come from recommendation.
53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Spurgeons Bridge Tel: 01-684 4300
Open 9.00-5.30 TUE-SAT. 01-684 5262
Closed 12.30-1.30 Closed All Day Mon. 24 hr. answering service
FM & TV AERIALS AND ROTATORS ON DISPLAY

South West Aerial Systems

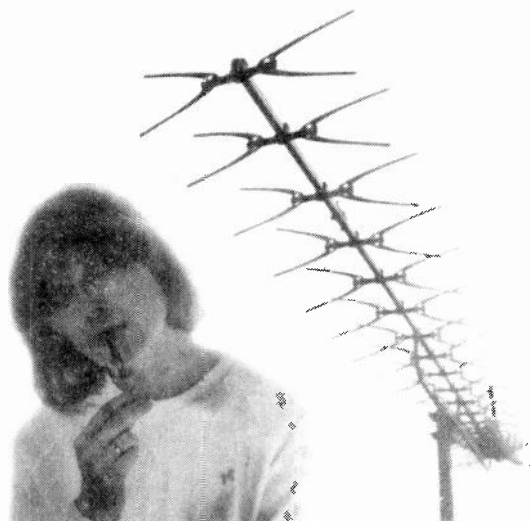10 OLD BOUNDARY ROAD,
SHAFTESBURY, DORSET.
SP7 8ND tel. 0747 4370



South West Aerial Systems – and Jane – wish their many friends a Merry Christmas and Happy 1982.

South West takes the doubt out of aerial technology by providing an expert and cost effective service in the design and supply of aerial/distribution systems for domestic, DX, fringe and alternative channel(s) reception, including active deflectors. We've a new range of high quality PSB aerials (air/marine), Band 2 wideband, for 'cordless' phones (SAE leaflet) and carry the renowned Plustronic TV range.


Our customer consultancy service will resolve your reception difficulties, and our 45p catalogue lists an ever increasing range of aerials, amplifiers, filters, mounting hardware and all the other necessary components too numerous to mention. Please include an SAE with your enquiry.



King Hassan of Morocco talks to RTM-TV (ch. E4).



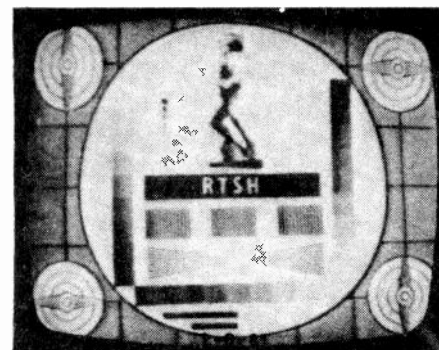TSS (USSR) received via Band III SpE on June 7th (ch. R9).



Albania ch. IC received in Holland via SpE.

Above photos courtesy of Ryn Muntjewerff.

Algerie" has also been seen in Holland on ch. E2 – fortunately it was photographed.

CB Interference

Our recent comments on this subject produced a mixed reaction. Complaining to the Post Office should in theory produce action, particularly where an active base station is reported, but in practice this doesn't always follow – at least in some areas. When the local (Southampton) Customs and Excise were approached in early September concerning an operator/base station, they refused to take action even when the operator was named and proved to be using an FCC standard a.m. transmitter. This was apparently "on instructions from above". In such cases one has to take preventive action oneself – or suffer.

Information has been received from three makers of CB filters. Labgear Ltd. are about to introduce their CM9700 filter. This has both braid and internal filtering, with a quoted attenuation at 27MHz of 70dB (transverse) and 26dB (longitudinal), falling to under 1dB in the group A spectrum and 0.5dB for groups B/C/D. The Packer Communications (Coniston, Cumbria LA21 8HQ) UL8 braid/inner break filter has been tried at a Southampton semi where the neighbour was operating a base station with a linear amplifier. This caused havoc with reception, but with the filter in circuit adjacent to the TV aerial socket there was only slight disturbance to an otherwise normal picture when the operator keyed to transmit. Other filters are available for hi-fi speakers, mains leads and v.h.f. (we hope to test this one shortly) – send s.a.e. for leaflet and prices. S. A. Collard (PO Box 40, Osmaston Works, Osmaston Road, Derby DE3 8NJ) also supply CB appliances, including their TV27, a 27MHz notch filter with 100dB attenuation falling to under 1dB above 470MHz (75Ω).

The PO Radio Services at Norwich advise that when fitting braid break filters the possibility of mains lead

breakthrough shouldn't be ignored. Suitable ferrite ring filtering should be included prior to the receiver's mains lead entry point to minimise the possibility of r.f. currents being induced in the chassis. I hope to report further on the problems of CB interference shortly.

From Our Correspondents . . .

Paul Barton, an experienced enthusiast from Harrogate, has sent details of an effective aerial phasing unit (see Fig. 1) which he has been using to null out the local ch. B2 sound for ch. E2/R1 reception. The design is much simpler than the one we presented last January, but provided the BBC signal at the local signal input is of higher strength than at the DX input the unit works well, with a considerable though not complete phasing null. The original circuit uses a BA182 in position D2, but I suggest that using a BA379 would be an advantage. As before, the idea is to get a phase shift between the unwanted signals at the two inputs and to adjust their amplitude so that they cancel at the output. Paul comments that SpE focusing must be occurring at times – as an example, he quotes strong reception from Tallinn (TSS) ch. R2 whilst the signal from Helsinki (ch. E2) only some 50 miles distant was very weak.

John Dempsey (Co. Tipperary) has been experimenting with reception from N. Ireland at u.h.f., using a home-made 22½ft diameter dish. At the focal point of the dish he used a Wisi bowtie, but this has since been replaced by a group A dipole plus oval reflector dish, giving improved and consistent results. The dish is mounted atop a 45ft tower!

Red Mathews reports that the HS Kabel-TV A/S relay company in Stavanger, Norway, has been given planning permission to erect a parabolic aerial some 18 metres high by 12 metres wide to receive BBC/ITV transmissions across the North Sea. A satisfactory service for 60% of the time is expected. The charge for connection to the cable network will be 3-4,000 Kroner – BBC radio will also be distributed.

Ed Baker (Cramlington) has spent an active summer with considerable success. He mentions that during a bullfight on August 9th – the usual protracted RTVE OB coverage of such events – the bull flattened the matador, jumped the barriers and got stuck halfway, scattering the spectators and confusing the picadors. I recall a similar event during the 60s, when the bull got behind the barriers and chased the spectators into the ring. This is not an activity I sympathise with however.

Finally Robert Copeman (Melbourne, Australia) reports improved F2 conditions during September with Vladivostock (TSS ch. R1) on the 13th plus various harmonics, including Spanish mobiles at 41MHz, and a harmonic from REE Spain at 35.2MHz on the 20th.

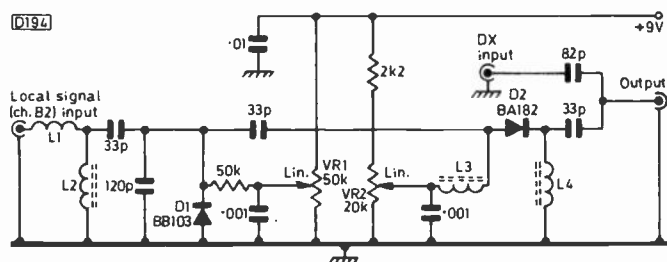


Fig. 1: Aerial phasing circuit used by Paul Barton. L1 consists of 10 turns of 20 s.w.g. wire, of 3/16in. diameter, 1½in. long. L2/3/4 are 15 turn close-spaced v.h.f. chokes.

VCR Clinic

Steve Beeching, T.Eng. (C.E.I.)

THERE'VE been a few moans since I announced that I was concentrating on writing my book on VCR servicing instead of reporting on VCR troubles for the magazine, so I thought I'd better mention some recent experiences.

First a Grundig SVR4004 – the very slow four-hour machine using the Philips format. The fault was that the video head drum went round at high speed. This was confirmed when the recorder almost hovercrafted off the bench – Andy offered to sit on it to hold it down, but I told him it would be better to deal with the fault.

The reason the drum went so fast was the absence of 50Hz reference pulses to the head drum servo. These are derived from a crystal oscillator, after division by a counter. The answer was simple enough – replace the counter i.c. That cleared the fault, but only for a while. Some time later the VCR was switched on again and the fault reappeared. The same i.c. was dead. Well, logic says that innocent little counter i.c.s don't just die. No, they're killed off by some nasty, evil cause. If in doubt, over to Grundig – ring Peter, that's my motto.

Peter said that it was probably the power supply capacitors, and that they'd come across the problem once before – there can be a voltage surge at switch on when the machine is plugged into the mains. As a result, the i.c. receives a higher supply than its usual 15V. Fair enough, I'd never have found that. So I whipped out the power supply panel and went over the capacitor connections with a soldering iron. Being smart (sometimes) I decided to watch the power supply waveform rise on the scope rather than immediately insert another sacrificial i.c. No overshoots or voltage peaks above the norm however. Check the 15V rail as the book says and find 15.1V, all o.k. Thinks "I'm missing something, better recheck the power supply at switch on." One does talk to oneself on occasions like this, doesn't one?

So we left the machine unplugged for a bit, then checked again. Apply mains and check the 15V rail. It rose to just over 15V and stayed there. Wait a minute – how much is "just over?" Check with the meter instead of the scope, and find 19V. Well CMOS i.c.s don't fancy that sort of voltage much, so out with the power supply again.

On the bench the power supply's off-load output was nearer 23V. Loaded with a lamp it settled at 15.1V. The manual lays down the conditions for measuring the 15V rail on full load, i.e. record. So the question was, should the power supply rise like it did off-load? To cut a long story short, the answer from Grundig was "no".

The power supply has an i.c. regulator with a Darlington power output transistor. As it was regulating, it seemed reasonable to replace the transistor. Wrong again! This time try the regulator i.c. That cured it, so we put in a new counter i.c., set up the machine and returned it to another satisfied customer with a long face (when he saw the bill).

Motor Trouble

A Toshiba V5470 machine came along for attention recently – in fact it was returned to us only some three weeks after we'd sold it. "Somat wrong wi' picture" was the complaint, so Andy tried a prerecorded tape and announced that the picture had lots of wiggles in the verticals. A quick check around the servo department

revealed the presence of a large a.c. waveform across the drum motor. Since this was not present at the servo's d.c. output, it was obviously the motor. Well, we hadn't got one, so we lent the customer another machine of the same sort.

Two hours later he was back again, complaining that his recording of Top of the Pops had been all right on the previous machine. This causes puzzlement sometimes, doesn't it? If a defective recorder makes a recording with the speed of its drum motor varying, the recording will replay all right on that particular machine, but a prerecorded tape will have bent verticals, as will the recording if replayed on a good machine. So he'd got a duff recording as well. Replacing the drum motor assembly cured the original fault.

Blow Up

We can all blow one up from time to time. I was merrily editing away on an HR7700 to provide myself with off-air colour bars as a test tape. The edits were necessary because the TV set I was using as a monitor kept on having colour drop-outs. When the tape was taken out, it was in two halves. It shouldn't happen of course, but the pinch roller solenoid drive transistor decided that my edits were a bit too fast and died, clamping the tape firmly between the pinch roller and the capstan as the transistor went short-circuit.

Microprocessor Faults

I've had a number of faults due to microprocessor logic problems. It's only fair to mention however that these tend to be isolated cases.

One such problem occurred with a Toshiba V8600. It had been out for a few weeks and came back with problems on the wired remote control. In this sort of case, a few minutes or so checking which controls work and which don't are minutes well spent. The machine would fast forward and rewind, but there was no play or end of tape stop. On the wired remote control unit, pressing fast forward gave play.

The functions seemed chaotic, but there was a pattern and a close scrutiny of the systems control microprocessor and its input signals showed that "scan line 2" was involved in the play and end of tape stop functions. The scope then showed that it was loaded down. There were several possibilities, including a remote control decoder i.c., so an advance replacement i.c. was ordered pending further investigation. Ordering this was a waste of time, because Toshiba hadn't got any. The i.c. was subsequently eliminated anyway, the fault being traced to the counter 0000 switch which had been pressed too hard, a lump of solder shorting to chassis. Easy enough to find on a quiet day with the wind in the right direction . . .

Another logic fault, on a JVC HR7700, looked more difficult than it was. Every so often the remote control wouldn't select channels properly. If channels 1, 2, 3 and 4 were selected, 5, 6, 7 and 8 came up – selecting these latter channels was all right. Also the clock, counter and programme setting tuner/timer functions wouldn't operate at all, yet all the tape transport functions – play, fast-forward, rewind, stop etc. – worked perfectly. The machine's on-board controls operated normally, so the instant diagnosis was a

faulty remote control unit. This was wrong, because the tape transport remote functions were o.k.

Analysis of the binary codes showed that a data bit D2 error would produce incorrect channel selections. So we checked the binary D2 line within the machine and discovered a faulty gating i.c. on the tuner/timer board – this little operation took half an hour.

Warping

Whilst on the subject of the HR7700, the last batches we've had have suffered from loud noises during rewind, due to warping of the tension arms and idler wheel brackets – they are all plastic/nylon, and catch on the turntables and opto-coupler housings.

Interruption

A brand new Ferguson 3V23 (HR7700) caused Andy some problems on test. It would stop dead after it had been on for only a few minutes, with the cassette still threaded, and would have to be switched off for a period of time before the cassette could be ejected. Just before it switched off, the picture would go spotty on the top half.

A scope was used to check and confirm the presence of an interrupt signal to the microprocessor – the interrupt signal indicates that the machine has stopped for some reason, rightly or wrongly. There mightn't be anything actually wrong, it's just that the machine thinks there is, so various inputs to the interrupt circuits have to be checked.

The drum flip-flop signal produced by the servo is used to tell the machine that the drum has stopped rotating – for example if the tape ties itself in a reef knot around the drum. The signal is a symmetrical squarewave, and when we took a look at it we found that there was some distortion – this could also be the explanation for the spots on the picture prior to the actual switch off. The culprit turned out to be IC3 in the servo circuit – it produces the flip-flop signal from the rotating drum. We found that the squarewave became distorted as the chip warmed up – squirting it with freezer restored the correct waveform.

Will it end up in the river?

Here's another difficult fault we had recently with an HR7700 – another new machine. We put it on our checking bench and tuned each channel to an off-air programme. So far so good. Incidentally Andy checks out all our machines before despatch, and we've had to put many a fault right. So our failure rate in the field is extremely low – if I was a customer and got a faulty machine, I'd certainly be upset! Anyway, the HR7700 was used by yours truly the following day only to discover that there were no off-air signals. After a period of torture (three episodes of Crossroads) Andy admitted that he may not have stored the tuning voltages in the memory. So we did it again, checked the memory, and everything was o.k.

The following day we discovered that the tuning memory had again gone (this time I had to watch Crossroads). So something was not quite right, and those of you who know what's involved in this "simple" process will by now be cringing at the thought of it all. Not me though! Oh no, I screamed obscenities at the dog, CP. (That's her name, from Candy to Candy Puff through CP30 to CP, and she answers to them all . . .) Back to the HR7700.

The first check with a case of this sort is to find out whether the memory is being erased at power on. Being an EPROM, the memory chip has three power supply lines and

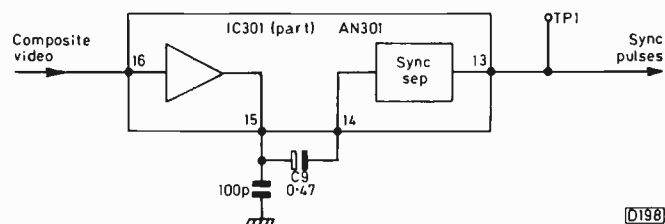


Fig. 1: Servo sync separator circuit, JVC Model HR3330.

a reset, the power supply lines being delayed at switch on so that they appear in sequence. We checked the lines and the delays, and everything was in order. The next move was to change the memory i.c., since it was now number one suspect.

Two days later, after yet another couple of memory losses, I was mucking about storing new programmes. As a result of this, a weird sequence came to light. Assuming that the memory was completely clear, I retuned channel 1. On switching to channel 2 however the memory had returned and was tuned in. So I checked channels 3, 4, 5 and 6 – all were blank. Try channel 4, get nothing, so press the store button and move up one to channel 5. Lo and behold, there's a picture. This meant that pressing the store button was getting the tuning voltage from the memory, which in turn indicated that the memory was storing data which was not being released by the microprocessor. Naughty micro. Arrrrgh! Change micro, tune in and leave over weekend.

Monday morning was a tense time. Will the tuning be there? Will Steve throw an HR7700 into the river Trent and claim the insurance? Well, it worked. Andy tied the boat back up and we put the recorder in stock. Latest score JVC 0, Steve 7.

Picture Jump

An HR3330 had a fault which persisted despite being sent to more than one service department. It had occasional picture jump with changes in off-air picture, to the point that the servo would sometimes be disrupted in the record mode. I'd a couple of gents with me at the time on a training course, so I asked them to run the machine until they could find a way of making the fault appear.

It transpired that the fault regularly coincided with recordings of ITV adverts, and we concluded that when the adverts were replayed the servo went off lock. Some time was spent waiting for the adverts with a scope, and sure enough during an advert picture change the servo went off lock. We then found that the fault occurred when the picture went from white to black, so we arranged for this with my pattern generator to get the problem to come and go at will. We then checked the field sync pulse input to the servo, and discovered that the pulses disappeared during the transition from white to black. I said it was capacitor trouble, someone else decided it was an i.c. and another remained uncommitted.

I won when it was discovered that C9 (see Fig. 1), which should have been 0.47µF, was actually 10µF – an assembly error. How did I manage to guess this one correctly? Well, having done some design work on video amplifiers, I knew that the d.c. level on which a video signal sits after capacitive coupling depends on the video signal amplitude, the level being critical with a sync separator circuit.

Manuals

Despite a bit of flak at times, I do have a good relationship with most video firms. But I must say that the

manuals they provide vary enormously. JVC's are excellent – all the information you need is there. Grundig are making a great effort. I've suggested to some of the importers that they spend less time running two-day courses that most people forget by the time they come face to face with a faulty VCR, and spend more money on producing decent

manuals in understandable English. Sectionalised details plus block diagrams and a detailed circuit description should be given, since a service engineer is in a better position to carry out repairs if he knows how the machine works and has the details to hand for easy reference. So how about it all you importers?

Letters

VDU MODIFICATION

A recent item in your *Service Bureau* column (October 1981, page 661) prompts me to say that I've found the Thorn 1690 monochrome portable to make an ideal VDU. It has an isolated chassis of course, and there's a link on the board ideally (intentionally?) positioned to form an injection and extraction point for video signals at a level tolerably close to the standard 1V peak-to-peak with negative-going syncs. The link, physically adjacent to R33, isolates the base of the video output transistor TR7, the input to the sync separator circuit and the 6MHz intercarrier sound rejection trap from the video driver transistor circuitry. A simple analogue changeover switch can be used to replace the link, providing selection between TV and VDU use. I've been using my set successfully for teletext and home computing use for some years.

J. W. Attwood,
Watford, Herts.

EHT PROBE

Looking through the many articles you've published in the past on c.r.t. testers and reactivators, I found no mention of discharging the e.h.t. potential which is generally still present at the final anode when the base is removed for tube testing/reactivating. On some colour sets, the single-standard Pye hybrids for example, there's no problem since the tube's capacitance gets discharged via the focus VDR. On most later sets however a hefty e.h.t. potential is left on the final anode and, as I've found from bitter experience, can cause havoc with video output transistors etc. when the base is refitted.

Having plenty of old Pye hybrid chassis focus units available, I decided to try some experiments with the carbon VDR rod from one of them. The main problem was obviously going to be insulation of the e.h.t. end of the probe. I came across a long, tapered plastic watering can spout from a Weedol applicator in the garden shed, and this became the basis of the probe (see Fig. 1). The older (black) type focus units have a red rubber sleeve which helps with the insulation problem.

The sleeve was pushed farther down the rod, to about half an inch from the end, the rod then being pushed into the plastic tube. The end was fastened with Araldite. Since the rod has wire connections, there's no problem with fitting

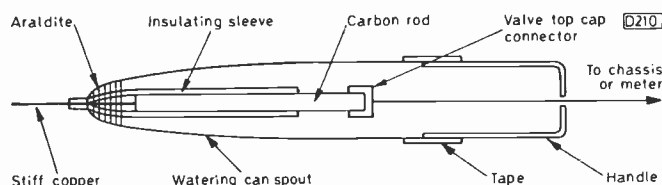


Fig. 1: P. Smith's e.h.t. probe.

a short copper connector at the e.h.t. end: the black earth connection is long enough to use at the earth end. A scrap soldering iron handle was then taped to the end of the tube, with the earth lead threaded through.

I was now ready to test the device – an old Rank A823 chassis was used for the purpose. A cheap, 20k Ω /V meter (1kV scale) was connected between the probe and chassis, and after switching the set off the arrangement was tried. Sure enough, the meter reading rose to about half f.s.d. and then slowly died away to zero. I then decided to switch on with the probe still connected. The reading rose to a steady one just above half f.s.d. I now realised that I had a means of making direct e.h.t. readings.

To cut a long story short, I fitted a crocodile clip to the earthy end of the carbon rod and by trial and error adjusted the clip to give me a reading of 25 on the 30V scale with the brightness turned down (switching the set off each time an adjustment was made). The rod was then cut off at this point and an earth connection made, using an old valve top cap pushed over the end of the rod. The probe has been used on many occasions subsequently, and was later found to be accurately calibrated by checking against a colleague's commercial e.h.t. meter.

The following safety precautions should be observed. (1) Insulate the copper connector so that no bare wire protrudes from under the e.h.t. connector's cover. (2) Always make connections with the set switched off – including moving or changing meter scales. (3) Keep the earthy end earthed at all times.

P. Smith,
Hathersage, Sheffield.

AN AWKWARD ONE

A Luxor solid-state colour TV receiver (Model no. 18066641) with automatic search tuning was brought into the radio/TV/electronics instruction department of the Irvine Skillcentre as a last resort, having been to a dealer who'd been unable to locate the cause of the trouble. On switching on we found that the vision was normal but the sound was absent; also the 850mA fuse on the power board had blown. On checking the transistors on the audio board, one of the output pair was found to be short-circuit base-to-collector. The two transistors (BD676 and BD675) and the 850mA fuse were replaced, but on switching on the fuse again blew.

We'd no service information on this particular model, so I decided to trace out the circuit. As a result, I was amazed to find that the transistor connections were wrongly printed on the top side of the board! The connections marked "B" were in fact connected to the positive and negative supply rails; the emitters were marked correctly; but the hole marked "K" was connected to the collector of the driver transistor.

On fitting two new output transistors the right way round, replacing the fuse and switching on the sound came up normally. A board error that could prove quite costly in components and time!

G. Sauter,
Kilwinning, Ayrshire.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon from page 99 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

RANK T20 CHASSIS

The initial problem was that the fusible resistor 5R3 in the h.t. feed to the line driver transistor would go open-circuit. Resoldering the spring would bring the picture back for about a week before the resistor would spring open again. The set is now giving the no results symptom, i.e. there's h.t. but the line timebase is not working. Components that have been checked include the line output transistor and the line oscillator i.c.

The opening fusible resistor suggests that the problem lies in the line driver rather than the line output stage. With no drive, the line output stage remains cut off. More obvious things to check are the line driver transistor 5VT3 and 5C5 which decouples 5R3. It would also be worthwhile checking (by substitution) the damping network components (5C2/5R4) in the driver transistor's collector circuit, and 5D1 which is in series with its emitter. A defective driver transformer (5T1) cannot be ruled out – it's inclined to suffer from short-circuit turns in this chassis.

NATIONAL MODEL TC85G

We're having problems with a line sync fault on this set. The flywheel sync circuit has been thoroughly checked and the waveforms in the line oscillator department all seem to be right. To start with, the set would take a long time to lock – the time gradually got longer. Now the picture won't lock at all – the line oscillator seems to be running fast.

We've had this one ourselves, though it doesn't seem to be a common fault. The characteristics of the sinewave line oscillator's coil, or more likely its core, change over a period of time (these sets are now seven years old). A new coil assembly will put matters right, but as a temporary measure the value of the tuning capacitor (C510, 8,200pF) can be changed to the next standard value and the coil retuned.

ALBA MODEL T14

There's tuning trouble with this set. To start with the picture would remain for only a short period, then loud hissing noises etc. would almost drown out the sound and the picture would go right out, leaving just the raster. Now the picture cannot be tuned in on any of the three channels – the sound can be tuned in, with a lot of noise and now and again patterning on the screen.

These sets are fitted with the Thorn 1591 chassis, and it would appear that the tuner unit is defective. You can either replace or repair it – Thorn four push-button tuners are advertised quite cheaply. Repair should consist of cleaning the spring washers which contact the tuner body to the

rotary spindle, removing the grease and improving the contact, and replacing one or both of the transistors as necessary. Ensure that the push bar is firmly soldered to the swing arms.

TELETON MODEL TVC20

The problem is lack of height – at the top and bottom of the screen. I've replaced the 21LU8 field oscillator/output valve and checked most of the associated resistors and capacitors, but the fault remains.

The main suspect is R725 (1.8M Ω) over in the line output section. It feeds the height control from the 700V boost rail. If this is o.k., check R616 (1.2M Ω) and R618 (1M Ω).

GRUNDIG MODEL 6010

When the set is switched on from cold the picture tends to roll diagonally across the screen for the first quarter of an hour. Once the set has warmed up however the picture is perfect.

The effect is due to weak or intermittent line sync. Check R408 (2.7M Ω) on the line sync panel – it provides bias for the sync separator stage in the TBA920 i.c. If this resistor is o.k., the chip itself is suspect. Set up the line hold control R426 when the repair has been completed.

SONY MODEL KV1300UB

This set was condemned by a dealer as requiring seven new transistors and a new tube. I tested the tube, which appears to be all right, so I decided to investigate further. On switching the set on, the cut-out operated. I disconnected the c.r.t.'s e.h.t. cap and left it off, then checked the chopper transistor Q903. This was short-circuit emitter-to-collector, so I fitted a replacement and tried again, with an e.h.t. probe connected to the e.h.t. supply and a meter connected to the 110V h.t. rail. The chopper transistor again blew, but I noticed that the e.h.t. rose to about 8kV and the h.t. line to about 100V before the cut-out operated. To check further, I applied an external 18V supply to the junction of D608/R574 and found that the line oscillator and chopper driver stages seem to be in order. But another chopper transistor went the way of the first two.

First check the line output transistor Q801 (2SC1034) and the flyback tuning capacitor C802 (7,500pF, 1.5kV). Then check the components associated with the crowbar action – D610 (12V zener), Q605 and thyristor Q606. The kick-start components C604 and D602 would be worth checking, also the chopper circuit "efficiency diode" D607 and, less likely, the chopper driver transformer T603.

DECCA MODEL DR21

The original fault on this set was incorrect line speed. This was cured by replacing C114, C116 and C120 in the line oscillator/discriminator circuit – they are all polystyrene capacitors. The problem now is foldover on 405 lines – the 625-line picture is o.k. This foldover is not at the side of the screen but part way across, giving the appearance of a pleat in the picture: there is also lack of width on the left-hand side.

You've had a go at the capacitors in the line oscillator circuit (we hope you used 5% Suflex replacements), now you'll have to check the resistors. The usual cause of this fault is R130 (580k Ω) going high in value, but the associated resistors R139 (330k Ω) and R140 (56k Ω) should also be checked. These resistors are all in the grid

circuit of one half of the ECC82 line oscillator valve – the other grid is tied to the line sync circuit. The fault can be confusing in showing up on one standard only.

THORN 3500 CHASSIS

The problem is pulling to the right with captions etc. The i.f. and sync transistors have been checked, and all relevant voltages except that at the collector of the luminance delay line driver transistor VT105 are correct. The latter is at 12V instead of 7.5V.

First check that R125 (a.g.c. adjustment) is not over advanced. Then check the sync separator's base bias resistor R215 (2.7M Ω) and the associated diode W201, and ensure that any substitute transistors used in the sync circuit (VT202 and VT203) are suitable, Thorn-approved types.

BEOVISION 3200

The set comes on normally, with a good picture, but after about five minutes the picture starts to blur then loses width. When the fault appears, the PY88 and PL504 valves overheat.

Try replacing the PY88 and PL504 valves, adding a 1k Ω , 5W wirewound resistor in series with the PL504's fusible screen grid feed resistor R540. If this fails, isolate the outer core of the screened lead feeding R532 and R533 in the PL504's control grid circuit (on the base panel) – it sometimes shorts to the inner core. If the fault persists and the line drive is present and correct, the line output transformer is suspect.

SCOPE USE

When I try to tackle solid-state chassis such as the Decca 100 with my 10MHz scope, the h.t. rectifier goes short-circuit. I appreciate that this is due to the chassis being live, but am not sure what procedure to adopt.

Your earthed scope introduces a short-circuit to earth when the probe is connected to the TV chassis. There are two possible solutions. Either operate the set from a mains isolating transformer, or remove the earthing lead from the scope's mains plug so that it's floating electrically.

HITACHI CNP860

The line driver transistor TR39 was replaced (it had gone short-circuit emitter-to-collector), also its h.t. feed resistor R720. This restored the picture, but there is a slight "belly dance" effect which is most noticeable when the set is used with a teletext decoder.

We suggest you check C713 and C711 (both 10 μ F) which smooth the supplies to the line driver and line oscillator stages respectively, also C718 (100 μ F) which is associated with the feed to the line output stage. If there's any suggestion of hum on the picture, check the series regulator transistor TR41 and the associated electrolytics.

TELEFUNKEN 711 CHASSIS

The tuner is stuck on channel 7 and won't change. The two i.c.s (SAS560 and SAS570) in the channel selector circuit have been replaced, but the problem is still present.

This fault is usually due to the SAS570 i.c. failing, and we're surprised that its replacement hasn't solved the problem. The only other trouble we've experienced has been leakage across the plastic of the touch sensor itself.

Disconnect R1007, the resistor connected to the number seven sensor, and see whether channel changing is then possible. If so, the touch sensor is faulty. Clean it with switch cleaner and gently scrape the plastic to remove any conductive material that could be present.

ITT CVC9 CHASSIS

When the set is first switched on, there's loss of colour lock – the colour breaks into one-inch horizontal bars. Rapidly switching the set off and on again produces a normal picture, but on changing channels colour lock is again lost – BBC-2 is particularly bad, the colour usually remaining unlocked and going almost to monochrome. Is the tuner suspect?

The trouble is unlikely to be in the tuner unit – a careful tweak of the reference oscillator frequency control R311 (at the top left-hand side of the chassis) may be all that's required. If the fault persists, replace D36 (1.5V zener) and C208 (6.8 μ F tantalum) in the reference oscillator control loop, then reset R311. If you replace D36, note that it's cathode goes to chassis.

DECCA CTV19

This set has developed an appetite for PL509 line output valves. The picture seems to be o.k., but after about ten minutes the line output valve glows red, its cathode current being about twice what it should be at 400mA. The line output transformer and the valves in the line timebase have been replaced, and the line drive seems to be correct (–60V at the PL509's control grid). There doesn't seem to be anything amiss in the line timebase.

It could be that the line drive waveform is the wrong shape – triangular instead of rectangular. This can happen if C400 (400pF) in the waveform shaping network or the line oscillator's anode load resistor R327 (39k Ω) is faulty. Also make sure that the line drive coupling capacitor C402 (0.01 μ F) is not leaky. Other possibilities are: short-circuit turns in the d.c. feed choke L408 or the shift choke L400 (the latter can be disconnected as a check), missing gapping paper in the line output transformer, or maladjustment of the harmonic tuning coil L405.

BUSH TV350

The trouble with this portable is no raster. When the set has been on for a few minutes the line output transistor becomes unbearably hot, its collector voltage falling to about 6V. The odd thing is that removing the tube's final anode lead produces a nice, healthy spark.

That spark is the clue! The e.h.t. rectifier stick is almost certainly faulty, due to leakage. If the fault persists after the stick has been replaced, the line output transformer is suspect.

QUERY COUPON

Available until 23rd December, 1981. One coupon, plus a £1.00 (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 98.

TELEVISION DEC. 1981

RANK T20 CHASSIS

The original trouble was very bad streaking of whites across the screen when a picture containing whites or captions was present. This was cured for a few days by replacing 3C16 (220 μ F) which decouples the supply to the TBA560C luminance/chrominance i.c. Before that a streak-free picture could be obtained only by reducing the brilliance and contrast controls to a very low level. The fault has now returned however, though it's not as bad. In addition, there are now flyback lines on the picture.

We suggest you check the luminance coupling capacitor 3C15 (100 μ F) and the clamp reservoir capacitor 3C18

(0.47 μ F) – substitute with known good components. If the problem persists, the TBA560C and TCA800 i.c.s are suspect.

SABA H CHASSIS

The fault with this set is pulling, first to the right, with increasing speed, then slowing down and pulling to the left. The picture then stabilises itself and there's no more trouble till the next time the set is switched on.

The TBA920 line oscillator i.c. is generally responsible for this, due to an intermittent internal fault. Replacing it should cure the problem.

TEST CASE

228

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Wednesday's a quiet day for most of the technicians hereabouts – our service department is closed on Wednesdays, save for one man. With his glorious but temporary title of Duty Engineer, he roams the lanes and villages armed with a bleeper and a handful of 10p pieces. With these he regularly interrogates the Answerphone machine, tending to the needs of those customers and TV sets that have the temerity to disturb the peace on our day off.

The Post Office two villages away also shuts on Wednesdays. In his den above the shop, the postmaster watches the horse racing on his Grundig TV set, the stamps and pension books temporarily forgotten while he sits there with the windows shut and curtains drawn. Cigarette in mouth, he stabs the buttons on his remote control unit – but the set adamantly stays on BBC-1. He's had this trouble before – batteries lasting no time, and the set fizzing and spluttering for half an hour from cold. He phones the service department.

When the technician called, he entered the smoke-laden room and listened to the postmaster's problems – remote control doesn't work unless the transmitter is close to the set, spitz-and-sparken in the back, dim picture. Pondering on how many fags a day his customer gets through and the state of his lungs, our technician removed the set's back. Sticky, yellow gunge had accumulated around the tube's final anode cavity, and this was the cause of the corona effect. The area was quickly cleaned with meths and a thin film of silicone grease was applied. That cured the fizz. A go over the tube face with the meths then brought up a brighter picture than the postmaster had seen for many a long day.

The remote control action was very weak. A new battery was tried, but gave little improvement. If the transmitter was held in line with the receiver and fairly close, it would work. With this set (Model 1632GB), the Tele-pilot 120 is used for remote control. The technician ascertained that another was available at the showroom, and a couple of days later called at Crowfield Post Office to try it. The results were rather better, but still not up to the standard of the one in the shop.

An oscilloscope check was next made at C1206, the output from the Tele-pilot preamplifier in the set. This was found to be low and doubtful when the transmitter was operated from a distance of eight feet. As a last resort, a new preamplifier was tried – but made not a jot of difference! As he examined the original preamplifier unit, our technician suddenly realized why the remote control system had become insensitive and was able to clear the problem. What did he do? Answer next month.

ANSWER TO TEST CASE 227

– page 46 last month –

A strange convergence problem and then a traffic warden confronted our man last month. Despite the salesman's confident diagnoses, neither the convergence system nor the tube was responsible for the red fringing effect on the Decca 30 series hybrid receiver. It will be recalled that only the vertical lines of the crosshatch pattern were affected, and that transposing the red and blue drives from the decoder transferred the fault to the blue raster, proving that the trouble lay on the decoder panel.


In fact the fault was in the red output stage. This smearing effect is usually due to reduced bandwidth: as the RGB output stages have to handle the combined luminance/colour signal, a bandwidth of 5MHz or so is required. This frequency response is achieved, as in most designs of this vintage, by the use of frequency-selective negative feedback in the emitter circuits of the RGB output transistors. In the Decca set's red output stage the key component is C262 (470pF), which has an increasing shunt effect across the emitter bias resistor R302 (1.2k Ω) as the frequency rises, i.e. the negative feedback introduced by R302 is reduced at the higher frequencies due to the decreasing reactance of C262. The stage's h.f. response is thus enhanced – not in our set however, since C262 was completely open-circuit!

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £10. Overseas £11 per annum payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

N7118 PAL COLOUR BAR GENERATOR

An extremely light, compact and durable instrument, designed for mobile Colour T.V. Maintenance in the customers home. The basic model includes a built-in rechargeable battery plus a Power Unit/Charger. (A fully charged battery gives 10 hours continuous use). All patterns and sync. pulses are derived from a single crystal controlled oscillator, producing extremely accurate, stable displays. The patterns available are: Standard Colour Bars, Red Raster, Linearised Grey Scale Step Wedge, Crosshatch and Peak White Raster. A Coaxial Socket on the rear panel provides a modulated UHF or VHF (please specify) signal of approx. 1mV for direct connection to Receiver Aerial Socket. An (optional) integral Sound board is available, producing a Sound Carrier (6MHz or 5.5MHz), frequency modulated by a 1KHz Sinewave. The N7118 will also house a third board that provides a 1 Volt p to p, 75 ohm Video Signal to a rear panel B.V.C. Socket.

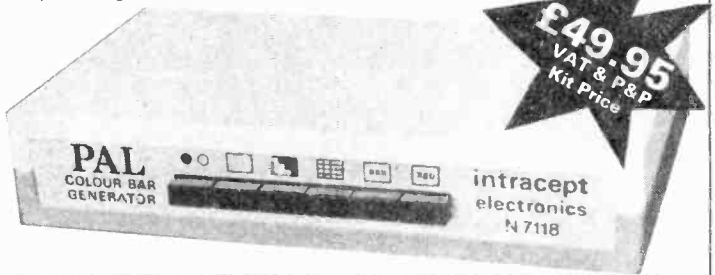
Complete kit, including a professional finished case, screen printed P.C.B., Ready Built P.S.U., and all components – **£59.50** inclusive. Sound and Video Boards, add **£10.29** per board. Ready Built – **£88.25** inclusive, Sound and Video Boards add **£11.45** per board. S.A.E. for details and specification.



N7121 VIDEO PATTERN GENERATOR

This Generator, based on the N7118 is designed for the mobile servicing of Colour Monitors and V.D.U.'s. It produces three separate Colour output signals at 1 Volt peak to peak into 75 ohms. Also provided is a separate sync. output which may be adjusted for positive or negative-going sync. tips. The Generator may be operated at 62.5/50MHz or (by operating a push switch on the rear panel) 52.5/60Hz.

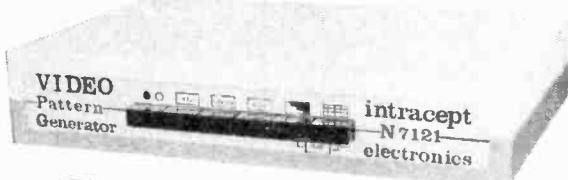The patterns available are colour bars, crosshatch, 8 step grey scale wedge, peak white plus many other combinations i.e., red raster, blue raster, yellow crosshatch etc., as defined by the three (red, green – blue) beam switches on the front panel. The generator is powered by an internal Ni-Cad battery and is supplied complete with the Charger/Power Unit.



Price (Built & Tested) **£75.00** + VAT & p. & p. Total **£88.25**.



INTRACEPT ELECTRONICS LIMITED

203 Picton Road, Liverpool L15 4LG.
Tel: 051-733 3042.

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY Z146 A640 A774 A816 A792 A793 A823 A823b A823av colour		INDESIT 20EGB 24EGB mono	
DECCA 1700 2001 2020 2401 MS2000 MS2400 2404 2420 2424 mono CS1730 1733 '30' series BRADFORD colour CS1830 1835 80 100 series colour		KB-ITT VC200 VC205 VC207 CVC5 CVC7 CVC8 CVC9 colour CVC20 CVC30 CVC32 series colour	
FERGUSON HMV MARCONIA ULTRA THORN 1590 1591 1592 1593 mono 1600 1615 series mono		PHILIPS 170 series dual std mono 210 300 series mono	COLOUR G8 series G9 series
G.E.C. 2000 to 2064 dual std mono 2047 to 2105 3112 to 3135 DUAL STD hybrid colour SINGLE STD hybrid colour	WALTHAM 125		
PRICES INCLUDE P. & P. & 15% VAT COLOUR LOPTS £10.50 RETAIL £9.00 TRADE MONO LOPTS £9.50 RETAIL £8.00 TRADE	WINDINGS		
	RANK BUSH MURPHY Colour hybrid quadrupler type		
	T20a T22 Z719 Z722 Pry & Sec £6.00		
	Z718 series primary £6.00		
	Z718 series EHT overwind £7.00		
ULTRA THORN 1690 1691 EHT overwind £7.00			
PHILIPS G6 EHT (exchange basis only) £7.00			
G6 primary £5.00			
PYE 691 to 697 EHT overwind £3.00			
691 to 697 primary* £4.00			

All lopts and windings are new and guaranteed for 6 months.

Open Mon.–Fri. 9 to 5.30 pm

Rewind Service Available

**PAPWORTH
TRANSFORMERS**

80 Merton High Street
London SW19 1BE

Barclaycard and
Access welcome



01-540 3955

ARE YOU

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial **CASH INCOME** with a starting capital of less than £20. Our new unique publication "**How to Deal Successfully in Used Colour Televisions**" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail – for both televisions **and** new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular updating service.**

You can start tomorrow – but you'll need our guide. The latest big illustrated edition is out now, and costs just **£4.95** – a small price to pay for financial independence!

ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, DARLEY ABBEY MILLS, DERBY.

To: Globus Industries Ltd., Unit 18, Darley Abbey Mills, Derby.
Please send by return post "How to Deal Successfully in Used Colour Televisions".
I enclose cheque/p.o. for **£4.95**.

NAME

ADDRESS

.....

**NEW
LONDON
BRANCH OPEN**

1000 colour TV's
**MUST
BE CLEARED**

● **THORN** ● **DECCA** ● **GRUNDIG**
● **SABA** ● **TELEFUNKEN** *etc. etc.*
Special prices to celebrate our new branch opening

REASONABLE OFFERS ACCEPTED FOR BULK PURCHASE!!

● Export enquiries welcome ● Call any branch ● All sets guaranteed complete

CELTEL

**NEW
BRANCH**

WARNERS MILL, SOUTH ST.,
BRAintree, ESSEX. 0376 43685

3A, KEMPS SHIPYARD, QUAYSIDE RD,
SOUTHAMPTON. 0703 331899

110 SHACKLEWELL ROAD,
LONDON N16. 01-249 9265

TRICOL REBUILT SONY TRINITRON TUBES

Two years guarantee with a four year option.
Hot pumped at 400°C.
Rf bombed at 800°C.
Armoured faceplate replaced (where applicable).
Rebanded for maximum safety.

18"-22" **£57 + VAT**
Portable 330AB22 etc. **£46 + VAT**

Please add £1.50 per CRT to cover cost of picking up and delivery by Securicor Parcel Service.

Also available: Matsushita Panasonic. Most types from
Carriage £1.50.

£49 + VAT

The above CRT's are offered on a "Regun of your own suitable glass" basis. Send your CRT securely packaged and clearly labelled with your name, address and telephone Nos via your nearest **SECURICOR PARCEL DEPOT** [Carriage Paid by TRICOL]. Rebuilt CRT's will be invoiced, and then delivered on receipt of payment. We buy Sony Glass.

Send your CRT or Telephone for details to:-

TRICOL,
CUPAR TRADING ESTATE, CUPAR, FIFE KY15 4SX
Tel. Cupar [0334] 55348

(N.B. Glass is breakable, please ensure correct packaging.)

**BUILD
AND LEARN**

Kits which have **PROVED** themselves!


Forgestone 500 TELETEXT

High quality colour television receiver
NEW INFRA-RED FULL FEATURE REMOTE CONTROL TELETEXT

- ★ Pin diode tuner
- ★ Glass epoxy printed circuit panels
- ★ Full technical construction manual
- ★ Hi-Bri tube
- ★ Eleven integrated circuits
- ★ Ready built and aligned IF module
- ★ High quality components
- ★ Modern cabinets
- ★ All solid state

- ★ Fully isolated and protected power supply
- ★ Diode split L.O.P.T.
- ★ Low consumption

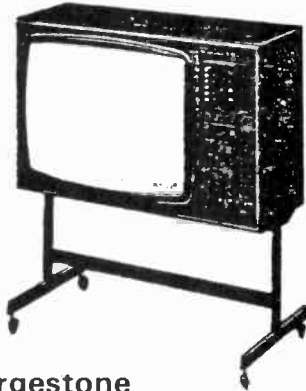Also ideal as a FULLY isolated COLOUR MONITOR for Home Computer Systems. R.G.B. or PAL Encoded Video inputs, with remote switching.



THE ULTIMATE in large screen 22" and 26" television receiver kits. Deluxe full spec. Teletext, 7 channel + VCR. Also video and audio in/out. 6 models in the 500 range.

Buy as you build. All Forgestone Kits are for the constructor of today, sections of the Kit are available separately. Please send stamp for further details of these quality products. Telephone or Mail Orders accepted on Access/Barclaycard

forgestone colour developments limited

Ketteringham, Wymondham,
Norfolk, NR18 9RY
Telephone: Norwich (0603) 810453

THE VERY LATEST SC110 LOW POWER, FULLY PORTABLE OSCILLOSCOPE.

The new Thandar SC110 represents a break-through in oscilloscope development. The SC110 is LESS THAN TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope.



1980 GOLD MEDAL winner of the B.R.N.O. EXHIBITION, the largest Trade Fair held in Eastern Europe.


Full Sized Performance

- 10 MHz bandwidth.
- 10 mV per division sensitivity.
- Full trigger facilities are provided including TV frame, or TV filtering.
- Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- Size 255mm x 148mm x 50mm.

**BRITISH
MADE**

Scope **£139.00** + £20.85 V.A.T.
Carry case **£7.70** + £1.16 V.A.T.
x 1 Probe **£8.50** + £1.28 V.A.T.
x 10 Probe **£10.00** + £1.50 V.A.T.
(AC Adaptor **£4.95** + £0.74 V.A.T.)
(Overseas purchasers please state voltage.)
Re-chargeable cells **£7.50** + £1.13 V.A.T.

**FULLY
GUARANTEED**

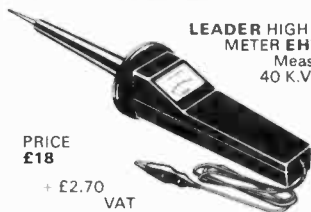

**LEADER HIGH VOLTAGE
METER EHT PROBE**
Measures up to
40 K.V. D.C. with
**SAFETY
BUILT
IN
METER**

PRICE
£18
+ £2.70
VAT

Also available:
Digital Multimeters
Oscilloscopes
Signal Generators
Digital Frequency Meters
Pattern Generators
CRT Tester/Rejuvenator
T.V. Field Strength
Meter

U.K. Post Paid. Export orders welcome, please deduct V.A.T. and include an additional £5.00 for Overseas carriage. Mail Order only. Callers by appointment. Barclaycard/Access orders welcome, or Cheque, Bank Draft etc., with order please. Large S.A.E. for technical leaflets of complete range.

B. K. ELECTRONICS, Dept. 'T',
37 Whitehouse Meadows, Eastwood,
Leigh-on-Sea, Essex SS9 5TY.
Tel: (0702) 527572.

Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs - and they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

City and Guilds Certificates:-

Telecommunications Technicians,
Radio, TV and Electronics Technicians,
Electrical Installation Work,
Technical Communications,
Radio Amateur,
MPT General Radio Communications
Certificate.

Diploma Courses:-

Electronic Engineering,
Electrical Engineering,
Computer Engineering,
Radio, TV, Audio Engineering, Servicing and
Maintenance. (inc. Colour TV)
New Self-Build Radio Courses with Free Kits.

Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful - at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name.....

Address.....

..... Phone No:

ICS International Correspondence Schools,
Dept. 285P Intertext House,
LONDON SW8 4UJ. Tel. 622 9911
(all hours)

THE
TELEVISION
COLOUR PORTABLE
RECEIVER PROJECT

We will be offering all the components as specified by the magazine for this latest project.

All items down to the last nut and bolt are available separately or in kit form, with the exception of the p.c.b.

C.R.T. BASE BOARD

Full Pack ref. no. 48811 £3.95

TIMEBASE BOARD

Resistor pack ref. no. 37811 £3.85
Capacitor pack ref. no. 37812 £8.00
Semiconductor pack ref. no. 37813 £12.50
Miscellaneous pack ref. no. 37814 £27.50

All four of the above packs purchased together ref. no. 37815 £44.00.

For individual component price list of above, send s.a.e., quoting ref. no. 37815L.

**SWITCH-MODE
POWER SUPPLY**

Full pack ref. no. 15815 £28.75

For individual component price list of above, send s.a.e., quoting ref. no. 15815L.

**REMOTE CONTROL
INTERFACE AND C.D.M.**

Full kits available shortly.

**TV PATTERN
GENERATOR**

Full pack ref. no. 1081 TVP £36.50

For individual component pack please send S.A.E. quoting reference 1081 TVP.


All kit prices are inclusive of VAT, p.&p., for UK orders.

J|C electronics

TRIANGLE BUILDINGS, 234R GREEN LANES,
PALMERS GREEN, LONDON, N13 5UD
TEL. 01-882 3531

TELEPART

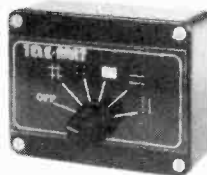13 WORCESTER ST.,
WOLVERHAMPTON,
WV2 4LJ
Tel: (0902) 773122
Telex: 336810



**Telepart
Pattern Generator**

- * Exceptionally light and durable
- * Pocket size for outside service
- * PP3 battery power source
- * Five different test patterns for colour and mono TV
- * Cross hatch grid
- * Dot matrix
- * White raster
- * Horizontals
- * Verticles

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)
POST & PACKING £1.04



**Telepart
Colour Bar Generator**

- * Exceptionally light & durable
- * Compact 13 x 17.5 x 5.5 cms
- * Battery powered for mobility
- * Cross hatch grid
- * White raster
- * Grey scale
- * Colour bars
- * Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.)
POST & PACKING £1.04

Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

**THE NO. 1 SOURCE
IN THE SOUTH**

Colour From £15
Mono From £2

BULK DISCOUNTS, DELIVERY ARRANGED.

1000's OF SETS TO CHOOSE FROM

TELETRADERS

ST. LEONARDS WAREHOUSE
ST. LEONARDS ROAD, NEWTON ABBOT, DEVON
Telephone: (0626) 60154

CARDIFF CENTREVISION

EX RENTAL T/V's

*In stock now. Philips G8 Thorn 3500

Philips K9 26" 110° VCR Position from 45.00
Capacity to supply 300 working sets weekly.
Large range of spares. Call and see our 4000 sq. ft. warehouse, you won't be disappointed.

Over 1,000 sets in stock

Unit 2 corner of Penarth Road and Hatfield Road.
Tel. Cardiff 0222 44754

**FANTASTIC
BONANZA**

Fresh stocks of TV's arriving daily - ALL MAKES, MODELS AND SCREEN SIZES For special offers call in or ring



PLEASE NOTE

THE OPENING OF OUR NEW DEPOT
AT WARRINGTON 2 MINUTES FROM
JUNCTION 11 ON THE M62 -
OPPOSITE BRITISH EMPIRE STORES -
GREAT OPENING OFFERS

Contact:
Des Walsh
WARRINGTON
21 Ravenhurst Court
Risley Road,
Birchwood,
Warrington
Tel: (0925) 817575

Contact:
Graham Ayres
LONDON
Cedar House,
Nobel Road,
Eley Estate,
Edmonton,
London N18
Tel: (01) 807 4090

Contact:
John Palmer
SOUTHERN
Watling Street,
Hockliffe,
North Dunstable
(On A5),
Leighton Buzzard
Tel: (0525) 210768

Contact:
Geoff Billett
WEST
Unit 4a, Bulwark
Industrial Estate,
Chepstow,
Nr. Bristol
Tel: Chepstow
(02912) 6652

Contact:
Sam Wilson
NORTHERN
Thornbury
Roundabout
Leeds Road,
Bradford 3
Tel: (0274) 665670

Contact:
Vera Wray
NORTHERN
Ebenezer
Chapel,
Fountain Street,
Morley
Tel: (0532) 532022

Contact:
Fraser Hunter
SCOTLAND
Peacock Cross
Industrial Estate,
Burrbank Road,
Hamilton
Tel: (0698) 282141

Contact:
Dave Harper
MIDLAND
48 52 Pershore Street,
Birmingham 5
Tel: (021) 622 1023

WITWORTH TRANSFORMERS

**TV LINE OUTPUT
TRANSFORMERS**

*BUY DIRECT FROM THE MANUFACTURERS
OF THE LARGEST RANGE*

OF LOPT'S IN THE COUNTRY:

**150 DIFFERENT TYPES IN STOCK
TOP QUALITY. COMPETITIVE PRICES**

All items new and guaranteed.

**Contact your nearest depot for service by return.
Callers welcome. Please phone before calling.
PHONE, OR S.A.E. WITH YOUR REQUIREMENTS.**

Tidman Mail Order Ltd.,
236 Sandycombe Road,
Richmond, Surrey.
Approx 1 mile from Kew Bridge.
Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm.
1.30 to 4.30 pm.
Sat 10 am to 12 pm.

Hamond Components
(Midland) Ltd.,
416, Moseley Road,
Birmingham B12 9AX.
Phone: 021-440 6144.

Mon-Fri 9 am to 1 pm.
2 pm to 5.30 pm.

FAST RETURN OF POST SERVICE

LOOK! Phone: LUTON
BEDS. 38716

**OPPORTUNITIES
TRADE SALES**

**ALL SETS GUARANTEED
COMPLETE**

OVER SIX HUNDRED SETS

ALWAYS IN STOCK

Pye 20T, Philips G8;

Ferguson 3-3k5

Murphy, Bush, Decca, GEC

All from

£35.00 £50.00

Square Screen, Mono's from

£5.00 ALL MODELS

Sets for spares from

£2.00

All include VAT

OPPORTUNITIES

9A, Chapel Street, Luton, Beds.

LUTON 38716

9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.

COLOUR BAR GENERATOR UHF AERIAL INPUT PATTERN GENERATOR

- ★ GREY SCALE VERTICALS ★
★ WHITE DOT MATRIX ★
★ HORIZONTALS CROSS HATCH ★



★ ADD ON PAL COLOUR BARS ★

Send SAE for full specifications.
Batteries not included.

PG6RF Kit **£28.75** Built **£37.95** ACCESS
C6 Kit **£20.75** Built **£29.90** ORDERS
CPG6RF Kit **£48.30** Built **£72.45** ACCEPTED



Price includes P&P and 15% VAT.
VHF versions available.
Full 12 month guarantee on built units.

MAIL ORDER ONLY FROM

TECHNALOGICS LTD. (Dept TV),
394 SCOTLAND ROAD,
TAYLOR STREET INDUSTRIAL ESTATE,
LIVERPOOL, 5.
051 207 3799

TELEVISION TUBE SHOP LTD

BRAND NEW TUBES AT CUT PRICES

A28-14W.....	£21.95	9AGP4.....	£21.82
A31-19W/20W.....	19.95	190AB4/C4.....	23.00
A31-120W/300W.....	17.95	230ADB4.....	28.50
A31-410W/510W.....	17.95	230DB4/CT468.....	26.60
A34-100W/510W.....	18.50	CT507 equiv.....	21.95
A38-160W/170W.....	17.50	CT512.....	27.50
A44-120W/R.....	27.00	310DGB4/DMB4.....	23.00
A50-120W/R.....	17.95	310EUB4.....	19.95
A59-23W/R.....	21.50	310EYB4.....	18.75
A61-120W/R.....	19.95	310FXB4.....	17.50
		310GNB4A.....	27.50
		310HCB4.....	27.50
		340AB4.....	22.50
		340AYB4.....	30.00
		340RB4/CB4.....	26.00
		340AHB4.....	26.00
		RIGONDA 6".....	14.00

**Some Rebuilt Japanese
& European Types
Available from
£14.00 + VAT £2.10**

COLOUR TUBES (NEW & MULLARD/THORN COLOREX)*

12VARP22.....	£62.50	A56-120X.....	£54.00
330AB22.....	73.50	A63-120X.....	69.50
A44-271X.....	60.00	A66-120X.....	65.00
A47-342X.....	63.00	A66-140X/410X.....	70.50
A47-343X.....	63.00	A67-120X.....	65.00
A49-191X.....	53.00	A67-140X/200X.....	69.50
A51-161X.....	67.00	A67-150X.....	75.00
A51-220X.....	55.00		

Old Bulb Required for Colourex


ADD 15% VAT TO ALL THE ABOVE PRICES.

ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED
52 BATTERSEA BRIDGE RD., LONDON, SW11.
Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10

LION TELETEXT PRESTEL ADAPTOR

why buy two separate adaptor's when one will do?

★ PRESTEL

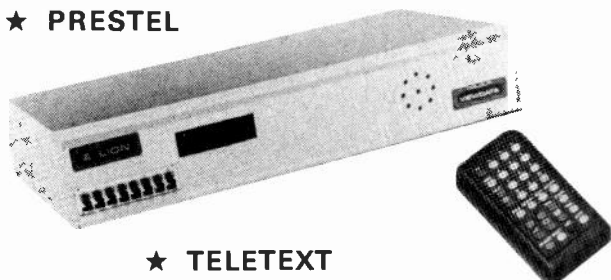

★ TELETEXT

Our adaptor has the plug-in Lion Teletext or Prestel and Teletext board which is used in our Television TXV 56 and our Ferguson Colourstar adaptor. Features include: Full Infra Red Remote Control, Printer Facility, Full alphanumeric Keyboard or microcomputer input, Cassette Recording Output, Autodial of Viewdata numbers, 8 Page Memory Option. Local Editing Facility and many other features.

Realistic Prices:

AXV03 **£250** AXV04 **£199** (teletext only)

LION TV

18 HARCOURT TERRACE, LONDON SW10
Tel: 01-373 5218

RADIO/TAPES BARGAINS

LW/MW Mains/Battery Radios **£9.00** each (P&P £1.00).
LW/MW Car Radios with Speaker **£9.00** each (P&P £1.00).
Small VHF/MW Battery Radios **£7.00** each (P&P 50p).
8-C60 High Gain Cassettes **£2.00** (P&P 50p).
5-C90 High Gain Cassettes **£2.00** (P&P 50p).
Stereo Headphones with Lead & Jack Plug **£4.50** (P&P 50p).

SIGNAL INJECTORS with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts dc. Complete with leads **£5.70** each.
All prices include VAT at 15%. P&P per order 30p. S.A.E. for leaflets. Access cards.

ELECTRONIC MAILORDER LTD,
62 Bridge Street, Ramsbottom,
Via Bury, Lancs. BL0 9AGT. Tel. Ramsbottom (070 682) 3036.

AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 - for mono or colour this is tunable over complete UHF television band.

B11 - for stereo or standard VHF/FM radio.

B12 - for VHF television band 1 & 3.

All amplifiers are complete and ready to use.

Battery type PP3 or 8v to 18v dc, next to the set type fitting. Prices **£6.70** each.

APOLLO

HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Just phone for a quotation. Delivery Manchester area free. Two year guarantee. Fitting while you wait or in your home £20 extra.

18"	A47 - 342x343x	£37.00
19"	A49 - 120x/192x	£37.00
20"	A51 - 220x/110x	£38.00
22"	A56 - 120x/123x/140x	£38.00
25"	A63 - 120x	£39.00
26"	A66 - 120x/A67 - 120x/140x/150	£39.00

These tubes replace many Toshiba types.

Callers welcome, please phone first.

061 799 0854 24 hour answering service.

Reg Office:

**43 Clarke Cres, Little Hulton,
Nr. Manchester M28 6XM.**

WMTV LTD. – THE TV PROFESSIONALS

With Discount TV's

- ★ Britains most reliable source of Quality T.V.'s.
- ★ Hundreds of working polished T.V.'s.
- ★ Full customer testing facilities.
- ★ Thousands of untested S/S Colour T.V.'s from **£10.**
- ★ Quantity deliveries arranged anywhere in Britain or the World.

MAIL ORDER TV's – Fully Tested

- ★ BRC 22"/26" **£70**
- ★ BRC 8000 17" **£65**
- ★ BUSH 184 22" **£40**
- ★ BUSH A823 22"/26" **£60**

Above MAIL ORDER prices include V.A.T. but please add **£12 p & p/T.V.Set.**

- ★ New T.V.Stands.
- ★ Fully adjustable.
- ★ **£6.25** plus **£1.75 p & p.**
- ★ Quantity discounts.
- ★ Price inc. V.A.T.



With Express Spares Service

★ Ex-equipment Panels

ALL PRICES INCLUDE VAT

	Con	Power	Line	Decoder	Video	IF	Frame	Tripler	LOPTX
RBM 823	7.00	6.00	14.00	14.00	—	6.00	9.00	3.00	3.00
BRC 3000	6.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
BRC 3500	9.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
GEC 2100	6.00	—	—	8.00	6.00	6.00	10.00	5.00	5.00
PYE 205	6.00	—	12.00	8.00	7.00	6.00	5.00	5.00	7.00

Postage & packing **£1.25** Panels **50p** Triplers

Ex-Equipment Valves

Untested

ECC82	10
PCF80	10
PCF802	9
PCL82	10
PCL84	10
PCL85/805	9
PCL86	10
PFL200	10
PL36	10
PL504	10
PL508	18
PL509	30
PL519	40
PL802	—
PY500	20
PY800/B1	10
PY801/88	10
30FL1/2	20

- ★ p & p paid but minimum order of £3.00 please.
- ★ Deduct 10% discount on orders over £20.00.

Ex-Equipment Colour Tubes

All fully tested

17" (A44-271X)	£18.00
18" (A47-342X)	£18.00
18" (A47-343X)	£18.00
19" (A49-191X)	£18.00
20" (A51-120X)	£25.00
22" (A56-120X)	£17.00
25" (A63-200X)	£10.00
26" (A66-120X)	£20.00
26" (A67-120X)	£17.00

Please add **£5.00 p & p** per C.R.T.

Equipment Spares

*Always available

- ★ Colour and Mono Scan Coils **£1.50** + **£1.00 p & p.**
- ★ Tuners for all makes of Colour and Mono **£4.00** + **£1.00 p & p.**
- ★ Mono Tubes fully tested. Callers only **£3.00.**
- ★ Reconditioned 50p meters **£92.00/Box of 10** incl. p & p.
- ★ PLESSEY SL918 colour ICs with ● circuit for substitution of SL917 **£2.00** + **25p p & p.**

WMTV LTD. 92 HIGH STREET, KINGS HEATH, BIRMINGHAM B14 7JZ TEL: 021-444 6464/2575

EMO – EUROSONIC – GRUNDIG – TELETON + ALL BRITISH MAKES ETC., ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE—TRADE ONLY

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX – EHT trays – droppers – OSC coils – switches – cans – smoothers – I.C.'s, etc., etc.

YOU CAN BE 95% SURE WE CAN SUPPLY ANY TV COMPONENT BY RETURN IF YOU NEED SPARES FAST – RING NOW!

ACCESS AND BARCLAYCARD ACCEPTED.

S.A.E FOR FREE WALL CHART

TELEPART (WTON) THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 773122

REBUILT CATHODE RAY TUBES

C.R.T. SERVICES LTD.

274 Chepstow Road, Newport, Gwent.

Tel. Newport (0633) 272005.

Also available from the following stockists:

L. R. Jones,
Manorbier,
Nr. Tenby.
Tel. 083-482 630

G.R.T.
Talwrn-y-Bont,
Pontrhydfendigaid,
Nr. Aberystwyth.
Tel. 09745 629.

N.G.T. COLOUR TUBES

First Independent Rebuilder with

B.S.I. CERTIFICATION

(Certificate No. 004)

2 year guarantee: 4 year option

All Colour Tubes are debanded, high temperature pumped and rebanded using new adhesives and new tension band.

19" **£30**, 20" **£32**, 22" **£33**, and 26" **£38.**


No exchange tube required on delta types.

N.G.T. ELECTRONICS LTD.,

120, SELHURST ROAD, LONDON S.E.25

Phone: 01-771 3535.

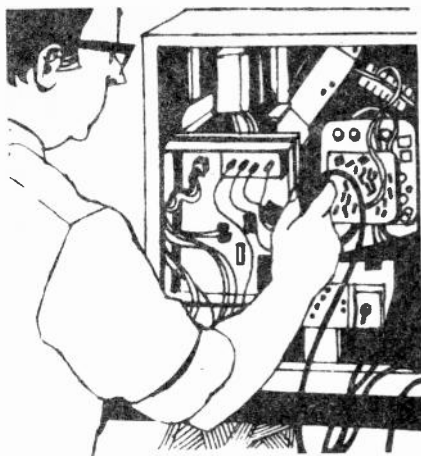20 years experience in television tube rebuilding. add VAT at 15%



SETS & COMPONENTS

EX-EQUIPMENT PANELS for most early single standard colour Televisions. SAE for list, Camber Television Centre, Lydd Road, Camber, Sussex.

QUALITY REBUILT TUBES

HIGH TEMPERATURE PUMPING

COLOUR (2 year Guarantee)

90° up to 19"	£33
90° 20" - 22"	£35
90° 25" - 26"	£36
110° and PIL	£40

MONO (including thin necks) from **£14.**

All prices + VAT

Delivery UK Mainland £6.

4 year Optional Guarantee

Send or phone for full list and terms.

WELTECH PICTURE TUBES

Unit 3-10 Wembley Commercial Centre, East Lane, Wembley, Middx. 01-908-1816

PHILIPS N1700 VIDEO CONVERSION KITS

5 HOUR DUAL SPEED RECORDINGS, EASY FIT - SUPERB PICTURE QUALITY.

NEW... ADD ON MODULE WITH FREEZE, PAUSE, FRAME ADV, SLO-MO & SEARCH.

For details of all our Philips conversions contact

EVANS VIDEO SERVICES
ON 061-439 8696... NOW

T.V.s FOR EXPORT

We have a selection of Bush and Ferguson colour T.V.s in good working order.

VHF/UHF suitable for countries using PAL system. We also supply The Home Market.

Write:

Tele Spares Ltd.,
7 Walkinstown Road,
Dublin 12, Ireland.
Tel: Dublin 520485.

SMALL ADS

The prepaid rate for classified advertisements is 29p per word (minimum 12 words), box number 60p extra. Semi-display setting £5.64 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

TELEVISION

R A D E

WE HAVE WAYS OF MAKING YOU BUY. WE ARE GOING TO THUMP YOU WITH BARGAINS, MAKE YOU SQUEAL WITH PAIN AT THE BIG DISCOUNTS, TWIST YOUR ARM WITH LOW PRICES.

NOW YOU'VE HAD ENOUGH, GET YOUR CASH AND A WAGON & COLLECT (OR YOU'LL BE SORRY!).

GENERAL FACTORS

GOOD MOTORWAY ACCESS
EXPORT ENQUIRIES

UNION ST, DONCASTER DN1 3AE
TELEPHONE (0302) 49583-68416

OPEN MON to SAT

TRIANGLE TELEVISIONS, Coleraine, N.I. Quality working sets. Clean cabinets, Decca, Bush, Kirting. Phone Coleraine 3600.

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

BILLINGTON VALVES, SAE lists. Probably the cheapest new guaranteed valves. $\frac{1}{2}$ KG electrical solder £4.95 p.p! 500 $\frac{1}{2}$ 2W resistors £3.00 p.p! Billington, 23 - Irwin, Horsham RH12 1NL.

Southern Valve Co.,

2nd Floor, 8 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. SAE Lists. Cash with order. Same Day Postal Despatch. (Mornings Preferred). Not Thurs.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 8 Potters Road, New Barnet, Herts.
Tel: 01-449 1834/5 (1934 Recording Machine).
Closed Thurs. Please phone for opening hours.

COLOUR T.V.s to the trade serviced or unserviced from £18. All sets full transistorised. 01-597 3872.

LOOK!

THORN 3000/3500 & 9000 TRIPLERS

High Quality Silicon Replacement Units
T3500 only **£4.95** inc. P.P. Add 74p V.A.T.
T9000 only **£5.45** inc. P.P. Add 82p V.A.T.
Quotes for 50+.

1 Year Guarantee

WING ELECTRONICS

15, Waylands, off Tudor Road, Hayes End, Middlesex.

GRUNDIG COLOUR, thyristor and valve sets. Export. Small quantities available. Also all tested panels etc. Telephone 0785 814643.

CAMPBELL ELECTRONICS LTD.

COLOUR T.V. PANEL EXCHANGE/REPAIR SERVICE

THORN, RANK, PHILIPS, GEC, DECCA, TELPRO, GRUNDIG etc.

90 Day Guarantee on all repairs - same day postal service.

Telephone Telford (0952) 502422
for catalogue and price list.

CAMPBELL ELECTRONICS LTD.,

Unit 5, Heath Hill Estate,
Dawley, Telford, Shropshire.

When replying to Television Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

COLOUR T.V.s

PHILIPS G8 COMPLETE

22" £45 26" £55

DISCOUNT FOR
BULK BUYERS

TEL: 965 1230 & 961 3997

**SMITH
ELECTRONICS**

43-43A, PARK PARADE,
HARLESDEN,
LONDON N.W.10.

Telephone: Northwood (Middx.) 27019 01-845 2036

RETACH LTD.

Rear 78 High St., Northwood, Middx.

NOW OFFER!!!

RANK 823 and THORN COLOUR from £20

ALSO

REBUILT COLOUR TUBES. From £28

2 year Guarantee.

ALL PRICES + VAT.

T.V. PATTERN GENERATOR

UHF output plugs straight into aerial socket no other connection required.

Features:

- ★ Crosshatch
- ★ White Raster
- ★ Grey Scale
- ★ UHF Output
- ★ Battery Powered
- ★ Pocket sized
- 100 x 75 x 40mm

Built ready for use £17.75.

Price includes P&P and VAT.

C. L. JERVIS

15 Mercer Grove,

Wolverhampton, WV11 3AN.

Tel. (0902) 23916.

TUBES £24

Re-gunned colour 20" (A51), 22" (A56) 1 year guarantee
2 FOR £46.

Ex-equipment factory tested 22" (A56)
£18 EACH 2 FOR £32 4 FOR £60
3 month guarantee

No need to spend £6 returning your old tube if you buy from us.

Delivery £6 each tube U.K. mainland.

Above prices inclusive.

U-VIEW (TUBES)

29, Warmsworth Rd., Doncaster,

Yorkshire DN4 0RP.

Tel: (0302) 855017

Callers ring first

SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.

Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBAND TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAIN'S LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

TRADE ONLY N. W. ELECTRONICS

Have for disposal large quantities of good class

COLOUR TVs,

Bush, Pye, GEC, Thorn, Hitachi, Philips, etc, (Ex Co-op). Not junk, very clean cabinets.

Genuine change over TVs and repossessions.

From only £20. Delivery arranged.

We export large quantities of TVs weekly, can we help you?

Call now and see our selection, over 1000 TVs to choose from.

N. W. Electronics, Bolingbroke Buildings,

Bolingbroke Street, Bradford 5.

3 Mins from Motorways.

Tel. 0274 390121.

CAMPBELL ELECTRONICS LTD.

Distributors of specialist spares to radio and television service depts.

We stock semiconductors, I/Cs, special T.V. and audio spares, service aids, rebuilt CRTs etc.

Fast off the shelf delivery of stock items.

Send S.A.E. or telephone for full catalogue and price list.

CAMPBELL ELECTRONICS LTD.,

Unit 5, Heath Hill Estate,

Dawley, Telford, Shropshire.

Telephone Telford (0952) 502422.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

LOPT TESTER

An entirely new instrument developed for checking Line O.P. transformers for shorted turns. It needs only one shorted turn on a LOPT to render it useless and this sensitive unit will detect it.

This will save every service workshop many hours every week in the increasingly endless elimination process of checking the Line OP stage and as often happens the unnecessary fitting of a new LOPT and putting the old one back.

Mains operated. Led indicators measures 4" x 3" x 1 1/2" with instructions and useful hints. £16.50 inclusive C.V.O.

Please note 3000-3500 Test set still available £15 inclusive.

J. BAKER & CO.

1, Old Shoreham Rd., Southwick, Sussex BN4 4RD
Tel. Brighton 593315

EXCELLENT QUALITY

USED COLOUR TV's

CHOOSE UNTESTED

OR FIRST CLASS

WORKERS ENGINEERED

IN OUR WORKSHOP.

TELFURB T.V. LTD.

WHEATLEY, OXFORD.

08677 3849

FREE DELIVERY T.V.

To many parts of U.K. Colour T.V. Pye 697 (i.e. 205). Guaranteed Good Working. £50 in 4's.

PLEAFORST LIMITED,

43 Hill View Road, Springfield, Chelmsford, Essex.
Tel. Chelmsford (0245) 353829 or 01-789 9468.

FOR SALE

NEW BACK ISSUES of 'Television' available 95p each post free. Cheque or uncrossed P/O returned if not in stock. - BELL'S TELEVISION SERVICES. 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

TVDX EQUIPMENT. System L TV sets for French TV from £45. Vhf/Uhf converter £10.50. BI mosfet preamplifier high gain, low noise. Mains powered £25.95. Band III type £25.50. Tunable masthead Uhf preamplifier plus set side power/tuning unit £35.00. Sae data. lists to: H. Cocks, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

BUSH 24"/20" S/S mono's. good working order, clean, polished. £10 each, minimum ten. Delivery anywhere (0706) 623404.

CASED ISOLATION TRANSFORMERS suitable for T.V. repair work £8.00 + £2.00 p.p. Ring Ardglass (0396) 841 631.

TELEVISION, all copies 1976 to 1980 inc. Offers, Hewitt, 25, Whincroft Way, Belfast. 791972.

COMMANDER-8 remote control system £10. Siemens FC365 CTV for spares/repair with manual £25. (0244) 671994.

TV ENGINEERS - Improve your efficiency by installing an Answercall Twin-tape P.O. Approved Telephone Answering Machine with remote Call-in. £229 inc. V.A.T. and delivery. Tel. (063876) 410.

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS,
CASSETTES, MUSIC CENTRES, ETC.

SERVICE SHEETS £1.25 PLUS S.A.E. SERVICE MANUALS ON REQUEST.

BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

TVT '80 TRANSISTOR EQUIVALENT & DATA BOOK. (A to Z). 295 Pages	£3.50
TVT '80 TRANSISTOR EQUIVALENT & DATA BOOK. (2N, 2S, ETC.). 440 Pages.....	£4.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King, Vol. 1	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King, Vol. 2	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King, Vol. 3	£9.75
COLOUR TELEVISION SERVICING by G. J. King, 2nd Edition	£9.80
COLOUR TELEVISION THEORY by G. H. Hutson	£7.95
LONG DISTANCE TV RECEPTION FOR THE ENTHUSIAST by R. Bunney.....	£2.35
AUDIO EQUIPMENT TESTS by G. J. King	£7.50
RADIO CIRCUITS EXPLAINED by G. J. King	£7.95
SERVICING WITH THE OSCILLOSCOPE by G. J. King, 2nd Edition.....	£7.20
TELEVISION SERVICING HANDBOOK by G. J. King, 3rd Edition	£7.95
BEGINNERS' GUIDE TO TELEVISION by G. J. King, 5th Edition	£4.00
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King, 2nd Edition	£4.00
CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett.....	£4.40
TELETEXT AND VIEWDATA by S.A. Money	£6.25
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR, 2nd Update	£10.35

COLOUR TV MANUALS

COVERING FOLLOWING MAKES
PLEASE SEND S.A.E. FOR QUOTATION

ALBA, BRC, BUSH, DECCA, GEC,
DEFIANT, MARCONI, EKCO, PYE,
FERGUSON, DYNATRON,
NATIONAL, HITACHI, INVICTA,
ITT/KB, RGD, GRUNDIG, SOBELL,
STELLA, SONY, MURPHY,
PHILIPS, HMV, ULTRA & OTHERS.

VCR SERVICE MANUALS

We can supply Service Manuals for the most popular makes
of Video Cassette Recorders. Please ring for a quote.

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.
FROM 1974-75 EDITION UP TO DATE. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 30p POSTAGE PER COPY.
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, ELECTRONICS TODAY, ELEKTOR

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. (HALF DAY WEDNESDAY) PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

Thousands of different full size service sheets Thousands of different manuals of all kinds in stock.

(Many of above are unique to us and obtainable nowhere else.) Any published single service sheet still only £1 + s.a.e.

British CTV circuit/layouts from dual to latest from Decca, GEC, ITT, Philips, Pye, Rank, Thorn, etc.
Continually updated - in 3 giant binders for only £39.50.

Revised foreign C.T.V. Repair System in 2 huge binders plus 3 Repair Manuals for £39.50.

Contains chassis from Grundig, Hitachi, Korting, Kuba, Luxor, Mitsubishi, National P., Nordmande, Sharp, Skantic, Toshiba, Zanussi.

Any Repair Manual only £6.50 for the first - £6 each thereafter.

Save £6.50 on complete set of 11 unique TV repair manuals - only £60. Mono + colour from dual standards to recent sets, McCourt & Tunbridge.

S.A.E. any quotation, also price lists, newsletter, bargain offers, details of our unique TV repair systems. Service sheets and all stock manuals by return of post.

Phone: 0698 883334, anytime. Callers 4-6 pm. weekdays, Saturdays 11 am.-1 pm. only.

G.T. TECHNICAL INFORMATION SERVICE
76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

30,000 SERVICE SHEETS IN STOCK COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £1.25. Tuners £1.25. Tape Recorders, Record Players, Transistors and Stereograms + S.A.E. from
£1.25 each. Also colour available. Car Radios £2.00 + SAE. All Radiograms FROM £1.25.

State if Circuit will do, if sheets are not in stock. All TV Sheets are full length 24 x 12, not in Bits & Pieces. All other Data full lengths.

Free Fault Finding Chart or TV Catalogue with order. Crossed PO's Returned if Sheets Not in Stock.

£2 Old Valve Radios.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882.

MAIL ORDER
SAE.

SERVICE SHEETS, Radio, TV, etc., 10,000 models.
Catalogue 25p plus SAE with orders-enquiries.
Telray, 5 Henderson Street. Preston PR1 7XP.

SANDHURST PUBLICATIONS

Television Service Sheet Specialists

Workshop Manuals, large selection Japanese TV
Sheets. Callers 5.30-6.30 pm. S.a.e. for catalogue
and enquiries:

49C Yorktown Road,

Sandhurst, Camberley, Surrey GU17 7AG.

SERVICE SHEETS, Radio, Television, Stereo etc.,
from 50p. Catalogue 25p. S.A.E. with orders, en-
quiries. Hamiltons, 47 Bohemia Road, St. Leonards,
Sussex.

COURSES

BE A COLOUR TV ENGINEER

Two years full time Higher Diploma
Course in Electronics, Colour TV and
V.C.R.

Next course commences Sept 81
and Jan 82.

APPLY:

Registrar, Reeswood College,
299a Edgware Road,
London W2 1BB.
Tel. 01-402 9985.

BOOKS & PUBLICATIONS

ANY PUBLISHED SERVICE SHEET £1 + S.A.E.
Thousands different repair/service manuals/sheets in
stock. Repair data your named TV £6.50 (with
circuits £8.50). S.A.E. Newsletter, price lists,
quotations. AUST, 76 Church Street, Larkhall,
Lanarkshire. (0698 883334).

OUT OF PRINT BOOK SERVICE, 17, Fairwater
Grove (E), Cardiff. Send S.A.E. for details.

PLANT FOR SALE

T.V. TUBE REBUILDERS: little used + in excellent
cond: 3 Hyvac 7 oil pumps + electric motors. 1
Raydyne induction heater type RD15 C/D. 1.5KW
complete with leads etc: Price £1200 o.n.o. Phone
evenings: after 7-30: 0980 610697.

PLEASE MENTION
TELEVISION
WHEN REPLYING
TO ADVERTISEMENTS

EDUCATIONAL

**TELEVISION COMPUTER
RADIOCOMMUNICATIONS
& RADAR SERVICING**

TWO YEAR full-time Modular Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- MICROELECTRONICS & DIGITAL TECHNIQUES
- MICROPROCESSORS & COMPUTERS
- RADIOCOMMUNICATIONS & RADAR

Each of the above Modules are 13 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £1575 per year (i.e. £525 per Module).

Next session starts January 4th.

Prospectus from:

**LONDON ELECTRONICS
COLLEGE**

Dept: TT, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721.

**BETTER JOB!
BETTER PAY!**

**GET QUALIFIED WITH ICS IN:
COLOUR & MONO TV SERVICING
COLOUR & MONO TV ENGINEERING
COLOUR & MONO TV MAINTENANCE**

PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,

NEW: Self-build radio courses with free kits

Train in your own home, in your own time with ICS, the world's most experienced home study college.

**RETURN THIS COUPON TODAY
FOR FREE BROCHURE!**

ICS Int. Correspondence Schools
284P Intertext House, Stewarts Road,
London SW8 4JJ. Tel: 01-622 9911

Name

Address

WANTED

V.C.R. TEST GEAR WANTED. Also dual trace scope. DMM frequency counter etc. 01-958 9292 (Edgware).

EX-RENTAL televisions wanted for export. Must be complete for refurbishing. Terms strictly cash. Phone 0272 775865.

WANTED COPIES "TELEVISION", '73 to '81 W.H.U. and price. T. McCrossan (E17A), Newtown-cunningham, Co. Donegal. Phone 56126

ENGINEER SEEKS T.V. BUSINESS or lock-up shop within 5 miles Edgware, Middx. Secondary position preferred. 01-958 9292.

PRE-PACKED. Screws, nuts, washers, solder tags studding. Send for price list. A1 Sales (TV), P.O. Box 402, London SW6 6LU.

THORN 2000 panels required. Phone Highcliffe (Dorset) 5711 evenings.

NEW VALVES and CRT's required, PCL805, PL504, PL509, PY500A etc. Cash waiting. Bearman, 8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

WANTED. Set of Newnes Radio and TV Servicing books. R. Gibson, Farndon 270809.

MISCELLANEOUS

C.E.D., C.R.T., tester reactorvator suitable for most types of colour and mono including P.I.L. and 20AX types. checks emission. detects and measures inter electrode leakage. incorporates a very effective boost facility. Not a kit but a professional instrument £85.10 inc. VAT. 10 day money back assurance. C.E. Developments. 54, Baronsmead Road, High Wycombe. Bucks HP12 3PG. Tel. High Wycombe 30307.

CENTURION BURGLAR ALARM EQUIPMENT. Send SAE for free list or a cheque/PO for £11.50 for our special offer of a full sized signwritten bell cover, to: Centurion Dept. T.E.L., 265 Wakefield Road, Huddersfield, W. Yorkshire. Access & Barclaycard telephone orders on 0484-35527.

RIGONDA AGENTS. For all spares and repairs. Fast despatch trade service available. 01-476 1928. Star Radio, 272 Barking Road, London E.13.

BURGLAR ALARM EQUIPMENT. Latest Discount catalogue out now. Phone C.W.A.S. Alarm. 0274 682674.

ADVERTISERS PLEASE NOTE

Our Box Number
Service is **NOT**
available for Mail-
Order Advertising

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for insertions. I enclose Cheque/P.O. for £
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME

ADDRESS

Send to: Classified Advertisement Manager,
TELEVISION,
Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846.
Rate
29p per word, minimum 12 words. Box No 60p extra.

Company registered in England. Registered No 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

DISPLAY ELECTRONICS

**LEADERS
IN TUBE
TECHNOLOGY
SINCE THE 60's.**

REGUNNED COLOUR TUBES 2 YEAR GUARANTEE

Up to 19"	£29.50
20"	£31.50
22"	£33.50
25"	£35.50
26"	£37.50

The above prices are for standard 38mm Delta Gun Types. Prices on application for P.I.L. Tubes etc. Some types available without pre-supply of glass at extra cost.

REGUNNED MONO TUBES 2 YEAR GUARANTEE

20"	£11.00
24"	£13.00

BUDGET CORNER

Buy any 5 mixed types Cash 'n Collect - Take 20% discount.

OR

Buy any 5 Mono mixed sizes Cash 'n Collect at **£8.50** (20") and **£10** (24").

PLEASE ADD 15% VAT.

CALLERS WELCOME

Late night Thursdays until 8pm Saturdays until midday.

N.B. Customers intending to collect orders are requested to telephone in advance:— even popular types may be out of stock for short periods.

V.D.U./RADAR TUBES

Home and export enquiries for Radar Display Tubes manufactured from new (with phosphors to specification) are invited.

**WATERLOO ROAD,
UXBRIDGE,
MIDDLESEX**

Telephone: Uxbridge 55800



**SHIELDWAY
LIMITED**
Quality rebuilt
Cathode Ray tubes

TYPE	PRICE
A44-271X	£36.00
A47-342/343X	£36.00
A49-191X	£36.00
A51-110X	£37.00
A56-120X/140X	£37.00
A63-120X	£37.00
A66-120X/A67-120X	£38.00

- All prices are inclusive of VAT. •
- All tubes guaranteed 2 years •
- Many inline types available •

U.K. Mail Order telephone for quotation.
.....
Delivery service available within a 20 mile radius of Bolton

**SWAN LANE MILL
HIGHER SWAN LANE
BOLTON BL3 3BJ.
TEL · 0204 64746**

STANDARD T.V. TUBE

**HIGH QUALITY COLOUR
REPLACEMENT TUBES AT
COMPETITIVE PRICES.**

- ★ Complete New Gun fitted to every Tube.
- ★ Two year Guarantee
- ★ Every Tube Electrically Tested.
- ★ Every Tube Picture Tested.
- ★ Supplier to Major Rental Companies.

18", 19"	£25
20", 22"	£27
25", 26"	£29

All prices quoted assume the return of your old glass rebuildable condition. Old CRT cash/cheque with order. Please add VAT at 15%.

S.STANDARD TV TUBE CO.
11-29, Fashion Street,
London E1

Tel. 01-247 3097

"TUBE REPLACEMENTS" PROUDLY OFFER

"WELLVIEW" EXCHANGE COLOUR

A44-271X	£29
A47-342X	£29
A47-343X	£31
A49-120X	£29
A51-110X	£29
A51-110LF	£31
A55-14X	£33
A56-120X	£33
A63-120X	£38.50
A66-120X	£38.50
A66-140X	£38.50
A67-120X	£38.50
A67-150X	£38.50

"WELLVIEW" EXCHANGE MONO

A44-120 WR	£11
A47-26 WR	£12
A50-120 WR	£11
A59-120 WR	£12.50
A61-120 WR	£13.50
A31-300 NEW	£15
A34-100-510 NEW	£16

All above plus VAT @ 15%.
Carriage £4.50 inc. VAT.

**ALL TUBES 18 MONTHS
GUARANTEE**

**ALSO YOUR VALVE SUPPLIER
NEW AND BOXED
(inclusive of VAT)**

DY802=74p	ECC81=64p	EF183=78p
EF184=64p	ECC82=64p	PCF802=98p
PCL82=78p	PCL84=92p	PCL805=97p
PFL200=£1.15	PCL86=97p	PL504=£1.38
PL509=£2.82	PL508=£1.30	PY88=70p
PY800=70p	PL509-19=£2.92	PY500A=£1.52

Postage and Packing 10p per valve. All orders over £10 Free of charge.

Colour Sets

1000 ex-rental TVs
Good sets good prices
Sets from £10 only
Bush, Pye, GEC,
Grundig, ASA, BRC,
Philips, Skantic
The prices will amaze
you.

TUBE REPLACEMENTS
Unit No. 1, Monmouth St.,
Bridgwater, Somerset.
Tel. 0278 425690-722816

EHT lead for split diode LOPT. £1.00	TLR 102 small red LED. 5p 20 small red LED. £1.00	NEW SONY KV.1400. Chroma Panel cost £60.00 £7.00 Tuner unit £3.50 Touch button unit with I.C. £3.50
6 push button unit UHF. For Pye £7.00	MAINS DROPPERS Thorn 50R-40R-1K5 50p Pye 69+161. 40p Pye 147+260r. 40p (731) 3+56+27r. 50p	FRONT END FOR MUSIC CENTRE VHF/MW/LW size 13x3½". 4 push button unit, 7 transistors, V/condenser, 10 coils rod aerial I/C decoder CA 758E (no power supply and output stage). Circuit supplied. £6.00 Output stage for music centre. £6.00
CVC 9 ITT Control panel. £4.00	CERAMIC FILTERS 5.5 MHz. 15p 6 MHz. 25p	AM/FM tuner unit (seconds). 50p
Philips TV IF Modules 38 Mc/s 1st and 2nd IF. each £1.50	3.5mm Jack socket. 7p	10 watt Mullard amps. NEW. £2.00
3500 6 push button unit for Thorn 3500. Varicap £1.00	NPN/PNP 60v 5 amp/80w. pair. 660-661. 20p	AT 1025/08 Blue lateral. 15p
6 position 12.5KV Resistor Unit for varicap. 50p	TV XTALS 4.433; 610 KHz. 50p	Thorn hearing aid unit for ext. loudspeaker. £2.00
I.T.T. (CVC 5) 7 push button unit for V/cap tuning £7.00	6 volt 23 watt soldering iron. £2.00	AD161/162, pair. 60p
New portable T/V chassis. Mono £10.00	Infra-red emitting diode, TIL30. 20p	731 PYE 600/300v, also Bush & GEC. 75p
New I.F. panel T/V 3 I.C. TBA750 & SC950 MSC950 £3.00	750 MFD 50V. 10p	EHT rectifier BY212. 10p 3X G770/HU37EHT. 10p
ELC 2000M New. £7.00	THERMISTORS 200+200+75+25 4 fuse holder +2BY133+resistors. I.T.T. panel. CVC 9. £1.50	EHT rec 2m/a small. 20p EHT rec 2m/a large. 30p
ELC 2060 New £7.00	ITT PT266 3W12 (Thermistor degausing) fits most sets. 15p PTH451A or B. 20p PT 37P. Fit Pye, Bush etc. 25p	Both 12KV. EHT rec used in Thorn 1400/1500 x 80/150 5p
V/U Meter 50p	H.T. thermistor neg. VA!104 35p	CSD 118xMH rec for Thorn 3500. 10p
GEC VHF/UHF 8CH touch tune units 41C 1xSN 29862N+1xSN 16861NG+2xCBF 16848N. £5.00	GEC 4700M/25v. 15p 22M/375v ITT. 20p	UHF T/V aerial for portable T/V 50p
New circuit supplied. CVC panel with pots and main switches 250K, 100K, 423 500K. £1.00	THYRISTORS Philips G11. G122M. 60p	Thorn TS 25-11TDT. £2.50 PYE TS25-11TBQ. £1.50 DECCA 80 £4.00
New (NSF/AEG) UHF/VHF Varicap tuner units. Cost £10. only £4.00	5 amp/300v. 25p 52600D 7 amp/400v. 30p RCA 40506. 50p	GEC Series 1028 2028 1040 1060 CS108 C2115 £4.00 G9 Tripler £4.00 CVC20/25/30 £3.50 Thorn 9,000 £4.00 Thorn 9,500 £4.00 GEC 2110 £3.50 GEC 2100 TVM25 £2.50 LP1194 731 Pye £3.50 Grundig TV52 £3.00 ITT BG100/41 £3.00 ITT BG100/61 £3.00
Convergence panel for GEC 2040, 11 pots, 5 coils, 2 resistors etc. New. £1.50	PYE 22N4444. 85p MR 501 3 amp/100v. 7p MR 508 3 amp/800v. 12p MR 856. 12p SP 8385 Thorn. 25p ELC 1043 AEG. £4.00	TS25-11TBW fits Autovox, Saba, Bang Olufson, Grundig, Tanberg. £3.75
PYE 731 6 push button unit and 100KA pots. £3.00	PHILIPS SNIPS: CUTS MOST THINGS. £1.50	Chroma Panel ITT, CVC 20.25.30.35.40. New £1.10
New circuit supplied with UHF 8ch Light action unit 4 i/c for Varicap tuning GEC C2001/C2201. £5.00	CO-AX plugs. 12p	Grundig 3000/3010, Seimens TVK 52. £3.00
GTE SYLVANIN F60B tuner unit. VHF/UHF £5.00 V/Cap	UHF Aerial socket and leads. PYE, ITT, THORN. 35p	ITT LP 1174/NC. £3.00
ITT Control Panel with Mains lead, 4 slider pots, Mains filter. £2.50	AE Isolating socket, UHF and lead, PYE, THORN, ITT. 35p	MULTI CAPACITORS 1000 + 2000/35v. 25p 2000 + 2000/35v. 30p 2500 + 2500/63v. 50p 150 + 200 + 200/300v. 70p
4 push button unit (for Varicap Tuning) 20K. 50p	GEC aerial T/V socket & lead 35p	
Philips T/unit UHF. £2.00	GEC Mains and battery switch. Or stand by. 30p	
Transistor UHF units with Ae socket and leads. GEC 2000 rotary type. £2.00	B9A print V/holder. 5p PYE 697 long. 15p	
Thorn UHF tuner unit and panel for 900 series. £8.00	TV 11 25p TV 13 25p TV 18 EHT. 40p	
Thorn 900 frame panel. £9.00	100k 40 turn pots for V/cap tuning. G9-G11 & Thorn. 20p	
Mullard VHF Tuner V/cap V314. £5.00	IF Mod CVC25 £5.00	
U321 T/unit V/cap. £6.00	ITT CVC23 Decoder £10 NEW	
U322 T/unit V/cap £6.00	ITT CVC20 Audio amp £1.50	
Thorn 3500. Thorn 8500 focus unit. Decca focus unit. Large or small. £1.00 each	ITT CVC20 Driver mod £1.50	
BUW 84 40p	ITT CVC9 Power supply board £1.50	
Decca Bradford Tuner, 5 button (4 push). £2.75	Neon Screwdriver 50p	
Line O/P Trans. CVC 20. £5.00	Mains on/off rotary. 13p Mains on/off push. 20p D/P push button on/off. 10p ITT mains on/off push button switches. 25p	
12" TV tube Hitachi A31/300W. £12.00	IF panel, Decca 5.5 £3.00	
SPEAKERS 5x 3 80r or 50r. 50p G5 70r. £1.00 5x3 35 ohm. 75p 6x4 15 ohm. £1.00 Philips G11 £1.00 GEC 8 ohm. 70p GEC 15 ohm. 70p	20 watt O/Put stage. £1.00	
NE 2B6H 2 small neon lamps used in GEC. 4p	DE-SOLDER PUMPS. £4.00	
Red and Green LED, 14 mixed. £1.00	ORP 12. 40p LP 1173/10 watt. £1.00 LP 1170. 50p	
		100 + 200/325v. 40p ELC1043 on panel for 400 + 200 + 200M 350v £2.00 600/250v 60p 175 + 100 + 100/350v to fit 3500 Thorn. £2.00 For T/V Sony Transformer & Lead & Sockets for earpiece. 8 ohms. £1.00 THORN SPEAKERS 1500 5½x2½ 3R 3500 7x3 80R 3500 5x3 80R 9000 7x3 16R 5x3 loudspeaker for GEC 15 £1.00 25 ohm 6x4 G11 Philips £1.00 UHF Modulator, CC1R. £3.00 Circuit supplied. Flush mounting socket. FM/TV 35p ELC 1042, Mullard. £6.00 ELC 1043/05, Mullard. £6.00 Moss Fits VHF/UHF D.X.T./Unit N.S.F. £10.00 Small DX Tuner V/cap 48-88 MHz and 175-220MHz automatic changeover. £5.00 New V/Cap tuner £3.50 50MHz to 300MHz Automatic Changeover Thorn Transductor. £1.00 Transductor AT4041/41 50p RANK TOSHIBA & ITT mains on-off solenoid switch. £1.50 R2540. £1.00 BUY 69 (RCA 1693). £1.00 THORN 1043 Tuner. New £5.00 Touch Buttons for Rank Toshiba 10p ITT Control Panel, 3 sliders, mains on/off. £3.50 FUA78M24UC 20p MC7724CP 20p TCE520 25p AF239 35p MTO309 Thorne 20p 25B566 10p 3500 Thorn CSD11 20p -1/1000V 15p TIP640 £1.00 25C2122A £1.00 SAS660 £1.00 SAS670 £1.00 TDA2541 £1.00 BRC1693 £1.00 TDA2522 £1.00

SENDZ COMPONENTS


63 BISHOPSTEIGNTON,
SHOEBURYNESS,
ESSEX SS3 8AF.

Reg. Office only.
Callers by appointment only.

Add 15% VAT.
Add 50p P. & P.

Add postage for all overseas parcels

VOLTS-OHMS-
MILLIAMPERES
MULTIMETER

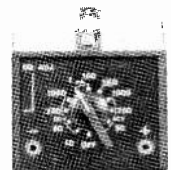

£4.00

1KΩ/V on DC/AC

