

JULY 1985

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50 **£1.10**

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS



**11GHz Low-noise Amplifier
VCRs and the Mains Supply
BBC Micro Test Pattern Program
Making PCBs • VCR Clinic
Approaches to TV Servicing
DX-TV • TV Fault Finding**

MANOR SUPPLIES

MKV PAL COLOUR
TEST GENERATOR FOR TV & VCR.

TEST
DEMONSTRATIONS
AT 172
WEST END LANE



- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.


Price of Kit **£70.00**
Case (10"×6"×2¼") app. **£7.40**
Optional Sound Module (6MHz or 5.5MHz) **£3.90**
Built & Tested in Case including Sound Module £105.00

SPECIAL TEST
REPORT
'TELEVISION'
DEC. 1982

Post/Packing £2.50
Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

4TH SUCCESSFUL YEAR

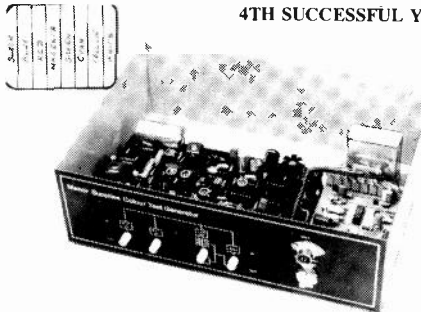

- ★ Output at UHF, applied to receiver aerial socket.
 - ★ In addition to colour bars R-Y, B-Y etc.
 - ★ Cross-hatch, grey scale, peak white and black level.
 - ★ Push button controls, battery or mains operated.
 - ★ Simple design, only five i.c.s on colour bar P.C.B.
- PRICE OF MK 4 COLOUR BAR GENERATOR KIT £30.00. CASE £7.40. BATT HOLDERS £2.80. MAINS SUPPLY KIT £4.20 (Combined P&P £2.20).**

MK 4 (BATTERY) BUILT & TESTED £58.00 + £2.20 P & P.
MK 4 (MAINS) BUILT & TESTED £68.00 + £2.20 P & P.
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS £5.75.
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

GEC TELETEXT EXTERNAL ADAPTOR UNIT
Complete & ready for use. Converts any TV into a Teletext Receiver with Infra-Red Remote Control (incl. 25 Button Handset) **£130.00** p.p. £3.00
TELETEXT EXTERNAL ADAPTOR KIT (Less case) TEXAS
with cable remote control **£120.00** p.p. £3.00
THORN TX10, teletext
Mullard Decoder panel + Interface **£35.00** p.p. £1.80
THORN TX10, PHILIPS G11 PRESTEL
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£60.00** p.p. £2.50
Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15%

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

LOPTs, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

SPECIAL OFFER GEC-Hitachi NP8CQ Chassis Colour TV Chassis, New Boxed **£35.00** p.p. £3.00
SPECIAL OFFER Philips, Pye KT3 Series infra-red remote control handsets ex rental (untested) Teletext or normal versions available **£2.50** p.p. 80p (£ for £10 p.p. £1.50). CTX, K35 Teletext + Video **£5.00** p.p. 80p.
THORN 9000 Fault Finding Guide **£1.00** p.p. 30p.
SPECIAL OFFER NEW VALVES Branded makes
PCF80, PY88, PFL200, PCL84 FOUR for **£2.00**. PL504 **£1.00** p.p. £80p
TX10 Remote & Tuning control panel (1515) **£9.40** p.p. £1.50
THORN TX10 Facia Control Panel incl. Infra Red Remote Control receiver **£7.50** p.p. £1.50.
THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£5.00** p.p. £1.50.
PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. £1.00.
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£29.50** p.p. £1.20.
THORN TX9, TX10 Saw Filter IF Panel. **£7.50** p.p. 80p.
PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. £1.00.
PAL ENCODER KIT (RGB to Video) **£18.50** p.p. £1.30.
TELETEXT DECODERS New & Tested Mullard VM 6101 **£30.00**, Texas XM11 **£40.00**, KT3 Tested **£30.00**, Untested **£5.00** p.p. £1.60
TELETEXT 23 Button De-Luxe Handset with 5 yds Cable. **£2.50** p.p. £1.20.
5V Stab. Power Supply **£3.80** p.p. £1.20.
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. £1.40.) **ADDITIONAL GREY SCALE** Kit **£2.90** p.p. 45p.
UHF SIGNAL STRENGTH METER KIT **£22.00** (VHF version **£24.00**). Alum. Case **£2.55**, De Luxe Case **£7.40** p.p. £1.80.
CRT TESTER & REACTIVATOR KIT For Colour & Mono with Panel Meter Indicator - can be adapted for latest CRTs **£28.60** p.p. £2.80.
BUSH A823 Convergence, Time Base Panels **£5.00** each. p.p. £1.80.
BUSH Z718 BC6100 series IF Panel **£5.00** p.p. 90p.
BUSH A816 IF Panel (Surplus) **£1.00**, 5 for **£4.00**.
GEC 2040 Convergence Panels, Decoder Panels. **£1.50** p.p. £1.80.
GEC 2110 PANELS Frame **£8.50** p.p. £1.40. Sound **£2.50** (tested) p.p. 80p.
GEC 20AX Switch Mode Power Supply **£5.00**, IF-Decoder **£12.50** p.p. £1.80.
PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. £1.45.
THORN TX9 Panels; ex factory for small spares. Includes I.Cs & Semiconductors etc. **£5.00** p.p. £2.00.
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. £2.80.
THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. £2.80.
THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. £3.00.
THORN TX10 IF/Decoder Panels salvaged ex factory. **£15.00** p.p. £2.00.
THORN 3000/3500 Power supply P.C.B. **£3.50** p.p. £1.00.
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. £1.80.
THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. £1.60.
THORN 9000 Series. Long panel facia unit incl. 6 Position Channel Selector & Loudspeaker **£6.00** p.p. £2.00.
PHILIPS G8/G9 IF/Decoder Panels for small spares incl ICs **£2.50** p.p. £1.60.
G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00** p.p. £2.50 (tested).
G11 PANELS, Power, Frame, IF, Decoder, **£18.00** each. p.p. £2.00 (tested).
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. £1.00.
VARICAP, ELC1043/5 **£7.80** p.p. 80p. Makers Controls **PYE CT200** 4PSN **£7.50**, **BUSH 4PSN** **£4.30**, **DECCA 4PSN** **£5.80**, **6PSN** **£6.80** p.p. 80p. etc.
BUSH "TOUCH TUNE" Varicap Control Z179, Z718 types **£3.80** p.p. 95p.
VARICAP UHF-VHF ELC2000S **£9.80**, **BUSH** **£7.80** p.p. 90p.
VARICAP VHF PHILIPS. **£6.90**, **ELC 1042** **£7.90** p.p. 80p.
UHF/625 TUNERS, many different types in stock. **DECCA** Bradford 5 position, **MULLARD** 4 position **£2.50**, **JAP** Rotary **£4.80** p.p. £1.80.
TV SOUND IF Panels **£6.80** p.p. £1.00.
LOPT TESTER, Service Dept approved **£15.90** p.p. £1.20.
LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins 80p.

BUSH 161 to 186 (twin panel)	£5.90	R.B.M. Z179	£9.80
BUSH, MURPHY 774 series	£8.50	R.B.M. T20, T22	£9.80
BUSH, MURPHY A816 series	£9.80	R.B.M. T20, T22 Bobbin	£5.60
FERG., HMV, MARCONI, ULTRA		DECCA Bradford (state Mod No)	£8.80
1400, 1500, 1590, 1591	£5.90	DECCA 80, 100	£8.80
THORN 1600, 1615, 1690, 1691	£9.15	GEC 2110 series	£10.60
GEC 2000 to 2038 series	£6.80	ITT CVC 5 to 9, CVC20	£9.80
GEC series 1 & 2	£8.00	ITT CVC25, CVC30 series	£9.80
INDESIT 2024EGB	£7.65	ITT CVC45	£8.80
ITT/KBVC200, 300	£7.65	PYE 691-697 (state model no.)	£10.00
MURPHY 1910 to 2414 (twin panel)	£5.90	PYE 713, 715	£6.80
PHILIPS 170, 210, 300 series	£7.65	PYE 725 (90°) 731 to 741	£9.20
PYE, INVICTA, EKCO, FERR.		PHILIPS G8	£8.80
368, 169, 569, 769 series	£7.65	PHILIPS G9	£10.80
		PHILIPS 570, 571	£6.80
		PHILIPS KT3	£9.80
		THORN 3000/3500 SCAN, EHT	£6.90
		THORN 8000, 8500, 8800	£12.80
		THORN 9000 to 9600	£12.90
		THORN TX9	£14.80

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO LOPTS, TRIPLERS Full range available. Mono & Colour.
Special Offer: Thorn 8000 (2 lead) EHT Tray **£2.80** p.p. 80p.
6-3V CRT Boost Transformers for Colour & Mono **£5.40** p.p. £1.20.
THORN TX10 focus control **£8.80** p.p. 80p.
THORN 8000 mains input choke **£6.80** p.p. £1.40.
CALLERS WELCOME AT SHOP PREMISES
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
TELEVISION MAGAZINE PROJECT PARTS & REPLACEMENTS
STILL AVAILABLE
Telephone 01-794 8751, 794 7346


MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
W. Hampstead British Rail Stns. (Richmond, Broad St) (St. Pancras, Bedford)
W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

PLEASE ADD VAT 15% TO ALL PRICES

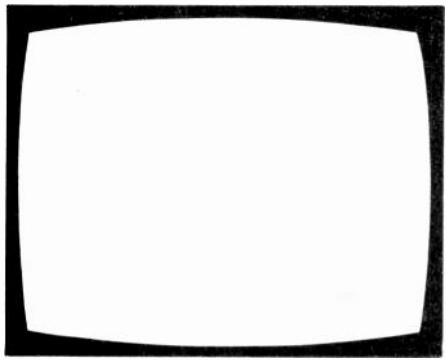

TELEVISION

July
1985

Vol. 35, No. 9
Issue 417

COPYRIGHT

© IPC Magazines Limited, 1985. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £13 in the UK, £15 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 483 Leader**
- 484 Letters**
- 489 Big Foot** *Les Lawry-Johns*
Someone seems to be getting error prone. He might even end up in court.
- 490 Teletopics**
News, comment and developments.
- 492 11GHz Low-noise Amplifier** *Hugh Cocks*
Building and testing a low-noise amplifier for satellite TV reception in the 11GHz band. The unit provides a gain of 25dB or better with a noise figure of around 3dB.
- 496 VCRs and the Mains Supply** *Derek Snelling*
VCRs are prone to a number of faults due to defective mains supplies. Symptoms and remedies.
- 497 Approaches to TV Servicing** *S. Simon*
One can work through test procedures that will eventually reveal the causes of most faults. Or one can assess the symptoms carefully and take short cuts based on experience. The latter course can save a great deal of time. Advice with examples based on common chassis.
- 499 Next Month in Television**
- 500 The Lid off Microcomputers, part 3** *Mike Phelan*
This time a look at the basic system – CPU, memories, etc. – used in the Amstrad CPC464 microcomputer.
- 502 TV Fault Finding**
Reports on TV faults and servicing from J. K. Potts, David Rainey, Mick Dutton, Philip Blundell, Eng. Tech., Stephen Howe and Malcolm Burrell.
- 506 VCR Clinic**
Reports on video faults from B. Ross, Steve Beeching, T. Eng., Derek Snelling, John Coombes and Philip Blundell, Eng. Tech.
- 508 Long-distance Television** *Roger Bunney*
Reports on DX conditions and reception, news from abroad and notes on DX equipment.
- 511 Making PCBs** *Malcolm Burrell*
A simple approach based on experience gained from producing boards for prototype equipment.
- 512 More on the Philips G8 Chassis** *Dennis Apple, B.Sc.*
Notes on servicing and fault finding. These sets can still give years of reliable operation if carefully serviced and adjusted.
- 514 Sonys and Suchlike** *Nick Lyons*
What have we done to deserve some of the odder problems that come our way? Sonys, a Contek portable and a troublesome monitor.
- 516 BBC Micro Test Pattern Program** *Patrick Kniveton, B.Sc.Eng.*
A program that provides most of the patterns normally produced by a TV pattern generator including a composite test card with circle.
- 518 Service Bureau**
- 519 Test Case 271**

OUR NEXT ISSUE DATED AUGUST WILL
BE PUBLISHED ON JULY 17

P. V. TUBES

HAVE MOVED

Just phone
your order
through, we
do the rest.

Buy with



Telephone: Accrington (0254) 36521
Accrington (0254) 32611
Telex: 635562 Griffin G (For P.V.)

104 ABBEY STREET, ACCRINGTON, LANCOS BB5 1EE.

SUPPLIERS
OF TELEVISION COMPONENTS

TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TRADE COUNTER CLOSED WEDNESDAY p.m.

VARICAP TUNERS	SWITCHES & ACCESS.	DID YOU KNOW WE'VE GOT LOTS OF NEW THINGS!	PHILIPS KT3 SPECIFICS	SPECIFIC COMPONENTS
ELC1043-05 8.40 ELC1043-06 8.40 ELC2003 16.50 Philips G8/G9 10.50 Philips G11 (U321) 8.50 U322 7.20 U341 9.50 Rank T20 13.00	On/off gen. purpose 4A 75 G8 on/off 1.38 G11 on/off 1.58 G11 on/off remote 1.58 Gen. purpose rotary 66 Thorn TX 9/10 1.06 GEC 2040 98 Thorn 1591 push on/off 2.90 Rank tuner buttons 1 1/2" x 1/2", 2" x 1/2", 2" x 3/8" Rank drive cams 35 GEC 2110 tuner neons 15 Thorn 3500 A1 beam 20 GEC 2110 A1 cont. R/B/G 70 ITT CVCS on/off 58 ITT mains switch + solenoid 4.50 Rank mains switch + solenoid 4.50 Rank T20 on-off switch 1.95	Decca speaker 8R 3.75 B+K tube bases Dynascan No. 3 9.50 No. 13 11.11 No. 6 11.08 No. 23 13.86 No. 8 10.08 L5 7" x 3 3/8" speaker 4.25 C15 computer cass. 30 C20 computer cass. 33 5 1/4" floppy disc s/s s/d 1.61 15R fused res. G9 1.24 G11 line in coil 2.95 G11 pot G2 R.G.B. 5.30 G11 line scan panel 54.00 G11 power panel 37.50 G11 timebase panel 37.50 G11 bridge trans. 97 G11 EW correc. coil 1.95 G11 final anode lead 1.50 G11 focus unit 5.80 G11 39R 3W resistor 60 G11 RGB 10G diodes 50 Televerta up converta 37.20 G11 47K pot plus switch 65	KT3 posistor 1.50 Mains electrolytic 225/25 380V 2.50 Selector unit Mod. 933 13.42 On/off switch Mod. 933 3.20 Tripler 10.65 Luminance chroma panel 24.00 R.G.B. panel 14.95 U321 IF module 13.50 U321 IF module 10.30 Sound panel 8.50 Power panel 10.60 Mains input panel 14.30 Line sync panel 10.20 Mark I chroma panel 16.50 Sound module 8.50 LOPT 9.70 Focus unit 3.70	Philips G8 knobs sm/Ag 50 90" transductor 2.60 Thorn 1591 speakers sm 6.20 lg 6.20 Thorn 1500 controls 59 390K frame 470K line contrast 1k5 each Focus control Thorn/GEC 1.83 Thorn 9000 focus unit 5.95 Thorn 8500 focus unit 4.75 Thorn Tx10 focus cont. 9.00 Decca bridge trans. 1.97 Decca 30 width cont. 50 Decca 2M2 HT cont. 25 Rank T20 focus cont. 2.20 Pye 731 HF choke 6.50 Delay lines DL20, DL60, DL70, DL50 2.20 CRT tube base 1.40 EHT final anode cap 53 6.3V CRT boost trans. 5.80 Focus rod 1.25 Focus holder 2.00 AFC unit G8 8.82 IF gain module 9.00 C.D.A. panel 20.00 G8 rear conv. panel 23.00 Philips K35 Tuner drawer 10.00
PUSH BUTTON ASS. Decca 4 way 6.88 6 way 7.50 GEC 2110 6 way 7.98 GEC Slim 6 way 6.50 GEC/ITT/PYE 7 way 14.50 Pye 4 way (713/15) 9.00 Pye 6 way (207/715) 16.00 Pye 697 repair kit 9.00 Pye 725-735 11.00 Pye 725-735 with tuning head 14.60 Philips G8 (early) 15.50 Philips G8 (late) 13.90 Rank A823 10.75 Rank T20A 9.75 Hitachi 4 way 10.75 Philips G11 unit 26.50 Philips KT3 14.50 Philips KT30 10.30 ITT CVC 8/9 (mod) 12.00 ITT 6 way with VCR 8.90 Thorn 9000 switchback 5.30 Decca 7 way piano key replacement kit 19.50	EAGLE MULTIMETERS KEW 7N 6.75 KEW 14 9.00 KEW 20 14.50 EM5 11.95 EM20A 15.95 EM10 13.95 MM50 31.25 Bench Meters MM100 44.50 MMT20 21.50 MM150 75.00 T1206 intercom 8.50 MMC100 21.95 Case TS350 21.95	SUNDRY EQUIPMENT Test Lead Set 4.20 Degaussing Coil Stick 17.00 Signal Injector 4.00 Elect. Circuit Tester 1.50 5A Choc Bloc (12) 40 Fuse Wire 5A, 15A, 30A 05 4-way 13A Mains Conn. 5.00 Safe Block (mains) 8.50 13A Plug Top (box 10) 4.80 Probes (x10) 10.90 Probes (x1) 10.90 Bell Wire (100m) 5.00 Mains Cable (circular 100m) (2 core) 10.75 (3 core) 13.25 Factory recon. Avo meters 119.00 Avo Batteries 2.95 Vero Board 2.59 Isolating trans. 500vA 240V 40.00 Solder 500g 7.00 D.I.Y. Solder 45 Solder Sucker 6.50 Nozzles 81 Trim Tools 16 Plastic Metal End 30	K30 SPECIFICS K30 LOPT 17.50 K30 focus unit 2.90 K30 EHT lead 8.30 Selector unit 1002 (early) 11.20 TMS 1000 panel 1234 13.00 Euro decoder panel 1234 46.00 Power supply 1234 23.50 A1 gun switches 70 On/off switch 2.60 Selector unit 1002 (late) 9.90 Hand set 1201 16.00 Hand set 1234 16.00 Diode ZTX 33B 90.00 DL 20 delay line 2.20	PLUGS Phono Plugs 12 DIN Plugs 3 pin 22 4 pin 22p 180° 5 pin 20p stnd 5 pin 20 Car Aerial Plug 18 2.5mm Jack Plug 14 3.5mm Jack Plug 14 Stand Jack Plug 20 Stereo Jack Plug 36 Coax Plugs each 18 ten 1.80 PL259 4.00 Reducers for PL259 16 Line Connectors 16 BNC Plugs 1.15
SERVICE AIDS SERVISOL Freeze-It 1.14 SUPER SERVISOL 98 SERVISOL Foam Cleanser 96 SERVISOL Plastics Seal 1.08 SERVISOL Silicone Grease 1.20 SERVISOL Tubes Silicone Grease 1.64 SERVISOL Aero Klene 90 SERVISOL Aero Duster 1.20 SERVISOL Excel Polish 92 SERVISOL Video Head Cleanser 86 Super 40 1.62 Fire Extinguisher 640G 2.86 Heat Sink Compound 25G 1.08 Silicone Rubber Tube 110G 2.98 Solda Mop standard reel 74	ANTEX SOLDERING EQUIPMENT C15W Iron 240V 6.20 C240 Element 2.75 Bits 102 1.10 106 1.10 820 1.10 821 1.10 CS17W Iron 240V 6.40 CS240 Element 2.75 Bits 1100 1.10 1101 1.10 1106 1.10 XS25W Iron 240V 6.50 XS240 Element 2.75 Bits 50 1.10 51 1.10 Temp. Controlled 30W Iron CSTC 16.95 40W Iron XSTC 16.95 Unit for above TCSU1 68.95 Stand 2.10 MLXS Auto Repair Kit 8.40	IC equivalent booklet £2.25 and transistor equivalent booklet £3.25	CATA BOOKS (Zero VAT) Pair of A-Z/2N2S TVT80 8.50 LIN IC Books (data only not equiv.) 5.95 LIN1 7.95 2M Fly Lead 2.95 4M Fly Lead 1.20 10M Fly Lead 1.90 Figure 8 Mains Lead 62 Computer to TV 97 7 pin din to 5 pin din 98 5 pin din to 5 pin din 98	CASSETTE DRIVE BELTS 35m 35 46mm 37 57m 37 66m 39 110m 59 76m 43 90m 43
ELECTROLUBE PRODUCTS Electrolube Adhesive 62 Electro-Mech lubricant 1.49 Elect. cleaning solvent 1.62 Freezer 1.49 Foam cleanser 1.12 Heat transfer compound 1.14 Silicone compound 1.94 Special contact fluid (Snorkell) 3.20 Permagard 1.52 Elec. mech. lubricant pen 74	WELLER Heat gun 12.00 Heat gun tips (pair) 57 3/16" Iron tips 25W (MT5) 57	OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, LOCAL AUTHORITIES ETC.	P.V. MICROCOMPUTER CENTRE Why not pay us a visit and see our range of Micros, Software Books and Peripherals. Please ring for prices. Spectrum 48K Amstrad Sanyo and QL Commodore 64 We are also authorised dealers for the BBC Micro and accessories.	
VIDEO Video care kits 3.50 VHS E30 video tape 3.06 VHS E60 video tape 4.00 Schoot E120 video tape 5.00 E180 video tape 4.50 Beta L500 video tape 4.90 Beta L750 video tape 5.80 VCC 240 6.20 VCC 360 8.30 VCC 480 10.21 Philips LVC 1700 1200 15.10	LABGEAR CM7261 Power Unit 12V 11.24 CM7262 Reg. Power Unit 12V 12.25 CM7060 MHA 10db 12V W/B 9.86 CM7065 VHF/UHF MHA W/B 12V 14.34 CM7066 13.38 CM7067 UHF 12V MHA (Specify A-B or C/D) 10.72 CM7068 UHF 12V MHA High Gain (Specify A-B or C/D) 15.95 CM7053 Behind Set UHF Amp. (Mains) 13.01 CM7054 Behind Set UHF Amp. (Battery e.g. Caravans) 10.42 CM7043 Second Set Amp. UHF 12.12 CM7093 Behind Set UHF Amp. 3 Sets 15.27 CM7063 Dist. Amp. VHF/UHF 17db/output 12V 22.17 CM7108 VHF/UHF 8+1 Dist. Amp. 43.26 CM9700 27mhz CB Suppress. 4.05 CM6011 Unit On/Off Splitter (2 way) W/B 7.83 CM9003 Flush Single Outlet 1.47 CM9010 Flush Twin Outlet 1.95 CM9034 UHF Group Filters with DC Through Pass (state A/B/CD) 7.69 CM6006 6 Way Passive Splitter 10.97 CM7042 TV Games Combin. 2.95 CM9009 Flush TV/FM Outlet 3.05 CM7091 Col. Bar Gen. 121.80	WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER	SHEILA'S SURPRISES SHARP VIDEO HEADS £55 VC2300 VC6300 VC7300/7700/7750 VC8300 VC220/381/383/388/9100/9300/9500 VC3300/9700 SANYO VIDEO HEADS £53 VTC 9300/9500 VTC 5300/5000 VTC 5350 VTC 5500 VTC 9350	
VIDEO RECORDER HEADS Philips V2000 57.00 Philips 1700 57.00 Video lamps 1.30 Video lamp holders 3.30		AERIAL EQUIPMENT Outdoor Splitter 5.50 Plastic Tape 50 F.M. Plugs 25 Set Top Aerial 2.30 Loop Aerial 1.00 Mast Amp/Power Unit WB 18.00 Aerial Isolator Kit 2.08 Attenuator 6dB, 12dB, 18dB 1.80 27MHz Filter 50dB 2.10 Cable Clips 7mm per 100 1.18 Single Outlets 80 Surface Splitter 1.70 A Splitter 70 100M Coax 15.00 Coax Plugs per 10 1.80 1" U Bolts 30 J Bolts 25	REMOTE CONTROL HAND UNITS Decca 100/101 Ultra Sonic Non Teletext £23.80 Grundig Telepilot 12 Series Infra Red £13.87 Grundig Telepilot 8 Series Infra Red £25.10 Grundig Telepilot 160 Series Infra Red £25.10 Grundig Telepilot 300 Infra Red £18.87 Philips KT3/K30 Infra Red Non Teletext £18.87 Philips G11 Ultra Sonic Non Teletext £22.00 Philips G11 8 Way Infra Red Teletext £23.80 Philips G11 Ultra Sonic 31 buttons £27.00 Philips G11 Ultra Sonic 2 function £21.00 Thorn TX10/JVC Infra Red Teletext £18.87	
VIDEO DRIVE BELT KITS JVC HR3330/3600 4.50 JVC HR3360/3660 4.50 JVC HR7650 4.50 Panasonic NV/300 4.50 Panasonic NV/7000 4.50 Sony SL7/SL7 4.50 Sony SL8000/8080 4.50 Toshiba V7540 4.50 Ferguson HR3330/3600 4.50 Video head cleaner 86 Sanyo video motor 20.00	STATIONERY Service Call Pad (100) 1.20 Repair Ticket (100) 3.90 Job Card (100) 2.50 Rental Payment Card (50) 3.50 H.P. Agreements (100) 3.50 Maintenance Agreement (100) 3.50	ANTIFERRENCE SB11 Splitter 2.37 COB11 Outlet 96 CS1000 Combiner/Splitter 6.15 PU1240 Power Unit 11.65 UP1300 MHA 9.09 XS2U Xtraset 14.56 4 way VHF/UHF Amp 40.71 6 way VHF/UHF Amp 50.68 XGB High Gain Aerial A-B-CD-WB 17.10	PLEASE ORDER FROM LATEST COPY OF MAG. TO AVOID PRICE INCREASES	
AUDIO HEADS AND MOTORS Mono record/playback 4.32 Stereo playback 4.79 Stereo record/playback 4.99 Stereo record/playback (Dolby) 6.90 Mono/stereo erase 2.25 Electronic/rotation clockwise motors 6V MD6515 4.95 9V MD9516 4.95 12V MD12517 4.95				

P. V. TUBES

TEL: 0254
36521/32611

104 ABBEY STREET, ACCRINGTON

T.T.L. 74LS SERIES				VOLTAGE REG.							
74LS00	58	74LS37	35	74LS92	65	74LS160	90	74LS245	2.30	7805	78
74LS02	58	74LS38	35	74LS93	60	74LS161	85	74LS251	65	7806	78
74LS03	58	74LS40	35	74LS97	80	74LS162	4.04	74LS253	95	7808	78
74LS04	58	74LS42	80	74LS109	58	74LS163	85	74LS257	1.20	7812	78
74LS05	58	74LS47	85	74LS112	50	74LS164	85	74LS258	95	7815	78
74LS08	58	74LS48	83	74LS113	44	74LS165	1.50	74LS259	1.70	7818	78
74LS09	58	74LS49	83	74LS114	70	74LS173	1.32	74LS273	1.90	7824	78
74LS10	58	74LS51	33	74LS123	80	74LS174	85	74LS283	1.30	7825	68
74LS11	58	74LS54	43	74LS125	85	74LS175	85	74LS293	1.20	78L08	68
74LS13	37	74LS55	60	74LS126	60	74LS191	1.02	74LS352	1.40	78L12	68
74LS14	46	74LS73	60	74LS132	63	74LS192	1.30	74LS353	1.40	78L24	68
74LS15	33	74LS74	65	74LS138	83	74LS193	1.30	74LS365	75	7905	98
74LS20	35	74LS75	65	74LS139	65	74LS194A	75	74LS366	82	7906	98
74LS21	35	74LS76	65	74LS151	85	74LS197	95	74LS367	1.65	7908	98
74LS22	35	74LS78	65	74LS153	85	74LS240	2.20	74LS368	65	7912	98
74LS26	44	74LS83A	89	74LS155	65	74LS241	2.20	74LS373	1.40	7915	98
74LS27	35	74LS86	39	74LS156	1.02	74LS242	2.20	74LS374	1.55	7918	98
74LS30	35	74LS89	98	74LS157	78	74LS243	2.20	74LS393	1.20	7924	98
74LS32	90	74LS90	1.22	74LS158	65	74LS244	2.20	74LS670	1.78	79L05	72
'4000 B' SERIES CMOS											
4001B	21	4032B	1.04	4072B	22	4511B	76	4539B	77	79L12	72
4002B	21	4035B	80	4073B	22	4512B	72	4541B	96	79L15	72
4008B	72	4038B	99	4075B	22	4513B	1.68	4543B	1.12	79L24	72
4011B	31	4040B	72	4076B	22	4514B	1.88	4551B	96	I.C. SOCKETS	
4012B	21	4042B	58	4077B	22	4515B	1.88	4553B	2.40	DIL TO DIL	
4013B	30	4043B	71	4078B	22	4516B	76	4556B	1.48	8 way 22	
4014B	74	4044B	71	4081B	22	4517B	1.68	4558B	1.70	14 way 29	
4015B	76	4046B	96	4093B	49	4522B	88	4580B	3.60	16 way 32	
4016B	42	4047B	70	4094B	1.56	4526B	88	4581B	1.84	18 way 32	
4017B	66	4049UB	32	4099B	1.20	4527B	1.20	4582B	80	20 way 32	
4018B	72	4050B	32	4160B	72	4528B	88	4583B	1.00	22 way 32	
4020B	76	4051B	72	4161B	72	4529B	1.04	4584B	40	24 way 34	
4021B	70	4052B	72	4162B	72	4530B	62	4585B	88	28 way 37	
4022B	70	4053B	72	4163B	72	4531B	72	4597B	1.84	DIL TO QUIL	
4023B	21	4060B	96	4502B	72	4532B	1.00	4598B	2.40	14 way 32	
4024B	50	4066B	43	4505B	1.88	4536B	1.64	4599B	2.00	16 way 36	
4025B	21	4068B	22	4510B	76	4538B	2.04			QUIL TO QUIL	
LINE OUTPUT TRANS.											
R.B.M. T20A	13.95	RECTIFIER TRAYS									
R.B.M. A774 Mono	11.74	THORN 950 Mk II	4.25	REPLACEMENT ELECTROLYTICS							
R.B.M. T179	15.00	THORN 1400 3 Stick	5.20	PYE 169 (200/200/100/32)	3.74	CAPACITORS AXIAL					
R.B.M. Z718 22"	19.50	THORN 1500 3 Stick	5.20	DECCA 30 (400/400/200V)	3.02	Volts	Mfd	Price	63V	1	12
PHILIPS 320	8.70	THORN 1500 5 Stick	5.29	DECCA 30 (400/400/350V)	3.74	6V3	33	9	2.2	12	
PHILIPS 210/300 Mono	10.00	THORN 1600	4.95	DECCA 80 (400/350V)	4.37	10V	22	10	4.7	12	
PHILIPS G8	8.75	THORN 3000/3500	7.98	DECCA 100 (800/250V)	4.37		47	10	10	11	
PHILIPS G9	7.75	THORN 8000	5.28	DECCA 1700 (200/200/400/350V)	5.32		100	10	15	12	
PHILIPS G11	13.50	THORN 8500/8800	7.15	PHILIPS G8 (600/300V)	2.53		220	15	22	13	
PYE 697 (Printed)	14.50	THORN 9000	8.70	PHILIPS G9 (600/300V)	2.44		470	20	47	19	
PYE 713/731	10.00	DECCA 1730/1830	4.48	PHILIPS G11 (470/250V)	3.19		33	11	100	23	
PYE 725 90°	10.50	DECCA 30	6.76	PYE 691/7 (200/300/350V)	2.97		68	11	220	37	
PYE 169	10.00	DECCA 80	6.60	PYE 731 (600/300V)	2.55		220	16	470	49	
DECCA 80/100	8.58	DECCA 100	7.50	RBM A823 (2500/2500/30V)	1.83		1000	27	1000	85	
DECCA 1700	9.00	UNIVERSAL ITT or REMO	6.00	RBM A823 (600/300V)	3.12		3300	53	2200	1.10	
DECCA 1730	8.58	GECC 2100	7.40	RBM Z146 (300/300/350V)	3.91		22	13	100V	12	
DECCA 2230	8.58	GECC 2200 (20AX)	6.50	RR1 T20A (220/400V)	3.28		47	15	47	20	
GECC 2110	16.75	GECC 2040/2028	6.60	ITT CVC5/9 (200/200/75/25)	2.20		100	15	100	36	
GECC 2040	9.50	GECC 2110 Pre Jan '77	7.00	ITT CVC 20 (220/400V)	2.20		220	29	220	70	
ITT CVC 1-9	10.85	GECC 2110 Post Jan '77	7.00	GECC 2110 (600/250V)	2.14		470	30	450	1	
ITT CVC 20	8.60	PHILIPS G8 Short Focus Lead	6.75	GECC 2040 (1000/2000/35V)	1.31		1000	55	4.7	30	
THORN 3000 EHT	9.95	PHILIPS G8 Long Focus 550	6.75	THORN 3500 (400/40V)	4.51		2200	51	10	30	
THORN 3000 SCAN	7.95	PHILIPS G9	6.37	THORN 950 (100/300/100/16/275V)	2.02		4700	98	22	65	
THORN 8000	11.33	Pye/Philips K3 Tripler	10.65	THORN 1400 (150/100/100/150/320V)	3.07		10	10	33	75	
THORN 8500	11.33	PYE 691/3	6.58	THORN 1500 (150/150/100/300V)	2.42		22	10	500	10	
THORN 3000/3500	10.00	PYE 713/4 Lead	8.79	THORN 1500 (12/300V)	35		400	48	600	0.1	
Mains	10.00	PYE 713/725	7.60	THORN 3500 (175/100/100/400/350V)	3.06						
THORN 1591	8.68	R.B.M. A823 (plug in) AV	7.60	THORN 3500 (1000/63V)	95						
THORN 1691	9.68	KORTING (similar to Siemens TVK1)	7.32	THORN 3500 (1000/70V)	95						
THORN TX10	15.00	ITT KB CVC20/25/30 (Mullard)	6.65	THORN 8000/8500 (2500/2500/63V)	3.72						
THORN 1615	9.75	RR1 T20	6.80	THORN 8000/8500 (700/250V)	2.55						
PHILIPS KT3	9.70	ITT CVC45	8.65	THORN 9000 (400/400V)	3.61						
RANK BUSHRANGER	£10.00			GECC (200/200/150/50)	2.91						
PYE 741	8.20			PHILIPS 69 2200.63V	1.38						
B+O (2000 3000)	12.70			THORN 4700 P/C 25V	1.32						
B+O (3000 EHT)	18.90			THORN 1591/1691 4700/25V	1.32						
				G11 Capacitor 7N5 1500V	1.40						
FUSES											
1 1/4" QUICK BLOW		Per Pack		NEW MONO TUBES				REBUILT COLOUR TUBES			
100ma		Type	of 10	MULL. A31/510 110° 12"	18.50	ALL AVAILABLE EX-STOCK ON GLASS FOR GLASS EXCHANGE FROM TRADE COUNTER. SOME TYPES AVAILABLE WITHOUT EXCHANGE FOR SMALL GLASS				SLIOPER POTENT	
250ma-500ma-750ma-1A			73	MULL. A34/510 110° 14"	20.00	17" A44/271X	32.00	Lin or Leg		MIDGET CONTROLS	
1.5A-2A-2.5A-3A-5A			60	A50/120WR 110° 20"	18.50	18" A47/342X (Low Focus)	32.00	470R-1K-2K2-4K7		Insulated Spindle Length 44mm	
			60	A61/120WR 110° 24"	20.50	18" A47/343X (Std Focus)	32.00	10K-47K-470K		Log or Lin Without Switch	
				VEGA 12" 90° (Jap Types)	15.00	20" A51/110X	30.00			5K-10K-25K-50K-100K-250K-500K-1M	
						22" A56/120X	30.00			With D.P.S.T. Switch	
						25" A63/200X	30.00			Log: 5K-10K-25K-50K-100K	
						26" A66/120X	34.00			250K, 500K, 1M, 2M	
						26" A67/120X	34.00			Dual gang Controls	
						22" A56/500X	60.00			16mm Rotary Controls 10K, 22K, 100K, 1M, 10K	
						A51 570X	72.00			THICK FILM RESISTOR NETWORK	
						A56 510	67.00			THORN 3500 (5 pin connection)	
						A66 510	92.00			PYE 731 (6 pin connection)	
										THORN 9000 (Circuit Ref. R704/7)	
										EVER READY BATTERIES	
										R20S 38 PP6 1.09	
										R6B 14 PP7 1.09	
										R14S 33 PP9 1.10	
										R03B 16 1289 6.0	
										PP3B 52	
										PP3S 72	
										CARBON RESISTORS*	
										1/4W 3R3-8M2 20	
										1/2W 3R3-8M2 20	
										1W 10R-10M 36	
										2W 10R-10M 62	
										Sold in packs of 10 per type i.e. per value	
										RECHARGEABLES	
										EVER READY	
										RX6 (HP7) 1.29	
										RX14 (HP11) 2.22	
										RX20 (HP2) 2.45	
										RX22 (PP3) 4.55	
										Universal Charger 7.50	
STOP PRESS											
Special Prices											
5 1/4" Floppy Disc											
Boxes of 10	40 Track	80 Track									
SS/SD	£10.50	—									
SS/DD	£11.00	£15.00									
DS/DD	£13.00	£16.90									
SERVICE MANUALS (Zero VAT)											
THORN 1590/1	4.00	VIDEO 3V00	24.00	PHILIPS G9	3.90						
1615	2.95	3V22	24.00	G11	3.90						
1640/1	5.00	3V29/30	33.00	K30	3.90						
9000	8.20	DECCA 30	4.75	KT3	3.90						
9800	6.80	80	5.35								
Tx9	16.50	70/90	3.90								
Tx10	19.20	100	4.80								
WIREWOUND RESISTORS*											
4W 1R-10K	24p										
7W 1R-22K	26p										
11W 1R-22K	29p										
17W 1R22K	32p										
RECHARGEABLES											

P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US
 104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.
 Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER

ADD 75p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degaus. coils please allow £1.30 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. invoice on request. Give us a ring - we'll give you our service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

SEMICONDUCTORS				INTEGRATED CIRCUITS				DIODES							
AC107	35	BC558	9	OT121	1.91	AN2140	3.91	SN76131N	2.00	TCA910	2.20	UPC1200V	1.18	AA119	9
AC126	30	BCY72	13	R2008B	1.90	AN240	3.84	SN76226DN	2.00	TCA940	1.95	UPC1211V	1.70	BA102	17
AC127	32	BD115	45	R2010B	1.92	AN318	3.98	R2010B	1.18	TDA440	2.20	UPC1212V	2.34	BA115	13
AC128	32	BD116A	65	R2265	1.50	AN262	2.45	R2265	1.70	TDA1002	1.95	UPC1215V	1.66	BA145	17
AC128K	40	BD124P	79	R2322	62	AN301	5.15	SN76033N	2.49	TDA1003A	5.50	UPC1216V	1.62	BA148	17
AC141K	39	BD131	50	R2323	67	AN7150	3.97	SN76544N	2.35	TDA1006A	2.50	UPC1217G	1.13	BA154	6
AC142K	38	BD132	49	R2461	1.50	AN6340	7.85	SN76650N	1.05	TDA1005	3.60	UPC1218H	1.80	BA155	14
AC176	35	BD133	60	R2450	2.80	AN6341N	5.10	SN76660N	8.00	TDA1010	1.54	UPC1223C	2.20	BA156	15
AC176K	35	BD135	38	RF457	2.20	AN6344	7.85	SN76666N	80	TDA1035	4.70	UPC1225H	2.00	BA317	26
AC186	41	BD136	38	RF458	43	BA521	2.80	SN76530A	1.47	TDA1037	2.95	UPC1226H	1.50	BA318	4
AC187	38	BD137	38	RF459	43	BA536	3.00	STK015	6.25	TDA1044	4.37	UPC1227V	1.20	BA319	8
AC187K	38	BD138	35	RF460 = BF462	86	CA555	46	STK032	=	TDA1060A	4.44	UPC1228H	5.4	BB105B	30
AC188	35	BD139	35	RF469	46	CA556	84	STK078	13.25	TDA1062	1.56	UPC1230V	3.95	BB105G	30
AC188K	39	BD140	44	RF470	66	CA558	46	STK043	11.05	TDA1083	1.68	UPC1238V	1.16	BY126	12
AD143	82	BD144	1.70	RF471	10	CA741	25	STK433	5.65	TDA1170S	3.00	UPC1245V	1.35	BY127	11
AD161	54	BD150	60	RF472	54	CA748	45	STK435	9.06	TDA1190	3.50	UPC1250V	4.15	BY133	15
AD162	54	BD159	65	RF473	54	CA748	45	STK436	5.50	TDA1180	2.91	UPC1353C	1.92	BY164	45
AD161/62 MP	1.15	BD166	70	RF474	54	CA748	45	STK437	7.85	TDA1200	2.95	UPC1365C	6.38	BY176	85
AF106	49	BD179	70	RF475	27	CA748	45	STK439	6.62	TDA1220A	2.12	UPC1356C2	2.08	BY179	63
AF114	49	BD182	1.20	RF476	27	CA748	45	STK459	8.20	TDA1270	3.95	UPC1367	2.08	BY182	87
AF118	1.20	BD183	75	RF477	85	CA748	45	STK441	8.10	TDA1327	1.70	UPC1378H	2.70	BY184	55
AF121	75	BD201	85	RF478	1.74	CA748	45	STK461 = 465	9.10	TDA1352B	1.60	UPC1358H	1.88	BY199	28
AF124	48	BD202	91	RF479	39	CA748	45	STK463	14.30	TDA1412	1.20	UPC1360C	2.20	BY206	14
AF125	46	BD203	80	RF480	39	CA748	45	STK463	14.30	TDA1415	1.40	UPC1363C	2.16	BY210/600	28
AF126	46	BD204	99	RF481	39	CA748	45	STK463	14.30	TDA1470	4.67	UPC1366C	1.84	BY210/800	33
AF127	38	BD222	46	RF482	39	CA748	45	STK463	14.30	TDA1770	5.60	UPC1368H2	2.15	BY222	30
AF139	58	BD223	56	RF483	40	CA748	45	STK463	14.30	TDA2002	2.80	UPC1370C2	2.58	BY227	28
AF178	1.54	BD225	47	RF484	42	CA748	45	STK463	14.30	TDA2003	1.20	UPC1382C	1.08	BY298	22
AF239	60	BD232	68	RF485	30	CA748	45	STK463	14.30	TDA2004	2.52	UPC1384	3.78	BY299	22
AL102	4.90	BD233	60	RF486	30	CA748	45	STK463	14.30	TDA2006	1.78	UPC1447H	5.8	BYX10	20
AU106	2.50	BD234	63	RF487	30	CA748	45	STK463	14.30	TDA2010	2.00	UPC41C	2.80	BYX36/10	30
AU113	5.20	BD235	60	RF488	46	CA748	45	STK463	14.30	TDA2140	5.95	UPC5743	3.8	BYX55/600	30
BC107	20	BD236	65	RF489	30	CA748	45	STK463	14.30	TDA2150	2.22	UPC577H	2.46	BYX71/600	90
BC108	20	BD237	57	RF490	24	CA748	45	STK463	14.30	TDA2020	4.66	UPC585C	1.28	YD224	2.00
BC109	20	BD238	65	RF491	95	CA748	45	STK463	14.30	TDA2030	2.80	TDA 1011	4.00	OA47	9
BC114	12	BD243	85	RF492	34	CA748	45	STK463	14.30	TDA2040	2.40	11A 4112	75	OA90	10
BC115	17	BD244	85	RF493	45	CA748	45	STK463	14.30	TDA2052	3.40	TAA570	3.98	OA91	10
BC116A	16	BD410	79	RF494	83	CA748	45	STK463	14.30	TDA2524	2.25			OA95	6
BC117	30	BD434	74	RF495	1.46	CA748	45	STK463	14.30	TDA2525	4.00	while stocks last		OA202	11
BC118	24	BD437	86	RF496	94	CA748	45	STK463	14.30	TDA2530	2.70			IN914	4
BC119	36	BD438	94	RF497	94	CA748	45	STK463	14.30	TDA2532	2.56			IN4001	4
BC139	28	BD507	52	RF498	98	CA748	45	STK463	14.30	TDA2540	3.84			IN4002	4
BC140	32	BD508	55	RF499	56	CA748	45	STK463	14.30	TDA2541	3.84			IN4003	4
BC141	26	BD509	56	RF500	45	CA748	45	STK463	14.30	TDA2560	3.50			IN4004	5
BC142	30	BD510	60	RF501	57	CA748	45	STK463	14.30	TDA2571	2.56			IN4005	10
BC143	31	BD278A	61	RF502	1.80	CA748	45	STK463	14.30	TDA2576	3.75			IN4006	5
BC147	13	BD517	80	RF503	89	CA748	45	STK463	14.30	TDA2577A	3.75			IN4007	10
BC148	9	BD520	75	RF504	1.65	CA748	45	STK463	14.30	TDA2578	4.50			IN4148	5
BC149	12	BD535	82	RF505	1.20	CA748	45	STK463	14.30	TDA2581	3.30			IN4448	10
BC157	16	BD536	91	RF506	1.20	CA748	45	STK463	14.30	TDA2582	2.60			IN5401	12
BC158	16	BD696A	1.49	RF507	1.60	CA748	45	STK463	14.30	TDA2590	3.25			IN5402	14
BC159	15	BD697	1.24	RF508	1.69	CA748	45	STK463	14.30	TDA2591	2.95			IN5403	12
BC160	52	BD698	1.29	RF509	1.69	CA748	45	STK463	14.30	TDA2592	2.95			IN5404	12
BC161	28	BD699	1.50	RF510	1.21	CA748	45	STK463	14.30	TDA2593	2.90			IN5405	13
BC170B	15	BD707	95	RF511	3.66	CA748	45	STK463	14.30	TDA2600	5.90			IN5406	16
BC171	15	BDX32	2.10	RF512	3.66	CA748	45	STK463	14.30	TDA2610	3.20			IN5407	16
BC172	15	BF115	3.8	RF513	1.20	CA748	45	STK463	14.30	TDA2611A	1.95			IN5408	20
BC173	12	BF117	3.6	RF514	2.00	CA748	45	STK463	14.30	TDA2620	2.92			ITT2002 = BAX16	
BC174	10	BF125	26	RF515	1.58	CA748	45	STK463	14.30	TDA2625	7.31			Y969 - Disc.	
BC177	27	BF127	47	RF516	1.80	CA748	45	STK463	14.30	TDA2653	5.90			REP BZX85 30V	
BC178	26	BF154	23	RF517	1.80	CA748	45	STK463	14.30	TDA2656	3.40				
BC182L	9	BF158	18	RF518	1.80	CA748	45	STK463	14.30	TDA2690	1.35				
BC183L	12	BF160	27	RF519	1.50	CA748	45	STK463	14.30	TDA3190	2.00				
BC184L	14	BF167	24	RF520	1.42	CA748	45	STK463	14.30	TDA3500	6.00				
BC186	35	BF173	22	RF521	1.80	CA748	45	STK463	14.30	TDA3560	6.90				
BC187	25	BF177	52	RF522	1.60	CA748	45	STK463	14.30	TDA3561	6.50				
BC204	10	BF178	46	RF523	1.65	CA748	45	STK463	14.30	TDA361A	4.50				
BC208	13	BF179	28	RF524	2.20	CA748	45	STK463	14.30	TDA4420	4.22				
BC209	10	BF180	39	RF525	2.20	CA748	45	STK463	14.30	TDA4600	2.95				
BC212	9	BF181	39	RF526	2.10	CA748	45	STK463	14.30	TDA9503	2.50				
BC212L	13	BF182	36	RF527	1.75	CA748	45	STK463	14.30	TEA1002	1.30				
BC213	13	BF183	29	RF528	1.70	CA748	45	STK463	14.30	TEA1009	3.57				
BC214	10	BF184	36	RF529	3.07	CA748	45	STK463	14.30	TEA1009	1.38				
BC237	14	BF185	36	RF530	2.30	CA748	45	STK463	14.30	TEA1009	1.38				
BC238	14	BF194/394	16	RF531	2.46	CA748	45	STK463	14.30	TEA1009	1.38				
BC251A	18	BF195	16	RF532	3.20	CA748	45	STK463	14.30	TEA1009	1.38				
BC252	12	BF196	16	RF533	1.40	CA748	45	STK463	14.30	TEA1009	1.38				
BC261	18	BF197	16	RF534	2.94	CA748	45	STK463	14.30	TEA1009	1.38				
BC262	18	BF198	16	RF535	1.45	CA748	45	STK463	14.30	TEA1009	1.38				
BC300	50	BF199	21	RF536	3.84	CA748	45	STK463	14.30	TEA1009	1.38				
BC301	53	BF200	35	RF537	1.50	CA748	45	STK463	14.30						

TRADE ANNOUNCEMENT

**LARGE QUANTITIES
AVAILABLE
OF THE FOLLOWING:—**

**FERGUSON
3V16/3V22
VHS VIDEOS**

**THORN
8800/9000/9600
COLOUR TV's**

**MAINLY REMOTE CONTROL
HAND UNITS NOW AVAILABLE**

**MINIMUM PURCHASE 5 UNITS
LOWEST PRICES IN U.K.**



**TELEPHONE
BOB MUNSON
01-985 6111**

★★★★ **GOOD NEWS FOR YOU!** ★★★★★

HUSSAIN CENTRAL T.V. LTD. NOW ALSO COLLECTING FROM RUMBELAWS TO OFFER YOU THE WIDEST CHOICES IN THE U.K. AT THE LOWEST PRICES

- *****
 * STAR BUY 22" T.V. WORKING..... from **£8.00** *
 * STAR BUY 22" T.V. UNTESTED..... from **£5.00** *
 * PHILIPS G8 550 22" FITTED WITH REGUNNED C.R.T. **£28.00** *
 ***** **PRICES TO REMEMBER** *****

LATEST T.V.'s NOW IN STOCK

G11 TELETEXT & REMOTE, ITT REMOTE CONTROL
 DECCA 80/88/100 SERIES, THORN REMOTE CONTROL
 THORN 9800/9600/9000/8800/8500/8000

SPECIAL OFFER ON WORKING T.V.'s

G8	550	22"	£20.00
G8	520	22"	£15.00
THORN	9000	20"	£35.00
THORN	8800	22"	£30.00
THORN	8500	19"	£25.00
GEC	FROM	—	£25.00

SPECIAL OFFER FOR UNTESTED T.V.'s

G8	550	26"	£5.00
G8	550	22"	£11.00
G8	520	22"	£9.00
THORN	8500	19"	£15.00
THORN	8800	—	£20.00
THORN	9000	—	£28.00
GEC	FROM	—	£20.00

ABOVE PRICES BASED ON QUANTITY

ABOVE PRICES BASED ON QUANTITY

VHS VIDEOS WORKING - 1000's IN STOCK

BRAND NEW 14" REMOTE CONTROL £100

BRAND NEW PYE 20", 22", 26"

WITH STEREO - TEXT - REMOTES

MANY MORE BARGAINS IN STOCK - PHONE AND HAVE YOUR ORDER READY FOR COLLECTION. LORRY LOADS DIRECT FROM SOURCES DELIVERED TO YOUR DOOR. ALL SETS HAVE FIRST CLASS CABINETS

★ **NEWS FLASH** ★

G11 TUBES TESTED £20.00

A56-120 REGUNNED TUBES £15.00

HOT LINE BIRMINGHAM

021-622 1023

021-622 1517

48/52 PERSHORE STREET,
 BIRMINGHAM B5 4RR

HOT LINE LONDON

01-807 4090

01-884 1314

CEDAR HOUSE, NOBEL ROAD,
 ELEY ESTATE,
 EDMONTON, LONDON

HOT LINE SOUTH WALES

0291-271000

UNIT 4,

BULWARK INDUSTRIAL ESTATE,
 CHEPSTOW, GWENT

★★★★

★★★★

TELEPART



Telegen-1

- PRICE £18.35 (Inc. VAT)
- * EXCEPTIONALLY LIGHT AND DURABLE
- * POCKET SIZE FOR OUTSIDE SERVICE
- * PP3 BATTERY POWER SOURCE
- * FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV
- * CROSSHATCH GRID * DOT MATRIX
- * WHITE RASTER
- * HORIZONTALS * VERTICLES
- * 3.5mm JACK SOCKET FOR OPTIONAL P.S.U.

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

- PRICE £34.45 (Inc. VAT)
- * EXCEPTIONALLY LIGHT & DURABLE
- * COMPACT 10 x 12 x 4.5 cms
- * RED RASTER * GREEN RASTER
- * BLUE RASTER
- * COLOUR BARS
- * 3.5 mm JACK SOCKET FOR P.S.U.
- * PROVIDES UHF SIGNAL APPROX. CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.
PRICE £4.55 (Inc. VAT)

ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)
All goods should be delivered within 4 working days.
32 TEMPLE STREET, WOLVERHAMPTON
WV2 4AN. TEL: (0902) 773122

FREE CAREER BOOKLET

Train for success, for a better job, better pay!

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your **FREE CAREER BOOKLET** today — at no cost or obligation at all.

GCE		Choose from over 40 'O' and 'A' level subjects.	<input type="checkbox"/>
COMPUTER PROGRAMMING	<input type="checkbox"/>	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	<input type="checkbox"/>	INTERIOR DESIGN	<input type="checkbox"/>
POLICE ENTRANCE	<input type="checkbox"/>	HOTEL MANAGEMENT	<input type="checkbox"/>
ELECTRONICS	<input type="checkbox"/>	COMMERCIAL ART	<input type="checkbox"/>

Please send **FREE DETAILS** for the courses ticked above.


Name _____

Address _____

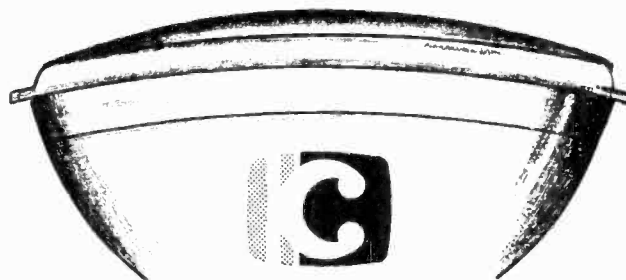_____ P. Code _____



Dept. EGS75, 312/314 High St., Sutton, Surrey SM1 1PR. Tel: 01-643 9568/9 or 041-221 2926 (all hours).



CHROMOVAC

QUALITY REBUILDS

SPECIAL OFFERS ON INLINE

Get on the hot-line today!

SUPERIOR QUALITY TUBES **051 428 8777**
DELTA RE-BUILDS
most types of Inline Re-builds or new ex-stock
★ 2 YEAR WARRANTY
★ 4 YEAR OPTIONAL

Delta Rebuilds

Up to 19"	£28
Up to 22"	£30
Up to 26"	£34
110° up to 22"	£34
110° up to 26"	£38
Low focus	+£2
A47 342 New	£28
17FHP New	£30
470EHB New	£30
Delta only. Less 5% +	

Inline Rebuilds

Up to 22"	£40
Up to 26"	£45
A56 - 540x	£56
A66 - 540x	£58
Bonded Coil	+£5

ALL SIZES OF NEW MONO TUBES AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

Please enquire types not listed

370 HFB-A37-590	£45	560 DMB	£62
370 HUB	£45	AXT 56-001	£62
AXT 37-001	£45	660 AB	£65
420 CSB	£45	A67-701	£65
420 EDB-A42-590	£45	670 CZB	£65
420 EZB	£45	A66-540	£65
420 ERB	£45	420FSB	£55
470 KUB	£50		
510 UFB/A51-590	£55		
510 VSB	£60		
AXT 51-001	£60		
560 DYB-560 DTB	£62		
560 EGB	£62		
560 CGB	£62		

CARRIAGE
£5 Singles, 2-3 £10, 4 £12
10 £15, 10+ Carriage paid
EXCLUSIVE OF VAT
TERMS
Cash with order

QUANTITY DISCOUNT AVAILABLE
Ask for details

★ OUR TECHNICAL DEPT. WILL ADVISE YOU ON PROBLEMS YOU MAY ENCOUNTER ON FITTING INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order. Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMOVAC

CHROMOVAC LTD. UNIT 7, BEAR BRAND COMPLEX, ALLERTON ROAD, WOOLTON, LIVERPOOL 25
Ask for Mr Butterworth or Betty Ford ON: 051-428 8777


EAST CORNWALL COMPONENTS

85

CATALOGUE

NEW 1985 CATALOGUE will be available July/August - range of components greatly increased - over 125 pages fully illustrated. Price £1.00 per copy (free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelope. Order your copy now - will be despatched as soon as available.

INTEGRATED CIRCUITS (E) EACH AN240P 3.42 SN76530P 1.40 AN2140 1.85 SN76533N 1.60 AN7150 2.90 SN76550N 1.05 CA3065 3.78 SN76660N 0.75 CA4031P 2.88 SN76666N 0.80 CA4012 3.30 STK015 6.50 CA4400 2.98 TA7108P 3.20 CA4422 3.07 TA7120P 2.20 LC7130 5.36 TA7129AP 3.85 LC7137 5.13 TA7130P 1.85 LM3808 1.65 TA7172 1.80 LM1303N 2.52 TA7172P 1.50 HA1151P 3.12 TA7176 2.50 MC1307P 1.85 TA7202P 4.18 MC1310P 1.85 TA7204P 1.96 MC1312P 2.25 TA7205AP 1.50 MC1327P 1.25 TA7208P 3.20 MC1330P 0.83 TA7210P 6.50 MC1349P 1.85 TA7222P 2.12 MC1350P 1.20 TA7223P 3.68 MC1351P 2.50 TA7227P 5.60 MC1352P 1.50 TA7310P 1.80 MC1357P 2.88 TA7611AP 2.88 MC1496L 1.15 TA7A623 2.46 ML231B 2.10 TA7A550 0.90 ML232B 2.10 TA7A570 1.50 ML237B 2.30 TA7A611A 3.50 MR475 1.25 TA7A605 3.90 MR479 5.20 TA7A618 1.70 MR477 10.00 TA7A70 3.80 NE555 0.50 TA7A80 2.38 C-Mos 555 0.88 TA7D100 2.80 NE556 0.80 TBA120 AS. 1.30 SAA1024 5.35 S.S.A.SB 1.30 SAA1025 8.40 Q.I.T.U.Q 1.32 SA5560A 2.50 TBA120B 1.30 SA5560S 1.85 TBA231 1.45 SA5570S 1.85 TBA281 2.65 SA5580 2.85 TBA395 1.20 SA5590 2.82 TBA480Q 1.50 SC9303P 1.10 TBA400 2.30 SL432A 4.00 TBA510 2.60 SL901B 5.20 TBA510Q 2.60 SL917B 7.25 TBA520Q 1.60 SL13270 1.10 TBA530Q 1.30 SN76023ND 2.90 TBA540Q 1.40 SN76033N 2.45 TBA560C 1.70 SN76110N 1.12 TBA60CQ 1.60 SN76155N 2.00 TBA570 1.50 SN76131N 1.65 TBA673 2.40 SN76226ND 1.80 TBA700 2.85 SN76227N 1.10 TBA750 2.80		CERAMIC CAPACITOR PACK 50V Ceramic Capacitors - 5 each value 25 valves - each value individually marked and packed - 125 total. £3.50 per pack. Male way way way d CONNECTORS 2 15 25 Angle 1.50 2.00 2.40 Female 2.40 2.40 2.40 Solder 4.00 3.00 3.00 Angle 1.00 1.45 1.85 1.50 2.00 2.40 Covers 80 80 PLUGS & SOCKETS Metal Co-ax Plug 0.18 Plastic Co-ax Plug 0.14 Single Line Socket 0.50 Plastic Phono 0.15 F.I.M. Plugs 0.25 PL25 Plugs 0.30 Reducer 0.15 Low loss splitter 1 in, 2 out 1.00 SOLDERING SECTION Soldering Station complete with 30W or 40W Iron (state which) 49.95 XS25 Watt Iron complete with steel and plug attached 7.20 CS 18W, as above 2.95 Antex 15W Iron 7.00 Antex 18W Iron 5.00 Antex 25W Iron 5.20 Antex elements 2.00 Antex bits 0.95 Antex stands 1.90 Solder sucker 4.50 Nozzles 0.65 TERMINAL BLOCKS 2 amp 12 way 0.19 5 amp 12 way 0.20 10 amp 12 way 0.40 15 amp 12 way 0.46 32 amp 12 way 0.90		SONY TV & VIDEO SPARES Rewind Kits SLCS-5L7 A-670-634-8A 4.50 SL6 A-670-639-1A 3.50 Video Heads SLCS-5L7 A-676-203-8A 4.25 SLCS A-676-204-4A 6.60 Motor Kit X-354-931-41 13.45 Idler Assembly X-365-331-50 0.95 Cap.Film 0.18mf/1.5kv 1-129-952-11 1.35 Relay 1-515-323-00 5.10 Switch Power 1-516-390-11 2.30 Switch Push Button 1-552-503-11 3.25 Thyristor SG264A 8-726-420-00 4.00 Service Manual SG6533 8-765-330-00 13.45 20.00 Send S.A.E. for our latest Sony Spares list Over 140 spares now available		PERSONAL STEREO CASSETTE Current stock incl. Omega & Murphy. Sorry, at this price we send what we have in stock at time. Complete with carrying strap & Headphones. £9.95 ea (plus addt post-age 50p) MULTISECTION ELECTROLYTICS THORN 850 100+300+100+16/300V 1.80 1400 150+100+100+100+150/320V 2.70 1500 150+150+100/300V 2.50 3000 100/63V 1.56 3500 175/400V+100+100/350V 0.70 8000/8500 250+250/63V 2.10 8000 700/250V 2.10 1000/70V 0.58 9000 400/400V 2.25 4700/25V 0.70 DECCA 1030 400+400/350V 2.45 1700 200+200+400/350V 3.52 GEC 2047 2048 2083 2084 2104 200+200+150+50/300V 1.32 600/250V 2.50 ITT/KB 200+200+75+25/350V 2.15 220/100V 1.95 PHILIPS G8 600/300V 1.50 G11 470/250V 1.50 G20 220/63V 1.26 EKCO T148 125+200+100+32/275V 1.65 691 Series 200+300/350V 2.80 600/300V 2.80 300+300/300V 1.05 RANK AB23 2500+2500/30V 0.98 600/300V 1.78		VDRs, etc. E220Z2 02/ 0.28 E298CD VA/2580.25 E298ED VA/2580.22 VA/2600.22 VA/2620.22 VA/2650.22 E299DD/P116- P354 all 0.23 E299DH VP/230 0.72 VA1015 0.92 VA1033/34/38/39/40/53 all 0.20 VA1055/56/56S/67s all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/11/12 all 0.24 VA8650 1.20 SCREENED CURLY LEADS Black 3 core (2 metres extended) 75p each 600/10	
ZENER DIODES 400mW Plastic 3V-75V 8p each, 10/75p. 1.3W Plastic 3V-200V 10/£1.40 1.5W Flange 4.7-47V £1.26 each 2.0W Stud 7.5-75V 64p each 2.0W Stud 7.5-75V £1.35 each ZENER DIODE PACK 400mW - 5 each value - 11 values - individually marked and packed - 55 Zener Diodes. £3.00 per pack		REPLACEMENT TV MAINS DROPPERS GEC2010 8R + 15R + 17R + 70R + 63R + 188R 0.95 GEC 2018 10R + 15R + 17R + 70R + 188R 1.15 Philips G8 2.2R + 68R 0.60 Philips 70 6R + 124R + 84R 0.88 Philips 300 118R + 148R (with link) 1.05 RRI A640 250R + 14R + 156R 50W 1.05 RRI A618 30R + 70R + 6.2R 0.78 Thorn 1500 350R 20R + 148R + 1.5K + 317R 1.34 Thorn 3000/3500 6R + 1R + 100R Fused 0.93 Thorn 8000 56R + 1K + 47R + 12R 1.28 Thorn 8500 1K5 + 40R + 50R 0.90		REPLACEMENT TV MAINS DROPPERS 8R + 15R + 17R + 70R + 63R + 188R 0.95 10R + 15R + 17R + 70R + 188R 1.15 2.2R + 68R 0.60 6R + 124R + 84R 0.88 118R + 148R (with link) 1.05 250R + 14R + 156R 50W 1.05 30R + 70R + 6.2R 0.78 350R 20R + 148R + 1.5K + 317R 1.34 6R + 1R + 100R Fused 0.93 56R + 1K + 47R + 12R 1.28 1K5 + 40R + 50R 0.90		RESISTORS - CARBON FILM 5% 1/4W 1R0 to 10M (E12 Range) 2p each 15p/10 75p/100 1/2W 2R2 to 10M (E24 Range) 2p each 15p/10 75p/100 1W 10R to 2M2 (E12 Range) 7p each 65p/10 600p/100 2W 10R to 2M2 (E6 Range) 8p each 70p/10 600p/100 RESISTOR KITS - each value individually packed 1/4W pack 10 each value E12 - 10R to 1M 610 pieces 5.00 1/2W pack 10 each value E12 - 10R to 1M 305 pieces 3.00 1/2W pack 5 each value E12 - 2R2 to 2M2 730 pieces 6.00 1W pack 5 each value E12 - 2R2 to 2M2 385 pieces 15.00 2W pack 5 each value E6 10R to 2M2 317 pieces 18.00 RESISTORS - WIREWOUND Generally 5% 2.5W - 0.22 to 270R - Available in preferred values 0.20 4W - 1R0 to 10K - Available in preferred values 0.21 7W - 0.47R to 22K - Available in preferred values 0.25 11W - 1R0 to 22K - Available in preferred values 0.29 17W - 1R0 to 22K - Available in preferred values 0.37			
VALVES Type Price (£) Type Price (£) Type Price (£) Type Price (£) Type Price (£) Type Price (£) DY82 0.75 6F7 0.40 6X4 0.30 6X5 0.32 6X6 0.32 6X7 0.32 6X8 0.30 6X9 0.30 6X10 0.30 6X11 0.30 6X99 0.30 6X00 0.30 6X01 0.30 6X02 0.30 6X03 0.30 6X04 0.30 6X05 0.30 6X06 0.30 6X07 0.30 6X08 0.30 6X09 0.30 6X10 0.30 6X11 0.30 6X12 0.30 6X99 0.30 6X00 0.30 6X01 0.30 6X02 0.30 6X03 0.30 6X04 0.30 6X05 0.30 6X06 0.30 6X07 0.30 6X08 0.30 6X09 0.30 6X10 0.30 6X11 0.30 6X12 0.30 6X99 0.30 6X00 0.30 6X01 0.30 6X02 0.30 6X03 0.30 6X04 0.30 6X05 0.30 6X06 0.30 6X07 0.30 6X08 0.30 6X09 0.30 6X10 0.30 6X11 0.30 6X12 0.30 6X99 0.30 6X00 0.30 6X01 0.30 6X02 0.30 6X03 0.30 6X04 0.30 6X05 0.30 6X06 0.30 6X07 0.30 6X08 0.30 6X09 0.30 6X10 0.30 6X11 0.30 6X12 0.30 6X99 0.30 6X00 0.30 6X01 0.30 6X02 0.30 6X03 0.30 6X04 0.30 6X05 0.30 6X06 0.30 6X07 0.30 6X08 0.30 6X09 0.30 6X10 0.30 6X11 0.30 6X12 0.30 6X99 0.30 6X00 0.30 6X01 0.30 6X02 0.30 6X03 0.30 6X04 0.30 6X05 0.30 6X06 0.30 6X07 0.30 6X08 0.30 6X09 0.30 6X10 0.30 6X11 0.30 6X12 0.30 6X99 0.30 6X00 0.30 6X01 0.30 6X02 0.30 6X03 0.30 6X04 0.30									

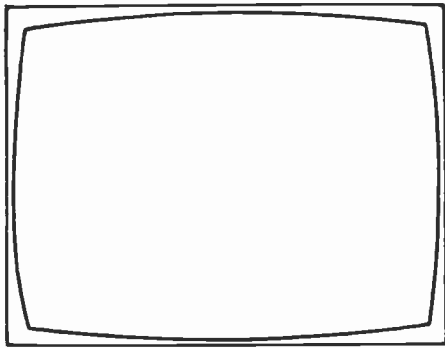

TELEVISION

Reflections at Show Time

This year's radio and TV trade shows were not noteworthy for displays of innovatory consumer electronics products. But then what should we expect? You can hardly have major advances on an annual basis. For the present it's stand still time, though business appears to have been good. What lies ahead? Well, there must obviously be satellite TV receiving equipment to sell once DBS services have started, but for the present the satellite TV equipment field is very much a specialised one, with small batch production.

One impression left behind is of the overwhelming dominance nowadays of the Japanese in the consumer electronics field. Japanese manufacturers certainly had a good year in 1984 - it's been company reporting time. As mentioned last month, Matsushita had a record year. Since then Hitachi have reported profits up 37 per cent, Mitsubishi Electric profits up 52.3 per cent, Sharp profits up 21.5 per cent and Toshiba profits up 38 per cent, all on substantially increased turnover. These profit/turnover increases are for the parent companies however and cover a wider field than just consumer electronic products. In this connection it's perhaps more relevant that JVC, which is predominantly a producer of consumer electronic products, managed a profit increase of only four per cent on turnover up by 18 per cent. Stiff price competition in the VCR field was one of the main factors blamed for this relatively poor result.

Japanese manufacturers have had a good run for their money. It looks as if they will do well again in 1985. This time the extraordinary thing is a sudden explosion in consumer demand in China, where over seven and a half million TV sets (a market size similar to that of Japan itself) are expected to be sold this year. The market is on Japan's doorstep, but it could well be an unpredictable one - demand has also been high recently for the whole range of domestic electrical products, from refrigerators and washing machines to pocket calculators. China is at present running a trade deficit and it's unlikely that the authorities will allow the situation to deteriorate to any marked extent. Furthermore the increased demand has been fuelled by an explosion of credit, which is unusual to say the least in a communist country. The central bank has expressed concern. There is of course a way around the trade deficit problem - another traditional Japanese ploy. This is to start up plants in the Chinese home market. Several joint venture projects have already been announced, by Philips as well as by Japanese manufacturers. It's a way of ensuring continued presence in a particular market, but one wonders how successful the ploy is financially. Japanese TV and VCR plants in the UK presumably exist primarily to guarantee a presence in the large EEC market, but they don't seem to have been wildly successful on a trading profit basis.

Internationally however fate has smiled upon the Japanese electrical manufacturers. When the European market reached saturation a couple of years ago there was a sudden increase in US demand. Now that the US market has turned flat the Chinese are clamouring for Japanese products. For how long can such a run of luck last? No sales chart has ever shown indefinite rising growth, and at some stage a halt to the rise is bound to occur. The developing world could certainly take a lot more production, but could it pay for this? One thing the Japanese expect is payment (you don't see Japanese banks lending billions upon billions to shaky S. American regimes - they leave that sort of thing to US and UK banks!). There is also the prospect of increased competition from Korea, which expects to export some two million VCRs over the next twelve months. We shall be seeing some of these in the UK, and they will sell at highly competitive prices. But Japanese electronics firms have managed to maintain their position despite competition from a number of lower cost producers in the far east. It will be interesting to see how the situation develops. After all Korea put the Japanese shipbuilding industry out of business many years ago now. But shipbuilding and steel manufacture are at the low-technology end of modern manufacturing. With consumer electronics the situation is rather different: the Japanese now dominate the technology, while the sheer size of their investment in modern plant would be hard to match. For the time being the Japanese lead in the field of TV and VCRs, but these are now mature markets in every sense. Product sales levels have reached saturation point in most markets, while technical development seems to have reached the end of its present phase. Money wouldn't have been poured into the FS tube if flat-screen displays were likely to be competitive, in terms of performance and price, in the foreseeable future, while digital TV doesn't for the present seem to offer much by way of improved performance. The field memory will give trick performance of the sort we're used to with VCRs, but will consumers want such features? One field that does offer scope for development and increased business is satellite TV of course.

In this connection the government's decision to relax the regulations on satellite TV reception in the UK is a curious one. Unnecessary restrictions should certainly be removed, but an odd situation could develop. Just suppose that a reasonable market develops for equipment to receive the medium-power satellites at present in operation providing signals intended primarily for cable networks. Mightn't this make it more difficult to get true DBS broadcasting, started, something that's proving difficult enough as it is? The decision looks to be a bit of a gamble, maybe just to get something, somehow, moving.

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

Please note that the telephone numbers above are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 473.

OBSCURE BRANDS

Many thanks to several readers who have provided information on Sovereign TV. We will be reporting next month. We have also received letters asking about Sonatel TV but have been unable to trace any source of spares, data etc. Can anyone provide information on this brand?

A DIFFICULT MONTH

Our apologies for any shortcomings this month. We've been involved in an office move (the address remains the same) which hasn't helped exactly. More seriously Dave Davies, who does our technical drawings, is in hospital. We are sure all readers will join in wishing him a speedy recovery.

FRONT COVER

This month's cover photograph shows a night scene at The London Teleport, British Telecom International's satellite-earth station in the Docklands. The Teleport transmits TV channels to cable networks in the UK and continental Europe. Our thanks to BTI for permission to reproduce the photograph.

Letters

IBA's TELETEXT EXPERIMENTS

Eugene Trundle's words of wisdom on "Dealing with Teletext Interference" (May issue) were useful and timely. As a result of the IBA tests he mentioned, the use of up to seven lines per field for teletext has now been authorized for all ITV regions. We had hoped to extend this to perhaps ten lines per field, but the tests in selected ITV regions showed that significant numbers of receivers that experience top-of-the-picture interference when a higher number of lines is employed are still in regular use. These are mostly older models and the number of lines will be limited to seven until most of these sets have either been modified or discarded.

On a point of history I'd like to make a correction. It was the IBA that made the first experimental transmissions of teletext-type signals from the Crystal Palace transmitter, during April 1973 – including "live" computer editing. The very first transmission was made during our "Engineering Announcements" on April 3rd, 1973. It was announced by Peter Ashforth as follows: "Just before we go this week, some of you may be interested to hear that for the past ten minutes or so during the bulletin we've been transmitting a special type of signal which carries information in data form: the information is transmitted during the blanking interval of the television and so, of course, can't be seen on a normal receiver." A filmed report of that early IBA teletext system, by Peter Fairley, then science correspondent of ITN, was broadcast during May 1973.

The IBA later willingly co-operated with the BBC, BREMA and the Home Office in establishing in 1974 the unified UK standard for teletext now used in some twenty countries across the world. Transmissions to this standard were first made by both the IBA and the BBC during the September 1974 International Broadcasting Convention. During our 1973 tests we identified the problems of data buzz and top-of-the-picture interference and the 1974 teletext specification took care to minimise the problem, which is inherently a question of receiver design.

The IBA "Engineering Announcements" referred to above still continue on the Channel 4/S4C network on Tuesdays at 9.15 a.m. and 12.15 p.m. IBA engineering information is also available at all times on Oracle page 590 (C4/S4C), with a list of Channel 4 transmitter conversions on page 390 (ITV).

Pat Hawker,

IBA Engineering Information Service.

SCOTCHTAPE CASSETTES

With reference to Mr. Henniker's letter in your May issue, the Lifetime Guarantee that 3M pledges with its market-leading Scotch videocassettes is supported by prompt, responsive action whenever a VCR owner or a retailer brings a faulty tape to our attention. It's a necessary part of the Guarantee that tapes presumed to be faulty are returned to us. To make returns painless – and free – for our customers all Scotch cassettes are sold with a Freepost label addressed to our Gorseinon, Swansea videotape factory. We check returned tapes to identify the problem – which in seven cases out of ten is due to machine damage or mishandling. We work closely with hardware manufacturers and retailers' service depart-

ments to ensure fault elimination and constant product improvement. What we cannot do is to replace tapes without seeing them.

Before writing to you Mr. Henniker was contacted by our Glasgow sales office, by our Bracknell head office, and was visited personally by our area representative – all in an attempt by 3M to give him satisfaction for his allegedly faulty L250 tape. On all occasions he has refused to return the tape to us.

Perhaps I can use your columns to appeal again to Mr. Henniker to send us the cassette? It will be replaced immediately with a new tape, and we would welcome the opportunity for our engineers to investigate the alleged fault.

D. J. Skinner, Field Service Manager,
Video Technical Centre, 3M United Kingdom PLC.

PYE HYBRID CTV MODIFICATION

I was recently asked by a friend to repair an ageing Pye hybrid colour set (691-697 chassis). The main fault was quickly dealt with. On viewing the picture however there appeared to be a lack of d.c. restoration, which I found annoying. The set had at some stage been fitted with a LEDCo CDA panel, so I looked up the circuit diagram given in the June 1979 issue of *Television*. This revealed a design problem with the link to the brightness control and since I wanted to do a good job for my friend (and I might occasionally have to watch the set myself) I decided to seek a solution. Although these sets are old many of them must still be in use so other readers may be interested in the solution I found. It's not perfect since the beam limiter action isn't as effective as it was.

Fig. 1(a) shows the initial arrangement with the luminance signal coupled by C39 to the first transistor (VT701) on the LEDCo panel. It will be seen that the base of VT701 is forward biased by R701/2. The voltage at the slider of the brightness control will be negative however (or possibly slightly positive – D39A will prevent the voltage at the top end of the control being much above zero). Hence the d.c. restorer diode D39 will always be heavily reversed biased and no d.c. restoration can take place. In the original valve circuit the luminance output pentode's control grid would have been biased negatively from the brightness control via R201 and D39 would have prevented any part of the video signal going below the voltage on C201, set by the brightness control. D.C. restoration of the signal was thus achieved.

The solution adopted was to remove R701 and R702 from the LEDCo panel and alter the brightness control

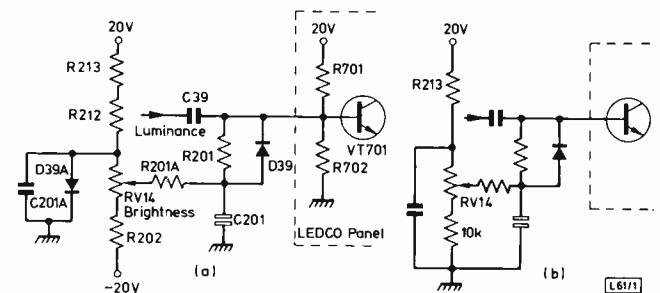


Fig. 1: Brightness control/d.c. restorer circuit used in the Pye 691-697 series chassis, (a) before modification, (b) after modification. Modification was required due to the use of a LEDCo solid-state CDA panel. Note that the collector of the beam limiter transistor VT35 is connected to the junction of resistors R212/R213, so the modification affects the limiting action.

circuit to provide a positive voltage on C201 so that the circuit could bias the base of VT701 directly, as it did the PL802's control grid in the original valve circuit. The modification is quite simple – see Fig. 1(b): D39A and R202 are removed, R212 is replaced with a link and an extra 10kΩ resistor is added between the bottom end of the brightness control and chassis.

The results were quite rewarding: dark pictures are really dark and bright pictures bright, with no black crushing. The only slight drawback is inadequate beam limiting: if the brightness or contrast is set too high there's severe loss of focus. This is no problem however with sensible settings of the controls. Time prevented further investigation into this problem – and I'm not sure that the tube wasn't partly responsible anyway. All in all a worthwhile exercise which should help keep these sets alive even longer.

*Anthony Marlow, M.A.,
Sale, Cheshire.*

BBC MICROCOMPUTER PROGRAM

Some alterations are required to the BBC microcomputer program in the June issue (page 446). First, the bit in brackets at the end of line 50 should be (10, “. ”). The difference is in the spacing – the string is too long with the additional spaces you had at each side of the stop. Secondly, in lines 70 and 80 6% should in each case read c%.

Adding an extra line at the beginning of the program as follows:

```
5 *TV0,1
```

stops the interlace jitter.

Changing the last line to:

```
180 IF GET=9
    MODE7:PRINTTAB(13,12)“GOODBYE”:
    END ELSE UNTIL 0
```

causes GOODBYE to be printed when exiting the program.

*Roger Goodman,
Wandsworth, London SW18.*

POINTS ON VCRs

In the May VCR Clinic Steve Beeching said that the Hitachi VT8700 was the first VCR he'd come across that would work without a cassette lamp. This gives the impression that the machine will work in the event of cassette lamp failure, which is not the case. As with all the VCRs in the Hitachi 8000 series, lamp failure is detected by the control microcomputer i.c.'s dew sense input (IC901, pin 33). Failure results in the stop condition with the stop light flashing. The relevant bit of circuit (for the VT8700) is shown in Fig. 2. Under normal operating conditions the lamp is alight and the cathode of zener diode ZD651 is held at a low voltage. If the cassette lamp fails there's no current flow via R653 and ZD651's cathode is at 15V. Being a 9V zener diode it conducts and, via D651, provides a high to IC901's dew sensor input. In Steve's case the lamp was o.k. but the feed resistor was open-circuit, so the safety circuit didn't operate. A weakness in the design perhaps, but it's the first case of this resistor going open-circuit I've heard of – and I've had only two faulty cassette lamps.

On the subject of liquids spilt into VCRs, a colleague recently had a Panasonic NV2000 which a pet had used as

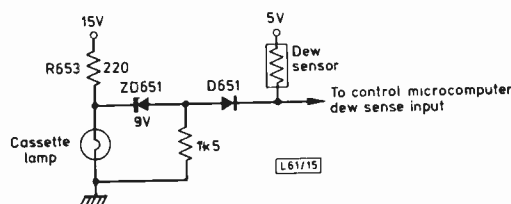


Fig. 2: Cassette lamp/dew sensor circuit used in the Hitachi VCR Model VT8700.

a toilet. It took three weeks to clean and locate the faults, was back with the customer for two weeks then had to come back for further repairs (it's still not fixed). The problem is that as fast as one fault is cured another appears, and they are all obscure faults that wouldn't happen under normal circumstances. I reckon we average one machine a month with spillage of some sort. With chargeable jobs, if the household insurance won't cover the repairs it can be uneconomical to try even without replacement panels – which some manufacturers won't provide anyway.

Finally, I must make a few comments concerning the letters about the present state of the TV trade and its future. I consider training in all industries to be the employer's responsibility, and that this is one of the country's biggest failings in the present economic climate. As to the future, while the service side is no longer expanding the increasing number of VCRs and microcomputers requiring attention are beginning to take up the slack caused by the increased reliability of TV sets. I agree that it's going to be difficult to get into the trade, but for those already in it the future should be reasonably secure, at least for another five to ten years – provided you keep up with the trends.

*Derek Snelling,
Brownhills, Staffs.*

TELETEXT BLANKING CIRCUIT

While chasing an intermittent fault in a Beovision 2600 I thought I'd try out the blanking circuit shown in Fig. 3(a) on page 372 of the May issue. I was suspicious about the connection shown to the field output transformer, feeling that the phasing was incorrect. Sure enough it is! If you connect up as shown the bottom half of the picture is blanked out with teletext flashing merrily in the upper half. The 0.1μF capacitor has to go to the same point on the transformer as the blanking circuit feed, i.e. the top of the winding shown in Fig. 3(a) not the bottom. Wired like this it works fine.

*Keith Cummins,
Southampton, Hants.*

PORTABLE CRT TESTER

With reference to Tony Thompson's comment about a portable CRT tester (May 1985) the converter circuit shown in Fig. 3 will produce a 240V a.c. output from a

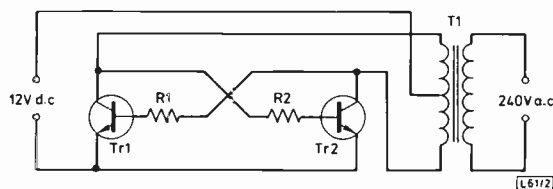


Fig. 3: Converter circuit for 12V d.c. to 240V a.c. Tr1, 2 type 2N3055; R1, 2 100Ω, 10W w.w.; transformer T1 is rated at 20VA and has 12-0-12V and 240V mains windings.

12V rechargeable dryfit lead-acid battery. It can be used with James Dilworth's CRT tester/booster which was described in the August 1981 issue of *Television*.

*N. E. Hawkins,
Milton Keynes, Bucks.*

THAT G11 MULTIFAILURE

With reference to Ivan C. Tucker's article on G11 problems, I'm sure that a lot of us have by now had first-hand experience of the red 470 μ F capacitor causing damage to the tube, the TDA2600 and the BU208A. Unfortunately the blue capacitors are not 100 per cent reliable either: I had to replace one two weeks ago because it destroyed BU208As.

So what happens if the same thing occurs again six months after replacing these parts? The customer complains to you! You return the tube with its unmistakable little star in the neck to the supplier, who won't replace it because he knows it was caused by the capacitor! The supplier of the capacitor *might* replace that but not the chip etc. Has anyone out there got a sensible answer before one of us gets really stung?

*J. Hopkins, The TV Workshop,
Wisbech, Cambs.*

SLIPPED SHADOWMASK

Here's an unusual "horror story" concerning a Bush set fitted with the Z718 chassis. On switching on one evening the picture showed severe colour errors, e.g. the snooker table was brilliant purple. A replacement decoder panel made no difference, so maybe it was a degaussing fault or a slipped shadowmask? The degaussing circuit turned out to be o.k., and putting the set on its side in the hope that the mask might return to its correct position brought no change.

We checked to see which guns were firing at which phosphors. Result, red was firing at green, green at blue and blue at red. So let's reconnect the video outputs appropriately. This gave true colours but shameful convergence. At this point we had a bit of luck, which we needed. Whilst examining the convergence strip at the top of the chassis we accidentally removed the convergence waveforms by disconnecting the plug from the line output board. With no waveforms to displace the beams we found we had an almost correctly converged picture. This was optimised by adjustment of the red and blue static convergence magnets, giving correct colour across four fifths of the screen with aberrations on the left-hand side. Viewing from ten feet gives a very reasonable picture which has remained stable for some three years.

*P. R. Atkins,
Southall, Middx.*

SPECTRUM TEST PATTERN PROGRAM

As a result of correspondence following my Spectrum test card program (May) I've discovered that not all editions of the Spectrum manual contain a colour bar program. Also when the colour bar program is included it has the bars at two brightness levels and they don't fill the bottom lines of the screen. They also have numbers printed on them to indicate the keys relating to the colours. This feature may be required to set up the Spectrum with a TV set or monitor, but for TV test purposes full-brightness bars filling the entire screen area are required.

Unfortunately there's no way in which the bars can

extend all the way to the border, but it's possible to use the bottom two lines by using the PRINT #1 command.

The original program can be modified as follows. Load the program, then enter the following lines:

```
472 IF i$="b" THEN BRIGHT 1: CLS: FOR n=0 to 21:
  FOR c=1 to 8: PRINT PAPER c(c);
  " "; NEXT c: NEXT n: PRINT #1; AT 0,0; FOR
  n=0 to 2: FOR c=1 TO 8: PRINT #1; BRIGHT 1;
  PAPER c(c); " "; NEXT c: NEXT n: LET i$=""
474 IF i$="c" THEN BRIGHT 0: CLS: RUN
572 IF i$="b" OR i$="c" THEN GO TO 472
```

In addition, change line 100 to:

```
100 POKE 23658,0: LET nn=0: BORDER 1: PAPER 0:
  INK 7: CLS
```

Adding the POKE in this line ensures that the shift is in lower case. Note that there are four spaces between the first two sets of quotes. After testing, resave the whole thing on your cassette or microdrive.

When the program is run the card now appears as usual. If you press "b" you get bars, if you press "c" you get the test pattern. Pressing ENTER stops the program. Pressing any other key turns the music on or off.

If you wish to enter the bars as a stand-alone program, enter just line 472 without the IF . . . THEN and leave out (c), i.e. use PAPER c instead of PAPER c(c). Then enter line 474 as follows:

```
474 IF INKEY$="" THEN GOTO 474
```

Do not leave this line out. The colours won't appear in the same order as the full program. Pressing any key ends the program.

All cassettes sent out from the address in the original article after May 10th contain the additions.

*John de Rivaz, B.Sc. (Eng.),
Truro, Cornwall.*

MORE ON PLUGTOPS

I've not seen all the correspondence mentioned in the letter headed "plugtop hints" in the March issue. It seems that readers have been concerned about burning of the neutral pin in 13A plugs. My working life mainly involved trouble-shooting for a large manufacturer of switchgear, control gear and accessories, and in my experience burning of the neutral pin is almost always due to the pin having receded into the plug moulding. In most plugs the neutral pin retention is different from that of the live pin. The neutral pin is usually held in position by the cap moulding pressing against its square head, there being a recess in the cap to accommodate the head of the pinching screw.

When a poorly designed plug or one made of inferior material is pushed into a good quality socket with good socket pressure, either the neutral pin cap retaining corners crumble (thermosetting material) or the neutral pin pushes into the cap (soft PVC or some other thermoplastic materials). The metal head in cheap plugs is often smaller than in good ones so that there's less area of plastic to withstand the force. If the cap is of soft PVC the heat from a well loaded fuse softens the whole cap and the pin recedes even more readily.

Once the pin has receded, contact in the socket is reduced and burning of the pin end occurs.

*L.E. Bevan,
Moseley, Birmingham.*

POST A PART ELECTRONICS
6 CHAPMAN COURT, CHARFLEETS ROAD,
CANVEY ISLAND, ESSEX SS8 0PQ.
Telephone 0268 690868
Telex 99305



TRADE COUNTER OPEN

ORDERS DESPATCHED SAME DAY
ADD 75p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 10Q 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70Q	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
TX9 Complete Tube Base Panel	2.75
TX10 Complete Tube Base Panel	3.75
TX90 Complete Tube Base Panel	4.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	45p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Insertor 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead. 12TCD-CT-10	65p
Degauss VDR E299D/H/230 3000/8000	1.80
Control Knob Thorn TX90	4 for 20p
On/Off Knob Thorn TX90	65p
Push Button Assy Thorn TX90	90p
Tube Neck Correction Assy. 20AX AT1081	5.00
EHT Cable	Metre 25p
BF259 with Heatsink	14p
TIP110 with Heatsink	40p
L129/130 131 Coil	10p
6MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
19006A Lum Delay Line	1.00
8K5/9K Lum. Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
Thorn 2000 Focus Pot	1.00
Thorn 9000 Focus Pot	3.75
Thorn 9600 Focus Pot	2.00
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn TX10 Focus Pot (New Type)	9.00

SERVICE AIDS

Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 2.25
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Amberclens Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS

3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES

20mm		1 1/4"	
50MA	10 for 70p	250MA	10 for 65p
750MA	10 for 50p	750MA	10 for 65p
315MA	10 for 50p	10A	10 for 50p
500MA	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn Mains TX 9000 (T701)	10.00
Thorn Mains TX 9600 (T512)	10.00
Thorn S.O.P.T 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9000	10.00
Thorn LOPT 9600	12.00
Thorn LOPT 1615	7.25
Thorn LOPT 1590/91	7.25
Thorn LOPT 1690/91	7.25
Thorn LOPT 8000	9.80
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.85
Thorn LOPT TX10	19.00
Thorn LOPT TX90	13.75
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT 69	8.80
Philips LOPT G11	13.75
GEE LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.80
Sanyo LOPT (CW21) 4:2751-44700	5.00
ITT LOPT CVC5-9	9.60
ITT LOPT CVC30	8.75
ITT LOPT CVC45	8.75
Baird 8750	10.25
Baird 8752	10.25
Thorn Line Drive TX. TX9 (T2)	3.00
Thorn Line Drive TX. 8K etc. (T402)	1.85
Thorn Line Drive TX. 9K (T705)	2.00
Thorn Switch Mode TX. 9K6 (T511)	3.75
Thorn Input Choke TX9 (L64)	4.00
Thorn Choke TX90 (L120)	2.95

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC174B	23	BCX33	22
AC131	40	BC177	24	BCX34	22
AC138	40	BC182LB	12	BD115	49
AC141K	39	BC183L	12	BD131	30
AC142K	38	BC184L	13	BD132	46
AC153	39	BC187	24	BD133	59
AC176	33	BC204	15	BD139	36
AC176K	33	BC208	9	BD140	38
AC128K	93	BC212L	9	BD144	1.70
AC188	38	BC213L	12	BD150	50
AD142	118	BC237	12	BD163	98
AD143	1.08	BC238B	8	BD201	74
AD149	98	BC238L	8	BD203	78
AD161	32	BC250A	15	BD204	9F
AD162	32	BC251	8	BD222	48
AD263	1.05	BC252A	20	BD225	52
AF127	45	BC294	37	BD232	50
AF139	38	BC301	32	BD233	60
AF239	41	BC303	31	BD234	60
BC107	15	BC307	10	BD237	55
BC108	15	BC308	8	BD238	65
BC109	15	BC309	14	BD241	59
BC115	16	BC327	18	BD244	85
BC117	21	BC328	17	BD278A	11
BC125	26	BC337	17	BD386	68
BC126	23	BC338	17	BD433	71
BC139	27	BC347	8	BD437	83
BC141	34	BC394	8	BD592	1.20
BC142	30	BC454	8	BD589	1.20
BC143	31	BC455	8	BD677G	1.35
BC147	12	BC456	10	BD679	1.42
BC148	12	BC460	40	BD701	1.04
BC149	12	BC463	22	BD702	1.12
BC153	16	BC546	8	BD707	95
BC1540R	16	BC547	12	BD708	95
BC154YL	16	BC548	12	BD833	1.30
BC157	12	BC549	8	BDX10	93
BC158	12	BC557	10	BDY20	1.09
BC159	15	BC558	10	BDY82	99
BC171	9	BC559	8	BF137	20
BC172	9	BC595	8	BF153	20

INTEGRATED CIRCUITS

BRC1330	1.40	SN76131ND	1.80	TBA530	1.26
BRC3064	1.00	SN76023N	1.80	TBA540	2.10
BRC/M/200	1.00	SN76033N	2.00	TBA550Q	1.82
BRC/M/300	1.00	SN76115	2.00	TBA560C	2.10
CA3060	1.58	SN76131N	1.58	TBA641	2.05
LM1303P	1.48	SN76278N	1.25	TBA651	2.50
ML231B	2.20	SN76227N	1.00	TBA720A	2.49
ML237B	2.80	SN76330P	1.20	TBA750	2.20
ML238B	2.86	SN76622N	1.00	TBA800	1.62
MC1327AP	1.25	SN76660N	80p	TBA810AS	1.00
MC1358P	1.30	SN76666N	75p	TBA820S	2.08
MC1455P	18p	SN76744	1.92	TBA950	1.95
MC14516BCP	60p	SN7513A	2.50	TBA1440	1.92
SAA1025	7.20	TA7117P	1.00	TCA270SA	1.05
SAA1124	4.50	TA7109AP	2.80	TCA270C	1.40
SAA5010	6.00	TAA611	1.40	TCA270CQ	1.05
SL432A	1.80	TBA120B	1.20	TDA1004A	4.00
SL1430	2.50	TBA120C	1.20	TDA1035T	3.50
SL1432	2.50	TBA120CQ	70p	TDA1037	2.72
SN15846N	60p	TBA120S	70p	TDA1170	2.15
SN74123N	65p	TBA120U	1.00	TDA1170S	1.25
SN74154N	1.40	TBA395	1.00	TDA1200	2.42
SN76001N	1.40	TBA480Q	1.40	TDA1270	2.76
SN76110N	1.14	TBA510	1.90	TDA1327	2.53

Thorn 8/8K5 ex equip panels untested	2.88
PSU	2.88
FTB	3.75
Decoder	4.00
Thorn 9K ex equip panels untested	12.00
PSU	5.00
Decoder	5.00
Thorn 9K6 ex equip panel untested	5.75
Decoder	5.75

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
20 Mixed Valve Bases	1.00

BF154	25	BF852	31	NKT276-	20
BF167	24	BF862	28	NKT452	1.65
BF173	29	BF881	29	OT112	1.32
BF179	32	BF887	25	OT121	2.08
BF180	33	BF890	1.74	R1038	80
BF181	30	BF891	2.08	R1039	80
BF184	30	BF892	30	R2008B	1.40
BF185	30	BF893	30	R2010B	1.10
BF194	16	BF938	40	R2030	7.00
BF195	16	BF950	30	R2265	1.30
BF196	16	BF951	34	R2305	80
BF197	15	BF952	34	R2322	50
BF198	19	BF116	1.50	R2443	25
BF199	15	BRC1693	1.43	RCA16446	30
BF223	18	BU105	1.00	RCA16549	1.25
BF224	19	BU126	1.10	RCA16680	1.40
BF238	20	BU207	1.05	RCA16789	1.13
BF240	9	BU208	1.15	RCA16840	1.42
BF241	21	BU208A	1.15	RCA16842	1.38
BF255	10	BU326A	1.30	RCA16845	1.20
BF256LB	38	BU407	1.70	SP8385	65
BF256S	38	BU408	2.76	SI299	2.25
BF257	28	BU500	2.30	S28000	1.25
BF259	28	BU526	2.46	T6050V	1.30
BF271	25	BU806	1.80	T6052V	1.30
BF272	14	BU807	2.94	T9003V	1.25
BF337	29	CI129	9	T9010V	1.45
BF338	41	CI172B	9	T9035V	1.30
BF354	40	ES386	54	T9054V	1.00
BF362	50	E9003	29	T9039V	1.10
BF391	21	E9005	25	TC145X	50
BF394	16	ME0404	19	TC146	48
BF422	47	ME0412	19	TC106C	40
BF423	53	ME6002	10	TIP29	42
BF450	43	MJ2501	2.36	TIP30	42
BF453	53	MJ3001	2.21	TIP31	35
BF456	37	MJE340	59	TIP2	43
BF459	40	MJE350	59	TIP33	61
BF461	59	MJE2955	1.40	TIP41	42
BF556B	35	MJE3055	15	TIP42	45
BF596	15	NKT241W	8	TIP110	61
BF694	16	NKT241G	8	TIS91	25
BF757	62	NKT241Y	8	ZTX550	30

TBA530	1.26	TDA2002	2.80
TBA540	2.10	TDA2030	2.10
TBA550Q	1.82	TDA2522	2.10
TBA560C	2.10	TDA2530	2.60
TBA641	2.05	TDA2540	3.50
TBA651	2.50	TDA2560	3.50
TBA720A	2.49	TDA2581	3.00
TBA750	2.20	TDA2591	1.95
TBA800	1.62	TDA2611A	1.96
TBA810AS	1.00	TDA2640	2.90
TBA820S	2.08	TDA2690A	1.50
TBA950	1.95	TDA4500	6.00
TBA1440	1.92	TDA5000	5.40
TCA270SA	1.05	TDA5003	2.90
TCA270C	1.40	TCEP100	3.48
TCA270CQ	1.05	TEA1009	1.95
TDA1004A	4.00	MC14426P	4.80
TDA1035T	3.50	MC14429P	4.80
TDA1037	2.72	UA1008A	5.00
TDA1170	2.15	UA759PC	2.50
TDA1170S	1.25	UA1008A	2.66
TDA1200	2.42	ULN2165	1.30
TDA1270	2.76	ULN2216A	1.25
TDA1327	2.53	UPC135C	5.75
		SC9483P	1.40
		SC9511P	1.40
		SW153	2.50

Thorn 3/3K5 ex equip panels untested	3.75
PSU	3.75
FTB	3.75
Video	2.50
Chroma	2.00
FTB	2.75
IF	1.75
Conv. 3K	3.00
Conv. 3K5	3.75
Autovox Decoder FG/01 boxed	5.00
Thorn 4000 Convergence panel ex-factory	3.75
Thorn 4000 PSU panel ex-factory	2.50
Thorn 3K5 beam limiter board new	1.75
Thorn 3	


INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

ALSO AVAILABLE
 Analogue Multimeters
 Digital Multimeters
 Oscilloscopes
 Signal Generators
 Digital Frequency Meters
 Pattern Generators
 CRT Tester/Rejuvenator
 T.V. Field Strength Meter
 Digital Capacitance Meter
LARGE S.A.E.
FOR COMPLETE LIST.

**LEADER LCT-910A
 C.R.T. TESTER-REJUVENATOR**


Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.

- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors. Size: H 230mm W 330mm D 120mm.

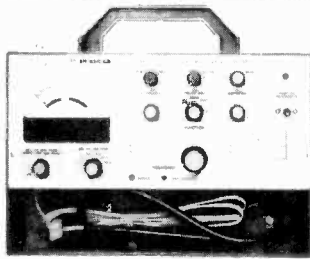

PRICE £199 + £29.85 VAT

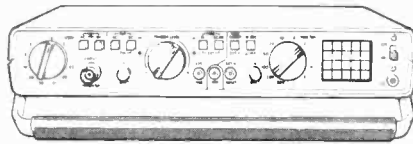**THE VERY LATEST SC110A LOW POWER,
 FULLY PORTABLE OSCILLOSCOPE.**



The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**

Full Sized Performance

- 10 MHz bandwidth.
- Full trigger facilities are provided including TV frame, or TV filtering adaptor.
- Size 255mm x 148mm x 50mm.
- 10 mV per division sensitivity.
- Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.


PRICE £165.00 + £24.75 VAT

Accessories: Carry Case £5.95 + £0.89 V.A.T.
 × 1 Probe £7.50 + £1.13 V.A.T.
 × 10 Probe £8.50 + £1.28 V.A.T.
 × 1/× 10 Switched Probe £10.50 + £1.58 V.A.T.
 AC Adaptor £6.95 + £1.04 V.A.T.

LOPT TESTER


BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER
 Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC

PRICE £25.99 + £3.VAT

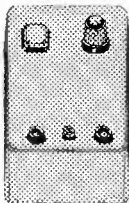

**LEADER HIGH VOLTAGE
 METER EHT PROBE**

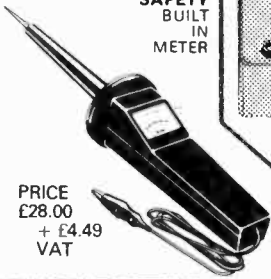Measures up to 40 K.V. D.C. with **SAFETY BUILT IN METER**



PRICE
 £28.00
 + £4.49
 VAT

* **FULLY GUARANTEED**

CRT TESTER-REJUVENATOR

BK's C.R.T. TESTER-REJUVENATOR
 Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC


PRICE £32.00 + £4.80VAT



**HAMEG HM 203-5 20MHz
 DUAL TRACE OSCILLOSCOPE**

SPECIFICATION:

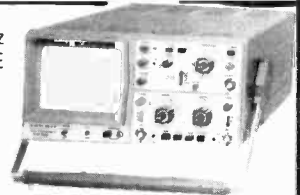- BANDWIDTH DC-20MHz
- SENSITIVITY CH1, CH2 2mV-50V/DIV
- TIMEBASE 40ns to 0.2S CM
- TRIGGER DC-40MHz Auto-Normal-TV
- CALIBRATION OUTPUT
- CH1 ADD AND INVERT FACILITY
- ALT/CHOP SWITCH
- LARGE RECTANGULAR SCREEN 8 x 10 cms
- BUILT IN SEMICONDUCTOR COMP. TESTER
- SIZE 285mm x 145mm x 380mm
- SUPPLY 110-125-220-240V AC 50-60Hz



**WITH COMPONENT
 TESTER**

PRICE
 £270.00 + £40.50 VAT
 Optional probes as above

2 YEAR WARRANTY

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.



B. K. ELECTRONICS Dept. 'T',

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,
 ESSEX. SS2 6TR TEL: 0702-527572



CentreVision

TEL: 0222-44754

SLOPER ROAD

LECKWITH

CARDIFF CF1 8AB

OPPOSITE CITY FOOTBALL GROUND

5 MINS FROM M4

TELEVISION/VIDEO

(VHS + BETA)

FROM £85

- ★ ITT CD752 REMOTE WORKING **£90**
- ★ PHILIPS G11 FROM **£40**
- ★ GEC STARLINE 22-20 (Remote) **£35**
- ★ PYE CHELSEA **£25**
- ★ THORN 9000 20" **£35**
- ★ DECCA 22" BLACK FRONT VERICAP **£15**
- ★ RANK T20 REMOTE **£48**
- ★ PHILIPS 550 IN 10's **£18**


PRICES SUBJECT TO VAT

OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30

SATURDAY 9.00 - 1.00

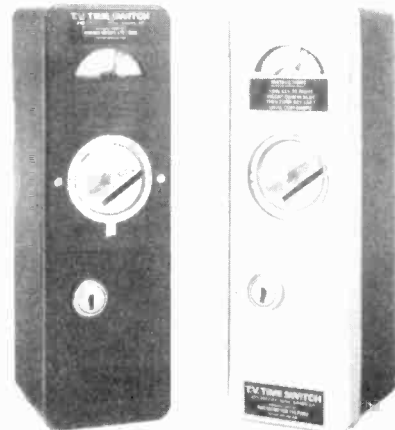**CUSTOMER CAN'T PAY?
 DONT LOSE HIM FIT A TV METER**



COINAGE
 AVAILABLE
 10p
 50p
 £1

COMPLETELY VARIABLE TIMINGS

Alberice METERS LIMITED

MANUFACTURERS OF TV COIN OPERATED

METERS CONTACT (0202) 674272

87-89 Sterte Avenue,

Poole, Dorset. BH15 2AW.

Telex: 418253 LUMIC G

Big Foot

Les Lawry-Johns

I thought I was the only one here who put his foot in it at least once a day – often more frequently. Now there are two of us. That puppy Zeb has grown rapidly and is now rather large. He'll get bigger – if he lives that long. Honey Bunch tried to bash in his brains (?) the other day after he'd ripped her prize plants out of the ground and then pulled them to pieces. I tried to act as peacemaker and ten minutes later was ready to kill him myself. He'd chased the cat through the shop and she'd leapt up on to a shelf and knocked off a record player just as the owner called to collect it.

Now that the weather is warmer I get a brief respite because he stays outside on a long lead for at least five minutes during which I can get just a little work done. To be fair though that's all we seem to be getting lately – just a little work, not really enough to pay the bills. Charge more they all shout. No. Not when there's not much work coming in. The time to charge more is when there are plenty of jobs and you can afford to lose a few.

What am I rabbiting on about? Sorry, it's the dog you see, he's having an effect on my nerves. When customers try to talk to me I stare past them with my face twitching and they think I'm going funny. Of course I'm not . . . I'm not . . . I'm not.

The CTV14R

Like the chap who brought in the Fidelity CTV14R. "It didn't cost much to buy so I don't want to spend much on having it repaired. Not more than say fifteen pounds."

So I took it in, hoping for a nice dry-joint. What a hope. The fuses were intact and there was a high voltage at the collector of the BUX84 chopper transistor. There was the same voltage, instead of 120V, at its emitter. It was short-circuit. So I stuck another one in. Switched on and there was a funny tripping noise as the h.t. started to rise and then collapsed. I was afraid that the line output transformer was at fault but didn't want to think about it. I checked the line output transistor carefully and then the diodes fed from secondary windings. One (D34) was short-circuit. Glory be. Now normally I would have checked around to see what had killed it, but I had to put my big foot in it. I put another diode in and of course the result was the same tripping. The reservoir electrolytic has shorted I thought, but although a short was found to be present it wasn't the capacitor's fault. When I isolated pins 2 and 5 of the TDA1170 field timebase i.c. the tripping stopped and a nice bright white line appeared across the screen to show that the set was happy to work without the chip to upset things.

So I looked for a TDA1170. I looked where they should be and then where they shouldn't. Perhaps I couldn't see properly? I looked at my glasses. They were smudged. I wiped the lenses and one broke away from the frame as the screw snapped off. Not my new glasses, my old ones – as you'll recall I can't wear my new ones as I can't see close up with them. I even have to take my old ones off to see really close. I knew I didn't have any screws small

enough so I had to stick a piece of wire through the metal frame and solder both sides as I'd done when the lens at the other side broke away long ago. That's why I got the new ones I can't wear. I still couldn't find any TDA1170s however.

"What's wrong" asked Honey Bunch, who was playing ball with the dog.

"I can't find any TDA1170s love, even though I've cleaned and mended my glasses."

"Perhaps you've used them all."

"If I'd used them they'd be on the order sheet."

So I looked at the order sheet and they were on it. Then back it came in a blinding glimpse of the obvious. The Normende. That's where they went, together with the 630mA fuses. So I whipped a TDA2600 off the shelf and dashed down to swap it with Don and Ray.

"Ah Les" they greeted me. "Glad to see you. You don't happen to have a spare TDA2600 up at your shop do you? We're right out what with all these G11's gobbling them up." So I produced the TDA2600 from my pocket and they were astounded. I modestly looked at the ceiling and then at the teapot.

"What do you want in exchange for it?" asked Don.

"Nothing really, but I'll take a TDA1170 if you like."

So after joining them over a cup of tea (they don't have whisky down there) I nipped off carrying my precious chip which completed the Fidelity repair when fitted. The heatsink is a pest to get off but nowhere near as difficult as the one on the Normende. Perhaps it's my Weller soldering gun that's getting old (tighten up the nuts you fool).

Mack and Millie

These very nice people are old friends of mine and live not too far away in a select area where not very much happens except when their grandchildren visit and all hell breaks loose. Mack had phoned to say that their 26in. G11 had broken down. Their house was on the right as I drove up so I pulled over and ran the nearside wheels on to the path outside their gate and switched off the lights. Now Millie is a local magistrate, and when I went in she was going on about thoughtless motorists parking on the pavements all over the town. After exchanging the usual pleasantries I got on with the set and found a funny fault in the power supply. To save time I nipped out to the car to get my spare panel and was back in a flash.

"My God that was quick" commented Millie.

"Well I've parked on the pavement just outside" I admitted.

"YOU'VE DONE WHAT?"

"See you in court Millie."

The Estimate

A chap had left an ITT CVC20 and a message to the effect that £25 was his limit. After quite some time it transpired that the tripler was faulty and that the line output transformer was overheating with the tripler disconnected. After replacing the BU208 and fitting all new parts (I was curious) a blank raster with just a shadow of a picture was resolved. The sound seemed to be o.k. but the contrast control had no effect. Tests cast doubt upon the TBA560 but replacing this merely produced an overbright raster with no signal (vision) at all. At this point I removed all the new stuff and carefully replaced all the faulty items. I should suffer. He was most upset when given an estimate.

Teletopics

IT'S NOW LEGAL

The government has altered the rules on satellite TV reception. Until now it has been necessary to apply to the Department of Trade and Industry for a licence, which was granted only to cable TV operators and organisations carrying out research. Individuals can now apply for a licence under the Wireless and Telegraphy Act – local planning permission to erect a dish aerial of any size is also likely to be necessary. Licences will also be available for linking TV signal distribution systems, for example in hotels and blocks of flats, to a master satellite TV receiver. Restrictions will be imposed to protect the interests of cable TV networks – a licence for SMATV (satellite master aerial TV) operation will not be provided in areas where a wideband cable franchise has been awarded or where a franchise has been advertised or is pending. The move has been welcomed by cable concerns and the TV industry, the hope being that business opportunities will be opened up, leading to increased UK production of satellite TV receiving equipment. Thorn EMI, Telefusion and Visionhire are amongst the companies that have already announced plans to supply satellite TV receiving installations.

SHOWTIME

As we go to press the annual London hotel radio and TV trade shows are in full swing. The main theme on the TV side is a far wider range of models fitted with FS tubes and greater emphasis on cabinet styling – the FS type tube seems to favour “monitor-look” cabinets. Mullard have announced the FSQ tube which is supposed to be even flatter and squarer and should be available in Philips and Pye sets later this year. Doric were showing large-screen (20-26in.) sets fitted with the new Rediffusion Mk.6 chassis. The new Network 14in. colour portable, Model NWC1430, is of interest in that full remote control can be added to an initially manually controlled version.

SATELLITE TV NEWS

Fresh hopes for the start of a UK DBS service have come with the announcement from Unisat of sharply reduced quotes for the provision of a satellite system. Unisat have offered the DBS consortium ten options for different degrees of satellite system management and operation. Meanwhile tentative agreement has been reached on what should be shown on the three DBS channels: the first channel would be used for recently released films and for TV series prior to their being shown on the existing networks, the second would concentrate on live sports coverage and a 24-hour news service while the third would feature popular entertainment such as TV games and soap operas.

GEC McMichael have developed an elliptical dish aerial which is claimed to offer much improved performance compared to the conventional circular designs. The dish is already being used in the Newshawk 14GHz portable satellite news gathering system. It features an offset feedhorn, maximum side-lobe rejection, reduced wind resistance and excellent portability.

Agreement has been reached between Ireland, Spain and Portugal to share a DBS satellite – the three countries were allocated the same orbital position at 31°W under the 1977 Geneva ITU agreement.

AUTOMATED TV PLANTS

Most TV receiver assembly lines have been highly automated for many years now, with the use of automatic component insertion in the PCBs. This is fine for the smaller components but larger, more awkward components have always presented problems. The difficulty is being overcome by adding robots to the assembly lines. The use of computer-controlled robots by Toshiba has for example increased the proportion of components that can be auto-inserted to 95 per cent. Use of computer control has additional advantages in that board revisions can be put into effect simply by keying the required information into the computer. Once a board design has been changed it can take as little as half an hour for the computer to revise the operation of the line robots.

Thorn EMI Ferguson have set up an advanced manufacturing development centre at their Enfield factory to investigate the application of the latest automation technology to the assembly of TV sets and VCRs. Amongst its facilities is a pilot assembly line using IBM robotics systems to insert a range of odd-form electronic components. The centre undertakes feasibility studies based on experimental data from working models. IBM's robotics systems employed at the centre are programmed using the IBM Advanced Manufacturing Language (AML), a high-level language designed for manufacturing engineers and manufacturing application programmers. Its key features are manipulator control, sensing, intelligence (the ability to modify system behaviour in accordance with preprogrammed ways) and data processing. These are being harnessed to investigate flexible assembly techniques.

SINGAPORE'S TELEVIEW SYSTEM

A consortium of UK firms lead by GEC has been awarded the contract to develop Singapore's Teleview system. This is an advanced system that combines features of teletext and viewdata: it's also a high-capacity system, enabling the service to carry high-definition pictures, graphics and Chinese language characters in picture form. Marconi are to supply an initial 1,100 terminals to Telecoms of Singapore – 800 with hand-held keypads for residential use and 300 keyboard versions for business use. The contract also includes editing terminals, some with full typewriter style keyboards: each terminal will double as a 256K RAM personal computer. Teleview uses both telephone links and off-air data transmission: users send out requests via the telephone link and receive signals off-air on their terminals. The service will also operate in both directions via the telephone links in the event of TV signal interruption. The Singapore Telecommunications Authority hopes to have a million subscribers to the service by 1990.

SERVICE BRIEF – THORN TX90

Cases of failure of the line output transistor TR112 in the Thorn TX90 chassis have been traced to leakage in transistor TR109 (BC307B) in the overvoltage trip circuit. This leakage results in reduced line drive. To overcome

the problem R246 (47k Ω) has been added between the base and emitter of TR110: it's recommended that this resistor is added in all cases of failure of TR112.

VCR NEWS

1984 was certainly the year of the VCR in the USA: sales increased by over 86 per cent, from just over four million to well over seven and a half million. The markets are now awaiting VCR exports from Korea – up till now these have been prohibited under the terms of the licence agreements with Japanese manufacturers. Models from Samsung are expected to be available in the UK this autumn – two models were on display at the Samsung trade show. The basic model is expected to sell for around £370.

VCRs using an improved Betamax specification are to be introduced in the USA. The new system – Super Beta – features increased luminance bandwidth plus new video noise reduction and pre-emphasis circuitry. According to Sony the result is a picture resolution of 300 lines and a signal-to-noise ratio of around 45dB.

The launch of Kodak 8mm video equipment in the UK has been postponed until next year “at the very earliest”.

The Ferguson Videosafe is an anti-theft device that sells for around £24. It's in the form of a VHS cassette that can be slotted in the machine and locked in place. If an attempt is made to move the machine or eject the device a 98dB alarm signal is produced until switched off using the right key. It's also available as the Videolok.

NEW TV SCREEN FILTER

A new range of easy-to-fit filters for use with TV sets and VDUs has been announced by Wireless and Electronics Ltd., 5 Lansdowne Way, London SW8 1HL (01-735 7910). The filter covers the whole screen and is available in sizes from 9in. to 26in. Each one is individually boxed and comes with neat brackets and clips to make fitting a simple matter. The filters are made of a hard plastic material and result in reduced flicker and the removal of most of the ultra-violet light radiation from the tube.


VIDEO CERTIFICATION

Certification of prerecorded videocassettes under the Video Recordings Act is to be carried out by the British Board of Film Censors which is to be renamed the British Board of Film Classification. Certification relates to films – music programmes are exempt unless they include depiction of sex and violence to “a significant extent”. There are 58,000 titles on the Department of Trade and Industry's register: certification of these will be carried out over a three year period from the implementation of the act – new releases will require immediate certification. Lists of certified films will be available from the Home Office at about £20 a set.

CABLE NEWS

Work has started on the installation of the Clyde CableVision and Croydon Cable Television systems. The Clyde system is of the switched-star type, qualifying for a 23-year licence. A key component is a new switch jointly developed by GEC and Delta Kabel for the UK market. British Cable Services have started work on the Guildford service. This will use the advanced System 8 network.

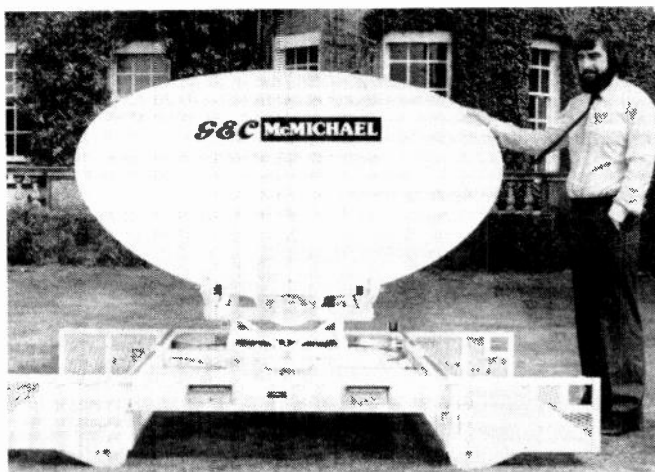Just one application has been made for each of the five



GEC McMichael's Newshawk satellite news gathering system features their new elliptical dish aerial.

recently advertised second group of cable TV franchises – London Docklands, W. Surrey/E. Hampshire, Wandsworth, Bolton, and Cheltenham/Gloucester. The Cable Authority has announced that it is not disappointed with the lack of competition for these franchises and that each application will be given the fullest scrutiny.

A monthly publication in full colour, the *Cable TV Guide*, started with the May issue. It covers the five main channels (The Movie Channel, Screen Sport, Sky Channel, Music Box and The Children's Channel) seen by 90 per cent of UK Cable viewers and is being sent free to some 500,000 cable TV subscribers and potential subscribers. It will also be available through newsagents at 35p a copy.

Qualified optimism on cable TV is expressed in a new report from Communications and Information Technology Research. 8.5 per cent of households in W. Europe are now connected to a cable network and the percentage is expected to double over the next ten years. Holland, Belgium and Switzerland have the highest percentage of households connected to cable systems. CIT believes that 6.5 per cent of UK homes will be linked to a cable network by 1989.

The Joint Industries Committee for Cable Audience Research (JICCAR) has carried out the first audience research survey of UK cable TV users. It gives cable TV a somewhat down-market image, though the incidence of VCR and microcomputer ownership amongst cable users is well above average. The specific cable channels account for 19 per cent of viewing in households connected to a cable network.

ODDS 'N' ENDS

A 13A moulded plug-and-lead set is now available to equipment manufacturers from Mullard. It's been introduced in the interests of improving the safe use of both industrial and domestic electrical equipment. The advanced design of the CW3102 plug-and-lead set incorporates the usual safety features plus extras including sleeved line and neutral pins, a built in fail-safe system and very high mechanical strength.

Non-electrical soldering is what you get with the Oryx Portasol soldering iron which is available from STC Electronic Services, Edinburgh Way, Harlow, Essex CM20 2DE. The iron uses a built-in butane gas supply that provides a power equivalent to 60W with a variable bit temperature up to 400°C. A single gas refill gives up to one hour's continuous use.

11GHz Low-noise Amplifier

Hugh Cocks

The 11GHz low-noise amplifier to be described is intended as a companion to the low-noise downconverter featured in the February issue. The use of waveguide at the input and output means that different LNA and downconverter combinations can be tried. Construction of the unit is reasonably straightforward if one is experienced in r.f. techniques. Those who have built LNAs for use at 4GHz will find the unit similar but more compact. A matching regulated power supply built around a d.c.-d.c. converter i.c. is used; alternatively the power unit described in the 4GHz LNA article (September 1983) can be adopted, though it's much larger physically.

The LNA's housing is similar to that of the downconverter module. Fairly elaborate screening is required between each of the gallium arsenide f.e.t.s to prevent instability which could occur since the width of the housing is sufficient to support waveguide propagation. Constructional details of the metalwork will be provided, though ready made metalwork and p.c.b.s are available. Before going farther a word of warning. If you're unsure about your abilities with this type of construction it's advisable to leave well alone – the GaAs f.e.t.s alone cost over £100 and are quite easily destroyed if care is not exercised.

Circuit Description

The design of the LNA is based on an application note from California Eastern Laboratories covering an 11.7-12.2GHz (US satellite band) LNA which employed two transistors. The circuit has been rescaled for 10.95-11.7GHz and an extra transistor has been added to increase the gain. The overall gain should be at least 25dB with a noise figure of around 3dB. The first two GaAs f.e.t.s are NEC type NE71083, the final one being an NE70083. Other devices, such as the Mitsubishi series, will work but since the board is not optimised for these

odd tuning effects will occur due to mismatches. The circuit is shown in Fig. 1; the PCB track layout is shown in Fig. 2.

The incoming signal is transferred by a pickup wedge (see later) to a 50Ω section of printed track. A 10pF chip capacitor then couples the signal to a section of track that acts as a 36Ω, quarter-wave transformer which is followed by two 23Ω open-circuit stubs. This network matches the 50Ω input impedance to the optimum source impedance of 26Ω. The coupling between the first and second stages is less complex because the source and load impedances are similar: a 50Ω, 0.538 wavelength transmission line is used. The second stage's output matching network is series resonated with a 50Ω, 0.04-wave line and a 21Ω, quarter-wave stub which is then coupled into the third stage via a 50Ω transmission line section and a 50Ω, quarter-wave stub (in practice this must be shortened, see later). The output from the third stage uses the same series resonant network as the second stage. This is coupled by a 10pF chip capacitor to a 50Ω section of track which feeds the output wedge, i.e. microstrip to waveguide launcher.

The bias and drain supplies for each stage are brought in via printed chokes, with 1,000pF decoupling chip capacitors. The arrangement is identical to that used in the 4GHz LNA. The 10pF coupling chip capacitors are special types with a high Q at 11-12GHz. Mount them with the body's dot indication on the side rather than parallel with the board. This is due to the unwanted resonance effects that can occur with capacitors used at this frequency – the 4GHz type of 10pF capacitors shouldn't be used.


Mechanical Details

The f.e.t. source leads go through the board. Due to the slight inductance still present a screen is placed across each transistor, with silver epoxy adhesive used to bond the screen to the source lead protruding above the board. These screens also prevent 11GHz signals being propagated down the housing.

The PCB is Teflon based, has a dielectric constant of around 2.2, and is 0.01in. thick! Both 3M Cu-Clad 217 and Rogers Duroid 5880 have been used with good results. Working with a PCB as thin as this takes a little getting used to: the main point to remember is that with too much heat the track will start to peel away, also that the board is easily marked by sharp objects.

The case is similar to that of the downconverter modulator. Make the main body of about 0.9mm thick tinfoil. With the prototype units the two sides and the bottom were bent from a single piece (see photo), flanges being soldered to each end. It's convenient to make the flange size identical to that of the downconverter module.

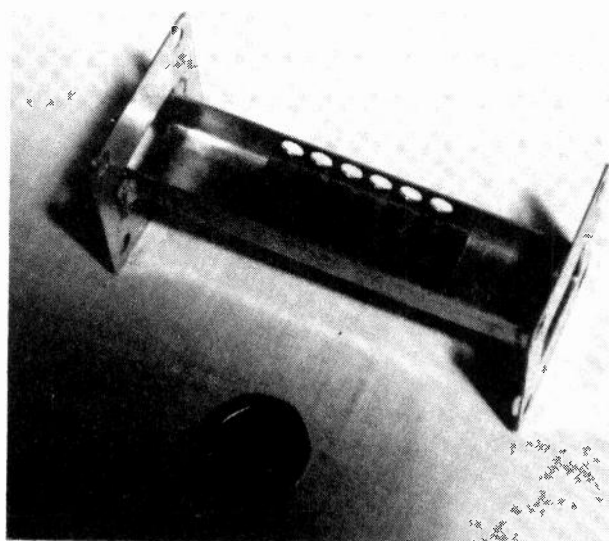The unit's lid is sectional and may be made from thinner gauge tinfoil if required. The input and output sections of the lid have the pickup wedges (see Fig. 3) attached to them. The upper, rear sections of the wedges go through slots in the lid, to which they are soldered: the wedges must not be soldered on the inside of the case.



Photograph of the LNA case, with the input and output flanges and the LNA board fitted and the side holes for the power supply feeds drilled.

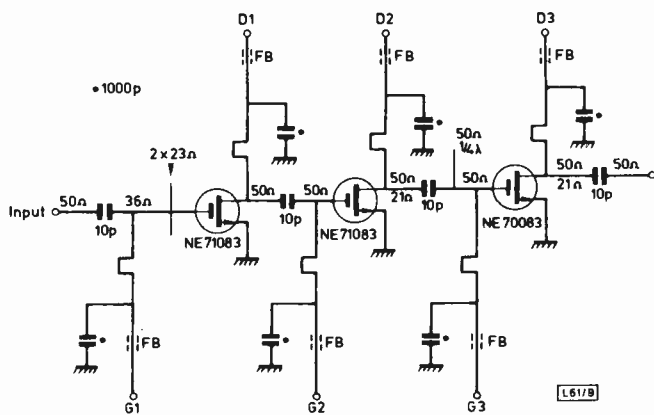


Fig. 1: Circuit diagram of the low-noise LNA.

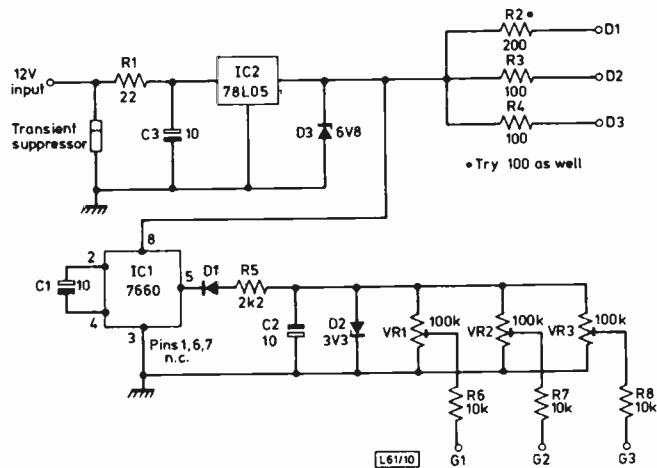


Fig. 4: Power supply circuit. Veroboard can be used.

of the PCB, then put solder through the holes carefully. It's a good idea to hold the board in place with a block of metal to act as a heatsink and prevent it warping in the heat. Make larger holes where the transistor source leads go through the board so that they can go right through to the outside of the case.

Six holes must be drilled in the side of the case to allow the bias and drain supply connections to be made. Because of the extremely small size of the circuitry normal feedthrough capacitors cannot be used – they are much too large. With the prototype units a ferrite bead was used on the inside, covering each lead going to its pad, and a ferrite bead was used in each hole. Sufficient decoupling is provided with the chip capacitors on the board. Solder the decoupling capacitor earthing pads to the side of the case.

After the amplifier has been built screening must be placed over the PCB. An internal wall runs along the length of the PCB over the dead area of the board to prevent any waveguide propagation. The three screens covering the f.e.t.s are then attached to this wall and to the unit's outer wall. By the time the ferrite beads are in place there's not too much room to attach the screening to the outer wall. Silver epoxy adhesive can be used here if it's difficult to use a soldering iron. A cutout for each transistor must be made in the screening: it must be a tight fit and silver epoxy must then be used to cover the remaining sections of source lead and connect to the screen (do this with extreme care, see later).

The lid covering the PCB must be cut into three sections. Odd effects can occur when these are put in place and this must be checked during construction.

The Power Supply

The power supply is relatively straightforward (see Fig. 4). The incoming 12V supply is fed via R1 to a 78L05 5V regulator i.c. which has a 6.8V zener diode connected across its output to provide protection in the event of regulator failure. Resistors R2-4 provide the drain supplies for the f.e.t.s. A simple d.c.-d.c. converter chip, type 7660 (RS stock no. 304-598), is used to generate the negative gate bias required by the f.e.t.s. The output from pin 5 of the i.c. is rectified by D1 and smoothed by R5/C2, with the 3.3V zener diode D2 providing regulation. VR1-3 set the gate bias voltages, the sliders being linked to the gates via R6-8. Miniature presets (RS 185-937) were used to fit the small board. By mounting the feed resistors vertically the board is small enough to fit on the bottom of

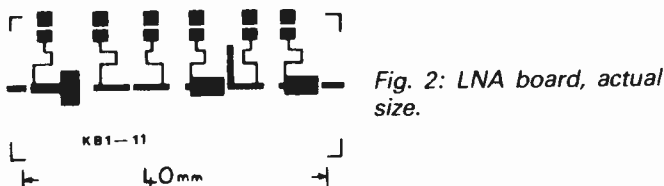


Fig. 2: LNA board, actual size.

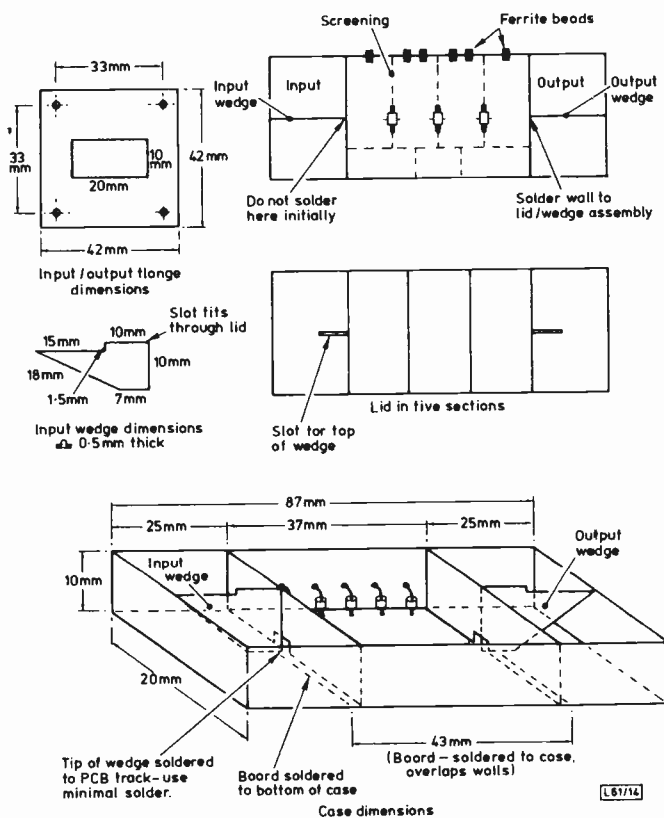


Fig. 3: Details of the case and screening.

Once the panel has been mounted in the case the wedge/cover assemblies are put in place and the "tips" of the wedges are soldered to the input and output striplines. Tuning screws can be inserted in the input and output waveguide sections in the same place as the downconverter input tuning screw. Wedge thickness does not appear to be too critical. The Mitsubishi downconverter module uses very thick metal: the prototype LNAs used about 0.5mm thick tinplate. Some experimentation here may prove beneficial.

Attach the PCB to the bottom of the case in a similar manner to that used in the downconverter: drill a small number of holes in the bottom of the case, tin the bottom

the LNA housing.

I recommend fitting a transient suppressor across the 12V input to prevent possible spikes killing the transistors. Provision for this is not made on the board but the suppressor can be soldered to the top of the input resistor (R1) and to the ground plane on the component side of the board. The type used is RS stock no. 283-261 which cuts in at 16V. Its response time to a transient is of the order of a picosecond – so far no transistors have blown in mysterious circumstances! The band end goes to the positive side of the supply.

As previously mentioned the 4GHz LNA power supply could be used but is much larger.

Test the unit thoroughly before connecting it to the f.e.t.s. On some boards D2 tends to load down IC1 a little. If this occurs, disconnect D2 – the negative supply obtained from the chip is fairly stable and only a small percentage of the available supply is required. By increasing R5 to say 22k Ω the potential dividing action with the presets will drop the voltage sufficiently.

Construction

Start soldering the components on the board after soldering the board to the case. Solder all six decoupling capacitors in place first then check for possible shorts across them – this can happen, and once a transistor is in place it's all too easy to blame it. Next fit the 10pF coupling capacitors. Follow the previously mentioned instruction about mounting them the correct way and use a very fine soldering iron bit and as little solder as possible, consistent with a good joint.

At this point it's advisable to connect the power supply and check that the voltages are reaching the stripline. The board can be fitted to the bottom of the case using either copper wire legs or double-sided tape: ensure that the print side of the board cannot be short-circuited to the case if pushed hard. Use thin, insulated wires through the ferrite beads. It's easiest to glue each bead on to the board and into the holes after taking the wire through.

Next comes transistor fitting – always a worrying time! Ensure that the thick source leads fit through the board: the best way to do this is to use a small, flat screwdriver blade to punch the board gently. The gate and drain leads must be cut as short as possible to connect with the stripline that butts right up to them: no appreciable length of lead should be on the stripline. The lead with the diagonal slash in it is always the gate lead, the one at 180° to it being the drain (the two source leads are much wider). NEC have moved the position of the red dot from being adjacent to the drain to adjacent to the gate lead recently so this is not an accurate guide. Once the leads have been cut it's all too easy to mount the device the wrong way round, so make a note of which way round the dot is to the gate/drain leads.

Solder the source leads initially using only a small amount of solder underneath, consistent with good earthing, in case the transistor (heaven forbid!) should need to be removed if it has died. Lay the gate and drain leads – what there is of them, no more than 0.1in. – flat on the stripline and solder quickly, using a minimum amount of solder. Normal soldering precautions should be taken with the GaAs f.e.t.s – earth the iron's bit to the case and make sure that you're not at a potential to the whole assembly. Never use a soldering gun if you wish the transistors to work afterwards!

When all three transistors have been connected, and

before the screening is inserted, check each one *individually* with its connections made to the power supply. Set the gate bias at around 0.5-1V negative (avoid using a meter at the gate connections) and monitor the drain current by checking the voltage at the drain feed resistor. The voltage should vary between 5V with high negative bias at the gate to less than 1V with minimum bias. Optimum bias is with around 2.5-3V at the drain. If all three transistors are connected to the power supply without screening and without the input/output terminations in place bad instability will occur. This will show as erratic drain current variations.

If all's well, solder the source leads properly on the bottom. If you find that the drain voltage won't move from around 0.5V there's either a short-circuit in the feed to the gate or the transistor has died. If the drain voltage is stuck at 5V it's not reaching the stripline. If there's a problem here cut the feed choke on the board to isolate the transistor as it could well be that the decoupling capacitor has shorted out or has a sliver of solder underneath it.

The screening must next be fitted. Fig. 3 shows the approximate positions of the screens. The sub-wall is attached to the main wall by two stand-off pieces of tinfoil. The end of this sub-wall should be soldered to the output wedge/lid assembly in due course but avoid soldering to the input wedge/lid assembly initially – sometimes the signal is better with it disconnected (check on a live signal later).

It's a good idea to smear the silver epoxy between the transistor and the screen as each transistor screen is fitted. Start with the centre screen and work outwards. Smear the adhesive just where the source leads protrude from the body. Be very careful not to smear any between the gate or drain leads and earth or the transistor won't work, being effectively shorted out by the glue. Silver epoxy has a consistency that's slightly different from normal epoxy – it's similar to hard butter. Small granules can come adrift, so make sure that it's firm. It also takes a long time to dry, but this doesn't affect the electrical performance materially.

Once this has been done, solder the input and output wedge lids to the case (on the outside only) and carefully solder the rear tip of each wedge to the panel, using only a small amount of solder. Leave any tuning screws at the input/output screwed fully out and check that all three transistors behave correctly as the d.c. bias is varied. Leave each transistor with about 3V at its drain. If all's well here we can proceed with the testing.

Testing

First of all cut down the stub between the second and third transistor to about half its original length – this is easier to do before the screening is in place. Access to it will be needed when the LNA is being tuned however.

Bolt the LNA (initially less any image filter) to the downconverter module and switch on the downconverter but not the LNA. When the LNA is switched on a vast increase in noise should be seen on the screen – the noise will vary depending on the settings of the bias presets.

If you find a mass of carriers/patterning on the screen as you tune across the band there's instability. See if it disappears when the output lid is placed over the third transistor. If it does, solder the lid in place, preferably leaving the cut down stub exposed for adjustment. If this doesn't cure the instability, try soldering the internal wall

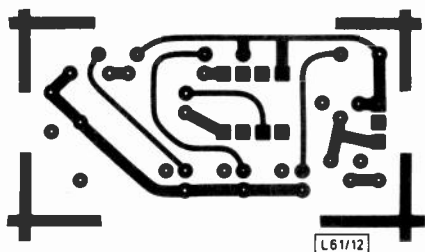


Fig. 5: PSU board track pattern.

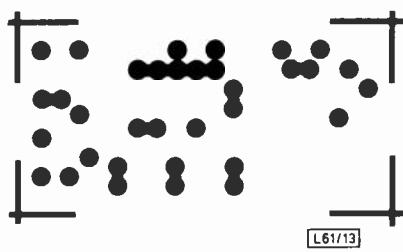


Fig. 6: PSU board groundplane side.

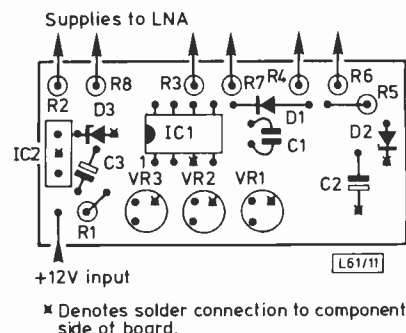


Fig. 7 (right): Power supply component layout.

to the front cover – these two actions should stop any instability. It's also worthwhile checking that the source leads are well earthed as poor earthing here will produce instability. Instability is in general much easier to cure than with a 4GHz LNA, though it can look more violent on the screen.

Connect the LNA to the feedhorn and keep a fairly high i.f. (700-800MHz). Use of a subreflector feed system helps a lot when testing and peaking the unit as all the electronics will be at the rear of the dish. When the dish is aligned with the satellite the signals should appear a lot stronger and u.h.f. breakthrough from local transmissions should be minimal. Without an image filter, signals at the top end of the band may seem noisier than those at the low end. This effect is caused by image frequency noise. With an i.f. of 700MHz the image of a signal at 11.6GHz is around 10.2GHz: the amplifier's gain at 10.2GHz will still be quite high and the noise produced will be superimposed on the wanted 11.6GHz signal. With the same i.f. and an 11GHz signal the image at 9.6GHz will be at a point where the LNA's response is much lower.

Peak the tuning screws and voltage presets for optimum pictures. If the signals are too strong for subjective evaluation of the picture quality move the dish slightly off the satellite. Screwing the downconverter tuning screw inwards from fully open will produce a notch where the wanted signal is lost. Just beyond this point the image frequency will be notched out, giving an improvement to a specific signal. The exact notch point will vary from signal to signal. If a signal meter is being used the signal strength will appear to fall due to the loss of image frequency noise drive to the meter.

If no microwave test gear is available alignment of the LNA is virtually impossible without a wideband image filter. Arrangements have been made to supply a filter in waveguide form to fit between the LNA and the downconverter. It has an insertion loss of 0.5dB and an attenuation of some 30dB at 10GHz. Because of the tight tolerances of the tuning elements in the waveguide it's not practical to give constructional details. Assuming that a filter has been obtained, final alignment of the LNA can begin.

Final Alignment

Check the effect of placing the remaining two covers over the first two stages of the LNA. The signals may increase slightly with the middle cover in place but with the input cover on they may decrease. If this is a problem it's probably best to glue a stout piece of plastic in place of the first metal cover.

Note the effect on the third stage of varying the length of the 50Ω stub. A useful tuning tool consists of a flat piece of wire on the end of a holder – note that due to the

dielectric effect of the plastic this can peak the LNA as well! Some performance compromise may be needed between the top and bottom end of the band. A small piece of wire soldered to the rear end of the input wedge can increase the signal level.

In general the input stripline won't need adjustment. The optimum settings of the bias presents may vary a little across the band. This is fairly normal and is caused by slight variation of the transistor S parameters with different currents – this alters the stripline tuning. If you get a violent effect the transistors aren't matched to the board: this should not occur if the specified types are being used.

It should be possible to achieve good signals from ECS-1 in the UK using a 1.5m dish and this LNA. The noise figure is around 3dB or a little better.

Once the system is working well, find a box to house the electronics. It may be best to use a "dead" section of waveguide at the input so that the LNA is a little away from the elements: cover the front with plastic to prevent ingress of moisture. Take great care to prevent this: microwave signals hate any form of corrosion!

Sources and Acknowledgements

Aspen Electronics Ltd. of 2 Kildare Close, Eastcote, Ruislip, Middlesex (01-868 1188) are the UK agents for the Dielectric Laboratories Inc. (DLI) 10pF chip capacitors type DI 2A 100K 50 LD. The 1,000pF decoupling capacitors are not too critical. Hugh Cocks TV Services of Cripps Corner, Robertsbridge, Sussex TN32 5RY (058-083 317) can supply the 10pF capacitors, ready etched LNA boards, metal housings and waveguide bandpass filters.

The NEC GaAs f.e.t.s can be obtained from Castle

MITSUBISHI

MGF-1402
MGF-1403
MGF-1412
MGF-1801

GaAs FETs

FROM STOCK


Aspen Electronics Limited

UK representative for Mitsubishi Electric

2/3 Kildare Close, Eastcote, Ruislip

Middlesex HA4 9UR

Tel: 01-868 1188 Tlx: 8812727

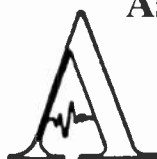

Microwave Ltd., Brookfield Drive, Aintree, Liverpool L9 7AN (051-523 4011). Printed circuit board material is available from Walmore Electronics, 11-15 Betterton Street, Drury Lane, London WC2 (01-836 1228) – the board must have a dielectric constant of 2.2 and be 0.01in. thick. The silver loaded epoxy adhesive is RS type 555-

673.

Finally my thanks to everyone who helped with this project: Dave Lewis for the PCB drawings and prototype case design, the two Johns for the image filter, and Mike Stone who had great fun playing with the prototypes and put much work into getting the project off the ground.

VCRs and the Mains Supply

Derek Snelling

The mains supply, or to be more accurate various forms of interference associated with it, can be responsible for many problems with VCRs. The most obvious problem is random fuse blowing: the mains fuse or fuses blow for no apparent reason, a replacement restoring normal operation. Less obvious are the effects on the various microcomputer i.c.s in a VCR caused by transients appearing on the supply lines.

Clock/Timer Problems

Clock/timer circuits are particularly susceptible, with faults such as all the days displayed, a.m./p.m. appearing on a 24-hour clock, the clock losing time dramatically, a meaningless display such as 64.83 hours, or inability to set various timer functions. The problem is often that an internal switch in an i.c. gets tripped into the wrong state: for example, some microcomputer i.c.s have automatic 50/60Hz switching which can get tripped into the 60Hz condition with the result that the clock loses time. The cure in such cases is to unplug the machine from the mains supply, count to ten, then reconnect it. This resets the microcomputer and clears the problem. In some cases a longer disconnection time is required to discharge the backup battery.

Control Circuit Troubles

Microcomputer troubles we've had apart from the clock/timer circuit have been confined to the Mitsubishi HS700 and HS304. With the former the usual symptom is that the cassette can't be ejected or that the lid won't stay closed. Luckily this machine has a reset button near the clock setting controls. Pushing the button with the point of a biro resets the micros and clears the fault. With the HS304 the symptoms are difficulty with closing the cassette lid, the motor running without a cassette in, very slow response to the controls or no response at all. With this machine you need to unplug from the mains, as for clock faults.

Fuse Blowing

Many years of experience have shown that with the exception of some Toshiba V31 and V33 VCRs, for which a modification was introduced, intermittent fuse blowing is generally caused by a faulty mains socket. On a couple of occasions the problem was due to a faulty wall socket; in a few more cases it was caused by a worn multiplug; in over ninety per cent of such cases however the cause has been a worn or faulty two-three way adaptor – the sort of thing where you can put plugs in at the top, front and sides. These adaptors are often worn to the point where a plug will fall out under its own weight. I even had a case

where the live pin stayed in place when the adaptor was pulled from the wall socket.

It's fair to say that when a VCR has a wall socket to itself and the socket is in good condition random mains fuse failure is very rare. One other possible source of trouble however is when the machine is unplugged each night. Not all VCRs have a mains on-off switch (the Mitsubishi HS306 for example), so unplugging and plugging in can result in sparking at the socket and a blown mains fuse.

In view of this, why do some VCRs suffer from random mains fuse failure more than others? The difference lies in the design of the mains filter and the choice of fuse size. For example, the Ferguson 3V29/30 have a 1.25A fuse and an 0.022 μ F mains filter capacitor while the Toshiba V31 was originally fitted with a 315mA fuse and an 0.1 μ F filter capacitor. The Ferguson machines don't suffer from fuse blowing while the Toshiba V31 does. Obviously the smaller the fuse value the more likely it is to fail under surge conditions: fuse sizes have been reduced to the limit in recent times in order to get BEAB approval. Also, the higher the mains filter capacitor value the lower the impedance presented by the capacitor at any specific frequency.

To overcome the problem of random mains fuse failure two courses can be adopted: increase the fuse rating and/or decrease the value of the filter capacitor. Care is required when increasing the value of the mains fuse otherwise safety problems will arise. Toshiba have officially increased the rating of the fuse used in the V31/33 to 630mA. Decreasing the value of the mains filter capacitor is less risky but reducing it to too low a value could allow too many mains-borne spikes to enter the machine and do damage. Toshiba recommend reducing the value of the mains filter capacitor in the V31/33 to 0.0047 μ F.

In Conclusion

To sum up, mains or mains related troubles can cause microcomputer confusion and fuse blowing. Can they cause one-off faults? The two established mains related faults have been confirmed by their relatively frequent occurrence. Apart from these I've had one instance where the capstan i.c. in a Mitsubishi HS306 failed and I'm ninety per cent sure that the cause was a faulty wall socket – I recall that when I did TVs repeated line output transistor failure in the Philips G11 chassis was often caused by faulty mains plug wiring. It would be interesting to hear from readers of any faults they can squarely attribute to a spiky mains supply.

Finally I'd like to emphasize that when I mention a spiky mains supply or mains interference the cause in the vast majority of cases lies within the household rather than coming via the mains distribution network.

Approaches to TV Servicing

S. Simon

We all have our own ways of tackling faulty equipment and tend to get rather set in our ways if we are not usually in the company of others engaged in the same profession. My own approach is to weigh up the symptoms reported and try to make a direct attack on the likely source of the trouble, basing this attack on my previous experience of the model concerned.

With a "no raster, sound o.k." condition for example the approach depends wholly upon the model. If the voltage supply for the sound circuits is obtained from the line output stage, as in most sets manufactured in recent years, it's likely that the line output stage is working and that e.h.t. is present. My first action therefore would be to check the tube base voltages to ensure that the cathode voltages are not too high and that the first anode voltages are high enough, i.e. about 150V at the cathodes and 400V at the first anodes. The next move depends on what these readings reveal.

It's quite common for example to find the first anode voltages missing in a receiver such as one of the GEC C2110 series though the line timebase is clearly in order (e.h.t. o.k. and sound present). My first move in this case would be to check the first anode supply presented to the convergence panel. I would expect to find it present and it usually is. The common failing is the resistor on this panel between PL30-4 and the first anode presets - R506, 560k Ω . In later production this resistor is not on the convergence board - instead it's on the small panel over the line output transformer where it's designated R616. The two nearby 1M Ω resistors R607/8 are also highly suspect in this chassis and are often found burnt up.

Thoroughness

I had an occasion recently to visit a local workshop and was present when one of these sets was put on the bench for servicing. The symptoms were as described above and I was interested in the young man's approach. First he stripped the supply plug and rewired it, checking the fuse etc. He then checked the condition of the 3-15A mains fuse in the set itself - at the top left - and its holder. Next he checked for shorts across the h.t. line and across the thyristor mains rectifier. Satisfied that all was well, he plugged the set in and listened for the e.h.t. to rustle up. He proceeded to check the h.t. voltage against that given in the manual, then most of the voltages on the video panel. Finally he turned to the tube base and found that the first anode supply was missing.

He saw my look and turned his nose up. "We were taught to be thorough in order to avoid comebacks" said he. I crept away and vowed that I too would be more thorough in future. But old habits die hard and I still tend to jump in at the deep end and leave the plugs etc. unchecked.

The Ferguson 9600 Chassis

Shortly after this a Ferguson set fitted with the 9600 chassis required attention. The no raster condition this time seemed to be the result of high cathode voltages at the tube base. We chased this condition back to the

signals panel where we found the 24V supply absent. So we moved over to the power supply panel where we expected to find fuse F511 open-circuit (34V feed to the 24V regulator on the scan panel). There was no voltage at either side of F511 and we then found that the relevant rectifier diode W518 (SKE2G2/02) was non-conductive in either direction. If we'd been more thorough and checked the supplies first we would have saved ourselves some time. Next time we'll check at the diagnostic sockets fitted as the makers suggest.

Pye 725 Chassis

The Pye 725 chassis is the one with the vertical panels. It's given us some headaches in the past. In this case the mains supply was present at the anode of the mains rectifier thyristor but there was nothing at the h.t. fuse and the associated resistors (surge, smoothing and anti-breathing). Not wishing to fall for the old one we carefully checked the continuity of these wirewound resistors (if the surge limiter section goes open-circuit there's no h.t. at either end and nothing starts up). As all was well we returned to the power unit. The two 82k Ω charging resistors R898/9 in the trigger pulse generator circuit are suspect and one of them was found to be open-circuit. In went another and we confidently switched on, expecting to hear the rush of sound and e.h.t. Silence.

We spent a lot of time checking this panel before we returned to the centre h.t. fuse. We were then surprised to find just over 100V present. Resetting the h.t. presets brought the voltage up to normal and the set then behaved impeccably. How were we to know that eager little fingers had adjusted the presets wrongly?

Incidentally if the centre h.t. fuse is found to be open-circuit, waste no time - look into the top of the screened line output section and note the position of the capacitor right at the top (C561, first anode supply reservoir). Note its leadout wires to the print and check for a direct short. Failure to do this can lead you on a merry dance - a replacement tripler can be the first of many unnecessary acts as disconnecting this may leave the fuse intact. We all know this one by now of course, but it's an example of how methodical testing according to the book can lead one astray. Incidentally C561 is 0.1 μ F, rated at 1.25kV.

Rank T20/T22 Chassis

Mention of the Rank T20/T22 chassis will bring groans from those who are fully conversant with these sets. This isn't for you: it's for the majority who are not so fortunate. It's essential with these models to have a clear idea of how the system works. The power supply module is situated beneath the tube. It's a fairly complex self-oscillating chopper circuit designed to deliver a 200V h.t. supply to the right side line output panel. In most cases it does this, the fault or faults being elsewhere.

If the 200V supply is absent, remove the plug from the upper right side, thus isolating the power supply for fault tracing. There are two fuses. The front left side one is the mains fuse. Failure of this should direct attention to the bridge rectifier diodes 7D14-17: it's common to find two

of them shorted, not one. BY127s are suitable for replacement purposes – they have a higher voltage rating than the BY126s originally fitted. If the diodes are not at fault, check the degaussing circuit resistor 7TH1 and the mains filter capacitor 7C19. Remove them for a positive check, though their appearance will often leave no doubt as to which one is at fault. If there is doubt, remove the resistor and shake it: if it rattles, fit a new one (there's science for you). In all probability however the mains fuse will be intact and the fuse that will have failed will be the one at the rear of the panel – the 1.6A HRC (high rupture capacity) d.c. fuse which is connected in the negative side of the supply. If it's open-circuit, carry out a general check on the BU326 chopper transistor and the associated diodes and thyristors.

HT Present

It's far more common to find that the 200V supply is present at the line output panel although the tube's heaters (fed from a winding on the line output transformer) show no signs of life. If the 27Ω wirewound anti-breathing resistor 5R11 is hot or the 800mA fuse 5FS1 (if fitted) has failed, the voltage at the body of the BU208A line output transistor, which is on the metal panel, will be low, suggesting that the transistor has gone short-circuit collector-to-emitter. Check for this. But don't replace it and reconnect the supply until further checks have been carried out. Possible causes of the death of the transistor could be failure of the $9.1nF$ tuning capacitor 5C14, which goes open-circuit, a shorted tripler (disconnect from the line output transformer) or a poor earth connection at pin 2 of 4Z2 on the centre, swing-down timebase panel. This is the long plug on the right side: if in doubt about the earth connection solder a long lead from pin 2 to the earthing on the line output panel.

BU208A Intact

It's more common to find that the full 200V is present at the body of the BU208A. In this event it's logical to check that the supply is also present at the collector of the driver transistor 5VT3. Under normal conditions the voltage here should be 125V: it's common to find the full 200V present, thus showing that the driver is inactive. In this event it's essential to appreciate the nature of the kick-start circuit used in these sets. The line oscillator is provided with an initial kick by 4C19 ($10\mu F$) on the right centre swing-down panel. With the set switched on this capacitor has 200V on one plate at all times: at the moment of switch on it charges via 4R49 and zener diode 4D14 on its negative side, the kick being applied via 4D13 to pin 3 of the TBA950 so that this i.c. gets going for long enough to enable the rest of the line timebase to come into operation – if it's in a condition to do so. The 12V regulator circuit should then start up and take over the supply to the TBA950 and the other low-voltage circuits. Shunting 4C19 with a wirewound resistor of some 5-10k Ω will maintain the supply to the TBA950 so that the trouble can be sorted out.

Short Cuts

That's the logical way to start fault tracing. In practice the writer employs a short cut once he's established that the 200V supply is present at the body of the BU208A. Release the top screws and unhinge the chassis outwards –

with the set switched off. With the meter switched to the low ohms range, check the EW modulator diodes 5D7 and 5D6 at the front end of the print. 5D7 should read about 20Ω both ways due to the circuit. 5D6 should read about 20Ω one way and 200Ω the other. One of the diodes could well be open-circuit or perhaps short-circuit. If these are o.k. move farther to the rear and check 5R8 which is in series with the BU208A's base. It should read 1Ω . It will often be found to read higher and when removed be found to be open-circuit. If 5R8 is in order, move over to the left side of the swing-down panel to check the value of 4R16 in the 12V regulator circuit. It should read 910Ω . If it's open-circuit the 12V regulator won't provide an output and the set will fail to get going after the initial kick start. These few quick checks will save a great deal of time.

Philips G11 Chassis

We've discussed the Pye/Philips G11 chassis in the past. There are now large numbers on the second-hand market however, so it will do no harm to outline the habits of this chassis briefly.

Most of these sets have two 3-15A anti-surge fuses mounted on the lower rear panel (some sets have only one fuse here). This is a convenient starting point in the event of a dead set. Are these fuses intact and is there 240V between them? If they have obviously blown one would assume that the fault is on the lower right power panel, and this would be so if the h.t. fuse F4037 on the upper left of the power panel is 1A as it's supposed to be. All too often however a higher rated fuse is found in this position so that if the fault is on the upper line timebase panel the excess current flows via the mains fuses which accordingly fail. So check this point first. If the h.t. fuse is rated at 1A, concentrate on the power supply panel: in particular, check the four diodes in the bridge rectifier circuit. Two of the diodes also form a bridge with the two thyristors which are far less often at fault. This "double bridge" arrangement means that the two diodes that form part of both bridges work harder than the other two: these will most often be found to be short-circuit, thus explaining the blown fuses.

If the fuses are intact and there's about 120V a.c. at the anode of each thyristor but no voltage at the h.t. fuse it's likely that trigger pulses are not being applied to the gates of the thyristors. There can be many reasons for this but a weak point is transistors T4085/6 in the excess beam current protection circuit. Since these two transistors are d.c. coupled and one is an npn device while the other is a pnp device it's impossible to check them by means of in-circuit ohmmeter readings: the pins from which a reading is required must be isolated. T4085 is the BC148 npn device and T4086 the BC158 pnp device.

A prime cause of trouble in these sets is poor connections – where the original soldered connections have become dry or burnt away, possibly due to arcing. Examine the panels very closely for signs of minor volcanic eruptions. Don't omit to look into the partially concealed corners of the panels.

HT but No Results

If there's h.t. at the 1A fuse but otherwise no results continue the search in the upper line timebase panel: this is a hotbed for dry-joints and close inspection really does pay dividends. The h.t. from the power panel does not go

direct to the line output stage. It's routed via the dynamic convergence correction panel (top centre) – through pins 3D7, 15A15, 15A16 and back to 3D6. This ensures that the h.t. is removed from the line output stage when the scan coils are disconnected. Check these contacts carefully if h.t. is not reaching 3D6 and pin 12 of the line output transformer. Check also the plug and socket connections that go off to the BU208A – these are at the top of the panel.

Remove this white plug in order to check the BU208A properly. The only readings to be obtained are from the base to the emitter and from the base to the collector (body). Switch to a high range to ensure that there's no reverse leakage.

If the h.t. supply is reaching the BU208A, check the supply to the driver transistor T3102 (BF355). There should be 127V at its collector. The supply comes via R3106 (820Ω) which often goes open-circuit.

HT Fuse Blown

If the 1A h.t. fuse has blown, check whether the BU208A (remove the plug to do this) or the BY223 EW modulator diode D3133 has gone short-circuit. The BY223 is the flat, black diode with the heatsink clip on it. There should be a low reading in one direction only. If it has gone short-circuit, the condition of the EW driver transistor T2150 (BD238) – upper left on heatsink – should also be checked. A shorted BY223 often signals the demise of the BD238. Failure to check this may result in the raster sides being curved in, i.e. no EW correction.

Access

To gain access to the components, fuses etc. check whether the original transit screws are still fitted, one at either side. Remove them and swing open the top clip. Lift the frame slightly and swing it open. The separate panels can be removed if necessary once the edge connectors have been pulled off (carefully, noting their positions and the holes for the locating pins). There are clips on the same side as the plugs: these allow the panel to be eased off the locating pegs and out of the slots at the outer edges.

We mentioned fuses. There's a row of them on the line timebase panel. Of these, the one most likely to fail is FS3143 (800mA) in the 37V supply to the field timebase.

Field Timebase

The TDA2600 field timebase chip is located on the left side upper panel. It's concealed beneath a Vee-shaped heatsink which is secured in position by two soldered tags above and below the staggered pins of the i.c. holder. Check the soldering to these pins in the event of erratic height variation, particularly the upper right pin 16 (output) – this is the most likely one to be found dry-jointed. If the holder is found to be discoloured at pin 16 when the heatsink is removed it must be replaced.

Apart from this pin, the holder can be responsible for erratic height, linearity etc., as can the TDA2600 itself. The chip has an appetite for fuses: the associated components can also be responsible for fuse blowing – amongst other things. The two 1,000μF scan coupling capacitors C2099/C2100 are particularly likely to short and blow the fuse. As they are shunted by a 470Ω resistor they should be isolated for checking.

next month in

TELEVISION

● THE BEOVISION 20AX CHASSIS

Eugene Trundle provides a run-down on common faults and guidance on circuit operation and setting up in the sections of the chassis unique to this design – mainly the remote control system, the power supply (a full-wave thyristor circuit) and the auto grey-scale correction system. These sets are not too difficult or expensive to sort out once their habits and operating principles are understood.

● VCR RECONDITIONING

Steve Bæeching decided to buy a batch of ex-rental VCRs (Sony and JVC/Ferguson) to do up during slack moments. A report on the sorts of troubles you can expect to encounter in second-hand machines.

● THE STRANGEST SET EVER

Our vintage TV series has looked at some odd sets in the past but the oddest so far must be the Murphy V134C/V136C. The line timebase used a pair of parallel-connected beam tetrodes in a self-oscillating arrangement while the field timebase employed the scan coils as a feedback transformer. The joys of TV in 1948!

● INITIAL VCR CHECKS

Is it safe to insert a tape in a faulty machine that's just come into the workshop? A few moments spent checking the tape deck and operating the machine without a tape can save a lot of time and expense. William Lockitt outlines a simple test procedure.

● COMMODORE 64 PROGRAM

This test pattern program provides a crosshatch then overlays colour bars on the upper part of the screen and a grey-scale wedge at the bottom. There's also switchable sound – a harmonious three-voice chord!

● APPROACHES TO TV SERVICING

S. Simon describes fault-finding problems with the ITT CVC20 chassis.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO (Name of Newsagent)

Please reserve/deliver the August issue of TELEVISION (£1.10), on sale July 17th, and continue every month until further notice.

NAME

ADDRESS

The Lid off Microcomputers

Part 3

Mike Phelan

In the first two parts of this series we took a fairly general look at the subject of home microcomputers. This time we'll take a closer look at a particular machine, the Amstrad CPC464. Its features include a 64K RAM, fairly powerful BASIC and a built-in cassette deck for saving/loading programs. Saving is recording on tape something that's in the computer's memory – usually a program, but it can also be other data, e.g. the screen part of the memory or a data file. Loading is playing back from the tape into the computer. The CPC464 comes with a monitor – either colour (RGB drive) or green screen monochrome (green instead of black and white to make viewing for long periods easier on the eyes).

To reduce the tangle of wires, the 5V supply for the computer/tape deck is obtained from the monitor. Thus there's a mains lead to the monitor and only two leads from the monitor to the computer – for RGB/sync and 5V. A modulator unit which contains a 5V supply and a PAL encoder is available to enable the computer to be used with a TV set that doesn't have RGB inputs (or 5V out!).

The layout inside the CPC464 is quite neat: apart from the cassette electronics, everything is on one large PCB. The keyboard is of the rubber membrane type, giving a nice feel and offering a degree of protection for the PCB against the various comestibles and liquids which descend in showers from the owners and their friends/relatives. Phelan's Law states that the amount of feeding electronic equipment receives is in proportion to the square of its intrinsic value.

A simple block diagram for the CPC464 is shown in Fig. 1. The CPU/microprocessor chip is a Z80A. The 16-bit address and 8-bit data buses are shown along the top. A simple reset generator consisting of an RC charging circuit and a couple of gates is used. The inverted reset line goes to the Z80A, the CRT controller i.c. and the

ULA i.c. (uncommitted logic array – a collection of gates etc. used for various purposes): the reset line goes to the PIO (parallel input/output) chip. The 64K RAM consists of eight i.c.s – one for each bit of the data word. At this point it's useful to take a look at the CPC464's memory map – see Fig. 2.

This shows the ROM divided into two blocks of 16K. The addresses used are also used by the RAM. So how does the CPU know whether an address refers to ROM or RAM? This brings us to the first function of the ULA, which starts life as just that – an assortment of gates and other logic units with no interconnections. The i.c. can be used for a variety of purposes therefore since the connections can be tailored to suit the job in hand. As far as home micros go the ULA is simply an assortment of bits of circuitry that don't fit in anywhere else – in early computers a dozen or so i.c.s would have been required to do the same work. One of the ULA's jobs is to produce control signals for the ROM and RAM. If the CPU is writing to a memory it must obviously be the RAM, but if it's reading information either the ROM or RAM could be the source of the required data. If the address is between #4000 and #BFFF it can't be the ROM. ULA produced control signals sort the matter out otherwise.

ROM Functions

When the computer is switched on the "bottom" section of ROM is started, clearing the memory etc. This then transfers control to the "top" BASIC interpreter section which awaits an input from the keyboard.

RAM Functions

Part of the RAM is used as working space by the operating system. The character set is also loaded into the

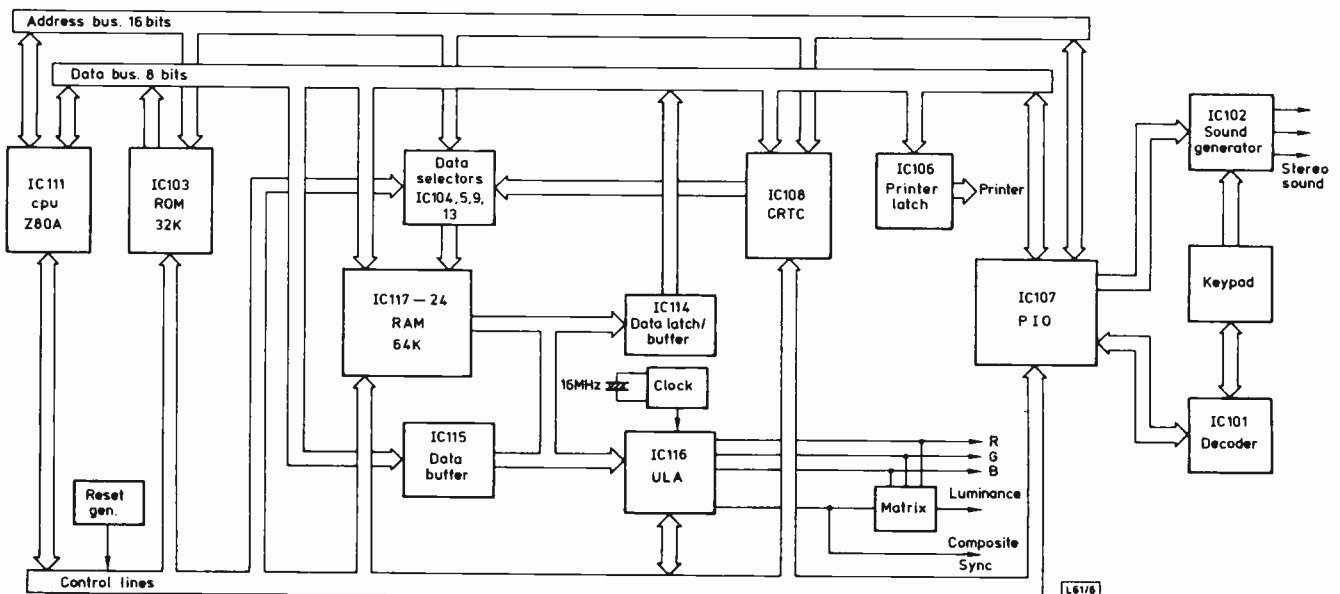


Fig. 1: Simple block diagram for the Amstrad CPC464.

RAM by the operating system. This is done so that we can redefine characters without in any way affecting the permanent character set. The screen memory is the "top" 16K section of the RAM and is arranged as follows. Each line of the screen consists of 80 bytes or 640 bits. This gives us 200 lines for 16K. Since each character consists of an 8 x 8 matrix it occupies eight lines, giving us 25 lines of characters. The top 80 bytes is the top line across the screen, the next 80 the ninth line and so on - this means that the top lines of all character rows are stored in a block, then the second lines, etc. Or, to put it another way, there's a 2K jump between adjacent lines.

The CPC464 has three screen modes. Mode one gives forty characters per line and four colours, mode zero twenty characters and sixteen colours, mode 2 eighty characters and two colours. The information stored in the screen section of the RAM is arranged to have what are called parallel attributes: this means that each byte contains information on what colour is to be displayed. Those who have had much to do with teletext will have met the alternative system where each screen memory byte contains either a character (ASCII) code or a control code that sets the foreground or background colour, graphics, double height etc. for the rest of the line. Some home micros use this system, which has the advantage of using less memory for the screen - 25 x 40 takes up 1K, not 16K. On the debit side, a control code (attribute) takes up one character square which can be occupied by nothing else - so you cannot, for example, have two adjacent letters of different colour. The parallel attribute system used in the CPC464 uses a lot more memory space but is much more flexible since each individual pixel colour can be determined by the user.

Each character consists of 8 x 8 pixels irrespective of mode. Since there are always 80 bytes or 640 bits per line of the screen the number of bits per pixel varies with the mode. In mode two there are 80 characters per line, so each character is one byte and each pixel is one bit which can be only zero or one - therefore only two colours can be used, one for foreground and one for background. In mode one the characters are wider, so each pixel is two bits giving four possible values or four colours. In mode zero with only twenty characters per line each pixel consists of four bits so we can have values from 0 to 15, giving sixteen colours. Table 1 summarises this.

From the software point of view there is no reason why a complete screen cannot be put in the portion of RAM from #4000 to #7FFF (it will be invisible of course) and then instantly (or nearly so) transferred to the top 16K. The effect from the user's point of view is that the whole display changes within a fraction of a second. This idea is made use of extensively in games software, where a

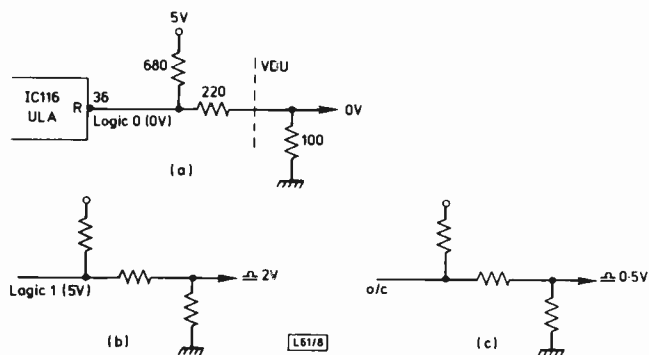


Fig. 3: Tri-state switching. (a) Logic zero output from the ULA provides 0V at the VDU; (b) logic one (5V) provides about 2V at the VDU; (c) the open-circuit state provides about 0.5V at the VDU.

complete screen can be loaded without being visible: a machine code program is then used to shift it to the visible screen section of the RAM.

Uses of the ULA

The ULA is driven by a 16MHz crystal clock. It divides this by four to provide a clock signal for the CPU. The clock signal also goes to the CRT controller IC108 whose job is to select the correct addresses in the RAM to provide screen information to the ULA, also to generate sync and blanking signals. The RAM is shared between the CRTC and CPU by means of the data selectors IC104, 5, 9 and 13 which switch the address bus between the CRTC and the CPU with a time ratio of 3:1 respectively. These i.c.s are controlled by signals from the ULA.

Next on the list of jobs for the ULA is the provision of a composite sync signal from the separate sync outputs provided by the CRTC. The ULA also contains a "palette latch" which is fed with information from the data bus to decide which colours to use - the CRTC decides which parts of the screen are to be of a particular colour. The software determines this. A total of 27 colours can be used, the number in use at any one time being restricted by the mode in use.

The palette latch output consists of a five bit code which is decoded within the ULA to give R, G and B outputs. How can we get 27 colours with only three bits? If each bit can be only zero or one we would have eight possible combinations. The answer lies in tri-state logic, in which each output can be one, zero or open-circuit. If you look at Fig. 3 you'll see how this works: each input to the colour monitor can be at one of three possible levels, i.e. there are $3^3 = 27$ possible combinations. Matrixing is used to produce a luminance signal to which the sync signal is added.

The ULA also stores the mode information until it's changed. It also generates the switching signals for RAM section selection: these are synchronised with the 4MHz clock. Each CPU instruction can take up to four clock cycles to complete. On the fourth, the CPU is halted by a

Table 1: CPC464 display modes

Mode	0	1	2
Bits per line	640	640	640
Characters per line	20	40	80
Colours available	16	4	2
Bits per pixel	4	2	1
Bytes per character	4	2	1

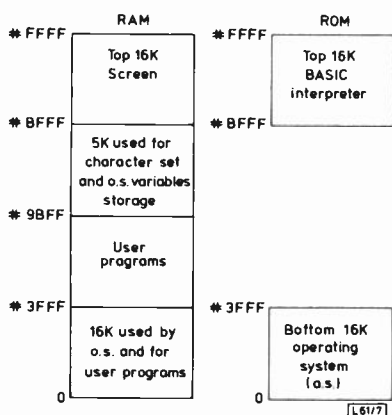


Fig. 2: RAM/ROM memory map for the CPC464.

signal from the ULA: the CRTIC is then connected to the RAM for one clock cycle.

Buffers

In an earlier instalment we mentioned that in computer parlance a buffer is a temporary storage area for small amounts of data. Computers also need to use the other sort of buffer with which we are more familiar – a stage to provide impedance conversion or isolation between its input and output. The various buses – data, address etc. – are connected to several parts of the circuit. It would not do for this to be done directly, otherwise if one bit went high or low the corresponding connections everywhere else would follow suit. To prevent this, tri-state buffers are used at the inputs and outputs: if a device is not in immediate use its ports are switched to the open-circuit state.

We also have buffer i.c.s that store one byte of information and read it out later. IC114 and IC115 are examples. The printer latch IC106 is another. Since a printer operates at a much slower speed than a computer

we must stop the computer after each byte has entered the latch. This is done by a “busy” signal from the printer. The CPU is restarted when each byte has been printed (one byte = one character). Larger computers have print buffers of typically 64K capacity: the computer ends up quite a long way in front!

VCR Microcomputer ICs

All this should have given you a better understanding of the operation of microcomputer i.c.s in video and TV equipment. The popular μ PD552 and μ PD553 used in JVC products are CPUs with their own ROM – the suffix number tells us which one. The ROM contains a complete program to operate the machine – and spends most of its time waiting for the user to press a key! These are 4-bit micros. The other main type is that used by Sharp and Toshiba, with a few parallel inputs for safety functions (these can be regarded as several levels of interrupt) and a serial input bus for key scans etc.

Next month we'll look at the PIO, sound and cassette electronics in the CPC464.

TV Fault Finding

GEC C2110 Series – Touch Tuning

Erratic channel changing and difficulty with changing stations are common problems with these sets. The usual solution is to change the neons then if necessary to change the high-value resistors. On one occasion this approach had little effect so we decided to strip down the touch tuner head assembly. When the aluminium escutcheon was removed we found that the centre carbon insert which connects the escutcheon to the rear panel via a spring had seized up and was not making contact due to an accumulation of dirt. We removed the insert and connected the escutcheon directly to the rear panel with 20 s.w.g. wire bent and trapped between the escutcheon and the front panel. This remedy has worked reliably on several of these sets. **J.K.P.**

Thorn 9800 Chassis

The fault was excessive width plus e.h.t. flashover after ten-fifteen minutes. A quick check revealed that the h.t. was high at about 210V instead of 181V. Further checks suggested that the fault lay in the ramp generator circuit. R724 (120k Ω) in the ramp generator transistor's base bias circuit turned out to be high in value. It's mounted on the little auxiliary panel on the power supply board. **D.R.**

ITT CVC1200 Chassis

I've been having a few problems with the power supply in this chassis. Here's an example of how to learn the hard way. The set was dead since a short-circuit BU508A chopper transistor had blown the mains fuse. In went a new BU508A, fuse and protective zener diode D702. Switch on: bang! – another BU508A short-circuit. Another BU508A was fitted, the other seven transistors in the power supply were replaced, a dummy load was connected instead of the line output stage and the set was powered from a variac set to 90V. The bulb (dummy load) lit but an arcing noise could be heard coming from

Reports from J. K. Potts, Mick Dutton, Philip Blundel, Eng. Tech., David Rainey, Malcolm Burrell and Stephen Howe

the set and a burning smell drifted across the workshop. A puff of smoke could be seen coming from the filter capacitor C701 which was arcing internally. So now the drill is to fit a new BU508A, D702 and C701, connect the dummy load and variac, then switch on with your left hand touching wood . . . **P.B.**

Philips CTX-E Chassis with VST

The report by P. Walsh in the May issue made interesting reading – it showed that I wasn't the only one having problems with these sets. When the mains bridge rectifier or the 4.7 Ω surge limiting resistor fails the TDA2541 i.f. i.c. sometimes goes short-circuit, open-circuiting its supply resistor and a coil in the earth line – L9157, which is not shown on the circuit diagram. With this coil open-circuit the supplies to the tuner and VST module go haywire, causing them dire distress. The VST microcomputer i.c. often dies, but when you've replaced it you could well find you've still got problems. Such as:

No green tuning line – check D5852.

Will not stop tuning when a station is found. If the tuning speed slows down when a station is found, suspect the LM339 or an incorrect a.f.c. signal from the main panel. If the tuning speed doesn't slow down, check that the mute/transmission ident signal at pin 2 of VST module plug V11 goes to 0V on station. If it does, the microcomputer isn't reading the signal. Suspect transistor T7856 and diodes D6840, D6841. The mute signal is generated in the line oscillator i.c. **P.B.**

Sharp C1491/Rediffusion Mk V

One of these colour portables came in with the complaint that the picture went off when the set warmed up. Sure enough when we tried it the set worked o.k. for about twenty seconds then the raster disappeared and a loud ticking noise came from the power supply. When the back

was removed it was clear from the way in which all the semiconductor devices in the power supply had been changed for European types that an unknown engineer had had a long and meaningful relationship with this part of the set. Now the switch-mode power supply and the line output stage work together in this set, and if the line timebase doesn't start up that ticking noise is what you get. A scope check showed that the line oscillator stopped when the fault occurred, so attention was turned to the protection circuit which acts to shut the oscillator down. Sure enough pin 9 of the i.c. in which the line oscillator lives (an IX0065CE) went high just before the oscillator stopped. The protection circuit monitors the beam current, the amplitude of the flyback pulses and the conditions in the field output stage. It transpired that zener diode ZD602 in the beam current sensing circuit was short-circuit.

P.B.

Grundig 2210

Last August I mentioned a tuning fault on the Grundig 2210 (not 2222 – sorry). I've since learnt that the tuning system is very prone to board cracking. The solution is to replace the board containing the carbon tracks. It's quite easy. Unsolder the lugs and slide the old one out. Move the contact wipers to one end, raise them with a strip of paper, then slip in the new board. Don't forget to remove the strip of paper.

M.B.

Rank T20 Chassis

This set was described as dead though a loud whistle came from the power supply. The h.t. was about 50V instead of 200V so I dived for the line output transistor which turned out to be faultless. Only then did I notice the tell-tale burn mark around plug 5Z1. Replacing this together with its socket provided a cure. The moral is, and always has been – make a quick visual inspection first.

M.B.

Binatone 01/9860

This set came in with the description "smoking". R512 which supplies the line driver stage was a little discoloured but not open-circuit. The line output transistor TR503 was short-circuit. Replacing this failed to produce any appreciable e.h.t. and I was beginning to have expensive thoughts. I then found that the boost reservoir capacitor C512 (220 μ F, 16V) was hot. It turned out to be leaky, a replacement restoring normal operation. I think this could become a common problem and since it upsets the operation of the line output stage it's always worth a check. Incidentally the line output transistor is type 2SC508 or 2SC2233: a BU508 (expensive) or a BD535 can be used.

M.B.

Grundig 5012

We got caught out nicely the other day with this set. It had two problems. First there was no blue tilt or parabola control. Simple this – C725 (0.22 μ F) had gone open-circuit. I've come across this one on several occasions. The second problem was excessive width. The width control worked, but at minimum the picture was still several inches too wide. We spent a lot of time checking the width control circuit – as everything seemed to be running cool we thought we were looking for a control circuit fault. Eventually we turned our attention to the scan circuit. The scan-correction capacitor was an 0.68 μ F

metal type. We thought this couldn't possibly be faulty. Wrong: a replacement cured the problem.

M.D.

Thorn 9800 Chassis

This set had no blue. There was no blue first anode voltage due to the 100k Ω series resistor R612 being open-circuit. A replacement got very warm however and we found that the associated spark gap was leaky.

M.D.

Philips TX Chassis

A quickie: the fault was no sync, due to R370 (820k Ω) which provides the sync separator transistor TS370 with base bias having gone open-circuit.

M.D.

Philips KT3 Chassis

The complaint with a Philips colour portable fitted with this chassis was no picture when warm. We ran the set up and found that after a few minutes the screen went blank. Turning up the brightness control produced a very faint picture. We checked the voltages around the decoder panel, which was of the older two-chip type, and found that with the contrast control at maximum the voltage at pin 16 of the TDA2560Q chrominance/luminance amplifier i.c. was only 0.7V instead of something like 4V. C3205 (0.022 μ F) which decouples this pin turned out to be leaky.

M.D.

Rediffusion Mk III and Mk V

Now that Rediffusion has been taken over by Granada we're finding that calls to service Rediffusion sets are beginning to come in. One of the first sets to come our way was fitted with a Sharp chassis (Rediffusion Mk. V chassis). The problem was field collapse. As we didn't have a circuit we wasted a lot of time trying to work out what did what.

Eventually we found that R513 (1.2k Ω) was open-circuit: come to think of it this was the subject of a Test Case item not so long since.

Another set was fitted with the Mk. III chassis. This one was dead. The fuse had blown and as we could find no obvious shorts we fitted a replacement and switched on. The set started to come on then tripped. We removed the power supply panel and found a dry-joint on the regulating thyristor 6THY2, but resoldering this failed to stop the tripping. Now regulation with this type of circuit is a sort of line output stage damping action, and for this purpose 6THY2 has to be fired – if it isn't fired excessive voltages build up and the trip operates. 6THY2 wasn't receiving trigger pulses because 6R17 (68 Ω) was open-circuit.

A couple of weeks later we had another of these sets tripping. This time the trouble was due to a faulty tripler.

M.D.

Thorn TX10 Chassis

The set would start up at switch on but after a few seconds it would shut down again. The set didn't go through the normal shut down/start up sequence: it simply remained dead after its first shut down. The fault was traced to the BC547 regulator transistor TR801 which provides the 12V supply for the chopper control i.c. It had gone short-circuit. In addition the associated 12V reference zener diode D802 was leaky.

S.H.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

15580H	2.48	2SA884	2.15	2SC620	1.46	AC138	0.09	BA318	0.09	BC463	0.64	BD538	0.67	BF479	0.61	BU111Y	4.16
15585R	2.48	2SA940	1.81	2SC643A	1.54	AC141	0.29	BA328 (IC)	4.77	BC464	0.64	BD544B	0.83	BF480	0.60	BU124	1.38
16029	1.24	2SA940-2	2.14	2SC668	0.67	AC151	0.28	BA333 (IC)	1.37	BC465	0.64	BD580	1.17	BF491	0.49	BU125	2.48
16181	1.04	2SA951	1.26	2SC673	1.23	AC153	0.34	BA401 (IC)	0.64	BC477	0.32	BD590	1.17	BF495	0.64	BU126	0.90
16182	1.04	2SA966	0.54	2SC681	1.40	AC176	0.30	BA5102A (IC)	5.97	BC478	0.32	BD598	1.25	BF506	0.43	BU134S	4.57
16334	0.51	2SB325	3.87	2SC684	4.65	AC179	0.28	BA511 (IC)	2.18	BC479	0.32	BD677	0.53	BF509	0.41	BU204	1.58
16335	0.80	2SB375	3.87	2SC685	0.00	AC183	0.72	BA521 (IC)	2.02	BC532	0.26	BD680	0.76	BF523	0.20	BU205	1.08
16446	0.98	2SB400	0.40	2SC685A	2.89	AC187	0.39	BA526 (IC)	7.98	BC546	0.17	BD681	1.48	BF594	0.27	BU206	1.27
16600	1.38	2SB407	3.24	2SC693	0.63	AC187K	0.43	BA532 (IC)	1.83	BC547	0.10	BD695	2.30	BF595	0.27	BU207	1.65
16799	2.62	2SB411	3.30	2SC710	0.69	AC188K	0.43	BA536 (IC)	3.44	BC548	0.09	BD696	2.47	BF596	0.18	BU208	1.27
16801	0.54	2SB449B	6.60	2SC711A	0.50	AC194K	0.65	BA6209 (IC)	4.71	BC549	0.10	BD697	3.60	BF597	0.27	BU20802	1.12
16802	1.14	2SB511	1.63	2SC717	1.14	AC76003N	2.72	BA6304A (IC)	2.92	BC550	0.40	BD698	1.85	BF617	1.05	BU208A	1.97
16803	5.30	2SB54	1.39	2SC734	1.43	AD140	1.06	BA843 (IC)	3.96	BC556	0.16	BD699	3.49	BF618	1.05	BU208D	1.43
16905	0.86	2SB546	3.64	2SC735	1.16	AD145	1.60	BAV18	0.21	BC557	0.10	BD700	3.70	BF694	0.22	BU209	1.93
17052	5.61	2SB56	2.23	2SC782	2.47	AD149	0.90	BAV19	0.11	BC558	0.10	BD701	3.48	BF757	0.58	BU229	2.39
17074	6.60	2SB618A	1.83	2SC783	3.98	AD162	0.45	BAV20	0.11	BC559	0.10	BD702	3.70	BF758	0.68	BU312	2.38
17088	4.80	2SB631	3.25	2SC806	11.29	AD262	1.05	BAV21	0.34	BC560C	0.10	BD709	1.12	BF759	0.64	BU326	2.00
17089	5.35	2SB643	0.40	2SC814	1.39	AF114	2.47	BAX12	0.11	BC635	0.20	BD710	0.80	BF760	0.65	BU326S	2.20
17127	5.51	2SB669	3.67	2SC828	0.28	AF115	1.24	BAX13	0.11	BC636	0.20	BD807	0.34	BF762	0.34	BU406	1.35
17376	1.58	2SB681	3.96	2SC867A	3.04	AF117	0.75	BAX16	0.11	BC637	0.24	BD809	0.75	BF870	0.30	BU407	0.82
17523	1.32	2SB695	1.98	2SC876	0.96	AF118	1.20	BB119	0.17	BC638	0.20	BD810	0.68	BF871	1.81	BU407D	1.29
17524	1.32	2SB75	1.04	2SC926A	1.42	AF127	0.50	BC107	0.13	BC639	0.20	BD879	0.71	BF900	0.83	BU412	4.80
1N4001	0.06	2SC8819	0.87	2SC930	0.54	AF139	0.53	BC107A	0.11	BC640	0.24	BD880	0.79	BF907	0.79	BU426	1.90
1N4002	0.06	2SC8861	0.85	2SC935	4.13	AF178	1.45	BC107B	0.11	BC879	0.31	BD895	2.18	BF959	2.48	BU426A	1.67
1N4003	0.06	2SC1050	4.03	2SC937	3.58	AF179	0.55	BC108B	0.15	BC880	0.31	BD899	2.48	BF960	1.90	BU500	1.78
1N4004	0.04	2SC1061	1.26	2SC940	4.68	AF180	0.68	BC109B	0.15	BCX32	0.42	BD901	0.70	BF970	0.61	BU508A	1.89
1N4005	0.08	2SC1096	1.16	2SC940Q	4.68	AF181	0.53	BC113	0.14	BCX33	0.27	BD902	0.61	BF972	0.44	BU526	2.02
1N4006	0.08	2SC1104	2.60	2SC982	0.70	AF182	0.55	BC116A	0.25	BCX34	0.40	BDV64B	1.26	BF952	0.50	BU688D	1.57
1N4007	0.07	2SC1106	4.54	2SD1051	0.75	AF186	0.53	BC126	0.20	BCX37	0.67	BDV65B	1.26	BF962	0.50	BU705	3.81
1N4148	0.04	2SC1114	6.75	2SD1128	2.25	AF239	0.53	BC132	0.14	BCY70	0.30	BDX32	1.75	BF979	0.29	BU800	1.79
1N4448	0.05	2SC1124	1.26	2SD1138	0.86	AF279	0.88	BC135	0.14	BCY71	0.21	BDX53	0.68	BF981	0.50	BU806	1.49
1N5401	0.14	2SC1128	0.00	2SD1265	0.76	AL100	4.03	BC137	0.18	BCY72	0.20	BDX53A	4.05	BF986	1.08	BU806D	1.49
1N5402	0.15	2SC1129	0.34	2SD1453	0.75	AL103	2.68	BC138	0.34	BD115	0.36	BDX53B	3.35	BF989	0.43	BU807	1.40
1N5403	0.16	2SC1131	0.50	2SD198	3.87	AL113	1.36	BC139	0.28	BD116	0.30	BDX54B	2.61	BFT41	0.30	BU826A	3.94
1N5404	0.15	2SC1151A	4.72	2SD234	0.47	AN155	1.89	BC141	0.31	BD124	1.31	BDX62A	1.96	BFT42	0.43	BU846	1.54
1N5408	0.87	2SC1152	4.68	2SD235	0.60	AN206	2.58	BC142	0.34	BD124P+KIT	0.69	BDX63A	1.96	BFT43	0.43	BU846A	1.24
1N914	0.04	2SC1157	4.54	2SD257	2.94	AN208	3.55	BC147	0.11	BD131	0.42	BDX64A	2.61	BF784	0.40	BUW81A	3.06
IS1555	0.20	2SC1162	1.05	2SD288	0.00	AN210	2.28	BC147A	0.12	BD132	0.42	BDX65A	2.61	BFV10	0.60	BUW84	1.39
IS44	0.09	2SC1172 TR	2.22	2SD291	2.94	AN214	2.26	BC148	0.13	BD133	0.53	BDX76	0.59	BFX29	0.34	BUX84	1.00
IS5012A	0.81	2SC1172Y	2.20	2SD292	2.59	AN214Q	1.86	BC148B	0.13	BD135	0.36	BDY720	1.21	BFX30	0.65	BUY69A	2.04
IS921	0.10	2SC1195	3.02	2SD313	2.59	AN231	14.43	BC148C	0.11	BD136	0.36	BDY81	1.18	BFX85	0.39	BY127	0.11
IS689	2.06	2SC1213	0.89	2SD315	2.94	AN234	5.09	BC149	0.11	BD137	0.46	BDY81	1.18	BFX87	0.59	BY133	0.13
IS751	2.06	2SC1226	1.46	2SD325D	0.91	AN236	3.33	BC149B	0.13	BD138	0.36	BDY81	1.18	BFX87	0.39	BY127	0.11
2N1302	0.27	2SC1306	1.98	2SD348	16.13	2SD348	5.48	BC153	0.14	BD139	0.40	BF115	0.40	BFX87	0.59	BY133	0.13
2N1303	0.38	2SC1307 TR	1.98	2SD350	5.20	AN239	4.35	BC154	0.14	BD140	0.34	BF117	0.67	BFX88	0.44	BY176	1.52
2N1248	6.27	2SC1316	4.10	2SD350A	2.29	AN240P	1.72	BC157	0.14	BD144	1.43	BF121	0.25	BFY50	0.27	BY182	1.05
2N2218	0.42	2SC1317	0.87	2SD353 TRA	6.12	AN241	1.71	BC158	0.10	BD150	1.19	BF123	0.13	BFY52	0.27	BY184	0.47
2N2219A	0.40	2SC1364	0.49	2SD389	2.41	AN245	4.49	BC159	0.16	BD157	0.67	BF127	0.13	BFY90	0.61	BY187	0.77
2N2222	0.38	2SC1383	1.20	2SD401	3.55	AN247P	3.95	BC161	0.28	BD159	0.53	BF137	0.13	BLY49	2.20	BY189	1.76
2N2646	0.80	2SC1391	2.45	2SD551	2.42	AN252	2.57	BC167	0.36	BD160	1.60	BF152	0.31	BR100	0.22	BY198	1.62
2N2904	0.36	2SC1396	0.84	2SD588A	1.99	AN253	2.97	BC168	0.36	BD163	0.71	BF153	0.58	BR101	0.70	BY201/2	1.50
2N2905	0.43	2SC1410	2.39	2SD600	3.25	AN262	1.96	BC170	0.16	BD165	0.82	BF154	0.26	BR103	0.66	BY203/20	0.20
2N2906	0.38	2SC1413	3.55	2SD621	12.67	AN272	7.92	BC171	0.11	BD166	0.42	BF157	0.33	BR303	1.26	BY206	0.17
2N2926 GRN	0.15	2SC1413A	5.26	2SD636	0.25	AN281	5.45	BC172	0.10	BD168	0.73	BF158	0.18	BR88B	0.64	BY207	0.22
2N2926 RED	0.19	2SC1475	0.37	2SD657	2.80	AN295	5.52	BC172B	0.27	BD175	0.43	BF159	0.18	BRC-M-300	0.97	BY208	0.46
2N3053	0.27	2SC1514	1.32	2SD669	3.67	AN301	5.55	BC173	0.17	BD177	0.43	BF160	0.31	BRC116	0.67	BY210-400	0.18
2N3054	0.99	2SC1573Q	1.25	2SD679	3.35	AN302	3.99	BC174B	0.27	BD179	0.48	BF167	0.38	BRC1330	1.76	BY210-600	0.27
2N3055	0.61	2SC1578	8.74	2SD731	2.11	AN303	4.39	BC177	0.20	BD181	0.59	BF173	0.34	BRC300	2.01	BY210-800	0.34
2N3055H	0.85	2SC1617	3.89	2SD787E	0.58	AN306	8.88	BC178	0.26	BD182	0.99	BF177	0.55	BRC4443	1.02	BY223	0.85
2N3442	1.16	2SC1670	3.13	2SD811	5.54	AN313	3.41	BC179	0.26	BD183	0.99	BF178	0.40	BRC4444	1.02	BY224-400	0.99
2N3702	0.14	2SC1678	1.98	2SD823	1.98	AN315	2.46	BC182	0.11	BD184	1.21	BF179	0.36	BRC5296	0.77	BY225-100	1.13
2N3703	0.14	2SC1810	1.70	2SD837	1.07	AN316	5.53	BC182	0.09	BD187	0.53	BF180	0.36	BRC6109	0.83	BY226	0.25
2N3704	0.14	2SC1815	0.66	2SD856	6.61	AN318	6.20	BC182B	0.26	BD189	0.39	BF181	0.32	BR282	1.08	BY227	0.49
2N3705	0.14	2SC1829	2.22	2SD869	7.17	AN320	5.47	BC182L									

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

CD4049	0.56	HM9015	3.24	M58478P	6.75	OA90	0.08	SAF1039	3.36	SN76131	1.92	T6059	1.16	TBA120AS	1.24	TDA1104	6.55
CD4050	0.58	HT4207	17.16	MA06	1.07	QA91	0.09	SAS5010	0.39	SN76226DN	1.98	T8001V	1.20	TBA120S	1.05	TDA1151	1.17
CD4052	0.75	ITT2003	0.22	MA1457	2.72	QA95	0.09	SAS560	2.52	SN76227N	0.75	T9003V	0.95	TBA120SB	0.95	TDA1170	2.37
CD4053	0.80	KL174YP	3.25	MA8001	0.82	OC28	2.38	SAS560S	1.65	SN76228N	3.27	T9005V	2.38	TBA120T	1.05	TDA1170S	2.04
CD4069	0.24	KA2101	2.65	MB3705	1.79	OC29	2.15	SAS560T	3.14	SN76231	2.55	T9007V	2.00	TBA120U	2.03	TDA1180	2.90
CD4081	0.29	KC581C	6.32	MB3712	1.85	OC35	2.06	SAS570	1.78	SN76242	5.23	T9008V	1.29	TBA1440	2.50	TDA1190	2.11
CD4093	0.72	KC582C	3.57	MB3713	1.69	OC36	1.28	SAS570S	2.75	SN76243	5.23	T9010V	0.96	TBA1440G	3.29	TDA1200	2.48
CD4511	1.10	KC583C	5.94	MB3730	3.49	OC44	0.36	SAS580	2.61	SN76222	2.77	T9011V	1.27	TBA240A	7.99	TDA120A	1.43
CD4516	1.17	KIV15B	5.74	MC13002	6.22	OC45	0.18	SAS580	2.85	SN76230	2.17	T9013V	1.96	TBA395	1.10	TDA1220	1.95
CP5521	17.83	L129V	0.25	MC1303P	2.16	OC72	0.44	SAS5800	2.89	SN76230	3.06	T9014V	1.76	TBA395Q	1.10	TDA1230	3.23
CX034	11.83	L200CV	1.69	MC1307P	1.92	OC75	0.75	SAS590	2.86	SN76236	2.90	T9016	1.02	TBA396	0.80	TDA1235	3.88
CX095D	3.14	LA11111AP	0.88	MC1310P	1.30	ON188	1.44	SAS590	2.55	SN76510N	1.05	T9019V	1.96	TBA400	2.39	TDA1236	4.30
CX104	9.64	LA1201	1.02	MC1327P	1.33	ON236	1.06	SAS660	2.97	SN76320P	1.57	T9034V	1.39	TBA440C	5.75	TDA1270	3.74
CX108	8.16	LA1210	1.38	MC1330P	1.69	OT112	1.08	SAS6600	1.33	SN76322N	0.91	T9035V	1.28	TBA440P	2.45	TDA1270A	1.50
CX109	7.86	LA1320	2.87	MC1349P	0.81	OT121	1.32	SAS660S	1.33	SN76323N	1.65	T9038V	9.42	TBA480	1.57	TDA1270	1.82
CX121	11.83	LA1352	1.54	MC1356P	1.21	PD144	2.24	SAS6610	1.33	SN76540N	1.98	T9051	7.71	TBA480Q	1.30	TDA1330	1.76
CX130	5.55	LA1357N	6.49	MC1351P	1.33	PT2014	3.04	SAS670	3.96	SN76544	2.89	T9053V	1.40	TBA500P	1.67	TDA1365	6.99
CX131	11.83	LA1363	6.21	MC1352P	1.12	PT5006	2.08	SAS6700	1.33	SN76545	4.87	T9054V	1.19	TBA510	1.38	TDA1412	1.05
CX134	11.04	LA1364	3.02	MC1357P	2.15	PT6042	1.79	SAS670S	1.79	SN76546	1.65	T9057V	0.70	TBA520	1.64	TDA1420	1.52
CX136	11.49	LA1365J	3.44	MC1358P	1.30	PT6045	6.12	SN76549	1.33	SN76549	2.59	T9063V	3.24	TBA520Q	1.88	TDA1470	2.90
CX137	11.83	LA1378	6.52	MC14001	2.40	R1038	2.19	SAS6800	2.53	SN76550	0.37	T9064	2.02	TBA530	1.30	TDA1512	2.89
CX139	11.83	LA1385	1.87	MC14011	0.26	R1039	2.19	SAS6810	1.43	SN76551	1.49	TA16420	5.98	TBA530Q	1.30	TDA1670	4.48
CX157	4.84	LA1387	7.60	MC14013	0.41	R2008B	1.93	SBA750	1.61	SN76570	3.08	TA16421	1.98	TBA540	1.15	TDA1770	2.90
CX158	4.10	LA3155	1.25	MC14016CP	0.84	R2009	1.38	SC9488P	2.09	SN76620	1.21	TA5814	5.49	TBA540Q	1.15	TDA1900	1.76
CX170	7.62	LA3300	1.54	MC14025	0.50	R2001B	1.33	SC9503	1.65	SN76620N	0.00	TAE6002	4.20	TBA550	5.25	TDA1908	3.20
CX177	6.75	LA3301	1.28	MC14049UBC	0.58	R2029	1.33	SC9511P	2.09	SN76611	2.59	TA7020P	4.80	TBA550Q	5.25	TDA1940	1.95
CX187	6.26	LA3350	1.43	MC1438R	1.05	R2030	1.33	SC9557	1.33	SN76620	2.59	TA7027	4.80	TBA560C	1.40	TDA1950	4.80
CX2000A	5.74	LA3361	1.23	MC14493P	2.82	R2257	2.38	SDA2112/2	1.02	SN76622	1.65	TA7050	1.74	TBA560CQ	1.60	TDA2000	0.91
CX506	9.33	LA4030P	4.20	MC14497	14.99	R2265	1.49	SD264A	5.26	SN76623	0.69	TA7051	1.74	TBA570	1.60	TDA2003	1.20
CX507	7.62	LA4031P	3.20	MC14510BAL	4.43	R2305	1.18	SD608	5.26	SN76630	2.55	TA7060AP	0.71	TBA570	1.71	TDA2004	2.25
CX758	7.62	LA4032P	1.92	MC14511BCP	1.10	R2306	1.36	SG613	8.75	SN76640	4.24	TA7061AP	1.27	TBA625A	2.17	TDA2005	5.08
D1683	2.59	LA4050P	1.57	MC1455	0.28	R2322	0.59	SG629	8.27	SN76650N	2.05	TA7069	3.13	TBA625B	2.17	TDA2006	1.55
DEC2	2.20	LA4051P	1.79	MC14556BCP	3.47	R2323	0.76	SG6533	10.31	SN76651	1.49	TA7070P	1.68	TBA625C	2.17	TDA2010	1.65
E1222	0.40	LA4100	1.25	MC1712	3.88	R2348	2.01	SI-1020H	10.89	SN76650N	2.48	TA7071	3.69	TBA641A12	4.13	TDA2020	2.77
E5024	0.28	LA4101	1.30	MC7274CP	3.49	R2354A	2.01	SI-1125HD	13.86	SN76655A	1.49	TA7072P	2.57	TBA641B11	3.03	TDA2030	1.99
E5386	0.25	LA4102	2.81	MC7818C	2.18	R2354B	2.01	SI1125H	13.86	SN76656B	1.41	TA7073AP	5.86	TBA641B1X1	1.79	TDA2140	1.59
E5529	0.25	LA4112	4.83	MC7824CP	4.68	R2441	1.36	SI-1130H	6.33	SN76705N	1.34	TA7073P	5.86	TBA651	1.76	TDA2150	1.60
E8021	1.29	LA4125	2.13	MC78M12	0.83	R2443	0.88	SKE102	1.20	SN76707	4.29	TA7074P	1.98	TBA673	2.45	TDA2151	6.23
E9003	0.46	LA4138 IC	3.39	MC78M24	0.94	R2461	1.50	SKE2F 1/04	1.39	SN76708	4.86	TA7076P	7.50	TBA700Q	2.00	TDA2160	4.01
E9005	0.50	LA4140	0.88	MC78M101	0.67	R2477	1.02	SKE2G 2/04	0.95	SN76709	5.12	TA7089M	1.56	TA720	2.50	TDA2161	1.85
ESM310BP	4.15	LA4192	3.65	MCR106/5	1.57	R2501	1.28	SKE2G 3/04	1.05	SN76730	4.66	TA7089P	1.50	TBA730	2.14	TDA2190	
ESM432C	4.60	LA4220	1.62	MCR220/7	2.28	R2540	1.98	SKE4F 1/02	1.39	SN76810N	0.60	TA7092P	6.84	TBA750Q	2.90	TDA2510	2.47
ESM532C	4.60	LA4400	2.22	ME0402	0.17	R2540X	3.30	SKE4F 2/06	0.73	SN76920N	2.90	TA7102P	5.88	TBA760	1.71	TDA2520	2.37
ESM632C	4.60	LA4420	1.72	ME0404	0.26	R2615	0.67	SKE4F 1/06	0.85	SN94041	5.54	TA7108P	1.61	TBA780	1.85	TDA2521	3.30
ESM732C	4.60	LA4422	1.72	ME0404/2	0.47	RC4195NB	2.16	SKE4F 2/08	0.86	SN94042	4.35	TA7109	3.71	TBA800	1.08	TDA2522	1.50
ML232B	2.92	LA4430	1.47	ME0411	0.26	RC416029	2.01	SKE4F 2/10	1.24	SP5422	1.83	TA7120P	0.64	TBA810AS	1.00	TDA2523	3.03
ETTR6016	3.33	LA4440	4.95	ME0412	0.24	RC416083	5.30	SKE4G 2/02	0.96	SP8385	0.55	TA7122P/B	0.92	TBA810S	1.61	TDA2524	4.50
FND500	5.78	LA4460	2.32	ME4102	0.50	RC416334	1.02	SKE5F 3/10	1.60	SPS5384	1.95	TA7124P	2.34	TBA810T	1.50	TDA2525	3.90
FT3055	1.16	LA4461	2.95	ME545B	10.02	RC416335	1.36	SKS110	2.15	ST1702L	0.99	TA7130P	1.27	TBA820M	0.74	TDA2530	2.50
GC374	1.33	LA5112N	2.56	ME8002	0.26	RC416800	1.38	SL1310	3.14	STA401	6.76	TA7136AP	1.27	TBA890	1.85	TDA2532	2.70
GF758	0.84	LA7020	7.33	ME5102	0.28	RC416799	2.38	SL1327E	1.33	STA441C	2.75	TA7137P	0.98	TBA900	2.48	TDA2533	2.10
GF759	1.13	LA7025	8.05	ME8001	0.29	RC416801	0.95	SL1430	1.39	STK0029	5.54	TA7141AP	3.87	TBA920	1.65	TDA2540	2.35
GF761	1.20	LA7027	9.35	MED411	0.75	RC416802	1.08	SL1430T	2.31	STK0039	5.35	TA7146P	4.23	TBA920Q	2.31	TDA2541	4.84
GH3F	1.82	LA7800	2.34	MJ2501	3.30	RC417028	2.48	SL1432	2.25	STK0050	7.67	TA7148P	1.67	TBA940	1.87	TDA2545Q	2.98
HA11211	2.53	LA7801	4.15	MJ2955	0.98	RC417074	6.60	SL414	3.69	STK0059	7.13	TA7149P	3.26	TBA950	1.55	TDA2560	3.10
HA11215	5.06	LB1274	1.49	MJ3000	2.37	RC417376	1.58	SL422A	3.44	STK0080	9.16	TA7152P	1.52	TBA970	1.79	TDA2571A	2.17
HA11223W	0.00	LC4011B	2.82	MJ3001	1.43	RC417523	0.83	SL437	7.43	STK011	3.96	TA7161P	6.23	TBA970Q	3.28	TDA2571AQ	3.60
HA11225	4.29	LC7800	7.89	MJ3028	2.00	RC420620	2.00	SL439	2.48	STK013	7.75	TA7162P	2.59	TBA990	1.82	TDA2575A	0.50
HA11226	8.71	LD3120	1.13	MJ481	1.53	RC6A08587	4.95	SL471	3.28	STK014	8.84	TA7169	9.54	TBA2031	1.52	TDA2576A	3.96
HA11229	2.88	LM1011N IC	3.46	MJ802	0.50	RGP10	5.45	SL480	3.10	STK015	7.75	TA7171P	2.79	TC4201	2.47	TDA2577	2.95
HA11235	2.48	LM1017N IC	3.41	MJE2955	1.89	RT402	1.58	SL490	2.37	STK016	6.91	TA7172P	1.41	TC4053BP	4.34	TDA2581	2.69
HA1124	5.25	LM1101	3.29	MJE3055	1.65	RT905A	2.38	SL901B	8.32	STK022	5.25	TA7176P	2.48	TC4069	1.52	TDA2590	2.50
HA11244	2.82	LM1111	4.94	MJE320	0.49	SO280	2.14	SL917B	11.96	STK025	8.27	TA7193AP	6.67	TC9002BP	10.38	TDA2591	2.50
HA1125	4.29	LM1130P/N	1.65	MJE520	0.49	SO281	2.14	SL918A	6.32	STK029	12.37	TA7193P	4.95	TC1150	1.79	TDA2591Q	0.83
HA11251	4.47	LM1310P/N	1.38	MJ520	0.99	S1239	4.74	SN16848	11.07	STK054	7.13	TA7201P	2.71	TC160B	1.79	TDA2593	3.47
HA1138	5.03	ML2208 IC	5.94	ML231	2.15	S15H	1.27	SN16861AN0	4.95	STK070	22.31	TA7202P	2.47	TC2700	2.71	TDA2594	2.08
HA11414	5.65	ML2877	4.53	ML232B	2.51	S175	31.48	SN16861N-07	2.72	STK077	7.67	TA7203P	2.18	TC2705	2.15	TDA2600	5.00
HA1144	7.52	ML3085N	0.85	ML237B	5.77	S2062D	2.07	SN16862AN	2.98	STK078	8.52	TA7204P	2.16	TC2705Q	2.16	TDA2610	2.79
HA1156	1.16	ML317CKC	1.38	ML741CS	0.58	S2900	5.78	SN16890N	3.63	STK082	11.86	TA7205	1.38	TC290A	2.39	T	

VCR Clinic

*Reports from Steve Beeching, T. Eng.,
Derek Snelling, B. Ross, John Coombes
and Philip Blundell, Eng. Tech.*

Sharp VC381

This machine would play back in colour but wouldn't record in colour. Everything was checked – a.f.c., 4.35572MHz carrier, there was even a down-converted output to the record drive stages. The level of the 625kHz signal seemed to be low however, though there were no levels shown in the service manual to confirm this. So the i.c. was changed – to no avail. At this point Andy made coffee and was asked to prohibit all disturbances whilst intense concentration took place. The conclusion reached was that the 5.06MHz output from filter FL503 was very low. Although a large difference does occur between the input and output from this filter, in this case the output was very, very low. The filter was suspected with some trepidation, since filters don't usually fail – unless it's in a Sharp VC381 that is! So beware: it's now a known stock fault. Just as a point of interest, the down-converted colour signal level at pin 1 of the colour i.c. should be 500mV p-p on colour bars. The carrier signal at pin 28 should also be around 500mV. S.B.

Mitsubishi HS300

The fault on this machine could be termed a video nasty. It was a classic symptom to put the blood pressure up a few points. The machine would run for a couple of seconds then stop – a system control fault. On closer inspection we noticed that the playback picture broke up into noise bars just before the machine stopped. This indicated that the r.f. switching pulse (flip-flop to you) was breaking up, which was confirmed when the trusty scope was connected to TP4C. The signal from the drum pick-up coil was correct at IC401 (AN6340) and no other problems were evident, so the i.c. was diagnosed as faulty and was replaced. Well, er, anyway the fault remained.

The monostable signals from within the i.c., at pins 21 and 22, were checked and found to remain stable even as the flip-flop pulses disintegrated. Rather disconcerting, since everything that followed was within the i.c. which we'd just changed. I then noticed that the pulse level at pin 22 was not as high as that at pin 21 – it was only about a third of the amplitude. Both monostables within the i.c., PG1 and PG2, are identical, with the same time-constants, but there's an extra "switching control" external to the PCB linked to pin 22. This control is mounted at the back of the machine and is labelled "still adjustment". We found that a screened cable to a plug marked ED had been badly positioned at some time and was forced tight against the potentiometer tag, cutting the PVC coating and forming a resistive path chassis. This reduced the voltage to the potentiometer. While the time-constant remained the same, the pulse level was reduced and this affected the triggering of the following internal bistable flip-flop. Phew! S.B.

Sony SLC7

The 400mA fuse (F004) had blown. Another blew whilst I tried to check the operate and standby switches. With a six inch nail across the fuseholder I was able to ascertain that the machine didn't switch off – it was on all the time. First impressions were that the clock display was reading

"E:E" and that all the red LEDs on the programme timer were lit. The power supplies were o.k. and something smelt hot: it was transistor Q3 on the timer panel – I got a blister on my finger! The programmable timer IC1 didn't have any switching pulses at pins 22-27, though the clock pulses at pin 1 were present and correct. A new i.c. (MB8841-180) and Q3 restored normal operation. The reason for the machine failing to switch off was that pin 11 of IC1 remained high, holding the power supply on via D1. It seems that most of the i.c.'s output pins were set high, hence the demise of Q3. S.B.

Sony SLC5

Eject and rewind were o.k. but there was no playback or fast forward. Move straight to the forward sensor i.c. (IC8) on the systems control panel. Output pin 8 was high with the result that the system control microcomputer i.c. thought the tape end sensor had operated. I think IC8 (BX342) also has a tendency to play up intermittently. S.B.

Grundig VS200

This is a fine machine but we have had a couple of problems. One had a faulty r.f. amplifier. As this is fixed to the tuner/i.f. panel it must be removed before being returned to Grundig – it's not necessary to replace the lot. A second VS200 produced spots on playback, similar to static discharge: there was also some noticeable sideways shift to the picture, as though the drum speed was changing. The cause was found to be grease on the motor wiper contacts, inside. If you have to remove the bottom fixing plate, mark it with respect to the outer casing of the motor – the reason for this is that rotating the plate with respect to the motor body (stator) will cause more interference. The plate is rotated during assembly for minimum electrical noise: either reassemble it where it was or carry out the "tuning" adjustment as specified in the manual. S.B.

Watch this Space!

We've just purchased some duff Sony SLC5s and SLC7s from one of the bulk suppliers in Birmingham. Most of them seem to have been abandoned due to system control faults. Watch this space! S.B.

The New Mitsubishiis

A few words on the new Mitsubishi models. The HS307 is a two-speed version of the HS306, with infra-red remote control. No skew correction etc. is incorporated in the long-play mode so visual search in this mode is poor. On the other hand narrower heads have been used than in the HS330, giving a better long-play picture. One possible problem is that there's no indication as to whether L.P. or S.P. has been selected.

The HS400 is a single-speed hi-fi machine. The standard sound is in mono and the pause is of the "instant stop" type with a noise bar where it happens to stop.

There are facilities for TV/external stereo/simulcast recording and the machine can be used as an audio only hi-fi recorder. The record levels can be set manually or automatically, two bar-type meters giving indication of the levels. There's audio dropout compensation for head switching. **D.S.**

Mitsubishi HS304

A fault we've had several times recently with these machines is dry-joints on IC2A0 (M51450P). This can give rise to various symptoms – intermittent picture on record, intermittent colour on record, intermittent speed variation and intermittent playback luminance. Care must be taken when resoldering this i.c. as many machines have a soft varnish sprayed over the solder side of the panel in this area: the varnish must first be scraped off thoroughly to make correct soldering possible. In fact it seems to be the machines with this varnish that suffer from dry-joints.

A weakness that's shown up on this model is the remote control socket. It's mounted directly on the corner of the presetter board and we've had four cases so far where the customer has pushed too hard when inserting the remote control plug with the result that the corner has broken off the panel. This can cause loss of signals as the return path for the tuning potentiometers passes near the socket. If the customer wishes to continue using the remote control system the panel should be replaced, since any repair is likely to fail after a couple of insertions of the remote plug. Fortunately the panel is quite cheap. **D.S.**

Ferguson 3V32

Dead VCRs are usually easy, aren't they? Don't be fooled, not all of them are! This one looked dead at first glance, until you noticed that the off light was illuminated. A quick check on the supply lines showed that nothing was wrong except that the switched 12V line was missing because the relay wasn't energising when the on switch was operated. Attention was turned to the tuner/timer board as this drives the relay. The clock oscillators were running and the reset/interrupt lines were normal. A study of the manual was called for. One of the tables shows the functions of all the microcomputer pins in detail. Using this we scoped each pin in turn. Pin 36 of the i.c. (IC206) is shown as being the power off/a.c. detector and was low when it should have been high. D207 rectifies an a.c. input from the tuner/timer subpanel and was found to be open-circuit. **P.B.**

Grundig 2 × 4 Super

The machine was playing back when unthreading was selected by remote control. It unthreaded and ejected the cassette but thereafter refused to load a cassette. Switching on subsequently started the head and reel motors, the machine appearing to be in the "stop" (still frame) mode. Fifteen seconds later the tape fault logic put a stop to things – confirmed by the keyboard (system control) module lines WS1/2/3 all reading high. The threading ring switch contacts and cassette compartment switches were checked, including the one hidden inside the cassette retaining lip. All were in order, as was the operation of the reel brake solenoid and the c/o switch.

We turned the threading motor manually to load and thread a cassette, switched on and found that the machine unthreaded correctly. Attention was then directed to the keyboard module, particularly to the power supplies.

During fault chasing the symptoms changed to playback LED lit, no motor action, with lines WS1/2/3 all low, meaning "tape" (stop mode). The relay remained de-energised.

At switch on a 150µsec reset pulse is sent to the microcomputer i.c. This is followed by an initiation cycle. If the power supplies to the keyboard module are low or slow to build up this time window may be missed. The back-up batteries and accumulator module were removed and tag A and AC1-5 on the power board linked. No improvement. Meter and scope checks on the reset line revealed a blip at switch on, implying that the reset pulse was present. The 15V rail was correct and the 5V line read 4.8V (it comes via a transistor until the relay energises). Further checks were made on the keyboard module. The clock signals were present and no obvious faults could be found. The previously mentioned switches were meter checked from strobe lines 5 and 6 to input lines AF1/2/3, proving that the connections via the motor connection board were sound – this is an area where poor connections can give trouble.

We diagnosed a faulty microcomputer i.c., but as the cost of this is half the cost of an exchange module and much of the board logic is interrelated an exchange unit was fitted. This produced play, record and the wind functions but cassette eject produced nothing followed by no other control functions. Controlled anxiety (deep depression) followed. We wound the threading motor manually to unload the cassette and return the slide rack to the end stop. Thereafter cassettes would load and unload and all functions worked. We can only assume that during fault finding the relative positions of the sliding rack and ring drive gear on the threading mechanics became displaced. One question remains: did the remote control unit that operates the strobe and input lines to the microcomputer i.c. cause the damage? **B.R.**

Mitsubishi HS320

For poor or no fast forward check the pinion cog which can slide down the shaft, removing the drive to the take-up reel. If you order the pinion cog for the HS330 you'll find that it has two grub-screw fitting, giving more secure positioning on the shaft. This fault can also break the tape in the playback or rewind modes and has been known to chew the tape in playback. **J.C.**

Hitachi VIP201P Disc Player

In the event of no stylus arm movement first ensure that the cartridge cover is locked in. If this is all right and the disc loads correctly but there's no arm movement check the arm motor. In one case we found the motor seized up: a drop of oil released the shaft to prove the point, a new arm motor restoring correct operation. **J.C.**

Panasonic NV333

The fault was no field lock in playback. The sync signal amplitude turned out to be only 1V p-p instead of 2V due to IC3003 (AN6327) in the luminance channel being defective. **J.C.**

Mitsubishi HS303

In the event of intermittent hum on sound, check the audio head switching relay K3F0 by replacement. **J.C.**

Long-distance Television

Roger Bunney

April saw a dramatic improvement in long-distance signal propagation, particularly towards the end of the month with improved Sporadic E conditions. There has also been productive auroral activity. A small event on April 9-10th gave Band I reception from Scandinavia in the northern UK. Over April 19-21st there was a much larger auroral event. A sudden, high-level disturbance on the sun produced storm conditions which were particularly intense on the 20th, giving auroral 144MHz amateur band propagation from Leningrad to the UK. During this period Band I was full of characteristically "hummy" vision signals from Scandinavian and E. European sources. The auroral conditions continued through to the early hours of the 21st, a smaller auroral opening occurring during the afternoon. Following this major event, ionospheric conditions remained very unsettled up to the end of April.

Tropospheric conditions also improved marginally over the month. During the evening of the 19th Benelux and W. German signals were received in the south and east of the UK in Band III and at u.h.f. A more intense tropospheric opening late on the 22nd produced more sustained Benelux, French and W. German signals over much of the UK, as far as the Midlands. As I write this on May 6th it looks as if a further tropospheric opening is about to occur. Several enthusiasts have reported an increased number of Band III Canal Plus stations during the slightest of tropospheric lifts. Caen ch. F9 has proved to be an easy catch here in the Southampton area. Lille ch. F5 can be received throughout much of the UK and along the N.E. coast – as it could be when the old 819-line system E transmissions were in use.

SpE provided the main excitement towards the end of the month, with four consecutive days of openings, most being of long duration with intense signal strengths. This is undoubtedly a sign of better things to come. Unfortunately some of the openings occurred during weekday working hours and will thus have been missed by many. The SpE log is as follows:

9/4/85 SRG (+PTT – Switzerland) ch. E2; ARD (W. Germany) E2; TSS (USSR) R1; CST (Czechoslovakia) R1.

15/4/85 ORF (Austria) E2a; CST R1.
 29/4/85 TSS R1, 2; CST R1; ORF E2a; JRT (Yugoslavia) E3; RAI (Italy) IA, B; SRG/+PTT E2; TVE (Spain) E2.
 1/5/85 TSS R1 (very strong during the early morning); ORF E2a, 4; MTV (Hungary) R1; RAI IA; TVP (Poland) R1; TSS R1, 2.
 2/5/85 ORF E2a; JRT E3, 4; unidentified ch. R1 and 2 signals.
 3/5/85 EPT (Greece) E3; JRT E3, 4; RAI IA, B; TVP R1, 2; TVR (Rumania) R2.
 An opening during the morning lasted up to 1200. Ray Davies (Norwich) received EPT during much of the morning period.

My thanks to Iain Menzies (Aberdeen), D. Patuzzo and Roger Pates (both in Nottingham), Dave Shirley (Hastings), Reg Roper (Torpoint), Cyril Willis (nr. Cambridge) and Ryn Muntjewerff (Holland) for their reception reports which supplement my own log.

Roger Pates mentions a mystery transmitter radiating Anglia TV in colour on ch. E10. It was noted towards the end of April – a query to the IBA failed to produce any information. Roger checked his immediate neighbourhood for a faulty, i.e. radiating, receiver then set out on a trip to try to establish the source of the signals, which are weak in the Nottingham area. He thinks they come from the Lincoln area.



From our Correspondents . . .

Fred Pilkington (Newmarket) lives for part of the year near Torremolinos in Southern Spain. In addition to TVE, signals can be picked up there from Morocco and Gibraltar. He reports that GBC presents problems, with only 250W e.r.p. at 70 miles – Fred is now using a ZL special Yagi to receive GBC, which has moved from ch. E12 to ch. E11 to avoid interference from RTM (Morocco).

News Items


France: Advertisements on Canal Plus during unscrambled transmission times started in early May: the service now claims to have over 300,000 subscribers. The TV5 French language satellite channel is to increase programming to four and a half hours this autumn: a further extension to eight hours is planned. A reciprocal agreement for the exchange of programmes has been reached by TV5 and Canada.

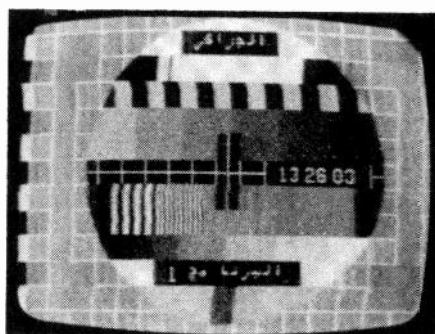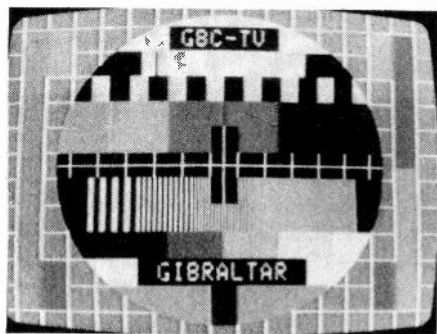Greenland: The 50-045MHz amateur radio beacon OX3VHF at Denmarks-Haven has closed down. Plans are to start up from another location in late July/early August.



EVL Bruxelles		
1	JRT	accident 1500-1508
2a	RAI	blessing 1510-1513
b		hunger 1513-1515
3	SABC/ITN	botha 1519-1520
4a	ITN	anti nuclear CANCELLED
b		easter parade 1525-1526
5	ETV/BBC	subarak 1505-1510
6	IRIB/ARD	p. de cuellar 1526-1530
add		
	TDF	caledoniens 1515-1519
	ETV/BBC	demo 1505-1506
c		
7	SVT	table tennis 1530-1532
8	NOS	fortuna 1533-1537
9	BT/ORF	bulgaria 1537-1539
10	TDF	tennis 1539-1543
11	VIS	safari CANCELLED
	ITM	uesthas 1543-1548

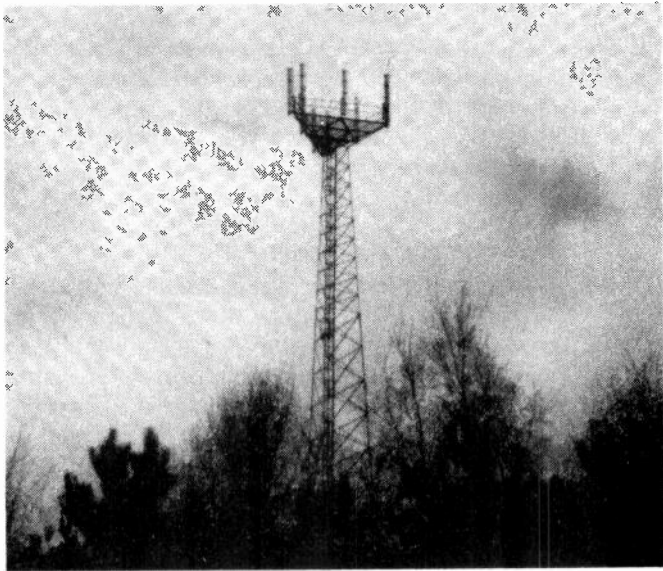Left: Gibraltar PM5544 test pattern received by Fred Pilkington at his flat near Torremolinos, S. Spain. Centre: Moroccan test pattern received by Fred Pilkington in S. Spain. Right: EBU News exchange at 4GHz, received by Frank Lumen in Denver, Colorado via a Satcom downlink.



Lattice aerial mast for the 900MHz cellular phone network, at Rhowams near Southampton. The mast carries several vertically polarised colinear arrays with corner reflectors.

New Zealand: Advertisements are to be allowed on the TV1 and TV2 networks for a similar amount of time daily – but not on Sundays, Christmas Day or Good Friday.

Pakistan: A second network is under construction. Programmes will be mainly educational. Three studio centres are being established, at Lahore, Karachi and Islamabad, feeding a network of eighteen transmitters via an extensive microwave link system.

USA: Ted Turner's CNN cable news service is to be made available to European cable networks this autumn, linked via an Intelsat satellite.


High Spec Ch. E2/R1 Amplifiers

The end of UK TV broadcasting in Band I has left the band relatively wide open for DX reception, though cordless phones are causing headaches for some enthusiasts. Multiple-hop SpE sometimes brings in ch. E2 signals from the Ghana/Nigeria region. In the past such signals have often been marred by distant BBC-TV signals on ch. B2. Along the south coast it would be worthwhile monitoring ch. E2 for the weak, scattered SpE signals that are commonly seen in central and southern France but are less frequently noted in the UK.

There's great interest at present in the 50-52MHz amateur radio allocation, use of which is currently on an experimental basis and restricted to non-TV hours. This interest has resulted in the appearance of high-specification 50MHz aerial amplifier kits on the market. It occurred to me that this type of preamplifier could be retuned to cover ch. E2, providing high gain, very low noise and good selectivity (i.e. no overloading from local CB operators, something that can happen with wideband preamplifiers). Apart from the specialised Mutek Model BBBA500u 20-500MHz aerial amplifier with its 1.5dB noise figure, most commercial amplifiers tend to have a noise figure of around 4dB at best.

The Cirkuit Holdings PLC (Park Lane, Broxbourne, Herts EN10 7NQ) kit type 40-08006 is available at £7.25 plus 60 postage, excluding VAT, for use on the six metre amateur band. I bought the kit with a view to using it to cover the ch. E2/R1 section of the band, though there's enough gain to pass ch. E3/R2 signals (ch. E4 signals suffer attenuation). Maximum gain of some 20dB is available over a bandwidth of around 3MHz, the gain

SOUTH WEST AERIALS

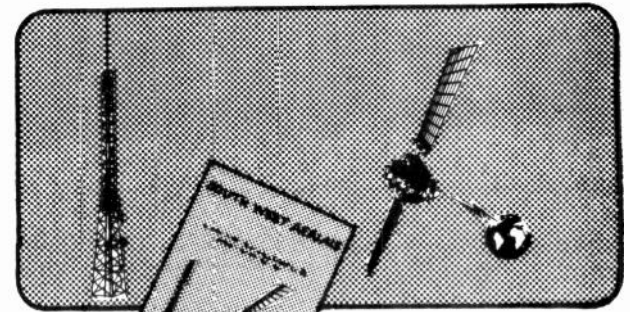

This catalogue is your key to solving a host of television and radio reception problems. We shall be delighted to forward your copy on receipt of 60p.

EQUIPMENT & PROFESSIONAL ADVICE

South West Aerials offer a unique blend of the best equipment and impartial professional advice for long distance Television DXing or simply better reception.

We have secured a small quantity of the following items and offer them at special prices for a limited period.

LABGEAR UPCONVERTERS ideal for TV-DXing, used but guaranteed in good working order, mains powered, limited stock £12.75
PHILIPS G8 SELECTIVITY Units, brand new in screening cans. £2.50 each or 2 for £4.50
PHILIPS G8 VISION GAIN Modules, same spec. and price as above.

Other examples from our range:

TRIAx Unix 92 Element 'Anodised' 17dB High Gain UHF Aerial, available in Groups A, B, C/D, E, K or Wideband (channels 21-68) £45.75
LABGEAR CM7006 High Gain (26dB) low noise, less than 2dB; Wideband (chs. 21-68) UHF Masthead Amplifier £18.25
LABGEAR CM7261 Matching Power Supply Unit for use with above amplifier £13.50
LABGEAR CM7093 UHF Wide band Set-Back Amplifier. One input, 3 outputs; one @ 8dB; one @ 10dB; one @ 12dB Gain, Mains Powered £18.15

Also available Black & White and Colour Multi-Standard VHF/UHF Televisions and Video Recorders (SAE or ring stating requirement)

We are **THE DXing Specialists**, advice given on ALL reception problems (SAE please)
 All prices inclusive of VAT and Carriage Delivery 7-10 days Access & Visa welcome



SOUTH WEST AERIALS (T)

11, Kent Road, Parkstone,

Poole, Dorset, BH12 2EH. Tel: 0202 738232.



falling rapidly on each side: the noise figure is 1.5-2dB. Construction is very simple apart from the need to wind a wideband toroidal transformer. The kit comes complete with a metal case, BNC sockets, PCB and all components. A dual-gate m.o.s.f.e.t., type 3SK45, is used: fitting a 3SK88/BF960 provides increased gain with a slightly reduced noise figure. The preamplifier was originally a REW project by Graham Leighton. Using the tuning capacitors and Toko coils provided I found that the input circuit wouldn't peak to give maximum gain on ch. E2 – further shunt capacitors were needed. With 4.7pF added across C1 and 3.9pF across C3 the bandpass coils L1 and L2 could be peaked as required. As a specialised amplifier for ch. E2/R1 DX use this project can be highly recommended.

For the more adventurous the narrow-band 50MHz

4GHz + 11GHz SATELLITE TV RECEIVING EQUIPMENT

4GHz LOW NOISE AMPLIFIERS, RECEIVERS,
 DOWNCONVERTERS, FEED HORNS.
 11GHz BLOCKCONVERTERS, DEMODULATORS.
 ANTENNAS FOR BOTH FREQUENCIES.
 SATELLITE RECEPTION FEASIBILITY REPORT.

A full report on reception feasibilities at a given location.
 PRICE: £50.00. Please state longitude and latitude.

For further details contact:

HARRISON ELECTRONICS

22 MILTON ROAD, WESTCLIFF-ON-SEA, ESSEX S20 7JX. Tel: (0702) 332338

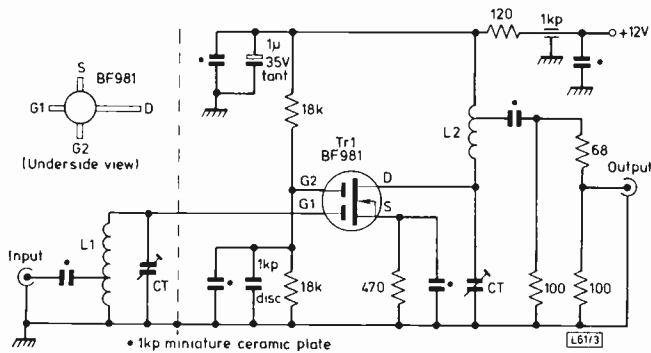


Fig. 1: G4IJE's 50MHz narrow-band preamplifier. L1 consists of 9 turns, 22g, tapped 2½ turns from the chassis end; L2 has 10 turns, 22g, tapped 1½ turns from the 12V end.

preamplifier (see Fig. 1) designed by Paul Turner (G4IJE) is worth serious consideration. Once again a dual-gate transistor is used, this time the higher performance BF981 which provides higher gain and lower noise than the device used in the Cirkit project. The input and drain load circuits are both tuned by miniature variable trimmers (5-65pF, RS type 125-660) and can be peaked above and below the 50MHz band. This circuit is for the more experienced r.f. operator, since care must be taken over the screening, decoupling and close observation of v.h.f. constructional techniques (i.e. minimal lead lengths etc.) if stability is to be achieved. Our thanks to Paul and the Six Metre Group for permission to reproduce the circuit which originally appeared in their bulletin *Six News*.

We'd be interested to hear from DXers of the results they achieve with narrow-band Band I amplifiers and if possible any observations on comparisons with the use of wideband amplifiers.

PAL/SECAM Converter Module

News of a converter module which can be fitted to a normal PAL-only colour receiver to enable it to display PAL or SECAM signals has come from our Dutch DX-TV friends. It's made in W. Germany by Dahner Elektrik and is available from S.A.P. of Wiesbaden-Bierstadt as Module KS478/SM1. It's suitable for use with most PAL only sets and will switch automatically on reception of an E. European SECAM signal, i.e. from GDR or another OIRT source. There are just eight wired connections and the module requires 85mA (typical) at between 12-30V d.c.

We understand that 6.5MHz system D sound adaptors are also available. The S.A.P. company will indicate connection points for specific receivers and the cost, at early April 1985, was DM 142 plus 14 per cent VAT. Ryn Muntjewerff tells us that he has been using one of these modules and that good SECAM is resolved.

For French system L SECAM reception, a VTK1

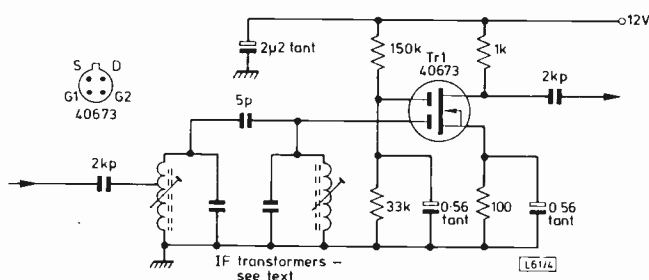


Fig. 2: Mike Gaskin's selective i.f. preamplifier circuit.

module can be used in conjunction with an SM1 to give vision and sound on a standard PAL receiver. It appears however that certain teething troubles have been experienced as a result of which marketing of the package has been delayed. We will pass on any further news received from our Benelux/German friends.

Simple Selective IF Preamplifier

Mike Gaskin (Caterham) has sent in the simple but effective i.f. preamplifier circuit shown in Fig. 2. It provides good selectivity using a 40673 dual-gate m.o.s.f.e.t. in a simple, non-critical circuit. The double-tuned, lightly coupled input transformers give (depending on whether peaked or stagger tuned) a variable bandpass characteristic. It's suitable for cascading, each stage providing a gain of some 12-15dB.

Mike used i.f. transformers taken from old transistor i.f. strips. He feels that they may give less than optimum matching to the 40673 transistor and suggests that experimentation could give improved results. Cirkit have a range of Toko 35MHz i.f. transformers that could be used in the circuit. Although Mike's prototype has the input tapped in at the hot end of the first coil there's no reason why the input shouldn't be experimentally coupled to the top of this coil.

Commercial Corner

East Cornwall Components (119 High Street, Wem, Shropshire SY4 5TT, telephone 0930-32689) tell us that they can supply 22in. remote-control v.h.f.-u.h.f. Decca/Tatung TV sets in single-standard format (e.g. system B/G with 5.5MHz sound) for either PAL or SECAM colour (the latter with a slight delay) at £295 inclusive of VAT, carriage paid in the UK. Apart from the French system L, sets for any system in use throughout the world can be supplied - apparently the service is used by people returning from the UK to countries where the prices of TV sets are vastly in excess of UK prices. Send enquiries to Mr. M. Cox at the above address.

The Worthing and District Video Repeater Group has available for ATV enthusiasts considering 23cm/1.3GHz operation a kit of parts to make a three full-wave colinear plus reflector aerial system with a gain of 10dBd over a dipole and a horizontal beamwidth of 60° (-3dB points). The array covers the whole 23/24cm band and has been found to give excellent results into France as far as Paris. The kit of parts costs £10.95, with instructions, and can be obtained from Mr. R. Stephens, Toftwood, Mill Lane, High Salvington, Worthing, W. Sussex - the price includes post and packing. The group has no other products available at present.

Satellite News

We understand that Sky Channel is to drop scrambling - this should be of interest to exiled UK residents along the south coast of Spain/Portugal.

The 4GHz Spacenet-2 satellite at 69°W has been received in Yorkshire (elevation 5°) with the CNN cable news feed.

The Intelsat organisation has given permission for their TV programme feeds to be downlinked via several US satellites, including Satcom 1, 3, 5, Comstar D4, Spacenet-1 and Galaxy-1. Frank Lumen in the USA checked and found that various European news feeds, including ITN, TG1 (Italy) and certain EBU services, were available via transponder 11 on Satcom F1.

Making PCBs

Malcolm Burrell

It often happens that you want to build something or even replace a damaged subassembly in a piece of equipment but the cost of a new board is exorbitant or one simply isn't available. The disadvantage of using Veroboard is that you can easily make mistakes while the amount of cutting and wiring can be time consuming. Varying the component layout can also sometimes cause problems. The solution is to make your own board.

Unless you are likely to be involved with a large number of projects the investment required for photographic board production is not worthwhile. It also remains a time consuming process. Recently I wanted to make a small number of boards. I couldn't afford much time or money but devised a compromise method that worked well.

Layout Design

The first step was to design the layout. I'd a working prototype built on Vero V-Q board and it was quite easy to sketch in the components on the paper template supplied. The previously wired sections were then linked as tracks and gradually a layout was developed. One thing to remember is that the print pattern is the reverse of the component layout. Dealing with this is quite easy really: draw your design on paper then soak it in varnish so that you can see the layout on the reverse side. This can be photocopied so that you have a record of the original design however much you mutilate the original drawing.

Making the Holes

Starting with the original drawing, it's easiest first to mark out the component mounting holes. Tape the drawing to the top of the board and use a 1mm drill to make the holes. The miniature drills advertised by firms such as Maplin are a useful investment. It's possible to use the average household DIY type of drill but these are clumsy and you'll all too easily break the small bits. If you intend to make two or three boards to the same circuit they can be stuck together with tape and drilled in one go. It's best to drill the mounting holes in the corners first, then temporarily fix the boards together using say 6BA screws.

Print Pattern

This will leave you with a plain board full of holes but with no print pattern. The holes will act as a guide: you can join them up by sketching in the print design with a felt-tipped pen. For a really neat job you can buy dry-print transfers – these are especially useful for i.c. pads.

Using this method of drilling the holes first you must make sure that all burrs have been removed. Then clean the board with alcohol to leave a clean surface for the transfers. A pen and ruler can give quite a good pattern without transfers however.

One way to make neat i.c. pads is to link all the holes

with a paint marker pen. When the paint is completely dry, score lines between the holes with a knife so that the bright copper shows through.

Having laid out the tracks I like to make each one as thick as possible without adjacent tracks touching. The paint marker pen is useful for this purpose since it gives thick, even lines that are less likely to be eroded by the etching acid. There are two other reasons for keeping the tracks thick – unless you're concerned with v.h.f. circuits. First, some circuits take a considerable current: there's nothing worse than to spend a lot of time making a neat board only to see the tracks melt like fuses when the power is switched on. Secondly, the acid can be reused several times: since its strength decreases as more copper is dissolved it's best to etch away only as much copper as necessary, leaving the rest behind to strengthen the board and ensure satisfactory connections.

Etching

Check the board before etching it. For the etching bath a good disposable plastic tray such as an old polythene sandwich box can be used, preferably with some plastic tongs. If you wish, attach a piece of thread to one corner of the board so that it can be moved without direct contact.

Take everything into the garden shed away from everyone – and wear old clothes! Pour enough acid into the tray to cover the board. Etching is a tedious business: agitate the acid every minute or so or it will take a very long time indeed. Etching should be complete after twenty to thirty minutes. Carefully remove the board from the etchant and plunge it into cold water. Cover the acid and rinse the board thoroughly under a tap – remember that all traces of acid must be removed from the holes.

Hints and Tips

If you wish to store the acid, either pour it into the original bottle using a funnel or use a secure glass bottle labelled "acid". I understand that it's dangerous and undesirable to dispose of acid into the sewerage system. If no neutralising agent is supplied the best course is to dig a hole in the garden and pour the used acid into this.

Painted markings on boards can be quite easily removed with alcohol. A touch with emery cloth will leave a bright copper surface for soldering. Once the components have been mounted and soldered it's a good idea to brush the print with varnish to help protect it from corrosion.

The print patterns are often given with projects in the magazine. If they are to scale it's better to photocopy them rather than to cut the magazine, using the photocopy as a template for drilling. It's all rather like painting by numbers, but you have the option to vary the layout or increase the size of the circuit to suit yourself.

Mounting the board in its case is easy if you use 6BA threaded spacers. Screw these into the case first, then use 1/4in. 6BA screws to secure the board. Alternatively plastic stand-offs can be used. These need slightly larger fixing holes, typically 0.2in. – I find a 3/16in. drill useful for these.

Prototype Working

A final hint. For prototype working, off-cuts of printed circuits can be etched without drilling and the components mounted on the print side.

More on the Philips G8 Chassis

Dennis Apple, B.Sc.

Tony Thompson's article in the May issue contained much valuable information on the Philips G8 chassis. The following notes may also be of interest to readers – they are based on experience gained servicing a large number of these sets.

Connector and Panel Faults

Before switching on, check the various plugs and sockets on all panels. A small needle can be used to close up slightly all tired spring holders within these connectors. Don't forget the tube base. Also ensure that the various fuses are all securely fitted in their holders. Finally the flying leads, especially those on the line scan panel, should be checked for tightness. A quick spray of cleaning fluid such as WD40 on all connectors prior to reassembly helps prevent further problems. It's surprising how many baffling, intermittent faults disappear after this treatment!

You may also find hairline cracks around each panel where the edge connectors are located, no doubt caused by someone's over-zealous attempt in the past to tighten the two retaining screws without first ensuring that the edge connector is correctly mated. The timebase panel is the one most likely to be affected by this problem. You will almost certainly find that the print under the contrast and field hold controls has suffered stress due to careless back cover fitting in the past: insert the knobs through the holes in the cover before locating the cover in its retaining groove.

Setting up the HT

The correct h.t. voltage at TP67 (either of the h.t. fuses) should be 205V under normal working conditions. The official setting up procedure is as follows:

- (1) Turn the set h.t. control R1370 to approximately mid-position.
- (2) Turn the overvoltage preset R1396 fully anticlockwise to disable the overvoltage protection circuit.
- (3) Turn R1370 until the reading at TP67 is 225V.
- (4) Turn R1396 clockwise until this reading falls to 220V. On a working set the picture will then flutter, showing that the overvoltage protection circuit is operating.
- (5) Turn R1370 to obtain 205V at TP67.

If you cannot carry out this procedure the power supply is faulty. The most common faults are picture flutter, inability to obtain the correct voltage, and intermittent fuse blowing.

Picture Flutter

The causes of picture flutter are usually as follows:

- (1) Defective BR100 trigger diac (D1377) in the power supply. In an emergency this device can be reversed. Testing is difficult since the device measures virtually infinite resistance both ways – substitution is the best way of proving the guilt or innocence of this component.
- (2) Defective power supply thyristor (SCR1379). A standard fault on the G8. It should be replaced whenever the power supply is suspect. The thyristor can appear to be all

innocent when checked with a tester but play silly games when in circuit. For example, in one case of picture flutter the thyristor was found to be light sensitive: its anode-cathode resistance fell to a few thousand ohms when a bright inspection light was shone on to it! Gentle heat had the same effect.

- (3) H.T. smoothing capacitor C5536 (600 μ F) on the line scan panel defective.
- (4) Very low field sync pulse amplitude due to a defective TBA550Q i.c. on the signals panel.
- (5) H.T. reservoir capacitor C1385 (600 μ F) on the power supply panel defective: this capacitor tends to leak horrible-looking gunge as it slowly loses capacitance.

Incorrect HT

Causes of inability to obtain correct h.t. voltage (205V) are usually:

- (1) Thyristor becoming leaky as the set warms up.
- (2) Assuming that no other faulty component is found, you'll probably find that one or both of the two high-stability resistors R1368 (470k Ω) and R1369 (8.2k Ω) has changed value. Such changes are usually small and difficult to detect using a normal test meter – substitution is by far the quickest way of testing these components. Temporarily dabbing a 1M Ω resistor across these suspects will show which – if either – has changed value. Be careful not to blow the set up by careless testing in this area: as you probably know, the line output transformer in this chassis has suicidal tendencies.

Fuse Blowing

The mains fuse is rated at 3.15A and is of the anti-surge type. It's useful to distinguish between violent fuse blowing (blackened, charred debris) and peaceful demise. In either case check the thyristor first by substitution.

Violent fuse blowing is often caused by:

- (1) The insulation between the "mains dropper" R1367/R1381 and the chassis mounted fixing lugs becoming defective.
- (2) A defective mains switch, especially when of the earlier open variety.
- (3) A short-circuit mains filter capacitor – C1366, 0.33 μ F.

In the event of non-violent fuse blowing simple replacement may restore normal operation. If not, suspect the h.t. reservoir capacitor C1385 and the line output transformer – the latter may blow fuse FS5557 (800mA) on the line scan panel.

Timebase Panel

The most common fault on the timebase panel is failure of the transducer, which can suddenly go up in a cloud of smoke. A quick check is to disconnect plug H, which will take the line section of the transducer out of circuit, but leaving the plug out permanently will impair the picture geometry. This can normally be observed only on a crosshatch pattern. Its importance depends on the screen size and the cost of repair.

Inability to set up the line hold can be caused by the 18V zener diode D4531.

Poor field lock and picture jumping between scenes can be caused by the TBA550Q i.c. on the signals panel.

Field collapse sometimes occurs when R4533 (if fitted) springs open. Resoldering often provides a permanent cure. Later boards were modified to prevent this.

C4452 in the field charging circuit can leak to give bottom foldover when cold.

Note that although the field scan coupling capacitor C4479 is shown with the correct polarity on circuit and wiring diagrams on some panels the connections are incorrectly printed. If the capacitor is fitted the wrong way round the whole picture floats gently upwards, no amount of field shift control adjustment restoring correct conditions. This occurs because as C4479 becomes more leaky more unwanted d.c. flows through the field scan coils.

Lack of height can be caused by the bootstrap capacitor C4469 (220 μ F) falling in value.

Line Scan Panel

The line scan panel, on which the driver and output stages are mounted, causes the majority of faults in the G8 chassis. The dreaded line output transformer lives here. Anyone attempting to service G8 chassis should have a stock of replacement transformers to hand if only to prove the innocence of this component should a weird symptom present itself. The cost of replacement transformers is fortunately not high and they are easy to obtain – perusal of advertisements in the magazine will soon confirm this.

For the uninitiated, the line output transformer can cause the following symptoms: (1) failure of fuse FS5557 (800mA), often intermittently; (2) reduced width with overheated windings; (3) intermittent crackles and picture fluctuations; (4) smoking from the overwinding.

If both line output transistors go short-circuit FS5557 blows. It's more common for one transistor to go short-circuit however, leaving the other to plod on. In this event the symptoms are a slightly oversize picture with low brightness and contrast, the picture size changing with alteration of the brightness control setting. In general the picture looks drab and lacks sparkle, giving the impression that the tube is about to meet its maker. Low h.t. voltage will also produce this state of affairs of course, so the prudent engineer will always start by checking the voltage at the two fuses on the power supply panel.

A quick, reliable check on the output transistors is to measure the voltages at the two heatsinks. Under normal conditions one voltage should be about half the other, i.e. 190V and 90V. If both collectors are at about 190V one transistor is probably short-circuit. The originals were BU105s: a pair of BU208s make ideal replacements.

There's a trap here for the unwary however. After replacing both transistors with known good ones the original fault symptoms may persist, with both heatsinks still at about 190V. In this case the fault is nearly always due to the balancing coil L5003, which is at the extreme top of the panel. In fact this may be all that was originally wrong. You'll almost certainly find that the core is stuck,

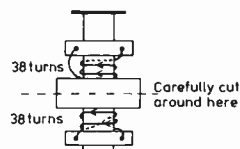


Fig. 1: Details of the line output transistor balancing coil L5003, which is at the extreme top of the line scan panel.

and any attempt to force it will result in the little metal cap breaking off. A replacement coil can be purchased, but a quick way of dealing with it is as follows:

(1) Unscrew the four mounting screws then unsolder the whole coil from the upper board (take care not to leave little solder bridges across the print).

(2) Very carefully cut around the centre of the coil former with a junior hacksaw until you just hear the blade contact the stuck ferrite core (see Fig. 1).

(3) Unscrew one half of the assembly from the other, gently – they are not connected electrically.

(4) Gently unscrew the protruding ferrite core from one half of the assembly, using hand pressure only.

(5) The threads of the former can now be cleaned and the core reinserted with a trace of silicone grease on its threads. The whole assembly can then be resoldered to the board. Use a small amount of Araldite to hold the cut halves of the coil together.

After refitting the coil, turn the core while observing a stationary test pattern. At the correct core position the picture will be of minimum width and the e.h.t. will be at its correct, maximum value. The voltages at the two transistor heatsinks should then be at approximately 190V and 90V. Note that zero voltage at the heatsink of the "lower" transistor T5532 can also be caused by misadjustment of L5003.

The whole surgical operation on the coil takes about five minutes and is easily carried out using the simplest of tools.

Always make the output transistor heatsink voltage test when dealing with this chassis – it saves so much heartache!

Failure of F5557 has been traced to D5567 (OA91) going short-circuit (very early version of the panel with original type of beam limiter circuit). Failure of F5560 (1.25A – late version of the panel) has been traced to the 25V rectifier diode D5539 (BY210-400).

It pays to check the various diodes on the line scan panel before condemning the output transformer.

Sound Faults

A crackling sound with the volume control turned to zero has been traced to noisy BD131 audio output transistors, also a noisy TAA570 intercarrier sound i.c. This i.c., used in the earlier versions of the chassis, has also been responsible for a range of symptoms including no sound and severe buzz. If the associated quadrature coil L2601 is misadjusted the result will be low sound with buzz.

Crackling on one channel only (or when using a VCR) can usually be removed by very careful adjustment of the extreme left-hand core in vision selectivity can U2800, i.e. L2807. Distorted sound can occur when one of the BD131 audio output transistors goes open-circuit. Usually however the print to one of these transistors becomes detached, giving the same symptom even though the voltages may not appear to be too far from their correct values.

Convergence Panels

The earlier, sturdy vertically mounted front convergence panel was very reliable. This cannot always be said of the later, rear chassis-mounted panel used in the 550 series. Convergence drift is caused by the heat-sensitive AC128 transistors and the electrolytics on this panel. The

electrolytics dry up in the heat produced by the convergence potentiometers, especially the infamous R1934 (10Ω – R/G parabola) which often causes the whole board to burn up. A replacement panel may well cost more than the set is worth. Guard against R1934 overheating by removing the printed card and placing a heatsink around R1934. Noisy potentiometers on this panel can easily be cleaned with a spray of silicone oil. This should be done before attempting convergence.

Chroma Panel

Faults on the chroma panel are usually due to defective i.c.s. Sometimes a dry-joint develops on the luminance delay line (or the print underneath it), causing a double side-by-side image. This symptom is very often intermittent and can make one feel schizophrenic until one realises the cause. Loss of one primary colour is usually caused by a dud output transistor, a broken track or a dry-joint, e.g. on one of the output transistor emitter resistors. The $39k\Omega$ TBA530 load resistors R7326/R7346/R7363 change value to give incorrect colours.

In General

I agree with Tony Thompson's remarks regarding trade disposal sets. A sharp eye is indeed required when examining sets prior to purchase. One supplier swore on a stack of bibles that all his sets were complete but denied all responsibility when I later found that two panels were missing from one set.

A very good indication of what's wrong with a set is often given by the state of its interior. A line scan panel

hastily put back in position so that it almost falls out of the set usually means line output transformer trouble. The tube base left disconnected suggests bad news about the tube. A thick layer of dust over everything usually means that the set has simply died and the owner decided to exchange it for a new one. In such cases the fault is often a trivial one and the set can be got going as good as new – bearing in mind that the tube may not be in its prime.

The biggest problem is usually with the state of the cabinet. Very often an otherwise excellent looking set bears horrible scratches on its highly polished surface. Attempts to mask such defects usually fail because the wood becomes discoloured. The only complete solution when dealing with cabinet defects is to scrape the wood along the grain, in the same direction, using a very sharp wide chisel, until the whole surface is restored to its original pristine condition. Two coats of semi-matt clear varnish will then bring the appearance back to new. The discoloured wood veneer surrounding the tube can also be given this treatment – be careful not to crack it as it's very brittle. Use a barely wet fine brush and silver paint to restore the worn tracery around some models. With patience the cabinet can be made to look like new, but only you can decide whether the time spent on this is worthwhile for the return it brings.

It's essential to soak test a G8 before delivering it to the customer. Some faults, such as convergence drift or varying field height, may make their appearance only the morning after delivery, the set having worked faultlessly the previous day. Generally speaking the G8 is an excellent chassis with readily available spares: provided it has been conscientiously serviced and adjusted, a set will give many years of trouble-free viewing.

Sonys and Suchlike

Nick Lyons

Oriental chassis can sometimes be a little mysterious to an old "Empire" brain. Few are more mysterious than Sonys. Although generally very reliable and providing good pictures, there are some models I find it hard to forgive. I do forgive the modified NTSC decoders used in the early colour sets, honest. Also the otherwise superb KV1340 which just looked as if it had two dozen boards, half of which were no bigger than a large box of matches, linked together with a wiring loom like a telephone exchange. There's one sin so vile however that I cannot find forgiveness within me: the gate-controlled switch. Why Sony found it necessary to use these when everyone else managed without I don't know. Anyway, enter on cue a KV1810 with a terminal tube, the bottom of the picture a third of the way up the screen and atrocious linearity. Ever wishing to avoid this set with its GCSs, I suggested to the owner that any fault worse than a loose mains plug wasn't worth bothering about with the tube in such a shocking state. This was not his view however, so without further ado battle commenced. At least the bloody GCSs hadn't gone I thought. More on that later.

The KV1810, Part 1

A linearity control tweak just made matters worse, i.e. the bottom started to fold over. Never trusting linearity networks my first and entirely useless move was to check the two $2.2\mu\text{F}$ electrolytics that are connected in series

with the linearity control. Let's move to the other end of the field timebase I thought and see what the output stage is doing. Well, what it was doing wasn't quite right. The Avo proved that the output transistors were o.k. but the scope revealed drive problems. Always suspicious of electrolytics, especially non-polarised ones, I pulled out the bootstrap capacitor C520 ($10\mu\text{F}$, 16V) and also the similar but polarised coupler C522. Both were useless: having replaced them (C520 with a non-electrolytic type – it was huge, but as half the circuit was on the back of the board anyway . . .) things looked better but not completely right. It was not until C529 ($10\mu\text{F}$, 16V) in the height circuit and C533 ($1\mu\text{F}$, 160V) in the field amplifier circuit had also been replaced that the correct range of height and linearity could be achieved.

This left the set displaying a remarkably linear picture on a very weak tube – not only dim and largely green, but it was of the "by the time it's bright enough to see you can't focus it any longer" variety. Focus adjustment on these sets is another pain, being a solder tag effort – this really isn't good enough on a colour set. It did however improve the performance – to pretty bad!

Attention was next turned to the grey scale – magenta blacks, pink dark greys and lime green white. Not very promising. Much twiddling proved that this was about the best of which the tube was capable – at this heater voltage. Now naughty though this is, I thought that the only recourse with this tube was to bump up the heater

voltage. The mains transformer in these sets (it was a Mark I version) supplies only the c.r.t. heaters and the primary is tapped at 200, 220 and 240V. I thought it would be a good idea to put a crocodile clip on the transformer tap flyhead so that I could quickly change taps with the set running to see whether any worthwhile improvement was achieved. Well it did seem a good idea at the time, but I'd reckoned without the GCSs. As soon as I moved the flylead from the 240V tap and dabbed it on the 220V tap – bump, hum and the set was dead. The back-e.m.f. from the transformer had put enough of a pulse on the mains to kill off the GCSs. By now I was beginning to think that the whole thing was a bad idea: both GCSs had gone dead short – heaven alone knows how well these sets fare in households with poorly suppressed vacuum cleaners and the like.

After replacing the GCSs and putting the tube on the 200V tap a barely passable image could be discerned in a dimly lit room, but at least it was in focus. Time to get it back to the customer in haste. It was to return however, almost as hastily. But first for something completely different.

Monitor Trouble

Professional video monitors are a strange breed and never like to do anything by halves. Here's a case in point. At switch on the e.h.t. rustled up: all should have been well but there was no raster. In this situation, with e.h.t. present but absolutely no screen illumination, it's always been a habit of mine to glance at the tube's heater before doing anything else – of course it's always been lit and the trouble has been elsewhere. Always that is except this time. No light at all. Out with the Avo which recorded around 1V across the heater pins. So the heater wasn't open-circuit, but something was amiss. The circuit diagram showed that there's a heater winding on the mains transformer, but this isn't connected directly to the heater. Nothing as crude as that. A bridge rectifier, reservoir capacitor, series resistor and an 8V regulator chip were all present. As with all hi-tech equipment it was the hi-tech bit, i.e. the chip, that had failed.

Slow Slog

It seems to me that I have to slog through even the simplest of faults. I must have been the last person on Earth to attribute almost any fault on a Rank T20 chassis to 4R16. I always attribute faults on these sets first to the start-up circuit then to the line output transistor's series base feed resistor. It seems however that there are those who are slower than I: a colleague was amazed at my revelation that the field cramping on his ageing relative's set (Thorn 1400 chassis) was due to the diode dropper in the heater line going short-circuit. It's successful diagnosis like this that keeps me going. Going where?

The Damaged Portable

Well, on my way to do a little training the chap at the sports centre counter waylaid me to recount a tale of woe. Apparently his dog had had a little sport with the family's Contek portable, bowling it over in the process. Although the case had suffered minimal damage, the same couldn't alas be said of the PCB. Quite extensive damage had occurred in the general area of the heaviest component, the line output transformer. Fortunately the cracks were

for the most part visible and the board could be patched up. In cases like this I always find switch-on to be a bit dicey. This was no exception. A fearful display of arcing from the line output transformer occurred, though the rest of the set seemed quite happy. Close examination showed that the transformer's case was cracked, with particularly bad damage around the moulding where the e.h.t. lead leaves. A new transformer would have cured the fault but one wasn't to hand and the expense had to be considered.

Repairing the LOPT

Strips of tape were used to make a pouch over the cracks in the casing, the tape forming the outer wall of the pouch which stood about an eighth of an inch away from the casing. A proprietary epoxy resin was then mixed and poured into the pouch. A piece of plastic pipe about 3/4in. in diameter and about as long was used to repair the damaged e.h.t. moulding. The pipe was slit open so that it could be got over the e.h.t. lead without having to remove the cavity connector, then positioned on top of the transformer around the lead moulding. Preparations were completed by taping the bottom of the pipe to the transformer and taping up the slit. Epoxy was poured in and left for half a day to set, after which the tape was removed, revealing a neat-looking job. But would it stand the best part of 30kV across it? I switched on with trepidation. The set sprang to life and all was well. Some weeks later it still is. So for a couple of feet of tape, a bit of tube, about a quarter of a pack of epoxy and not a lot more time than it would have taken to fit a new transformer if I'd had one the set was back in service. I wouldn't expect this to work with all transformers or in every case but with transformers of this type of construction (similar to TX10 types) a reasonable success rate looks likely.

The KV1330

Set dead said the report, and so it was. This particular Sony KV1330 had run faultlessly from new (must have been the best part of ten years). The input fuse had popped with some force. On replacing it and measuring the mains input with an Avo a dead short was recorded. Clearly the mains filter capacitor had died and there it was, obvious on the input panel. I removed it, a brown toffee-looking thing, and fitted a purpose-designed mains filter capacitor. Sony had been generous, drilling several sets of spare holes in the panel to accommodate various lead spacings. Incidentally I'd recommend fitting purpose-designed mains filter capacitors for both safety and reliability – if you do use a standard type, use one rated at 1kV d.c. or 400V a.c. at least. Having said all this, as you'll probably have guessed by now the fuse blew at switch on. Why? Well there are actually two such capacitors in this set, the other one residing on the power regulator panel. It was actually this one that had died, C601 by name.

Return of the KV1810

Which brings us back to the KV1810 which had by now reappeared with more field trouble. We'd replaced most of the electrolytics last time. What was left? Well the scan coupling capacitor C517 (22µF, 160V) for a start. When it was removed a ring of goo was left on the panel. It had indeed gone to its maker.

BBC Micro Test Pattern Program

Patrick Kniveton, B.Sc.Eng.

The following program was designed to provide most of the patterns normally produced by a TV pattern generator plus one or two extras. All operations are called from the function keys – a small identifying strip can be used to label each key. Operation of one of the keys calls up the appropriate procedure: these are all initially listed on the Menu screen which can be recalled at any time by pressing f8. The program is written in BASIC and is therefore slow in parts – readers will no doubt be able to suggest improvements.

The patterns available are: crosshatch; colour bars; dots; vertical lines; horizontal lines; circle (for linearity setting); red, green, blue, magenta, cyan, yellow, white and black rasters; a composite test card. The program can be saved on tape or disc.

```
20 REM TV SERVICING AID
40 REM BBC MICRO B
60 REM (C) P.E. KNIVETON 1985
100 *KEY0 MODE0:M PROCxhatch:M
110 *KEY1 MODE2:M PROCcbars:M
120 *KEY2 MODE2:M PROCdots:M
130 *KEY3 MODE0:M PROCvert:M
140 *KEY4 MODE0:M PROChoriz:M
150 *KEY5 MODE0:M PROCcircle:M
160 *KEY6 MODE5:M PROCraster:M
170 *KEY7 MODE2:M PROCcard:M
180 *KEY8 MODE7:M PROCmenu:M
190 PROCmenu
200 END
210 DEFPROCxhatch
220 CLS
230 FORY=0TO1023 STEP 64
240 MOVE0,Y
250 DRAW1279,Y
260 NEXTY
270 FORX=91TO1188 STEP 91
280 MOVEX,0
290 DRAWX,960
300 MOVE(X+2),0
310 DRAW(X+2),960
320 NEXT X
330 ENDPROC
340 DEFPROCcbars
350 CLS
360 MOVE0,1000
370 PLOT85,0,0
380 FORbar=1TO8
390 IF INT(bar/2)=bar/2 THEN colour=(8-bar)/2 ELSE
    colour=(8-bar)+INT(bar/2)
400 GCOL0, colour
410 PLOT85,(bar*160),1023
420 PLOT85,(bar*160),0
430 NEXTbar
440 VDU23,1,0;0;0;0;
450 ENDPROC
460 DEFPROCdots
470 CLS
480 FORX=91TO1188 STEP 91
490 FORY=0TO1023 STEP 64
500 MOVE X,Y
510 DRAW,Y+1
520 NEXTY
530 NEXTX
540 VDU23,1,0;0;0;0;
```

```
550 ENDPROC
560 DEFPROCvert
570 CLS
580 FORX=91TO1279 STEP 91
590 MOVEX,0
600 DRAWX,959
610 MOVE(X+2),0
620 DRAW(X+2),959
630 NEXTX
640 VDU23,1,0;0;0;0;
650 ENDPROC
660 DEFPROChoriz
670 CLS
680 FORY=0TO1023 STEP 64
690 MOVE0,Y
700 DRAW1279,Y
710 NEXTY
720 VDU23,1,0;0;0;0;
730 ENDPROC
740 DEFPROCcircle
750 CLS
760 VDU29,640;512;
770 MOVE350,0
780 FORC=0TO2.1*PI STEP 0.05
790 PLOT5,350*COSC,350*SINC
800 PLOT5,352*COSC,352*SINC
810 NEXTC
820 VDU23,1,0;0;0;0;
830 ENDPROC
840 DEFPROCraster
850 CLS
860 IF GET$="K" THEN VDU19,0,0,0,0,0
870 IF GET$="R" THEN VDU19,0,1,0,0,0
880 IF GET$="G" THEN VDU19,0,2,0,0,0
890 IF GET$="Y" THEN VDU19,0,3,0,0,0
900 IF GET$="B" THEN VDU19,0,4,0,0,0
910 IF GET$="M" THEN VDU19,0,5,0,0,0
920 IF GET$="C" THEN VDU19,0,6,0,0,0
930 IF GET$="W" THEN VDU19,0,7,0,0,0
940 IF GET$="E" THEN GOTO960
950 GOTO860
960 VDU19,0,0,0,0,0
970 ENDPROC
980 DEFPROCmenu
990 CLS
1000 PRINT TAB(9,2);CHR$(141);CHR$(130);"TV
    SERVICING AID"
1010 PRINT TAB(9,3);CHR$(141);CHR$(130);"TV
    SERVICING AID"
1020 PRINT CHR$(129);CHR$(157);CHR$(135);"f0";
    CHR$(156);CHR$(135);"Crosshatch"
1030 PRINT
1040 PRINT CHR$(129);CHR$(157);CHR$(135);"f1";
    CHR$(156);CHR$(135);"Colour bars"
1050 PRINT
1060 PRINT CHR$(129);CHR$(157);CHR$(135);"f2";
    CHR$(156);CHR$(135);"Dot pattern"
1070 PRINT
1080 PRINT CHR$(129);CHR$(157);CHR$(135);"f3";
    CHR$(156);CHR$(135);"Vertical lines"
1090 PRINT
1100 PRINT CHR$(129);CHR$(157);CHR$(135);"f4";
    CHR$(156);CHR$(135);"Horizontal lines"
1110 PRINT
1120 PRINT CHR$(129);CHR$(157);CHR$(135);"f5";
    CHR$(156);CHR$(135);"Circle"
```

1130 PRINT
 1140 PRINT CHR\$(129);CHR\$(157);CHR\$(135);"f6";
 CHR\$(156);CHR\$(135);"Raster"
 1150 PRINT TAB(9);"(Press R for Red, G for Green,"
 1160 PRINT TAB(10);"B for Blue, C for Cyan,"
 1170 PRINT TAB(10);"M for Magenta, Y for Yellow,"
 1180 PRINT TAB(10);"E to ESCAPE raster routine)"
 1190 PRINT
 1200 PRINT CHR\$(129);CHR\$(157);CHR\$(135);"f7";
 CHR\$(156);CHR\$(135);"Test card"
 1210 PRINT
 1220 PRINT CHR\$(129);CHR\$(157);CHR\$(135);"f8";
 CHR\$(156);CHR\$(129);"RETURN TO THIS MENU"
 1230 VDU23,1,0;0;0;0;
 1240 ENDPROC
 1250 DEFPROCcard
 1260 CLS
 1270 FOR Y=0 TO 1023 STEP 64
 1280 MOVE0,Y
 1290 DRAW1279,Y
 1300 NEXT Y
 1310 FOR X=91 TO 1188 STEP 91
 1320 MOVEX,0
 1330 DRAWX,960
 1340 NEXT X
 1350 COLOUR 132
 1360 PRINT TAB(8,28);"
 1370 PRINT TAB(8,29);"TSA1"
 1380 PRINT TAB(8,30);"
 1390 PRINT TAB(0,0)
 1400 VDU29,640;512;
 1410 GCOL0,0
 1420 MOVE0,0
 1430 MOVE0,1
 1440 FOR D=0 TO 2.1*PI STEP 0.1
 1450 PLOT4,0,0
 1460 PLOT85,315*COSD,315*SIND

1470 NEXT D
 1480 MOVE320,0
 1490 GCOL0,7
 1500 FOR C=0 TO 2.1*PI STEP 0,02
 1510 PLOT5,320*COSC,320*SINC
 1520 NEXT C
 1530 MOVE0,0
 1540 MOVE309,75
 1550 FOR F=0.24 TO 3.0 STEP 0.1
 1560 PLOT85,309*COSF,309*SINF
 1570 PLOT85,0,0
 1580 NEXT F
 1590 MOVE-100,0
 1600 MOVE-100,-201
 1610 PLOT85,100,0
 1620 PLOT85,100,-201
 1630 GCOL0,0
 1640 MOVE-100,0
 1650 MOVE-100,201
 1660 PLOT85,100,0
 1670 PLOT85,100,201
 1680 GCOL0,7
 1690 MOVE-60,0
 1700 DRAW-60,303
 1710 MOVE-300,-75
 1720 MOVE-300,75
 1730 L=-225
 1740 FOR J=1 TO 8
 1750 IF INT(J/2)=J/2 THEN B=(8-J)/2 ELSE
 B=(8-J)+INT(J/2)
 1760 GCOL0,B
 1770 PLOT85,L,-75
 1780 PLOT85,L,75
 1790 L=L+75
 1800 NEXT J
 1810 VDU23,1,0;0;0;0;
 1820 ENDPROC

CAPACITORS 91 5 x .0047/1500 AB23 Chassis 1.50 92 10 x 220MFD 16V Elect 0.50 93 10 x .047MFD 400V Mul Pol 0.50 94 5 x 4.7/100V C514 T3500 1.25 95 5 x .47/1000 Dubilier 3.00 97 10 x 0.1/2000V W/E 2.00 98 5 x 1/250 Supp IIT etc. 1.50 EHT TRAYS 50 IIT CVC 5/9 3.00 51 Decca 1730/1830 5.00 52 Decca 80 Series 4.50 53 GEC 2040 Hybrid 3.00 54 T1500 5 Stick 3.50 55 Thorn 9000 7.00 56 Thorn 1400 2.00 57 Philips G9 3.50 58 Universal IIT Type 4.50 59 5 x TV11 EHT Rec for PTV's 1.00 60 3 x TV45 EHT Rec Z718 1.00 61 IIT CVC 45 4.00 63 RRI Z179 3.00 64 Pye 691/697 3.50 65 Pye CT200 4 Lead 3.50 66 Pye CT200 5 Lead 4.50 67 Korting 90 DGR Hyb 5.00	68 Grundig 3010/1500 3.00 69 Thorn 3500 7.50 70 Thorn 8500 5.40 71 Philips G8 6.30 72 Pye 731 4.50 89 10 x Anti Track EHT Cap 2.00 INTEGRATED CIRCUITS 140 5 x TDA440 3.00 141 5 x TBA120AS 1.80 142 5 x TBA540 4.00 143 5 x TBA540Q 4.00 145 5 x TBA560 3.50 146 5 x TBA810S 3.00 147 5 x TBA920Q 4.50 148 5 x TBA930 3.25 149 5 x TBA520Q 4.00 150 5 x TBA530 4.25 151 5 x TBA960 4.50 154 10 x TCA270S0 4.00 155 5 x MC1327Q 2.50 160 TDA1170 1.35 161 TDA1190 1.90 162 TDA1006A 1.45 164 TDA1035 1.83 165 TDA1044 2.23 166 TDA1190 1.90 167 TDA1412 0.90 172 TDA2002 1.80 173 TDA2020 2.50 174 TDA2030 2.15 178 TDA2523 2.35	179 TDA2532 2.40 180 TDA2540 1.85 181 TDA2541 2.67 182 TDA2560 3.28 183 TDA2571 2.15 184 TDA2591 0.98 185 TDA2593 2.23 190 TDA2600 4.00 191 TDA2611 1.24 192 TDA2640 2.35 210 ETR6016 2.28 211 ETR6016 2.28 212 BT6018 2.28 220 SL9018 Int Circuit 5.00 LINE OUTPUT TX 001 Philips G8 7.50 002 Decca 30 Series 7.00 003 Decca 100 Series 6.50 004 IIT CVC 25/30/32 7.00 005 Philips G9 7.50 006 RRI T20 9.92 007 RRI A823 7.00 008 RRI Z718 18" 18.95 009 RRI Z718 20/22/26" 18.95 010 RRI A774 Mono 10.87 011 Thorn 1690/91 7.00 012 Thorn 1615 6.50 013 IIT CVC 45 6.50 014 Phil TX Chass. 5.00 015 RRI Ranger 1/2 5.00 016 IIT CVC 5/9 8.50 017 Philips E2 Chass. 5.00 018 Thorn 9000 12.00 019 Thorn 9500/9600 8.50 020 Polish 161 Mono 6.00 021 Thorn 3500 Scant 4.50 022 Thorn 8500 11.00 023 Thorn 1590/91 8.50 024 Thorn 1500 15KV 4.00 025 GEC 2040/2100 Hybrid CTV 4.00 026 Bush 161 Mono 5.00 027 GEC Single Std Mono 5.00 028 Pye 691 (wired) 5.00	030 GEC 2100 Hybrid 4.00 032 Thorn T x 9 Chass. 14.50 033 Philips KT3 8.00 034 RRI T24 Chass. 14.00 035 Sanyo CTP5101 9.50 037 Split Diode EHT Lead 1.35 PUSH BUTTON UNITS 110 Pye 713 4 Way 7.87 111 Pye 715 6 Way 11.95 112 Phil G8 Square 12.75 113 Phil G8 Sloping 14.98 114 Thorn 9000 2.50 115 Thorn 1615 4 Way 7.87 116 Decca 6 Way 6.95 117 Decca 4 Way 6.50 118 GEC 2110 6 Way 7.95 119 GEC 2136/7 Tapered 7.95 120 IIT CVC5 9.25 121 IIT CVC8 11.45 122 IIT 6 Way with V.C.R. 7.95 123 RRI A823 etc. 7.95 124 Hitachi 4 Way 7.95 125 RRI T20 6 Way 8.95 SMOOTHING CAPACITORS 80 220/400 CVC32/T20 1.20 81 200+300 Pye 691 2.00 82 600/300 Phil G8 1.90 83 175+100+100 T3500 1.50 84 2000/100 Volt 0.50 85 470 Mfd G11 1.50 86 400+400 Decca 30 2.50 87 200+200+75+25 IIT CVC5/9 1.50 88 400/400V Tho 9000 1.50 89 470/25 Thorn 1590/ 91 1.50 90 0.80	SPECIFIC COMPONENTS 351 Thorn 1591 Speaker 2.00 352 Thorn 1600 Dropper 0.50 353 T x 10 Preset Drawer 3.00 354 T x 10 CRT Base Assy 4.00 355 3" Round BR Speaker 1.00 358 5 x Tho/3500 200 Conv. Pot. 1.00 359 5 x Tho/3500 50R Conv. Pot. 1.00 114 Thorn 9000 360 5 x TCE3500 A1 Rectifier 0.75 362 19000 Rem. Receive Assy 5.00 363 T3500 Mains TX 5.00 364 T8500 Mains TX 7.50 365 T8500 (PLastic) Cut Out 1.50 370 Pye 731 Thick Film Resis. 1.50 371 Pye 713/731 Vis. Gain Mod. 6.50 372 Pye 731 3R3 50V Metal cld. 1.29 373 100Kx3 Drawer P'set Alt Pye 731 2.00 378 Grundig 5010/6010 Vid Mod. 4.00 384 5 x 10R Phil. G8 Conv. Pot. 2.40 385 5 x 15R Phil. G8 Conv. Pot. 2.40 386 5 x Phil. G8 2kx2 Lin. Bright. 2.50 387 5 x Phil. G8 10k Log. Colour 2.50 388 5 x Phil. G8 47k Log. Vol. 2.50 389 G8 Plastic Mains Switch 0.75	390 G8 Metal Mains Switch 1.23 391 G8 Line Stor/Eql. Coil 2.25 392 G8 R/G Symetry Coil 3.33 397 20 x 3.15A A/S 20mm Fuse 1.50 398 20 x 800MA A/S 20mm Fuse 1.50 399 20 x 2.5A A/S 20mm Fuse 1.40 401 20 x 1A A/S 20mm Fuse 1.40 402 20 x 1.25A A/S 20mm Fuse 1.40 403 5 x RRI T20 Tube Base 4.35 410 Phil. G11 E/W Load/ Coil 1.50 411 Phil. G11 Bridge TX 1.50 412 Phillips G11 Speaker 1.50 413 10 x TDA2600 IC Holder 1.50 415 PALKT3 Speaker 1.50 435 10 x Decca 30 10R Fusible 0.50 436 5 x Decca 30 3R9 Modulohm 1.75 437 Decca 30 47k Vol.+Switch 1.25 453 5 x 5R Universal Conv. Pot. 1.00 454 5 x 20R Universal Conv. Pot. 1.00 455 5 x 100R Universal Conv. Pot. 1.00 456 5 x 470R Universal Conv. Pot. 1.00 457 10 x 100k Tun/Pres TCE etc. 3.00 458 10 x 100k Tuner Pre- set G8 3.00 459 ELC1043/05 Tuner 6.00	460 ELC1043/06 Tuner 6.00 461 U321 New Tuner 7.95 462 U322 New Tuner 7.95 463 98003 Posister 0.99 464 98009 Posister 0.99 465 Mull.DL50 Delay Line 0.95 466 5 x VA1104 2.70 469 Cut Out Metal GEC 2100 1.00 470 5 x GEC2100 3 Leg Thermist. 1.00 479 5 x Gen. Purp. Rotary Switch 3.50 480 5 x Gen. Purp.Push/ Switch. 3.75 481 20 x Neons GEC etc. 2.25 482 5 x Univ. Aerial Skt Kit 5.50 483 10 x Metal Coax Plug 1.70 484 Focus Unit T20 Type 1.25 485 Foc/Unit Thorn 8500 Type 1.25 486 4.43Mhz Crystal 0.40 488 10 x Ring Type Spk/ Gap 1.50 496 TX10 Chass. Focus Unit 7.00 497 De-Soldering Pump 3.50 498 1 x 10 Trimming Tool 1.00 TRANSISTOR/DIODES 230 10 x AC128 1.50 235 50 x BC213L 2.50 250 10 x BD124 9.00 251 10 x BD131 1.60 270 10 x BU208A 8.50 271 10 x BU208 7.50 272 10 x BU326 10.00 273 5 x BU205 3.75 280 25 x 2N3055 (Texas) 7.50 281 10 x 2N2905 (Equiv. BC161/303) 0.50 290 10 x BT106 Thyristor 9.00 292 5 x BT119 4.50 293 5 x BT120 4.50 335 50 x BV127 Diodes 3.00 340 25 x TIP41A 6.50 341 25 x TIP41C 7.00
--	--	---	--	--	--	--

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.

Please add 15% VAT and 90p P & P

QUICK SAVE T.V. SPARES

MUXTON HOUSE, MUXTON, TELFORD, SALOP.
 REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

BEOVISION 4000 CHASSIS

The problem is fluctuating h.t. It will steady if the voltage is reduced to below 150V by using the h.t. preset.

A common cause of this problem is failure of one of the two 56k Ω resistors 6R29 and 6R30 in the thyristor's trigger pulse generator circuit. They tend to go high in value. If necessary go on to check 6C20 (47 μ F), 6R27 (1 Ω) and the setting of the current limiter trip preset 6R33. We've also known leakage in the 39V zener diode 6D19 in the excess current sensing circuit to cause this fault.

WAX-SEALED CORES

I've been trying to convert a foreign Hitachi portable (Model 1A-51) for use in the UK. 6MHz coils have been fitted but there's still a buzz present. Hitachi have suggested tuning T401 and T402 for best sound but the cores are fixed with hard wax.

We've found that the most effective way to deal with waxed-up cores is to invert the chassis and gently heat the relevant can, using a hairdryer, until the wax runs out. The cores should then be movable after applying a couple of drops from a commercial ear-drop preparation. Tune carefully for minimum buzz on a vision with teletext or similar transmission with lots of hard white captions.

BUSH BC6004

The trouble with this Saba manufactured 14in. colour portable is that the chopper/line output transistor (Wessel circuit) lasts for only a few weeks. We've replaced the damping components C841/R841 and have made thorough checks but have been unable to find anything amiss. To start with the transistor would last for about three months: now it's down to a few weeks.

On past experience we'd suggest replacing D687 (SKE4F1/10) which is in series with the line scan circuit, the efficiency diode D688 (BY223) and the flyback tuning capacitor C688 (0.0013 μ F), also R941 (100k Ω , 1.5W) which biases the base of the driver transistor. In addition, check thoroughly for dry-joints and similar "physical" faults.

DECCA 10 SERIES CHASSIS

The colour control has to be turned by at least three-quarters of its travel before there's any colour. The colours are otherwise all right, but surely the control shouldn't operate like this?

This effect is not uncommon on some Decca 10 series sets. There may however be some lack of chroma gain. If there's any sign of Hanover bars, check the setting and condition of the controls in the chroma delay line

matrixing circuit – VR267 and L206. If the matrixing is all right, check the following components in the order given: the second chroma amplifier transistor's emitter decoupling capacitor C230 (5 μ F), the a.c.c. reservoir capacitor C222 (5 μ F) and the chroma delay line driver transistor's emitter resistor R268 (82 Ω).

SONY C5

The trouble with this machine is failure to record sound off-air. There's sound with playback of prerecorded tapes. I understand that this is not uncommon.

On every occasion when we've encountered this fault the cause has been the TBA120U intercarrier sound i.c. If replacing it fails to restore the sound an oscilloscope will be necessary to check and trace the signal.

RANK T20 CHASSIS

There's ringing on the left-hand side of the screen, similar to the effect that occurs when a line linearity coil's damping resistor goes open-circuit. Adjusting the fifth harmonic tuning coil has reduced the vertical bands considerably but they are still noticeable.

We assume that you've checked the line linearity coil's damping resistor 5R12 (680 Ω). If not, check this, the EW correction coupling capacitor 5C15 (1 μ F) and if necessary 5C16 (0.068 μ F) in the first anode supply network. For reliability, it's important that the fifth harmonic tuning coil 5L3 is correctly adjusted as per the manual. If replacing the above mentioned components fails to clear the fault and 5L3 cannot be set up correctly it's likely that the line output transformer is defective.

THORN 1690 CHASSIS

The original problem with this set was caused by a faulty line output transformer. When this was replaced the picture was found to be greatly expanded in the middle. The height control will correct the top and bottom of the picture but the linearity control has very little effect. I've checked the electrolytics and transistors in the field amplifier/driver/output stages.

The field waveform is generated across C104 (0.047 μ F). Check this item and the associated charging resistor R128 (330k Ω). The next suspects are the 390 Ω resistors R133/4 which bias the emitters of the driver transistors. They can and do change value. This is also true of R132 (27k Ω), the amplifier transistor's load resistor.

SONY SLC7 VCR

After fitting a Sony chopper power supply replacement kit and a new control i.c. the machine came to life for five seconds then went dead again. On investigation the chopper transistors, the surge limiter resistor and the mains fuse had failed. With a replacement fuse the readings on the control i.c., powered via the start-up supply, were found to be correct – apart from the pins linked to the chopper supply output of course. Any suggestions before a second replacement kit is fitted?

The operation of the control i.c. can be checked by disconnecting D204 (soft-start control circuit) and applying an external source of 12V to C203. A 3V sawtooth should then be seen at pin 5 of the i.c. (TP1) and a 20V p-p squarewave at pins 8 and 11. If these waveforms are o.k., the rectifier diodes D201/2 and the 4.7 μ F electrolytics C110/1 are in order, and no excessive loading is present on the 12V line, suspect short-circuit turns in the chopper transformer T102 – it can happen.

DECCA 30 SERIES CHASSIS

The problem is intermittent horizontal bands across the screen. They are about half an inch wide and comprise six scanning lines, the first two lines being quite dark while the rest are progressively less intense.

This sort of thing can be caused by discharges inside the focus spark gap. Try replacing it – also check the earthing connections between the tube's outer coating and the base panel, thence to chassis.

TEST CASE

271

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

It's generally acknowledged that Bang and Olufsen TV sets have always had the edge over the competition in terms of picture and sound quality. Their reliability has not always been of the best however, and early solid-state chassis from this stable are no strangers in our workshop. No matter what the source, many of the faults that arise in these sets result in a "pumping" action in the power supply as a result of one or other of the protection circuits coming into operation. This month's story is about one such Beopump . . .

The set was a Beovision 6002 (type 3522-3532) with a beautiful rosewood cabinet – and a complete lack of raster and sound. A gentle pumping sound at a rate of about once per second came from within it. Some quick preliminary checks showed that no obvious short-circuits were present in the line output stage while the h.t. line, which should record 148V at 6TP2, was pulsing to about 100V on each pump cycle. A scope check at 5R18 (18Ω) which is in series with the 148V h.t. line produced a waveform with an amplitude of about 16V, about twice what's normal, indicating that excessive current was flowing in the line output stage.

It didn't take long to unload the various power supplies derived from the line output transformer: 6D9, which produces a 37V supply for the field timebase and the EW modulator drive circuit, was found to be heavily burdened – its removal brought the set to life, albeit with no field scan. We decided to check the field timebase module, 8003200, where a dead short to chassis was found at the supply input point – P19-5. A few more minutes investigation showed that the TDA1270 field timebase chip 71C1 was the culprit – pin 2 was solidly shorted to the heatsink tabs.

After fitting a new chip we confidently replaced the module and switched the set on. No pumping – but no field scan either! In the next twenty minutes we had the

module in and out several times while we checked the output transistors, their joints, the module socket connections and so on. Then we got sensible and reasoned that if there was no field scan activity the white line on the screen would fade within seconds of switching on – which it didn't – due to lack of gating pulses in the auto grey-scale shift circuit. Sure enough a scope check at the i.c.'s output pin 4 produced a 50Hz waveform which was also found to be present at the emitters of the output transistors 7TR2/3. The waveform wasn't the usual "spiked-sawtooth" however: it was virtually a squarewave with a peak-to-peak amplitude of almost 40V. At this point experienced TV trouble-shooters will be leaping up and down with the correct answer. Are you amongst them? If so, what's the accompanying symptom that sometimes gives a further clue to the cause of the trouble? For the answer to both these questions, see next month . . .

ANSWER TO TEST CASE 270 – page 456 last month –

In our last "tableau" we were huddled around a Philips colour set fitted with the G8 chassis. Its problem was an intermittent red raster that occurred only spasmodically and only when the set had thoroughly warmed up. Various substitution checks had been made in the field and the set was now on the workshop bench for investigation.

The simple and effective way to deal with this situation is to interchange the video drive between the suspect channel (red in this case) and a known good one. So the red and green leads to the tube base were swapped over and the resulting strange colours were suppressed by turning the saturation control to zero. When the fault next occurred the monochrome picture became suffused with red, and since the red gun was now being driven by the green channel this implied that the tube was faulty.

So it turned out to be, though exactly what was happening within the tube was not clear. Any interelectrode short involving the red control grid would have elevated all three grids to a high potential and turned on all three guns. We suspect that the red grid connection to pin 3 was going open-circuit intermittently, though this is very uncommon with the type of Mullard tube used.

No, the customer didn't have a new tube fitted – and we didn't get a bean for all our efforts!

QUERY COUPON

Available until 17th July 1985. One coupon, plus a £1.50 (inc. VAT) cheque or postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 518.

TELEVISION JULY 1985

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £13, overseas (surface mail) £15 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

AA117 9p	BC337 6p	BF184 20p	BFV57 25p	TIP32A 24p	ZN 1131 28p	BY296 20p	7818 35p	PCL805 55p	LA-4461 180p	TBA560 100p	74LS22 24p
AA119 9p	BC338 6p	BF185 20p	BFV64 25p	TIP32C 28p	ZN 1132 28p	BY298 28p	7824 35p	PFL200 85p	LA-5112 120p	TBA750 100p	74LS24 47p
AA132 9p	BC357 6p	BF194 5p	BFV90 45p	TIP33 28p	ZN 1133 28p	BY299 28p	7905 35p	PL36 80p	LM301 26p	TBA800 35p	74LS26 24p
AC107 28p	BCY32 150p	BF195 5p	BLV48 85p	TIP34 50p	ZN 1711 24p	BY476 90p	7912 40p	PLB2 45p	LM311 35p	TBA105 60p	74LS27 24p
AC126 15p	BCY33 150p	BF196 5p	BLV48 85p	TIP34 50p	ZN 1712 24p	BY477 90p	7915 40p	PLB3 45p	LM312 35p	TBA110 60p	74LS28 24p
AC127 15p	BCY34 150p	BF197 5p	BR100 14p	TIP41C 22p	ZN 2160 300p	BYX5750 30p	7918 40p	PLB4 50p	LM324 35p	TBA20 100p	74LS28 24p
AC128 25p	BCY42 150p	BF198 7p	BR101 43p	TIP42A 22p	ZN 2218A 24p	BYX5600 30p	7924 40p	PLB5 140p	LM325 45p	TBA50 100p	74LS30 24p
AC128K 23p	BCY56 16p	BF199 6p	BR103 37p	TIP42C 22p	ZN 2219 24p	BYX5700 30p	78L05 28p	PL500 110p	LM326 45p	TBA90 100p	74LS32 24p
AC141K 11p	BD124 15p	BF240 16p	BSX20 11p	TIP120 40p	ZN 2262 22p	BYX7000 30p	78L12 28p	PL504 20p	LM348 60p	TBA200 100p	74LS33 28p
AC142K 30p	BCY70 16p	BF241 10p	BSX26 18p	TIP48 40p	ZN 2262 23p	BYX7050 32p	78L15 28p	PL508 170p	LM380 100p	TCA800 200p	74LS37 24p
AC153K 23p	BCY72 16p	BF242 10p	BSX29 19p	TIP50 40p	ZN 2389 15p	BYX7080 36p	78L18 28p	PL519 450p	LM381 150p	TCA900 100p	74LS38 24p
AC176 18p	BD115 26p	BF255 12p	BT106 90p	TIP51 120p	ZN 2484 20p	BYX7600 80p	78L24 28p	PV81 70p	LM382 130p	TD1170 100p	74LS40 24p
AC176K 20p	BD124 15p	BF256 12p	BT105 85p	TIP120 40p	ZN 2504 35p	O447 15p	78L25 40p	PV83 45p	LM383 100p	TD1172 100p	74LS42 48p
AC187 15p	BD131 25p	BF259 18p	BT116 80p	TIP53 120p	ZN 2904 20p	OAS0 40p	78L25 40p	PV500A 100p	LM389 40p	TD2002 80p	74LS47 78p
AC187K 20p	BD128 25p	BF262 25p	BT119 100p	TIP54 140p	ZN 2905 20p	OAS1 40p	78L25 40p	AN-214P 200p	LM389 40p	TD2003 150p	74LS48 78p
AC188 17p	BD131 25p	BF262 25p	BT120 100p	TIP105 65p	ZN 2906 18p	OAS20 7p	78L25 40p	AN-240P 150p	LM382 130p	TD2020 140p	74LS51 24p
AC188K 20p	BD136 25p	BF262 25p	BT120 100p	TIP106 65p	ZN 2907 18p	OA200 7p	78L25 40p	AN-240P 150p	LM387 100p	TD2020 140p	74LS52 48p
ACY18 48p	BD132 25p	BF262 25p	BU104 100p	TIP107 65p	ZN 2926 8p	IN 914 2p	78L25 40p	AN-300 120p	LM387 100p	TD2020 140p	74LS52 48p
ACY19 48p	BD136 25p	BF262 25p	BU105 80p	TIP110 47p	ZN 2929 8p	IN 4001 4p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AD142 60p	BD137 20p	BF273 15p	BU108 100p	TIP111 60p	ZN 3053 18p	IN 4002 4p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AD149 45p	BD138 20p	BF311 21p	BU111 140p	TIP115 45p	ZN 3054 35p	IN 4004 4p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AD162 22p	BD139 20p	BF324 25p	BU124 60p	TIP116 45p	ZN 3055 35p	IN 4005 4p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AF124 25p	BD144 90p	BF337 20p	BU126 70p	TIP117 60p	ZN 3440 58p	IN 4006 4p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AF125 25p	BD150 30p	BF338 20p	BU204 75p	TIP120 43p	ZN 3442 85p	IN 4007 4p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AF126 25p	BD157 38p	BF355 28p	BU205 75p	TIP121 43p	ZN 3702 4p	IN 4144 8p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AF127 25p	BD166 30p	BF367 13p	BU208 75p	TIP122 47p	ZN 3703 9p	IN 5400 9p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AF139 22p	BD175 30p	BF371 13p	BU208A 80p	TIP125 47p	ZN 3704 9p	IN 5401 10p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AF239 22p	BD181 30p	BF414 18p	BU208B 100p	TIP126 50p	ZN 3705 9p	IN 5402 10p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AL112 40p	BD170 30p	BF414 18p	BU209 100p	TIP127 50p	ZN 3706 9p	IN 5403 10p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AL113 40p	BD170 30p	BF414 18p	BU209 100p	TIP127 50p	ZN 3706 9p	IN 5403 10p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AS215 100p	BD181 45p	BF421 18p	BU209 100p	TIP142 90p	ZN 3707 9p	IN 5404 11p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AS217 100p	BD182 60p	BF422 21p	BU209 100p	TIP145 90p	ZN 3771 85p	IN 5405 12p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AY102 110p	BD183 60p	BF423 21p	BU209 100p	TIP145 90p	ZN 3772 85p	IN 5406 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
AY106 180p	BD183 60p	BF423 21p	BU209 100p	TIP145 90p	ZN 3772 85p	IN 5406 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BA145 10p	BD202 38p	BF455 14p	BU407 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BA148 10p	BD203 42p	BF458 16p	BU408 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BA154 6p	BD244 42p	BF459 19p	BU409 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BA157 12p	BD252 31p	BF461 60p	BU409 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BB101 13p	BD225 31p	BF462 62p	BU409 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BB103 18p	BD232 31p	BF469 30p	BU409 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BB105B 18p	BD234 42p	BF469 30p	BU409 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BB205B 24p	BD235 28p	BF471 28p	BU409 95p	TIP305 42p	ZN 3819 29p	IN 5407 13p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC107 7p	BD236 30p	BF479 30p	C106D 23p	VK1010 88p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC108 7p	BD237 21p	BF493 18p	MJ2501 100p	VN 10KM 60p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC109 7p	BD238 24p	BF494 16p	MJ2501 110p	VN 46AF 85p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC115 10p	BD244 50p	BF595 18p	MJ2955 55p	VN 66AF 100p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC118 11p	BD245 50p	BF596 16p	MJ3001 115p	VN 89AF 110p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC140 19p	BD433 28p	BF597 10p	MJ3001 115p	VN 89AF 110p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC141 19p	BD434 30p	BF615 30p	MJ3001 115p	VN 89AF 110p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC142 19p	BD435 31p	BF758 42p	MJE29A 30p	ZTX108 11p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC143 19p	BD437 28p	BF869 22p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC147 6p	BD438 36p	BF870 22p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC148 6p	BD439 40p	BF872 23p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC149 6p	BD440 38p	BF873 23p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC157 6p	BD441 40p	BF963 40p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC159 6p	BD442 40p	BF964 38p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC182 6p	BD533 50p	BF966 38p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC182K 6p	BD534 38p	BF940 25p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC183 6p	BD535 38p	BF951 21p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC183K 6p	BD536 38p	BF962 21p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC184 6p	BD537 40p	BF979 25p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC184K 6p	BD538 40p	BF980 25p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC212 6p	BD675 40p	BF991 59p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC212K 6p	BD676 40p	BF992 59p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC213 6p	BD677 38p	BF984 20p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC213K 6p	BD678 38p	BF985 20p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310 140p	LM387 100p	TD2020 140p	74LS52 48p
BC214 6p	BD679 40p	BF987 15p	MJE30A 30p	ZTX109 12p	ZN 4443 78p	2N 4443 78p	78L25 40p	AN-310			

MANTEL

No 1 for Quality TVs & Videos
100s of V.H.S. Videos in stock

Large Quantities of Late Model Thorn TVs. All
with first class cabinets.

TELE-TEXT/ULTRASONIC/INFRARED/REMOTES
All at UNBEATABLE PRICES for QUANTITY & QUALITY

Also Philips G11/Pye G11/Basic/Remote/TELE-TEXT

Some examples of QUALITY working TVs

THORN 8800 ***** £25
THORN 8800(remote) ***** £30
THORN 9000 ***** £30
THORN 9000(remote) ***** £35
THORN 9600 ***** £40
THORN 9600(full feature remote) *** £45

THORN 9600 TELETEXT from £75
(VARIOUS MODELS)
THORN 9900 ***** £50
THORN 9900 f/f remote ***** £60
PHILIPS G11 ***** £55

(prices quoted are based on quantity)

NO DEALER TOO LARGE OR SMALL. SINGLES SOLD

**Brand New Remote Control Hand Sets Available for the
majority of British & European TV sets.**

1000s of UNTESTED Colour TVs

I.E. DECCA 30s
GEC 2110
GRUNDIG
TANBERGS

G8s 520s-550s
Thorn 3500/8000/8500
TT
PYE, ETC.

(Many of these untested TVs just switch on)

ALL AT LOW LOW PRICES

VAN LOADS DELIVERED DIRECT FROM SOURCE
RING FOR QUOTE

New TV Trolley Stands **£4.95** Also Video Stands **POA**
Colour TV panels & tubes available

All prices subject to V.A.T.

CALLERS WELCOME

Export Orders Welcome for those Countries using the P.A.L. System

**419 BARLOW MOOR ROAD,
CHORLTON, MANCHESTER M21 2ER.**

TEL: 061-861 8501

TRAINING COURSES

TELEVISION & VIDEO SERVICING

THESE FULL-TIME COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

VIDEO CASSETTE RECORDER SERVICING 6 WEEKS FULL-TIME (September 16th to October 25th)

Intensive course intended for qualified television service engineers or applicants with similar background.

The course combines the advantages of industrial and academic training and includes a high percentage of practical work.

Selected applicants will be eligible for a full grant from MSC under TOPS to cover tuition fees and maintenance.

**6 MONTHS
LEC DIPLOMA
TELEVISION & VIDEO SERVICING**
(Suitable for applicants with previous electronics training - e.g. BSC, HND, CGLI, B/TEC, etc.)
(Course commences on Sept. 16th)

**ADDITIONAL FULL-TIME COURSES
APPROVED BY THE BUSINESS &
TECHNICIAN EDUCATION COUNCIL**
(These courses commence on Sept. 16th)

**2 YEAR
BTEC National Diploma (OND)
ELECTRONIC &
COMMUNICATIONS ENGINEERING**
(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

**15 MONTHS
BTEC National Certificate (ONC)
ELECTRONIC EQUIPMENT SERVICING**
(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

**15 MONTHS
BTEC National Certificate (ONC)
COMPUTING TECHNOLOGY**
(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

**9 MONTHS
BTEC Higher National Certificate (HNC)
COMPUTING TECHNOLOGY & ROBOTICS**
(Microprocessors, Microcomputer Fault Diagnosis, Robotics & Control Systems, CAD/CAM & CAE Principles)

OVERSEAS STUDENTS ARE CHARGED THE SAME TUITION FEES AS UK STUDENTS

Full Prospectus from:

**LONDON ELECTRONICS COLLEGE (Dept TF)
20 PENYWERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-373 8721**

D.I.Y. TV TUBE POLISHING

with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25* tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £49 inc P&P and VAT. Available from Luton only.
*Depends on depth and area to be polished.

AQUADAG COATING £17.25 per litre inc P&P and VAT. Sufficient for approx 100 tubes.
Available from Luton only.

TV TUBES FREE DELIVERY*

5% DISCOUNT ON TUBES COLLECTED FROM LUTON
Quality, High Temperature Reprocessing

TUBE SIZE	DELTA i.e. A51-110X A56-120X A66-120X	DELTA SPECIALS i.e. 510GLB22 A47-342X A67-150X	JN LINE & PIL i.e. A51-161X A51-570X A56-510X A66-510X	HITACHI IN LINE i.e. 490DVB22 510VLB22 560DZB22	SONY TRINITRON
UP TO 20"	£30	£32	£40	£44	£58
UP TO 22"	£34	£36	£42	£46	£64
UP TO 26"	£36	£38	£44	£48	£70

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee.

All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. From £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 or 2 tubes £6. 3 or more tubes FREE DELIVERY*

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-1pm. Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

Retach Ltd., Northwood, Middx. Tel. 09274 27019.

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.

Tel. 024 06 3609

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901

Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562

WANTED A56/A66-510X/540X Old glass for cash

VIDEO HEADS MONOLITH

electronic products

HIGH QUALITY UNIVERSAL VIDEO HEAD
REPLACEMENTS FOR ALL VHS AND BETAMAX
VCR MACHINES

VHS Part No. 3HSS (5mm Centre Hole) £29.95 PRICE

VHS Part No. 4HSS (15mm Centre Hole) £29.95 EACH

BETAMAX Part No. PS3B £38.95 EX.

REPLACEMENT KIT (17 Pieces Boxed) £17.35 V.A.T.

PLEASE ADD 15% V.A.T. PLUS P&P £2.00 PER ORDER

OUR FULL CATALOGUE AVAILABLE ON REQUEST.

Please allow between 14 and 28 days for delivery.

AUDIO + VIDEO HEADS - MOTORS - PARTS

Suppliers to most U.K. Distributors/Service Organizations

THE MONOLITH ELECTRONICS CO. LTD

5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0460) 74321 Telex 46306 MONLTH G

TUNERS + TUNERS

- ★ If you repair sets regularly - phone us today and we will dispatch immediately - no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

T&P

32 Temple Street,
Wolverhampton WV2 4LJ.
Phone: (0902) 773122.

HITACHI VHS COLOUR CAMERAS

Mains/Mains Battery Portable

TESTED WORKING

VHS VIDEOS FERGUSON

3V00, 3V22, 3V23, 3V16, 3V29, 3V30, 3V31, 3V32, 3V35

NATIONAL PANASONIC NV8600, 8610, 2000, 7000, 370, 333, 2010

SHARP

620, 630, 640, 2300 H T/P

BETAMAX

SANYO VTC 9300, 5000, 5300

SONY C5, C6, C7, C9 and SL F1UB T/P

Also Bush, Toshiba, Hitachi and Blau Punkt

PLUS

17" 18" 20" 22" 26" Hybrid/Solid State CTVs Remote Control & Teletext

Discount for Quantities

JOHN CARTER (Electrical) LTD
FURNACE ROAD,
GALLOW'S INN,
ILKESTON

Phone: 0602 303124

OSCILLOSCOPES

COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual . . . £200
S.E. LABS SM111. Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual . . . £150
ADVANCE OS250TV Dual Trace 10MHz. With Manual . . . £150
TELEQUIPMENT S54A. Single Trace 10MHz. Solid State. With Manual . . . £110
TELEQUIPMENT D45. Dual Trace 25MHz. With Manual . . . £110
TELEQUIPMENT S43. Single Trace 25MHz. With Manual . . . £75

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester . . . £515
HAMEG OSCILLOSCOPE 203.5". Dual Trace 20MHz. Component Tester . . . £264
BLACK STAR FREQUENCY COUNTERS P&P £9
Meteor 100-100MHz . . . £99
Meteor 600-600MHz . . . £126
Meteor 1000-1GHz . . . £175
BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 . . . £110

MULTIMETERS

PHILIPS DMM2517. 4 digit. Auto ranging. Complete with batteries & leads. (Un-used) . . . £95
AVO TEST SET No 1 (Similar to Avo8 Mk3). Complete with batteries, leads & carrying case £80
AVO Model 7x Complete with batteries, leads & carrying case . . . £40
AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads . . . £25
AVO 72 - Similar to above but no AC current range. With batteries & leads . . . £18

HUNG CHANG DMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4 . . . £33.50
MULTIMETER type U4324. 33 ranges. Complete with batteries and leads. P&P £4 . . . £16

OSCILLOSCOPES PROBES. Switched x1; x10. P&P £2 . . . £11

ADVANCE AM/FM Signal Generator type SG63. 7.5-230MHz . . . £75
ADVANCE AM Signal Generator type 62. 150KHz - 220MHz . . . £35
PHILIPS WOBBULATOR GM2877S. 5 - 220MHz & 440-880MHz . . . £65
METRIX WOBBULATOR type 210. 5 - 220MHz . . . £20

UNBELIEVABLE

AVO 8 Mk V FOR ONLY £65
Complete with batteries & leads.

NOW ONLY £12 p&p £3

AVO TRANSISTOR TESTER TT169
Handheld. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions.

LABGEAR COLOUR BAR GENERATOR. CM6037 . . . £60 P&P £2
LABGEAR CROSSHATCH GENERATOR. CM6004 . . . £15 P&P £2
LABGEAR CROSSHATCH GENERATOR. CM6038. Input 240V AC or 6V DC . . . £25 P&P £2

WAYNE KERR COMPONENT BRIDGE. B521 (CT375) L 100uH - 500KHz, C 1pF - 5F, R 1 milliohm - 1000 Mohm . . . £35
HUNTS CAPACITANCE ANALYSER & RESISTANCE BRIDGE type CR3B . . . £20 P&P £7

LABGEAR UHF FIELD STRENGTH METER CM6016 . . . £50 P&P £5
LABGEAR DEGAUSSER COILS E5186 £10 P&P £3

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total of Goods & Carriage.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: 0734 68041



Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive



HIGH QUALITY COLOUR TELEVISIONS

Thorn, Phillips, GEC R/Controls, ITTs, T/Text etc., etc., etc. . . .

NEW BRAND NAMED STOCKS AVAILABLE!

Various Hi-Fi Systems . . . £55.00
Videos (Phillips 2020) . . . £35.00
Computers . . . ONLY £10.00
TELETEXT COLOUR TELEVISIONS . . . P.O.A.

LARGE RANGE OF PART EXCHANGE & EX-RENTAL COLOUR TELEVISIONS IN EXCELLENT CONDITION . . . FROM ONLY £5.00 . . .

Amplifiers (complete with Speakers) AVAILABLE NOW!!!

(P.O.A. - price on application)

EXCELLENT PRICE OFFER FOR ORDERS ABOVE 40 UNITS

COLOURTRADE

221 Bridge St West, Hockley, Birmingham 021-359 0449

**UNTESTED
EX-RENTAL CTVs
OVER 1500 WEEKLY**

WITH THIS QUANTITY WE DO NOT
HAVE TIME TO PLAY ABOUT.

NO BUMPED TUBES

BEST SOURCE IN U.K.

COLOUR TVs FROM £3

**VIDEO RECORDERS
FROM £60**

TANDBURG S/S CTVs
DUAL TUNERS IDEAL FOR
EXPORT

VIDEO RECORDERS:
SONY C5: C6: C7 & C9
PANASONIC : SHARP
FERGUSON : GRUNDIG ETC.

CALL & SEE OUR SELECTION
DELIVERY ARRANGED FOR
BULK PURCHASES
LOAD DIRECT FROM SOURCE
AT VERY KEEN PRICES

**22"/26" TELETEXT VIEWDATA
COLOUR IN STOCK NOW**

CASH ONLY

FRANK FORD
(TV TRADE DISPOSALS)
SCHOOL LANE
GUIDE
BLACKBURN, LANCS
TEL: 0254 64489

**WD-TV
100's of
WORKING
COLOUR TVs**

DECCA · PHILIPS G8 & G11
BUSH · PYE s/s · ITT · THORN
8800 9000 9600 · GEC s/s
KORTING · JAPS

PRICES FROM

£15 + VAT

Videos

Always Available

**Tested Tubes
All sizes from**

£10 + VAT

Always Scrapping Down
Decca, Philips & Thorn
– Spares Always Available

WD-TV

TV Warehouse
(former Tritel Place),
The Chestnuts,
Watling Street (A5),
Hockliffe, Bedfordshire.
(Junct. 12 M1 – 3 miles)

Tel: 0525 210768 & 210686.

HOCKLEY DISCOUNT TELEVISIONS

North-East Branch:

NORTHERN T.V. DISTRIBUTORS,
Unit 2, Perth Court,
Eleventh Avenue,
Team Valley Trading Estate,
Gateshead, Tyne & Wear
Tel. 091-487-5389
ASK FOR JOE

Midlands Branch:

HOCKLEY DISCOUNT TELEVISIONS,
94 Soho Hill,
Hockley, Birmingham B19 1AE.
Tel. 021-551-2233
ASK FOR JAZZ

NOW THE MOST RAPIDLY EXPANDING WHOLESALERS WITH
HUGE STOCKS

TO ENSURE YOU OF **BETTER BARGAINS!**

LORRY LOADS DELIVERED **DIRECT FROM SOURCE!**

PRICES START FROM £6

WORKING SETS FROM £12

100's OF G11's IN STOCK 22" & 20". VHS VIDEO'S NOW IN STOCK

UNLIMITED SELECTION OF:

PHILIPS G8's (G11 Now in Stock)
PYE SOLID STATE
PYE CHELSEA
GEC SOLID STATE, STARLINES

SONY
LATEST HITACHI
I.T.T CVC30, CVC45
BUSH T20, T22

SPECIAL OFFER ON VARICAP 6 BUTTON DECCA

* Delivery can be arranged.

SPRING SALE

BARGAIN OFFERS

10 BUSH 2 CHIP	£50
10 SALORA	£50
10 GEC SOLID STATE (WOOD CABINET)	£150
10 DECCA 6-BUTTON 20" & 22"	£120
10 REDIFFUSION MARK 1 REVAMP	£120
10 THORN 8000 17"	£150

ALSO BUSH T20, G11, 9000, 9600, 9800,
GEC STARLINES

DIRECT LOADS FROM SOURCE
RING FOR QUOTE

ALL + VAT

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154
THE NO. 1 WHOLESALER IN THE SOUTH

COMPONENT SPECIALISTS

Anything - Anywhere
Bulk Orders, Export Orders
Purchase of Excess Stock

Thousands of Components Ex-Stock

Simply phone us
0934-419147

Freeway Components, The Airport
Weston Super Mare, Avon BS24 8RA

APOLLO MANCHESTER

FAST MAIL ORDER GB 3-4 DAYS ALL AREAS PLEASE PHONE FOR COST
FREE LOCAL DELIVERY SAME DAY ● FITTING SERVICE £20

2 YR GUARANTEE - QUANTITY DISCOUNTS - PILL GLASS BOUGHT

A47 342/343X - 470 BCB22/CTB22/BGB22	£39
470-ESB22/E-B22/ERB22/FTB22	£49
A51-220X/192X	£39
A51-161X/162/163/168	£49
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£49
510-VLB22/DTB22/001/RFB22/RCB22/SFB22	£49
A51-570X/583/001/210/241	£49
A56-120X/123/140/410	£39
560-DZB22(ES3)/HB22/AKB22/TB22/AWB22	£49
560-ETB22/DTB22/CSB22/DMB22/DNB22	£49
A56-611X/615X	49
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X/510X - A66-500X/510X	£49
30AX - A56-540X - A66-540X	£53

If your tube type is not in stock we can arrange collection - rebuilding + redeliver

PLEASE PHONE BEFORE CALLING

061-799 0854. 24 hour answering service
43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL

**NEW
OFFER**

LONDON'S LARGEST
TELEVISION WHOLESALER . . .
with over 4½ thousand sq. feet.

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnal Green Road)
LONDON E2. FREE CAR PARK
Tel: 01-739 2707
01-739 3123

**NOW
AVAILABLE**

We specialise (where the other wholesalers don't) for the busy dealer who wants a clean compact parcel of six SERVICED Colour Televisions delivered to his doorstep! . . .

PS

Special FREE opening offer . . .
6 Monos Included – NO CHARGE!

**DELIVERY FREE TO THE GREATER
LONDON AREA AND A SMALL CHARGE
FOR OUTSIDE LONDON!**

**SERVICED
COLOUR
TELEVISIONS £35
EACH**

LORRY LOADS DELIVERED DIRECT FROM
SUPPLIERS – NO CHARGE FOR DELIVERY!

TELEPHONE BARRY OR JOHN

01-739 2707 → 2 LINES ← 01-739 3123

FREE CAR PARK + NO YELLOW LINES OUTSIDE!

IRISH T.V. DEALERS

(PLEASE NOTICE)

LARGE SELECTION OF RECONDITIONED PRECISION-IN-LINE UHF-VHF COLOUR TVs, SOME WITH RE-GUN TUBES FITTED, "CABINETS RESTORED TO A1 CONDITION". PRICES START @ £60.00. ALSO 20" & 22" RE-GUN TUBES IN STOCK, QUANTITY DISCOUNT, DELIVERY ARRANGED.

(EXPORT SPECIALISTS)

T.V. TRADE SALES
E.D.I. HOUSE
KYLEMORE PK. WEST
DUBLIN 10.
Tel: 01-264139

ALSO

T.V.T.S.
CLOVER PLACE
COLLEGE ST.
KILLARNEY.
Tel: 064-33655

SATELLITE RECEIVING SYSTEMS

1m and 2m Parabolic Dishes, other sizes available.

A range of other components available, eg, LNAs, Downconverters, receivers, for both 4 and 11 GHz. Complete Terminals for ECS and Intelsat, both single channel and tunable versions.

Terminals for other frequencies available.

Demonstration by appointment.

L & S Bear Electronics Ltd
Yeo Lane, Colley Lane,
Bridgwater, Somerset.

Telephone: Bridgwater (0278) 421719

TOP TWENTY VIDEO SPARES

Cassette lamp (Ferg/JVC)	£1.80	Video head (Ferg) (state model).....	£37.50
Cassette lamp (Panasonic).....	£1.80	Video head (Panasonic) (state model).....	£39.50
Take-up clutch (Ferg).....	£6.95	Head cleaning fluid.....	£1.50
Belt kit (Sony) (state model).....	£6.50	Head cleaning sticks (each).....	50p
Belt kit (Ferg) (state model).....	£6.50	Reel Drive Pulley (Sanyo VTC5000).....	£8.88
Belt kit (Panasonic) (state model).....	£6.50	Reel Motor (Sanyo VTC5000).....	£14.20
Belt kit (Sanyo 9300).....	£6.50	Reel Motor (Sharp).....	£12.96
Rewind kit (Sony C7).....	£6.95	Overhaul kit (Ferg) (state model).....	£19.95
Reel idler (Sharp VC).....	£3.45	Overhaul kit (Sony) (state model).....	£19.95
Video head (Sony C7/C5).....	£39.50	Overhaul kit (Sharp) (state model).....	£19.95

Most spares available for Hitachi, Panasonic, Sony, Sanyo, Sharp etc.
Prices on request.

TELEVIDEO SERVICES NOTTINGHAM (0602) 226070

76 Wollaton Rd., Beeston, Nottingham

Please add 50p post & packing and then add 15% VAT to total
ALL ORDERS DESPATCHED BY RETURN OF POST

Send 22p stamp for full catalogue.

TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE


Delivery by return of post.

RANK BUSH MURPHY		ITT: VC200 to VC402	9.20
A774 with stick rectifier	9.78	CVC1, CVC2 (FORGESTONE)	11.50
A816, T16, T18, Z712, Z715	10.35	CVC5, CVC7, CVC8, CVC9 series	9.20
T20, T22, T26, Z179, A823	11.50	CVC20	10.35
Z718 Basic unit	13.50	CVC25, CVC30, CVC32, CVC45	9.20
T24e, T24h split diode	P.O.A.	CVC40, CVC1200, 1210, 1215	P.O.A.
		FT110, FT111. P/no AT2063/02	11.50
DECCA: 1210, 1211, 1511	11.50	PYE: 169, 173, 569, 368 series	9.20
1700, 2001, 2020, 2401, 2404	9.20	CT200, CT200/1, CT213 series	10.35
CS1730, 1733, 1830, 1835	9.20	725-731, 735, 737, 741 Series	9.78
30, 70, 80, 90, 100, 130 Series	9.20		
FERGUSON, THORN: 1590, 1591	9.20	PHILIPS: 170, 210, 300 series	9.20
1690, 1691. built in rect.	9.78	320 series	9.78
1600, 1615, 1700 series	P.O.A.	TX, T8 mono	P.O.A.
1790 mono portable	P.O.A.	G8 and G9 Series	9.20
3000, 3500, 8000, 8500, 8800	P.O.A.	KT2, KT3. series colour	9.20
9000, 9200, 9300 series	12.00	G11. K30. split diode	P.O.A.
9500, 9600, 9650 series	10.99		
9800, TX9, TX10 series	P.O.A.	BINATONE: 9909, 9798, 9860	P.O.A.
MOVIESTAR 3781, 3787	12.00	DORIC Mk3	11.50
		FINLUX 9560, 9670	P.O.A.
FIDELITY: FTV12 mono	10.35	GRUNDIG: most models in stock	
CTV14R, CTV14S colour	15.83	NORDMENDE: FC125, Z206, Z306	11.50
		SANYO: 5101, 5103, 7118, 7130	P.O.A.
G.E.C. 2047 to 3135 mono	9.20	SHARP: C1851H, C2051H	P.O.A.
1201H, 1501H, 2114, 3133, 3135	9.20	TOSHIBA: C800, C800B	19.45
DUAL & SINGLE hybrid col.	10.00	TANDBURG: 190, CTV2-2, CTV3-3	P.O.A.
SINGLE STD solid state	12.00	TELEFUNKEN: most models in stock	
SINGLE STD split diode	P.O.A.	LINE OUTPUT TESTER	16.79
INDESIT: 24EGB hybrid	9.50		
12LGB, 12SGB mono portables	10.35		
WINDINGS			
TYNE: main winding	6.80		
RBM: T20, T22, T26, Z179	6.33		
WALTHAM: W125 eht winding	2.37		
WALTHAM: W190, W191 eht coil	£6.00		
KORTING: hybrid winding	6.90		

Tidman Mail Order Ltd.,
236 Sandycombe Road,
Richmond, Surrey.
 Approx. 1 mile from Kew Bridge.
Phone: 01-948 3702
 Mon-Fri 9 am to 12.30 pm &
 1.30-4.30 pm
 Sat 10 am to 12 noon.

REBUILT TUBES?

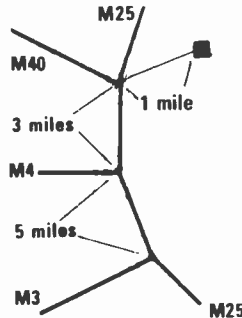Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



WE ARE LOCATED IN ◀ **UXBRIDGE**

At probably the most accessible part of S.E. England. Construction work on the Poyle/Uxbridge section of the M25 is now in progress. When completed we shall be less than 10 minutes from M3/M25 junction 2/12. M4/M25 junction 4/14. M40/M25 junction 1/15.

**LOCAL AREA MAP AND PRICE LIST
 AVAILABLE ON REQUEST**

DISPLAY ELECTRONICS LTD.

**UNIT 4, SWAN WHARF,
 WATERLOO ROAD,
 UXBRIDGE, MIDDLESEX.
 UXBRIDGE (0895) 55800.**

N.G.T. COLOUR TUBES

First Independent Rebuilder with
B.S.I. CERTIFICATION

DELTA - IN-LINE - PIL - BONDED YOKE
 including
 AXT Series, DZB series 20AX - 30AX
 A56 610/67 610 series, A51 570/580/590X
 A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

N.G.T. ELECTRONICS LTD.,
120 SELHURST ROAD, LONDON SE25
Phone: 01-771 3535.

25 years experience in television tube rebuilding.

**EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
 ETC. ETC. ● ALL SPARES READILY AVAILABLE ●**

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it — no quibble — no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ — EHT trays — droppers — OSC coils — switches — cans — smoothers — I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
 TV COMPONENT BY RETURN
 IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

**32 TEMPLE STREET,
 WOLVERHAMPTON (0902) 773122**

IRISH T.V. DEALERS & ENGINEERS

Make extra money selling
 Ex-Rental Colour TV's.

NEW LOW summer prices. Off the pile from **£30**, good working order from **£50**, all prices **VAT INCLUSIVE**. Most leading makes in stock, fresh stocks weekly. Delivery to any part of Ireland.

Export orders welcome for countries using PAL System. We also stock VHS Videos and regunned Colour tubes.

TELE SPARES LTD.

Unit 113, Elm Road,
 Western Industrial Estate,
 Dublin 12, Ireland.
 Telephone: Dublin 521211/521756.

SETS & COMPONENTS

PHILIPS G11 AND BUSH T20 regular supplies. For prices phone 01-845-2036.

HITACHI, Mitsubishi, Panasonic, Sony, Toshiba, JVC, Sharp, Sharp fully refurbished. PEARSON TELEVISION, 0484 863489. Delivery arranged.

BRISTOL TELEVISION TRADE DISTRIBUTORS (BTTD)

4 Victoria Street
(Bristol Bridge) BS1 6BN

Ex-rental/trade in TV sets, supplier to trade only, wide range, large quantity, right price, regular supply.

Tel: (0272) 25266

THORN, GEC, DECCA's. Stripped for spares, panels, tuners from £2.50. Phone for prices: Wellington, Dartford 0322 337212.

WANTED - SURPLUS COMPONENTS, Valves, Transistors, Transformers, ICS Capacitors. Ring (0246) 211682, immediate settlement.

NEW VIDEOS, Televisions boxed guaranteed below retail prices. Details Hemel Hempstead 44351.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

QUALITY SETS FROM CORNWALL. Workers/non workers. Spares, panels, etc. Details ring 0726-81-5389.

GRUNDIG TELEVISIONS, telequipment oscilloscopes. Also spares. Manuals. Panel exchange. Ochremill. 0785 814643.

TELEQUIPMENT STORAGE OSCILLOSCOPES. Normal, variable persistence, store. 25MHz. Bandwidth but response beyond 50MHz. Trigger delay simplifies adjustments. From £300. Ochremill 0785 814643.

DXTV: MULTISTANDARD 26", British/French/European Pal/Secam, every refinement, private, bargain £250. Shoreham (Sussex) 2747.

SECOND HAND TELEVISION panels. Send stamp for lists. 154 Poplar Avenue, Edgbaston, Birmingham B17 8EP.

BOURNEMOUTH COLOUR TV Working Colour Prices

3500 Elec	£30	8800	£35
8000	£30	9000	£40
8500	£30	9200	POA
9600	POA		

Remote and Teletext
G8550 £35 G11 POA
ITT, GEC, BUSH, HITACHI, etc.

(0202) 432884.

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.30 per single column centimetre (minimum 2.5 cms). Classified advertisements 37p per word

SCREENPLAY *Your Friend in the TV Business*

COLOUR SETS FROM £5.00

MONOS FROM £3.00

PANELS BY POST - PRE-CALIBRATED

WORKING SETS TO ORDER

Phone Baldock 894905

SECTION 3, UNIT 4,

SERL COMPLEX,

LONDON ROAD,

BALDOCK, HERTS.

OPEN 6 DAYS 10-6.30pm/10-5pm SAT.



- * Britain's most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * GEC Starline
- * Decca 80
- * Decca 88
- * Decca 100
- * Pye G11
- * Thorn 8800
- * Pye 222 Series

All working and polished. These are not from major companies. A lot are from hotels and have had very little use.

Excellent reliable sets for rental.

Krystal Marketing Ltd,
Breedon Cross
Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

TELEVISION

Trade & Retail supplies of s/h colour & mono TVs. Most makes available, workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Brentpark Industrial Estate,
Southall, Middx. UB2 5LL.
01-574 4631, Ext 28

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

NORTHERN IRELAND DEALERS

COME AND SEE OUR LARGE RANGE OF
S/H COLOUR TVs AT LOWEST PRICES EVER

CONTACT:

S. M. ELECTRONICS

11 SANDHOLES ROAD, COOKSTOWN, CO. TYRONE

Telephone: Cookstown 06487/64277

Open: Mon.-Sat. 9.00 am-6.00 pm (Closed Wednesday)

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

EAST ANGLIA SUPPLIES

For your fully serviced colour televisions ready for sale or rent at realistic prices with free delivery (just petrol charged) anywhere for sensible sized orders.

G11s	£70 + VAT	MANY OTHER
T20s	£65 + VAT	MAKES
S/state from		REGULARLY
ITTs	£55 + VAT	STOCKED AND
Decca from	£55 + VAT	CHEAPIES FROM
		ONLY £25 + VAT
		FULLY SERVICED.

Contact John, Dave or Steve for personal friendly attention on
0223 69215 or 0353 61462

TELEVISION

GOOD QUALITY TRADE TVs COLOUR OR MONO SUITABLE FOR SALE OR RE-RENT, WIDE CHOICE OF MAKES AND MODELS

GENERAL FACTORS

UNION STREET
DONCASTER
DN1 3AE

TEL (0302)
68416

GOOD MOTORWAY ACCESS

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Cross-hatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. **£75.90**

OUTPUTS PROVIDED
UHF OUTPUT
VIDEO OUTPUT
SOUND OUTPUT
LINE PULSE
FIELD PULSE



Same as above plus RGB output **£81.50**
Line Output Transformer Tester **£11.50**
B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale UHF output **£18.50**
Same as above but with Video Output **£20.50**
Capacitance Meter measures 10pF to 1µF complete with moving coil meter **£14.75**
Car Alarm with built in Siren **£20.50**

S.A.E. for details. - Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

FOR INFORMATION ON
CLASSIFIED ADVERTISING
PLEASE RING PAT BUNCE
01-261 5942

COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-
DECCA 13/30	3.00	-	7.00	5.00	-	4.00
BUSH A823	4.00*	-	10.00*	5.00*	2.50	4.00
THORN 8/84	-	-	10.00	5.00	-	5.00
PYE 205	3.00	3.50	5.00	10.00	-	-
THORN 3/34	5.00	5.00	5.00	8.00	-	10.00
G8	6.00	-	8.00	7.00	15.00	5.00

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.),

Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273

Callers by appointment only.

VIDEO & HI-FI ELECTRONICS

379 Edgware Road, London W2.

Tel: 01-258 0328

ALL VHS PARTS AVAILABLE

EXAMPLES:

VIDEO HEADS	
JVC, Ferguson, Akai, Saba, Telefunken.....	£32.00
Sony (Betamax).....	£39.00
National Panasonic.....	£45.00
INTEGRATED CIRCUITS	
UPC 1365C.....	£7.30
UPD 553C.....	£14.75
UPD 552C.....	£10.56
HA 1171I.....	£14.20
UPD 548C.....	£14.65
BA 841.....	£22.95

All prices inclusive of VAT. Add £2.00 for postage & packing.

STARLITE ELECTRONICS

NOW MOVED TO:
WILLOWS FARM,
A13 RAINHAM, ESSEX.
Rainham 23225 also
Hornchurch 50238.

- TV TUBES -

2 year guarantee
Most types available

Japanese including Sony

Ex-Rental TVs from£15.00

Untested Panels.....£4.00

INDEPENDENT TELEVISION AND VIDEO COMPANY

LARGE STOCKS TO CLEAR
EVERY WEEK

COMPETITIVE PRICES

EXAMPLES:

B&W 20"-24"	From £1.00
COLOUR:	
Bush 1-2 I.C.	£4.00
Philips 520-550, 26"	£6.00
Thorn 3500	£6.00
GEC-Decca-ITT	£6.00

Philips 550 22"	£10.00
Pye 18"-20"-22"	£10.00
GEC 20"-22" 26"	£12.00
Thorn 8800-9000-9800	£15.00

Many Other Modern Sets
and VHS Videos

PHILIPS G11 - ITT - Bush T20-T22-
T26, Hitachi, Nat. Pan. - Sony
Off Pile from £40

Phone Frank: Nottingham
(0602) 864627

Unit 3

Meadow Trading Estate,
Meadow Lane,
Nottingham NG2 3HQ.

IRISH TV TRADE

CAN WE BE OF SERVICE TO YOU?

Regular supplies of Quality Colour TVs
LOWEST PRICES

Working Sets from £18 Non-working Sets from £8
FREE DELIVERY ANYWHERE

contact:

J. M. G. Electronics

Omagh, Co. Tyrone,
Northern Ireland.
Omagh (0662) 46032 night
Omagh (0662) 47911 day




N.W. ELECTRONICS


25 YEARS SUPPLYING THE TRADE

New Low Prices That's a Fact!

100's of good class HP Repos and
Ex Rental Colour TV's reduced to
ROCK BOTTOM PRICES!

Bush T20 (Excellent Cabs)	was £60	NOW £40
Bush 718 P.I.L. Tube	was £30	NOW £25
Bush 2 Chip Decoders	was £15	NOW £8
Philips G8	was £28	NOW £23
Philips G11	was £70	NOW £55
GEC 2010	was £25	NOW £20
Thorn 3500	was £12	NOW £8

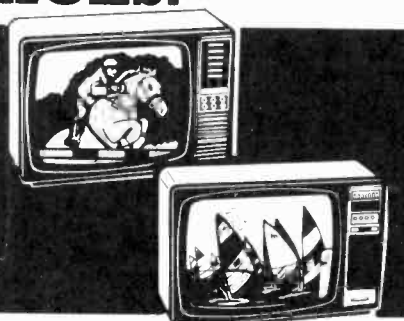

Hybrids £5 all makes!  Many more inc Pye KT30, Ferguson TX etc.

Fully Refurbished TV's Ready for Rent/Sale

Models include **Bush T20 £55, Pye G11 £68**
Pye KT3 £85, Bush Z718 £38, GEC £38

Many Other Makes in Stock.
Ring for Quotation.

White goods

Hoover Twins from £6. Hotpoint 1460 from £10.
Autos all makes from £10.

SPARES! SPARES! TV PANELS

	I.F.	DECODER	LINE D/P	POWER	CONVERG	VIDEO	FRAME T3
BUSH 2 CHIP	3.00	8.00	8.00	3.00	3.00	—	5.00
3000/3600	2.00	4.00	8.00	8.00	5.00	5.00	6.00
G8	5.00	7.00	14.00	8.00	5.00	—	5.00
WITH SOUND							
PANEL							
GEC 2110	10.00	5.00	12.00	8.00	5.00	5.00	5.00
BUSH 718	8.00	15.00	25.00	3.00	5.00	—	15.00
BUSH 720	8.00	15.00	20.00	20.00	5.00	—	15.00
THORN 8000	—	12.00	25.00	—	—	—	10.00
PYE 222	15.00	10.00	15.00	10.00	4.00	—	6.00

LOUDSPEAKERS £1 each

CASH ONLY—NO CHEQUES
DELIVERY CAN BE
ARRANGED—TRADE ONLY

P&P 1 panel £1.50, 2 panels £2.00, 3 panels
£2.50 etc. Quick Despatch - C.W.O. please.
All prices plus VAT

(0274) 688458 OPEN 6 DAYS A WEEK

Unit 12, Wharfedale Road
M606 Euroway Estate
Bradford

OPEN MON-SAT 9-5.30
Don't forget! We are open
all day Saturday!

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.
Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50
INLINE TUBE TYPE FROM £35.00
MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed
to Original Manufacturers Specifications.

Trent Tubes

31 RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM
PHONE: (0602) 813329
THE QUALITY REBUILDER

ALL tubes guaranteed for 2 YRS EXTENDABLE TO 4 YRS

All Standard Delta types one price
£29.50

A51-161 - A51-163 £42.00

A56-500/510, A66-500/510 (20AX) £43.00
Buy 10 at ONLY £38.00 ea

A56-540, A66-540 £49.00

Buy 10 at ONLY £44.00 ea

560DZB22, 560EGB22, 510VLB22 £46

SONY types from £55.00

1000's more available. VDU, MONO, Industrials etc.

Technical Advice Service. All Prices + VAT & exchange

Suppliers to Broadcasting Authorities & National Companies

WE SPECIALISE IN JAPANESE TYPES

STOCKISTS

N & S Ireland
Conway Bros
Cookstown
064 8763771

Peterborough
H Donner
0733 71809

STOP PRESS

A44-271 ONLY £14.00 LIMITED QUANTITY

TUBES

£29.00 INCLUSIVE, REGUNS TWO YEAR
£14.50 GUARANTEE, QUANTITY DISCOUNTS
SIX MONTH GUARANTEE SLIGHTLY
USED

A56-120 A56-140 A51-110 A49-191 A47-342 or 343
A44-270-1 A66-120 A66-140 (410) A67-120
(All 26" add £5)

No need to spend £5 returning old delta tube.

Slightly used in-line tubes from £29.
Six months guarantee.

IN-LINE 1 YEAR GUARANTEE

51-161
51-510
56-500
56-540
66-540
66-500

£45

inclusive

£55

inclusive

SPECIAL OFFER

NEW MULLARD

£64

inclusive

SONY

All sizes £66 INCLUSIVE
Some in stock send old glass later.

HITACHI

490DKB22

£34

560DZB22

£49

Plus 490 DVB 510 or 560 VLB

Philips G11s and Bush Z718

Panels from £10.00, Breaking for spares, Push button
units, Tube bases for sale or exchange etc. All good
working order.

G8 line panels with new LDPT £16.00.
Timebase, good working £6.50.

RADIO and TELEVISION SERVICING BOOKS

(MacDonalds). New 74/75 £15; 75/76, 76/77, 77/78,
78/79, 79/80, 80/81, 81/82, 82/83, 83/84 £22.50.

FREE DELIVERY

Except Tubes £5 each
All prices are inclusive

U-VIEW

29, Warmsworth Road,
Doncaster, Yorkshire DN4 0RP.
Tel: 0302 855017.

Callers ring first, open every day including Sunday
½ a mile from A1

WORKING CTVs THE BEST & CHEAPEST IN LANCASHIRE SPECIAL OFFER

Working Decca Bradford Including
Black Fronts

18" 20" 22" 26" ONLY £20.00 each in 6
units

Working GEC Plastic & Wooden. All models
20" 22" 26" ONLY £22.00 each in 6 units

Working Bush 20" 22" 26"

ONLY £15.00 each

Philips G8 (520) 22" & 26"

ONLY £20.00 each

Plus many more makes & sizes in stock,
inc. Tanburg, Nordmende, Thorn.

1st COME 1st SERVED

ALL SETS TESTED & WORKING

CALL

JOHN POWNEY

TRADE TV SALES & SERVICE

Unit 31 Progress Industrial Estate,

Kirkham, nr Preston

(0772) 683392

UNTESTED PANELS FOR ALL MAKES OF TV
£1.25 per panel plus post & packing

R.B.M. A823 PANELS. S.A.E. for details:
SCHÖFIELD, 28 St Albans Road, St Abbes, Lancs.
FY8 1TH.

WOODSDALE COMPONENTS RANK BUSH MURPHY TRANSFORMERS

Line Output

Z718 (T703A, T706A)

New (Complete) £19.50

Less Focus Module and

Rectifier £10.50

T20, T22 (T705A) £11.00

T26 (T705B) £11.00

TDA2190 Plug-in Replacement
module suitable for Bush T22/26 and
any set using same device £7.50

Switch Mode

T114A/B £8.00

Genuine RBM Units.

Prompt Postal Service P&P Paid.

Add 15% VAT to all prices.

DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,

Pinner, Middlesex. HA5-2QT.

Tel: 01-868 5580.

N. Skehan

Agents Office, Callers by appointment only.

CARTRIDGES AND STYLII at competitive prices.
Useful equivalents/price lists. I.s.a.e. GEOFF
DAVIES (Radio) 13 Bowen Road, Rugby,
Warwickshire.

TRADE REPAIR WORKSHOP

VIDEO, T.V., HI-FI. ANY MAKE.
EXCHANGE PANELS G8, G9, G11, GEC,
Grundig SO11 6011.

COLOURTRONIC SERVICES,
96 Ilford Lane, Ilford, Essex.
01-478 0782

C.T.V. PANEL SERVICE

Exch/repair & sales - chemically cleaned - no burned
or damaged print. 3 months g'tee, large range incl.
Decca 80 & 100, G11, G8, ITT, GEC, Rank, TCE, Jap &
euro models, despatched same day.

Send S.A.E. for lists or ring with your requirements:

Argo Services (Birmingham),
Elliott Road, Birmingham 29.
Tel. 021-471 4697

Telephone orders accepted using Access/Mastercard
CALLERS RING FIRST

BUSINESS FOR SALE

RETAIL BUSINESS FOR SALE

Bournemouth: established six-
teen years: excellent retail outlet
producing substantial profits.
Situated busy main road and
comprising large showroom and
workshops with spacious luxury
3 bedroom flat over. Immaculate
property. Retirement sale.

FREEHOLD AT

£95,000

0202 - 35653

VIDEO TV. HI FI SHOP NW6

+ Stock Rooms/Workshop.
T/O exceeding £115,000 p.a. (£4,000 from repair).
Main dealership.

12 years new lease. Rent £2,300 p.a.
PRICE £25,000 FOR QUICK SALE

Please reply to:

TV BOX 197

BUSINESS OPPORTUNITIES

TELEVISION AND RADIO REPAIR BUSINESS

Shop, workshop and store in affluent area
outskirts W. Sussex seaside resort.

£18,000 for lease (16 years remaining).
All current clients.

S.A.V. if required - 0243 22671.

T.V. VIDEO & HI-FI REPAIR & RECON SALES BUSINESS

Ilford area.
Established 9 years. Long lease. Large fully equipped
workshop. Shop showroom. Great potential.

Capital investment needed.
Would consider partnership
or for sale £20,000.

BOX No. TV 196

FOR SALE



Sabaco

For a great deal!

VAN LOAD DIRECT FROM SOURCES

ALL SETS OFF THE PILE

Most makes/sizes available, any quantities.
e.g. Black faced Decca £10, solid state GEC £10, PYE 22"/18" (solid state) £12, Thorn 8800/9000 etc. £20, Thorn 3500 £8, Philips G8 (550/520) £9, ITT (CVC5, 8, 9) £9, Grundig 5010/6010 £10, 26" (3500/G8 etc.) £5, Jap £10, Pye GEC Hybrid £4, B/W £1.

All above offers minimum quantity of 15 sets or more.

ALL PRICES SUBJECT TO VAT & AVAILABILITY.

Sabaco


Saba House,

46A Derby Road, Sandiacre, Nottingham.

Open 6 days a week

9.30 a.m. - 5.45 p.m.

Telephone: (0602) 397555

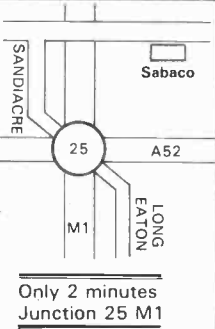

Only 2 minutes

DEVONICS

Quality Rebuilt Tubes

2 YEAR WARRANTY

In line from £41

Deltas from £30

NEW TUBES ex stock complete with scan coils

370 KRB 22

A51 JAR00X02

560 DYB 22

£40 ea + £5 carr + VAT

2A BARTON HILL ROAD,
TORQUAY TQ2 8JH

0803 - 33035

WE ARE SO

~~SHAW~~ SURE!

OF OUR QUALITY PRODUCTS
THAT WE GUARANTEE THEM

ALL FOR ONE

FULL YEAR!

THIS MONTH'S SPECIALS:

PUSHBUTTON SWITCHERY

1. G8 SLOPING PUSHBUTTON..... £12.75
2. G8 PLASTIC MAINS SWITCH..... £0.75
3. PHILIPS G11 WITH REMOTE MAINS SW..... £1.45
4. ITT 6 WAY PUSHBUTTON WITH VCR..... £7.50

P+P £1.00 + VAT

SHAW ELECTRONIC SERVICES

38 Rudland Close,
Thatcham, Berks RG13 4XW.

S.A.E. for lists of other BARGAINS

TUBE RE-GUNNERS. - Radyne Induction Generator - Model RD15CD, 1.5kw with hand lead and coils. Water cooled. Good condition. £300. Ring evenings 0980 610697.

TELEVISION SERVICING EQUIPMENT, Oscilloscope 25MHz, AVO 8 Function Generator, Tools, Panels, Manuals, Stock. 01-809 2312.

TELEQUIPMENT DM64 Storage oscilloscope, dual channels with manual, £90, Chelmsford 75103 after 6 pm.

SOLARTRON DUAL TRACE OSC. 15MHZ B.W. test probes and instruction book. £150.00 o.n.o. Tel. Colin Mitchell 091-234 0037.

THANDAR SC110 OSCILLOSCOPE as new £150. Offers? Swap for VHS video. 2 Philips 2000's needing attention - any offers? 0326 311648.

WORKING COLOUR/B&W Televisions, also panels, good prices. FOUR ACES ELECTRONICS, 74 Old Oak Comon Lane, London W3. 01-749 9338.

76 TELEVISION Copies 1975/1976 to 1981 £35.00. Tel. (Oldham) 061 652 5856.

COMPLETE TUBE RE-GUNNING PLANT FULLY OVERHAULED

Also some brand new items including electric ovens with automatic process control. Regunns 15 colour (Sony, Trinton, Pil, In-Line etc) tubes 24 hour cycle. Training provided and assistance available for installation and setting up of a plant.

EXPORT ENQUIRIES WELCOMED

ONLY £8,500

Tel. 0582 410787

WANTED

FAULT FINDING, Thorn 1615, wanted. Reverse charges. and phone 01-253 9794.

LATE MODEL COLOUR TELEVISIONS, videos, etc. Any quantity. Monitec. Tel. 0299 400233/400933.

VIDEOS WANTED. Working or not. VHS and Beta only. Upminster (040227) 20549.

1000 COLOUR SETS WANTED. Send fullest details and prices to LACOSTE, Box 3514, Vineta, Swakopmund, Namibia.

WANTED 50-100 Television rental accounts. North Bucks area/radius 30 miles. Box TV47.

WANTED EX RENTAL COLOUR T.V.s. Any quantity. Prompt collection. Cash paid. Sheffield 754865.

HUSSAIN CENTRAL TV

URGENTLY REQUIRES UP TO

£250,000 BANKRUPT STOCK.

TELEPHONE 021-622 1023

SITS VACANT

Electronics Engineers

To work on the maintenance of the extensive viewing facilities at our South Bank Television Centre.

Aged 25-35, you should have several years' workshop experience repairing domestic television receivers and, ideally, some experience in the repair of home video recorders.

Salary £9,729 - £13,000pa according to experience.

Please telephone 01-261 3237 for an application form.

An equal opportunities employer



London Weekend Television

SERVICE SHEETS

Alba, Cossor, Baird, GEC,
Defiant, Echo, Ferguson, Philips etc. etc.

30,000 SERVICE SHEETS IN STOCK ALL AT £3.00 + SAE
ALSO COLOUR MANUALS AVAILABLE AT £6.00 EACH

TV Sheets, Black and White, also Radiograms, Record Players, Music Centres. Japanese models in stock.
Circuit diagrams only. Also Tape Recorders etc. Car radios also in stock. Radio Mobile, Sharps etc.,
Philips, Car Radios Service sheets £3 + SAE. Manuals £6 + SAE. Old radios AM/FM
Ferguson, Pye, Please forward s.a.e. Send cheque or P.O. and Valves.
Sanyo. Mono C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. Old transistors, TV.

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

Colour £2.00 Mono £1.50

Manual prices on request.

All our prices include post and packing costs.

Send stamped envelope for free catalogue and enquiries.

SANDHURST TV SERVICES (MAIL ORDER)

49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

AERIALS

AERIAL BOOSTERS

B45H/G-UHF TV next to the set fitting, gain about 20dbs, PP3 battery or 8V to 14V/working. Price £8.70. P&P 30p.

UHF TV BOOSTER MODULE. PCB ready made up to cover the complete UHF TV band. Gain 10dbs, noise 1.9dbs. 8V to 14V/W. Price £2.50. P&P 30p.
SET/TOP AERIAL and matching aerial booster (trebles and gain). Price £8.70. P&P 50p.

Video Transmitters transmit with Aerial Boosters £8.70. S.A.E. Leaflets.

ELECTRONIC MAILORDER,
62 Bridge Street, Ramsbottom,
Lancashire, BL0 9AG.
Tel: Ramsbottom (070 682) 3036.

S.A.E. for leaflets. Access/Visa Welcome.

CLEARVIEW AERIALS

Clearview have pleasure in announcing a full and comprehensive range of signal amplification equipment. For example: low noise electronically remote controlled masthead pre-amp 1.6db noise. CH. 17-69. Set side amplifiers, distribution amplifiers, notch filters 4 in 1 or 2 in 1 etc. Combiners for 2 UHF aerials 3db gain or 4 6db gain. Trade and retail.

Send large SAE for our comprehensive catalogue

CLEARVIEW AERIALS,
173 Kings Road,
Kingston Upon Thames, Surrey.

EVERYTHING NECESSARY for multi-outlet and high gain installations. Cables, outlets, splitters, channelpass filters, duplexers, masthead amplifiers, distribution amplifiers, brackets, masts, aerials, etc. Use trade gear and save pounds. Catalogue 50p (refundable). Professional advice. WRIGHTS AERIALS, 43 Greaves Sike Lane, Micklebring, Rotherham.

Euro-Sat

Parabolic Dish Antennas

(Parent company est. in TV communications since 1969)

SATELLITE TVRO ANTENNAS

TOP QUALITY SOLID

GLASSFIBRE DISH ANTENNAS


1M DIA 11-12.4 GHZ BANDS	£77.00
1.2M DIA 11-12.4 GHZ BANDS	£33.00
2M DIA 11-12.4 GHZ BANDS	£215.10
3M DIA 11-12.4 GHZ BANDS	£437.00

All dishes come complete with lead support

Trade & Export Enquiries Welcome
Prices do not include delivery

Euro-Sat

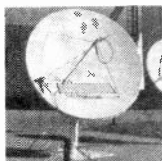107 Cross Street, Sale, Cheshire, England.
Tel. 061-437 2631 061-881 4249



BOOKS AND PUBLICATIONS

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

FULL SIZE TOP QUALITY service sheets £2.50 + l.s.a.e. CTV/Music Centres £3.50 + l.s.a.e. Repair data almost any named TV/Video £10.50 inc. circuits. L.s.a.e. brings any quite free magazine/pricelists. TIST, 76 Churches, Larkhall, Lanarkshire. Tel. 0698 883334.

RADIO AND TELEVISION SERVICING BOOKS. New 74/75 £15. 75/76, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84 £22.50 each. Free delivery. U-VIEW, 29. Warmsworth Road, Doncaster. 0302 855017. Callers ring first.

MISCELLANEOUS

GET SHARP PARTS FAST

TELEPHONE

0734 - 876444

TELEX 848953



SHARP

Main U.K. Spare Parts Distributor

Audio-TV-Video ★ Microwave ★ Photo-copier ★ Typewriter

All U.K. model spares available. Same day despatch of orders received before 1pm.

Microwave, photocopier and typewriter spares to authorised service dealers/centres only.

WILLOW VALE ELECTRONICS LTD.,
11 Arkwright Road, Reading, Berks.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

A-Z LIST OF MANUFACTURERS ADDRESSES. All major TV, audio etc, plus many hard to get ones. Send cheque/PO for £3.75 to DOWNS ELECT, 79 High Street, Dalkeith, Midlothian.

The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

Part 1.

The Colour Signal

Part 2.

The Receiver Decoder

Part 3.

Receiver Installation



VHS★★★★V2000★★★★
BETAMAX★★★★UMATIC

For full details telephone

0253 725499 (Day)

0253 712769 (Night)

Or send for precise details

FLINTDOWN CHANNEL 5

339 CLIFTON DRIVE SOUTH,

LYTHAM ST ANNES FY8 1LP

(enclosing this advert)

NAME

ADDRESS

..... TEL:.....

METERS

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

VIDEO

EUROLEC VIDEO SERVICES

Tel. 01-669 2611

Telex 893819 Eurlec

Address for correspondence only

35 Sandy Lane South,
Wallington, Surrey SM6 9RF

All Philips VCR Tapes available as per our previous advertisements.

Second user Umatic and Professional equipment available - constantly changing stocks - Export Service available.

NTSC - PAL - NTSC TRANSFERS

(OPTICAL) £15 per hour plus VAT

VAT Reg. No. 335 7096 45

EX RENTAL VHS VIDEOS

★ ★ ★

100's IN STOCK

★ ★ ★

CONTACT MICK ON
021-772 1591

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares New 9000 Decoder £8.50 9000 Frame panel £8 9000 Cyclops panel £1.50 8000/8500 timebase panel £6 8800 convergence panel £6 8500 convergence panel £6 4000 Power supply £3 1600 Mains lead, switch £1.50 3500 6 push button + cable form £1.50 T605 1VNP/T066 3x6A £10p 9000 Sound output panel £1 3500 Focus unit £1.50 3500 Mains Trans £4 3500 ext outs 10 for £4 3500 I7 panel £2 3500 Frame panel £3 3500 Line panel £3 3500 A1 Diode £20p Export 3500 IF par £2 IC board with set of SN74LS £4 4000 Tube base £4 3500 A1 pots £50p Beam limiter pane £1.50 3500 Fower panel with Y969 £1 3 Way regulated adaptor 240V 6V/7.5V/300mA £3.50 Rank/Toshiba prel unit 0354 £9.50 2 banks of 3 PB unit. Pye 731 £1.00 4 Push button unit preh £1.00 6 Push button VH ² /UHF for v/cap. GEC-Decca type £7.00 7 Push button for CVC5 ITT £8.00 KT3 12 Push button unit £2.00 KT3 (Export) 12 F.B.U. £2 6 Push button Uni. Thorn £1.00 6 Push button Uni. fits GEC & Decca etc. £6.00 Hearing aid unit £6.00 6 Push button unit Pye 713 £7.00 7 Button Unit GEC with Lamps £7		XX 3123 THORN 50p Hitachi 2A/1500V metal case wire end £13 FARST/REC 20p 20 AX GEC Degaussing Panel 809 with PT37 £1.00 Line Transformers Hitachi Split Diode and GEC 1981 to 1994 £13 GEC 2110 £3.00 Mullard AT 2036 £1.50 Pye 169 Line Trans £3.00 Pye mono £3.00 Rank mono T704A £3.50 Split Diode Trans £7.00 GEC 20 AX Rank Z522 £3 Rank L.O.P.T. Z970 £3 CVC 5-8-9 £3.00 CVC20 ITT £3.50 AT2080/15 £5.00 CVC30 ITT £5.00 CVC32 Line Tran £4.75 GEC80 Line Trans £6.00 CVC40 Slip/Diode £12.00 CVC 45 £5.00 GEC Portable G10T2041 £3.00 GEC Portable G10T2046 £3.00 EHT Split Diode Leads ITT £1.00 Ex panel "14" Fidelity portable £5 3500 L.O.P.T. & HT Trans each £2 LOPT Rank Z763 £5		5 Volt Mains Transformer 2 Amp £30p 30V Power Supply 500MA 4x2 1/4 £2.50 Pye 731 Power Panel £13 6 Diode Universal Triplers £3.25 NEW PYE 725 line O/P panel with L.O.P.T. & Tripler £10.00 Thorn Mains Isolator unit for 70-80W. Ex-speaker £2 NEW GEC 20AX Power Supply Switch Module £17.00 Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.cap./LOPT1 £10 Field + Jangle panel for GEC 3133/3135 £1.50 GEC 2110 line panel with transformer £7.00 GEC 2110 tuner unit + IF Panel £12.00 Pye/Chelsea Line on panel £2.00 Pye 713 IF panel and tuner £2.00 Pye 713 Chroma £1.00 Pye/Chelsea Timebase panel with LOPT1 £10.00 Pye 731 Frame Panel £5.00 Pye 731 Convergence Panel £25.00 Pye 731 Chroma £5.00 Pye 731 IF panel + tuner £25.00 Pye 607/205 Line panel with transformer £10.00 Pye CDA/205 panel £10.00 GEC portable chassis + LOPT1 2114 New £6.00 Thorn 1613/1713 chassis £9.75 G9 Line Panel £2.00 G9 Power Panel £7.00		Mains Droppers GR 2R2+68R £1.25 GR 47R 15 watt 75p Pye 731 3+56+27R 50p Pye 3R5/15R/45R 50p Thorn 50/17/1K5 £1.00 120/20/20/48/117 £1.00 270/106 for Thorn 4000 £1.10 18/320/70/39 50p Thorn 50-40R-1K5 50p Ac Socket & Lead £2.5p GEC ITT, Philips, Pye 7x3 3/4 Thorn £2.5p Rank Toshiba Tube Bases 30p		NEW MULLARD TELETEX Decoder Panel (VM6230) £15.00 Panel 6101 £15.00 Panel 6330 £15.00 G8 Tuner Unit + Panel £6.00 G8 Convergence Panel (late type) £12.00 G8 Power Supply £6.00 G8 6 Sloping PBU £8.00 G8 IF & Chroma £10.00 G8 Chroma £6.00 G11 IF Detector £3.00 G11 Selector gain module £3 Complete CVC 825 Chassis (both panels) £40.00 AEC V/Cap Resistor Unit UHF with IC £4.00 SAS660 SAS670 £3.00 Z714 RANK IF Panels 6MHz 1 I.C. £2.40 SL437F £3.00 Z999B RANK IF Panels £2.50 Export 5.5MHz 2 I.C.'s £2.50 TBA1205B TCA2705Q £2.50 Z743 RANK IF Panel £2.50 Export 5.5MHz 3 I.C.'s £2.50 TBA750+SC9504P+SC9503P £1.50 Pye G11 Front panel with transducer, pots, tuner pots, 6 pb switch+lead £5.00 Pye 6 button switch portable £1.00 GEC V/cap VHF/UHF tuner and IF+ sound O/P PC 706B3 (Export) £12.00 GEC Line O/P PC 659B3 £6.00 2110 GEC Power Panel £8.00 GEC Power Supply (Export) £10.00 G11 dynamic correction panel £6 CVC 20 Front panel with sliders + mains input panel £4 CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14 CVC9 slider pots panel 50p CVC 5 Mains on/off + 5 pots £2 Universal Focus. Fits Pye, Thorn and Decca Units. £75p Large Type 75p Decca Small 75p KT3 Focus Unit 75p K30 Focus Pot 75p TX10 Focus Units £6.00 CVC 32 Focus Unit 75p Fidelity Focus Unit 14R-14S 30p 3500 Thorn Focus Unit £1.00 ITT Small for use with Split Diode 50p TV11 50p Remo TV12SP 50p TV13 50p TV14 50p TV18 60p TV20 £1.00 TV45 50p Thorn 14/1500 rec stick 5p G7000 Philips Video Games Packs £8.00 each 11 types G11 drawer ASS 3 pots Mains switch and lead £2.00 Line O/P panel GEC 2217/2218/2213/2214/2226/2227/2228 £10 CLOCK DISPLAY £1.00 4 SEG ACDM45 £1.00 4000 thick film £2.00 DISPLAYS 4040 Clock £1.00 7seg Red LED 50p 2 digit LED 8.8 50p 2 digit LED +1.8 with panel + MCI4511 £1.00 4000/63 £1.50 CVC 20-25-30 Mains Switches £75p Infra Red and Ultrasonic G11 Teletext Decoder Panel £30 RANK & ITT Mains Remote On-Off Switch (720R) £1.50 RANK & ITT Mains Remote Switch 2865 chm £1.50 RANK & ITT Remote Switch 2800 ohm £1.50 G11 Mains Switch 50p 4 amp Mains Switch 25p GEC Mains Switch 4 amp 30p KT3 Mains Switch 50p THORN Rotary Mains Switch £1.00 G8 Mains Switch 50p Thyristor 6004 amp C106/2 £1.00 G11 Preh Red LED P/Button for C.H. Change £1.00 RANK TOSHIBA Transducers TPC-2011 £50p Mains Switch ITT Long Type Print £75p Mains Switch Philip Long Type TAG £75p Mains Switch GEC Long Type TAG £75p Thorn 12 or 24 volt battery convertor for portable colour TV £6.00 Tape Heads R/Play/Back Mono/Stereo £1.00		Mains Isolation Transformer (R.S. 500VA Type) in case £25.00 Rank Secam Decoder Panel UHF & VHF T115A £13.00 NEW GRUNDIG SPARE PANELS Set No. SC4127, SC4337, SC6217, SC6237 £10.00 GRUNDIG MODULE TYPES Tuner IF, AF TRX LOP, TP preamplifier £1.50 Tuning board. Colour RGB. LED Board £7.00 Deflection Board £3 From £3 to £8 Multi-Caps 350V 300M + 300M £1.00 400V 400M 60p 350V 400M 60p Thorn 3500 £1.00 175/100/100/350V £1.00 KT3/200/25/25/385V £1.00 300+300+150+100+50MFD £1.00 350V £6.00 47/220/350V £2 150/150/100/100/100/320V £2.00 2500/2500/63V 50p 150/200/200/300V 70p 400/400/200V £1.70 300/100/100/16/275V £1.50 100/200/325V 40p 150/150/100/375V £1.50 300/300/100/32/32/300V 2.00 1500/2000/30V 50p Jelly pot Thorn 00D4013 £3 150/150/100/100/320V £2.00 100/350 + 300/200/100/16/275V £2.00 225+25/380 GEC 70p 200/100/100/350V £1.50 500/500/25V 50p 150/150/100/300V 75p 200/150/100/300V 1.00 ITT Panels CVC 40/2 Chassis, new £30, complete with intrafe panel £3.00 CVC 820 Line O/P Panel £1.00 CVC20 Mains Panel £3.00 ITT 8 & 6 Push Button Unit £1.00 CVC40/2 New Chroma Panel £10.00 CMA 10 £2.00 CMA 11 £2.00 CMA 40 £1.50 CMA 102 £4.00 CMC 16 £5.00 CMC 38 £8.00 CMC 45 £1.50 CMC 47 £1.00 CMC 52 £15 CMC 57 £6.00 CMC 58 £8.00 CMC 59 £8.00 CMC 67 £3.75 CMC 67/2 £4.00 CMC 68 £4.00 CMC 120 £4.00 CMC 110 £5.00 CMC 33 £5.00 CMC 40 £5.00 CMC 41 £5.00 CMC 800 £10.00 CMC 25 £2.00 CMC 26 £2.00 CMC 40 £2.00 CMC 41 £1.50 CMC 31 £1.00 CMC 12 (untested) £4.00 CMC 30 (untested) £4.00 CMN 20 £1.50 CMN 21 £1.50 CMN 40 £1.00 CMN 45 25p CMP 10 £2.00 CMP 11 £4.00 CMP 40 £2.00 CMS 11 £2.00 CMS 40 £2.00 CMU 12 £10.00 CMU 14 £8.00 CMU 30 £7.00 CMU 45 £7.00 CMZ 30 £5.00 GMA 90 £5.00 GMC 120 £2.50 GMR 64 £5.00 TMN 2 £2.00 VCA 20 £1.00 VCA 21 £10.00 VMC 26 £1.00 VMC 34 £4.00 VMC 44 + 45 £5.00 VMC 51 £5.00 Hand Sets G11 Ultrasonic Teletext Handset £24.00 R.C.H. Ultrasonic GEC Full Remote C2014/1 £18 C2219H £15.00 New Replacement for G11 Ultrasonic Full Remote £12.00 Thorn 4000 insert with 7 buttons £5.00 Decca RC 11 £14.00 Decca RC 12 £14.00 G11 Infra-red full teletext £24.00 Rank, Infra-red £10.00 Dynatron-Full remote CTV 62, 63, 64 £19.00 Hitachi infra red handset £18 Philips full remote KT3, 16C928/21C934, 7228/7324, K12 26C 797/1ST 66K 1826 £12.00 G11, Full remote top button assy. £12.00 G11, Full remote repair service (exchange unit) £12.00 Philips infra red full remote 9 channel for CP2605 £6.00 Philips infra red full remote 12 channel for CP2605 £12.00 Philips Key Pad set KT3/K30 £3.00 KT3/K30 T/Text £15.00 KT3/K30 Full remote £15.00 KT3 Power supply £4.00 Hitachi 8 button unit with resistor unit Last year model £7.00 GEC infra-red 2236-2026 £4.00 GEC push pad hand set button blebs 10p each Pye & Philips handset KT3-K30 chassis. No RC4001-RC1510-RC5176-RC971 RC5177 £13.00 Special Price ITT Hand Set with TV-Teletext-VCR £12.00	
--	--	---	--	---	--	---	--	---	--	---	--

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF

SAME DAY SERVICE

All items subject to availability.
No Accounts: No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage

Add Postage for overseas

Callers: To shop at 212 London Rd.,

Southend. Tel. 0702-332992

Open 9-1/2-30.6. GMT + school orders accepted on official

headings add 10% handling charge.

Tuner Units	
V/Cap Rank UHF Z776F/Unit	£6
V/Cap Rank VHF Z773T/Unit	£5
NFW G8 Tuner V/Cap	£5.50
ELC2000 on Panel	£2.50
GEC 6 Push Button Unit	£6
ITT 6 Push Button Unit	£6
DECCA 6 Push Button Unit	£6
GEC or Hitachi 6 push button unit 2110 Conversion	£8
GEC 2110 V/Cap	£5
ELC1043 (Ex Panel)	£3.75
ELC1042 NEW	£5.00
ELC2000	£4.00
ELC2004	£10.00
ELC2006 NEW	£10.00
GEC Tuner V/Cap Hitachi After 1979 E1548, E1547, E1545	£10.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
V317 (VHF)	£5
V334 (VHF)	£5
U321	£6
U341 UHF	£7.00
U342 (UHF)	£5
U411 UHF	£7.00
U.V. 411 Tuner	£10.00
ELC1043/05 Thorn	£5.90
ELC1043/06 Thorn	£5.00
Small V/Cap Mitsumi	£4.00
UHF	£3.00
VHF	£3.00
G8 Tuner	£6.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF VHF Variacap (old type)	£8.00
Mosfit UHF/VHF (new type)	£8.00
UE2-B31 Fidelity V/Cap TU unit	£6.00
Thorn Tuner PANEL with 6x100K pots & cursors NO TUNER	£1.00
HITACHI 20 Turn Pot	40p
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Videon MTS 900	£2.50
Mullard Video Modulator.	
Application, video tape recorders, VCR cameras, video games, closed circuit TV, C.C.I.R. system, Data supplied.	£10.00
VT 100 Sound Tuner Kit. TV. Viosound. The latest design in low noise fitted with DNR, RF output and audio	£30.00
Sylvania UHF F4201B	£6.00
Sylvania VHF 900	£6.00
Small Tuner DX 175-220MHz Auto Changerover	£5.00
9000 Thorn Tuner on Panel	£7.00
D.P.D.T. switch Black knob. Chassis or PCB mount each or 40 for £1.00.	4p

THORN 1400 4P.B. Mech. Tuner	BTT822	£1.00
THORN 1500 4P.B. Mech. Tuner	BTT6016	£1.20
THORN 1500 4P.B. Mech. Tuner	BTT16018/ML237B	£1.50
THORN 3500 4P.B. Mech. Tuner	BTT6218	£1.50
THORN 8000 4P.B. Mech. Tuner	BTT8124	£1.00
THORN 8500 Mech. Tuner	BTT8224	£1.00
All new & boxed.	£4.00 each	
Delay Lines		
DL20A 80p	DL600	£1.00
G8 (Old Type)		£1
DL600		£1.00
DL170		£1.00
UDL11		30p
KT 3 Luminance		75p
Luminance Delay Line (CVC 45)		50p
10x630ma luse		25p
10x2A fuse		50p
10x3.15 fuse		50p
10x500ma		80p
10x1 amp		80p
20 3.15 AS Fuses		£1.70
Co-Ax Joint		15p
Co-Ax Belling Lee Plug		12p
Co-Ax Splitter		£1.00
UHF Modulator CCIR		£3.00
Infra Red Emitting Diode		20p
NE2861 Small Neon Lamps GEC & Philips		5p
Mullard 5 Watt Amps. LP1162 New		75p
T.V. Tubes		
12" A31/300 Hitachi		£10
15" A38/170W Hitachi		£8
18" Hitachi PIL tube with scan coils 470 KCB22 TC03		£25
10" Black and white tube scan coils & line trns.		£6.00
12" 90° Tubes Type 310GNB4		£12
14" 110° Tubes Type 310GNB4		£12
Integrated Circuits		
AC76013		£1.50
AM251 S23PC		10p
BAV40		40p

SAB4209	£2.00	SN76033	£1.50	MJE661	25p
TB00124	£1.00	SN76110N	£1	MJE3055	£1.00
SAAS000A	£1.50	SN76115AN	50p	MJE2801	30p
SAAS012A	£5.00	SN76131	50p	MJE2955	50p
SAAS020	£3.50	SN76141N	£1.00	MJE13005	30p
SAAS503	£5.00	SN76226	£1.00	Sanikron Diode	30p
SAAS504	£3.50	SN76227N	£1.00	Philips Cartridges	
SAAS504A	£4.40	SN76228N	£1.00	GP422 (4CH)	£6.00
SAAS5050	£3.50	SN76270	£1.00	GP412	£6.00
SAF1032P	£2.50	SN76532N	50p	GP412/11	£6.00
SAF1039	£2.00	SN76544N	£2.00	GP406	£6.00
SAS560	£2.00	SN76546	£1.00	Transistors	
SA5670	£1.00	SN76550	30p	A1222	15p
SA5660	£1.00	SN76552	30p	A1223	15p
SA5580	£1.50	SN76570	£1.00	AC106	15p
SA5590	£1.50	SN76620	50p	AC121	15p
SL901B	£4.50	SN76650	50p	AC124	15p
SL918	£4.50	SN76660N	40p	AC128	15p
TA7122	£1.15	SN76620AN	£1.00	AC137	15p
TAAS320A	50p	SN76666	50p	AC151	15p
TA4470	£1.50	SN76705N	75p	AC131	15p
TAAS570	75p	SN76707N	£1	AC138	15p
TAA611B	50p	SN76708AN	75p	AC152	15p
TAA621	£2.00	SN76720	£1.00	AC153K	15p
TAA661	50p	SN76728N	40p	AC142K	15p
TAA611	£1.50	SN76750	40p	AC169	15p
TA7108P	£1.00	UA783PC	40p	AC176K	15p
TA7117	50p	TA100A02	40p	AC178K	15p
TA7120P	50p	BT138/10A	70p	AC179	15p
TA7315AP	50p	BT146	30p	AC186	15p
TA7677AP	50p	TBA5400	£1.50	AC187K	15p
TA7649P	50p	TBA2700	£1.00	AC188	15p
TBA120A	40p	TBA2705	£1.00	AC188K	15p
TBA120AS	40p	TC A2705O	£1.00	ACY21	25p
TBA120SA	40p	TC A700	£1.00	AD143	50p
TBA120SB	40p	TC A740	£1.00	AD149	50p
TBA120T	50p	TC A830	£1.00	AD161/162	pair 25p
TBA120SU	£1.00	TC E120CO	£1.00	AD161	25p
TBA120U	75p	TDA440Q	£1.00	AD162	25p
TBA120V	30p	TDA1003A	£1.00	AD163	25p
TBA120X	40p	TDA1010	£1.00	AD164	25p
TBA1441	£1.00	TDA1010A	£1.00	AD165	25p
TBA231	75p	TDA1061A	£1.50	AD166	25p
TBA306Q	50p	TDA1035T	£3.50	AD167	25p
TBA306Q	£1.00	TDA1035S	£2.00	AD168	25p
TBA306	75p	TDA1072	£1	AD169	25p
TBA440P	£1.00	TDA1151	30p	AD170	25p
TBA440C	£1.00	TDA1170	£1.00	AD171	25p
TBA480Q	£1.00	TDA1190	£1.00	AD172	25p
TBA520	£2.00	TDA1200	75p	AD173	25p
TBA530	£2.00	TDA1207A	£1.00	AD174	25p
TBA540	£1.00	TDA1365	£3.00	AD175	25p
TBA550Q	£1.75	TDA1412	50p	AD176	25p
TBA560CQ	£1.00	TDA1413	50p	AD177	25p
TBA570	£1.50	TDA1420	80p	AD178	25p
TBA625	50p	TDA1420A	80p	AD179	25p
TBA625	£2.00	TDA1420B	80p	AD180	25p
TBA651	£2.00	TDA1420C	80p	AD181	25p
TBA651	£2.00	TDA1420D	80p	AD182	25p
TBA673	£1.00	TDA1420E	80p	AD183	25p
TBA720A	£1.50	TDA1420F	80p	AD184	25p
TBA750A	£1.50	TDA1420G	80p	AD185	25p
TBA780	£1.50	TDA1420H	80p	AD186	25p
TBA800	50p	TDA1420I	80p	AD187	25p
TBA810AP	60p	TDA1420J	80p	AD188	25p
TBA810S	60p	TDA1420K	80p	AD189	25p
TBA820	60p	TDA1420L	80p	AD190	25p
TBA890	£1.00	TDA1420M	80p	AD191	25p
TBA900	£1.50	TDA1420N	80p	AD192	25p
TBA920	£1.50	TDA1420O	80p	AD193	25p
TBA920K	£1.50	TDA1420P	80p	AD194	25p
TBA950	£1.50	TDA1420Q	80p	AD195	25p
TBA900Q	£1.00	TDA1420R	80p	AD196	25p
TMS1000NL	£2.00	TDA1420S	80p	AD197	25p
TMS1943N2L	£1.00	TDA1420T	80p	AD198	25p
(clockchip)	£1.00	TDA1420U	80p	AD199	25p
TMS9980	£4.00	TDA1420V	80p	AD200	25p
TMS9901	£1.00	TDA1420W	80p	AD201	25p
TMS2716JL	£1.00	TDA1420X	80p	AD202	25p
TMS3529	£2.00	TDA1420Y	80p	AD203	25p
TMS3720A	£1.00	TDA1420Z	80p	AD204	25p
TMS3720ANS	£1.00	TDA1420AA	80p	AD205	25p
TMS4014	70p	TDA1420AB	80p	AD206	25p
FX-012	£1.00	TDA1420AC	80p	AD207	25p
TMS9902	£1.20	TDA1420AD	80p	AD208	25p
ULN2216	75p	TDA1420AE	80p	AD209	25p
UPC5661H	£1.00	TDA1420AF	80p	AD210	25p
UPC585C	£1.00	TDA1420AG	80p	AD211	25p
UPC1031H	£2.00	TDA1420AH	80p	AD212	25p
UPC1353C	£1.00	TDA1420AI	80p	AD213	25p
UPC1366C	£1.00	TDA1420AJ	80p	AD214	25p
UPC2002	75p	TDA1420AK	80p	AD215	25p
UPD849HC	£2	TDA1420AL	80p	AD216	25p
SN2948	50p	TDA1420AM	80p	AD217	25p
SN29770BN	£1.00	TDA1420AN	80p	AD218	25p
SN29771BN	£1.00	TDA1420AO	80p	AD219	25p
SN29772BN	£1.00	TDA1420AP	80p	AD220	25p
SN7402N	£1	TDA1420AQ	80p	AD221	25p
SN7472N	£1	TDA1420AR	80p	AD222	25p
SN74107	£1.00	TDA1420AS	80p	AD223	25p
SN74167	£3.00	TDA1420AT	80p	AD224	25p
SN7412N	£3.00	TDA1420AU	80p	AD225	25p
SN7472N	70p	TDA1420AV	80p	AD226	25p
SN7472N	20p	TDA1420AW	80p	AD227	25p
SN75108AN	£1.00	TDA1420AX	80p	AD228	25p
SN76001	£1.00	TDA1420AY	80p	AD229	25p
SN76003	£1.00	TDA1420AZ	80p	AD230	25p
SN76013ND	£1.00	TDA1420BA	80p	AD231	25p
SN76018	£1.00	TDA1420BB	80p	AD232	25p
SN76008	£1.50	TDA1420BC	80p	AD233	25p
SN76023N	£1.00	TDA1420BD	80p	AD234	25p

BF694	10p	2SK30A	10p
BF758	30p	BC107	10p
BF760	30p	BC108	10p
BF734	15p	BC109	5p
BF143	10p	BC113	10p
BF184	8p	BC114	10p
BFW11	20p	BC115	10p
BFX29	30p	BC116	10p
BFX84	25p	BC117	10p
BFY50	15p	BC119	20p
BFY52	20p	BC125	10p
BFY90	25p	BC126	10p
BL Y49	25p	BC139	10p
BPW41	25p	BC140	30p
BRX116	25p	BC141	25p
BRX43	15p	BC143	25p
BRX48X	10p	BC147	10p
BRY56	30p	BC148	10p
BSS68	10p	BC149	10p
BSY79	10p	BC153	10p
BSY95a	10p	BC154	10p
BTY80	20p	BC157a	10p
BSX19	17p	BC158	10p
BSX20	17p	BC159	10p
FT3055	30p	BC160/16	10p
TCF82	30p	BC171	10p
2N2940	5p	BC172	10p
2N2221	8p	BC173	10p
2N2222	8p	BC174	10p
2N2906	10p	BC183	10p
2N3055	40p	BC184	10p
2N3566	10p	BC204	10p
2N3702	10p	BC207	10p
2N3711	10p	BC212	10p
2N3583	50p	BC213	10p
2N3904	15p	BC214	10p
2N4355	10p	BC237	10p
2N4442	£1.00	BC238	8p
2N4444	£1.00	BC239	10p
2N5296	40p	BC250	8p
2N5983	40p	BC251	8p
2N6069	40p	BC252	10p
2N6109	40p	BC262	10p
2N6130	50p	BC263b	20p
2N6133	20p	BC294	30p
2N6348	20p	BC298	10p
2N6399	10p	BC300	30p
7X 2N6099 on heat sink	50p	BC301	20p
2SA437	20p	BC303	20p
2SB407 Sanyo TO3	10p	BC308	7p
2SB474	10p	BC309	7p
2SB566	30p	BC327	10p
2SC381	10p	BC328	10p
2SC458	50p	BC328/338 pair	15p
2SC515	10p	BC337	10p
2SC732	10p	BC338	10p
2SC733	10p	BC349b</	