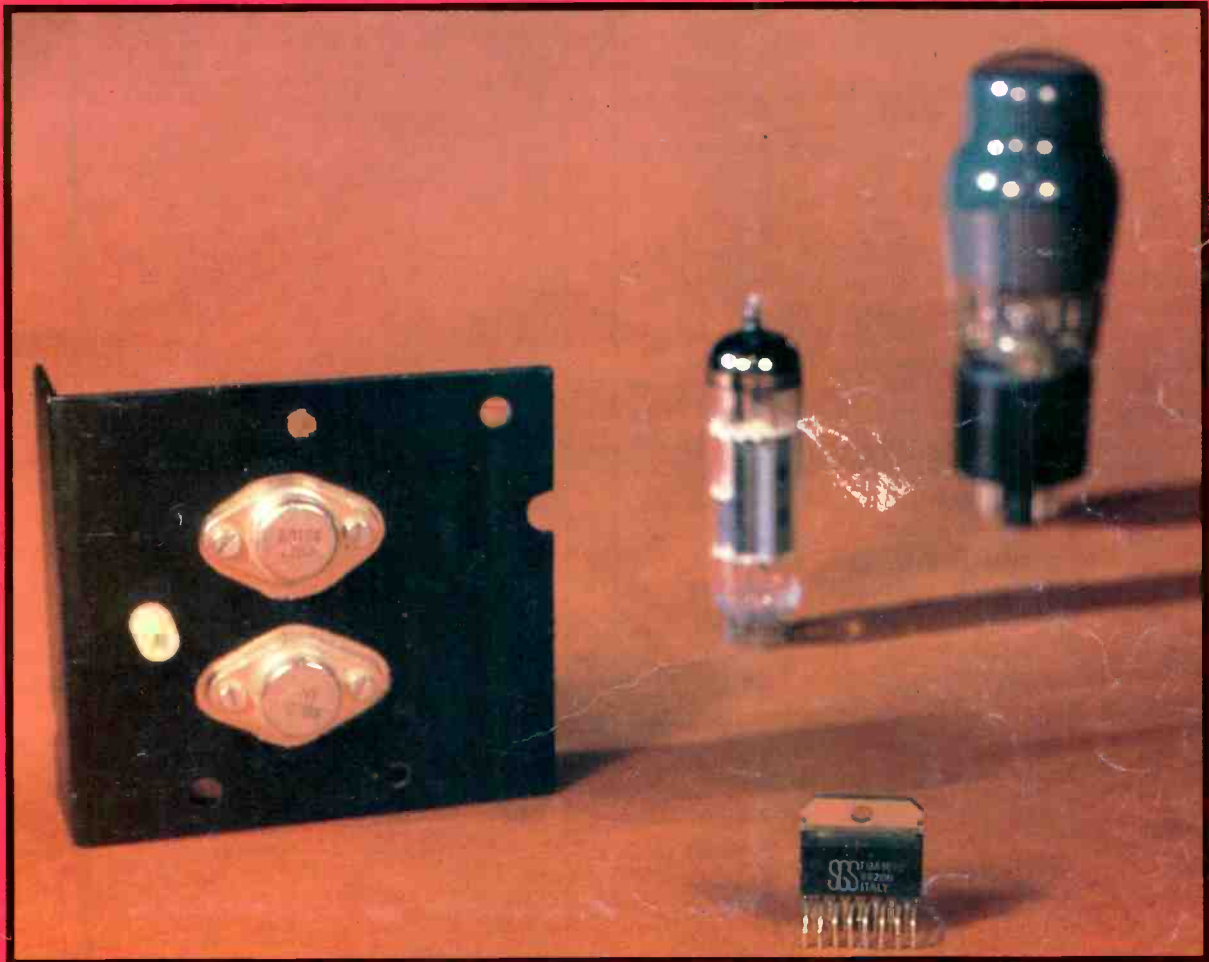


OCTOBER 1985

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50 **£1.10**

# TELEVISION

**SERVICING·PROJECTS·VIDEO·DEVELOPMENTS**



**Field Timebase Circuit Survey**  
**Philips G11 Fault Finding Chart**  
**TV Line Selector Unit**  
**Quick Checks on the Rank A823**  
**VCR Clinic • Test Report**  
**TV Fault Finding • DX-TV**

# MANOR SUPPLIES

**MKV PAL COLOUR  
TEST GENERATOR FOR TV & VCR.**

TEST  
DEMONSTRATIONS  
AT 172  
WEST END LANE




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**  
Case (10"×6"×2¼") app. **£7.40**  
Optional Sound Module (6MHz or 5.5MHz) **£3.90**  
Built & Tested in Case including Sound Module **£105.00**

SPECIAL TEST  
REPORT  
'TELEVISION'  
DEC. 1982

Post/Packing £2.50  
Add VAT 15% TO ALL PRICES

## PAL COLOUR BAR GENERATOR (Mk4)

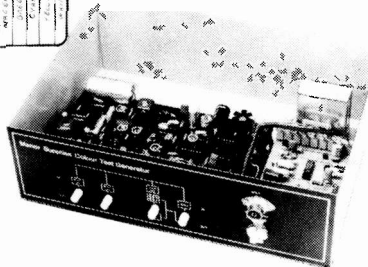

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

**PRICE OF MK 4 COLOUR BAR GENERATOR KIT  
£30.00. CASE £7.40. BATT HOLDERS £2.80. MAINS  
SUPPLY KIT £4.20 (Combined P&P £2.20).**

MK 4 (BATTERY) BUILT & TESTED £58.00 + £2.20 P & P.  
MK 4 (MAINS) BUILT & TESTED £68.00 + £2.20 P & P.  
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS £5.75.  
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

### GEC TELETEXT EXTERNAL ADAPTOR UNIT

Complete & ready for use. Converts any TV into a Teletext Receiver with Infra-Red Remote Control (incl. 25 Button Handset) new, boxed and fully tested. **£130.00** p.p. **£3.00**

### THORN TX9 MK2/3, TX10, teletext

Mullard Decoder panel + Interface **£35.00** p.p. **£1.80**  
THORN TX10, PHILIPS G11 PRESTEL  
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£48.00** p.p. **£2.50**

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15%

## TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF  
TECHNICAL EXPERTS

LOPTs, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

- PHILIPS G11 PANELS** (tested).  
Power, frame, IF, decoder **£18.00** each p.p. **£2.00**.  
Scan Panel **£28.00** p.p. **£2.80**.  
**PHILIPS G11 PANELS** ex rental (untested).  
Power, frame, IF, decoder **£10.00** each p.p. **£2.00**.  
**SPECIAL OFFER** Philips, Pye KT3 Series infra-red remote control handsets ex rental (untested) Teletext or normal versions available **£2.50** p.p. **80p** (5 for **£10** p.p. **£1.50**). CTX, K35 Teletext + Video **£5.00** p.p. **80p**.  
**THORN 9000** Fault Finding Guide **£1.00** p.p. **30p**.  
**THORN 9000** Remote Control Handset (2-button) **£10.00** p.p. **£1.00**.  
**TX10** Remote & Tuning control panel (1515) **£9.40** p.p. **£1.50**.  
**THORN TX10** Facia Control Panel incl. Infra Red Remote Control receiver **£7.50** p.p. **£1.50**.  
**THORN TX10** Series Facia Control Panel with 8 position Channel Selector **£5.00** p.p. **£1.50**.  
**PHILIPS UHF** Modulator (Audio & Video Input) **£15.00** p.p. **£1.00**.  
**SAW FILTER IF AMPLIFIER PLUS TUNER** complete and tested for T.V. Sound & Vision. **£28.50** p.p. **£1.20**.  
**THORN TX9, TX10** Saw Filter IF Panel. **£7.50** p.p. **80p**.  
**PAL DECODER KIT** (Video to RGB) for Monitors **£27.00** p.p. **£1.00**.  
**PAL ENCODER KIT** (RGB to Video) **£18.50** p.p. **£1.30**.  
**TELETEXT DECODERS** New & Tested Mullard VM 6101 **£30.00**, Texas XM11 **£40.00**, KT3 Tested **£30.00**, Untested **£5.00** p.p. **£1.60**.  
**TELETEXT 23** Button De-Luxe Handset with 5 yds Cable. **£2.50** p.p. **£1.20**.  
5V Stab. Power Supply **£3.80** p.p. **£1.20**.  
**CROSS HATCH UNIT KIT**, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. **80p**. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. **£1.40**.) **ADDITIONAL GREY SCALE Kit** **£2.90** p.p. **45p**.  
**UHF SIGNAL STRENGTH METER KIT** **£22.00** (VHF version **£24.00**). Alum. Case **£2.55**, De Luxe Case **£7.40** p.p. **£1.80**.  
**CRT TESTER & REACTIVATOR KIT** For Colour & Mono with Panel Meter Indicator - can be adapted for latest CRTs **£28.60** p.p. **£2.80**.  
**BUSH A823** Convergence, Time Base Panels **£5.00** each. p.p. **£1.80**.  
**BUSH Z718** BC6100 series IF Panel **£5.00** p.p. **90p**.  
**BUSH A816** IF Panel (Surplus) **£1.00**, 5 for **£4.00** p.p. **£1.40**.  
**GEC 2040** Decoder Panels, **£1.50** p.p. **£1.80**.  
**GEC 2110** PANELS Frame **£8.50** p.p. **£1.40**. Sound **£2.50** (tested) p.p. **80p**.  
**GEC 20AX** Switch Mode Power Supply **£5.00**, IF-Decoder **£12.50** p.p. **£1.80**.  
**PYE 691-7** CDA Panels. Makers tested stock. **£6.00** p.p. **£1.45**.  
**THORN TX9** Panels ex factory for small spares. Includes I.Cs & Semiconductors etc. **£3.00** p.p. **£1.80**.  
**THORN TX9** Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. **£2.80**.  
**THORN TX9** Panels ex factory salvaged complete cond. **£20.00** p.p. **£2.80**.  
**THORN TX10** T.B. Panels salvaged ex factory. **£15.00** p.p. **£3.00**.  
**THORN 3000/3500** Power supply P.C.B. **£3.50** p.p. **£1.00**.  
**THORN 8000/8500** IF/Decoder Panels salvaged **£3.20** p.p. **£1.80**.  
**THORN 9000** IF/Decoder Panels Salvaged. **£5.00** p.p. **£1.60**.  
**THORN 9000** Series. Long panel facia unit incl. 6 Position Channel Selector & Loudspeaker **£6.00** p.p. **£2.00**.  
**PHILIPS G8/G9** IF/Decoder Panels for small spares incl ICs **£2.50** p.p. **£1.60**.  
**G11 PANELS**, Ex Rental SCAN (incl LOPT) **£28.00** p.p. **£2.50** (tested).  
**G11 PANELS**, Power, Frame, IF, Decoder. **£18.00** each. p.p. **£2.00** (tested).  
**GRUNDIG 8630** Series Varicap Tuners **£5.00** p.p. **£1.00**.  
**VARICAP**, ELC1043/5 **£7.80** p.p. **80p**. Makers controls **PYE CT200** 4PSN **£7.50**, **BUSH 4PSN** **£4.80**, **DECCA 4PSN** **£5.80**, **6PSN** **£6.80** p.p. etc.  
**BUSH "TOUCH TUNE"** Varicap Control Z179, Z718 types **£3.80** p.p. **95p**.  
**VARICAP UHF-VHF** ELC2000S **£9.80**, **BUSH** **£7.80** p.p. **90p**.  
**VARICAP VHF** PHILIPS, **£6.90**. ELC 1042 **£7.90** p.p. **80p**.  
**UHF/625** TUNERS, many different types in stock. **DECCA** Bradford 5 position. **MULLARD** 4 position **£2.50**, **JAP Rotary** **£4.80** p.p. **£1.80**.  
**TV SOUND** IF Panels **£6.80** p.p. **£1.00**.  
**LOPT TESTER**, Service Dept approved **£15.90** p.p. **£1.20**.  
**LOPTS** New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins **80p**.
- |   |              |   |               |
|---|--------------|---|---------------|
| <b>BUSH MURPHY 774</b> series.....        | <b>£9.80</b> | <b>R.B.M. T20, T22</b> Bobbin .....       | <b>£5.60</b>  |
| <b>BUSH MURPHY A816</b> series.....       | <b>£9.80</b> | <b>DECCA</b> Bradford (state Mod No)..... | <b>£8.80</b>  |
| <b>FERG., HMV, MARCONI, ULTRA</b>         |              | <b>DECCA 80, 100</b> .....                | <b>£8.80</b>  |
| 1400, 1500, 1590, 1591.....               | <b>£5.90</b> | <b>GEC 2110</b> series.....               | <b>£10.60</b> |
| <b>THORN 1600, 1615, 1690, 1691</b>       | <b>£9.15</b> | <b>ITT CVC 5 to 9, CVC20</b> .....        | <b>£9.80</b>  |
| <b>GEC 2000 to 2038</b> series.....       | <b>£6.80</b> | <b>ITT CVC25, CVC30</b> series.....       | <b>£8.80</b>  |
| <b>GEC series 1 &amp; 2</b> .....         | <b>£8.00</b> | <b>ITT CVC45</b> .....                    | <b>£9.80</b>  |
| <b>INDEST 2024</b> EGB.....               | <b>£7.65</b> | <b>PYE 691-697</b> (state model no.)..... | <b>£10.00</b> |
| <b>IT/FKB VC200, 300</b> .....            | <b>£7.65</b> | <b>PYE 713, 715</b> .....                 | <b>£6.80</b>  |
| <b>PHILIPS 170, 210, 300</b> series.....  | <b>£7.65</b> | <b>PYE 725 (90F) 731 to 741</b> .....     | <b>£9.20</b>  |
| <b>PYE, INVICTA, EKCO, FERR.</b>          |              | <b>PHILIPS G8</b> .....                   | <b>£8.80</b>  |
| 368, 169, 569, 769 series.....            | <b>£7.65</b> | <b>PHILIPS G9</b> .....                   | <b>£10.80</b> |
| <b>SPECIAL OFFER</b>                      |              | <b>PHILIPS 570, 571</b> .....             | <b>£6.80</b>  |
| <b>DECCA 2024, 1700, 2000, 2401</b> ..... | <b>£3.80</b> | <b>PHILIPS KT3</b> .....                  | <b>£9.80</b>  |
| <b>GEC 21143/Junior</b> Fineline.....     | <b>£2.80</b> | <b>THORN 3000/3500</b> SCAN, EHT.....     | <b>£6.90</b>  |
| <b>PHILIPS 320</b> .....                  | <b>£2.80</b> | <b>THORN 8000, 8500, 8800</b> .....       | <b>£12.80</b> |
| <b>RBM A823</b> .....                     | <b>£4.80</b> | <b>THORN 9000 to 9600</b> .....           | <b>£12.90</b> |
| <b>GEC 2028, 2040, 2100</b> .....         | <b>£4.80</b> | <b>THORN 9800</b> .....                   | <b>£19.80</b> |
| <b>R.B.M. T20, T22</b> .....              | <b>£9.80</b> | <b>THORN TX9</b> .....                    | <b>£14.80</b> |

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO LOPTS.

**TRIPLERS** Full range available. Mono & Colour.  
**Special Offer:** GEC 2040/2100 EHT Tripler **£2.50** p.p. **£1.30**.  
6-3V CRT Boost Transformers for Colour & Mono **£5.40** p.p. **£1.20**.  
**THORN TX10** focus control **£8.80** p.p. **80p**.  
**THORN 8000** mains input choke **£6.80** p.p. **£1.40**.

CALLERS WELCOME AT SHOP PREMISES

THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED  
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS  
TELEVISION MAGAZINE PROJECT PARTS & REPLACEMENTS  
STILL AVAILABLE

Telephone 01-794 8751, 794 7346


## MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door  
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford)  
W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)

Access from all over Greater London.

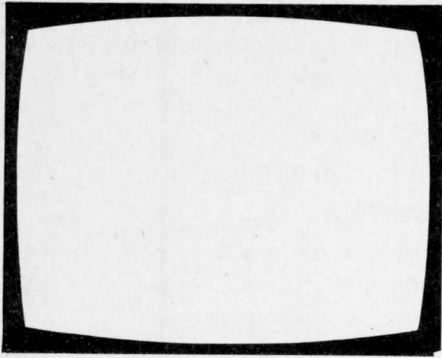Mail Order: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT  
PLEASE ADD VAT 15% TO ALL PRICES



# TELEVISION

October  
1985

Vol. 35, No. 12  
Issue 420

## COPYRIGHT

© IPC Magazines Limited, 1985. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

## SUBSCRIPTIONS

An annual subscription costs £13 in the UK, £15 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

## BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

## BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month

- 677 Leader**
- 678 Quick Checks: Rank A823 and Pye 725 Chassis** *S. Simon*  
How to deal quickly and efficiently with common faults on the Rank A823 series and Pye 725 CTV chassis.
- 680 Test Report** *Eugene Trundle*  
The MiniScope is an unusual soldering iron whose small bit can generate a great deal of heat, making it suitable for a wide variety of uses. A report on how it fared in day-to-day work on the bench.
- 683 The Lid off Microcomputers, Part 6** *Mike Phelan*  
A look at the sorts of faults that can arise in the computer itself and in peripheral equipment.
- 684 Letters**  
Including fault notes on the ITT CVC20/30 series chassis and two microcomputer programs.
- 686 Teletopics**  
News, comment and developments. How the first European DBS satellite, the French TDF-1, is likely to be financed and run.
- 688 VCR Clinic**  
Fault reports from J. Hopkins, Mick Dutton, William G. Lockitt and Philip Blundell, Eng. Tech.
- 690 Field Timebase Circuit Survey, Part 1** *S.W. Amos and E. Trundle*  
Start of a new series describing the techniques used in TV field timebase circuitry. This part deals with the basic drive and output waveforms and valve circuits from the pre-war era to the hybrid chassis of the early 1970s.
- 695 TV Fault Finding**  
Reports from Les Grogan, Larry Ingram and John Coombes.
- 698 The Tantrums of Tiny Tim** *Les Lawry-Johns*  
Tim got real mad when he found someone had done something naughty to a CVC5, then discovered that he was in terrible trouble.
- 699 Next Month in Television**
- 700 Line Selector Unit** *A.R. Bradshaw*  
A method of obtaining trigger pulses so that the lines with test signals during the field flyback blanking period can be examined on an oscilloscope. Also provides bright-up and X-scan signals.
- 702 Philips G11 Fault-finding Chart** *Dennis Apple*  
A comprehensive guide to faults in the Pye/Philips G11 chassis arranged in chart form for easy reference.
- 704 Long-distance Television** *Roger Bunney*  
Reports on DX conditions and reception and news from abroad, with notes on changes to the DTI's radio interference service and the US satellite TV scene.
- 707 Service Bureau**
- 708 Test Case 274**

OUR NEXT ISSUE DATED NOVEMBER WILL  
BE PUBLISHED ON OCTOBER 16

# P. V. TUBES

## HAVE MOVED

104 ABBEY STREET, ACCRINGTON, LANCBS BB5 1EE.

TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TRADE COUNTER CLOSED WEDNESDAY p.m.

Just phone your order through, we do the rest.

Buy with



Telephone: Accrington (0254) 36521  
Accrington (0254) 32611  
Telex: 635562 Griffin G (For P.V.)

SUPPLIERS OF TELEVISION COMPONENTS

VARICAP TUNERS	SWITCHES & ACCESS	DID YOU KNOW WE'VE GOT LOTS OF NEW THINGS!	PHILIPS KT3 SPECIFICS	SPECIFIC COMPONENTS	
ELC1043-05 8.40 ELC1043-06 8.40 ELC2003 16.50 Philips G8/G9 10.50 Philips G11 (U321) 8.50 U322 7.20 U341 9.50	On/off gen. purpose 4A 75 G8 on/off 1.38 G11 on/off 1.58 G11 on/off remote 1.58 Gen. purpose rotary 66 Thorn Tx 9/10 1.06 GEC 2040 98 Thorn 1591 push on/off Rank tuner buttons 2.90 1 1/2" x 1/2", 2" x 1/2", 2" x 3/8"	Decca speaker 8R 3.75 B+K tube bases Dynascan No. 3 9.50 No. 15 16.44 No. 5 9.09 No. 19 10.83 No. 6 11.08 No. 21 14.40 No. 8 10.08 No. 23 13.86 No. 13 11.11 No. 24 27.07 No. 14 16.63 No. 25 12.57 LS 7" x 3 3/8" speaker 4.25 C15 computer cass. 35 C20 computer cass. 33 5 1/4" floppy disc s/s/s/d 1.61 15R fused res. G9 55 G11 line in coil 2.95 G11 pot G2 R.G.B. 5.30 G11 line scan panel 54.00 G11 power panel 37.50 G11 timebase panel 37.50 G11 bridge trans. 97 G11 EW correct. coil 1.95 G11 final anode lead 1.50 G11 focus unit 5.80 G11 39R 3W resistor 60 G11 RGB 10G diodes 60 Televista opt converta 37.20 G11 47K pot plus switch 65 Dynascan 399	KT3 posistor 1.50 Mains electrolytic 225/25 380V 2.50 Selector unit Mod. 933 13.42 On/off switch Mod. 933 3.20 Tripler 10.65 Luminance chroma panel 24.00 2003 IF module 14.95 U321 IF module 13.50 R.G.B. panel 10.38 Sound panel 8.50 Power panel 10.60 Mains input panel 14.30 Line sync panel 10.20 Mark II chroma panel 16.50 Sound module 8.50 LOPT 9.70 Focus unit 3.50 Infra Red Teletext remote hand set 18.87	Philips G8 knobs sm/rg 50 90° transductor 2.60 Thorn 1591 speakers sm 6.20 lg 6.20 Thorn 1500 controls 59 390K frame 470K line contrast 1k5 each Focus control Thorn/GEC 2.95 Thorn 9000 focus unit 5.95 Thorn 8500 focus unit 4.75 Thorn TX10 focus cont. 9.80 Decca bridge trans. 1.97 Decca 30 width cont. 50 Decca 2M2 HT cont. 25 Pye 731 HF choke 6.50 Delay lines DL20, DL60, DL700 DL50 2.20 CRT tube base 1.40 EHT final anode cap 63 6.3V CRT boost trans. 5.80 Focus rod 1.25 Focus holder 2.00 AFC unit G8 8.82 IF gain module 9.00 C.O.A. panel 20.00 G8 rear conv. panel 23.00 Philips K35 Tuner drawer 10.00	
<b>PUSH BUTTON ASS.</b> Decca 4 way 6.88 6 way 7.50 GEC 2110 6 way 7.98 GEC Slim 6 way 6.50 GEC/ITT/PYE 7 way 14.50 Pye 4 way (713/15) 9.00 Pye 6 way (207/715) 16.00 Pye 697 repair kit 9.00 Pye 725-735 11.00 Pye 725-735 with tuning head 14.60 Philips G8 (early) 15.50 Philips G8 (late) 13.90 Rank A823 10.75 Rank T20A 9.75 Hitachi 4 way 10.75 Philips G11 unit 26.50 Philips KT3 14.50 Philips KT30 10.30 ITT CVC 8/9 (mod) 12.00 ITT 6 way with VCR 8.90 Thorn 9000 switchback 5.30 Decca 7 way piano key replacement kit 19.50	<b>EAGLE MULTIMETERS</b> KEW 7N 7.50 KEW 14 9.95 KEW 20 14.50 EM5 11.95 EM10 13.95 MM50 31.25 Bench Meters MM100 44.50 MM150 89.00 T1206 intercom 8.50 MMC100 21.95 Case TS350 25.00	<b>SUNDRY EQUIPMENT</b> Test Lead Set 4.20 Degaussing Coil Stick 17.00 Signal Injector 4.00 Elect. Circuit Tester 1.50 5A Choc Bloc (12) 40 Fuse Wire 5A, 15A, 30A 05 4-way 13A Mains Conn. 5.00 Safe Block (mains) 8.50 13A Plug Top (box 10) 4.80 Probes (x10) 10.90 Probes (x1) 10.90 Bell Wire (100m) 5.00 Mains Cable (circular 100m) (2 core) 10.75 (3 core) 13.25 Factory recon. Avo meters 119.00 Avo Batteries 2.95 Vero Board 2.59 Isolating string. 500vA 240V 40.00 Solder 500g 7.00 D.I.Y. Solder 45 Solder Sucker 6.50 Nozzles 81 Trim Tools 16 Plastic Metal End 30	<b>K30 SPECIFICS</b> K30 LOPT 17.50 K30 focus unit 2.90 K30 EHT lead 8.30 Selector unit 1002 (early) 11.20 TMS 1000 panel 1234 13.00 URO decoder panel 1234 46.00 Power supply 1234 23.50 A1 gun switches 7.00 On/off switch 2.60 Selector unit 1002 (late) 9.90 Hand set 1201 16.00 Hand set 1234 16.00 Diode ZTX 33B 90 DL 20 delay line 2.20	<b>PLUGS AND SOCKETS</b> 5 pin DIN plugs 180° 20 5 pin DIN chassis sockets 180° 28 5 pin DIN line sockets 180° 28 5 pin DIN plugs 360° 28 5 pin DIN chassis sockets 360° 28 5 pin DIN plugs 360° 28 6 pin DIN chassis sockets 28 6 pin DIN line sockets 28 7 pin DIN plugs 35 7 pin DIN chassis sockets 38 7 pin DIN line sockets 38 8 pin DIN plugs 56 8 pin DIN chassis sockets 64 8 pin DIN line sockets 65 Phono plugs 12 Phono chassis sockets 10 Phono line sockets 28 2.5mm Jack plugs 11 2.5mm Chassis sockets 14 2.5mm Line sockets 17 3.5mm Jack plugs 15 3.5mm Chassis sockets 17 3.5mm Line sockets 24 6.3mm Stereo jack plugs 25 6.3mm Stereo chassis sockets 25 6.3mm Stereo line sockets 28 Standard mono jack plugs 18 Loud speaker plugs 2 pin 10 I.D.C. plugs 36 conn. 5.90 I.D.C. sockets 36 conn. 6.90 BNC plugs 1.15 Coax plugs Each 18p Pack of ten 1.80 Line connectors 16 Double ended female sockets 1.20 Car aerial plugs 18 PL259 with reducer 1.30 Reducers for the PL259 16 FM plugs 25	
<b>SERVICE AIDS</b> SERVISOL Freeze-It 1.14 SUPER SERVISOL 98 SERVISOL Foam Cleanser 96 SERVISOL Plastics Seal 1.08 SERVISOL Silicone Grease 1.20 SERVISOL Tubes Silicone Grease 1.64 SERVISOL Aero Klene 90 SERVISOL Aero Duster 1.20 SERVISOL Excel Polish 92 SERVISOL Video Head Cleanser 86 Super 4 1.62 Fire Extinguisher 640G 2.86 Heat Sink Compound 25G 1.08 Silicone Rubber Tube 110G 2.98 Solda Mop standard reel 74	<b>ANTEX SOLDERING EQUIPMENT</b> C15W Iron 240V 6.20 C240 Element 2.75 Bits 102 1.10 106 1.10 820 1.10 821 1.10 CS17W Iron 240V 6.40 CS240 Element 2.75 Bits 1100 1.10 1101 1.10 1106 1.10 XS25W Iron 240V 6.50 XS240 Element 2.75 Bits 50 1.10 51 1.10 Temp. Controlled 30W Iron CSTC 16.95 40W Iron XSTC 16.95 Unit for above TCSU1 68.95 Stand 2.10 MLXS Auto Repair Kit 8.40	<b>WELLER</b> Heat gun 12.00 Heat gun tips (pair) 57 3/16" Iron tips 25W (MT5) 57	<b>DATA BOOKS (Zero VAT)</b> Pair of A-Z/2N2S TVT80 LIN IC Books (data only not equiv.) 8.50 LIN1 5.95 2M Fly Lead 70 4M Fly Lead 1.20 10M Fly Lead 1.90 Figure 8 Mains Lead 62 Computer to TV 97 7 pin din to 5 pin din 98 5 pin din to 5 pin din 98	<b>CASSETTE DRIVE BELTS</b> 35m 35 46mm 37 57m 37 66m 39 110m 59 76m 43 90m 43	
<b>ELECTROLUBE PRODUCTS</b> Electrolube Adhesive 62 Elect. cleaning solvent 1.62 Freezer 1.49 Foam cleanser 1.12 Heat transfer compound 1.14 Silicone compound 1.94 Special contact fluid (Snorkell) 3.20 Permagard 1.52 Elec. mech. lubricant pen 74	<b>LABGEAR</b> CM7261 Power Unit 12V 11.24 CM7262 Reg. Power Unit 12V 12.25 CM7060 MHA 10db 12V W/B 9.96 CM7065 VHF/UHF MHA W/B 12V 14.34 CM7066 13.38 CM7067 UHF 12V MHA (Specify A-B or C/D) 10.72 CM7068 UHF 12V MHA High Gain (Specify A-B or C/D) 15.95 CM7053 Behind Set UHF Amp. (Mains) 13.01 CM7054 Behind Set UHF Amp. (Battery e.g. Caravans) 10.42 CM7043 Second Set Amp. UHF 12.12 CM7093 Behind Set UHF Amp. 3 Sets 15.27 CM7063 Dist. Amp. VHF/UHF 17db/output 12V 22.17 CM7108 VHF/UHF 8+1 Dist. Amp. 43.26 CM9700 27mhz CB Suppress. 4.05 CM6011 Outdoor Splitter (2 way) 7.83 WB 7.83 CM9003 Flush Single Outlet 1.47 CM9010 Flush Twin Outlet 1.95 CM9034 UHF Group Filters with DC 1.70 Through Pass (state A/B/CD) 7.69 CM6006 6 Way Passive Splitter 10.97 CM7042 TV Games Combin. 2.95 CM9009 Flush TV/FM Outlet 3.05 CM7091 Col. Bar Gen. 121.80 CM9006 VHF/UHF Diplexer 3.60	<b>OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, LOCAL AUTHORITIES ETC.</b>	<b>WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER AERIAL EQUIPMENT</b> Outdoor Splitter 5.50 Plastic Tape 50 F.M. Plugs 25 Set Top Aerial 2.30 Loop Aerial 1.00 Mast Amp/Power Unit WB 18.00 Aerial Isolator Kit 2.08 Attenuator 6dB, 12dB, 18dB 1.80 27Mhz Filter 50dB 2.10 Cable Clips 7mm per 100 1.18 Single Outlets 80 Surface Splitter 1.70 A Splitter 70 100M Coax 15.00 Coax Plugs per 10 1.80 H.P. Bolts 30 J Bolts 25	<b>SHARP VIDEO HEADS £55</b> VC2300 VC6300 VC7300/7700/7750 VC8300 VC220/381/383/388/9100/9300/9500 VC3300/9700 <b>SANYO VIDEO HEADS £53</b> VTC 9300/9500 VTC 5300/5000 VTC 5350 VTC 5500 VTC 9350	<b>REMOTE CONTROL HAND UNITS</b> Decca 100/101 Ultra Sonic Non Teletext £23.80 Grundig Telepilot 12 Series Infra Red £13.87 Grundig Telepilot 8 Series Infra Red £25.10 Grundig Telepilot 160 Series Infra Red £25.10 Grundig Telepilot 300 Infra Red £18.87 Philips KT3/K30 Infra Red Non Teletext £18.87 Philips G11 Ultra Sonic Non Teletext £22.00 Philips G11 8 Way Infra Red Teletext £23.80 Philips G11 Ultra Sonic 31 buttons £27.00 Philips G11 Ultra Sonic 2 function £21.00 Thorn TX10/JVC Infra Red Teletext £16.87 Philips KT3 Infra Red Teletext Remote Hand Set £18.87 KT3/K30 Teletext Remote £16.00
<b>VIDEO</b> Video care kits 3.50 VHS E30 video tape 3.06 VHS E60 video tape 4.00 Scotch E120 video tape 5.00 E180 video tape 4.50 Beta L500 video tape 4.90 Beta L750 video tape 5.80 VCC 240 6.20 VCC 360 8.30 VCC 480 10.21 Philips LVC 1700 1200 15.10	<b>VIDEO HEADS</b> 3HSS VHS 32.50 4HSS VHS 32.80 PS3B Beta/Sony 42.00	<b>VIDEO RECORDER HEADS</b> Philips V2000 57.00 Philips 1700 57.00 Video lamps 1.30 3V23 Cassette Lamp with plug 1.95	<b>VIDEO DRIVE BELT KITS</b> JVC HR3330/3600 4.50 JVC HR3360/3660 4.50 JVC HR7650 4.50 Panasonic NV300 4.50 Panasonic NV7000 4.50 Sony SL7/SL17 4.50 Sony SL8000/8080 4.50 Toshiba V7540 4.50 Ferguson HR3330/3600 4.50 Video head cleaner 86 Sanyo video motor 20.00	<b>IC equivalent booklet £3.25 and transistor equivalent booklet £3.25</b>	<b>REMOTE CONTROL TESTER £29.94</b>
<b>AUDIO HEADS AND MOTORS</b> Mono record/playback 4.32 Stereo playback 4.79 Stereo record/playback 4.99 Stereo record/playback (Dolby) 6.90 Mono/stereo erase 2.25 <b>Electronic/rotation clockwise motors</b> 6V MD6515 4.95 9V MD9516 4.95 12V MD12517 4.95	<b>STATIONERY</b> Service Call Pad (100) 1.99 Repair Ticket (100) 3.90 Job Card (100) 2.50 Rental Payment Card (50) 3.50 H.P. Agreements (100) 3.50 Maintenance Agreement (100) 3.50 Rental Agreements (100) 3.95	<b>ANTIFERRENCE</b> SB11 Splitter 2.37 COB11 Outlet 96 CS1000 Combiner/Splitter 6.15 PU1240 Power Unit 11.65 UP1300 MHA 9.09 XS2U Xtraset 14.56 4 way VHF/UHF Amp 48.71 6 way VHF/UHF Amp 50.68 XG8 High Gain Aerial A-B-CD-WB 17.10	<b>WEILA'S SURPRISES</b>	<b>REMOTE CONTROL TESTER £29.94</b>	

# P. V. TUBES

TEL: 0254  
36521/32611

104 ABBEY STREET, ACCRINGTON

T.T.L. 74LS SERIES			
74LS00	58 74LS37	35 74LS92	65 74LS160
74LS02	58 74LS38	35 74LS93	60 74LS161
74LS03	58 74LS40	35 74LS107	80 74LS162
74LS04	58 74LS42	80 74LS109	58 74LS163
74LS05	58 74LS44	85 74LS112	50 74LS164
74LS08	58 74LS48	83 74LS114	44 74LS165
74LS09	58 74LS49	33 74LS114	70 74LS173
74LS10	58 74LS51	30 74LS123	80 74LS174
74LS11	58 74LS54	43 74LS125	85 74LS175
74LS13	57 74LS55	60 74LS126	60 74LS191
74LS14	46 74LS73	60 74LS132	63 74LS192
74LS15	33 74LS74	65 74LS138	83 74LS193
74LS20	35 74LS75	65 74LS139	65 74LS194A
74LS21	35 74LS76	65 74LS151	85 74LS197
74LS22	35 74LS78	65 74LS153	85 74LS240
74LS26	44 74LS83A	89 74LS155	65 74LS241
74LS27	35 74LS86	39 74LS156	1.02 74LS242
74LS30	35 74LS85	98 74LS157	1.02 74LS243
74LS32	90 74LS90	1.22 74LS158	65 74LS244

VOLTAGE REG.	
7805	78
7808	78
7812	78
7815	78
7818	78
7824	78
78L05	68
78L08	68
78L12	68
78L24	68
7905	98
7906	98
7908	98
7912	98
7915	98
7918	98
7924	98
79L05	72
79L12	72
79L15	72
79L24	72

'4000 B' SERIES CMOS			
4001B	21 4029B	21 4068B	22 4510B
4002B	21 4032B	39 4069B	22 4511B
4008B	72 4035B	64 4070B	22 4512B
4011B	31 4038B	90 4071B	40 4513B
4012B	21 4040B	1.04 4072B	22 4514B
4013B	30 4042B	80 4073B	22 4515B
4014B	74 4043B	99 4075B	22 4516B
4015B	76 4044B	72 4076B	80 4518B
4016B	42 4046B	58 4077B	80 4518B
4017B	66 4047B	71 4078B	22 4519B
4018B	72 4049B	71 4079B	22 4520B
4019B	70 4050B	71 4081B	1.68 4522B
4020B	76 4051B	96 4093B	1.56 4526B
4021B	70 4052B	32 4099B	1.20 4527B
4022B	70 4053B	32 4160B	72 4528B
4023B	21 4060B	72 4161B	72 4529B
4024B	50 4066B	72 4162B	72 4530B
		72 4163B	72 4531B
		96 4502B	72 4532B
		43 4505B	1.88 4536B

I.C. SOCKETS	
DIL TO DIL	
8 way	22
14 way	29
16 way	32
18 way	32
20 way	32
22 way	32
24 way	34
38 way	45
40 way	84
DIL TO QUIL	
14 way	32
16 way	34
18 way	37
QUIL TO QUIL	
14 way	32
16 way	36

MAINS DROPPERS	
DECCA 20	2.48
DECCA 27R/47R	1.40
DECCA 56R/68R	1.40
R.B.M. A823 56R/68R	94
R.B.M. 161	82
GE 2000/2018	70
GE 27840	64
PYE 725/31 3R0/56R/27R	1.84
PYE 725 56R/27R	1.04
PHILIPS 210/5050 30R/125R/2K85	1.75
PHILIPS 210/5051 -118R/148R	93
PHILIPS G8/5081 47R Section	50
PHILIPS G8/5083 2R2/68R	95
THORN 1400	1.20
THORN 1500	1.38
THORN 1600	1.77
THORN 3500	94
THORN 8000	1.24
THORN 8500	1.36
THORN 9800	1.30
DECCA 3R5	96
DECCA 2R9 Modulohm	60

NEW VALVES	
30FL2	1.70
EF183	99
EF184	1.09
EH90	1.02
EL34	3.50
EL84	1.05
EY88/7	5.28
EY800A	6.5
EZ80/1	5.6
GY501	1.45
GZ34	3.50
KT66	8.50
KT77	8.50
KT88	12.00
PC92	3.00
PC97	1.65
PCC85	8.50
PCF80	1.00
PCF85	1.80
PCF86	1.30
PCF87	1.60
PCF88	1.38
PCF89	1.13
PCF90	1.12
PCF91	1.12
PCF92	1.12
PCF93	1.12
PCF94	1.12
PCF95	1.12
PCF96	1.12
PCF97	1.12
PCF98	1.12
PCF99	1.12
PCF00	1.12

THER- MISTORS	
VA1104	75
VA1040	75
VA8650	55
VA1039	35
GE C Dual	69
Posistor 1.68	
GE C Dual	69
2 0 4 0	
(CK1)	1.98

CRYSTALS & FILTERS	
6Mhz	74
5.5Mhz	74
4.3Mhz	1.30
8.8Mhz	1.30
9.94Mhz	6.00
10.692Mhz	6.00

MULTITURN POTS	
100K	55
GE C TCE	55
PHILIPS G8	55
DECCA, RANK	55

THERMAL CUT OUT	
THORN 3000 2A Metal	2.20
GE C 2040 Metal	2.50

L.E.D's	
5mm Red, Green, Yellow	14
T1 3/4 Amber	22
T1 3mm Red, Green, Yellow	14
Flashing Red COX21	62
COX22	66
Panel Clips 3mm	4
5mm	4

LINE OUTPUT TRANS.	
R.B.M. T20A	13.95
R.B.M. A774 Mono	11.74
R.B.M. Z179	15.00
R.B.M. Z718 22"	19.50
PHILIPS 320	8.70
PHILIPS 210/300 Mono	10.00
PHILIPS 68	8.75
PHILIPS G9	7.75
PHILIPS G11	13.50
PYE 697 (Printed)	14.50
PYE 713/731	10.00
PYE 725 90°	10.50
PYE 169	10.00
DECCA 80	8.58
DECCA 100	8.58
DECCA 1700	9.00
DECCA 1730	8.58
DECCA 2230	8.58
GE C 2110	16.75
GE C 2040	9.50
ITT CVC 19	10.85
ITT CVC 25/30/32	8.65
ITT CVC 20	8.60
THORN 3000 EHT	9.95
THORN 3000 SCAN	7.95
THORN 8000	11.33
THORN 8500	11.33
THORN 3000/3500	11.33
Mains	10.00
THORN 1591	8.68
THORN 1691	9.68
THORN TX10	15.00
THORN 1615	9.75
PHILIPS KT3	9.70
RANK BUSHRANGER Early T16A	£10.00
RANK BUSHRANGER Late T18A	£10.00
PYE 741	8.20
B+0 (2000, 3000)	12.70
B+0 (3000 EHT)	18.90
ITT CVC 45	9.50

RECTIFIER TRAYS	
THORN 950 Mk II	4.25
THORN 1400 3 Stick	5.20
THORN 1500 3 Stick	5.20
THORN 1500 5 Stick	5.29
THORN 1500	4.95
THORN 3000/3500	7.98
THORN 8000	5.28
THORN 8500/8800	7.15
THORN 9000	8.70
DECCA 1730/1830	4.48
DECCA 30	6.76
DECCA 80	6.60
DECCA 100	7.50
UNIVERSAL ITT or REMO	6.00
GE C 2100	7.40
GE C 2200 (20AX)	6.50
GE C 2040/2028	6.60
GE C 2110 Pre Jan '77	7.00
GE C 2110 Post Jan '77	7.00
PHILIPS G8 Short Focus Lead	6.75
PHILIPS G8 Long Focus 550	6.75
PHILIPS G9	6.37
Pye/Philips K3 Tripler	10.65
PYE 691/3	6.58
PYE 713/4 Lead	8.79
PYE 713 Doubler 5 Lead	8.79
PYE 731/725	7.60
R.B.M. A823 (plug in) AV	7.60
KORTING (similar to Siemens TVK1)	7.32
ITT KB CVC5/9	6.90
ITT KB CVC20/25/30 (Mullard)	6.65
RRI T20	6.80
ITT CVC45	8.65

REPLACEMENT ELECTROLYTICS	
PYE 169 (200/200/100/32)	3.74
PHILIPS 320 (400/400/200V)	3.74
DECCA 30 (400/400/350V)	3.74
DECCA 80 (400/350V)	4.37
DECCA 100 (800/250V)	1.00
PHILIPS G8 (600/300V)	2.53
PHILIPS G9 (600/300V)	2.44
PHILIPS G11 (470/250V)	3.19
PYE 691/7 (200/300/350V)	2.97
PYE 731 (600/300V)	2.55
RBM A823 (2500/2500/30V)	1.83
RBM A823 (600/300V)	3.12
RBM Z146 (300/300/350V)	3.91
RRI T20A (220/400V)	2.20
ITT CVC5/9 (200/200/75/25)	3.28
ITT CVC 20 (220/400V)	2.20
GE C 2110 (600/250V)	2.14
GE C 2040 (1000/2000/35V)	1.31
GE C 2040 (300/300/150/100/50)	4.51
THORN 3500 (400/40V)	3.3
THORN 950 (100/300/100/16/275V)	2.02
THORN 1400 (150/100/100/150/320V)	3.07
THORN 1500 (150/150/100/300V)	2.42
THORN 1500 (12/300V)	3.5
THORN 3500 (175/100/100/400/350V)	3.06
THORN 3500 (1000/63V)	95
THORN 3500 (1000/70V)	95
THORN 8000/8500 (2500/2500/63V)	3.72
THORN 8000/8500 (700/250V)	2.55
THORN 8000/8500 (400/350V)	2.82
THORN 9000 (400/400V)	3.61
GE C (200/200/150/50)	2.91
PHILIPS 69 2200/63V	1.38
THORN 4700 P/C 25V	1.32
THORN 1591/1691 4700/25V	1.32
G11 Capacitor 7N5 1500V	1.40

CAPACITORS AXIAL					
Volts	Mfd	Price	63V	1	12
6V3	33	9		2.2	12
10V	22	10		4.7	12
	47	10		10	11
	100	10		15	12
	220	15		22	13
	470	20		47	19
16V	33	11		100	23
	68	11		220	37
	220	16		470	49
	1000	27		1000	85
25V	3300	53		2200	1.10
	10	11	100V	10	13
	22	13		22	15
	47	15		47	20
	100	15		100	36
	220	29		220	70
	470	30	450	1	33
	1000	55		4.7	30
	2200	59		10	30
40V	4700	98		22	65
	10	10		33	75
	22	10	500	10	32
	400	48	600	0.1	41

DISC CERAMIC CAPS	
8kV (12kV)	
200pF	40p
150pF, 220pF, 180pF, 250pF	
63V/100V	
A range of pref. values 22pF-4700pF	12p

POLYESTER CAPS	
250V 0.01mF	12p
0.1mF	
0.22mF	
400V 0.01mF	12p
0.1mF	
0.22mF	

TANTALUM CAPACITORS		
6.3V	47mF	42
	100mF	90
16V	10mF	28
	22mF	28
	47mF	1.03
25V	22mF	46
35V	0.1mF	13
	0.22mF	13
	0.47mF	13
	1mF	13
	2.2mF	17
	4.7mF	26
	10mF	57

FUSES	
1 1/4" QUICK BLOW	
100ma	73
250ma-500ma-750ma-1A	60
1.5A-2A-2.5A-3A-5A	60
1 1/4" ANTSURGE	
250ma, 500ma, 630ma, 750ma, 850ma, 1A, 1.25A, 1.5A, 2A	1.70
2.5A, 3A, 5A	2.70
20mm ANTSURGE	
80ma	4.80
100ma	2.50
160ma, 200ma	2.20
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.6A, 2A	1.60
2.5A, 3.15A, 4A, 400ma, 5A	1.90
20mm QUICK BLOW	
100ma, 250ma, 500ma, 630ma, 800ma	90
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	60
1" MAINS	
2A, 3A, 5A, 10A, 13A	1.00

NEW MONO TUBES	
MULL. A31/510 110° 12"	18.50
MULL. A34/510 110° 14"	20.00
A50/120WR 110° 20"	18.50
A61/120WR 110° 24"	20.

# P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US

104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.

Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

## HOW TO ORDER

ADD 75p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degausers, coils please allow £1.30 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

## SEMICONDUCTORS

AC107	35	BC558	9	BF355	56	R2265	1.50
AC126	30	BCY72	13	BF362	68	R2322	62
AC127	32	BD115	45	BF363	72	R2323	67
AC128	32	BD116A	65	BF371	30	R2461	1.50
AC128K	40	BD124P	79	BF392	35	R2540	2.80
AC141K	39	BD131	50	BF422	34	RC4558	2.20
AC142K	38	BD132	49	BF423	46	RCA16334	90
AC176	35	BD133	60	BF435	35	RCA16029	99
AC176K	35	BD135	38	BF457	35	RCA16039	99
AC186	41	BD136	38	BF458	43	RCA16041	94
AC187	38	BD137	38	BF459	43	RCA16044	86
AC187K	38	BD138	35	BF460	46	RCA16334	90
AC188	35	BD139	35	BF460 = BF462	86	RCA16335	90
AC188K	39	BD140	44	BF470	66	RCA16957	2.88
AD143	82	BD144	1.70	BF470	10	TIC45	2.88
AD161	54	BD150	60	BF597	10	TIC46	60
AD162	54	BD159	65	BF757	54	TIC46	60
AD16162 MP	1.15	BD166	62	BF758	54	TIL32	65
AF106	49	BD179	70	BF839	27	TIL78	48
AF114	49	BD182	1.20	BF840	30	TIP29C	43
AF118	1.20	BD183	75	BF849	27	TIP30A	47
AF121	1.20	BD201	85	BF879	85	TIP30C	43
AF124	48	BD202	91	BF890	1.74	TIP31C	52
AF125	46	BD203	80	BF742	39	TIP32C	46
AF126	46	BD204	99	BF743	39	TIP33B	75
AF127	38	BD222	46	BFW10	60	TIP34B	1.06
AF139	58	BD223	56	BFX29	40	TIP41C	47
AF178	1.54	BD225	47	BFX84	42	TIP42C	50
AF239	4.90	BD232	68	BFX85	30	TIP47	70
AL102	4.90	BD233	60	BFX86	30	TIP120	65
AU106	2.50	BD234	63	BFX88	46	TIP2955	90
AU113	5.20	BD235	60	BFY50	30	TIP3055	63
BC107	20	BD236	65	BFY51	30	TIS91	21
BC108	20	BD237	67	BFY52	24	TU106/02	1.80
BC109	20	BD238	65	BFY90	24	2N696	21
BC114	12	BD243	85	BR100	34	2N918	82
BC115	17	BD244	85	BR101	45	2N905	51
BC115A	16	BD410	79	BR101	45	2N2904	28
BC117	30	BD434	74	BR103	83	2N3054	60
BC118	24	BD437	86	BR303	1.46	2N3055	60
BC119	36	BD438	94	BRC4443	94	2N3702	11
BC139	26	BD507	92	BRC4444	98	2N3703	10
BC140	32	BD508	56	BRY39	56	2N3705	10
BC141	26	BD509	55	BRY55	45	2N3706	10
BC142	30	BD510	60	BRY56	57	2N3708	17
BC143	31	BD278A	81	BSR59	1.80	2N5294	48
BC147	13	BD517	80	BSV57B	89	2N5296	48
BC148	9	BD520	75	BT100	1.65	2N5298	69
BC149	12	BD535	82	BT101	1.20	2S837	1.86
BC157	16	BD696A	1.49	BT102/500	1.20	2N5496	53
BC158	16	BD697	1.24	BT106	1.60	2N6107	75
BC159	15	BD695	1.39	BT108	1.69	2N6109	81
BC160	52	BD698	1.50	BT109	99	2SA175	1.98
BC161	28	BD707	95	BT116	1.21	2SC495	1.10
BC170B	15	BDX32	2.10	BT119	3.66	2SC496	1.31
BC171	15	BF115	38	BT120	3.66	2SC643A	1.50
BC172	15	BF117	36	BT121	2.20	2SC1096	1.72
BC173	12	BF125	26	BU104	1.20	2SC1172Y	2.20
BC174	10	BF127	47	BU105	1.58	2SC1173Y	1.69
BC177	27	BF154	23	BU108	1.80	2SC1306	2.73
BC178	26	BF158	18	BU124	1.90	2SC1307	3.00
BC182L	9	BF160	27	BU126	1.75	2SC1449	1.67
BC183L	12	BF167	24	BU204	1.50	2SC1520	68
BC184L	14	BF173	22	BU205	1.42	2SC1678	2.67
BC186	35	BF177	52	BU206	1.80	2SC1909	2.90
BC187	25	BF178	52	BU208	1.60	2SC1953	1.44
BC204	10	BF179	46	BU208A	1.65	2SC2028	1.82
BC208	13	BF181	39	BU208D	2.20	2SC2029	2.60
BC209	10	BF182	36	=BU800	2.20	2SC2078	2.90
BC212	13	BF183	36	BU208.02	2.10	2SC2091	1.34
BC213	13	BF184	36	BU326A	1.75	2SC2166	2.73
BC214	10	BF185	36	BU407	1.70	DEC1	2.20
BC237	14	BF194/394	36	BU426	3.07	DEC2	2.20
BC238	14	BF195	36	BU500	2.30	THY15/80	2.20
BC252A	12	BF196	16	BU526	2.46	THY15/85	2.20
BC261	18	BF197	16	BU508	3.20	BUW81A	3.84
BC262	18	BF198	16	BU806	1.40	T6006V	1.50
BC300	50	BF199	21	BU807	2.94	T6021V	90
BC301	53	BF200	35	BUJ84	1.45	T6022V	1.80
BC303	33	BF224	25	BUX84	1.50	T6026V	90
BC307	20	BF225	25	E1222	45	T6027V	63
BC308	25	BF241	25	MCR101	45	T6028V	66
BC323	99	BF256	55	MCR220	1.50	T6029V	3.98
BC327	18	BF257	28	ME0411	20	T6034V	81
BC328	18	BF258	25	MJE340	68	T6036V	90
BC337	18	BF259	35	MJ3000	50	T9002V	1.12
BC338	18	BF262	84	MJ3000	1.98	T9003V	60
BC461	30	BF263	75	MFS492	35	Transistor mounting kit TO66, TO3, TO220AB	30
BC547	13	BF271	24	MR814	45		
BC548	13	BF273	24	MR854	55		
BCX32 = BC637	39	BF274	24	MR475	2.46		
BC549	8	BF336	36	MR479	2.60		
BC550	7	BF337	41	OT112	1.91		
BC557	8	BF338	41	RT0121	1.91		
				R20108	1.92		

## INTEGRATED CIRCUITS

AN214Q	3.91	SN76131N	2.00	TCA940	1.95
AN240	3.84	SN76226DN	2.00	TDA440	2.20
AN318	3.98	SN76227N	1.18	TDA1002	1.95
AN262	2.45	SN76533N	1.70	TDA1003A	5.50
AN301	3.15	SN76533N	2.49	TDA1006A	2.50
AN7150	5.97	SN76544N	2.35	TDA1005	3.60
ANG340	7.85	SN76650N	1.05	TDA1010	1.54
ANG341N	5.10	SN76660N	80	TDA1035	4.70
ANG344	7.85	SN76666N	80	TDA1037	2.95
BA521	2.80	SN76530A	1.47	TDA1044	4.37
BA536	3.00	STK015	6.25	TDA1060A	4.44
CA555	46	STK032	=	TDA1052	1.56
CA556	84	STK078	13.25	TDA1083	1.68
CA741	25	STK043	11.05	TDA1170S	3.00
CA748	45	STK433	5.65	TDA1180	3.50
CA3065	1.80	STK435	9.06	TDA1190	2.91
HA1151	3.89	STK436	5.50	TDA1200	2.95
HA1342	2.49	STK437	7.85	TDA1220A	2.12
HA1306N	2.60	STK439	6.62	TDA1327	3.95
HA1366WR	2.80	STK459	8.20	TDA1327	1.70
HA1392	3.95	STK461	8.10	TDA1352B	1.60
HA11219	2.49	STK461=465	9.60	TDA1412	1.20
HA11244	1.98	STK463	14.30	TDA1415	1.40
HA4031P	3.21	SW153	2.74	TDA1470	4.67
LA4032P	2.90	TA7050P	95	TDA1770	5.60
LA4032P	2.90	TA7051P	95	TDA2002	2.80
LA4032P	2.90	TA7063P	2.20	TDA2003	1.20
LA4032P	2.90	TA7074P	1.00	TDA2004	2.52
LA4032P	2.90	TA7108P	3.43	TDA2006	1.78
LA4032P	2.90	TA7120P	2.43	TDA2150	2.00
LA4032P	2.90	TA7129AP	3.76	TDA2140	5.95
LA4032P	2.90	TA7129AP	1.93	TDA2150	2.22
LA4032P	2.90	TA7146P	4.67	TDA2020	4.66
LA4032P	2.90	TA7193P	5.67	TDA2030	2.80
LA4032P	2.90	TA7171P	1.85	TDA2522	3.40
LA4032P	2.90	TA7172P	1.85	TDA2523	2.40
LA4032P	2.90	TA7173P	1.85	TDA2524	2.25
LA4032P	2.90	TA7176P	2.50	TDA2525	4.00
LA4032P	2.90	TA7202P	4.27	TDA2530	2.70
LA4032P	2.90	TA7204P	3.77	TDA2532	2.56
LA4032P	2.90	TA7205AP	3.72	TDA2540	3.84
LA4032P	2.90	TA7208P	3.40	TDA2541	3.84
LA4032P	2.90	TA7210P	6.60	TDA2560	3.50
LA4032P	2.90	TA7222	2.42	TDA2571	2.56
LA4032P	2.90	TA7223P	3.74	TDA2576	3.75
LA4032P	2.90	TA7227P	5.98	TDA2576A	3.75
LA4032P	2.90	TA7228P	5.98	TDA2577	4.50
LA4032P	2.90	TA7310P	2.98	TDA2582	2.60
LA4032P	2.90	TA7609P	4.39	TDA2582	2.60
LA4032P	2.90	TA7611AP	2.92	TDA2591	3.25
LA4032P	2.90	TAA310	2.83	TDA2591	2.95
LA4032P	2.90	TAA320	2.00	TDA2593	2.95
LA4032P	2.90	TAA550	5.50	TDA2600	5.90
LA4032P	2.90	TAA630	3.90	TDA2610	3.20
LA4032P	2.90	TAA8400S1	1.96	TDA2611A	1.95
LA4032P	2.90	TAA861B	1.20	TDA2640	2.92
LA4032P	2.90	TBA120A	80	TDA2652	7.31
LA4032P	2.90	(A), (S), (AS), (SA)		TDA2653	5.90
LA4032P	2.90	TBA120B	1.30	TDA2680	3.40
LA4032P	2.90	TBA120SB	1.37	TDA2690	1.35
LA4032P	2.90	TBA120T	95	TDA3190	2.00
LA4032P	2.90	TBA120U	1.10	TDA3500	6.90
LA4032P	2.90	TBA395	1.20	TDA3560	6.00
LA4032P	2.90	TBA396	80	TDA3561	6.50
LA4032P	2.90	TBA440N	2.75	TDA3562	6.00
LA4032P	2.90	(TBA1441)		TDA3571	3.75
LA4032P	2.90	TBA440P	2.50	TDA3651A	4.50
LA4032P	2.90	TBA4800	1.50	TDA4420	4.22
LA4032P	2.90	TBA510	3.00	TDA4600	2.95
LA4032P	2.90	TBA520(Q)	1.68	TDA9503	2.50
LA4032P	2.90	TBA530(Q)	1.38	TEA1002	3.50
LA4032P	2.90	TBA540	1.68	TEA1009	1.37
LA4032P	2.90	TBA5600	1.59	UPC554	1.34
LA4032P	2.90	TBA570	1.79	UPC566H	2.95
LA4032P	2.90	TBA690	1.50	UPC575C2	3.40
LA4032P	2.90	TBA6418X1	3.50	UPC576H	1.90
LA4032P	2.90	TBA673	2.45	UPC587C2	1.60
LA4032P	2.90	TBA700	2.12	UPC1025H	2.95
LA4032P	2.90				

**TRADE ANNOUNCEMENT**

**FERGUSON  
3V16/3V22  
VHS VIDEOS**

**THORN  
8800/9000/9600  
COLOUR TV's**

MAINLY REMOTE CONTROL  
HAND UNITS NOW AVAILABLE

**MINIMUM PURCHASE 5 UNITS  
LOWEST PRICES IN U.K.**



**OTV TRADE DIVISION  
OTV HOUSE  
144 LEA BRIDGE ROAD  
LONDON E5 9RB**

**Telephone: Bob Munson 01-985 6111**





# MANTEL

**No 1 for Quality TVs & Videos  
100s of V.H.S. Videos in stock**

Large Quantities of Late Model Thorn TVs. All  
with first class cabinets.

**TELE-TEXT/ULTRASONIC/INFRARED/REMOTES**  
All at UNBEATABLE PRICES for QUANTITY & QUALITY

*Also Philips G11/Pye G11/Basic/Remote/TELE-TEXT*

**Some examples of QUALITY working TVs**

THORN 8800 \*\*\*\*\* £25  
THORN 8800(remote) \*\*\*\*\* £30  
THORN 9000 \*\*\*\*\* £30  
THORN 9000(remote) \*\*\*\*\* £35  
THORN 9600 \*\*\*\*\* £40  
THORN 9600(full feature remote) \*\*\* £45

THORN 9600 TELETEXT from £75  
(VARIOUS MODELS)  
THORN 9900 \*\*\*\*\* £50  
THORN 9900f/f remote \*\*\*\*\* £60  
PHILIPS G11 \*\*\*\*\* £55

*(prices quoted are based on quantity)*

**NO DEALER TOO LARGE OR SMALL. SINGLES SOLD**

**Brand New Remote Control Hand Sets Available for the  
majority of British & European TV sets.**

## **1000s of UNTESTED Colour TVs**

I.E. DECCA 30s  
GEC 2110  
GRUNDIG  
TANBERGS

G8s 520s-550s  
Thorn 3500/8000/8500  
TT  
PYE, ETC.

(Many of these untested TVs just switch on)

**ALL AT LOW LOW PRICES**

**VAN LOADS DELIVERED DIRECT FROM SOURCE  
RING FOR QUOTE**

New TV Trolley Stands **£4.95** Also Video Stands **POA**  
Colour TV panels & tubes available

*All prices subject to V.A.T.*

*CALLERS WELCOME*

Export Orders Welcome for those Countries using the P.A.L. System

**419 BARLOW MOOR ROAD,  
CHORLTON, MANCHESTER M21 2ER.**

**TEL: 061-861 8501**


**INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT**

**ALSO AVAILABLE**  
 Analogue Multimeters  
 Digital Multimeters  
 Oscilloscopes  
 Signal Generators  
 Digital Frequency Meters  
 Pattern Generators  
 CRT Tester/Rejuvenator  
 T.V. Field Strength Meter  
 Digital Capacitance Meter  
**LARGE S.A.E.**  
**FOR COMPLETE LIST.**

**LEADER LCT-910A  
 C.R.T. TESTER-REJUVENATOR**


Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.

- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors. Size: H 230mm W 330mm D 120mm.

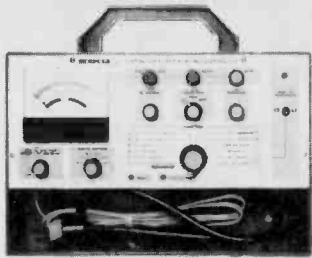

PRICE £210 + £31.50 VAT

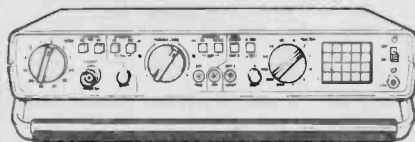**THE VERY LATEST SC110A LOW POWER,  
 FULLY PORTABLE OSCILLOSCOPE.**




The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**

- Full Sized Performance**
- \* 10 MHz bandwidth.
  - \* Full trigger facilities are provided including TV frame, or TV filtering.
  - \* Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
  - \* Size 255mm x 148mm x 50mm.
  - \* 10 mV per division sensitivity.
- PRICE £165.00 + £24.75 VAT

- Accessories:** Carry Case £5.95 + £0.89 V.A.T.  
 × 1 Probe £7.50 + £1.13 V.A.T.  
 × 10 Probe £8.50 + £1.28 V.A.T.  
 × 1/10 Switched Probe £10.50 + £1.58 V.A.T.  
 AC Adaptor £6.95 + £1.04 V.A.T.

**LEADER HIGH VOLTAGE  
 METER EHT PROBE**

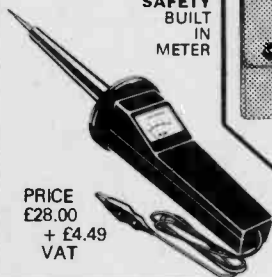Measures up to 40 K.V. D.C. with **SAFETY BUILT IN METER**





PRICE  
 £28.00  
 + £4.49  
 VAT

**\* FULLY  
 GUARANTEED**

**LOPT TESTER**

**BK's REVOLUTIONARY DYNAMIC  
 'LOPT' TESTER**  
 Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC

PRICE £25.99 + £3.VAT

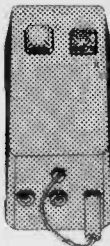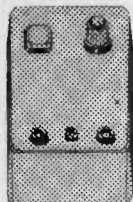


**CRT TESTER-REJUVENATOR**

**BK's C.R.T. TESTER-REJUVENATOR**  
 Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

PRICE £32.00 + £4.80VAT

**HAMEG HM 203-5 20MHz  
 DUAL TRACE OSCILLOSCOPE**

- SPECIFICATION:**
- \* BANDWIDTH DC-20MHz
  - \* SENSITIVITY CH1, CH2 2mV-50V/DIV
  - \* TIMEBASE 40ns to 0.25 CM
  - \* TRIGGER DC-40MHz Auto-Normal-TV
  - \* CALIBRATION OUTPUT
  - \* CH1 ADD AND INVERT FACILITY
  - \* ALT/CHOP SWITCH
  - \* LARGE RECTANGULAR SCREEN 8 x 10 cms.
  - \* BUILT IN SEMICONDUCTOR COMP. TESTER
  - \* SIZE 285mm x 145mm x 380mm.
  - \* SUPPLY 110-125-220-240V AC 50-60Hz

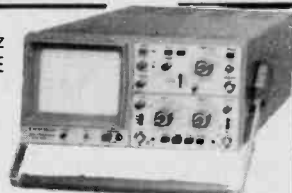

**WITH COMPONENT  
 TESTER**

PRICE  
 £270.00 + £40.50 VAT  
 Optional probes as above

**2 YEAR WARRANTY**

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.



**B. K. ELECTRONICS** Dept. 'T'

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
 ESSEX. SS2 6TR TEL: 0702-527572



**TELEPART**

**Telegen-1**

- PRICE £18.35 (Inc. VAT)  
 \* EXCEPTIONALLY LIGHT AND DURABLE  
 \* POCKET SIZE FOR OUTSIDE SERVICE  
 \* PP3 BATTERY POWER SOURCE  
 \* FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV  
 \* CROSSHATCH GRID \* DOT MATRIX  
 \* WHITE RASTER  
 \* HORIZONTALS \* VERTICLES  
 \* 3.5mm JACK SOCKET FOR OPTIONAL P.S.U.



A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

**Telegen-2**

- PRICE £34.45 (Inc. VAT)  
 \* EXCEPTIONALLY LIGHT & DURABLE  
 \* COMPACT 10 x 12 x 4.5 cms  
 \* RED RASTER \* GREEN RASTER  
 \* BLUE RASTER  
 \* COLOUR BARS  
 \* 3.5 mm JACK SOCKET FOR P.S.U.  
 \* PROVIDES UHF SIGNAL APPROX. CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

**Power Supply**

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.  
 PRICE £4.55 (Inc. VAT)

ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)  
 All goods should be delivered within 4 working days.

**32 TEMPLE STREET, WOLVERHAMPTON  
 WV2 4AN. TEL: (0902) 773122**

**D.I.Y. TV TUBE POLISHING**

with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25\* tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

**Kit Price £49 inc P&P and VAT.** Available from Luton only.  
 \*Depends on depth and area to be polished.

**AQUADAG COATING £17.25 per litre inc P&P and VAT.** Sufficient for approx 100 tubes.  
 Available from Luton only.

**TV TUBES FREE DELIVERY\***

**5% DISCOUNT ON TUBES COLLECTED FROM LUTON**  
 Quality, High Temperature Reprocessing

TUBE SIZE	DELTA i.e. A51-110X A56-120X A66-120X	DELTA SPECIALS i.e. 510GLB22 A47-342X A67-150X	IN LINE & PIL i.e. A51-161X A51-570X A56-510X A66-510X	HITACHI IN LINE i.e. 490DVB22 510VLB22 560DZB22	SONY TRINITRON
UP TO 20"	£30	£32	£40	£44	£58
UP TO 22"	£34	£36	£42	£46	£64
UP TO 26"	£36	£38	£44	£48	£70

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee.

All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. From £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 or 2 tubes £6. 3 or more tubes FREE DELIVERY\*

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

**WELL VIEW**

114-134 Midland Rd,  
 Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-1pm. Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

H. K. Television, London, E.2. Tel. 01-729 1133.

Ex rental TV supplier to the trade.

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.  
 Tel. 024 06 3609

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901

Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562

WANTED A56/A66-510X/540X Old glass for cash



# VHS VIDEOS



*Securicor Delivery £5 per unit extra*

*Franchises Available*

**£87  
WORKING**

**£74  
UNTESTED**

**£61  
NOT WORKING**

*Minimum Order 10 - Any Mix*

**10,000 TV's IN STOCK  
inc REMOTES & T/TEXT.**

## Kent Ledgerwood Wholesale Ltd.

### TRITEL TV.

**NORTH**  
1043 Leeds Road  
Thornbury  
Roundabout  
Bradford  
Tel: 0274 665670

### WESTSIDE TV.

**SOUTH**  
29/31 West Side Centre  
Luton  
Tel: 0582 24177

### TRITEL TV.

**SCOTLAND**  
Unit 4  
Peacock Cross  
Industrial Estate  
Burnbank Road  
Hamilton  
Tel: 0698 282141

### WEMBLEY TV.

**LONDON**  
Unit 4,  
Fourth Way,  
Wembley.  
(off South Way,  
Behind Wembley Stadium)  
Tel: 01 903 7587



**CHROMOVAC**

**QUALITY  
REBUILDS**

**SPECIAL  
OFFERS**  
ON  
INLINE



Get on the hot-line today!

SUPERIOR QUALITY TUBES

051

**DELTA RE-BUILDS**

**428 8777**

most types of Inline Re-builds or  
new ex-stock

★ 2 YEAR WARRANTY  
★ 4 YEAR OPTIONAL

**Delta Rebuilds**

Up to 19" .....	£28
Up to 22" .....	£30
Up to 26" .....	£34
110° up to 22" .....	£34
110° up to 26" .....	£38
Low focus .....	+£2
A47 342 New .....	£28
17FHP New .....	£30
470EHB New .....	£30
Delta only. Less 5% 5+	

**Inline Rebuilds**

Up to 22" .....	£40
Up to 26" .....	£45
A56 - 540x .....	£56
A66 - 540x .....	£58
Bonded Coil ....	+£5

ALL SIZES OF  
NEW MONO TUBES  
AT COMPETITIVE PRICES

**IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS**

Please enquire types not listed

370 HFB-A37-590.....	£45	560 DMB .....	£62
370 HUB .....	£45	AXT 56-001 .....	£62
AXT 37-001 .....	£45	660 AB .....	£65
420 CSB .....	£45	A67-701 .....	£65
420 EDB-A42-590 .....	£45	670 CZB .....	£65
420 EZB .....	£45	A66-540 .....	£65
420 ERB .....	£45	420FSB .....	£55
470 KUB .....	£50		
510 UFB/A51-590 .....	£55		
510 VSB .....	£60		
AXT 51-001 .....	£60		
560 DYB-560 DTB .....	£62		
560 EGB .....	£62		
560 CGB .....	£62		

CARRIAGE  
£5 Singles. 2-3 £10. 4 £12  
10 £15. 10+ Carriage paid  
EXCLUSIVE OF VAT  
TERMS  
Cash with order

QUANTITY  
DISCOUNT  
AVAILABLE  
Ask for details

★ OUR TECHNICAL DEPT. WILL ADVISE YOU ON  
PROBLEMS. YOU MAY ENCOUNTER ON FITTING  
INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order.  
Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

**CHROMOVAC**

CHROMAVAC LTD. UNIT 7, BEAR BRAND COMPLEX,  
ALLERTON ROAD, WOOLTON, LIVERPOOL 25

Ask for Mr Butterworth or Betty Ford ON: 051-428 8777

**VALVES**

High Quality  
Best Prices  
Large Stocks  
Rapid Delivery

**Edicron**

Serving industry for over 25 years

Tel: (1)961 2020 Tlx: 265531

1-7 Wesley Avenue, London NW10 7BZ.

Cable: Edicron London NW10

**PHILEX  
REPLACEMENT  
INFRA RED REMOTE CONTROLS**



**DISTRIBUTORS**


CGS (MASTERCARE) LTD - High Wycombe  
CPC LTD - Preston  
COOPERS - Dublin  
COMPONENT BUREAU - Cambridge  
CHARLES HYDE & SON LTD - York  
DOUBLE 'D' DISTRIBUTORS - Poole  
HRS ELECTRICAL CO LTD - Birmingham  
KILROY BROS - Dublin  
MONOLITH ELECTRICAL CO LTD - Somerset

**NORTHERN IRELAND ELECTRONICS**

Belfast  
PV TUBES - Accrington  
NORMAN ROSE - London  
PACT - Peterborough  
RADIO SUPPLIES - Hartlepool  
SEME - Milton Mowbray  
TAIT COMPONENTS - Glasgow  
WILLOWVALE ELECTRICAL LTD - Reading  
WIZARD - Manchester  
McLELLAND - Leeds

**PHILEX**

01-631 0985

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US			<b>G.G.L. COMPONENTS</b> 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY PHONE (0228) 20358/39693			BUY WITH 			E.H.T. TRAYS		
<b>INTEGRATED CIRCUITS</b>			<b>TRANSISTORS</b>			<b>THORN SPARES AVAILABLE</b>			<b>DIODES</b>		
TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
AN214.....	1.95	BC107.....	14	BD235.....	32	BU508A.....	1.95	DECCA 80.....	7.20	BY127.....	10
AN301.....	3.45	BC108.....	14	BD236.....	43	BU526.....	2.00	DECCA 100.....	7.35	BY133.....	15
AN303.....	3.45	BC109.....	14	BD237.....	40	BU826A.....	3.20	ITT CVC 20/30.....	6.85	BY179.....	65
AN305.....	3.50	BC141.....	26	BD410.....	50	R2010B.....	1.45	ITT CVC 25/30/32.....	8.00	BY227M.....	23
AN7110.....	1.93	BC142.....	23	BD434.....	50	R2540.....	2.35	ITT CVC 45.....	8.45	BY239/600.....	87
AN7114E.....	2.33	BC143.....	25	BD437.....	70	TIP31C.....	46	PHILIPS G8.....	8.75	BY258/400.....	24
AN7115.....	2.37	BC144.....	25	BD438.....	78	TIP33.....	80	PHILIPS G11.....	13.50	BYX55/600.....	25
AN7116.....	2.35	BC147.....	09	BD439.....	70	TIP34.....	95	PHILIPS KT3.....	9.95	BYX10.....	20
AN7145.....	3.25	BC148.....	09	BF194.....	1.05	TIP41C.....	48	PHILIPS KT3.....	9.95	BYX55/600.....	25
BA312.....	1.25	BC157.....	10	BF195.....	13	TIP42C.....	48	PHILIPS KT3.....	9.95	BYX17/600.....	26
BA511A.....	1.95	BC158.....	10	BF196.....	11	TIP47.....	75	PHILIPS KT3.....	9.95	BYX55/600.....	25
BA521.....	1.85	BC159.....	11	BF197.....	11	TIP295.....	70	PHILIPS KT3.....	9.95	BYX17/600.....	26
BA532.....	1.95	BC182L.....	11	BF211.....	11	TIP305.....	50	PHILIPS KT3.....	9.95	BYX55/600.....	25
BA536.....	2.55	BC183L.....	11	BF256LC.....	25	TIP305.....	50	PHILIPS KT3.....	9.95	BYX17/600.....	26
HA1166.....	2.65	BC184L.....	11	BF258.....	25	2N3055.....	3.45	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1322.....	2.10	BC212.....	10	BF259.....	26	2N3773.....	3.45	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1338.....	2.78	BC213.....	10	BF337.....	28	15/80H.....	2.25	PHILIPS KT3.....	9.95	BYX17/600.....	26
HA1339.....	2.40	BC237.....	11	BF338.....	28	15/85R.....	2.25	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1342A.....	2.20	BC327.....	11	BF458.....	30	2SA 771.....	2.95	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1366 W/WR.....	1.95	BC328.....	12	BF459.....	36	2SA 835.....	1.55	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1370.....	2.75	BC337.....	11	BF757.....	75	2SB 618.....	2.45	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1374.....	2.45	BC338.....	10	BF757.....	75	2SB 867A.....	3.25	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1377.....	3.80	BC547.....	10	BF800.....	1.10	2SC 1034.....	4.65	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1388.....	4.20	BC548.....	10	BR100.....	18	2SC 1061.....	1.15	PHILIPS KT3.....	9.95	BYX55/600.....	25
HA1397.....	3.90	BC557.....	10	BR101.....	32	2SC 1114.....	4.75	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA1201.....	1.75	BC558.....	10	BR103.....	55	2SC 1124.....	97	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA1230.....	2.30	BD124M.....	1.05	BR303.....	2.95	2SC 1316.....	3.20	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA1365.....	2.45	BD131.....	33	BT106.....	1.15	2SC 1413A.....	3.95	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA3350.....	1.65	BD132.....	33	BT116.....	1.30	2SC 1739.....	2.45	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4031.....	2.45	BD201.....	80	BT151.....	1.30	2SC 1942.....	2.95	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4032.....	2.30	BD202.....	70	800R.....	1.10	2SC 1962.....	1.65	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4101.....	1.50	BD203.....	70	BU126.....	1.78	2SC 1969.....	1.95	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4102.....	1.95	BD204.....	83	BU205.....	1.42	2SC 2078.....	1.55	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4400.....	2.50	BD222.....	50	BU208A.....	1.45	2SC 2335 (Kit).....	7.55	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4430.....	2.45	BD225.....	55	BU208B.....	1.85	2SC 2369.....	3.25	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4440.....	3.55	BD232.....	50	BU326A.....	1.48	2SC 257.....	2.45	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA4460.....	2.95	BD233.....	37	BU407.....	1.12	2SD 588A.....	1.97	PHILIPS KT3.....	9.95	BYX55/600.....	25
LA461.....	2.95	BD234.....	40	BU407D.....	1.45	2SD 725.....	7.95	PHILIPS KT3.....	9.95	BYX55/600.....	25
MB3712.....	2.30	BU500.....	1.80	BU500.....	1.80	2SD 870.....	5.95	PHILIPS KT3.....	9.95	BYX55/600.....	25
MB3713.....	2.25							PHILIPS KT3.....	9.95	BYX55/600.....	25
ML231B.....	2.35							PHILIPS KT3.....	9.95	BYX55/600.....	25
ML232B.....	2.55							PHILIPS KT3.....	9.95	BYX55/600.....	25
ML237B.....	2.50							PHILIPS KT3.....	9.95	BYX55/600.....	25
ML238B.....	4.22							PHILIPS KT3.....	9.95	BYX55/600.....	25
SA1124.....	3.45							PHILIPS KT3.....	9.95	BYX55/600.....	25
SA1125.....	4.70							PHILIPS KT3.....	9.95	BYX55/600.....	25
SA11250.....	3.85							PHILIPS KT3.....	9.95	BYX55/600.....	25
SA11251.....	4.95							PHILIPS KT3.....	9.95	BYX55/600.....	25
SA11252.....	4.95							PHILIPS KT3.....	9.95	BYX55/600.....	25
SA11253.....	5.10							PHILIPS KT3.....	9.95	BYX55/600.....	25
SA11254.....	5.70							PHILIPS KT3.....	9.95	BYX55/600.....	25
SAF1032P.....	3.25							PHILIPS KT3.....	9.95	BYX55/600.....	25

SONY SPARES		CASS MOTORS		SUNDRIES	
C5/C7 Rewind Kit.....	4.65	6V C/W.....	5.00	G8 TRANSDUCTOR.....	2.25
C5/C7 Belt Kit.....	3.50	9V C/W.....	5.00	G8 ON/OFF SW.....	1.40
C6 Rewind Kit.....	4.35	12V C/W.....	5.00	G11 E/W Coil.....	1.65
C7 Pinch Roller.....	4.85	13.2V C/W.....	4.95	G11 Lin Coil.....	1.80
SG 613/6533.....	8.95			G11 Bridge Coil.....	1.35
CX 143A.....	6.55			G11 EHT Lead.....	2.25
				PHY IF Gain MOO.....	7.85
				ITT On/Off SW.....	1.10
				THORN On/Off SW.....	1.00
				CUT OUT 2A.....	1.95
				THORN 9000.....	8.70
				SKESF3/10.....	8.00
				W005.....	55
				1N4001-7.....	17
				1N5401-8.....	06

TV ELECTROLYTICS	PUSH BUTTONS/NEW TUNERS
DECCA 30(400/400)350V.....	DECCA/ITT 6 way.....
DECCA 80-80(100/400)350V.....	PHILIPS G8 S/L.....
(800)250V.....	PHILIPS G8 S/O.....
PHILIPS G8(600)300V.....	PYE-G11 P/B.....
PHILIPS G9(2200)63V.....	HITACHI 4 way.....
PHILIPS G11(470)250V.....	ITT CVC5 7 Button.....
RBM A823(2500/2500)30V.....	ITT CVC8/9.....
RBM T20A(220)400V.....	1043/05.....
THORN 1690/1(4700)25V.....	U321.....
THORN 3500(1000)70V.....	U322.....
THORN 9000(400)400V.....	

Available also a range of 2SA/B/C/D Transistors. Phone or write for lists.

**ORDERING**  
Please Add 50p For P/P U.K.  
Add 15% VAT To This Total.  
Export Orders — Cost.  
DELIVERY BY RETURN ON ALL STOCK ITEMS.

# SPECIAL OFFER - SUMMER SALE

**MINIMUM LOTS OF 20**

DECCA 20" VARICAP	£10
DECCA 22" MECHANICAL	£8
DECCA 22" VARICAP	£10
DORIC 20" & 22"	£10 each
SALORA 22" HYBRID	£4.50
SALORA 26" TOUCH TUNE	£10
BUSH A823 20" & 22"	£5 each
GEC 2110 22" & 26"	£12 each

TOUCH TUNE VCRs and other CTVs also available.  
All Plus VAT  
Please allow 14 days for delivery

## SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,  
Brent Park Industrial Estate,  
Southall, Middlesex UB2 5LL  
Tel: 01-574 4631

## FREE CAREER BOOKLET

**Train for success, for a better job, better pay!**

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.  
Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!  
Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.  
Send for your FREE CAREER BOOKLET today — at no cost or obligation at all.


GCE		Choose from over 40 'O' and 'A' level subjects.	
COMPUTER PROGRAMMING	<input type="checkbox"/>	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	<input type="checkbox"/>	INTERIOR DESIGN	<input type="checkbox"/>
POLICE ENTRANCE	<input type="checkbox"/>	HOTEL MANAGEMENT	<input type="checkbox"/>
ELECTRONICS	<input type="checkbox"/>	COMMERCIAL ART	<input type="checkbox"/>

Please send FREE DETAILS for the courses ticked above.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
P. Code \_\_\_\_\_

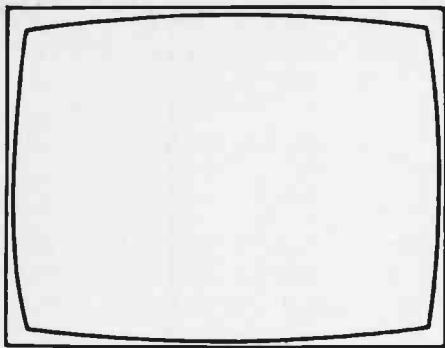**ICS** Dept. EGSA5, 312/314 High St., Sutton, Surrey SM1 1PR. Tel: 01-643 9568/9 or 041-221 2926 (all hours).





# TELEVISION

## Long-term Strategies

It is quite common to hear criticism of city institutions and large firms for failing to take a long-term view of investment. The argument is that when a quick return on investment is the prime aim long-term industrial development will suffer and we shall all end up the poorer. Investment is seen as a good thing that should be encouraged, undertaken with long-term developments in mind and maintained despite market hiccups. Well yes, but one must also acknowledge that long-term investment and research are very difficult things to control and that they require the discipline of constant economic monitoring. Some research programmes can and have in the past got out of control, developing a momentum of their own that has eventually led to the creation of a white elephant – aptly described recently by Karl-Erik Sahlberg (see below) as “a magnificent product that is hopeless to market”.

In practice terms like investment and research cover a vast number of very different things. The development of a new aeroplane engine or main-frame computer requires long-term commitment indeed. But few firms are engaged in activities of this sort. At the other end of the scale the practical development of a simple idea can produce a very quick return. Such investment is often into ways of making things rather than in scientific research.

Our own industry highlights the divers results of research and investment. Perhaps the most profound discovery was of the bipolar transistor effect. The extraordinary thing is that it was discovered by accident, which seems to suggest that commitment to long-term research is a wise course on the ground that something is bound to turn up eventually! Well maybe, but spotting a significant discovery and exploiting its potential is the vital thing.

The world of TV displays a more purposeful approach to what research and development can achieve. The famed development of a complete TV system by EMI-Marconi in the early thirties occurred within a very brief span of time. When one looks at the history of the period however one sees that many people worldwide were working along similar lines. The c.r.t. had been in existence in primitive form since the end of the nineteenth century, which also saw the discovery of photosensitive materials. Someone was bound to come up with a working photosensitive electron tube before long. The problem at that time was not so much any lack of ideas so much as sheer shortage of money in a period of acute economic depression. Basic TV, and radar for that matter, are two results of effective research that developed from an idea to its practical realisation very quickly. More recently the development by the Japanese of domestic VCR systems is another example of applied research producing quick results. It can be done: the problem is in getting it done.

The British Association's annual meeting, held recently, had as its main theme putting science to work. Many speakers were concerned with the relationship between commercial firms and the research activities of the educational institutions. GEC's chief scientist Dr Cyril Hilsom stressed the importance of market research in innovation, something at which our Japanese competitors have always been particularly good. One of the factors that has underpinned electronic development has been research into materials. The development of the VCR depended on suitable tape becoming available, and solving that problem took a great deal longer than devising the mechanics and circuit techniques. The problem with early camera tubes was the lack of a suitable target material. Materials technology has of course been vital to semiconductor development, also to such things as producing mechanical parts with the best characteristics. But few firms carry out much research on materials. This area tends to be the preserve of academic research.

Much was made at the BA meeting of problems in this area, of the need to link universities and industries in common innovative objectives (Cyril Hilsom again) and of the need for research to be interdisciplinary (Professor Gareth Roberts, chief scientist of Thorn EMI). These are old problems that still seem to block innovative progress. Gareth Roberts commented on the need to restructure science research funding and on authorities being “too compartmentalised and wedded to a peer review system that's inherently weak at exploiting the interfaces between sciences”. The BA's president, Professor Sir Hans Kornberg, spoke of the need for scientists in industry to become involved with research in universities at an early stage and to blur the distinction between “basic” and “strategic” research.

The problem of getting things right, i.e. of short-, medium- and long-term strategies, in research and innovation, lies not only in the provision of funds therefore, i.e. the traditional criticism made of the city. There's the problem of whether industry can make the best use of academic research and how the latter should respond to industry's needs; also the problems of the best use of available funds and how to monitor progress. It's interesting that in a recent interview with the *Financial Times* Karl-Erik Sahlberg, managing director of the Swedish firm Perstorp, reported that his firm had closed down its central research and development unit in 1971, each separate business area instead being responsible for its own R and D work and for keeping its researchers close to its marketing staff.

There's little doubt that the control of research and innovation is a difficult and demanding business. One thing that's certain is that simply pouring more money in, as is so often advocated, is no solution at all. The vital element (Karl-Erik Sahlberg again) is “to find the right people to manage innovation projects”. Also, one might add, to keep long-term strategies under continuous review and retain maximum flexibility so that opportunities can be seized as they arise.

## EDITOR

John A. Reddihough

## ADVERTISEMENT MANAGER

Roy Smith  
01-261 6671

## CLASSIFIED ADVERTISEMENTS

Pat Bunce  
01-261 5942

Please note that the telephone numbers above are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 665.

## COVER PHOTO

Four generations of field output device are shown in our cover photograph this month. Taking us way back is a Cossor 61BT output tetrode with international octal base. Still with us is the PCL805 field timebase triode-pentode. A pair of BD124s, on the heatsink used in the Pye 697 chassis, represents early transistor practice. In the forefront an SGS TDA1670 provides almost a complete field timebase in i.c. form.

## HELP!

Can anyone assist with a source of spares/service information on another obscure make of colour portable – Contec? We've received several requests for this information.

## CORRECTION

The international video camera market survey published by Euromonitor, mentioned in Teletopics last month, costs £250 not £25.

# Quick Checks: Rank A823 and Pye 725 Chassis

S. Simon

We have received comments recently to the effect that we ought to mention more of the older models. After all they're the ones that are more likely to require attention, and the right approach is required to save time and patience. One chassis mentioned is the still popular Bush A823 series (Model CTV1122 etc.), so we'll kick off with this.

## RANK A823 SERIES

### No Sound or Raster

In the event of no sound or raster one should first appreciate that whilst a conventional thyristor regulated power supply circuit is used to provide the h.t. line most sections of the receiver, including the line driver stage, are operated from l.t. lines derived from the mains transformer at the bottom left-hand side. Hence lack of sound and a picture could well be the result of l.t. supply failure. As a first step, a glance at the rear of the tube will show whether the transformer is being supplied. If the tube's heaters are out, make your first voltage check at the h.t. fuse at the top of the panel (630mA, anti-surge). If 200V is recorded here, you know that the mains supply is intact, including the 3.15A anti-surge (5A on early models) mains fuse at the bottom of the panel. Thus if the tube's heaters are out but h.t. is present either the mains transformer isn't being fed or (very rarely) it's defective. In this event look for a floating line fuse in the feed to the transformer. Most versions don't have this extra fuse but if the tube's heaters are out the chances are that the set does have it. It has a low-current rating – 315mA maximum.

If the tube's heaters are glowing the transformer is functioning and the chances are that the 2A l.t. fuse (anti-surge again) midway on the rear edge of the power board has failed. If this is so, don't replace the fuse until the circuit has been checked for shorts. The usual failure is a faulty bridge rectifier which may consist of a single unit or four separate diodes. In the latter case you may well find that two are short-circuit – BY126 diodes can be fitted. If you find a short-circuit single unit a BY225 can be used as the replacement. There can be many other causes of l.t. fuse failure of course, but the usual one is a shorted bridge.

### Sound but no Raster

With the sound present but no raster symptom you know immediately that the transformer is functioning and therefore (you hope) the tube's heaters are glowing. So the fault is probably in the h.t. supply, and this is where most confusion seems to arise. Check for 200V at the top fuse. If there is h.t. at one end only it will be necessary to check for shorts. Before diving into the line output stage – disconnecting the tripler etc. – check under the centre section where you will find that a 47k $\Omega$  resistor is wired across the tags of both electrolytics. These resistors are included to render the circuit stable and safe in the event of an open-circuit. They deteriorate with age and heat

however and often decrease in value, getting lower until the rush of current completes their demise and blows the h.t. fuse. Check these points. Incidentally, the connections to the tripler are plugs so disconnection is simple indeed – just pull out the rear end plug to leave the line output transformer unloaded. But we digress: back to the power supply.

If the fuse is intact but there's no h.t. present, check that a.c. is reaching the anode of the thyristor (body of the BT106). If 240V a.c. is present here, switch off and check the continuity of the wirewound resistors under the centre section in front of the electrolytics. The left side one (h.t. smoothing) is suspect and should read 68 $\Omega$ . If this is open-circuit the thyristor will not be triggered and no h.t. will be produced. A replacement resistor must be rated at 20W or more and the contacts must be mechanically sound – a dab with the soldering iron will not do as considerable heat is dissipated.

If there's no a.c. on the body of the thyristor it's highly likely that the VA1104 thermistor, a disc type on the lower part of the panel next to the degaussing thermistor, has deteriorated – perhaps to the point where the disc has parted company with the contact wires and has dropped out. It's common practice in some quarters merely to twist the wires together, thus leaving out the surge limiter. This is not the correct action: a new thermistor should be fitted to preserve the life of other components. If the thermistor is intact, or replacement still leaves the thyristor without a.c., check the continuity of the tracks to and from the thermistor – they could have burnt away, though this should have been seen when the thermistor was replaced.

What if the h.t. supply is in order and there's sound but no raster? Remember what we said about the l.t. supplies. Check the condition of 8R2 at the upper left of the power panel. This 6.8 $\Omega$  wirewound resistor supplies the line oscillator and driver stages. If it's cold it could be open-circuit and replacing it could restore normal results. If the new resistor runs hot or the original one is found to be running hot suspect the BD131 line driver transistor – on the right side of the timebase board, bottom right. Fit a new one with heatsink washers or a frame to dissipate the heat if a heatsink isn't fitted.

If the line drive is in order, remove the line output stage cover and hold a neon near the transformer. If it lights up, the line output stage is probably in order and the tube base voltages should be checked (if this has not already been done). The first anode voltages on the tube base give a good indication as to whether or not the line output stage is working.

If the neon doesn't light up, first try disconnecting the tripler to see what effect this has. If it makes no difference, check the h.t. voltage on the body of the line output transistors. If h.t. is present on one only, switch off and prepare to remove the timebase panel to gain access to the reverse side of the output transistors (remove small panel). There should be a very low resistance reading between the base and emitter of each transistor due to the presence of the secondary windings on the driver transformer and two low-value resistors. A reading of just below 10 $\Omega$  suggests that the associated 2.2 $\Omega$  series resistor



is open-circuit – remove and check it.

If you suspect that the set has been tampered with, check the setting of the overvoltage preset on the timebase panel – 5RV1 in the A823 chassis, 5RV5 in the A823A chassis. If in doubt, set this midway.

Rapid fluctuation of the picture size is often due to a faulty item on the power supply panel. The BT106 thyristor is the usual culprit, though the BR100 trigger diac can also be responsible. It cannot be measured: if a replacement is not to hand, removing it and reversing its connections could solve the problem, i.e. try turning it round.

There are many other common faults we could discuss, but the aim here is to outline quick steps to take to deal with basic fault conditions.

## No Colour

We will however discuss one other common problem since the following points could save much time and worry. In the event of no colour the tendency is to rush to the decoder panel and accuse the SL917 i.c. (on later panels – earlier ones used discrete circuitry in this area, i.e. just one i.c. instead of two) of causing the trouble. The correct procedure is first to check on the upper left side of the i.f. panel, where the chroma amplifier resides. On the later models there's a small preset control adjacent to the amplifier's screening can. This is often the cause of the trouble – it may need only a clean and adjustment. If the preset is not at fault, remove the screening can and check the three transistors (two BC148s and one BC158) in the usual way. The small round types are more suspect than rectangular ones. If all is well here move over to the decoder panel and check the SL917's voltage supply which comes from the BC148 emitter-follower 3VT2. Check this transistor if necessary. If the voltages are present the SL917 may be suspect, but check the other transistors on the panel first as one or two of these can give trouble and the SL917 is an expensive item compared to say a BC148. Note that in the earlier A823 chassis, which does not have the preset next to the chroma amplifier can, the transistors within the can are two BC148s and a BF197 (no pnp transistor).

## PYE 725 CHASSIS

This chassis is used in the Pye Models CT222, CT223 etc. We mentioned it briefly in the first article in this series (July) but only to illustrate a point or two. It's worth making some general points.

## Power Supply Faults

Most problems centre around the power supply board on the lower right side. To obtain access, remove the top strap (if still fitted), raise the bottom latch and slide out the vertical panel containing the field output (upper) and power supply (lower) boards. When the panel has been withdrawn a certain way it can be rotated to provide access to both sides. This enables the 3.15A mains fuse F913 to be replaced if necessary, also possibly the mains filter capacitor C915 which often goes short-circuit, leaving the fuse with a distressed appearance (if the glass is left intact that is). Replace the fuse with the normal 3.15A anti-surge type and the capacitor with an 0.22 $\mu$ F type rated at 1kV or 300V a.c.

If there's no sign of life but the mains supply is clearly

in order check that a.c. is present at the anode of the mains rectifier thyristor. The input choke L909 often works itself loose on the print, as do the main electrolytics – a check on these points will often pay dividends.

If the a.c. is reaching the thyristor but this is not being fired check the condition of the two 82k $\Omega$  charging resistors R898/899. These tend to deteriorate and go open-circuit. If these are in order, switch off and check the conditions of the centre section dropper elements – the 3.3 $\Omega$  section R978 often goes open-circuit to produce the dead set symptom and your search will often end here.

If the droppers are intact go back to the power supply and carry out a general check on the transistors, resistors, zener diodes etc. The preset controls should also be checked to ensure that they are intact and don't have a dud spot where the wiper contacts the track.

You will often find that the h.t. supply is all right but the h.t. fuse F971, on the centre section, is open-circuit. Remember what we said before, because this can be difficult. Check the 0.1 $\mu$ F, 1.25kV capacitor C563, which lives under the top of the line output section, first. This may save a lot of heartache and unnecessary replacement of the tripler etc. On the other hand it may already have ruined the tripler, the transformer and the BU208.

## Thick Film Unit

The other weak spot in this chassis is at the top of the left side signals panel. The thick film unit resides here – it's an angled metal structure which contains the load resistors for the RGB output stages and the feedback resistors. If there's no voltage here check R476 (47 $\Omega$ ) to the left of the unit. This is the h.t. feed resistor and may be found open-circuit. Normally h.t. will be found at the body of the unit. If the voltages at the collectors of the three BF336 transistors are not roughly equal, first check the TBA530Q i.c.'s 39k $\Omega$  output load resistors R474/R458/R442. If these are in order, remove and check the thick film unit. The act of removing it may complete its demise, leaving no choice other than replacement.

## Grainy Picture

We should also mention the other trouble spot in these sets – the i.f. gain and filter unit. This is the screened unit at right angles to the tuner on the lower part of the left side. The faults that occur tend to throw suspicion on the tuner, producing as they do the grainy, weak reception typical of a faulty tuner. It's a fairly easy matter to unsolder the pins and remove the unit. This done, concentrate on the input end. Carefully resolder the coil ends and remake all the soldered joints, carefully lifting the small capacitors to ensure that the solder is in contact with the leads. The unit can then be refitted with a good chance that all will be well and that the trouble will not recur. On the rare occasions when this does not produce the desired result the tuner may after all be at fault – or a second attack on the gain/filter unit may be required.

## The Moral

These various points show that each type of TV chassis calls for a different approach even though the symptoms or the reported faults may appear to be the same. Next month we'll outline the approach required to deal with some of the hybrid CTV chassis, many of which are still in constant use and seem to confuse younger engineers.

# Test Report: MiniScope Soldering Iron

Eugene Trundle

Up to now I've known only two basic types of electric soldering iron for radio/TV work: the gun type, in which the bit is part of a loop incorporating the secondary winding of a mains transformer; and the conventional type, which contains a resistive heating element to raise the temperature of the bit. In the latter type, the bit acts as a heat reservoir, interfacing the varying load presented by the soldering job (in terms of duty cycle and thermal suck-out) and the steady heat output from the element, which is typically rated at about 25W.


Unless the iron is thermostatically or thermomagnetically controlled, the bit temperature depends very much on circumstances – it stabilises when the heat gained from the element equals the heat lost by radiation and convection from the bit. This is fine for light work, but there can be a tendency to run out of steam as it were during prolonged operation on heat-hungry components such as screening cans.

As a result it's been necessary to have available two or more soldering irons to cater for the variety of work we encounter – typically a small-bit, 15-25W type for PCB and light applications and a 60W gun for use where heatsinks, screening cans and the old-fashioned metal chassis have to be tackled. A thermostatically-controlled iron has a wider range of applications; but again a single type is unlikely to cover all requirements.
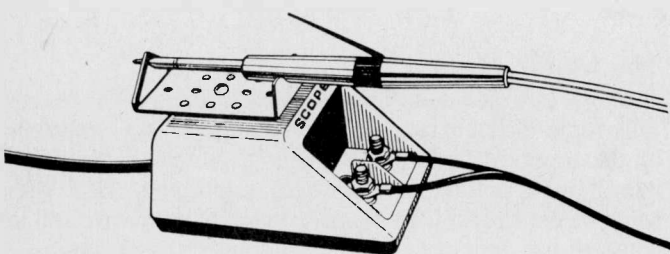
## Enter the MiniScope

The Australian manufactured Scope iron uses a principle of operation that's totally different from those described above. Instead of storing heat in the bit, this design develops heat energy within a very small bit assembly that's intended purely as a heat conductor. It works as follows. A voltage of around 4V, a.c. or d.c., is applied between the body of the iron (including the copper bit) and an insulated central stem which moves axially along the centre of the barrel. The stem is spring-loaded and has a small plug of carbon at its front end. When the operating lever is depressed this plug is pushed into contact with the rear face of the carbon bit. The contact resistance depends on the physical pressure: the current flow can reach 20A, giving a capability of around 70-80W.

As can be imagined, having a dissipation of this order in a bit with a volume roughly equivalent to a matchstick can be dramatic. If the operating lever is held down without any thermal load for the bit you'll have a red hot bit in eight seconds! In practice the effective dissipation is regulated by "dabbing" the control lever. An equivalent power from 10W upwards can thus be achieved.



The iron is supplied with about a one and a half metre length of heavy-duty twin cable with eye terminations. These bolt to the terminals of the mains power supply unit, which consists of a transformer housed in a smart orange case with a metal holder for the iron on top. The transformer provides a "floating" supply of 3.3V r.m.s., 30A intermittent rating.

## On the Bench

I used the MiniScope iron exclusively for all TV, video etc. bench work for some weeks. It took three-four seconds to reach the operating temperature, and I was amazed at its thermal capacity – I could use it to solder a large bracket to the body of an ELC1043 tuner and to deal with very heavy copper heatsinks such as those used on sound and field output chips etc. I've no doubt that it would be well able to tackle tinplate, brass and copper assembly work at up to reasonable sizes – s.h.f. plumbers take note!

At the other end of the scale, the tiny pointed bit was equally capable of dealing with i.c. leadouts on PCB assemblies, though it's necessary to maintain a suitable temperature by dabbing the operating lever – I found that with the iron too hot the print tends to lift from the PCB surface rather than component damage occurring.

At one point the gorgeous lady presenter of a children's programme on a soak-testing TV set (Louise H.T. for those who know her) attracted my attention and I went into a daydream with the lever pressed down. This resulted in virtual collapse of the bit. Apart from this episode I got on well with the iron, and it with me . . .

It was difficult in the time I had during the trial to gauge the life of the bit and the carbon-block element. There's no doubt that the latter will need replacement more often than the element in a conventional iron. At 75p plus VAT each however bit and element expenses won't break the bank.

## Conclusion

The iron is very versatile and easy to use once the "switch-mode" technique of temperature control has been mastered. I was impressed by the range of jobs it can tackle – a unique feature in my experience. Some colleagues expressed concern at the exposure of the output terminals at the front of the mains unit, not from the point of view of shock hazard but because of the danger of a conductive object accidentally short-circuiting them. I found that the moulded side and centre shields provided adequate protection against this possibility, but perhaps a cover flap would have been a good idea: it's not too difficult to devise a suitable shroud if required.

The price of £21 for the iron and £16.15 for the power supply gives a total of £37.15 plus VAT. Certainly the ensemble would be worth this to most potential users, but I wouldn't be happy about any higher price!

The MiniScope is available from SEME Ltd., Units 2E and 2F, Saxby Road Industrial Estate, Melton Mowbray, Leics LE13 1BS (0664 65392).

# POST A PART ELECTRONICS

6 CHAPMAN COURT, CHARFLEETS ROAD,  
CANVEY ISLAND, ESSEX SS8 0PQ.

Telephone 0268 690868  
Telex 99305



TRADE COUNTER OPEN

ORDERS DESPATCHED SAME DAY  
ADD 75p P&P, THEN 15% VAT.  
ADD POSTAGE FOR OVERSEAS ORDERS.  
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thom 10Q 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70Ω	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 725 Complete Tube Base Panel	1.25
TX9 Complete Tube Base Panel	2.75
TX10 Complete Tube Base Panel	3.75
TX90 Complete Tube Base Panel	4.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	45p
Tube Base Socket Thom 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt Anode Cap	90p
Sanyo Anode Cap Assy + Lead. 12TCD-CT-1G	47p
Degause VDR E29D/HP230 3000/8000	25p
Degause Thermister C8 ROH (TX90)	1.80
Control Knob Thom TX90	4 for 2.00
On/Off Knob Thom TX90	65p
Push Button Assy Thom TX90	9.80
EHT Neck Correction Assy. 20AX AT1081	5.00
EHT Cable	Metre 25p
BF259 with Heatsink	14p
TIP110 with Heatsink	40p
L129/130/131 Coil	10p
6MHz Ceramic Filter	25p
01700 (Philips) Chroma Overlay Line	1.00
0150 Chroma Delay Line	1.00
T906A Lum Delay Line	1.00
8K5/9K Lum Delay Line	1.00
Plastic Cover for 3K5 SP8385	5p
TX9 Gain Control 100R	15p
TX9 Back Control 100R	15p
Thom 2000 Focus Pot	3.75
Thom 9000 Focus Pot	3.00
Thom 9600 Focus Pot	2.00
Thom 8K5 Focus Pot	2.40
Thom 4000 Focus Pot	2.75
Thom TX10 Focus Pot (New Type)	9.00

### SERVICE AIDS

Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 2.25
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Amberlens Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

### THICK FILM RESISTOR UNITS

3500 Thom (5 Pin Connection) video	1.70
4000 Thom (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

### FUSES

20mm		1 1/4"	
50MA	10 for 70p	250MA	10 for 65p
250MA	10 for 50p	750MA	10 for 65p
315MA	10 for 50p	7A	10 for 50p
500MA	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thom Mains TX 3000/3500	7.50
Thom Mains TX 8000/8500	10.00
Thom Mains TX 9000 (T701)	10.00
Thom Mains TX 9600 (T512)	10.00
Thom S.O.P.T 8000/8500	3.50
Thom Scan TX 3000/3500	6.00
Thom EHT TX 3000/3500	6.00
Thom LOPT 9000	10.00
Thom LOPT 9600	12.00
Thom LOPT 1590/91	7.25
Thom LOPT 1690/91	7.25
Thom LOPT 8000	9.80
Thom LOPT 8500	9.80
Thom LOPT TX9	9.85
Thom LOPT TX10	19.00
Thom LOPT TX90	13.75
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT 69	8.80
Philips LOPT 811	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.80
Sanyo LOPT (CW21) 4-2751-44700	5.00
ITT LOPT CVC5-9	9.60
ITT LOPT CVC30	8.75
ITT LOPT CVC45	9.75
Baird 8750	10.25
Baird 8752	10.25
Thom Line Drive TX TX9 (T2)	1.85
Thom Line Drive TX 8K etc (T402)	1.85
Thom Line Drive TX 9K (T705)	2.00
Thom Switch Mode TX 9K6 (T511)	3.75
Thom Input Choke TX9 (L64)	4.00
Thom Choke TX90 (L120)	2.95

300 Mixed Resistors	1.50	10 Spark Gaps	1.00
300 Mixed Capacitors	1.50	10-16 pin Quil IC Socket	90p
150 Mixed Electrolytics	2.00	20 Assorted TV Knobs	1.00
100 W/W Resistors	1.00	10-16 pin Quil to Dil IC Socket	90p
20 Mixed Conv Pots	1.00	100 Mixed Diodes	1.00
40 Mixed Pots	1.50	50 Mixed Mica Washers	65p
20 Mixed Sliders	1.00	300 Mixed Resistors & Capacitors	1.50
40 Mixed Presets	60p	10-16 pin Dil to Dil IC Socket	1.00
20 Mixed VDR & Thermistors	1.00	50 Electrolytics & 50 Capacitors	1.00
100 Mixed Ceramic Discs	1.00	50 Mixed Poly Capacitors	1.00
20 Mixed Valve Bases	1.00	20 Mixed Valve Bases	1.00

AC128	39 BC174B	23 BCX33	22 BF154	25 BFR62	31 NKT276	20
AC131	40 BC177	24 BCX34	22 BF167	24 BFR62	28 NKT453	1.65
AC138	40 BC182LB	12 BD115	11 BF179	29 BFR81	29 OT112	1.92
AC141K	39 BC183L	12 BD131	30 BF181	32 BFR90	25 OT121	2.08
AC142K	38 BC184L	13 BD132	46 BF184	30 BFT42	30 R2008B	1.40
AC153	39 BC187	24 BD133	59 BF185	30 BFT43	30 R2010B	1.10
AC176	33 BC204	15 BD139	36 BF194	16 BFX38	40 R2030	7.00
AC176K/	BC208	9 BD140	38 BF195	16 BFY50	30 R2265	1.30
AC128K	93 BC212L	9 BD144	1.70 BF196	16 BFY51	34 R2305	80
AC168	38 BC213L	12 BD150	50 BF197	15 BFY52	34 R2322	50
AD142	1.18 BC227	12 BD163	98 BF198	19 BR116	1.50 R2443	25
AD143	1.08 BC238B	8 BD201	74 BF199	15 BR1693	1.43 RCA16446	30
AD149	98 BC238L	8 BD203	78 BF223	18 BU105	1.00 RCA16599	1.25
AD161	32 BC250A	15 BD204	99 BF224	19 BU126	1.10 RCA16600	1.40
AD162	32 BC251	8 BD222	48 BF238	20 BU207	1.05 RCA16799	1.13
AD263	1.05 BC252A	20 BD225	52 BF240	9 BU208	1.15 RCA16800	1.42
AF127	45 BC294	37 BD232	50 BF241	21 BU208A	1.15 RCA16802	1.38
AF139	38 BC301	32 BD233	60 BF255	10 BU326A	1.30 RCA16815	1.20
AF239	41 BC303	31 BD234	60 BF256LB	38 BU407	1.70 SP8385	2.65
BC107	15 BC307	10 BD237	55 BF256S	28 BU408	2.76 S1299	2.25
BC108	15 BC308	8 BD238	65 BF257	28 BU500	2.30 S2800	1.25
BC109	15 BC309	14 BD241	59 BF259	28 BU526	2.46 T6050V	1.30
BC115	16 BC327	10 BD244	85 BF271	25 BU626	1.80 T6052V	1.35
BC117	21 BC328	18 BD278A	81 BF274	11 BU807	2.94 T9003V	1.25
BC125	26 BC337	17 BD386	68 BF337	29 C1129	9 T9010V	1.45
BC126	23 BC338	17 BD433	71 BF338	34 C1172B	9 T9053V	1.30
BC139	27 BC347	8 BD437	83 BF355	40 E5386	54 T9054V	1.00
BC141	34 BC394	8 BD592	1.20 BF362	50 E9003	28 T9039V	1.10
BC142	30 BC454	8 BD589	1.20 BF391	21 E9005	25 TIC45X	5.00
BC143	31 BC455	8 BD677G	1.26 BF394	16 ME0404	10 TIC46	48
BC147	12 BC456	10 BD679	1.12 BF422	47 ME0412	10 TIC106C	40
BC148	12 BC460	40 BD701	1.04 BF423	53 ME6002	10 TIP29	42
BC149	12 BC463	22 BD702	1.12 BF450	43 MJ2501	2.36 TIP30	42
BC153	16 BC546	8 BD707	95 BF453	53 MJ3001	2.21 TIP31	35
BC1540R	16 BC547	12 BD708	95 BF458	37 MJE340	50 TIP32	43
BC154YL	16 BC548	12 BD708	1.30 BF459	40 MJE520	50 TIP33	61
BC157	12 BC549	8 BDX10	93 BF461	59 MJE2955	1.40 TIP41	42
BC158	12 BC557	10 BDY20	1.09 BF556B	35 MJE3055	1.50 TIP42	45
BC159	15 BC558	10 BDY82	99 BF596	15 NKT241W	8 TIP110	61
BC171	9 BC559	8 BF137	20 BF694	16 NKT241G	8 TIS91	25
BC172	9 BC595	8 BF153	20 BF757	62 NKT241Y	8 ZTX550	30

### INTEGRATED CIRCUITS

BRC1330	1.40 SN76013ND	1.80 TBA530	1.26 TDA2030	2.10
BRC3064	1.00 SN76023N	1.80 TBA540	1.00 TDA2522	2.10
BRC/M/200	1.00 SN76033N	2.00 TBA560C	1.82 TDA2530	2.61
BRC/M/300	1.00 SN76115	2.00 TBA641	1.50 TDA2540	3.50
CA3060	1.58 SN76131N	1.58 TBA651	2.05 TDA2560	3.50
LM1303P	1.48 SN76226N	1.25 TBA720A	2.49 TDA2581	3.00
ML231B	2.20 SN76227N	1.00 TBA750	2.20 TDA2591	1.90
ML239B	2.86 SN76227N	1.00 TBA810S	1.82 TDA2640	1.95
ML1327AP	1.25 SN76600N	80p TBA810AS	1.00 TDA2690A	1.50
MC1358P	1.30 SN76666N	75p TBA920	1.00 TDA3560	6.00
MC1455P	18p SN76744	1.20 TBA950	1.00 TDA4500	5.40
MC14516BCP	60p SY153A	2.50 TBA1440	2.90 TDA8903	2.90
SAA1025	7.20 TA7117P	1.00 TCA2705A	2.54 TCEP100	3.48
SAA1124	4.50 TA7109AP	2.80 TCA270C	1.92 TEA1009	1.95
SAA9010	6.00 TAA611	1.40 TCA2700Q	1.05 MC14426P	4.80
SL432A	1.80 TBA120B	1.20 TDA1035T	1.05 MC14514	4.50
SL1430	2.50 TBA120C	1.20 TDA1037	1.05 UA758PC	2.50
SL1432	2.50 TBA120CQ	1.30 TDA1170	3.75 UAA1008A	2.66
SN15846N	60p TBA120S	70p TDA1170S	2.15 ULN2165	1.30
SN14123N	65p TBA120U	1.00 TDA1200	1.76 ULN2216A	1.25
SN74154N	1.40 TBA395	1.00 TDA1270	2.42 UPCI365C	5.75
SN76001N	1.40 TBA480C	1.00 TDA1327	95 SC9889P	1.40
SN76110N	1.14 TBA510	1.20 TDA2002	2.76 SE9511P	1.40
			2.53 SW153	2.50

Thom 8/8K5 ex equip panels untested	3.75	Thom 3/3K5 ex equip panels untested	3.75	Thom 4000 Convergence panel ex-factory	3.75
PSU	2.88	PSU	3.75	Thom 4000 PSU panel ex-factory	2.50
FTB	3.75	LTB	3.75	Thom 3K5 beam limiter board	1.75
Decoder	4.00	Video	2.50	new	1.75
		Chroma	2.00	Thom 3/3K5 EHT & scan TX + untested	2.75
		FTB	1.75	R2008B on alum chassis ex-factory	1.80
Thom 9K ex equip panels untested	12.00	IF	3.00	Thom 8/8K5 damaged FTB for spares	1.25
PSU	5.00	Conv. 3K	3.75	Thom 8/8K5 damaged decoder for spares	2.25
Decoder		Autovox Decoder FG/01 boxed	5.00		

UHF TV Aerial for portable	50p	Coax Plugs	10 for 1.65
Indoor Aerial With Reflector		Band Change Switch Assy, Pye 725	40p
to Help Combat Ghosting Problems		Coax Cable Low Loss	per Metre 72p
Line Connectors		38p Switched Flush Fitting Aerial Outlet	1.00

Pye 78+161	50p	EHT TRAYS	
Pye 147+260	50p	Thom 3000	5.50
Thom 56+1K+47+12	1.24	Thom 8000	4.50
Thom 50+40+1K5	60p	Thom 8500	6.00
Thom 128+16+1K7+	50p	Thom 9000	7.90
116+462+126	50p	Thom 9600	6.00
Thom 120+72+300	50p	Thom 900/950	1.50
RBM 250+14+58	63p	Thom 1500 3 stick	2.40
(TV161)	63p	Pye 713 4 lead	5.83
Pye 3R5+15+45 (713)	90p	Pye 713 5 lead	5.97
Philips 2R2+682	90p	Pye 725	6.35
Philips 47R	52p	Decca Bradford	5.00
Thom 6+1+100	92p	Baird 8750	7.10
Thermal Cut-Out		Korting AZ9100	7.10
Thom 3000 Metal	1.45	Philips G8 (520)	6.50
Thom 8/8500 Plastic	1.45	Philips G8 (550)	6.50
		Universal	5.00

### MULTISECTION CAPACITORS

220+47	350V 65p	200+200+100	350V 55p	
200+150+50 350V	60p	200+200+75+25	350V 60p	
200+200+100		50+50+8	300V 55p	
32+32+16	325V 52p	100+50+100	350V 55p	
200+200+100+32		100+150+50	350V 55p	
100+50+150	350V 70p	2500+2500 (Thom 8K)	63V 1.20	
400+400	200V 72p	150+150+100	300V 1.80	
32+32+16	350V 52p	200+47	250V 65p	
200+32+300+100		500+500 175V	Thom TX9	1.00
225+25	350V 50p	175+100+100 350V	Thom 3K5	2.25
200+200+100		400 400V Thom 9K	2.50	
200+100	350V 70p	470 250V Weldtel Type	Philips G11	1.71
200+100+100+50				
350V 60p				

### CAN TYPES

0.2MF 250V	50p	1250MF 40V	50p
2MF 250V	50p	1250MF 50V	50p
22MF 275V	50p	1500MF 100V	1.05
50MF 275V	50p	2000MF 30V	50p
100MF 150V	65p	2200MF 40V Thom 4K	9p
100MF 250V	70p	2200MF 63V Philips G9	1.25
220MF 450V Thom 4K	1.30		
400MF 350V Thom 8K	2.50	2500MF 35V	65p
400MF 400V Thom 9K	1.00	2500MF 40V	65p
400MF 450V Thom 9K	2.95	3000MF 30V	65p
800MF 250V			

# TRADE ANNOUNCEMENT

## CHROMA VISION (Manchester) NOW OPEN!!!

95 LANGWORTHY RD, SALFORD M6 5PH. Tel. No. 061-736-6333

811 WASHWOOD HEATH RD, WARD END, BIRMINGHAM 8. Tel. No. 021-784-2561

*Large range of late model TV's and Videos at low, low prices*

**THORN AND PHILIPS TELE-TEXT, REMOTES AND BASICS**

### ★ PHILIPS

Working			Untested	
G11 660 .....	£45	Tested G11	G11 660 .....	£35
G8 550 22" .....	£20	Tubes .....	G8 550 .....	£12
G8 520 22" .....	£15		G8 520 .....	£8
G8 560 20" .....	£30		G8 560 .....	£20

### ★ THORN

9600 .....	£38	Tested Thorn	9600 .....	£30
9000 .....	£28	9000 Tubes .....	9000 .....	£20
8800 .....	£20		8800 .....	£15

### ★ PYE

G11 .....	£55	Tested 22" 26"	G11 .....	£45
222 22" .....	£20	Delta Tubes .....	222 22" .....	£15
725 20" .....	£25		725 20" .....	£20
Chelsea 18" .....	£25		Chelsea 18" .....	£20

### ★ ITT

CVC 30 .....	£38	Buy in one's	CVC 30 .....	£30
CVC 20/3 .....	£35	or 100's	CVC 20/3 .....	£25
CVC 20 .....	£30		CVC 20 .....	£25

### ★ GEC

In line (Starline) .....	£50	And Many More, i.e. Bush T20 .....	£35
G.E.C. 2201 .....	£25	Decca 100 .....	£35. Japs, Tandburg etc.

*Too many to list! Why not come along and have a look*


★ **WORKING & SERVICED!!! VHS VIDEOS 100's IN STOCK**

**1000's MORE UNTESTED SETS OFF THE PILE**

★ **Lorry loads direct from source** ★ **Delivery arranged**

All prices subject to V.A.T.

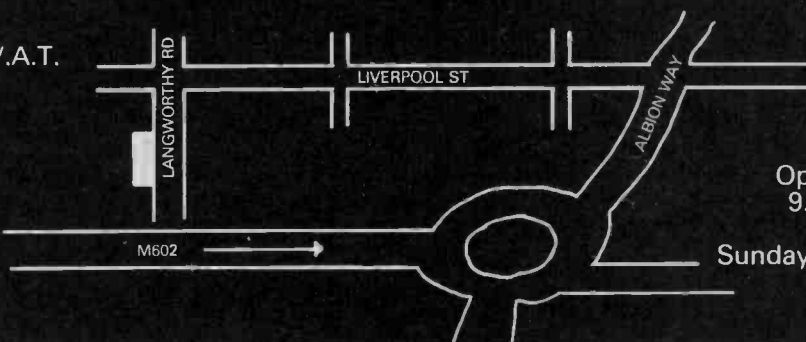WE ARE HERE  
Only 2 minutes from  
end of motorway



Open 6 days a week  
9.30 a.m.-6.30 p.m.

Sundays by appointment

# The Lid off Microcomputers

Part 6

Mike Phelan

From the servicing point of view microcomputer faults fall into similar categories to those experienced with other forms of consumer electronics equipment. A goodly proportion result from owner misuse in one way or another. This category includes mechanical damage (including spillage), operating errors, misuse of or faults in peripheral equipment, and defective software.

There's also a "grey area" where the user is trying to make the computer do, via his own software, things it was never intended to do. This may be due to a misunderstanding of the language dialect or maybe because the user is unaware of operating system changes that affect his programs, particularly those written wholly or partially in machine code. Dealing with this type of "fault" requires a fairly good acquaintance with the microcomputer concerned.

Taking mechanical damage first, in addition to obvious things like damaged plugs, sockets and edge connectors the keyboard is susceptible to spillage. The rubber membrane type, as used in the Amstrad CPC464, is fairly waterproof. If liquid gets on to one of the printed boards there can be a lot of trouble, especially if the machine is switched on before it has dried out. Spilt liquids can corrode the printed tracks, i.e. pins and holders, in which case a new board is the only cure. In less severe cases a good wash in warm soapy water, followed by thorough drying, may do the trick.

Peripheral failures can cause many problems. Monitor faults should be easy to diagnose (we'll discuss the Amstrad monitors next month).

## Printer Troubles

Printer troubles can be mechanical or electronic. The latter usually show up when one of the bits of the parallel printer code is either missing or stuck at one or zero. Careful comparison between what's been printed and what should have been printed will usually pinpoint this. Don't forget that the cause of this sort of fault can lie in the computer's print latch or buffer – or the lead to the printer.

## Cassette Failures

Cassette department failures probably account for more complaints than anything else, especially with first time users of a machine that doesn't have its own cassette recorder. The best way to illustrate what's involved is to list the requirements for the system to work – this application is far more critical than normal audio signal recording. To load and save software successfully we must have:

- (1) Correct azimuth setting of the record/playback head.
- (2) A clean head, tape transport system and a good h.f. response. Don't use a stereo machine.
- (3) An undamaged tape, recorded at correct level on a machine with correct azimuth and a good h.f. response.
- (4) The recording must start after the tape starts, otherwise information contained in the header will be lost.
- (5) Correct playback level – this often means using the

external speaker socket on the recorder rather than the "audio output" which is at a much lower level.

Attention to these points will eliminate most troubles. It's worth bearing in mind that there are recorders whose response has been tailored to make them suitable for computer use – other models can be given a slight h.f. boost by altering the values of feedback or equalisation capacitors. A good way to set the azimuth is to play a good commercial software tape and listen to the audio: the correct azimuth setting should be obvious and fairly critical.

## Computer Faults

This leaves us with genuine microcomputer faults. Due to the operating principles, fault finding can be difficult – especially with intermittent faults or those of a thermal nature, since the symptoms may remain even when the fault clears.

Quite often a test ROM and/or test cassette is available from the manufacturer. This carries out a series of tests, maybe selected by the user from a menu. The test ROM takes the place of the normal one so it cannot test this, while a test cassette relies on the cassette interface working correctly.

Obvious faults would be things like malformed characters, e.g. the lower dot missing every time a colon is printed. Finding the cause may not be so simple however. Say the fault is in the ROM. At switch on the character set is loaded into the RAM so that the symptom would remain even if the ROM fault cleared as the machine warmed up. Alternatively the character location in the RAM could be corrupt, giving the same symptom except that in this case the contents could be put right by the user. One of the tests provided by a test ROM or tape is to fill every RAM location with ones and zeros and read these back. Any failure has its address displayed so that the i.c. concerned can be replaced.

CRTC failure affects the screen display, sync or blanking, or there may be failure to scroll or for anything to appear on the screen. With many microcomputers there's a faint, audible breakthrough from the speaker when a programme is running – almost like a repetitive tune. This can prove that the CPU is operating though the screen may be blank.

Failure of the operating system to get the computer going correctly can result in some strange errors that will persist even when the fault clears – until a complete reset is performed. A screen full of garbage could be the result of something like this, or of a missing or malformed system reset pulse at switch on. This type of fault often leaves the keyboard dead.

The Amstrad test ROM includes a very useful test of the cassette interface. It gives a display like a spectrum analyser of two groups of frequencies corresponding to ones and zeros. These should be in two well-defined groups, with not too many "stragglers" between – the latter would mean poor "eyeheight". Don't forget that in most programs there's at least one bit that if changed will cause a system crash (stop): this bit would coincide with a

section of missing tape oxide or a crease. The result could be anything from premature finish of a game of Space Invaders to the loss of five years' household accounts.

The most critical part of a BASIC program consists of the byte(s) stored at the beginning of each line to show where the next line starts in the RAM. It needs only one of these links to be corrupt for the program from that point onwards to be lost. To explain this further, say the microcomputer in question fills its RAM with 01010101 at switch on then loads the operating system. All unused RAM will still contain 85 (01010101 binary). Lines of BASIC are stored with a zero to show the end of a line while the first two bytes in each line are the address of the start of the next line (link address). If one of these link addresses is corrupt (usually due to excessive playback

level from tape) it will probably point to an unused section of RAM. As this will be taken as the next line, the link address for the following line will be #5555 (85, 85). So will the line number – it will be taken as 21845, i.e.  $(85 \times 256) + 85$ . The line will be shown as a string of capital zeros (ASCII 85) – pages and pages of them until the micro finds something else! We can sometimes get out of this: if we edit a program the operating system is forced to recalculate all the link addresses from that point on. So if you load a BASIC program that comes out as a few lines of good code followed by 2184500000 etc. add a line then remove it. This should put matters right. Then check the cassette volume.

Next month a slight move towards TV servicing as we look at the Amstrad CTM640 colour monitor.

## Letters

### ITT CVC20 SERIES

Having serviced many ITT sets I found S. Simon's article on the CVC20 chassis and its derivatives (August issue) interesting. It covered the majority of common faults, though more obscure troubles are beginning to occur as these sets age. I've come across the following faults and hope that these notes will be of help.

The most common cause of a dead set, i.e. no LEDs alight on the CVC30 etc., is the tags on the on/off switch parting company with the PCB. Hand wiring to the spare tags at the top of the switch is more effective.

A fault we've occasionally had on the CVC30 chassis is R28 (820Ω) going open-circuit. The result is a bright, blank unmodulated screen. R28 feeds the flyback pulse from the line output transformer to the TBA560C i.c. in the decoder.

Continuous springing of R101 in the CVC20 chassis with nothing amiss on the EW modulator panel and the driver transistor T17 o.k. is caused by the EW modulator transformer L33/L34 burning up. This burning up can be the result of C72 (4.7μF) going open-circuit.

As mentioned in the article D8 in the CVC20's field output stage can fail, causing field collapse. But this component has a habit of being intermittent: it's the first component to replace when a set with intermittent field collapse comes along. The driver transistor T8 (BC337) can be destroyed during one of D8's tantrums. Demise of the output pair T9/T10 at regular intervals has been traced to C21 (10μF), the reservoir capacitor for the negative supply to T7, drying up – a clue to this is that the anode of D8 is at around 5.6-5V instead of 8V.

C19 (22μF) and C20 (10μF) in T7's base circuit can be responsible for insufficient height with bottom foldover.

If C26 (22μF) and C24 (1μF) – C23 (22μF) in the CVC30 chassis – in the field flyback – blanking circuit go open-circuit text/flyback lines are visible at the top of the screen. The print from these capacitors is quite thin as it goes around the aerial socket. We've known this to break on its way to plug L1.

The most common cause of field collapse or lack of height in the CVC30 is the print around the emitter of T9 disconnecting itself from the chassis. Slight field bounce is caused by C2001 (2.2μF) going open-circuit.

C701 (all chassis) on the line oscillator panel drying up

(its value is 100μF) results in the set tripping a few times before coming on. It can also cause a slight line squeal. Another electrolytic on this panel, C708 (4.7μF), is responsible for striations extending a few centimetres from the top of the screen.

C45 (4.7μF) – C42 in the CVC30 chassis – drying up can result in intermittent tripping, horizontal black lines and a deafening whistle. This electrolytic is in the power supply.

Low volume has been traced to the audio output coupling capacitor C3 (470μF) – it's C5 in the CVC30.

In the event of a hum bar, with hum on sound and reduced height, check the soldering of the earth tags around the line output transformer. Similar symptoms can be present when the 12V regulator transistor plays about – T14 (BD136) in the CVC30, T15 (BD132) in the CVC20.

Finally, with a tripping set removal of the line oscillator panel tells you whether there's a direct or an indirect short across the h.t. supply.

Ray Dunleavy,  
Raphoe, Co. Donegal.

### SONY KV1810UB MODIFICATION

I dreaded the fate of my Sony KV1810UB every time my wife Hoovered from the same bank of mains sockets. Last week the inevitable happened, and I decided I wouldn't spend any more money on GCSs. Instead I turned to Bernard Pruden's article in the December 1984 issue (page 82). I want to thank him for that article, because the KV1810UB now works a treat and I no longer have the fear of big expense.

The article was concerned mainly with the Mk. I version of the set but the suggestions worked for my Mk. II. Instead of a BU426A I used a BU326A with further mechanical modification to the original chopper metal plate. I also kept the old line driver transformer: I cleaned its metal fin and put plenty of heat transfer compound between the fin and the main aluminium framework.

Anyone willing to convert their KV1810UB should not hesitate about following the recommendations in the article. The modification really does work.

G. Bakawala,  
G.B. Electronics, Coventry.

### THORN 1613 CHASSIS

An interesting but simple fault came our way recently on a 12in. Ultra portable fitted with the Thorn 1613 chassis. The basic symptom was a noticeable drop in brightness over several months. The first anode voltage was checked

and found to be correct and we then found that a good brightness range could be obtained by adjusting the set video level preset. This produced four or five faint vertical lines however, approximately one third of the way in from the left-hand side. Checks in the line timebase failed to reveal anything amiss and after much head scratching we found that the lines disappeared when the brightness was reduced. We also obtained a clue by doing this – the third of the screen with the lines went dark more quickly than the other two thirds of the screen.

The penny then dropped. The supply for the video output transistor is obtained from a winding on the line output transformer. W14 is the rectifier concerned and C106 (10 $\mu$ F) the reservoir capacitor. When C106 was removed it was found to be open-circuit, a replacement restoring normal results. The same sort of thing happens with the National Panasonic Model TC85G when the reservoir capacitor for the supply to the luminance output transistor dries up, producing a darker display on the left-hand side of the raster.

*Michael Dranfield,*

*Dranfield and Harrop, Buxton, Derbyshire.*

### BBC MICROCOMPUTER PROGRAM

The following program for the BBC microcomputer Model B will provide an external trigger pulse, coincident with each field, for an oscilloscope. Sync, which can be taken from PB7 at the user port, can use the negative-going transition at the start of each field or the positive-going transition 10,240 $\mu$ sec later, about half-way through the field.

```
10 MODE 2
20 ?&FE6B = &80
30 !&220 = &FFA60074
40 !&72 = &28A90000
50 !&76 = &60FE658D
60 VDU&419; 0; 1023; &419; 0; 0; 5
70 FOR a% = 7 TO 0 STEP -1
80 VDU18; a%/2+4*(a%AND1), &5119; 160; 1023; &5119;
0; -1023;
90 NEXT a%
100 *FX14, 4
110 IF GET MODE 7
120 *FX13, 4
130 END
```

*J. M. Collick,*

*Westbury-on-Severn, Glos.*

### SUPPRESSING MAINS TRANSIENTS

In connection with Derek Snelling's article on VCRs and the mains supply in the July issue, Maplin have a component which can be fitted inside the mains plug of these expensive units. It's referred to as a mains transient suppressor, type HW13P (Maplin list number), and is very good. Whilst it looks like and is about the size of an ceramic disc capacitor it's very different, acting like a high-power, bidirectional zener diode. When connected across the live and neutral terminals it conducts when the voltage across them exceeds a certain value, around 600-800V, thus clipping any spikes present. The usual mains filter components within the VCR, microcomputer or whatever then reduce what's left of the spikes further, leaving all those micro chips to get on with their work undisturbed. Note that when an HW13P is used in a mains plug the fuse there should be of 3A maximum, and quick-blow at that.

I think the time will soon come when the manufacturers of VCRs, microcomputers etc. will have to provide at the end of their mains leads a big plug case containing a very good mains filter – if you rock the mains plug of a microcomputer when inserted in the socket a number of nasties can occur in the computer circuits.

*R. M. Porter,*

*Bristol.*

### SPECTRUM 48K PROGRAM

The following program produces on the 48K Spectrum a crosshatch pattern with the horizontal lines extending into the border at the edge of the screen. Lines 10-50 enter the code into the memory while line 60 tests for the correct check sum. Note that this test is not infallible, so save the program before trying it out. After the screen goes dark, press any key to get the crosshatch: the break key returns to BASIC.

```
10 LET C = 0
20 FOR Z = 32802 TO 32975
30 READ N: POKE Z, N
40 LET C = C + PEEK Z
50 NEXT Z
60 IF C <> 18810 THEN PRINT "ERROR IN PROGRAM":
STOP
70 RANDOMIZE USR 32883
80 DATA 251, 201, 62, 10, 237, 71
90 DATA 237, 94, 118, 62, 0, 211
100 DATA 254, 227, 227, 134, 134, 0
110 DATA 14, 30, 205, 102, 128, 6
120 DATA 150, 16, 254, 13, 32, 246
130 DATA 62, 127, 219, 254, 31, 48, 2
140 DATA 24, 225, 62, 62, 237, 71
150 DATA 237, 86, 205, 107, 13, 201
160 DATA 80, 82, 79, 71, 82, 65, 77
170 DATA 32, 66, 89, 32, 77, 32, 74
180 DATA 32, 69, 68, 73, 83, 62, 7
190 DATA 211, 254, 6, 16, 16, 254
200 DATA 62, 0, 211, 254, 201, 62, 0
210 DATA 205, 155, 34, 62, 7, 50, 141
220 DATA 92, 205, 107, 13, 62
230 DATA 2, 205, 1, 22, 17, 83, 128, 1
240 DATA 19, 0, 205, 60, 32, 1, 0, 0
250 DATA 205, 61, 31, 205, 107, 13
260 DATA 62, 255, 230, 255, 24, 2
270 DATA 214, 15, 245, 79, 6, 191
280 DATA 197, 175, 120, 205, 176, 34
290 DATA 205, 236, 34, 193, 16, 244
300 DATA 241, 32, 235, 6, 7, 14, 0
310 DATA 197, 175, 120, 205, 176, 34
320 DATA 6, 32, 54, 255, 35, 16, 251
330 DATA 193, 120, 198, 10, 71, 254
340 DATA 191, 56, 234, 205, 36, 128
350 DATA 201
```

*M. J. Edis, G4RPT,*

*Broughton, Northants.*

### VIDEOTAPE BIASING

In reply to Mr. Catchpole's letter "Videotape Warning" (September), as with audio tape recorders the bias frequency for recording must be chosen for the tape type and the speed of the tape past the heads. The effective tape speed with the V2000 system is different from that of the VHS system, so the tape isn't biased correctly. The "fundamental difference in the composition of the tapes" is thus the tape bias frequency.

*Colin McCormick,*

*Plymouth, Devon.*

# Teletopics

## SATELLITE TV MOVES

While UK efforts to start a DBS service have for the time being fizzled out the French are busy getting their DBS act together. The four-channel French DBS satellite TDF-1 is due to be launched next July. The company running it will be 50 per cent French and 50 per cent foreign owned, with the French government taking a 34 per cent blocking interest. Of the foreign organisations, Robert Maxwell (Pergamon Press/Mirror Group Newspapers) has taken the largest interest, 20 per cent. The Luxembourg financial institutions Sofilec and Marner are expected to share a 17 per cent interest, Silvio Berlusconi who runs Italy's largest private TV network is to take an 8 per cent interest while the remaining 5 per cent interest will be held by Philips. The initial capital will be FFr 30m (£2.5m): this is expected to rise to FFr 600m.

At least 150m W. Europeans will be within the satellite's service area. One of TDF-1's channels is to be devoted to a cultural/educational service for which the French government is to provide funds totalling FFr 700m. Robert Maxwell plans to run a second channel which will provide general entertainment and be financed by advertising. The other two channels may be run by CLT (Compagnie Luxembourgeoise de Telediffusion).

It seems that many financial details remain to be sorted out. CLT for example is unhappy at the suggested charge of FFr 90m (£7,625,000) a year to lease a channel in view of the small initial audience (the charge for leasing a channel on the lower power ECS-1 satellite is FFr 15-20m).

One interesting aspect is the transmission standard to be used. Japanese setmakers would be able to supply receiving equipment very quickly if the signals were transmitted in PAL or SECAM form. The MAC system, developed in the UK for satellite TV use, would provide improved performance and is protected by IBA patents. Considerable investment has gone into MAC decoding chips and the use of this system would give European setmakers an initial advantage. Unfortunately it would make the receivers more expensive and it might well be thought by the TDF-1 authorities that this would be detrimental to getting the service started on an economic basis.

A World Administrative Radio Conference with representatives from some 120 countries is at present being held in Geneva to consider procedures for the allocation of orbital positions and frequencies for geostationary communications satellites. Developing countries have been demanding orbital allocations and have expressed concern that the geostationary orbit is being rapidly filled with satellites. There are already some 120 satellites in this orbit and a further 100 are expected to be launched during the next five years. The USA has called for a simplified procedure for notifying plans for satellite launches to the ITU and a voluntary moratorium on the use by industrial countries of certain frequency bands.

Unisat, the consortium set up by GEC-Marconi, British Aerospace and British Telecom to produce the satellites for the now abandoned UK DBS project, has closed its London office. It will not be shut down completely: a holding operation is to be retained in case of future DBS

work coming its way. Unisat invested £50m in the DBS project and whether any of this can be recovered is in doubt.

## REDIFFUSION TV PLANTS FOR SALE

A question mark hangs over the future of the Rediffusion setmaking operations. The plants, at Bishop Auckland, Co. Durham, Billingham, Teesside and Rochdale – there is also a design centre at Chessington, Surrey – have a maximum production capacity of 150,000 sets a year. They were originally established to supply sets for the Rediffusion cable and rental operations – the sets have also been sold by Doric Radio, a Rediffusion subsidiary, and under the Murphy brand name. When Granada bought the Rediffusion rental chain from BET in mid-1984 an agreement was reached that Rediffusion would supply Granada with sets until the end of 1985. It seems that Granada, who have at various times bought sets from Salora, GEC, ITT and Tatung, are unwilling to continue to take Rediffusion sets while BET wishes to withdraw from the consumer electronics field completely. BET has been having discussions with overseas companies on the future of Rediffusion Consumer Manufacturing. While BET would prefer to sell RCM a joint venture has not been ruled out. Sharp has provided technical know-how in the past (the Rediffusion Mk. V small-screen TV chassis): since it's the only major Japanese setmaker without production facilities in the UK Sharp might be interested in running the plants.

Tatung (UK) Ltd. has decided to move its Research and Development Department from Bradford, W. Yorkshire to Telford, Shropshire, adjacent to the new Tatung CTV plant.

## TED TURNER

Our June leader commented on the attempt by Ted Turner's Atlanta based Turner Broadcasting Systems to take over the USA's premier television network CBS. CBS responded by taking protective measures, including a buy back of shares, but before the crunch came Ted Turner decided to take over MGM/UA instead, offering \$29 a share. The deal, which has yet to be finalised (Ted Turner still has to find \$1bn), is a complex one which will be partly financed by selling United Artists to the group's main investor Kirk Kerkorian for \$470m. The attractions of MGM to Ted Turner include its large film library, world-wide distribution network and production studios. MGM's profit record has been patchy in recent years but Ted Turner evidently feels that the price he is paying – twice the market value before takeover speculation began – will be worthwhile once MGM has been linked up with his cable and satellite TV interests.

## SERVICING PROSPECTS

In a recent address to the Television and Radio Industries Club Dr. Jim Maxmin, director of Thorn EMI's home electronics division, had some ominous comments to make on the prospects of the domestic electronics servicing trade. It's possible, he said, "to envisage a situation where service is reduced to virtually nil and when a major fault occurs you simply replace the set". Well, he did say a major fault: those of us dependent on the servicing trade can console ourselves with the thought that mains switches and aerial sockets will continue to break, tuners to drift,



transistors to leak, electrolytics to dry up and dry-joints to put in an appearance. With all due respect to Dr. J., we've heard this one before! It's unlikely that the public will ever accept that its treasured tellys have to be scrapped when simple or even not so simple faults occur. The setmakers could be awkward of course and refuse to supply things like LOPTs etc., but past experience has always been that when there's a proven need for such an item some bright spark will produce a suitable replacement type. Odder still was Dr. Jim's remark that dealers will be deprived of the support of their servicing revenue. For all too many dealers the servicing side has traditionally been a pain in the neck!

Perhaps a more interesting development is Sony's decision to sell a 50 per cent interest in its five servicing centres to existing managers and engineering staff. The centres, at Dulwich, Oldbury, Cumbernauld, Leeds and Staines, will continue to trade as Sony Service Centres. Sony's future plans are to reduce its financial interest in the centres further and to set up additional independent service centres. In fact Sony seem to be open to offers right now - provided the proposed location is suitable.

### **MULLARD WIDEBAND HF AMPLIFIER IC**

Mullard have introduced a new four-terminal, fixed-gain, wideband h.f. amplifier, type NE5205, which is designed to provide a non-inverted gain of 20dB from d.c. to 500MHz with low noise - the -3dB bandwidth extends to over 600MHz. A 6V supply at 25mA is required and the noise figures are 4.8dB in a 75Ω system and 6dB in 50Ω applications. It's available in several packages include SO and TO46 - plastic DIL and cerdip packs are to follow. Applications include cable TV decoder circuits, aerial amplifiers etc.

### **RECORD INDUSTRY IMPROVING**

Not a TV matter perhaps but of interest nevertheless to those who watch the trade. It seems that the compact disc is at last catching on: deliveries during the second quarter rose to 542,000 in comparison to 135,000 during the same quarter last year. Sales of records, cassettes and compact discs have all been on the increase and expansion seems to be the present preoccupation in the record industry, with proposals for several large new stores having recently been announced.

### **VIDEOCONFERENCING EQUIPMENT**

GEC McMichael have developed some sophisticated equipment for videoconferencing use - videoconferencing enables groups of people to hold conferences via a video link. The Hilton Hotels Corporation has inaugurated a network in four major US cities (New York, Washington, Chicago and San Francisco) using GEC McMichael video codecs. These transmit only those parts of the TV picture that change between one field and the next, allowing the picture to be transmitted at lower cost without loss of quality. GEC McMichael's new split-screen unit, Model TE561, enables the images from two cameras to be transmitted over a single video link. This allows the number of participants at a table to be increased to at least six when showing their heads and shoulders. The unit exploits the inherently superior linearity and resolution of the centre horizontal portion of the picture. The top and bottom portions of the pictures from two cam-

eras, each viewing three individuals, are eliminated using digital techniques: the resulting half-height pictures are then stacked one above the other and transmitted to the remote conference room. If the remote terminal has TE561 facilities the stacked images can be decoded and viewed on two adjacent screens to recreate the original scene. In the absence of decoding facilities the stacked images can be viewed on a single monitor.

### **CES DOUBTS**

There seem to be doubts as to whether the 1986 Consumer Electronics Show (see Teletopics June) will in fact take place. Twenty two major brown goods manufacturers and suppliers have decided instead to hold the traditional hotel shows and many, including Binatone, Grundig, Hitachi, JVC, Luxor, Mitsubishi, NEC, Network, Panasonic, Salora, Samsung, Sanyo, Sharp, Teleton and Toshiba, have already made bookings. Alan Taylor, organiser of CES, nevertheless reports that out of 10,000 square metres of space available at Earl's Court some 6,300 have already been reserved, about half of which have been actually booked.

### **BBC MICROCOMPUTER SYSTEM**

The BBC has announced that from August 1st the price of the teletext adaptor part of the BBC microcomputer system, required for telesoftware use, has been reduced to £149 including VAT. The adaptors are available by mail order from Vector Marketing, London Road, Wellingborough, Northampton NN8 2RL.

### **CABLE NEWS**

The Cable Authority has announced approval of the second batch of cable franchise applications - final confirmation of the schemes has to come from the DTI. Schemes approved are East London Connections in the London Docklands development area; Bolton Telecable in Bolton, Lancs; British Cable Services (Rediffusion) in W. Surrey/E. Hampshire; Cotswold Cable in Cheltenham and Gloucester; and Shaw Cable in Wandsworth, London. The East London Connections scheme is of particular interest in that it will involve laying two sets of cables, one to provide an entertainment service and the other for voice and data communications. The intention is to offer customers connections to the British Telecom and Mercury telecommunications networks and overseas links. Members of the East London Connections consortium include Mercury Telecommunications, United Telecoms of the USA, Ferranti and various city organisations.

Robert Maxwell's SelecTV company, which runs a number of the older types of cable networks, has reported a reduced loss of £355,570 for the year to end March and is considering a substantial rights issue to enable it to participate in new cable franchise applications. Managing director Alan Morris reported that the number of subscribers had increased during the year.

Greenwich Cable continues to make losses and has reported a continuing and substantial loss of subscribers during the spring and summer months. The company has halved its staff, abandoned its local TV and radio production facilities and is endeavouring to raise further funds.

Rediffusion's Reading cable network has introduced an information and classified advertisement channel called LocalVision. It will carry Shop TV, Littlewoods' home

teleshopping service, which is already available on Prestel. The goods on offer will vary from week to week and will initially include electrical and electronic lines: orders are placed by phone and payment is by credit card, with free delivery to the door and a satisfaction or money-back guarantee. Reading LocalVision is the first channel to use a highly automated cable advertising system from Diverse Pictures Systems, specialists in high-resolution quality graphics.

### TV PRINTERS

Mitsubishi are to launch two new TV printers, successors to the SCT-P50 digital TV printer that was introduced in October 1983. The new printers, types SCT-P60 and SCT-P70, offer far higher resolution – 630 dots horizontal by 476 dots vertical, more than four times higher than the SCT-P50's resolution. Black-and-white prints are made in 16-shade gradation and the print-out speed has been increased. The new printers incorporate facilities for connection to various types of equipment. Features include duplication for multiple copies of the same picture, negative/positive reversal printing, three-step contrast change, 525/625-line switching and field mode/frame mode switching.

### TV SETS

The recently introduced Sony 14in. colour monitor Model KX14CP1 has been designed for microcomputer and

video enthusiasts, offering high resolution (a fine aperture grill is used in the Trinitron tube), multi-standard capability (PAL, SECAM and 3-54/4-43 NTSC) and a wide range of input sockets including eight-pin digital RGB, 21-pin SCART (analogue RGB, composite video and audio), composite video via BNC and phono connectors and audio phono, catering for most microcomputer systems.

Ingersoll have introduced a mains/battery portable, Model XK512, comprising a 5.5in. colour TV section and a two-band radio. VCR input and earphone sockets are provided. The suggested price is around £220.

Goodmans Loudspeakers (2 Marples Way, Kingscroft Centre, Havant, Hants.) has been appointed sole distributor for Saba TV and video equipment in the UK and will be honouring all outstanding guarantees. Saba is a subsidiary of Thomson-Brandt.

### VIDEO EQUIPMENT

Sanyo's latest Beta VCR, Model VTCNX100, features instant timed recording and has a suggested price of under £300. Panasonic's latest VCR, Model NV230B, switches on and off automatically as a cassette is loaded or unloaded. The suggested price is £430.

Canon is about to introduce an 8mm camcorder, Model 8VM-E1, with a suggested price of around £920. Features include a sophisticated infra-red auto-focusing system. Unlike other mainly photographic firms, Canon manufacture the camcorder themselves. Sanyo is to introduce a Sony-sourced 8mm camcorder.

## VCR Clinic

### Sharp VC9300

This Sharp machine came in with a no-go fault. The tape was inside the machine and was badly screwed up. Now it's quite common for the reel motor to have a tight spot on this model and although it's not a two minute job replacement is simple enough. So I set to with a will and having removed what was left of the tape I loaded up and watched the action. Sure enough the reel motor hesitated. So out came the old one and in went a new one. Switch on, insert cassette and select play. Nothing!! Try fast forward and rewind. Again nothing. Faulty motor? Try record and it works . . .

At this moment the missus brought in the tea and asked why I was so distressed. "Is that all?" she said, "probably a dry-joint." I think she must have gone to school with Les's wife. My Sharp manual is not too hot to say the least: no waveforms and a magnifying glass is needed to read the circuit diagrams. Oh well . . .

The only thing common to all functions is a 64-pin microcomputer i.c. The supplies were o.k. and the clock pulses present so it seemed sensible to replace the i.c. Just then John came round. He works for himself so I suppose we are in competition but we don't work on it. "Had that fault yesterday and it was the cassette down switch" he said, "but it wouldn't record. If you haven't lost one of the supply voltages it must be the microcomputer i.c."

A new i.c. left the situation exactly as before of course. Time for a closer look at the circuit. What happens when you push record and what happens when you push play? Well on record waveform AD5 comes into the push-button unit as a row of spikes and goes to diode D8109.

*Reports from J. Hopkins, Mick Dutton, Jeff Herbert, William G. Lockett and Philip Blundell, Eng.Tech.*

On play, fast forward, rewind and stop waveform AD4 does the same thing, passing through four other diodes. That was it then, no waveform AD4. It was present on the main board and at the connector to the small board but not at the diodes, due it turned out to a dry-joint under plug HA13 – under the nice protective paint there was a hair crack too small for my old eyes. Can't tell the missus, she'd never let me live it down. **J.H.**

### Sanyo VTC5400

Wow on sound was the complaint. On investigation we found that the problem was actually capstan speed fluctuation: the speed was approximately correct but there was no tracking servo action. We disconnected the output from pin 23 of Q4002 to disconnect the capstan phase servo. The speed could then be set with VR4008 to just run through. Checks were then made on the waveforms around the i.c. When we came to the monostable we found that it had an equal mark-space ratio. The voltages here were correct so we started to check components by substitution. When C4040 (0.47µF) was changed the servo locked in solidly, though we ran through the servo set-up procedure to be on the safe side. **M.D.**

### Sharp VC7700

The customer moved house and during this process the machine got knocked. When he came to use it he found that a tape had jammed in the loaded position. We removed the covers, hinged down the bottom panel and

found that the loading motor was trying but the loading rings were jammed. These are held in place by three plastic retaining clips, one of which had broken. Fitting the replacement was very difficult and after doing this the loading motor wouldn't rotate – because the thermal cutout in the main solenoid had succumbed. Replacing this restored the machine to working order but the action of the loading motor was still weak. We had to replace Q8091 which controls the loading motor: it's a Darlington type and was not switching hard on, with the result that the loading motor was not receiving the full supply voltage. It's worth noting that this transistor grounds one side of the loading motor to switch it on. **M.D.**

### Ferguson 3V29

The customer complained that this machine kept switching itself off. We found that when a cassette was inserted and play was selected the tape would load up then unload and return to stop. The capstan motor wasn't turning, so with no take-up drive the reel sensor stopped the machine. In playback the voltage across the capstan motor was found to be only 0.2V instead of 9.3V. The circuit says that the motor's d.c. resistance is 70Ω, but it measured only 17Ω. Short-circuit turns perhaps? We measured the d.c. resistance of a new motor and found that it was 17Ω, so we amended the circuit (the machine has the combined mechacon/servo panel) and checked back to the drive transistor Q216 (2SD880).

The problem was loss of base drive. When 10V was applied to the base via the variable bench supply the capstan motor turned. The lack of drive was traced back to IC204 which was producing no output at pin 1. Replacing this i.c. made no difference and to keep the machine running the bench supply was set to 11.1V and connected to pin 1 – otherwise the reel sensor would shut the machine down before any voltage or waveform checks could be made. The next step was to move back to IC1 (VC1029) which contains the capstan speed control circuit (frequency-to-voltage converter). The speed control output voltage at pin 10 was low at 1.2V instead of 2.7V. Applying 2.7V here from the bench power supply got everything working correctly so a new VC1029 was fitted. This time we'd got the right i.c.! Pin 10 of IC1 drives pin 3 of IC204: the voltage at this latter pin had been 5.9V instead of 6.2V, a difference that's easy to miss.

After a soak test in the play mode the machine failed to complete a loading cycle and again went to stop. This time the loading belt was slipping just before the loading rings reached their stops – a new belt cured this trouble.

**J.H.**

### Hitachi VCRs

Faults that have come our way on Hitachi machines are as follows.

**VT8300:** (1) Squeaking and distortion on sound. Check the audio/control head. (2) Machine will not work, stop light flashing. Cassette bulb open-circuit.

**VT8000:** No record, no sound or vision in the E-to-E mode, no channel lights, playback o.k. Check the 12V line on the tuner/i.f. board. Check the not-12V playback voltage. R069 (1.5kΩ, 0.5W) may be open-circuit.

**VT9300:** Take-up spool stops, tape chewing. Replace the playback idler wheel.

**VT9700:** Runs slow intermittently. Capstan motor has an internal short.

**VT8500:** Goes to stop when put in the cue/review mode.

Also does this with remote operation. Check the voltage at pins 3 and 4 of the HD44801A05 i.c. (IC901). Should be low. If high suspect the i.c.

**VT11:** Chews tapes. Replace the playback/rewind/fast forward idler.

**VT14:** Will not change channels up or down. Check around the programme control chip IC721. If the voltage at pin 13 is low (should be 10V) check C712 (0.01μF).

**W.G.L.**

### Philips VR2020

We've had the following faults on this model.

**Pressure roller doesn't engage after threading up.** Suspect T7008 (BD577) or T7007 (BC548) in module U180.

**Machine threads up, pressure roller flicks over and back, then the machine unthreads and cuts out.** The pressure roller solenoid SK5 is not engaging. Check the voltage at pin 15 of module U220: if low (below 5V) T7002 (BC548) is suspect.

**No sound on loop-through, playback and record o.k.** Replace IC7051 (RC4559) in module U160.

**Video tuning mark on all the time.** Check T7005 (BC548) in the U140 sync module. **W.G.L.**

### Sharp VCRs

Some faults we've had on Sharp VCRs are as follows.

**VC9300:** For no rewind, fast forward o.k., check relay R7751 – this relay changes the polarity across the reel motor.

**VC8300:** Check the drum belt if the cassette ejects after insertion – it may be broken or stretched.

**VC2300:** Machine dead with tape trapped in the laced-up position – check Q914 (2SA770) on the servo board.

**VC9300:** Machine plays for three seconds then the capstan and drum motors stop with the tape still threaded: press the play button and the machine works. The after-loading switch is faulty. **W.G.L.**

### Sanyo VCRs

We've logged the following faults on Sanyo machines.

**VTC5000:** No results with the mains fuse F5201 open-circuit, a replacement fuse blowing – suspect the STK7216 switch-mode power supply i.c. (IC5101).

**VTC9300:** No picture on record, E-to-E and playback o.k. Check Q4 (2SK68A) on board W1.

**VTC5150:** No playback colour. Check the chroma signal at pin 27 of IC1009 (TP1016), also the voltage at pin 26. If the latter is incorrect check R1297 (12kΩ).

**VTC5600:** No E-to-E colour, loop-through o.k. Check the pilot burst cleaning pulse: suspect Q177 (2SC536KE). **W.G.L.**

### Mitsubishi HS306B

Here's another stock fault on these machines – intermittent tuning drift and a whistling noise on the sound. The cause is a dry-joint on C703 which decouples the tuning voltage. **P.B.**

### Grundig 2 × 4GB

The fault with this machine was a negative picture on E-to-E and playback for the first ten minutes. The –22V/R supply to the modulator was found to be low at –14V due to R477 (27kΩ) having gone high-resistance. **P.B.**

# Field Timebase Circuit Survey

## Part 1

S.W. Amos and E. Trundle

The main emphasis in this series will be on field output stage circuits: we will review practice from the earliest days to the present. The task of the field output stage is to drive the field deflection system, i.e. to supply it with a signal (voltage or current) of waveform and amplitude suitable to give the required vertical deflection of the scanning electron beam. The normal requirement is to deflect the beam downwards linearly with time. With the moderate deflection angles used in early picture tubes the field output stage was called upon to supply a linear sawtooth or ramp signal to drive the deflection system. Such a waveform is shown in idealised form by the solid line in Fig. 1. With the wider deflection angles used in modern flat-faced tubes the scanning beam must slow up at each end of the working stroke to give a truly linear scan on the face of the tube: the dashed part of the waveform in Fig. 1 shows the required wave shape. This alteration to the basic sawtooth waveform is called scan correction. Methods of achieving it will be described later.

### Electrostatic Deflection

The chief application for early cathode-ray tubes was in oscilloscopes. So it was natural, when public service television started in late 1936, that the first picture tubes should resemble oscilloscope tubes and use the electrostatic deflection system employed in oscilloscopes. The e.h.t. voltage used for these early tubes was by today's standards modest – around 3-4kV – but even so sawtooth voltages of the order of 1kV peak-to-peak were needed on the deflection plates. Moreover it was desirable to drive each pair of plates in push-pull to get a truly rectangular raster. Fig. 2 shows a simplified circuit of a typical field output stage of that era. Note that an h.t. voltage of 700V was needed to give the required output voltage swing.

The basic sawtooth is generated by the charging circuit C1, R1, with switch S1 (the field oscillator) providing periodic discharge of C1. As C1 charges via R1 the voltage across it increases. This rise in voltage is used as the forward stroke of the field sawtooth output waveform. At the end of the forward stroke S1 closes, short-circuiting C1 to produce the flyback. The next forward stroke commences when S1 opens again.

A variety of field oscillator arrangements have been used over the years. A blocking oscillator or multivibrator is perhaps the most common circuit. Thyratrons were widely used in the pre-war and early post-war periods while the modern equivalent, the silicon controlled switch, was quite common in early solid-state field timebase circuits. The oscillator is synchronised by the field sync signal and provides a once per field period short-circuit path to discharge C1.

The voltage rise across a capacitor that charges from a d.c. source via a resistor is of course exponential, but the early part of such a curve is a good approximation to a linear rise. In this example (Fig. 2) only 20V out of a possible 700V voltage rise is used as the forward stroke: the departure from linearity over such a small proportion of the full potential is negligible. The curvature of the voltage rise can however be used to provide scan correc-

tion in the second half of the forward stroke – an example will be described in Part 2.

Since two output stages of the type shown in Fig. 2 were required – the other for line deflection – such timebase systems were rather extravagant in terms of valves and h.t. power. During the years preceding the war it was gradually realised that an electromagnetic deflection system would be more economical on both counts though the design of the coils and the circuit was a more difficult proposition. Moreover as larger-screen tubes requiring large deflection angles and short necks were introduced the superiority of electromagnetic deflection became more obvious: it soon became standard practice in TV receivers.

### Coil Current and Voltage Waveforms

The ideal sawtooth waveform shown in Fig. 1 has a linear forward stroke and a linear flyback. With electromagnetic deflection the field output stage has to drive a current with such a waveform through the field deflection coils. Although the output was specified as a current (because it's on the current that the deflection of the beam depends) this doesn't mean that the voltage waveform is unimportant. Consider the shape of the voltage waveform. At the low field frequency the coil windings are predominantly resistive, but there's necessarily an inductive component: the coils can be represented as a resistance and an inductance in series. In flowing through the resistance the sawtooth current generates across it a voltage of the same sawtooth waveform – see Fig. 3(a). In flowing through the inductance the sawtooth current generates across this a voltage proportional to the rate of change of the current, i.e. a pulse waveform – see Fig. 3(b). The voltage across the coils is therefore the sum of these, see Fig. 3(c), and this is the voltage waveform that the field output stage must supply. As we shall see later, this voltage waveform's excursion during the flyback can be large enough to damage valves and transistors so that protective measures may be necessary.

### Frequency Response Required

Now consider the frequency range required for a field output stage. A waveform such as that shown in Fig. 1 obviously contains a strong component at the fundamental frequency of 50Hz, but in addition there is a wealth of harmonics extending theoretically to an infinite frequency. In fact Fourier analysis of the waveform shows that the amplitude of the fundamental component is nearly two thirds that of the sawtooth. Odd harmonics predominate, and their amplitudes are inversely proportional to their order, e.g. the third harmonic has one third the amplitude of the fundamental. Thus the 51st harmonic has less than two per cent of the amplitude of the fundamental and in consequence this and the higher harmonics have only a small effect on the shape of the waveform. This means that the effective upper limit to the frequency range need extend to a few kHz only – in fact the overall frequency range is similar to that of an audio amplifier.

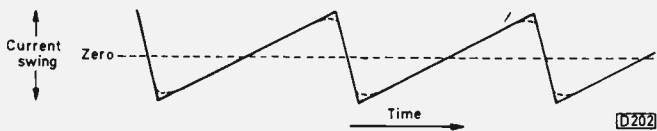


Fig. 1: Ideal sawtooth waveform (solid) with modification for scan correction shown in broken line at top and bottom.

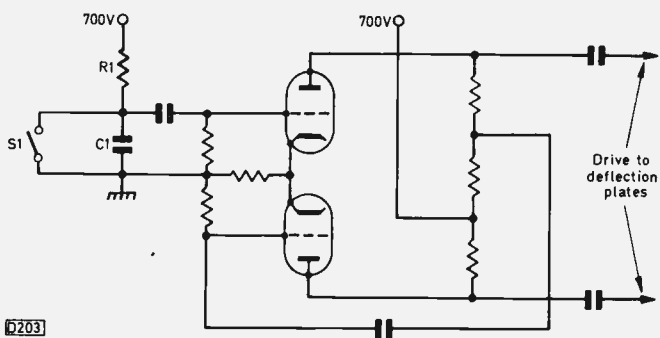


Fig. 2: Field output stage for electrostatic deflection.

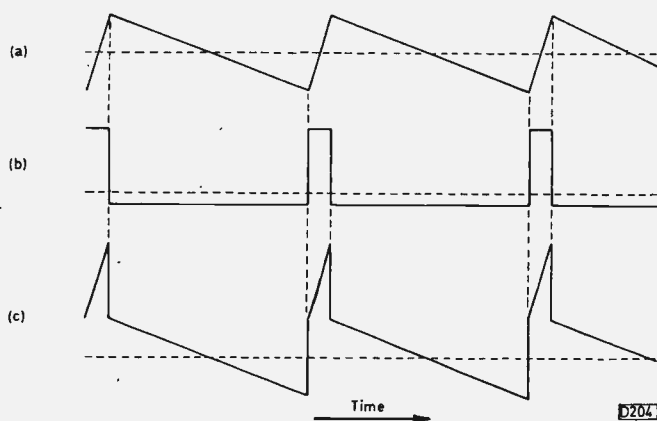


Fig. 3: Voltage across (a) a resistor, (b) an inductor and (c) the sum when a sawtooth is passed through them.

The output power required from a field output stage is usually a few watts, again similar to the requirement with an audio output stage. It's not surprising therefore that many field output stage circuits bear a strong resemblance to those of audio output stages. This analogy with a.f. practice is useful but must not be pushed too far. The signals handled by the two types of output stage are quite different for example: the field output stage handles a repetitive waveform of constant amplitude and frequency whereas the audio output stage handles a complex signal whose components are constantly changing in amplitude and frequency. At times an a.f. signal can have zero amplitude: if this occurred in a field output stage there would be something radically wrong somewhere!

### Field Scan Coils

With electromagnetic deflection the angle through which the electron beam is bent is proportional to the magnetic field set up in the tube by the scan coils: this in turn depends on the product of the number of turns on the coils and the current flowing through them – the ampere-turns in fact. Provided the ampere-turns product remains constant there can be considerable variation in the two. For example a low-impedance pair of coils might have 200 turns and require a peak-to-peak current swing of 0.5A for full deflection. This gives an ampere-turn product of 100: such a pair of coils might have a resistance

of 15Ω and an inductance of 7mH. At the other extreme a high-impedance pair of coils might have 2,500 turns and require a current swing of only 40mA for full deflection. The resistance is likely to be about 2kΩ and the inductance around 1H.

To give some idea of the practical magnitude of the currents and voltages, consider the low-impedance coils mentioned above. The peak-to-peak current required for full deflection is 0.5A, i.e. +0.25A to -0.25A. By a simple application of Ohm's Law we know that the voltage across the resistance will swing between +3.75V and -3.75V. If, to get an approximate answer, we take the field forward stroke as occupying 19ms and the flyback 1ms, then the voltage across the inductance during the forward stroke is given by  $L.di/dt$ , i.e.  $7 \times 10^{-3} \times 0.5/(19 \times 10^{-3}) = 0.18V$ . During the flyback the voltage is 19 times as great, i.e. 3.5V. The voltage across the coils thus swings between -3.93V during the forward stroke and +7.25V during the flyback, a total swing of 11.18V – 50 per cent greater than for the resistance alone.

If we repeat this calculation for the high-impedance coils with an inductance of 1H, a resistance of 2kΩ and a 40mA peak-to-peak current flow we find that the voltage across the resistance swings between -40V and +40V while that across the inductance swings between 2.1V during the forward stroke and 40V during the flyback. The voltage across the coils thus swings between -42.1V and +80V, a total change of 122.1V – again about 50 per cent greater than for the resistance alone.

### Early Valve Circuits

In the early days of television the only active device available for use in field output stages was of course the valve. The obvious way to drive the field deflection coils was to pass the anode current of a class A amplifying stage directly through them, a sawtooth input voltage being applied to the valve. High-impedance coils would clearly be needed to provide the valve with a load approximating to the optimum value, but if direct connection is used the static deflection produced by the d.c. component of the anode current is a nuisance, as also is the considerable dissipation in the scan coils themselves.

These disadvantages can be overcome by using RC coupling between the valve and the coils – see Fig. 4(a). This arrangement was used in a number of early TV receivers. The coupling capacitor had to have a value of around 64μF in order to maintain an adequate response at 50Hz. It was sometimes connected on the chassis side of the coils – see Fig. 4(b) – as a result of which the coils were at h.t. potential, say 250V. This arrangement was adopted not so much to catch out unwary service engineers (though there's little doubt that it did do this – see Chas E. Miller, *Television* May 1984, page 374) but because an electrolytic capacitor was used and it was convenient to mount it directly on the metal chassis to provide a connection to its negative terminal. Dissipation in the anode load resistor (commonly between 2-7kΩ) was considerable, necessitating a 5W or 10W component. In some designs this dissipation was reduced by using a choke instead of a resistor but the choice of choke inductance posed a difficult problem which is discussed below.

With 30mA mean anode current the valve, usually a pentode but sometimes a triode, could readily accommodate the ±20mA anode current swings and, with an h.t. supply of 250V, the 112V anode voltage swing needed

by the high-impedance coils whose characteristics were quoted above. For input the valve typically required a sawtooth voltage of 10V peak-to-peak which could be readily obtained with good linearity from an *RC* charging circuit connected across the 200-250V h.t. supply. Thus it was common in valve TV sets for the field timebase to consist of a single output valve driven by an *RC* charging circuit controlled by the field oscillator. This was fortunate because it's difficult to design intervalve coupling circuits that give the exceptionally good low-frequency response required to preserve a 50Hz sawtooth. Direct coupling is perhaps the best technique to employ but this isn't easy with valves. As shown in Part 2, transistor field timebases normally have a number of stages – an oscillator, driver and output transistor at least – but transistors, particularly complementary-symmetry pairs, lend themselves readily to direct coupling.

### Transformer Coupling

When TV receiver manufacture resumed after the war most makers decided to use low-impedance field scan coils requiring deflection currents of up to 1A, with coupling by means of a matching transformer (sometimes an autotransformer) as shown in Fig. 4(c). The transformer's turns-ratio was chosen to present the valve with a suitable value of load impedance. The coils were more robust than the high-impedance type and the transformer eliminated static beam deflection. This seemed to be an ideal solution though the effective shunt reactance present, due to the transformer magnetising current required, caused difficulties – this applied also with choke-capacitance coupling to high-impedance coils.

Ideally the inductance of the primary winding should be so large that its reactance at the lowest frequency of interest (50Hz) is many times the optimum load of the valve. It then has negligible shunting effect. If the optimum load is  $3k\Omega$ , the shunt reactance should not be less than  $30k\Omega$ , which at 50Hz calls for an inductance of approximately 100H (with probably 30mA of d.c. flowing in the primary winding). Such a component is large, heavy and expensive, so it's not surprising that setmakers preferred to use smaller transformers and to compensate in some way for the deficiencies in performance resulting from the inadequate primary inductance. For example, if the matching transformer didn't have to carry d.c. it would not require a gapped magnetic core and could thus have greater inductance. Accordingly some setmakers *RC* coupled the transformer to the output pentode as shown in Fig. 4(d). But this again necessitated the use of a high-wattage anode load resistor and a coupling capacitor with a large value. So the standard technique was to pass the anode current directly through the transformer's primary winding. The shunt reactance then causes a bad l.f. loss.

The loss of a dB or so at 50Hz in an audio amplifier might worry the hi-fi fiends but is hardly disastrous because the listening process can effectively restore the attenuated components. In a field output stage however such a loss at the fundamental frequency would introduce obvious errors in the vertical linearity of the display and these could not be corrected subjectively. The low-frequency response of a field output stage must therefore be excellent. To obtain this the loss due to the primary winding's shunt reactance can be offset by introducing a low-frequency boost. This is done by modifying the primary current waveform as shown in Fig. 5, which illustrates the effect of the increased boost needed to

maintain a good sawtooth output as the primary winding's inductance is reduced. A significant point is that if the primary inductance is reduced below a certain critical value the primary current waveform must start each forward trace with a negative-going slope. It's difficult to design a network to produce such a waveform, though it's comparatively easy to devise a means of producing waveforms such as OA which have zero initial slope and a positive slope thereafter. Fig. 6 shows the anode current waveform required in practice: the output transformer has the minimum inductance consistent with this waveform and the valve's drive waveform is adjusted to achieve the required output current waveform. The next problem is to provide the required predistortion.

### Waveform Shaping

The shape of the curve shown in Fig. 6 is similar to the *I<sub>a</sub>-V<sub>g</sub>* characteristic of a triode valve and in some immediate post-war sets this characteristic was used to shape the primary current waveform, the valve being driven by a sawtooth input voltage from the charging circuit. It was also possible to exploit the full length of the charging waveform. Unfortunately the shape of the *I<sub>a</sub>-V<sub>g</sub>* characteristic varied from valve to valve of the same type and also changed as the valve aged. A preset control was therefore included in the circuit to provide linearity adjustment as the valve's characteristic changed. This preset was usually part of an *RC* combination – such combinations were and still are widely used to obtain waveform shaping.

By suitable choice of component arrangement and time-constant, *RC* networks can be used to derive from a recurrent waveform any shape between the first derivative and the time integral of the waveform: by combining a controlled amount of the waveform thus obtained with the original waveform it's possible to alter the shape considerably. In this way setmakers were able to obtain an approximation to the waveform shown in Fig. 6, starting with the sawtooth waveform provided by the charging circuit. It's still considered desirable to have at least one preset resistor to give a degree of linearity control.

The *RC* shaping networks required could be included in the valve's control grid coupling circuit, but as valve ageing would still affect the performance it became the general practice to include the networks in a negative-feedback loop, thus making the output stage's performance substantially independent of the valve's characteristic and thus of valve ageing. It must not however be thought that the values of *R* and *C* used in the shaping circuits were arrived at empirically: there were sound theoretical reasons for the choice as the following account shows.

When negative feedback is used to linearise the waveform of the current flowing in the secondary winding the feedback voltage should ideally be directly proportional to this current and should be taken from a low-value resistor in series with the field scan coils. If the coils have a low impedance the value of the series resistor should not exceed about  $1\Omega$  in order to minimise waste of scan power. But the voltage generated across such a resistor is unlikely to exceed 1V peak-to-peak, which is too small to be of use as negative feedback for application to the control grid of an output pentode, where the normal input signal is likely to be around 10V peak-to-peak. If there was an earlier stage of amplification the voltage feedback could be applied to its input, but as

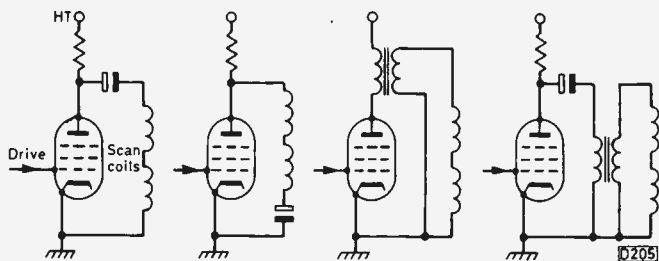


Fig. 4: Field scan coil coupling arrangements.

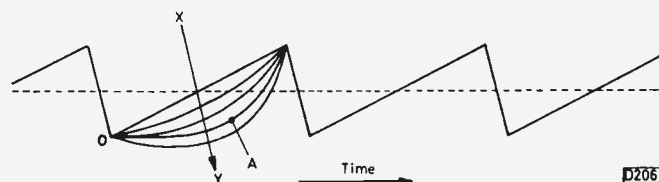


Fig. 5: The effect on the primary current waveform required to produce a sawtooth in the secondary winding as the inductance of the primary winding is reduced. X-Y shows the primary current waveform needed for a sawtooth secondary current as the primary inductance is reduced.

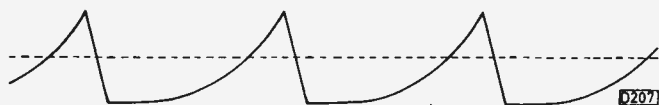


Fig. 6: The primary current waveform used in practice.

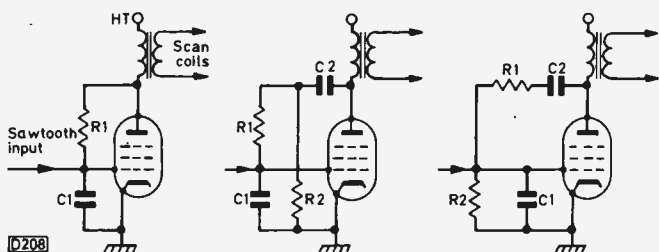


Fig. 7 (left): Feedback circuit to correct for the effects of coil and leakage inductance.

Fig. 8 (centre): Addition of i.f. boost (C2, R2).

Fig. 9 (right): Alternative arrangement to Fig. 8.

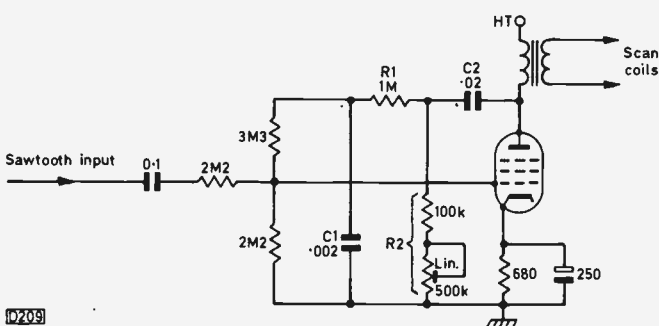


Fig. 10: Field output circuit used in the Pilot TV107.

we've seen with valve field timebases the output stage is driven by the RC charging circuit without intervening stages.

The only practical solution to this problem is to take the negative feedback voltage from the output pentode's anode, where there is no lack of signal voltage. Unfortunately the voltage waveform at the anode is not proportional to the current flowing in the scanning coils - due to the effect of the inductance of the coils and of the leakage inductance in the output transformer. There's a simple method of overcoming this difficulty however: as shown in

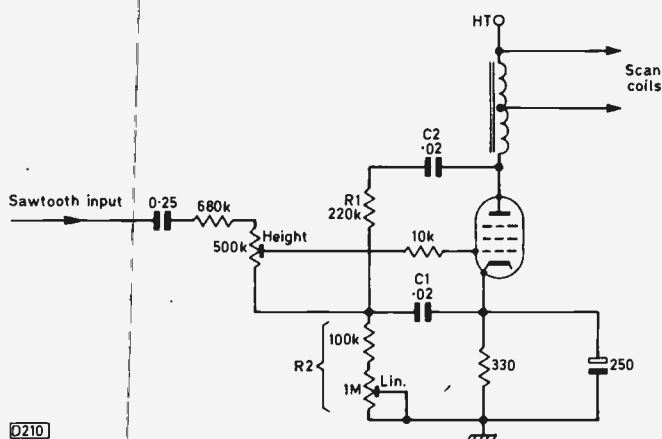


Fig. 11: Field output circuit used in the Cossor 948.

Fig. 7, the anode voltage can be applied to an RC circuit with the voltage developed across the capacitor used as the feedback. Provided a suitable time-constant value is used, the voltage across C1 is proportional to the current flowing in the scan coils.

The value of time-constant required is equal to that in the valve's anode circuit, i.e.  $(Lc + Ll)/(Rc + Rs)$  where  $Lc$  is the inductance of the coils,  $Ll$  the transformer's leakage inductance,  $Rc$  the resistance of the coils and  $Rs$  the resistance of the secondary winding. If for example  $Lc = 7\text{mH}$ ,  $Ll = 6\text{mH}$ ,  $Rc = 15\Omega$  and  $Rs = 2\Omega$ , the time-constant required is  $760\mu\text{s}$ . Somewhat greater values were used in practice and the resistor was made preset for linearity adjustment. For example in one chassis the capacitor was  $0.05\mu\text{F}$  and a  $50\text{k}\Omega$  preset was used, giving a maximum time-constant of  $2,500\mu\text{s}$ .

A second RC combination has to be included in the feedback path to provide the l.f. boost necessary to produce the current waveform shown in Fig. 6. C2, R2 in Fig. 8 give the required effect provided a suitable time-constant is used (R1, C1 compensate for the effects of coil and leakage inductance as before). An indication of the order of time-constant required is given by  $Lp/Rp$ , where  $Lp$  is the inductance and  $Rp$  the resistance of the primary winding. Typical practical values are  $20\text{H}$  and  $500\Omega$ , giving a time-constant of  $0.04\text{s}$ . The Alba Model T744 used  $0.03\mu\text{F}$  and  $2.2\text{M}\Omega$ , giving a time-constant of  $0.066\text{s}$ .

The negative feedback due to R1, C1, being concerned with correcting deficiencies due to coil and leakage inductance, is effective chiefly at the upper range of the field-frequency spectrum; that due to R2, C2 is concerned with the other end, being required to provide l.f. boost. It's possible therefore to combine the networks as shown in Fig. 9. At very low frequencies the reactance of C1 is so high that the network is effectively  $(R1 + R2)C2$  - equivalent to R2, C2 in Fig. 8. At very high frequencies R2 is large compared with the reactance of C1 and the network is effectively C1, R1, C2 which is similar to Fig. 7 if we neglect the effect of C2.

### Practical Circuits

Most of the field output stage designs of the immediate post-war period and the fifties were based on the principles described above. As illustrations, here are a few examples. The circuit shown in Fig. 10 was used in the Pilot Model TV107 which was introduced in September 1956 - it's the same as that shown in Fig. 8. The circuit shown in Fig. 11 was used in the Cossor Model 948 (August 1958) and is an example of the combined net-

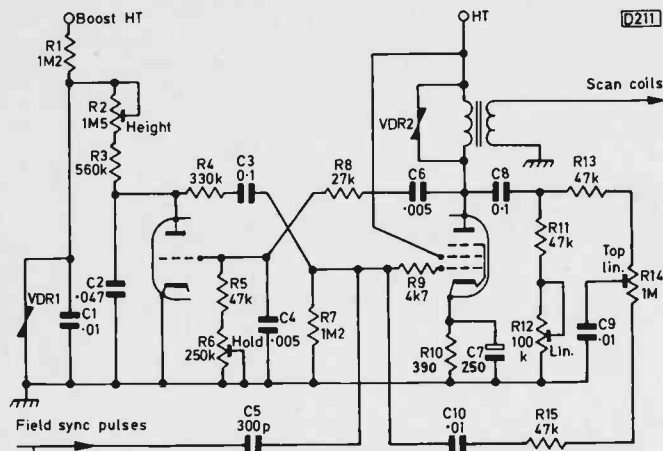


Fig. 12: Triode-pentode field timebase circuit used in many GEC chassis, with the pentode section acting as the output valve and as half the oscillator (multivibrator).

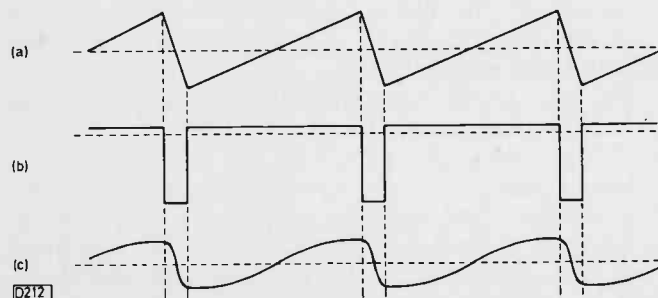


Fig. 13: Sawtooth waveform (a), its first derivative (b) and the waveform obtained (c) when the time-constant is comparable to the period of the input waveform.

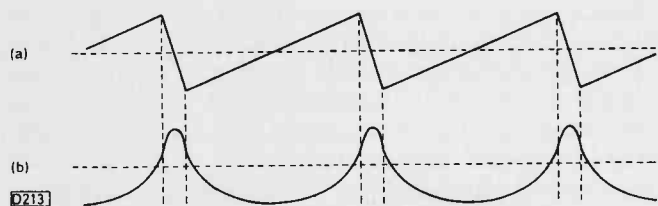


Fig. 14: Sawtooth waveform (a) and its integral (b).

work arrangement (Fig. 9).

Because valves age, die and have to be replaced, one of the aims in designing valved equipment has always been to keep the valve complement to a minimum. Any opportunity to economise in the number of valves used was eagerly seized (paradoxically the aim in modern equipment seems to be the opposite – to use as many active devices as possible: modern i.c.s use them by the thousand!). One way of reducing the valve count was to make one valve do the work of two. This became the practice with valve field timebase circuits where a triode-pentode would provide all that was required: the pentode section often acted as half of a multivibrator circuit in addition to being the output valve – Fig. 12 shows a typical circuit which was used in a number of GEC chassis up to and including the final hybrid monochrome ones.

The triode and pentode are cross-coupled to form an astable multivibrator: the grid circuit time-constants are markedly dissimilar so that the pentode conducts for a much longer period than the triode. During this time the triode is cut off and C2 charges via R2 and R3 to produce the basic sawtooth. Feeding the height control via the potential divider R1/VDR1 provides a stable charging supply: taking this supply from the boost rail helps to give

a linear sawtooth. We can ignore the multivibrator action during the forward stroke when the pentode acts as a straightforward output valve. The feedback network follows the lines previously described, with C8, R11, R12 providing l.f. boost and R13, R14, C9 contributing h.f. correction. Negative-going field sync pulses cut off the pentode just prior to the natural oscillatory cycle to initiate the flyback, which is produced by primary current reversal in the output transformer. The VDR across the primary winding reduces the flyback pulse voltage.

## RC Networks

Before going on to transistor field timebases in Part 2 it's worth mentioning another way of looking at the waveform correction brought about by R1, C1 and R2, C2 in Fig. 8. Instead of regarding them as h.f. and l.f. correction networks or as correctors for leakage inductance and shunt inductance they can be treated simply as waveform shapers used to get the required signal shape. This is worth considering in more detail.

Any recurrent signal applied to a series RC combination yields two outputs – one across the resistor and the other across the capacitor. When the output is taken from the resistor the circuit is often referred to as a differentiating network because, if the time-constant is small compared to the period of the input signal, the output waveform approximates to the differential coefficient (or first derivative) of the input. Thus if the input is a sawtooth as shown in Fig. 13(a) the output is the pulse waveform shown in Fig. 13(b), the relationship between them being that the ordinate at any instant in waveform (b) measures the gradient at the corresponding instant in waveform (a). If the time-constant is not short but is comparable with the period of the input the output waveform is as shown in Fig. 13(c). With a long time-constant the input and output waveforms are the same, this being the condition required for an interstage RC coupling network in an analogue amplifier.

If the output from the series RC combination is taken from the capacitor the arrangement is known as an integrating network because, if the time-constant is long compared with the period of the input signal, the output waveform approximates to the time integral of the input. Thus if the input is a sawtooth, as in Fig. 14(a), the output has the parabolic form shown at (b), the relationship between them being that the ordinate at any instant in waveform (a) measures the gradient at the corresponding instant in curve (b). In this case when the time-constant is decreased the output waveform changes until, with a small time-constant compared to the period of the input waveform, the input and output waveforms resemble each other.

It's possible therefore with suitable choice of output point and time-constant to obtain from a series RC combination any shape of signal between the full differential and the full integral of the input. Sometimes the output from the RC circuit is itself the wanted waveform: this is the case when the network is used as an integrator or differentiator. Alternatively the network can be used to give a correcting signal which, after attenuation if necessary in a potentiometer, can be added to or subtracted from the waveform to be shaped. Thus the use of RC networks is a most versatile method of waveform shaping and is one that's extensively used in field timebases. With wide-angle tubes the values are adjusted to achieve the scan-correction required.



# TV Fault Finding

Reports from Les Grogan  
Larry Ingram and John Coombes

## Decca 130 Series Chassis

An unusual fault came our way on a Decca/Tatung set fitted with the 130 chassis, remote control and teletext: the set would intermittently go into standby when changing channels, either manually or via remote control. Changing the microcomputer i.c. on the frequency synthesis panel made no difference and the d.c. supplies from the regulators on this panel checked o.k. with a digital voltmeter. A scope check on the output from the 5V regulator (IE01) provided a clue: there was a nasty hum present on this rail, which feeds the microcomputer i.c. The input to this regulator is obtained from the centre tap on the standby transformer winding that feeds the bridge rectifier. The winding has two 7V a.c. sections and one of these was open-circuit. A new standby transformer cleared the trouble. **L.G.**

## Hitachi CTP1471/1473

The picture collapsed, then went off. Several things were found to be faulty, the root cause apparently being the chopper i.c. (IC901). The field output i.c. – two diodes and the output pair of transistors encapsulated in a block – and two associated resistors R772 and R682 were found to be faulty (the resistors were charred and one of the output transistors was leaky). Unfortunately the i.c. is available only from the makers. Further examination revealed that the 2SD898B line output transistor was leaky and when we checked the h.t. with a dummy load we found it to be 175V instead of 111V. Replacing IC901 and the associated components didn't effect a cure so the makers were contacted. It appears that early production runs of the chopper i.c.s sometimes went haywire, and that this can be the case with stock items. The "modification" kit from Hitachi consists of IC901 (STR6020), a 2SD898B, Q681 (2SC1213A), fusible resistor R772 and an STA441C field output i.c. if this was found to be faulty. **L.I.**

## Thorn 8500 Chassis

At odd times over many months the red button cutout would operate. Resetting it would restore the vision and sound for days or weeks on end with no other reported symptoms. After three days on soak test there was a slight increase in picture size and the cutout operated. Eventually R724 (120k $\Omega$ ) in the set h.t./e.h.t. control network was found to be varying in value. **L.I.**

## Hitachi CBP260 (NP9A Chassis)

The complaint was erratic starting from cold using the on/off switch while it became increasingly difficult to switch on and off by means of the remote or mains switch as the set warmed up. The switch operated correctly and it seemed that the cause of the trouble was something to do with the chopper circuit. This is on its own board in the middle of the main board and is not very accessible. The chopper transistor's collector fixing screw was found to be loose but tightening this and replacing the transistors and small electrolytics in the control circuit didn't improve matters.

At this point a similar set arrived in the workshop. In this case the chopper circuit stopped working intermit-

tently when hot. There was no reason to suspect dry-joints – everything looked quite sound – but each and every joint on the PCB was resoldered with great care. This cured the problem. Back to the first set. Maybe it was the same trouble? Again nothing looked at all suspect, but the same treatment worked. There was still the problem of intermittent starting. The plug and leads were checked one more time: solder up, tighten again and the fault had been cured. **L.I.**

## Grundig CUC720 Chassis

There was no field scan and R2771 (6.8 $\Omega$ ) in the supply to the output section of the TDA2653 field timebase i.c. on the deflection module had burnt out. The i.c. was replaced and we found that the flyback boost capacitor C2768 (100 $\mu$ F) between pins 7 and 11 had a nasty leak. This has been the trouble on several occasions: C2768 seems to be the start of the problem and should be changed if there is any suspicion. In passing, most of the field timebase modules of this and similar Grundig types seem to have daylight between the i.c. heatsinks as fitted. It would seem to be good practice to correct this. **L.I.**

## Decca 70/90/110 Series Chassis

Here's a summary of some of the faults we've had on these sets.

**Set tripping:** Check, in the following order, the overvoltage zener diode D602 (ZPD22) for leakage, the current sensing resistor R636 for being open-circuit, and C633 (680pF) in the h.t. rectifier circuit for being short-circuit or leaky. Other possible causes are the TDA2581 chopper control i.c. (IC601) – check by substitution – and a break in the c.r.t.'s Aquadag earth return.

**Intermittent tripping:** Check C617 (6.8nF) in the set-h.t. control circuit for leakage.

**Intermittent chopper transistor failure:** Check whether R637 (2.2k $\Omega$ , 7W) in the snubber circuit is open-circuit and for dry-joints around Tr604 (BSR59) in the driver circuit.

**Power supply not working:** Check whether the bridge rectifier's reservoir capacitor C624 (100 $\mu$ F) is open-circuit.

**White screen/curved black area on the screen:** Check the TDA2571 line oscillator/sync i.c.

**Vertical red stripes on the screen:** Check the R–Y coupling capacitor C208 (22nF).

**Poor field lock:** Check whether C308 (10 $\mu$ F) in the field sync pulse integrator stage is open-circuit.

**Lack of brightness:** Check R910 (180k $\Omega$ , 1W) in the first anode supply circuit for being open-circuit, also if necessary the control (VR908, 2.2M $\Omega$ ) for the same condition. (70/90 series chassis).

**Bright red/green/blue raster with flyback lines:** Check R913 (220k $\Omega$ ) on the tube base panel for being open-circuit. (110 series chassis.) **J.C.**

**Editorial note:** An error occurred in Fig. 1, page 597 of the September 1983 issue. The output across C637 should have been shown as 150V, not 195V, for the 90 series chassis. The diagram showed the switch-mode power supply circuit used in these sets.

# ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

16181	1.04	ZSC1124	1.26	2SD348	16.13	AN5435	3.08	BC186	0.27	B0222	0.49	BF195	0.14	BSR59	1.29	BZ79 RANGE	0.10
16182	1.04	2SC1151A	4.72	2SD350	5.20	AN5610	7.43	BC187	0.20	B0225	0.49	BF196	0.17	BSS38	0.59	BZ788 RANGE	0.10
16334	0.51	2SC1152	4.68	2SD350A	2.29	AN5612	3.51	BC204	0.16	B0228	0.63	BF197	0.16	BSTC0146	4.98	C106D	0.46
16335	0.80	2SC1162	1.05	2SD353	7.50	AN5613	3.41	BC207	0.14	B0229	1.05	BF198	0.17	BSTC0246	2.48	C1129	0.58
16446	0.98	2SC1172	2.22	2SD389	2.41	AN6320N	4.28	BC212	0.11	B0231	0.50	BF199	0.17	BSTC0246	6.99	CA1310E	2.70
16600	1.38	2SC1172Y	2.20	2SD401	3.55	AN6326	3.98	BC212B	0.26	B0232	0.50	BF200	0.17	BSTC0233	6.12	CA3044	3.50
16799	2.88	2SC1195	3.26	2SD451	2.42	AN6342	1.61	BC212L	0.10	B0234	0.42	BF216	0.36	BSTC1233	4.34	CA3046	2.06
16801	0.54	2SC1213	0.89	2SD568A	1.99	AN6344	5.07	BC212LB	0.26	B0237	0.47	BF218	0.36	BSTC3146	0.79	CA3060	1.65
16802	1.14	2SC1226	1.46	2SD600	3.25	AN6363	16.80	BC213	0.10	B0238	0.45	BF222	0.56	BSTC00143	3.07	CA3065	1.29
16803	5.30	2SC1306	1.98	2SD621	12.67	AN6551	0.68	BC213L	0.10	B0239	0.45	BF224	0.47	BSTC0643	3.37	CA3089	0.83
16905	0.86	2SC1307	1.98	2SD636	0.40	AN6552	0.68	BC213LB	0.15	B0240	0.37	BF237	0.16	BSV57B	3.49	CA3089E	1.43
17074	9.30	2SC1316	4.10	2SD657	2.80	AN7115	2.52	BC214	0.10	B0241	0.39	BF240	0.17	BSW68	0.60	CA3090	1.38
17127	3.51	2SC1364	0.49	2SD679	3.35	AN7145	2.80	BC214L	0.14	B0242	0.50	BF241	0.17	BSX19	0.34	CA3094	2.20
1N4001	0.06	2SC1383	1.20	2SD731	2.11	AN7146	9.90	BC214LB	0.26	B0243	0.50	BF244	0.47	BSX20	0.34	CA3131EM	3.12
1N4002	0.06	2SC1398	0.84	2SD787E	1.80	AN7150	2.45	BC225	0.40	B0243A	0.37	BF245A	0.37	BSX21	0.87	CAH76023N	6.60
1N4003	0.06	2SC1410	2.39	2SD811	5.54	AN7151	2.26	BC237	0.10	B0244	0.51	BF255	0.20	BSY52	0.50	CBF16848N-07	1.56
1N4004	0.04	2SC1413	3.55	2SD823	1.96	AN7156	2.40	BC238	0.10	B0244A	0.85	BF256	0.28	BSY79	0.51	CD4001	0.38
1N4005	0.08	2SC1505	1.00	2SD856	6.61	AN7158	6.75	BC238A	0.13	B0245C	0.99	BF256LC	0.42	BT100A	1.61	CD4002	0.27
1N4006	0.08	2SC1578	8.74	2SD869	7.17	AN7218	1.64	BC239	0.12	B0246C	0.86	BF257	0.34	BT106	1.18	CD4008	1.06
1N4007	0.07	2SC1617	3.89	2SD898B	7.45	AP58076	4.68	BC239B	0.12	B0253	1.05	BF258	0.33	BT108	1.45	CD4011	0.29
1N4148	0.04	2SC1670	3.13	40408	0.50	ASS560S	1.58	BC251A	0.25	B0278A	0.80	BF259	0.34	BT109	1.46	CD4012	0.24
1N4448	0.05	2SC1678	1.98	40594	1.53	AU113	2.97	BC252	0.10	B0317	2.60	BF262	0.57	BT112	2.48	CD4013	0.47
1N5401	0.14	2SC1810	1.70	40595	1.53	AY105K	2.08	BC258	0.25	B0318	2.59	BF263	0.57	BT113	2.68	CD4016	0.46
1N5402	0.15	2SC1815	0.66	40636	1.43	AY106	1.09	BC261A	0.22	B0375	0.42	BF264	0.37	BT116	1.20	CD4017	0.82
1N5403	0.16	2SC1829	2.22	40671	1.53	BA130	0.14	BC262	0.22	B0377	0.26	BF271	0.34	BT119	1.76	CD4020	1.23
1N5404	0.15	2SC1855	1.88	40672	1.53	BA1310	1.98	BC287	0.50	B0379	0.76	BF273	0.20	BT120	2.17	CD4021	0.39
1N5408	0.35	2SC1875	4.77	60857	1.21	BA1320	1.38	BC294	0.50	B0380	0.76	BF274	0.20	BT121	2.48	CD4023	0.28
1N914	0.04	2SC1891	3.69	74LS30	0.32	BA1330	2.75	BC301	0.45	B0410	0.49	BF324	0.23	BT122	2.98	CD4025	0.64
1S44	0.09	2SC1893	3.02	7805 TO-220	0.63	BA145	0.19	BC302	0.53	B0412	6.27	BF336	0.32	BT123	1.48	CD4028	0.84
1S5012A	0.81	2SC1929	2.25	7805 TO-3	1.16	BA148 DIOD	0.33	BC303	0.10	B0418	0.87	BF337	0.36	BT125	2.48	CD4047	1.06
1S921	0.10	2SC1942	5.70	7806	0.73	BA154	0.40	BC307	0.18	B0433	0.41	BF338	0.40	BT126	2.68	CD4049	0.46
2N1302	0.27	2SC1945	4.53	7808	2.39	BA156	0.05	BC307A	0.14	B0434	0.43	BF355	0.49	BT128	2.48	CD4050	0.55
2N1303	0.38	2SC1953	1.93	7812 TO-3	0.64	BA157	0.22	BC308	0.18	B0435	0.49	BF362	0.60	BT128P	3.07	CD4052	0.75
2N2218	0.42	2SC1957	0.95	7812 TO-220	1.16	BA159	0.12	BC308A	0.11	B0436	0.60	BF363	0.60	TBA970	3.06	CD4053	0.80
2N2219A	0.40	2SC1959	0.31	7815	0.64	BA182	0.19	BC309	0.17	B0437	0.41	BF371	0.50	BT151-800R	1.15	CD4069	0.29
2N2222	0.38	2SC1962	1.93	7818	0.70	BA222	1.66	BC317A	0.13	B0438	0.49	BF391	0.49	BT151 500R	1.38	CD4081	0.35
2N2646	0.80	2SC1969	2.92	7824	0.64	BA284/2	0.17	BC327	0.15	B0441	1.42	BF393	1.25	BT16018	2.48	CD4093	0.72
2N2904	0.36	2SC1985	1.75	AC107	0.73	BA301	0.87	BC328	0.11	B0442	0.66	BF417	0.84	BT16218	2.42	CD4511	1.10
2N2905	0.43	2SC1983 TR	7.00	AC117	0.43	BA302	1.24	BC337	0.08	B0507	0.60	BF418	1.87	BT18024	4.43	CP5521	17.83
2N2906	0.38	2SC2009	0.34	AC123K	0.43	BA311	1.32	BC338	0.12	B0509	1.42	BF422	0.29	BT18124	4.89	CV12E	3.07
2N3053	0.27	2SC2029	2.33	AC128	0.34	BA312	0.97	BC360	0.34	B0510	0.75	BF423	0.29	BT18214	5.99	CG034	11.83
2N3054	0.99	2SC2027	1.42	AC138	0.09	BA313	0.76	BC368	0.24	B0518	1.50	BF435	0.54	BT18224	2.97	CG050D	3.14
2N3055	0.61	2SC2028	2.11	AC141	0.29	BA317	0.04	BC440	1.09	B0519	1.09	BF450	0.35	BU105	1.50	CH104	9.64
2N3055H	0.85	2SC2057	1.18	AC142K	0.43	BA318	0.09	BC441	0.44	B0529	1.32	BF451	0.29	BU106	2.48	CH108	8.16
2N3442	1.16	2SC2073	1.54	AC151	0.28	BA328	4.77	BC454	0.36	B0530	1.10	BF457	0.41	BU108	1.50	CH109	7.86
2N3702	0.14	2SC2078	2.39	AC153	0.34	BA333	1.37	BC455	0.36	B0533	0.67	BF458	0.39	BU109	2.25	CH121	11.83
2N3703	0.14	2SC2091	1.30	AC176	0.30	BA401	0.64	BC460	0.42	B0534	0.53	BF459	0.52	BU110	5.69	CH130	5.55
2N3704	0.14	2SC2122A	5.12	AC179	0.28	BA511	2.18	BC461	0.47	B0535	0.77	BF460	0.39	BU111Y	4.16	CH131	11.83
2N3705	0.14	2SC2141	1.86	AC183	0.72	BA521	2.02	BC462	0.30	B0536	0.61	BF469	0.51	BU124	1.38	CH134	11.04
2N3706	0.14	2SC2166	1.98	AC187	0.39	BA524	8.94	BC463	0.64	B0537	0.74	BF470	0.55	BU125	0.90	CH136	11.49
2N3707	0.16	2SC2216	0.69	AC187K	0.43	BA526	7.98	BC464	0.64	B0538	0.67	BF471	0.31	BU134S	4.57	CH137	11.83
2N3711	0.11	2SC2233	2.20	AC188	0.37	BA532	2.67	BC465	0.62	B0544B	0.83	BF472	0.33	BU204	1.58	CH139	11.83
2N3717	2.04	2SC2271	4.01	AC188-01	0.44	BA536	3.44	BC477	0.34	B0580	1.17	BF479	0.61	BU205	1.08	CH157	4.84
2N3772	1.79	2SC2278	1.14	AC188K	0.43	BA6304A	2.92	BC478	0.32	B0580	1.17	BF480	0.60	BU206	1.27	CH158	4.10
2N3773	2.29	2SC2314	0.87	AC193K	0.65	BA843	3.96	BC479	0.41	B0588	1.25	BF491	0.49	BU207	1.65	CH170	7.62
2N3819	0.40	2SC2335	10.41	AC194K	0.65	BAV18	0.21	BC532	0.28	B0677	0.53	BF495	0.64	BU208	1.12	CH177	6.75
2N3823	1.17	2SC2526	1.87	AD140	1.06	BAV19	0.11	BC546	0.17	B0679	0.57	BF506	0.43	BU208/02	0.57	CH506	9.33
2N3904	0.62	2SC2551	1.26	AD145	1.60	BAV20	0.11	BC547	0.10	B0680	0.76	BF509	0.40	BU208A	1.12	CH507	7.62
2N3908	0.62	2SC2570	2.39	AD149	0.90	BAV21	0.34	BC548	0.10	B0681	1.48	BF523	0.21	BU208B	1.43	CH575	12.95
2N4101	1.33	2SC2570A	1.05	AD161	0.56	BAX12	0.11	BC549	0.10	B0685	2.30	BF594	0.27	BU209	1.93	CH578	7.62
2N4240	3.30	2SC2578	6.75	AD162	0.45	BAX13	0.11	BC550	0.40	B0686	2.47	BF595	0.27	BU225	2.45	D1693	2.59
2N4444	0.90	2SC264A	4.82	AD262	1.05	BAX16	0.11	BC556	0.16	B0687	3.60	BF596	0.28	BU312	2.38	DEC1	2.20
2N4914	0.72	2SC2671	1.99	AF114	2.47	BB119	0.17	BC557	0.10	B0688	1.85	BF597	0.17	BU326	2.00	DEC2	2.20
2N5064	0.71	2SC2728	0.95	AF115	1.24	BC107	0.13	BC558	0.10	B0689	3.49	BF617	1.05	BU326A	2.20	E1222	0.40
2N5293	0.50	2SC2785	0.75	AF117	0.75	BC107B	0.11	BC559	0.10	B0700	3.70	BF618	1.05	BU326S	2.20	E5024	0.28
2N5294	0.50	2SC372	1.40	AF118	1.20	BC108	0.15	BC560C	0.16	B0702	3.70	BF684	0.27	BU406	1.49	E5836	0.25
2N5296	0.49	2SC373	1.16	AF127	0.50	BC108B	0.15	BC635	0.34	B0707	1.06	BF757	0.59	BU407	0.82	E5529	0.25
2N5297	0.50	2SC383	1.33	AF139	0.53	BC109	0.12	BC636	0.20	B0709	1.12	BF758	0.65	BU407D	1.29	E8021	1.29
2N5298	0.61	2SC388	0.50	AF178	1.46	BC109B	0.15	BC637	0.24	B0710	0.80	BF759	0.47	BU412	5.29	E9003	0.46
2N5490	1.49	2SC394V	0.81	AF179	0.55	BC113	0.14	BC638	0.20	B0807	0.34	BF760	0.35	BU426	1.90	E9005	0.50
2N5496	0.59	2SC41	2.19	AF180	0.55	BC116A	0.25	BC639	0.20	B0809	0.7						

# ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

HA1338	7.50	M1130	5.36	NE646N	2.98	SAS560	1.85	SN76620	2.59	TA7109	3.71	TC4053BP	4.34	TD2611AQ	2.96	TIP30C	0.40
HA1339	2.33	M191	6.32	NE650N	4.34	SAS560S	1.65	SN76622	1.65	TA7120P	0.64	TC150	1.79	TD2612Q	4.68	TIP31A	0.34
HA1342	2.23	M193	18.55	NE654BN	4.18	SAS560T	5.42	SN76623	0.69	TA7122B/P	0.92	TC160B	1.79	TD2620	1.96	TIP31B	0.38
HA1350	3.27	M51102L	6.26	NP1106	5.61	SAS570	1.78	SN76630	2.25	TA7124P	1.24	TC270Q	1.71	TD2630	1.96	TIP31C	0.50
HA1365	4.02	M5115P	5.24	OA200	0.11	SAS570S	2.61	SN76640	4.24	TA7130P	1.27	TC270TS	2.15	TD2631	2.73	TIP32B	0.69
HA1366WVR	1.86	M51231P	3.04	OA202	0.11	SAS570T	5.42	SN76651	1.49	TA7136AP	1.27	TC270SQ	1.65	TD2640	2.59	TIP32C	0.40
HA1367	4.32	M5124P	4.82	OA47	0.14	SAS580	2.85	SN76660N	2.48	TA7137P	0.98	TC290A	2.39	TD2643	1.12	TIP33C	0.80
HA1368	1.90	M5134-9341	4.13	OA90	0.08	SAS5800	2.89	SN76665N	1.49	TA7141AP	3.87	TC4A20A	1.16	TD2651	2.95	TIP34	1.18
HA1368R	1.90	M51394P	11.97	OA91	0.09	SAS590	2.85	SN76666N	1.41	TA7146P	4.23	TC4A40	1.62	TD2652	6.95	TIP41A	0.49
HA1370	3.71	M5142P	5.49	OA95	0.09	SAS5900	2.56	SN76705N	1.34	TA7148P	1.67	TC4A500A	2.15	TD2653	6.18	TIP41B	0.31
HA1374A	8.80	M5143P	7.33	OC28	2.52	SAS660	2.97	SN76707N	4.28	TA7149P	3.26	TC4A50	2.16	TD2654	4.73	TIP41C	0.45
HA1377	3.96	M5144P	3.77	OC29	2.15	SAS6600	1.33	SN76709	5.12	TA7161P	6.23	TC4A60	10.26	TD2655B	5.44	TIP42A	0.49
HA1389	2.39	M51513L	2.55	OC35	1.06	SAS660S	1.33	SN76709N	5.45	TA7162P	2.89	TC4A650	2.04	TD2660	5.47	TIP42B	0.79
HA1389R	2.05	M51515BL	3.23	OC36	1.28	SAS6610	1.33	SN76730	4.66	TA7169	9.54	TC4A660B	3.30	TD2661	2.47	TIP42C	0.82
HA1392	3.90	M51516L	3.95	OC44	0.35	SAS670	3.96	SN76810N	0.60	TA7171P	2.79	TC4A70	3.81	TD2670	2.48	TIP47	0.65
HA1394	3.95	M51517L	3.71	OC45	0.18	SAS6700	1.33	SN76920N	2.90	TA7172P	1.41	TC4A70	1.41	TD2670A	1.94	TIP48	0.48
HA1397	3.76	M5152L	2.88	OC75	0.44	SAS670S	1.33	SN94041	5.54	TA7176P	2.48	TC4A750	2.25	TD2680	3.20	TIP49	3.61
HA1398	3.98	M51522	5.39	ON188	1.87	SAS6710	1.33	SN94042	4.35	TA7193AP	6.67	TC4A800	5.95	TD2690A	2.65	TIP59A	1.65
HA1406	2.07	M5191P	4.94	ON236	1.06	SAS6800	2.53	SP8385	0.55	TA7193P	7.26	TC4A800Q	5.95	TD2780AQ	5.14	TIS43	3.24
HA1452	1.63	M5192	2.20	OT112	1.02	SAS6810	1.43	ST4441C	2.75	TA7201P	2.71	TC4A830S	2.71	TD2790Q	6.52	TIS90	0.21
HA17723	5.94	M5194AP	5.74	OT121	1.38	SBA550B	2.15	STK0029	5.54	TA7202P	2.47	TC900	2.04	TD2791	2.50	TIS91	0.29
HBFA030AF	2.48	M53274P	1.02	PD144	2.24	SBA750	1.61	STK0039	5.35	TA7203P	2.18	TC9A10	1.65	TD2795	2.75	TMS1000NL	11.86
HD38750A53	8.71	M53274P	1.33	PT2014	3.04	SC9488P	2.09	STK0050	7.67	TA7204P	2.93	TC9A90E	2.93	TD2800	2.95	TMS3748HS	16.13
HD4480	17.16	MA06	1.07	PT5006	2.48	SC9503	1.65	STK0059	7.13	TA7205	1.38	TC9E30	3.89	TD2800A	11.49	TMS4116	2.06
HD44801A05	17.49	MA8001	0.82	PT6042	1.79	SC9504P	1.95	STK0080	9.16	TA7206P	6.25	TC9E57	1.86	TD2810	2.68	TV106	1.76
HEF4001P	0.67	MB3705	1.79	R1038	2.19	SC9511P	2.09	STK011	3.96	TA7207P	3.34	TC8E2	1.08	TD28300B	6.47	UY601B	1.14
HEF4001BP	0.67	MB3712	1.85	R1039	2.19	SCR957	1.33	STK013	9.25	TA7208P	2.15	TC8E3	1.08	TD28300	4.25	UY60G	2.97
HEF4011	0.29	MB3713	1.69	R2008B	1.33	SG264A	5.06	STK014	8.84	TA7210P	3.58	TC8E4	1.08	TD28301	12.09	U143M	3.08
HEF4528	0.00	MB3730	3.25	R2009	1.98	SG613	8.75	STK015	7.75	TA7214P	3.63	TCEP100Q	10.25	TD28306	9.98	U37003	0.49
HM6231	9.81	MC13002	6.22	R2001B	1.33	SG629	8.27	STK016	6.91	TA7215P	2.58	TCEP100	9.61	TD28310	6.55	UA723CA	5.53
HM6232	8.89	MC1303P	2.16	R2029	1.33	SG6533	10.31	STK022	5.25	TA7217AP	1.37	TD190	0.95	TD28320	9.71	UA758PC	5.29
HM9102	3.22	MC1307P	1.92	R2030	1.33	SI-1125HD	13.86	STK025	8.27	TA7222	1.95	TD3F700H	6.60	TD28321	13.39	UA783PC	3.38
HM9104	3.24	MC1310P	1.30	R2257	2.38	SI1125H	7.50	STK040	8.70	TA7227P	2.81	TD3F800H	4.86	TD28322	2.98	UA783PC	2.25
HM9105	3.24	MC1327P	1.33	R2265	1.49	SKE2F 1/04	1.39	STK043	10.48	TA7229P	4.45	TD3F800R	3.66	TD28360	5.00	UA8180	2.36
HT4207	17.16	MC1330P	1.69	R2305	1.18	SKE2G 2/04	0.95	STK054	7.13	TA7233P	3.25	TD3F900H	4.16	TD28361	6.50	ULN2165	1.49
ITT2003	0.22	MC1349P	0.81	R2306	1.36	SKE2G 3/04	1.05	STK070	22.31	TA7240AP	7.83	TD41003A	1.79	TD28361A	7.20	ULN2204	2.36
K174YP	3.46	MC1350P	1.21	R2322	0.59	SKE4F 1/02	1.39	STK077	7.67	TA7245P	2.70	TD41005A	2.22	TD28371A	6.54	ULN2216F	2.15
KA2101	2.92	MC1351P	1.33	R2323	0.76	SKE4F 1/06	0.73	STK078	8.52	TA7314	5.94	TD41006A	1.69	TD28371Q	2.03	UPC1009C	6.32
KC581C	6.32	MC1352P	1.12	R2348	2.01	SKE4F 2/06	0.85	STK082	11.86	TA7325P	0.98	TD41010	1.33	TD28376	7.83	UPC1001H	2.75
KC582C	3.97	MC1357P	2.15	R2354A	2.01	SKE4F 2/08	0.86	STK086	10.89	TA7609	3.17	TD41011	2.40	TD28390	6.79	UPC1026C	1.24
KC583C	5.54	MC1358P	1.30	R2354B	2.01	SKE4F 2/10	1.24	STK2101	6.32	TA7676P	2.81	TD41028	2.45	TD28390B	1.54	UPC1028H	2.00
L129V	0.25	MC14001	2.40	R2441	1.36	SKE4G 2/02	0.96	STK2110	7.30	TAA300	2.97	TD41029	4.89	TD4A050A	3.47	UPC1029H	2.77
L200CV	1.69	MC14013	0.41	R2443	0.88	SKE5F 3/10	1.60	STK2230	7.73	TAA310A	1.16	TD41035	2.55	TD4A180P	1.92	UPC105A	2.90
LA1111AP	0.88	MC14016CP	0.84	R2461	1.50	SL1310	3.14	STK415	7.70	TAA320A	1.87	TD41034B	1.20	TD4A260	1.54	UPC1032H	0.47
LA1201	1.02	MC14011	0.26	R2477	1.02	SL1327E	1.33	STK433	4.95	TAA350A	0.80	TD41037	2.95	TD4A280	7.20	UPC1030H	0.27
LA1210	1.56	MC14025	0.60	R2501	1.28	SL1430	1.39	STK435	5.54	TAA435	1.82	TD41037D	3.25	TD4A290	4.47	UPC1031H	8.58
LA1230	2.87	MC14049UBC	0.58	R2540	1.98	SL1430T	2.31	STK436	7.21	TAA550	0.37	TD41041	2.16	TD4A40	4.90	UPC1031H2	6.00
LA1320	2.87	MC1438R	1.05	R2540X	3.30	SL1432	3.25	STK437	7.80	TAA570	1.70	TD41044	2.62	TD4A400	2.27	UPC154H	1.93
LA1352	1.54	MC14493P	2.82	R2615	0.67	SL1414	1.14	STK439	8.31	TAA611B12	1.34	TD41047	4.10	TD4A420	3.95	UPC156H	2.96
LA1357N	6.49	MC14556BCP	3.47	RC4195NB	2.16	SL432A	3.44	STK441	11.28	TAA621AX1	2.48	TD41054M	1.21	TD4A422	8.32	UPC1185H	1.84
LA1363	6.21	MC1712	3.88	RCA16083	5.30	SL437	7.43	STK443	10.29	TAA640	4.24	TD41059B	0.80	TD4A430	4.78	UPC1182H	2.92
LA1364	3.02	MC7724CP	3.49	RCA16029	2.01	SL439	2.48	STK459	9.40	TAA661B	1.00	TD41060	2.59	TD4A431	2.27	UPC1186H	1.05
LA1365J	4.44	MC7818C	2.18	RCA16334	1.02	SL480	3.14	STK460	10.75	TAA700	2.59	TD41062	3.06	TD4A432	2.27	UPC1181H	1.25
LA1378	6.52	MC7824CP	4.68	RCA16335	1.36	SL490	2.37	STK461	9.68	TAA840	1.60	TD41104	6.55	TD4A400	2.87	UPC1213C	2.97
LA1385	1.87	MC78M12	0.83	RCA16600	1.38	SL901B	8.32	STK463	11.53	TAA930	4.87	TD41151	1.17	TD4A600	2.84	UPC1217C	0.44
LA1387	7.60	MC78M24	0.94	RCA16799	2.38	SL917B	11.96	STK465	10.31	TAA970	2.83	TD41170	2.37	TD4A610	3.11	UPC1212C	1.72
LA3155	1.25	MCR100	0.38	RCA16801	0.95	SL918A	9.07	STK466	11.77	TAD100	2.52	TD41170S	3.25	TD4A620	4.46	UPC1351C	1.81
LA3300	1.54	MCR101	0.67	RCA16802	1.08	SN16861N-07	2.72	STR441	10.73	TAG232-600	1.03	TD41180	3.25	TD4A500	2.73	UPC1353	7.05
LA3301	1.41	MCR1065	1.57	RCA17028	2.48	SN16880N	3.63	STR453	8.16	TAG626-600	0.76	TD41190	2.11	TD45700	2.31	UPC1350C	1.87
LA3350	1.43	MCR2207	2.28	RCA17074	6.60	SN16965	8.95	STR6020	8.31	TBA120	1.05	TD41190Z	2.48	TD4A940	2.92	UPC1355C	2.13
LA3361	1.23	ME0402	0.17	RCA17376	1.58	SN16966N	10.25	TB007V	0.95	TBA120A	1.05	TD41200A	1.43	TD4A940S	5.15	UPC1362	8.75
LA4030P	4.20	ME0404	0.26	RCA60857	4.95	SN29715N	6.04	TB007	0.62	TBA120AS	1.24	TD41220	1.95	TD4A950	2.92	UPC1365	7.10
LA4031P	3.20	ME04042	0.47	RGPI0	0.50	SN29716N	3.66	TB016	0.40	TBA120S	1.05	TD41230	3.23	TD4A9513	5.44	UPC1366	7.14
LA4032P	1.92	ME0411	0.28	RT402	1.58	SN29717N	7.19	TB017	0.72	TBA120SB	1.05	TD41235	3.88	TE527	1.38	UPC1360C	4.56
LA4050P	1.57	ME0412	0.24	RT905A	2.38	SN29722	11.95	TB018V	0.72	TBA120T	0.95	TD41270	3.76	TE538	0.40	UPC1458	8.61
LA4051P	1.79	ME4102	0.50	S0280	2.14	SN29723AN	7.65	TB021	0.40	TBA120U	2.03	TD41327A	1.82	TE626	1.49	UPC2022	2.48
LA4100	1.25	ME545B	10.02	S0281	2.15	SN29744N	2.29	TB022V	3.92	TBA1440	2.05	TD41327B	1.80	TEA1002	3.47	UPC30C	1.51
LA4101	1.30	ME6002	0.26	S1299	4.74	SN29764AN	1.38	TB026	0.98	TBA1440G	1.82	TD41330	1.76	TEA1009	1.86	UPC32C	4.94
LA4102	2.81																

# The Tantrums of Tiny Tim

Les Lawry-Johns

Tiny Tim had seen the set before but couldn't remember much about it.

"It keeps flicking in from the sides, sort of bowing in if you know what I mean, and we've still got those bars that travel up the screen" said Mr. Crankcase.

"Sometimes they travel down" said Mrs. Crankcase, "but we don't mind that – we're used to the bars."

"Don't worry" said Tiny Tim, "I'll sort it out tout suite."

Clearly impressed by Tim's confidence, the Crankcases departed and left him to it.

## The CVC5

The 26in. CVC5 proved to be a nightmare. Bowing in at the sides on a set fitted with a 90° tube and no EW diode modulator circuit . . . Tim plugged the set into the mains supply and pressed the on/off switch. Being a hybrid chassis, the valves lit up and Tim waited. And waited. There was no cover over the line output stage (shades of Ike Hodge) so Tim held his little neon near the PL509. It didn't light up and he noticed that the valve was getting red hot. So he checked the h.t. supply to the PCF802 line oscillator valve. This was present and the PL509 cooled down. Suspecting the polywhat'sname capacitors in the line oscillator stage Tim changed the PCF802 – this was easier than changing the capacitors. There was no further trouble with the line drive and the e.h.t. rustled up. The picture appeared but it kept flicking sideways and doing all sorts of funny things like bowing in quickly then bowing out again.

Tim's diagnosis was immediate. "Up with this I'll put no more" he said, "it's poor earthing like in the Bush TV181 series, tabs not soldered properly." So he ran wires from the top to the bottom of the chassis and soldered them securely at each earth point. This solved the flicking and bowing and left Tim with the hum bar.

## The Hum Bar

Now we all know what to do about this. Change the AD161 series regulator transistor in the l.t. supply and the bridge rectifier for a start. Tim did all this and more, though the curve that accompanied the hum bar should have told him that the l.t. supply wasn't responsible. He turned to the h.t. lines and found that all the electrolytics had been resoldered – not very tidily.

"I'll shunt them one by one" he thought. He switched off and used a 470 $\mu$ F test capacitor with jump leads and crocodile clips. First he clipped it across the h.t. reservoir capacitor – that couldn't be it because the h.t. was well up, but just in case – and switched on. No change. Why had he switched off? Because the spark might have frightened him (and the dog). Actually he hadn't switched off, he'd pulled the plug out – that was easier. Now that the test capacitor was charged it could be applied to the other electrolytics without frightening him and the dog.

While he was playing around the lower electrolytic he accidentally touched the earth tag with the live lead. This should have produced a nasty spark and made him jump.

It didn't and he frowned a little. He touched it to the main frame and jumped for his life at the loud crack. The dog fled and Tinker Bell came in demanding to know what he'd done to him.

"Sod the dog" said Tiny Tim. "What about me? I nearly jumped out of my skin."

"Yes but you know what happens when you discharge those things. The dog doesn't."

So Tinker Bell went out and Tim was left on his own. Why hadn't the capacitor discharged when he'd touched the lower electrolytic's earth tag? Because it wasn't earthed. He connected the voltmeter to the tag and it said 200V. He took his glasses off and peered closely. The earth track was very thin and was open-circuit. Tim soldered another wire in to ensure that the earthing was sound. But he still hadn't cured the hum trouble.

"If it's not the smoothing, what else?" thought Tim, getting a bit edgy now. Heater-cathode leakage in the PCF802? He'd just replaced that. Fit another one. Still no change. That side ripple had a sort of ghost like foldover in the background, like you get when the tuning is out and the a.f.c. is off.

So Tim operated the a.f.c. switch, which is incorporated with the brightness control. The set went off. The switch had already been in and pressing it had allowed it out (a.f.c. off). So he pressed it in and the set came back on. He pressed the volume control switch – the real on/off switch – and nothing happened. Tim jumped up and down in rage. "Where's the bloody cat" he bawled.

"She's in the kitchen and she'll stay there until you've done your job properly" said Tinker Bell. "She's not here for you to kick when you can't think of anything better to do."

"Someone's taken the mains leads off the volume control and connected them to the brightness control" moaned Tim.

"What's wrong with that?" asked Tinker Bell.

"Putting them on the brightness control will put hum on the picture" said Tim.

"In that case" said Tinker Bell "putting them on the volume control will put the hum on the sound, and anyway why don't you take the mains leads off the controls and tape them up so that the set is on all the time, like on that Philips portable you were so proud of – no set should have an on/off switch you said, they're dangerous."

So Tim did what he was told. He took the leads off the a.f.c. switch and connected them together. He replaced the plug and was rewarded with a cloud of smoke from the i.f. strip. The neutral mains lead should have gone to chassis via the switch. He'd taken off the mains live and neutral leads, also the a.f.c. lead that's taken to chassis via the switch. The net result was that mains neutral was finding its way to chassis via the a.f.c. circuit.

Tim bashed his head on the bench and broke his glasses. He replaced the burnt out 470 $\Omega$  resistor and checked inside the a.f.c. can. There was a scorched resistor but the transistor read all right. He decided to put the lot back in and wired the neutral direct to chassis, refitting the brown a.f.c. lead back to chassis where it

belonged. Then he plugged in, gingerly, and waited.

The picture came on and was lovely. Who said he wasn't a good engineer? – apart from Tinker Bell. Mr. Crankcase came back at five o'clock to pick up his set and was told that in accordance with Tiny Tim's new rules the on/off switch was no longer operative.

"We never used it anyway. We always pulled the plug out." Mr. Crankcase took out the CVC5 and came back in with a CVC20. "Run the rule over this will you Tim?"

### The CVC20

Tim peered into the back and was surprised to see the front control panel lying inside the set in pieces. This upset him in view of the trouble he'd had with the previous set. His little mind immediately rang up fifteen quid. He removed the pieces and put them back together. The control panel now fitted nicely and he had a.c. leaving it and making its way across to the chopper. But nothing came from the chopper.

The driver is often the cause of this but turned out to be o.k. Tim then took out the chopper control subpanel and checked this, that and the other. He could find nothing wrong and was by now feeling fed up. So he locked up the shop, put out the lights and went upstairs.

### The Next Day

Tim was up bright and early next day – in a vain bid to stop the dog chewing the morning paper.

"You're not a dog. You're just a pig and barking machine. We'd be better off with a tape recorder that makes barking noises than with you" said Tim.

"Leave the dog alone" bawled Tinker Bell. "What's he done for you to kick up such a fuss?"

"He only chewed up your competition page. The rest is untouched."

"I'll kill the dog when I come down."

Tim hurriedly taped together the pieces of the page then got on with breakfast.

"Before you start eating, nip down to the newsagent and get me an untorn paper" said Tinker Bell, "I must have my entry in the post before nine o'clock."

What a start. But Tim was soon at work on the CVC20. He put the chopper control panel back, switched on and was surprised to hear the e.h.t. rustle up and the sound boom out. "Fancy that" he said. "The control panel couldn't have been making proper contact. What a clever boy I am". He then wrapped it up and moved it to the soak test bay – the other end of the bench.

### Another ITT

Tim was a bit surprised to see this CVC5 come back since it had been collected only a couple of days ago after he'd restored the colour. He'd spent some time checking around the top left corner of the chassis and had eventually moved down to the chroma amplifier transistors T27 and T28 where he'd found that slight pressure applied to T28 (the small round BF128) would restore the colour. Although there didn't appear to be any poor contacts he'd resoldered the base, emitter and collector. After doing that the colour couldn't be lost: the set had behaved itself on test but here it was back again with the same fault.

This time he dived straight for the BF128 transistor. A cold check revealed that it was non-conductive. So he fitted a BF197, leaving the screen unused, and switched

# next month in

# TELEVISION

## ● USING A LOGIC PROBE

Logic circuitry has been used in VCRs from the start for system control purposes. As a result there are many faults that can be dealt with only on a trial-and-error basis or by investigating the logic conditions. Voltage readings provide some clues but the type of scope used for TV servicing will not usually handle fast changing pulse trains. The simplest approach to this problem is to use a logic probe – a device that will become more useful to you the more you get to use and know it, and will of course also help to sort out problems in TV control systems and microcomputers. David Botto outlines the minimum requirements for a probe for servicing purposes and describes its use in typical circuitry.

## ● COMMISSIONING TVRO SYSTEMS

Many dealers and enthusiasts are probably thinking about installations for satellite TV reception, something that can already provide additional channels in the UK from low-power satellites. What's involved technically and what sort of expense is likely to be involved? Geoff Lewis provides a simple guide in question and answer form.

## ● SERVICING HYBRID CTVs

The Decca Bradford and ITT CVC5-9 series chassis have proved to be able to provide fine pictures over a much greater than originally expected life span. Many are still in use and of course fail from time to time, causing confusion to those engineers who know only solid-state circuitry. Sam Simon provides a quick-check guide to dealing with common basic faults.

## ● TRANSISTOR FIELD TIMEBASE CIRCUITS

While the vast majority of valve field timebase circuits employed the same basic configuration a wide variety of circuit techniques, including class A, B and AB operation, have been used in transistor field timebases. Part 2 of this series describes the operation of these circuits.

**PLUS ALL THE REGULAR FEATURES**

**ORDER YOUR COPY ON THE FORM BELOW:**

TO ..... (Name of Newsagent)

**Please reserve/deliver the November issue of TELEVISION (£1.10), on sale October 16th, and continue every month until further notice.**

NAME .....

ADDRESS .....

on. He was bitterly disappointed to find no colour. A voltage check showed that there was no forward base bias, a cold check revealing a short-circuit from the base to chassis. This was due to a speck of solder between the base and the screen (unused) print: a flick of the screwdriver blade restored normal operation which lasted for hours on end.

### Tim's Terrible Trouble

Tim thought it was time he paid some bills. So he gathered them all together and added them up. The total frightened him out of his life and as he lay dead Tinker Bell came in to find out what the scream had been for. She kicked Tim in the ribs and he stirred and moaned.

"Get up and get something done you fool. How am I going to get a new dress if you just lie there moaning?"

Tim got to his feet and showed Tinker Bell his piece of paper. "Look, this is what we owe. Now look at this one which shows what we've got. It's not enough."

"You ought to be able to afford me a new dress" snapped Tinker Bell. "If you can't earn enough by mucking about with those daft TVs you could always write about them like that clever Mr. Trundle and that Silly Simon. I've been looking at that magazine and I'm sure the editor is a nice man who might pay you if you could bestir yourself and do a bit of writing instead of keep complaining and trying to kick the cat."

"He might, he might" mused Tiny Tim. "If I could learn to type, that is."

# Line Selector Unit

A. B. Bradshaw

Many lower-priced oscilloscopes have good wideband deflection systems but poor triggering facilities. This is particularly a disadvantage if you want to examine the vertical interval test signals transmitted during the field flyback blanking period – these signals are very useful for monitoring the performance of the TV transmission path.

The unit described in this article has been in use for several years to provide improved TV triggering. It's in two sections, the first of which produces trigger pulses for display of the selected line. The second section was originally designed to provide X-scan and bright-up signals for the Hewlett-Packard 1707 oscilloscope, but if required the unit can be used to provide line triggering only. If the unit is also used to provide X-scan and bright-up outputs the only oscilloscope controls that need to be operated are horizontal and vertical position with sweep magnification by ten times. In this mode the oscilloscope's timebase is switched to "external" – see Fig. 1 for typical connections. When the oscilloscope's timebase provides the X scan the unit provides a selectable line trigger pulse at the start of the line required. Fig. 2 shows the complete circuit.

There are three switches which provide the following functions. The rotary switch S1 selects the line to be displayed. The latching push-button fast-scan select switch S2 is for use with the oscilloscope's sweep magnification  $\times 10$  control, enabling the 2T pulse to be displayed over a large percentage of the scan – thus K rating graticules can be used. The non-latching field select push-button switch S3 is used to give a "field slip" so that the alternate field can be selected. This latter arrangement is a simple solution – the alternative logic circuit technique would

mean that the last line of the field would have to be identified (half or full line). The "field slip" method is not elegant but is very cheap!

### Circuit Operation

Positive-going composite video with an amplitude of 1V peak-to-peak is fed to Tr1 which provides a voltage gain of ten. The output is capacitively coupled to the base of Tr2 with d.c. restoration by means of D1. The sync pulses are stripped off at the collector of Tr2 while Tr3 provides a TTL compatible output for the following i.c.s.

IC1 and one of the gates in IC2 are arranged as a field sync pulse separator, the output being made available at TP2. IC3 is a "start delay" monostable multivibrator which drives IC4. This latter i.c. is used to provide an enable pulse for the following BCD decade counter IC5. Line sync drive for IC5 is provided by IC2b. When enabled, IC5 counts the line sync periods: its outputs are decoded by the BCD-to-decimal decoder IC6.

The decimal decoded outputs from IC6 are brought out to Vero pins on the PCB. These are the basic line trigger pulses used for display selection. IC6's outputs are "loose wired" to a low-capacitance rotary selector switch (S1). Switching the live logic signals in this way is done for cheapness: the method works satisfactorily in practice provided the leads are kept short (2in.).

We now have pulses for each line during the flyback period of interest. The second part of the circuit provides bright-up and X-scan signals. The emitter-follower Tr8 is used to drive the cable bright-up pulse feed to the oscilloscope. The reason for the unusual arrangement in its collector circuit is to provide a measure of protection should the feed from Tr8 become short-circuit.

The selected line trigger pulse is fed to the fast-scan latching switch S2 and to the delay gates IC2c/d. The need for this delay in the fast-scan position will vary depending on the starting rate of the X amplifier in the scope and may require adjustment to the values of C9 and C10 to centre the displayed pulse in the scan.

The selected line pulse is also fed to IC7 and Tr4, via R22/C11 and R23/D6 respectively. Tr4 is used to discharge C13/14. When Tr4 is off, these capacitors charge linearly via the constant-current source Tr5. The resultant voltage ramp is buffered by the cascaded voltage-followers

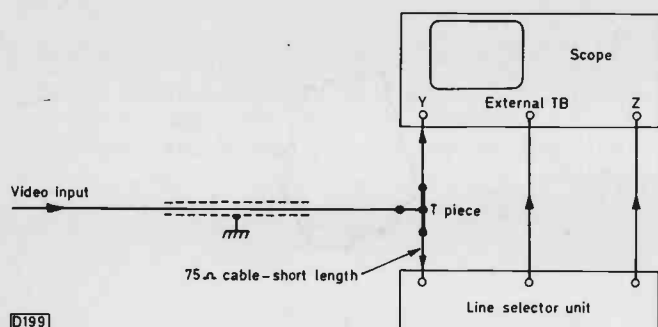


Fig. 1: Typical scope/line selector unit connections.

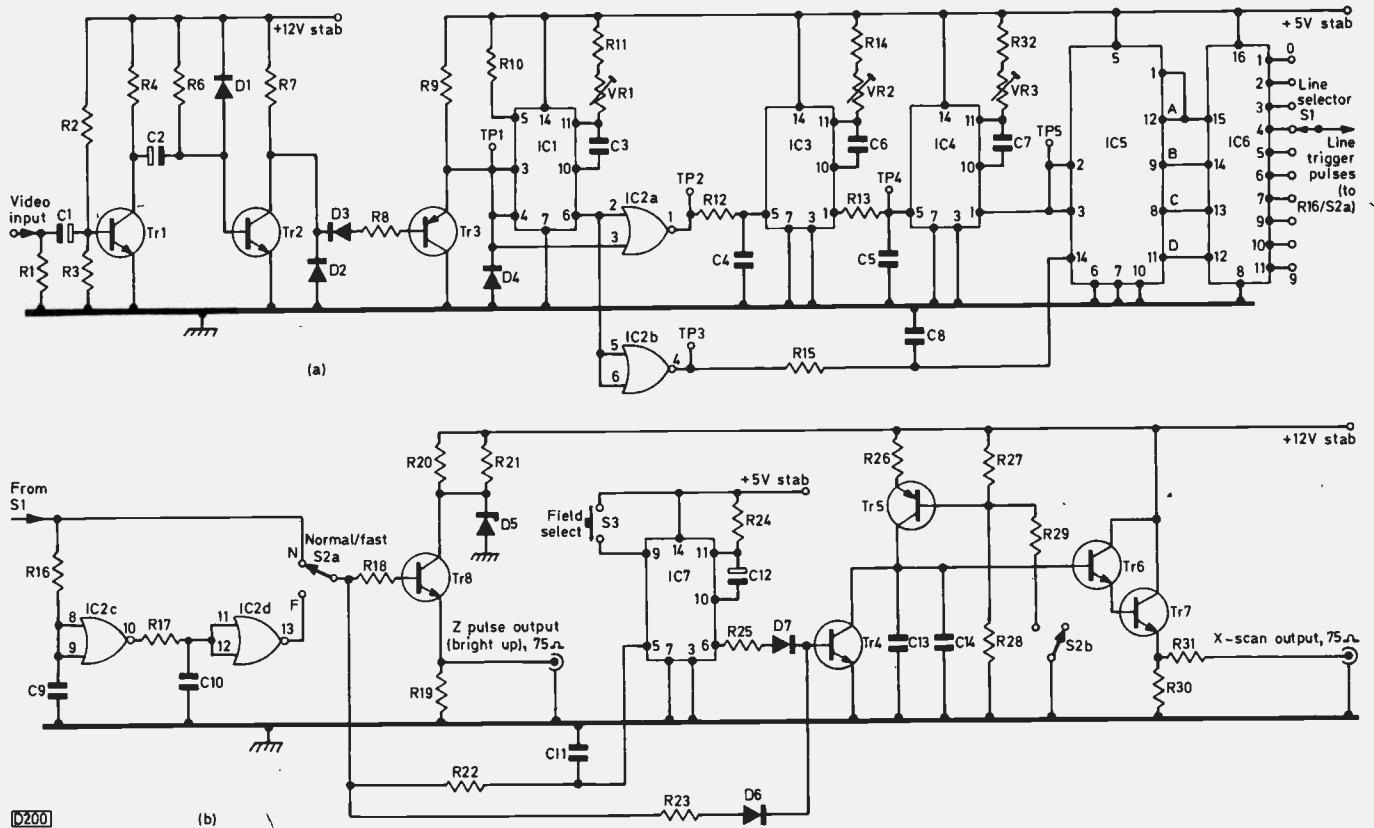


Fig. 2: Circuit diagram. (a) Line selector section. (b) Scan generator section.

Tr6/7 to provide a low-impedance output – the X-scan signal. The charging rate is increased when the fast-scan push-button switch S2 is operated.

The field gating multivibrator IC7 is made to slip to the alternative field by operating S3.

## Components list

### Resistors:

R1 75Ω	R30 1k
R2 56k	R31 1k
R3 10k	R32 3k9
R4 1k	All 5% and
R5 100Ω	0.25W unless
R6 1M	otherwise
R7 10k	indicated
R8 1k8	
R9 10k	
R10 1k	
R11 13k	
R12 100Ω	
R13 100Ω	
R14 8k2	
R15 100Ω	
R16 100Ω	
R17 100Ω	
R18 27k	
R19 1k	
R20 680Ω, 1W	
R21 680Ω, 1W	
R22 100Ω	
R23 100k	
R24 5k2	
R25 10k	
R26 100Ω	
R27 13k	
R28 100k	
R29 75k	

### Presets:

VR1-3 10k multitur

### Semiconductor devices:

Tr1,2 BC107
Tr3 2N4121
Tr4 BC107
Tr5 BCY70
Tr6-8 BC107
D1-4 BAX16
D5 6V8, 1W
D6,7 BAX16
IC1 74121
IC2 7402
IC3,4 74121
IC5 7490
IC6 7442
IC7 74121

### Capacitors:

C1 100, 12V
C2 20, 12V
C3 820p, S.M.
C4 470p, S.M.
C5 470p, S.M.
C6 0.1, polyester
C7 0.1, polyester
C8 0.001, polyester
C9 0.022, polyester
C10 0.022, polyester
C11 150p, S.M.
C12 6.4, tant
C13 2.200p, S.M.
C14 0.033, polyester

### Switches:

S1 Low-capacitance, 10-pole 1-way rotary  
S2 Dual-latching push-button  
S3 Single push-button (non-latching)

A dual-beam oscilloscope is required to set up the unit as the various start and stop waveforms must be related to the TV waveform. VR1/2/3 are adjusted until the correct waveforms are obtained at the test points – see Fig. 3.

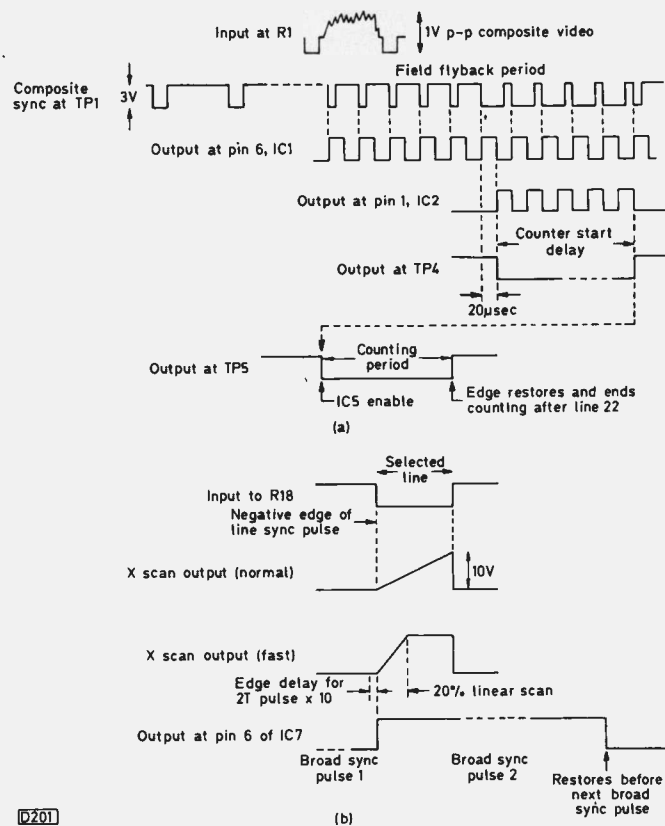


Fig. 3: Waveforms at various points (a) in the counter section and (b) in the scan generator section.

# Philips G11 Chassis Fault Chart

Dennis Apple

Before itemising specific fault conditions we'll provide some general comments on the chassis.

## Voltage Surges

The G11 has been found to be susceptible to h.t. and mains surges which tend to destroy the BU208A line output transistor and the TDA2600 field timebase chip, also other components as indicated later. Such surges can be caused by intermittent mains leads and by the h.t. reservoir capacitor C4029 (470 $\mu$ F) which tends to produce internal arcing due to poor riveting at its terminals. Since other components can be responsible for mains fuse blowing, failure of the line output transistor etc. the following procedure is recommended in cases where this transistor breaks down for no apparent reason – as well as to ensure more reliable working:

- (1) Check that the mains plug is securely wired and that the bared mains wires have not been soldered before fitting into the mains plug (any connections so made tend to become intermittent over a period of time).
- (2) Change the h.t. reservoir capacitor C4029 to a DALY/ITT type (Philips part no. 124-47056).
- (3) Check for dry-joints, especially around the top, right-hand line scan panel.
- (4) Connect a 1 $\Omega$ , 4W resistor (Philips part no. 113-80245) in series with the anode of each of the mains rectifier thyristors (4018/4020).
- (5) Remove mains fuse FS1302 and replace it with a 1.5 $\Omega$ , 10W resistor – ensure that it's well clear of surrounding components.
- (6) Ensure that the mains on/off switch is in good condition, with fast snap action. The contacts should be clean and nonpitted.

## Intermittent Faults

Erratic performance and various intermittent faults have usually been found to originate in dry-joints, loose connections etc. on the various panels. These poor joints and connections are common on the line scan panel at the top right-hand side of the chassis. Attention should be paid to this section first not only when the chassis has obvious poor connections but also when the symptoms range from a completely dead set through lack of width to bowed picture edges etc. By tapping the panels whilst the set is switched on the poor joints are often revealed as the set resumes normal operation, often giving a spark to assist with the accurate location of the faulty part of the panel. In severe cases it may be quicker to resolder the whole line scan panel than attempt to trace transient faults that seldom seem to put in an appearance when the set is on the bench.

Now to specific faults.

### 1: Dead set.

Check R3106 (820 $\Omega$ ); R2010 (5.6k $\Omega$ ); R4044 (120k $\Omega$ ); R3120 (15 $\Omega$ ); R4059 (15k $\Omega$ ); diodes D4091, D4092 in the mains bridge rectifier circuit; Tr4085 (BC148) and Tr4086 (BC158) in the beam limiter circuit; the BF458 RGB

output transistors. Also check for dry-joints in the interconnecting plugs and sockets, especially around 3D6, 3D7, 15A15 and 15A16; on the top right line scan panel around R3106; and at the mains filter chokes.

### 2: Blown mains fuses FS1301/2.

Check mains bridge rectifier diodes D4091/2. It's best to replace all four diodes in the bridge with more robust types, e.g. BY127s. Carry out modifications given in the introductory comments, especially if no specific reason can be found for the fuse blowing.

### 3: Blown h.t. fuse FS4037.

Check D3133 (BY223) which often destroys Tr2150 (BD238) as well; the h.t. decoupling capacitor C4040 (47 $\mu$ F); the series smoothing transistor Tr4032 (BD201); the 27V zener diode D4021; C4029 (see introductory comments); the BU208A (see general comments and fault 8); C3135 (0.91 $\mu$ F). Ensure that the screened cable between the timebase panel and the line output panel is making good contact and that the screening is earthed at both ends, also that the foil on the line output transistor's heatsink is not punctured.

### 4: No sound or raster, e.h.t. present.

Check the TDA1412 12V regulator (IC5073) on the i.f. panel.

This i.c. can go faulty a short time after switch on, in which case the picture fades away and colour is lost. It can be responsible for many symptoms including a dark picture with normal sound, and a dark picture with no colour and the h.t. pulsating when the brightness is turned up.

### 5: Blank screen, e.h.t. present.

Check the 4.7V zener diodes D4090 and D6011 in the beam limiter circuit (in later sets D4090 was replaced with an 0.0022 $\mu$ F ceramic capacitor); Tr2164 (BC148) in the field flyback blanking circuit.

### 6: Blank raster, no sound.

Check Tr6462 (BF196) in module U5400.

### 7: Blank raster with teletext sets (sound normal).

Check the SAA5050 i.c. on the teletext panel.

### 8: BU208A line output transistor short-circuit.

Check C4029 (see introductory comments); the screened cable from the timebase panel to the line output panel (see fault 3); C3135 (0.91 $\mu$ F) – this capacitor sometimes disintegrates spontaneously. Also check for sparking at the mains switch or plug.

### 9: Intermittently pulsating raster.

Check R4059 (15k $\Omega$ ) on the power supply panel.

### 10: Dark picture, no colour, h.t. pulsating.

Check the TDA2590Q sync separator/line generator i.c. (IC2510). In later sets this i.c. is a TDA2591Q which is a direct replacement.



**11: Intermittent h.t. variations.**

Check the TDA2590Q i.c. (see fault 10); R4059 (15k $\Omega$ , 9W); and for dry-joints, especially around the upper right-hand line scan panel.

**12: Intermittent tripping, i.e. regular clicks heard from an otherwise dead set.**

Check the diode-split line output transformer.

**13: No h.t. at fuse FS4037.**

Check R4059 (15k $\Omega$ ) and the beam limiter transistors Tr4085/6 – to confirm, temporarily disconnect the emitter of Tr4086.

In sets with full ultrasonic remote control check standby switch transistor T519 (BC158) on the remote control receiver panel.

**14: Hum bars.**

Check Tr4032 (BD201); Tr4033 (BCX32); C4034 (10 $\mu$ F); D4021 (BZX79-C27).

**15: Field flyback lines present (often intermittent).**

Check C2156 (0.0022 $\mu$ F) – this component may be found dry-jointed.

**16: Whole raster shifts vertically (often intermittently) followed by blowing of FS3143 after a short time.**

Check IC2520 (TDA2600); poor timebase panel connections; poor contact at pins of IC2520; C2099/2100 (both 1,000 $\mu$ F).

**17: Striations (faint vertical lines, especially at the left-hand side of the screen).**

Add a ferrite tube on the wire link between tag 14 of the line output transformer and C3128; ensure that flying leads are correctly tied in their original positions.

**18: Dark vertical bar at the right-hand side of the screen.**

Check the TDA2590Q sync separator/line generator i.c. – see fault 10.

**19: Line jitter.**

Most likely with sets using a TDA2591Q sync separator/line generator i.c.: to eliminate, connect a 27k $\Omega$  resistor in parallel with C2029.

**20: Field collapse with FS3143 probably blown.**

Check IC2520 (TDA2600) – destruction of this i.c. is often caused by a defective C4029 (see introductory comments); poor contact between IC2520 and holder (fault may be present after FS3143 has been replaced); R2066 if the voltage at pin 16 of the TDA2600 is much lower than 19V; C2099/2100 (both 1,000 $\mu$ F); L2092/C2060/R2066 – dry-joints around these components are likely.

**21: Top cramping, often with bright horizontal line.**

Check C2072 (4.7 $\mu$ F).

**22: EW raster distortion with width and shaping controls inoperative.**

Check D3133 (BY223); Tr2150 (BD238); D3132 (BYX55-600); L3134; L3137; Tr2119 (BC148C)/Tr2140 (BC158)/Tr2149 (BFX85). Check also for dry-joints around the above components – a dry-joint is often found at pin 14 of

the line output transformer, usually on the wire link to C3128.

**23: Field bounce with VCR operation.**

Check the tuner a.g.c. smoothing capacitor C5010 (150 $\mu$ F). Ensure that C2039 on the timebase panel is 0.0039 $\mu$ F; if necessary R2003 can be reduced in value but not below 1.5M $\Omega$ .

**24: No field sync (vertical rolling).**

Check for broken print at the left-hand corner of the timebase panel. If necessary check C2072 and C2080.

**25: Narrow picture.**

Check C3135 (0.91 $\mu$ F).

**26: Intermittent black horizontal lines.**

Suspect the tuner. This is normally not repairable though it may be worth using a very hot iron to resolder all earth connections etc.

**27: Inability to tune over the whole range.**

Suspect the tuner – assuming that preset adjustments have not been altered.

**28: Low gain.**

Suspect the tuner.

**29: Tuning stuck on channel 1.**

Check for poor contact at pin 2, plug 4C, on the power supply panel.

**30: Gradual detuning over a long period.**

Replace the TAA550 tuning voltage stabiliser i.c.; check for dry-joints on the control panel.

**31: Set goes into the standby mode when remote control on/off is operated.**

Suspect failure of small contact pair on the mains on/off switch.

**32: Volume and brightness controls inoperative in manual or remote mode.**

Check IC1 (SAA5010) and R49 (10 $\Omega$ ) on the remote control panel.

**33: Loss of one colour.**

Check for open-circuit print in control unit 1617.

**34: Remote control unit battery has limited life.**

IC3606 (SAA5000) has been replaced by an SAA5000A to reduce current drain: with this the values of R3601-5 and R3609 are increased to 100k $\Omega$  (from 33k $\Omega$ ).

**35: Loss of colour.**

Check C6062/6070 (both 0.33 $\mu$ F) on the decoder panel; alignment of L5630 in module U5600.

**36: Pulsating red/green/blue picture.**

Check relevant BF458 RGB output transistor – Tr6105 blue, Tr6093 green, Tr6083 red.

**37: Intermittent bottom cramping.**

Check C2083 (15 $\mu$ F).

**38: Picture pulsates on high contrast scenes.**

Check C3129 (0.47 $\mu$ F).

# Long-Distance Television

Roger Bunney

Though Sporadic E reception during July was less than during the exceptional preceding month of June, conditions were nevertheless very good. There was also tropospheric enhancement on several days, producing central European Band I/III/u.h.f. signals in the UK. The collated UK SpE reception log is as follows:

- 7/7/85 ARD (West Germany) ch. E2; ORF (Austria) E2a; MTV (Hungary) R1; NRK (Norway) E2, 3, 4; JRT (Yugoslavia) E3; RAI (Italy) IA; TVE (Spain) E2, 3, 4; RUV (Iceland) E3; TSS (USSR) R1, 2.
- 8/7/85 EPT (Greece) E3; RAI IA, B; SR (Sweden) E2; CST (Czechoslovakia) R1; TSS R1; YLE (Finland) E3.
- 9/7/85 RAI IA; RTP (Portugal) E2, 3; TSS R1, 2, 3; SR E2, 3, 4; NRK E2, 3, 4; ARD E2.
- 10/7/85 RAI IA, B; TVE E2, 4; RTP E2, 3; MTV R1, 2; JRT E3.
- 11/7/85 RAI IA, B; TVE E2; TVE-2 E2; EPT E3; JRT E4; RTS (Albania) IC; CST R1; ORF E2a.
- 12/7/85 RAI IA, B; EPT E3; DR (Denmark) E3; TVE E3; SR E2; VOA harmonic on ch.E2!
- 13/7/85 NRK E2, 3, 4; SR E2; TSS R1, 2; CST R1; JRT E3, 4; RAI IA.
- 14/7/85 RAI IA.
- 15/7/85 RAI IA; TVE E3; CST R1; SR E3; DR E3.
- 16/7/85 MTV R1, 2; JRT E3, 4; RAI IA; TVE E3; TSS R1, 2; DR E3.
- 17/7/85 RAI IA, B; MTV R1, 2; JRT E3, 4; ORF E2a; CST R1, 2; TVR (Rumania) R2; TVE E2, 3, 4; ARD E2; DR E3; SR E3; +PTT (Switzerland) E2, 3.
- 18/7/85 ARD E2; ORF E2a; RAI IA, B; CST R1, 2; JRT E3, 4; TVP (Poland) R1; SR E3; TSS R1.
- 19/7/85 ORF E2a; TSS R1, 2; RAI IA, B.
- 20/7/85 TVE E2, 3, 4; TVE-2 E2; RAI IA, B; RTP E2; MTV R1.
- 21/7/85 CST R1, 2; JRT E3, 4; ORF E2a; ARD E4; TSS R2; TVP R2; TVE E2, 4; Aramco TV ch. E3, see later.
- 22/7/85 RAI IA, B; NRK E2, 3; TVE E2, 3.
- 23/7/85 JRT E3; RAI IA, B; NCT (Udine - Italian private station) E3; EPT E3; MTV R1, 2; NRK E3; TVE E2, 3, 4; Arabic exotics on chs. E2, 3 - see later.
- 24/7/85 TSS R1, 2; CST R1; YLE E3; TVE E2, 3, 4; RAI IA.
- 25/7/85 TSS R1, 2; TVP R1, 2; CST R1, 2; DR E3; TVE E3; ARD E2.
- 26/7/85 TVE E2, 3, 4; TVE-2 E2; RAI IB; ORF E2a; ARD E2, 4; DFF (GDR) E4; MTV R1; JRT E3; +PTT E3; RTP E2, 3; SR E2, 3, 4; NRK E2, 3, 4; RUV E4; YLE E3, 4; TSS R1, 2; CST R1, 2.
- 27/7/85 TSS R1, 2; NRK E2, 3; SR E3; YLE E3, 4; CST R1; RAI IA.
- 28/7/85 RUV E3, 4; NRK E2, 3, 4; TSS R1, 2; TVR R2; ORF E3; TVE E2, 3; suspected RTM (Morocco), see later.
- 29/7/85 MTV R1; JRT E3, 4; RAI IA, B; RTS IC; CST R1; DR E3; NRK E3; SR E2, 3, 4.
- 30/7/85 TSS R1, 2; SR E2, 3, 4; NRK E3; TVP R1; JRT E3; RAI IA, B; TVE E2, 3, 4; RTP E2, 3.
- 31/7/85 MTV R1; JRT E3, 4; RAI IA, B; TVE E2, 3, 4; TVE-2 E2; TVR R2, 3; NRK E2.
- 1/8/85 NRK E2, 3; TSS R1, 2.

Several exotic signals were received during the month. Between 0855-0945 BST on July 21st Tim Anderson (St. Leonards) noted a ch. E2 electronic test pattern compris-

ing pulse and bar/sawtooth - rather smeary and unstable - from the south. Thoughts as to the origin suggest GBC (Ghana) though I wonder if it could have come from Dubai? At 1840 on the same evening Iain Menzies (Aberdeen) clearly identified the station logo "Aramco TV Saudi Arabia" on ch. E3 from the south east, floating over a JRT signal. This transmitter is sited at Dhahran and has an e.r.p. of 5kW - a very good catch.

Between 1656-1706 on the 23rd Tony Privett (Basingstoke) noted Arabic type figures with "Kurdish" style headgear on ch. E3. This would suggest JTV (Amman). On the 28th Iain Menzies logged a ch. E4 Arabic-subtitled programme without VITS from the south, consisting of Tom Sawyer with US dialogue. This suggests RTM (Morocco) though the time (1130 BST) seems a little too early for RTM to be on programme.

There was an intense Band I opening on July 30th, to the eastern USA as far south as Florida: various UK amateurs worked two-way contacts with many US amateurs from 2230 onwards at 50MHz. This suggests that the path could have supported ch. A2 vision but at the time of writing there have been no reports of TV reception. The opening came some 28 days (solar rotation) after an aurora but I feel that the mechanism was more likely to be intense E layer ionisation giving multiple-hop propagation. Unfortunately I was away on holiday from July 27th through to August 4th - typical!

Tropospheric propagation was similarly very active. Two small openings on the 7th and 13th produced Benelux and French Band III/u.h.f. signals in the southern UK. The main event occurred on 23rd/24th however when an intense spell produced very strong Band I/III/u.h.f. signals throughout much of the UK and central Europe. In particular W. German Band III signals were well received in the midlands and as far west as Plymouth late on the 23rd and from early on the 24th to midday. Switzerland was well received along the south coast on chs. E4, 7, 12, 30, 31 and 34. Very deep fading was experienced here at Romsey in Band III. At the same time West German signals were noted by several enthusiasts in the south west. TVE ch. E3 was a very steady signal from 2250BST at St. Leonards, with picture quality up to P5 (noise free).

Swiss signals on chs. E3, 4, 9, 30, 31, 35 and 59 were again seen on the 24th. French Band III/u.h.f. signals were present during this period at very high levels. There appeared to be a degree of ducting with many of the more distant signals. The tropospheric lift didn't help much with reception in the north of the UK. Finally, NOS Lopik ch. E4 has in recent weeks been seen with an occasional FUBK test pattern, fortunately including an identification. Sound tests with two-channel stereo and mono information are carried from 0945-1020 and 1345-1420 CET on Mondays-Saturdays.

In all a good month. My thanks to the following for sending in details of their reception: Reg Roper (Torpoint), Tony Privett (Basingstoke), Roger Pates (Nottingham), Simon Hamer (Powys), Jeremy Cecil (Shoreham), Alan Beech (Dollar), Tim Anderson (St. Leonards), Cyril Willis (Ely), Dave Shirley (Hastings), Bill Cotteril (Tipton) and Iain Menzies (Aberdeen).

## News Items

**France:** Changes are being made to the structure of TV broadcasting in France. Briefly, there will be four private TV channels; the existing third channel FR3 will be split into two forms of programming, one purely regional and the other as "the foundation of a European cultural

channel" which will eventually be broadcast to Europe by satellite; Canal Plus is being reorganised as a non-subscription channel, obtaining finance from commercials. Incidentally the French government has been providing technical and financial assistance for a radio/TV service in the overseas colony of Cape Verde.

**Finland:** The Swedish first programme is to be transmitted by a number of local stations in Finland, starting with Aaland Island (ch. E28, 20kW) and Pyhavuori. YLE has proposed a third channel, financed by advertising, to start initially in built-up areas.

**Hungary:** MTV is drawing up plans for a third channel, with regional content, to start in the late 1980s. Additional programming may be obtained via satellite links. MTV-2 currently has regional programming in Budapest, Pecs and Szeged.

**Eire:** A new (July 1985) transmitter network information sheet is available from Reception Investigation Department, Radio Telefis Eireann (RTE), Dublin 4, Eire - those interested should send a stamped s.a.e. (foolscap) for a copy.

**UK V.H.F. allocations:** Further information on the reallocation of the emptied v.h.f. TV bands has been released. Apart from a 500kHz paging service (frequency not specified) the 49.82-49.9MHz band will be used for "low-power devices, such as toys and telemetry equipment" - this may result in greater use of cordless phones, a situation that must be monitored. There's to be a considerable expansion of private mobile radio in Band III throughout the UK, though not with networking, i.e. excluding circuit interconnections. Five 1MHz blocks in Band III are to be used for commercial cordless phones. Various data handling systems will also be permitted.

### DTI Radio Investigation Service

Until now the DTI's Radio Investigation Service could be called in to investigate causes of interference to the reception of broadcasting services at domestic premises. The DTI recently announced a "phased withdrawal" from the provision of this service, justifying this action on the basis that most complaints are due to defective aerials, poor installations or customer misuse of equipment. The RIS staff is to be reduced from the present 340 to around 240 and will be mainly concerned with tracing radiation from unlicensed sources. The following measures have been announced:

- (1) A comprehensive booklet, available from post offices now and including pictures, has been published to assist viewers in identifying the causes of problems.
- (2) BS905, which specifies minimum interference immunity standards, is to be incorporated in legally binding regulations as soon as possible, making it an offence to make, sell or import receivers not complying with this standard.
- (3) A charge of £21 will be made prior to an RIS call to a domestic property, the call being subject to confirmation that an external aerial is in use and that a detailed log of interference observations has been made on the appropriate form.
- (4) The names of all applicants for an interference call will be sent to the TV licence office.
- (5) From January 1st 1987 visits will be made only when they coincide with other visits to the same area and when a TV dealer has been unable to remedy or identify the cause of the problem.
- (6) From January 1st 1988 the RIS will only visit receivers that comply with BS905.



We are the sole UK retailer for the impressive and unique 'TV-BILDKATALOG' the up to date (1985) Test Card guide for Europe. Of very high quality, it runs to 114 pages, contents include **European Test Cards, Logos**, broadcast organisations/abbreviations, transmission standards and **Regional Maps**. Another useful feature is the **Picture Section of Clocks**, essential for **All DXers**.

Roger Bunney's new TV-DX Book - **TV DXING FOR THE ENTHUSIAST** is due out this Autumn - we'll have the first retail supplies. Enlarged and completely revised from the earlier Babani BP52 editions, this is essential reading for enthusiasts at all levels. We are taking advance orders on this new book. For DXing the correct way, consult **SOUTH WEST AERIALS** the experts, we carry a vast range of Aerials, Amplifiers (head, distribution, set-backs etc.) Cable, Rotators, Filters and many other items too numerous to mention, but all listed in our comprehensive 22 page **CATALOGUE** costing only 60p. Why not send for a copy today.

**TV-BILDKATALOG** 1985 Test Card guide for Europe..... £5.65  
**TV-DXing For The Enthusiast** by Roger Bunney (new edition) available Oct '85 £2.95  
**AMATEUR TELEVISION HANDBOOK** completely revised edition ..... £2.95  
**WALTHAM 416 6"** screen VHF/UHF Television for DXing, covers Bands 1, 3 & UHF with continuous varicap tuning; System B/G operation (adjustment to 6MHz sound for UK TV standard available at additional cost of £2.50); 12 volt and mains operated ..... £73.70

Also available Colour Multi-Standard PAL/SECAM Televisions and Video Recorders. We are **THE DXING Specialists**, advice given on ALL reception problems (SAE please).

All prices inclusive of VAT and Carriage Delivery 7-10 days  
**ACCESS & VISA** Mail and Telephone orders welcome



**SOUTH WEST AERIALS (T)**  
 11, Kent Road, Parkstone,  
 Poole, Dorset, BH12 2EH. Tel: 0202 738232.



## TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

<b>RANK BUSH MURPHY</b>		<b>ITT:</b> VC200 to VC402	9.20
A774 with stick rectifier	9.78	CVC1, CVC2 (FORGESTONE)	11.50
A816, T16, T18, Z712, Z715	10.35	CVC5, CVC7, CVC8, CVC9 series	9.20
T20, T22, T26, Z179, A823	11.50	CVC20	10.35
Z718 Basic unit	13.50	CVC25, CVC30, CVC32, CVC45	9.20
T24e, T24h split diode	P.O.A.	CVC40, CVC1200, 1210, 1215	P.O.A.
		FT110, FT111. P/no AT2063/02	11.50
<b>DECCA:</b> 1210, 1211, 1511	11.50	<b>PYE:</b> 169, 173, 569, 368 series	9.20
1700, 2001, 2020, 2401, 2404	9.20	CT200, CT200/1, CT213 series	10.35
CS1730, 1733, 1830, 1835	9.20	725-731, 735, 737, 741 Series	9.78
30, 70, 80, 90, 100, 130 Series	9.20	<b>PHILIPS:</b> 170, 210, 300 series	9.20
<b>FERGUSON, THORN:</b> 1590, 1591	9.20	320 series	9.78
1690, 1691, built in rect.	9.78	TX, T8 mono	P.O.A.
1600, 1615, 1700 series	P.O.A.	G8 and G9 Series	9.20
1790 mono portable	P.O.A.	KT2, KT3, series colour	9.20
3000, 3500, 8000, 8500, 8800	P.O.A.	G11, K30, split diode	P.O.A.
9000, 9200, 9300 series	12.00	<b>BINATONE:</b> 9909, 9798, 9860	P.O.A.
9500, 9600, 9650 series	10.99	<b>DORIC</b> Mk3	11.50
9800, TX9, TX10 series	P.O.A.	<b>FINLUX</b> 9560, 9670	P.O.A.
<b>MOVIESTAR</b> 3781, 3787	12.00	<b>GRUNDIG:</b> most models in stock	
<b>FIDELITY:</b> FTV12 mono	10.35	<b>NORDMENDE:</b> FC125, Z206, Z306	11.50
CTV14R, CTV14S colour	15.83	<b>SANYO:</b> 5101, 5103, 7118, 7130	P.O.A.
<b>G.E.C.</b> 2047 to 3135 mono	9.20	<b>SHARP:</b> C1851H, C2051H	P.O.A.
1201H, 1501H, 2114, 3133, 3135	9.20	<b>TOSHIBA:</b> C800, C800B	19.45
DUAL & SINGLE hybrid col.	10.00	<b>TANDBURG:</b> 190, CTV2-2, CTV3-3 P.O.A.	
SINGLE STD solid state	12.00	<b>TELEFUNKEN:</b> most models in stock	
SINGLE STD split diode	P.O.A.	<b>LINE OUTPUT TESTER</b>	16.79
<b>INDESIT:</b> 24EGB hybrid	9.50		
12LGB, 12SGB mono portables	10.35		
<b>WINDINGS</b>			
<b>TYNE:</b> main winding	6.80		
<b>RBM:</b> T20, T22, T26, Z179	6.33		
<b>WALTHAM:</b> W125 eht winding	2.37		
<b>WALTHAM:</b> W190, W191 eht coil	£6.00		
<b>KORTING:</b> hybrid winding	6.90		

**Tidman Mail Order Ltd.,**  
 236 Sandycombe Road,  
 Richmond, Surrey.  
 Approx. 1 mile from Kew Bridge.  
 Phone: 01-948 3702  
 Mon-Fri 9 am to 12.30 pm &  
 1.30-4.30 pm  
 Sat 10 am to 12 noon.

(7) From the present time all commercial users will be charged at a business rate for diagnostic/remedial work.

If there is sufficient demand, the RIS may provide training courses in interference location and correction.

These changes mark a profound alteration to a service that's been available for many years. Weak-signal enthusiasts will in future have to carry out much more investigative work themselves. Rectification of mains-operated equipment causing interference must be carried out by qualified and experienced personnel, but location of many sources of interference can be carried out using a cheap a.m. v.h.f. air-band portable with its whip aerial, by gradually closing the whip as one gets closer to the source.

We're always interested in hearing about readers' interference problems – and any solutions devised. Notes on this subject may well be featured in future columns.

### **From our Correspondents . . .**

Jeremy Cecil of Shoreham has written to tell us of his experiences as a DXer over some twenty years. He commenced TV-DXing with a rented TV set and 13-channel turret tuner, using a home-made double eleven-element Band III array with adjustable polarity via four parachute strings. This gave such 405-line memorabilia as St. Hilary, Lichfield and Emley Moor, plus at times 819-line signals from RTF (France). He found that reception of long-haul signals was often best with polarisation of other than the correct (transmitted) type – his infinitely variable polarisation system was obviously most effective (has anyone any comments on this polarisation shift?).

His experiments continued until 1977 when he married and moved to Portslade, some seven metres a.s.l., where he concentrated on reliable daily reception of Caen using a single 21-element group A Yagi which cost all of £2.19s.6d! In 1981 he acquired a PAL/SECAM Grundig set able to receive B/G/I/L standard transmissions, a Fuba XC391 u.h.f. array and a three-element wideband Trumatch Band I array. In addition a VCR with system L capability was acquired. He also uses a Philips VR2120 (2000 system) machine that works well in terms of stability with deep fading signals – unlike the VHS machine.

He's at present using a Salora Model J60/90, an all singing/dancing set with system B/G/I/L/D capability, plus teletext and stereo sound, giving v.h.f. coverage from 45-300MHz and slightly extended u.h.f. coverage. Teletext DX reception has been successful and Jeremy is seeking any comments on real-time and recorded teletext recovery. As a result of ill health Jeremy has now retired, but his DX-TV activities provide him with a full and satisfying hobby. We wish him the best of luck with future reception.

### **US Satellite TV**

As mentioned briefly last month, Frank Lumen of Denver, Colorado paid us a short visit recently. He had much of interest to tell us about the satellite TV scene there. Readers may recall that we showed a shot of his dish last December (page 95). Frank is now using an 85°K LNA feeding a Luxor (Swedish) 4GHz satellite receiver, his interest having drifted from v.h.f. DX-TV because of the large number of high-power local transmitters that can be received at his location, leaving few channels open for DXing.

Satellite TV has become big business in the USA as viewers seek alternatives to their normal programmes. Over 15,000 dealers attended the recent Las Vegas SPACE/STTI trade show where over 600 dish aerials were

on display. Services at 4GHz are seen as the growth market, with an estimated sale of some 600,000 units this year. Two problems are beginning to arise for satellite TV viewers however. First, zoning (planning) control – local authorities are beginning to take an interest in large dishes in suburban back yards. Secondly there's the prospect of programme scrambling. The 4GHz satellites were originally intended for programme distribution to cable networks, the cable operators paying for the programme material they received and put out over their networks. The explosion in 4GHz TVRO installations means that there's no check on who is actually watching, a situation with which the programme companies are not exactly happy – hence the likelihood that scrambling will be increasingly used.

The many US satellite TV magazines are full of advertisements for dishes, LNAs, LNBs, receivers, feedhorns, actuators and even dish surface warming elements (to prevent snow/ice build up, dish distortion and thus reduced gain). Many include programme guides. There is generally 4° spacing between satellites, but with the shortage of orbital space 2° spacing is being suggested. This will introduce problems where smaller dishes are used since these tend to have a beamwidth of 2° at –3dB: sidelobes will add to the possibilities of adjacent satellite interference. Dishes start at 5ft in diameter: most of those sold are in the 6-10ft range but dishes are available at up to 30ft diameter.

The large number of satellites that can be received means that computer control of the aerial is desirable. You pre-programme the computer with the positions and polarities of your favourite satellite transponders then just push the button and the dish swings to the appropriate position, adjusting the polariser for either vertical or horizontal polarisation. The market has reached the stage where discount satellite outlets are being opened.

Many of the domestic US satellites (DOMSATS) have up to 24 downlink transponders with output powers of 8-10W. With such a large number so the programming is comprehensive, from popular sit-coms to specialised language programmes for ethnic majorities and of course not forgetting prime-time movie channels. As an example of ethnic programming, RAI-TGI (Italian TV news) is uplinked via a N. American Intelsat bird and downlinked via Satcom 1, giving US-wide RAI though the programme was originally intended for a community in New York. Frank views ITN news (News at One, News at 5.45) which is again Intelsat uplinked then cross linked via Satcom 1 from New York to Los Angeles where a further Pacific link takes it to TCN9 Sydney. The signals Frank receives have PAL colour and 625 lines.

Frank can receive signals from 19 satellites at his Denver home. With anything up to 20 downlinks on some of these craft Frank reckons that 150 channels are available to him for viewing with acceptable quality. His future plans include a lower noise LNA, possibly down to 65°K, and resiting his dish so that it can see several Atlantic ocean satellites which are at present obscured by a neighbour's house. With prices for complete systems starting at \$1,000 for a system with 6ft dish and 100°K LNA one can readily appreciate how satellite viewing has grown as both a hobby and a source of home entertainment. With a mass of equipment that can be merely plugged in (your friendly local satellite dealer will install) no technical knowledge is required apart from the need to be able to programme the dish control system.

We hope to include some photos of reception next month.

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a £1.50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## FERGUSON 3V29

The problem is loss of colour on playback. Colour is present to start with but fades when the machine has warmed up. Checks around the AN6360 colour signal processing chip revealed that pin 16 is 6.3V instead of 1.4V, but fitting a replacement chip has made no difference.

It looks as if either the coupling capacitor C415 (120pF) between pins 16 and 17 of the i.c. is defective or that the burst gating pulse at pin 4 is missing or low in amplitude. This pulse gates the burst to provide the a.c.c. action. Suspects are L407 (5.6 $\mu$ H), C441 (0.012 $\mu$ F), C440 (1 $\mu$ F) and IC402 (AN6362) in that order, plus all the tubular pink capacitors in this part of the circuit. Use of freezer and a hairdryer should localise the component responsible.

## HITACHI CNP190

There are two faults on this set. First excessive ballooning when the brightness is turned up. Secondly retuning is necessary every ten-fifteen seconds. The latter condition is present whether the set is warm or cold and applies to all buttons.

The tuning control assembly used in these sets gives a lot of trouble. A replacement four-button unit can be obtained from Hitachi or wholesalers such as HRS and SEME and may well solve the problem. If not the tuner is suspect. For the ballooning, check the h.t. voltage as the brightness control is adjusted. If it varies, suspect the series regulator transistor TR41 and its control circuit, especially the zener diode CR40. If the h.t. remains steady, suspect the e.h.t. rectifier circuit which is inside the line output transformer assembly.

## ITT CVC32 CHASSIS

A month after fitting a new line output transformer the EW correction transformer L22/3 burnt up and the driver transistor T13 failed. These items were replaced with the correct types but two days later they again failed following the appearance of centre line foldover. No obvious faults can be found in this area.

The trouble can be caused by intermittent failure of one of the capacitors in this part of the circuit. Suspects are C65 (EW tuning), C68/69 (scan correction) and C70 (T13 collector supply filtering). Ensure that the replacement EW correction transformer is fitted the right way round.

## DECCA 100 CHASSIS

A fault in the line output stage keeps blowing the mains fuse. To start with there was what looked like loss of EW drive (bowing at the sides). A few weeks later the fuse blew

and the BU208A line output transistor was found to be short-circuit. The line drive waveform is correct but the set will operate for only a fraction of a second before ruining the BU208A. A new line output transformer has been fitted and no obvious faults can be found on the line output panel.

The e.h.t. tripler could well be at fault, loading the line output stage. Check by disconnecting it. If the problem persists, ensure that no reverse leakage can be measured in the EW modulator diodes D401 and D402. If these are o.k. the EW correction transformer T402 could be in trouble: the only way to check it is by substitution.

## PHILIPS G8 CHASSIS

There's intermittent ballooning which lasts for only a fraction of a second. It occurs every few seconds and is sometimes more pronounced than at other times.

The problem is probably due to an h.t. voltage fluctuation, but a scope will be required to confirm this – a meter will not respond quickly enough. The BT106 mains rectifier thyristor could be responsible but the BR100 trigger diac is a more likely suspect. The 4EX581 is a more reliable replacement which will work only one way round: if you fit one, change R1382 to 47 $\Omega$ . Also make sure that the set-h.t. control R1370 is in good condition and working smoothly.

## SONY KV1810UB

The display consists of three separate rasters displaced from each other by about one and a quarter inches. Disconnect the red and blue drives and you get a perfectly centred, linear green picture. Reconnect red and a second, impure green picture appears to the left of centre. The picture produced by the blue gun is to the right of centre.

The effect is tied up with the convergence voltage that's passed to the c.r.t.'s button connector along with the e.h.t. The e.h.t. lead and tube connector are both coaxial types. Remove the e.h.t. cap carefully and check the central spring and claw connector. If these are in order and not shorted, and adjustment of the static convergence control (mounted on the tripler) doesn't eliminate the problem, a new tripler assembly will be required.

## TOSHIBA V9600

The rewind is at first sluggish, then ceases. The counter turns slower and slower and finally stops. The fault has become progressively worse over a period of months though some tapes rewind satisfactorily. I suspect the rewind idler clutch assembly – would you agree with this suggestion?

The problem is unlikely to be in the reel drive mechanism: excessive friction in the tape path is more likely.

## QUERY COUPON

**Available until 16th October 1985.  
One coupon, plus a £1.50 (inc. VAT)  
cheque or postal order, must accom-  
pany EACH PROBLEM sent in accor-  
dance with the notice printed above.**

TELEVISION OCTOBER 1985

First check the voltage across the reel motor (pins 1 and 3 of connector P611 on the servo/syscon/audio panel). This should be at least 11V: if not, replace the two Darlington drive transistors Q636 and Q640. If this check proves o.k., replace the upper drum assembly above the video heads – the fault is almost certainly due to the tape sticking to the surface of this assembly. Toshiba changed the type of alloy used for this, so a replacement will provide a permanent cure. Some improvement can be achieved by removing the assembly and scouring the surface with fine steel wool used wet. When replacing it, make sure that the surface is hard up against the vertical locating post: take care not to disturb any spacers fitted and to avoid damage to the heads themselves.

# TEST CASE

274

*Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.*

The most common fault with the Sony C5, C6 and C7 series VCRs is failure to rewind as a result of problems in the friction-drive system for the feed spool turntable. So when a C7 arrived in the workshop with the complaint that it “sometimes fails to rewind” we weren’t expecting any great challenge to our intellect!

After confirming with a known good prerecorded tape that the video heads were in reasonable condition we dismantled the cassette cradle and fitted the rewind modification kit. This was the work of a few minutes (we’ve had plenty of practice) and within another twenty minutes the deck had been serviced – heads cleaned, tensions checked, guide alignment tested and so on. In went an L750 tape to record a test card while we wrote out the invoice. That completed it remained only to replay the recording as a test before wrapping up the job.

Pressing the rewind button stopped the tape transport system but did nothing to wind the tape back. The fast-forward mode worked correctly, as did the cue (search forward) function. The tape wouldn’t reverse on selecting review, and it soon became apparent that this had nothing to do with the mechanics of the reel-drive system – which had just been renewed anyway.

It seemed obvious that the cause of the trouble lay in the tape-end sensor system, the likelihood being that it was falsely signalling “end-foil present” to the syscon department, thus inhibiting rewind. In Betamax machines the sensors take the form of ferrite-cored coils which are mounted close to the tape path. Their inductance falls considerably when the tape’s end-foil passes nearby, this

loading effect stalling an oscillator of which the sensor coil forms a part. When this happens a “high” signal passes to the syscon chip which then prevents tape transport in the prohibited direction.

The forward (left-hand side of the deck) and rewind sensors in the C7 use identical circuits, each built around a BX342 chip that contains an oscillator and a detector. In view of the intermittent nature of the fault we started by thoroughly checking for dry-joints in the relevant plugs, sockets and PCBs. Finding none, and with the fault becoming rarer, we had an inspiration: we interchanged the two BX342 chips so that if the suspect IC9 was responsible the fault would be transferred to the forward sensor department. It was fairly easy to transpose the two i.c.s, but when we’d done this the forward and rewind functions behaved perfectly!

The machine was set to run on test, with us thrashing the rewind and fast-forward buttons at frequent intervals. Nothing untoward happened until next morning, when the machine once again malfunctioned, shutting down halfway through a rewind cycle. So it wasn’t the chip! We’d taken the precaution of hooking an oscilloscope to the rewind sensor coil and were able to see the sinewave “twitter” and fall in amplitude before the syscon shut the show down. No amount of tapping, flexing, heating or cooling of the SY11 (syscon) or LS3 (junction) panels would instigate or settle the fault.

The next test we made established with certainty the faulty component, but in carrying it out we had to take certain precautions to forestall the murder of a tape cassette. What were they? And where lay the root of the evil? Fast forward to next month’s issue!

## ANSWER TO TEST CASE 273 – page 646 last month –

September’s puzzle was a mixture of nostalgia and recalcitrance! You’ll recall that the display obtained on a set fitted with the ITT VC200 hybrid monochrome chassis obstinately lacked width while there was some overheating of the large components in the line output stage. All likely and several unlikely suspects were fruitlessly checked before we were left wondering whether we’d have done better (and quicker) to exchange the whole chassis for the one in the scrap set.

Our approach in such cases however is “better the devil you know” – what evil faults, intermittent or otherwise, might have been lurking in the other well-worn chassis? In fact if we’d replaced it complete the fault would still have been present!

So what cabinet or tube mounted component could have been responsible? The deflection coils of course. There must have been short-circuit turns in the line section because swapping over the yokes produced a full-width raster, enabling us to reclaim most of the bits and pieces we’d fed into the falsely accused line oscillator and output stages. With normality restored to this vintage set, back to the problems associated with more recent equipment – see test case 274 alongside!

Published on approximately the 22nd of each month by IPC Magazines Limited, King’s Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (Asia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £13, overseas (surface mail) £15 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. “Television” is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

# CENTRAL T.V. & VIDEO WHOLESALER

UNTESTED		WORKING	
PHILIPS G11 .....	£30	PHILIPS G11 .....	£45
PHILIPS G8 550 22" .....	£8	PHILIPS G8 550 22" .....	£15
PHILIPS G8 520 22" .....	£6	PHILIPS G8 520 22" .....	£12
PHILIPS G8 560 20" .....	£18	PHILIPS G8 560 20" .....	£25
★★			
THORN TEXT 9650 .....	£45	THORN 9600 REMOTE .....	£40
THORN REMOTE 9600 .....	£30	THORN 9800 .....	£35
THORN 9800 .....	£25	THORN 9000 .....	£30
THORN 9000 .....	£20	THORN 8800 .....	£20
THORN 8800 .....	£14	THORN 8500 .....	£15
THORN 8500 .....	£10	THORN 3500 .....	£10
THORN VERYCAP 3500 .....	£5		
★★			
DECCA 80 .....	£20	DECCA 80 .....	£30
DECCA 88 .....	£30	DECCA 88 .....	£40
DECCA 100 .....	£25	DECCA 100 .....	£35
DECCA HYBRID .....	£5	DECCA HYBRID .....	£10
★★			
PYE 200 18" .....	£14	PYE 200 18" .....	£20
PYE CHELSEA 18" .....	£18	PYE CHELSEA 18" .....	£25
PYE 222 .....	£10	PYE 222 .....	£15
PYE 725 20" .....	£18	PYE 725 20" .....	£25
★★			
ITT SOLID STATE .....	£23	ITT SOLID STATE .....	£30
ITT FULL REMOTE .....	£50	ITT FULL REMOTE .....	£60
ITT HYBRID .....	£5	ITT HYBRID .....	£10
★★			
GEC 18"-20" IN-LINE .....	£20	GEC 18"-20" IN-LINE .....	£30
GEC SOLID STATE .....	£10	GEC SOLID STATE .....	£15
GEC 2201 .....	£18	GEC 2201 .....	£25
		JAP STOCK .....	£20

Prices based on quantity and are +15% VAT. Large stocks of Audio B. Grade.

## LATE MODEL VIDEO SOFT TOUCH – REMOTE

**B. GRADE T.V.'s 22"-20" TEXT, 20"-22"-26" REMOTE,  
14" BRAND NEW IN BOX £110**

**22" STEREO-TEXT BRAND NEW IN BOX WITH STAND £270  
ALSO 20 20 PHILIPS VIDEO £30 WORKING**

**HOTE LINE LONDON**

**01-807 4090**

**01-884 1314**

**CEDAR HOUSE, NOBLE RD.,  
ELEY ESTATE,  
EDMONTON, LONDON**

**HOT LINE**

**0291-271000**

**UNIT 4**

**BULWARK INDUSTRIAL ESTATE,  
CHEPSTOW,  
GWENT**

# TRAINING COURSES

## TELEVISION & VIDEO SERVICING

THESE FULL-TIME COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

### VIDEO CASSETTE RECORDER SERVICING 6 WEEKS FULL-TIME

(September 16th to October 25th)

Intensive course intended for qualified television service engineers or applicants with similar background.

The course combines the advantages of industrial and academic training and includes a high percentage of practical work.

Selected applicants will be eligible for a full grant from MSC under TOPS to cover tuition fees and maintenance.

### 6 MONTHS

#### LEC DIPLOMA

#### TELEVISION & VIDEO SERVICING

(Suitable for applicants with previous electronics training - e.g. BSC, HND, CGLI, B/TEC, etc.)

(Course commences on Sept. 16th)

### ADDITIONAL FULL-TIME COURSES APPROVED BY THE BUSINESS & TECHNICIAN EDUCATION COUNCIL

(These courses commence on Sept. 16th)

#### 2 YEAR

#### BTEC National Diploma (OND)

#### ELECTRONIC &

#### COMMUNICATIONS ENGINEERING

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

#### 15 MONTHS

#### BTEC National Certificate (ONC)

#### ELECTRONIC EQUIPMENT SERVICING

(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

#### 15 MONTHS

#### BTEC National Certificate (ONC)

#### COMPUTING TECHNOLOGY

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

#### 9 MONTHS

#### BTEC Higher National Certificate (HNC)

#### COMPUTING TECHNOLOGY & ROBOTICS

(Microprocessors, Microcomputer Fault Diagnosis, Robotics & Control Systems, CAD/CAM & CAE Principles).

OVERSEAS STUDENTS ARE CHARGED THE SAME TUITION FEES AS UK STUDENTS

Full Prospectus from:

**LONDON ELECTRONICS COLLEGE (Dept TF)**  
20 PENYVERN ROAD, EARLS COURT,  
LONDON SW5 9SU. Tel: 01-373 8721

### OSCILLOSCOPES

COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual ..... £200  
S.E. LABS SM111. Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual ..... £150  
ADVANCE OS250TV. Dual Trace 10MHz. With Manual. .... £150  
TEKTRONIX 547 DUAL TRACE 50MHz Dual TB. Delay Sweep. With Manual. .... £140  
TELEQUIPMENT D43. Dual Trace 15MHz. With Manual. .... £100

### PHILIPS DIGITAL MULTIMETERS

4 digit, auto ranging. Complete with batteries and leads (p&p £5)  
TYPE PM2517E (LED) ..... £75  
TYPE PM2517X (LCD) ..... £95

### MULTIMETERS

UNBELIEVABLE - AVO 8 Mk IV and AVO 9 Mk IV, complete with batteries & leads. FOR ONLY £65  
AVO TEST SET No 1 (Similar to Avo8 Mk3). Complete with batteries, leads & carrying case £80  
AVO Model 7x. Complete with batteries, leads & carrying case ..... £40  
AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads ..... £25  
AVO 72 - Similar to above but no AC current range. With batteries & leads ..... £18

AVO TRANSISTOR ANALYSER CT446. Suitcase style - battery operated (batteries not supplied). With Information ONLY £20 EACH

AVO TRANSISTOR TESTER TT169 Handheld. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12

MARCONI RF MILLIVOLTMETER TF2603 50KHz-1500MHz; 1mV-3V. FSD ..... £175

MARCONI ELECTRONIC VOLTMETER TF2604 20Hz-1500MHz; AC/DC/Ohms AC300mV-300V. FSD ..... £95

MARCONI VALVE VOLTMETER TF2600 10Hz-10MHz; 1mV-300V. FSD ..... £40

### NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605 Dual Trace 60MHz. Delay Sweep. Component Tester ..... £115  
HAMEG OSCILLOSCOPE 203.5 Dual Trace 20MHz. Component Tester ..... £70

BLACK STAR FREQUENCY COUNTERS P&P £4  
Meteor 100-100MHz ..... £99  
Meteor 600-600MHz ..... £126  
Meteor 1000-1GHz ..... £175  
BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 ..... £110

HUNG CHANG DMM 6010 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4 ..... £33.50  
MULTIMETER type U4324. 33 ranges. Complete with batteries and leads. P&P £4 ..... £16

OSCILLOSCOPES PROBES. Switched x1; x10. P&P £2 ..... £11

ADVANCE AM/FM Signal Generator type SG63. 7.5-230MHz ..... £75

ADVANCE AM Signal Generator type 62. 150KHz-220MHz ..... £35

METRIX WOBBLATOR type 210. 5-220MHz ..... £20

LABGEAR COLOUR BAR GENERATOR. CM6037 ..... £60 P&P £2

LABGEAR CROSSHATCH GENERATOR. CM6004 ..... £15 P&P £2

LABGEAR CROSSHATCH GENERATOR. CM6038. Input 240V AC or 6V DC ..... £25 P&P £2

WAYNE KERR COMPONENT BRIDGE BS21 (CT375) L 100uH - 500KHz; C 1pF - 5F; R 1 milliohm - 1000 Mohm ..... £35

HUNTS CAPACITANCE ANALYSER & RESISTANCE BRIDGE type CR38 ..... £20 P&P £7

LABGEAR DEGAUSSER COILS E5186 £10 P&P £3

PROFESSIONAL 9" GREEN SCREEN MONITORS made by KGM for REUTERS Gives quality 80 column x 24 line display. Composite video in. Cased. Good condition ONLY £40 each

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total of Goods & Carriage. Please allow 21 days for delivery.

### STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: 0734 68041



Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive



# CLEARANCE SALE

## Massive Savings

### TELEVISION

Secondhand and ex rental. Many to clear at **£5** and **£10**.

New but faulty or marked remote control Teletext from only **£90**.

### AUDIO

Music centres, Hi-Fi, Radios, Cassettes, etc., etc.

Many to choose from.

### VIDEOS

#### VHS and SONY

Several models and types at various prices. Stocks are constantly changing.

Please phone now for further details:

### COLOURTRADE

221, Bridge St. West, Hockley, Birmingham, B19 2YU.

Telephone 021-359 0449



AA117	9p	BC337	6p	BF184	20p	BFY57	25p	TP32A	24p	2N1131	28p	BY296	20p	7818	35p	PCL805	55p	LA4661	180p	TBA560	100p	74LS22	17p
AA119	9p	BC338	6p	BF185	20p	BFY58	25p	TP32B	24p	2N1132	28p	BY297	20p	7819	35p	PCL806	55p	LA5112	120p	TBA750	100p	74LS24	38p
AA132	9p	BC339	6p	BF186	20p	BFY59	25p	TP32C	24p	2N1133	28p	BY298	20p	7820	35p	PCL807	55p	LA3001	28p	TBA800	35p	74LS26	17p
AC107	28p	BC340	6p	BF187	20p	BLY48	85p	TP32D	24p	2N1134	28p	BY299	20p	7821	35p	PL2	40p	LM311	35p	TBA810S	60p	74LS27	17p
AC126	17p	BC341	6p	BF188	20p	BLY49	85p	TP41A	22p	2N1210	50p	BY300	20p	7822	35p	PL3	32p	LM324	35p	TBA820	75p	74LS28	17p
AC127	25p	BC342	6p	BF189	20p	BR100	14p	TP41C	25p	2N2160	300p	BY301	20p	7823	35p	PL4	40p	LM325	45p	TBA830	100p	74LS30	17p
AC128	15p	BC343	6p	BF190	20p	BR101	14p	TP42A	25p	2N2218A	14p	BY302	20p	7824	35p	PL5	50p	LM326	45p	TBA840	100p	74LS32	17p
AC128K	23p	BC344	6p	BF191	20p	BR102	14p	TP42B	25p	2N2219	24p	BY303	20p	7825	35p	PL6	40p	LM327	45p	TBA850	100p	74LS33	17p
AC141K	30p	BC345	6p	BF192	20p	BSX20	15p	TP47	40p	2N2221	23p	BY304	20p	7826	35p	PL7	40p	LM328	45p	TBA860	100p	74LS34	17p
AC142K	30p	BC346	6p	BF193	20p	BSX26	18p	TP48	40p	2N2222	23p	BY305	20p	7827	35p	PL8	40p	LM329	45p	TBA870	100p	74LS35	17p
AC153K	23p	BC347	6p	BF194	20p	BSX27	18p	TP49	40p	2N2223	23p	BY306	20p	7828	35p	PL9	40p	LM330	45p	TBA880	100p	74LS36	17p
AC176K	20p	BC348	6p	BF195	20p	BT109	90p	TP51	120p	2N2484	20p	BY307	20p	7829	35p	PL10	40p	LM331	45p	TBA890	100p	74LS37	17p
AC176	18p	BC349	6p	BF196	20p	BT110	90p	TP52	120p	2N2486	20p	BY308	20p	7830	35p	PL11	40p	LM332	45p	TBA900	100p	74LS38	17p
AC176K	20p	BC350	6p	BF197	20p	BT111	90p	TP53	120p	2N2488	20p	BY309	20p	7831	35p	PL12	40p	LM333	45p	TBA910	100p	74LS39	17p
AC187	15p	BC351	6p	BF198	20p	BT112	90p	TP54	120p	2N2490	20p	BY310	20p	7832	35p	PL13	40p	LM334	45p	TBA920	100p	74LS40	17p
AC187K	20p	BC352	6p	BF199	20p	BT113	90p	TP55	120p	2N2492	20p	BY311	20p	7833	35p	PL14	40p	LM335	45p	TBA930	100p	74LS41	17p
AC188	17p	BC353	6p	BF200	20p	BT114	90p	TP56	120p	2N2494	20p	BY312	20p	7834	35p	PL15	40p	LM336	45p	TBA940	100p	74LS42	17p
AC188K	23p	BC354	6p	BF201	20p	BT115	90p	TP57	120p	2N2496	20p	BY313	20p	7835	35p	PL16	40p	LM337	45p	TBA950	100p	74LS43	17p
AC191	48p	BC355	6p	BF202	20p	BU100A	110p	TP106	65p	2N2907	18p	BY314	20p	7836	35p	PL17	40p	LM338	45p	TBA960	100p	74LS44	17p
AD142	60p	BC356	6p	BF203	20p	BU101	110p	TP107	65p	2N2926	8p	BY315	20p	7837	35p	PL18	40p	LM339	45p	TBA970	100p	74LS45	17p
AD149	45p	BC357	6p	BF204	20p	BU102	110p	TP108	65p	2N2928	8p	BY316	20p	7838	35p	PL19	40p	LM340	45p	TBA980	100p	74LS46	17p
AD161	22p	BC358	6p	BF205	20p	BU103	110p	TP109	65p	2N2930	8p	BY317	20p	7839	35p	PL20	40p	LM341	45p	TBA990	100p	74LS47	17p
AF124	22p	BC359	6p	BF206	20p	BU104	110p	TP110	65p	2N2932	8p	BY318	20p	7840	35p	PL21	40p	LM342	45p	TBA1000	100p	74LS48	17p
AF125	25p	BC360	6p	BF207	20p	BU105	110p	TP111	65p	2N3053	18p	BY319	20p	7841	35p	PL22	40p	LM343	45p	TBA1010	100p	74LS49	17p
AF126	25p	BC361	6p	BF208	20p	BU106	110p	TP112	65p	2N3054	18p	BY320	20p	7842	35p	PL23	40p	LM344	45p	TBA1020	100p	74LS50	17p
AF127	25p	BC362	6p	BF209	20p	BU107	110p	TP113	65p	2N3055	18p	BY321	20p	7843	35p	PL24	40p	LM345	45p	TBA1030	100p	74LS51	17p
AF128	25p	BC363	6p	BF210	20p	BU108	110p	TP114	65p	2N3056	18p	BY322	20p	7844	35p	PL25	40p	LM346	45p	TBA1040	100p	74LS52	17p
AF129	25p	BC364	6p	BF211	20p	BU109	110p	TP115	65p	2N3058	18p	BY323	20p	7845	35p	PL26	40p	LM347	45p	TBA1050	100p	74LS53	17p
AF130	22p	BC365	6p	BF212	20p	BU110	110p	TP116	65p	2N3442	85p	BY324	20p	7846	35p	PL27	40p	LM348	45p	TBA1060	100p	74LS54	17p
AF131	22p	BC366	6p	BF213	20p	BU111	110p	TP117	65p	2N3443	85p	BY325	20p	7847	35p	PL28	40p	LM349	45p	TBA1070	100p	74LS55	17p
AF132	22p	BC367	6p	BF214	20p	BU112	110p	TP118	65p	2N3444	85p	BY326	20p	7848	35p	PL29	40p	LM350	45p	TBA1080	100p	74LS56	17p
AF133	22p	BC368	6p	BF215	20p	BU113	110p	TP119	65p	2N3445	85p	BY327	20p	7849	35p	PL30	40p	LM351	45p	TBA1090	100p	74LS57	17p
AF134	22p	BC369	6p	BF216	20p	BU114	110p	TP120	65p	2N3446	85p	BY328	20p	7850	35p	PL31	40p	LM352	45p	TBA1100	100p	74LS58	17p
AF135	22p	BC370	6p	BF217	20p	BU115	110p	TP121	65p	2N3447	85p	BY329	20p	7851	35p	PL32	40p	LM353	45p	TBA1110	100p	74LS59	17p
AF136	22p	BC371	6p	BF218	20p	BU116	110p	TP122	65p	2N3448	85p	BY330	20p	7852	35p	PL33	40p	LM354	45p	TBA1120	100p	74LS60	17p
AF137	22p	BC372	6p	BF219	20p	BU117	110p	TP123	65p	2N3449	85p	BY331	20p	7853	35p	PL34	40p	LM355	45p	TBA1130	100p	74LS61	17p
AF138	22p	BC373	6p	BF220	20p	BU118	110p	TP124	65p	2N3450	85p	BY332	20p	7854	35p	PL35	40p	LM356	45p	TBA1140	100p	74LS62	17p
AF139	22p	BC374	6p	BF221	20p	BU119	110p	TP125	65p	2N3451	85p	BY333	20p	7855	35p	PL36	40p	LM357	45p	TBA1150	100p	74LS63	17p
AF140	22p	BC375	6p	BF222	20p	BU120	110p	TP126	65p	2N3452	85p	BY334	20p	7856	35p	PL37	40p	LM358	45p	TBA1160	100p	74LS64	17p
AF141	22p	BC376	6p	BF223	20p	BU121	110p	TP127	65p	2N3453	85p	BY335	20p	7857	35p	PL38	40p	LM359	45p	TBA1170	100p	74LS65	17p
AF142	22p	BC377	6p	BF224	20p	BU122	110p	TP128	65p	2N3454	85p	BY336	20p	7858	35p	PL39	40p	LM360	45p	TBA1180	100p	74LS66	17p
AF143	22p	BC378	6p	BF225	20p	BU123	110p	TP129	65p	2N3455	85p	BY337	20p	7859	35p	PL40	40p	LM361	45p	TBA1190	100p	74LS67	17p
AF144	22p	BC379	6p	BF226	20p	BU124	110p	TP130	65p	2N3456	85p	BY338	20p	7860	35p	PL41	40p	LM362	45p	TBA1200	100p	74LS68	17p
AF145	22p	BC380	6p	BF227	20p	BU125	110p	TP131	65p	2N3457	85p	BY339	20p	7861	35p	PL42	40p	LM363	45p	TBA1210	100p	74LS69	17p
AF146	22p	BC381	6p	BF228	20p	BU126	110p	TP132	65p	2N3458	85p	BY340	20p	7862	35p	PL43	40p	LM364	45p	TBA1220	100p	74LS70	17p
AF147	22p	BC382	6p	BF229	20p	BU127	110p	TP133	65p	2N3459	85p	BY341	20p	7863	35p	PL44	40p	LM365	45p	TBA1230	100p	74LS71	17p
AF148	22p	BC383	6p	BF230	20p	BU128	110p	TP134	65p	2N3460	85p	BY342	20p	7864	35p	PL45	40p	LM366	45p	TBA1240	100p	74LS72	17p
AF149	22p	BC384	6p	BF231	20p	BU129	110p	TP135	65p	2N3461	85p	BY343	20p	7865	35p	PL46	40p	LM367	45p	TBA1250	100p	74LS73	17p
AF150	22p	BC385	6p	BF232	20p	BU130	110p	TP136	65p	2N3462	85p	BY344	20p	7866	35p	PL47	40p	LM368	45p	TBA1260	100p	74LS74	17p
AF151	22p	BC386	6p	BF233	20p	BU131	110p	TP137	65p	2N3463	85p	BY345	20p	7867	35p	PL48	40p	LM369	45p	TBA1270	100p	74LS75	17p
AF152	22p	BC387	6p	BF234	20p	BU132	110p	TP138	65p	2N3464	85p	BY346	20p	7868	35p	PL49	40p	LM370	45p	TBA1280	100p	74LS76	17p
AF153	22p	BC388	6p	BF235	20p	BU133	110p	TP139	65p	2N3465	85p	BY347	20p	7869	35p	PL50	40p	LM371	45p	TBA1290	100p	74LS77	17p
AF154	22p	BC389	6p	BF236	20p	BU134	110p	TP140	65p	2N3466	85p	BY348	20p	7870	35p	PL51	40p	LM372	45p	TBA1300	100p	74LS78	17p
AF155	22p	BC390	6p	BF237	20p	BU135	110p	TP141	65p	2N3467	85p	BY349	20p	7871	35p	PL52	40p	LM373	45p	TBA1310	100p	74LS79	17p
AF156	22p	BC391	6p	BF238	20p	BU136	110p	TP142	65p	2N3468	85p	BY350	20p	7872	35p	PL53	40p	LM374	45p	TBA1320	100p	74LS80	17p
AF157	22p	BC392	6p	BF239	20p	BU137	110p	TP143	65p	2N3469	85p	BY351	20p	7873	35p	PL54	40p	LM375	45p	TBA1330	100p	74LS81	17p
AF158	22p	BC393	6p	BF240	20p	BU138	110p	TP144	65p	2N3470	85p	BY352	20p	7874	35p	PL55	40p	LM376	45p	TBA1340	100p	74LS82	17p
AF159	22p	BC394	6p	BF241	20p	BU139	110p	TP145</															

CAPACITORS		INTEGRATED CIRCUITS		SPECIFIC COMPONENTS		PUSH BUTTON UNITS		SMOOTHING CAPACITORS		TRANSISTOR/DIODES	
91 5 x .0047/1500 AB23	68 Grundig 3010/1500 3.00	140 5 x TDA440 3.00	179 TDA2532 2.40	351 Thorn 1591	110 Pye 713 4 Way 7.87	80 220/400 CVC32/T20 1.20	030 GEC 2100 Hybrid 4.00	81 200+300 Pye 691 2.00	390 G8 Metal Mains Switch 1.23	230 10 x AC128 1.50	460 ELC1043/06 Tuner 6.00
Chassis 1.50	69 Thorn 3500 7.50	141 5 x TBA120AS 1.80	180 TDA2540 1.85	Speaker 2.00	111 Pye 715 6 Way 11.95	82 600/300 Phil G8 1.90	032 Thorn T x 9 Chass. 14.50	83 175+100+100 T3500 1.50	391 G8 Line Stor/Equ. Coil 2.25	235 50 x BC213L 2.50	461 U321 New Tuner 7.95
92 10 x 220MFD 16V	70 Thorn 3500 5.40	142 5 x TBA540 4.00	181 TDA2541 2.67	352 Thorn 1600	112 Phil G8 Square 12.75	84 2000/100 Volt 0.50	033 Philips KT3 8.00	85 470 Mid G11 1.50	392 G8 R/G Symmetry Coil 3.33	250 10 x BD124 9.00	462 U322 New Tuner 7.95
Elect 0.50	71 Philips G8 6.30	143 5 x TBA540Q 4.00	182 TDA2560 3.28	Dropper 0.50	113 Phil G8 Sloping 14.98	86 400+400 Decca 30 2.50	034 RRI T24 Chass. 14.00	87 200+200+75+25 ITT CVC5/9 1.50	393 20 x 3.15A A/S 20mm Fuse 1.50	251 10 x BD131 1.60	463 98003 Posister 0.99
93 10 x .047MFD 400V	72 Pye 731 4.50	144 5 x TBA560 3.50	183 TDA2571 2.15	353 T x 10 Preset Drawer 3.00	114 Thorn 9000 2.50	88 400/400V Tho 9000 1.50	035 Sanyo CTP5101 9.50	89 4700/25 Thorn 1590/91 0.60	394 20 x 2.5A A/S 20mm Fuse 1.40	252 10 x BU208A 8.50	464 98009 Posister 0.99
Mul Pol 0.50	73 Pye 731 4.50	145 5 x TBA560 3.50	184 TDA2591 0.98	354 T x 10 CRT Base Assy 4.00	115 Thorn 1615 4 Way 7.87	89 4700/25 Thorn 1590/91 0.60	036 Sanyo CTP5101 9.50	90 4700/25 Thorn 1590/91 0.60	395 5 x 15R Phil. G8 Conv. Pot. 2.40	270 10 x BU208A 8.50	465 Multi.DL50 Delay Line 0.95
94 5 x 4.7/100V C514 T3500 1.25	74 Pye 731 4.50	146 5 x TBA810S 3.00	185 TDA2593 2.23	355 3" Round BR Speaker 1.00	116 Decca 6 Way 6.95		037 Split Diode EHT Lead 1.35		396 20 x 800MA A/S 20mm Fuse 1.50	271 10 x BU208 7.50	466 5 x VA1104 2.70
95 5 x .47/1000	75 Pye 731 4.50	147 5 x TBA920Q 4.00	190 TDA2600 1.25	358 5 x Tho/3500 200 Conv. Pot. 1.00	117 Decca 4 Way 6.50				397 20 x 2.5A A/S 20mm Fuse 1.40	272 10 x BU326 10.00	469 Cut Out Metal GEC 2100 1.00
Dublier 1.00	76 Pye 731 4.50	148 5 x TBA990 3.25	191 TDA2611 4.94	359 5 x Tho/3500 50R Conv. Pot. 1.00	118 GEC 2110 6 Way 7.95				398 20 x 1.25A A/S 20mm Fuse 1.40	273 5 x BU205 3.75	470 5 x GEC2100 3 Leg Thermist. 1.00
97 10 x 0.1/2000V W/E 2.00	77 Pye 731 4.50	149 5 x TBA520Q 4.00	192 TDA2640 2.35	360 5 x TCE3500 A1 Rectifier 0.75	119 GEC 2136/7 Tapered 7.95				400 20 x 2A A/S 20mm Fuse 1.40	274 10 x BU326 10.00	475 5 x Gen. Purp. Rotary Switch. 3.60
98 5 x 1/250 Supp ITT etc. 1.50	78 Pye 731 4.50	150 5 x TBA530 4.25	193 TDA2640 2.35	362 T9000 Rem. Receive Assy 5.00	120 ITT CVC5 9.25				401 20 x 1A A/S 20mm Fuse 1.40	275 5 x BU205 3.75	480 5 x Gen. Purp. Push/Switch. 3.75
	79 Pye 731 4.50	151 5 x TBA950 4.50	194 TDA2660 1.25	363 T3500 Mains TX 5.00	121 ITT CVC8 11.45				402 20 x 1.25A A/S 20mm Fuse 1.40	276 10 x BU205 3.75	481 20 x Neons GEC etc. 2.25
	80 Pye 731 4.50	152 10 x TCA270SQ 4.00	195 TDA2660 1.25	364 T8500 Mains TX 7.50	122 ITT 6 Way with V.C.R. 7.95				403 5 x RRI T20 Tube Base 4.35	277 10 x BU205 3.75	482 5 x Univ. Aerial Skt. Kit 5.50
	81 Pye 731 4.50	153 5 x MC1327Q 1.50	196 TDA2660 1.25	365 T8500 (PLastic) Cut Out 1.50	123 RRI A823 etc. 7.95				404 Phil. G11 E/W Load/Coil 1.50	278 10 x BU205 3.75	483 10 x Metal Coax Plug 1.70
	82 Pye 731 4.50	160 TDA1170 2.35	197 TDA2660 1.25	370 Pye 731 Thick Film Resis. 1.50	124 Hitachi 4 Way 7.95				405 Phil. G11 Bridge TX 1.50	279 10 x BU205 3.75	484 Focus Unit 1.20
	83 Pye 731 4.50	161 TDA1190 1.90	198 TDA2660 1.25	371 Pye 731 Vis. Gain Mod. 6.50	125 RRI T20 6 Way 8.95				406 Phil. G11 Bridge TX 1.50	280 25 x 2N3055 (Texas) 7.50	485 Foc/Unit Thorn 8500 Type 1.25
	84 Pye 731 4.50	162 TDA1006A 1.45	199 TDA2660 1.25	372 Pye 731 3R3 50W Metal cid. 1.29					407 Decca 30 47k Vol.+ Switch 1.25	281 10 x 2N2905 (Equip. BC161/303) 0.50	486 4.43MHz Crystal 1.50
	85 Pye 731 4.50	163 TDA1035 1.83	200 TDA2660 1.25	373 100Kx3 Drawer P'set Alt Pye 731 2.00					408 10 x Decca 30 10R Fusible 0.50	282 25 x 2N3055 (Texas) 7.50	487 10 x Ring Type Spk/Gap 1.50
	86 Pye 731 4.50	164 TDA1044 2.23	201 TDA2660 1.25	378 Grundig 5010/6010 Vid Mod. 4.00					409 TX10 Chass. Focus Unit 7.00	283 50 x BY127 Diodes 3.00	488 TX10 Chass. Focus Unit 7.00
	87 Pye 731 4.50	165 TDA1090 1.90	202 TDA2660 1.25	384 5 x 10R Phil. G8 Conv. Pot. 2.40					410 Phil. G11 Bridge TX 1.50	284 25 x TIP41A 6.50	489 TX10 Chass. Focus Unit 7.00
	88 Pye 731 4.50	166 TDA1190 1.90	203 TDA2660 1.25	385 5 x 15R Phil. G8 Conv. Pot. 2.40					411 Phil. G11 Bridge TX 1.50	285 50 x BY127 Diodes 3.00	490 1 x 10 Trimming Tool 1.00
	89 Pye 731 4.50	167 TDA1412 0.90	204 TDA2660 1.25	386 5 x Phil. G8 2kx2 Lin. Bright. 2.50					412 Phillips G11 Speaker 1.00	286 25 x TIP41C 7.00	
	90 Pye 731 4.50	168 TDA2002 1.80	205 TDA2660 1.25	387 5 x Phil. G8 10k Lvs. Colour 2.50					413 10 x TDA2600 IC Holder 1.50		
	91 Pye 731 4.50	169 TDA2020 2.50	206 TDA2660 1.25	388 5 x Phil. G8 47k Lvs. Vol. 2.50					414 Phil. G11 Bridge TX 1.50		
	92 Pye 731 4.50	170 TDA2030 2.15	207 TDA2660 1.25	389 G8 Plastic Mains Switch 0.75					415 PALKT3 Speaker 15R 1.50		
	93 Pye 731 4.50	171 TDA2523 2.35	208 TDA2660 1.25						416 PALKT3 Speaker 10R 1.50		
	94 Pye 731 4.50	172 TDA2523 2.35	209 TDA2660 1.25						417 Decca 30 47k Vol.+ Switch 1.25		
	95 Pye 731 4.50	173 TDA2523 2.35	210 TDA2660 1.25						418 10 x Decca 30 10R Fusible 0.50		
	96 Pye 731 4.50	174 TDA2523 2.35	211 TDA2660 1.25						419 TX10 Chass. Focus Unit 7.00		
	97 Pye 731 4.50	175 TDA2523 2.35	212 TDA2660 1.25						420 25 x 2N3055 (Texas) 7.50		
	98 Pye 731 4.50	176 TDA2523 2.35	213 TDA2660 1.25						421 10 x 2N2905 (Equip. BC161/303) 0.50		
	99 Pye 731 4.50	177 TDA2523 2.35	214 TDA2660 1.25						422 25 x BT119 4.50		
	100 Pye 731 4.50	178 TDA2523 2.35	215 TDA2660 1.25						293 5 x BT120 4.50		
	101 Pye 731 4.50	179 TDA2523 2.40	216 TDA2660 1.25						335 50 x BY127 Diodes 3.00		
	102 Pye 731 4.50	180 TDA2540 1.85	217 TDA2660 1.25						340 25 x TIP41A 6.50		
	103 Pye 731 4.50	181 TDA2541 2.67	218 TDA2660 1.25						341 25 x TIP41C 7.00		
	104 Pye 731 4.50	182 TDA2560 3.28	219 TDA2660 1.25								
	105 Pye 731 4.50	183 TDA2571 2.15	220 TDA2660 1.25								
	106 Pye 731 4.50	184 TDA2591 0.98	221 TDA2660 1.25								
	107 Pye 731 4.50	185 TDA2593 2.23	222 TDA2660 1.25								
	108 Pye 731 4.50	190 TDA2600 1.25	223 TDA2660 1.25								
	109 Pye 731 4.50	191 TDA2611 4.94	224 TDA2660 1.25								
	110 Pye 731 4.50	192 TDA2640 2.35	225 TDA2660 1.25								
	111 Pye 731 4.50	193 TDA2640 2.35	226 TDA2660 1.25								
	112 Phil G8 Square 12.75	194 TDA2660 1.25	227 TDA2660 1.25								
	113 Phil G8 Sloping 14.98	195 TDA2660 1.25	228 TDA2660 1.25								
	114 Thorn 9000 2.50	196 TDA2660 1.25	229 TDA2660 1.25								
	115 Thorn 1615 4 Way 7.87	197 TDA2660 1.25	230 SL901B Int Circuit 5.00								
	116 Decca 6 Way 6.95	198 TDA2660 1.25									
	117 Decca 4 Way 6.50	199 TDA2660 1.25									
	118 GEC 2110 6 Way 7.95	200 TDA2660 1.25									
	119 GEC 2136/7 Tapered 7.95	201 TDA2660 1.25									
	120 ITT CVC5 9.25	202 TDA2660 1.25									
	121 ITT CVC8 11.45	203 TDA2660 1.25									
	122 ITT 6 Way with V.C.R. 7.95	204 TDA2660 1.25									
	123 RRI A823 etc. 7.95	205 TDA2660 1.25									
	124 Hitachi 4 Way 7.95	206 TDA2660 1.25									
	125 RRI T20 6 Way 8.95	207 TDA2660 1.25									

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.

Please add 15% VAT and 90p P & P

# QUICK SAVE T.V. SPARES

MUXTON HOUSE, MUXTON, TELFORD, SALOP.

REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.

## CentreVision

TEL: 0222-44754

SLOPER ROAD

LECKWITH

CARDIFF CF1 8AB

OPPOSITE CITY FOOTBALL GROUND

5 MINS FROM M4

TELEVISION/VIDEO

(VHS + BETA)

FROM £85

- ★ ITT CD752 REMOTE WORKING £90
- ★ PHILIPS G11 FROM £40
- ★ GEC STARLINE 22-20 (Remote) £35
- ★ PYE CHELSEA £25
- ★ THORN 9000 20" £35
- ★ DECCA 22" BLACK FRONT VERICAP £15
- ★ RANK T20 REMOTE £48
- ★ PHILIPS 550 IN 10's £18

PRICES SUBJECT TO VAT

OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30

SATURDAY 9.00 - 1.00

## TOP TWENTY VIDEO SPARES

Cassette lamp (Ferg/JVC).....£1.80	Video head (Ferg) (state model).....£37.50
Cassette lamp (Panasonic).....£1.80	Video head (Panasonic) (state model) £39.50
Take-up clutch (Ferg).....£6.95	Head cleaning fluid.....£1.50
Belt kit (Sony) (state model).....£6.50	Head cleaning sticks (each).....50p
Belt kit (Ferg) (state model).....£6.50	Reel Drive Pulley (Sanyo VTC5000).....£8.88
Belt kit (Panasonic) (state model) £6.50	Reel Motor (Sanyo VTC5000).....£14.20
Belt kit (Sanyo 9300).....£6.50	Reel Motor (Sharp).....£12.96
Rewind kit (Sony C7).....£6.95	Overhaul kit (Ferg) (state model).....£19.95
Reel idler (Sharp VC).....£3.45	Overhaul kit (Sony) (state model).....£19.95
Video head (Sony C7/C5).....£39.50	Overhaul kit (Sharp) (state model).....£19.95

Most spares available for Hitachi, Panasonic, Sony, Sanyo, Sharp etc.

Prices on request.

## TELEVIDEO SERVICES

### NOTTINGHAM (0602) 226070

76 Wollaton Rd., Beeston, Nottingham

Please add 50p post & packing and then add 15% VAT to total

ALL ORDERS DESPATCHED BY RETURN OF POST

Send 24p stamp for full catalogue.

## TUNERS + TUNERS

- ★ If you repair sets regularly - phone us today and we will dispatch immediately - no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

**TELEPART**

32 Temple Street,  
Wolverhampton WV2 4LJ.  
Phone: (0902) 773122.

## TVS TRADE SERVICES BROMSGROVE

Large selection of quality clean TV & Video  
always in stock, including:

BUSH T20/24      DECCA 80/100  
GEC STARLINE  
HITACHI      ITT (full remote)  
PHILIPS G8  
PHILIPS G11      PHILIPS KT3  
THORN 9600 including TELETEXT  
THORN 8800      THORN 9000  
(remote)      (remote)  
THORN TX

**VHS VIDEO from £85 (working)**

We specialise in working sets, fully serviced and ready to deliver to your customer's home. Spares back up service available to customers. You've seen the junk, so why not now come and pay us a visit - we think you will be pleasantly surprised by our prices and the quality of our equipment. Delivery service available.

For further details phone:

**COLIN BROOMFIELD,**  
UNIT 7, STATION STREET,  
BROMSGROVE, WORCS.  
(0527) 37037



# CELTEL

## NOW OPEN AT

### M25 JUNCTION 30

#### EX-THORN

### TVs + VIDEOS

#### TELETEXT PORTABLES ETC

#### ALL IN IMPECABLE CONDITION

### 2 BREACH ROAD

### WEST THURROCK

PURFLEET 0708  
861404

## UNTESTED EX-RENTAL CTVs OVER 1500 WEEKLY

WITH THIS QUANTITY WE DO NOT  
HAVE TIME TO PLAY ABOUT.

**NO BUMPED TUBES**

**BEST SOURCE IN U.K.**

**COLOUR TVs FROM £3**

**VIDEO RECORDERS  
FROM £60**

TANDBURG S/S CTVs  
DUAL TUNERS IDEAL FOR  
EXPORT

VIDEO RECORDERS FROM £50:  
SONY C5: C6: C7 & C9  
PANASONIC : SHARP  
FERGUSON : GRUNDIG ETC.

CALL & SEE OUR SELECTION  
DELIVERY ARRANGED FOR  
BULK PURCHASES  
LOAD DIRECT FROM SOURCE  
AT VERY KEEN PRICES

**22"/26" TELETEXT VIEWDATA  
COLOUR IN STOCK NOW**

**CASH ONLY**

## FRANK FORD

(TV TRADE DISPOSALS)  
SCHOOL LANE  
GUIDE

BLACKBURN, LANCs  
TEL: 0254 64489

# HOCKLEY DISCOUNT TELEVISIONS

**GOOD NEWS!** We have now expanded our Midlands Branch  
**THAT MEANS!** More bargains for you & more selection

We now have **HUGE STOCKS** of TV's & V.H.S. VIDEOS

**LORRY LOADS DELIVERED DIRECT FROM SOURCE!**

Prices start from **£6.00**

Working Sets from **£12.00**

Unlimited Selection of:

Philips G8's & G11's  
Pye Solid State  
Pye Chelsea  
G.E.C. Solid State  
Rediffusion Mk. I & Mk. III

Thorn 8800, 9000  
9600, TX9, TX10  
Latest Hitachi  
I.T.T. CVC30, CVC45  
Bush T20, T22

**Midlands Branch:** HOCKLEY DISCOUNT TELEVISIONS, 94 Soho Hill, Hockley, Birmingham, B19 1AE.  
Tel. 021-551-2233 - *Ask for Jazz*

**North-East Branch:** NORTHERN T.V. DISTRIBUTORS, Unit 2, Perth Court, Eleventh Avenue, Team Valley Trading Estate, Gateshead, Tyne & Wear. Tel. 091-487 5389 - *Ask for Joe*

## SUMMER BARGAINS

10 BUSH 2 CHIP	£50
10 PHILIPS G8 550	£150
10 DECCA 6-BUTTON 20"	£70
10 REDIFFUSION MARK 1 REVAMP	£120
10 THORN 8000 17"	£150

ALSO BUSH T20, G11, 9000, 9600, 9800,  
GEC STARLINES

PL509 £1.50, PY500 £1  
ELC 1043 Tuners Ex-panel £2.50  
RING FOR QUOTE

ALL + VAT

## TELETRADERS

Forde Road, Brunel Industrial Estate,  
Newton Abbot, Devon  
Telephone: (0626) 60154  
**THE NO. 1 WHOLESALE IN THE SOUTH**

## SATELLITE RECEIVING SYSTEMS

1m and 2m Parabolic Dishes, other sizes available.

A range of other components available, eg, LNAs, Downconverters, receivers, for both 4 and 11 GHz. Complete Terminals for ECS and Intelsat, both single channel and tunable versions.

Terminals for other frequencies available.

Demonstration by appointment.

**L & S Bear Electronics Ltd**  
Yeo Lane, Colley Lane,  
Bridgwater, Somerset.

Telephone: Bridgwater (0278) 421719

## VIDEO HEADS MONOLITH electronic products

HIGH QUALITY UNIVERSAL VIDEO HEAD  
REPLACEMENTS FOR ALL VHS AND BETAMAX  
VCR MACHINES

**VHS Part No. 3HSS** (5mm Centre Hole) **£29.95** PRICE  
**VHS Part No. 4HSS** (15mm Centre Hole) **£29.95** EACH  
**BETAMAX Part No. PS3B** **£38.95** EX.  
**REPLACEMENT KIT** (17 Pieces Boxed) **£17.35** V.A.T.  
PLEASE ADD 15% V.A.T. PLUS P&P £2.00 PER ORDER  
OUR FULL CATALOGUE AVAILABLE ON REQUEST.

Please allow between 14 and 28 days for delivery.

**AUDIO + VIDEO HEADS - MOTORS - PARTS**  
Suppliers to most U.K. Distributors/Service Organizations

**THE MONOLITH ELECTRONICS CO. LTD**  
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England  
Telephone Crewkerne (0460) 74321 Telex 46306 MONLTH G

AN1270	£1.75	CX095C	£2.00	LA4051P	£1.60	STK439	£5.50	TA7226P	£2.20	2SA74	£0.60	2SB471	£3.50	2SC1047	£0.35	2SD718	£1.50	LM361	£2.60	TBA673	£1.20	£1.20
AN203	£2.20	CX1000	£5.75	LA4100	£1.00	STK441	£6.00	TA7227P	£1.60	2SA82	£1.60	2SB475	£0.60	2SC1061	£0.35	2SD734	£2.80	MC396	£1.00	TBA700	£1.50	£1.50
AN210	£1.75	CX101G	£5.75	LA4101	£1.00	STK443	£6.95	TA7228P	£3.00	2SA101	£3.00	2SB481	£0.60	2SC1096	£0.60	2SD734	£2.80	MC396	£1.00	TBA700	£1.50	£1.50
AN211A	£2.25	CX130	£4.50	LA4102	£1.20	STK457	£5.50	TA7230P	£1.75	2SA102	£1.75	2SB482	£0.75	2SC1098	£0.75	2SD822	£2.95	MC396	£1.00	TBA810SH	£1.75	£1.75
AN214Q	£1.80	CX136	£5.50	LA4110	£1.40	STK458	£5.75	TA7232P	£2.75	2SA103	£2.75	2SB509D	£0.60	2SC1114	£0.60	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN217B	£2.20	CX143A	£7.50	LA4112	£1.30	STK460	£7.50	TA7310P	£1.40	2SA104	£1.40	2SB511C	£0.60	2SC1115	£1.20	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN228W	£2.75	CX157	£3.95	LA4120	£2.50	STK461	£6.50	TA7312P	£1.30	2SA201	£1.30	2SB536	£0.60	2SC1124	£0.95	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN236	£2.50	CX158	£3.50	LA4125	£2.00	STK463	£7.40	TA7313	£1.30	2SA202	£1.30	2SB536	£0.60	2SC1124	£0.95	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN239Q	£2.50	CX160	£2.50	LA4140	£0.70	STK465	£8.50	TA7315	£1.75	2SA203	£1.75	2SB565	£0.60	2SC1124	£0.95	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN240P	£1.50	CX161A	£2.50	LA4200	£1.50	STK0025	£4.95	TA7325	£0.85	2SA203	£0.85	2SB565	£0.60	2SC1124	£0.95	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN241P	£1.50	CX162	£3.40	LA4220	£1.20	STK0029	£4.35	TA7328	£1.60	2SA221	£1.60	2SB647	£0.60	2SC1170B	£2.95	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN247P	£2.50	CX170	£6.50	LA4230	£1.75	STK0039	£4.25	TA7607	£2.75	2SA224	£2.75	2SB688	£0.60	2SC1172A	£2.75	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN259	£2.75	CX180	£8.50	LA4400	£1.90	STK0040	£5.50	TA7608	£3.50	2SA225	£3.50	2SB754	£0.65	2SC1307	£1.25	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN282	£1.50	CX171	£8.50	LA4420	£1.40	STK0049	£5.75	TA7609	£3.50	2SA341	£1.75	2SB755	£1.75	2SC1308	£2.70	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN271A	£2.50	HA1125	£1.50	LA4422	£1.20	STK0059	£6.00	TA7611	£1.15	2SA342	£1.15	2SC352	£2.50	2SC1316	£2.70	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN274	£2.50	HA1137	£1.75	LA4430	£1.30	STK0080	£6.50	TA7658	£1.50	2SA350	£1.50	2SC370	£2.50	2SC1317	£2.70	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN295	£3.25	HA1149	£1.40	LA4440	£2.20	STK2028	£6.50	TA7658	£1.50	2SA353	£1.50	2SC371	£2.50	2SC1342	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN303	£2.50	HA1156	£1.10	LA4460	£3.75	STK2029	£3.75	TA7658	£1.50	2SA355	£1.50	2SC372	£2.50	2SC1342	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN313U	£2.75	HA1166	£1.60	LA4461	£1.75	STK2230	£6.00	TA7658	£1.50	2SA355	£1.50	2SC373	£2.50	2SC1364	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN315	£2.00	HA1197	£1.50	LA7800	£1.85	STK2240	£5.75	TA7658	£1.50	2SA485	£1.75	2SC380A	£1.75	2SC1417	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN316	£3.50	HA1199	£1.40	LC7120	£3.50	STK3042	£6.50	TA7658	£1.50	2SA495	£1.85	2SC382	£3.00	2SC1419B	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN318	£4.75	HA1306W	£1.60	LC7130	£3.50	TA7028M	£1.90	TA7658	£1.50	2SA509	£1.25	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN331	£2.75	HA1319	£2.00	LC7131	£3.75	TA7045M	£1.30	TA7658	£1.50	2SA539	£1.25	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN360	£1.20	HA1322	£1.80	LC7136	£2.75	TA7050P	£0.80	TA7658	£1.50	2SA562	£2.00	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN362L	£1.30	HA1339A	£1.80	LC7137	£2.75	TA7051P	£0.80	TA7658	£1.50	2SA624	£2.00	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN366P	£1.50	HA1342A	£1.70	M5106P	£2.25	TA7054	£1.70	TA7658	£1.50	2SA678	£1.95	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN610P	£1.75	HA1366W	£1.50	M5115P	£3.50	TA7063	£0.80	TA7658	£1.50	2SA699A	£2.20	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN612	£1.75	HA1366WR	£1.50	M5134P	£2.75	TA7066	£1.40	TA7658	£1.50	2SA720	£2.20	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN572Z	£1.50	HA1367	£3.20	M5135P	£2.30	TA7070P	£1.50	TA7658	£1.50	2SA726	£1.75	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN5730	£1.85	HA1368	£1.80	M5155	£2.75	TA7072P	£1.20	TA7658	£1.50	2SA748	£1.00	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN5732	£1.85	HA1368R	£1.65	M5153L	£1.50	TA7073P	£2.25	TA7658	£1.50	2SA762	£1.95	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN5753	£1.95	HA1374	£4.50	M51514AL	£1.75	TA7074P	£1.95	TA7658	£1.50	2SA777	£0.60	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN6250	£2.30	HA1377A	£2.20	M51515BL	£2.50	TA7104P	£1.35	TA7658	£1.50	2SA844	£0.35	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN6344	£4.75	HA1388	£2.75	M51516L	£2.50	TA7108	£1.50	TA7658	£1.50	2SA899	£0.75	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7105	£2.20	HA1389	£1.75	M51517L	£2.50	TA7109	£2.30	TA7658	£1.50	2SA940	£0.75	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7110	£1.40	HA1389R	£1.40	M51518L	£1.75	TA7119	£1.75	TA7658	£1.50	2SA950	£0.35	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7114E	£1.80	HA1392	£2.30	MB3705	£1.60	TA7120P	£0.50	TA7658	£1.50	2SA1015	£0.30	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7115E	£1.60	HA1397	£2.50	MB3712	£1.50	TA7130P	£1.00	TA7658	£1.50	2SA1102	£0.30	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7120	£1.40	HA1398	£2.40	MB3730	£1.75	TA7136P	£1.00	TA7658	£1.50	2SA1103	£1.50	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7130	£1.50	HA1457	£0.90	MB3731	£2.50	TA7137P	£0.80	TA7658	£1.50	2SA1104	£1.50	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7145M	£1.80	HA11221	£2.30	MB3756	£2.60	TA7139P	£1.50	TA7658	£1.50	2SA1105	£2.25	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7146M	£1.80	HA11225	£1.95	MB8719	£3.50	TA7145P	£1.80	TA7658	£1.50	2SA1106	£2.25	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7154	£1.75	HA11235	£2.00	PL101A	£2.30	TA7146	£2.50	TA7658	£1.50	2SB22	£1.20	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7156N	£1.80	HA11705	£4.75	PL103A	£4.95	TA7150P	£1.80	TA7658	£1.50	2SB33	£1.20	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7158N	£3.25	LA1111P	£0.80	SI-1125	£7.50	TA7152P	£1.70	TA7658	£1.50	2SB54	£0.70	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7310	£0.80	LA1201	£0.85	SI-1125H	£5.75	TA7153P	£1.60	TA7658	£1.50	2SB56	£0.95	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
AN7311	£1.00	LA1222	£0.80	STK011	£3.75	TA7176P	£1.50	TA7658	£1.50	2SB75	£0.80	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
BA301	£0.75	LA1230	£1.50	STK013	£6.25	TA7193P	£3.50	TA7658	£1.50	2SB155	£0.35	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
BA311	£0.95	LA1240	£1.75	STK014	£6.25	TA7200	£2.00	TA7658	£1.50	2SB156A	£2.20	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
BA313	£0.75	LA1240	£1.50	STK015	£5.00	TA7201	£2.00	TA7658	£1.50	2SB171	£1.00	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
BA318	£1.30	LA1355	£1.20	STK016	£4.75	TA7202P	£2.00	TA7658	£1.50	2SB172	£0.80	2SC382	£3.00	2SC1427	£3.00	2SD816	£3.50	MC3403L	£0.60	TBA900	£1.50	£1.50
BA402	£0.75	LA1368	£2.20	STK020	£4.50	TA7203P	£1.80	TA7658	£1.50	2SB177	£2.30											

## HITACHI VHS COLOUR CAMERAS

Mains Only Tested/  
Working

## VHS VIDEOS

FERGUSON

3V00, 3V22, 3V23, 3V16, 3V29,  
3V30, 3V31, 3V32, 3V35

NATIONAL PANASONIC  
NV8600, 8610, 2000, 7000,  
370, 333, 2010

SHARP

620, 630, 640, 2300 H T/P

## BETAMAX

SANYO VTC 9300, 5000, 5300

SONY C5, C6, C7, C9  
and SL F1UB T/P

Also Bush, Toshiba, Hitachi and Blau Punkt

PLUS


17" 18" 20" 22" 26" Hybrid/  
Solid State CTVs  
Remote Control & Teletext  
Discount for Quantities

Complete loads delivered from pick up point

**JOHN CARTER  
(Electrical) LTD  
FURNACE ROAD,  
GALLOWES INN,  
ILKESTON**

**Phone: 0602 303124**
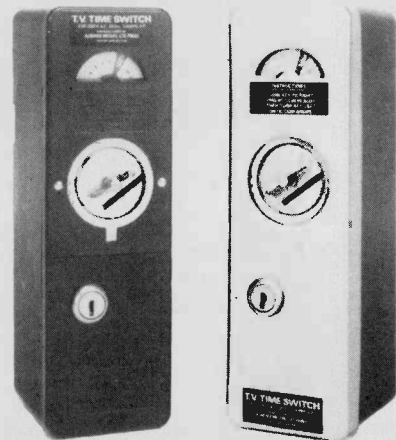
## CUSTOMER CAN'T PAY? DONT LOSE HIM FIT A TV METER



COMPLETELY VARIABLE TIMINGS

 **Alberice** METERS  
LIMITED

MANUFACTURERS OF TV COIN OPERATED

METERS CONTACT (0202) 674272

87-89 Sterte Avenue,  
Poole, Dorset. BH15 2AW.

Telex: 418253 LUMIC G

## MAIL ORDER ADVERTISING

### British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

### Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded."

# JUNCTION 11

A NEW COMPANY IN THE NORTH WEST  
OFFERING A FRIENDLY, FIRST CLASS SERVICE  
TO THE TRADE AT COMPETITIVE PRICES


OUR RANGE INCLUDES

**G.E.C. PYE PHILIPS I.T.T. DECCA R.B.M.**

Now in stock V.H.S. V.C.R.s from £60 plus full range of Thorn remote control including T/Text

★ **DISCOUNT FOR QUANTITY** ★

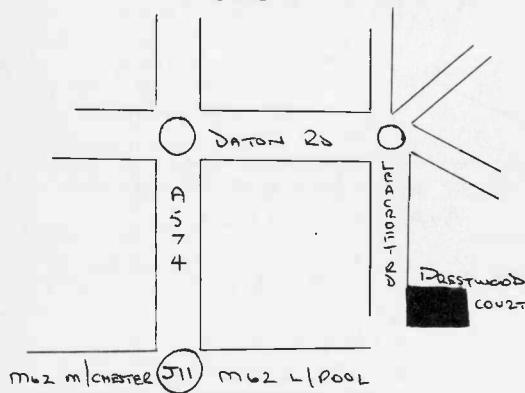The directors of this new company assure all our prospective customers of a warm welcome, and a fair deal.



**COME TO JUNCTION 11, M62,  
YOU'LL FIND US HERE**

**JUNCTION 11  
TV TRADE DISPOSALS LTD.,  
Unit 11, Prestwood Court,  
Leacroft Road,  
Birchwood, Warrington.  
Phone 0925 826387.**

Open 6 days 9 - 5.30 (later by appointment)

## WELLVIEW TUBES

(REBUILT UNDER LICENCE)

FOR TELEVISION TUBES AT KEEN  
PRICES REBUILT IN OUR OWN FACTORY  
AND FULLY GUARANTEED

## TUBE REPLACEMENTS

(Prop. Middletons TV Ltd)

MONMOUTH TRADING CENTRE,  
BRIDGWATER, SOMERSET.

Tel: 0278-425690-722816

We also do Mail Order.

## JUST OPENED

FOR

South Yorkshire/Derbyshire Dealers

Come and see our range of  
Colour TVs from £6

## BARGAINS GALORE

PHONE 0246 411325

Chesterfield

The World of . .  
P+P 1 PANEL £1.50  
2 PANELS OR MORE  
£3.00

## "TELEPANELS"

52 Mount Pleasant Road, Chigwell, Essex. Tel: 01-729 0506.



	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	5.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731			10.00		18.00	10.00	7.00	8.00		4.50
BUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
DECCA BRADFORD	3.00		7.00			4.00		4.00		
DECCA 80	12.00	POA	14.00		12.00	10.00		14.00		POA

**POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!**

# WD-TV 100's of WORKING COLOUR TVs

DECCA · PHILIPS G8 & G11  
BUSH · PYE s/s · ITT · THORN  
8800 9000 9600 · GEC s/s  
KORTING · JAPS

PRICES FROM

**£15** + VAT

Videos

Always Available

**Tested Tubes**

**All sizes from**

**£10** + VAT

Always Scrapping Down  
Decca, Philips & Thorn  
- Spares Always Available


**WD-TV**

TV Warehouse  
(former Tritel Place),  
The Chestnuts,  
Watling Street (A5),  
Hockliffe, Bedfordshire.  
(Junct. 12 M1 - 3 miles)

Tel: 0525 210768 & 210686.
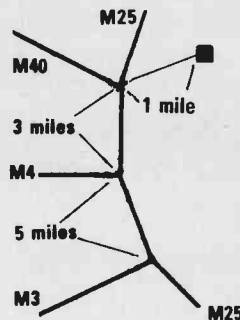
## REBUILT TUBES?

Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



### WE ARE LOCATED IN UXBRIDGE

At probably the most accessible part of S.E. England. The nearest junction of the M25 is only about 1 mile away and we are less than 10 minutes from the interchanges on the M25/M3, M25/M4, M25/M40. The Poyle/Colnbrook section of the M25 was completed in September with the exception of the M25/M4 interchange which will be completed soon.

LOCAL AREA MAP AND PRICE LIST  
AVAILABLE ON REQUEST

### DISPLAY ELECTRONICS LTD.

UNIT 4, SWAN WHARF,  
WATERLOO ROAD,  
UXBRIDGE, MIDDLESEX.  
UXBRIDGE (0895) 55800.

### APOLLO MANCHESTER

FAST MAIL ORDER GB 3-4 DAYS ALL AREAS PLEASE PHONE FOR COST  
FREE LOCAL DELIVERY SAME DAY ● FITTING SERVICE £20

2 YR GUARANTEE - QUANTITY DISCOUNTS - PILL GLASS BOUGHT

A47 342/343X - 470 BC822/CTB22/BGB22/DHB22	£39
470-ESB22/EPB22/ERB22/FTB22	£49
A51-220X/192X	£39
A51-161X/162/163/168	£49
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£49
510-VLB22(E53) DTB22/001/RFB22/RGB22/SFB22	£49
A51-590 New	£56
A51-570X/580/001/210/241	£49
A56-120X/123/140/410	£39
560-DZB22(E53)/HB22/AKB22/TB22/AWB22	£49
560-ETB22/DTB22/CSB22/DMB22/DNB22	£49
A56-611X/615X	49
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X/510X - A66-500X/510X	£49
30AX - A56-540X - A66-540X	£53


If your tube type is not in stock we can arrange collection - rebuilding + redeliver

PLEASE PHONE BEFORE CALLING

061-799 0854. 24 hour answering service

43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL
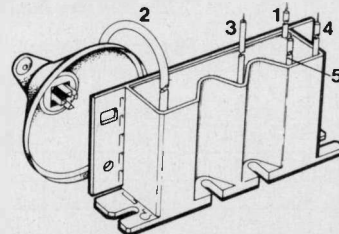
### UK 'Universal' TRIPLER from £5.00 inc post & VAT



**BWARE IMITATIONS**

1x10 (£5.00 each)	£50.00
1x 5 (£5.50 each)	£27.50
1x 3 (£5.75 each)	£17.25
1x 2 (£5.95 each)	£11.90

**NB:** Includes Post & VAT

1. Input 200mm. 2. Output 780mm. 3. Focus 390mm. 4. Pulse 390mm. 5. Earth 390mm.  
Instruction sheet available on request

Strictly cash with order.  
Goods despatched by return.  
Access Barclaycard accepted

**TELEPART**

32 TEMPLE STREET  
WOLVERHAMPTON WV2 4LJ  
PHONE (0902) 773122



AT LAST!!

# QUALITY USED TELEVISIONS

EXCELLENT CABINETS – GOOD WORKERS

Thorn 9600 Teletext	£85.00	Remote	£55.00
Thorn 9200 Remote	£45.00	Basic	£35.00
Thorn 9000 Remote	£30.00	Basic	£25.00
Thorn 8800 Remote	£30.00	Basic	£25.00
Philips G11	£55.00		
Bush T20 Remote	£60.00	Basic	£45.00
Thorn Mechanical VIDEO 7 day timer	£110.00		

All remotes with handsets Delivery can be arranged

*We also have large stocks of TV, Video, Small Appliances, etc:*

MANUFACTURERS END OF LINE  
MANUFACTURERS B GRADE  
CATALOGUE RETURNS

**WESTCO,**  
Unit D, Perrywood Trading Park,  
Wyld's Lane, Worcester.  
Telephone: (0905) 359003.

## IRISH T.V. DEALERS

(PLEASE NOTICE)

LARGE SELECTION OF RECONDITIONED PRECISION-IN-LINE UHF-VHF COLOUR TVs,  
SOME WITH RE-GUN TUBES FITTED, "CABINETS RESTORED TO A1 CONDITION".  
PRICES START @ £60.00 VAT INCLUDED. ALSO 20" & 22" RE-GUN TUBES IN STOCK,  
QUANTITY DISCOUNT, DELIVERY ARRANGED. VIDEO HEADS ALSO IN STOCK.

(EXPORT SPECIALISTS)

<b>T.V. TRADE SALES</b>	ALSO	<b>T.V.T.S.</b>
<b>E.D.I. HOUSE</b>		<b>CLOVER PLACE</b>
<b>KYLEMORE PK. WEST</b>		<b>COLLEGE ST.</b>
<b>DUBLIN 10.</b>		<b>KILLARNEY.</b>
<b>Tel: 0001-264139 (Local calls 01-)</b>		<b>Tel: 064-33655</b>

LONDON'S LARGEST  
TELEVISION WHOLESALER...  
with over 4½ thousand sq. feet

## "TELEMANN"

8-10 RHODA STREET (off Bethnal Green Road)  
LONDON E2. FREE CAR PARK

**SPECIAL OFFER!!**

Parcel of 25 Monos .....	£1.00
Parcel of 10 Philips 22" G8 550 .....	£15.00
Parcel of 10 Decca Bradfords .....	£8.00
Parcel of 10 Japs Colour .....	£20.00

LORRY LOADS DELIVERED DIRECT FROM  
SUPPLIERS — NO CHARGE FOR DELIVERY!

**01-739 2707** → <sup>2</sup> LINES ← **01-739 3123**

FREE CAR PARK + NO YELLOW LINES OUTSIDE!

## N.G.T. COLOUR TUBES

First Independent Rebuilder with  
B.S.I. CERTIFICATION

DELTA – IN-LINE – PIL – BONDED YOKE  
including  
AXT Series, DZB series 20AX - 30AX  
A56 610/67 610 series, A51 570/580/590X  
A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

**N.G.T. ELECTRONICS LTD.,**  
120 SELHURST ROAD, LONDON SE25  
Phone: 01-771 3535.

25 years experience in television tube rebuilding.

## SETS & COMPONENTS

**LEADER LCT** - 910A Tester, complete, all bases, boxed, little use, £150. Clacton 435700.

**BIRMINGHAM AREA-TRADE.** Service workshop, all makes Video-Audio T.V. Free warranty repairs for Sony, Sharp, Ferguson, Sanyo. Two minutes from H.R.S. ARGO SERVICES (B'HAM), B.HAM 4. 021-359-3753.

**HITACHI PANELS REPAIRED/EXCHANGED.** CSP680, CNP190/192/CTP202/204, CTP203, CTP210, CBP220 etc. Phone Littlehampton 0903-714717.

**QUALITY SETS FROM CORNWALL.** Workers/non workers. Spares, panels, etc. Details ring 0726 81 5389.

**OCHRE MILL TECHNICAL** for GRUNDIG sets, moduales, manuals. TELEQUIPMENT OSCILLOSCOPES spares, manuals. Assorted items RECONDITIONED TEST EQUIPMENT. 0785 814643.

**HITACHI, Mitsubishi, Panasonic, Sony, Toshiba, JVC, Sharp.** Sharp fully refurbished. PEARSON TELEVISION. 0484 863489. Delivery arranged.

**TURN YOUR SURPLUS** capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

**R.B.M. A823 PANELS.** S.A.E. for details: SCHOFIELD, 28 St Albans Road, St Annes, Lancs. FY8 1TH.

**PHILIPS G11 AND BUSH T20** regular supplies. For prices phone 01-845-2036.

**THORN GEC** Deccas stripped for spares. Panels, tuners from £2.50, phone for prices. WELLINGTON, Dartford 0322 337212.

## WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for THORN, PHILIPS, PYE, RANK, GEC, SHARP, SONY, DECCA, ITT and now also FIDELITY.

Did you know we also stock

FUSES	I.Cs
TUBES	TOOLS
AERIALS	VIDEO LEADS
AEROSOLS	AUDIO LEADS
RESISTORS	SEMICONDUCTORS
CAPACITORS	SERVICE MANUALS
VALVES	TEST EQUIPMENT
HANDSETS	TV/VIDEO TROLLEYS

AND MUCH MORE

Counter open Monday-Friday 9am-4.45pm

**TRADE ONLY**

**EMPRESS STREET WORKS,  
EMPRESS STREET,  
MANCHESTER M16 9EN.  
Tel: 061-872 5438; 061-848 0060.**

## HALTON TV TRADE DISPOSAL

Wide range of TVs available.  
Working and non-working.

**TRADE ONLY**

(We have NO retail outlet)  
St Michaels Industrial Estate, Widnes  
Tel. 051 423 1577

# TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.78 per single column centimetre (minimum 2.5 cms). Classified advertisements 40p per word

## NORTHERN IRELAND DEALERS

COME AND SEE OUR LARGE RANGE OF  
S/H COLOUR TVs AT LOWEST PRICES EVER

**CONTACT:**

## S. M. ELECTRONICS

11 SANDHOLES ROAD, COOKSTOWN, CO. TYRONE

Telephone: Cookstown 06487/64277

Open: Mon.-Sat. 9.00 am-6.00 pm (Closed Wednesday)

## TELEVISION

Trade & Retail supplies of  
Ex Rental TVs and Video  
Recorders. Most makes.  
Workers and Non-Workers.

## SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,  
Brent Park Industrial Estate,  
Southall, Middx. UB2 5LL.  
01-574 4631. Ext 28

### COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound, Grey scale, Colour Bars, Red, Green & Blue Raster, Cross-hatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. £75.90

### OUTPUTS PROVIDED

UHF OUTPUT  
VIDEO OUTPUT  
SOUND OUTPUT  
LINE PULSE  
FIELD PULSE



Same as above plus RGB output £81.50  
Line Output Transformer Tester £11.50  
B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale UHF output £18.50  
Same as above but with Video Output £20.50  
Capacitance Meter measures 10pF to 1µF complete with moving coil meter £14.75  
Car Alarm with built in Siren £20.50  
S.A.E. for details. - Prices include P&P & VAT.

### C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,  
Wolverhampton WV1 3DW.  
Tel: (0902) 871563

## INDEPENDENT TELEVISION

### AND VIDEO COMPANY

LARGE STOCKS TO CLEAR  
EVERY WEEK

### COMPETITIVE PRICES

**EXAMPLES:**  
B&W 20"-24" From £1.00  
COLOUR:  
Bush 1-2 I.C. £4.00  
Philips 520-550, 26" £6.00  
Thorn 3500 £6.00  
GEC-Decca-ITT £6.00

Philips 550 22" £10.00  
Pye 18"-20"-22" £10.00  
GEC 20"-22" 26" £12.00  
Thorn 8800-9000-9800 £15.00

Many Other Modern Sets  
and VHS Videos

PHILIPS G11 - ITT - Bush T20-T22-  
T26, Hitachi, Nat. Pan. - Sony  
Off Pile from £40

Phone Frank: Nottingham  
(0602) 864627

Unit 3  
Meadow Trading Estate,  
Meadow Lane,  
Nottingham NG2 3HQ.

## T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537  
194, Acton Lane, London W.4.

# SERVICE PAGES

(minimum 12 words), box number 70p extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

## NOW OPEN FOR THE BEST QUALITY AND BEST PRICES IN BIRMINGHAM.

WORKING AND NON-WORKING  
TVS AND VIDEOS IN STOCK.

**RING SINGH – 021-772 2733**

**WILTSGROVE LIMITED**  
(Next Door to **UNCLE'S DISCOUNT STORE**)  
**128-130 Ladypool Road,**  
**Sparkbrook, Birmingham B12 8JA.**

### WOODSDALE COMPONENTS RANK BUSH MURPHY TRANSFORMERS

Line Output Z718 (T703A, T706A)	£19.00
New (Complete) Less Focus Module and Rectifier	£10.50
T20, T22 (T705A)	£11.00
T26 (T705B)	£11.00
TDA2190 Plug-in Replacement module suitable for Bush T22/26 and any set using same device	£6.00
Switch Mode T114A	£6.00

Genuine RBM Units.  
Prompt Postal Service P&P Paid.  
Add 15% VAT to all prices.  
DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,  
Pinner, Middlesex. HA5-2QT.  
Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

### STARLITE ELECTRONICS

NOW MOVED TO:  
WILLOWS FARM,  
A13 RAINHAM, ESSEX.  
Rainham 23225 also  
Hornchurch 50238.

– TV TUBES –  
2 year guarantee  
Most types available  
Japanese including Sony  
Ex-Rental TVs from .....£15.00  
Untested Panels.....£4.00

### C.T.V. PANEL SERVICE

Exch/repair & sales – chemically cleaned – no burned  
or damaged print. 3 months g'tee, large range incl.  
Decca 80 & 100, G11, G8, ITT, GEC, Rank, TCE, Jap &  
euro models, despatched same day.  
Send S.A.E. for lists or ring with your requirements:  
Please note new address:

**Argo Services (Birmingham),**  
53 Lawley Street, Birmingham B4 7XH.  
Tel. 021 359 3753  
Telephone orders accepted using Access/Mastercard  
CALLERS RING FIRST

### WORKING CTVs THE BEST & CHEAPEST IN LANCASHIRE SPECIAL OFFER

Working Decca Bradford Including  
Black Fronts  
18" 20" 22" 26" **ONLY £20.00 each** in 6  
units

Working GEC Plastic & Wooden. All models  
20" 22" 26" **ONLY £22.00 each** in 6 units

Working Bush 20" 22" 26"  
**ONLY £15.00 each**

Philips G8 (520) 22" & 26"  
**ONLY £20.00 each**

Plus many more makes & sizes in stock,  
inc. Tanburg, Nordmende, Thorn.

1st COME 1st SERVED

**ALL SETS TESTED & WORKING**

CALL

JOHN POWNEY

**TRADE TV SALES & SERVICE**

Unit 31 Progress Industrial Estate,  
Kirkham, nr Preston  
(0772) 683392

UNTESTED PANELS FOR ALL MAKES OF TV  
£1.25 per panel plus post & packing

**NORMAN  
ENTERPRISES LTD**  
Weston-Super-Mare, Avon.  
Tel: 418545/413991

Colour TVs fully engineered  
with a special care on tubes

Hitachi 217 Remote Control ...	£95
Thorne 9000 Remote Control ..	£45
Pye G11 .....	£49
Rank T20 .....	£40
Pye Chelsea 6 Button....	£29.50
Pye 725 .....	£40
Pye 721 .....	£35
Thorne 9600 .....	£55
Thorne 9200 .....	£49.50
Bush T20 Remote Control ..	£55
Bush T24 .....	£75

All above prices include hand  
sets and VAT.  
Ready for sale.

Phone now, limited number each month. All  
the above off the pile, less a 3rd

### TRADE TVs

Yorkshire New Outlet  
Ex-Rental & Reposes TVs  
Colour From £10  
Mono From £2

**TRADE REPAIRS AND SPARES**

### TELEFIX

Ellingthorpe Street,  
Wakefield Road, Bradford 4.  
Phone: 0274 480281 or 733373.

# N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

**COLOUR TV'S AND VIDEOS  
H.P. REPOS AND EX. RENTALS**

**ANNUAL CLEARANCE  
ROCK BOTTOM PRICES**

PYE G11 EXC CAB.....	£40	BUSH 718.....	£20
BUSH T20/26 CH.....	£35	BUSH 2 CHIP.....	£8
HITACHI 191.....	£20	GRUNDIG 5010.....	£10
FERGUSON TX (NOT D.E.R. Etc.).....	£65	PYE KT3.....	£50
GEC 2010.....	£20	GEC 2213.....	£30
PYE 222.....	£20	THORN 3000.....	£7
PHILIPS 550.....	£15	GRUNDIG G415/4206	

Best Stock in the Country — over 2000 in stock (90% of our TV's Switch on)  
Special Price Quoted For Bulk Purchases From Source.

## REFURBISHED TV'S




BUSH T20/T26.....£45, G11.....£50,  
PYE KT3.....£70, Others done to order.

DISCOUNT FOR QUANTITY
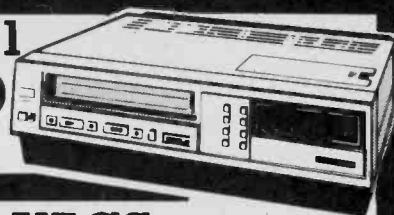
## VIDEO

SHARPS 7300, 8300, 9300, HITACHI, VT11  
FERGUSON 3V29 (Not Ex D.E.R. etc.)  
SANYO, SONY, BETA



**100's PX HOOVER JUNIOR VACS**

— All models in stock

Fully reconditioned HOOVER JUNIORS (Like new) £27

**TEL. 0274 688458**

**UNIT 12, Wharfedale Rd  
M606 Euroway Estate  
Bradford**

**CASH ONLY**

**OPEN 6 DAYS  
SAT 9-5.30**

# SCREENPLAY

Your Friend in the TV Business

COLOUR SETS FROM £5.00  
 MONOS FROM £3.00  
 PANELS BY POST - PRE-CALIBRATED  
 WORKING SETS TO ORDER

Phone Baldock 894905  
 SECTION 3, UNIT 4,  
 SERL COMPLEX,  
 LONDON ROAD,  
 BALDOCK, HERTS.  
 OPEN 6 DAYS 10-6.30pm/10-5pm SAT.

## TUBES

£29.00 INCLUSIVE, REGUNS TWO YEAR  
 GUARANTEE. QUANTITY DISCOUNTS SIX  
 £14.50 MONTH GUARANTEE SLIGHTLY USED  
 A56-120 A56-140 A51-110 A49-191 A47-342 or 343  
 A44-270-1 A66-120 A66-140 (410) A67-120  
 (All 26" add £5)  
 No need to spend £5 returning old delta tube.  
 Slightly used in-line tubes from £29.  
 Six months guarantee.

### IN-LINE 1 YEAR GUARANTEE

51-161 TOSHIBA NEW 51-110  
 51-510 47-342 47-343  
 51-570 £45 inclusive £29 inclusive  
 56-500 Special discounts for more  
 than 2

56-540 £55 inclusive  
 66-540  
 66-500

SONY £66 inclusive  
 330AB · 470 KLB · FWB · DLB · KTB · KLB 520 HB ·  
 TB · KB · LB · NB · MB · 570 HB EB · DB · GB · JB  
 MOST IN STOCK. IMMEDIATE DELIVERY

HITACHI PORTABLE COLOUR  
 490DKB22 £34 TUBES MOST SIZES  
 560DZB22 £49 NEW

### Philips G11s

Panels from £10.00. Breaking for spares, Push button  
 units, Tube bases for sale or exchange etc. All good  
 working order.

### RADIO and TELEVISION SERVICING BOOKS

(MacDonalds) New 74/75 £15; 75/76, 76/77, 77/78,  
 78/79, 79/80, 80/81, 84/85, 82/83, 83/84 £22.50.

### FREE DELIVERY

Except Tubes £5 each. All prices are inclusive  
 U-VIEW

29, Warmsworth Road, Doncaster,  
 Yorkshire DN4 0RP. Tel: 0302 855017.  
 Callers ring first, open every day including Sunday  
 1/2 a mile from A1

## BRISTOL TELEVISION TRADE DISTRIBUTORS (BTTD)

4 Victoria Street  
 (Bristol Bridge) BS1 6BN

Ex-rental/trade in TV sets,  
 supplier to trade only, wide  
 range, large quantity, right price,  
 regular supply.

Tel: (0272) 25266

Thorn 3000/3500  
 Thorn 9000  
 UNIVERSAL £4.95 inc. p&p  
 1 year guarantee

The UNIVERSAL TRIPLER can be used in most  
 G.E.C., I.T.T., Pye, Rank, Decca & Continental  
 sets.

### WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

## T.V PANELS

REPAIR EXCHANGE SALES SERVICE  
 PRICES FOR REP. EXC. AS FOLLOWS

Chassis	IF	Decoder	Line Scan	Power Supply	Frame
Philips G11	18	16	20	18	16
Bush T20	X	12	16	15	12
Bush T26	X	16	18	15	X
Bush 718	X	12	18	X	12

All panels are repaired and aligned according to  
 rank std.  
 Ring for prices to buy panels. Prices shown  
 inclusive of postage, etc.  
 All panels guaranteed for 3 months.

T. K. PANELS SERVICE  
 31 Bronte Paths, Stevenage (0438) 61567

## VIDEO & HI-FI ELECTRONICS

379 EDGWARE ROAD  
 LONDON W2  
 TEL. 01-258 0328

ALL VHS PARTS AVAILABLE  
 EXAMPLES:

VIDEO HEADS  
 JVC, Ferguson, Akai, Saba, Telefunken ..... £35.00  
 Sony (Betamax) ..... £45.00  
 National Panasonic ..... £45.00

INTEGRATED CIRCUITS  
 UPC 1365C ..... £7.30  
 UPD 553C ..... £14.75  
 UPD 552C ..... £10.56  
 HA 11711 ..... £14.20

Many other parts available. Send SAE for list.  
 ALL PRICES INCLUSIVE OF VAT  
 ADD £2.00 FOR P&P



- \* Britain's most reliable source of quality TVs.
- \* Hundreds of working polished TVs.
- \* GEC Starline
- \* Decca 80
- \* Decca 88
- \* Decca 100
- \* Pye G11
- \* Thorn 8800
- \* Pye 222 Series

All working and polished.  
 These are not from major  
 companies. A lot are from  
 hotels and have had very  
 little use.  
 Excellent reliable sets for  
 rental.

Krystal Marketing Ltd.  
 Braedon Cross  
 Storage,  
 Dale Road, Selly Oak,  
 Birmingham B29 6A0.

Phone 021-471 3023  
 Telex 335540-G  
 Ask for Les

## GEMINI TUBES

THE PRICE IS RIGHT  
 FOR QUALITY REBUILDS  
 ALL WITH 2 YEAR WARRANTY

Phone now on St. Helens 37672  
 Or call at Unit 3,  
 Delphwood Drive,  
 Sherdley Road Ind. Estate,  
 St. Helens.

## TELFORD ELECTRICAL SPARES & SERVICE

GENUINE  
 SONY SPARES

NEW - GENUINE  
 FERGUSON SPARES

VIDEO HEADS

**TESS  
 SERVICE**

SINCLAIR  
 COMPUTER PRODUCTS

Beswick FUSES

TRANSFORMERS

INSTRUMENTS

E.H.T. TRAYS

UNIT 42,  
 HEATH HILL  
 INDUSTRIAL  
 ESTATE,

AERIAL PRODUCTS

AUDIO PRODUCTS

DAWLEY, TELFORD,  
 SHROPSHIRE

RESISTORS

CAPACITORS

TF4 2RH.

VALVES

TUNERS

Telephone:  
 Telford (0952) 501618

SEMICONDUCTORS  
 Integrated Circuit  
 & Socket

SEMICONDUCTORS  
 Diode

TRADE  
 COUNTER  
 OPEN 6  
 DAYS  
 EACH  
 WEEK

TUBES  
 Monochrome &  
 Regunned Colour

SOLDERING IRONS

Television  
 Video  
 Audio  
 Microwave

SOLDER &  
 ACCESSORIES

S.A.E. FOR FREE  
 CATALOGUE. A4 SIZE

Try Us.

We endeavour to provide a fast delivery of top  
 quality components for the keenest price.

## TRADE REPAIR WORKSHOP

Video, T.V., Hi-Fi. Any make. Free Estimates same day. Exchange  
 Panels G8, G9, G11, GEC, Thorn 3000, 8500, 9000, 9600, Grundig  
 S011 6011, Bush T20/22, 3 months guarantee.  
 Panels £17.25 + £2.50 p/p.

COLOURTRONIC SERVICES,  
 96 Ilford Lane, Ilford, Essex. 01-478 0782

ACCESS - VISA

## EAST ANGLIA SUPPLIES

For your fully serviced colour televisions  
 ready for sale or rent at realistic prices  
 with free delivery (just petrol charged)  
 anywhere for sensible sized orders.

G11s from £70 + VAT  
 KT3s from £85 + VAT  
 K30s from £95 + VAT  
 ITTs from £50 + VAT  
 Decca from £50 + VAT  
 T20s from £50 + VAT  
 9000s from £35 + VAT  
 VHS Videos.  
 Ferg 3V29, 3V30  
 NatPan NV2000, NV2010

MANY OTHER  
 MAKES  
 REGULARLY  
 STOCKED AND  
 CHEAPIES FROM  
 ONLY £25 + VAT  
 FULLY SERVICED.

Contact John, Dave or Steve for personal  
 friendly attention on  
 0223 69215 or 0353 61462

## BOURNEMOUTH

LARGE STOCKS OF  
WORKING  
NON-WORKING SETS,  
MOST MAKES AND  
SIZES.

FAIR PRICES –  
TRADE ONLY  
WAREHOUSE OPEN:  
Mon-Fri 9-1, 2-5; Sat 9-1

HILLIER'S, UNIT 2A,  
11-15 FRANCIS AVENUE,  
WALLISDOWN. TEL: 0202 581932

## Trent Tubes

31 RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM  
PHONE: (0602) 813329

ALL tubes guaranteed for 2 YEARS  
EXTENDABLE TO 4 YEARS

THE PROFESSIONAL REBUILDER

All STANDARD DELTAS (A56, A66/120 etc.)  
ONE PRICE £30.00

A51-161 – A51-163 £43.00

A51-A56-A66/500/510 (20AX)  
One price £43.00

A56-A66/540 (30AX) £49.00

560DZB22, 510VLB22 £46.00

SONY TYPES FROM £55.00  
SPECIALIST SONY SERVICE

1000's more types available. VDUs, MONOs, Industrials etc.

Suppliers to Broadcasting Authorities  
& National Companies

ALL PRICES EX WORKS + VAT & EXCHANGE

WE SPECIALISE IN JAPANESE TYPES

DELIVERY SERVICE AVAILABLE

QUANTITY DISCOUNTS

TECHNICAL ADVICE SERVICE AVAILABLE

## IRISH T.V. DEALERS

Brand new re-gunning plant operating.

— TOP CLASS TUBES —

B/W – Delta – In-Line – P.I.L.

CHRIS KELLEHER'S T.V.

Kanturk, Co. Cork

Store open 9 to 8 pm. Sunday 10-1 pm.  
029-50046 – Wanted 300 VHS video tapes

ONE  
MONTH  
ONLY  
OFFER

## INTERTEL TRADE TV'S

ALL  
SOLID  
STATES

– ONE PRICE ONLY

£16.00 + VAT  
(Off Pile Price)

DIRECT FROM SOURCE  
DELIVERIES ARRANGED  
DISCOUNTS ON QUANTITY  
MOST MAKES AVAILABLE

INTERTEL  
UNIT 27  
WHESOE ROAD  
DARLINGTON  
CO DURHAM

HOT LINE  
DARLINGTON  
0325  
486896

# TELEVISION

## COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	–	–
DECCA 13/30	3.00	–	7.00	5.00	–	4.00
BUSH A823	4.00*	–	10.00*	5.00*	2.50	4.00
THORN 8/8½	–	–	10.00	5.00	–	5.00
PYE 205	3.00	3.50	5.00	10.00	–	–
THORN 3/3½	5.00	5.00	5.00	8.00	–	10.00
G8	6.00	–	8.00	7.00	15.00	5.00

\*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.  
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

**GOLCAR T.V. SERVICES** (formerly LAVITE LTD.),  
Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273  
Callers by appointment only.

## FOR SALE

## Sabaco

For a  
great deal!

VAN LOAD DIRECT FROM SOURCES

### ALL SETS OFF THE PILE

Most makes/sizes available  
e.g. Black faced Decca £10,  
Thorn 8800/9000 etc. £20,  
B/W £1.

All above offers minimum  
quantity of 10 sets or more.

ALL PRICES SUBJECT TO  
VAT & AVAILABILITY.

VHS VIDEOS  
with guarantee


in good

working order.

Ferguson 3V22

from £100. Any

quantity

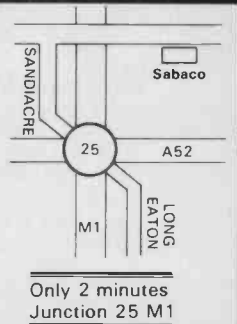


Only 2 minutes  
Junction 25 M1

## ANNOUNCEMENT TO SCOTTISH TRADERS TOP QUALITY OF VHS VIDEO'S & TV'S

Large selection of VHS Video's  
and TV's in quantities of  
2's or 100's at very  
competitive prices.

OPEN 6 DAYS A WEEK  
9.30 am to 5.45 pm

For further details telephone:

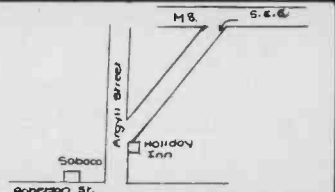

Sabaco  
75 Robertson Street, Glasgow.  
Glasgow. 041-221 2146.  
(2 minutes from M8).

Sabaco  
46A Derby Road,  
Sandiacre,  
Nottingham. (0602) 397555.

LEADER LCT910A C.R.T. Tester rejuvenator. 5  
months old. Used twice. As new and complete £149.  
M. Russell, 01-891 4268.

## REPAIR SERVICE

### PRINTED PANEL REPAIR SERVICE

Printed panels and remote control handsets  
repaired. Most makes and models serviced.

RING 0934 418545  
for Price List or Quotation.

2 SETS of fully reconditioned tube re-gunning plants  
for sale. Training provided from only £3,995. Tel: 0582  
410787.

YAESU. Scanners up to 902 MHZ. (No gaps) others  
from £175. Heathkit SB200 1200W. Linear. AR88D.  
B40 Lafayette £85. Oscilloscopes wavemeters. Receiv-  
ers. Transceivers. Large stock manuals. Crystals. etc.  
SSB PRODUCTS, 42 Halvarras Road, Playing Place,  
Truro. (0872) 862575 – SAE.

SALDELCO Field strength meter model FS-719-BE  
coverage V.H.F. 47.5-230 U.H.F. 470-860 built in  
speaker & 2 x 20 db ATT £150 05672 371 evenings.

TELEVISION AND VIDEO BUSINESS. Rental ac-  
counts. Sales and repairs. Includes service equipment,  
spares and stock. No premises. £15,000. Tel. South-  
ampton 814318 for details.

# SERVICE PAGES

## TORQUAY, South Devon

### TV Sales, Repairs and Rental Business.

Warehouse + W/shop, Office  
and Display area. Established  
10 years.

Main Agency and Sole  
Distributor in Devon for  
Colour TV manufacturer.

Long lease.  
Profit Margin 30% per annum.  
Price £65,000.

Reply to:  
Box No. 200 please.

## DEVONICS

### Quality Rebuilt Tubes 2 YEAR WARRANTY

470 ERB22	£43
510 KCB22	£45
A51-161/500/510/ 570/580/590X	£45
560 AKB/DZB/TB22	£45
A56-500/510X	£45
A56-540X	£53
A66-500/510X	£46
A66-540X	£53
670 XB22	£46

Deltas from £30  
Plus carriage and VAT  
2A BARTON HILL ROAD,  
TORQUAY TQ2 8JH  
0803 - 33035

## SERVICE SHEETS

### TECHNICAL INFO SERVICE - 76 Church St - Larkhall - Lanarkshire ML9 1HE

World's sole publisher of Comprehensive T.V. Repair Manuals. Largest known stocks of Service Manuals & Sheets from 1935 to latest for all kinds of equipment, espec. T.V. & Video.

Save time & expense - our big catalogues of Service Manuals & Sheets with Chassis Guide & £4 Vouchers - only £3 - updated free.  
Any published Service Sheet £2.50 & I.s.a.e. except CTV/Music Centres - £3.50 & I.s.a.e.  
Service Manuals from £4.50 to £39 - e.g. Thom 8000/8004/8500/8600 only £9.50.

T.V. Repair Manuals £8.50 each. Special offers The 5 McCourt £40. The 11 Tunbridge £88.  
Video Repair Manuals £4.50 per Chassis or all 10 for £25.

Comprehensive Practical T.V. Repair Manual £9.50. The Practical Radio Servicing & Repair Manual £9.50.

#### UNIQUE COLLECTIONS OF CIRCUITS & LAYOUTS

British CTV from hybrid to modern in 3 giant binders for only £55. Also 2 giant binders packed full for £35 pair.

Foreign CTV. Portable/Standard Mono TV. Domestic Equipment.

NEW RELEASE:- Offered to 'TELEVISION' readers for £20 (full price £25).

Giant collection of modern portable British CTV circuits and layouts.

The Integrated British CTV Repair System - 4 giant binders full of circuits & layouts with 6 big Repair Manuals. Covers 1968 to the '80s. Plus! £140.

The Integrated TV Repair System - 16 big Repair Manuals/8 giant binders plus service data and other manuals. Covers 1968-1985. Priced separately over £300. Our Offer for £250 cwo or supplied in 12 monthly sections at £25 month. Offer includes any new TV publications we publish during 1 year from placing order. Service manuals to cover our range would cost over £1,000.

The Integrated Video Repair System - 10 booklets and 4 giant binders cover the early videos, all formats to V2000, 3V30, Sanyo 9300. Only £55.

S.A.E. brings any quotes required plus free magazine, service sheet & other offers.

Phone 0698 884585 before 5 pm; 0698 883334 after 4 pm.

Thousands of service sheets in stock not listed here. Tape recorders, TV, radio, record players, transistors, amplifiers. All main chassis sheets @ £3.00 each. Tuner sheets @ £3.00 each plus large stamped addressed envelope. Please mention name of model when ordering. All orders received 8 am any morning, posted off by 9 am-1 o'clock same day. Please pass on to a friend, if not wanted. Free fault finding chart if wanted.

CAR RADIOS: PHILIPS, MOTOROLA, RADIO MOBILE, HITACHI ETC.

C. CARANNA 71 BEAUFORT PARK, LONDON NW11.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

★★★★★★★★★★★★★★★★★★★★  
SERVICE PAGES SERVICE PAGES  
PLEASE MENTION TELEVISION WHEN  
REPLYING TO ADVERTISEMENTS  
SERVICE PAGES SERVICE PAGES  
★★★★★★★★★★★★★★★★★★★★

## TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

Colour £3.00 Mono £2.00

Manual prices on request.


All our prices include post and packing costs.

Send stamped envelope for free catalogue and any enquiries.

SANDHURST TV SERVICES (MAIL ORDER)

49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 8DU.

## AERIALS

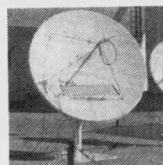

**Euro-Sat**  
Parabolic Dish Antennas  
(Parent company est. in  
TV communications since 1969)  
SATELLITE TVRO ANTENNAS  
TOP QUALITY SOLID  
GLASSFIBRE DISH ANTENNAS

1M. DIA 11-12.4 GHZ BANDS	£77.00
1.2M DIA 11-12.4 GHZ BANDS	£93.00
2M DIA 11-12.4 GHZ BANDS	£215.10
3M. DIA 11-12.4 GHZ BANDS	£437.00

All dishes come complete with feed support  
Trade & Export Enquiries Welcome  
Prices do not include delivery

**Euro-Sat**  
107 Cross Street, Sale, Cheshire, England.  
Tel. 061-437 2631 061-881 4249

## AERIAL BOOSTERS

**B45-UHF TV** next to the set fitting. Gain 10db (trebles gain), works off PP3 type battery or 8V to 14V working. Price complete (excluding battery) £5.00.

**Video Transmitter.** This will transmit good quality pictures and sound more than 30ft. Price £8.90 (S.A.E. for more details).

We also make aerial boosters for VHF/FM radio £7.70, and VHF television, prices £7.70 & £8.70. p&p 50p per order.

**ELECTRONIC MAILORDER,**  
62 Bridge Street, Ramsbottom,  
Lancashire, BL0 9AGT.

Tel: Ramsbottom (070 682) 3036.  
S.A.E. leaflets. Access/Visa Welcome.

## CLEARVIEW AERIALS

Tunable masthead amplifiers for FM and Band 3 (most) gain 30dB. NF 0, 7dB and UHF incl. amateur band gain 30dB NF. 1, 6dB. 15dB and 26dB masthead ampl. WB, grouped NF 2dB splitters, combiners, notchfilters, diplexers etc. Trade and retail.

Send large SAE for our comprehensive catalogue

**CLEARVIEW AERIALS,**  
173 Kings Road,  
Kingston Upon Thames, Surrey.

EVERYTHING NECESSARY for multi-outlet and high gain installations. Cables, outlets, splitters, channelpass filters, diplexers, masthead amplifiers, distribution amplifiers, brackets, masts, aerials, etc. Use trade gear and save pounds. Catalogue 75p (refundable). Professional advice. WRIGHTS AERIALS, 43 Greaves Sike Lane, Micklebring, Rotherham.

## SATELLITE T.V. RECEPTION EQUIPMENT

Throughout Ireland

2m G.R.P. dish with feed support and polar mount. 11GHz block downconverters and indoor receivers. PAL/SECAM colour T.V.'s with in-built receiver.

**KESH ELECTRICS LTD.**  
Main St., Kesh, Co. Fermanagh, N. Ireland  
Phone Kesh (03656) 31449.

## BUSINESS OPPORTUNITES

### T.V. VIDEO & HI-FI REPAIR & RECON SALES BUSINESS

Ilford area.

Established 9 years. Long lease. Large fully equipped workshop. Shop showroom. Great potential. Capital investment needed.

Would consider partnership  
or for sale £20,000.  
BOX No. TV 196

### VIDEO TV. HI FI SHOP NW6

+ Stock Rooms/Workshop.

T/O exceeding £115,000 p.a. (£4,000 from repair).  
Main dealership.

12 years new lease. Rent £2,300 p.a.  
PRICE £25,000 FOR QUICK SALE

Please reply to:

TV BOX 197

MISCELLANEOUS

GET  
**SHARP PARTS FAST**

TELEPHONE  
**0734 - 876444**  
TELEX 848953



**SHARP**  
Main U.K. Spare Parts Distributor


Audio-TV-Video ★ Microwave ★ Photo-copier ★ Typewriter

All U.K. model spares available. Same day despatch of orders received before 1pm.  
Microwave, photocopier and typewriter spares to authorised service dealers/centres only.

WILLOW VALE ELECTRONICS LTD.,  
11 Arkwright Road, Reading, Berks.

**The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes**

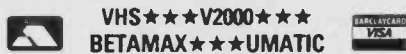- Part 1. The Colour Signal
- Part 2. The Receiver Decoder
- Part 3. Receiver Installation



VHS★★★V2000★★★  
BETAMAX★★★UMATIC

For full details telephone  
**0253 725499 (Day)**  
**0253 712769 (Night)**

Or send for precis details  
**FLINTDOWN CHANNEL 5**  
339 CLIFTON DRIVE SOUTH,  
LYTHAM ST ANNES FY8 1LP  
(enclosing this advert)

NAME .....

ADDRESS .....

TEL: .....

SOLE SUPPLIERS TV/VIDEO Repair manuals/circuits, 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/m.centres/stereos £3.50. LSAE with every order/query please brings free price list/magazine inc s/sheet - or phone 0698 884585 (883334 outside business hours) TIST, 76 Church Street, Larkhall, Lanarkshire.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

**BOOKS AND PUBLICATIONS**

MACDONALDS R & TV BOOKS. New 74/75 £15. 75/76, 76/77, 77/78, 78/79, 79/80, 80/81, 82/83, 83/84, 84/85 £22.50. Free delivery. U-VIEW, 29 Warnsworth Road, Doncaster. 0302 855017.

NEWNES RADIO AND TELEVISION servicing, book one to 1974-75. 25 books £60. Tel. 0767 260524.

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years usually in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

**WANTED**

WANTED. FREQUENCY COUNTER and Sweep Marker generator for video servicing. Telephone Grimsby 884362.

WE PURCHASE UNDAMAGED old T.V. tubes of types A67-150X A66-500X or equivalents. Good prices paid. Phone 052 785 2639.

WANTED. Good condition exhaust pumps. Backup and diffusion with inlet port. For tube plant. What available and price Box 199.

AGENTS REQUIRED. To wholesaler FULL range of rebuilt CR tubes. Full details: 0602 813329.

WANTED, EX RENTAL colour TVs. Any quantity. Prompt collection, cash paid. Sheffield 754865.

WANTED. For new small business, regular supplies of good ex-rental videos - colour TVs, trade repair enquiries welcome. Doncaster 0302 744330.

**METERS**

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

**AVON METERS**

We buy and sell and repair TV coinmeter. Reasonable prices, one year guarantee.

213 Cheltenham Road,  
Redland, Bristol.  
0272-425281

**VIDEO**

**EX RENTAL VHS VIDEOS**

★ ★ ★

100's IN STOCK

★ ★ ★

**CONTACT MICK ON**  
**021-772 1591**

**Satellite TV available now!**

Manufacturers and suppliers of low-cost TVRO equipment and components for European and worldwide satellite TV reception.



Satellite TV Antenna Systems Ltd.  
10 Market Square, Staines.  
Middlesex TW18 4RH


Please send free information on Satellite TV Reception

Name .....

Address .....

Post coupon to: Satellite TV Antenna Systems Ltd  
Freeport, Staines, Middlesex TW18 1BR.

TV

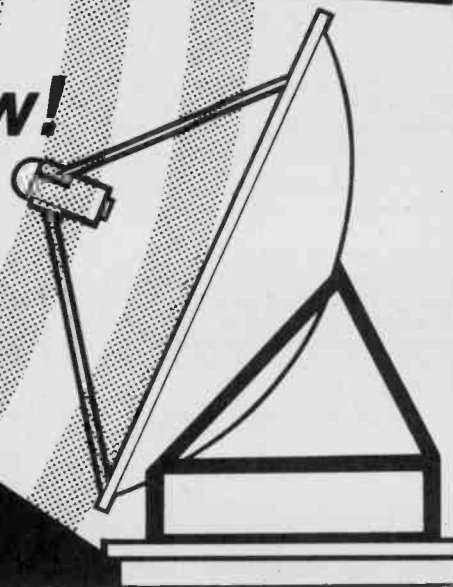



If an advertisement is wrong we're here to put it right.

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

**The Advertising Standards Authority** ✓

ASA Ltd. Dept 3  
Brook House, Torrington Place,  
London WC1E 7HN

## IRISH T.V. DEALERS & ENGINEERS

Make extra money selling Ex-Rental Colour TV's.

**NEW LOW** summer prices. Off the pile from **£30**, good working order from **£50**, all prices **VAT INCLUSIVE**. Most leading makes in stock, fresh stocks weekly. Delivery to any part of Ireland.

Export orders welcome for countries using PAL System. We also stock VHS Videos and regunned Colour tubes.

### TELE SPARES LTD.

Unit 113, Elm Road,  
Western Industrial Estate,  
Dublin 12, Ireland.  
Telephone: Dublin 521211/521756.

## TUBES

We are specialist suppliers of new and rebuilt T.V. tubes including:

44-271	66-510
47-342	66-540
47-343	67-611
49-191	67-701
51-110	470ERB22
56-120	470ESB22
56-140	470FTB22
63-120	470GYB22
66-120	490DVB22
66-140	510HGB22
67-120	510JEB22
67-200	510JGB22
67-150	510JKB22
	510KCB22
470BGB22	510RCB22
470EJB22	510RFB22
490DKB22	510RJB22
510GLB22	510SFB22
	510VLB22
AXT37-001	510VSB22
AXT51-001	560AKB22
AXT56-001	560AWB22
37-590	560BYB22
51-161	560DAB22
51-500	560DMB22
51-510	560DTB22
51-570	560DYB22
51-580	560DZB22
51-590	560EGB22
56-500	560HB22
56-510	560TB22
56-540	560VB22
56-611	560ZB22
56-701	670XB22
66-500	

## T.V.s


We have quantities of Trade T.V.s including:

Philips G8  
Thorn 8.8K  
Thorn 9K  
Thorn 9.8K  
Decca 80  
Decca 100  
Bush T.20


## EXPRESS T.V. SUPPLIES

The Mill, Mill Lane,  
Rugeley, Staffs.

08894 77600

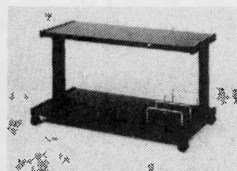

**T.V. VIDEO  
STANDS  
from £2.50**

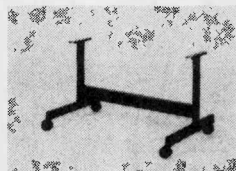

Direct from manufacturer, slight seconds, ends of runs and current models.

For details . . . TELEPHONE: 0422 240011

or write: **ACRE PRODUCTS LIMITED**  
Jumple - Mixenden - Halifax - W. Yorks HX2 8UD

EMCO - EUROSonic - GRUNDIG - TELETON + ALL BRITISH MAKES  
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●

### IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it — no quibble — no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY  
TV COMPONENT BY RETURN  
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

**TELEPART (WTON)**

32 TEMPLE STREET,  
WOLVERHAMPTON (0902) 773122

TDA2008 £2		1A/1600V 10p	G11 condenser £1.75	HITACHI CPT225 CHASSIS WITH TELETEXT £30	
Philips small stereo headphones £4	2 amp bridge rec. wire end 15p	CV 8617 10p	300M + 700 320V £1.80	10 Mixed TV & radio speakers £4	Philips GP422.4CH (£40 cost) £6
Stereo Philips headphones Electret N6325 £13	Y 716 10p	Y 729 30p	200 + 100 + 100 + 50 300V 50p	Philips car radio speaker door pair £7	MODEM Line Terminal Unit VM6501 £6
SN76545N (Tynr IC) £3.50	Y 730 10p	Y 827: 6A/1KV 20p	150 + 200 + 250M 300V 50p	2x HI-FI Philips car tune up tweeter EN8320 £10	Designed to work at 1200/75 or 1200/1200. Diagram and Connection Data Supplies
TCEP100 4000 Thorn i.c. £1.75	Y 963 5p	Y 939 50p	Chassis complete £35	ITT CVC45 8 way resistor unit for v/cap £3	Indicator Tube ITT 58705 £1
Rank UHF 4 push button tuner £4	Y 997 30p	Min 12 volt Relays 75p	Computer Transformer 20V/2.25A; 20V/1.5A; 17V/5A; 19V/5A; 28V/0.5A £3	12 Volt Aerial Changer over Relays 144 Mc/s 45 watts 50p	8 Seg Display FND500 20p
GRC power supply PC743B £10	R 1038 40p	R 1039 40p	Torroidals 240V/240/6V/4 amp/6v 500mA in / out ----- £3.75	8 SEG LED Display with driver I.C. LM1017 50p	Mullard 12.5V/170 Mc/s 45 watts £4.00
Rank front panel Z950 £5	R 2010b £1	R 2019 50p	Mains trans 240/12v-0-12v 2 amp £3.50	20AX GEC Split Diode lead £1.00	BLW60C Mullard Broadband R.F. power modules UHF, BGY22E £10.00
Power panel 8.500 Thorn £5	R 2210 50p	R 2219 50p	Voltage Regulators +5V/UA78P0SSC 30p	Various Tools and Accessories	PT4236C, PT8706C £3
Fidelity mains switch & lead and filter panel £1	R 2257 50p	R 2265 50p	-5V/LM79MO5CP 25p	TV V/Aerial 3000 or 750 L.C.D. clock display with alarm * D/P push mains switch 20p each	ITT Micro Phone M5 50p
Fidelity mono lopt with diode FBS1245AE £3	R 2305 50p	R 2306 50p	-8V/79M08c 30p	Mains lead & two pin socket for radio cassette 35p	Sub-min Relay low voltage 50p
6 TAG print mains switch PREH 1983 ITT 75p	R 2322/2323 pair 80p	R 2323 15p	+6V/78M06c 30p	3 Video Leads £1.00	Mains relay coil 230v 30p
T134A Lopt panel £10	R 2396 50p	R 2461 80p	+10V/78LA10 20p	Xceltr cutter £3.90	Philipp P33 batteries 10 for £3
Rank T603A tuner on panel £6	R 2461 80p	R 2030 80p	LM 337 30p	TV loop aerial 75p	12v battery holders A.A. 50p 1.5 battery lead 30p
Scan control panel Z544 £3	R 2030 80p	R 2443=BD124 R2737 1 40p	LM 342/18 30p	Radio Telescopic Aerial £1.00	
Rank Z582 IF £3	R 2461 80p	R 2737 1 40p	LM 340T 5.0 30p	Philips Neon Lamps for TV sets 5p	
Rank convergence Z910 £3	R 2461 80p	R2738=TIP41 R2775=TIP41c R3129=TIP47 40p	+12V/LM 340T12 50p	Freeze £1.20	
GEC IF tuner panel PC786B £12.50	R 2030 80p	S 2008/8 40p	+15V/78M15 15p	Foam Cleaner £1.20	
ML 232 I.C. on panel tuch unit Fidelity £3	S 2008/8 40p	S2D898B £1	+18V/MC78M18 20p	Contact Cleaner £1.20	
Httachi power panel PC036A £1	S2D898B £1	Httachi sets etc.	+24V/78M24 30p	Cans of Anti Static, Degrease Cleaner and Anti Corona All at £1.20	
Rank IF 742 £3	STR454 £2	STR454 £2	MC 7724cp 40p	Push Button Mains 75p	
Rank decoder Board MTS 200/1 Tuner & IF £12.	25C940 £1	BU 105/04 80p	TIS 90 10p	Lorlin Full Remote Relay Switch fit most T/V sets, mains 4 tag, 2 tag 12 volt £1.00	
Z733 Rank mains in put-panel £1	BU 108 80p	BU 124 50p	TIS 91 20p	Mains timer. 13 amp — up to 2 hours: easy to use, plugs into socket £3.00	
G11 Chroma Can 3113 108 25300 £3	BU 126 80p	BU 180a 65p	TIS 92 20p	Sellotape PVC Electric Insulation 50mm x 20M 70p	
20AX Line in coil 50p	BU 204 70p	BU 205 60p	TIS 93 20p	Screen locking agent, large can £1.50	
GEC switch mode trans 20AX £1.00	BU 206 60p	BU 207 60p	U 19885 40p	20 GEC Service Manuals £5.00	
ITT CVC20 etc mains switch 60p	BU 208 80p	BU 208A 80p	U 3832 15p	Red E.H.T. LAED and Anode Cap 10 x G11 Cap 470/250 £15.00	
ITT 2,800 mains remote switch 50p	BU 208A 80p	BU 208D 90p	U 3845 15p	Weller solder iron 15 watt/25 watt £5.00	
Panel £8.00	BU 222 80p	BU 222 80p	MR 508 10p	2 way baby alarm/intercom with long leads £5	
Line o/p frame panels GEC 20AX £10.00	BU 326 80p	BU 407 60p	MR 501 10p	Philips universal battery tester/charger, fuse/bulb tester To Clear £2.50	
GEC 20 AX £1.00	BU 407 60p	BU 426V 60p	MR 502 10p	12V Nicad pack. "AA" £6.00	
Transductor ITT CVC40 Push Button Unit & Mains Switch £8	BU 426V 60p	BU 500 60p	BCW 71R 10p	Hitachi 7.2v/1.8A Nicad pack £7.00	
Rank Panels Z904 18" Line Panel £10	BU 500 60p	BU 508A 60p	BYF 1202 10p	Hitachi TP 007 Battery pack 7.2v/1.6A £6.00	
Z905B Decoder £10	BU 508A 60p	BU 526 75p	BYF 1204 10p	Hitachi Silver Oxide Battery G13 UCC357 IEC SR44 1.5V 60p	
Z736 Tuner I.F. £10	BU 526 75p	BU 807 75p	BYF 3126 40p	70ML Silicone Sealer (clear) £1	
A805 Conv. 7/8 £2	BU 807 75p	BU 824 50p	BYF 3214 40p	100 Coax Plugs £12.00	
T136A Scan Drive £10	BU 824 50p	BUW 84 30p	BYX 10 6p	De-solder pump + 2 nozzels £5.20	
Z780 Line O/P £10	BUW 84 30p	BYW 20-08-9 £1	BYX 36/600 35p	Plastic box for i.c.s 6"x3"x1/2" 50p	
Z968 £10	BYW 20-08-9 £1	TIC 106a 30p	BYX 38/300 25p	Can of handy oil 'mobil' 40p	
Z582 I.F. Panel £5	TIC 106a 30p	TIC 116m 40p	BYX 49/600R 75p	Flat Red LED £7	
Rank Power Panel (T092 case 2A/400V) 20p	TIC 116m 40p	TIC 116n/Y 1003 35p	BYX 55/300 10p	500gm 60/40 solder reel £2p	
300+300m with diodes degaussing £3	TIC 126N 40p	TIC 206m 30p	BYX 55/600 (Bead) 10p	Clearweld glue pack 30p	
BA 301 35p	TIC 225S 40p	TIC 226E 40p	BYX 71/350 20p	Dual v/u meter -20 - +10db £1	
TA 4127 £3	TIC 226E 40p	TIC 226m 30p	BYX 71/600 20p	K30 thermistor 232266298009 £75	
HD 3884 2A23 £3	TIC 226m 30p	TIC 236m 30p	BYX 72/300 20p	GEC Mains Power Supply R.E.G. 1kg reel of solder £8.00	
TA 4184 £1	TIC 236m 30p	TICV 106D 10p	BYX 36/600 50p		
TA 2125 £1	TICV 106D 10p	TIP 29 20p	BYV 95B 10p		
TA 4190 £1	TIP 29 20p	TIP 30A 35p	BVY 95C 12p		
TA 4138 £1	TIP 30A 35p	TIP 30B 40p	BYZ 106 10p		
TA 4196 £1	TIP 30B 40p	TIP 30C 45p	BPW 41 15p		
TA 4174 £1	TIP 30C 45p	TIP 31 30p	BYW 56 2A/1000v G11 8p		
TA 4139 £1	TIP 31 30p	TIP 32 25p	BZU 15/24 54p		
TA 4198 £1	TIP 32 25p	TIP 33B 50p	BZY 93c75 50p		
TA 4167 £1	TIP 33B 50p	TIP 33C 50p	BZV 15/18 30p		
TA 4199 £1	TIP 33C 50p	TIP 34A 60p	BZV 15/30 30p		
BA 546 £1	TIP 34A 60p	TIP 34B 60p	BZW 70c6v2 10p		
BA 328 £1	TIP 34B 60p	TIP 34C 70p	BZX 79.3v 10p		
TA 4176 £1	TIP 34C 70p	TIP 35B 50p	Bush thyristor RCA 76122 £1		
TA 4145 £1	TIP 35B 50p	TIP 35C 70p	Transformer 240v/20v-500MA 75p		
TA 4191 £1	TIP 35C 70p	TIP 35D 80p	Chassis type Transformer 240v/12 Volts 500mA 75p		
HA 11710 £1	TIP 35D 80p	TIP 36 30p	240V/2 tube base £2		
TA 4188 £1	TIP 36 30p	TIP 36C 70p	Tube Base Rank & G11 £1.20		
TA 4197 £1	TIP 36C 70p	TIP 41B 40p	6v-9v-13v tape motor 75p		
TA 4183 £1	TIP 41B 40p	TIP 41D 70p	Swiss made 250rpm/240V motor very small 75p		
TA 4197 £1	TIP 41D 70p	TIP 42/BRC 6109 30p	Infra red led LD57CA 15p		
TA 4183 £1	TIP 42/BRC 6109 30p	TIP 48 30p	Mono scan coil £3		
TA 4197 £1	TIP 48 30p	TIP 49 30p	G 8 transductor £1.25		
TA 4183 £1	TIP 49 30p	TIP 57 30p	AT 4041/41 transductor £1		
TA 4197 £1	TIP 57 30p	TIP 100 30p	VHF 3 Transistor rotary tuner £1		
TA 4183 £1	TIP 100 30p	TIP 102 30p	DX-TV £1		
TA 4195 £1	TIP 102 30p	TIP 115 50p	15K-20 turn pots 20p		
TA 4175 £1	TIP 115 50p	TIP 117 50p	Thorn panel 6x100 pot + changeover switch (Irish) 50p		
TA 4177 £1	TIP 117 50p	TIP 120 35p	Battery converter TA 75 for colour TV, 1224v Thorn 3787 £6		
TA 4192 £1	TIP 120 35p	TIP 125 35p	Thorn 3500 2A cut out 50p		
TA 4146 £1	TIP 125 35p	TIP 130 30p	Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit £6		
The Service Engineers Guide to Teletex £1.50	TIP 130 30p	TIP 131 25p			
Teletex Colour Training Manual £3	TIP 131 25p	TIP 136 50p			
Mains Trans C. Core 240v 4v+4v 4v04v 2AMP 12v lamp £2	TIP 136 50p	TIP 140 50p			
Mullard split diode AT2076/80 £6	TIP 140 50p	TIP 640 60p			
4 Types Fidelity front panels with i.c. & pots £2 each	TIP 640 60p	TIP 2955 35p			
Amstrad TV chassis Complete damaged print £5 + £5 post	TIP 2955 35p	T 6032 30p			
BB 103 £1	T 6032 30p	T 6036 40p			
BB 105A x12 £1	T 6036 40p	T 6040 40p			
BB 105B x12 £1	T 6040 40p	T 6047 40p			
BB 105G x12 £1	T 6047 40p	T 6049 40p			
BB 121a 10p	T 6049 40p	T 6051 40p			
47 10p each	T 6051 40p	T 6052 40p			
A 823A chassis Scan drive £5	T 6052 40p	T 9004 40p			
IF £3	T 9004 40p	ZTX 107 10p			
Scan control panel NEW A31/510 tubes with s/coil £6 + £2 post	ZTX 107 10p	ZTX 108c 10p			
	ZTX 108c 10p	ZTX 109k 5p			
	ZTX 109k 5p	ZTX 213 5p			
	ZTX 213 5p	ZTX 341 10p			
	ZTX 341 10p	ZTX 342 10p			
	ZTX 342 10p	ZTX 384 10p			
	ZTX 384 10p	ZTX 451 10p			
	ZTX 451 10p	ZTX 550 10p			
	ZTX 550 10p	MJ 2253 60p			
	MJ 2253 60p	MJE 3040 60p			
	MJE 3040 60p	MJE 2209 10p			
	MJE 2209 10p	SP 8385 50p			
	SP 8385 50p	SAB 3205 £1.00			
	SAB 3205 £1.00	SAB 4209 £1.00			
	SAB 4209 £1.00				

# SENDZ COMPONENTS

## TO ORDER SEE BACK PAGE

<b>Thorn Spares</b>		KT3 Decoder	£8
New 9000 Decoder	£8.50	K30 Sound OP	£4
9000 Frame panel	£8	Hitachi 2A1500V metal case wire end	£20p
9000 Cyclops panel	£1.50	FARST/REC	£20p
8000/8500 timebase panel	£8	Fidelity Tube Base with transistor & focus pot	£1.50
8800 convergence panel	£6	Bush Tube Base on panel	£1.00
8500 convergence panel	£6	<b>Line Transformers</b>	
4000 Power supply	£3	1690 Lopt	£6
1600 Mains lead, switch		Hitachi Split Diode and GEC 1981 to 1984	£13
3500 6 push button + cable form	£1.50	2 J/Pots 3,500 1 off each type	£3.00
1705 1vNPN T066 80v/6A	10p	G8 Symmetry Coil	£2.00
9000 Sound output panel	£1	G8 Trans. Philips	£7.00
3500 Focus unit	£1.50	G11 Split Diode	£2.00
3500 Mains Trans	£4	CVC820 Split Diode ITT	£10.00
3500 cut outs	10 for	Thorn B/W AD5308F + Stik + Lead	£1.50
3500 IF panel	£2	1690 Thorn EHT over-wind with diode lead & anode cap	£2.50
3500 Frame panel	£3	GEC 2040	£3.00
3500 Line panel	£3	GEC 2110	£7.00
3500 A1 Diode	20p	Mullard AT 2036	£1.50
Export 3500 IF panel	£2	Pye 169 Line Trans	£3.00
IC board with set of SN74LS4000 Tube base	£4	Pye mono	£3.50
3500 A1 pots	50p	Rank mono 1704A	£3.50
Beam limiter panel	£1.50	Split Diode Trans	£7.00
3500 Power panel with Y969	£1	GEC 20 AX Rank Z522	£3
3 Way regulated adaptor 240V 6V/7.59V/300mA	£3.50	Rank L.O.P.T. Z970	£3
Rank/Toshiba preh unit 0354	£9.50	CVC 5-8-9	£3.00
2 banks of 3 PB unit, Pye 731	£2	CVC20 ITT	£3.50
4 Push button unit preh	£1.00	A12080/15	£5.00
6 Push button VHF/UHF for v/cap. GEC-Decca type	£7.00	CVC30 ITT	£5.00
7 Push button for CVC5 ITT	£8.00	CVC32 Line Tran	£4.75
KT3 12 Push button unit	£2	CVC300 Line Trans	£6.00
KT3 (Export) 12 P.B.U.	£2	CVC40 Slip/Diode	£12.00
6 Push button Unit Thorn	£1.00	GEC 45	£5.00
6 Push button Unit fits GEC & Decca etc.	£6.00	GEC Portable G10T2041	£3.00
Hearing aid unit	£3	GEC Portable G10T2046	£3.00
6 Push button unit PYE 713	£7.00	EHT Split Diode Leads ITT	£1.00
7 Button Unit GEC with Lamps	£7	1x panel "14" Fidelity portable	£5
Bush T151A 6 button unit with Pos & mains lead, 6 bush buttons. Bush	£6.00	3500 L.O.P.T. & HT Trans	each £2
		LOPI Rank Z763	£5
<b>Mains Droppers</b>		<b>Triplers</b>	
G8 2R2 + 6R	£1.25	ITT CVC 5-8-9	£3.50
G8 47R 15 watt	75p	Rank T251E Tripler	£2.00
Pye 731 3+56+27R	50p	Rank ITTCP A823	£3.50
Pye 3R5/15R/45R	50p	TU 25 30K Rank	£3.00
Thorn 50/17/1K5	£1.00	8500 Triplers	£6.50
120/20/20/48/117	£1.00	11 TEZ Rank	£3.00
270/106 for Thorn 4000	50p	G9 Philips	£4.00
18/320/70/39	£1.10	GEC 2110	£4.00
Thorn 50-40R-1K5	50p	3500 Thorn	£3.00
Ae Socket & Lead		9000 Thorn	£5
GEC, ITT, Philips, Pye	25p	9500 Thorn	£4.50
7x332 Tubes	£1	2040 GEC	£3.50
Rank Toshiba Tube Bases	30p	GEC TVM25 Tripler	£2.00
		Universal Tripler	£5.00
		TVK 769	£3.00
		G8	£4.00
<b>Speakers</b>		GEC 825 ITT CVC 20/25/30/32	£3.50
Pair 25 watt 4Ω speaker & tweeter in cabinet	£15.00	Decca 80 TVK 52	£4.50
6x4 G11	25 ohm	Grundig TVK 52	£2.50
5/2x2/2/2	3 ohm	ITT BQ Pye 731	£3.00
5x3	80 ohm	11THY	£4.00
5x3	50 ohm	D22 for Pye 18" colour portable	£4.00
5x3	35 ohm	LP 119363	£4.00
6x4	15 ohm	BG 10041	£3.25
7x3	70 ohm	ITT ultrasonic rec'r panel	£14.00
8x5	8 ohm 15 watt	Video cassette lamps on lead.	
8x5	8 ohm	12-14V	50p or 3 for £1.00
5x3	8 ohm	20 for £5.00	200 for £25.00
7x3	16 ohm	GEC 8 touch unit assy complete with all I.C.s + pots	£4.00
5" dia	16 ohm	G11 E.W. Transformer	50p
5" dia	8 ohm	G11 E.W. coils	£1.00
6 1/2" dia	4 ohm	G11 Transient Suppressors 245V	10 for £1.00
6 1/2" dia	3 ohm	G11 Scan Coils	£5.00
2 1/4" dia	8 ohm	G11 100K tuner pots	12 for £1
3" dia	8 ohm	KT3 IF panel	£6.00
4 1/2" sq.	15 ohm	KT3 line OSC transformer	£1
KT3 speaker	K30	KT3/K30 infra-red receiver head	£1
3" dia	15 ohm	K30 drawer unit with IC's (home)	£10
1690 5x3	12 ohm	K30 drawer unit with IC's (export)	£10
K45 Philip	15 ohm	KT3 AE Sockets	50p
K30 15 watt	75p	KT3 receiver panel	£8
		KT3 line driver transformer	50p
		Pye, K30, GEC, etc. Pre-mains stand-by switch	£1
		Decca 80/100 IF panel	£5
		NPN PNP 80V 6 Amp TO66 O.P. Trans.	pair 25p
		5 button touch tuner BBC121 TV1/2 video with ic SAs 564T/570T	£7.00
		Control panel 5 sliders + mains lead	£1.50
		G11 8 touch button unit replaces old P.B.U.	£24
		Tube base + base unit for 820 Euro chassis	£4.00
		GEC Line O/P Trans. & Rec Stiek for Portable	£3.00
		CVC 20/25/30/35/40 decoder panel	£10
		CVC 25/30/35/40 decoder panel	£10
		(untested)	£5
		CVC 40/45 IF panel	£5
		40K Transducer	50p
		PHILIPS NES11N	£1.20
		LM337M Reg.	30p
		20 GEC Black Spark Gaps	£1.00
		G11 Line Driver Transformer	35p
		KT3 Front Panel Control	10p
		BTW 3050	50p
		<b>TELETEXT DECODER</b>	
		L.C. SAA 5051	K30
		L.C. SAA 5042	
		L.C. SAA 5030	
		L.C. SAA 5020 etc.	£8.00

NEW 1617 THORN Chassis with ICs & AU113	£8.00	9V Power Supply THORN 9V 200 mA	£2.00
30V Power Supply 500MA 4x2V4	£2.50	Rank Secam Decoder Panel UHF & VHF T115A	£13.00
Pye 731 Power Panel	£13	<b>NEW GRUNDIG SPARE PANELS</b>	
6 Diode Universal Triplers	£3.25	Set No. SC4127, SC4337, SC6217, SC6237	
NEW PYE 725 line O/P panel with L.O.P.T. & Tripler	£10.00	<b>GRUNDIG MODULE TYPES</b>	
Thorn Mains Isolator unit for 70-80W. Ex-speaker	£2	Tuner IF. AF TRX LOP. TP preamplifier	
NEW GEC 20AX Power Supply Switch Mode	£12.00	Tuning board, Colour RGB. LED Board.	
Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.capt OPTI	£10	Deflection Board	
Field + Jungle panel for GEC 3133/3135	£1.50	From £3 to £8	
GEC 2110 line panel with transformer	£7.00	<b>Multi-Caps</b>	
GEC 2110 tuner unit + IF Panel	£12.00	4.700/75 6 amp Rip	£2.00
Pye/Chelsea Line op panel	£12.00	350V 300M + 300M	£1.00
Pye 713 IF panel and tuner	£7.00	400V 400M	60p
Pye 713 Chroma	£7.00	350V 400M	60p
Pye/Chelsea Timebase panel with L.OPTI	£10.00	Thorn 3500	
Pye 731 Frame Panel	£5.00	175/100/100/350v	£1.00
Pye 731 Convergence Panel	£5.00	KT3/200/25/385v	£1.00
Pye 731 Chroma	£10.00	300+ 300+ 150+ 100+ 50MFD	
Pye 731 IF panel + tuner	£10.00	350V	£2
Pye CDA/205 panel	£6.00	47/220/350v	60p
GEC portable chassis + LOPTI 2114 New	£4.00	150/150/100/100/320v	£2.00
Thorn 1613/1713 chassis	9.75	250/250/400/350	50p
G9 Power Panel	£6.00	150/200/200/300v	70p
Mono RANK Chassis 127A NEW	£10.00	400/400/200v	£1.70
NEW G9 Frame Panel	£10.00	300/100/100/16/275v	£1.50
NEW G11 IF Panel	£10.00	100/200/325v	40p
		150/150/100/375v	£1.50
		300/300/100/32/32/300v	2.00
		1500/2000/30v	50p
		Jelly pot Thorn 00D4013	£3
		150/150/100/320v	£2.00
		100/350 + 300/200/100/16/275v	£2.00
		225 + 25/380 GEC	70p
		200/100/100/350v	£1.50
		500/500/25v	50p
		150/150/100/300v	75p
		200/150/150/300v	1.00
		<b>ITT Panels</b>	
		CVC 402 Chassis, new £30, complete with	
		infracap panel	
		GEC 820 Line O/P Panel	
		CVC20 Mains Panel	
		ITT 8 & 6 Push Button Unit	
		CVC402 New Chroma Panel	
		CMA 10	
		CMA 11	
		CMA 30	
		CMA 40	
		CMA 10/2	
		CMA 36	
		CMA 38	
		CMA 45	
		CMA 47	
		CMA 52	
		CMA 57	
		CMA 58	
		CMA 59	
		CMA 67	
		CMA 68	
		CMA 72	
		CMA 12	
		CMA 33	
		CMA 40	
		CMA 41	
		CMA 42	
		CMA 163	

# SENDZ COMPONENTS

63 Bishopsteignton,  
Shoeburyness, ESSEX SS3 8AF  
SAME DAY SERVICE

All items subject to availability.  
No Accounts - No Credit Cards  
Postal Order/Cheque with order  
Add 15% VAT, then £1 Postage  
Add Postage for overseas

Callers: To shop at 212 London Rd.,  
Southend. Tel. 0702-332992

Open 9-12.30-6. GVMT + school orders accepted on official  
headings add 10% handling charge.

<b>Tuner Units</b>	
V/Cap FAG or SCF29	£8
V/Cap Rank UHF Z776T/Unit	£6
V/Cap Rank UHF Z773T/Unit	£5
NEW G8 Tuner V/Cap	£5.50
ELC2000 on Panel	£2.50
GEC 6 Push Button Unit	£6
ITT 6 Push Button Unit	£6
DECCA 6 Push Button Unit	£6
GEC or Hitachi 6 push button unit 2110 Conversion	£8
GEC 2110 V/Cap	£5
ELC1043 (Ex Panel)	£3.75
ELC1042 NEW	£5.00
ELC2000	£4.00
ELC2004	£10.00
ELC2006 NEW	£10.00
GEC Tuner V/Cap Hitachi After 1979 ETS48, ETS47, ETS46, ETS41B	£8.00
ASTEC UM1183	£10.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
V317 (VHF)	£5
V334 (VHF)	£5
U321	£6
U341 UHF	£7.00
U342 UHF	£5
U4 UHF	£7.00
U.V. 411 Tuner	£10.00
U.V. 417	£10.00
ELC1043/05 Thorn	£5.90
ELC1043/06 Thorn	£5.00
Small V/Cap Mitsumi	£4.00
UHF	£4.00
VHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF/VHF Varicap (old type)	£8.00
Mosfit UHF/VHF (new type)	£8.00
UE2-B31 Fidelity V/Cap T/Unit	£6.00
UHF-VHF V/Caps on panel	£3.00
Thorn Tuner PANEL with 6x100K pots + cursors NO TUNERS	£1.00
HITACHI 20 Turn Pot	40p
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Videon MTS 900	£2.50
Mullard Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system. Data supplied.	£10.00
V100 Sound Tuner Kit. TV Visound. The latest design in low noise fitted with DNR. RF output and audio	£30.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Small Tuner DX 175-220MHz. Auto Changerover	£5.00
9000 Thorn Tuner on Panel	£7.00

D.P.D.T. switch Black knob:	4p
Chassis or PCB mount	each or 40 for £1.00
THORN 1400 4P.B. Mech. Tuner	50p
THORN 1500 4P.B. Mech. Tuner	50p
THORN 1590 4P.B. Mech. Tuner	50p
THORN 3500 4P.B. Mech. Tuner	50p
THORN 8000 4P.B. Mech. Tuner	50p
THORN 8500 Mech. Tuner	50p
All new & boxed.	£4.00 each
Delay Lines	
DL20A 80p	DL600 £1.00
G8 (Old Type)	£1
DL600	£1.00
DL710	£1.00
UDL11	30p
KT 3 Luminescence	75p
Luminance Delay Line (CVC 45)	
10x630ma fuse	25p
10x2A fuse	50p
10x3.15 fuse	50p
10x500mA	80p
10x1 amp	80p
20 3.15 AS Fuses	£1.70
Co-Ax Joint	15p
Co-Ax Beelling Lee Plug	12p
Co-Ax Splitter	£1.00
UHF Modulator CCIR	£3.00
Infra Red Emitting Diode	20p
NE286H Small Neon Lamps GEC	5p
Mullard 5 Watt Amps. LP1162	75p

BT18124	£1.00
BT18224	£1.00
CA270AE	50p
CA270CW	50p
CA270CE	50p
CA920AE	£1.00
CA1310	50p
CA3046	50p
CA3065Q	50p
CA3089Q	50p
CA3094AE	50p
CA3123	40p
CA3146	£1.00
CA3189	40p
CBF6848	50p
CD4510	30p
DM7492	50p
HA1196	40p
HA1370	£2.00
HA11273	40p
HEF4001	10p
HEF4011AF	10p
HEF4053B	30p
HD3890C	£3.00
K5731D 100102	£1.00
LA3260	£1.00
LM1011N	£1.00
LM8361	£3.00
M913	£2.00
MI024=AAA	£2.00
MI025=AAA	£2.00
MC1307	75p
MC1312	50p
MC1330	75p
MC1349	50p
MC1352	£1.00
MC1358	£1.00
MC14002	£1.00
MC14013	25p
MC14016	25p
MC14066	30p
MC14514	80p
MC1484	80p
MEM486	£1.00
ML231	£2.50
ET16016	£2.00
ML232	£2.00
ML236E	£1.00
ML237B	£1.00
ML238B	£4.00
ML239	£2.00
ML926	£1.00
MM5387	£1.00
MM5611	£1.00
MM5640	75p
MM5290N-4	75p
MM53108N	£4
MRI1366	20p
NE6100	£1.00
NE65P	60p
NE555	60p
HD3890C	£1.00
IL-1	20p
OPT600	20p
OPT601	20p
SA A611	20p
SA A661	£1.75
SA A1020	£4.00
SA A1021	£4.00
SA A1024	£4.00
SA A1025	£2.50
SA A1073	£3.00
SA A1075	£3.00
SA A1124	£2.00
SA A1130	£2.50
SA A1174	£3.00
SA A1176	£3.00
SA A1250	£3.00
SA A1251	£4.00
SA A1272	£3.00
SA A1276	£3.00
SA A3027P	£4.00
SA B300A	£1.50
SAB4209	£2.00
TBO0124	£1.00
SA A5000A	£1.50
SA A5012A	£5.00
SA A5030	£5.00
SA A5040A	£3.50
SA A5050	£3.50
SA F1032p	£2.00
SA F1039	£2.00
SA S560	£2.00

<b>T.V. Tubes</b>	
12" A31/300 Hitachi	£10
15" A38/170W Hitachi	£8
18" Hitachi PIL tube with scan coils 470 KCB22-TC03	£25
10" Black and white tube scan coils & line trans	£6.00

<b>Integrated Circuits</b>	
AC76003	£1.50
AM25LS23PC	10p
BAV40	40p

SAS560	£1.00
SAS570	£1.00
SAS580	£1.50
SAS590	£1.50
SAS3210	£2.00
SL437F	£4.00
SL901B	£4.50
SL918	£4.50
TA7122	£1.15
TAA320A	50p
TAA470	£1.50
TAA570	75p
TAA611B	50p
TAA621	£2.00
TAA661	£1.50
TAA641	£1.50
TA7108P	£1.00
TA7117	50p
TA7120P	50p
TA7315AP	50p
TA7607AP	40p
TA7609P	50p
TBA120A	40p
TBA120AS	40p
TBA120SA	40p
TBA120B	40p
TBA120SB	40p
TBA120T	50p
TBA121SQ	£1.00
TBA120U	75p
TBA120Q	30p
TBA120C	40p
TBA1441	£1.00
TBA231	75p
TBA395Q	50p
TBA396Q	£1.00
TBA396	75p
TBA440P	40p
TBA440C	£1.00
TBA480Q	£1.00
TBA520	£2.00
TBA530	£2.00
TBA540	£1.00
TBA550Q	£1.75
TBA560C	£1.00
TBA570	£1.50
TBA625	50p
TBA641	£2.00
TBA651	£2.00
TBA673	£1.50
TBA720A	£1.50
TBA750Q	£1.50
TBA780	£1.50
TBA800	50p
TBA810AP	60p
TBA8105	60p
TBA820	60p
TBA890	£1.00
TBA900	£1.50
TBA920	£1.50
TBA920Q	£1.50
TBA950	£1.50
TBA990Q	£1.00
TMS1000NL	£2.00
TMS1943 N2L (clockchip)	£1.00
TMS2716JL	£1.00
TMS2716L	£1.00
TMS3259	£1.00
TMS3720ANS	£3.00
TMS4014	70p
TX-012	£1.00
TMS9902	£1.20
ULN2216	75p
UPC566H	£1.00
UPC585C	£1.00
UPC1031H	£2.00
UPC1353C	£1.00
UPC1363C	£2.75
UPC1366C	£1.00
UPC2002	35p
UPD1849HC	£2.00
SN29848	50p
SN29770BN	£1.00
SN29771BN	£1.00
SN29772BN	£1.00
SN7402N	£1
SN7472N	£1
SN74107	£1.00
SN74167	70p
SN7472N	20p
SN7418AN	£1.00
SN76011	£1.00
SN76013	£1.50
SN76018	£1.00
SN76018	£1.00
SN76023N	£1.50
SN76033	£1.50
SN76110N	£1
SN76115AN	50p
SN76131	30p
SN76141N	£1.00
SN76226	£1.00
SN76227N	£1.00
SN76228N	£1.00
SN76270	£1.00
SN76532N	50p

SN76544N	£2.00
SN76546	£1.00
SN76550	30p
SN76552	30p
SN76570	£1.00
SN76620	50p
SN76620N	40p
SN76666	£1.00
SN76705N	75p
SN76707N	£1
SN76708AN	75p
SN76708AN	£1.00
SN76720	£1.00
UA783P3C	40p
BT100A/02	40p
BT8810A	70p
BT146	30p
TBA540C	£1.50
TCA270	£1.00
TCA270C	£1.00
TCA640	£1.00
TCA660	£1.00
TCA270S	£1.00
TCA270SC	£1.00
TCA740	£1.00
TCA800	£5.00
TCA830	£1.00
TCA940	£1.00
TCEP100	£2.25
TCE120CQ	£1.00
TDA440Q	£1.00
TDA1003A	£1.00
TDA1010	£1.00
TDA1060A	£1.50
TDA1035S	£3.50
TDA1035S	£2.00
TDA1072	£1.00
TDA1151	30p
TDA1170	£1.00
TDA1190	£1.00
TDA1200	75p
TDA1327A	£1.00
TDA1365	£3.00
TDA1412	£2.00
TDA2002	80p
TDA2003	80p
TDA2004	£2.00
TDA2010	£2.00
TDA2020	30p
TDA2030	£2.00
TDA2140	£3.50
TDA2160	£1.00
TDA2190	£4.00
TDA2525	£2.00
TDA2640	£2.00
TDA2522	£1.50
TDA2530	£1.50
TDA2532	£1.50
TDA2541	80p
TDA2541	£1.00
TDA2560	75p
TDA2571AQ	£2.50
TDA2575A	£1.00
TDA2575A	£1.00
TDA2591	£2.00
TDA2590	£2.50
TDA2591	£1.00
TDA2593	£1.00
TDA2560	50p
TDA2600	£5.00
TDA2611AQ	£1.00
TDA2653	£4.00
TDA2008	£1.00
TDA2640	£2.00
TDA2680	£2.00
TDA2690	£1.00
TDA2593	£1.00
TDA3190	£1.00
TDA3560	£4.00
TDA3571Q	£1.50
TDA3650	£4.00
TDA3651AQ	£3.00
TDA3710	£3.50
TDA9403	£1
UPC1365	£3.00
UPC1363C	£1.50
TDA3300B	£6.00
SN74LS 125AN	30p
SN74LS 248	50p
SIL4516	50p
SN16861NG	50p
SN16862AN	£1.00
SN16864AN	50p
SN29764AN	£1.00
UA721	40p
UA730	40p
RGP30G	40p
MPSA14	10p
MPSA43	10p
MJ13005	30p
MJE51T	25p
MJE340	25p
MJE660	25p

MJE661	25p
MJE3055	£1.00
MJE2801	30p
MJE2955	50p
MJE13005	50p
Sanikron Diode	30p

<b>Philips Cartridges</b>	
GP422 (4CH)	£6.00
GP412	£6.00