

PRACTICAL WIRELESS

JULY
1974


25p

THE POPULAR NEW ELECTRONIC GAME

TELE-TENNIS

PART
ONE

PLAYED ON THE TELEVISION SCREEN

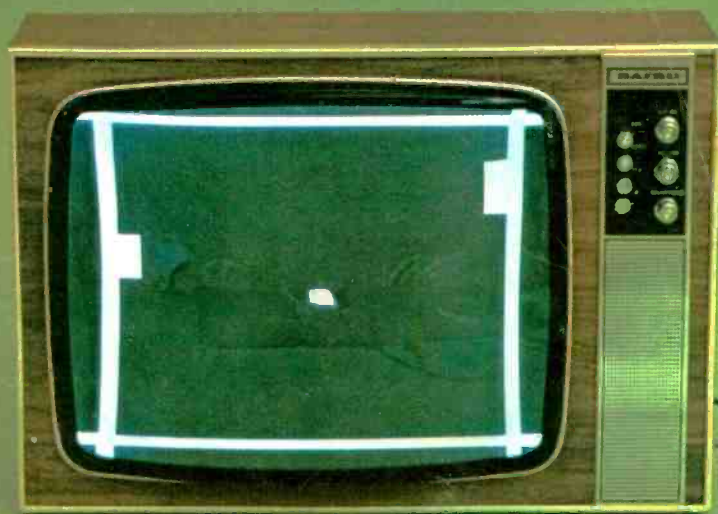

ALSO:-
THE 'SEVERN' 4-BAND PORTABLE
GENERAL PURPOSE PREAMPLIFIER

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder


- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNT.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

Total Building Costs
£7-23 P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 72p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

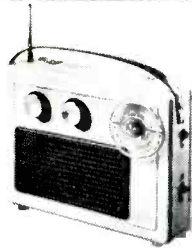

Nine Transistors, 9 Tuneable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors, 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 30p (Free with parts).

Total Building Costs **£6-95** P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 69p)

NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£2-73** P & Ins. 30p
(+ 10% VAT 27p)
(Overseas P & P £1-25)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£3-60** P & Ins. 30p
(+ 10% VAT 36p)
(Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 20p. Free with parts. Overseas P & P £1-05

Total Building Costs **£4-08** P & Ins. 31p
(Overseas P & P £1-85)
(+ 10% VAT 40p)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL




7 Tuneable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced gauged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shale with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

Total building costs **£6-98** P & Ins. 47p
(Overseas P & P £1-85) (+ 10% VAT 69p)

ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

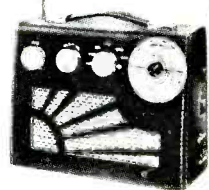

10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers. 9 Tuneable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Latest 4" 2 watt ferrite magnet loudspeaker.

Built in Ferrite Rod Aerial for MW/LW. Retractable-chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Gauged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

Total building costs **£8-50** P & Ins. 52p
(Overseas P & P £1-85) (+ 10% VAT 85p)

POCKET FIVE

3 Tuneable wavebands. M.W. LW. and Trawler Band. 7 stages, 5 transistors and 2 diodes. supersensitive ferrite rod aerial, moving coil loudspeaker, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List 15p (Free with parts).



Total Building Costs **£2-28** P & Ins. 26p
(Overseas P & P £1-25) (+ 10% VAT 22p)

TRANSONA FIVE


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts).

Total Building Costs **£2-50** P & Ins. 26p
(+ 10% VAT 25p) (Overseas P & P £1-25)

TRANS EIGHT 8 TRANSISTORS and 3 DIODES

8 Tuneable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for MW, LW. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

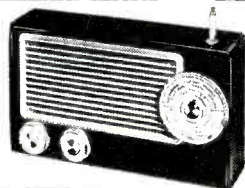Total building costs **£4-48** P & Ins. 33p
(+ 10% VAT 44p)
(Overseas P & P £1-25)



ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tuneable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages - 6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Plans and parts price list 25p (FREE with parts).

Total building costs **£3-98** (Overseas P & P £1-85)
(+ 10% VAT 39p)

"EDU-KIT"



Build Radios, Amplifiers, etc., from easy stage diagrams.

Components include:

Tuning Condenser, 2 Volume Controls, 2 Slider Switches, Fine Tone 3" Moving Coil Speaker, Terminal Strip, Ferrite Rod Aerial, Battery Clips, 4 Tag Boards, 10 Transistors, 4 Diodes, Resistors, Capacitors, Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

Total building costs **£5-50** P & Ins. 33p
(Overseas P & P £1-85) (+ 10% VAT 55p)

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelis" shop.
★ Open 10-1, 2.30-4.30, Mon. Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel.: 0234 52367. Reg. No. 788372.

I enclose £..... for
Name
Address
(Dept. PW24.)

PRACTICAL WIRELESS

VOL. 50 NO. 3

ISSUE 809

JULY 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR Morris A. Colwell
ASSISTANT EDITOR
Lionel E. Howes, G3AYA
ART EDITOR Peter Metall
TECHNICAL EDITOR
Eric Dowdeswell, G4AR
**PRODUCTION & NEWS
EDITOR** Colin R. Riches
PROJECTS SUB-EDITOR
Geoffrey C. Arnold
TECHNICAL ARTIST
Alan Martin
SECRETARIAL Jenny Maunder
01-634 4292 Susan Corne
ADVERTS. MANAGER
01-634 4293 Roy Smith
CLASSIFIED ADVERTS.
01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £3.50 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". Binders (£1.34) and indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 206 CURIOSITY!—Leader article and August preview
- 207 NEWS . . . NEWS . . . NEWS . . .
- 226 LETTERS
- 226 TELEVISION—Coming in the July issue
- 231 NEXT MONTH IN PRACTICAL WIRELESS
- 240 HOTLINES on recent developments by Novus
- 253 DOUBLE SCOOP TV Games in July TELEVISION
- 254 PRODUCTION LINES—Products reviewed by Colin Riches
- 257 ON THE AIR
- 257 Broadcast Bands, Short Waves—Malcolm Connah
- 258 Medium Waves—Charles Molloy
- 258 VHF/FM—Simon David
- 261 Amateur Bands, Short Wave/VHF—Eric Dowdeswell, G4AR

● CONSTRUCTIONAL

- 208 The "SEVERN" Portable—F. G. Rayer, G3OGR
- 229 EXPERIMENTAL WORKSHOP—Potential Divider Biasing and Grounded Base Amplifiers—M. J. Hughes, M.A.
- 232 TELE-TENNIS, Played on the TV Screen, Part I—M. J. Hughes, M.A.
- 241 MODIFYING THE "QUICKWIPE"—P. S. Collins
- 242 GENERAL PURPOSE PREAMPLIFIER—A. Foord
- 246 TAKE 20 No. 61 Personal TRF Receiver—David Andrews

● OTHER FEATURES

- 217 I.C. OF THE MONTH TBA651—M. J. Darby
- 221 UNDERSTANDING DISTORTION, Part 2—A. Foord
- 238 GOING BACK—Equipment of yesteryear—Colin Riches
- 247 OSCILLOSCOPE TECHNIQUES Part 5—Alan C. Ainslie
- 253 TECHNICROSS No. 5

RSC 100watt DISCO SYSTEM

50 WATT SPEAKER 50 WATT SPEAKER
TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER

AT FANTASTIC LOW PRICES!

Complete with lid HEADPHONES MICROPHONE

DISCOMASTER TWIN TURNTABLE POWER CONSOLE
Garrard SP25 or McDonald MF60 turntables, Sonotone or Acos cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £11.48 and 9 monthly payments £11.48 (Total £114.80) **£99.95**

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS
All types 15 Ohms covered in Rexine and Vynair
TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback howl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £2.96 and 8 m'thly payments £2.61 (Total £23.08) Carr. 65p.
TYPE C8/70 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £9.95 & 8 m'thly pymts. £4.31 (Total £44.48) Carr. 85p. **£39.95**

ALL RSC PRICES INCLUDE VAT INTEREST CHARGES REFUNDED on Credit Purchases settled in 3 months

FANE CRESCENDO SPEAKERS
Full range available at ALL BRANCHES

MINSTREL 8W GUITAR AMP.
Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: Deposit £3.95 and 8 monthly payments £2.39 (Total £23.07) Carr. free **£19.95**

FAL PHASE 50 Mk. III AMPLIFIER 50 WATT
Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speaker/s 3 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £9.93 & 8 monthly payments £4.81. Total £44.41. **£39.93**

RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.
For Lead Guitar, Mic., Gram. Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £6.39 and 8 monthly payments £6.39 (Total £57.51). Carr. £1.50 SAE for leaflet UK Mainland **ONLY £49.95** SPECIAL PRICE for limited period

REGENT 50X AMPLIFIER
A powerful high quality unit for lead, rhythm, guitar, vocalists, gram, radio, tape. Peak Output rating. Not for Bass Guitar.
★ Two extra heavy duty 12in. speakers.
★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "milkees". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £7.99 & 9 monthly payments of £7.99 (Total £79.90) Carr. £2.50 **£69.95**
REGENT 50B for Bass Guitar and general purposes. Or Dep. £9.19 & 9 m'thly pymts £9.19. (Total £81.90). Carr. £2.50 **£79.95**

GP30 AMPLIFIER For Guitar, Vocal or Instrumental Group
A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £3.58 and 8 monthly payments of £3.58 (Total £32.22). Carr. 75p **£27.95**

C4/100 HEAVY DUTY COLUMN SPEAKERS
Suitable for Public Address or Vocal and Instrumental Groups. Fitted four 12" 50 watt speakers. Robust attractive Vynide covered cabinet 58" x 16" x 10" approx. SPECIAL Carr. £1.50 PRICE £1.50 Or Dep. £20 and 12 m'thly pymts £3.90 (Total £66.90) **£59.95**

NOW SEVEN NEW BRANCHES BOLTON, COVENTRY DONCASTER, STOCKPORT SUNDERLAND, PRESTON and NOTTINGHAM

NEW LARGER PREMISES AT HULL, DARLINGTON, NEWCASTLE & DERBY

RSC Barclaycard and Access accepted
All items subject to availability. Prices correct at 24.5.74 E. & O.E.
HI-FI CENTRES LTD.

R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).
COVENTRY 17 Shelton Square, The Precinct.
DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41381
DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs)
EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
GLASGOW 326 Argyll St. (Closed Tues.). Tel. 248 4158
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
LEICESTER 32 High Street (Closed Thurs.). Tel. 50420
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252
LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
LONDON 238 Edware Road, W.2. (Closed Thurs.). Tel. 723 1629

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778
MIDDLESBROUGH 106 Newport Rd. (Closed Wed.).
NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469
NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068
PRESTON 41 Friargate Walk, St. Georges Shoppo Prec.
SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg. (Closed Thurs.). Tel. 20716
STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777
SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

Units listed below
(a) DISCOMASTER TWIN T. TABLE CONSOLE with integral 100W amp.
(b) PAIR OF HI-FI HEAD- PHONES
(c) MATCHING DYNAMIC "MIKE" (attached to h'phone)
(d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets. Size approx. 18" x 18" x 8"
(a) (b) (c) & (d) Carr. £3.00 **£149.95**

RSC TDI DISCO CONSOLE
Incorporating twin Garrard SP25 or BBR MF60 type turntables and Sonotone or Acos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls, Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid, see illustration on left. Or Dep. £7.99 and 9 m'thly pymts £7.99 (Total £79.90) Carr. £1.50 **£69.95**

Terms Deposit £19.95 & 19 m'thly. payments of £7.87 (Total £169.48).

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100Watt 14,000 gauss 8/15Ω £29.70 Dep. £8.80 and 5 m'thly payments £3.80 (Total £24.20)	12" 60Watt 14,000 gauss 8/15Ω £16.95 Dep. £3.17 and 8 m'thly payments. £2.17 (Total £19.53)	12" 50 Watt 13,000 gauss 15Ω £12.99 Dep. £1.95 and 8 monthly payments £1.71 (Total £15.63)

FOR BASS GUITAR, ELECT. ORGAN, ETC.

NEW 'POP' 55 12" 60W
Gauss 15,000 Imp 8/15Ω Or Dep £2.45 & 8 monthly payments £2 (Total £18.45) Carr. Free **£15.95**

FANE SPEAKERS 'POP' 25/2 12 in. 30 WATT
Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£8.99** CREDIT TERMS (PAIRS ONLY) Dep. £2.80 & 8 m'thly pymts £2.30 (Total £21.20).

GROUP EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK. III AMPLIFIER PR. FANE POP 55/30W L/SPEAKERS Terms: Deposit £6.77 and 8 monthly payments of £6.77 (Total £60.93)	£89.93 £17.98 £67.91	PACKAGE PRICE £52.95 carr. £1.10
F.A.L. PHASE 50 MK. III AMPLIFIER PR. FANE POP 50 L/SPEAKERS Terms: Deposit £20 and 12 monthly payments of £3.90 (Total £66.90)	£89.93 £25.98 £65.91	PACKAGE PRICE £59.99 carr. £1.10
F.A.L. PHASE 50 AMPLIFIER PAIR L12/20 SPEAKERS in Cabinets Terms: Deposit £20.00 and 12 monthly payments £3.90 (Total £66.90)	£89.93 £25.90 £65.83	PACKAGE PRICE £59.99 carr. £2.00

HIGH QUALITY LOUDSPEAKER UNITS
ALL TWO TONE REXINE AND VYNAIR FINISH
L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1.50
Or deposit £7.99 and 8 monthly pymts. of £4.72. Total £45.71
L12/20 12" 25 WATT 13,000 lines 15 ohm. Terms for Pairs. Dep. £3.32 & 8 m'thly pymts £3.32 (Total £29.88) Carr. 55p. **£12.95**
L12/10 10-15 Watt Veneered cabinet 12" unit 8-15 ohm. Approx. 14" x 14" x 9" Carr. 65p. Terms for Pairs. Dep. £2.05 & 8 m'thly pymts £2.05 (Total £18.45). **£7.95**

HUGE DISCOUNTS

ON LEADING BRAND HI-FI

All R.S.C. Prices include VAT

*Full labour and material guarantees for 12 months
LOW DEPOSIT TERMS OVER 8 MONTHS

Wharfedale 150 ISODYNAMIC HI/PHONES £24.05 **£17.95**
 WHARFEDALE DENTON £43.09 Pr. **£29.95**
 WHARFEDALE LINTON £53.35 Pr. **£35.95**
 LEAK 150 SPEAKERS £51.30 Pr. **£31.95**
 LEAK 250 SPEAKERS £60.86 Pr. **£42.50**
 LINEAR 202 AMPLIFIER £39.93 **£24.75**
 Wharfedale Denton Tuner/Amp £95 **£54.95**
 ALSO SHURE CARTRIDGES, BASF TAPE ETC.
 Prices shown correct at 24th May 1974



HI-FI 10 + 10W STEREO SYSTEM

AUDIOTRINE STEREO 20 AMPLIFIER SPECIAL PURCHASE **£55**
 GARRARD TURNTABLE with Sonotone Cartridge wired on Plinth with cover. Worth Double
 PAIR DIPLOMAT 10W SPEAKERS, Teak Veneer finish, Carr. £2

RSC G66 MkII 6.6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db.

Treble Control ± 13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 — 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS **£12.75** 40p
 OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.50 or dep. £2.12 and 8 monthly payments £2.12 (Total £19.08).

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db.

Treble Control ± 13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 — 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS **£12.75** 40p
 OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.50 or dep. £2.12 and 8 monthly payments £2.12 (Total £19.08).

AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.

Exceptional performance at low cost.
 HF80T 8" 10W £5.55 HF120D 12" 15W £8.50
 HF10SD 10" 10W £5.30 HF12S 12" 15W £7.95
 HF120 12" 15W £5.95 HF12SD 12" 15W £8.50

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω.

PLEASE STATE IMPEDANCE REQUIRED List £4.50
 MODEL 807T 8" 10w with ceramic Tweeter. **£3.99**
 Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15Ω. **£5.50** List £6.50

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET

Only high grade components by leading manufacturers

- Push Button Selector Switching
 - Jack Socket for Headphones
 - Neon Indicator
 - Satin Silver Finish Metal Fascia
 - Solid State Circuitry
 - Twenty Silicon Transistors
 - Four Diodes, Four Rectifiers
- Send S.A.E. for full descriptive leaflet.

R.S.C. STEREO FM III TUNER. IN CABINET. **£37.95**

Visually matches Super 30 Mk. III

AKAI TAPE UNITS

All £1 carr.
 GXC 36D £64.95 Rec. £112.75
 GXC 38D £99.95 Price £139.90
 GXC 36 £89.95 £125.50
 GXC 40T £135.95 £189.50

GXC 46D £114.95 Rec. £160.50
 GXR 82D £89.95 £124.90
 4000 DS £94.95 £132.50
 1721 L £86.95 £120.75
 CR 81D £69.95 £84.10

GOLDRING GL72 T/Table & P.U. £29.95 (Rec. Price £37.29) Carr. 75p with Free Goldring G800 Cartridge worth over £10 fitted to above unit.

GOLDRING GL75 T/Table & P.U. £34.95 (Rec. Price £57.19) Carr. 85p with Free Goldring G800 Cartridge worth over £10 fitted to above unit.

PIONEER PL12D T/Table on plinth & cover £39.95 List £55.97

MacDonald MP60T/Table and P.U. £9.95 List £14.94

T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER
 GARRARD SP25 with G850 or G800 Special Price **£19.95** (Carr. £1)
 MacDonald MP60 with G800 or G850 ... **£18.95** (Carr. £1)
 GOLDRING GL75 with G800 Special price **£39.95** (Carr. £1)

A HI-FI-30 + 30W STEREO SYSTEM

AUDIO FIDELITY MODEL 60 AMPLIFIER. PAIR AUDIO FIDELITY MARQUESS 30 SPKRS. **£99.95**
 GARRARD SP25 Mk IV or McDONALD MP60 with G800 Cartridge. Ready wired on Plinth with Cover. Total Value approx. £165 Carr. £3
 Cabinets finished in Teak Veneer. Send S.A.E. for leaflet.

HI-FI SPEAKER ENCLOSURES

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 45p per enc.
 JE8 Size 16" x 11" x 9". Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. **£5.95**
 SE8 For optimum performance with any 8in. Hi-Fi speaker. Size 19 x 10 1/2 x 9in. **£6.95**
 SE10 For outstanding results with 10in. Hi-Fi spkr. Size 25 1/2 x 16 x 9in. Ported. **£6.95**
 SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter. Size 25 1/2 x 16 x 9in. **£7.95**

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£7.45** Carr. 45p
 OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£7.95** Carr. 50p

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Response 30-20,000 c.p.s. -2dB. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. O/P rating I.H.F.M. Enclosed enamelled case 9 1/2 x 2 1/2 x 5 1/2in. Silver finish fascia 10 1/2 x 3 1/2in. **£7.95** Carr. 40p. FACTORY BUILT Complete kit, wiring diagrams and instructions. **£10.95**

R.S.C. TA12 MKIII 6.5+6.5 WATT STEREO AMPLIFIER

Fully Transistorised, Hi-Fi/Op of 6.5 watts per channel. Optimum performance with any crystal or ceramic P.U. Cartridge, Radio Tuner, Tape Rec. etc. Input Sel. Switch, Bass, Treble, Vol. & Bal. Controls. COMPLETE KIT OF PARTS WITH FULL **£12.99** Carr. 40p. Send S.A.E. for leaflet. WIRING DIAGRAMS & INSTRUCTIONS **£16.95** Carr. 40p. Factory built with Teak Veneer. Dep. £2.50 & 8 mthly pymts 12 mths guarantee **£19.95** Veneer housing **£22.50** (Total £22.50).

AUDIO FIDELITY FR1 SPEAKER KIT

Response 30Hz-15KHz. Rating 15 watts in sealed cabinet Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material. Screws, Terminal Panels. **£11** each. SPECIAL **£14.99** Pair Carr. Free. OFFER Carr. 60p

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms
 Performance comparable with COMPLETE KIT units costing considerably more **£25.95** Carr. Consists of (1) 12in. 15w Bass **75p** unit with cast chassis. Roll rubber cone surround for ultra low resonance. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) Dome Pressure Tweeter. (5) Quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms. Deposit £4.71 and 8 monthly payments **£3.12** (Total £29.67)

FANE HIGH FIDELITY LOUDSPEAKERS AT LESS THAN HALF-PRICE

UNREPEATABLE OFFER BRAND NEW BOXED FULLY GUARANTEED for High-Fidelity NOT Group Disco use Available by Mail Order only due to small quantities of some models. SAE for leaflets. Please state impedance required.

Model No.	Price (incl. VAT)	Model No.	Price (incl. VAT)	Model No.	Price (incl. VAT)	Model No.	Price (incl. VAT)	Model No.	Price (incl. VAT)	Model No.	Price (incl. VAT)	Model No.	Price (incl. VAT)
505	£2.75	1002	£4.19	121/15	£4.61	138/15	£4.51	122/10TLR	£6.38	122/14LR	£9.19	152/10	£9.26
506	£2.61	1005	£3.85	121/15LR	£5.88	138/15LR	£4.93	122/12	£8.76	122/14ALR	£9.52	152/12	£10.84
507	£1.08	1008	£3.19	138/10TLR	£2.18	138/10TLR	£4.96	122/12A	£7.08	122/17A	£10.58	152/12A	£11.38
508	£.96	1008	£2.93	138/10T	£3.31	101/10A	£4.27	122/12D	£6.88	122/17A	£10.59	152/14	£12.49
801	£3.95	1001LR	£5.09	138/10TLR	£2.50	101/14	£6.64	122/12T	£7.08	122/17T	£10.59	152/14	£12.49
802	£3.69	1006LR	£4.37	138/10TLR	£2.63	101/14A	£6.74	122/14	£6.47	122/17LR	£10.98	152/17	£14.96
802T	£3.82	121/10	£3.37	138/11	£3.55	122/10	£5.16	122/14A	£8.90	122/17LR	£11.81	153	£17.48
802T	£2.25	121/10T	£3.37	138/11LR	£3.87	122/10A	£5.49						
806	£2.56	121/11	£3.58	138/13	£3.95	122/10LR	£6.03						
1001	£4.37	121/11T	£3.78	138/13LR	£4.15	122/10T	£5.49						

All Transformers available as previously advertised



THE WEST HYDE PRESTIGE CASE
The smartest of the West Hyde cases all anodised aluminium, with top and bottom panels only, in black PVC covered steel (plain or louvered). Free standing or 19in. rack mounting with aluminium brackets. Supplied ex stock, fully assembled, with SS Pozidrive screws.

Prices include panels, feet P & P and VAT. State whether 1 or Full Panels required.

BC21 (3 1/4" whole rack)	£13-46	88p	74p
BC22 (3 1/4" half rack)	£10-90	88p	74p
BC31 (5 1/2" whole rack)	£15-53	£1-24	74p
BC32 (5 1/2" half rack)	£12-79	£1-24	74p

Prices correct May 1974

A smart miniature case in tough, rigid, high-gloss black A.B.S. Front panels in either aluminium or white PVC/Steel. Built-in slots for PC cards, dividers, or screens. Chassis or PC boards can be supported on "P" clips from internal pillars. Excellent as encapsulation boxes. Prices include P. & P. and VAT. Less for quantities. Also available less panel and screws. Minimum order £1.



M2 65mm x 100mm x 50mm	1 off	10 off
2 1/4" x 3 1/4" x 2"	51p	45p
M3 100mm x 130mm x 50mm	67p	58p
3 1/4" x 5" x 2"		

Prices correct May 1974



- (1) No. 285 Anodised aluminium centre bar. Black plastic brackets with moulded-in core. 75mm. 87p. 5 more sizes up to 154mm.
 - (2) No. 281.1. Nylon 112mm. Load 50kg. 45p.
 - (3) No. 277. All. ground, polished, anodised. 88mm. 94p. 120mm. £1-06.
 - (4) No. 268. Satin all. 57-5mm. 84p. 102mm. £1-01. 145-5 £1-17.
 - (5/6) No. 250. Black nylon. Very comfortable. 75mm. 29p. 110mm. 41p. 155mm. 67p.
- Prices correct May 1974

P. & P. 22p any quantity. Write or phone for new catalogue



AMTRON METAL CABINETS GIVE EXTRA VENTILATION
Ideal for Stabilised Power Supply Units. A lightweight case with perforated sides and top. The front panel is of heavy gauge anodised all. The top, bottom, sides and back interlock, secured by 4 screws. The front frame is a clever moulding holding the panels allowing for 4 hidden fixings for a chassis if required (not supplied). Integrally moulded front feet also form the mounting for the tilt support which is standard with this matt blue painted case.

Height	Length	Depth	Code	1 off
120mm	284mm	138mm	00 3009-00	£8-46
120mm	224mm	138mm	00 3009-10	£5-61
120mm	284mm	188mm	00 3009-20	£7-07

Less for quantity
Prices include feet, tilt, VAT and P. & P.
Prices correct May 1974



W.	H.	D.	1 off	W.	H.	D.	1 off
A 4-5"	3"	6-5"	£3-60	M 4-5"	3"	13"	£4-44
B 4-5"	7"	6-5"	£4-44	N 4-5"	7"	13"	£5-44
C 4-5"	10"	6-5"	£4-91	O 4-5"	10"	13"	£6-91
D 8"	3"	6-5"	£4-91	P 9"	3"	13"	£3-44
E 9"	6"	6-5"	£5-44	Q 9"	7"	13"	£6-91
F 9"	10"	6-5"	£6-28	R 9"	10"	13"	£8-41
G 13"	3"	6-5"	£5-44	S 13"	3"	13"	£6-91
H 13"	7"	6-5"	£6-28	T 13"	7"	13"	£8-41
I 13"	10"	6-5"	£6-91	U 13"	10"	13"	£10-20
J 18"	3"	6-5"	£6-28	V 18"	3"	13"	£8-41
K 18"	7"	6-5"	£8-41	W 18"	7"	13"	£10-20
L 18"	10"	6-5"	£10-20	X 18"	10"	13"	£12-21

Woodgrain: D £5-44, E & G £6-28, H £6-91. Prices include screws, rubber feet, one or two chassis according to size and P. & P. and VAT.

WEST HYDE (WH)
WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRES., NORTHWOOD HILLS, MIDD. HA6 1NN. Tel: Northwood 24941 or 28732 Telex: 923231

NEW ALL SILICON!



PRACTICAL WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, supplied with deluxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit £7-97 U.K. Post Free
De-Luxe Kit £9-62 U.K. Post Free

Quantity Discounts:

Trade and Overseas	1-5	Nett	6-9	Less 10%
Enquiries Invited	10-49	Less 15%	50-99	Less 20%
Mail Order Only	100-999	Less 25%	1000 up	Less 30%

ALL PRICES INCLUDE VAT

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET, WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365

PLUGS & LEADS

Plugs

Pack 107 5 pin Din	25p
Pack 108 3 pin Din	20p
Pack 135 1/2" Jack	30p
Pack 130 1/2" Jack Stereo	50p
Pack 103 Loudspeaker Plug	20p
Pack 100 Phono Plug	10p
Pack 230 3 pin Socket	25p
Pack 236 5 pin Socket	35p
Pack 234 Loudspeaker Socket	35p

Ready-made Leads

3 pin to 3 pin Din	70p
3 pin to open end	55p
5 pin to 5 pin Din	£1-00
5 pin to open end	70p
5 pin to 4 phono plugs	£1-00

All leads approx. 5ft. in length

Speaker lead Din to spade 12ft. 50p
Extension lead Din plug to socket 12ft. 80p

DIAMOND STYLI
8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8.All at 80p each.
Double Diamond £1.25
Diamond suitable for Orbit NM22; G800; M3D £2.25 each

CARTRIDGES

Goldring G800	£6-00
Orbit NM22	£4-00
Shure 75/6	£6-00
Sonotone 9TAHC (Dia)	£2-00
Sonotone 8TA4 (Dia)	£1-50
Ronnette 105 (Dia)	£1-25

Prices include VAT and post
Prices correct at time of going to press but subject to change without notice

RECORD CARE

Cecil Watts Dust Bug	£1-20
Parastatic Disc Preener	45p
Antistatic Fluid	20p
Dust Bug Spares (Brush & Roller)	15p

CASSETTE TAPES
Audio-Magnetic C60
Qty 3 6 10 20
Price(£1-00)£1-90(£3-20)£6-30
Cassette Caddy £1-20
Cassette Head Cleaner 35p

ZONAL ILFORD TAPE

5" Standard 600ft	25p
5 1/2" Standard 900ft	50p
7" (Plain boxed) 1200ft	60p
7" (Westminster Boxed) 1800ft	£1-25
7" Reel of Leader Tape (Blue or green)	75p

HEADPHONES

Sennheisser HD414	£12-50
AKG K50	£6-50
Beyer DT48S	£35-00

MICROPHONES

AKG D109	£12-65
AKG D202E1	£43-45
AKG D190C	£18-70
AKG D190E	£20-02
AKG D224	£55-00
Sennheisser MD211N	£49-50
Sennheisser MD413N	£29-70
Sony ECM50	£93-50
Audio RMS7F Radio Mike	£231-00

SPEAKERS

E.M.I. 350 Kit Bohms	£8-20
E.M.I. 450 Kit Bohms	£4-50

J. J. Francis (Wood Green) Ltd
MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS
Telephone: Matching 476

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	5p	BCY72	14p	D10 (NTGD10)	OC83	25p	2N1307	39p	7447	
AC107	50p	BD124	75p		OC84	25p	2N1308	34p	7450	
AC126	20p	BD131	40p	HP5082	29p	OC139	25p	2N1309	34p	7451
AC127	25p	BD182	40p	HS822-33	40p	OC170	25p	2N1559(CR1)	7453	
AC128	24p	BD131/132	80p	HT841-33	£2-24	OC171	30p	401C	71p	7454
AC128/AC176		BDY20	81p	HT881-33	£2-90	OCPT1M	42p	2N1613	15p	7460
	44p	BF115	23p	HT341-33	£1-02	ORP12	50p	2N1711	15p	7470
AC151	20p	BF163	35p	IR2160	85p	ORP60	50p	2N1693	54p	7472
AC152	25p	BF167	25p	IRC20	44p	ORP61	50p	2N2218	33p	7473
AC153	20p	BF173	20p	IRT84	£2-24	ORP69	50p	2N2218A	44p	7474
AC176	20p	BF177	25p	JAA424	£2-08	PM7A2	£1-85	2N2219	39p	7475
AC153/176K	52p	BF178	31p	MC13003L	£1-75	PM7A6	£2-50	2N2219A	53p	7476
AC187K	17p	BF180	30p	MC13009P	£2-80	PN70	16p	2N2308	17p	7480
AC188K	23p	BF184	25p	MC1307P	£1-02	PN71	16p	2N2309	17p	7482
AC187/188K	40p	BF186	18p	MC1310P	£2-90	PN107	8p	2N2399A	17p	7483
AC178	27p	BF190	18p	MC1330P	90p	PN108	8p	2N2484	42p	7486
ACY18	20p	BF200	30p	MC1382P	£2-90	PN109	8p	2N2646	45p	7490
ACY19	20p	BF234	14p	MC1486L	£4-20	PN319 (2N3819)	2N2904	44p	7491A	
ACY20	20p	BF255	18p	MC1488L	£2-88		2N2904A	49p	7492	
ACY21	19p	BF X13	25p	MC4022P	£2-25	SL103A	50p	2N2905	85p	7493
ACY22	18p	BF X38	25p	MC4044P	£2-15	SL403A	50p	2N2905A	75p	7494
AD140	60p	BFX84	25p	MFC4000B	85p	(Rectifier)	80p	2N2924	18p	7495
AD149	60p	BFX85	34p	MFC6030	£1-65	SL803A	80p	2N2925	20p	7496
AD161	44p	BFX86	25p	MFC6040	£1-18	ST2	20p	2N2926	10p	74100
AD162	44p	BFX87	30p	MFC6010	£1-34	TAA263	£1-12	2N3053	24p	74107
AD161/162	90p	BFX88	24p	MFC6040	£1-24	TAA293	£1-17	2N3054	65p	74121
AF106	25p	BFY56	21p	MJ480	67p	TIL112	£2-86	2N3704	65p	74141
AF114	27p	BFY51	10p	MJ5371	86p	TAA320	75p	2N3226	£1-10	74150
AF115	27p	BFY52	20p	MJ520	85p	TAA861	45p	2N3391A	20p	74151
AF116	25p	BFY53	17p	MJ521	82p	TAD100	£1-97	2N3525	£1-04	74153
AF117	25p	BFY90	£1-20	MJ5295	£1-09	TAD110	£1-97	2N3702	14p	74154
AF118	44p	BPX29	£1-46	MJ5305	80p	TBA103	£1-08	2N3703	12p	74155
AF124	25p	BFY58	£1-50	MJ480	67p	TIL112	£2-86	2N3704	12p	74156
AF125	24p	BR100	20p	MJ481	£1-25	TIL209	30p	2N3705	12p	74190
AF126	24p	BRY35	45p	M491	£1-35	TIP31A	60p	2N3706	12p	74191
AF139	47p	BSX18	18p	MJ802	£4-12	TIP32A	70p	2N3707	12p	74192
AF166	40p	BSX20	10p	MJ802/MJ4502	TIP41A	85p	2N3708	12p	74193	
AF239	82p	BSX21	20p		£2-50	TIP42A	£1-90	2N3709	12p	74196
AF270	84p	BSY27	20p	MJ800	£1-90	TIS43	30p	2N3710	12p	74197
AS Y26	20p	BSY28	25p	MJ1000	£1-50	TR1	20p	2N3711	12p	40250
AS Y27	30p	BSY55A	12p	MJ4902	£4-44	VA1039	15p	2N3773	£2-50	40309
AS Y28	22p	BT106	£1-20	MLM300K	£1-90	VA1040	15p	2N3819	28p	40310
AS Y29	30p	BTY76/400R	MPF102	37p	VA1066A	15p	2N3820	60p	40311	
BA138	15p		£1-80	MPF103 (2N5457)	VA1077	15p	2N3823E	28p	40312	
BB103	20p	BY100	20p		10p	W005	25p	2N3826	36p	40320
BB104	24p	BY127	22p	MPF104 (2N5458)	W001	20p	2N3866	£1-16	40380	
BB105	20p	BZY58C3V3	40p		40p	W02	25p	2N3904	26p	40381
BC107	18p	io		MPF106 (2N5459)	W04	27p	2N3906	28p	40382	
BC107/BC177	30p	BZY98C30V	10p		40p	W06	32p	2N4058	13p	40406
BC108	18p	BZX81C7V5	NE555V	78p	W08	41p	2N4060	13p	40407	
BC108/BC176	20p		10p	NKT10033	60p	ZTX107	12p	2N4081	13p	40408
BC109	16p	BZY93C30V	20p	NKT121	25p	ZTX108	11p	2N4082	13p	40409
BC109/BC175	16p	BZY93C18V	70p	NKT212	25p	ZTX300	13p	2N4441	70p	40410
BC110C	30p	BZY93C18V	70p	NKT213	25p	ZTX302	16p	2N4444	£2-20	40430
BC111	18p	CA3004	£2-92	NKT218	25p	ZTX303	15p	2N4871	44p	40488A
BC117	18p	CA3008	£1-50	NKT223	25p	ZTX314	23p	2N4990	60p	40511
BC140	20p	CA3011	60p	NKT271	18p	ZTX330	11p	2N4991	40p	40878
BC147	12p	CA3012	£1-17	NKT274	18p	ZTX500	14p	2N4992	45p	40879
BC148	11p	CA3014	£1-37	NKT278	20p	ZTX501	15p	2N5458 (MPF103)	40p	40800
BC149	12p	CA3018A	70p	NKT279A	12p	ZTX502	18p	2N5459 (MPF105)	40p	40803
BC157	13p	CA3018A	80p	NKT281	20p	ZTX503	17p	2N5459 (MPF105)	40p	40898
BC158	12p	CA3024E	60p	NKT381	75p	ZTX504	44p	2N5756	£1-20	40739
BC159	13p	CA3028A	70p	NKT401	70p	1N914	4p	2N5777	45p	
BC147/157	25p	CA3035	£1-37	NKT402	83p	1N3754	4p	2N6027 (D13T1)	4p	45p
BC148/158	23p	CA3043	£1-37	NKT403	71p	1N4001	4p		3p	84
BC149/159	25p	CA3044	£1-38	NKT404	60p	1N4002	4p		3p	128
BC167	11p	CA3046	70p	NKT406	87p	1N4003	7p	3N128	73p	
BC168	18p	CA3048	60p	NKT408	87p	1N4004	7p	3N140	82p	
BC169	11p	CA3052	£1-32	NMC449	£1-90	1N4005	8p	3N152	82p	
BC169C	12p	CA3053	£1-32	NMC449	£1-90	1N4006	8p	741/T05	45p	
BC177	20p	CA3062	£1-28	NMC305	£3-90	1N4007	8p	741/BDIL	34p	
BC178	16p	CA3065	£1-28	NTGD10	60p	1N4148	4p	741/T05	45p	
BC179	20p	CA3068	£1-28	OA191(NTGD10)	1N4490	11p	741/T05	£1-95		
BC182	14p	CA3069	£1-28	OA47	40p	1N4500	25p	747/ADIL	£1-08	
BC188L	14p	CA3122	£1-99	OA7	8p	1N4501	25p	747/ADIL	40p	
BC183	13p	CD4006AE	50p	OA79	8p	1844	4p	748/ADIL	30p	
BC183L	14p	CD4001AE	50p	OA80	8p	13920	7p	3015F	£1-48	
BC184	17p	CD4007AE	50p	OA81	8p	13940	8p	3015G	£2-00	
BC184L	18p	CD4008AE	£1-18	OA85	8p	2400	23p	7400	24p	
BC212	16p	CD4001AE	50p	OA800	8p	2N698	15p	7401	24p	
BC212L	16p	CD4018AE	50p	OA802	7p	2N697	17p	7042	24p	
BC238	16p	CD4013AE	£1-11	OC25	40p	2N698	30p	7403	24p	
BC238/308	30p	CD4013AE	£2-02	OC28	70p	2N706	10p	7404	30p	
BC281	11p	CD4017AE	£2-08	OC29	70p	2N706A	12p	7405	30p	
BC282	15p	CD4018AE	£2-08	OC36	60p	2N708	18p	7408	30p	
BC283	12p	CD4020AE	£1-08	OC39	60p	2N911	30p	7409	24p	
BC287	12p	CD4024AE	£2-09	OC41	40p	2N914	30p	7410	24p	
BC308	16p	CD4027AE	£1-73	OC42	40p	2N918	42p	7413	30p	
BCY30	25p	CD4028AE	£4-12	OC44	20p	2N929	25p	7429	24p	
BCY31	48p	CD4048AE	90p	OC45	20p	2N930	28p	7435	30p	
BCY32	90p	CR1/081C	34p	OC71	20p	2N131	24p	7439	24p	
BCY33	12p	CR1/081C	71p	OC72	80p	2N182	34p	7449	20p	
BCY34	25p	CRS2/08AF	OC78	25p	2N192	17p	7442	£1-30		
BCY38	30p		£1-06	OC78	25p	2N1303	17p	7443	£1-74	
BCY58	18p	CRS3/40AF	OC77	40p	2N1304	24p	7444	£1-74		
BCY70	12p		£1-53	OC81	20p	2N1305	24p	7445	£2-47	
BCY71	30p	CZ0	17p	OC81D	20p	2N1306	30p	7449	£1-74	

TEST METER

This compact, robust Meter contains a transistorized amplifier enabling a very high input impedance to be achieved (at least 200K ohms per volt).

DC & AC Ranges £27.50 each
Further details on request - ask for leaflet 08-351.

LOGIC CHECKER

The fast effective way for checking Digital DIL IC's. Checks DIL gate, flip-flops, counters shift registers, decoders, etc., etc.
Clip on logic plates clarify circuit state.
No interference with circuit. Input impedance responds to one TTL load.
Instant display by LED's.
Power supply automatically selected.
Full instructions supplied with each device at £25.95 each.

INTEGRATED CIRCUIT TEST CLIP

Indispensable aid to the engineer working with DIL IC's. For use with both 14 & 16 lead packages. Clips on to device under test. Can be used as a removal tool. Accidental shorting of IC leads eliminated & Capacitance effects at HF are negligible. £1.95 each

INTEGRATED CIRCUIT PINS

The lowest priced IC mounting available. Pin Sockets come in a reel, just drill your board at required centres, drop in pins and solder, break off frame holders-your DIL mounting is complete!
Pin Sockets 1,000 pieces £7.00
Pin Sockets 100 pieces £1.00

TRANSDUCERS - ULTRASONIC

A new type of 40 kHz Ultrasonic Transducers designed to transmit and receive a 40 kHz signal. Supplied with transmitter/receiver circuit sheets.

SOLD ONLY IN PAIRS NEW LOW PRICE £4.95 per pair
Type No. 83181

CA3123E Superhet System with RF Amp. IF Amp. Mixer, OSC. I.C. g.c. Detector and Voltage Regulator. Ideal for car radio applications. £1.90

APPLICATION SHEET & DATA 15p

SEVEN WATT AUDIO AMP. I.C.

TBA8105 £1.00
Featuring thermal protection. Ideal for car radio applications.

APPLICATION SHEET & DATA 15p

PACKAGED CIRCUITS

The complete range of Newmarket modules currently being featured in magazine articles. See catalogue for details.

ANTEX SOLDERING EQUIPMENT

X25/240v 25w Iron. £1-05 X32/240v 15w kit £3-20
MLX 18v 25w kit, essential for car tool kit £3-95
X50TC 240v 50w temperature controlled £2-95

ARROW SPECIALISE IN EDUCATIONAL AND GOVERNMENT ORDERS

—See catalogue for further details.

ARROW SERVICE PLUS

10% DISCOUNT OVER £4. NO POSTAGE AND PACKING. TOP QUALITY PRODUCTS ALWAYS BY RETURN **COMPREHENSIVE CAT.**

Important Notice "All prices are exclusive of V.A.T. Please add 10% V.A.T. to the final total of your order after deducting any discount which may be due" VAT. REG. 246008672

ARROW ELECTRONICS LTD.
DEPT. PW 11, 7 COPTFOLD ROAD
BRENTWOOD
ESSEX CM14 4BN

I enclose PO/Cheque for 10p
Name _____
Address _____
Arrow Electronics Limited
Dept. PW 11
Coptfold Road
Brentwood
Essex
CM14 4BN
REGISTRATION No. 1062424

CHROMASONIC electronics

Dept 1
56, Fortis Green Road, London, N10 3HN
telephone: 01 883 3705

MINITRON



Filament indicator, 16 Pin D11, 10mm
Character Height
0-9 Digit Ref 3015F
1 Overflow/Polarity Ref 3015G


NEW PRICE £1.29

74 SERIES TTL

1st GRADE BRANDED PRODUCTS

7403 2P	7402 8P	7490 82P
7401 2P	7405 E1 7P	7491 E1 10
7402 2P	7404 E1 8P	7492 82P
7403 2P	7404 A1 8P	7493 82P
7404 2P	7408 E1 10	74100 E2 37
7405 2P	7410 33P	74121 45P
7410 2P	7473 41P	74122 86P
7411 2P	7474 41P	74141 E1 10
7413 2P	7475 63P	74154 E1 82
7400 2P	7476 44P	74192 E2 15
7430 1P	7486 49P	74193 E2 53
7441 81P	7489 E4 75	74196 E1 73

PHOTO-DARLINGTON

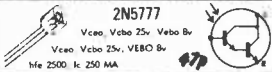

OPTOELECTRONICS



Red
Green
Yellow

Seven Segment
MAN 71 MAN 73
MAN 51 MAN 53
MAN 81 MAN 83


DL 707
0.3" high character
14 pin DIL

DL 747
0.6" high character
L.H. Dec P

All Common Anode Left Hand Decimal Point
Character Height 0.3"

OUR PRICE £2.65 each £2.19 £2.89

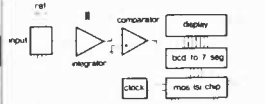3 1/2 DECADE DIGITAL VOLTMETER INTEGRATED CIRCUIT



This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet.

OUR PRICE ONLY £7.79

(booklet alone 10p)

SIEMENS



LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing.
Ref AN412R 13mm character height. Can be directly driven by National Semiconductors Alom Clock chip MM5316

OUR PRICE £16.50

LIGHT EMITTING DIODES

- 0.125" dia TIL209 Type
Red 24p each, Yellow 9p each
Green 41p each, White 33p each
- 0.125" dia
Red (LED2) 26p ea
Green (LED4) 69p ea
0.175" dia green (LED5) 75p ea
- 0.2" dia MLED 650/750/850 Type
Red 70p each
Green 85p each
Yellow 70p each

T092 style MLED 500 still only 17p (RED)

NEW **LOW COST**

RED (Led 7)
GREEN (Led 18)
YELLOW (Led 21)

all at £9.99 for 5

VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH
VAT INVOICES ON REQUEST
R&P On U.K. Orders min 10p. Overseas Orders at Cost

WE WILL QUOTE
FOR QUANTITIES
ON REQUEST

16 CHERRY LANE BRISTOL BS1 3NG THE RADIO SHOP TELEPHONE 0272-421196

TRIACS

1 6AMP PLASTIC TOS	6 5AMP ISOLATED TAB	10AMP ISOLATED TAB
NAS0161W 100V -27	NAS0651W 100V -46	NAS1001W 100V -63
NAS0161X 100V -28	NAS0651X 100V -44	NAS1001X 100V -60
NAS0162W 200V -30	NAS0652W 200V -58	NAS1002W 200V -78
NAS0162X 200V -28	NAS0652X 200V -56	NAS1002X 200V -74
NAS0164W 400V -40	NAS0654W 400V -84	NAS1004W 400V 1-09
NAS0164X 400V -38	NAS0654X 400V -80	NAS1004X 400V 1-04
NAS0166W 600V -55	NAS0656W 600V 1-05	NAS1006W 600V 1-34
NAS0166X 600V -52	NAS0656X 600V 1-00	NAS1006X 600V 1-28
3AMP "CLIPPED TAB"	8-5AMP ISOLATED TAB	16AMP ISOLATED METAL
NAS0301W 100V -30	NAS0851W 100V -52	NAS1601W 100V -84
NAS0301X 100V -28	NAS0851X 100V -50	NAS1601X 100V -80
NAS0302W 200V -36	NAS0852W 200V -67	NAS1602W 200V -90
NAS0302X 200V -34	NAS0852X 200V -64	NAS1602X 200V -86
NAS0304W 400V -52	NAS0854W 400V -97	NAS1604W 400V 1-32
NAS0304X 400V -50	NAS0854X 400V -92	NAS1604X 400V 1-28
NAS0306W 600V -70	NAS0856W 600V 1-20	NAS1606W 600V 1-88
NAS0306X 600V -68	NAS0856X 600V 1-14	NAS1606X 600V 1-80

Devices with Internal Trigger have "W" suffix. "X" denotes Standard Triac

THYRISTORS

1-6AMP MINI TOS	4AMP ISOLATED TAB	6AMP ISOLATED TAB
NAS006R 50PIV -20	NAS106S5 50V -26	NAS206S5 50V -29
NAS006S 100PIV -23	NAS106T5 100V -30	NAS206T5 100V -33
NAS006T 200PIV -25	NAS106U5 200V -38	NAS206U5 200V -42
NAS006V 400PIV -35	NAS106V5 400V -60	NAS206V5 400V -68
NAS006X 600PIV -45		
8AMP ISOLATED TAB	16AMP ISOLATED TAB	
NAS306S5 50V -32	NAS306S5 50V -45	
NAS306T5 100V -38	NAS306T5 100V -53	
NAS306U5 200V -47	NAS306U5 200V -66	
NAS306V5 400V -75	NAS306V5 400V -85	

CLOCK CHIP CT7001
The unique CT7001 represents a major breakthrough in Clock Chip design, incorporating many features available for the first time:
365 DAY CALENDAR - 12/24 HR. OPERATION - ALARM - SNOOZE ALARM - SIX DIGIT CAPABILITY - DIRECT DRIVE TO LED DISPLAY - CONTINUOUS OPERATION DURING MAINS FAILURES.
Copy of data available - please send 10p stamp.
Special kit comprising 1 CT7001 & 4 LED 7 segment displays and data sheets and socket **£8-95**
Price add 10% VAT to all listed prices. Postage and packing 15p per order. Send 10p stamp for latest catalogue. Callers welcome.

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDEGE, YORKS WF15, 6PQ TEL. HECKMONDWIKE 405285

SPECIAL OFFER
Used 19" TV Tubes. Type AW 47-91. Perfect condition. 6 months guarantee. £3 carr. paid.

Complete untested TV Sets 19" 405-line Types £3-50 carr. and ins. paid.

19" 625-line types untested. Complete with UHF Tuner £5-50 carr. and ins. paid.

One Students and One Instructors Wireless Procedure Training Set, each unit housed in a small wood box and comprises Mike, Single L.R. Phone and connectors. Requiring Bell Battery (not supplied) to make intercom. £1-30 post paid.

Small Clock Type Sangamo Weston 200-250v 200 r.p.m. mains motor with Gear train (ex slot machine) Fair condition 60p post paid.

1/2 cwt. of ex Government Scrap Resistors, Panels, Gears, etc 30p carr. 80p.

Speakers removed from TV sets. All 3 ohm, 2 1/2 watts 7 x 4, 6 x 4, 8 x 2 1/2. All at 27p. Post and packing 12p.

Top Quality Tape, Reel to Reel 5" LP 55p, 5 1/2" LP 60p, 7" ST 66p, 7" LP 80p. Cassette Types C60 35p, C90 45p. Post on any tape 12p.

Jap Earpiece, 8 ohm, magnetic, 3-5 12p post paid.

Ex Equipment Valves all Tested before despatched. 3 months guarantee on all valves. Single valves post 3p, over post paid.

ARPI2 6p	EF184 20p	PY801 17p
DY86 20p	PCF80 6p	PY82 10p
EB91 5p	PCC84 6p	PY33 20p
EF80 10p	PCL82 15p	UI91 20p
EBF89 15p	PCL84 15p	6BV7 12p
ECC81 12p	PCL85 20p	6F23 15p
ECC82 12p	PL36 17p	30F5 12p
EY86 20p	PY81 10p	30FL1 20p
EF183 20p	PY800 17p	30P19 10p

ABOVE PRICES INCLUDE V.A.T.

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

5p for 1 Valve.
Each additional Valve add 2p.

DM70	0-83	EF80	0-46	PC86	0-75	PL84	0-66	30C15/	
DY51	0-85	EF83	1-08	PC88	0-75	PL504	0-88	PCF800	1-05
DY86/7	0-42	EF85	0-43	PC90	0-58	PL509	1-55	30C17/	
DY802	0-45	EF86	0-90	PC84	0-52	PL802	0-28	PCF805	0-90
KABC80	1-00	EF89	0-81	PC89	0-65	PT33	0-68	30F5/FF818	
EB01	0-88	EF91	1-30	PC189	0-65	YF81/800	0-50		1-10
EB081	0-75	EF92	1-40	PCF80	0-51	YF82	0-55	30FL1/	
EBF80	0-60	EF95	1-95	PCF82	1-30	UABC80	0-66	PCE800	0-75
EBF83	0-42	EF183	0-40	PCF86	0-65	YF500A	1-05	30FL2	0-75
EBF89	0-58	EF184	0-60	PCF200	0-95	YF801	0-50	30FL12	1-05
EC86	0-75	EH90	0-56	PCF201	0-87	U26	1-00	30FL14	0-85
EC88	0-77	EL34	0-95	PCF801	0-85	U191	1-00	30L1/PC84	
EC881	0-45	EL36	1-05	PCF802	0-71	U193	0-50		
EC882	0-43	EL81	0-80	PCF806	0-66	UABC80	0-80	30L15/PC805	
EC883	0-45	EL84	0-47	PCH200	0-98	UBC51	0-70		1-05
EC884	0-42	EL85	0-55	PCL82	0-64	UBF99	0-80	30L17	0-90
EC885	0-48	EL88	0-95	PCL83	0-63	UC85	0-60	30P4MR	1-30
EC888	0-75	EL95	0-70	PCL84	0-69	UCH81	1-00	30P12/PC801	
ECCL189	0-71	EL91	1-31	PCL85	0-63	UCL82	0-70		1-05
ECF80	0-56	ELL80	1-30	PCL86	0-68	UCL83	0-70	30P19/PC802	
ECF82	0-78	EM84	1-18	PCL805/85		UF89	0-80		1-00
ECF85	0-71	EM87	1-18			U14	0-85	30P1/PC801	
EC8H1	1-00	EY81	0-88	PD500	1-55	UY85	0-50		0-95
EC8H3	1-00	EY86/87	0-42	PLF200	0-90	6/30L12/		30FL19/	
EC8H4	0-78	EY88	0-64	PL36	0-58	EC804	1-00	PCF150/	
ECL80	0-58	EZ80	0-61	PL81	0-78	6P23/EF812		30FL80	1-20
ECL82	0-61	EZ81	0-40	PL81A	0-88			30FL14/	
ECL83	0-42	EZ81	0-40	PL82	0-50			PCL88	1-25
ECL86	0-63	GZ84	0-78	PL83	0-96	30C1/PCF80	0-51	30PL15	1-05

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0-60	EF80	0-95	PC86	0-60
AZ31	0-55	EF85	0-82	PC88	0-60
CLB131	1-20	EF86	0-30	1C97	0-50
CL33	1-50	EF89	0-28	PC900	0-60
CY31	0-50	EF91	0-37	PC84	0-40
DAF91	0-30	EF92	0-50	PC88	0-55
DAF95	0-50	EF95	0-40	PC89	0-50
DC90	0-35	EF98	0-50	PC189	0-60
DF91	0-30	EF183	0-50	PCF80	0-50
DF96	0-50	EF184	0-35	PCF82	0-35
DK91	0-45	EL32	0-60	PCF86	0-60
DK92	0-70	EL33	1-75	PCF801	0-50
DK96	0-60	EL34	0-50	PCF802	0-60
DL92	0-40	EL36	0-50	PCF805	0-99
DL94	0-48	EL37	2-50	PCF806	0-75
DL96	0-55	EL41	0-90	PCF808	0-90
DY86/7	0-38	EL42	0-90	PCL82	0-55
DY802	0-37	EL84	0-28	PCL83	0-38
EABC80	0-38	EL95	0-40	PCL84	0-45
EAF42	0-75	ELL80	1-00	PCL85	0-50
EB91	0-22	EM80	0-45	PCL86	0-45
EB33	1-00	EM81	0-60	PCL805/85	
EB41	0-75	EM84	0-35		0-50
EB81	0-83	EM85	1-00	PD500	1-30
EBF80	0-40	EY81	0-40	PEN45	0-75
EBF83	0-40	EY86	0-40	PL36	0-55
EBF89	0-38	EZ40	0-75	PL81	0-50
EBL31	1-50	EZ41	0-75	PL82	0-45
EC881	0-40	EZ80	0-28	PL83	0-45
EC882	0-38	EZ81	0-29	PL84	0-40
EC883	0-38	YF801	0-90	PL500	0-75
EC884	0-35	GZ30	0-45	PL504	0-75
EC885	0-40	GZ32	0-50	PL508	1-00
EC888	0-40	GZ34	0-65	PL509	1-55
ECH35	1-26	GZ37	1-25	PL802	0-85
ECH42	1-00	HN309	1-50	YX4	3-50
EC8H1	0-80	KT61	1-75	PX25	3-50
EC8H3	0-45	KT66	2-50	PY31	0-50
ECL80	0-55	KT81 (7C5)		PY81	0-50
ECL82	0-85			PY82	0-35
ECL83	0-70	KT81	1-75	PY83	0-38
ECL86	0-40	KT88	2-90	PY88	0-40
ECLL800	3-20	KTW61		PY300	1-05
EF3A	1-20	MU14	1-00	PY81/800	0-50
EF39	1-20	N78	2-75	PY801	0-50

8P41	3-00	8J6	0-80
8P61	0-75	8J7M	0-45
8T1	1-00	8J7G	0-40
U14	1-00	8K6GT	0-75
U25	0-85	8K7M	0-45
U26	0-85	8K7G	0-30
U191	0-75	8K8M	0-70
UABC80	0-40	8K8G	0-45
UAF42	0-75	8K2E	0-75
UBC41	0-75	8L6G	0-55
UBC81	0-45	8Q7M	0-50
UBF80	0-40	8Q7G	0-50
UBF89	0-40	8SL7GT	0-48
UC85	0-45	8SN7GT	0-48
UCH42	0-75	8GQ42	0-55
UCH81	0-40	8U6G	0-55
UCL82	0-25	6V6G	0-40
UCL83	0-70	6V6GT	0-45
UF41	0-75	6X4	0-40
UF89	0-40	6X5G	0-40
UL41	0-85	6X5GT	0-45
UL84	0-43	7B6	0-75
UY41	0-48	7B7	0-70
UY85	0-40	7C5	1-30
VR105-30	0-40	7C6	0-75
VR150-30	0-40	7H7	0-70
OA2	0-40	7B7	0-75
OB2	0-40	7B7	2-25
OR5	0-45	7Y4	0-75
OR5	0-80	12A7E	0-40
IT4	0-80	12A7T	0-40
384	0-40	12A7U	0-45
3V4	0-70	12A7V	0-48
3V4	0-80	12A7X	0-48
3V4	0-80	12A7Y	0-48
3V4	0-80	12A7Z	0-48
3V4	0-80	12BAA	0-45
3V4	0-80	12BEB	0-50
3V4	0-80	30C1	0-80
3V4	0-80	30C15	1-05
3V4	0-80	30C17	1-10
3V4	0-80	30C18	0-90
3V4	0-80	30F5	1-10
3V4	0-80	30FL1	0-80
3V4	0-80	30FL2	0-75
3V4	0-80	30FL14	0-90
3V4	0-80	30L15	1-05
3V4	0-80	30L17	0-95
3V4	0-80	30P4MR	1-30
3V4	0-80	30P12	1-05
3V4	0-80	30P19	1-00
3V4	0-80	30PL1	0-95
3V4	0-80	30PL13	1-20
3V4	0-80	30PL14	1-25
3V4	0-80	35W4	0-50
3V4	0-80	35Z4GT	0-70
3V4	0-80	60C16	1-40
3V4	0-80	60C19	1-00
3V4	0-80	60C23	1-05
3V4	0-80	60C25	1-05
3V4	0-80	60C26	1-05
3V4	0-80	60C27	1-05
3V4	0-80	60C100	1-05

TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

EXPRESS POSTAGE

3p for first Transistor.
for each additional add 1p.

AA119	0-7	BD132	0-50	OC16	1-00	ZTX501	0-15	2N2904	0-20
AA213	0-10	BF115	0-25	OC20	2-00	ZTX503	0-18	2N2904A	0-25
AA215	0-10	BF167	0-22	OC23	1-25	ZTX531	0-25	2N2905	0-25
AC107	0-35	BF173	0-28	OC25	0-40	ZTX550	0-18	2N2905A	0-25
AC126	0-25	BF179	0-33	OC28	0-70	1N914	0-08	2N2906	0-20
AC127	0-25	BF180	0-35	OC35	0-55	1N4001	0-8	2N2926	0-10
AC128	0-20	BF181	0-35	OC36	0-68	1N4002	0-8	2N3053	0-20
AC176	0-25	BF194	0-13	OC42	0-40	1N4003	0-8	2N3055	0-10

-The lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G399A AF1102
T10	8 2G417 2N137

All 55p each pak

ND 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for BXZ 21, G 407, 2N 1893 120voh.

1	25	100
0	19	0 17 0 16

8H. trans. suitable for P.E. Organ. Metal TO-18 Ekvst. ZFN 300 6p each. Any Qty

GP 100 TO3 METAL CASE GERMANIUM

Veho=80V. Vceo=50V. I.C.=10 amps. Ptot=30W. hfe=30-170.

Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100
0	48	0 44 0 40

GP 300 TO3 METAL CASE SILICON

Veho=100V. Vceo=60V. I.C.=15 amps. Ptot=115W. hfe=20-100FT. 1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

1	25	100
0	55	0 53 0 51

NEW 8th EDITION

250 pages

TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. £1.85 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

UT 48 UNIJUNCTION TRANSISTORS

Direct replacement for TIN 43rand BEN 3000 also electrically equivalent to 2N2946

1	25	100
0	30	0 28 0 22

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY-27/29/95A.

All usable devices to open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP

20	For	0 55
50	For	1 10
100	For	1 82
500	For	8 25
1000	For	14 30

SIL. G.P. DIODES 5p

300mA	30	0 55
40V(Min.)	100	1 85
Sub-Min.	500	5 50
Fully Tested 1,000	9 80	

Ideal for Organ Builders.

R 2400 TO3 NPN SILICON HIGH VOLTAGE

Veho 250V.	Vceo 100V.	I.C. 6 amps.	Ptot 30W.	hfe typ. 20
1	25	100		
0	55	0 50	0 44	

ADI161/162

M/P COMP GERM TRANS. OTR LOWEST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS in PRACTICAL ELECTRONICS RADIO CONSTRUCTOR

SILICON PHOTO TRANSISTOR TO-18 Leads and NPN Sim. to BFX25 and P21 BRAND NEW.

Full data available. Fully guaranteed.

Qty. 1-24 25-99 100 up
Price ea. 69p 44p 35p

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 x 7400	0 55	UIC46	6 x 7446	0 55	UIC90	5 x 7490	0 55
UIC01	12 x 7401	0 55	UIC48	6 x 7448	0 55	UIC91	5 x 7491	0 55
UIC02	12 x 7402	0 55	UIC50	12 x 7450	0 55	UIC92	5 x 7492	0 55
UIC03	12 x 7403	0 55	UIC51	12 x 7451	0 55	UIC93	5 x 7493	0 55
UIC04	12 x 7404	0 55	UIC53	12 x 7453	0 55	UIC94	5 x 7494	0 55
UIC05	12 x 7405	0 55	UIC54	12 x 7454	0 55	UIC95	5 x 7495	0 55
UIC06	8 x 7406	0 55	UIC60	12 x 7460	0 55	UIC96	5 x 7496	0 55
UIC07	8 x 7407	0 55	UIC70	8 x 7470	0 55	UIC100	5 x 74100	0 55
UIC10	12 x 7410	0 55	UIC72	8 x 7472	0 55	UIC121	5 x 74121	0 55
UIC20	12 x 7420	0 55	UIC73	8 x 7473	0 55	UIC141	5 x 74141	0 55
UIC30	12 x 7430	0 55	UIC74	8 x 7474	0 55	UIC151	5 x 74151	0 55
UIC40	12 x 7440	0 55	UIC76	8 x 7476	0 55	UIC154	5 x 74154	0 55
UIC41	5 x 7441	0 55	UIC80	5 x 7480	0 55	UIC193	6 x 74193	0 55
UIC42	5 x 7442	0 55	UIC81	5 x 7481	0 55	UIC199	6 x 74199	0 55
UIC43	5 x 7443	0 55	UIC82	5 x 7482	0 55			
UIC44	8 x 7444	0 55	UIC83	5 x 7483	0 55			
UIC45	5 x 7445	0 55	UIC86	5 x 7486	0 55			

Packs cannot be split, but 26 assorted pieces (our mix) is available as PAK UIC X1

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 5p
Q1	20 Red spot transistors PNP	0 55
Q2	16 White spot R.F. transistors PNP	0 55
Q3	4 OC 77 type transistors	0 55
Q4	6 Matched transistors OC44/45/81/81D	0 55
Q5	4 OC 75 transistors	0 55
Q6	5 OC 72 transistors	0 55
Q7	4 AC 128 transistors PNP high gain	0 55
Q8	4 AC 126 transistors PNP	0 55
Q9	7 OC 81 type transistors	0 55
Q10	7 OC 71 type transistors	0 55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0 55
Q12	3 AF 116 type transistors	0 55
Q13	3 AF 117 type transistors	0 55
Q14	3 OC 171 H.F. type transistors	0 55
Q15	7 2N2926 8H. Epoxy transistors mixed colours	0 55
Q16	2 GET880 low noise Germanium	0 55
Q17	5 NPN 2 x MT 141 & 3 x MT 140	0 55
Q18	4 MADD*82 x MAT 100 & 2 x MAT 120	0 55
Q19	3 MADD*82 x MAT 101 & 1 x MAT 121	0 55
Q20	4 OC 44 Germanium transistors A.F.	0 55
Q21	4 AC 127 NPN Germanium transistors	0 55
Q22	20 NKT transistors A.F. R.F. coded	0 55
Q23	10 OA 202 Silicon diodes sub-min.	0 55
Q24	8 OA 81 diodes	0 55
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0 55
Q26	8 OA85 Germanium diodes sub-min	0 55
Q27	2 10A PIV Silicon rectifiers 18A25R	0 55
Q28	2 Silicon power rectifiers BYZ 13	0 55
Q29	4 Silicon transistors 2 x 2N698, 1 x 2N697, 1 x 2N698	0 55
Q30	7 Silicon switch transistors 2N706 NPN	0 55
Q31	6 Silicon switch transistors 2N708 NPN	0 55
Q32	3 PNP Silicon transistors 2 x 2N1181, 1 x 2N1182	0 55
Q33	3 Silicon NPN transistors 2N1711	0 55
Q34	7 Silicon NPN transistors 2N2309, 500MHz (code 1397)	0 55
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0 55
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0 55
Q37	3 2N3053 NPN Silicon transistors	0 55
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0 55

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales: Constant of Frequency and Wavelength, Calculation of L, C and fo of Tuned Circuits, Reactance and Self Inductance, Area of Circles, Volume of Cylinders, Resistance of Conductors, Weight of Conductors, Decibel Calculations, Angle Functions, Natural Logs and " Functions, Multiplication and Division, Squaring, Cubing and Square Roots, Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 22 cm x 4cm. Complete with case and instructions. Price each: £3 69

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE	PRICE
2-3V.	400mV (DO-7 Case) 12p ea. 14W (Top Hat) 15p ea. 10W (SO-10 Stud) 22p ea.

NEW LOW PRICED TESTED S.C.R.'s

Pak No.	Contents	Price
P1V 3A	5A 5A 7A 10A 16A 30A	0 55
T05	T06 T08 T08 T048 T048 T048 T048	0 55
500	0 26 0 28 0 39 0 39 0 52 0 55 0 59 1 27	
100	0 29 0 37 0 52 0 52 0 65 0 64 0 70 1 54	
200	0 39 0 41 0 54 0 54 0 63 0 67 0 83 1 76	
400	0 48 0 62 0 62 0 62 0 74 0 83 1 03 1 93	
600	0 59 0 63 0 75 0 75 0 85 1 07 1 38	
800	0 70 0 77 0 88 0 88 0 99 1 32 1 65 4 40	

F.E.T.'S

POST OFFICE TELEPHONE DIALS 80p each.	2N3819 31p	2N3458 35p
	2N3820 55p	2N5459 44p
	2N3821 30p	BFW10 66p
	2N3823 31p	MFF105 41p

CADMIUM CELLS

ORP12 48p

One 55p Pak of your own choice free with orders valued £4 or over

2N3055

115 WATT SIL POWER NPN 55p EACH

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price 5p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0 55
U 2	60 Mixed Germanium Transistors AF/RF	0 55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0 55
U 4	40 Germanium Transistors like OC81, AC128	0 55
U 5	60 200mA Sub-Min. Silicon Diodes	0 55
U 6	30 8H. Planar Trans. NPN like B8795A, 2N706	0 55
U 7	16 8H. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 0 55	
U 8	50 8H. Planar Diodes DO-7 Glass 250mA like OA200/202	0 55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0 55
U10	20 BA750 charge storage Diodes DO-7 Glass	0 55
U11	25 PNP 8H. Planar Trans. TO-5 like 2N1152, 2N2904	0 55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0 55
U13	30 PNP-NPN 8H. Transistors OC200 & 2N 104	0 55
U14	160 Mixed Silicon and Germanium Diodes	0 55
U15	25 NPN 8H. Planar Trans. TO-5 like BFT61, 2N697	0 55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0 55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0 55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0 55
U19	25 Silicon NPN Transistors like BC108	0 55
U20	12 1 5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0 55
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0 55
U23	30 MADD*82 like MHz Series PNP Transistors	0 55
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0 55
U25	25 300 MHz NPN Silicon Transistors 2N708, B8Y27	0 55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0 55
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0 55
U29	10 1 Amp SCR's TO-5 can. up to 600 PIV CR81/25-600	1 10
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0 55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise AMP 2N3707	0 55
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0 55
U33	18 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0 55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0 55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0 55
U36	25 Silicon Planar NPN Transistors TO-5 BF500/51/52	0 55
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0 55
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0 55
U39	30 R.F. Germ. PNP Transistors 2N1303/5 TO-5	0 55
U40	10 Dual Transistors 6 lead TO-5 2N2060	0 55
U41	25 R.F. Germanium Transistors TO-1, OC46, NKT2	0 55
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0 55
U43	25 8H. Trans. Plastic TO-18 A.F. BC113/114	0 55
U44	20 8H. Trans. Plastic TO-5 BC116/116	0 55
U45	7 3A SCR. TO66 up to 600PIV	1 10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SIL. RECTS. TESTED

Pak No.	Contents	Price
P1V 300mA	750mA 1A 1.5A 3A 10A 30A	0 55
50	0 04 0 06 0 06 0 08 0 16 0 23 0 66	
100	0 04 0 07 0 06 0 15 0 18 0 26 0 83	
200	0 06 0 10 0 07 0 16 0 22 0 27 1 10	
400	0 07 0 15 0 08 0 22 0 30 0 41 1 38	
600	0 08 0 18 0 11 0 25 0 38 0 50 2 05	
800	0 11 0 19 0 12 0 28 0 41 0 61 2 29	
1000	0 12 0 28 0 14 0 33 0 51 0 70 2 75	
1200	0 37 0 42 0 63 0 83	

DIACS TRIACS

FOR USE WITH TRIACS.	VBOM 2A 6A 10A TO-5 TO-6 TO-4s
BR100 (D32) 41p each	2p 2p 2p
	100 83 55 83
	200 55 66 99
	400 77 83 1 21

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV 99p each

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 11p. Overseas add extra for airmail.


Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

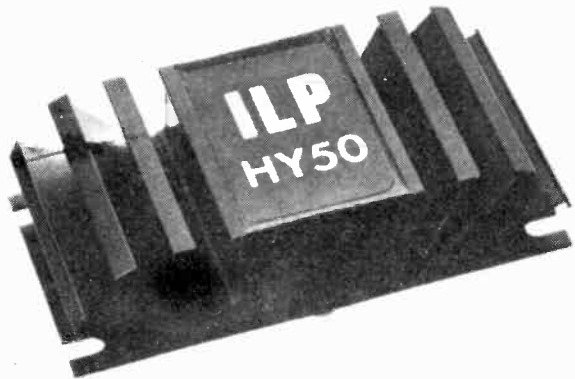

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy, sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of 'King-size' cigarettes.

Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

OUTPUT POWER: 25 watts RMS, 50 watts peak music power
LOAD IMPEDANCE: 4-16Ω into 8Ω
INPUT SENSITIVITY: 0db (0.775 volts RMS)
INPUT IMPEDANCE: 47KΩ
TOTAL HARMONIC DISTORTION: Less than 0.1% at 25 watts typically 0.05 better than 75db
SIGNAL/NOISE RATIO: 10Hz-50KHz ± 1db
FREQUENCY RESPONSE: ± 25 volts
SUPPLY VOLTAGE: 105 x 50 x 25 mm
SIZE:


SPEC.

25 watts RMS, 50 watts peak music power
4-16Ω into 8Ω
0db (0.775 volts RMS)
47KΩ
Less than 0.1% at 25 watts typically 0.05 better than 75db
10Hz-50KHz ± 1db
± 25 volts
105 x 50 x 25 mm

Price £5.80 mono, £11.60 stereo

Price inclusive of VAT & P & P

NEW HY5 PRE-AMPLIFIER

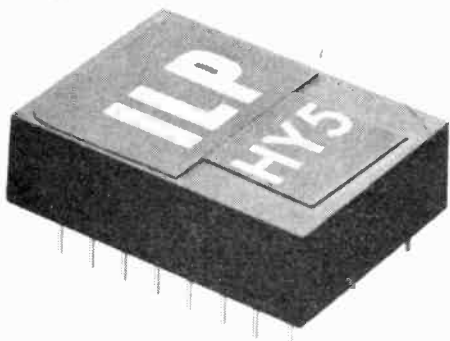

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components & has been redesigned to run off a split power-line with improvements in signal/noise, overload, capability & reduced distortion. The output has been increased to match the power module (0db), and to share the same power supply. Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 & power supply only potentiometers are required to complete a simple mono amplifier with input & output facilities expected to be found on Hi-Fi amplifiers. The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

INPUTS
Magnetic Pick-up 3mV (within 1db RIAA curve)
Ceramic Pick-up up to 3mV
Microphone 10mV
Tuner 250mV
Auxiliary 3-100mV
Input impedance 47kΩ 1kHz

SPEC.

OUTPUTS
Tape 100mV
Main output, 0db (0.775volts)

ACTIVE TONE CONTROLS
Treble ± 12db at 10kHz
Bass ± 12db at 100Hz

OVERLOAD CAPABILITY (equalization stage) 40db on most sensitive input


OUTPUT NOISE LEVEL (below 10mV magnetic input) 68db

DISTORTION 0.05% at 1kHz
SUPPLY VOLTAGE ± 15-25 volts

SUPPLY CURRENT 15mA

Price £4.85 mono, £9.70 stereo
Price inclusive of VAT & P & P

POWER SUPPLY PSU50

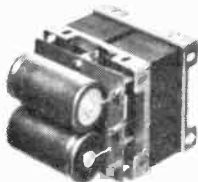

The new PSU50 has a low profile look being only 2½ inches high and can be used for either mono or stereo systems.

SPEC.
OUTPUT VOLTAGE ± 25 volts
INPUT VOLTAGE 210-240 volts
SIZE L. 70, D. 90, H. 60 mm

Price £5.23
Price inclusive of VAT & P & P

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.



**for fast, easy
reliable soldering**

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

**EASY-TO-USE
DISPENSERS**



Size 5
Savbit alloy
18 swg, 24p
(illustrated).
Size 19A
60/40 alloy
18 swg, 25p
Size 15
60/40 alloy
22 swg, 28p

**IDEAL FOR HOME
CONSTRUCTORS**


Size 1 cartons in 40/60, 60/40
and Savbit alloys
in 7 gauges 36p



Size 12 Reel
for Service
Engineers and
Electricians.
18 swg
Savbit alloy. £1.16



BIB WIRE STRIPPER AND CUTTER

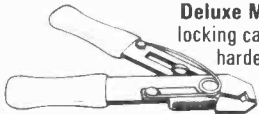

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive, 88-108Mcs, with circuit diagram. £2.30p.

P-C BOARDS (not computer panels)

- 1 off 6 transistors single wave band
- 1 off 4 transistor audio
- 1 off 3 transistor £1.60 the three.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 30p each, 4 for £1.00.

ELECTROLYTIC CAPACITORS 32/32/32µf. 325v. 2" x 1 1/4", 35p, 3000µf. 50v. 4" x 1 1/4", 40p, 2000µf. 30v. 2" x 1 1/4", 25p, 2000µf. 30v. 2 1/2" x 1", 25p, 2000µf. 35v. 3" x 1", 30p, 470µf. 100v. 3" x 1 1/4", 25p, 2000/2000µf. 25v. 2" x 1 1/4", 35p, 30,000µf. 25v. 4 1/4" x 2 1/4", 50p, 200µf. 350v./300/100/32µf. 300v. 3" x 2", 50p, 700µf. 200v. 3 1/4" x 1 1/4", 30p, 16/16µf. 275v. 1 1/2" x 1 1/2", 20p, 40/40/20µf. 275v. 3" x 1", 20p, 4500/900/900µf. 30v. 2 1/4" x 1 1/4", 50p, 4000µf. 35v. 3" x 1 1/4", 40p, 200/100/50/100µf. 325v. 3" x 1 1/4", 50p.

Colour Translator panels, as used on well known British E.V.R. Teleplayer. All new panels and components. Type and contents of transistors listed below. Each panel £3.50 each.

- X605. .14 off BC148. RCA ca3014(ic). 1 crystal 4.433618MHz.
- Z607. .12 off BC148. 1 BC158. 1 BC108. 1 RCA ca3046. 1 RCA ca3045(ic).
- Z608. .23 off BC148. 2 BC158.
- Z612. .12 off ME4102. 2 BC251B. 1 BFY50.

CRYSTAL CALIBRATOR (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz-10MHz (harmonics up to 30MHz) power required 300V DC 15mA. 12V 0.3A DC. Test equipment for 62T M/RC. £2.50 each.

WIRE-WOUND RESISTORS. Our selection of mixed Ohms and Watts. 25 for £1.50, 50 for £2.50, parcel of 1,000 £30.00.

AUDIO AMPLIFIER MODULE. Due to bulk purchase we can now offer the Audio Amplifier Module (Mullard LP1173) output power, nominal 10 watt. Supply voltage — 24 volt, with reference data for £2.50.

ALL ITEMS INCLUDE VAT
All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

Guest Speaker


The Castle 8.RS.DD.



A highly sensitive, full range eight inch unit designed for use in the recommended cabinet, or one of similar dimension.

Suitable for use with good quality stereo installations, tape recorders, car radios, public address and background music systems, it has a frequency range of 50 to 20,000 kHz - the lower limit variable with increases in cabinet volume. Recommended retail price is £9.00 excluding VAT.

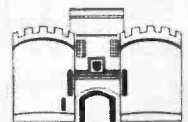- Aluminium Voice Coil
- High Flux 14,000 Oersted's Ceramic Magnet
- Roll Surround
- Double Diaphragm
- 8" Die-cast Chassis
- 8 ohms Impedance
- 15 Watt DIN Power Handling



Castle Acoustics Limited

Park Mill, Shortbank Road,
Skipton, Yorks. Tel: Skipton 5333.

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT PW, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m.-5 p.m.

PLEASE ADD 10% VAT

RESISTORS

$\frac{1}{2}$ W Iskra high stability carbon film—very low noise—capless construction.
 $\frac{1}{2}$ W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.
 $\frac{1}{2}$ W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	Price
$\frac{1}{2}$	5%	4.7 Ω -2.2M Ω	E24	1-3p
$\frac{1}{2}$	10%	3.3M Ω -10M Ω	E12	1-3p
$\frac{1}{2}$	2%	10 Ω -1M Ω	E24	3-5p
$\frac{1}{2}$	10%	1 Ω -3.9 Ω	E12	1-3p
$\frac{1}{2}$	5%	4.7 Ω -1M Ω	E12	1-3p
4	10%	1 Ω -10 Ω	E12	8p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7 Ω to 1M Ω .
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5k Ω to 2M Ω , log or linear (log $\frac{1}{2}$ W, lin $\frac{1}{2}$ W).
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch, 25p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 Ω and decades to 5M Ω . Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of
gas or smoke into an electrical signal. The sensor decreases its electrical
resistance when it absorbs deoxidizing or combustible gases such as hydrogen,
carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-
dioxide containing air or smoke. This decrease is usually large enough to be utilized
without amplification. Full details and circuits are supplied with each detector.
Detector GDI £2. Kit of parts for mains operated detector, including GDI but
excluding case, £5.60. Suitable case £1.50. Kit of parts for 12 or 24V battery
operation, including GDI and P.C. Board, £7.70. As above for PP9 battery, £6.90.
NOTE: The battery operated kits incorporate our patented circuit to minimise
battery drain. Typically 90mA for 24V.

PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to
dry, and immerse the board in the etchant. On removal the circuit remains
in high relief.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001 μ F, 0.0015 μ F, 0.0022 μ F, 0.0033 μ F, 0.0047 μ F, 3p. 0.0068 μ F, 0.01 μ F, 0.015 μ F,
0.022 μ F, 0.033 μ F, 3 $\frac{1}{2}$ p. 0.047 μ F, 0.068 μ F, 0.1 μ F, 5p. 0.15 μ F, 6p. 0.22 μ F, 7 $\frac{1}{2}$ p. 0.33 μ F, 11p.
0.47 μ F, 13p.

160V: 0.01 μ F, 0.015 μ F, 0.022 μ F, 0.033 μ F, 0.047 μ F, 0.068 μ F, 3p. 0.1 μ F, 3 $\frac{1}{2}$ p. 0.15 μ F, 4 $\frac{1}{2}$ p.
0.22 μ F, 5p. 0.33 μ F, 6p. 0.47 μ F, 7 $\frac{1}{2}$ p. 0.68 μ F, 11p. 1.0 μ F, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01 μ F, 0.015 μ F, 0.022 μ F, 0.033 μ F, 0.047 μ F, 0.068 μ F, 3p.
0.1 μ F, 4p. 0.15 μ F, 0.22 μ F, 5p. 0.33 μ F, 6 $\frac{1}{2}$ p. 0.47 μ F, 8 $\frac{1}{2}$ p. 0.68 μ F, 11p. 1.0 μ F, 13p. 1.5 μ F,
20p. 2.2 μ F, 24p.

MYLAR FILM CAPACITORS 100V

0.001 μ F, 0.002 μ F, 0.005 μ F, 0.01 μ F, 0.02 μ F,
3p. 0.04 μ F, 0.05 μ F, 0.068 μ F, 0.1 μ F, 4p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS

(μ F/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63,
22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10,
100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 8p. 47/63, 100/40, 150/25, 220/25, 330/10,
470/6.3, 7p. 68/63, 150/40, 220/40, 330/16, 1000/4, 10p. 470/10, 680/6.3, 11p. 100/63, 150/63,
220/63, 1000/10, 12p. 470.25, 680/16, 1500/6.3, 13p. 470/40, 680/25, 1000/16, 1500/10, 2200/6.3,
18p. 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1 μ F 35V	2.2 μ F 35V	22 μ F 16V	12p
0.22 μ F 35V	4.7 μ F 35V	33 μ F 10V	
0.47 μ F 35V	6.8 μ F 35V	47 μ F 6.3V	
1.0 μ F 35V	10 μ F 25V	100 μ F 3V	

VEROBOARD

2 $\frac{1}{2}$ x 3 $\frac{1}{2}$	0.1	0.15
24p	20p	
2 $\frac{1}{2}$ x 5	28p	28p
3 $\frac{1}{2}$ x 3 $\frac{1}{2}$	28p	28p
3 $\frac{1}{2}$ x 5	32p	32p
17 x 2 $\frac{1}{2}$	85p	67p
17 x 3 $\frac{1}{2}$	120p	108p
17 x 3 $\frac{1}{2}$ (plain)	76p	52p
17 x 2 $\frac{1}{2}$ (plain)	—	41p
2 $\frac{1}{2}$ x 5 (plain)	—	12p
2 $\frac{1}{2}$ x 3 $\frac{1}{2}$ (plain)	—	11p
Pin insertion tool	62p	62p
Spot face cutter	52p	52p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	28p	2.5mm Insulated	12p
Standard insulated	18p	3.5mm Insulated	12p
Stereo screened	40p	3.5mm screened	18p
Standard socket	20p	2.5mm socket	11p
Stereo socket	30p	3.5mm socket	11p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180, 5 pin 240, 6 pin, 7 pin.
Plug 12p. Socket 8p.
4 way screened cable, 25p/metre.
6 way screened cable, 30p/metre.

BATTERY ELIMINATOR

£1.70
9V mains power supply. Same size as PP9 battery.



become a RADIO-AMATEUR!

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

**BRITISH NATIONAL RADIO &
ELECTRONICS SCHOOL** P.O. Box 156, JERSEY


NAME: _____

ADDRESS: _____

WB74
BLOCK CAPS please

Stereo Radio

update
your
tuner.

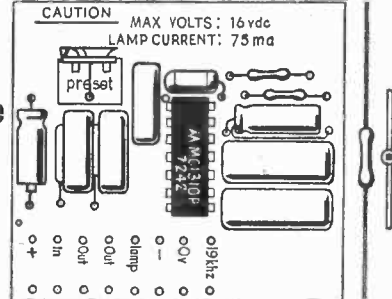

Jermyn now offer a stereo decoder module that simply and
easily converts your existing mono tuner for stereo reception.
Multiplex output equipped tuners simply have the module plug-
ged in, older types need the de-emphasis capacitor disconnected.

The unit will do justice to the most expensive equipment and
has the following specification.

Channel separation: Typically 40dB
Distortion: Typically 0.3% at 560mV RMS
Composite input signal
Stereo switching: Automatic with lighted indicator
Power supply: 10-16 volts.


Assembled and fully tested with a no-strings 12 month
guarantee the module costs an astonishing £6.90. Excluding VAT.
(Also available as a Kit at £4.90.) Beat that!

To Jermyn Industries Please rush me Kit(s), made up Stereo decoders.
164 Vestry Estate I enclose cheque/postal order for £
Sevenoaks Kent


Name
Address




Block Capitals Please

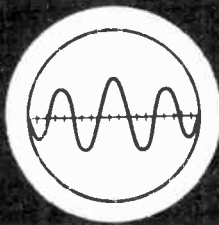

TUAC

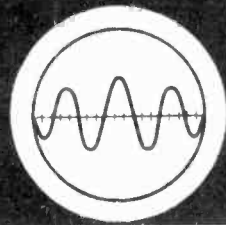

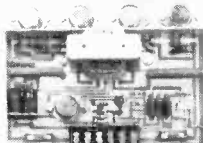NEW TUAC POWER MODULES. Now in their second successful year offering more power and quality than ever before.



TP100 ★ 125 Watts RMS continuous sine wave output
 Illustrated ★ 4 RCA 150 Watt 15 Amp output transistors
£17.25 ★ Special layer wound driver transformer
 ★ Short, open, and thermal overload protection
 ★ Compact size: 7 x 6½ x 3 in.

TL30 **£9.50**
 ★ 30 Watts RMS sine wave
 ★ Full thermal overload protection
 ★ Short and open circuit proof
 ★ Rugged transformer driver



TL100 ★ 100 Watts RMS sine wave
 Illustrated ★ 2 RCA 15 Amp output transistors
£13.00 ★ Rugged transformer driver
 ★ Full thermal overload protection
 ★ Compact size: 5 x 5 x 3 in.


TL60 **£12.00**
 ★ 60 Watts RMS sine wave
 ★ RCA 115 Watt output transistors
 ★ Only six connections to make
 ★ Same size as TL100

Specification on all three power modules :

All output power ratings ±1dB. Output impedance 8-15 Ohms. THD at full power 1% typically 0.5%. Input sensitivity 60mV into 10kΩ. Frequency response 10Hz-25kHz ±2dB. Hum and noise better than -75dB.

Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:

PS 125 ± 50 volts for one TP100	£11.75
PS 100 ± 45 volts for one TL100	£10.75
PS 60 ± 40 volts for one TL60	£9.50
PS 30 + 50 volts for one TL30	£7.00
PSU 2 for supplying Disco Mixer	£4.75

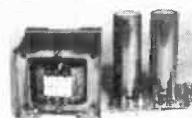

PRE AMPLIFIERS

All Tuac audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into the various wide range tone control circuits, producing superb sound quality from any signal. Previous range still available. 40V d.c.; 60mV o/p.

- VA08** Vol, Treb, Mid and Bass Controls. HI IMP. FET I/P. Suitable Mic, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treb +35dB at 16kHz, Mid +20-15dB at 1kHz, Bass +20-10dB at 40Hz. **£5.00**
- VA06** Vol, Treb and Bass Controls. 8mV sensitivity. Treb +28-15dB at 12kHz, Bass ±18dB at 40Hz. **£4.25**
- AMF01** Tuac Auto Fade Unit fades music when you speak. Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade O/P to main Amp. 30mV operating level. Depth and Vol. Controls. **£5.00**


VA08 ILLUSTRATED



SIZE 6½" x 2" x 1"

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING

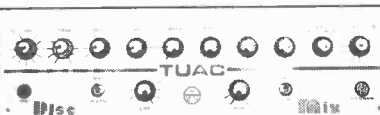ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS.



TUAC DISCOTHEQUE MIXER WITH AUTO FADE

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw. Tape Vol, L & R Deck Faders, Deck Volume. Treb. & Bass. H. Phon Vol, Selector. Master Vol, on/off sw. Max. output 1V RMS. Specification as VA06. **£27.00**

TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last



50 WATT RMS SINE WAVE ALL PURPOSE AMPLIFIER

Suitable for Disco, PA, Guitar. 4 inputs, 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leather-cloth covered case, short and open circuit protection. Tone control specification as VA08 pre-amp. FULLY FUSED.

50 WATT **£44.00**

100 WATT **£66.00**

NEW FROM TUAC!!

100W 2 x 12 Disco/Group cabs, fitted 2 50W RMS super heavy duty speakers **£66.00** (car. £1.00)
 100W 4 x 8 P.A. Cols, fitted 4 15W heavy duty speakers. **£75.00** pair (carr. £2.00).

TUAC MAIN DEALERS

BRISTOL DISCO CENTRE,
 86 Stokes Croft, Bristol 1
 Tel. Bristol 41666

CALBARRIE AUDIO
 38 Cromwell Road, Luton, Beds.
 Tel. Luton 411733

SOCODI,
 9 The Friars Canterbury, Kent.
 Tel. Canterbury 60948

CALLERS ONLY PLEASE

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
 SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
 OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.




TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD.
 DEPT. W
 163 MITCHAM ROAD, LONDON SW17 9PG
 01-672 3137/9080

R T V C

FOR AUDIO ON A BUDGET

PUSH BUTTON^(*) CAR RADIO KIT

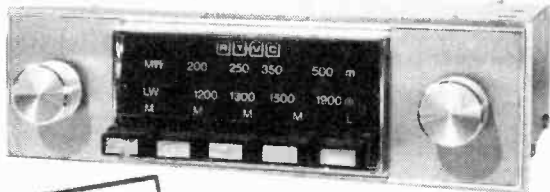

The first time Motor magazine have nominated a push button car radio for their Top Ten Accessory Awards



NOW BUILD YOUR OWN AWARD WINNING PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
- 2.) Integrated circuit output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.

Size Chassis 7 ins. wide, 2 ins. high and 4 ¹/₈ ins. deep approx.

NOTE: The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p free with kit.

Car Radio Kit

£6.60 + 55p. postage & packing.

Speaker including baffle and fixing strips
£1.65 + 23p. postage & packing.

Recommended Car Aerial - fully retractable and locking.
£1.35 post paid.

STEREO 21



QUALITY SOUND^(*) FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit, - no soldering required. Includes:-

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded:-

Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout.

Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx.

15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6". Complete only £18.95

Extras if required.

Optional Diamond Styli £1.37 £1.60 p & p.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. £3.85.



DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.


INPUT SENSITIVITIES

- 1) Crystal Mic or Guitar 9mV.
- 2) Moving coil Mic or Guitar 8mV.
- 3), 4), 5) Medium output equipment (Gram, Tuner, Monitor, Organ, etc.) - all 250mV sensitivity.

AC Mains 240V. operation, Size approx. 12 1/2 ins x 6 ins x 3 1/2 ins

£15.00 + 60p. postage & packing

DISCO 50

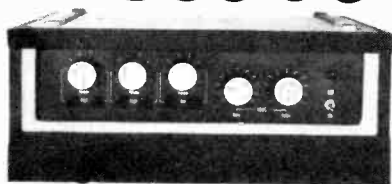


45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 1/4 x 10 1/2 x 8 ins. approx. Amplifier £27.50 + £1.50 p. & p

Special Offer: Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on opposite page). Complete £57.00 + £4.00 p&p.

COMPLETE (*) STEREO SYSTEM

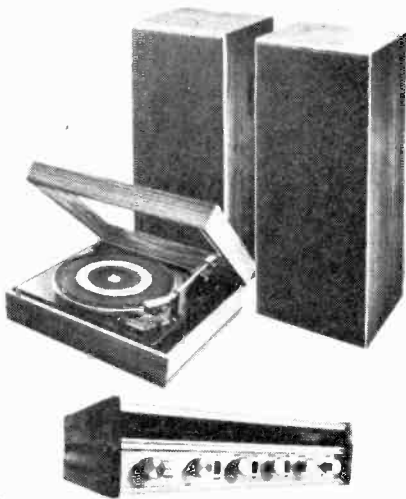

£51.00

40 Watt Amplifier.
Viscount III - R102 now 20 watts per channel.
System I includes.
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.
Specification
20 watts per channel into 8 ohms.
Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within -1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power).
Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics:* Bass: -12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble -12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.
Crosstalk better than 35dB on all inputs.
Overload characteristics better than 26dB on all inputs. Size approx. 13 3/4" x 9" x 3 3/4".
Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.
Two Duo Type II matched speakers - Enclosure size approx. 17 3/4" x 10 3/4" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter (10 watt handling)

Complete System £51.00

£69.00

System II
Viscount III amplifier (As System I)
Garrard SP. 25 (As System I)
Two Duo Type IIIA matched speakers - Enclosure size approx. 31" x 13" x 11 1/2". Finished in teak veneer. Drive units approx. 13 1/2" x 8 1/2" with 3 1/2" HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

Complete System £69.00

PRICES: SYSTEM 1
Viscount III R102 amplifier £24.20 + £1 p & p
2 Duo Type II speakers £14.00 + £2.20 p & p
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover £21.00 + £1.75 p & p.
total £59.20


Available complete for only **£51.00 + £3.50 p. & p.**

PRICES: SYSTEM 2
Viscount R102 amplifier £24.20 + £1.00 p. & p.
2 Duo Type IIIA speakers £39.00 + £4.00 p. & p.
Garrard SP25 with MAG cartridge de luxe plinth and hinged cover £21.00 + £1.75 p. & p.
total £84.20

Available complete for only **£69.00 + £4 p. & p.**

EMI SPEAKERS AT FANTASTIC REDUCTIONS

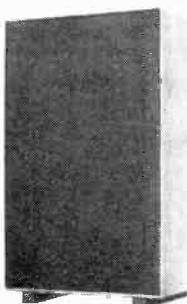THE ULTIMATE COMPLETE SPEAKER SYSTEM
EMI LE 315 listed price **£86.00**



A professional standard five way speaker system with enclosure giving top quality performance.

Enclosure Dimensions

approx. (3ft. x 2ft. x 1ft.)

Drive Units

Hand built - 15" diameter bass with 3" voice coil. - two 5" diameter Mid Range units. - two 3 1/2" HF units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment

Power Handling

Continuous rating 35 W rms. Peak power rating 70 W

Frequency Response

20 Hz 20,000 Hz. Imp. 8 ohms.

Our price **£45.00 + £3.50 p. & p.**

Recommended retail price **£86.00**




15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price **£40.80.**

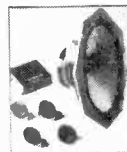OUR PRICE **£18.70 + £1.50 p & p + £1.50 p & p Special Offer.**



950 KIT

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz. Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00.

OUR PRICE £19.50



BUILD YOUR OWN STEREO AMPLIFIER (*)

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£7.64 + 55p. p & p



8 TRACK CARTRIDGE PLAYER (*)

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21

Technical specification: Mains input, 240V. Output sensitivity 125mV

Comparable unit sold elsewhere at £24.00 approx.

Yours for only £10.95 + 90p. p & p



Just write your order giving your credit card number

DO NOT SEND YOUR CARD

Mail orders to Acton. Terms C.W.O.
All enquires Stamped Addressed Envelope.
Goods not despatched outside U.K.

Leaflets available for all items listed thus (*)
Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG /c
323 Edgware Road, London W2

Personal Shoppers — Edgware Road: 9a.m.-5.30p.m. Half day Thurs.
Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

NO OVERSEAS ORDERS

SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original Scorpio Electronic Ignition System - with a big plus over all the other kits - the Electro Spares Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car or motor cycle.

When your Scorpio Mk. 2 is installed, you instantly benefit from all these Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE(C)
Tel: Sheffield (0742) 668888

TRAMPUS

MONEY BACK IF NOT SATISFIED
All brand new, full spec. Top grade.
FREE fabulous NEW catalogue. Send S.A.E.



Red + data. 1/8" pin source LED's 17p. TIL 209 and clip 22p
BIG 1/2" panel clip and RED LED 28p. GREEN and clip 59p.
INFRA RED LED £1. IC photo amp 44p and amp/switch 85p.

DIGITAL DISPLAY. LEO 1/3" 0-9 DP. DIL. £1-69. Minitor type 0-9 DP DIL £1-19. SOCKETS 13p. Calculator batt/mains from £19.

CHIPS. Texas etc. with 4 displays £12-6 displays and chip £14. Mostek data and alarm chips with 5 displays £19. pcb £1-49.
KIT: All parts and case. National chip. 4 digit £20. 6 x £23.
GAS sensor TGS 308 £2. KIT £4-69. Fully built £8.

With data **INTEGRATED CIRCUITS** 741: 8 pin 28p, to 99 and 14 pin 27p. 748 33p, 709 21p, 710 35p, 723 59p, 555 timer 79p. ZN414 rx. £1-10. 703 rf if £2p, mc 1310 and led £2-76, mc 1339 51¢, TAD 100 and if £2

1 AMP + REGULATOR 7805, 5 (& 7-20) V. also 12 & 15V £1-49.
AUDIO AMPS: mfc 4000 50p; 1 and 2W £1-19; 3W £1-29

74N TTL low prices

Gates 7400, etc. 16p, 7413 32p, 7447 £1-25, 7470/72 32p, 7474/76 39p, 7490 63p, 7492 69p, 74121 49p and all others in cat.
NEW 16 pin counter/driver 90/47 £2-25. DALO p.c.b. PEN 69p,
DIL SOCKETS: Professional/gold P. Pins hi or lo Profile 8, 14, 16 Pin 13p.
2N3055 33p four £1. BC107, BC108, BC109 all 9p each.
IN914 3p, ZENERS BZY88 8p, 1A RECTS 50V 3p, 400V 5p, BRIDGE 20p,
FETS: 2N3819 19p, 2N3823E 20p, 4416E 25p, BC182/3/4 10p, BC212/3/4 11p,
BCY70 13p, BD131/2 35p ea., BFY51/2/3 15p, TIS43 25p, 2N2926 Oy 7p, 2N3053 15p,
2N3702/3/4/5/6/7/8/9/10/11 all 9p ea., 2N3904/6 14p. HEATSINKS 51/TO5, 181/TO18 5p, TO3: 4YL 29p, TV3 14p
CAPACITORS: 25V 10, 50, 100 uf 5p, DISCS 4p, PRESETS 5p, CARBON-PTS 11p. Switch + 11p. Dual 59p. ULTRASONIC TRANSDUCERS £2 ea.
FLUORESCENT LIGHTS, 8W 13" 12 VOLT £2-59.

Trampus
electronics

ADD 10% VAT TO C.W.O.

P. & P. 10p CR.

P.O. BOX 29, BRACKNELL, BERKS.

L & M SUPPLIES

Barclaycard

Credit Terms for Callers

Access

Speaker Bargains

S.M.I. 450 kit 8 ohms	£4-50
13 x 8 3, 8 or 15 ohms	£2-15
13 x 8 co. axial "	£2-20
13 x 8 twin tweeter "	£3-41
13 x 8 350 8 ohm 20 watt	£7-70
13 x 8 EV 20watt with crossover	£6-05
Baker Group 25 3-8-15 ohms	£6-25
" " 3-8-15 ohms	£7-70
" " 50/12; 8-15 ohms	£12-40
Baker major	£7-50
" de luxe	£9-60
" superb	£12-00
" regent	£7-00
" major module	£9-30

Cabinets available for above units P & P 75p/pair.
Send S.A.E. for details.

Headphones. 1000-£2-42. 4000 £7-15 5000 £9-90 RE 227 £4-95. RE 240 £7-70. RE 255 £13-75. RE 245 £9-35. P & P 35p.
Cartridges Goldring G.800 £3-85. Sonotone 9 thac £1-80.
Cassettes Audio Magnetic Low Noise.
C.60 6 .. £1-91 10 .. £3-08
C.90 6 .. £2-84 10 .. £4-62 P & P 20p for 10.
Garrard SP25 Mk. 4 G.800 package £16-50.

Many popular Hi Fi systems at half price available at any of the following branches:- 57 Grays Inn Road, W.C.1. (Closed Sat) 242.5627


Hainault House, Hainault Street, New Eltham, S.E.9. 850-0892

Breamish House, Bilton Road, Erith, Kent. Erith 41327
347 Coventry Road, Smallheath, Birmingham 10.

360 Lymington Road, Highcliffe Hants. 042 52-6929

Sandringham House, Sandringham Drive, Bramcote, Nottingham 0602. 253051.

'BIG' Discounts

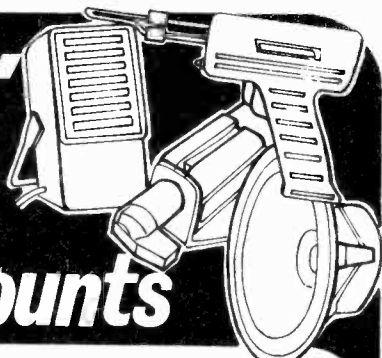

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS

EMI 13" x 8" 3, 8 or 15 ohm	£
Plain	2.00
With Co-Axial Tweeter	2.20
Twinn Tweeter	3.55
Type 350 8 or 15 ohm,	
20 watt	7.50
6 1/2" 8 ohm, 10 watt	2.30
8" 8 ohm, 10 watt	3.75
12" 8 ohm, 20 watt	5.50
8" x 5" C/Mag. 5 watt	1.20
8" x 5" Dualcone	
8 ohm, 10 watt	2.45
GOODMANS 6 1/2" 8 ohm	2.20
Dualcone	

ELAC 8" 8 ohm Dualcone	2.25
ELAC 8 ohm Dualcone 10 watt	3.35
FANE 7" x 4" 3 or 8 ohm	1.00
CELESTION 8" 15 ohm	1.55
ADASTRA 10" 8 or 15 ohm,	
10 watt	3.05
BAKER GROUP 25 12" 8 or	
15 ohm, 25 watt	7.65
P. & P.	.25
5" 8 ohm, 5 watt C/Mag.	.85
2 1/2" 8 ohm or 64 ohm	.50
P. & P.	.10

TWEETER & CROSSOVER

EMI 3 1/2" 3 or 8 ohm C/Mag.	1.00
Cone Tweeter 8 or 15 ohm,	
10 watt	2.40
Cone Tweeter 8 ohm, 3 watt	1.40
Horn Tweeter 8 ohm, 20 watt	5.85

Dome Tweeter 8 ohm, 30 watt	4.85
Crossovers CN23 (3 ohm),	
CN28 (8 ohm), CN216 (16	
ohm)	1.05
P. & P.	.10

KIT FORM CABINETS TEAK VENEER

12 x 12 x 6 with 8" 8" x 5" or	2.45
6 1/2" and 3 1/2" cut out	
17 x 10 x 9 with 8" or 13" x 8"	
cut out	3.50
18 x 11 x 9 with 13" x 8" cutout	4.25
for EMI 350	
P. & P. ea.	.35

MICROPHONES

CM70 Planet stick metal,	
switch crystal	1.55
DM160 Dynamic omni-dir.	
ball metal	4.95
UD130 50K/600 ohm, uni-dir	
ball me al	5.50

TW206	5.75
CONDENSER MIKE 600 ohm,	
uni-dir	9.50
Cassette Stick Mike with R.	
Control on/off switch	1.50
(2.5 & 3.5mm J/Ply)	.15
P. & P.	

SOLDERING IRONS

ANTEX GN240 15 watt	1.90
SK 1 Kit (15 watt Iron	
2 spare Bib etc.)	3.30

X25 25 watt (low	
leakage)	1.90
P. & P.	.10

CARTRIDGES

ACOS GP91/25C or GP91/35C	
Stereo comp.	1.00
GP93/1 Stereo crys.	1.35
GP94/1 Stereo crys.	1.75
GP95/1	1.35
GP96/1	1.75
GP101	.75
GP104	1.60

BSR SC5M Stereo ceramic	2.70
SX6H Stereo crystal	1.75
SX6M Stereo crystal	1.75
X5H Mono/stereo	1.45
X5M Mono/stereo	1.45
GOLDRING G800, G850 £3.85	£2.95
G800E	7.50
STYLI for above cartridges	
Sapphire .35 D. Diamond	1.25
GOLDRING G800 G850	1.95
G800E	3.95
P. & P.	.05

SONOTONE

9THAC Stereo cer. diam.	1.80
19-T1 Stereo crystal	.80

BATTERY ELIMINATORS

240v Input 6, 7.5 or 9 300mA	2.20
12v d.c. input (specify output)	

6, 7.5 or 9 d.c. output at	
300mA	2.20
P. & P.	.10

TAPES

Std.	LP	DP	
5" 45p	55p	70p	7"
5 1/2" 55p	65p	95p	

Std.	LP	DP
70p	1.00p	1.30p
P. & P. 1-3, 9p ea. 4 or more, lot 30p		

LOW NOISE CASSETTES

1-5	6-10	11-20	
C60 35p	33p	30p	Cassette Head Cleaner 35p
C90 45p	43p	40p	P. & P. 1-5, 3p ea. 6-10, 15p lot.
C120 55p	52p	50p	11-20, Post Free.

PLASTIC LIBRARY CASES

For 5" Reels	18p	
5 1/2" Reels	22p	
7" Reels	25p	

CASSETTE CASES	10p
P. & P. 1-3, 5p ea. 4 or more, 20p	

BIB ACCESSORIES

Tape Editing Kit Ref. 23	1.30
Recording Tape Splicer Ref. 20	1.15
Cassette Tape, editing Ref. 24	1.40
Cassette Salvage Kit Ref. 29	40p
12" Cassette Case Ref. 34	£1.00
Stylus Balance Ref. 32A	1.15
Spirit Lever Ref. 46	.50

Hi-Fi Stereo Test Cassette	1.90
Groove-Kleen Record Cleaner	1.90
P. & P.	.10

SPECIAL OFFER
 Unrepeatable!
 De-Lux Cassette Recorder,
 Mains/Battery, Portable, Remote
 Control Mike etc. Fantastic Value
 at £14.95 all Inclusive.
 WORTH DOUBLE.

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED.

Riversdale Electronics
 Mail Order Department **PW1**
 P.O. Box 470, Manchester M60 4BU.

TO SPARK YOUR IMAGINATION!

Kit comprises EVERYTHING:
 Case, cables,
 coil connectors,
 Silicon grease,
 8-page
 instruction
 leaflet.



NEW the **SPARKRITE** Mk II
Electronic Ignition Kit
 only £11.62

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £11.62 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available: £14.85 inc. V.A.T. and postage. GUARANTEED 5 YEARS.

ORDER NOW To: ELECTRONICS DESIGN ASSOCIATES,
 82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £11.62. Or for ready built unit £14.85

NAME _____

ADDRESS _____

(Live near Walsall? Call in for an actual workshop demo. It really is convincing.)

PW 7

HURRY – WHILE STOCKS LAST!

A COMPLETE RADIO STATION

FOR

ANY LOCATION FOR £64.52

DELIVERED OUR RISK. SECURICOR £3.00 EXTRA

ASSEMBLED IN SECONDS READY TO USE, COMPRISING—

1. **9R59DS** communications receiver 550 kHz to 30MHz continuous. Electrical band-spread on 10, 15, 20, 40, 80 metres. Fine tuning also on 160 metres, SWBC bands, Marine Band: **SSB-CW-ANL-BFO; S METER; MECH. FILTER; IF 445kHz; 1½W. OUTPUT;** Built-in quality Speaker; AC mains.
2. **JOYSTICK V.F.A.** The World Record Award Antenna (7' 6" long)
3. **JOYMATCH 111A A.T.U.** tunes above frequencies (transmitting amateurs, used with **V.F.A.** handles 300W **PEP SSB PA** input)
4. **ALL** necessary accessories incl. 8ft **V.F.A.** feeder and insulators for externally locating **V.F.A.**; terminated leads etc. In fact all **YOU** provide is the mains plug!

PLUS——a **FREE "DX-CRYSTAL SET"** incl. unique aerial (£2.42 separately).

JOYSTICK V.F.A. £13.75; **JOYMATCH TX/RX A.T.U. 111A** (see 3 above) £13.75; **JOYMATCH LO-Z 500 ATU TX/RX 500W SSB** (PA input) with RF meter £19.91; Communications Headphones 8Ω (suitable TRIO, EC10 etc) £3.14; **OA2** Mains stabiliser (plugs into 9R59DS) 74p; 6 spare **9R59DS** valves £2.35; Full set spare **9R59DS** valves incl. **OA2** £4.29; **Artificial Earth** (as used on oil Rigs) £5.80; **Aerial Bandswitch** tuned Aerial for domestic receivers £5.80; **ATU Kit 1.8–30MHz** receive and transmit (300w PEP SSB PA input) £5.80 (assembled £7.01)

Send stamp for details plus extra stamp for **9R59DS** brochure.

NO VAT ON overseas orders (deduct 1/11 from prices quoted), but EXTRA CARRIAGE and insurance necessary.

BOX 4 **PARTRIDGE**
BROADCASTERS NENT ENGLAND
ELECTRONIC

G3CED – G3VFA
FOR EXPERT ADVICE AND INFORMATION
Telephone: 0843 62535 or 62839
evenings and weekends



Save a massive £10 on the popular Sinclair Cambridge kit...

now only £14.95!

(PLUS VAT)

An advanced 4-function calculator in kit form

The Cambridge kit is the world's largest-selling calculator kit.

It's not surprising – no other calculator matches the Sinclair Cambridge in functional value for money; and buying in kit form, you make a substantial saving.

Now, simplified manufacture and continuing demand mean we can reduce even the kit price by a handsome £10. For under £15 (plus VAT), you get the power to handle complex calculations in a compact, reliable package – plus the interest and entertainment of building it yourself!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{3}'' \times 2'' \times \frac{1}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of normal use before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

Total cost? Just £16.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £27.45 – so you're saving £11! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- ✳️ Uniquely handy package. $4\frac{1}{3}'' \times 2'' \times \frac{1}{16}''$, weight $3\frac{1}{2}$ oz.
- ✳️ Standard keyboard. All you need for complex calculations.
- ✳️ Clear-last-entry feature.
- ✳️ Fully-floating decimal point.
- ✳️ Algebraic logic.
- ✳️ Four operators (+, -, x, ÷), with constant on all four.
- ✳️ Constant acts as last entry in a calculation.
- ✳️ Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £17.
- ✳️ Calculates to 8 significant digits.
- ✳️ Clear, bright 8-digit display.
- ✳️ Operates for weeks on four U16-type batteries.

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents :

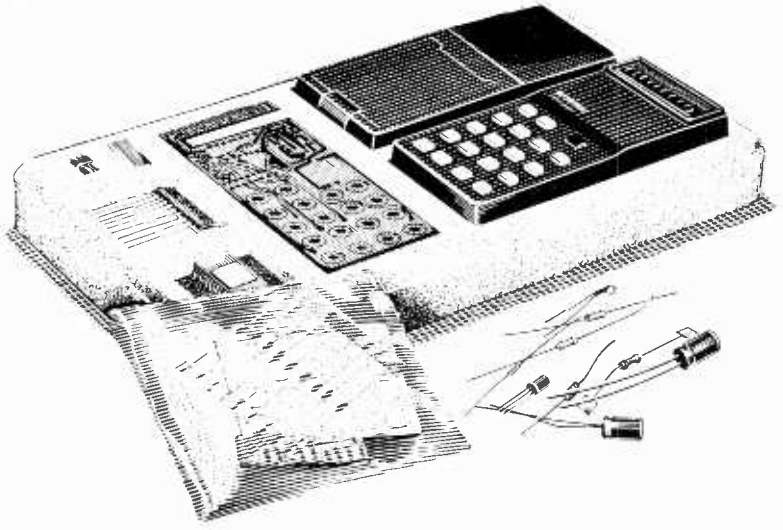
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

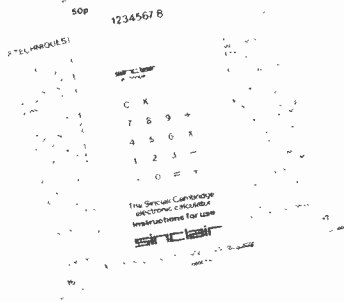But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

Why only Sinclair can make you this offer

The reason's simple : only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 80 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £14.95 + £1.50 VAT. (Total: £16.45)
Price fully built: £24.95 + £2.50 VAT. (Total: £27.45)

PW/7/74

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me

a Sinclair Cambridge Calculator kit at £14.95 + £1.50 VAT (Total: £16.45)

a Sinclair Cambridge calculator ready built at £24.95 + £2.50 VAT (Total: £27.45)

*I enclose cheque for £ _____, made out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/Access account. Account number _____

*Delete as required.

PLEASE PRINT

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

CURIOSITY!

WHENEVER some new idea or application appears on the public scene, we are often asked if we are going to publish a full project design so that constructors can make one. It may be that such an application has no existing off-the-shelf version that can be purchased by anyone.

Over the past year there has been a steady growth in the appearance of slot machines that offer two games of "tennis" or "football" for 10p. In the past six months they have been popping up like mushrooms, in pubs, restaurants, hotels, clubs, discotheques, railway stations and so on. Maddening, isn't it! There you are, confronted by a television screen and this white blob drifting about at random angles across the screen. How does it work? Can we make one for domestic television sets?

We hope that most of your questions on this subject, that have been coming to us recently, will be answered now. In this issue we start a do-it-yourself project that enables a domestic television set to be used to play "tennis". The principles employed are similar to the commercial version but the circuit design detail is totally original. We have carried out considerable work on this kind of project and have come up with a straightforward design for connection direct into the aerial socket of a u.h.f. 625-line receiver. We must however warn constructors that it is not cheap to make and it is important that the published design detail must be strictly followed to avoid problems that can occur in using digital integrated circuits.

Having said this we sincerely hope that the lesser experienced constructor will not be frightened off by the amount of hardware used, because the project is not difficult to build if you take care at every stage and avoid using unknown or doubtful alternative components.

For the more experienced constructor who wants something of a challenge, we recommend that you follow the design starting in the July issue of "Television". By following through all stages you can make a "tennis" game (not the same design as that in P.W.) then progress to football and possibly golf. In the latter, the circuitry is more involved enabling you to move the players into any position on the "field". The design in *Television* depends on some connections being made inside the television set and you should have some knowledge or experience in television before tackling it.

With these two designs we hope to have satisfied a great deal of curiosity that has been aroused. They represent for both magazines a significant achievement in development that, so far as we are aware, is unparalleled in any other magazine. They are original in detail and a "double-first" for do-it-yourself magazines.

M.A. COLWELL—Editor


The August issue sees another milestone for P.W.; the first of the "P.W. Super Separates" is a headphone amplifier—a top design by a top designer. Later in this series there will be a modern design f.m. stereo tuner with high sensitivity for long distance reception. Also in the August issue, we have a converter for the two-metre band. You cannot afford to be without Practical Wireless.

Further details on page 231

(All advanced details are subject to the current industrial situation)

NEWS...

Fuba-Goon!

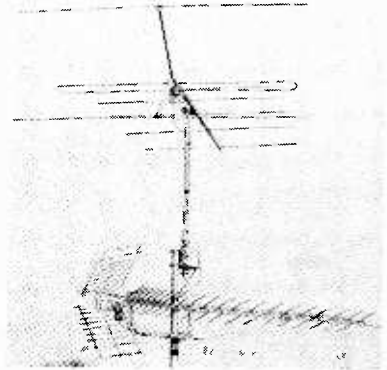

Peter's aerial system.

FUBA aerials (Audio Workshops Ltd.) have been supplied to Peter Sellers in his London home.

The requirement was for a top quality u.h.f. aerial signal in both colour and black and white to supply four outlets and to provide an excellent v.h.f./f.m. signal for home and continental reception.

It was decided to fit a Fuba XC 381 B u.h.f. aerial to cater for the three London channels, and a UKA Stereo 8 array with automatic rotator to cater for the f.m. requirement. Problems were encountered with reflections from nearby power station chimneys and other high buildings, but fitting the aerials on to a 15ft x 2in mast overcame the main difficulties.

The Fuba UKA 8 f.m. was fitted to a 3ft stub mast on a rotator on top of the 15ft mast. The u.h.f. array was sited below the rotator and set for best possible results.

Audio Workshops Ltd. of Robertsbridge, Sussex are the sole UK distributors of Fuba Aerials. *Audio Workshops Ltd., 29 High Street, Robertsbridge, Sussex.*

CQ column

THE CQ column is a valuable way of obtaining back numbers from other readers, but please reimburse expenses and the price of the magazines to those who have kindly offered to help!

MinPosTel

THE Ministry of Posts and Telecommunications has been abolished. Mr. Anthony Wedgwood Benn the Secretary for Industry, becomes responsible for the Post Office.

Those parts of the MinPosTel relating to the Wireless Telegraphy Acts are under the wing of the Home Office and Mr. Roy Jenkins.

Queen's Award

THE BBC announces that it has received the Queen's Award to Industry for the second time in five years. The award is for technological innovation in the transmission of sound and vision signals over a single vision link and relates to an original development by engineers of the Corporation's Research and Design Departments.

Arthur Bulgin, O.B.E.**Stars at Henry's of Harrow**

PETER SELLERS ably assisted by the Wombles of Wimbledon was the star attraction at the Gala opening of Henry's Hi-Fi Centre at Harrow recently.

Thousands of people turned up to see the festivities and in particular Peter Sellers—who lapsed into inspired “goonery” for a radio interview with Douglas Cameron of London Broadcasting. The Wombles set about encouraging the audience to tidy up the streets of Harrow just as they themselves do to Wimbledon Common!

After he had cut the ceremonial tape to officially declare the Hi-Fi Centre open, Peter Sellers then drew the winning entries for the Henry's Hi-Fi Contest in which £300 of Hanimex stereo/audio equipment was given in prizes. Lucky winner was Mrs. Joanne Courtney, of Pinner View, Harrow. She won a complete stereo outfit and four runners-up each received cassette players. The contest was run in conjunction with London Broadcasting who gave live coverage to the opening.

Delighted at the crowds who turned up for the opening Henry's Retail Director, David French remarked “You can't beat the old-time showmanship when it comes to attracting the crowds. At times it was reminiscent of Beatlemania outside the store”.

He had good reason to be pleased. The new Centre opened to bumper business and after the stars had left, the people of Harrow got down to the serious business of inspecting the vast range of hi-fi equipment on display.

The Hi-Fi Centre at Harrow is the first in a series of suburban developments by the Henry's radio group—which has hitherto had a concentration of shops in Central London.



Peter Sellers and the Wombles at Henry's.

FOLLOWING a short illness Mr. Arthur F. Bulgin, O.B.E., died at his home in Westcliffe on the night of Friday, 29th March, aged 75 years.

He was a well-known personality not only in Barking, Essex., where A. F. Bulgin & Co. Ltd. manufactures an extensive range of electrical and electronic component parts, but also in the electronics industry, being one of the six founders in 1932 of the Radio & Electronic Component Manufacturers Federation. Mr. Bulgin's passing marks the end of 51 years in the industry.

The chairmanship of the company now continues with his son, Mr. Ronald Bulgin who also shares joint managing directorship with A.F.B.'s brother, Mr. Stanley Bulgin.

Mr. Ronald Bulgin, M.A., C.Eng., M.I.E.E., has been with the company for over sixteen years. At the present time he is also chairman of the Radio & Electronic Component Manufacturers Federation.

SORRY WE ARE LATE!

We apologise for the late appearance of Practical Wireless. The delay has been caused by an industrial dispute within the printing industry.



THE 'SEVERN' PORTABLE

F. G. RAYER
G3OGR

WITH a multi-band receiver it is convenient to have a ferrite rod aerial for long and medium wave reception and a telescopic aerial for the short wave bands, with provision for connecting an external aerial when necessary. This receiver is this type and the four bands tuned are approximately as follows:

- (1) 160-260kHz long wave.
- (2) 575-1450kHz medium wave.
- (3) 1.8-5.0MHz shipping and short wave.
- (4) 5.7-15MHz general short wave.

The receiver has an inexpensive but robust case with a bottom compartment for holding logs of transmissions or other records. Five tuned IF circuits give good selectivity while the output stage provides adequate volume for ordinary purposes.

MIXER STAGE

Switching is used to select any of the four bands and this unavoidably results in some complication of the frequency changer circuit. Despite this, there should be no particular difficulty, especially as the receiver can be tested with coils for one band only before adding the other connections for full coverage.

Fig. 1 shows the mixer stage in which a 7-pole 4-way switch is used. Operation will become clear if each section is dealt with separately.

When an external aerial is used it is taken to socket A1 and in LW and MW positions of S1 is connected to the winding L4 on the ferrite rod. For normal MW or LW reception no external aerial is needed. In the other positions, S1 takes the aerial to the coupling windings L7 or L10 on the SW ranges.

Section S2 of the switch transfers the aerial tuning capacitor VC1 to L1/L2 for LW/MW reception or to L5 or L8 on SW. Aerial connection A2 is for a telescopic aerial. To ensure that there is no loss of

efficiency due to errors in alignment, when aerials are changed, the panel trimmer VC3 is provided to peak this circuit. S3 transfers the base to L3 for MW and LW reception or to the base coupling windings L6 and L9 for SW. S4 short circuits the LW coil L2 for MW reception and for LW reception, S4 brings in C2 with the trimmer TC2, for appropriate coverage of the LW/MW oscillator coil L11.

Switch section S5 selects the appropriate collector coupling winding of the oscillator coils, L12 for LW/MW and L15 or L18 for the short wave ranges. S6 similarly switches the emitter circuits. The emitter bias resistor R6 in series with the LM/MW winding L13 is different value from R5, used for both SW bands, permitting optimum results.


Switch section S7 transfers the oscillator tuning capacitor VC2 to the appropriate windings. C6 is a padder for the LW/MW coil L11, and TC3 and TC4 are trimmers on the SW coils L14 and L17.

A socket E allows an earth to be connected which is helpful when bringing in weak signals, in the 1.8-5MHz range in particular. Much general listening is of course possible on all frequencies with no external aerial. But reception of weak amateur and other signals on 1.8-2.0MHz, 3.5-3.8MHz and other bands will be greatly improved by an external aerial.

IF AMPLIFIER


This is assembled on a separate board, using the circuit in Fig. 2. IFT1 and IFT2 are double tuned, but in IFT3 only the primary is tuned. As these IFT's are pre-aligned the cores should be left as they are, pending any slight final adjustment for best results.

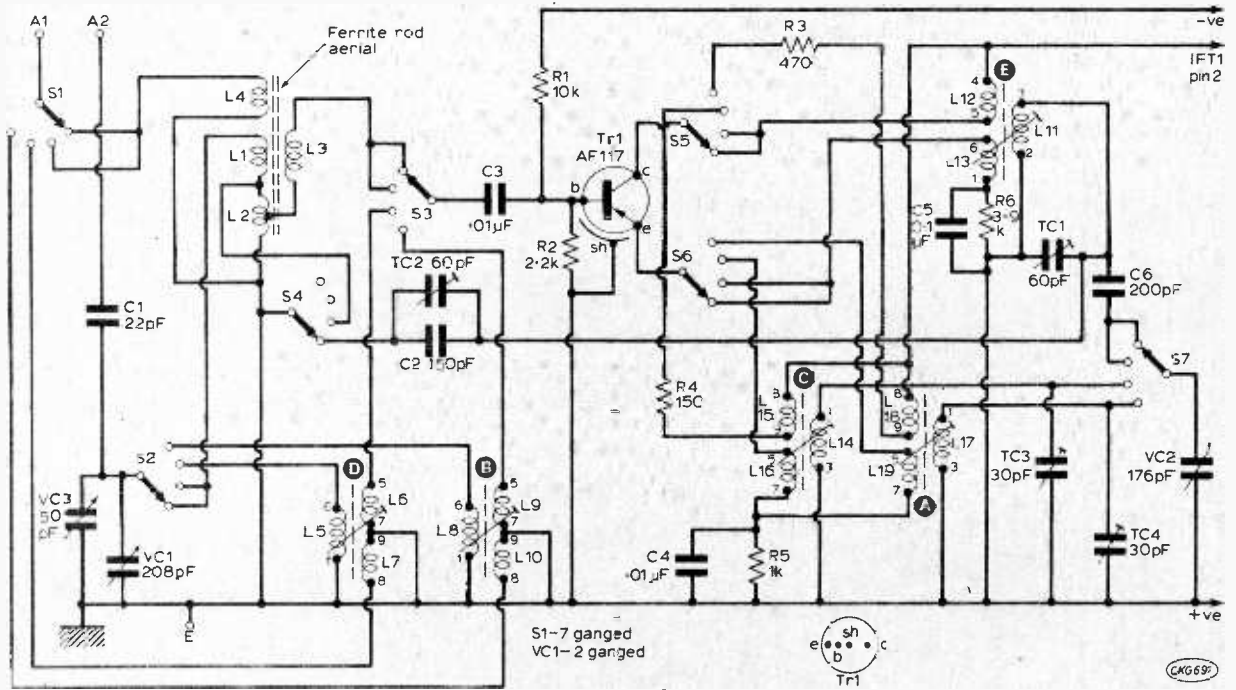This circuit gives very good sensitivity and selectivity. Audio output is taken from D1 to the volume control. The positive or earth line will go to the metal panel of the receiver when the amplifier is



▲ Fig. 1. Circuit of the mixer stage with four switched ranges covering 160kHz to 15MHz.

▼ Fig. 2. Two stage IF amplifier circuit with diode detector which drives the audio amplifier, Fig. 3.

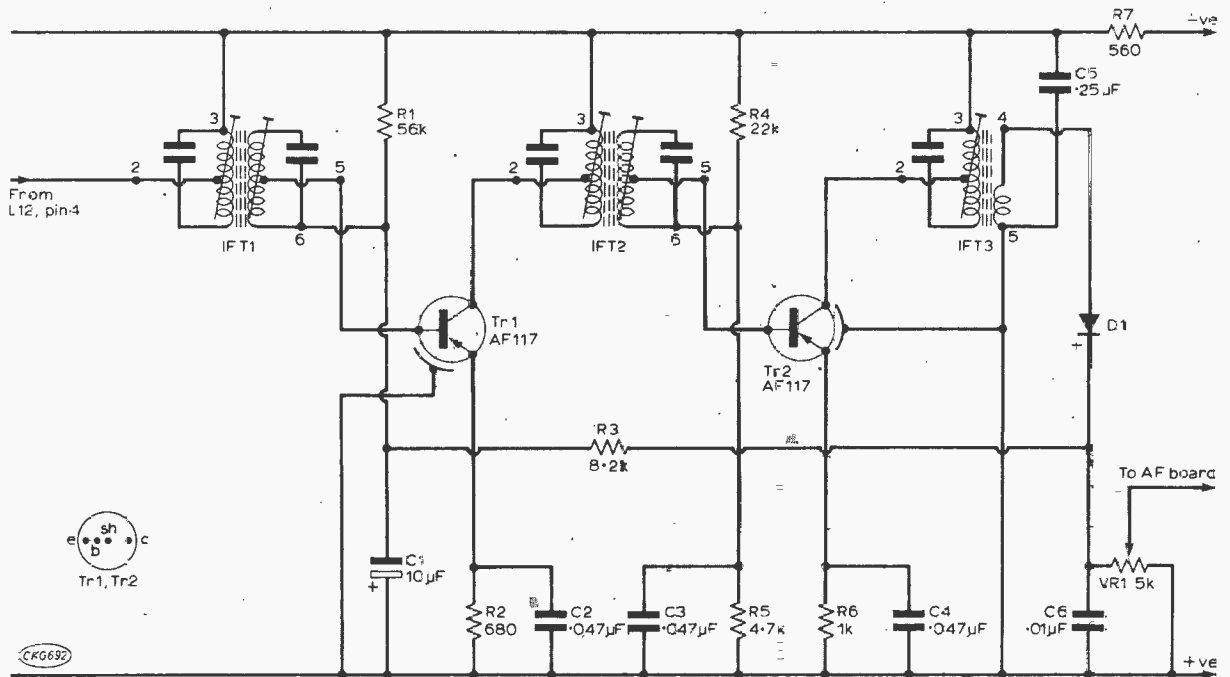


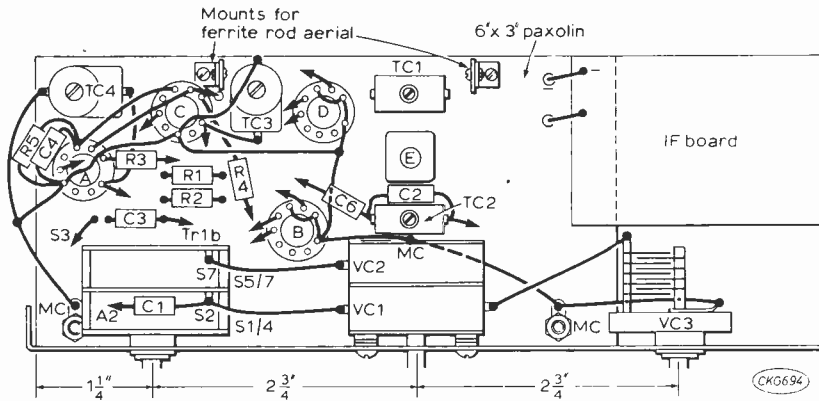


Fig. 4. Layout of mixer stage. Transistor Tr1 is located to the rear of switch wafer S5-7 and wired directly to the switch tags. See photograph.

Fig. 5. Wiring underneath the mixer stage board. It may be necessary to drill holes to clear the adjusting screws on TC1 and TC2.

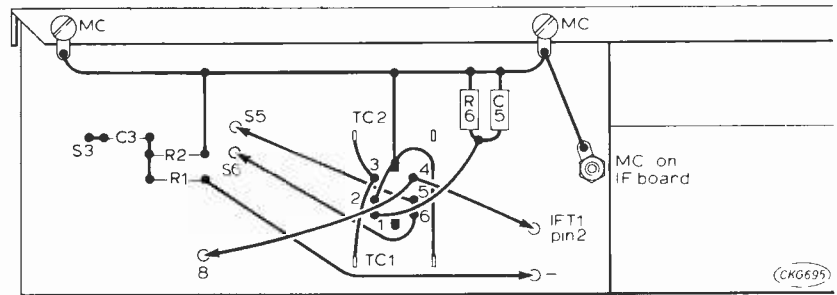

The switch and VC3 are $2\frac{3}{4}$ in from VC1/2. Drill a 6 x 3in paxolin board and the lower flange so that these can be bolted together as in Figs. 4 and 5. The tags MC are for connections to the metal chassis.

MIXER ASSEMBLY

As the full band switching results in quite a lot of wiring, this is probably the most difficult section. Referring to Fig. 4, A is the Range 4 oscillator coil and B the Range 4 aerial coil, C is the Range 3 oscillator coil and D the aerial coil. E is the LW/MW oscillator coil and its pins are wired underneath as in Fig. 5.

Connections to the switch are shown in Fig. 6. S1, S2, S3 and S4 are on the wafer nearest the panel, seen from behind. S5, S6 and S7 are similarly the contacts of the rear wafer. As contacts for sections S3 and S4, in particular, cannot be reached when the switch is fitted, lengths of thin insulated connecting wire should be soldered on first. It is of course essential that switch connections are correct. There should be no difficulty in seeing how the switch works. If there is, check its operation with

a meter or any other means of indicating continuity, for each position in turn.

S2 and S7 are near VC1 and VC2, as in Fig. 4. All other leads should be reasonably short and direct. Place Tr1 near the rear wafer with collector to S5 and emitter to S6, Fig. 6. Take the base lead down to C3, Fig. 4, and the screen lead to the positive line. It may be preferred to wire in coils A and B only, at first, and to test the receiver, adding the other bands afterwards.

Leave flying leads from C1 and S1 for aerial connections later. Also provide leads to run to the IF board.

FERRITE AERIAL

Two small brackets are bolted as in Fig. 4, holding vertical strips of paxolin about $2\frac{1}{2} \times 1\frac{1}{2}$ in each with a notch in the top to take the aerial rod which is secured with thread or elastic through holes in the strips.

The MW winding lies over TC4, its large winding is L1 and small winding L3. The LW winding has a tapping, and it is necessary to connect this coil so that the tapping is electrically near the earthed end.

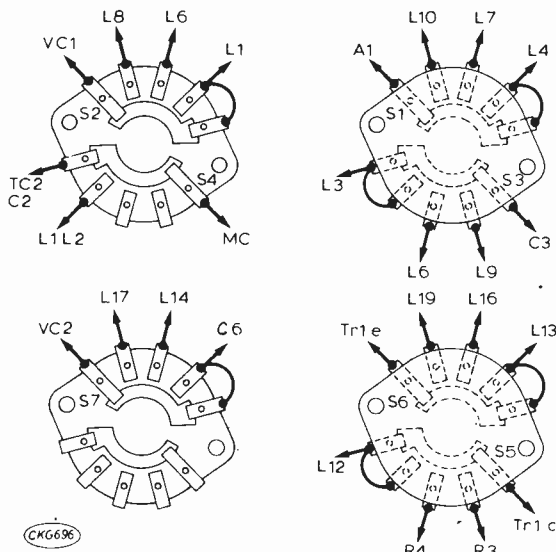


Fig. 6. Connections to switches S1-4 on the front wafer and S5-7 on the rear wafer.

Should it subsequently prove impossible to align the aerial circuit on long waves, slide the LW winding off the rod, turn it over, then replace it. The external coupling winding L4 can be anywhere near the centre of the rod and its leads are connected from S1 to MC.

IF BOARD WIRING

The IF board is $3\frac{1}{2} \times 1\frac{3}{4}$ in and Fig. 7 shows both sides. Drill holes for the IFT pins and screening can tags not forgetting a central hole to allow the lower cores to be reached for tuning. A very small round file will be helpful if some holes are not quite exactly placed.

Two tags MC are fixed with $\frac{1}{2}$ in 6BA bolts for chassis returns. Connect up according to Fig. 7, placing sleeving on any leads where this is necessary. C1 and D1 must be wired in with the correct polarity. This section is very straightforward and there is plenty of space for components.

The completed amplifier can be tested before fitting by connecting the volume control from the pin VR1 to MC and placing the lead from a signal generator near to pin 2 of IFT1. Audio output from the diode can be checked with phones or an audio amplifier. With low input from the generator the five cores can be adjusted for best results, using a correctly fitting tool (such as the TT5, available from the IFT maker). Only a very small adjustment should be necessary for any core.

The IF board is mounted by passing the one bolt through a hole in the mixer board, Fig. 5. At the other end of the IF board a strip of metal runs from the MC tag bolt to the flange of the panel, to which it is secured.

AUDIO BOARD WIRING

This board is $3\frac{3}{4} \times 1\frac{1}{2}$ in and is wired as in Fig. 8. Two bolts with tags again provide MC return points. Veropins are inserted for external connections to speaker, battery negative, R1 and for the negative lead from the IF board.

★ components list

MIXER BOARD

Resistors

R1 10k Ω	R3 470 Ω	R5 1k Ω
R2 2.2k Ω	R4 150 Ω	R6 3.9k Ω

Capacitors

C1 22pF	C3 0.01 μ F	C5 0.01 μ F
C2 150pF SM	C4 0.01 μ F	C6 200pF SM
VC1/2 208+176pF (Jackson Type 00)		
VC3 50pF variable (Jackson Type C804)		
TC1/2 60pF preset	TC3/4 30pF preset	

Inductors

Blue range 3T and 4T. Red range 3T and 4T (Denco—For transistor usage)
MW/LW Oscillator coil (Denco TOC1)
MW/LW Ferrite rod aerial (Denco)

Miscellaneous

Tr1, AF117. Switch, 7(8) pole, 4 way on two wafers (each wafer 4 pole 4 way). Paxolin sheet, 6 x 3 in.
Slow motion drive (Jackson 4489/C).

IF BOARD

Resistors

R1 56k Ω	R4 22k Ω	R7 560 Ω
R2 680 Ω	R5 4.7k Ω	VR1 5k Ω log. pot.
R3 8.2k Ω	R6 1k Ω	with switch S8

Capacitors

C1 10 μ F 6V	C3 0.047 μ F	C5 0.25 μ F
C2 0.047 μ F	C4 0.047 μ F	C6 0.01 μ F

Semiconductors

Tr1 AF117	Tr2 AF117	D1 OA81
-----------	-----------	---------

Miscellaneous

IFT1/2 (Denco IFT18/465). IFT3 (Denco IFT14).
Plain veroboard, 0.15 in. matrix, $3\frac{1}{2} \times 1\frac{1}{2}$ in.

AUDIO BOARD

Resistors

R1 2.7k Ω	R6 100 Ω	R11 2.2k Ω
R2 47k Ω	R7 680 Ω	R12 3.9k Ω
R3 3.3k Ω	R8 39 Ω	R13 390 Ω
R4 150 Ω	R9 5.6 Ω	VR2 50 or 100 Ω
R5 1.2k Ω	R10 5.6 Ω	WW preset

Capacitors

C1 2 μ F 6V	C3 8 μ F 6V	C5 250 μ F 10V
C2 100 μ F 10V	C4 100 μ F 6V	C6 25 μ F 6V
C7 100 μ F 10V		

Semiconductors

Tr1 OC71	Tr2 AC128	Tr3 AC128	Tr4 AC176
----------	-----------	-----------	-----------


Miscellaneous

Plain veroboard, 0.15 in. matrix, 4 x $1\frac{1}{2}$ in.
Speaker 15 Ω , 3 in. (Up to 6 x $3\frac{1}{2}$ in. can be accommodated)

All resistors 5 or 10% \pm or $\frac{1}{2}$ W

CABINET ETC.

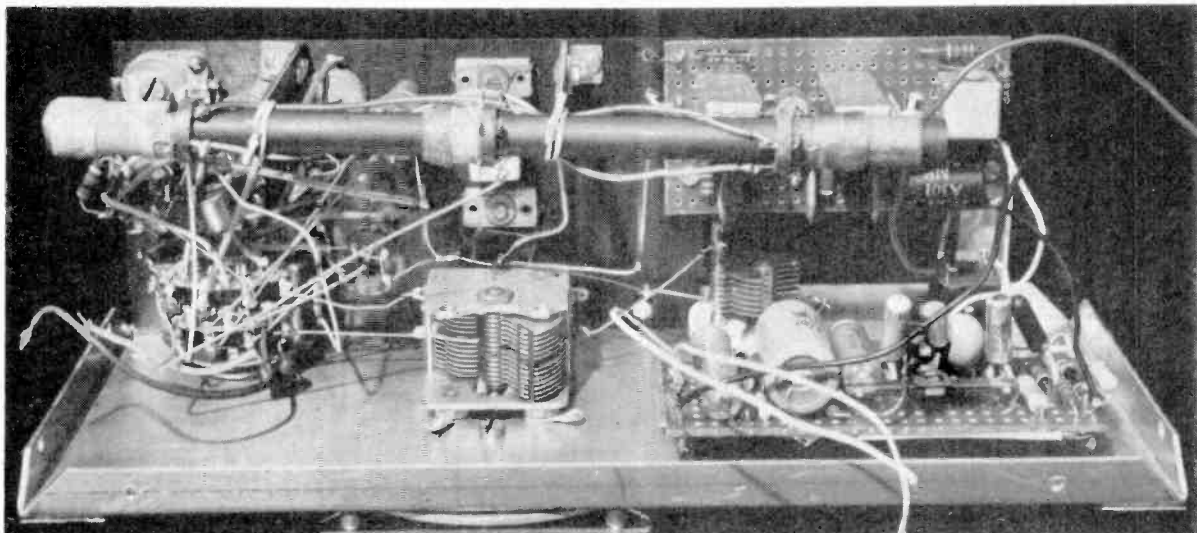Panel, 10 x 4 in., flanged universal chassis member
Cabinet top, 10 x 2 in., universal chassis member (Home Radio)
Plywood 6mm. Sides 9 x $3\frac{1}{2}$ in. (2). Baffle 10 x 4 in.
Bottom 10 x $3\frac{1}{2}$ in. Back $10\frac{1}{2}$ x $8\frac{1}{2}$ in. Drawer 10 x 1 in. and $8\frac{1}{2}$ x $3\frac{1}{2}$ in.
Telescopic aerial. Knobs. Handle.



In this view of the Severn portable the mixer stage transistor Tr1 can be clearly seen at the rear of the wafer switch, left. The audio board is mounted on the front panel. The IF board is below the right-hand end of the ferrite rod aerial.

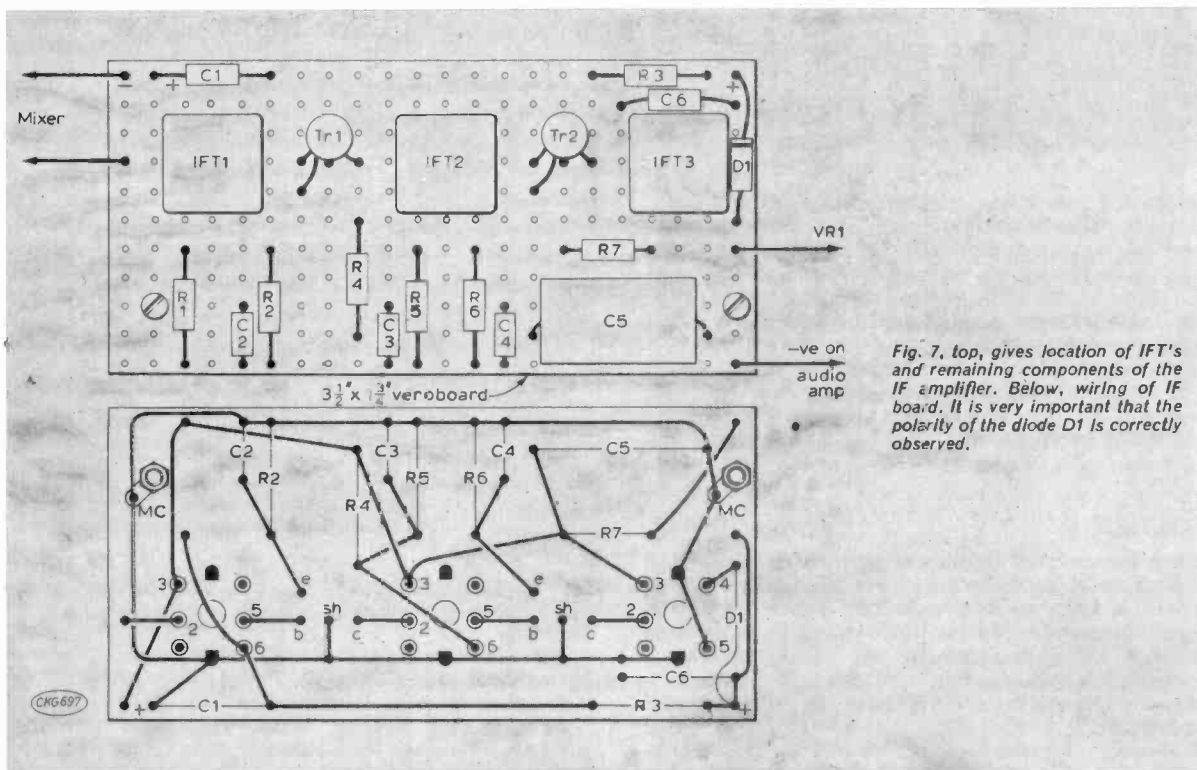


Fig. 7, top, gives location of IFT's and remaining components of the IF amplifier. Below, wiring of IF board. It is very important that the polarity of the diode D1 is correctly observed.

The completed board fits above VC3 and the volume control. To avoid drilling the receiver panel, extra nuts are put on the bolts and locked to a strip/piece of metal which is in turn held in position by the bushes of VC3 and VR1. After the amplifier has been fitted in this way, connections to the IF board, and VR1 and the on/off switch can be completed. The battery supply should not be connected until the speaker is wired to the amplifier.

With the switch set for the highest frequency band, check the coverage obtained. This can be modi-

fied at the low frequency end of the band by adjusting the core of L17 and at the high frequency end of the band by adjusting trimmer TC4. The panel trimmer VC3 should peak up signal strength throughout the whole tuning range. Adjust the core of L8 until this is so. VC3 should not be fully open or fully closed, with or without an external aerial or with the telescopic aerial extended. If necessary, TC4 may be re-adjusted to secure this result.

The receiver is then switched to the lower SW range and TC3, L14 and L5 similarly adjusted. The

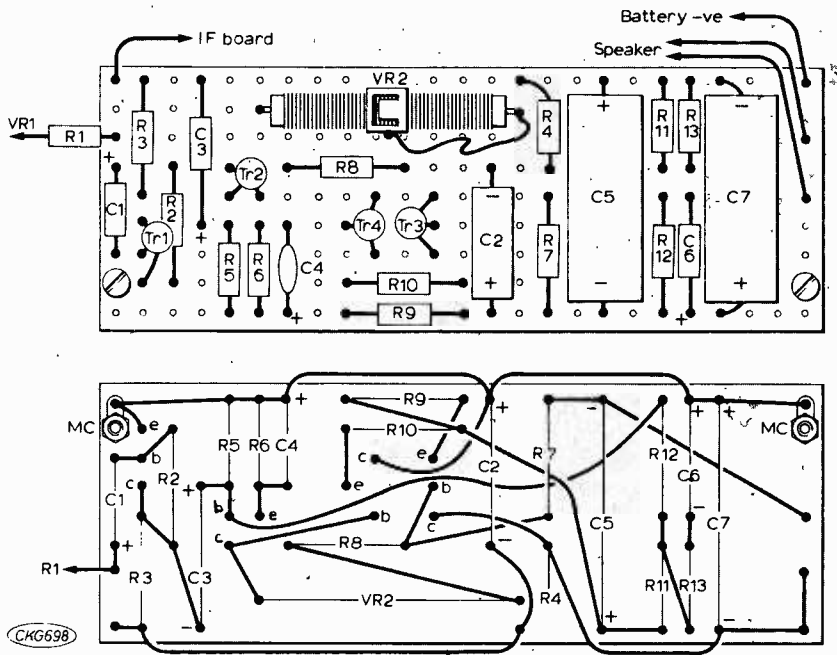


Fig. 8. The two sides of the audio amplifier board. Again, check polarity of the several electrolytic capacitors. VR2 may be replaced by a fixed resistor whose value may be found by first wiring in a potentiometer and adjusting it as described in the text.

next switch position is for MW reception and band coverage depends on L11 and TC1. Subsequently, move L1 on the ferrite rod for maximum volume when receiving signals near the LF end of the band (VC1/2 nearly closed). With correct alignment, very little re-adjustment of VC3 will be necessary, when tuning through the range.


The final position is for LW reception and alignment is obtained by moving L2 on the rod and adjusting TC2. The windings can be fixed with adhesive, when correctly positioned and coil cores may be locked with 6BA nuts.

CABINET

Each side of the cabinet is plywood 9 x 3 $\frac{3}{4}$ in and cut back to 2 $\frac{1}{4}$ in at the top to form a slope 4 in long. Two 6BA bolts each side secure the 10 x 2 in universal chassis flanged member which is flush with the back and $\frac{1}{8}$ in from the top. This member is covered with self-adhesive material before fitting.

Secure the receiver 1 in from the bottom, also inset about $\frac{1}{8}$ in, with two bolts each side. A piece of plywood 10 x 4 in with top and bottom edges bevelled is cemented to the plywood sides only. Corner strips cemented inside will strengthen this. Cut a 3 in dia speaker aperture, sandpaper and varnish this baffle before fitting. Cover the hole inside with speaker gauze. Screw on the speaker from behind, using a piece of hardboard with aperture if necessary, and checking that screws cannot penetrate the front.

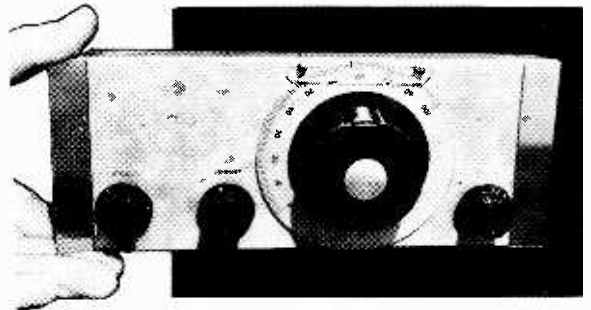The bottom is 10 x 3 $\frac{1}{2}$ in plywood, cemented in, with the back 10 $\frac{1}{2}$ x 8 $\frac{1}{2}$ in hinged to it. Two self-tapping screws through the back into the top runner hold the back closed. Screw a carrying handle to the top. The drawer is plywood, sliding between



The finished chassis before mounting in the cabinet.

strips cemented to the case sides and the case bottom and is 1 in deep.



A strip of scrap metal about 7 x 1 in is bent to hold the PP9 battery which is placed with its fasteners towards the wooden side. This strip is held by a screw securing the carrying handle, and screws into the side.

A black socket on the side is used for Earth and is connected to the panel by a tag held by one of the fixing nuts. A red socket for an external aerial is connected to S1. C1 may be connected to a telescopic aerial mounted on the side of the case. Alternatively, fit another socket, so that a short aerial, consisting of a few feet of flexible wire, can be plugged in here, for short wave reception. It is possible to remove the receiver without disturbance to the cabinet by unscrewing the four bolts holding the panel.

look! electronics really mastered

... practical
... visual
... exciting!

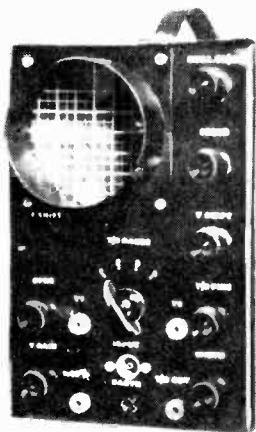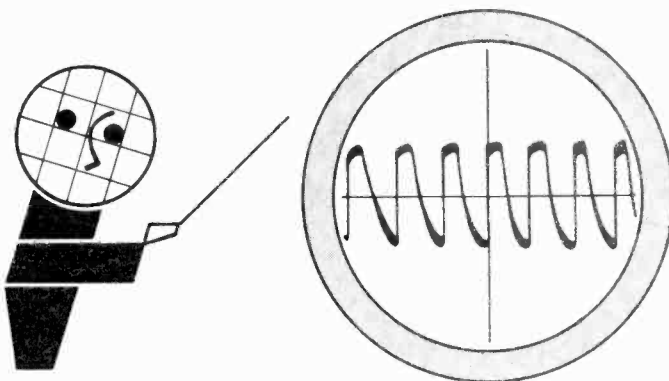no previous knowledge
no unnecessary theory
no "maths"




BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

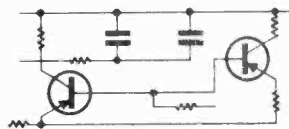2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE

**POST NOW
for
BROCHURE**

To: BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives

NAME

BLOCK CAPS

or write if you prefer not to cut page

ADDRESS

PLEASE WL74

special free gift also to all our students

Henry's

DON'T RELY ON YOUR MEMORY BUY NOW AT BARGAIN PRICES
Hi Fi and Transistors - Up to date
Brochures on request

HENRY'S CATALOGUE
Due to rapid price changes, shortages of paper and raw materials, all prices in the existing catalogues no longer apply. Call or phone for latest prices. A new catalogue will be available for Aug/Sept. 1974.

UK's LARGEST RANGE OF KITS & GADGETS



TEST EQUIPMENT

MULTIMETERS

- (carr. etc. 30p)
- ITI-2 20K/Volt Slimline 6 75
 - M210 (Case £1 25) 20K/Volt Slimline de-luxe 5 95
 - TLH33D 2K/Volt Robust 7 50
 - U437 10K/Volt Steel case. AC up to 40 KHz 4 95
 - AF105 (Case £1 90) 50K/Volt 11 95
 - U4313 20K/Volt AC current. Steel case 10 50
 - US431 Plus Built in transistor tester 10 50
 - Model 500 (Case £1 95) 30K/Volt 9 95

OTHER EQUIPMENT

- SE250B Pocket Signal Injector 2 10 carr. 15p
- SE500 Pocket Signal Tracer 1 70 carr. 15p
- TE15 Grid Dip meter 400kHz-280MHz 15 00 carr. 30p
- TE40 AC Millivoltmeter 1.2mhz 19 75 carr. 35p
- TE65 28 Range valve voltmeter 22 50 carr. 40p
- TE20D 120kHz-500mhz RF Generator 18 95 carr. 40p
- TE22D 20Hz-200kHz Audio Generator 19 95 carr. 40p
- SE350A Deluxe Signal Tracer 12 50 carr. 20p
- SE400 Volts/ohms/R-C sub./RF field/RF gen. 14 75 carr. 20p

New Revolutionary Supertester 680R


- | | | |
|--------------------------|----------------------|-------|
| 680R Multi-tester £18 50 | Accessories | |
| | Transistor tester | 11 00 |
| | Electronic voltmeter | 18 00 |
| | Amplamp | 11 95 |
| | Temperature probe | 11 95 |
| | Gauss meter | 11 95 |
| | Signal Injector | 5 95 |
| | Phase Sequence | 5 95 |
| | EHT Probe | 5 95 |
| | Shunts 25/50/100A | 4 50 |

A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester 6 95 p & p 15p
- Q4002 Piezoelectric System £13 70
- E1310 Stereo mag. cart. preamp. 4 80 p & p 26p
- Easphone D1201 telephone amplifier 7 50 p & p 20p
- D1203 Teleamp. with PU coil 8 40 p & p 25p
- LL1 Door Intercomm. and chime 8 40 p & p 25p
- 1 Kw Dimmer/controller 3 00 p & p 10p
- 9" Twin spring unit For 3 30 p & p 15p
- 16" Twin spring unit Reverbs 6 85 p & p 25p
- US50 Ultrasonic Switch Transmitter/Receiver £12 75
- C3041 1-250 Mhz £4 25
- C3043 5CH 1-300 Mhz £4 25
- VHF 105 Aircraft Band Converter 4 50 p & p 15p
- B2005 4 Ch. mic. mixer 4 20 p & p 15p
- B2004 2 ch. Stereo mixer 6 75 p & p 15p
- BK3 KII. Etc your own ptd circuits £1 95 p & p 20p

BUILD THIS RADIO

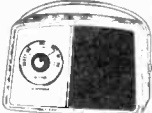Portable MW/LW radio kit using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600mW output. All parts £7 98 (battery 22p), carr. etc. 32p.




EXCLUSIVE: SPECIAL OFFERS

- MW/LW CAR RADIO Pair Akai ADM microphones. £6 95 c/p. 20p.
- PORTABLE CASSETTE TAPE PLAYER—for car or carry around. £7 25 c/p. 20p.
- HANIMAX BC808 POCKET CALCULATOR WITH % KEY. £28 95
- HANIMAX BC811M MEMORY VERSION £33 75
- MAINS UNIT for BC808 * BCM807 % Key £22 95
- * BCM850 % Key + Memory £33 95
- RH700 £10 25
- RH430 £4 14
- Wain W500 Battery/Mains Cassette Recorder £12 75
- AKAI GX40 Stereo cassette recorder. £54 50 Price £39 95. Plus free pair of stereo phones.

SPECIAL PURCHASES

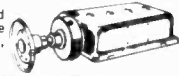UHF TV TUNERS CHANNELS 21 TO 64
Brand new transistorised geared tuners for 625 Line Receiver IF output. £2 50, Post 20p.



EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

- | | | |
|-----------|--|-------|
| Model No. | | |
| 310 | Radio control receiver | 3 29 |
| 300 | 4-channel R/C transmitter | 6 61 |
| 345 | Superhet R/C receiver | 6 61 |
| 65 | Simple transistor tester | 1 66 |
| 120 | 12 watt Amplifier | 4 50 |
| 125 | Stereo control unit | 4 73 |
| 130 | Mono control unit | 6 61 |
| 125 | Mono control unit | 14 16 |
| 605 | Power supply for 115 | 5 31 |
| 610 | Power supply for 120 | 5 31 |
| 615 | Power supply for 2 x 120 | 6 64 |
| 230 | AM/FM aerial amplifier | 3 29 |
| 240 | Auto packing light | 6 90 |
| 275 | Mic. preamplifier | 6 98 |
| 5705 | LF generator 10Hz-1mHz | 21 45 |
| 5755 | Sq. wave generator 20Hz-20KHz | 19 77 |
| 590 | SWR meter | 9 47 |
| 630 | STAB Power supply 6-12v 0.25-0.1A | 9 24 |
| 690 | DC motor speed Gov. | 3 31 |
| 700 | Electronic Chaffinch | 7 92 |
| 760 | Acoustic switch | 12 57 |
| 780 | Metal Detector (electronics only) | 10 91 |
| 790 | Capacitive Burglar alarm | 7 92 |
| 835 | Guitar preamp. | 4 99 |
| 840 | Delay car alarm | 6 99 |
| 875 | CAP. Discharge ignition for car engine (-Ve Earth) | 13 99 |
| 80 | Scope Indicator | 2 65 |
| 255 | Level Indicator | 6 98 |
| 525 | 120-160mhz VHF timer | 8 97 |
| 715 | Photo cell switch | 11 31 |
| 795 | Electronic continuity tester | 4 97 |
| 860 | Photo timer | 15 51 |
| 235 | Acoustic Alarm for driver | 8 61 |
| 465 | Quartz XTAL checker | 9 90 |
| 220 | Signal Injector | 2 30 |
| 390 | VOX | 15 50 |
| 432 | Testakit | 19 30 |
| 670 | Buffer Battery Charger | 6 55 |
| 850 | Electronic Keyer | 18 75 |
| 820 | Electronic Digital Clock | 58 50 |

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY Prices correct at time of preparation. Subject to change without notice.



BUILD THIS TUNER

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4 85, carr. 15p.

MULTI-USE & RADIONIC KITS

- 10-1 10 Projects 3 60
- 50-1 10 Projects 8 00
- 150-1 150 Projects 13 20
- Telephone Communicator 7 20
- X20 20 (Elec.) } Projects 4 95
- X40 40 (radio) } 9 45

All transistor circuits with hand books

TBA800 5 WATT I.C.
Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output. With circuits and data £1 50.



STROBE TUBE ZFT74A. Suitable for December '73 Pract. Electronics £3 00.



- ST2 (D32) DIAC 25p
- CRS1/40 SCR 45p
- ZFT4 £3 00
- ZFT8 £3 50



UK'S LARGEST RANGE OF TRANSISTORS AND DEVICES

- JUST A SELECTION**
- 10Y BA800 5 Watt IC £1 50
 - *SINCLAIR ICR 6 Watt IC £1 20
 - *ZN4141C Radio £1 20
 - *Ultrasonic Transducers £5 90 pr.
 - *3015F TSEG Indicator £1 70
 - TIL 209 LED 24p each. 22p each per 10

With circuits/data sheet
OVER 1500 DIFFERENT SEMI-CONDUCTOR DEVICES IN STOCK
Free stock list—latest edition (Ref. 36) on request. Includes radio valves, I.C.'s Rectifiers, Triacs, SCRs, LED's, etc. More types—better prices—discounts for quantity small or large.

GARRARD BATTERY TAPE DECK



GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/Eraser heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9 50 carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post. etc. 15p any quantity).

Singles Log and Lin
5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.


Ganged Log and Lin
10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. £1 75 (Quantity discounts available) Complete with knobs.

MARRIOTT TAPE HEADS

- 4 TRACK MONO or 2 TRACK STEREO
- '17' High Impedance £2 50
- '18' Med. Impedance £2 50
- '36' Med. Impedance £5 00
- R730/E73 2 track mono Record/Erase low imp. 75p pair.
- Erase Heads for '17', '18' and '36'
- '63' 2 track mono, HI imp. £1 75
- '43' Erase Head for '63' 75p

SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

- AMPLIFIERS (carr., etc. 20p)
- 4-300, 0.3 watt 9 volt. 1 75
- 104, 1 watt 9 volt 3 10
- 304, 3 watt 9 volt 3 95
- 555, 3 watt 12 volt 4 10
- E1208, 5 watt 12 volt 5 10
- 608, 10 watt 24 volt 4 95
- 10, 10 watt 28 volt 4 95
- E1206, 30 watt 45 volt 9 95
- E1210, 24 + 24 watts 12 volt 7 75
- RE500, 5 watt IC, mains operated Amplifier with controls 6 30
- SAC14, 7 + 7 watt Stereo with controls 11 75
- SAC13, 15 + 15 watt Stereo with controls 14 95
- SP40-5 2240/stereo 80/PZ5 25 00
- SP40-6 2240/stereo 80/PZ6 27 75
- SP60 2260/stereo 80/PZ8 30 45
- Transformer PZ8 3 95

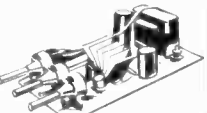

POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
- 470C 6 7/8" 9 volt 300 mA (includes Multi-Adaptor for Tape Recorders, etc.) 2 15 post 20p
 - Car Lighter Voltage Adaptors 300mA (State voltage 6v, 7.2v, 9v) 1 95 ea. post 25p
 - SC202 5 1/2" 9 volt 400mA 3 85 carr. 30p
 - HC244R Stabilised version 4 90 carr. 30p
 - P500 9 volt 500mA 3 20 post 20p
 - P11 24 volt 500mA (chassis) 2 90 post 20p
 - P15 26/28 volt 1 amp (chassis) 2 90 post 20p
 - P1080 12v 1 amp (chassis) 4 50 post 20p
 - P1081 45v 0.9 amp (chassis) 7 50 post 20p
 - P12 44-12 volt 0.4-1 amp (Stab.) 7 15 post 30p
 - SE101A 3/6/9/12 volt 1 amp (Stab.) 12 50 post 25p
 - RP164 6 7/8" 9/12 1 amp (Stab.) 12 95 post 30p

FIBRE OPTICS

- 0-01 Diam. Mono Filament £3 00
- per 50 metre reel 0.13 Diam. 64 Fibres Sheathed. £1 00 per metre.
- SPRAYS 15mm Diam. (Mares Tail Spray £10 50 7mm. Diam. £5 00)




All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.

Henry's RADIO LIMITED
EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
309 PA - Disco - Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres. London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Marrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

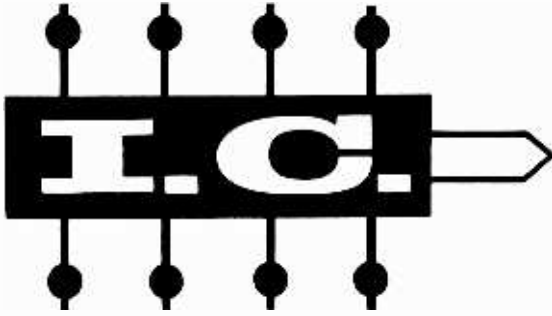All mail to: 303 Edgware Road, London W2 1BW
All stores open 9 am to 6 pm five days a week
Hi-Fi - Tape Equipment Discount Stock List Free at all stores



OF THE MONTH

Number 45

SGS TBA651 RADIO TUNER

DURING the past few years many new types of integrated circuits have been introduced which are specifically designed for use in radio receivers. The use of such devices enables smaller, high performance radio receivers to be produced. In addition, the reduced number of components results in the labour cost of assembling the receivers being minimised.

Description

The TBA651 contains the RF, oscillator, mixer and IF stages of a conventional type of superheterodyne receiver in a single integrated circuit. In addition, it contains a voltage regulator which keeps the performance almost constant as the supply voltage and/or temperature vary.

It is not possible to include tuned circuits on the silicon chip so they must therefore be connected externally to the device. In addition, some decoupling capacitors are required as well as a detector and an audio amplifier.

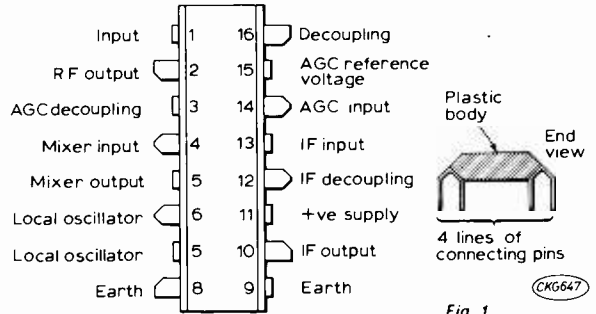


Fig. 1.

The TBA651 can be used in high quality domestic radio receivers and in car radio receivers for amplitude modulated signals at input frequencies up to 30MHz (10 metres). The device provides high gain, low noise and an excellent AGC characteristic. It is encapsulated in a 16 pin quad-in-line plastic case, the outline of which is shown in Fig. 1. IC's of this

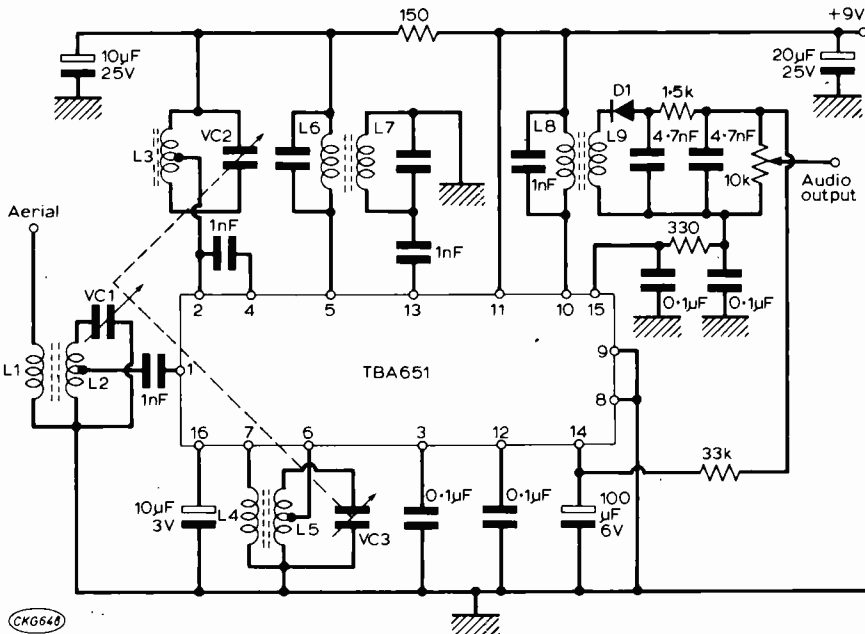


Fig. 2. Suggested circuit for a radio receiver designed around the TBA651. A capacitor, about 0.1µF, must be used to couple the audio output to the audio amplifier as DC is present at the output. A ferrite rod aerial may replace L1 and L2. Permeability tuning could be used in car radio applications.

type have alternate pins on each side of the body bent so that their ends form four lines (as shown in the end view). Sockets for these devices are not readily available and it is generally more convenient to solder directly to the pins.

Circuit

A typical circuit using the TBA651 is shown in Fig. 2. It includes a diode detector D1, which can feed an audio amplifier consisting of either discrete components or another integrated circuit.

The aerial signal is coupled to the input of the RF stage at pin 1 by means of L1 and the tuned circuit L2/VC1. The output signal from the RF amplifier appears at pin 2 across the tuned circuit L3/VC2. The two tuned circuits provide good image signal rejection. The capacitor connected to pin 3 provides AGC decoupling.

A signal taken from the tapping on L3 is fed to the mixer input, pin 4. The local oscillator tuned circuit is connected to pin 6 and the feedback winding to pin 7. The three variable capacitors VC1, VC2 and VC3 are ganged together and form the tuning capacitor.

The output from the mixer stage at pin 5 appears across the tuned circuit containing L6 and then coupled into the second IF tuned circuit containing L7, then feeding into the IF amplifier input stage at pin 13. The IF output appears at pin 10 across the tuned circuit containing L8. It is coupled to the untuned circuit containing L9 and detected by D1. It is filtered by the two 4.7nF capacitors and the 1.5k Ω resistor to remove the IF signal before being passed to the volume control and hence to the output.

It is important to note that the audio output from the volume control contains a steady voltage in addition to the audio signal. The output must therefore be capacitively coupled to the audio amplifier. A 0.1 μ F capacitor may be used.

Power supply

The TBA651 can be operated from a power supply voltage as low as 4.5V. The normal maximum operating voltage is about 16V but the device may be damaged if the absolute maximum permissible voltage of 18V is exceeded. The device requires about 12mA from a 12V supply, but much less at lower supply voltages.

Improvements

The simple circuit of Fig. 2 contains only three IF tuned circuits. The performance may be improved by the use of a more complex filter between pins 5 and 13, consisting of a number of tuned circuits resonant at the IF. However, it is generally more convenient to use one of the ceramic filters which are available. For example, the Toko filters contain an input and output tuned circuit coupled by a resonant ceramic disc. Such filters can provide a selectivity curve with the desirable flat top for good quality reproduction and the very steep skirts desirable for good adjacent channel selectivity. Nevertheless, ordinary tuned circuits are also required to provide good selectivity at frequencies away from the desired signal.

Filters of this type may have a pass band at least 6kHz wide (within the -6dB limits) and a response over 26dB down at 10kHz on each side of the centre frequency.

Performance

The gain of the RF mixer and IF stages are respectively about 20dB, 40dB and 60dB without AGC, but the losses associated with the tuned circuits must be subtracted from these values.

Fig. 3 shows how the output voltage from the receiver varies with the input level. The upper curve is for a 1.6MHz signal modulated at 30% at 1kHz, whilst the lower curve is the noise output when an unmodulated signal is fed to the input. It can be seen from the upper curve that the AGC action results in the audio output increasing from 0.5V at 20 μ V input level to only 1V at about 0.5V input. AGC is applied to the RF and mixer stages.

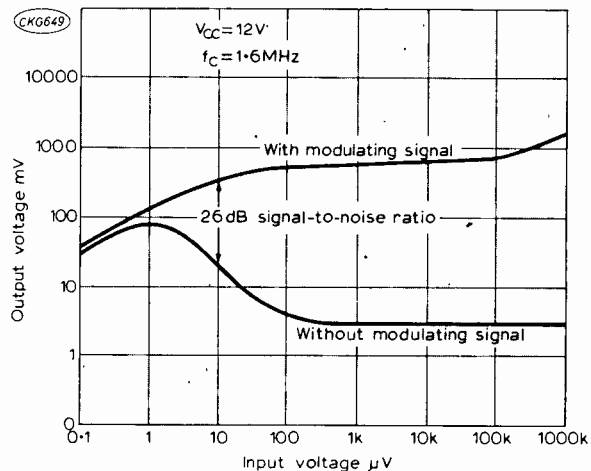


Fig. 3. Graph demonstrating the AGC characteristic of the TBA651.

The vertical distance between the two curves is a measure of the signal-to-noise ratio at the input level concerned. The high gain of the RF stage is largely responsible for the good signal-to-noise ratio even at low input signal voltages. The AGC applied to the RF stage is delayed until the input voltage exceeds a certain level so that the gain of the RF stage is a maximum at low input voltages thus providing a maximum signal-to-noise ratio. The amount by which the AGC is delayed can be reduced by connecting a resistor between pins 3 and 15 or increased by connecting a resistor between pins 3 and 14.

The TBA651 is a well-known device which is equally useful to the equipment manufacturer and to the amateur experimenter. Although no band switching is shown in Fig. 2, this circuit is suitable for use from the long wave band up to the highest short wave frequency used for long distance communication.

The TBA651 is available from Ambit International Ltd., 37 High Street, Brentwood, Essex, CM14 4RH at about £1.82 at the time of writing. This company also stocks Toko ceramic filters suitable for use with the IC.

QUALITY STEREO SOUND

ALMOST **1/2 PRICE OFFER!** SOLENT AUDIO SYSTEM



£5 down

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM
OUR PRICE **£49.95**

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,00 Hz) Tape record and playback facilities. Dimensions 18" x 8½" x 3¼". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £2.50. Send £7.50 today.

Chassis only available for cash at £35.00.


Full 12 months Guarantee.

CALLERS WELCOME.

FREE Stereo headphone supplied with every order.

LEWIS radio W.S. 7/74, 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-886 9666/3733

Great Holiday Project

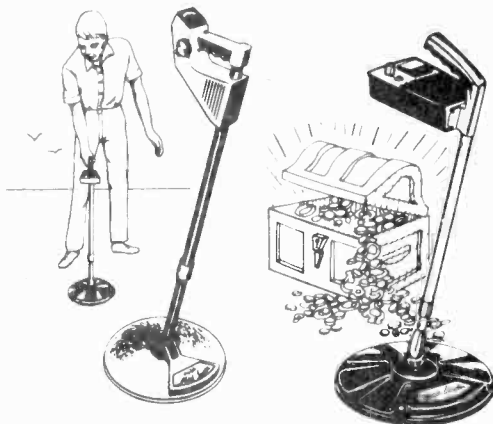

In only two evenings you can build one of these Heathkit Professional Metal Locators.

Your kit comes complete down to the last nut and bolt—all you have to do is follow our simple step-by-step instructions and you're ready to go. You'll be really amazed at how easy it is.

Ideal for:

- Treasure hunting
- Beachcombing
- Locating dropped coins and other metal objects
- Tracing hidden piping underground and many other uses in and around the home.

For details about these and many more models in our range, send for your FREE copy of the Heathkit Catalogue—today!

SOLDERING GUN



240 VOLTS A/C


£2.75

VAT PAID

P & P 33p

New surplus stock as illustrated. AC240 volts. Input power 100 VA. Instant heat at touch of trigger switch in handle. Constructed in robust plastic casing with work light in front and 4' x 3' core cable.

PROGRAMME TIME SWITCHES

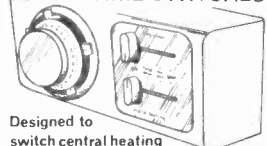

Designed to switch central heating and hot water on/off twice a day. Suitable for any electrical appliance up to 3 amps 240volts A.C.

£5.50 P & P 28p

VAT paid.

New surplus stock as illustrated. Size 7" x 4" x 3"

Smiths Time Switch with 24 hour dial which is simple to set to switch on/off twice per day at any times required. Also fitted with two lever switches which can be set to operate two circuits which can each be set to operate on Time Switch twice per day, all day, continuous, or off. Mounted in robust white plastic casing Drilled for fixing on back supplied with wiring instructions. Ideal for shop lighting and many other applications.

SAE FOR CATALOGUE WITH MANY OTHER BARGAINS TO

C. W. WHEELHOUSE & SON,
9/13 BELL ROAD,
HOUNSLOW.
PHONE 01-570-3501.

Please send me the FREE Heathkit Catalogue plus details of your low deposit terms. Without obligation.

NAME _____

ADDRESS _____

HEATH
Schlumberger
Heath (Gloucester) Ltd.,
Dept. PW/7/74, Bristol Road,
Gloucester GL2 6EE



WILMSLOW AUDIO

THE Firm for speakers!


SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£7.75
Baker Group 35, 3, 8 or 15 ohm	£8.50
Baker Group 50/12, 8 or 15 ohm	£12.50
Baker Deluxe	£10.75
Baker Major	£8.50
Baker Superb	£14.50
Baker Regent	£7.75
Celestion PST8 (for Unilex)	£2.55
Celestion MF1000, 8 or 15 ohm	£10.45
Celestion HF1300, Mk II	£6.16
Celestion G12M, 8 or 15 ohm	£12.00
Celestion G12H, 8 or 15 ohm	£15.00
Celestion G15C, 8 or 15 ohm	£24.00
Celestion G18C, 8 or 15 ohm	£33.00
EMI 13 x 8, 3, 8 or 15 ohm	£2.15
EMI 13 x 8 d/c, 3, 8 or 15 ohm	£2.35
EMI 13 x 8 t/tw, 3, 8 or 15 ohm	£3.60
EMI 13 x 8 type 350, 8 or 15 ohm	£8.25
EMI 8 x 5, cer. mag., 8 ohm	£1.65
EMI 8 x 5, 10 watt d/c roll surr., 8 ohm	£2.50
EMI 6 1/2" 93850, 4 or 8 ohm	£2.80
EMI 5" 98132CP, 8 ohm	£2.30
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2.65
Elac 6 1/2" d/c roll surr., 8 ohm	£3.35
Elac 6 1/2" d/cone, 8 ohm	£2.65
Elac Tweeter TW4 4"	£1.21
Elac 10" 8 ohm	£2.65
Fane Pop 100 watt 18"	£22.50
Fane Pop 60 watt 15"	£13.00
Fane Pop 50 watt 12"	£11.00
Fane Pop 25/2 12"	£6.40
Fane Pop 15 watt 12"	£4.40
Fane Crescendo 12A or 12B	£29.00
Fane Crescendo 15	£36.00
Fane Crescendo 18	£47.50
Fane 807T 8" d/c roll surr. 8 or 15 ohm	£3.85
Fane 808T 8" d/c 8 or 15 ohm	£2.75
Goodmans 8P 8 or 15 ohm	£4.49
Goodmans 10P 8 or 15 ohm	£4.70
Goodmans 12P 8 or 15 ohm	£11.65
Goodmans 15P 8 or 15 ohm	£18.00
Goodmans 18P 8 or 15 ohm	£31.00
Goodmans 12P-D 8 or 15 ohm	£15.25
Goodmans 12P-G 8 or 15 ohm	£14.50
Goodmans 12AX Audiomax 8 or 15 ohm	£39.65
Goodmans Audiom 100	£9.50
Goodmans Axent 100	£6.60
Goodmans Axiom 401	£15.10
Goodmans Twinaxiom 8, 8 or 15 ohm	£6.79
Goodmans Twinaxiom 10, 8 or 15 ohm	£7.61
Kef T27	£4.75
Kef T15	£5.75
Kef B110	£6.75
Kef B200	£7.50
Kef B139	£11.75
Kef DN8	£1.92
Kef DN12	£4.12
Kef DN13	£2.75
Richard Allan 12" d/c 3 or 15 ohm	£2.50
Richard Allan CG8T 8" d/c 8 ohm	£6.35
WMT1 speaker match. trans. 3-15 ohm	£1.10
Wharfedale Super 10 RS/DD	£9.80
2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm	£1.38
7" x 4" 3, 8 or 15 ohm	£1.38
8" x 5" 3, 8 or 15 ohm	£1.38
10" x 6" 3, 8 or 15 ohm	£1.92
S.T.C.4001 G Super Tweeter	£6.19

SPEAKER KITS

Wharfedale Linton 2 (pair)	£19.25
Wharfedale Glendale 3 (pair)	£34.50
Wharfedale Dovedale 3 (pair)	£52.00
Richard Allan Twinkit (each)	£8.25
Richard Allan Triple 8 (each)	£13.00
Richard Allan Triple (each)	£18.00
Richard Allan Super Triple (each)	£21.50
Goodmans DIN 20 (each)	£8.75
Fane Mode 1 (each)	£9.90
Peerless 20-2 (each)	£10.41
Kefkit 2 (each)	£23.50
Kefkit 3 (each)	£24.00
Helme XLK25 (pair)	£18.17
Helme XLK50 (pair)	£37.18
Baker Major Module	£10.75

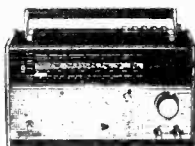P.A. and Hi-Fi Speaker Cabinets.
Send for Free booklet "Choosing a Speaker".
Carr. and Insurance 75p per kit (£1.50 pair).



PA/DISCO AMPLIFIERS

Carriage and Insurance £1.00	
Baker Major 100 watt	£46.00
Linear 30/40	£30.00
Linear 40/60	£35.00
Linear 80/100	£59.75
Linear 100 watt slave	£44.00

RADIOS/CASSETTES

Grundig Solo Boy	£16.00
Grundig Top Boy	£17.75
Grundig Party Boy 500	£22.75
Grundig Melody Boy 500	£26.75
Grundig Elite Boy 500	£26.75
Grundig Signal 500	£26.50
Grundig Yacht Boy 210	£34.00
Grundig Melody Boy 1000	£38.75
Grundig Satellit 2000	£121.00
Grundig C410 Cassette	£28.50
Grundig RF430 mains radio	£26.75
Grundig RF310 mains radio	£22.00
Tandberg TP41	£43.00
ITT Weekend Auto	£18.00
ITT Golf Preset	£24.50
ITT Colt	£11.50
ITT Europa	£20.50
ITT SL53 Cassette	£25.75
ITT Studio 60M Cassette	£32.75
ITT Studio 73 Cassette	£48.00
Bush VTR178 5 band (inc. air)	£29.00
Koyo KTR1770 11 band	£58.95
Koyo KTR1663 or 1664 8 band	£42.00
Koyo KTR1883 5 band	£22.00
Murphy BA209 Radio/Cassette	£22.75

Carriage and Insurance 75p.
FREE with each radio—World radio stations book.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 35p per speaker (tweeters and crossovers 20p)

ALL PRICES QUOTED INCLUDE V.A.T.

WILMSLOW AUDIO Dept. P.W.

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

The items below are from the April Supplement to our 1974 Catalogue. You can receive this Catalogue and the next 12 supplements by sending 60p.



THIS MONTH'S SNIP Cassette Tape Player Recorder. With dynamic microphone. First class Jap. made tape recorder and player. Push button operated and with automatic level control of recording. Standard cassettes clean jacks for mic. (which has motor stop/start switch) for recording from radio and for being powered by mains. A bargain at £8.95 plus 35p post, etc.

Mullard Unilex. The 4 Mullard modules—2 EP9000, 1 EP9001, 1 EP9002, for £7.50 plus 30p post. The control panel kit, with spun aluminium faced knobs and silk screened front plate cannot be reduced, but at least we will hold the price at £9.30 despite increases in price.

Spartan Portable Radio. Long and medium wave band, telescopic pull up aerial, leather carrying case, size approx. 6" x 4" x 2". 7 transistors ferrite rod aerial. Uses comparatively large speaker, so tone better than average. Brand new in original packing case, untreated, only £1.95 each. Instant Start Fluorescent Lighting bargains. Starterless control gear, resin filled, super-silent coil running, by very famous maker. 4ft 40w £1.50, 5ft 65w £1.60, 5ft 80w £1.75, 6ft 85w £1.95. These are about one week of maker's current prices and can't be repeated once stocks are cleared: Add 20p per piece carriage.

Mini Screwdriver. Only 3" long with plastic handle. Exceptionally good quality steel. Ideal to carry in your ticket pocket. Fits all terminal blocks, etc. 5p each, 10 for 46p.

Wall Mounting Thermostat. Kit containing neat ivory plastic case, thermostat that will switch 15A at normal mains voltage and pointer knob. Price £1.25 lot.

Hooper Siren. Battery operated. Works from 11V-41V upwards. Useful for burglar alarm or personal alarm. Has its own battery holder. Price 30p.

50 ohm Wire Wound Control Colvern with standard 1" spindle for knob. 3 watt size. 30p each.

Sensor Head for Smoke/Gas Detection. Ceramic semi-conductor which changes its resistance very rapidly when atmospheres become polluted by smoke, coal gas, natural gas, alcohol, exhaust fumes, paint vapour and fire damp, etc., etc. Price £2.20 each.

Plug-in Base. For Smoke detector head. 6p each.

Bargain Parcel of I.C.s. 5 Brand name and perfect devices—all type coded and made by Plessey Semiconductors and supplied complete with technical data. Also thrown in for good measure 3 un-coded devices for experimenting, etc. No data given on these. Whole pack £1.

Ultra Sensitive Relay. Single changeover contacts. 24V at extremely low current as coil value is 5100 ohms. P.C.B. Mounting. Price 65p each.

Synchronous Vibrator. Ref. X331B, 12V. Self-starting 8 pin to fit standard octal holder Ministry equipment, so this is obviously of high quality but are slightly storage soiled. Only 50p each.

3 Gang Tuning Condenser. By Jackson Bros. 50 pf each section. 85p each.

Heating Elements. Three more types to add to our considerable stock.

(1) 230/240V 1 KW straight 5/16" diameter tube nearly 6ft long. This is mineral filled, nickel alloy metal clad and can be moulded to almost any shape you like. Price £1.25 plus 25p post, etc.

(2) This is the old type 1 KW spiral wire in clay refractory, bowed and size approx. 11" long, 3" wide. Standard replacement in many old type radiant heat fires. Price 85p plus 25p post.

(3) 400W wire spirals in clay refractories, held in metal jacket, overall size 18" x 11". Probably a replacement for some old type Jackson cookers. Price 85p plus 22p post.

Washing Machine Thermostat. Sometimes known as a mixer stat. Teddington type TBF. The bellows, as it expands with the heat, operates first one and then another switch to give fine control of water temperature. Current rating 6A-380V. Price 75p each.

Oven Thermostat. With calibrated control knob and "on" indicator lamp. Made by famous Diamond H company. Makers Ref. No. 2TH 43C3-92. This is an expensive stat fitted to some Jackson and other good class cookers. The temperature setting by the calibrated knob ranges from 150° to 550°F. Price £1.75 each.

Message tapes, 250' best quality PVC tape (USA made) on a 3" spool. Packed in small mailing box 30p each. 3 for 75p.

TERMS—Add 10% V.A.T.
Send postage when quoted—other terms, post free if order for these items is £6.00, otherwise add 20p.

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.),
102/103 Tamworth Road,
Croydon CRO 1XX

understanding

DISTORTION

PART 2

A. FOORD

Typical Driver-output Circuits

In Fig. 12 a current source is used to drive the output transistors. A voltage gain can be provided in the output stages, which is an advantage in reducing the swing demanded from the previous stage. Another possible arrangement is shown in Fig. 13. Since this output stage has a unity gain this does give good thermal stability, but demands a high output swing from the previous circuit. Although integrated circuits are available for supplies of $\pm 40V$ (such as the MC1536) their slew rate is inadequate and a completely discrete pre-driver stage is essential.

This circuit can be modified for a small gain

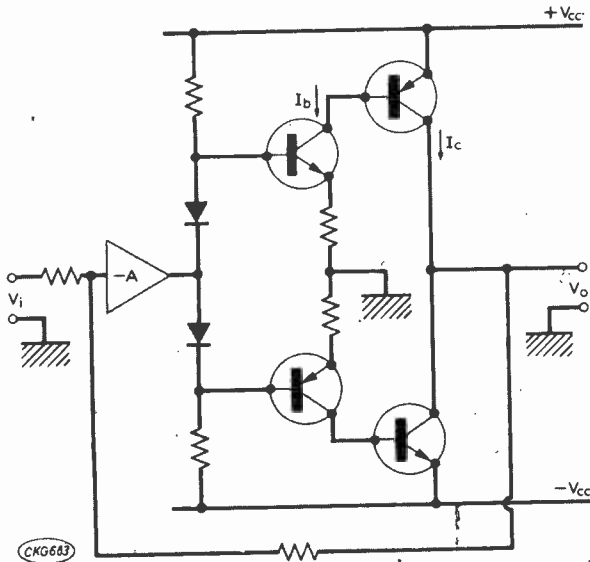


Fig. 12: A fully complementary driver-output circuit, using current drive for the output transistors.

(perhaps 5 times), as in Fig. 14, but the thermal stability is reduced and care must be taken in designing the DC conditions. However this basic configuration is very popular, and several variations are found in practical circuits. It has been shown that if Z_1 is inductive this can increase crossover switching spikes, but if made capacitive may reduce switching spikes. In some designs a capacitor in the order of $0.1\mu F$ may be connected across Z_1 . In addition a capacitor in the order of $1000pF$ may be connected across R_3 to control the frequency response of the output stage.

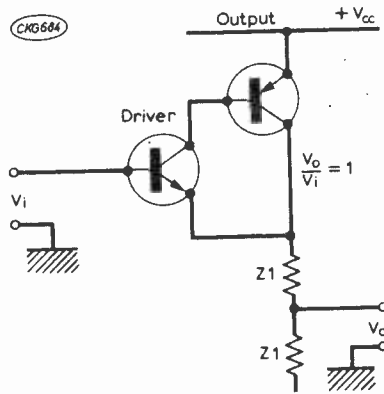


Fig. 13: One half of a unity gain driver-output circuit, using current drive for the output transistor.

Complete Circuit

To illustrate this article the circuit of Fig. 15 was constructed. The required voltage gain is provided by the integrated circuit, supplemented by the output stage, while the current gain is given by the class B output stage. The BC109 small signal transistor allows the potentiometer to set the quiescent current. There is 100% overall negative feedback at DC to maintain the output close to earth potential under no signal conditions, and direct coupling to the load allows a good LF response without using a large coupling capacitor.

For this amplifier graphs of distortion against output power level are shown in Fig. 16. For a 1kHz signal the distortion is below 0.02% for all power levels up to 4 watts, and rises to 0.1% at 30 watts.


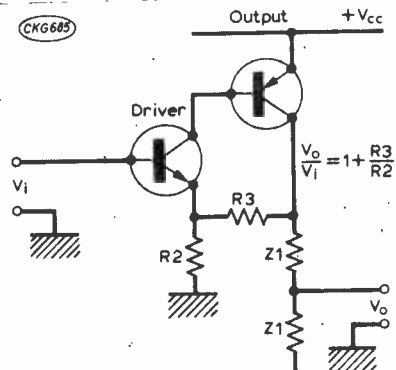



Fig. 14: One half of a driver-output circuit which gives a small voltage gain.

The 741 integrated circuit has a gain of 60dB at 1kHz, falling to 40dB at 10kHz, a factor of 10. This is manifest in the distortion measurements at 10kHz, where the levels are approximately ten times that of the 1kHz measurements. This illustrates the importance of maintaining a high loop gain throughout the audio band.

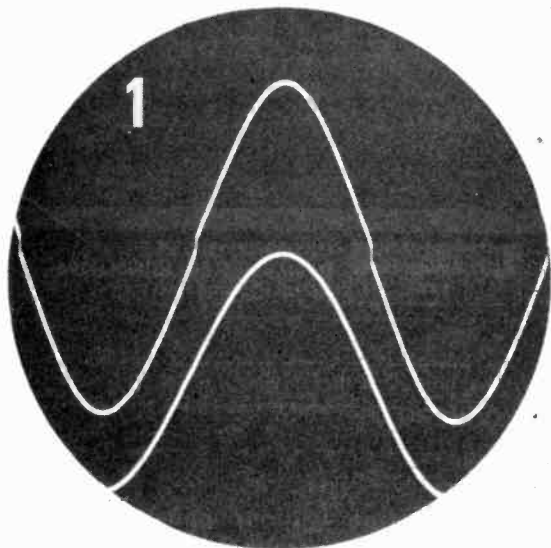
The photographs show the results on the basic amplifier under various circuit conditions.



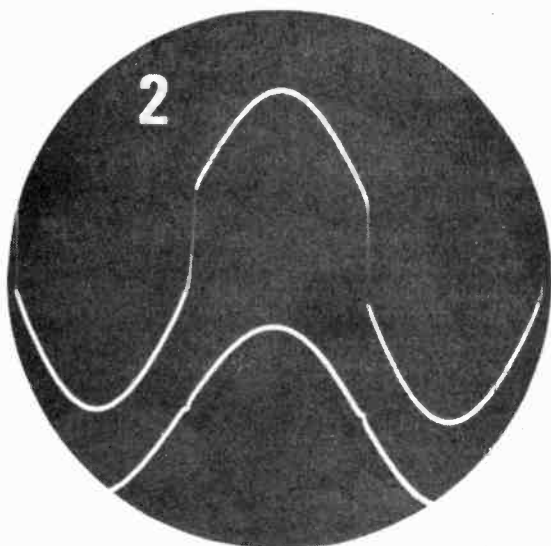
Photograph 1 Here the output power level is 5 watts with no quiescent current in the output transistors. The upper trace shows the output of the integrated circuit (pin 6), while the lower trace shows the power amplifier output. The overall feedback is inadequate to completely reduce the crossover distortion.



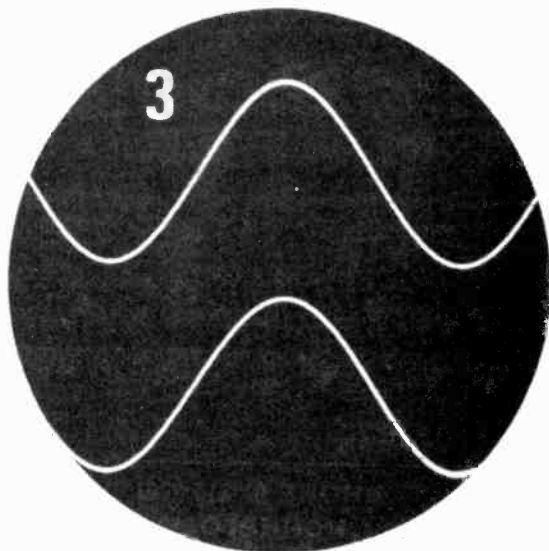Photograph 2 Here the output power level is 100mW, with no quiescent current for the output transistors. This clearly shows the 0.3 volts step at the integrated circuit output as the loop gain attempts to 'force' the output stage through the non-linear region.



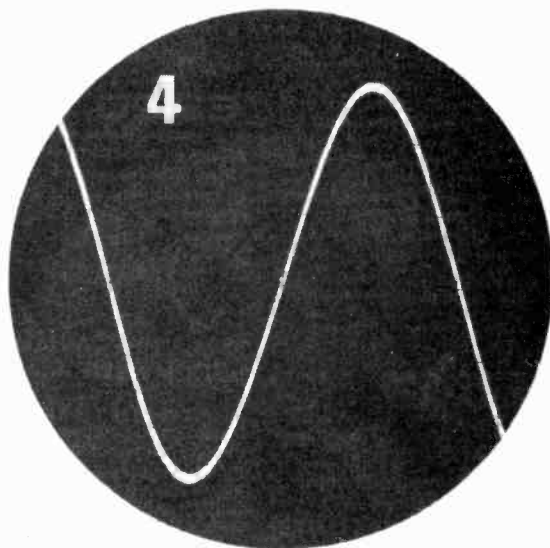Photograph 3 Here the output power level is 100mW, with 20mA quiescent current for the output transistors. Neither the integrated circuit output nor the power amplifier output show any trace of crossover distortion.



Photograph 4 This shows the output of the power amplifier for an output level of 50 μ W. Even at this very low level there is no trace of crossover distortion.

For photographs 1, 2 and 3 the oscilloscope sensitivity for the integrated circuit output (upper trace) was five times that for the power amplifier output (lower trace).

Power Integrated Circuits

Several of the more recently available integrated or hybrid circuits are capable of delivering large currents not normally associated with conventional operational amplifiers. The National Semiconductor LH0021 series, for example, is supplied in an 8 pin TO-3 package rated at 20 watts with a suitable heat

—continued on page 225



Josty~the brains behind electronic success!

Use Josty's experience.

First, the background knowledge you need is in 'Amateur Electronics' – the programmed guide to the science for the beginner and a valuable reference book for the professional.

It's the nearest thing to private tuition in book form and it's only £3.30.

Inside every copy there's a free circuit board suitable for use with ten different circuits.

Among the dozens of Josty Kits—amplifiers, tuners, filters, receivers—you'll find some out-of-the-way items that are just as easy to assemble. Like the AT65 Psychedelic Light Kit, only £16 complete.

Look at the full price list and see just how inexpensive electronic success can be.



JOSTY KIT RETAIL PRICE LIST

Model No.	Description	Total RRP inc. V.A.T.
AF20	Mono Transistor Amplifier	5.28
AF25	Mixer	3.96
AF30	Mono Transistor Pre-Amplifier	2.87
AF35	Emitter Amplifier	2.50
AF80	Small 0.5 W Amplifier for Microphone	4.65
AF305	Intercom	8.28
AF310	Mono Amplifier (for Stereo use two)	6.50
M160	Multivibrator	1.88
M1302	Transistor Tester	9.30
M191	Vu-Meter	5.01
M192	Stereo Balance Meter	5.47
LF380	Quadrophonic Device	12.50
AT60	Psychedelic Light Control, Single Channel	8.58
AT65	Psychedelic Light Control, 3 Channel	16.00
AT25	Window Wiper Robot	6.40
AT30	Photo Cell Switching Unit	6.27
AT50	400w Triac Light Dimmer Speed Control	5.28
AT56	2,200w Triac Light Dimmer Speed Control	7.59
AT5	Automatic Light Control	2.84
GU330	Tremolo Unit for Guitars, etc	8.25
HF61	Diode Detector	3.66
HF75	Frequency Modulated FM Transmitter	2.97
HF75	FM Transistor Receiver	3.16
HF310	FM Tuner Unit	13.39
HF325	De Luxe FM Tuner Unit	26.53
HF330	Stereo Decoder for use with HF310 or HF325	10.95
GP310	Stereo Pre-Amp for use with 2, AF310	23.39
GP312	Basis Circuit Board	12.60
GP304	Basis Circuit Board	5.44
HF380	Aerial Amplifier for LW to VHF	5.54
HF395	Broadband Aerial Amplifier	1.94
NT10	Power Supply 100m/9V Stabilised, 12v Unstabilised	6.76
NT300	Professional Stabilised Power Supply	13.76
NT305	Voltage Converter	4.95
NT315	Power Supply 240V a.c. to 4.5 - 15V d.c. 500mA	10.52
AE1	Output Stage 100mW	1.82
AE2	Pre-amplifier	1.38
AE3	Diode-receiver	2.20
AE4	Fletcher	1.20
AE5	Astable Multivibrator	1.16
AE6	Monostable Multivibrator	1.12
AE7	RC Generator	1.17
AE8	Bassfilter	1.09
AE9	Treblefilter	1.09
AE10	CCIR - filter	1.09


All items available from your local Josty Kit stockist or from mail order addresses below.

FREE

Ask for the free catalogue, 'The Josty Way of Life'.

Mail Order Addresses:
 Audiotronics Wholesale Ltd., Unit 4, The Hyde Industrial Estate, The Hyde, London NW9 6JJ.
 Newmart Electronics, Altham House, Belmont Street, Lansdown Road, Monton, Eccles, Manchester M30 9PA.
 Television, 414 Catcote Road, Hartlepool, Co. Durham.
 Electro Spares, 288 Ecclesall Road, Sheffield S11 8PE.
 Cormatronics, 12 George Street, Hastings, Sussex.
 Chas. H. Young, 170 Corporation Street, Birmingham.
 Channel Islands Distributor: Phoenix Electric Co. Ltd., Paragon Buildings, 6 Duhamel Place, St. Helier, Jersey and North Esplanade, Guernsey.

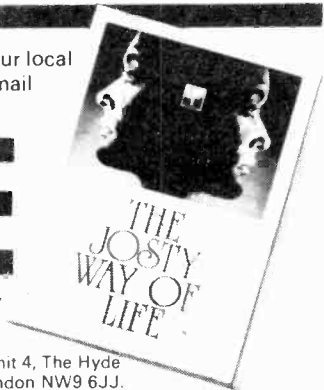JOSTY KIT (UK) LTD (Sole UK distributors)
 P.O. BOX 68, BOROUGH ROAD, MIDDLESBROUGH, CLEVELAND.





GIRO NO. 331 7056
C.W.O. only. P. & P. 10p on orders below £5
Discount: £10-10%, £20-15% (except net items)
Export Order enquiries welcome (VAT free)
Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS (Prices include post & packing)
10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.65 net
10E12 1/4W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.45 net
25E12 1/4W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.35 net
20E12 1/2W KIT: 20 of each E12 value, 22 ohms—2M, a total of 1220 (METAL FILM 5%), £11.05 net
15E12 1/2W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £13.35 net
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £17.15 net

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3½p. 0.068µF, 0.1µF, 0.15µF, 4½p. 0.15µF, 4½p. 0.22µF, 5½p. 0.33µF, 8p. 0.47µF, 9p. 0.68µF, 12p. 1µF, 15p. 1.5µF, 23p. 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2½p. 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3½p. 0.047µF, 0.068µF, 0.1µF, 4½p. 0.15µF, 6½p. 0.22µF, 8½p. 0.33µF, 12p. 0.47µF, 14p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2½p. each. 0.1, 30V, 4½p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p. 6800, 10,000, 4½p.

RESISTORS
CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%.

W. Type Range	1-99	100-499	500-999	1000-	Size mm
1/2 CF 22-1M	1	0.75	0.60	0.55	2.4 x 7.5
1/4 CF 22-2M2	1	0.75	0.60	0.55	3.9 x 10.5
1/2 CF 22-1M	1	0.75	0.60	0.55	5.5 x 16
1/4 MF 10-2M7	2	1.54	1.32	1.1	3x7
1/2 MF 10-2M2	2	1.43	1.21	0.99	4.2 x 10.8
1/4 MF 10-10M	3	1.98	1.81	1.65	6.6 x 13
2 MF 10-10M	4.5	3.52	3.08	2.75	8x17.5

For value mixing prices, please refer to our catalogue. (Price in pence each)
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN: 0.05W Vertical, 100 Ω to 220K Ω 5p each

B. H. COMPONENT FACTORS LTD. (P.W.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ
Tel.: Cheddington 668446 (Std. Code 0296)
PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electrolytics

1.0µF 63V 6½p	68µF 16V 6½p
1.5µF 63V 6½p	68µF 63V 12p
2.2µF 63V 6½p	100µF 10V 6½p
3.3µF 63V 6½p	100µF 63V 12p
4.0µF 40V 6½p	100µF 63V 14p
4.7µF 63V 6½p	150µF 16V 6½p
6.8µF 63V 6½p	150µF 63V 15p
8.0µF 40V 6½p	220µF 6.4V 6½p
10µF 16V 6½p	220µF 10V 6½p
10µF 25V 6½p	220µF 16V 8p
10µF 63V 6½p	220µF 63V 21p
15µF 16V 6½p	330µF 16V 12p
15µF 63V 6½p	330µF 63V 25p
16µF 40V 6½p	470µF 6.4V 9p
22µF 25V 6½p	470µF 40V 20p
22µF 63V 6½p	680µF 16V 15p
32µF 10V 6½p	680µF 40V 25p
33µF 16V 6½p	1000µF 16V 20p
33µF 40V 6½p	1000µF 25V 25p
32µF 63V 6½p	1500µF 6.4V 15p
47µF 10V 6½p	1500µF 16V 25p
47µF 25V 6½p	2200µF 10V 25p
47µF 63V 8p	3300µF 6.4V 26p

VEROBOARD 0.1 0.15

2½ x 3½"	28p 28p
3½ x 3½"	26p 19p
3½ x 5"	32p 33p
3½ x 3½"	28p 28p
2½ x 1 1/8"	7p 7p
2½ x 5" (Plain)	— 14p
2½ x 3½" (Plain)	— 12p
5 x 3½" (Plain)	— 22p
Insertion tool	59p 59p
Track Cutter	44p 44p
Pins, Pkt. 25	10p 10p

TRANSISTORS

AC127 16½p	BC212L 12p
AC128 22p	BC213L 12p
BC107 11p	BC214L 17p
BC108 12p	OC44 18p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	T154J 33p
BC183L 12p	2N2926 11p
BC184L 13p	2N3702 11p

POTENTIOMETERS
Carbon Track 5K Ω to 2M Ω, log or lin. Single, 16½p Dual Gang 46p. Log Single with switch 26p
Slider Pots: 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001 6½p	IN4002 7½p
IN4003 9p	IN4004 9½p
IN4005 12p	IN4006 14p
IN914 7p	IN916 7p
BA100 10p	OA5 42p
OA47 9p	OA81 11p
OA200 8p	

Integrated Circuits

µA709C 50p	µA741C 55p
µA723C 51p	ZN414 £1.32

ELECTROLYTIC CAPACITORS. Tubular & Large Cans
(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 50/100, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 90p, 2000/25, 30p, 2000/100, 95p, 2500/25, 38p, 2500/50, 62p, 3000/50, 80p, 5000/25, 66p, 5000/50, £1.10.

HI-VOLT: 4/450, 14p, 8/350, 19p, 8/450, 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/500, 88p.

METALLISED PAPER CAPACITORS
250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7½p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7½p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 28p.

NEW KIT
SE12W Metal Film 5%, Ultra Low Noise New Resistors with full colour coding, 5 each E12 value 10ohm/1M total 305 £2.75 Net.

AMBIT '74 cat.20p or free with orders over £6.50

37A HIGH STREET BRENTWOOD ESSEX CM14 4RH (216029)
New prices - *100+ applies to mixes of multiples of 10 per item.

TYPE NUMBER	1-19	20-99	100-999	MIX *100+
AUDIO				
LM380 (2-3w amp)	1.00	0.90	0.75	0.80
LM381 (dual pre)	1.85	1.63	1.33	1.45
TBA810S (7w amp)	1.50	1.17	0.90	1.08
RADIO				
CA3039E (FM IF)	1.95	1.55	1.31	1.42
CA3053 (IF AMP)	0.52	0.38	0.31	0.37
TBA120 (FM IF)	1.00	0.85	0.52	0.55
TDA651 (AM/FM/SSB)	1.80	1.46	1.13	1.25
CA3123E (AM)	1.40	1.13	0.94	1.14
uA753 (FM gain)	0.99	0.78	0.65	0.77
STEREO				
MCT310 (PLL DEC.)	2.85	2.30	1.80	2.04
CA3090Q (PLL DEC.)	3.75	3.25	2.55	2.85
PLL				
NE561B	3.19	2.75	2.07	2.24
NE562B	3.19	2.75	2.07	2.24
NE565/LM505	2.75	1.80	1.50	1.85
NE567/LM567	2.75	1.80	1.50	1.85
Regulators				
LM309K	2.20	1.80	1.50	1.80
uA7805	1.75	1.32	1.07	1.30
uA7812	1.75	1.32	1.07	1.30

Regulators (contd.)	1-19	20-99	100-999	* 100+
uA723C	0.80	0.66	0.52	0.66
NE550A	0.80	0.66	0.42	0.66
OP AMPS				
741CV	0.40	0.34	0.32	0.35
LM3900 (Quad amp)	0.66	0.53	0.45	0.53
(710 Comp.)	0.52	0.40	0.34	0.40
OTHERS				
ICL8038CC (funct.gen)	3.10	2.85	2.18	2.47
NE555V	0.78	0.66	0.52	0.66
LM1496	1.02	0.67	0.55	0.66

see our new '74 A4 size catalogue for details of our range of devices and products.

TOKO inc. (mix price applies to TOKO items only here)

CFS10.7	0.45	0.38	0.26	0.34
CFT455B & C	0.45	0.38	0.25	0.36
CFU455	0.50	0.43	0.32	0.39
MFH41T or 71T	1.40	1.24	1.02	1.15
KACS586 (FM quad.det)	0.30	0.22	0.14	0.20
BLR2011N (198.38kHz)	1.95	1.67	1.23	1.45
5.1mH & 43mH min.chokes	27	0.21	0.15	0.20
2mH choke for CA3090Q	.30	0.22	0.14	0.20
ET703UA FM tunerhead with AM gang.				
	3.50	3.00	2.35	2.45
LP1186(FM tunerhead)	3.75	3.05	2.35	3.05
LP1185 (FM IF)	3.90	3.17	2.45	3.09

Trade and professional enquiries welcomed.

TERMS: PRICES EXCLUDE VAT. PLEASE INCLUDE 10% VAT WITH ALL ORDERS.
CWO please. Credit accounts by prior arrangement only, payable monthly nett.
POSTAGE: Order value less than £1 : 18p
£5 : 15p

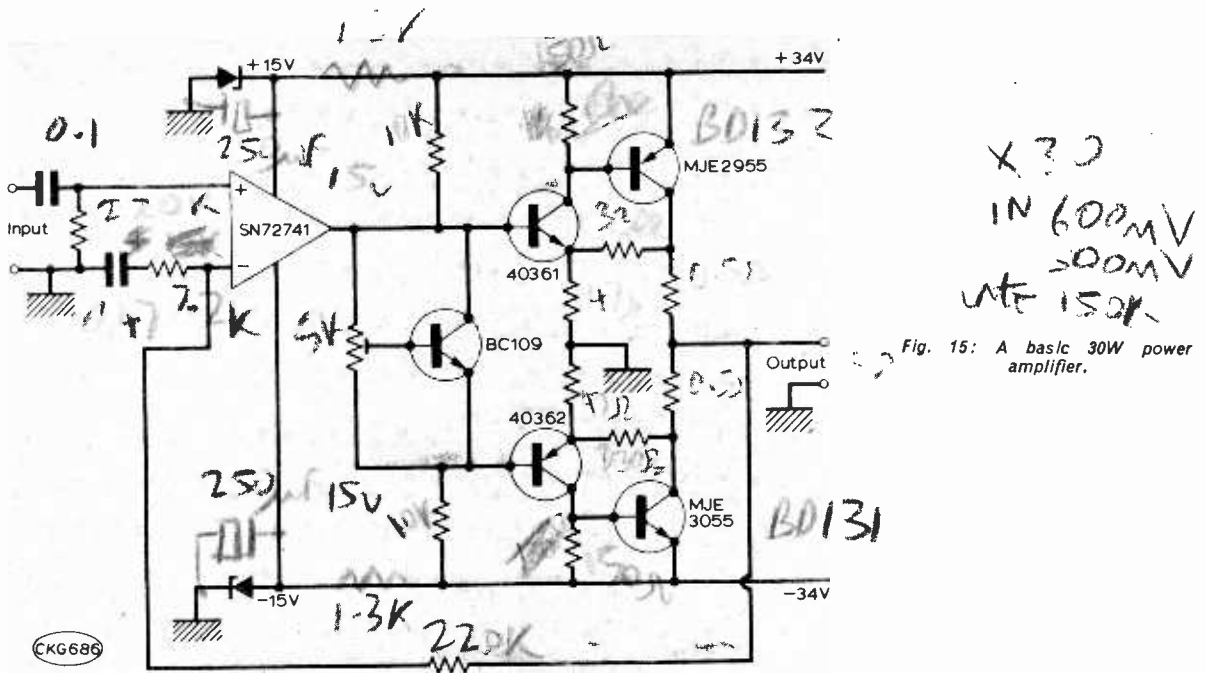


Fig. 15: A basic 30W power amplifier.

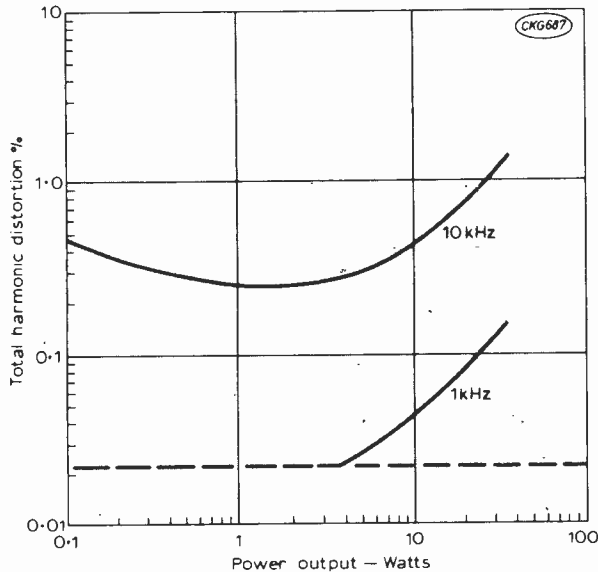


Fig. 16: Total harmonic distortion measurements for the amplifier of Fig. 15.

—continued from page 222

sink. This operational amplifier is suitable for DC servomechanisms, programmable power supplies, etc. Fig. 17 shows a 35 watts audio amplifier using two in a push-pull configuration. Similarly the RCA-HC2000 power hybrid operational amplifier can deliver 100 watts into a 4 ohm load, as shown in Fig. 18.

Conclusions

The reduction in β , the 0.6V V_{be} for each output transistor, and the other effects discussed here can cause an increase in distortion at low and high signal levels. However the problems associated with distortion in power amplifiers can be solved, at a price. Certainly the best amplifiers are limited in perform-

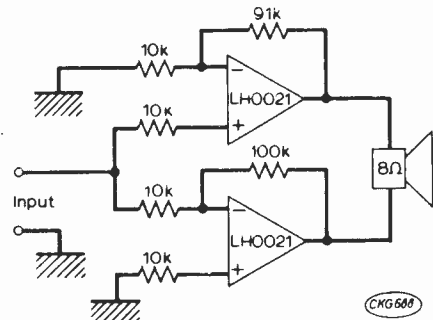


Fig. 17: A 35W power amplifier using a push-pull output stage.

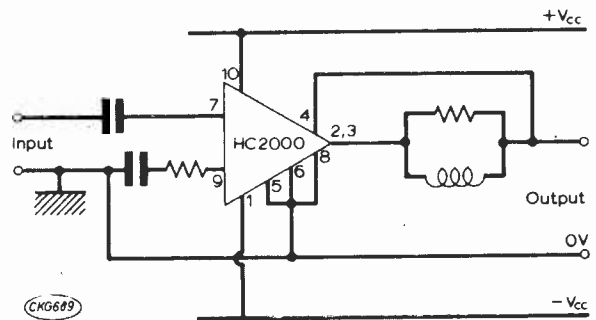


Fig. 18: A 100W hybrid power amplifier.

ance by the remainder of the Hi-Fi system, the loudspeaker, microphone, tape recorder, pickup, etc., and the necessity for further distortion reduction in power amplifiers may be challenged. However there is a good case for increased power output in power amplifiers, since loudspeaker efficiency decreases with fidelity, and high power may be demanded to drive the very best loudspeakers on transients. Efficiency may be typically 0.5%. At such power levels speaker and amplifier unit protection is essential, but that is another problem. ■

Dear Sir,



Test Gear

I congratulate you on your decision to start a series of constructional projects on test equipment. It's a pleasant change from the unending series of amplifiers of astronomical output and ever-increasing perfection that so many amateur constructional magazines publish.

Personally, I started taking "P.W." regularly in the hope that something which could be adapted for use in instruments would come up, so your series is very timely. In particular, a simple wobulator to cover 465kHz and 10.7MHz for lining up I.F.s on a scope, a transistor voltmeter of enormous input impedance, a

gadget for tracing valve/transistor characteristics on a 'scope (which according to Mr. Scroggie can be done, but which may be too complicated) and a transistorised beam-splitting switch (as currently advertised by Chiltmead) are what I'd like.

I do, of course, totally disagree with your remarks about test equipment being uninteresting and wish you good luck in this new line.—**R. G. Roberts (Herts)**

Weaned on transistors?

It was with great interest that I read your "Going Back" article about the History of *Practical Wireless*. Might it be possible, however, to reprint some of your articles from these earlier issues to show these transistor weaned people what proper electronics is all about?!

I have written before on this subject, and there seemed to be some success for several months but then the valve disappeared again. As one of the multitude who delight in the thermionic glow, I would like to hear what other readers think on the subject!—**T. G. Watton (Kingston upon Hull)**

Surplus Gear

In your "C Q" feature, there are numerous queries for information on Government Surplus Equipment. I feel it would be of assistance to the interested parties, to obtain the book on the subject, called "Govt. Surplus Wireless Equipment Handbook."

I have no connection with the publisher, but have recently purchased one from Gerald Myers, 18 Shaftesbury St., Leeds LS12 3BT.—**K. F. Tunnicliffe (Leics)**

WIRELESS TELEGRAPHY ACT

Readers and advertisers are reminded of the requirements laid down by the Wireless Telegraphy Act. It is an offence in the U.K. to install or operate wireless telegraphy apparatus except under the provisions of the Act and, except in the case of broadcast sound-only receivers, a licence must be obtained.

Included within the provisions of the Act are any apparatus transmitting deliberate signals for any purpose such as "walkie-talkies", radio-controlled models or servos and some types of metal detectors. Apparatus radiating interference signals are subject to controls which also come under the administration of the same Ministry. If you require full information, please write to *Waterloo, Bridge House, Waterloo Road, SE1 8UA*.

TELEVISION

IN THE JULY ISSUE

TELEVISION GAMES

Most people will have seen the TV games machines installed in pubs and amusement centres and we have received many requests for information on how to adapt TV sets to operate in this way. A unit is required which will generate a video signal corresponding to the basic features of the game and the movement—under control of the players—of the ball. This month we start a series of articles which will present the basic information required. This will lead up to a football game in monochrome or colour with players which can be moved at controlled speed across the "pitch".

AFC MUTING

When channel changing it is necessary to mute the a.f.c. applied to the tuner unit. This is generally

done by specially designed switch units which remove the a.f.c. for the required time. A simple Yaxley switch can be used if a slow-start power supply to the a.f.c. circuit is used. Details of the simple circuitry which makes this possible will be given.

FAULT-FINDING/RENOVATING

The GEC 13in. portable Model 2015 dating from 1966 gives excellent results and is worth while renovating for use as a second set. John Law describes the set and the parts of the circuit that may require attention to bring the performance up to scratch.

PLUS ALL THE REGULAR FEATURES

Details of the July issue are subject to the current national situation at time of going to press.

TO **MR. H. R. HUMPERNICKLE**
(Name of Newsagent)

Please reserve/deliver the JULY issue of TELEVISION (25p) and continue every month until further notice.

F. BLOGGS
NAME
ADDRESS **10 BELGRAVE SQUARE**
LONDON

ELECTROVALUE

Present

THIS MONTH'S SELECTION OF GUARANTEED-TO-SPECIFICATION COMPONENTS

Everything Brand New ★ Attractive Discounts ★ Free Postage (U.K.)

TRANSISTORS

and semi-conductors of many types from simple diodes to ICS photo-sensitive devices, threshold switches, etc. etc.

MINITRON DIGITAL INDICATORS

3015F Seven segment filament, compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL (some alphabetical symbols available) £1-20
Suitable BCD decoder driver 7447 £1-15
3015G showing + or - & 1 & dec. pt. £1-20

CAPACITORS

DALY ELECTROLYTIC

in cans, plastic sleeved
1000mF/25V 28p 1000/50 41p
5000/100 £2 91 2000/50 57p
5000/25V 62p 5000/50 £1-18
2200/100 £1-56

POLYESTER TYPE C.280

Radial leads for P.C.B. mounting. Working voltage 250V d.c.

0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p
0-068, 0-1, 0-15 ea. 4p

0-22, 5p, 0-33 7p, 0-47 8p, 0-68 11p, 1-0 14p, 1-5 21p, 2-2 24p

SILVERED NICA

Working voltage 500V d.c.
Values in pFs—2 to 820 in 32 stages ea. 6p
1000, 1500 7p; 1800 8p; 2200 10p; 2700, 3600 12p;
4700, 5000 15p; 6800 20p; 8200, 10,000 25p

TANTALUM BEAD

0-1, 0-22, 0-47, 1-0 mF/35V ea. 13p
2-2/16V, 2-2/35V, 4-7/16V, 10/6-3V ea. 13p
4-7/35V, 10/16V, 22/6-3V ea. 16p
10/25V, 22/16V, 47/6-3V 100/3V ea. 18p

POLYCARBONATE

Type B42540 Working Voltage—250V
Values in mF: 0-0047, 0-0068, 0-0082, 0-01, 0-012, 0-015 ea. 3p
0-018, 0-022, 0-027, 0-033, 0-039, 0-047, 0-056 ea. 4p
0-068, 0-082, 0-1 ea. 4p

CERAMIC PLATE

Working voltage 50V d.c.
in 26 values from 22pF to 6800pF, each, 2p

POTENTIOMETERS

ROTARY CARBON TRACK. Double wipers for good contact and long working life

P.20 SINGLE linear 100ohms to 4-7megohms, ea. 14p
P.20 SINGLE log. 4-7Kohms to 2-2megohms, ea. 14p

JP.20 DUAL GANG lin. 4-7Kohms to 2-2megohms, ea. 48p
JP.20 DUAL GANG log. 4-7Kohms to 2-2megohms, ea. 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only ea. 48p

2A DP mains switch for any of above 14p extra.
Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets Type PR, horizontal or vertical 6p each.

SLIDER

Linear or log. 4-7K to 1 meg. in all popular values ea. 30p
Escutcheon plates, black, white or light grey, ea. 3p
Control knobs, blk/wh/red/yel/grn/blue/dk. grey/lt. grey ea. 7p

JACKS AND PLUGS

Sockets
2-circuit unswitched S1/SS 12p
2-circuit /2 break contacts S1/BB 15p
3-circuit unswitched (Not GPO) S3/SSS 17p
3-circuit with 3 break contacts S3/BBB 20p
2 circuit with chrome nut and black/white/red/green or grey unswitched S5/SS 16p
with 2 break contacts S5/BB 20p
Miniature 3.5mm 2-circuit, (black) 2 br. cont S6/BB 9p

Plugs

2 circuit screened top entry P1 24p
side entry SEP3 46p
Line socket mono 231 40p
Line socket stereo 244 45p
3 circuit unswitched, blk/grey/wh. P4 36p
2 circuit, unswitched, blk/wh/red/bl/grn/gr P2 18p
3 circuit screen top entry P3 53p
side entry SEP3 53p
Miniature 3-5mm 2-circuit screened P5 13p
Min. 3-5mm 2-circ. unscrnd. various colours P6 10p

EV CATALOGUE 2nd printing

112 pages, thousands of items; illustrations; diagrams; much useful technical information. The 2nd printing of this catalogue has been updated as much as possible on prices. It costs only 25p post free and includes a refund voucher for 25p for spending when ordering goods list value £5 or more.

INSULATED SCREW TERMINALS

In moulded polypropylene, with nickel plate on brass. With insulating set, washers, tag & nuts. 15A/250V in blk/brown/red/yel/grn/bl/gry/wh. Type TP.1, ea. 14p
Suitable plugs Type TP4, 4mm each 7p
Type TP2, 2mm each 4p

ZENER DIODES

Full range E24 values: 200mW: 2-7V to 33V, 14p each; 1W: 6-8V to 82V, 21p each; 1-5W: 4-7V to 75V, 48p each, 20W: 7-5V to 75V, 69p each. Clip to increase 1-5W rating to 3 watts (type 268F), 5p.

RESISTORS

Code Watts Ohms 1 to 9 10 to 99 100 up
(see note below)
C 1/3 4-7-470K 1-3 1-1 0-9 nett
C 1/2 4-7-10M 1-3 1-1 0-9 nett
C 3/4 4-7-10M 1-5 1-2 0-9 nett
C 1 4-7-10M 3-2 2-5 1-9 nett
MO 1/2 10-1M 4 3-3 2-3 nett
WW 1 0-22-3-9 9 8 8
WW 3 1-10K 7 7 6
WW 7 1-10K 9 9 8

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide, Electrofil TR5, ultra low noise.
WW = wire wound, Plessey.

Values: All E12 except C 1W, C 1W, and MO 1W, E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% ±0-05Ω under 10Ω and MO 1W 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

VEROBOARD

Copper clad 0-1 matrix—2-5 x 3-75 ins. 27p; 3-75 x 3-75 ins.—30p; 2-5 x 5 ins.—30p; 3-75 x 5 ins.—20p; 3-75 x 3-75 ins.—30p; 2-5 x 5 ins.—30p; 3-75 x 5 ins.—36p.
Vero spot face cutter (any matrix) 48p.
0-040 pins (for 0-1 matrix) per 100—36p.
0-052 pins (for 0-15 matrix) per 100—36p.

ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily: Sat 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

ELECTROLYTICS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
µF	3V	6-3V	10V	16V	25V	40V	63V	100V
0-47	—	—	—	—	—	11p	11p	8p
1-0	—	—	—	—	—	—	—	8p
2-2	—	—	—	—	11p	—	—	8p
4-7	—	—	—	—	—	8p	8p	8p
10	—	—	—	—	—	8p	8p	8p
22	—	—	8p	—	—	8p	8p	10p
47	8p	—	9p	8p	9p	8p	10p	13p
100	9p	8p	8p	8p	9p	10p	12p	19p
220	8p	8p	9p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	41p	—	—
4,700	25p	30p	39p	4p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

KNOBBS

In a great variety of modern types, for 1/4" shaft, from plastic to solid aluminium including pointer and numbered types.

CONNECTORS

DIN from two way to 7 way plugs and sockets, phono types mains connections, etc. etc. Page 88 in Catalogue 7

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14 90.
The size and weight of this product obliges us to charge 70p part cost of carr. in U.K.
Equaliser Assembly, £2-30.
Loudspeaker Unit 59RM109, £2-45.
Cabinet Kit (to Baxandall design), £10 45.
Cross-over choke for additional woofer not included in kit £1-30

This is EV Service

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14-99. 15% on orders £15 and over.

PACKING AND POSTAGE FREE

In U.K. For pre-paid mail orders, except Baxandall. For orders list value £2 and under there is an additional handling charge of 10p.

GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale.

GIRO ACCOUNT No. 38/671/4002

Prices quoted do not include V.A.T., for which 10% must be added to total nett value of order. Every effort is made to ensure correctness of information and prices at time of going to press. Prices subject to alteration without notice.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PW7. S.A.E. with enquiries requiring answers.

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Pri. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref.	VA	Weight	Size cm.	P & P
No.	(Watts)	lb oz		£ p
07	20	1	7.0 x 6.0 x 6.0	2.55 30
149	60	3	9.9 x 7.7 x 8.6	3.79 36
150	100	5	8.9 x 8.9 x 8.6	4.17 52
151	200	8	0 12.1 x 9.3 x 10.2	7.09 52
152	250	13	12.1 x 11.8 x 10.2	9.25 67
153	350	15	0 14.0 x 10.8 x 11.8	12.32 82
154	500	19	8 14.0 x 13.4 x 11.8	17.87
155	750	29	0 17.2 x 14.0 x 14.0	24.31
156	1000	38	0 17.2 x 16.6 x 14.0	29.87
158	2000	60	0 21.6 x 15.3 x 18.1	49.25

PLEASE NOTE
 NEW ADDRESS
 AS BELOW

AUTO TRANSFORMERS

Ref.	VA	Weight	Size cm.	Auto Taps	P & P
No.	(Watts)	lb oz			£ p
113	20	1	0 5.8 x 5.1 x 4.5	0-115-210-240	1.34 22
64	75	2	4 7.4 x 6.7 x 6.1	0-115-210-240	2.64 30
4	150	3	4 8.9 x 7.7 x 7.7	0-115-200-220-240	3.18 36
46	300	6	4 9.9 x 9.6 x 8.6	"	6.19 52
67	500	12	8 12.1 x 11.2 x 10.2	"	9.20 67
84	1000	19	8 14.0 x 13.4 x 14.3	"	16.71 82
93	1500	30	4 14.0 x 15.9 x 14.3	"	24.19
95	2000	32	0 17.2 x 16.6 x 14.0	"	31.57
73	3000	40	0 21.6 x 15.3 x 18.1	"	39.17

ENCLOSED AUTO TRANSFORMERS
 115V 500W enclosed transformer, with mains lead and two 115V outlet sockets. £9.49, P & P 67p. 20 Watt version £2.02 P & P 27p.

PRIMARY 240 250 VOLTS 12 AND OR 24 VOLT RANGE

Ref.	12V 24V	Weight	Size cm.	Secondary Windings	P & P
No.	Amps	lb oz			£ p
111	0.5	0.25	3 4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.34 22
213	1.0	0.5	4 6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.58 22
71	2	1	1 12.7 x 6.4 x 6.1	0-12V at 1A x 2	2.09 22
18	4	2	2 12.8 x 7.7 x 7.0	0-12V at 2A x 2	2.95 30
70	6	3	3 8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.52 42
108	8	4	4 9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.96 52
72	10	5	6 4 9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.67 52
116	12	6	6 12.9 x 10.2 x 8.6	0-12V at 5A x 2	5.61 52
17	16	8	8 12.1 x 9.9 x 10.2	0-12V at 8A x 2	7.22 52
115	20	10	11 8 14.0 x 9.6 x 11.8	0-12V at 10A x 2	9.20 67
187	30	15	15 8 14.0 x 12.1 x 11.8	0-12V at 15A x 2	16.94 82
226	60	30	32 0 17.2 x 15.3 x 14.0	0-12V at 30A x 2	31.28

30 VOLT RANGE

Ref.	Amps.	Weight	Size cm.	Secondary Taps	P & P
No.		lb oz			£ p
112	0.5	1	4 6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.56 22
79	1.0	2	4 7.0 x 6.7 x 6.1	"	2.11 36
3	2.0	3	4 8.9 x 7.7 x 7.7	"	3.18 36
20	3.0	4	8 9.9 x 8.3 x 8.6	"	3.96 42
21	4.0	6	4 9.9 x 8.6 x 8.6	"	4.67 52
51	5.0	6	12 12.1 x 8.6 x 10.2	"	5.87 52
117	6.0	8	0 12.1 x 9.3 x 10.2	"	6.94 52
88	8.0	12	0 12.1 x 11.8 x 10.2	"	9.00 67
89	10.0	13	12 14.0 x 10.2 x 11.8	"	11.36 67

50 VOLT RANGE

Ref.	Amps.	Weight	Size cm.	Secondary Taps	P & P
No.		lb oz			£ p
102	0.5	1	12 7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.09 30
103	1.0	2	12 8.3 x 7.4 x 7.0	"	3.08 36
104	2.0	5	8 9.9 x 8.9 x 8.6	"	4.26 42
105	3.0	6	12 9.9 x 10.2 x 8.6	"	5.79 52
106	4.0	10	0 12.1 x 10.5 x 10.2	"	7.69 52
107	6.0	12	0 14.0 x 10.2 x 11.8	"	11.38 67
118	8.0	18	0 14.0 x 12.7 x 11.8	"	12.40 97
119	10.0	25	0 17.2 x 12.7 x 14.0	"	18.62

60 VOLT RANGE

Ref.	Amps.	Weight	Size cm.	Secondary Taps	P & P
No.		lb oz			£ p
124	0.5	2	4 7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.12 36
126	1.0	3	4 8.9 x 7.7 x 7.7	"	2.97 36
127	2.0	6	4 9.9 x 9.6 x 8.6	"	4.67 42
125	3.0	8	12 11.8 x 9.9 x 10.2	"	7.11 52
123	4.0	13	12 12.1 x 11.8 x 10.2	"	9.20 67
40	5.0	12	0 14.0 x 10.2 x 11.8	"	10.83 87
120	6.0	15	8 14.0 x 12.1 x 11.8	"	13.35 82
121	8.0	25	0 14.0 x 14.7 x 11.8	"	15.01
122	10.0	25	0 17.2 x 12.7 x 14.0	"	22.10
189	12.0	29	0 17.2 x 14.0 x 14.0	"	24.74

MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref.	MA	Weight	Size cm.	VOLTS	P & P
No.		lb oz			£ p
238	200	2	2 8x2.6x2.0	3-0-3	1.44 10
212	1A 1A	1	4 6 1x5.8x4.8	0-6-0-6	1.67 22
13	100	1	4 3.9x2.6x2.9	9-0-9	1.23 10
235	330,330	4	4 8x2.9x3.5	0-9, 0-9	1.67 10
207	500, 500	1	0 6 1x5.4x4.8	0-8-9, 0-8-9	2.23 22
208	1A, 1A	1	12 7.0x6.4x6.1	0-8-9, 0-8-9	3.00 30
216	200, 200	1	4 4.8x2.9x3.5	0-15, 0-15	1.67 10
214	300, 300	1	4 6 1x5.8x4.8	0-20, 0-20	1.76 22
221	700 (D.C.)	1	8 7.0x6.1x6.1	20-12-0-12-20	1.55 30
206	1A, 1A	2	12 8.3x7.7x7.0	0-15-20, 0-15-20	4.05 36
203	500, 500	2	4 8.3x7.0x7.0	0-15-27, 0-15-27	3.10 38
204	1A, 1A	3	4 8.9x7.7x7.7	0-15-27, 0-15-27	3.15 38

PLEASE ADD 10% FOR V.A.T.
 INCLUDING P. & P.

BARRIE electronics
 3, THE MINORIES, LONDON EC3N 1BJ
 TELEPHONE: 01-488 3316/8
 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

MOVING COIL INSERTS will work as mic or earpiece 50 ohm new 65p. **YAXLEY SWT 3p**, 6w 3b with knob 45p. **PHOTO CELLS** selenium type 1½" dia will work 500Ua meter direct okay for exp meters 55p. **UNISELECTORS** 50v coil 25w 4b £2.50. **VIDICON CAMERA TUBES** E.E. type P862 standard 1" type with data grade A £9.50. grade B £6.60. **VALVES** 829B £2.40 with base. **NEONS** wire ended type req 470K res for 240v 10 for 65p. **METER** 500Ua 1½" dia scale 0 to 5 £1.45. **DIODES** 800 PIV 750Ma new 15 for £1.10. **DIODES** 200 PIV 8 amp 4 for 75p. CRT type VCR138A with base & shield 3.5" green med screen okay for scope use with data £4.50. **INSULATED TERMINALS** in blk, blue, red, yell, green, grey, brwn, wht, new 4 for 60p. **COAX CABLE** 75 ohm grey 15 meters for £1.20 new. **NOISE DIODES** heater 6.3v two on panel with bases 55p. **RELAYS** 12v 2pc/o small 44p. **H/PHONE** Lead 5ft with high to low res matching trans standard plug new 70p. **LAMP PANEL** Ass with red, green & wht ind 24v Lps 44p. **DUAL GANG** 10K pot 2½" dia W.W. type with knob £1.35. **TRANSFORMERS** 230v Pri Sec 1125-0-1125v at 565Ma new £8.80 matching choke £1.50 also 415-0-415v at 360 Ma new £3.50.

The above goods ex equipment unless stated otherwise prices inc. VAT & postage.

List No. 10 now available.

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL 444278 (0742)

BAKER 12" MAJOR £11.55
 30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. **BASS RESONANCE** 40 cps 20 watt RMS.

MAJOR MODULE KIT £14.85
 30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 9in x 12½in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W £10.45	Superb 12 in. 20W £18.70	New Group 50/12
Major 12 in. 20W £11.55	Group 25 12 in. 25W £10.45	12 in. 50W £17.60
Deluxe 12 in. 15W £13.20	Group 35 12 in. 35W £11.55	

BAKER LOUDSPEAKER CO., BENSAM MANOR PASSAGE
 THORNTON HEATH, SURREY Tel. 01-684 1665
 ALL PRICES INCLUDE V.A.T. HI-FI ENCLOSURE PLANS 42p

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Switches, Potentiometers, Knobs, IF's, Tag Strips, Drive Drums, Transistor Panels etc., etc. Save yourself £s on these well selected parcels 6lbs net weight £1.00, p.p. 40p.

Brand new Wire-wound Resistors. Good Selection. 100 for £1.00, p.p. 15p.

Flexible Connecting Wire, assorted colours. 100 yards for £1.00.

Eddystone Die-Cast Boxes with Lid 4½" x 2½" x 1½" 50p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection. 300 for £1.00, p.p. 20p.

Mullard Ferrite Cores. LA3 100 to 500kHz 50p. LA4 10 to 30kHz 35p. LA2100 3 to 200kHz 50p.

Rotary Switch 1 pole, 14 way, 3 bank, good quality, excellent value 35p.

Colvern W/Wound Potentiometer Spindle Type 10 ohms 35p.

Please include 10% VAT to total cost of goods.

MAIL ORDER ONLY

XEROZA RADIO
 1, EAST STREET, BISHOPS TAWTON, DEVON

EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

LEARNING BY PRACTICAL PROJECT STEPS

PART 9—POTENTIAL DIVIDER BIASING & GROUNDED BASE AMPLIFIERS

(continued from the June issue)

We now move away to a different type of amplifier stage; the *grounded base stage*. The basic circuit is shown in Fig. 65. In many respects it looks similar to that we have just described but it has considerable differences. Signal input is at point A (at the emitter) for a start. This circuit has very low input impedance and quite a high output impedance; it provides us with a very useful voltage amplification but no current gain. It is used when we have a signal source that has low resistance and very low output voltage (e.g. low impedance microphones or some guitar pick-ups). Unlike the grounded emitter stage there is no change of phase between input and output.

The resistors R3 and R4 provide a fixed bias so you can assume that the transistor is conducting on a linear portion of its characteristic and there will be a collector current flowing (ideally just sufficient to give us a mid rail output at the collector).

This collector current merges with base current within the transistor and emerges as emitter current. Most of the emitter current is made up of the original collector current. If we change the emitter current (by the application of an external signal at point A) we will—indirectly—alter the collector current. Because R2 is of small value it does not need much in the way of voltage at A to create reasonable changes in current flowing through R2 (but, of course, the source of current must also have a low resistance). These changes in emitter current are converted, by the transistor, to similar changes in collector current flowing through R1 but as R1 has a high resistive value we will get much larger voltage changes across it than we applied to R2—hence voltage amplification. This is a very over-simplified explanation but we hope it conveys the operating method of the circuit without having to resort to complicated mathematics.

We can arrive at component values by using a similar technique to that adopted for the grounded emitter stage. The main difference is that we want to keep the quiescent potential at A as low as possible—so that the voltages that generate our input

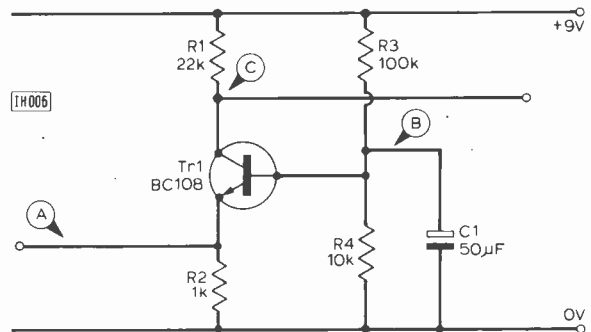


Fig. 65: Basic circuit of a grounded base stage.

current are significant. In this case we have based our component calculations on the assumption that the potential at A is to be approximately 200mV. This means that the potential at B will be +800mV. It is essential that the base current we supply to the transistor is highly stable and as the bias chain is not going to create input impedance problems in this case we can arrange for a much higher standing current to flow through R3 and R4. To prevent the base potential being affected by signals we swamp any changes there might be with the large capacitor C1. Make up the circuit for Fig. 65 and measure the respective potentials and then go on to experiment with the working circuit of Fig. 66. The input signal should come from a very low impedance source but at the same time should be decoupled from the emitter of the grounded base stage as far as d.c. is concerned (C1) otherwise we would alter our quiescent working point. We suggest an old miniature loudspeaker (any impedance from 3 to 35 ohms will do) as a microphone but you could use an ex Post Office telephone earpiece as a rough and ready microphone. Alternatively you could make up a crude form of guitar pick-up by winding about 100 turns of fine enamelled copper wire on an Eclipse button magnet. As soon as a

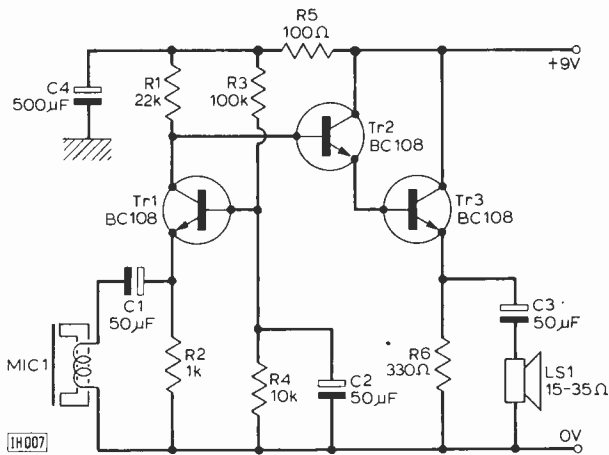


Fig. 66: Using a grounded base stage to amplify a signal from a low impedance source. MIC 1 could be a 35Ω loudspeaker, a moving armature earpiece (or P.O. telephone earpiece) or a variable reluctance transducer—see Fig. 70.

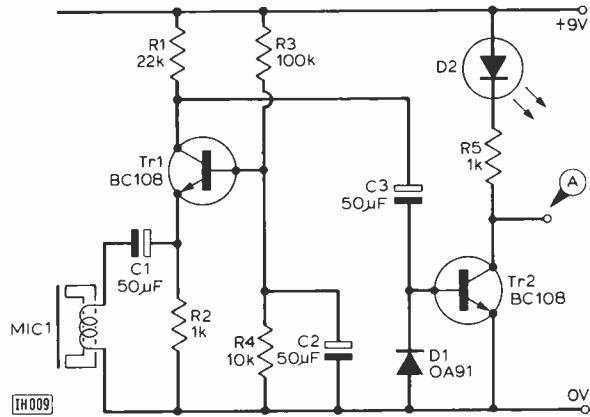


Fig. 68: Changes in flux in the variable reluctance transducer cause the LED (D2) to flash. Simultaneously the potential at A drops in negative going spikes.

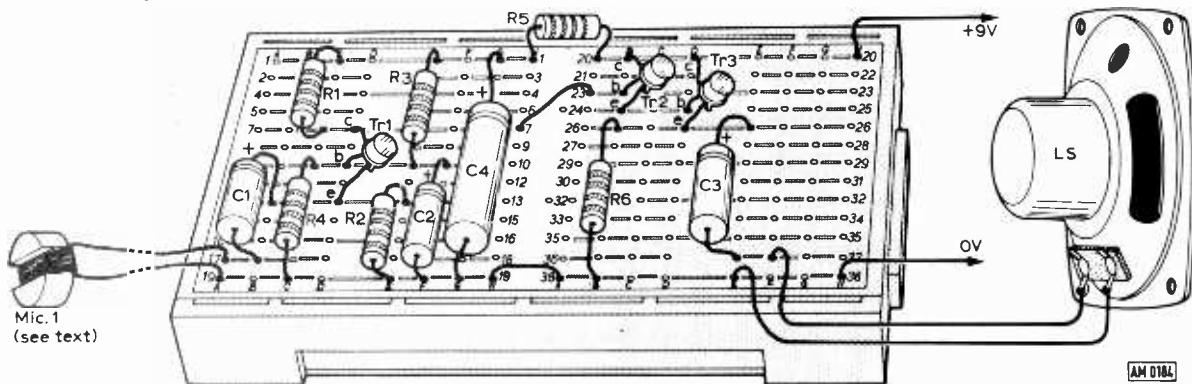


Fig. 67: Layout for Fig. 66.

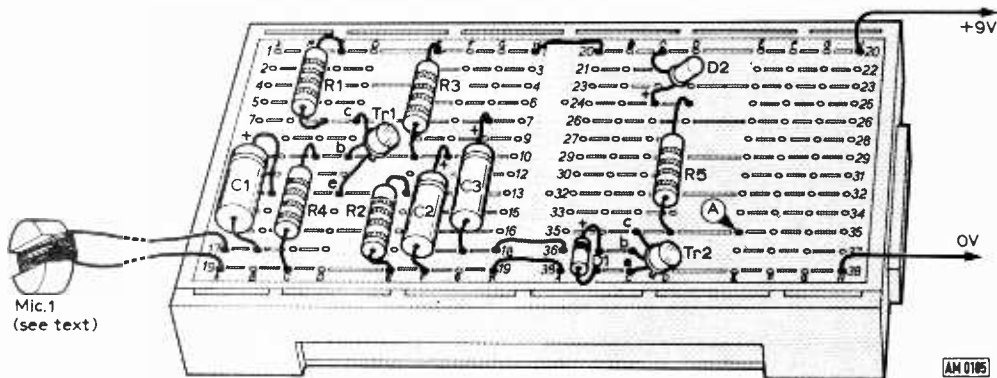


Fig. 69: Layout for Fig. 68.

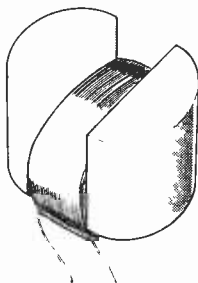



Fig. 70: A variable reluctance transducer can be made by winding about 100 turns of 36 s.w.g. enamelled wire around the base of an Eclipse button magnet. This type of transducer could be used as a simple guitar pickup—provided steel strings are used.

piece of ferromagnetic material touches the magnet you should hear a loud “clunk” from the amplifier. A steel string vibrating between the poles will vary the reluctance of the magnetic circuit at the frequency of the string and this would give rise to a low a.c. output voltage from the transducer.

By modifying the circuit to that of Fig. 68 you can make the light emitting diode flash whenever a piece of iron, or steel, comes in contact with the transducer. Any low power LED will do for D2 but please take note of the connection polarity!

next month—Loudspeaker Drivers.


IN NEXT MONTH'S PRACTICAL WIRELESS

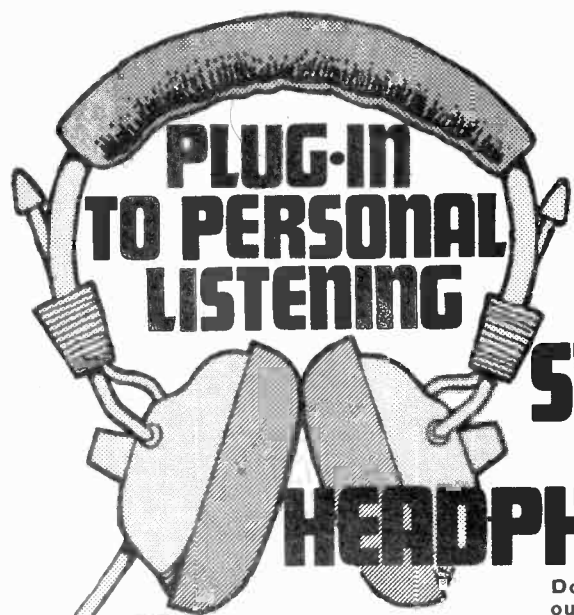

STEREO HEADPHONE AMPLIFIER

PW DERBY

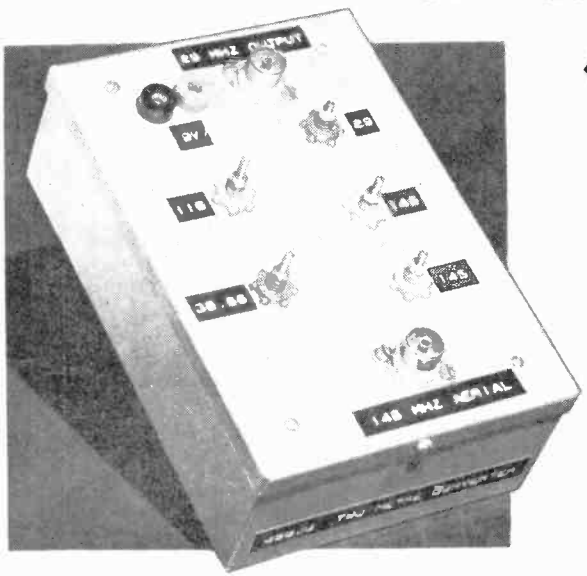Do you run your expensive, high-power stereo Hi-Fi outfit just to listen on your headphones?? Of course you do!! Then why not build the 'Derby' which incorporates only the necessary stereo/mono preamplifier stages, plus full-range tone controls, to drive your headphones? Lightweight, mains operated, it can be fed from your radio or record deck.




◀ TWO-METRE CONVERTER

Tune round the exciting 2 metre VHF amateur radio band on your own short wave receiver! Converts the incoming signals to the 10 metre band. No special coils or components required and simple alignment virtually guarantees first-time operation. A small 9V battery will operate the four transistor circuit.

**MANY OTHER CONSTRUCTIONAL
ARTICLES, SPECIAL FEATURES
AND REGULAR COLUMNS
AUGUST ISSUE ON SALE IN JULY**

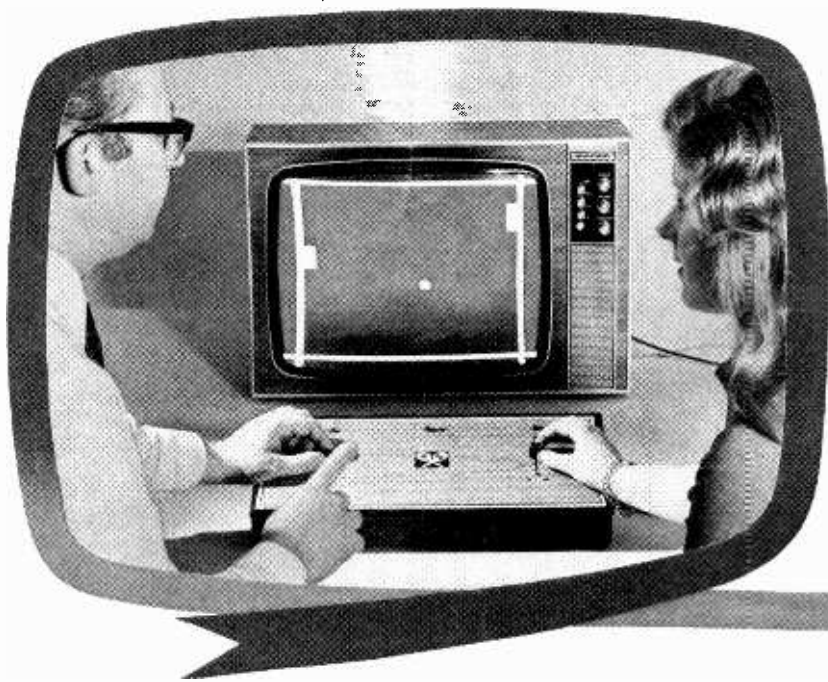The above details are subject to the national industrial situation at the time of going to press.



THE POPULAR NEW ELECTRONIC TELEVISION TENNIS PLAYED ON THE TELEVISION SET PART 1

IT seems an awful waste that the most sophisticated electronic instrument most houses boast should be used only to watch Bugs Bunny or Coronation Street. Already the broadcasting authorities are considering the domestic television set as the basis for a data display terminal in the proposed Oracle and Ceefax systems. Why should we not use the same equipment for exciting new indoor games, puzzles and competitions? This series describes how you can make your own version of a game that is sweeping pubs and clubs throughout America and is rapidly being introduced over here.

The game is "Television Tennis", it involves skill and coordination, can be played by two people and provides excitement which can be shared by young and old. A word of warning to the proud; the author's 6 year old son can hold his own against most competition when playing the game, so there is plenty of challenge for the adult! It is an ideal indoor pastime for rainy days, but many private clubs or social societies might find benefit to their funds in building one of these fascinating, but addictive games.

Once built, the game is simplicity to install; only two connections are required—one to a mains socket and the other via a coaxial lead to the aerial socket of a domestic television. No alterations are needed to the TV except to tune in to a fourth channel and the set can be used normally at any time. Either a colour or black and white set can be used; the only limitation is that it must be a UK standard UHF 625 line model.

Before embarking on the original design the author had some misgivings about the potential complexity of the project and whether it would be suitable for the amateur constructor. By careful design and the use of integrated circuits and printed circuit boards there is no reason why it could not be undertaken by anyone with reasonable soldering ability. The cost of the project might be a bit high for some people—nevertheless it works out much less than a medium quality stereo amplifier. We are giving a complete list of components in this first part so that you may

judge the likely cost for yourself before embarking on the project.

Those who decide to go ahead can make use of this list to obtain best prices for quantity purchases. All the components are now commonplace devices but, as many readers will know, there is a general shortage of components and you may expect delays in delivery of some of the integrated circuits.

In this issue we will describe the general principles of the instrument. Subsequent parts will carry construction details for each of the six circuit boards used, starting with the power supply and UHF modulator. The constructor will then be able to use his domestic TV set as a setting-up instrument for the remaining circuitry thus obviating the need for an oscilloscope.

Presentation

For those who have not yet seen the commercial version—now becoming fairly standard in most amusement arcades—Fig. 1 shows the appearance


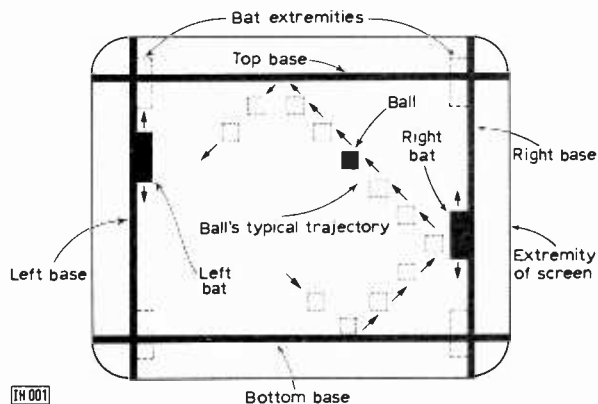


Fig. 1: Appearance of the game identifying the various parts of the display.

ELECTRONIC GAME

15 VISION SCREEN

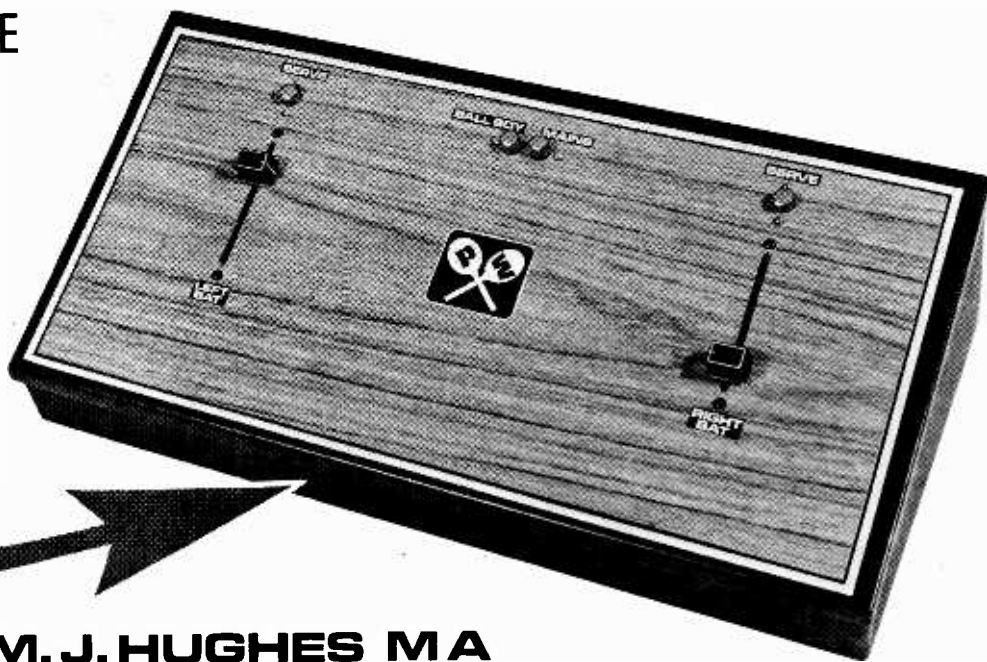

M. J. HUGHES MA

of the game. The television screen displays a representation of a tennis court bounded by two horizontal and two vertical base lines; these are designated the top, bottom, left and right bases. A short vertical bar occurs on the inside surfaces of the left and right bases; these bars represent the players' racquets or bats and their vertical positions along the base lines are controlled by two slider potentiometers on the front panel of the game. Each player can thus control the position of his own bat. To start a game, one of the players presses his "service" button and a ball (small square) will appear out of his base line and move rapidly across the screen towards his opponent. The ball takes an oblique path and, as there is no telling from what point on the base line it will start, it might head straight for the top or bottom base. If the ball hits either of these bases it "bounces" back into the court just like a billiard ball off a cushion. If the opponent positions his bat so that the ball eventually hits it the ball rebounds towards the first player—and so the game progresses. If, however, one of the players misses the ball it will hit the left or right base and disappear until the next service.

No sound effects have been built in, but two signals are provided which could be used to make a "clack" whenever the ball hits either of the bats. This would require extra circuitry which was felt to be rather a luxury and was therefore omitted from the prototype.

TV picture principles

To appreciate how the system works it is essential to understand how a picture is built up on a television screen and to note one or two features of a television raster.


A raster is the regular set of lines which appear on the face of the television tube—whether or not any picture is being displayed. It comprises approximately 625 lines going from left to right on a modern UK standard set. We say approximately

because some of the lines are not seen—occurring above the top of the picture. Referring to Fig. 2, the lines are made by a spot which starts scanning across the top of the tube from left to right. When it reaches the right hand side, the time taken being $64\mu\text{s}$, it returns very rapidly to the left side (this is called the line fly back), steps down the screen a short way and repeats its left to right scan. This periodic scan continues for $1/50$ of a second (20ms) and each time a new line is drawn.

At the end of 20ms you can calculate that with a line frequency of 15.625kHz there will be $312\frac{1}{2}$ horizontal lines drawn at successive vertical positions across the screen forming one field. In a normal television signal the spot then flies back to the top left hand corner (this is called the field fly-back) to a position in between the original scanned lines and repeats the operation. This technique is known as interlaced scanning and the 625 line picture, with which we are all familiar, is actually made up of two separate fields of $312\frac{1}{2}$ lines interlocking with each other. The effect of interlace is to give a very high resolution picture with an effective repetition rate of 25Hz.


Our system is NOT fully interlaced. The picture we display on the screen is generated complete on the $312\frac{1}{2}$ lines of one field. We repeat the field scan at a frequency of 50Hz so that in $1/25$ of a second we still build up a total of 625 lines—although they do not necessarily interlace precisely. Resolution is not a problem in our application and the use of random interlace, as it is called, considerably simplifies design.

Summarising, we have a spot that moves from left to right every $64\mu\text{s}$ and from top to bottom in 20ms. Electronically we can identify the start of every 20ms field scan with an electronic pulse (a field sync pulse) and in a similar way we can "tag" the start of every line using a line sync pulse. In a single field there are $312\frac{1}{2}$ lines each of which starts scanning at a precise interval of time after the field sync pulse.

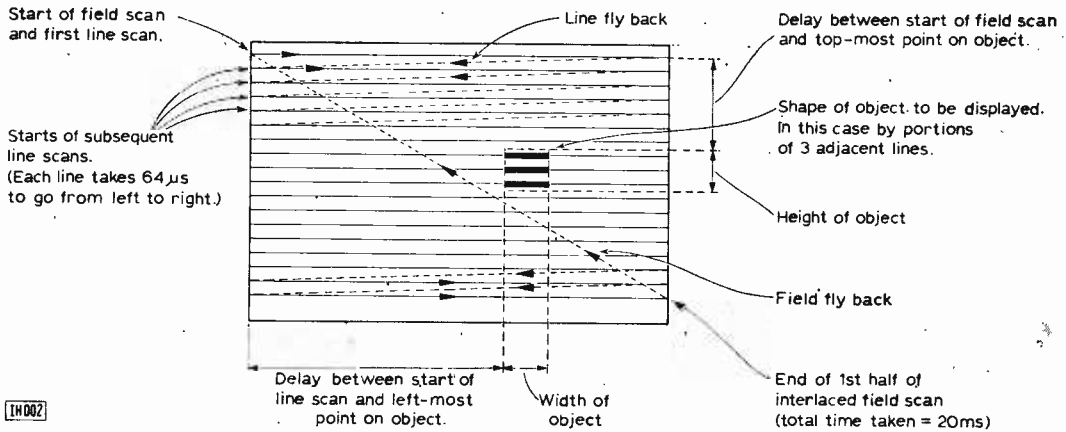


17002

Fig. 2: Elements of a TV raster showing how an object's position can be represented by times within the field and line scans.

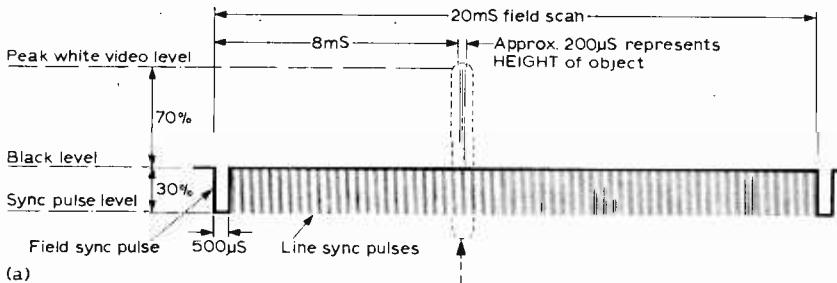

(a)

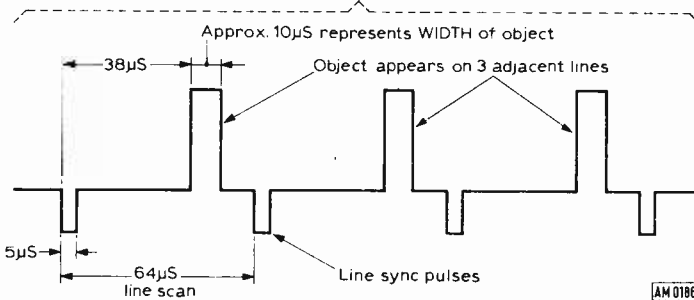

(b)

AM 0186

Fig. 3: The periodic waveform required to produce the object shown in Fig. 2.

Picture generation

Suppose, for example, we want to delineate a square block on the screen at a certain position as shown in Fig. 2. We can do this by specifying on which of the horizontal lines the block is to occur and how far along those lines the block should extend. This can be done by coordinating the block in terms of time from the start of the field (this specifies on which line the block starts to be delineated) and time from the start of the line in question. The width of the block is determined by the length of time we allow the spot to "Bright-Up" along the line and the height of it by the number of successive lines we allow to bright-up. This number of lines is equally determined by time.

The waveforms of Fig. 3 show the signals which would delineate the block shown in Fig. 2. We take +300mV as an arbitrary zero signal level, called black level; any signals going from +300mV in a negative direction are the sync pulses—mentioned earlier. For simplicity of circuitry, we generate a single field-sync pulse rather than the train of pulses normally used in broadcast TV practice. In our case we make the field sync pulse 500μS long (Fig. 3a)

and between it and the next we generate approximately 312 line sync pulses—each 5μS long (Fig. 3b). Positive going signals above +300mV are video levels; these control the brightness of the spot on the television tube. A standard of 700mV above black level is taken as peak white.

To produce the block of Fig. 2 we want to make use of three lines occurring about 8mS down the field. It takes $64 \times 3 = 192\mu\text{S}$ for three adjacent lines to scan across the screen, so we can say that the height of the block is contained within a window of about 200μS occurring 8mS after the field sync. The horizontal position of the block is just to the right of screen centre, say 38μS after line sync. To give the required width the duration of the video signal on each of the three lines would, in this case, be 10μS. Thus you can see that the video signal we want occurs over a very small portion of the field waveform and equally over a very small portion of the three lines.

To generate the signal in the correct time position we need a number of time delay elements, controlled by the synchronisation pulses. One sets the vertical position while another sets the height relative to the field sync. A third sets the horizontal position

★ overall components list

Resistors

$\frac{1}{4}$ or $\frac{1}{2}$ W, 5%:-

330 Ω -6	1.8k Ω -2	15k Ω -5
470 Ω -1	2.2k Ω -6	22k Ω -3
620 Ω -4	3.9k Ω -1	27k Ω -2
1k Ω -10	4.7k Ω -16	68k Ω -1
1.2k Ω -4	12k Ω -1	100k Ω -3
12 Ω 5W-1	68 Ω 1W-1	
220 Ω $\frac{1}{2}$ W-1		

Potentiometers

Linear Sliders:-	5k Ω -2
Submin presets, vertical mounting:-	
5k Ω -1	25k Ω -3
10k Ω -1	100k Ω -3
	250k Ω -2
	1M Ω -2

Capacitors

Polystyrene:-		
1000pF-3	1500pF-4	2200pF-4
Polyester:-	0.1 μ F-15	0.47 μ F-1
	0.33 μ F-2	2.2 μ F-2
Electrolytic:-	47 μ F 25V-4	100 μ F 25V-1
1000 μ F 12V-1	2000 μ F 25V-2	3000 μ F 25V-1

Semiconductors

Diodes:-	1N914-24	1N4004-4
Transistors:-		BC108-2
I.C.'s:-	7805 (regulator)-1	$\frac{1}{2}$ 741
NE555-12	10 LM741C-2	SN7400-16

Miscellaneous

I.C. sockets:- 14-lead DIL-16, 8-lead DIL-14
 Transformer:- Pri: 240V. Sec: 12/15V 0.5A
 Switches:- Push-button type.
 DPCO, non-locking-3
 DP Push-ON/Push-OFF, 250 VAC rating-1
 UHF Modulator kit by Crofton Electronics,
 15/17 Cambridge Road, Kingston-upon-Thames,
 Surrey KT1 3NG
 plus PCBs, cabinet, output socket, etc.

Notes

- The PCBs are available to order from:-
 R. Whittaker
 57 Mungo Park Way
 Orpington, Kent
 at £7.50 per set of six boards including p.p. and VAT. The boards are fully drilled and are available by mail order only.
- An undrilled cabinet in 16swg aluminium is available to order from:-
 H. L. Smith & Co.
 287 Edgware Road
 London W.2
 at £3.00 including p.p. and VAT.

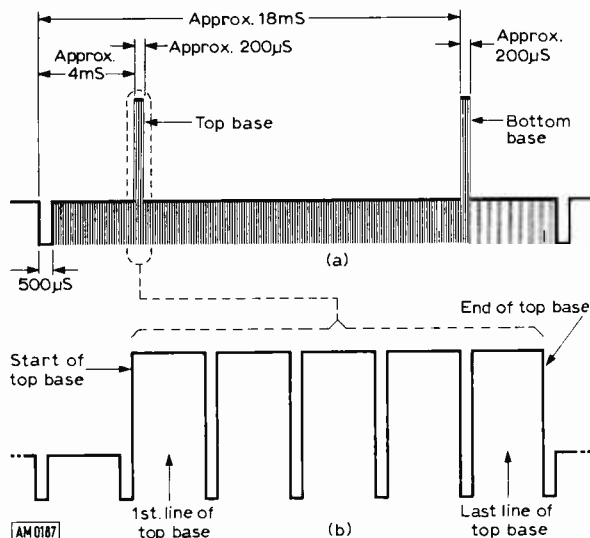


Fig. 4: The top and bottom baselines each occupy the whole of five line scans.

and a fourth the width. We take the field and line video waveforms so produced and combine them in an AND gate to give the video signal in its correctly coordinated time position.

It is a little difficult to grasp this at first because we are dealing in times as opposed to normal vertical and horizontal dimensions. Nevertheless, after a bit of thought, one can quickly get used to thinking of vertical and horizontal times as being equivalent to dimensions across the face of the screen. What we have just described is the technique for producing the video signal for the ball in our game. The position of the ball on the screen and its apparent movements are set by the time delays after the field and line sync pulses. These delays are generated by voltage controlled timing units.

The top and bottom base lines are somewhat simpler to produce because they extend the full width of the screen. We need only define the respective vertical positions and heights (number of lines to be brightened up). These waveforms are shown in Fig. 4. Similarly the left and right bases occur on every line so we need only define their coordinates in terms of time across the screen, Fig 5.

In practice we have to prevent video information appearing in our composite waveform during field and line synchronisation pulses. This is accomplished by means of blanking pulses which, for reasons of simplicity, are made the same length as the sync pulses. In other words the front and back porches normally present on line sync pulses are missing. We use conventional TTL logic levels of +5V and 0V to generate and define all video and sync information and only in the last stage do we convert to normal television signal voltages. In the descriptions that follow a logical "1" or +5V denotes that a video signal is in the state that would bright-up the spot on our screen. To simplify descriptions we have adopted a crude form of Boolean Algebra terminology to describe our waveforms. For example if we use the term "BALL" we mean the waveform that, if fed to the screen, would display the ball—BALL is therefore the inverted waveform for the ball. Other terms that we use include LEFT BASE, LEFT BASE, RIGHT BASE, RIGHT BASE, LEFT BAT, LEFT BAT etc. We shall define other terms later.

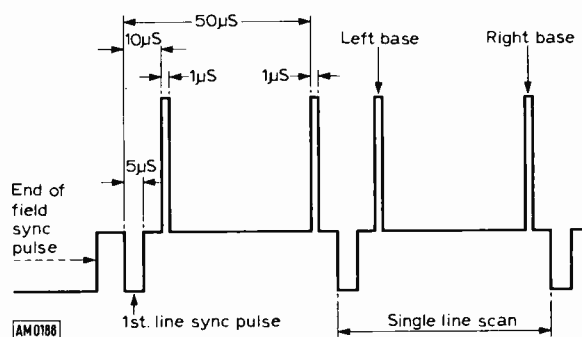


Fig. 5: The left and right base lines occur on every line of the field.

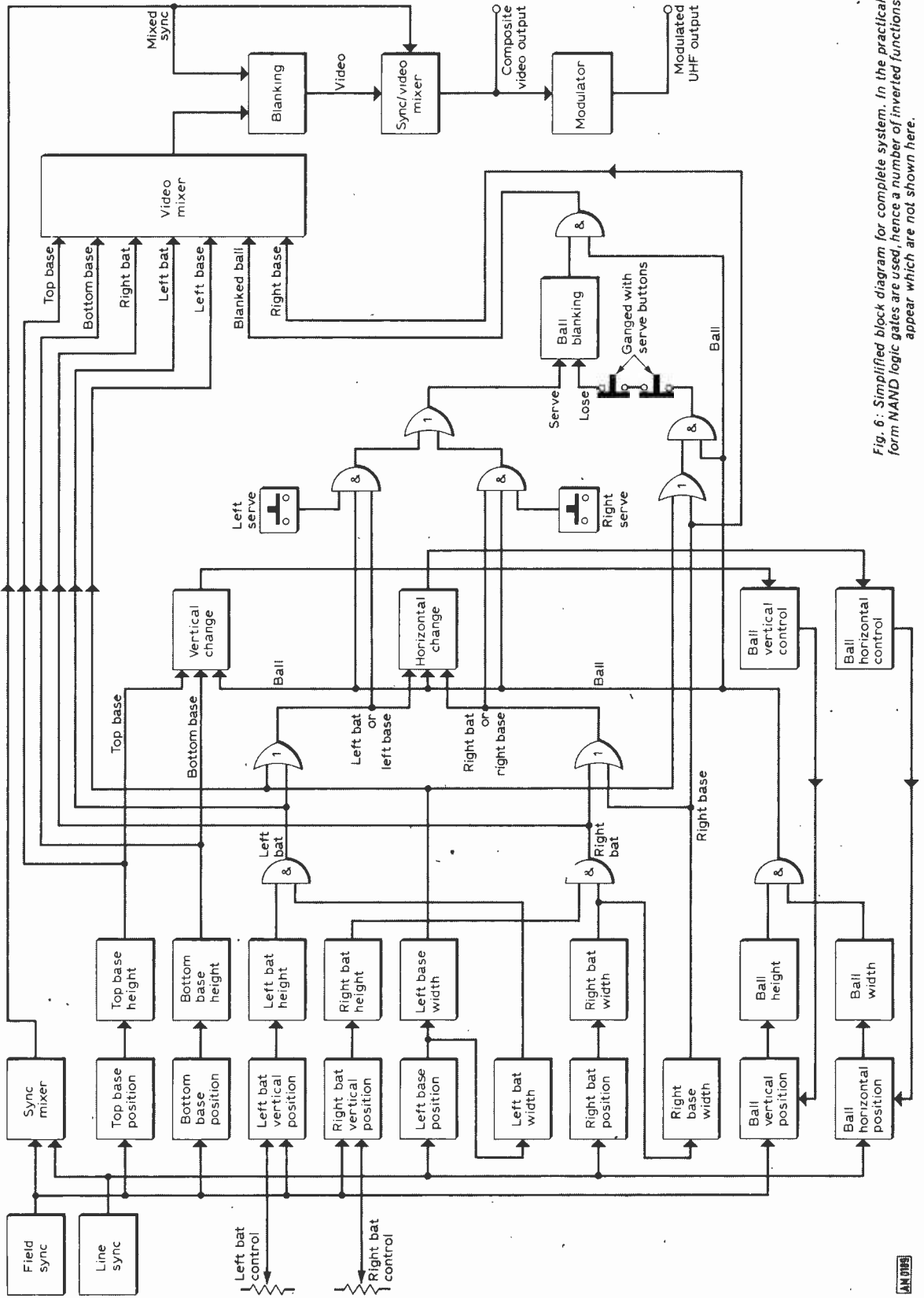


Fig. 6: Simplified block diagram for complete system. In the practical form NAND logic gates are used, hence a number of inverted functions appear which are not shown here.

System description

A simplified block diagram of the complete system is given in Fig. 6. Note that we show basic AND and OR functions in this diagram; in practice NAND gates are used and the logic connections are rather more involved. These will be dealt with in detail in subsequent parts. It is more important at this stage to try to understand the overall system.

All operations are linked to the field and line sync generators. These feed all the delay units which generate the functions of base lines, bats, bat positions, ball and ball positions. Notice, immediately, that the left and right bat vertical positions are set by voltages from potentiometers feeding voltage controlled delay units. Similarly the ball's horizontal and vertical positions are set by the Ball Horizontal and Vertical Control units—each of which is triggered by a Horizontal and Vertical Change signal. All the other delay parameters are preset.

The AND gates just to the right of the delay units provide horizontal and vertical coordination for the left and right bats and ball. The seven waveforms emanating from the delay units are: TOP BASE, BOTTOM BASE, LEFT BAT, RIGHT BAT, LEFT BASE, RIGHT BASE and BALL.

Ball control

Generating these waveforms utilises most of the systems circuitry; the remainder performs fairly simple logic operations on these signals. Although the ball is only seen on the screen during a game it is there all the time, bouncing around between top and bottom or left and right base lines or the bats! Between games it is blanked by the logic circuitry.

Now to deal with that circuitry. First of all the Vertical Change unit which detects when the ball "hits" the top or bottom base lines. A "hit", in reality, is coincidence of signal between the BALL and one of the base line waveforms. If we get BALL. TOP BASE (coincidence between the ball AND top base) the vertical change system detects this with an AND gate. This sets a flip flop, the output signal of which causes a ramp generator to start a voltage sweep that increases the delay in the Ball Vertical Position unit. Eventually, of course, there will be coincidence provided by BALL. BOTTOM BASE; this is detected by Vertical Change and the direction of the control ramp is reversed by the Vertical Change flip flop changing state.

To control the ball horizontally we need it to "bounce off" either the left or right base lines or the bats. Because the bats are inside the court, when they are in the correct vertical position we shall get coincidence with their signals before the respective base lines. Nevertheless it is necessary to get Horizontal Change signals from either BALL. (LEFT BAT + LEFT BASE) or BALL. (RIGHT BAT + RIGHT BASE). These signals are detected and processed by the Horizontal Change unit in exactly the same way as for the vertical operation. Provided both these systems work the ball will stay within the court, bouncing about as already stated. There is only one problem—the ball must be inside the court to start with, otherwise it can never get in. This is a switch-on ambiguity and is overcome by means of a push button on the front panel which, for want of a better name, we call the Ball Boy. This centralises the output voltages of the two ramp generators. It is not shown on this simple diagram.

Service


To complete the system all we need is a method of brightening up the ball at the start of a service and ensuring that it stays bright until one of the players misses it. A miss is detected by coincidence between the ball and either the right or left base lines. In ideal play the ball never hits these because it would have hit a bat first. BALL is ANDED with RIGHT BASE + LEFT BASE and the LOSE signal is then fed via the push button contacts S2b and S3b to the Ball Blanking circuit. If either of these coincidences occurs, the flip flop in Ball Blanking prevents the ball waveform passing through the following AND gate. The ball will then stay blanked until the next service.

Each player has a push button which generates either a RIGHT SERVE or a LEFT SERVE signal. We arrange that if the LEFT SERVE signal is present and the BALL is coincident with either LEFT BASE or LEFT BAT it will bright-up. This logic is effected by the AND gate shown immediately below the representation of the Left Service button. A similar signal is produced if the RIGHT SERVE signal is present when the ball hits the right hand base line or the right bat. Both right and left serve control signals are fed via an OR gate into the other side of the Ball Blanking flip flop. The switches on the input to the LOSE side of this flip flop prevent coincident signals on both inputs. This could have been done by logic but it was felt more economic to use the spare contacts of the service push buttons. We have now modified our original BALL waveform to BLANKED BALL.


Video mixer

All the waveforms are now combined in the Video Mixer which is a simple diode OR gate. They are then blanked to prevent their occurrence during field and line sync pulses and fed to the Sync-Video Mixer. This circuit algebraically adds the correct proportions of video and sync to produce the composite video output signal. The source impedance is a few hundred ohms as opposed to the normal 75 Ω , but the signal level is greater than the standard 1V peak to peak so when loaded with 75 Ω this drops to a normal amplitude. It is assumed that not many people will want to use a video monitor and so this signal is used to modulate a uhf carrier for injection into the aerial socket of a conventional television set. The modulator used was designed by the British Amateur Television Club and is offered in kit form by Crofton Electronics.

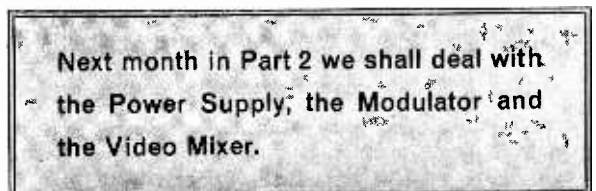This design will only operate satisfactorily on UK 625-line standard. The same principles can be adopted for other TV systems but some of the timing components will need different values, and radio frequencies and modulation polarities will be at variance.



GOING BACK...

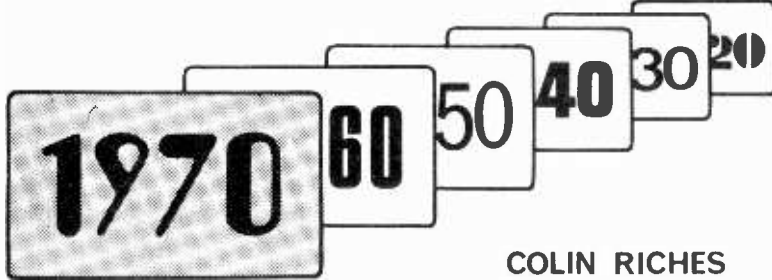

COLIN RICHES

The Edison "Gem"

IN 1892 the British rights of the Bell-Tainter and Edison phonograph were sold to the Edison Bell Phonograph Corporation Limited.

1898 saw the re-organisation of the company as the Edison Bell Consolidated Phonograph Company. It was amalgamated with Edison Limited, a company which had been importing machines from America.



Our Edison "Gem".

One of the most popular cylinder playing machines manufactured by Edison was the "Gem" like that shown in the accompanying pictures. It is described as the "baby" of the Edison phonograph range and first appeared in 1899 when it was introduced to compete with other small models then on the market.

Collectors of cylinder machines will find that the "Gem" is still the smallest practical machine for regular use although most have a motor mechanism which tends to be somewhat noisy. Five models were manufactured.

The "Model A" had a simple spring motor which played one 2-minute cylinder per wind. In the very early models, the motor was fitted in the left-hand end

of the casing as viewed from the front of the machine but was, in later models, turned 180° and mounted at the other end.

It is thought that this change in positioning of the motor took place around 1901 when the "Gem" was fitted into a cabinet. All "Model A Gems" were fitted with a black-japanned horn.

From 1899 to 1901, the "Gem" was supplied minus a cabinet though a "drip pan" to catch the excess oil was screwed to the base. In 1901 it was equipped with the round-topped cover and wooden base and looked rather like a mini sewing machine.


The body was cast iron finished in black enamel with gilt embellishments. The mandrel, over which the cylinder fitted was of polished nickel. Early cabinets had "Edison Gem Phonograph" branded on the lid but this soon gave way to the more familiar "banner" transfer like that on our machine.

The speed adjustment screw and starting knob were combined on the right-hand front corner of the body but in 1901 this was moved to the left-hand side. It was a knurled button which operated a cam movement.

"Model B" was basically the same as its predecessor but the winding key gave way to a crank which was wound clockwise through the inclusion of an extra gear. An aluminium horn was supplied with the "Model B" and this is thought to have been a step introduced to tide the machine over until a larger and more effective horn came into production.

The "Model C" was very similar to "Model B" but had a socket fitted on the body to enable a crane rod to be slotted. This supported a rather large horn.

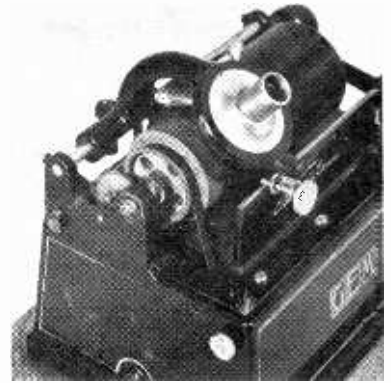The "Gem Model D" was introduced into this country in 1909




Drive belt and speed adjuster.

and was the only "Gem" designed to play both 2- and 4-minute cylinders. The cabinet was oak and the metal body of the machine was finished in maroon with gilt and black lining.

1912 saw the introduction of the "Model E". It had 4-minute gearing only but in all other respects was similar to "Model D".

The "Gem" range was discontinued in 1913 with the price of the "Model E" being £3 3s.

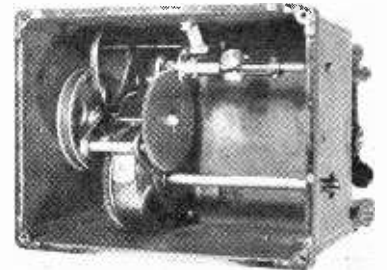An excellent book, if you are interested in learning more about Edison Cylinder Phonographs, is entitled, "A Guide to The Edison Cylinder Phonograph". It contains details of the spring-driven models produced from 1859-1929 and has been compiled by George L. Frow to whom I am indebted for supplying some of the information on the "Gem" machines.



Speed governor mechanism.

Mr. Frow is always on the look-out for new information on Edison machines, so if anyone would like to write to him, he can be contacted at "Salters", Seal Hollow Road, Sevenoaks, Kent. Another useful reference for vintage "gramophone" enthusiasts is the Talking Machine Review. It is edited by Mr. Ernie Bayly and appears at regular intervals throughout the year. Further information may be obtained by sending a s.a.e. to Mr. Bayly, 19 Glendale Road, Bourne-mouth, BH6 4JA.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1-05p** P & P 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **27 1/2p** POST & PACKING 16p

Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	55p
B81	10	Reed Switches, 1" long, 1/4" dia. High Speed P.O. type	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated Circuits, 4 Gates BMC 982, 2 Flip Flops BMC 945	55p
H41	2	Sil Power transistors comp pair BD131/132	55p
H63	4	2N3055 type NPN Sil. power transistors. Below spec. devices	55p
H64	4	3819 N Channel FETs 2N3819 in plastic case	55p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200. OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H16	15	Experimenters' Pak of Integrated Circuits, Data supplied	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p
H67	10	3819N Channel FETs plastic case type	55p

Make a rev counter for your car

The 'TACHO BLOCK' This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

£2.75 p.p. 38 1/2p Per Instrument

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73p.

Extension Telephones. 71p each. p.p. 27p. £1-37 for 2. P.&P. 55p.

These phones are extensions and do not contain bells.

Electronic Transistor Ignition £6-60

Complete kit incl. V.A.T. p. & p. 11p
Ready built & tested unit £9-90 incl. V.A.T.
Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility

New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available

Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3" x 5 1/2" x 3". We have already received a large order from a major T.V. Rental company.

Ready built unit only **£10-92** Complete kit **£8-72**

(includes V.A.T. and p. & p. but no batteries)

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can
TYPE "B" PNP Silicon, plastic encapsulation
TYPE "E" PNP Germanium AF or RF
TYPE "F" PNP Silicon plastic encapsulation
TYPE "G" NPN silicon similar ZTX 300 range
TYPE "H" PNP silicon similar ZTX 500 range

8 RELAYS FOR VARIOUS TYPES P & P 27 1/2p £1-10p

High Speed Magnetic Counter



4 digit (non-reset) 24V or 48V (state which)
4 x 1 x 1 in. 33p. P.&P. 5p.

Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shattering low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min. 15. HFE Min. 15.
40 Watt 1-12 13-25 26-50
22p 20p 18p
90 Watt 26 1/2p 24 1/2p 22p

Range 2. VCE. Min. 40. HFE Min. 40
40 Watt 1-12 13-25 26-50
90 Watt 33p 31p 29p
38 1/2p 36 1/2p 33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in *Practical Wireless* Dec. Issue, complete with application data £1 10p.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 15p Wall Chart 18p

LOW COST DUEL IN LINE I.C. SOCKETS
14 pin type at 16p each | Now new low profile 16 pin type at 18p each | type

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak.
Please ask for Pak P.1. only 55p

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co Reg No 82C 09

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344

HOTLINES

ON RECENT DEVELOPMENTS

BR-BR, BR-BR

Have you ever wondered what is going on behind the scenes as you stand and wait for your train as accident, industrial dispute or weather strike at services. The worst part often seems to be that no-one knows what is happening. When will a train materialise and, when it does, what platform will it be on? The fact that the only visible means of communication for some station staff is one of those mahogany-cased telephones of yesteryear hardly inspires confidence.

The problem is, of course, that any industry where safety is so vital has to be very sure indeed of the reliability of equipment and systems before adopting them for general use. There have been changes — recently the more observant will have spotted the UHF pocket radiotelephones in use by senior platform staff of some regions of British Rail.

Those of you who brave the melée of London Bridge each day may well have wondered what the future holds, with all the new signalling arrangements now being installed.

In a paper presented recently to the Institution of Railway Engineers, it was revealed that a mini-computer installation with disc storage at London Bridge will form the heart of the new system. The track diagram in the signal box is divided into eighteen sections and includes CRT displays of train running and signal aspect information.

At the associated London termini, station supervisory staff will have visual display units (VDU's) which can be switched to show the situation on any of the eighteen sections. Information displayed will include the position of trains, whether moving or at platforms, identified by their alphanumeric reporting numbers. "Train ready to start" signals will appear as a flashing symbol. The station platform "Next train" indicators will also be controlled by the computer.

Trials already carried out by B.R. have proved the feasibility of

operating a computer continuously all the year round in the environment of a railway signal box equipment room. An MTBF of about 8000 hours has been achieved in these trials. Additional reliability in the London Bridge installation is provided by a standby mini-computer, whilst VDU's are available in the signal box for use in the event of failure of one of the main CRT displays.

Facilities are included for timetable changes to be fed into the system and activated automatically on the due date. A future addition may be for the computer to control routing at junctions. If that comes about, it sounds as if the system will almost run itself!

COWSHED COMPUTERS

Latest application of data processing is in the running of dairy herds. Using a micro-computer to maintain records of feed, health and milk yield of each cow is claimed to double the number of cows which can be handled efficiently by a herdsman. The farmer will also be provided with data on operating costs and income.

STRIKE A LIGHT

Talked about for quite a while, the light-sensitive thyristor is here at last. Announced by Motorola at the Paris Components Show are two ranges of device handling 250 and 400mA with PIV ratings from 15 to 200V.

Also new from Motorola are three Darlington power transistors with 15A current capability and large-signal current gains of up to 5000. Base to emitter shunt resistors and a shunt diode between collector and emitter of the output transistor are incorporated —all this in a standard TO3 package!

ON THE BEAM

We hear that scientists at the RCA Laboratories are working on a modulator which could put 25,000 telephone calls or 20 TV channels on a single laser beam.

The device requires very much lower modulating powers than previously necessary and is compatible with ICs. Modulating voltages are applied to metal fingers which influence the passage of light through a thin-film optical waveguide.

OPEN SESAME!

Hitherto more or less confined to the realms of science fiction or detective novels, the voice-operated lock could become a practical proposition in a couple of years if research now under way at the Westinghouse Laboratories in New York is successful.

When we speak, air is expelled from the lungs past the vocal chords, causing them to vibrate. These vibrations chop the air stream up into a string of pulses which travel up the vocal tract to the lips, giving the basic pitch to the voice. On their way, the frequency spectrum of the pulses is modified by resonances of the tract, chiefly in the throat, mouth and nose, to produce the final sound.

These resonances, which are known as formants, are different for each person and produce "voice-print" patterns as distinctive as fingerprints.

Voice-identifying locks have been produced before, but needed complex filters and large computers and cost up to \$100 000. By using a different filter system and a smaller computer, Westinghouse hope to produce their lock for under \$100.

The lock could be set to respond to several voices and the password changed as often as necessary. Besides security applications, the system could be used for "no-hands" operation of machinery.

One point worries me. What happens when you have a cold or a sore throat, or even on the morning after the night before?

Novus

MODIFYING



P.S. COLLINS

DU E to the series arrangement of the 'start' and 'park' switches of the wiper motor on some cars, Fig. 1, the original circuit and wiring must be modified. Figure 2 shows the modified circuit. The basic circuit remains the same, but Tr5 drives a relay instead of the motor directly. The relay contacts effectively replace the car's wiper switch. S1 is thus rewired to provide the choice of variable delay or continuous operation, with centre 'off'.

It will be noted that in the continuous position RL1 is driven by a direct earth through S1b and S1a provides the 12V. 12V is also present on the rest of the delay circuit but its effect is nil as Tr5 is short circuited.

Figure 3 shows the modified wiring arrangement. RL1 may be glued to the box lid or a larger box (RS Comps. type 993) could be used to house all the components including the relay.

The circuit shown is for negative earth systems. For positive earth, D3 must be reversed. ■


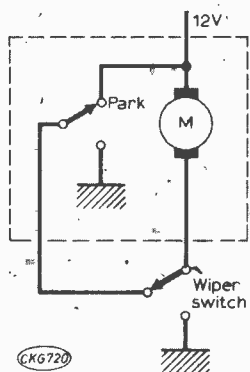
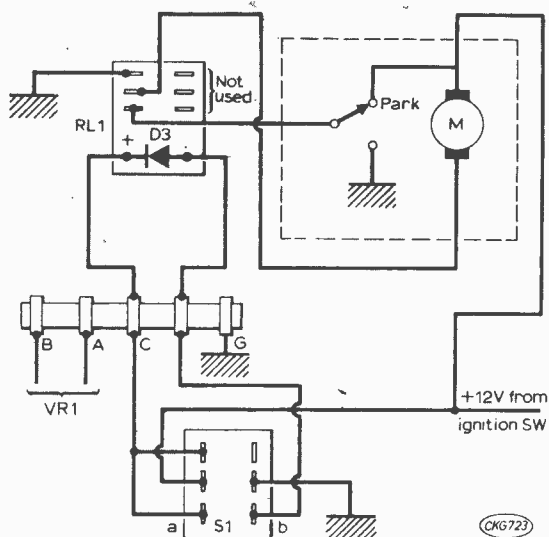


Fig. 1: This switching arrangement of windscreen wipers found on some vehicles will prevent the proper operation of the Quickwipe circuit described in the April Issue.

Fig. 2: bottom left, is the modified circuit using a relay to drive the wipers.

Fig. 3: Rearrangement of the wiring to incorporate the new relay circuit. Unless a sealed relay is used the relay should be enclosed in a box with the rest of the components. The connections from the PCB to the terminal strip remain as in the original article.

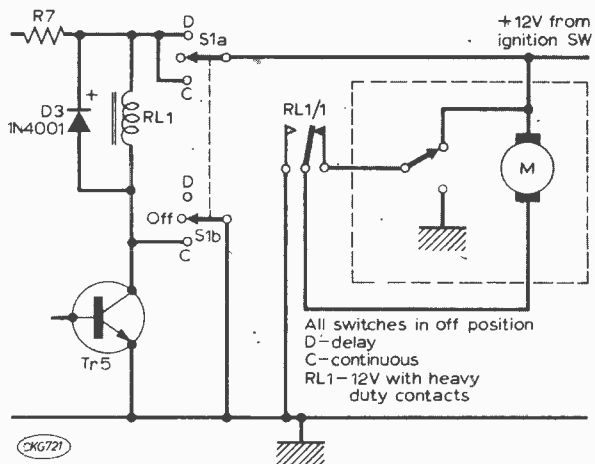

GENERAL PURPOSE PREAMPLIFIER

A. FOORD


THIS amplifier is designed for audio or measurement applications where an AC coupled amplifier of well defined gain and low noise characteristics is required. Fixed gains of 20, 30, 40, 50 and 60dB are provided. The noise referred to the input is $0.5\mu\text{V}$, which is low enough for most audio requirements.

General purpose amplifiers such as the 741 types are limited in frequency response and have a relatively high input noise. For example, the 741 circuit shown in Fig. 1 will have a bandwidth of about 1kHz when the overall gain is 60dB. With the 741 the open loop frequency response is shaped so that the closed loop is stable under all conditions, including unity gain applications. Some amplifiers such as the 748 and 301 have external frequency compensation which can be tailored to suit the application. However the improvement is only a factor of ten, giving a bandwidth of 10kHz when the overall gain is 60dB. Even the less readily available amplifiers, such as the LM318, which are designed for wide bandwidths can only give a 30kHz bandwidth when the gain is 60dB.

CAUSE OF LIMITED BANDWIDTH

The frequency is normally limited by the bandwidth of the lateral PNP transistors used for level shifting in the input stages and by the low collector currents which are used so that the input bias currents may be reduced and an excellent DC performance obtained. For many AC applications the DC characteristics are of secondary interest.

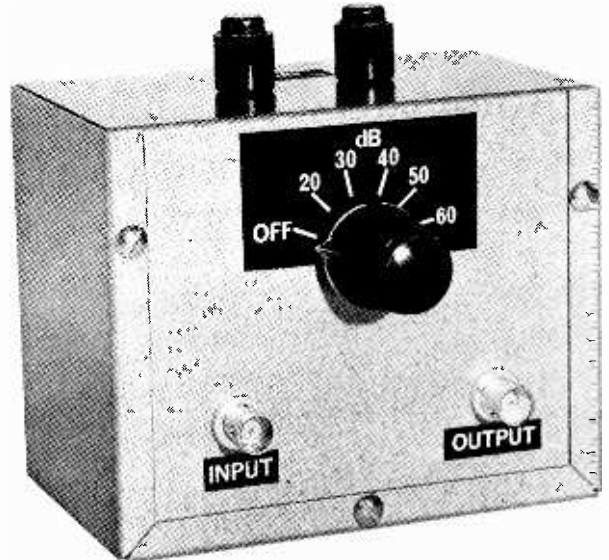While special low noise integrated circuits are available the approach indicated here gives an improved performance with little added complexity and cost. In Table 1 this technique is compared with the readily available standard integrated circuits.



Maximum Output	4V RMS
Output Resistance	50Ω
Input Resistance	47kΩ
Gain (dB)	Bandwidth
20	10 Hz to 700kHz
30	10 Hz to 700kHz
40	15 Hz to 700kHz
50	10 Hz to 700kHz
60	20 Hz to 400kHz
Bandwidth	Noise referred to input (50Ω source)
100Hz to 10kHz	0.31μV
100Hz to 30kHz	0.48μV

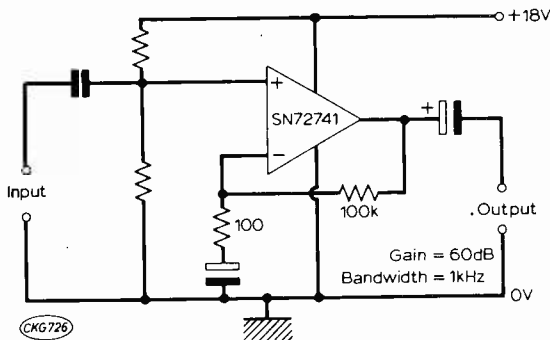


Fig. 1: Simple amplifier using the standard 741 integrated circuit.

TABLE 1

AMPLIFIER	GAIN (dB)	BANDWIDTH (kHz)	RELATIVE NOISE
741 series (internal compensation)	60	1	20
LM318 wideband amplifier	60	30	15
LM381 low noise amplifier	60	20	5.5
301 series (external compensation)	60	10	16
748 series (external compensation)	60	10	20
Suggested Circuit	60	400	2.1

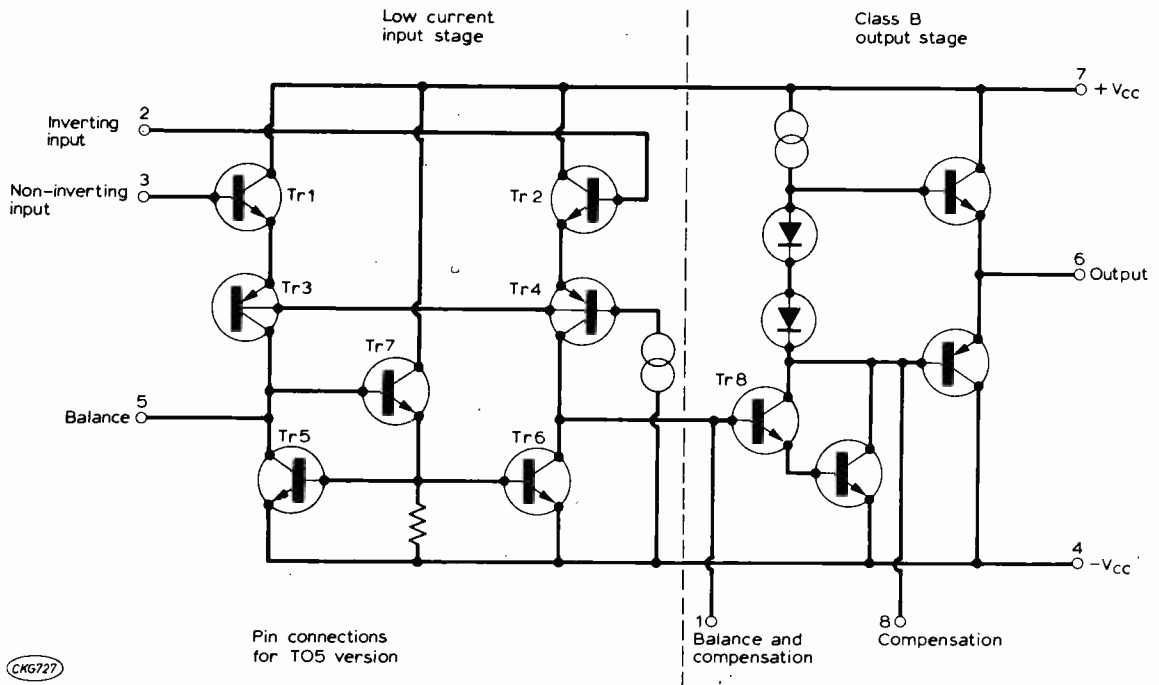


Fig. 2: Simplified diagram for the 301 integrated circuit.

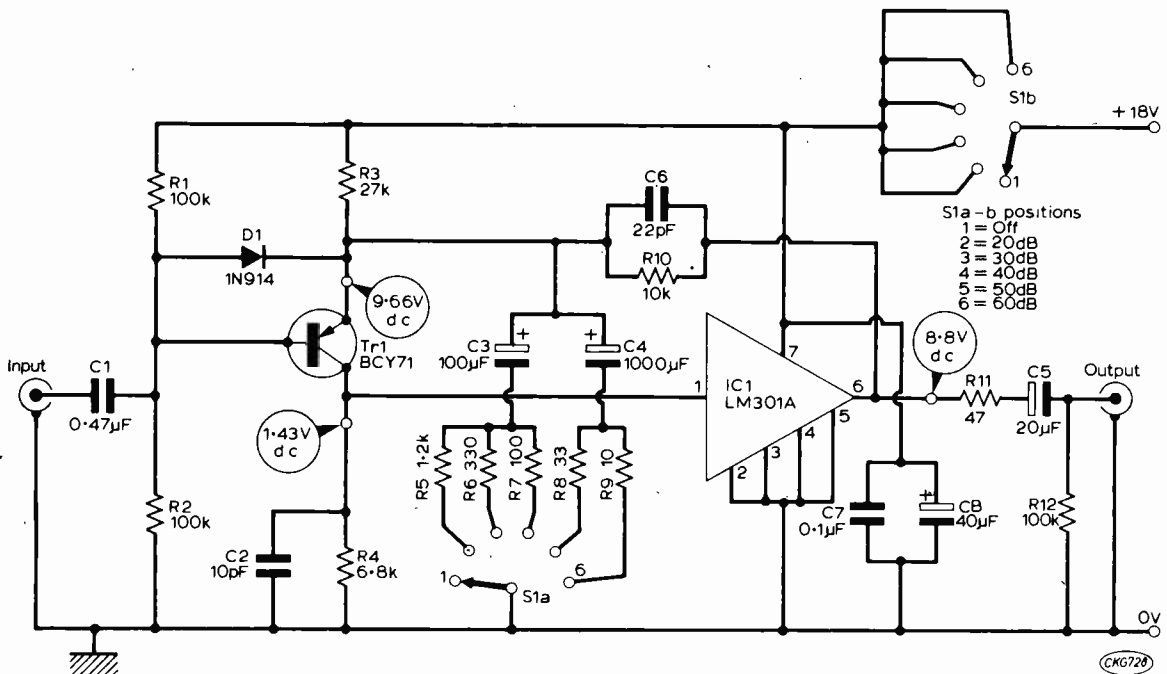



Fig. 3: Complete circuit of the final arrangement of the wideband pre-amplifier.

A simplified diagram of the 101, 201 and 301 family is shown in Fig. 2. The main limiting components occur in the input stages, before Tr8. The second stage, from the base of Tr8 onwards, has a high gain with good bandwidth, good current capability and short circuit protection. This section of the integrated circuit should be retained, but the input stage should be replaced. Fortunately the base of Tr8 is accessible because this point was used for offset voltage


balancing purposes. If pins 2, 3 and 5 are connected to the most negative supply point (pin 4) then the complete input stage is effectively disconnected.

COMPLETE CIRCUIT

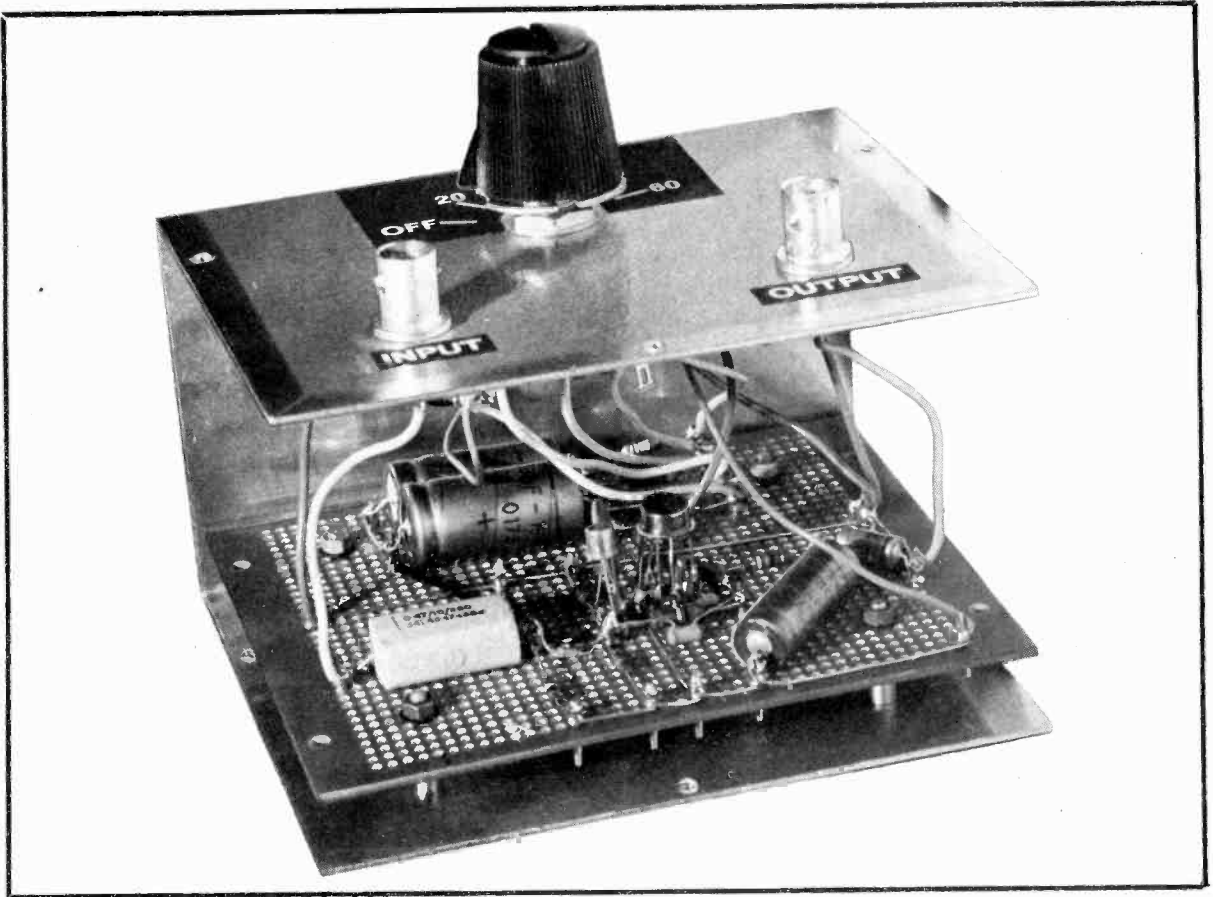The construction is straightforward, Fig. 4, but the input stage is replaced by a single PNP transistor Tr1 in a common emitter configuration which drives the output stage via pin 1. The gain without negative



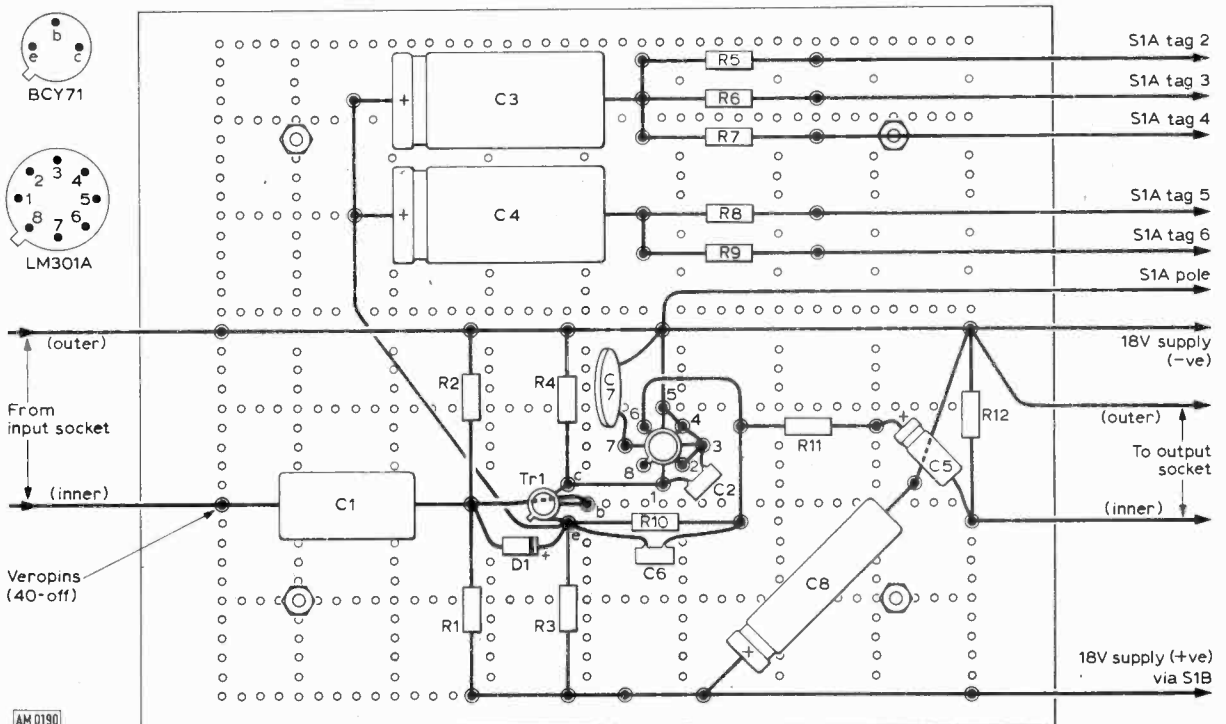In the finished pre-amplifier, above, the circuit board is mounted about $\frac{1}{4}$ in. off the case to clear the veropins.
 Fig. 4: (below) gives the board layout and wiring.




feedback is about 80dB which allows the gain with feedback to be well defined. This is achieved by R10 and R5 to R9, to give the switched gains shown. Capacitors C2 and C6 shape the frequency response and ensure stability for the closed loop gains allowed by S1.


When the unit is switched on C3 or C4 will take a little while to charge up to the operating voltage and the base-emitter junction of Tr1 will be reverse biased for this time. Although the breakdown current would be limited to a 'safe' value this action can increase a transistor's noise level. Any reverse base-emitter voltage is therefore limited to a safe value by the conduction of D1. Under normal operating conditions D1 is reverse biased and cannot affect the circuit's operation.

CONSTRUCTION

The construction is straightforward, Fig. 4, but the unit must be placed in a metal box if hum pickup is to be avoided at high gain levels. Due to the bandwidth of this circuit all wiring should be kept short and the decoupling capacitor C7 placed directly across the pins of IC1. In critical applications the unit should be run from batteries (inside or outside the box) to reduce hum and earth loop difficulties.

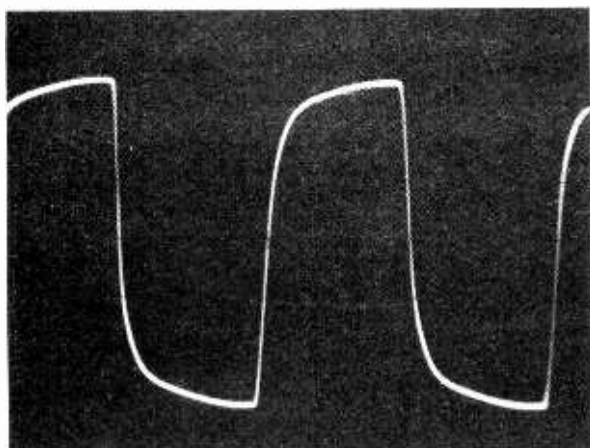

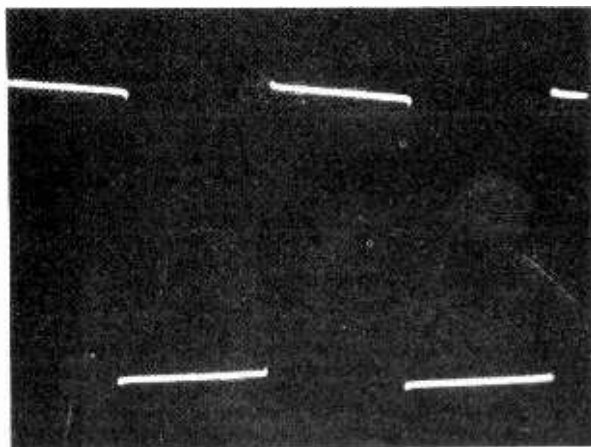The output of the amplifier with the gain at 60dB and a 100kHz square-wave input.



Here the gain is still 60dB but the input is 1kHz squarewave.

★ components list

Resistors

R1 100kΩ 5%	R7 100Ω 2%
R2 100kΩ 5%	R8 33Ω 2%
R3 27kΩ 2%	R9 10Ω 2%
R4 6.8kΩ 5%	R10 10kΩ 2%
R5 1.2kΩ 2%	R11 47Ω 5%
R6 330Ω 2%	R12 100kΩ 5%

All resistors are $\frac{1}{4}$ watt

Capacitors

C1 0.47μF polyester	C5 20μF 16V
C2 10pF ceramic	C6 22pF ceramic
C3 100μF 16V	C7 0.1μF " disc
C4 1000μF 16V	C8 40μF 25V

Semiconductors

D1 1N914	Tr1 BCY71
IC1 LM301A, SN72301A or similar TO5 version	

Miscellaneous

S1, 2 pole 6 way wafer switch. Terminals (2).
Sockets (2). Veroboard and pins. Knob.
Case approx 5 x 4 x 3in.

When the unit is tested a single DC measurement at the output of IC1 (pin 6) will confirm that the circuit conditions are correct. This is a low impedance point and it does not matter if the multimeter requires a few milliamps to operate it. Although a nominal 8.8V was measured on the prototype, variations of perhaps ± 1 volt would be normal. If an oscilloscope is available R3 may be changed, by one preferred value up or down, until the output limits symmetrically.

NOISE LEVELS

The design of a low noise amplifier is complex, depending on the source impedance, the gain and bandwidth required and the transistor parameters. For this application a collector current of 220μA has been chosen for Tr1; which is a good compromise for general wideband applications. For all transistors the noise increases at low frequencies.

If the circuit is specifically required for audio applications, where the 40kHz bandwidth is not necessary, the performance may be improved by reducing Tr1's collector current. Experienced constructors with the necessary test equipment could redesign the circuit for a collector current of between 50 and 100μA. ■

P.W. ELECTRONIC COMPONENTS BUYERS' GUIDE

Special supplement in the October issue giving details of components commonly available, followed by additional sections in succeeding issues. More details on page 116 of the June issue.

COMPONENT SUPPLIERS

Have you sent us your catalogues or lists for use in compiling the P.W. Buyers' Guide? Closing dates: 17th June for information; 1st July for advertisers in the October supplement only.

TAKE 20

DAVID ANDREWS



No. 61

PERSONAL TRF RECEIVER

A series of simple transistor projects, using not more than twenty components.

UNLIKE many simple radio receivers this one will operate first time without any messing about with regeneration. It uses a straightforward parallel tuned circuit with the coil wound on a ferrite aerial rod. This is directly coupled to the RF amplifier/detector formed by Tr1 and Tr2; the rectified carrier is suppressed by C1 and the detected audio fed to one stage of AF amplification Tr3. The output goes to a crystal earpiece and when the set was operated in a notoriously bad reception area in a valley in the South East it pulled in ALL the major broadcasting stations, including London Broadcasting and Capital Radio. The output level was almost comparable with a similar circuit using a ZN414 followed by an identical amplifier!

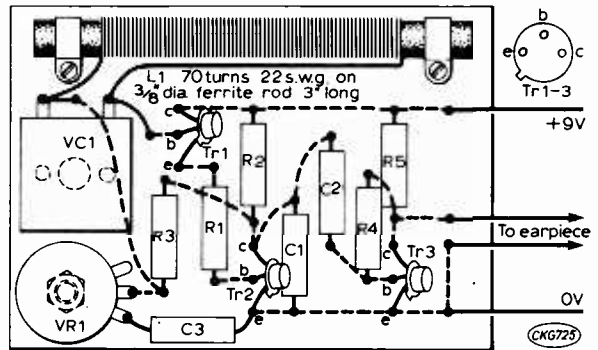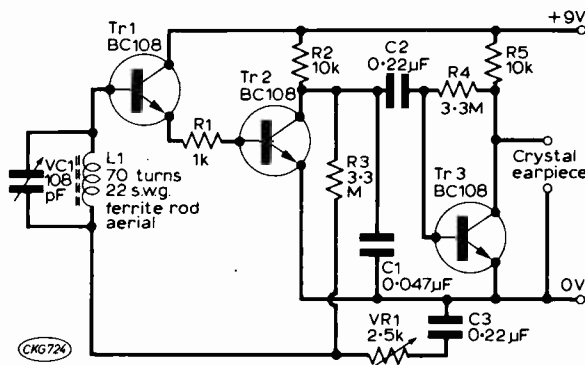There are only two snags. The circuit is rather sensitive to fluorescent light interference and if operated too close to mains cables a certain amount of hum is induced. As a pocket portable neither of these points should present practical problems.



The set may be built on a piece of Veroboard, with pins, as shown here

Sensitivity is so high that it is necessary to include a volume control (we really do mean this, if you have any local stations!). To achieve this we introduce a controllable amount of negative feedback by adjusting the effect of decoupling capacitor C3 with VR1. Several test models have been built and with some high gain transistors there is a tendency for the circuit to oscillate which is easily prevented simply by reducing the gain by turning down VR1. For those who can't afford a ZN414 we assure you that this circuit gives very comparable results.

Circuit of the TRF receiver. No external aerial is required with this set.

The secret of its excellent selectivity is the very high input impedance provided by the emitter follower action of Tr1; the loading on the tuned circuit is minimal and maximum Q can thus be obtained. A warning to some constructors—the tuning is so sharp that you have to tune slowly to prevent overshooting the station. There is a high degree of RF amplification which obviates the need for regeneration. The quality is thus excellent and there are no setting up problems.

★ components list

R1	1kΩ	VR1	2.5kΩ linear
R2	10kΩ	VC1	108 or 150pF
R3	3.3MΩ	L1	See Fig. 2
R4	3.3MΩ	Tr1	BC108
R5	10kΩ	Tr2	BC108
C1	0.047μF	Tr3	BC108
C2	0.22μF		Crystal earpiece
C3	0.22μF		Ferrite Rod 3" × 1/4" dia.

SPARE A THOUGHT...

TO what extent do you maintain your fullest interest in radio, electronics and allied practical activities? Maybe you consider it to be a winter pastime, but from evidence that we have, summer issues of P.W. are still gobbled up from the bookstalls at an incredible rate. What does seem to be the case is that often you may decide to get your copy from a different source, for example in holiday resorts or nearer your home, whereas previously you might have purchased from the station bookstall on the way to your place of work.

Regular orders through newsagents can be delivered to your door, but if it does not arrive when expected, the newsagent is the first in the firing line for questions. Occasionally, factors outside his immediate control intervene and delay publication. We cannot, unfortunately, inform all newsagents and readers quickly enough when this happens and it is regretted that these occasions ever have to occur. So please have some patience with the newsagent. It may not always be his fault!

oscilloscope

PART 5

techniques ALAN AINSLIE

X DEFLECTION AND TIMEBASE

In the first part of this series we considered the requirements for a timebase system, namely the generation of a linear sawtooth coincident with the recurrence of the signal under observation. There are two basic modes of timebase operation, sync or trigger. We shall consider sync timebases first.

The synchronised timebase is a free-running generator of sawtooths; when one cycle is complete the next one starts with no time gap. A portion of the Y signal, derived from the Y amplifier by a cathode follower, is fed to a "sensitive" part of the circuit and this keeps the timebase in step with the Y signal. Fig. 1 shows how a sine wave is traced on the screen in this manner. However, the timebase is unable to cope with the requirement of a scan of duration less than one period of the waveform being examined.


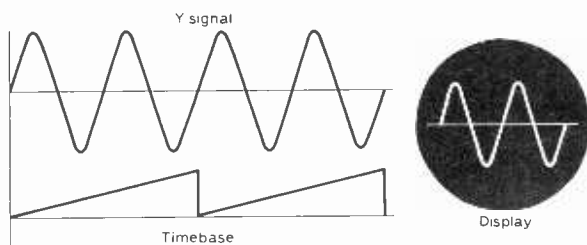


Fig. 1: Generation of a sine wave on a CRT screen

The sawtooth can be generated in a number of ways, all involving charging a capacitor linearly and producing the scan, then discharging it, producing the flyback. The flyback trace interferes with the main trace and so a means of cutting off the trace during flyback has to be found. If the capacitor charges up in a positive manner and is then discharged through a resistor, this resistor will have a positive pulse across it during flyback. If this pulse is capacitively fed to the CRT cathode the trace will blank out during retrace, as required.

CONTROLS

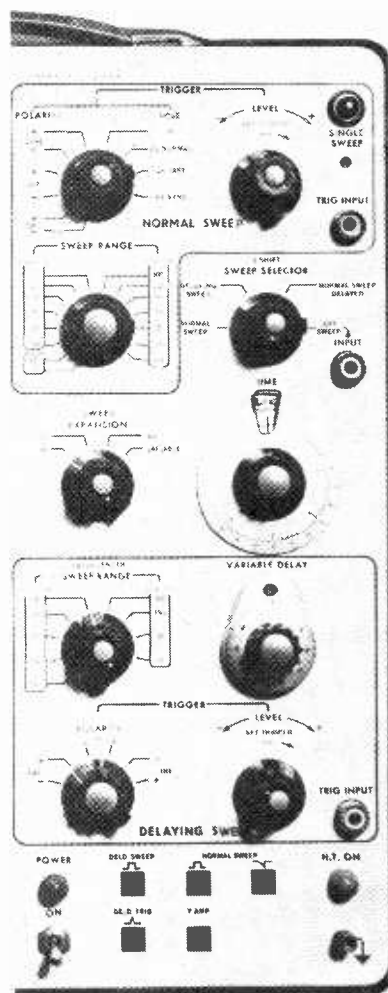The controls on a sync timebase are frequency, sync and, sometimes, width. The sync control selects the amount of Y signal used to sync the timebase. If too little is applied the trace will not lock and if too much is applied the trace will "fold up". The width control is adjusted for a satisfactory image width on the screen.



The timebase facilities on a dual timebase oscilloscope

The output from the timebase is applied to an X amplifier which may have to produce 100 or 200V deflection. The bandwidth required is only a couple of MHz and small scopes may use a simple single valve output. Usually push-pull or balanced output is used and the sawtooth can be applied to one valve and again (as in the Y system) a calibrated shift control can be used to drive the other grid. Fig. 2 shows the X amplifier used in the EMI WM16 scope.

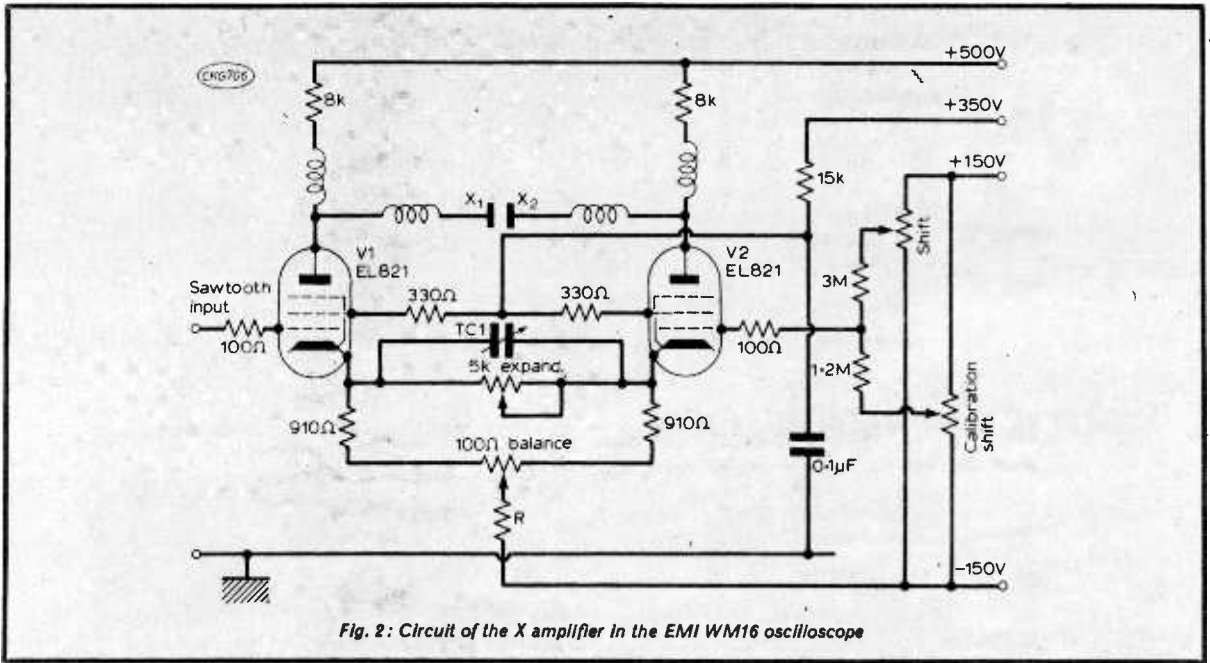


Fig. 2: Circuit of the X amplifier in the EMI WM16 oscilloscope

TYPICAL X AMPLIFIER

The two valves can be seen to form a simple phase splitter. The coils and TC1 peak the HF response. The 5kΩ variable pot between the cathodes is in fact a switched series of preset resistors giving calibrated X expansion. Resistor R in the cathode is in fact a constant-current valve. The operating point of the valve can be adjusted to vary the X plate potentials and these are adjusted to be equal to the potential of the Y plates with the spot central, to minimise spot distortion. The balance control is set so that the cathodes of the two valves are at the same potential when the spot is central (i.e. varying the 5kΩ between cathodes has no effect on the spot when central).

TRIGGERED TIMEBASES

Most timebases in use are of the triggered variety permitting much greater flexibility than the sync timebase. In this mode of operation a sweep length control selects the duration of the sweep, the sweep beginning when the timebase generator receives a pulse from the trigger amplifier.

Fig. 3 shows the general requirement for a trigger amplifier. The Y signal is sampled from the Y amplifier by a cathode follower. The signal is amplified

and "phase split". A "trig polarity" switch selects one or the other of the phase splitter outputs which is applied to a comparator and compared with a DC level set by the "set trig level" control. The comparator produces a pulse when the comparator input bears a certain relation to this DC voltage selected on the "set trig level" control. This pulse is taken to the timebase to initiate the scan process. The pulse will occur once per input cycle at the same level as shown in Fig. 4.

The trigger pulse "flips" a bistable which starts the capacitor charging process. The multivibrator will now accept no further trig pulses until it returns to its former state. The capacitor selected by the range switch is charged by a constant-current valve, the value of the current being set by variable resistors also selected by the range switch, these being the sweep calibration presets. The ramp produced by the charging of the capacitor is amplified by a cathode follower and fed to the X' amplifier and also to a comparator. When the level of the ramp passes a certain level the comparator produces a pulse which initiates the discharge of the capacitor. The bistable is also triggered into its original state, but is only allowed to return at a rate comparable with 2% of the sweep length, allowing complete recovery of the circuits before trigger pulses are again accepted.

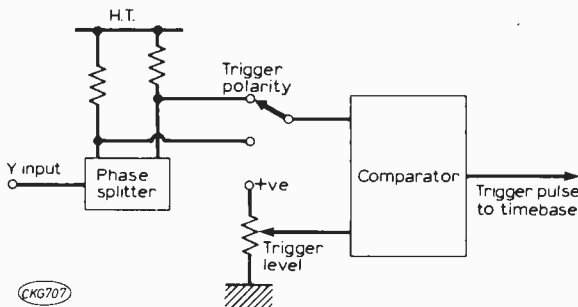


Fig. 3: Basic arrangements for a trigger amplifier

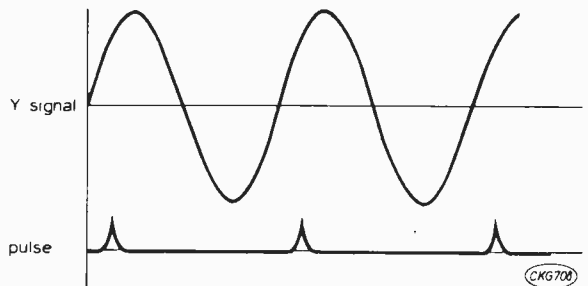


Fig. 4: Relationship between Y signal and trigger pulse

A trigger sensitivity control, "set trigger" or "stab" allows for variation of sensitivity of the bistable and when the control is fully clockwise it is usual for the bistable to "free run" with the sawtooth giving a continuous output. Any signal applied to the grid of the bistable will synchronise the timebase, rather than trigger it, and a position of the trig polarity switch usually allows for the Y signal to be fed to the grid of the bistable, rather than the normal pulse.

The bistable is also used to provide bright-up for the tube. Sync timebases require only flyback blanking but as a triggered timebase may be "waiting" for a trigger pulse the tube is normally cut off and is brightened up by a bright-up pulse occurring during the scan. Fig. 5 shows the sequence of events as a time graph. Note that the bistable takes slightly longer than does the ramp to revert to its initial state. The waiting time is also clearly seen.

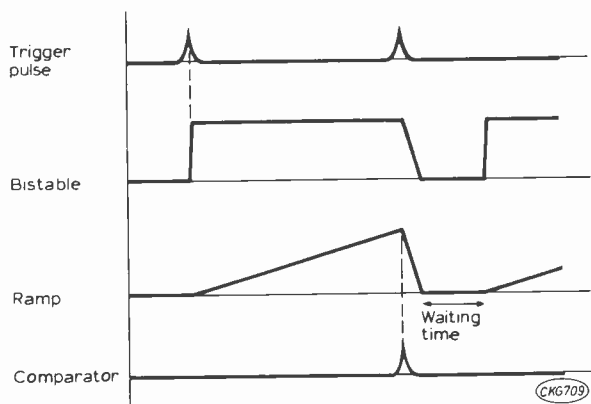



Fig. 5: Waveforms at different points in the triggered timebase

In use there are only about five controls. The sweep length control is set to the required sweep period (it can of course be much shorter than the period of the signal being viewed). There is usually a trigger polarity switch and a mode switch. This allows for triggering from very low frequencies, or very high frequencies or automatically. Oscilloscopes for TV use also have TV frame and line positions in which a sync separator is switched into the circuit. The trig level and stability controls have already been mentioned and operation of the timebase is very straightforward. Automatic triggering is used on simple waveforms as there is no need to set the trig level control. Operation is thus simplified.


The mode switch is set to that which seems most suitable and the "stab" or "sensitivity" or "set trigger" control is set fully clockwise and the timebase should then free run. Backing off the "stab" control and rotating the "trig level" control should give a point at which a rock steady image is obtained. The sweep length control can then be switched to any range without any other adjustments being necessary.

DUAL TRACE PROBLEMS

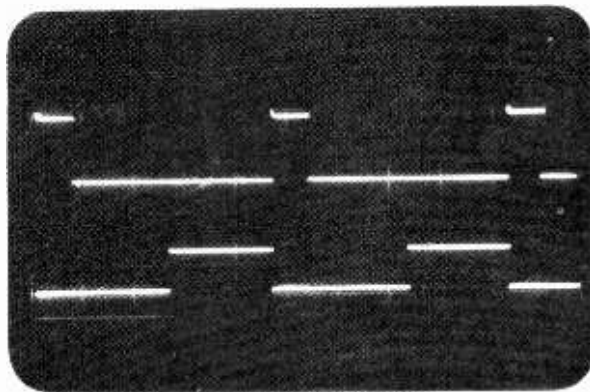
When triggering from a dual trace display (produced electronically) in the "ALT" mode it is possible to lock to one trace or the other, but not both unless they are overlapping. This can be overcome by very careful adjustment but the best way is to apply external trigger pulses from one of the signals if the loading of the trig input is not too great. Other-



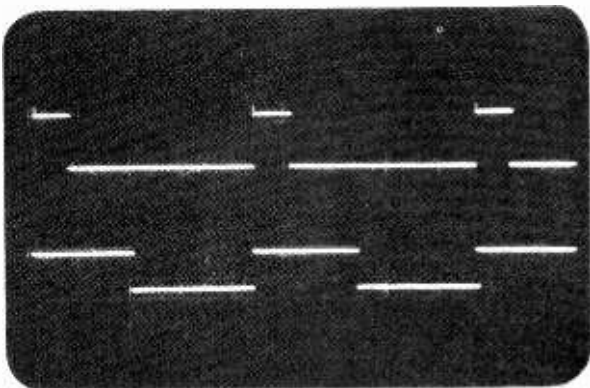The two outputs of a double pulse generator shown correctly on "ALT" with external trigger. It can be seen that the lower trace dropping to logic '0' triggers the upper trace to logic '1' . . .



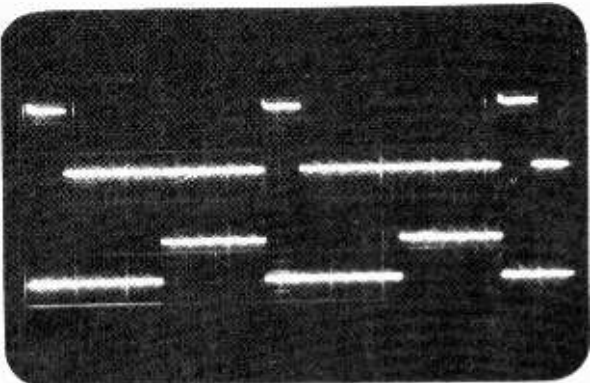The same pulse generator output on 'ALT' but with internal trigger. The two traces both lock on the positive going edge and the time relationship is meaningless




The same pulse generator displayed on 'CHOP' with internal trigger. The 'trig level' control is set so that the timebase triggers from one signal only. The timing relationship is correctly displayed. Unfortunately the sweep speed is such that switching transients upset the trace considerably

wise it will be necessary to allow some overlap and adjust the trig level control to trigger off the overlapping portion. Similar difficulties arise in the "chop" mode because the scope tends to lock to the beam switching waveform. Once again external triggering may be needed.

TIMEBASE OPERATION

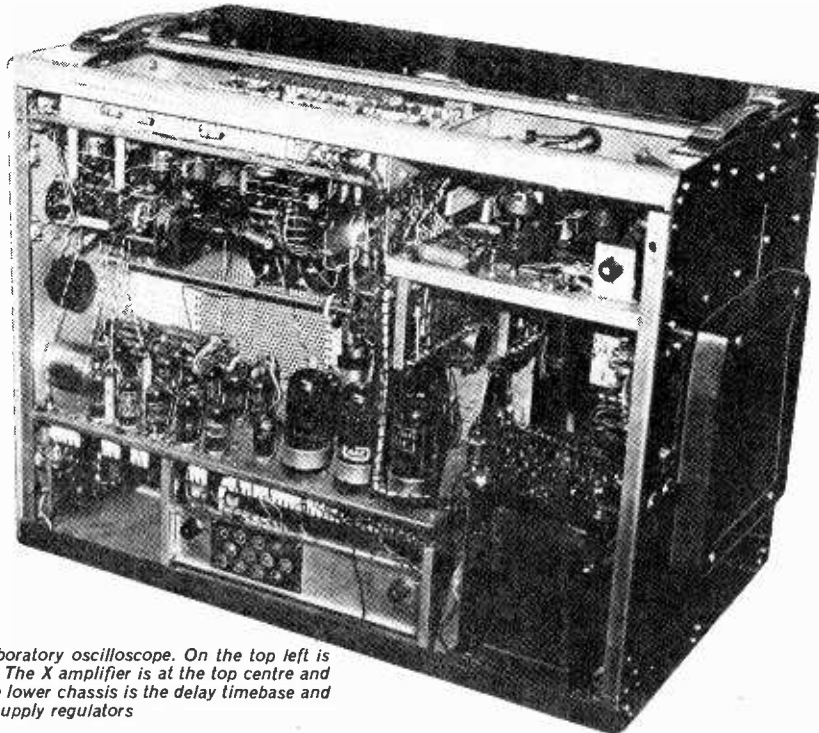Most oscilloscopes provide an external X input but it must be remembered that the bandwidth is only a few MHz except in XY oscilloscopes where the X



The timebase section of a laboratory oscilloscope. On the top left is the main timebase generator. The X amplifier is at the top centre and the EHT unit at top right. The lower chassis is the delay timebase and power supply regulators

and Y amplifiers are identical. Several oscilloscopes are provided with two timebases, one being the normal one, the second being a delay timebase. The second timebase can be identical with the main timebase or very much simpler, as in the Cossor 2000. The purpose of the delay timebase is, as its name implies, to delay the main timebase. It is triggered from the signal and starts its sweep. At a certain point the main timebase triggers from the sweep and scans the CRT. The operation of the delay timebase is shown in Fig. 6. The time of the delay is adjusted by selecting the point at which the delay trig pick-off produces a pulse.

In order to gain some idea as to the operating point of the main sweep most scopes arrange for the

delay timebase to scan the tube. Thus the triggering can be seen to be correct. No bright-up pulse (or only a small one) is produced by the delay timebase so the trace will brighten up when the main timebase runs. It is essential to ensure that the main timebase is switched to external trig and that no trig is applied so that it will only trigger off the delay pulse. As the delay pick-off control is turned the bright patch can be seen to move along the trace. When it is at the correct point the scope is switched to "main sweep delayed" and the small portion viewed. If the trace tends to jitter the main timebase controls can be set to trigger from the incoming waveform, if suitable trigger points exist. This eliminates jitter but is not such a flexible method.

APPLICATIONS

The most obvious application of these methods is in the viewing of the test pulses inserted in lines 18 and 331 of a TV picture, or to extract the colour bars from the top of the test card. The delay sweep is locked to the field of the receiver and the main sweep set to give about one scan per two lines (150 μ sec per sweep). Rotation of the delay pick-off pot will enable the user to go through the whole picture line by line. Oscilloscopes that have simple delay circuits are usually arranged to function in this manner but the trace brightness is rather poor, even when 10 or 12kV PDA is used.

Sometimes only a single sweep of the timebase is required, particularly when photographing traces. Most scopes provide for this by making the gating bistable need resetting manually to receive any more trig pulses. The single shot trigger can be provided by an external signal (camera shutter and battery), internally from a transient on the signal or by a button on the front panel. The method of operation varies greatly from one scope to another and so it would be pointless to outline any one method.

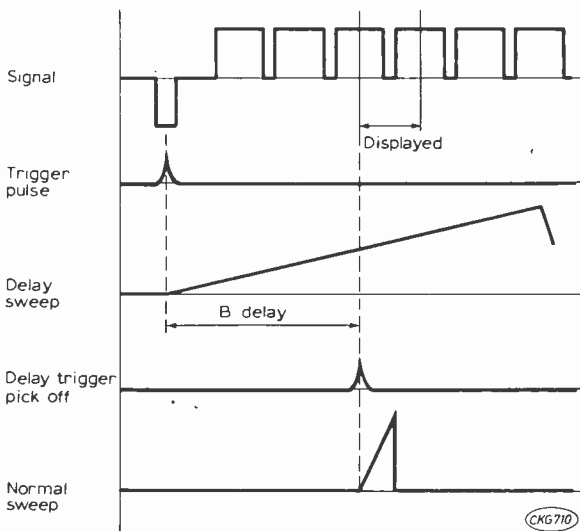


Fig. 6: Sequence of operations in a delay timebase

RESISTORS

½W & ¼W
CARBON FILM

Manufactured by AEL
to DEF 5112A

E24 Series
½W 5% 4E7 to 1M
¼W 5% 4E7 to 2M2 then 10% to 10M

As Appointed Distributors we welcome trade enquiries

Write or phone Trade Dept. W
ERITH 30737

PW Q4 PROJECT

Unit 'A' Rs, Cs, S/C's £2.10
Unit 'B' Rs, Cs, S/C's £4.87
Multi-System Decoder Extra Rs, Cs, Pots, Sw £5.51
Power Supply Rs, Cs, S/C's, T/former £3.17
PCBS (Set of 5) Fibreglass, drilled, tinned £2.60

Send S.A.E. or International Reply Coupon for Free List of other kits & PCBs for PW & PE projects, Individual component prices, and with all other enquiries.

U.K. Orders add 15p P&P and 10% V.A.T. to total (Incl. V.A.T.)
Overseas Orders P&P will be charged at cost (weights in list)
Mail Order only Write to Dept PW7

PHONOSONICS, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW

NEW from A.S.P.

also available ½ watt at 70° C Carbon film resistors E 12 range 10 Ω 2-1 M Ω 5% tol above 470 K Ω 10% tol at 97p per 100.

CASED AUTO TRANSFORMERS

240 Volt Mains to 115 Volts, smart steel-cased units coated in tough resin, fitted with power lead, fuse and 115 Volt American type socket up to 500VA, above 500VA cable entry.

VA (Watts)	Price	Post
200 ..	£5.56	£0.38
500 ..	£9.50	£0.67
1000 ..	£15.92	£0.82
2000 ..	£29.70	£1.50

20VA version uncoated, no fuse £2.52 £0.30

POWER UNIT Type A125

Supplying 6 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5 A mains plug. 2 metre output lead with 4-way multiplying giving 2.1 and 2.5 mm sockets and 3.5 mm plugs.

Price £2.25. Post 10p.



ELECTRONIC MAINS TIMER

A reliable unit ideal for timing Bathroom/Toilet Ventilators Stairway/Cloakroom Lighting etc. Gives up to 30 mins delay before switching off. Delay 1-30 mins. adjustable.

Max Load 400VA or 1000 watts resistive. Ivory Case 3½" x 3½" x 2". Fitting instructions included.

Trade Price £5.80, Post 20p.




MAINS KEYNECTOR

The safe, quick, connector for electrical appliances, 13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains, ideal for testing, demonstrating, window displays, etc.

Warning Light, interlocked to prevent connecting when live.

Trade Price: £2.95. Post 25p.

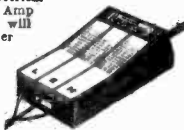

PANEL METERS 2" & 4"

Modern Wide View Face. Moving Coll. Wired for Illumination (lamps extra).

50 mA 1250 ohms
1 mA 170 ohms
VU 5050 ohms (with Detector)
Face Size 60 x 45 x 40mm (2")
110 x 82 x 48mm (4")

PRICE: 2" £2.95 4" £3.95 + POST 10p

TRANSFORMERS

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA (watts)	Ref. No.	Cased	Price	Open	Post
90	149	—	£3.74	0.38	—
100	150	—	4.18	0.52	—
200	151	£9.48	7.48	0.52	—
250	152	12.05	9.57	0.65	—
350	153	14.00	11.44	0.80	—
500	154	15.80	18.20	1.00	—
1000	155	30.70	27.40	1.20	—
2000	158	60.95	55.44	—	—
3000	159	79.53	72.49	—	—

12 & 24 Volts Prim. 200-240V.

Amps	24V	Ref. No.	Price	Post
0.3	0.15	242	1.34	0.22
0.5	0.25	111	1.84	0.22
1	0.5	213	1.59	0.22
2	1	71	2.09	0.22
4	2	18	2.75	0.38
6	3	70	3.56	0.42
8	4	108	3.96	0.52
10	5	72	4.67	0.52
12	6	116	5.07	0.52
16	8	17	6.64	0.62
20	10	115	10.23	0.69
30	15	187	13.75	0.97
40	20	232	18.28	1.00
60	30	226	22.52	1.10

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 80V.

Amps	Ref. No.	Price	Post
0.5	112	1.58	0.22
1	79	2.20	0.38
2	8	3.19	0.38
3	20	3.96	0.42
4	21	4.68	0.52
5	51	5.80	0.52
6	117	6.63	0.62
8	88	9.00	0.67
10	89	10.00	0.67

AUTO TRANSFORMERS (Open)

VA (Watts)	Ref. No.	Price	Post
20	113	£1.32	22p
75	64	£2.63	30p
150	4	£3.29	39p
200	65	£3.95	40p
300	66	£4.64	52p
500	67	£5.93	67p
1000	84	£13.50	82p
2000	95	£25.30	£1.00
3000	73	£33.00	£1.20

50 Volts

Prim. 200-240V. Sec. 10, 25, 33, 40, 50V.

Amps	Ref. No.	Price	Post
0.5	102	2.11	0.30
1	103	3.08	0.38
2	104	4.29	0.42
3	105	5.77	0.52
4	106	7.48	0.52
6	107	11.00	0.67
8	118	14.19	0.97
10	119	17.60	0.97

60 Volts

Prim. 200-240V. Sec. 24, 30, 40, 48, 60V.

Amps	Ref. No.	Price	Post
0.5	124	2.10	0.38
1	126	2.97	0.38
2	127	5.77	0.42
3	125	7.15	0.52
4	123	9.85	0.67
5	40	11.55	0.67
6	120	13.87	0.82
8	121	16.00	1.00
10	122	19.00	1.00
12	189	21.82	1.10

MINIATURE AND EQUIPMENT

Prim. 240V with screen. Volts

Sec. 1	Sec. 2	Sec. 1	Sec. 2	Ref. No.	Price	Post
3-0-3	—	200	—	238	1.23	0.10
0-6	0-6	500	500	234	1.30	0.10
0-6	0-6	1000	1000	212	1.68	0.22
0-9-9	—	100	—	13	1.23	0.10
0-9	0-9	330	330	235	1.43	0.10
0-8-9	0-8-9	500	500	207	2.28	0.22
0-8-9	0-8-9	1000	1000	208	3.08	0.30
15-0-15	—	40	—	240	1.23	0.10
0-15	0-15	200	200	236	1.30	0.10
20-0-20	—	30	—	241	1.23	0.10
0-20	0-20	150	150	237	1.30	0.10
0-15-20	0-15-20	500	500	205	2.97	0.38
0-20	0-20	300	300	214	1.70	0.22
0-20	—	3500	NO SCREEN	1116	3.00	0.40
20-12-0-12-20	—	700 (D/C)	—	221	1.55	0.30
0-15-20	0-15-20	1000	1000	206	3.80	0.38
0-15-27	0-15-27	500	500	203	3.08	0.38
0-15-27	0-15-27	1000	1000	204	3.24	0.38

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 65p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 89p	100 P.I.V. 89p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 89p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 89p

ADD 10p P & P PER ORDER



QUALITY INSTRUMENT CASE

Strongly moulded in High Gloss Grey Plastic (Flame Retardant ABS).

Two interlocking halves secured by four corner bolts (supplied).

Interior Size: 6½" x 6½" x 2½".

Wall Thickness: ¼"

Weight: 1½ ozs.

Price: £1.50, Post 16p.



PLEASE ADD 10% FOR V.A.T.

A.S.P. LTD. BYRE HOUSE, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: Canterbury (0227) 52436

CALIBRATION

Calibration of a timebase is relatively easy providing a good marker generator is available. However for those who have not got a high accuracy generator a few useful time periods are listed below.

TV frame period	20ms
Main period	·20ms
Line period (405)	98·8μs
Line period (625)	64μs
Radio 2 (1500m/200kHz)	5μs

The gain of the output stage is set so that rotation of the calibration shift moves the spot the required distance. The sweep speeds are then set using a calibrated pulse generator and the sweep speed adjusted so that a rotation of the calibrated shift moves the correct number of markers past a point on the graticule. Calibration is easily achieved to 5% and better is possible. It is perhaps interesting to note that the timebase velocity is given in time/cm, not cm/sec as would be expected. It seems to mean more the first way, which, perhaps, is why it has been retained for so long. At high sweep speeds non-linearity of the trace becomes evident due to bandwidth limitations and often capacitors are provided to linearise the faster ranges, using a high frequency sine wave as the display. General non-linearity of the output stage does not affect calibration of the calibrated shift, but non-linearity arising from bandwidth limitations does cause accuracy to suffer.

To be continued

TELEVISION & PRACTICAL WIRELESS DOUBLE SCOOP

YOU CAN RUN YOUR OWN "WORLD-CUP" SOCCER OR "OPEN TENNIS" CHAMPIONSHIPS.
BUILD THE


TV FOOTBALL GAME

Suitable for colour or monochrome television sets.

Simulate the green football pitch, red and blue players, pink touch-line. See the ball kicked hard or soft across the pitch. Move your players to any position on the screen. Simple to operate joystick control.

This project will appear in **TELEVISION** only, starting in the July issue. Not to be confused with **TELE-TENNIS**, another TV game project appearing in **PRACTICAL WIRELESS**.
Ideal for fund raising events.

PW TECHNICAL PUZZLE No. 5

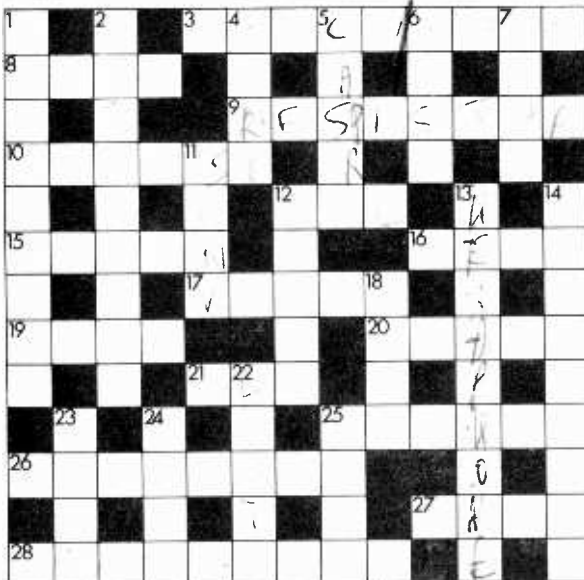

ACROSS

- 3 Permanent method for a good set! (5, 4)
- 8 Lamp worked round open terminal? (4)
- 9 Opponent of current circuits? (8)
- 10 Not conscious of such signals? (6)
- 12 Shortage of a dial system? (3)
- 15 Reduces the volume of gale-warnings? (5)
- 16 Drama Marconi's Mum got into? (4)
- 17 Gives some sort of reception! (5)
- 19 Swearing about a hot switch? (4)
- 20 Winners run through such recordings? (5)
- 21 Member needed over the gramophone? (8)
- 25 Sound on ears inwardly disconnected! (6)
- 26 They're driven from the TV chairs! (3, 5)
- 27 & 1 Down Currently going through with impure stuff? (4, 9)
- 28 Handy army alternative to radio (9)

DOWN

- 1 See 27 Across
- 2 A bouncer needed for TV reception? (9)
- 4 Sir, a twist to correct distorted melodies! (4)
- 5 Where to find a radio part on the map? (5)
- 6 Buzzer used to jam? (4)
- 7 Old sound transmitter with strings? (4)
- 11 Metal dish for a separator network? (4)
- 12 Waste amps with non-electric radio involved? (5)
- 13 They're designed for individual listeners (9)
- 14 Press television to cover these? (4, 5)
- 18 Knock-out in wireless tuning! (4)
- 22 Range of arc he got into a transformer (5)
- 23 Appendage of sound equipment (4)
- 24 Broken bit of a signal from the continent (4)
- 25 Final receiver of what the employer makes (4)

FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH

PRODUCTION LINES

colin riches

SINCLAIR "SCIENTIFIC"

Sinclair, announce that they are marketing a 12-function, scientific pocket calculator at a recommended retail price of £49 plus VAT. The "Sinclair Scientific" is identical in size to the "Cambridge" model (reviewed Nov. 1973)—measuring only $4\frac{1}{2} \times 2 \times \frac{3}{8}$ ins. deep and weighing just $3\frac{1}{2}$ ozs.

It features an 'upper' and 'lower' case operation allowing all 12 functions to be obtained using only four function keys.


Apart from the basic four (+ - × ÷) operator keys the "Scientific" incorporates the following additional functions: logarithms to base 10, antilogarithms, sine, cosine, tangent, arcSine, arcCosine and arcTangent. These enable rapid squaring, doubling and x' including square and other roots. Post fixed operators give full flow calculation facility on all functions.

Entry and result are in scientific notation with a signed 5 digit mantissa and a signed 2 digit exponent giving the "Scientific" a capacity for very large or very small numbers from 10^{-99} to 10^{99} .

Sinclair has managed to pack these features into a tiny chip less than $\frac{1}{5}$ in. square. This results from the use of a new set of algorithms for the transcendental functions devised by Clive Sinclair, managing director, and by special programming techniques used by Dr. Nigel Searle who is also a director of the company.

The calculator is powered by four standard Mallory batteries giving around 20 hours of continuous use. Guarantee is one year. —Sinclair Radionics Limited, London Road, St. Ives Huntingdonshire PE17 4HJ. Telephone St Ives (04806) 4311

THE "SECUREYE"

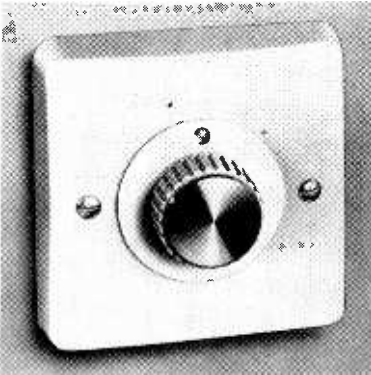

Here's a useful little device—it's a light dimmer (up to 500W) and a photo-electrically operated switch. In addition it serves as a normal on/off switch when required.

It is an immediate replacement for most existing flush-mounted wall switches and takes only a minute or two to fix.

There is a hole in the flange at the base of the control knob. This acts as a pointer so that when the "light level" switch function is required, this is rotated until the hole uncovers the "magic eye".

This very versatile unit has a myriad of uses, the first one coming to mind being that of house security. With a Secureye, you can be away on holiday for a fortnight but because your house lights are automatically switched on and off, would-be burglars would think twice before "doing a job".

Price is £5.60 plus VAT. *Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex.*


STORAGE BOX

I'm afraid I'm one of those constructors who keeps all his components in odd tins, jars and plastic aerosol can lids and gets in a muddle whenever he wants to find a 56kΩ resistor in a hurry.

Well Protocraft Products Ltd., seem to have come up with the answer to my problem, for they have introduced a neat 4-drawer storage cabinet. Overall size is $14\frac{1}{2} \times 11\frac{3}{8} \times 9\frac{1}{2}$ ins. It's made from plywood and has a satin-white exterior. Drawer fronts are solid beech.

Also available is a matching cupboard and an open unit. They can all be interlocked to form a stacked group arrangement.

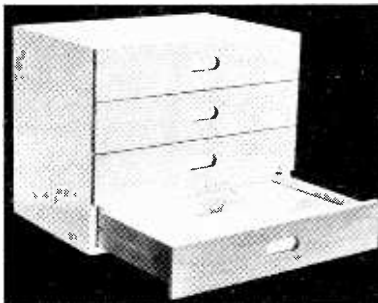The firm supply plastic divider trays and 35mm photographic slide racks taking 180 slides per drawer. These are extras and prices may be obtained from Protocraft.



Rec. prices are: £12.65 for the drawer unit (illustrated) £8.23 for the cupboard and £5.87 for the open unit.

Further gen. from *Protocraft Products Ltd., 3 Blatchford Road, Horsham, Sussex, RH13 5QR.*

P.C. TRANSFERS

Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all drilling positions automatically marked.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes—i.e. edge connectors, lines, pads, dual in line I.C.'s,

8-10-12. T.O.5 Cans, 3-4 lead transistors, etc, etc, which only require pressing into the required positions on the p.c. board before etching.

The complete system including post and VAT £2.00. Individual sheets 22p. Sample sheet 22p. Copper laminate (boards) size $6 \times 4\frac{1}{2}$ in. 6 sheets 50p.

E. R. Nicholls, 46 Lowfield Road, Stockport, Cheshire.



MAPLIN ELECTRONIC SUPPLIES


★ SAME DAY SERVICE



LARGE or SMALL Centurion

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

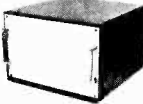Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white.



Model 120			
Dimensions in inches.	W	H	D
Model 120	8	2 1/2	6
220	8	6	3 1/2
221	8	6	6
320	12	8	12

Chassis for model 320 £2.14 extra.

Please send s.a.e. for fully illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

- ★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE 1k. master oscillator.
- ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up for other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra.
- ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3 7/16" x 4 5/16". ★ Very low power consumption.

★ EXTREMELY ECONOMICAL. ★ S.a.e. please PRICE. ★ Ready built, tested for full technical and fully guaranteed. ★ Details. DMO2T (with tremulant) ONLY £14.25. Trade enquiries welcome.

DMO2 (without tremulant) £12.25. SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

MAPLIN: Projected side of London's third airport.

TRANSISTORS, DIODES & IC's.

AC127	25p	BF194	15p	0A90	7p
AC128	20p	BFY51	22p	0A91	6p
AC176	17p	MPF102	36p	1N914	4p
AD149	47p			1N4148	4p
AD161/2	72p	OC44	20p	1N4001	6p
BC107	10p	OC71	20p	1N4002	6 1/2p
BC108	10p	TS43	28p	1N4003	7p
BC109	13p	2N1711	24p	1N4004	7 1/2p
BC147	10p	2N2219	25p	1N4005	8p
BC148	10p	2N2946	45p	1N4006	8 1/2p
BC149	12p	2N2905	33p	1N4007	8p
BC168	13p	2N2907	25p	W005	30p
BC169C	12p	2N29260	10p	W04	33p
BC182L	10p	2N2926Y	10p	741C 8-pin	
BC204	14p	2N3053	18p	D.I.L.	36p
BC209C	14p	2N3055	49p	741C 14-pin	
BD131	45p	2N3819	30p	D.I.L.	45p
BD132	54p	AA119	7p	D.I.L. Sockets	
BD133/2	£1.20	BY127	16p	8-pin	20p
BD135	36p	BY184	58p	14-pin	15p

See our catalogue for our full range of transistors. 74 series I.C.'s bridges etc.

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1.5 63 6p	68	6.3 6p	6p
1.5 63 8p	68	16 6p	6p
2.2 63 6p	68	63 10p	6p
3.3 63 6p	100	4 6p	6p
4.7 63 6p	100	10 6p	6p
6.8 40 6p	100	25 6p	470
6.8 63 6p	100	40 6p	470
10 25 6p	100	63 12p	470
10 43 6p	150	6.3 8p	680
15 16 6p	160	16 6p	680
15 40 6p	160	25 6p	680
15 63 6p	160	40 10p	680
22 10 6p	150	63 12p	1000
22 25 6p	220	4 6p	1000
22 63 6p	220	10 6p	1000
33 6.3 6p	220	16 6p	1000
33 16 6p	220	25 10p	1500
33 40 6p	220	40 12p	1500
37 4 6p	220	63 18p	1600
47 10 6p	330	4 6p	2200
47 25 6p	330	10 6p	2200
47 40 6p	330	16 10p	3300
47 63 6p	330	63 22p	4700

PLUGS AND SOCKETS



- DIN PLUGS**
 - 2 pin (1 flat) 8p
 - 3 pin 9p
 - 4 pin, 5 pin A line socket. Per (180°), 5 pin B pair 28p
 - (240°), 6 pin 10p
- MAINS**
 - P360 3 pin 1.5A chassis plug with 4 pin, 5 pin A line socket. Per (180°), 5 pin B pair 28p
 - SA 2190 3 pin 5A chassis plug 20p
 - SA 1862 line socket for above 23p
- RSH 8 way chassis socket** 82p
- PHONO**
 - Plug plastic 5p
 - Plug screened 12p
 - Chassis socket 4p
- JACK**
 - Std. 1" mono plug 13p
 - Std. 1" mono plug 3.5mm. plug plastic screened 15p
 - 21p
- STEREO**
 - Std. 1" stereo plug Plastic 18p
 - Screened 30p
 - Open mono socket 1" 10p
 - Moulded mono socket 1" with 2 break contacts 14p
 - Moulded stereo socket 1" with 3 break contacts 18p
 - 3.5mm. plug plastic screened 15p
 - open socket 8p.
- MCMURDO**
 - RF8 8 way chassis plug 47p

WE KNOW YOU NEED IT!



The MES 1974 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system, EXCITED by our BIG VALUE discount vouchers, STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send 10p 25p for our beautifully produced catalogue and leave the rest to us!

POTENTIOMETERS

Retary miniature carbon track 1" spindle Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 14p



- Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 44p.**
- Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 28p**
- PRESETS**
 - Sub-miniature 0.1W Vert or Horiz 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p

OMNIUM GATHERUM

- PP3, 6 etc. battery clip dual min. 9p
- PP1, 9 etc. battery clip separate per pair 6p
- Pair crocodile clips 1 red, 1 black insulated sleeve. 10p
- Solder Multicores 22swg 10 metres 20p
- Silicone grease in special dispensing 20ml. 43p
- Red neon 240V panel mounting 25p
- Lacing Cord Strong rayon cored PVC 25m. 51p
- Panel fuse holders 20mm 20p; 14" 35p
- Transformers**
 - LT700 min. output transformer Pri. 1.2k Ω Sec. 5 Ω 200mW 50p
 - Sub-min. Mains Transformer 6-0-6V 100mA 95p
 - 12-0-12V 50mA 95p
 - Size: Both approx. 30 x 27 x 25mm.
 - Min. Mains Transformer (Size: 46 x 31 x 38mm) 0-12V 250mA, 0-12V 250mA £1.88
 - Mains transformer MT3AT Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A £3.31
 - Mains Transformer MT206AT Pri. 200-220-240V, Sec. 0-15-20V 1A £3.98
 - 0-15-20V 1A
- Also in stock: Wide range of brass and nylon nuts, bolts and washers + solder tags, shakeproof washers etc.

LINEARS

- CA3046 89p
 - LH0042C. TO99 (TO5), FET 1/p Op Amp £4.25p
 - LM301A. 8-pin DIL Op Amp 50p
 - MC1395L. 14-pin DIL Stereo Preamplifier £1.38p
 - MC1310P. 14-pin DIL FM Stereo Decoder (no coils, needed) £3.15p
 - MFC6040. electronic attenuator 95p
 - MFC8010. 8-pin base. 1W Audio Power Amp £1.37p
 - MFC4000B 1/2 watt Audio Amp 38p
 - NE355V. 8-pin DIL Precision Timer 79p
 - NE6511C. 16-pin DIL Phase Locked Loop £4.48p
 - SG3402N Amplifier/Multiplier £1.68p
 - SG1495D. 14-pin DIL Four Quadrant Analogue Multiplier £2.70p
 - µA723C. TO99 (TO5), 2 to 37V Voltage Regulator 80p
 - µA723C. 14-pin DIL, 2 to 37V Voltage Regulator 80p
 - µA741C. 8-pin DIL Op Amp 45p
 - µA741C. 14-pin DIL Op Amp 45p
 - µA747C. 14-pin DIL Dual Op Amp £1.05p
 - µA748C. 8-pin DIL Op Amp 38p
 - ZN414. TO5. TRF Radio £1.20p
- Full data, pin connexions, etc., on nearly all types listed in our catalogue. Price 25p

RESISTORS

- Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12 1p
- Carbon Film 1/4W 5% 1Ω to 100; 10% 1.2M to 10M E12 1p
- Carbon Film 1/4W 5% 11Ω to 910k E12 A E24 1p
- Carbon Film 1W 5% 10Ω to 10M E12 3p
- Carbon Film 1W 5% 10Ω to 10M E12 A E24 4p
- Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms E12 12p
- Wirewound 2 1/2W 5% 1ohm to 27ohms E12 12p
- E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

SWITCHES

- Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 32p.
- Mains rotary DPST 250V 2A 20p.
- Slide Sub-miniature DPDT 9p
- Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl. toggle) 3A 70p
- Toggle 250V 1.5A with ON/OFF plate 25p.

VAT Please add 10% to the final total.

Post & packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. PHONE SOUTHDEN (0702) 44101

NO EXTRAS
ALL PRICES INC. VAT
FREE! P. & P.

AMPLIFIERS

Keltron
KSA 1000 10+10 watt Mk. II 25-95
KSA 1500 15+15 watt Mk. II 29-95
Tripletone
Hi-Fi 77 7+7 watt Mk. II 35 00
Hi-Fi 1818 18+18 watt Mk. II 39 95
Teleton SAQ307 8+8 watt 27 00
Rotel RA 211 37 00
Rotel Tuner/Amp. RX150A 59 00
SANSUI models in stock.

RECORD DECKS

Garrard SP25 Mk. IV 11 00
BSR MP60/GX6H 11 00
Connoisseur BB1 Kit 11 00
HD2 Chassis 29 50
SAUZ Pick-up Arm 12 25
SCU1 Cartridge 4 95

RECORD DECK PACKAGES

SP25 Mk. II. in Plinth & Cover 219 95
SP25 Mk. IV/G600 P. & C. 20 95
Plinth & Cover for Garrard SP25/2025TC 3 95

SPEAKER BARGAINS

EMI 13" x 8" 3, 8 or 15 ohm
Plain 2 15
with Co-Axial Tweeter 2 30
Twin Tweeter 9 95
Type 350 8 ohm or 15 ohm, 20 watt
6 1/2" 8 ohm, 10 watt 2 65
8" 8 ohm, 10 watt 3 90
12" 8 ohm, 20 watt 5 75
8" x 5" C/Mag. 5 watt 1 40
8" x 5" Dualcone 8 ohm 2 70

FANE 7" x 4" 3 or 8 ohm 1 15
CELESTION 8" 15 ohm 1 75
ADASTRA 10" 8 or 15 ohm, 10 watt 3 25
BAKER GROUP 25
12" 8 or 15 ohm, 25 watt 7 75
8" 8 ohm, 5 watt C/Mag. 95
2 1/2" 8 ohm or 64 ohm 80
ELAC 8" 8ohm Dualcone 2 35
10" 8ohm Dualcone, 10 watt 3 45
SELECTION OF GOODMAN AND
WEARDALE SPEAKERS ALSO
AVAILABLE.

KIT FORM CABINETS-TEAK VENEER

12 x 12 x 6 with 8", 8" x 8", or 6 1/2" and 3 1/2" cutout 2 75
17 x 10 x 9 with 8" or 13" x 8" cutout 3 95
18 x 11 x 9 with 13" x 8" cutout for EMI 350 4 60

TWEETER & CROSSOVER

EMI 3 1/2" 3 or 8 ohm C/Mag. 1 10
Cone Tweeter 8 or 15 ohm, 10 watt 2 50
Cone Tweeter 8 ohm, 3 watt 1 60
Horn Tweeter 8 ohm, 20 watt 5 95
Dome Tweeter 8 ohm, 30 watt 4 95
Crossovers CN2 (3 ohm), CN28 (8 ohm), CN218 (16 ohm) 1 15

CARTRIDGES

ACOS GP91/25C or GP91/38C Stereo comp. 1 05
GP93/1 Stereo crys. 1 35
GP94/1 Stereo crys. 1 75
GP95/1 1 35
GP96/1 1 75
GP101 75
GP104 1 65

SONOTONE

9TAHC Stereo ceramic, diam. 1 80
9TAHC/G Slim fit, stereo crys. diam. 1 80
19-T1 Stereo crystal 85
BSR SC5M Stereo ceramic 2 75

SX6H Stereo crystal 1 80
GX6M Stereo crystal 1 80
X6H Mono/stereo 1 50
X6M Mono/stereo 1 50
GOLDRING G800 8 85
G800 2 95
G800 7 50
AUDIO Tecnica AT-55 1 75

STYLII For Above Cartridges

Sapphire 30
D. Diamond 1 25
GOLDRING G800 G850 1 95
G800E 3 95

MICROPHONES

CM70 Planet stick metal, switch crystal 1 70
DM160 Dynamic omi-dir, ball metal 4 00
UD130 50K/800 ohm, uni-dir, ball metal 5 65
TW209 5 90
CONDENSER MIKE 600 ohm, uni-dir. 9 85

Cassette STICK MIKE with R. Control on/off switch (2.5 & 3.5 mm J/Ply).

1 60
MIKE MIXERS Mono 4 10
Mono/stereo de luxe 5 50

CASSETTES

Type	Low noise	Phll. lips	Mem. orex	Am. pex
C45			60p	45p
C60	85p	50p	65p	55p
C90	45p	65p	75p	75p
C120	55p	105p	110p	110p

Cassette Head Cleaner 45
BIB Stereo Test Cassette 1 65
AMPEX Head Cleaner De-magnetiser 1 65
PLASTIC LIBRARY CASES for 5" Reels 20p, 5 1/2" Reels 25p, 7" Reels 50p, CASSETTE CASES 1 2p
TAPES 8std. L.P. D.P.
5" 55p 85p 80p
6" 85p 75p 1 00
7" 80p 1 05 1 40



Credit Terms for Callers

SPECIAL OFFER

Unrepeatable!

De-Luxe Cassette Recorder/Main/Battery, Portable, Remote Control Mike etc.
Fantastic Value at £14.95 all inclusive.

WORTH DOUBLE

AKAI TAPE DECK

4000DS Tape 95 50
GXC36D Cassette 83 00

HEADPHONES

AMSTRAD HP85A 4
ROTEL 430 4 90
490 6 20
700 8 95
AKAI ASE 115 5 75
ASE 20 7 95
KOSS K711 (Black or Red) 9 95
K6 11 95
K6LC (with Vol. control) 13 25
K0727B 15 75
K0747 15 55
HVI 15 50
PRO4AA 26 90
PRO6LC 28 75
ESP6 42 75

LEESSON ELECTROSTATIC

Mono/stereo super de luxe 8-16Ω 15 50
Headphone Adaptor 2 75
Curly Ex, Leaf 201t, 2 80
1 10

IN-CAR ENTERTAINMENT SECTION

Car Cassette Stereo Player and Two Speakers 20 95
Car 8-track Stereo Player and Two Speakers 16 50
Pair of Car Stereo Speakers 8 85
Pair of Car Stereo Speakers (Door Mounting) 8 95

NEWMART ELECTRONICS

ALL MERCHANDISE FULLY GUARANTEED

MAIL ORDER DEPT. (PW/7)

**BELMONT STREET
MONTON, ECCLES
MANCHESTER**

Tel. 061-789 5268

PERSONAL CALLERS WELCOME

Manchester 30-32 Shudehill 061-832 7710
Liverpool 15 Whitechapel 051-236 0738
Leeds 4 New Market St. 0532 42708

BETTER GET 'SET'

FAMOUS NO. 19 SET TRANS/RECEIVER

TR50/51 2-8 MHZ in 2 bands. 11 valve. 80T PA Power reqs 12VLT 275-VHT REC 500VTM. Rebuilt £12 50, Carr. £1.

Complete station 12 VDC PSU. Mic. Cables £23 50, Carr. £2 50.

TR55 VHF 60-90 MH 2S XTAL 3C

3 channel 12 valve super Het. 12 VDC Sync Internal Supply, size 14" x 12" x 7" as new £16 50 Carr. £1 25.



TE76/CT52
A superb Miniature Oscilloscope £25, Carr. £1 50. Mains operation.

RE102 42/MAST
12-3" 6" x 2" sections WIRE GUYS STRAINERS in carry holdall £23 50 Carr. £2.

AERIAL RODS
3' x 1" screwed M & F ends 10 £2 Post 75p. 25 £5 c.p.

AE101. Telescopic mast antenna £3 75. Carr. £1 25 List 25p refundable with purchase.

XTAL CALIBRATOR
No. 10
1/2 10MHZ Harmonics 30 MHZ £3 Post 50p.

No. 62 RC/TM 1.5-10MHz £15 Carr. £2. VAT 10% Price & Carr. (included)

Surplus Electronic Trading
P.Q. BOX No. 19, HITCHIN, HERTS. SG4 8TN

EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data. 10 boards 50p (12p)
25 boards for £1 (30p)

Dural extruded heatsinks outline 10D black anodised. Drilled for 4 x TO3 transistors. 5 x 4 x 1 1/2" 40p (14p)
Similar to above but 5 x 8 x 1 1/2" drilled for 8 x TO3 70p (26p)

COMPUTER GRADE ELECTROLYTICS

12,000µ 100v, 5 x 2 1/2 dia £1 (25p)
30,000µ 25v 65p (20p)

ELECTROLYTICS


4,000µ 70v, 3,600µ 40v, 4 1/2 x 2 in dia 55p (14p)
10,000µ 35v, 5,000µ 35v, 4 1/2 x 2 in 40p (12p)

100 piv 20A, Si diodes 4 for £1 (10p)
100 piv 3A, Si diodes 4 for 50p (7p)
250 mixed resistors 60p (9 1/2p)
250 mixed capacitors 60p (9 1/2p)
200 Si planar diodes 50p (7p)
Min. glass neons 8 for 50p (7p)
Reed relays mixed 10 for 50p (7p)
Micro switches 8 for 50p (9p)
Papst extractor/blower fans 100 c.f.m. 4 1/2 x 4 1/2 x 2in £3 50 (28p)
QH bulbs 12v 55w 50p (6p)

Postage and package shown in brackets.
ADD 10% VAT to TOTAL

KEYTRONICS
(Mail Order only)
**44 EARLS COURT ROAD
LONDON W8. 01-478 8499**

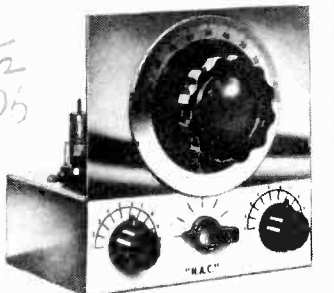
H.A.C. SHORT-WAVE KITS
WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1974 "DX" RECEIVER
Complete kit—Price £4 30 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valve!"
This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits & components. Test Report available.
EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

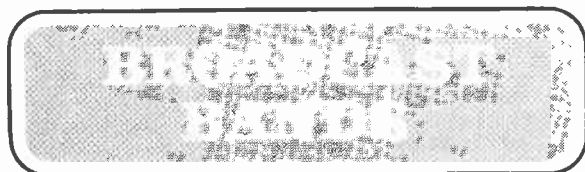"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX No. 16, EAST GRINSTEAD, SUSSEX RH19 3SN



SHORT WAVE DX by MALCOLM CONNAH

RADIO New Zealand has been heard by our reader **John Godwin** of Rugeley in Staffordshire. John says this in a letter which arrived just too late for inclusion in the last article.

He reports that the best frequency for reception is 11780kHz; he hears the station just after he gets up in the morning (about 0715 GMT) until about 0800 GMT. John suggests the following method of locating the station: First he looks for Radio Australia on the 25 metre band; the strength of this signal being a good pointer to the possibility of receiving New Zealand; then he tunes very carefully up in frequency, about 20kHz, to find Radio New Zealand.

The equipment used was a pre-war HRO and a Joystick antenna. John reports March as being the best month for reception so we will probably have to wait until next year for another chance to hear this elusive station.

Readers' Logs

Strangely enough the first report for this month also includes a logging of New Zealand. The report in question comes from **A. McIntee** of Angus in Scotland who used a 120 foot long-wire antenna with a choice of three receivers; Philips 7 transistor, Codar Multi-band 6, Homebrew crystal set with transistor amplifier; to hear the following:

- 4985 R. Kiev noted at 1950.
- 6020 R. Kiev noted at 1930.
- 6180 BBC relay Cyprus on at 1900.
- 7215 AIR, Delhi noted at 1918.
- 11780 R. New Zealand noted at 0700.

Trevor Enefer of Cleethorpes has been concentrating on the lower frequency bands where his Lafayette HA600 and 50 foot end-fed antenna produced the following results:

- 3250 SABC, South Africa in English at 2315.
- 4820 HRVC, Honduras in English at 0330.
- 4820 R. Gambia in English at 2300.
- 4832 R. Reloj, Costa Rica noted at 0140.
- 4845 R. Fides, Bolivia. Ident. at 2235.
- 4845 R. Bucaramanga, Colombia noted at 0340.
- 4875 SABC, South Africa in Afrikaans at 0400.

- 4880 R. Universo, Venezuela noted at 03555.
- 4885 Ondas del Meta, Colombia at 0400.
- 4972 5 R. Cameroon, Ident. in French at 2215.
- 4980 Ejura, Ghana in English at 2245.
- 4990 R. Nigeria, S/off in English at 2305.
- 5038 R. diff. Nationale Centrafricaine at 2205.
- 5047 R. diff. du Togo, Ident. in French at 2255.
- 6000 R. Inconfidencia, Brazil noted at 0130.
- 6006 R. Reloj, Costa Rica noted at 0140.

Paul Broadhurst of Clevedon in the new county of Avon has added a Codar PR40 preselector to his Trio 9R-59DS, this set-up plus a 150 foot long-wire and two half wave dipoles produced the following:

- 6050 RAI, Italy with S/on at 2030.
- 6065 R. Sweden with S/on at 1600.
- 6160 WYFR, Family Radio noted at 2250.
- 6165 R. Kiev noted at 1945.
- 9545 Radio Accra, Ghana noted at 2215.
- 9550 R. Finland noted at 2046.
- 9735 VOA, Monrovia, Liberia at 2120.
- 9745 Radio Baghdad, Iraq noted at 2200.
- 11765 Radio Australia noted at 0800.
- 11880 Voice of Turkey, S/on at 2200.
- 15120 Voice of Nigeria noted at 1620.
- 15140 Radio Havana, Cuba noted at 2030.
- 15185 WINB, Red Lion noted at 2115.
- 15275 TWR, Bonaire at 2140.
- 15300 HCJB, Quito, Ecuador noted at 2010.
- 15325 Radio Canada International at 2100.

Stephen Fletcher of Bromsgrove, Worcestershire has a homebrew Heathkit SW717 with a 60 foot end-fed and a 150 wire in the loft. A Grundig Yacht Boy with internal 4 foot telescopic was also available during the compilation of the log:

- 6080 HCJB, Quito, Ecuador in English at 0930.
- 6130 R. Norway, news in Norwegian at 1100.
- 6160 R. Australia in English at 1459.
- 9525 RSA, South Africa in English 2253.
- 9670 Adventist World Radio, Portugal at 0845.
- 9770 VOA relay in Greece, English at 0729.
- 11740 R. Nederland via Malagasy relay at 1909.
- 11860 BBC, Ascencion Is. relay in English at 0730.
- 15012 Voice of Vietnam, news in English at 2124.
- 15165 R. Denmark in Danish at 1158.
- 15410 United Nations Radio at 1800.
- 15415 R. Kuwait in English at 1735.
- 17830 R. Pakistan in English at 0735.

The final report for this month comes from **Albert E. Ord** of South Shields who used his Trio 9R-59DS with a Joystick and Hamgear Preselector to hear:

- 4975 R. San Topez, Peru in Spanish at 0200.
- 4990 R. Barquisimeto, Ven. in Sp. at 0130.
- 7235 R. Australia noted at 2115.
- 11670 R. Pakistan in Hindu at 1315.
- 15185 R. Finland in English at 2030.
- 21520 RSA, South Africa in English at 1030.

MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

INDEPENDENT Local Radio came to Manchester on April 2nd when Piccadilly Radio appeared on 1151kHz (261m) medium waves and 97MHz v.h.f. A press notice from IBA gives details of the medium wave outlet which is located at Ashton Moss, three miles south of Oldham. A directional aerial consisting of four 235ft masts beams an effective radiated power of 4kW towards Manchester and away from Glasgow, Birmingham and London where the same frequency is allotted to independent local radio. Programmes from Manchester are on the air daily from 0500hrs (0600hrs on Sunday) until 0200hrs.

Roy Patrick (Derby) has been listening to Africa on the medium and long waves with his National 1400 receiver. Three Algerians were heard—Tipaza on 252kHz (1195m) in French during the daytime; Ain Beida on 533kHz and Cran on 548kHz, both in Arabic. From West Africa, Dakar in Senegal was logged on 746kHz at 2325hrs and Conakry, Guinea on 1403kHz after 2300hrs. Roy reports hearing the BBC Eastern Mediterranean relay station in Cyprus relaying the BBC World Service on 1322kHz at 2300hrs GMT. A number of medium wave outlets in Africa are audible in this country after dark. On the long waves listen on 209kHz (1435m) for Arabic music from Azilal in Morocco while on the medium waves Bissau, Portuguese Guinea on 1070kHz can be heard after 2300hrs GMT, usually with pop music. Others to look for are:— Tenerife, Canary Islands in Spanish on 620kHz; Djedeida, Tunisia on 629kHz; El Gawarsha, Libya on 674kHz; Radio Kinshasa, Zaire on 629kHz; Radio Algiers on 890kHz; Tunis on

962kHz; Algiers on 980kHz; El Peida, Libya on 1124kHz and Radio Tangiers on 1232kHz.

Local Radio enthusiast **Stephen Fletcher** (Bromsgrove, Worcs) reports hearing BBC Radio Derby on 1115kHz; BBC Radio Oxford on 1484kHz and BBC Radio Bristol on 1546kHz, using his Grundig Yacht Boy portable receiver. Roy Patrick has heard Radio Clyde on 1151kHz after the close down of Radio Birmingham which operates on the same channel. Local radio is now well established on the medium waves with BBC stations operating on 755kHz (397m); 854kHz (351m); 998kHz (301m); 1034kHz (290m); 1106kHz (271m); 1115kHz (269m); 1457kHz (206m); 1484kHz (202m); 1502kHz (199m); 1520kHz (197m); 1546kHz (194m) and 1594kHz (188m). IBA stations are found on 557kHz (538m); 719kHz (417m).

Ioan ab Elfed (Worcester) is a recent 'convert' to the medium waves. He has built a MW loop aerial and he would now like to join a DX club that caters for the MW Dxer as well as the short wave enthusiast. The World Wide DX Club, Postfach 1263, D-6380 Bad Homburg, West Germany has a useful medium wave section in its monthly DX Magazine and the Danish SW Club International, DK-8382 Hinnerup, Denmark publishes Short Wave News monthly which caters adequately for DXers with an interest in the long and medium wave bands. Each club has a large international membership and their bulletins are printed in English.

Robert Bonsall (Buxton) would like information about an aerial suitable for MW Dxing. The MW loop is the aerial favoured by the majority of medium wave DXers. An article giving constructional details appeared in the April 1973 *Practical Wireless*.

VHF/FM DXING

by SIMON DAVID

ONE of the aspects of f.m. DXing is that you may be lucky to get a long distance transmission (or "skip" as it is called) for about ten minutes, then never hear it again. It could quite easily come in on what seems to be the wrong frequency. For example it has been known for "communist bloc" countries, who normally broadcast sound only in the 70MHz region and television sound in the 85 to 92MHz and 93 to 100MHz bands, to break through with short skips into the UK, although it is rare. However, the GDR uses the same f.m. band as the UK and should not be confused with Poland and Hungary who are on the 66 to 72MHz band.

For the readers who have reported to me of frustrated attempts, my advice is don't give up. Earlier advice on aerials and the use of modern highly sensitive receivers will help you. If the "local" station only about 100 miles away seems tame to you, it is a start and with perseverance you will improve. If you run a portable, as so many do, take it up to some high open ground, such as the hills in Wales, Sussex, the Midlands, and Yorkshire. Take some sort of portable three- or four-element aerial that you can rig up temporarily on a telescopic mast.

It is amazing how many people will happily pay £25 to £30 for a tuner or receiver and begrudge £7 or £8 for a good aerial. Without it you cannot expect reliable results, especially if you want stereo.

A useful tip comes from **David Jack** of Bolton who has been DXing from 30 miles west of the Pennines. He suggests cutting out the Atlantic weather chart

from the daily paper and sticking it in your log or desk diary. Trends can be followed and rough forecasts made. He has built the Gemini tuner and has picked up Norddeutscher Rundfunk (West Germany) on 99.8MHz and Roermond (Holland) on 88.2MHz on 8th and 9th April.

My thanks to all the other readers who have asked about matters related to this article, including **Stephen Fletcher** of Bromsgrove, **Michael Suttle** of Kilmacanogue, Ireland, **P. Shaw** of Sandbach. Unfortunately, I cannot send out details or recommendations for particular receivers as there are so many. Many of you are unsure of the stations you hear and unable to identify them. It does help if you can recognise the language; have a copy of the World Radio and TV Handbook at your elbow, or even a cassette recorder ready to go when something strange comes through. If you have any doubts and can record what you hear on a cassette, I will try to help you identify the source; of course there should be some speech. The R.S.G.B. reports propagation conditions on Sunday mornings starting at 9.30 (local time) on 3.6MHz. The first station in the south-east is GB2RS and repeats are made in other regions at half-hour intervals. These news bulletins cover many aspects of amateur radio and are broadcast on s.s.b. transmission.

There is a chart available that gives a summary of most of the British and European f.m. stations on the 87.5 to 103MHz band, that are likely to be picked up over long distances. It is a very useful quick reference, especially if reception conditions are changing rapidly. Any reader who would like one should write to me personally and enclose a 25p postal order to cover the cost of printing and postage.


SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- | | | |
|---|----------------------------|---|
| SA35
35W RMS 25-50V
7 transistors, 7 diodes | £4-45
Carr. free | ★ 25Hz-25kHz
★ 0.2% distortion
★ Noise—80dB
★ 500mV into 20K
★ 4-16 ohms |
| SA50
50W RMS 25-65V
7 transistors, 7 diodes | £5-65
Carr. free | ★ Simple wiring
★ Short and open circuit proof
★ Continuously rated
★ Top-grade components |
| SA100
100W RMS 45-70V
11 transistors, 6 diodes | £10-90
Carr. 60p | |

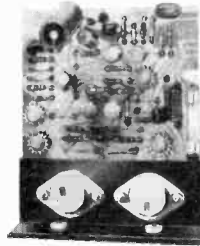120 watt module complete with built-in supply—extra heavy duty **£19-75** Carr. 60p



THE SA100 MODULE


POWER SUPPLIES

- | | | | |
|---------------------|-------------------------|--------------|------------|
| UNSTABILISED | | | |
| PU45 | Suits 2 SA35 or 1 SA50 | £4-90 | Carr. 30p |
| PU70 | Suits 2 SA50 or 2 SA100 | £7-75 | Carr. 40p |
| STABILISED | | | |
| PS45 | Suits 2 SA35 or 2 SA50 | £3-50 | Carr. free |
| MT45 | Transformer for above | £3-50 | Carr. 30p |
| PS70 | Suits 2 SA100 | £4-90 | Carr. free |
| MT70 | Transformer for above | £4-90 | Carr. 40p |

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £19-75 Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.

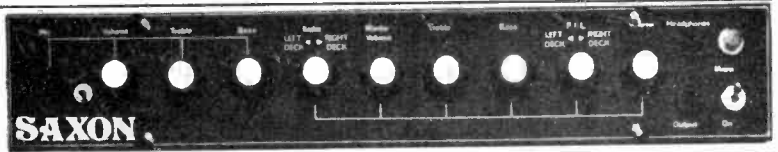

DISCO MODULE £8-00 Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22-50 Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



ADD 10% VAT TO ALL ORDERS


SINGLE CHANNEL VERSION £7-50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

MULTI-PURPOSE MIXERS

M4HL £18-50 Carr. 50p **M6HL £27-50 Carr. 50p**

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

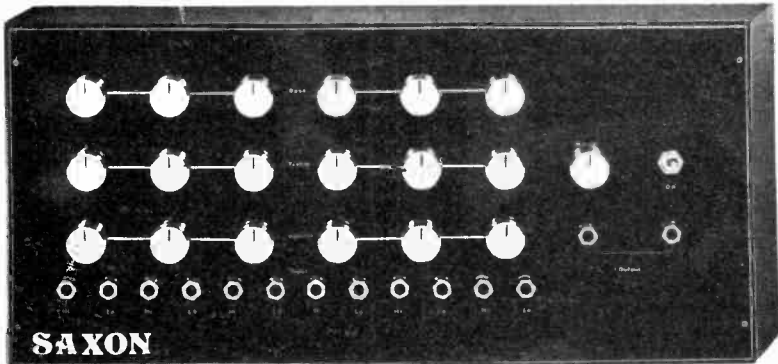
VA30 CHANNEL MODULE £3-50 Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



SAXON CSE 100 COMPLETE AMPLIFIER

£34-90
Carr. free

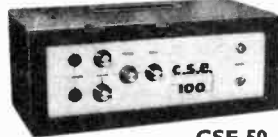100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vyndie case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29-50 Carr. free



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output from twin loudspeaker

SAXON 100 COMPLETE AMPLIFIER £53-00
Carr. free

SAXON 50 £37-50
Carr. free

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)


SHOP HOURS: 9 a.m. 5 p.m. — LUNCH 12.30 1.30 p.m. MAIL ORDER DESK: 10 a.m. 3 p.m.
24 HOUR ANSWER SERVICE TEL. 01-684 6385

SEND 10p FOR OUR NEW 26-PAGE MANUAL which gives full details of the above products.
TERMS OF BUSINESS: C.W.O. or C.O.D. on receipt of 50p C.O.D. charge.
Please include S.A.E. with all enquiries.
VAT at 10% must be added to all orders including postage and carriage charges.

BI-PRE-PAK

AUDIO BARGAINS

STEREO

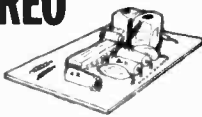

DECODER
£4.95

incl. P. & P. and V.A.T.


Ready built unit, ready for connection to the I.F. stages of existing FM Radio or Tuner. A tell take light can be connected. The Unit is a small printed circuit, no further alignment necessary. L.E.D. is recommended as the indicating light. Suitable device available from us at 36 $\frac{1}{2}$ p. Instructions included.

3 W.R.M.S. I.C. AMP


only £1.65 incl. P. & P. and VAT
Order Code I.C.A. 1

on P.C. Board with all components
or 2 on one board for £2.86

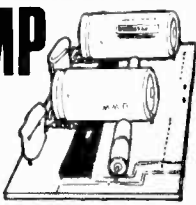Order Code I.C.A. 1/5
These amps. are supplied with a free booklet
on connecting up, specifications and easy to
build projects using the I.C.A. 1



5W & 10W AMPS

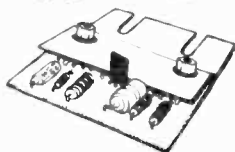

5W ONLY £1.98
10W ONLY £2.49

incl. P. & P. and VAT

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 $\frac{1}{4}$ " x 1 $\frac{1}{2}$ ". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the UK. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit 15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain crystal or ceramic pick-up cartridges. £1 21

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. £1 69

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. £1 21

Instruction leaflet supplied with all units. Post and packing and VAT included in prices.

1 to enclose £ for Decoders,
3W Amps/..... 5W Amps 10W Amps
Stereo Pre-Amps 1 Stereo Pre-Amps 2
Stereo Tone Controls
(Please insert quantities and delete those not applicable)
Name
Address

BI-PRE-PAK

Dept. D, 222/224 West Road,
Westcliff-on-Sea, Essex SS0 9DF
Telephone: Southend (0702) 46344

Co. Regn. No. 820919

Trannies

4 Bush House,
Bush Fair, Harlow,
Essex.

PRICES INCLUSIVE
OF V.A.T.

★ Retail Shop open 9 to
5.30 Mon. to Sat

★ Post & Package 15p.

★ 1974 Catalogue 20p.

TRANNIES DISCO UNIT



Includes
★ DJ 100W discotheque amp with
full mixing and PFL facilities. £94.75.

★ Stereo headphone with boom
microphone. £9.90.

★ Trannies disco console with 2
Garrard SP25 Mk. IV turntables.
£59.90

★ Pair 50W Speakers £47.00

OR COMPLETE SYSTEM £189.97.
carriage £5.00. Terms available, no
deposit. £10.16 monthly for 24
months.

We stock a full range of Disco Equip-
ment. Send for list or pay a visit.

£1 BARGAIN PACKS

£1 10 Silicon NPN Power transistors
like 2N3055. Below spec

£1 10 Plastic FETs unmarked-un-
tested similar to 2N3819 (random
test showed good yield).

£1 20 TOS transistors NPN or PNP.
state which. 2 to 5 amp. untested.

£1 20 TO18 transistors PNP like
BC178 BC179 etc. Untested.

£1 30 Plastic Power NPN transistor
TO220 case like 2N3055. Untested.

£1 10 General Purpose fully tested
FETs.

£1 200 mixed capacitors.

£1 250 mixed resistors.

★ Any 5 packs £4.50 ★

SEMICONDUCTORS	BRIDGE RECTIFIERS
AC126 14p	OC44 16p
AC127 16p	OC45 10p
AC128 15p	OC71 11p
AC141K 26p	OC81 12p
AC142K 26p	2N706 14p
AC176 18p	2N1131 24p
AC187 24p	2N1132 28p
AC188 24p	2N2904 20p
AC187K 23p	2N2926 11p
AC188K 23p	2N7053 26p
AD149 49p	2N3054 55p
AD161 33p	2N3055 49p
AD162 40p	2N3702 14p
AF114 20p	2N3703 13p
AF115 20p	2N3704 14p
AF116 20p	2N3705 13p
AF117 20p	2N3706 12p
BC107 13p	2N3707 13p
BC108 12p	2N3708 11p
BC109 13p	2N3709 12p
BC147 13p	2N3710 12p
BC148 13p	2N3711 12p
BC149 13p	2N3819 35p
BC182 13p	4046 55p
BC183 11p	40362 55p
BC184 14p	40636 69p
BC212 13p	1N914 8p
BC213 13p	1N916 8p
BC214 13p	1N4001 7p
BD131 68p	1N4002 8p
BD132 90p	1N4003 10p
BF194 16p	1N4004 10p
BF195 17p	1N4006 15p
BF244 27p	1N4148 6p
BFY50 18p	1N5400 16p
BFY51 18p	1N5401 17p
BFY52 17p	1N5402 19p
MP111 36p	1N5404 24p
OC28 50p	1N5406 28p
OC26 50p	3-3 to 33 volt 11p each

Resistors

1/2 watt 5% carbon	1p
1 watt 5% carbon	1p
1 watt 10% carbon	3p
range 10 ohms to 4.7 megohms.	
1/2 watt m/o 2%	4p
range 10 ohms to 1 megohms.	

VEROBOARD

0-1	0-15
24 x 34	24p
24 x 5	27p
34 x 34	27p
34 x 5	31p
17 x 34	82p
17 x 34	11-10
17 x 5 (Plain)	90p
Pin insertion tool	57p
Spot face cutter	46p
Pk 36 Pins	20p

Electrolytic Capacitors

6.3 VOLT	220µF 9p	40 VOLT	47µF 64p
68µF 64p	680µF 17p	100µF 9p	68µF 10p
150µF 64p	1000µF 17p	220µF 11p	470µF 19p
470µF 11p	1500µF 25p	680µF 25p	1000µF 25p
680µF 13p	2000µF 43p	2200µF 44p	
1500µF 18p	25 VOLT		
2200µF 18p	10µF 64p		
3300µF 26p	22µF 64p		
	47µF 64p		
	100µF 8p		
	150µF 8p		
	220µF 10p		
	470µF 13p		
	470µF 10p		
	1000µF 11p		
	1500µF 20p		
	2200µF 24p		
	5000µF 68p		
		63 VOLT	1µF 64p
			2.2µF 64p
			4.7µF 64p
			6.8µF 64p
			22µF 64p
			47µF 64p
			100µF 11p
			150µF 13p
			220µF 19p
			330µF 22p
			470µF 26p
			1000µF 44p

VOLUME CONTROLS

Potentiometers
Carbon track 500Ω to 2.2MΩ
Log or Linear
Single 13p. Dual gang (stereo) 43p.
Single type with D.P. switch 13p.
extra.

CARBON SKELETON

PRESETS
Small high quality type (linear
only). All valves 100-5 meg ohms.
-1 watt 6p each
-2.5 watt 64p each


VISIT OUR RETAIL
SHOP AT BUSH FAIR
Monday to Saturday 9 to 5.30.

SLIDE SWITCH
SPST 11p each. D.P.D.T. 13p each.

**MINIATURE NEON
LAMPS**
240V or 110V 1-4 5p. 5 plus 4p
each.

Mullard Polyester Capacitors

C280 SERIES	250V P.C. mounting: 0.01µF, 0.015, 0.022, 3p, 0.033, 0.047, 0.068, 4p, 0.1, 44p, 0.15, 0.22, 51p, 0.33, 7p, 0.47, 94p, 0.68, 12p, 1µF, 14p, 1.5µF, 22p, 2.2µF, 27p.
C295 SERIES	400V 0.001µF, 0.0015, 0.0022, 0.0033, 0.0047, 3p, 0.0068, 0.01, 0.015, 0.022, 0.033, 34p, 0.047, 0.068, 0.1, 44p, 0.15, 44p, 0.22, 84p, 0.33, 12p, 0.47, 144p, 160V: 0.01µF, 0.015, 0.022, 0.033, 0.047, 0.068, 34p, 0.1, 44p, 0.15, 44p, 0.22, 51p, 0.33, 7p, 0.47, 94p, 0.68, 12p, 1µF, 14p, 1.5µF, 22p, 2.2µF, 24p.

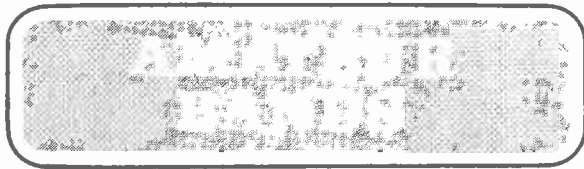

by Eric Dowdeswell G4AR

DELAYS in the publication of Practical Wireless, for reasons beyond editorial control, make it a toss-up as to whether items of news included herein may be out of date by the time that you read this page.

It is hoped that most of you will be aware of the RSGB's annual National Field Day, an old and revered HF bands CW contest, when Clubs put their crack operators to work and actually invite families and friends to go along and watch (and cook and wash up, usually!). If you're not actually taking part then sit down at home and listen in to the lads working worldwide DX on CW with just 10W input. It's the better-than-at-home aerials out in the country that do the trick. Note the date, June 8/9.

Incidentally, if your listening times generally are rather limited in number then try to make them coincide with a contest, then you will be assured of some activity. There is nothing more annoying than to arrange to spend an hour on the receiver only to find that the band is seemingly dead when, in fact, it is just simply lack of activity. International contests such as those organised by the RSGB, ARRL and CQ Magazine brings to life all kinds of rare stations and countries seldom heard normally. So if you are interested in lengthening your 'countries heard' list then this is the time to do it. I once worked 99 different countries in a week-end CW contest and still have the flattened ears to prove it!

When G9ZZZ down the road is working the DX see if you can hear these stations as well. If you can't then there is something wrong, unless he is using an elaborate aerial at 60 feet against your few yards of wire in the loft.

SSTV on 80m

The MPT's decision to permit UK amateurs to use SSTV on 80m has not met with much enthusiasm judging by the rude remarks heard so far from the usual inhabitants of the band. It remains to be seen whether SSTV will be a workable proposition amid all the other noises on the band.

Personally I doubt it, except for perhaps local working where the strong signals may override interference, deliberate and otherwise! Somehow I don't think that SSTV and SSB are going to mix in the few kHz at the top end of the band.

Our amateurs can often be heard airing their views on non-amateur noises on 80m but they seem to forget that this is a shared band here and that a lovely S9 signal from some DX station is equally just a noise to some other service sharing the band.

Goodbye MPT!

Not many amateurs seem to be aware yet of the intention of the present Government to abolish the Ministry of Posts and Telecommunications. Among other responsibilities the Home Office will administer the Wireless Telegraphy Acts which are of immediate concern to amateurs here. The MPT, or whatever it was called at different times in the past, has always had a very close and amicable relationship with the amateur, mainly through the good offices of the RSGB, and it is to be hoped that this happy state of affairs will long continue. It will not profit our movement if we have to deal with faceless Civil Servants knowing nothing of our hobby.

In spite of the scarcity of sunspots the HF bands are improving generally with the increasing hours of daylight which we are now enjoying. Except, of course, that it generally means a transfer of personal activity at home from the inside to the outside! So when you are ostensibly doing a bit of weeding or shoeing the birds from the seedlings why not shove up a rhombic aerial or at least a nice long wire as high as possible. With copper being so pricey these days don't overlook the possibility of using aluminium wire as a substitute, preferably hard drawn to avoid stretch.

GB2MT

The Marconi Centenary station GB2MT, operated by Ralph Barrett G2FQS, and mentioned last month, managed 235 QSO's on SSB from Marconi's old home in Bayswater, London. Unfortunately, on the great day itself, April 25th, no contact was made with I4FGM, the Italian counterpart of GB2MT, located in the mausoleum where Marconi now rests. This was in spite of a schedule and a reminder by Telex from the Marconi Company here. Plenty of other Italian stations were worked around the same time. It is understood that I4FGM will be active for the rest of the year but only on Saturday afternoons.

Apologies again for the lack of any reports from readers, which would normally form the backbone of this page. My appeal in the last issue for reports will not produce any response in time for this month's page because of the delayed publication dates. Once things get back to normal, hopefully with the July issue, it will be possible to raise matters in one issue and to deal with them in the next, said he, optimistically!

BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 27 Lismore Road, Highworth, Swindon, Wiltshire, SN6 7HU.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.


VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the middle of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashstead, Surrey, KT21 2TW.

**G. F. MILWARD, 369 Alum Rock Road,
Birmingham B8 3DR. Tel. 021-327 2339**

12 VOLT FLUORESCENT LIGHTING

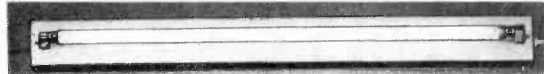

- INVERTER TRANSFORMERS 13/15 WATT (CIRCUIT INCLUDED) **70p**
- "CURRENT ECONOMY" TRANSISTOR (600 ma.) **50p**
- "MAXIMUM LIGHT" TRANSISTOR (1.3A) **50p**
- RESISTORS/CAPACITORS TO SUIT **15p**
- LAMP HOLDERS (LONG LEAD) **30p PAIR**
- (SHORT LEAD) **20p PAIR**
- WHITE ENAMEL CASE, 18" or 21" **70p**
- TUBE, 18"-15 WATT or 21"-13 WATT **45p**
- (NOTE:- TUBE ONLY SUPPLIED IF CASE ORDERED, TO PREVENT POSTAL DAMAGE)
- 13 WATT FITTING READY BUILT AND TESTED—INCLUDING TUBE **£3.75**
- POST/PACKING **20p PER ORDER**

ALL GOODS PLUS 10% V.A.T.

SILICON P.N.P.			
Type	Voltage	Frequency	Price
BCY 71	45	200 MHz	12p
BFS 92	100	70 MHz	55p
BFS 95	40	70 MHz	17p
BFX 10	25	210 MHz	16p
2N 2906	60	200 MHz	15p
2N 3906	80	100 MHz	12p
2N 3703	50	100 MHz	12p

SILICON N.P.N.			
Type	Voltage	Frequency	Price
BC 108	30	150 MHz	15p
BC 109	30	150 MHz	15p
BF 179	225	125 MHz	40p
BF 190	30	625 MHz	25p
BFW 58	80	80 MHz	15p
BFX 43	30	500 MHz	20p
BFX 86	40	50 MHz	17p
BFY 53	30	50 MHz	10p
2N 607	60	40 MHz	12p
2N 709	15	900 MHz	30p
2N 718	60	60 MHz	12p
2N 753	25	250 MHz	12p
2N 744	20	300 MHz	12p
2N 1613	75	60 MHz	17p
2N 2220	60	250 MHz	15p

SILICON N.P.N.			
Type	Voltage	Frequency	Price
2N 3035	60	100 MHz	17p
2N 3707	30	100 MHz	12p
2N 5179	20	900 MHz	40p

GERMANIUM P.N.P.			
Type	Voltage	Frequency	Price
ACY 44	50	1 MHz	10p
ADY 26	80	75 watts	£1
AF 124	20	75 MHz	20p
AFY 19	32	350 MHz	20p
ASY 32	25	5 MHz	10p
ASZ 21	15	450 MHz	20p
GET 113	32	2 watts	10p
GET 120	32	1 MHz	10p
OC 123	50	1 MHz	10p
OCY 70		Light-sensitive	20p
2N 1307	30	10 MHz	15p
2N 1309	30	15 MHz	15p
2N 448	60	150 watts	£1

HIGH FREQUENCY POWER			
Type	Voltage	Frequency	Price
BFR 64	40	1,200 MHz	£1
BLY 80A	35	650 MHz	£5
BLY 93A	60	500 MHz	£5
BLY 218	36	1,200 MHz	£2
2N 709	15	800 MHz	15p

MICROWAVE DEVICES

Type	Frequency	Price
CL 8300	Gunn effect oscillator	9.4 GHz £40
CL 8370	ditto	9.5 GHz £10
CL 8380	ditto	10.5 GHz £10
CL 8390	ditto	11.5 GHz £10
CL 8430	ditto	9.35 GHz £40
CL 8450	ditto	9.35 GHz £40
CL 8470	ditto	9.35 GHz £40
BXY 27	Varactor Diode, "S" Band, Cut-off	70 GHz £1
BXY 28	Varactor Diode, Cut-off	100 GHz £1
BXY 32	Frequency Multiplier, "X" Band	150 GHz £1
BXY 35A/C	ditto	25 GHz £1
BXY 36C/D	ditto	75 GHz £1
BXY 37C/D	ditto	100 GHz £1
BXY 38C/E	ditto	120 GHz £1
BXY 39C/D	ditto	150 GHz £1
BXY 40C/E	ditto	180 GHz £1
BXY 41C/D/E	ditto	200 GHz £1

£1 100 1/2 WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 20p PACK No. 1

£1 1 VERO-BOARD CUTTER
5 1/4 in. x 1 in. x 15 BOARDS
50 SQ. INS. "ODD PIECES"
VERO

POSTAGE 20p PACK No. 3

£1 20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108 ETC.

POSTAGE 20p PACK No. 5

£1 6 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS
& CAPACITORS

POSTAGE 27p PACK No. 7

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

POSTAGE 20p PACK No. 2

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

POSTAGE 20p PACK No. 4

£1 1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT

POSTAGE 20p PACK No. 6

£1 100 RESISTORS
100 CAPACITORS
(ASSORTED TYPES)

POSTAGE 20p PACK No. 8

ESSENTIAL BOOKS FOR RADIO AMATEURS

NEW!

TEST EQUIPMENT for the radio amateur

by **H. L. Gibson, CEng, MIEE, G8CGA**

This book explains in detail the theory behind modern measurement techniques, and describes many items of equipment of special interest to the home constructor. Readers are taken through the basics of indicating and electronic instruments and on to techniques of frequency, power and noise measurement, using up-to-the-minute components and methods. Other topics include signal sources, attenuators, oscilloscopes, swept measurements, aerials and transmission lines. There is also an extensive section of reference data. Detailed instructions are given for the construction of many items of test gear; including a wide-range fet multimeter, a transistorized dip oscillator, an oscilloscope for use up to 146MHz, an i.f. sweep generator and digital frequency meter.

Price **£2**, including p & p

TELEPRINTER HANDBOOK

by **D. J. Goacher, G3LLZ, and
J. G. Denny, G3NTT**

This recent RSGB publication covers the theory and practice of radio teleprinter techniques. In addition to full descriptions and maintenance data for all widely used machines, both European and American, the handbook fully covers the design and use of ancillary equipment. There is also an extensive reference section covering commercial equipment and terminology, and a bibliography.

The contents include: theory, practice and standards; teleprinters; associated machines; power supplies; terminal units; auxiliary equipment; frequency shift keying; filters; test equipment; interconnection and control; operating procedures.

A "must" for every rtty enthusiast, this volume is also invaluable to all who use, design or service teleprinter equipment.

376 pages

£5.35 (inc. p & p)

These are just two of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The **RSGB** is the national society representing all **UK** radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.



RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688


SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts

r.m.s. into 8 ohm. Frequency response 12Hz-30KHz ± 3 db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. **PRICE £12.00.** P. & P. 50p.

DE LUXE STEREO AMPLIFIER

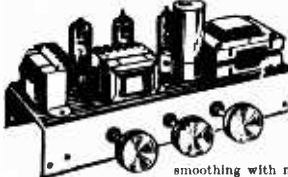

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate

smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard.

PRICE £10.40. P. & P. 60p.

POWER SUPPLY UNIT 200/240v. A.C. Input. Four switched fully smoothed D.C. outputs giving 6v. and 74v. and 9v. and 12v. at 1 amp on load.

Fitted installed output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" w x 4" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. **PRICE £5.00** P. & P. 35p.

FEW ONLY!

High grade mains transformer with grain orientated lamination. Primary 200/240 secondary 18.5 volts at 0-6 amps and 4-6 volts at 0-3 amps. Size 2" h x 2 1/2" w x 2" d overall. **£1.25** plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-10-15-20-25-30-35-40-60v. half wave at 1 amp, or 10-10-10, 20-20-20, 30-30-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. **Price £2.81** P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. £1.10. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.21. P. & P. 25p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.82. P. & P. 35p.

HI-GRADE COPPER LAMINATE BOARDS 8" x 6", Five for 80p plus 30p P. & P.

For personal callers only!

Limited number of stereo radiogram chassis, covering LW/MW/FM bands. Mono radio and stereo gear. Overall size—approx. 16 1/2" w, 6 1/2" H, 8" Depth. 4 watts per channel output. only **£16.50.**

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. **Price £1.00.** P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. **ONLY 40p.** Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents 80p
Transistor Equivalents 90p
Transistor Characteristics £1.15
POST FREE
All three together £2.60

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias 95p, Post Free
8 pole 3 way 2 bank low loss Yaxley type switches 1 1/2" sections. Standard spindle. 2 switches 86p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.

A few minutes from South Wimbledon Tube Station.

SPECIAL BARGAIN OFFER!

Limited number of BSR C193 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. **ONLY £8.00 + p. & p. 60p.**

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 2500, 5100, SP25 II and III, BL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). **NOW ONLY £4.95.** P. & P. 70p.

LATEST ACOS GP9/18C mono compatible cartridge with 1/2 stylus for LP/EP/78. Universal mounting bracket. **£1.50.** P. & P. 15p.

SONOTONE STARC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. **ONLY £2.80** P. & P. 15p. Also available fitted with twin Diamond T/O stylus for Stereo LP. **£2.80.** P. & P. 15p.

LATEST ROSETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. **£1.42** P. & P. 15p. **LATEST ROSETTE T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only **£1.44.** P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7in. wide x 8in. deep x 6in. high. Ready built and tested. **PRICE £6.90.** P. & P. 50p. **ALSO AVAILABLE** mounted on board with output transformer and speaker. **PRICE £6.90.** P. & P. 60p.

SPECIAL OFFER ! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynal front. Size 18" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" base unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £9.25 Carr. 75p

Cabinet Available Separately **£4.95.** Carr. 65p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter **£7.15.** Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely ready built, completely wired and tested with good quality output transformer. **£3.85** P. & P. 40p BARGAIN PRICE

LOUDSPEAKER BARGAINS

5in. 3 ohm **£1.25.** P. & P. 15p. 7 x 4in. 3 ohm **£1.40.** P. & P. 20p. 10" x 6in. 8 ohm **£2.10.** P. & P. 30p. E.M.I. 8 x 6in. 3 ohm with high flux magnet **£1.76.** P. & P. 20p. E.M.I. 13 1/2" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm **£2.80.** P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network **£4.66.** P. & P. 30p. E.M.I. Ceramic magnet heavy duty tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. **£1.25 + 20p.** p. & p. **BRAND NEW.** 12in. 15w. H/D Speakers, 3, 4 or 15 ohms. State which. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly **£9.90.** Guitar models: 25w. **£9.90.** 35w. **£11.00.** P. & P. 45p.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS

With large ceramic magnet and plasticised cone surround. 8 ohm impedance. **£9.70.** P. & P. 85p.

Also available specification as above but size 10" x 6" £2.70 and size 8" round **£2.60.** P. & P. 35p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 8 or 15 ohm (state which) **£2.95.** P. & P. 30p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER. Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only **£5.55** each. P. & P. 34p.

VYNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our prices **£1.10** yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Output stage: 14 watts r.m.s. per channel into 8 ohms. Frequency response ± 3 dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: ± 3 dB 12-15,000 Hz. Bass boost approx. to ± 12 dB. Treble cut approx. to -16 dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Full output: 14 watts r.m.s. per channel into 8 ohms. list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT £11.55 P. & P. 25p
POWER PACK KIT £3.50 P. & P. 35p
CABINET £2.50 P. & P. 35p

(Post Free if all units purchased at same time)

Also available ready built and tested **£25.10.** Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discographic use, etc.




8-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£20.00.** P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£5.00.** P. & P. 45p.

10 1/2" WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 5-15 Ω speaker and 2 independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP86 and E280 rectifier. Simple instruction booklet 15p + SAE (Free with parts) All parts sold separately. **ONLY £9.00** P. & P. 60p. Also available ready built and tested **£18.00** P. & P. 70p.

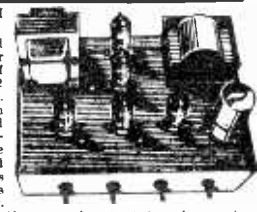

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexfoam ear-cuffs. Wired and fitted with standard stereo 1/4" jack plugs. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. **PRICE £3.30.** P. & P. 25p.

PRICES INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES



FOR QUALITY COMPONENTS

MOTOROLA		
F. M. Multiplex Stereo Decoder	MC1310P	each 2.93
Four Channel SQ Decoder	MC1312P	1.75
O/P Power Transistor	2N3055	0.85

SIGNETICS		
I/C Timer	NE555V	0.80
Dual I/C Timer	NE556A	1.40
High Phased Locked Loop	NE560B	4.20
High Phased Locked Loop with AM Demod	NE561B	4.20
High Phased Locked Loop with Open VCO	NE562B	4.20
Precision Phased Locked Loop	NE565A	2.90
Function Generator	NE566V	1.55
Tone Decoder	NE567V	2.90

G.I.		
Eight Digit Calculator Chip	C500	11.00
Eight Digit Calculator Chip	C550	9.50
3 1/2 Decade DVM Chip	AY-5-3510	6.40

MONSANTO		
(MAN3M) 0.115" LED Seven Segment Display	Q2501	1.10

FERRANTI		
Radio Receiver	ZN414	1.20

Data information supplied with each device.


Write for free catalogue of our large stocks of Ferranti, Motorola, G.I., Monsanto, Mullard, Signetics and R.C.A. components.

Add 20p Postage and Packing + 10% V.A.T. on total of order

S.C.S.
P.O. Box No 26,
(Dept PW)
Wembley,
Middlesex HA0 1SD,
England

Why pay more - look at our Fantastic Bargain Offer!


THE AVON AUDIO SYSTEM

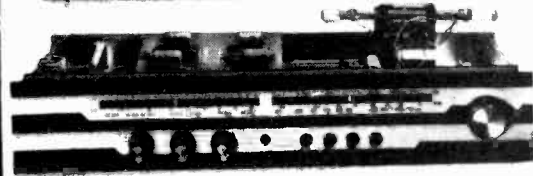

The uncabineted system is ideal as an economical replacement for an outdated chassis. Stereo Amplifier for Stereo/Mono record reproduction. Tuner with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

LATEST BSR STEREO/MONO RECORD CHANGER plays all types of 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play.

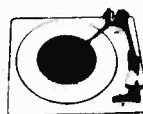TWIN ELLIPTICAL SPEAKERS These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.



EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £35.00. Credit Terms £3.50 deposit plus £2 Post & Packing followed by 9 payments of £4.10 (Total Credit Terms £44.40) Don't miss this bargain.

SEND £5.50 TODAY

ALL EQUIPMENT COVERED BY OUR 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

100 Chase Side, Southgate,
London N14 5PL
Tel: 01-886 3733/9666

LEWIS Radio PW 7/74

Train for television

Course commences 4th September, 1974

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS

(Dept. PW4) 34a Hereford Rd., London W2 5AJ



and make no mistake

People ask Laskys because of their keenly competitive pricing policy. People ask Laskys because of their staggering range of choice. People ask Laskys because every item they sell is fully guaranteed for a year with no sneaked in charges for labour or parts. People ask Laskys because they give advice that can be trusted.

AUDIOTRONIC Model ATM1


Top value 1,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 V AC and DC. DC current 0.1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £3.25 P&P 15p

AUDIOTRONIC Model ATM5

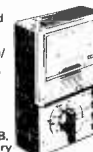
Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0.3/15/150/300/1200V AC. (2500 opv). 0.6/30/300/600V DC. (5000 opv). 0-300 uA/0-300mA DC. Resistance: x 10 & x 100. -10 to +18dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £3.50 P&P 15p

MODEL TH12

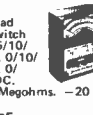20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/250/1000V AC. 0/10/50/250/1000V AC. 0-50uA/25/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.



OUR PRICE £5.95 P&P 15p

HIKIKI Model 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50uA/250mA. 0-20k/2 Megohms.



OUR PRICE £5.97 P&P 20p

MODEL PL436


20,000 opv DC. 8000 opv AC. Mirror scale. Ranges: 6/3/12/30/120/600V DC. 3/30/120/600V DC. 50/600uA/60/600mA. 10/100k/1 Meg/10 Meg Ohm. -20 to 46dB.



OUR PRICE £6.97 P&P 15p

UA323 MULTIMETER

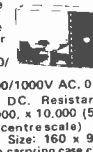20,000opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/50/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: x 10, x 100, x 1,000, x 10,000 (50k). 50k, 5k, 50k (centre scale). Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £7.00 P&P 20p

MODEL HIKKI 730X

30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 60/60uA/30mA/300mA. 2k/200k. 2 Meg Ohm. 10 to 63dB.



OUR PRICE £7.50 P&P 15p

MODEL TE300

30,000 opv. Mirror scale. Overload protection. 0/0.6/3/15/60/300/1200V DC. 0/6/30/120/600/1200V AC. 0/30uA/6mA/60mA/300mA/600mA. 0.8k/80k/800k/8 Meg ohms. -20 to +63dB.



OUR PRICE £7.50 P&P 15p

UA324 MULTIMETER


High sensitivity, overload protected. 20,000opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



OUR PRICE £8.00 P&P 20p

UA325 MULTIMETER

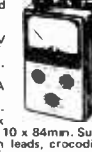20,000opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2.5A DC. 5/25/100mA/0.5/2.5A AC. Resistance: 0.3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with test leads, crocodile clips and steel carrying case.



OUR PRICE £8.75 P&P 20p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 0/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.



OUR PRICE £10.50 P&P 20p

TMK MODEL TW50K

46 ranges, mirror scale. 50kV/1 AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts: 1.5/3/15/10/25/50/125/250/500/1000. DC current: 25/50/100/250/500/1000. AC current: 10k/100k/1 Meg. 10 Meg ohms. -20 to +81.5dB.



OUR PRICE £12.50 P&P 17p

UA4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 6670 opv. Ranges: 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/6mA/15/60mA/150/600mA/1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £9.75 P&P 25p

MODEL 500

30,000 opv with overload protection. Mirror scale. Complete with sturdy metal carrying case, leads and instructions. Ranges: 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA/12A DC. 0/60k/6 meg/6 megohms.



OUR PRICE £13.95 P&P 20p

HIKIKI 705X VOLT-OHM-MILLIAMMETER


43 ranges: 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1200V AC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/60uA/600/120V DC. mA/6/12A. Resistance: 0-3/300k/30Mohms. Decibels: -10 to +17dB. Output: 0-3/6/15/30/60/120/300V ac ± 3% DC. ± 4% AC. Sensitivity: 50,000 opv AC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.



OUR PRICE £11.95 P&P 40p

HIKIKI Model 700X

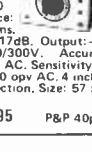100,000opv. Overload protection. Mirror scale. 0.3/0.6/1.2/1.5/3/6/12/30/60/120/300/600/120V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/60/150/500mA/6/12A DC. 2k/200k/2M/20M Ohms. -20 to +63dB.



OUR PRICE £14.95 P&P20p

Model HT10084 MULTIMETER

Overload protected, shock proof circuits. 9.5uA Meter with 50kV/1 AC. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/150/500mA/6/12A DC. 2k/200k/2M/20M Ohms. DC resistance 0-20/200k/2/20 Meg. ohms. DC current: -0/250uA/2.5/25/250 mA/10A. AC current: -0/10A. -20 to +62dB. Operates from 2 x .5V batteries. Size: 180 x 134 x 79mm.



OUR PRICE £17.50 P&P 40p

MODEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10uA/6/60/300mA. 12 Amp. 0/2k. 200K/2M/200 Meg Ohm. -20 to -17dB.



OUR PRICE £17.50 P&P 20p

TMK 100K LAB TESTER

100,000opv. 6 1/2" scale. Buzzer short circuit check. Sensitivity 100,000 opv DC. 5kV AC DC. Volts: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC. current 10/100uA/10/100/500mA/2.5/10A. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: -10 to +49dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.



OUR PRICE £19.95 P&P 27p

370WTR MULTIMETER

Features: DC current ranges: 20,000 opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A. 0/5k/50k/500k/5 Meg/5 Meg. Decibels: -20 to +62dB.



OUR PRICE £19.95 P&P 25p

KAMODEN 72.200 Multitester

High sensitivity tester. 200,000 opv. Overload protected. Mirror scale. Ranges: -0/0.6/3/3/30/120/600/1200V DC. 0/3/12/60/300/1200V AC. 0/6uA/1.2mA/12mA/600mA/12A DC. 0/12A AC. -20 to +63dB. 0/2k/200k/2 Meg/200 Megohms.



OUR PRICE £22.50 P&P 30p

UA4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer. 86mm. mirror scale. Ranges: 300V AC. 0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/5/15/100/500mA/1.5A DC. 0.26/0.5/1/5/10/50/250mA/1.5A AC. Resistance: 0.5/10/100/200 ohms/1.3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.



OUR PRICE £15.00 P&P 20p

MODEL UA4311 Sub-standard Multi-range Volt-Ammeter

Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/200/750uA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5A AC. 7.5A DC. 0/25/7.5/15/30/75/150/300/750mA/1.5/3/7.5A AC. 0/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.



OUR PRICE £49.00 P&P 50p

TE65 VALVE VOLTMETER

28 range. DC volts 1.5-1500V AC volts 1.5-1500V. Resistance up to 1000 Megohms. 200/240V AC operation. Complete with probe and instructions.



OUR PRICE £17.50 P&P 30p

MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0.6/3/12/30/300/600/200V DC. 0/30uA/6/60/300 mA. 12 Amp. 0/10k/1m/10m, 100 Meg Ohms. -20 to 17dB.



OUR PRICE £12.50 P&P 20p

LB3 TRANSISTOR TESTER

Tests ICO and B. PNP/NPN. Operates from 9V battery. Instructions supplied.



OUR PRICE £3.95 P&P 20p

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5 batteries. Complete with instructions etc.



OUR PRICE £4.50 P&P 20p

UA4341 Multimeter & Transistor Tester

27 ranges. 16,700opv. Overload protected. Ranges: 0.3/1.5/15/30/60/120/300/900V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA AC. 0.3/3/30/300mA AC. Resistance: 0.06/0.6/2.5/25/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.



OUR PRICE £10.50 P&P 20p

S100TR MULTIMETER TRANSISTOR TESTER


100,000opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0.6/3/12/30/120/600V AC. 0/12/60uA/12/300mA/1.2/30/100/1 Meg/100 Meg. -20 to +50dB. 0.01-0.2 MF/D. Transistor tester measures Alpha, Beta and ICO. Complete with instructions, batteries and leads.



OUR PRICE £19.95 P&P 25p

KAMODEN HMG500 insulation resistance tester

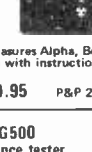
Range 0-1,000 Megohms. 500V. Battery operated. Wide range clear meter. 4 x 1.5 batteries. Complete with deluxe carrying case, batteries and instructions.



OUR PRICE £19.95 P&P 30p

C15 PULSE OSCILLOSCOPE

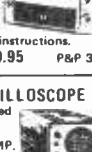
For display of pulsed and periodic waveforms in electronic circuit. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz V RMS/mm: 0.1-25; HORIZ. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz V RMS/mm: 0.1-25; Preset triggered sweep 1-3000usec. Free running 20-200 kHz in nine ranges. Calibrator pipe. 220 x 360 x 430mm. 115-230V AC.



OUR PRICE £39.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE

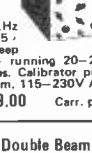
5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2usec. to 100 milli-sec/cm. Free running time base. 50Hz-1MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.



OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID OIP METER

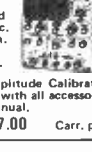Transistorised. Operates as Grid Dip Oscillator. Absorption Wave Meter and Oscillating Wave Meter. Frequency range 40kHz-280MHz. In six cells. 500mA meter. 9V battery operation. Size: 180 x 80 x 40mm.



OUR PRICE £19.95 P&P 20p

Also see following pages

ALL PRICES EXCLUDE VAT

SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedance 52 Ω Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.



OUR PRICE £4.25 P&P 25p

AT201 Decade ATTENUATOR

Frequency range 0-200kHz. Attenuator. 0-111dB, 0.1dB steps. Impedance 600 ohms. Input power maximum 30dBm. Size: 180 x 90 x 56mm.



OUR PRICE £12.50 P&P 37p

TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm \pm 1% Inductance: 6 ranges: 1 microhenry-111 henries \pm 2% Capacity: 6 ranges: 10pf-1110 mfd \pm 2% Turns Ratio: 6 ranges: 1:1/1000-1:11100 \pm 1% Bridge Voltage at 1,000cps. Operated from 9-volt battery. 100 micro-amp meter indication. Size 7 1/2" x 5" x 2".

OUR PRICE £25.00 P&P 25p

TE16A TRANSISTORISED SIGNAL GENERATOR

6 ranges, 400Hz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.



OUR PRICE £8.97 P&P 25p

MODEL TE20 RF SIGNAL GENERATOR

Six bands. 120kHz-260MHz. Dual output terminals. Separate variable audio output. Accuracy \pm 2%. Audio output to 8V. Power requirements: 105-125V, 220-240V A.C. Size: 193 x 265 x 150mm. Complete with test leads etc.



OUR PRICE £17.50 P&P 40p

TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 216mm x 170mm.



OUR PRICE £17.50 P&P 30p

TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 500 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.



OUR PRICE £24.95 P&P 37p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output TV maximum. 220/240V AC operation. Complete with instructions and leads.



OUR PRICE £37.50 P&P 50p

Also see previous page

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR

Range 19-220,000Hz Sine Wave 19-100,000 Hz Square Wave Output Sine or Square wave 10V P to P Size 180 x 90 x 90mm Operation 220/240V A.C.

OUR PRICE £19.95 P&P 37p

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.



OUR PRICE £19.95 P&P 25p

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiring. Continuous rating. Wide range available in stock. Single hole fixing. 1/2" diameter shafts. Bulk quantities available.



25 WATT 10/50/100/250/500/1000 Ohms £1.15 P&P 10p
50 WATT 10/25/50/250/500/1000/2500/5000 Ohms. £1.62 P&P 10p
100 WATT 1/10/25/50/100/250/500/1000/2500 Ohms £2.34 P&P 15p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 220/240/250V. Output 0-250V.

MODEL S260 BENCH MOUNTING

1A £10.50 30p
2.5A £12.00 35p
5A £19.50 37p
8A £30.35 50p
10A £33.75 75p
12A £35.50 75p
20A £85.00 125p
25A £95.00 130p
40A £120.00 150p



MODEL S260B PANEL MOUNTING

1A £10.00 30p
2.5A £12.00 35p

BV05 Vernier TUNING DIAL

App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm. deep including knob and coupling. 1/2" diam. shaft



OUR PRICE £1.62 P&P 15p

240° Wide Angle 1mA METERS

MW 1-6 60x60mm £6.50 P&P 15p
MW 1-8 80x80mm £6.90 P&P 15p



CP110 CHASSIS PUNCH SET

Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.



OUR PRICE £3.00 P&P 40p

HITACHI FLUORESCENT LANTERN L1901

A portable battery operated lantern ideal for home, motoring, camping etc. Approx. 10" tall. Provides brilliant light from 9 1.5v batteries (not supplied).



OUR PRICE £7.19 P&P 25p

KE630 3 Station INTERCOM

Master and two substations. Can be used on desk or wall mounted. Complete with cable and batteries



OUR PRICE £5.25 P&P 50p

WALKIE TALKIES

LIMITED STOCKS

SKYFON 100mW

P302 Two Channel 300mW **OUR PRICE £24.95** per pair
P1003 Three Channel 1 Watt **OUR PRICE £71.25** per pair
P&P 50p per pair
N.B. Unlicenable in U.K.

DT55G DIGITAL CLOCK MECHANISM

Features 24 hour alarm setting, on/off and auto alarm 'sleep' switch, illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V-3 Amp.

OUR PRICE £5.95 P&P 30p

SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER

Complete with printed circuit mounting board.

OUR PRICE £2.35 P & P 15p.

LH025 STEREO HEADPHONES

Light weight head phones with padded ear pieces. 4/16 ohms 20-20,000Hz. Impedance 2,500 ohms (60 ohms DC).

OUR PRICE £1.97 P&P 30p

TE1018 Deluxe Mono High Impedance Headset.

Sensitive magnetic headset with soft ear pads. Impedance 2,500 ohms (60 ohms DC). Frequency response: 200-4,000Hz.

OUR PRICE £2.25 P&P 30p

TE1035 Stereo HEADPHONES

Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and stereo jack plug.

OUR PRICE £2.60 P&P 30p

SH80V MONO/STEREO HEADPHONES

Volume control for each channel, 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.

OUR PRICE £4.97 P&P 30p

BH011 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching, communications etc. Headphones impedance 16 ohms. Microphone impedance 200 ohms.

OUR PRICE £5.95 P&P 30p

EMI LOUSPEAKERS

Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.

OUR PRICE £7.50 each P&P 37p

Model 450 13 x 8" with twin tweeter/crossover.

55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms

OUR PRICE £3.62 each P&P 25p

SPECIAL PURCHASE LIMITED QUANTITY! Tannoy 12" DR/8 Bass Speakers

8 ohms 30 watt Heavy duty. Ideal for Hi-Fi PA. Group

OUR PRICE £12.60 P&P 50p

SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS

High quality 2 way speaker systems. 25 Watts 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 255mm. approx. Wood grain finish with black fronts.

OUR PRICE £26.95 PR. P&P £1

SPECIAL BARGAIN!! STEREO SOUND SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 368 x 229 x 190mm. 8 ohms. 8 watts RMS, 16 watts peak. Complete with Din lead.

OUR PRICE £12.95 P&P 50p

FM TUNER CHASSIS

6 transistor high quality tuner. Size 101 x 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.

OUR PRICE £8.95 P & P 20p

Model A1018 FM TUNER

6 transistor high quality tuner. Size 101 x 153 x 101 x 63mm 3IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.

OUR PRICE £13.50 P&P 30p

SINCLAIR "SCIENTIFIC" CALCULATOR

8 digit display Four functions plus logarithms to base 10, antilog, sine, cosine, tangent, arcSine, arcCosine and arcTangent. Complete with instructions, case and batteries Rec Price £49.00

OUR PRICE £44.50 P & P 25p plus VAT.

SINCLAIR SYSTEM 2000 STEREO AMPLIFIER AND TUNER

Amplifier output 8 watts per channel RMS. Distortion less than 0.06%. Silicon transistors Two pick-up plus radio and tape inputs. tape output and scratch filter. Excellent Value

OUR PRICE £28.50 P & P 60p.

FM TUNER

Excellent selectivity and sensitivity. Twin dual-varicap tuning. 4 pole ceramic filter 19 transistor stereo demodulator giving 40 dB separation. Distortion 0.2% output. Fantastic Value.

OUR PRICE £28.50 P & P 60p

SINCLAIR Project 80 Modules

240 Power Amplifier..... £5.45
260 Power Amplifier..... £5.95
Stereo 80 Pre-Amplifier..... £11.95
Active Filter Unit..... £6.95
Project 805..... £26.95
P25 Power Supply..... £4.98
P26 Power Supply..... £7.98
P28 Power Supply..... £7.98
Transformer for P28..... £4.05

SINCLAIR Project 80 Packages

2 x 240/Stereo 80/P25..... £25.00
2 x 260/Stereo 80/P26..... £27.75
2 x 260/Stereo 80/P28..... £30.45
POST & PACKING 35p each.

MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 4mV 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k.

OUR PRICE £8.97 P&P 20p

HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by 1 year guarantee.

Post and Packing 15p per kit.

- AF20 Mono amplifier..... £4.80
- AF25 Mixer..... £3.60
- AF30 Mono pre-amplifier..... £2.61
- AF35 Emitter amplifier..... £2.27
- AF80 0.5W mic. amplifier..... £2.22
- AF305 Intercom..... £9.52
- AF310 Mono amplifier..... £5.91
- AT5 Automatic light control..... £2.58
- AT25 Window wiper motor..... £5.82
- AT30 Photo cell switch unit..... £5.70
- AT50 400W triac light dimmer/speed control..... £4.80
- AT56 2,200W triac light dimmer/speed control..... £6.90
- AT60 1 channel light control..... £7.80
- AT65 3 channel light control..... £14.55
- GP304 Circuit board..... £4.94
- GP310 Stereo pre-amplifier for use with 2 x AF310..... £21.27
- GP312 Circuit board..... £11.45
- GU300 Tremolo unit..... £7.50
- HF61 Diode detector..... £3.32
- HF65 FM transmitter..... £2.70
- HF75 FM receiver..... £2.87
- HF310 FM tuner..... £15.81
- HF325 Deluxe FM tuner..... £24.12
- HF330 Stereo tuner..... £9.96
- HF380 10V/hf aerial amplifier..... £4.94
- HF395 broadband aerial amp. £11.76
- LF380 Quadraphonic decim. £1.37
- MF50 Motivator..... £1.71
- M191 VU Meter..... £4.55
- M192 Stereo balance meter..... £4.97
- M1302 Transistor tester..... £8.45
- NT10 Stabilised power supply..... £6.15
- NT300 9V..... £12.51
- NT305 12V converter..... £4.50
- NT315 Power supply 240V AC to 4,5/15V DC, 500mA..... £9.57

Amateur Electronics by Josty-Kit, the professional book for the amateur

-covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.

OUR PRICE £3.30 (No VAT) P&P 25p plus VAT.

- AE1 100mW output stage..... £1.50
- AE2 Pre-amplifier..... £1.15
- AE3 Diode receiver..... £1.82
- AE4 Flasher..... 99p
- AE5 Astable multi-vibrator..... 95p
- AE6 Monostable multi-vibrator..... 95p
- AE7 RC generator..... 97p
- AE8 Bass filter..... 90p
- AE9 Treble filter..... 90p
- AE10 CCR Filter..... 90p

1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facilities for stereo headphone switching. Two gain controls, speakers on-off slide switch, stereo headphone socket.

OUR PRICE £2.25 P&P 15p

AUDIOTRONIC LOW NOISE CASSETTES

TYPE 5 10 25
C50 £5.67 £3.00 £7.08
C90 £2.24 £4.25 £10.00
C120 £2.73 £5.17 £12.24

AUDIOTRONIC C/02 CASSETTES

TYPE 5 10 25
CR60 £3.92 £7.72 £18.12
CR90 £5.32 £10.46 £25.22

AUDIOTRONIC 8 TRACK CARTRIDGES

TYPE Each 5 10
40M 85p £4.00 £7.50
80M £1.15 £5.40 £10.25
P&P Cassettes 3p, Cartridges 5p each
OVER 10 of either POST FREE!

AUDIOTRONIC AH101 Stereo Headphone Amplifier

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUT: 5mV and 100mV. OUTPUT: 50mV per channel.

OUR PRICE £8.50 P&P 20p

EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphones, guitar etc. and output to your amplifier. Volume control and depth of reverbation control. Walnut cabinet. 184 x 77 x 108mm.

OUR PRICE £7.50 P&P 20p

ALL PRICES EXCLUDE VAT



CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3.80
100uA	£3.75
200uA	£3.70
500uA	£3.65
50-0-500uA	£3.75
100-0-1000uA	£3.70
1mA	£3.65
5mA	£3.65
10mA	£3.65
50mA	£3.65
100mA	£3.65
500mA	£3.65
5A DC	£3.65
10A DC	£3.65
5V DC	£3.65
10V DC	£3.65
15V DC	£3.65
300V AC	£3.75
VU Meter	£3.90



*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4.30
100uA	£4.25
200uA	£4.20
500uA	£4.15
50-0-500uA	£4.25
100-0-1000uA	£4.20
1mA	£4.10
5mA	£4.10
10mA	£4.10
50mA	£4.10
100mA	£4.10
500mA	£4.10
5A DC	£4.10
10A DC	£4.10
5V DC	£4.10
10V DC	£4.10
15V DC	£4.10
300V AC	£4.20
VU Meter	£4.40



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£3.95
100uA	£3.85
200uA	£3.80
500uA	£3.75
50-0-500uA	£3.85
100-0-1000uA	£3.80
500-0-5000uA	£3.70
1mA	£3.70
1-0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.80
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
20V DC	£3.70
30A DC	£3.85
50A DC	£4.05
5V DC	£3.70
10V DC	£3.70
15V DC	£3.70
20V DC	£3.70
50V DC	£3.70
150V DC	£3.70
300V AC	£3.70
15V AC	£3.80
50V AC	£3.80
150V AC	£3.80
300V AC	£3.90
500V AC	£3.80
S Meter 1mA	£4.10
VU Meter	£3.70
300V DC	£3.70
15V AC	£3.80
50V AC	£3.80
150V AC	£3.80
300V AC	£3.90
500V AC	£3.80
S Meter 1mA	£4.10
VU Meter	£3.70



CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.60
100uA	£4.50
500uA	£4.30
50-0-500uA	£4.50
100-0-1000uA	£4.45
1mA	£4.30
1A DC	£4.30
5A DC	£4.30
20V DC	£4.30
50V DC	£4.30
300V DC	£4.30
150V AC	£4.45
300V AC	£4.45
VU Meter	£4.90



CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm


50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.00
50-0-500uA	£3.15
100-0-1000uA	£3.10
500-0-5000uA	£2.95
1mA	£2.95
5mA	£2.95
10mA	£2.95
50mA	£2.95
100mA	£2.95
500mA	£2.95
1A DC	£2.95
5A DC	£2.95
10V DC	£2.95
20V DC	£2.95
50V DC	£2.95
300V DC	£2.95
15V AC	£2.95
300V AC	£3.05
S Meter 1mA	£2.95
VU Meter	£3.40
1A AC	£2.95
5A AC	£2.95
10A AC	£2.95
20A AC	£2.95
30A AC	£2.95



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.50
100uA	£4.45
200uA	£4.40
500uA	£4.35
50-0-500uA	£4.45
100-0-1000uA	£4.40
1mA	£4.20
1A DC	£4.20
5A DC	£4.20
20V DC	£4.20
50V DC	£4.20
300V DC	£4.20
15V AC	£4.20
300V AC	£4.30
VU Meter	£4.70

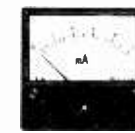

EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.15
100uA	£4.10
200uA	£4.05
500uA	£3.90
50-0-500uA	£4.15
100-0-1000uA	£4.05
1mA	£3.85
300V AC	£3.95
VU Meter	£4.30



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.




50uA	£8.50
100uA	£7.90
50-0-500uA	£7.90
1mA	£7.80
1-0-1mA	£7.80
1A DC	£7.60
5A DC	£7.60
5V DC	£7.60
10V DC	£7.60
15V DC	£7.60
20V DC	£7.60
50V DC	£7.60
300V DC	£7.60
500mA/5A DC	£8.60
5V/15V DC	£8.60
1A/5A DC	£8.60
1A/15A DC	£8.60

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5.45
100uA	£5.40
200uA	£5.35
500uA	£5.25
50-0-500uA	£5.40
100-0-1000uA	£5.35
500-0-5000uA	£5.20
1mA	£5.20
1-0-1mA	£5.20
5mA	£5.20
10mA	£5.20
50mA	£5.20
100mA	£5.20
500mA	£5.20
1A DC	£5.20
5A DC	£5.20
15A DC	£5.20
30A DC	£5.40
10V DC	£5.20
20V DC	£5.20
50V DC	£5.20
150V DC	£5.20
300V DC	£5.20
15V AC	£5.30
50V AC	£5.30
150V AC	£5.30
300V AC	£5.30
500V AC	£5.30
S Meter 1mA	£5.20
VU Meter	£5.55
1A AC	£5.20
5A AC	£5.20
10A AC	£5.20
20A AC	£5.20
30A AC	£5.20

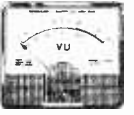

CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.50
100uA	£3.45
200uA	£3.40
500uA	£3.35
50-0-500uA	£3.45
100-0-1000uA	£3.40
1mA	£3.30
5mA	£3.30
10mA	£3.30
50mA	£3.30
100mA	£3.30
500mA	£3.30
1A DC	£3.30
5A DC	£3.30
10A DC	£3.30
5V DC	£3.30
10V DC	£3.30
20V DC	£3.30
50V DC	£3.30
300V DC	£3.30
15V AC	£3.45
300V AC	£3.45
VU Meter	£3.65



BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£5.25
50uA	£4.00
100uA	£3.95
500uA	£3.85
50-0-500uA	£3.95
100-0-1000uA	£3.90
500-0-5000uA	£3.60
1mA	£3.60
1-0-1mA	£3.60
5mA	£3.60
10mA	£3.60
50mA	£3.60
100mA	£3.60
500mA	£3.60
1A DC	£3.60
5A DC	£3.60
10A DC	£3.60
15A DC	£3.60
20A DC	£3.60
30A DC	£3.60
5V DC	£3.60
10V DC	£3.60
15V DC	£3.60
20V DC	£3.60
50V DC	£3.60
150V DC	£3.60
300V DC	£3.60
15V AC	£3.60
50V AC	£3.60
150V AC	£3.60
300V AC	£3.60
500V AC	£3.60
S Meter 1mA	£3.60
VU Meter	£3.60



POSTAGE & PACKING 15p

CALL INTO YOUR NEAREST LASKYS BRANCH OR ORDER WITH CONFIDENCE BY MAIL ORDER

CENTRAL LONDON

481 OXFORD ST.	01-493 8641
10 TOTTENHAM CT. RD.	01-437 2232
27 TOTTENHAM CT. RD.	01-636 3715
33 TOTTENHAM CT. RD.	01-636 2605
42/45 TOTTENHAM CT. RD.	01-636 0845
87 TOTTENHAM CT. RD.	01-580 3739
257/8 TOTTENHAM CT. RD.	01-580 0670
3 LISLE ST. WC2	01-437 8204
34 LISLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-453 5812
152/3 FLEET ST. EC4	01-353 2833

ESSEX

86 SOUTH ST. ROMFORD	70-20218
----------------------	----------

KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS	0892-23242
-----------------------------------	------------

LEICESTERSHIRE

45 MARKET PLACE, LEICESTER	0533-537678
----------------------------	-------------

SURREY

1046 WHITGIFT CENTRE, CROYDON	01-681 3027
27 EDEN ST. KINGSTON	01-533 8455
32 HILL ST. RICHMOND	01-948 1441

WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM	021-236 3503
---------------------------------	--------------

ALL BRANCHES OPEN FROM 9am to 6pm MON. TO SAT.

BARCLAYCARD & ACCESS

Holders welcome call into any branch or telephone your order to head office. CREDIT TERMS available for Personal Shoppers

EXPORT Personal experts arranged for overseas visitors at all our branches. Goods dispatched to all parts of the world through our Export Mail Order Department. Immediate attention given to orders.

CHEQUES ACCEPTED FROM PERSONAL SHOPPERS ONLY WITH BANKERS CARD.

All prices correct at 13-5-76 but subject to change

ALL PRICES EXCLUDE VAT



and make no mistake

A member of the Audiotronic Group of Companies



FOR MAIL ORDER

We offer a speedy and efficient service by mail order. Remember to add 10% VAT to total value of goods including post and packing

TO LASKYS HEAD OFFICE AND MAIL ORDER DEPARTMENT
Audiotronic House, The Hyde, London NW9 6JJ. Tel. 01-205 5651/3/735

Please send me the following items

TOTAL PURCHASE PRICE _____ (inc P&P and VAT) cheque postal order

NAME _____ money order

ADDRESS _____ I wish to pay by Barclaycard/Access and my number is _____

Registered in England No. 347947 at 12 Lower Grosvenor Place London SW1 0EX

Signature _____

PW7

Another!
winner!

fane **MODE ONE**

**HIGH FIDELITY
LOUDSPEAKER KIT**



Recommended
retail price

£10.98

including V.A.T.

Please
send S.A.E.
for fully
descriptive
leaflet.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

SPECIFICATION OF UNITS

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	3"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	2kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. SIZE 15½" x 10½" x 9".

*When used with above cabinet.

Distributors to the wholesale
and retail trade
LINEAR PRODUCTS LTD.
Electron Works, Armley, Leeds
LS12 3SA. Tel. 630126

Manufactured by
FANE ACOUSTICS LTD.
Hick Lane, Batley, Yorkshire.
Tel. Batley 6431

ALL PRICES INCLUDE VAT

AERIAL MAST POLES. Approx. 5ft. 2in. high, 2in. dia. Interlocking ends. Minimum order 3. As new, £1.25 (each) P. & P. 40p each.

AERIALS. As new. Whip Type 11ft. £1 each. Collapsible type. P. & P. 20p. New Bases for the above 75p, P. & P. 30p.

PAIR OF 4 x 150A VALVES complete with bases ex-equip not tested. Good condition £3, P. & P. 30p.

BARGAIN PARCELS 14lb at £1.60 plus 35p p.d.; 28lb at £3.00 plus 57p p.d.; 56lb at £4.95 plus £1.37 p.d. Contains pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save ££s. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £2 post paid.

TRANSISTOR BOARDS—consisting of transistors, diodes and resistors etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 30p. Quotations for quantity.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2½in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 30p. minimum order of six.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft £1, d. & d. 25p.

AERIAL POLES 4ft high 2" in diameter push-in type as new £1 each p. & p. 25p each minimum four.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall,
Staffs.

FELSTEAD ELECTRONICS (PW81) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE

STYLI Replacements for virtually all ACOS, BSR, COLLARO, GARRARD, PHILIPS, RONETTE, SONOTONE. Single Tip: Sapphire 16p, Diamond 35p. Double Tip: Can be Stereo/LP+78 or ST/LP+ST/LP Sapphire 32p. Double Tip: Diamond ST/LP+Sapphire 78 65p. Diamond ST/LP+Diamond ST/LP £1.20. For GOLDRING Diamond (800, 0800H and 0850) at £1.80 each. GR00E at £2.75. FREE LIST (FOR 8AE) FULL DETAILS AND CARTRIDGE EQUIVALENTS including SHURE, PICKERING, AUDIO-TECH, B. & O., AND MANY MORE STYLI FOR MAGNETIC AND CRYSTAL PICK-UPS. Charges 9p any quantity.

CARTRIDGES. All with styli and fittings. Replacements for ACOS GP/91 SC (Stereo-mono compatible series) at £1.05, GP93 Stereo at £1.45, GP94 Stereo Ceramic at £1.98; for RONETTE DC/4008CM (Speed change switch at front for GP67, TC8 & c.) at £1.15; for BBR X3H, X5H and X6M at £1.30 each, 8X5H and 8X5M at £1.65 each. TC8H at £1.45, TC8 Stereo, 3 pins, £2.10; charges 9p any quantity.

RECORDING TAPE. ALL FINEST BRITISH MYLAR: 5" 600 ft. 40p; 5" 900 ft. 55p; 5½" 1200 ft. 76p; 7" 1800 ft. £1.05. Charges for 5" and 5½", 1-4, 9p each; 5 and over, 33p the lot. Charges for 7", 1-3 11p each, 4-5 33p the lot, 6 and over 39p the lot.

SPEAKERS 2½", 3, 8 or 64 ohms (state which) 55p. Charges 9p each. 12" round, fitted cone tweeter, 6 watt* indistorted, 3, 8 or 15 ohms (state which) £2.40 (charges 80p) OR, PAIR FOR STEREO, £5.15 charges paid.

CONNECTING WIRE. Pkts. of 5 coils, asstd. coils, each 5 yds. Solid core 10p (8p charges). Flexible 21p (10p charges).

EARPIECES. Magnetic. 2.5 or 3.5mm plug (state which) 15p. CRYSTAL (3.5mm only) 35p (all 9p up to 8).

VIBRATORS. 7 pin SYNCH. (128R7 type) 75p. 4-pin NON-synch (121HD4) 45p (all 9p each).

Send 8AE for free styli, cartridge and components list. All prices include VAT.



**CONTACTLESS
IGNITION BY MOBELEC**

FROM ONLY £13.95 p&p 25p

We break the price barrier with this trouble-free inductive discharge contactless ignition which replaces contact points by a solid-state trigger-head giving high energy spark for excellent cold-weather starting and super-smooth tick-over. Designed for 4 or 6 cylinder neg. earth cars at a price you can afford. Easy to fit, clear illustrated instructions, free fitting kit. State model, make and year. Other Mobelec capacitive discharge E series models available. Mobelec E series for high performance engines. 4 & 6 cylinder NEG. AND POS. EARTH. £22.82. 8 cyl. £24.75. Post free.

SILHILL PRODUCTS

Dept. PW/6, 226 Mary Street,
Birmingham B12 9RJ. Tel: 021-440 3600

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone 6743

0A2	.40	5BA6	.28	8L6GT	.58	12K7GT	.45	35Z4GT	.65	5R2CC	1.00
0B2	.40	6BC8	.80	6L7	.50	12Q7GT	.45	35Z6GT	.75	E180T	1.00
0Z4	.47	6BE2	.82	6L18	.55	12B7	.60	50B5	.85	E182CC1	1.00
1A5GT	.50	6B16	.70	6L19	2.00	12B8G	.40	50C5	.45	E1148	.58
1A7GT	.55	6BQ7A	.55	8N7GT	.60	12B37	.44	50RH5	.55	E1A76	1.00
1B3GT	.60	6BR7	1.00	6C7GT	.50	12B27	.55	50L5GT	.65	E1A80	1.00
1R3GT	.55	6BR8	.85	6Q7GT	.50	14H7	.55	85A2	.60	E1A91	.75
1L4	.80	6B87	1.40	6Q7(M)	.55	14S7	.80	85A3	1.00	E1A24	.60
1N9GT	.65	6BW6	.60	6R7G	.75	19A4Q5	.50	90C1	.75	E1A801	.75
1R5	.45	6BW7	.68	6R7M	.75	19G6	1.40	90C2	2.40	E1B34	.95
1B4	.38	6B26	.49	6R8A	.44	20D4	2.00	180B2	.75	EB1	.15
1U4	.40	6CB9A	.40	68C7GT	.35	20P2	.75	215G9	.60	EDC61	.65
1U5	.75	6C4	.80	68GT	.50	14H7	.55	85A2	.60	E1A91	.75
2D21	.40	6C6	.40	68H7	.44	20P2	.80	5702	.80	EBF80	.39
2GK5	.55	6C9	1.25	68J7	.55	20P4	1.00	6057	2.00	EBF89	.43
2X2	.50	6CD6G	1.00	68K7GT	.44	20P5	1.80	6080	2.00	EBF89	.30
2A4	.50	6CG8A	.75	68Q7GT	.45	25A6G	.38	6087	1.00	EBL21	2.00
3D6	.40	6CH6	.80	6V6G	.17	25L6G	.80	7475	1.00	EC86	.70
3Q4	.55	6CL8	.55	6V6GT	.45	25V6G	.70	AC7P8	.98	EC788	.70
3Q8GT	.55	6CL8A	.80	6X4	.40	25Z4G	.88	AC9/PEV	.88	EC92	.45
3R4	.85	6CM7	.75	6X5GT	.40	25Z5	.80	DD	.98	EC93	1.50
4C86	.55	6CU5	.75	7B6	.75	25Z6G	.70	AC6PEN	.88	EC935	.95
4CB8	.55	6CW4	1.00	7B7	.70	28D7	1.00	AC/TH1	21	ECC40	1.00
5R4GY	.75	6DE7	.75	7H7	.75	30A5	.85	AL60	1.00	ECC81	.34
5U4G	.85	6D7RA	.75	7R7	.80	30C15	.75	ATP4	.40	ECC82	.88
6V4G	.64	6E76	.65	7Y4	.85	30C17	.80	AZP1	.90	ECC83	.85
5Y3GT	.45	6E5	1.00	7Z4	.80	30C18	.78	AZ31	.60	ECC84	.80
6C23	.70	6F1	.70	9D7	.65	30P5	.80	AZ41	.65	ECC85	.86
6Z4G	.85	6F6G	.40	10C2	.85	30FL1	.75	DL63	5.00	ECC86	.85
6Z4GT	.45	6F13	.55	10D7	.55	30FL2	.75	CL33	1.50	ECC88	.44
6R0L2	.80	6F14	.75	10F1	.80	30FL12	1.00	CY1C	1.00	ECC89	.65
6A8G	1.25	6F18	.55	10F9	.85	30FL13	.55	CY31	.45	ECC90A	.80
6A7C7	.49	6F23	.80	10F18	.55	30FL14	.70	DAF91	.30	ECC90T	1.00
6A65	.87	6F24	.85	10DL11	.70	30L15	.75	DAF96	.44	ECF80	.84
6A16	.80	6F25	1.00	10P13	.70	30L17	.70	DF91	.30	ECF82	.38
6A15	.75	6F28	.80	10P14	.50	30P4MR	1.00	DF96	.44	ECF86	.75
6A16	.84	6F32	.85	12A6	1.00		1.00	DK40	.70	ECF89A	.44
6A16	.80	6F36G	.75	12AC8	.65	30P12	.80	DK92	.70	ECF89B	2.10
6A8A	.65	6F18A	.75	12AD8	.85	30P19	.85	DK96	.60	ECH21	2.00
6A8N	.60	6G82	.65	12AE8	.85	30P4	.75	DL92	.35	ECH38	1.25
6A65	.42	6G07	.75	12AT6	.88	30P1L	.68	DL96	.55	ECH42	.70
6A16	.55	6H6U2	.25	12AU6	.45	30P1L3	.75	DM70	.44	ECH81	.30
6A77	1.00	6J5GT	.40	12AV6	.50	30P1L4	.80	DM77	5.00	ECH83	.44
6A8E	.88	6J6	.25	12BA6	.40	30P1L5	.80	DY87/8	.40	ECH84	.44
6A16	.80	6J7G	.80	12BB6	.55	35A3	.65	DY92	.38	ECL80	.40
6A16	.88	6J8A	.75	12BH7	.50	35D5	.75	E80CC	1.65	ECL82	.34
6A16	.88	6J8A	.75	12E1	3.00	35L6GT	.55	E80F7	1.20	ECL83	.57
6AX4	.75	6K80	.45	12J7GT	.55	35W4	.40	E83F	1.20	ECL84	.60
6B8G	.80	6L1	2.00	12K5	1.00	35Z3	.75	E88CC	1.00	ECL85	.60

ECL86	.40	EZ41	.27	PRN45	.60	UCF80	.65	AA119	.17	BA129	.14	OA70	.17
EP23	1.50	GY301	.75	PEN45DD	.80	UCH22	.70	AA129	.17	BA130	.15	OA71	.17
EF40	.75	GZ32	.54		.80	UCH42	.70	AA129	.17	BA153	.17	OA79	.10
EF41	.70	GZ33	1.00	PEN46	.50	UCH61	.88	AA129	.17	BC107	.14	OA81	.10
EF42	.55	GZ34	.65	PEN45DD	.80	UC128	.88	AC107	.17	BC108	.14	OA85	.09
EF73	1.50	GZ37	.87		3.00	UC135	.55	AC113	.28	BC113	.28	OA90	.14
EP78	.28	HABC90	.50	PENDD		UF41	.70	AC126	.14	BC115	.17	OA91	.10
EP93	.95	HL2DD	.75	40Z0	2.00	UF42	.70	AC127	.19	BC116	.28	OA95	.10
EP85	.84	HL4DD	.88	PL32	.50	UH50	.45	AC128	.28	BC118	.25	OA200	.10
EP86	.80	HL4DD	.70	PL36	.55	UF85	.44	AC132	.22	BCY10	.50	OA202	.11
EP99	.87	HN309	1.50	PL81	.44	UF86	1.00	AC134	.28	BCY12	.55	OC22	.48
EP91	.87	HL4DD	.70	PL81A	.55	UF89	.88	AC136	.22	BCY33	.22	OC23	.48
EP92	.40	HVR2A1	1.00	PL82	.40	UL41	.65	AC137	.28	BCY34	.25	OC24	.48
EP97	.80	KT2	.50	PL83	.45	UL84	.42	AC138	.28	BCY38	.25	OC25	.48
EP98	.80	KT41	.98	PL84	.38	UH50	.45	AC139	.28	BCY39	.25	OC35	.47
EP184	.29	KT44	2.00	PL84/500	U41	.49	AC138	.45	BCZ11	.88	OC44	.11	
EP184	.29	KT66	1.40		.67	UY85	.88	AC176	.61	BF158	.88	OC45	.19
EP804	1.20	KT81	2.00	PL605	1.15	U10	1.00	AC177	.81	BF159	.88	OC46	.17
EP804	1.20	KT81	2.00	PL608	.90	U12/14	1.00	AC177	.88	BF163	.88	OC70	.14
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC71	.14
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC72	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC73	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC74	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC75	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC76	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC77	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC78	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC79	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC80	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC81	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC82	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC83	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC84	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC85	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC86	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC87	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC88	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC89	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC90	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC91	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC92	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC93	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC94	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC95	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC96	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC97	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC98	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC99	.19
EP804	1.20	KT81	2.00	PL609	1.15	U19	1.78	AC178	.88	BF173	.88	OC100	.19

MATCHED TRANSISTOR SETS:—
LP18 (AC113, AC154, AC157, AA120) 58p
per pack, 1—OC81D & 2—OC81, 47p, 1—OC82D & 2—OC82 58p, Set of 3—OC83 75p.

VALVES ALSO REQUIRED FOR CASH. LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.
All goods are unused and subject to the standard 90 day guarantee. Cash or cheque with order only. Despatch charges—Orders below £5, add 10p per order up to three items, each additional item 3p extra. Orders between £5 and £10 add 25p total. Orders over £10 are post free. Same day despatch. Any parcel insured against damage in transit for only 3p per order extra. Terms of business free on request. Many others in stock too numerous to mention.
Please enclose S.A.E. for reply to any correspondence.

STILL at £42.50
Solartron CD 711S-2 Double Beam Oscilloscope DC-9 mc/s; 3 mV/cm; trigger delay; crystal beam calibrator; 4" flat faced tube, in good working condition. Carr. £1.50.

12" LONG PERSISTENCE CRT.
Full spec. Price £7.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5.50. P. & P. 25p. (Not cased, not calibrated.)

NEW WIDE RANGE WOBBLULATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10" or 12" TV alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6 3V A.C. and use within minutes of receiving. All this for ONLY £5.75. P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR.
Four ranges. Independent amplitude controls, thermostat stabilised. Ready to use, 9V supply required. £7.85 each. P. & P. 25p. (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 5p each. P. & P. 5p. £1 worth of 'UFS'. Six Brand new capacitors all between 15V and 100V. Total capacitance not less than 7,000pfd. P. & P. 45p.

Large quantity of good quality components — **NO PASSING TRADE** — so we offer 3lbs of **ELECTRONIC GOODIES** for £1.50. Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 2 off 4pole 2 way etc.). 50p P. & P. 20p.

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors $\frac{1}{2}$ and $\frac{1}{4}$ watt, many high stabs, etc.

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio & Electronics School, P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME Block
ADDRESS Caps.
..... Please
..... W.C. 74

**BRITISH NATIONAL RADIO
AND ELECTRONICS SCHOOL**

Audio

THE HI-FI
MAGAZINE FOR
LEISURE LISTENING

Britain's exciting new-style magazine in music and hi-fi, AUDIO is about every important aspect of the modern sound scene from the make-up of sound, to the latest means of reproducing it . . . the equipment, its installation and its operation. AUDIO examines new trends, looks at the latest discs and tapes, shows you how to get the most for your money in clarity, definition and craftsmanship.

Audio

Published third Friday of each month 25p

FERRIC CHLORIDE

Anhydrous to Mil-spec in 1lb sealed packs. 1lb 55p (20p); 3lb £1.32 (30p); 10lb £3.85 (60p).

VERSATILE POWER UNIT

Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1-7-10-5V output with 2 extra capacitors. Brand new, only 83p (20p). Also available in a toy garage with press switch, lamp, etc. (Used for 'Hot Wheels'). Only £1.65 (30p).

AMPLIFIER UNIT

In fully screened case 5 1/2 x 5 x 3 1/2" 2 GET116 on heat sink, 2 zeners, 3 pot cores, 4 small transformers, 1 1/2 R's, C's, etc. 70p (30p).

3W CASED AMPLIFIER

Polished wooden cabinet 14 x 13 x 9", containing a sensitive (20uV) 4 valve amplifier with tone & volume controls. Gives 3 watts output to the 7 x 4" 3Ω speaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation. £3.50 (£1). Suitable cassette £1.10 (30p). Spare head 33p. Tape (ex-computer) 75p (20p). Amplifier chassis only, complete and tested (2 x ECC83, EL84, EZ80) + speaker £2.50 (40p).

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, pots, switches, + PC boards with transistors & diodes, also crystals and loads of odds and ends. Amazing value £1.82 (40p).

Scopes in stock for callers, ring for details. SAE List. All prices include VAT. Carriage in brackets, small parts 5p.

DEKATRON UNITS

Contain 2 CV2271 dekatrons, 2 4-digit resettable counters, 2 sealed relays, 2 x ECC81, R's, C's, etc. Only £1.70 (30p).

COMPUTER PANELS

31bs asstd £1.10 (30p); 71b £2.20 (40p); 561b £12 (£2). 12 high quality panels with IC's, power transistors, trim pots etc. £2.20 (30p), 100-£12 (£1). Panel with 72k 100pF 33p (10p). Pack containing 50 14pin DIL IC's, Inc. 7400, 04, 10, 20, 30 7474 etc, also MC types £2.20 (20p).

COMPONENT PACKS

500 asstd resistors £1.10 (20p), 2500 £4 (50p) 10000 £13 (£1), 100000 £80 + carr. 150 poly, ceramic, mica caps 60p (10p).

NEW COMPONENTS

400V 5A SCR 60p, 200V 44p, OC71 9p, 14 for £1.10, OC81D 9p, 100/£5.50, 741C TO92 35p, 2N3055 30p, .05/500V disc 100/£1.65, 1000pF disc £1.65/100 80+80+20uF 350V 10p, 10/83p (30p), 8uF 2500V £2.20 (50p), 4 pole 8-way Yaxley switches 33p (8p), 2 pin DIN plug 10p, 5 pin 160° 11p, 3-5mm plug 8p, phono 5p, 7 pin DIN plug 11p, 6 pin DIN plug 11p, speaker cable 5p/metre 4 core individually screened 20p/metre.

Transformers, mains PRI, SEC 16-0-16V @ 1 1/2A+9V tap £1.85 (30p); 350V @ 375 mA, 250V @ 75mA, 6-3V @ 1A £2.20 (65p), P.O. 4 Digit Counters 2500Ω 50V 55p (12p) 33pF 12kV caps 70p/10 2uF 600V block paper 33p (10p) G150/2D Thyratrons ex-equip 33p, 6 x 4" 4Ω New Speakers £1.10p (20p). Hewlett-Packard 100MHz counter/timer 524D £86+carr.

GREENWELD ELECTRONICS (PW4)

51 SHIRLEY PARK ROAD, SOUTHAMPTON

New wholesale/retail shop and mail order dept. Other retail shops at 21 Deptford Bdy, SE8 & 38 Lower Addiscombe Rd, Croydon.

poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker
Super-thin construction
permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£7-50 each Stereo pair £14-50

INCLUSIVE OF VAT AND POSTAGE

web europa

P.O. Box 162, Watford WD1 1AA



W.H.M. 20W AUDIO POWER AMPLIFIER

- ★ involves radical departures in conception.
 - ★ Class A performance with Class B economy.
 - ★ T.H.D. < 0.05% at all frequencies and power levels.
 - ★ No crossover distortion.
 - ★ Unsurpassed stability into reactive loads.
- £7.28 + VAT. £15 per stereo pair inc.
Full spec. on written request.

Sydney House, 35 Villiers Road, Watford

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in.



£6.75 Post 35p.

PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Chrome fittings. £4.50 Post 35p. Motor board cut for BSR deck.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2 x 10 x 8 1/2 in. 3 watts per channel, plays all records 33 rpm, 45 rpm. Separate volume & tone controls. 240v AC mains.



Attractive Teak finish Weight 13lbs. Bargain Price £25 85p carriage

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob Turn on or off at full or intermediate settings. Makers Last list price £4.50. Brand new and fully guaranteed. Fully insulated. OUR PRICE £1.65 Post 25p



WEYRAD P50—TRANSISTOR COILS

BA2W Ferrite Aerial. 85p Driver Trans. LFDT4. 65p Osc. P50/1AC. 40p Printed Circuit, PCA1. 65p I.F. P50/ECC 470 kc/s. 40p 3rd I.F. P50/3CC. 40p Spare Cores. 3p OPT1. 65p Ferrite Rod 8 x 1/2 in. 20p 6 x 1/4 in. 20p 3 x 1/2 in. 10p

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 65p. D.P. 75p. Edge 5K.S.P. Transistor 25p

80 Ohm Coax 5p. yd. BRITISH AERIALITE. AERAXIAL-AIR SPACED 40 yd. £1.75; 60 yd. £2.00. FRINGE LOW LOSS Ideal 625 & colour 10p yd.

8in & 10 x 6in ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 c/s. Bass resonance 55 c/s. 8 ohm 10 watt. £3.75 Each Post 52p 10 inch 12 watt £4.50



E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. £4.50 State 8 or 8 or 15 ohm. (As illustrated) Post 25p

With flared tweeter cone and ceramic magnet, 10 watt. Best res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p



BOOKSHELF CABINET

Size 16 x 10 x 9 1/2 in. teak finish £6.60 Post 25p

E.M.I. 13 x 8 in. BASS WOOFER, 20 WATTS 15Ω RUBBER CONE SURROUND. £5.50 Post 25p.

BLANK ALUMINIUM CHASSIS. 18 s.w.s. 2 1/2 in. sides 6 x 4 in. 45p; 9 x 6 in. 55p; 10 x 7 in. 65p; 12 x 8 in. 85p; 14 x 9 in. 90p; 16 x 8 in. 90p; 12 x 8 in. 50p; 18 x 10 in. 21. ALUMINIUM BOXES 3 x 3 in. 31p; 4 x 4 in. 41p; 6 x 4 in. 41p; 9 x 4 in. 41p; 12 x 4 in. 41p; 12 x 4 in. 41p. 21. ALUMINIUM PANELS 18 s.w.s. 6 x 4 in. 12p; 8 x 5 in. 19p; 14 x 3 in. 20p; 10 x 7 in. 24p; 12 x 6 in. 25p; 12 x 8 in. 34p; 16 x 8 in. 34p; 14 x 9 in. 40p; 15 x 12 in. 47p; 16 x 10 in. 60p FAXOLIN PANEL 10 x 8 in. 20p.

SPECIAL OFFER

100 ohm 20W Rheostat 2 1/2 in. diam. Ceramic Former, screw terminals, 1/2 in. diam. spindle. 95p. Post 25p.

ANOTHER RGS BARGAIN!

ELAC 9 x 6in. HI-FI SPEAKER, TYPE 59RM. THIS FAMOUS AND WIDELY USED UNIT, NOW AVAILABLE AT BARGAIN PRICE £3.30. 10 WATT, 8 OHM. CERAMIC MAGNET.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2.20 Post Details S.A.E. Size 3 1/4 x 1 1/4 in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line. 200-300. c.d. operation. Size 1 1/2 x 1 1/2 x 1". Response 25 kc/s. to 25 Kc/s. 26 dB gain. For use with transistor equipment. Post Full instructions supplied. Details S.A.E. 99p 20p

E.M.I. WOOFER AND TWEETER KIT

Woofer 10 1/2 x 6 1/2 in. Ceramic Magnet, 44oz. 13,000 lines. Tweeter 3 1/2 in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms. Power 12 watts. £6.75 Post 45p.

BRITISH FM/VHF TUNING HEART

88 to 108 M/Cs British made. 2 Transistors ready aligned requires 107 M/Cs I.F. Complete with tuning gang. Connections supplied but some technical experience essential. Our price £3.95 Post 20p

MAINS TRANSFORMERS

Eagle MT12 12-0-12V 50mA. 90p
250-0-250 80 mA. 6.3V 3-5A 6.3V 1A or 5V 2A. 25.00
350-0-350 80 mA 6.3V 3-5A. 6.3V 1A or 5V 2A. 23.00
300-0-300V 120mA. 6.3V 4A C.T.; 6.3V 2A. 23.25
MINIATURE 220V 20mA. 6.3V 1A 2 1/2 x 2 1/2 in. 75p
MIDGET 220V 45mA. 6.3V 2A 2 1/2 x 2 1/2 in. 90p
HEATER TRANS. 6.3V 1 1/2 amp. 75p
GENERAL PURPOSE LOW VOLTAGE. Trapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V 23-00
1 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 23-00
2 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 24-00
3 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 23-00
5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 29-75
5, 8 and 18V 5 amp £1.20. 3 amp, 3, 5, 8, 10, 13 and 5-0-5V 20.00, Dito 5 amp. £1.50; 6-0-6V 500mA 90p
9V 1 amp 95p 12V 300mA 75p 12V 600mA 85p 12V 750mA 95p
40V 1 amp £1.75 5 amp £4.50
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £2.25; 500W 26.25; 750W 51.00; 1000W 21.00
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1 1/2 amp £1.50; 2 amp £1.80; 4 amp £3.50
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2.4 amp £4.5 amp £4.50
FULL WAVE BRIDGE CHARGER RECTIFIERS; 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE £10 Carr. Famous make. (Value 218) 50p
Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V .. 14p	100/25V .. 10p	32+32/350V .. 40p
4/350V .. 14p	250/25V .. 14p	50 50/300V .. 50p
8/450V .. 18p	500/25V .. 20p	60+100/350V .. 85p
16/450V .. 22p	1000/25V .. 35p	32+32/250V .. 20p
32/450V .. 35p	1000/50V .. 47p	32+32/450V .. 60p
32/500V .. 50p	8+8/450V .. 22p	32+32+32/350V 85p
28/25V .. 10p	8+8/450V .. 25p	32+32+32/450V 85p
50/50V .. 10p	16+16/450V 40p	

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p. 500mF. 12V. 15p; 25V. 20p; 50V. 30p. 1000mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p. 2000mF. 47V. 25V. 42p; 50V. 57p. 5500mF. 50V. 62p; 8000mF. 25V. 47p; 50V. 65p. 5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 50V. 85p; 50V. 95p.

CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0-1 4p, 0-5 15p; 1mF 15p; 2mF 150V 15p. 500V-0-001 to 0-05 4p; 0-1 5p; 0-25 8p; 0-47 25p. SILYER MICA. Close tolerance 1%, 2-2-500pF 6p; 560-2-200p 3p 10p; 2,700-5-600pF 20p; 6,800pF-0-1m, mfd 30p; etc. TWIN GANG. 400 20pF x 175pF 65p; 500pF standard 75p; 365+365 with 25+25pF Slow motion drive 50p. SEORT WAVE. SINGLE. 10pF 30p; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS. 250V AC/DC Amber 25p. RESISTORS. 1W. 1/2W. 1W. 20% 1p; 2W. 5p. 10Ω to 10MΩ. HIGH STABILITY. 1/2W. 2% 10 ohms to 8 meg. 10p. Dito 5% 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each. TAPE OSCILLATOR COIL. Valve Type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 12in. 50 watt GROUP 50/12 or 15 ohm high power full range. Professional quality. £17.60

BAKER MAJOR 12" £9.90

Post free 30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total area of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50 Post free Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS Post free
'Group 25' 12 inch £8.80 25 watt 35 watt 3 or 8 or 15 ohm
'Group 35' 12 inch £9.90 35 watt 3 or 8 or 15 ohm
'Group 50' 15 inch £22 80 watt 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS
For 12in. or 10in. dia. speaker 20 x 13 x 9" £10.50 Post 25p
For 13 x 8in. or 8in. speaker 16 x 10 x 9" £6.60 Post 25p
For 8 x 6in. speaker 18 x 8 x 6" £4.95 Post 25p
For 6in. and tweeter 12 x 8 x 6" £4.00 Post 25p
LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

EMI 6in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns, Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/4 in. Suitable Tweeter £2.00. £4



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt, 8 ohm Suitable £1.90 Post 20p Crossover £1.30

SPEAKER COVERING MATERIALS. Samples Large S.A.E. HORN TWEETERS 2-18kc/s. 10W 8 ohm or 15 ohm £1.25 CROSSOVERS TWO-WAY 3000cps 3 or 8 or 15 ohm £1.30 LOUDSPEAKERS 3 OHMS. 7 x 4in. £1.25; 6in. £1.60. 8 x 5in. £1.60 8in. £1.75; 10 x 6in. £1.90; 12in. £2.00. SPECIAL OFFER: 8ohm, 2 1/2in.; 2 1/2in. 35 ohm. 2 1/2in. 2in. 25 ohm. 2 1/2in. dia. 5in. dia. 6" x 4in. 7" x 4in. 8" x 5in. I.T. TYPH 3 ohm, 2 1/2in.; 2 1/2in.; 2 1/2in. dia. (6 x 4in. 8 ohm £1.50) RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. diameter 4 watt £2.50, 10in. diameter 5 watt £2.50; 12in. diameter, 6 watt £2.95. VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50:1 40p. MIKE trans. mu metal 100:1 £1.25.

MAJOR 100 WATT ALL PURPOSE GROUP OR DISCO AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass control. SUPER VALVE MODEL 100 WATT CALLERS ONLY 46p. £49 Carr. £1.00



BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIKED. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £4.50

TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, treble and bass control 18V. DC operation. £4.50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p COAXIAL OUTLET BOXES, surface, 35p. BALANCED TWIN FEEDER 300 ohms 5p yard. JACK SOCKET 5id. open-circuit 14p. closed-circuit 25p. Chrome Lead Socket 4p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS Std. Chrome 20p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 6-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 10p; CAN 5p.

REVERSIBLE 4 POLE MOTOR £2.25

1,400 r.p.m. Reversible 42 Watt, Post 25p spindle 1 1/2 x 7/16", size 3 1/2 x 3". As illustrated. With Cooling Fan 240V A.C.

E.M.I. GRAM MOTOR £1.00
120v. or 240v. A.C. 2,400 rpm. 2-pole Post 25p.
70mA. Size 2 1/2 x 2 1/2 in.

RADIO COMPONENT SPECIALISTS


Minimum post 20p. Illustrated Brochure, Radio Books & Components Lists 10p.

337 WHITEHORE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

Sinclair Project 80

exciting

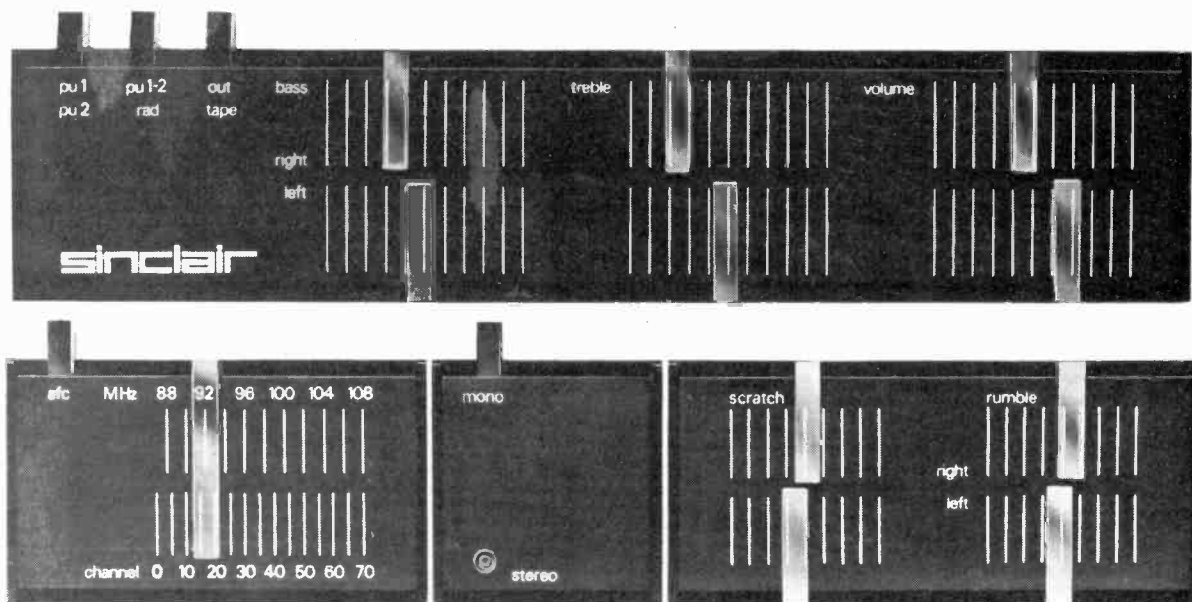


only $\frac{3}{4}$ " deep x 2" high

Living with hi-fi takes on new meaning with Sinclair Project 80. The electronics of these revolutionary new modules are all contained within elegantly designed matching cases no more than three-quarters of an inch deep. They are designed for mounting on any appropriate flat surface by means of 6BA bolts extending from the rear of each module and which pass through suitably drilled holes. Connections are taken away out of sight in a similar manner. The possibilities opened up by Project 80 are endless – superb hi-fi systems can be installed in ways hitherto only dreamed about and never before made practical. No more cutting out and shaping to put modules in position. A few holes drilled with the aid of templates supplied and the job is done. Now you need never again be faced with problems of keeping the hi-fi from clashing with carefully thought-out furnishing schemes. (That will surely please wives!) Slider controls have been introduced in place of knobs and all modules in the range incorporate new up-dated circuitry with emphasis on performance standards and built-in protection against overload and shorting. The aim was to re-think modular construction completely – to make it infinitely more versatile, even simpler and more reliable – the result – Project 80 – another triumph for Sinclair, and the most exciting construction modules ever.

the slimmest, most elegant hi-fi modules ever made

Typical Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	£5 45 + 54p V.A.T.
Majors powered record player	Z.40, PZ.5	£10 43 + £1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; PZ.6	£30 83 + £3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amp.	2 x Z.60s, Stereo 80; PZ.8	£33 83 + £3.38 V.A.T.
Indoor P.A.	Z.60, PZ.8	£14 93 + £1.49 V.A.T.

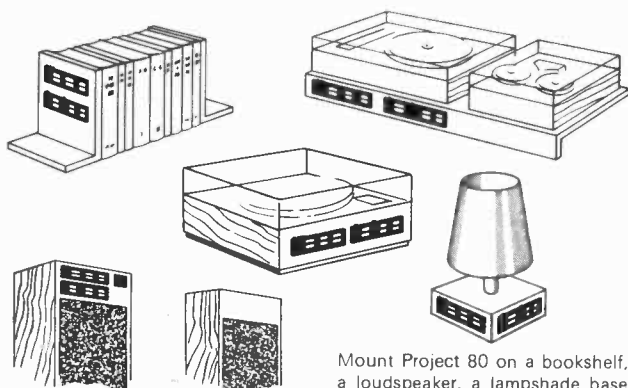


Mount Project 80 on a bookshelf, a loudspeaker, a lampshade base a false wall with two Q.16 loudspeakers... almost anywhere.

Project 80 FM tuner, decoder, and A.F.U. may be added as required

new thinking in modular hi-fi

Stereo 80 pre-amplifier and control unit

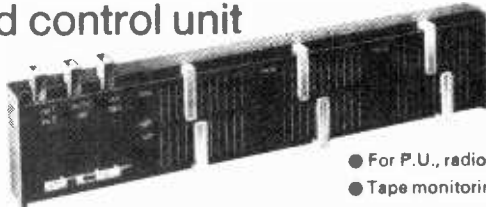

- For P.U., radio and tape
- Tape monitoring switch
- Simplest ever fixing


Each channel has its own separate tone and volume controls operated by sliders, enabling ideal environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry that ensures the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS

Size - 260 x 50 x 20mm (10 1/2 x 2 x 3/4 ins)
 Finish - Black with white indicators and transparent sliders
 Inputs - Magnetic pick-up 3mV RIAA corrected; Ceramic pick-up 300mV
 Radio 300mV; Tape 30mV
 Signal/noise ratio - 60dB
 Frequency range - 20Hz to 15KHz ± 1dB, 10Hz to 25KHz ± 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV + AB monitoring for tape
 Controls - Press button for tape, radio and P.U. Sliders for volume, bass (-12dB to -14dB at 100Hz) treble (+11dB to -12dB at 10KHz)

R.R.P. **£11.95** +£1.19 V.A.T.

Project 80 FM tuner and stereo decoder

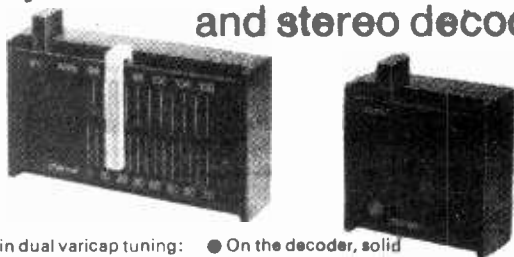

- Twin dual varicap tuning: 4 pole ceramic filter: switchable A.F.C.
- On the decoder, solid state stereo indicating beacon.

Making the Project 80 F.M. tuner and decoder available separately gives a wider choice of systems and saves money where stereo reception may not be required. The tuner is a triumph of electronic design and assures excellent performance. The decoder gives a 40dB channel separation with 150mV output per channel. Both units may be used with other than Project 80 systems.

TECHNICAL SPECIFICATIONS OF TUNER

Size - 85 x 50 x 20mm (3 1/2 x 2 x 3/4 ins)
 Tuning range - 87.5 to 108 MHz
 Detector - i.c. balanced coincidence for good A.M. rejection
 One i.c. equal to 26 transistors
 Distortion - 0.2% at 1KHz for 30% modulation
 4 pole ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Output - 300 mV for 30% modulation
 Power requirements - 23 to 33 volts

DECODER

Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/4 ins)
 One +19 transistor i.c.

R.R.P. **£11.95** +£1.19 V.A.T.

R.R.P. **£7.45** +0.74 V.A.T.

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge.

Z.40 & Z.60 power amplifiers totally short-circuit proof



Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.

Z.40 TECHNICAL SPECIFICATIONS

Size - 55 x 80 x 20mm (2 1/4 x 3 1/4 x 3/4 ins) 9 transistors
 Input sensitivity - 100mV
 Output - 15 watts RMS continuous into 8 Ω (35V)
 Frequency response - 10Hz - 100KHz ± 1dB
 Signal/noise ratio - 64dB
 Distortion - at 10 watts into 8 Ω less than 0.1%
 Power requirements - 12 to 35 volts

Z.60 TECHNICAL SPECIFICATIONS

Size - 55 x 98 x 15mm (2 1/4 x 3 7/8 x 3/4 ins) 12 transistors
 Input sensitivity - 100-250mV
 Output - 25 watts RMS continuous into 8 Ω (45V).
 Distortion - typically 0.03%
 Frequency response - 10Hz to more than 200KHz ± 1dB
 Signal/noise ratio - better than 70dB
 Built-in protection against transient overload and short circuiting
 Load impedance - 4 Ω min, max safe on open circuit

Z.40 R.R.P. **£6.45** - 0.54 V.A.T. Z.60 R.R.P. **£6.95** - 0.69p V.A.T.

Project 80 active filter unit

Makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls applied to each channel make it easier to obtain ideal stereo balance.

TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/4 ins)
 Voltage gain - minus 0.2dB
 Frequency response - 36Hz to 22KHz controls minimum
 Distortion - at 1KHz - 0.03% using 30V supply
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct. slope
 L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct slope

- For scratch and rumble control
- Transistorised active circuitry

R.R.P. **£6.95** +0.69 V.A.T.

Power supply units


PZ.8

Stabilised. Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 45V.

R.R.P. **£7.98** + 0.79p V.A.T.
 Without mains transformer

PZ.5 30V un stabilised
 R.R.P. **£4.98** + 0.49p V.A.T.

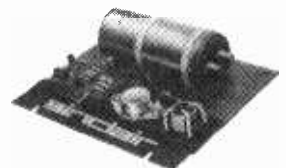PZ.6 35V, stabilised
 R.R.P. **£7.98** + 0.79p V.A.T.



sinclair

Sinclair Radionics Ltd. London Road, St. Ives, Huntingdon PE17 4HJ
 Telephone St. Ives (0480) 64646

To **SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ**

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 10p per word (minimum 12 words), box number 20p extra. Semi-displayed setting £8.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Aerials

GENUINE FULL SIZE
18 element TV aerial
as used by leading
TV companies

ITV, BBC1 & 2/B/W & Colour Guaranteed Perfect Pictures. Save ££s We supply this genuine UHF aerial for only £2.20 can be fitted outside or inside. Quality made technically advanced design Precision grid/reflector eliminates ghosting Complete with clamp instructions advice Money Back Refund Wall/Caravan Bracket 25p Low Loss Cable 10p per yard Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters SEND DIRECT TO DEPT. PW10 219 Mansfield Rd. Nottingham.

FOR ONLY **£2.20** + 35p cart

IMPERIAL TRADING INDUSTRIES LTD.
the quality Annual Specialists

J & A TWEEDY LTD. Incorporating R. Baines. All Prices Include VAT. Postage paid on aerials mainland. Full range of J Beam Aerials for TV, FM Stereo and Amateurs. Parabeam: PBM 12 £3.60, PBM 18 £4.60. Multi-beam: MBM 30 £4.70, MBM 46 £7.40, MBM 70 £12.95. Stereobeam: SBM2 £3.15, SBM 3 £4.70, SBM 4 £5.15, SBM6 £7.75. Aerial Rotators: AR30 £27.50, AR40 £33.00 (postage 50p). Amplifiers: VHF or UHF £9.07, Setback £4.50. Certron Cassettes: C60 43p, C90 58p, C120 71p. Copal Digital Clocks: 222 £5.50, 227 with alarm £7.10 (post 25p). Amtron Kits: a good range of these in stock. BIB Hi-Fi Accessories. Opening times Tues-Sat 9 till 5.30. 79 Chatsworth Road, Chesterfield S40 2AP.

Wanted

TOP PRICES PAID for NEW VALVES and TRANSISTORS
popular T.V. and Radio types.
KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

EARLY WIRELESS receivers, components and magazines, details to Johnson Raffles, Haverbreaks, Lancaster.

WANTED. Radio and TV Servicing books from 1964 onwards. £2.00 per copy, paid by return of post. Bell's Television Services, 190 Kings Road, Harrogate, Yorkshire. Telephone 0423-55885.

For Sale

TV LINE OUTPUT TRANSFORMERS
Tidman Mall Order Ltd., 236 Sandycombe Rd., Richmond, Surrey. TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

LIGHTSHOW PROJECTORS from only £17, effect wheels from only £4. Many lightshow bargains at **ROGER SQUIRE'S** (Disco Centre), 176 Junction Road, London N19. Tel. 01-272 7474.

VALVES LARGE STOCK, 1930 to 1974. SAE for quotation. List 10p. Cox Radio, The Parade, East Wittering, Sussex. Phone West Wittering 2023.

LIMITED OFFER. 100 each nuts, bolts & washers. 300 pieces, £1.20. Available in 2, 4, 6 or 8BA. State which. Also 300 assorted self tap screws, £1.20. Prices include VAT, post. Lewis, 10 Marple Hall Drive, Marple, Stockport, SK6 6JN.

Service Sheets

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
ALL AT 40p EACH

"PLEASE ENCLOSE LARGE S.A.E WITH ALL ENQUIRIES & ORDERS"
Otherwise cannot be attended to
(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE
We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 20p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Record Players, Tape Recorders, etc., from 5p with free Fault-Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

Books and Publications

Technical Books - Radio & Electronics

Handbook of Tested Transistor Circuits.....	£0.40
Radio Servicing for Amateurs.....	£0.25
Radio TV and Electronics Data Book.....	£0.20
Cool Design and Construction Manual.....	£0.30
How to Solve Solid State Circuit Troubles.....	£1.75
Transistor Circuits Manual No. 1.....	£0.15
Transistor Circuits Manual No. 2.....	£0.15
Jack Darr's Service Clinic.....	£1.35
Transis Circuits for Radio Controlled Models.....	£0.40
Rad & Electr Colour Codes and Data Chart.....	£0.15
Handbk of Transistor Equiv. and Substitutes.....	£0.40
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0.75
Radio Servicing Problems.....	£0.45
Electronic Circuits for the Amat Photographer.....	£0.60
Handbook of Simple Transistor Circuits.....	£0.35
How to build Solid State Audio Circuits.....	£1.75
Sound and Loudspeaker Manual.....	£0.50
Practical Car Radio Handbook.....	£0.30
Radio TV and Industrial Tube & Valve Equiv.....	£0.40
Transistor Test Equip and Servicing Manual.....	£0.25
Television Servicing Vol. No. 1.....	£0.85
Television Servicing Vol. No. 3.....	£0.60
Television Servicing Vol. No. 4.....	£0.85
Using an Oscilloscope.....	£0.70
Servicing Transistor Radio Receivers.....	£0.75
Television Timebase Circuits.....	£1.00

NEW TITLES NOW AVAILABLE

2nd Book of Hi Fi Loudspeaker Enclosures.....	£0.60
Manual of Electronic Circuits for the Home.....	£0.50
Modern Crystal Set Circuits for Beginners.....	£0.35
Electronic Novelties for the Motorist.....	£0.50
2nd Book of Transistor Equiv. & Substitutes.....	£0.95
Handbook of Electronic Musical Novelties.....	£0.50
Transistorised Novelties for Hi Fi Enthusiast.....	£0.35
Fault Location Exercises in Rad. & TV Vol. 1.....	£0.80
Fault Location Exercises in Rad. & TV Vol. 2.....	£1.35
Colour TV Picture Faults.....	£2.50
Practical Transistor Novelty Circuits.....	£0.40
Semi-conductors from A-Z.....	£1.50
Radio Receiver Construction using ICs & Transis.....	£0.60
104 Ham Rad. Proj. for Novice & Technician.....	£1.25
ICs & Transistor Gadgets Construction Handbk.....	£0.60
Integrated Circuits Equiv. & Substitutes Hbk.....	£0.75

PLEASE ADD 10% FOR POSTAGE & PACKING
FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

UFO Charts: Wave Prediction, 49p; Daily Flight Pattern, 44p; Map, 44p; TV UFO Detection, 2 Optical Circuits, 55p; Propulsion Theory, 55p; Circuits: Transistor Optical, 66p; Radiation/Optical, 40p; Microdetector with memory, LSI 75p. R. & E., Highlands, Needham, Suffolk.

Ladders

LADDERS. 'Special Offer' Unvarnished triples. 9ft 7in closed—23ft lin extended. £18.90 delivered. Home Sales Ladder Centre (WLS2) Haldane (North) Halesfield (1) Telford, Shropshire. Tel: 0952 586644.



The international music, electronics and leisure Group.

Estimators

Experienced Estimators are required in the Production Department of the Systems and Weapons Division, EMI Electronics Ltd. (Feltham & Hayes, Middx.)

Shop Loading Estimators

will be required to compile manufacturing and/or assembly and wiring estimates, in terms of hours, for shop loading. They will participate in shop cost control and reporting procedures.

The work involved is light electro-mechanical devices and electronic equipment.

Works Cost Price Estimators

will have the skills of a Shop Loading Estimator and in addition be required to estimate the costs of labour, overheads, material and components, liaising with other departments so as to produce a complete Works Cost Price estimate suitable as a basis for quotation to the customer.

Familiarity with Ministry Production Contracts, would be an advantage.

We would also consider the training, for estimating, of men with appropriate practical shop floor experience.

Applicants should apply in writing or by telephone to:

J. Morrison, Personnel Officer, EMI Electronics Ltd., Victoria Road, Feltham, Middlesex. Tel: 01-890 3600 Ext. 44 or outside normal working hours please ring 01-890 3921.

**MEN!
£70p.w.
can be yours**

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

**London
Computer Operators
Training Centre**

T68, Oxford House
9-15, Oxford Street, W.1.
Telephone: 01-734 2874

Educational

C AND E EXAM

Make sure you succeed with an ICS home study course for C and E Electrical Installation Work & Technicians, Radio/TV/Electronics Technicians, Telecomms Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits.

Get the qualifications you need to success. Free details from: International Correspondence Schools, Dept 732P, Intertext House, London SW8 4UJ. Or phone 01-622 9911.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

AMIMI, MAA/LMI DIPLOMA, City & Guilds, etc. Thousands of passes. For details of postal courses in all branches of Engineering and illustrated book—FREE—BIET (Dept. BPW.03) Aldermaston Court, Reading RG7 4PF. Accredited to CACC. Member A.B.C.C.

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, T.V. Computers, Draughtsmanship, Building, etc. FREE book form: BIET (Dept. BPW.04 Aldermaston Court, Reading, RG7 4PF. Accredited by CACC. Member A.B.C.C.

Receivers and Components

A BONANZA FOR CONSTRUCTORS— B. B. SUPPLIES OFFER

CURLIES, 5ft., 3-core, 15p ea. 4-core, 20p ea. STRAIGHT Cords, 25ft., 4-core, 25p ea. DIODES, Silicon, CV7040 (OA 202), 3" leads 4 for 25p. DIALS, (GPO Type), plastic face, metal mech. 30p ea. TRANSISTOR panels, type M4, comprising: 5 BCY34, 4 ACY 17, diodes, resistors & capacitors (ex new equipment—rel. long leads) 50p ea. INTRODUCTORY OFFER: 1 of each above plus surprise item for £1-25p (offer ends 31-7-74). MONEY back guarantee—prices Inc. VAT and pp. ORDERS or SAE for complete list to:-
38 Heathwood Gardens, Swanley, Kent BR8 7HM

MORE RANGES FOR LESS MONEY

AC/DC Multimeter type U4324

A-DC 0-06-3A - 6 Ranges.
A-AC 0-3-3A - 5 Ranges.
V-DC 0-6-1200 V - 9 Ranges.
V-AC 3-900 V - 8 Ranges.
Freq.: In the range of 45 to 20KHz
Resistance: 500 Ohm to 5 MOhm
5 Ranges. Decibel: -10 to +12dB
Accuracy $\pm 2.5\%$ DC $\pm 4\%$ AC
Dimensions: 167 x 98 x 63 mm.



Only **£8.00**



SUPRETESTER 680R ICE
10 Fields - 80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC - Temperature -50C to +200C - Magnetic fields up to 15 KGauss - Phase indicator - EHT 25kV Electronic Volt Ohm - meter Transistor Diode Tester etc.


Dimensions: 128 x 95 x 32 mm - 300 grams - 20kOhm/V Accuracy 1% DC. Ask for free catalogue

£18.50

Accessories Extra

ALPHANUMERIC NIXIE TUBES B7971

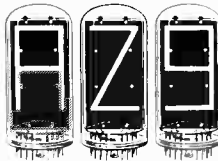The Alpha-numeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including:



★ All DC operation ★ Uniform, continuous line characters of equal height
★ Memory with simple solid state drive circuits
★ Readability in high ambient light—200 foot-lamberts brightness ★ Long life with no loss of brightness ★ Character height 2 1/2".

Price only **99p** each plus 16p P/P.

Add 10% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel: 837 7781

12 VOLT FLUORESCENT LIGHTS

(as illustrated by Thorn/AEI)



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12 ins. 8 watt **£4.00** post paid
Including V.A.T.
Callers Welcome

For lists or enquiries, large s.a.e.
SALOP ELECTRONICS, 23 WYLE COP
SHREWSBURY, SHROPSHIRE.
Tel.: Shrewsbury 53206

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel, choice of 70 types, send for free list, Bazelli Instrument Cases, Dept 25, St. Wilfrids, Foundry Lane, Halton LA2 6LT, Nr. Lancaster.

HARDWARE SUPPLIES. Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon. Warwks. CV37 9JF.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ Pocket-sized **MAXI-VOLT** Big Inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.). send **£1.35** for your Maxi-Volt now!


★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£5.90** for yours now!

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send **£2.20** now! (all prices include V.A.T., packing & postage.)

Send remittance to:

BOFFIN PROJECTS,
4 CUNLIFF ROAD,
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)

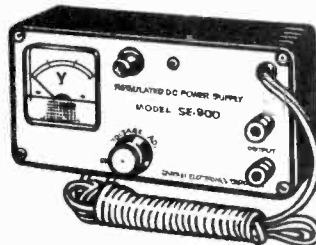Or for more details, send 20p for lists. plus free design project sheet.



DC POWER SUPPLIES

Regulated power supply variable up to 15V 0.5A. Model SE800. Ideal for development work. **£11**

Cash with order includes VAT & p. & p.

J. H. ASSOCIATES LTD.
Cricketfield Lane, Bishop's Stortford, Herts.

MICRO ELECTRONIC TRANSMITTER

(BUILD OR BUY)



A precision piece of equipment that has been designed and produced after 2 years research and development. The smallest transmitter available in the U.K. 2" x 1" approx. Fits in the palm of your hand. Can pick up and transmit voices and minute sounds, excellent range, 500 yds at least. Can be worn round the neck, held in the hand or placed on a shelf. Receive on a VHF radio. Universal battery connections enable use of P13 battery operates 9-15 volts, no other connections, completely self contained; to operate, simply switch on. Used the world over, many applications. Fully transistorised printed circuit. Guaranteed for 12 months.

Assembled unit ready to use **£15.80**
Kit with step-by-step assembly instructions **£11.60**
If required, suitable radio for receiving transmitter **£13.80**

Ins., P. & P. 45p.

MULHALL ELECTRONICS (PW)

Arldglass, Co. Down, U.K. BT30 7SF
(Exporters to 14 countries)

To comply with regulations, amateur licence required from M.P.T.C.

TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete kit Post 35p

£9.80

Built tested and guaranteed Post 35p

£13.75

MINIKITS ELECTRONICS,
35a LANGLEY DRIVE, WANSTEAD
LONDON, E11 2LN (Mail order only)

AMAZING OFFER! ELECTRIC SOLDERING GUN WITH BUILT IN TRANSFORMER

A MUST FOR EVERY DIY MAN




UNIQUE SEE IN THE DARK LIGHT

INSTANT HEAT

ONLY **£2.25** P&P25p

This Soldering Gun is a MUST for D.I.Y. Men, Motorists, Mechanics, etc. A rugged, strong construction that will last a lifetime. Now you can do all those repairs that would normally cost you £2s at any electrical shop. Voltage 240 AC. 50c/s. LIMITED QUANTITY AVAILABLE. Similar product sells at **£4.50**. C.W.O. Immediate despatch. Refund if not delighted.

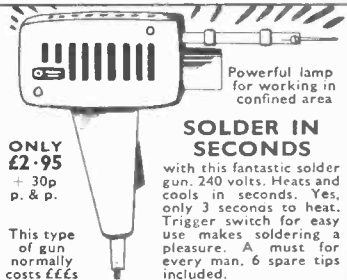V.G.S. INTERNATIONAL (SGW10)
Pickworth, Sleaford, Lincolnshire.



Powerful lamp for working in confined area

SOLDER IN SECONDS

with this fantastic solder gun. Heats and cools in seconds. Yes, only 3 seconds to heat. Trigger switch for easy use makes soldering a pleasure. A must for every man. 6 spare tips included.

ONLY **£2.95** + 30p p. & p.

This type of gun normally costs ££s more
Send now

10 days money back refund if not delighted.
To: **MAIL-SALES, DEPT. P.W.1,**
87 Queens Road, London, E17 8QR
(10 days money back undertaking)

Darned Electronic Wizardry

by Dewtron (VAT extra.)

Famous kits, e.g. waa-waa complete kit **£2.95**; Fuzz kit **£5.50** auto rhythm modules P & P 20p min. Ring Modulator modules **£8** and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.V. Ltd., 254 Ringwood Road, Ferndown, Dorset.

PRINTED CIRCUIT BOARDS. Any P.C.B. Published in **PRACTICAL WIRELESS/ELECTRONICS**, E.T.I. etc. etc. Any month any year. 5p/sq in. Postage Free. (Min. 50p). Also Artwork and/or photography undertaken. S.A.E. Footscap for full details. P. Lancaster, 11 Chesterton Road, Cambridge CB4 3AD.

LOW COST I.C. MOUNTING. Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

CAR RADIO/STEREO SPARES. Motorola, Radiomobile etc., Lists 10p. Atom Radio & Audio Services, Station Road, Walker, Newcastle-on-Tyne NE6 3UQ.

AERIAL WIRE. High quality p.v.c. covered multi-strand copper 25ft-23p (6p), 50ft-45p (9p), 75ft-67p (12p), 100ft-89p (15p), 150ft-£1-32p (23p), 200ft-£1-76p (25p), 250ft-£2-21p (26p), 300ft-£2-66p (30p). EGG insulators 11p pair (5p). P&P in brackets, SAE all enquiries. A.I. Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

PRACTICAL WIRELESS. First six Volumes 1932 on with index 100s others. Offers or exchange. Ham gear. Tel. 061-928 7632.

Please mention
PRACTICAL WIRELESS
when replying to
Advertisements

AERIAL BOOSTERS—£3-30

We make three types of Aerial Boosters:—
B45-UHF 625, B12-VHF 405, B11-VHF RADIO.

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3-30 :—
ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF85, PCF89, PCF90, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, PC66, PC88.

19" UHF/VHF (BBC2)—£6-00

Thorn 900 Series or Pyc, with set of spare valves. Carriage £2-00 (Untested).

100 MIXED RESISTORS—65p

↓ to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Ceramic Capacitors from 1PF to 82000PF (our choice) 65p.

PLUGS—SOCKETS

Price per item, in brackets for ten.
C-O-AK Plugs—5p (50p), Socket Surface—7p (10p), Connectors—4p (35p).

D.I.N. PLUGS

2 Pin, 3 Pin and 5 Pin—20p (£1-65).

JACK PLUGS. Standard—18p (£1-50), 3.5mm—10p (80p), 2.5mm—10p (80p)

All prices include V.A.T. p. & p. 10p per order. Money back refund. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel: Rams 3036

SINCLAIR CALCULATORS

Cambridge Kit £19-95 (£2-25)
Cambridge Assembled £21-95 (£2-50)
Executive £27-95 (£3-05)
Executive With Memory £34-95 (£3-75)
New Sinclair Scientific £39-95 (£4-25)

FERRANTI ZN414

IC radio chip with data £1-20 (23p). Also available kit of extra parts to complete a radio £2-39 (40p). Send sae for free leaflet.

SINCLAIR PROJECT 80

AFU £6-95 (69p)
Z40 £3-45 (54p)
Z60 £8-95 (69p)
Q16 £7-70 (77p)
PZ5 £4-98 (49p)
PZ6 £7-98 (79p)
PZ8 £7-98 (79p)
Decoder £7-45 (74p) Trans for PZ8 £3-35 (50p)
Tuner £11-95 (£1-19) Stereo 80 £11-95 (£1-19)
Project 805 £26-95 (£2-69)
2 x Z40/Stereo 80/PZ5 £23-90 (£2-50)
2 x Z40/Stereo 80/PZ8 £27-75 (£2-77)
2 x Z60/Stereo 80/PZ6/Transformer £33-11 (£3-31)
Write for our most competitive quotation



SINCLAIR GOES QUADRAPHONIC!!

Introducing the Napolex QA10 self-contained matrix quadraphonic synthesizer. Just feed the output of a Project 80 stereo system into it and hook on 4 speakers to obtain the latest experience in sound. Send for free leaflet. Only £9-95 (£1-30)



SINCLAIR SUPER IC12

6W rms power. With 44 page booklet and printed circuit £2-10 (43p)



SWANLEY IC TOMORROW £1-80 (40p)

The world's most powerful IC amplifier. Similar to IC12 but rated at 10W r.m.s. power. Supplied with data but no printed circuit. Write for leaflet.

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-60 (27p). Stereo model with balance control £3-60 (48p)

IC12 POWER KIT

Supplies 28V 0.5 Amps £2-67 (50p)

LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1-10 (27p). 5" x 8" 8 ohm £1-55 (37p)

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1-35 (25p). Stereo model £2-40 (36p)
Type 2 for ceramic or crystal pickups. Mono 65p (18p). Stereo £1-30 (25p)

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3, 4½, 6, 7½, 9 and 12V at 500mA. £4-15 (70p)



Other eliminators stocked:

250mA:—3 way switched model giving 6, 7½ and 9V £2-95 (60p).
50mA: 6V £1-80 (30p), 9V £1-80 (30p), 7½V cassette type £2-25 (30p), Double 6V+6V £2-50 (35p), 9V+9V £2-50 (35p)

S-DECS AND T-DECS

S-DEC £1-98 (31p)
T-DEC £3-63 (47p)
M-DEC A £3-99 (51p)
M-DEC B £6-99 (81p)



IC carriers:

16 dil: plain 8p (15p) with socket £1-77 (25p)
10 TO5: plain 78p (15p) with socket £1-68 (24p)
Experiment guides: A £1-50 (26p), B £1-77 (29p), C 90p (15p), D £2-40 (35p), E £4-24 (53p)

**SWANLEY ELECTRONICS
PO BOX 68, SWANLEY,
KENT BR8 8TQ.**

Please add the sum shown in brackets after the price to cover the cost of post and V.A.T. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied complete and ready to plug into your cassette-recorder. (State voltage, make and type of plug required, if in doubt send diagram of recorder socket).



ONLY £2-95

PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v., 7½v. and 9v. DC. Attractive case mains lead output socket, plug and lead. Size 4½ x 3½ x 2½in.



ONLY £3-50

Extra lead with plug to fit your cassette recorder 55p. (State model and plug required.)

MAINS UNIT FOR TRANSISTOR RADIO ONLY

For single outputs, 6v, 9v £2-40.
For two separate outputs, 6v + 6v, 9v + 9v, £3-95 per unit. (Please state outputs required).



All units are completely isolated from mains by double wound transformer ensuring 100% safety.

ALL PRICES INC VAT & P. & P.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.)
36 Raymond Ave., South Woodford
London, E18 2HG

4-STATION INTERCOM

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 67p



£13.95

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £23-95 per pair P. & P. 60p

INTERCOM/BABY ALARM

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire and Battery. P. & P. 35p



OUR PRICE ONLY £8-50

Why not boost business efficiency with this incredible Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.7)
169 KENSINGTON HIGH STREET, LONDON, W.8. **£4.95**

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 0.15 in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

THE MANAGEMENT ADVISES WITH REGRET THAT DUE TO RISING COSTS AND STAFF SHORTAGE THE MAIL ORDER SERVICE HAS TO BE CURTAILED. FROM 1ST JANUARY 1974 ALL MAIL ORDERS ACCOMPANIED BY REMITTANCE WILL BE SUBJECT TO A MINIMUM CHARGE OF £5.00 EXCLUDING V.A.T., I.E. £5.50 INCLUDING V.A.T. GOODS OF VALUE UNDER £5.00 WILL BE AVAILABLE ONLY TO PERSONAL CALLERS, EITHER AT OUR RETAIL BRANCH, 85, TOTTENHAM COURT ROAD, W.1, OR TRADE COUNTER AT 44A WESTBOURNE GROVE, LONDON W2. MINIMUM ORDER CHARGE FOR APPROVED ACCOUNT CUSTOMERS IS £10.00 EXCLUSIVE OF V.A.T.

TAUT SUSPENSION MULTIMETERS

MADE IN USSR




8 models of multimeters from simple 22-range instrument priced at £7.00 to sophisticated 43-range instrument with transistorised safety trip circuit, priced at £17.00. Models available with transistor testing facilities (U4341) and built-in audio/I.F. oscillator (U4323).

All the above instruments and full range of other test equipment are included in our new 1973/74 combined catalogue/price list which covers valves, semi-conductors and passive components, basic specifications of semiconductors, cathode ray tubes, Klystrons and magnetrons, as well as transistor substitution list.

RECHARGEABLE

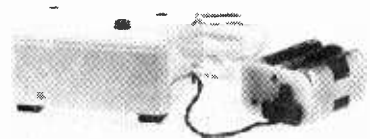Mallory Cells in U2, U11 and Penlite U7 sizes, **KESTREL BATTERY CHARGING UNIT . . .**



Use for

Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you *must* have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestrel Charging Unit which has been specially designed for these new type batteries.

PRICES
Batteries U2 equiv. -£1.92 tax paid
Penlite U equiv. 61p tax paid
U11 equiv. £1.24 tax paid
Charging unit £8.72 tax paid with one battery holder

ALL PRICES INCLUDE V.A.T.




Send to:
275 WEST END LANE
LONDON, N.W.6 1QS
01-794 9611

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. I D have space dividers. Build up any size cabinet for wall, bench or table top.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

DISCOUNT PRICES

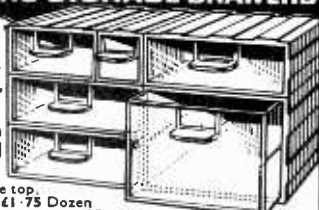

SIZES
ALL INTER LOCK

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.75 Dozen
DOUBLE UNITS £3.00 Dozen. TREBLE (3D) £2.90 for 8
DOUBLE TREBLE £4.25 for 8
EXTRA LARGE SIZE (6D1) £3.90 for 8
Carriage 40p. Orders over £10 post free.
QUANTITY DISCOUNTS 5% in £1 for orders over £15
7 1/2% over £30. 10% over £50. Quotations for large quantities.
PLEASE ADD 10% VAT TO TOTAL REMITTANCE.

FLAIRLINE SUPPLIES

(Dept. PW7), 124 CRICKLEWOOD BROADWAY,
LONDON N.W.2 01-450 4844

NEW! TODAY'S MOST EXCITING SPEAKERS



Never before have speakers of such superb performance and low cost been available. Produced by us to quality standards the new GS Range offer you true high fidelity at a fraction of the cost. Both models employ fully sealed bass reflex enclosures made from quality compressed woods and our modern compact designs ensure optimum performance at all times. Finished in Rich American Walnut effect. Black Satin front these speakers offer today's best value in high quality equipment.

TECHNICAL SPECIFICATIONS GS500 Power 30 Watts Peak (15 Watts RMS) Frequency Range 33Hz to 19000Hz Impedance 8 Ohms Bass Unit 16 cm round long throw Treble Unit 7.5cm round Crossover 5kHz Dimensions 45cm x 22.5cm x 22.5cm (18" x 9" x 9") Volume 17 litres.

TECHNICAL SPECIFICATIONS GS300 Power 20 Watts Peak (10 Watts RMS) Frequency Range 42Hz to 16500Hz Impedance 8 Ohms Drive Unit 20cm x 13cm long throw with integral coaxial tweeter Crossover 5kHz Dimensions 40cm x 20cm x 20cm (16" x 8" x 8") Volume 12 litres.

GS 500 £11.98 post free GS 300 £9.98 post free
ECONOMY Speaker System Ideal for budget hi-fi Stereo Etc. This unique 8 Ohm system comes complete with leads and super woodgrain finish £9.99 pair post free
PLEASE ADD 10% VAT TO ALL ORDERS TRADE ENQUIRIES WELCOME

GREGG ELECTRONICS PW4 24 Cranbourn Street
Leicester Square London WC2

GREGG

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.L.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold"—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW01 Aldermaston Court, Reading RG7 4PF.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers A.M.S.E. (Mech.) Institute of Engineers & Technicians (A.M.I.E.) CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work Eng. Inspection Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) General Draughtsmanship Elec. Draughtsmanship Architectural Draughtsmanship Technical Drawing	<input type="checkbox"/> A.B.T. Clerk of Works Construction Surveyors Institute—L.C.S.I. CITY & GUILDS General Bldging (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities, Estimates Hydraulics Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers A.M.S.E. (Elec.) CITY & GUILDS Gen. Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng. Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS, Radio, TV Electronics CITY & GUILDS Telecoms. Gen. Radio & TV Eng. Radio Amateurs Exam Radio Servicing TV Servicing Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Accnts. Computer Programming Works M'nt. Work Study Gen. Production Eng. Estimating & Planning Storekeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I.I. MAA IMI CITY & GUILDS Auto Eng. Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage M'nt. ARB Aero Engineering Certs. Gen. Aero Eng.	<input type="checkbox"/> G.C.E. — choose from 58 'O' & 'A' level subjects.
	<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers—A.M.S.E. (Civ.) Institute of Building—L.I.O.B.	<input type="checkbox"/> Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW1 QN
Aldermaston Court, Reading RG7 4PF BPW01

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____
AGE _____

Accredited by C.A.C.C. Member of A.B.C.C.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi Fi and Transistors - Up to date
Brochures on request

**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept. 1974.

130 LOVE



You pay less
VAT with Henry's
Low Prices

BUILD THE TEXAN

**20 + 20 WATT IC
STEREO AMPLIFIER**

As featured by
Practical Wireless
1972



Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2", 6 IC's, 10 transistors, stabilisers, Gardeners low field transformer, Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES.** On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21

Kit price **£28-50** (+VAT + 50p carr/packing) or built and tested **£35-00** (+VAT + 50p carr/packing) as illustrated.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise, IF stages, LED indicators. Tuning meter, AFC, easy to construct and use. Mainly operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 530p). Henry's are sole distributors UK and Europe.




KIT PRICE **£21-00** (+VAT) or built and tested **£24-95** (+VAT)

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI** A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98-50**
As above but with Slider Controls **£118-50**
100 watt amplifier for above **£49-50**
SDLS 100 watt mixer/amplifier with slider controls **£69-00**
R50 50 watt mixer/amplifier **£49-50**
R100 100 watt mixer/amplifier **£57-50**
DISCO AMP 100 watt mixer/amplifier Northcourt: **£73-00**
400 40 watt mixer/jamp **£37-50**
800 80 watt mixer/jamp **£45-00**
DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers) **£49-50**
SDLI (rotary controls) **£58-50**
SDLS (slider controls) the complete disco preamp **£72-00**
DJ100 100 watt power amplifier for above **£49-50**
DJ30L Mk II 3 channel 3kw sound to light **£41-25**
DJ30L Mk III slider controls **£45-50**
DJ DISC LITE as 30L-2 plus variable speed flashes **£54-00**
Carlsbro Reverberation Unit **£44-00**
Disco anti-feedback microphone **£11-95**
Colt 150 watt liquid wheel projector **£23-50**
150 watt Q1 cassette wheel projector **£50-00**
Spare Effects and liquid cassettes large range of patterns **£6-00**
6 inch Liquid wheels **£5-00**
Various cassettes **£6-00**
Mini spot bank fitted 3 lamps **£12-95**
Auto Trilite (mini) with flashers **£17-00**
Bubblemaker with liquid **£22-50**

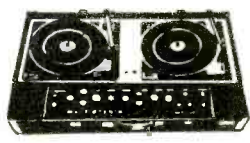Mixers/Mics/Speakers/Lighting
U.K.'s largest range of Disco Lighting. **FREE STOCK LIST REF. NO. 18 ON REQUEST.**
AKG / RESLO / DJ / CARLSBRO / EAGLE MICS., STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURNTABLES, PUBLIC ADDRESS COMPONENTS.



All prices carr. paid (UK) (VAT EXTRA)
Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter systems. 8" Bass/Midrange and Melinex Domed HF radiator plus crossover **£12-50** per pair of systems (carr./pack. 40p) or built into veneered cabinets, size 18 x 12 x 6 1/2" **£19-50** pair (carr. £1)

HI-FI TAPE EQUIPMENT




U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17). Phone 01-402-4736 for Barclay/Access Card. Direct orders and latest prices.

TRANSISTORS/SEMI-CONDUCTORS

U.K.'s largest range for every application. Small quantity discounts. Also Trade, Export and Industrial enquiries invited. Latest stock list (Ref. No. 36) including valves on request.

ELECTRONICS SUPPLIES

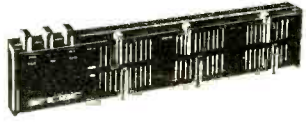Specialists in electronics for more than 30 years. Trade and industry supplies—every type of component and equipment.



- NEW SINCLAIR PROJECT 80**
Stereo PreAmplifier **£11-95**
Audio Filter Unit **£6-95**
Z40 15 Watt Amplifier **£5-45**
Z60 25 Watt Amplifier **£6-95**
PZ5 Mod. for 1 or 2 Z40 **£4-98**
PZ6 Mod. (5 Tab) 1 or 2 Z40 **£7-98**
PZ8 Mod. (5 Tab) 1 or 2 Z60 **£7-98**
TRANSFORMER FOR PZ8 **£3-95**

NEW FM TUNER **£11-95**
STEREO DECODER **£7-45**
All items post paid.

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN 1/2 REC. PRICES COMPLETE WITH LIBRARY CASES

	3 for	6 for	10 for	25 for
C 60	£1-10	£1-98	£3-00	£7-40
C 90	£1-46	£2-80	£4-60	£11-25
C 120	£1-80	£3-45	£5-45	£13-45

Quantity and trade enquiries, invited



LEARN A LANGUAGE—complete with phrase book: German — French — Spanish — Italian **£1-36** per course. **£5** for any 4.

LOW COST HI-FI SPEAKERS

SPECIAL OFFERS

- EMI 1 1/2" x 8" full range speakers (post 20p each or 30p pair)
*150TC—8 ohms Twin Cone 10 watt **£2-20** each or **£4-00** pair.
*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms **£3-85** each
EW 15 watt 8 ohms C/o Tweeter **£5-25** each or **£7-40** per pair
350 20 watt C/o Tweeters 8 or 15 ohms **£7-80** each
* Polished wood cabinet **£4-80** post 35p.



8 ohms full range (post 20p)

FR4	4"	5 watt	£4-75
FR65	6 1/2"	10 watt	£6-30
FR8	8"	15 watt	£8-50
FR23	9 x 6"	15 watt	£8-40

BASS & MID RANGE—8 ohms (post 20p)

AA12	5"	15 watt	£3-75
B110	5 1/2"	15 watt	£7-20
B200	8"	15 watt	£8-50
B139/2	1 1/2" x 8"	30 watt LF	£13-75

TWEETERS AND CROSSOVERS (post 20p)

K2006	10 watt	8 or 15 ohms	£2-10
FHT6	15 watt	8 ohms	£3-35
K2011	30 watt	8 ohms	£4-80
T27	KEF		£5-52
Axcent 100	30 watt	8 ohms	£2-70
K4009	14W 4kHz C/o		£3-10
SN75	3kHz var. C/o		

SPEAKER KITS (carr. etc. 35p)

20-2	8"	30 watt	£24-50 pair
20-3	8"	40 watt	£35-95 pair
LINTON 2		20 watt	£18-30 pair
GLENDALE 3		30 watt	£32-95 pair
DOVEDALE 3		50 watt	£51-50 pair
KEF KK2			£55-00 pair
KEF KK3			£78-00 pair

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—this is the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is 92-page booklet explaining how to calculate Logs, Tangents, Sines etc.



£19-95 Also available assembled ready to use. **£22-50** + VAT.

10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E & O E. Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402-8791. See page 163 of this magazine

Henry's RADIO LIMITED

EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
309 PA - Disco - Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres, London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
114 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-863 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to
6 pm six days a week
Hi-Fi Tape Equipment
Discount Stock List
Free at all stores