

RADIO... ELECTRONICS... INSTRUMENTS... AUDIO....

practical WIRELESS

50p

Australia 85c
New Zealand 85c
South Africa 80c
Malaysia \$2.25

MAR 1979

8-PAGE
SUPPLEMENT

EXTRA

HINTS & TIPS
FOR
CONSTRUCTORS



**Using
power
FETs**

THE **Pw**

'WINTON'
STEREO AMPLIFIER

50 + 50W



also: THE **Pw**
'SOUNDLITE'
SOUND TO LIGHT UNIT

TTL ★★

7401	11p	74109	25p
7402	16p	74118	75p
7403	10p	74120	80p
7404	10p	74121	25p
7405	12p	74122	35p
7406	25p	74125	35p
7407	25p	74126	35p
7408	12p	74128	80p
7409	12p	74130	120p
7410	12p	74131	90p
7411	15p	74132	45p
7412	15p	74135	90p
7413	25p	74136	80p
7414	25p	74137	55p
7415	45p	74138	100p
7416	25p	74141	50p
7417	25p	74142	180p
7420	12p	74143	270p
7421	20p	74144	270p
7422	15p	74145	270p
7423	20p	74147	100p
7425	20p	74148	90p
7426	22p	74150	65p
7427	22p	74151	45p
7428	25p	74154	45p
7430	12p	74155	45p
7432	20p	74155	45p
7433	28p	74156	45p
7437	20p	74157	45p
7438	20p	74160	55p
7440	12p	74161	55p
7441	45p	74162	55p
7442	40p	74163	60p
7443	60p	74164	60p
7444	60p	74165	60p
7445	65p	74166	75p
7446	50p	74167	160p
7447	50p	74170	160p
7448	50p	74173	80p
7450	12p	74174	60p
7451	12p	74175	60p
7453	12p	74176	50p
7454	12p	74177	50p
7460	12p	74178	75p
7470	25p	74180	120p
7472	25p	74181	130p
7473	25p	74182	130p
7474	25p	74182	120p
7475	25p	74185	100p
7476	25p	74188	320p
7480	40p	74190	70p
7481	85p	74191	70p
7482	75p	74192	60p
7483	70p	74193	60p
7484	60p	74194	55p
7485	60p	74196	50p
7486	60p	74196	50p
7489	130p	74197	50p
7490	25p	74198	100p
7491	40p	74199	100p
7492	35p	74293	90p
7493	30p	7LS00	18p
7494	70p	74S112	80p
7495	45p		
7496	45p		
7497	120p	7805	100p
74100	80p	7812	100p
74104	80p	7815	100p
74105	40p	7815	100p
74107	25p	7816	100p
74108	100p	7824	100p

POWER SUPPLY CAPACITORS

2200/16	35p	4700/63	120p
2200/63	80p	4700/70	135p
2200/100	150p	10000/10	100p
3300/30	50p	10000/25	150p
3300/63	90p	15000/15	150p
4700/25	50p	22000/25	200p
4700/40	65p		

ENQUIRIES FOR ANY OTHER TYPES

CMOS

4000	12p	4047	80p
4001	12p	4048	50p
4002	12p	4049	50p
4006	80p	4050	25p
4007	14p	4054	100p
4009	30p	4055	130p
4011	12p	4056	120p
4012	12p	4060	100p
4013	30p	4066	35p
4015	50p	4069	12p
4016	30p	4070	12p
4017	50p	4071	12p
4018	55p	4072	12p
4019	40p	4081	12p
4020	50p	4082	12p
4022	50p	4093	70p
4023	12p	4510	60p
4024	40p	4511	70p
4025	12p	4516	65p
4026	80p	4518	65p
4027	30p	4520	65p
4028	45p	4528	80p
4029	50p	4583	70p
4030	30p		
4032	80p		
4033	100p		
4040	60p		
4043	60p		
4046	80p		

FX1593 FERRITE RINGS
O/D 12mm, I/D 6mm
10 for 70p

TOGGLE SWITCHES SUB MIN
Single Pole C.O. 65p
Single Pole C.O. Biased 85p

RESISTORS 1/3RDW
100 of 1 type £1.00p £12 only

LINEAR

AY3550	450p	NE556	90p
CA3039	70p	NE562B	400p
CA3046	60p	SAD1024	1500p
CA3060	225p	SL917E	653p
CA3065	200p	SN76003N	150p
CA3076	250p	SN76013N	110p
CA3080	75p	SN76013ND	125p
CA3123E	25p	SN76023N	110p
CA3085	85p	SN76023ND	125p
CA3086	60p	SN76033N	150p
CA3088	190p	SN76227N	160p
CA3089	160p	SN76228N	180p
CA3090AQ	360p	SN7662DN	75p
CA3123E	130p	TAA A300	100p
CA3130	100p	TAA A350	190p
CA3140	60p	TAA A550	35p
LF356	80p	TAA A570	220p
LF357	80p	TAA A661B	140p
LM211H	250p	TAA A700	350p
LM300TR5	170p	TAA A750	350p
LM301AN	90p	TAD100	150p
LM304	200p	TAD110	130p
LM307N	65p	TBA120S	60p
LM308T05	100p	TBA120T	85p
LM308DIL	100p	TBA483Q	200p
LM309K	100p	TBA520C	200p
LM310T05	150p	TBA530Q	200p
LM311T05	150p	TBA540	200p
LM317K	325p	TBA550Q	250p
LM324	70p	TBA560C	250p
LM339	60p	TBA64A12	250p
LM348N	90p	TBA703	180p
LM380	60p	TBA720Q	225p
LM381N	90p	TBA750Q	200p
LM382	150p	TBA800	80p
LM391	180p	TBA810	100p
LM555	25p	TBA810	100p
LM709C	40p	TBA820	100p
LM710T05	69p	TCA920Q	280p
LM710DIL	65p	TCA270Q	200p
LM723T05	40p	TCA270S	220p
LM723DIL	40p	TCA780	300p
LM733	120p	TCA4500A	450p
LM741	20p	TD1A1008	300p
LM748	40p	TD1A1034	450p
LM1303N	100p	TD A2022	200p
LM145E	100p	TD A2020	300p
LM3080	75p	TL084	120p
LM3900	55p	XR320	250p
LM3909N	65p	XR2206	450p
MC1310P	140p	XR2207	450p
MC1312P	150p	XR2216	650p
MC1314P	190p	XR2567	650p
MC1315P	230p	XR4136	150p
MK50398	60p	XR4202	150p
MMS314	380p	XR4212	150p
MMS316	480p	XR4739	150p
NE529K	150p	ZN414	100p
NE555	25p	95H90	700p

ELEC CAPACITORS

0.47/25	7p	47/10	8p
1/16	7p	47/16	8p
1/25	7p	47/25	8p
1/50	7p	47/35	8p
2-2/25	7p	47/50	8p
2-3/25	7p	100/10	8p
2-3/25	7p	100/16	8p
4-7/10	7p	100/25	8p
4-7/16	7p	100/50	8p
4-7/25	7p	100/63	16p
4-7/50	7p	220/16	12p
6-8/25	7p	220/25	14p
10/10	7p	220/50	10p
10/16	7p	330/25	17p
10/25	7p	330/35	18p
10/50	7p	330/50	18p
22/6V3	7p	470/10	14p
22/10	7p	470/25	19p
22/16	7p	470/35	20p
22/25	7p	470/50	24p
22/35	7p	1000/16	27p
22/50	8p	1000/25	30p
33/6V3	7p	1000/35	40p
33/16	8p	1000/40	40p
33/25	8p	1000/63	50p
33/40	8p	1200/63	60p
33/50	9p	2200/10	30p

POLY CAPS

1000 PF	5p	0-1 uF	6p
2200	5p	0-2 uF	7p
3300	5p	0-3 uF	9p
4700	5p	0-4 uF	12p
6800	5p	1-0 uF	12p
0-01 uF	5p	2-2 uF	25p
0-022 uF	5p	4-7 uF	35p
0-033 uF	5p	6-8 uF	40p
0-047 uF	5p	10 uF	60p

TANT. BEADS

0-1/35V	14p	3-3/16V	14p
0-1/15/35V	14p	4-7/16V	14p
0-2/2/35V	14p	4-7/25V	14p
0-3/3/35V	14p	4-7/35V	14p
0-4/7/10V	14p	6-8/6V3	14p
0-4/7/35V	14p	6-8/35V	14p
0-8/35V	14p	0/35V	14p
1-0/10V	14p	2/15V	21p
1-0/35V	14p	3/16V	25p
1-5/35V	14p	4/7/3V	25p
2-2/25V	14p	4/7/16V	25p
2-2/35V	14p	100/3V	25p

SPECIAL OFFER

2000uF 35v 40p 100/£30

REED INSERTS One Price
26MM Long 10 for £1.00p
50MM Long 10 for £1.00p

TRANSISTORS

AA113	10p	BC171	12p	BDX42	50p	BU208	220p
AA217	30p	BC172	12p	BDY10	100p	BY100	25p
AC121	30p	BC177	15p	BF115	20p	BY126	15p
AC126	20p	BC178	15p	BF120	50p	BY127	15p
AC127	20p	BC182	10p	BF121	45p	BY133	25p
AC127/01	25p	BC182L	12p	BF123	45p	BY164	50p
AC128	20p	BC183	10p	BF125	45p	BYA94	8p
AC151	25p	BC184	10p	BF127	50p	C1120	30p
AC153	30p	BC184	10p	BF137	35p	C1164	20p
AC153K	30p	BC184L	12p	BF154	18p	E100	42p
AC154	30p	BC186	20p	BF160	18p	E300	47p
AC154	30p	BC204	12p	BF161	18p	E310	60p
AC187	20p	BC205	12p	BF173	20p	E420	180p
AC188	20p	BC207	12p	BF178	25p	E430	126p
AC197	35p	BC212	11p	BF179	25p	MJE340	45p
AC199	35p	BC212L	12p	BF180	30p	MPSA05	30p
AC200	35p	BC213	12p	BF182	30p	MPSA06	32p
AC240	50p	BC213L	15p	BF183	25p	TIP29	35p
AC241	50p	BC214	15p	BF184	20p	TIP29A	40p
AC242	50p	BC237	10p	BF186	25p	TIP29C	40p
AD130	150p	BC237B	15p	BF194	10p	TIP30	35p
AD143	150p	BC268	16p	BF195	10p	TIP30A	40p
AD149	30p	BC294	30p	BF196	10p	TIP30B	40p
AD161	30p	BC300	25p	BF197	10p	TIP30C	45p
AD162	30p	BC301	25p	BF198	25p	TIP31	40p
AD161/2MP	30p	BC303	25p	BF199	25p	TIP31A	45p
AF114	70p	BC303	15p	BF200	30p	TIP31B	50p
AF115	25p	BC308	15p	BF201	20p	TIP31C	55p
AF116	25p	BC317	12p	BF225	20p	TIP32	40p
AF116	25p	BC318	12p	BF241	16p	TIP33	60p
AF118	80p	BC323	30p	BF244B	15p	TIP33	60p
AF178	50p	BC325	18p	BF255	25p	TIP34	70p
AF199	35p	BC327	17p	BF257	25p	TIP35	200p
AF239	45p	BC337	17p	BF258	25p	TIP41A	7

practical WIRELESS

MARCH 1979
VOLUME 55
NUMBER 3
ISSUE 865

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "*Practical Wireless*" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 75p each, including post and packing to addresses at home and overseas.

Binders are available (Price £2.85 to UK addresses or £3.45 overseas, including post and packing) each accommodating one volume of *PW*. Please state year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.**

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

NEWS & VIEWS

- 20 **Editorial**
Sorry!
- 20 **PW Personality**
Debbie Chapman
- 21 **News . . . News . . . News . . .**
- 24 **RAE Reprint Announcement**
- 24 **Letters**
Comments from *PW* readers
- 56 **Kindly Note**
Car Radio LW Converter, Dec 1978. Digital Door Chimes, Dec 1978. *PW* "Sandbanks" Metal Detector, Jan 1979. Breadboards Supplement, Dec 1978. *PW* "Purbeck" Oscilloscope
- 59 **Production Lines** Alan Martin
Information on the latest products

FOR OUR CONSTRUCTORS

- 25 **PW "Soundlite"** T. P. Hopkins
An economical 3-channel sound-to-light unit
- 31 **Idea Department**
Step Tone Generator. Car Cassette Power Supply
- 34 **PW "Hythe" Marine Band Receiver—2** . M. Tooley & D. Whitfield
Using the receiver, plus some add-on units
- 39 **PW "Winton" Stereo Amplifier—1** E. A. Rule
A high quality, 50W per channel design, using power f.e.t.s
- 48 **Follow-up to the PW "Avon"** Peter Preston
Increased power and 12V operation
- 49 **Wide-band Noise Source** D. Whitfield
An r.f. noise generator for receiver testing
- 51 **Tone-burst Generator** P. Hodson
An audio oscillator for v.h.f./u.h.f. repeater access

GENERAL INTEREST

- 54 **IC of the Month** Brian Dance
The TDE1607 interface device
- 60 **On the Air**
Amateur Bands Eric Dowdeswell
MW Broadcast Bands Charles Molloy
SW Broadcast Bands Charles Molloy
VHF Bands Ron Ham
VHF Personalities—The Two Erns Ron Ham

☆ FREE THIS MONTH

"HINTS & TIPS FOR CONSTRUCTORS" — A special 8-page supplement on all aspects of construction

We regret that, owing to circumstances beyond our control, the size of this issue of *Practical Wireless* has had to be reduced at short notice by eight pages. We apologise to readers for any disappointment caused.

B. BAMBER ELECTRONICS

Dept. P.W.5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

OSMOR 10V REED RELAY COILS 1k ohm coil to fit $\frac{1}{2}$ " reeds (not supplied) 2 for 50p.
HF CHOKES wound on $\frac{1}{2}$ " x 1" long ferrites, 4 for 50p.
VHF CHOKES wound on 6-hole tubular ferrites, 5 for 40p.
DUAL T018 HEATSHINKS 1" x $\frac{1}{2}$ " x $\frac{1}{2}$ " with screw-in clamps, 3 for 50p.

MAINS TESTER SCREWDRIVERS 100 to 500V. Standard size 50p. Large 70p.
RADIO PLIERS 5 $\frac{1}{2}$ " £1-80. 6 $\frac{1}{2}$ " £2-00.

SMALL SIDE CUTTERS (with wire holding device) £4.50.
MINIATURE FILE SETS. Set of 6 £2-20.
HIGH QUALITY RELAYS, 4 pole C/O, 3A contacts, 12V DC coil, 150 ohm. Size approx. 1" x $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ", with plastic covers, 80p each or 2 for £1-50.

LARGE ELECTROLYTIC PACKS. Contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces, £3-00 per pack (+12 $\frac{1}{2}$ % VAT).

Slider Switches, 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.

DUE TO A CHANGE OF SUPPLIER, OUR STOCK ALUMINIUM BOXES AND VINYL COVERED EQUIPMENT CASES WILL BE AS FOLLOWS

Aluminium boxes with lids	
AL1 3" x 2" x 1"	60p
AL2 4" x 3" x 1 $\frac{1}{2}$ "	70p
AL3 4" x 3" x 2"	80p
AL4 6" x 4" x 2"	90p
AL5 6" x 4" x 3"	£1-25
AL6 8" x 6" x 2"	£1-50
AL7 8" x 6" x 3"	£1-75

Vinyl Equipment Cases
Blue Vinyl covered steel tops with plain aluminium lower sections.
BC0 5" x 2 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " £1-00
BC1 6" x 4 $\frac{1}{2}$ " x 2" £2-00
BC2 8" x 4" x 3 $\frac{1}{2}$ " £2-25
BC3 8" x 5 $\frac{1}{2}$ " x 2" £2-50
BC4 10" x 6 $\frac{1}{2}$ " x 3" £3-00
BC7 12" x 6 $\frac{1}{2}$ " x 5" £3-25

MAINS TRANSFORMERS. Type 15/300 240V input, 15V at 300mA output, £1-50 each.

MAINS TRANSFORMERS. Type 45/100, 240, 220, 110, 0V input, 45V output, £1-50 each.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED
CELESTION 8" x 5" ELLIPTICAL SPEAKERS, 20 ohm, 3 watts rated, £1-50 each + 12 $\frac{1}{2}$ % VAT.
IC AUDIO AMP PCB. Output 2 watts into 3 ohm speaker, 12V DC supply, size approx. 5 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " x 1" high, with integral heatsink, complete with circuits, £2-00 each.

NICAD CONVERTER PCB. (Low power inverter). Size approx. 4" x 1 $\frac{1}{2}$ " x 1" high, 12V DC supply, 60V DC output, through pot on pcb, for charging Nicads, etc. (ideal for charging portable batteries from mobile supply). Only needs one BFY50/51/52 or similar transistor, which can be mounted direct on the pcb pins on board, fitted with a star-type heatsink (Not Supplied), £2-00 each.

THE NEW EAGLE INTERNATIONAL CATALOGUE IS AVAILABLE ON REQUEST containing Audio, In-car, and test equipment, etc.

DECIMAL KEYBOARDS, pressure sensitive type, when pressed contacts go from O/C to approx. 25 ohms. Switches only, no encoders. Size approx. 3" x 3", with large square touch plates, O-9 Clear, A, B, Dual Watch, and spare. Few only, £2-00 white stocks last.

TYPE 8079 FULL RANGE SPEAKER, 10" dia, 15 ohm, £5-00 each (or 2 for £9-00) + 12 $\frac{1}{2}$ % VAT.

SEMICONDUCTORS
BX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type T05 Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
2N3819 Fet., 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAV 31 Signal Diodes, 10 for 35p.
IN 4148 (IN914), 10 for 25p.
BC107 (Metal can) 4 for 50p.
SCRs 400V at 3A, stud type, 2 for £1-00.
Tip2955 Silicon PNP power transistor, 60V at 15A, 90 Watts, Flat pack type, 2 for £1-50.
GERMANIUM DIODES, approx 30 for 30p.
741CG op amps by RCA, 4 for 70p.
RED LEDs (Min. type) 5 for 70p.
T03 transistor insulator sets, 10 for 50p.

SPECIAL OFFER FOR COMPUTER BUILDERS, ETC.
18 way ribbon cable, decimal coded, 4 metres for 1.25.
13 way heavy duty ribbon cable, decimal coded, (ideal for PSU runs) 3 metres for £1.50.

CLAREED REED RELAYS, complete with reeds, TYPE 1, Size approx. 2 $\frac{1}{2}$ " x $\frac{1}{2}$ " x $\frac{1}{2}$ " 1 pole make, 9V 400 ohm coil, 35p each, TYPE 2, Size approx. 2 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " x $\frac{1}{2}$ ", 2 pole make + 2 pole break, 2 x 9V 200 ohm coils, 60p each.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6-50 each, Brand New.

IC TEST CLIPS, clip over IC while still soldered to pcb or in socket. Gold-plated pins, ideal for experimenters or service engineers, 28 pin DIL £1-75, 40 pin DIL £2-00. Or save by buying one of each for £3-50.

GLASS BEAD FEEDTHROUGH INSULATORS. Solder-in type, overall dia. approx. 5mm. Pack of approx. 50 for 50p.

PLASTIC PROJECT BOXES with screw on lids (in black ABS) with brass inserts.
Type NB1 approx. 3 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " 45p each
Type NB2 approx. 4 $\frac{1}{2}$ " x 3" x 1 $\frac{1}{2}$ " 55p each
Type NB3 approx. 4 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " 65p each
Type NB4 approx. 8 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " £1-50.

DIE/CAST ALUMINIUM BOXES
Send for Latest Price List.

PLUGS AND SOCKETS
BNC Plugs, new 50p each.
N/T type Plugs 50 ohm, 60p each, 3 for £1-50.
PL259 Plugs (PTFE) brand new, packed with reducers, 75p each.
SO239 Sockets (PTFE), brand new (4-hole fixing type), 60p each.

SOLDER SUCKERS (Plunger type). Standard Model, £5-50. Skirted Model, £6. Spare Nozzles 60p each.

NEW MARKSMAN RANGE OF SOLDERING IRONS
S1400 40W 240V £4-50.
S125DK 25W 240V + bits etc., KIT £5-50.
BENCH STAND with spring and sponge for Marksman Irons £2-70.
Spare bits MT9 (for 15W) 60p, MT5 (for 25W) 50p, MT10 (for 40W) 55p.
ALL PRICES + 8% VAT.

TCP2 TEMPERATURE CONTROLLED IRON. Temperature controlled iron and PSU. £30 + VAT (£2-40).
SPARE TIPS
Type CC single flat. Type K double flat fine tip. Type P, very fine tip £1-50 each + VAT (8p). **MOST SPARES AVAILABLE.**

WELLER SOLDERING IRONS
EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN S100D £12-00.
EXPERT SOLDER GUN KIT (spare bits, case, etc.) £15-00. Spare bits 40p pair.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

BSR AUTOCHARGE RECORD PLAYER DECKS with cue device, 33-45-78 RPM, for 7", 10", 12" records. Fitted with SC12M Stereo Ceramic cartridge and stylus. Brand new £14-00 + 12 $\frac{1}{2}$ % VAT.

GARRARD AUTOCHARGE RECORD PLAYER DECKS, Model 6-300, with cue device, 33-45-78 r.p.m., for 7", 10", 12" records. Fitted with KS41B Stereo Ceramic cartridge and stylus. Brand new £16-00 + 12 $\frac{1}{2}$ % VAT. Please note, record decks sent by Roadline, allow 14 days for delivery.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK, SAE FOR LIST.

VARICAP TUNERS Mullard type ELC1043/05. Brand New, £5-00 + 12 $\frac{1}{2}$ % VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Saeonric Manufacture. Approx 100. £1-50 per pack + 12 $\frac{1}{2}$ % VAT.

Dubiller Electrolytics, 50 F, 450V, 2 for 50p.
Dubiller Electrolytics, 100 μ F, 275V, 2 for 50p.
Plessey Electrolytics, 470 μ F, 63V, 3 for 50p.
TCC Electrolytics, 1000F, 30V, 3 for 60p.
Dubiller Electrolytics, 5000 μ F, 35V, 50p each.
Dubiller Electrolytics, 5000 F, 50V, 60p each.
ITT Electrolytics, 6800 F, 25V, high grade screw terminals, with mounting clips, 50p each.
PLEASE ADD 12 $\frac{1}{2}$ % VAT TO ALL CAPACITORS.

Terms of Business: CASH WITH ORDER, MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING, (UK ONLY), SAE with ALL ENQUIRIES Please: PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.

OPEN UP THE EXCITING WORLD OF SHORT WAVE LISTENING



SRX 30
For the advanced, keen short wave listener, the choice of receiver has usually been between cheap and nasty or very good but very expensive equipment. We think that the SRX-30 will provide that listener with excellent performance at a reasonable cost and is the answer to this eternal problem. The SRX-30 is based on an advanced drift cancelling loop system which gives spot on dial accuracy at any frequency between 500 KHz and 30 MHz together with easy to understand frequency readout. Suitable for all users from raw beginners, thanks to its simplicity of operation; to experienced listeners and amateur operators thanks to its advanced technology, the SRX-30 is the best communications receiver available in its price range today.

Completely self contained, including operation from mains or 12 volts dc, the SRX-30 is at home on broadcast or amateur bands. All mode reception of AM, CW, USB, and LSB is provided and receiver selectivity is automatically switched to give optimum performance on any mode. Send for full details today or give us a ring and we'll tell you all about the SRX-30. Price £175 inc. vat. Carriage by Securicor £3.

NEW. Bellsonic power supply giving fully regulated 12 V dc output at 3 amps continuous rating and 5 amps peak rating from 220-240 V ac mains input. Automatic over current trip for safety. Multitude of uses for the amateur experimenter or professional user. Incredibly low price £17.28 inc. vat. P & P 86p.

We also stock the RAK Listener 3 aerial system for the man who demands the best and has the room for it. Double dipole system complete with H/D alloy wire, insulators, coaxial feeder, centre connector etc. in an overall length of 75 feet covering the frequency range up to 30 MHz. Price £18. inc. vat. P & P 86p.

Also available is the Listener 1 loaded end fed single wire aerial system for restricted space situations. Overall length only 15 feet due to use of loading coil and element folding. Ideal aerial for any user of short wave bands. Price £7.50 inc. vat. P & P 86p.

If you need professional oscilloscopes at reasonable prices, please contact us for details of terrific TRIO range. Full range of other test equipment stocked.

For all that's good in Amateur Radio, contact:

LOWE ELECTRONICS LTD., 119 Cavendish Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817.

For full catalogue, simply send 45p in stamps and request catalogue CPW.

GLOUCESTER INDUSTRIAL SALES AND AUCTIONS LTD

Eastington Trading Estate, Nr. Stonehouse Gloucester

Tel: STONEHOUSE 4118

(M.5. MOTORWAY-EXIT No. 13)

We hold regular monthly Auction Sales of mostly New Electronic and Electrical Goods consisting of Transistors, Triacs, Integrated Circuits, Diodes, Capacitors and Resistors, together with Fractional Motors, Transformers, Power Packs, etc. etc. Phone or write to be put on our Auction Mailing List.

Why not get in touch with our Mr. Jack Bailey and enquire about our terms for the disposal of your surplus stocks etc. through our Auctions.

FABULOUS PROFESSIONAL DISCO SYSTEM

F.A.L. De Luxe PROFESSIONAL Carr. CONSOLE (Powered) etc. £15

Slide Fade Controls. Autofade with Music Override on both mic. and jingle inputs. Headphone pre-fade monitor with 5 Push-button selector. Illuminated V.U. meters. Illuminated rocker switches. LED cue indicators. Tape or jingle inputs, unity gain. Mic. channel with Bass & Treble. Slave outlet.

Treble Control (Music Channel) Output into line (Slave)
 Treble Control (Mic. Channel) Autofade Recovery
 Bass Control (Music Channel) Microphone Input.
 Bass Control (Mic. Channel) Tape/Jingle. 1/P

£399
SAVE £100

DEPOSIT £28.88

and
38 weekly payments of £9.74
 (Total £399)


Turntables BSR P200 Belt-drive are Garrard 125SB Belt-drive with low Mass 'S' and magnetic cartridge per system £10 for Garrard only.

POWER: 120 watts continuous RMS into 4 ohms
DECK LIGHTS: Fully adjustable flexi-beams over each turntable with independent switching.
CABINET: Solidly made to withstand the rigours of transporting. Covered in heavy duty leather cloth type material in attractive colour combinations Corner cap protectors Recessed carrying handles.

List £320.76

INTEREST FREE CREDIT
 on this system only

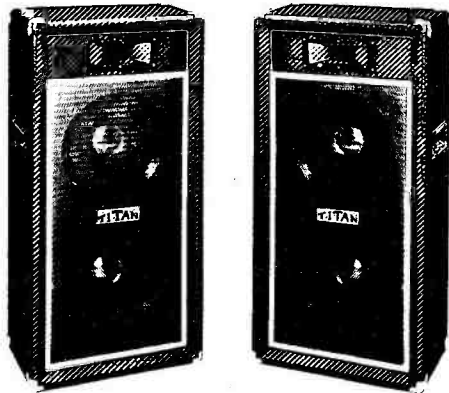ALL THREE UNITS PRODUCED BY BRITAINS LARGEST MAKERS OF DISCO EQUIPMENT



PAIR MATCHING FULL RANGE De Luxe 80w LOUDSPEAKERS

Each inc. Pair of Powerful 12" Bass units (with aluminium centre domes), and High Frequency Horn unit to extend frequency range to above 17 kHz. Normally £89.95 ea.



Make your own Console with these DISCO MODULES


FANTASTIC SPEAKER OFFER

TWIN 12" SPEAKER CABINET PLUS PAIR 12" SPEAKERS

of Robust vibration-proof construction. Fitted protective corner pieces. Removable Vynair covered front with silver effect trim. Sunken jack socket with escutcheon at the rear.

Pair 12" 15w speakers for wiring up and front mounting in above supplied to complete a 30w unit for lead guitar or P.A.

£19.95

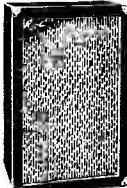

Carr. £2.50

CONTROL UNIT (mains powered)

Vol. (Left) Vol. (Right) Tape input and volume control. Bass, Treble, ON/OFF switch for each Table. **£25.00** Carr. £1

MONITOR UNIT With H/Phone Socket and Vol. Control Carr Free **£7.95**

FADER UNIT Carr Free **£7.95**

100w OUTPUT UNIT **£29.95** Mains powered Carr. £1.50

TITAN GROUP/DISCO SPKRS

	Value	RSC Price
T12/45R 12" 45w	£15.00	£12.95
T12/60R 12" 60w	£22.50	£14.95
T12/100 12" 100w	£36.00	£25.95
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£51.00	£39.95



Rating RMS Imp 8-15 ohms

Carr. £1.20, under £18, over this add 6p per £1.

CABINETS FOR ABOVE Heavy duty, finished in black Vynide with Vynair fronts, protective corner pieces, various sizes cut-outs. TE1 1 x 12" £11.95. TE2 2 x 12" £16.95. Deposit Terms orders over £20.

RSC 100 WATT DISCO SYSTEM



Consisting of (1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES (2) & (3) PAIR 50 WATT LOUDSPEAKERS including 12" UNITS

£169.95

Carr. £4.75

ALL RSC PRICES INCLUDE VAT

50 WATT AMPLIFIER SACRIFICE

Limited stocks of **TITAN TA/50A**

to be cleared to make way for a re-styled model.

Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. with corner protectives. Value £60. Terms: Dep. £7.95 & 8 monthly payments £4.72 (Total £45.71). Matching Cabinets 1 x 12" £29.95. 2 12" £49.95 Carr. £1



£44.95

New Branches at

*** LEEDS, * LIVERPOOL & * WOLVERHAMPTON**

*** WOLVERHAMPTON**

OPEN ALL DAY SATS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349

BIRMINGHAM 30/31 Great Western Arcade. (Closed Wed.) Tel. 021-236 1279

CARLISLE 8 English Street (Closed Thurs.). Tel. 38744

COVENTRY 17 Shelton Sq., The Precinct. (Closed Thurs.) Tel. 25983

DERBY 97 St. Peter's Street (Closed Wed.). Tel. 41361

DEWSBURY 9/11 Kingsway (Closed Tues.). Tel. 468058

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069

EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501

GLASGOW 326 Argyle St. (Closed Tues.). Tel. 041-248 4158

HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505

LEICESTER 32 High Street (Closed Thurs.). Tel. 56420

LONDON 238 Edgware Road, W.2 (Closed Thurs.). Tel. 723 1629

*** LEEDS** 16-18 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 449609

*** LIVERPOOL** 35 Dawson Way, St. John's Precinct (Closed Wed.). Tel. 708 9380



Barclaycard & Access PHONE ORDERS quoting CARD NUMBER accepted

MAIL ORDERS & EXPORT ENQUIRIES TO:— AUDIO HOUSE, HENCONNER LANE, LEBDS. 18. Tel. 0832 877831.

MAIL ORDERS MUST NOT BE SENT TO SHOPS TERMS C.W.O. or G.O.D. No. G.O.D. under £3. POSTAGE 60p PER ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.

MIDDLESBROUGH 103 Linthorpe Rd. (Cl. Wed.) Tel. 247096

*** NEWCASTLE UPON TYNE** 59 Grainger St. (Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068

SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716

*** WOLVERHAMPTON** 8 Wulfrun Way (Closed Thurs.). Tel. 26612

*** MUSICAL INSTRUMENTS & ACCESSORIES** in stock at these branches

TRANSMITTER RECEIVER. MK.123. Very compact Army unit for use in range 2.5 to 20 Mc/s, receiver section 7 valves inc RF stage & BFO provides O/P for 4 K ohm phones, 3 bands with direct cal 2.5 to 5.5 to 10 & 10 to 20 Mc/s. Tx section 2.5 to 20 Mc/s in 3 ranges O/P 15/25 watts over range C.W. only, 2 valves Crystal Osc & 5B251M P.A. stage, will match into the following Aerial loads 25, 100, 500 & 1500 ohms as int tune up meter, reqs crystals type FT243 in range 2.5 to 10 Mc/s int morse key fitted with plug for ext key. Mains P.U. self contained unit for 115 or 200/250v AC overhaul size inc Rx, Tx & P.U. 30x9x14 Cm weight 4 Kg. also supplied with ext inverter unit for 12v DC. Supplied in clean cond with 80 page handbook giving circ details etc (no details on 12v P.U.) £54.

TAPE RECORDERS. Made for use in language lab equipment 240v I/P uses BSR type TD.10 3 speed deck 5" spools, two chan transis amps with provision for playback & record can be used for stereo. P.U. and circ boards are mounted below tape deck approx size 12x11x7" intended to work phones. Supplied in clean condition may be less knobs & ind lamps some circ details supplied. No ext case. £13 also sim valve unit TD.2 deck £8.50.

U.H.F. CAVITIES. New spares for 2C39/7289 valves will tune over range 990/1040 Mc/s with int fittings circ supplied £6.50, also Rx section tunable preselector 1080/1130 Mc/s 4 section with 1N21 mixer diode for 60 Mc/s IF with circ £4.50.

ELECTROSTATIC VOLTMETERS range 0 to 15Kv AC or DC usable scale 3 to 15Kv complete in wood carrying case 8x9x6" £10.80.

HELIPOT DIAL standard 10 turn type to fit 1/4" shaft size 1 3/4" dia. £1.50 or with 100K helipot £2.

RECTIFIER UNITS ex-Army unit 200/250v I/P provides two DC O/Ps of 12v DC at 3 amps ea can be connected for 12v 6 amp or 24v 3 amp will do 4 amp okay for battery chargers good cond £10.80.

INFRA RED LAMPS light & heat units sealed beam 115v 500 watts size 7" dia 4 1/2" deep new American G.E. okay for paint drying etc two for £5.40.

V.H.F. TEST SET provides RF O/P over range 20 to 88 Mc/s in 4 bands, as int 2 Mc/s check, noise generator with 50 Ma meter, int pulse or C.W. O/P complete in case with cal charts & Ae rods, circ & notes. These req ext supplies of 250v & 6.3 £13.

CRYSTAL OVENS. Miniature type to take 1 Hc6/u or 2 Hc18 crystals 12/24v operation size inc base 2x1 1/4x3/4" new £1.20 either type.

PANEL METERS. 100 Ua scale 0 to 100 linear 2" dia £3 also 1 Ma FSD special scale 2" dia £1.30 both new.

FREQ METERS type BC221 125Kc to 20 Mc/s with int crystal check, with charts & book require 135v HT & 6.3v £27.

HEAD & MIKE SETS for use with 19 set m.c. type with hand mike nom 100 ohm new £4.

HANDSETS No. 3 m.c. with press to take swt suitable 19/62 sets elec okay store soiled £2.50.

HEATERS flat tubular 240v 150 watt approx size 6 1/2x10" new £1.80.

DYNAMOTOR UNITS 24v DC I/P O/P 200 & 400v DC 280 Ma int, by removing fan these can be used as powerful 12/24v DC motor with shaft 1x3/4" £6.50.

CABLE miniature 25 core flex non-screened 5/16ths osd colour coded new 10 Mts for £3. Single flex 23/006 okay for Ae wire new 25 Mts for 85p.

CRYSTALS mixed 10X & 10XJ types in range 5 to 8.5 Mc/s 20 for £2.20.

I.F. TRANS min type 465Kc new with sec tap 3 for £1.30.

COAX PLUGS & SKS standard type ex new equip 5prs for £1.30.

THERMISTORS bead type 3.8 mm dia 160 ohm at 200'c 20k at 20'c new 80p.

RADIO STATION KIT contains, long wire aerial, dipole aerial, 75 ohm twin feeder, miniature morse key, handset, head & mike set, misc fittings. In carrying bag new cond. for use in 2/10 Mc/s range. £10.80.

FILTER UNITS 100Kc crystal filters precision units by Marconi 75 ohm imp in case size 8 1/2x3 3/4x5" available in 1 or 2 Kc bandwidths with connectors £5.40 either type.

Above prices include Carriage & VAT.

Goods ex equipment unless stated new.
S.A.E. for enquiry or List 21.

A.H. SUPPLIES
122, HANDSWORTH RD. SHEFFIELD S9 4AE
Phone: 444278 (0742)



Wilmslow Audio

THE firm for speakers!


SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMAN ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNON ● VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

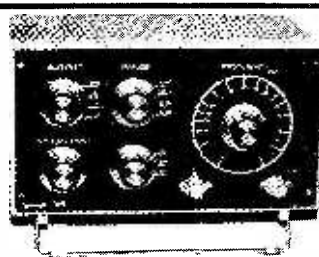

Model 146
VERY LOW DISTORTION (.0015%) AUDIO SIG. GENERATOR

Based on J. Linsley Hood design (W.W.)
£36.00

(Kit. £31.00) + tax 8%

Low cost version, AO113 (.02% dist.) £27.50 (Kit. £23). Other instruments include Millivoltmeter, Tachometer, Noise level meter, Distortion Analyser, F.M. Sig. Gen. Crystal Frequency Standard. KEF Speaker Units. Send S.A.E. for lists. VAT extra 8%. Post/Pkg. £1.50.

TELERADIO ELECTRONICS

325 Fore Street, Edmonton N.9. 01-807 3719

Closed all day Thursday

Printed Circuit Coils

(Pat. App. For)

For the **P.W. Sandbanks**, only available from the designer of the detector. By reducing the coil capacitance, vast improvements in sensitivity to gold and silver can be achieved and only four resistors need to be changed for maximum sensitivity. A complete kit including the PC coil to fit the Ambit International moulding, the four resistors required, and instructions for only £2.50 are available from:

PLESSIS ELECTRONICS,
Castle House, Old Road, Leighton Buzzard, Beds.
Callers by appointment only

LOOK! Here's how you master electronics. the practical way.


This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

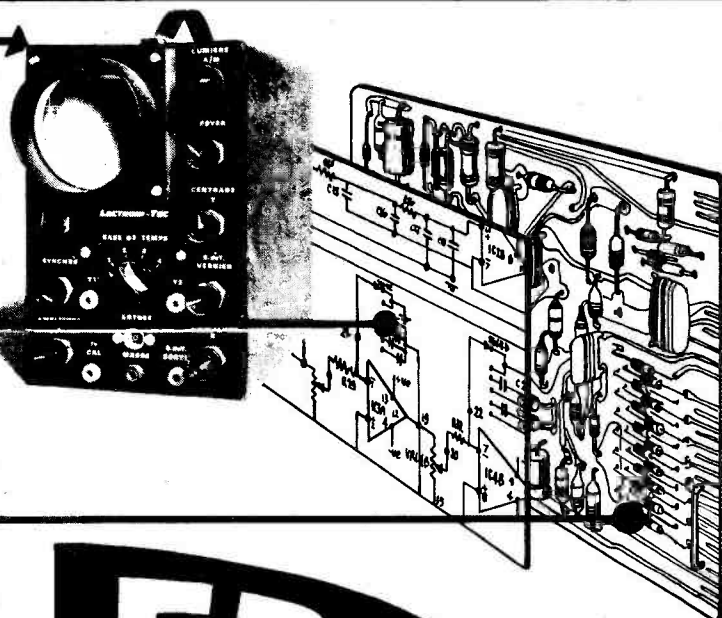1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

FREE

Post now, without obligation, to:-


BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

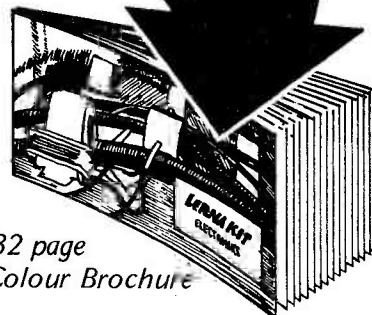

32 page
Colour Brochure

WB379

ambit international [®]

Production of the new catalogue has been held up for a few weeks - since we have just been appointed as distributors for two of the most exciting ranges of radio components products yet: The Micrometals range of iron dust torroids cores and formers, and the OKI range of VLSI for digital frequency displays for receivers. We apologize for any inconvenience, but these two ranges are really worth the wait, and include some products you will find hard to believe, like the MSM5523 IC, an IC with less than ten internal components that gives AM frequency readout to 1kHz from LW to 39.999MHz, FM frequency readout in 100kHz steps - (all usual IF offsets programmable by diodes), a 24 hour format clock with 12 hour display, independent on and off timers, time signals on the hours, stopwatch facility and a sleep timer. This costs £14 with its timebase crystal, and makes all that has gone before an expensive and time wasting exercise. Rather like the way the Intersil ICM7216 has revolutionized the instrument counter market. (See the OSTs ad.) And those of you familiar with Amidon and IG dust torroids, favoured in many new RF designs, will be pleased to know Ambit will be stocking a broad range of the Micrometals types for applications from EMI filters to RF PA stages.

OKI frequency counter ICs: details in cat2
MSM5523 for CA LEDs with RHDP such as FND507 £14 inc xtal
MSM5525 for 3½ digit LCD AM/FM with direct segment drive, no clock or timers £11 inc xtal
Other types for fluorescent displays etc OA

Other new semiconductor additions:
KB4437 pilot cancel mpw decoder 4.35
KB4438 muting stereo preamp 2.22
HA1370 supercides TD A2020 2.99
TDA1090 HiFi AM/FM 3.35
TDA1220 low cost AM/FM 1.45

PRICES DOWN ON VMOS: as expected, this new technology in power transistors is getting cheaper. 120v comp pairs /100W for £10.00

Price reduction on CA3189E ...now £2.20

New varicaps: to add to the biggest range....

KV1211 2-9v bias to tune MW, like the KV1210, but a double diode £1.75

New pilot tone filters from TOKO.....

208BLR series, individual per channel with a 26/38kHz version for pilot cancel decoder applications. Flat to 15kHz £0.90

New crystal filter for amateur NBFM.....

TOYO 10M4B1 with over 90dB adjacent ch. rejection for 2m NBFM. 10.7MHz £14

New ceramic IF filters for 455kHz.....

CFM455H 6kHz/6dB, 15kHz max /60dB - ideal for MC3357 etc. £10

A brief summary of some of our range of ICs:
TDA1062/1.95; TDA1083/1.95; HA1197/£1.40
CA3123E/£1.40; TBA651/£1.81; CA3089/1.94
HA1137/£2.20; MC1310/£2.20; HA1196/£3.95
KB4424/£2.75; KB4423/£2.53; SD6000/£3.75
KB4412/£2.55; KB4413/£2.75; KB4417/£2.55
MC1495L/£5.86*; MC1496P/£1.25
LM381N/£1.81; LM1303/£0.99; ULN2283B/£1.00; LM380N/£1; TB A810AS/£1.09
TC A940E/£1.80; TD A2002/£1.95;
ICL8038CC/£4.50*; NE566/£2.50*; NE567/£2.50*; NE560B/£3.50; NE561B/£3.50;
NE562B/£3.50*; NE565A/£2.50*

SEE THE OSTs ADVERT FOR CMOS/TTL REGULATORS, OPTO DISPLAYS, and other types of linear devices.

Some transistors for RF specifically:

BF256LB/0.34; 40822/0.43*; 40823/0.51* 40673/0.55*; BF900/961/0.80*; BF960/1.60*

BF224/0.22; BF274/0.18; BF195/0.18; BF240/0.22; BF241/0.22; BF362/0.70; BF479/0.86; BF679S/0.70; BFY90/0.90*

PIN and other Varicap diodes:

BA102/0.30; BA121/0.30; ITT210/0.30
BB104B/0.40; MVAM2/£1.48; MVAM115/£1.05; MVAM125/1.05; KV1210/£2.75
BA479/0.35; TDA1061/0.95; BA182/0.21

METER MADE low cost panel meters:

3 x 930 series with blanks and dry transfer sheet of scales and legends for £12.5*

TERMS etc: CWO please. VAT on Ambit items is generally 12½%, except where marked (*). Catalogue part 1:45p, part 2 50p all inclusive. Postage 25p per order, carriage on tuner kits £3. Phone Brentwood (0277) 216029/227050 9am-7pm. Callers welcome inc. Saturdays.

At last, DIY Hi Fi which looks as if it isn't.

That's not to say it doesn't look like Hi-Fi - just that it doesn't look like the usual sort of thing you have come to associate with DIY Hi-Fi. The Mk3 outstrips and outperforms all British made Hi-Fi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if it isn't. It's something else.....

- * Exceptionally high performance - exceptionally straightforward assembly
- * Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- * Various options and module line-ups possible to enable an installation approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- * Matching both the style and design concepts of the MkIII HiFi FM tuner
- * Hitachi VMOS power fets - characterized especially for HiFi applications
- * Power output readily multiplied by the addition of further MOSFETs
- * VU meters on the preamp - not simply dancing according to vol level
- * Backed with the usual Ambit expertise and technical capacity in audio


The PW Dorchester-LW, MW, SW, & FM stereo tuner



In much the same way as we have swept away the 'old technology' in frequency/timer counters - with the OKI and Intersil single IC counters, we now offer a single IC "All Band" radio tuner. Don't confuse this one chip radio with things like the ZN414 - for this is a genuine superhet receiver with a mechanical AM IF filter, and ceramic IF filters for FM. The AM section employs a balanced input mixer section, covering all broadcast bands - plus a BFO and MOSFET product detector for SSB/CW - though at this price, the tuner is not intended as a "communications receiver" - although we know of many lesser designs that make that claim. The AM sensitivity is nevertheless better than 5uV, and FM sensitivity is 1.2uV for 30dB S/N. As a multiband broadcast superhet receiver, it is a unique constructor project that fulfills the requests we very frequently get for a general coverage circuit that isn't over complicated. The set has CA3089E FM performance, with mute etc., and a PLL stereo decoder with full pilot tone filtering. The tuner board - with "on board" PCB mounted switching, all components etc : £33.00
The case/cabinet with PSU, meter and mechanics etc £25.00
An SAE for full details please. See the feature article in Practical Wireless (Dec/Jan)

2 Gresham Road, Brentwood, Essex.

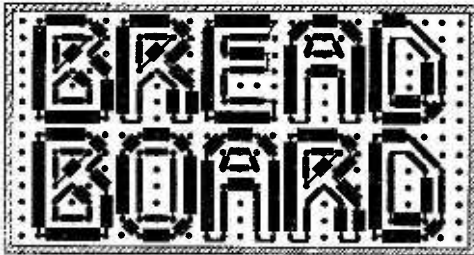Following the success of Breadboard '78, Trident Exhibitions announce



The second hobby electronics show

Information on exhibiting from:
Trident International Exhibitions Limited,
Abbey Mead House, 23a Plymouth Road,
Tavistock, Devon. PL19 8AU.
Telephone (0822) 4671 Telex 45412 TRITAV

December 4th - 8th Royal Horticultural Hall, Westminster, London SW1

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ainslie) Copy of original article supplied on request

- IF Sub-Assembly (G8) £6.80. P & P 75p.
- Mullard ELC1043 V'cap UHF Tuner £5.50. P & P35p.
- 3-way Station Control Unit £1.20. P & P 25p.
- 6-way Station Control Unit (Special Offer) £1.00.
- Power Supply Prtd Circuit Board £1.00. P & P 30p.
- Res, Caps, Semiconds, etc. for above £5.80.
- Mains Transformer for above £2.50. P & P 30p.
- Add 12½% VAT to price of goods. P & P all items 85p.

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751



ACE MAILTRONIX LTD
Dept. PW, Tootal Street
Wakefield, W. Yorkshire WF1 5JR

TOPS THE PACK!

- COMPONENTS** - Now over 1,000 types in stock!
- KITS** - See the new range of low-cost 'ELEKITS'.
- MODULES** - New ready-built functions.
- SERVICE** - 1st Class same day despatch.
- QUALITY** - All guaranteed products.
- PRICES** - Many reductions!
- MAGAZINE PROJECTS** - Trouble-free!

I enclose 30p*, please send catalogue.

Name _____
Address _____

*Refundable with future orders over £5.00.

OSTS

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

SEE THE AMBIT AD TOO!

CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	59p	4069	20p	4532	125p
4010	59p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4016	52p	4075	20p	4541	141p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	60p	4078	20p	4553	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	396p
4023	17p	4086	82p	4558	117p
4024	75p	4089	150p	4559	385p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4180	90p	4572	251p
4032	100p	4181	90p	4580	600p
4033	145p	4182	90p	4581	319p
4034	200p	4183	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	85p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	99p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	55p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

Micromarket

6800 series	8216	1.95	2114	£10
6800P	8224	3.50	2708	£10.55
6820P	8228	4.78		
6850P	8251	6.25		
6810P	8255	5.40		
6852				
8080 series	2102	£1.70		
8080	2112	£3.40		
8212	2513	£7.54		
	4027	£5.78		

PRICES SLASHED TTL: Standard AND LP Schottky

'N'	'LSN'	'N'	'LSN'	'N'	'LSN'	'N'	'LSN'	'N'	'LSN'	
7400	13	20	7455	35	74126	57	44	74185	134	
7401	13	20	7460	17	74128	74		74188	275	
7402	14	20	7463		74132	73	78	74190	115	
7403	14	20	7470	28	74133		29	74191		
7404	14	24	7472	28	74136		40	74192	105	
7405	18	26	7473	32	74138		60	74193	105	
7406	38		7474	27	74139		60	74194	105	
7407	38		7475	38	74141		60	74195	95	
7408	17	24	7476	37	74142	265		74196	99	
7409	17	24	7478		74143	312		74197	85	
7410	15	24	7480	48	74144	312		74198	160	
7411	20	24	7481	86	74145	65		74199	160	
7412	17	24	7482	69	74147	175		74248		
7413	30	52	7483A		74148	109		74249	93	
7414	51	130	7484	97	74150	99		74251	90	
7415	30	24	7485	104	74151	64	84	74253	105	
7416	30	24	7486		74153	64	54	74257	108	
7417	30	24	7489	205	74154	96		74258	153	
7420	16	24	7490	33	74155	54	110	74259	420	
7421	29	24	7491	76	74156	80	110	74260	153	
7422	24	24	7492	38	74157	67	55	74261	353	
7423	27	27	7493	32	74158		60	74266	40	
7425	27	27	7494	78	74159	210		74273	124	
7426	36	27	7495A	65	99	74160	82	130	74275	312
7427	27	29	7496	58	120	74161	92	78	74279	52
7428	35	32	7497	185		74162	92	130	74283	120
7430	17	24	74100	119		74163	92	78	74290	90
7432	25	24	74104	62		74164	104		74293	95
7433	40	32	74105	62		74165	105		74295	100
7437	40	24	74107	32	38	74166			74298	100
7438	33	24	74109	63	38	74167	20		74324	157
7440	17	24	74110	54		74168			74325	242
7441	74		74111	68		74169		200	74326	237
7442	70	99	74112	88		74170	230	200	74327	247
7443	115		74113			74172	625		74352	100
7444	112		74114		38	74173	170		74353	100
7445	94		74116	198		74174	87	120	74362	715
7446	94		74118	83		74175	87	110	74365	49
7447	82		74119	119		74176	75		74366	49
7448	56	99	74120	115		74177	78		74367	43
7449	99	99	74121	25		74180	85		74368	49
7450	17		74122	46		74181	165	350	74373	77
7451	17	24	74123	48		74182	160		74374	77
7453	17		74124	38	44	74183		210	74375	60
7454	17	24	74125	38	44	74184	135		74375	450p

Voltage Regs

NEW LOW PRICES

7800 series UC TO220 package 1A	all 95p
7900 series UC TO220 package 1A	all £1
78MUC series TO220 package 1/2A	all 90p
78LCP series TO92 100mA	all 35p

L200 up to 3A/adjustable V&A 195p

78MGT2C 1/2amp adjustable volts	175p
79MGT2C 1/2amp adjustable volts	175p
723C precision controller	65p

MAINS FILTERS FOR NOISE/RFI etc

1 amp in IEC connector	£4.83
5 amp in 'wire in' case	£3.87
NE550A	73p

LINEARS non-consumer

BIMOS

CA3130E	84p	LM339N	66p
CA3130T	90p	LM348N	186p
CA3140E	35p	LM3900N	60p
CA3140T	72p	709HC to5	64p
CA3160E	90p	709PC dil	36p
CA3160T	99p	710HC to5	65p
Op amps		710PC dil	59p
LM301AH	67p	723CN	65p
LM301AN	30p	741CH to5	66p
LM308H	121p	741CN 8dill	70p
LM308N	97p	747CN	27p
LM318H	29p	748CN	36p
LM318N	224p	NE531T	120p
		NE531N	105p

OPTO 7 seg displays

0.43" High Efficiency HP:

5082-7650	red CA	
5082-7653	red CC	
5082-7660	yellow CA	233p
5082-7663	yellow CC	
5082-7670	green CA	
5082-7673	green CC	

0.3" Standard HP

5082-7730	red CA	147p
5082-7740	red CC	

0.5" Fairchild

FN0500	red CC	150p
FN0507	red CA	150p

TERMS: CWO p.s.e., VAT to be added at 8% (inland), pp 25p per order. When ordering from the OSTs and Ambit - a single combined remittance and pp charge is sufficient. Account details OA.

2 Gresham Road, Brentwood, Essex.

The ICL7216BIP1 is still the cheapest way to make a full 8 digit/ 10MHz frequency counter/timer, and with 10 external components + display - it is also one of the simplest. For £19.82, it takes a lot of beating. The mains filters have been extended now to include a 6amp IEC version at £5.10, and with the amount of electronic noise on the average supply (next door's fridge, for instance) it is a really worthwhile addition to any sensitive equipment. LPSN TTL now includes many more of latest types, all - of course - are absolutely prime first quality types. And don't forget our range of OPTO displays includes Hewlett Package high efficiency 0.43" types in all colours - renowned as the finest quality in the market. For other types of component - discrete LEDs, radio and audio devices, tuner modules, kits etc., see our other advertisement for more details - or send for the AMBIT catalogue system. Part one (45p) includes details of our background 'standard' items, and the new part two includes all the latest introductions and developments, plus a rundown on OSTs.

PROGRESSIVE RADIO
31 CHEAPSIDE, LIVERPOOL L2 2DY

MICROPHONES: EM506 Electret Dual Imp (50K + 600Ω) Imp Stick Mic, with Battery £11.00. Electret Model ECM105 Pencil Hand Mics IKΩ impedance, with standard jack £2.85. EM104 Tie Clip. Electret supplied with battery 1K imp £4.95. UD130 Dual Imp (50K + 600Ω) moving-coil dynamic mic, cardioid response £8.25p.

BUZZERS, GPO open type 3-6V 30p. Large plastic domed type loud note 6 or 12 volts 50p. Solid state buzzers, miniature, 6-9-12-24 volt 15ma 75p each.

MAINS TRANSFORMERS, all 240V AC primary, postage shown in brackets per transformer. 6-0-6 100ma, 9-0-9 75ma, 12-0-12 50ma 75p each (65p). 0-4-8-9 150ma no mounting bracket, 65p (20p). 12-0-12 100ma 85p (45p). 12V 500ma 85p (22p). 12V 2 amp £2.25 (45p). 12V 4 amp £2.75 (54p). 15-0-15V 1 amp £2.10 (45p). 30-0-30V 1 amp £2.75 (54p). 0-12-15-20-24-30V tapped at 2 amp £4.50 (54p). 20-0-20V 2 amp £3.50 (54p). 25V 1.5 amp £1.45 (45p). 18V 1.5 amp rectified £2.00 (45p). 35V 2 amp, 2.5V 2 amp Toroid £2.95 (54p). 20V 2.5 amp, £2.20 (54p). Murata MA401L 40KHz rec/send transducers £3.25 pair.

SMITHS TRANSISTORISED AUDIBLE WARNING DEVICE, 6-12V, 30p.

BOARDS SURPLUS. Reed Board with 14 12v Reed SP c/o RLAS £1.75. LM309K 5v Regulator Panel 65p.

NEW LOW COST MULTIMETERS.
KRT100, 1000Ω. P.V. 1KV AC/DC. 150mA DC current. 0-100KΩ res. mirror scale, switched range selector. £4.65.
KRT101, same as KRT100 but range selection is by prod insertion, £3.50.

TAPE HEADS Mono Cassette £1.50. Stereo version £3.00.

SOLDER SUCKER, high suction eye protection shield £4.95.

PROJECT BOXES, black plastic ABS with lid 75 x 56 x 35 44p; 95 x 71 x 35, 52p 115 x 95 x 36 60p.

TERMS: cash with order, (or official orders from colleges etc). Postage 30p unless otherwise shown, overseas post at cost. VAT inclusive prices. New illustrated catalogue now ready. S.A.E. please.

Progressive Radio, 31 Cheapside, Liverpool L2 2DY. Tel: 051 236 0982.

SOLVE your component buying problems with this famous Catalogue




- The finest components catalogue yet published.
- 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Profusely illustrated.
- Bargain List sent free.
- At £1.25, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD.,
Dept. PW., 234-240 London Road,
Mitcham, Surrey CR4 3HD

WH BRIGHTCASE

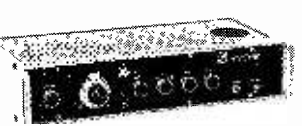Box your "HYTHE" MARINE BAND RECEIVER (P.W. Jan. & Feb.) in our BRIGHTCASE BC2 121 X (£27.25 without front panel: add 8% VAT).



Use our Swiftcase SWF 222 (£16.95 plus 8% VAT) for your Burley P.S. (P.W. Nov. 78) Send for catalogue.

WEST HYDE DEVELOPMENTS Ltd.,
Unit 9, Park St. Ind. Est., Aylesbury, HP21 1ET.
Aylesbury 20441. Telex 83570.

POST THIS COUPON
with cheque or P.O. for £1.25

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

HOME RADIO (Components) LTD., Dept. PW., 234-240 London Road, Mitcham, Surrey CR4 3HD. (Regn No London 912966)

The best things come in little packages?

Are you shopping for Antennas and Receivers?

The JOYSTICK VFA gives you a six amateur band or continuous tuning (0.5-30MHz) effective ground plane, efficient, substantially harmonic free, space saving antenna. Proven performance, testimonials world-wide bulge in our files!

In use by amateur transmitting and SWL stations world-wide and in Government communication.

**JOYSTICK ANTENNAS
SYSTEM "A" £41.00**
200 w. p.e.p. OR for the SWL

SYSTEM "J" £47.95
500 w. p.e.p. (Improved "Q" on receive)

"PACKAGE DEALS" COMPLETE RADIO STATIONS FOR ANY LOCATION

All packages include the JOYSTICK VFA (System "A") 8ft feeder, all necessary cables, matching communication headphones. Delivery Securocor our risk. ASSEMBLED IN SECONDS. You SAVE £14.15 on each PACKAGE DEAL!

PACKAGE No. 1 £222.00
Features R. 300 Rx.

PACKAGE No. 2 £237.45
Features FRG7 Rx.

PACKAGE No. 3 £212.45
Features SRX 30 Rx.

PACKAGE No. 4 £402.00
Our "Rolls" - RX. FRG 7000

RECEIVERS ONLY

R.300 £184.50 FRG7 £199.95
SRX 30 £174.95 FRG 7000 £364.50

All prices are correct at time of going to press and include VAT at 12½% and carriage.



Just telephone
your card number
Phone 0843 62535 (ext.5)
(or 62839 after
office hours)



or write for details, send 9p stamp

G3CED



G3VFA

5, Partridge House, Prospect Road, Broadstairs,
CT10-1LD. (Callers by appointment).

ELECTROVALUE

FOR A GOOD DEAL BETTER THAN MOST

WE PAY POSTAGE on C.W.O. orders in U.K. over £5.00 list value.

WE GIVE DISCOUNTS on U.K. C.W.O. orders — 5% for list value over £10.00; 10% for list value over £25.00.

WE GUARANTEE all goods are brand new, clean and to specification — no seconds, no surplus.

WE GIVE SERVICE to all orders large or small — to help we microfilm orders, computer processing and double check personal supervision.

Specialist
Mail Order
Suppliers
Since 1961

This month's ELECTROVALUABLES

'Electrovaluables' are our own overstock items offered from time to time at greatly reduced prices. Orders should quote 'Electrovaluables' and state description and price as advertised. PRICES ARE NET AND V.A.T. MUST BE ADDED + 8% or 12% where prices show ●

- | | | | |
|-----------------------------------|---------|-----------------------------------|------------|
| Aluminium knobs (Eagle) | 40p | Laquer film (professional) | 4 for £1 |
| K30/1 (dia 13 mm) | 40p | Siemens B32110 1/2F 250V | each £1 |
| K30/3 (dia 17 mm) | 40p | B32120 4-7F 63V | each £1 |
| K30/5 (dia 24 mm) | 50p | 4-7F 160V | each £1.50 |
| JV knob pairs. | | 10V 63V | each £1.50 |
| JV23/6T & JV18/4 in yellow, | 50p pr. | Polystyrene Siemens | |
| Green or Blue | | B31110. 7pF, 160, 200, 560pF | |
| JV18 in Red, Yellow, Blue 20p ea. | | (160V) 820pF (63V) any 100 for £2 | |
| JV23 in Red, Yellow, Light | 20p | B31310. 4700pF (63V) | £2.50 |
| Grey | | for | |
| Veroboard 5" x 3-4" x 2" matrix | 20p | Polypropylene Siemens B33063 | |
| Transformer cores 0-5W 50 Hz | 20p | 100, 470, 2200, 4700, 5100, | |
| Unisil, Belclere kit ES | 20p | 6800, 10000 pF any 100 for £4 | |
| Edge connectors 36 way .1" | 50p | Polyester Siemens B32231 | |
| 16 way .15" gold flash | 80p | axial lead .033/400 ● .047/ | |
| 24 way .15" gold flash | 80p | any 15 for £1 | |
| Rocker switches 15A | 250V | High voltage polyester | 50p |
| DPST No 50A | 25p | Siemens B32227 | 30p |
| DPDT No 50D centre-off | 25p | 0-1/2F 4KV each | |
| Ceramic capacitors | | 0-25/2F 1KV each | |
| disc .02, B37448 40V .022 100 | £2● | Polyester PC Mounting | 10p |
| for | | Siemens B32234 | |
| | | 0-68/250V each | |

WE ARE NATIONAL DISTRIBUTORS FOR



NASCOM MICROCOMPUTER KITS
for delivery from stock from £197.50 net
+ V.A.T.

Also supporting Nascom items available now.
Enquiries invited. Quantity discounts.

**MOTOROLA D.2 MICROPROCESSOR
EVALUATION KIT**
(for the M.680 Microcomputer — £175.87 net
+ V.A.T.)

CATALOGUE 9

**Yours for the asking —
and it's FREE**

Completely revised, up-dated and more attractively presented. 120 pages—semi-conductors, I.C.s, Opto-electronics, Rs, Cs, materials, tools, connectors, etc. etc. And you'll be delighted with our three-month competitive stabilised price list.

**Two depots to serve you
One North, One South**

All communications, orders etc., to Englefield Green address, Dept. PW3.

ELECTROVALUE LTD


28, ST. JUDES ROAD, ENGLEFIELD GREEN,
EGHAM, SURREY TW20 0HB

Telephone Egham 3603 · Telex 264475
Northern Branch - 680, BURNAGE LANE,
BURNAGE, MANCHESTER M19 1NA(061)432 4945
Shop hours 9-5.30: 1.00 pm Sat.

The Sinclair PDM35.

A personal digital multimeter for only £29.95

(+8% VAT)

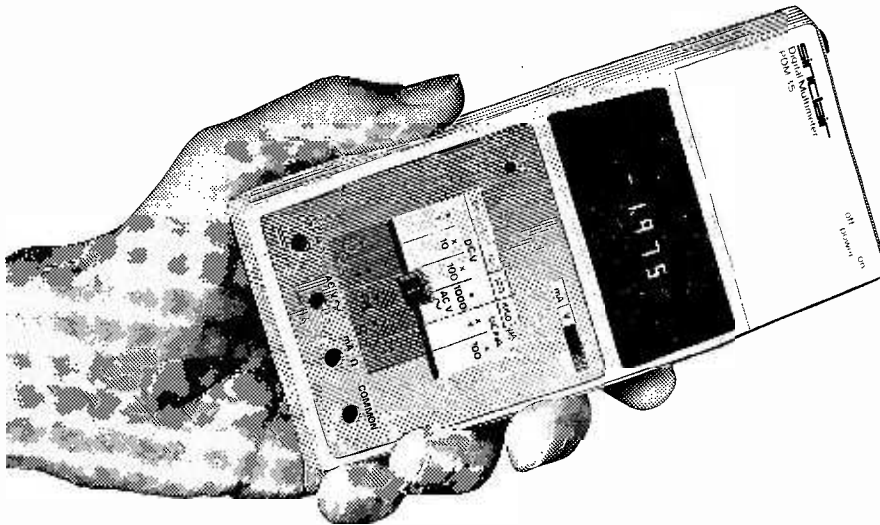

Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

What you get with a PDM35

3½ digit resolution.

Sharp, bright, easily read LED display, reading to ±1.999.

Automatic polarity selection.

Resolution of 1 mV and 0.1 nA (0.0001 µA).

Direct reading of semiconductor forward voltages at 5 different currents.

Resistance measured up to 20 MΩ.

1% of reading accuracy.

Operation from replaceable battery or AC adaptor.

Industry standard 10 MΩ input impedance.

Compare it with an analogue meter!

The PDM 35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 MΩ is 50 times higher than a 20 kΩ/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

Technical specification

DC Volts (4 ranges)

Range: 1 mV to 1000 V.

Accuracy of reading 1.0% ± 1 count.

Note: 10 MΩ input impedance.

AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading: 1.0% ± 2 counts.

DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading: 1.0% ± 1 count.

Note: Max. resolution 0.1 nA.

Resistance (5 ranges)

Range: 1 Ω to 20 MΩ.

Accuracy of reading: 1.5% ± 1 count.

Note: Also provides 5 junction-test ranges.

Dimensions: 6 in x 3 in x 1½ in.

Weight: 6½ oz.

Power supply: 9 V battery or Sinclair AC adaptor

Sockets: Standard 4 mm for resilient plugs.

Options: AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV high voltage probe.

An unbeatable pedigree

The Sinclair PDM35 comes to you from the same stable as a whole range of electronic world-firsts – from custom large-scale IC's and laser-trimmed resistor networks, to programmable pocket calculators and miniature TVs.

Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

We'll mail your PDM35 by return!

Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon,
Cams., PE17 4HJ, England.
Regd No: 699483.

Send to: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cams., PE17 4HJ.
Please send me a Sinclair PDM35 @ £29.95 plus £2.40 (8% VAT) and 65p P&P, total £33.00.

Please include (tick items required): De-luxe padded carrying case @ £3.00 (inc VAT).
AC adaptor for 240 V 50 Hz power @ £3.00 (inc VAT)

I enclose cheque/PO for.....
(indicate total order value), made payable to Sinclair Radionics Ltd. PW3

Name.....

Address.....

I understand that if I am not completely satisfied with my PDM35 in every way, I may return it within ten days for a full cash refund.



sinclair
World leaders in fingertip electronics



FIRST with the NEW MODULAR KEYBOARD SYSTEM

Catronics Ltd. are proud to announce the introduction of the World's First Modular Keyboard Kit available to the home constructor!

The PCB is designed to take a maximum of 70 keys but may be assembled with a smaller number of keys for a simpler keyboard.
The board is not dedicated to any specific coding, allowing it to be used for any project whether it requires ASCII, Baudot or any other code. This makes it suitable for many projects including:

- E.T.I.—System 68 MPU (54 keys)
- RadCom—G3PLX RTTY VDU (36 keys)
- Auto Morse sender, etc.

The Keyswitches themselves are single pole push-to-make type and require no extra mechanical mounting arrangements.
A legend sheet is provided with each kit enabling the constructor to label the keys to suit individual requirements.

Kit for 70 station Keyboard £29.00
Please add 50p for postage.

SPECIAL PRICES for 7400 SERIES TTL

All new, full specification, full Guarantees.
Mostly National and Texas products

7400	14p	7421	31p	7483	78p	74145	£1.24	74177	84p
7402	14p	7427	29p	7485	£1.12	74150	£1.07	74180	92p
7403	14p	7428	38p	7486	33p	74153	69p	74188	£3.40
7404	15p	7430	18p	7490	36p	74157	72p	74192	£1.38
7406	40p	7432	27p	7492	52p	74161	59p	74193	£1.38
7408	18p	7440	18p	7493	39p	74164	£1.12	74195	£1.03
7410	16p	7442	73p	7496	97p	74165	£1.12	74196	£1.00
7411	22p	7447	75p	74107	35p	74166	£1.60	74221	£1.75
7412	24p	7473	35p	74121	28p	74170	£2.48	74H00	35p
7414	75p	7474	29p	74123	79p	74174	94p	74H04	44p
7420	17p	7475	46p	74126	61p	74175	94p	74H10	39p

10% DISCOUNT on TTL orders over £20.
Prices INCLUDE VAT but please add minimum of 30p for post & pkg.

Send SAE for FREE PRICE LIST or 45p+ large (A4) 18½p SAE for copy of our DATA CATALOGUE.



Catronics Ltd. (Dept 983), Communications House, 20 Wallington Square, Wallington, Surrey SM6 8RG
Telephone: 01-669 6700. Open Mon.-Fri. also Sat. a.m.



for VALUE & VARIETY in FREQUENCY COUNTERS

In addition to our popular 250MHz and 500MHz counters we have produced a NEW 200MHz COUNTER KIT specially for home constructors.

Our new KF200 counter, although small, is a no-compromise design. It offers:

- ★ A full 8 digit LED display.
- ★ A frequency range of 10Hz to 200MHz.
- ★ An accuracy of 10Hz at 30MHz, 50Hz at 150MHz in normal home environments.
- ★ 5/6 volt operation from batteries or mains PSU.
- ★ Power consumption of only 1W maximum.
- ★ A crystal oscillator at 5MHz which doesn't need any special setting up equipment.
- ★ Small size 4" x 2" x 1".
- ★ Uses only 4 i.c.s.
- ★ Assembly time of about 2 hours.
- ★ Full illustrated assembly instructions.

The KF200 consists of 2 PCB assemblies, one being the complete input and counter unit (Suitable for direct driving an 8 digit common cathode display), the other, the display unit. Both units are available in kit or assembled/tested module form. Prices (INCLUDING VAT).

Input/Counter Kit	£59.00	Display Kit	£12.96
Input/Counter Module	£68.50	Display Module	£16.64

Add 75p for Post & Pkg.

This new Catronics model KF200 complements our DFM5, a 250 MHz, 7 DIGIT MAINS/12v HIGH QUALITY Frequency Counter, and the DFM 500 — a REAL 500 MHz — try some of the others actually at this frequency.


Both are absolute value for money and are available now with better than 1-in-10⁷ reference oscillators as /S models.

Special Prices, INCLUDING VAT:

DFM5	£148.50	DFM5/S	£191.70
DFM 500	£177.12	DFM500/S	£220.86

Add £5 for Insurance and for Securicor Delivery

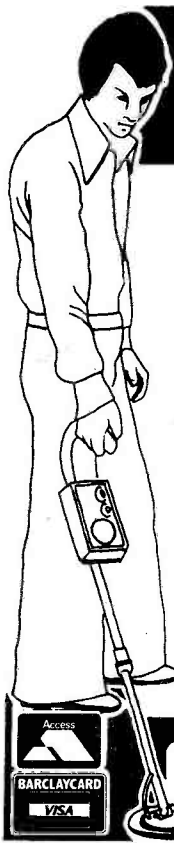Leading detector designs now available as kits



Super performance true TR/IB (Transmit Receive/Induction Balance) metal detector using the very latest integrated circuitry. The most sophisticated detector now available in kit form. Range for coin 8" to 12" depending on conditions; PP3 battery lasts over 50 hours; fully adjustable shaft & search head. Plus many other refinements. If you are thinking of buying any other detector — phone us first (without obligation) for a frank comparative assessment. Or send S.A.E. for instruction sheet which gives more information than space here permits.

- "Shadow" metal detector £29.95 post paid
- "Shadow" kit (pre-wound coils) £22.50 post paid
- Padded headphones £5.50

Send 25p for assembly manual refundable against kit purchase

Building your own detector? Then we can supply the hardware "shell". Including fully adjustable shaft with handle. Special clips to mount your own control housing (any box is suitable) and search head mouldings with adjustable ball joint hinge.


Suitable for any type of detector (BFO-TR-IB-PI, etc.) including those published in this and other magazines. As used for our own "Shadow" detector. Supplied undrilled as a kit with full instructions.

Detector "Shell" kit £7.50 post paid

SPECIAL OFFER: To every purchaser of our "Shell" kit we are giving away a copy of our publication "Metal detector design notes" which gives much useful information on many different types of metal detectors and detection techniques, including TR, IB, BFO, PI, VLF, Proton Magnetometer, Discriminators, Phase locked loops, Harmonic mixing, Hall effect, Off resonance, Coupled field, Faraday shields, Push button tuning, Legal frequencies, other legal requirements, how to obtain Home Office approval, etc. etc. Contains many interesting circuits (including commercial designs) too numerous to list. A wealth of priceless information much of which has not been published before.

QUALITY NOTE: All Altek detectors use high epoxy glass/roller tinned boards. Some manufacturers still use plain copper which quickly corrodes in damp weather. All Altek detectors are Home Office approved. Phone in your credit card number now (24 hour answering).

A good all round low cost metal detector, 200mm (8") annular search head gives wide scan with easy pinpointing. Simple high efficiency B.F.O. circuitry draws <1.5mA, inexpensive battery gives over 100 hours search time. Ferrous/non ferrous discrimination possible. Extra lightweight, 300 gms (10.5 ozs) with battery—eliminates arm fatigue, even for a child. The lowest priced metal detector.
ALT3—£12.95 + £1 towards p+p.

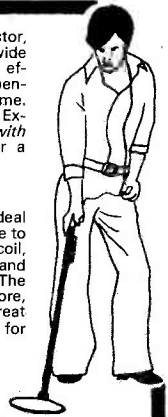


Build it yourself. Very detailed manual—ideal for a beginner as a first project (must be able to solder). Pre-wound search loop and tuning coil, absolutely everything supplied except tools and battery. The least expensive way of buying. The parts bought separately might cost you more, certainly it'd take more time. Makes a great present for a younger brother, etc. (buy it for him—use it yourself!).
ALT3 (kit)—£9.95 + £1 towards p+p.

- Accessories for ALT3
- Stethoscope adaptor 85p post paid
- Padded headphones £4.90 post paid

Send 25p for Assembly Manual refundable against kit purchase.

All prices include VAT

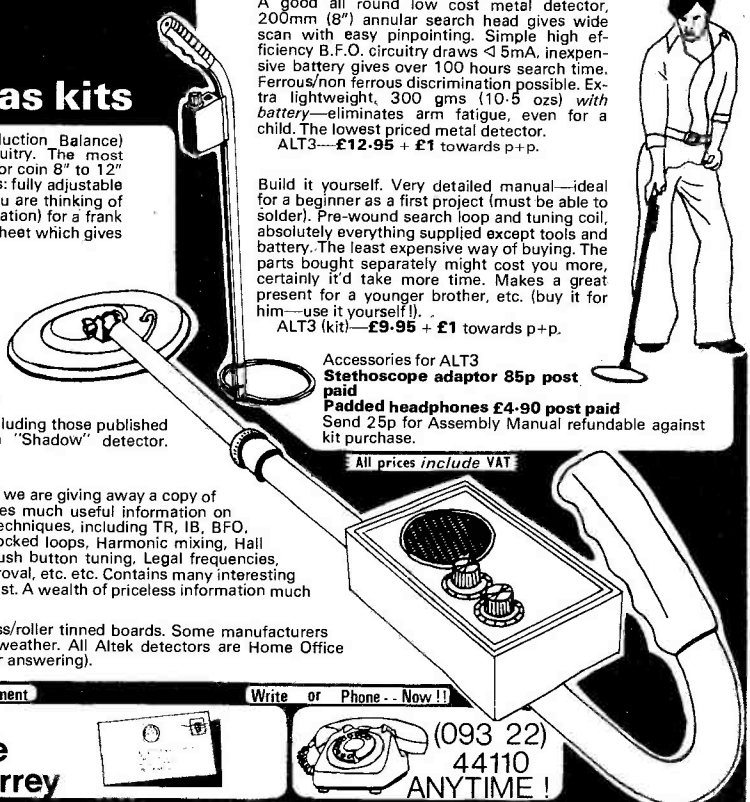

Mail Order only please Callers by appointment

Write or Phone - Now!!

Altek Instruments
Dept. PA 1 Green Lane
Walton-on-Thames Surrey



(093 22)
44110
ANYTIME!




EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround; 2 1/2" approx. Audaux tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95 Per stereo pair + £3.40 p&p.

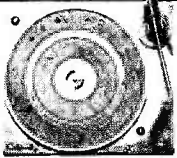As above but complete with all woodwork in kit form, finished in simulated teak veneer, with instructions Size approx 20" x 11" x 9 1/2" £28.00 Per stereo pair + £5.00 p&p.



BSR Manual single play record deck with auto-return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited from home or disco use. OUR PRICE £10.95 p&p £2.55

TURNTABLE BARGAINS FOR PERSONAL SHOPPERS

GARRARD 86SB Deck

£26.95

GARRARD SP25 MKIV Deck with Shure head

£25.95

Plinth and cover for BSR decks £6.00

BARGAINS FOR PERSONAL SHOPPERS

PORTABLE STEREO RADIO CASSETTE RECORDER

UNREPEATABLE

MW, LW, SW and Stereo VHF. 6 watts output Battery/Mains operation.

160 16 VOLT MAINS TRANSFORMER, 2 1/2 amp.

Garrard Record auto deck on plinth with stereo cartridge ready wired.

LED 5 function men's digital watch stainless steel finish

LCD 5 function men's digital watch stainless steel finish

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish.

Battery/Mains cassette recorder with built in mic.

AM/FM DIGITAL CLOCK RADIO

Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.

£11.95

125 Watt Power Amp Module

Mains power supply for above unit.

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/2" x 14 1/2" x 7 1/4" approx.

MULLARD Built power supply

DECCA DC 1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads.

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers

VIDEOMASTER Super Score TV Game with pistol mains operation

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock.

LW, MW, SW, VHF mains/Battery operation.

7" TAPE TRANSPORT Mechanism—a selection of models from

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 3/4" x 1 1/4" x 2" approx.

£7.50 p+p £1.50p

AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE WITH DECODER

Ready built. Designed in a slim form for compact, modern installation.

Rotary Controls Va, On/Off, Bass, Treble, Balance.

Push Buttons for Gram, Tape, VHF, MW, LW and 5 button rotary

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz (150mV/100K) deviation

FM signal Frequency Range (Audio) 50Hz to 17KHz within ±1dB

Radio FM sensitivity for 3dB below limiting better than 10 uV

AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre

Size approx length 16" x height 2 1/2" x depth 4 1/2" p&p £19.95 £2.50

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE

PRICE £ AT OVER 25 PER PACK

SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE p+p £1.00 **£4.95**

2 PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2. Stereo pre amp for magnetic, ceramic and auxiliary inputs. OUR PRICE p+p £1.00 **£7.45**



GARRARD BARGAIN

LIST PRICE ~~£95.00~~



OUR PRICE **£39.95**

ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. £1.00 p+p

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE. p+p 50p **95p**

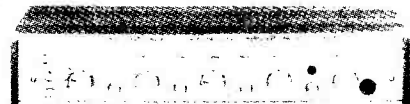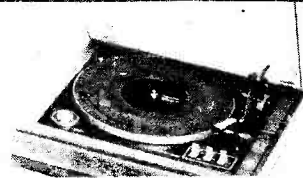86 SB MKII. Belt drive, 2 speed turntable module with plinth and cover.



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver fascia with aluminium rotary controls/pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus luse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers. £29.90 + £2.50 p&p

SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

FREE. 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet. p&p £2.50 in each case.

£23.00 + £2.50 (NOTE Cabinet not available separately.) £29.00 + p&p £2.50 complete with cabinet.

SPECIAL OFFER COMPLETE WITH 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3% approx. tweeters and crossovers. £49.00 + p&p £4.00

BUILT AND READY TO PLAY 39.00

30x30 Viscount. Available fully built and tested. + p&p £2.50



323 EDGWARE ROAD, LONDON W2
21D HIGH STREET, ACTON W3 6NG

ALL PRICES INCLUDE VAT AT 12 1/2%
All items subject to availability. Price correct at 14.12.78 and subject to change without notice.

50 WATT MONO DISCO AMP

£29.95

P&P £2.50

Size approx 13 1/2" x 5 1/4" x 6 1/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume. SPECIAL OFFER. The above 50 watt amp plus 4 Goodmans Type 8P 8" speakers. Package price £45.00 + £4.00 P&P.

70 & 100 WATT MONO DISCO AMP

£57

Size approx 14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls. Five vertical slide controls: master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading. 140 watt peak p & p £4.00. Output 100 watts RMS 200 watts peak. 100 watt £65

STEREO CASSETTE TAPE DECK ASSEMBLY

Consisting of ready built tape transport system/mechanism, mated to the electronics. Unit is ready built for installing into cabinet of own choice. Features include pause control, solenoid assisted auto-stop, 3 digit tape counter, belt driven balanced fly wheel by DC motor with electronic speed control, twin VU meters. Specification Power Output, more than 0.5w. m.c. -65dB 10KHz, DIN -47dB 100KHz. Track 2 channel stereo record play-back. Tape speed 4.8cm/sec. Freq. response 50.1200 Hz signal to noise ratio 42dB Recording system AC bias. Erasing system AC erase Bias freq. 57KHz. Compatible for both normal and chrome dioxide tapes. Size of mechanism only 4 1/2" x 6 1/4" x 11 1/4" approx. included a moulded top-plate as illustrated. 13 1/4" x 9 1/4" approx. with circuit diagram £25.00 P&P £2.50 Opt. extras Mains transformer to suite £2.50 + £1 p & p.

ENGINEERS

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

- | | | |
|--|--|--|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Radio, Servicing & Repairs | <input type="checkbox"/> Painting & Decorating |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT) | <input type="checkbox"/> Radio Amateur's Exam. | <input type="checkbox"/> MECHANICAL |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> A.M.S.E. (Mech.) |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> Motor Mechanics | <input type="checkbox"/> General Mech. Eng. |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> C. & G. Motor V. Technicians | <input type="checkbox"/> Inst. Engineers & Technicians |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> General Auto Engineering | <input type="checkbox"/> Maintenance Engineering |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Welding |
| | <input type="checkbox"/> Air Registration Board Certs. | |
| | <input type="checkbox"/> M.A.A./I.M.I. Dip. | <input type="checkbox"/> MANAGEMENT & PRODUCTION |
| <input type="checkbox"/> RADIO & TELECOMMUNICATIONS | <input type="checkbox"/> CONSTRUCTIONAL | <input type="checkbox"/> Computer Programming |
| <input type="checkbox"/> Colour TV Servicing | <input type="checkbox"/> Heating, Ventilating & Air Conditioning | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> DRAUGHTSMANSHIP & DESIGN |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> General Draughtsmanship |
| <input type="checkbox"/> Radio & TV Engineering Course | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> A.M.I.E.D. |
| | <input type="checkbox"/> Plumbing Technology | <input type="checkbox"/> Electrical Draughtsmanship |
| | <input type="checkbox"/> General Building | |



G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPW 24, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, London EC2Y 9DT. Tel. 628 2721.

NAME (Block Capitals)
ADDRESS
Postcode.....
Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF. Tel: 20767

- 400mW ZENERS unmarked Good 3-6, 6-8, 10, 11, 12, 13, 16, 18, 24, 30, 33, 36v. All at 10 for 40p.
ERIE RED CAP .01uf 100v.w. SUB-MINIATURE CAPACITORS @ 5p each.
BD187 4 Amp NPN PLASTIC POWER NPN TRANSISTORS @ 5 for £1.
MURATA 10.7MHz CERAMIC FILTERS @ 27p, VERNITRON FM4 10.7MHz FILTER @ 50p, MURATA 455KHz BFB FILTER @ 30p.
10 Amp S.C.R.s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
DAU TRIMMERS 2 to 9pf @ 10p, 6 to 45pf @ 10p, 0 to 125pf @ 12p, 8 to 140pf @ 15p, TETTER VHF TRIMMERS 10pf @ 18p.
VHF POWER TRANSISTORS unmarked Good 2N 3375 @ £1, 2N 3866 @ 3 for 75p, 2N 3553 @ 3 for £1-10.
ELECTROLYTIC CAPACITORS 1000uf 100v.w. @ 50p, 2200uf 100v.w. @ 60p, 3300uf 64v.w. @ 60p, 3300uf 40v.w. @ 50p.
HCBU CRYSTALS 38MHz, 40MHz, 44-3MHz, 45-9MHz, 46-5MHz, 46-7MHz, 48-3MHz, 50-1MHz. All at 50p each.
3 PIN PLUG AND SOCKET like R.S. European Type with Two Metres of Cable @ 75p pair.
10 ASSORTED PUSH BUTTON BANKS less knobs for £1-30.
SUB-MINIATURE TANTALUM 4-7uf 10v.w. @ 5p, 6 for 25p.
50 2 Watt ZENERS assorted untested @ 57p.
DISC CERAMICS .01uf 50v.w. @ 20p doz, .1uf 18v.w. @ 25p doz.
100 MINIATURE DIODES CV 9637 pre-formed leads @ 57p.
VHF FETS 40673T @ 33p, E304 @ 25p, J310 @ 20p, MFE 131 @ 60p, BF 256 @ 25p, 2N 3819T @ 20p.
MINIATURE BUTTERFLY PRE-SET VARIABLE CAPACITORS spindles easily extended 25 x 25pf @ 50p, 38 x 38pf @ 60p, 38 x 38pf Wide Spaced @ 65p.
50 VARI-CAP DIODES LIKE BA 102 untested @ 57p.
200 1/2, 1/4 Watt RESISTORS assorted for 75p.
MULLARD VARIABLE CAPACITORS Solid Dielectric 195 +80pf @ 40p.
30 ASSORTED 10XAJ CRYSTALS @ £1-10, 20 FT 243 CRYSTALS assorted @ £1-50, 20 FT 241A CRYSTALS assorted @ £1-10.
50 10X CRYSTALS assorted @ £1-50 (P. & P. £1-50).
TRANSISTORS BC 548 @ 10p, 6 for 50p, BC 549 @ 10p, 6 for 50p.
PLASTIC TRIACS 400 PIV 6 Amp @ 60p each.
COIL FORMERS 3/4" Dia. with core at 6 for 25p.
McMURDO 8 PIN PLUGS @ 20p, 8 PIN SOCKETS @ 20p, COVERS @ 15p.
500MHz FREQUENCY 8 DIGIT COUNTERS HFC 600 @ £115.
2 GHz STRIPLINE NPN TRANSISTORS @ £1 each.
100uf 100v.w. WIRE ENDED ELECTROLYTICS 10p, 5 for 35p.
MC 3340 ELECTRONIC ATTENUATOR I.C. with data @ 50p.
1uf 25v.w. ELECTROLYTICS at 6 for 25p.
20 PHOTO TRANSISTORS AND DARLINGTONS assorted untested @ £1.
SOLDER-IN FEED THRU's 6-8pf, 1000pf all 20p doz.
MULLARD T PACK 800MHz TRANSISTORS BF 362 @ 25p.
CRYSTALS 10X 8010KHz @ 40p, 10XAJ 7010KHz @ 30p.
VARIABLE CAPACITORS 25 + 25 + 25pf 1/4" Spindle direct drive @ 75p.
ELECTRET MICROPHONE INSERTS with FET Pre-amp @ £1-85.
 Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas post at cost.

- SINCLAIR PRODUCTS** microvision tv uk model E89-95, PDM35 £27.25, mains adaptor £3-24, case £3-25, DM350 £67-80, DM450 £96-50, DM235 £49-45, £3-70, enterprise prog calculator £21-95, cambridge prog calculator £13-13, prog. library £3-45, mains adaptor £3-45.
COMPONENTS send s.a.e. for full list. 1 lb FeCl £11-05, dalo pen 73p, 60 sq. ins. pcb 55p, laminate cutter 75p, small drill 20p, zn14 £1-05, pcb and extra parts for radio £3-85, case £1, 1N4148 1-4p, 1N4002 2-9p, 723 29p, 741 15p, NE555 23p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4-5p, plastic equivs bc107, bc109 4-8p, 1W 5% E12 resistors 10R to 10M 1p, 0-8p for 50+ of one value, electrolytics 16v .5/1/2/5/10/22mf 5p, 100mf 6p, 1000mf 10p, 1500mf (PC) 3-4p, 10v 2mf 1-7p, 1000mf 5-1p, 2200mf 6p, polyesters 250v .015, .068, .1mf 13p, ceramics 50v E6 22pf to 47n 2p, polystyrenes 63v E12 10pf to 10n 3p, zeners 400mW E24 2v7 to 33v 7p.
TV GAMES send s.a.e. for data, AY-3 8500 + kit £8-95, AY-3 8600 + kit £12-50, Wipe out chip + kit £17-90, Stunt cycle chip £6-90, kit £4, Rifle kit £4-95, Road race chip + kit £17-90.
TRANSFORMERS 6-0-6v 100ma 74p, 1 1/2 £2-35, 6-3v 1 1/2 £1-89, 9-0-9v 75ma 74p, 1a £2, 2a £2-60, 12-0-12v 100ma 90p, 1a £2-45.
IC AUDIO AMPS with pcb JC12 6W £1-60, JC20 £2-95, JC40 20W £2-95.
BATTERY ELIMINATORS 3-way type 6/7 1/2/9v 300ma £2-95, 100ma radio type with press-studs 9v £3-35, 9+9v £4-50, stabilized type 3/6/7 1/2/9v 400ma £5-30, 12v car converters 3/4 1/2/6/7 1/2/9v 800ma £2-50.
BATTERY ELIMINATOR KITS send s.a.e. for data. 100ma radio types with press-studs 4 1/2v £1-40, 6v £1-40, 9v £1-40, 4 1/2+4 1/2v £1-80, 6+6v £1-80, 9+9v £1-80, stabilized 8-way types 3/4 1/2/6/7 1/2/9v 100ma £2-80, 1amp £6-40, stabilized power kits 2-18v 100ma £3-60, 2-30v 1A £6-95, 2-30v 2a £10-95, 12v car converter 6/7 1/2/9v 1a £1-35.
T-DEC AND CSC BREADBOARDS s-dec £3-17, t-dec £4-02, u-dec £4-40, u-dec £5-73, 16 all adaptor £2-14, exp300 £6-21, exp350 £3-40, exp650 £3-89, exp45 £2-48.
BI-PAK AUDIO MODULES s450 £23-51, AL60 £4-86, pa100 £15-58, spm80 £4-47, bmt80 £5-95, stereo 30 £20-12.
SWANLEY ELECTRONICS (Dept. PW)
 32 Goldsel Rd., Swanley, Kent.
 Post 30p extra, prices include VAT.

HAVE YOU DONE IT LATELY!

Fit a new tape head and transform the performance of your tape recorder

MONOLITH

THE MONOLITH ELECTRONICS CO LTD

Regd No. 1016768.

QUALITY REEL TO REEL AND CASSETTE TAPE HEADS



Full Catalogue 25p


Please enclose 20p P&P with order

B24-RP stereo cassette glass/ferrite record/playback £9.84
 B12-01 mono cass. playbk. £1.60 B24-Q1 stereo cass. playbk. £2.80
 A28-05 stereo 8tk cartridge £1.80 E12-09 stereo/mono cass. erase £1.80

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321

From Science of Cambridge: the new MK 14. Simplest, most advanced, most flexible microcomputer – in kit form.

**only
£39.95
(+8% VAT)**

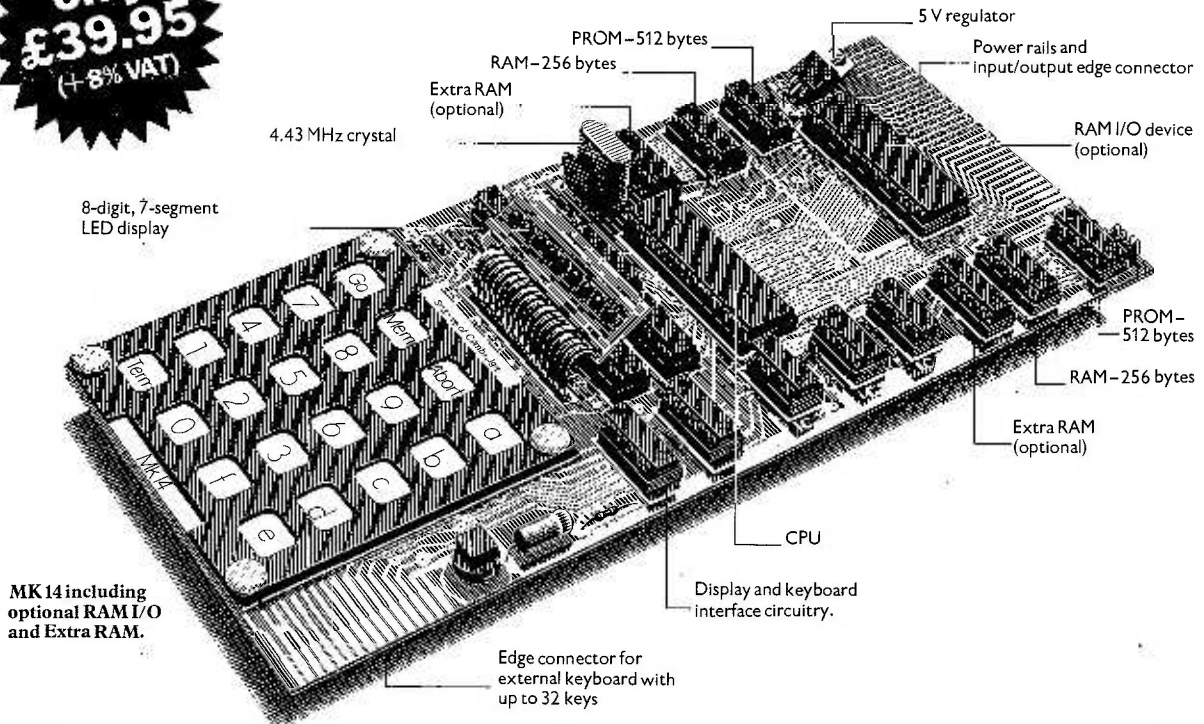

MK 14 including optional RAM I/O and Extra RAM.

The MK 14 is a complete microcomputer with a keyboard, a display, 8 x 512-byte pre-programmed PROMs, and a 256-byte RAM programmable through the keyboard.

As such the MK 14 can handle dozens of user-written programs through the hexadecimal keyboard.

Yet in kit form, the MK 14 costs only £39.95 (+£3.20 VAT, and p&p).

More memory – and peripherals!

Optional extras include:

1. Extra RAM – 256 bytes.
2. 16-line RAM I/O device (allowed for on the PCB) giving further 128 bytes of RAM.
3. Low-cost cassette interface module – which means you can use ordinary tape cassettes/recorder for storage of data and programs.
4. Revised monitor, to get the most from the cassette interface module. It consists of 2 replacement PROMs, pre-programmed with sub-routines for the interface, offset calculations and single step, and single-operation data entry.
5. PROM programmer and blank PROMs to set up your own pre-programmed dedicated applications.

All are available now to owners of MK 14.

A valuable tool – and a training aid

As a computer, it handles operations of all types – from complex games to digital alarm clock functioning, from basic maths to a pulse delay chain. Programs are in the Manual, together with instructions for creating your own genuinely valuable programs. And, of course, it's a superb education and training aid – providing an ideal introduction to computer technology.

SPECIFICATIONS

- Hexadecimal keyboard ● 8-digit, 7-segment LED display ● 8 x 512 PROM, containing monitor program and interface instructions
- 256 bytes of RAM ● 4 MHz crystal ● 5 V regulator ● Single 8 V power supply ● Space available for extra 256-byte RAM and 16 port I/O ● Edge connector access to all data lines and I/O ports

Free Manual

Every MK 14 kit includes a Manual which deals with procedures from soldering techniques to interfacing with complex external equipment. It includes 20 sample programs including math routines (square root, etc), digital alarm clock, single-step, music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

Designed for fast, easy assembly

The MK 14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

How to get your MK 14

Getting your MK 14 kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK 14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,
6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me the following, plus details of other peripherals:

MK 14 Standard Microcomputer Kit @ £43.55 (inc 40p p&p.)

Extra RAM @ £3.88 (inc p&p.)

RAM I/O device @ £8.42 (inc p&p.)

I enclose cheque/money order/PO for £..... (indicate total amount.)

Name _____

Address (please print) _____


Allow 21 days for delivery.

Science of Cambridge


TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

STEREO PRE-AMPLIFIERS

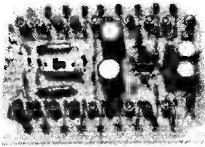

MC 1

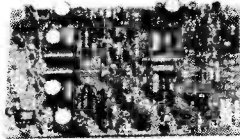

CPR 1

CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < 0.05% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 85dB; slew-rate 3V/uS; T.H.D. 20Hz-20kHz < 0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ± 15 volts.

MC 1—PRE-PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170uV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/uS; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER AMPLIFIER KIT

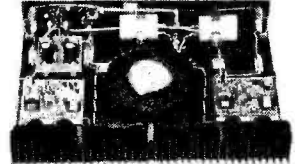The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



POWER AMPLIFIER MODULES

CE 608 50W/8 ohms 35-0-35v £16.30
 CE 1004 100W/4 ohms 35-0-35v £19.22
 CE 1008 100W/8 ohms 45-0-45v £23.22
 CE 1704 170W/4 ohms 45-0-45v £29.12
 CE 1708 170W/8 ohms 60-0-60v £31.90

TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £14.47
 CPS2 for 2 x CE 1004 or 2/4 x CE 608 £16.82
 CPS3 for 2 x CE 1008 or 1 x CE 1704 £17.66
 CPS4 for 1 x CE 1008 £15.31
 CPS5 for 1 x CE 1708 £22.68
 CPS6 for 2 x CE 1704 or 2 x CE 1708 £23.98

HEATSINKS

Light duty, 50mm, 2°C/W £1.30
 Medium power, 100mm, 1.4°C/W £2.20
 Disco/group, 150mm, 1.1°C/W £2.85
 Fan, 80mm, static 120 or 240v £18.50
 Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max. with two 170W modules £29.16
 THERMAL CUT-OUT, 70°C.. £1.90

POWER AMP KIT

..... £32.40

PRE-AMPS:

These are available in two versions—one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.
 CPR1 £29.49
 CPRIS ... £39.98
 MCI £18.50
 MCIS £29.50

POWER SUPPLY

REG1 £6.75
 TR6 £1.75

BRIDGE DRIVER, BDI

Obtain up to 340W using 2 x 170W amps and this module BDI £5.40

CRIMSON ELEKTRIK

1A STAMFORD STREET,
 LEICESTER. LE1 6NL

Tel: (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

Distributor—

"MINIC TELEPRODUKTER
 BOX 12035: S-750 12
 UPPSALA 12, SWEDEN"

A Guide to Amateur Radio


PAT HAWKER G3VA 17th Edition

A Guide to Amateur Radio will assist the newcomer to learn about the hobby and help him to obtain a transmitting licence. It includes information on the new RAE and there is a selection of 'sample' questions. It also provides a valuable reference source for information on amateur receivers and transmitters as well as providing details of home-built equipment and new data on recent trends in equipment and simple multi-band aeriels. The whole range of amateur equipment is covered — test gear, fixed, mobile and portable stations and constructional details are given on h.f. receivers and transmitters. This new edition will be indispensable to all who want to know about amateur radio and forms a valuable introduction to a hobby which knows no boundaries.

0 408 00385 5
 £4.95 approx. US \$11.25 approx.



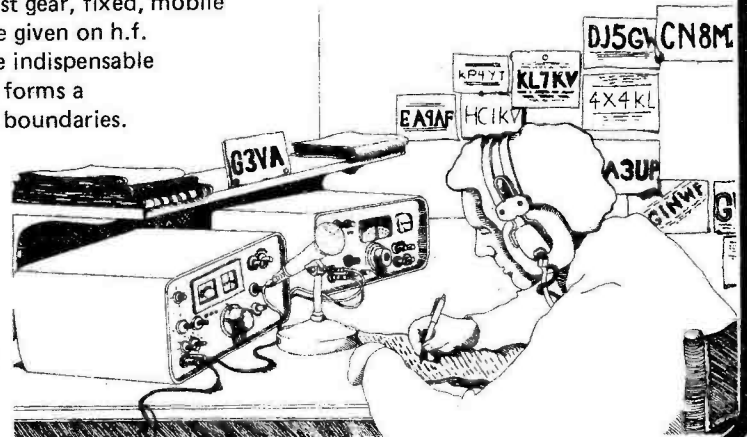NEWNES-BUTTERWORTHS
 Borough Green, Sevenoaks,
 Kent TN15 8PH



Sonic

HI-FI DISCOUNT CENTRES



DISCOUNT SPEAKERS

Imp 8 or 15 as app.
Guarantees:
TITAN 5 years
FANE LIFETIME
OTHERS 1 year
ALL PRICES INC. VAT

Prices correct at 7.12.78

HI-FI TYPES

	List/Value	Sonic Price
5" FANE 501 Mid or Full range	Sp. Price	£4.95
8" A.F. Model 80 Dual Cone	Sp. Price	£4.95
8" A.F. Model 83 Dual Cone	Sp. Price	£3.95
FANE 8" 80BT Dual Cone	Sp. Price	£3.95
WH'FEDEALE LTON 3xP kit Pr.	£60.70	£43.95
10" DENTON 2xP KIT Pair	£39.15	£26.95
10" GLENDALE 3xP KIT	£82.44	£58.95
A.F. FRI 8" SPKR KIT	Sp. Price Pair	£14.95
8" FANE MODE ON KIT	Sp. Price Pair	£19.95
10" ELAC Model 10RM 10-15w	Sp. Price	£2.50

CABINETS (TEAK VENEERED)

20" x 11 1/2" x 9 1/2" Suitable for Model 1 or FRI Kits and Models 80, 83 or 80BT Spkrs.

Limited Number £6.95 ea.

GROUP/DISCO TYPES

12" TITAN T12/45R	£15.00	£12.95
12" TITAN T12/60R	£22.50	£14.95
12" TITAN T12/100A 100w	£36.00	£22.95
12" CELESTION G12M	£16.50	£11.95
12" CELESTION G12H 30w	£22.00	£14.95
12" CELESTION G12/50w	£25.75	£18.95
12" GOODMANS 12 PD	Sp. Price	£21.95
12" GOODMANS 12 PG	Sp. Price	£18.95
12" FANE 'SPECIALIST' P.A. 80	£29.95	£18.95
12" " DISCO 80	£29.95	£19.95
12" " DISCO 100	£31.95	£21.95
12" " GUITAR 80L	£29.95	£19.95
12" " GUITAR 100L	£31.95	£19.95
12" " GUITAR 80B	£29.95	£19.95
12" FANE CRESCENDO 80	£44.95	£29.95
12" " 80LT	£49.95	£34.95
12" " 12A	£64.45	£41.95
12" " 12L	£67.67	£39.95
12" " 12 BASS	£63.95	£39.95
15" TITAN T15/60 60w	£26.00	£17.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£29.95
15" FANE 'SPECIALIST' BASS 85	£41.95	£29.95
15" " BASS 100	£44.50	£31.50
15" GOODMANS 15P	Sp. Price	£23.95
15" FANE CRESCENDO/15	£82.66	£51.95
15" " BASS	£85.95	£51.95
15" " 15/100LT	£74.65	£51.95
15" " 15/160 160w	£107.23	£72.95
15" " COLLOSSUS 20W	£121.91	£72.95
18" TITAN T18/100 100w	£51.00	£39.95
18" GOODMANS 18P	Sp. Price	£39.95
18" CELESTION G18B	£53.00	£41.95
18" FANE CRESCENDO 18A	£114.97	£72.95
18" " BASS	£101.86	£59.95
18" " COLLOSSUS' 200w	£129.81	£75.00

PLEASE STATE IMPEDANCE.

HORN UNITS

	(Carr. 85p)	£13.75
CELESTION MH1000 25w	£17.00	£10.95
FANE 910 MK II 50w	£17.75	£10.95
" 920 100w	£20.95	£12.95
" J44 30-50w	£7.95	£4.95
" J73 50w	£11.75	£7.95
" J104 50-70w	£16.95	£10.95

HIGH POWER 'CROSS-OVERS'

FANE HPx1R or HPx2R Carr. 35p	£3.65	£2.25
-------------------------------	-------	-------

ADD-ON HIGH FREQUENCY UNITS

F.A.L. Add-on Carr. £1	£41.95	£35.95
TITAN T1H 70w Carr. £1	£33.00	£23.95
TITAN TS2H 100w Carr. £1	£33.00	£23.95
TITAN T2H Carr. £1	£39.00	£26.95

EXTRA SPECIAL MAIL ORDER OFFER

TITAN TA/50A 50w AMPLIFIER



High sensitivity
Multi purpose
three m.
controlled inputs.
Controls Bass.
Treble presence.

Robust, well styled compact cabinet, Black Vynide covered. Attractive Black/Silver Fascia £39.95
12 months Guarantee. Carr. £1

Also for personal shoppers only

AMPS, TTABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, CREDIT TERMS AVAILABLE orders £20 over

Phone orders accepted from Access & Barclay card holders.


403 SAUCIEHALL STREET
Tel: 041 332 0700

GLASGOW

Mail Orders/Export enquiries only... to 24 Newgate Shopping Centre, NEWCASTLE. Add £1 carr. on Hi-Fi spkrs. or kits. Otherwise add £1.25 (12" Spkr), £1.50 (15") £2.50 (18")

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

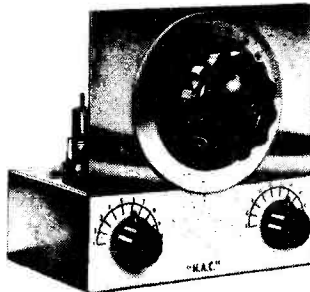

'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories to suit the novice and the expert.

£10.50 INCLUSIVE—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

NEW T TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £12.50 this receiver is outstanding value, and will give you hours of interest and entertainment.

Lastly the K and K plus (illustrated above) for the more advanced constructor. This receiver has recently been re-designed for even better reception. All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.

6-3V 1-5A £2.45; 3A £3.00; 6A CT £5.30; 12V 1.5A

£3.00; 3A CT £5.30; 6A CT £6.85; 15V 0.5A £2.50; 18V

1.5A CT £5.30; 24V 1.5A CT £5.30; 3A CT £5.85; 5A

CT £14.00; 8A CT £23.00; 12A CT £30.00; 40V 3A CT £10.00

TWIN SEC TRANSFORMERS: Prim 240V ac.

6V 0.6A + 6V 0.6A; 9V 0.4A + 9V 0.4A; 12V 0.25A +

12V 0.25A; 20V 0.15A + 20V 0.15A; all at £3.50 each; 15V

0.75A + 15V 0.75A £4.85; 15V 1.5A + 15V 1.5A £7.00;

18V 1A + 18V 1A £5.50; 18V 1.5A + 18V 1.5A £7.50;

20V 1.5A + 20V 1.5A £7.50; 12V 4A + 12V 4A £8.50;

25V 2A + 25V 2A £8.50.

MIDGET RECTIFIER TRANSFORMERS: 240v ac.

6-0-6V 1.5A or 9-0-9V 1A £2.50 each; 12-0-12V 1A or

20-0-20V 0.75A £3.00 each; 9-0-9V 0.3A or 12-0-12V

0.25A or 20-0-20V 0.15A £2.50 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.

0-10-12-14-16-18V 2A £3.00; 4A £7.00; 0-12-15-20-24-30V

2A £5.75; 4A £9.00; 0-5-20-30-60V 1A £7.00; 2A £8.50;

0-40-50-60-80-100-110V 1A £210.00.

MAINS TRANSFORMERS SPECIAL OFFER:

Prim 240V ac.

250-0-250V 60Ma 6-3V 1A £1.75; 250V 100Ma 6-3V 2A

£2.50; 9V 3A £2.50; 20V Auto. 110/240V £1.75. 25V .3A

LOUDSPEAKERS £1.00.

2 1/2in 8Ω; 2 1/2in 8 or 25Ω; 2 1/2in 8Ω, 3in 35Ω, 3 1/2in 3,

25 or 80Ω, all at £1.25 each; 5 1/2in 2, 15 or 25Ω;

£1.50; 7 x 4in 3, 8, 16, 25 or 80Ω, £1.75; 8 x 5in 4, 8 or

25Ω, £3.00; 8in 8Ω, £2.50.

"INSTANT" BULK CASSETTE/TAPE ERASER

Instant erasure of cassettes and tape spools, any diameter, demagnetises tape heads, 200/240V ac, £5.50.

POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.

New, British manufacture, smoothed d.c. output 20V

1.5A, plus stabilised output of 15V 100Ma, plus 12V ac

0.5A output, complete with diagram, £3.25.

EDGEWISE LEVEL METER FSD 200µA

Size 19 x 18 x 20mm 800Ω, £1.10.

CHARGING METERS 1 1/2in diameter.

2A or 3A £1.25 each; 5A or 10A £1.50 each.

CHRONOMETER GEARED MOTORS, 240V ac.

Brand new, built in gearbox, 1 or 20 RPH, at £1.20 each.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS

P.P. sec tapped 3-8-15, A-A 6K 30V, £11.50; A-A 3K

50W, £17.00; 100W (Ei31, KT88, etc) £22.00.

G.E.C. MANUFACTURER OF POWER AMPLIFIERS

Covers valve amplifiers 30W to 400W, 75p.

MULTIWAY SCREENED CABLE, PVC COVERED

36 way £1.00; 25 way 75p; 14 way 50p; 8 way 25p; 4 way

20p; 2 way 10p; 1 way 8p; 4 way individually screened

25p per metre, fig 8 twin stereo do screened 15p.

MAINS CABLE

4 way 30p 3A; 3 core mini cable ideal for speakers; inter-

coms; telephones etc; £4.50 100 M.

CONDENSERS

Electrolytic, 400/400V 75p; 2000/30V 30p; 1200/75V; 50p;

2200/40V 40p; 3900/100V £1.25; Paper tubular, W/E,

4/160V, 6/160V, 2/150V, each 25p, 0-1/2000V 30p.

CARRIAGE EXTRA ON ALL ORDERS

ALL PRICES INCLUDE V.A.T.

Callers by appointment only. S.A.E. enquiries, lists

46 Kenilworth Road, Edgware, Middx.

HA8 8YQ. Tel: 01-958 9314

74 Series TTL

7400	0-12	7476	0-25	74161	0-75
7401	0-12	7480	0-50	74162	0-75
7402	0-15	7482	0-73	74163	0-75
7403	0-12	7483	0-60	74164	0-85
7404	0-15	7485	1-05	74165	0-85
7406	0-25	7486	0-30	74166	1-25
7407	0-25	7489	2-45	74167	2-95
7408	0-18	7490	0-34	74173	1-45
7409	0-18	7491	0-75	74174	1-05
7410	0-12	7492	0-45	74175	0-80

7411	0-18	7493	0-45	74176	1-05
7412	0-20	7494	0-90	74177	0-95
7413	0-36	7495	0-55	74180	1-10
7420	0-12	7496	0-55	74181	2-10
7425	0-25	74100	1-35	74182	1-20

7427	0-25	74104	0-45	74185	2-10
7430	0-12	74105	0-45	74190	1-05
7432	0-27	74107	0-35	74191	1-05
7437	0-27	74121	0-30	74192	0-95
7438	0-27	74122	0-40	74193	0-95

7440	0-12	74123	0-52	74194	0-95
7441	0-49	74125	0-45	74195	0-95
7442	0-50	74126	0-55	74196	0-95
7445	0-60	74132	0-65	74197	0-95
7446	0-60	74136	0-75	74198	1-95

7447	0-55	74141	0-60	74199	1-95
7448	0-50	74145	0-70		
7450	0-12	74150	0-90		
7451	0-15	74151	0-55		
7453	0-15	74153	0-65		


7460	0-15	74154	1-05		
7472	0-27	74155	0-70	4000	0-16
7473	0-27	74156	0-70	4001	0-16
7474	0-27	74157	0-65	4002	0-16
7475	0-33	74160	0-70	4007	0-16

				4010	0-45
				4011	0-15
				4012	0-15
				4013	0-36
				4014	0-90
				4015	0-90

				4016	0-40
				4017	0-90
				4018	0-90
				4022	0-90
				4023	0-

RADIO EXCHANGE LIMITED

NEW ELECTRONIC MASTER KIT

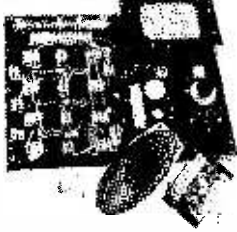

With special V.H.F. Tuner Module to construct. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws, etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeveing, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

Projects:

V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster.

£14.99 + P & P £1.10

V.H.F. AIR CONVERTER KIT




Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome-plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. Size 5½" x 1½" x 3½". All parts including case and plans.

£4.95 + P & P and Ins. 60p

ELECTRONIC CONSTRUCTION KIT E.C.K. 2

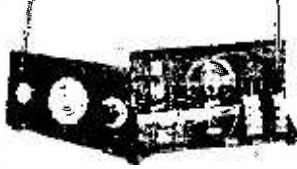

Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 3 in. loudspeaker, gain control, 7 section chrome-plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P.7 battery (not supplied with kit). Complete kit of parts

£7.95 + P & P and Ins. 90p

NEW MODEL R.K.1.



MultiBand A.M. Receiver. M.W.L.W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.

£8.99 + P & P 90p

EDU KIT JUNIOR




Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including Loudspeaker, Earpiece, M.W. Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.95 + P & P and Ins. 90p

NEW ROAMER TEN MODEL R.K.3.

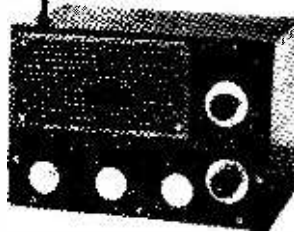

Multiband V.H.F. and A.M. Receiver. 13 Transistors and Six Diodes. Quality 6" x 3" Loudspeaker

With Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain. Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9—9 volt Battery.

Complete kit of parts including carrying strap. Building Instructions and operating Manuals.

£14.79 + P & P £1.10


E.V.6 PLUS ONE



Build this exciting new design. Now with 7 Transistors and 4 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5½in. x 2½in. approx. All parts including Case and Plans.

Total Building Costs: **£6.95 + P & P and Ins. 90p**

EDU-KIT MAJOR

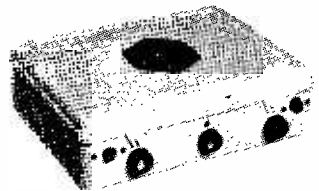

Completely solderless Electronic Construction Kit. Build fifteen projects including:—
● Signal Injector ● Transistor Tester NPN-PNP ● 7 Transistor Loudspeaker Radio MW/LW ● 5 Transistor Short Wave Radio.

Components include:

- 24 Resistors ● 21 Capacitors
 - 10 Transistors ● 5" x 3" Loudspeaker ● Earpiece ● Mica Base-board ● 3 12-way Connectors
 - 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser
 - 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeveing, etc.
- Complete kit of parts including construction plans.

Total building costs:

£9.99 + P & P and Ins. £1.10

RADIO CONSTRUCTION KIT Q7



A compact small radio kit covering Medium Wave and Long Wave bands. Rugged Micanite construction and simple square design allows for easy carrying and positioning. Ideal for the Garage, Workroom, Kitchen, etc., has seven Transistors and four Diodes, quality Loudspeaker, ready wound Ferrite Rod Aerial and Carrying Strap. Size 4½" x 4½" x 4½". All parts and plans including 9v PP7 Battery.

£6.25 + P & P and Ins. 75p

POCKET FIVE



NOW WITH 2½" LOUDSPEAKER 3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans.

Total Building Costs **£4.95 + P & P and Ins. 80p**

To: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 1SA

Tel.: 0234 52367

- Callers side entrance "Lavelis" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

Reg. No. 788372

I enclose £.....for.....

Name

Address

PW379

It's W-W-WINTER S-S

74 SERIES TTL IC'S

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.07	7427	£0.21	7472	£0.19	74107	£0.22	74165	£0.85
7401	£0.09	7428	£0.25	7473	£0.22	74110	£0.35	74166	£0.75
7402	£0.09	7430	£0.08	7474	£0.22	74111	£0.55	74167	£2.00
7403	£0.09	7432	£0.20	7475	£0.27	74118	£0.75	74174	£0.60
7404	£0.09	7433	£0.28	7476	£0.22	74119	£1.10	74175	£0.60
7405	£0.09	7437	£0.20	7480	£0.40	74121	£0.22	74176	£0.55
7406	£0.22	7438	£0.20	7481	£0.80	74122	£0.35	74177	£0.55
7407	£0.22	7440	£0.10	7482	£0.65	74123	£0.38	74180	£0.80
7408	£0.12	7441	£0.45	7483	£0.55	74136	£0.50	74181	£1.25
7409	£0.12	7442	£0.38	7484	£0.42	74141	£0.50	74182	£0.55
7410	£0.09	7443	£0.68	7485	£0.65	74145	£0.54	74184	£1.00
7411	£0.15	7444	£0.68	7486	£0.22	74150	£0.65	74190	£0.68
7412	£0.14	7445	£0.64	7489	£1.60	74151	£0.45	74191	£0.88
7413	£0.22	7446	£0.60	7490	£0.30	74153	£0.45	74192	£0.85
7414	£0.45	7447	£0.45	7491	£0.60	74154	£0.80	74193	£0.50
7416	£0.22	7448	£0.52	7492	£0.32	74155	£0.45	74194	£0.55
7417	£0.22	7450	£0.09	7493	£0.28	74156	£0.48	74195	£0.50
7420	£0.09	7451	£0.09	7494	£0.70	74157	£0.48	74196	£0.60
7421	£0.19	7452	£0.09	7495	£0.45	74160	£0.55	74197	£0.58
7422	£0.19	7453	£0.09	7496	£0.48	74161	£0.60	74198	£1.00
7423	£0.20	7454	£0.09	74100	£0.80	74162	£0.60	74199	£1.00
7425	£0.18	7460	£0.09	74104	£0.35	74163	£0.60	74279	£1.00
7426	£0.21	7470	£0.24	74105	£0.35	74164	£0.65		

CMOS I.C.'S

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.12	CD4017	£0.65	CD4031	£1.60	CD4055	£1.00
CD4001	£0.13	CD4018	£0.70	CD4035	£0.90	CD4056	£1.15
CD4002	£0.13	CD4019	£0.35	CD4037	£0.78	CD4069	£0.15
CD4006	£0.80	CD4020	£0.80	CD4040	£0.78	CD4070	£0.15
CD4007	£0.80	CD4021	£0.75	CD4041	£0.68	CD4071	£0.15
CD4008	£0.80	CD4022	£0.75	CD4042	£0.68	CD4072	£0.15
CD4009	£0.40	CD4023	£0.13	CD4043	£0.78	CD4081	£0.15
CD4010	£0.42	CD4024	£0.55	CD4044	£0.78	CD4082	£0.18
CD4011	£0.13	CD4025	£0.13	CD4045	£1.15	CD4510	£0.80
CD4012	£0.14	CD4026	£1.00	CD4046	£0.95	CD4511	£0.80
CD4013	£0.35	CD4027	£0.75	CD4047	£0.75	CD4516	£0.85
CD4014	£0.70	CD4028	£0.60	CD4049	£0.35	CD4518	£0.85
CD4015	£0.70	CD4029	£0.75	CD4050	£0.35	CD4520	£0.85
CD4016	£0.35	CD4030	£0.40	CD4054	£0.95		

BOOKS BY BABANI

The following books are offered at 10% off their normal retail price

		Normal Price	Sale Price
BP6	Engineers & Machinists Reference Tables	£0.40	£0.36
BP14	Second Book of Transistor Equivalents & Substitutes	£1.10	£0.99
BP22	79 Electronic Novelty Circuits	£0.75	£0.68
BP24	52 Projects using IC's for equivalents	£0.75	£0.68
BP26	Radio Antenna Handbook for Long Distance Reception & Transmission	£0.85	£0.77
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	£0.60	£0.54
BP32	How to Build Your Own Metal & Treasure Locators	£0.85	£0.77
BP34	Practical Repair & Renewal of Colour TVs	£0.95	£0.86
BP35	Handbook of IC Audio Preamplifier & Power amplifier construction	£0.95	£0.86
BP36	50 Circuits using Germanium, Silicon & Zener Diodes	£0.75	£0.68
BP37	50 Projects using Relays SCR's and Triacs	£1.10	£0.99
BP39	50 (FET) Field Effect Transistor Projects	£1.25	£1.13
BP40	Digital IC Equivalents & Pin Connections	£2.50	£2.25
BP41	Linear IC Equivalents & Pin Connections	£2.75	£2.48
BP42	50 Simple LED Circuits	£0.75	£0.68
BP43	How to make Walkie-Talkie	£1.25	£1.13
BP44	IC 555 Timer Projects	£1.45	£1.31
BP45	Projects on Onco-Electronics	£1.25	£1.13
BP46	Radio Circuits using IC's	£1.35	£1.22
BP47	Mobile Discotque Handbook	£1.35	£1.22
BP48	Electronic Projects for Beginners	£1.45	£1.31
BP49	Popular Electronic Projects	£1.35	£1.22
BP50	IC LM3900 Projects	£1.35	£1.22
BP55	Radio Stations Guide	£1.45	£1.31
BP160	Coil Design & Construction Manual	£0.75	£0.68
BP202	Handbook of Integrated Circuits (ICs) Equivalents & Substitutes	£0.75	£0.68
BP205	First Book of Hi-Fi Loudspeaker Enclosures	£0.75	£0.68
BP213	Electronic Circuits for Model Railways	£0.85	£0.77
BP215	Shortwave Circuits & Gear for Experimenters and Radio Hams	£0.85	£0.77
BP216	Electronic Gadgets & Games	£0.85	£0.77
BP217	Solid State Power Supply Handbook	£0.95	£0.86
BP221	28 Tested Transistor Projects	£0.95	£0.86
BP222	Solid State Short Wave Receivers for Beginners	£0.95	£0.86
BP223	50 Projects using IC CA3130	£0.95	£0.86
BP224	50 CMOS IC Projects	£0.95	£0.86
BP225	A Practical Introduction to Digital ICs	£0.95	£0.86
BP226	How to Build Advanced Short Wave Receivers	£1.20	£1.08
BP227	Beginners Guide to Building Electronic Projects	£1.25	£1.13
BP228	Essential Theory for the Electronics Hobbyist	£1.25	£1.13

VPS30 Variable Regulated Stabilised Power Supply Module

Incorporating a short circuit protection and current limiting:
Voltage Regulation 2-30V
Regulated Current 0-2A
AC Input Maximum 25V
Eliminates the use of batteries and thus saves £'s—can be used time and time again.
ONLY £7.60 + V.A.T.

Brand New
ITT 923 Silicon Diodes 200mA 200V
100 off—£2.00
500 off—£3.00
1,000 off—£5.00
10,000 off—£130.00

Single-Sided Fibre Glass Board
12" x 3½" approx. 2 pcs £0.60

THYRISTORS

No. THY1A/50	1 Amp	50 volt	TO5	18p
No. THY1A/400	1 Amp.	400 volt	TO5	32p
No. THY3A/50	3 Amp	50 volt	TO64	25p
No. THY3A/200	3 Amp	200 volt	TO64	32p
No. THY3A/400	3 Amp.	400 volt	TO64	40p
No. THY5A/50	5 Amp	50 volt	TO66	25p
No. THY5A/400	5 Amp.	400 volt	TO66	40p
No. THY5A/600	5 Amp.	600 volt	TO66	50p
No. C106/4	6 Amp.	400 volt	TO220	42p

TRIAC

S84	8 Amp.	400 volt	TO220 Plastic	80p
-----	--------	----------	---------------	-----

DIACS

ITT	V413	equit		12p
BR100	D32	each		12p

CAPACITOR PAKS

16201	18 Electrolytics	4.7µF—10µF		
16202	18 Electrolytics	10µF—100µF		
16203	18 Electrolytics	100µF—880µF		

All 3 at SPECIAL PRICE of £1.20*

16160	24 Ceramic Caps	22pF—82pF		
16161	24 Ceramic Caps	100pF—390pF		
16162	24 Ceramic Caps	470pF—3300		
16163	21 Ceramic Caps	4700pF—0.04µF		

All 4 at SPECIAL PRICE of £1.60*

RESISTOR PAKS

Order No.				
16213	60½W	100 ohm—820 ohm		
16214	60½W	1K—8.2K		
16215	60½W	10K—82K		
16216	60½W	100K—820K		
All 4 at SPECIAL PRICE of £1.60*				
16217	40½W	100 ohm—820 ohm		
16218	40½W	1W—8.2K		
16219	40½W	1K—8.2K		
16220	40½W	100K—820K		
All 4 at SPECIAL PRICE of £1.60*				

VOLTAGE REGULATORS

No. MVR7805	µA7805	TO220	55p	
No. MVR7812	µA7812	TO220	55p	
No. MVR7815	µA7815	TO220	55p	
No. MVR7818	µA7818	TO220	55p	
No. MVR7824	µA7824	TO220	55p	
Negative				
No. MVR7905	µA7905	TO220	75p	
No. MVR7912	µA7912	TO220	75p	
No. MVR7915	µA7915	TO220	75p	
No. MVR7918	µA7918	TO220	75p	
No. MVR7924	µA7924	TO220	75p	
µA723C TO99	38p	72723 14 pin Dtl	38p	
LM309K	TO3	£1.20		

SWITCHES

No. S17	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak	
	4 x Assorted types multi bank and singles	
	Latching and non-Latching	£1.00*

AUDIO LEADS

Order No.			
127	Audio lead 5 pin DIN plug to 4 phono plugs		90p*
129	Audio lead 5 pin plug to 5 pin DIN plug Mirror Image		70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline socket		45p*

AUDIO PLUG AND SOCKET PAKS

Order No.				
S2	5 x 3.5 mm Plastic Jack Plugs			40p*
S3	5 x 2.5 mm Plastic Jack Plugs			40p*
S3	4 x Std. Plastic Jack Plugs			50p*
S4	2 x Stereo Jack Plugs			30p*
S5	5 x 5 Pin 180° DIN Plugs			50p*
S6	8 x 2 Pin Loudspeaker Plugs			50p*
S7	8 x Phono Plugs Plastic			50p*
S8	8 x 3.5 mm Chassis Sockets (Switched)			25p*
S9	8 x 2.5 mm Chassis Sockets (Switched)			25p*
S11	2 x Stereo Jack Sockets with instruction leaflet for Hi/Phone connection			50p*
S12	5 x 5 Pin 180° DIN Chassis Sockets			40p*
S13	8 x 2 Pin DIN Chassis Sockets			50p*
S14	6 x Single Phono Sockets			40p*

P.C. BOARD

S110	Mixed Bundle. P.C.B., Fibre-glass/paper, single and double-sided. Fantastic value.			75p
------	--	--	--	-----

SPECIAL OFFER! UNTESTED

SEMICONDUCTOR PAKS

Code No's shown below are given as a guide to the type of device. The devices themselves are normally unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40p
No. 16131	150 Germ. Point contact diodes like OA70/81	40p
No. 16132	100 200mA Sil. diodes like OA200	40p
No. 16133	150 75mA Sil. Fast switching diode like 1N4148	40p
No. 16134	50 750mA Sil. top hat Rects. like OA70/81	40p
No. 16135	20.3 amp Sil. stud Rect.	40p
No. 16136	50 400mw Zeners D.O 7 case	40p
No. 16137	30 NPN Plastic trans. like BC107/8	40p*
No. 16138	30 PNP Plastic trans like BC177/8	40p*
No. 16139	25 PNP trans. like 2N897/2N1711 TO39	40p
No. 16140	25 PNP trans. like 2N2905 TO39	40p
No. 16141	30 NPN trans. like 2N706 TO18	40p
No. 16143	30 NPN Plastic trans. like 2N3906	40p*
No. 16144	30 PNP Plastic trans. like 2N3905	40p*
No. 16145	30 PNP Germ. trans. like OC71	40p
No. 16147	10 NPN TO3 Power trans. like 2N3055	80p

I.C. SOCKET PAKS

No. S66	11 x 8pin DIL Sockets	£1.00
No. S67	10 x 8 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 20 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

MAMMOTH I.C. PAK

Approx. 200 Pieces. Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked—you to identify

Order No. 16223 £1.00


MATCHED PAIRS OF PNP GERMANIUM MED. POWER TRANS

VCE	VCB	HFE	750mV	
NKT301	40	60	30-100	35p per pair
NKT302	40	60	50-150	35p per pair
NKT303	20	30	30-100	25p per pair
NKT304	20	30	50-150	25p per pair

From U.S.A. by

DINDY

SCREW CASED
LOW NOISE
CASSETTES

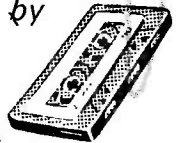

Order No. S53 10 for £3.50 C90

HEAD-CLEANING CASSETTE 45p each

RETURN OF THE AL20A.
By popular demand—this useful 5W RMS power amplifier is offered at the re-introduitory price of

SALE T-T-TIME again!

SPECIAL OFFER! COMPONENT PAKS

Order No.	Quantity	Price
16188	5 pieces Assorted Ferrite rods	40p
16189	2 pieces Tuning gangs MW/LW	40p
16170	50 meters Single strand wire assorted wire	40p
16171	10 Reed switches	40p
16172	3 Micro switches	40p
16176	20 Assorted electrolytics	40p
16177	1 pack Assorted Hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p
16184	15 Assorted Fuses 100mA 5 amp	40p
16188	60 1/2W resistors mixed values	40p
16187	30 meters stranded wire assorted colours	40p
S100	120 1/2 watt resistors. Pre-formed 1978 Prod. Our mix	60p*
S101	120 1/2 watt resistors. Pre-formed 1978 Prod. Mixed values	60p*
S102	250 1/2 watt resistors Range 100 ohms - 10 meg	£2.00*
S103	220 1/2 watt resistors Range 100 ohms - 10 meg	£2.00*
S104	60 Low ohms 1/2 watt resistors 10 - 100 ohms	60p*
S105	40 Low ohms 1/2 watt resistors 10 - 100 ohms	60p*
S106	25 Mixed wirewound resistors	60p*
S107	20 Tantulum bead caps 0.22 - 100mF. Our mix	£1.00*
S108	High quality electrolytics 10mF - 500mF voltage range 15 50V Our mix. 40 for	£1.00*
16204	C280 Pak Contains 50 metal foil caps	£1.00*

POTENTIOMETERS

Slider 40mm TRAVEL

Order No.	Quantity	Price
S24	6 x 470 Ohm LIN Single	40p*
S24	6 x 1 K LIN Single	40p*
S25	6 x 5 K LIN Single	40p*
16193	6 x 22 K LIN Single	40p*
16196	6 x 47 K LOG Single	40p*
16194	6 x 47 K LIN Single	40p*
S27	6 x 100 K LIN Single	40p*
S28	6 x 100 K LOG Single	40p*
S29	6 x 500 K LOG Single	40p*
S32	6 x 50 K LIN Single	40p*

Slider 60mm TRAVEL

S30	6 x 2.5 K LOG Single	40p*
S34	4 x 5 K LOG Dual	40p*
S36	4 x 100 K LOG Dual	40p*
S37	4 x 4.2 MEG LOG Dual	40p*
S34	6 x 220 K LIN Single	40p*
S95	6 x 100 K LOG Single	40p*
S96	6 x 500 K LIN Single	40p*
S38	Mixed slider pots, various values and sizes. Our mix	only £1.00*
S39	6 x Chrome slider knobs	40p*

WIREWOUND

S90	Wirewound Pots Linear 1 Watt rating Mixed useful values 5 for	£1.00*
-----	---	--------

CARBON TYPES

S91	Car Radio type Dual Switched Pot. P.C. mounting 100 K Lin switched. 2.5 K Lin	each 60p*
-----	---	-----------

DUAL POTS P.C. MOUNTING

6mm Shaft

S92	4 x 100 K Lin	£1.00*
S93	4 x 100 K Log	£1.00*
16173	15 Rotary Pot Assorted	40p*
16186	25 Pre-sets Assorted Values	40p*

ZENER PAKS

No. S55	20 mixed values 400mW Zener diodes 3-10V	£1.00
No. S56	20 mixed values 400mW Zener diodes 11-33V	£1.00
No. S57	10 mixed values 1W Zener diodes 3-10V	£1.00
No. S58	10 mixed values 1W Zener diodes 11-33V	£1.00

SILICON POWER TRANS. N.P.N.

S97	BD371 2 Amp 1.2w. 60Vceo Hfe 40-400. Case TO92 with heat tab 5 for	60p*
S98	2N5293 R.C.A. 36w 4 Amps 75Vceo Hfe 30-120. 5 for	£1.00*

CRYSTAL EAR PIECES

S126	Less plug	£0.20
Plugs for above		
No. 16106	2.5 plastic	£0.09
No. 1697	3.5 plastic	£0.11

Mono Crystal Cartridge		
S127	CP91/15C	£1.00
Special Offer		

Nickel Cadmium Rechargeable Batteries 1-25V		
S128	3500 Cell size = U2	£2.50
S129	900C Cell size = JUI1	£0.90
S130	Complete kit of parts to build nickel cadmium charger	£3.50

Super Save Pak		
S124	6 x 741P	£1.00
S125	5 x 555	£1.00
S138	Surplus/end of manufacturers line/pre-amp. with base, treble, volume control and circuit diagram supplied. ONCE ONLY OFFER	£1.25

S137	20 Assorted Slider Knobs—Chrome/Black	£1.00
S131	2 x 12V Relays plastic case	£0.70
S132	2 x 24V Relays plastic case	£0.80
S133	1 switch bank 5-way incl silver knob	£0.75
S134	2 x Magnets suitable for reed switches	£0.10
S135	1 Veroboard pak 2 pcs 45sq. ins. approx.	£0.80
S136	15 Veroboard pak 2 pcs 60sq. ins. approx.	£1.10
16199	1 Veroboard pak 30sq. ins. approx.	£0.50
16200	15 Veroboard pak 30sq. ins. approx.	£0.50

TOOLS

No. 2011	5 in. wire cutters	£1.55
No. 2012	5 in. long wire pliers	£1.45

SUPER DUPER COMPONENT BOX

Min. 3lb in weight consisting of a fantastic assortment of Electronic Components—Pots, Resistors, Condensers, Switches, Relays, Board—Semiconductors, wire, hardware, etc., etc., etc., . . .

This is a large box and is sent separate to your order*

£2.50 including p. & p.

TRANSFORMERS SALE OFFER

S141	0235 240V primary 0-55V at 2A secondary	£4.50* + £1.00 p. & p.
S142	0349 240V primary 0-20V at 2A secondary	£3.50* + £0.86 p. & p.

COMPLETE AMPLIFIER KITS:

STA 15	15 watts per channel amplifier kit Consists: 2 x AL80, 1 x PA100, 1 x SPM80, 1 x 2334, transformer, 2 x coupling capacitors. £37.76 inc. VAT. 85p P&P.	
STA25	25 watts per channel amplifier kit Consists: 2 x AL80, 1 x PA100, 1 x SPM120/45 - 1 x 2040; transformer: 1 x reservoir capacitor; 2 x coupling capacitors. £41.45 inc. VAT. £1.16 P&P.	
STA35	35 watts per channel amplifier kit Consists: 2 x AL80, 1 x PA100, 1 x SPM120, 1 x 2341; transformer: 1 x reservoir capacitor, 2 x coupling capacitors. £48.45 inc. VAT. £1.16 P&P.	
STA50	50 watts per channel amplifier kit Consists: 2 x AL120, 1 x PA200, 1 x SPM120/65 - 1 x 2041; transformer: 1 x reservoir capacitor, 2 x coupling capacitors. £58.20 inc. VAT. £1.10 P&P.	
STA125	125 watts per channel amplifier kit Consists: 2 x AL250, 1 x PA200, 2 x SPM120/65 - 2 x 2041; transformers: 1 x reservoir capacitor, 2 x coupling capacitors. £72.85 inc. VAT. £1.25 P&P.	

TRANSISTORS BRAND NEW—FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	*9p	TIP32A	34p	2N1613	15p
AC126	14p	BC178	12p	BF195	*9p	TIP32B	35p	2N1711	15p
AC127	16p	BC179	12p	BF196	*12p	TIP32C	36p	2N1893	28p
AC128	16p	BC182	*9p	BF197	*12p	TIP41A	34p	2N2218	15p
AC128K	24p	BC182L	*9p	BF200	25p	TIP41B	35p	2N2218A	18p
AC176	18p	BC183	*9p	BF229	22p	TIP41C	36p	2N2219	15p
AC176K	24p	BC183L	*9p	BF284	19p	TIP42A	36p	2N2219A	18p
AC187	16p	BC184	*9p	BFY50	12p	TIP42B	37p	2N2221	15p
AC187K	26p	BC184L	*9p	BFY51	12p	TIP42C	38p	2N2221A	18p
AC188	16p	BC212	*10p	BFY52	12p	TIP2955	65p	2N2222	15p
AC188K	26p	BC212L	*10p			TIP3055	42p	2N2222A	16p
AD161/162 MP	80p	BC213	*10p	MPSA05	*22p	ZTX107	*6p	2N2369	10p
AF139	30p	BC213L	*10p	MPSA06	*22p	ZTX108	*7p	2N2904	14p
AF239	30p	BC214	*10p	MPSA55	*22p	ZTX109	*7p	2N2904A	15p
BC107	6p	BC214L	*10p	MPSA56	*22p	ZTX300	*7p	2N2905	15p
BC108	6p	BC251	*10p	OC44	12p	ZTX301	*7p	2N2905A	15p
BC109	6p	BCY70	12p	OC45	12p	ZTX302	*9p	2N2906	12p
BC118	*10p	BCY71	12p	OC71	9p	ZTX500	*8p	2N2906A	14p
BC147	*8p	BD115	40p	OC72	12p	ZTX501	*10p	2N2907	12p
BC148	*8p	BD131	*35p	OC81	14p	2N696	10p	2N2926G	13p
BC149	*8p	BD132	*37p			2N697	10p	2N2926V	*7p
BC154	*16p	BF115	17p	TIP29A	35p	2N708	*7p	2N3053	12p
BC157	*9p	BF167	19p	TIP29B	36p	2N708A	8p	2N3055	35p
BC158	*9p	BF173	20p	TIP29C	38p	2N708	8p	2N3702	*7p
BC159	*9p	BF180	25p	TIP30A	36p	2N1302	12p	2N3703	*7p
BC160	*10p	BF181	25p	TIP30B	37p	2N1303	15p	2N3704	*6p
BC170	5p	BF182	25p	TIP30C	38p	2N1304	15p	2N3903	*11p
BC171	*6p	BF183	25p	TIP31A	32p	2N1307	18p	2N3904	*11p
BC172	*6p	BF184	25p	TIP31B	33p	2N1308	22p	2N3905	*11p
BC173	7p	BF185	25p	TIP31C	34p	2N1309	22p	2N3906	*11p

RESISTORS

40 MIXED VALUES 1 watt & 2 watt Resistors no S143 £0.60*

PROGRAMMABLE UNIJUNCTIONS

2N6027 with data £0.24

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	BAX16/		Type		IS44	3p
AAZ13	4p	OA202	5p	BY216	30p	OA85	7p
BA100	6p			BY217	28p	OA90	6p
BA115	5p	BY100	15p	BYZ18	28p	OA91	7p
BA144	5p	BY127	*10p	BYZ19	28p	OA95	7p
BA148	10p	BY210	32p	OA47	5p	IN34	5p
BA173	10p	BY211	32p	OA70	5p	IN60	6p
BAX13/		BY212	32p	OA79	7p	IN914	4p
OA200	5p	BY213	30p	OA81	7p	IN4148	4p

LINEAR I.C.'s

TBA800	*£0.75	µA711	£0.25	µA748	£0.28
TBA810	*£0.85	µA703	£0.20	72558	£0.45
TBA820	*£0.65	741P	£0.18	MC1310P	£1.25
LM380	*£0.80	72741	£0.20	76115	£1.25
LM381	*£1.25	µA741C	£0.20	NE555	£0.20
72709	£0.20	72747	£0.55	SL414A	£1.80
µA709	£0.20	748P	£0.28		

ZN 414 RADIO CHIP 75p*

OPTOELECTRONICS

Displays	707 LED Display	£0.70	LED CLIPS		
No. 1510	747 LED Display	£1.50	No. 1508/125 -125	5 for	£0.12
No. 1511	707 Dual LED Display	£1.55	No. 1508/2 -2	5 for	£0.15
No. 1512	727 Dual LED Display	£1.55	No. S139	Infra Red Detector Fairchild FP100	£0.50

LED's	No. S120 -125 Bright Red	£0.09
No. S121 -2 Bright Red	£0.09	
No. S102 -125 Green	£0.12	
No. S105 -2 Green	£0.09	
No. S103 -125 Yellow	£0.12	
No. S106 -2 Yellow	£0.12	
No. S82	Clear -2 Illuminating Red	£0.10

2nd QUALITY LED PAKS

No. S1507	10 Assorted Colours & Size	£0.75
No. S122	10 x -125 Red	£0.80
No. S123	10 x -2 Red	£0.80

P.O. RELAYS

S85 - 2 Off Post Office relays	40p
--------------------------------	-----

BATTERY HOLDERS

to take 6 x HP7's	
Order No. 202	10p each

EX. G.P.O. MICROSWITCHES

Order No. S51	4 for 50p
---------------	-----------

CABLE CLIPS

S65 - 50 2mm round single pin fixing	30p
--------------------------------------	-----

SPECIAL REDUCTIONS

No. S154	NORP 12	45p each
No. S76	OC771	5 for £1.00
No. S83 5	NIXIE Tubes ITT 5870 ST	£2.00 (including Data)
No. S77	Neon Indicator Lamps 230V A.C. State Colour (Red, Amber and Green.)	25p each

Sorry!

EDITOR Geoffrey C. Arnold
 ASSISTANT EDITOR Dick Ganderton C. Eng., MIERE
 ART EDITOR Peter Metalli
 TECHNICAL EDITOR Ted Parratt, BA
 NEWS & PRODUCTION EDITOR Alan Martin
 TECHNICAL SUB-EDITOR Peter Preston
 TECHNICAL ARTIST Rob Mackie
 ASSISTANT ART EDITOR Keith Woodruff
 SECRETARIAL Sylvia Barrett
 Debbie Chapman

EDITORIAL OFFICES
 Westover House,
 West Quay Road,
 POOLE, Dorset BH15 1JG
 Telephone: Poole 71191

ADVERTISEMENT MANAGER
 Telephone: 01-261 6671 Roy Smith

REPRESENTATIVE
 Telephone: 01-261 6636 Dennis Brough

CLASSIFIED ADVERTISEMENTS
 Telephone: 01-261 5762 Colin R. Brown

MAKE UP & COPY DEPARTMENT
 Telephone: 01-261 6570 Dave Kerindi

ADVERTISEMENT OFFICES
 Kings Reach Tower, Stamford St.,
 London, SE1 9LS
 TELEX: 915748 MAGDIV-G

TO those readers who have suffered delay and disappointment in obtaining their copies of *Practical Wireless* of recent months, we offer our sincere apologies. In some of the more remote parts of the UK, late publication and some hiccups in distribution have combined to produce a particularly trying situation. We hope that these difficulties are now being overcome and that the magazine will be on sale by the specified date each month.

Another disappointment for some of our readers, is being unable to obtain a copy of an issue because every one has been snapped up, and their newsagent just cannot get any more. Worse still is picking up a casual copy of *PW* only to find that an interesting series has been running for some months and they can't get hold of the previous issues. We always do what we can to help someone in this predicament, and have recently increased the number of magazines put aside each month for our back numbers service (see page 1). Unfortunately though, many issues are now completely out of print, and only very limited stocks exist of some others. The table below summarises the situation as we went to press.

	1979	1978	1977	1976	1975	1974
JANUARY	✓		✓			
FEBRUARY	✓	✓			✓	
MARCH		✓		✓		
APRIL			✓		✓	
MAY				✓		✓
JUNE		✓				
JULY						
AUGUST		✓				✓
SEPTEMBER		✓				
OCTOBER		✓			✓	
NOVEMBER		✓				
DECEMBER		✓	✓			

If you want to make sure of getting your copy of *PW* each month, either place a regular order with your newsagent, or take out a subscription—again, see page 1 for details.



Debbie Chapman, Copy Typist

A secretarial course which she completed immediately after her normal schooling at the Purbeck School, Wareham, led Debbie into her first job which, luckily for us, was with *PW*.

She was born in Kenya, where her father was serving in the Army, and most of her life so far has been spent on a "world trip" with her father and the rest of the family. Dad is an instructor with the 3rd Royal Horse Artillery at Bovington Camp, specialising in tanks.

Mum also works for the Army, and Debbie is engaged to a Police Constable—she certainly maintains an interest in uniforms!

Among her other interests, which include swimming and looking after children, she quotes cooking as the most important. Future husband Martin seems to have it made in no uncertain terms—good food and a willing baby sitter while he's out working can't be bad.

Well done Erzsebet

The 1978 Girl Technician Engineer of the year is Mrs Erzsebet Kibble (see News, October 1978): the award was announced by The Secretary of State for Education and Science, The Rt Hon Mrs Shirley Williams, MP, at a meeting of The Institution of Electrical and Electronics Technician Engineers (IEETE) in London on Monday, 4 December.



Erzsebet, aged 25, is an Assistant Test Manager with Thorn-Ericsson Telecommunications (Sales) Ltd. Born in Hungary, Erzsebet is married to an Englishman and lives in Woking, Surrey. She joined her present employers in 1974 and gained the Higher National Certificate in Electrical and Electronic Engineering in 1976.

The Award, accompanied by a cheque for £250 and an inscribed rose bowl, is sponsored by The Caroline Haslett Memorial Trust and the IEETE. Its aim is to focus attention on electrical and electronic engineering as a worthwhile career for women. *IEETE, 2 Savoy Hill, London WC2R OBS. Tel: 01-836 3357*

New catalogues

Barrie Electronics Ltd. inform me that their latest catalogue is available. Although the 32 page catalogue lists a good deal of Barrie's stock, they have many other components, too numerous to list. They also invite readers to contact them if they need assistance with purchasing any difficult items.

The catalogue is obtainable for 15p, from: *Barrie Electronics Ltd., 3 The Minories, London EC3N 1BJ. Tel: 01-488 3316/7/8.*

Suhner Electronics, the UK subsidiary of the Swiss company Huber &

Suhner, have recently issued 2 new catalogues covering just part of the range of connectors they manufacture.

1. High Voltage Connectors; this 16 page catalogue covers 3 different series of coaxial high voltage connectors with 50 ohm nominal impedance and bayonet coupling mechanisms. In all a total of 80 different connectors.

2. RF Connectors Series TNC; this comprehensive 28 page catalogue details Suhner's range of TNC medium-sized coaxial cable connectors.

Copies of these catalogues are available, free of charge, from: *Suhner Electronics Ltd., Telford Road, Bicester, Oxfordshire.*

Three new parts of the Mullard Technical Handbook are now available. They are: RF power devices—Book 1, Part 2—£2.00; Thyristors and triacs—Book 1, Part 5—£1.50; Loudspeakers, television assemblies and modules—Book 3, Part 5—£2.00.

The Mullard Technical Handbook is broken down into twenty-one different parts which can be purchased separately—the prices depend on the contents and include P&P.

The handbooks and a leaflet giving further details is available from: *Central Enquiry Handling Unit, Mullard Ltd., New Road, Mitcham, Surrey CR4 4XY.*

Operation Drake

Radio communications equipment, supplied by companies in the GEC-Marconi Electronics group, will play a big part in Operation Drake—the two year round-the-world voyage by parties of experienced explorers, scientists and 24 young explorers in the 150 ton brigantine *Eye of the Wind*, which left Plymouth on Wednesday, 8 November, to celebrate the 400th anniversary of Sir Francis Drake's circumnavigation of the globe.

Marconi Marine is providing one of its new 400 watt Transocean/Pacific s.s.b. radiotelephones to satisfy the vessel's requirements for m.f. and h.f. communications with shore-stations round the world. This equipment is powered by the vessel's a.c. mains supply.

In case of generator failure on board, Marconi Marine is also supplying a 24V d.c. operated Falcon II, a m.f./h.f. s.s.b. radiotelephone as a back-up set for the main equipment.

When working within 40 miles of the coast, the primary ship-to-shore

communications will be supplied by an Argonaut S v.h.f. radiotelephone.

For emergency purposes Marconi Marine is also to provide a Survivor II survival craft radio equipment.

Communications in the v.h.f./f.m. bands will be provided by three UK/VRC353 transceivers for the overland expeditions.

PW Gillingham

It has come to our notice that readers are having difficulty obtaining the 1.280MHz crystal for the PW Gillingham Short-wave Receiver Frequency Readout, published in the October 1978 issue.

A special arrangement has been made to supply these devices, at an inclusive price of £4.15, from *P. R. Gollege Electronics, Merriott, Somerset TA16 5NS. Tel: (0460) 73718.*

Project Index

A new index of electronic projects has been compiled by M. L. Scaife, Principal Librarian (Technical) of North Tyneside Libraries and Art Department.

The index provides a descriptive guide to over 2500 projects published between 1972 and 1977, in journals such as *Practical Wireless, Practical Electronics, Wireless World* and *Television Magazine*.

The project is not intended as a profit-making venture, as the following inclusive prices indicate: 1-2 copies—£1.50, 3-6 copies—£1.40, 7-10 copies—£1.35, over 10 copies—special rates.

Copies of the index are obtainable from: *M. L. Scaife, Central Library, Northumberland Square, North Shields, Tyne and Wear NE30 1QU. Tel: (08945) 82811.*



QSO? GB2RN

The amateur radio station aboard *HMS Belfast* moored in the pool of London, between Tower Bridge and London Bridge, has been granted the use of the special callsign GB2RN when the ship is open to the public. Summer hours 1100 to 1800, winter hours 1100 to 1630, all British local time.

The station is interested in establishing schedules with other museum and special interest stations worldwide, these and other stations who would like to arrange skeds, please contact *Don Walmsley G3HZL*, 153 Worple Road, Isleworth, Middlesex TW7 7HT, England.

All h.f. bands from 1.8 to 28MHz are covered on c.w. or s.s.b.; it is hoped to have RTTY in the near future.

G4HMS will be operational outside of the stated hours.

LCDs

Two liquid crystal displays (l.c.d.s) will be available from Mullard in quantity early in the year. These devices join the Company's already established ranges of solid-state and plasma display devices. This announcement is the result of a long-term development programme which not only involved investigation into different techniques but also into basic materials in order to ensure that the displays would give continuing high-standard performance coupled with assured long-term reliability.

The technology selected for the Company's l.c.d.s was field-effect twisted-nematic. This technology has been in the market place for some time, but the Mullard l.c.d.s will incorporate the latest developments in this field. In particular, nematic liquid crystal materials have been developed to provide high standards of chemical stability and special precautions have been taken to eliminate chemical reaction between the different materials used. Also, to ensure satisfactory viewing, the l.c.d.s incorporate the results of a great deal of research into viewing angles, colour balance and the brightness ratio of the character to the background areas.

Many different types of l.c.d.s are in use today in watches, clocks, calculators and a great deal of instrumentation where their low power consumption, compared to that of l.e.d.s, enable them to be driven

directly by m.o.s. devices.

The Mullard l.c.d.s were designed specifically for time displays and provide a 4-digit read-out with a colon between the second and third digits. Each digit is 12mm high and is formed from 7 segments. The first of these l.c.d.s, type LTC001R, is designed for use in the reflective mode: that is, it collects ambient light and reflects it back to the viewer. The second l.c.d., type LTC001T, is used in the transmission mode with a light source behind the display.

Mullard Limited, Mullard House, Torrington Place, London WC1E 7HD.

GB3WM

The Home Office have granted the special callsign GB3WM to the Wireless Museum at Arretton Manor, near Newport, Isle of Wight. Arretton Manor is the home of The Count and Countess Slade de Pomeroy, the Manor is open daily from Easter until November, and also by appointment during the winter months.

The Wireless Museum contains a unique collection of very early radio and television receivers, including a 30-line Baird Televisor with spinning-disc mechanical scanning.

It is now planned to build an exhibition short-wave experimental transmitting station, as used by radio amateurs before the last war, and display it side-by-side with a modern piece of equipment, showing a direct comparison between the old type of rack-mounted equipment and today's "state of the art".

All amateur bands will be used, with both c.w. and s.s.b. on the high frequencies and f.m. on two-metres (via GB3SN, the Alton, Hampshire repeater).

Official station operators will be Messrs. D. Byrne G3KPO (Museum Curator), A. R. Williams G3KSU, D. E. Denny G3ZQE, A. Wakeley G3MAD, R. W. Fisher G2DZN, K. B. Pearce G3MLC, F. D. Cawley G2GM, H. Childs G3IOW, L. Critchley G3EEL, D. Hoult G400 and W. Carter G2NJ.

A special QSL card will be printed and issued to all initial QSOs. Short-wave listeners are also invited to send in report cards, for which QSLs will be exchanged—all via the RSGB Bureau, or on receipt of an s.a.e.

D. Byrne G3KPO, The Wireless Museum, Arretton Manor, near Newport, Isle of Wight.

TIMETRON**TEMPUS**

Until TEMPUS have re-established their business we will be pleased to supply you from the superb range of

QUALITY CASIO PRODUCTS

A well known consumer magazine has published a report on digital watches which supports our opinion that CASIO and SEIKO are probably the best watches in the world, with CASIO offering unbeatable value for money.


NEW CASIO 46CS-27B

Almost certainly the slimmest and most sophisticated alarm/chronograph watch available today. Liquid crystal display of hours, minutes, seconds, day; and with day, date, month and year perpetual calendar.

- Optional 12 hour clock (with am/pm indicators) or 24 hour display.
- 24 hour alarm setting.
- Optional hourly chimes.
- Chronograph measures in units of 1/1000 second to six hours.
- Net, lap and 1st & second place times.
- All stainless steel case only 7.8mm thick.
- Mineral glass face.
- Water res. to 100ft.
- 10 seconds/month RRP £89.95.

£74.95**CASIO CHRONOGRAPH**


45CS-22B Similar functions to the above watch but without the alarm and chime. (RRP £69.95) £54.95. CASIO SPORTS WATCHES. LCD. 6 digits, 1/100 second stopwatch; net, lap and 1st & 2nd place times. Time and calendar display. F-100 Resin case, strap (£29.95) £24.95. 52QS-14B S/S encased, bracelet (£44.95) £34.95).

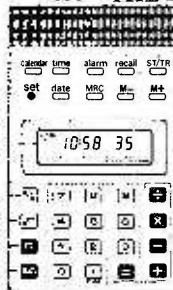NEW CASIO CARD WATCH THE INCREDIBLE MQ-11

Microcomputer Quartz Sensor Touch keys LC Display of hours, minutes, seconds, am/pm, full calendar display of day, date & every Sunday. Also digital date, month, year; and day, Sundays. Three date memories. Two independent alarms with hold & display fac. Countdown alarm/timer, or Time Memory (24hr), or 1/10 sec. stopwatch. Will display any monthly calendar from 1901 to 2099. Memories and displays three optional important dates. Calculator with Sensor Touch keys, full memory, %, .K. Battery life approx. 1 year. * 2 1/2 x 3 1/2 ins. Leatherette wallet with window (£34.95).

An incredible £29.95**NEW CASIO CQ-82**

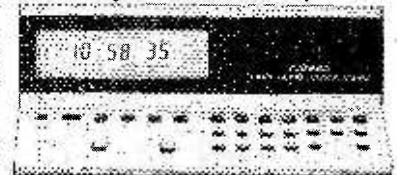LCD calculating alarm clock with snooze facility.



6 digit LC Display of time, with nightlight. Four alarms, one with snooze facility. Calculator with %, .K. Long battery life, compact size (£24.95) **£19.95**

CQ 81 Calculating alarm clock now only **£14.95**

PQ-7 Alarm clock, alarm/timer, stopwatch. Now **£17.95**

NEW CASIO AQ-2000

Calculating alarm clock with stopwatch and calendar **£24.95**
ST-24 Card Time. Calculator, stopwatch, 2 alarm/timers. **£19.95**

NEW

LCD calculators with full memory, %, .K. Most have battery saving APO (Automatic Power-Off).
LC-79 Sensor touch Mini Card with APO. A very rigid 2 1/2 x 3 1/2 ins. Beautifully styled. Pouch **£15.95**.
LC-841 APO. Rigid 4 x 2 1/2 x 4 1/2 ins. Pouch **£15.95**.
NEW HL series. Two AA batteries last 6,000-10,000 hours
HL-801 8 digits **£9.95**. HL-101 (10) **£12.95**. HL-121. **£19.95**.
LCD Scientific Calculators. FX 48 **£19.95**. FX 2500 **£21.95**. FX-3100 **£25.95**. FX 8000 **£29.95**.

Most CASIO products in stock. Send 15p for brochures.

Prices include VAT, P & P. Send cheque, P.O. or phone your Access or B'card number to:—

TIMETRON

Calculators on stock by appointment

Dept. F.W. Basement
Suite 116 167 East Road
Cambridge CB1 1LB
Telephone 0224 675003

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE


LOUDSPEAKER BARGAINS
 3 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 8 x 5in. £2-50. 5in. £1-50.
 6 1/2in. £1-80. 8in. £2-60. 10in. £3. 12in. £4.
 8 ohm. 2 1/2in. £1-50. 3in. £1-50. 5in. £1-50. 10in. £3. 12in. £4.
 16 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 5in. £1-50. 8in. £2-60. 10in.
 £3. 12in. £4.

THE "INSTANT" BULK TAPE ERASER
 Suitable for cassettes, and all sizes of tape reels.
 A.C. mains 200/249V.
 Leaflet S.A.E. **£4-95** Post 50p



HEAD DEMAGNETISER £4-75

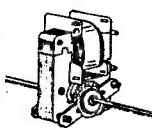A.C. ELECTRIC MOTORS
 2 Pole, 240V. 2 Amp. Spindle — 1.43 x 0.212in. £1-75. 2 pole, 240V. 1.5 Amp. Double spindle — 1.75 x 0.16in. Each £1-50. 2 Pole, 120V. 5 Amp. Spindle — 0.75 x 0.2in. Two in series — 240V. 7.5p each. Brush Motor. From a Food Mixer 240V. 3 Amp. High Speed and Powerful. Spindle — 0.5 x 0.25in. £2-95 each.



BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p; 8 x 6in. £1-40; 10 x 7in. £1-55; 14 x 9in. £1-90; 16 x 6in. £1-85; 12 x 3in. £1-20; 16 x 10in. £2-50; 12 x 8in. £1-70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1-16.

ALUMINIUM ANGLE BRACKET 6 x 1/2 x 1 1/2in. 15p.
ALUMINIUM BOXES, MANY SIZES IN STOCK.
 4 x 2 x 2in. 86p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1; 8 x 6 x 3in. £1-90; 12 x 5 x 3in. £2; 6 x 4 x 4in. £1-30.

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in. With CERAMIC STEREO CARTRIDGE



£17-50
 All Post £1.

BSR Budget Autochanger stereo ceramic cartridge. £14-95
 Garrard 5300. Autochanger with ceramic cartridge. £14-95
 Garrard Minichanger. Plays all size records. Ceramic cartridge. Stereo. £9-95
 BSR. P182. Snake arm, flared Aluminium Turntable Stereo ceramic cartridge. Latest model. £22-50

BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER



Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4.8-16 ohm. Slave output. Guaranteed. **£79** Carr. £1-50 Details S.A.E. A/C mains 120v and 240v.

BAKER 50 Watt AMPLIFIER 2 inputs £59.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Will control up to 480 watts AC mains. Post 35p **£3-25**

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. Post 85p **£2-95**

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watts each. Will operate from 200MV. to 100 watts signal source. Suitable for home use. Cabinet extra £4. **£17**

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4.


MAINS TRANSFORMERS

6 VOLT 3 AMP. £1-00 3 AMP. £1-95 9 VOLT 3 AMP. £2-75 12 VOLT 3 AMP. £1-00 750 MA. £1-30 20 VOLT 2 AMP. £2-50 30 VOLT 5 AMP. AND 34 VOLT 2 AMP. C.T. £3-45 20 VOLT 1 AMP. £2-00 20-0-20 VOLT 1 AMP. £2-95 30 VOLT 1 1/2 AMP. £2-75 40 VOLT 2 AMP. £2-95 30V 2 AMP. £3 0-20-40-60 VOLT 1 AMP. £3-50 2 x 18 VOLT 6 AMP. £9.

GENERAL PURPOSE LOW VOLTAGE. Voltages available at 2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V. £5-80 1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8-50 2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8-50 3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11-00 5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £14-50

R.C.S. TEAK COMPACT SPEAKERS

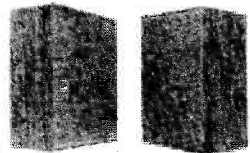13 x 10 x 6in. 50 to 14,000 cps. 12 watts rms. 8 ohms **£19 pair** Post £1-50



BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "35" £14-00
 12in. 40 watt 4.8 or 16 ohms.

GROUP "50/12" £21-00
 12in. 60 watt professional model. 4, 8 or 16 ohms. Response 30 — 16,000 cps. With aluminium presence dome.

GROUP "50/15" £33-00
 15in. 75 watt 8 or 16 ohms.

Send for leaflets on Disco, P.A. and Group Gear.



R.C.S. MINI MODULE HI-FI KIT 15 x 8 1/2 in 3-way Loudspeaker System, EMI 5in, Bass 5in, Middle 5in, Tweeter with 3-way Crossover and Ready Cut Baffle. Full assembly instructions supplied. Response = 60 to 20000cps 12 watt RMS. 8 ohm. £10-95 per kit. Two kits £20. Postage 75p.

E.M.I. 13 1/2 x 8in SPEAKER SALE!
 With tweeter. And crossover. £7-95 10W. State 3 or 8 ohm. Post 45p
15W model £10-50 8 ohms. Post 65p
GOODMANS 20W Woofer £9-95 Size 12 x 10in. 4 ohms. Rubber cone surround. Hi-Fi Bass unit. Post 65p



337 WHITEHORSE ROAD, CROYDON

Open 9—6 Sat. 9—5 (Closed all day Wednesday) Phone your order. Tel. 01-684 1665.

RADIO COMPONENT SPECIALISTS

Minimum post 30p. Components List 20p. Access & Barclay VISA welcome.

CHROMASONIC electronics

your soundest connection in the world of components

Dept PE1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

The items shown in this advert are just a small selection taken from our new 78/79 Catalogue which is now available. It contains everything from Resistors to the latest in Micro-processors. Don't delay order your copy today. The price is only 40p (inc. 45p vouchers).

TELEPHONE: 01-883 3705

Low Power Schottky and TTL CMOS i.c. sockets BITS and PIECES Regulators Linear I.C's

Low Power Schottky and TTL				CMOS				i.c. sockets				BITS and PIECES				Regulators				Linear I.C's														
N	LS	N	LS	N	LS	N	LS	DIL (Texas)	Static RAM's	1+	17-63 64+	78M Series	CA3080	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS					
7400 13*	19*	7449	87*	74136	—	38*	74131 121*	75*	4000 15*	4053 81*	2102A (350ns)	1.05* 95*	88*	7401 13*	19*	7450 16*	—	74138	—	55*	74192 121*	185*	4002 16*	4056 146*	14in 13*	2102A-2 (650ns)	1.29*	1.15*	1.08*	CA3140E	30			
7402 15*	19*	7451 16*	18*	74139	—	55*	74193 121*	185*	4006 92*	4059 518*	2111A-1 (500ns)	2.46*	2.19*	2.05*	7402 15*	19*	7453 16*	—	74141	76*	—	74194 121*	185*	4007 18*	4060 124*	16in 13*	2112A-2 (250ns)	2.14*	1.90*	1.78*	LM301AN	30		
7404 16*	21*	7454	—	19*	74145 75*	1.05*	74195 101*	1.05*	4008 92*	4066 48*	21102 (350ns)	1.07*	96*	7404 16*	21*	7455	—	74146	75*	—	74196 118*	1.25*	4009 12*	4068 21*	22 pin 24*	21102 (350ns)	1.07*	96*	79M Series	LM324N	73			
7405 16*	21*	7456	—	19*	74147 159*	1.05*	74197 118*	1.05*	4010 40*	4069 21*	MM5257 (TMS4044)	8.10*	7.19*	6.75*	7405 16*	21*	7457	—	74148	77*	78*	74198 118*	1.05*	4011 18*	4070 21*	22 pin 24*	2114 (450ns)	8.10*	7.19*	6.75*	LM345N	99		
7406 28*	—	7458	—	19*	74149 102*	—	74199 181*	—	4012 18*	4071 21*	6810	3.50*	2.97*	2.52*	7406 28*	—	7459	—	74149	102*	—	74199 181*	—	4013 18*	4072 21*	28 pin 30*	6810	3.50*	2.97*	2.52*	LM380N	1.73		
7407 28*	—	7470 27*	—	19*	74150 102*	—	74199 181*	—	4012 18*	4071 21*	6810	3.50*	2.97*	2.52*	7407 28*	—	7471 28*	—	74151	87*	88*	74199 181*	—	4013 18*	4072 21*	28 pin 30*	6810	3.50*	2.97*	2.52*	LM382N	1.33		
7408 17*	19*	7472 23*	—	19*	74151 87*	88*	74199 181*	—	4012 18*	4071 21*	6810	3.50*	2.97*	2.52*	7408 17*	19*	7473 23*	—	74152	87*	88*	74199 181*	—	4013 18*	4072 21*	28 pin 30*	6810	3.50*	2.97*	2.52*	LM388N	65		
7409 17*	19*	7473 23*	—	19*	74153 87*	88*	74199 181*	—	4013 18*	4072 21*	6810	3.50*	2.97*	2.52*	7409 17*	19*	7474 23*	—	74154	87*	88*	74199 181*	—	4014 92*	4072 21*	28 pin 30*	6810	3.50*	2.97*	2.52*	LM390N	70*		
7410 15*	19*	7474 23*	—	19*	74154 87*	88*	74199 181*	—	4014 92*	4072 21*	6810	3.50*	2.97*	2.52*	7410 15*	19*	7475 24*	—	74155	87*	78*	74241	—	4015 92*	4072 21*	28 pin 30*	6810	3.50*	2.97*	2.52*	LM390N	70*		
7411 25*	19*	7475 44*	—	19*	74156 87*	78*	74241	—	4015 92*	4072 21*	6810	3.50*	2.97*	2.52*	7411 25*	19*	7476 44*	—	74156	87*	78*	74241	—	4016 43*	4082 21*	14 pin 34*	6810	3.50*	2.97*	2.52*	LM390N	70*		
7412 18*	19*	7476 44*	—	19*	74156 87*	78*	74241	—	4016 43*	4082 21*	6810	3.50*	2.97*	2.52*	7412 18*	19*	7477 44*	—	74157	87*	78*	74241	—	4017 81*	4085 82*	16 pin 37*	1702AD	5.57*	8795P	1.49*	79 Series	SN7600N	2.32	
7413 27*	40*	7478	—	29*	74157 67*	55*	74243	—	4017 81*	4085 82*	6810	3.50*	2.97*	2.52*	7413 27*	40*	7479	—	74158	—	58*	74247	—	4018 92*	4086 82*	16 pin 43*	2708Q	7.87*	8795P	1.49*	79 Series	SN76023N	1.55	
7414 71*	79*	7482 73*	—	19*	74158	—	74247	—	4018 92*	4086 82*	6810	3.50*	2.97*	2.52*	7414 71*	79*	7483	—	74159	—	58*	74247	—	4019 56*	4089 81*	20 pin 55*	TriState Buffers	74365	75*	8795P	1.49*	79 Series	TCA840	1.75
7415	—	7483	—	75*	74160 121*	99*	74248	—	4019 56*	4089 81*	6810	3.50*	2.97*	2.52*	7415	—	7484	—	74161 121*	99*	74248	—	4020 92*	4089 181*	24 pin 60*	81LS95	75*	8795P	1.49*	79 Series	SN76031N	1.55		
7416 25*	—	7485 118*	—	88*	74161 121*	99*	74248	—	4020 92*	4089 181*	6810	3.50*	2.97*	2.52*	7416 25*	—	7486 25*	—	74162 121*	125*	74251	—	4021 92*	4092 82*	28 pin 65*	81LS96	75*	8795P	1.49*	79 Series	TBA81DAS	90		
7417 34*	—	7486 25*	—	29*	74162 121*	125*	74251	—	4021 92*	4092 82*	6810	3.50*	2.97*	2.52*	7417 34*	—	7487 25*	—	74163 121*	125*	74251	—	4022 92*	4092 82*	28 pin 65*	81LS97	75*	8795P	1.49*	79 Series	SN76033N	1.55		
7418 28*	19*	7488 280*	—	74163 121*	125*	74251	—	4022 92*	4092 82*	6810	3.50*	2.97*	2.52*	7418 28*	19*	7489 30*	—	74164 102*	115*	74257	—	4023 18*	4092 82*	28 pin 65*	81LS98	75*	8795P	1.49*	79 Series	TBA81DAS	90			
7419 27*	40*	7478	—	29*	74157 67*	55*	74243	—	4023 18*	4092 82*	6810	3.50*	2.97*	2.52*	7419 27*	40*	7479	—	74165 87*	78*	74258	—	4024 65*	4092 82*	28 pin 65*	81LS99	75*	8795P	1.49*	79 Series	SN76033N	1.55		
7420 18*	19*	7489 30*	—	74163 121*	125*	74251	—	4024 65*	4092 82*	6810	3.50*	2.97*	2.52*	7420 18*	19*	7490 34*	—	74166 102*	115*	74257	—	4025 18*	4092 82*	28 pin 65*	81LS99	75*	8795P	1.49*	79 Series	SN76033N	1.55			
7421	—	7490 34*	—	62*	74168 102*	115*	74257	—	4025 18*	4092 82*	6810	3.50*	2.97*	2.52*	7421	—	7491 34*	—	74169 102*	115*	74257	—	4026 18*	4092 82*	28 pin 65*	81LS99	75*	8795P	1.49*	79 Series	SN76033N	1.55		
7422	—	7491 34*	—	1.05*	74165 87*	78*	74258	—	4026 18*	4092 82*	6810	3.50*	2.97*	2.52*	7422	—	7492 34*	—	74170 185*	1.65*	74279	—	4027 51*	4092 82*	28 pin 65*	81LS99	75*	8795P	1.49*	79 Series	SN76033N	1.55		
7423 25*	—	7492 34*	—	75*	74166 102*	115*	74257	—	4027 51*	4092 82*	6810	3.50*	2.97*	2.52*	7423 25*	—	7493 34*	—	74171 185*	1.65*	74279	—	4028 70*	4092 82*	28 pin 65*	81LS99	75*	8795P	1.49*	79 Series	SN76033N	1.55		
7424 25*	—	7493 34*	—	65*	74168 102*	115*	74257	—	4028 70*	4092 82*	6810	3.50*	2.97*	2.52*	7424 25*	—	7494 34*	—	74172 185*	1.65*	74279	—	4029 118*	4092 82*	28 pin 65*	81LS99	75*	8795P						

So You Want to Pass the RAE?

A reprint of the complete series, including details of the new examination format being introduced in 1979, is now available. The reprint will cost 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:—

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street, London
SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No Value

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME.....
(BLOCK LETTERS)

ADDRESS.....
(BLOCK LETTERS)

.....

.....

.....

..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

Cut round dotted line

Letters

The Editor,
PRACTICAL WIRELESS,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG

Radio 3

Sir: While admiring the ingenuity of the BBC Engineering Department in replacing Radios 1, 2, and 4 transmitters, I must complain about the allocation of 1215kHz for Radio 3. This frequency is only fit for its original purpose—a back-up for l.w. transmissions in big cities. The map on page 41 of 18-24 Nov 1978 issue of *Radio Times* confirms this. The 1215kHz frequency is subject to hideous phase distortion here, and swamped by Radio Albania after 3 pm.

I am primarily concerned with conditions during daylight hours. Most people have v.h.f. at home, although that is difficult in some parts of this town, and v.h.f. car radio is ineffective here.

I am waiting for the howls of protest, when we have the first "Test Match Special" on m.w. only. I have had a long correspondence with the BBC and I am now hopeful that they will, after 23 November, try to improve Radio 3 outlets. Small relays could go on an international common frequency—or even a borrowed one, as at Cambridge (that is not on the Geneva list). What we urgently need is one more frequency to be used by alternative main stations as for Radios 1 and 2. We still have, as yet unused, an allocated frequency of 227kHz, although it may be liable to interference.

It is a scandal that the Home Office did not even ask for extra channels at Geneva (see Richard Last, page 12, *Daily Telegraph*, 13 November 1978). How did small countries like Belgium, Holland and Eire, manage to get new valuable long and medium wave allocations, all more efficient than the 648kHz, which is now lost to us, for the BBC European Service.

I hope that all your readers who enjoy Radio 3, especially in cars, as I have done for years, will make their views known to the BBC as soon as possible. Then, perhaps, some improvements will occur.

Dr H. S. Brodribb
St Leonards-on-Sea

Any offers

Sir: I have for sale approximately 150 copies of various electronic magazines, such as PW, PE, EE and WW. Some of the issues date back to 1946/7, if anyone is interested, I would accept any reasonable offer plus postage.


I also have a quantity of electronic bits and pieces (valves, transistors, transformers, motors etc.), for which all I require is the postage.

Mr. H. C. Leivers
4 Cavendish Place
Gwaun Miskin
Beddau CF38 2RP

THE 'PW' SOUNDLITE

SOUND TO LIGHT UNIT

T. P. Hopkins

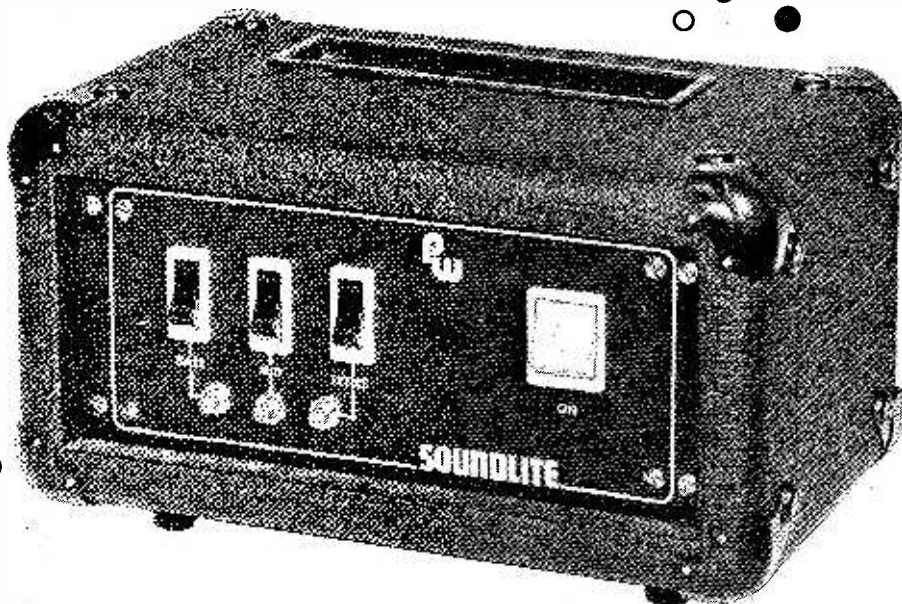

In recent years, Sound-to-Light (STL) units, in various forms, have become extremely popular for discos, pop concerts, parties, shop displays and so on. In its simplest form, a STL unit consists of three or more CR filters fed from the loudspeaker terminals of an audio amplifier, feeding transistors which trigger triacs (or thyristors) via pulse transformers. Each channel has its own level control, and there may be a "master" control as well. This form of STL has several drawbacks; the sensitivity is low (an audio signal of 2-3V may be required) and continual adjustment is required to compensate for changes in volume and tone. The apparent separation between channels is poor, due to the simple filters used: the unit generates interference spikes on the mains, since the triacs may be triggered at any point on the mains cycle, and it uses several heavy and/or expensive transformers.

The STL unit to be described overcomes all of these disadvantages; it uses interference-free "zero-voltage switching", so that the triacs are triggered only when the

voltage across them is very low; it has active filters for excellent separation between channels and automatic gain control (a.g.c.) amplifiers to eliminate manual adjustments; the sensitivity is approximately 700mV to control 1kW of lights per channel, and it uses only one inexpensive transformer. Due to the virtual elimination of transformers, this design is little more expensive to construct than the conventional version described above.

The Circuit

As can be seen from the simplified block diagram (Fig. 1), the circuit comprises several blocks each with a well-defined action. Each block is identified in the circuit diagram (Fig. 2). The signal from the loudspeaker circuit of an audio amplifier is fed via transformer T1. This provides isolation between the amplifier and the remainder of the circuit, which is at **mains line voltage**. Consequently, **extreme caution** is required when constructing the circuit.

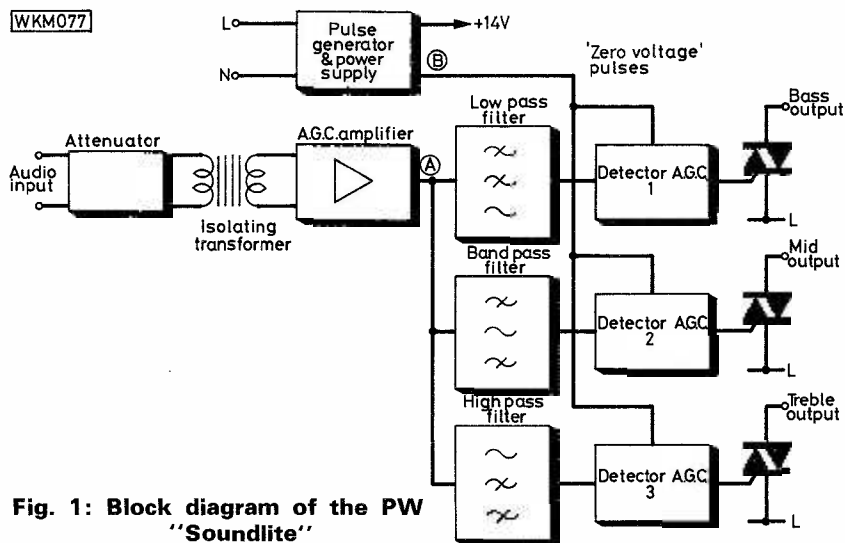


Fig. 1: Block diagram of the PW "Soundlite"

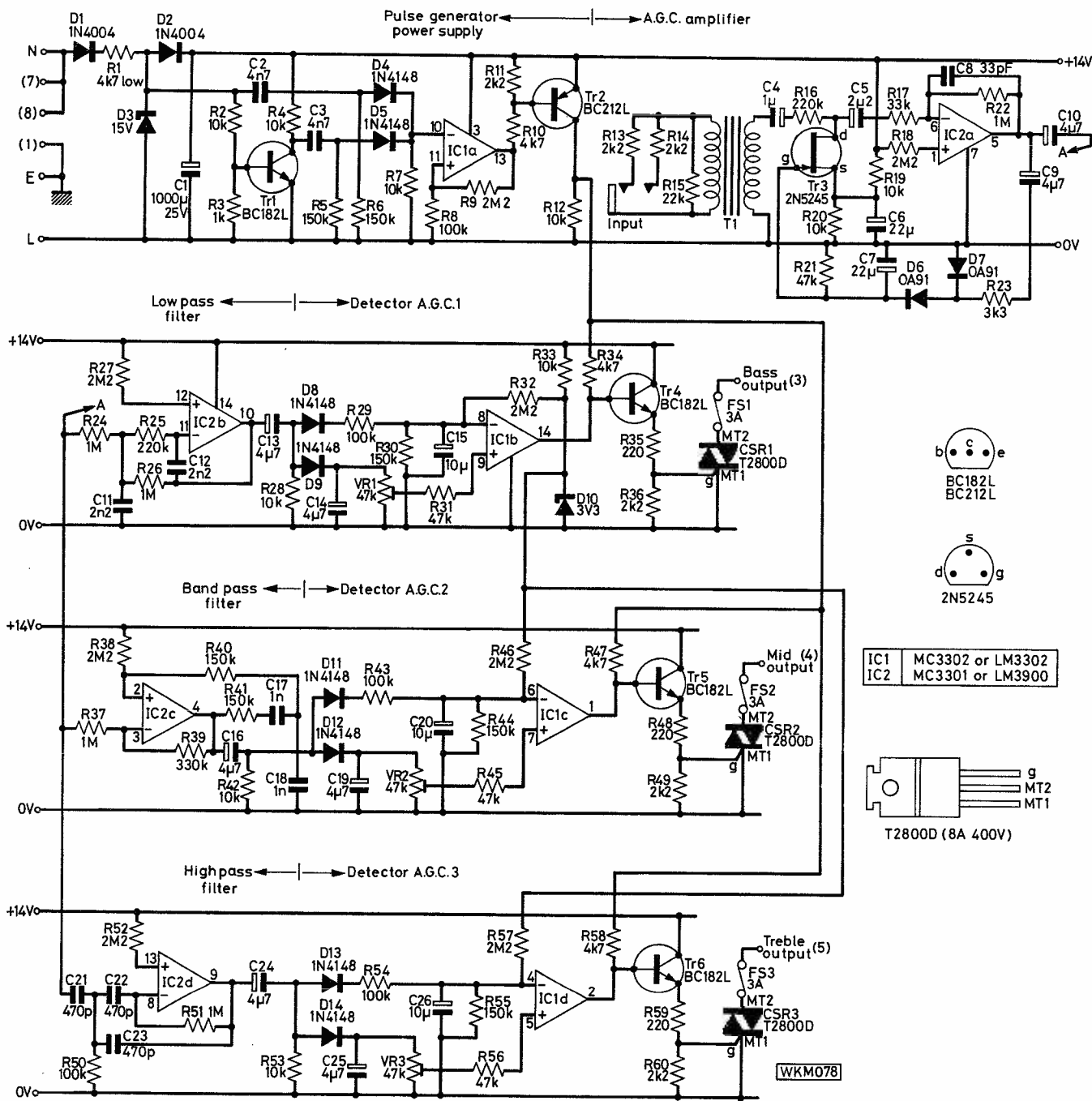


Fig. 2: Complete circuit diagram (excluding options)


Note that T1 is actually a miniature mains transformer, which has good isolation and adequate frequency response for this application. The audio signal then enters an a.g.c. amplifier which allows the STL to operate with inputs from 700mV r.m.s. (0.12W/4Ω to 25V (150W/4Ω). This consists of a voltage controlled attenuator R16/Tr3, followed by a X30 amplifier IC2a, with a control voltage derived from the rectifier circuit D6/D7.

If more sensitivity is required, R13/R14 may be reduced to, say, 1kΩ 1W, but this loads the audio amplifier somewhat more, and increases the possibility of noise affecting the lights. If a high voltage source is used (e.g., 100V lines) R13/R14 should be increased to 15kΩ 1W. Note that a stereo input is provided; if mono only is

required, both inputs should be tied together, alternatively a mono jack plug in the (stereo) jack will work with slightly reduced sensitivity.

After processing in the a.g.c. amplifier, the audio signal is fed to three active filters: low-pass (bass, IC2b), bandpass (midrange, IC2c) and high-pass (treble, IC2d). These have their cut-off frequencies chosen to give subjectively good separation between channels with most types of music from a variety of sources from a portable transistor radio to powerful discotheque systems. The output of each filter is connected to one of three identical detector/a.g.c. circuits constructed around a quad comparator integrated circuit.

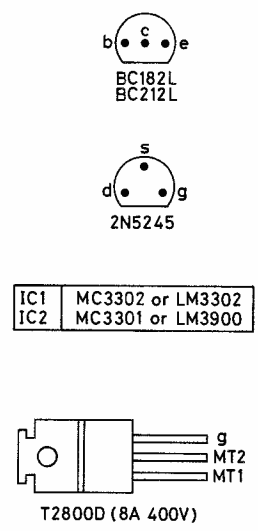For simplicity, consider the circuit connected to the low-pass filter (IC1b). If there is no audio signal, the comparator output will be low due to the bias voltage from D10 and R32, and no trigger pulses will be applied to the



triac. Now, if a steady audio tone is applied, capacitor C14 will rapidly charge via D9 and the comparator output will go high. This allows trigger pulses, timed to coincide with the points in the mains cycle where the voltage is zero, to be applied to the triac. Thus, the triac will turn on when the voltage across it is small and the appropriate lights will come on without any interference being generated. However, C15 slowly charges via D8 and eventually the voltage across it exceeds that on C14. The comparator switches again, turning the lights off. With more complicated dynamics in the audio signal the situation is more complex, but it can be seen that this circuit provides


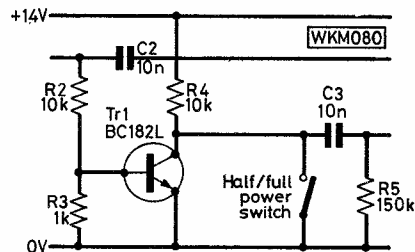
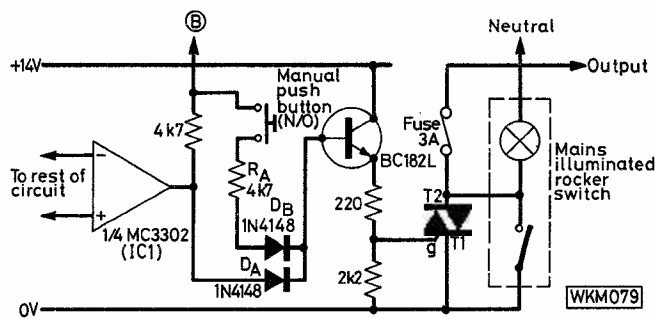


Fig. 3: (a) (top) Addition of push-button and switched override facilities. (b) Half/full power switching

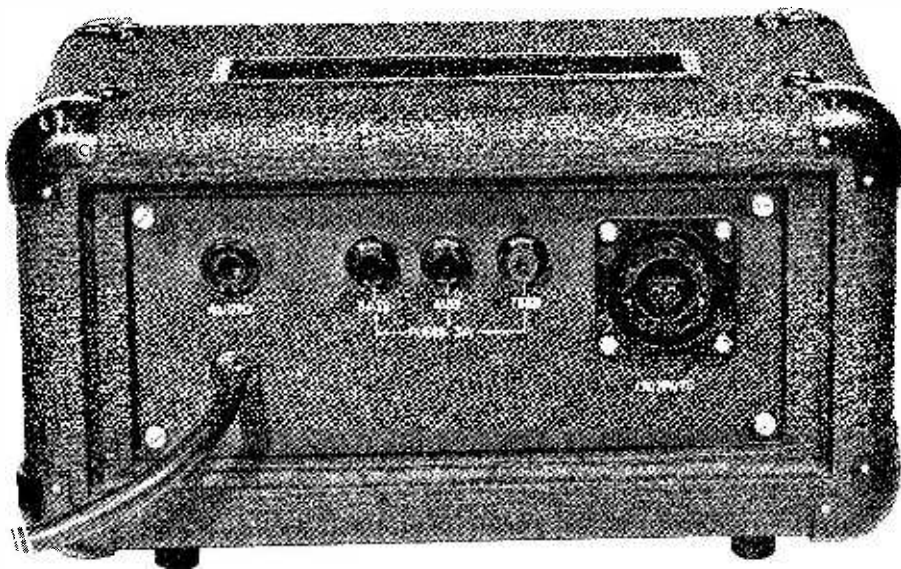

A rear view of the prototype, showing input jack, fuses and eight-way output socket

an a.g.c. type action. The preset VR1 allows adjustment of the operating point of the circuit for optimum operation.

The detector circuits described above are fed with “zero voltage” pulses from the pulse generator circuit Tr1/IC1a. The mains input is clipped by D3, and an inverted squarewave is produced at Tr1 collector. The positive-going edges of both are differentiated by CR networks, and trigger a comparator IC1a providing short positive-going pulses at Tr2 collector. The positive supply for the whole unit is provided by D2 and C1.

Circuit Modifications

The circuit described so far is capable of forming a simple but effective “no frills” STL unit, with no external controls whatsoever! If, like the writer, you prefer more facilities, several additions can be made, some of which are provided for on the printed circuit board described later.

First, a mains on-off switch can be provided—useful for quick changes between lighting effects. Switches can be provided (Fig. 3(a)) to override the triacs on each channel, switching the lights permanently on. If the switches have built-in neon indicators, these can be connected to provide monitoring of the light display. These switches must be capable of carrying the full load current. However, low power switches or push-buttons may be used with a simple diode gate (also shown in Fig. 3(a)), providing fast, noise-free switching. This method is particularly suitable for push-buttons, allowing the lights to be rapidly flashed under manual control. These additions are included in the version described in the constructional details and positions for the extra components required are included on the p.c.b.

Other improvements include the addition of a half/full power switch (Fig. 3(b)). This short-circuits Tr1, so that only half of the differentiated pulses reach the comparator. Thus, the triacs are only triggered on positive half-cycles, so the lights will be less bright. In a similar manner, an audio on/off switch can be added, allowing the override push-buttons to be used alone. This switch short-circuits R15, preventing audio signals from reaching the a.g.c. amplifier.

More ambitious modifications include making presets VR1–VR3 front panel controls (for the “knobs with everything” man!) or even providing controls with a switched “automatic” position. If this is tried, the controls must be well insulated. Also, a sequencer facility can be added, using transistors in place of the push-buttons in Fig. 3(a), or a dimmer control can be added using a 555 oscillator. These modifications are left to the more experienced constructor.

Construction

WARNING: Most of the circuit board and wiring is at MAINS LIVE VOLTAGE and EXTREME CAUTION is necessary when testing or adjusting the circuit. The use of an Epoxy Glass Fibre p.c.b. is strongly recommended; Veroboard, etc., is NOT suitable, as it has insufficient intertrack voltage rating.



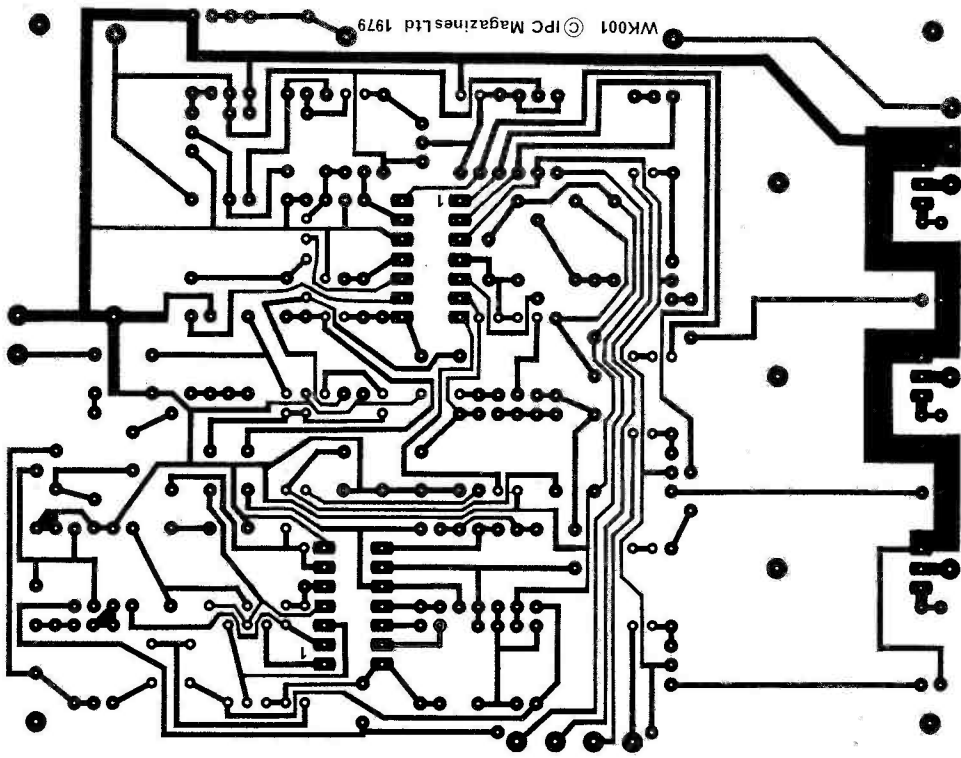


Fig. 4 (above): Printed circuit board track pattern, shown full size.

Fig. 5 (below): Component layout

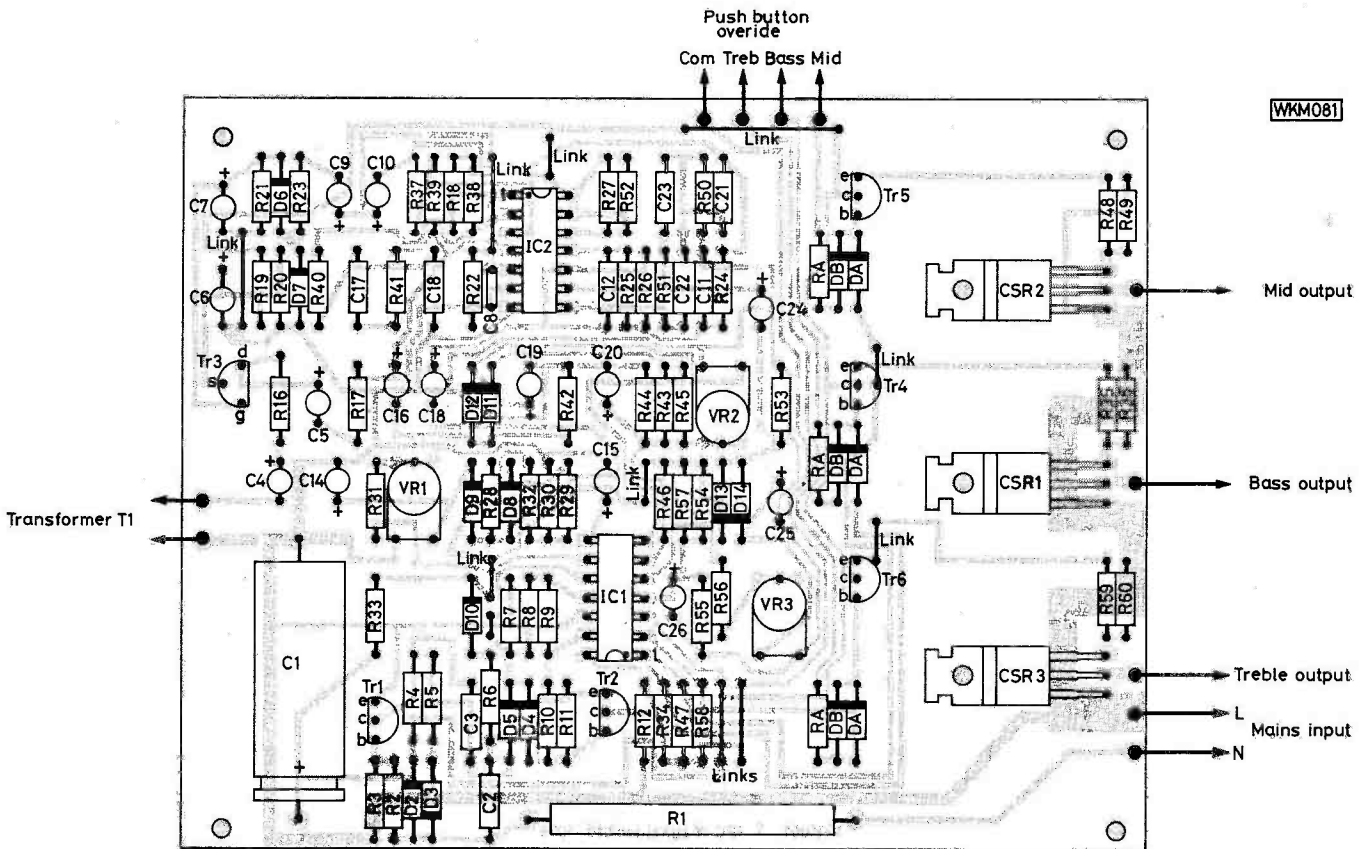

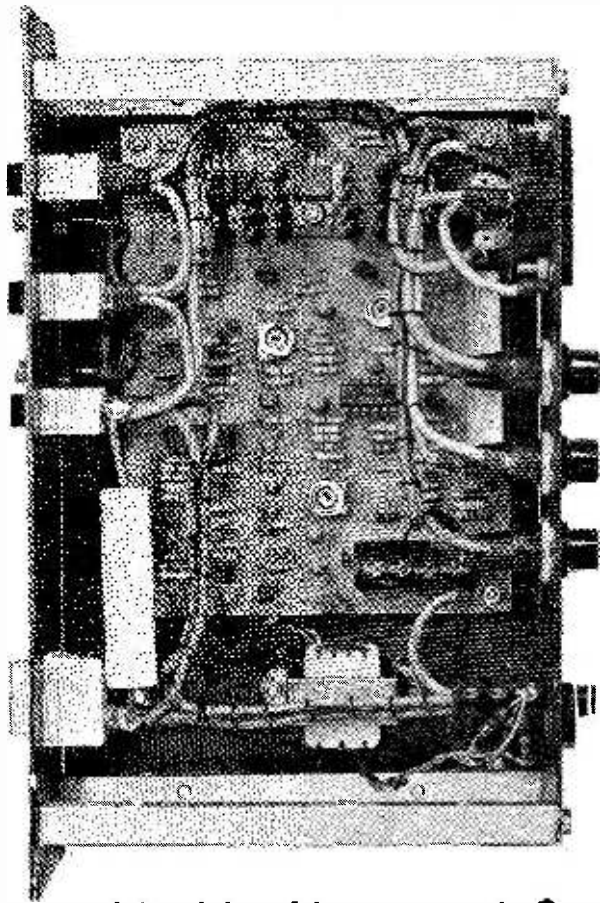


Internal view of the prototype unit ▲

The p.c.b. track pattern is shown in Fig. 4 and the component layout in Fig. 5. Constructors should have little trouble in assembling the board provided the specified components are used. The usual precautions against the effects of static electricity should be taken when handling the two c.m.o.s. integrated circuits. It is safest to use sockets as specified in the components list, and insert the i.c.s only when the remainder of the components have been fitted to the p.c.b. Note that the wirewound resistor R1 gets hot in operation and should be mounted away from the board. Also, the triacs may require larger heatsinks if the unit is constructed in a small, enclosed box. If a common heatsink is used, mica washers and insulating bushes will be required. If the push-button override facility is not required (this is shown on the layout diagram), D_A, D_B and R_A (three of each) may be omitted and D_A replaced by a wire link. Finally, the p.c.b. has extra holes to allow the presets to be replaced by fixed resistors when the optimum values have been found.

The wiring of the unit is not critical and any convenient layout may be used. For guidance, the wiring used in the writer's unit is shown in Fig. 6, drawn flat for clarity. All mains wiring should, of course, use thick wire, say 40/0.2mm, remembering that some leads can carry up to 12A! Note that diode D1 is mounted off the board and resistors R13-R15 are mounted on the input jack JK1. Any convenient case may be used, but the circuit must be securely protected from prying fingers. All metal parts except the heatsinks must be efficiently earthed. The writer's unit was constructed on a metal chassis in a wooden sleeve as shown in the photographs, but alternative construction methods could easily be used.

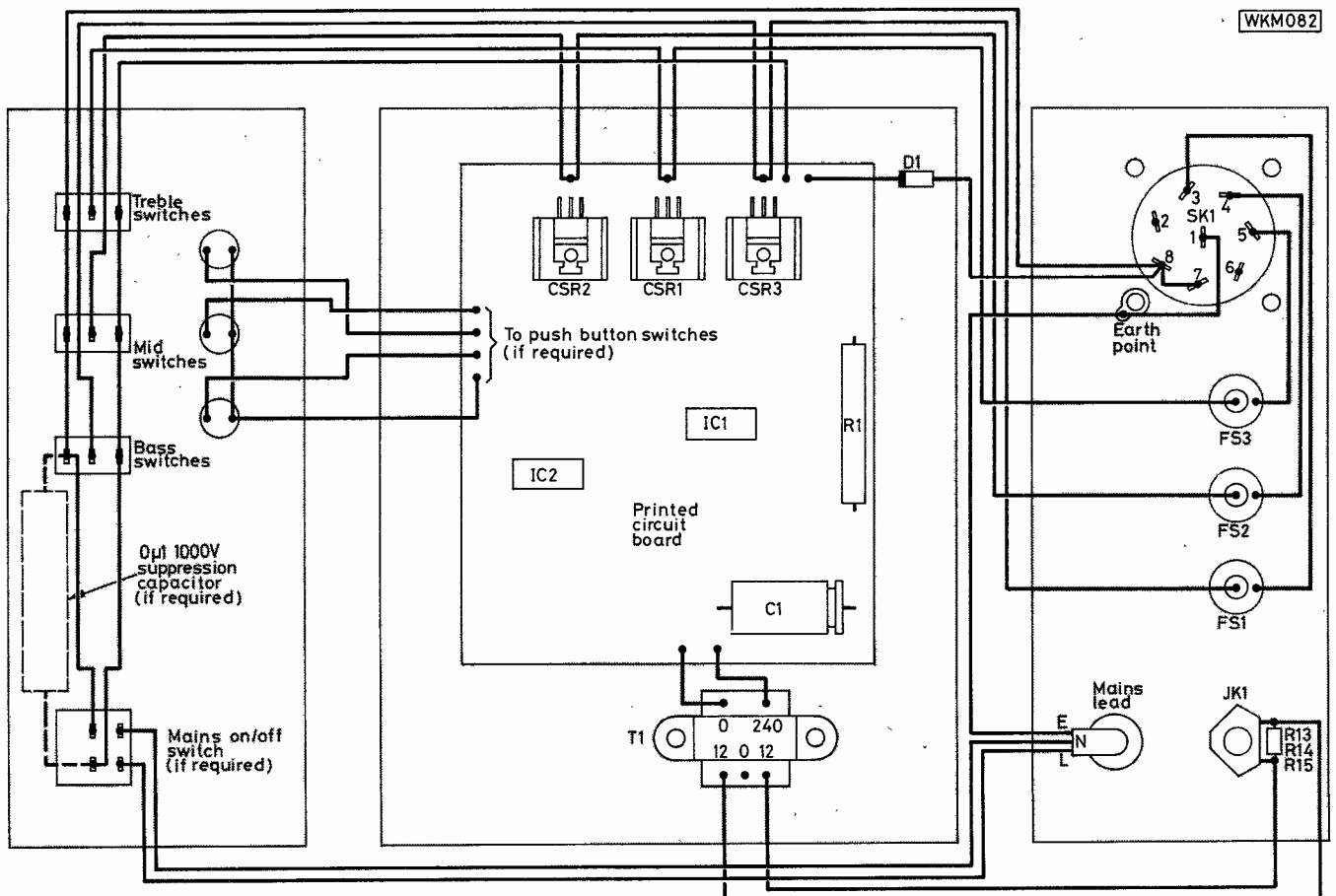▼ Fig. 6: Wiring diagram of a unit incorporating options of Fig. 3(a)



Resistors

$\frac{1}{4}$ W 5%		
220 Ω	3	R35, 48, 59
1k Ω	1	R3
2.2k Ω	4	R11, 36, 49, 60
3.3k Ω	1	R23
4.7k Ω	4	R10, 34, 47, 58
10k Ω	10	R2, 4, 7, 12, 19, 20, 28 33, 42, 53
22k Ω	1	R15
33k Ω	1	R17
47k Ω	4	R21, 31, 45, 56
100k Ω	5	R8, 29, 43, 50, 54
150k Ω	7	R5, 6, 30, 40, 41, 44, 55
220k Ω	2	R16, 25
330k Ω	1	R39
1M Ω	5	R22, 24, 26, 37, 51
2.2M Ω	8	R9, 18, 27, 32, 38, 46, 52, 57
1W 5%		
2.2k Ω	2	R13, 14 (see text)
10W 5%		
4.7k Ω	1	R1

Potentiometers

Min. horizontal presets

47k Ω	3	VR1, 2, 3
--------------	---	-----------

Capacitors

50V plate ceramics

33pF	1	C8
470pF	3	C21, 22, 23
1nF	2	C17, 18
2.2nF	2	C11, 12
4.7nF	2	C2, 3
16V tantalum bead		
2.2 μ F	1	C5
4.7 μ F	8	C9, 10, 13, 14, 16, 19, 24, 25
10 μ F	3	C15, 20, 26
22 μ F	2	C6, 7
35V tantalum bead		
1 μ F	1	C4
25V electrolytic		
1000 μ F	1	C1

Semiconductors

Integrated circuits

MC3301P	1	IC2 (or LM3900N)
MC3302P	1	IC1 (or LM3302N)

Transistors

BC182L	4	Tr1, 4, 5, 6
BC212L	1	Tr2
2N5245	1	Tr3

Diodes

BZX61C15V	1	D3 (or similar 15V 1W Zener)
BZY88C3V3	1	D10 (or similar 3.3V 400mW Zener)
OA91	2	D6, 7
1N4004	2	D1, 2
1N4148	8	D4, 5, 8, 9, 11, 12, 13, 14

Triacs

T2800D	3	CSR1, 2, 3 (or similar 8A 40V triacs)
--------	---	---------------------------------------

Miscellaneous

T1 Min. mains Transformer, 12-0-12V secondary; FS1-3 3A ceramic quick-blow fuses, with panel-mounting holders; JK1 6mm ($\frac{1}{4}$ in) stereo jack (see text); SK1 8-pin socket; Bulgin P552 (plus mating plug P551); Mains on/off switch, d.p.s.t. (if required); Soldercon socket strips to mount IC1 and IC2; Heat-sinks for CSR1-3. Printed circuit board. Box to suit

OPTIONAL EXTRA FACILITIES

1—Push-button control

Resistors

$\frac{1}{4}$ W 5%		
4.7k Ω	3	R _A (x 3)

Diodes

1N4148	6	D _A , D _B (x 3)
--------	---	---------------------------------------

Switches

Normally open push-buttons s.p.s.t. 3

2—Switched override

Switches

Illuminated mains rocker s.p.s.t. 3

3—Half/full power switch

Switch

Toggle s.p.s.t. 1

Testing and Setting Up

After construction is completed, all wiring should be double-checked and all presets set to their central position. Connect a set of lights and switch on. The lights may flicker briefly then they should remain off. The push-button switches (if fitted) should be tested at this point; this checks the operation of the triacs. If all seems well, switch off and connect an audio source. Setting up is best done with a moderately large input signal (2-3V r.m.s.). Switch on again and the lights should show some response. The presets should be adjusted, with an insulated tool, to give the best results with various types of music; this need only take 15 minutes or so. Finally, vary the volume over a wide range and check that the display is similar at different volume levels. The a.g.c. amplifier takes a second or so to "catch up" after rapid changes in volume, so allow a little time between adjustments, etc.

Any faults found are likely to be due to incorrect assembly (e.g., short-circuits on the board, reversed tantalum capacitors), faulty semiconductors or "dry" joints. Note that it is no use trying to test the unit using only the neon indicators in the override switches (where fitted), instead of external lamp loads. The neons do not draw sufficient current to hold the triacs on after they have been triggered.

In cases where there is an exceptional amount of electrical noise on the mains supply from other sources, the lights may flicker even when no audio signal is present. If this is a problem, a 0.1 μ F 1000V capacitor across the mains supply should cure it (see Fig. 6); alternatively, or in extreme cases additionally, the sensitivity may be reduced slightly by increasing the value of R17.

The unit described has been very reliable in use, and several prototypes have been constructed. With care, constructors will have a Sound-to-Light unit of professional standard, capable of long service. ●


Ideas DEPARTMENT

Some original circuit ideas provided by our readers. These designs have not been proved by us, and we cannot therefore guarantee their effectiveness. They should at least provide a basis for experimentation.

Why not send us your idea? If it is published, you will receive payment according to its merits. Articles submitted should follow the usual style of PW in circuit diagrams and the use of abbreviations. Diagrams should be clearly drawn on separate sheets, not included in the text.

Each idea should be accompanied by a declaration that it is the original work of the person submitting it, and that it has not been accepted for publication elsewhere.

STEP TONE GENERATOR

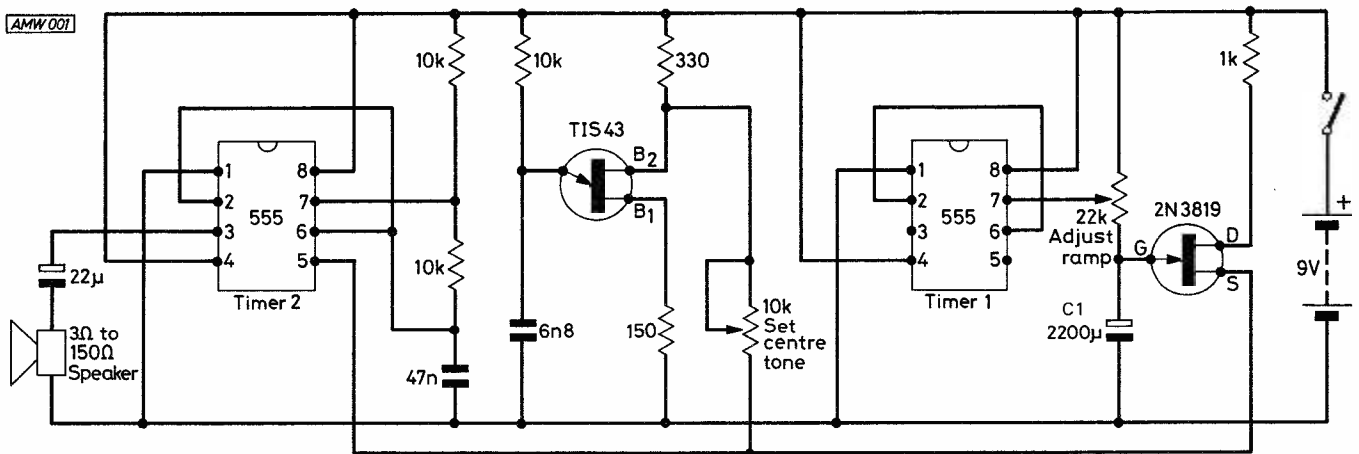

This circuit produces a sound which relates to defined increments stepping up and down a musical scale. No shift register or counter is required to produce each step, and with the exception of the peripheral components the circuit consists of only two 555 timers, an f.e.t., and a unijunction transistor.

One 555 is used as an astable driving a loudspeaker, with the other functioning as a triangular waveform generator providing a control ramp for feeding back into the astable.

Increments are provided by spikes from the unijunction at intervals of $100\mu\text{s}$, which are impressed onto the triangular waveform. The output of the astable is fre-

quency modulated at the same rate, and as the triangular waveform changes, a series of loud beats are produced, running up and down the musical scale. The f.e.t. acts as a buffer to prevent loading of C1. This circuit could be modified to become a "blind man's d.v.m." or a relatively sophisticated voltage to frequency noise scrambler.

*D. Brown GM8FFH,
South Hawthornhill,
Dumbarton.*

CAR CASSETTE POWER SUPPLY

This simple circuit uses a 7805, which is a compact device used mainly with TTL i.c.s and fed with an ample input of at least 8V will produce a stabilised output of 5V at up to 1 amp, provided it is mounted on a heat sink. The minimum of smoothing is required, and the overall circuit will provide 5.6V to power a cassette player from a car battery.

Only a handful of components are needed and R1 was selected such that no voltage drop occurred at maximum volume and of course, the voltage never rises beyond 5.6V without a load. There is, therefore, little chance of the device becoming faulty and damaging the cassette recorder. If a higher output voltage is needed, another diode


PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS

can be connected in series with D1 giving 6.2V but for safety, the existing output is sufficient for most applications.

The output can either be connected directly to the battery connectors in the recorder or alternatively a low voltage power plug can be used to connect externally to the recorder if a socket is fitted.

The unit will work with cars using either positive or negative earth but if a metal box is used as a case, care must be taken to prevent it coming into contact with any part of the car body, especially if a positive earth is used.

M. Burrell,
Halstead,
Essex.

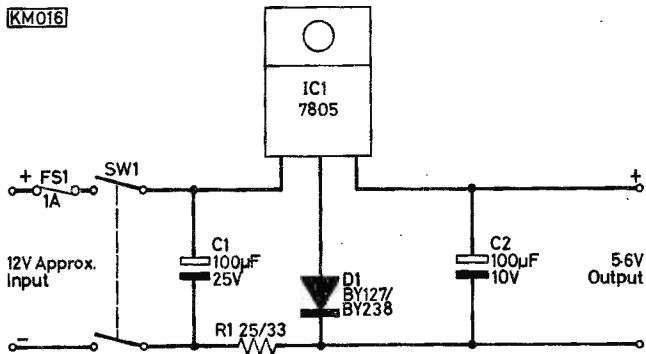

Every month is the right frequency

When you're building a major project from a PW design, you want to be sure of getting every issue in sequence! Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) U.K. £10.60. Overseas £10.60.



practical WIRELESS SUBSCRIPTION ORDER FORM

Please send me Practical Wireless each month for one year. I enclose a Sterling cheque/international money order for.....(amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss _____

ADDRESS _____

POSTCODE _____

Make your crossed cheque/MO payable to IPC Magazines Ltd., and post to: Practical Wireless, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

NEXT MONTH IN...


practical

WIRELESS

ON SALE 2ND. MAR.


2 METRE MONITOR RECEIVER

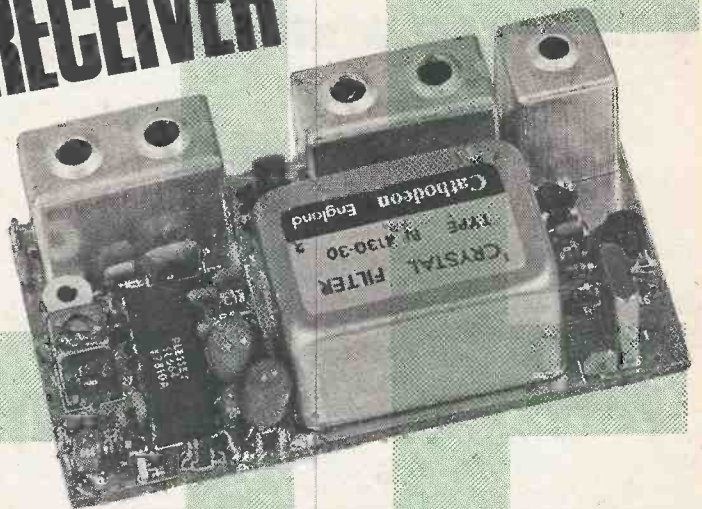A miniature high-performance, single-channel v.h.f. receiver for narrow-band f.m. operation, based on the Plessey Semiconductors SL6640 integrated circuit



VHF/UHF FOLDED COLINEAR AERIAL ARRAY

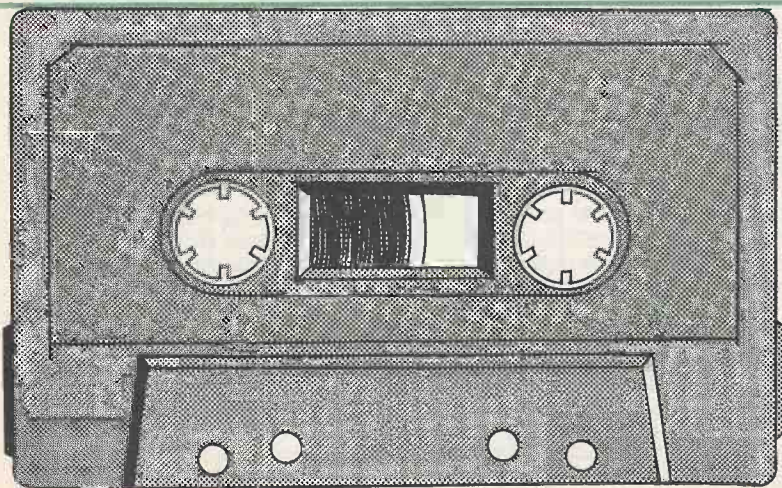An omni-directional, vertically polarised design, giving 3dB gain over a dipole. Details are given for both 2 metre and 70cm versions



THE CASSETTE TAPE MEDIUM

The development of the Compact Cassette system from its inception to the present day is reviewed by Gordon J. King

HYTHE marine band receiver **Part 2**

M. TOOLEY & D. WHITFIELD



After completing the assembly of the receiver as shown in Fig. 5, a careful visual check should be carried out on all wiring, the unit connected to a 12V d.c. supply and the supply current measured. This should be approximately 75mA in the absence of a signal. If a signal generator is available, this should be connected to the aerial socket via a suitable attenuator, and set to 455kHz (± 1 kHz) with internal modulation. A tone should be heard when the receiver is switched to give a.m. reception, and it should be possible to peak IFT1 and the filter IFT2 for maximum output. If necessary, increase the attenuation between the signal generator and the receiver progressively as the i.f. circuits are peaked. This alignment is best done with a relatively weak signal since the a.g.c. action will, to some extent, mask changes in the output level for strong input signals.

An input to the receiver of about 1mV at 455kHz will be all that is required in order to produce a strong audio output signal if the i.f. stages are working correctly. If a signal generator is not available, the i.f. stages may be aligned by tuning the receiver for a weak signal and then adjusting IFT1 and the filter for maximum output. In either case, the alignment process is greatly simplified by reference to the signal strength meter. To adjust the meter, VR4 is first set to mid-position and, with the aerial disconnected, VR5 is then adjusted to zero the meter. VR4 may later be set to calibrate the meter. Constructors should note, however, that there may be a slight interaction between these two controls and the setting-up procedure may have to be repeated whenever the calibration is being altered.

After completing the i.f. alignment, the r.f. tuned circuits of L1 and L2 should be aligned. The signal generator should be set to 1.45MHz with internal modulation and VC1 set for maximum capacitance (i.e., vanes fully meshed). VC2 should be set to mid-position and the core of L2 adjusted until a strong signal is heard. The core of L1 is then peaked for maximum signal. The signal generator is then set to 3.5MHz and VC1 adjusted to near minimum capacitance (i.e., vanes almost fully open) until a strong signal is again heard. The core of L1 should again be peaked for maximum signal but the core of L2 should

be left alone. If, however, the 3.5MHz signal is not located, the core of L2 may be adjusted until a signal is heard at minimum capacitance. This establishes the high frequency end of the receiver's tuning range. There will be a noticeable difference in the settings of the core of L1 at 1.45MHz and 3.5MHz, due to the "tracking" error. With VC2 still set to mid-position, the signal generator is tuned to 2.5MHz and a strong signal located at approximately mid-position of VC1 (i.e., middle of the tuning range). The core of L1 is peaked for maximum, when its position should be roughly mid-way between the 1.45MHz and 3.5MHz positions.

If a signal generator is not available, signals on known frequencies can be used as an aid to alignment. These could include broadcast signals at around 1.5MHz, coastal radio stations on frequencies around 2MHz, and the 2.5MHz standard frequency and time signal. The vernier dial can be calibrated by first removing the scale, painting it with a matt-finish white or silver paint, and then using dry transfers to provide markings every 100kHz from 1.5MHz to 3.5MHz. Alternatively, a somewhat simpler solution is to draw a calibration curve for the receiver and to refer to this whenever exact frequency readout is required. A typical calibration curve is shown in Fig. 6.

BFO

In order to align the b.f.o. transformer, IFT4, a strong carrier, preferably with no modulation, should be selected. With the receiver switched for a.m. reception, VC1 should be carefully tuned to provide maximum indication on the signal strength meter. The mode switch, S1, is then set to the s.s.b./c.w. position and, with VR3 set to mid-position, the core of IFT4 is adjusted for zero-beat.

A beat note may not, in some cases, immediately be heard since the heterodyne produced may lie outside the audible range. If this is the case, adjustment of the core of IFT4 should readily produce an audible note. The quadrature detector tuned circuit, IFT3, is best adjusted using a known f.m. signal of preferably 3kHz peak devia-

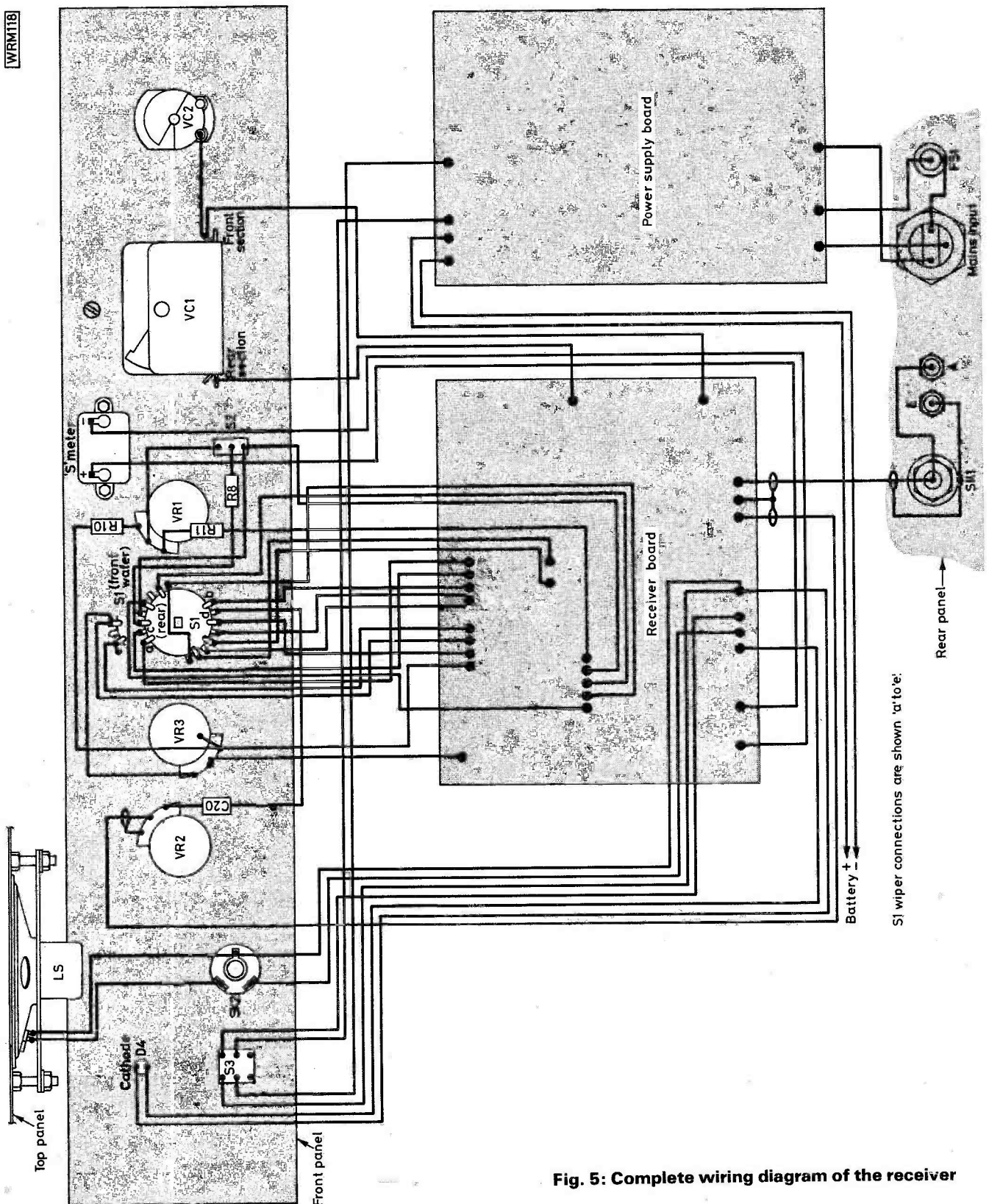


Fig. 5: Complete wiring diagram of the receiver

tion. The receiver is switched to f.m. and the core of IFT3 is then adjusted for maximum undistorted audio output.

Note that the recovered audio level may be significantly less on f.m. than for a.m. The volume control can be adjusted accordingly to compensate for this reduction in level. This completes the alignment and calibration of the receiver, which is now ready for "air testing".

Using the Receiver

The receiver is simple to use and automatic gain control is provided for a.m. reception, but this may be switched out if required when c.w. or s.s.b. signals are being received. This facility will be found to be most useful when strong signals are concerned; the r.f. gain is then simply

backed off for best results. The facility to receive f.m. (which is very rarely used at h.f.) was thought to be a useful addition to a receiver which can potentially be used as a tuneable i.f. in conjunction with a v.h.f. converter. The f.m. facility provides for the reception of narrow-band f.m. signals of typically not more than 3kHz peak deviation. Limiting action is automatically provided for strong signals. The f.m. detector will, however, not perform well with wide-band f.m. signals and, should this be an important consideration, constructors are advised to replace the i.f. filter IFT2 with a comparable type having a wider bandwidth (e.g., the CFT455B which has a nominal 8kHz bandwidth and is pin-compatible).

The receiver is eminently suitable for either fixed or portable use. In each case the receiver will benefit greatly from the use of a properly designed aerial system and tuning unit or preselector. This ensures optimum performance and also helps to reject signals on the image channel. These sometimes appear as breakthrough of strong h.f. signals spaced by twice the intermediate frequency (i.e., 910kHz) above the wanted signal. A particular problem associated with sensitive low- and medium-frequency receivers is that of line-timebase interference from nearby television receivers. There is often little that can be done to prevent this nuisance, but in exceptional circumstances it may be necessary to site the aerial some distance away from dwellings and to employ a buried coaxial feeder with its screen earthed at each end.

For mobile use, a simple base-loaded whip aerial should be adequate although, here again, some form of pre-selector or tuning unit will give vastly improved results.

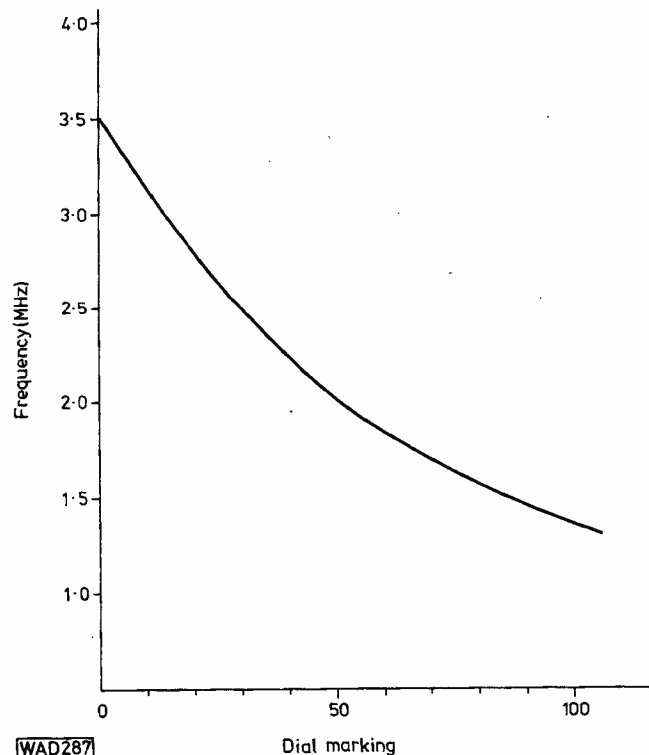


Fig. 6: Tuning calibration curve, used as an aid to alignment

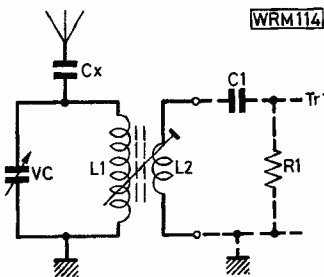


Fig. 7: The basic circuit of the image channel rejector

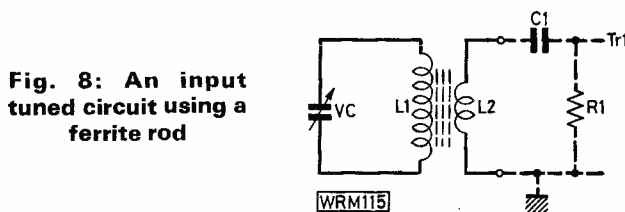


Fig. 8: An input tuned circuit using a ferrite rod

Aerial Matching

The additional tuned circuit shown in Fig. 7 will provide an extra 20dB of image channel rejection. The variable capacitor VC should have a maximum value of about 500pF. L1 consists of 100 turns of 36 s.w.g. enamelled copper wire wound in two layers on a 4.8mm diameter former fitted with a dust core, base and screening can. L2 consists of 10 turns of 30 s.w.g. over-wound on L1. C_x can be 47pF for short aerials or 15pF for a long-wire aerial.

If desired, this form of circuit can be modified to use a ferrite-rod aerial, as shown in Fig. 8, though it should be remembered that such an aerial is directional. Here, VC should have a maximum value of 208pF. L1 is 22 turns of 30 s.w.g. enamelled copper wire wound at one end of a 180mm ferrite rod (see Fig. 9), and L2 is 5 turns of 30 s.w.g. enamelled copper wire over-wound on L1. The ferrite rod should be mounted on pillars about 50mm long, either above or to the rear of the receiver.

An aerial matching unit provides an excellent method of improving the r.f. selectivity of the receiver, thus adding considerably to the image channel rejection, and also acts as an impedance match. In the circuit of Fig. 10, Tr1 is operated as an emitter follower which exhibits a voltage gain of slightly less than unity with a high input impedance and a low output impedance. The circuit can be constructed on a small piece of Veroboard or matrix board. Component details for the input tuned circuit are shown in the table.

Tuned Circuit Details for the Aerial Matching Unit

L1	L2	VC	Notes
5 turns 30 SWG wound on ferrite rod	22 turns 30 SWG	208pF	Not recommended for use with external aerials, directional
10 turns 30 SWG wound on 4.8mm dia. former with dust core	100 turns 36 SWG	365pF or 500pF	Recommended for use with external aerials

★ components

POWER SUPPLY UNIT

Resistors
 $\frac{1}{4}$ W 10% carbon
 470 Ω 2 R1, 2
 1k Ω 1 R5
 4.7k Ω 2 R3, 4

Variable Resistors
 Min. horizontal preset
 10k Ω 1 VR1

Capacitors
 25V electrolytic
 10 μ F 1 C2
 470 μ F 1 C1

Semiconductors

Diodes
 1N4001 4 D1, 2, 4, 5
 BZY88C6V2 1 D3

Transistors
 BC548 1 Tr2
 BD131 1 Tr1

Miscellaneous
 T1 240V primary, 2 x 15V secondaries, 6VA
 FS1 1A 20mm fuse, with panel holder
 Printed circuit board. Heat-sink for Tr1

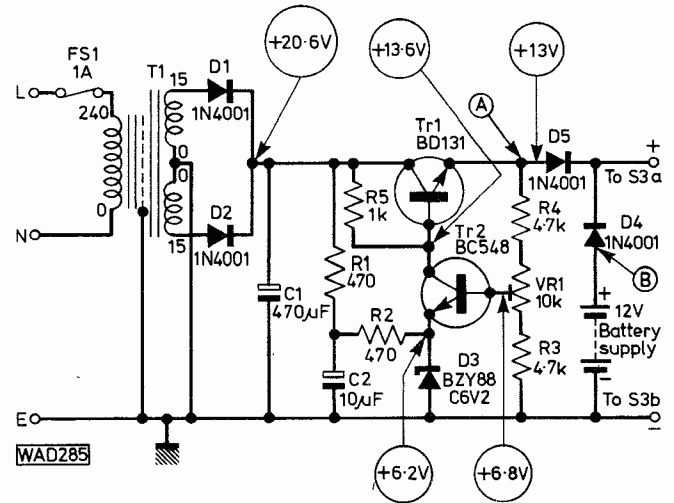


Fig. 11: The circuit diagram of the mains power supply unit

WRM116


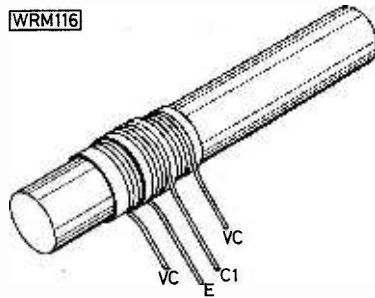
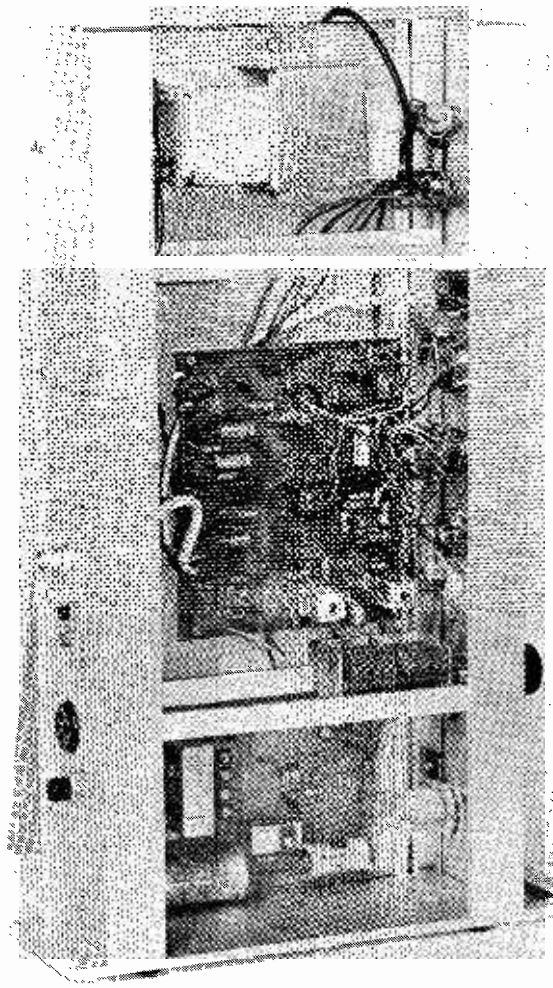


Fig. 9: Details of the ferrite rod aerial

Fig. 10 (below) the circuit diagram of the aerial matching unit

WRM117


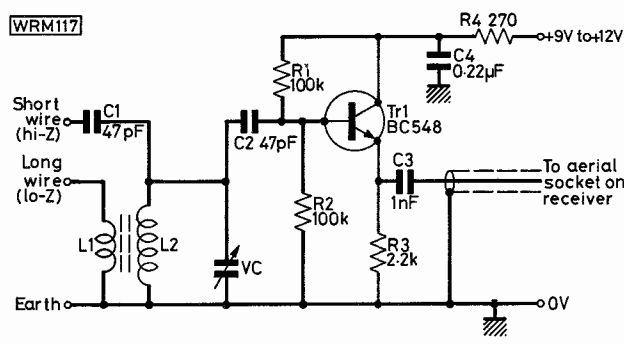


Power Supply

The receiver will give many hours of operation from its internal battery supply which consists of eight U11 cells or equivalent. However, a mains power supply is a very useful addition to any receiver which is likely to be used for any length of time at a fixed location. The circuit diagram of a suitable supply is given in Fig. 11, with p.c.b.

track pattern and component layout shown in Figs. 12 and 13 respectively.

A centre-tapped mains transformer T1, and a full-wave rectifier (diodes D1 and D2) are used to build up a d.c. voltage across the reservoir capacitor C1. The smoothed output is stabilised by the series regulator transistor Tr1, driven by a d.c. amplifier based on Tr2. Control of the output voltage from the unit is achieved by supplying the base of Tr2 from an adjustable tap on the potential divider

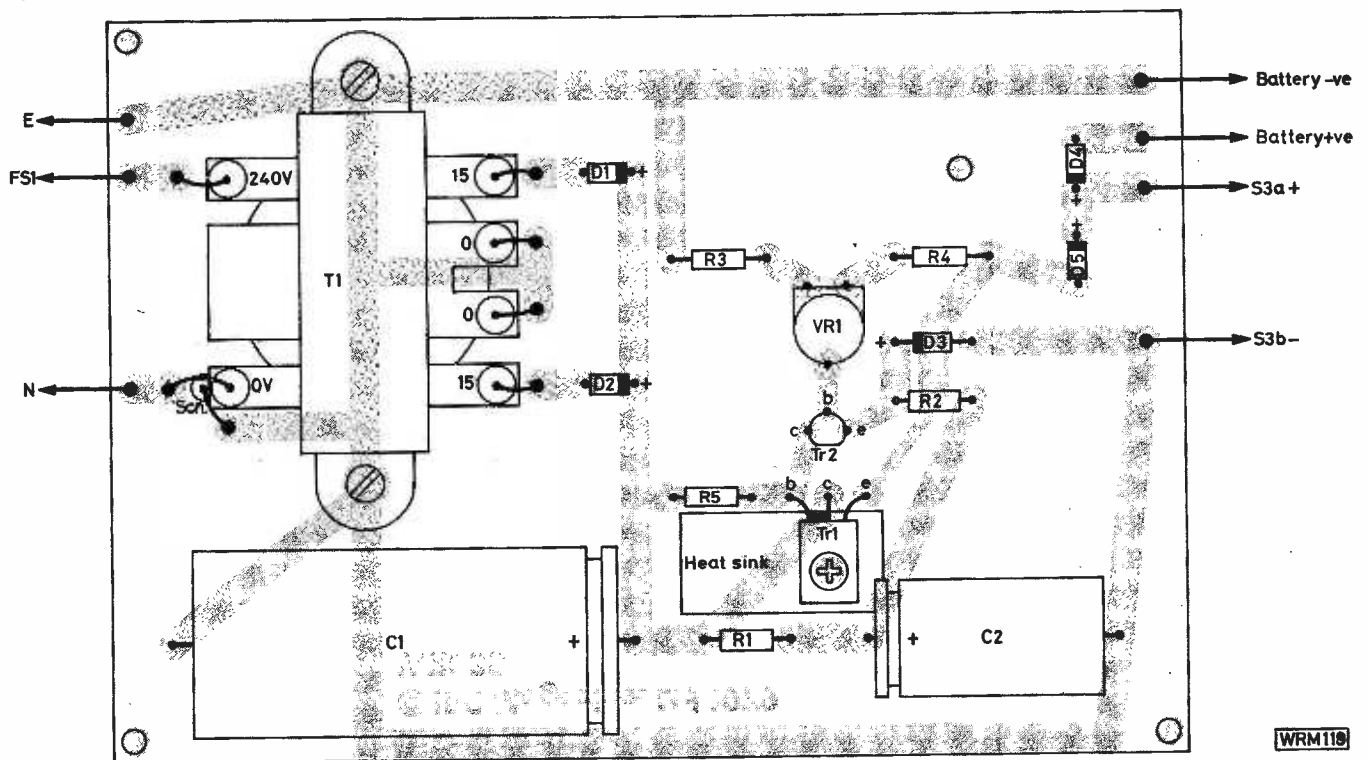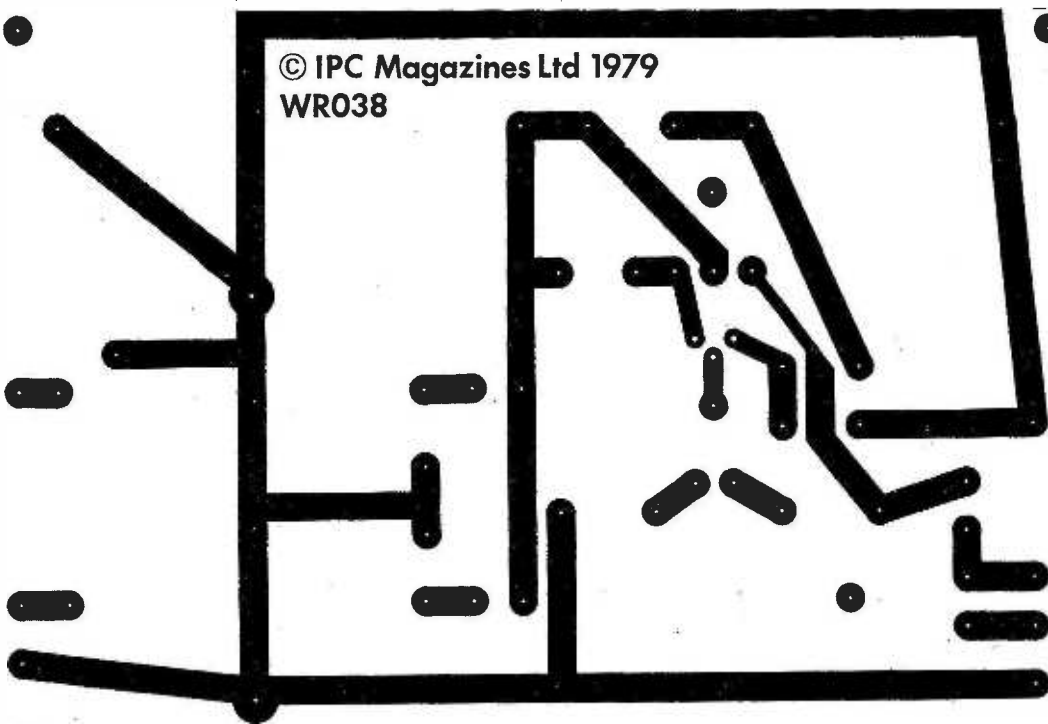

Copper track pattern and layout of the power supply unit shown full size

formed by R4, VR1 and R3. Zener diode D3 provides an emitter-reference potential for Tr2. Changeover from a.c. mains to battery power is automatic in the event of a supply failure. This is achieved by the steering diodes D4 and D5. When the mains supply is present, the potential at point "A" will exceed that at point "B" (see Fig. 11). This will reverse-bias D4 and forward-bias D5, effectively open-circuiting the battery supply. When the mains supply is removed, either by accident or design, D4 will be forward-biased and D5 reverse-biased, supplying battery power to the receiver.

The power supply is straightforward to build and only one adjustment is necessary. Before connecting the output of the supply to the receiver board, the voltage at point "A" should be set to +13V by adjustment of VR1. In case of any problems, typical test voltages as measured using a 20k Ω /V multimeter on the 25V range are indicated on the circuit diagram.

The a.c. mains plug should be removed from the supply when the receiver is not required for operation over an extended period, since the mains unit remains working independently of the front panel on/off switch.

THE **PW** 'WINTON' Stereo Amplifier

Part 1

* E.A.RULE

The Winton amplifier has been designed primarily for the home constructor who would like a high fidelity amplifier equal to the best commercial design available, but at a price that enables it to be built within a sensible domestic budget, the total outlay being in the region of £110 for the complete project.

All the components are available and no special test equipment is needed for testing or setting up. The amplifier uses the very latest techniques and is capable of a standard of performance at least equal to the best commercial designs available with similar power ratings. In some aspects of its design it will outperform other amplifiers costing very much more.

Power f.e.t.s are used in the output stage and allow a wider power-bandwidth response with lower distortion than could be obtained if conventional bipolar output transistors were used. In the control unit section, bi-f.e.t. op.amps are used. These have an improved slew rate over the more common types, as well as much lower distortion. In the disc (magnetic) pre-amplifier, a three stage circuit using ultra low noise transistors enables noise figures of -68dB *unweighted* relative to 50W output to be obtained, with distortion so low that the input (normally 3mV) has to be increased to 140mV ($+33\text{dB}$) before the distortion even reaches 0.1%. A full circuit description will be given later.

On the front panel the Winton amplifier has controls for Volume, Balance, Bass, Treble and push buttons for selecting, Disc, Tuner, AUX 1, AUX 2, Tape monitor, Mono, h.f. and l.f. filters. Plus switches for mains on/off and loudspeaker or phones.

The headphone socket is also mounted on the front panel. DIN sockets are fitted on the rear panel for all inputs, terminals for the loudspeaker connections, an earth terminal, and fuse for the mains and each loudspeaker output. The heat sinks for the power f.e.t.s are also mounted on the rear panel.


Power f.e.t.s

Until recently bipolar transistors have been used in almost every Hi-Fi available (the exceptions using valves). Bipolar transistors require a wide area of Safe Operation to achieve reliability and a large gain-bandwidth product so that large amounts of negative feedback can be used at the higher audio frequencies to reduce the distortion. They also have a positive temperature coefficient which means that any increase in transistor temperature causes an increase in transistor collector current which causes the temperature to increase further, and so on requiring careful design to avoid thermal runaway. Also, as bipolar transistors are minority carrier devices, they suffer from storage effects at high frequencies which can cause a most objectionable distortion, which may well account for the so called "transistor sound".


In the light of all these problems a considerable amount of money and research has gone into looking for a better device. One result of this has been the power f.e.t.s developed by Hitachi Ltd., of Tokyo, Japan. Some advantages over conventional transistors are:

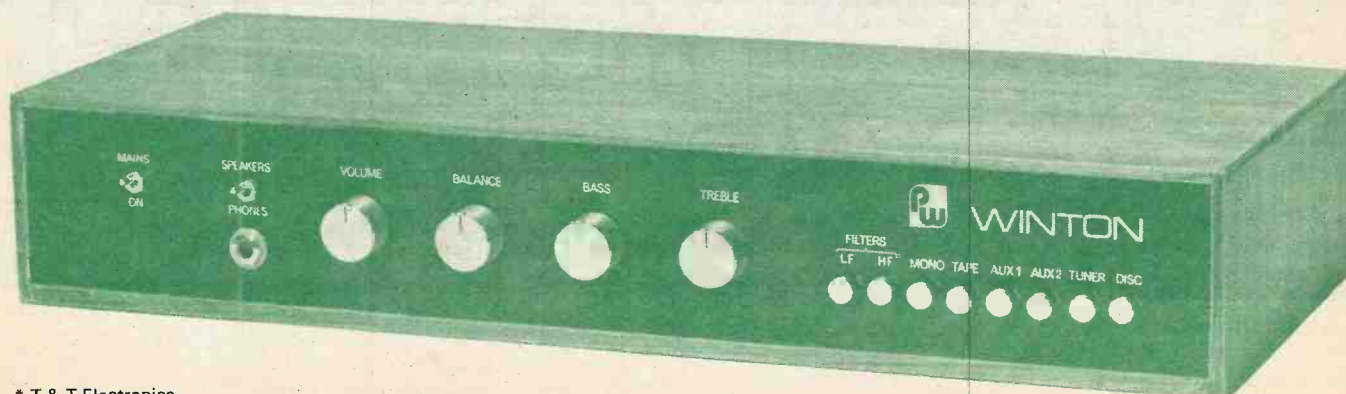- 1) Good frequency response because of fast carrier speed.
- 2) No storage effect.
- 3) Negative temperature coefficients, so no risk of thermal runaway.
- 4) No secondary breakdown.
- 5) High input impedance and high gain.


The Winton amplifier uses a complementary pair of Hitachi power f.e.t.s Type 2SJ48 (*p*-channel) and 2SK133 (*n*-channel). These devices have a maximum dissipation rating of 100W each, so when used in an amplifier of 50W output, each device is only dissipating about 25W, or just ticking over! In fact combined with a 120V drain to source breakdown voltage and a drain current of 7A they are almost indestructible when used in the Winton, which



* T & T Electronics

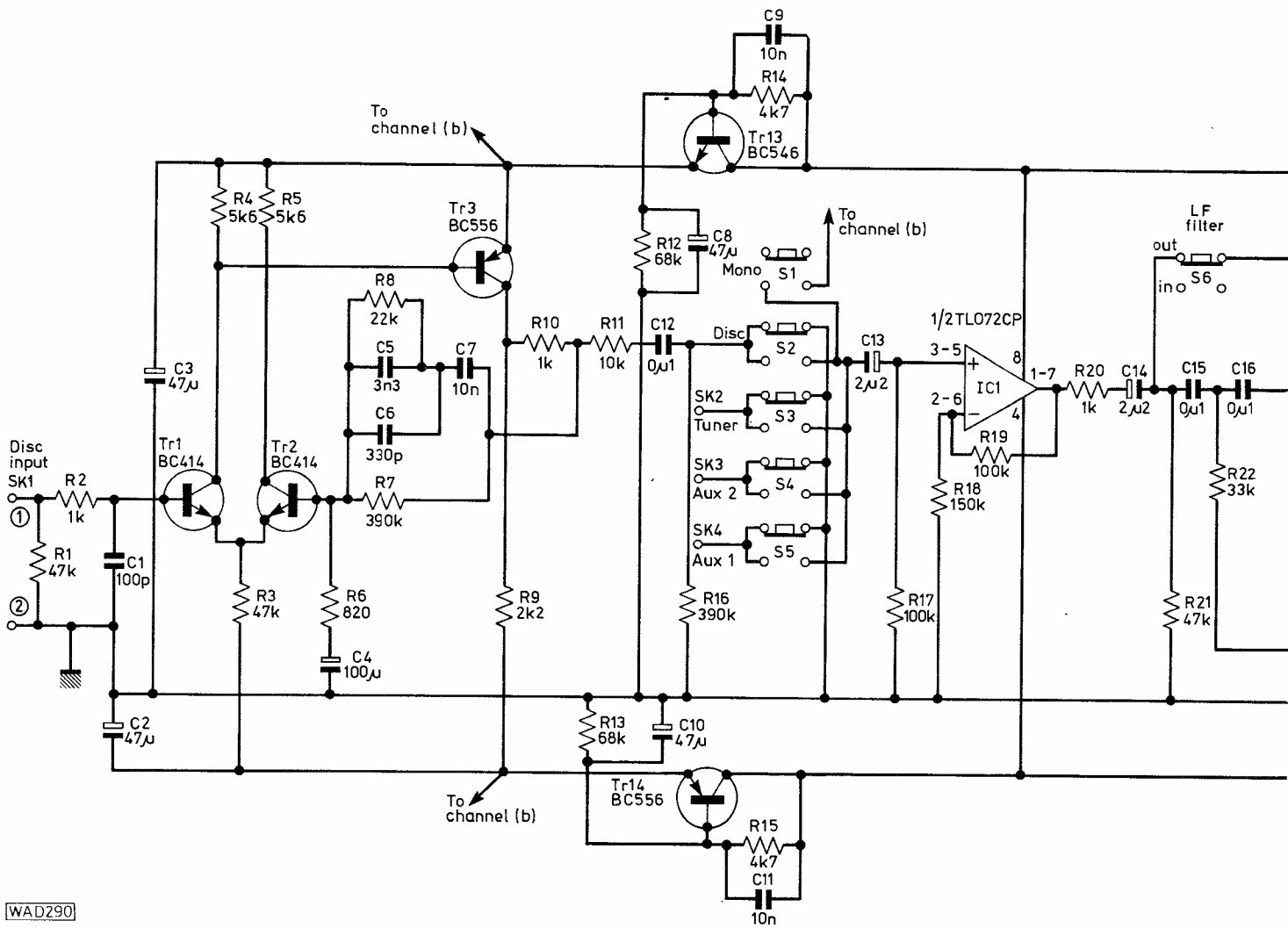

WAD290

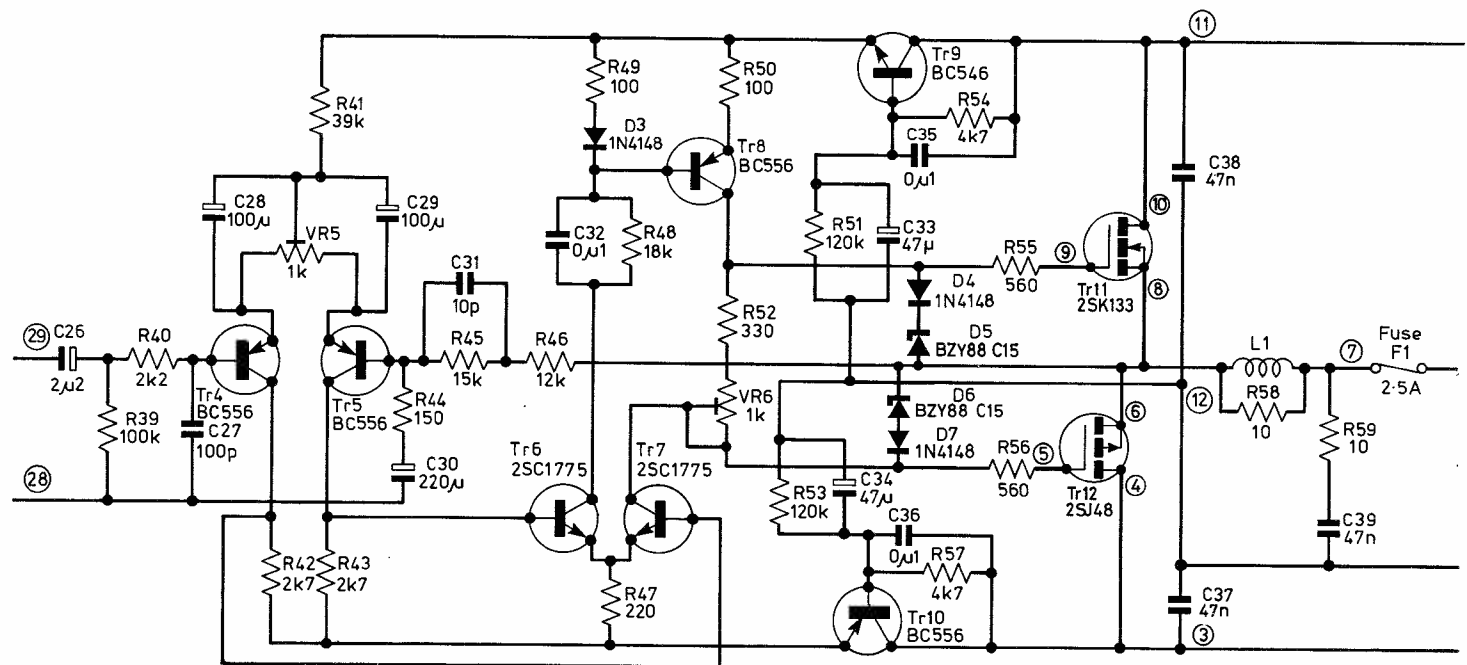

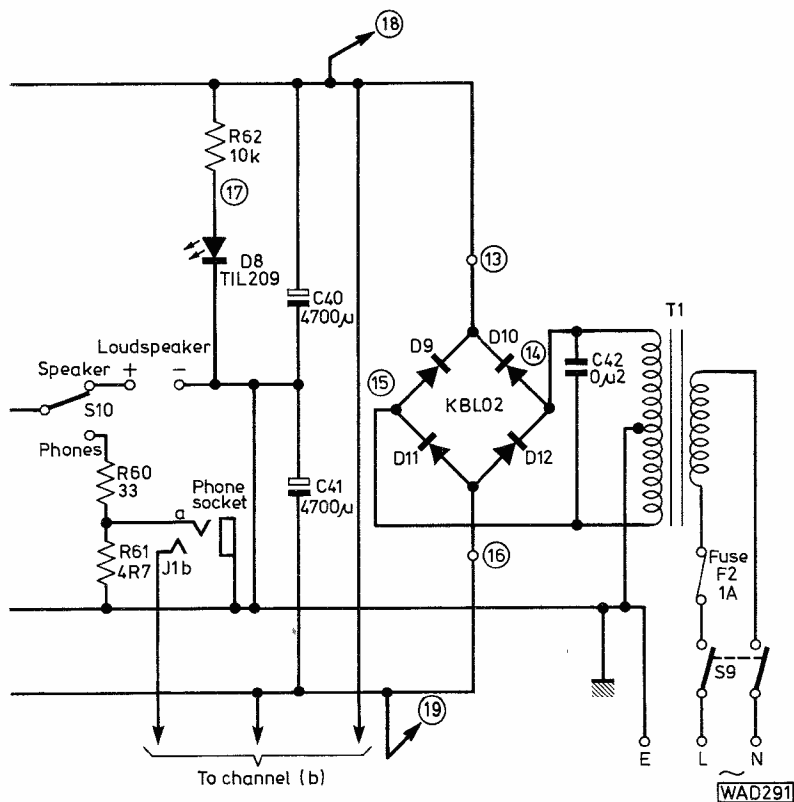
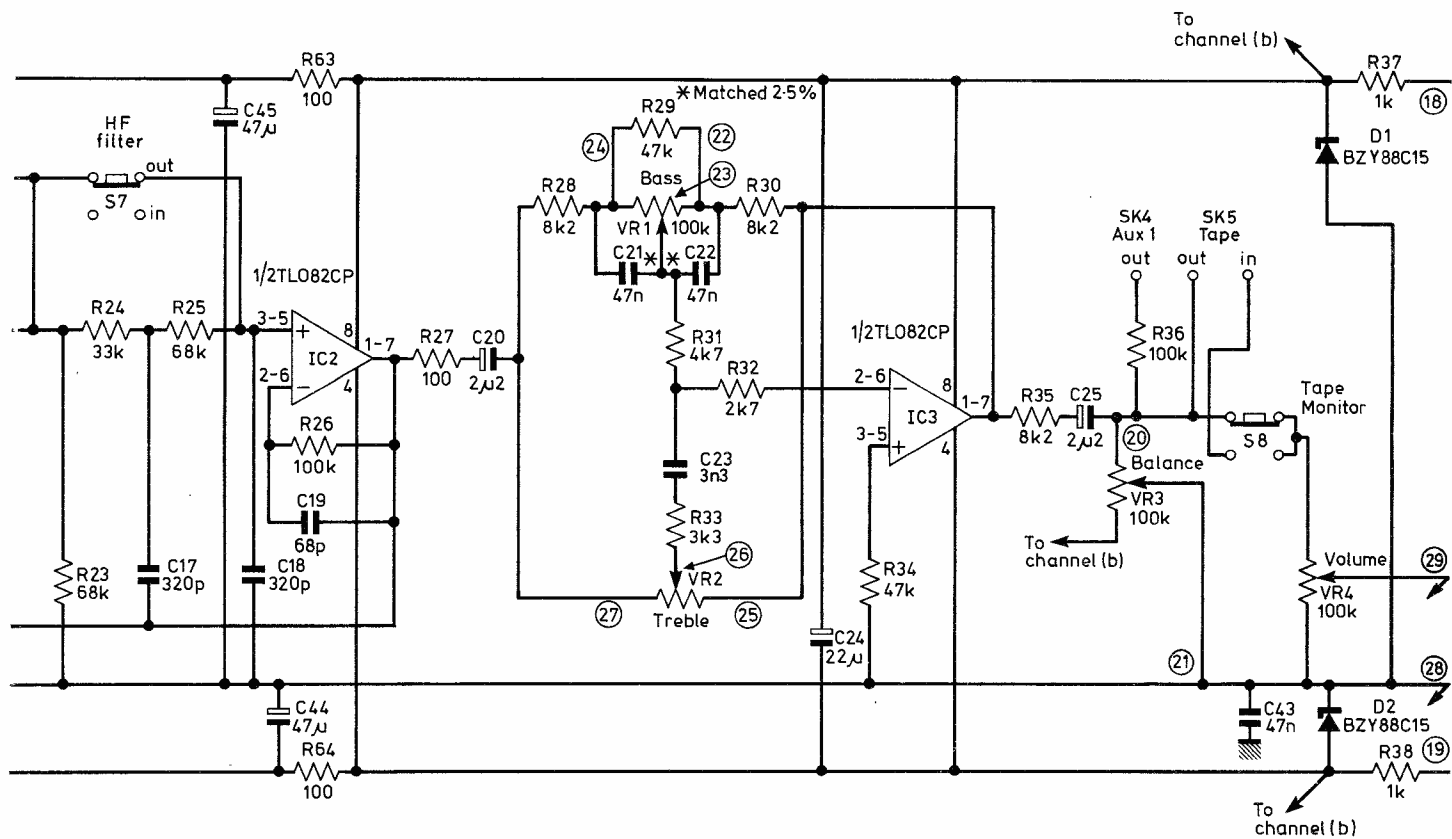


Fig. 1: Circuit diagram of the PW "Winton" stereo amplifier, showing Channel "a" (left) only. The following components are shared between the two channels: R12-15, 37, 38, 62-64; C2, 3, 8-11, 24, 40-45; Tr13, 14; IC1-3; D1, 2, 8-12; VR3; T1; F2; S9. The remainder are duplicated for the other channel

★ specification

Power Output

Continuous sine wave power, both channels driven
50 + 50W into 8Ω

Power Bandwidth (power amp. only)

-1dB 15Hz - 100kHz

Frequency Response (power amp. only)

-0.5dB 10Hz - 40kHz
-3dB 5Hz - 150kHz

Harmonic Distortion (50 + 50W)

1kHz 0.013%
10kHz 0.015%
20kHz 0.018%
100Hz 0.011%
20Hz 0.019%
No significant increase at lower powers

Intermodulation Distortion (28V pk into 8Ω)

$f_1 = 15\text{kHz}$ $2f_1 - f_2$ 0.005%
 $f_2 = 16\text{kHz}$ $2f_2 - f_1$ 0.004%
 $f_2 - f_1$ 0.003%

Damping Factor

20Hz - 1kHz 80
20kHz 20

Rise Time (power amp. only) 2μs

Slew Rate (power amp. only) 26V/μs

Stability - Unconditional

Sensitivity for 50W

Disc 3mV
Tuner 100mV
AUX 100mV
Tape 100mV

Input Impedance


Disc 47kΩ
Tuner 100kΩ
AUX 100kΩ
Tape 100kΩ

Maximum Input for 0.1% t.h.d.


Disc 140mV
Tuner 4V
AUX 4V

Frequency Response ±0.5dB

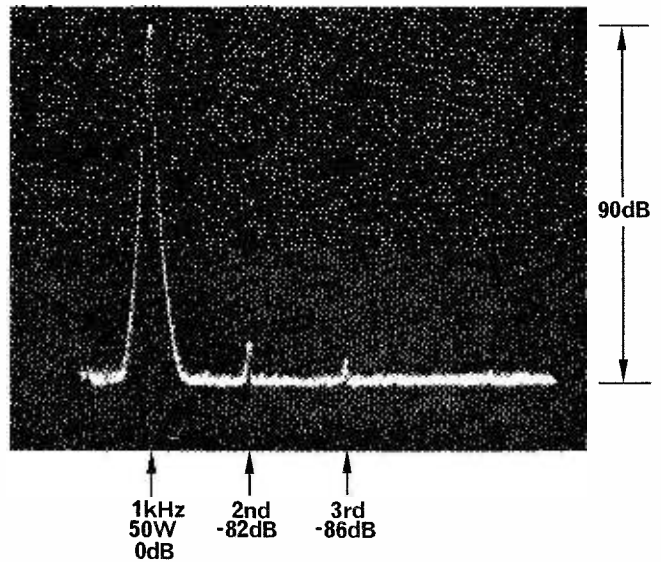Disc RIAA
Tuner 20Hz-20kHz
AUX 20Hz-20kHz
Tape 10Hz-40kHz




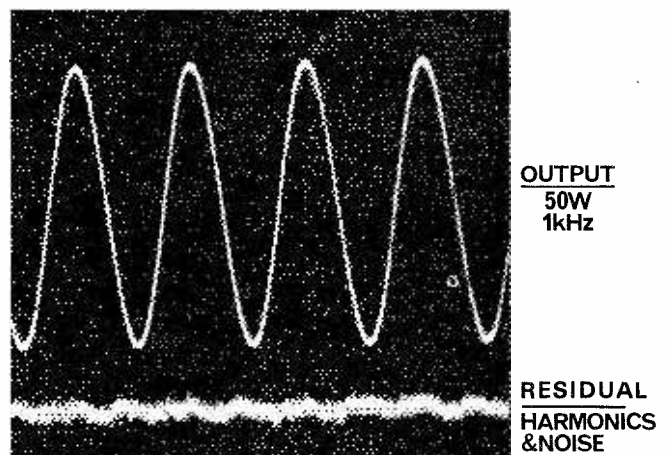Plot of Harmonic Distortion components generated when handling a 1kHz signal dissipating 50W in an 8Ω load. The 2nd harmonic is at -82dB and the 3rd harmonic -86dB relative to the fundamental



The upper trace shows the PW "Winton" output when handling a 1kHz signal dissipating 50W in an 8Ω load. Note the complete absence of crossover distortion

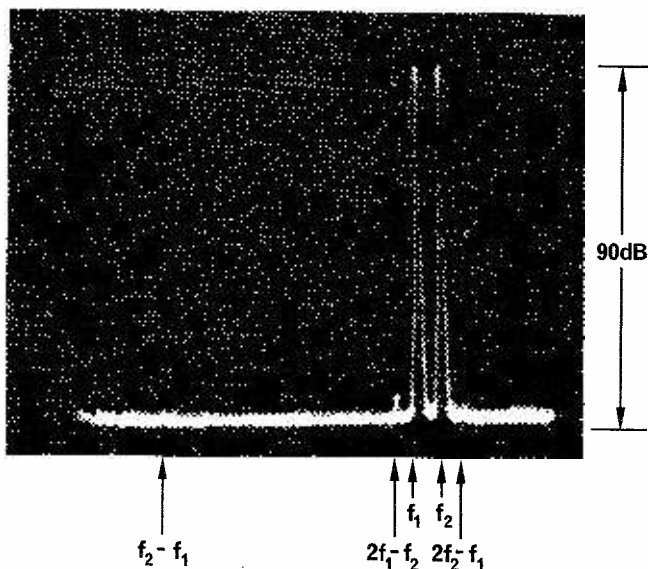The lower trace shows the residual harmonic content of the above signal, after the fundamental had been removed by the distortion meter filter. The total harmonic distortion is about -78dB, but is masked by noise



Plot of Intermodulation Distortion components generated when driven to full power into an 8Ω load by two equal-amplitude signals, $f_1 = 15\text{kHz}$, $f_2 = 16\text{kHz}$. Component $2f_1 - f_2$ is at -86dB , $2f_2 - f_1$ at -88dB , and $f_2 - f_1$ estimated at about -90dB

This test, using these frequencies, is very critical of the power-bandwidth capability of an amplifier, and is seldom given in specifications due to the generally poor figures obtained

Hum & Noise

Unweighted with reference to rated sensitivity*

Disc -70dB

Tuner -75dB

AUX -75dB

Tape -75dB

Hum & Noise

Disc input with reference to 10mV input

Unweighted 80.5dB

Cross Talk** -48dB

Tape Output 100mV

AUX 1 100mV via 100kΩ

* See comments regarding specifications.

** Important to note that cross talk residual is clean, i.e., does not introduce distortion into the other channel—a common failing in many amplifiers and seldom mentioned.

Tone Controls

Bass $\pm 10\text{dB}$ at 100Hz

Treble $\pm 10\text{dB}$ at 10kHz

Balance Control

+0.5dB to zero, each channel

Channel Matching 0.5dB

Filters

l.f. -3dB 50Hz 12dB/Octave

h.f. -3dB 5kHz 12dB/Octave

Subsonic, disc only, non-switchable

(IEC 65) -3dB 20Hz

-8dB 10Hz

-17dB 5Hz

Ultrasonic, all inputs except tape, non-switchable

-3dB 60kHz

-7dB 100kHz

Before making any measurements, the amplifier was pre-conditioned for 1 hour at 30% full power with both channels driven. Measurements were made after a further 5 minutes at full power.

Unless otherwise stated, the volume control was at maximum, tone controls at centre and filters switched out.

The stability tests were made using various combinations of loads with capacitors up to $2\mu\text{F}$ and also with capacitors up to $2\mu\text{F}$ without additional load. Square wave signals were used over a frequency range of 20Hz to 20kHz.

The figures given are those obtained on the prototype amplifier.

Test Equipment

Hewlett Packard HP3580 spectrum analyser; Kron-Hite 4100 low distortion oscillator; Sound Technology 1700B distortion analyser, power output meter and low distortion oscillator; Telequipment D83 oscilloscope; Polaroid oscilloscope camera.

This equipment was kindly made available by Armstrong Audio Ltd., at their research laboratory.

General Comment

Be very careful when comparing specifications of other amplifiers with the Winton. Many other published specifications use a weighted signal to noise figure. This would allow an extra 10dB or so to be added to their figures and tends to favour the poorer quality amplifiers at the expense of the really good amplifiers.

means that the circuit can be kept simple as no protection circuits are required, eliminating another source of distortion.

The Bi-f.e.t. Op.amps

The use of the Texas bi-f.e.t.s in the control unit section offers a number of advantages over the more usual 741 type of op.amp. The main ones being:

- 1) Wider bandwidth. 3MHz typical.
- 2) High slew rate 13V/μs.
- 3) Low distortion 0.01%.
- 4) High input impedance j.f.e.t. input stage.
- 5) Low noise 18nV/Hz (TL072CP).
- 6) 80dB supply ripple rejection.

When used in low or unity gain circuits using large amounts of negative feedback the noise and distortion from the device is almost unmeasurable. The Winton amplifier has a basic sensitivity at the AUX inputs of 100mV and this has to be increased to 4V before the distortion reaches 0.1%. At any normally used input level the distortion is below the noise and completely inaudible.

Circuit Description

Both channels are identical and are pre-fixed "a" for left and "b" for right. Only the "a" channel will be described. See Fig. 1.

The Disc Pre-Amplifier

The input from a magnetic cartridge is fed into the base of Tr1, a low noise BC414 via the input load R1, 47kΩ, and an r.f. filter R2 C1. The transistor Tr1 forms one half of a differential input pair. Operating at a low current, approximately 100μA each half, ensures the minimum amount of noise.

The output from Tr1 is coupled directly to Tr3 a BC556. This in turn is coupled to a subsonic filter (as recommended by IEC65) consisting of C12, R16 and R17. This subsonic filter has its -3dB point at 20Hz, Fig. 2. This response, coupled with the normal RIAA response provides a 12dB/octave filter at subsonic frequencies and prevents intermodulation at low frequencies caused by warped records, etc., from being produced and affecting the overall sound quality. The RIAA negative feedback equalising circuit consists of R7, R8, C5, C7 and is connected between the output of Tr3 and the base of Tr2.

In order to ensure further the low noise factor in the disc amplifier, electronic decoupling is used, Tr13 (BC546) Tr14 (BC556) in each supply rail to remove any ripple or noise from the power supply. This supply has already been decoupled and stabilised by the Zener diodes, D1, D2.

The output from the disc pre-amplifier then goes to the selector switches S 1-5.

Control and Filter Section

From the selector switches S 1-5, each channel goes to one half of IC1 a bi-f.e.t. op.amp, Type TL072CP. This is used as a low noise buffer amplifier (with 4dB of gain) to provide a high impedance input, and a low impedance output suitable for driving the next stage, which also uses a bi-f.e.t. op.amp, Type TL082CP. This is used as an active high- (C15, C16, R22, R23) and low- (C17, C18, R24, R25) pass filter. Operating at unity gain, the filter is designed to provide a 12dB/octave cut-off with the -3dB points at 50Hz and 5kHz respectively, Fig 3. A slope of 12dB/octave is considered to be optimum for Hi-Fi use as a steeper slope could introduce ringing on transients, which would sound most objectionable.

The tone controls follow the filters, again using a bi-f.e.t. op.amp, Type TL082CP, and the circuit is a Baxandall negative feedback type.

This type of tone control circuit keeps distortion and noise to a much lower level than the passive type and also provides frequency response contours more acceptable to the ear, Fig. 4.

The amount of bass and treble boost and cut has been restricted to around + or - 10dB at 100Hz and 10kHz. Although it is possible to obtain up to 20dB boost and cut at these frequencies by removing R29 and reducing R33, extreme amounts of boost or cut are considered by the author to be bad design, as in practice large amounts can rarely be used. For example, suppose we have a signal requiring +10dB at 100Hz, with our circuit we can obtain this with only an extra dB or so at lower frequencies. If the unrestricted circuit was used, 10dB of boost at 100Hz would also produce 20dB of boost at 20Hz, as the response would continue to rise as shown in Fig. 4. The effect of this would be to increase all the rumble and other low frequencies a further 10dB over the required level at 100Hz. This would be in effect asking the amplifier for a considerable increase of power at low frequencies and as it cannot provide this, severe distortion would result. Note:

10dB of boost equals a voltage ratio of 3.16:1.

If our amplifier is already producing 50W into 8Ω, i.e., 20V, then $20V \times 3.16 = 63.2V$, power = $V^2 \div R = 3994 \div 8 = 499.28$ watts!!

Even with the amount of boost restricted to + 10dB, if the bass control is at maximum and the amplifier is just reaching maximum power (50W) at say 20Hz then the maximum power at 1kHz must be limited to 5W (assuming a flat frequency response of the input signal). In practice, the tone controls are normally used to make up for the deficiency in the incoming signals, i.e., to restore the signal to an overall "flat" response, so the power restriction normally won't apply.

The output from the tone control circuit then passes to the balance control and the tape monitor switch S8. This switch selects either the output from the control unit section or the output from a tape recorder (connected to the tape socket) and feeds the signal via the volume control to the power amplifier. A tape output signal is permanently connected from the control unit output to both the tape socket and via 100kΩ resistors to the AUX 1 socket. This arrangement allows the use of either or both reel to reel and cassette recorders with the Winton. When using a reel to reel or cassette recorder fitted with a monitor head (plugged into the "tape" socket) tape monitoring can be achieved by simply pressing the "tape" button.

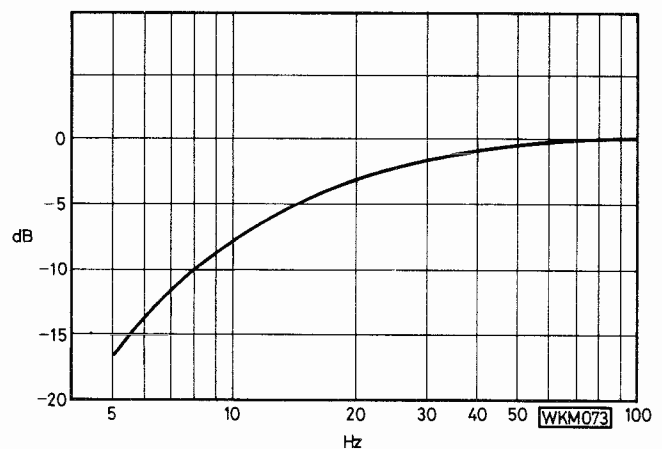


Fig. 2: Disc input — Subsonic filter response

Fig. 3: Frequency response of l.f. and h.f. filters

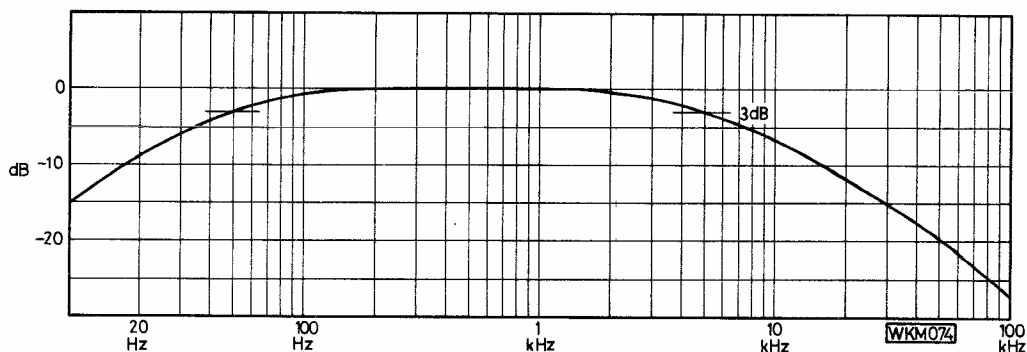


Fig. 4: Frequency response range of Bass and Treble controls


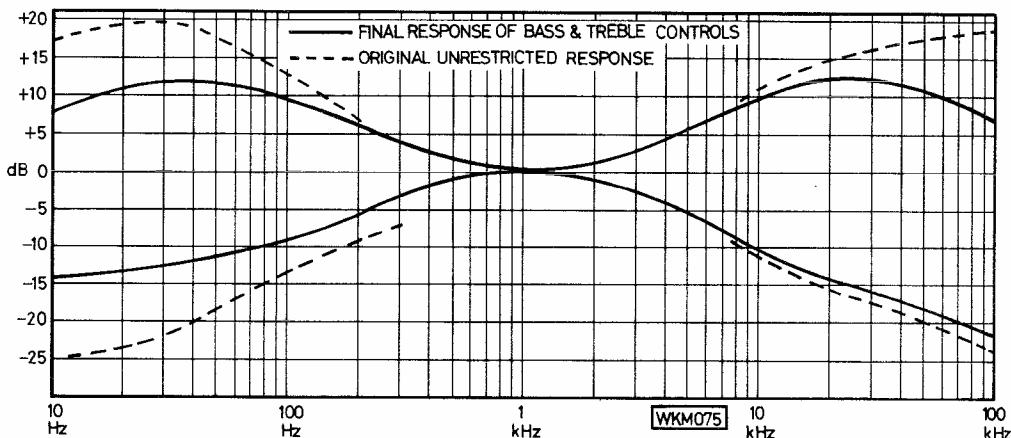


Fig. 5: Cross-talk between the two channels, for Disc and Auxiliary inputs

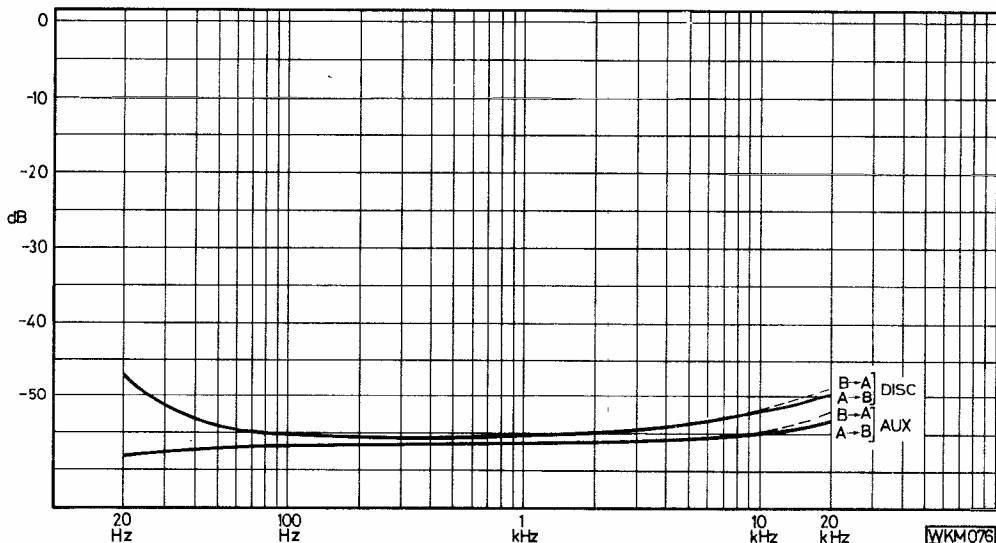

Power Amplifier

The circuit used for the power amplifier is based on a design produced by Hitachi for their power m.o.s.f.e.t.s. The original circuit has been modified by the author to suit the requirements of the Winton and electronic decoupling added to further improve the overall specification.

The signal from the volume control, VR4 is fed via an r.f. filter R40, C27 to the base of Tr4. This is one half of a differential pair Tr4, Tr5 using low noise transistors Type BC556. These in turn drive a second differential pair, Tr6, Tr7, Type 2SC1775, which has an active collector load (current mirror formed by Tr8 and D3), to maintain the pushpull action. The power m.o.s.f.e.t.s Tr11, Tr12 are driven directly from the second differential pair. As the

inherent distortion of the amplifier is very low, only 45dB of negative feedback is used, this is fed from the output, back to the base of Tr5 via R46, R45, C31. The use of less feedback means that, at the overload point, the onset of distortion is less severe than would be the case with amplifiers using considerably more negative feedback. Diodes D4, D7 and Zeners D5, D6 form an overdrive protection circuit to prevent the gates of the m.o.s.f.e.t.s from receiving excessive drive voltages in the event of a fault condition.

Due to the excellent high frequency response of the amplifier only minimal feedback phase correction is required via C31, R45, and L1, R58, R59, C39. The amplifier is unconditionally stable.

As mentioned earlier, electronic decoupling has been included in each power amplifier to reduce the power

★ components

Resistors

5% 0.25W

100Ω	8	R27, 49, 50, 63, 64
150Ω	2	R44
220Ω	2	R47
330Ω	2	R52
560Ω	4	R55, 56
820Ω	2	R6
1kΩ	6	R2, 10, 20
2.2kΩ	4	R9, 40
2.7kΩ	6	R32, 42, 43
3.3kΩ	2	R33
4.7kΩ	8	R14, 15, 31, 54, 57
5.6kΩ	4	R4, 5
8.2kΩ	6	R28, 30, 35
10kΩ	2	R11
12kΩ	2	R46
15kΩ	2	R45
18kΩ	2	R48
22kΩ	2	R8
33kΩ	4	R22, 24
39kΩ	2	R41
47kΩ	10	R1, 3, 21, 29, 34
68kΩ	6	R12, 13, 23, 25
100kΩ	10	R17, 19, 26, 36, 39
120kΩ	4	R51, 53
150kΩ	2	R18
390kΩ	4	R7, 16

5% 0.5W

10Ω	2	R59
10kΩ	1	R62

5% 1W

10Ω	2	R58
4.7Ω	2	R61
1kΩ	2	R37, 38

7W wirewound

33Ω	2	R60
-----	---	-----

Potentiometers

100kΩ + 100kΩ lin.	2	VR1, 2
100kΩ + 100kΩ log.	1	VR4
100kΩ lin.	1	VR3

Min. Preset horizontal mounting

1kΩ	4	VR5, 6
-----	---	--------

Switches

Min. toggle d.p.d.t.	2	S9, 10
Push button unit 8 keys	1	S1 to 8 (T & T Electronics)

Capacitors

Electrolytic

2.2μF 63V	10	C13, 14, 20, 25, 26
22μF 63V	1	C24
47μF 63V	10	C2, 3, 8, 10, 33, 34, 44, 45
100μF 16V	6	C4, 28, 29
220μF 16V	2	C30
4700μF 63V	2	C40, 41 (Note: 7A ripple rating)

Polystyrene

10pF	2	C31
60pF	2	C19
100pF	4	C1, 27
320pF	4	C17, 18
330pF	2	C6
3.3nF	4	C5, 23
10nF	2	C7

} 2.5%

Polyester

0.2μF	1	C42
0.1μF	12	C12, 15, 16, 32, 35, 36
47nF	7	C37, 38, 39, 43
47nF	4	C21, 22 (Note: matched 2-5%)
10nF	2	C9, 11

Semiconductors

Diodes

TIL209	1	D8
BZY88C15	6	D1, 2, 5, 6
1N4148	6	D3, 4, 7
KBL-02	1	D9-12

Transistors


BC414	4	Tr1, 2
BC556B	11	Tr3, 4, 5, 8, 10, 14
BC546B	3	Tr9, 13
2SC1775E	4	Tr6, 7
2SK133	2	Tr11
2SJ48	2	Tr12

Integrated Circuits

TLO72CP	1	IC1
TLO82CP	2	IC2, 3

Miscellaneous

PCB Winton (T & T Electronics), Mains Transformer, Belclera 6854/3 (T & T Electronics), Chassis and front panel, Winton (T & T Electronics), Case Winton (T & T Electronics), Pins, RS 433-630 (47); Fuse holder, RS 412-879 (3); Fuse 2.5A Quick Blow (2); Fuse, 1A Slow-Blow (1); Pillars, RS 543-737 (5); Cable Ties, RS 543-349 (8); Cable Ties, RS 543-428 (6); 4mm Terminals, Black (1), Blue (2), Red (2); DIN Socket 5-way 180° (5); Jack Socket, RS 478-015 (1).

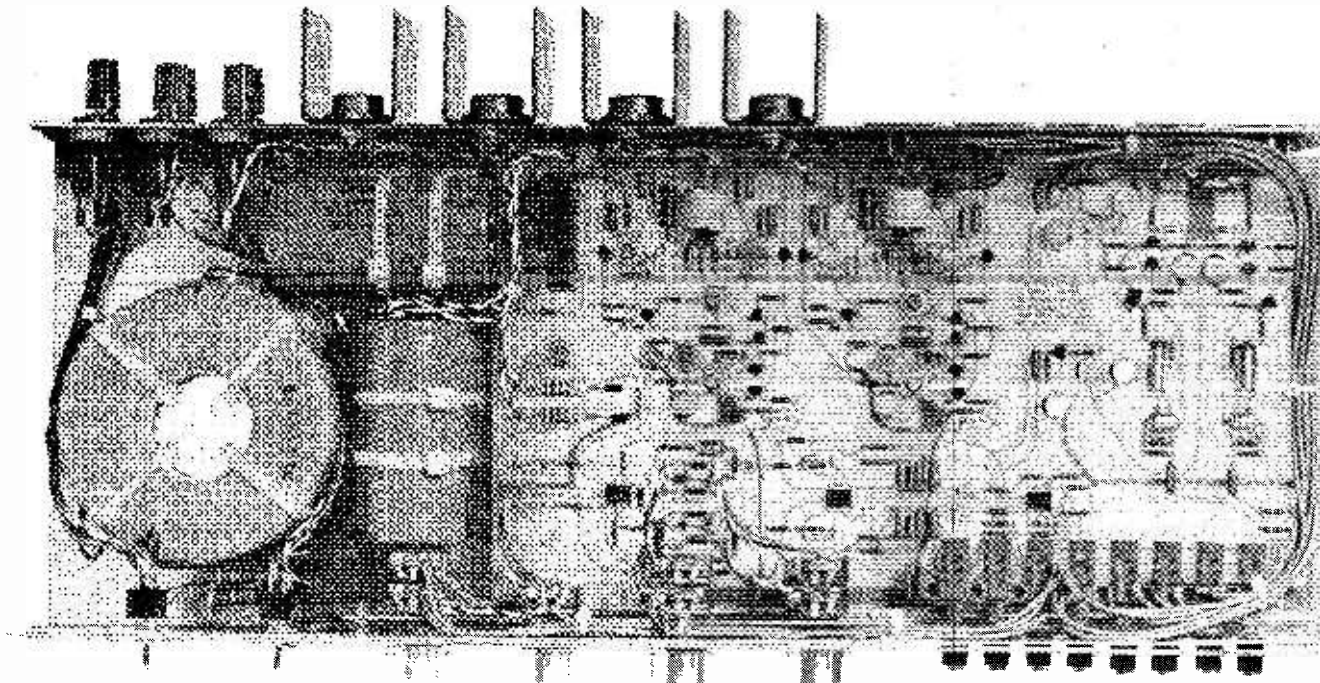

Internal view of the PW "Winton" amplifier. Here, we show the final version using a printed circuit board. The model illustrated on our front cover is the prototype, which was constructed on perforated board with hard wiring

supply noise and ripple voltage, as well as improving the cross-talk (Fig. 5) between channels. Transistors Tr9, BC546 and Tr10, BC556 are used for the decoupling circuit.

Provision is made to adjust the d.c. offset at the output to zero. By adjusting VR5, the current through the differential input stage can be adjusted to compensate for the slight gain variation in each half of the differential pairs. It is very important that the output from the amplifier does not contain any d.c. voltage, as this would cause the loudspeaker cone to take up a position away from its centre which in turn would cause distortion because of the resulting non-linear cone movement.

Power Supply

By no means least important, the power supply of the Winton has been subjected to the same standard of design as the rest of the circuits, although on the surface it may look simple.

In a high fidelity amplifier the power supply can either turn a good amplifier into a top quality model or into a not so good one. There are two main reasons for this:

- 1) The regulation of the supply volts must enable the amplifier to reach its full power potential under the worst possible signal conditions. At the same time, it must not let the voltage rise to dangerous levels under quiescent conditions.
- 2) The external magnetic field from the transformer must not inject any hum into the amplifier circuits, particularly the disc amplifier.

To enable the full performance that the Winton is capable of to be achieved, it was decided to use a toroidal type of transformer. The design and development of this special low-field transformer was carried out by Belclere Ltd., and this transformer is now available from T & T Electronics.

The output from the transformer goes to a bridge rectifier and then to the two 4700 μ F capacitors C40, C41. These, and the electronic decoupling circuits used in the

power amplifiers, coupled with the Zener stabilised supply to the control unit and further electronic decoupling to the disc pre-amplifier, ensure that only about 0.001% of the total output from the Winton is noise from the power supply. Even on the disc input the total noise in the output from all sources combined is only about 0.04%.

Heat Sink Ratings

When designing an amplifier for domestic use, the design is almost always a compromise between all the various requirements. In the case of the Winton amplifier this applies to the size of the heat sink and mains transformer.

It is possible to make both of these components in such a way that the amplifier could deliver 50 + 50W continuous power for hours on end without much temperature rise. The cost of doing this would be so high as to put the amplifier out of reach of most peoples' budget. On the other hand these components could be made down to a low price and the amplifier allowed to run very hot, which would lower the reliability.

In the design of the Winton the author has arranged that these two components will allow the power f.e.t.s and the transformer to run well inside their respective maximum rating under continuous drive conditions, although under these conditions both the heat sink and transformer will reach quite high temperatures and certainly be too hot to touch.

When used for its normal purpose, i.e., reproducing music, the temperature rise is very much less and after some hours of loud music will still be only moderately "Hot". The actual heat sink may reach 60°C under these conditions.

This compromise doesn't reduce the quality of the reproduced sound in any way, but it does avoid a severe pain in the wallet.

NEXT MONTH
Constructional details

Follow-up to THE PW 'AVON'

Peter Preston

Those who built the Avon transmitter described in *PW*, July 1978, may be interested in one or two simple yet significant modifications which were ultimately incorporated into the prototype. The purpose was to increase the power output to approximately 20 watts for the original 24 volt supply and to give some consideration to a repeater access facility. The question of powering the transmitter from 12 volts—a car battery, for instance—was also examined, and the update caters for this at a reduced r.f. output of around 9 watts.

In the first place, the "Calibrate" facility provided by S1 in the switching arrangements of Fig. 10, p. 52 (*PW*, Aug. '78) was dispensed with and the switch re-assigned to a toneburst facility for repeater working. Details of the toneburst module appear elsewhere in this issue: the board on which it is constructed can easily be accommodated in the available space.

Step two is to replace the 15V regulator (7815) with a 12V type 7812. Our attentions are then directed towards the power amplifier board, where the majority of changes take place. Here a little care is needed, although the modifications are far from complex. The revised board could, of course, be constructed as an "afterburner" which would provide a substantial increase in output from, say, a hand-held transceiver.

Initially, remove the resistor R1 (82Ω 2W) and take the h.t. feed (now 12V) directly to the board. The collector supply to the p.a. transistors remains routed to the *input* of the 7812 voltage regulator, via the switching of Fig. 10 (Aug. '78).

Now take out the BLY83 transistors and carefully expand the holes in the p.c.b. to accommodate the new 2N5642 devices. The leads will require a little trimming and this should be done fairly accurately to permit the transistors to fit on the appropriate islands on the board.

The increased output of the new p.a. inevitably means that appreciably more heat will be dissipated by the final stages. Additional heatsinking will have to be provided and in the prototype this took the form of a piece of aluminium 100 × 50 × 4mm, drilled to accept the studs of the power transistors. The sink is fixed to the main chassis by means of a suitable nut and bolt in each corner and the surface in contact with the chassis coated with Thermopath grease or similar compound. Insert the 2N5642 devices and tighten down, carefully soldering the connections to the p.c.b. afterwards (Fig. 1).

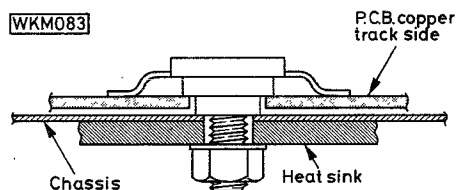


Fig. 1: Mounting the power transistors

The installation of the toneburst module designed by Philip Hodson is extremely simple. A power supply is taken, via the defeat switch S1, from across the energising coil of the keying relay RLA, which is shunted with a diode to absorb switching transients. Miniature screened lead feeds the signal input to the base of Tr2 (Board 1), with a 1μF tantalum capacitor placed in series.

The prototype exhibited some problems which ultimately were attributed to stray r.f. entering the microphone input. It is therefore recommended that a


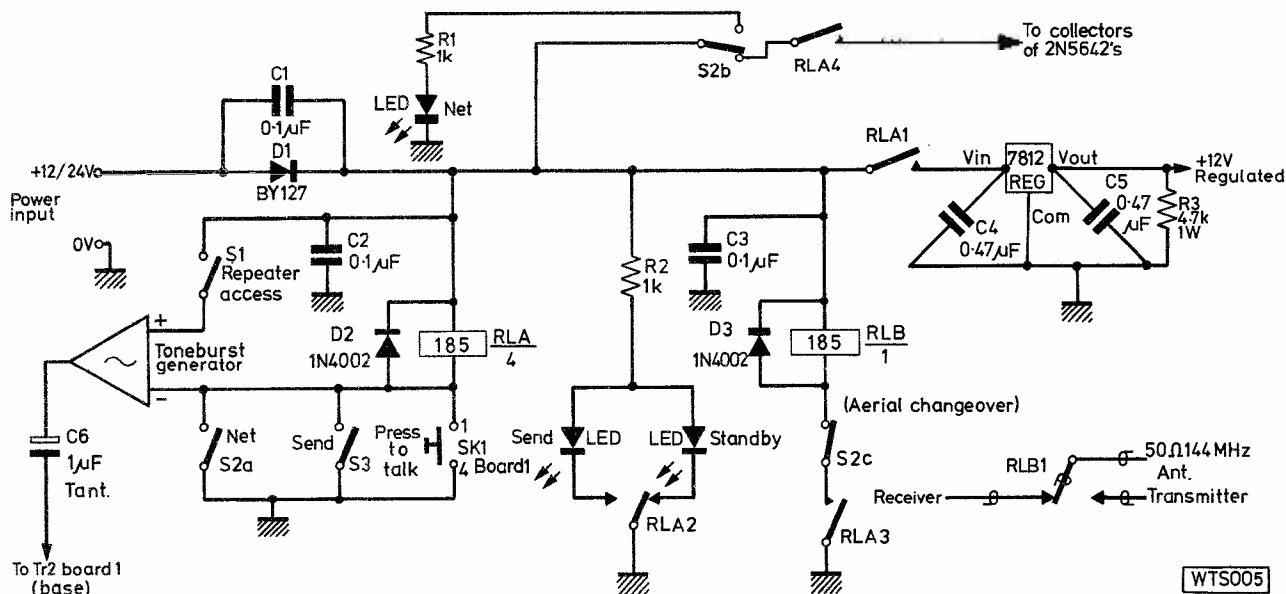


Fig. 2: The new switching arrangements — note the earth on changeover contacts RLA2, the option of different coil resistances for RLA and RLB from the original article, and the addition of diodes D2 and D3

continued on page 53

Wideband RF Noise Source

D. Whitfield

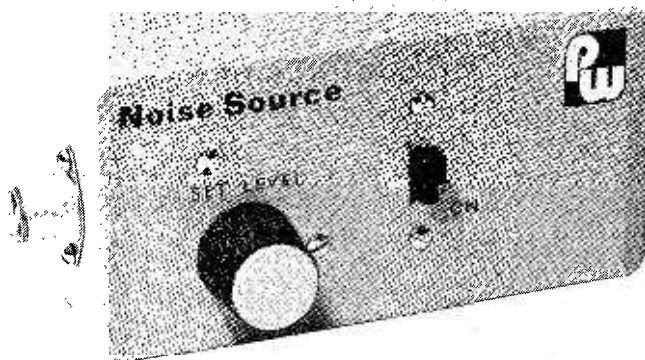

A wideband r.f. noise generator is a most useful device for carrying out rapid performance checks on all types of h.f. and v.h.f. receiver. The wide variety of applications of such an instrument includes gain checks, receiver sensitivity measurements and, where a calibrated attenuator is available, the noise generator may also be used to carry out accurate measurements of gain, noise figure, a.g.c. characteristics, and the calibration of signal strength meters.

The noise generator described here uses a minimum of components, is simple to construct and, although its output level is uncalibrated, is eminently suitable as a source for receiver alignment with an output which is substantially of constant level over a very wide frequency range. A previous article dealt with the construction of a matching calibrated 50Ω attenuator.

True "white" noise can be thought of as a signal which is evenly distributed over an infinitely wide range of frequencies and, although the instantaneous voltage varies randomly, the r.m.s. noise voltage developed into a resistive load will be constant when measured over a short time period. The noise power developed into a purely resistive load is thus directly proportional to the bandwidth in which it is measured.

Generating Noise

The simplest form of noise source is that due to thermal agitation current in a conventional carbon resistor. The fluctuation in current caused by the random movement of electrons is evenly distributed in frequency but the noise voltage produced is usually extremely small. Practical noise generators do not provide an infinite noise spectrum. This is due both to the limitations of the noise source itself and to the bandwidth of any following amplifier. The choice of noise source depends on a number of factors.

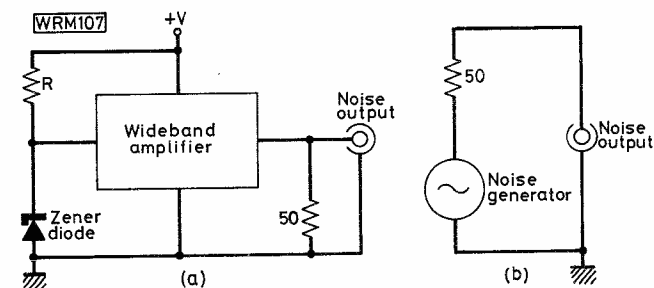


Fig. 1: Block diagram (a) and Thevenin equivalent circuit (b) of the noise source

Thermionic diodes are popular in commercial noise generators but, for economy of supply and portability, the noise source employed in this design is a conventional Zener diode. A considerable noise voltage is developed across the series load resistor of a Zener diode when it is undergoing breakdown. It is, however, usually necessary to include a stage of amplification following a noise source so that its output voltage is of a sufficient level for general purpose use. This has the added advantage that the amplifier stage also provides a degree of isolation between the noise source and the input of the circuit or receiver under test.

Circuit Description

A block diagram of the noise generator, together with its Thevenin equivalent circuit, is shown in Fig. 1. The noise output of the Zener diode is amplified using a two-stage wideband amplifier, Tr1 and Tr2. Both transistors operate in the common emitter mode and the gain of the second stage, Tr2, is made variable by the application of negative feedback by means of VR1. The device used in the Tr2 position has an effect on the bandwidth of the noise output. For use at v.h.f. the transistor recommended is a BFY90 as this has a very high cut-off frequency. For general purpose use at h.f. (i.e. to at least 30MHz) a much less expensive transistor may be used, and the 2N706 is quite adequate.

In order to facilitate matching to a standard 50Ω system, the output of the wideband amplifier is terminated in a 56Ω carbon resistor. This, together with the parallel effect of the collector load resistor of Tr2, ensures an output resistance of almost exactly 50Ω . The output noise voltage can be thought of as being generated in this resistor and thus the Thevenin equivalent circuit of Fig. 1b is realised.

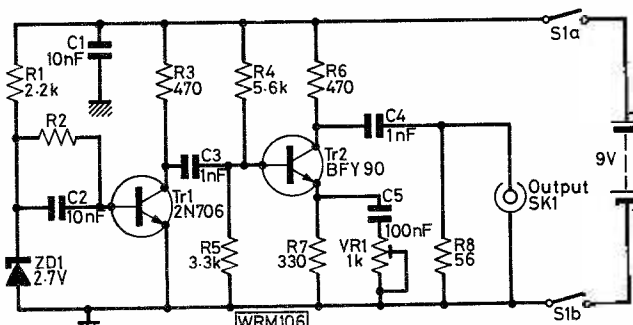


Fig. 2: Circuit diagram of r.f. noise source

Construction

Construction is straightforward and the use of the printed circuit board layout described is highly recommended. Where a printed circuit board is not used, care must be taken to ensure that all wiring is neat and as direct as possible. The noise generator is housed in a standard diecast box. Any alternative screened metal box can be used provided that the leads from the printed circuit board to the output socket are kept as short as possible. A small

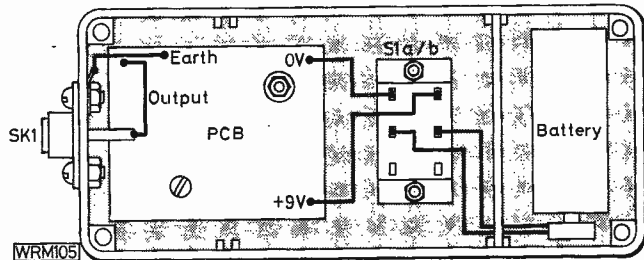


Fig. 3: Internal arrangement of components

★ components

Resistors

All $\frac{1}{4}$ W carbon 5%

56 Ω	1	R8
330 Ω	1	R7
470 Ω	2	R3, 6
2.2k Ω	1	R1
3.3k Ω	1	R5
5.6k Ω	1	R4
22k Ω	1	R2

Potentiometer

Miniature, horizontally-mounted pre-set

1k Ω 1 VR1 (Linear law)

Capacitors

Miniature polyester

10nF 2 C1, 2

100nF 1 C5

Miniature ceramic

1nF 2 C3, 4

Semiconductors

Diodes

2V7 1 ZD1 BZY88 series 2.7V Zener

Transistors

2N706 2 Tr1, 2 (Replace Tr2 with BFY90 for h.f. and v.h.f. version)

Miscellaneous

S1, d.p.d.t. slide switch; Diecast box, 120 x 60 x 44mm; SK1, coaxial socket; Stand-off pillars, 6BA (2); PP3 Battery connector. Printed circuit board


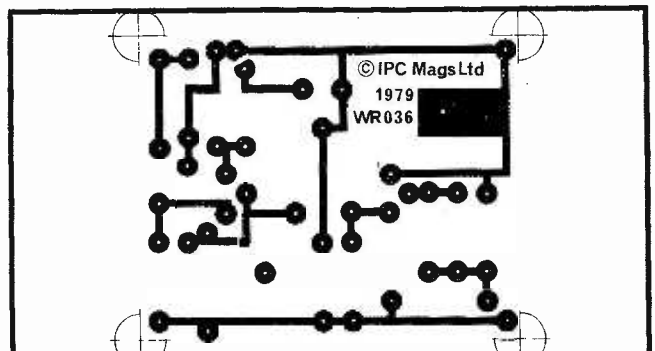


Fig. 4: Printed circuit board copper track pattern shown full size


Fig. 5: Component placement on p.c.b.

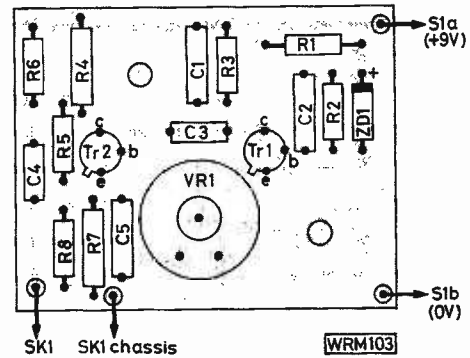

hole is made in the front panel of the box to provide access for the adjustment of VR1. Either a skeleton type or a knob type pre-set may be used. The latter will prove to be more satisfactory where frequent adjustments of output level are likely to be made. Care should be taken to ensure that the hole made in the case aligns correctly with the adjusting slot or shaft of the pre-set. Standard variable resistors are not recommended for use since they are not only too large but have considerable stray reactance which may impair the frequency response of the amplifier. The BFY90 is available in both TO18 and TO72 packages—the latter type should have pin 4 (case connection) clipped off before soldering the remaining connections to the board.

Testing

When the wiring of the noise generator has been completed, a thorough visual check should be made before connecting the battery. Connect the noise generator to the input of a receiver and check that an output is obtained. If the receiver has a signal strength meter this should show a steady indication; if no signal strength meter is fitted a 'rushing' sound should be heard from the loudspeaker. Adjustment of VR1 should cause a change in the noise level. If possible, a check should be made over a range of frequencies. If the receiver sensitivity is constant over a range of frequencies its signal strength reading (or audible output level with a.g.c. off) should remain constant as the receiver is tuned across its entire frequency coverage. Receiver alignment may be carried out using the receiver's signal strength meter in a conventional manner. The use of an a.f. voltmeter connected across the loudspeaker terminals as an output level indicator is strongly recommended when alignment is carried out on receivers not fitted with a signal strength meter.

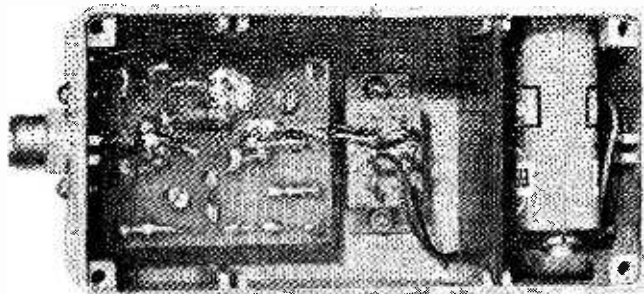

tone-burst generator

PHOENIX

Amongst the majority of would-be and newly-licensed amateurs there still seems to exist an air of uncertainty with regard to repeaters. This is quite apparent by the number of new 2m stations openly admitting "I'm recently licensed and don't fully understand repeater operation". This article looks at the principle of repeater working and suggests a suitable design for a toneburst generator with which to access them.

Operation via Repeaters

A repeater may be simply described as a remotely-operated transceiver which simultaneously transmits on one frequency and receives on another. Such a function is usually referred to as *duplex*, as opposed to *simplex*, when transmission and reception occur on the same channel but not at the same time. In the duplex mode, the repeater transmit and receive frequencies are well separated, the transmit channel being the higher of the two. This difference is referred to as the "shift" and is 600kHz in the case of 2m and 1600kHz at 70cms.

The amateur therefore would normally transmit on the repeater receive channel, which is known as the input. Some confusion arises here, especially when the term "reverse repeater" is used. This, as the name implies, refers to the amateur transmitting on the repeater **transmit** channel, effectively by-passing the facility. The function can be useful when calling a station known to be within point-to-point distance, and under normal circumstances you would transfer to one of the simplex channels when contact has been established. For obvious reasons you should not call a station in this mode unless you can hear him on the repeater input.

Table 1: 2m Repeater Channels

Channel	Frequency (Receive)	Frequency (Transmit)
R0	145.000	145.600
R1	145.025	145.625
R2	145.050	145.650
R3	145.075	145.675
R4	145.100	145.700
R5	145.125	145.725
R6	145.150	145.750
R7	145.175	145.775
R8	145.200	145.800
R9	145.225	145.825

Table 1 shows the frequency and channel allocations for duplex repeater operation. Not all of these are at present in use within the UK however, our own stations being between R3 and R7 inclusive.

Access to a repeater is gained by a short burst of tone (1750Hz) generated at the beginning of the transmission and lasting for 500ms typically. Some repeaters require this to be followed by several seconds of speech without loss of carrier, and this is quite difficult to arrange if all the switching is done manually. The device described in this article fulfils all these functions by one operation of the push-to-talk switch.

Most repeaters, with the notable exception of GB3LO (London), restrict the duration of transmission. After a pre-determined period a *time-out* occurs and the repeater releases, having first sent a series of "pips" to advise the receiving station of its intention.

When the input of the repeater senses the absence of a carrier, an advisory signal is sent, indicating that the station is ready to be re-accessed. Here it should be clearly understood that the terms "access" and "re-access" do not relate to the same function. Re-access involves the resetting of the timing mechanism immediately after the repeater has been used, whereas access is given to mean "starting from cold", as it were.

British repeaters vary considerably in the method by which re-access takes place. Some require a toneburst with or without speech to follow, others operate on receipt of speech alone whilst some require only to receive a carrier, whether modulated or not. Some very interesting information is given in the *International VHF-FM Guide*†, for those who would like to consider individual cases.

The Toneburst Module

Referring to the circuit of Fig. 1, we can see that the crystal oscillator operates at a frequency of 910kHz. The Schmitt trigger IC2a converts the waveform into a sharp-edged square wave which is fed to the twelve-stage ripple counter IC3 as the clock reference. This counter, in conjunction with other gates, divides the clock frequency by 520, thereby obtaining the required 1750Hz necessary. The output is routed via another Schmitt trigger IC2c into a 3-pole Butterworth filter, which produces a relatively pure sine wave.

† Available from J. Baldwin (G3UHK), 41 Castle Drive, Maidenhead, Berkshire (90p post free).

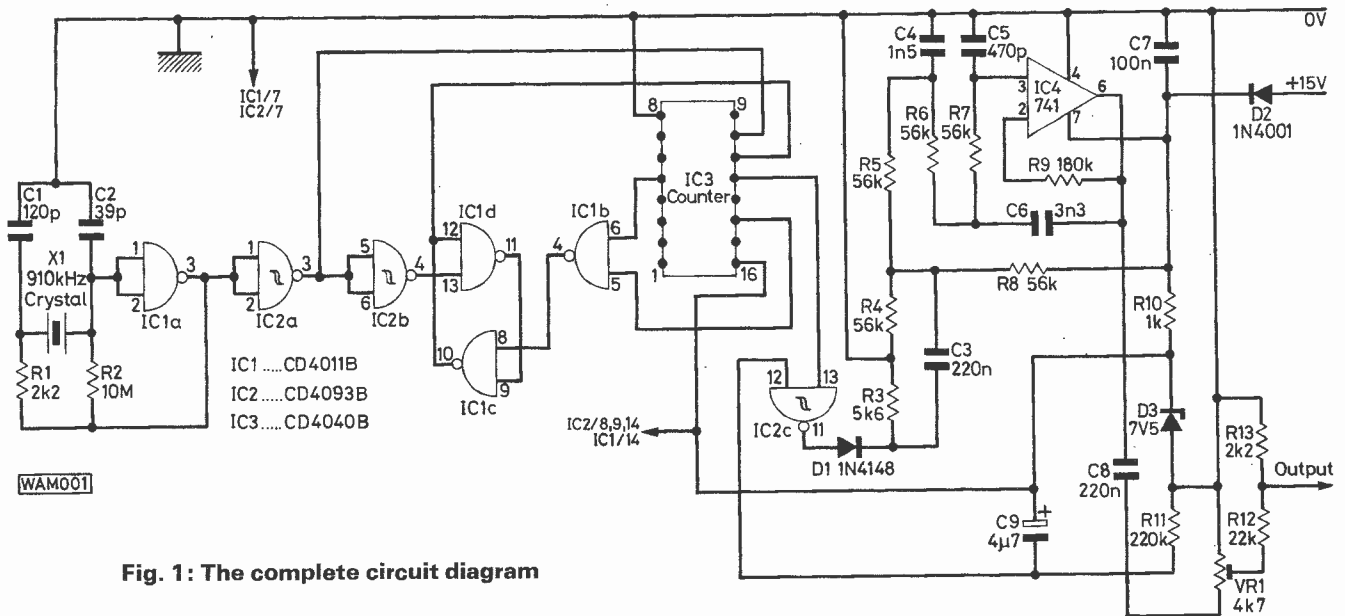


Fig. 1: The complete circuit diagram

Immediately power is applied, the capacitor C9 starts to charge through R10. As the potential rises towards that of the supply, a point is reached where IC2c changes state, effectively blocking the path of the 1750Hz signal. When this occurs, the system has to be re-set by disconnecting the power supply and consequently allowing the capacitor to discharge.

By installing the toneburst module in such a way that on pressing the microphone p.t.t. switch power is simultaneously applied to the transmitter, the access signal will be generated on the initiation of each "over" and the possibility of dropping carrier is eliminated. The provision of a switch in the power supply to the module permits its isolation when working simplex.

★ components

Resistors

1/4W 5%		
1kΩ	1	R10
2.2kΩ	2	R1, 13
5.6kΩ	1	R3
22kΩ	1	R12
56kΩ	5	R4, 5, 6, 7, 8
180kΩ	1	R9
220kΩ	1	R11
10MΩ	1	R2

Pre-set, horizontally mounted

4.7kΩ	1	VR1
-------	---	-----

Capacitors

Miniature ceramic plate

39pF	1	C2
120pF	1	C1

Miniature polystyrene

470pF	1	C5
1.5nF	1	C4
3.3nF	1	C6

Miniature polycarbonate

220nF	2	C3, 8
-------	---	-------

Ceramic disc

100nF	1	C7
-------	---	----

Tantalum, 16 volt 10% tubular, Axial leads

4.7µF	1	C9
-------	---	----

Semiconductors

Integrated circuits

CD4011B	1	IC1
CD4093B	1	IC2
CD4040B	1	IC3
741	1	IC4

Diodes

1N4148	1	D1
1N4001	1	D2
BZY88C7V5	1	D3

Miscellaneous

Crystal 910kHz 30pF HC6U. Available from C. P. Developments, 16 Hughendon Road, High Wycombe, Bucks; Printed circuit board.

Construction

The discrete components should be mounted initially, leaving the crystal and integrated circuits until last. Omit resistor R12 at this stage, otherwise it will have to be removed in order to test the board.

If you do not wish to use holders, leave IC1-3 until last. These devices are c.m.o.s. and so should be handled as infrequently as possible prior to installation. The techniques for soldering these components have been considered on many occasions within these columns and in other publications. These should be closely adhered to if damage is to be avoided from static charges. The crystal is also susceptible to damage from excessive heat. The best method of soldering this is to use a very hot iron and to complete the process as quickly as possible.

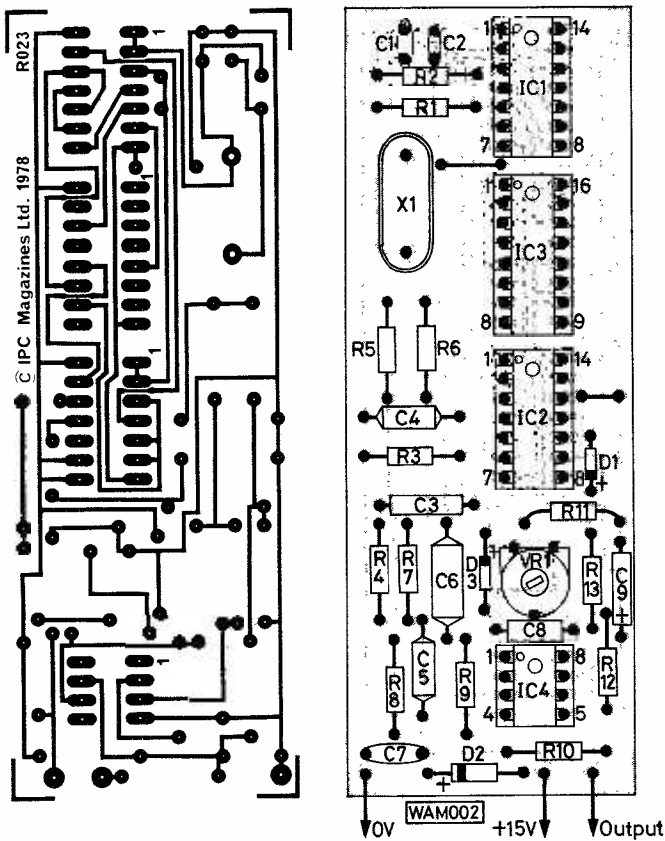


Fig. 2 (left): Copper track layout of the p.c.b. shown full size and (right) the component layout

The capacitor C9 is specially selected, and it has been found that only the type in the components list is suitable. Most tantalum beads have a tolerance of 20%, and these gave rise to problems in the prototypes. For this reason a tubular version with axial leads and a tolerance of 10% is required. Increasing the value of this device will lengthen the duration of the toneburst.

Testing the Board

Make certain that you have not fitted R12 before commencing. Now connect a small loudspeaker or pair of headphones between the slider of VR1 and earth, then temporarily short across C9 with a small piece of wire. Apply around 15 volts and you should hear a continuous 1750Hz tone. Disconnect, and remove the short across C9. Re-apply power, and the tone should occur for a period of approximately half a second. Should it happen that the burst is appreciably longer, then reduce the value of the capacitor slightly. Selection of the correct value proved to be the only variable in the prototypes. The final decision to use 4.7µF was taken only after exhaustive experimentation, which indicated that this value produced the most consistent results. Provided the burst duration falls between 540 and 650ms, no difficulties should be encountered.

After carrying out these procedures, don't forget to insert R12!

If you are installing the module into the Avon transmitter, the following information may be helpful. Connect a microphone to the transmitter, key the device and adjust VR1 on Avon Board One to obtain a clear and undistorted speech output. Do not attempt to set for maximum volume; this is not the function of the deviation control.

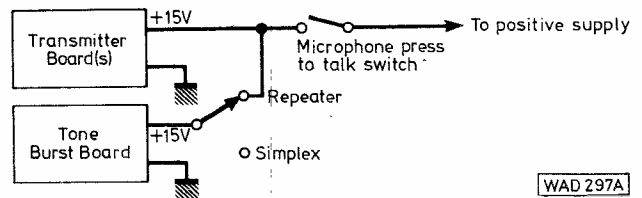


Fig. 3(a): The toneburst module fitted to a simple push-to-talk arrangement

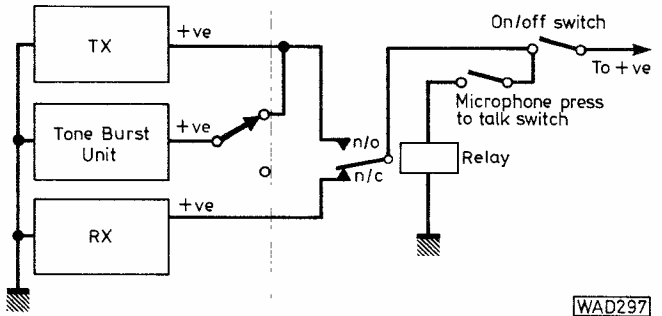


Fig. 3(b): Fitting the module into a high-power transmitter, where a keying relay is used

Too little deviation is preferable to an excess. Once adjusted, do not touch this control again, but alter VR1 on the toneburst module to give a level of tone slightly lower than that obtained with speech. If you are lucky enough to have access to an oscilloscope, the speech should be set for a maximum deviation of 5kHz and the toneburst limited to 3.5kHz.

Follow-up to the PW Avon

continued from page 48

100pF silver mica capacitor be connected from the input to earth, as close to the p.c.b. as possible, to provide the necessary decoupling.

Replace the p.a. board and the modifications are now complete. Retuned, the transmitter will produce about 9 watts of r.f. with a power supply of 12 volts, rising to around 20 watts for the original 24 volt supply.

Operating the microphone pressel switch with the "Access Repeater" facility enabled will automatically generate toneburst, thus providing the required conditions to open repeater stations.


The power supply featured in the September '78 issue of *PW* can easily be modified to handle the increased current drain, provided the transformer is capable of delivering it. Merely place another 0.47Ω 25 watt precision wirewound resistor in parallel with R2 (Fig. 1, p. 30, September '78 issue).

C8RBY TONE BURST KIT AS IN THIS ISSUE

910 KHz Xtal	2.16	4093	46p
3.3 F Tant	27p	4040	65p
4011	24p		

Resistors, capacitors diodes, trimpot £1.35 plus 25p post and packing OR all above for £5.00 inclusive. Prices include VAT.

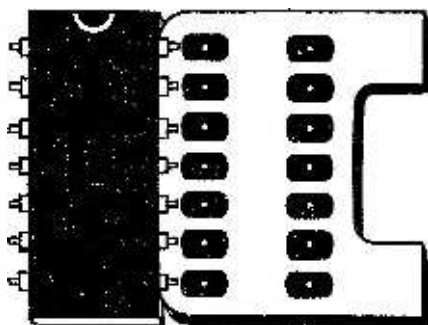**C. P. Developments, 16 Hughenden Road,
High Wycombe, Bucks. HP13 5DT.
Tel: (0494) 30043
ACCESS welcome by mail or telephone**



THOMSON-CSF TDE 1607

When using a small current (such as that from a t.t.l. or c.m.o.s. logic device) to control a much larger current in a load, it is possible to employ a simple transistor amplifier in some cases, whereas if a higher current gain is required a power Darlington device may be used as an amplifier. However, simple circuits employing such devices do not incorporate any means of limiting the current in the load so as to protect both the load and the amplifier device from possible damage. Also they do not incorporate any means of protecting the amplifier device if it should undergo an excessive temperature rise.

The TDE 1607 is a new integrated circuit from Thomson-CSF which can be used to overcome these problems. Basically it is a protected operational amplifier, being designed for fairly high currents and voltages, and is specifically intended for the control of the current in such loads as relays, lamps and stepping motors.

The TDE 1607 is essentially fail-proof in operation provided that the absolute maximum permissible supply voltage and input voltage (both 36V) are not exceeded. An external resistor can be incorporated in the circuit so as to limit the current in the load to any chosen value up to 0.5A (although the TDE 1607 has a maximum permissible output current of 1A). If the silicon chip in the device becomes too hot for safety, the internal circuit will automatically reduce the output current and thus prevent possible damage.

Connections

The TDE 1607 is supplied in a small circular metal transistor-type package with 6 leads. The connections are

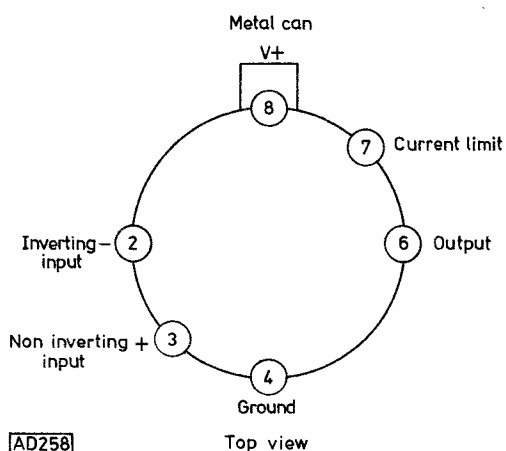


Fig. 1: Package outline and connections

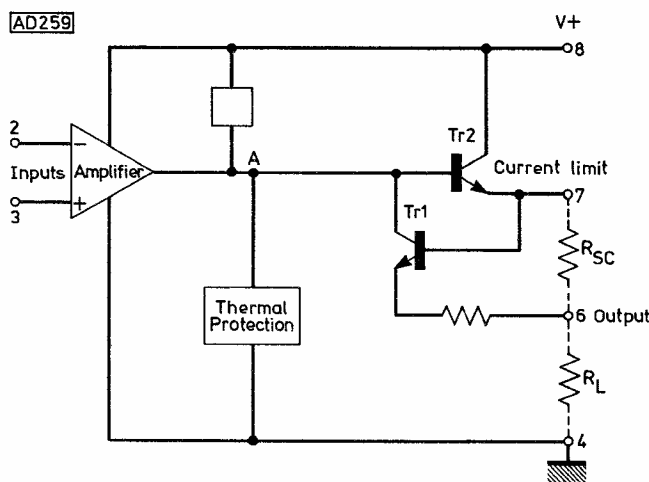


Fig. 2: Block diagram and "pass" transistors

shown in Fig. 1, but it must be remembered that this is a top view. This device can operate over the wide temperature range of -25°C to $+85^{\circ}\text{C}$.

The way in which the device operates can be understood using the block diagram of Fig. 2. When the non-inverting input to the amplifier (marked +) is at a voltage greater than that of the inverting input at pin 2 (marked -), the output voltage from the amplifier at point A in Fig. 2 will be relatively high (only a little below that of the V^+ supply line).

The output from the amplifier will then normally feed a current into the base of the transistor Tr2 (inside the TDE 1607) so that this transistor conducts and passes a current through the external resistor R_{sc} and through the load, R_L . The value of the current sensing resistor R_{sc} determines the maximum current which can flow in the output circuit. For example, if the value of R_{sc} is about 1.5Ω , a current of 0.5A will produce about 0.75V across R_{sc} and this voltage is applied between the base and emitter of the transistor Tr1. It is adequate to cause this transistor to commence to conduct, so instead of the current from A passing to the base of Tr2, it will pass to the collector of Tr1. Thus Tr2 will pass only just enough current to maintain a large enough voltage across R_{sc} to keep Tr1 conducting. The current passing through R_{sc} is equal to the load current, so the internal transistors Tr1 and Tr2 can be used to limit the load current.

If R_{sc} has the value of 1.5 ohms mentioned above, the load current will be limited to about 0.5A, whereas as R_{sc} is increased to 3 ohms, the maximum load current will be

about 0.25A. The writer found experimentally that still larger values of R_{SC} could be used, a value of 100Ω producing a maximum current of some 10mA. The exact value of the maximum current varies somewhat with the case temperature of the device, typical values being plotted in Fig. 3. Obviously the output current will never exceed the value of V^+ divided by $(R_L + R_{SC})$, since an adequate voltage is required to cause the current to flow.

The output current will flow only when the non-inverting input of the internal amplifier (pin 3) has a potential exceeding that of the inverting input (pin 2); if this condition is not satisfied, the device will be 'off' and little output current will flow. If the silicon chip of the device ever becomes too hot for safety, the thermal protection circuit of Fig. 2 passes current from point A to ground so that there is little bias current to feed the internal transistor Tr2; the output current therefore falls until the device cools. However, it is unwise to operate the device for an appreciable time at such a high temperature that the thermal protection circuit is in operation, since such high temperature operation can tend to impair device reliability and certainly tends to produce surface defects on the chip. It should rather be regarded as a safety circuit which is not normally used.

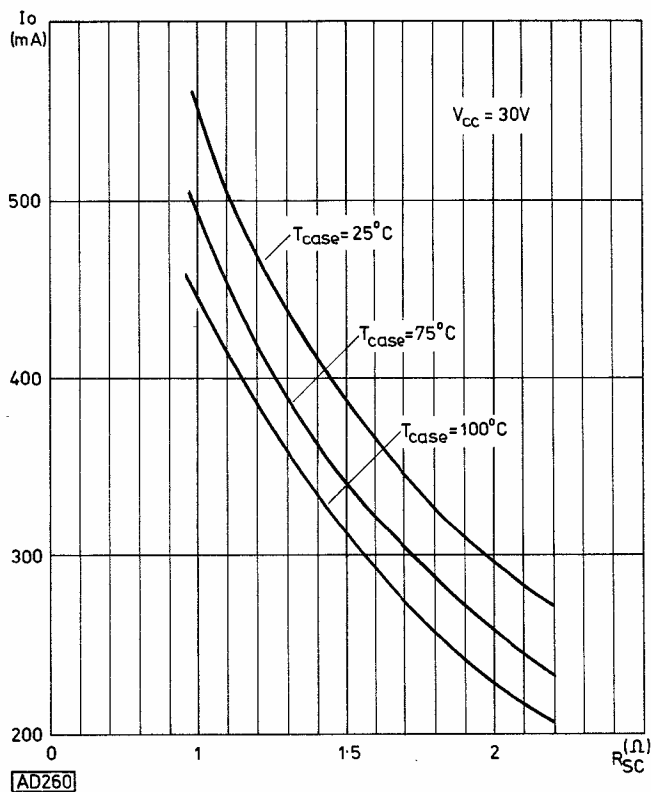


Fig. 3: Typical output current plotted against case temperature

Power Supply

It is recommended that TDE 1607 device is fed from a power supply of between 10V and 30V; it is, of course, possible to use $\pm 15V$ balanced supplies if desired. The supply current is typically only 3mA (maximum 5mA for any TDE 1607 device) from a 24V supply, when the output current is zero.


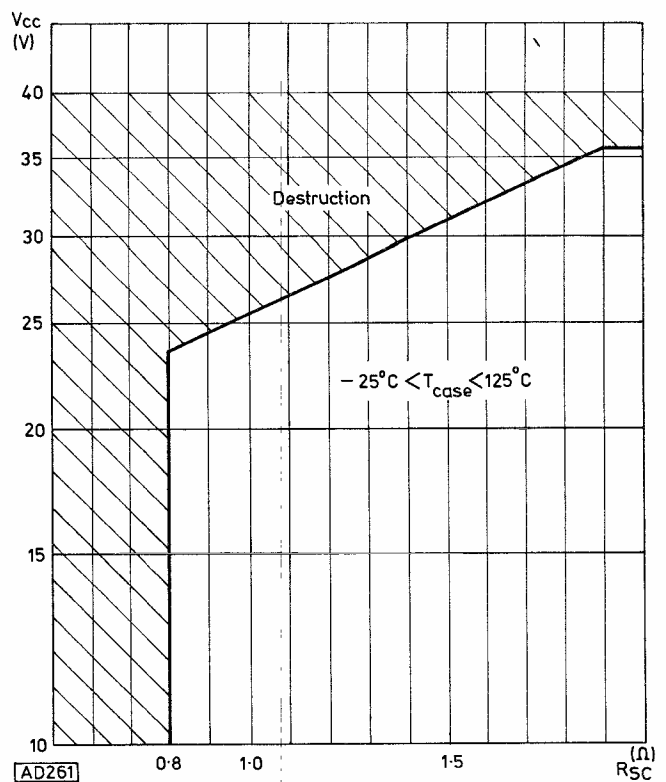


Fig. 4: Graph showing safe operating area

When the output voltage from the device is low, ideally no output current should flow and the output voltage should be zero. In practice, an output leakage current of up to 100μA can flow through the load at a junction temperature of 20°C or up to 500μA at a temperature of 85°C, whilst the output voltage may be a volt or so above the potential of the ground line. Similarly, when the output voltage is in the high state, there may be a potential of up to 1.8V between the output and the positive supply line.

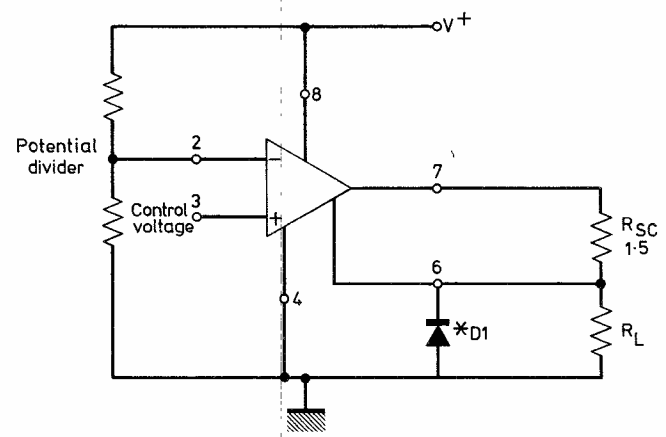The input currents required by the TDE 1067 are quite small, typically 100nA (maximum 1.5μA). The input offset voltage at which switching from one state to the other occurs is typically 2mV (maximum 50mV) between the two inputs.



AD262 *D1: Required if inductive load used

Fig. 5: An application circuit of the device

In order to provide adequate protection for the device, the value of the resistor R_{sc} should be chosen so that one operates within the unshaded area of the graph of Fig. 4. For example, with supply volts of up to 24V the value of R_{sc} should not be less than 0.8Ω so that the output current is never allowed to exceed about 1A. Obviously there is no objection to the use of larger values of R_{sc} where a smaller output current is adequate for the application concerned.

Typical Circuits

A typical application circuit for the TDE 1067 is shown in Fig. 5. The inverting input is biased by the potential divider to the desired value; a load current flows when the potential of pin 3 exceeds that of pin 2.

The diode D1 is required only if the load is inductive, such as a relay. When the current ceases to flow through the relay or other inductive load, a short transient reverse voltage can be developed across the relay coil. The diode is used to short this transient voltage to ground, since transients can damage the TDE 1067 device.

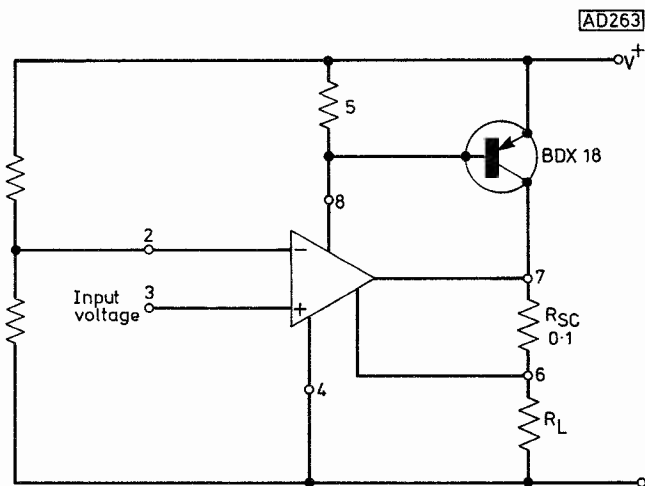


Fig. 6: Extension of the Fig. 5 circuit providing higher output current

5A Output

To provide a higher current than the TDE 1067 can itself supply, the circuit of Fig. 6 may be used in which an extra *pnp* power transistor fitted to a heat sink is used with the TDE 1067. Current limiting is again provided by the resistor R_{sc} , but the value of this component is much smaller owing to the higher current passing through it. Such small resistors are conveniently made from a length of resistance wire wound around a high wattage resistor of much higher value.

Conclusion

The TDE 1067 is a versatile device which can be operated by very low currents to its inputs. When used correctly in circuits, it is almost impossible to damage the device even if the output is short-circuited to ground. At the time of writing the price is £2.99 (including VAT) plus £0.20 for packing and postage from Phoenix Electronics Ltd, 46 Osborne Road, Southsea, Hants PO5 3LT.

KINDLY NOTE!

Car Radio LW Converter, December 1978.

The MVAM115 varicap diodes are shown on the circuit diagram but omitted from the components list. They are available from Ambit International, Gresham Rd., Brentwood, Essex.

Breadboards Supplement, December 1978.

On the 5V regulated supply (p. 2 of supplement), D1 is shown incorrectly. The configuration should be identical to that of D2.

Digital Door Chimes, December 1978.

In the audio amplifier section in Fig. 1, Tr3 (BC160) is shown inverted. The emitters of Tr2 and Tr3 should be linked. The collector of Tr3 goes to chassis.

Sandbanks Metal Detector, January 1979.

C17, 18, 19, and 20 are incorrectly shown in the components list (p. 50) as 10nF. These should all be 1nF, as correctly shown on the circuit diagram on p. 49. In the circuit diagram, Fig. 2, diode 3 should be reversed in polarity.

PW "Purbeck" Oscilloscope

Some readers seem to have misunderstood the information given in the "Follow-up" article (p. 55 January 1979) regarding the mains transformer.

Due to an unfortunate combination of circumstances, the differing characteristics of the transformers supplied by Watford Electronics with their PW "Purbeck" kits were not picked up by the author when incorporating the sample transformer in the original PW "Purbeck" oscilloscope. This oscilloscope and transformer have been in daily use now for many months, but two changes have proved necessary as follows.

If you are using one of the original Watford Electronics transformers then, as stated in the follow-up article, all that need be done is to replace R103 by a wire shorting link, and to reduce the value of R101 to around 120Ω (5W wire-wound), or better still, replace R101 by a wire shorting link. This provides a greater margin for low mains voltage. **It is NOT necessary to change the transformer.**

Don't forget to check, as stated previously, that the X and Y Boards draw 20mA and 30mA respectively from the $\pm 150V$ stabilised supply.

Please note that, when adjusting the input attenuator trimmers (C3-C10), a metal-bladed screwdriver is not suitable. An insulated coil-core adjuster should be used, and the hand held well clear to reduce stray capacitance effects.

AUDIO MODULES

1 Stereo Cassette Deck N999

Complete with electronics uses:— music centres, disco consols, tape editing etc. Freq resp 63Hz-10kHz WOW: 0-15% FLUTTER 0-18% channel: separation 55dB. Electronic speed control. ALC Mic and line inputs. JAPANESE Manufacture — requires 12V DC. **£23.95**



2 Preamp Amp — PSU Wimborne 11W per channel

Four rotary controls. Vol Bass Treb Bal. 2xPSUs for RF Board — cassette deck, LM 387 preamp IC driver. TIP 31+TIP 32 Output Pairs. Special price includes transformer **£16.95** (October 1978 PW)



3 AMP 041

8 watt RMS per channel amp+preamp supplied with pots. Fully complementary requires 28V DC. Price complete **£6.99**



4 AMP 020

Stereo power amp 30W RMS per channel. Class AB1 TIP 34AxTIP 33A. 16 Transistor circuit Fre resp 15Hz-18kHz — 1dB. **£7.99**



5 Matching HiFi Preamplifier

Four rotary controls — Vol, Bal, Treb, Bass. Treble 14dB Bass 14dB facility for loudness control **£6.99**



RF MODULES

6 Surplus RF Board 020

Complete MW/LW/FM/MPX Tuner uses 3 stage FET front end 2 ceramic filters 3089E — 1310 Decoder. AM section built around 3132E. 2 stage tuning comes complete with 4 way switch — ferrite rod aerial — **£9.99**



7 RF 030


Improved version of above extra gain stage imposed S/N ratio and 1.5uV sensitivity for 26dB S/N way selector switch AFC stereo/mono switching — 2 additional inputs **£19.95**

8 RF 020

MW/LW/FM/MPX varicap tuned RF board as per 78 Nov/Dec PW Dual gate MOSFET front end. 2x1F gain stages 3189 Deviation mute, interstation mute, MPX filters. Stab PSU 1uV sensitivity and 75dB S/N ratio. AM Section also varicap tuned HA1197 excellent performance. Special price **£28.95**

9 VT01

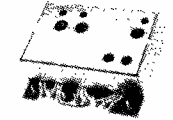108-150MHz MOSFET front end 26dB gain 10-7MHz 1F output. Covers 2 metres. Amateurs. Aircraft etc. **£7.99**



10 IF15

Matching IF Strip double conversion 10-7MHz/470kHz AM/NB FM excellent performance **£12.95**

We have all parts in stock for the Wimborne Music Centre — parts for amps/tuner amps and music centres up to 25 Watts per channel. We stock all hardware and trim to give units a professional finish. Front panels, meters, knobs, sockets, etc.

All prices include VAT paid P £1 per item. Max £2 for combined order.
All models supplied with full data. **3 YEAR GUARANTEE** 7 day delivery.
E.S.E., RAILWAY HOUSE, HARDHAM CROSSING, PULBOROUGH, SUSSEX.

Marshall's

Electronics



A. Marshall (London) Ltd., Dept: PW Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 0805 Retail Sales
London: 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Road, W2. Tel: 01-723 4242.
Glasgow: 85 West Regent Street, G2 2GD. Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, BS16 2LX. Tel: 0272 654201

2N929	0-37	2N3417	0-25	2N4062	0-20	2N5245	0-37	AF106	0-80	8C182L	0-15	AY-3-8500	6-50	CA3051	1-83	LM340T5	0-83	LM741C	0-70	LM7805KC	1-75	SN76013N	1-50
2N930	0-37	2N3439	0-35	2N4121	0-27	2N5248	0-44	AF109	0-22	8C183A	0-17	CA3000	3-30	CA3052	1-78	LM340T12	0-83	LM741C.8	0-30	LM7812KC	1-75	SN76012ND	1-30
2N1131	0-32	2N3441	0-82	2N4122	0-27	2N5293	0-44	AF114	0-70	8C183LA	0-15	CA3001	4-25	CA3053	0-77	LM340T15	0-83	LM741C7A	0-30	LM7815KC	1-75	SN76018KE	1-60
2N1303	0-36	2N3442	1-45	2N4123	0-19	2N5294	0-84	AF115	0-70	AC194	0-12	CA3002	3-30	CA3054	1-10	LM340T24	0-83	LM747CN	0-99	LM7824KC	1-75	SN76023N	1-50
2N1306	0-30	2N3555	0-25	2N4124	0-13	2N5401	0-66	AF116	0-70	8C184L	0-15	CA3005	2-50	CA3059	2-10	LM341P5	0-80	LM748-8	0-50	LM7805ZC	0-30	SN76023N	1-50
2N1501	0-30	2N3556	0-25	2N4125	0-18	2N5416	0-69	AF24	0-70	8C205	0-12	CA3006	4-80	CA3062	3-75	LM341P12	0-80	LM748-14	0-50	LM7811ZC	0-30	SN76023N	1-30
2N1613	0-30	2N3557	0-25	2N4126	0-18	2N5447	0-16	AF20B	0-70	8C212A	0-15	CA3007	4-15	CA3064	1-10	LM341P15	0-80	LM716	1-00	LM78115C	0-30	SN76033N	2-35
2N1637	0-77	2N3638	0-17	2N4235	1-35	2N5448	0-16	AF20U	1-30	8C213B	0-15	CA3008	2-55	CA3065	1-10	LM341P24	0-80	LM900	0-50	LM78224CZ	0-30	SN76115N	1-65
2N1890	0-30	2N3639	0-30	2N4236	1-05	2N5449	0-20	AF201	1-30	8C2138	0-15	CA3009	1-10	CA3066	3-80	LM348N	0-95	LM911	0-50	MC1035F	1-80	SN76116N	1-60
2N1893	0-30	2N3644	0-40	2N4237	1-05	2N5457	0-35	AF20B	0-70	8C213LA	0-12	CA3013	1-85	CA3070	1-80	LM358N	0-80	LM921	0-50	MC1327P	1-70	SN76131N	1-30
2N1991	1-10	2N3662	0-25	2N4237	1-05	2N5458	0-35	AF24	1-25	8C214	0-12	CA3014	2-20	CA3071	1-80	LM360N	0-60	LM1303N	1-15	MC1330P	1-10	SN76228N	1-68
2N2193	0-50	2N3663	0-29	2N4240	1-70	2N5555	0-85	AF27E	0-80	8C214L	0-14	CA3018	0-75	CA3072	1-80	LM370N	3-30	LM1304N	1-52	MC1332P	1-70	SN76227N	1-30
2N2194	0-42	2N3702	0-14	2N4250	0-26	2N5558	0-85	AF28E	0-85	8C237B	0-11	CA3018A	1-10	CA3075	1-70	LM371H	2-35	LM1307N	1-22	MC1435G	3-85	SN76228N	1-55
2N2217	0-55	2N3703	0-14	2N4266	0-32	2N5612	0-44	AF28H	1-30	8C238B	0-13	CA3020	2-20	CA3078	2-12	LM3737N	2-40	LM1308N	1-15	MC1456R	2-20	SN76531N	0-82
2N2218	0-35	2N3704	0-14	2N4284	0-38	2N6123	0-48	AF28H	0-70	8C239C	0-17	CA3022	2-20	CA3080	1-85	LM3737N	2-40	LM1309N	1-22	MC1456R	2-20	SN76532N	1-55
2N2219	0-38	2N3705	0-14	2N4286	0-32	2N6124	0-45	AF28H	0-70	8C256A	0-29	CA3020A	2-50	CA3080	1-85	LM374N	3-35	LM1310N	2-10	MC1456R	2-20	SN76533N	1-30
2N2221	0-25	2N3706	0-14	2N4287	0-22	2N6125	0-47	AF28H	0-70	8C257A	0-18	CA3021	2-40	CA3080A	2-10	LM377N	1-80	LM1311N	1-30	MC1456R	2-20	SN76544N	1-60
2N2222	0-25	2N3707	0-14	2N4288	0-22	2N6289	0-29	AF28H	0-70	8C258B	0-24	CA3022	2-20	CA3086	0-50	LM377N	2-40	LM1311N	1-30	MC1456R	2-20	SN76545N	1-60
2N2270	0-48	2N3708	0-12	2N4292	0-27	2S702	3-38	AF28H	0-70	8C2598	0-24	CA3023	2-20	CA3086	0-50	LM378N	1-80	LM1458N	0-45	MC1458R	3-30	SN76546N	1-58
2N2388	0-27	2N3709	0-12	2N4302	0-31	2S703	3-35	AF28H	0-70	8C261A	0-23	CA3026	0-96	CA3088F	1-87	LM378S	4-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2389	0-27	2N3710	0-12	2N4303	0-31	40232	0-56	AF28H	0-70	8C262B	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2483	0-30	2N3712	1-39	2N4401	0-29	40311	0-65	AF28H	0-70	8C263B	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2613	0-30	2N3714	1-55	2N4402	0-29	40316	0-81	AF28H	0-70	8C264B	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2646	0-38	2N3715	1-55	2N4403	0-29	40383	1-45	AF28H	0-70	8C265A	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2848	1-18	2N3716	1-70	2N4403	0-29	40389	0-79	AF28H	0-70	8C266A	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2904	0-28	2N3794	0-21	2N4822	0-63	40408	0-62	AF28H	0-70	8C268C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2905	0-31	2N3819	0-36	2N4870L	0-58	40440	0-78	AF28H	0-70	8C269C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2906	0-24	2N3820	0-39	2N4871L	0-58	40512	1-70	AF28H	0-70	8C270C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2907	0-24	2N3821	0-95	2N4872	1-59	40596	0-87	AF28H	0-70	8C271C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2923	0-17	2N3822	0-95	2N4873	1-59	40596	0-87	AF28H	0-70	8C272C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2924	0-17	2N3823	0-95	2N4874	1-59	40596	0-87	AF28H	0-70	8C273C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N2925	0-19	2N3824	0-95	2N4875	1-59	40596	0-87	AF28H	0-70	8C274C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3011	0-37	2N3855A	0-19	2N4904	1-75	40617	0-48	AF28H	0-70	8C275C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3020	0-75	2N3855A	0-20	2N4905	1-40	40617	0-48	AF28H	0-70	8C276C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3053	0-25	2N3859A	0-22	2N4920	0-83	40617	0-48	AF28H	0-70	8C277C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3054	0-72	2N3860	0-18	2N5086	0-30	40617	0-48	AF28H	0-70	8C278C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3055	0-75	2N3866	1-98	2N5087	0-30	40617	0-48	AF28H	0-70	8C279C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3108	0-75	2N4801	0-30	2N5088	0-30	40617	0-48	AF28H	0-70	8C280C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3133	0-50	2N5904	0-18	2N5089	0-30	40617	0-48	AF28H	0-70	8C281C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3242	0-64	2N5905	0-18	2N5129	0-62	40617	0-48	AF28H	0-70	8C282C	0-24	CA3028A	0-96	CA3088F	1-87	LM380N8	0-25	LM1468N	1-87	MC1458R	3-30	SN76552-2	0-57
2N3250	0-35	2N5906	0																				

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% Telephone 6743

OA2	1.20	6AM8A	.70	6F24	1.00	7F8	2.00	12SR7	1.00	35Z4GT	70
OB2	.50	6AN8	.78	6F25	1.00	7H7	1.00	13D8	2.00	35Z5GT1.00	
OC4	.50	6AO5	.85	6F26	.50	7R7	2.00	14H7	1.00	43	2.00
OCZ	.75	6A08	.50	6F28	.50	7Y7	2.00	14ST	1.00	50B5	1.00
IA3	.60	6AR5	1.05	6F32	1.00	7Y4	.80	14T5	1.00	50C5	.75
IA3GT	.55	6ASTG	1.50	6G6G	1.00	7Z4	.80	19AQ5	.65	50CD6G	
IA7GT	1.00	6AT6	.75	6G8A	.80	8D2	.50	19BG6G		4.00	
IB3GT	.65	6AU6	.62	5GK5	.75	8D8	.55		1.00	50EH5	.85
IC2	1.00	6AV6	.75	6K6	2.00	9BW6	1.00	50L6GT1.00		6.00	
ID5	1.00	6AWSA1.15		6CU7	1.00	9D7	1.00	19H	1.00	66KU	1.00
IG6GT	1.00	6AW5GT	.50	6H6GT	.50	9B8	.45	3Y3	.50	72	.70
IH5GT	1.00	6BR6	.75	6J5GT	.80	10C2	1.00	20D1	.70	77	.75
IL4	.30	6BA6	.65	6J6	.50	10C14	.65	20D4	2.50	85A2	1.75
ILD5	1.00	6B8C	1.00	6J7G	.50	10D1	1.00	20F2	.85	85A3	2.00
ILNS	1.00	6BE6	.70	6J7M	.75	10D7	1.50	20L1	1.20	90C1	1.50
IN5GT	1.00	6BG6G	1.00	6J8A	1.00	10F3	1.50	20P1	1.00	108G1	.50
IR5	.50	6BY7	1.00	6K7C	.50	10F9	1.00	20P3	1.00	150C2	2.00
IS4	.40	6B16	1.10	6K8G	.50	10F18	.75	20P4	1.00	21SSG	1.00
IS5	.40	6BK7A	1.00	6K8GT	.55	10L14	.55	20P5	1.50	807	1.10
IT4	.40	6BN8	1.50	6L1	2.50	10LD11	1.50	25A6G	1.50	956	.55
IU4	.70	6BO5	.50	6L2	1.00	10LD12	.60	25L6G	1.00	1625	2.50
IU5	.85	6B07A	1.40	6L7	.50	10PL12	.75	25Y5	1.00	1821	1.50
2K5	1.00	6BR7	2.00	6L8	1.70	10P13	1.00	25Y5G	1.00	5687	2.00
2X2	1.00	6BR8	1.25	6L9	2.00	10P14	3.00	25Z4G	.75	5702	1.20
3A4	.60	6BW6	3.75	6LD12	.50	12A6	1.00	25Z5	1.00	5763	3.65
3B7	1.00	6BW7	1.00	6LD20	1.00	12AC6	.80	25Z6G	1.00	6057	2.00
3D6	.40	6BX6	.45	6N7GT	.75	12AD6	.80	28D7	2.00	6060	2.00
3Q4	.80	6BY7	1.00	6G1A	.50	12A7	.85	30A5	1.50	6067	2.00
3Q5GT	1.00	6BZ6	1.50	6P15	.50	12AT6	.50	30C1	.80	6146	4.70
3S4	.65	6C4	.50	6Q7G	.75	12AT7	.52	30C15	1.00	6211	2.00
3V4	1.00	6C6	.50	6Q7GT	.75	12AU6	.60	30C17	1.00	6463	2.00
4CB6	1.00	6C9	2.00	6Q7M	.75	12AU7	.62	30C18	1.25	6550A	6.75
4GK	1.00	6C0	1.00	6R7C	1.00	12AV6	.80	30F5	1.00	7025	2.00
4CG8	1.00	6AX6A	.65	6SA7	.75	12AX7	.62	30FL2	1.20	7193	.60
5R4GY	1.20	6C12	.55	6SC7GT.100		12BA6	.60	30L1	.40	7475	2.00
5T4	2.00	6CD6G	4.00	6SG7	.80	12BE6	.85	30L15	1.00	9002	.75
5U4G	1.00	6C8A	.90	6SH7	.80	12BH7	.75	30L17	1.00	9066	.75
5V4G	1.00	6CL7	.75	6S7	.80	12E	3.50	30P4MR		A3042	6.00
5Y3GT	.65	6CL8A	1.40	6L8A	1.50	12G7	.75	30P11	1.50	AC2PE1.20	
5Z3	1.50	6CM7	1.00	6SK7GT.70		12J7GT	.75	30P12	1.00	AC2PE2.00	
5Z4G	.75	6CS6	.75	6SL7G	2.00	12K5	1.50	30P19		1.50	
5Z4GT	1.00	6CU5	1.00	6SN7G	2.00	12K7GT	.60	30P4	1.00	AC2PEN/	
6/30L2	1.00	6D3	1.00	6S07	.80	12K8	.75	30P16	.50	DD	1.50
6A8G	1.40	6DE7	1.00	6G4GT	1.00	12Q7GT	.60	30P18	.65	AC6PEN	
6A8G	1.40	6E7A	.85	6AC7	.85	12PL2	.50	30P1	2.00		
6A8G	.65	6EW6	.85	6UR	.55	12SC7	.55	30PL12	.65	AC/P4	1.50
6A8G	.75	6E8	2.00	6VG	.60	12SG7	.50	30PL13	1.30	ACTH1	1.50
6A16	1.00	6F1	1.00	6X4	.95	12SH7	.50	30PL14	1.50	AL60	2.00
6A16	.70	6F6G	.80	6X5GT	.60	12S7	.60	30PL15	1.30	ARP3	.60
6A18	.55	6F12	.50	6YG	1.00	12SK7	.60	35A3	1.00	ATP4	.50
6A18	.55	6F12	.50	6Y7G	2.00	12SN7G	.60	35A1	1.00	AZ1	1.00
6A16	1.00	6F15	.85	7A7	1.50	2.00	35D5	1.00	AZ31	1.10	
6A18	.50	6F18	1.00	7B6	1.50	12SQ7	.80	35L6GT	.85	AZ41	.60
6A18	.50	6F18	1.00	7B7	1.00	12SQ7GT	.55	35W4	.60	B36	2.00
6AM6	.70	6F23	1.00	7D6	2.00	.80	35Z3	1.00	B719	.50	

B729	1.00	EB34	.50	EF92	.75	HL42DD		PEN45	1.50	UF41	1.10	AA120	.18	BF180	.35
BL63	2.00	EB91	.40	EF93	.65			PEN45DD		UF80	.50	AA129	.18	BF181	.47
CV33	2.00	EC41	.50	EF94	.62	HN309	2.00	UF85	1.50	UF85	.50	AA213	.21	BF185	.47
CV61	.60	EC81	1.00	EF95	.50	HR2	1.00	UF89	.55	UF89	.55	AC107	.18	BFY50	.26
CV61	.60	EC90	.75	EF97	.90	HR2A1.00		PEN453DD		UL8	1.00	AC126	.18	BFY51	.23
CV988	.25	EB90	.75	EF98	.90	KT2	1.00	UL84	.90	UL84	.90	AC126	.18	BFY52	.23
CY1C	1.00	EF80	1.00	EF183	.55	K78	3.00	PENDD4020		UM80	1.00	AC127	.20	BY100	.21
CY31	1.00	EF83	1.00	EF184	.55	KT32	1.00	UM84	1.50	UM84	1.50	AC128	.20	BY101	.21
D1	.50	EB21	.50	EF804	6.25	KT41	1.50	PFL2001.35		UR150	1.00	AC132	.23	BY116	.21
D63	.50	EBL12	2.00	EK90	.60	PL33	.80	UL12	.50	UL12	.50	AC136	.20	BY126	.18
DAC321.1.00		EC52	1.00	EK90	.70	KT63	.80	UL36	1.00	UY41	.75	AC137	.30	BY127	.21
DAC91.40		EC53	1.50	EL32	1.00	KT66	3.50	UL81	.65	UY42	.75	AC137	.30	BY128	.21
DAF96	1.00	EC54	1.50	EL34	2.50	KT71	1.00	PL81A	.75	UY85	.70	AC165	.30	BY129	.30
DC90	1.00	EC86	1.00	EL37	3.00	KT81	2.50	PL82	.50	U10	1.50	AC166	.30	BY130	.30
DD4	1.00	EC84	1.00	EL41	1.00	KT88	6.75	PL83	.50	U12/14	1.50	AC168	.44	BY131	.30
DF33	1.00	EC90	.50	EL81	.60	PC3	.80	PL84	.65	U18	2.00	AC172	.65	FSV14	.26
DF91	.40	EC92	1.00	EL83	1.00	LN119	.75	PL95	1.00	U19	1.00	AC177	.32	FSV41A	.26
DF92	.30	EC97	1.00	EL84	.50	LN309	2.00	PL504/500		U25	1.00	AC178	.35	OA9	.14
DL96	1.00	EC32	1.00	EL86	.80	LZ319	.80	U26	.90	AC19	.35	AC19	.35	OA7	.12
DH63	.75	EC33	2.00	EL90	.85	M8136	2.00	PL505	3.10	U33	2.00	AC20	.35	OA70	.18
DH76	.50	EC35	2.00	EL95	.95	M8137	2.00	PL508	1.85	U35	2.00	AC21	.35	OA71	.18
DH77	.75	EC40	1.25	EL360	2.50	M8162	2.00	PL519	3.10	U37	2.00	AC22	.35	OA73	.18
DH81	1.50	EC81	.52	EL506	2.50	M8195	3.00	PL519	3.75	U81	1.00	AC28	.35	OA79	.11
DK32	1.00	EC82	.62	EL509	2.50	MHL4	1.50	PT4D	1.50	U191	.50	AD140	.50	OA81	.11
DK40	1.50	EC83	.62	EM80	1.00	MHLD6		Y31	.50	U251	1.00	AD161	.53	OA85	.11
DK91	.50	EC84	.50	EM81	1.00			Y32/2	.50	U301	1.00	AF14	.30	OA90	.14
DK92	.70	EC84	1.00	EM82	1.00	MX40		N150	1.00	Y81	.60	U404	.60	OA91	.11
DL33	1.00	EC86	2.00	EM85	1.20	N308	1.50	Y82	.50	U801	1.00	AF121	.35	OA95	.11
DK96	1.00	EC88	.72	EM85	1.00	N709	.50	Y83	.60	U4020	1.00	AF124	.36	OC36	1.00
DL63	1.00	EC91	.50	EM87	1.45	N709	.50	Y88	1.12	VP23	1.00	AF180	.56	OC44	.35
DL82	1.50	EC189	1.00	EM8083		P61	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DL92	.65	EC204	1.00			PABC80	.45	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	EC21	1.00	EY51	8.00	P80	2.05	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DL96	1.00	EC80	.65	EY81	1.50	PC88	.80	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DM70	1.50	ECF82	.55	EY83	1.50	PC92	.85	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DM71	1.75	ECF86	.80	EY86	.75	PC95	1.00	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DW4	1.50	ECF85	2.00	EY88	1.00	PC97	.80	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF84	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF85	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF86	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF87	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF88	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF89	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF90	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF91	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14
DD27	1.00	ECF92	1.00	EY83	1.00	PC99	.75	Y88	1.12	VP41	1.00	AF186	.64	CC70	.14


PRODUCTION LINES

alan martin

Easy

Verospeed have announced the introduction of two "Zero Insertion Force" (AB 052) d.i.p. sockets, available in 16- and 24-way configurations. They are designed to eliminate mechanical damage to expensive integrated circuits during test, burn-in or programming operations. The i.c.s may be inserted or removed with zero force on the leads.

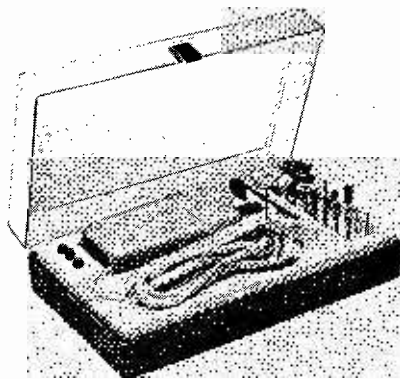When the lever is operated the socket exerts uniform force on the leads and compensates for varying lead thicknesses. They are priced at £5.36 and £7.10 respectively and are available from: *Verospeed, Barton Park Industrial Estate, Eastleigh, Hants SO5 5RR. Tel: (0703) 618525.*



Mini-drill

Recently introduced by Boss Industrial Mountings Ltd. is a mains drill plus accessory kit housed in a specially designed carrying/presentation case with transparent lid.

This small but powerful 220/240V a.c. BIMDRILL is supplied with 4 collets capable of accepting tools with shanks of 1mm, 2mm, 2.4mm and 0.125in diameter, and will readily drill brass, steel, aluminium and p.c.b.s.

Complete with spring-loaded on/off switch and a 2 metre long cable fitted with a 2-pin DIN plug, this BIMDRILL has a fully insulated, high impact, ABS body, weighs less than 250g and has an off load speed of approximately 7500 r.p.m.

The accessories include 20 assorted twist drills, mops, burrs, grinding wheels and mounted points, all individually and securely located within the 230 x 130 x 50mm case. Priced at £22.14 which includes VAT and P&P, the kit is available from: *Boss Industrial Mountings Ltd., Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU. Tel: 01-737 2383.*

Wire-wrapping


OK are probably the only company who produce wire-wrapping equipment specifically for the hobby market and their latest kit HW-K1 brings power wire-wrapping within economic reach of the home electronics enthusiast.

The main item in the kit is a newly designed battery-operated wire-wrapping gun, based on the design of the company's industrial units. It is for use with 0.6 x 0.6mm mini-wrap terminals and has a bit and sleeve to give modified wrap. The tool is also self indexing and has a back force device to prevent overwrapping.

It is powered by two NiCad batteries, the two batteries provided having a year's guarantee, and a mains-operated charger is included. Also in the kit is a handy 'pocket-sized' wire dispenser, containing 50ft of 0.25mm

wire. The other item is a hand tool which can strip wire, wrap and unwrap.

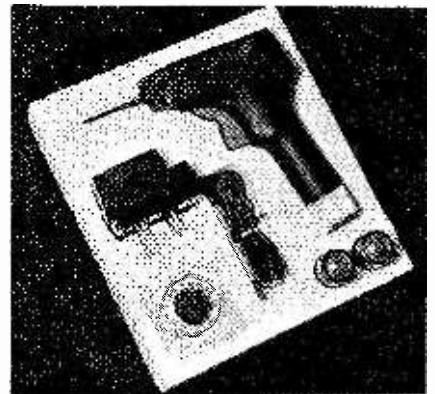Suggested retail price of the HW-K1 is £46.28 (inc. VAT and carriage). *OK Machine & Tool (UK) Ltd., 48a The Avenue, Southampton, Hants SO1 2SY. Tel: (0703) 38966/7.*




Drill-Mills


A circuit board without a track? A single Stahler drill-mill bit simultaneously drills holes and mills isolated pads in plain copper clad board to produce circuit boards without etching.

Drill-mills are designed to perform two separate functions—Isolated-pads drill-mill drills a hole and mills a circular moat leaving an electrically isolated copper pad. Insulated-spot drill-mill also drills a hole, but instead of milling a moat, it mills out a disc

from the copper cladding around the hole. The application is to provide clearance spots for ground-plane mounting of d.i.p. sockets, feed-through sockets, etc.

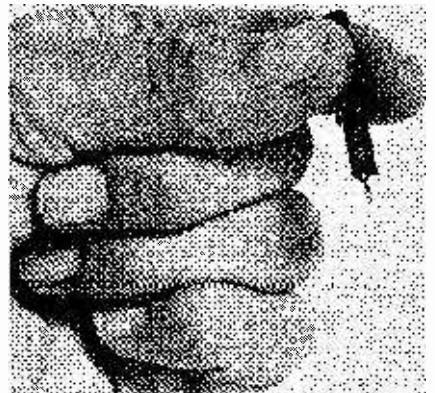In each case the tools comprise a replaceable high speed or carbide twist drill, either 0.0400in diameter or 0.0292in diameter. Each tool is also available in three pad milling sizes, 0.01in, 0.15in and 0.20in. Prices and a free catalogue are available from: *Carel Components, 40-44 The Broadway, London SW19 1SQ. Tel: 01-540 7186.*



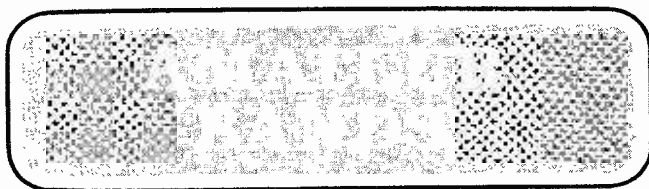

by Eric Dowdeswell G4AR

An interesting letter from **Les Light G3KDL** of Wembley, Middx, prompts me to write a few words for the reader who may be reading this column for the first time, perhaps after having had interest aroused elsewhere by contact with amateur radio.

Les received a letter from a young but obviously enthusiastic listener simply saying he had heard Les on the 80m band. Time and frequency were given, but little else, except some details of the receiver and aerial. Now, with the best will in the world, the report was not of much use at all, but Les, no doubt thinking back to his own early days in amateur radio, did send a QSL.

It is naturally very exciting for the newcomer to listen to amateurs for the first time especially when they realise the comparatively low power of the amateur, possibly being accustomed to the high power stuff on the BC bands. So off goes a report such as quoted above, with a request for a QSL, and probably no s.a.e!

With the advent of so much commercial gear and high-gain beam aerials, worldwide working by amateurs is commonplace and the excitement of working and then getting a QSL from some DX spot has waned somewhat. QSLing had decreased over the years to the extent that some amateurs don't even bother to have cards printed!

So the report from a listener, even if from the other side of the world, is of little use, generally speaking. It has got to be something unusual in the reception, or perhaps the other fellow is using very low power, before it is worth sending a report. I would counsel any beginner to first get the *Guide to Amateur Radio* from the RSGB to see what it is all about and to study, in particular, the section dealing with QSL matters.

The cost of QSL cards and postage today is enough to deter anyone from the hobby, so if you must send a report and request for a QSL, then make it easy for the other station by sending a s.a.e., or International Reply Coupons for overseas stations, and a report worthy of attention. Don't use these silly 5 x 3in envelopes! Send something a bit bigger. Having sent tens of thousands of QSLs out when I was ST2AR I rate the small envelope as the biggest annoyance of all!

Collecting QSLs can be fun, or used to be, but if there is any intention of going on to get a transmitting licence I would say the best policy is to spend the money on the receiver and associated gear rather than on QSLs and QSLing. You'll need every penny for the entrance fee for the RAE and the ticket itself. Then you can have your own QSL card, and receive them from stations you work, when they really mean something.

General Notes

An interesting note from **Owen Frame G4EIF** of Reading, Berks, on the mysterious H44LW mentioned in the December issue. Owen confirms that it is the Solomon Islands, as he has a QSL for an s.s.b. QSO. QTH is Box 19, Honiara. Owen added, that he used to be ST2WF in Khartoum in 1934 with the RAF, with 80W of c.w. from 12V accumulators! As he says: "happy days".

N. Eddy writes from Truro, Cornwall, for the first time although he has been reading *PW* for many years. He is a member of the Cornish ARC and sports an AR88 and BC348 with main interest on 14MHz. He also has a 62H receiver which he'd like to convert for 2m operation, if any reader can help him on mods. Write to: Little Tregadles, Laity Moor, Ponsanooth, Truro, Cornwall, all expenses paid of course. **John Bell BRS40279** in Melksham, Wilts, had "quite an amazing response" to his request for info on the AR88, particularly from **Michael Swain G8MMP**. John recently got hold of an Eddystone EC10 and, as an instructor to mentally handicapped people, he is going to try to teach elementary geography using the EC10 to demonstrate the reception of BC stations from various parts of the world. Apparently a fellow instructor has had some success this way.

Newcomer to the column **Derek Brabrook** of Laurgharne, Dyfed, Wales, has been using a domestic type Pye set for a couple of years or so, as it goes up to 26MHz. However, he finds his 223ft aerial "difficult and poor". I'm not surprised! It must be overloading the front end I imagine on the stronger signals, as I doubt whether there is any r.f. gain control, and selectivity can't be much good on such an old set. Instead of blaming the set, I suggest keeping the aerial and getting a more modern set!

In Oswestry, Salop, **David Wyatt** aged 14, has acquired a BC348 and promptly found KC4USX in Antarctica on 20m s.s.b. His main regret is that it does not go above 18MHz so he can't listen to the 10 and 15m bands. Again, a case for a converter. David offers to reply to any readers who'd like to write to him on the BC348 at 11 Prince Charles Road, Oswestry. You might be overwhelmed, as the receiver was a very popular one OM! David is also learning the code from records and threatens to send in c.w. reports before long. We are certainly short of them of late; hint, hint, to other readers!

Round the Bands

Very little in the way of logs this month, unless the season's rush on the PO has held them up in the pipeline. Could be everyone's waiting to see if Father Christmas has remembered them with a nice, shiny, new receiver! **Bernard Hughes** BRS25901, who hasn't written in for a while from Worcester, liked my article on receiver accessories and wants more! Drop a line to the Editor OM! In spite of a new 20m dipole Bernard found the most interesting DX on other bands with his Drake receiver. Latest QSL received of any note was from PYORO on St Peter & Paul Rocks. Worthy of note in his log were HS1ABD, STORK (!) VR3AH and XT2AT on the 10m band, KJ6BZ VP2DAY on 15m and HR1H MV, YS1RRD and 4W1BC on 40m, all s.s.b.

From Leigh-on-Sea, Essex, **Ian Marquis** A9140 keeps up the good work keeping his ears open on all the h.f. bands from Top to Ten with stuff like JA2EMU TR8BA on 80m, KL7IRT and ZL4AV on 40m, and FP8, FR7, PZ5, TU2, ZD8 and 7P8 on the 15m band, again all s.s.b.

A letter from **Bernie Crockford** ZS1BW mentions a contest for amateurs and SWLs to celebrate the 150th anniversary of the University of Cape Town, from Saturday Feb 17 to Sunday March 4, 1979, with operation from 0600 to 2000 on Sundays, and 0700 to 1000 and 1500 to 2000 weekdays. Likely frequencies are 7050, 14210, 21200, 28580, subject to QRM. Contact/log ZS1UCT plus two other ZS1s for award. Details from: Awards Manager ZS1MO, PO Box 5100, Cape Town 8000, Rep. of South Africa.

Club Activity

Much more from the clubs this month than individual readers! **RAIBC** secretary, Frances Wooley G3LWY, reports that the Strumech tower raffled at the Leicester Show was won by disabled member Shirley Hesketh G4HES! Shirley has already coached to success several blind girls at Chorleywood College, for the RAE. Club net 3750kHz s.s.b. 1000 Tuesdays and 1400 Wednesdays. The Cheshire Homes net is on 3650 to 3700kHz on Thursdays 1330.

The **Silverthorn RC** meets Fridays 1930 at Friday Hill House, Simmons Lane, Chingford, London E4, with details from: C. J. Hoare, at that address. Newsletter "Spurious" would be considerably improved with less large cartoons and virtually useless photographs, and more details of events to come! Surely you must have a winter programme chaps? Tars Talk, journal of the **Torbay ARS** reveals that G3LHJ will give a slide show on Feb 24, with the society's annual dinner being held on March 10. Meetings are held at Bath Lane, Torquay (rear of 94 Belgrave Road). Details from: F. Bolton G3VTQ, 2 Lower Coombe Road, Blindwell Park, Kingsteignton, Newton Abbot, Devon.

Stevenage and District ARS continues to meet at British Aerospace, Gunnels Wood Road, Stevenage, Herts on first and third Thursdays at 2015. March 1 sees talk by GB3HR repeater group on proposed 23cm and 10GHz beacon, while the 10th sees a visit to the VHF Convention at the Winning Post, Twickenham, Middx. AGM is on the 15th. The **West Kent ARS** report in for the first time with details of meetings held at 2000 at the Adult Education Centre, Tunbridge Wells, on Fridays, with a junk sale on March 2. On March 30 an interesting talk by Tony Tory on microprocessors in amateur radio. Informal chit-chat and code practice on Tuesdays at the Drill Hall, Victoria Road, says Brian Castle G4DYF, 6 Pinewood Avenue, Sevenoaks, Kent, who will supply details.

A new QTH for the **Swansea ARS** at the Sketty Park Sports and Social Club, Aneurin Way, Sketty Park, Swansea, on alternate Tuesdays, Feb 6 and 20 et seq. New members welcomed with open arms and a pint! Ring Peter Jones GW4GRI on Swansea 873986 for info or write to: 27 Gorwydd Road, Gowerton.

J. Bazley G3HCP, President of the RSGB, will be guest of honour at the 31st annual dinner of the **Sutton & Cheam RS**, taking place at the Woodstock Hotel on Saturday March 24. Details and tickets from: G. W. Brind G4CMU, 26 Grange Meadow, Banstead, Surrey.


Events to be held by the **Cheltenham AR Assoc** include: a constructors contest on Friday Feb 16 and a talk on i.c.s by Eric Hibbett G8LAY on Thursday March 1, with G4BSO and G3SSO discoursing on aerial planning permission on the 16th. Meetings at the Old Bakery, Chester Walk, Cheltenham at 2000. Info from: G. Martin G3IER, 88 Tennyson Road, Cheltenham, Glos.

Log Extracts (All s.s.b.)

B. Hughes:—10m HS1ABD KZODX P28NKV S79MC STORK VS6FI VR3AH XT2AT 15m D68AD KJ6BZ TJ2AP VP2DAY 40m HR1H MV HK5BCI YS1RRD ZP5LX 4W1BC

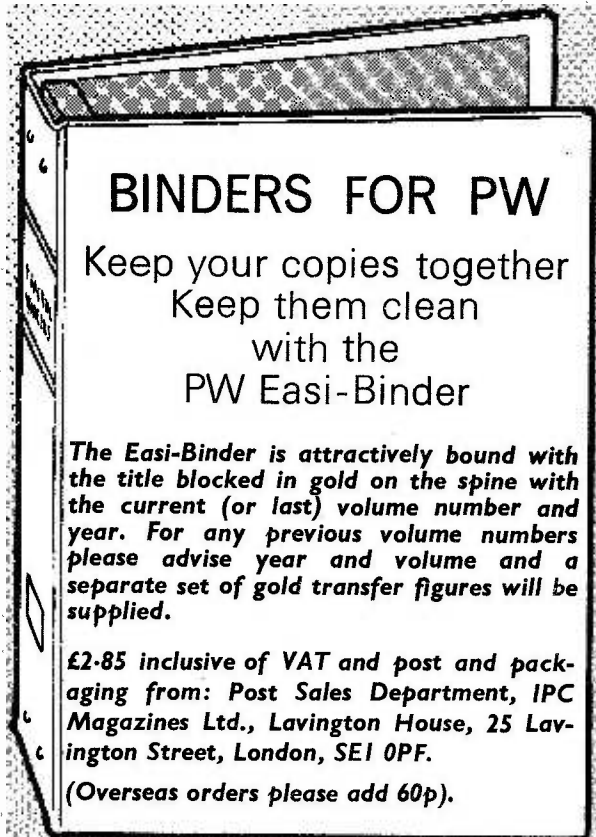I. Marquis:—10m HP1PJ VP2MBD ZL3AAX 15m CT2BB FP8DX FR7ZN PZ5AA TU2FH ZD8RG ZF2AG 7P8BC 20m VP2DAO ZE3JO 40m HK5DUS KL7IRT ZL4AV 80m FP8DX JA2EMU LX1ST TR8BA 9H1EU

Remember, all logs and letters by 15th of the month.




BINDERS FOR PW

Keep your copies together
Keep them clean
with the
PW Easi-Binder

The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.

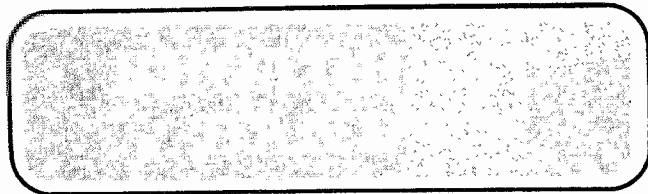£2.85 inclusive of VAT and post and packaging from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.
(Overseas orders please add 60p).



MEDIUM WAVE DX

by Charles Molloy G8BUS

It may be arguable, whether humility is the greatest virtue that a m.w. DXer should possess, but there is no doubt at all that selectivity is the attribute to look for in a receiver to be used for serious medium wave DXing. It is not that other factors such as sensitivity, stability, scale accuracy, freedom from overloading and cross-modulation, are unimportant. The present overcrowded state of the band, means that you should have the facility to wrinkle out DX that is close to a strong local station, and this means using a receiver that has good selectivity.

What is selectivity? It is the ability a receiver has to separate stations that are close to one another in the band. You can regard a receiver as a window into the frequency spectrum, the width of this window depending on the degree of selectivity. A narrow window means narrow (good) selectivity. It would be an easy matter, if all you had to do was to separate adjacent carriers, since a receiver with high selectivity would do the trick. Unfortunately the programme (modulation) requires space, the amount of space depending on the highest audio frequency. If it is 3kHz then a 6kHz bandwidth is required, i.e., 3kHz above and 3kHz below the carrier with the double sideband system currently in use. If bandwidth is reduced in order to reduce QRM then the audio range is reduced too, and in an extreme case speech becomes unintelligible.

How Selectivity is Measured

The handbook of a well-known receiver quotes the selectivity as 4kHz at -6dB and 18kHz at -40dB. What do these parameters mean? The first is the important one. 6dB is shorthand for 6 decibels and -6dB means "one half of the original value", so the signal at the sides of the 4kHz window is half that at the centre. Selectivity is invariably measured at the 6dB points. The statement 18kHz at -40dB is less important. It means simply that at 9kHz on either side of the carrier the signal will be 40dB down which is 1/100th of its original value. Ideally the signal would be zero at the sides of the window, but in practice it falls off gradually.

What to Look For

If you want to judge a receiver's ability to separate stations then look for the bandwidth at the 6dB points. It will be found under "Selectivity" in the handbook or specification. Sometimes it isn't mentioned at all so one can draw the appropriate conclusion. Occasionally on imported receivers the bandwidth is given as a plus or minus figure such as ± 2 kHz. Multiply by 2, as the real bandwidth is 4kHz! I recently studied a one-page "spec" for a receiver currently available and after some searching found Selectivity near the end. It was 4kHz at the 6dB points which is not very good for DXing. A few years ago I tried an experiment with CJON (now CJYQ) on 930kHz using a bandwidth of 2.4kHz. It could be heard easily between the Europeans on 926 and 935. When the bandwidth was in-

creased to 5kHz, CJON just disappeared, as the stations on either side spread out to meet each other.

My BRT400 communications receiver has a six-position selectivity switch which gives bandwidths of 0.5, 1.0, 2.0, 5.5, 9.0 and 13.0kHz at the 6dB points. Normally I use 2kHz when tuning around and this is increased to 5.5kHz or even 9kHz, QRM permitting, if I want to listen to the programme. A receiver with fixed selectivity must compromise between the needs of the DXer and the listener, and I would question whether such a receiver should be entitled to use the term "communications". A personal view that many will disagree with. It is a pity that the Q Multiplier, referred to recently by Eric Dowdeswell, has gone out of fashion as this simple device provides an easy means of obtaining variable selectivity, and it was incorporated in a number of moderately-priced receivers a few years ago.

If you do have a receiver with narrow selectivity then it is possible to use this facility and still hear the modulation. If the programme quality deteriorates as selectivity is increased, then detune slightly, away from the offending QRM. Speech quality will immediately improve, as your window will now look out on only one of the two sidebands. It may come as a surprise to some DXers to find out that the programme is actually carried twice on an a.m. double-sideband system. There is a sideband complete with programme on each side of the carrier and it is only necessary to tune to one of these to extract the modulation. You could double the number of channels on the medium waves by suppressing one sideband but there are problems in doing this.

The New Band Plan

I remained up late on the night of the big change over last November, just in case I might be missing something, and was well rewarded with the feeling that I was listening to history being made. After hearing the short announcement on 200kHz, at midnight, I tuned round the medium waves to be greeted by tuning notes on nearly every channel. The change at the h.f. end of the band was striking. Where the German power-house on 1602 had been, only a few minutes earlier, was now the third international common frequency with nothing to be heard but a burble. That evening I hunted around for any DX between channels, but all I could find was an unidentified Arab on 1570. It looks as if Asiatic DX has disappeared, in the evenings at any rate.

Readers' Letters

Steve Whitt (Cambridge) is interested in QSLs and he reports that he has had 100% returns from the 24 US stations he has reported to so far, but from further south, Radio Margarita on 1020 and Radio Coro on 1210 have not replied. This is a common experience as Latin Americans are notoriously difficult to QSL. One approach is to write a personalised letter to the station giving details of one's self, and perhaps a photo of the shack, or the locality. WEVD 1330 broadcasts in Hebrew, and Steve wonders how he can compile a report, as the programme material is meaningless to him. Make a tape of the DX and if you cannot get it translated then send the tape to the station. Many DXers send tapes instead of reports though it is rather an expensive way of doing it.


Two other questions come from Steve: 1. What is the station on 593 (pre-Geneva) underneath the West German that relays the BBC World Service? It is probably cross-modulation which can occur in the ionosphere as well as inside the receiver. If you listen on the open carrier of any

high power European, just before sign-off, you may hear this effect. There are so many megawatts floating around the ionosphere these days, that all sorts of weird effects can be observed. 2. What is the easiest English speaking DX from the Caribbean? None is easy. Try ZDK Antigua on 1100 or Radio Paradise, St Kitts on 1265, but you will have to stay up late to hear them.

DX Heard

John Faulkner (Mansfield) reports hearing 19 Canadian and 13 US stations with his Trio 9R59D receiver and 40 inch *PW* loop. Toronto was logged on three points on the dial with CBL on 740, CJBC 860 and CFRB on 1010. Others include WHAM Rochester, NY on 1180 and Fort Wayne, Indiana on 1190kHz.

An HMV domestic receiver and loop are in use in Birmingham by **John Dennis Court** and his log contains two not-so-often heard stations in Newfoundland; VOWR on 800 at 0030 and VOAR on 1230 at 0200. There are still a few outlets in Newfoundland that use the old prefix "V" in the call sign, VOXM on 590 being the one that is usually heard. **Noel Cosgrave** (Dublin) has a Mullard MAS1659 receiver and 36 inch loop, which brought him Radio Belgrano, Buenos Aires on 950kHz at 0255, Radio Tupi in Rio de Janeiro on 1280 at 0315 and CB57 Santiago, Chile on 570kHz.

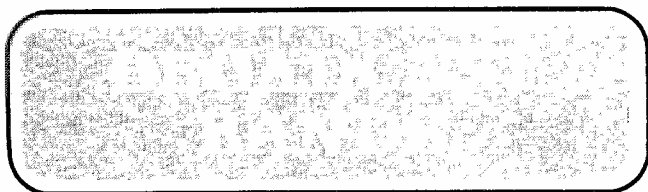

SHORT-WAVE BROADCASTS

by Charles Molloy G8BUS

Skip is a term frequently used by DXers and it is one that may confuse the newcomer to the hobby. Very briefly it refers to a zone around a transmitter where little or no signal can be heard. The ground wave travels only a few miles from a short-wave station before petering out, while the nearest place where the sky wave returns to earth may be hundreds of miles away. The distance between the two is the skip distance. Anyone situated nearer to the transmitter than the point where the sky wave returns, will be in the skip zone and consequently will not hear the station at all, unless of course he is within range of the ground wave. This is the reason why BBC short-wave transmitters in this country are not heard within the UK. The sites of these transmitters incidentally are at Daventry in Northamptonshire, Skelton in Cumberland, Wooferton near Ludlow and Rampisham in Dorset.

The Sky Wave

Great stuff, you may say, but why is it that the sky wave fails to come back to the earth inside the skip zone. To understand this you have to look at what happens to a wave sent up vertically. If the frequency is low enough then the signal will travel some distance into the ionosphere before being returned to the transmitter. A higher frequency will go up a bit further before coming back, and if frequency is increased gradually, a time will

come when the wave will travel right through the ionosphere and off into space. The highest frequency to be returned is called the critical frequency and is usually designated f_c .

Vertical radiation is not much use for broadcasting so in practice a lower angle is employed. A wave travelling at an oblique angle will have to travel a greater distance through the ionosphere than a vertical one, before coming out at the top, so frequencies higher than the critical frequency can be used at low angles. The highest frequency that will be returned will be when the wave is at a low angle, just above the horizon, which is the case for long distance transmission and this frequency may be three or four times f_c . The Maximum Usable Frequency (m.u.f.) for any particular angle can be calculated from f_c which in turn is fairly easy to measure. One final point. To get the maximum signal into the target area it is desirable to transmit as near as possible to the m.u.f., and any radiation at a higher angle than required for this distance will therefore penetrate the ionosphere and be lost. This is what happens to the signal that is missing in the skip zone.

Propagation and DXing

About 4000km is the maximum distance that can be covered by a single hop from low angle radiation and in this case the skip will be great. If the target is nearer than 4000km then a higher radiation angle will have to be used at the transmitter and a lower frequency will be needed as well. Obviously the skip will also be lower. Reception areas further away than 4000km will be reached by multiple hops, the wavefront being reflected from the earth's surface back into the ionosphere after the first hop. So, at any particular time of day, season of the year or period of the sunspot cycle, all of which affect the critical frequency, the highest frequencies available will be used for long distance working and lower ones for short distances. There is no use looking for your favourite European local on 13 metres, for even if the band is open the skip will be too great.

19 Metre Band (15MHz)

Following on from last month we will now have a look at 19 metres whose limits are 15 100 to 15 450kHz, though there is some spread on either side. 19 metres is mainly a daytime band with world-wide reception being possible. Look for Vietnam on 15 012kHz, Teheran 15 084, Japan 15 105, RSA 15 220, New Zealand 15 130, Tanzania 15 435. Some medium range DX can be heard during the day, such as Norway on 15 175, Morocco 15 195, Sweden 15 240 and Finland on 15 265, but these disappear as dark approaches and the m.u.f. falls.

During the evening Latin American DX can be heard and although at first sight this may appear surprising, it should be noted that the signal path is from the south-west from the southern hemisphere, where the greater part of the route will still be in daylight. DX heard regularly in the UK includes: Chile on 15 115, Brazil on 15 145, Chile on 15 150, Radio el Mundo Argentina on 15 290, Radio Nacional Colombia on 15 335, R. Mexico on 15 385, Venezuela on 15 400, and from the same area, Radio Grenada on 15 105kHz.

Readers' Letters

The MCR1 wartime receiver is mentioned again by **Trevor Goodenough**, who has two of them which he uses regularly with a 300ft long wire and an a.t.u. DX heard with this set-up includes Radio Japan and Radio

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

Australia. Trevor is anxious to get hold of a copy of the circuit diagram or the manual for the MCR1 and if anyone can help, would they please contact Trevor direct at 8 Glenraig Terrace, Fenwick, Ayrshire. Postage will be refunded.

The logging of Radio New Zealand on 15 130kHz at 0630 by S.I. Fass in the December issue, is referred to by **T. W. G. Elsenham**, who points out that the RNZ schedule says that this channel closes down at 0450. Schedules are always changing and cannot be relied on. Mr Elsenham goes on to refer to the pre-war BBC weekly *World Radio*. This had a feature covering stations heard by readers which included details of the programmes, and he wonders if we could do the same here. Sounds a very good idea. There are some interesting programmes to be heard on the short waves, usually from the less conspicuous broadcasts. Details of programmes from DX stations should be brief and give the date, time, and frequency (if known).

DX Reported


An unusual log of 60 metre DX, all of Venezuelan stations, has been received from **Leon R. Sin Sun** of Aberdeen, who used a Sony CF9JOS between 2300 and 0400 to pull in Radio Lara on 4800kHz, Bolivar on 4770, Universo 4870, Juventud 4900, Yaracuy 4940, Rumbos 4970, Ecos del Torbes 4980, Barquisimeto 4990, Continente 5030. Programmes heard included local popular music, folklore and interviews which would be of interest to DXers who understand Spanish. Leon does not use any special aerial as he is rather short of space. Try the outside TV aerial if you have one or alternatively a Joystick plus a.t.u. might be useful, but consult the manufacturer, Partridge Electronics, who advertise in *PW*, to make sure that a Joystick can be used with your Sony receiver.

An FRG-7 plus 60ft loft aerial and a.t.u. are in use in Wigan by **Jim Edwards**, who reports hearing KGEI, La voz de Amistad, on 9575 at 1030, Baghdad on 9745 at 2130, Lagos Nigeria on 11 770 at 0630, WINB Red Lion on 15 185 at 2000. Jim reports that he is now a monitor for Family Radio WYFR, which he finds an interesting diversion when he is not DXing.

Australian Domestic Short-wave Stations

Lex Arnold, Hemel Hempstead (R107 ex-WD communications receiver and 9ft indoor aerial), sends some notes about the domestic service of the Australian Broadcasting Commission. He reports that ABC Melbourne has been heard regularly between 1000 and 1300 on 9680kHz. From past experience Lex suggests that DXers should try for stations in this network between late November and mid-April, especially during February and March. Listen for VLH9 on 9690 between 0730 and 1300, VLH11 on

11 880 from 1900 to 2115, VLH15 on 15 230 from 2230 to 0715, all from Melbourne; VLM4 on 4920 and VLQ 9660 between 2200 and 1400, which are in Brisbane; VLW6 on 6140 and VLW9 on 9610 from 2200 to 0100 and 1000 to 1600, both in Perth. Readers who think that Radio Australia is not really DX should try for some of these domestic stations. There is also Port Moresby in New Guinea with P2T9 on 4890 between 0715 and 1400 and again from 2000 to 2200 plus P2T9 on 9520 between 2215 and 0700.

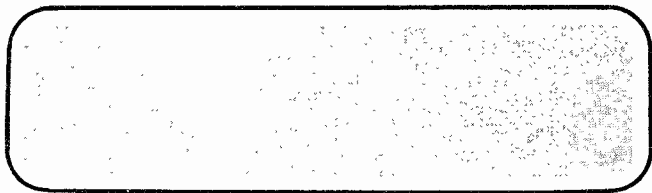

by Ron Ham BRS15744

First, our sincere congratulations to our reader **Robin Bellerby** G3ZYE, Hove, Sussex, on his election to the council of the Radio Society of Great Britain. Robin, a member of the Brighton and District Radio Society, the Mid-Sussex Amateur Radio Society and the Sussex Repeater Group, is actively interested in all bands from 160m to 70cm. News of his election victory came just after the Brighton and District RS had made Robin the first recipient of their trophy, the Bill Pitfield Memorial Award, given for meritorious service to amateur radio by a club member. Like all RSGB council members, Robin has some hard work ahead, what with society affairs, conferences, conventions and WARC 79, the outcome of which may well affect all of us. Congratulations also to **D. J. Stewart**, ex-G8MZP, on passing his Morse test and now sporting the call sign G4HSY.

Solar Activity

Nigel Fisher, **Goff Gill**, **Robin Knight**, **Peter Mynheer** and **Chris Peeder** have recently completed a 60MHz radio telescope for the radio section of the South-East Essex Astronomical Society, and were delighted when their new instrument, built with the r.f. and i.f. sections of an old TV receiver, recorded solar activity on December 10, 11 and 12, as did the 136MHz telescope of **Cmdr Henry Hatfield**, Sevenoaks, and the 146MHz receiver which I use. Henry recorded a slight increase in solar radio noise during the afternoon of November 24, and again on the 25th and, using his spectrohelioscope, he observed a large prominence on the north-west limb of the sun which lived for about 24 hours and he saw another on the east limb on the 26th.

It must have been this solar activity which caused the blackout on 80m, reported by **Alan Baker** G4GNX, Newhaven, at midday on the 25th, the aurora during the same afternoon and the ionospheric disturbance reported by the BBC World Service at 0215 on the 26th. At 1015 on the 25th, I did not hear any International Beacon Project signals on 10m and Alan said that on 80m, even the strong shipping stations which share the band were weak and, from Applecross, Western Australia, Anthony Mann writes: "November 26, absolutely dead, nil above 28MHz all day".

Aurora

The land lines were soon buzzing with an alert once **Roy Bannister** G4GPX, Lancing, **John Cooper** G8NGO, Cowfold, and **Dermot Cronin** G4GRO, Royal Sovereign, heard auroral signals on 2m. Dermot worked GI and GM and G4GNX, who was soon in on the action, heard PA3. **Dave Cox** G8OPR, Andover, Hants, worked stations in 5 different QRA locator squares during the event which included 3 GMs and a GI. For **John Branegan** GM8OXQ, Saline, Fife, this aurora was a novel event because, at 1135, he had a QSO with SM4IVE and soon after with G8OGD via OSCAR 8J. The SM thought an aurora was starting over central Sweden and the G8 told John that his signal had an auroral tone.

At 1320, John again contacted SM4IVE via OSCAR 8J, who reported that the auroral activity in Sweden and Finland was fading and thought to be heading towards Scotland. Between 1340 and 1400 John was receiving auroral signals from the Russian satellite, RS-1, and when he left the satellite he found a full scale aurora affecting the 2m band, which he monitored until 1840. During the period he heard tone "A" signals from the 2m beacons in Cornwall GB3CTC, France FX0THF, Germany DL0PR, Lerwick GB3LER, Northern Ireland GB3GI, and Wrotham GB3VHF, in addition to amateur stations from EI, G, GD, GI, GM and SM. GM8OXQ said there was another, but much weaker, aurora on the 26th but only the northern GMs beyond Aberdeen could use it. **Anthony Mann** says: "It would be lovely to witness an aurora here", and thinks that the only two visible there were during the 1946/7 sunspot maxima. It really is a wonderful sight Anthony, I will never forget the beauty of the one I saw from southern England, following a big solar event in August 1972.

The 10 Metre Band

M. Mrzyglod is delighted with the performance of his new FRG-7 and with his 10m ground-plane aerial, he has been logging the IBP signals from Bermuda VP9BA, Canada VE3TEN, Germany DL0IGI and s.s.b. signals from amateurs on both sides of the Atlantic. M. Mrzyglod is looking for a circuit which he thinks was published in *Practical Wireless* some years ago for a Band I converter. If anyone can help, please let me know. Neil Clarke BRS 34306, Nottingley, York has been enjoying the DX on 10m and logging A4XFA, OX3CO, and VS6FI.

Like myself, John Branegan has found that the signal from the Bahrain beacon A9XC, was very consistent between November 19 and December 15, in fact, I heard it every day except during the blackout on November 25. John, Alan Baker and I, also heard signals from 5B4CY, DL0IGI, N4RD, VP9BA and 3B8MS. On his newly acquired Eddystone 770R communications receiver, John can tune through Bands I and II, and has already observed the effect of F2 conditions on the American and European stations which operate between 30 and 40MHz. He is looking forward to using it during the coming sporadic-E season.

From Down Under

Anthony Mann reports strong sporadic-E disturbances on November 16 and 28, producing Band I colour on an indoor aerial and m.u.f. lapping Band II. On November 18: "The best F2 opening so far", says Anthony who received strong signals from the BBC, Channel B1 sound, 41.5MHz, French Channel F2 sound, 41.25MHz, a watchable picture from a South Korean station, strong Chinese video, 57.770MHz, strong Russian TV sound,

east and west Malaysian video, and strong signals from Japanese amateurs in the 6m band. We are all very envious Anthony.

Tropospheric

During the morning of November 22, Alan Baker worked F1E2P and Mick Senior G4EFO, Horsham worked F6DOP, both through the Brighton repeater GB3SR, R3, and for most of the 22nd and 23rd I heard GW stations working through GB3BC, R6. At 2201 on the 19th, Alan had an unusual contact which lasted 28 minutes, through GB3SR; he worked N2AFE/MM, Ralph, from 5th Avenue, Brooklyn, New York, who was in the engine room of the *Export Patriot* in the English Channel, and as soon as other people realised what was on, suddenly Ralph had 19 stations after him.

A more extensive v.h.f. opening took place on December 5, 6 and 7, during which time I received strong signals from both the Bristol Channel and Dover 2m repeaters. Throughout the 6th I received good pictures from the IBA transmitter at Lichfield, Channel 8, 189MHz, and signals from several continental broadcast stations in Band II. At 0030 on the 6th, John Cooper phoned G4GNX to say that he had worked a station through a Belgian repeater, and G4GNX reported hearing ON0OV on R4. During the morning, GU2FZC, St Peter Port and F1EBE, Rouen, worked through the Brighton repeater and in the afternoon GB3BC was putting a strong signal into east Sussex. Periodically, throughout the day, Band V TV suffered from co-channel interference and in the evening, G6GL, Radlett, Hertfordshire, had an effortless QSO with G3TIR in Crawley, Sussex, via the Hampshire repeater, GB3SN, R5. Signals from the French repeater on R9 were heard on December 8 by G4GNX and G4GPX, and G3TRY, High Wycombe worked a station in Yorkshire through extreme QSB.

Satellites

On December 1, our satellite expert, John Branegan, wrote: "Being a thorough optimist I still go on OSCAR 8A despite the high m.u.f., and though the ionosphere must be as thick as treacle, I have twice got across to W2BXA in New Jersey". The W2 told John that he was the only European he had heard for some time. "On Mode J at weekends it is a very different story", says John, who in 10 QSOs in November, worked 4 stations, W9KDR Conn, WB2OXJ New Jersey, WA3ZHW Penn, and VE2LI Montreal. By the end of November, John, by working his first east-German, DM2DIN, s.s.b., made his score 27 countries on 8J and pushed his total up to 35 countries via satellite.

Contests


As usual the RSGB have catered for the v.h.f./u.h.f. enthusiasts in their contests calendar for 1979, and reports will be welcome from any of our readers who take part in either the transmitting or receiving sections of any of the following events:

March 3 and 4	144/432MHz and SWL
April 8	432MHz open and SWL
April 29	70MHz Open
May 26 and 27	144MHz Portable
July 7 and 8	VHF NFD
August 18 and 19	70MHz Open
September 1 and 2	144MHz Open and SWL
October 21	70MHz Fixed
December 2	144MHz Fixed

PERSONALITY

by **RON HAM**

"THE TWO ERNS"

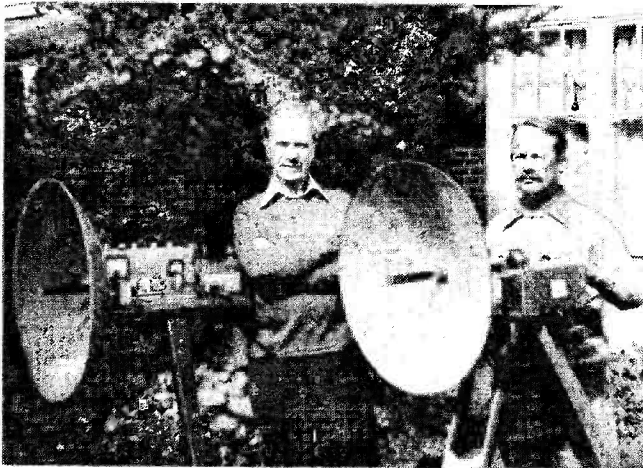

One of the fascinations for me when writing my column is to realise that my readers are using wavelengths from 10 metres through to 3 centimetres, which in frequency terms, is 30 million to 10 thousand-million hertz. It is men like Ern Downer G8GKV of Worthing (right), and Ern Hoare, G8BDJ of nearby Southwick (left), known locally as "The Two Ern's", who are pioneering the microwave end of the radio frequency spectrum.

Ern Downer's schoolboy interest in amateur radio was fostered by a neighbour, the late G2XO of London. During the early 1930s Ern built himself a number of short-wave receivers, from designs published in the amateur radio press. His introduction to v.h.f. came in the second world war with the Royal Tank Regiment. After the war he spent some years in East Africa where he used "point-to-point" links, and on his return to the UK, a colleague, G3YHM, invited him to join the Worthing Amateur Radio Club. In May 1972 he took the RAE, and by August, his call, G8GKV, was heard on the air.

In 1927, the 10-year-old Ern Hoare began building crystal sets, progressing to valve sets, and later to a 30-line scanning disc television receiver, through which he did get a picture of sorts. Ern was a radar operator with the Royal Artillery during the second world war, using both v.h.f. and microwave systems. Later, he volunteered for the 6th Airborne Division, where he used the famous 38 sets for 3in mortar fire control. He took the RAE in 1962 and was first licensed as G3RZD/T, constructing his own gear for amateur TV. When his call was changed to G8BDJ he used home-brew gear on 2m, 70cm and 23cm.

Due to common interests, both G8GKV and G8BDJ began to inhabit the local hill tops, operating portable stations on 2m. When 'BDJ began building equipment for 10GHz, 'GKV was hooked, since when "The Two Ern's" have never looked back. Now, with some very impressive home-brew portable stations, they each hold many well deserved awards, and apart from entering the RSGB's 10GHz contests, they spend a great deal of time trying out "difficult" paths of microwavelength communications.

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, TV Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
Also MPT Radio Communications Certificate

Diploma Courses

Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV and Audio, Engineering and Servicing
Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept E276 Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name


Address

Telephone Number

TTLS BY TEXAS		74221		160p		74LS192		140p		74C157		250p		LINEAR I.C.s		TRANSISTORS		TIP41C		78p		DIODES	
7400	13p	7407	180p	74251	140p	74LS193	140p	74C160	155p	*AY1-0212	600p	*MC1496	100p	AC127/8	20p	BFY51/2	22p	TIP42A	70p	*2N3866	90p	*BY127	12p
7401	14p	74100	130p	74259	250p	74LS195	140p	74C161	155p	*AY1-1313	688p	*MC3340	120p	AD149	70p	BFY56	33p	TIP42C	82p	*2N3903/4	18p	*OA47	9p
7402	14p	74104	85p	74265	90p	74LS196	120p	74C162	155p	*AY1-5050	212p	*MC3360	120p	AD161/2	45p	BFY90	90p	TIP2855	78p	*2N4036	85p	*OA81	15p
7403	14p	74105	65p	74278	250p	74LS221	100p	74C163	155p	*AY5-1315	600p	*MFC400B	120p	BC107/8	11p	BLY83	700p	TIP3055	70p	*2N4056/9	12p	*OA85	15p
7404	17p	74107	34p	74274	140p	74LS240	175p	74C164	150p	*AY5-1320	320p	NE531	130p	BC109	11p	BRV39	145p	*TIS43	34p	*2N4060	12p	*OA90	9p
7405	18p	74109	55p	74283	190p	74LS241	175p	74C173	120p	*CA5019	80p	NE543K	225p	*BC117/8	9p	BSX19/20	50p	*TIS93	30p	*2N4061/2	18p	*OA91	9p
7406	32p	74110	55p	74284	400p	74LS242	175p	74C174	160p	*CA5046	70p	NE555	25p	*BC149	10p	*BU105	190p	*ZTX108	12p	*2N4123/4	22p	*OA95	9p
7407	32p	74111	70p	74285	400p	74LS243	175p	74C175	210p	*CA3048	225p	NE566	25p	*BC157/8	10p	*BU108	250p	*ZTX300	13p	*2N4125/6	22p	*OA200	9p
7408	19p	74116	200p	74290	150p	74LS245	175p	74C192	150p	*CA3080E	72p	NE566	25p	*BC159	11p	*BU205	220p	*ZTX500	15p	*2N4289	20p	*OA202	10p
7409	19p	74118	130p	74293	150p	74LS251	200p	74C193	150p	*CA3095E	225p	NE566	25p	*BC162C	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN184	4p
7410	15p	74119	210p	74294	200p	74LS257	120p	74C194	200p	*CA3099A	360p	NE566	135p	*BC172	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7411	24p	74120	110p	74295	140p	74LS259	175p	74C195	110p	*CA3099A Q	360p	NE566	135p	*BC177/8	17p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7412	20p	74121	28p	74296	200p	74LS298	240p	74C221	175p	SERIES		CA3130S	100p	*BC182/3	19p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7413	30p	74122	15p	74366	150p	74LS373	200p	4000	4000	CA3140E	100p	IC1706	925p	*BC184	11p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7414	60p	74123	55p	74367	150p	74LS374	195p	4000	15p	CA3160E	75p	IC1803B	340p	*BC212/3	31p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7415	27p	74125	55p	74368	150p	81LS95	120p	4001	17p	FX209	750p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7417	27p	74126	60p	74390	200p	81LS96	160p	4002	17p	IC1706	925p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7420	17p	74128	75p	74393	200p	81LS98	160p	4006	95p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7421	40p	74132	75p	74490	225p	81LS98	160p	4007	80p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7422	22p	74136	75p	74490	225p	81LS98	160p	4007	80p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7423	34p	74141	70p	SERIES		81LS98	160p	4008	80p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7425	30p	74142	200p	74LS00	18p	81LS98	160p	4009	40p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7426	40p	74145	90p	74LS02	20p	81LS98	160p	4010	40p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7427	34p	74147	190p	74LS04	20p	81LS98	160p	4011	17p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7428	38p	74148	150p	74LS08	22p	81LS98	160p	4012	18p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7430	17p	74150	100p	74LS10	20p	81LS98	160p	4013	50p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7432	30p	74151A	70p	74LS10	20p	81LS98	160p	4014	84p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7433	40p	74153	70p	74LS14	100p	81LS98	160p	4015	84p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7437	35p	74154	100p	74LS20	22p	81LS98	160p	4016	45p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7438	35p	74155	90p	74LS22	22p	81LS98	160p	4017	80p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7440	17p	74156	90p	74LS27	38p	81LS98	160p	4018	85p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7441	70p	74157	70p	74LS30	22p	81LS98	160p	4019	45p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7442A	60p	74159	150p	74LS47	20p	81LS98	160p	4020	100p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7443	112p	74160	100p	74LS55	30p	81LS98	160p	4021	110p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7444	112p	74161	100p	74LS73	50p	81LS98	160p	4022	100p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7445	100p	74162	100p	74LS74	40p	81LS98	160p	4023	22p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7446A	93p	74163	100p	74LS75	50p	81LS98	160p	4024	20p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7447A	70p	74164	120p	74LS83	110p	81LS98	160p	4025	20p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7448	80p	74165	130p	74LS85	100p	81LS98	160p	4026	130p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7450	17p	74166	140p	74LS86	40p	81LS98	160p	4027	50p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7451	17p	74167	200p	74LS90	60p	81LS98	160p	4028	84p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7453	17p	74170	240p	74LS93	60p	81LS98	160p	4029	100p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7454	17p	74172	720p	74LS107	45p	81LS98	160p	4030	55p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7460	17p	74173	120p	74LS107	45p	81LS98	160p	4031	200p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7470	36p	74174	85p	74LS112	100p	81LS98	160p	4032	180p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7472	30p	74175	85p	74LS123	75p	81LS98	160p	4033	110p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7473	34p	74176	90p	74LS133	60p	81LS98	160p	4034	100p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7474	30p	74177	90p	74LS138	60p	81LS98	160p	4035	100p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7475	36p	74178	160p	74LS139	60p	81LS98	160p	4036	80p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7476	35p	74180	35p	74LS151	100p	81LS98	160p	4037	80p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7480	50p	74181	200p	74LS153	60p	81LS98	160p	4038	90p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7481	100p	74182	90p	74LS157	60p	81LS98	160p	4039	110p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7482	84p	74184A	150p	74LS158	120p	81LS98	160p	4040	100p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p	*IN186	7p
7483A	90p	74185	150p	74LS160	100p	81LS98	160p	4041	50p	LM301A	350p	LM301A	350p	*BC214	12p	*BU208	240p	*ZTX504	30p	*2N4299	20p		

ANNOUNCING

THE NEW EUROBOARD

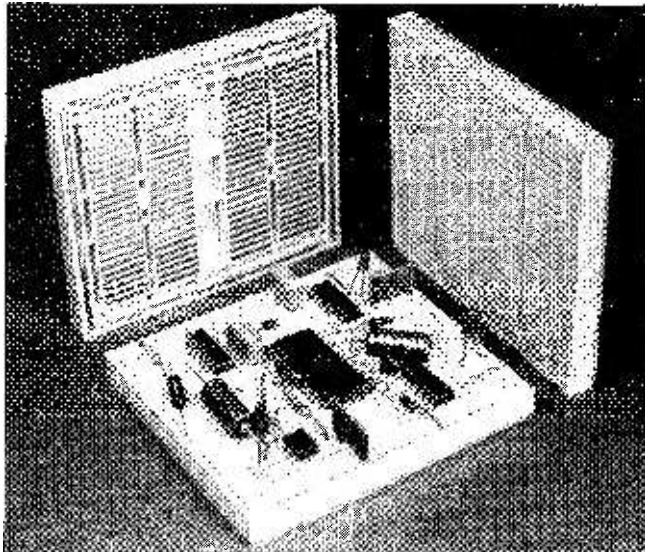

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points.

4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

Double-sided, nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m.ohms)

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

What other breadboarding system has as many individual contacts, offers all these features and only costs £5.80 inclusive of VAT and P.P. - NONE.

At £5.80 each The EuroBreadBoard is unique value for money. At £11 for 2 The EuroBreadBoard is an indispensable design aid.

Snip out and Post
David George Sales, r/o 74 Crayford High St., Crayford, Kent, DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

Please send me 1 EuroBreadBoard @ £5.80 Please
or 2 EuroBreadBoards @ £11.00 Tick

(All prices include VAT and P.P., but add 15% for overseas orders).

Name
Company
Address
.....
.....
Tel. No. PW379

Please make cheque/P.O.'s payable to David George Sales

MAIL ORDER DEPT.
CRESCENT RADIO LTD
1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ. 01-888 3206




"FLIP"
PUSH BUTTON HEADS OR TAILS
Complete kit and full instructions supplied.
A pocket game, easy to build and great to play.
KIT PRICE = £5-25 + 8% VAT. Post free.


75 OHM
2 1/2" (57mm) LOUDSPEAKER BARGAIN
This ever popular many project loudspeaker.
Only while stocks last. 65p + 12 1/2% VAT.

REAR SHELF CAR SPEAKERS
5W 8 ohm good quality car stereo
loudspeakers.
Still only £3-75 + 12 1/2% per pair.

HEAVY DUTY XOVER
2 WAY 8 OHM
A 2 way 8 ohm H/D Xover suitable
for L/S systems up to 100 watt.
Fitted with screw terminals for
input and a three position 'HF
LEVEL' switch which selects either
Flat, -3dB or -6dB.
ONLY £3-00 + 8% VAT

A CRESCENT 'SUPERBUY'
Goodmans 5" 8 ohm long throw
H/D loudspeaker.
Mounting plate is integral with L/S
chassis and has fixing holes with
centres spaced at 5 1/4" (diagonally).
ONLY £5-00 + 12 1/2% VAT

CR. 3000. SCREWDRIVER SET

£1.75p.
+ 8% VAT
In neat plastic case. Consists of: awl,
jewellers screwdriver, watchmaker's
screwdriver, radio screwdriver, philips
screwdriver. All fit into master swivelling
handle.

CR. 4110. DESOLDERING PUMP

ONLY £6
+ 8% VAT
High suction pump with automatic ejection.
Knurled, anti corrosive casing. Teflon
nozzle.

CR. LV1. 12v DRILL

£12.00p.
+ 8% VAT
BRITISH MADE "Versadrill", 12 volts DC.
Compact battery operated power tool, sufficiently
powerful to perform all the
operations associated with 240v drills.
Dimensions:- 150 x 50mm (dia.)

LOUDSPEAKERS + 8% VAT
12" "McKENZIE" 8 ohm 75W
Bass **£23-62**
12" "McKENZIE" 8 ohm 75W dual
cone **£23-62**
12" "McKENZIE" 8 ohm 75W
general purpose **£18-75**
12" "GOODMANS" 'Audiom 12P'
8 ohm 50W **£23-73**
12" "FANE" POP 33T 16 ohm 33W
£12-92
12" "FANE" POP 50/2 16 ohm 50W
£15-70



P & P. Orders up to £5, add 30p. Orders
£5-£10, add 50p. All orders over £10
post free! Please add V.A.T. as shown.
S.A.E. with all enquiries please.



Personal callers welcome at: 21 Green Lanes, Palmers Green N13.
Also 13 South Mall, Edmonton Green, Edmonton.

STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA

ENGLAND
Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers.
Full range of VHF receivers—transceivers. Mobile equipment pre-
selectors—filters—antennas. Stabilised power supplies from 2 to 20 Amp.
Antenna switches—converters. Aluminium masts—clamps. Antenna rotators.

Yaesu
FRG7-FRG7000-FR101

TRIO
R-300-R599D-R820S

Drake
SSR-1*SPR4*R4C*

Secondhand Equipment
Our secondhand equipment stock changes
daily. Send S.A.E. for latest price list. Part
exchanges welcome.
Access-Barclaycard and H.P. facilities.

Antenna Multituners
Designed and manufactured by ourselves.
Over 1000 sold in over 50 countries.

Mk2 covers 550 Khz 30mhz **£25-00**
Prices include VAT and postage.

SOUTHERN VALVE CO.

Telephone 01-440/8641

SECOND FLOOR, 8 POTTERS ROAD,
NEW BARNET, HERTS.

MAIL ORDER ONLY. MINIMUM ORDER 80p

Some leading makes available. VAT invoices issued on request.
All New and Boxed. "Quality" Branded Valves. Guaranteed 3 months. BVA etc.

8% Allowed in lieu of Guarantee! Already deducted from our Prices!

NOTE: PLEASE VERIFY CURRENT PRICES. Correct only at time of going to press.

DY86/7	53p	EF86	55p	IGY501	£1.40	PCF802	80p	PL36	£1.00	PY500A	£1.80
DY802	53p	EF89	55p	PC86	78p	PCF805	£1.70	PL31A	65p	UBF89	42p
EC81	54p	EF183	55p	PC88	78p	PCF806	75p	PL83	50p	UCF85	50p
EC82	60p	EF184	55p	PC97	75p	PCF808	£1.70	PL84	50p	UCH81	50p
EC83	60p	EH90	60p	PC900	65p	PC82	63p	PL500		UCI82	72p
EC85	50p	EL34	£1.85	PCC84	35p	PCL83	90p	PL504	£1.15	UCL83	£1.00
ECH81	55p	EL84	50p	PCC85	50p	PCL84	65p	PL508	£1.60	UF89	52p
ECH84	85p	EL509	£2.90	PCC89	50p	PCL805	85p	PL509	£3.05	UL41	90p
ECL80	52p	EM84	90p	PCC189	55p	PCL85		PL519	£3.30	UL84	90p
ECL82	62p	EY86-7	46p	PCF80	80p	PCL86	80p	PL802	£2.80	UY85	60p
ECL86	70p	EY500A	£1.60	PCF86	60p	PCL200	£1.40	PY88	85p	U25	60p
EF80	41p	EZ80	42p	PCF200	£1.60	PD500	£3.60	PY800	63p	U26	60p
EF85	45p	EZ81	44p	PCF801	60p	PFL200	£1.35	PY801	63p		


We offer return of post service. C.V.O. ONLY. No C.O.D. MANY OTHERS
Post free over £20. £6 to £20-80p (max.) AVAILABLE

Items in stock at time of going to press but subject to possible market fluctuations
if unavoidable.

STOP PRESS! One valve post 13p, each extra valve 6p. Large valves 2p each extra.
STOCKISTS MAX 75p. LISTS AND ENQUIRIES. S.A.E. PLEASE!
"MICRO" AERIAL! ALL PRICES INCLUDE VAT @ 12 1/2%
SIZE 1 1/2" x 3"

ENQUIRIES WELCOMED FROM TRADE AND RETAIL (same prices)

A breadboard as big as your ideas.

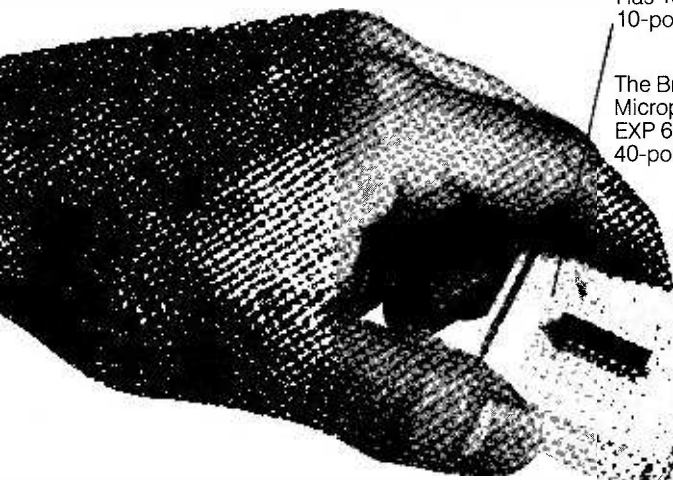

EXPERIMENTOR 325 £2.54

The ideal Breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin IC's. Has 130 contact points including two 10-point bus-bars.


EXPERIMENTOR 600 £7.88

The Breadboard for quick construction of Microprocessors and other circuits. EXP 600 has 550 contacts including two 40-point bus-bars with 0.6" centres.

EXPERIMENTOR 650 £4.70

Perfect for checking out Microprocessors. EXP 650 has 270 contacts including two 20-point bus-bars with 0.6" centres.

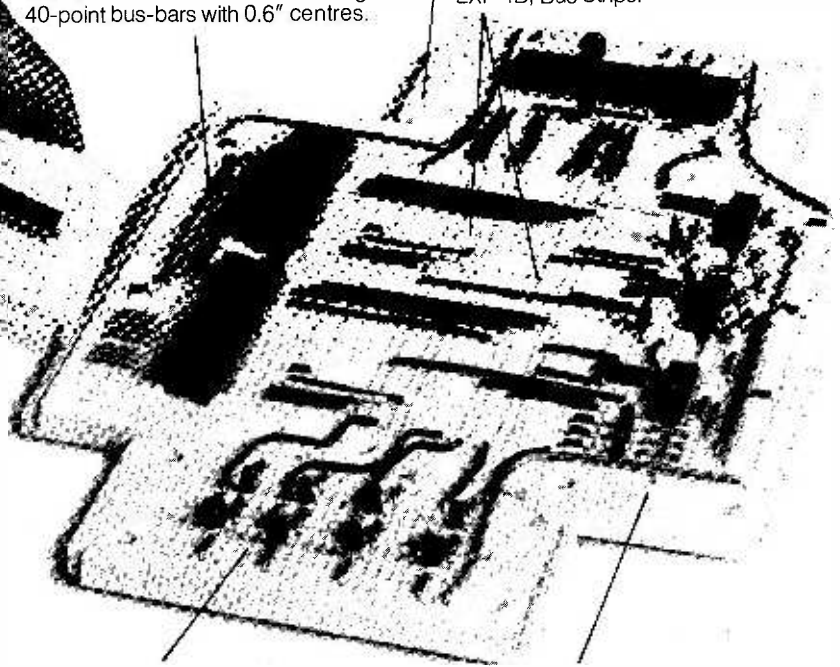EXPERIMENTOR QUAD BUS STRIP £3.29 Need more bus-bars, clip on an EXP 4B and you have four 40-point bus-strips with 8-, 12- and 16-line address, create data-buses by combining EXP 4B, Bus Strips.



No soldering simply plug all standard components in and out, nickel-silver contacts allow Breadboard and components to be used over and over again without damage.

Adaptable accepts any component without adaptors or jumper leads, use 22-30 gauge solid wire for jumper leads.

Mix and Match large and small chips in the same circuit. Use 300 series for smaller and 0.3" pitch DIP's. 600 series for Microprocessors with 0.6" centre channel for full fan-out with larger chips.

Smallest to Biggest, remember CSC's Breadboards "snap-lock" together so you can start with a small idea and expand your ideas to as Big a Breadboarding area as you like.

Easy Permanent Mounting, using four screws from front or six self-tappers from rear. Vinyl-insulated backing lets you fasten to any surface.

Pick any project that you want to build, or any part of a project that you want to test or modify. Count up the number of IC's you need for the project. Then simply look up in the box opposite the Breadboard you require. If you need more than two bus-bars simply add the correct number of Quad-Bus Strips. **GET STARTED NOW FOR AS LITTLE AS £2.54.**

EXPERIMENTOR 350 £4.21

EXP 350, specifically designed for the hobbyist working with up to 3 x 14 DIP IC's. With 270 contact points including two 20-point bus-bars the EXP 350 accepts any size DIP with 0.3" spacing.

Marked Contact Points transfer component by component from letter/number position on Breadboard to finished P.C. Board or Wiring Table.

Ruggedly built of abrasion-resistant materials that withstand 100°C.

EXPERIMENTOR 300 £7.29


The hobbyists ideal Breadboard, accepts 6 x 14 DIP or 5 x 16 DIP, has 550 contact points including two 40-point bus-bars, accepts any size DIP with 0.3" spacing.

Tailor-Made Breadboards e.g. a project requires up to 5 x 14 DIP chips and needs up to six bus-bars. Which to buy? Easy from the table below select an EXP 300 plus an EXP 4B, total cost £10.58.

MODEL NO.	NUMBER OF CONTACT HOLES	IC CAPACITY (14-pin DIP's)	UNIT PRICE (includes Post & VAT)
EXP 300	550	6	£7.29
EXP 600	550	use with 0.6" PITCH DIP's	£7.88
EXP 350	270	3	£4.21
EXP 650	270	use with 0.6" PITCH DIP's	£4.70
EXP 325	130	1	£2.54
EXP 4B	FOUR 40-point Bus-Bars	—	£3.29

How to order. Telephone 0799 21682 and give your Access, American Express or Barclaycard number, and your order will be in the post that night. Or send your order, enclosing cheque, postal order, or stating credit card number and expiry date. For full catalogue showing all CSC products for the engineer and hobbyist send large S.A.E.

CONTINENTAL SPECIALTIES CORPORATION

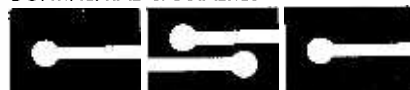

Europe, Africa, Mid-East: **CSC UK LTD. Dept. 6K**, Shire Hill Industrial Estate, Units 1 and 2 Saffron Walden, Essex CB11 3AQ Telephone Number: SAFFRON WALDEN 21682 TLX 817477


**TO ALL TRADERS, MAIL ORDER HOUSES
CONTACT MRS TINA KNIGHT FOR "PROFIT-PACKAGE" DETAILS**

The latest kit innovation!

from **Sparkrite**

Sparkrite was featured by Shaw Taylor in "DRIVE IN"

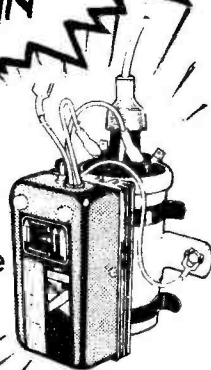the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing. U.K. only.

Electronic Design Associates, 82 Bath Street, Walsall, WS1 3DE

Electronics Design Associates, Dept. PW3
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name _____
Address _____
Phone your order with Access or Barclaycard
Inc. V.A.T. and P.P. QUANTITY REQ'D. Send SAE if brochure only required.
I enclose cheque/PO's for £ _____
Cheque No. _____

X4 KIT	£16.65
TACHOPULSE SLAVE UNIT	£3.85

Please state polarity pos. or neg. earth
Access or Barclaycard No. _____

FF1 WALL MOUNTING KIT FOR HI-FI SPEAKERS



Fidelity Fastenings FF1 is a precision made, vibration damped wall fastening for Hi-Fi and Stereo Speakers of up to 50lbs weight each. Almost undetectable when fitted, the FF1 allows easy adjustment of speaker angle, and the rubber mounting ensures that they do not move accidentally. Speakers can also be quickly and easily lifted off for dusting, cleaning and redecorating.

Available from all good Audio, Hi-Fi and electrical shops at

£6.49

in case of difficulty, direct from the manufacturer at £6.89 inc P & P

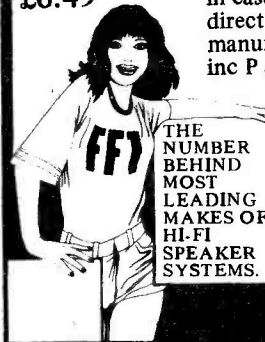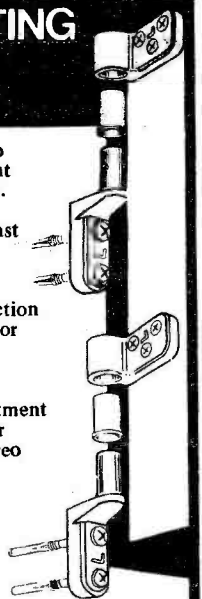- ★ Holds up to 50lbs weight per speaker.
- ★ Precision cast mounting brackets.
- ★ Rubber friction mounting for complete stability.
- ★ Easy adjustment of angle for precise stereo image.



PRECISION AUDIO PRODUCTS FROM



The Ridgeway, Iver, Buckinghamshire
Tel: (0753) 654222

NEW! BUILD-IT-YOURSELF TEST GEAR KIT

BASIC SERVICING INSTRUMENTS WITH EASY STAGE BY STAGE BUILDING INSTRUCTIONS—IDEAL FOR THE AMATEUR

MULTI RANGE TEST METER

A general purpose meter covering all usual ranges of A.C. and D.C. volts current and resistance measurements

AUDIO SIGNAL GENERATOR

New design covering 10Hz to 10KHz and variable output. Distortion less than 0.01% Ideal for HIFI Testing.

OSCILLOSCOPE

A basic 3" general purpose cathode ray oscilloscope for simple testing and servicing work. Sensitivity 0.3 volts/cm

SEND NOW FOR FREE DETAILS

To LERNAKITS, P.O. Box 156, Jersey. W03/79

Name _____
Address _____

15-240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4-7k Ω at 1kHz.


OUTPUTS: Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0-1% at 1kHz. Signal/Noise Ratio 88dB.

OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE** \pm 16-50V.

Price £6-27 + 78p VAT P&P free.

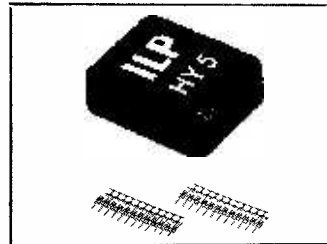

HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω ; **DISTORTION** 0-1% at 1-5W.

INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

SUPPLY VOLTAGE \pm 18V.

Price £6-27 + 78p VAT P&P free.



HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most flexible and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


SPECIFICATIONS: **INPUT SENSITIVITY** 500mV

OUTPUT POWER 25W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-04% at 25W at 1kHz

SIGNAL/NOISE RATIO 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

SUPPLY VOLTAGE \pm 25V **SIZE** 105 50 25mm

Price £8-18 + £1-02 VAT P&P free

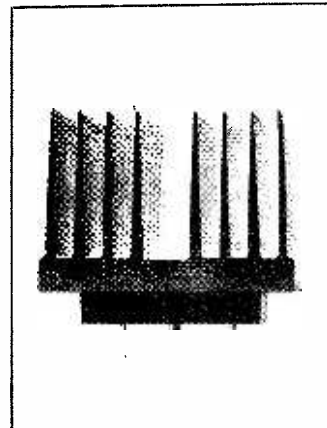

HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS:

INPUT SENSITIVITY 500mV.

OUTPUT POWER 60W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-04% at 60W at 1kHz

SIGNAL/NOISE RATIO 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 25V

SIZE 114 50 85mm

Price £19-01 + £1-52 VAT P&P free.

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS:

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-05% at 100W at 1kHz.

SIGNAL/NOISE RATIO 95dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 45V

SIZE 114 50 85mm

Price £27-99 + £2-24 VAT P&P free.

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial


SPECIFICATIONS:

OUTPUT POWER 240W RMS into 4 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-1% at 240W at 1kHz

SIGNAL NOISE RATIO 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 45V

INPUT SENSITIVITY 500mV **SIZE** 114 100 85mm

Price £38-61 + £3-09 VAT P&P free.

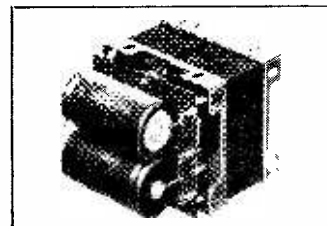

POWER SUPPLIES

PSU36 suitable for two HY30's £6-44 plus 81p VAT. P/P free.

PSU50 suitable for two HY50's £8-18 plus £1-02 VAT. P/P free.

PSU70 suitable for two HY120's £14-58 plus £1-17 VAT. P/P free.

PSU90 suitable for one HY200 £15-19 plus £1-21 VAT. P/P free.

PSU180 £25-42 + £2-03 VAT.

B1 £0-48 + £0-06 VAT.


TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., GROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.

I.L.P. ELECTRONICS LTD.,
GROSSLAND HOUSE, NACKINGTON,
CANTERBURY, KENT, CT4 7AD.
Tel: (0227) 64723.

Regd No. 1032630.

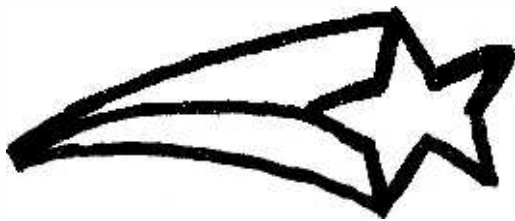Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name and Address _____
Signature _____



A NEW STAR ON THE WORLD'S HI-FI HORIZON.

PW
WINTON

PW and T. & T.

HAVE COLLABORATED TO BRING TO PW'S READERS A WORLD FIRST ON THE HOME CONSTRUCTOR HI-FI KIT SCENE.

Ted Rule, a member of the design team of T. & T. Electronics was commissioned by P.W. to design a High Fidelity Stereophonic Amplifier in a form suitable for the Home Constructor which would supersede the now ageing "Texan".

This, bearing in mind the phenomenal success story of the Texan was a daunting brief for any design team, but we are both delighted and proud to announce that Ted as well as achieving his original design brief, has far exceeded it.

Ted, (who has 30 years experience in Hi Fi design) has excelled himself in producing the P.W. WINTON amplifier, which we sincerely believe to BETTER SIGNIFICANTLY ANYTHING CURRENTLY AVAILABLE TO THE HOME CONSTRUCTOR IN THIS POWER RANGE.

The almost unbelievable specification for this design (published in full in the WINTON article) was achieved by utilising the latest "state of the art" devices available including the revolutionary POWER MOS-FETS developed by HITACHI Ltd., and BI-FET Op Amps from TEXAS.

The HITACHI research has we feel rendered the use of Bi-Polar Power Output Transistors obsolete in any design which has any pretensions towards true HIGH FIDELITY.

Because we are so excited at the performance obtainable, and to avoid disappointment caused by the use of sub-standard components, we have decided to market a complete kit of parts to ensure that the Home Constructor can achieve the same superb results.

As with Rolls-Royce quality doesn't come cheaply, and we make no apologies at all for the fact that our kit costs a bit more than the average Bi-Polar design, we firmly believe that the standard of reproduction obtainable is a reflection in part of the quality of the components used in the kit, and that discerning Audiophiles the world over will recognise the inescapable truth that today you usually get just what you pay for.

The WINTON Kit is available in the following form:-

Pack (A) Capacitors & Fixed Value Resistors	£21.45
Pack (B) Switches, Potentiometers, Pre-Sets & Knobs	£13.26
Pack (C) Printed Circuit Board, and Terminal Pins	£8.10
Pack (D) Hardware Pack, consisting of Chassis, Heat Sinks, Cabinet, Screws, Wire, Fuseholders etc., and a Brushed Aluminium Fascia Front Panel.	£32.99
Pack (E) Semiconductors (including HITACHI MOS Power Fets)	£30.53
Pack (F) Toroidal Mains Transformer	£17.22
Complete Kit of all parts necessary to build the WINTON	£120.00

ORDER WITH COMPLETE CONFIDENCE (Cash with order please) FROM:-

T. & T. ELECTRONICS. GREEN HAYES, SURLINGHAM LANE, ROCKLAND ST. MARY, NORWICH, NORFOLK. NR14 7HH. PLEASE ALLOW 28 DAYS FOR DELIVERY.

NO DISCO SYSTEM IS COMPLETE WITHOUT...



CITRONIC MM 313 MIXER

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch. mono. inc. LED indicators. connections via phono sockets at rear. Bargain price, including PSU
£80.46 inc. VAT (P.P. £1.50)

PIEZO HORNS

FANTASTIC SPECIAL OFFER TO READERS OF PRACTICAL WIRELESS
Tweeters for your disco, PA system or Hi-Fi. Frequency range 5K-20K No X over required. They can be used in any PA system up to 100W. Why pay more?
OUR PRICE ONLY **£4.99** each (P&P 35p each)



BULGIN OCTAL PLUGS AND SOCKETS

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET
£0.65 (P&P 35p) P551 PLUG **£1.84** (P&P 35p)
Carriage on 10 or more nominal £1.00. Also available 8-way multicore cable (6 Amps per core) ex stock £0.65 per metre. Please phone for carriage quote



PROJECTORS

SQUIRE MULTIFECT 150
— including rotator and effects wheel! A truly versatile projector which uses a powerful 150W Tungsten bulb, all effects attachments simply slot in ready for use
A BARGAIN AT £40.50 (P&P £1.00)



STARLITE 250

An exclusive new line to Roger Squire's Disco Centres. Superb high powered 250 W quartz halogen bulb, fan cooled, accepts wide range of multifect attachments. Unique connection slot for orbit prism revolvers. Only **£65.00+** VAT attachments extra

PLUS MANY DISCO ACCESSORIES

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES. For example: Fane and H/ H Disco Speakers 12" and 15" BSR and Garrard decks at discount prices.



Plus sockets Fuses, Plugs, etc etc.

Roger Squire's DISCO GEAR

Personal callers: ROGER SQUIRE'S DISCO CENTRES
LONDON: 175 Junction Road, Tufnell Park N19 5DQ 01-272 7474
BRISTOL: 125 Church Road, Redfield, Bristol BS5 5JR 0272-550550
MANCHESTER: 251 Deansgate M3 4EN 061-831 7676
GLASGOW: 1 Queen Margaret Rd., (off Queen Margaret Drive) Kelvinside, Glasgow G20 6DP
Open from 10-5 Tues-Sat
10-8 Weds
Closed Mondays
Tel. 041 946 3303

VALVES


A1065	1.25	EF80	0.40	PC900	1.25	SP61	0.85	3E29	5.50	6H6	4.20	12SJ7	0.55
AR8	0.80	EF83	1.50	PCC84	0.45	TT21	7.50	3S4	0.50	6J4WA	1.75	12X07	0.55
AR3	0.50	EF85	0.55	PCF82	0.40	U191	0.75	3V4	0.85	6J5	0.75	12Y4	0.40
ATP4	0.50	EF86	0.55	PCF84	0.65	U201	0.50	5B2544M6.50	6J5GT	0.55	1306	0.60	
B12H	3.00	EF91	0.65	PCF86	0.65	U301	0.50	5V4G	0.65	6K7G	0.55	19H5	17.00
CY31	0.50	EF92	0.75	PCF200	0.30	U801	0.80	5Y3GT	0.65	6K8GT	0.55	20D1	0.60
DAF96	0.60	EF95	0.45	PCF201	0.50	UABC80	0.60	5Z3	1.00	6L6M	1.90	20F2	0.60
DET22	19.50	EF183	0.65	PCF201	0.50	UAF42	0.75	5Z4G	0.70	6L6GT	0.90	20L1	1.00
DF96	0.50	EF184	1.50	PCF80	0.65	UCC84	0.60	5Z4GT	0.75	6L18	0.60	20P1	0.40
DH76	0.40	EF804	2.00	PCF805	1.00	UBF89	0.50	6AB7	0.60	6LD20	0.50	20P3	0.60
DK96	0.80	ELF200	0.75	PCF806	0.85	UBL1	1.00	6AC7	0.60	607B	0.50	20P4	1.10
DL92	0.50	EH90	0.60	PCF808	1.80	UBL21	0.75	6AN6	0.70	6L7G	0.65	20P5	1.00
DY802/87	0.55	EL32	0.90	PCF200	0.30	UCC84	0.60	6AK5	0.55	6SA7	0.55	25L6GT	0.80
DY802	0.55	EL34	2.20	PCF201	0.50	UCC85	0.60	6AK8	0.40	6SG7	0.75	25Z46	0.70
ES1	7.50	EL37	3.00	PCL81	0.60	UCC85	0.60	6AL5	0.40	6SJ7	0.70	30C15	1.00
EB8 CC01	1.30	EL41	0.80	PCL82	0.65	UCH81	0.60	6AL5W	0.65	6SL7GT	0.50	30C17	1.10
E180CC	1.30	EL81	1.05	PCL86	0.70	UCL82	0.75	6AM5	1.60	6SK7	0.60	30C18	see
E180E	6.00	EL82	0.80	PCL805/65	0.75	UF41	0.80	6AM6	0.85	6SL7GT	0.70	PCF805	
E182CC	3.50	EL84	0.60		0.75	UR80	0.45	6AN8	0.85	6SN7GT	0.75	30F5	1.00
EA76	2.00	EL88	0.95	PD500	3.25	UR85	0.50	6A05	1.30	6SG7	0.75	30T12	1.20
EAB8C80	0.50	EL90	1.30	PF200	1.35	UL41	0.75	6A05W	0.85	6VB6GT	0.35	30L12	1.20
EB91	0.40	EL91	1.60	PL36	0.80	UL84	0.75	6A05W	0.85	6X4	0.60	30FL14	1.80
EBC33	1.00	EL95	0.75	PL81	0.75	UM80	0.60	6A56	0.80	6X5GT	0.55	30L15	1.00
EBF80	0.50	EL504	0.80					6AT6	0.75	6Y6G	0.95	30L17	1.00
EBF83	0.50	EM87	1.50					6AU6	0.40	6Z4	0.85	30P12	1.00
EBF89	0.50	EL222	3.00					6AV6	0.50	7B7	0.80	30L13	1.10
EC52	0.40	EM31	0.75					6AX5GT	1.00	7V4	0.60	30P14	1.10
ECC81	0.55	EM80	0.60	PL82	0.50	UM84	0.40	6B07A	0.60	902	0.60	35L6GT	1.00
ECC82	0.50	EM81	0.60	PL83	0.50	UY82	0.55	6B7	0.75	906	0.75	35W4	0.60
ECC83	1.15	EM84	0.40	PL84	0.85	UY85	0.50	6B6A	0.40	906	0.60	35Z4GT	0.70
ECC84	0.45	EM87	1.00	PL504	1.40	VR105/30	1.80	6BE6	0.50	10C2	0.60	50C5	0.70
ECC85	0.50	EY51	0.45	PL508	1.30	VR150/30	1.25	6BE6	0.50	10F18	0.60	50C6G	1.20
ECC86	1.25	EY81	0.45	PL509	3.25	X66	0.75	6BG6G	1.00	10P13	0.80	50C7	1.00
ECC88	0.60	EY86/87	0.55	PL802	2.80	X61M	1.50	6B6G	1.10	11A2	1.10	75C1	0.80
ECC189	0.80	EY88	0.55	PL80	1.80	Z800U	3.00	6B07A	0.60	12A6	0.60	76	0.80
ECF80	0.50	EZ60	0.45	PY33	0.60	Z801U	3.50	6BR7	2.30	12AT6	0.45	78	0.75
ECF82	0.45	EZ81	0.60	PY80	0.60	Z900T	1.50	6C4	0.40	12AT7	0.55	80	0.75
ECF801	0.75	GY501	0.90	PY81/800	0.55	1A3	0.60	6C6	0.55	12AU7	0.50	85A2	2.20
ECM34	0.95	GZ32	0.65	PY82	0.45	114	0.30	6CH6	3.00	12AV6	0.70	723A	11.00
ECM35	1.85	GZ33	3.50	PY83	0.50	12A7	0.50	6CL6	0.75	12B6	0.50	80C3	6.00
ECM42	0.85	GZ34	2.00	PY88	0.65	1R5	0.50	6C16	0.75	12B6	0.50	80C5	18.00
ECM81	0.45	GZ7	7.50	PY88	0.65	1S4	0.40	6C75	0.80	12B6	0.60	8105	18.00
ECM84	0.95	KT66	4.00	PY500	1.35	1S5	0.40	6D6	0.50	12B6	0.60	8105	18.00
ECL80	0.60	KT88	5.75	PY859	5.75	1T4	0.40	6E8A	0.80	12B6GT	0.60	813	19.50
ECL82	0.55	MH4	1.00	PY801	0.60	1U4	0.60	6F6G	0.90	12C8	0.55	8228	11.00
ECL83	1.20	ML6	1.00	QV03-12	2.50	1X28	1.10	6F8G	0.75	12E1	4.25	839A	4.50
ECL85	0.85	OA2	0.55	QV03-12	2.50	2021	0.55	6F12	0.85	12K7GT	0.60	866A	2.80
ECL86	0.55	OB2	0.60	QV06-40A		2K25	11.00	6F14	0.80	12K8GT	0.70	831A	6.00
EF37A	1.50	PARC80	0.40		14.00			6F15	0.80	1207GT	0.50	955	0.95
EF39	2.90	PC85	0.50	QV03-12	2.00	3A4	0.60	6F17	1.00	1207GT	0.50	955	0.95
EF40	0.70	PC86	0.85	SC1/400	4.00	306	0.60	6F24	0.90	12SC7	0.55	956	0.95
EF41	0.75	PC88	0.75	SC1/600	4.00	3D21	20.00	6F33	4.20	12SH7	0.70	957	0.90

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free, minimum order £1.


A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

COLOMOR 907353/ London
(ELECTRONICS) LTD.
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

The professional scopes you've always needed.

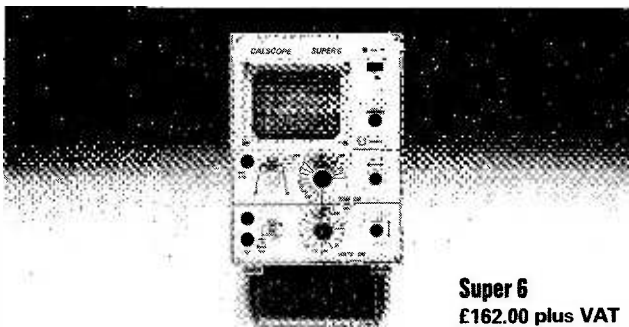

Super 6
£162.00 plus VAT

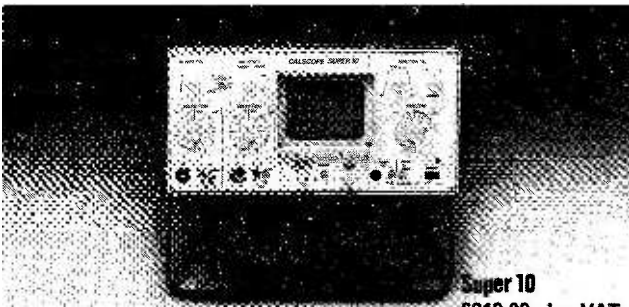

Super 10
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

CALSCOPE DISTRIBUTED BY
Marshall's Electronic Components,
Kingsgate House,
Kingsgate Place,
London, N.W.6.

Audio Electronics,
301 Edgware Road, London W.2.
Tel: 01-724 3564
Access and Barclay card facilities
(Personal Shoppers)

Maplin Electronics Supplies Ltd.
P.O. Box 3
Rayleigh, Essex.
Tel: 0702 715 155
Mail Order

CALSCOPE

You know it's easy with Heathkit.

Electronics Courses

New series of courses on car electrical systems.
New series of courses on electronic equipment.
DC electronics.
AC electronics.
Semi-conductors.
Electronic circuits.
Digital techniques.
Microprocessors.

Heathkit self-instruction electronics courses are complete, low-cost learning systems. All you need is the will to learn and the Heathkit courses will teach you at your own pace.

It's easy because the courses are based on step-by-step programmed instructions, with audio records (or optional cassettes), self evaluation quizzes to test your understanding, and interesting experiments that encourage you to learn the easy "hands-on" way with the optional Heathkit experimenter-trainers.

Thousands of people just like you have already learnt electronics the easy Heathkit way - at home, in educational establishments and in industry throughout the world.

You'll find it easy too. Full details are in the Heathkit catalogue, together with hundreds of kits you can build yourself, for the home, car and workshop.

Send for your copy now.



New Kits

Line printer.
Dual floppy disc.
Dual trace 5MHz and 35MHz oscilloscopes.
Memory expansion for digital trainer.
2M hand-held transceiver.

To Heath (Gloucester) Limited, Dept PW 3/79, Bristol Road, Gloucester GL2 6EE. Please send the items I have ticked.
 Heathkit catalogue (enclose 20p in stamps). Computer brochure (enclose 20p in stamps).

Name _____
Address _____

NB. If you are already on the Heathkit mailing list then you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon. Registered in England, number 606177.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester. (Gloucester 29451).



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

COMMUNICATION

AM/CW/SSB/RECEIVER and preselector modules. 453.5 kHz Mesh Filter Modules 2.1 kHz BW, with diode-switching. **CRYSTALS** Brand new high precision HC33/U: 1.0, 2.0, 3.0, 1.008, 2.5625 MHz £3.35, 1.28 MHz £4.15, HC13 100 kHz £3.25, HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 10.0, 10.7, 10.7, 18.0, 20.0, 38.6667, 48.0, 100.0, 116.0 MHz £3.50, HC25/U 0.80333 MHz (S20) £3.00. Large stocks of standard freqs for MPU etc. Any freq made to order 6 weeks from £3.75.

WINKLE PICKERS Winkle out DX from the QRM with pin-sharp 250 Hz 8-pole crystal CW filters specially manufactured to fit TRIO and YAESU: FT/FR-101, FT-301, TS-520, TS-820. £25.90 each. All prices inc. VAT and UK post. SAE Lists.

P. R. GOLLEGE ELECTRONICS, G3EDW, Meriott, Somerset, TA16 5NS. Tel. 0460 73718.

ATTENTION SWL'S & DXers. HIGH QUALITY, LOW COST equipment. ATU's PRESELECTORS etc., covering medium & short wave. S.A.E. Details. AMTEST, 55 Vauxhall Street, Worcester WR3 8PA.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V. 0.47, 1.0, 2.2, 4.7 & 10 mfd.—5p. 22, 47—5½p. (50V—6p). 100—7p. (50V—8p). 220—8p. (50V—10p). 470—11p. (50V—16p). 1000/15V—15p. 1000/25V—18p. 1000/40V—35p.

Subminiature bead tantalum electrolytics. 0.1, 0.22, 0.47, 1.0 at 35V & 4.7 at 6.3V—5p. 2.2/35V & 4.7/25V—9p. 10/25V & 15/16V—12p. 22/16V, 33/10V, 47/6V, 68/3V, 100/3V—14p.

Subminiature Ceramic Caps. E12 Series 100V. 2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p. 10% 390 pf. to 4700 pf.—4p.

Vertical Mounting Ceramic Plate Caps. 50V. E12 22 pf.—1000 pf.—E6 1500 pf. to 47000 pf.—2p.

Polystyrene E12 Series 63V. Horizontal Mtg. 10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p.

Miniature Polyester 250V Vert. Mtg. E6 Series. .01 to 0.1—4p. .15 & .22—5p. .33 & .47—8p. 0.68—11p. 1.0—14p. 1.5—20p. 2.2—23p.

Mylar (Polyester) Film 100V. Vertical Mtg. .001, .002, .005—3½p. .01, .02—4½p. .04, .05—5½p.

Miniature resistors Highestab. 5% E12 Series. 0.125W mixed metal/carbon film 10Ω—2MΩ—1p. 0.25W carbon film 1Ω—10MΩ (10% over 1MΩ)—1p. (E24 series in ½W c. film 2.0Ω—2MΩ only). 0.25W, 0.5W & 1W metal film 2.0Ω—2MΩ—2p. 1N4148—2p. 1N4002—4p. 1N4006—6p. 1N4007—7p. BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—9p. 8 pin i.c.'s 741 Op. amp.—18p. 555 timers—24p. 20 mm. fuses—15, 25, 5, 1.0, 2.0, 3.0 & 5A—3p. Printed circuit fuseholders for 20 mm. fuses—5p. 400 mW. Zener diodes E24 series 2V7—33V—8p.

Prices VAT inclusive Post 10p. (free over £4.00.)
THE C.R. SUPPLY CO.
127, Chesterfield Rd., Sheffield S8 0RN

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Tel: 31803. No Lists. Enquiries S.A.E.

SMALL ADS

The prepaid rate for classified advertisements is 22 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

THE VINTAGE WIRELESS COMPANY 1920 to 1950

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet.
THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.

CODESPEED Electronic Mail Order

TO3 HEAT SINKS !!! Two types of heat sink. Equipment, but condition as new. Most still contain a power transistor (condition unknown). 'Christmas tree' type, 92 x 66 x 35 mm **20p each**. Rectangular type 130 x 63 x 32 mm **30p each**. Please add 25p per heat sink post and packaging.

PACK M1 2 Calculator keyboards. Each has 17 keys and two switches. Only **£1.00**.

PACK M2 1 x 2102, a 1024 bit static RAM. The most popular of all RAM's in professional or amateur electronics. With data sheet **£1.25**.

PACK M3 Build your own calculator! MM5725 calculator chip and data book. (Not compatible with Pack M1) **£1.00**.

CALCULATOR PACK M4 Contains a production line reject calculator. Either fix them (not much wrong with some we checked) or strip them for spares (which ever part is defective the rest must be good value for money—case/keyboard/display/chip/PCB). We include all the info. we can find on repairing calculators. What a bargain at **£2.50**.

PACK C1 10 x 12 pin Hybrid circuits each containing 16 resistors/capacitors. Useful values. Ideal for semiconductor circuits and PCB miniaturisation. With data 10 hybrid circuits for **50p**.

PACK P1 An MM5330 Digital Voltmeter I.C. Now build your own digital multimeter or panel meter using this versatile chip.

With data and circuit diagram **£3.95**.
PACK T3 1 x MM5316 Digital Alarm Clock I.C. 12 or 24 hour. Will drive LED, LCD or fluorescent disc plays. With full instructions **£2.75**.

PACK T4 1 x 0.8" giant multiplexed red LED Clock Display. Common cathode, 3½ digit with amp/m indicator. An excellent display for your digital clock project at only **£3.95**.

PACK E2 An 8 digit calculator style Liquid Crystal display. 0.33" high digits with right hand decimal points and overflow indicator. With data. **£2.95**.

PACK E3 Same as Pack E2 but with 0.5" high digits. **£4.25**.

PACK E6 Contains a brand new 6 digit Texas Instruments LED display. Multiplexed with built-in bubble magnifiers. 0.1" high digits. Common cathode. **£1.00**.

PACK E8 A miniature 5 digit, 7 segment 0.09" common cathode LED display. Mounted on 16 pin dual-in-line I.C. package. Terrific value at only **75p**.

Satisfaction guaranteed or return complete pack for replacement or refund

Postage and Packaging please add 25p (Overseas orders add 60p)

For free catalogue send stamped addressed envelope

CODESPEED, P.O. Box 23, 34 Seafield Road, Copnor, Portsmouth, Hants. PO3 5BJ

VALVES

Radio—T.V.—Industrial—Transmitting

Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 30p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.
Dept. P.W. The Parade, East Wittering,
Sussex BN16 9UN
West Wittering 2023 (STD Code 024366)

D.V.M. THERMOMETER KIT



Based on the ICL7106 single chip DVM the kit contains a 3 digit LCD, a PCB ICL7106, and all components and instructions to make a 0-200mV FSD DVM. Components also supplied to enable this to be converted to a digital thermometer. Requires a 2mA 9V supply (PP3 battery). **ONLY £21.99**

TOUCH CONTROLLED LIGHTING KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touch plates. Easy to follow instructions.

NEW! TD300K—TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. **£8.99**

Extension kit for TD300K permits operation from another location, two-way switching, etc. **£1.50**

TSD300K—TOUCHSWITCH-DIMMER—One alternate ON/OFF action. Small knob for presetting lamp brightness. **£5.50**

TS300K—ON/OFF TOUCHSWITCH. Two touch-plates **£4.30**

TSA300K—AUTOMATIC TOUCHSWITCH. Time delay variable 2 secs to 3½ mins. **£4.30**

LD300K—300W LIGHTDIMMER KIT **£3.00**

24 HR. CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs and full instructions. **£14.90**

White box 56 x 131 x 71 mm with red Acrylic window. **£2.20**

White box as above ready drilled for kit **£2.50**

Ready-built in box, incl. mains cable **£22.50**

400V PLASTIC TRIACS	OPTO	COMPONENTS
3A 58p	0.2" dia LEDs	955 28p (4 @ £1)
8A 74p	Red 12p (E1/10)	741 22p (5 @ £1)
12A 84p	Green 20p	LM3911
15A 105p	Yellow 25p	Temperature control IC £1.00
20A 166p	DL727 £1.50	ZN1034E £1.80
25A 190p	LCD 0.5" £8.10	ICL7106 £9.25
6" with trigger 50p	LDR sim	TIC106D SCR 60p
8A* 80p	DRP 50p	Diac 20p
* Isolated tab	Neon 8p	2N6027 34p
		AY-5-1230 £4.50

QUANTITY DISCOUNTS ON REQUEST

ADD 8% VAT + 25p P&P. Callers by appointment only.

T. K. ELECTRONICS
106 STUDLEY GRANGE ROAD, LONDON W7 2LX

GRADE 1 semiconductors, passives, hardware, + security. Immediate services.—Texas 1N4148 £1.50 per 100.—RCA. CD4001/11 18p.—RCA. 741 8 pin dil. £1.00 per 5.—555 £1.00 per 4.—CEH. PC. housings 60p. Capacitors, resistors, keyswitches, Texas IC. sockets, control panels. S.A.E. brings complete catalogue.—CEH Audio-Visual (F), 48 Whistler Road, Tombridge, Kent.

Record Accessories

STYLI for Hi-Fi. Music Centres. III. List free for S.A.E. also cartridges, leads, accessories. Details—**FELSTEAD ELECTRONICS (PW)**, Longley Lane, Gatley, Cheshire, Chas. SK8 4EE.

Tapes

Tapes. Low noise cassettes. Free library cases. Delighted or money back. C60 six or more 29p each. Sample 32p. No more to pay. A. W. & J. M. West, 56 Frankwell Drive, Coventry CV2 2FB.

Service Sheets

REG. OFFICE 14B QUEENS PARADE, NORTH EALING W5 3HU

SERVICE SHEETS—COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders £1. Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers by return of post
**B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON
 H.M.V. MARCONI AND MANY MORE**

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court. S.A.E. for details. MAIL ONLY TO

G. T. TECHNICAL INFORMATION SERVICE
 10 Dryden Chambers, 119 Oxford St., London W1R 1PA

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 24p, plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

LARGE SUPPLIER OF SERVICE SHEETS

and Colour Manuals, TV Mono Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E. except colour TV and Car Radios. State if Circuit will do, if sheets are not in stock. All TV Sheets are full lengths 24 x 12, not in Bits & Pieces. Free Fault Finding Chart or TV Catalogue with order.

C. CARANNA
 71, Beaufort Park, London, NW11 6BX
 01-458 4882

Educational

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford RM7 0XU (Tel: Romford 66841).

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. E277 Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. E277 Intertext House, London SW8 4UJ
 Tel. 01-622 9911 (all hours)
 State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
 Dept. E277 Intertext House, London SW8 4UJ
 Tel. 01-622 9111 (all hours)
 State if under 18

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Ladders

LADDERS varnished 22" extd. £30. Carriage £2-80. Leaflet. Also Alloy ext. up to 62½ft. **LADDER CENTRE** (WLS3), Halesfield (1), Telford. Tel: 586644.

Wanted

WANTED Constructor to assemble an electronic steam whistle and model train Chuffer. Full instructions and most parts supplied. N. Taylor, 27, Nethergate Street, Bungay, Suffolk.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1-00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 King's Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc., with free fault-finding guide, from 50p and S.A.E. Catalogue 25p, and S.A.E. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex.

Equipment Wanted



Tempting prices paid for

Oscilloscopes · Signal Generators
 DVM's · Small Computers
 Receivers · Teletypes · VDU's etc.

Electronic Brokers Ltd
 49/53 Pancras Road
 London NW1 2QB
 Telephone 01-837 7781

For Sale

BACK ISSUES FROM 1955. P.W.P.E. P.T. R.C. 35p plus post or exchange. Telephone Amersham 22434.

NEW BACK ISSUES OF "PRACTICAL WIRELESS" available 70p each, post free. Open P.O. Cheque returned if not in stock—**BELL'S TELEVISION SERVICE**, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

	Price	Post/Pack.	
Circuit Breakers 50A Triple Pole	£5.00	£1.00	
30A 4 Pole 50V coil contactor	£1.50	£1.00	
40A 3 Pole 24V coil contactor	£1.50	£1.00 O.A.T.	
Transformer 115V-230V Prim.			
950V-900V ct sec.	£3.00	£2.00	
Collins output trans. 20,000 Ω ct			Plus V.A.T.
800 Ω ct	50p	50p	
Collins output trans. 12,000 Ω ct			
600 ct	50p	50p	
Call and see our wide range of surplus electronic equipment. Closed all day Tuesday.			
SKIPTON ELECTRONIC SUPPLIES 29, Keighley Road, Skipton, Nr. Yorks. Tel. 0756-4397.			

SEEN WHISTONS CAT? 5,000 odds and ends. Mechanical/Electrical Cat Free. **WHISTON** (Dept. PW), New Mills, Stockport.

PRACTICAL WIRELESS. May 70 to Dec. 78. Perfect condition. Enquiries: 0782 321487.

Books and Publications

COMPREHENSIVE TV REPAIR INSTRUCTIONS for your set £5-00 with circuit (if requested). Free catalogue unique TV/other publications. **AUSE (PW)**, 76 Church Street, Larkhall, Lanarkshire ML9 1HE.

Build your own P.A., GROUP & DISCO SPEAKERS by R.F.C. Stephens

Save money with this practical guide. Plans for 17 different designs. Line source, I.B., Horn and Reflex types, for 8"-18" drive units. **£3-95** post free (£8 overseas).

THE DALESFORD SPEAKER BOOK by R.F.C. Stephens. This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B. and Reflex designs for 10-100 watts. Also unusual centre-bass system. **£2-20** post free (£5 overseas).

VAN KAREN PUBLISHING
 5 SWAN STREET, WILMSLOW, CHESHIRE.

WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS. A genuine opportunity to success. **LARGE PROFITS.** You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. **NO PREVIOUS KNOWLEDGE IS REQUIRED**, as the manual covers in 13 chapters, where to obtain all the work you need, materials required, all instructions, rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. **£4-00** plus 30p P&P. UK. CWO, to **INDUSTRIAL SUPPLIES**, 102, Parrswood Rd., Wittington, Manchester 20, Dept. PW.

RADIO BOOK SERVICE

WORLD RADIO TV HANDBOOK 1978 Edition £8-28
 50 CMOS IC Projects (R. A. Penfold) £1-05
 A Practical Introduction to Digital IC's £1-05
 28 Tested Transistor Projects (R. Torrens) £1-05
 50 Projects using Relays, SCR's & TRIAC's (F. G. Rayer) £1-20
 How to build your own Metal & Treasure Locators (F. G. Rayer) £1-10
 Practical Repair & Renovation of Colour TV's (C. F. Miller) £1-05
 Fun & Games with your Electronic Calculator (J. Vine) £0-85
 How to build Advanced Short Wave Receivers (R. A. Penfold) £1-30
 Radio Antenna H'book for Long Distance Reception £0-95
 50 (Fet) Field Effect Transistor Projects (F. G. Rayer) £1-35
 Servicing Transistor Radio Receivers £0-85
 Solid State Short Wave Receivers for Beginners £1-05
PRICES INCLUDES POSTAGE & PACKING...S.A.E. FOR FULL LIST

4 CAILCHESTER COURT, WICKHAM 99, BEXHEAM WIMBORNE SQW

Miscellaneous



BELLS AND SIRENS
 CARTERS SIREN £5.53
 INDUSTRIAL SIX INCH
 BELL £8.27
 PRICES INCLUSIVE



BARGAIN OFFER 12v D.C.
 The incredible value of this self-contained smoke detector/fire alarm, similar unit of which normally sell for between £30-50, is enough to warrant special note. The Dormalarm uses the professional ionisation chamber principle with a radio active source of less than one microcurie of Americium 241, which detects the products of combustion at the very earliest stage. It is powered by a single 9V Mallory Duracell MN 1604 battery (supplied) which will last greater than one year. The built-in sounder is very loud (85dB at 3 metres). When the battery is running low, the Dormalarm will give periodic beeps, reminding you to change the battery. As there is no wiring, installation is simplicity itself—just 3 screws. The whole unit is contained in an attractive circular white ABS moulded case, size 175mm diameter x 37mm. **PRICE—AN INCREDIBLE £18.95 INCLUSIVE.** Trade enquiries welcome. Send Cheque, P.O. to:

CWAS ALARM
 11 Denbrook Walk, Bradford BD4 0QS.
 SAE for full Price List of
 Professional Burglar Alarm Equipment

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept. No. 25, St. Wilfreds, Foundry Lane, Halton, Lancaster LA 6LT.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. **£1-25** for Booklet 'Nickel Cadmium Power' plus Catalogue. Write or call: Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764 or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

SINGLES HOLIDAYS/Houseparties. Friendship introductions. Free details—Christian Friendship Fellowship, Dept. B89, Edenthorpe, Doncaster (S.A.E.).

ALFAC etch resist transfer and other p.c. board drawing materials available from stock. S.A.E. details. **RAMAR CONSTRUCTOR SERVICES**, Masons Road, Stratford upon Avon CV37 9NF.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
Reg. Office 22 Coningsby Gdns

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

14 & 16	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT
SAE brings list of copper & resistance Wires
Dealer Enquiries Invited

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
Cassette B: 12-24 w.p.m. for professional examination preparation.
Morse by light systems available. Morse Key and Buzzer Unit for sending practice.
Price each Cassette (including booklets) £4-50. Morse Key and Buzzer £4-50.
Prices include postage etc., Overseas Airmail £1-50 extra.
MHEL ELECTRONICS (Dept. P.W.), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

GUITAR/PA/MUSIC/AMPLIFIERS

100 watt with superb treble bass overdrive, 12 months guarantee. Unbeatable at £40; 50 watt £35; 200 watt £56; Twin channel sep treble/bass per channel £52; 60 watt £46; 200 watt £69; 100 watt four channel sep treble/bass per channel £65; 200 watt £79; Slaves 100 watt £32; 200 watt £48; Fuzz boxes great sound £7-90; Bass fuzz £8-50; 100 watt combo superb overdrive, sturdy construction, castors, unbeatable £85; Twin channel £95; Bass Combo £95; Speakers 12in, 100 watt £22-50; 60 watt £14-50; Shure mic unidyne B £26.

Send Cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Ave, Dukinfield, Cheshire.
Tel. 061-344 5007

Resistors 1/2W 5% 2R2-2M2 (E12). 10 each or more of each value 90p/100. 100 assorted, our mixture 75p/100. C60 cassettes in library cases 30p each. Miniature relays 17 x 30 x 28mm 6000 coil 4 sets change over contacts 50p each. Prices include V.A.T. Add 10% postage.

SALOP ELECTRONICS

23 Wyle Cop, Shrewsbury.



TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield.
- Speaker and earphone operation
- 4,000 already sold
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete **£15-95** Built & tested **£20-95**
Kit Post £1-29+£1-77 VAT Post £1-29+£1-77 VAT

MINIKITS ELECTRONICS,
5a CLEVELAND ROAD,
LONDON, E18 2AN

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP7 (AA) £1-13, SUB C £1-47, HP 11 (C) £2-15, HP 2 (D) £3-27, PP3 £4-09 (PP3 not suitable for fast charge), PP3 charger £5-31. All above Nickel Cadmium batteries are guaranteed 'EVER READY' full spec. and are supplied complete with solder tags (except PP3). Just in stock—New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc., 1-2 amp hr. 6v. £4-40 6 amp hr. 6v. £5-65.

Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type), all prices include VAT. Please add 10% P & P on orders under £10, 5% over £10.

Cheques, postal orders, mail order to: **SOLID STATE SECURITY DEPT. PW., 10, Bradshaw Lane, Parbold, Wigan, Lancs. 0257-4726.**

AERIAL BOOSTERS Improve weak VHF Radio and Television reception, price £5-00 S.A.E. for Leaflets. **ELECTRONIC MAILORDER LTD.,** Ramsbottom, Bury, Lancashire BL0 9AG.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

DX DOWN?

QRM UP? NOW you can dig RARE DX from tiring whistles and cw with a Tunable Audio Notch Filter, inc. speaker amplifier, £8-90.

V.L.F.7 10-150 KHz Receiver only £10-70.

MISSING RARE DX? Crystal Calibrator, 1 MHz, 100, 25 KHz markers to vhf. £13-80.

SIG. GEN., 10Hz-200KHz, sine/square, £10-80.

ANTENNA NOISE BRIDGE, 1-150 MHz, £9-80.

HOW LOW CAN YOU GO? 100-600 KHz to 4-1-4-6 MHz Converter, snoop low for £9-90.

Europe add 40p. Giro 21-923-4000. Each easy-assembly kit includes all parts, printed circuit, case, postage etc., money back assurance so SEND off NOW.

CAMBRIDGE KITS
45 (PQ) Old School Lane, Milton, Cambridge.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager

PRACTICAL WIRELESS,
GMG, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5846

Rate
22p per word, minimum 12 words. Box No. **60p** extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS				
Ref	Amps	£	P & P	OA
111	0.5	2.20	0.45	
213	1.0	2.64	0.78	
71	2	3.81	0.78	
18	4	4.03	0.96	
85	0.5	5.35	0.96	
70	6	5.35	0.96	
108	8	7.42	1.14	
72	10	8.12	1.14	
116	12	8.99	1.32	
17	16	10.72	1.32	
115	20	13.98	1.32	
187	30	15.05	2.08	
226	60	36.74	OA	

30 VOLT RANGE				
Ref	Amps	£	P & P	OA
112	0.5	2.64	0.78	
79	1	3.57	0.96	
20	2	5.77	0.96	
21	4	7.99	1.14	
111	5	9.87	1.32	
57	6	11.17	1.45	
88	8	14.95	1.64	
89	10	17.25	1.84	

50 VOLT RANGE				
Ref	Amps	£	P & P	OA
102	0.5	3.41	0.78	
103	1	4.57	0.96	
104	2	7.16	1.14	
105	3	8.56	1.32	
106	4	11.41	1.50	
107	6	15.06	1.64	
118	8	20.28	2.08	
119	10	24.98	OA	

60 VOLT RANGE				
Ref	Amps	£	P & P	OA
124	0.5	3.88	0.96	
126	1	5.91	0.96	
127	2	7.60	1.14	
125	3	11.00	1.32	
123	4	12.52	1.84	
120	5	15.84	1.64	
120	6	18.06	1.84	
121	8	25.56	OA	
122	10	29.55	OA	
189	12	34.06	OA	

MAINS ISOLATORS (SCREENED)				
Ref	VA (Watts)	£	P & P	OA
107	20	4.40	0.79	
149	60	7.00	1.14	
150	100	7.61	1.14	
151	200	11.16	1.50	
152	250	13.28	1.84	
153	350	16.43	1.84	
154	500	20.47	2.15	
155	750	29.06	OA	
156	1000	37.20	OA	
157	1500	51.38	OA	
158	2000	81.81	OA	
159	3000	86.66	OA	

AUTO TRANSFORMERS				
Ref	VA (Watts)	£	P & P	OA
113	150-0-115-210-240V	2.48	0.71	
64	75-0-115-210-240V	4.01	0.96	
4	150-0-115-200-220-240V	5.35	0.96	
67	500-0-115-200-220-240V	10.99	1.94	
84	1000-0-115-200-220-240V	18.76	2.08	
93	1500-0-115-200-220-240V	23.36	OA	
95	2000-0-115-200-220-240V	34.82	OA	
73	3000-0-115-200-220-240V	59.21	OA	
80	4000-0-115-200-220-240V	79.86	OA	
57	5000-0-115-200-220-240V	89.50	OA	

HIGH VOLTAGE ISOLATORS				
Ref	VA	£	P & P	OA
60	243	6.70	1.32	
350	247	16.43	1.84	
1000	250	37.10	OA	
2000	252	61.81	OA	

CASED AUDIO TRANSFORMERS				
Ref	VA	£	P & P	OA
75	7.73	1.14	64W	
150	10.01	1.14	4W	
200	9.92	1.45	65W	
250	10.49	1.45	69W	
500	19.17	64	67W	
750	23.41	1.76	83W	
1000	27.88	OA	84W	
1500	26.02	OA	93W	
2000	49.97	OA	95W	

SEN0 15p FOR CATALOGUE Prices correct 21-11-78. Please add VAT after P & P.

SCREENED MINIATURES				
Ref	mA	Volts	£	P & P
238	200	3	2.57	0.55
212	1A, 1A	0.6-0.6	2.85	0.78
13	100	9-9	2.14	0.38
235	330, 330	0.9-0.9	1.99	0.38
207	500, 500	0.8-9, 0.8-9	2.77	0.71
208	1A, 1A	0.8-9, 0.8-9	3.53	0.78
236	200, 200	0.15-0.15	1.99	0.38
214	300, 300	0.20-0.20	2.80	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0.15-20-0-15-20	4.63	0.96
203	500, 500	0.15-27-0-15-27	3.99	0.96
204	1A, 1A	0.15-27-0-15-27	6.04	0.96
239	50	12-0-12	2.57	0.38

COMPONENT PACKS				
65	1W Metal Oxide Resistors.	100V	100A*	£2.10
65	1W Metal Oxide Resistors.	100V	2A	£0.45
150	Mixed Value Capacitors.	400V	4A	£0.85
400V	10 Reed Switches.	6A	6A	£1.25
50	Wire Wound Resistors.	500V PM7A6	12A*	£2.85
10	3000 F30V Capacitors.	VAT 12½%	15p P & P*	VAT 8%
25	Assorted presets.	66p		VAT 8%
50	3 tag terminal strips.			
Hardware	8A nuts, bolts.			
200	Mixed Resistors.			
Each pack	70p.			
P & P	40p.			VAT 12½%

BRIDGE RECTIFIERS				
100V	100A*	£2.10		
100V	2A	£0.45		
400V	4A	£0.85		
400V	6A	£1.25		
500V PM7A6	12A*	£2.85		
VAT 12½%	15p P & P*	VAT 8%		
66p				VAT 8%

TEST METERS				
AVO 8 Mk5	£81.70	Megger BM7 battery		
AVO 71	£33.50	£45.15		
AVO 73	£44.20	U4315 Budget Meter		
AVO MM5	£28.66	20KΩ/V Ranges to		
Veg Megger	£66.90	1000V, 2.5A AC/DC		
EM272	£52.70	500KΩ. In steel case		
DA 16 digital	£102.00	£15.85		
AVO T1169 In circuit Transistor Tester	£34.75			
P & P	£1.15	VAT 8%		

250VA ISOLATOR				
0-200-220-240V	Sec 0-240V C.T.			
250VA	£5.20.	P & P	95p.	Ref. 62.

15V RANGE				
0-C.T. 15V.				
Ref	Price			
171	500 mA	2.09	45	
172	1A	2.96	78	
173	2A	3.59	78	
174	3A	3.75	86	
175	4A	5.73	86	

MINI-MULTIMETER				
DC-1000V AC-1000V DC-100mA Res-150kΩ				
1000Ω/V Bargain	£7.20.	VAT 8%	P & P	62p.

Aluminium Boxes—with ½" lip lid & screws.				
B1	5 ½"	2 ½"	1 ½"	62p
B2	4	4	1 ½"	62p
B3	4	2 ½"	1 ½"	62p

S-DECS				
Solderless bread boarding				
S Dec 70 contacts	£3.10			
T Dec 208 contacts	£4.35			
U Dec "A" for I.C.s etc	£4.50			
U Dec "B" for I.C.s etc	£6.99			
P & P	8p.	P & P	40p.	

NEW RANGE TRANSFORMER				
Pri 120V or 220/240V	Sec 0-36-48	twice to give		
36-0-36V	48-0-48V	72V or 92V.		

ANTEX SOLDERING IRONS				
15W	£3.75	Stand	£1.52+	VAT 12½%
25W	£3.95	Stand	£1.52+	VAT 12½%

Electronic Construction Kit				
Home electronic teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box, full instructions.				
£8.29 + 96p P & P.	VAT 8%.			

PANEL METERS				
43mm x 43mm	82mm x 78mm			
0-50µA	0-50mA	£6.70		
0-500µA	0-500mA	£6.70		
0-1mA	0-10mA	£6.70		
0-30V	0-30V	£6.70		
VU Ind. Panel 90mm x 25mm		£3.36		
VU Ind. Edge 54mm x 14mm 250µA FSD		£2.60		
650 Carriage	8% VAT.			

ABS PLASTIC BOXES				
inset brass nuts, slots to take P.C. cards flush fitting lid.				
PB1 180mm x 62 x 40	65p			
PB2 100mm x 75 x 40	73p			
PB3 120mm x 100 x 45	87p			
PB4 215mm x 130 x 85	£2.54			
P & P	29p*	VAT 8%.		

Magnetic to Ceramic Cartridge Converter				
MPA 30				
Operating voltage 20-45V				
P & P	44p.	VAT 12½%.		

Special Offer—Quality low noise cassette tapes. £60 30p, C90 42p. P & P 15p VAT 8%.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEW! HANDBOOK TIPS!

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2½in x 2½in). £3.50 DOZEN.

DOUBLE UNITS (2D) (5in x 4½in x 2½in). £5.50 DOZEN.

TREBLE (3D) £5.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D) £7.90 for 8.

EXTRA LARGE SIZE (6D1) £6.90 for 8.

PLUS QUANTITY DISCOUNTS

Orders over £20, less 5%. Orders over £60, less 7½%. PACKING/POSTAGE CARRIAGE: Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage. Quotations for larger quantities. Please add 8% V.A.T. to total remittance. All prices correct at time of going to press.

4-WAY IN-LINE 13 AMP POWER PANEL

Modern, slim-line power panel, countless uses in home, office, factory, showroom. Perfectly safe, unbreakable. Can be mounted on wall or trailed anywhere in room. Neat rubber base. Smart PVC outer cover. White £3.30 P & P 60p.

FLAIRLINE SUPPLIES (Dept. PW3)
124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices—signal diodes, high voltage rectifiers and zeners may all be included. These are being offered at the incredibly low price of £1.25/1000—or a bag of 2500 for £2.25. Bag of 10,000 £8. Box of 25,000 £17.50. Box of 100,000 £62.

50 Diode Circuits Book 75p.

PC ETCHING KIT Mk III

Now contains 200 sq. ins. copper clad board, 1lb Ferric Chloride. DALO etch resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25.

RELAYS

W847 Low profile PC mntg 10 x 33 x 20mm 6V coil, SPCO 3A contacts. 93p.

W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole 0/rated 10A. 95p.

W877 675R 12-27V DPCO 23 x 20 x 10mm sealed can. 88p.

W880 230V ac DPCO 10A contacts, enclosed case. £1.30.

W930 200R 8-12V DPCO 23 x 20 x 10mm sealed can. 88p.

Send S.A.E. for illustrated relay list.

1979 CATALOGUE

64 big pages with 50p discount vouchers + qty prices for bulk buyers + reply paid envelope—All this for just 45p inc. post.

PUSH BUTTON BANKS

Illustrated list of types from 30p in our Bargain List No. 6—Send S.A.E.

OSCILLOSCOPES

We have available from stock the following SCOPEX models: 4D 10A—DC-10MHz; 10mV sensitivity; Stab Power supplies; Dual beam; 3% accuracy; Excellent value at £214 inc. VAT and Carr.

456—DC-6MHz; 10mV sensitivity. Ideal portable scope. Solid state circuitry. All for £150 inc. VAT and Carr.

RESISTOR PACK

Carbon Film 5% mostly ½W, few ¼W resistors. Brand new, but have performed leads, ideal for PC mntg. Wide range of mixed popular values at the unrepeatable price of £2.50 per 1000; £11 per 5000.

DIN SOCKET OFFER

2 pin switched speaker socket, PC mounting; 5 pin 180° PC mntg or chassis mntg (clip fit). All the same price, any mix. 10 for 70p, 25 for £1.60, 100 for £5.50.

BC182B OFFER

Special Offer for quantity users 1k .035 + VAT; 5k .032 + VAT. Price negotiable on 10k Approx. 100k available.

NIXIETUBES

ITT Type GNP7AH. Supplied with data 60p each. 7-seg display, very ended tube NEC type LD8012 ½" high, with data 65p.

7-seg display, (as above) Futaba type DG-10Q10-3" char. 70p with data.</


WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	
AA119	15
AA129	25
AA130	25
AA150	15
AA100	10
BA100	15
BY100	24
BY126	24
BY127	24
CR033	148*
OA9	75
OA47	12
OA70	12
OA79	12
OA81	12
OA85	15
OA90	6
OA91	6
OA95	9
OA200	8
OA202	8
IN914	4
IN400/2*	5
IN400/3*	6
IN400/5*	6
IN400/7*	7
IN4148	27
3A/100V*	20
3A/200V*	20
3A/300V*	20
3A/400V*	20
3A/500V*	20
3A/600V*	20
3A/100V/30	65
3A/600V	65
SCR's Thyristors	
1A50V	38
1A100V	42
1A200V	47
1A400V	52
1A600V	70
3A300V	35
3A600V	43
3A300V	48
3A500V	58
3A600V	55
12A300V	59
12A500V	92
12A600V	38

OPTO ELECTRONICS*	
LEDS - Clip	7
TIL209 Red	13
TIL211 Gm	18
TIL212 Yellow	22
0.2" Red	15
0.2" Yellow,	0.2
Grn, Amber	19
ORP61	84
ORP12	65
ZN5777	45
OPTO ISOLATORS	
TIL111/2	85
TIL114	95
TIL117	110
VOLTAGE REGULATORS*	
T03 Can Type	Plastic (T0220) case
1A +ve: 5V, 12V,	-ve 0.5A; 5V, 6.2V,
15V, 18V	8.2, 15, 15V
LM309K	135
LM323K	598
LMVRS or 12	150
1A -ve: 5V, 12V	220
TRIACS*	
3A/100V	48
3A/200V	54
3A/300V	54
3A/400V	64
3A/500V	108
3A/600V	108
12A/100V	60
12A/200V	70
12A/300V	70
16A/400V	75
16A/500V	105
25A/800V	295
DIAC's	95
ST2	25
ZENERS	
Rng: 2V7-39V	4
400mW	9p
Rng: 3V3-33V	5
1-3W	17p
VARICAPS	
MVAM115120	7
BA102	25
BB104	40
BB1058	40
BB106	40
Noise Diode	
Z5J	160
ALUM. BOXES with lid	
3x2x1"	48
4x2x1"	68
4x4x1"	68
4x2x2"	94
4x2x3"	78
4x2x4"	64
5x4x2"	82
6x4x2"	88
7x5x2"	114
10x7x3"	148
10x4x3"	142
12x5x3"	165
12x8x3"	220
VEROBOARD*	
Pitch	0.1 0.15 0.1 0.15
(copper clad)	(plain)
2 1/2 x 3 1/2"	48p 39p 31p 24p
3 1/2 x 5"	55p 50p 31p
3 1/2 x 7"	55p 50p 31p
3 1/2 x 9"	62p 67p 50p 43p
2 1/2 x 17"	185p 135p 92p
3 1/2 x 17"	218p 180p 141p 120
4 1/2 x 17"	280p 85p
Plat of 36 pins	85p
Spot face cutter	120p
Pin insertion tool	92p
SOLDERING PEN*	
Spool	325p
Spare Wire (Spool) 80p;	Combs 7p ea.
FERRICHLORIDE*	
1lb bag Anhydrous 85p	+ 30p p. & p.
DALO ETCH RESIST PEN*	
Plus spare tip	75p
COPPER CLAD BOARDS*	
Fibre Single-sided	SRBP
Glass sided	7 5/8"
6" x 8"	75p
6" x 12"	130p 175p
SOLDERON PINS*	
100 pins 50p;	1000 pins 400p
DIL SOCKETS*	
Low Profile (TEXAS)	
8 pin 10p;	14 pin 12p;
16 pin 13p;	18 pin 13p;
20p; 20 pin 27p;	22 pin 30p;
24 pin 30p;	28 pin 42p;
40 pin 55p;	64 pin 220p

SWITCHES*	
TOGGLE 2A 250V	28
SPST	34
DPST	38
DPDT	38
4 pole on/off	54
SUB-MIN TOGGLE	
SP changeover	59
SPST on/off	54
SPST biased	55
DPDT 6 tags	70
DPDT C/OFF	79
DPDT Biased	115
SLIDE 250V	
1ADPDT	14
1ADPDT C/O	13
1ADPDT	15
4 pole 2-way	24
PUSH BUTTON	
Spring loaded	
Latching	
SPST on/off	60
SPST C/over	65
DPDT 6 Tag	85
MINIATURE	
Non Locking	15
Push to make	
Push Break	25
ROCKER: (Black)	
on/off 10A 250V	23
ROCKER: (white)	
5A 250V SP change-over centre off	30
ROCKER: (illuminated, red)	
Bezel 5A 250V SP	52
ROTARY: "Make-A-Switch" Make your own multiway Switch. Adjustable Stop Shafting Assembly. Accommodates up to 6 Wafers	
Mains Switch DPST to fit	69
Break Before Make Wafers, 1 pole/12 way, 2p/6 way, 3p/4 way, 4p/3 way, 6p/2 way	64
Spacer and Screen	47
ROTARY: (Adjustable Stop)	
1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way	41
ROTARY: Mains 250V AC, 4 Amp	45
PW PROJECTS	
General Coverage Receiver, Chromachase, 24hrs. Digital Clock, "JUBILEE" Electronic Organ, General Purpose SW Receiver, Gas & Smoke Sensor Alarm, Metal Locator, "PURBECK" Oscilloscope, Audio Distortion Meter, "AVON" 2m FM Transmitter. Acoustic Delay Line.	
Send SAE 5p per list.	

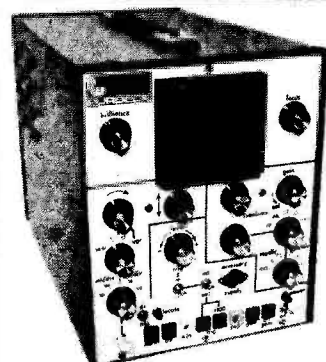

"PURBECK OSCILLOSCOPE"
 AUTHOR APPROVED PARTS including PCBs available.
 Cathode Ray Tube 3BPI £7.75*
 (p & p insured 90p).
 Send S.A.E. for leaflet.

74LS* (TEXAS)	
74LS00 13	74LS47 63
74LS01 13	74LS48 120
74LS02 14	74LS49 120
74LS03 14	74LS51 24
74LS04 14	74LS52 28
74LS05 23	74LS53 30
74LS08 22	74LS63 150
74LS09 22	74LS73 48
74LS10 20	74LS74 41
74LS11 22	74LS75 48
74LS12 23	74LS76 40
74LS13 38	74LS78 40
74LS14 75	74LS83 115
74LS15 30	74LS84 115
74LS20 20	74LS86 43
74LS21 22	74LS90 38
74LS22 22	74LS91 104
74LS26 48	74LS92 89
74LS27 28	74LS93 89
74LS28 48	74LS95 116
74LS30 22	74LS96 116
74LS32 22	74LS102 44
74LS33 39	74LS109 55
74LS38 39	74LS112 55
74LS40 28	74LS113 50
74LS42 98	74LS114 50
74LS44 98	74LS115 50
74LS47 63	74LS116 50
74LS48 120	74LS117 50
74LS49 120	74LS118 50
74LS51 24	74LS119 50
74LS52 28	74LS120 70
74LS53 30	74LS121 70
74LS54 28	74LS122 70
74LS55 30	74LS123 70
74LS56 30	74LS124 180
74LS57 40	74LS125 60
74LS58 40	74LS126 80
74LS59 40	74LS127 80
74LS60 40	74LS128 80
74LS61 40	74LS129 80
74LS62 40	74LS130 80
74LS63 150	74LS131 80
74LS64 150	74LS132 80
74LS65 150	74LS133 80
74LS66 150	74LS134 80
74LS67 150	74LS135 80
74LS68 150	74LS136 80
74LS69 150	74LS137 80
74LS70 150	74LS138 80
74LS71 150	74LS139 80
74LS72 150	74LS140 80
74LS73 48	74LS141 80
74LS74 41	74LS142 80
74LS75 48	74LS143 80
74LS76 40	74LS144 80
74LS77 40	74LS145 80
74LS78 40	74LS146 80
74LS79 40	74LS147 80
74LS80 40	74LS148 80
74LS81 40	74LS149 80
74LS82 40	74LS150 80
74LS83 115	74LS151 80
74LS84 115	74LS152 80
74LS85 115	74LS153 80
74LS86 43	74LS154 80
74LS87 43	74LS155 80
74LS88 43	74LS156 80
74LS89 38	74LS157 80
74LS90 38	74LS158 80
74LS91 104	74LS159 80
74LS92 89	74LS160 128
74LS93 89	74LS161 98
74LS94 89	74LS162 138
74LS95 116	74LS163 102
74LS96 116	74LS164 114
74LS97 116	74LS165 75
74LS98 116	74LS166 226
74LS99 116	74LS167 190
74LS100 116	74LS168 185
74LS101 116	74LS169 150
74LS102 44	74LS170 288
74LS103 44	74LS171 288
74LS104 44	74LS172 288
74LS105 44	74LS173 105
74LS106 44	74LS174 106
74LS107 44	74LS175 110
74LS108 44	74LS176 110
74LS109 55	74LS177 110
74LS110 55	74LS178 110
74LS111 55	74LS179 110
74LS112 55	74LS180 110
74LS113 50	74LS181 398
74LS114 50	74LS182 398
74LS115 50	74LS183 298
74LS116 50	74LS184 298
74LS117 50	74LS185 300
74LS118 50	74LS186 300
74LS119 50	74LS187 300
74LS120 70	74LS188 300
74LS121 70	74LS189 300
74LS122 70	74LS190 140
74LS123 70	74LS191 140
74LS124 180	74LS192 140
74LS125 60	74LS193 130
74LS126 80	74LS194 166
74LS127 80	74LS195 136
74LS128 80	74LS196 100
74LS129 80	74LS197 140
74LS130 80	74LS198 140
74LS131 80	74LS199 140
74LS132 80	74LS200 348
74LS133 80	74LS201 348
74LS134 80	74LS202 348
74LS135 80	74LS203 175
74LS136 80	74LS204 236
74LS137 80	74LS205 236
74LS138 80	74LS206 236
74LS139 80	74LS207 236
74LS140 80	74LS208 236
74LS141 80	74LS209 236
74LS142 80	74LS210 236
74LS143 80	74LS211 236
74LS144 80	74LS212 236
74LS145 80	74LS213 236
74LS146 80	74LS214 236
74LS147 80	74LS215 236
74LS148 80	74LS216 236
74LS149 80	74LS217 236
74LS150 80	74LS218 236
74LS151 80	74LS219 236
74LS152 80	74LS220 236
74LS153 80	74LS221 96
74LS154 80	74LS222 96
74LS155 80	74LS223 96
74LS156 80	74LS224 155
74LS157 80	74LS225 155
74LS158 80	74LS226 155
74LS159 80	74LS227 155
74LS160 128	74LS228 155
74LS161 98	74LS229 155
74LS162 138	74LS230 155
74LS163 102	74LS231 155
74LS164 114	74LS232 155
74LS165 75	74LS233 155
74LS166 226	74LS234 155
74LS167 190	74LS235 155
74LS168 185	74LS236 155
74LS169 150	74LS237 155
74LS170 288	74LS238 155
74LS171 288	74LS239 155
74LS172 288	74LS240 155
74LS173 105	74LS241 155
74LS174 106	74LS242 155
74LS175 110	74LS243 155
74LS176 110	74LS244 155
74LS177 110	74LS245 155
74LS178 110	74LS246 155
74LS179 110	74LS247 155
74LS180 110	74LS248 155
74LS181 398	74LS249 155
74LS182 398	74LS250 155
74LS183 298	74LS251 155
74LS184 298	74LS252 155
74LS185 300	74LS253 142
74LS186 300	74LS254 142
74LS187 300	74LS255 142
74LS188 300	74LS256 142
74LS189 300	74LS257 142
74LS190 140	74LS258 142
74LS191 140	74LS259 142
74LS192 140	74LS260 142
74LS193 130	74LS261 142
74LS194 166	74LS262 142
74LS195 136	74LS263 142
74LS196 100	74LS264 142
74LS197 140	74LS265 142
74LS198 140	74LS266

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Reg No. 242 1255 03

Please send all correspondence and Mail-Orders to Head Office

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

IB3GT	0-65	6AX4GTB	1-00	6CY5	1-00	12AT6	0-60	ECF200	0-90	EM84	0-60	PCL81	0-65	PY82	0-55	UCC84	0-75
IR5	0-50	6AX5GT	1-30	6CY7	1-00	12AT7	0-50	ECF201	0-90	EM87	1-00	PCL82	0-60	PY83	0-70	UCC85	0-55
IX2B	1-20	6BA6	0-45	6D06B	1-45	12AU6	0-65	ECF801	0-95	EY81	0-50	PCL84	0-75	PY88	0-75	UCF80	0-75
5AT8	0-80	6BE6	0-48	6DT6	0-80	12AU7	0-47	ECF802	0-95	EY87	0-50	PCL86	0-85	PY500A	1-30	UCH42	0-90
5T4	0-75	6BF5	0-85	6DT8	0-80	12AV6	0-80	ECH42	1-10	EY88	0-55	PCL805	0-75	TT21	7-80	UCH81	0-70
5U4G	0-60	6BF6	0-75	6DW4	0-90	12AV7	1-00	ECH81	0-55	EY500A	1-50	PCL86	0-75	TT22	7-80	UCL81	0-70
5U8	0-75	6BG6G	0-30	6E55	1-00	12AX7	0-55	ECH200	0-80	EZ80	0-50	PL36	1-10	U25	1-00	UCL82	0-75
5V4G	0-60	6BH6	0-85	6EV5	1-50	12AY7	0-85	ECL80	0-60	EZ81	0-50	PL81	0-80	U26	1-00	UCL83	0-80
5X4G	0-80	6BJ6	1-20	6EW6	0-80	12BA6	0-80	ECL81	0-75	GY501	0-90	PL82	0-55	UABC80	0-58	UF41	1-00
5X8	0-90	6BJ7	0-85	6GH8A	0-80	12BF6	0-67	ECL82	0-60	GZ30	0-65	PL83	0-50	UAF41	0-80	UF80	1-00
5Y3GT	0-65	6BK4B	1-40	6K5	0-70	12BH7A	0-75	ECL83	1-15	GZ32	0-65	PL84	0-75	UAF41	0-70	UF85	0-50
5Z4GT	0-65	6BN4A	0-90	6K6	0-90	12BL6	0-70	ECL84	0-70	GZ33	3-80	PL504	1-05	UBC81	0-80	UF84	0-85
6AB7	0-60	6BN6	0-80	6J4	1-20	12B06	0-90	ECL85	0-65	OA2	0-55	PL508	1-30	UBF80	0-60	UM80	0-60
6AC7	0-80	6B07A	0-65	6J5GT	0-80	12BY7A	0-80	ECL86	0-85	OA3	0-75	PL802	2-80	UBF89	0-60	UM81	0-75
6AD8	0-60	6BR8A	1-20	6J6	0-55	12CU6	0-90	EF80	0-40	OB2	0-60	PY81	0-70	UBL21	0-85	UM84	0-45
6AF4A	0-80	6BS7	2-30	6J7	0-80	19A05	0-75	EF85	0-48	OB3	0-75						
6AG5	0-65	6BU8	0-85	6K5GT	0-75	19BG6G	0-50	EF86	0-60	OC2	1-40						
6AG7	0-85	6BW7	1-00	6K6GT	0-85	35A3	0-70	EF92	0-75	OC3	0-75						
6AH6	0-85	6BZ6	0-65	6L6GT	0-85	35B5	0-65	EF97	0-70	OD3	0-75						
6AJ5	0-85	6BZ7	0-70	6N7GT	0-85	35C5	0-70	EF98	0-90	PABC80	0-45						
6AK5	0-65	6C4	0-55	6O7	0-90	50C5	1-00	EF183	0-70	PC86	0-85						
6AK6	0-75	6CSGT	0-60	6SA7	0-80	50EH5	0-85	EF184	0-70	PC88	0-85						
6AK7	0-85	6C6	0-50	6SG7	0-80	DAF96	0-80	EFL200	1-20	PC96	0-50						
6AL5	0-40	6C8G	0-60	6SK7	0-80	OF96	0-60	EH90	0-60	PC97	0-95						
6AM6	0-70	6C8B	0-55	6SL7GT	0-70	DK92	1-00	EL33	2-50	PC900	1-00						
6AM8	0-70	6CG7	0-70	6SN7GT	0-70	DL96	0-80	EL36	0-95	PCC84	0-50						
6AN5	2-50	6CG8A	0-75	6S07	0-80	ECC84	0-60	EL81	0-65	PCC85	0-60						
6AN6	0-85	6CM7	0-80	6SR7	0-80	ECC85	0-48	EL82	0-60	PCC88	0-65						
6AO5	0-85	6CN7	1-20	6V6GT	0-65	ECC86	1-25	EL83	0-60	PCC89	0-75						
6AS6	1-00	6CO8	0-75	6X4	0-60	ECC88	0-75	EL84	0-45	PCC189	1-00						
6AS7G	1-20	6CS7	0-85	6X5GT	0-60	ECC89	0-80	EL86	0-75	PCF80	0-65						
6AT6	0-75	6CU5	1-00	6X8	0-80	ECC189	0-80	EL95	0-70	PCF82	0-45						
6AU6	0-50	6CU6	1-00	12A6	0-60	ECF80	0-60	EL504	0-80	PCF84	0-85						
6AV6	0-75	6CW4	3-75	12AL5	0-65	ECF82	0-55	EM80	0-65	PCF86	0-75						
6AW8A	0-75	6CX8	1-00	12A05	0-60	ECF86	0-80	EM81	0-60	PCF806	1-00						

OSCILLOSCOPE TUBES

current production. Made in USSR

One inch Tube Type 3LO 11. This tube is a good replacement for 1CP31. Tube characteristics are identical with those of 1CP31. As the connections are different the tube is supplied complete with base, connection diagram and technical data **£12.00**.

Three-inch tube Type 3BP1. This well known tube used in "PURBECK" Oscilloscope can be supplied for **£7.50**. 14-pin base for the above **£0.80**.

VAT is not included. Please add 12½% on all items except those marked with asterisk, on which VAT is 8%. Postage and packing charges are **£0.10** per £ subject to a minimum of **£0.30**. Minimum order charge for Approved Credit customers **£20.00**. Minimum Transaction Charge for mail orders **£1.00**.

OUR NEW 1978/1979 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

TRANSISTORISED INVERTER UNITS

CASED UNITS

Designed to operate reliably in continuous or intermittent use, low standing current drain, proportional current consumption with regard to the connected load, assembled in vinyl covered instrument cases with grade one silicon power transistors—Guaranteed 2 years—DC input fused.

12 volt DC inputs—200/240V AC outputs regulated, at 50Hz square wave or optional smoothed and filtered wave form circuitry for sensitive equipment:

25 watts 4" x 4" x 3"	£8.40
40 watts 6" x 4" x 3½"	£11.30
140 watts 6" x 4" x 3½"	£21.60
200 watts 8" x 7" x 3½"	£27.70
300 watts 10" x 7" x 4"	£37.00
400 watts 12" x 5" x 6"	£48.40
500 watts 14" x 6" x 6"	£59.90
700 watts 14" x 10½" x 9"	£84.00

Case sizes subject to variations

All inverters are ready assembled, DC input via heavy duty cables with attached battery clips, AC mains output via a 13 amp socket.

PANEL ASSEMBLIES

These inverter panels are assembled on aluminium sheets, all are uncased. Suitable for general purpose applications, plain DC leads in/and AC output leads

Square output waveforms 50Hz regulation is optional at extra cost of **£1.10**.

12v DC in/200/240v AC out at 20 watts 4" x 3" x 3" **£4.40**

12v DC in/200/240v AC out at 40 watts 4" x 3" x 3" **£6.60**

12v DC in/240v AC out 50Hz at 100 watts 6" x 9" x 4" **£16.80**

OPTIONAL EXTRAS

Smoothed and filtered waveform circuitry **£2.50**; Additional 13 amp mains output socket fitted **£1.20**; Panel fuse/holder 20mm for mains protection fitted **£1.00**.

TERMS OF BUSINESS

Cash/P.O./Cheque with order. Postage/Carriage inclusive. Delivery 10/14 days, urgent 48hr service available 25% extra.

ELECTROVANCE

Callers by appointment. Telephone enquiries welcome
P.O. Box 191, LONDON, S.W.6. 2LS
Tel: 01-736 0685

Mail Order Protection Scheme


The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

Model TCSU1 Soldering Station

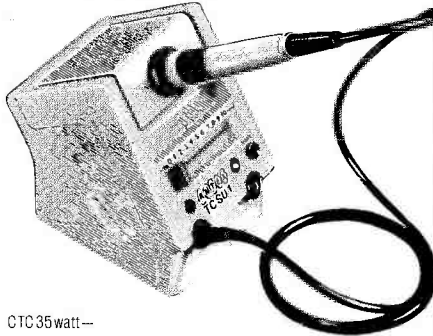

CTC 35 watt -



The TCSU1 soldering station with either the XTC 50 watt - 24/26 volt soldering iron or the CTC 35 watt - soldering iron for pin point precision and exceptionally fast recovery time. We have packed 250W as much power into irons which are already well known for good recovery time. The temperature control stops the iron from overheating the "fail-safe" electronic circuit provides protection even if the thermocouple fails. TCSU1 soldering station £38.10 XTC and CTC irons £14.85 inclusive of VAT and P & P.

Model CX - 17 watts



A miniature iron with the element enclosed first in a ceramic shaft, then in a stainless steel. Virtually leak free. Only 7 1/2" long. Fitted with a 3/32" bit £4.37 inclusive of VAT and P & P. Range of 5 other bits available from 1/8" down to 3/64"

Model X25 - 25 watts



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at £4.37 inclusive of VAT and P & P. Range of 4 other bits available.

Model SK3 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at £6.21 inclusive of VAT and P & P. It makes an excellent present for the radio amateur, modelmaker or hobbyist.


Model SK4 Kit



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at £6.21 inclusive of VAT and P & P.

Model SK1 Kit

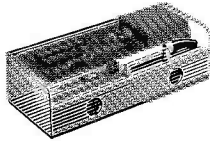This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet, How to solder. Priced at £6.48 inclusive of VAT and P & P.



Model MLX Kit

The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price £4.83 inclusive of VAT and P & P.



Now heat to any level

between 145° - 400°c
(with accuracy of 2%)



With the **Antex TCSU1 Soldering Station**

All Antex soldering irons are made on the principle of putting the heating element inside a shaft, then the desired bit is eased over the shaft giving maximum heat transference, this is why so often a small Antex iron can do the job of a larger conventional iron. The precision made slide on bits are slit to make them easily interchangeable.

The ANTEX multi purpose range of soldering equipment is fast becoming a must for every home. Built with precision for long life, each iron is fully tested and guaranteed.

ANTEX soldering irons are made in England to strict local and international standards of safety.

Stocked by many wholesalers and retailers or direct from us if you are desperate.



Mayflower House, Armada Way,
Plymouth, Devon.
Tel: 0752 67377/8
Telex: 45296

Please send me the Antex colour brochure I enclose cheque/P.O. (Giro No. 236 1000)
Please send the following
Name _____ Address _____



A quality range of British made electrical accessories plus a How to... book. Do your own home electrical work with complete confidence. See cat. pages 129 to 134.



This superb organ - build the first working section for just over £100. Full specification in our catalogue.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Mobile amateur radio, TV and FM arials plus lots of accessories are described in our catalogue.



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554155.



A superb technical bookshop in your home! All you needs out catalogue. Post the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £13.88 incl. VAT & p & p MA1023 module only £2.42 incl. VAT.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.

Post this coupon now for your copy of our 1979-80 catalogue price 75p. Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____
 ADDRESS _____

pull out

★ **special feature**

8-PAGE SUPPLEMENT

hints & tips for constructors

Practical Wireless

March 1979

contents

Finishing it off	Two
The mystic art of soldering	Four
Identifying components	Six
Component buying	Seven
Handling c.m.o.s.	Eight

Finishing it off

Give your project a really professional appearance

A growing number of home constructors seem to be aiming to finish their projects in a more professional manner. There is a growing interest in using better looking and better finished cases and cabinets and the days of the old tobacco tin seem, fortunately, to have passed.

The choice of cases available to the home constructor has improved in recent months and several companies have made some of their professional cases available on the amateur market.

In most projects presented in *Practical Wireless* the decision as to the type and style of case to be used has already been taken. A lot of thought goes into the choice of case for each project, bearing in mind such parameters as price, the use to which the project will be put, availability and styling.

Simple Boxes

Some simple projects can be adequately housed in a simple plastic box if electrical screening is not required, or in the traditional diecast aluminium box if it is needed. Plastic boxes have been developed by several makers into quite sophisticated units offering many advantages for the amateur user. They are relatively inexpensive and can be easily drilled for controls using only simple hand tools, although some degree of care is needed if the smooth polished surfaces are not to be marked. A wide range of sizes and styles are available and several types have mounting facilities for printed circuit boards moulded into the box, simplifying construction.

The diecast box in its simplest form has been around for several decades and there are probably more pieces of electronic equipment built into one of these


than into any other type, with the possible exception of the infamous tobacco tin. It has several disadvantages for the amateur, being quite difficult to work on with simple hand tools and having a rather indifferent appearance in the 'as bought' state. Versions are available with a respectable gloss painted finish, but these are very expensive and unless the electrical screening properties of the diecast box are really needed then the plastic versions are better, and cheaper.

The plain simple aluminium box with removable lid offers a stark and cheap housing without any pretensions as to style or elegance.

Test Gear

When it comes to projects such as test equipment, domestic audio or amateur radio projects, some respectable form of housing becomes essential.

Test equipment should be built to be used, and must offer reliability and confidence and it cannot really give of its best housed in a piece of bent aluminium. The case design chosen must be mechanically robust, easily worked and allow the controls to be ergonomically positioned. If the instrument is intended to be used in the workshop then allowances should be made for maximum utilisation of bench or shelf space. Take a look at what the commercial instrument makers use and don't be ashamed to take the best ideas from all of them. Don't be tempted to use a case that is so small that the controls have to be cramped together making the instrument awkward to use. You should be proud of the finished instrument and not be ashamed to leave it permanently on the workshop bench where it will get maximum use.

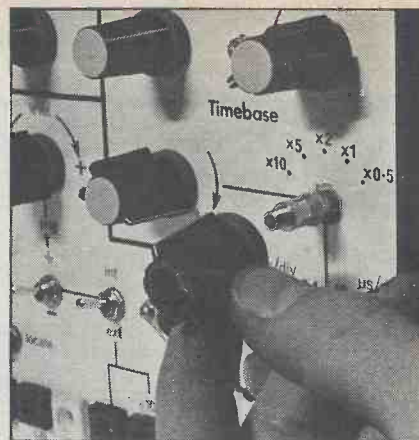

Audio equipment tends to be rather fashion conscious and so the cases and cabinets used for amplifiers and tuners change styles rapidly. Because this type of project is on show to anyone who enters your home it is very important to ensure that the workmanship put into the cabinet and front panel of any audio project is of the very best. Probably the easiest way to achieve this is to build from a complete kit where the cabinet is provided. However, if you are designing your own circuits or insist on making the entire unit yourself then there are a few recent additions to several makers' case ranges which would lend themselves to audio equipment.

For the amateur radio enthusiast the need is for a functional but still attractive case at a respectable price and it also probably needs to be all metal as well.

Metalwork

Although very respectable work can be turned out on the kitchen table using nothing more than a pair of scissors, an old file and a simple hand drill if you have the patience, it is very much easier with a few basic tools.

The home constructor needs to be able to drill holes in metal or plastic panels, file rectangular holes for meters or plugs, cut pieces of metal to size and shape and bend them into simple shapes such as brackets. To perform these operations a few basic tools are essential and you must learn how to use them properly.


Some means of holding the work is essential if painted or polished surfaces are not to be scratched.

Ensure that your cutting tools and drills are all kept sharp and in tip-top condition. Blunt and rusty tools do not

Drilling sizes


Thread	Clearance	Tapping
OBA	6.10mm	5.10mm
2BA	4.80mm	4.00mm
4BA	3.70mm	3.00mm
5BA	3.30mm	2.65mm
6BA	2.85mm	2.30mm
8BA	2.25mm	1.80mm
10BA	1.80mm	1.40mm
12BA	1.40mm	1.05mm

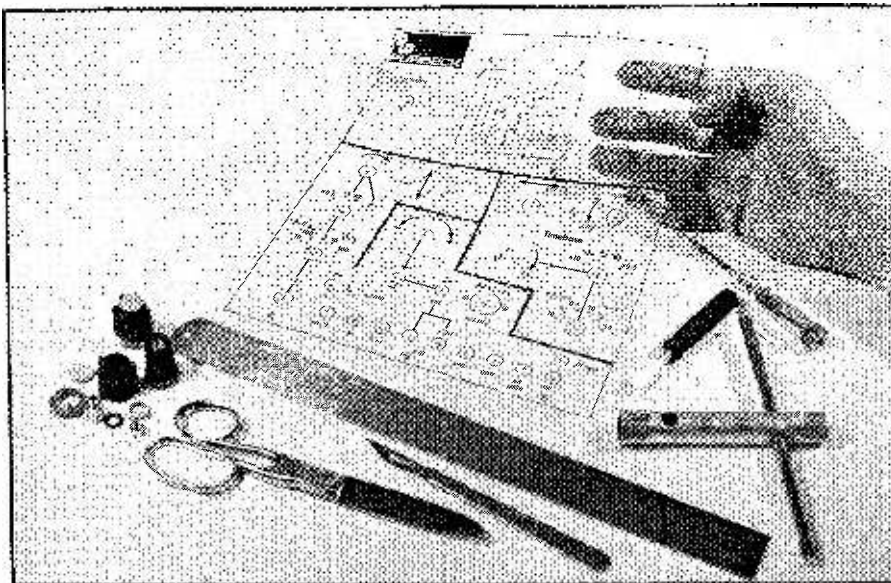A professional look can be achieved with the *PW* Front Panel Overlay System. This picture shows the overlay for the *PW* Purbeck oscilloscope. The overlay can be used over a plain white card panel or over a coloured one if preferred. A thin Perspex sheet can be fitted over the film to protect it and hold it firmly in place



help to make a good job. Mark out the positions of the holes and cut-outs accurately, paying particular attention to ensuring that groups of holes are correctly positioned relative to each other. Centre-pop each hole before drilling a small diameter pilot hole first then following up with the correct size drill. Rectangular cut-outs are made by drilling holes at each corner and using an Abrafile fitted in the hacksaw frame cut along the four sides. Use a suitable file to finish the cut-out to size.

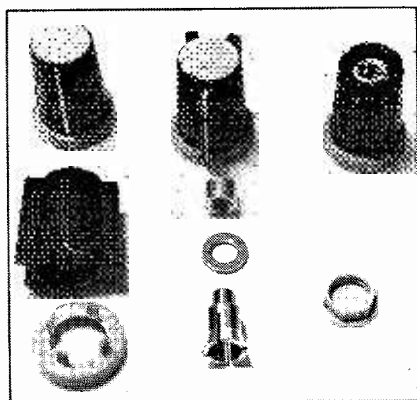Wherever possible try to use components that have some sort of bezel to cover up the holes. This gives you much more leeway with your metalwork.



Collet type knobs provide a firm fastening together with ease of positioning on the shaft. These are Sifam knobs and the various component parts can be seen

Front Panels

Lettering on the front panel can make or mar a project. Although press down letters and numerals can be used with good effect they are not as easy to use properly as is widely imagined and unless they are carefully fixed with special varnishes they tend to rub off quickly in use.

A system to enable constructors to produce professional looking hard wearing front panels for many *PW* projects has been evolved.

This uses a photographically produced transparent film of the front panel which can be carefully cut out and placed over the main panel. A thin sheet of Perspex can be placed over the film to hold it flat, the "sandwich" being held in place by the controls.

A further stage in the production of front panels is to use the film overlay as a photographic master to make a thin metal panel which is then stuck onto the main front panel. This method produces superb panels but does require the use of ultra-violet lamps, specially sensitised metal sheet and the appropriate chemicals.

Knobs

To complement the front panel design you should choose suitable knobs, bearing in mind the use to which the unit is to be put. For test equipment where ease of use is vital it is difficult to better a collet type of knob. These fit tightly onto the control shaft by a simple collet action and do not

require a flat on the shaft for a grub screw.

For audio units more fashionable knobs can be chosen but remember that good knobs cost more than poor ones. ●

Wire sizes

s.w.g.	dia. mm	s.w.g.	dia. mm
10	3.251	30	0.315
12	2.642	32	0.274
14	2.032	34	0.234
16	1.626	36	0.193
18	1.219	38	0.152
20	0.914	40	0.122
22	0.711	42	0.102
24	0.559	44	0.081
26	0.457	46	0.061
28	0.376	48	0.041

Basic tool kit

Hand drill with $\frac{1}{8}$ inch chuck
 Drills 1mm, $\frac{1}{16}$, $\frac{1}{8}$, $\frac{1}{4}$, $\frac{3}{8}$ inch diameter, countersink bit
 Junior hacksaw
 Abrafiles (to fit hacksaw)
 Centrepunch
 Small ballpein hammer
 Small files including round, half-round and three square
 Steel rule, 12 inches long
 Small engineer's square
 Scalpel and blades (also use as scriber for marking out)
 Small vice
 Screwdrivers
 Pliers, small and large
 Sidecutters
 BA spanners
 Soldering irons 15W, 30W


The mystic art of soldering

Assemble your projects correctly

The absolute success of any electronic or wireless project lies with the workmanship put into the construction. This applies especially to the quality of the soldering. One dry joint and the entire project is likely to fail to work, causing despair to the beginner.

It is simply not sufficient to assume that a project can be thrown together anyhow, the solder blobbed onto the joints, the power switched on and it will work. With modern circuits and exotic components this is just not the case. The would be wireless constructor should aim to master the various constructional techniques used.

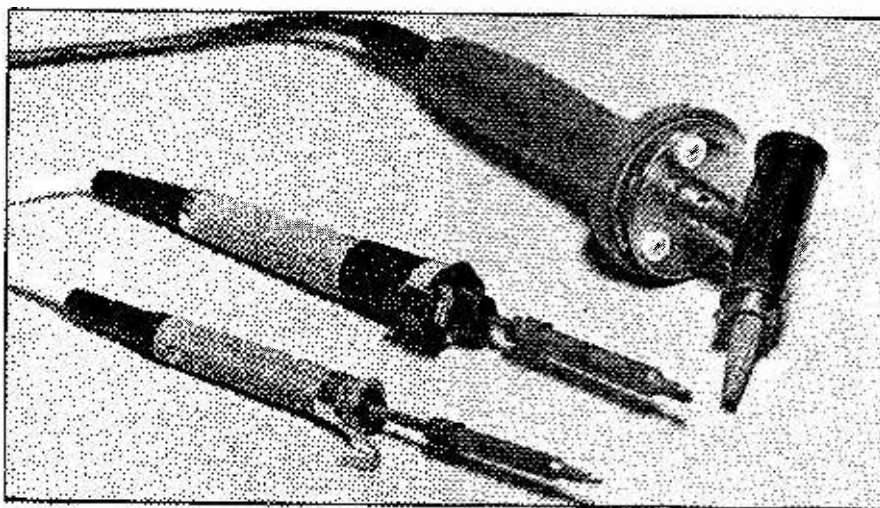The basic art which must be perfected before starting any constructional project is the technique of soldering.



A soldered joint is used for two purposes in electronics. The first is to provide a mechanical fastening for the various electronic components.





The second and main purpose of the solder is to provide a low resistance electrical path between the leads of the components. It can only do this if the solder "wets" each lead to be connected.

The art of good soldering is not difficult to master and requires the joint to be clean and free from greases, the iron to be really hot and perfectly clean and the correct grade of solder to be used.

Choice of Iron

Let us discuss the choice of iron first as this has a direct bearing on how easily you can make a given joint. The only purpose of the iron is to heat the metals to be soldered to the correct temperature so that the solder flows properly. It is not intended to be used as a means of carrying the solder to the joint or as a tool for bending lead ends over. The iron should ideally be matched to the joint being made so that the temperature is neither too hot nor too cold. If the temperature is too hot it is probable that the more delicate components might be damaged while if it is too cold the solder will not melt properly and the joint will be dry.

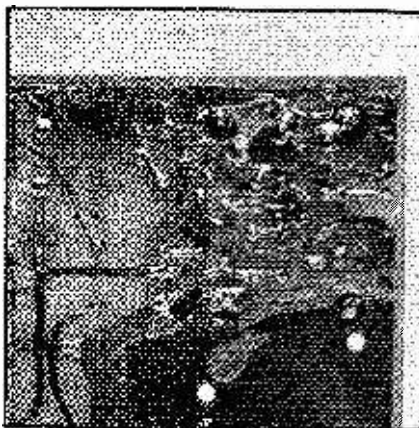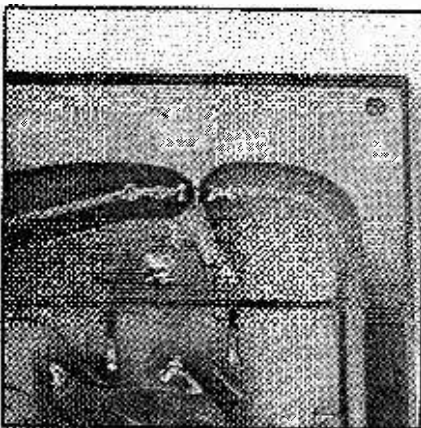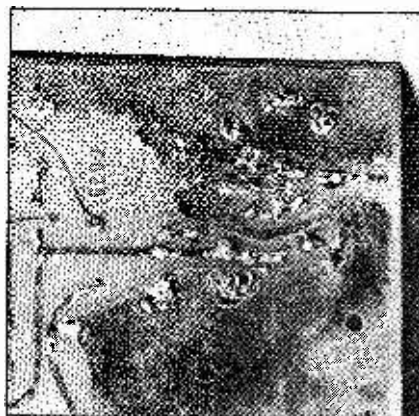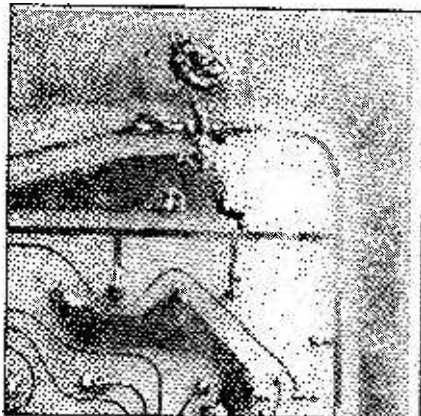Soldering irons are available in a wide variety of sizes and shapes. The first figure to be quoted when talking about irons is the wattage of the element and these vary from about 10W up to about 240W—ideal for soldering the seams on your car radiator. For our purposes a 15/17W miniature iron with an iron plated copper bit of about 2.3mm diameter is ideal for modern p.c.b. work



Top left is a badly made soldered joint on a p.c.b. probably made with an iron that was cold and dirty. Too much solder has been used and has bridged across the three pads. Below it is the same area of the board after the excess solder had been removed and the joint made with a clean hot iron. Top right shows a solder bridge across two adjacent pads. Below are the same joints properly made. The heading picture shows a Stiron 75W iron and Antex 30W and 17W miniature irons

and will cope with most joints to be found on *PW* project boards.

However where large diameter earth wires, metal screens and components with heavy gauge wires are met with then such a small iron will not be capable of supplying enough heat to bring the metals up to soldering temperature rapidly enough and a poor joint will be the result. For this type of work and also for older projects such as those using valves a 25/30W iron with a bit of around 3.2mm diameter is needed.

If you want to go in for some really heavy brass metal chassis bashing then you will need at least a 60W iron with a large bit and you might even find that a small propane gas blowtorch is better.

Preparation

When preparing the components for soldering ensure that the leads are clean and, if necessary, tin them by applying the hot iron to the leads together with a resin cored solder so that the lead is completely covered by a thin layer of solder.

The leads should then be carefully bent so that the component fits into place without any strain on its leads. Place the hot iron onto the joint and immediately apply resin cored solder to the joint. The solder should flow easily and quickly to completely cover the joint, when the solder and iron can be removed and the joint allowed to cool. It is very important that the components are not allowed to move during the cooling down period as this will affect the quality of the joint.


When it has cooled down and the solder solidified the joint can be inspected. The solder should completely surround the joint and be bright and shiny. If the joint is dull or crystalline in appearance the joint is "dry" and must be remade. Likewise any small blowholes or areas where the solder has not "wetted" the leads means that the joint is suspect.

One very common fault is to use far too much solder on each joint. Only enough solder should be applied to the joint to completely cover it. An excess of solder is not only untidy, and could cover a bad joint but it is also expensive.

If you find that you have to remove a component from a p.c.b. at any time this can be easily done by using a de-soldering



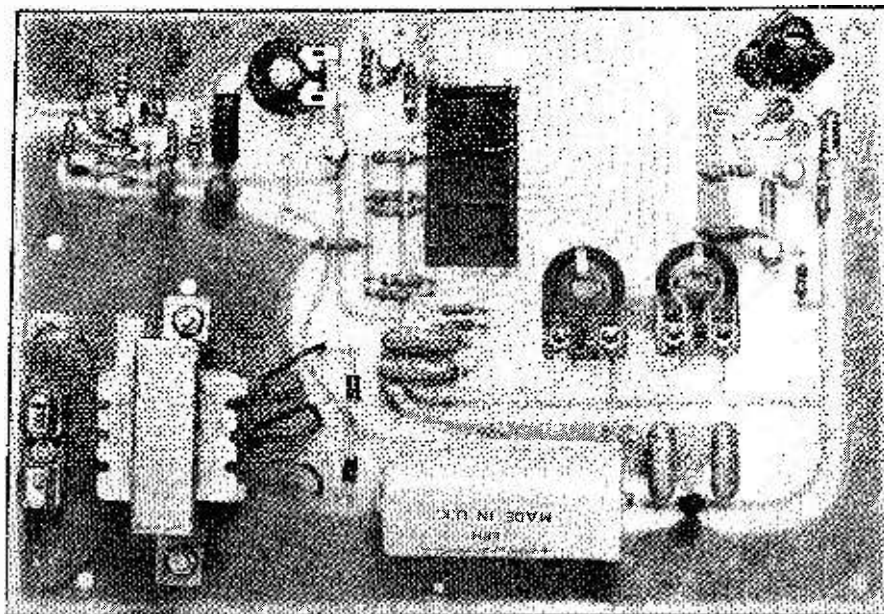These two pictures show a TV game p.c.b. as built by a novice (above) and after rebuilding correctly (below). Note how the components are poorly formed and placed in the upper picture with the transformer hanging on one small screw. All components should be neatly formed and positioned with great care and precision to obtain maximum reliability



braid. This braid is placed on the joint and a clean iron applied. The solder melts and is literally sucked into the braid by capillary action. A clean piece is used for each joint, of course.

The soldering iron bit must be kept clean and this is best achieved by using a damp sponge and wiping the hot bit with it after each joint is made. Several stands are available to hold the iron when it is not in use and these usually incorporate the sponge in their bases. Remember to

keep the sponge damp though.

Never use any other solder than a resin cored variety which has been specially formulated for electrical and electronic work. Fluxes such as Baker's Fluid or other highly active varieties must never be allowed to get anywhere near an electronic component, the results will definitely prove disastrous for the component as well as shortening the life of your soldering iron bit. Leave these corrosive fluxes to the plumbers. ●

Identifying components

The resistor and capacitor colour code explained

Although there are some minor differences in specific capacitor ratings, both resistors and capacitors follow the same colour code. In the case of resistors, where the colour code is in use, it refers to a nominal value in ohms, the unit of resistance. There are of course other types of resistor which do not utilise a colour code, such as wirewound types (high current or high stability) and some which simply have the resistance value written as a figure on the resistor body itself, but the vast majority of carbon, metal oxide, and thick film types use the colour code.

The way in which the code works is very simple, the colours being read off from one end of the resistor to the other, beginning at the end where the colours are concentrated. The first ring of colour indicates the first digit, the second ring the second digit, and the third indicates the multiplier or number of zeros in use. The fourth colour indicates the tolerance over the stated range, brown indicating 1%, red 2%, gold 5%, and silver 10%.

A typical resistor might read yellow, purple (or violet if you prefer), red, and gold. This indicates 4700ohms, variously written as 4.7k, 4.7kΩ, or 4k7, and a tolerance of 5% over that range. It is important to appreciate that the third colour (the multiplier) actually denotes the number of zeros, thus a 47Ω resistor would appear as yellow, purple, black, with a tolerance band following, indicating that there are *no* zeros in the multiplier.

In general, the colour code is restricted to carbon or metal oxide types, and these resistors will of course be suitable for all types of circuit application. On the other hand, wirewound types, which normally have their value stamped or printed on the body of the resistor, will possess inductive properties, which may render them unsuitable for r.f. circuits.

The stability and tolerance of a particular resistor is to a great extent dictated by the materials of which it is made, as is the inherent electrical noise

which it produces. High stability items are typically constructed from carbon film (5% tolerance) or metal oxide (2% tolerance) cermet ("thick film") also 2% tolerance, but precision items are of course wirewound, giving a rated tolerance of 0.1%.

In the case of power dissipation, wirewound forms are inevitably the favoured construction, giving a dissipation in specific items up to about 50W commercially, but once again, fairly high levels of dissipation can be managed with moulded carbon compound types, up to about 2W.

Where low noise levels are concerned, metal oxide and thick film types are used.

Capacitor Markings

Although the colour code is the same as that for resistors, it is generally

restricted to ceramic disc, tantalum bead, and some moulded or dipped types. In the case of capacitors, there is some extra information necessary, notably the working voltage. The general code is read in the same way as with resistors, beginning at one end and moving towards the wire ends, the last line of colour indicating the working voltage. In the most common form, the polyester dipped type, red = 250V and yellow 400V. In these types a white tolerance band indicates 10% and black 20%.


Caution must be exercised where colour bands are similar to the colour of the capacitor body, as for example, a 2200pF (2.2nF or 2n2) polyester dipped type might well appear as a totally red item, made up from red = 2 (first digit), red = 2 (second digit or tens), and red = 2 (multiplier or number of zeros).

Tantalums are usually low voltage types and the code, again, is read from the free end, away from the wire ends. The first colour is the first digit, the second the tens in the figure, the next the multiplier, and the final colour the working voltage. These voltage bands follow a colour code, black indicating 10V, yellow 6.3V, green 16V, blue 20V, grey 25V, white 30V and salmon pink 35V.

Applications

The non-electrolytic categories, such as silvered mica, ceramic, paper, polyester and polycarbonate are highly suitable in all signal processing applications, both audio and radio, with the principal restriction being each type's working voltage and temperature capabilities. Ceramics are normally used in situations where their good temperature characteristics are an advantage, such as tuned circuits. Polyester, paper and polycarbonates are universally useful in high voltage situations where good insulation resistance is required such as pulse circuitry in television, and general signal and power stages in radio and audio circuits. In the main, coupling in transistor a.f. stages etc. utilises specific polyester items, due to their smaller physical size and good tolerance.

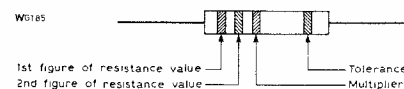Electrolytics are used where high capacitance values are needed, and in the de-coupling of power supplies, where hum and ripple may be a problem. ●



COLOUR	1st & 2nd BAND	MULTIPLYING FACTOR	TOLERANCE
BLACK	0	1	—
BROWN	1	10	±1%
RED	2	10 ²	±2%
ORANGE	3	10 ³	—
YELLOW	4	10 ⁴	—
GREEN	5	10 ⁵	—
BLUE	6	10 ⁶	—
MAUVE	7	10 ⁷	—
GREY	8	10 ⁸	—
WHITE	9	10 ⁹	—
SILVER	—	10 ⁻¹	±5%
GOLD	—	10 ⁻²	±10%

Table of Multipliers

(referring to all electrical functions—current, voltage, resistance, inductance, frequency, power, and time)

p = pico = $\times 10^{-12}$

n = nano = $\times 10^{-9}$

μ = micro = $\times 10^{-6}$

m = milli = $\times 10^{-3}$

k = kilo = $\times 10^3$

M = mega = $\times 10^6$

G = giga = $\times 10^9$

Component buying

How and where to purchase those elusive parts

"Where can I buy the components for the *PW* 'Whathaveyou' project?" is one of the commonest queries received. This article will try to explain the pitfalls of purchasing electronic components, and show how to overcome them.

Unless you can buy a complete kit for a project it is quite probable that you will have to undertake some detective work to uncover the relevant suppliers.

The first thing that any serious home constructor needs is a library of catalogues from various suppliers of components. A run through the adverts in *PW* will indicate who produces a catalogue and you really cannot have too many of them. Using your library you can select the appropriate supplier for most components. You can compare prices for various components to try to obtain the best deal if this sort of exercise takes your fancy.

Exotic projects

Consulting your favourite supplier's catalogue is all right for the common or garden components such as resistors, capacitors and semiconductors, but what about the special items often specified for the more exotic projects?

Often these are available only from one source and where this is so the source is given in the components list or in the text of the article describing the project.

One name that keeps appearing in component lists is that of RS Components. This company is a component distributor who produce a comprehensive catalogue widely used in industry. All the components sold by RS are "own brand" and they only sell to *bona fide* trade customers. Because of their rapid service and well-produced technical catalogue,

their components are used widely by authors when preparing projects, and the staff of *PW* also use them for similar reasons.

This leads to complications when a components list calls for an RS Components part number as many readers will find it difficult to obtain them. One way out is to befriend your local radio and TV repair shop who will certainly have an account with RS. It must be remembered that the prices given in their catalogue are not retail prices, and do not include VAT either, so be prepared to have to pay around 50% above catalogue price.

Up until recently RS Components' sister company Doram supplied to the amateur market but this service has been withdrawn. However several of the regular advertisers in *PW* will obtain any RS Components part on request.

By the way, try and persuade your friendly repairman to let you have an old issue of RS Components' catalogue, it is a mine of valuable information on components, giving such information as sizes, connections and specifications.

Cases and cabinets

When it comes to the cabinet or case to fit the project, these are usually available from several advertisers, most of whom carry a range from two or three manufacturers. In most projects the actual case style is a matter of personal choice and the one used by the author need not be copied. However, some projects are built using specially designed cases or utilise some particular feature of a case, and then it is important that only that case is used.

If you are the type who enjoys making your own chassis and cases then you will

need to find a supplier of raw materials. This is not always easy and it pays in this case to have a copy of *Whiston's Catalogue* (K. R. Whiston Ltd., New Mills, Stockport SK12 4PT). This lists small quantity sizes of aluminium, brass, steel, etc., and is available for an s.a.e.

Printed circuit boards for *PW* projects should be obtainable from advertisers, but, individual readers can, if they have the equipment, make their own boards from the copper track patterns given full-size in the magazine. Another way is to take the track pattern to your local printed circuit board company and get them to make you a board. This is likely to be expensive as they will have to make you a photographic master from the drawing first (note that this must only be made for you and boards must not be made for resale by this method without obtaining permission and paying royalties to the copyright holder). You can find the address of p.c.b. makers in your local "Yellow Pages", which can also prove useful in locating component stockists, metal stockists, etc.

Semiconductors

When buying semiconductors for a project you will have to make up your own mind as to whether you risk using cheap unmarked types or spend out more money for guaranteed ones. Most suppliers will honour the maker's warranty and change faulty i.c.s or transistors so long as they have not been soldered into a circuit. With c.m.o.s. types, do not be tempted to take them out of their packaging to look at them. They are very prone to damage from static which builds up on all humans these days. Leave these i.c.s firmly in their conducting foam or silver foil wrappers until you are ready to insert them into their sockets. If you are supplied with c.m.o.s. not protectively wrapped in foil, conducting foam or a special housing, get in touch with the supplier immediately. If possible it is best to buy such components only from suppliers who are recognised or franchised by the manufacturer.

Finally, if you have exhausted all the above possibilities and feel that you simply must ask the magazine staff, please enclose a s.a.e. and don't expect miracles, and please, oh please, only after you really have tried yourself!

Handling c.m.o.s.


Avoid killing your i.c.s with static

Unlike t.t.l. (transistor-transistor logic), c.m.o.s. (which stands for "complementary metal oxide semiconductor") devices are very prone to damage if handled or fitted into circuits without due precautions having been taken.

It is true that one or two digital c.m.o.s. devices are fairly robust, and can usually only be destroyed by reversing polarity of the supplies or by feeding a high signal at low impedance into the inputs while the device is without a supply, but general c.m.o.s. "chips" for use in the audio, video, music and radio fields are highly susceptible to static charges and extremes of temperature.

A great deal has already been written on somewhat amusing lines concerning the wearing of nylon clothing while working on such devices, but the basic facts are quite simple and need no "scripting" in order to emphasise the requirements.

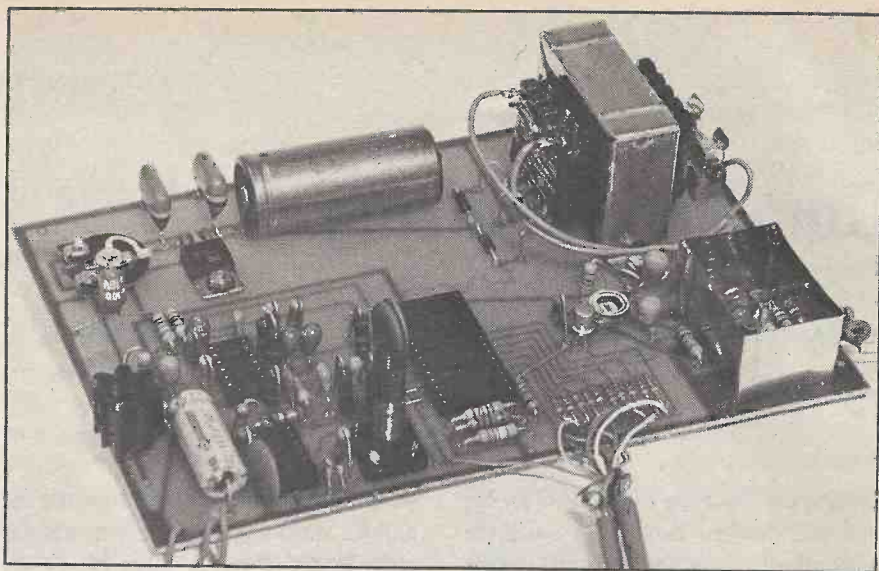- 1) Unused inputs should always be tied to ground or positive supply, depending upon requirements.
- 2) Polarity of supplies *must* be carefully checked before any connections are made.



As it should be, neat and tidy.

- 3) Low impedance sources, including charged electrolytic capacitors, must not be connected directly to the input terminals, especially in the case of logic "chips". It is essential to use a surge limiting resistor in such cases of at least 1000Ω .
- 4) Input terminals must not be allowed to "float" and must be, like unused inputs, tied to ground or positive via a high resistance.
- 5) Where devices are supplied in packages of conductive foam, conducting foil, or the specialised conducting tubes which are becoming typical of c.m.o.s. packaging, they should not be removed until the very last moment in order to avoid the effects of any local static charges.
- 6) It is as well to avoid wearing nylon shirts or similar synthetic

fibre clothing while working on these "chips", and the same point applies to plastic coverings for bench tops, which should be removed.

- 7) Where possible, the device should be inserted directly into the i.c. holder without any actual contact being made between operator and device.
- 8) In extreme cases, the body can be earthed via a loose chain on the wrist, this technique being used with operatives during manufacture. A metal-covered bench is also used.
- 9) The pins of the device should not be touched with the fingers.
- 10) The device must not be disconnected or otherwise removed from the associated circuitry while it is functioning.
- 11) When soldering to such devices, an earthed bit must be used.

Care taken in handling, or not handling, c.m.o.s. components will greatly increase the reliability of projects which use this type of integrated circuit. Properly used c.m.o.s. offers a lot of advantages for the hobbyist and attention to the advice given above will ensure your confidence in the finished project. ●

How not to build your project. This untidy "heap" shows many faults such as trying to fit an 8-pin d.i.l. package i.c. into a p.c.b. designed for a TO99 circular package by tacking short lengths of wire to each lead to extend it

