

RADIO



BOOKS

Tape and Wire Recording. A selection of articles reprinted from the pages of *The Radio Constructor*, covering both the theory and practical applications. A really useful book on this latest development of the hobby. 2/8

Receivers, Preselectors and Converters. Practical articles, again reprinted from past issues of *The Radio Constructor*, which will prove of interest to many radio enthusiasts. 2/8

TV Fault Finding. Profusely illustrated with photographs taken from a television screen depicting the faults under discussion, and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. 5/3

Inexpensive Television. Build yourself a television from surplus. Latest edition includes all the data necessary for any area. 2/8

World Radio Handbook (1955 edition). The S.W. broadcast enthusiasts' handbook. You are missing something from your hobby if you have not a copy of this excellent publication. 9/9

Report Pads. If you need that QSL card, send a comprehensive report. A convenient and accurate form for reporting. 3/9

Radio Amateur Operator's Handbook. An indispensable aid to the amateur transmitter and listener, containing all details of information which are constantly required. Prefix Lists, Zone Boundaries, Call Areas, Codes, and Mileage Tables, together with Maps and much other useful operating data. Revised edition. 3/2

Inexpensive Car Radio. In which two versions, one constructed from surplus and one from new components, are described. 1/8

Radio Control for Model Ships, Boats and Aircraft, by F. C. JUDD, G2BCX. A comprehensive work on this fascinating subject. Standard edition, 8/9. Cloth bound edition. 11/9

All above prices include postage and packing

All available from your local bookseller, or from:

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6518

Printed in Great Britain for the Proprietors and Publishers Data Publications Ltd., 57 Maida Vale, London, W9, by A. Quick & Co. Ltd., Oxford House, Clacton-on-Sea, Essex. Is obtainable abroad through the following: Collets Subscription Service, Continental Publishers & Distributors, Ltd., William Dawson & Sons Ltd. Australia and New Zealand: Gordon & Gotch Ltd. South Africa: Central News Agency. U.S.A.: Gilfer Associates. Holland: "Radio Electronica." Scandinavia: Intrapress. Registered for transmission by Magazine Post to Canada (including Newfoundland).




Jones
The

RADIO CONSTRUCTOR

for the Radio and Television Enthusiast

Volume 8
Number 10
MAY
1955

The "FULL-TONE"

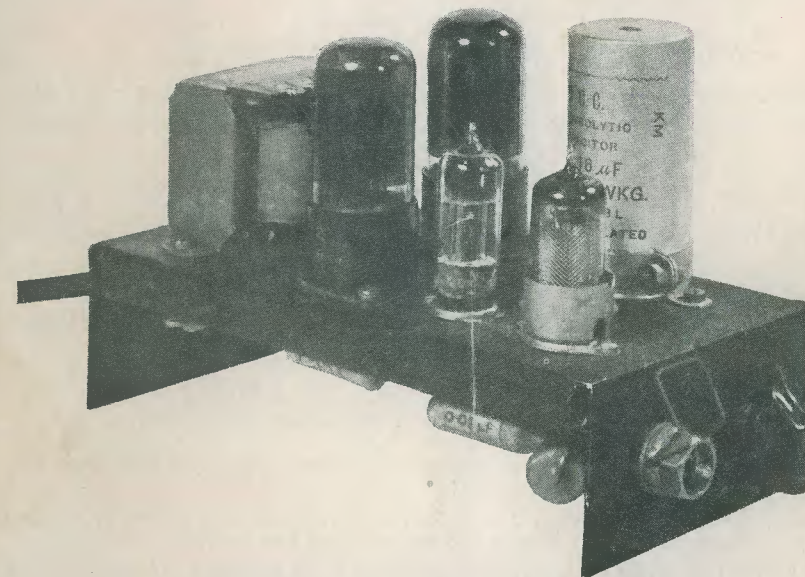

8-Watt AMPLIFIER

ALSO IN THIS ISSUE

RESISTANCE BRIDGE & CIRCUIT ANALYSER

CONSTRUCTIONAL CONTEST DETAILS

BATTERY COMMUNICATIONS RECEIVER

BAND III TEST CARD DESCRIPTION · BATTERY PRE-SELECTOR

CRYSTAL CONTROLLED RADIO CONTROL TRANSMITTER

TUNING INDICATOR FOR F.M. RECEIVERS

PROGRESSIVE RECEIVER, Part 2

USING METAL RECTIFIERS

INEXPENSIVE SERIES HEATER RESISTANCE, etc., etc.

16

The New GERNSBACK Library

High Fidelity: Design, Construction and Measurements. 12s. Postage 4d.

Transistors: Theory and Practice. By R. P. Turner. 16s. Postage 4d.

High Fidelity Techniques. By J. R. Langham. 8s. Postage 4d.

Model Control by Radio. By E. L. Stanford. 8s. Postage 4d.

Practical Disc Recording. By R. H. Dorf. 6s. Postage 4d.

Basic Radio Course. By J. T. Frye. 18s. Postage 6d.

Radio and TV Test Instruments. 12s. Postage 4d.

Radio Tube Fundamentals. By G. J. Christ. 8s. Postage 4d.

Radio and TV Hints. 8s. Postage 4d.

The Oscilloscope. By G. Zwick. 18s. Postage 4d.

Television Technotes. 12s. Postage 4d.

TV Repair Techniques. 12s. Postage 4d.

THE MODERN BOOK CO

BRITAIN'S LARGEST STOCKISTS OF ENGLISH & AMERICAN TECHNICAL BOOKS

Please write or call for our catalogue

19-23 PRAED STREET (Dept RC) LONDON W9

Open 6 days 9-6 p.m.

PADDINGTON 4185

Scottish Insurance Corporation Ltd.

62-63 CHEAPSIDE · LONDON · E.C.2

Established 1877

Telephone CITY 4936-9 (4 lines)

THE SHEDDING OF A LOAD

An ACCIDENT can cause serious financial embarrassment. Could you meet your commitments on the National Insurance Benefit?

A "SCOTTISH" Policy will carry the load for you if you are disabled by ANY ACCIDENT and will pay compensation for as long as two years for any one accident.

For a BENEFIT of £5 PER WEEK the annual premium varies between £1 10s. and £2 2s. 6d. according to occupation, and the premium can be paid half-yearly or quarterly if desired.


If you will complete and return this form to the Corporation's office at the above address, a quotation will be sent with a proposal for completion, or write for details quoting reference /JB.

NAME (Block Letters)

OCCUPATION

ADDRESS (Block Letters)

/JB

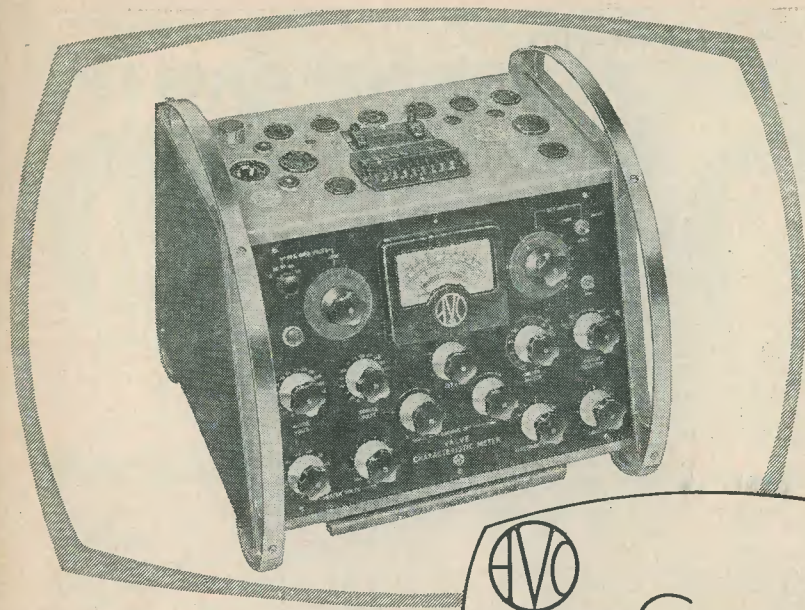

AVO
VALVE Characteristic
METER Mk III

The AVO Valve Characteristic Meter Mark III offers the Radio Engineer far more than is generally implied by the words "a valve tester".

This compact and most comprehensive Meter sets a new high standard for instruments of its type. It will quickly test any standard receiving or small transmitting valve on any of its normal characteristics under conditions corresponding to a wide range of D.C. electrode voltages.

A new method of measuring mutual conductance ensures that the instrument can deal adequately with modern valves of high slope and short grid-base such as are commonly used in T.V. receivers.

List Price £60



Regd. Trade Mark

A comprehensive Instruction Book and detailed Valve Data Manual are provided.

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.

AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD · LONDON · S.W.1.

Phone: VICTORIA 3404 (9 lines)

V.C.A.

PROVIDES all necessary data to enable Ia/Va, Ia/Vg, Ia/Vs, etc. curves to be drawn.

MEASURES mutual conductance up to 30mA/V.

DETERMINES inter-electrode insulation with heater both hot and cold.

GIVES direct measurement of "gas" current.


TESTS rectifying and signal diodes under reservoir load conditions.

COVERS all normal heater voltages up to 117V.

CIRCUIT improvements provide accurate setting and discrimination of grid voltage over the full range to 100V. negative.

A relay protects the instrument against damage through over loading the H.T. circuits and also affords a high measure of protection to the valve under test.

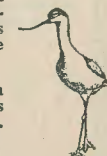The instrument is fitted with a hinged fold-over lid which protects the valve holders when not in use.



AVOCET

TRADE MARK

V.C.A.

"A great help and worth a fortune"

**ABSOLUTELY ESSENTIAL TO
EVERY RADIO AND T.V.
SERVICE ENGINEER**

**SAYS OWNER OF THE
LAST EDITION which was
COMPLETELY SOLD OUT
IN A FEW WEEKS!**

**YOURS for 7 days'
Free Examination**

T.V. SERVICING DATA FOR :-

Ace, Alba, Ambassador, Argosy, Baird, Beethoven, Bush, Champion, Cossor, Decca, Ekcovision, English Electric, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B., McMichael, Marconiphone, Masteradio, Mullard, Murphy, Pam, Peto Scott, Philco, Philips, Pye, Raymond, Regentone, R.G.D., Sobell, Stella, Ultra, Vidor, etc.

RADIO SERVICING DATA FOR :-

Ace, Ambassador, Beethoven, Bush, Champion, Cossor, Decca, Denco, Eddystone, Ekco, Etronic, Ever Ready, Ferguson, Ferranti, G.E.C., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Mullard, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Pye, Rainbow, Raymond, Regentone, R.G.D., Sobell, Ultra, Vidor.

- ★ 5 volumes strongly bound in maroon cloth.
- ★ 2,592 pages of up-to-the-minute data, and practical information written by skilled Radio & T.V. engineers.
- ★ 1,250 models and more—the wanted data you must have for profitable servicing work.
- ★ 2,700 circuit, component and chassis layout diagrams. Also photographs and explanatory illustrations.
- ★ **FREE** 2 Years' Technical Advisory Service.

NOTHING TO PAY
and there is no obligation
Do not miss this opportunity

*Owners of the last edition wrote :—
"The books are a great help and worth a fortune" (S.R.E., Whitby).
"I have serviced lots of television receivers with your invaluable books" (M.B.W., Berwick-on-Tweed).
"Thank you for your wonderful service" (F.W., London).*

POST THE CARD TO-DAY

JUDGE IT FOR YOURSELF!

For office use
AT

Please send me Newnes RADIO AND TELEVISION SERVICING. It is understood that I may return the work within eight days. If I keep it I will send a first payment of 7s. 6d. eight days after delivery, and 10s. 0d. monthly thereafter, until the sum of £8. 17s. 6d. has been paid. Cash price within eight days is £8. 10s. 0d.

Name.....

Address.....

Occupation.....

Your Signature.....
(Or your Parent's Signature if under 21)

Place X where it applies

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

RTV. 55

GREAT NEW EDITION ENLARGED! EXTENDED!

NEWNES

"Radio and Television Servicing"

GET IT NOW!

7 DAYS' FREE EXAMINATION

**1,250 MODELS (INCLUDING 1954)
2,700 DIAGRAMS • 2,592 PAGES**

**BAND I (B.B.C. ALL AREAS) and
BAND III (I.T.A. Commercial Stations)**

THIS CERTAIN MONEY MAKER is now ready for you—enlarged, extended, and with wanted servicing data for more than 1,250 Radio and TV models. Packed with circuits and information you constantly need, the work is an investment which will pay for itself almost as soon as you receive it—and it will keep on making money for you!

The work provides details of Band I (B.B.C. all areas) and Band III (I.T.A. Commercial Stations) receivers, and the first British combined amplitude modulation/frequency modulation radio receivers.

This up-to-the-minute edition will be snapped up even more eagerly than the last one, which was sold out in a few weeks—so send for Free Examination now. Judge the value of this complete guide to profitable servicing—it's yours for 7 days, without obligation IF YOU HURRY. POST THE CARD NOW.



**ALL THE POPULAR MODELS
SEE LIST ON BACK**

IN 5 VOLUMES

Postage
will be
paid by
George Newnes
Ltd.


No Postage
Stamp
necessary if
posted in
Gt. Britain or
Northern Ireland

BUSINESS REPLY CARD
Licence No. W.C. 1129

GEORGE NEWNES, LIMITED,
66/69, GREAT QUEEN STREET,
LONDON, W.C.2

MAXI-Q
REGD.


IMPROVED I. F. TRANSFORMERS

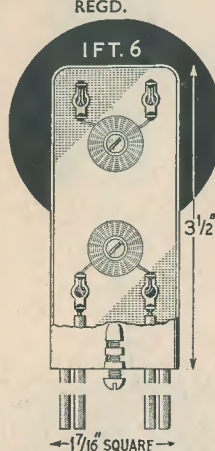

IFT.6/465 kc/s or 1.6 Mc/s.—A superior I.F. transformer for use in high quality receivers and tuners. Permeability tuned, Litz wound coils, using iron dust cores, and high quality silver mica condensers housed in an extruded aluminium can. Termination is made by four coloured leads. Coupling is optimum at 465 kc/s and slightly sub-optimum for increased selectivity at 1.6 Mc/s. IFT.6/465: Q at 465 kc/s—130. IFT.6/1.6: Q at 1.6 Mc/s—125. The IFT.6A has all leads brought out at the bottom, while IFT.6B has a screened-grid lead. When ordering full details should be given, e.g., IFT.6A/465.

Fixing: Two P.K. self-tapping screws on $1\frac{1}{2}$ " centres. Retail Prices: Type A, 9/- each, Type B, 9/4 each.

IFT.11/465 kc/s or 1.6 Mc/s.—Miniature I.F. transformers for 465 kc/s or 1.6 Mc/s, giving excellent performance at low cost. The coils are Litz wound and permeability tuned with high-grade iron dust cores. Coupling is critically adjusted to give maximum gain with good selectivity. Ideal for use with miniature B9A or B7G based valves. IFT.11/465: Q at 465 kc/s—75. IFT.11/1.6: Q at 1.6 Mc/s—100. Also available for 10.7 Mc/s. Fixing: Two 6 B.A. screws provided. Screening Can: Extruded aluminium. Retail Price: 6/- each.

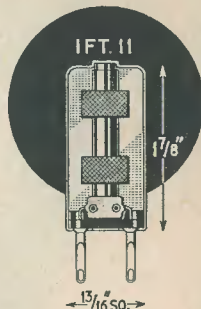

Obtainable from all reputable stockists, or in case of difficulty direct from **DENCO (CLACTON), LTD.** Send 1/- in stamps for General Catalogue.

DENCO (CLACTON) LTD 357/9 Old Rd. Clacton-on-Sea Essex

STOP PRESS: Osram "912" and Mullard "5-10" Amplifier chassis and bronze finished front panel 21/- each. Long and Medium wave TRF Coils, wound on polystyrene formers 9/- per pair. IFF.1, improved 465 kc/s I.F. Filter, wound on polystyrene former 4/1.

LINE OUTPUT TRANSFORMER TYPE L.O.352

Type L.O.352 is the type number of an entirely new Allen line output auto-transformer now available to manufacturers and the home-constructor. It functions in conjunction with PL81 PY81 valves, and provides an E.H.T. voltage whose regulation is better than 5MΩ. The associated components are the D.C.605/C scanning yoke, G.L.16 linearity control, and G.L.18 width control.

Line Output Transformer type L.O.352, 42/6.

Scanning Yoke type D.C.605/C 39/6.

Width Control type G.L.18, 7/6.

Linearity Control type G.L.16, 7/6.

Our standard, well proven components are also available:

Line Output Transformer type L.C.308, 40/-.

Scanning Yoke type D.C.300/C, 39/6.

All the above are available direct from

ALLEN COMPONENTS LIMITED

Crown Works 197 Lower Richmond Road Richmond Surrey
Telephone PROspect 9013

Send 9d. and S.A.E. for recommended Wide-Angle Circuit Diagrams

NEW!

EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY

Specialty prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business—these Practical Courses are intended for YOU—and may be yours at Very Moderate Cost.

EASY TERMS FROM 15/- A MONTH

POST THIS COUPON TODAY

To E.M.I. INSTITUTES, Dept. 179X,
Grove Park Road, London, W.4.

SUBJECTS(S) _____

NAME _____

ADDRESS _____

FREE



COURSES WITH PRACTICAL EQUIPMENT INCLUDE: Radio (Elementary and Advanced), Television, Mechanics, Electricity, Chemistry, Photography, Carpentry. Also Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages, Etc.

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation

May

1956

Instrument cases in steel, complete with light alloy front panel. Colours Black (Red and Green 10 per cent extra). Back punched for ventilation.

Type "9," 8" x 9" x 8" is 18/6 with panel in light alloy.

Type "12," 10 1/2" x 12" x 10 1/2" is now 25/- with panel in light alloy.

Type "9-12," 9" x 12" x 9" is now 21/- with panel in light alloy.

Chassis at the following prices. These are in aluminium of 18G.

6 x 4 x 2 1/2	5/6	6 x 5 x 2 1/2	7/6
8 x 6 x 2 1/2	8/-	10 x 6 x 2 1/2	8/6
10 x 7 x 2 1/2	9/-	10 x 8 x 2 1/2	9/6
12 x 8 x 2 1/2	10/6	10 x 9 x 2 1/2	11/-
14 x 8 x 2 1/2	13/9	14 x 9 x 2 1/2	14/-
16 x 8 x 2 1/2	14/9	16 x 9 x 2 1/2	15/6

Suppliers of technical publications. A full range of components, by well-known manufacturers, are stocked, Mullard, Brimar, Cossor, T.C.C., Dubilier, Erie, R.E.P., Wearite, Elstone, Morganite, etc. High stability 1, 2 and 5 per cent resistors available from stock or to order.

INTRODUCING RADIO RECEIVER Price Post
SERVICING by E. M. Squire 10/6 6d.

RADIO RECEIVER CIRCUITS
HANDBOOK by E. M. Squire 6/- 6d.

RADIO RECEIVER SERVICING AND
MAINTENANCE by E. J. G. Lewis 12/6 6d.

RADIO SERVICE TEST GEAR
by W. H. Cazaly 6/- 6d.

SHORT WAVE RADIO
by J. H. Rayner 10/- 6d.

ELECTRONIC MEASURING INSTRUMENTS
by E. H. W. Banner 45/- 1/1

TELEVISION SIMPLY EXPLAINED
by R. W. Hallows 10/6 5d.

RADIO LABORATORY HANDBOOK
by M. G. Scroggie 25/- 6d.

FOUNDATIONS OF WIRELESS
by M. G. Scroggie 12/6 6d.

RADIO DESIGNERS HANDBOOK
F. Langford-Smith 42/- 1/6

Any book on Radio T.V. or Electronics can be supplied either from stock or to order at short notice.

KENDALL AND MOUSLEY LIMITED

Electronic Engineers and Laboratory Equipment Manufacturers
18 MELVILLE ROAD BIRMINGHAM 16

Smith's of EDGWARE ROAD

Component Specialists since
Broadcasting Started

for all Components required to construct the

"LODESTAR" TAPE RECORDER


Send for Price-list of parts, also
for Booklet containing full con-
structional details, price 3/6.

Demonstrations at the address below

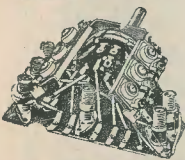H. L. SMITH & CO. LTD
287/289 EDGWARE ROAD · LONDON · W2
Hours 9 till 6 (Thurs. 1 o'clock). Tel.: Paddington 5891
Near Edgware Road Stations, Metropolitan and Bakerloo

LEADING RECEIVER MANUFACTURERS ARE SURE OF TOP COIL PERFORMANCE

Be like the many famous firms who, by specifying
Osmor High "Q" Coils in thousands, take no
chances about quality!




'Q' COILPACKS size only
1½ x 3¼ x 2¼ with variable iron-
dust cores and polystyrene
formers; built-in trimmers; tropi-
calised; realigned receiver-tested
and guaranteed; only 5 connec-
tions to make. All types for
mains and battery superhets and
T.R.F. receivers. Ideal for the

reliable construction of new sets, also for conversion of the
21 Receiver. TRI 196, type 18, Wartime Utility and others.

Our Technical Dept. will be pleased to answer (by letter
only) any enquiry relating to circuits in which Osmor Coils
or Coil Packs are used or are intended to be used.

Super 'Q' Cup Coils for Max.

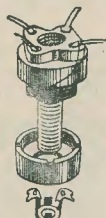Selectivity A full range is avail-
able for all popular wavebands and
purposes. The magnetic screening of
the cup prevents other components
from absorbing the coil's power thus
maintaining the high 'Q' value. Simple
one-hole fixing. * Only 1" high.
* Packed in damp-proof containers.
* Adjustable iron-dust cores. * Fitted
tags for easy connection. L or MW.



inc. Circuit 5/-

OSMOR RADIO PRODUCTS LTD. (R.C.23)
418 BRIGHTON ROAD, SOUTH CROYDON
SURREY Telephone CROYdon 5148-9

ARTHURS HAVE IT!

LONDON'S OLDEST RADIO DEALERS
LARGE VALVE STOCKS

AVOMETERS IN STOCK
Avo Test Meters and Signal Generators
and Taylor Meters
Leak Point One Amplifiers and Tuning
Units

Chapman Tuning Units
Crystal and Moving Coil Mics.
Decca Replacement Heads and Pickups
Goodman's Axiom 150 Speakers
Partridge Output Transformers for
Williamson Amplifier
All Components for the Radio Construc-
tor's 16" Telesvisor

Weare & Wright Tape Deck, £35
LATEST VALVE MANUALS

Mullard, Osram & Brimar No. 4, 5/- each
Mazda 2/- each Postage 6d. each
TELEVISION SETS, WIRE AND TAPE
RECORDERS ALWAYS IN STOCK
Goods offered subject to price alterations
and being unsold

Arthurs first Est
1919

Proprietors: ARTHUR GRAY LTD.

OUR ONLY ADDRESS Gray House
150-52 Charing Cross Road
London WC2

TEMPle Bar 5833/4 and 4765 WRITE FOR LISTS

Frequency Modulation Tuner

described in the July and Sept. 1954
issues.

JACKSON BROS. dial and condenser
£1 5 3

Completely drilled chassis 8 0

All coils with S.M. Condensers and
cans £1 2 6

Complete Set of Parts, (1 ss valves)
including pair of matched Ger-
manium crystals and small items
such as nuts and screws £5 0 0

Complete Tuner, assembled and
aligned £10 0 0
(P.T. extra)




JASON MOTOR COMPANY

328 CRICKLEWOOD LANE
LONDON NW2

All these  CRYSTAL PRODUCTS

—and more too—go to show that

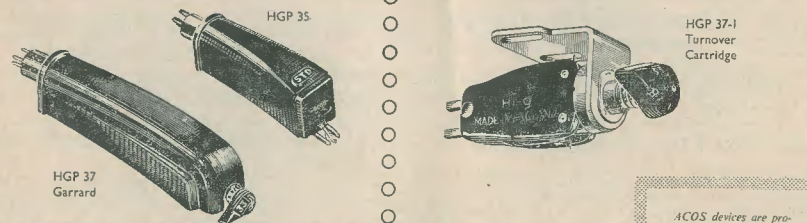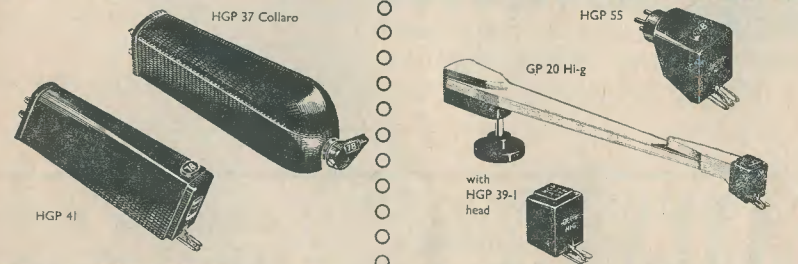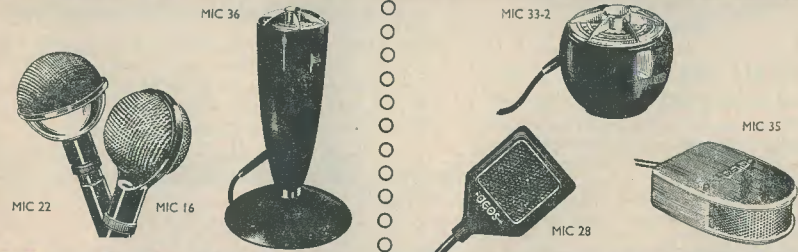FAITHFUL REPRODUCTION NEED NOT BE EXPENSIVE



ACOS devices are pro-
tected by patents, patent
applications and regis-
tered designs in Great
Britain and abroad.



.....always well ahead

COSMOCORD LTD · ENFIELD · MIDDX · Telephone Enfield 4022



**POST TODAY FOR OUR BROCHURE ON
THE LATEST METHODS OF HOME
TRAINING FOR OVER 150 CAREERS
& HOBBIES**

PRIVATE & INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M.Brit. I.R.E. Examinations, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training

- ★ The teaching methods are planned to meet modern industrial requirements.
- ★ A tutor is personally allotted by name to ensure private and individual tuition.
- ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

**NEW LEARN THE PRACTICAL WAY
COURSES WITH EQUIPMENT**

With many of our courses we supply actual equipment which is sent upon enrolment and remains your property. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

**Courses
from 15/-
per month**

POST THIS COUPON TODAY

Please send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 179K, Grove Park Road, London, W.4. May

NAME _____
ADDRESS _____
SUBJECT(S) _____ IC.38

EMI INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation.

LANES (RADIO) LTD
The Amateur's Paradise

11 GARDNER STREET
— BRIGHTON 20773

ALL LEADING MAKES OF STANDARD COMPONENTS FROM STOCK

★ **NOTE—All Tools advertised in April issue still available. LET US QUOTE inclusive price for your full requirements**

FREE To introduce our service to *Radio Constructor* readers a free copy of Denco's FM Feeder Unit booklet will be given with all orders of £1 or over.

ELECTROLYTIC CONDENSERS

16mfd. 450V	3/8
8mfd 450V	2/-
32 x 32mfd 350V	4/6
0.001 mica	4d.

**COMPLETE RANGE OF RESISTORS
from 10 ohm to 10 meg**

$\frac{1}{4}$, $\frac{1}{2}$, 1W, also 3.5 10.15W

**CRYSTAL DIODES 1/6 each
FILAMENT TRANSFORMERS
230V 6.3 1.5A 5/- each**

**LANE
OSCILLATOR
UNITS**

DENCO DETAILED PRICE LIST AND AERIAL DATA

TERMS.—Cash with order or C.O.D. (over £1). Please add postage and packing on orders below £1. Over £1 POST FREE

For FM Units 1/6
Drilled Chassis 7/6
Set of Fixed Condensers 31/-
Set of Resistors 10/6

★ **LANE
Mk. 6
TAPE
TABLES
£18.10.0**

SCREWDRIVER MAINS TESTER 6/9 ea. RODING COIL PACKS 3-WAVE BAND L.M.S. £2.9.9

The **Radio Constructor**

incorporating THE RADIO AMATEUR



CONTENTS FOR MAY

- 584 Suggested Circuits: A Tuning Indicator for F.M. Receivers, by G. A. French
- 586 Club News
- 587 In Your Workshop—including a Circuit for a Battery Communications Receiver, by J. R. D.
- 592 A Pre-Selector for the R.C.S. Battery Receiver, by J. Sinclair
- 596 "Belling-Lee" Band III Transmitter—including description and illustration of the Test Card
- 597 Inexpensive Series Heater Resistance, by M. C. Paul
- 600 Using Metal Rectifiers, by C. Noall
- 604 Book Reviews
- 605 Combined Resistance Bridge and Circuit Analyser, by J. Chandler
- 608 The "Full-Tone" 8-watt Amplifier, Part 1, by M. Harvey
- 613 Can Anyone Help?
- 614 A Progressive Receiver, Part 2, by A. S. Carpenter
- 616 Notes on Radio Control: Part 7, A Crystal Controlled Transmitter, by Quench Coil
- 620 Radio Miscellany, by Centre Tap
- 622 Indoor Transmitting Aerials, by O. J. Russell, B.Sc. (Hons.), G3BHJ
- 626 Let's Get Started: Part 23, Frequency Measurements, by A. P. Blackburn
- 630 Portable Amateur Radio Equipment Contest—Details of a Constructional Contest organised by the QRP Society

VOL. 8 NO. 10
ANNUAL SUBSCRIPTION 18/-
MAY 1955

Editorial and
Advertising Offices

57 MAIDA VALE LONDON W9

Telephone
CUNNINGHAM 6518

Telegrams
DATABUX, LONDON

Editor
C. W. C. OVERLAND, G2ATV

Advertising Manager
F. A. BALDWIN, A M I P R E

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor. Opinions expressed by contributors are not necessarily those of the Editor or proprietors


NOTICES

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

All MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

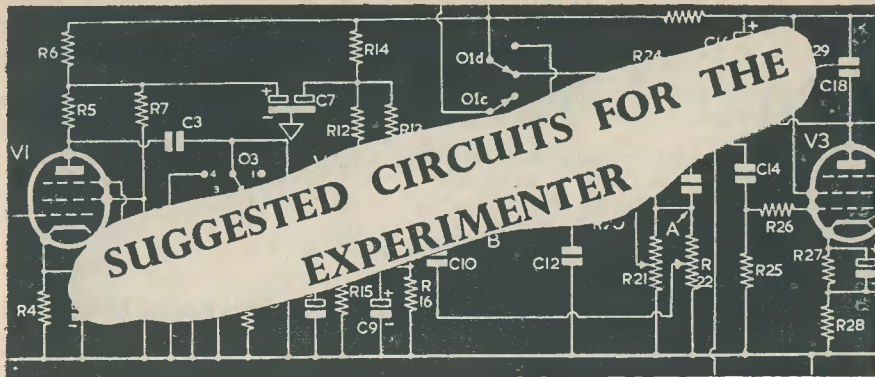ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR, 57 Maida Vale, London, W.9 Telephone CUN. 6518



The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

No. 54: A TUNING INDICATOR FOR F.M. RECEIVERS

ONE OF THE MORE DIFFICULT PROBLEMS to tackle in the design of f.m. receivers is that of accurate tuning indication. The situation is further complicated by the fact that such indication is even more necessary for f.m. reception than it is for a.m. reception. This is due to the fact that an f.m. receiver which is apparently correctly tuned, and which introduces no distortion at all at normal modulation levels, may give rise to considerable distortion when these levels are increased; as can occur during the louder passages of music in a symphony concert, for instance.

In this country, the most generally accepted commercial method of indicating the position of correct tuning of f.m. receivers consists, at present, of running a normal tuning indicator from the negative end of the discriminator stabilising condenser (possibly via a fixed potentiometer to reduce the voltages obtained). Whilst this process offers a simple and inexpensive solution to the tuning indicator problem it is not entirely satisfactory, since the i.f. response of an f.m. receiver is, ideally, flat; and recourse has to be made to "peaking" the i.f. transformers at the centre frequency in order to obtain a final, sharp, tuning indication. Unfortunately, i.f. transformer "peaking" cannot be carried too far without introducing distortion, with the result that the final "peaked" tuning indicator deflection is usually small compared with the initial deflection given by tuning in the station

which is being received. Also, such "peaks" as are given are liable to drift away from the centre frequency with time, this being due to spread and deterioration in the i.f. valves, plus any accidental i.f. detuning which may result from knocks, heat, and similar causes.

It is evident, that, for best results, some alternative method of tuning indication is required. This month's circuit suggests an accurate tuning indicator which may be fitted to f.m. receivers employing a balanced ratio discriminator stage.

The Discriminator

A typical discriminator of this type is illustrated in Fig. 1. In this diagram, the stabilising load resistor ($R_{11} + R_{12}$) is centre-tapped, the tap being taken to chassis. The audio take-off point is taken from the tertiary winding of the discriminator transformer.

When the discriminator transformer is correctly adjusted and an r.f. signal is injected into its primary, a d.c. voltage appears across the stabilising condenser, together with another between either end of the stabilising condenser and the audio take-off point. When the injected signal is of the correct frequency the second voltage should be equal to exactly one-half of the first. Since the voltage across the stabilising condenser appears also across the load resistor $R_{11} + R_{12}$, which is centre-tapped to chassis, it follows that the voltage appearing at the take-off point has a value which is zero with

respect to chassis. This is, in practice, what occurs. If, however, the injected frequency varies, the voltage at the take-off point varies also; becoming positive with respect to chassis for a change in frequency in one direction, and negative for a change in frequency in the other direction.

The d.c. voltage at the take-off point with respect to chassis provides a precise measure of tuning accuracy; the position of correct tuning being represented by zero voltage.

centre-reading 0-1 millimeter. Zero voltage is represented by the centre reading of the meter.

As may be seen, the value of the circuit lies in the fact that the two triodes are balanced against each other. Because of this, variations in h.t. and heater supply voltages are largely cancelled out. Also, the fact that a double triode is used provides some insurance that shifting characteristics in the individual triodes due to age will lie closely together.

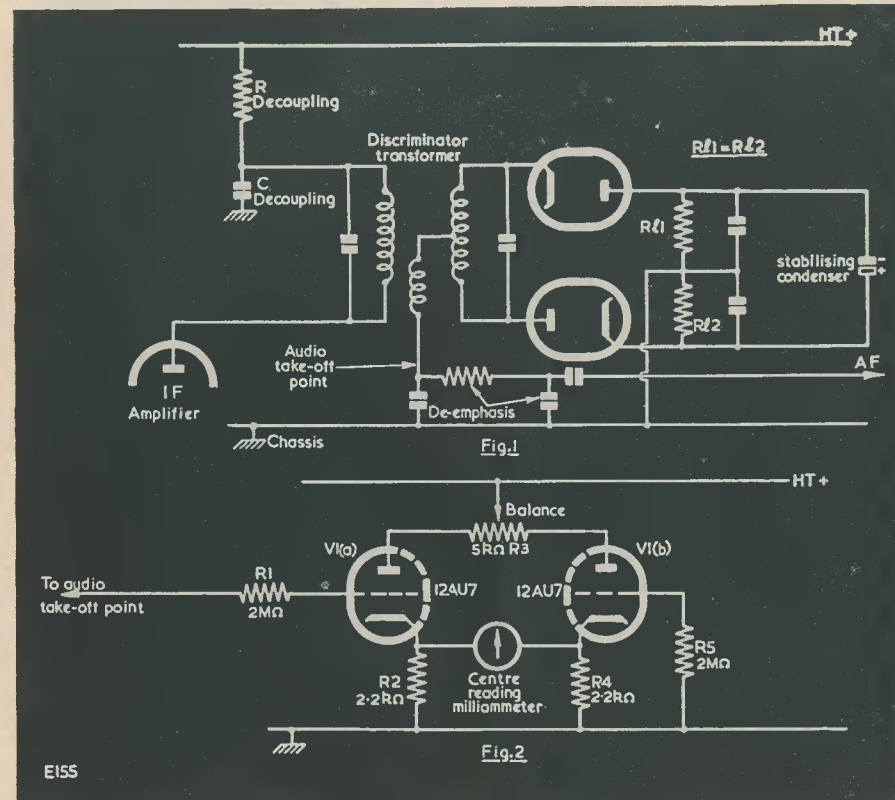


Fig. 1: Typical discriminator circuit

Fig. 2: Tuning Indicator circuit described in this article

Tuning Indicator

The tuning indicator which forms the basis of this month's contribution is illustrated in Fig. 2. It employs a double triode and gives its final indication by means of a

It will be noted that R_1 and R_5 both have the same value. This, again, helps to ensure balanced operation; it being assumed that the d.c. source impedance at the take-off point is very low compared with R_1 . For

best results it would probably be advisable to have the values of the two cathode resistors, R2 and R4, within 5% of each other.

Setting Up

As shown in the diagram, the indicator will give full meter deflection for input voltages of 1.5 to 2 volts on either side of zero. If the receiver with which the indicator is to be used provides larger voltages, it will be necessary to insert a limiting resistor in series with the milliammeter. The value of this resistor should be found by experiment.

If the milliammeter employed has very light damping, it is possible that its needle may flicker at high modulation levels. If this occurs, the tendency may be cleared by connecting a 0.01 μ F condenser between the grid of V1(a) and chassis.

The indicator circuit is finally set up by short-circuiting the audio take-off point to chassis and adjusting R3 to give a centre reading of the meter. This reading will then be that which corresponds to accurate tuning of the receiver.

CLUB NEWS

Details for insertion in this section should reach us not later than 7th of month before publication.

YORK AMATEUR RADIO SOCIETY

The Annual General Meeting was held on the 11th February, when the following officers were elected: Chairman, E. Warwick, G3GDE; Secretary, J. O. Yarker, G3GJY; Treasurer, L. Brown, G3HLT. Committee: G. F. Nottingham, G3DTA; P. S. Robson, G3FYP; A. Horner, G3FTS; P. Dekker. The meeting night has been changed to Thursdays at 7.30 p.m. The club room is in Fetter Lane facing rear entrance of Queen's Hotel. Lectures and demonstrations of radio equipment are a weekly feature. Morse lessons are now in progress each week. Prospective members and visitors are cordially invited. Hon. Sec.: J. O. Yarker, 14 Bewlay Street, Bishopthorpe Road, York.

* * *

EAST KENT RADIO SOCIETY

The Society meets fortnightly on Tuesdays at "The Two Brothers," Northgate Street, Canterbury. Nearly all radio and electronic subjects are covered. Raffles are held regularly, and lectures with demonstrations are given. New members are welcome, also visitors in the district. Hon. Sec.: Mr. D. Williams, "Llandogo," Bridge, Canterbury.

* * *

CAMBRIDGE AND DISTRICT AMATEUR RADIO CLUB

The Annual General Meeting was held on the 25th March, when the following officers were elected: President, Mr. C. H. Babbs, G5IG; Chairman, Mr. L. Gostelow, G2FOW; Treasurer, Mr. P. J. Broom, G5DQ; Secretary, Mr. F. A. E. Porter.

Meetings are held every fourth Friday at the "Jolly Waterman," Chesterton Road, and new members are welcome. The next meetings are on the 20th May and the 17th June (junk sale). A Morse practice class has been started for beginners. Hon. Sec.: F. A. E. Porter, 38 Montague Road, Cambridge.

THE SLADE RADIO SOCIETY

Headquarters: The Church House, High Street, Erdington, Birmingham 23.

Forthcoming events: 8th May, first of the season's Harcourt Trophy tests; 13th May, "Amateur Radio Direction Finding," by N. B. Simmonds (member); 22nd May, R.S.G.B. National D/F Contest, Slade/Rugby preliminary; 27th May, "Past and Present in Amateur Radio," by E. G. H. Brown, G5BJ.

The club station at the Church House is open every day of the week for the use of members. Transmitting and receiving equipment is being installed and constructional facilities are available. Full particulars of the Society and its activities are obtainable from the Hon. Sec.: Mr. C. N. Smart, 110 Woolmore Road, Erdington, Birmingham 23.

* * *

EAST GRINSTEAD AND DISTRICT AMATEUR RADIO CLUB

At the time of writing the club has to share a hall with other clubs, which restricts activities, but it is hoped soon to obtain exclusive accommodation. The club transmitter is now under construction and it is hoped to be on the air this year. Morse classes are held weekly. New members are welcomed; full particulars can be obtained from the Hon. Sec.: Mr. R. A. Burnett, 19 Stockwell Road, East Grinstead, Sussex.

* * *


CLIFTON AMATEUR RADIO SOCIETY

The first DF contest in the 1955 series takes place on Sunday, 8th May in the vicinity of Farnborough, Kent. The club station, G3GHN/A, will be operating portable between 11.00 hrs. and 16.00 hrs. on a frequency of 3,504 kc/s and as only low power will be used reports and QSO's will be welcomed.

Tape recording will be covered by Mr. L. Barnes on 20th May and the evening will comprise a demonstration and talk on the equipment being used.

Meetings are held every Friday at the clubrooms, 225 New Cross Road, London, S.E.14, at 7.30 p.m. Details of membership may be obtained from the Hon. Sec.: C. H. Bullivant, G3DIC, 25 St. Fillans Road, Catford, S.E.6.

IN YOUR WORKSHOP

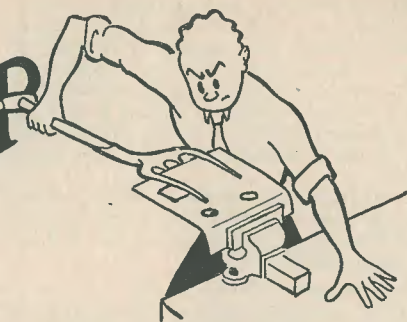

In which J. R. D. discusses Problems and Points of Interest based on Letters from Readers and his own experience

I DON'T KNOW WHY IT SHOULD BE, BUT IT nevertheless seems to be an unassailable fact that as soon as anyone buys a television receiver these days they immediately assume a meanness of outlook which they never exhibited before. One would think that a person who buys a television would also be prepared to pay something towards its upkeep; but this does not seem to be the opinion of the set-owner. Whenever possible, he wants his repairs done on the cheap.

Bitter Experience

I think a number of readers will agree with me on this point; and I know quite a few technical people around London who have all had more or less the same sort of experience that I have had myself.

What usually happens is that the person who owns the television approaches any of his technical friends and informs him that some little thing has gone wrong with his receiver. "Some little thing" can, of course, be anything between the line-hold control out of adjustment to a nice, obscure, intermittent shorted turn or two in the deflector coils. However, the technician is assured that there cannot be much wrong with the set; and perhaps he would care to pop in one evening and just "have a look" at it. If that technician is mug enough to fall for that one he would quite probably end up by carting all his test gear around to the house and spending an entire evening wrestling with the dusty innards of a receiver which should have gone in for overhaul years ago. Furthermore, once he has touched the set, even if only to change a valve, he is "married" to that set for evermore. If it goes wrong at any later date he is the person who will be blamed for it.

I know I sound a little bitter about all this, but some television-owners have an almost incredible amount of neck. If one is "awkward" enough to get them to state

why they won't take their set to a shop to have it repaired, one finds out eventually that they just don't want to fork out the money to have the job done properly. They would prefer to plague their acquaintances instead.

I know that some television repair bills are high, but that is mainly because television servicemen nowadays are skilled men who deserve every penny of the salary they earn. In any case, if the television owner wants to keep his repair bills down there are plenty of retailers who run maintenance schemes at very reasonable prices.

Alternatively, of course, it may quite simply be that I move in the wrong circle of acquaintances!

Caravan Dweller

I have recently received a letter from a reader who has just moved into a caravan. He is a short-wave enthusiast and naturally feels rather keenly the fact that he now has no mains supply available; especially so since this deprives him of the use of his R.1155 and all the gear he has made to go with it. He asks if it is possible to give some information on the construction of a communications receiver employing 1.4V B7G valves; the set to include a crystal filter, variable selectivity and a b.f.o.

Apart from the crystal filter and the variable selectivity, such a receiver should not be too hard to make. There are one or two important points to remember, however.

The first of these is that 1.4V battery valves are by no means as "lively" as are mains valves, and it is necessary to pay greater attention to circuit constants if the maximum amount of gain is to be extracted from them. Secondly, battery frequency changers do not oscillate as readily as do their mains counterparts. In consequence of this, it may be difficult to obtain a high

value of conversion conductance (i.e., change in current, at i.f., at the anode of the frequency changer for change in voltage, at signal frequency, at the signal grid) all over a short-wave band whilst using the conventional 500pF tuning condenser. If one is looking for optimum results it would probably be best to use a tuning condenser of, at most, 350pF.

Apart from this, the use of battery valves does not raise too many difficulties. Indeed, it can introduce simplifications, as the following notes may show.

Battery Receiver

Fig. 1 shows the i.f. and a.f. stages of a practicable battery communications-type receiver employing valves from the current Brimar range (or their direct equivalents). There are several points of interest in this circuit.

Starting at the output stage in the diagram, it will be seen that either a loudspeaker or headphones may be used. The latter can be either high or low impedance and are plugged into appropriate jacks. The speaker may also be switched out, if desired. In order to obtain the maximum audio output, a speaker transformer having as close a ratio as possible to that specified should be chosen. It might be advisable to try and obtain a speaker transformer designed especially for battery output valves: such transformers often have a primary wound with a large number of turns (of finer wire) than is normally used in speaker transformers intended for general use.

A grid bias battery is employed in the circuit. Whilst a battery of this type is usually considered to be somewhat old-fashioned these days, its inclusion is certainly worth while in this instance. The reason for this is that if bias were obtained from the voltage dropped across a resistor in series with the negative h.t. supply lead (i.e., "automatic bias"), this voltage would be liable to vary considerably with a.v.c. voltage, since a large number of the valves in the set are a.v.c. controlled. Also, the requirement of an r.f. volume control necessitates having available a source of fairly high negative voltage, and it would be wasteful to obtain this from the h.t. battery with the aid of an automatic bias dropping resistor.

The diode-pentode stage is quite conventional, the single diode necessitating a common load, (R9), both for a.v.c. and sound detection. In consequence of this common load the a.v.c. has no delay.

The circuit around the r.f. volume control, R10, also merits some consideration. This control only becomes effective when a.v.c. is switched out, and it varies the potential of the entire a.v.c. line. The 9-volt bias

voltage obtainable from a single grid bias battery should be sufficient to cause the receiver to be almost completely muted at the minimum setting of the r.f. volume control. However, should this not occur when powerful signals are being received, two grid bias batteries may be connected in series to provide a higher total negative control voltage. The bias supply is switched out of circuit when the receiver is switched off in order to prevent a continual discharge through the volume control. As is to be expected with a receiver of this nature, overloading at the diode detector, or at the last i.f. stage, will almost inevitably occur when the r.f. volume control is turned to its maximum setting whilst receiving strong signals.

B.F.O. Stage

A b.f.o. stage is provided with the receiver as well. This is only brought into operation when the a.v.c. circuit is cut out. Otherwise, it would be possible for the output of the b.f.o. to be rectified by the diode of V3, and thus generate a high a.v.c. voltage which would reduce the sensitivity of the receiver. The b.f.o. stage should be completely screened, and its trimmer, C13, may be brought out as a panel control. A Colpitts circuit is shown in the diagram. This circuit has the advantage of allowing a single, untapped coil (L1), to be used; untapped coils being readily available to the amateur from discarded i.f. transformers and similar components. The two condensers C15 and C16 should each have approximately the same value, their combined capacity, in series, being slightly less than that normally required by the particular coil chosen to resonate at the intermediate frequency. The trimmer C13 will then make up the requisite tuning capacity. The grid leak, R11, may require slight final adjustments in value in order to provide an oscillation which gives a pure tone free from squegging.

The b.f.o. is switched on and off by switching its filament supply. This is more economical on battery drain than would be the alternative method of switching the h.t. supply. The b.f.o. stage is coupled into the receiver capacitively; the coupling being provided by twisting its insulated output lead several times around the lead to the second detector diode. The resulting capacity (some 2 to 10pF) will then provide adequate coupling.

Variable Selectivity

A measure of variable selectivity is provided by the switch S1. This switch cuts out the last i.f. stage, V2, when it is required to use the receiver for normal broadcast reception. S1 should be fitted into the circuit with some care as, should any capaci-

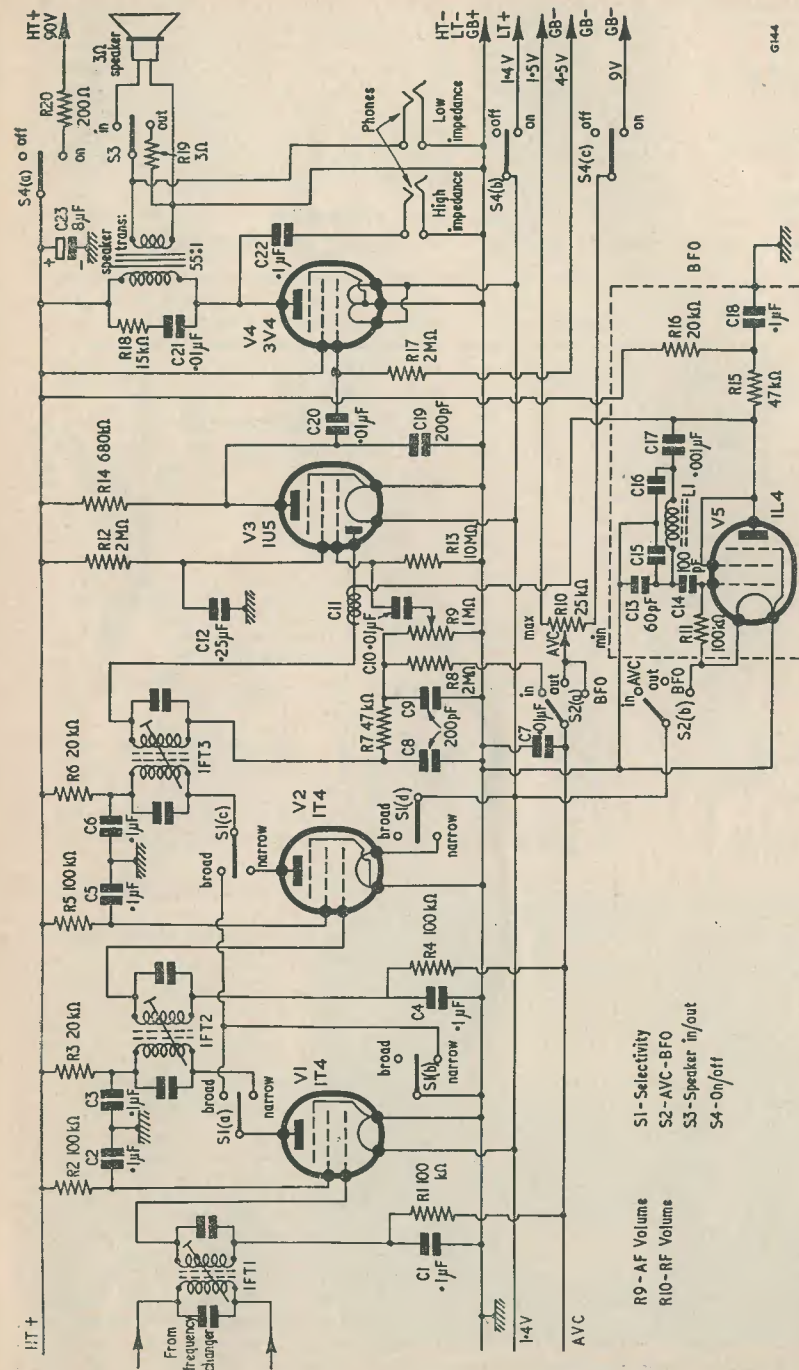


Fig. 1. The i.f. and a.f. stages of a battery communications receiver. Where condenser values are not shown, they are discussed in the text. C11 is a "twisted pair"

tive coupling exist between the two sections S1(a) and S1(c), V2 may go into oscillation when switched in. The best method of preventing such coupling consists of screening the sections S1(a) and S1(c) from each other. When the i.f. stage is switched in for the "narrow" bandwidth condition, the lead linking the two sections is earthed by S1(b) to prevent any capacitive r.f. feedback occurring along this route. A suitable procedure for constructing the i.f. stages would consist of getting them to function

in the receiver exists in these stages, and they are consequently most prone to instability. To obviate such instability, all grid and anode leads must be kept as short as possible, and all decoupling components placed very close to the circuit they bypass. It would be preferable to provide the two i.f. amplifying valves, as well as the diode-pentode, with screening cans,

The R.F. Circuits

A typical frequency changer and r.f.

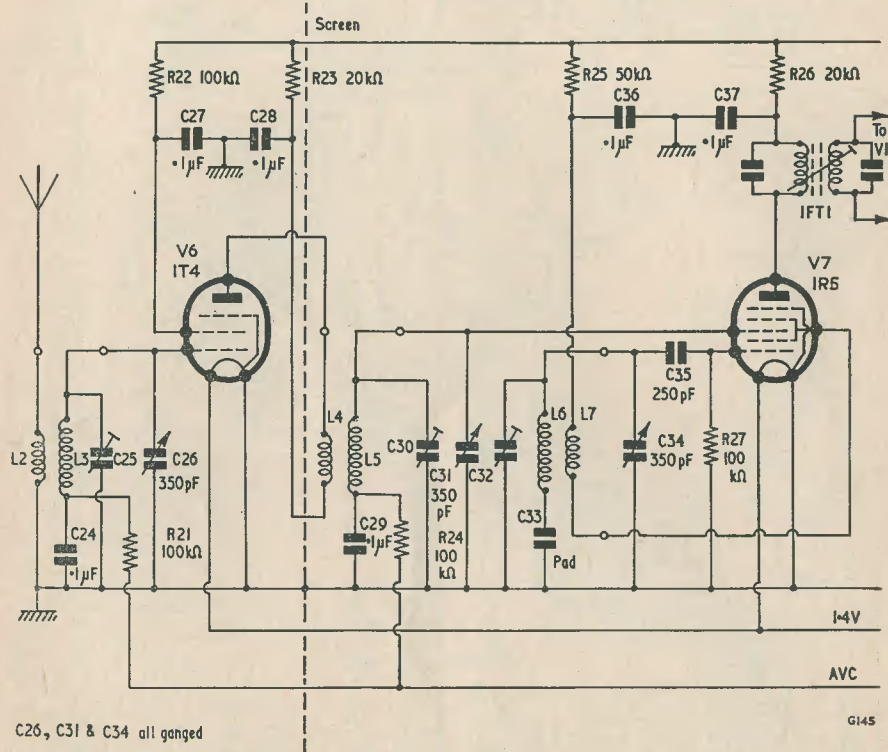


Fig. 2. The r.f. (optional) and frequency changer stages of the battery communications receiver described in the text. Range switch contacts would be inserted at the points where the circuit lines are broken by circles

satisfactorily primarily without having S1 in circuit at all. This switch can then be fitted, whereupon any instability it may introduce can be tracked down and cured more easily.

In a receiver of this nature, considerable care has to be taken with regard to the layout of the i.f. stages. This is due to the fact that the greatest degree of amplification

amplifier circuit is illustrated in Fig. 2. The r.f. amplifier is optional, of course. Should it not be desired, the aerial and earth may be connected to the coupling coil, L4; deleting all components to the left of the screen in Fig. 2. This diagram illustrates the conditions required for one range only. If range switching is employed, the switch contacts should be inserted at the points

where the circuit lines are broken by circles. Alternatively, a coil turret may be employed.

Many constructors would prefer to use a coil-pack for this part of the circuit. If this is the case, they should first of all ensure that the coil-pack chosen is intended specifically for battery valves; and they should study the manufacturer's suggestions for its incorporation into the circuit. In some instances, manufacturers may recommend, for their particular product, grid leak and condenser values which differ slightly from those shown in Fig. 2.

Once again, careful attention has to be paid to decoupling and layout; this being especially true of the frequency-changer stage. It must not be forgotten that, although the signal and oscillator grids of the frequency-changer are not tuned to the i.f. their circuits are still capable of picking up any radiation from i.f. components and wiring; resulting, thereby, in possible i.f. instability. It is necessary to emphasise this point, since the receiver described in this article has greater i.f. gain than that normally given in conventional superhets. A further important point is that the second detector stage should be kept some distance away from the r.f. and frequency-changer stages. This is not only on account of instability, but also because i.f. harmonics are liable to be generated at the second detector, and these may cause whistles with received stations.

"Postage Stamp" Rectifiers

Just as I was on the point of completing this month's contribution, a friend of mine lent me some samples of a new series of h.t.

rectifiers introduced by Westinghouse. These rectifiers carry out exactly the same functions as those of the ordinary metal rectifiers with cooling fins which we know so well. The only difference is that they are about one-sixth of the size!

To gain an idea of the dimensions of these rectifiers, one, which is intended for use in television receivers (250 volts at 300mA, half-wave rectification), is only 6 in. long, by 2 in. wide, by 3/8 in. thick. Another, which would be ideal for normal sound receivers (250 volts at 60mA, half-wave rectification), is 1 1/2 in. long, by 1 1/2 in. wide, by 3/8 in. thick. The baby of the bunch (250 volts at 20mA, half-wave rectification), has the same thickness, (3/8 in.), and is so small that it can almost be completely hidden under a postage stamp. I understand that this latter is already being used in commercial record-players employing an ECL80 in a two-stage amplifier. The three rectifiers just described are, of course, only typical types chosen from a wide range.


These little components are designated "Contact-Cooled Rectifiers," and their name gives the clue to their small size. They are intended to be mounted flat against the metal of the chassis in which they are fitted; whereupon the heat dissipated in the rectifier is conducted away by the chassis itself. The chassis also, of course, provides a large surface area for subsequent radiation and cooling by convection.


I am told that these Westinghouse rectifiers will be on sale shortly (if not already) for use by the home-constructor. I know I shall be among the first to buy one of those little 20mA jobs!

Band III Photo

The photograph, taken by Mr. John Cura of "Tele-Snaps" fame, shows the Belling-Lee test card now being radiated on the commercial t.v. band, as actually received at Wandsworth Common. Although not far from the transmitter, this is actually a very poor reception location owing to intervening hills. The aerial is a Belling-Lee type 904 6-element vagi, comprising reflector, folded dipole and four directors, and it is mounted on a chimney stack three floors up. The signal strength, measured at the aerial feeders, was 200µV. No attenuation was used, as against 14db employed for reception of the B.B.C. programmes. The contrast control was a quarter advanced from zero. The receiver was an H.M.V. 1805 TRF, with an experimental 2-valve converter.

(see also page 596)

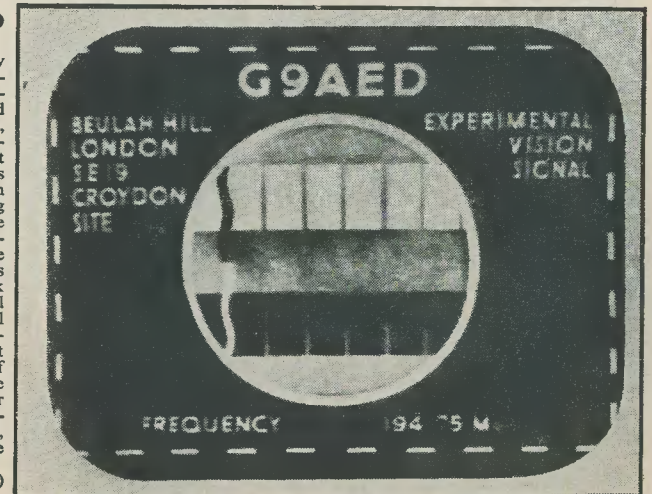

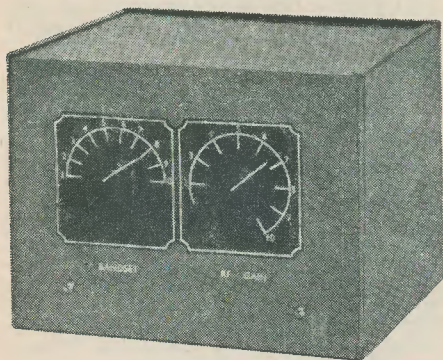

A PRE-SELECTOR for the R.C.S. BATTERY RECEIVER

by J. SINCLAIR

IN THE JULY, AUGUST AND SEPTEMBER issues (1954) of this journal, a full description of this receiver was given, together with detailed point-to-point instructions of the wiring. This was followed by the October edition when the mains power unit was discussed. Since that time, many beginner readers—according to information given to the writer—have built the complete three valve receiver and power unit. Many of these readers are now apparently desirous of adding an RF stage to this receiver and, in response to this demand, a simple design has been evolved.

The addition of an RF stage to the 3-valve receiver (0-v-2) will not only greatly increase the range but will also considerably increase the selectivity. The dampening effect of an aerial connected directly to a detector stage has several disadvantages, one of which is to make direct calibration of the dial extremely unreliable; others are that it causes interference to nearby receivers when the detector is oscillating, and reaction may become erratic. These faults are eradicated by the addition of an RF stage.

From the photographs it will be seen that the whole unit, when completed, is housed within a grey sprayed metal cabinet which matches the receiver and power unit. This cabinet, size 5½ in. × 4 in. × 4 in., is supplied complete with a removable top in order to effect easy removal, and replacement, of the coils selected to cover the range of frequencies for which the receiver was designed. The Bandset and R.F. Gain control transfers shown are those supplied with the Panel-Signs No. 1 set.

In the above-chassis view of the prototype it will be noticed that the same type valve as used throughout the receiver has again been utilised in the pre-selector. This was done in order to keep the valve types used throughout the equipment to a minimum. Thus, one spare 954 Acorn would suffice as a replacement for any stage. In addition, the fact that only one type is used tends to keep the cost at a low level, a most important point to the younger members of the radio fraternity.

All the components specified are currently available on the market. The chassis and cabinet are supplied pre-punched and drilled. All that the beginner has to do is assemble, solder and operate.

The Circuit

This is shown in Fig. 1, from which it will be seen that the aerial is fed to the coil primary winding direct. The secondary winding is tuned by the variable condenser C1; in operation, this must be kept "in step" with the receiver tuning condenser so that both units are tuned to the same frequency. R.F. Gain control is essential in order to avoid overloading the receiver on strong local transmissions. This control has been incorporated in the cathode line to earth. The fixed resistor R1, together with R2—a variable component—will, in operation, take the pre-selector from nil to full gain. C2 is the cathode bypass condenser. The screen grid (grid No. 2), is taken to the h.t.+ line via R3 and bypassed to earth via the condenser C3. The suppressor grid (grid No. 3), is connected directly to the

chassis. The anode is connected to the h.t.+ line via R4—the anode load resistor—and the r.f.c. (radio frequency choke). This latter component is necessary in order to prevent the precious r.f. signal from wasting into the h.t.+ line. This r.f. energy is fed via C4 into the receiver aerial input terminal.


The power supply of the pre-selector is taken from the same power unit that supplies the receiver. The earth, or chassis, of the unit should be connected to that of the receiver. This leaves the h.t.+ and l.t.+ to be connected to the pack. Thus, four connections are necessary in adding the pre-selector—h.t.+, l.t.+, chassis and output. Of these, the first two are connected to the power pack and the remaining connections to the receiver itself.

Next, bolt into position both the valve and the coil holders—a glance at the photographs will show the correct positions of these. Having proceeded thus far, fix both the potentiometer and the variable condenser to the front panel. This completes the assembly, and we are now ready to commence the actual wiring of the pre-selector.

Wiring Instructions—Step by Step. (Colours refer to markings on R.C.S. components).

Dealing with the under chassis wiring first, proceed as follows:—

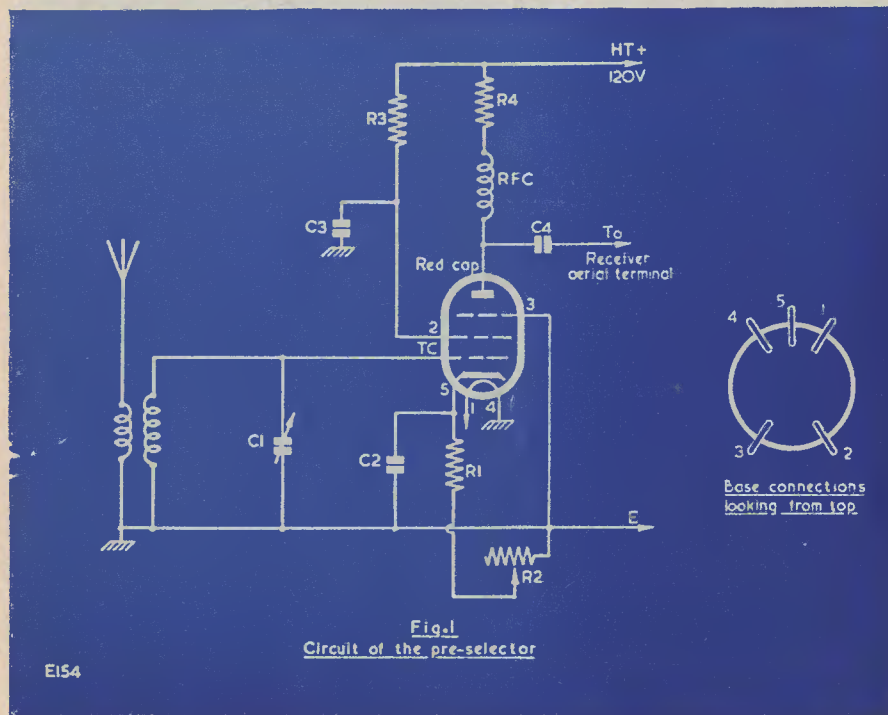- STEP No. 1. From aerial terminal to YEL-LOW on coil holder.
- „ No. 2. From earth terminal to BLUE on coil holder.
- „ No. 3. From WHITE on coil holder to RED on condenser.
- „ No. 4. To RED on 3-way tag strip



Assembly


Fix the chassis and panel together by means of the two nuts and bolts provided. At the rear of the chassis bolt into position both the aerial input and output paxolin strips. Through the central holes of these strips respectively, affix two bolts and double nut them, i.e., fix two nuts to each.

- STEP No. 5. To RED on tag strip solder length of RED connecting wire and allow this to protrude through chassis drop. (This wire is the h.t.+ lead from the power unit).
- „ No. 6. Cover free end of R3 with

systoflex, feed through chassis deck and solder to YELLOW on valveholder.

- STEP No. 7. Solder free end of R4 to one end of r.f. choke.
- „ No. 8. Solder other end of r.f. choke to one end of C4, other end of C4 to solder tag on output terminal.
- „ No. 9. To junction of r.f. choke and C4, solder short length of wire at the other end of which is soldered a valve connecting clip.
- „ No. 10. To centre tag on 3-way strip solder length of BLACK wire and push this through chassis backdrop. (This wire is the h.t., l.t., connection, i.e., taken to chassis of receiver).

- STEP No. 12. Continue with above chassis wiring as follows: From YELLOW on valveholder solder one end of C3, the other end of which is secured to GOLD on valveholder.
- „ No. 13. To GOLD on valveholder solder length of bare wire and secure other end to WHITE on valveholder. Next, centre of this bare wire should be soldered to earth tag fitted on valveholder bolt.
- „ No. 14. To WHITE on valveholder solder short length of wire, other end of which is taken to RED on potentiometer (R2).
- „ No. 15. To centre tag of potentiometer solder one end of R1. Other end of R1 to RED on valve-

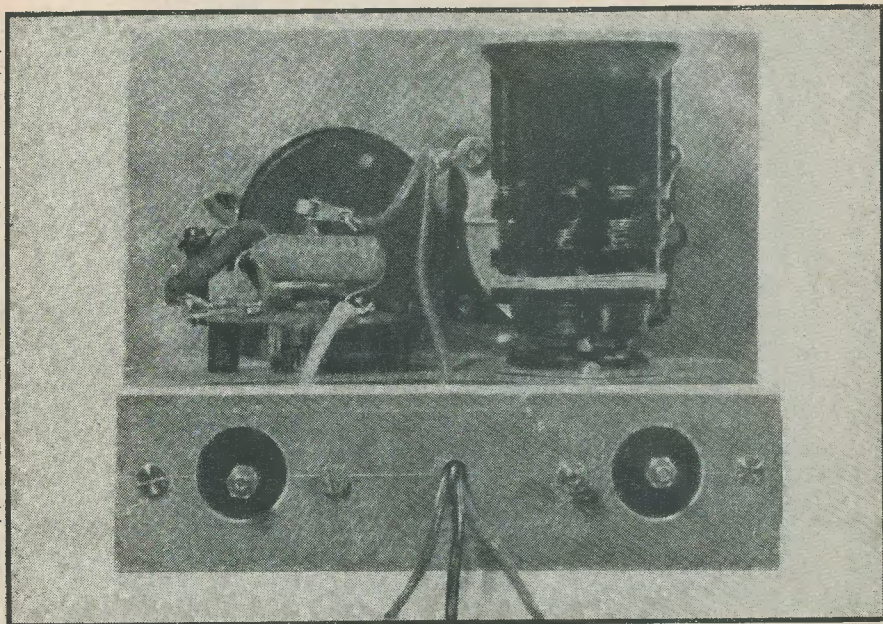

View from rear, showing components above chassis

- STEP No. 11. To YELLOW on 3-way tag strip solder length of BLUE wire and push through chassis backdrop. (This wire is the l.t.+ input lead from the power unit). Also to this YELLOW tag solder length of BLACK wire, push through chassis deck and connect to BLUE on valveholder.
- holder.
- STEP No. 16. To RED on valveholder affix one end of C2, other end of which is soldered to earth tag on valveholder.
- „ No. 17. To RED on variable condenser secure short length of wire the other end of which is soldered to a valve clip.
- „ No. 18. Secure this valve clip to the

top connection of the valve. (Note: The valve is placed into position with the RED end protruding through and under the chassis, the clear end being therefore uppermost, i.e., connected to the variable condenser. Care should be exercised in placing the valve into position. It should be pressed by the pins firmly but gently into the valveholder).

- STEP No. 19. To the RED end of the valve, connect the valve clip that is soldered to the junction of r.f. choke and C4.

This completes the wiring of the pre-selector.

Connecting the Pre-Selector

Having completed the assembly and wiring of the unit, we now proceed to connect both to the receiver and power pack. Firstly, place into position the coil selected (same coverage as that in the receiver). With the power pack switched off and disconnected from the mains, fasten into position the RED wire to the h.t.+ line and the BLUE wire to the l.t.+ line. Connect the BLACK wire to the receiver earth terminal. Disconnect the aerial from the receiver and fasten it to the pre-selector input terminal. From the pre-selector output terminal, fasten a short length of wire and connect other end of this to the receiver aerial input terminal.

The receiver earth terminal may be left connected to the external earth connection or, if preferred, it may be connected to the pre-selector earth. Later, a length of metal braided co-ax cable should be used for feeding the signal into the receiver, the outer braiding of which should be earthed at both ends to the receiver and pre-selector. Connect to the mains and switch on. The pre-selector valve will be seen to light up. Tune in a station on the receiver and bring the pre-selector into line by rotating the tuning condenser. Turning the r.f. gain control clockwise will greatly increase the signal strength. Having tested the unit, it should now be disconnected and placed within the cabinet supplied. Having done this and re-connected as previously described, fix the two Panel-Signs into position and fit two suitable knobs to the spindles of the r.f. gain control and tuning control respectively. Fixing varnish is not required with this unit, little heat being generated, therefore the gum on the Panel-Signs will suffice for fixing purposes.

The performance of this simple pre-selector is very good indeed and it may be used to great advantage with the receiver referred to earlier. It has also been used in conjunction with another receiver, a super-het having no RF stage, with surprisingly good results. As a pre-selector it may therefore be used with any such receiver; taking little current, a small amount of time to construct, and costing little.

A NEW MAGNETIC RECORDING TAPE

High Performance at Low Price

A new magnetic recording tape with an exceptional performance has been introduced by Salford Electrical Instruments Limited, at an unusually low price. Sold under the trade name of "Puretone" for 20s. a spool, it is a paper based material with an output and frequency response which compares favourably with those of plastics tapes costing almost twice as much.

The new tape is sold in lengths of 1,200ft. wound on specially designed plastic spools slotted to facilitate rapid threading, and other lengths of tape will shortly be available. The 1,200ft reels give 32 minutes playing time at 7½ inches/second or 64 minutes at 3½ inches/second. Twin track recording is also possible and this doubles the playing time; the tape can be used on all types of recorders. The highest grade oxide, with

a particle size range from 0.5-1.5 microns, is used in the magnetic coating. The base, which is superior to that of many other paper tapes, consists of a high quality super calendered Kraft paper.

The coating has an unusually high gloss finish, which, coupled with the addition of a lubricant, greatly reduces the friction and wear on the recorder heads. Intimate contact with the heads and improved high frequency response is thus ensured. On a typical recorder the response curve is substantially flat within ±1db over a range of frequencies from 50c/s to 10kc/s.

"Puretone" has the high tensile strength of about 6lb./sq. in. breaking strain with a coercive force and remanence of 220 oersteds and 700 gauss respectively. "Static," the principle disadvantage of plastics based tapes, is eliminated with the use of "Puretone."

"BELLING-LEE" BAND III TRANSMITTER

G9AED is the call sign allocated to the band III experimental transmitter for which the P.M.G. has issued a licence to "Belling-Lee." Through the helpful co-operation of the Independent Television Authority the transmitter and mast are located on part of the same piece of ground as their temporary mast and transmitter. The site is actually named on the 1" ordnance map sheet No. 170, as "Beulah Hill" with a map reference 333696.

Transmissions commenced on April 1st.

The test card is primarily intended for the investigation of ghost images and provides the following features.


(a) A wavy line in black and white, followed by white, grey and black. This line is wavy to differentiate from the vertical

adjustments to be made to the receiver.

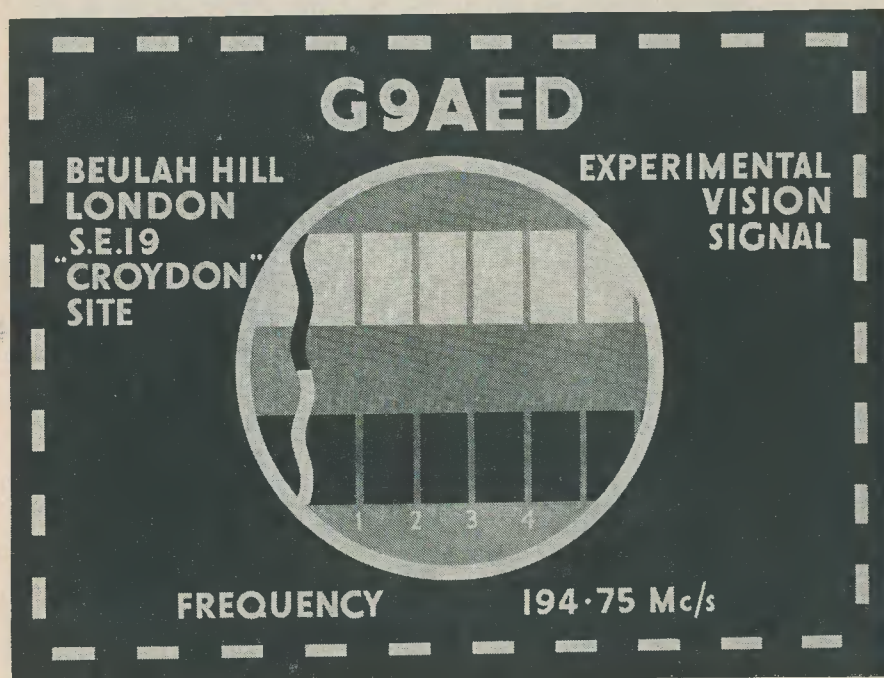(d) The black and white border to the card corresponds to the similar design on test card C and indicates the edge of the picture.

The "Belling-Lee" mast is a 75-foot self-supporting "Skytower" to which has been added a 16-foot top mast carrying the aerial system comprising four stacked bays, each of four vertical half-wave folded dipoles spaced equidistantly. Thus there are sixteen dipoles designed to give all round coverage and, it is hoped, a power gain of four.

The transmitter, which has been designed and constructed in its entirety at Enfield, has an output of 250 watts, thus the E.R.P. of the station will approximate 1 kW. The equipment is housed in a temporary wooden hut measuring 24 x 10 feet.



range marks. With ghost signals the wavy line predominates, and positive or negative ghosts can be identified.

(b) Vertical lines numbered 1, 2, 3 and 4 indicating the additional path in miles that the ghost has travelled, i.e. if the reflecting object is situated directly behind the receiving aerial, in line with the transmitter, the distance of the reflecting object is exactly half the extra distance travelled by the delayed image

(c) A circle to enable approximate linearity

It is hoped to transmit between the hours of 10 and 12 and certain unspecified periods during the afternoon, excluding Saturdays, Sundays and public holidays. It should be appreciated that the equipment is just as liable to develop a "technical hitch" as is that used by other television services, and that it has not been possible in the time to build standard-by equipment for every stage, so in the event of breakdown there will be a certain amount of unavoidable inconvenience.


INEXPENSIVE SERIES HEATER RESISTANCE

M. C. PAUL

THE DESIGN OF AC/DC EQUIPMENT, whether home or commercial, entails the provision of a line cord or wire-wound resistance; some, indeed, aspire to a condenser. Whichever of these is favoured, price and an awkward ohmic value are deciding factors, and in most cases the possibility of future replacements must be kept in view.

wide scope afforded. A stock of less than ten lamps will cover practically all requirements.

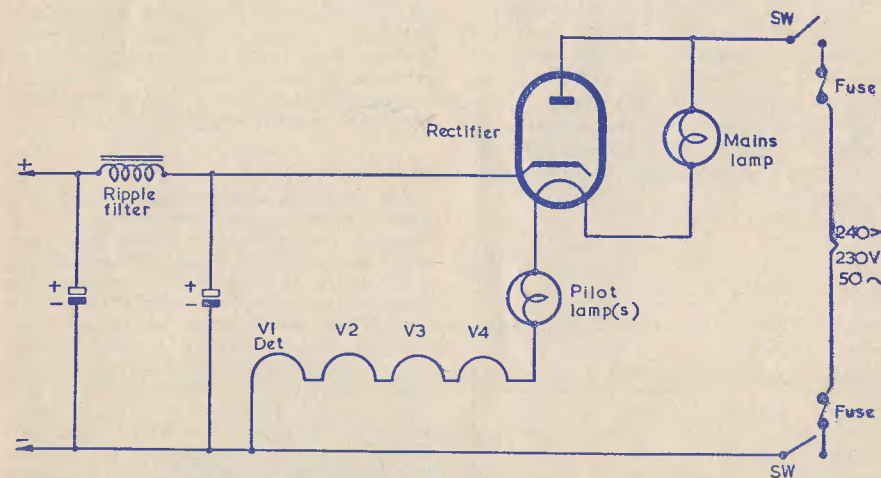In orthodox circuits series droppers have very awkward values—thanks to awkward people who patent certain valves. Lamps also have awkward values, but these and AC/DC requirements tally very well. In designing one's own equipment it is an



Showing the connection of lamp as series heater resistance in a typical AC/DC line-up


E117

The author has for some time adopted what he feels to be a simple and inexpensive answer to this problem; i.e., an AC mains lamp in series with the heater chain. In this the author does not claim novelty—who can? However, all too few enthusiasts realise the versatility of the method and the

easy matter to include such a lamp; any small adjustment in ohmic value being made by the inclusion of a suitable pilot lamp(s) of the dry battery type.

Suitable AC mains lamps and their values are listed in Table 1, together with their respective current ratings which on no

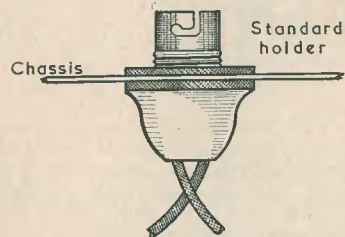account must be exceeded. For the sake of beginners in radio construction an example is given.



Suggested method of mounting lamp

E116

Required line up:—ECH33, EF39, CBL31, CY32. Total consumption of heaters:—86.6 volts at 0.2 amps. Mains supply:—240 volts. Required voltage drop:—(240-86.6) 153 volts at 0.2A. Series resistance of lamp= $V/I=765$ ohms. It will be seen from Table 1 that the nearest lamp resistance to that required is 768 (240V, 75 watt). This is close enough for all practical purposes.

TABLE 1

Normal Working Conditions			Resistance (Ω)
Volts	Amps	Watts	
230	0.43	100	529
240	0.42	100	576
250	0.40	100	625
230	0.33	75	705
240	0.31	75	768
250	0.30	75	833
230	0.36	60	882
240	0.25	60	960
250	0.24	60	1,042

Should pilot lamps be required, the next lower lamp resistance must be taken, 705Ω (230V, 75 watt). Hence the pilot lamps must together equal $(765 - 705) = 60\Omega$. Two 8 volt 0.3 amp "bulbs" will fulfil this condition. The higher rating, i.e., 0.3 amp, should be chosen for pilot lamps in 0.2 amp heater chassis as they are primarily DC lamps, and on AC at full nominal rating (RMS value), the peak filament current would exceed 0.3 amp and shorten the life of the bulb.

In compiling Table 2 the author has taken 240V as the input mains voltage to each combination. This entails only a 4% error in the event of use on a 230 volt supply or a rise to 250 volts due to bad supply regulation. Such a small error is negligible.

The valves listed are confined to a few manufacturers, but other makes may of course be similarly combined and interchanged providing their heaters are identical. Thus it is obvious that Table 2 does not purport to exhaust the possible combinations, but is rather a ready-made guide for beginners.

Most readers would object to the abundant luminosity so freely provided by this method. The author also objected to it, strongly, but in view of the other advantages decided to try black enamelling the lamp—this worked extremely well, allowing heat to be freely dissipated whilst trapping the light.

Mounting the Lamp

Two methods of mounting a lamp in a radio chassis present themselves, i.e., a standard batten holder, which is rather bulky, and the ordinary lamp holder mounted in the chassis as shown in the accompanying sketch, which is both neat and accommodating. If very small chassis are desired, then a batten holder screwed to the cabinet interior would serve, being wired from the chassis underside via a grommet in the chassis deck. This method would reduce risk of shock, should the lamp be accidentally changed whilst the equipment is energised. Such replacements should never be made under 'live' conditions, as surges would occur, with the risk of resulting damage to components.

(There is, of course, a further way of incorporating such a lamp bulb as a series heater resistance, and one in which the light is not wasted. This is to construct the cabinet so that it fulfills its normal purpose and also acts as a table lamp standard. Apart from the decorative appearance which can be obtained, there is a further advantage in that the heat dissipated by the lamp is removed from close proximity to the receiver components.—EDITOR.)

TABLE 2

	VALVE LINE-UP					PILOT LAMPS			MAINS LAMP	
						No.	Volts	Amps	Volts	Watts
0.1 Amps	X101	W101	DH101	KT101	U101	—	—	—	230	100
	W101	W101	DH101	KT101	(MR)	—	—	—	250	60
	10C1	10F9	10LD11	10P14	U404	—	—	—	250	60
0.2 Amps	ECH33	EF39	EBC33	CL33	CY32	1	8	0.3	240	75
	ECH33	EF39	CBL31	CY32	—	2	8	0.3	230	75
	EF39	EF39	CBL31	(MR)	—	2	8	0.3	250	75
	EF39	EF39	EBC33	CL33	(MR)	1	3.5	0.3	230	60
	EF36	EF36	CL33	CY32	—	—	—	—	250	75
	EF36	CBL31	(MR)	—	—	—	—	—	240	60
0.3 Amps	EF36	EF36	EL32	EL32	(MR)	1	9	0.3	250	60
	6K8	6K7	6Q7	25L6	25Z4	2	8	0.4	230	100
	6K8	6K7	6Q7	25L6	(MR)	1	8	0.4	250	100
	6K7	6K7	25L6	25Z4	—	1	8	0.4	240	100
	6K7	6K7	25L6	(MR)	—	2	8	0.4	250	100
	6J7	6J7	(50L6 50L6)	25Z4	—	1	8	0.4	230	100
	6J7	25L6	25Z4	—	—	—	—	—	250	100
6J7	6J7	25L6	25L6	(MR)	1	8	0.4	240	100	

(MR) = Metal Rectifier.

CORRECTIONS

In the MULLARD booklet *The "Universal" Large Screen A.C./D.C. Televisor and Radiogram*, there is an error in the diagram on page 17. Here, on the left, coils L2A and L2B are wrongly described. L2A, the mixer winding, is actually made of fine wire, and L2B, the oscillator coil, is of tinned copper.

In the MULLARD *5-Valve 10-Watt High Quality Amplifier* point-to-point wiring diagram given on page 280 of the December issue, there was an omission. The centre terminal of the 6.3V winding on the mains transformer should have been connected to the bus-bar. Various makes of mains transformer were specified for this amplifier, and some have no heater centre-tap. In these cases an artificial centre tap is made, by connecting two 20Ω resistors one from each side of the dial lamp to the bus-bar. The wiring diagram was taken from a chassis equipped with one of the former types of transformers, whilst the photograph was of a chassis where the artificial centre tap was employed. One of the resistors can be seen in the photograph on page 281, the other being hidden by the shadow cast by the screen. Incidentally, the dial lamp was omitted from the circuit diagram.

USING METAL RECTIFIERS

by C. NOALL

WHENEVER THE BUILDING OF RADIO apparatus for mains use is under review, the question inevitably arises: "What kind of rectifier shall I use?" If a published design is being employed, the average constructor usually works from it uncritically in regard to the power supply, at least, whilst if original work is to be carried out, he just "follows his fancy" so far as the rectifier is concerned. And that, in most cases, means sticking in a U50, or something similar.

The writer believes, however, that a little more care and forethought expended on this rectifier business would result in a great economy in both construction and maintenance costs—particularly the latter. It must be admitted further that bitter experience has left him with a strong "anti-valve" bias (no joke intended!), though he would be the last to suggest that metal rectifiers should be used on all occasions.

Let us try to get the matter in true perspective. Firstly, we will take a look at the valve rectifier—the "plus one" of the conventional superhet circuit. It is expensive—quite expensive, in fact; even the ex-WD types are not greatly below the BVA prices nowadays; moreover, it is notoriously short-lived. My own 1940 vintage domestic receiver has "eaten" six valve rectifiers in its time, though most of the other bottles are still "originals." Faultily made rectifiers, too, have a nasty habit of giving up the ghost just after the expiry of the three month guarantee period.

The most serious drawback to the valve rectifier, however, lies in the damage it can do to the rest of the circuit when it fails. Most of us have seen the havoc that can be wrought by a valve rectifier in its last dying moments—burnt-out mains transformer, ruined mains energised speaker, shorted electrolytics and—in very bad cases—damaged valves as well. In fact, many an elderly set, which might otherwise have enjoyed an active and useful old age, has had to be condemned to the scrapheap following such an accident. The fitting of an HT fuse can, of course, greatly minimise such damage; but how many of us always remember to put it in?

Where economy in current consumption is important—as in car radios, for example—the valve rectifier is at a discount, because of its heavy heater drain. It must, in fact, be regarded as a most inefficient converter of AC to DC, whilst the heat it generates can be a very great nuisance indeed, particularly in the smaller kind of set.

After all this, one may wonder whether anything favourable can be said for the valve rectifier at all. Well, of course, there can. In cases where delayed HT is a "must" it can hardly be dispensed with, whilst the absence of voltage drop is a great virtue in many cases. Moreover, the fact that it can be used in a full-wave circuit means that smaller and cheaper components may be employed in the smoothing section.

So much, then, for the valve. What of the metal rectifier? So far as initial expense is concerned, it is rather difficult to make a comparison with the valve, as the various types available may range from about half a crown to well over two pounds. However, a good 250 or 350 volt metal rectifier can be bought in the surplus market for about six to ten shillings, which compares well with the price of an average valve rectifier.

Even if the original cost proves greater than that of a valve, the investment will soon pay for itself by the elimination of replacement costs. Metal rectifiers are practically indestructible in normal use, and disasters such as often happen with valve rectifiers can hardly ever occur with them. The HT fuse should never be omitted from the power pack, however, no matter what kind of rectifier is employed.

The metal rectifier does offer a certain opposition to the flow of current, even during the conducting phase, and this manifests itself in reduced HT voltage.

The degree of voltage drop which may be expected varies somewhat with individual types of rectifier. It is, however, generally rather less than most constructors appear to believe. Here are listed a few typical MR's showing their respective input AC and output DC voltages, from which it will be seen that the voltage loss can be less than

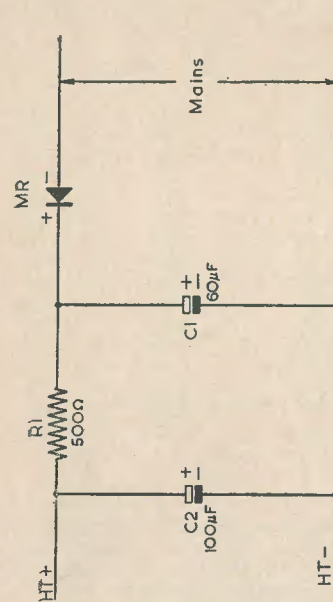


Fig. 3
Resistor-capacity smoothing

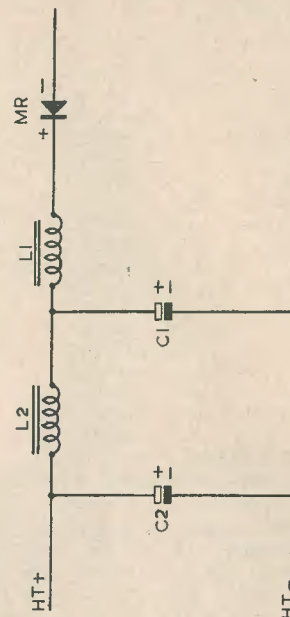


Fig. 4
Choke input filter

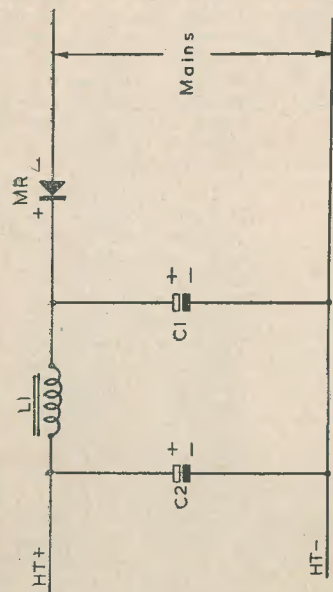


Fig. 1
Half-wave rectification

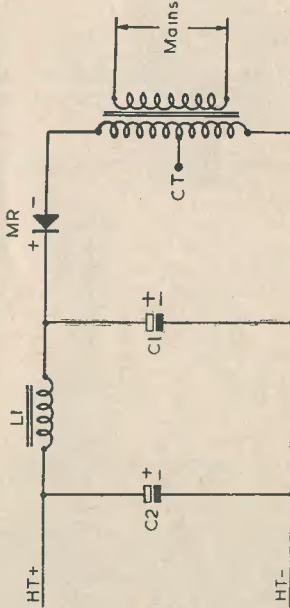


Fig. 2
HW Mains isolated power pack

5%, whilst in some instances an actual voltage gain is indicated:

In the case of commercial rectifiers in current production, no difficulty should be

Make	Type	Purpose	Input Volts RMS	Output Volts DC	mA max
Surplus	ZA-15406	HW	250	240	80
Westinghouse	HT42	VD†	270	450	100
Westinghouse	HT46	HW	250	240	120
Westinghouse	HT47	HW	250	260	60
?	—	HW	130	125	25
Brimar	RM1	HW	125	140*	60
Brimar	RM1	VD†	125	240*	60
Brimar	RM2	HW	125	135*	100
Brimar	RM2	VD†	125	270*	100
Brimar	RM3	HW	125	150*	120
Brimar	RM3	VD†	125	300*	120
Brimar	RM4	HW	250	275*	275
Brimar	RM4	FW†	210-0-210	225*	550
Brimar	RM4	VD†	250	550*	275
Brimar	RM5	HW	250	250*	300
Brimar	RM5	VD†	250	560*	300

† 2 Rectifiers.

* approximate voltage with 32μF reservoir.

The actual DC output of any MR depends on the capacitance value of its reservoir condenser (C1 in Fig. 1). For this reason, this capacitor should never have a value of less than 16μF in a half-wave circuit, whilst 32μF should be used when a fairly high load is presented to it. It should be rated at 350 volts working for direct mains use, whilst a correspondingly higher VW rating must be used following a step-up transformer. The effectiveness of the smoothing circuit may be expressed as the product of L1 multiplied by

experienced in getting all the necessary data regarding input and output voltages, ratings, etc., from the manufacturers concerned. With the cheap ex-WD rectifiers, however, the position is somewhat different.

The dealer from whom they are purchased can often provide the relevant data, whilst some published information has appeared on this subject. A most useful surplus MR which the writer has employed on numerous occasions with excellent results is the ideal for working a TRF or small superhet directly from the mains, and still appears to be in fairly plentiful supply.

The metal rectifier will be most familiar to constructors from its monotonous appearance in all kinds of AC/DC apparatus. In these circuits it is unfortunately displayed to the worst possible advantage, since its DC output is here severely limited by the low applied mains voltage—220-240V in most districts. Most modern valves require 250V or more to give of their best; and

though they will function after a fashion on 200V or even less, one can only expect an inferior performance under such conditions.

To get a suitable output voltage, the mains input should be stepped up to 250V or more by means of a transformer. This could be of the auto type (see Fig. 5) but a mains-isolated secondary winding may

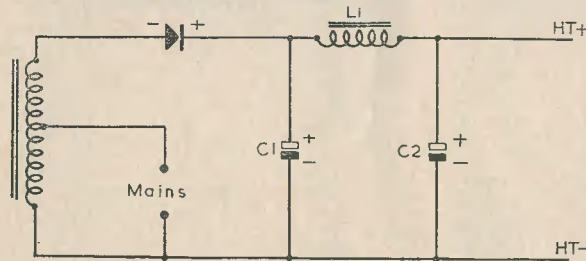


Fig. 5
Using an auto-transformer

C2. The constructor should aim at keeping the choke resistance to a reasonable minimum, however, so that, broadly speaking, it is better to increase the capacity rather than the inductance value to obtain any required degree of smoothing. (N.B.—C1 and C2 may be combined in a 16×16 or 32×32μF block).

also be employed. It is, generally speaking, more convenient to use a half-wave rather than a full-wave winding, as only one rectifier is then required. If ordering a transformer of this type, the secondary should be specified as, say, 0-300V, not 300-0-300V as in a conventional CT winding. The current rating of this transformer should be somewhat in excess of the MR's to ensure cool running.

The writer recently built such a power pack, using for the transformer a very good American job whose secondary was rated at 150-0-150V, 150mA. The centre-tap connection was ignored, and an output of

formers, plus the inevitable snags in this kind of smoothing circuit, make the proposition of using MR's in a full-wave HT pack quite an attractive one. Two MR's must be used in such an arrangement, and each must be rated to stand the full input voltage applied by the transformer secondary.

Many readers will at once be tempted to ask: "Can I substitute MR's for the valve rectifier in any existing apparatus?" To this, the guarded answer must be: "Yes, if delayed HT is unnecessary, and if you can tolerate a slightly reduced performance. If you want the same performance as before, you will have to increase the voltage rating

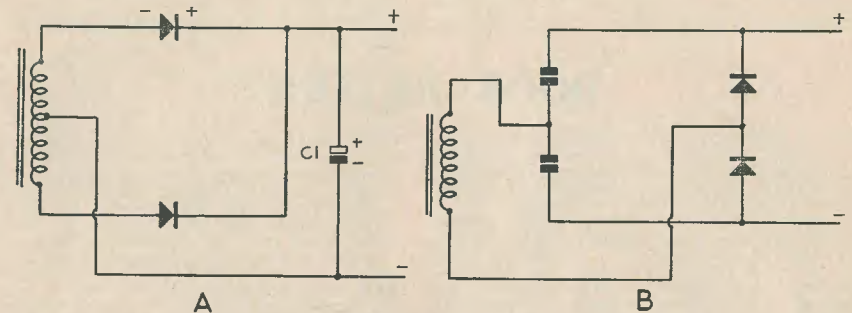


Fig. 6
Full-wave (A) & voltage doubler (B) circuits

E135

300V at 40mA was obtained quite comfortably. After dropping by the rectifier and smoothing network, this became a nice, steady 260V—ideal for driving a small mains receiver. (Fig. 2).

The HW power pack unhappily suffers from certain inherent disadvantages, which are: (1) a large-value choke is necessary; (2) high-capacity smoothing condensers must be employed; and (3) the mains transformer (if used) must have quite a large core to overcome the "saturation" effect of unidirectional pulse current. Little can be done to overcome the two last drawbacks; but it is now a common practice to eliminate the heavy, iron-cored inductance, substituting for it a high-wattage resistor of about 500-1,000 ohms. With such an arrangement, the values of the electrolytic capacitors should be still further increased if the HT voltage is to be maintained at a satisfactory level (Fig. 3). Resistor-capacity smoothing is only really effective, however, where the load is comparatively light, as in midget receivers, test gear, etc.

The difficulty of obtaining HW trans-

of your transformer secondary to compensate for any introduced voltage drop." This higher voltage might be obtained by playing around with the mains input tappings, but any heater windings on the same bobbin would simultaneously be rendered unusable. It would also be highly advisable to use higher capacity reservoir capacitors than is general with valve rectifiers.

When dealing with receivers and amplifiers which present a fairly steady HT load, the question of accurate voltage regulation is not usually of great importance. In transmitters and certain other types of apparatus where the HT load does vary within certain rather wide limits, precautions must be taken to stabilise the HT voltage, however. The simplest way of doing this is to use the choke input filter arrangement (Fig. 4). The value of L1 becomes somewhat critical here, and should be calculated (in Henrys) by dividing the load resistance by 500. (Example; with total load of 10,000 ohms, L1 is

$$\frac{10,000}{500} \text{ which equals } 20\text{H.}$$

This choke should, preferably, be of the "swinging" type.

Note.—The threaded rod which projects at each end of the normal MR is for chassis attachment; it is not connected electrically to the rectifier itself. The terminals are nearly always marked red and black. The black end goes to the mains (or secondary of the mains transformer), the red to C1 and the smoothing choke. The disc-like projections from the body of the rectifier are heat-radiators. When fully loaded the rectifier runs quite warm, but the heat should never be sufficient to scorch the paint with which it is normally protected. It sometimes happens that an MR for a particular voltage rating or type of smooth-

ing circuit is unprocurable; in this case, lower-voltage rectifiers may be used in series or in voltage-doubling arrangements to give the required voltage. At a pinch, too, a higher-voltage MR could be used in a lower-voltage circuit (i.e., a 400V MR could be fed with 300V AC), but a bigger voltage drop must be expected under such circumstances.

In this article, the term "metal rectifier" has been used indiscriminately to cover both selenium and copper oxide types. Purists may object to such usage on the grounds that selenium is not, strictly speaking, a metallic element; but we need hardly stop to argue that one here. Generally speaking, selenium is used for low-current rectifiers (up to about 100mA) and copper oxide for higher ratings.

BOOK REVIEWS

SINGLE SIDEBAND FOR THE RADIO AMATEUR. 176 pages, 250 diagrams and illustrations. Published by the American Radio Relay League. Obtainable from The Modern Book Co. (Dept. RC), 19-23 Praed Street, London, W.2. Price 14s. Postage 4d.

During the past few years the American radio journal "QST" has devoted a fair amount of space to articles on single sideband technique. Contributions which have the widest field of interest have been edited and collected in this present book. It is particularly well produced and will doubtless prove valuable to the increasing number of amateurs in this country who are attracted by this method of transmission. It follows, of course, that reception of such signals also requires some difference in receiver design. This, too, is catered for in the book, so it will be of use to those who happen to concern themselves only with reception.

The contents are divided into eight main headings; these cover a general survey of SSB technique, methods of modulation, detection, lattice filters, receivers, phasing systems, linear amplifiers and miscellaneous accessories. In each of these chapters various aspects of the particular equipment are dealt with.

The photographs and diagrams are very clear, and one is impressed by the high standard of construction depicted in the illustrations. An outstanding example is to be seen in the receiver design described in the article by Robert W. Ehrlich, W4CUU.

There is much to commend in the idea of such a digest of the literature on a specific technique, for not only does it make the information conveniently and quickly available; it may well be that certain articles are, or will be, preserved when they would otherwise be out of print. One might suggest that those who require, and will use, the considerable amount of authoritative material in this book would regard its cost as moderate. Indeed, the price is not too high even if the book is purchased solely for study.

WORLD RADIO-TELEVISION HANDBOOK, 1955. 160 pages. Published by O. Lund Johanson, Copenhagen, Denmark. English agents, Messrs. Wm. Dawson & Sons Ltd., Cannon House, Macklin Street, London, W.C.2. Price 9s. 6d.

The 9th edition of this familiar guide has been received from the English agents. Previous editions have been reviewed in these columns. The present issue follows the usual pattern and is no less informative than its predecessors.

Short wave listeners will find considerable interest in the book, for it contains a vast amount of material concerning broadcasting stations throughout the world. They would no doubt find, as the writer of this notice has found during the time the book was in his hands, that it can be of great help in identifying many of the

lesser-known stations, and even enable one to look out for stations that otherwise would have been passed over.

GUIDE TO MODERN VALVE BASES, by B. B. Babani, and **ELECTRONIC MULTIMETER CONSTRUCTION FOR THE HOME CONSTRUCTOR.** Price 2s. 6d. each. Published by Bernard's (Publishers) Ltd., The Grampians, Western Gate, London, W.6. Obtainable from Kendall & Mousley Ltd., Technical Book Dept., 18 Melville Road, Edgbaston, Birmingham 16.

These two publications have been received from Kendall & Mousley Ltd. for review. They are broad-sheets, in stiff covers, which open out to approximately 28in x 19in.

The guide to valve bases is very suitable for affixing to a wall for quick and easy reference. It deals with B7G miniature and B9A noval base valves, 201 base diagrams appearing in the centre of the sheet. On each side of this panel some 700 valve types are listed with a reference to their appropriate base diagram.

The broadsheet dealing with electronic multimeters is printed on both sides and provides full details (i.e. technical data, circuit and wiring diagrams, parts lists, chassis and panel dimensional drawings) for constructing a mains-operated and/or a battery-operated instrument.

Suitable metal cases, and specially calibrated 100 μ A Pullin meters, can be supplied by Kendall & Mousley Ltd.

The battery version will measure resistance up to 1.0M Ω in three ranges, insulation between the limits 100k Ω -1,000M Ω in three ranges, and voltages 0-1, 0-10, 0-100 with an input impedance of 1.5M Ω . There is a "volts x 10" range to enable measurements up to 1,000V to be made, the input impedance then being 15M Ω .

Similar resistance and insulation ranges are provided in the mains-operated version, but with this model two more basic voltage ranges are available. The ranges are thus 0-1, 0-3, 0-10, 0-30, 0-100 with an input impedance of 1.0M Ω , the "volts x 10" facility then permitting readings up to 1,000V with an input impedance of 10M Ω .

These two valve voltmeters are of simple basic design which will not cause difficulty to the most "amateur" of constructors to make or get going, for provided that the specified components are used, neither instrument would need initial calibration. However, the limitations of the instruments' utility should be realised, for neither of them has provision for A.C. or R.F. measurements. Nevertheless, for their designed purpose, the cost would probably be less than a comparable volt-ohm meter of the normal moving coil type.

W. E. THOMPSON

THE RADIO CONSTRUCTOR

COMBINED RESISTANCE BRIDGE AND CIRCUIT ANALYSER

by J. CHANDLER

WITH A HOME BUILT TEST-METER IT IS often found that the self-contained logarithmic range is insufficiently discriminating when measuring fairly high resistance, so that when doing a job which requires reasonable accuracy, away from home, a resistance bridge is required and another piece of apparatus must be carried.

It was with this fault in mind that I devised a simple circuit which with little extra cost would give a much more accurate indication of resistance.

The instrument may be conveniently divided into two separate circuits:

1. A.C./D.C. Voltage and Current Analyser.
2. Linear Resistance Bridge.

Little extra expense is incurred; as can be seen from the circuit diagram, only 4 extra resistors, 2 potentiometers and a battery are required.

Circuit Analyser

The circuit analyser follows the conventional pattern. It incorporates voltage measuring ranges of 5, 20, 50, 100, 250, 500 and 1,000 volts, both a.c. and d.c., and current ranges of 1mA, 10mA, 100mA, and 1 amp. on d.c. The ranges chosen are calculated to give a needle deflection on any voltage range of at least one quarter full scale deflection.

The use of one set of resistors for both a.c. and d.c. ranges (i.e., R5-R11) naturally results in a discrepancy in the a.c. reading, if the d.c. range is regarded as the basic, but this can be overcome in one of two ways:

- (1) By putting an additional scale on the meter,
- (2) By placing a chart inside the lid of the meter box showing reading corrections.

Resistance Bridge Circuit

This is a conventional Wheatstone Bridge circuit which is switched in and out by means of S2b and S2c.

R4 is a fixed 1% tolerance resistor which with R1, R2, and R3 (also 1% tolerance)

gives a multiplicative factor of 1, 10, 100 respectively. VR2 is a wire-wound linear potentiometer which must be calibrated against some standard to the following formula:—

$$\frac{R3}{R4} = \frac{VR2}{\text{Standard}}$$

$$VR2 = \frac{R3 \times \text{Standard}}{R4}$$

By using one or two standard resistors (which if not owned can usually be borrowed from a fellow constructor), VR2 can be calibrated sufficiently accurately for most purposes.

Better tolerance resistors are, of course, available for use in the ratio arms, but this was considered unnecessary as the meter accuracy is, more often than not, no better than 1%, and thus no useful purpose would be served by using really high grade resistors unless a sub-standard meter were used.

VR1 is merely a battery limiting resistor, and its value must be determined by the voltage of the bridge energising battery. For a 1.5V battery and a 1mA meter, a 2.5k potentiometer should be adequate.

Switching

The rectifier switching is self-explanatory, being achieved by a 4-way 2-position switch.

The range selection switch is of the eleven-way single-pole type with four wafers. The wafers are as follows:

- | | |
|-----|-------------------------|
| S2a | Voltage range selector |
| S2b | Bridge cut out |
| S2c | Bridge cut out |
| S2d | Current range selector. |

The wafers are connected so that when the bridge is in use (i.e., S2b and S2c are closed) S2a and S2d have no connection. This is so that the voltage resistors and current shunts do not affect the bridge.

It will be seen that connected directly to the positive Voltage/Current terminal is a single-pole cross-over switch. This is used to connect the terminals to either the voltage

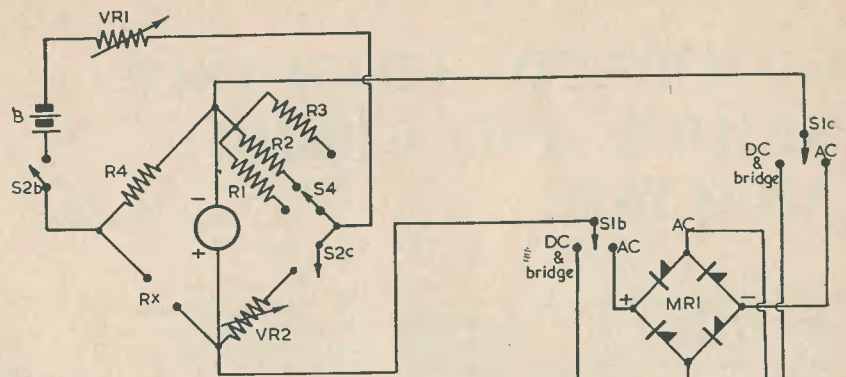


Fig.1
Circuit diagram

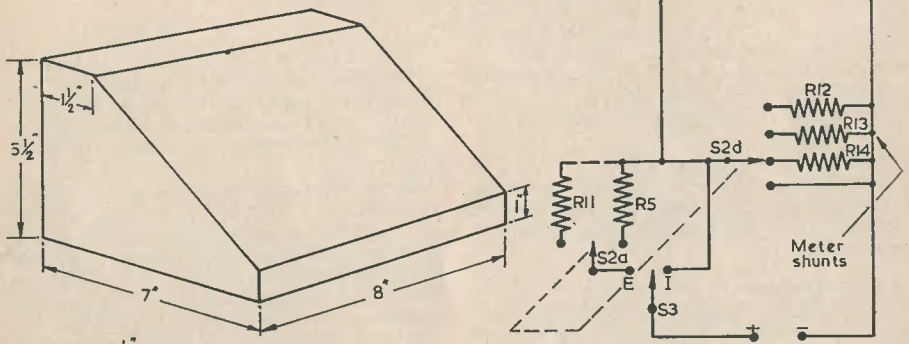


Fig.2
Case design

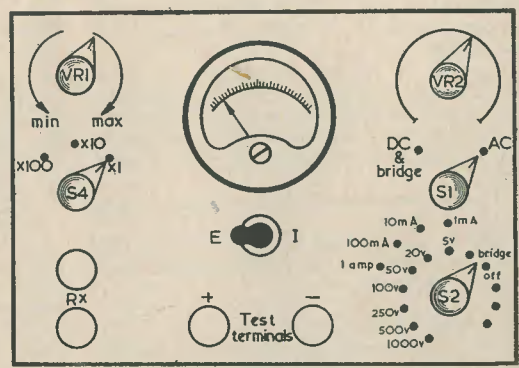


Fig.3
Panel layout

or current switch wafer, as can more easily be seen from the circuit diagram.

Components

A 1mA meter movement of internal resistance 100Ω was used in the original circuit, for which components are given below together with those for a 5mA movement. It is not advisable to use a 5mA movement except in cases of extreme necessity, since the load placed on the source being measured is rather large and may lead to erroneous readings. The more sensitive the meter, the more accurate are the readings obtained, as the resistance of the meter circuit is much higher and the current drain is much less.

Construction of Meter Case

The meter case was made of aluminium to the dimensions given in the diagram. The object of making it to such dimensions was in order to carry it in an ex-W.D. transit case 10D/11780; these are, however, in short supply and some constructors who have other cases may wish to alter the sizes given.

The use of the sloping panel is a great advantage since it eliminates reading the meter from awkward angles.

The construction of the end pieces, is, with the aid of the diagram, self explanatory. Flat plates of metal are bolted to flanges

COMPONENT LIST

Component	Function	1mA	5mA
R1	.. Bridge Ratio Multiplier	(100 ohms)	
R2	.. Bridge Ratio Multiplier	100Ω 1%	100Ω 1%
R3	.. Bridge Ratio Multiplier	1,000Ω 1%	1,000Ω 1%
R4	.. Bridge Ratio Multiplier	10kΩ 1%	10kΩ 1%
R5	.. Voltage Dropper 5V	100Ω 1%	100Ω 1%
R6	.. Voltage Dropper 20V	5kΩ 1%	1kΩ 1%
R7	.. Voltage Dropper 50V	20kΩ 1%	4kΩ 1%
R8	.. Voltage Dropper 100V	50kΩ 1%	10kΩ 1%
R9	.. Voltage Dropper 250V	100kΩ 1%	20kΩ 1%
R10	.. Voltage Dropper 500V	250kΩ 1%	50kΩ 1%
R11	.. Voltage Dropper 1,000V	500kΩ 1%	100kΩ 1%
R12	.. Current shunt 10mA	1MΩ 1%	200kΩ 1%
R13	.. Current shunt 100mA	11Ω	See
R14	.. Current shunt 1 Amp	1.01Ω	Calculation
VR1	.. Bridge Battery Limiter	0.1Ω	Below
VR2	.. Bridge Ratio pot'meter	To suit battery	To suit battery
MR1	.. Meter Rectifier	1.5kΩ for 1.5V	250Ω for 1.5V
Sw1	.. Rectifier Switch	1kΩ w/w 1%	1kΩ w/w 1%
Sw2	.. Range Selector Switch	This should allow for any excess of current and should be capable of handling 2-3 times the basic max. meter current for f.s.d.	
Sw3	.. Voltage/Current Selector	4-way 2-position 1-pole	
Sw4	.. Bridge Multiplier Switch	8-position, single-pole (4 wafers)	
Miscellaneous	—2 Terminals, 6 knobs, 2 crocodile clips, wire, etc.	Cross-over switch	

Calculation of Current Shunt

Let Rs be shunt resistance
 Rm be internal meter resistance
 N be current multiplying factor.
 Then $R_s = \frac{R_m}{N-1}$

e.g.:
 A meter of f.s.d. 1mA having an internal resistance of 100Ω is required to read up to 10mA. What is the shunt resistance?
 $R_m = 100\Omega$ $N = 10$
 $R_s = \frac{100}{10-1} = \frac{100}{9} = 11.1\Omega$

A, B, C and D, whilst on flange E the meter panel is fitted.

If G.K.N. anchor nuts are rivetted to the underside of flange E in line with the bolt holes, the meter panel can be fitted and removed at will quite simply.


Panel Layout

Most of the controls in constant use are placed on the righthand side of the panel to prevent obscuring the meter with the hand when changing range, although the disposition of the components is in no way critical.

THE "FULL-TONE"

8 Watt

AMPLIFIER

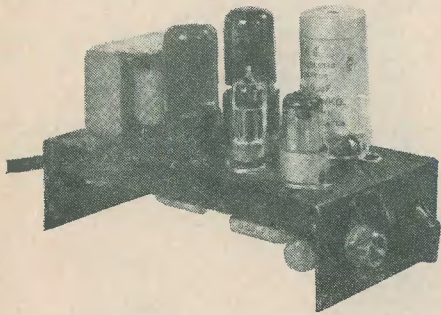

PART 1.

by M. HARVEY

Another "Radio Constructor" Design For The Beginner

FOLLOWING THE SUCCESS OF THE "EASI-BUILD" Receiver, (published in the September, October and November, 1954, issues of *The Radio Constructor*), it appears evident that there is a considerable demand from readers for articles describing simple but serviceable items of radio equipment which can be constructed at home with the very minimum of tools and test gear. As readers may remember, the "EASI-BUILD" was a t.r.f. receiver which required no trimming adjustments at all after it had been completed. As soon as the last connection had been made, the set was ready to work.

The "Full-Tone" Amplifier

The "Full-Tone" Amplifier, described in this and the succeeding issue, is in the same category. This is a simple general-purpose amplifier capable of offering a high level of fidelity, and designed especially for ease of construction. No "trick" circuits are employed and, so long as the layout given in the instructions is followed, it should work correctly immediately it has been completed. Although a conventional test-meter is of use during the construction of the amplifier (it being employed mainly to test for h.t. shorts, etc., before the power supply is connected up and switched on), such a meter is by no means essential. No other test gear at all is required.

A small amount of negative feedback is employed, this feeding back directly from the output transformer secondary to the cathode circuit of the input stage. This small amount of feedback is very useful, insofar as it flattens the response curve quite appreciably without being so large as to cause any instability when used in combination with the condenser-coupled stages which are, for simplicity, employed in the amplifier. The negative feedback has the secondary advantage of reducing any hum which may be caused by an insufficiently smoothed h.t. line from the power pack. Because of the feedback loop it is necessary to make temporary connections only between the output anodes and the speaker transformer tags during the period of construction. When the amplifier is completed these connections may have to be reversed to ensure that the feedback given is, indeed, negative and not positive. The procedure needed to check this point is extremely simple and takes only a few moments to carry out. This is the only process which is required that could be conceivably described as "setting-up".

Performance

The "Full-Tone" amplifier consists of a high-gain pentode feeding into a triode phase-splitter (actually a double-diode-triode with the diode anodes strapped to the cathode)

and thence into the output stage. The latter comprises two 6V6GT's in Class A push-pull. (The phase-splitter does not, of course, provide any amplification). The two 6V6GT's are connected to a speaker transformer which is wound to provide two output impedances. One of these is at 3Ω, the other at 15Ω. The negative feedback connection is taken from the 15Ω tapping.

The power output of the amplifier depends, to a large extent, upon the h.t. voltage applied to it. This voltage may lie anywhere between 180 and 275 volts. At the lower voltage, the power output is approximately 4 watts. At 275 volts it is in excess of 8 watts.

whose quality of reproduction is well above the sort of thing one has grown used to these days, even from the better class of radiogram. The gain level is such that it will provide more than adequate volume if connected directly after the detector of an a.m. tuner, or the discriminator of an f.m. tuner. Tone control circuits are not included in the amplifier itself as it is intended that, if needed, such circuits be employed in a separate unit designed to suit the type of equipment feeding into the amplifier.

Components

Most readers who wrote to the author concerning the "Easi-Build" receiver stated

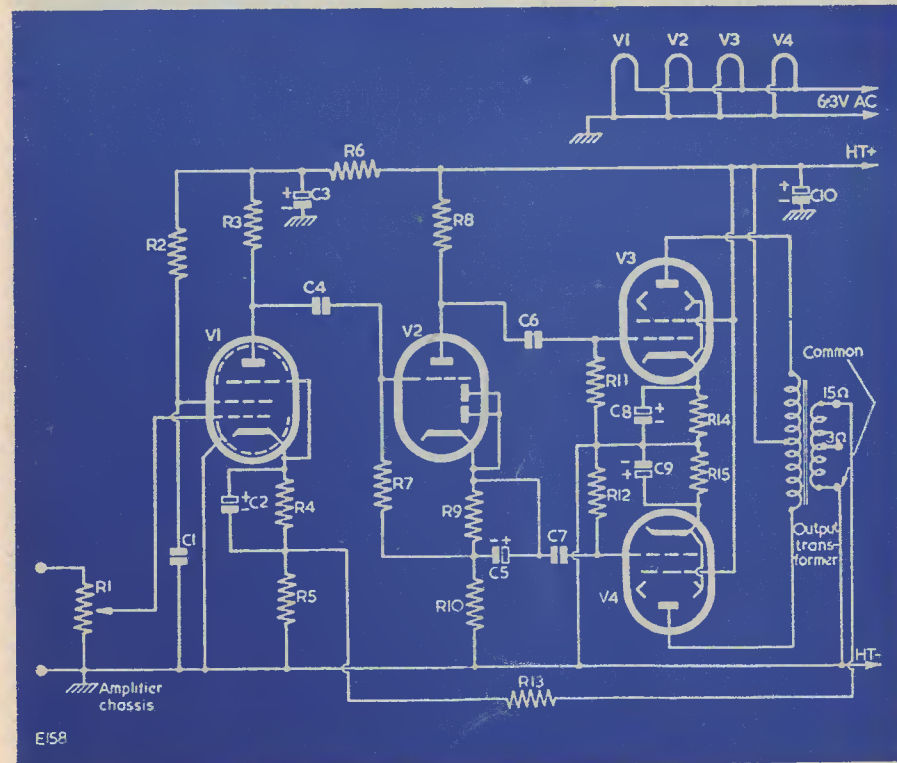


Fig. 1. Full circuit of the "Full-Tone" Amplifier

The "Full-Tone" is not intended to be considered as a "high-fidelity" amplifier (using the term in its un-debased sense as applied, to say, the Williamson amplifier) because, quite simply, it is not in the price class of such an amplifier. Nevertheless it provides excellent fidelity, giving an output

that they appreciated the fact that manufacturers' reference numbers were given for the components. One correspondent, however, was critical of this procedure. His argument was that one could not walk into a "popular" radio component shop and buy all the components specified for the design straight

off the shelf. He complained especially that, in his own particular shop, the essential coils and transformers were not available, and that he had to use alternatives. This was rather a pity, because both coils and transformers for the "Easi-Build" were, and still are, available direct from the manufacturers concerned by mail-order, as well as through retail sources. Indeed, the two firms supplying these components quoted mail-order prices, in their advertisements, in the same issues of *The Radio Constructor* as were devoted to the "Easi-Build!"

available both through retail sources or direct from the manufacturer by mail-order. Whilst on the subject of components, a further item of interest is given by the fact that a Pye-type co-axial socket is recommended for the input connections. A socket of this type is excellent in this position since it allows the input lead to be fully screened all the way to the amplifier chassis. Pye plugs and sockets will be readily available from most stockists.

It may have been noted, also, that a plain valveholder is specified for V1 whereas a

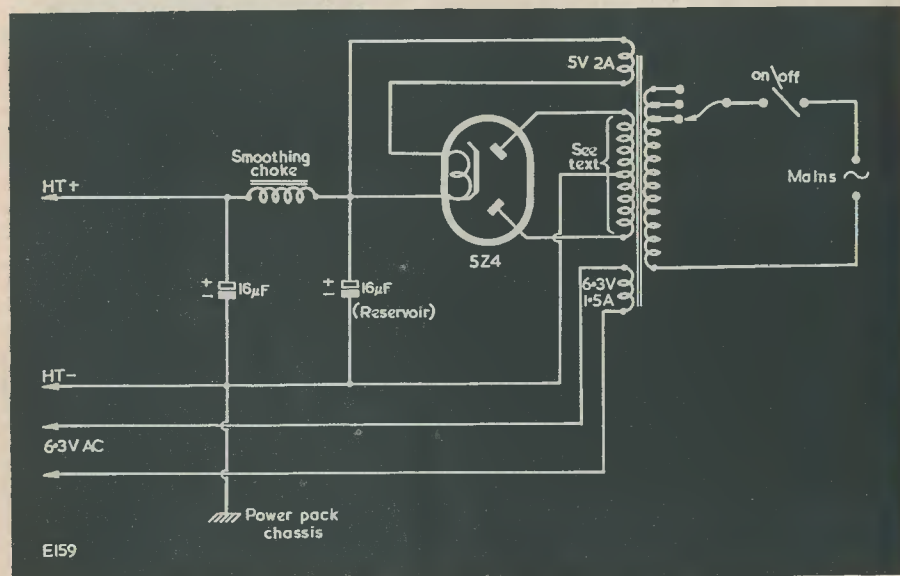


Fig. 2. A suitable power-pack for the amplifier. The smoothing choke may have an inductance of 8H or more, and should be capable of passing a steady current of 110mA. The mains transformer is discussed in the text

Where applicable, component specifications by manufacturer's name and reference number have, again, been given for the "Full-Tone." As with the "Easi-Build," constructors may use alternatives if they wish, but this course will not help to guarantee that the alternative components may not cause trouble due to altered layout and consequent short-comings in performance. The possible use of alternatives does not apply to the output transformer, however. The employment of a component differing from that specified is, indeed, somewhat inadvisable, since the circuit has been designed around it. The writer has been assured that the output transformer will be

valveholder fitted with a skirt (to take a screening can) is shown in the photographs. The choice of a plain valveholder is quite in order, since the valve types employed are fitted with their own internal screens.

A further point is given by the fact that an output socket for the speaker terminals is not specified, since it is intended that the speaker connection be taken direct from the output transformer tags themselves. However, should the constructor feel that he would prefer to fit such a socket, plenty of room has been left available for it on the rear apron of the chassis.

Finally, readers may be interested to learn that, by the time this article appears

in print, suitable chassis will be available, already drilled and cut to size, from an advertiser in this issue.

The Circuit

The circuit of the amplifier is illustrated in Fig. 1. As may be seen, it is quite simple and straightforward.

The input a.f. voltage is applied to the volume control R1, the slider of which connects directly to the grid of V1. V1 is a high-gain pentode whose output is fed, via C4, to the phase-splitting valve, V2. V2 works in a conventional circuit, a.f. voltages of opposing phase being built up across the two equal resistors R8 and R10. These voltages are next applied, via C6 and C7, to the output valves, V3 and V4. Two separate bypassed cathode resistors are used for these valves, this method of connection being found empirically to offer slightly better results than is given by a single cathode resistor for cases when the two valves are not too accurately matched. V3 and V4 feed into the output transformer which, as was mentioned above, has secondary

tappings at impedances of 3Ω and 15Ω. A negative feedback loop connection is taken from the 15Ω tapping and applied, via the potentiometer given by R13 and R5, to the bottom of the bypassed cathode resistor of V1, thereby applying negative feedback over the whole amplifier.

It will be noted that especial care has been taken to ensure that the h.t. rail is adequately decoupled. For instance C3, which is half of a dual 16+16µF electrolytic condenser, ensures adequate decoupling for the anode and screen-grid of V1. Similarly, C10, the second half of this dual condenser, decouples the h.t. rail employed for the output valves and phase-splitter.

Incidentally, C10 is not fitted merely to improve the smoothing of any power unit which may be connected to the amplifier; it also performs the more important function of providing a low-impedance decoupling path, over short leads, between h.t.+ and chassis within the amplifier chassis itself.

The amplifier circuit does not include a power-pack. The reason for this is that it is presumed that most readers will either

Component List

Resistors (All ±20% unless otherwise stated).
R1 250kΩ, potentiometer, log law, screened, without switch

- R2 1MΩ, ¼ watt
- R3 220kΩ, ¼ watt
- R4 2.2kΩ, ¼ watt
- R5 33Ω, ¼ watt
- R6 22kΩ, ¼ watt
- R7 680kΩ, ½ or ¼ watt
- R8 100kΩ, ¼ watt ±5%
- R9 3.3kΩ, ¼ watt
- R10 100kΩ, ¼ watt ±5%
- R11 470kΩ, ½ or ¼ watt, ±10%
- R12 470kΩ, ½ or ¼ watt, ±10%
- R13 6.8kΩ, ¼ watt
- R14 250Ω, 1 watt, ±5%
- R15 250Ω, 1 watt, ±5%

(N.B.—R8 and R10 may be ±20%, matched within 5% of each other. Similarly, R11 and R12 may be ±20%, matched within 10% of each other).

Condensers

- C1 0.25µF, 350V wkg; T.C.C. Type 343
- C2 50µF, 12V wkg; T.C.C. Type CE87B (Micromite)
- C3 See C10
- C4 0.05µF, 350V wkg; T.C.C. Type 343
- C5 50µF, 12V wkg; T.C.C. Type CE87B (Micromite)
- C6, 7 0.05µF, 350V wkg; T.C.C. Type 343
- C8, 9 50µF, 25V wkg; T.C.C. Type CE88CE (Micromite)

C10+C3 16+16µF, 350V wkg; T.C.C. Type CE28L (with Clip No. S.3372).

Valves

- V1 EF86, Mullard
Z729, Osram
(Also 6BR7, Brimar, see text).
- V2 EBC90, Mullard
DH77, Osram
Or 6AT6, Brimar
- V3, V4 6V6GT, Brimar.

Valveholders

- 1 B9A, plain, McMurdo type BM9/U
- 1 B7G, plain, McMurdo type BM7/U
- 2 Int. Octal, McMurdo type B8/U.

Transformer

- 1 Push-pull output transformer. Allen Components, type OP1348*

* Anode to anode impedance 10kΩ.

Plugs, Sockets

- 1 "Pye" co-axial socket
- 1 Plug for same

Tag-Strips

- 3 5-way, centre earthed, length 1½ in. (R. Davies, Swansea)

Chassis

- Either home-constructed or obtainable from R. Davies, Swansea

Sundries

- 2 Grommets, d1 ¼ in.
- Connecting wire, sleeving, etc.
- 4-way power cable.

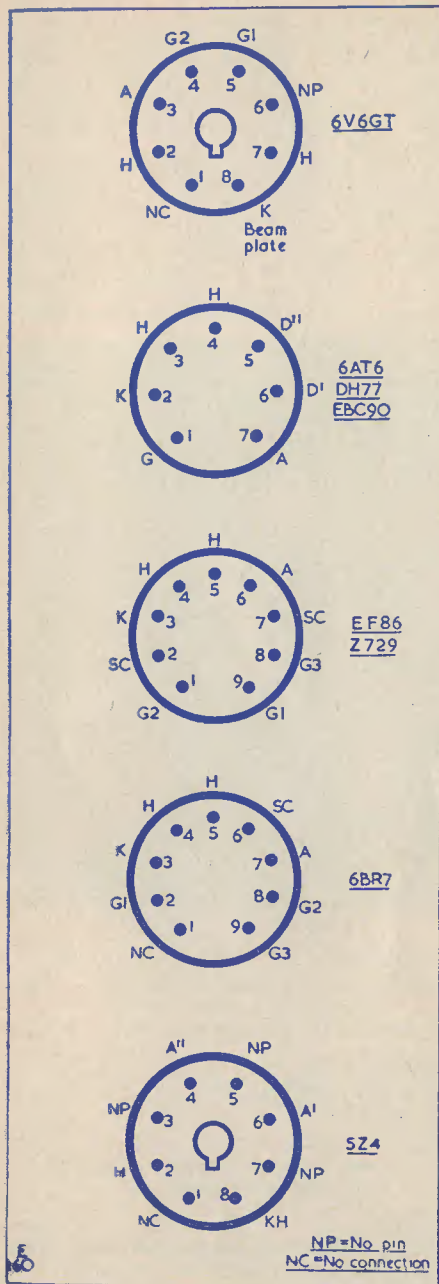


Fig. 3. Base connections of valves suitable for the "Full-Tone" Amplifier. (See text concerning the 6BR7)

have a power-pack, or power-pack components, already on hand. When it is separate from the amplifier proper, the power-pack is not at all critical so far as layout and components are concerned. It may, therefore, be built entirely to suit the constructor's own particular needs; and can employ any components which he already has or wishes particularly to obtain. The minimum output requirements from the power-pack are 6.3 volts a.c. at a current of 1.5 amps, and an h.t. supply between 180 and 275 volts. (See remarks above concerning amplifier output power). The h.t. current required at 180 volts will be a minimum of 80mA; at 200 volts, 90mA; and at voltages in excess of 225, 110mA.

A suitable power-pack circuit is shown in Fig. 2. (If desired, equivalent rectifier types may be employed in place of the 5Z4 specified in the diagram). Using the 5Z4 in the circuit of Fig. 2, a good-quality 250-0-250V transformer will supply an h.t. voltage to the amplifier in the neighbourhood of 270 volts, the increase in voltage over the transformer secondary r.m.s. value being occasioned by the 16 μ F reservoir condenser. A 200-0-200V transformer, on the other hand, will provide an h.t. voltage in the same circuit of approximately 205 only. An indirectly-heated rectifier, such as the 5Z4, is preferable to a directly-heated type since it helps to prevent excessive voltages being applied to the h.t. electrolytic condensers during the time that the amplifier valves are warming up after switching on.

Another point of importance is given by the 6.3V heater supply. One side of this supply is earthed in the amplifier chassis itself. In consequence, the heater supply must not be earthed at the power-pack chassis at all, or short-circuits, with consequent damage to the mains transformer, may result.

It is intended that the amplifier be connected to the power unit chassis by means of a flexible 4-way cable, preferably terminated in a suitable plug at the power-pack end, and whose length suits the constructor's requirements.

Valves

A few words concerning valves may not be out of place in this introductory article. As specified, the output valves, V3 and V4, are 6V6GT. There are, however, other equivalents of this valve in manufacturers' catalogues, and these may be used in place of the 6V6GT's if desired, so long as the h.t. voltage applied does not exceed the equivalent valves' maximum ratings. (If "metal" 6V6's are used, their pins No. 1 should be connected to amplifier chassis). The point-to-point wiring diagrams which

are given in the succeeding article apply only to 6V6GT valves or to their *direct* equivalents.

V2 is, as specified, a Brimar 6AT6, an Osram DH77, or a Mullard EBC90.

V1 is specified as Mullard EF86 or Osram Z729. An alternative for this valve is the Brimar 6BR7. However, the pin connections of the 6BR7 differ from those of the EF86 and Z729, with the result that this valve could not be plugged *directly* into a valve-

holder wired up for one of the other two valves. The point-to-point wiring diagrams which follow apply to the EF86 or Z729 only.

Fig. 3 gives details of pin connections for the valves mentioned.

Next Month

In next month's article, constructional details of the "Full-Tone" amplifier will be given.

Can Anyone Help?

DEAR SIR—May I request as a regular reader if anyone has a copy of the B.21.A Tuner Amplifier manual, or circuit diagram, which I could borrow or purchase.—H. Shannon, 1 Orcaes Green, Walney Island, Barrow-in-Furness.

* * *

DEAR SIR,—May I take this opportunity of using your service to find out whether any reader can help me. I have just acquired a BC348/J receiver, and would like help from anyone who has a circuit or information on this type of set. I will reimburse anyone for the expense involved in sending circuit on loan or for sale. I wish to convert for mains use.—J. E. Howard, 48 Hazledene Road, Chiswick, London, W.4.

* * *

DEAR SIR,—May I appeal through your columns for the circuit or, preferably, service sheet of the Gamages 49 model radiogram for a.c. mains. I would gladly refund costs and expenses.—S. W. J. Green, 6 Elmwood Avenue, Baldock, Herts.

* * *

DEAR SIR,—Over the past three years I have tried to obtain data for my Romac TV189 TV set, without success. Can any reader please help me?—G. Caunt, 11 Crescent Green, Kendal, Westmorland.

* * *

DEAR SIR,—May I appeal through your "Can Anyone Help?" columns for information as to where I can obtain a circuit diagram of the R.C.A. Monitor Amplifier type 8L/C4, or any details on connections to the output transformer. This amplifier uses four 6J7's, two 1622 in push-pull, and a 5U4G rectifier.—M. Halvey, 16 Fleetwood Road, Norbiton, Kingston-on-Thames, Surrey.

DEAR SIRS,—Can any reader help our school radio society with information on converting the 1191A Wavemeter to work on a.c. mains, using 6.3V valves?—C. W. Sutcliffe, Handicrafts Master, Greenford County Grammar School, Ruislip Road, Greenford, Middx.

* * *

DEAR SIR,—Would you allow me space to ask if any other reader can lend, or preferably sell, the circuit of the Indicator Unit type 184A.—J. H. Dewhurst, 100 Railway Road, Adlington, near Chorley, Lancs.

* * *

DEAR SIR,—I have a German A.E.G. set which to me is sacred, but I am in trouble with the valves, which I am told cannot be obtained in this country. Has anyone a set, new or used, please? They are Telefunken AL4, AH1 and AF7. Full cash sent.—R. Clapp, 16 Market Hall, Kingston, Hereford.

* * *

DEAR SIR,—Could any of your readers help me by supplying the circuit of the "Eddystone All-World Eight" battery communications receiver, please? J. Heinrichson, 21 High Street, Annan, Dumfriesshire.

* * *

DEAR SIR,—Can any reader supply me with the manual for the receiver type DST100 Mark II. I am willing to purchase.—W. Shaw, 31 Boris Crescent, Great Moor, Stockport, Cheshire.

* * *

DEAR SIR,—May I ask if anyone has details of the plug connections on the Canadian Wireless Set 58, Mk. 1, i.e. the battery Rx and Tx h.t. leads, which are separate. I have traced the wiring and have the set working, but would like to check. Any expense will gladly be refunded.—J. Wilkinson, "Fern-Royd," 113 Meadow Lane, Coalville, Leics.

(continued on page 625)

A PROGRESSIVE RECEIVER

PART 2

by A. S. CARPENTER

Stage 2

TO COMPLETE THE RECEIVER THE FOLLOWING additional components are required:—

- C19 50pF (mica)
- C20, 21 0.1 μ F (350V)
- C16, 17 50pF compression type trimmers
- C18 200pF
- C22 25 μ F, 12V (Bias)
- R11, 12 1M Ω , $\frac{1}{2}$ watt
- R13, 14 500k Ω , $\frac{1}{2}$ watt
- R15 1k Ω , $\frac{1}{2}$ watt

- One Osmor Coil type QA9
- One Osmor Coil type QO6
- One WX6 Metal Rectifier (V6)
- One IO Valveholder
- One 6SH7 (V7)
- One 2-pole, 2-way Yaxley type switch

Fit the wavechange switch in position, and also the IO valveholder, in the holes already drilled out during Stage 1. Next, fit the QA9 coil close to the medium wave aerial coil and the QO6 coil close to the medium wave oscillator coil.

Now rewire the frequency changer circuit of V1 until it conforms to that shown in Fig. 3. This is not as complicated as it may appear. Break the wiring at point 'B' (Fig. 2), and connect one pole of the wave change switch to the top cap of V1 and also to the aerial section of the twin gang condenser. Note that the primary windings of the two aerial coils are in series. This saves complicating the switching somewhat. The 'top' ends of the aerial coils are connected to their respective positions on the switch and the two 'bottom' ends of the secondaries are connected together to C1, R1, which are already in position. A 50pF trimmer should be fixed across the long wave aerial coil secondary.

The oscillator section can now be tackled. Break the wiring at point 'C' (Fig. 1) and connect C7 and the oscillator section of the twin gang condenser to the other pole on the wavechange switch. A 50pF trimmer (C17) can be wired across the long wave oscillator coil. Note that the 'bottom' ends of the two oscillator coils are connected to C9 (already in circuit). The 'top' ends are

connected one to each terminal of the wavechange switch, but a 200pF (C18) should be put in series with the QO6 coil. The recommended padding condenser for this coil is 150pF. C9 is therefore too large, and C18 must be put in series with it to reduce the overall capacity.

When all this has been completed, the receiver may be tested out and the long wave coils lined up. Do not alter the settings of the IFT cores. Trim with the new trimmers and pad with the cores.

Fitting the AVC

Firstly, disconnect R1 from chassis at point 'E' (Fig. 1) and fit the additional components as shown in Fig. 4. The 'bottom' ends of the aerial coil secondaries should now be connected to chassis via R1, R12, R11, in that order. Make sure that this is so, otherwise V1 will not receive its correct bias. This part of the circuit operates as follows: Part of the IF present at the anode of V2 is fed, via C19, to the small rectifier (V6), the cathode (red end) of which is held positive with respect to chassis by virtue of the voltage drop across R10. V6, therefore, is held in a non-conducting condition until the peak IF applied to its anode exceeds that of its cathode, when it conducts and a negative voltage is developed across R11. This is smoothed by R12 and C20 and fed back, through the aerial coils, to the grid of V1, so reducing its gain. If the peak IF applied to V6 is less than the delay voltage, then the AVC is inoperative, so enabling full sensitivity to be regained.

Before proceeding with the alterations it may be as well to once again try out the receiver to make sure all is well.

Incorporating an LF Stage

The circuit diagram is shown in Fig. 5. It consists of a 6SH7 triode-connected, and used as such will give a large amount of low frequency amplification. Lead 'D' (Fig. 1) is now taken to pin 4 on this valve and the output developed across R13 is conveyed, via C21, to the grid of V4, R14

being used in order that the output valve may receive its proper bias.

This is quite a straightforward stage to fit, but note that pin 8 is the anode and that it is situated between pins 1 and 7. Pin 1 is the valve metallising and pin 7 the heater, so take care. These remarks also apply to V2, of course.

Conclusion

Either or all of these modifications may be carried out irrespective of the other. The AVC circuit can be used and the LF stage omitted, or *vice versa*. Also, the long waveband may not be required in the user's locality. If, however, all the additions to Fig. 1 are made, a powerful receiver will result.

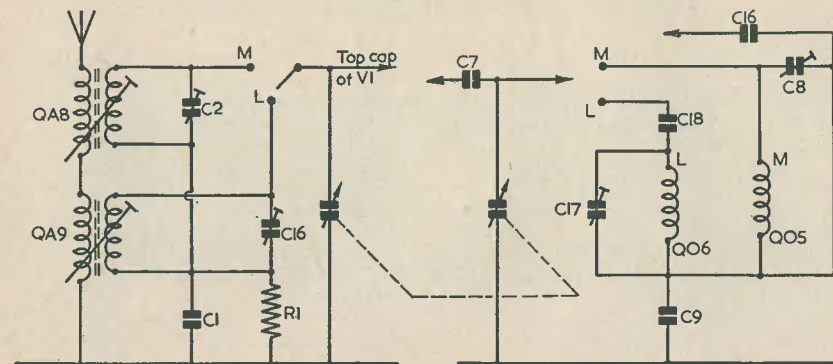


Fig. 3

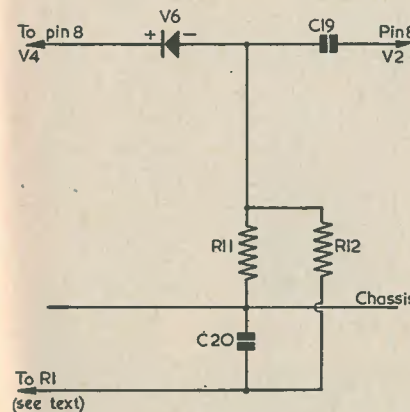


Fig. 4

E161

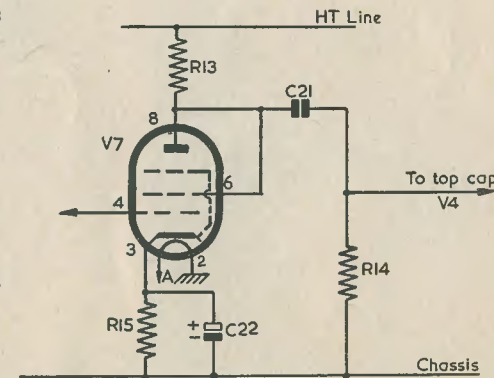


Fig. 5

Commencing next month . . .

A HIGH QUALITY ALL-WAVE TUNER

Suitable for addition to quality amplifiers

NOTES ON RADIO CONTROL

7: A Crystal Controlled Transmitter

by QUENCH COIL

HAVING WORKED OUR WAY, SO TO SPEAK, through the simpler types of transmitter, we will now consider what one might term the "ultimate" in radio control transmitter design. There is no doubt that whilst crystal control of the transmitter frequency does add complications to the circuit, the consequent freedom from worry that the transmitter is not operating within the radio control frequency band is well worth the extra effort needed in construction.

The circuit consists of two valves, the first a type 3A5, being a double triode—really two valves in one—and the second being a type 3A4.

acitor C_4 in its anode circuit being designed to tune to 27Mc/s. This 27Mc/s output is fed to the second valve via capacitor C_6 , being amplified up to a worth-while signal.

The first section of V_1 generates a number of frequencies from the 9Mc/s crystal, i.e. the fundamental as well as numerous harmonics. The second section, by reason of the tuned circuit L_2C_4 , selects the third of these harmonics, that is the one on 27Mc/s, thus providing a stable frequency for the transmitter to work on.

As both L_2C_4 and L_4C_8 are operating at the same frequency, these two tuned circuits

those associated with V_2 , being located in the other compartment.

The chassis itself should be of good quality tinplate, 7in×4in×2in deep and, as already

variable capacitors C_4 and C_8 have to be insulated from the chassis. The easiest way to arrange this is to fix a polythene or paxolin panel to one side of the chassis, either cutting

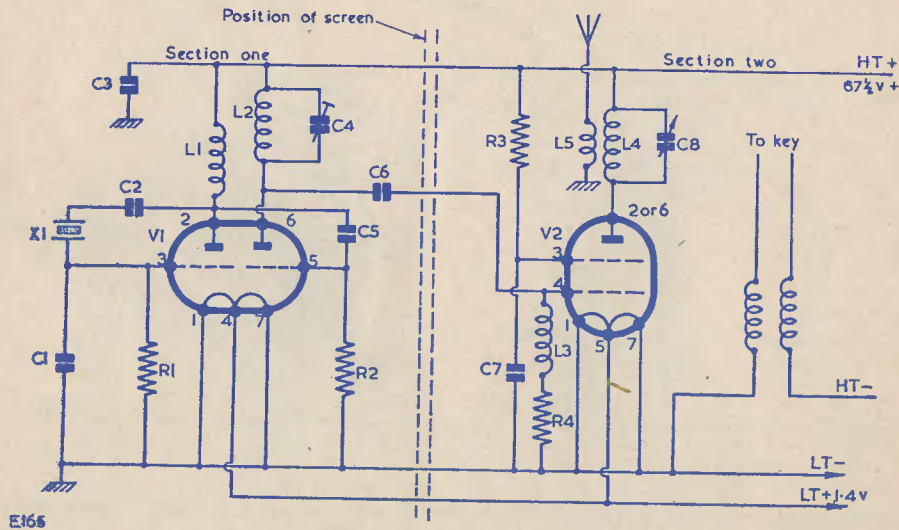


Fig. 1. Circuit of the Crystal Controlled Transmitter

The first half of the 3A5 is the crystal oscillator section, oscillating at 9Mc/s, a crystal for this frequency being connected up as at X1 in the circuit diagram. The second half of this valve is wired up as a tripler circuit, the inductance L_2 and cap-

must be carefully isolated from each other. This is done by dividing the chassis on which the unit is built into two compartments by a metal screen, the components constituting L_2C_4 being in one of these compartments, and the components forming L_4C_8 , together with

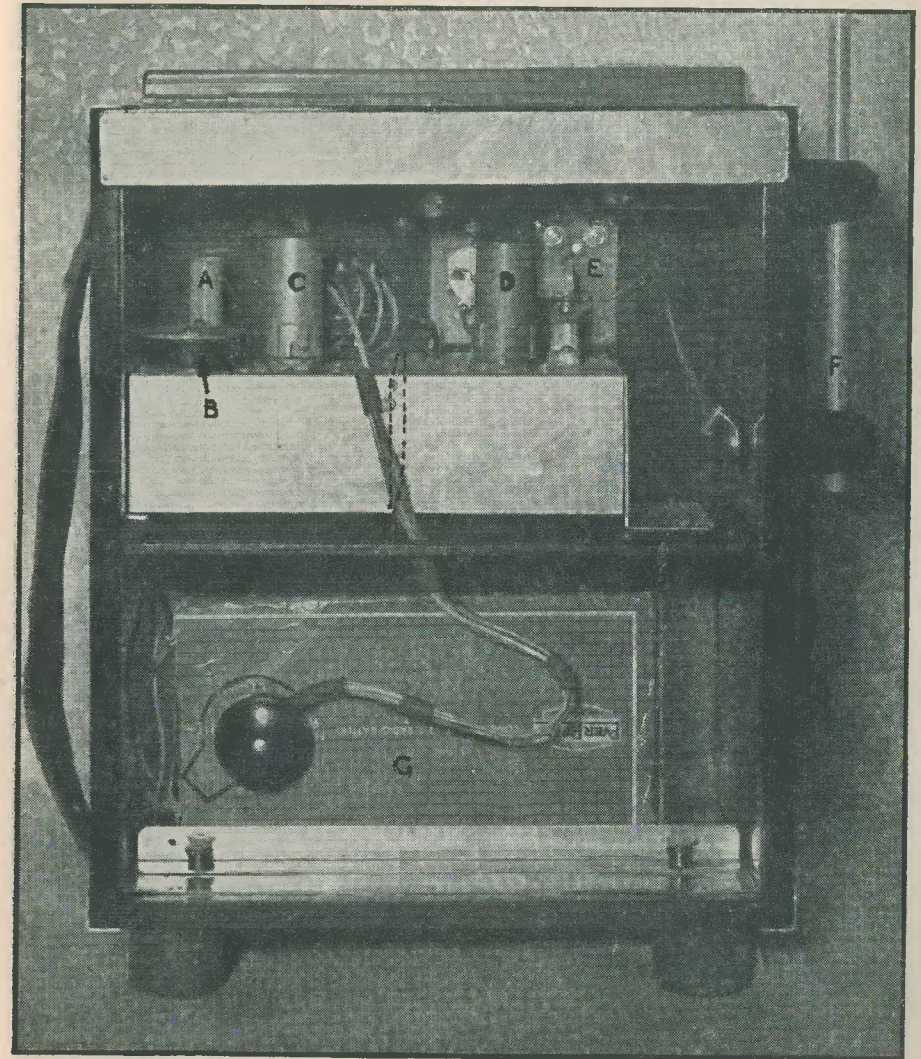


Fig. 2. Rear view of complete Transmitter. Note the clean layout. Key to Notation: A, keying chokes; B, crystal; C, 3A5 valve; D, 3A4 valve; E, built-in wavemeter; F, aerial; G, h.t.-l.t. battery. Size of chassis 7in×4in×2in.

stated, is divided by a screen across the centre, the screen being soldered in position, not bolted. The position of valves and other components is shown in Fig. 2. The two

out this side of the chassis entirely, or cutting holes in it sufficiently large to clear the capacitors. The keying chokes, valves and crystal are the only components which are

mounted on top of the chassis, everything else going beneath in one or other of the compartments. The insulated panel already referred to can be made sufficiently large to fill the front opening of the case, when the meter, etc., can also be mounted on it. Alternatively, this panel can be fixed directly to the cabinet, extension spindles being fitted to the variable capacitors.

As symmetrical a layout of components should be arranged as possible. Wire up with 22 s.w.g. tinned wire and sleeve where possible. Twist all battery leads together and keep short.

Coil Data

Coils should be constructed as already indicated in previous articles. L_2 consists of 10 turns of 16 s.w.g. tinned copper wire wound on a $\frac{3}{8}$ in diameter former, the winding extending about $1\frac{1}{2}$ in long; L_4 , 11 turns 16 s.w.g. tinned copper wire on $\frac{3}{8}$ in former, length of winding again being $1\frac{1}{2}$ in. The aerial link coil L_5 should consist of two turns of insulated wire around L_4 , one end being taken to an earth tag on the chassis, the other going to the aerial socket. Make sure that the link is wound in the same direction as the coil windings. Some experimenting may be advisable with regard to the number of turns of the link coil and its actual position on coil L_4 .

Keying Chokes

Two keying chokes should be fitted in the leads from the keying switch, as shown in the circuit diagram. They should be wound on polythene formers $\frac{1}{2}$ in diameter, $1\frac{1}{2}$ in long,

TELEVISION SOCIETY PREMIUMS

The Television Society has awarded the following Premiums, value £5 each, for outstanding papers read before the London meetings in 1954:

The "Electronic Engineering" Premium: To Dr. G. N. Patchett of Bradford Technical College, for his paper on "Problems of Interlacing."

The Mullard Premium: To Messrs. G. B. Townsend, E. Ribchester, and D. Bauer (G.E.C.) for their paper on "An Investigation of the 625-line C.C.I.R. System."

The E.M.I. Premium: To Messrs. R. J. Boddy and C. D. Gardner (E.M.I. Research Dept.) for their paper on "An Industrial Television Channel."

A special premium for the Society to Mr. G. G. Gouriet (B.B.C. Research Dept.) for his papers on "Colour Television."

with 30 s.w.g., s.c.c. wire, close wound. The two chokes should be mounted side by side on the top of the chassis.

Tuning Up

With this type of transmitter the frequency is set, as we have said, by the crystal. On first switching on, oscillation will take place in V_1 if all is well. To check that this is happening, place the loop of a lamp-loop over the end of L_1 . A lamp-loop consists of a flash lamp bulb, to the terminal points of which has been soldered a single turn of insulated wire. This will pick up enough radio frequency energy to cause the lamp filament to glow and thus indicate that a circuit is oscillating.

Having checked that the crystal is functioning properly, L_2C_4 must be tuned to 27Mc/s by means of a wavemeter as described before. Once this circuit is functioning properly the final circuit L_4C_8 can be similarly tuned, the aerial not being connected to start with. Tuning L_4C_8 will produce a drop in the h.t. current as read on the meter, and coupling up the aerial should produce an increase in this current. With full length aerial fitted, the current reading should be about 30mA, with 90 volts h.t. supply.

The Case

Details of the case can be seen from the photos illustrating this article. In the writer's case, aluminium lined wood was used, as the writer is a much better carpenter than metal worker! At the same time it is a cheaper method of construction. The actual size and type of case can, of course, be left to the individual requirements of the constructor. That shown will act as a guide to the general plan to be followed, and the sizes given will prove adequate to house the transmitter and batteries.

Component List

- C1 10pF ceramic, Erie
- C2 100pF ceramic, Erie
- C3 0.1 μ F 350V, T.C.C.
- C4 5-50pF air-spaced trimmer
- C5 50pF 350V mica
- C6 100pF 350V mica
- C7 0.01 μ F 350V T.C.C.
- C8 5-50pF air-spaced trimmer
- R1 33k Ω type 9, Erie
- R2 47k Ω type 9, Erie
- R3 2.2k Ω type 9, Erie
- R4 33k Ω type 9, Erie
- X1 9Mc/s crystal
- V1 3A5 (Mullard DCC90 direct equivalent)
- V2 3A4 (Mullard DL93 direct equivalent)
- L1 2.5mH R.F. choke
- L2 10 turns, see text
- L3 2.5mH R.F. choke
- L4 11 turns, see text
- L5 Aerial loop, 2 turns around L_4

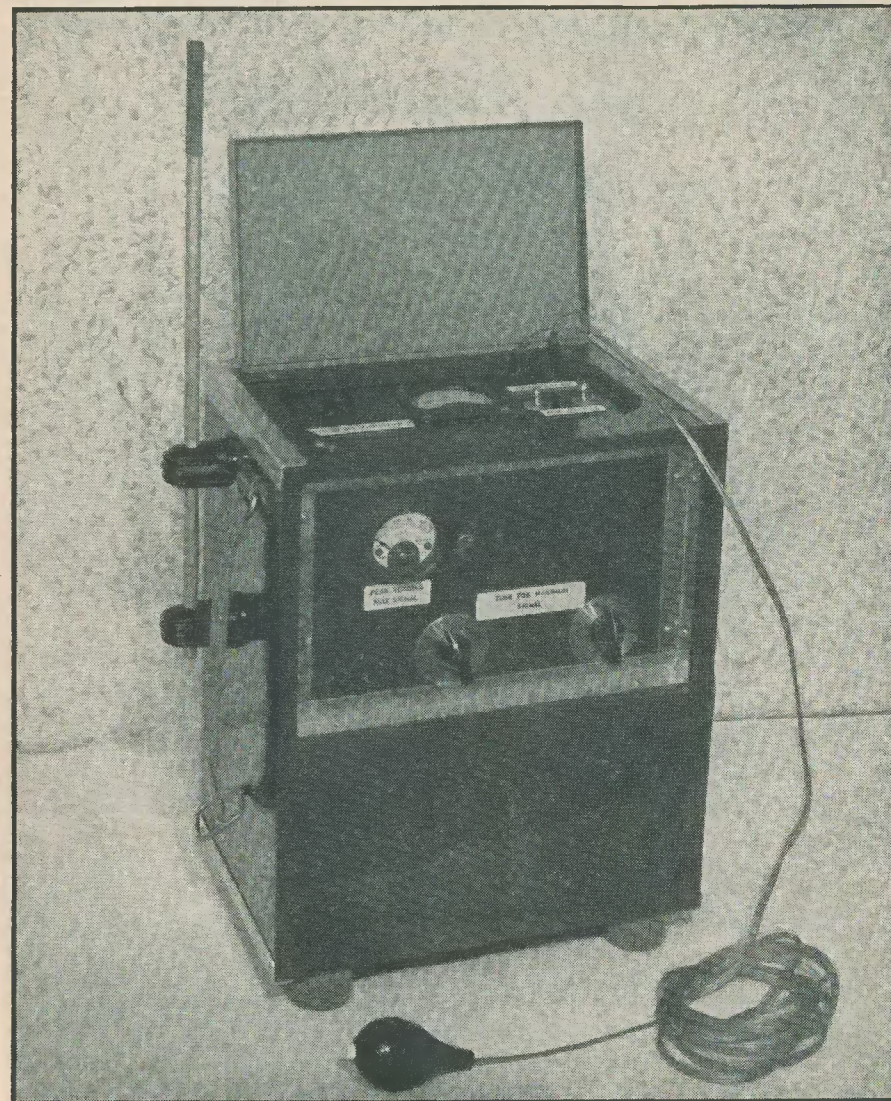


Fig. 3. Front view of Transmitter, taken before the front panel lid was fitted. The dimensions of the case are $11\frac{1}{2}$ in high, 9 $\frac{1}{2}$ in wide, and 6 $\frac{1}{2}$ in deep, and it stands on four rubber feet. The carrying handle is in two lengths fixed to the sides, and secured in the middle by a buckle. The opening in the top measures $7\frac{1}{2}$ in \times 4 $\frac{1}{2}$ in, the panel fitting in from underneath, and it is covered by a metal lid. The front opening measures 9in \times 5 $\frac{1}{2}$ in deep, also covered by a metal lid, and the panel of insulating material fits from inside. The aluminium angle is $\frac{1}{2}$ in \times $\frac{1}{2}$ in. The meter is part of the built-in wavemeter. Underneath it is the dial and knob of C_8 , and to the right those of C_4 .

Radio Miscellany

THAT NO ONE HAS YET CONSCIOUSLY written a best-seller is a truism. Authors simply write books, and one, for no predictable reason, suddenly happens to catch on and begins to sell like wildfire. Something of the same thing occurs in column writing. When I was less experienced I used to think to myself after writing on some controversial point, "I'll bet somebody has something to say about *that*." Invariably nobody raised an eyebrow. Then, perhaps in the very same column, an item which I felt was a minor point would create quite a stir.

This sort of thing once again happened to me a couple of months ago, when I wrote of the remarkable cutting power of a combined wire stripper and cutter. Actually I was relating what I thought to be a humorous little incident. Almost before the printer's ink was dry, the Editor began to receive enquiries from readers (a couple of them even telephoned) to ask who made them. The next we heard was from the makers. A reader sent to them to know if theirs were the cutters I was referring to—if so, he'd take a pair! Would I please confirm?

As a consequence I have had a caution telling me next time I write anything which is going to cause such a fuss, to be careful to mention the make so as to reduce unnecessary work.

Readers are warned that any cracks about this column containing as many "plugs" as a commercial TV programme are entirely undeserved.

P.S.—I nearly forgot to include the name of the cutters once more! They were the "Bib," manufactured by Multicore Solders Ltd.

All over the Place

In previous years I have confessed to a seasonable weakness for spring-cleaning the workshop and shack. Fortunately it doesn't recur every year. It just comes at irregular intervals—possibly after a bad winter. Thus

it came this spring, extra early. The attack came on after reading a convincing advertisement for a super spray gun. I seem to have sampled every sort of crinkle finish there is, and the fancy came over me for some of the lustrous unfinger-markable coachwork finishes one sees nowadays.

Already I am going to break the new rule. I am not divulging the name, simply because it is the only home spray gun I have ever handled, so I don't know whether it is better or worse than the average. Perhaps it is only my ignorance, but I have a notion that it is not the gun that is so important, as much as the paint.

I have for some time been the owner of a double-action footpump—one which pumps on both the upward as well as the downward stroke. Although it cuts out half the labour it costs three times as much as the ordinary sort, so it cannot be claimed as a real bargain. Except, of course, for its snob value. This can be quite a bit if you can only find the right moment to put it across your pals.

Spraying enamels cost quite a bit. The chap who wrote that advert. about the gun forgot to mention that, or about the primer surfacer. However, my first project was to spray a few lightly rubbed-down enamelled surfaces, so I was able to charge up with the real stuff and connected up the pump. A couple of beefy jabs and the gun sent out a jet like a flame thrower. Obviously the first thing one must learn is just how far to stand back. This, in turn, requires the user to gain some proficiency in the matter of markmanship.

At the moment of writing I am on my third lot of enamel; and although the family still dive for cover when the gun comes out, that is only their idea of being funny. Indeed, I shall soon be reasonably sure of getting some 25 per cent of the spray on the target area.

After reckoning the cost of the gun (without the pump) it works out to very little more than four times the expense to do a job than

to have it done professionally. Still, it is good fun and, naturally, the more you use it the cheaper the rate. Like the old lady selling the oranges who said, "It's not what you lose on each one that matters. It's the number you sell."

Thinking, too, of publishers, also recalls the old farmer who bought a disappointing book and then bitterly complained: "The chap as writ the advert. ought to writ the book." To this I would add the chap who thought up that spray gun advertisement ought to explain how much paint you want to learn to use the wretched thing. Most of us buy our experience the dear way, which is why radio sometimes unfairly gets the reputation of being an expensive hobby.

Yeoman Service

The skyline of TV aerials to be seen in and near the fringe areas makes an unsightly array at the best of times, but after the winter's rough weather they are apt to become a positive eyesore, as well as a possible source of danger should they collapse. The erection of a normal "H" aerial costs several pounds, and for every foot they are pushed nearer the clouds the cost goes up by leaps and bounds—as well as increasing the risk of having the elements askew after high winds.

CENTRE TAP

talks about

CUTTERS SPRAY GUNS NO-AERIAL TV

Many purists would like to see TV aerials done away with altogether, and the recent press reports of the disappearance of the aerials on the living quarters at the Tower of London has been eagerly seized upon as a sign that all aerials might be out of sight if only somebody "did something" about it.

True, an unsightly collection of aerials projecting at all angles from the Tower is very much out of character with the building's historical associations and with national dignity. Fortunately, the Ministry of Works were well able (at the taxpayers' expense) to arrange for an invisible master aerial and distribution amplifier. The cost, of course, was beyond what anyone could be expected to pay for, say, a private block of flats.

The work was carried out by E.M.I. and entailed the use of nearly half a mile of lead-covered cable, and a couple of roads had to be dug up. Nor was that all. The Tower is

still supplied by d.c., so a rotary converter to power the distributor amplifier had to be installed. In all, this was quite an undertaking and is, I hear, working very successfully. Naturally, *all* these difficulties would not be encountered on other sites, but "doing away" with TV aerials is not so simple (or cheap) that it is likely to become general—just yet!

Crystal Gazing

Chatting with a few friends over a pint, we discussed the elimination of outside TV aerials altogether, which subject soon led us round to arguing about the finality of design of television receivers. Any form of mechanical system, of course, we dismissed out of hand. CRT projection methods received some support, but were voted out because they will be expensive and "tricky" to bring to a standard high enough for colour viewing in bright daylight. They would also be bulkier than the ideal demanded.

Any attempt to look into the future must take into consideration not only colour, but 3-D. The complication of circuits of present-day colour TV receivers (for those who have examined them) almost makes one feel giddy. To superimpose on top of that a second picture to obtain a stereoscopic effect would

require an enormous number of valves or transistors.

We eventually decided the approach must be something simpler than that. After several pints we visualised the future TV receiver as taking the form of a specially prepared surface consisting of a mosaic of a million or so spots which, when electrically excited, will glow in three colours in their proper lineal (and colour) sequence. But, seriously, development on lines of this sort is well within the bounds of early possibility. Indeed, to anyone who has studied the crude beginnings of television (from the disc scanning of thirty years ago) it will seem less of an advance than we have made to the existing type of set.

Then, of course, we shan't need outdoor aerials at all—except in the wide-flung fringe areas—and historical buildings will be safe from disfigurement.

INDOOR TRANSMITTING

AERIALS

by O. J. RUSSELL, B.SC.(HON.) G3BHJ

HAVING CONCLUDED A PERIOD OF SOME five months of "A" operation using an indoor transmitting aerial, it is clear that a few words on this neglected subject are in order. In these days of restriction and housing shortages, there must be many potential and actual holders of a ticket who are faced with special difficulties in the realm of aerial erection. In many cases, due to living in rooms, or flats, it is impossible to consider hanging even the most modest skyhook out of the window, and the outlook may appear black. However, as in the case of unavoidable QRP operation, those who are determined to put out some signal whatever the difficulties may be agreeably surprised at the results.

We must first consider one or two points connected with the simpler aspects of indoor aerials. So much could be written on the subject, that to cover the aspects even partially would require several articles. However, the following points may be taken as "first steps" in the subject. The ideal, of course, is to get up at least a resonant length of wire, for earthing difficulties if one is in a flat or room render Marconi and similar "against-ground" aerial systems an uncertain and difficult proposition in most cases. The possibility of centre-feeding a resonant length of wire is also of some help as a discrimination against harmonics, and centre-fed systems have other advantages, not to mention the important fact that BCI troubles appear to be less frequent than with end-fed systems. This may appear to be a counsel of perfection, except upon 10 and 2 metres, where a resonant length is not impossible to obtain even in a very small room. In some rooms, however, even on 10 metres, it is not possible to put up a straight stretch of wire, and it is necessary to let the excess length hang down vertically. For 10 metres, however, a vertical length of wire allowed to hang from the window, is nearly always possible . . . except perhaps for the basement dweller who has our heartfelt sympathy!

Even such limited arrangements have their disadvantages, however. A 10 metre length of wire slung across the room is definitely not likely to meet with the approval of the average landlady, and the picture rail must be employed as a more discreet support. With the restriction of wire necessarily concealed behind the picture rails, the outlook for bands lower than 10 metres would appear hopeless; but by employing known facts about aerials, it is possible to operate on 40 metres with a resonant aerial, and on 80 and even 170 metres with loaded aerials. We must consider carefully the following points about aerials, as the writer was forced to do, before neglecting the lower frequency bands.

It is not generally realised that a 40 metre dipole of, say, 67 feet in length, centre-fed with quarter wave feeders, is actually an 80 metre half-wavelength if we include the feeder length. We have two feeder wires each of $33\frac{1}{2}$ feet, so that the overall length of the system is 134 feet, which is just a half-wave at 80 metres. The system can be imagined as derived from an 80 metre half-wave dipole, in which the centre portion has been folded in to make the feedline. Such a system will resonate overall as a half-wave at 80 metres, and will require current feed, that is a series tuned circuit at the end of the feeders, to transfer power efficiently. This point is very often overlooked and should be stressed more in antenna handbooks, for such a use of an aerial apparently at half the resonant frequency of the top is actually quite efficient. It is generally to be preferred to operating the system against ground as a Marconi for 80 metres, with the feeders tied together, again because the symmetrical centre-feeding is highly advantageous. Those who have normal 40 metre doublets with suitable feeder length, should try a series tuned aerial feeding circuit for 80 metre operation. Having used powers from $1\frac{1}{2}$ watts upwards on such a system, it is confidently recommended for normal outside aerial working.

Such a use is strangely enough often overlooked, particularly as the need for a series tuned aerial circuit is not considered, and attempts to use a parallel circuit will not succeed. On the top fundamental and harmonics, of course, such a system is exclusively voltage fed from a parallel tuned circuit. The change to a series tuned circuit for 80 operation is so simple that it is hoped those with normal aerials who are in difficulty will try it. This little considered point about aerial systems with tuned feeders has to be realised. In a tuned feeder system it is not possible to separate the feeder portion and the radiating top, as they are in fact together one resonant system. The obsession of getting a resonant top, and then adding a resonant feeder, completely overlooks the fact that the top can be any length, provided that the total length of wire in the system adds up to a resonant length. Thus the normal half-wave 40 metre aerial with its quarter-wave two-wire feed line is actually an 80

This would have a 33 foot top, say, with a 17 foot length of tuned two-wire feeder. There would be nothing to stop the top length being, say, 47 feet, and the feeder length 10 feet, or the top being reduced to, say, 25 feet, and centre-fed with 21 feet of two-wire line, as the total resonant length remains unaltered at 67 feet. To a writer of text-books on aerials, such points are of little importance, but to the amateur who has to make the best of circumstances they are of primary importance. In any case the radiation patterns are very little different from conventional dipoles, and the efficiency may actually be higher in cases where the top length is greater than a half-wavelength. The practical difference is not worth worrying about, especially in cases where such systems represent the solution to putting up a reasonable system as against an odd length of wire. In any case the fundamental resonant length is unaltered, only the amount used as the radiator is, and this flexibility is

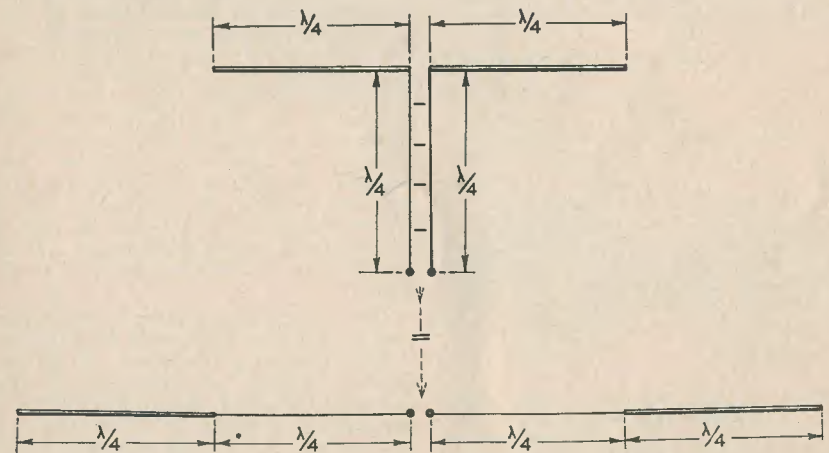


Fig. 1. The half-wave top centre-fed with quarter-wave feeders totals one full wavelength of wire, so that the whole system may be resonated with current feed at half the frequency of the top. A 40-metre doublet with quarter-wave feeders can be used in this way as an effective 80-metre radiator. Why not try it?

metre fundamental resonant system. Once this fact is grasped, we can free ourselves from the tyranny of using exactly resonant lengths of radiating top, provided that the total system is of the right resonant length. This is of considerable importance to any amateur who has restricted space, for quite obviously the simplest resonant system for 40 metre operation is actually a 20 metre half-wave fed with quarter wave feeders.

of importance in all cases where aerial difficulties are encountered.

We can now see that any amateur faced with restricted space can effect a certain degree of control over the actual radiating length of wire employed, more especially when the special case of indoor operation is considered. Assuming that we are restricted to the picture rail as the support for an aerial which must be unobtrusive, there is one

type of aerial that can form a basic type for discussion. This is the square aerial, in which a half-wave of wire is bent into a horizontal square, and can be centre-fed. Such a system can be made to fit more or less into a room. A 20 metre system of this type will just about fit an average small room, and it should be noted that the radiation efficiency is equivalent to a normal dipole. Naturally, for indoor operation, the efficiency of any aerial will be affected by proximity effects, partial shielding, etc., so that full outdoor efficiency is not to be

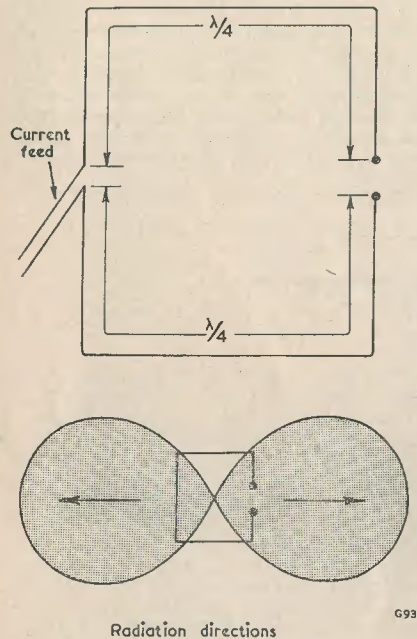


Fig. 2. The square dipole. A half wave-length of wire arranged as a horizontal square loop. It can be centre-fed as shown. Ideal for a "picture rail" indoor aerial

expected; but with reasonable care, results from a system of this sort can be very little different from a conventional outdoor antenna. Due to the closeness to the walls, some adjustment of the resonant length may be necessary, but this is relatively easy when the transmitter tuning controls and aerial circuit are, together with the aerial, all within easy reach . . . perhaps the only real advantage of an indoor system! The directivity is bi-directional along the line

joining the centre to the open ends, and closely resembles that of a normal dipole, so that the aerial can be lined up for radiation in a desired direction. However, in this connection, remember that the open end is the "hot" end, and should be kept away from waterpipes or other metallic bodies if possible.

The above system, if arranged for 20 metres, would be centre fed by a quarter-wave tuned line, and this would require voltage feed from a parallel-tuned aerial circuit, which could be link coupled to the transmitter tank. Such a system, as we have previously seen, would actually be basically resonant at 40 metres, providing we series-tuned the aerial circuit. So far so good, but due to space limitations, even this may not be fully practical. The following solution has been adopted at G3BHV/A. Starting with a resonant 66 feet of wire, 20 feet were combined into 10 feet of spaced tuned feeder. This left 46 feet of wire, which was carried round the picture rail. Instead of forming the full loop, which was impracticable, the remaining lengths were allowed to hang down from opposite walls. Actually a few odd feet were left lying on the floor at each end, although this is concealed from view. The object of leaving the vertical hanging sections is that they will form an out-of-phase pair of vertical elements which are expected to add useful radiation when operating on 10 and 20. So far operation has been restricted to forty metres, but the system should be of use from at least 80 and even 160 metres down to 10. Further details may be given in a later article on this aspect.

The above considerations were turned over mentally for a long time before placing such a system in operation. A perfectly good transmitter was lying on the floor gathering dust, and the use of the receiver was more than enough to excite a desire to return to the air, especially as hopes of a QTH where an outdoor aerial could be erected, receded further away. Something had to be done, and it was hoped to make it as effective as possible, even though the room was not at the top of the house, but only on the first floor in an average type of locality. The memories of excellent reception results on indoor aerials during the early thirties even at ground level, meant that some sort of signal should be radiated. Even a local contact or two would be preferable to an indefinite period of inactivity. The system was accordingly erected, and the feeder terminated in a series-tuned circuit link coupled to the PA, running a modest fifteen watts. The first evening produced exactly zero contacts, but after a second evening contacts resulted. Results were not too

good, however, and the system did not appear to load the PA too well. Struck by a sudden thought, the six-turn link coil around the aerial tuning coil was cut down to three turns. This made a startling difference, as the PA could be loaded up to 25 or 30 watts easily, and the aerial bulb

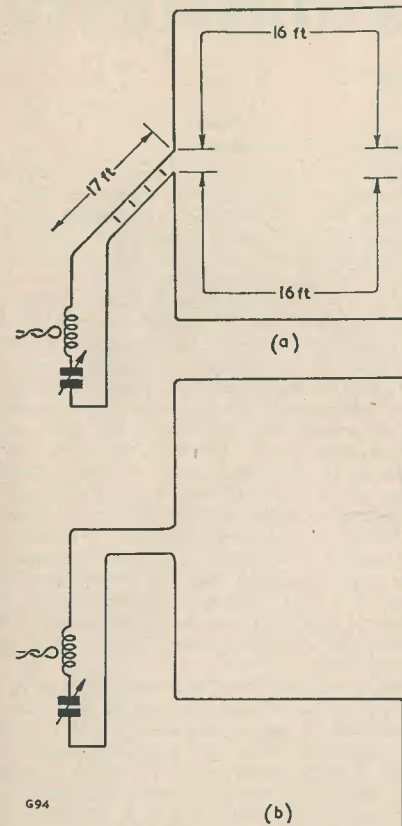


Fig. 3 (a). The smallest square aerial that will tune to 40 metres, makes up the total length to 66 feet with the feeders. The loop need not even be square.
Fig. 3 (b). The picture rail aerial made up to 66 feet with short feeders, and vertical hanging ends to give as much radiating length as possible

coupled loosely into one side of the feeders lit brilliantly as a pleasant change from its former modest orange glow. Results from then on appeared little different from those obtained a year earlier at a nearby QTH

when a full outdoor half-wave 40 metre dipole was used. Due to concentrating exclusively on 40 metre CW, instead of wandering off into the lotus land of phone ragchews, about 20 countries were worked in very few hours of operation over a period of 3 months. No BCI reports have been obtained, despite the fact that at least three other receivers are in use in the house. No phone operation has as yet been seriously contemplated.

The above results may perhaps hearten those faced with a similar situation, as the experience is that not only are contacts possible under restricted conditions, but contacts are in fact easily possible. The experiences of G4HT, who is also forced to work out of indoor aerials, have been a stimulating factor towards trying out an indoor aerial. Although the outdoor aerial is the ultimate goal, the results obtained on an indoor aerial can be very little inferior to a normal aerial system, and one has the added satisfaction of overcoming the special difficulties one has had to face.

Can Anyone Help?

(continued from page 613)

DEAR SIR,—I have recently acquired a Power Unit type 266; input 80V 1.5kc/s a.c., outputs h.t. 120V d.c., bias 3V and 9V, 1.t. 2V, smoothed and stabilised, with 5U4G valve and VS110 stabiliser, 12V 1A metal rectifier, etc. I wish to run the R1224 receiver with same, and wonder if any reader could help me re the parts to re-wire, etc., I should be most grateful for any help received.—J. L. Murray, 21 Highfield Road, Winchmore Hill, London, N.21.

* * *

DEAR SIR,—Can any reader full conversant with the B2 equipment inform me of the correct connections in the bakelite plug which connects from the B2 receiver to the power pack? This bakelite plug is in two halves, clamped together. In each half there are six slots or grooves on the inner side. When clamped together, six pins are held in position, but only five of these carry wire connections. The sixth pin, somewhere in the middle, appears to be only a dummy. Any information as to correct assembly will be gratefully received.—C. N. Blatherwick, G3VU, "Villette," 20 The Drive, Roundhay, Leeds 8.

* * *

DEAR SIR,—Can anyone lend me the handbooks on the Army Set 38 and 68/P/R/T types, also the 46 Set for portable operation? I also wish to buy a copy of "QST" for November 1951.—G. V. Haylock, G2DHV, 63 Lewisham Hill, London, S.E.13.

Let's Get Started 23:

FREQUENCY MEASUREMENTS

by A. P. BLACKBURN

ROUGHLY SPEAKING, MEASUREMENT FALLS into two classes. One is the measurement of signals and supplies, and the other deals with the determination of values of components. This is a broad generalisation, but it serves as a satisfactory classification to the radio man. We have already seen how the first category applies to the measurement of supplies (h.t., l.t., etc.). The voltage of a signal may also be measured by similar means, but special techniques have to be used to determine its frequency.

As in most cases of measurement, it is necessary to take someone else's word for the accuracy of the result. If the frequency were low enough, it would be possible to count the number of cycles occurring per second, and a stopwatch would be needed to fix the second accurately. So it is obvious that the primary requirement is to have an

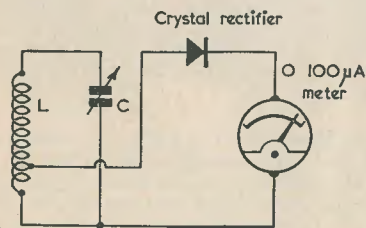


FIG. 1. ABSORPTION WAVEMETER

accurately measured second. This, of course, does not concern us, but it does concern the people who set the standard—a standard upon which we have to rely. It is unfortunate, perhaps, that we have to be dependent upon an outside factor in this respect, but the easiest and most effective method of frequency measurement is by comparison. We shall hear more later of the number of sources to which we may refer ourselves.

Absorption Wavemeters

Let's say we have an r.f. oscillator, all set up ready and working. But we would like to know at what frequency it is oscillating. There is a very simple device called the absorption wavemeter which can give an answer to this with a fair degree of accuracy.

Fig. 1 shows the circuit of the wavemeter. You can see that it consists merely of a tuned circuit, a crystal detector and a meter. The coil, L, is brought reasonably close to the circuitry of the oscillator, and the tuning capacitor rotated until a reading is obtained on the meter. At this point the L and C of the wavemeter are tuned to the same frequency as the oscillator. If the tuning capacitor is provided with a knob and scale calibrated in frequency, our problem is solved.

There are many versions of this simple wavemeter, which only vary in complexity. The one illustrated has the crystal tapped down L. This relieves the tuned circuit of some of the load due to the detector and meter, and enables a reasonable Q value to be obtained.

If the oscillator produces insufficient power to deflect the meter, the coil of the wavemeter can be moved very close to the coil of the oscillator. This will stop the oscillator from working when the LC circuit of the wavemeter is tuned to the same frequency as the oscillator. This is not a particularly accurate method, however, since the close proximity of the wavemeter coil affects the frequency at which the oscillator is working. In view of this, if the oscillator does produce a reasonable power, the wavemeter should be held as far as possible from the oscillator, consistent with a deflection on the meter.

When using the meter, the circuit absorbs a little power from the oscillator. As the wavemeter is moved closer, it absorbs more and more power until it is so close that it absorbs all that the oscillator can give, and the oscillator stops. Of course, this is all very well, but how is the wavemeter to be calibrated in the first place? And here it is that we find ourselves in the deep water of all measurement.

Beating

A way out of this difficulty is by a further comparison. Ordinary radio stations work on pretty accurately defined frequencies, all of which we can easily look up if we wish to know them. But one could scarcely expect broadcast radio signals to provide sufficient power to deflect the meter on our wavemeter. So we must build an oscillator and compare it with, say, the signals from a few radio stations. The way we compare two signals is by beating them together. All that is necessary is to tune a radio receiver to any station and place the oscillator close to the aerial of the receiver. The oscillator is tuned until a whistle is heard superimposed upon the programme. If you continue to tune the oscillator, the whistle will decrease in frequency, until eventually it disappears. Further tuning will cause the whistle to start again at a low frequency, which will increase as tuning is continued in the same direction. The centre point of the period having no whistle is the point where both signals are of the same frequency. Once again, the oscillator should be placed as far as possible from the receiver aerial, consistent with introducing enough signal to produce the whistle.

We may, therefore, calibrate this oscillator against any number of broadcast stations, which also enables us to calibrate our wavemeter from the oscillator. We could have found the frequency of the original oscillator by beating it against a broadcast signal, if there had been a convenient signal at the frequency of the oscillator. By using the wavemeter, we may calibrate at any frequency.

Standards

It is often useful to have permanent gear set up in the workshop with which frequency may be checked. Then, of course, the question of accuracy arises. We have to decide to what limits of accuracy we want to work.

The wavemeter is an excellent device if a rough check only is required. It requires no power supplies and is usually made up in a small box with a handle, so that it may be used in awkward places without a mass of leads. Its drawback is that the stability of calibration is not very good unless considerable precautions are taken. The discrimination depends upon the Q of the circuit. Discrimination in this context means how

accurately the maximum reading on the meter can be judged. If, for example, the tuning control could be moved 50kc/s at 5Mc/s without a noticeable change in meter reading, we could not hope to read to better than 50kc/s accuracy at this frequency.

A permanently built calibrated oscillator (a signal generator, for example) can be made to be more reliable and accurate. In this case, the discrimination can be a few cycles

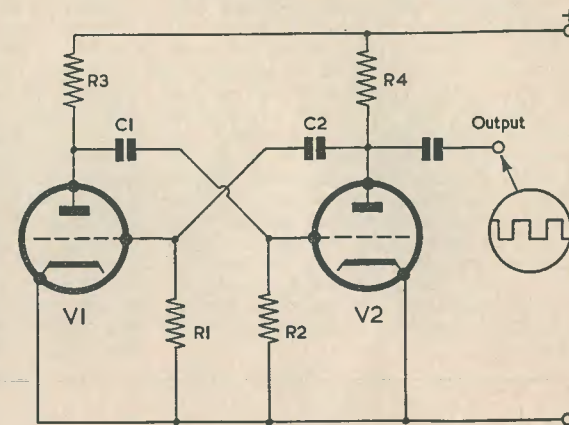


FIG. 2. THE MULTIVIBRATOR

per second at any frequency, but once again it is necessary to take considerable care in the design and construction of such an oscillator, if it is to hold its calibration.

The answer to stability problems in oscillators lies, of course, in the quartz crystal. We substitute a crystal in place of the L and C, but the oscillator will be fixed at one frequency. Unless, however, we are willing to invest in a few dozen crystals, which would be very expensive indeed, we are stuck at one frequency. Fortunately for us, someone has been faced with this problem before us, and has found a very ingenious answer. It is called the frequency divider.

Frequency Dividers

These devices serve to generate a frequency less than the primary oscillator frequency. Suppose a crystal oscillator running at 1Mc/s has been produced, and it is desired to obtain a signal at 100kc/s, at the same accuracy and stability as the crystal.

The circuit for achieving this result is probably new to some readers. It is a particular form of oscillator, known as the "multivibrator," and the circuit is shown in

Fig. 2. It consists of two valves, V_1 and V_2 with the anode of each valve coupled to the grid of the other.

We will imagine that, upon switching on, some small disturbance at the grid of V_1 causes the voltage at the anode of V_1 to drop. This drop in voltage will be passed to the grid of V_2 via C_1 . As the grid voltage goes negative, the current in the valve will decrease, and the standing voltage drop across the anode load R_4 will also decrease. The anode of V_2 will become more positive. This increase in volts will be passed to the grid of V_1 via C_2 , which will cause V_1 to pass more current, and the voltage at the anode will drop even more. This regenerative process will continue until V_2 is cut off, that is, passes no current. In such a condition, V_1 is passing current heavily and V_2 is cut off. The circuit remains in this condition until C_1 has discharged through R_2 , which will cause the grid of V_2 to move positive again. When the grid is sufficiently positive to allow current to start flowing in V_2 , the anode of V_2 will drop. The drop will be passed via C_2 to the grid of V_1 and the whole process will continue until V_1 is cut off and V_2 is conducting.

forms are shown in Fig. 3a. The fact that these waveforms are "square waves," that is, highly distorted from the sinusoidal, means that they contain many harmonics. If they occur at a rate of 100,000 per second, then harmonics will be found at 200kc/s, 300kc/s, and so on, up to many megacycles. If this multivibrator were coupled to a receiver, therefore, signals would appear at intervals of 100kc/s throughout the band.

The circuit has another interesting characteristic. The frequency of oscillation is inherently unstable. We can use this characteristic in the following way. If we feed a voltage of stable frequency to the appropriate point in the multivibrator, the multivibrator will fall into step with the applied voltage. If the frequency of the multivibrator, when "free running," were one-tenth of the applied locking frequency, the multivibrator, when locked, would fall into step at one-tenth of the applied frequency. For example, if we feed the output of a crystal oscillator operating at 1Mc/s to the multivibrator oscillating at 100kc/s, the multivibrator will run at exactly one-tenth of 1Mc/s, i.e. 100kc/s—if the circuit is properly designed. The important thing is that the 100kc/s is as accurate

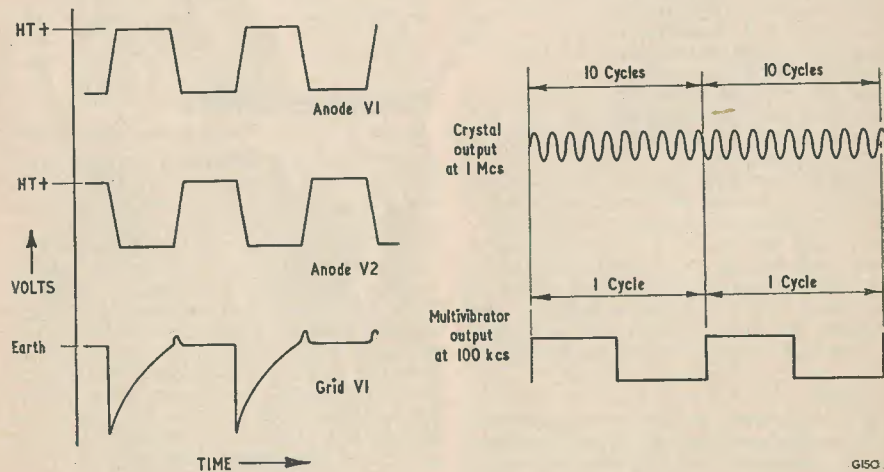


FIG. 3(a) MULTIVIBRATOR WAVEFORMS

FIG. 3(b) FREQUENCY DIVISION

From the description, we can see that this is an oscillator which works in jerks, with a pause in between. In these circumstances we can hardly expect to find a nice even sine wave appearing at either anode. The wave-

forms are shown in Fig. 3a. The fact that these waveforms are "square waves," that is, highly distorted from the sinusoidal, means that they contain many harmonics. If they occur at a rate of 100,000 per second, then harmonics will be found at 200kc/s, 300kc/s, and so on, up to many megacycles. If this multivibrator were coupled to a receiver, therefore, signals would appear at intervals of 100kc/s throughout the band.

The crystal oscillator may also be designed

to produce a vast range of harmonics. The crystal oscillator-multivibrator combination can, therefore, produce 1Mc/s signals or 100kc/s signals over a very wide band of frequencies.

disconnect h.t.) tune over a few megacycles on the receiver. At intervals of 100kc/s a hiss should be heard. These are the harmonics of the crystal oscillator. Mark these points on the dial or take note of the dial

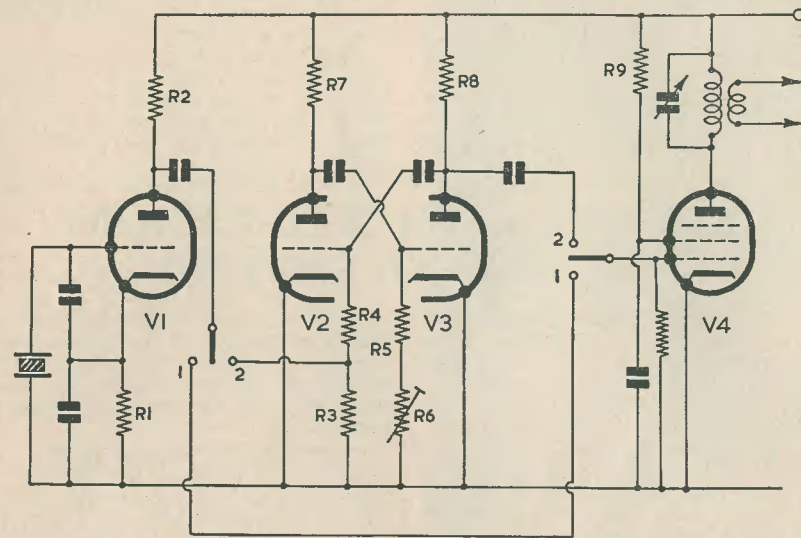


FIG. 4. FREQUENCY STANDARD

G151

Setting Up

To set up a system such as that we have described naturally involves a certain amount of work. Fig. 4 shows a typical circuit with a few refinements. V_1 is a crystal oscillator; V_2 and V_3 are the multivibrator valves. To vary the frequency of the multivibrator, R_6 has been made variable, and this is adjusted until the multivibrator falls into step with the crystal oscillator at the correct division ratio, say 10 : 1. Let us assume that V_1 is oscillating at 100kc/s. The multivibrator will therefore be oscillating at 10kc/s. The last valve, V_4 , is used to combine the 100kc/s and 10kc/s signals if required. Its anode circuit is a tuned circuit so that the required harmonic may be selected.

Setting up can best be carried out with an oscilloscope. The waveforms to be expected are shown in Fig. 5. If such a luxury as a scope is not included in your inventory, an ordinary short wave receiver may be used. A short lead should be substituted for the aerial, and the lead should be placed near the frequency standard circuitry. With the multivibrator stopped (remove a valve or

readings. Start the multivibrator and allow a few minutes for it to settle down. Tune the receiver between any two of the 100kc/s

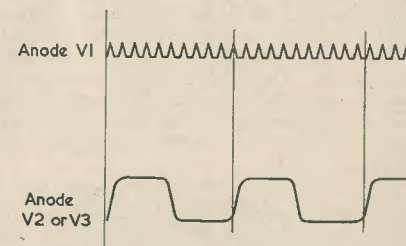


FIG. 5. WAVEFORMS OF FIG. 4.

G152

points, and there should be nine points at which a hiss is heard from the receiver. If the number is short or more than this, R_6

should be adjusted until the correct number is obtained. The aerial may then be connected to the output terminals (Fig. 4) and the same result obtained, except that tuning the anode of V₄ will make the hiss louder.

Receiver Calibration

The above process may be used for accurately calibrating a receiver. The main difficulty arises in finding which harmonic the receiver is tuned to. If the receiver is completely uncalibrated, it would be necessary to find a station of known frequency. This point may then be marked temporarily on the receiver dial. The nearest 100kc/s

point above and below this point may then be found by using the harmonics of the crystal as already described. Further points may be obtained by counting away from the established points as each 100kc/s harmonic is tuned in. When these points have been marked on the dial, the 10kc/s points may be marked by switching to the multivibrator and tuning to its harmonics.

There are, of course, many refinements to all these techniques, and very elegant measuring systems may be set up, but they nearly all rest upon the principles of wavemeters, reference oscillators, and crystal oscillators.

PORTABLE AMATEUR RADIO EQUIPMENT CONTEST

IN AN ENDEAVOUR TO INCREASE INTEREST in, and encourage development of, low-power and essentially portable equipment by radio amateurs, the QRP Society introduce "P A R E C," the

PORTABLE AMATEUR RADIO EQUIPMENT CONTEST

open to ALL licensed amateurs and SWLs, either as individuals or in club teams. The Society acknowledge with sincere thanks the valuable assistance offered by DATA PUBLICATIONS LTD., publishers of *The Radio Constructor*, in accepting responsibility for the provision of an unbiased panel of judges for the entries.

The contest will be divided into four classes, in which equipment will be eligible as follows:—

Class "A"—For "hand" portable (valve) gear. Open to receivers up to 3 lb weight, transmitters up to 5 lb weight, and transceivers up to 7 lb weight. All equipment in this class must be dry battery operated, but the weights quoted are *exclusive* of batteries, phones, key, antenna or any other ancillary equipment. The judges will give special consideration to economy of battery consumption, lightness, compactness, versatility, radio coverage, ease of handling and operation.

Class "B"—For "mobile" equipment—transmitters, receivers or transceivers of 10 lb maximum weight. Equipment in this class may be powered by dry or wet batteries, or vibrator units. The maximum weight is *exclusive* of batteries and ancillary equipment, but is *INCLUSIVE* of any necessary vibrator unit. The judges will give special attention to soundness of design, compactness, mechanical and electrical strength, versatility, radio coverage and ease of operation.

Class "C"—For transistor sets of a maximum weight of 2 lb, exclusive of ancillary equipment. The judges will look particularly for radio versatility, coverage, robustness and cleanliness of design and construction.

Class "D"—For portable test gear of any type (as, for example, wavemeters, signal generators, etc.) without restriction except that all entries must be battery operated and **TRULY PORTABLE**. The judges will especially consider size, weight, versatility, soundness of construction and design and accuracy of performance.

Apparatus for P A R E C need not be specially built for the contest, as existing gear will be eligible if it meets the above specifications, but **ALL ENTRIES MUST BE AMATEUR BUILT EQUIPMENT**.

How to make your entry.—A description of the entry, laid out as follows, should be sent to the Hon. Secretary, QRP Society (J. Whitehead, 92 Rydens Avenue, Walton-on-Thames, Surrey), and should be written as clearly as possible (or preferably type-written) on foolscap paper, using one side of the paper *only*.

Sheet 1, the title page, should contain the following information **ONLY**: "QRP Society, P A R E C" (in the top left corner); Name, call (if any) and address of sender (top right corner); Title of gear submitted (centre, above middle of page). The bottom half of the sheet should be left blank for judges' comments.

Sheet 2: Theoretical diagram and components list **ONLY**.

Sheet 3: Layout sketches. Photographs may be attached but are not essential for initial consideration. (The judges may request photographs at a later date.)

Sheet 4 upwards (as necessary): Detailed description of the apparatus, which should be carefully checked to include **ALL** information relative to the gear and its performance. **AT THE TOP OF SHEET 4** the following information should be clearly tabulated: Type of apparatus; power consumption; weight; overall size; band coverage.

Entry forms, set out as above, will be scrutinised by a Selection Committee of the QRP Society (who may ask the entrant to furnish further information where necessary). This committee will assess the best three entries in each class, and to each of these twelve entrants A **SPECIAL CERTIFICATE** (13 in by 8 in) will be awarded by the QRP Society. The twelve entrants thus selected will be invited to forward the apparatus itself to the Editor of *The Radio Constructor* (c/o Data Publications Ltd., 57 Maida Vale, London, W.9), who has kindly offered the services of his staff to give their unbiased judgment in the selection of the final winners of each class and of the contest as a whole.


Apparatus should not be sent in **BEFORE** a date to be notified to the finalists upon receipt of their certificates. Great care should be exercised in providing sufficiently protective packing. Return packing and postage will be paid for by the QRP Society. All possible care will be taken of apparatus while in the hands of Data Publications Ltd., but no responsibility can be accepted for any loss or damage sustained either then or during transit.

Prizes (the nature of which will be announced at a later date) will be awarded to each class winner, and also for the best entry by a QRP Society member. There will, in addition, be a prize for the best entry by a club team.

A detailed article on the winning entry will be published (and paid for at usual rates) in *The Radio Constructor* as soon after the conclusion of the contest as possible. The QRP Society retain the right to publish in their Society Journal "QRP" full accounts of any or all of the equipment submitted.

Overseas Entries will be particularly welcomed and a certificate (as detailed above) will be awarded to the best overseas entry in each of the four classes. Since, however, it will obviously be impossible for overseas participants to send in the actual apparatus itself, they will not be asked to submit gear for the final judging and will not, in consequence, be eligible for the finalists' prizes (other than QRP Society certificates).

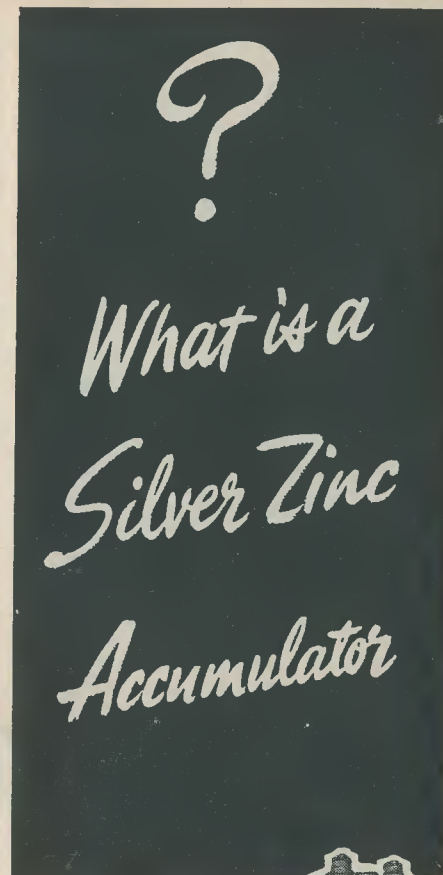Closing Date for receipt of entry forms by the Hon. Sec., QRP Society, will be 30th September, 1955. Entries ready prior to this date should be submitted as soon as available in order to avoid any "last minute rush."



What is a
Silver Zinc
Accumulator

A Silver Zinc Accumulator is the smallest and lightest type of rechargeable accumulator in worldwide use. It has other advantages too — such as constant voltage and high rate of discharge — full particulars on request.



VENNER
ACCUMULATORS

Write for Publication RC/A

VENNER ACCUMULATORS LTD
KINGSTON-BY-PASS NEW MALDEN SURREY
Telephone MALden 2442

Associated Cos. Venner Limited — Venner Electronics Ltd.

G2ACC offers you . . .

SWITCH SERVICE

Special types of paxolin and ceramic wafer rotary switches made to individual requirements. Wafers: single pole up to 11 way, 2-pole up to 5 way or 3-pole up to 3 way and up to six banks of wafers per switch. The moving contacts are normally of the "shorting" type, which maintains connection with one contact until after the next is made. Contacts of the "non-shorting" type, which break connection with one contact before the next is made, may be had if specified. Switch supplied complete with fixing nut and locking washer. Paxolin type for general wave-change switching: 1-bank 7/6; 2-bank 11/6; 3-bank 15/-; 4-bank 18/-; 5-bank 21/-; 6-bank 24/-. Ceramic type for low loss and where H.T. between 250 and 1,000 volts may be used: 1-bank 9/-; 2-bank 14/6; 3-bank 20/-; 4-bank 26/-; 5-bank 32/-.

CATALOGUE No. 9 (56 pages illustrated of general short-wave and radio components. Free on request. U.K. only.)

Postage extra on orders under £2

SOUTHERN RADIO & ELECTRICAL SUPPLIES

SORAD WORKS

REDLYNCH · SALISBURY · WILTS

Telephone Downton 207

20 CIRCUITS FOR 2/6 ONLY

NEW 1955 EDITION

Our Supa-Handbook, "The Home Constructor" (76 pages) now incorporates:

- ★ **20 CIRCUITS**—Superhets, T.R.F. Sets, Amplifiers, Feeder Units, Test Equipment, etc.
- ★ **SUPERHETS**—Full constructional details, supra-simplified layout and point-to-point wiring diagrams for building a variety of superhets.
- ★ **COIL PACK**—Full Constructional details for building a superhet coil pack.
- ★ **CAR RADIO**—Full constructional details.
- ★ **BATTERY CHARGER**—Details for building a CHEAP charger.
- ★ **RADIO GEN**—Pages of information, Resistance, Colour Code, Formulae and "know-how."
- ★ **RADIO CONTROL**—General information and list.
- ★ **RADIOGRAM**—Constructors list.
- ★ **CATALOGUE**—Profusely illustrated price list of components covering a wider range than ever before.
- ★ **WOLF CUB**—Home constructor equipment details.

You Can't Get Better Value—IT'S TOPS!

*"The most helpful book in the trade."

SEND 2/6 FOR YOUR COPY TO-DAY

SUPACOILS (Dept. RC5)

21 MARKHOUSE ROAD · LONDON · E17
Telephone KEYstone 6896

NEW SURPLUS . . .


0Z4A 6/-	6C4 5/-	6Q7G 8/6	EF39 6/-
1R5 7/6	6CH6 6/6	6Z4 5/-	EF50 5/-
1S5 7/6	6AM5 6/6	7C5 7/6	EF50 (Syl) 7/6
1T4 6/6	6F6G 7/6	7S7 9/-	EF54 6/-
1A3 4/6	6F7 7/6	12BE6 7/6	EF80 10/-
1L4 4/6	6G6G 5/-	12AX7 8/6	EF91 5/-
2D21 8/6	6H6M 5/-	15D2 4/6	EF92 5/-
2A3 7/6	6J5GT 6/-	25L6GT 10/-	EL35 8/6
2X2 3/6	6J7G 5/-	50L6GT 9/-	EL91 6/6
3A4 7/6	6J7M 7/6	813 60/-	EL84 11/6
3D6 5/-	6J6 5/-	866A 12/6	EY51 11/6
5Y3GT 7/6	6K6GT 6/6	954 5/-	PCC84 12/-
5U4G 8/6	6K7G 5/-	955 5/-	PL82 10/-
5Z4G 8/6	6K7GT 6/6	956 5/-	U22 8/6
6AB7M 7/6	6K7M 6/6	9001 5/-	UCH42 10/-
6AC7M 6/-	6K8G 8/6	9002 5/-	VS110A 4/6
6AG5 3/6	6L7M 7/6	9003 5/-	VU120A 3/6
6AG7M 9/-	6L6G 9/-	CBL1 10/-	VR105/ 30 7/6
6AK5 6/6	6SA7M 8/6	CV286 7/6	VR150/ 30 7/6
6AL5 5/-	6SG7M 7/6	CV287 7/6	W77 5/-
6AM6 5/-	6SK7M 7/6	EBC3 10/-	Z77 5/-
6AQ5 9/-	6SL7GT 7/6	EB91 5/-	X66 7/6
6AT6 7/6	6SN7GT 6/6	ECC81 10/6	807 (USA) 8/6
6BA6 7/6	6SS7M 6/6	ECC82 10/6	
6BE6 7/6	6USG 6/6	ECH35 10/-	
6BJ6 7/6	6V6GT 6/6	ECH42 10/-	
6BS7 6/6	6X4 7/6	ECL80 11/6	
6BW6 7/6	6X5GT 7/6	EF37 7/6	

Cyldon 5 channel Teletuners, less valves, 10/6 each
"Pan!" Crackle Paint 3/- tin

Post/packing: under 10/- add 6d.; 20/- add 1/-; 40/- add 1/6; free over 40/- All despatched by return

JOHN ANGLIN

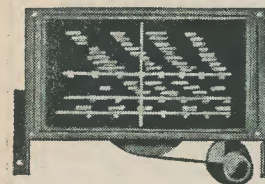160 CLEETHORPE ROAD GRIMSBY Lincs
Telephone 56315



The
S.L.8
Spin Wheel
Drive

Complete with 3-wave band glass scale 9" x 4 1/2" — 27/6

The S.L.8 Spin Wheel Drive gets easy control through a ratio 24:1. Fitted with constant velocity coupling, it eliminates strain on the Condenser, providing mechanical and electrical isolation from vibration and noise.

S.L.5, similar, but fitted with reverse vernier drive, gives ratios of 18:1 search and 50:1 reverse vernier. 26/6.

Please write for our list of Condensers and Drives

JACKSON BROS.
(London) Ltd.

KINGSWAY · WADDON · SURREY


Telephone CROYDON 2754-5

Telegrams WALFILCO, SOUPHON, LONDON

WORLD-WIDE DX IS CERTAIN

with the

Labgear 150 Watt TRANSMITTER

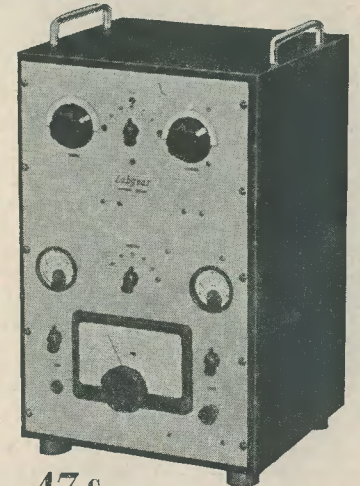


PRICE 47 Gns. Send S.A.c. for leaflet RC5035

Labgear (Cambridge) Ltd
WILLOW PLACE · CAMBRIDGE · Telephone 2494-5

Quality Equipment Designers Ltd.


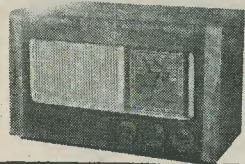
75 GRAND PARADE, HARRINGAY
LONDON, N.4. Phone: STA. 3712



THE NEW LOOK T.R.F. RECEIVER—Build this superb radio £5.15.0 Complete set of components plus 2/6 pkg./carr. A 3 valve T.R.F., plus Metal Rectifiers. V.L.U. 6K7 (HF), 6J7 (Det), 6V6 (Output). Coverage 180/550 metres Medium, and 800/2,000 metres Long. Cabinet is latest design and outstanding in appearance. Assembly instructions 1/- (post free), include point-to-point wiring, chassis layout, etc. Also stock list of priced components (may be purchased separately). Can be purchased completely built and ready for use for £6 15 0 plus 3/6 pkg./carr. All components guaranteed one year. Valves 3 months.

THE 'ROFTON' 11.F.I.B. AMPLIFIER ★ Separate Bass ★ Separate Treble ★ Separate Volume ★ Feeder unit input socket ★ Radio, gram, mike input sockets ★ Negative feedback ★ Fully shrouded Mains Trans. ★ O.P. Trans. tapped 3 and 15 ohms ★ Matched 6V6's ★ Chassis sprayed Metallic Bronze. V.L.U. 6SL7, 6SN7, two 6V6's, 5Z4, mains 200/250V A.C. Has passed all tests for true reproduction, placing it at the top in the Audio Field. Supplied in KIT FORM at £10 7 6 plus 4/- pkg. Instruction book with theoretical circuit, chassis layout, etc., 1/-.

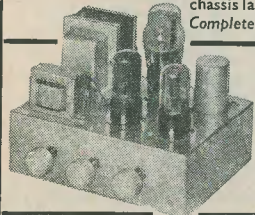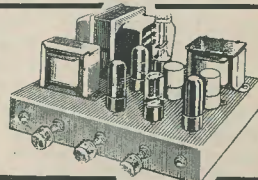Completely built and tested £11.12.6 plus 5/-pkg., etc.



THE 'ROFTON' FOUR—A HIGH QUALITY AMPLIFIER ★ Separate Bass ★ Separate Treble ★ Separate Volume ★ Fully shrouded Mains Trans. ★ Output 4 watts ★ Chassis sprayed Metallic Bronze ★ Engraved Control Knobs (Ivory or Walnut) ★ Negative feedback ★ LS/PU plugs and screen lead for PU provided. V.L.U. 6SL7, 6V6, 5Z4. Mains 200/250V A.C. Can be supplied in KIT FORM at £4 15 0 plus 2/6 pkg. Instructional book, theoretical circuit chassis layout, etc., 1/-.

Completely built and tested £5.12.6 Plus 2/6 pkg., etc.

TERMS: Cash with order or C.O.D. All orders for small items totalling over £2 post free unless otherwise stated. Write to Dept. R.C. Personal shoppers welcomed—alight at Harringay Arena. Open 9-6 Mon.—Sat. (Early closing Wed.).

G2AK THIS MONTH'S BARGAINS G2AK

Talking of TABLE TOPPERS

The Ideal Power Transformer for the Table Top Rig.

This Parmeko-made Transformer has the following conservative ratings. Primary, 230V 50c/s. Secondary, 620/550/375/0/375/550/620V. Rated at 275VA. It will give 620 or 550 volts at 200mA simultaneously with 375V at 250mA. All the HT you require for RF and Modulator. Also 2-5V 3A windings for suitable rectifiers such as 5R4GY, 5Z3, 83, 5U4, etc., weight 24½lb. Size 6½" x 6½" x 5½" high. Worth at least £7. Our price £3 only, carr. paid. C.W.O. Only. No C.O.D.

We regret that orders from EIRE or ABROAD cannot be accepted

METERS: 2½" Scale Flush Mounting, 0-10mA, 0-30mA and 0-100mA, 12/6 each. 2" Scale Square Flush 0-50mA, 0-150mA, 0-3A Thermo, 0-20V d.c., and 20/0/20A d.c., 7/6 each. 2½" Scale Proj. Type Thermo 0-15A, 7/6 each. 2" Scale Round Flush 0-½A Thermo and 0-350mA Ditto, 7/6 each.

Carriage paid on all orders over £1 except where stated.

CHAS. H. YOUNG, G2AK

MAIL ORDERS TO Dept. 'R,' 102 HOLLOWAY HEAD, BIRMINGHAM Midlands 3254 Central 1635

SPECIAL VALVE OFFER: TZ40 35/-; 6L6G, 10/6; 5R4GY, 12/6; 829/3E29, 60/-; 100TH, 90/-; 866A, 17/6, or 30/- per pair; 807, 10/- each or 17/6 per pair; 931A, 45/-; 813, 80/-

FISK SOLARISCOPIES. Complete with Charts, give World Time, light and dark paths. Invaluable to the DX man. List 21/-. Our price 7/6 post free.

PANL HOME CRACKLE. Black, brown or green, 3/- tin, p. & p. 8d.

H.S. KEYING RELAYS (Siemens). 1700 x 1700 coils, 12/6.

TWIN FEEDER: 300 ohm twin ribbon feeder, similar, K25, 6d. per yard. K35B Telcon (round), 1/6 per yard. Post on above feeder and cable, 1/6 any length.

AIRSPACED CO-AXIAL CABLE 150 ohms (normal price 3/11 per ft.), 20-yd. coils only £1 per coil, post free.

PI CIRCUIT OUTPUT TUNING CONDENSERS. Made by E. F. Johnson Co. U.S.A. Max. cap. 500pF 1,500V rating. Ceramic insulation, size 5" long x 2½" wide—2½" high, excluding spindle projection. Our price only 15/- post free.

AR88 SPARES: Cabinets, £4 15s., packing and carriage, 7/6; complete set of 14 valves, £5 10s.; Perspex escutcheons, 22/6; "D" type, i.f.s., 12/6. Output Transformers to Government specification, 37/6 each.

COPPER WIRE: 14G, H/D 140ft, 15/-; 70ft, 7/6. Post and packing, 2/-. Other lengths pro rata.

RACK MOUNTING PANELS: 19" x 5½", 7", 8½" or 10½", black crackle finish, 5/9, 6/6, 7/6, 9/- respectively, postage and packing, 1/6.

ABSORPTION WAVEMETERS. 3.00 to 35.00Mc/s in 3 switched bands. 3.5, 7, 14, 21 and 28Mc/s. Ham Bands marked on scale. Complete with indicator bulb. A Must for any Ham Shack. Only 10/6, p. and p. 1/-.

THIS MONTH'S SPECIAL

VIBRATOR POWER UNITS

12V d.c. input, 300V 100mA output. Fully smoothed and filtered. In black crackled finished case, 39/6, p. & p. 1/6

Please include small amount for orders under £1

ALL CALLERS TO 110 DALE END, BIRMINGHAM

PLEASE PRINT YOUR NAME AND ADDRESS

Midlands 3254 Central 1635


CONSTRUCTORS build these at low cost!

PERSONAL PORTABLE RADIO

30/-

Post Free

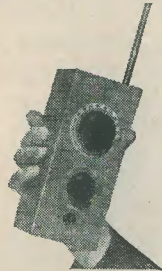This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Ideal for the holiday, hiking, fishing, camping, cycling, etc. Use it at home, at the office, in bed, or just anywhere.



Send 2/- for layout, Wiring diagram and Components Price List.

PRESELECTOR

Component parts for this unit, as featured on page 592 of this issue, are available as follows:

Panel and Chassis 3/6
Coil Holder 9d.
Coil to cover reqd. range 10-23, 20-43, 40-100; and MW range each 3/6
954 Valve 3/-
Valve Holder 2/-
0.00016uF Condenser 4/-
RF Choke 2/-
Variable potentiometer 3/-
Suitable resistors 2/6
Suitable condensers 2/6

POWER UNIT TYPE PUI


An ideal power supply for both these receivers and the Preselector. Also for inclusion in Test Equipment. 120V at 20 ma, 6.3V at 1.5A

32/6

ALL-WAVE RADIO

30/-

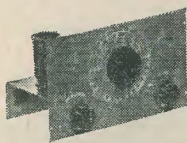Ideal for the beginner or for those requiring a simple standby receiver.



This 1 valve S.W. receiver can be built for 30/-, from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.

R.C.S. PRODUCTS (RADIO) LTD
11 OLIVER ROAD (Mail order only) LONDON E17



Rapid Heating
—Extreme
Lightness—
20 different
models — Bit
sizes, 1/8",
3/16", 1/4",
5/16", 3/8"—
Prices from 9/6
Details of full
range in folder
No. 58
sent on request

- NO TRANSFORMER NECESSARY
- FOR MAINS OR LOW VOLTAGES

Sole Manufacturers and Distributors
LIGHT SOLDERING DEVELOPMENTS LTD
106 GEORGE ST. CROYDON SURREY
Telephone CROydon 8589

VALVES

NEW TESTED AND GUARANTEED							
1R5	7/6	6F8G	8/6	12AX7	8/6	ECH42	11/6
1S5	7/6	6G6G	4/9	12AT7	8/6	ECL80	12/6
1T4	7/6	6J5GT	6/6	12K8GT	8/6	EF22	7/6
3V4	7/6	6K7G	5/6	12K7GT	8/6	EF36	7/6
5U4G	8/6	6K8G	8/-	57	7/6	EF37A	14/6
5Y3GT	9/6	6L6G	9/6	58	7/6	EF39	7/6
5Z4C	8/6	6O7G	8/-	5763	7/6	EF80	11/6
6AG5	6/9	6O7GT	8/6	954	2/6	EF85	11/6
6AM6	7/6	6S17	8/-	9006	5/6	EF91	7/6
6AT6	8/-	6SK7	8/-	AZ31	10/6	EF92	4/6
6BE6	8/-	6SL7GT	8/-	DAF91	7/6	EL32	7/6
6BW6	8/-	6SN7GT	8/-	DF91	7/6	EY51	12/6
6B7G	8/6	6SS7	6/9	DL63	8/6	EZ35	8/-
6B8	7/6	6U7G	8/6	DL94	7/6	KT66	11/6
6B8G	7/6	6V6G	7/6	EAS0	2/-	PL82	10/6
6BA6	8/6	6U5G	7/6	EAC91	6/-	PY82	10/6
6BR7	8/-	6X4	8/-	EAF42	9/6	UCH42	11/6
6BS7	8/-	6X5GT	8/-	EB91	6/6	UL41	9/6
6SA7	8/-	7H7	8/6	EBC33	8/6	UY41	8/6
6F6G	8/6	12AH7	7/6	EBC41	8/6	X65	10/6

Matched Pairs KT66, 25/-; 6V6G and GT, 17/- per pair. 6K8G, 6O7G, 6V6G, 5Z4G, 6K7G, 34/6 per set. 1R5, 1T4, 1S5, 3V4, 27/6 per set.

ELECTROLYTIC CONDENSERS

Tubular Type
2/350v B.E.C., 1/3
8/350v T.C.C., 1/6
8/450v B.E.C., 2/-
16/275v T.C.C., 2/-
16/450v T.C.C., 3/3
16/450v B.E.C., 3/-

Can Type
8/500v Dubilier, 1/9
8 x 8 450v B.E.C., 4/-
8 x 16 450v B.E.C., 5/-
16 x 16 450v B.E.C., 5/6
4 x 4 x 4 450v, 3/6
32 x 32 450v B.E.C., 5/9

Bias Condensers. 12/50v T.C.C., 9d. 25/25v, 1/3.
25/50v, 1/6 50/25, 1/6 50/50v, 2/- Small Mica: 2-2000 pF.
6d. .003-1 MFD, 500v Tubular, 8d. 25-1 MFD 500v, 1/-.
Mica: 1000v wkg. T.C.C., .0015, .002, .0025, .003, .004.
.005, .008, .01, 1/- Paper Block T.C.C., .25/1500v, 2/3.
2 MFD 100v, 1/3. 4/100v, 1/6. 2/350v, 2/6. 4/350v, 3/-.
2.5 x 2.5 x 1/400v, 3/6.

Meters. 0-4 Amp. Thermo, 0-2mA M.C. movement, 2in scale, 3½ x 2½, 7/6.

Microphones. Marconi hand type, carbon with switch, 4/6.

Potentiometers. All values, Long spindled, s.p., 4/- d.p., 4/9. Less SW, 3/-.

Resistors. ¼w, 4d. ¼w, 6d. 1w, 8d. 2w, 10d. 6w, 1/- 10w, 1/3.

Switches. Midget long spindled, 1P, 12w; 2P 6w; 3P 4w; 4P 2w; 4P 3w, 4/-.

Co-Axial Cable. Stranded, 75ohm, ¼in, 7d. yard.

B7G V. Holders. Ceramic with Seng. can, 1/- B9A, moulded, 2/-.


Toggle Switches. Q.M.B., Sp, 2/-; spdt, 3/6; dpst, 3/9; dpdt, 4/6.

O/P. Transformers. Pen. 60mA, 4/6; 45mA, 3/6; Chokes, 15h, 80mA, 4/9.

All goods new and guaranteed. Post 6d.

R. COOPER
32 SOUTH END CROYDON SURREY
CROYDON 9186

BUILD ONE OF THESE SETS!

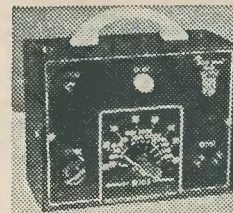

This can be built for only 49/6. Build this exceptionally sensitive twin-triode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6½in. x 5in. x 3in. Covers all medium and long waves, uses one only all-dry battery which lasts many months as H.T. Consumption is only 1 to 1.5 m.a. Ideal for bedroom, garden, holidays, etc. Complete Kit only 49/6, Post Free (sent by return with full set of clear, easy-to-follow plans). All parts sold separately. C.O.D. 1/6 extra.

This can be built for only 97/6. **AMAZING VALUE!** Complete kit of 3 valves, plus metal rectifier, A.C. Mains set, only 97/6. Terrific new circuit, with optional negative feedback circuit giving beautiful tone. Covers all Medium and Long Waves. Ready to use chassis (Punched, etc.). Every component tested before packing. Cabinet size 12in. x 6in. x 5in. For A.C. Mains 200/250 volts. Complete kit with valves, speaker, cabinet, etc., only 97/6, plus 2/6 Post and Packing. (Sent with full set of clear, easy-to-follow plans.) All parts, cabinet, speaker, etc., sold separately. C.O.D. 1/6 extra. **BRIGHTON RADIO & TELEVISION CO** (Dept. RC12) 69 PRESTON ST., BRIGHTON

"FULL TONE" 8 WATT AMPLIFIER

We can supply all the components for this new quality amplifier from stock. Send S.A.E. for detailed price list

Chassis ready punched and complete with three 5-way tag strips, 8/6.

Valves, new and guaranteed, 6V6GT, 9/-; 6AT6, 10/-; EF86 (new Mullard B.V.A.), £1/3/3; 5Z4G (new Brimar B.V.A.), 13/11.

Transformers, Allen OPI348, 15/-. Various mains transformers available.

Condensers, T.C.C., 16 x 16 CE28LE, 9/-; 50mfd CE88CE, 3/-; 50mfd CE87B, 2/9; 0.25mfd type 343, 1/6; 0.05mfd type 343, 1/-.

Potentiometers, 250K log less switch, 3/-.

Resistors, complete set of suitable resistors for this amplifier, 7/6, post paid.

Valveholders, international octal, B9A and B7G, 9d. each

Co-axial Plug, Belling, 1/3.
Co-axial Socket, Belling, 1/2.

All parts in stock for the "Jason" (Radio Constructor) F.M. Tuner Unit. S.A.E. for detailed price list. Demonstration model working

HOME RADIO of MITCHAM
187 LONDON ROAD MITCHAM SURREY
MIT 3282

★ "RF 26" F.M. CONVERTER UNIT—88/100 mc/s ★

This well-known RF26 Unit is now adaptable for F.M. reception using 2—I.F. stages and separate local Oscillator and tuned by a Muirhead graduated vernier drive, and can be converted Low cost, 92/6.

Send 2/- for 8-page Descriptive Booklet containing full wiring instructions, circuits and lay-out diagrams.

COMPONENTS OFFERED TO COMPLETE F.M. UNIT

New RF26 UNIT WITH THREE VALVES—VR137, EF54, EF54. Chassis stamped out for easy conversion £1 15 0

COMPLETE SET OF ALL COMPONENTS FOR CONVERSION, including 2-6BA6 and EB91, tuning condenser, I.F.T.'s and OSC coils, resistors and fixed condensers, plugs, wire and tag strips ... £4 12 6

INSTRUCTION BOOK with technical circuit and complete lay-out diagrams ... 2 0

SPECIAL OFFER OF ALL ABOVE ITEMS, INCLUDING RF26 and book ... £6 5 0

Postage 3 0

CHARGE FOR ALIGNMENT WHEN COMPLETED 7 6

COMPLETE SET as above and 6 valves—aligned and ready for use ... £8 10 0

N.B.—VOLTAGE REQUIRED: 250V 50 M/a and 6.3V 2 amps.

CATHODE-RAY TUBES

VC97. Guaranteed full TV picture (carr. 2/-), £2.

VC957C full TV picture, £1 15s.

Mu-Metal Screens for above 10s.

VCRI39A (ACR10). For TV or 'scope, brand new and boxed £1 15s.

VC97 Brand new, slight cut-off but suitable for 'scopes. 15/-, Post and package, 2/-.

3PB1 Boxed. 30 -

R.F. UNITS

RF24, 20-30 Mc/s. ...	15/-
RF25, 40-50 Mc/s. ...	19/6
RF26, 50-65 Mc/s. ...	35/-
RF27, 60-80 Mc/s. ...	35/-

All Brand New with Valves

INDICATOR UNIT TYPE 182A

Limited Quantity Available Suitable for TV or Oscilloscope. "Radio Constructor" 'Scope constructional circuit included.

Offered BRAND NEW (less relay) at 67/6 (plus 7/6 carr.).

U.S.A. INDICATOR UNIT BC929A

Complete with 3BPI C/R Tube and Shield. 7 valves. 2-6SN7GT. 6G6, 2X2, 6X5G volume controls, etc. Black crackle case, 1 1/2" x 9" x 9". Ideal for portable 'scope. Brand new condition 65/-, Carriage 5/.

CRYSTALS

200 kc/s 2 pin U.S.A.	10/-
465 kc/s 2 pin U.S.A.	10/-
500 kc/s 2 pin British	15/-

Postage up to £1. 1/-; £2 or over, 2/-, unless otherwise stated SEND STAMPS FOR 28-PAGE CATALOGUE

WE HAVE OVER 50,000 VALVES IN STOCK AT VERY COMPETITIVE PRICES. SEND 3d. FOR 28 PAGE CATALOGUE

LATEST TYPES NOW IN STOCK

EBC41	10/-	ECL80	12/6
EY51	12/-	50B5	10/-
EF41	11/-	PL81	12/6
EL41	11/-	PL82	10/-
EZ40	10/-	PY81	10/-
EM34	10/-	PY82	10/-
UL41	11/-	PCC84	12/6
UY41	11/-	PCF82	12/6
UF41	11/-	50C5	10/-
UCH42	12/6	12AT6	8/-
UBC41	10/-	12AT7	9/-
DK40	10/-	12AU6	9/-
EF80	10/6	12BA6	9/-
EABC80	10/-	12BE6	10/-
ECC85	10/-	6X4	8/-
EL80	9/-	35W4	8/-

SPECIAL REDUCTION FOR SETS OF VALVES

IA7GT, 1N5GT, 1H5GT, 1A5GT (or 1Q5GT), 40/- set; 10EF50 (Ex-Brand New Units), 5/- each, 45/- set; 10 6AM6 valves, £4 set; 6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G, 37/6 set; 1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4), 27/6 set; TP25, HL23/DD, VP23, PEN25 (or OP25), 25/- set; 6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 (or 25Z6G), 37/6 set; 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50L6GT), 37/6 set; 12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT or 50L6GT, 37/6 set.

RCA 931A PHOTO-ELECTRIC CELL AND MULTIPLIER

For facsimile transmission, flying spot telecine transmission and research involving low light-levels, 9-stage multiplier. Brand new and guaranteed, only £2 10s. Special 11-pin base, 2/-. Data sheets supplied. Equivalent to Mazda 27M1 and 27M2.

"38" SPECIAL OFFER WALKIE TALKIE SETS

We have purchased large quantity of the above "38" Trans/Rec. sets, and can now offer same complete with five valves, 4-VP23 & ATP4, Throat Microphones, Headphones, Junction Box and Collapsible Aerial in absolutely new condition and guaranteed Air Tested. Freq. range 7.4 to 9 Mc/s. Range approx. 5 miles. 59/6. Carriage 5/-.

U.S.A. PACKARD-BELL PRE-AMPLIFIER

Complete with 6SL7GT and 28D7GT Relay Condensers and Resistors. Brand new with Instruction Book, 12/6. P.p., 2/-.

HENRY'S (RADIO LTD.) SHOP HOURS

Mon.-Sat. 9 a.m.-6 p.m. Thursday 1 p.m. Telephone Paddington 1008/9 & 0401

5 HARROW RD. LONDON W.2

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 8d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 1/- will be made. Terms: Cash with order. All copy must be in hand by the 10th of the month for insertion in the following month's issue.

PRIVATE

FOR SALE. Premier Magnetic Televisor, complete chassis with valves, 12" tube mount, £6. Free delivery London area. Brownlow, 4 Broomhall Buildings, Sunningdale, Berks.

FOR SALE. E.H.T. Transformer 4kV., £1. Line transformer, 15s. Scanning Coils, £1. Focus Coil, 15s. Pair T41 thyratrons, 10s. All perfect order, suitable 9 inch CRT. Also large walnut console for 12 inch CRT, £4. Offers: 50 Chaldon Common Road, Caterham, Surrey.

FOR SALE. AVO 40 Meter, £8 10s. AVO DC Minor, £2. Taylor Signal Generator 65B, £8. Taylor Circuit Analyser, new, £10 10s. G.E.C. RC Bridge, £8 10s. AC/DC Meter, 12-480 volts, circuit test, 200 ohms/V. £2 10s. Pye PCR2 Communication Receiver with Power Pack and Speaker, £11. Corbett, 63 Calvert Road, High Barnet, Herts.

100 VALVES, faultless. 807, EF91, 3A4, 6AG5, 5s. UCH42, UBC41, UF41, UL41, 6s. EBF80, PY80, 6s. 6d. SAE List others. Blackwell, 25 Barons Way, Egham, Surrey.

SOUNDMASTER Tane Recorder, set Brenell components, new, cost £13 13s., original cartons, £10 or exchange Signal Generator. 11 Harrison Road, Fareham, Hants.

BARGAIN SALE. A number of small SW Receivers. Cover all bands, fully calibrated spread, etc., and other gear, all excellent condition in full working order. Very cheap. All enquiries welcomed with SAE for full descriptions. Box No. D150.

OFFERS. The Radio Constructor, volumes one to seven, complete. Richardson, 18 Auckland Avenue, Darlington, County Durham.

WILLIAMSON amplifier kit, unused, new, guaranteed valves, £16. Two Hoover HT32, rotary trans., 15s. each. Quantity of highest grade plastic tape, used once tested, 1,200 ft., 29s., plus 1s. postage. Box No. D151.

FOR SALE. Evershed & Vignoles Bridge, Megger 250V in perfect order. Measures from 0.01 ohm-999,999 ohms, 0.1% accuracy. Also 10k ohm-infinity on meg test. Bargain at £20. German Battery Receiver, Medium and Long wave band version of E52B. BFO, 8 positions of selectivity, IF 60 kc/s. In working order, 9 valves. Bargain, £10. Wright & Weaire Tape Deck, with manual, Model 2A, perfect, £22 10s. AVO Model 7, as new, £12 10s. Box No. D152.

WANTED R1224 receiver, good condition. Richards, 2 Bryn Eglwys, Glyndwr, nr. Bridgend, Glamorgan.

AVO MINOR £5. 250V Bridge Megger, £9. G.E.C. 6504A flat face tube, aluminised, unused, £9. Stabilised power unit 250-300V adjustable, 150mA max load, £5. Premier magnetic TV with valves, vision unit modified for EF91s needs finishing, £8. Home-built 'scope less VCR. 139A, £4 10s. Custom-built Williamson, perfect, £12 10s. 5 PM 6" speakers in walnut cabinets, £5 (or 25s. each). Hand mike, built-in pre-amp, for Williamson, £3. Goodmans Axiom 12, £4. Osmor type A dial, unused (list 24s. 6d.) 15s. 2 Muirhead 4" SM drives brass, 6s. each, 10s. pair. Quantity of valves, send for list. Wearite QD/6 6V sync. vibrator with base and transformer, 250V 70mA, new, unused, £2 10s. Box No. D153.

[continued on page 639]

The Walk-around Shop

Offers you :- CONDENSERS U.S.A.

(Solar) size 5" x 4" x 1 1/2", with stand-off insulators, 8/6; 4mfd 1,000V wkg. (Cornell Dubilier), 2 1/2" x 4 1/2" x 1", stand-off insulators, 5/6; 1mfd 1,000V wkg. (Aerovox), 2" x 2" x 1", 2/6; 1mfd 600V wkg. (Cornell Dubilier), 1 3/4" x 1 1/2" x 1", 2/6; 8 x 8mfd 475V wkg. (Sprague), electrolytic 1 1/2" tubular, 3/6. NOTE: Prices include postage.

RECEIVER UNIT Ex-TR1143A. Suitable for conversion to 2 metres and F.M. Wrotham. Circuit diagram free. Price, less valves, 9/-, post paid.

TRANSMITTER UNIT Ex-TR1143A. Suitable for conversion to 2 metres. Circuit diagram and coil conversion details supplied free. Price, less valves, 5/-, post paid.

AMPLIFIER UNIT Ex-TR1143A. A 3-stage transformer coupled amplifier. Push pull VT52s output to modulate push pull VT501s. Circuit diagram free. Price, less valves, 4/6, post paid.

SPECIAL PURPOSE VALVES: 713A VHF triode (door knob type), 9/-; GL446A disc sealed triode (Lighthouse Tube), 25/-; 6SN7, 6/9; 6SL7, 6/9; 6SQ7, 7/-; 807 (American), 6/6; VT52 (EL32), 7/-; TT11 (VT501), 5/-, Note: Prices include postage.

70 c.m. UNIT. Brand new, consisting of pair of tuned lines, 2 acorn valveholders, coarse and fine tuning. Suitable for mixer or oscillator unit. Size 5" x 3 1/2" x 8", 6/6 post paid.

NOTE: Orders and Enquiries to Dept. "R."

PROOPS BROS. LTD. • 52 Tottenham Court Road W1 • Open all day Saturday

Hours 9-6 p.m. Thursday to 1 p.m. LAngham 0141

SPEAKERS 12/9. P.M. 8", 6 1/2", 5 and 3 1/2" used, tested and guaranteed 2-5 ohms. Postage 1/9.

SPEAKERS 2/9. M.E. 8" 1K, 1 1/2K and 2K field, used, tested, guaranteed. Post 1/9.

O.P. TRANSFORMERS 1/9. Standard size. Salvage, tested and guaranteed. Post 6d.

VHF I124 RECEIVER 17/6. Complete with valves. 30.5-40Mc/s. 6-channel switching covers TV, sound, fire, amateurs, etc. Convertible to mains (AC or AC/DC). Drawings free. Post 2/-.

2-gang Condensers 2/9. Standard size, 0.0005. Post 6d. Salvaged guaranteed.

TRANSFORMERS 9/9. 350-0-350 6V and 5V heaters, also at 5/9, 350-0-350 12V and 4V heaters. Primary 100 to 250V (this makes ideal auto-transformer), Post 2/-.

1% Resistors 2/9. 1 meg wire wound IRC U.S.A. Post 3d.

0.2 Droppers 1/3. Used, tested. Post 4d.

IF COILS 2/9 each. Standard size 465 IF's. Post 6d. per pair.

AMPLIFIERS. 7 watts, push-pull, universal, 77/6. 4 watts 57/6 AC or universal. Ideal for p.u. or mike. Post 2/6.

AMPLIFIER 97/6. 10 watts AC. Special for mike and p.u. triple controls or 5 valve giving extra pre-amp stage, £5 10s. Post 3/6.

DUKE & CO

621 ROMFORD ROAD • LONDON • E12

Telephone GRA 6677

RADIOVISION

4 PRAED STREET
LONDON W2
Telephone AMB 4670

We have a very large selection of
Valves and Spares at the Lowest
Possible Prices

We have a Large Selection of used but
perfect C.R. Tubes. Every Tube carries
a 6 week guarantee. Callers can see picture
on premises.

9"	£4 0 0
12"	£6 0 0
15"	£8 10 0

Post, Packing and Insurance, 10/-

URGENTLY WANTED


COMMUNICATION RECEIVERS TEST
EQUIPMENT. RADIOS—and TELE-
VISION SETS, TAPE RECORDERS.
Best Prices Given

Phone or Call

★ TELETRON SUPER INDUCTOR COILS ★

Type HAX selective crystal diode coil, as
specified for the "Paragon" Tape Recorder,
3/-; HAX L (LW), 3/6. Dual wave TRF coils
type A/HF with adjustable iron dust cores,
matched pairs, 7/- (as illustrated). Type
WA5 for the "R.C. Simple Wobbulator,"
4/- each. Complete range of superhet coils,
I.F. transformers, wavetraps, etc., etc., 3d.
stamps for complete list and circuits. All types
available from leading stockists.

TELETRON FERRITE ROD AERIALS

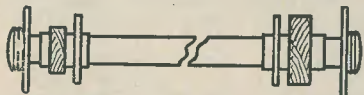

Wound on high permeability Ferroxcube rod.
No external aerial required. Full sensitivity.
Reduces static and whistles. Extremely select-
ive. Simply fitted as replacement for Ae. coil
or frame aerial. Ideal for battery portable
receivers.

Medium wave type FRM, 4" x $\frac{5}{16}$ " ... 8/9
Dual wave type FRD, 8" x $\frac{5}{16}$ " ... 12/9

THE TELETRON CO LTD
266 NIGHTINGALE ROAD · LONDON · N9
HOW 2527

Trade enquiries to sole distributor
S. Mozer, 95 Kendal Ave. N18 EDM 7707

HANNEY of BATH offers

OSRAM 912 Erie resistor-pot, kit with ceramic tube
resistors, very highly recommended, 29/6; Lab resistor
kit, 32/4; T.C.C. condensers, 55/-; PARTRIDGE Com-
ponents, with loose lead terminations, Mains trans., 44/-;
Smoothing Choke, 29/6; Output trans., 76/9. Price
includes Partridge carriage-packing charge. Printed
panel, 14/6. W.B. chassis, 28/6. DENCO 16 S.W.G.
Ali-Chassis with beautiful Bronze Front Panel, 21/-
(Printed). S.A.E. List.

MULLARD 5 VALVE, 10 WATT AMPLIFIER;
T.C.C. Condensers, 45/-; Erie resistor-pot kit, 37/6;
Elstone Mains trans., 36/-; Elstone Output trans., 45/-
(both types); Denco chassis, 14/6. Small parts as per
our list. Matched pairs of valves are available for both
the above designs.

COILPACKS. DENCO, CP4/L and CP 4/M, 33/4;
CP 3/70 pf and CP 3/550 pf., 42/8. OSMOR "Q" HO,
48/-; LM, 40/-; Batt., 50/-; TRF, 40/-; HF stage for
HO pack, 20/-; ETA 4-Station pack, 43/8.

WIDE ANGLE COMPONENTS. ALLEN. Teiking
Chassis, 50/-; Coils (TK & Super-Visor), 44/6; LO
308, 40/-; FO. 305, 21/-; DC. 300c., 39/6; FC. 302, 31/-;
GL. 16 & 18, 7/6 each; SC. 312, 21/-; AT. 310, 30/-;
OP. 117, 9/-; BT. 314, 15/-; DENCO Chassis Magna-
view, 37/6; Chassis, Super-Visor, 51/6; Coils (TK &
Magnaview, 41/2; WA/DCA1, 43/-; WA/FCA1, 31/-;
WA/LC1 and WCL, 7/6 each; WA/FMA1, 21/-;
WA/LOT1, 42/-; WA/FBT1, 16/-). Send 6d. stamps
for our General List of components for Viewmaster,
Soundmaster, Williamson Amplifier, Teiking, Magna-
view (Brimar & English Electric large screen TV),
Super-Visor, Mullard Universal, Close tolerance Silver
Micas, etc., etc. Please add 2/- postage to orders under
£3.

L. F. HANNEY

77 LOWER BRISTOL ROAD BATH
Telephone 3811

TELEKIT SUPPLY

CHANTRY LANE
BROMLEY · KENT

When ordering, please mention
RADIO CONSTRUCTOR and enclose 6d. postage

VALVES		Guaranteed			
1B24	35/-	6BE6	6/-	9D2	5/-
1L4	5/6	6BR7	8/6	11D3	6/-
*1LN5	3/-	6BS7	7/-	*12A6	5/-
1S5	6/-	6BW6	6/6	12AT6	7/6
1T4	6/6	6CH6	6/6	12BE6	6/6
1U5	6/-	6J5	5/-	*1299	5/-
3V4	6/6	6K7	4/-	15D2	4/-
6AM6	6/-	6U5	6/-	EF50	5/-
6AQ5	8/-	6X4	6/6	OZ4	4/-
6AT6	7/6	6X5	7/-	TT11	6/-
6A8	8/-	7D5	6/-	13D1	7/-
6B8	6/-	7D8	6/-	50C3	8/-
W77	5/-	5763	8/-		

Valves marked * Slightly Soiled

NEW RETAIL SHOP NOW OPEN
AT 104 HIGH STREET BECKENHAM KENT

Telephone BEC 3720

SMALL ADVERTISEMENTS

continued from page 637

TRADE

BLUEPRINTS. High Gain 10 Metre Converter, with
a de-luxe circuit comprising EF91 RF stage, ECC91
double triode mixer and oscillator, EF92 IF amplifier,
with stabilised voltage supply via a 7475, 1s. 8d. post
free with full instructions. Data Publications, 57
Maida Vale, London, W.9.

KENDALL AND MOUSLEY LTD. Manufacturers of
Laboratory Equipment, chassis and instrument cases,
also suppliers of B.V.A. valves. Radio and TV
components. 18 Melville Road, Birmingham 16.

COILS, COILS, COILS. We can supply coils for all
frequencies, RF Chokes, Filters, etc., Coils wound
to specification—send details for estimate. Send SAE
for circuits and data. The Teltron Co., 266 Nightin-
gale Road, London, N.9.

I.P.R.E. PUBLICATIONS. 5 730 Alignment Peaks for
superhets, 5s. 9d. Sample Copy *The Practical Radio
Engineer*, 2s. Membership examination particulars,
1s. Syllabus of TV and Radio Courses free and post
free. Secretary, I.P.R.E., 20 Fairfield Road, London,
N.8.

FREE! Brochure giving details of Home Study
Training in Radio, Television, and all branches of
Electronics. Courses for the hobby enthusiast or
for those aiming at the A.M.Brit.I.R.E., City and
Guilds, Telecommunications, R.T.E.B., and other
professional examinations. Train with the College
operated by Britain's largest Electronic Organisation,
moderate fees. Write to E.M.I. INSTITUTES,
Postal Division, Dept. RC28, E.M.I. Institutes,
London, W.4.

MEDICAL BOOKS. In addition to radio publications,
you can obtain from us the following popular works
on health subjects. *Smoking and Cancer*, 2s. A com-
prehensive discussion on this important subject. *So
You're Grown Up Now*, 1s. Personal information for
the Teen-ager. *So You're Expecting a Baby*, 9d. A
most helpful book for the young Mother-to-be.
Please add 2d. for postage. Data Publications, Ltd.,
57 Maida Vale, London, W.9.

OSMOR—for efficient coils, coilpacks, etc. Send 5d.
stamp for FREE circuits and lists. Dept. RCC,
Osmor Radio Products, Ltd., 418 Brighton Road,
South Croydon, Surrey. Telephone Croydon 5148/9.

JOIN THE ISWL. Free services to members including
QSL Bureau, Translation, Technical and Identifica-
tion depts. DX certificates, contests and activities
for the SWL. Monthly magazine "MONITOR"
duplicated, containing articles of general interest to
the SWL and League members, 12s. 6d. per annum,
post free. ISWL HQ., 86 Barringer Road, London,
N.10.

YOUR OWN tape recording transferred to disc.
Queensway Recording Studios, 123 Queensway, W.2.
Bay 4992.

RADIO STETHOSCOPE signal tracer as probe unit
originally described in *Radio Constructor*. Enabling
easier servicing or students practical aid. 10s. 6d.
with instructions, post 6d. SAE illustration, etc.,
Wilkinson, 42 Frances Road, Windsor, Berks.

BAND III TV Aerial, for service area only, indoor type,
comprising two rod elements and junction box, 7/6d.
post 6d. F.M.: 8/3d. plus 6d. Wireless Marketing Co.
(Supplies) 29 Praed St., London W.2.

FRANKLIN & HALL do not regret that they do
not deal with ex-Govt. or manufacturers' surplus
equipment. All items are guaranteed BRAND NEW
and orders sent by registered post.

FREQUENCY MODULATION—Denco feeder
unit. Complete set of components (except valves)
exactly as specified, £5 5 0. Denco technical bulletin
issued free with complete kit, or send 1/6 for bulletin
and price list of individual components.

OSRAM 912 AMPLIFIER components. Set of all
components except valves and speaker, £14 10 0.
Osram instructional book issued with above, or send
3/6 for book and price list of individual components.
SOUNDMASTER TAPE RECORDER components.
Constructional details, 6/6. Price list of individual
components free.

FRANKLIN & HALL (Mail Order
Department)
371 HAVANT ROAD FARLINGTON
PORTSMOUTH HANTS

OUR NEW

GOVERNMENT SURPLUS CATALOGUE No. 12

containing over 400 items, price 1/6 post free.
2/6 overseas seamail

ARTHUR T. SALLIS (R.C.)
93 NORTH ROAD BRIGHTON
SUSSEX Telephone BRIGHTON 25806

H.A.C. SHORT-WAVE EQUIPMENT

Suppliers for over 18 years of Radio S.W. Receivers of Quality
One-Valve Kit, price 25/-; Two-Valve Kit, price 50/-.
Improved designs with Denco coils. All kits complete
with all components, accessories and full instructions.
Before ordering, call and inspect a demonstration
receiver, or send stamped addressed envelope for
descriptive catalogue.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

GUARANTEED — Over 3,000 in Stock VALVES

6AM6, 6C4, EF92, 6AL5, EAC91, 6J6, 5/-,
12AT7, 12AX7, 6AK5, 6F33, EC91, EL91, 6SN7, 6SL7,
6SK7, 6SJ7, R10, 6BA6, 6F17, 6CH6, 6BW6, 7/6,
12AU7, 2D21, 9/-

A. A. W. SKILLMAN
74 FRANCHISE STREET · WEYMOUTH


HIGH FIDELITY

COMPONENTS IN STOCK FOR THE
MULLARD 5-10 AMPLIFIER circuits 2/6
OSRAM 912 AMPLIFIER circuits 3/6
DENCO FM TUNER circuits 1/6

Price lists available on request

J. T. FILMER MAYPOLE ESTATE
BEXLEY · KENT
Telephone BEXLEYHEATH 7267

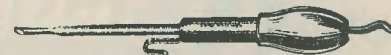ADCOLA (Regd. Trade Mark) SOLDERING INSTRUMENTS



Reg. Design No. 860302 (British, U.S. and Foreign
Patents)

Designed for wireless assembly and
Maintenance

Supplied for all volt ranges from 6/7V to 230/250V
3/16" Dia. Bit Standard Model, 25/6
Sole Manufacturers ADCOLA PRODUCTS
LTD.

Sales Office and Works Cranmer Court
Clapham High St. London SW4 (MAC 4272)

REPANCO HIGH GAIN

*** COILS ***

Dual range miniature
Crystal Set Coil with
circuit, type DRX1 **2/6**

Dual range Coil with
reaction with 2 mains
and 2 battery circuits,
type DRR2 **4/0**

Matched pair Dual Range T.R.F. Coils
with reaction; with battery and mains
circuits, type DRM3 **8/0 Pr.**

Standard I.F. Transformers, type SE, $1\frac{1}{2}'' \times 1'' \times 2\frac{1}{2}''$, pre-aligned 465 k/c. **13/6 Pr.**

Miniature I.F. Transformers, type MSE, $1\frac{1}{2}'' \times 1\frac{1}{2}'' \times 1\frac{1}{2}''$, pre-aligned 465 k/c **12/6 Pr.**

Ferrite Rod Aerial, type FRI, long and
medium wave, complete with fixing
brackets **12/6**

- ★ All Coils wound on low loss formers
- ★ Individually tested and guaranteed

★ Post 3d. on all orders ★ Trade supplied

Distributed by

RADIO EXPERIMENTAL PRODUCTS LTD
33 MUCH PARK STREET COVENTRY
Telephone Coventry 62572



(Regd. Design)

Constructors bargains

CABINETS. Steel, lift-up lid, complete with panel (al), both grey sprayed; plain al chassis. Cabinet $8\frac{1}{2}'' \times 4'' \times 4\frac{1}{2}''$, ideal for test gear, small receiver, etc., **10/6**

COILS. Full Teletron range. Type A/D, dual-wave matched pairs, tuned anode R.F., reaction winding Det., 7/- pr. T.R.F. Ag/H.F., tuned grid and H.F. trans., with circuit (6K7, 6I7 6V6), 7/- pr. R.F. Mixer, Osc. coils, 10/30, 15/50, 60/220, 180/550, 750/2000m, 3/- ea. All-wave R.F. Chokes, 10mH, 2/6 ea. I.F. Whistle Filter, 450/500kc/s, 3/6. M.W. Filter, 200/350m., 6/-; 341/500m., 6/- Min. I.F. Trans., 465kc/s., 12/6 pr. Type HAX, triple wound for Xtal Set, circuit supplied, 3/- ea. Ferrite Rod Aerials, FRM, 180/550m., 8/9; FRD, 180/2000M., 12/9. Electronic Xtal coil, FX1, 3/6. FXI Choke, 3/6.

VALVES

1N5	10/-	6D6	7/6	ARPI2	2/6	PL80	11/6
1Q5	10/-	6H6	7/6	EF36	6/6	PL81	11/6
1R5	7/-	6K7M	6/-	EF50	4/6	PY81	10/-
3Q5	10/-	6K8	8/6	EF80	10/-	PX4	11/-
3V4	7/-	6V6G	7/-	EF91	6/-	T41	10/6
5U4	8/-	25L6	9/-	EY51	11/-	U22	8/-
5Z4M	10/-	80	9/-	OZ4	4/6	954	4/-

TV TUBES

9", £4; 12", £6; 16", £8 10s. All tubes guaranteed. Picture tested on premises. Carriage and insurance 10/-

AC Radio-Gram chassis, all-wave, complete with all valves, new and boxed, 5 valve, £10; 7 valve push-pull output, £12 10s. Carriage on each 6/-.

TV & FM AERIALS. See our small advertisement.

Postage: under 10/- add 6d.; £1 add 3d. Over £1 free.

Wireless Marketing Co. (Supplies)

29 PRAED STREET LONDON W2
Established 1926 Telephone PAD 1907

TELETRON FERRITE ROD AERIALS

Wound on high permeability Ferroxcube rod and designed for use with 500pF (max.) tuning condenser. Nominal inductance for type. F.R.M. 165, u/h. Q at 1Mc. 185. Waveband 550kc/2Mc., 8/9. FRD, 2.2MH. Waveband 150kc/2Mc/s. LW and MW, 12/9. 3d. postage.

THE TELETRON CO LTD

226 NIGHTINGALE ROAD . LONDON N9

Telephone HOW 2527


EVERYTHING for the AEROMODELLER and RADIO ENTHUSIAST

We stock all brands of Kits, Engines, Accessories and Radio Spares, including parts for the "Aeromodeller" Transmitter and Receiver. So why not take advantage of our famous 48 hour Service!

TO ORDER BY POST cash with order or C.O.D. Add postage: under 10/-, 1/-; up to 25/- add 1/4; up to 40/- add 1/8; over 40/- Free.

Send for our NEW 40-page CATALOGUE
Price 1/-

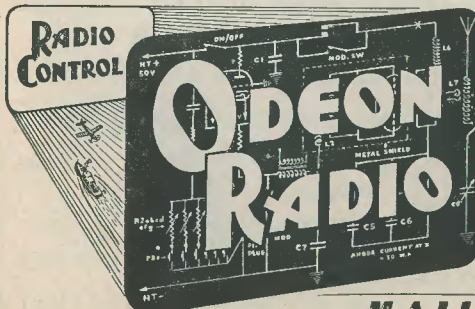56 COLLEGE ROAD : HARROW : MIDDX
Telephone HARrow 5778



MAIL ORDER SERVICE

THE "FULL-TONE" AMPLIFIER

We know that we are offering excellent value for money in the completely-drilled chassis which we have had manufactured for constructors of the "Full-Tone" Amplifier. These chassis are superior to the sort of thing normally offered on the home-constructor market, because they are precision made in heavy-gauge mild steel, and are finished in *hammered bronze* enamel. Use one of these chassis, and your amplifier will have that beautiful Custom-Built look that everyone admires.

The Chassis 7/6
Three tag-strips, as specified 1/-
(Plus 10d. p.p. for chassis, or chassis and tag-strips)

"HOME CONSTRUCTORS' HANDBOOK"

published by RODING LABORATORIES

This famous handbook is now available in the NEW 1955 edition. It contains 22 tested circuits, complete with descriptions, constructional details, full parts lists, etc., etc. Also contains hints, formulae, data. Circuits include superhets, communications receiver, oscilloscope, signal tracer, tape recorder, amplifiers, beginner's receiver, and many more items of gear. And the book is backed by Roding Laboratories, who are so well known for their quality home-constructor products. This 70-page book represents unbeatable value at 2s. 6d. (plus 3d. postage and packing). Order now and take immediate advantage of the wealth of information it affords.

DATA BOOKS

We have available the latest editions of all Radio Books by Data Publications. Standard Prices.

FIRST ON THE MARKET!

Wind your high-Q SW, TV, FM coils with *genuine solder-through* wire. You don't have to clean the wire—the enamel becomes flux at soldering temperatures. *This is the real thing!*

At present, 26 s.w.g. only.

Price: 1d. per yard. P.P. 3d. on all orders.

R. DAVIES 54 NEWTON ROAD · MUMBLES · SWANSEA

MAIL ORDER ONLY—NO C.O.D.

YOU CAN RELY ON US

We specialise **ONLY** in radio and electronic components, a comprehensive stock of which are held by us, to supply Government, educational and commercial laboratories. Can we be of some help to you, the experimenter and constructor? ?

Here are a few of our many stock lines—

Tapped Volume Controls, $\frac{1}{2}$ mg, $\frac{3}{8}$ mg, 1mg, 7/6 each; Linear, $\frac{1}{2}$ mg, $\frac{1}{4}$ mg, 1mg, 6/6; Surplus Stock Potentiometers, less switch, 2/3; with, 4/3; D/P, 5/-; midget, wirewound, preset, etc., in stock.

All J.B. Scales and Gangs. Full vision, 13/9; SL8, 27/6; SL5, 26/-; 3-gangs in .0003 and .0005, 18/3; Single gang .0005, 9/-; Twin midget gang, covered, 11/-.

Bulgin Plugs, Sockets, Panel Lights, etc. Belling-Lee Co-ax. Plugs, 1/3, Sockets, 1/2. Plugs, Sockets, etc. Resistors, 10 ohms to 15 mgs in $\frac{1}{4}W$, $\frac{1}{2}W$, 4d.; 1W, 8d.; 2W, 1/4; midget $\frac{1}{2}W$ 'T' type, 6d.; High stability 2% 100-2 megs, 1/6 each; wirewound (green vitreous), 33 ohms to 10K, 10 watts Max., 2/- each.

Over 200 T.C.C. types of Condenser. 189 types of Hunts. Electrolytics new and surplus. 10,000 surplus Valves plus large stock BVA Valves.

1% Silver Micas, 1.5pF to 100pF, 1/-; 100pF to 280pF, 1/2; 300pF to 500pF, 1/4 515pF to 815pF, 1/6; 1,000pF to 5,000pF, 2/6.

COILS.—COMPLETE RANGE OF DENCO, WEYMOUTH, WEARITE, OSMOR, R.E.P., DENCO F.M. UNIT PARTS, '912' PARTS, MULLARD '510' PARTS—ALL TAYLOR, AVO INSTRUMENTS IN STOCK, CELESTION, ROLA, ELAC, W.B., WHARFEDALE, GOODMANS SPEAKERS.

Send now for our Supplementary Winter List with H.P. Terms—Quotes S.A.E. Please. Postage extra.

Next to South Ealing Tube Station. 65 Bus.

82 SOUTH EALING ROAD
LONDON W5 Telephone EAL 5737

RADIO SERVICING CO