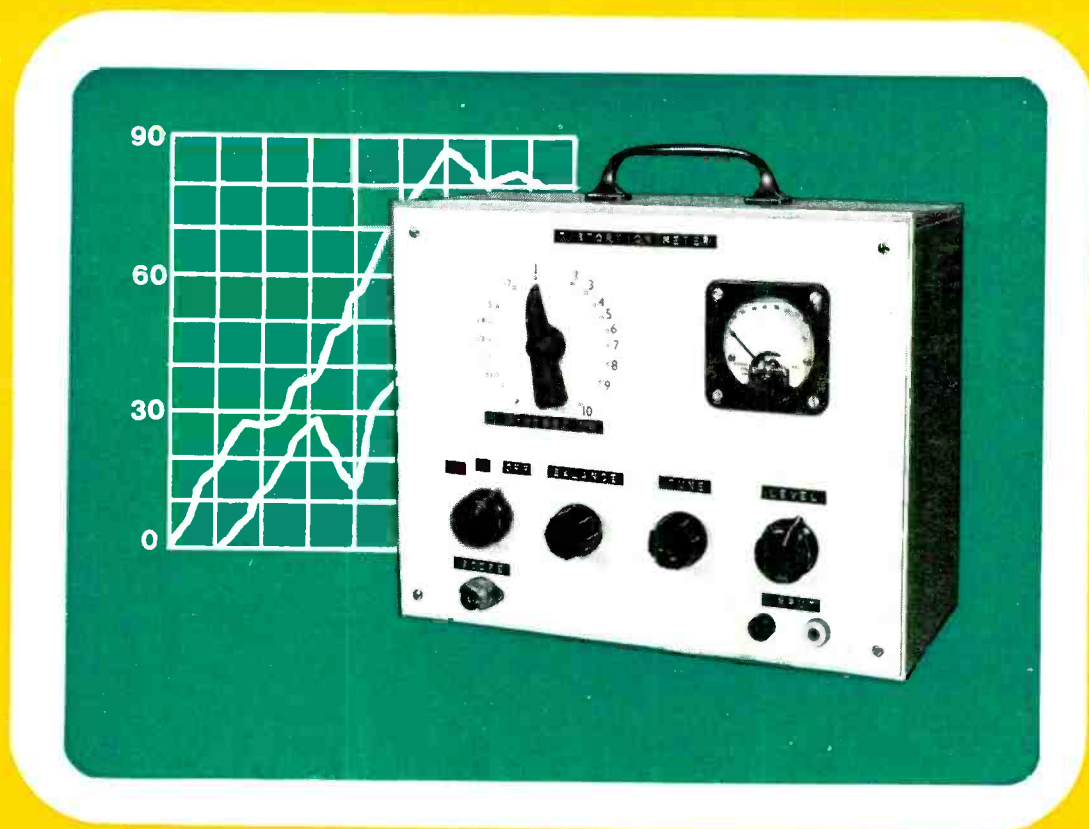


THE RADIO CONSTRUCTOR

Vol. 23 No. 10

MAY 1970

3/6



SOLID-STATE DISTORTION METER

A simple design measuring directly, percentage distortion of A.F. amplifiers over the range 0.2% to 10% at 1,000Hz. Plans and Instructions inside



Special
IN THIS ISSUE

FREE INSIDE
Detachable Plans
for above Meter

EXCLUSIVE
Motoring
Offer

AMATRONIX LTD.

396 Selsdon Road,
South Croydon,
Surrey, CR2 0DE

MAIL ORDER ONLY. PROMPT SERVICE.
Orders over 10/- UK post paid. Discounts:
Orders over £3, 10%; over £10, 15%.

NEW & PERFECT TRANSISTORS

AD161-2	12/-	HK041	2/6	2N3707	3/6
AF239	10/-	HK101	2/-	2N3794	3/-
B5000G	11/3	HK601	2/6	2N3983	6/6
BD121	18/-	I544	1/4	2N4058	4/-
BC107	3/-	SF115	3/-	2N4285	3/-
BC168	2/3	TI407	6/6	2N4289	3/-
BC169	2/6	TI560M	4/8	2N4291	3/-
BF167	5/3	TI561M	4/11	2S8187	2/-
BF178	9/-	2N706	2/7	2S8405	5/-
BF225	5/-	2N2926G	2/6	2SD72	5/-
BFY51	4/6	2N3702	3/-	40468A	7/6
GET693	1/3	2N3704	3/6		

RECTIFIERS:

800piv, 500mA Si. IS557, 3/-; 50piv, 100mA, 1/- Submin. Selenium Bridge, 30Vrms, 150mA dc, 3/6; Contact-cooled Sel. Bridge, 30Vrms, 700mA dc, 6/-; Silicon Bridge, 80Vrms, 1Adc, 10/- All new and perfect.

NEW!

"IDENTICAL RESONATORS": new Brush Clevite Transfilters for do-it-yourself ceramic i.f. filters. Four of these plus seven fixed capacitors give razor-sharp selectivity to superhets with 455kHz i.f. Kit of 4 resonators and all capacitors, plus notes on use, 35/- Single resonators, 10/- each, 4 for 30/-

"R.C." MILLIVOLTMETER (Jan., p. 342). Our AX10 Printed Circuit accommodates the main part of the circuit (not TR1). With layout drawing and hints, 15/-

COMPONENT KITS

AMPLIFIER PACKAGES, Reliable and efficient, and still far cheaper than i.c.'s!

AX2	9V, up to 300mW	12/6
AX3	9V, up to 800mW in 8 ohms	22/6
AX4	24V, 5W, 8 ohms, 3W, 15 ohms	30/-
AX5	12-15V, 3W, 3-5 ohms. NEW!	35/-

CAPACITORS

Polystyrene: 160V, small, low-loss, tol. 1pF or 2 1/2%. New prices: 10-1500pF, 1/-; 2200-22,000pF, 1/6. In stock: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 560, 680, 820, 1000, 1500, 2200, 3300, 4700, 6800, 8200, 10,000, 15,000, 22,000pF. Miniature Metallised Polyester: .01uF, 8d; .1uF, 10d; .22uF, 1/- 250V wkg. Tuning: 300pF max. Jacksons Dilemin sub-min single tuner, 10/-.

RESISTORS

Carbon Film, 1/4W, miniature, low noise. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82Ω and so on to 10M. Tol. ± 5% to 1M, 10% above 1M. All 3d. each. Carbon Skeleton Presets. 5ubmin., vertical, linear, 100mW. 50, 150, 500Ω and so on to 1.5M. Egen Type 467, 1/6 each. Volume Control, 10K log. with d.p. switch and long aluminium spindle with flat. Standard size, Egen, 5/6 each.

R. F. CHOKES. Repanco: CH1, 2.5mH, 2/6; CH2, 5mH, 3/-; CH3, 7.5mH, 3/-; CH4, 10mH, 3/-; CH5, 1.5mH, 2/6. All small, ferrite-cored.

FERRITE RODS: 4in. or 4 1/2in. x 1/2in., wound for MW (300pF), 5/-; unwound, 2/-; oval, unwound, 2 x 1/2 x 1/2in., with data, 2/6.

TRANSFORMERS, MINI. A.F.: Eagle LT700, 1200Ω c.t. to 3Ω, 200mW, 5/-; Repanco TT47 driver for single ended push-pull, 4.5 to (1) + (1), 6/-.

TELESCOPIC AERIALS: 7 1/2in. opening to 47in., 9/-.

BATTERY HOLDER BH2 for two 1.5V pen cells, with snap connector, 2/6.

EARPIECES, all 3.5mm plugged, crystal, 4/9; magnetic, 8Ω, 2/6.

'GEN' GALORE!

Regular customers know that we supply really practical data sheets with our mains transformers, component kits, ceramic resonators, f.e.ts, i.c.s, etc. All part of the normal Amatronix service.

BUILD A MINI MAINS PACK



Components as shown, and hints 17/6.

Mini Mains Transformers 30x30x37 mm

MT7	7-0-7V	120mA	13/6
MT9	9-0-9V	80mA	12/6
MT12	12-0-12V	50mA	13/6

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	2s. 6d.
DTB4 Transistor & Valve circuitry for D.P. Coils	2s. 6d.
DTB9 Valve Type Coil Pack Application circuitry	2s. 6d.
MD.1 Decoder Circuitry for Stereo Reception	4s. 0d.

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers.

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast, modern* way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING**. The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book — 'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 370B, Aldermaston Court, Aldermaston, Berkshire.

To: B.I.E.T., Dept. 370B, ALDERMASTON COURT, ALDERMASTON, BERKS.

I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 164-page book.

name

address

age

POST THIS COUPON NOW!

BI-PAK=LOW COST IC'S

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these **Exclusive Low Prices**. T.T.L. Digital SN 74N Series fully coded, brand new to manufacturers specifications. Dual In-Line plastic 14 & 16 pin packages.



BI-PAK ORDER NO.	DESCRIPTION	PRICE	AND QTY.	PRICES
			1-24	25-99 100 up
BP 00 = SN 7400N	Quad 2-Input NAND GATE		6/6	5/6 4/6
BP 01 = SN 7401N	Quad 2-Input NAND GATE - OPEN COLLECTOR		6/6	5/6 4/6
BP 04 = SN 7404N	HEX INVERTER		6/6	5/6 4/6
BP 10 = SN 7410N	Triple 3-Input NAND GATE		6/6	5/6 4/6
BP 20 = SN 7420N	Dual 4-Input NAND GATE		6/6	5/6 4/6
BP 30 = SN 7430N	Single 8-Input NAND GATE		6/6	5/6 4/6
BP 40 = SN 7440N	Dual 4-Input BUFFER GATE		6/6	5/6 4/6
BP 41 = SN 7441AN	BCD to decimal decoder and N.I.T. Driver	22/6	20/-	17/6
BP 42 = SN 7442N	BCD to decimal decoder (TTL O/P)	22/6	20/-	17/6
BP 51 = SN 7450N	Dual 2-Input AND/OR/NOT GATE expandable	6/6	5/6	4/6
BP 53 = SN 7453N	Single 8-Input AND/OR/NOT GATE - expandable	6/6	5/6	4/6
BP 60 = SN 7460N	Dual 4-Input - expandable	6/6	5/6	4/6
BP 70 = SN 7470N	Single JK Flip-Flop - edge triggered	9/-	8/-	7/-
BP 72 = SN 7472N	Single Master Slave JK Flip-Flop	9/-	8/-	7/-
BP 73 = SN 7473N	Dual Master Slave JK Flip-Flop	10/-	9/-	8/6
BP 74 = SN 7474N	Dual D Flip-Flop	10/-	9/-	8/6
BP 75 = SN 7475N	Quad Bistable Latch	11/-	10/-	9/6
BP 76 = SN 7476N	Dual Master Slave Flip-Flop with preset and clear	11/-	10/-	9/6
BP 83 = SN 7483N	Four Bit Binary Adder	26/-	22/6	20/-
BP 90 = SN 7490N	BCD Decade Counter	22/6	20/-	17/6
BP 92 = SN 7492N	Divide by 12 4 Bit Binary Counter	22/6	20/-	17/6
BP 93 = SN 7493N	Divide by 16 4 Bit Counter	22/6	20/-	17/6
BP 94 = SN 7494N	Dual Entry 4 Bit Shift Register	22/6	20/-	17/6
BP 95 = SN 7495N	4 Bit Up-Down Shift Register	22/6	20/-	17/6
BP 96 = SN 7496N	5 Bit Shift Register	24/-	21/-	18/6

Brand new. Full to manufacturers specification.

BP 709 OPERATIONAL AMPLIFIER

Dual-in-line 14 pin package. = SN 72709 and similar to MIC 709 & ZLD 709C. PRICE EACH 1-24 25-99 100 up

10/6 9/- 8/-

This is a high performance operational Amplifier with high impedance differential inputs and low impedance output.

INTEGRATED CIRCUITS

Manufacturers "Fall outs" - out of spec devices including functional units and part functional but classed as out of spec from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work, on testing some will be found perfect.

PAK NO.	PAK NO.
UIC 00 = 5 x 7400N . . . 10/-	UIC 50 = 5 x 7450 . . . 10/-
UIC 01 = 5 x 7401N . . . 10/-	UIC 53 = 5 x 7453 . . . 10/-
UIC 10 = 5 x 7410N . . . 10/-	UIC 72 = 5 x 7472 . . . 10/-
UIC 20 = 5 x 7420N . . . 10/-	UIC 74 = 5 x 7474 . . . 10/-
UIC 30 = 5 x 7430N . . . 10/-	UIC 75 = 5 x 7475 . . . 10/-
UIC 40 = 5 x 7440N . . . 10/-	UIC 90 = 5 x 7490 . . . 10/-
UIC 41 = 5 x 7441AN . . . 10/-	UIC XI = 20 x As'd 74's 30/-

Packs cannot be split but 20 assorted pieces (our mix) is available as Pak UIC XI. Every Pak carries our Bi-Pak Satisfaction or money back Guarantee.

Motorola Digital I.C.'s MDTL Dual In-line Package Price
Type MC 844P Expandable dual 4-input Nand Power Gate 10/- each
Type MC 845P Clocked Flip-Flop 15/- each
Full Data supplied with Units.

Data is available for the SN 74N Series of Integrated Circuits in booklet form. Price 2/6.

Please send all orders direct to our Warehouse and despatch department, postal address:

BI-PAK Semiconductors, P.O. BOX 6, WARE, HERTS.

Postage and packing add 1/- Overseas add extra for Airmail. Minimum order 10/- Cash with order please.

THE MODERN BOOK CO

TRANSISTOR, AUDIO AND RADIO CIRCUIT

For Radio Receivers, Radiograms, Record Players,
Tape Record Players and Hi-Fi Equipment

30s.

A Mullard Publication

Postage 1s.

Transistor Substitution Handbook
No. 19. 18s. Postage 1s.

Colour Television PAL System
by G. N. Patchett. 40s. Postage 1s.

Radio and Line Transmission, Vol. 3
by G. L. Danielson. 45s. Postage 1s.

Solid State Hobby Circuits Manual
by R.C.A. 17s. 6d. Postage 1s.

Transistor Manual
by General Electric Company. 21s.
Postage 1s. 6d.

SCR Manual
by General Electric Company. 25s. Postage 2s.

Transistor Transmitters for the Amateur
by Donald L. Stoner. 21s. Postage 1s.

110 Semiconductor Projects for the Home
Constructor by R. M. Marston. 18s. Postage 1s.

Practical Integrated Circuits
by A. J. McEvoy & L. McNamara. 18s.
Postage 1s.

Servicing with the Oscilloscope
by Gordon J. King. 28s. Postage 1s.

Hi-Fi in the Home
by John Crabbe. 40s. Postage 1s. 6d.

VHF-UHF Manual
by G. R. Jessop. 21s. Postage 1s.

Television Engineers' Pocket Book
by J. P. Hawker & J. A. Reddihough. 21s.
Postage 1s.

Questions & Answers Transistors
by Clement Brown. 10s. Postage 6d.

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2

Telephone PADDington 4185

Read all about building a —

DIGITAL PROPORTIONAL

6-CHANNEL RADIO CONTROL OUTFIT

in "RADIO MODELLER" magazine

● SPECIAL OFFER —


TWO ISSUES—Containing the 2-part article
on building up the Remcon "QUANTUM SIX"
six function digital proportional superhet
receiver and transmitter

for only 5/- (normally 7/-)

Send now, enclosing 5/- P.O. or cheque to:—

● RADIO MODELLER, (Dept. S.O.),
64 WELLINGTON ROAD, HAMPTON HILL, MIDDLESEX

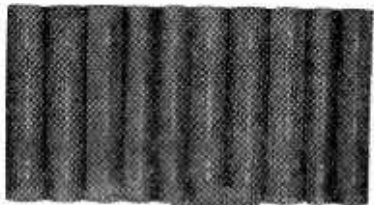BOUND VOLUME No. 22 of "The Radio Constructor" FOR YOUR LIBRARY



Comprising
800 pages
plus index

AUGUST 1968
to JULY 1969

PRICE 35/- Postage 4/6

Special discount of 10/- for regular readers

Just cut the heading from each month's contents page, including title and month of issue, and this will be sufficient evidence of readership to qualify for the discount.

Thus regular readers will still retain their copies for workbench use, while having a splendid bound volume containing issues in mint condition.

PRICE 25/- Postage 4/6

We regret all earlier volumes now completely sold out.

Available only from:-

Data Publications Ltd.
57 Maida Vale London W9


Never Built a Kit Before?

Why not prove how easy it is the HEATHKIT way.
Build one of these beginner kits.



Stereo Record Player

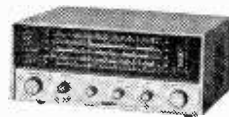Exciting sound; budget price. Kit: K/SRP-1.
£27-6-0 Carr. 5/-



Economy SW Receiver

World-wide reception, 1 to 30 MHz plus 550-1620 kHz. Kit: K/GR-64.
£24-16-0 Carr. 9/-




Deluxe Car Radio

Heathkit value; powerful output. Kit: K/CR-1 (less speakers).
£12-12-0 Carr. 5/-

Versatile Service VVM

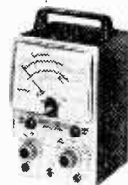7AC, 7DC, 7ohm ranges. Kit: K/IM-18U
£16-14-0 Carr. 5/-



'Severn' AM/FM Radio

Beautiful looks; luxury sound. Kit: K/Severn.
£18-18-0 Carr. 5/-

Portable VVM




For hobbyists - householders. Kit: K/IM-17.
£14-8-0 Carr. 6/-



Model Builders' Tacho

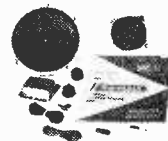Low cost; accurate. Kit: K/GD-69.
£11-0-0. Carr. paid



D.I.Y. Speaker Set

As SSU-1 (less cabinet). Kit: K/SCM-1. £6-10-0. Carr. 5/-

Many more kits in the FREE Catalogue

Please rush me a copy of your FREE Catalogue.

Name.....

Address.....

53/5

Post Code.....



A Schlumberger Company

DAYSTROM LTD.
Dept. 53/5
Gloucester GL2 6EE



IF YOU'RE BUYING A HOUSE

Mortgage Protection

is the best Policy for you

If you're buying your house with the help of a Building Society or a private loan, a "Yorkshire" Mortgage Protection Policy will take care of your outstanding payment in the event of your premature death. And, if you wish, you can arrange a Protection "Plus" Policy, which

gives you a substantial cash return at the end of the mortgage term. It costs so little yet means so much to your dependants. Leave them a home not a mortgage!

Please send for further details, without any obligation, of course.

THE YORKSHIRE INSURANCE COMPANY LIMITED

Becket House, 36-37 Old Jewry, LONDON, E.C.2.

It pays to be protected by a **General Accident** company

Please send me further particulars of the Mortgage Protection Policy

Name.....

Address.....

.....

.....

5304

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	3/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N711	10/-
AF115	3/6	2N1302-3	4/-
AF116	3/6	2N1304-5	5/-
AF117	3/6	2N1306-7	6/-
AF186	10/-	2N1308-9	8/-
AF139	10/-	2N3819	9/-
AF239	12/6	Power	
BFY50	4/-	Transistors	
BSY25	7/6	OC20	10/-
BSY26	3/-	OC23	10/-
BSY27	3/-	OC25	8/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/6
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/6
OC44	2/6	AD149	10/-
OC45	2/6	AUY10	30/-
OC71	2/6	2N3055	15/-
OC72	2/6	2S034	10/-
OC73	3/6	Diodes	
OC81	2/6	AA42	2/-
OC81D	2/6	QA95	2/-
OC83	4/-	OA79	1/9
OC139	2/6	OA81	1/9
OC140	3/6	IN914	1/6

ANOTHER SCOOP FOR BI-PRE-PAK

JUST RELEASED FROM STOCK, A.E.I. INTEGRATED CIRCUITS

These are brand new genuine surplus stocks, marked and guaranteed to full makers specification and not remarked rejects.

NE806A	Dual 4 1/P Expander TTL	7/-
NE808A	Single 8 1/P NAND Gate TTL	7/-
NE816A	Dual 4 1/P NAND Gate TTL	7/-
NE825A	D.C. Clocked J-K Flip-Flop TTL	17/6
NE840A	Dual 4 1/P Exclusive OR Gate TTL	7/-
NE855A	Dual 4 Power Gate TTL	7/-
NE870A	Triple 3 1/P NAND TTL	7/-
NE880A	Quad 2 NAND TTL	7/-
SP616A	Dual 4 NAND Gate DTL	7/-
SP631A	Quad 2 1/P Gate Expander DTL	7/-
SP670A	Triple 3 NAND Gate DTL	7/-
SP806A	Dual 1/P Expander TTL	7/-
SP808A	Single 8 1/P NAND Gate TTL	7/-
SP816A	Dual 4 1/P NAND Gate TTL	7/-
SP825A	D.C. Clocked J-K Flip-Flop TTL	17/6
SP840A	Dual 4 1/P Exclusive OR Gate TTL	7/-
SP855A	Dual 4 Power Gate TTL	7/-
SP870A	Triple 3 1/P NAND TTL	7/-
SP880A	Quad 2 1/P NAND TTL	7/-
NE500K	Video Amplifier	40/-
NE501K	Video Amplifier 40 MHz	40/-
NE806J	Dual 4 1/P Expander TTL	7/-
NE808J	Single 8 1/P NAND Gate TTL	7/-
NE816J	Dual 1/P NAND Gate TTL	7/-
NE825J	D.C. Clocked J-K Flip-Flop TTL	17/6
NE840J	Dual 4 1/P Exclusive OR Gate TTL	7/-
NE855J	Dual 4 Power Driver TTL	7/-
NE870J	Triple 3 1/P NAND TTL	7/-
NE880J	Quad 2 1/P NAND TTL	7/-
ST620A	J-K Flip-Flop DTL	17/6
ST659A	Dual 4 Buffer/Driver DTL	7/-
ST680A	Quad 2 NAND DTL	7/-

Suffix: A=DIP 14 lead K=10 lead TO.5
J1=Flat Pack

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries, .3 to .5V, .5 to 2mA.	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. output. Pair	10/-
B81	10	Reed Switches. Mixed types large and small.	10/-
B89	2	5SP5 Light Sensitive Cells. Light res. 400Ω. Dark 1MΩ.	10/-
B91	8	NKT163/164 PNP Germ. to -5. Equiv. to OC44, OC45.	10/-
B92	4	NPN Sil. Trans. A06=BSX 20, 2N2369. 500 MHz, 360 mW.	10/-
B93	5	GET113 Trans. equivalent to ACY17-21 PNP Germ.	10/-
B94	6	NPN Sil. Planar Epitaxial Trans. CS4 similar to BSY38 or BC108.	10/-
B96	5	2N3136 PNP Sil. Trans. TO-18. HFE100-300. IC.600mA. 200 MHz.	10/-
B98	10	XB112 & XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-
B99	200	Capacitors, Electrolytics, Paper, Silver Mica, etc. Postage on this pak 2/6.	10/-
H4	250	Mixed Resistors. Post & packing 2/-.	10/-
H7	40	Wirewound resistors. Mixed values. Postage 1/6.	10/-

FREE! Packs of your own choice up to the value of 10/- with orders over £4.

LOOK! TRANSISTORS ONLY 6d. EACH

TYPE A	TYPE B	TYPE D
PNP SILICON ALLOY TO-5 CAN Spec:- hFE 15-100. ICER at VCE=20V 1mA Max. These are of the 2S300 range which is a direct equivalent to the OC200-205 range.	PNP SILICON PLASTIC ENCAPSULATION Spec:- hFE 10-200 ICER at VCE=10V 1mA Max. These are of the 2N3702-3 and 2N4059-62 range.	NPN SILICON PLANAR PLASTIC PACKAGE Spec:- VCB 10v VCE 10v Ptot 500 mW hFE 50 min. Audio Preamplifier Transistor, similar to BC 113/4/5.

Return of the unbeatable P.1 Pak.

Now greater value than ever

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

P.1 PLEASE ASK FOR PAK P.1 ONLY 10/-
2/- P & P on this Pak.

NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits, Data & Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN, Sil. in TO-5 can.	10/-
B82	10	OC45, OC810 & OC81 Trans. Mullard glass type.	10/-
B83	200	Trans. Makers rejects. NPN/ PNP. Sil. & Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200. OA202.	10/-
B66	150	High quality Germ. Diodes. Min. glass type.	10/-
B86	50	Sil. Diodes sub. min. IN914 & IN916 types.	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN. PNP. equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7-Watt Zener Diodes. Mixed voltages.	10/-
H5	16	1 Amp. Plastic Diodes. 50-1000 Volts.	10/-
H6	40	250mW. Zener Diodes DO-7 min. Glass Type.	10/-

MAKE A REV. COUNTER for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for 20/- each any car.

FREE CATALOGUE AND LISTS for:- ZENER DIODES TRANSISTORS, RECTIFIERS FULL PRE-PAK LISTS & SUBSTITUTION CHART

MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.


P.O. RELAYS 8 FOR 20/-
Various Contacts and Coil Resistances. No individual selection. Post & Packing 5/-

SPECIAL OFFER
12 volt Stabilised Power Units
Input 110-250V. AC
Output 11-13V. Stabilised At 1 Amp.
Brand new Makers surplus at the unrepeatable price of **£5** each plus P & P 7/6

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

the BIG one...

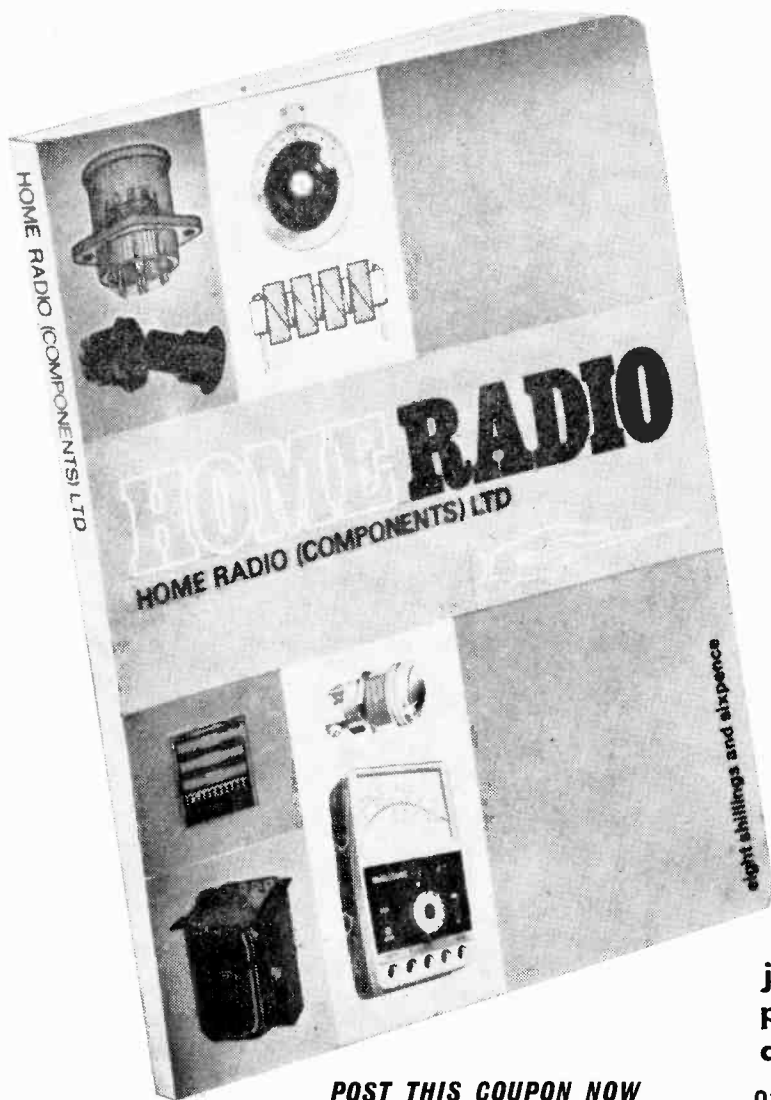

350
pages
8,000
components
1,500
illustrations

The HOME RADIO CATALOGUE – the complete and easy answer to the problem of tracking down components. This Catalogue really is a *must* if you are interested in Radio and Electronics. It is one of the largest ever compiled. Also, with each catalogue we supply a Book Mark giving Electronic Abbreviations, a Price Supplement and an Order Form. All for only 12/6 (8/6 plus 4/- P. & P.). In addition, every catalogue contains 6 vouchers each worth 1/- when used as indicated.

The price of 12/6 applies only to catalogues purchased by customers residing in the United Kingdom.

**just a
phone call
away**

01-648 8422



**POST THIS COUPON NOW
with cheque or P.O. for 12/6**

Please write your Name and Address in block capitals

Name.....

Address.....



HOME RADIO (Components) LTD., Dept RC,
234-240 London Road, Mitcham, Surrey CR4 3HD

And for users of our Catalogue . . .

**a CREDIT ACCOUNT SERVICE to
simplify and speed up your orders.**

You can now order components just by picking up a telephone any time of day or night, including Sundays. No need to bother with postal orders, cheques, registering envelopes, every time you make an order. Special prepaid envelopes and order forms are provided and only one postal order or cheque is required to settle the account each month . . . and no minimum invoice charge. So simple, 8,000 items just as near to you as your telephone. It's well worth the small deposit which enables you to use this Home Radio Credit Account Service. Write for more details or phone 01-648 8422.

THE RADIO CONSTRUCTOR

THE **Radio Constructor**



Incorporating **THE RADIO AMATEUR**

MAY 1970

Vol. 23 No. 10

CONTENTS

Published Monthly (1st of Month)
First Published 1947

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1970. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription 48s. (U.S.A. and Canada \$6) including postage. Remittances should be made payable to "Data Publications Ltd.". Overseas readers please pay by cheque or International Money Order.

Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. Queries should be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Letterpress.

ELECTRONIC SIREN MODULE	590
NEON-L.D.R. A.F. OSCILLATOR (Suggested Circuit No. 234)	593
SIMPLIFIED SOLID-STATE DISTORTION METER	596
CURRENT SCHEDULES	601
NEWS AND COMMENT	602
BBC WORLD RADIO CLUB	604
NOW HEAR THESE	605
INCREASING TRANSISTOR RADIO COVERAGE	606
HUBBLE BUBBLE - TOIL AND TROUBLE	609
QSX	610
THE "FETAFLEX 4" TRANSISTOR PORTABLE (Part 2)	611
C.R.O. BEAM SWITCHING UNIT	614
UNDERSTANDING TAPE RECORDING (Part 1)	621
RADIO CONSTRUCTOR MOTORING OFFER	628
ELECTRONIC CHRONOMETERS	629
IN YOUR WORKSHOP	634
CURRENT TRENDS	640
LATE NEWS	641
RADIO CANADA	641
LAST LOOK ROUND	641
RADIO CONSTRUCTOR'S DATA SHEET No. 38 (Abbreviations - A to L)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W.9.

The *Radio Constructor* is printed by Kent Paper Company Ltd, London and Ashford, Kent.

**JUNE ISSUE WILL BE PUBLISHED
ON JUNE 1st**

ELECTRONIC SIREN MODULE

by

P. L. MATTHEWS

A neat and simple oscillator circuit which produces an a.f. output whose frequency continually rises and falls

THE NEED OFTEN ARISES FOR A BUZZER OR ALARM bell to operate in conjunction with a burglar alarm or similar circuit, but it is difficult to obtain a device producing a really distinctive sound. The transistorised siren module to be described will admirably fulfil this need as it produces a warbling sound similar to that of an American police car siren. Both the pitch and change of pitch can be adjusted indefinitely by suitable choice of components, and a useful feature is the independent control of the rise and fall of the note. The siren, which is built on a small piece of Veroboard, employs four general purpose silicon n.p.n. transistors and consumes about 5mA from a standard 9 volt battery. It is designed to feed into a power amplifier with an input impedance of 10k Ω or more. The prototype was connected to a 9 volt transistorised amplifier module and a series resistor was added to attenuate the signal and increase the effective load impedance accordingly.


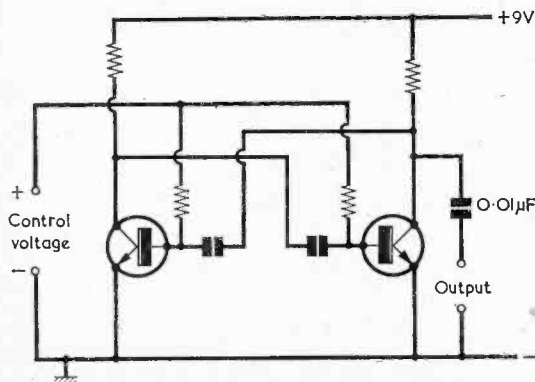



Fig. 1. The multivibrator shown here is capable of having its frequency of oscillation varied by alterations in control voltage. Virtually linear control of frequency is achieved for positive control voltages from 1 to 4 volts

In order to simulate the changing pitch of a siren, it is necessary to develop an audio oscillator whose frequency can be varied by alteration of a control voltage. Fortunately, this is not difficult to arrange and most simple oscillator circuits can be adapted quite easily. The author selected the multivibrator circuit shown in Fig. 1 as a basis for the siren because it has several advantages over apparently simpler circuits such as blocking oscillators and RC ladder circuits. One such advantage is an approximately linear variation of frequency against control voltage. A second advantage is the low loading imposed on the control voltage source, which enables the voltage to be obtained across a capacitor without significant discharge. This is important as it simplifies the remaining circuitry, avoiding the need for a buffer amplifier. It can be seen, therefore, that the circuit of Fig. 1 provides a convenient basis for the development of the siren, and the next step is to generate a suitable periodic sawtooth waveform to control its frequency.

It is difficult and unnecessary to design complex circuitry to obtain a pure sawtooth waveform, and a simple method, which nevertheless produces a satisfactory result, will next be described. The circuit of Fig. 2(a) depicts a capacitor C which, via a resistor R, can be alternately charged from a battery or discharged. Fig. 2(b) shows the voltage across C as a function of time when the switch is set to charge for 5 time constants and then set to discharge for a further 5. The time constant, in microseconds, is of course the product of C in microfarads and R in ohms, and is the time taken for C to charge to 63% of E or, after having been fully charged, to discharge to 37% of E. We require a circuit which will produce a voltage varying from

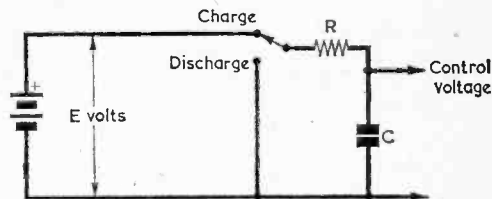


(a)

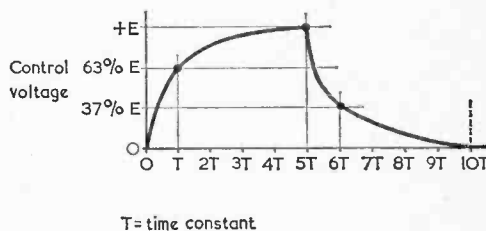

(b)

Fig. 2(a). One method of producing an approximately sawtooth waveform
(b). The waveform provided by the switching circuit. The switch is set to 'Charge' from zero to 5T, then returned to 'Discharge' from 5T to 10T

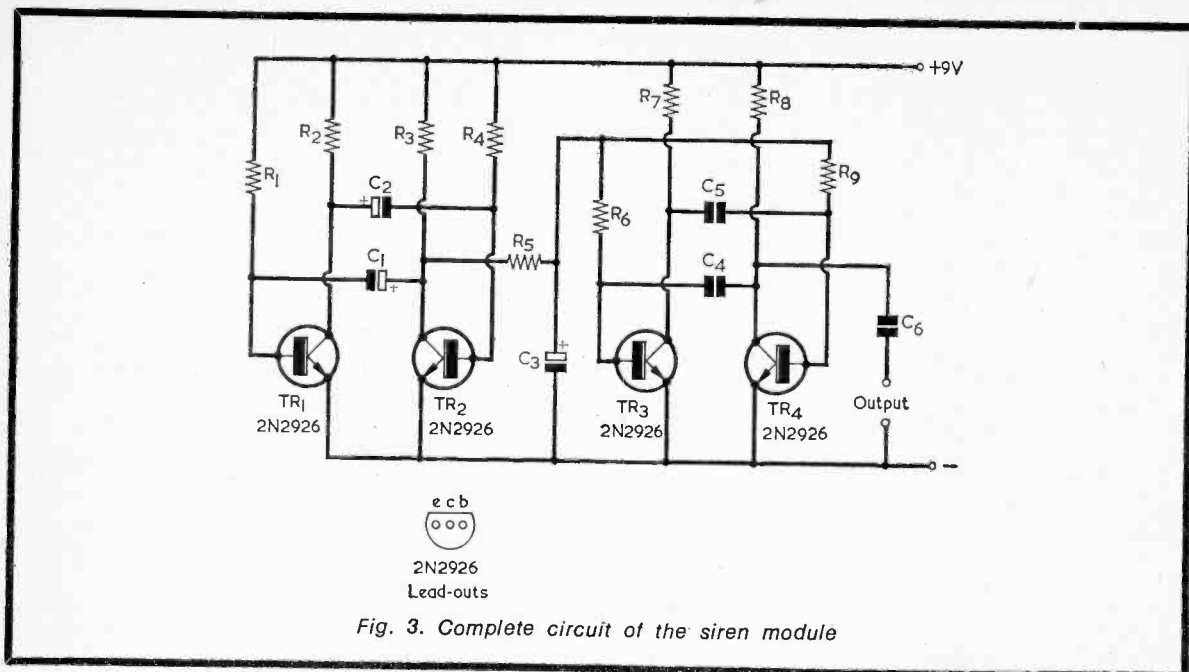

a minimum of 1 volt to about 4 volts to obtain reasonable control of multivibrator frequency. Since this circuit will be operated from a 9 volt supply it is obvious that the capacitor must be charged for somewhat less than the time constant. The siren is intended to produce a rising pitch for about 1 second, whereupon it follows that a time constant of about this magnitude will be needed. The mechanical switch must also be replaced by an electronic equivalent, and this can be a second multivibrator.

It was decided to have the duration of the falling pitch shorter than that of the rising pitch. This is obtained by adjustment of the coupling capacitors

in the controlling multivibrator so that their values are in the ratio 3:1.

The final circuit of the siren module is given in Fig. 3. It can be seen that TR1 and TR2 constitute the controlling multivibrator, with C1 controlling the duration of the falling pitch, and C2 the duration of the rising pitch. R5 and C3 serve to produce an approximate sawtooth waveform (with R3 entering

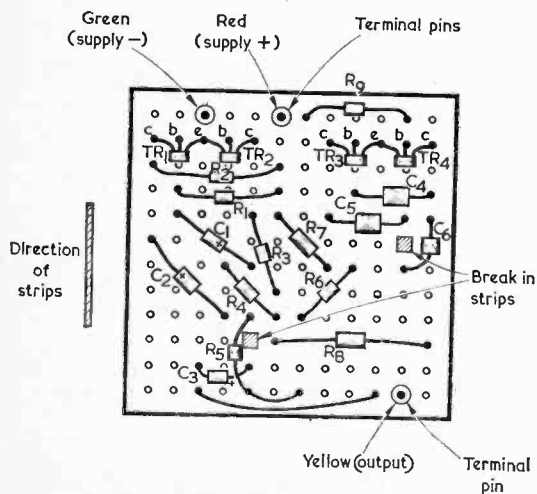


Fig. 4. The Veroboard assembly, as viewed from the component side. The terminal pin coded green provides one of the output connections in addition to the negative supply connection

COMPONENTS

Resistors

(All 10% 1/4 watt)

R1	56k Ω
R2	4.7k Ω
R3	4.7k Ω
R4	56k Ω
R5	4.7k Ω (see text)
R6	56k Ω
R7	4.7k Ω
R8	4.7k Ω
R9	56k Ω

Capacitors

C1	5 μ F miniature electrolytic, 10V wkg.
C2	16 μ F miniature electrolytic, 10V wkg.
C3	100 μ F miniature electrolytic, 10V wkg.
C4	0.0068 μ F, paper or plastic foil
C5	0.0068 μ F, paper or plastic foil
C6	0.01 μ F, disc ceramic

Transistors

TR1 - TR4 2N2926 (see text)

Miscellaneous

Veroboard, 0.15in. matrix, 12 x 12 holes
 3 Veroboard terminal pins
 Sleeving, solder, etc.

the charge circuit when TR2 is cut off), the waveform being applied to the "signal" multivibrator as already described. The output signal is taken from the collector of TR4 via C6 and may then be applied to the subsequent amplifier.

The transistors quoted are 2N2926, and it should be noted that this type has a maximum reverse base-emitter rating of 5 volts. As the reverse base voltage in the multivibrators approaches the supply voltage when the transistors cut off, there would appear to be a risk of breakdown. However, the question of using silicon transistors such as the 2N2926 in multivibrator circuits received an airing in the technical press some years ago, in which a leading semiconductor manufacturer was quoted as stating that all base to emitter limiting ratings are well below voltage breakdown. The prototype was run for several hours at 18 volts and no breakdowns occurred, and it would seem to be quite safe in practice to use 2N2926's in the present circuit with a 9 volt supply. In any event the choice of transistor is not critical and the constructor could employ silicon (or germanium) alternatives having a higher reverse base-emitter rating if so desired.

CONSTRUCTION

As mentioned earlier, the prototype was assembled on a square piece of Veroboard, this being of 0.15in. matrix and having 12 by 12 holes. It was cut from a larger sheet. Fig. 4 gives a view of the board as seen from the side on which the components are mounted. Three terminal pins of the type intended for use with Veroboard are fitted for battery and output connections. It will be found convenient to pass pieces of 1mm. plastic sleeving over the pins, these having different colours to assist identification later. In the diagram the battery negative pin is shown as green, the battery positive pin as red, and the output pin as yellow.

Construction is quite straightforward, it being necessary first to cut the board to size and make the two breaks in the copper strips, as shown. The pins and non-electrolytic capacitors can then be mounted, followed by the electrolytic capacitors and finally the transistors. Care should be taken to ensure that adjacent conductors, including metal transistor cases, do not come into contact with each other. Unnecessary heat due to excessive application of the soldering iron should also be guarded against, and the usual precautions taken when soldering the transistors.

CHECKING

After construction the siren module may be tested and checked. If the siren fails to function but is consuming a reasonable current, suspect the "signal" multivibrator and transistors TR3 and TR4. The normal collector voltage of these transistors will be in the region of 6 volts, varying in sympathy with the pitch. A high voltage reading indicates that no collector current is flowing. If the signal circuitry is functioning but the pitch is steady, check the "control" multivibrator and the coupling circuit.

To provide a narrower pitch range than in the prototype, the value of R5 may be increased to slow down the rate of charge and discharge of C3.

POLES

May and poles are traditionally lumped together, although it is many years now since such an erection, with its attendant colourfully dressed dancers and intertwining ribbons, have been seen on our village green—and more's the pity! It is said that tradition dies hard, but this one, together with its charming ceremony of crowning the equally charming May Queen, seems in the main to have almost passed softly away unnoticed. Perhaps one reason for this sad state of affairs is the difficulty of obtaining, locally at any rate, a wooden pole of suitable size.

Having worked up an over-sized enthusiasm to get cracking on Top Band, the obvious prerequisite to achieve anything like successful county chasing was a 132ft. skywire and it follows that this should have some means of support. It all seemed so simple at the time.

Parking unobtrusively beside a ramshackle shed, there issued from this the rending sound of bandsaws, whisks of sawdust and an individual whose crowning glory was a battered bowler hat that had obviously seen better days. "Wotcher want, mate," he growled through sawdust encrusted lips. "An aerial pole," I replied, hopefully. "Huh, yer won't get one of them things 'ere, but yer can try the orifice." He grimaced, jerked his grimy thumb in the direction of a nearby shed and derisively added: "They fink they know it all there, that lot do," with which parting shot Bowler Hat turned and vanished into the cloud of sawdust from whence he came.

The "orifice" proved to be a maze of interconnecting sanctums and finally, after brusque but poleless encounters with the denizens of two of them, the final arbiter of the pole quest was contacted. Located behind a desk of gargantuan proportions and visibly ensconced on a high stool reminiscent of Dickensian times, the worthy occupant of this "orifice" ruminated over my request at some length. I quickly discovered that everything about this character was long-suffering. Getting off his high stool, he towered above the dusty floor by at least 7ft.! Frowning down at me rather pityingly, I thought, he educated me in measured sonorous tone. "People don't use wireless poles these days," he said incredulously, "they use transistor sets". With the awful finality of that technical logic I found myself stumped! How could I explain the long and short of it to one so elevated in outlook?


From the ensuing lecture delivered by the High Priest of the Woodyard I gathered that a wood pole *could* be ordered from London but it *would* be an expensive transaction as a one-off affair. "Better get an ally pole from your TV aerial erector," Lofty advised. Stretching to my full height and gazing direct into his midriff I apologetically replied that I would, and was sorry to have bothered him with such a trivial matter.

Returning to the car brought a final encounter with Bowler Hat. "Ow jer git on, mate?", he enquired. "I didn't," I replied disconsolately. "I toldjer, didn't I," was the triumphant rejoinder. How was I to know that wood poles for aerials were unobtainable? Presumably this also applies to Maypoles!

C.W.

NEON-L.D.R. A.F. OSCILLATOR

by G. A. FRENCH

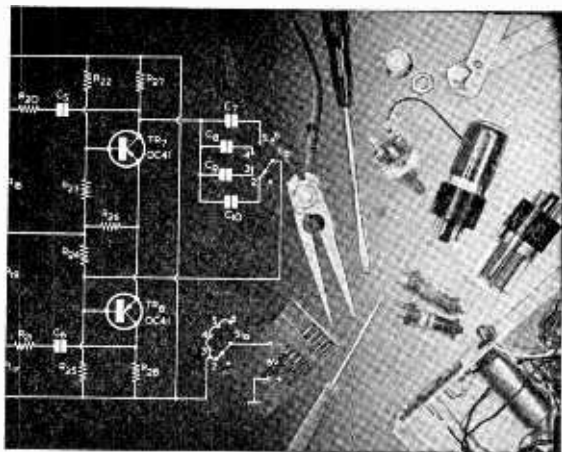

IN ELECTRONIC WORK WE TEND to fall into the habit of looking upon an oscillator as being essentially an amplifying device whose output is fed back to its input via a frequency-selective network, such a network normally comprising either capacitance and inductance (together with an inevitable small resistance) or capacitance and resistance. An alternative way of examining the oscillator feedback network is to assume that it causes a *time delay* to take place before a signal at the output of the amplifying device reappears at its input. This second concept is, perhaps, easiest to accept with an oscillator of the phase-shift variety. Here, an output signal is applied to a network of three or more series capacitors and shunt resistors, whereupon a time delay—dependent upon the values of the capacitors and resistors and equal to the time taken up by one half-cycle of the oscillation—occurs before the output signal is fed to the input.

The a.f. oscillator to be described in this article functions by virtue of a time delay inherent in one of the components employed, and its operation does not require capacitance either in conjunction with inductance or with resistance. The oscillator is extremely economical of components and, so far as the writer is aware, has not been previously described.

OSCILLATOR CIRCUIT

The basic circuit of the oscillator appears in Fig. 1. In this diagram a d.c. potential lying between 150 and 300 volts and of either positive or negative polarity is applied to a parallel combination of a light dependent resistor (l.d.r.) and a

neon bulb, these being in series with a 470k Ω resistor. The oscillator output is taken from the 470k Ω resistor via a 0.01 μ F d.c. blocking capacitor. The light dependent resistor, or to give it its more recently acquired name, photoconductive cell, is illuminated by the neon bulb, and both are enclosed in a light-proof box.

The photoconductive cell is an ORP12 and, as most readers will already know, this exhibits a high resistance (of the order of 10M Ω) in complete darkness, and a low resistance (of the order of 75 to 300 Ω) when fully illuminated. One of its two important functions here is to present a decreasing resistance when illuminated, and vice versa. An incidental characteristic of photoconductive cells of the ORP12 class is that these devices do not, when there is a change in illumination level, show an *immediate*

decrease or increase in resistance. They are, instead, quite sluggish in operation, especially for resistance increase due to decrease of illumination. This sluggishness enables the ORP12 to perform its second important function in the present circuit, that of providing the necessary time delay to allow oscillation to take place.

Let us assume that the d.c. supply of Fig. 1 has just been applied. The ORP12, in the light-proof box, will be in darkness, and it exhibits a high resistance. The ORP12 forms one section of a potential divider, the other section being the 470k Ω resistor. Thus, when the supply is initially applied, the ORP12 allows the full striking voltage to appear across the neon bulb, whereupon the latter lights up and illuminates the cell. The resistance of the illuminated cell commences to decrease, causing the voltage across


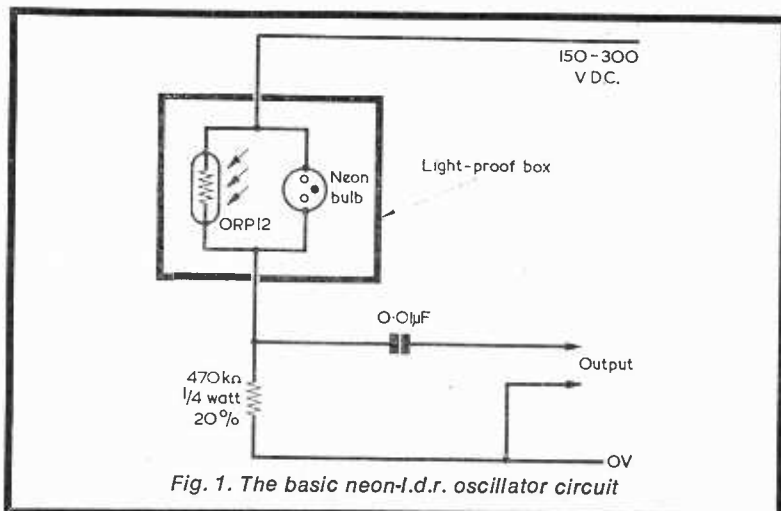


Fig. 1. The basic neon-l.d.r. oscillator circuit

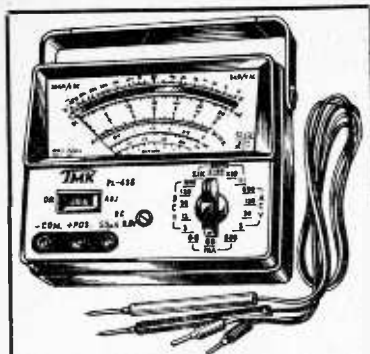

**SUPERB LARGE SCALE
MULTIMETER
AT A PRICE YOU CAN AFFORD**

- ★ 20,000Ω/volt
- ★ Mirror Scale
- ★ Overload Protection
- ★ Free Batteries
- D.C. VOLTS: 0.6, 3, 12, 30, 120, 300
- A.C. VOLTS: 3, 30, 120, 600
- D.C. AMPS: 50μA, 600μA, 60mA, 600mA.
- RESISTANCE - 10k, 100k, 1meg, 10megs
(half scale reading: 60Ω, 600Ω, 6000Ω, 600kA)
- DECIBELS: -20 to +46 db.
- SIZE: 6" x 4½" x 2½"

MONEY BACK IF NOT SATISFIED

ONLY £6.5.0 Plus 3/- p.p.

**IVORYET LTD. 31 Albert Road
Hendon, London, N.W.4**

The
RADIO CONSTRUCTOR

**ANNUAL
SUBSCRIPTIONS**

**to this magazine
may be obtained
through your
newsagent
or direct from the
publishers
ONLY 48/-
per year, post free**

Please send remittance with name and address and commencing issue required to:

**DATA PUBLICATIONS LTD
57 Maida Vale London W9**

the neon bulb to drop until it falls below the maintaining value. The bulb extinguishes, after which the ORP12 resistance starts to increase, reaching a value which is sufficiently high to enable the neon bulb to strike again and light up. The resistance of the once more illuminated ORP12 starts to decrease and a further cycle commences.

The length of each cycle depends upon the sluggishness of operation of the specific ORP12 employed. Several ORP12's, which had been purchased at various times from different retail sources in the past, were checked by the author in the prototype circuit and offered no significant alteration in performance. It would seem reasonable to assume, therefore, that equivalent results should be given with most, if not all, photoconductive cells of ORP12 type. The cycle length depends also upon the difference between the firing and maintaining voltages of the neon bulb, and here again there is a slight possibility that some discrepancy in results may be experienced with different bulbs. Since both the cell and the bulb are employed in the circuit because of characteristics which are incidental to their intended function, the oscillator has to be considered as being somewhat experimental in this respect.

The output of the oscillator is, of course, by no means sinusoidal. The prototype produced an a.f. tone at around 100Hz having a resemblance to the sawtooth offered by a relaxation oscillator, and with one pronounced pulse cycle due to the firing of the neon bulb. The frequency varied only slightly for supply voltages between 300 and 150, but dropped noticeably when the supply potential was reduced to values lower than 150 volts. At about 90 volts the oscillator produced pulses with a spacing of approximately 1 second, and it ceased to function when the supply potential was lowered further. The peak-to-peak amplitude of the oscillation is equivalent to the difference between the striking and maintaining voltages of the particular neon bulb employed, and is of the order of 4 to 6 volts. Over the supply voltage range of 90 to 300 volts the oscillator started reliably on application of the supply. With the circuit given in Fig. 1, the oscillator output should be applied to a high impedance, preferably at least 250kΩ, or its performance may be modified.

NEON BULB

The neon bulb is an inexpensive wire-ended component having two tubular electrodes. Suitable types are the Hivac type 16L or 34L available from Henry's Radio Ltd.,

or the bulb retailed under Cat. No. PL32A by Home Radio Ltd.

Since the neon bulb and the ORP12 are in parallel, it is a simple matter to fit them in their light-proof box. For best operation the neon bulb body should lay across the face of the ORP12, as in Fig. 2. This method of positioning allows the leads of the bulb to be soldered direct to the stouter lead-out wires of the photoconductive cell, as shown. The lead-out wires of the cell may then be anchored to suitable tags inside the box. Experiments with the circuit showed that oscillations could be obtained with the neon bulb spaced away from the ORP12 by as much as 1in. For best results, though, the closer positioning illustrated in Fig. 2 is to be preferred.

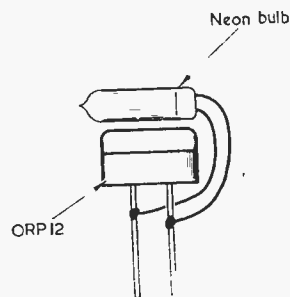


Fig. 2. For optimum results the neon bulb body should lie across the face of the ORP12, as illustrated here

The light-proof box need not be elaborate as the circuit is capable of working at low ambient lighting levels without enclosing the cell and bulb at all. For a quick check-up of the circuit in all but the brightest ambient lighting (as is given by direct sunlight) it is quite in order to fit the two components inside an empty match-box, keeping the box in shadow by placing a sheet of cardboard or other opaque material over it. The only requirement of the light-proof box is that it should exclude sufficient light for the ORP12 to exhibit a resistance high enough to enable the neon bulb to strike. As an instance of what can be expected, the prototype oscillator functioned reliably when both the cell and neon bulb were completely exposed in the low ambient light level evident at dusk. It was interesting to note that oscillation could be stopped under these conditions by striking a match 18ins. away from the face of the photoconductive cell. There appeared to be little 'backlash' between the light level which stopped oscillation and that which enabled it to recommence, and the

THE RADIO CONSTRUCTOR

writer hopes to describe a precisely-operating light-controlled switch which takes advantage of this property in a future article.

ADVANTAGES AND DISADVANTAGES

Like all electronic circuits, the oscillator of Fig. 1 has advantages and disadvantages. Its main advantages are its considerable simplicity, and the small number of components it requires. Because of these two points, it may be assembled in full working order in a very short time. Also, it provides an a.f. output at a relatively high amplitude, and is not very critical so far as component values and supply voltage are concerned. Further, the supply polarity is unimportant, and the oscillator offers potential use in a light-operated switching device. A final advantage is that the current it consumes, being limited by the 470k Ω resistor, will always be considerably less than 1mA. The principal disadvantages are that the output is non-sinusoidal and its frequency cannot be varied (or, at least, cannot be varied if the circuit is to retain its simplicity), and that the supply voltage required is rather high.

oscillator output to grid and anode points in the equipment, using normal signal-tracing techniques. The oscillator output will be just audible if the probe is applied to the primary of a valve speaker transformer, and will be reproduced at more than adequate level when connected to an output valve grid. The 0.01 μ F capacitor shown in Fig. 3 should have a working voltage of at least 400 volts, to ensure that there is no risk of its breaking down if the probe is applied to anode circuits in the equipment under test. The 470k Ω resistor of Fig. 1 is replaced by a 500k Ω potentiometer in Fig. 3, this latter component functioning as an output amplitude control. If the potentiometer is set to a central position the probe may be applied to low impedance points without seriously affecting oscillator operation.

In Fig. 3, all the components are enclosed in a light-proof box, with terminals brought out for the two crocodile clip leads and the test prod lead. This method of assembly eases construction and still ensures that light is excluded from the photoconductive cell and the neon bulb. The box should be made of an insulating material

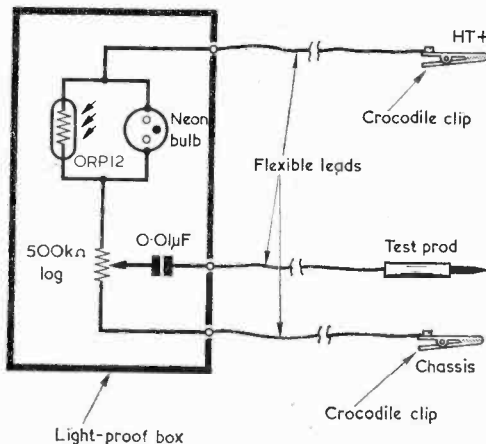



Fig. 3. One application for the oscillator is as an a.f. signal injector, whereupon it obtains its power supply from the equipment being tested

Apart from the normal applications to which any a.f. oscillator may be put, the circuit can be adapted for use as a servicing aid, as in Fig. 3. Here, the oscillator is intended as an a.f. signal injector for radio, television and a.f. amplifier equipment employing valves. The two crocodile clips are connected between chassis and the h.t. positive line of the equipment being checked, whereupon power automatically becomes available for the oscillator. The test prod may then apply the

and *not* of metal, since it can then be positioned on or near the chassis of the equipment under test without risk of shock or accidental short-circuit. The potentiometer may be fitted with a pointer knob backed by a scale graduated in even divisions from, say, 1 to 10. After familiarity with the device has been acquired, the scale will then provide a rough idea of the output level needed for application

(Continued on page 628)

AUDIO AMPLIFIERS

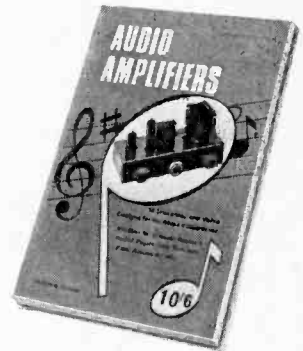

16 Transistor & Valve Designs for the Home Constructor

Amplifiers for Tuner Units, Record Players, Tape Recorders, Public Address, etc., etc.

Includes contributions by such well-known authors as

A. S. Carpenter, A. Kinloch, E. Govler, G. A. French, F. G. Rayer, P. F. Bretherick, K. Jones, D. Aldous, R. Murray-Shelley, C. Swires, G. A. Stevens and V. E. Holley.

Edited by J. R. Davies

124 pages

PRICE 10s. 6d.

Postage 8d.

To: DATA PUBLICATIONS Ltd., 57 Maida Vale London W9

Please supply copy(ies) of "Audio Amplifiers", Data Book No. 18. I enclose cheque/crossed postal order for.....

Name.....

Address.....

.....

.....

.....RC

BLOCK LETTERS PLEASE



SIMPLIFIED SOLID-STATE DISTORTION METER

by

G. A. STANTON, G3SCV

This simple design enables the percentage distortion of a.f. amplifiers to be measured directly over the range 0.2% to 10% at 1,000 Hz. Consumption from the self-contained 9 volt battery is 8mA only

READERS FAMILIAR WITH AUDIO SPECIFICATIONS will know that it is standard practice for these to include a figure indicating the total harmonic distortion. This is usually expressed as a percentage related to the rated output of the equipment concerned with a 1,000Hz test input. While other factors are obviously involved (e.g. frequency response, etc.) the distortion factor can be regarded as a guide to the goodness of audio equipment and the description high fidelity is normally reserved for equipment introducing less than 1% total distortion.

From this it will be obvious that in testing audio equipment some means of checking the total distortion is very desirable. Likewise when experimenting with audio circuits it is very useful to be able to compare results in terms of the distortion factor. Commercial distortion meters are available for this purpose but tend to be sophisticated instruments covering at least the audio spectrum, and because of this are relatively expensive. Consequently, they are rarely found outside the professional laboratory and the larger service department. The instrument to be described in this article is a simplified version designed to meet the needs of the home experimenter.

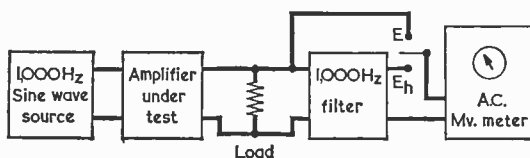


Fig. 1. A simple means of evaluating harmonic distortion

It enables distortion checks to be made at the standard 1,000Hz frequency and measurements to be made from 0.2% to 10%. Output is also provided for monitoring the distortion waveform on an external oscilloscope.

DISTORTION MEASUREMENT

A detailed analysis of harmonic distortion and its measurement is beyond the scope of this article, and the interested reader is referred to standard textbooks on the subject. The basic principles on which the present instrument works can be understood from a study of Fig. 1. Here, it will be seen, a 1,000Hz sine wave signal is fed to the amplifier under test; the output from the amplifier, which must be correctly loaded, is then passed via a selective filter to an a.c. millivoltmeter. A pure sine wave fed to a perfect amplifier would result in an amplifier output

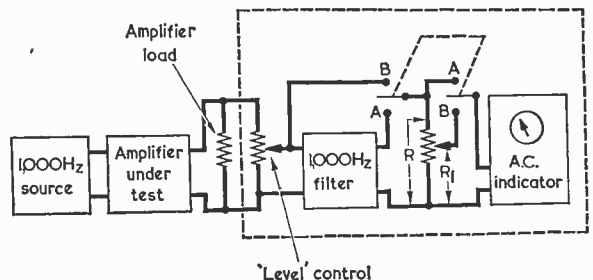


Fig. 2. An alternative approach which considerably eases performance requirements in the a.c. indicator

Cut along this line



SIMPLIFIED SOLID-STATE DISTORTION METER

Workshop plans presented free with the May 1970 issue of 'The Radio Constructor'



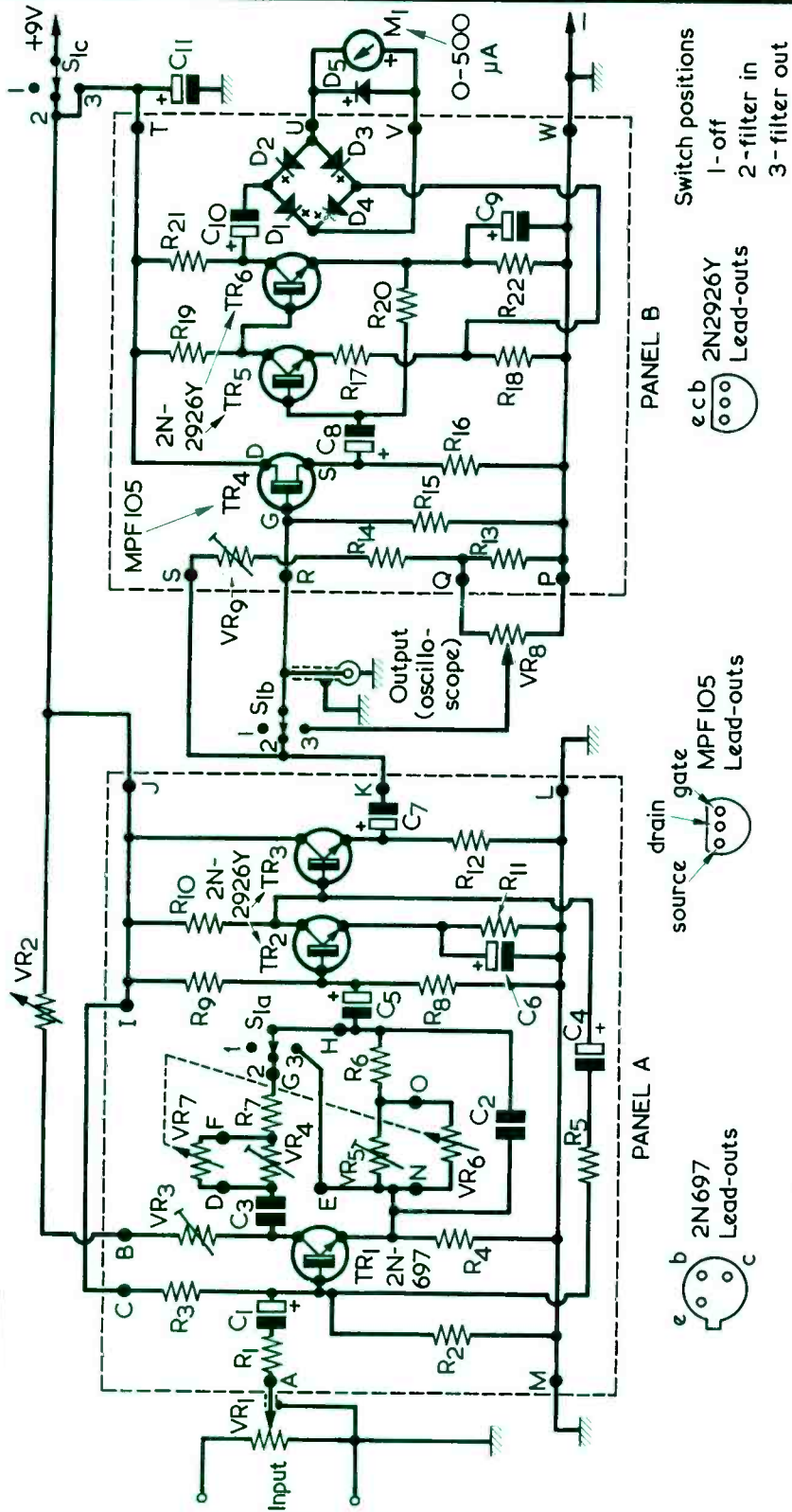



Fig.3. Complete circuit of the Distortion Meter described in this article

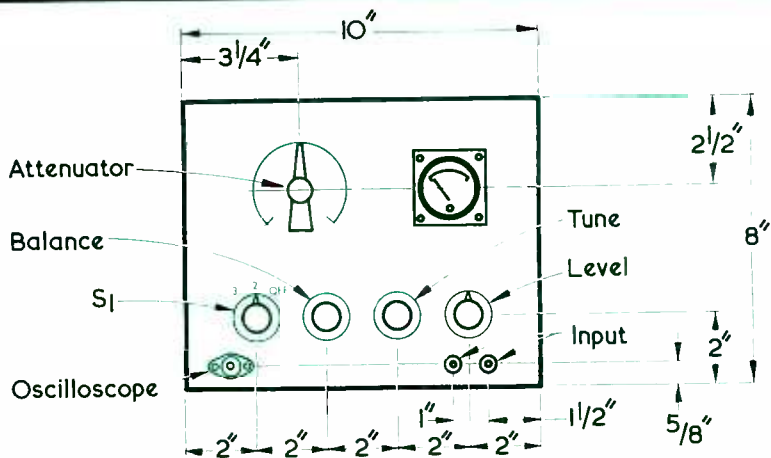

(a)

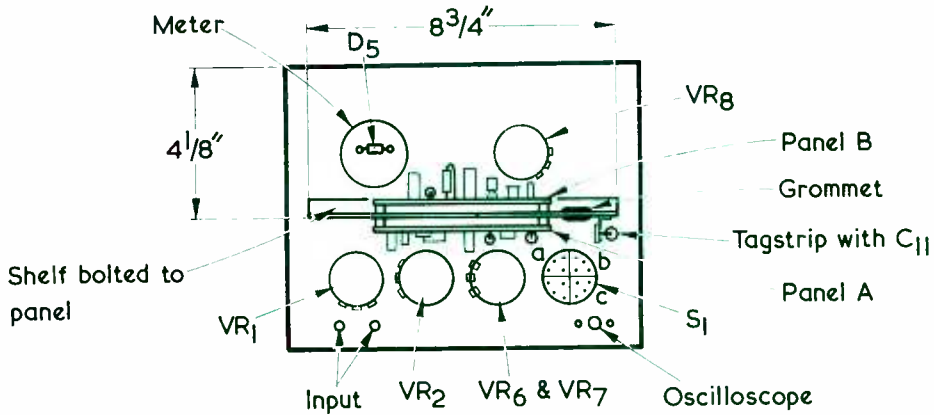

(b)

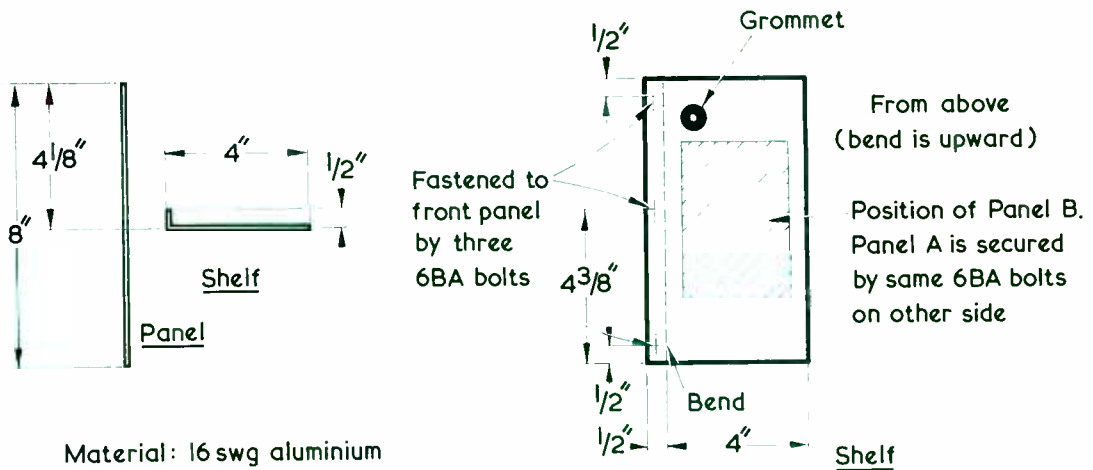

(c)

Fig. 4a Layout and control positions on the front panel

4b Layout of components and printed circuit boards behind the panel

4c Illustrating how the panel and shelf are assembled

consisting solely of the fundamental frequency (i.e. 1,000Hz). This in turn would be completely "absorbed" by the filter and the meter would remain at zero. In practice, of course, even the best amplifier will have some degree of non-linearity and the sine wave will become distorted. The output will then contain extraneous frequencies in harmonic relationship with the fundamental. The filter will absorb the latter but the harmonics will pass to the meter for measurement. The percentage harmonic distortion can be represented by the expression

$$\frac{E_h}{E} \times 100$$

where E_h is the voltage amplitude of the harmonics and E is the voltage amplitude of the sine wave signal.

This is of course an approximation, for the output of the amplifier will also include hum and noise. These are measured along with the harmonic content, but the accuracy will suffice for all but the most stringent tests, for which a more sophisticated instrument would be needed in any case.

The scheme indicated in Fig. 1 assumes the use of

a wide range calibrated a.c. voltmeter which would be required to take measurements from 1mV or less to at least 10 volts. Such a meter is an expensive item but fortunately, by the use of a calibrated attenuator, a relatively simple indicating meter can be substituted. This is the practice followed in the instrument being described, and the method of operation can be seen in Fig. 2. A switch is so arranged that in position A the meter is connected directly to the output of the filter and indicates the amplitude of the harmonics present. The switch is then moved to position "B", whereupon the filter is bypassed and the meter connected to the attenuator. The attenuator is adjusted until the same indication is obtained on the meter; at this setting the ratio

$\frac{R1}{R}$ equals $\frac{E_h}{E}$. The percentage distortion is thus

$\frac{R1}{R} \times 100$, and the attenuator can be calibrated to

read directly in terms of percentage distortion.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10% unless where otherwise stated)

R1	47k Ω
R2	4.7k Ω
R3	15k Ω
R4	1.2k Ω
R5	10k Ω
R6	2.2k Ω , 5% or better
R7	2.2k Ω , 5% or better
R8	4.7k Ω
R9	27k Ω
R10	4.7k Ω
R11	470 Ω
R12	2.7k Ω
R13	120 Ω , 5%
R14	910 Ω , 5%
R15	1.5M Ω
R16	2.7k Ω
R17	33 Ω
R18	5.6 Ω
R19	6.8k Ω
R20	6.8k Ω
R21	680 Ω
R22	330 Ω
VR1	500k Ω pot, log track
VR2	200 Ω pot, lin track
VR3	5k Ω pot, preset skeleton
VR4	5k Ω pot, preset skeleton
VR5	5k Ω pot, preset skeleton
VR6, 7	25k Ω + 25k Ω ganged dual pot, lin track
VR8	5k Ω pot, log track
VR9	250 Ω pot, preset skeleton

Capacitors

C1	16 μ F electrolytic, 15V wkg.
C2	0.047 μ F polyester, 10% or better
C3	0.047 μ F polyester, 10% or better
C4	1 μ F electrolytic, 15V wkg.
C5	10 μ F electrolytic, 15V wkg.
C6	25 μ F electrolytic, 15V wkg.
C7	32 μ F electrolytic, 15V wkg.
C8	16 μ F electrolytic, 15V wkg.
C9	32 μ F electrolytic, 15V wkg.
C10	16 μ F electrolytic, 15V wkg.
C11	250 μ F electrolytic, 15V wkg.

Semiconductors

TR1	2N697
TR2	2N2926 Yellow
TR3	2N2926 Yellow
TR4	MPF105
TR5	2N2926 Yellow
TR6	2N2926 Yellow
DI-D4	OA90
D5	OA85

Meter

M1	0-500 μ A moving-coil meter
----	---------------------------------

Switch


S1	3-pole 3-way miniature rotary (4-pole 3-way may be employed, if desired, with one pole unused)
----	--

Battery

9 volt battery (see text)

Miscellaneous

2	printed circuit boards
5	knobs (see Fig. 4(a))
1	coaxial socket
2	insulated sockets
1	4-way tagstrip
16	s.w.g. aluminium sheet
	Grommet, nuts, bolts, etc.

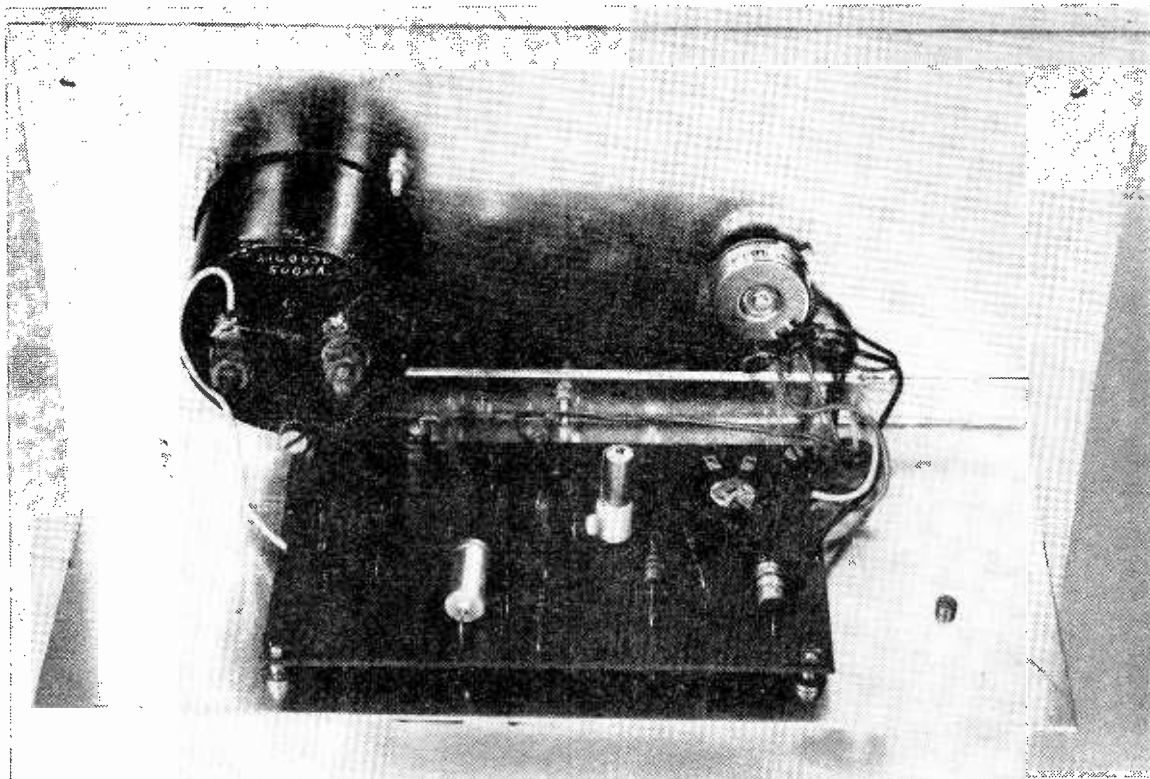

View illustrating the upper side of the shelf, and showing the meter, the Level control potentiometer and Panel 'B'

CIRCUIT DIAGRAM

The complete circuit diagram is given in Fig 3, and is in two sections. The first is the filter section which is of the Wein Bridge type; one arm of this comprises C2 in parallel with VR5, VR6 and R6; the other arm consists of C3 in series with VR4, VR7 and R7. The values of these components are such that the filter can be balanced between 900Hz and 1,500Hz by means of the ganged potentiometer VR6 and VR7. The filter is switched in or out as required by S1(a), the filter being in circuit at position 2 of this switch and out of circuit at position 3. With the filter in circuit, TR1 operates as a phase splitter feeding the two arms of the bridge from its emitter and collector respectively. VR2 forms part of the collector load and assists in enabling the bridge to be accurately balanced. When the filter is switched out of circuit, TR1 operates as a simple emitter follower, passing the unfiltered signal to the base of TR2 which is a straightforward voltage amplifier. Negative feedback is provided by R5 and C4 connecting the collector of TR2 with the base of TR1. Feedback in this circuit is extremely important for two reasons: it reduces any distortion likely to be introduced by TR1 itself, but more important it considerably sharpens the filter null. Without feedback the filter "tuning" would be too broad and the harmonics reduced along with the fundamental. This would then give a false indication of the harmonic content and defeat the purpose of the instru-

ment. VR1 controls the input and is used to set the level of the signal.

The second section of the instrument is the voltmeter circuit which consists of an f.e.t. source follower (TR4) and a two-stage amplifier. The f.e.t. provides the high impedance input essential for the correct working of the attenuator. Output is taken from the collector of TR6 via a full wave bridge rectifier to a standard 500 μ A moving-coil meter. The meter need not be calibrated and no attempt has been made to linearise the scale readings. The sensitivity of the section is such that full-scale deflection is obtained for an input to TR4 of approximately 3mV r.m.s. The meter is protected from severe overloading by a germanium diode (D5) connected across it.¹

The two sections are coupled by S1(b), which is so wired that when the filter circuit is 'in' the output of TR3 is taken directly to the gate of TR4. With the filter 'out', the signal is taken to TR4 via the attenuator, this being formed by the network VR8, R13, R14, and VR9. VR9 is adjusted so that VR8 in parallel with R13 offers exactly one-tenth of the

¹ The meter employed by the author was an ex-W.D. type having a lower resistance, at approximately 100 Ω , than that of many 0-500 μ A meters currently available on the home-constructor market. The author has checked the circuit with a higher resistance meter and it still functioned satisfactorily. If it is found, however, that the presence of D5 seriously restricts higher scale readings when a high resistance meter is employed, the single diode may be replaced by two or more similar diodes connected in series to offer an increased low current forward voltage.—Editor.

total resistance. VR8 then controls voltages up to 10% of the total present at point S in the diagram. For convenience VR8 should be a logarithmic type.

Power requirements are very modest, being 8mA from a 9 volt battery. Voltage readings to be expected at various points of the circuit are given in the Table. A third section of S1 switches the instrument on and off.

In Fig. 3, the two rectangles drawn in dashed line do not indicate screens; instead, they show the boundaries of the associated printed circuit panel assemblies. For convenience of presentation VR6, VR7 and S1(a) are drawn inside the Panel "A" rectangle, but in practice these components are external to the panel. The letter references apply to the printed circuit connections which are shown, later, in Figs. 5(a) and (b).

A minor point which needs to be mentioned is that the inset in Fig. 3 which shows the f.e.t. lead-outs indicates that the drain lead-out is in the centre, whereas some (but not all) Motorola literature shows the source as the centre lead-out. In practice, the source and drain of the MPF105 are interchangeable, since this is a symmetrical transistor. The 2N2926 Yellow transistors specified for TR2, TR3, TR5 and TR6 are the basic 2N2926 with an h_{fe} between 150 and 300. They are available from a number of suppliers, including Electrovalue, 32a St. Jude's Road, Englefield Green, Egham, Surrey.

(Continued on page 630)

THE 'DISCOVERY' S.W. RECEIVER

For the interest of all the many beginners who are known to have constructed this popular design, Further Notes on the 'Discovery' Receiver will appear in the July issue - this providing full information on modifications increasing the versatility of the receiver.



"We weren't able entirely to eliminate the human element!"

MAY 1970

CURRENT SCHEDULES

Times = GMT

Frequencies = kHz

★ CUBA

17705 Radio Havana (100kW) transmits an English programme to Europe from 2010 to 2140. Radio Havana can also be heard on **15345** from 1810 to 1855 in Arabic, 1855 to 2030 in Spanish, 2030 to 2110 in Arabic and from 2110 to 0010 in French. Also on **17885** in parallel.

★ ISRAEL

9009 'Kol Yisrael', Tel Aviv (7.5/50kW) now has an English service to Africa from 2015 to 2030 and an English service to Europe from 2015 to 2100.

★ MALAYSIA

7120 The BBC transmitter at Tebrau (7.5/75kW) relays the BBC World Service from 1300 to 1815 on this channel. On **7234** from 0900 to 1000 and from 1100 to 1115. On **9580** from 1345 to 1815. On **9725** from 0900 to 1000. On **9740** from 1345 to 1815. On **11750** from 0900 to 1815. On **11955** from 0900 to 1000 and from 1645 to 1815. On **15310** from 0900 to 1000. On **15434** from 1300 to 1330 and on **17880** from 0900 to 1330.

★ SWEDEN

9625 and **15315** The English language broadcasts of Radio Sweden, currently effective, are as follows - **9625** and **15315** (100kW) from 1100 to 1130 to Europe and N.E. America; **15105** and **21690** (100kW) from 1230 to 1300 to Far East and Africa; **15315** and **21585** (100kW) from 1400 to 1430 to S. Asia and N. America; **6065** and **11860** (100kW) from 1600 to 1630 to Europe and Middle East; **11705** and **15240** (100kW) from 1900 to 1930 to Middle East and Africa; **6065** and **11910** (100kW) from 2045 to 2115 to Europe and Far East; **11705** and **15310** (100kW) from 2245 to 2315 to Europe, S. America, Australia and N. Zealand; **11790** (100kW) from 0030 to 0100 to N. America; **9725** (100kW) from 0330 to 0400 to Western North America and on **17840** from 0515 to 0545 to S. Asia.

★ AUSTRALIA

The Darwin relay stations of Radio Australia carry programmes in English on Sundays from 2200 to 0800 on **21485**, from 2300 to 0030 on **15130** and from 0030 to 0800 on **15355** and **17715**. Daily English programmes may be heard from 0800 to 1130 on **15355** and from 0800 to 1000 and 1100 to 1330 on the new channel of **21485**.


★ REPUBLIC OF RWANDA

Radio Rwanda, Kigali, radiates programmes in English, French and Swahili from 0945 to 1045 on **15410** (250kW). At 1045 they announce continued transmissions on **6055** (50kW). The former channel then continues with a relay of Duetsche Welle.

★ SEYCHELLES

The FEBA transmitter at Victoria (2kW) is still testing on **11760** from 0030 to 0200 and on **15265** from 0205 to 0230 and 1300 to 1630. The regular transmitter will be in operation from May 3rd with a power of 40kW.

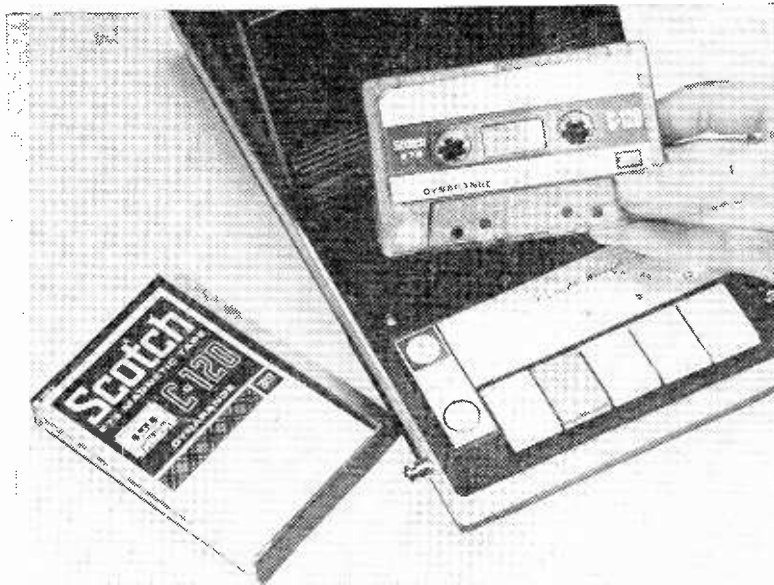Acknowledgements to our own Listening Post and Swedish Dx'ers.



The Scotch C-120 cassette, which gives two hours' playing time, uses Scotch low-noise Dynarange magnetic tape. The design is claimed to contribute towards longer recorder battery life

The range of Scotch magnetic tape cassettes has been expanded to include a two-hour version.

A feature of this new Phillips-compatible cassette – the Scotch C-120 – is an improved shim material which offers reliability while eliminating tape binding and jamming – previously a problem with ultra-thin tape.

The Scotch C-120 cassette retails at a recommended price of 33/6d.

As with the other cassettes in the range (the Scotch C-60 which gives 60 minutes recording and the Scotch C-90 giving 90 minutes) the new cassette is supplied in a durable hinged plastic case designed to protect the tape and provide easy storage.

ALL-PURPOSE POCKET TOOL – THE REXEL VERSICUT

The Versicut, an ingenious multi-purpose pocket tool, costing only 7s. 6d. (recommended retail price), has recently been launched by Rexel Ltd. Shaped like an elegant chuck pencil, the Versicut is a knife blade, pin and two-width screw-driver in a single pen-size unit that slips conveniently into the pocket.

In the head of the Rexel Versicut is an engineered chuck mechanism, which is designed to grip the tool pieces, so that, in turn, the instrument becomes a screw-driver, piercing and probing tool, or a cutting device.

When not in use, the tool pieces either drop out of sight behind the chuck mechanism, or are contained in the hollow barrel. Changing the function of the Versicut or adjusting the length of the gripped item can be accomplished in seconds. While one of the tool pieces is in use, the other two remain in the barrel.

The Versicut is available from most stationers and department stores, and the price includes a spare knife blade. Packs of five individually wrapped replacement blades are available at 3s. 4d. (recommended retail price).

INTERESTING MULLARD PAMPHLETS


The Mullard Educational Service has produced two new pamphlets, one entitled 'Introducing Thyristors' and the other describing how to build a simple, inexpensive, f.e.t. voltmeter.

The first pamphlet contains a brief description of the construction and operation of the thyristor. An explanation of the thyristor characteristic is followed by a section on the basic power control circuit and feedback control. The pamphlet ends with a short description of the diac and the triac.

The second pamphlet describes how to build a simple, inexpensive f.e.t. voltmeter. The meter has eight ranges, the smallest being 0 to 250mV and the largest 0 to 500V. Because it has a high input impedance of at least 10M Ω on each range, the instrument is suitable for measuring d.c. levels in transistor and valve circuits.

The meter described is not a sophisticated piece of equipment and no claim is made to its accuracy; it contains no close-tolerance resistors and the least expensive f.e.t. transistor (type BFW61) has been used. Nevertheless, the educational prototype has been in constant use since it was built twelve months ago. However, design information is given for those who wish to make a more accurate instrument.

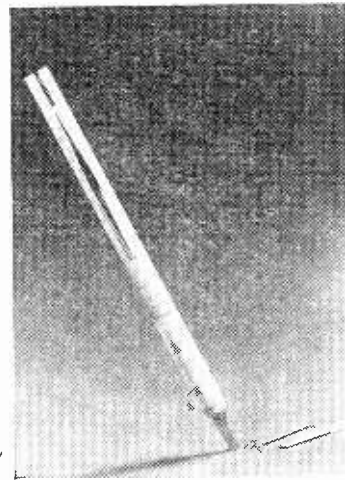Teachers, lecturers and others professionally concerned with science education can obtain sample copies of the pamphlets from the Mullard Educational Service, Mullard Ltd., Mullard House, Torrington Place, London, W.C.1.



THE RADIO CONSTRUCTOR

COMMENT

BRITISH AMATEUR TELEVISION CLUB 21st ANNIVERSARY CONVENTION

The Convention will be held in Churchill College, Cambridge, and will start with a Get-together on Friday evening, 24th July.

On the Saturday morning the Exhibition of Amateur Equipment will open and there will be lectures, films, video tapes and a visit to a TV transmission equipment manufacturer.


In the evening there will be a Convention Dinner in Churchill College.

Sunday morning will continue with visits to Amateur stations, films, etc. In the afternoon there will be a B.A.T.C. Business Meeting (Members only), followed by tea.

The Conference registration fee is 15/- (£1 non-members), tickets for the dinner are 32/6 each and residential accommodation in the College will be available at £7.10s.0d., per person.

Fuller details from D. S. Reid, 71a Rose Valley, Brentwood, Essex.

NIPPON DENSO AERIAL

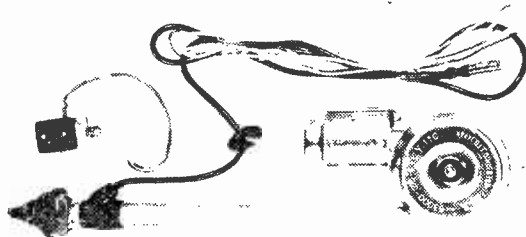

This new aerial is of very compact and robust construction. Its underwing length is 13½ in., its mast (four section chromium) is 36 in. long and the motor is a powerful permanent magnet type of small dimensions.

It is supplied complete with a spring loaded 2-way control switch, but there is an interesting optional switch which can be connected so that it gives overall control of the radio as well as the aerial.

The retail price of the aerial, complete with standard control switch, is £9 9s. 0d. and the optional extra switch, £2 18s. 0d.

MUSIC FROM AN INVISIBLE SOURCE

A new device which reproduces music through a variety of ordinary household materials from an apparently invisible source is now available. Called the Sound Scan Capsule, the unit may be concealed in the ceiling, under floorboards, or behind doors, to envelop the whole room in an even volume of music no matter where the listener may be standing or sitting.

This effect is achieved simply by linking the unit to the output socket of any record player (mono or stereo), tape recorder, or amplifier with from 1½ to 12 watt output. The capsule will work on almost any flat surface such as a table, picture or window, and will diffuse sound over large areas – up to 2,000 square feet in ideal circumstances. It is weather-protected, will play underwater and comes with a five-year warranty.

Measuring about 4 in. in diameter and less than 2 in. in depth, the Sound Scan Capsule is technically known as an audio-transducer. It was invented in the U.S.A. where it has been successfully marketed by Photo-Scan International of Los Angeles, manufacturers of electronic systems to combat shoplifting and pilferage.

At present, the Capsule – which costs a recommended £10 retail – is being demonstrated to the public at Selfridges and Gammages in London, and major stores in the Home Counties and the South of England. It will eventually be available throughout the country from radio and electrical shops.

Further details from: Mr. Colin Stewart, Sound Scan Ltd., Oakwood House, 63 Pound Lane, Marlow, Bucks. Tel: Marlow 6655.



"Oh, look – it was only that it wasn't switched on!"

BBC World Radio Club

The *World Radio Club* is one of the BBC's world service programmes and was first radiated in July of 1967. The object of the Club is to cater for an audience generally interested in radio but with SWL's specially in mind and to pass on technical information in an easily understood manner in addition to Dx tips, etc. Some of the programme content includes information about technical achievement in the field of communications with the emphasis placed on British innovations and the BBC's own contribution to the science.

The degree of understanding of the technical programme content tends to vary in differing countries and when such items are included due consideration is given to the technical development and understanding in such areas—especially those at present underdeveloped. Such technical material is rightly presented in simple, uncomplicated English, even when describing the very latest communication equipment.

Programme content has been varied from that of simple short wave aerial arrays to basic communication receiver operation and techniques. Advice on how best to operate the equipment which many listeners possess and how to further improve the

results are often broadcast. The first principles of radio communication have also been a feature of the programme.

Perhaps the most interesting part of the programme is the *Dx News Bulletin*. With all the resources of the BBC Monitoring Service at their disposal the Club is able to present up to the minute reports on station frequencies, call signs and other material of interest to the Broadcast band Dx'er. The *Dx News Bulletin* is only part of the programme in order that other interesting subjects may be covered in the allotted quarter-hour on the air.


Members of the *World Radio Club* receive frequency charts and are eligible to enter Club competitions and such members number many thousands.

The Club receives many letters from listeners all over the world and, in conformity with BBC practice, answers each and every letter. Some of the most interesting are answered over the air. It was in March, 1968, that the BBC first issued a QSL card to listeners reporting on the short wave transmissions.

RECENT PROGRAMME

A recent programme content provides some idea of the interests covered.

Opening with a five-minute talk on the life of Michael Faraday, there followed *Band Scan* at 0820 GMT. This part of the programme, as its title implies, presents the results of a listening session over a chosen range of Broadcast band frequencies at a given time. That chosen for this particular programme was from 7100 to 7300kHz and consisted of a list of various stations logged during an operating session commencing at 2000GMT.

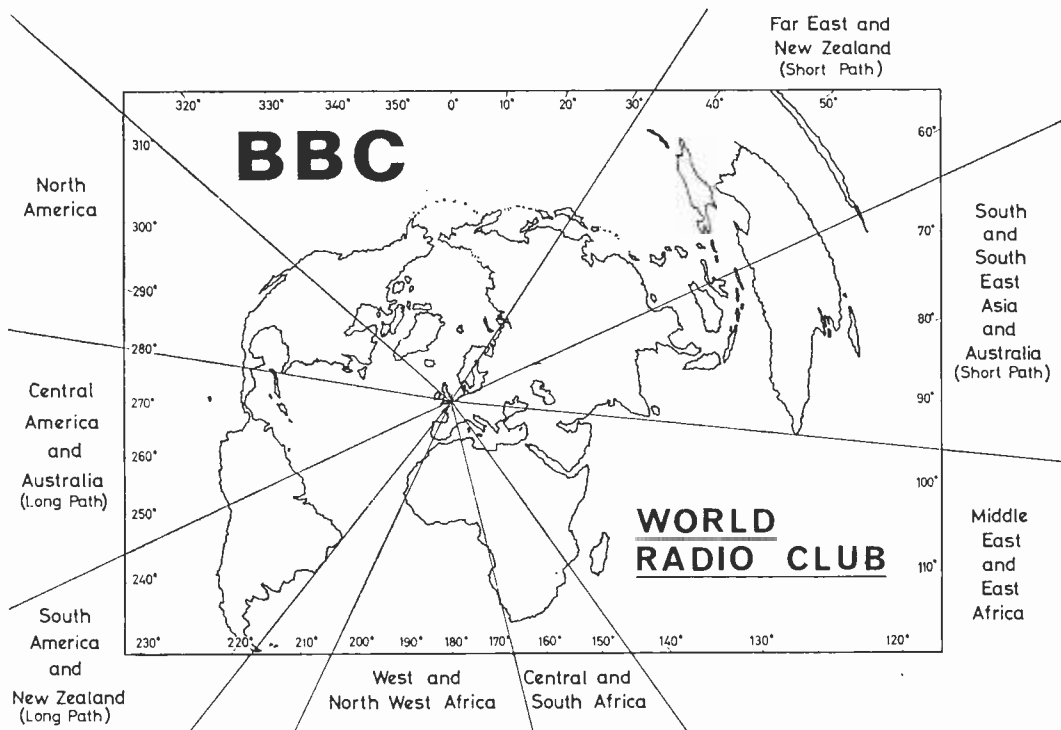



Doug Crawford, World Radio Club compère

None of the stations mentioned were by any means of Dx standard, but considering the band and the time chosen this was not surprising. For the beginner, *Band Scan* would be of interest in bringing to his notice just how many countries could be logged with fairly simple equipment at the time stated. This part of the programme lasted approximately five minutes and was followed by a short talk on constructing an amateur band transmitter until 0828 GMT. The remaining two minutes were devoted to a conversation between the two listeners who had conducted *Band Scan*. Mentioning that logging South American stations was a favourite facet of short wave listening for them, and with which they would deal the following week, an admission was made by one that the more difficult to receive Far Eastern Station "always just miss my receiver".

EDITOR'S NOTE

The statement is somewhat surprising for a short wave listener reporter to utter. Our own Listening Post has regularly logged and reported such stations, having even taped some of them during the recent 'season' for reception of Far Eastern transmissions. Such stations as Nusantara Tiga, Medan, Indonesia, on 5084kHz closing at 1600GMT; Djambi, Indonesia, on 4927kHz closing at 1600GMT; Phnom Penh, Cambodia, on 4907kHz as early as 1345GMT; Foochow, China, on 4975kHz at 1525 GMT; Singapore on 5055kHz at 1540GMT; Hanoi, North Vietnam, on 4823kHz at 1410 GMT; Penang, Malaysia on 4790kHz at 1530GMT; and Palembang, Indonesia, on 4855kHz at 1455GMT. Additionally, stations in India, Ceylon and the Maldive Islands have also been logged.

WHEN TO LISTEN

For those who would like to listen to *World Radio Club*, the broadcast times are—Sundays at 0815 GMT, Mondays at 1445GMT, Thursdays at 1245 GMT and Fridays at 2345GMT. The writer regularly listens on Sunday mornings at 0815GMT (0915 clock time) on 15070kHz.

MAY 1970

NOW HEAR THESE

Times = GMT

Frequencies = kHz

● BRAZIL

ZYZ32 Radio Rural Brasileira (7.5kW) listed on 15105 has been heard on 15095 around 2000 to 2100 hrs. with announcements in Portuguese. The station location is Porto Alegre and not Rio de Janeiro.

● TAIWAN

BED60 Taipei, the Voice of Free China is being heard regularly from 1800 to 1900 on 15125 (100kW). BED39 Taipei (50kW) is in parallel on 17720.

● COSTA RICA

TIFC Faro del Caribe (Lighthouse of the Caribbean) San José on 6037 (2kW) has been heard, on extended schedule, with an English programme at 0400 on Sundays.

● HAITI

4VEH Cap-Haitien now transmits an English programme at midnight on 9770 (0.5kW). Also in parallel on 11835 (2.5kW).

● PAKISTAN

An unidentified station radiating Asian-type programmes has been under observation by our Listening Post since late February on 3940 from around 1600 to close down at 1730. This unlisted station has now been identified as Peshawar.

● UNITED ARAB REPUBLIC

English programmes from Cairo may now be heard on 9740 from 2145 to 2300. Reports are requested and the address is - U.A.R. Broadcasting Corporation, POB 566, Cairo, Egypt.

● TURKEY

Radio Ankara may be heard with an English programme from 2200 to 2230 on 15160 (100kW) and from 1415 to 1445 on 17820 (100kW). A new 250kW transmitter will be in operation later this year.

● PORTUGAL

CSA66 Lisbon has been heard with an English programme from 1400 to 1425 on 17895 (50/100kW).

● VATICAN

Vatican Radio has been logged with a programme in English from 1500 to 1515 on 9645 (100kW).

● YUGOSLAVIA

Radio Belgrade heard with a programme in English and newscast at 1530 on 9620 (100kW).

● CANADA

Sackville heard with a programme in English at 2125 on 11905 (50kW).

● EL SALVADOR

YSS Radio Nacional de El Salvador, San Salvador has an English and French transmission from 2200 to 2230 on 5980 and 9555 (5kW). Schedule is from 1700 to 0500.

● GHANA

Accra may be heard with a talk in English and station identification at 2230 on 4915 (10kW).

● LIBERIA

Radio St. Elwa, Monrovia has been logged at 0640 with an English programme and station identification on 4770 (10kW).

Acknowledgements to our own Listening Post and Swedish Dx'ers.

INCREASING TRANSISTOR RADIO COVERAGE

by

C. F. DOREY

The frequency range of a transistor portable radio may be extended to cover 1,570 to 3,800kHz, thereby taking in the 160 and 80 metre bands as well as the 'Trawler Band', by mixing on the second harmonic of the oscillator. The receiver to be modified must, of course, have sufficient space to accommodate the extra switch and ferrite rod required, and it will be necessary to have a signal generator available

THIS ARTICLE WILL SHOW HOW A TRANSISTOR portable radio can be modified to go beyond providing entertainment broadcast reception and function as a simple and inexpensive receiver up to 3.8MHz. In its modified form it will be more suitable for this purpose than, say, an ordinary broadcast receiver employed with a converter for "Trawler Band" reception. The simple theory underlying the modification will also be dealt with.

EXTENDING FREQUENCY COVERAGE

Extended frequency coverage can be achieved by using the second harmonic of the local oscillator as it is tuned over its normal medium wave range. No additional coil or switching is required in the oscilla-

tor circuit, but a switch is added to bring in a new ferrite rod aerial in place of the medium wave windings on the existing ferrite rod. In this article, the new frequency range thus obtained will be referred to as the "Trawler Band".

The switching circuit employed with the writer's receiver is illustrated in Fig. 1. S1 is the existing medium and long wave switch, and now selects long waves on position "L" and either medium waves or "Trawler Band" on position "MT". When the additional switch, S2, is set to position "M", the medium wave tuned and base coupling windings are connected into the same medium wave circuit as existed before the modification. The author's receiver has a coaxial socket for an external aerial, and S2(c) and S2(d) couple this to the "car aerial coupling

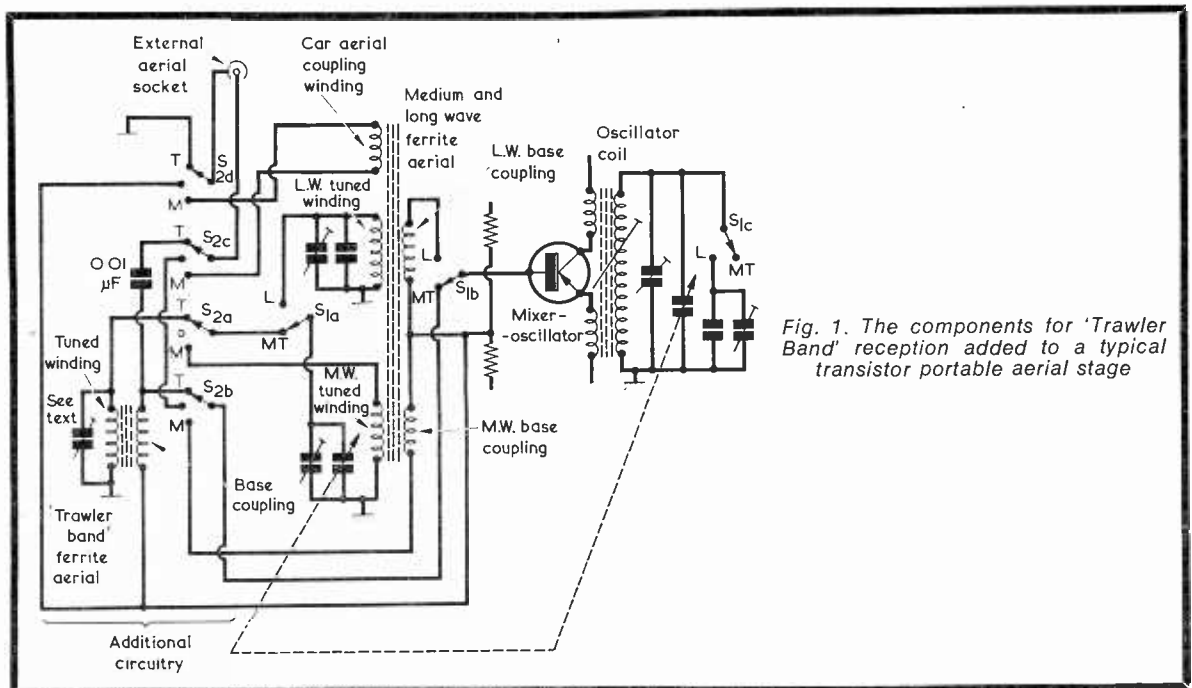


Fig. 1. The components for 'Trawler Band' reception added to a typical transistor portable aerial stage

winding" on the existing medium and long wave ferrite aerial. Setting S2 to "T" causes the existing aerial tuning capacitor to be coupled across the tuned winding of an added "Trawler Band" ferrite aerial, and the base of the mixer-oscillator transistor to be connected to a base coupling winding on this ferrite aerial. At the same time, S2(c) enables an external aerial to be coupled via a 0.01 μ F capacitor to the non-earthly end of the "Trawler Band" base coupling winding. S2(d) connects the outer contact of the external aerial socket to chassis.

The central position of S2 is employed for a purpose not connected with the present modification. It causes the external aerial socket to be connected direct to the base circuit of the mixer-oscillator transistor. This is intended for use with short wave converters having an output tuned coupling circuit tuned to the first i.f. of the converter and receiver combination. It allows the converter output to be applied directly to the mixer-oscillator, thereby obviating the interference that would result if the receiver ferrite rod were left in circuit.

As will be noted, the basic functions of the switching circuit of Fig. 1 are, first, to switch in a new ferrite tuned circuit; second, to switch in a new ferrite base coupling winding; and third, to provide a means of coupling an external aerial to the new base coupling winding by way of an 0.01 μ F capacitor. The constructor should be readily able to devise a similar switching circuit for receivers whose existing switching arrangements vary from the particular example given in Fig. 1. The facility offered by the central position of S2 is not necessary for the present modification. It may be omitted, if desired, whereupon S2 can be a 2-way instead of a 3-way component.

SECOND HARMONIC OPERATION

Operating with the oscillator second harmonic has been used in commercial broadcast receivers, and is said to be capable of a sensitivity only 0.5dB down on the medium wave sensitivity of the receiver.

Coverage up to 3.8MHz is desirable, to include the 80 metre Amateur band, and for this the highest local oscillator frequency required is given by:

$$2f_o - 3,800 = 470$$

where f_o is the oscillator frequency in kHz, and the receiver i.f. is 470kHz.

Therefore,

$$f_o = \frac{470 + 3,800}{2} \\ = 2,135\text{kHz.}$$

The corresponding highest signal frequency with the aerial switch in the medium wave position is given by


$$f_s = 2,135 - 470 \\ = 1,665\text{kHz.}$$

The receiver must be aligned to place the high frequency end of the medium wave band at this point or slightly above. Although the top end of the medium wave band is usually reckoned to be 1,640 kHz, the new value of 1,665kHz should be attainable by adjustment of the oscillator trimmer capacitor; if necessary the oscillator coil core can also be adjusted, thus sacrificing a little low fre-

MAY 1970

RADIO CONSTRUCTOR

JUNE ISSUE

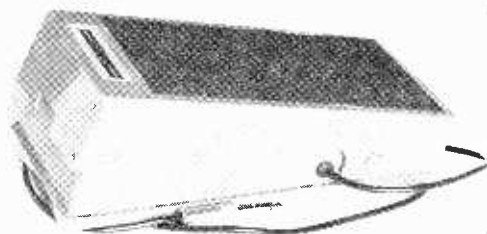

'WAH-WAH' PEDAL UNIT

With the aid of this unit the brilliance of electric guitar reproduction will be enhanced by providing a continuously variable frequency response which may be controlled by the guitar player's foot - resulting in the well-known 'wah-wah' effect often used to back up the performance of many leading professional groups.

CYBERNETIC CYNTHIA

The first of a 2-part series describing an electronic device having artificial intelligence. Cynthia, short for CYberNeTic Highly Intelligent Animal, is an electronic 'snail' who displays rudimentary reasoning power in her reactions to external stimuli. The device takes advantage of simple electronic logic circuits, and the more venturesome experimenter may wish to add his own ideas to those employed here.

SPRITE LITES

A very simple but highly efficient direct voltage to alternating voltage inverter circuit, using an OC35 transistor on a printed board assembly, is described in this article. Two versions are featured, one using an 8 watt and the other a 13 watt fluorescent tube. By means of this unit, mains-type lighting is provided from a 12 volt car battery. An ideal project for the camping, boating and caravan enthusiasts.

PLUS

- OTHER CONSTRUCTIONAL PROJECTS
- DATA SHEET 39
- SUPPORTING FEATURES

ON SALE JUNE 1st

quency end coverage of the medium and long wave bands. (In a transistor receiver the long wave band often uses the medium wave oscillator coil with extra capacitance added across it.) Let us assume that the low end of the medium wave band will be reached, after this adjustment, at 550kHz.

Then, the oscillator frequency will be 550 + 470, or 1,020kHz. The corresponding signal frequency on the new waveband will be

$$(2 \times 1,020) - 470 = 1,570\text{kHz.}$$

Thus the new wavebands will consist of a medium wave band of 550 to 1,665kHz and a "Trawler Band" of 1,570 to 3,800kHz.

Since the new band has the lower ratio of maximum to minimum frequency it will be easy to arrange for the correct swing by putting extra capacitance across the tuned winding of the new aerial. The value of this capacitance will be low enough to be provided by a small trimmer, the correct setting of which can be found by experiment. It can be shown (see Appendix) that, with a 208pF tuning capacitor the additional capacitance required is 16.5pF. This may be obtained by means of a 30pF trimmer, the exact setting of which can be found by experiment. If a larger tuning capacitor, of 408pF, is employed, the additional capacitance calculates at 33.5pF and may be provided in practice by a 50pF trimmer.

FERRITE AERIAL TURNS

It is easiest to introduce a completely new ferrite rod to carry the "Trawler Band" tuned aerial winding. The coupling between this winding and those for the medium and long wave bands will then be very small, and troubles due to self-resonance of one winding within the coverage of another will be avoided.

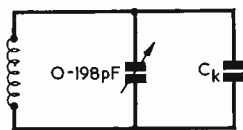


Fig. 2. Basic tuned circuit, as used for calculating the added capacitance required across the 'Trawler Band' tuned aerial winding

The number of turns required for the tuned winding will depend on the dimensions of the ferrite rod and the type of ganged capacitor used in the receiver to which it is added. In the author's receiver, with a signal gang section of 408pF, and a rod of 3/8 in. diameter and 8 in. long, the tuned winding required 17 turns. The wire employed was 9/46 s.w.g. stranded. This arrangement had an unloaded Q value of 140 at 4MHz and 220 at 1.55MHz (as measured on an Advance T2 Q-meter). If the more common 208pF tuning capacitor is used with the same ferrite rod, about 25 turns will be required. (Since the capacitance is halved the inductance must be doubled, and L varies as n². Thus the number of turns must be multiplied by √2.) Some final slight experimental adjustment of turns will, in any event, be very probably needed.

It was reckoned that the input impedance of a typical transistor mixer on the new band would be about 1kΩ. A resistor of this value was connected across coupling windings of various numbers of turns and it was found that 1½ turns loaded by 1kΩ gave loaded Q values of 72 at 4MHz and 140 at 1.55MHz, i.e. it reduced the Q roughly to half its unloaded value. Thus, near-optimum power transfer is obtained and the working Q is not too low to give reasonable protection against spurious responses, such as medium wave broadcast station breakthrough, which is a hazard with this type of mixer operation.

In general, the number of turns on the base coupling winding should be about one-twelfth of those on the tuned winding. In consequence, a coil with 25 turns on the tuned winding will require a base coupling winding of 2 turns. More turns than this may increase the signal at the mixer input, but will also increase the loading of the mixer on the tuned winding and reduce its working Q value.

CONSTRUCTION

The coil should be wound, single layer, on a former made by wrapping a strip of brown paper about 2 in. wide several times around the ferrite rod. The winding should be carried out with a tension such that the completed coil and former assembly will slide fairly easily on the rod, thereby allowing a certain amount of inductance adjustment. It is suggested that coils should first be wound dry and the ends secured by elastic bands until the correct number of turns for the tuned winding has been found experimentally. Then a final winding should be made, the turns being painted with low loss varnish as they are put on. A suitable varnish can be made by breaking up a piece of clear polystyrene and dissolving the pieces in benzene. (Benzene is the only common solvent for polystyrene which is non-polar, i.e. contains no (OH) molecules. It will produce a varnish which has low loss properties at r.f. and so will not lower the Q of the completed coil.

The mixer base coupling winding should be wound over or adjacent to the earthy end of the tuned winding.

Since the local oscillator sweep is the same for the 1,570 to 3,800kHz band as for the medium wave band, the receiver need only be calibrated for frequency on the broadcast bands. Dial readings for "Trawler Band" frequencies can then be calculated.

APPENDIX

We will next give an example of the calculation of additional capacitance across the aerial tuned circuit for a frequency coverage of 1,570 to 3,800kHz. A tuning capacitor of 10-208pF will be assumed.

In Fig. 2 the coil is tuned by a 10-198pF variable capacitor, the 10pF minimum being taken up in Ck, which is the total fixed capacitance.

$$\text{Since } f \text{ varies as } \frac{1}{\sqrt{C}},$$

$$\frac{f \text{ max}}{f \text{ min}} = \sqrt{\frac{198 + C_k}{C_k}}$$

At the same time, for medium wave coverage,

$$\frac{f_{\max}}{f_{\min}} = \frac{1,665}{550} = 3.03.$$

Thus,

$$\begin{aligned} \frac{198 + C_k}{C_k} &= 3.03^2 \\ C_k &= 9.18. \\ 198 &= 8.18C_k \\ \therefore C_k &= 24\text{pF (approx.)} \end{aligned}$$

For coverage of the new band,

$$\frac{f_{\max}}{f_{\min}} = \frac{3,800}{1,570} = 2.42.$$

So that (where C_k is the new total fixed capacitance),

$$\begin{aligned} \frac{198 + C_k}{C_k} &= 2.42^2 \\ C_k &= 5.9. \\ \therefore C_k &= \frac{198}{4.9} \\ &= 40.5\text{pF (approx.).} \end{aligned}$$

Thus, 16.5pF must be added and a 30pF trimmer would be suitable, the exact final setting being found by experiment. ■

REVERBERATION UNIT MARK 2

Regular readers will recall the 'Transistorised Reverberation Unit' which was described in the July 1969 issue of *The Radio Constructor*. The specialised components for this unit, or a complete kit of parts, have been available from Wilsic Electronics Ltd.

Wilsic Electronics have now produced a Mark 2 version of the reverberation unit, this differing slightly from the design described in the July 1969 issue. The main change is the provision of a single printed circuit for the electronic components, this replacing the previous main amplifier with separate pre-amplifiers and tagstrip assemblies. The stage line-up and operating principles remain unchanged, and all transistors are silicon devices.

The Mark 2 Reverberation Unit is now available in kit form from Wilsic Electronics Ltd., 6 Copley Road, Doncaster.

NORTH DEVON AMATEUR RADIO CLUB

The meetings of this club, newly formed, are held on the second and fourth Wednesday in each month at 7.30BST at 'Crinnis', High Wall, Sticklepath, Barnstaple.

At 6.30BST, prior to the general meeting, a study group for the RAE (including a morse class) is held. The next meetings will be held on 10th June (Lecture) and 24th June (Informal).

All are welcome and further enquiries should be directed to the Hon. Sec., H. G. Hughes, G4CG.

MAY 1970

HUBBLE BUBBLE— TOIL AND TROUBLE

Most of us I suppose engage in toil of one sort or another and have our share of trouble. Some have toil and trouble over it, others have trouble and toil over it, whilst many must be saddled with both sets of harness. Most of us wish we were entirely free of these twin afflictions which, like Tweedle-Dum and Tweedle-Dee, always seem to go together. It is probably symptomatic of human nature to envisage a world in which the denizens are complete strangers to the terrible twins of T and T! A world in which it would be impossible for the Wicked Witch to mutter the incantation "Hubble bubble, toil and trouble!" However, our world is as it is and not as we would like it to be.

We even have T & T in our home workshops. Take, for example, that latest multi-transistor or valved monstrosity spread out across the workbench. There it crouches menacingly, stubbornly refusing to work despite all efforts, glowering balefully and somewhat defiantly whilst, it seems, silently challenging us to make the *Thing* ackle!

With what high hopes we set out on some of these constructional projects – only to sometimes find that all our *initial* efforts are to no avail. We read the article in one of the excellent monthly journals, study the circuit and decide enthusiastically that this is the very project for us, that this is the design we have been waiting for and impetuously conclude that it is imperative we build it without delay. The snag is that *Trouble* besets us from the outset!

We must first obtain the components either by personally shopping around or by studying a catalogue and ordering through the post. One particular component it seems is either "temporarily out of stock and there is a long time delay before replenishment", or "it is out of production and discontinued" and/or "the specification has been changed". "Would we accept the enclosed component as a substitute?" Having reluctantly decided that we would, we now ruefully wonder if this particular component is the cause of all the head-scratching and the wilful refusal of our latest 'dear-to-one's-heart-project' to function properly – if at all!

Why is it, we ponder sadly, that the Editorial Staffs of radio magazines don't ensure that all components are currently obtainable when the article is published. The answer is, of course, that they do just that – the trouble lies not with the hard working Editorial Staffs but with factors outside their control. Manufacturers rarely inform them when a component is withdrawn from production, etc., despite the fact that it appears in their current catalogue – the main checking source!

During the inevitable delay from article checking to the time of publication it sometimes happens that the component in question vanishes from the scene – in which case not only is the constructor in trouble – so are the luckless Editorial Staffs who, by this time, most likely are bemoaning their fate! Despite the toil and trouble of checking catalogues, letter writing and telephone calls – all to ensure availability – the component then does the vanishing act!

Life isn't easy, it seems, either for Editorship or Readership – whichever course we sail we can all founder on the twin rocks of *Toil* and *Trouble*. *Hubble bubble!*

C.W. ■



Q
S
by **X**

FRANK A. BALDWIN
(All Times GMT)

● **AMATEUR BANDS**

Dx activity has been high on these bands in recent weeks with both s.s.b. and c.w. signals coming through at very good signal strengths. Any short wave listener who has been active over the period will have found plenty of interest in the Dx fare provided. We commence with—

1.8MHz

Top Band continued to carry Dx signals at the c.w. end of the band as the following shows—

CW: EUROPEAN

DL9KRA, EI9J, GI3JXS, GM3EZQ, GM3FSV/A, GM3IAA, GM3IGW/A, GM3TMK, GW3UCB, GW3UPK, HB9CM, HB9NL, HB9QA, OE1KU, OH2VO, OK1AF, OK1AHH, OK1AR, OK1ARB, OK1ARZ, OK1ATG, OK1ATP, OK1ATY, OK1AUK, OK1AUN, OK1AWQ, OK1AZZ, OK1DVK, OK1FBP, OK2BFN, OK2BMR, OK3CDO, OL5ACY, OL5AMT, OL6AKP, OL6AMB, OL6AMQ, OL7AM, OL8ANL, 4U1ITU, (U.N. Geneva).

CW: USA

K1BPW, K2GNC, K2IXJ, W1BB/1, W1HGT, W2GLL, W4BGO.

3.5MHz

CW: WB2IZG, WA3HOM, WA3NAZ, W3BY, WA4HAA, WA4LCO.

The s.s.b. end of this band continued to hold up for Dx signals especially around 0400 to 0600hrs.

SSB: HK3WO, HP1JC, K2DPA, K3UZE, TG9EP, VE1AMJ, VE2OB, W2AC, W2JBU, WB2LWH/VP9, W3BLS, W3GM, W4FIB, W4JNJ, W4NQM, W4RDV/P/VP9, W4ZFH, WA8OBG, WA8TPV, WA8VMQ, YV5BWG, 4X4BL.

7MHz

CW: AP5HQ, CO2DC, CO3DB, CO7VJ, CR6CA, CX2AN, K4BUR, PJ2HT, PY7CY, VE2BKA, W1MBB, WA2THA, W3HDQ, W3HQA, WA5GNM, W9JXX.

14MHz

As is usual, this band continued to carry most of the traffic and could be relied upon to provide Dx reception almost around the clock. One half-hour spent on the c.w. end of the band during the first week in April, from 2030 until 2059hrs, operating over the 14015 to 14075kHz range, produced the following — JA1KRU, JA8FGG, JH1BYJ, OX3UD, PY5ASN, PY7HO, ZM3BJ, ZS3CV and 6W8CQ.

CW: AP5HQ, AX2EK, AX3LV, CE3CF, CR6AL, CR6CA, CR6GO,

CX4CO, ET3USA, HS4ABV, JA2SFB, JA6KYS, JW7UH, KB6AG, KH6AG, KH6SP, KL7JDO, KP4ABD, KV4AB, LU6AX, OA4MS, OX3UD, OY1R, PJ2HT, PY6FI, PY7AEW, PY7AHO, PZ1NC, TG4SR, VK3KF, VK3MR, VQ8CR, ZC4BX, ZE1DL, ZL2CBO, ZM2CH, ZM3GQ, ZS3AG, ZS6ED, ZS6JK, 5S3KJ, 5V3RT, 5Z4KL, 9V1PB.

SSB: AX3BCM, CR6LF, HK4CAV, HP2EF, JX4YM, KV4AB, LU6AEC, OA4KY, PY7AL, VP2AZ, YA1HD, YS1ASE, ZL2JO, ZS1GP, ZS1HL, ZS1JA, 5Z4KM, 8P6AZ, 9L1RP, 9Y4MM.

HS4ABV gave his QTH as N.E. Thailand and his QSL manager as W5PJR. OA4KY gave his QTH as POB 538, Lima.

21MHz

CW: JA2AUB, KZ5KBN, LU3DD, PY2DRP, TG4SR, XE1JO, ZC4CB, ZS6AR.

SSB: EL8RL, KG4AA, XE1FR, ZS6OS.

That completes the Amateur band roundup, except for a brief visit to **28MHz** which produced, on c.w., HC1TH, PJ2HT and ZE1DC.

Before going on to the Broadcast bands, I should thank Dick Donald, ZL1AYH, for sending along his QSL card consequent upon his callsign appearing on this page. Dick tells me it is his pleasure to QSL all SWL's who care to send him, a report. The address is: 27 Tauranga Road, Waihi, New Zealand.

● **BROADCAST BANDS**

The season for reception of the South American stations is now upon us as the following report illustrates. The best listening times for S. American reception is from midnight to 0500hrs.

3940kHz 1700 Peshawar, Pakistan, with Asian-type music and 6 'pips' followed by newscast in dialect. Closes at 1730. This station is unlisted and was finally identified after many listening sessions over a period of 3 weeks!

4690kHz 0500 San Jose, Costa Rica, with Latin American songs and the identification "Radio Reloj".

4712.5kHz 0315 HCAV3 Loja, Ecuador, with Latin American songs and music. Identification as "Radio Luz y Vida".

4755kHz 0415 HJKC Bogota, Colombia, radiating typical S. American music with identification as "Emisora Nuevo Mundo". Bogota is the capital city, located in E. Cordilleras 9,000ft. above sea level.

4770kHz 0330 HCJF2 R.Guayaquil, Ecuador, featuring a programme of Latin American music. Coca Cola advert and identification at time stated.

4795kHz 0400 HIAS Santa Domingo, Dominican Republic, with identification as "Onda Musical" followed by 'pop' records.

4906kHz 0420 HJAG Barranquilla, Colombia, with Latin American music and identification as "Emisora Atlantico". Identification again repeated at 0435. This station is listed as inactive! Barranquilla is a port near the mouth of the river Magdalena.

4915kHz 0415 HJSG Valledupar, Colombia, radiating songs, music in the usual exotic style and station identification as "Radio Guatapuri".

4920kHz 0625 YVKR Caracas, Venezuela, with a programme of 'pop' music and identification. Caracas is the capital city located 8 miles inland from its port, La Guaira.

4955kHz 0347 HJCC Bogota, Colombia, with 3 chimes, identification and closing down.

4960kHz 0345 YVQA Cumana, Venezuela, heard with 4 chimes and station identification. Cumana is on the north coast of Venezuela.

4995kHz 2210 ZYX2 Goiania, Brazil, with newscast in Portuguese. Goiania is the capital city of the mountainous and forested Goias State in central Brazil and is situated on the Vermelho river.

5045kHz 0450 CP38 La Paz, Bolivia, with Latin American music and identification "Radio Altiplano". La Paz is the capital city of the department of that name and the seat of government, although the legal capital is Sucre. The Department is traversed by the high Andean range — hence the station identification.

5093kHz 0402 HJGG Bogota, Colombia, with newscast in Spanish, 3 chimes and identification.

● **BEGINNERS CORNER**

This month we present for beginners firstly two easily received stations and two that will prove more difficult.

9665kHz 1600 Stockholm, Sweden, with news in English.

17880kHz 0745 CSA45 Lisbon, Portugal, with the English programme.

11795kHz 2130 WINB Red Lion, Pennsylvania, USA, with identification.

9485kHz 1445 Radio Pakistan with Asian type music. Identification and news in English at 1500. This is a new and unlisted channel.

● **ASIAN STATIONS**

Should any beginner wish to try these, here are some recently logged — **9480kHz 1505** Peking; **11705kHz 1230** Tokio; **15013kHz 2000** Hanoi; **17795kHz 0804** Peking and **17855kHz 0758** Tokio.

At the times stated, NHK Tokio can easily be recognised by the tinkling musical box interval signal and identification in English, Hanoi features a programme in English, whilst more difficult to identify, Peking radiates programmes in a Chinese dialect. ■

THE "FETAFLX 4" TRANSISTOR PORTABLE

(Part 2)

by


SIR DOUGLAS HALL, K.C.M.G., M.A. (Oxon)

In this concluding article our contributor describes the assembly and setting up of the "Fetaflex 4" receiver. Also dealt with is the construction of a neat functional cabinet which can be readily made up in the home workshop

WITH THE "FETAFLX 4" design it is essential that the relative positions of L1, L2 and L3 be correct when laying out the receiver. Apart from that, the exact positioning of components is not unduly critical provided


common sense is used, and convenience may dictate slightly different positions for some parts from those in the author's layout, which is illustrated in Fig. 3.

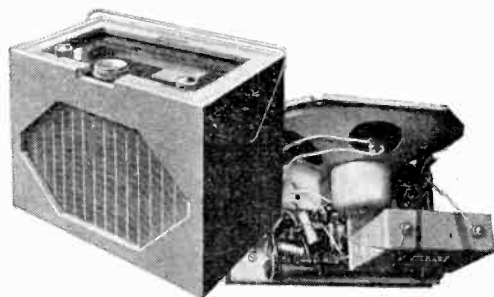Most of the components are mounted on a 16-way groupboard



(cut down from a Radiospares "Standard" 18-way groupboard) which is fitted on a piece of plywood, 8in. by 5in. as shown in Fig. 3. T1 may be fixed in position with adhesive, as it is very light. T2 is mounted on the plywood, a convenient method consisting of passing screws through solder tags soldered to the feet of its clamp, the feet being bent through 90 degrees.

Ferrite aerial coil L1 has 55 turns of 32 s.w.g. enamelled wire, close-wound on a paper sleeve able to slide along a 6in. by 3/4in. ferrite rod. L2 has 200 turns of 38 s.w.g. enamelled wire close-wound on a similar sleeve able to slide along a 5in. by 3/4in. rod. (The 5in. rod is available from G. W. Smith and Co. (Radio) Ltd., 3 Lisle St., London W.C.2.) The rods have rubber

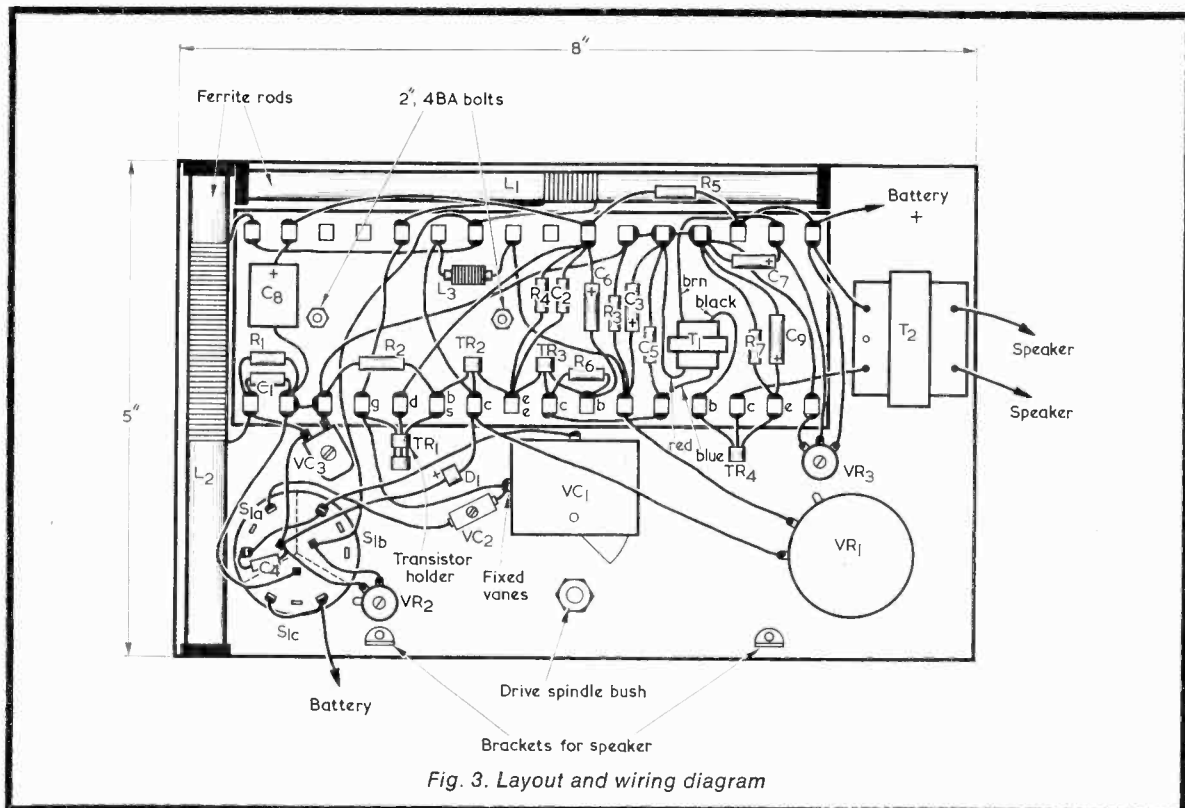

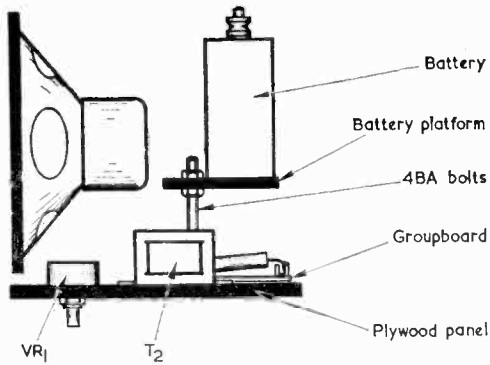


Fig. 4. Detail showing the position taken up by the battery platform

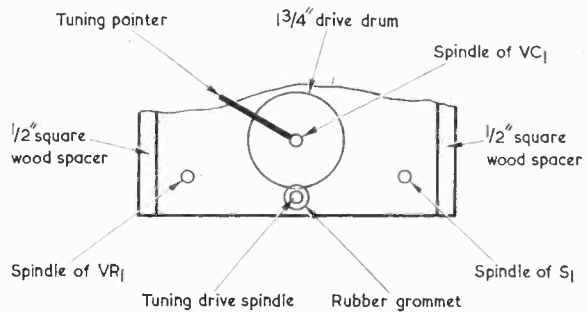


Fig. 5. How the tuning drive is assembled

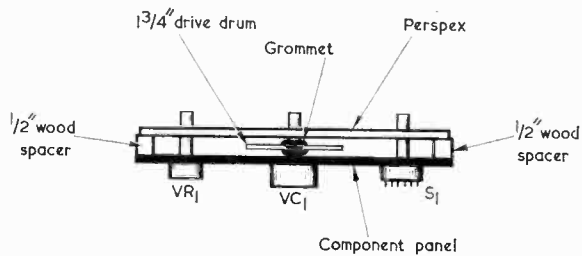


Fig. 6. Side view, showing the Perspex panel

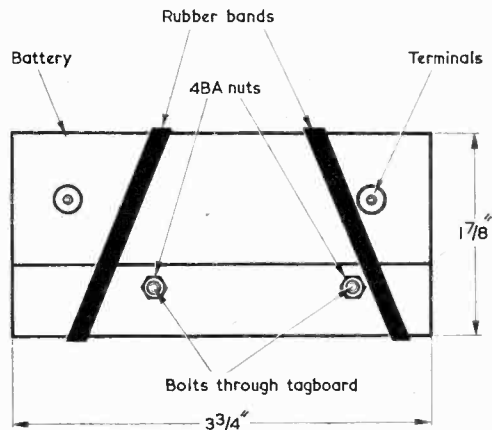


Fig. 7. Top view of the battery on its platform

grommets fitted at each end which are tied with cord (not wire) through suitable small holes in the plywood panel. L3 is mounted as shown, so that the axis of its core is parallel to the axis of L1.

The gate insulation of TR1 can be broken down very easily by static voltages, or by the voltage on the tip of an unearthed soldering iron. Because of this a transistor holder is included in the Components List, and this *must* be used. Make all the connections for TR1 to this holder and then insert the f.e.t. afterwards. In this circuit no connection is made to the substrate lead-out of TR1.

Switch S1 is shown as a 3-pole 3-way miniature rotary switch in Figs. 2 and 3. However, it will probably be found easier to obtain a 4-pole 3-way miniature rotary switch and such a component can, of course, be used with one of the poles ignored. Before wiring the switch into circuit identify, with a continuity meter or by visual inspection, the outside tags which correspond to the individual switch arm tags. The relative tag positioning may vary, with some switches, from that shown in Fig. 3.

It may be necessary to shorten the spindle of VC1 to ensure that it does not foul the underside of a Perspex panel which is fitted after the receiver has been set up. Details of the panel and its mounting are given later under "Tuning Drive", and the information given there should be read before cutting the

capacitor spindle. The spindle should be cut before the capacitor is mounted in position. Use a junior hacksaw with the unwanted length of spindle held securely in a vice.

Note the two 2in. 4BA bolts which pass through appropriate holes in the tag board. These serve to hold the board to the plywood panel, and will later take a small platform on which the battery is held in place, as illustrated in Fig. 4. The bolts should be in position before any components are wired in. Note also the small brackets for holding the 8 by 5in. speaker in place. The exact positions for these brackets will depend on the

spacing between the two holes in the speaker frame through which this component will be bolted to the brackets. The shape and depth of the speaker may also determine, to some extent, the exact positions of the holes through the panel required to take S1, VC1 and VR1. Thus, the speaker should be temporarily placed in position to assist in marking out the holes for these three components.

A drive is required for VC1, and this is discussed later.

SETTING UP

When construction has been completed as shown in Fig. 3, the receiver may be set up. At this stage the speaker is connected but not mounted in position. The battery platform is also not fitted.

VR3 should be initially adjusted so that its slider is at the end of the track connected to the negative supply line. A No. 126 4.5 volt battery is connected up with a meter, set to give a clear reading of 26mA, inserted in the positive lead. Switch on and adjust VR3 so that a reading of 26mA is shown and held after the receiver has been switched on for about 10 minutes, then switch off again.

Next, L1 should be set at the extreme right hand end of the rod (right hand as shown in Fig. 3), VC3 adjusted to about half of full tightness, and VC1 set with its vanes about three-quarters enmeshed. Switch S1 to medium waves. There may be oscillation, even with VR1 at or near zero resistance, in which case remove L1 from the rod, turn it through 180 degrees and replace it on the rod. Alternatively, change over the connections to the leads of L1. If oscillation still takes place with VR1 set well back, move L1 towards the middle of the rod until

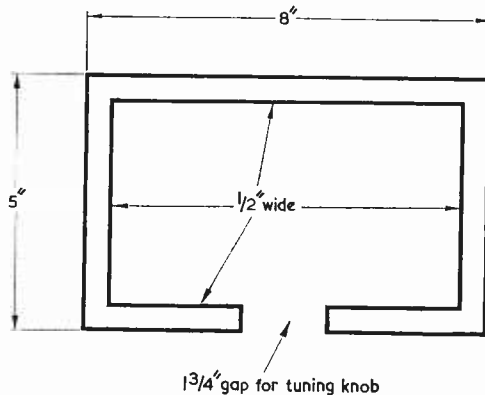


Fig. 8. This plywood frame fits over the Perspex panel

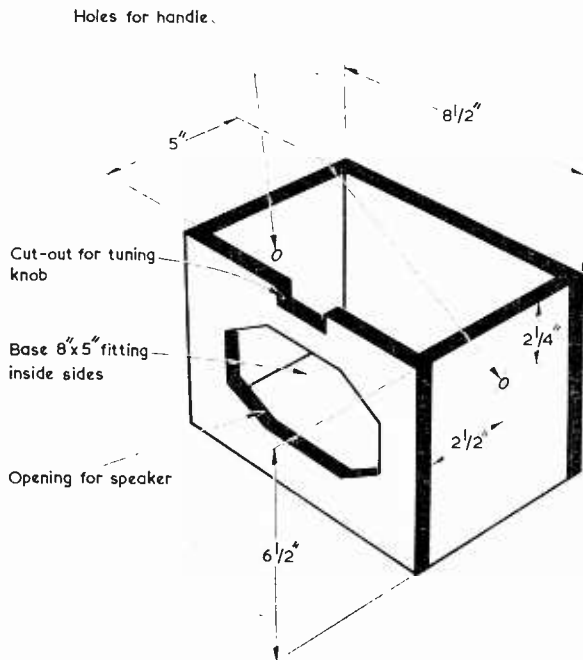


Fig. 9. The receiver cabinet. The dimensions given here are for guidance and may require slight modification

(Continued on page 627)



Cover Feature

C.R.O. BEAM SWITCHING

Incorporating standard parts in a simple single-beam oscilloscope to display simultaneous signals

P. CAIRNS, A.I.


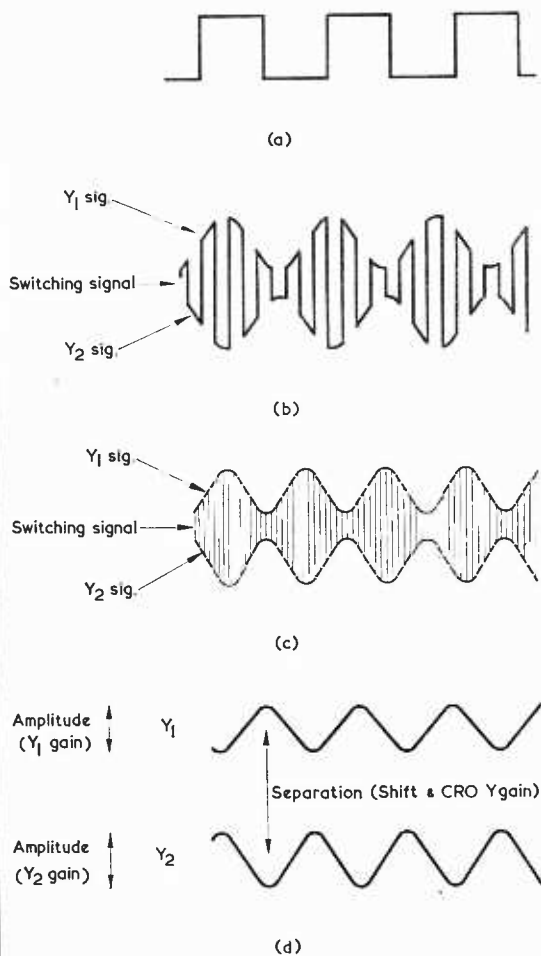


Fig. 1(a). The basic switching waveform
 (b). Showing the effect of sampling two traces with the aid of the switching waveform. Trace frequency here is only slightly lower than switching frequency
 (c). A 'dotting' effect is evident for a lower trace frequency, and the switching waveform is not clearly discernable
 (d). The 'dotting' effect and switching waveform disappear at still lower trace frequencies. The two traces now appear continuous, due to persistence in the human eye and the c.r.t. phosphor

THIS ARTICLE DESCRIBES A SIMPLE THOUGH USEFUL transistor beam switching unit suitable for use with almost all types of cathode ray oscilloscope. As may be observed from the accompanying specification, it compares favourably with many much more complex circuits which have been produced from time to time. Like all beam switching circuits it has very definite limitations but should still prove very useful for low frequency and audio work by allowing the more basic facilities of a double-beam oscilloscope to be utilised with a single-beam instrument. Such a device is particularly useful for the direct observation of phase shifts between signals and simultaneous input-output levels in low frequency and audio circuits.

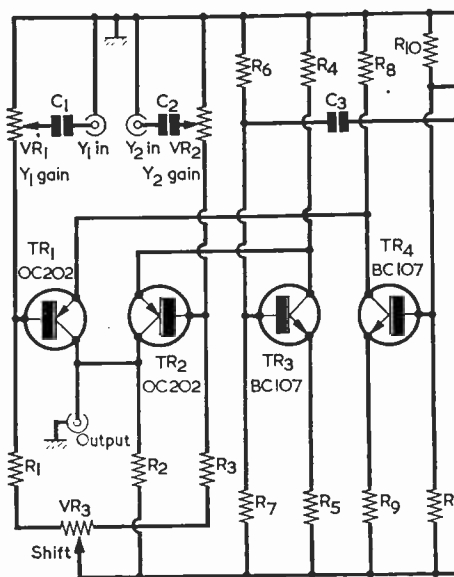

OC202
Lead-outs

Fig. 2. Complete circuit diagram THE RADIO CONSTRUCTOR

SWITCHING UNIT



COMPONENTS


circuit, this beam switching unit allows two completely separate traces at the same time

I.P.R.E., G3ISP

DESIGN APPROACH

When considering the design of a circuit of this nature many conflicting factors have to be allowed for. Basically, no form of beam switching can be considered as a satisfactory substitute for a double-beam oscilloscope employing a double gun or beam splitting cathode ray tube; at best it is only a compromise. This does not detract, however, from the fact that in certain situations some method of beam switching will achieve results which could otherwise not be easily obtained on a single-beam instrument.

Beam switching is basically a method of sampling two (or sometimes more than two) signals and displaying them simultaneously but separately on a

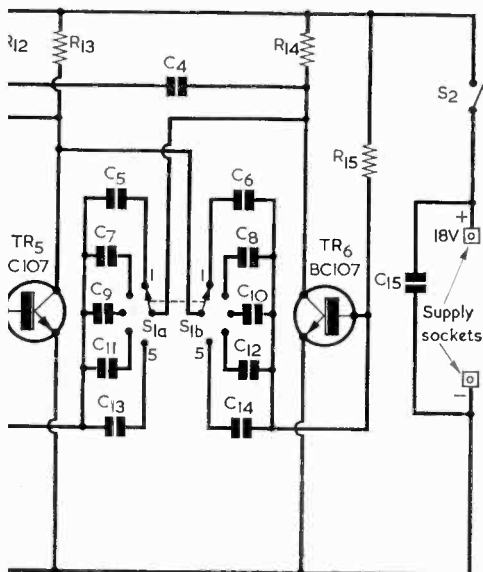

BC107
Lead-outs

for the beam switching unit

MAY 1970

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

R1	22k Ω
R2	1.5k Ω
R3	22k Ω
R4	560 Ω
R5	270 Ω
R6	68k Ω
R7	5.6k Ω
R8	560 Ω
R9	270 Ω
R10	68k Ω
R11	5.6k Ω
R12	56k Ω
R13	5.6k Ω
R14	5.6k Ω
R15	56k Ω
VR1	10k Ω potentiometer, linear, wire-wound
VR2	10k Ω potentiometer, linear, wire-wound
VR3	100k Ω potentiometer, linear, wire-wound

Capacitors

(All paper capacitors 50V wkg.)

C1	2.2 μ F, paper
C2	2.2 μ F, paper
C3	1 μ F, paper
C4	1 μ F, paper
C5	0.01 μ F, paper
C6	0.01 μ F, paper
C7	0.0047 μ F, paper
C8	0.0047 μ F, paper
C9	0.0022 μ F, paper
C10	0.0022 μ F, paper
C11	0.001 μ F, silver-mica
C12	0.001 μ F, silver-mica
C13	470pF, silver-mica
C14	470pF, silver-mica
C15	0.5 μ F, paper

Transistors

TR1, TR2	OC202 (Mullard)
TR3-TR6	BC107 (Mullard)

Switches


S1 (a) (b)	2-pole 5-way, Yaxley
S2	s.p.s.t., toggle

Sockets

- 3 coaxial sockets
- 2 single insulated sockets (for Belling-Lee O-Z plugs, or banana plugs)

Miscellaneous

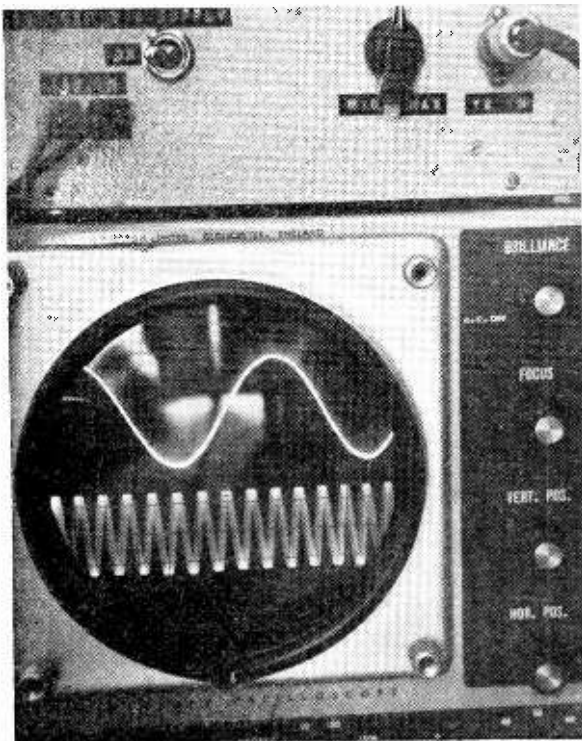- Printed circuit board or Veroboard (see text)
- 4 pointer knobs
- Cabinet, 8 x 6 x 6in., Type W, H. L. Smith & Co. Ltd.
- Aluminium sheet for sub-chassis



The beam switching unit in action. Here, an oscilloscope simultaneously displays two completely separate traces

single-beam deflection system. This is achieved by having two identical amplifiers which are alternately switched on and off at a frequency much faster than the frequency of the two input signals being applied to the amplifiers. By using a square wave having a fast rise and fall time a small portion of each input signal is alternately displayed on the top and bottom edges of the square wave. The faster the switching frequency compared with the signal frequency, the cleaner the display appears on the tube face. As the signal frequency approaches the switching frequency a definite dotting appears on the display, thus limiting the use of the device to the lower frequency range.

The design of a beam switching unit for the display of high frequencies involves much more complex circuits, with an attendant increase in expense,

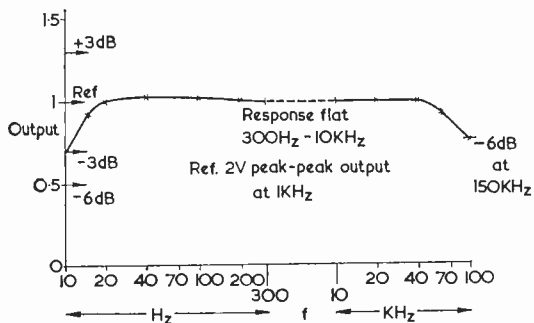


Fig. 3. Response curve of the prototype Y amplifiers

and in practice is very seldom an economic proposition. The method by which a beam switching display functions is illustrated in Fig. 1 (a) to (d). The fact that the alternate gaps in the upper and lower traces are not noticeable with a high signal to switching frequency ratio is due to the comparatively long persistence of the human eye and also, to some extent, to the phosphor persistence of the cathode ray tube.

In practice, switching speeds in the order of fifteen to twenty times the signal frequency are necessary if a useful display is to be obtained. Other features which are desirable with beam switching circuits are independent gain controls on both signal inputs, provision for selecting a number of different switching speeds and a shift control which allows the upper and lower traces to be either transposed or superimposed, one over the other. There should also be the minimum of interaction between the two amplifiers and their controls. A reasonable frequency response is also desirable, despite the frequency limitations of these units, as it is often desired to display square waves with quite fast rise and fall times. Also, the amplifiers have to cope with the relatively fast switching times. A small degree of gain in the amplifiers is often an advantage though of rather less importance than the other features mentioned.

Despite its simplicity and the fact that only six transistors are used, the circuit shown in Fig. 2 achieves, to a greater or lesser extent, all of the above requirements. The relatively low gain of X2 per channel is accompanied by a good bandwidth, being only 3dB down at 100kHz. As signal frequencies much higher than 2kHz are approaching

SPECIFICATION

- Maximum input per channel: 2V peak-to-peak
- Maximum output per channel: 4V peak-to-peak
- Gain per channel: X2
- Maximum switching amplitude: 8V peak-to-peak
- Frequency response per channel: -3dB at 10Hz and 100kHz; -6dB at 150 kHz. (See Fig. 3)
- Input impedance per channel: 5kΩ approx. at 1kHz
- Output impedance: less than 1kΩ
- Beam switching speeds: 2kHz to 40kHz in 5 steps
- Supply: 18V d.c. from internal battery or external supply; drain 25mA
- Dimensions: Height 6in., width 8in., depth 6in.

the upper useful limit of the unit, such a bandwidth is adequate for the display of square and pulse waveforms. A complete frequency response characteristic is shown in Fig. 3. Switching speeds are covered in five switched steps from 2 to 40kHz. Both amplifiers have independent gain controls while a shift control allows both traces to be transposed or superimposed at will. The output switching pulse is of sufficient amplitude to allow two 4-volt peak-to-peak signals to be displayed simultaneously without overlapping. Throughout the design, components of standard type only are used.

CIRCUIT OPERATION

The functioning of the circuit, shown in Fig 2, may be explained in the following manner. TR5 and TR6 form a conventional astable multivibrator,

THE RADIO CONSTRUCTOR


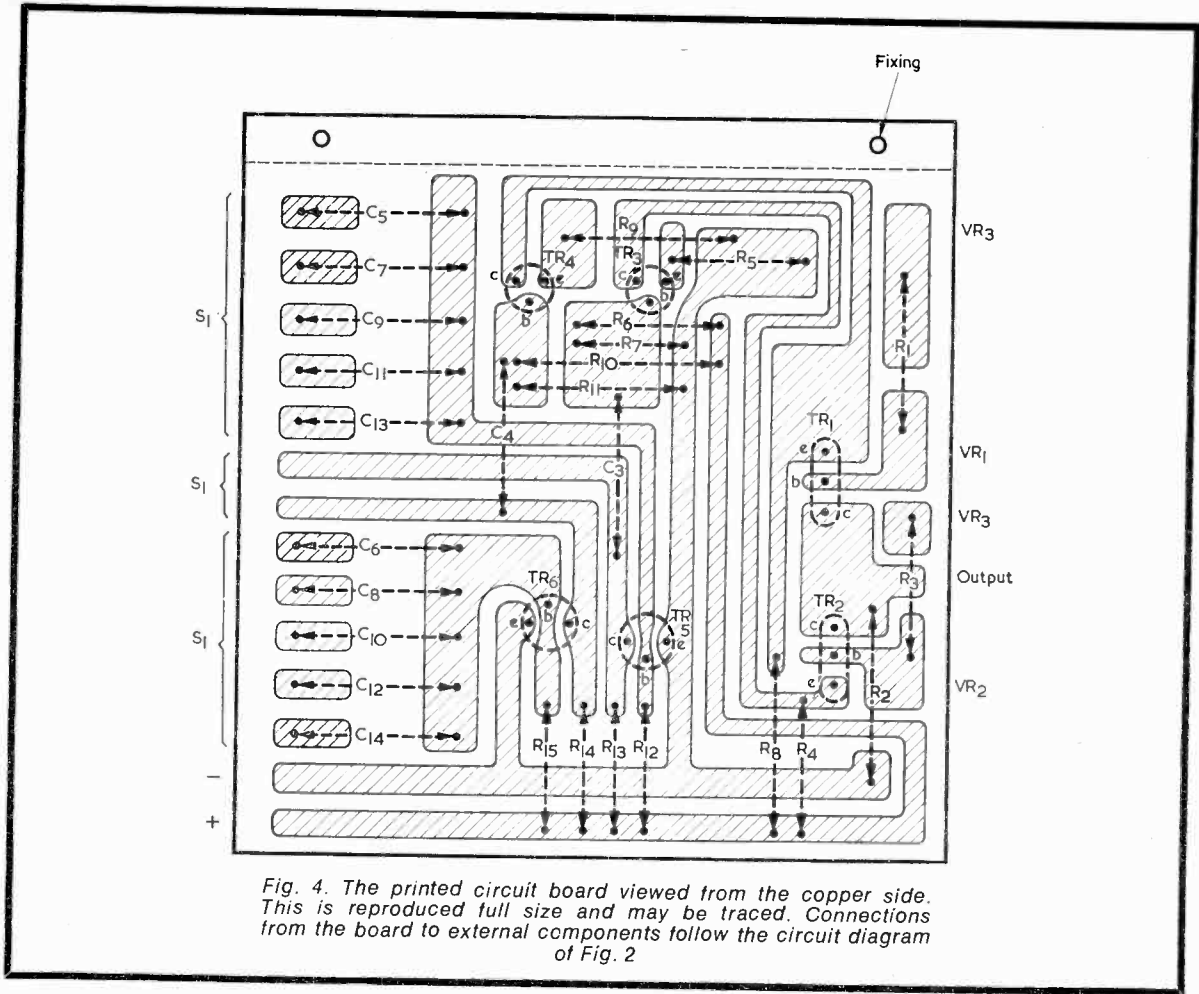


Fig. 4. The printed circuit board viewed from the copper side. This is reproduced full size and may be traced. Connections from the board to external components follow the circuit diagram of Fig. 2

the various switching speeds being selected by S1, which selects the capacitors C5 to C13 in one bank and C6 to C14 in the other bank. These alter the time constant and thus the switching speed of the circuit. A square wave is thus developed across each load resistor, R13, R14, in turn, each transistor being alternately switched on and off. The outputs obtained at the collectors of these transistors are two square waves which are effectively 180° out of phase. These are coupled to the two switching transistors, TR3 and TR4, by the coupling and d.c. blocking capacitors, C3, C4. These are of sufficiently large value to maintain a good low frequency response and so preserve a good waveform.

The resistor dividers, R6-R7, and R10-R11, keep the bases of TR3 and TR4 at a fixed d.c. level and provide biasing. The emitter resistors R5 and R9 provide a large measure of negative feedback and maintain the emitters at a fixed potential above the negative supply line, while the output signal is developed across the load resistors R4 and R8. These resistor networks maintain the selected d.c. conditions of the transistors and allow an output waveform of large amplitude and fast rise and fall time to be made available for driving the amplifier stages. The signals applied to the bases of TR3 and TR4, being quite large in amplitude, ensure

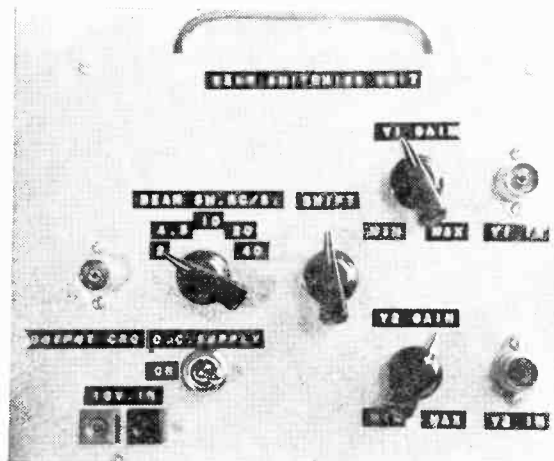that these switching transistors are driven very hard between their on and off conditions. The waveform obtained at the collectors of these transistors are therefore a larger and squarer (faster rise and fall) replica of the multivibrator outputs. Thus



Front panel of the prototype switching unit

when TR3 is cut off TR4 is bottomed and vice versa, the transition between these two states being very fast and the frequency of transition being dependent upon the frequency of the multivibrator.

TABLE

CIRCUIT MEASUREMENTS

Frequencies. Measured frequencies of beam switching speeds: (1) 1,920Hz; (2) 4,330Hz; (3) 9,360Hz; (4) 20.24kHz; (5) 41.51kHz.

Impedances. Measured input impedances at 1kHz (VR1, VR2 at max. settings): Y1, 4.6Ω; Y2, 4.8kΩ. Measured output impedance at 1kHz: 820Ω.

Voltages. All voltages measured with 20kΩ/volt instrument and are with respect to positive line. Gain controls at minimum, shift control central and fastest switching speed (5) selected.

D.C. supply	-18V
TR1, TR2 base	-2V (-1.2 to -5.3V for full turn of VR3)
TR1, TR2 collector	-14.5V (-11.5 to -14.8V for full turn of VR3)
TR3, TR4 collector	-5.7V (-5.5V to -7.3V for full turn of VR3)
TR3, TR4 emitter	-15.6V
TR3, TR4 base	-17.3V
TR3, TR6 collector	-13.4V
Current. Measured current drain from 18V supply:	25.8mA

controls VR1, VR2, and s0 to the bases of the transistors. The gain controls, R1, R3 and VR3 form the divider network for maintaining the d.c. conditions on the two bases and supplying the necessary d.c. bias. In this case, however, the positive ends of the dividers are commoned into the shift control VR3. This allows the standing d.c. level on either base to be raised or lowered by a fixed amount. As one base is raised the other is lowered by a corresponding amount and vice versa. The two collectors are connected to a common load, R2, across which the composite output signal is developed and fed to the c.r.o. input.

The standing d.c. voltage on the common collector output of TR1 and TR2 is blocked by the Y amplifier input capacitor in the c.r.o. In the case of oscilloscopes with switched d.c. or a.c. inputs, the a.c. input is of course selected.

It will be noticed that TR1 and TR2 are p.n.p. transistors and are thus complementary to the switching transistors, which are n.p.n. The emitters of TR1 and TR2 can therefore be d.c. coupled to the collectors of the switching transistors. Thus R4 and R8 are not only the collector loads of the switching transistors but act as emitter resistors for the signal amplifiers. This allows a measure of negative feedback to be applied to the amplifiers as they are switched. Since TR3 and TR4 are being alternatively driven on and off, the emitters of TR1 and TR2 will be switched on and off in turn. The two amplifiers will therefore be driven on and off and so provide the desired beam switching effect.

The unit is fed from an 18 volt d.c. supply, either an external power unit or two 9 volt batteries in series being used. As the current drain is only in the region of 25mA and beam switching units are generally used only intermittently, two batteries of the type employed for transistor radios will last quite some time. The d.c. supply is decoupled by C15 and if an internal battery is used the sockets provided for an external supply allow the battery voltage to be checked without removing the unit

Transistors TR1 and TR2 are the signal amplifiers. The two input signals for display are fed via the blocking capacitors C1, C2, to the gain

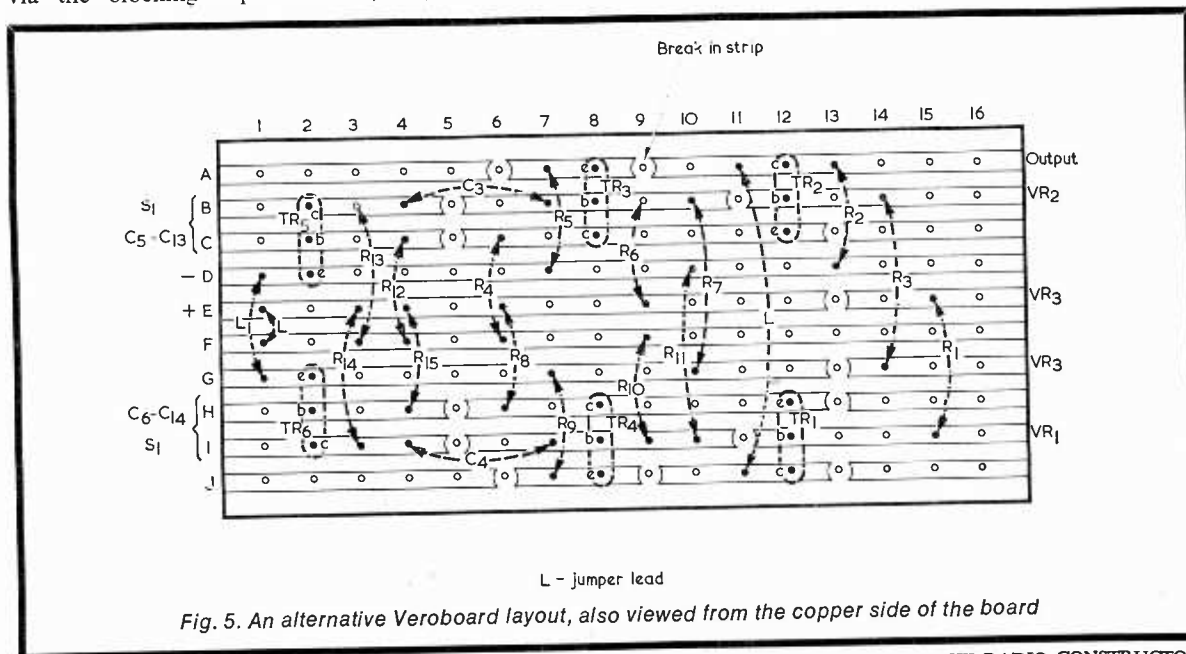


Fig. 5. An alternative Veroboard layout, also viewed from the copper side of the board

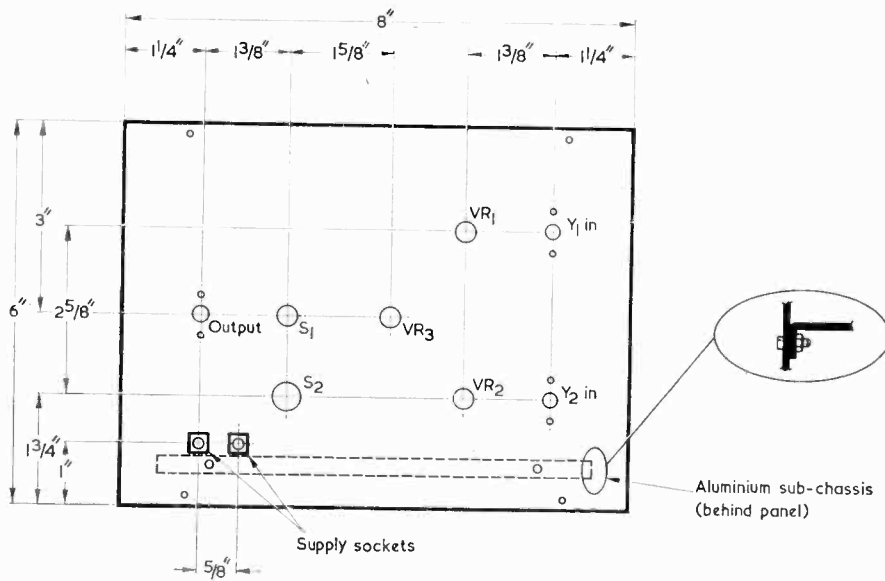


Fig. 6. Drilling dimensions and component layout for the front panel. A side view showing the method of securing the sub-chassis is given in the inset

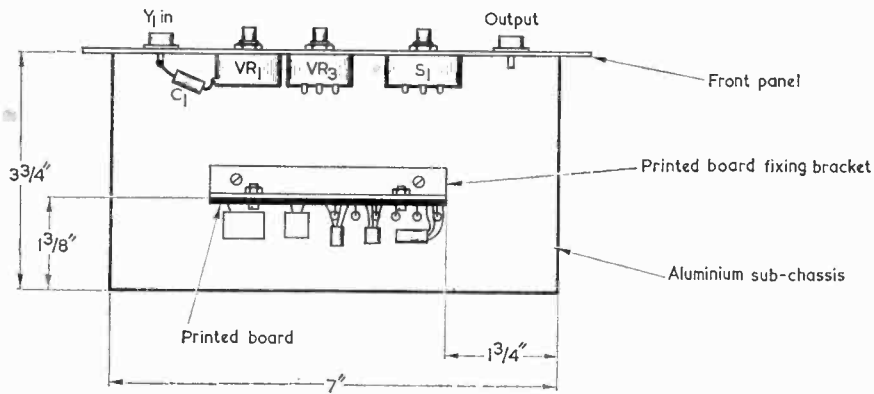


Fig. 7. Top view of the assembly with a printed circuit board

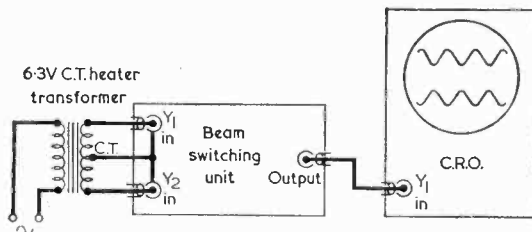



Fig. 8. A simple method of checking the beam switching unit

from its case. If desired, C15 may be connected, alternatively, after switch S2.

VR1 and VR2 are specified as wirewound since these types normally last longer, from the physical wear and tear point of view, than carbon track potentiometers. They also produce less noise. Tests showed that any inductance introduced by wirewound potentiometers in the VR1 and VR2 positions had no noticeable effect on the performance of the circuit.

CONSTRUCTION

The construction of the beam switching unit is quite straightforward. While the type of cabinet used by the writer is quoted in the Components List, any form of cabinet and layout may be used to suit individual requirements. There is nothing particularly critical about the layout and construction. Most of the smaller components are best mounted on printed circuit board or Veroboard, full details together with component layout for both types of board being illustrated in Figs. 4 and 5. An alternative method, though not so neat, is to mount all the components on a large tag board or tag strip. Provided interconnecting wires are kept as short as possible no fall-off in performance should be noticed. Indeed, the original model for checking circuit operation was constructed by the writer in this fashion without any problems being encountered.

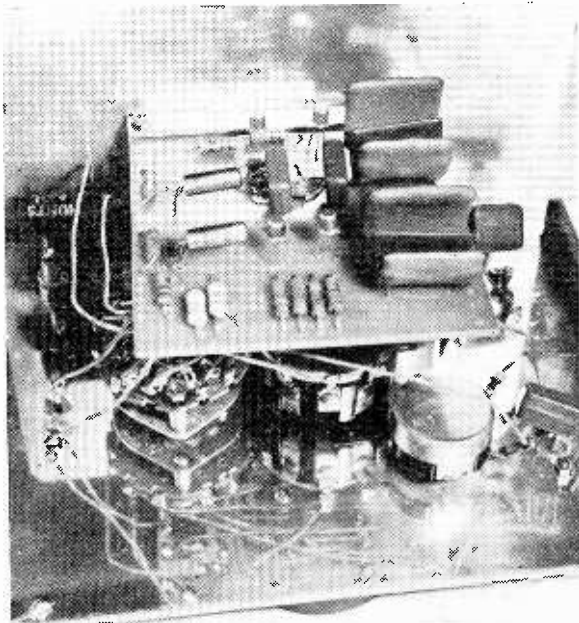

A view behind the panel, showing the position taken up by the printed circuit board

The Veroboard employed by the author for the layout shown in Fig. 5 had a matrix of 0.2in. However, the more readily available 0.15in. Veroboard may be employed instead, if desired. It should be mentioned that the collector of the BC107 is common with its case.

The front panel layout with relevant dimensions

is shown in Fig. 6. All necessary front panel wiring is connected before the printed board of Veroboard and its associated sub-chassis are mounted. The board, complete with components, is mounted by means of a small angle bracket to a flat aluminium sub-chassis having a lip bent along one edge for clamping to the front panel by means of 6BA screws. This is shown in Fig. 7. As may be seen, the actual component board is mounted edge-wise on the chassis and parallel to the front panel. Connections between the board and front panel components are as short and direct as possible.

The multivibrator capacitors, C5 to C14 are mounted on the board when a printed circuit is used, but not when Veroboard is employed. In the latter case they are mounted directly on the switch wafer. This method of wiring reduces the size of the Veroboard which would otherwise be necessary.

Final embellishments in the way of rubber feet and carrying handle may be added as desired.

TESTING AND SETTING UP

No elaborate testing or setting up should be necessary. Before switching on, however, check the circuit wiring and transistor connections, remembering that both p.n.p. and n.p.n. types are used. Connect the output of the switching unit to the c.r.o. Y input, the Y sensitivity of the oscilloscope being set to about 0.5 to 1V/cm. The trigger or sync. control should be set for internal operation and the c.r.o. time base to a relatively slow speed, 10 to 50 millise./cm being suitable. The Y shift control on the switching unit should be set to either extreme of its travel, the two Y gain controls being set to about mid-point. The switching speed is set to position 4 or position 5.

When the unit is switched on, two separate time base lines should be observed on the oscilloscope. The shift control on the switching unit should allow these lines to be superimposed or changed completely over, upper to lower and vice versa. With the shift control set to one extreme the oscilloscope Y gain should be adjusted to give a suitable separation on the tube face. The brightness should be kept as low as possible to prevent "haze" between the upper and lower beams.

Two low frequency signals can now be applied to the Y1 and Y2 inputs to try out the unit, the 50Hz output from a centre-tapped heater transformer secondary being ideal. This circuit can be connected up as shown in Fig. 8. With the two signals applied, the Y1 and Y2 gain controls are adjusted until both traces are of the same amplitude and the lowermost sections of the upper signal are not quite overlapping the uppermost sections of the lower signal. No clipping should be present under these maximum signal conditions. The shift control will allow the vertical positions of the two signals to be changed with respect to one another. If the beam switching speed is reduced the "dotting" effect mentioned earlier can be observed.

Having satisfactorily completed these tests the instrument is ready for use, and should prove a useful and reliable accessory for any oscilloscope. As an aid to servicing or fault-finding, measurements taken throughout the circuit are listed in the accompanying Table.



UNDERSTANDING TAPE RECORDING

by W. G. Morley

THE DOMESTIC TAPE RECORDER has nowadays become such an accepted feature of modern life that there must be very few people who, even if they have not actually operated a recorder, have not at least observed one in use.

The fundamental steps involved in the use of a tape recorder are simple and well-known. If we have a recorder of the familiar domestic type and wish to employ this for recording say, a spoken message, we commence by switching the instrument to the 'Record' function. A motor causes the magnetic recording tape to be drawn across the *record-playback head* of the recorder, and we then speak into its microphone. When we have finished we switch the recorder so that it re-winds the tape after which, having selected the 'Playback' function, we run it past the record-playback head once more. We are then able to hear the message we have previously recorded from the loudspeaker of the recorder.

RECORDING AND PLAYBACK


The electronic circuits we have set up in this simple example of tape recorder use are illustrated, in very simplified form, in the block diagram of Fig. 1. In Fig. 1(a) we have the situation where we record the message. Here, the electrical output of the microphone is applied to the input of an a.f. amplifier, an amplified signal being then passed to the record-playback head. This carries out the recording function and causes the signal to be recorded on the tape. Fig. 1(b) shows what occurs when we play back the recording. The record-playback head now provides a playback function, and its output is fed to an a.f. amplifier. The amplifier then drives the loudspeaker.

An amplifier is required for both the record and playback processes. It is necessary for recording partly because the electrical output from the microphone in Fig. 1(a) is not

This is the first of a new series which sets out to describe, in simple terms, exactly what occurs during the processes of recording and playing back a signal on a tape recorder. The article published this month discusses the function of recording, and deals also with constant current drive and the frequency response required in the recording amplifier

sufficiently large to be applied directly to the record-playback head; and it is necessary for playback partly because the output from the record-playback head in Fig. 1 (b) is not powerful enough to drive the loudspeaker.

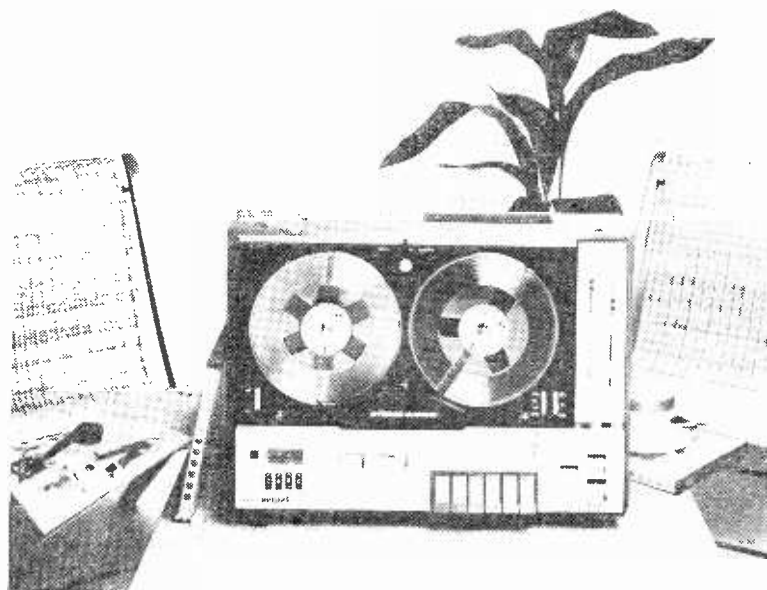Up to now we have referred to recorders having a single record-playback head which is capable of both recording the signal onto the tape and of retrieving it afterwards during playback. The use of a single dual-function head in this



An excellent example of modern styling and engineering. This is the Phillips mains operated stereo tape recorder type N4500, which is designed to very high standards and incorporates a pre-amplifier unit

manner is very common in lower-price domestic recorders. More expensive instruments, and particularly those intended for 'professional' applications, frequently have separate record and playback heads, one being designed to offer optimum performance for recording and the other to offer optimum performance for playback. However, it is possible to obtain extremely good results with a single record-playback head, and the obvious economy which results makes the use of such a head attractive for machines intended for the domestic market. (Before leaving this particular subject it may be added, incidentally, that the use of separate record and playback heads enables a recording to be monitored whilst it is being made. This is done by positioning the playback head so that the tape passes over it after leaving the record head.)

Since an amplifier is required both for record and for playback, a useful saving in costs may be effected by employing a single amplifier for both functions. A typical instance, as encountered in domestic recorders, is shown in Fig. 1(c) where either the record or playback process is selected by means of a multi-section 'Record-Playback' switch. When 'Playback' is selected the record-playback head is coupled to the amplifier input, whilst the loudspeaker is connected to the amplifier output. When 'Record' is selected, the microphone is connected to the amplifier input and the record-playback head to an auxiliary output (obtained normally at a point immediately preceding the output stage) from the amplifier. Thus nearly all of the amplifier stages that are used to amplify the playback signal are brought into use to amplify the record signal as well, and a significant economy is achieved. More expensive recorders may have separate record and playback amplifiers, each being designed for optimum results for their particular function.

The simplified block diagrams in Fig. 1 omit a second head, which is found in all standard recorders. This precedes the record-playback head (or both the record and playback heads if these are separate) and is referred to as the *erase head*. Its primary function is to erase any previous signal that may be present on the tape when a recording is being made, and its method of operation will be described in a later article. Another omission is that the Record-Playback switch in Fig. 1 (c) does not include a section for altering the frequency response of the amplifier when it is changed from one of its two functions to the other. As we shall see in this and next month's

article, it is necessary for the amplifier to have quite different frequency responses for the record and playback functions if the over-

all response from record to playback via the recording on the tape is to be kept 'flat'. When separate record and playback am-

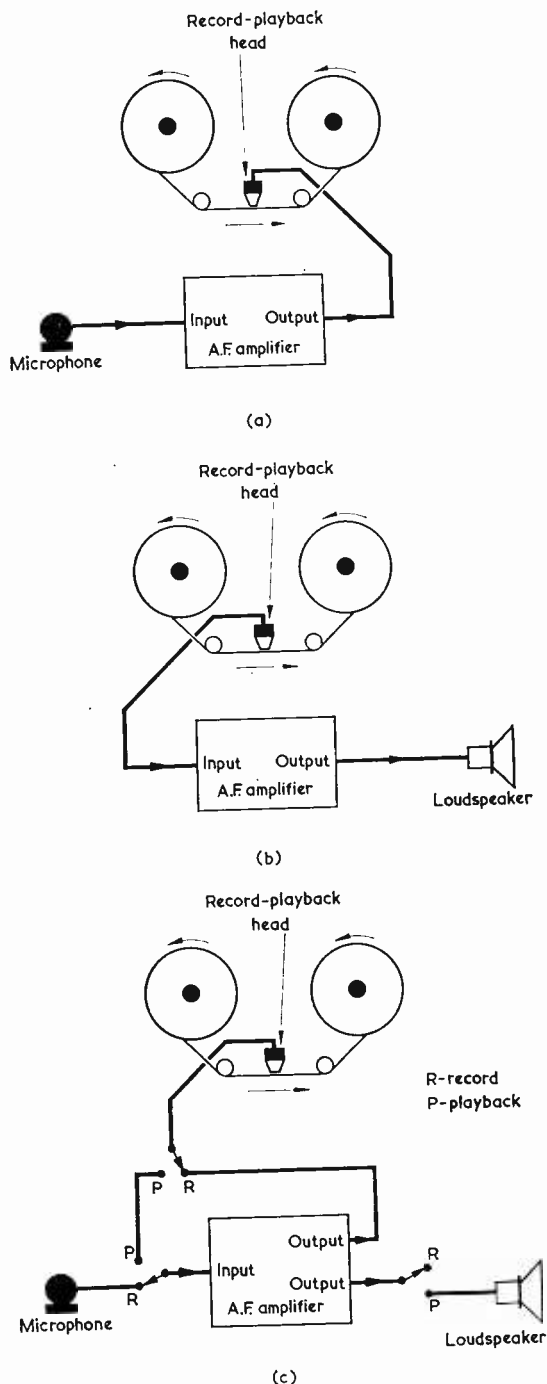


Fig. 1. Illustrating, in very simplified form, the processes involved in recording when using a recorder with a common record-playback head. In (a) a recording is being made whilst, in (b), it is being played back. In domestic recorders most of the stages in the a.f. amplifier are common to both functions and (c) shows, in theoretical form, how the requisite function switching could be carried out

plifiers are used, they may each be permanently provided with frequency-selective filter circuits which provide the response applicable to their function.

THE RECORDING PROCESS

The fundamental process of recording a signal on magnetic tape can be explained with the aid of Fig. 2(a). Here we see the record head (which, in domestic tape recorders (which, in domestic tape recorders of the type we have just discussed, will also serve as playback head) and the magnetic tape. The core of the head consists of a ring of magnetic material having a very narrow gap across which the tape is drawn. There is also a gap at the rear of the head, the purpose of which will be dealt with in a later article. Thin shims (i.e. thin slips to fill up the spaces) of non-magnetic metal are inserted in these gaps. The head core is made of a 'soft' magnetic material, the term 'soft' in this context inferring that the material demagnetises readily after having been magnetised. A typical construction for the head core would comprise a stack of laminations made from similar metal to that used for the cores of a.f. transformers. A coil

is wound around the two halves of the core. In consequence, if an alternating current, such as that provided by an a.f. signal, is caused to flow through the coil, a corresponding magnetic field appears at the gap across which the tape travels. This gap is very narrow (typically 0.0002 in. with a record-playback head) and its length is at right angles to the direction of travel of the tape, as shown in Fig. 2(b).

The tape, which is about $\frac{1}{4}$ in. wide, consists of a plastic base coated on one side with magnetic iron oxide in the form of very tiny particles suspended in a binding medium. Unlike the magnetic material of the head, the iron oxide offers 'hard' properties, and does not readily demagnetise after having been magnetised. The oxide coated side of the tape is held firmly in contact with the gap of the head by means of a pressure pad made of felt or similar resilient material. To ensure good mechanical contact between the tape and the head gap the head surface at the gap is smooth and highly polished.

Let us now see what happens if we feed a signal current through the coil of the head whilst the

tape is drawn past the gap. For convenience we may choose a sine wave having a relatively low frequency, and we turn next to Fig. 3 which illustrates the effect on the tape resulting from the application of this sine wave current. In Fig. 3(a) we see the sine wave at zero level, whereupon no current flows in the coil and zero magnetising force is exerted on the 'soft' core of the head. In Fig. 3(b) we see the sine wave at an intermediate value between zero and peak, whereupon a current flows in the coil and a magnetising force is exerted on the core. Lines of magnetic force (which by convention are assumed to flow from South to North within the body of a magnet, as the head core now effectively is) appear in the core. In Fig. 3(b) they are, for convenience, represented by a single line. At the gap they pass through the oxide coating of the tape since this offers a much higher permeability (i.e. it allows a much higher flux density to appear in it) than does the shim of non-magnetic metal in the gap. In consequence, the iron oxide suffers magnetisation at this point. The arrow drawn inside the tape indicates tape magnetisation which has already taken place, this commencing immediately after the sine wave amplitude rose above zero. Fig. 3(c) shows the situation a little later. The tape has moved further forward and the sine wave is now at its maximum amplitude. Magnetisation of the tape oxide with the field flowing in the same direction continues to take place, this time at maximum level.

As the tape continues to pass over the gap it will continue to be magnetised with the field in the direction shown until, when zero signal amplitude is reached once more at the end of the half-cycle, no magnetising force is exerted on the core of the head. During the following half-cycle the same process will be carried out, but the field will be in the opposite direction.

Since the iron oxide on the tape is a 'hard' magnetic material it retains the magnetism imparted to it during the half-cycle of the sine wave. If we were to draw a graph showing the strength of the magnetism retained in the oxide over a number of cycles, we would find that the tape oxide exhibits maximum magnetisation at the same time as the input signal exhibits maximum amplitude. Also, that when the signal goes through zero level so also does the magnetisation and that when the signal changes polarity the magnetisation follows suit.

Such a graph can be considered to represent the state of affairs shown in Fig. 4, in which it is

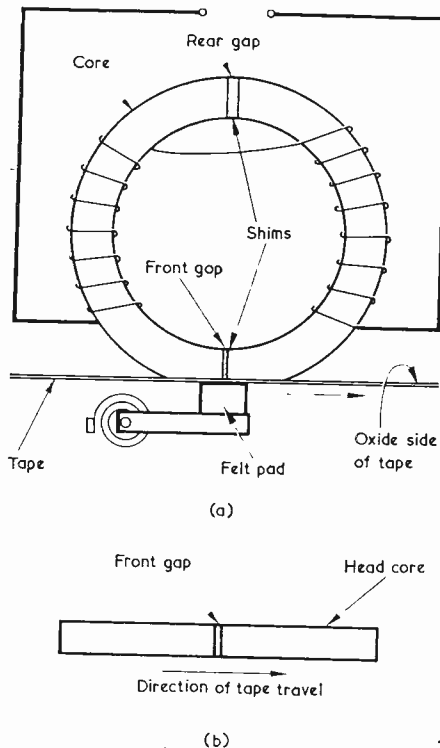


Fig. 2(a). The basic construction of a record or playback head, or of a head combining both functions. The felt pad presses the tape against the front gap of the head

(b). End view of the head, illustrating that the gap length is at right angles to the direction of tape travel

assumed that a series of bar magnets has been created in the oxide of the tape due to the process of magnetisation. The length of each of these 'magnets' corresponds to one half-cycle of the signal fed to the record head, whilst the length of two magnets corresponds to a full cycle. There are, of course, no actual magnets inside the tape oxide; instead there is a remanent magnetic field whose direction and amplitude continually change along the length of the tape. Also, the analogy is not perfect because actual bar magnets would exhibit maximum field strength at their extremities, whereas the 'magnets' in the tape have zero field strength at their extremities. Nevertheless, it is very convenient to talk in terms of individual bar magnets since this concept assists in explaining some of the further basic factors in tape recording which will next be dealt with.

The length of each magnet produced in the tape under the conditions shown in Fig. 3 was considerably greater than the width of the gap. If we increase the frequency of the signal applied to the record head the length of each magnet will become smaller because it is produced in a shorter section of the tape. If we continue to increase the frequency we shall eventually arrive at the situation where the length of each magnet is not very much greater than the width of the gap itself. As frequency rises towards this state of affairs, the simple principle of tape magnetisation illustrated by Fig. 3 tends to be replaced more and more by a much more complex process in which a section of the tape can be subjected to magnetising forces of different magnitude and, even, polarity during the period in which it travels across the gap. This effect will, obviously set a limit to the highest frequency which can be usefully recorded on the tape. A more important effect, though, is that as magnet length in the tape oxide decreases there is a continually increasing tendency for the oxide material to demagnetise after it has left the gap. The shorter magnets are unable to maintain the permanence exhibited by the longer magnets which were created at the lower signal frequencies. The demagnetising effect starts to become apparent at a frequency well below the highest frequency which may be recorded on the tape, becoming progressively more pronounced as the frequency approaches this level. Falling-off in recording efficiency at the higher frequencies is dictated partly by the onset of the complex magnetising process previously mentioned, but it is mainly due to self-demagnetisation in the tape. Speaking in very ap-

proximate terms, the highest frequency at which useful recording may be carried out is given when the magnet length in the tape is of the order of ten times the width of the record head gap.

Additional factors which also

limit recording efficiency at the higher frequencies include eddy current losses in the record head and fall-off in performance, as frequency increases, in the magnetic material of the head core. These particular high frequency losses are,

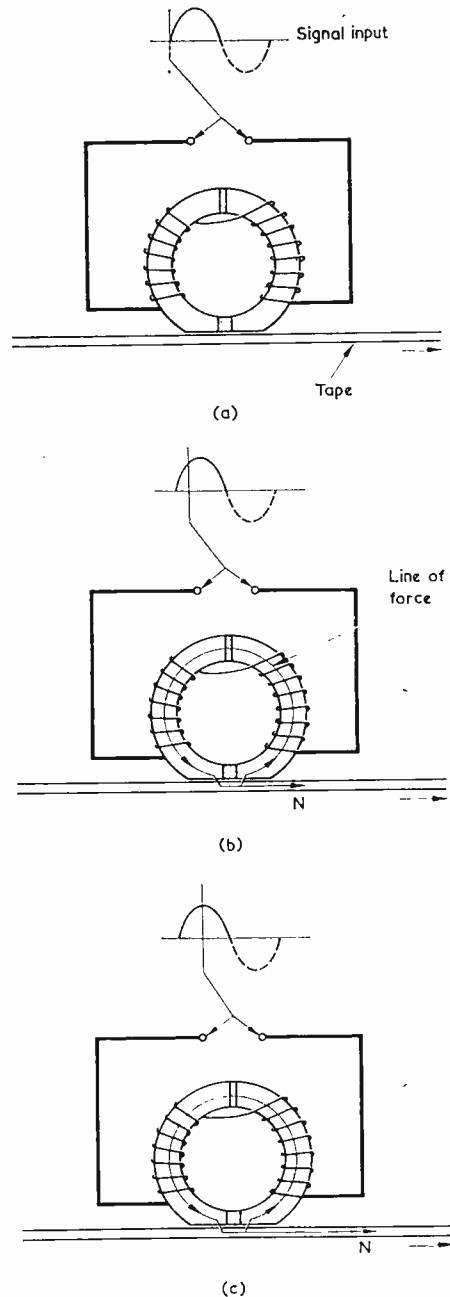


Fig. 3 (a). When the signal input current is at zero, no magnetising force is imposed on the record head core
 (b). As the signal current increases from zero a field is set up in the core, the lines of force flowing through the oxide coating of the tape as it passes over the gap. The arrow inside the tape indicates magnetisation which has already taken place
 (c). At maximum signal current amplitude the tape coating undergoes maximum magnetisation

however, a function of record head design rather than of the actual process of recording onto the tape. The maximum useful recording frequency can be raised by the very simple process of increasing

the speed at which the tape is drawn past the record head gap. If tape speed is doubled so also, at any given frequency, are the lengths of the magnets created within its iron oxide surface. It

follows that the recording frequency may then itself be doubled before the same degree of tape demagnetisation occurs. This is largely borne out in practice. The more commonly encountered tape speeds in domestic equipment are $7\frac{1}{2}$ in. per second (usually abbreviated to i.p.s.), $3\frac{3}{4}$ i.p.s. and $1\frac{1}{4}$ i.p.s. With good head design it is possible to record up to frequencies, in kHz, which are one to two times the i.p.s. figure. Thus, one could expect to record up to some 3.75 to 7.5kHz at a tape speed of $3\frac{3}{4}$ i.p.s., and up to some 7.5 to 15kHz at a tape speed of $7\frac{1}{2}$ i.p.s. More expensive machines may feature tape speeds of 15 i.p.s. and 30 i.p.s., these offering further enhanced high frequency performance (although head losses here may cause the upper frequency limit to be somewhat less than double the i.p.s. figure). Another tape speed, encountered in equipment which is not usually expected to offer a wide frequency range, is 15/16 i.p.s.

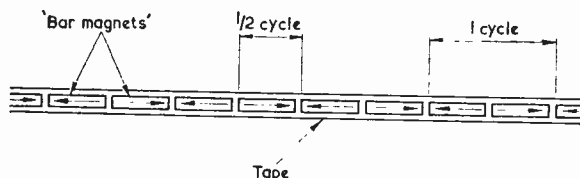


Fig. 4. A useful analogy is given by the assumption that the process illustrated in Fig. 3 has created a number of 'bar magnets' inside the tape, as shown here. The arrow inside each 'magnet' indicates direction of field

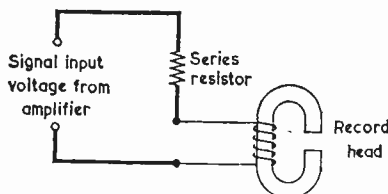


Fig. 5. 'Constant current' record head drive may be achieved with the aid of a high value series resistor


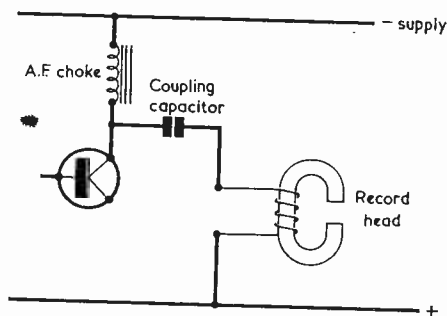


Fig. 6. A method of obtaining 'constant current' drive when the available supply voltage is low. The transistor is in the a.f. amplifier stages of the recorder

RECORDING CHARACTERISTIC

In general, magnetic tape tends to overload at about the same magnetising level, irrespective of frequency. Disregarding for the moment the self-demagnetising effect in the tape which takes place at the higher frequencies it is, in consequence, desirable to arrange matters such that the tape magnetising force falls in the same range of amplitudes at all frequencies that are intended to be recorded. This requirement can be met by ensuring that the frequency response of the recording amplifier, as expressed in terms of the *output current flowing in the record head coil*, is 'flat' over the recording frequency range. It is important to note the emphasis on record head current, because the magnetising force exerted on the record head is proportional to the *current* which flows in its coil, and not to the voltage appearing across that coil or to the power dissipated in it.

A record head is essentially an inductive component, which means that it offers an impedance that increases with frequency. In consequence, it is very common practice to feed a record head via a series fixed resistor having a value which is well in excess of the difference between the head impedances at the maximum and minimum recording frequencies. The circuit is shown in Fig. 5. Due to the presence of the high value series resistor, very nearly the same current flows in the head winding for the same input voltage, regardless of frequency. A head drive circuit of this nature is referred to as a 'constant current' circuit, because the head current tends

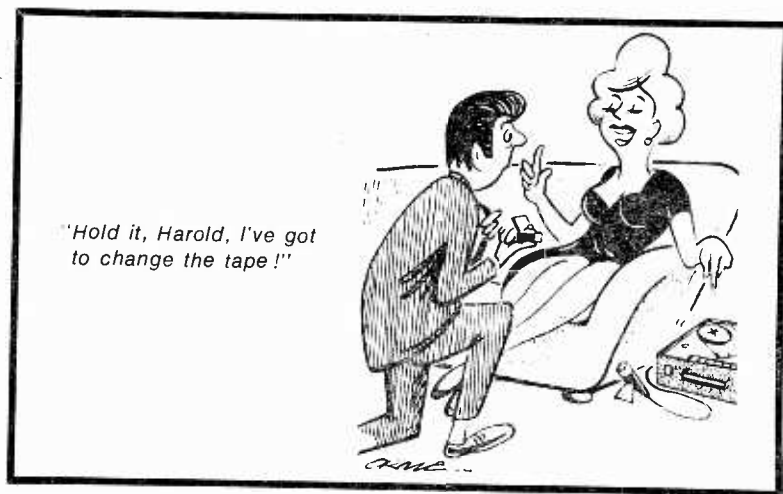

towards a constant current (for the same input voltage) throughout the frequency range. In mains-driven recorders, the head drive voltage may be obtained from the anode of a voltage amplifier valve or from the collector of a transistor. In the former case, the value of the series resistor is usually of the order of 100 to 200k Ω , whilst in the latter it is of the order of 20 to 50k Ω , thus reflecting the lower impedances at which transistors work. The head will, itself, also have a lower impedance winding in the transistor recorder. At first sight, the presence of the series resistor might give the impression that a high proportion of output recording power is lost due to the signal voltage that is dropped across it. In practice, this loss is not of great importance because satisfactory recording may be achieved when the a.f. power fed to the combination of head and series resistor is of the order of 25mW only.

The low supply voltage available with battery-operated transistor recorders makes it difficult to employ a series resistor for constant current drive, since it is impossible to obtain a sufficiently high signal voltage amplitude. An alternative approach consists of developing the record head drive voltage across an a.f. choke, as shown in Fig. 6. The choke offers a low impedance at low frequencies and a high impedance at high frequencies. As a result a low signal voltage is available for the record head at low frequencies and a high signal voltage at high frequencies, whereupon the circuit approximates to constant current operation.

In discussing the drive to the record head we have, so far, ignored the falling-off in recording efficiency at the higher frequencies due to tape self-demagnetising and allied effects. To overcome these, the 'flat' response of the amplifier is modified by introducing a boost at the higher frequencies. This counterbalances the effect of self-demagnetisation in the tape (and of the other high frequency losses) and enables the magnetisation of the tape to be constant over most of the frequency range of the recorder. Since high frequency losses appear in the playback process also, the high frequency boost on record may be made even greater than is needed to overcome tape self-de-


magnetisation. The risk of tape overload under these conditions is negligibly low because the relative strength of high frequency signals in the audio spectrum is usually much less than that of signals at the medium and lower frequencies.

A typical recording characteristic is given in Fig. 7(a). As may be seen this is virtually 'flat' up to some 1kHz, after which there is quite a considerable treble boost extending to +15dB. (=5.62 times, in terms of voltage or current) at 10kHz. Recorders having more than one tape speed may modify


the treble boost for each speed, a typical example being shown in Fig. 7(b). As will be seen, less treble boost is applied as the tape speed increases.

NEXT MONTH

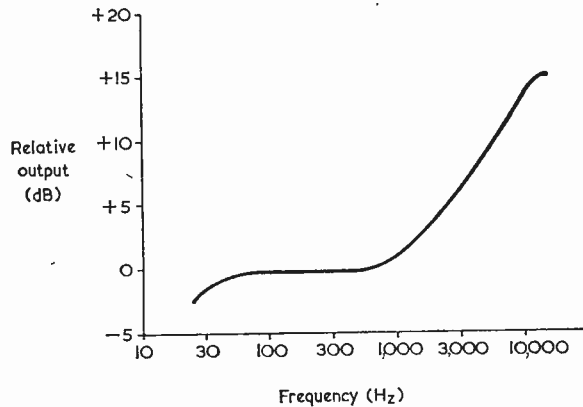In next month's issue we shall examine the process of playback and shall deal with the equalising response characteristics which are employed to provide a 'flat' response for the overall process of recording and playback.



(a)

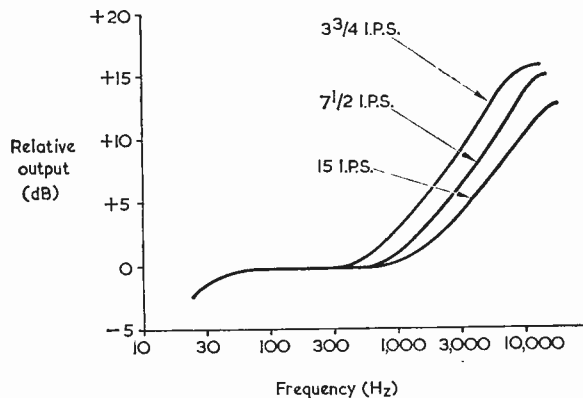

(b)

Fig. 7(a). Representative curve illustrating the treble boost that is applied in a tape recorder amplifier during recording
(b). The degree of treble boost may be varied in recorders offering more than one tape speed

CLANDESTINE STATIONS

The clandestine station Voice of the People of Thailand has been heard at 1600GMT on 6035kHz.

Radio Liberation, another clandestine transmitter, has been heard from 2000 to 2030GMT in French to Europe, and to S.E. Asia, from 1920 to 2000GMT on 10224kHz. Also from 2230 to 2300 on 7416, 10224 and 21000kHz.

THE 'DISCOVERY' S.W. RECEIVER

In the circuit diagram of this receiver, published on page 465 of the March issue, the stick-on symbol for C6 was accidentally removed, and that for R2 damaged, during the block making process. All our circuit diagrams are processed through five separate checking stages. The accidental damage occurred subsequent to the scrutiny procedure.

"FETAFLEX 4" TRANSISTOR PORTABLE

(Continued from page 613)

oscillation does not start without VR1 being near its maximum position. If oscillation does not start with VR1 at maximum, twist L3 a little one way or the other, until oscillation takes place. Remember that L1 is fitted in the right direction when moving it toward the centre of the rod reduces the tendency to oscillate. Now open the vanes of VC1 fully, or nearly fully, and adjust VC3 to a point where oscillation starts smoothly with VR1 advanced about two-thirds of the way towards maximum. Enmesh the vanes of VC1 again and make any small adjustment to the position of L1 as may be necessary, then re-open the vanes of VC1 and adjust VC3 if necessary. Note that movement in L1 has the greater effect at the low frequency end of the scale, and adjustment to VC3 has the greater effect at the high frequency end. Each adjustment has some effect throughout the tuning range.

When L1 and VC3 are both correctly adjusted, and L3 is oriented to best advantage, oscillation should start at the high frequency end of the scale with VR1 set about two-thirds of the way towards maximum, and at the low frequency end with VR1 nearly at maximum, there being a need to advance VR1, progressively, as VC1 is turned throughout its movement. An indication that VC1 has too high a capacitance will be failure to obtain oscillation at all with VC1 fully open, this being combined with lack of selectivity. Uncontrollable oscillation with the vanes of VC1 open means that VC3 has too low a capacitance. If by any unlikely chance the best setting for VC3 should appear to be lower than the minimum capacitance it can offer, C1 can be reduced in value to, say, 300pF. Similarly C1 can be increased to 750pF if best results are obtained with VC3 screwed up tight.

Now turn S1 to long waves and adjust VR2 so that its slider is central on its track. Set VC1 with its vanes slightly enmeshed, to the equivalent of about 225 metres on the medium wave band. Adjust VC2 until Radio 2 is received. Adjust VR2 so that oscillation comes in smoothly. Try moving L2 along the rod for best results, and try also reversing the direction of L2 on its rod or changing the connections to its leads. These adjustments will have less effect when receiving Radio 2 than similar adjustments had with L1 on the medium wave band. No adjustments should be

made to L1 and VC3 when setting up for Radio 2. It is just possible that some distortion will be present, particularly on Radio 2, which can be removed by reversing the connections to the red and blue leads of T1, though this action is not likely to prove necessary.

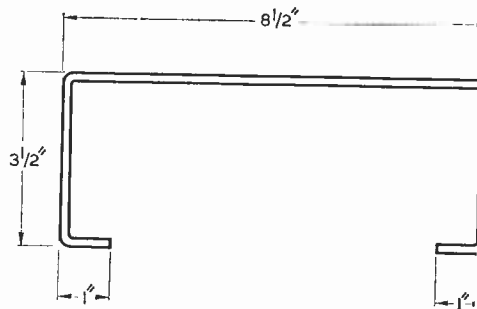


Fig. 10. The carrying handle is made of stiff wire, as illustrated here

TUNING DRIVE

The tuning drive for VC1 is obtained by fitting a standard cord drive drum over its spindle and coupling a second spindle to it in the manner shown in Fig. 5. A rubber grommet, having a diameter which allows it to be a tight fit over the drive spindle, bears against the edge of the drum on VC1 spindle, enabling a simple and effective tuning drive to be obtained. The author used a drum with a diameter of 1 1/2 in. but a 1 1/4 in. drum should be equally suitable. The drive spindle requires a bush and this may be salvaged from an old component or purchased new. (A suitable bush is the Home Radio Cat. No. DI.52C). The bush is positioned to provide the required mechanical coupling between the drive spindle and the drive drum, with the rubber grommet pressing hard up against the drum. When drilling the hole for the bush take care not to damage any component, including in particular the moving vanes of VC1. A suitable pointer may be secured to the drive drum in any convenient way. For instance, the grub-screw of the latter may be replaced by an ordinary screw with a nut passed over its threads. After tightening the screw the nut can then secure a pointer wire.

A Perspex panel measuring 8 by 5 in. fits over the plywood panel as shown in Fig. 6. Three holes are required in the Perspex panel for

the spindles and it is spaced off with 1/2 by 1/4 in. wood spacers. The tuning scale is marked out on a piece of white card and is glued to the plywood panel, the underside of the Perspex panel being partly masked to hide the tuning drive and to provide a window for the scale. A suitable masking material is Fablon, possibly in a contrasting colour to that of the cabinet. The spindle of VC1 should have been previously shortened if necessary, to ensure that it does not foul the underside of the Perspex panel.

BATTERY AND CABINET

The battery is held in position as shown in Fig. 7. The small plywood platform illustrated here is cut and drilled and is then slipped onto the two 4BA bolts shown in Fig. 3, with 4BA nuts beneath and above. The nuts are adjusted such that when the battery is in position and held by the rubber bands shown, the receiver is capable of standing upright, the battery terminals forming feet on one side and the unsecured long edge of the speaker providing support on the other.

The Perspex panel of Fig. 6 next has affixed over it the plywood frame illustrated in Fig. 8. A suitable cabinet can be made from 1/4 in. plywood, as shown in Fig. 9. Before the pieces for this cabinet are cut out the reader should take accurate measurements of the receiver "chassis", as some speakers may have slightly different dimensions from that used by the author, and the original plywood panel may not have been cut exactly to size. The dimensions in Fig. 9 are mainly intended for guidance and they should be modified as required in practice. Although not shown in Fig. 9 it is advisable to fit a small wooden pad at the inside base of the cabinet to take the centre of the battery and thereby relieve pressure on its terminals. This may necessitate slightly re-adjusting the 4BA nuts which

RADIO CONSTRUCTOR

SPECIAL EXCLUSIVE OFFER

MASERATI AIR HORNS

● DUAL HORNS


Ideal for Motorway or Continental driving. Will fit under the bonnet of any car. Available in 6, 12 or 24 volts. This unit incorporates a new extra powerful compressor, which is only available with Maserati Air Horns. Extra tough red plastic trumpets, both 6½ in. long, base diameter of each 3 in. Compressor height 4½ in., diameter 2½ in. Total weight, including box, 4½ lbs. Complete with relay, tubing, securing nuts and bolts and fixing instructions. List Price 5 gns.

OUR PRICE 69/6 plus p. & p. 6/-.

● TRIPLE HORNS

Three alternating notes in fast sequence. Can also be sounded together by operating the dash switch. A very pleasant musical warning attracting immediate attention. Extremely compact, will fit on all cars. Available in 6 and 12 volts only. **OUR PRICE 135/- plus p & p 6/-.**

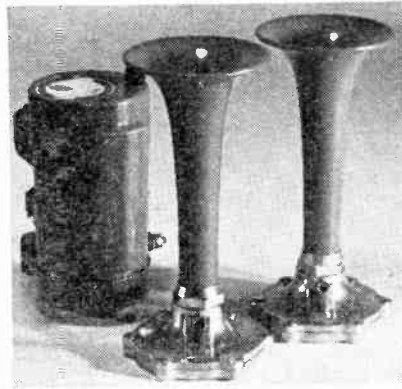These famous air horns are proving a popular fitting on small and medium sized boats.



**COVERED BY A
SEVEN-DAY MONEY BACK GUARANTEE**

To Data Publications Ltd.
57 Maida Vale, London, W.9

Please supply:

..... Dual Horns Triple Horns
(State voltage required)

I enclose cheque/crossed postal order for

Name

Address

Block Letters Please

secure the battery platform. Note the cut-outs, both in Fig. 9 and Fig. 8, for the tuning knob. These allow a knob of reasonable diameter to be used. The cut-out in Fig. 9 should match up to that in Fig. 8. A suitable speaker fabric should be secured behind the cabinet speaker aperture. The "chassis" slips in through the top of the cabinet.

The cabinet, and the frame in Fig. 8, can be covered with Fablon for a neat finish. A stiff wire carrying handle may be made up to the dimensions given in Fig. 10.

RECEIVER PERFORMANCE

The sensitivity of the prototype "Fetaflex" receiver is very good, being comparable to that given with the author's "Spontaflex" S.A.4 Transistor Portable (described in the May 1968 issue). Selectivity is unusually good for a single tuned circuit receiver though it is not, perhaps, quite as sharp as with the S.A.4, which was quite exceptional in this respect.

Selectivity is partly dependent on the use of the M3 diode

specified. Although the receiver will work with a silicon diode, such a diode will cause a marked fall off in selectivity.

Signal-to-noise ratio is particularly good, being better than with the S.A.4 design and better than that given by the average small superhet, which this design outperforms in nearly all respects except adjacent channel selectivity with powerful local stations.

With a new battery TR1 and TR2 will take about 4mA between them. The distribution of current will depend on the exact characteristics of the semiconductors used, but may be expected to be about 2mA each. TR3 should pass about 120µA, and the base current of TR4 plus current drawn by VR3 will account for about 1mA. TR4 passes 21mA, making for a total of about 26mA as already mentioned. Undistorted output is about 45mW (dissipation by TR4 being 90mW) which is ample for many purposes provided a sensitive speaker is employed.

(concluded)

NEON L.D.R. A.F. OSCILLATOR

(Continued from page 595)

to one, two or more stages of audio amplification.

As a final point, the writer would like to refer to the experience of one reader who built up an earlier 'Suggested Circuit' which similarly incorporated a small wire-ended neon bulb. It was found that neon bulb operation in this circuit became erratic when the bulb was maintained in complete darkness. This effect can occur with some neon bulbs of the type used here, these requiring a small amount of incidental light for initial ionisation. Should it be found that the present oscillator circuit functions satisfactorily at low ambient light levels but shows evidence of irregular operation when completely enclosed, it is permissible to provide a small aperture in the light-proof box to ensure that the neon bulb is not in the totally dark condition. There was, incidentally, no evidence, with the prototype circuit that this precaution would be needed.

THE RADIO CONSTRUCTOR

ELECTRONIC CHRONOMETERS

Whilst electronics have spread rapidly during the past few years to almost every aspect of ships' equipment, one of the items which has undergone little change until recently is the ship's chronometer. Although not such an essential piece of navigational equipment now that radio time signals can be received in almost every part of the high seas, it is still carried as the navigational timepiece by practically every ship engaged in ocean crossings.

During the last few years very successful crystal-controlled electronic chronometers have been developed to the point where they are now commercially available.

The basis of these new chronometers is a quartz crystal-controlled transistorised oscillator circuit which can be sufficiently well temperature compensated to enable accuracy of time-keeping to be maintained to within one-hundredth of a second per day over wide changes of atmospheric temperature. Furthermore, these instruments do not have to be mounted in gimbals, as are the conventional clockwork chronometers, to protect them from the effects of vessel motion but can, if desired, be mounted horizontally or vertically in instrument panels.




These electronic chronometers are powered by miniature dry cells enclosed in the instrument casing and are thus independent of the electric power supply.

Another system which has also been successfully developed for similar electronic time-keeping uses a miniaturised tuning fork maintained in oscillation by an electronic circuit powered by self-contained miniature batteries. This system is used in the Bulova Accutron Marine Navigating Clock shown in the illustration.

MAY 1970

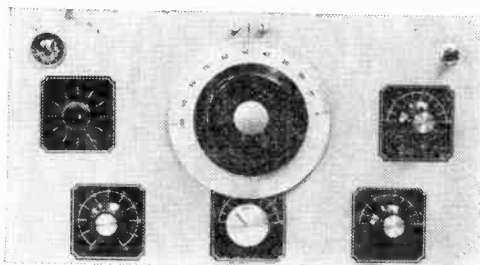NEW HANDIPAK PANEL SIGNS IDEAL FOR WORKSHOP USE



- Easy to fix
- Permanent and durable
- Stapled in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish

- ★ Set 3 Wording—WHITE
- ★ Set 4 Wording—BLACK
- ★ Set 5 DIALS—clear background
- ★ Set 6 DIALS—black background

The Perfect Transfer for
the Home Constructor

Each Set contains Six Sheets

5/- per set

(postage 4d.)

To Data Publications Ltd.
57 Maida Vale, London, W.9

Please supply:

.....Set 3Set 4Set 5Set 6

I enclose cheque/crossed postal order for.....

Name.....

Address.....

RC

BLOCK LETTERS PLEASE



SIMPLIFIED SOLID-STATE DISTORTION METER

Continued from page 601

CONSTRUCTION

Construction is straightforward, a panel-shelf arrangement being used as indicated in Fig. 4. All the components are standard, the larger ones being mounted directly on the front panel and most of the smaller on the two printed circuit boards. The layouts of these are given in Figs. 5(a) and (b), which show the boards from the copper side. These boards are reproduced full size and the copper pattern may be traced from the diagrams. The filter circuit panel ("A") is mounted on the lower side of the shelf and the voltmeter panel ("B") on top. Figs. 5(a) and (b) show the orientation of the panels by indicating the edge which is nearest the front panel. Both panels, it will be noted, are secured by the same four 6BA bolts, each panel being kept clear of the shelf by suitable metal spacers. In order to ensure correct alignment of the printed boards it is recommended that both panels be drilled together, i.e. the panels clamped with the copper sides in contact. This operation should be carried out before etching. The author has also found it convenient to drill the fixing holes for the various preset potentiometers before marking out the circuit boards. No measurements are given for these components because the exact dimensions will depend upon the make of components used. It is immaterial which of the two connections to a preset potentiometer mounted on a panel is made to the slider or to the track, and the constructor may choose that which is most convenient in practice.

A small 4-way tagstrip positioned as shown in Fig. 4(b) provides a mounting for C11. The battery leads may also be anchored to this tagstrip or to the switch tags, as convenient. Any small 9 volt battery capable of fitting in the space available under the shelf (such as an Ever Ready PP6) may be used, this being clamped inside the cabinet.

The wiring external to the printed circuit boards follows the circuit diagram of Fig. 3. Chassis connections to points "M", "L" and "W" are automatically made via the mounting 6BA bolts and spacers. Wires connecting to other points on the boards may be soldered direct to the copper or, preferably, passed through small holes drilled for them in the boards and then soldered.

The Input connection is provided by two insulated sockets mounted on the front panel, these connecting to the outside tags of VR1 by short unscreened leads. The slider of VR1 connects to point "A" of Panel "A" by way of screened cable. The braiding of this cable connects to a chassis tag under the 6BA securing nut adjacent to point "A" and, at the other end, to the earthy Input socket. The Output socket

is a coaxial socket and it connects via screened cable to the appropriate tag of S1(b). The braiding is earthed by way of a chassis tag under one of the socket securing nuts.

A piece of matt white Formica board, cut slightly smaller than the front panel and mounted on it will give a good finish to the instrument, and also provide a good surface for the attenuator calibrations. Exact dimensions of the front panel will depend upon the meter used. In the prototype this was an ex-W.D. type with a 2in. scale. The case for the prototype was made of wood with dimensions appropriate to the size of panel and the rear projection of the shelf.

CALIBRATION

Before connecting VR8 into the circuit, this component will require calibration for use as the attenuator. This can be carried out in one of two ways. In the first a suitable ohmmeter (e.g. the appropriate range of a multimeter) or resistance bridge is connected between the central and earthy terminals of the potentiometer. The scale is then marked at 500 Ω intervals between 5k Ω and 500 Ω and at 50 Ω intervals between 500 Ω and zero. The shape of the scale will be similar to that given in Fig. 6, which also indicates the corresponding values of percentage distortion.

A more accurate method of calibration requires a high resistance voltmeter (i.e. an instrument with at least 20,000 ohms per volt sensitivity) and a 10 volt d.c. supply, a variable voltage transistor type power pack being ideal for the latter. The outer terminals of VR8 are connected to the 10 volt source, and the voltmeter to the central and earthy terminals. The scale is marked at 1 volt intervals from 10 volts to 1 volt and at 0.1 volt intervals from 1 volt to zero. Fig. 6 again gives the relationship between the voltage markings and percentage distortion.

After calibration is complete VR8 is connected into the circuit, and the preset component VR9 adjusted. For this operation S1 is set to the "Off" position and a convenient d.c. voltage applied between point S and the chassis. A voltmeter is connected across VR8, and VR9 is adjusted until the voltmeter reads exactly one-tenth of the total voltage applied.

The final adjustments, before the instrument is ready for use, concern the preset potentiometers in the Wein Bridge network—VR4 and VR5. These are easily adjusted with the aid of an ohmmeter. With the ganged control at maximum resistance the meter is connected across VR6, and VR5 is adjusted for a reading of exactly 1,200 Ω . The operation is repeated with the ohmmeter across VR7, VR4 being set for the same reading.

With a battery connected, the instrument switched to the "Filter In" position, and a 1,000Hz input, the level control is set for full scale deflection on the meter. Rotation of VR6/VR7 will now produce a dip in the meter reading. With VR2 set at its mid-point, VR3 is carefully adjusted to produce the maximum dip. As the null point is reached it will be necessary to progressively increase the level of the input. Final adjustments are made with VR2. Once set, VR3 should not require further attention. The instrument is now ready for use.

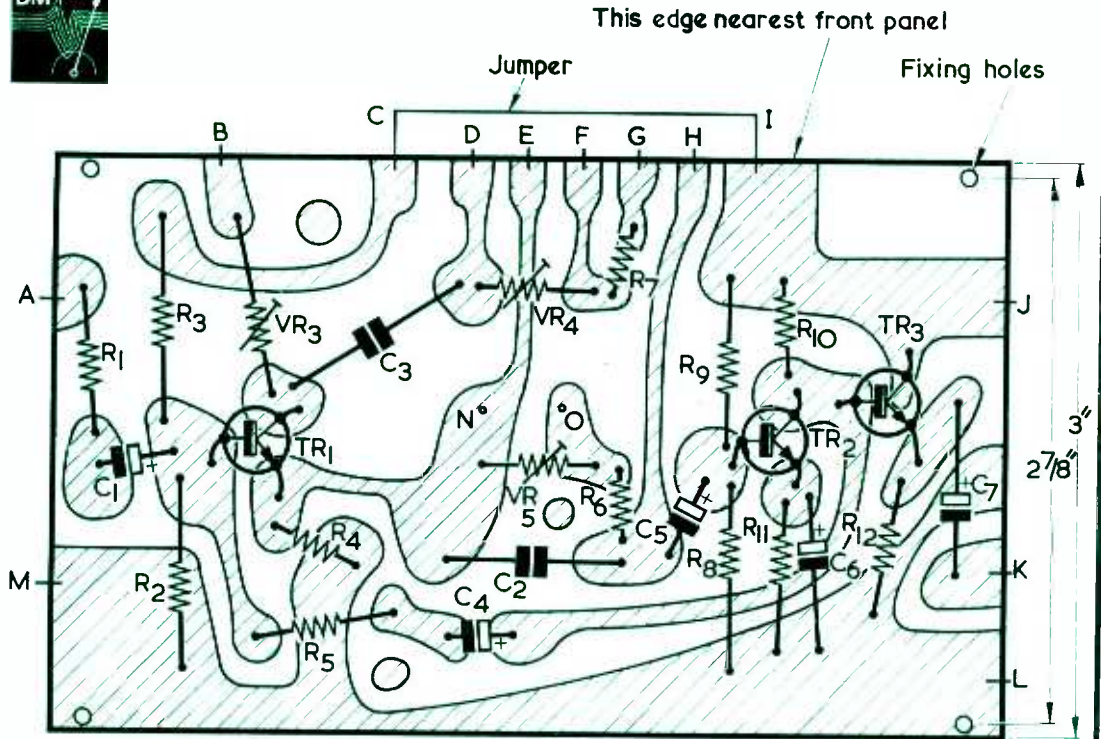


Fig. 5a. Layout of components on Panel 'A', as viewed from the copper side of the board

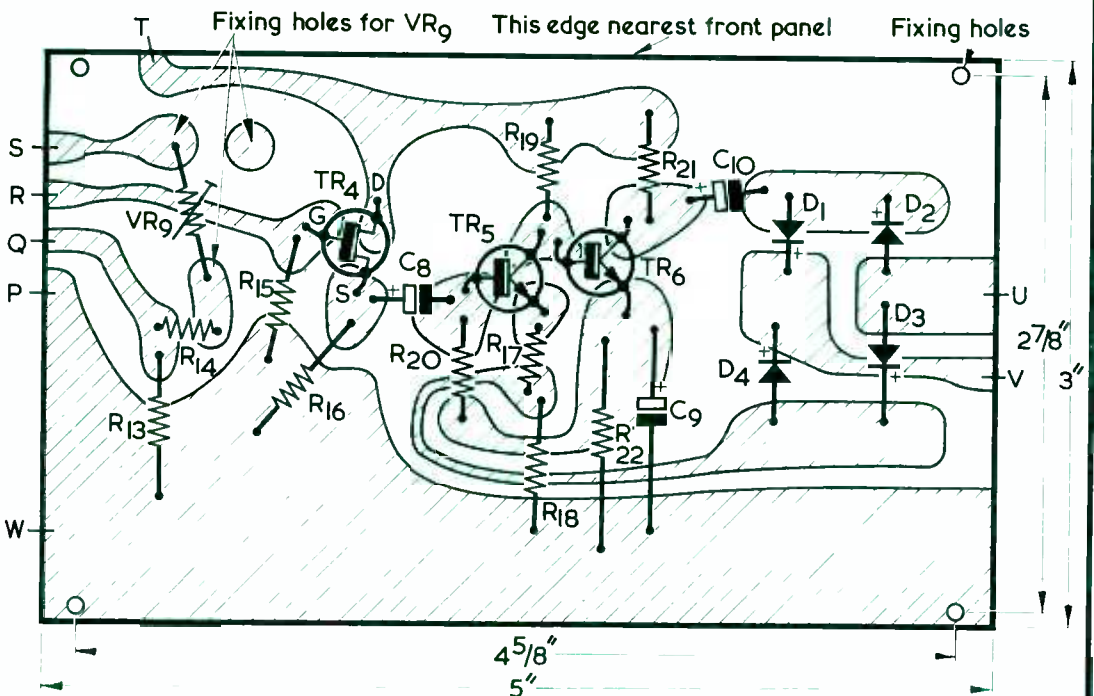


Fig. 5b. The components on Panel 'B'. Again, the copper side of the board is towards the reader

Cut along this line

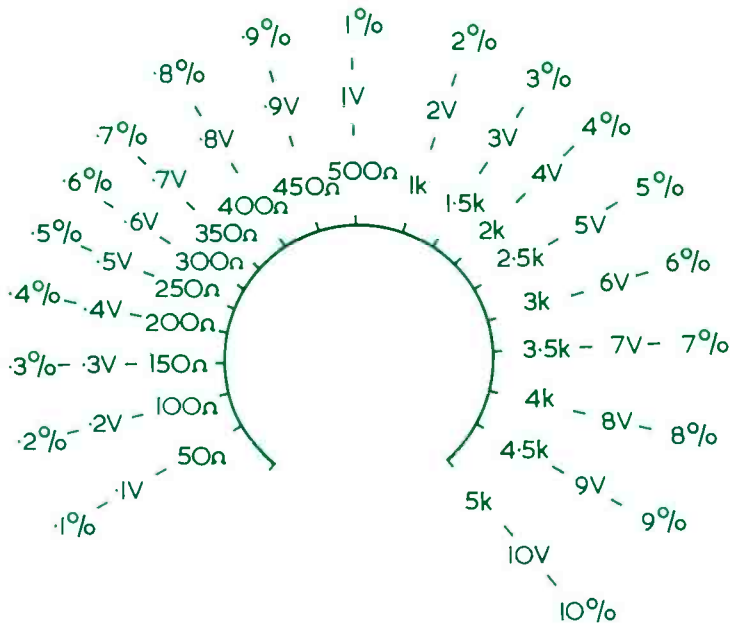


Fig.6 The attenuator control may be calibrated in terms of resistance or voltage readings. This diagram shows the corresponding percentage points for either method of calibration


TABLE
Prototype Voltage and Current readings

TR ₁	V _c = 5.5 V
	V _b = 1.6 V
	V _e = 1.0 V
TR ₂	V _c = 4.5 V
	V _b = 1.1 V
	V _e = 0.5 V
TR ₃	V _c = 9V
	V _b = 4.5 V
	V _e = 3.8 V
TR ₄	V _d = 9V
	V _s = 3.5 V
TR ₅	V _c = 1.5 V
TR ₆	V _c = 5.5 V
	V _b = 1.5 V
	V _e = 0.75V

Total current = 8 mA

Input to MPF105 (TR₄) for full deflection is approximately 3mV r.m.s. at 1,000 Hz

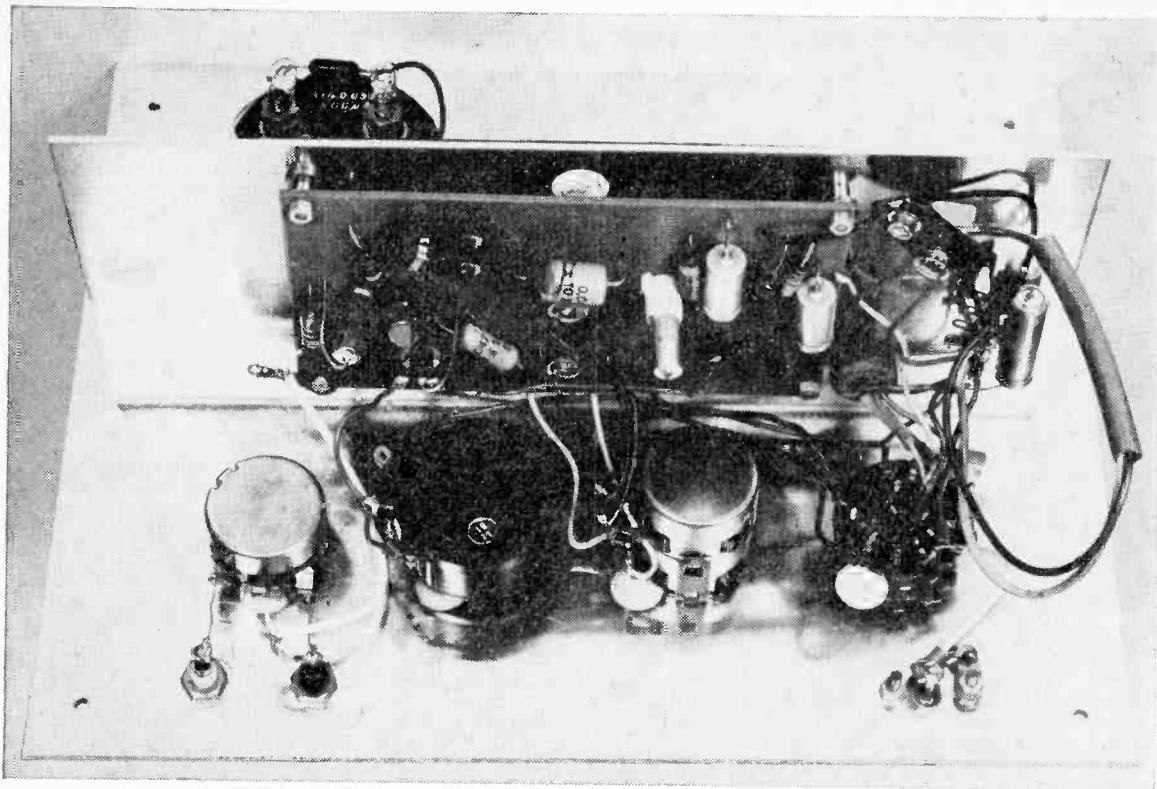All voltages taken with valve voltmeter (11MΩ input)



The lower side of the shelf, with Panel 'A'. Note the battery-connector at the end of its two flying leads

USING THE METER

In use, the equipment under test is set up according to design with an appropriate resistive load (i.e. 3Ω , 15Ω , etc.) connected to its output. A 1,000Hz test signal is fed to the amplifier input and adjusted to produce the rated output. The Distortion Meter is connected across the amplifier load and switched to the "Filter In" position. The balance and tuning controls are carefully adjusted for minimum reading on the meter; after which the "Level" control (VR1) is set for a convenient reading which is then noted. The Distortion Meter is now switched to the "Filter Out" position and the attenuator adjusted to produce the same reading on the meter, care being taken not to disturb any of the other settings. The percentage distortion can then be read directly from the attenuator scale.

It will be obvious that the test signal must itself be above reproach and should itself be checked by the Distortion Meter. A good quality source is called for but the generator need not be elaborate, and a fixed frequency type producing a low distortion sine wave would be ideal.

It should also be noted that the "Level" control should be set as low as convenient during the test in order to prevent any possibility of overloading the input stage of the Distortion Meter. Overloading this stage would, of course, introduce extra distortion and invalidate the test.

To conclude, a few practical results can be mentioned to illustrate the instrument in use. The Distortion Meter gave the distortion present at the output of a B.S.R. L.O.50A audio generator as 0.75%. Calculations based upon measurements taken with a T-Bridge filter gave the figure as 0.8%. The Meter took approximately two minutes to use; the calculations about fifteen! With an oscilloscope coupled to the Distortion Meter outlet socket, the distortion waveform was seen to be composed mainly of second and third harmonic but with an amount of radio frequency; the latter due to the fact that the L.O. 50A is a beat frequency type of generator. With a tuned L.C. filter in the output of the generator, the Distortion Meter showed that the distortion was reduced to 0.3%.²

Using the Distortion Meter, a standard type of valve amplifier, with an EL84 output stage, was found to have just over 2% distortion, which the oscilloscope revealed to be mainly of third harmonic. Calculations based upon the T-Bridge filter gave the figure as 2.1%. Again the Meter took two minutes to operate and the calculations fifteen.

² It should be noted that the Output socket of the Distortion Meter couples direct to the gate of the f.e.t., TR4. Care should be taken to ensure that no voltages are applied to this socket which could cause breakdown in the transistor.—Editor.

In your work-shop



"DASH IT ALL SMITHY," protested the outraged Dick, "what you propose to do is nothing short of a violation of my rights as a citizen."

"On the contrary," retorted Smithy sternly, "what I intend to do is entirely within my authority."

"Aren't I," asked Dick belligerently, "to have any privacy in this Workshop at all?"

"Not," returned Smithy, "so far as that overflowing junk-box you keep on your bench is concerned. I'm sick to death of hearing you spend one half of the day chucking stuff into it, and the remaining half of the day scrabbling around inside it for odds and ends which shouldn't have been put there in the first place. You must have enough rubbish in that box to start your own refuse collection. Dash it all, I've never seen you empty it out once over all the years you've been working here!"

Smithy drew breath.

"So," he finished, "if you won't clear it out, then I'm jolly well going to clear it out for you myself."

"You've got a junk-box."

"I," Smithy corrected him primly, "maintain a *spares* box. What's more, I sort it out every month to see what's worth keeping and what needs throwing out. Also, the stuff I do keep goes into properly labelled containers which enable me to locate what I want without delay."

SPARES BOX SYSTEM

Proudly, the Serviceman indicated a neat array of tins at one end of the shelf behind his bench.

Whilst an Englishman's home may not, these days, be as much his castle as it used to be, a service engineer's junk-box still remains his own private and highly personal treasure trove. With this fact in mind we can readily appreciate the sense of affront Dick experiences when Smithy callously decides that the contents of his assistant's own junk-box are long overdue for clearing out

"Most of the stuff I hang on to," he went on, "falls into the hardware category, and consists of odd nuts and bolts, small metal brackets and things like that. The whole point behind my scheme is that I can always find anything I want with the minimum of delay or difficulty."

"I suppose," said Dick condescendingly, "you could say that that is one way of tackling the junk problem. But what about the time you waste sorting things out so that they can be put into their separate tins?"

"The time I waste?" repeated Smithy incredulously. "The way I deal with my spare bits and pieces doesn't waste time, it *saves* it, mate. If I've got any odds and ends left on my hands when I'm concentrating on a job I just put them in the spares box and forget all about them. Then, about once every month, I sort out what's collected in the box during the period. This sorting out process only takes about half-an-hour or so."

"Ah" broke in Dick triumphantly, "now that's where my system beats yours. I never sort out anything in my junk box ever, which means that whenever I want anything it's *always* there!"

"That statement," said Smithy, rising decisively from his stool, "just about clinches the matter. Your junk-box is going to be cleared out, Dick, and it's going to be cleared out right now."

Dick returned to the attack.

"Is nothing sacred?" he wailed. "A service engineer's private junk-box is something which is personal to him."

"I don't care," returned Smithy doggedly. "I've made up my mind and I'm not going to change it."

Ignoring Dick's continued protestations, Smithy unfolded a newspaper and laid it out flat on his bench. Watched by his mutinous assistant, he reached to the rear of Dick's bench and pulled forward a large wooden box with an open top. Staggering under its weight, Smithy carried it over to his own bench and, with one decisive gesture, up-ended it onto the newspaper. There was a shattering crash as a myriad of pieces of metal,

plastic and glass cascaded onto his bench, to form a precarious pyramid. Several dozen screws rolled off the newspaper and clattered onto the floor. They were closely followed by a large bulbous valve on a British 4-pin base, which imploded loudly as it struck the Workshop linoleum. The contents of the box had, apparently, been hovering around critical mass; albeit in a condition of stability until disturbed. Suddenly, a dense mushroom cloud of fine dust appeared above the heap on Smithy's bench, then gradually commenced to diffuse through the Workshop.

Smithy retreated hastily.

"Ye gods," he spluttered. "This is the biggest accumulation of rubbish I've ever seen in all my life."

Dick surveyed his prized collection, now rudely exposed to the public gaze, with an air of resignation.

"All I can say," he remarked, shrugging his shoulders, "is that when I start to collect junk, I certainly make a proper job of it."

"I'll say you do," grunted Smithy. "This must be the most unsavoury and insanitary heap of debris I've ever clapped my eyes on."

By now the cloud of dust had begun to disperse, and Smithy edged warily towards the pile.

"Right," he announced briskly. "Now, let's see what we've got here."

Smithy gazed at the wide diversity of objects he had emptied out onto his bench.

"I must say that you do go in for variety," he remarked, a grudging note of admiration entering his voice. "Where did all these transformer lams come from?"

"Lams? Oh, you mean laminations! They're from an old mains tranny I stripped down way back in 1965 or 1964."

"Couldn't you," asked Smithy a little testily, "have kept them all together in a little cardboard box or something?"

"So far as I remember," replied Dick airily, "I did originally put them in a neat little pile in the corner of the junk-box. Since then, though they've tended to get distributed a bit."

THE RADIO CONSTRUCTOR

"You can say that again," returned Smithy shortly. "Well, I'll put them on one side as I come to them."

Smithy placed about a dozen laminations tidily at the edge of his bench, then dug into the junk once more.

"What are these?"

"What are what?"

"These cylinders of fluff with wires poking out each end."

"Those," replied Dick with dignity, "are 0.01 μ F wax covered paper capacitors which I snipped out of an old TV."

"Then, said Smithy decisively, "they can be ditched right here and now. To start off with, you should always look upon old wax covered paper capacitors with suspicion, especially if they're ex-equipment and have therefore been subjected to a number of heating and cooling cycles. This is because they tend to become leaky more frequently than the plastic or metal cased types. However, so far as these particular specimens are concerned there's no point in even worrying about their internal leakage. The leakage path on the outside through the grime and dust which has got stuck onto the soft wax covering will be more than conductive enough to render them unserviceable. Blimey, more laminations!"

Smithy threw the capacitors of hirsute appearance into his rubbish bin, after which a further pile of laminations clattered on top of those already stacked on the edge of his bench.

WIRE-WRAP TAGS

Smithy once more delved into the pile.

"Blow me," he commented. "What's this?"

"That?" replied Dick, turning his attention reluctantly to the object Smithy had produced. "Why, it's just the edge of a broken printed circuit board, that's all."

"What on earth," asked Smithy, holding up the jagged-edged piece of Paxolin, "did you want to keep this for?"

"Because it's got a neat row of tags on it," explained Dick. "I'd intended—when, that is, I could snatch a fleeting second from my onerous duties repairing radios and TV's—to cut off the broken edge with a hacksaw and then use that bit of Paxolin as a tagstrip. Incidentally, there weren't half some queer connections to those tags originally. The wires were merely twisted around them without being soldered at all. I just peeled them off."

"These," pronounced Smithy, looking at the tags more closely, "are wire-wrap tags."

"Wire-wrap tags?"

"That's right," confirmed Smithy. "Wire-wrap tags have been used quite a lot in domestic TV sets. If you look at each tag closely you'll see that the bit which takes the wire has a rectangular cross-section with quite sharp corners. (Fig. 1(a)). The wire connecting to it is wound on it under tension with a special wire-wrap tool."

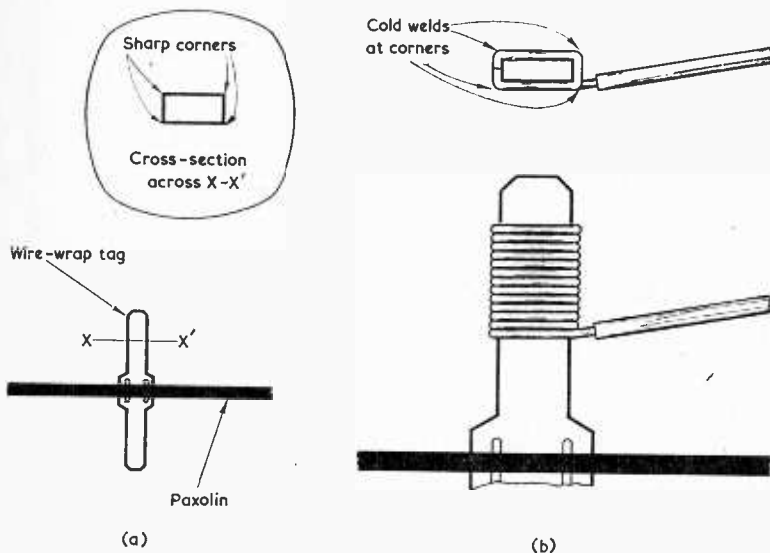


Fig. 1(a). The basic shape and cross-section of a wire-wrap tag
(b). Side and top views, showing how the connecting wire is wrapped around the tag

Your Local Supplier

LONDON

Established 1910

**H. L. SMITH
& CO. LTD.**

*Comprehensive stocks of
components by
all leading makers.*

287-9 EDGWARE ROAD
LONDON W.2.

Tel: 01-723 5891

THE
MODERN BOOK CO.

*Largest selection of English &
American radio and technical
books in the country.*

19-21 PRAED STREET,
LONDON, W.2

Tel: PADdington 4185/2926

TAKE THE SLOG OUT OF SOLDERING

With this lightweight miniature solder iron fitted with high efficiency nickel plated bit, & powerful 15 watt element ANTEX model CN240 volts
Special low price. ACT NOW **29/11**

TRANSISTORS

ACY22 1/9 OC45 1/9 ZTX300 1/9
BC108 1/9 OC71 1/9 2N706 1/9
BFY51 1/9 OC200 1/9 2N2926 1/9
BFY52 1/9 OC202 1/9 2N3708 1/9

All the above types are available at 1/6 for £1. Brand New. Individually tested.

MONEY BACK GUARANTEE p&p 1/-

J. M. KING (W), 17 Buckridge,
Portpool Lane, London, E.C.1

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

**FORRESTERS NATIONAL
RADIO SUPPLIES LTD.**

70-72 Holdenhurst Road

Bournemouth

Telephone 25232

"No solder?"

"None at all," said Smythy. "Due to the shape of the tag and the tension on the wire when it's wrapped round it, you get cold welds at each corner. (Fig. 1(b)). The joints are said to be more reliable than those you get with ordinary soldered joints. In fact, wire-wrap tags are used quite extensively at telephone exchanges and places like that instead of soldered tags."

"That's news to me," remarked Dick. "What happens if you have to take the existing wire off a wire-wrap tag and then put a new one on in its place? Do you just twist the new wire round the tag?"

"Oh no," replied Smythy, shocked. "You can't make a wire-wrap joint without using the proper wire-wrap tool. If you ever have to disturb a wire-wrap joint you afterwards treat the tag as though it were an ordinary solder tag, and solder all the connections that are made to it. Hallo, what have we here?"

Amidst a flurry of laminations, Smythy unearthed a cylindrical aluminium component having a diameter of about 3 ins., and with a hole passing through its centre. At one end were three mounting brackets spaced at 120° intervals.

"It's a TV focus magnet assembly," volunteered Dick.

"So I see," agreed Smythy thoughtfully. "This is the type which used two ceramic ring magnets, each of which exhibited one pole on one of its plane surfaces, and the other pole on the other plane surface." (Fig. 2(a)).

"That's right," put in Dick eagerly. "The assembly fitted over the neck of the c.r.t. and you adjusted the magnetic field it exerted on the beam in the tube by varying the distance between the two magnets. (Fig. 2(b)). The magnets had similar poles facing each other, whereupon the intensity of the field inside the tube neck could be altered until it produced correct focus on the screen."

"These focus assemblies are a bit out of date now," commented Smythy, "seeing that modern tubes use electrostatic focusing. Still, they're worth stripping down, if only for the sake of the magnets. The ceramic magnets that are used in them are extremely powerful and they're just the job for mounting on the back of the bench for holding things."

"What sort of things?"

"Small ferrous objects of the type that are always getting lost," replied Smythy. "Paper clips, razor blades and things like that. (Fig. 2(c)). When you've finished with any of these you just chuck it in the general direction of the magnet. The magnet is so strong that the

object shoots straight towards it and is then conveniently kept available for the next time you need it."

Dick picked up the focus assembly and carried it purposefully back to his own bench.

"I'll strip this down later on," he called out. "You can have one of the magnets for your own bench, Smythy."

"Fair enough," said the Serviceman. "Incidentally, if you're unlucky you may find that the magnets are secured inside the assembly with adhesive, whereupon you may not be able to remove them. In most of these assemblies, though, the magnets are held down by

means of simple clamps which can be readily unscrewed."

As Dick returned to Smythy's bench he found the Serviceman busily probing further into the contents of his junk-box. The Serviceman had already salvaged a sizeable quantity of nuts, bolts, washers and similarly useful items of hardware. The stack of laminations at his side had grown to about an inch in height. As Dick sat down alongside him, Smythy contemptuously threw into his rubbish bin a $\frac{1}{2}$ watt carbon resistor, whose lead-out wires protruded by slightly less than 1/32in.

"Dash it all, Dick," grumbled Smythy, as he reached into the heap once more, "I've never ever seen so much muck before. Yeuk, what's *this* revolting mess?"

Smythy picked up another transformer lamination, to find a further half-dozen laminations adhering loosely to it by means of a sticky mass of yellow gelatinous material. Whilst the shuddering Serviceman held the first lamination up in the air, the weight of the remaining laminations caused the viscous coagulation which bonded them together to slowly extend in length until it became stretched out in the form of a thin string. Smythy gazed at this phenomenon with fascinated aversion, then started as the string suddenly snapped and he was left holding the single lamination on its own. The released laminations returned to their previous junk-box companions with a clatter, followed by a little puff of dislodged dust.

With an expression of acute disgust, Smythy threw the lamination he was holding into his refuse bin.

"Blimey," he gasped. "I'm going to have nightmares tonight, that's for certain. Just what *was* that horrible sticky wedge of stuff?"

Dick frowned.

"Search me, Smythy," he replied. "I never knew I had that in there. Wait a minute, though!"

Suddenly, his brow cleared.

"I remember what it was now," he went on cheerfully. "If you can cast your mind back you may recall that I had a very heavy cold three or four Christmases ago. I'd just started sucking this cough lozenge when I had an uncontrollable urge to sneeze."

Dick leaned forward, picked up the laminations which were still held in the sticky embrace of the congealed yellow substance, and regarded the latter with affection.

"I've often wondered," he remarked, "just where that cough lozenge did get to."

REFRACTIVE INDEX

Irascibly, Smythy snatched the laminations from his assistant's

THE RADIO CONSTRUCTOR

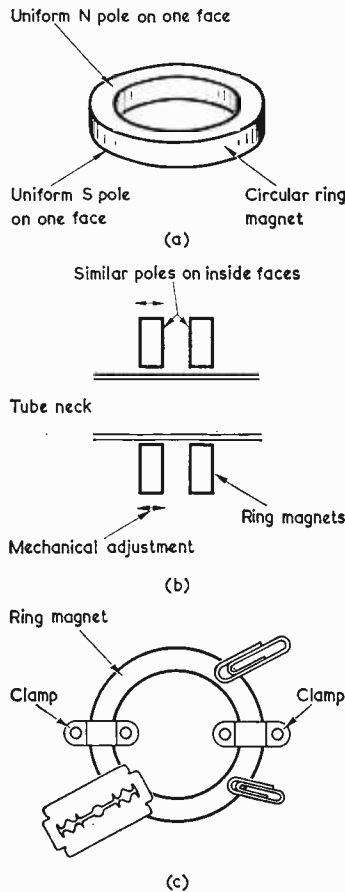


Fig. 2(a). Before the general use of electrostatic focus cathode ray tubes in TV receivers, magnetic focus assemblies employed ceramic ring magnets, as here (b). The distance between the two magnets in a focus assembly was adjusted to vary the focusing field inside the tube neck

(c). The magnets from discarded assemblies are very powerful, and are extremely useful for holding razor blades and similar ferrous items which normally tend to get lost

hand and cast them into his bin. "Well, we know where it went now," he said irately. "Let's see what further abominations we can unearth from the contents of this Pandora's box of yours."

Once more, Smyth attacked the heap of component parts which had been deemed worthy by Dick to share the dusty comforts of his junk-box. The collection of salvaged laminations and small items of hardware on Smyth's bench grew, interrupted on frequent occasion by a grunt of disapproval and the disposal of some hapless component into his refuse bin.

"There's a piece of glass rod here," said Smyth suddenly. "Now, I wonder what you intended to use this for."

Although Dick had largely forgotten his original indignation at Smyth's cavalier action in investi-

"What," he growled, "is so special about it?"

"It gives different degrees of refraction," explained Dick, "for different colours of light."

"Well," remarked Smyth, unwillingly allowing his curiosity to rise. "All glass does that to a small extent, doesn't it?"

"Not as much as that sample of glass you've got there," stated Dick. "The refraction shown by the particular glass that rod is made of varies as much as 180 degrees from one colour to the next."

"Come off it," snorted Smyth. "A statement like that cannot possibly be true."

"Yes it can," persisted Dick. "And, what's more, I'll prove it to you! Let's borrow your note-pad for a moment."

Reluctantly, Smyth passed his pad over to his assistant.

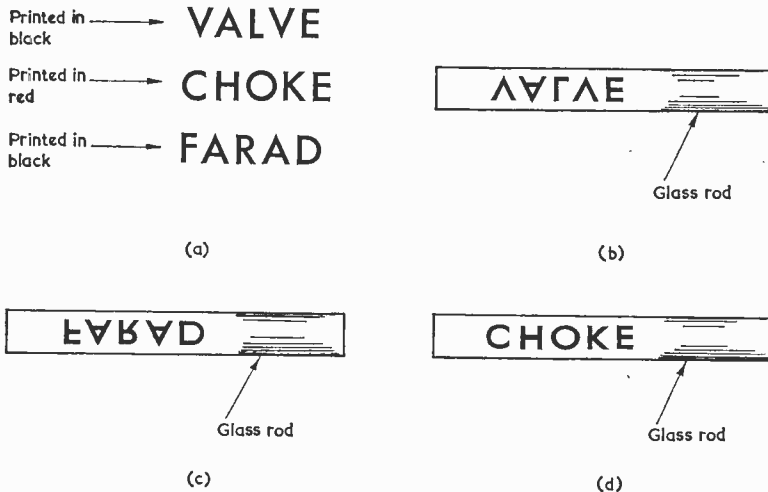


Fig. 3. An interesting exercise in refraction, employing a glass (or Perspex) rod of circular cross-section as a lens. In (a) three words are printed on a sheet of paper, two in black and one in red. When viewed through the glass rod the two words in black appear inverted ((b) and (c)) whereas the word in red appears as printed. This experiment (which can be extremely puzzling to the uninitiated) may be readily repeated by readers

gating the contents of his junk-box, a feeling of affront still prevailed. As he looked at the rod Smyth held up in the air a sudden, and immediately suppressed, gleam came into his eye.

"That," he remarked mysteriously, "is not an ordinary glass rod."

"Isn't it?" queried Smyth. "It looks perfectly ordinary to me. Just a round solid glass rod about 4 inches long and $\frac{3}{8}$ inch in diameter."

"I'm not talking about its dimensions," returned Dick airily. "I'm talking about the glass itself. It's the glass that's special."

Smyth squinted suspiciously at the rod.

"Right," said Dick, reaching in his pocket and taking out two ball-point pens. "Now I'll print three words on this pad, two in black and one in red. The actual words don't matter, so let's choose some that have to do with electronics. At the top I'll print the word 'VALVE' in black. Then I'll print 'CHOK' in red and, finally, put 'FARAD' at the bottom, in black. All right?" (Fig.3(a)).

"I can't see anything wrong so far," grunted Smyth distrustfully. "What happens next?"

"I'd like you," said Dick, "to hold that glass rod over the paper so that it's level, horizontal and

Your Local Supplier

KENT

EMSAC BASIC ANTENNA SYSTEMS

CN1 Nuvistor 2 metre converter. IF 28MHz. Absolutely complete with separate mains power supply. £11.10.0 Converter only. £8.10.0 P&P 4/6.

GD1 A G5RV type multi-band dipole 102 ft. top. 100 ft. feeder. Complete and ready to go! 80/-.

GV1 General purpose vertical, useful range 1.8MHz to 28MHz. Adjustable 7 ft. to 23 ft. 92/-.

TU2 Receiver antenna tuning unit. Amateur and SW broadcast bands 1.5 to 30 MHz. 90/-.

Send SAE for details. Open weekends. G31AR Carriage extra

ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD.
Highfield House, West Kingsdown, Kent
Tel: West Kingsdown 2344

SURREY

Portable Transistor Amplifier



Many uses - Intercoms, Baby Alarms, Guitar Practice, Telephone or Record Player Amplifier. ONE WATT OUTPUT. Wooden cabinet 12x9x4". Rexine covered two-tone grey. Four transistors, 7x4" speaker. Volume control. Jack socket. Uses PP9 battery. Brand new - full makers' guarantee. Full List 1/-

Worth double our price

79/6

Post Free

Radio Component Specialists

337 Whitehorse Road, West Croydon, Surrey. Phone 01-684-1665

SUSSEX

E. JEFFRIES

For your new television set, tape recorder, transistor radio, and hi-fi equipment.

PHILIPS, ULTRA, INVICTA, DANSETTE, MASTERSON, PERDIO, MARCONI, PHILCO, FIDELITY

6A Albert Parade, Victoria Drive, EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of IRISH enthusiasts we supply:

The Radio Constructor, Data Books and Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

about half an inch away from the paper surface. First pass it over the top word in black. Now, what do you see?"

"What I'd expect to see," growled Smyth impatiently. "The word 'VALVE' upside-down." (Fig.3(b)).

"Now do the same over the bottom word in black."

"The same thing happens," said Smyth irritably. "This time, it's the word 'FARAD' which is inverted." (Fig.3(c)).

"That inversion," remarked Dick knowledgeably, "is given because those two words are printed in black. Now, hold the glass rod over the word that's printed in red."

Smyth held the rod over the central word, glanced down at it then exclaimed with astonishment. (Fig.3(d)).

"Blow me," he gasped, "the word's right way up!"

With an expression of incredulity Smyth examined the glass rod closely. This enterprise yielding no clue he held the rod over the paper once more, then passed it slowly over the three printed words on its surface.

"This," he muttered to himself, "just cannot be happening."

"I told you," said Dick triumphantly, "that that rod was made of special glass. But you wouldn't believe me, would you?"

"I still don't," returned Smyth flatly. "But at the same time I don't know why it inverts only the two words printed in black and not the one printed in red."

Yet again, the frowning Serviceman passed the rod over the three words. Scowling ferociously, he gazed deeply at the paper and then at the rod. Suddenly, he gave vent to a great roar of laughter.

"You crafty devil," he chuckled. "You certainly had me on the hook there for a bit, didn't you?"


"D'you see how it's done?" "I do," grinned Smyth. "And I'll also agree that you succeeded in putting one over on me as well. You will, of course, get the same effect with any solid glass rod of about the same diameter."

"That's right," agreed Dick. "A solid Perspex rod will do it just as well, too. For best results you want to print the letters so that their height is a little less than the diameter of the rod."

"Very good," commended Smyth. "Very good, indeed. Well, after that little diversion let's get back to this junk of yours."

RESISTANCE BOX

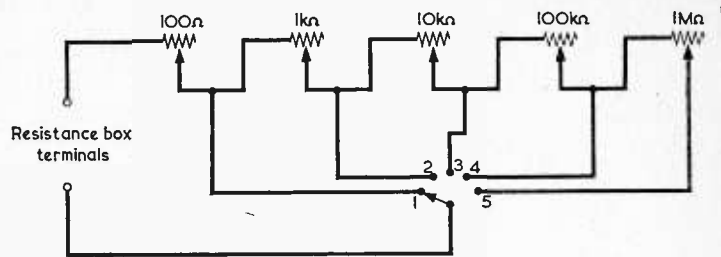
Smyth cleared some further laminations from the pile, abstracted a few more nuts and bolts, then picked out about a dozen panel-mounting potentiometers.




Ranges

- 1 - 0-100n
- 2 - 100n-1.1kn
- 3 - 1.1kn-11kn
- 4 - 11kn-110kn
- 5 - 110kn-1.1Mn

(a)

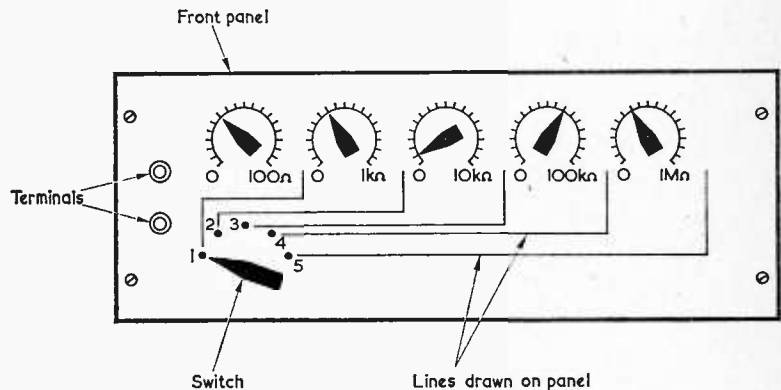

(b)

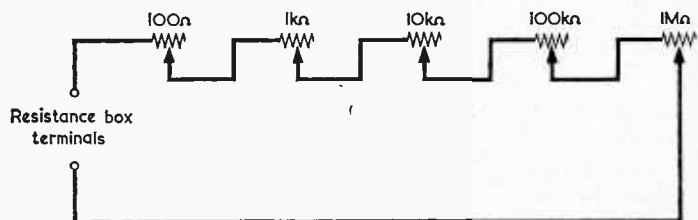

(c)

Fig. 4(a). A simple resistance substitution box. All the potentiometers have linear tracks. The function of the switch is to cut out of circuit the potentiometers having track values higher than the resistance required across the terminals; this fact is reflected in the range figures quoted

(b). A suitable front panel layout. The lines drawn on the panel illustrate graphically the potentiometers that are switched into circuit

(c). Dick's alternative circuit, which omits the switch, is not satisfactory in practice

"Why, that's interesting," he remarked. "You've got quite a lot of pots here which look pretty new to me. Funnily enough, they're all linear track types. Let's have a look at their values."

Smithy examined the potentiometers carefully.

"There's quite a nice little run of values as well," he resumed, laying the potentiometers on his bench in a row. "Amongst them, there's a 100Ω, a 1kΩ, a 10kΩ, a 100kΩ and a 1MΩ."

"I didn't know I had all those," admitted Dick. "They must have gone into the box at different times and somehow managed to find the same level afterwards."

"If they're in working order," remarked Smithy musingly, "you could make them up, together with a single pole 5-way switch, into a simple little resistance substitution box."

"Could I?" asked Dick. "How?" Smithy retrieved his note-pad, removed the top sheet on which Dick had printed his three words, two in black and one in red, then scribbled out a circuit on the sheet underneath. (Fig. 4(a)).

"Here we are," he remarked. "This circuit is for a simple resistance substitution box offering continually variable resistance values from about 10Ω to about 1.1MΩ. You need five linear track pots, with values respectively of 100Ω, 1kΩ, 10kΩ, 100kΩ and 1MΩ. What you do is to mount the pots on the panel of a suitable box, then fit them with pointer knobs and scales. (Fig. 4(b)). Each scale is calibrated in terms of the resistance the particular pot behind it inserts into circuit, the calibration being carried out with the aid of a testmeter switched to read ohms, or of any other resistance-measuring instrument."

"What's the function of the 5-way switch?"

"To select the range of resistance you want to appear at the two terminals of the box," replied Smithy. "If, for instance, you want a resistance in the range of 1.1 to 11kΩ you set the switch to Range 3. The 100Ω, 1kΩ and 10kΩ pots are then in series and the total resistance appearing across the terminals of the box is equal to the sum of the resistances shown on the scales of these three pots."

Dick looked impressed.

"It occurs to me," he said, after a moment's thought, "that you could do all this without a switch at all. All you need to do is simply connect all the pots in series."

Dick picked up Smithy's pad and sketched out a further circuit. (Fig. 4(c)).

"This," he announced, "is what I have in mind. If you want resistances up to say 10kΩ, all you

need then do is to set the 100kΩ and 1MΩ pots to zero and adjust the 100Ω, 1kΩ and 10kΩ pots to the value you require."

"In theory that's fine," replied Smithy. "But in practice it wouldn't work."

"Why not?"

"Because ordinary panel-mounting pots of the type we're discussing here don't always give zero resistance when their spindles are turned fully to the limits of their travel. What usually happens is that a small amount of the track is still left in circuit. The resistance offered by that small section of the track doesn't upset the operation of the pot in its normal application because it's usually a tiny fraction of the overall track resistance. But in the present application that small amount of resistance could upset things completely. Let's say, for instance, that when the 1MΩ spindle is turned fully anti-clockwise, the resistance between the slider and the appropriate end terminal is 100Ω. This is negligibly low compared with the full track resistance of 1MΩ. In the present circuit, though, that 100Ω would completely upset the accuracy of results given with the 100Ω and 1kΩ pots. A further argument against omitting the switch is that the minimum resistance obtained with the 1MΩ pot wouldn't always be constant in any case; it's so very tiny compared with total track resistance that you're bound to get variations in its value."

"You've got me convinced," grinned Dick. "In other words, you adjust the switch so that the minimum number of pots is employed for setting up the resistance you require."

"That's right," confirmed Smithy. "Not only would a resistance box of this nature use up those gash pots you've had lying around all those years, but it would also be quite a useful bit of experimental gear in its own right. Anyway let's get some more of this junk of yours cleared out."

HIDDEN OCCUPANT

Smithy had been automatically sorting out further components from the heap on his bench as he spoke. When he turned his full attention to the parts left on his newspaper he was surprised to find how much progress he had made. Only about a twentieth part of the original mass of components remained.

"Laminations, laminations, laminations," he grumbled, as he added several dozen more to what had now become quite an impressive pile at his side. "These darned transformer lams seem to have got in everywhere amongst this rubbish.

Why, here's another dozen, all spread out. Ooh, my Gawd!"

Smithy suddenly snatched back the hand which had been on the point of picking up the laminations. He clutched Dick's arm in panic.

"What on earth's up?"

"There's a *thing* in there amongst those lams," whispered Smithy. "A horrible, stealthy, hairy thing. It just slithered under the top lam as I put my hand out towards it."

Unconcernedly, Dick poked his finger at the lamination in question.

"For heaven's sake," gasped Smithy, "have a care, boy. Who knows what nameless horror lies lurking amongst those lams?"

"Corluvaduk," said Dick in disgust. "What's all the fuss about? It's probably only a spider."

"A spider? A *spider*? What species of spider is it that can live all these years on bits of brass and copper and tin and p.v.c.?"

"He's probably been living on all the other insects that are left in there."

Smithy's lower jaw sagged and he gazed at the remaining junk with revulsion.

"I'm not," he remarked resolutely, "going to entertain a whole crowd of insects on *my* bench."

With a shrinking gesture, Smithy carefully gathered up the four corners of the newspaper on his bench, then used this to carry its burden of electronic and entomoid scrap through the door of the Workshop. The hasty banging of the dustbin lid outside next proclaimed that Smithy, as befits any honest ratepayer, had decided to entrust his difficulties to the good offices of the local Cleansing Department.

This is, perhaps, a fitting moment at which to leave our pair as, after having satisfactorily settled the problem of Dick's junk-box, they turn their energies to the more prosaic and predictable pursuit of repairing faulty radio and television receivers. There remains only the question of those words in black which were inverted by Dick's glass rod, and of that in red which was not. Readers who have not already spotted the simple secret of this phenomenon have merely to do a little inversion of their own in order that they may read what follows.

LETTER INVERSION

The word 'CHOKE' was, of course, inverted by the glass rod in just the same way as were the other two words. However, the individual letters in 'CHOKE' are asymmetrical about their horizontal centre line and appear the same after they have been inverted. Other letters offering the same result are B, D, I and X.

CURRENT TRENDS

ITT Components Group Europe are now introducing a range of high-quality, low-cost electric counters to the U.K. market. Basic models are:

E507 ELECTRIC COUNTER

A compact, reliable 5-digit electric counter. Tamperproof and non-resetting, it is well suited to vending application. Standards models designed to UL specifications are available for normal d.c. voltages and 240V 50/60Hz, but other voltages and frequencies can be supplied. Count pulse length may be from 50 ms upwards; minimum pulse off time is 50 ms.

The frame is finished in bright aluminium, and base or panel mounting variants are offered. Operating ambient temperature range is 0°F to 160°F. The unit will count accurately at speeds up to 600 counts per minute through a minimum life of one million

counts. Power consumption 3.6 watts.

E602 ELECTRIC COUNTER

A high-speed 6-digit counter with pushbutton quick reset (instant zeroing). Speed is up to 1,000 counts per minute and life is conservatively rated at 10 million counts. It can be actuated by any switch, relay, photoelectric or other circuit breaking device that makes and breaks without chatter, minimum duration for both make and break being 30 ms.


Power consumption is 6 watts and the counter is available in 6V, 12V, 24V, 48V and 100V d.c. ratings, and 100V, 120V, 200V and 240V 50/60 Hz a.c. ratings. It meets a wide range of requirements on laboratory equipment, office machines, coin-operated machines and many kinds of industrial machines.

E610 & E410 ELECTRIC COUNTERS


Very fast counters intended for long service. The 6-digit E610 is rated at 2,100 counts per minute, the E410 at 1,200, and conservative life rating in each case is 30 million counts. Both feature pushbutton quick reset (instant zeroing), and are available for base or panel mounting.

Consuming 5 watts at 6V, 12V, 24V, or 48V d.c. as required, they can be actuated by any chatter-free switch or circuit breaking device. Minimum pulse on time for the E610 is 19 ms, minimum pulse off time is 9.6 ms. Corresponding times for the E410 are 25 ms and 25 ms.


Both counters have die-cast hous-

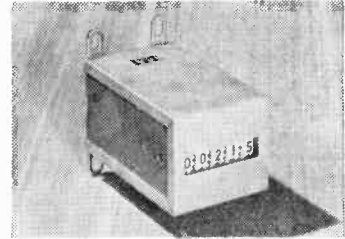

The E507 Electric Counter

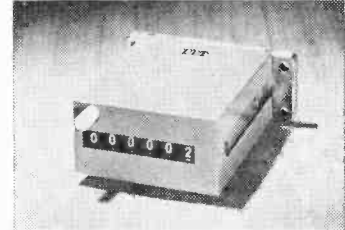


The E602 Electric Counter

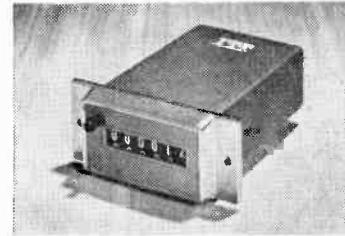

The E610 Electric Counter

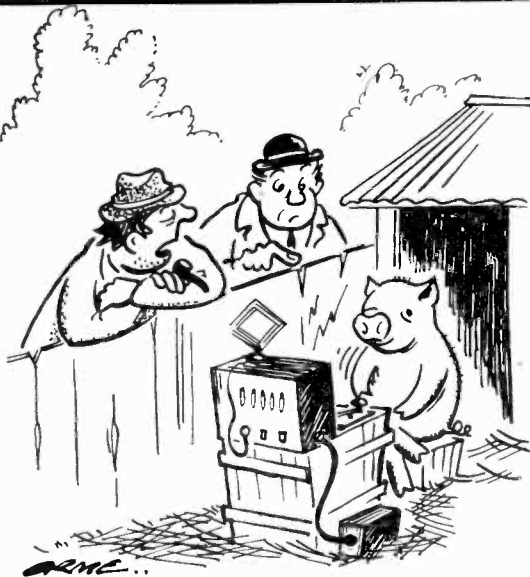ing with nickel-plated aventurine finish. They provide a wide range of requirements for built-in counters on industrial, laboratory and office equipment, coin-operated machines, and conveyor lines. From: ITT Components Group Europe, Trading Services, Edinburgh Way, Harlow Essex. Telephone Harlow 26811, telex 81146.



"Do you mean to say you've never heard of a ham radio operator?"

SGS PUBLICATIONS

Two publications - 'Industrial Discrete Devices' and 'Integrated Circuits' - are now available from SGS (United Kingdom) Ltd. 'Industrial Discrete Devices' lists all SGS discrete semiconductor devices (diodes, transistors and phototransistors) intended for industrial applications, together with full details of characteristics and operating conditions. A short section at the beginning of the publication enables specific devices to be located quickly in terms of the more important characteristics and applications. 'Integrated Circuits' has a similar section at the beginning for location of integrated circuits, then gives full information on all SGS integrated circuits, including linear and logic units. Both publications may be obtained from Data Services Department, SGS (United Kingdom) Ltd., Planar House, Walton Street, Aylesbury, Bucks. The price of each is 21s.

LONDON AMATEUR RADIO MOBILE RALLY

The Ealing and District Amateur Radio Society is holding its first Mobile Rally on 10th May, 1970 at Hanwell Community Centre, Westcott Crescent, Hanwell, London, W.7. The rally is believed to be the first ever held in London.

THE RADIO CONSTRUCTOR

LATE NEWS

★ AMATEUR BANDS

● SWITZERLAND

4U1TU has been heard on Top Band cw and also on 21MHz. QTH given as U.N. Geneva.

● PORTUGUESE GUINEA

CR3KD heard using cw and ssb modes on 14MHz band.

● 3.5MHz

Dx activity at the ssb end of the band still continues apace during the early mornings. Heard recently were - HC2GG/1, OA4LNA, OA8V, PZ1AH, VO1FX, W3GQF, W4OKZ and W4RDD/VP9.

● SENEGAL

Very active on 14MHz cw recently has been 6W8DQ. If you can work him under the 'wolf-pack' QRM you'll be lucky!

★ BROADCAST BANDS

● LEBANON

Beirut (100kW) now broadcasts to Africa from 1830 to 2030 on 15350 and to S. America from 2300 to 0100 on 17715. The service to N. America from 0230 to 0300, in English, on 11790 remains unchanged.

● PAKISTAN

Another new channel has been observed by our Listening Post (see Now Hear These, April issue) and was first heard early in February. Now identified as Peshawar on 3940, with Indian-type music at 1640. At 1700 a newscast in Urdu is preceded by 6 'pips'. Closes at 1730.

● HAITI

Radio Lumiere has increased power to 10kW. Listed on 2410, schedule from 1000 to 0300 and 9635, schedule from 1300 to 0330, both with a power of 250 watts.

● INDIA

All India Radio is currently installing two new 100kW transmitters for European coverage. Tests are expected to commence next month. Reports will be required.

● MALTA

Duetsche Welle is to set up a relay station for services directed to Africa mainly in the Arabic language.

● VENEZUELA

Radio Barquisimeto is reported to have increased power from 10 to 15kW. R. Barquisimeto operates on 4990 and 9510kHz. On the former channel the schedule is from 1000 to 0400GMT and on the latter from 1200 to 0300GMT. The address is - Apt. 567 y 576, Barquisimeto and verification is by QSL card.

● CUBA

Radio Havana (50kW) has changed frequencies for the English to N. America programme and is now on 9550 and 11970, replacing 9525 and 11860.

● SYRIA

Damascus (50kW) has moved back to 15165 from 9670, broadcasting to Europe in German at 1830, French at 1900 and in English at 2030 to 2200 sign off.

Acknowledgements to our own Listening Post and Swedish Dx'ers.

RADIO CANADA

On February 25th, Radio Canada celebrated its 25th anniversary. Plans for the development of CBC's short wave transmitters, located at Sackville, New Brunswick, include the installation of five 250kW transmitters to supplement the three 50kW units which have been in operation since 1945. The aerial arrays will be improved to handle the increased power.

Owing to financial restrictions, the improvements will have to be phased over a period of some four to five years. Two of the new higher-powered transmitters however should be in operation early next year. For the initial transmitting period of from twelve to eighteen months, these new transmitters will only radiate programmes directed to Europe.

In 1945, when the Canadian Broadcasting Corporation began regular international short wave broadcasts of the twenty countries engaged in this activity Canada was in the forefront. At the present time there are about 150 countries having international broadcasting services and Canada has slipped out of the top 50 in terms of

numbers and powers of transmitters. The Radio Canada transmitters operated for seven hours daily in 1945 but today they are

on the air for 22 hours every day serving not only the International Service but also the Northern and Armed Forces Services.

LAST LOOK ROUND

COIL TOIL

Winding coils by hand is always a bind! Induce yourself to make the *Coil Winder* featured in our next issue. Using it is a better method of coil toil than the former!

KNOCK FOR KNOCK!

The motorists amongst us will shudder at the thought! We can, however, remove one of the knocks of life by substituting the knocker with a doorbell. Having a ding-dong is more preferable than a knock-knock! See *Simple Electronic Doorbell* in the June issue.

TAPE RECORDING

If you want to get this subject taped and erase any misconceptions, you certainly won't be on the wrong track if the information on pages 621 to 626 is recorded in your mind. Playing time for this subject is the next seven issues.

Choice + Value + Service

equals Lasky's!

Absolutely unlimited choice from the largest stocks in Great Britain of everything for the radio, Hi-Fi and tape recording enthusiast, electronics hobbyist and home constructor, serviceman and communications ham. Unbeatable value – exclusive lines at Lasky's exclusive prices including Budget Stereo Systems and Package Deals. Outstanding service backed by over 36 years experience in every aspect of audio and electronics. Visit any of our West End and City branches, including two specialised high fidelity centres: 42-45 Tottenham Court Rd., W.1 and 118 Edgware Rd., W.2 or send at once for the 1970 edition of our famous **Audio - Tronics and Hi-Fi Catalogue** bringing 1000's of items from our vast stocks to you in the comfort of your own home **PLUS our amazing monthly Money Vouchers worth over £25.**

THIS MONTH'S VOUCHER WORTH 40/-

Send your name, address and 2/- to cover post only and the inclusion of your name on our regular mailing list – to Dept. RC, 3-15 Cavell Street, London, E.1.

Branches

42-45 TOTTENHAM CT. RD., LONDON, W.1	Tel.: 01-580 2573
33 TOTTENHAM CT. RD., LONDON, W.1	Tel.: 01-636 2605
118 EDGWARE ROAD, LONDON, W.2	Tel.: 01-723 9789
207 EDGWARE ROAD, LONDON, W.2	Tel.: 01-723 3271
152/3 FLEET STREET, LONDON, E.C.4	Tel.: 01-353 2833

MAIL ORDERS : 3-15 CAVELL ST., LONDON, E.1

Lasky's
MEMBER OF THE HFDA



RADIO CONTROL FOR MODELS



RADIO CONTROL FOR MODELS

SHIPS, BOATS and AIRCRAFT

By F. C. JUDD

With sections on servo-mechanisms by

RAYMOND F. STOCK

More than 200 illustrations – circuits, working diagrams, photographs & tables. Each page is packed with information.

192 Pages

15s. Postage 9d.

This book is basically an amalgamation of "Radio Control for Model Ships, Boats and Aircraft" and "Radio Control Mechanisms". Additional material has been added on Multi-Channel Operation; Transistorised Radio Control Receivers—Simple and Three-Channel; A Compact Efficiency Aerial; Deac Battery Information; Licence Conditions, etc.

To Data Publication Ltd., 57 Maida Vale, London, W.9

Please supply.....copy(ies) of your publication "RADIO CONTROL FOR MODELS" DATA BOOK No. 16.

I enclose cheque/crossed postal order for.....

NAME

ADDRESS

BLOCK LETTERS PLEASE

THE RADIO CONSTRUCTOR

SMALL ADVERTISEMENTS

Rate: 9d. per word Minimum charge 12/-
Box No. 2/- extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, The Radio Constructor, 57 Maida Vale, London, W.9.)

NEW CATALOGUE NO. 18, containing credit vouchers value 10/-, now available. Manufacturers new and surplus electronic and mechanical components, price 4/6d. post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex.

SERVICE SHEETS. Radio, Television, Transistors, Tape Recorders, Record Players. Catalogue 2/6d. S.A.E. please. Hamilton Radio, 54 London Road, Bexhill, Sussex.

BUILD IT IN A DEWBOX robust quality plastic cabinet 2in. x 2½in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now—right now.

TRANSISTOR AMPLIFIER KIT. 9V, 500mW into 3 ohms. Low current drain, 3-transistor. All parts with circuit, 10/6d., p.p. 1/6d. Tested transistors sim. AC128-OC81, 1/- each. Resistors—mixed, 1/6d. dozen. A. Manley, 111 Mayow Road, Sydenham, London, S.E.26.

TO CLEAR. Back numbers of "The National Geographical Magazine", from January 1959. 3/6d. each post paid. Box No. G110.

"FLAME FROM THE AIR". A revolutionary cigarette lighter that has no wick, flints or moving parts; uses no petrol, gas or batteries; cannot be blown out. Awarded gold medal Luxembourg International Trades Fair. 39/6d. plus 2/6d. p.p. from: JW Exports (Dept. M01), 44 Earls Court Road, Kensington, London, W.8.

BOOKS TO CLEAR: "The Upper Atmosphere", Massey & Boyd, 50/-; "KEOEIT", story of the Aurora Borealis 20/-; "The Living Brain", Grey Walter, 10/-; "Teach Yourself Russian", 5/-; "Principles of Modern Book-keeping", 5/-; "Outlook", elementary weather forecasting, 7/6d.; "Practical Nucleonics", experiments in Nuclear Physics, Pearson & Osborne, 25/-; "Health Physics", principles of radiation protection, Rees 50/-; "Violent Universe", Calder, 15/-. All plus postage. Box No. G111.

MUSICAL MIRACLES. Send s.a.c. for details of Drum Sound Modules, versatile bass-pedal accompaniment unit, self-contained with unique effects. Kits for Waa-waa pedals, 49/-. Also bargain components, reed switches, etc. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 35s. per annum. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

WANTED: Glass paper weights. Details to Box No. G117. (Continued on page 645)

BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm, The Old Police Station
LONDON, N.W.1. Gloucester Road
LITTLEHAMPTON, Sussex
01 - 722 9090 PHONE 6743

Please forward all mail orders to Littlehampton

5Z4G	7/-	ECC85	5/6	PC88	10/3	U26	11/9	AC157	5/-	BY126	3/-
6AQ5	5/6	ECC86	8/-	PC95	8/3	U191	12/6	AD140	7/6	BY127	3/6
6AT6	4/-	ECC88	7/-	PC97	8/6	U301	11/-	AD149	8/-	BY210	5/-
6C4	5/-	ECC189	9/6	PC900	7/6	U404	7/6	AD162	9/-	BY211	5/-
630L2	12/-	ECC80	6/6	PC884	6/3	UB01	19/6	AF106	10/-	BY212	5/-
6BR7	15/9	ECC82	6/6	PC835	6/6	UABC80	6/6	AF114	4/-	BY213	5/-
6BW7	13/-	ECC86	9/-	PC888	9/9	UBC81	9/-	AF115	4/3	OC78	3/-
6F23	14/3	ECH42	12/9	PC889	9/6	UBF80	5/9	AF117	4/6	OA79	1/9
6F28	14/-	ECH81	5/9	PC1189	10/6	UBF89	6/9	AF115	3/-	OA81	1/9
6L6GT	7/9	ECH83	8/-	PCF80	6/6	UC92	5/6	AF117	6/-	OA90	2/6
9D7	15/6	ECH84	7/6	PCF82	6/3	UCC84	8/-	AF126	5/-	OA91	1/9
10F18	7/-	ECL80	7/-	PCF84	8/-	UCC85	7/3	AF139	13/-	OA95	1/9
30C15	13/-	ECL82	6/6	PCF86	12/9	UCF80	6/3	AF180	9/6	OA200	5/-
30C17	16/-	ECL83	9/-	PCF200	13/3	UCH21	9/-	AF186	11/-	OA202	2/-
30C18	14/-	ECL86	8/-	PCF801	7/-	UCH42	12/-	AF139	7/6	OC22	5/-
30F5	16/-	EF22	12/6	PCF802	9/-	UCH81	6/6	BA202	9/-	OC23	5/-
30FL1	13/9	EF41	10/-	PCH200	12/3	UCH82	7/-	BA115	2/8	OC24	5/-
30FL14	14/6	EF80	4/6	PCL82	7/3	UCH83	10/-	BA116	5/-	OC25	5/-
30FL15	13/9	EF85	5/3	PCL83	10/-	UF41	10/-	BA129	2/6	OC26	5/-
30L17	15/6	EF86	6/3	PCL84	7/6	UF80	6/9	AF186	11/-	OC27	5/-
30P4	12/-	EF89	5/-	PCL85	9/-	UF85	6/9	BC107	4/-	OC35	5/-
30PAMR	17/6	EF91	3/3	PCL86	8/6	UF86	9/-	BC108	3/6	OC36	7/6
30P12	13/9	EF183	6/-	PEN45DD	15/-	UF89	6/9	BC113	5/-	OC38	8/6
30P19	12/-	EF184	6/-	PFL200	11/9	UL41	10/6	BC118	4/6	OC44	2/-
30P1L	13/9	EH90	7/6	PL36	9/6	UL84	6/6	BCY10	5/-	OC45	1/9
30P13	15/6	EL11	9/6	PL81	9/6	UM80	6/6	BCY12	5/-	OC46	3/-
30PL14	15/-	EL34	10/6	PL82	6/6	UY41	6/6	BCY33	4/-	OC78	3/3
DY87	5/9	EL41	11/-	PL83	6/6	UY85	5/9	BCY34	4/6	OC71	2/-
EB8CC	12/-	EL84	4/9	PL84	6/6	2N404	6/-	BCY38	5/-	OC72	2/-
EABCB80	6/6	EL95	5/3	PL500	13/-	2N1756	10/-	BCY39	4/6	OC74	2/6
EAF42	10/-	EM80	7/6	PL504	13/6	2N2297	4/6	BCZ11	3/6	OC75	2/-
EB7	3/-	EN31	7/6	PL509	28/9	2N2369	4/3	BD119	9/-	OC78	3/-
EB91	2/3	EM8	6/6	PY81	5/3	2N2613	7/9	BFY50	4/-	OC78D	3/2
EBAC41	9/6	EM85	11/-	PY81	5/3	2N3053	6/6	BFY51	4/6	OC81D	2/3
EBBC81	6/6	EM87	7/6	PY82	5/3	2N3703	3/9	BFY52	4/6	OC82	2/3
EBFB0	6/9	EY51	7/6	PY83	5/9	2N3709	4/-	BFY59	5/-	OC83	2/3
EBFB3	8/-	EY87	6/6	PY88	6/9	2N3988	10/-	BF163	4/-	OC84	3/-
EBF89	6/3	EZ40	7/6	PY800	7/6	25323	10/-	BF173	7/6	OC123	4/6
EC92	6/6	EZ80	4/6	PY801	6/9	AA119	3/-	BF180	6/6	OC129	4/6
ECC81	3/9	EZ81	4/9	QQV03/1024	AC113	BY100	3/6	OC172	4/-		
ECC82	4/6	HVR2	10/6	R19	7/6	AC127	2/6	BY101	3/-	OC200	4/4
ECC83	4/6	KTW62	12/6	U19	34/6	AC154	5/-	BY105	3/6	OC202	4/4
ECC84	6/3	PC86	10/3	U25	13/-	AC156	4/-	BY114	3/6	OC203	4/6

Terms of business: Cash with order only. No C.O.D. Post/Packing 6d. per item. Orders over £5 post free. All orders despatched same day as received by first class mail. Complete catalogue including transistor section and components with terms of business 1/-. Any parcel insured against damage in transit for 6d. extra. Business hours 9 a.m.—5.30 p.m. Saturdays 9 a.m.—1 p.m. Littlehampton closed Sats.



EST. 1891

TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success.

Diploma courses in Radio TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- * C. & G. TELECOMMUNICATION TECHNICIANS CERTS.
- * C. & G. ELECTRONIC SERVICING
- * R.T.E.B. RADIO AND TV SERVICING CERTIFICATE
- * RADIO AMATEURS EXAMINATION
- * P.M.G. CERTIFICATES IN RADIO TELEGRAPHY

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-test meter and professional-type valve voltmeter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF ASSOC. OF BRITISH CORRESPONDENCE COLLEGES.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 248, Intertext House, Stewarts Road, London, S.W.8.


NAME _____

Block Capitals Please

ADDRESS _____

570

The "NEOPHYTE" AMPLIFIER

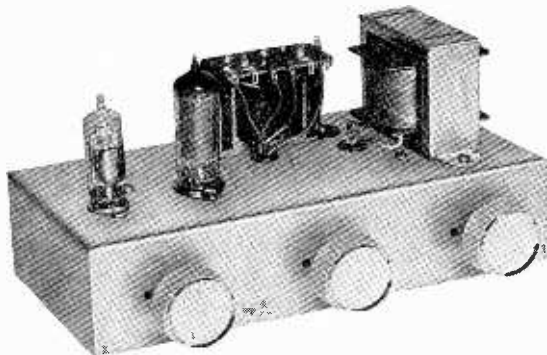

TELERADIO new Hi Fi dept are stocking all parts to build this interesting project.
(SEE OCTOBER ISSUE)

Full details of this and other amplifiers in kit form, from

TELERADIO ELECTRONICS
325-7 Fore St., Edmonton, London N9

JACKSON

the big name in PRECISION components

Precision built radio components are an important contribution to the radio and communications industry.



No. 6/36 DRIVE

Incorporating the Dual Ratio Ball Drive providing 36-1 Slow drive and 6-1 Fast drive under one knob with co-axial control. Scale is calibrated 0-100 and an extra blank scale is provided for individual calibration.

The unit consists of aluminium back plate, drive unit, scale, spare scale, transparent cover, hair-line pointer, escutcheon and knob. Fits in front of panel which may be any thickness up to 1/4" (or more by providing longer screws). Price 24s. each.

JACKSON BROS. (London) LIMITED

Dept. RC, KINGSWAY-WADDON, CROYDON, CR9 4DG
Phone Croydon 2754-5 (01-688) Grams Walfilco, Croydon
U.S. Office: M. Swedgal, 258 Broadway, N. York. N.Y. 10007

UNDERSTANDING TELEVISION



by
J. R. DAVIES

Over 500 pages
300 diagrams

37/6 POSTAGE
3/-

UNDERSTANDING TELEVISION deals with:

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television
- **COLOUR TELEVISION** – 80 page section deals comprehensively with this subject

The reader is required to have only a basic knowledge of elementary radio principles. The treatment is non-mathematical throughout, and there is no necessity for any previous experience in television whatsoever. At the same time, UNDERSTANDING TELEVISION is of equal value to the established engineer because of the very extensive range it covers and the factual information it provides.

To Data Publications Ltd.,
57 Maida Vale, London, W.9

Please supply
UNDERSTANDING TELEVISION, 'Data Book No. 17

I enclose cheque/crossed postal order for.....

NAME.....

ADDRESS.....

BLOCK LETTERS PLEASE

SMALL ADVERTISEMENTS

(Continued from page 643)

MAGAZINES TO CLEAR: *CQ* 1947–November, 1955–April, 1957–February to June, 1959–July to December, complete, 1964–March missing, 1965–complete, 1/6d. per copy. *QST*, 1948 October, 1961 October to December, 1962 September, 2/- per copy. *RSGB Bulletin*, 1956–May, September, October, 1957–August, September, 1958–February, July to December, 1959–60–complete, 1961–August, September missing, 1962–February to May, 1/- per copy. 73, 1963–July, August, September to November, 1967–January, October, 1968 January, February, April & November, 1/6d. per copy. *Wireless World*, 1947–December, 1958–September, 1960–January, April, June, September to December, 1964–January, December, 1965–January to June, 2/- per copy. Box No. G114.

"MEDIUM WAVE NEWS" Monthly during Dx season. —Details from: K. Brownless, 7 The Avenue, Clifton, York.

TELETYPE Instructions booklets for Creed No. 54, Nos. 7 and 8, No. 47, No. 75, No. 85, 6S/6, 'N' type keyboard. 7/6d. each. Relays – Sigma type 72OAZ, octal socket plug-in, £2. Miniature DPDT 10/6d. Box No. G116.

FOR SALE: Transistors mixed (untested), 50 for 12/6d. p.p. 1/6d. Brand new guaranteed transistors 16 for 19/6d. Mixed components, hundreds of resistors and capacitors, 19/6d. Write for list: Edmund Clark Electronics, 377 St. Johns Street, London, E.C.1.

WORLD DX CLUB covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs 25s. a year. Enquiries to Secretary, WDXC, 17 Taunton Road, Bridgewater, Somerset.

FOR SALE: 330 *Radio Constructors*, *Practical Wireless*, etc. Also components. S.A.E. 43 Highgate Lane, Farnborough, Hants.

FOR SALE: Mains transformer, unused. Primary 245V Secs. 4 x 28V, 1A, 1 x 30V, 250mA, £3 10s. Capacitors 1250mf. 50V, 3/-. Silicon rect. 100V p.i.v. 2A, 1/6d. Box No. G120.

ARE YOU A MOTORING ENTHUSIAST? The Seven Fifty Motor Club caters for all types of motor sport—racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancer's End", St. Winifred's Road, Biggin Hill, Kent.

WANTED: Ilford Elmo 8TL-6 or 4 standard 8 cine camera, with 100ft. magazine. Box No. G121.

SURPLUS BOARDS. Grey/green. Compressed laminate. 4in. x 3in. Suit transistor projects. Twelve 3/6d. Six 2/-, post free. Box No. G122.

FREE GIFT when you request our quality stamps, supplied on approval. Generous discounts. Details from: Watson's Philatelic Service, 6 Beech Avenue, Brentwood, Essex.

TO CLEAR: Metal rectifier, Radiospares REC22, 15/-. Push-pull interstage trans. Repanco TT4, 5/-. Pair Mullard OC36 transistors, 15/-. Heat sink to match, 5/-. 50 assorted resistors, 10/-. 50 assorted capacitors, 15/-. Tanoy hand mic., 10/-. Eddystone 2½in. coil formers, 7/6d. Mains transformers: 350-0-350V 250mA, 5V 2A +2, 6.3V 2A, 2V 1A, 15/-. 250-0-250V 100mA, 4V 6.3V 2A, 10/-. 0-140V tapped out, 250V a.c. tapped in, 10/-. Box No. G123.

ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

WANTED: Books, brochures, pamphlets, etc. re FAX. Any information of interest. G2UK, "East Keal", Romany Road, Oulton Broad, Suffolk.

(Continued on page 647)

THE WILSIC MK II REVERBERATION UNIT KIT

A new, all silicon version of our self-contained, 6 transistor, reverberation chamber to which microphones, instruments, tuners or tape recorders may be connected for added dimensional effect. The output is suitable for most amplifiers and the unit is especially suitable for use with electronic organs. A ready-built spring and transducer assembly is used. (58/11 if bought separately).

Complete easy-to-build kit, with constructional notes and circuits: £7.10.0. Pre-drilled and printed case 34/- extra. All parts available separately. Send 1/- for circuit and construction details.

THE IMPROVED WILSIC SIGNAL INJECTOR. Now all-silicon circuit for extra high frequency harmonics. Light and compact, measuring only 3¼" x ½" (excluding probe). Price ready for use, including battery 32/6 post free.



THE WILSIC WAH-WAH PEDAL KIT

SELECTIVE AMPLIFIER MODULE. The basis of the Wah-Wah pedal. Kit contains all the components to build a 2-transistor circuit module, also the sockets, control, etc., required for the constructor to assemble his own design. 35/-.

Assembled and tested module 42/6.

FOOT VOLUME CONTROL PEDAL. Foot pedal unit in very strong fawn plastic. Fitted with output lead and plug for connection to guitar amplifier. May be used for volume control or converted to Wah-Wah by adding the module.

Pedal unit only £5.12.6.

Complete kit for Wah-Wah pedal £7.0.0.

All post free.

Send 1/6 for our catalogue of components, testmeters, musical electronics and more details of the above items.

Callers welcome.

WILSIC ELECTRONICS LIMITED
6 COPLEY ROAD, DONCASTER, YORKSHIRE

FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy ?

ENGINEERING OPPORTUNITIES is a highly informative 164 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses administered by our Specialist Electronics Training Division — explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

"Satisfaction or refund of fee" terms

Whatever your age or experience you cannot afford to miss reading this famous book. Send for your copy of "ENGINEERING OPPORTUNITIES" today — FREE.

Practical Equipment including Tools

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Basic Practice and Theoretical Courses for beginners in Radio, T.V., Electronics, etc. Ask for details.

Which is your pet subject ?

A.M.I.E.R.E. City & Guilds Radio Amateur's Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

The B.I.E.T. is the leading institute of its kind in the world.

Please send
Free Books and
Full Information

**British Institute of
Engineering Technology**

NAME.....

ADDRESS.....

Subject
of interest..... Age.....



ALDERMASTON COURT, Dept 480D, Aldermaston, Berks.

RADIO OPERATORS

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1970 and in subsequent years.

Specialist training courses lasting approximately nine months, according to the trainee's progress, are held at intervals. Applications are now invited for the course starting in September 1970.

During training a salary will be paid on the following scale:-

Age 21	£800 per annum
22	855 " "
23	890 " "
24	925 " "
25 and over	965 " "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade 1 scale:-

Age 21	£965 per annum
22	1025 " "
23	1085 " "
24	1145 " "
25 (highest age point)	1215 " "

then by six annual increases to a maximum of £1,650 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must normally be under 35 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:-

**Recruitment Officer (R.O./63),
Government Communications
Headquarters,**

**Oakley,
Priors Road,
CHELTENHAM,
Glos., GL52 5AJ.
Tel: Cheltenham 21491. Ext. 2270.**

Electronic Test Engineers

Pye Telecommunications of Cambridge has immediate vacancies for Production Test Engineers. The work entails checking to an exacting specification VHF/UHF and SSB radio telephone equipment before customer delivery; applicants must therefore have experience of fault finding and testing electronic equipment, preferably communications equipment. Formal qualifications, while desirable, are not as important as practical proficiency. Armed Service experience of such work would be perfectly acceptable.

Pye Telecom is the world's largest exporter of radio telephone equipment and is engaged in a major expansion programme designed to double present turnover during the next 5 years. There are therefore excellent opportunities for promotion within the Company. Pye also encourages its staff to take higher technical and professional qualifications. These are genuine career opportunities in an expansionist company so write, or telephone, for an application form without delay. Interviews can be arranged anywhere in the country at locations to suit the majority of applicants.

Mrs A. E. Darkin, Pye Telecommunications Ltd., Cambridge Works, Haig Road, Cambridge. Telephone: Cambridge 51351



Pye Telecommunications Ltd



SMALL ADVERTISEMENTS

(Continued from page 645)

FOR SALE: Sinclair Z30 amplifiers, 78/-. Stereo Sixty, 178/-. Eagle A.M. Tuner AMT35, 79/-. P. & J. miniature mains transformers 9-0-9V 80mA, 12-0-12V 50mA, 10/-. Further details: Box No. G124.

BOOKS TO CLEAR: At 1/6d each post paid:- Pelican books - *Man, Microbe & Malady*, *Cine-Biology*, *Science News* Nos. 11, 30, 33, 35 and 51. "Quiet, Evolution of a Scientist", "Discovery". Puffin Book. "Aquarium Management", "Chemistry", "Industrial Electronic Apparatus", "Electronics Made Easy". All at 2/6d. each post paid:- "Mid-century Journey", *Man & The Universe* Lodge, "Men of Science & their Discoveries", "1001 Mechanical Facts", Marshall, "Workshop Hints & Tips", Model Engineer Handbook. All at 5/- each post paid:- "On Scottish Hills, Humble, "Model Engineering Practice", Camm, "Disease & Its Conquest, Hollis, "Ski-ing for Beginners", "Footsteps in Civilisation", "Hotels-Admin. & Accounts", "Principles of Executorship Accounts". All at 7/6d. post paid:- "Radio & Electronic Hobbies" Judd, "The M.E. Lathe Manual" Westbury, "Engines for Small Craft" Barnard, "Thyratrons", Phillips, "Sound & Cine for Beginners", "Maritime Meteorology", Earl, "Cloud Types for Observers" Met. Office, "Science Today & Tomorrow" 2nd Series. "Science Survey No. 3", *Life & Sunday Times World Library: S.E. Asia, Scandinavia, Brazil, Japan, Israel, Britain, Italy, Russia, Mexico, France, India, Germany, Greece, Tropical Africa.* Life Science Library: *Man & Space, Planets, Energy. "The Story of Atomic Energy" Soddy, "The Colour of Canada", "Frontier to Space" Burgess, "Earth Satellite" Moore, "Man The Adventurer", "Man on the Moon", "Practical Yacht Racing".* Box No. G125.

HIGH QUALITY R.F. Generator. 150kc/s - 435Mc/s $\pm 1.5\%$ accuracy. Recently aligned and tested for sale purposes. Fully comprehensive controls. For further details telephone evenings: 01-730-5067.

PROPERTIES for sale and to let in London and suburbs. Apply to Maggs & Stephens, Estate Agents, 229 Maida Vale, London, W.9. MAIDA VALE 8123.


WANTED: Meter for Eagle EP100KN multimeter. Write, quoting price, to G. McCombie, 16 Leamington Road Villas, London, W.11.

POSTAL ADVERTISING? This is the Holborn Service, Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list.—The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407-1495.

HENRY'S RADIO LTD. 303 EDGWARE ROAD, LONDON, W.2

HAVE THE FOLLOWING VACANCIES IN THEIR ORGANISATION
SALES ASSISTANT: Young man with good general knowledge of electronic components required for our retail sales dept. Please telephone 723-1008/9 ext. 1.

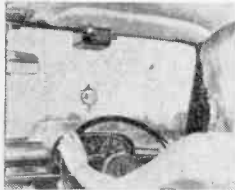SALES ASSISTANT, HI-FI DEPT. Young man with a good general knowledge of HIGH FIDELITY EQUIPMENT required for our retail HI-FI SALES DEPT. Please contact MR. STEVENS, Telephone 723-6963.



RADAR SPOTTER

Protect your Priceless Driving Licence!

Completely self-contained. Clips on to Sun Visor. Detects radar speed trap signals up to two miles on motorways. Completely legal. Six month guarantee. Size 4 1/2" x 3 1/2" x 3". £13.5.0 including p.p. C.O.D 5/- extra. For technical details ring Stan Bennett on 01-660 2896, or send 8d. in stamps to:

RADATEC, (Box 38), 45 GREEN LANE, PURLEY, SURREY

MAY 1970

INTERNATIONAL SHORT WAVE LEAGUE



Membership 35s. 0d. per annum (U.S.A. \$5.00) including 12 monthly issues of *Monitor* — the League journal. Including free use of all Services, QSL Bureau, etc.

THE LARGEST S.W.L. ORGANISATION IN THE WORLD

For full details write to:

The Secretary,

I.S.W.L.,

60 WHITE STREET, DERBY

FERGUSON RADIO CORPORATION LTD.

TROUBLE- SHOOTERS

Urgently required within a colour television receiver Production Department. Applicants should hold a City and Guilds Intermediate or Final Certificate in Radio and Television Servicing or alternatively have had considerable practical experience. Excellent working conditions and rates of pay.

Please apply, completing details below:
to:

Personnel Manager Ts/Rc Ferguson Radio Corporation Ltd.,
Great Cambridge Road, Enfield, Middx. 01-363 5353 Ext. 2320

NAME

ADDRESS

TEL. NO.

QUALIFICATIONS



CHASSIS and CASES by




H. L. SMITH & CO. LTD.
287/9 Edgware Road
London W2
TEL: 01-723 5891

BLANK CHASSIS

FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	6/3	2/11	10x8x2 1/2"	12/-	5/6
7x4x1 1/2"	6/-	3/2	12x7x2 1/2"	12/-	5/11
7x5x2"	7/6	3/5	12x9x2 1/2"	13/9	7/-
8x4x2"	7/-	3/4	13x8x2 1/2"	13/9	6/11
8 1/2x5 1/2"	8/-	3/9	14x7x3"	14/6	6/6
9x7x2"	9/3	4/10	14x10x2 1/2"	16/-	8/7
10x4x2 1/2"	9/-	3/9	15x10x2 1/2"	16/6	9/1
12x4x2 1/2"	10/-	4/3	17x10x3"	19/6	10/1
12x5x3"	12/-	4/9			

CASES		ALUMINIUM, SILVER HAMMERED FINISH		Type	N	Price
N	8x6x2"	18/-	W	12x7x7"	37/6	
N	6x6x3"	17/6	W	15x9x8"	48/6	
N	4x4x2"	11/-	Y	8x6x6"	29/-	
N	4x4x4"	11/-	Y	12x7x7"	45/-	
U	5 1/2x4 1/2x4 1/2"	17/-	Y	13x7x9"	50/6	
U	8x6x6"	23/-	Y	15x9x9"	53/6	
U	9 1/2x7 1/2x3 1/2"	24/-	Z	17x10x9"	72/6	
U	15x9x9"	49/-	Z	19x10x8 1/2"	78/-	
W	8x6x6"	23/-			*Height	

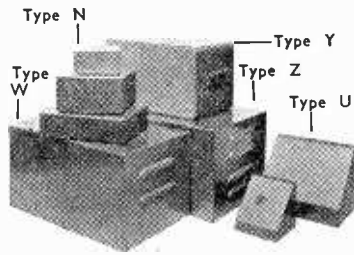

Type N has removable bottom, Type U removable bottom or back, Type W removable front, Type Y all screwed construction, Type Z removable back and front. Plus p. & p.

TO FIT OUR CASES

7x5 1/2x1 1/2"	7/-	3/9	12x6 1/2x2"	10/9	5/11
7x5 1/2x2"	7/9	3/9	14x8 1/2x2"	13/6	7/11
11x6 1/2x1 1/2"	10/-	5/6	15 1/2x9 1/2x2 1/2"	17/-	9/6
11x6 1/2x2"	10/-	5/6	17 1/2x9 1/2x2 1/2"	18/6	10/6

Plus post & packing

PANELS: Any size up to 3ft. at 6/- sq. ft. 16 s.w.g. (18 s.w.g. 5/3). Plus postage and packing.

YUKAN SO PROFESSIONAL THE SELF-SPRAY YUKAN AEROSOL WAY-
Get these air drying GREY HAMMER NOW! OR BLACK WRINKLE (CRACKLE) finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 16/11 carriage paid, per push-button self-spray can. All 16 Durable, heat and water resistant Black Matt Finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Polor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:
DEPT: N/3 YUKAN, 307a, EDGWARE ROAD, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations - We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

Other Yukan Air Drying Aerosols, 16 ozs. of 18/11 cart. pack includes:
Zinc Chromate Clear Lacquer
Metallics: Grey, Blue, Bronze and Gold.

Be well-equipped

You need not worry about the painful and lingering minor burns that occur from time to time in leisure pursuits if you keep BURNEZE close to hand. This unique new scientific aerosol cools and anaesthetizes. BURNEZE takes the heat out of a burn in just 8 seconds, then controls the blistering and pain that steal skill from nimble fingers. Be well-equipped - buy BURNEZE, from chemists.

Potter & Clarke Ltd Croydon CR9 3LP

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
124 pages. Price 8/6, postage 8d.
- DB6 THE RADIO AMATEUR OPERATOR'S HANDBOOK**
64 pages. Price 6/-, postage 6d.
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price 15/-, postage 1/-.
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price 37/6, postage 3/-.
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 10/6, postage 8d.

I enclose Postal Order/Cheque for..... in payment for

NAME.....

ADDRESS.....

(Please use Block Capitals for both name and address)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order

All publications are obtainable from your local bookseller

Data Publications Ltd., 57 Maida Vale, London W.9

Please mention **THE RADIO CONSTRUCTOR** when writing to advertisers

ABBREVIATIONS — A to L

The Table lists the more commonly employed abbreviations, from A to L inclusive, which are encountered in electronic work.

A	ampere	e.s.u.	electrostatic unit
a.c.	alternating current	eV	electron-volt
a.f.	audio frequency	F	farad
a.f.c.	automatic frequency control	f	frequency
ag.c.	automatic gain control	f.c.	frequency changer
Ah	ampere-hour	f.m.	frequency modulation
a.m.	amplitude modulation	f.s.d.	full-scale deflection (meter)
a.n.l.	automatic noise limiter	f.s.k.	frequency-shift keying
a.t.u.	aerial tuning unit	f.w.	full wave
a.v.	alternating voltage	gc	conversion conductance
b.f.o.	beat frequency oscillator	gm	mutual conductance
B.S.S. or B.S.	British Standard Specification	H	Henry
C	capacitor or capacitance	h.f.	high frequency
C.C.S.	continuous commercial service rating	h.t.	high tension
c.g.s.	centimetre-gramme-second system of units	h.w.	half wave
c.o.	crystal oscillator	Hz	Hertz (= 1 cycle per second)
c.r.o.	cathode ray oscilloscope	I	current
c.r.t.	cathode ray tube	i.c.w.	interrupted continuous wave
c/s	cycles per second (now superseded by Hz)	i.f.	intermediate frequency
c.w.	continuous wave	i.f.t.	intermediate frequency transformer
dB or db	decibel	i.s.b.	independent sideband
d.c.	direct current	J	Joule
d.c.c.	double cotton covered	K	Kelvin (absolute) temperature
d.p.d.t.	double pole, double throw	kHz	kilohertz (= 1,000 cycles per second)
d.p.s.t.	double pole, single throw	kV	kilovolt
d.r.c.	double rayon covered	kVA	kilovolt-ampere
d.s.b.	double sideband	kVh	kilovolt-hour
d.s.c.	double silk covered	kW	kilowatt
d.v.	direct voltage	kΩ	kilohm
e.c.o.	electron-coupled oscillator	L	inductor or inductance
e.h.f.	extremely high frequency	LC ratio	inductance/capacitance ratio
e.h.t.	extra high tension	l.f.	low frequency
e.m.f.	electromotive force	l.s.	loudspeaker
e.m.u.	electromagnetic unit	l.w.	long wave
e.r.p.	effective radiated power		

HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES


BUILD A QUALITY 4 TRACK TAPE RECORDER



To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This contains a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board. It takes everything for making a superb 4-track Recorder. You need no experience of technical skills to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises Deck, Amplifier, Cabinet and speaker with microphone. 3000 tape and spare spool. ASK FOR BROCHURE No. 22. TODAY'S VALUE £60. PRICE 39 gns. p.p. 22/6. NOTHING ELSE TO BUY.

SCOOP! STAAR RECORD PLAYER

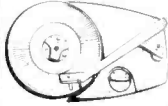Deck plays 33, 45, 78 R.P.M. records 9 volt operated, with mono cartridge. BRAND NEW as illustrated.



PRICE 59/6
p.p. 3/6
Send for leaflet
No. 7




MULLARD 1 WATT AMPLIFIER

Portable Transistor Unit ideal for Intercoms, Baby Alarms, Tele phone, Record Players or Suitcase Practice. 3 volt 50 transistor with volume control, output 3 ohms. Ideal for use with STAAR RECORD DECK.

PRICE 45/- p.p. 2/6.

OTHER ITEMS Suitable 7 x 4 inch 3 ohm speaker 12, 9 and 1 1/2. Revers covered capacitor 12 x 9 - 4 12.6 and 2.6 P.P. 9 volt battery 3.9. Write for leaflet No. 2.

GARRARD RECORD DECKS

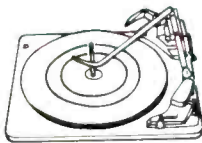

All the latest models BRAND NEW and guaranteed - TERRIFIC SAVINGS!
Model 50 - 9TANC dia £ 8.10.0
3000 STEREO - 9TANC diam. £ 9.15.0
SP 25 Mc 11. £ 11. 9.8
A70 M 11. £ 12.10.0
SL 65B £ 14.9.8
AP 75 £ 17.15.0
401 £ 28. 0.0
TSL 72B £ 25. 0.0
TSL 75B £ 31. 0.0
TSL 95B £ 39. 0.0
GL 75 GOLDRING £ 33. 0.0
GL 75 P GOLDRING £ 48. 0.0
ALSO IN STOCK - THORENS - LENC0 - B S R Carriage/Insurance 7/6 extra on any model.
BASES/COVERS p.p. 5/- £ 4.15.0
DELUXE p.p. 7/- £ 8.10.0
TOELUXE p.p. 7/- £ 8.10.0
Special prices with choice of cartridge.
SEND FOR 10-PAGE BROCHURE 16/17 TODAY.

BUILD YOURSELF A QUALITY RADIO



New printed circuit design with full power output. Fully tuneable on both mw/lw bands. 7 Mullard transistors, Fitted 5 speaker, Room Filling Power. Easy to build with terrific results. All local and continental stations. Complete detailed instructions.
TOTAL COST £6.19.6 p.p. 4/6
Ask for Leaflet No. 1

TRANSISTORS DIODES RECTIFIERS

WE HAVE THE MOST COMPREHENSIVE STOCK IN GREAT BRITAIN. NEW LIST OF 1000 TYPES. SEND FOR FREE COPY TODAY (LIST 36). FREE 18-PAGE TEST EQUIPMENT CATALOGUE - LOW COST UNITS FOR EVERY PURPOSE (Ref. No. 33).

HENRY'S RADIO Fully Illustrated CATALOGUES

ALL TYPES OF ELECTRONIC COMPONENTS TEST EQUIPMENT KITS BUILT UNITS



B HIGH FIDELITY & GENERAL AUDIO EQUIPMENT CATALOGUE

A The new 350 page fully detailed and illustrated with more than 6,000 stock items. Everything for amateur and professional use. Complete with 5 vouchers 10/- value, for use with purchases. 6th impression now available. ORDER AS CATALOGUE A. PRICE 7/6. p.p. 2/- B New audio and high fidelity catalogue. 120 pages containing ideas and equipment for every application. Special low prices for all leading makes. Plus 12/6 extra discount voucher. ORDER AS CATALOGUE B. PRICE 5/- p.p. 1/-

WHY NOT SEND AWAY TODAY!


AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dynalite Mk. III. Each unit or system will compare favourably with other professional equipment selling at much higher prices.

£11.12.6 to £38.17.6 (all units available separately).

THE FINEST VALUE IN LOW COST HIGH FIDELITY - CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS

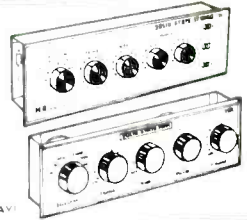SEND FOR BROCHURES No. 17, 14 and 21 TODAY!



HI-FI equipment to suit EVERY POCKET



FREE 10-PAGE STOCK/SYSTEMS LISTS (Nos. 16, 17)

VISIT OUR NEW HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS - IT'S TO PAY US A VISIT. AUDIO SYSTEMS £40 - £300 TO SUIT EVERY POCKET. DEFERRED TERMS AVAILABLE. SEND FOR ILLUSTRATED BROCHURE 16/17. TWO DEMONSTRATION ROOMS

HENELEC 5-5 STEREO AMPLIFIER

ASK FOR BROCHURE 13

PRICE £13.10.0 p.p. 7/6. (Leaflet on request)

Complete Stereo System 5-5. Garrard 2025 IC or 3000 CM with 9TANC Diameter Ceramic Cartridge. 5-5 Amplifier. Plinth/Cover. Two 10 watt speakers with tweeters in polished cabinets.

Usual price £50.0.0. OUR PRICE £39.10.0 p.p. 20/-



SINCLAIR STEREO 60

Z30 75/- P25 79/6 Stereo 60 £8.10.0

SPECIAL OFFER - Two Z30 P25 Stereo 60 (RRP £23.18.0) PRICE £18

BP10103 Watt IC Amp. £15.0
MC 1304 Stereo IC £15.0
TAD 100 Am Tuner £2.7.6
MC 1303 Stereo Pre-amp IC £12.18

All post paid, delivery from stock.

OTHER TYPES OF INTEGRATED CIRCUITS

RCA CA3014 29/6
RCA CA3018 22/6
RCA CA3020 29/6
RCA CA3026 18/6
Sinclair I.C. 10 59/6
G.E. PA230 22/6
G.E. PA234 20/0
G.E. PA237 37/6


G.E. PA246 52/6
SI 403 Plessey 49/6
S.G.S. UL910 10/0
S.G.S. UL900 10/0
S.G.S. UL914 11/0
Mullard TAA263 15/0

*Data sheets 3 to get for these for others see catalogue.

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 VOLT BANDWIDTH PRINTED CIRCUIT HIGH FIDELITY REPRODUCTION MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it. VHF FM gives the REAL sound.

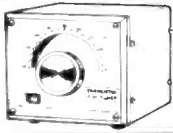PARTS TOTAL COST £6.19.6. DECODER £5.19.6. ASK FOR LEAFLET No. 3 (FOR STEREO)



ELECTRONIC ORGANS

COMPLETE KITS FOR THE HOME CONSTRUCTOR

Start building for as little as £10

START FEATURES
ALL TRANSISTOR PRINTED CIRCUIT DESIGNS
"BRITISH DESIGN" STEP BY STEP DETAILED INSTRUCTIONS "GAVE" UP TO 50% ON COMMERCIAL EQUIVALENT. EVERYTHING SUPPLIED DOWN TO THE LAST ITEM. FULL AFTER SALES SERVICE & ADVICE. "CREDIT SALE" W.H.P. TERMS AVAILABLE.

MODELS FROM £9.9 1350

We are pleased to offer the choice of FOUR British designs from a single manual portable at £99 THE MAYFAIR for light or classical music to a two manual five octave deluxe model with OAK CONSOLE from £285 for the serious musician.



These kits are the result of years of research and design and offer the best that is essential to good organ designs, coupled with excellent value. A true real high most powers. No technical skill or knowledge is required in construction, with the aid of the STEP BY STEP illustrated manuals with complete instructions that will be a delight to own and use and will give years of trouble free entertainment for the future family.

SEND FOR ILLUSTRATED BROCHURES 9/10/11 TODAY! When in LONDON CALL IN SEE HEAR PLAY FOR YOURSELF

ILLUSTRATION OF CHRISTENSON ELECTRONIC ORGAN

We are able to supply all items for this value - details on request

Built models available from £124

HENRY'S RADIO LTD.

Mail Order Dept., Components, Organ Dept.
303 EDGWARE ROAD, LONDON W.2.
Telephone: 01-723 1008/9

High Fidelity and Equipment Centre
309 EDGWARE ROAD, LONDON W.2.
Telephone: 01-723 6963

OPEN MON-SAT 9am-6pm THURS 9am-1pm