

RADIO & ELECTRONICS CONSTRUCTOR

MAY 1975

30p



**Mains
table
radio**

VOLTAGE
CONTROLLED
OSCILLATOR



**ALSO
FEATURED**

**THE 'SLIDE RULE' RECEIVER CUM
CAPACITANCE METER - Part 1**



1 Household contents and personal possessions up to £600.



2 All Risks cover on personal belongings up to £60.



3 Personal accident insurance (road, rail and sea risks) - £3 per week



4 Loss of cash up to £20



5 Household removal cover up to £600.




6 All Risks cover on sports equipment up to £30.



7 Personal liability cover for the family up to £20,000.



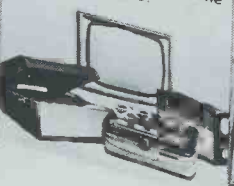8 Cover on Radio, Television etc., for damage in the home up to £60.



9 Holiday deposits cover up to £20.



Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine!

You can build up to the cover you need by additional units (or 1/2 units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances. And remember - as you buy more possessions just add more Home Units at any time. *Quote Ref. 20/9468*

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue, Southend-on-Sea, Essex, SS2 6BT

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

.....

.....

It pays to be protected by a **General Accident** company

20/9468



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm £7.75
 Baker Group 35, 3, 8 or 15 ohm £8.50
 Baker Group 50/12, 8 or 15 ohm £12.50
 Baker Deluxe 12", 8 or 15 ohm £10.75
 Baker Major 3, 8 or 15 ohm £8.50
 Baker Superb 8 or 15 ohm £14.50
 Baker Regent 8 or 15 ohm £7.75
 Baker Auditorium 12" £12.50
 Celestion PST8 (for Unilex) £3.25
 Celestion G12H 8 or 15 ohm £15.00
 Celestion G12M 8 or 15 ohm £12.00
 Celestion G15C 8 or 15 ohm £24.00
 Celestion G18C 8 or 15 ohm £33.00
 Celestion MH1000 8 or 15 ohm £10.95
 Coral 6 1/2" d/cone roll/surr. 8 ohm £2.50
 Coral 6 1/2" (larger magnet) 8 ohm £3.15
 Coral 8" d/cone, roll/surr. 8 ohm £3.25
 EMI 13 x 8, 3, 8 or 15 ohm £2.25
 EMI 13 x 8, d/cone 3, 8 or 15 ohm £2.50
 EMI 13 x 8 t/w, 8 ohm £3.75
 EMI 13 x 8 type 350, 8 or 15 ohm £8.25
 EMI 10 x 6 20 watt bass £6.60
 EMI 5" 14A/730 mid-range 8 ohm £3.00
 EMI 6 1/2" 93850 4 or 8 ohm £3.00
 EMI 8 x 5, cer. mag. 8 ohm £1.65
 EMI 8 x 5, 10 watt, d/c roll/s 8 ohm £2.50
 EMI 10 x 6 93870 8 ohm £2.25
 EMI 2 1/2" tweeter 8 ohm .65
 Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm £2.80
 Elac 6 1/2" d/cone, roll surr. 8 ohm £3.50
 Elac 6 1/2" d/cone 8 ohm £2.65
 Elac TW4 4" tweeter £1.50
 Elac 10" 10RM239 d/c 8 ohm £2.65
 Elac 8" 3 ohm £2.50
 Eagle Crossover 3, 8 or 16 ohm £1.50
 Eagle CT5 cone tweeter 8 ohm £1.75
 Eagle CT10 tweeter 8 or 16 ohm £2.55
 Eagle DT33 dome tweeter 8 ohm £5.45
 Eagle FF5 3 way crossover £3.15
 Eagle SN75 crossover with tw. control £4.00
 Eagle FF28 multicell, horn £7.75
 Eagle HT15 horn tw. 16 ohm £3.80
 Eagle HT21 horn tw. 8 ohm £5.88
 Eagle MHT10 horn tw. 8 ohm £3.80
 Eagle FR4 4" full range £5.30
 Eagle FR65 6 1/2" full range £8.35
 Eagle FR8 8" full range £10.65
 Fane Pop 15 watt 12" £5.25
 Fane Pop 25T 30 watt 12" £7.25
 Fane Pop 50 watt 12" £12.00
 Fane Pop 55 12" 60 watt £12.50
 Fane Pop 60 watt 15" £13.25
 Fane Pop 7 watt £15.95

SPEAKERS

Fane Pop 100 watt 18" £24.50
 Fane Crescendo 12A 8 or 15 ohm £29.00
 Fane Crescendo 12B 8 or 15 ohm £30.00
 Fane Crescendo 15, 8 or 15 ohm £36.00
 Fane Crescendo 18, 8 or 15 ohm £51.95
 Fane 701 twin ribbon horn £35.00
 Fane 910 horn £12.75
 Fane 920 horn £33.00
 Fane 152/12a 15" 15 ohm £16.00
 Fane 801T 8" d/cone roll surr. £7.00
 Fane 805T 8" d/cone roll surr. £3.50
 Fane 808T 8" d/cone £2.95
 Fane 807T 8" d/cone roll surr. £3.85
 Goodmans 8P 8 or 15 ohm £5.50
 Goodmans 10P 8 or 15 ohm £5.80
 Goodmans 12P 8 or 15 ohm £13.95
 Goodmans 12P-D 8 or 15 ohm £16.95
 Goodmans 12P-G 8 or 15 ohm £15.95
 Goodmans 12AX 100 watt 8 or 15 ohm £36.50
 Goodmans 15AX 100 watt 8 or 15 ohm £40.25
 Goodmans 15P 8 or 15 ohm £21.00
 Goodmans 18P 8 or 15 ohm £36.00
 Goodmans Midax 750 £16.00
 Goodmans Axent 100 tweeter & crossover £7.25
 Goodmans Audiom 100, 8 or 15 ohm £12.00
 Goodmans Axiom 401, 8 or 15 ohm £17.25
 Goodmans Twinaxiom 8" 8 or 15 ohm £8.75
 Goodmans Twinaxiom 10" 8 or 15 ohm £9.25
 Gauss 12" full range 8 ohm £69.50
 Gauss 12" Bass 8 ohm £69.50
 Gauss 15" full range 8 ohm £75.00
 Gauss 15" Bass 8 ohm £75.00
 Gauss 18" full range 8 ohm £80.00
 Gauss 18" Bass 8 ohm £80.00
 All the above Gauss (American) speakers are fitted with 4 1/2" voice coils and can handle 200 watts RMS.
 Kef T27 £5.25
 Kef T15 £6.00
 Kef B110 £7.25
 Kef B200 £8.25
 Kef B139 £14.25
 Kef DN8 £2.00
 Kef DN12 £4.95
 Kef DN13 £3.30
 Richard Allan 12" d/cone 3 or 15 ohm £2.75
 Richard Allan CG8T 8" d/c roll surr. 8 ohm £6.35
 STC 4001G super tweeter £5.70
 2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm .65
 2 1/2" 75 ohm .50
 7" x 4" 3, 8 or 15 ohm £1.40
 8" x 5" 3, 8 or 15 ohm £1.50
 10" x 6" 3, 8 or 15 ohm £2.30

SPEAKER KITS (Carr. 75p each. £1.50 pair)

Baker Major Module 3, 8 or 15 ohm each £10.95
 Goodmans Mezzo pair £40.75
 Goodmans DIN 20 4 ohm each £11.75
 Helme XLK25 pair £22.00
 Helme XLK30 pair £14.95
 Helme XLK50 pair £39.95
 Kefkit 1 pair £41.90
 Kefkit 3 each £36.75
 Peerless 3-15 (3 sp. system) each £15.00
 Peerless 20/2 each £14.95
 Peerless 30/2 each £20.95
 Peerless 20/3 each £22.95
 Peerless 50/4 each £34.95
 Richard Allan Twinkit each £8.95
 Richard Allan Triple 8 each £13.75
 Richard Allan Triple each £19.95
 Richard Allan Super Triple each £23.75
 Wharfedale Linton 2 kit pair £19.25
 Wharfedale Glendale 3 kit pair £34.50
 Wharfedale Dovedale 3 kit pair £52.50

COMPLETE RADFORD RANGE IN STOCK

PA/DISCO AMPLIFIERS (Carr. and ins. £1)

Baker Major 100 watt £49.75
 Linear 30/40 £30.00
 Linear 40/60 £35.00
 Linear 80/100 £58.95
 Linear 100 watt slave £44.00
 Eagle PRO A120, 120 watts RMS £129.00
 Eagle PRO A65, 65 watts RMS £98.50
 Eagle PRO A35, 35 watts RMS £77.00
 Eagle TPA40 mains/12v mobile £50.00
 Eagle HHS 36 watts mobile 12v. £37.50
 Eagle TPA20 paging amplifier £45.00
 Eagle RA859 Reverb (p. & p. 75p) £18.25
 Eagle RA856 Reverb (p. & p. 75p) £12.50

MICROPHONES (p. & p. 50p)

Shure 515 SB Low Impedance £14.95
 Shure 515 SA High Impedance £15.75
 Shure 545 Dual Impedance £29.95
 Shure 588 SB Low Impedance £19.95
 Shure 588 SA High Impedance £20.50

FREE with loudspeaker orders over £7 - "HiFi Loudspeaker Enclosures" book

All items guaranteed new and perfect
 Prompt despatch

Carriage: 38p per speaker, 12" and up 50p each, 25p per tweeter, crossover or 2 1/2" / 70mm speaker, kits 75p each (£1.50 pair)

ALL PRICES QUOTED INCLUDE VAT.

Send stamp for free booklet 'Choosing a speaker'
 Big discounts on Grundig, ITT, Koyo, etc.
 Send stamp for list

WILMSLOW AUDIO

DEPT RC

LOUDSPEAKERS: SWAN WORKS
 BANK SQUARE, WILMSLOW, CHESHIRE

AMPLIFIERS, RADIO ETC.

10 SWAN ST., WILMSLOW, CHESHIRE

The Ultimate Radio!


GRUNDIG SATELLIT 2000

You've got your yacht, private aircraft, Rolls Comiche? — then all you need for a full set of status symbols is this latest model Grundig Satellit, Germany's top radiol Radio performance, appearance and sound quality are all superb. VHF/FM, MW, LW 10 SW bands plus bandspread, 27 transistors and 22 diodes, Battery/Mains (110/240v.), 2 speakers, 57" telescopic aerial.

Our Price £129.50 inc. carr. & ins.

Big discounts on Grundig, ITT, Koyo, etc.
 Send stamp for list.

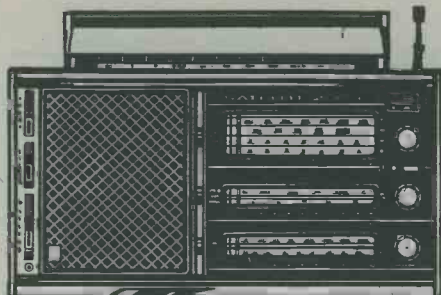WILMSLOW AUDIO, 10 SWAN STREET, WILMSLOW, CHESHIRE



- the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10 AL20 AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0.25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE --3dB	Po = 2 WATTS	50 Hz-25KHz
SENSITIVITY for RATED O/P	Vs = 25V. R1 = 8Ω f = 1KHz	75mV. RMS
DIMENSIONS	—	3" x 2 1/2" = 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. (RL = 8Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2.19
AL 20. 5 watts	£2.59
AL 30. 10 watts	£3.01

POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30)	95p
SPM 50. (Use with AL60)	£3.25
FRONT PANELS FP 12 with Knobs	£1.00

PRE-AMPLIFIERS

PA 12. (Use with AL10, AL20 & AL30)	£4.35
PA 100. (Use with AL60)	£13.15

TRANSFORMERS

T461 (Use with AL10)	£1.60 P. & P. 22p
T538 (Use with AL20, AL30)	£2.30 P. & P. 22p
BMT80 (Use with AL60)	£2.75 P. & P. 40p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with *Ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response—
20Hz-50KHz (—3dB)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
*Input 2. Impedance
30 K ohms
Sensitivity 4mV


Look for our

SEMICONDUCTOR ADVERTISEMENTS in
Practical Wireless Wireless World Practical Electronics

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch, volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz.

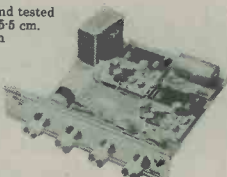

£14.45 p. & p. 45p

TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) Size 10 1/2" x 8 1/2" x 3", £3.95 plus 30p postage.

SPH80 STEREO HEADPHONES

4-16 ohms impedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume controls. £4.95


NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £4.25



- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 1KHz
- Supply voltage 15-50 volts

- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

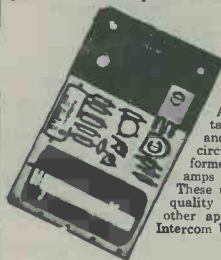Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.



STABILISED POWER MODULE SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available 10p PRICE £3.25

TRANSFORMER BMT80 £2.75 p. & p. 40p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATIONS

Frequency Response 20Hz—20KHz ± 1dB
Harmonic Distortion better than 0.1%
Inputs: 1. Tape Head
2. Radio, Tuner
3. Magnetic P.U.
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.
Base Control ± 15dB at 20Hz
Treble Control ± 15dB at 20KHz
Filters: Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than —65dB
Input overload + 28dB
Supply + 35 volts at 20mA
Dimensions 292mm x 82mm x 35mm

ONLY £14.25

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BTM80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £29.75 plus 45p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets, etc. Kit price: £29.95 plus 45p postage.

All prices quoted in new pence Cirlo No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 20p. Overseas add extra for airmail
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn - and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy - making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering - yet you learn faster than you ever dreamed possible. Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits - assemble components - build things - experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for **FREE** 76 page book - see how easy it is - read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**NOW AVAILABLE . . .
LATEST
BOUND VOLUME
No. 27
of
"Radio & Electronics
Constructor"**



AUGUST 1973 to JULY 1974

Comprising 772 pages **PRICE £2.40 P&P 50p** inc. index

**BOUND VOLUME No. 25
(August 1971 to July 1972)
BOUND VOLUME No. 26
(August 1972 to July 1973)**

PRICES
VOL. 25
£2.00 per volume. P&P 50p
VOL. 26
£2.10 per volume. P&P 50p

Limited number of these volumes still available.

We regret all earlier volumes are now completely sold out.

Available only from
DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

**POST
TODAY FOR
FREE BOOK**

To: ALDERMASTON COLLEGE
DEPT: CRE 05
READING RG7 4PF

CRE 05

Yes, I'd like to know more about your course. Please send me free details - plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS

POSTCODE



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

THE MODERN BOOK CO

WORLD RADIO TV HANDBOOK 1975

A Complete Directory of International Radio & TV

Price: £3.85

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR

by R. M. Marston PRICE £1.95

BASIC MATH COURSE FOR ELECTRONICS
by H. Jacobowitz PRICE £1.65

HANDBOOK OF IC CIRCUIT PROJECTS
by J. Ashe PRICE £1.65

THE AUDIO HANDBOOK
by G. J. King PRICE £5.30

UNDERSTANDING & USING THE
OSCILLOSCOPE by C. Hallmark PRICE £1.95

COLOUR TELEVISION SERVICING
by G. J. King PRICE £4.85

ESSENTIAL FORMULAE FOR ELECTRONIC &
ELECTRICAL ENGINEERS
by N. M. Morris PRICE £1.05

TOWERS' INTERNATIONAL TRANSISTOR
SELECTOR by T. D. Towers PRICE £3.30

WORKING WITH THE OSCILLOSCOPE
by A. C. W. Saunders PRICE £1.75

THE RADIO AMATEUR'S HANDBOOK 1975

by A.R.R.L. PRICE £3.70

HOW TO GET THE BEST OUT OF YOUR
TAPE RECORDER by P. J. Guy PRICE £1.70

BEGINNER'S GUIDE TO ELECTRONICS
by T. L. Squires PRICE £2.15

COLOUR T.V. WITH PARTICULAR
REFERENCE TO THE PAL SYSTEM
by G. N. Patchett PRICE £5.25

RADIO SERVICING POCKET BOOK
by V. Capel PRICE £2.20

STEREO F.M. RADIO HANDBOOK
by P. Harvey PRICE £2.75

110 SEMICONDUCTOR PROJECTS
FOR THE HOME CONSTRUCTOR
by R. M. Marston PRICE £1.35

FIRST STEPS IN TELEVISION
by B. Sexton PRICE £4.75

THE PRACTICAL AERIAL HANDBOOK
by G. J. King PRICE £3.05

ALL PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	28p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	28p
DTB9 Valve Type Coil Pack Application circuitry	..	28p
MD 1 Decoder Circuitry for Stereo Reception	..	28p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

NEW STYLE SELF-BINDER

for

"Radio & Electronics
Constructor"



The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE
£1.00


including V.A.T.
P. & P. 20p

Available only from:—

Data Publications Ltd. 57 Maida Vale London W9 ISN

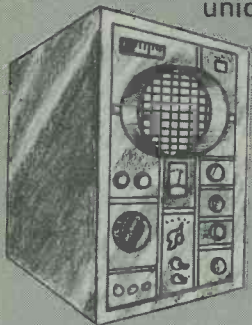1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

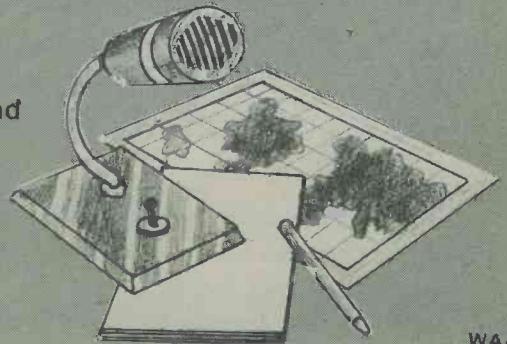2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept AX 575
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

If you're interested in electronics You'll like the NEW LITESOLD SUPER IRONS

We've been supplying the electronics industry with soldering irons for many years and we have now put all our experience into an iron for the electronics enthusiast.

The new LITESOLD SUPER IRONS have all the features you have been looking for; a neon indicator which glows only when the supply is connected correctly and the iron is safely earthed, an unbreakable nylon handle, a burn-proof mains lead, a special oxydised binding, a long life element. A range of bit shapes to suit every job and a special bench stand are also available.

There are three SUPER IRONS the \$90

12 watts for miniature jobs at £4.77

the \$142

20 watts for medium jobs at £4.85

the \$187

24 watts for heavy jobs at £4.89

and the special spring stand at £2.24.

If you want an economy iron, the Litesold Standard is the one for you.

Model 90 12 watts at £2.97

Model 142 20 watts at £3.02

Model 187 24 watts at £3.15

Get your LITESOLD SUPER IRON direct from

Light Soldering Developments Limited
97-99 Gloucester Road Croydon Surrey
Telephone 01-689 0574

All prices include postage, packing and VAT but not the diamond ring.



PRECISION

POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+-10%)	63V Range	+1%	+2%	+5%
0.1µF (1 1/2" x 1/2") 50p	0.47µF	56p	46p	36p
0.22µF (1 1/2" x 1/2") 59p	1.0µF	66p	56p	46p
0.25µF (1 1/2" x 1/2") 62p	2.2µF	80p	65p	55p
0.47µF (1 1/2" x 1/2") 71p	4.7µF	£1.30	£1.05	85p
0.5µF (1 1/2" x 1/2") 75p	6.8µF	£1.64	£1.29	£1.09
0.68µF (2" x 1/2") 80p	10.0µF	£2.00	£1.60	£1.40
1.0µF (2" x 1/2") 91p	15.0µF	£2.75	£2.15	£1.90
2.0µF (2" x 1") £1.22	22.0µF	£3.50	£2.70	£2.55

TANTALUM BEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 10p EACH; 10 for 95p; 50 for £4.00.

TRANSISTORS:

BC107/8/9 9p	BC183/183L 11p	BF194 12p	BFY51 20p
BC114 12p	BC184/184L 12p	BF196 13p	BFY52 20p
BC147/8/9 10p	BC212/212L 14p	BF197 13p	OC71 12p
BC153/7/8 12p	BC547 12p	AF178 30p	2N3055 50p
BC182/182L 11p	BC558A 12p	BFY50 20p	2N3702/4 11p

1N914 6p; 8 for 45p; 18 for 90p. 1N916 8p; 6 for 45p; 14 for 90p.
1S44 5p; 11 for 59p; 24 for £1.00. 1N4148 5p; 6 for 27p; 12 for 48p.

LOW PRICE ZENER DIODES: 400mW; Tol. +-5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 6 for 39p; 14 for 84p. SPECIAL: 100 Zeners for £5.50.

RESISTORS: High stability low noise carbon film 5%, 1/2 W at 40°C; 1/4 W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p for 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

SILICON PLASTIC RECTIFIERS - 1.5 Amp - Brand new wire ended DO27: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p).

BRIDGE RECTIFIERS: 2 1/2 Amp. 200V - 40p; 350V - 45p; 600V - 55p.

SUBMINIATURE VERTICAL PRESETS - 0.1W only: ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 250K, 680K, 1M, 2.5M, & 5M.

PLEASE ADD 8% V.A.T. TO ORDERS. PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5.00. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

MARCO TRADING

Dept. C5, The Old School, Edstaston, NR. WEM, Salop.
Tel: WHIXALL (Salop) 4645 (STD 094872) (Props: Minicost Trading Ltd.)

GUEST ELECTRONIC DISTRIBUTION LIMITED

Guest, normally supplying electronic components to industry, are making available packs of specially selected components for the home constructor. These components are of professional quality at hard to beat prices.

PACK 1 - CAPACITOR PACK

30 Miniature vertical mounting electrolytic capacitors 50 V working.

5 x 0.47µF	5 x 10µF	
5 x 1.0µF	3 x 22µF	£2.00 (one pack)
5 x 2.2µF	2 x 33µF	£3.50 (two packs)
5 x 3.3µF		

PACK 2 - RESISTOR PACK

Pack of 200 medium power (0.75 + 1W) resistors. Assorted values throughout E24 range 5%. £2.00 (one pack).

PACK 3 - POTENTIOMETER PACK

Pack of skeleton potentiometers linear 1/4 W.

4 x 250Ω	4 x 10KΩ	
4 x 500Ω	4 x 50KΩ	£2.50 (one pack)
4 x 1KΩ	4 x 100KΩ	
4 x 2.5KΩ	4 x 2.5MΩ	

PACK 4

A special pack designed for the constructor who is 'stocking up' generally and seeks excellent value.

Comprising: Selection of electrolytic capacitors (30 +)
Comprehensive selection of medium power resistor (5%) E24 series (100 +)
Selection of skeleton potentiometers (32 +)
Selection of lampholders (5 +) and lamps
Miniature 250V 2A toggle switches, 3 or 4 poles (2 +)
£5.50 (one pack)

All prices include VAT and Post and Packing. Please send cheque/P.O./Cash, clearly stating pack required and address to:

BRIAN WOODS (REF: M.D.) Marketing Services, Guest Distribution, Redlands, Coulsdon, Surrey, CR3 2HT.

COMPONENTS

HOBBYIST - PROFESSIONAL - DOMESTIC - SURPLUS - INDUSTRIAL
 JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - SEND STAMPED
 ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS.
 PAY US A VISIT. OVER 90% OF STOCK BELOW QUANTITY
 WHOLESALE PRICE. RETURN POSTAL SERVICE UNLESS CHEQUE.

Goods sent at customer's risk, unless sufficient payment for insurance included (2p per £1 Min 5p) U.K. only.

VALVE BASES	
Printed circuit B9A - B7G	4p
Chassis B7 - B9G - B7G	4p
Shrouded chassis B7G - B9A	6p
B8A - B9A chassis - B12A tube	6p

Speaker, 6" x 4", 5 ohm, ideal for car radio etc. £1

TAG STRIP - 6 way 3p		WRIST COMPASS	
9 way 5p	Single 1p	30p with Needle Lock	

1 1/2 glass fuses— 250 m/a or 3 amp (box of 12)	18p
3" tape spools	8p
Brand new Boxed 6K7G	25p
PVC or metal clip on M.E.S. bulb holder	5p
Gearred Knob, Inner to Outer Ratio 8:1	60p
Bulgin, 5mm Jack plug and switched socket (pair)	30p
12 volt solenoid and plunger	40p
250 RPM 50 c/s locked frequency miniature mains motor	50p
200 OHM coil, 2 1/4" long, hollow centre	10p
Belling Lee white plastic surface coax outlet Box	30p
R.S. 12 way standard plug and shell	30p

SWITCHES			
Pole	Way	Type	
4	2	Sub. Min. Slide	18p
6	2	Slide	20p
4	2	Lever Slide	15p
2	2	Slide	10p
1	3	+ off Sub. min. edge	10p
1	3	13 amp small rotary	12p
2	2	Locking with 2 to 3 keys	£1.50
2	1	2 Amp 250V A.C. rotary	16p
1	2	Toggle	10p
Wafer Rotary, all types			30p
S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting			30p

PIANOKEY SWITCH UNIT	
5 lever, interlocking 2 pole mains + 3 pole 2 way + 3 of 6 pole 2 way	15p

COMPUTER AND AUDIO BOARDS
 VARYING PANELS WITH ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.

3lb. for 85p + 60p post and packing
 7lb. for £1.75 + 75p post and packing

Skeleton Presets	Clear Plastic Boxes
Slider, horizontal or vertical standard or submin. 5p	For component storage or projects, sliding lid. 1 3/4" x 1 1/2" x 1" 10p

KNOBES
 SILVER METAL PUSH ON WITH POINTER, OR WHITE PLASTIC, GRUB SCREW WITH POINTER AND SILVER CENTRE 8p EACH.

ZM1162A INDICATOR TUBE
 0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £2.00

RESETTABLE COUNTER
 English Numbering Machines LTD.
 MODEL 4436-159-989
 6-14 volt. 6 digit, illuminated, fully enclosed. £2.50

TO3 Mica Washer	2p
18 volt 4 amp charger, bridge rectifier	50p
GC10/4B Cold Cathode	£3.00

Telescopic aerial
 Closed 9 1/2", open 38 1/2"
 Fitted right angle TV plug, 50p

1 1/8 - 1/4 - 1/2 watt	1p
1 watt	2p
Up to 5 watt wire wound	10p
10 watt wire wound	12p
15 watt	14p

RESISTORS
 Philips transformer, safety fused. In 200-220-240v. Out 240v 60ma + 6.3v 1a approx 2" x 2 1/2" x 2 1/2" £1.50

POTS	
Log or Lin carbon	12p
Switched	23p
Dual Pots	38p
Dual & switch	50p
Lin wirewound	25p
Slider Pot	26p
Dual Slider	45p

THERMISTORS	
VA1008, VA1034, VA1039, VA1040, VA1055, VA1066, VA1082, VA1100	7p
VA1077, VA1005, VA1026	10p
	15p

RELAYS	
12 volt S.P.C.O octal mercury wetted high speed	75p
P.O. 3000 type, 1,000 OHM coil, 4 pole c/o	60p
12 volt d.p.c.o. heavy duty octal	80p

ELECTROLYTICS MFD/VOLT. Many others in stock

Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD									
10	4p	5p	6p	8p	8p	12p	16p	20p	
25	4p	5p	6p	8p	8p	15p	18p	20p	
50	4p	5p	6p	9p	13p	18p	—	—	
100	5p	6p	10p	12p	19p	20p	—	—	
250	9p	10p	11p	17p	28p	—	—	—	
500	10p	11p	17p	24p	45p	—	—	—	
1000	13p	17p	40p	—	—	—	—	—	
2000	23p	37p	45p	—	—	—	—	—	

As total number of values are too numerous to list, use this price guide to work out cost of your actual value requirements, i.e. 2MFD, 30V would be 5p, or 330MFD, 50V would be 14p, etc. etc. 8/20, 10/20, 12/20 Tubular tantalum 15p each 16-32/275, 32-32/275, 100-100/150, 100-100/275 50-50/300 20p each 12,000/12, 32-32-50/300, 700/200, 100-100-100-150-150/320 50p each 20-20-20/350 40p each

INDICATORS	
Bulgin D676 red, takes M.E.S. bulb	20p
12 volt red, small pushfit	20p
Mains neon, red, pushfit	16 1/2p

CAPACITOR GUIDE - maximum 500V
 Up to .01 ceramic 2p. Up to .01 poly 3p. Up to 1000PF silver mica 5p. 1,200PF up to .01 silver mica 10p. .013 up to .25 poly etc. 4p. .27 up to .68 poly etc. 6p
 Over 500 volt order from above guide and few others listed below.
 6p. .1/600:10p. .01/1000, 1/350, 8/20, .1/900, .22/900, 4/16, .25/250 AC (600vDC) .1/1500 40p. 5/150, 9/275AC, 10/150, 15/150, 40/150.

TRIMMERS, 20p each	
100PF Ceramic, 30PF Beehive, 12PF PTFE 2500PF 750 volt, 33PF MIN. AIR SPACED 5PF, MIN. AIR SPACED, 50PF CERAMIC.	

CONNECTOR STRIP	
Belling Lee L1469, 4 way polythene.	3p each
Strong grey plastic box same design as die cast ali 4 3/8" x 2 3/8" x 1 1/4"	40p

1" or 1 3/8" or 3/4" CAN CLIPS 2p

MAINS DROPPERS	
36+79 ohm	20p
66+66+158 ohm, 66+66+137 ohm, 17+14+6 ohm, 266+14+193 ohm	25p
50+40+1k5 ohm	35p
285+575+148+35 ohm	
25+35+97+59+30 ohm	

5 1/2" x 2 3/4" Speaker, ex-equipment	3 ohm	30p
2 Amp Suppression Choke		5p
3 x 2 1/2 x 1 1/8" PAXOLINE		2p
4 3/8 x 1 1/2 x 1 1/8" } 2 for 1p		
220K & 100 ohm 3 watt resistors		4p
VALVE RETAINER CLIP, adjustable		2p

OUTPUT TRANSFORMERS	
Sub-miniature Transistor Type	25p
Valve type, centre tapped or straight	40p

3 pin din to open end, 1 1/2yd twin screened lead 35p
 Whiteley Stentorian 3 ohm constant impedance volume control way below trade at £1
 Drive Cord 1p per yd.

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11
 Open 9.30 a.m. till 8 p.m. Monday to Saturday Phone 01-223 5016
 also Sunday afternoons

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC107 .. 14p	BC178A/B .. 13p	BF178/9 .. 25p
AC127/ .. 11p	BC179B .. 14p	BF180/1/2/3 .. 22p
AC128/176 .. 8p	BC186/7 .. 20p	BF184/5 .. 15p
ACY28 .. 18p	BC213L .. 10p	BF194/5/6/7 .. 8p
AD149 .. 40p	BC327/8 .. 19p	BF194A .. 12p
AD161/2 matched pr. 69p	BC337/8 .. 14p	BF200 .. 20p
AF116/7 .. 12p	BC547/8 .. 11p	BF262/3 .. 23p
AF124/6/7 .. 20p	BC558A .. 11p	BF336 .. 25p
AF139/178 .. 30p	BCX20 .. 13p	BFS28 Dual Mosfet 92p
AF180/1 .. 30p	BCX32/36 .. 12p	BFW10/11 F.E.T. 45p
AF239 .. 20p	BCY40 .. 60p	BFX29/30 .. 16p
ASY27/73 .. 25p	BCY70/1/2 .. 9p	BFX84/88 .. 16p
BC107A or B .. 9p	BD112/3/5/6 .. 50p	BFY50/1/2 .. 11p
BC107/8/9 .. 7p	BD131 .. 24p	BFY90 .. 50p
BC108A/B/109B/C 10p	BD132 .. 30p	BR101 .. 30p
BC147/8/9 .. 7p	BD135 .. 28p	BRY39 } Programmable Unj Junction 34p
BC147A/B .. 8p	BD201/2/3/4 .. £1.00	BRY56 } 34p
BC148A/B, 9B/C/S 8p	BD232/4/5 .. 49p	BSV64 .. 40p
BC157/8/9 .. 9p	BDX77 .. £1.40	BSV79 F.E.T. £1
BC158A/B .. 11p	BF115 .. 15p	BSV80 F.E.T. 90p
BC159B/C, 157A 11p	BF167/173 .. 20p	BSV81 Mosfet 90p

BSX20 .. 13p	OTHER DIODES
BSX21 .. 16p	IN916 .. 6p
BU105/01 .. 93p	IN4148 .. 1 1/2p
CV7042 (OC41 OC44, ASY63) 7p	BA145 .. 14p
GET111 .. 40p	Centercel .. 10p
OC35 .. 32 1/2p	BZY61 .. 10p
ON222 .. 30p	BB110 B Varicap 20p
2N393/MA393 .. 30p	BA182 .. 24p
2N706 .. 8p	OA577/10 .. 10p
2N987 .. 35p	BZY88 Up to 33 volt 6p
2N2219 .. 18p	BX161 11 volt .. 15p
2N2401 (ASY26-27) 20p	BR100 Diac. .. 19p
2N2904/5/6/7 .. 13p	INTEGRATED CIRCUITS
2N2907A .. 15p	741 8 pin d.i.l. 25p
2N3053 .. 13p	TAD100 AMRF £1.00
2N3054 .. 35p	TAA570 £1.20
2N3055 (or equiv.) 33p	CA3001 R. F. Amp £1.00
2N3819 FET .. 16p	TAA300 1wt Amp £1.25
2N5036 .. 60p	NE555v Timer 48p
TIS88A FET .. 33p	TAA550 Y or G 41p
ZTX 300 .. 13p	TAA263 Amp 65p
40250 .. 60p	SN7483 TTL 82p

BRIDGE RECTIFIERS

Amp	Volt			
1/2	1,600	BYX10	30p	
1	140	OSH01-200	30p	
1.4	42	BY164	35p	

TRIACS

Amp	Volt		
6	400	Plastic	74p
25	900	BTX94-900	£5.00
25	1200	BTX94-1200	£7.00

RECTIFIERS

Amp	Volt		
IN4004	1	400	5p
IN4005	1	600	6p
IN4006	1	800	7p
IN4007	1	1,000	7p
SR100	1.5	100	7p
SR400	1.5	400	8p
REC53A	1.5	1,250	14p
LT102	2	30	10p
BYX38-600	2.5	600	40p
BYX38-300R	2.5	300	36p
BYX38-900	2.5	900	45p
BYX38-1200	2.5	1,200	50p
BYX49-600	2.5	600	34p
BYX49-300	2.5	300	26p
BYX49-900	2.5	900	40p
BYX49-1200	2.5	1,200	52p
BYX48-300	6	300	40p
BYX48-600	6	600	50p
BYX48-900	6	900	60p
BYX48-1200	6	1,200	80p
BYX72-150R	10	150	35p
BYX72-300R	10	300	45p
BYX72-500R	10	500	55p
BYX42-300	10	300	30p
BYX42-600	10	600	65p
BYX42-900	10	900	80p
BYX42-1200	10	1,200	95p
BYX46-300*	15	300	£2.00
BYX46-400*	15	400	£2.50
BYX46-500*	15	500	£2.75
BYX46-600*	15	600	£3.00
BYX20-200	25	200	60p
BYX52-300	40	300	£1.75
BYX52-1200	40	1,200	£2.50

OPTO ELECTRONICS

ORP12	44p	Photo transistor
BPX40	65p	BPX29 £1.00
BPX42	£1.50	OCPT7 35p
BPY10	£1.00	BIG L.E.D. 0.2" 16p
(VOLT/AC)		RED 15p
BPY68	} £1.00	ORANGE 16p
BPY69		GREEN 16p
BPY77		YELLOW 16p
Diodes		

PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp £1.00

.3" red 7 segment L.E.D. 14 D.I.L. 0-9 + D.P. display 1.9v, 10m/a segment 83p

CQY11B L.E.D. Infra red transmitter £1 One fifth of trade

Wire ended glass neons 5p

Plastic, Transistor or Diode Holder 1p
Transistor or Diode Pad 1p
Holders or pads 50p per 100

Philips Iron Thermostat 15p
Bulgin 2-pin flat plug and socket 10p
McMurdo PP108 8-way edge plug 10p

TO3 HEATSINK

Europlec HP1 TO3B individual 'curly' power transistor type. Ready drilled 20p

Tested unmarked, or marked ample lead ex new equipment

ACY17-20	8p	OC71/2	5p
ASZ20	8p	OC200-5	10p
ASZ21	15p	TIC44	24p
BC186	11p	2G240	2-50
BCY30-34	10p	2G302	6p
BCY70/1/2	8p	2G401	10p
BF115	10p	2N711	25p
BY127	8p	2N2926	7p
BZY88 series	5p	2N598/9	6p
HG1005	2p	2N1091	8p
HG5009	2p	2N1302	8p
HG5079	2p	2N1907	2-50
L78/9	2p	Germ. diode 1p	
M3	10p	GET120 (AC128 in 1" sq. heatsink)	
OA81	3p		
OA47	2p		
OA200-2	3p		
OC23	20p	GET872	12p

THYRISTORS

Amp	Volt		
1	240	BTX18-200	50p
1	400	BTX18-300	65p
1	240	BTX30-200	40p
6.5	500	BT102-500R	75p
10	700	BT106	85p
15	500	BT107	£1.00
6.5	500	BT101-500R	90p
6.5	500	BT109-500R	90p
20	600	BTW92-600RM	£3.00
15	800	BTX95-800R Pulse Modulated	£10.00
30	1000	2BT10 (Less Nut)	£4.00

PAPER BLOCK CONDENSER

0.25MFD	800 volt	30p
1MFD	250 volt	15p
2MFD	250 volt	20p
10MFD	500 volt	80p
4MFD	250 volt	20p
15MFD	150 volt	50p

METAL CHASSIS SOCKETS

Car Aerial .. }
Coax .. }
5 or 6 pin 240° din } 6p
Speaker din switched }
3.5mm Switched Socket }

8 way Cinch standard 0.15 pitch edge socket 20p

U.E.C.L. 10 way pin connector 2B6000 OA1P10 10p

U.E.C.L. 20 way pin connector 2A60000A1P20 20p

U.E.C.L. 10 way pin socket 2B606001R10 10p

U.E.C.L. 20 way pin socket B260800A1R20 20p

BELLING LEE L1354 TV Aerial diplexer 10p

Philips electronic engineer kits add on series E1004 £1.00 each (parts worth more)

SOLDER

Multicore - 2 1/2p foot ENAM. COPPER WIRE SWG. PER YD. 18 3p 20-24 2p 26-42 1p

GARRARD

GCS23T Crystal Stereo Cartridge £1.00

HANDLES

Rigid light blue nylon 6 1/2" with secret fitting screws 5p

Rotor with neon indicator, as used in Seafarer, Pacific, Fairway depth finders 20p each

Miniature Axial Lead Ferrite Choke formers 2p

DEE PLUG

McMurdo DA15P 15 way chassis plug 15p
Fairway 18009 Coax. socket 3p

TIE CLIPS

Nylon self locking 7" or 3 1/2" 2p

CINCH 150

12 way edge socket 10p
1lb Mixed nuts, bolts, washers etc. 35p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE
LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.
TOTAL GOODS PLUS CARRIAGE, ADD V.A.T.

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11
Open 9.30 a.m. till 8 p.m. Monday to Saturday also Sunday afternoons
Phone 01-223 5016

**Essential
for the
Short Wave
Enthusiast**

THE RADIO AMATEUR OPERATOR'S HANDBOOK

13TH EDITION

MAKE SURE OF YOUR COPY

NOW!

88 PAGES ONLY 70p

P. & P. 10p



- ★ AMATEUR PREFIXES
 - ★ AMATEUR CODES
 - ★ LOCAL TIME CONVERSIONS
 - ★ 8 MAPS
 - ★ FREQUENCY/WAVELENGTH CONVERSION TABLES
 - ★ POST OFFICE REGULATIONS
- MANY OTHER ESSENTIAL ITEMS

SIMPLE SHORT-WAVE RECEIVERS



If you are interested in the hobby of receiver construction and short wave listening this is the book for you. It covers the whole field of s.w.l'ing from construction to operating – both Broadcast and Amateur bands. It explains how the circuits work, how to assemble the parts, how to wire-up the circuits with point-to-point wiring diagrams, step-by-step instructions and how to test and operate the completed projects.

by F. A. Baldwin

- ★ FOUR DESIGNS - 1, 2 and 3 Valves
 - ★ INTRODUCTION TO SHORT WAVE LISTENING - 14 Comprehensive Sections
 - ★ WORKSHOP PRACTICE
 - ★ SOLDERING NOTES
 - ★ RECEIVER AND BENCH POWER SUPPLIES
- etc. etc.

140 Pages **80p** P. & P. 12p

TO DATA PUBLICATIONS LTD 57 Maida Vale London W9 1SN

Please supply copy(ies) of "Radio Amateur Operators Handbook", Data Book No. 6
 Please supply copy(ies) of "Simple Short Wave Receivers", Data Book No. 19
 (Please tick which book is required)

I enclose cheque/crossed postal order for

NAME

ADDRESS

BLOCK LETTERS PLEASE

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 7p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

TRANSISTOR PACKS ALL 50p each TESTED AND GUARANTEED

- | | | | | | |
|-----|-----|---|-----|---|---|
| B79 | 4 | IN4007 Sil. Rec. diodes. 1,000PIV 1 amp. plastic | H39 | 6 | Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945 |
| B81 | 10 | Reed Switches, 1" long 1/8" dia. High-speed P.O. type | H41 | 2 | BD131/BD132 Complementary Plastic Transistors |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked | H65 | 4 | 40361 Type NPN Sil. Transistors TO-5 can comp. to H66 |
| H38 | 30 | Short lead Transistors, NPN Silicon Planar types | H66 | 4 | 40362. Type PNP Sil. Transistors TO-5 can comp. to H65 |

UNMARKED & UNTESTED

- | | | | | | |
|-----|-----|--|-----|----|--|
| B1 | 50 | Germanium Transistors PNP, AF and RF | H20 | 20 | BY126/77 Type Silicon Rectifiers 1 amp. plastic. Mixed volts |
| B66 | 150 | Germanium Diodes | H34 | 15 | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can |
| B84 | 100 | Min. glass type Silicon Diodes DO-7 glass equiv. to OA200, OA202 | H67 | 10 | 3819N Channel FET's plastic case type |
| B86 | 100 | Dil. Diodes sub. min. IN914 and IN916 types | | | |

SILICON POWER TRANSISTORS—

40 WATT	Gain	VCE		PLASTIC Price
40N1	15	15	NPN	20p
40N2	40	40	NPN	30p
40P1	15	15	PNP	20p
40P2	40	40	PNP	30p
90 WATT				
90N1	15	15	NPN	25p
90N2	40	40	NPN	35p
90P1	15	15	PNP	25p
90P2	40	40	PNP	35p

NEW X-HATCH GENERATOR Mk.2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U.2 type batteries (extra).

P & P add 30p Complete kit £7.93 Ready built unit only £9.93

OVER 1,000,000 TRANSISTORS IN STOCK!

CAPACITOR DISCHARGE IGNITION UNITS

Transistorised. Simple to Fit. Improves performance, cuts fuel costs

P & P add 25p £7.50

MNFRS. AM/FM CHASSIS

To clear. NO instructions or tuning drives, useful for experimenters. Not too difficult to get working. Make good portables

EACH £1

SUNDRY

Metrication Pocket Charts 12p. 8 assorted relays £1.00. Rev. counter device (for cars) £1.00. U.H.F./TV Tuner Units, 625 lines, Rotary Tuning £2.50. L.M.380 Audio I.C. £1.00 and technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do NOT include V.A.T. Please add V.A.T. at current rate to total value of your order including postage. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 20p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

challenging values!



Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.

AMPLIFIER MODULES

- Pre-amplifiers: tone control**
- SS.100 Active tone control unit to provide bass, treble, balance and volume controls £1.60
 - SS.101 Pre-amp for ceramic cartridge, tape and radio £1.60
 - SS.102 Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction ...1dB at 1K £2.25

POWER AMPLIFIERS

- SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6 to 22. Size 3 1/2" x 2" £1.75
- SS.103-3 Stereo version of above using one I.C. on each channel £3.25
- SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2 1/2" x 1 1/2" £1.95
- SS.110 Similar in size to SS.105 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26 to 32V. £2.40
- SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0-15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms £3.60

THE MODULES TO BUILD A STEREO F.M. TUNER

- SS.201 Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6V—16V £6.25
- SS.202 I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4-5 to 14V. £5.25
- SS.203 Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c. £5.62

POWER SUPPLY STABILIZER


- SS.300 Add this to an unregulated supply (say typically 45V. output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving and very reliable. Ideal for workbench use. £3.25

MAINS TRANSFORMERS FOR ABOVE


- Add 35p P. & P. per transformer
- Type A 18v/1A (Suit SS. 103) £1.50
 - Type B 25v/2A (Suit SS. 110) £2.00
 - Type C 30v/2A (Suit SS. 140) £3.25
- Bridge Rectifier Type A 27p Type B/C 38p

STIRLING SOUND DISCO MINOR

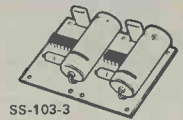
Fully transportable. Console fitted twin turntables with cross fade, monitoring, L-R cueing, mic. with over ride. Ampower 40 loudspeaker has built-in mains powered 40 watt RMS power amp. Up to 10 Ampower may be added. With one Ampower and console £100 plus V.A.T. at current rate. Carr. U.K. £3.50




SS-103-3

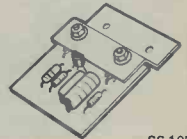


SS.105

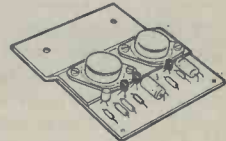


SS.140

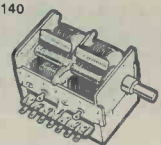

SS.201

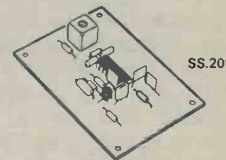

SS.202

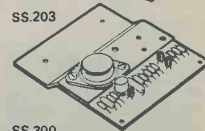

SS.300

BI-PRE-PAK LTD

Co. Reg. No. B207919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHD (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose inc. V.A.T.

Name

Address

REC 5




For Prices see Supplement

HOME RADIO (COMPONENTS) LTD.

CONSTRUCTIONAL KITS—Continued

KT4B. Radiokit No. 4B. A unique one valve model with world-wide range. Continuous coverage from approx. 10 metres to 47 metres, this covers the usual long-distance broadcasts. Band spread tuning. This set which was designed by us, uses only the finest components. Jackson and Wavemaster capacitors, Wearie P Coils and Mazda valves. Great fun both to build and to use. Under favourable atmospheric conditions you will be able to hear such far off places as Moscow, Australia and America.

KT4B

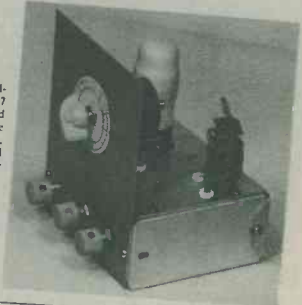

Recently I've been telling you just why I've been a customer of Home Radio Components for so long. I've given special emphasis to their superb catalogue, and now it's time to show you a typical page. The problem is . . . which one? There are 240 to choose from — for example, 17 pages of capacitors, 6 of resistors, 10 of switches and 8 of stylis. These are run-of-the-mill things, but here's a page that's specially interesting . . . page 91, showing a Short Wave Kit and an Etching Kit.

The managing director of Home Radio Components tells me there's quite a story behind these items. Briefly, Home Radio Components always listed a SW Kit, but eventually the firm making them ceased trading so H.R.C. decided to produce their own. When they looked around for an Etching Kit they were unable to find any at a sensible price, so again they said "Right, we'll make our own!" Sounds simple, but the managing director told me that if you produce any kit within 12 months of deciding to go ahead you're doing very well. "As for the problems of producing an Etching Kit," he said, "I could write a book about it!" Incidentally, if you want to order either of these kits the prices are:

AN ETCHING KIT

KT 253. Etching Kit. An ideal kit for the Constructor wishing to Etch his own Circuits. All essentials and detailed Instructions included in every Kit.



KT253

Contents:—

- (1) Plastic Dish.
- (2) Suitable pieces of copper clad board.
- (3) Laminator cutter.
- (4) Ferric Chloride.
- (4A) Large Plastic Spoon.
- (5) Deco-etch resist pen (An alternative may be supplied if this is not available. If at any time items are not available the kit will be supplied minus these articles and the price adjusted accordingly.)
- (6) Instructions (4 Pages).

94

ETCHING MATERIALS LISTED ON PAGE 95

KT4B, S.W. Kit, £4.75 plus VAT, plus 35p for p & p.
 KT253 Etching Kit, £3.75 plus VAT, plus 35p for p & p.

In any case, you'll surely want to study all the other pages in this famous catalogue. There are getting on for 2,000 illustrations by the way. Simply send the coupon below, with cheque or PO for 98p (65p plus 33p for post, packing and insurance). The catalogue contains 14 vouchers, each worth 5p when used as directed, so you can soon recover 70 pence of your investment. You just can't go wrong!



65p.
plus 33p POST AND PACKING

Send off the coupon today.

The price of 98p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. RC
 234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No.
 912966, London

RADIO & ELECTRONICS CONSTRUCTOR

MAY 1975

Volume 28 No. 10

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

© Data Publications Ltd., 1975. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £4.00 (U.S.A. and Canada \$10.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

CONTENTS

VOLTAGE CONTROLLED OSCILLATOR by A. Foord	590
CAN ANYONE HELP?	595
NEWS AND COMMENT	597
SEQUENTIAL LAMP CIRCUIT (Suggested Circuit 294) by G. A. French	598
CATALOGUE	602
RECENT PUBLICATIONS	603
FOUR CHANNEL SYNTHESISER – Part 2 by R. A. Penfold	604
ELECTRONIC EGG TIMER by R. J. Caborn	605
MAINS TABLE RADIO by A. P. Roberts	608
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	614
VERSATILE VERTICAL FOR TOP BAND by V. S. Evans	616
THE 'SLIDE RULE' RECEIVER CUM CAPACITANCE METER – Part 1 by Sir Douglas Hall, K.C.M.G.	620
RADIO TOPICS by Recorder	626
IN YOUR WORKSHOP – Inexpensive A.M. Receivers	628
NEW PRODUCTS	634
CONSTRUCTOR'S DATA SHEET No. 98 (Common Musical Terms II)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio & Electronics Constructor is printed by Carlisle Web Offset.

JUNE ISSUE WILL BE
PUBLISHED ON 2nd JUNE

VOLTAGE CONTROLLED OSCILLATOR

By A. Foord

Using basic linear i.c. principles, this ingenious design is capable of being controlled over a frequency range of 100 to 1. Outputs are square and triangular, and the addition of a converter enables a sine wave output to be produced as well

VOLTAGE CONTROLLED OSCILLATORS ARE USEFUL IN many applications. Typical of these are the recording of very low frequency signals on a normal tape recorder, swept frequency response measurements, and electronic music.

A v.c.o. should have good stability, excellent linearity and a wide frequency range. There are several possible circuit approaches, depending on the maximum operating frequency and other parameters chosen. Unfortunately, integrated circuits such as the NE566 function generator can only be modulated over a 10 to 1 frequency range. This article describes how an integrator, a comparator and an inverting amplifier can be used to produce a waveform generator which can be voltage controlled over a range of 100 to 1.

BASIC V.C.O.

The basic form for this v.c.o. is shown in Fig. 1. The input voltage range is 0 to 10 volts and IC1 provides a unity gain inversion for the input. IC2 is the integrator with IC3 as a comparator.

Initially assume that V3 is negative and TR1 turned off. The input signal V1, which must be positive, forces a current through R2 into the summing junction of the integrator. The output voltage of IC2 will slew negatively at a rate which depends on V1, R2 and C1. When it reaches -V the comparator output, V3, will go positive. This switches on TR1 and changes the comparator reference to +V.

With TR1 turned on a current is drawn, through R1, out of the summing junction which is twice that supplied into the junction through R2. This results in a net current out of the summing junction which is equal to, but opposite in magnitude to the previous current. V2 now slews positively. When it reaches +V the comparator will again switch to the -V level, which cuts off TR1. This allows the cycle to repeat.

For the conditions shown, where IC1 forms a unity gain inverter and there are equal currents into and out of the integrator capacitor for each half-cycle, the waveform is symmetrical. The frequency is given by the equation included in the diagram.

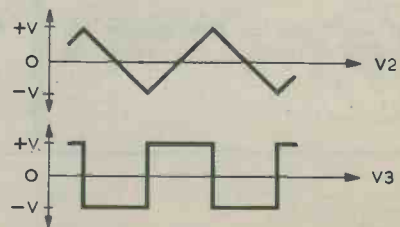
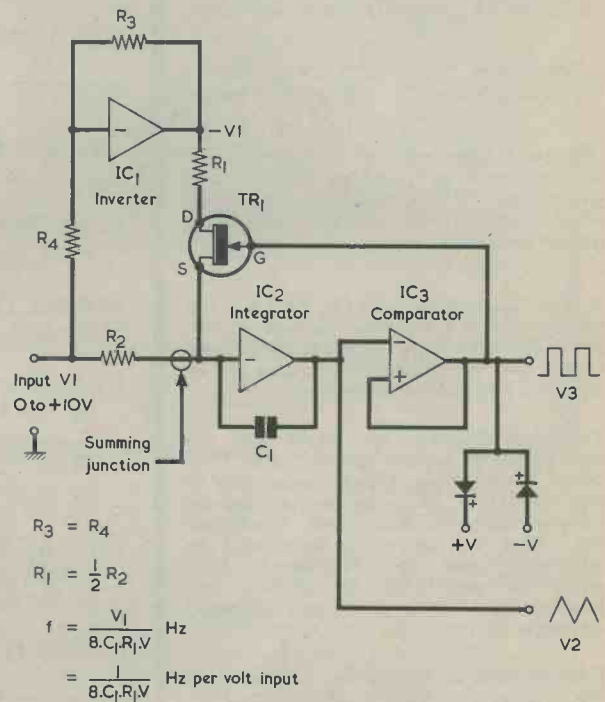


Fig. 1. A basic voltage controlled oscillator

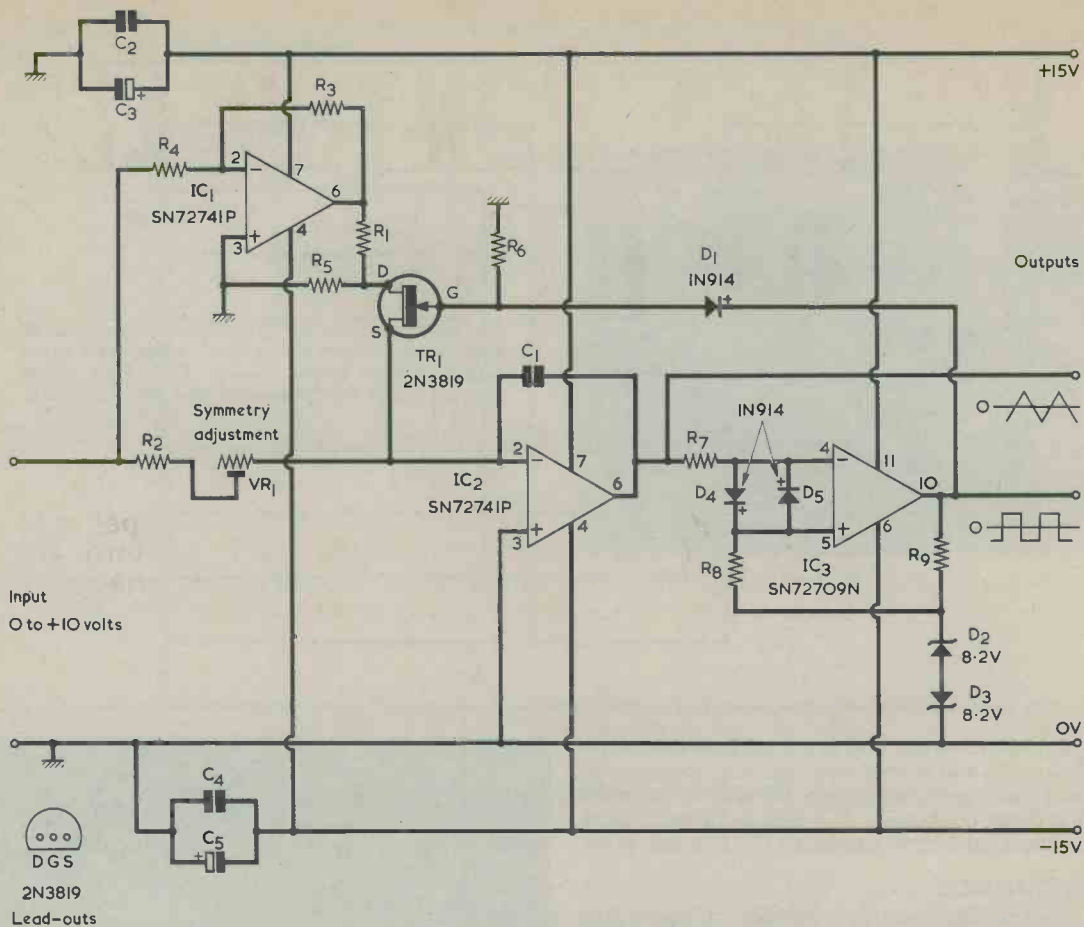


Fig. 2. The practical voltage controlled oscillator

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1	10k Ω	R12	270 Ω
T2	18k Ω	R13	390 Ω
R3	10k Ω	R14	220 Ω
R4	10k Ω	R15	220 Ω
R5	2.2k Ω	R16	390 Ω
R6	22k Ω	R17	270 Ω
R7	10k Ω	R18	120 Ω
R8	10k Ω	R19	2.2k Ω
R9	1.8k Ω	R20	27k Ω
R10	2.2k Ω	R21	12k Ω
R11	120 Ω	R22	8.2k Ω

VR1	10k Ω multiturm
VR2	10k Ω multiturm

Capacitors

C1	1,000pF and 470pF in parallel, 5%
C2	0.1 μ F ceramic
C3	10 μ F electrolytic, 16 V. Wkg.
C4	0.1 μ F ceramic
C5	10 μ F electrolytic, 16 V. Wkg.

Semiconductors

TR1	2N3819
D1	1N914
D2	8.2V zener, 400mW
D3	8.2V zener, 400mW
D4-D13	1N914, 10 off

Integrated Circuits

IC1	SN72741P
IC2	SN72741P
IC3	SN72709N
IC4	SN72741P

Miscellaneous

Printed circuit board, 7.5 x 10.25cm.


PRACTICAL CIRCUIT

A practical circuit for 0.1 to 10kHz operation is shown in Fig. 2. For the 8.2 volt zener diodes, V3 will be limited to about plus or minus 8.8 volts. With C1 at 1,470pF, R1 at 10k Ω and V at 8.8 volts:

MAY 1975

$$f = 0.97\text{kHz per volt input.}$$

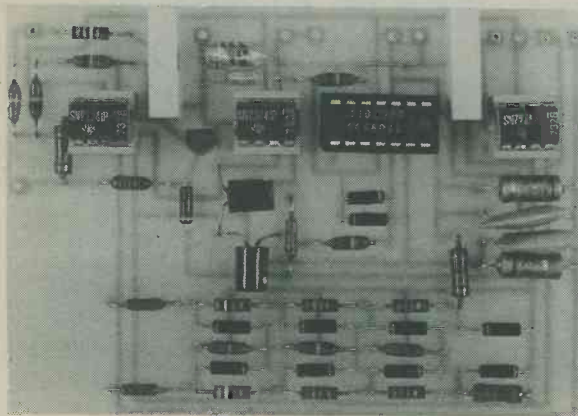R5 attenuates the drain voltage of TR1 so that it can be held off even for high values of V1. This resistor will not affect the magnitude of the current injected into the



The voltage controlled oscillator and triangular to sine wave converter are both assembled on a single printed circuit board. This then offers square wave, triangular and sine wave outputs

summing junction when TR1 is on because one end is referred to earth and cannot inject or remove current at the virtual earth summing point. R7 and R8 with D4 and D5 prevent latch-up of IC3 during turn-on transients. R9 limits the output current of IC3 to a safe value.

PERFORMANCE

The input voltage against frequency characteristics for two values of C1 are shown in Fig. 3. These rates are about 8% lower than the theoretical values due to component and other tolerances. For example, the inverter IC1 may not give exactly unity gain, and the f.e.t. has an 'on' resistance of about 200Ω. The setting up procedure using VR1 produces a symmetrical waveform but allows errors in the theoretical rate. If an exact rate is required this may be achieved by trimming C1 or by scaling the input voltage. The accuracy of the circuit was plus or minus 5% over the range of 100Hz to 10kHz for a value of 1,470pF in C1.

The accuracy at low input voltages is limited by voltage and current offsets in the integrated circuits. For example, an input voltage of 100mV might give a frequency of 100Hz in theory. However, an integrated circuit offset error of 5mV would give a 5% error in frequency.

Consequently, the performance measured on the prototype for low input voltages is better than that to be expected in general from such a circuit, where no attempt is made to balance out offset errors.

SINE WAVE CONVERTER

The triangular waveform is converted to a sine wave by a diode function generator. This provides the facility of approximating a non-linear relationship with a series of straight line segments. The point where two straight line segments join is called the 'break point', and may be altered, together with the slope of each segment, to provide the required non-linear function. A complete network of resistors, diodes and bias supplies may be used on its own or connected around an amplifier.

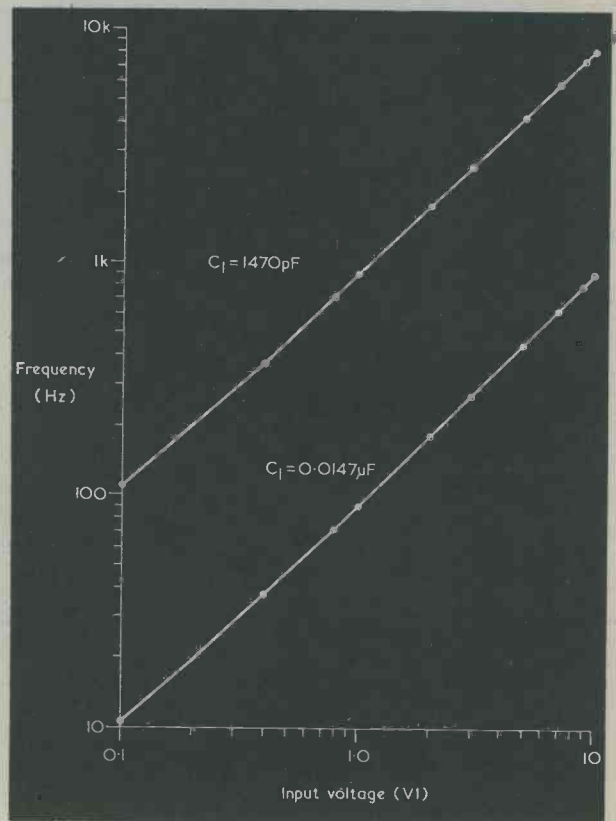


Fig. 3. Voltage-frequency characteristics for two values of C1

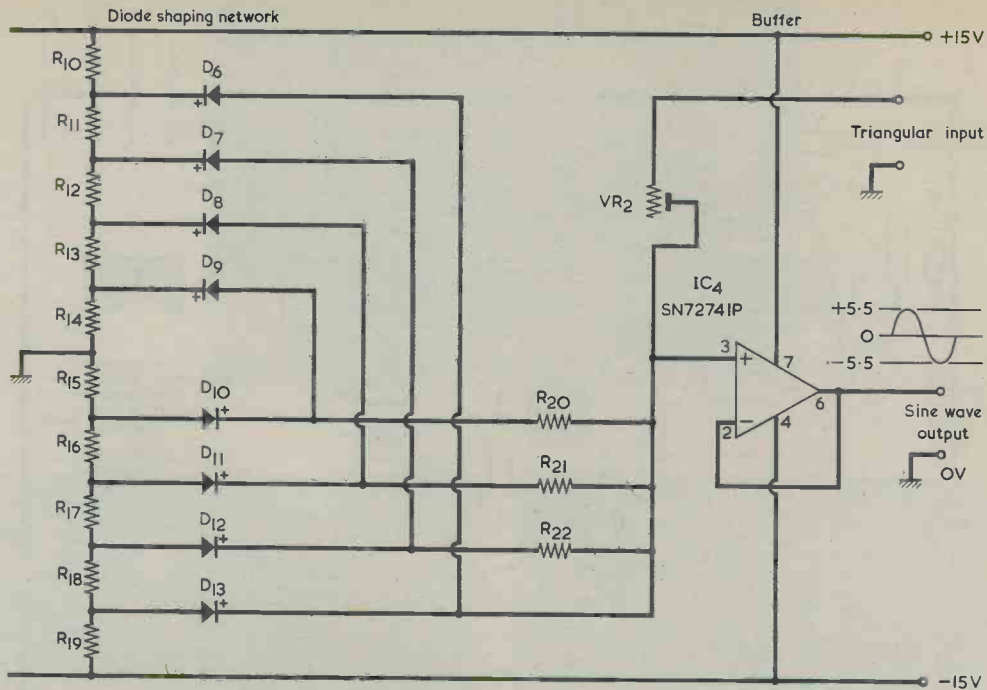


Fig. 4. A triangular to sine wave converter

A triangular to sine wave converter is shown in Fig. 4, and is followed by a buffer amplifier.

When the input in Fig. 4 is initially zero then all the diodes are reverse biased. If the triangular waveform is rising linearly then the output is progressively reduced as D9, D8, D7 and D6 conduct. As the input voltage decreases back towards zero each diode is cut off in the reverse order to give the second quarter of the sine wave. For negative half-cycles diodes D10, D11, D12 and D13 conduct in a similar manner.

The points at which the slopes change are not sharp but are rounded by the non-linear forward characteristics of the diodes. One of the difficulties of this approach is that the adjustment of the slope of each line segment influences all the following segments, and it is impossible to just 'touch up' an intermediate slope.

VR2 should be adjusted for the best possible waveform.

The Table shows the relative amplitudes of the sine wave fundamental, at 5kHz, and the harmonics. It can be seen that the second harmonic is 39dB down on the fundamental, so that the sine wave is quite distorted at a total harmonic distortion of 1.8%.

CONSTRUCTION

The circuits of Figs. 2 and 4 are combined in a single unit, and this may be assembled on a printed circuit board, as in Fig. 5. The copper pattern is reproduced full-size in Fig. 6, which can be traced. Small multi-turn potentiometers are required for VR1 and VR2, and suitably dimensioned components are miniature 15-turn Cermet Trimpots available from Doram Electronics, Ltd. Before preparing the printed circuit, confirm the positioning of the connection points shown in Fig. 6 for

the potentiometers with the actual potentiometers to be used. If there are any differences modify the printed circuit pattern to agree with the actual components.

IC1, IC2 and IC4 are the 8-pin d.i.l. version of the 72741. IC3 is the 14-pin d.i.l. version of the 72709. There is room on the board for two capacitors in parallel for C1.

The completed unit has the following performance.

Input impedance	= 6.6k Ω
Square wave output	= ± 13 volts
Triangular output	= ± 8.8 volts
Sine wave output	= ± 5.5 volts.

TABLE

Harmonic content for a 5kHz sine wave

Frequency (kHz)	Relative Amplitude (dB)
5	0
10	-39
15	-43
20	-56
25	-38
30	-59
35	-76
40	-76
45	-77
50	-68

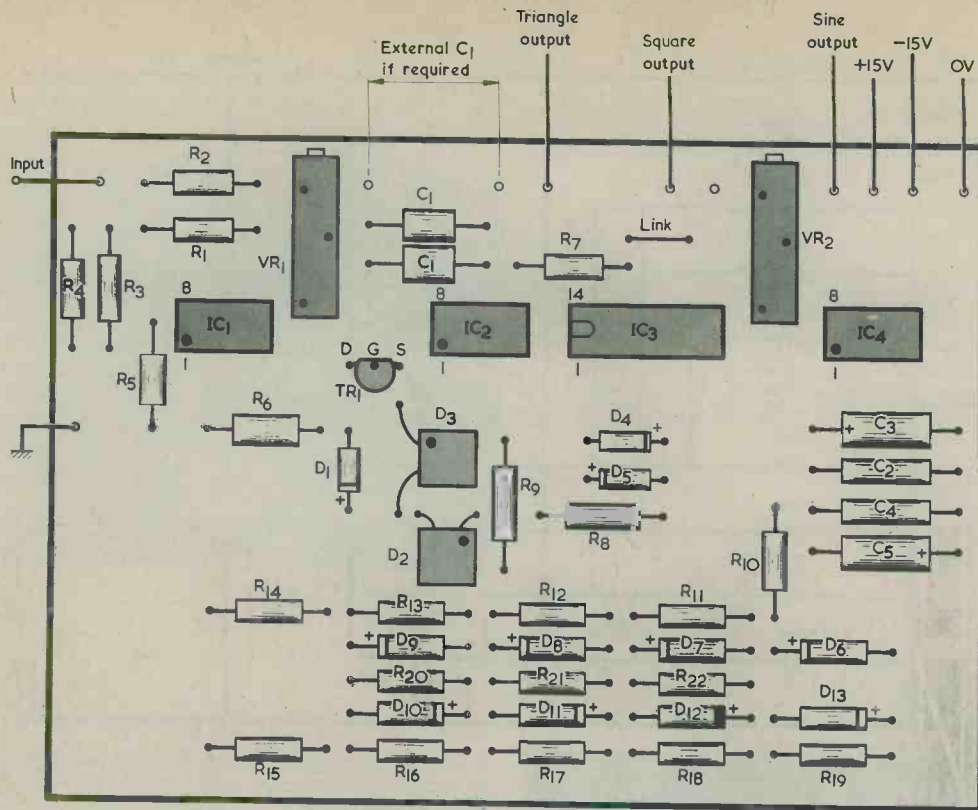


Fig. 5. The component side of the printed circuit board



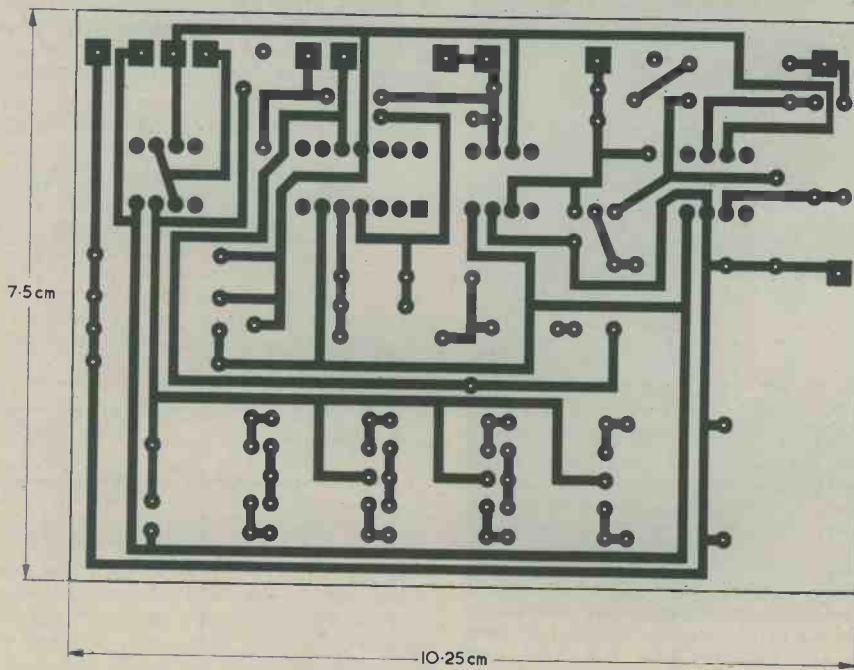



Fig. 6. The copper side of the p.c. board. This is reproduced full size and may be traced

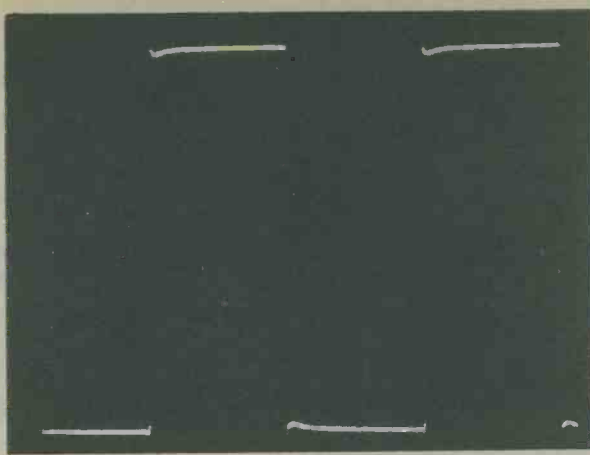

The square wave produced at 5kHz

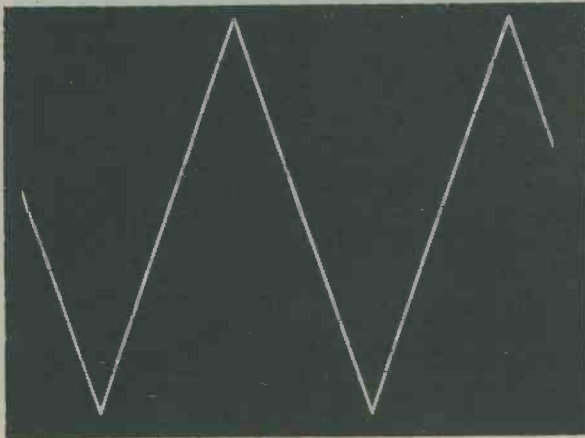

5kHz triangular wave

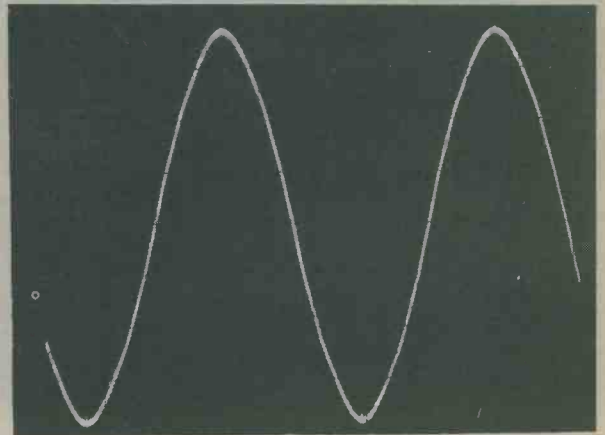

The sine wave output at 5kHz

The accompanying photographs show the completed unit and the three output waveforms. The latter were all

taken at 5kHz.

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received for to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

Geloso Front End Converter 10-80 Metres – S. Crabtree, 48 Southfield Road, Middlesborough, Cleveland. – Circuit or any other details, to borrow or purchase.

Ex-Service Wireless Set No. 19 MK III – G. Ellis, 9 Fraser Gardens, Southbourne, Emsworth, Hants, PO-108-PY – Circuit diagrams, operating instructions or any information.

DST 100 MK III Communication Receiver – W. H. Hale, 83 Merthyr Road, Pontypridd, Glamorgan – Circuit or any other data to borrow or purchase.

Microvolter 10b, Service No. 503 and Philco Battery 1 Valve Signal Generator – F. Higgins, 4 Rural Cottages, Shrawardine, Shrewsbury. – Any information or circuit diagrams.

Bendix RA – 10RX and R101 – B (ARN-6) – A. D. Beresford, 49 Blake Road, Gt. Yarmouth, Norfolk. – Circuits or any data.

Radio Constructor, April 1968 issue – R. A. Read, 7A The Close, Salisbury, Wilts. – Loan or purchase.

ASSEMBLE YOUR OWN COMPUTER



Electronic Computer (Model 0600) you assemble yourself which comes complete with 112-page illustrated instruction manual containing fifty programmes. You can even make up your own programmes. Works on the same principle as a real computer. Programmes in the manual include: playing chess and other computerised games; matching wits against the computer; predicting the weather; mathematical calculations; cybernetics; solving puzzles.

It is believed the kit is the first of its kind in this country and is from a concept originated in Germany by FranckH'sche Verlagshandlung Kosmos. It is being made to the original specification and copyright by Logix Enterprises of Montreal, and Patterson Edwards Ltd. (makers of Leeway Toys) are the sole distributors in the U.K.

Approximate retail price including VAT, £17.95.

MARCONI MARINE 75 YEARS OLD — THE EARLY DAYS

The Marconi International Marine Company Limited, the world's first marine wireless company, celebrated the 75th anniversary of its inception on 25th April.

Created in 1900 on the 26th birthday of its founder Guglielmo Marconi, The Marconi International Marine Communication Company Limited, with offices in London and Brussels and agencies in Paris and Rome, began as it has continued — a world leader in the marine communications field.

The business was established to offer to ship-owners an entire service whereby wireless apparatus, operators and use of Marconi stations ashore were provided on a rental basis. This service still operates today with the exception of the Marconi shore stations which are now under Post Office control.

Marconi's chief interest had always been wireless for those at sea, and just prior to the formation of the company, he took the first major step in achieving one of his foremost ambitions, to end the isolation of ships at sea. Working from a point on the South Wales coast near Penarth he succeeded in sending a message to an island in the Bristol Channel — a distance of just three-and-a-half miles. Thus began the chain of events which brought marine radio communication to vessels sailing the world's seven seas.

In 1901 came further experiments which achieved communication over 198 miles between the Isle of Wight and the Lizard, and then, Marconi's greatest achievement the successful transmission of Morse code from Poldhu, Cornwall, to St. John's, Newfoundland.

A short time later further tests were carried out between Poldhu and the American liner *Philadelphia* when messages were received up to a distance of 1,551 miles.

The British and Italian navies had quickly adopted Marconi wireless and the system had been introduced to the USA, where a company was registered later to become the Radio Corporation of America.

INCREASE IN V.A.T.

The Budget statement announcing increases in V.A.T. was made too late for advertisers to alter their copy. Therefore prices should be checked with advertisers before placing orders.

NEW OXIDE AVAILABLE ON REEL

LH-Super, BASF's newest tape coating using maghemite in its purest form, is now available as a reel-to-reel tape in long play and double play versions.

Both versions, product-named LP35 LH-Super and DP26 LH-Super, come in three reel sizes — 5in, 5½in, and 7in — and are packaged in plastic swivel boxes.

LH-Super contains even smaller and more evenly sized oxide particles than ordinary LH tape. This results in a 2 dB reduction in tape hiss; a 3 dB increase in permissible recording level (at 5% harmonic distortion); greatly reduced headwear; and virtually no drop-outs.

Recommended retail prices of reel-to-reel LH-Super are: LP35 LH-Super, £2.66 (5in); £3.20 (5½in) and £4.54 (7in). DP26 LH-Super, £3.50 (5in); £5.08 (5½in) and £6.28 (7in). All prices exclude VAT.



COMMENT

WIRELESS MUSEUM AT STATELY HOME

The Vintage Wireless Museum of the Wireless Preservation Society is being transferred from its former site in South Lincolnshire to a stately home in the Isle of Wight, which is open to the public throughout the year - Arreton Manor, the home of Count and Countess Slade de Pomeroy.

The manor, which dates back to the Middle Ages, already houses a folk museum, exhibition of domestic and agricultural by-gones, as well as a superb collection of dolls, dolls' houses and toys.

Established a few years ago, the Wireless Preservation Society is exclusively devoted to the collection, preservation and restoration of wireless, electronic and sound reproducing equipment, including gramophones and television receivers, for purely cultural, educational and historical purposes.

An entirely non-profit-making organisation, all its officers are honorary. The curator and secretary is Mr. D. Byrne, G3KPO, who has now moved to No. 32 Luccombe Road, Shanklin from whom further information can be obtained.

QUOTE

"Now that Parliament is to be broadcast on the radio, may we hope that the two sides of the House will be distinguishable by means of stereo?"

From a reader's letter published in the *Radio Times*.

TRANSISTOR HEATER

An unusual heating technique is employed in a temperature stabilizer circuit which is described in *Mullard Outlook* No. 2 for 1974. The function of the circuit is to maintain a small metal block at a constant temperature. Components such as quartz crystals may then be housed in a cavity in the block, whereupon they run at the constant temperature.

The temperature sensing device in the control circuit is a thermistor which is clamped to the block. This is connected in a bridge circuit which couples to an operational amplifier. In its turn, the output of the latter connects, via a current limiting resistor, to the base of a p.n.p. silicon power transistor type BD132.

A clever feature of the design is that the transistor itself acts as the heater

which raises the temperature of the metal block to the desired level. For close thermal coupling the transistor is clamped to the block alongside the thermistor. When the temperature of the block falls, the corresponding changing bridge voltages cause the op-amp output to go negative, thereby making the transistor conductive. When the block temperature rises the op-amp output swings positive, thereby turning the transistor off. A typical operating temperature is around 69°C.

To have a power transistor driving a resistive heater element would be a common approach in a set-up of this nature. But to use the transistor itself as the heating element strikes me as being one of the most ingenious ideas we've bumped into for quite a long time.

CAR STEREO CASSETTE PLAYER



The sound of the '70s comes through loud and clear on the new Beltek MW/LW Car Stereo Cassette Player introduced by Eagle International of Wembley, Middlesex.

Designated Model M6680 this latest extension to the Beltek range of precision engineered home and car stereo equipment has been added due to the rapidly increasing popularity of the series. Both new and existing car stereo owners are turning to versatile Beltek units for their next experience of in-car entertainment.

M6680 gives top quality reproduction at 8 + 8 watts power output. It has fast forward, rewind and eject; medium and long wave radio; illuminated function indicators; push button MW/LW switching; end of tape run indicator; instant play loading mechanism. Recommended retail price is £66 + VAT.

THE GREEKS HAD A WORD FOR IT

Did you know that the derivation of the word stereo comes from the Greek word *stereos* meaning solid?

MAY 1975



"A time like this - and all he can think of is inventing something he calls 'Ark Welding'!"

597

SEQUENTIAL LAMP CIRCUIT

By G. A. French

Suggested Circuit 294

MOST READERS WHO HAVE ATTENDED fairgrounds or visited large cinemas or halls will have seen a form of display lighting in which individual lamps in a rectangle are successively lit and extinguished in a manner which gives the impression that the light from the lamps is moving around the rectangle in one direction. The scheme is shown on a small scale in Fig. 1 at a particular instant in time. In this diagram, every third lamp is extinguished. Shortly afterwards, the extinguished lamps will light up and the lamps next to them in the direction of the arrows will be extinguished, after which the subsequent lamps along the rectangle will be extinguished, and so on. The extinguishing of every third

bulb proceeds continually along the lamps, and the overall effect is that the light itself is in motion.

This month's Suggested Circuit presents a simple means of achieving a small sequential lamp switching display in this manner, the controlled lamps being standard m.e.s. torch bulbs. The resulting display can be employed in a shop window display, as a novelty in a small discotheque or for any similar purpose. The circuit is classed in the experimental category because the oscillator controlling the lamps requires capacitors having a performance not covered in manufacturers' specifications, and because this oscillator runs at a frequency approaching its higher limit.

FOUR WIRE SYSTEM

A series of lamps offering the effect illustrated in Fig. 1 may be controlled by a four wire system, as illustrated in Fig. 2 (a). This shows six lamps. The four wires continue to the right, coupling to succeeding lamps which are connected up in the same manner as the six illustrated. If the lamps form a rectangle, the first lamp, PL1, may be any lamp in that rectangle. The lamps then proceed in groups of three arriving eventually at a group of three which is immediately followed by PL1. Any number of lamps may be employed, provided that the total is a multiple of three. All lamps share a common return wire. If a voltage is applied to Input 1 and the Common wire, the first lamps in all the groups of three are lit. Should a voltage be applied to Input 2 all the second lamps in the groups of three are lit, and if a voltage is applied to Input 3 all the third lamps in the groups of three are lit.

Fig. 2 (b) shows the waveforms which need to be applied to the three inputs to achieve sequential switching of the lamps.

Between points A and B in Fig. 2 (b) Input 1 is off and Inputs 2 and 3 are on, with the result that the first lamps in each group of three are extinguished and the second and third lamps are lit. Between points B and C, Inputs 1 and 3 are on whilst Input 2 is off. The consequence is that the second lamps in the groups of three are unlit whilst the first and third are illuminated. Both Inputs 1 and 2 are turned on between points C and D whilst Input 3 is off, causing the third lamps of each group to be extinguished, and the first and second to be lit. Between points D and E the situation reverts to that given between points A and B, and another cycle has commenced.

RADIO & ELECTRONICS CONSTRUCTOR

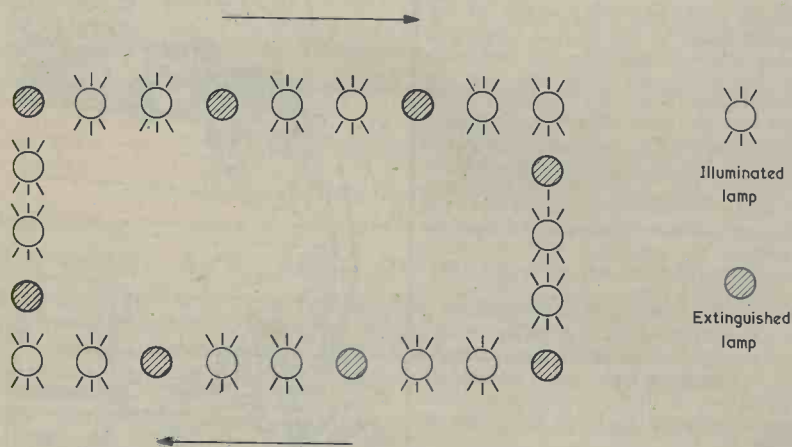


Fig. 1. A layout of twenty-four lamps illustrating the 'moving light' effect

The length of a complete control cycle is that between points A and D, after which it repeats once more and continues to repeat. The lamps can, in consequence, give the desired 'moving light' effect if the three waveforms of Fig. 2 (b) are applied to Inputs 1, 2 and 3 of Fig. 2 (a).

CONTROL OSCILLATOR

The basic circuit of a suitable control oscillator appears in Fig. 3. In this arrangement the three transistors turn off successively and, between transitions from one state to the next, two transistors are always turned on and one transistor is always turned off.

To explain oscillator operation let us examine the circuit of Fig. 3 at an instant when TR1 is turning off. Both TR2 and TR3 are turned on. As TR1 turns off its collector goes negative, causing C1 to charge via R2 and the base-emitter junction of TR2. C1 acquires a charge which is nearly equal to the supply voltage. After a period TR1 turns on again whereupon its collector takes the negative terminal of C1 towards the lower supply rail. The positive terminal of C1, which is now charged, takes the base of TR2 positive of the lower supply rail, with the result that TR2 turns off. As with TR1, TR2 collector goes negative, thereby allowing C2 to charge via R4 and the base-emitter junction of TR3. At the same time, C1 is discharging via R3. When C1 is nearly fully discharged the base of TR2 will become sufficiently negative for this transistor to pass collector current. It turns on, whereupon its collector goes positive and, by way of the charged C2, takes TR3 base positive and turns off TR3. The cycle then continues, with TR3 turned off until C2 has discharged into R5. TR3 then turns on and turns off TR1, and so the cycle repeats. Each transistor turns off in turn following the sequence TR1, TR2, TR3, TR1, TR2, TR3, and the length of time that each transistor is turned off depends upon the values of the capacitor and the resistor in its base circuit. If all the capacitor and resistor values are equal, then each transistor is turned off for the same length of time.

There is no regenerative feedback in this three-transistor oscillator as occurs in a two-transistor multivibrator and, indeed, the coupling from one collector to the following base would be degenerative if the transistors were allowed to function as linear amplifiers. In consequence, the oscillator will only run at relatively very low frequencies which allow the transistors to operate as switches, with at least one transistor always turned hard on to break any linear amplification chain through the three. It is necessary for the collector resistors to have significantly lower values than the following base resistors in order that the capacitor between them charges more rapidly than it discharges. The three transistors are germanium instead of silicon types for the following two reasons. Firstly,

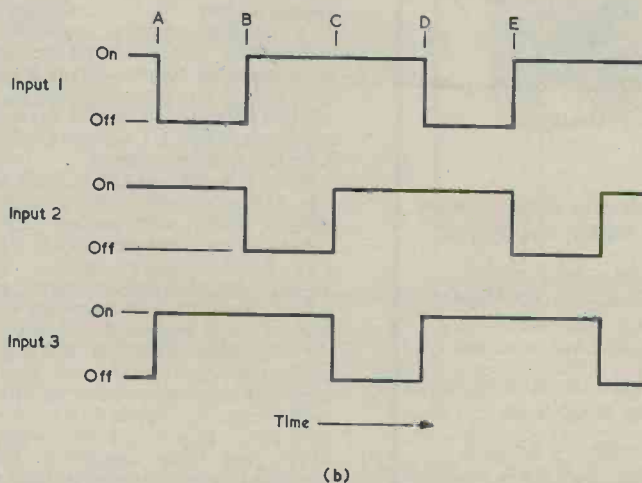
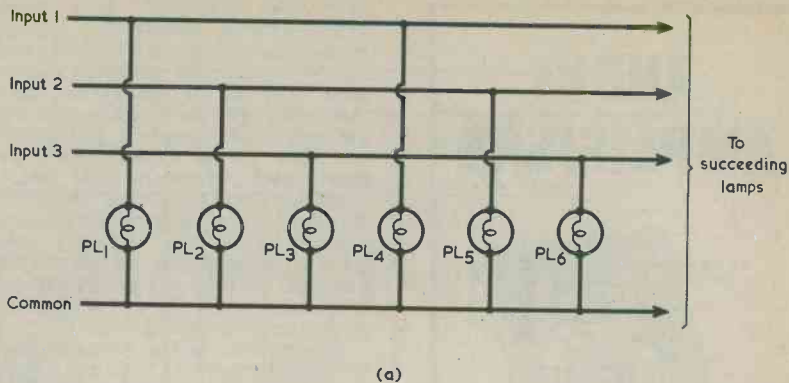


Fig. 2(a). The lamps may be connected in groups of three in a four wire system
(b). The waveforms which need to be applied to the three input wires

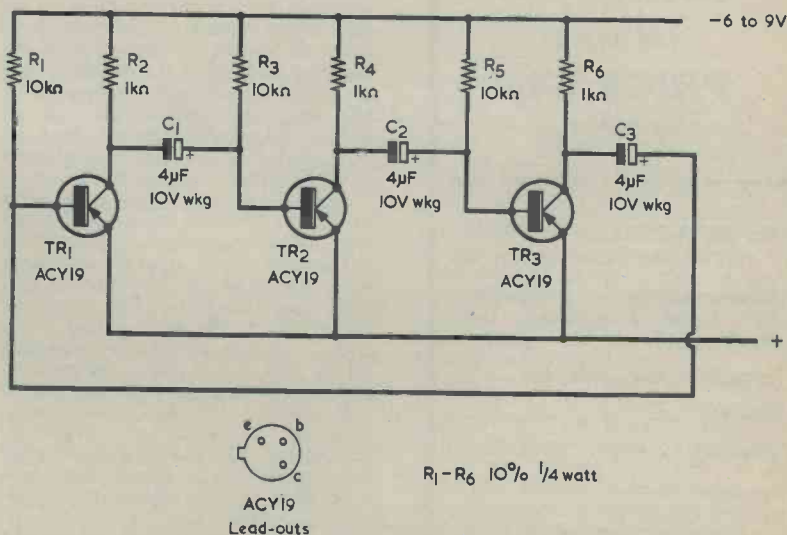


Fig. 3. An unusual oscillator, in which each transistor turns off successively

AUDIO AMPLIFIERS



16 Transistor & Valve Designs for the Home Constructor

Amplifiers for
Tuner Units, Record Players,
Tape Recorders,
Public Address, etc., etc.

Includes contributions by such well-known authors as

A. S. Carpenter, A. Kinloch,
E. Govier, G. A. French,
F. G. Rayer, P. F. Bretherick,
K. Jones, D. Aidous,
R. Murray-Shelley, C. Swires,
G. A. Stevens and V. E. Holley.

Edited by J. R. Davies

124 pages

PRICE 53p

P & P 12p.

To: DATA PUBLICATIONS Ltd.,
57 Maida Vale London W9

Please supply copy(ies)
of "Audio Amplifiers", Data
Book No. 18. I enclose cheque/
crossed postal order for.....

Name.....

Address.....

.....

.....

.....RC

BLOCK LETTERS PLEASE

germanium transistors have much higher reverse base-emitter voltage ratings than do silicon transistors and so they present no problems due to zener effect at the base-emitter junctions. Secondly, the base and collector voltages of a turned-on germanium transistor are at approximately the same level whereas, with silicon transistors, the base of a turned-on transistor is at a higher voltage than the collector. If silicon transistors were used in the oscillator the electrolytic capacitor between any two turned-on transistors would have a voltage of reverse polarity applied across it.

The oscillator of Fig. 3 runs particularly satisfactorily if C1, C2 and C3 are given values of the order of 100 μ F. It then completes a cycle in about 2 seconds. Interestingly, despite the lack of obvious regenerative feedback it is self-starting, and will begin oscillation both when the supply voltage is raised gradually from zero volts or if it is applied abruptly. Whatever capacitors are employed for C1, C2 and C3 should have low leakage currents.

With C1, C2 and C3 at 4 μ F, as in Fig. 3, the frequency rises to approximately 12Hz, and leakage current requirements in the electrolytic capacitors become more rigorous. The author's circuit failed to operate when a 4 μ F capacitor with a leakage resistance of 1M Ω was employed in one of the capacitor positions, although it performed very reliably and gave the same self-starting operation as with the 100 μ F capacitors when 4 μ F capacitors with much higher leakage resistances were used. The capacitors finally employed were miniature Mullard type C426 components. There is no reason to doubt that other makes and type of capacitor would have been equally suitable if they had been available. If, incidentally, an ordinary multimeter switched to an ohms range is used to measure the leakage resistance of an electrolytic capacitor, the meter positive lead should be connected to the negative lead-out of the capacitor and the meter negative lead to the positive lead-out. The meter needle will, of course, take some time to reach its final setting as the capacitor charges from the battery in the meter.

The maximum leakage current quoted by Mullard for a 4 μ F 10 volt type C426 capacitor is 4.1 μ A, which corresponds to a leakage resistance, with 10 volts across the capacitor, of a little more than 2M Ω . The capacitors employed by the author had much higher leakage resistances than this figure and it has been the writer's experience that this is a general characteristic of C426 capacitors, although it cannot of course be guaranteed. The author has not tried the circuit with tantalum electrolytic capacitors or with plastic foil capacitors of the same value.

A second factor which makes the circuit of Fig. 3 experimental is concerned with the highest frequency at which it will run. Here, the author

has not had experience with a quantity of oscillators employing the circuit and can only relate to his practical experience with the prototype. It was found that the oscillator continued to oscillate, at a higher frequency, when one of the 4 μ F capacitors was replaced by a 1 μ F capacitor, but that it refused to operate when a 0.5 μ F capacitor was substituted. This argues that, with 4 μ F capacitors, the circuit is approaching the upper limit at which it can run.

These points having been made, the author can state that the prototype oscillator ran very reliably, as should others made up to the circuit, but that it may be necessary to select coupling capacitors. The transistors do not appear to have any noticeable effect on oscillator running although it is conceivable that low gain or excessively leaky specimens may cause difficulties. In the writer's view, the advantage given by the extreme simplicity of the oscillator considerably outweighs the disadvantage that components are a little critical.

It will ease construction if the oscillator of Fig. 3 is initially made up and checked for correct operation. Oscillation will be indicated if a voltmeter is connected across R2, R4 and R6 in turn and it is found that the meter needle flicks at oscillation frequency in all three instances. The circuit can be powered temporarily by a 6 or 9 volt battery. Once the oscillator is running satisfactorily, the remaining parts may be obtained and assembled.

SEQUENCE SWITCHING

The full sequence switching circuit appears in Fig. 4. Here, the oscillator of Fig. 3 is slightly modified by inserting lamp switching transistors in the collector circuits. TR1 to TR3, C1 to C3 and R1 to R6 are the same as in Fig. 3, and have the same type numbers or values. A 6.3 volt heater transformer, T1, is now incorporated to power both the oscillator and the lamps. The oscillator supply is given by rectifier D1 and the reservoir capacitor C4.

When TR1 is turned on its collector current flows into the base of TR4, causing TR5 to become fully conductive. Current may then flow, on mains half-cycles when the lower end of T1 secondary is positive, through silicon rectifier D2, through the lamps connecting to Input 1, and through TR5 to the upper end of T1 secondary. When TR1 is turned off so also are TR4 and TR5, and no current flows in Input 1. The lamps connected to Input 2 and Input 3 similarly turn on and off in sympathy with TR2 and TR3 respectively.

It is necessary to insert D2 in series with the Common line because, otherwise, negative half-cycles could be applied to the collectors of TR5, TR7 and TR9. Forward current would then flow in the collector-base junctions of these transistors and could upset circuit operation. When a resistive load

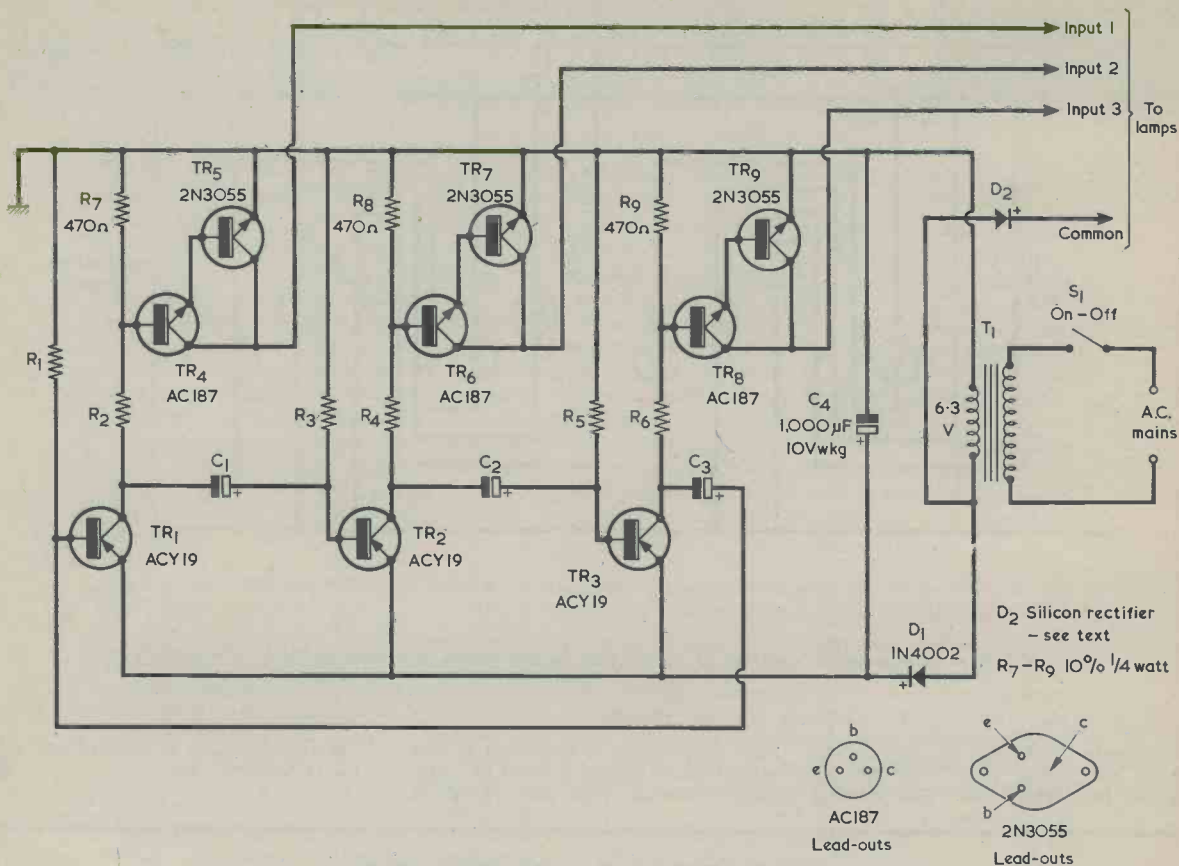


Fig. 4. The oscillator employed in the sequential light switching circuit

is connected via a diode to a sine wave alternating voltage, the effective heating voltage across the resistor is equal to 0.7 times the r.m.s. value of the alternating voltage. This relationship holds true regardless of the current in the load. In consequence the effective heating voltage applied to the lamps is 0.7 times 5.1 volts (6.3 volts minus about 1.2 volts dropped across D2 and the switching transistor) or 3.6 volts. The lamps could, in consequence be 6 volt types, whereupon they would be significantly underrun, or 3.5 volt types, whereupon they would be overrun by a negligible amount. Alternatively, 2.5 volt lamps could be used in series, as shown in Fig. 5. When a voltage is applied to Input 1 of Fig. 5 both PL1 and PL4 light up, whilst applying a voltage to Input 2 causes PL2 and PL5 to be illuminated. A voltage at Input 3 lights up PL3 and PL6. This arrangement has the advantage that inexpensive lamps are employed at a voltage

RADIO & ELECTRONICS CONSTRUCTOR

not excessively lower than their nominal rating, whereupon they should have a long life. Also, overall current consumption is low, being effectively a little less than 0.15 amp per lamp. The only disadvantage is that the total number of lamps must be a multiple of six instead of three.

The number of lamps which can be controlled is limited by lamp switching surge currents to 30, using the circuit arrangement of Fig. 5. The actual number of lamps is left to the constructor to decide, and the current rating of T1 secondary should be adequate for the total lamp current. This should be considered as the current consumed by *all* the lamps, and not by just two-thirds of them. D2 should have a forward current rating of at least twice the total lamp current to take up surges as the lamps are turned on. It may have a p.i.v. of 50 or 100 volts. The maximum collector current rating of transistors TR5, TR7 and TR9 is 15 amps, which should be more than

adequate for present purposes.

TR5, TR7 and TR9 are turned on and off fairly rapidly and, when the associated oscillator transistor is conductive, pass collector current for half the time only. The dissipation in each of these transistors is low and they will probably require heat sinks only when a large number of lamps are to be controlled. A check on their temperature should be maintained when the circuit is initially switched on, and heat sinks employed if it is found that the transistors run warm.

The author's prototype circuit incorporated 12 lamps using the arrangement of Fig. 5, and this is probably the minimum number of lamps which will enable the 'moving light' effect to be produced. The fact that the lamps run on half-cycles of a.c. does not produce any flicker. If the lamps are formed up in a rectangle they should be positioned accurately in straight lines. They could alternatively be laid out in a circle, whereupon the lamps should be

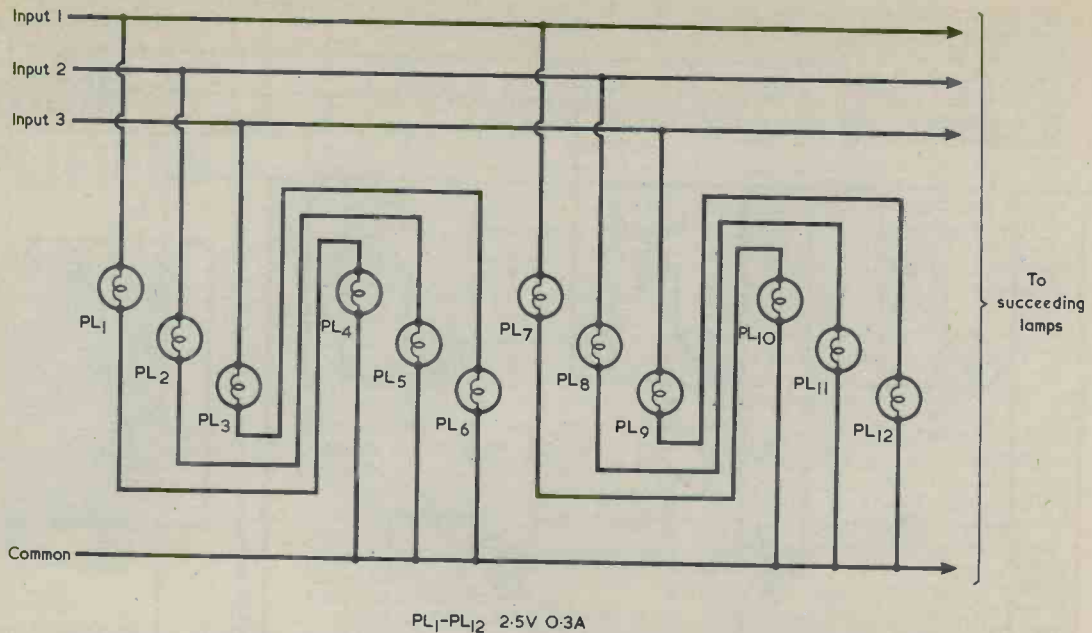



Fig. 5. A recommended method of connecting up the lamps in a practical four wire system

accurately positioned on that circle. Also, the lamps should be equally spaced from each other. The 'moving

light' impression is enhanced if they are mounted behind a sheet of translucent material. With only 12 lamps,

the 2N3055's ran quite cool and did not require heat sinks. ■

CATALOGUE

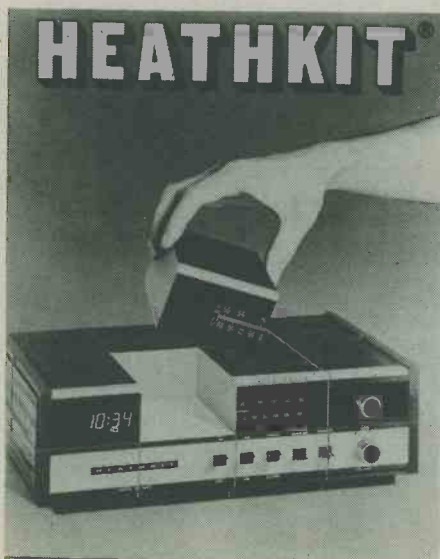

A NEW HEATHKIT CATALOGUE IS NOW AVAILABLE, THIS giving details of the latest kits available from Heath (Gloucester) Limited. An exceptionally wide range of kits is listed, these including hi-fi equipment, testers and analysers for the motorist, calculators, intercoms, burglar alarms, digital clocks, metal locators, amateur radio transmitters and receivers, oscilloscopes, meters and signal generators. Also available are kits for scientific work, for marine electronics, for radio control of models, and for transistor radios and a monochrome television receiver.

Amongst the new items introduced in this 64-page catalogue are an exhaust gas analyser, a triggered dual-trace oscilloscope, a function generator, a desk-top slide rule calculator, an s.s.b. transceiver with digital readout and an s.s.b. linear amplifier.

The catalogue is available free from Heath (Gloucester) Limited, Bristol Road, Gloucester, GL2 6EE. Alternatively, it can be collected at the Heath Gloucester showroom, which is next to the Bristol Road factory, or at the London Heathkit Centre at 233 Tottenham Court Road. ■

RECENT PUBLICATIONS



RADIO CONTROL FOR MODELS. By R. H. Warring. 220 pages, 245 x 190 mm. (9½ x 7½ in.)
Published by Sir Isaac Pitman & Sons, Ltd. Price £5.50

This large and well illustrated hard cover book is stated to be the most comprehensive yet produced on the subject of model control. It has a very attractive presentation, with many photographs of models, equipment and rallies, together with clear line drawings illustrating mechanical and electrical modes of operation.

At the start the book deals with some of the earlier radio control methods, such as those incorporating multi-channel reeds, and then takes the story all the way up to modern proportional control. This is a good approach, particularly for the newcomer to the hobby, as it shows the developments which have taken place over the years and illustrates how shortcomings in performance have been gradually and successfully designed out of radio control systems.

The work commences with a short review of all the radio control systems then, after dealing with radio fundamentals and single channel operation, carries on to a large section devoted to proportional control. This is followed by details of aircraft installations, radio control engines, and radio controlled boats and vehicles. The book concludes with advice on batteries and workshop procedure.

RADIO SERVICING POCKET BOOK, Third Edition. By Vivian Capel.
236 pages, 185 x 120 mm. (7¼ x 5 in.) Published by Newnes-Butterworth. Price £1.95.

The first edition of this book appeared in 1955 and the second in 1962. Over the last thirteen years there have been wide changes in domestic radio receiver design, and this book has been entirely rewritten to take these in for its current third edition. Large amounts of new material have been added and much obsolete matter, now out-dated, has been dropped. The result is a very practical book which is almost entirely concerned with receivers incorporating transistors and integrated circuits. As any service engineer will confirm, valves have not entirely faded from the servicing scene. Quite a few families still cherish their old valve radios, and a 20 page chapter in the book covers the essential details that are required here.

Approximately the first half of the book deals with household and car radios of all types, components, stereo broadcasting, aeriels and interference. The contents then turn to workshop practice, test equipment and workshop techniques, carrying on to fault diagnosis and alignment. The last two chapters cover useful data and provide a directory of service depots, or addresses where service replacements and information may be obtained, for over 140 radio manufacturers.

The book, which is in hard cover, provides a considerable amount of very useful technical information, and this is interlaced throughout with good common-sense advice. The section on workshop organisation takes in not only the running of a servicing centre employing a number of engineers but also the situation in which the serviceman is running his own one-man business. Attention is paid to the rapid location of faults, an essential feature of economic servicing. The book will be of particular value to the younger service engineer who is starting in the career, and also to the spare time serviceman who carries out repairs for friends and acquaintances.

AMATEUR RADIO TECHNIQUES, Fifth Edition. By Pat Hawker, G3VA.
304 pages, 245 x 185 mm. (9½ x 7¼ in.) Published by Radio Society of Great Britain. Price £2.

A 'huff and puff' stabilizer is a device which holds a *variable* frequency oscillator to within a few cycles of its adjusted frequency by means of t.t.l. chips. The oscillator frequency is applied to a 7400 gate so controlled by a crystal oscillator and divider chain that it opens for precise periods of time. A 74191 binary counter 'counts' the number of cycles from the v.f.o. passing through the gate and the logic number on one of its outputs is then checked. For decimal digits of 0 to 7 the output at pin 7 of the 74191 will be a logic zero and for digits from 8 to 15 the output will be a logic 1. At the pin 6 output, digits 0 to 3 give an output of zero whilst 4 to 7 give logic 1. The v.f.o. is then made to swing between the zero and 1 conditions from either of these two outputs by way of a varactor diode. The overall effect is that the v.f.o. is tuned by hand to the desired frequency, after which the stabilizer takes over and holds the oscillator frequency at the nearest value which lies between the zero and 1 logic output conditions.

This stabilizer is only one of many hundreds of circuits, ideas and tips which are to be found in the fifth edition of the book under review. Made up from items in the 'Technical Topics' feature of *Radio Communication*, the volume includes over 700 diagrams, and the text runs to about a quarter of a million words. Intended primarily for the amateur transmitting enthusiast, the book will be of value to anyone working in electronics. It is a veritable treasure-chest of information, both for reference and as a source of ideas.



FOUR CHANNEL SYNTHESISER

Part 2

By R. A. Penfold

In this concluding article, details are given for obtaining correct phasing of the two rear speakers. Also discussed are adjustments for optimum volume and balance

IN LAST MONTHS' ISSUE THE CONSTRUCTION AND PRINCIPLE of operation of the synthesiser were described. We now carry on to details of setting up the unit.


NOTES ON USE

Carefully check all the synthesiser wiring before switching it on. When it has been ascertained that all is correct, the two rear 8Ω speakers may be connected. The synthesiser input is then coupled to the stereo amplifier in the manner described in the preceding article.

Speaker phasing may next be checked. It is assumed that the phasing of the two front speakers is correct already. When checking the speaker phasing of a stereo system a common practice consists of playing a record or tape which has plenty of bass content, then playing it again after having transposed the connections to one speaker. Unfortunately, this approach is not feasible here as the synthesiser works on a frequency selective basis.

The method used by the author was to deal first with the right front and rear speakers and then with the left front and rear speakers.

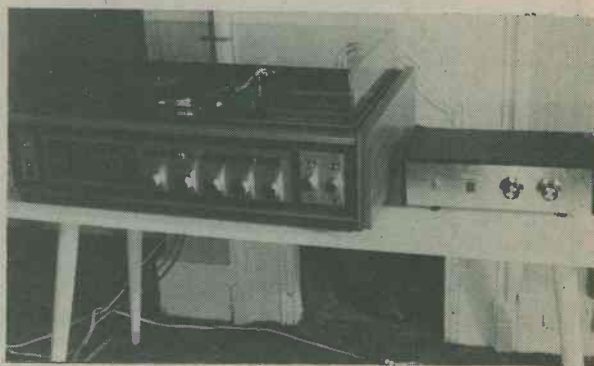Turn the synthesiser balance control fully clockwise to favour the right hand channel, and similarly adjust the balance control of the stereo amplifier. Play part of a record, then play it again with the connections to the rear right speaker transposed. With the connections one




The synthesiser coupled up to a hi-fi Music Centre


way round the sound will appear to come either from the front or the rear with little or nothing of the signal appearing to originate between the two. With the connections the other way round there should be a noticeable effect with which the sound appears to come from between the speakers. This second method of connection provides the correct phasing for the right rear speaker.

When this procedure has been completed for the right front and rear speakers the two balance controls are turned to fully favour the left front and rear speakers and the process is repeated. This time the connections to the left rear speaker are changed over to find the method of connection which provides the desired effect. The system is then ready for use.

In normal operation the stereo amplifier volume and balance controls should be set up for correct reproduction from the front left and right speakers. The synthesiser controls are then adjusted for best results from the rear speakers. These are intended to complement the sound from the front speakers, and the synthesiser volume control should not be set too high or the overall effect will be unrealistic. The synthesiser volume and balance controls are best set up when the system is reproducing a *tutti* passage of music, during which a large orchestra is fully employed. ■

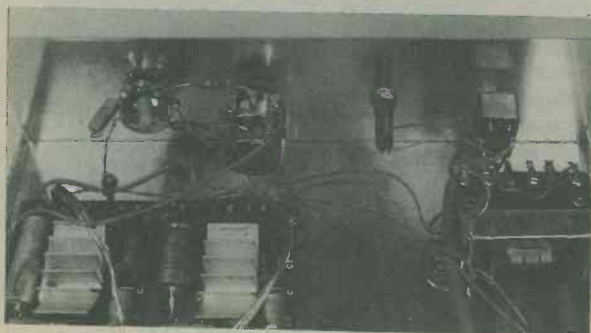

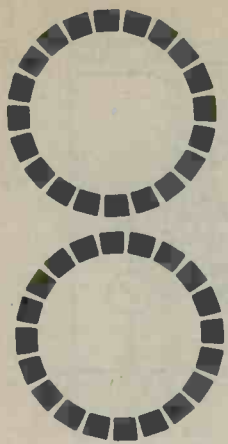A rear view of the front panel of the synthesiser



ELECTRONIC EGG TIMER

By R. J. Caborn

The 555 does yet another hat.

ALTHOUGH THE RATHER LIGHT-HEARTED DESIGN described in this article is intended primarily as a quite attractive egg timer, the basic principles can be applied to more serious use. Of interest to the experimenter will be the fact that the circuit employs that versatile i.c., the 555, in a novel and unusual manner. The 555 i.c. is available, incidentally, as NE555V, LM555CN or as the R.S. Components '555 type' timer.

The device is operated simply by turning on a switch, whereupon a light-emitting diode on its front panel becomes illuminated. After $3\frac{1}{2}$ minutes a loudspeaker produces a loud tone which rises continually in frequency until, after some 15 seconds, it is at a peak both in terms of frequency and volume. The siren-like character of the tone readily catches the attention, and the tone ceases when the device is switched off. The device is then at once ready for another cycle of operation.

THE 555

The egg timer incorporates a 555 i.c. in conjunction with a single transistor. The 555 produces the audible tone, whilst the transistor provides the $3\frac{1}{2}$ minute timing run.

The block diagram for the 555 internal circuitry will be familiar to many readers, and it is reproduced again in Fig. 1. The reader's attention is drawn to the infrequently used Reset facility which is available at pin 4. This pin connects to the base of an internal p.n.p. transistor, whose collector couples to the base of the internal n.p.n. Discharge transistor. When pin 4 of the i.c. is taken close to earth potential the p.n.p. transistor turns on and its collector drives a high base current through the n.p.n. Discharge transistor. The result is that the n.p.n. transistor turns hard on and discharges any capacitance which is connected between pin 7 and earth.

MAY 1975

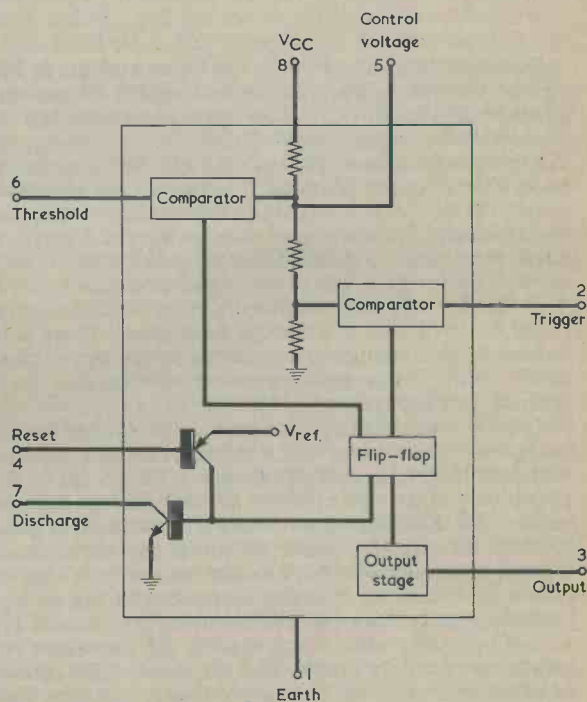


Fig. 1. The internal circuitry of the 555 i.c., with particular emphasis placed on the Reset facility

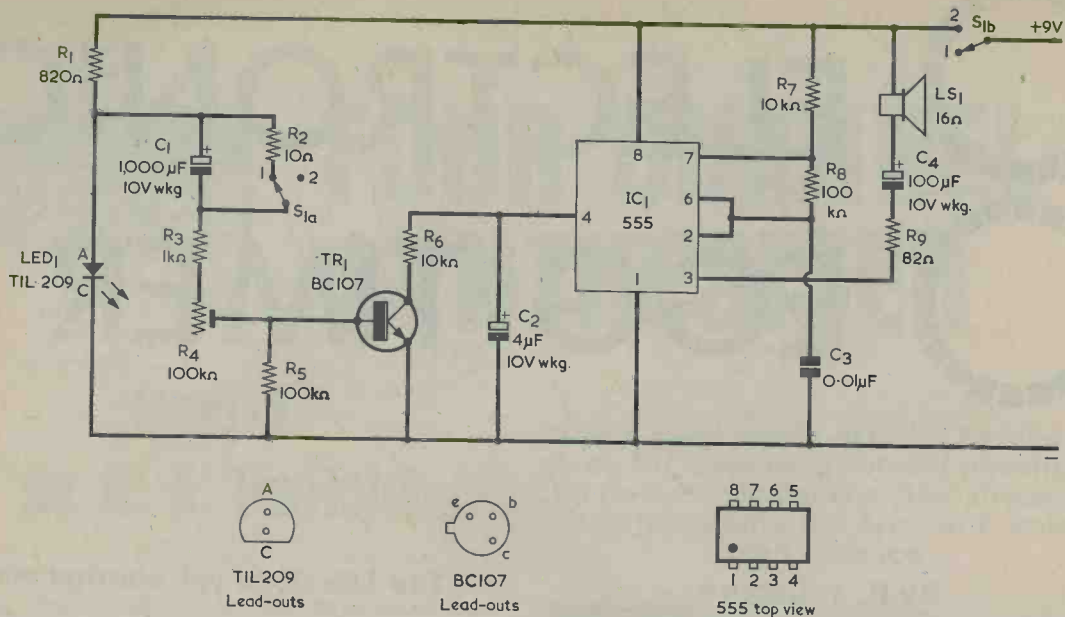


Fig. 2. The complete circuit of the timer. The i.c. functions as an a.f. multivibrator which is controlled by the external transistor

The complete circuit of the egg timer appears in Fig. 2, and it will be helpful to initially consider the network given by R7, R8 and C3. These appear in a standard 555 multivibrator configuration. When C3 is charging, the charging current flows through R7 and R8 in series. As soon as the upper plate of C3 reaches the threshold voltage at pin 6 the internal flip-flop changes states and the Discharge transistor turns on, taking pin 7 nearly to earth potential. C3 then discharges into R8 on its own until its upper plate falls to the trigger potential at pin 2. The flip-flop changes state again, the Discharge transistor turns off and C3 charges once more. There is in consequence a triangular waveform on the upper plate of C3. With the component values chosen, this has a frequency of approximately 700Hz.

The flip-flop also feeds into the output stage of the i.c. and a near-square wave which changes state in sympathy with the flip-flop is available at pin 3. This is fed to the 16Ω loudspeaker via capacitor C4 and current limiting resistor R9. The near-square wave is reproduced at good level by the speaker, whilst R9 limits any initial surge current to about 100mA. A louder output tone can be obtained, if desired, by using a speaker having an impedance greater than 16Ω and reducing the value of R9 accordingly. The sum of the speaker d.c. resistance (as measured by an ohmmeter) and the value of R9 should be of the order of 90Ω. The author found, however, that the output volume given with the component values shown was perfectly adequate.

RESET CONTROLS

The circuit, as so far described, represents an orthodox 555 multivibrator driving a speaker, with the exception that pin 4 of the i.c. is not, as would normally be the case, returned to the positive supply rail. Pin 4 is

usually taken to the positive supply to ensure that the Reset transistor of Fig. 1 is cut off, whereupon this transistor has no effect on circuit operation.

The Reset transistor also has no effect if pin 4 of the i.c. is left open-circuit, because there is still no bias current applied to its base. If, on the other hand, pin 4 is connected to the negative supply rail the multivibrator oscillation stops, since the Reset transistor in the i.c. then turns the Discharge transistor hard on and the multivibrator capacitor cannot charge.

In an initial experiment, the author wired up the multivibrator and loudspeaker components, then took pin 4 of the i.c. to the slider of a potentiometer connected across the supply rails as shown in Fig. 3. It was found that the multivibrator operated for all potentials at pin 4 above 0.8 volt, and that it ceased functioning for all potentials at pin 4 below 0.8 volt. As the voltage at pin 4 was reduced, the multivibrator oscillation ceased abruptly at the 0.8 volt level. The oscillation commenced similarly abruptly as pin 4 voltage was raised past the 0.8 volt level. There was no hysteresis between the turning-off and turning-on voltage levels.

An RC timing control circuit which held pin 4 below 0.8 volt for 3½ minutes could be coupled directly to this pin, but it was felt that more reliable results would be given by employing a buffer transistor between the timing circuit and the i.c. This would then take up possible differences in Reset transistor base current between one i.c. and the next.

TIMING CIRCUIT

The timing circuit is quite simple and incorporates the components which are shown to the left of the i.c. in Fig. 2. When on-off toggle switch S1(a)(b) is in position 1, timing capacitor C1 is short-circuited via current

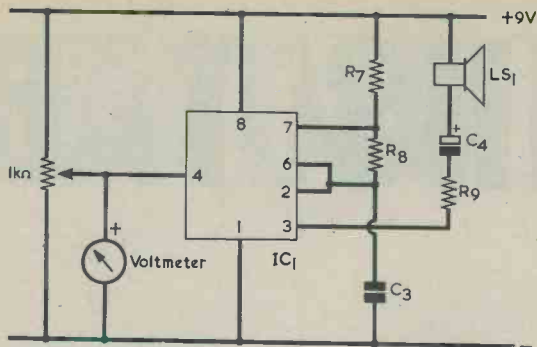


Fig. 3. An experimental circuit which demonstrates that the multivibrator can be stopped or started by the voltage applied to pin 4 of the i.c.

limiting resistor R2 and is consequently discharged. Setting S1(a)(b) to position 2 switches on the unit, and the short-circuit is taken off C1. A stabilized voltage of about 1.6 volts appears across the illuminated light-emitting diode LED1. This voltage is also applied, via the discharged C1, to the upper end of R3, whereupon current flows via R3 and R4 into the base of TR1, turning this transistor on. A small proportion of the current also flows in R5. TR1 collector now assumes a voltage slightly positive of the negative supply rail. Pin 4 of the i.c. is similarly held at a low potential, whereupon multivibrator oscillation is inhibited and there is no sound from the loudspeaker.

C1 commences to charge via R3, R4, R5 and the forward biased base-emitter junction of TR1. As C1 charges, the current drawn by TR1 base reduces and eventually becomes the small bias current needed to maintain pin 4 of the i.c. below the 0.8 volt level. The base current drawn by the internal Reset transistor in the i.c. also reduces when TR1 collector voltage rises, until the condition is reached where nearly all the charging current for C1 flows through R5. Finally, a stage is reached where the voltage at TR1 base falls below cut-off, whereupon there is no collector current from TR1 for the base of the Reset transistor in the i.c. The Reset transistor also cuts off, allowing the i.c. multivibrator to run and the tone to be reproduced by the loudspeaker.

In practice, the multivibrator oscillation does not commence at full level because there is a relatively gradual transition from the fully on to the fully off state in the i.c. Discharge transistor. The first few oscillations are at low level, but they soon rise to nearly full amplitude, after which the frequency of oscillation increases until the multivibrator settles down to its final frequency. The initial low multivibrator frequency is probably the result of shift in reference voltage levels in the i.c. resulting from the small remanent emitter current in the Reset transistor. The rise in frequency occurs over a 15 second period, which is reasonably short considering that it takes place after a 3½ minute timing run. The rise in frequency is, indeed, an advantage, because it draws attention to the tone from the loudspeaker.

TR1 collector cannot be connected direct to pin 4 of the i.c. because there would then be an unbroken amplifier chain consisting of TR1 and the Reset and Discharge transistors inside the integrated circuit. The

circuit could then go through a period of instability during the timing run if all three transistors happened to be in a state between the fully on and fully off conditions. R6 and C2 are included to break the amplifier chain. It is necessary for C2 to be a good quality component to ensure that there is negligible base current in the Reset transistor at the end of the timing run. It might appear desirable to have a high value resistor, of say 1MΩ, between pin 4 of the i.c. and the positive supply rail to ensure that pin 4 is taken further positive at the end of the timing run, and the author tried the effect of adding a resistor of this value between these two points. The resistor slightly reduced the length of the timing run but otherwise had no effect. Such a resistor can be added in other units built up to the circuit, if it is found that the Reset transistor in the i.c. does not cut off fully.

TIMING ADJUSTMENTS

The length of the timing period is adjusted with the aid of R4. Varying R4 offers two conflicting effects, and these may be more readily understood when it is remembered that the timing run commences with TR1 turned on and it ends when TR1 base voltage is so low that this transistor turns off. When R4 is set to insert zero resistance into circuit, the charging current for C1 is at its highest and it charges most quickly. At the same time, the highest proportion of the voltage between C1 negative plate and the negative supply rail is applied to TR1 base whereupon C1 has to charge to a relatively high voltage before the run terminates. Conversely, when R4 is set to insert maximum resistance into circuit the charging current for C1 is at its lowest level, but against this is the fact that the lowest proportion of the voltage on its negative plate is applied to TR1 base. Of these two effects the first has greater precedence, and the outcome is that R4 has a much lower control over the length of the timing run than a first examination of its value in conjunction with R3 would indicate. With the prototype, the timing run was about 60 seconds when R4 inserted minimum resistance and just over 4 minutes when R4 inserted maximum resistance. Intermediate settings of R4 produced intermediate timing periods.

When the unit has been completed, R4 should be set to insert minimum resistance and the timer operated over several timing runs. These will prove circuit operation without having to wait too long for each timing run to end, and will also help to 'form' C1 if this is a new component which has been in store for a long time. R4 is then experimentally adjusted until the desired timing period, which will normally be 3½ minutes, is given. This last process is a little tedious but is unavoidable. If it is found impossible to obtain a sufficiently long run with R4 in the maximum resistance position, a second capacitor may be connected across C1, as required. If it is needed, the second capacitor will probably only be of the order of 100 or 200μF.

The current drawn from the 9 volt supply by the author's unit was 15mA during the timing run, rising to 30mA at the end of the run with the multivibrator operating. Due to the relatively low currents in TR1 base and collector circuits, the unit should be housed in a box which gives reasonable protection against the ingress of steam and moisture from cooking operations. All fixed resistors are 10% in tolerance and, with the exception of R9, may be ¼ watt types. R9 should be rated at 1 watt. The variable resistor, R4, can be a small skeleton potentiometer. ■

MAINS TABLE

By A. FF

By taking advantage of two popular integrated circuits this receiver can be assembled with only a small quantity of discrete components. Reception is given on medium and long waves at an output power level considerably higher than that offered by the more conventional battery powered radio

WITH THE ADVENT OF THE PORTABLE TRANSISTOR RADIO and the stereo f.m. receiver, the popularity of the broadcast band mains table type of receiver has diminished considerably. This is perhaps a pity, because receivers of this type were capable of a better quality of reproduction than the smaller transistor portables which superseded them, and they also had a higher output power. Further, since they were mains powered their running costs were extremely low.

This article describes a simple medium and long wave receiver incorporating two integrated circuits which can be regarded as a modern equivalent of the earlier valve table receivers. Apart from the necessity of connecting to the mains, it is self-contained, and it is capable of a maximum r.m.s. output power of about 4 to 5 watts. The quality is good due to the wide bandwidth of the t.r.f. front end and the use of a high fidelity integrated circuit audio amplifier. The combined maximum total harmonic distortion for the two i.c.'s is 3%, and is typically somewhat less than this. An internal speaker of up to 8 by 5 in. can be used.

Full coverage of the medium and long wave band is given, and a number of Continental stations can be received at very good volume in addition to the usual B.B.C. transmissions. The construction of the set is simple and straightforward.

THE CIRCUIT

The circuit of the receiver is shown in Fig. 1. A basically similar circuit has been discussed earlier in this journal.*

* M. J. Darby, 'Radio Receivers Using Two Integrated Circuits', *Radio & Electronics Constructor*, December 1973 and January 1974.

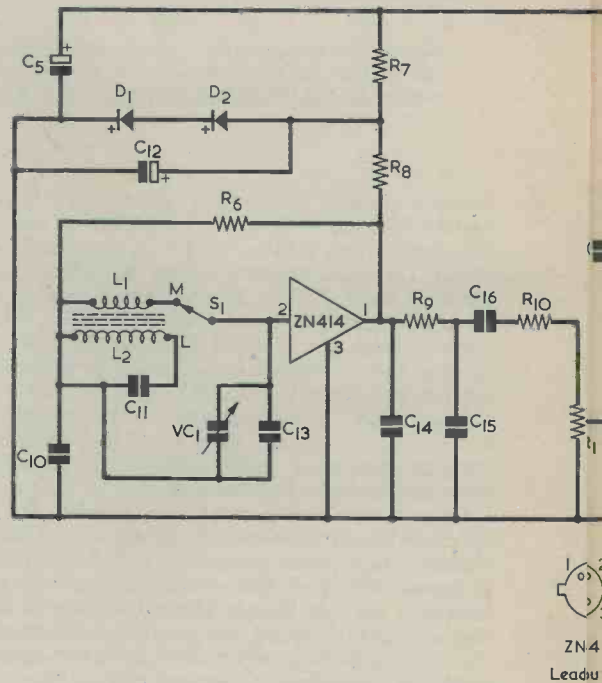


Fig. 1. The r.f. and a.f. stages of the mains table receiver on the printed circuit board.

The front end section is based on the popular ZN414 i.c., and this provides all the r.f. amplification in the receiver, together with the detection and a.g.c. functions. D1 and D2 are two forward biased silicon diodes and they provide a stabilized voltage for the ZN414 of about 1.3 volts. L1 and L2 are the medium and long wave aerial coils respectively, and are part of a ready-made ferrite aerial. S1 is the wavechange switch and VC1 the tuning capacitor. C11 and C13 are included in circuit to provide the correct frequency range.

The detected a.f. output of the ZN414 is taken from its pin 1. In order to avoid instability, any r.f. signal which is present here must be well filtered out before coupling the signal to the a.f. amplifier section. C14, R9, C15, R10 and C2 form a comprehensive r.f. filter. VR1 is the volume control.

A Sinclair Super IC-12 is employed as the a.f. pre-amplifier and output stage. The IC-12 consists basically of an operational amplifier having a Class AB power output stage. The audio signal from the volume control

AINS TABLE RADIO

By A. P. Roberts

ular
can
small
Re-
long
cond by
battery

DIO
the
min-
use
of
oles
her
red

ave
can
olve
ing
of a
tts.
the
ted
otal
is
of

A
his
ted
per

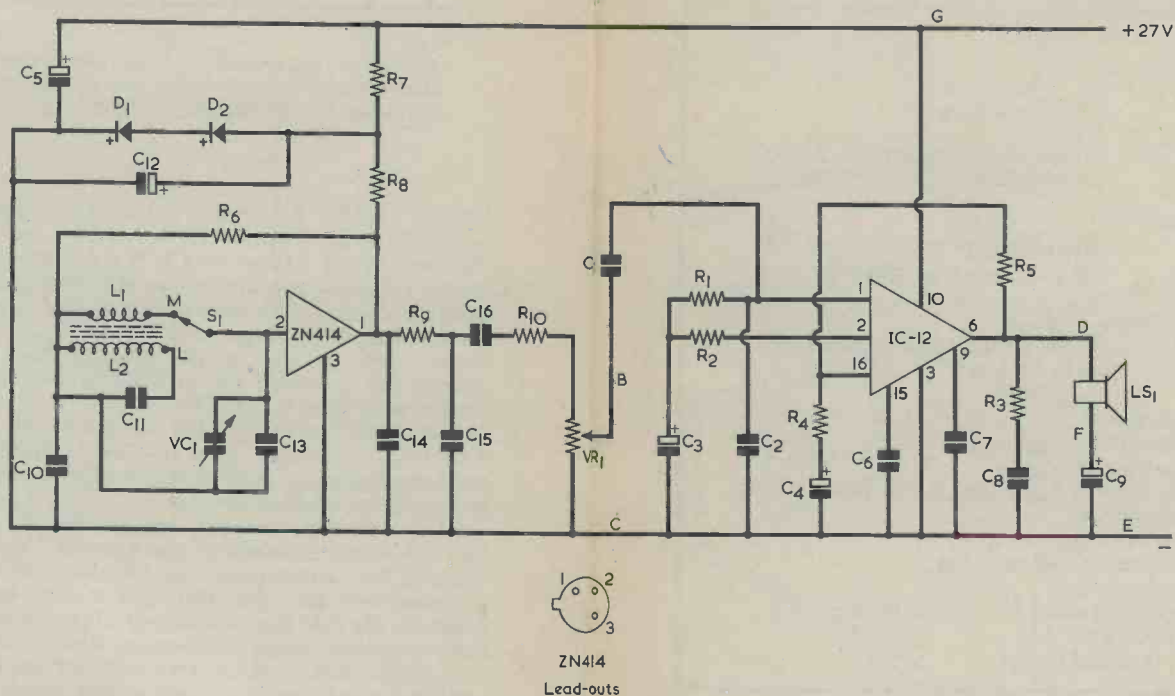


Fig. 1. The r.f. and a.f. stages of the mains table receiver. The letters 'B' to 'G' refer to connection points on the printed circuit board for the IC-12

The front end section is based on the popular ZN414 i.c., and this provides all the r.f. amplification in the receiver, together with the detection and a.g.c. functions. D1 and D2 are two forward biased silicon diodes and they provide a stabilized voltage for the ZN414 of about 1.3 volts. L1 and L2 are the medium and long wave aerial coils respectively, and are part of a ready-made ferrite aerial. S1 is the wavechange switch and VC1 the tuning capacitor. C11 and C13 are included in circuit to provide the correct frequency range.

The detected a.f. output of the ZN414 is taken from its pin 1. In order to avoid instability, any r.f. signal which is present here must be well filtered out before coupling the signal to the a.f. amplifier section. C14, R9, C15, R10 and C2 form a comprehensive r.f. filter. VR1 is the volume control.


A Sinclair Super IC-12 is employed as the a.f. pre-amplifier and output stage. The IC-12 consists basically of an operational amplifier having a Class AB power output stage. The audio signal from the volume control

is coupled to the non-inverting input of the i.c. at pin 6. Negative feedback is provided between the output at pin 6 and the inverting input at pin 16 via R4 and R5, values of which determine the overall gain of the amplifier. C6, C7, C8 and R3 are compensating components which maintain stable operation. R1 and R2 provide a suitable bias voltage for the non-inverting input from an internal potential divider. C3 and C4 provide supply decoupling.

The circuitry incorporating R1 to R5 and C1 to C9 that recommended by the manufacturers of the IC-12 and the resistor and capacitor suffix numbers in Fig. 1 agree with the suffix numbers in the Sinclair circuit diagram. This eases construction since the IC-12 is supplied on a printed circuit board whose non-copper side is marked out in terms of resistor and capacitor numbers. A few of the component values in Fig. 1 differ from those in the Sinclair circuit. The values shown are intended to meet present circuit requirements and the altered values are all within the permissible range of variation.

E RADIO

Roberts

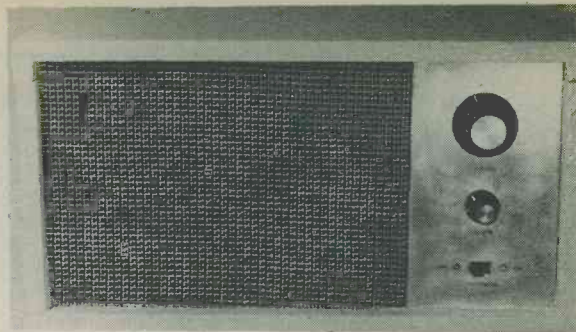


POWER SUPPLY UNIT

Fig. 2 shows the circuit of the simple unregulated power supply unit. The mains transformer has a 9-0-9 volt secondary, and the total secondary winding feeds an r.m.s. voltage of 18 volts to the bridge rectifier given by D3 to D6. The rectified output is then coupled to the smoothing circuit consisting of C17, R11 and C18, from which a low ripple output is available for the receiver. It will be noted that C5 of Fig. 1, which is on the IC-12 printed circuit board, is in parallel with C18. The power supply ensures that there is a low level of hum in the complete receiver.

Theoretically, the output from the power supply should not be able to rise above some 24 volts under no-load conditions, but in practice the voltage across C18 under quiescent loading is about 27 volts. This somewhat greater figure is presumably due to the fact that the mains transformer is wound to offer slightly higher than its nominal secondary voltage under low loading conditions. Since the absolute maximum voltage rating for the IC-12 is 28 volts, a mains transformer having a nominal secondary voltage greater than 18 volts must not be used. The transformer employed by the author was an Osmabet MT9V, which is available from Home Radio.

S2 is the on-off switch for the receiver, and this is ganged with the volume control, VR1.

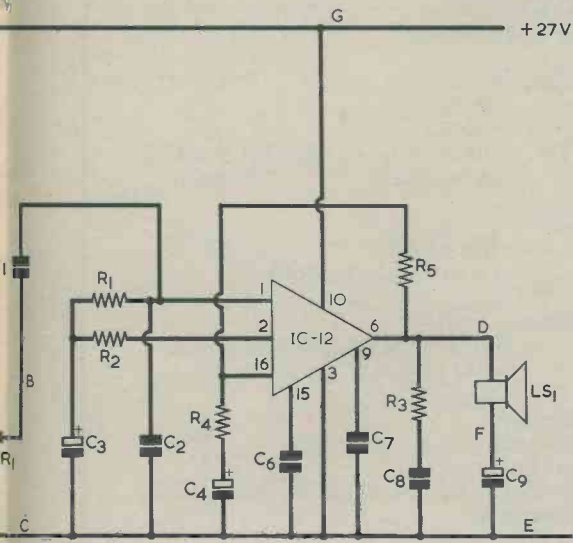The smoothing resistor, R11, is specified as 1Ω at 1 watt. It may be difficult to obtain this low value in 1 watt, whereupon it will be necessary to employ a 1Ω



receiver. The letters 'B' to 'G' refer to connection points on the board for the IC-12

is coupled to the non-inverting input of the i.c. at pin 1. Negative feedback is provided between the output at pin 6 and the inverting input at pin 16 via R4 and R5, the values of which determine the overall gain of the amplifier. C6, C7, C8 and R3 are compensating components which maintain stable operation. R1 and R2 provide a suitable bias voltage for the non-inverting input from an internal potential divider. C3 and C5 provide supply decoupling.

The circuitry incorporating R1 to R5 and C1 to C9 is that recommended by the manufacturers of the IC-12, and the resistor and capacitor suffix numbers in Fig. 1 agree with the suffix numbers in the Sinclair circuit. This eases construction since the IC-12 is supplied with a printed circuit board whose non-copper side is marked out in terms of resistor and capacitor numbers. A few of the component values in Fig. 1 differ from those in the Sinclair circuit. The values shown are intended to meet present circuit requirements and the altered values are all within the permissible range of variation.

MAY 1975

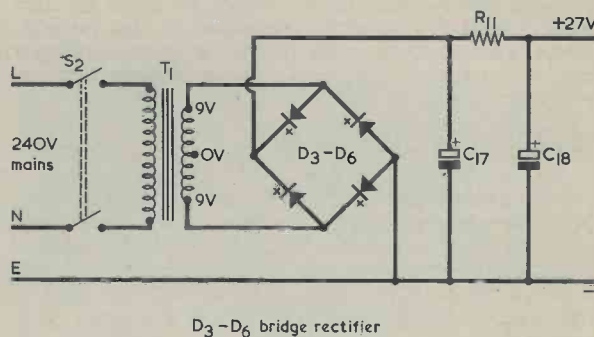


Fig. 2. The receiver circuit is completed by the power section, which is shown here

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10% unless otherwise stated)

R1	27k Ω
R2	150k Ω
R3	15 Ω
R4	100 Ω
R5	47k Ω
R6	100k Ω
R7	22k Ω
R8	560 Ω
R9	220 Ω
R10	820 Ω
R11	1 Ω 1 watt (see text)
VR1	5k Ω potentiometer, log, with switch
S2	

Capacitors

C1	0.22 μ F plastic foil
C2	82pF ceramic
C3	10 μ F electrolytic, 16 V. Wkg.
C4	100 μ F electrolytic, 15 V. Wkg.
C5	100 μ F electrolytic, 30 V. Wkg.
C6	0.001 μ F paper or plastic foil
C7	0.001 μ F paper or plastic foil
C8	0.01 μ F plastic foil
C9	1,000 μ F electrolytic, 16 V. Wkg.
C10	0.01 μ F plastic foil
C11	150pF silvered mica
C12	500 μ F electrolytic, 2.5 V. Wkg.
C13	15pF silvered mica
C14	0.047 μ F plastic foil
C15	0.047 μ F plastic foil
C16	0.47 μ F plastic foil, type C280 (Mullard)
C17	1,500 or 1,600 μ F electrolytic, 30 V. Wkg.
C18	1,500 or 1,600 μ F electrolytic, 30 V. Wkg.
VC1	300-360pF variable, air-spaced (see text)

Inductors

L1, L2	medium and long wave ferrite rod aerial type FRA. 1 (Denco)
T1	mains transformer, secondary 9-0-9V at 1A, type MT9V (Osmabet)

Integrated Circuits

ZN414	(Ferranti)
Super IC-12	(Sinclair)

Semiconductors

D1	1N4002
D2	1N4002
D3-D6	silicon bridge rectifier, P.I.V. 100V, 1A minimum

Switches

S1	slide switch
S2	d.p.s.t. toggle (part of VR1)

Loudspeaker

LS1	8-15 Ω impedance, 5 watt rating, up to 8 x 5 in.
-----	---

Miscellaneous

1 large knob
1 small knob
Perforated s.r.b.p. panel, 0.1 in. matrix (R.S. Components)
6-way tagstrip (see Fig. 4)
3-core mains lead and plug
$\frac{1}{2}$ in. chipboard
Aluminium sheet, 22 s.w.g. or thicker
Speaker fabric
$\frac{1}{2}$ x $\frac{1}{2}$ in. wood batten

resistor of a higher wattage rating. Alternatively, a number of higher value resistors could be connected in parallel, and suitable results would be given by four 3.9 Ω $\frac{1}{4}$ watt 5% resistors connected in this fashion. There is ample space in the receiver to accommodate a higher wattage resistor, or a number of lower wattage resistors in parallel.

CASE CONSTRUCTION

The case is constructed from $\frac{1}{2}$ in. (or 12 mm.) chipboard with an aluminium front panel, and constructional details are shown in Fig. 3. The photographs will also be helpful in illustrating how the case is assembled, and it should be noted that the centre and left hand area of the aluminium panel is covered on the front with speaker fabric.

There are two options open to the constructor in dealing with the front panel. In the prototype, the front panel was common with the moving vanes of VC1, since the capacitor frame was not insulated from the panel. The moving vanes of VC1 connect to the negative



A view giving the general layout of sections inside the case

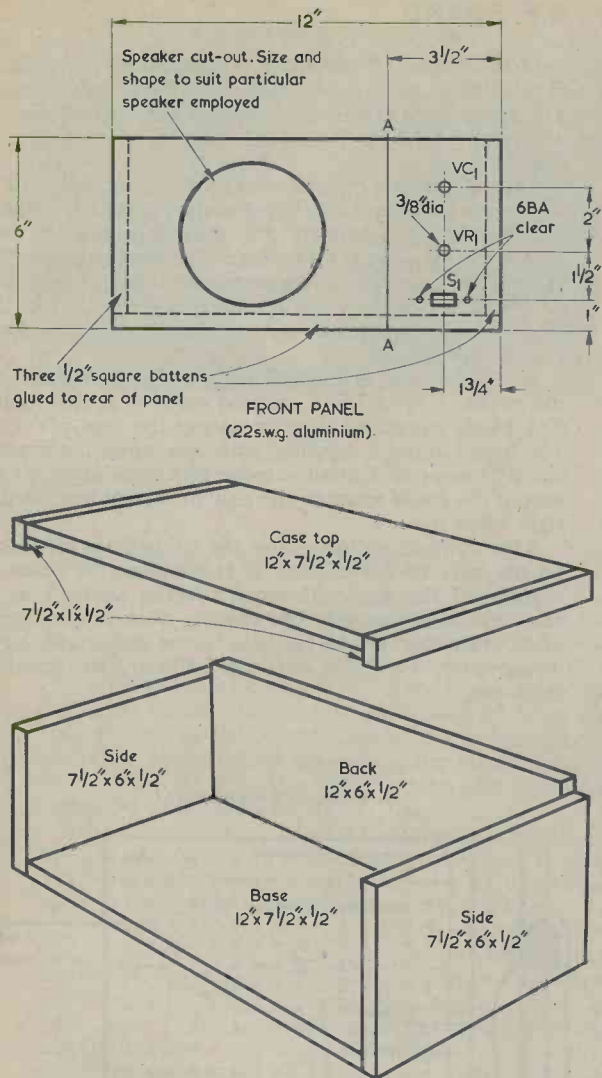


Fig. 3. Details of the front panel and the case. The area of the front panel to the left of line A-A is covered with speaker fabric

supply rail via C10. At the same time, the mains earth connects to the negative supply rail also, with the result that the panel was not connected direct to the mains earth but was instead connected thereto by way of C10. This arrangement worked quite adequately and there were no problems due to hand capacitance or similar effects.

Although the whole receiver circuits are isolated from the mains by the mains transformer, it may be considered more desirable by some readers to have the front panel connected to the mains earth. When this is done it is then necessary to devise an insulated mounting for VC1 which will ensure that its moving vanes are insulated from the panel. This second approach will result in increased protection against accidental shock.

The first process in making the case consists of cutting out and drilling the front panel. The prototype employ-

ed 22 s.w.g. aluminium sheet, but a slightly thicker gauge can be used if this is more readily available. The rectangular cut-out for S1 can be made by first drilling a central $\frac{1}{4}$ in. hole, and then filing this out to the required shape. The actual dimensions required depend upon the particular switch which is employed. The speaker cut-out for the prototype was made with a fretsaw.

A $\frac{3}{8}$ in. hole is required for VR1. Only the centre of VC1 spindle is dimensioned in Fig. 3, as the hole or holes required here depend upon the particular capacitor to be employed and whether or not it is to have an insulated mounting. The precise capacitance of VC1 is not critical, and any air-spaced component with a value between 300 and 360pF may be employed. If necessary, a 2-gang capacitor may be used with its two sets of fixed vanes connected together. Thus a 2-gang 176+176pF capacitor, giving a total of 352pF, could be used. There is adequate space for any capacitor of reasonable size.

As already mentioned, the centre and left hand side of the panel are covered with a piece of speaker fabric. It is best to cut this a little too large so that it can be left overhanging at the top, bottom and left hand side. The fabric can be secured with any general purpose household adhesive, and when this has dried the overhanging edges of the fabric are trimmed with scissors. Three battens of $\frac{1}{2}$ by $\frac{1}{2}$ in. cross-section are then glued to the rear of the panel, as indicated in Fig. 3.

The chipboard sides and base may next be cut out and assembled to the front panel. The panel is set back by about $\frac{3}{8}$ in., as indicated in the photographs. Any good quality woodworking glue may be employed here. The case back, and the three pieces for the lid, may also be cut out at this stage, but they are not assembled yet. There is greater access to the interior of the case during construction if the back is fitted later.

P.S.U. CONSTRUCTION

The internal layout of the receiver can be seen from the photographs. Fitted to the base with woodscrews are, from left to right, the mains transformer T1, the power supply components on a tagstrip, the printed circuit board for the IC-12 and a perforated board for the ZN414 section. The ferrite rod aerial is at the back.

With the exception of T1 and S2, all the power supply unit components of Fig. 2 are wired up on a 6-way tag-



Close-up view of the mains transformer and power supply components

FRONT OF RECEIVER

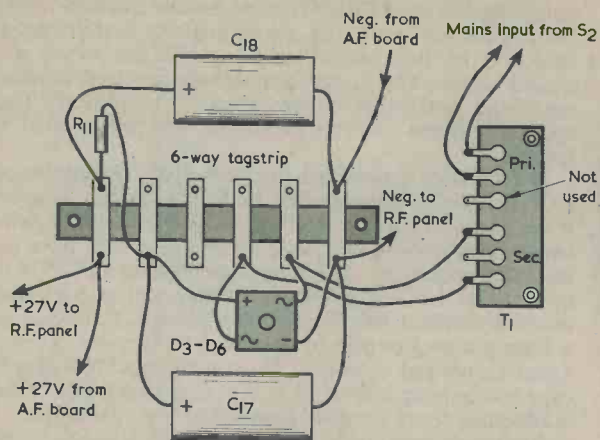


Fig. 4. The wiring of the power supply section

strip having a mounting hole at each end. The necessary connections are illustrated in Fig. 4. The tagstrip should be wired up before it is mounted on the base of the cabinet. T1 and the tagstrip are each secured with two woodscrews. Small spacing washers are fitted over the woodscrews under the tagstrip to keep the tag undersides clear of the chipboard and to prevent strain on the strip. The connections to T1 primary are made later.

Next, VC1, VR1 and S1 are mounted on the front panel. The speaker is glued in position behind its cut-out, using a powerful epoxy resin adhesive such as Araldite.

AUDIO STAGE

The IC-12 components are next assembled on its printed circuit board, and these provide the audio stage. As stated earlier, the component reference numbers here correspond with those in Fig. 1. It is therefore merely necessary to mount and connect the components in their marked positions.

The polarities of electrolytic capacitors are indicated, except for C3 which has its positive end towards R5 and its negative end towards the i.c. Be sure to connect the i.c. right way round. A dot after the legend 'Sinclair Super IC-12' on the heatsink indicates pin 1 of the i.c., and the position of pin 1 is marked on the printed circuit board. Alternatively, an identification groove on the plastic body of the i.c. indicates the pin 1 end.

Before the printed circuit board is mounted in position the following connections need to be made to the points indicated by the letters. The wiring is carried out with suitable lengths of insulated lead. Points 'D' and 'F' on the board connect to the speaker tags. Point 'G' connects to the positive output of the power supply unit, and point 'E' to the negative output of the supply unit. Point 'B' connects to the slider and point 'C' to the earthy tag (minimum volume end) of VR1. The printed circuit board is then fitted to the cabinet base, with small spacing washers underneath. These should be thick enough to ensure that there is no strain on the board when it is screwed in position.

612

R.F. BOARD

Most of the r.f. circuitry is contained on a plain perforated panel of 0.1 in. matrix having 16 by 27 holes. The component layout of this panel and the remaining wiring of the r.f. section, apart from C13, are shown in Fig. 5.

The panel is cut from any larger piece by means of a Junior hacksaw, and the two mounting holes are drilled. The various components are then mounted in the appropriate positions. Their lead-outs are bent over flat against the underside of the panel and soldered together to conform with the wiring details given in Fig. 5. Wiring under the panel is represented by the broken lines in the diagram.

When the panel is finished it is wired up to the rest of the circuit. C11 and C13 are also wired in at this stage, C13 being connected directly across the tags of VC1. The ferrite aerial is supplied with two mounting brackets. By means of 4 small woodscrews these are used to mount the aerial towards the rear of the cabinet on the right hand side.

After completing the wiring, the r.f. panel is mounted on the base of the cabinet. It is necessary to space it slightly off the base with small spacing washers, as it may otherwise fracture. The spacing washers employed in securing the various sections to the chipboard may, incidentally, be 4BA nuts, or similar, of suitable thickness.

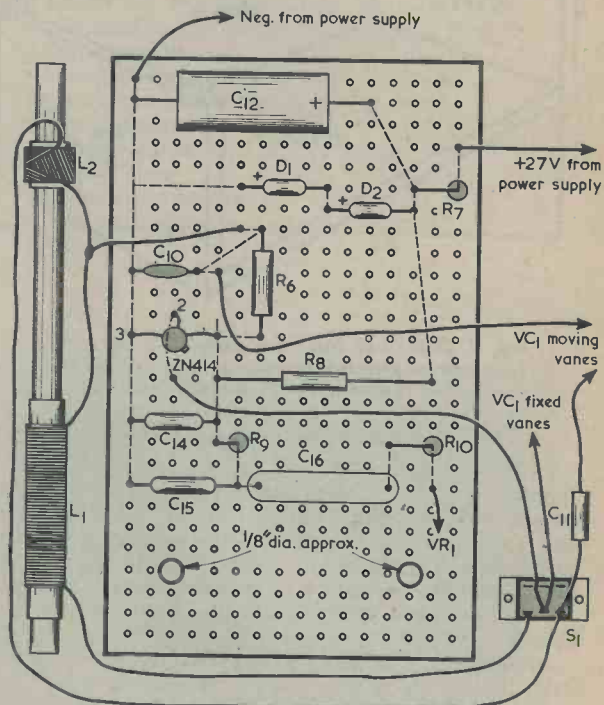


Fig. 5. Layout and wiring on the r.f. panel. For convenience of presentation, the ferrite aerial and switch S1 are shown on either side of the panel. In the actual receiver layout, C12 is towards the front of the receiver and the ferrite aerial is behind it



The a.f. and r.f. boards. The orientation of the a.f. board can be readily observed here

COMPLETING THE RECEIVER

The mains lead may next be connected. Its live (brown) and neutral (blue) leads are soldered to S2, and its earth (green-yellow) lead to the earthy tag of VR1. This is the tag to which point 'C' of the IC-12 board was connected earlier. If the tag positioning of S2 is unknown, identify the correct tags with an ohmmeter or continuity tester before connecting the mains wires. A short length of twin flex then couples the remaining tags of S2 to the primary of T1.

If VC1 is insulated from the aluminium panel, the panel is also connected to the mains earth. The connection is made from the earthy tag of VR1 to a solder tag held under one of the mounting nuts of S1.

Next drill a hole in the case back to allow the mains lead to pass through, then glue the back in position. Preferably, the mains lead should be anchored inside the case by a plastic clamp screwed to the adjacent side. The three pieces comprising the top are next glued together, and the receiver finished by painting the chipboard or covering it with a self-adhesive plastic material such as Fablon. As a finishing touch, legends taken from 'Panel Signs' Set No. 4 may be affixed to the front panel. The prototype had the legends 'Tuning', 'Volume' and 'Waveband' below VC1, VR1 and S1 respectively. The legend 'Off' was affixed at the appropriate point alongside VR1 knob, and 'MW' and 'LW' were positioned on either side of S1.

TESTING AND ADJUSTMENT


Before turning the receiver on, check all the wiring thoroughly, paying particular attention to the power supply section. Confirm also that the polarities of D1 and D2 are correct. If either or both of these is connected wrong way round, the ZN414 will probably be destroyed.

Having fully examined the wiring, the receiver can be switched on and checked on both bands. The only adjustment that is required is to slide the two aerial coils along the ferrite rod to find a setting which gives correct frequency coverage. When the required settings have been found, the coils may be taped to the rod to maintain them in position. The receiver is then ready for use.

RADIO & ELECTRONICS CONSTRUCTOR

JUNE ISSUE FEATURES INTEGRATED CIRCUIT SUPERHET

Part 1

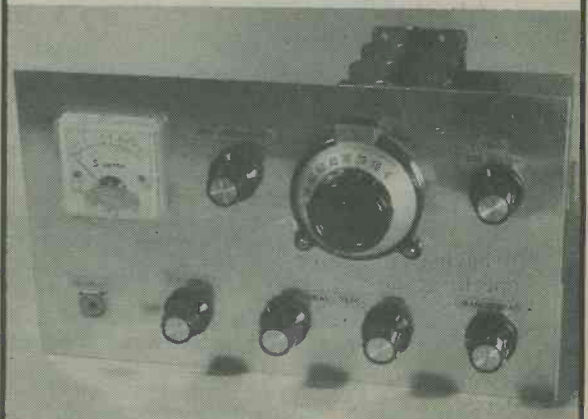

Covering the standard medium wave band together with two short wave bands from 180 to 20 metres, this superhet receiver is designed around the R.C.A. integrated circuit type CA3088E. It may be made up either for headphone or loudspeaker reception. The concluding second article will appear in the following issue.



SOFT AUDIO LIMITER

Our contributor discusses two low level voltage limiting circuits, one of which gives hard limiting whilst the other provides soft limiting.

ALL THE USUAL FEATURES PLUS MANY OTHER ARTICLES


PRICE 30p

Copies may also be obtained direct from the Publishers, 38p including postage. Published by Data Publications Ltd., 57 Maida Vale, London W9 1SN.

RADIO & ELECTRONICS CONSTRUCTOR

SHORT WAVE NEWS

FOR DX LISTENERS

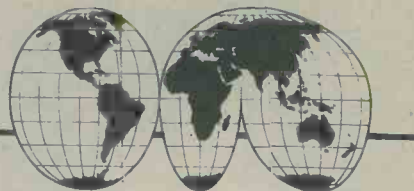

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

In the last issue, mention was made of some Asian-based clandestine transmitters, the promise also being made that some non-political European clandestines would be listed - here they are.

All of these stations operate just above the 6MHz band and most of them are to be heard in full cry (and that just about describes the noises they emit) on Sunday mornings. Programme content is mostly of pop records.

Radio Passad 6210 operates from 1000 to 1200.

BBMS 6210 from 1100 to 1300 and from 1400 to 1530.

Radio Freedom 6220 from 0900 to 1000.

Thames Radio International 6225 schedule not known.

West Coast Radio 6225 from 1000 to 1030.

Radio Victoria International 6225, from 1140 to 1205 and from 1935 to 2005.

Radio London 6230 from 1500, sign-off time not known.

Radio King Kong 6230 from 1000 to 1030.

Jesus Radio 6234 from 1100 to 1200.

Time Radio 6235 from 1000 to 1100.

Tower Radio 6240, Sundays only.

ABC-Europe 6250 0800 to 1300.

United Radio Europe 6255 from 1030, sign-off time not known.

Radio Star 6260 schedule not known.

I am indebted to Poul Foged of the Danish Short Wave Clubs International writing in his Pop and Pirate Radio page in their journal "Short Wave News" January issue, for the above information.

But we haven't finished with the clandestines yet; how about another Asian-based transmitter - "Voice of the Revolutionary Party for Reunification". This one operates mostly in Korean, so you can easily guess what it is all about and the transmissions emanate (what - no surprise!) from North Korea. Probably the best chances of hearing this one, according to the time of year, would be from around 1500 to 1600 and from 2200 to 2300 when they are in Korean to South Korea and from 2300 to 2330 when they are in English, all on 4557.

Coming nearer home, try the Voice of the Communist Party of Turkey, "Tuerkiye Komunist Partisinin Sesi", which may be heard on Tuesday and Sunday from 0810 to 0840 on 6200.

Or, how about the PLO "Voice of Palestine, Voice of

the Palestine Revolution", transmitted by Radio Baghdad from 1600 to 1635 on 7300.

Then we have "Voice of Palestine", which can be heard in Arabic from 1200 to 1300 on 6662.

One we have mentioned from time to time is the "Voice of the People from the Heart of the Arabian Peninsular". This Arabic-language, anti-Saudi station has recently been reported on 11800 from 1200 to 1230.

A new one is "Phnom-Penh National United Front of Cambodia" which broadcasts in Cambodian anti-government material in the same manner as "Voice of the National United Front of Cambodia" from a location thought to be in North Vietnam. For the Phnom-Penh station, listen on 7287, the schedule being from 0100 to 0130, 0700 to 0730 and from 1300 to 1330.

The VNUFC (Voice of the United Front of Cambodia) is reported currently radiating on variable frequencies centred on 4675, 6142, 7015, 9985, 10080, 10120 and on 12005 from 0001 to 0100, from 0100 to 0200, from 0400 to 0500, from 1030 to 1130, from 1130 to 1230 and from 1330 to 1430.

From Zambia there is a broadcast presented by the African National Congress (ANC) under the title "Radio Freedom" on 9580 from 1700 to 1800 in English, Afrikaans and vernaculars, this being radiated from the Radio Zambia studios at Lusaka.

CURRENT SCHEDULES

● TURKEY

Radio Ankara - "The Voice of Turkey" has an English transmission directed to Europe, North Africa and North America from 2200 to 0115 on 11880. Ankara also operates a service in Turkish for Turks abroad from 0400 to 0600, 0900 to 1330 and from 1630 to 2100 on 11880, also from 0400 to 2200 on 9515.

● MALAYSIA

The "Voice of Malaysia", Kuala Lumpur, broadcasts in English to South East Asia in the External Service from 0625 to 0855 on 6173 and 11900, also on 15280 from 0830. Kuala Lumpur can also often be heard on 15295 from 1530 to 1630 when radiating in Arabic, listen for the tuning signal prior to 1530, a series of chimes repeated.

● **SRI LANKA**

A broadcast in English from Colombo is beamed to Europe from 1900 to 2030 on 9720, 11800 and on 15120. See also under Around the Dial.

● **NIGERIA**

The "Voice of Nigeria", Lagos, has an English programme from 1800 to 1930 on 7275, 11710 and on 15120, see also under Around the Dial.

● **CHINA**

Radio Peking has minority languages schedules in the domestic service, these currently being as follows - in Kazakh from 0130 to 0225 and from 1400 to 1455 on 6620 and on 8565; relayed by Urumchi on 4970 and on 5440. In Korean from 2130 to 2225 on 4620 and 6550; from 0400 to 0455 on 6560 and 8260; from 1000 to 1055 on 4620 and 6560. In Tibetan from 2330 to 0025 on 6620 and 7360; from 1100 to 1155 on 8565 and on 9820, relayed by Lhasa on 4035, 9490 and on 9655. In Uigher from 1300 to 1355 and from 0030 to 0125 on 6620 and 8565, relayed by Urumchi on 4110 and on 7050.

● **SOUTH YEMEN**

From Aden, the "Radio of the People's Democratic Republic of Yemen" transmits a Home Service in Arabic from transmitters at al-Hiswah from 0300 to 0530 on 5060 and 7190; from 1100 to 1500 on 5060 and 11770; from 1500 to 1730 on 5060, 7190 and on 11770; from 1730 to 1900 on 5060, 5970 and on 7190 and from 1900 to 2200 on 5060.

● **ARGENTINA**

"Radiodifusion Argentine al Exterior" (RAE), Buenos Aires, beams a programme in English to Europe (except Saturdays and Sundays) from 2100 to 2200 and from 2300 to 2355 on 11710.

● **CHILE**

"Radio Nacional - La Voz de Chile", Santiago, operates a service in English, the evening transmission of which is from 2210 to 2230 on 11810 and on 15150. Other transmissions in English are from 0030 to 0050, 0230 to 0250 and 0430 to 0450 on the same channels.

● **SPAIN**

The "Spanish National Radio" (RNE), Madrid, presents a service in English to North America from 0100 to 0345 on 6065 and 11925.

● **SPANISH SAHARA**

"Radio Sahara", Al'Uyun, has recently been broadcasting test transmissions on 6095 from 1945 to 2215 in Arabic with Spanish announcements after 2200, also with test transmissions on 11805 from 0800 to 1800.

● **EGYPT**

Radio Cairo broadcasts to Africa in English in the "Voice of Africa" service from 1715 to 1830 on 17890 and from 2030 to 2200 on 17725.

AROUND THE DIAL

● **NORTH KOREA**

Radio Pyongyang at 1210 when radiating a commentary in English to South East Asia, the schedule of this being from 1200 to 1440, logged on 9370 but the transmission is also in parallel on 3560, 7580 and 15630.

MAY 1975

● **INDONESIA**

Medan on 4764 at 1504 at which time a talk in Malindo was being radiated and just audible under some utility interference.

● **INDIA**

AIR Delhi on 3925 at 1610, OM with a talk in English about the recent war with Pakistan and the aftermath.

● **NEPAL**

Radio Nepal, Kathmandu, at 1622 on 3425, OM with a talk and announcements in Nepali.

● **MALDIVES**

Radio Maldives on 4740 at 1643, light music programme with OM announcer in English.

● **GHANA**

Ejura on 3350 at 1936, colourful local music complete with female chorus. This is the National Service the evening transmission of which is from 1600 to 2300.

● **CLANDESTINE - 1**

Azad Kashmir on 3380 (formerly on 3915) at 1616, OM with talk in a local dialect. Azad (Free) Kashmir programmes are thought to be radiated via the facilities of Radio Pakistan.

● **MALAYSIA**

BBC Tebrau on 3915 at 1608, OM with a newscast in English for S.E. Asia.

● **AUSTRALIA**

ABC Brisbane on 4920 at 0800, 6 pips, short march then OM with "Here is the National News".

● **CLANDESTINE - 2**

Radio Pathet Lao on a measured 6212.5 at 1537, YL in Lao, local music and songs at 1543 then YL in Lao again until sign-off at 1600.

● **SOUTH AFRICA**

Johannesburg on 9525 at 2100, identification and a newscast in English, mainly about African affairs, directed to West Africa and Europe.

● **U.S.S.R.**

The "Voice of Armenia", Yerevan, on 4990 at 1513, YL with identification in Arabic in a programme for the Arabic world from 1500 to 1530, also in parallel on 6085.

● **PORTUGAL**

Radio Portugal, Lisbon, on 6025 at 2230 with identification and schedule announcements, also in parallel on 9740.

● **NIGERIA**

"Voice of Nigeria", Lagos, on 15120 at 1830 with station identification and a newscast in English.

● **SRI LANKA**

Colombo on 11800 at 1915 with a newscast in English during a test transmission directed to Europe and the U.K., announced in parallel on 9720 and 15120.

● **MEXICO**

Radio Fiesta on 15110 at 2300 with identification in Spanish (formerly Radio Tricolour), announcements then into local pop music programme.

VERSATILE VERTICAL FOR TOP BAND

By V. S. Evans

A neat aerial design primarily intended
for mobile working on Top Band



The smart appearance of the Top Band vertical, as fitted to the author's car. It can be readily removed and replaced by a broadcast aerial when not required

THE LOADED VERTICAL AERIAL FOR THE 160 METRE BAND has been around for a very long time. Many are the types and methods of construction, these varying from really Heath Robinson assemblies to sophisticated commercial models. A varying assortment can be seen adorning participating vehicles at almost any Amateur Mobile Rally, including the 6 ft. fibre glass whip waving around wildly in the breeze and the gruesome 2 in. diameter steel scaffold pole secured in the bumper region with hefty steel brackets.

The author has evolved what could become a standard method of construction for the amateur, using readily available materials and parts. The result is neat and aesthetically pleasing. The overall length of the basic antenna is about 4½ ft., and it can be employed for mobile or fixed station use. It is possible that with a modification to the loading coil the system of construction could be applied to other frequency bands, although for higher power than that permitted for 160 metres in the U.K. the plastic tubing used may need to be changed. The coil would also have to be wound with thicker wire.

Various methods of mounting the aerial will be suggested, but in this respect it is left to the constructor to decide his own requirements.

CONSTRUCTION

The main materials used are round wood dowelling, white plastic conduit tubing, aluminium or aluminium alloy tubing, and Jubilee hose clips. Also required are enamelled copper wire for the coil, a roll of plastic insulating tape and a tube of conductive grease. The tools needed are of the simplest, and consist of a screwdriver, hammer, hand drill and small hacksaw.

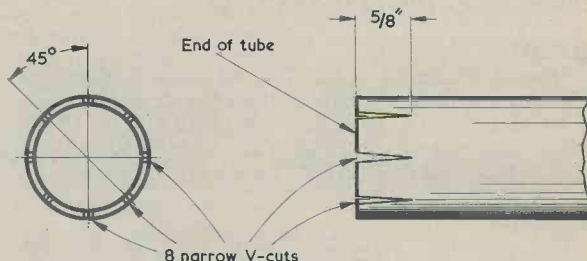


Fig. 1. Where necessary, tubing ends are given 8 V-cuts in the manner shown here

Where necessary, tube ends, both aluminium and plastic, have 8 narrow V-cuts made in them as illustrated in Fig. 1. A tube end prepared in this manner then has a hose clip placed over it, whereupon the end is capable of being tightened up securely onto a slightly thinner tube inserted inside it.

The aerial consists basically of a lower and upper aluminium tube with the loading coil between them. At the top of the upper tube is a short telescopic section, this consisting of a third aluminium tube which can be moved in or out to finally tune the aerial. This third tube will be referred to as the 'top tube'.

First obtain a 21 in. length of ½ in. diameter round wood dowelling. Give it two coats of varnish. When dry, it is wrapped over its length with plastic insulating tape laid edge to edge, i.e. not overlapping.

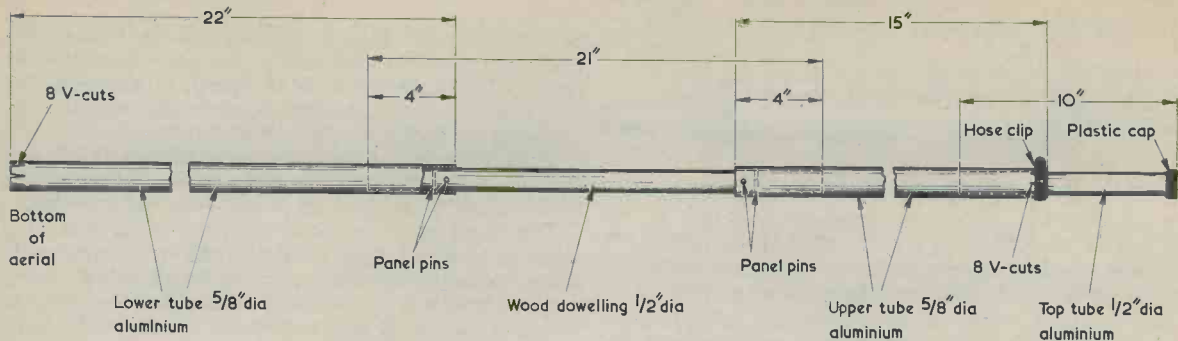


Fig. 2. The three aluminium tubes and the wood dowelling which form the basic parts of the aerial. For convenience, thicknesses are drawn twice scale size

The lower tube consists of a 22 in. length of $\frac{3}{8}$ in. o.d. aluminium tube, and the upper tube consists of a 15 in. length of the same tube. The lower tube has 8 V-cuts at its lower end, as in Fig. 1. These enable it to be fastened later to a $\frac{1}{2}$ in. mounting rod or tube. The upper end of the upper tube also has 8 V-cuts. These enable the upper end to be clamped tight around the top tube.

The upper end of the lower tube is passed over the $\frac{1}{2}$ in. wood dowelling to a depth of 4 in., as in Fig. 2. Two small holes are drilled through the tube and dowelling at right angles to each other, one hole being $\frac{1}{4}$ in. from the end of the tube and the other $\frac{1}{2}$ in. from the end of the tube. Panel pins are driven through the holes and cut off flush both sides. They should be a tight fit.

The lower end of the upper tube is passed over the dowelling for 4 in. also. It is secured to the dowelling with panel pins in exactly the same manner. The top tube consists of 10 in. of $\frac{1}{2}$ in. o.d. aluminium tube and it is inserted into the upper end of the upper tube to any depth. A hose clip around the upper end of the upper tube is tightened to hold the top tube firm. A plastic cap, cork or rubber bung is fitted to the top of the top tube to keep out rain. The assembly should now be as shown in Fig. 2. For ease of presentation all tube diameters in Figs. 2 to 5 are shown approximately twice as wide as they would be if drawn to scale.

both ends. It is passed over the coil former, positioned centrally and lightly clamped at both ends with hose clips, as in Fig. 4.

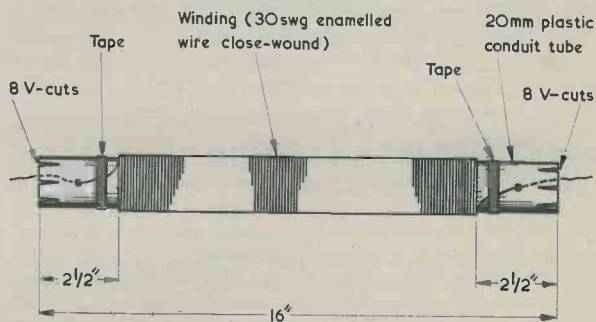


Fig. 3. The central loading coil wound on its former

LOADING COIL

The former for the loading coil consists of a 16 in. length of 20mm. plastic conduit tube. (20 mm. is equal to 0.787 in.) It has 8 V-cuts at both ends. The winding starts $2\frac{1}{2}$ in. from one end and finishes $2\frac{1}{2}$ in. from the other end. The wire is 30 s.w.g. enamelled copper, and is close-wound in a single layer with all turns touching and none overlapping. A 2 oz. reel will provide sufficient wire. Bands of insulating tape secure the winding ends, and there should be 4 in. free wire at both ends for connections. The enamel is cleaned off the wire ends and these should be tinned over most of their length. Small holes are drilled in the plastic tube near the coil ends and the wires are passed through these to the inside and brought out. Do not be tempted to varnish the coil. It is shown in completed form in Fig. 3.

Next to be prepared is the protective cover for the coil. This consists of $14\frac{1}{2}$ in. of 25 mm. plastic conduit tube. (25 mm. is equal to 0.984 in.) It has 8 V-cuts at

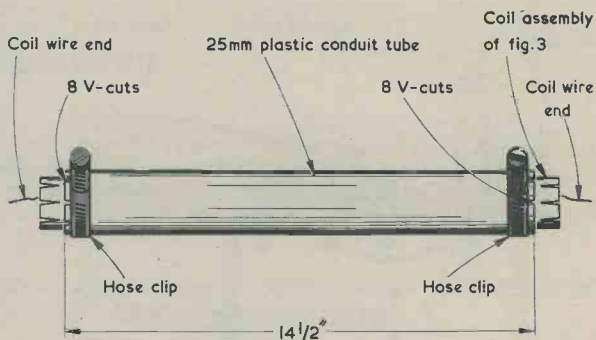


Fig. 4. A protective cover is fitted over the loading coil

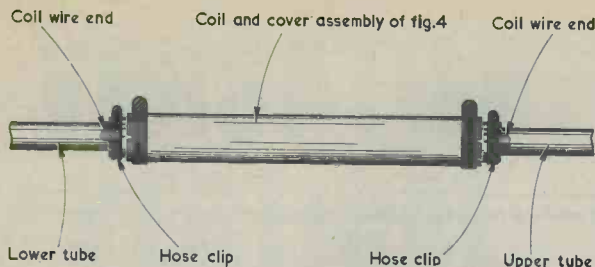


Fig. 5. The loading coil and cover assembly mounted centrally over the wood dowelling

A hose clip should be loosely placed over each end of the coil former, after which the completed assembly of Fig. 4 is passed over the lower end of the assembly of Fig. 2 and continued up until it lies centrally over the wooden dowelling, as illustrated in Fig. 5. Positioning is such that the lower and upper tubes each penetrate the coil former by $1\frac{1}{2}$ in. Indeed, the lower and upper tubes can be previously marked $1\frac{1}{2}$ in. from their ends as a guide. Before finally securing the coil former move it slightly to one side and then to the other to allow the sections of the aluminium tubes which will be covered to be smeared with conductive grease. This is Electro-lube 2G-X (Home Radio). The hose clips at the ends of the former are tightened, and it should be noted that the coil wire ends pass out from the inside of the former and are then folded back and clamped under these hose clips. Also tighten the two hose clips which secure the protective cover over the coil. Apart from providing a means of mounting, the aerial is now complete.

EXPERIMENTAL MOUNTING

For testing and experimental purposes a base mount may be made with a cheap G-cramp. A piece of $\frac{1}{2}$ in. o.d. aluminium tube 2 in. long is also required, together with a $2\frac{1}{2}$ in. bolt, nut and $\frac{1}{2}$ in. washer. The bolt head should not be wider than $\frac{1}{2}$ in. The G-cramp is drilled near one end with a clearance hole for the bolt. Three further holes are drilled to take a block of insulating material on which is mounted a coaxial socket. The insulating block may be wood, Perspex or any other suitable material, and the complete mounting is illustrated in Fig. 6. The coaxial socket is secured with

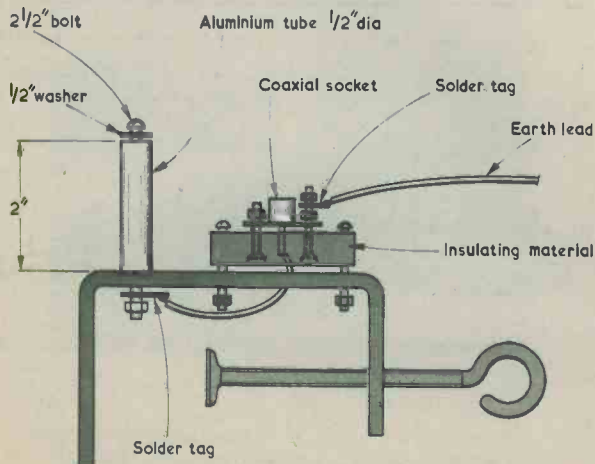


Fig. 6. A simple temporary mounting for the aerial

two countersunk bolts in suitably recessed holes, thus ensuring that there is no contact between the outer connector of the socket and the G-cramp. A short length of wire connects the centre connector of the socket to the cramp at the end of the $2\frac{1}{2}$ in. bolt.

The bottom end of the lower aerial tube can be passed over the 2 in. length of $\frac{1}{2}$ in. tube on the cramp, and is then secured by a hose clip passed over the 8 V-cuts.

The G-cramp is common with the aerial and so it must be clamped to an insulated object. Alternatively, some insulating material, such as tough rubber sheet, must be interposed between the cramp and the object to which it clamps. A lead connected to one of the bolts securing the coaxial socket is taken to a ground rod or other suitable earth.

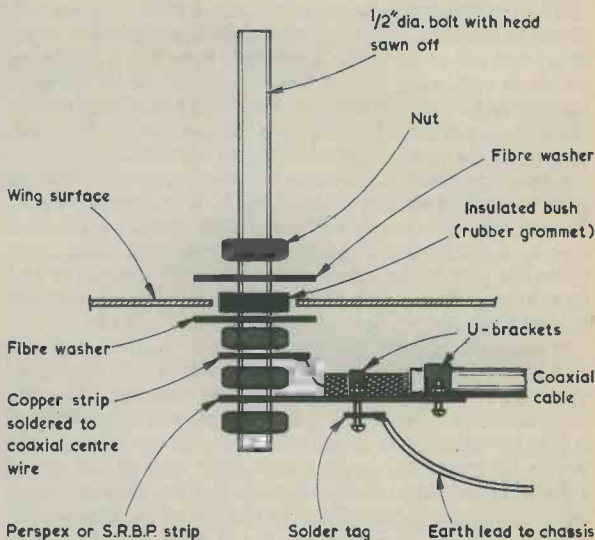


Fig. 7. A mounting which may be installed at a car wing

MOBILE WING MOUNTING

A suggested car wing mounting is shown in Fig. 7. Rear wing mounting is less likely to incur trouble with electrical interference from a forward engine compartment, and vice versa. As the aerial angle cannot be adjusted with this arrangement, the surface chosen for the mount must be flat and horizontal if the aerial is to be vertical. The author obtained a $\frac{1}{2}$ in. diameter 6 in. long brass bolt from a boat-builder for his version of the mounting, this having the head sawn off. A cadmium plated or Sherardized bolt would also be acceptable.

An advantage with this mounting is that a simple aluminium tube acting as an aerial for broadcast reception can be fitted in place of the 160 metre aerial when the latter is not required.

BUMPER MOUNTING

Bumper mounting involves the use of a bottom extension tube to bring the loading coil above the general car body area. A piece of $\frac{3}{4}$ in. o.d. aluminium tube with 8 V-cuts at the top is needed, and this can be some 3 to 4 ft. in length. For insulation, a tight fitting rubber hose is passed over it at its lower end. As will be seen from Fig. 8, a metal plate drilled with four holes

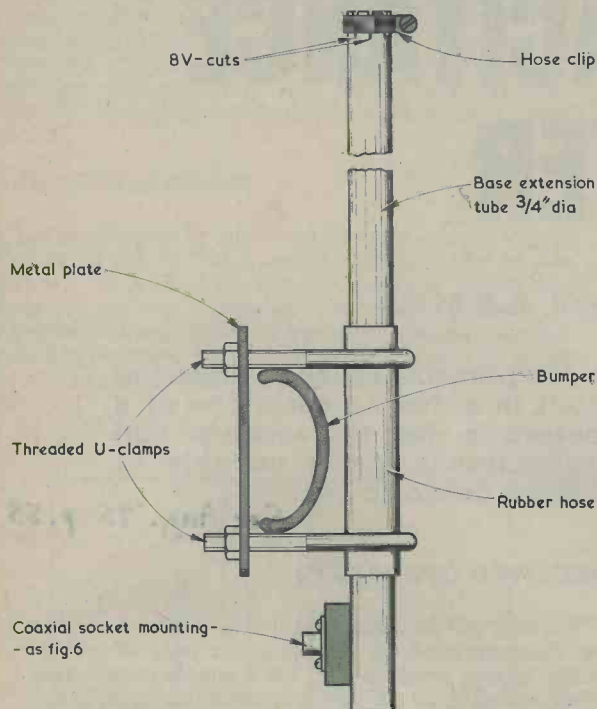


Fig. 8. Mounting the aerial to a car bumper

and two threaded U-clamps are required. The clamps can be obtained as exhaust brackets or television aerial fittings. The lower end of the aerial is inserted in the

$\frac{3}{4}$ in. tube and the hose clip at the top of this tube is then tightened.

A coaxial socket and insulating block similar to that employed in Fig. 6 is fitted to the bottom of the extension tube. This arrangement is more suitable for 'static mobile' operating than for road travelling.

FIXED STATION MOUNTING

A similar arrangement to the bumper mount can be adapted for attachment to a wooden mast. In this case the coaxial socket earth lead will be taken to earth at a copper ground rod, buried metal plate or other suitable earth point. A gable end of the house, chimney stack or even the garage roof can be utilised. In these instances, television fittings could be put to good use.

USING THE AERIAL

Having set up the aerial system, a coaxial feed line is taken from its coaxial socket to the transmitter. The first operation is to locate a point of resonance with the s.w.r. meter. Initially, the top tube should be extended by 1 in. only. Further extension will lower the frequency at which the system resonates. S.W.R. figures of less than 2:1 should be readily achieved.

With this type of aerial the usable bandwidth will be fairly narrow. Where the aerial is readily accessible, as when mobile, the telescopic top tube can be adjusted to that part of the band the operator wishes to use at a particular time. This may not be possible in a fixed station, and the author is working on a simple electronic switching arrangement whereby the working segment of the 160 metre band can be changed from inside the shack, and he hopes to publish details of this in a future issue.

Returning to the present design, sources of supply for the aluminium tubes consist of TV aerial erecting firms and aluminium stockists and merchants. A glance through the Yellow Pages may be helpful here. The plastic conduit tube is available from most electrical contractors. Since there could be discrepancies in wall thickness with some tubes, the constructor should verify for himself that the parts obtained will fit inside each other as described before purchasing. The tubing lengths are all relatively short, whereupon it may be possible to obtain all that is required from oddments stocks. For neatness, the Jubilee hose clips should be for the specific diameters at which they are positioned. ■

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is the cover price stated on the issue, plus 8p postage.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

THE 'SLIDE RULE' RECEIVER CUM CAPACITANCE METER

Part 1

By Sir Douglas Hall, K.C.M.G.

This 2-part series describes an ingenious portable receiver covering 120 to 1,900 metres which can be built in either an earphone or a loudspeaker version. An unusual feature is that the receiver can also be employed as a sensitive capacitance meter capable of measuring capacitance values down to 1pF

See Aug. '75 p.55


THIS IS A DESCRIPTION OF A SMALL PORTABLE RECEIVER which may be built either for use with an earphone only or to operate a speaker in addition, and which doubles up as an instrument to measure the values of capacitors from zero to about 5,000pF. The receiver coverage is from about 120 metres to the low frequency end of the medium waveband, together with sufficient of the long waveband to tune in Radio 2 and several other stations.

When used to measure capacitance, the principle of operation involves the use of a sharply tuned variable inductance and a receiving circuit with very little input capacitance, so that an increase of applied capacitance of as little as 1pF requires a noticeable change of inductance for the circuit to remain tuned to the same frequency. A trimmer is provided as a zero-set adjustment to compensate for an ageing battery or for changes in ambient temperature.

RECEIVER OPERATION

The unit will be considered first as a receiver and in the form designed for earphone use only. It will be found to give sensitive and, for a simple circuit, very selective results on the medium waveband. In addition, by using the position of the switch selected when the unit is being employed to measure capacitance, band-spreading of the higher frequency end of the medium waveband is provided, together with efficient coverage of the 'trawler band' and the 160 metre amateur band. Coverage down to about 120 metres is possible. From about 190 to 250 metres sensitivity is exceptionally high using this position of the switch, owing to the very high inductance-capacitance ratio obtaining. However, in these circumstances selectivity is not quite so good as on the normal medium waveband, where an extra 56pF tuning capacitance is in circuit. It might seem that theory would dictate that the exceptionally high inductance-capacitance ratio given when less than 15pF tuning capacitance is in circuit would result in the best possible selectivity. But self-capacitance in the inductor itself tends to modify the operation of the tuned circuit when the physical parallel capacitor has a very low value. In practice, the constructor has a choice of two switch positions for the part of the medium waveband lying between 190 and 250 metres, one offering the greater sensitivity and the other giving maximum selectivity.

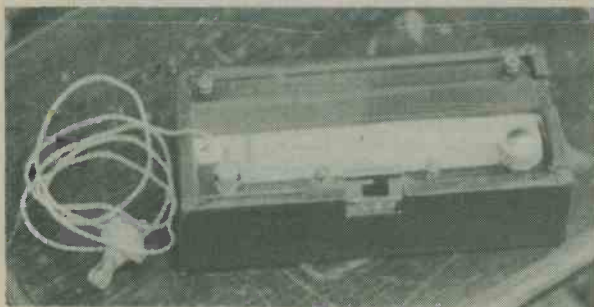As a capacitance meter the unit depends on reasonable reception of Radios 1, 2 and 3, although any station giving a good signal between 200 and 250 metres may substitute for Radio 1, and any station providing a reliable signal between 450 and 550 metres may be used instead of Radio 3. If the long wave Radio



The completed 'Slide Rule' receiver when constructed as a personal earphone set

2 is unobtainable, and no other station in the middle of that band can be received, then the unit will not measure capacitances above about 560pF unless a signal generator is pressed into service to substitute for Radio 2.

On the capacitance scales there is about $\frac{1}{4}$ in. spacing between the zero capacitance and 1pF points, and about 1 in. between the 1 pF and 10pF points, so the unit is easy to use for measuring very small capacitances. It should be remembered that there will be appreciable standing capacitance between any clips which might be used to hold the capacitor, and this standing capacitance should be measured first and subtracted from the final figure given when the capacitor being measured is connected. It may be found that capacitors with inefficient dielectric may not give a clear reading, owing to the consequent damping on the receiver tuned circuit.

CIRCUIT DIAGRAM

Let us now turn to the circuit diagram given in Fig. 1, looking at the unit as a receiver. It is similar to the author's "S.A. Junior" Portable Receiver which was described in the November 1972 issue of *Radio & Electronics Constructor*. There are, however, several modifications and the present design is more sensitive on medium waves than the earlier set.

For the time being, we shall ignore the a.f. section to the right of the broken line and will consider the circuit as an earphone receiver only. We shall introduce the a.f. section in the concluding article to appear next month.

The incoming signal picked up on coil L1 is applied to the base of TR1. This acts as an emitter follower at r.f. and the current amplified signal at its emitter is coupled to the base of TR2, which also functions as an emitter follower. L3 acts as an intermediate load, being damped slightly by R2 to prevent unwanted peaks which would otherwise cause instability at the higher signal frequencies. TR1 and TR2 function effectively as a Darlington pair, giving a considerable level of current gain and a high input impedance for r.f. at TR1 base. D1 is the detector and rectifies the signal, causing the detected a.f. to be applied back to TR2 emitter. This transistor operates as a common base amplifier at a.f. and an amplified a.f. signal appears at its collector. This is coupled to the base of TR1 via R4 and L1, whereupon TR1, acting this time in the common emitter configuration, provides further amplification. A small amount of negative feedback is given here by R1, which keeps the a.f. input impedance of TR1 high so that it more closely matches the output impedance at TR2 collector. The detected signal is thus finally built up across R6 and is coupled to the phone socket via C7. A crystal earphone

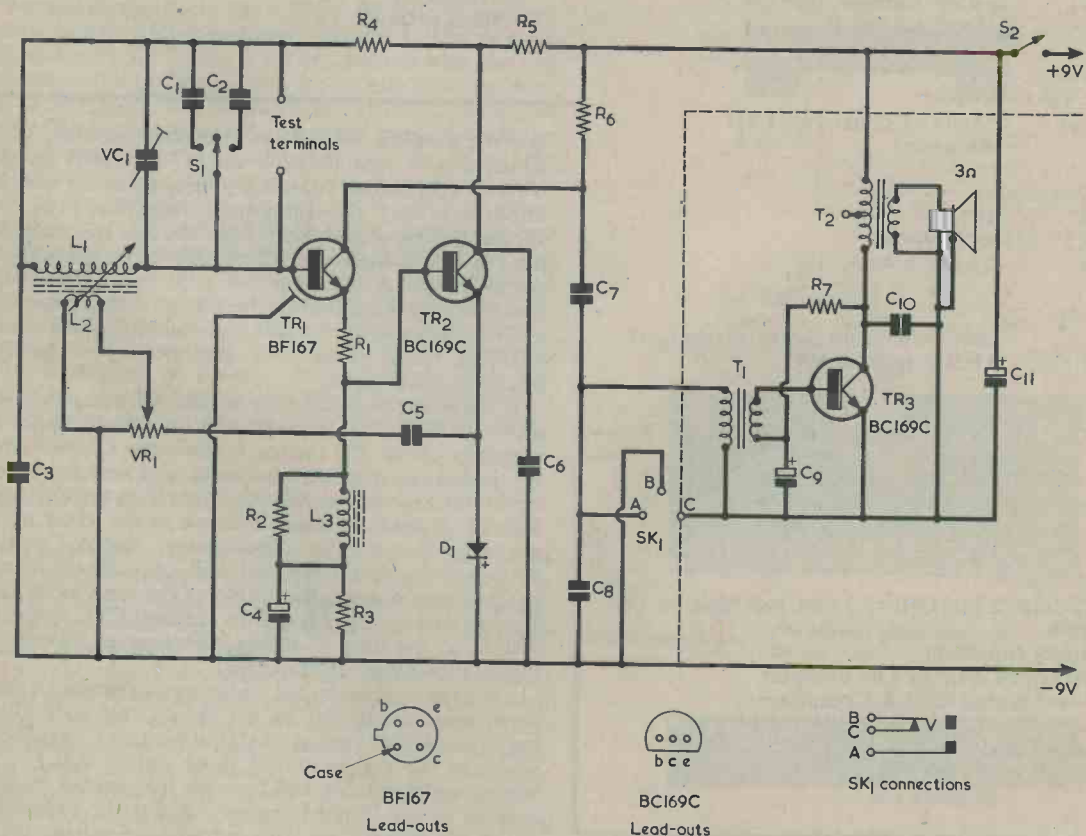


Fig. 1. The circuit of the 'Slide Rule' receiver. This will also measure the values of capacitors connected to the test terminals

COMPONENTS

Basic Earphone Version

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1	100 Ω
R2	18k Ω
R3	3.3k Ω
R4	10k Ω
R5	47k Ω
R6	22k Ω
VR1	5k Ω potentiometer, linear, with switch S2 (see text)

Capacitors

C1	56pF silvered mica or tubular ceramic
C2	820pF silvered mica (see text)
C3	1,000pF silvered mica or tubular ceramic
C4	10 μ F electrolytic, 2.5 V. Wkg.
C5	0.01 μ F polyester
C6	1,000pF silvered mica or tubular ceramic
C7	0.1 μ F polyester
C8	2,000pF silvered mica or tubular ceramic
VC1	2-25pF trimmer, type D7 (Henry's Radio)

Inductors

L1, L2	See text
L3	2.5mH r.f. choke type CH1 (Repanco)

Semiconductors

TR1	BF167
TR2	BC169C
D1	OA10

Switches

S1	Slide switch with centre off (see text)
S2	S.P.S.T. (part of VR1)

Socket

SK1	3.5 mm. jack socket with break contact
-----	--

Battery

9 volt battery type PP3 (Ever Ready)

Miscellaneous

Crystal earphone with 3.5 mm. jack plug
Knob
Battery connector
Ferrite rod, 6 in. by $\frac{3}{8}$ in. diameter
18-way tagboard, R.S. Components
'Standard' (see text)
6BA terminal nuts
 $\frac{1}{4}$ in. plywood, Perspex, s.r.b.p., Fablon or Contact, etc.

A.F. Output Stage

Resistor

R7	470k Ω $\frac{1}{4}$ watt 10%
----	--------------------------------------

Capacitors

C9	2.5 μ F electrolytic, 2.5 V. Wkg.
C10	0.047 or 0.05 μ F polyester
C11	1,000 μ F electrolytic, 10 V. Wkg.

Inductors

T1	Driver transformer type LT.44 (Eagle)
T2	Output transformer type LT.700 (Eagle)

Transistor

TR3	BC169C
-----	--------

Speaker

3 Ω speaker, 5 by 3 in. (see text)

Battery

9 volt battery type PP6 (Ever Ready)

Miscellaneous

Speaker fabric


into the winding. With S1 in its central position, VC1 is adjusted such that Radio 1 on 247 metres is tuned in with the rod almost completely inserted in the coil. It is important that the minimum capacitance of VC1 should not be greater than 2pF, though the maximum need not be as high as the 25pF offered by the component specified. A maximum of 10pF would be ample. Sharp tuning is ensured by the high r.f. input impedance at TR1 base, and by the fact that reaction, controlled by VR1, is taken from TR2 emitter to the feedback coupling winding, L2.

If there is no capacitance across L1 other than that given by VC1, the receiver will tune from about 120 metres to about 250 metres. S1 switches C1 into circuit for the normal medium waveband, and switches C2 into circuit for long waves. Sensitivity on long waves is not as high as on medium waves because of the lower inductance-capacitance ratio. Nevertheless, Radio 2 and one or two Continental stations will be received in most parts of the country. Reception of the long wave Radio 2 signal will be improved if the value of C2 is reduced to 470pF, at the cost of losing reception at wavelengths higher than about 1550 metres.

Let us next consider the circuit as a capacitance meter. A pointer is coupled to the ferrite rod such that it traverses three tuning scales and three capacitance scales as the rod is moved in or out of coil L1. The tuning scales are marked up with frequencies or wavelengths in the normal manner, whilst the capacitance scales are marked up with capacitance values. On the lowest capacitance scale the pointer is at zero pF when S1 is in the central position and Radio 1 is tuned in. If a 1pF capacitor is now connected to the test terminals it will be necessary to withdraw the rod a little in order to keep Radio 1 tuned in, and the new position of the

should be employed. If the output at the phone socket is to be fed to an a.f. amplifier the latter must have an input impedance of 20k Ω or more.

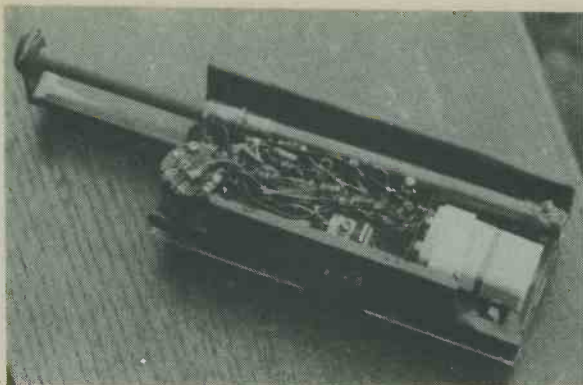Tuning is effected by changing the inductance of L1, this being done by varying the insertion of a ferrite rod



A view inside the receiver with the ferrite rod partly out of its coil

tion applies, incidentally, to S1 also.

The various pieces needed for the 'chassis' of the receiver are illustrated in Figs. 2, 3 and 4, whilst Fig. 5 shows how they fit together to form a complete assembly. First, cut out and drill three pieces of $\frac{1}{4}$ in. plywood as shown in Figs. 2(a), (b) and (c). The $\frac{7}{8}$ by $\frac{1}{2}$ in. cut-out in Fig. 2(b) is intended to take the body of the slide switch just mentioned. If a toggle switch is used this cut-out is not required, and a hole to take the switch bush is required instead. The toggle switch should take up approximately the same position as would the slide switch.

A clip to take the PP3 battery should be cut out from aluminium sheet or tinplate and screwed to the piece of Fig. 2(a) with a short woodscrew. The $\frac{3}{8}$ in. recess in this piece is to allow for the slide switch, and may need to be modified if a toggle switch is fitted. In Fig. 2(b) there are two $1\frac{1}{4}$ in. 6BA bolts with their heads on top, i.e. towards the reader, and these screws form part of the test terminals. They are cheese-head or round-head and each has a solder tag under the head. They are fitted with nuts and tightened up. So also is the remaining $1\frac{1}{4}$ in. 6BA bolt, which is countersunk and has its

pointer will be at the 1pF calibration point on the scale. This process can be repeated for any values of test capacitance up to about 56pF, at which capacitance the rod will have been removed some way from the coil. The process cannot be repeated for test capacitances much above 56pF as the Radio 1 signal then becomes rather faint due to the relatively small length of rod in the coil.

For test capacitances above 56pF, S1 is set to medium waves, bringing C1 into circuit across L1. The receiver will now pick up Radio 3 on 464 metres with the rod well inserted into the coil, and the pointer now indicates test capacitances on a second scale. If test capacitances up to 560pF are connected across the test terminals the rod will again have to be removed from the coil to tune in Radio 3, and the pointer will indicate the test capacitance on the second scale. For values of 560pF or more, Radio 2 on 1,500 metres can be tuned in with the rod well inserted, whereupon the pointer indicates the test capacitance on a third scale. In areas where Radio 2 provides a good signal it will be possible to tune it in with up to 5,000pF across the test terminals. If Radio 2 is received at lower level the limit of easy identification will be reached at around 3,000pF across the test terminals, at which value critical reaction is only just possible due to the unsatisfactory inductance-capacitance ratio.

CONSTRUCTION

We turn next to the construction of the receiver in its earphone-only version. As we shall see next month it is an easy matter to add the a.f. stage shown to the right of the broken line in Fig. 1 to this version, should loud-speaker reception be desired.

Two points concerning components need to be raised at this stage. The switch employed for S1 in the prototype was a slide switch having a centre off position. This type of switch is not currently advertised by the large mail order houses although readers who live near component retailers may be able to obtain one. If not, a satisfactory substitute is a small toggle switch having a centre off position. The toggle switch can be single pole or double pole; if the latter only one pole is used. The second part which requires mention is VR1/S2. This component should not be greater than 1 in. in diameter and it should not project back from the panel on which it is mounted by more than 1 in. The same depth restric-

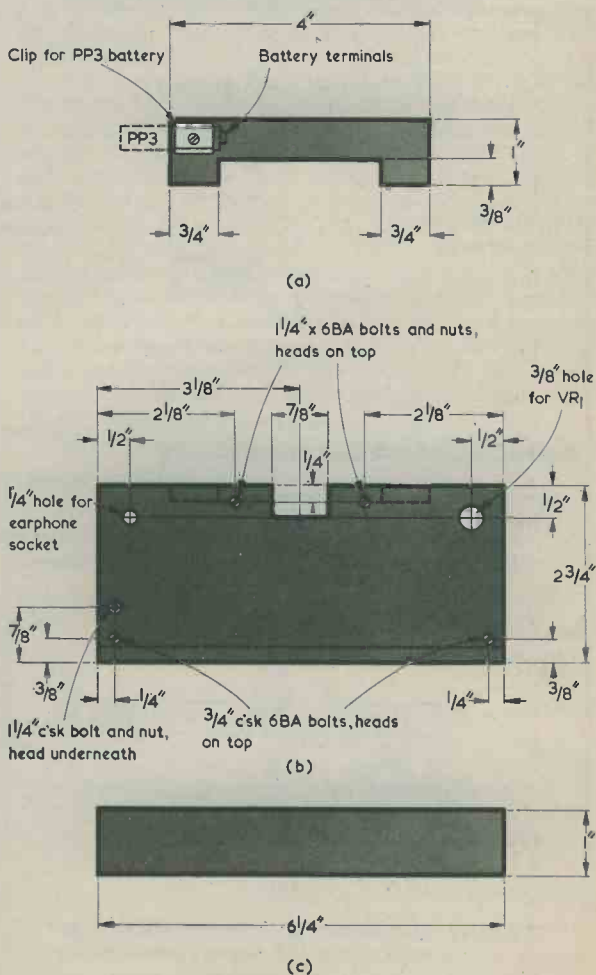


Fig. 2. The three basic parts of the receiver 'chassis'

head underneath the plywood piece, away from the reader. The two $\frac{3}{8}$ in. 6BA bolts are pushed into place but are not fitted with nuts. The three pieces are screwed together as indicated by the dashed lines, and the assembly is covered on the outside with Fablon or Contact.

Next cut out a piece of $\frac{1}{2}$ in. plywood as shown in Fig. 3(a), cover it with Fablon or Contact and glue a stiff wire into a $\frac{1}{16}$ in. hole as shown. This piece slides sideways with the ferrite rod, and the wire is the scale pointer. Cut out the piece in Fig. 3(b) from s.r.b.p. ('Paxolin') or Formica and cover it with Fablon or Contact. Fit a grommet with a $\frac{3}{8}$ in. centre to the $\frac{1}{2}$ in. hole, and screw the piece of Fig. 3(b) to that of Fig. 3(a). After the coils have been wound, the end of the ferrite rod will be fitted to the grommet, making up the assembly shown in Fig. 3(c).

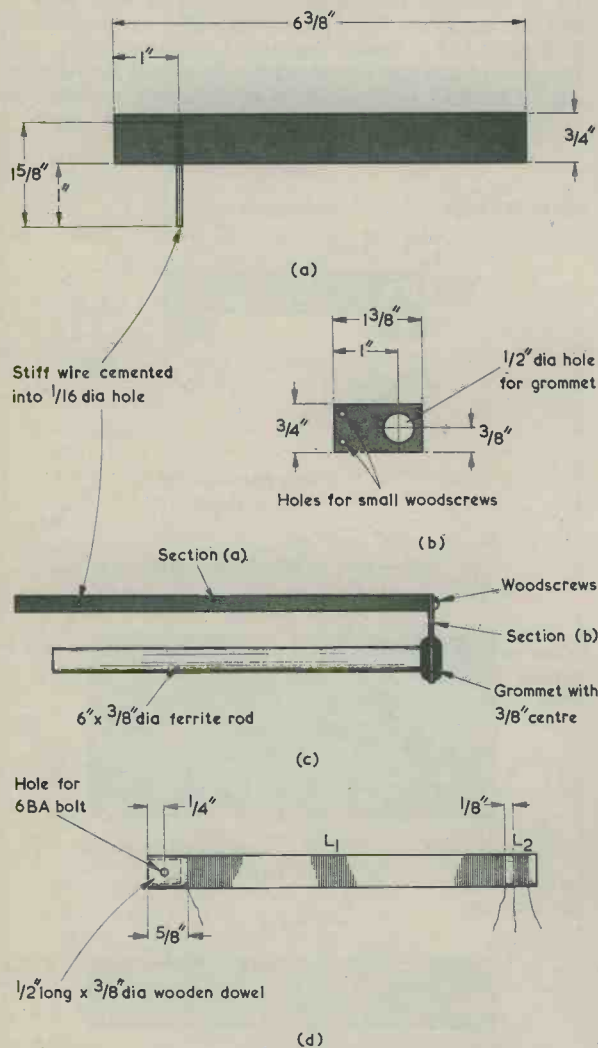


Fig. 3(a). This length of plywood slides sideways along the upper surface of the receiver
 (b). S.R.B.P. item which holds one end of the ferrite rod
 (c). The sliding ferrite rod assembly
 (d). Details of coils L1 and L2


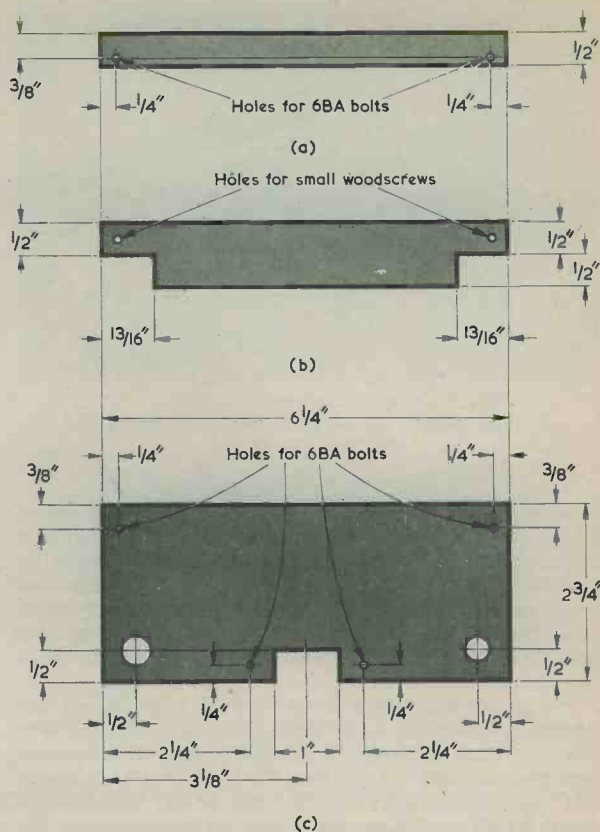


Fig. 4(a). Guide and spacer for the item of Fig. 3(a)
 (b). Second guide for the item of Fig. 3(a). This also provides the backing for the tuning and capacitance scales
 (c). The Perspex panel which is on top of all the pieces so far illustrated

COIL WINDING

Coils L1 and L2 should now be wound. Cut a piece of Fablon 6 in long by $1\frac{1}{2}$ in. wide, and remove a $\frac{1}{2}$ in. strip of backing paper from one 6 in. side. Wrap the Fablon around the ferrite rod with the $\frac{1}{2}$ in. exposed strip last so that this sticks to the layer of Fablon underneath, thereby making up a self-supporting tube. This tube should be a fairly tight fit but should still be removable from the rod. Cut a second piece of Fablon 6 in. by 6 in., and remove $\frac{1}{2}$ in. of backing paper from one edge. Wrap this round the ferrite rod and the first tube with the $\frac{1}{2}$ in. exposed strip last, thus making a second tube. Remove both tubes from the rod, then remove the first tube from the second and discard it. The second, thicker, tube is now the coil former and it will be found to be an easy, loose fit on the rod. Leave the rod inserted in the tube.

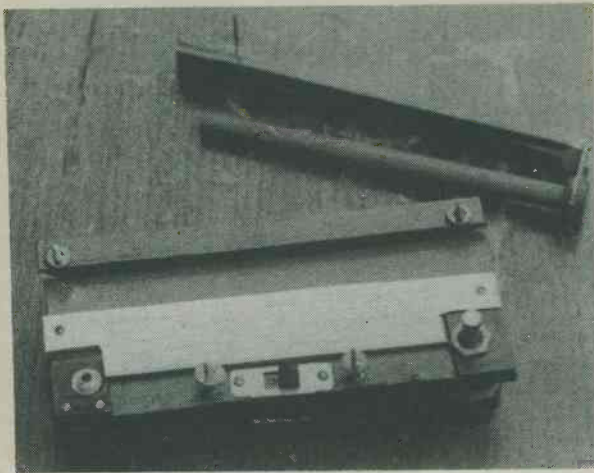Fix the end of a length of 24 s.w.g. enamelled wire with Sellotape to the tube at a point $\frac{5}{8}$ in. from one end. Wind on 180 turns in a single layer, each turn touching the next, for L1. The end of the winding is then fixed with Sellotape.



Showing the ferrite rod assembly before it is inserted in position

There is a slight possibility that the ferrite rod obtained may be Blue grade, this being a low permeability grade which was marketed some years ago by R.S. Components and which has since been discontinued. Some stocks may still, however, be held by retailers, and ferrite rod of this type is readily distinguishable because of a blue coding mark at one end. If the ferrite rod is Blue grade, L1 requires 225 turns of 26 s.w.g. enamelled wire. Should the ferrite rod have any colour coding other than blue, or no coding at all, then L1 needs the 180 turns of 24 s.w.g. enamelled wire just mentioned. There is nothing magical in these grades of wire: they are chosen merely to ensure that L1 has as great a length as is practicable, thereby ensuring that the ferrite rod has a wide travel as it tunes the receiver. Either coil will be approximately $4\frac{1}{4}$ to $4\frac{1}{2}$ in. long.

L2 starts $\frac{1}{8}$ in. from the end of L1 and is also close-wound. It has 15 turns wound in the same direction as L1 and employs the same wire as was used for L1. It is held in place with Sellotape.

A $\frac{1}{2}$ in. length of $\frac{3}{8}$ in. wood dowelling has a few turns of Sellotape wound on it to ensure a good fit and is then inserted in the end of the Fablon tube, as shown in Fig. 3(d). The ferrite rod is now removed from the tube and fitted to the grommet, as in Fig. 3(c). A 6BA clear hole is next drilled through the Fablon and the dowelling, as indicated. Take up the assembly of Fig. 2 and position it so that the head of the $1\frac{1}{4}$ in. countersunk 6BA bolt is underneath. Fit a nut and then a washer to this bolt, then fit the Fablon tube and the dowelling over this, with the bolt passing through the 6BA clear hole just drilled. Fit another washer and another 6BA nut. Do not tighten the nuts yet. Next turn the Fig. 2 assembly over so that the head of the $1\frac{1}{4}$ in. countersunk 6BA bolt is on top and slide the rod assembly of Fig. 3(c) into position so that the rod enters the coil and the plywood piece of Fig. 3(a) lies on top of the Fig. 2 assembly. Adjust the nuts holding the coil former so that the latter is parallel with the underside of the Fig. 2(b) piece, and then finally tighten them.

Next cut out and drill the three items shown in Fig. 4. That in Fig. 4(a) is made of $\frac{1}{4}$ in. plywood, that in Fig. 4(b) of s.r.b.p. or Formica, and that in Fig. 4(c) of $\frac{1}{8}$ in. Perspex. It will be helpful at this stage to refer also to Fig. 5 from time to time to gain an idea of the complete construction. The piece of Fig. 4(a) is covered with Fablon or Contact and it passes over the $\frac{3}{8}$ in. bolts in the Fig. 2 assembly. The Fig. 4(b) item is fitted to the top of the Fig. 2 assembly with small woodscrews, and is positioned so that it lies under the pointer and is close enough to the piece of Fig. 3(a) to allow the latter to slide smoothly and without wobble as it takes the ferrite rod in and out of the coil. A piece of white card is cut to the same dimensions as Fig. 4(b) and will later be marked up with the scales and fitted over this item. It should have two small holes matching those in Fig. 4(b). The Perspex piece of Fig. 4(c) passes over the same two 6BA bolts which pass through Fig. 4(a) and it passes also over the $1\frac{1}{4}$ in. test terminal bolts. The two large holes in this piece should have diameters which will, respectively, accommodate the bush of VR1 and allow the earphone plug to pass into its socket.

Before fitting the Perspex panel place thin washers

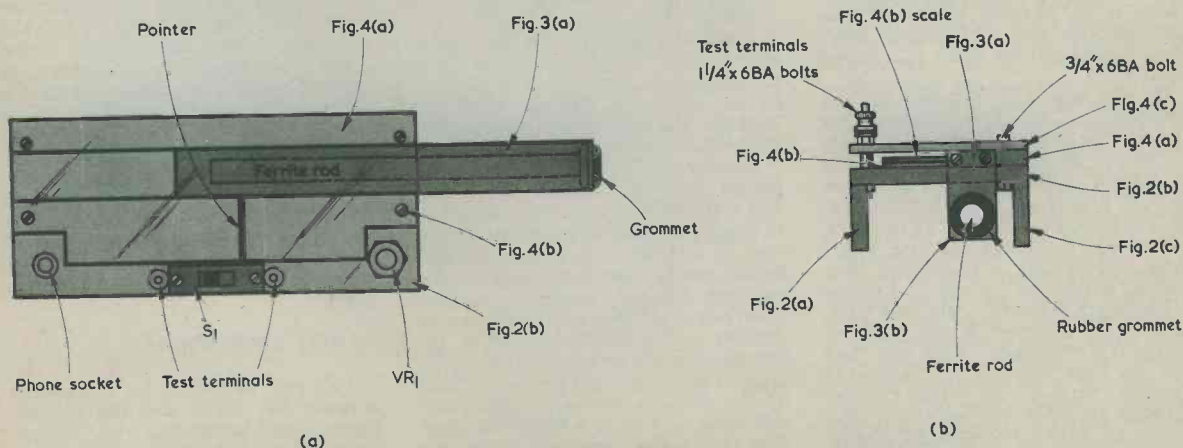


Fig. 5(a). View from above of the previous items when assembled together
(b). Side view of the complete assembly

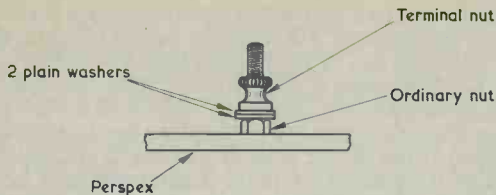


Fig. 6. How the terminals are made up above the Perspex panel

over the $\frac{3}{4}$ in. bolts passing through the Fig. 4(a) part, and fit spacing washers over the test terminal bolts which will space off the Perspex panel from the top of the Fig. 2 assembly by slightly more than $\frac{1}{4}$ in. Ordinary nuts may be used to secure the Perspex at the $\frac{3}{4}$ in. bolts, although dome nuts or terminal nuts will look better.

Nuts, washers and terminal nuts are passed over the test terminal bolts, as illustrated in Fig. 6.

Since the Perspex piece is spaced off by slightly more than $\frac{1}{4}$ in., the ferrite rod assembly should be free to slide in and out smoothly.

NEXT MONTH

Next month's concluding article will give details of wiring and will also describe how the a.f. stage and loudspeaker may be added.

A complete Components List is given this month and this includes the parts required for the a.f. section. If it is intended to build the 3-transistor version from the start, then the PP3 battery will not be required. The textual references to the speaker and tagboard will be dealt with in the next article.

(To be concluded)

Radio Topics

★ ★ ★ By Recorder ★ ★ ★

NUMBERS ARE FASCINATING THINGS and I can well understand mathematicians who become completely immersed in them, regardless of their connection with the physical world in which they fit. For those of us who like to play around with numbers at a simpler level there are, also, many intriguing features to discover about them.

THINK OF A NUMBER

Think of any number less than 10. Multiply 37 by that number, then multiply the answer by 3. Say we chose the figure 2. 37 multiplied by 2 comes to 74, and that number multiplied by 3 gives 222. Try it with any other number. There is an obvious reason for the answers you get, but please don't write in and tell me when you realise it!

If we take the squares of the numbers, 1, 2, 3, 4, 5, 6... in order we find that we have the series, 1, 4, 9, 16, 25, 36... Should we then take what are known as the 'first differences', we get 3, 5, 7, 9, 11... The 3 is 4 minus 1, the 5 is 9 minus 4, the 7 is 16 minus 9, and so on. Note that the first differences increase by 2 each time. The 'second differences', given by 5 minus 3, 7 minus 5, 9 minus 7, etc., are all 2. This is an example of the 'Law of Constant Differences'. You may feel that this little gimmick is a matter of academic interest only, but Charles Babbage used it as the basis of operation in his ill-fated 'difference engine' of the 1820's. The 'difference engine' was a mechanical calculating machine, but the engineering skills of the day

were not sufficient for the manufacture of the precisely dimensioned gears which the machine required, and the 'difference engine' as conceived by Charles Babbage never became a practical proposition. It was to be followed by work on his 'analytical engine' which, in theory, was a mechanical forerunner of the modern computer. The tragedy for Charles Babbage was that the mechanical equipment available to him could not match up to the brilliance of his ideas. Ironically, a Swedish-made 'difference engine', based partly on Babbage's design, did appear during his lifetime and functioned satisfactorily.

FURTHER NUMBERS

Returning again to numbers themselves, there is a little trick of which advantage was taken by G. A. French in his Suggested Circuit, "'Magic' Number Indicator". This appeared in the March 1972 issue of this journal.

Since more than two years have passed since G. A. French's article was published, I think it's reasonable to quickly repeat the numerical artifice that he described. Take any number having two or more digits. It could, for instance, be your telephone number. Then rearrange the digits to give a new number which is different from the first number and subtract the smaller of the two numbers from the larger. Add up the digits in the remainder. These will come to 9 or to a higher number. If it is a higher number add up the digits again and, if necessary, repeat. The final result will always be 9.

To take an example, let's say that


our first number is 3,017. We can rearrange this to 1,703. If we subtract 1,703 from 3,017, we get 1,314, the digits of which add up to 9. We could have rearranged 3,017 to become 7,013, whereupon 7,013 minus 3,017 is 3,996. The digits in 3,996 add up to 27. A second addition then produces 9 again. Try it with numbers of any size having two digits or more.

The reason for this phenomenon is that the digits in any multiple of 9 always add up to 9 or to a multiple of 9. This fact is self-evident from the 9-times table where we have the series 18, 27, 36, 45, and so on. Any number greater than 9 must be a multiple of 9 or a multiple of 9 plus a remainder from 1 to 8. The number we chose, 3,017, is a multiple of 9 plus the remainder 2, because the digits in the number add up to 11. If we rearrange 3,017 in any way, its digits still add up to 11, and the number is still a multiple of 9 plus the remainder 2. When we subtracted 1,703 from 3,017 we were subtracting a multiple of 9 plus 2 from another multiple of 9 plus 2. The two 2's disappeared during the subtraction whereupon the result was a multiple of 9 minus another multiple of 9. The answer must then itself be a multiple of 9.

AERIAL AMPLIFIERS

Two new amplifiers for connection between the aerial and the receiver have been introduced by Wolsey Electronics, a division of AB Electronic Components Ltd.

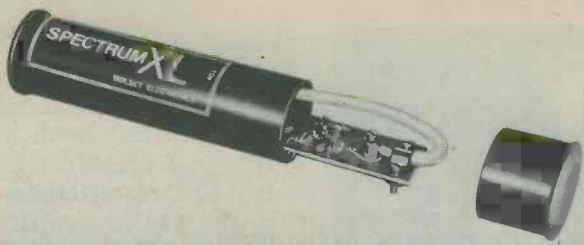The first of these is the 'Clearsound' Signal Booster, which is designed for RADIO & ELECTRONICS CONSTRUCTOR



The Wolsey Electronics 'Spectrum XL' Masthead Amplifier. This boosts television signals in the u.h.f. Bands IV and V

the amplification of v.h.f. f.m. signals. Wolsey Electronic state that the minimum signal level for good stereo radio reception must be 8 to 10 times (18 to 20 dB) greater than that required for mono reception. In areas where signal strength is poor and the stereo decoder cannot be locked in properly the 'Clearsound' amplifier can raise the incoming signal comfortably over the stereo threshold.

The 'Clearsound' booster incorporates a low noise silicon transistor and has a frequency range of 87.5 to 100MHz with a minimum gain of 20 dB. Ideally, it should be fitted to the aerial mast close to the aerial but it can be located nearer the f.m. receiver if masthead mounting is difficult.

The second signal booster from Wolsey Electronics is the 'Spectrum XL' Masthead Amplifier. This is also fitted with a low noise silicon transistor and it is intended for u.h.f. colour

or monochrome television reception. The amplifier is completely weather-proof and is positioned close to the u.h.f. aerial. Two amplifiers can be wired up in cascade, if desired. Typical minimum gain is 10 dB with a noise figure of between 2.5 and 3.5 dB. Three models of the 'spectrum XL' are available, these covering Group A (Channels 21 to 34), Group B (Channels 39 to 51) or Group D (Channels 49 to 68). The amplifier can be seen in the accompanying photograph.

Further details on these amplifiers can be obtained from Wolsey Electronics, Cymmer Road, Porth, Rhondda, Glamorgan, CF39 9BT.

VARIABLE INDUCTOR

My second photograph illustrates a variable inductor intended for transmitting work. The whole coil former is capable of being rotated by means of

the shaft projecting from the centre of the assembly end-plate, whereupon the pulley rides along the spiral which constitutes the coil. Connection is made to the pulley by way of the rod on which it turns.

This particular unit is one of a range of special inductors now being handled by Vero Electronics Limited, Industrial Estate, Chandler's Ford, Eastleigh, Hants. The range includes fixed and variable inductors incorporating copper wire, ribbon or tubing, and non-standard inductors can be made to special order. These products are manufactured by the American firm, E. F. Johnson Company, and some are already in use in U.K. broadcasting stations.


DOWN WITH NANOFARADS!

You can call me a square old reactionary if you like, but I can't for the life of me see any point in making changes where changes are not required.

I have just been looking at a rather poorly reproduced circuit diagram, and spent some time wondering why an r.f. bypass capacitor was given the unusual value of $2\mu\text{F}$, when I suddenly realised that the capacitor wasn't $2\mu\text{F}$ at all. The smudgy character after the figure '2' wasn't ' μ ' for 'microfarad' but was 'n' for 'nanofarad'. As you know, nanofarads come between microfarads and picofarads, and 1 nanofarad is equal to 1,000 picofarads. So that r.f. bypass capacitor I was looking at had the eminently reasonable value of 2,000pF. (Or, as Dick of 'In Your Workshop' fame would have put it some years ago, it had a 'puffage' of 2,000).


For more than twenty years now we have been pressing on quite contentedly with just the two units of capacitance: microfarads and picofarads. They have met our requirements perfectly adequately and there can surely be no reason at all in complicating matters by introducing nanofarads. In many circuit diagrams these days the letter 'F' is omitted from capacitance values, whereupon these values may be shown as, say, ' 10μ ' or ' 50p '. There is little risk of confusion between the symbols ' μ ' and ' p ', and in most instances the actual value in figures and the function of a capacitor indicate with little room for doubt what the capacitance unit is. But such is not the case when values in nanofarads are allowed to creep in.

It would be interesting to find how many errors due to the use of the nanofarad as a unit have arisen in manufacturers' research and development work; in which, say, drawing office personnel have mistaken the symbols for capacitance in engineers' sketched circuits. Enough, I would guess, to make the letter 'n' stand strictly for 'nuisance value' rather than for an unnecessarily introduced unit of capacitance. ■

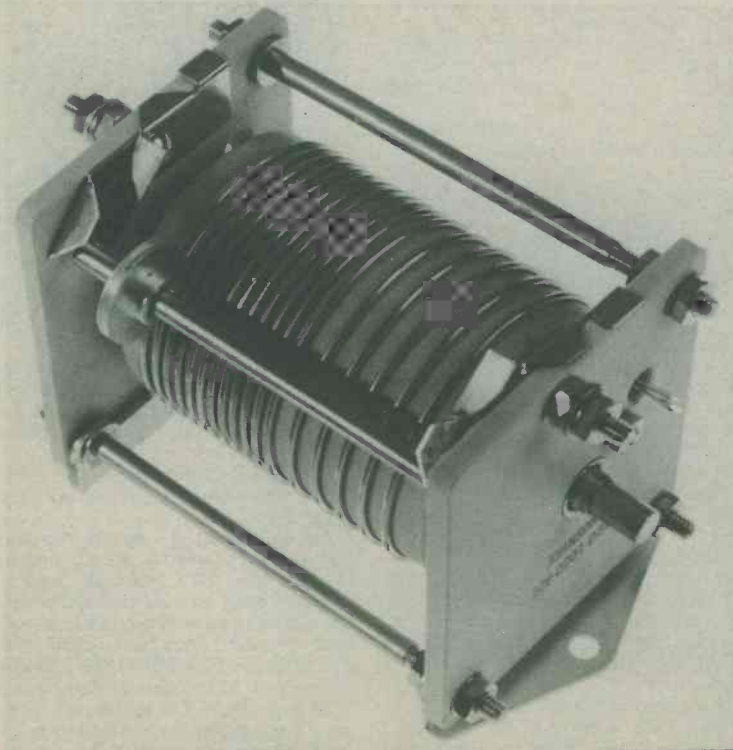

A variable inductor from the range now being marketed by Vero Electronics Limited

In your workshop



This month Dick and Smithy embark on the repair of a small imported a.m. radio which does not even boast a manufacturer's name. The Serviceman demonstrates some simple servicing techniques which can be carried out on receivers of this type.

"HOORAY," SAID SMITHY JUBILANTLY, "that's my last job for today cleared up."

He carried the television receiver he had repaired over to the racks then returned to his bench. Contentedly, he tidied up his tools and test equipment, picked up a small brush and swept the day's debris of solder blobs and wire ends into his rubbish bin. Glancing over at Dick's bench, he saw that his assistant was engrossed in a small object in front of him. Smithy walked over to Dick's side.

"Still busy, eh?" he said chattily. "That's what I like to see!"

Dick looked up.

"I've just this minute started on this job," he remarked. "It's a little imported a.m. radio, and so far I can't get a thing out of it."

NO-NAME RADIO

Smithy leaned over and looked at the set on Dick's bench. It still had the back on and he picked it up to examine it more closely. It was a small pocket radio having two controls only, one being a rim operated volume control and on-off switch at the side and the other a tuning knob on the front. As Smithy turned the latter, figures from "6" to "16" appeared hopefully in a small window. He examined the case carefully and searched unsuccessfully for a manufacturer's name. The little set did, however, possess some identity, and this was proclaimed by a paper rectangle, peeling at one corner, which stated bravely: "Dreadnought"

"This is peculiar," grunted Smithy, frowning. "We don't usually accept these cheap little radios for servicing. The cost of fixing them is often more than the original cost when they were bought new. Still, we've cleared out all the other sets that are in for repair today so we might as well have a stab

at this one before we finally pack in. I don't want to be too late tonight, by the way; I've got a fairly full evening on down at my club."

"I've got a fairly full evening in front of me, too," said Dick morosely. "But I can't say I'm looking forward to it."

"Why not?"

"I've been press-ganged into doing a job for one of my aunts," explained Dick unhappily. "I'm going to have a really hilarious time."

Even Smithy would have conceded that Dick had more than his fair share of aunts. The Serviceman clicked his tongue sympathetically.

"Oh well," he said comfortingly.

"Perhaps it won't be too bad."

"Let's hope not," stated Dick. "Incidentally, what do those tuning numbers stand for?"

"What tuning numbers?"

"The ones from 6 to 16 on the tuning dial of that set."

"Oh, those," replied Smithy, bringing his thoughts back to more immediate matters. "Why, they're probably intended to be hundreds of kHz. As there's no wavechange switching this is almost certainly a medium wave only job, so the range will be from about 600 to 1,600kHz."

"It seems funny," remarked Dick, "to think of a medium wave band which is marked out in frequency instead of wavelength."

"Not really," replied Smithy. "Other countries have an a.m. broadcast band equivalent to our medium waves, but they identify the stations in it by frequency. It's us who are probably behind the times sticking to wavelengths."

He glanced at his watch.

"Well," he went on, handing back the set to Dick, "we've got half an hour to fix this set, so let's get down to it right now. Routine checks to start

off with!"

"Fair enough", replied Dick equably, taking the set from Smithy. "I'll get the back off first."

He soon found the manner in which the back was secured, and he removed this with a click to reveal a tiny printed circuit board on which were packed four diminutive square metal cans, two a.f. transformers and a minor forest of other components. A small ferrite slab aerial was fixed to one end of the board. At the other end was a black plastic battery holder in which two 1.5 volt cells were visible. Dick looked quickly for obvious faults but could find none. There were two small tags on the battery holder, to which were connected two wires from the board. He pulled his testmeter towards him, selected a low voltage range and applied its prods to the two tags. The meter needle rose to around 4 volts on its scale. Dick switched on the receiver, whereupon the voltage reading dropped to less than 2.5 volts. He switched the set off again.

"The battery's had it," he remarked, removing the cells from the battery holder and examining them. "Could you get me four U7 cells please, Smithy?"

"Okeydoke," replied Smithy obligingly. "Incidentally, they're HP7 cells these days."

He walked to the spares cupboard and returned with a plastic package holding four HP7 cells. He split the package open and handed the cells to his assistant who fitted them into the battery holder. Dick next picked up the testmeter prods and once more checked the voltage at the battery holder tags.

"That's funny," he remarked, frowning. "I should be getting 6 volts here."

"What are you getting?"

"3 volts."

Smithy sighed.

RADIO & ELECTRONICS CONSTRUCTOR

"I should have known better than to help you on this job," he stated irritably. "I've been in a good humour all day, and now you've started spoiling it."

"Well, there's no need to get all uptight about it," said Dick defensively. "These new cells must be duffy."

"What is infinitely more likely," snorted Smithy, "is that you've put one of them in wrong way round." (Fig. 1.)

Dick looked down at the battery holder.

"Gosh, you're right, too," he said. "Well, I'll soon put that right."

Quickly, he removed one of the cells, turned it round and refitted it. The voltmeter now gave a reading of 6 volts.

"That's more like it," said Smithy, mollified. "Let's see how the set works."

He leaned over, turned the receiver volume up and adjusted the tuning knob. He soon found a signal giving adequate volume at the high frequency end of the scale. It had an unpleasantly distorted quality. Smithy turned down the volume and the distortion increased very noticeably.

"I would guess," he remarked judiciously, "that we've probably got a case of crossover distortion in the Class B output transistors here. You heard that there was quite good volume and that the distortion increased when the volume went down. This makes crossover distortion a reasonable possibility because the signal range over which this distortion takes place occupies a larger proportion of the overall signal at lower volume levels." (Fig. 2.)

"Yes, I think I can follow your reasoning there," remarked Dick. "But what could be causing the crossover distortion?"

"The output transistors," replied Smithy, "won't be getting sufficient quiescent bias. I hardly need to tell you that Class B output stages are given a bias which allows them to pass a few milliamps, when no signal is present."

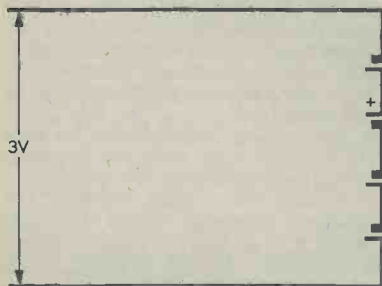


Fig. 1. How four 1.5 volt cells, with one inserted incorrectly in a battery holder, produced a total voltage of 3 volts

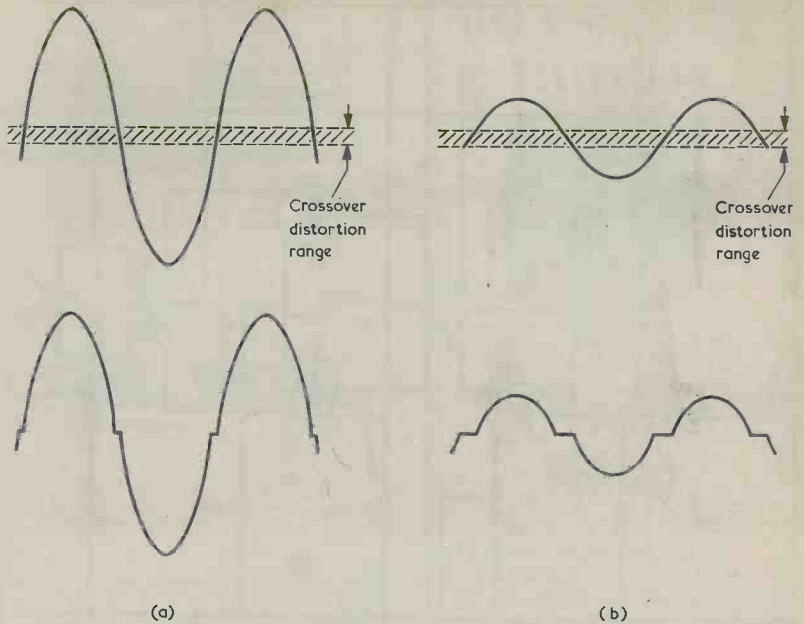


Fig. 2(a). If a Class B output stage is operated without quiescent bias the central part of the signal is not amplified and crossover distortion results. The input waveform is shown at the top and the distorted waveform below
(b). If the input waveform has a low amplitude the effect of crossover distortion is relatively higher

Dick gazed down at the crowded printed circuit board of the receiver.

"That's all very well," he said helplessly, "but where the heck do we start looking for bias faults in this little lot? It isn't as if we had a service manual, even."

"The fault shouldn't be too hard to trace," said Smithy. "As you can see, there are two a.f. transformers on that printed board. These are bound to be an a.f. driver and an a.f. output transformer. A.F. circuits incorporating a driver and an output transformer are virtually the same in nearly all these small sets. Look, I'll show you."

OUTPUT CIRCUIT

Glancing over Dick's bench he spotted his assistant's note-pad and pulled it over towards him. He took out his pen and quickly sketched out a circuit. (Fig. 3.)

"Here you are," he said. "This is the sort of thing you get in the driver and Class B output stage when these use transformers. I've shown p.n.p. transistors because driver and output transformer are more liable to appear in older receivers, but the circuit could equally well employ n.p.n. transistors with the supply polarity reversed. If you look at the secondary of the driver transformer you'll see that its outer ends go to the bases of the output transistors whilst its centre-tap has one

resistor going to the negative supply rail and the other going to chassis."

"Do these resistors provide the quiescent bias?"

"They do," said Smithy. "If the output transistors are germanium types, the upper resistor can have a value of around 4.7kΩ and the lower one a value of around 100Ω. More often the lower resistor will be replaced by a thermistor, or by a thermistor and resistor in parallel."

"What does the thermistor do?"

"It prevents distortion due to changes in ambient temperature," said Smithy. "If the temperature goes up the output transistors try to pass more current. But the increased temperature also causes the resistance of the thermistor to reduce, whereupon the bias voltage for the output transistors goes down and counteracts their tendency to pass increased current."

"There's another resistor in that circuit of yours. The one between the output emitters and chassis."

"Ah yes," said Smithy. "Well, that resistor is a low value job and is usually in the region of 2 to 4 ohms. It's to guard against thermal runaway in the output transistors. If these pass a heavy current, the voltage across that resistor rises and causes the base-emitter bias voltage to reduce. Another point I should mention is that there's normally a negative feedback circuit coupling back from the output trans-

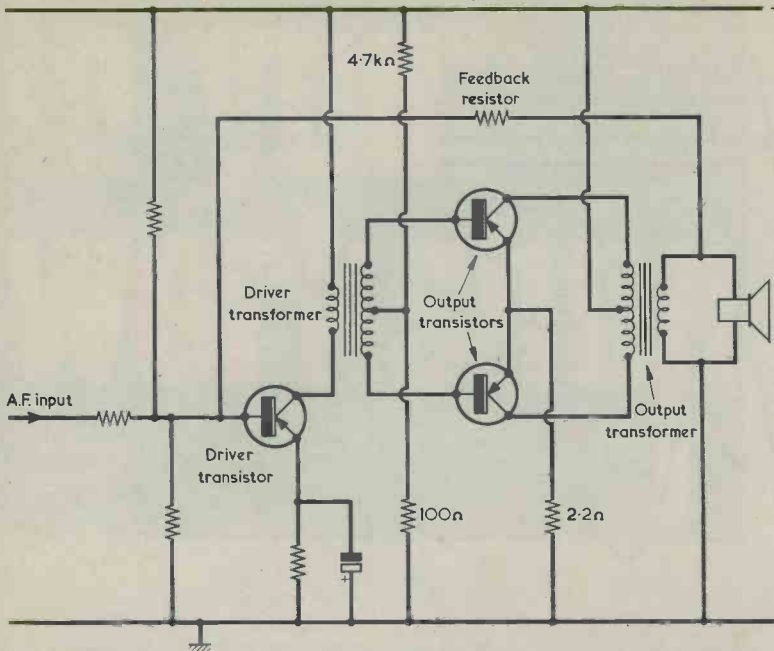


Fig. 3. Nearly all small transistor radios incorporating a driver and a.f. output transformer employ this output transistor bias circuit. The component values shown here are representative

former secondary to the base or emitter of the driver transistor. In my diagram I've shown it coupling back to the base of the driver transistor but you'll find variations on this in most sets. However, the remaining part of the circuit including the quiescent bias supply arrangement is pretty standard for all sets."

"Isn't this business of using transformers rather old-fashioned?"

"Oh, definitely," agreed Smithy. "There are much more effective a.f. driver output circuits available these days which don't require transformers at all. What I find surprising is that quite recent transistor radios, both those made here and those imported, still incorporate transformers. I suppose the transformer circuit has the advantage of simplicity and that the transformers can be produced pretty cheaply. So far as servicing is concerned, you and I will be seeing transistor radios with a.f. transformers in them for a few more years yet. But you're quite right in calling the use of transformers old-fashioned."

A thought suddenly crossed Dick's mind and his face took on an expression of gloom.

"Talking of things being old-fashioned," he grumbled, "has reminded me that I've got to do that dratted job for my aunt tonight. She's so old-fashioned it just isn't true."

"Which aunt is it?"

"Aunt Effie."

"Is she the one who puts ruffles on the piano legs?"

"That's the one. The family all call her Effie the Ineffable and what I can't understand is that they then all fall about laughing over it. Another thing I don't understand is that they're all queueing up to do jobs for her. Or rather," he added darkly, "getting me to do jobs for her."

"Perhaps," said Smithy consolingly, "they have their reasons. Anyway, let's get back to this set and our assumption that it's suffering from crossover distortion. If this is the case, there's a strong likelihood that the resistor coupling the upper supply rail to the centre-tap of the driver transformer secondary has gone open. You shouldn't have much difficulty tracing that resistor on the board because it connects to the driver transformer centre-tap."

"Fair enough," commented Dick. "Hey, wait a minute! How will I know which transformer is the driver one?"

"The other one," said Smithy sweetly, "connects to the speaker."

"Blimey, of course. I'll get the printed circuit out then."

"Righty-ho," remarked Smithy. "Be careful with it. Some of these little sets have pretty tricky fastening arrangements."

But Dick was in luck. The tuning knob pulled off without any difficulty and, after removing three small screws, the circuit board came free complete with the speaker. It was only necessary to unsolder the two leads at the battery holder tags. And Smithy was lucky, too. After a little searching Dick

located the upper bias feed resistor and found that it had, indeed, become open-circuit. It was colour-coded 3.9kΩ, and Dick soon fitted another of this value in its place. He replaced the board in the cabinet and resoldered the two wires at the battery holder. He then fitted the tuning knob and switched on. He returned to the station previously selected by Smithy and adjusted the volume control. The quality of the reproduction offered by the little receiver was now quite adequate for one of its ilk.

POOR TRACKING

"Job done," he announced joyfully. "You certainly pin-pointed that snag, Smithy."

An outside observer might have noted that Dick's pleasure at the successful repair was considerably higher than the situation would apparently warrant.

"I wish all the faults we dealt with were as easy," remarked the Serviceman. "Let's see how the set handles now."

Smithy leaned over and checked the performance of the receiver at different tuning positions. He frowned.

"It doesn't," he remarked, "seem to be tracking very well. It's quite sensitive at the high frequency end of its scale but it's not so hot at the low frequency end. Let's see if the ferrite aerial coil needs a little adjustment."

He switched off the receiver, turned it over and placed an exploratory finger on the aerial coil mounted on its ferrite slab.

"Darn it," he said irritably. "This blasted coil's immovable."

"How do you mean?"

"Well," said Smithy, "the ferrite slab is held at its extreme ends by two brackets and the aerial coil takes up nearly all the space between these brackets. So I can't move the ferrite slab and I can't move the coil!"

"That's a funny set-up, isn't it?"

"It's a very annoying one," stated Smithy. "I bumped into a similar situation in another little imported set some years ago and I cursed that one too. Anyway, before going any further, let's see if the coil *does* need to be moved. In other words, lets see if it needs a little more or a little less inductance at the low frequency end of the scale for its resonant frequency to be at the signal frequency selected by the oscillator."

"You mean," asked Dick, "to see if it's resonant at the oscillator frequency minus the intermediate frequency?"

"That's right," said Smithy. "The oscillator frequency selects the signal which is to go into the highly selective i.f. amplifier. It's the function of the aerial tuned circuit to bring that signal up to its optimum level. With these little sets it's particularly important for the aerial coil to be at the correct frequency and give maximum signal boost."

"How," asked Dick, "are you going to see if the aerial coil needs more or

less inductance if you can't move it along the ferrite slab?"

"I have a trick up my sleeve here," stated Smithy. "Have you ever heard of a tuning wand?"

"A tuning wand? No, that's a new one on me."

"Well," said Smithy, "it's an insulated rod which has a piece of iron-dust core material at one end and a brass slug at the other." (Fig. 4.)

"What do you use it for?"

"We used to use it, in the days before ferrite aerials, to check signal tuned circuits in which the coils did not have iron-dust cores. If we wanted to check whether a signal frequency coil needed more inductance we put the iron dust core end of the wand into the coil. This increased its inductance and if, say, signal strength increased as a result then we knew that the coil required more inductance. If signal strength decreased, then we at least knew that the coil didn't need any more inductance. We then put the brass slug end of the rod into the coil. This decreased its inductance, and if the process caused signal strength to increase, then we knew that the coil needed less inductance."

"I get it," said Dick brightly. "Following from this, I suppose that if signal strength decreased both when the iron-dust end was inserted and when the brass end was inserted then the coil inductance was spot on."

"That's the idea."

"How does that apply to this receiver here? You can't poke a tuning wand into its ferrite aerial coil."

"But we can do a very similar thing," said Smithy. "Hang on a bit whilst I have a dig in my junk box."

He walked over to his bench, pulled a cardboard box towards him and rummaged around in its contents. With a grunt of satisfaction he picked out a small object, then returned to Dick.

"What," asked Dick, "have you got there?"

"A four inch length of ferrite rod," replied Smithy. "Now let's see if we can find a station near the low frequency end of this receiver's range."

He switched the receiver on again and tuned in a weak station at the low frequency end of its scale. He then picked up the ferrite rod and, holding it parallel with the ferrite slab in the receiver, brought it up to the slab. When the ferrite rod was about an inch away from the slab the signal



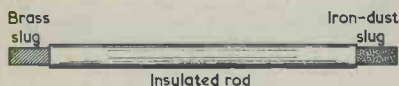



Fig. 4. A tuning wand. This can be made up from scrap materials and a suitable length is of the order of 6 inches

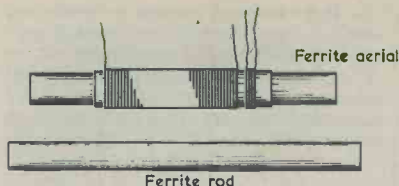

(a)

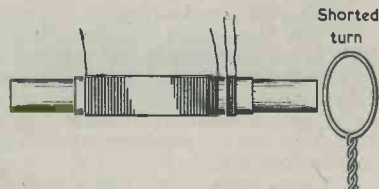

(b)

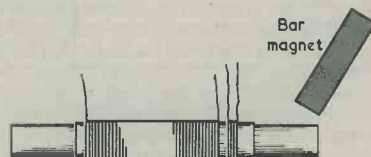

(c)

Fig. 5(a). Bringing a ferrite rod close to a receiver ferrite aerial increases the inductance of the latter. This can provide a simple check to determine whether a ferrite aerial coil requires increased inductance for accurate tracking

(b). The inductance of a ferrite aerial coil may be reduced by bringing a shorted turn up to and, if necessary, over one end of its ferrite rod (c). The ferrite aerial coil inductance may also be reduced if one pole of a bar magnet is brought close to one end of the ferrite rod. This approach is not as effective as that employing the shorted turn, but can still be helpful if the ends of the ferrite aerial rod are inaccessible

commenced to decrease in strength. It grew weaker and weaker and had almost completely disappeared when Smithy had the ferrite rod as close to the slab as was possible. (Fig. 5 (a).)

"What," asked Dick, "does that tell us?"

"It tells us that the aerial coil doesn't need more inductance. Bringing that ferrite rod up to the coil increased its inductance."

"How can you set about decreasing its inductance?"

UNDERSTANDING TELEVISION



by

J. R. DAVIES

Over 500 pages
300 diagrams

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- COLOUR TELEVISION - 80 page section deals comprehensively with this subject

£2-10

P. & P.
40p

To: DATA PUBLICATIONS Ltd., 57 Maida Vale London W9

Please supply copy(ies) of "Understanding Television" Data Book No. 17. I enclose cheque/crossed postal order for

Name

Address

.

. RC
BLOCK LETTERS PLEASE

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English &
American radio and technical
books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ST. HELEN'S RADIO

HI-FI Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10
Tel: 01-969 3657

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.
70-72 Holdenhurst Road
Bournemouth
Telephone 25232

SURREY

WITWORTH TRANSFORMERS

TV Line out-put transformers
Manufacturers of the largest range in
the country. All makes supplied.

Modern
BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.
For "By-return" service, contact
London 01-948 3702

Tidman Mail Order Ltd., Dept. R.C.
236 Sandycombe Road,
Richmond, Surrey TW9 2EQ

Callers welcome.

"If it were an ordinary ferrite rod with its ends free of any mounting," replied Smithy, "I could do it by bringing a shorted turn up to the end of the rod which is nearer the coil under investigation. As the shorted turn approaches the rod it causes coil inductance to decrease in just the same way as the brass slug in the old tuning wand used to do. The shorted turn can just be an odd bit of bare wire with its ends twisted together and having a diameter of about an inch or so." (Fig. 5 (b).)

"Can't you try that here?"

"Not very easily," replied Smithy. "The way that ferrite slab is mounted it's difficult to bring a shorted turn up to it in the required manner. However, I've got another little dodge to fall back on here. Let's have another dig in my junk box."

Smithy once more walked over to his bench. After the sound of further searching in his cardboard box, he returned with another small object.

"What is it this time?" queried Dick.

"A bar magnet," replied Smithy. "Now lets see what happens if I bring one pole of this magnet up to the ferrite slab."

Slowly, Smithy brought the magnet up to one end of the ferrite slab. When it was very close to the ferrite slab the volume level of the signal from the receiver increased noticeably in strength. Smithy took the magnet away again. (Fig. 5 (c).)

"Hell's teeth," said Dick, supremely impressed by this manifestation. "What happened there?"

"Bringing the magnet up to the ferrite slab," explained Smithy, "reduced its incremental permeability and caused the aerial coil to have less inductance. The magnet isn't as effective as the shorted turn, but it does give an indi-

cation when the aerial coil has just a little too much inductance."

"Is there any risk of permanently magnetising the ferrite slab?"

"Not to my knowledge. I've tried this magnet scheme on quite a few rods and slabs, and it's caused no trouble even when the magnet actually touched the ferrite material. If you wanted to play safe you could just ensure that the magnet and rod don't come into contact although as I say, I've never had any trouble on this score myself. The magnet needs to be a pretty strong one. The one I've got here is primarily intended for operating dry reed relay switches."

OSCILLATOR ALIGNMENT

"What do we do next?" asked Dick. "We can't just send this set out with a magnet stuck to the ferrite slab, can we?"

"Not really," chuckled Smithy. "Since we can't change the aerial coil inductance to agree with the oscillator tuning, we'll have to do the next best thing and change the oscillator tuning to agree with the aerial coil inductance. This means that stations from the middle to the low frequency end of the band will be shifted to slightly different places on the tuning scale, but this doesn't matter if we get increased sensitivity as a result."

"What about the trimming capacitors? Will we have to adjust these?"

"Probably not," replied Smithy. "As you know, part of the general alignment procedure for a set of this nature is to trim, by adjusting the trimming capacitance, at the high frequency end of the band. After that we pad, by adjusting the inductance of the oscillator coil and where possible that of the aerial coil at the low frequency end of the band." (Fig. 6.)

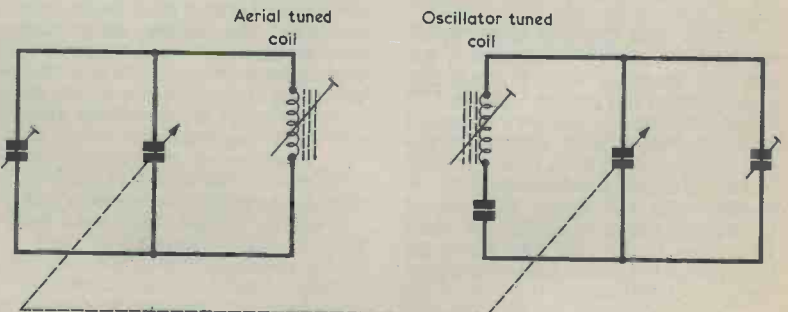


Fig. 6. In a single band superhet r.f. alignment normally consists of adjusting the trimmers at the high frequency end of the band and adjusting coil inductance (padding) at the low frequency end

Smithy looked inside the receiver. "The trimming situation raises no problem," he went on. "There are two trimmers integral with the 2-gang tuning capacitor, and one of these will obviously be the oscillator trimmer and the other the aerial trimmer."

Smithy picked up the receiver and adjusted its tuning control near the high frequency end of the scale. He readily picked up a loud transmission.

"Isn't that Radio One?" asked Dick. "It is," confirmed Smithy. "Now, Radio One is on 1,214kHz, and it's turning up just above the '12' marking on this scale. This would indicate that the oscillator trimmer is set fairly accurately. Let's tune up a little higher."

He adjusted the receiver for a higher frequency and was able to tune in a weak signal near the high frequency end of the scale. He picked up a small screwdriver.

"What, asked Dick, "are you going to do now?"

"Adjust the aerial trimmer."

"But how do you know which one is the aerial trimmer?"

"I don't," replied Smithy. "But I'll soon find out after I've checked what each one does."

Carefully, Smithy adjusted one of the trimmers very slightly. The signal disappeared, then reappeared as Smithy brought the trimmer back to its original setting.

"Adjusting that trimmer," announced Smithy, "gave the same effect as tuning the whole receiver. So that will be the oscillator trimmer, and the other one will be the aerial trimmer."

He applied his screwdriver to the remaining trimmer, and was able to increase the strength of the received signal by a very small amount.

"Not much improvement there," remarked Dick.

"Indeed not," returned Smithy. "Anyway, now that we've checked that the trimming at the high frequency end of the band is all right, we can turn our attention to the low frequency end."

Smithy retuned the receiver to the weak signal at the low frequency end of the scale.

"What come's next?" asked Dick.

"I'm going to readjust the oscillator core so that this signal comes in at maximum strength."

"But," protested Dick, "if you adjust the oscillator core you'll tune the set off the signal."

"No, I won't," replied Smithy, "because whilst I'm adjusting the oscillator core I shall also continually rock the receiver tuning back and forth through the signal. As the tuning scale position of the signal changes I'll be able to keep up with it."

Dick looked at the four screening cans on the printed circuit board.

"The oscillator coil," he remarked, "is certain to be in one of these cans. Do you know which one it is?"

"I'll have to make a guess at it," replied Smithy. "The oscillator coil can

is bound to be near the tuning capacitor and is most likely to be that closest to it. There's one can here which meets that description, so I'll try that first."

Smithy picked up an insulated trimming tool and carefully adjusted the core in the can he had selected. He found that he could tune the signal in and out by adjustment of the core in much the same way as with the oscillator trimmer.

"This is the one," he grinned. "If it had been an i.f. transformer the signal would just have gone down a little in strength without the detuning effect. Right, now I'll finish the job."

Smithy rocked the receiver tuning control across the signal and slowly adjusted the oscillator core setting. He found that as he screwed the core in the signal increased in strength. He very soon reached a setting where the received signal was at its strongest.

"There we are," he said, pleased. "That oscillator core only needed three-quarters of a turn or so. Let's check the trimming again."

The Serviceman returned to the high frequency end of the band, to find that the aerial trimming had not been noticeably affected by the oscillator core adjustment. He then tuned over the whole range of the receiver. It was now patently more sensitive over the middle and lower frequencies.

FINAL STEPS

Dick listened with an expression of unmitigated joy.

"That's really something," he remarked, happily. "That oscillator adjustment has improved the set no end."

He picked up the receiver, switched it off and started to refit the back.

"It is better, isn't it?" replied Smithy, pleased. "I think I should mention that the little bit of alignment I did there should only be attempted with sets having simple trimming and padding arrangements. If the set has a long wave band it's best to leave the trimming and padding alone if the service sheet isn't available. That's because adjustments on medium waves can mess up adjustments on long waves if the alignment isn't carried out as laid down by the maker of the set."

He looked down at his watch.

"Ah good," he remarked, "It's right on packing-up time. Now I must go home and get ready for my evening at the club. I'll be thinking of you while you're working at your aunt's."

"You needn't," returned Dick, grinning. "It looks as though I'll have my evening free after all."

"Free? But you've been moaning no end about this job you had to do for her."

"Not now I'm not."

"Why's that?"

"Because," replied Dick, as he slipped the little radio into his pocket and made hastily for the door, "you've just done it for me!"

Your Local Supplier

SUSSEX

E. JEFFRIES

*For your new television set
tape recorder, transistor radio
and hi-fi equipment*

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

**ELECTRONIC COMPONENTS
RADIO & TELEVISION**

*For the convenience of Irish
enthusiasts we supply*
Radio & Electronics
Constructor
Data Books and
Panel Signs Transfers
Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL

**SUBSCRIPTIONS
to this magazine
may be obtained
through your
newsagent
or direct from the
publishers**

**ONLY £4.00
per year, post free**

*Please send remittance with name
and address and commencing issue
required to:*

DATA PUBLICATIONS LTD
57 Malda Vale London W9 1SN

New Products

SINCLAIR DM2 MULTIMETER



A new portable multimeter from Sinclair combines the precision of a digital instrument with the convenience and low cost of an analogue meter. Priced at £59+VAT the 3½ digit DM2 Multimeter is powered by a single, standard 9V battery which gives up to 60 hours life. A connection is provided for an external 9V stable DC source.

The Sinclair DM2 measures AC and DC volts, AC and DC current and resistance in a total of 20 combinations - 5 functions each with 4 ranges - at a basic accuracy of 0.4 per cent. Operation is by press-button selection and contact is made by two clip probes on long leads.

Large 8mm LED displays, behind a violet screen maintain contrast in high ambient light conditions. Maximum reading is 1.999.

Designed around an MOS integrated circuit the DM2 utilises dual slope integration and features high operational repeatability and reliability. Protection against severe overload is also provided with separate fuses for current and resistance ranges.

Automatic dual polarity, automatic over-range and overload indications are incorporated in the instrument. A high basic input impedance is achieved by a MOSFET op-amp input buffer.

The DM2 Multimeter is housed in a strong, extruded aluminium case which provides complete screening from external interference. Finish is matt black. A carrying handle also doubles as a support for bench top use. Weight is 1kg including battery. Size is 155mm x 225 x 56mm (9in x 6in x 2in) plus handle. Optional extras include a carrying case, £5 + VAT which extends the versatility of the instrument, and a mains converter at £1.85 + VAT. Guarantee is 12 months.

'ELECTRONIC' PLIERS AND CUTTERS



Vero Electronics Limited have announced the introduction of a precision range of 'electronic' pliers and cutters, which are now available from stock.

These tools are drop forged from special alloy tool steels and are manufactured to high standards. All pliers and cutters have pinned hinges and it is this feature, which by creating a movable inside jaw, considerably increases the quality and life of the tools.

In addition all tools are oiled hardened but the cutting pliers are also inductively age hardened (high frequency hardened) and are suitable for both soft and hard wires.

Other features of these pliers and cutters include, polished head and hinge and plastic coated handles with integral spring. Further information from Vero Electronics Limited, Industrial Estate, Chandler's Ford, Eastleigh, Hants.

HANDY PACK TAPPING FLUID

New packaging in the form of a handy 250ml (8.8 oz) tin has been introduced by Isaac Bentley & Co. Ltd. of Naylor Street, Liverpool, for the company's Vincol tapping fluid, widely used in the metalworking industry for thread making.

The new tin will give the product small-user application, for example in DIY work, for electricians threading conduits, and for model makers for more intricate threading.

The new design of tin has a screw top, drip tube to enable the tapping fluid to be applied in exactly the right area and the precise quantity required.

Vincol has particular advantages over other tapping fluids in that its high penetration and lubrication qualities makes it suitable for a wide range of metals, from softer materials to hard alloys, giving a consistently clean thread in all conditions.



VINCOL
TAPPING FLUID

Tap life increased Thread finish improved.

INSTRUCTIONS.

Application spout inside. Apply fluid to tap and hole.

WARNING

Avoid smoking and unnecessary inhalation of the vapour.

Minimum Contents 250 ml (8.8 fl oz).

ISAAC BENTLEY & CO. LTD.
Naylor Street, Liverpool L3 6DS

AN IRI PRODUCT

RADIO MODELLER

ELECTRONIC BOOKS

● MODEL RADIO CONTROL


Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system. 134 pages.

Price £2.25

U.K. Packing & Postage 32p

ON SALE NOW
at all leading shops
or direct from:-

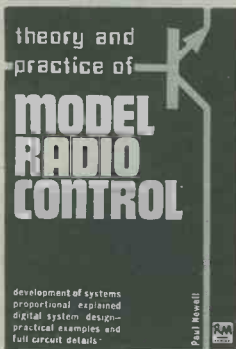**RADIO MODELLER
BOOKS DIVISION,
64 Wellington Road,
Hampton Hill, Middx.**



BUY THIS BEST SELLER

NEW EDITION OF
T.V. FAULT FINDING
405/625 LINES



REVISED & ENLARGED

Edited by J. R. Davies
132 pages **PRICE 90p**

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price 90p from your bookseller.

*or post this Coupon together
with remittance for £1.02
(to include postage) to*

DATA PUBLICATIONS LTD.
57 Maida Vale, London, W9 1SN

Please send me the 5th revised edition of TV Fault Finding. Data Book No. 5

I enclose cheque/crossed postal order for

NAME

ADDRESS

BLOCK LETTERS PLEASE

INTERNATIONAL



SHORT WAVE LEAGUE

Membership £3.75 per annum (U.S.A. \$10.00) including 12 monthly issues of *Monitor* — the League journal. Including free use of all Services, QSL Bureau etc.

**THE LARGEST S.W.L. ORGANISATION
IN THE WORLD**

For full details write to:

**The Secretary,
I.S.W.L.,
1, GROVE ROAD, LYDNEY,
GLOS. GL15 5JE.**

SMALL ADVERTISEMENTS

(Continued from page 635)

FOR SALE: Minuteman 6 calculator £10.00. Sinclair Cambridge £15.50. Sinclair Executive £20.00. Mains auto transformer 8A, £5.00, 16A, £8.00. FM transmitter kit £4.50. Avo 47A £15.00. Low band Pye Rangers £10.00. Philips N2204 cassette recorder £22.00. Portable 8-track with 2 band radio £15.50. Overhauled Avo 8 with calibration certificate £28.50. 110V a.c. 7A stereo amplifier £8.50. C-size rechargeable ni-cad cells £1.50; U7 size £1.25. Box No. G.257.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

WORLD DX CLUB covers all aspects of SWling on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.60 a year. Enquiries to John Rush, 12 Northfield Road, Thatcham, Berks.

FOR SALE: Super Servisol switch cleaner 70p, 5 tins £2.50. 100 feet insulated copper aerial wire 75p. 9-digit calculator £13.50. 4½" watchmaker's pliers £1.00. ¼ H.P. electric motor £5.50. 2" watchmaker's screwdrivers 5p. Second book hi-fi loudspeaker enclosures 60p. Second book transistor equivalents 95p. Sound and loudspeaker manual 50p. BIB34 cassette case £1.50. Hi-Fi test cassettes and cartridges £1.90. Box No. G259.

8 VOLUMES Newnes *Radio & Television Servicing* from Volume 1 to 1959/60 edition. £16.00, post paid. Bell's Television Services, 190 Kings Road, Harrogate, Yorkshire. Telephone: 0423-55885.

GUARANTEED BRAND NEW SEMICONDUCTORS. BC107 transistors gen. purpose n.p.n. 9p; BC177 transistors gen. purpose p.n.p. 11p; 2N3055 transistors, high power 45p; IN4004 diodes, 400V p.i.v., 1A 5p; IN4143 diodes 4p. Data sheets for each of the above 4p. P. & P. 15p per order. VAT extra. C.W.O. All orders despatched same day. Send large s.a.e. for full lists of semiconductors, caps., res., nuts, screws, etc. Nestra Electronics Ltd., Scott Street, Bognor Regis, Sussex.

WANTED: Decoder Type 6, ex Grundig radiogram KS560. Also wanted Tannoy truncated horn speaker. Leevs, Kingsnympton, North Devon.

FOR SALE: 10 pre-recorded cartridges and cassettes £9.00. £1.00 for sample. 100 records £7.50. 25p for sample. Box No. G260.

FOR SALE: Teak finish wooden amplifier sleeves. Internal 3½ x 10½ x 7 ins. £1.75 plus 50p P. & P. 29 Laburnham Grove, Winchmore Hill, London N21. Telephone: 01-360 4499.

FOR SALE: Four Bound Volumes of "Radio Constructor" August 1957 to July 1961. Offers? Not mint but good condition. Box No. G261.


WANTED: *Everyday Electronics* Volume 1 Nos. 1-5, May 1973. Also *Practical Wireless* January 1973. Price please to:- J. W. Farrar, 11 Constantine Road, North Bitchburn, Crook, Co. Durham.

WHEREVER YOU LIVE Partridge have the key, to the DX! World Record patented VFA aerial system guarantees a solution to your short wave reception problem. Stamp for brochure. Partridge Electronics Ltd., Broadstairs, Kent.

(Continued on page 638)

REVOR OPTICAL & TECHNICAL

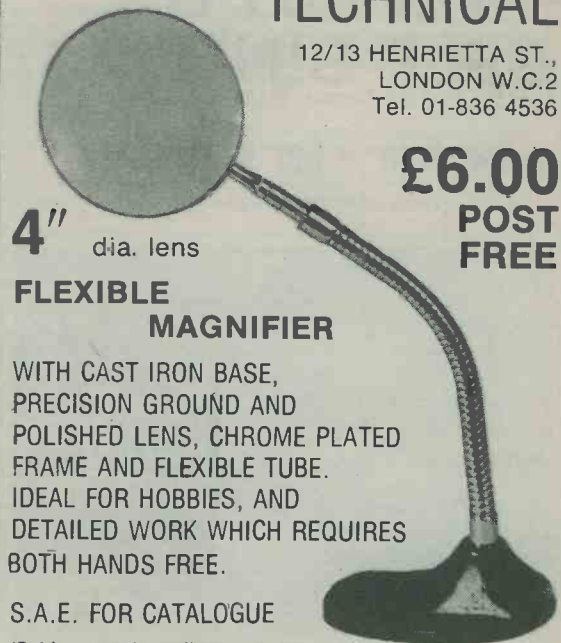12/13 HENRIETTA ST.,
LONDON W.C.2
Tel. 01-836 4536



£6.00
POST
FREE

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

S.A.E. FOR CATALOGUE

(Subject to price ruling at the time of issue)

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through our low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer.

Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



POST NOW

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- | | | | | | |
|---|--------------------------|--|-------------------------------------|---|--------------------------|
| Build-As-You-Learn | <input type="checkbox"/> | Electronic Engineering | <input type="checkbox"/> | CITY & GUILDS Installations and Wiring | <input type="checkbox"/> |
| PRACTICAL RADIO AND ELECTRONICS (with kit) | <input type="checkbox"/> | Computer Electronics | <input type="checkbox"/> | CITY & GUILDS Electrical Technicians | <input type="checkbox"/> |
| Electrical Engineering | <input type="checkbox"/> | Computer Programming | <input checked="" type="checkbox"/> | CITY & GUILDS Telecommunications | <input type="checkbox"/> |
| Electrical Installations and Wiring | <input type="checkbox"/> | General Radio and TV Engineering | <input type="checkbox"/> | Radio Amateurs' Exam etc. etc. | <input type="checkbox"/> |
| Electrical Draughtsmanship | <input type="checkbox"/> | Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> | G.C.E. 58 'O' & 'A' LEVELS | <input type="checkbox"/> |
| Electrical Mathematics | <input type="checkbox"/> | Transistor Technology | <input type="checkbox"/> | Coaching for many major examinations | <input type="checkbox"/> |

To **ALDERMASTON COLLEGE**, Dept. ERE 05 READING RG7 4PF **ERE 05**

NAME (Block Capitals Please)

ADDRESS

POSTCODE

Other subjects' Age

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines
(max. format 7½" x 9½")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE 95p P. & P. 20p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 637)

LONG DELIVERY or discontinued I.C.'s - 2527V, 55 off £160; 2533V, 10 off £75; MM5051, 20 off £65. Enquiries to Box No. G262.

RADIO & ELECTRONICS CONSTRUCTOR. Due to loss in warehouse fire, we require copies of the June and July 1973 issues. Cover price paid, remittance by return. Send to Data Publications Ltd., 57 Maida Vale, London W9 1SN.

FOR SALE: Regulated power supply. PU189, 0-15V, 0.4 amps, meter to monitor voltage. £14.40. Touch sensitive switch drive TTL or relay, £1.25. T. Edwards, Box No. G263.

SERVICE SHEETS for Radio & TV etc. 40p each plus s.a.e. Bell's Television Services, 190 Kings Road, Harrogate, Yorkshire, Telephone: 0423-55885.

WANTED for cash or loan, circuit details of "Lerna-Kit" oscilloscope also *Practical Wireless* April 1971 and other issues containing "Workshop Oscilloscope". Box No. G264.

STEREO JACK PLUGS (standard) desoldered from new equipment, 50p for 5 (including P. & P.). Price for larger quantities on request. 5 Powderham Road, Exeter, Devon, EX2 9BS.

CONSTRUCT Highest performance metal detector for approximately £1. Equal to £50 models. Simple illustrated plans. Send £1. C. H. Lucas, 241 Upminster Road South, Rainham, Essex.

FOR SALE: *Wireless World* April 1964 - December 1974, *Television* August 1971 - December 1974. 10p each plus postage. S.A.E. for enquiries. Box No. G265.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

SHACK CLEARANCE. Diodes (from 1p), transistors (from 3p), valves, transformers, resistors, capacitors, computer boards, PSU, etc. S.A.E. list. Box No. G266.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 4p. Data Publications Ltd., 57 Maida Vale, London W9 1SN.

(Continued on page 639)

RADIO & ELECTRONICS CONSTRUCTOR

SMALL ADVERTISEMENTS

(Continued from page 638)

1972 *World Radio TV Handbook*, only 75p post paid. Bell's Television Services, 190 Kings Road, Harrogate, Yorkshire.

FERRIC CHLORIDE, VEROBOARD, sirens, relays, electronic components, all cheap. List No. 9 6p. Grimsby Electronics, Lambert Road, Grimsby, Lincs. (Callers Saturdays only).

TREMENDOUS VALUE. Pack of over 500 components. Resistors, Capacitors, transistors, diodes, etc. Plus circuit boards crammed with components. Send only £1.50 to: Capital Components, BCM 3276, London WC15 6XX.

1975 **B.A.R.T.G. CONVENTION** will be held this year at the village hall, Meopham, Kent, on Saturday 24th May, from 11.00 to 18.00 hours. The village hall is located on the east side of the A227 road, to the south of Meopham village centre. Transport will meet trains from London at Meopham station until 1.00 p.m.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

YOUNG MAN DISABLED needs work at home. Electronic/wire assembly. Would collect and deliver. Mr. B. Grimes, Llawnen, Glanrhyd, Cardigan, Wales, SA43 3PE.

HOLIDAY ACCOMMODATION. Burwood Lodge Hotel, Dawlish Road, Teignmouth, South Devon. Especially suitable for parents with young children. Facing south, on the cliffs, direct access by private path to the sea. Mothers' kitchen, automatic washing machines, baby listening service. Licensed lounge. Ample free parking.

ARE YOU ADVENTUROUS? If so, you can make exciting new friends. Write: S.I.M. Computer Dating, (REC/3), 109 Queens Road, Reading, Berks.

LONDON COMPANY REQUIRES Partner to establish an independent local branch of expanding business in one of a number of selected areas throughout the British Isles. Box No. G258.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

ESSEX GARDENERS. Buy your Bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

ESSENTIAL BOOKS!

POWER SUPPLIES FOR ELECTRONIC EQUIPMENT. J. R. Nowicki. Published recently in 2 vols. A full treatment of all power supplies is given. Includes rectification, inverters, transverters, silicon diodes and other electronic devices. With full circuit diagrams and component values. Originally published at £4.50 per volume. Bargain price £4 for the 2 volumes incl. postage.

THE MOBILE RADIOTELEPHONE EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus some valuable modification details for COMMERCIAL RADIOTELEPHONE equipment. Price of this edition including postage £6.25.

HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION. 40p, p.p. 15p.

HOW TO MAKE 2M & 4M CONVERTORS FOR AMATEUR USE. Fully comprehensive. Contains circuits layouts, component lists, diagrams and full instructional notes. Price 60p, p.p. 15p.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus valuable information for British/USA receivers, transmitters, trans/receivers. £4 including postage.

DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS! Gives details of surplus wireless equipment stores and dealers including addresses plus equipment and spares that they are likely to have available. A valuable book only 50p, p.p. 15p.

GETTING THE BEST FROM YOUR COLOUR TV. R. Maude. Essential advice for colour TV engineers and owners. Could save you pounds. 50p, p.p. 15p.

THE THEORY OF GUIDED ELECTROMAGNETIC WAVES. The most comprehensive book yet written about waveguides, transmission lines, cavity resonators. Over 500 pages. Ideal for anyone interested in Radar and UHF. Published at £11.50. Special offer £4.50 p.p. 50p.

INTERNATIONAL DICTIONARY OF SEMICONDUCTORS. A 2-volume electronics dictionary published at £16 available at less than half price. In 7 languages it proves an invaluable addition to any collection of electronics reference books. Contains are 1373 pages packed with information. In leather styled finish. Only £6.50, p.p. 50p.

THE RADIO CONTROL MANUAL. Contains numerous plans, photographs and instructions. A large format hardback book published at £1.25. Bargain price 60p, p.p. 20p.

THE THEORY AND DESIGN OF MAGNETIC AMPLIFIERS. 487 pages. Published at £1.75. Bargain price 75p, p.p. 25p.

WORKED EXAMPLES IN ALTERNATING CURRENT. A must for the student, technician and electrical engineer. Contains numerous examples and how they were arrived at. Published at £1.25. Bargain price 60p, p.p. 20p.

THE BARGAIN BOOK GAZETTE. Contains thousands of interesting new and out of print books at bargain prices. Subjects include all types of hobbies, collecting, 1001 interests. Published regularly and sent free on request.

Dept. R. C. GERALD MYERS (Publisher & Bookseller), 138 Cardigan Rd., Headingley, Leeds 6, Yorks. (Callers Welcome).

MORSE MADE EASY!!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. IN 4 WEEKS GUARANTEED. Complete course, 3 Records and Books, £4.95 incl. P.P.I. etc. (Overseas surface mail £1 extra. (Or details only, 4p stamp. Or phone S. Bennett, G3HSC, 01-660 2896.

Box 38, 45 GREEN LANE, PURLEY, SURREY.

BARGAIN COMPONENT PARCELS contain some very useful bits and pieces. Save yourself £s on these well selected parcels 2 kilos nett weight £1.80.

BRAND NEW WIRE-WOUND RESISTORS 1-7 watts, good selection, 100 for £1.55.

ASSORTED CAPACITORS, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection 300 for £1.55.

SPECIAL OFFER — Metallised Polyester Capacitors by Brie, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed, 100 for £1.95.

Please note all prices include Postage and V.A.T.

MAIL ORDER ONLY
XEROZA RADIO
1, EAST STREET,
BISHOPS TAWTON,
DEVON

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN
 Please insert the following advertisement in theissue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 5p
= 75p.

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

I enclose remittance ofbeing payment at 5p a word. MINIMUM 75p.
 Box Number, if required, 10p extra.

NAME.....
 ADDRESS

Copy to be received four weeks prior to publication. Published on the 1st of every month.

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
132 pages. Price 90p, P. & P. 12p
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**
88 pages. Price 70p, P. & P. 10p
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price 75p, P. & P. 15p
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price £2.10, P. & P. 40p
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 53p, P. & P. 12p
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price 80p, P. & P. 12p

I enclose Postal Order/Cheque for.....in payment for.....

NAME.....
 ADDRESS

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.
 Overseas customers please pay by International Money Order.
 All publications are obtainable through your local bookseller.
 Data Publications Ltd., 57 Maida Vale, London W9 1SN*

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

COMMON MUSICAL TERMS II

The Table gives generally accepted definitions of common musical terms, and completes the list started in Data Sheet No. 97.

Meno	less	Rallentando	with decreasing speed
Mezzo-forte (mf)	half loud	Reprise	repeat of a passage
Mezzo-piano (mp)	half soft	Requiem	Mass for the dead
Mimuet	graceful slow dance	Ritardando (rit.)	slower
Moderato	in moderate time	Ritenuito (riten.)	held back
Molto	much, extremely	Rondeau	form of poem
Molto fortissimo (fff)	same as fortissimo	Rondo	movement, musical setting for a rondeau
Molto pianissimo (ppp)	same as pianissimo	Rubato	in irregular rhythm
Mosso	moved	Saraband	slow Spanish dance
Motet	sacred cantata	Scherzo	lively, playful passage
Moto	motion	Scordato	out of tune
Non	not	Scordatura	stringed instruments intentionally detuned
Obbligato	musical accompaniment of independent importance	Secco	plain, unaccompanied
Pastorale	idyllic opera or cantata	Sforzando (sfz)	sudden emphasis on chord or note
Pianissimo (pp)	very soft	Sostenuto	sustained
Pianississimo (ppp)	as soft as possible	Spirito	spirit, energy
Piano (p)	soft	Staccato	abrupt, disconnected
Piu	more	Stringendo	accelerating the tempo
Pizzicato	strings plucked	Tarantella	Neapolitan dance
Plain-song	recitative choral music	Tempo	time, rhythm
Poco	little, small	Tremolo	continual variation of amplitude
Polka	Bohemian dance	Troppo	too much
Polonaise	Polish dance	Tutti	all
Prelude	introductory movement, prefatory piece	Vibrato	continual variation of pitch
Prestissimo	as quick as possible	Vivace	lively, vivacious
Presto	quick, quicker than allegro	Vivacissimo	very lively
Prima	first		
Prima-donna	leading female singer		

