

The Wireless Constructor

6^D
MONTHLY

EDITED BY
PERCY W. HARRIS

CONTENTS.

Vol. I. No. 2. DECEMBER, 1924.

HOW TO MAKE:
A SEVEN-CIRCUIT CRYSTAL SET.
A CABINET SINGLE-VALVE
RECEIVER.

Both by Percy W. Harris.

MORE ABOUT THE RESISTOFLEX.
By John Scott-Taggart, F.Inst.P., A.M.I.E.E.
REFLEX CIRCUITS IN PICTORIAL
FORM.

HOW TO LAY OUT A PANEL.
HOW TO ADD A VALVE TO YOUR
PRESENT SET.

By E. Redpath.

HOW TO CHOOSE A VALVE.

By R. W. Hallows, M.A.

TUNING THE NEUTRODYNE.


Hundreds of Practical Hints and Tips
for the Beginner.

1/6 Blueprint
FREE inside.



BLUE PRINT FREE IN THIS ISSUE

For Detection—Use H.F.

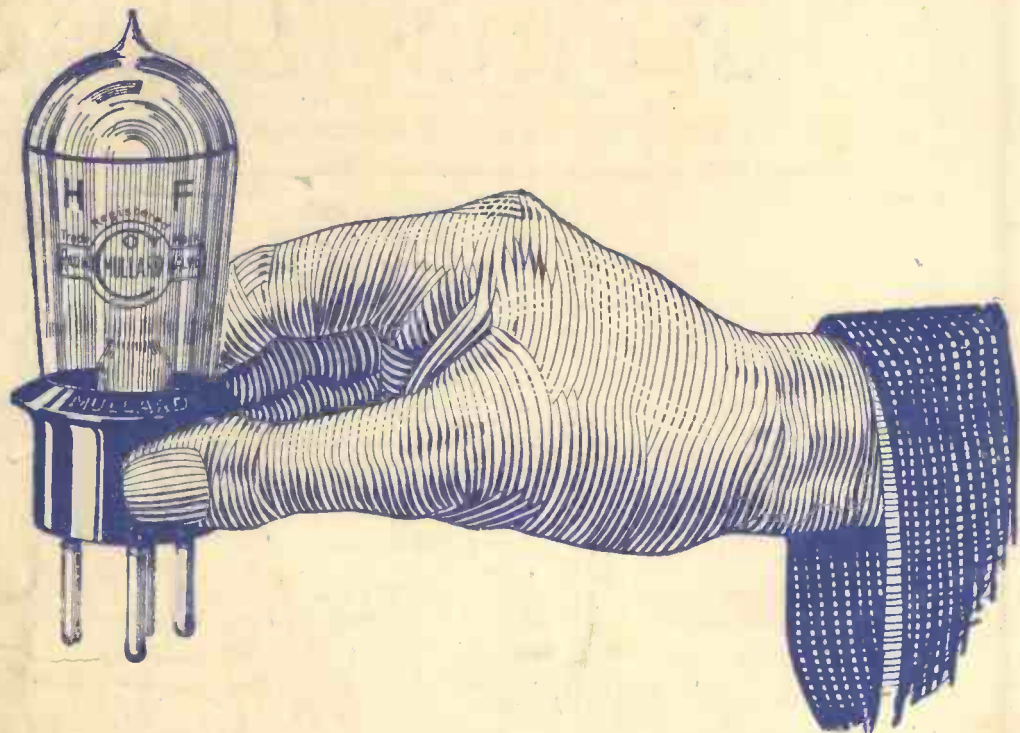

MASTER VALVES have MASTER REASONS

FOR DETECTION—USE MULLARD H.F. VALVES.

Because : MULLARD H.F. VALVES have positive grid current.

Reason : Grid current is essential for the operation of a grid leak detector : without grid current there can be no grid leak rectification.

FOR H.F. AMPLIFICATION—USE MULLARD H.F. VALVES.

Because : MULLARD H.F. VALVES have the correct amount of positive grid current.

Reason : Positive grid current is necessary for stability in H.F. operation.

FOR L.F. AMPLIFICATION—USE MULLARD L.F. VALVES.

Because: MULLARD L.F. VALVES have NO harmful positive grid current.

Reason : Positive grid current damps L.F. amplification and causes distortion.

Stipulate MULLARD H.F. Red Ring Valves for H.F. AMPLIFICATION AND DETECTION—12/6 each.

Stipulate MULLARD L.F. Green Ring Valves for L.F. AMPLIFICATION—12/6 each.

These Master Valves only require a 4-volt battery.

Leaflet M.8 can be obtained from your dealer, and avoid accident to your valves by asking for the Mullard Safety disc, free on request.

Send us his name and address, if you cannot get what you want, and we will supply him.

MULLARD WECO, 1-volt ORA, and D.F. ORA, are now reduced to 25/-

Mullard

THE MASTER VALVE

The WIRELESS CONSTRUCTOR

— Edited by Percy W. Harris —

VOL. I. No. 2.

DECEMBER

CONTENTS

The Seven-Circuit Crystal Set By TH: EDITOR.	87	More About "The Wireless Constructor" Neutrodyne Set	125
How to Lay Out a Panel	94	By PERCY W. HARRIS.	134
Wireless in Germany	97	How it Works. The Rheostat	138
The Resistoflex Receiver	98	Radio Press News	141
By JOHN SCOTT-TAGGART, F. Inst. P., A.M.I.E.E.		Six Simple Crystal Valve Circuits in Pictorial Form	147
WJAZ, America's Portable Broadcasting Station	101	Some Radio Questions Answered	153
A Simply-Made Single-Valve Receiver	103	Practical Workshop Hints	157
By PERCY W. HARRIS.		When the Beginner Buys a Valve	160
Something About Galena	111	By R. W. HALLOWS, M.A.	
By CHARLES H. BUTCHER.		Adding a Valve to a Crystal Set	160
A Single-Valve Portable Set...	116		
By NORMAN K. JACKSON.			



SQUARE LAW CONDENSERS at the price of ordinary

Fallon's, in accordance with their usual custom, are giving the public the benefit of the improvements they have effected in their new model Square Law Condensers without increasing the price.

The New Fallon Square Law Condensers, which embodies all the features which have made the Fallon A.11 model world-famous, are absolutely the last word in perfect condenser construction.

Extremely handsome appearance, all parts being heavily plated .068 spacing (the closest possible). In the new model the overall length of the .001 condenser is only 4 1/4 ins. as against 5 1/2 ins. in the old model, and by a new idea in spacing washers, rigidity of construction, never before achieved in any make of condenser, has been obtained.

FALLON FIXED CONDENSERS

Fallon FIXED Condensers are made of the highest quality mica and copper foil, each one tested and guaranteed. Fitted with soldering tags and nuts for making clean connections.

Features include—
ONE HOLE FIXING, TAG CONNECTIONS, HEAVY ALUMINIUM TOP AND BOTTOM PLATES. Metal to metal adjustable bearings, stout, well-cut aluminium vanes. Complete as illustration.

Reputation.—A condenser with the name Fallon imprinted indicates the finest obtainable.

Plates.	Price.
.001	8/-
.005	6/-
.003	5/6
.0025	5/-
.002	4/6
Vernier	5 4/-
Vernier	3 3/8

Capacities up to .001 ... 1/3 each.
" .0015 and .002 ... 2/-
Fallon FIXED Condensers are right up to "Fallon" Standard.

Write direct for Trade Terms.

FALLON CONDENSER CO., LTD.,
The Condenser People. Tottenham 1932.
WHITE RIBBON WORKS, BROAD LANE, TOTTENHAM, N.15.

All Correspondence and Post Orders to above address
City Depot: 143, Farringdon Road, E.C.1. Manchester Depot: 3, King Street West, Deansgate. Glasgow Depot: 120, Wellington Street.



IGRANIC
Concert Coil.

Make a point
of seeing



or

Stands 9 and 14


at the

RADIO EXHIBITION &
WIRELESS CONVENTION

WHITE CITY,

Shepherd's Bush, W.12

Nov. 15 to 29

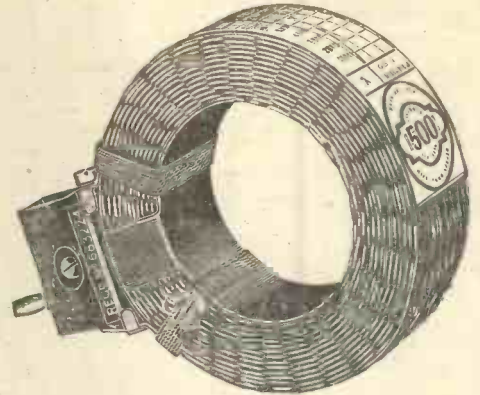

IGRANIC
Plug Mounted Coil.

Honeycomb—the ideal Inductance

Low self-capacity—Small Absorption Factor—Minimum H.F. Resistance—No dead-end losses—High self-Induction—these are the qualities of the ideal inductance. They are found to perfection in IGRANIC Honeycomb Duolateral Coils.

Because Igranic Honeycomb coils are so wound that each wire (except where insulated wire comes in contact) is surrounded by an air pocket, *the self-capacity and also the absorption factor is very low.*

Because the surface area of the wire used in the making of Igranic Honeycomb Coils is as large as is compatible with the maintenance of the air pockets, *high-frequency resistance is at its minimum.*

Because Igranic Coils may be obtained in 20 sizes to cover wave-lengths between 100 to 23,000 metres there is a type for the wave-length you use, which will thus ensure *complete absence of dead-end losses.*

Because of these characteristics of Igranic Coils one may transfer to the detector and utilise the maximum of energy and so obtain the highest efficiency.

If you feel that you are not getting the best results—get Igranic Honeycomb Coils and start better reception to-day.

IGRANIC Radio Devices include: Honeycomb Coils, Variometers, Variocouplers, Bi-plug Coil Holders, Tri-plug Coil Holders, Filament Rheostats, Battery Potentiometers, Intervalve Transformers, Vernier Friction Pencils, etc. *They carry a six months' guarantee and are obtainable of all reputable dealers.*

Write for List Z293.



Birmingham—73-74,
Exchange Buildings.

Bradford—18, Woodview
Terrace.

Cardiff—Western Mail
Chambers.

Glasgow—50, Wellington
Street.

Manchester—30, Cross
Street.

Newcastle—90, Pilgrim
Street.

IGRANIC Honeycomb Concert Coil

This coil has been specially developed to provide for the reception of the B.B.C. concerts and the telephony transmitted by experimenters on shorter wave-lengths. For purity of tone, distortionless reproduction, and maximum volume it fills a long-felt want.

Prices: 4/10, 5/- & 5/2 according to wave-length.

IGRANIC Plug Mounted Coil.

Made in twenty sizes for wave-length ranges of 100 to 23,000 metres, each size having a definite wave-length range dependent upon the capacity of the condenser used in association with it.

Prices from 5/- to 15/- each.

IGRANIC Gimbal Mounted Coil

This coil is mounted upon two gimbals, or studs, positioned diametrically opposite, and these form the terminals and the means of fixing to the coil holder. As a result, it is possible to obtain a wide range of precise and accurate adjustments. As in the plug mounted type, it is made in twenty sizes providing the same approximate range of wave-lengths.

Prices from 4/10 to 15/- each.

149, Queen Victoria Street, London
Works: Elstow Road, BEDFORD.

The WIRELESS CONSTRUCTOR

Scientific Adviser:
Prof. G. W. O. HOWE,
D.Sc., M.I.E.E.

Advisory Editors:
Prof. R. WHIDDINGTON
M.A., F.Sc.

Prof. C. L. FORTESCUE,
M.A., M.I.E.E.

Staff Editors:

E. H. CHAPMAN, M.A.
D.Sc.

A. D. COWPER, M.Sc.
R. W. HALLOWS, M.A.

G. P. KENDALL, B.Sc.
S. G. RATTEF,
Member I.R.E.

Vol. 1.

DECEMBER, 1924.

No. 2

THE "SEVEN-CIRCUIT" CRYSTAL SET

By the Editor.

I WONDER how many designs for crystal sets have been published since first the broadcasting boom began? We have had crystal sets with sliders, crystal sets with variometers, crystal sets with plug-in coils, crystal sets without plug-in coils, and even crystal sets in match boxes. Every design has had its adherent and many people will swear by a form of circuit which others condemn as inefficient. With so many designs available and such a wealth of advice proffered, the beginner in wireless may well feel puzzled as to which set to make.


In this article I am going to show you how to build a crystal receiver which you will find on building is distinctly more efficient than the average crystal receiver, while its construction is of the simplest character. In this very simplicity there are certain virtues, not all obvious even to the more advanced experimenters. When you have built the set you will probably find it is better than

any you have previously tried. Any crystal receiver can be divided into two parts. We have, on the one hand, the apparatus which enables us to tune the aerial to the wavelength we desire to receive, and on the other hand, we have to provide a detector and a pair of telephones; if signals are

the knob of the variable condenser. In the past it has been customary to wind the coil with fairly thin wire so as to occupy a small space, but experiments lately have shown that distinct virtues rest in the use of thick wire, and my own work goes to show wire of No. 16 gauge double cotton covered is preferable to practically any other.

A good crystal receiver should be so adjustable that any wavelength within the British broadcasting band can be received with ease, for while it is generally not possible to receive more than one station (the nearest) it must be remembered that THE WIRELESS CONSTRUCTOR goes to every part of the country and the design must suit any of the B.B.C. stations.

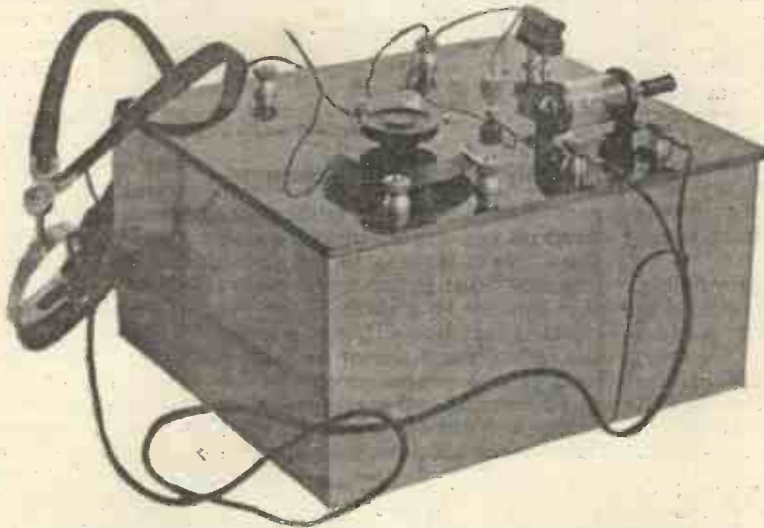Now, if we tune a given coil with a variable condenser, the width of the wavelength band which can be covered with the condenser depends upon the size of the condenser. Thus a coil may tune from 200 to 300 metres with one condenser, while a larger



This set is designed to give the highest efficiency on any aerial.

strong, of course, we can operate several pairs of telephones. The tuning apparatus can take a variety of forms and in this case takes the shape of a coil of thick wire and a variable condenser. There are no sliders to give trouble, and tuning is effected by varying




condenser may tune the same coil from 200 to 350 metres. It is not advisable to have a very large condenser with a tuning coil, for when the value is great the signal strength tends to suffer. I have therefore provided certain tappings on this coil and a simple arrangement of plugs and sockets so that a wide wavelength range is coverable with a reasonable sized variable condenser.

A Novelty

The particular virtue of this instrument, however, is its ability to serve for a number of different kinds of tuning circuits, out of which the experimenter can choose that which best suits his own aerial. I can say from experience that an arrangement which is effective on one aerial is quite unsuitable on another, which accounts to a very large extent for the various preferences shown by different people. In *Modern Wireless* for September last I published a description of a crystal receiver which has achieved remarkable popularity, largely, I think, owing to the several different kinds of circuit that are possible with it. I have received hundreds of letters from all parts of the country speaking in the highest terms of the set, and a large number of readers have given me particulars of the arrangement which best suits their own conditions. Many readers have obtained the best results on an arrangement which on my own aerial proved the poorest. In the present receiver even more variations are possible.

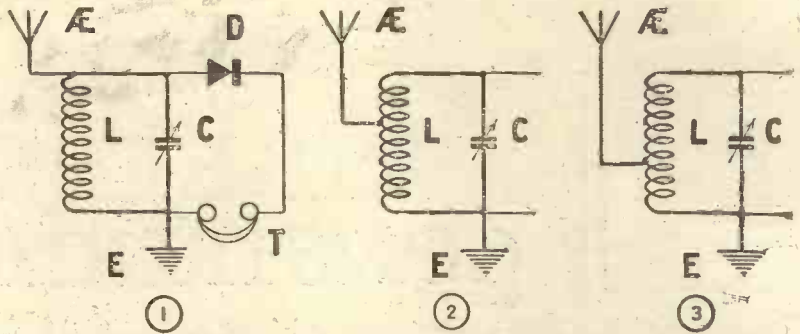If you examine the collection of circuits on this page you will see in diagrammatic form the various arrangements possible. We may, for example, include all of the inductance in both aerial and detector circuit. Another arrangement enables us to use two-thirds



Three useful circuits. For simplicity the crystal and telephones are shown only in the first diagram.

and still another one-third of the total inductance. The last of these arrangements will only be used on very large aerials or with very short wavelengths. Another arrangement which many people will find effective uses only


be received. With some aerials louder signals would be obtained with this arrangement, and in those cases, of course, the additional selectivity is a further advantage.

The appearance of the instrument is quite pleasing and should vie with the best of the commercial sets. The components are relatively few and the cost quite low, while the work should not tax the abilities of the veriest tyro. Let us see what we need.

Components


Both appearance and efficiency are improved by mounting the parts on an ebonite panel, provided, of course, the ebonite is of good quality. The only real safeguard is to purchase ebonite of a well-known make, being sure that it is guaranteed free from leakage by the makers. New recruits to the wireless ranks may wonder why I lay emphasis on this point, but the more experienced know that much of the ebonite sold is made in such a way that the surface conducts electricity instead of preventing its flow. The surface layer with such ebonite has to be removed by the laborious process of rubbing it with sand or emery paper. Guaranteed ebonite is free from the need of this preliminary treatment, and whilst it may cost a little more than the cheap varieties of unguaranteed ebonite, it is well worth the additional cost. In the instrument under description I have used a high-grade insulated material known as "Radion Mahoganite." It has a beautifully finished surface and a grain resembling rich mahogany. Any of the guaranteed ebonite advertised in this journal can be used with certainty of satisfaction. The size of the panel is 10 in. by 9 in.

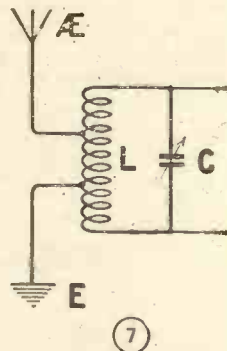A suitable box for this will be needed, and I recommend you to buy this ready made. A number of dealers will supply a box to these measurements, and




A highly selected arrangement.

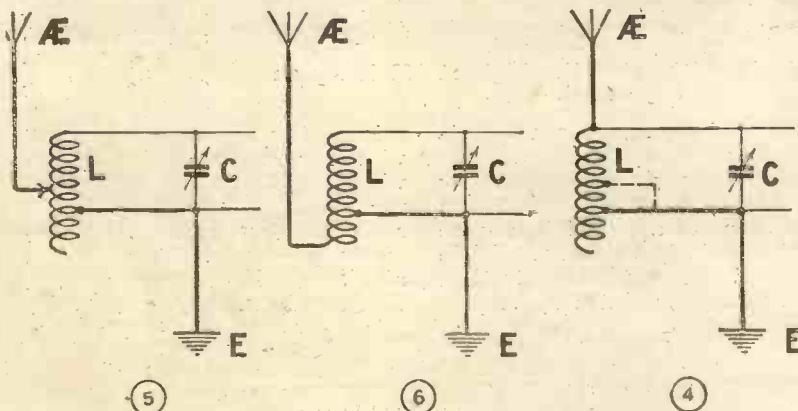part of the inductance (either one-third or two-thirds) in the aerial, the whole of it being in the closed circuit. In those cases where the listener is disturbed by the interference from ship's signals, the arrangement shown in Figs. 3 and 7 will prove excellent, for these circuits are particularly selective and cut out a great deal of interference which would otherwise



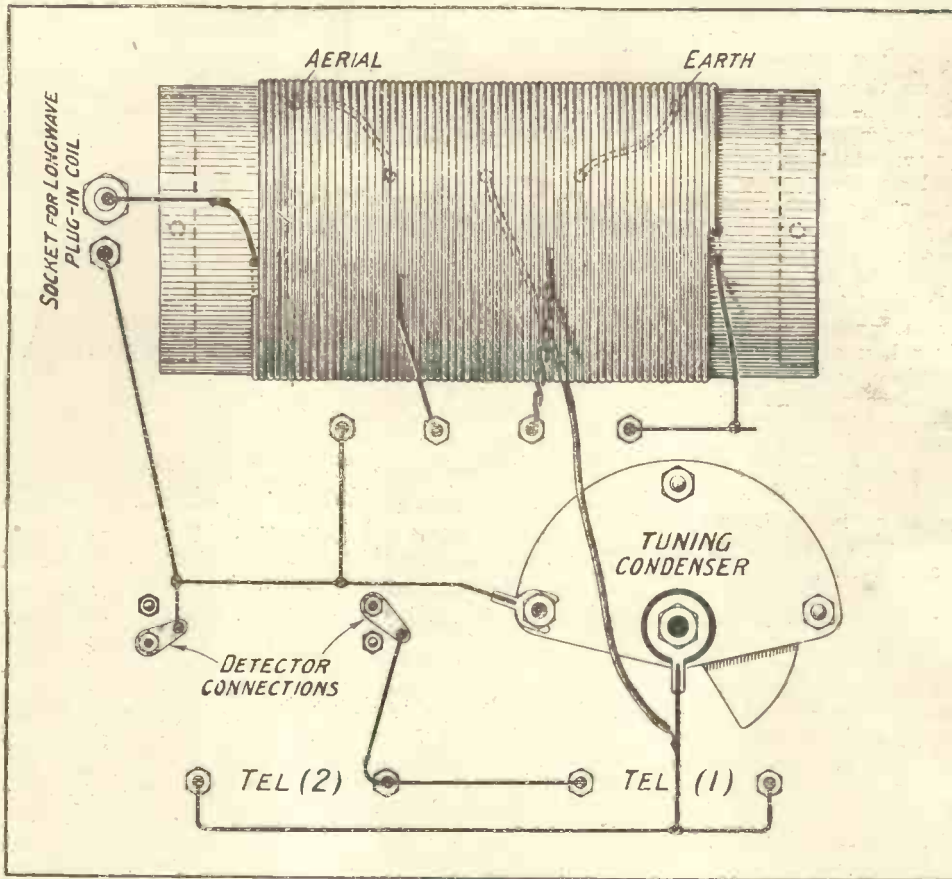Three more interesting circuits. In Fig. 4, the dotted line shows an alternative connection.



The back of panel wiring is very simple.

the quality, of course, will depend on what you care to spend.

The remaining components are :
 One cardboard tube 3 in. diameter, measuring 7 inches long.

About $\frac{3}{4}$ lb. No. 16 D.C.C. wire (don't be put off with anything smaller, if you want to get as good results as I have obtained).

Two small pieces of wood cut as shown to support the tube against the panel.

Four Clix sockets.

Three Clix plugs.

One variable condenser square law .0005 mfd. (I have used a "Fallon" here. There are a number of square law condensers on the market of good quality, so that you will have a wide choice of make.)

Six terminals. (There are two pairs of terminals for telephones as most people use at least two pairs.)

One crystal detector. (I have used a Burndept glass enclosed. Here, again, you have a wide choice, as any good crystal detector will do. If you buy a detector to stand without a crystal then you will need to fit one of the modern crystals marketed under a trade name ending with "ite." There are so many good makes available that there is no point in naming any particular one.)

One socket for plug-in coils.


One short-circuiting plug for this socket.

Notice I do not specify a telephone condenser which forms a part of so many designs. I have found such condensers unnecessary and no longer incorporate them in my crystal set designs. If you have any doubt on the subject, try connecting such a condenser across the telephones. You will probably find it makes no difference

whatever, either in quality or strength of signals.

The Cabinet

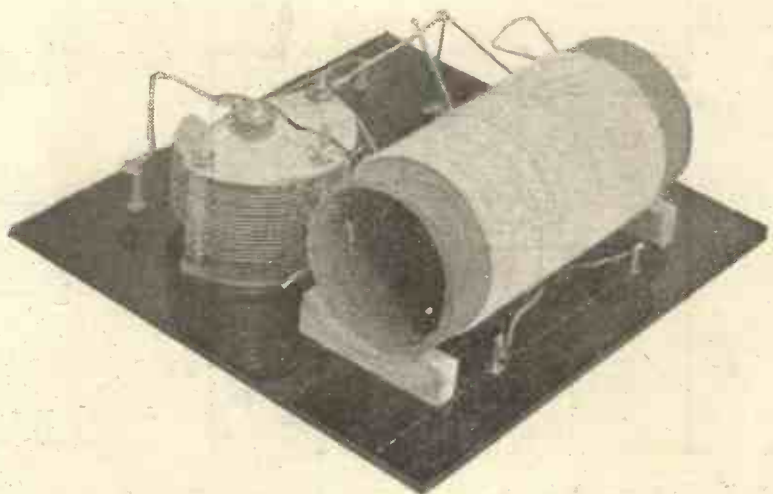The simplest way to start, of course, is to buy a cabinet ready fitted with an ebonite panel, but if you buy a piece of ebonite not exactly of the size needed, you will have to cut it to shape, which you can do with the aid of a hack-saw. Hints on marking out and drilling ebonite panels are given



A perspective view.

on another page of this issue, so I need spend no time in giving particulars here. Make all the holes needed in your ebonite, including one or two small ones to hold the panel to the cabinet, and mount your terminals and crystal detector together with the variable condenser. If your variable condenser should not be of one of the makes designed for one-hole fixing, you will probably find in the container box a paper or cardboard template, which you lay on the panel as a guide for drilling. Here, again, I would refer you to the article on laying out and drilling panels. When the terminals, crystal detector and variable condenser have been mounted on the panel, this can be laid aside and work begun on the coil.

None of the work in making this receiver is difficult, but winding the coil is certainly not the easiest. Until you have the knack, No. 16 wire is liable to give some trouble and you must, at all costs, avoid making kinks. The best way is to buy the wire in a hank of about a foot in diameter, and to enlist




How to wind the coil. Keep the turns close to one another with the thumb, and wind tightly.

the help of some other member of the family in winding the coil.

Winding the Coil

Take the cardboard former and at about 1 in. from one end make two holes about $\frac{1}{2}$ in. apart of a size that the No. 16 wire can pass through. Push one end of the wire through one hole and bend

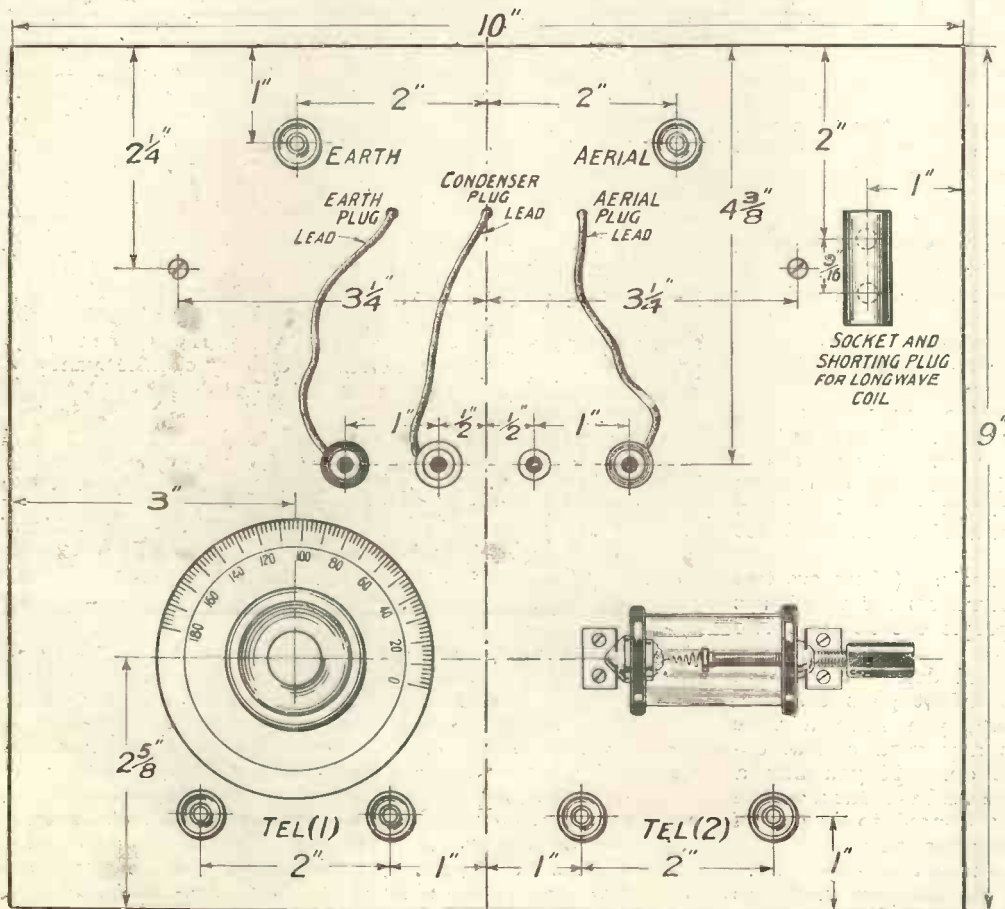it round so as to bring it up through the second hole, leaving about 6 in. projecting. The bends will secure the wire in place, as it is quite stiff and does not easily slip out of the securing hole. Now get someone else to hold the hank of wire and to pay it out to you by rotating the hank as you wind the wire on to the former.



Drilling diagram of the receiver. One or two pairs of telephones are provided for.



When it is desired to hear Chelmsford, the shorting plug is withdrawn, and a number 150 coil inserted.

You will see from the photograph how to wind this, your thumb being used to hold the wire firmly in place and against the adjacent turns. Carry on with your winding until you have wound 60 turns, then, without leaving go of the wire, pierce two other holes and thread the end of the wire in one hole and out of the other, giving a slight bend as before to secure in place. Leave at the end about 6 in. free for connecting.

A Warning.

Your coil will now be finished as far as winding is concerned. Do not shellac or paraffin wax this coil or treat it in any way with paint or varnish. I am inclined to think that any slight advantage gained by waterproofing the coil is lost in other directions. Now take two pieces of ½-inch wood and shape them as shown in the picture, using two small wood screws at each end to hold the cardboard former to its wooden support.

When you have done this count 20 turns from one end and at the 20th turn raise the wire slightly by pushing a pocket knife underneath it. With another knife, or in some similar fashion, scrape away the cotton covering from this 20th turn for about ¼ in. A match pushed underneath this turn will cause it to stand out from the other turns. Treat the 40th turn in the same way.

Now solder two short lengths of wire to the 20th and 40th turns; do not worry about

the exact length of these wires at the moment, 6 in. will do. Now take a smooth file and file the ends of the terminals and the Clix sockets and tin these carefully with solder. The variable condenser will probably have terminals or it may possess soldering lugs. If these latter are provided then

off any superfluous wire when you find out how much you want. You can use either flexible wire in insulating sleeving, or square section tinned copper wire as you will. The square section tinned wire is better and is probably slightly more efficient, although in this receiver you will not notice the difference between the two kinds of wire. All other wiring connections are obvious.

Flexible Leads.

You will notice there are three holes in the panel through which I have passed three flexible leads, which on the underside of the panel are joined to the points shown. These are made from untwisted electric lighting flex. You will see there are three of these flexible wires, one joined to aerial, the second to earth, and the third to the moving plates of the variable condenser. These wires are passed through the panel and are cut off to such a length that the Clix sockets which are attached to the end of them will just reach nicely into any of the sockets shown. In attaching the ends of the wires to the Clix plugs you need not use solder. It will be quite sufficient if you use the gripping screw provided. Do not pass the wire through the top hole as this will



The various combinations of plugging are very fascinating.

the lugs can be tinned at the same time.

Fixing

With all the points tinned, secure your coil to the panel as shown by a couple of wood screws through the top, and begin your wiring up. A half scale wiring diagram is given on page 89, and this will be sufficient guide for you. Solder the four coil connections to the four Clix sockets as shown, cutting

be needed as a socket in some arrangements. When you have finished wiring up and fitting the plugs and sockets, secure the panel to its cabinet and join aerial and earth wires to the terminals shown. A pair of high resistance telephones should be connected to either pair of telephone terminals, and the catwhisker of the detector placed in contact with the crystal.


Place the aerial plug in the extreme right-hand socket, the earth plug in the second socket from the left, and the condenser plug in the back of the earth plug. This will give you the second circuit in Fig. 1, and will probably enable you to tune in your local broadcasting station quite easily. Insert the short-circuiting plug in the coil socket (this socket is only used for the loading coil used for 5XX), and turn the knob of your variable condenser. You will soon pick up the station, and a little adjustment of the crystal detector will give you good signals if you are not more than 10 or 15 miles away. If conditions are favourable, you will get strong signals at much greater distances than this, but generally I do not recommend a crystal receiver for use more than 15 miles from a station, unless the reader is willing to put up with weak signals.

Experiments

When you have satisfied yourself that the crystal is properly adjusted and that you are getting good signals and tuning properly you will probably want to experiment with the other circuits, and this you can easily do by varying the position of the plugs. The only change necessary to receive Chelmsford is to withdraw the short-circuiting plug and to plug in a No. 150 coil, tuning with the condenser dial as before. The

aerial plug must be kept in the right-hand socket and the condenser and earth plugs in the last on the left. If you are pleased with the set write and tell me about it. I receive so many letters that

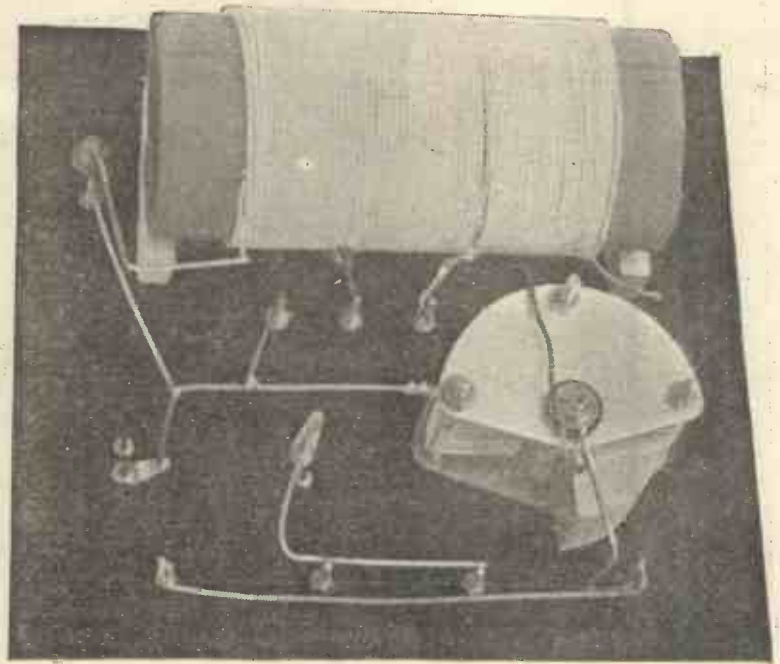I cannot reply to them all individually, but readers' reports of results are always welcome and in a large number of cases, when published, are of great interest to other readers in the same locality.



A further view of the panel wiring.

A REMARKABLE CHRISTMAS NUMBER.

The third issue of THE WIRELESS CONSTRUCTOR will be the finest yet published. Two big features will be:—

THE WIRELESS CONSTRUCTOR "TWIK-VALVE" RECEIVER.

MR. SCOTT-TAGGART'S great contribution to simplicity in home loud-speaker reception. A FREE BLUE-PRINT of this set will be presented with each copy.

THE "SPECIAL-SIX." A new Harris set with THREE STAGES OF HIGH FREQUENCY AMPLIFICATION.


The work of many months' close study of the problems of high frequency amplification.

A LOUD-SPEAKER AMPLIFIER

For your Crystal Set. Full Constructional Details.

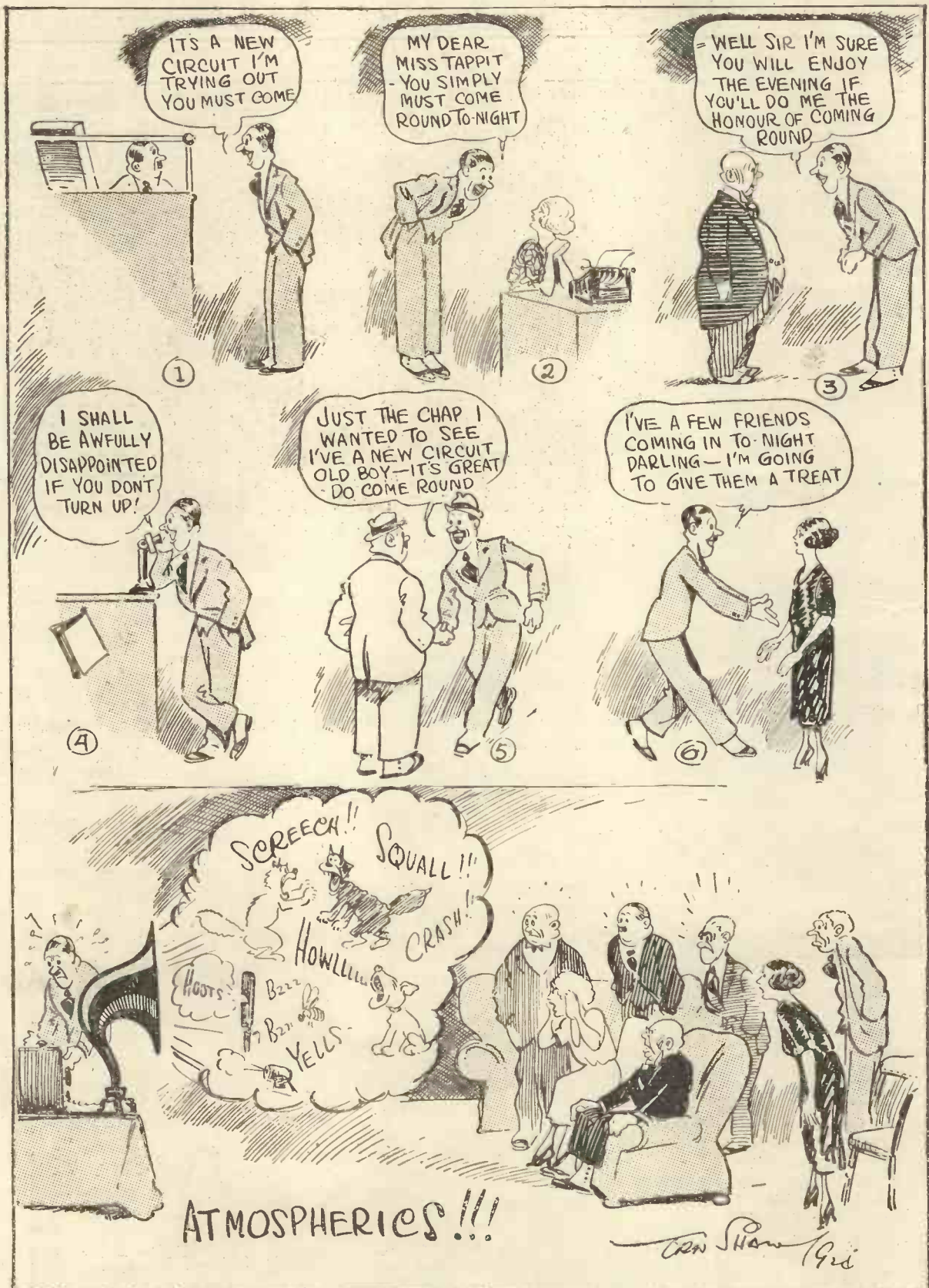TWO NEW REGULAR FEATURES WILL START IN THIS ISSUE, OUT 15th DECEMBER. ORDER EARLY.





HAS IT EVER HAPPENED TO YOU?

HOW TO LAY OUT A PANEL.

THE series of photographs given here have been specially prepared to indicate the correct methods of marking out a panel. For the beginner the importance of correct procedure cannot be too highly stressed, and a careful perusal of the following will help to lay the foundation for consistent and accurate work in this respect.

The tools necessary for this work are few, and consist of a 12 in. steel rule, suitably engraved in inches and sub-divisions (the Metric System has not yet come into extensive use for wireless work),

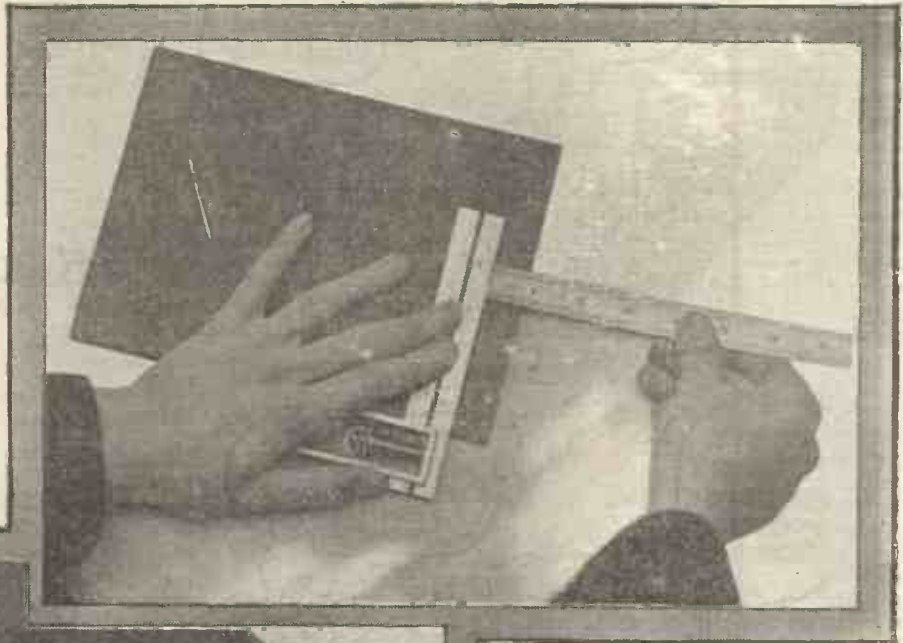


Fig. 1.—Measuring distance for Terminals.

finishing the last edge in the same way.

It is never safe practice to mount your terminals nearer than $\frac{1}{4}$ in. from the edge of the panel, and the photograph of Fig. 1 illustrates the correct method of marking off this distance. All such markings should be made on the underside of the panel, using the scribe. It will be observed that the square is used in the left hand.

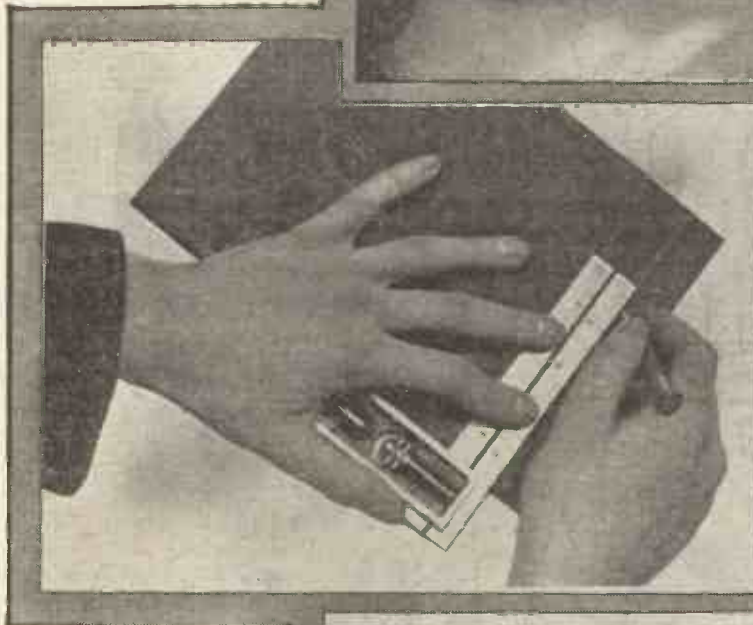


Fig. 2.—Scribing guiding lines.

an accurate square as shown, a small light hammer, a steel scribe and a centre punch.

If your ebonite is guaranteed free from surface leakage, work may begin at once, otherwise it will be necessary to remove the surface with fine emery paper, a final finish and polish being given by washing the surface with methylated spirit containing a trace of vaseline.

True up the longest edge, mark off the required length and square up the two shorter edges,



Fig 3.—Laying out Terminal Positions.

Do not forget that on the back of the panel the order of parts is reversed.

The photograph of Fig. 2 indicates the method of marking a line parallel to the edge and at a distance of $\frac{1}{4}$ in. from it. The positions for the terminals, which should preferably be spaced not less than $\frac{1}{2}$ in., are marked out as shown in the next photograph (Fig. 3). A point to notice here is that the eye should be placed vertically over the point of the scribe to avoid errors due to parallax, and that a short line at right-angles to the marking line, and not a dot or indentation on the panel surface, should be made.

The centre punch is then used as illustrated in the photograph of Fig. 4. The point is placed at the intersection of the lines, the punch placed vertically, and given a sharp tap on the head with the hammer. This will make an indentation sufficient to give a start for the drill


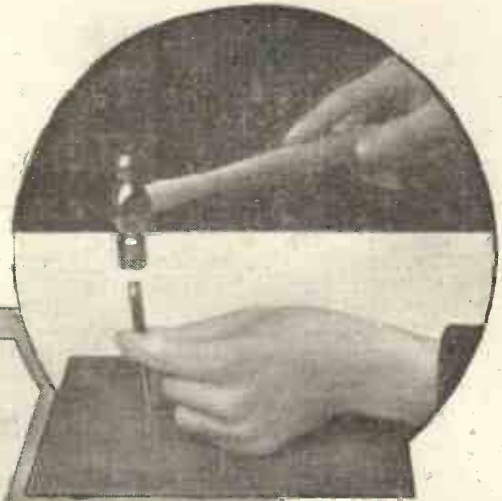


Fig. 4.—Using the centre punch.

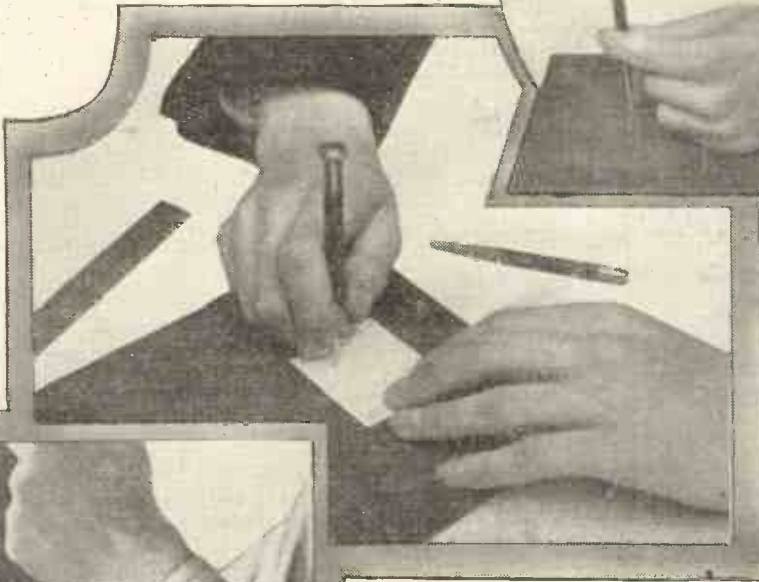

the template. This method is not recommended, and readers are advised to prick the positions of the holes through the template with a sharp pointed scribe, subsequently removing the template and using the centre punch as described.

Fig. 5.—How to use paper templates.

For all the above operations a centre reference line should be first scribed on the panel.

Fig. 7 illustrates the method of marking distances to the left or right using the centre line for reference.



Fig. 6.—Be sure to hold the drill vertically.

in drilling the holes to accommodate the shanks of the terminals.

Many manufacturers are now supplying templates with certain types of apparatus to facilitate the marking out and drilling of panels, and the photograph of Fig. 5 shows the method of employing these. Some constructors place the paper or thin cardboard template in the required position on the panel and punch the necessary holes through

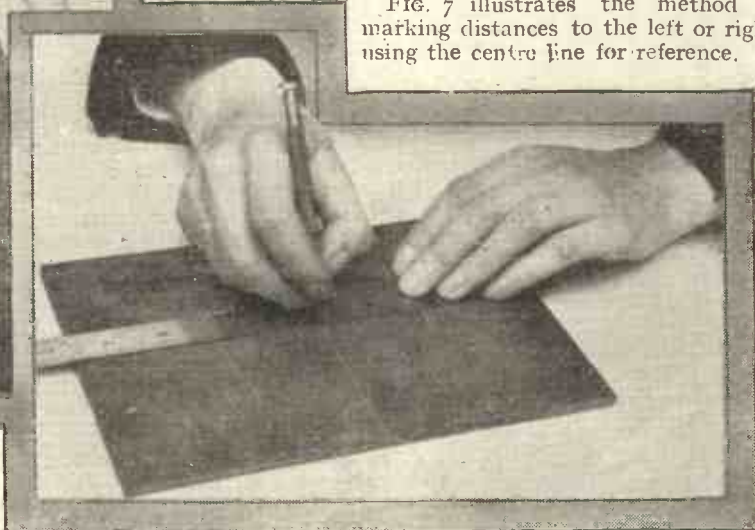


Fig. 7.—It is helpful to mark out from a middle line.

Having completed the marking out of the panel, using only the tools previously mentioned (on no account should a lead pencil be employed), the drilling may be commenced. Systematic drilling of all holes of the same size is recommended, thus obviating many changes of drills, and consequent loss of time. The drilling operation is illustrated


in the photograph of Fig. 6. A final clean up and polish is given to the panel after the operations of marking out and drilling have been performed.

In conclusion, one cannot be too emphatic in advising strict adherence to the methods outlined above.

Unsymmetrical panels, lacking in symmetry, will thus be avoided, and the constructor will be amply repaid for any extra trouble incurred. Efficiency and elegance approaching that of the best commercial receivers should be the aim of every wireless constructor.

A Drilling Tip

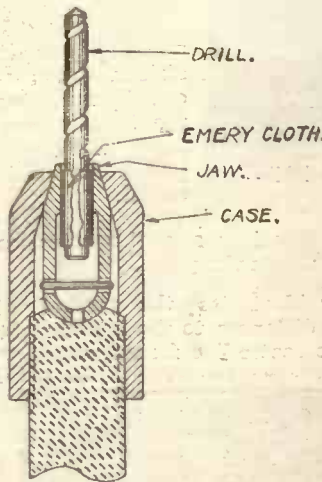If drills are used in a carpenter's brace, it will be found that there is a tendency to slip. This can be obviated by wrapping a



SECTION THROUGH CHUCK.

thin strip of emery cloth round the shank of the drill before placing it in the chuck. The accompanying sketch shows the method clearly.

Receiving Broadcast without Crystal or Valve.

By J. F. Johnstone (5 LG)

SEVERAL crystal set owners seem to have made the discovery that they can sometimes still hear the local station *very faintly* with the crystal removed and the cats'-whisker making contact with a perfectly empty crystal cup.

The writer once succeeded in receiving quite good Morse signals using the contact between a telephone tag and his finger and thumb as the rectifier, and without any kind of tuning apparatus. However, on this occasion the station was *very* near and *very* powerful.

The results obtainable by the above means are in the majority of cases very poor when the nearness and power of the transmitting station are taken into account, and the signals are in no way comparable with those produced by orthodox receiving apparatus under similar conditions.

Nevertheless, it occurred to the writer that it might be worth while to carry out a few experiments to see if some such contact could not be discovered which would give some really useful results. For this purpose a tuner of proved efficiency was used, with 'phones attached and provided with two terminals to which the contacts to be tried could be connected.

As it seemed likely that in the case of the cat's-whisker-empty-crystal-cup contact the rectification was produced at the slightly oxidised surface of the brass cup, a start was made with a contact between a piece of copper wire and a piece of steel (a metal that oxidises very readily indeed). It was found that when the copper

wire was laid lightly across a slightly rusty (oxidised) needle, and a good contact was made at another part of the needle, quite good rectification was obtainable. The signals were not, indeed, quite as good as those produced by a really good crystal set, but music and speech from 2ZY at eight miles distance was pleasantly clear and distinct on a moderate outside aerial.

It was found that a *very* rusty piece of iron gave, if anything, somewhat inferior results to the *slightly* rusty needle. The copper wire (about No. 22) had to be laid across a rusty place *very lightly* and then moved about until the best results were obtained.

Radio Press Information Department

OWING to the tremendous increase in the number of queries, and the policy of the Radio Press to give expert advice and not merely "paper circuits," it has been found necessary to enlarge our staff dealing with such matters. In view of the expense incurred, we are reluctantly compelled to make a charge for replies of 2s. 6d., according to the rules below.

All queries are replied to by post, and therefore the following regulations must be complied with:

- (1) A postal order to the value of 2s. 6d. for each question must be enclosed, together with the coupon from the current issue and a stamped addressed envelope.
- (2) Not more than three questions will be answered at once.
- (3) Complete designs for sets and complicated wiring diagrams are outside the scope of the department and cannot be supplied.
- (4) Queries should be addressed to Information Department, Radio Press, Ltd., Bush House, Strand, London, W.C.2, marking the envelope "Query."



THE BARGAIN.

Wireless in Germany.

The Vox Haus Station.

Now that German stations are frequently heard in England, the Article below will be read by many with interest.

DR. ING. MAX. M. HAUSDORFF called in to see us the other day and gave us some details of the Vox Haus broadcasting station in Berlin.

There are two stations operated by the same programme in the evenings. One of the stations has the power of $1\frac{1}{2}$ kilowatt and the other 600 watts. The wavelengths used for these stations are 500 metres and 430 metres, respectively.

Two Stations

The high-power station is supplied by the German wireless firm Huth, while the smaller powered station is run by the Telefunken Company, another big wireless concern in Germany.

The 430-metres station is for use in Berlin and district, whereas the $1\frac{1}{2}$ kilowatt station is intended to cover Germany generally.

Why there should be two stations working on wavelengths so close together seems very curious. We suggested that the 500-metres station with $1\frac{1}{2}$ kilowatt could be received by Berlin listeners even better than the 600-watt station on 430 metres. The idea of having two stations of similar wavelengths and power and, be it noted, a similar programme reminds us of the professor who had a special dog-kennel made with one opening for the parent and a smaller separate opening for the puppy which inhabited the same kennel.

Simultaneous Work


These stations work together in the evening from a single programme, which on special occasions is also radiated from Königswusterhausen. This latter station

works on 2,600 metres with 5 kilowatts power.

Licensing

It is interesting to note that the Deutscher Radio-Club, which corresponds to our Radio Society of Great Britain, is the licensing authority in Germany; at any rate, wireless receiving licences are issued by the Government, but reliance is entirely placed on the discretion of the Deutscher Radio-Club, which actually issues the licences and decides who is competent to have an experimental licence, and to whom only a broadcast receiving licence shall be given.

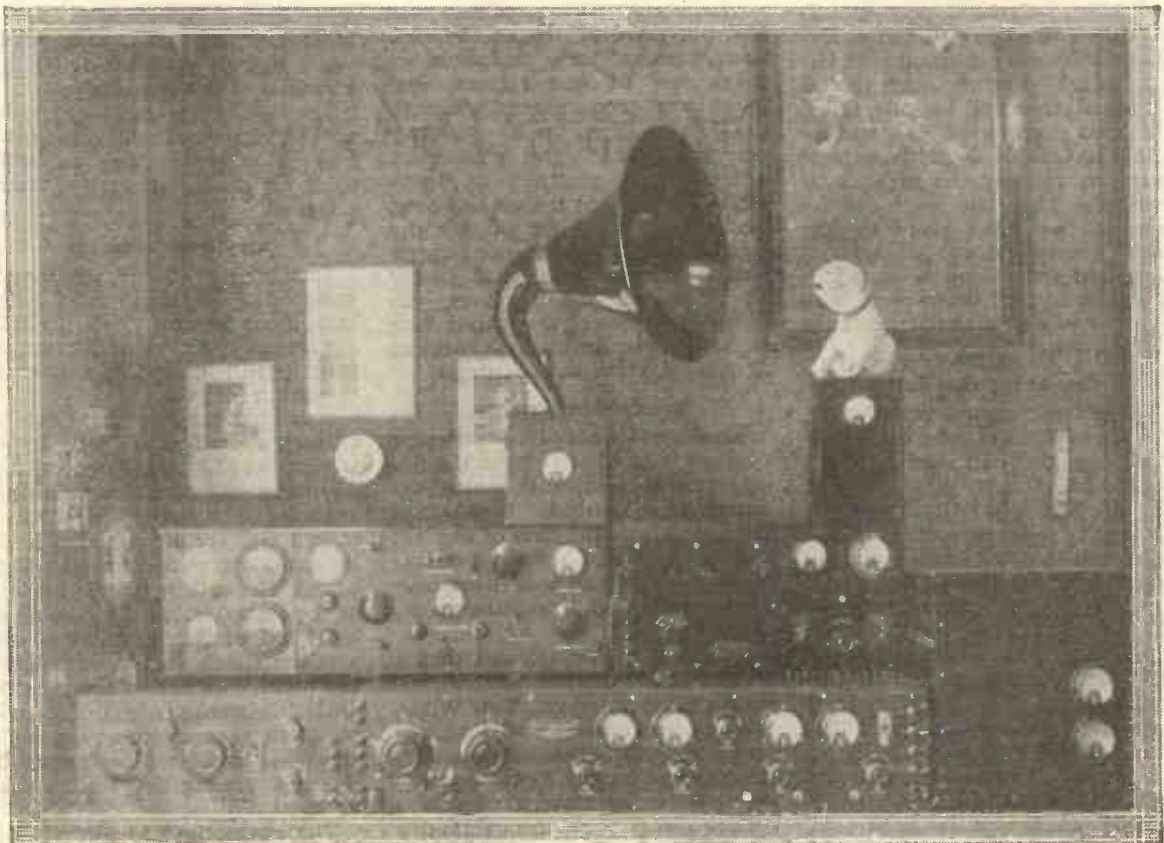This delightful arrangement contrasts with the British Post Office attitude towards recommendations for transmitting licences made by the R.S.G.B.



Dr. Hausdorff's receiving apparatus. The long cabinet at the bottom houses an American built superheterodyne.

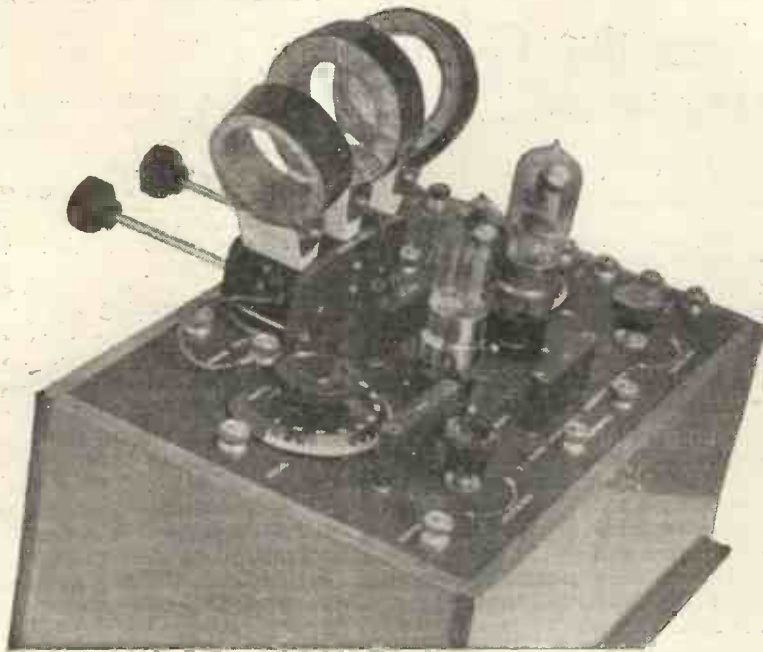


Fig. 7.—The disposition of the components on the panel is clearly shown here.

THE instructions given in the first part of this article should enable the reader to obtain a good idea of the general layout of the different components, but three additional photographs are shown in Figs. 7, 8 and 9, and the actual wiring diagram is in the form of a blue print, which should be found inserted in this issue. This blue print is full size; and by its aid no trouble should be experienced in making the right connections. The photographs of the back of the panel given in last month's issue, and also in this issue, show how the wiring is arranged. It will be noticed that square wire is employed and that the joints are all soldered.

Operating the Set

When first connecting up the set, I would advise the use of a No. 50 or a No. 35 plug-in coil in the aerial circuit, *i.e.*, the left-hand coil of Fig. 7. The middle coil may be a No. 50 or a No. 75, and the actual value will depend largely on the tendency of the receiver to oscillate. The larger the coil the more easily will the set oscillate; so that to be on the safe side it is probably as well to use a No. 50 coil in the anode circuit. The grid circuit of the second valve—*i.e.*, the right-hand coil of Fig. 7—is a No. 75 or a No. 50. The former value will usually be suitable if a .0003 μ F variable condenser is connected across the coil. For the relay stations and stations using wavelengths near 300 metres a No. 50 coil had better be used, but for the

longer wavelengths, including 2LO and above, a No. 75 should be employed.

Troubles to Expect

When the ST100 circuit was first published in *Modern Wireless* there were hundreds, and probably thousands, of constructors who failed to get proper results, although the description was perfectly straightforward and accurate. Letters were received at these offices saying that the set had been made exactly as described, but the results were very inferior, or no results at all were obtained. After about six months, however, the complaints ceased altogether, and reports of excellent results came in from all parts of the country.

Faulty Components

The first instinct of a constructor of a set is to blame either the designer or the paper in which the design is published. Nothing is more unfair in the case of any set described in Radio Press publications, because the actual set may be inspected and, in suitable cases, demonstrated.

It must be remembered that a quarter of a million wireless enthusiasts have bought THE WIRELESS CONSTRUCTOR, and that out of this huge total there are bound to be some who buy faulty components or make some mistake. Troubles do not always occur through faulty wiring; this is one of the least frequent causes of a set not working properly. Faulty soldering and faulty components are responsible

THE RESISTOFLEX RECEIVER.

BY

JOHN SCOTT-TAGGART,

F.Inst.P., A.M.I.E.E.

.....
The second part of an article which commenced in our November issue.

for a great deal of trouble. Many readers seem to be under the impression that if they go into a shop and buy something like that illustrated in a photograph they will obtain satisfaction. As a matter of fact, it is, as a general rule, extremely unsafe to buy anything which does not possess a name. It may be merely an imitation of some successful component, but made of inferior materials, such as cheap insulating "composition."

Anode Resistances

In this particular set you may be tempted to buy some weird nameless anode resistance or gridleak. An inferior anode resistance, of course, will completely spoil the operation of the whole set. A variable anode resistance which has packed up will also stop the set working at all. A faulty condenser anywhere will also give trouble.

Probably the most likely trouble with a receiver of this kind is the incorrect connections to the three coils. The coil in the grid circuit of the second valve, *i.e.*, the right-hand coil of Fig. 7, has two connections which go to terminals on the panel. It makes a very great deal of difference indeed which way round these connections are made, and you should try both ways by simply reversing the leads on the terminal.

The connections to the grid coil of the first valve (*i.e.*, the aerial coil) are, of course, equally important. When first connecting up your set, the aerial coil, the

left-hand one of Fig. 7, should be kept flat, *i.e.*, well away from the middle coil. The right-hand coil of Fig. 1, which is in the grid circuit of the second valve, should be coupled tightly to the middle coil. If, when tuning-in the two variable condensers, oscillation is

Now, leaving everything else as it is, reverse the connections to the aerial coil and note the effect. The next change, after leaving everything as in the last experiment, is to reverse the leads to the right-hand coil.

In all these cases try varying

battery terminal is connected to the H.T. - terminal. The L.T. + and the L.T. - terminals are, of course, connected to your accumulator, and to begin with, if you like, you can join G.B. + and G.B. -, the grid bias terminals, by a piece of wire. Don't forget these terminals, as many readers often do; either short-circuit them or connect a battery between them so that the positive terminal of the grid battery is connected to G.B. + and the negative terminal to G.B. -. With the ordinary general purpose valves I have found that about - 3 volts on the grid of the first valve is desirable.

Tuning

Many a beginner makes the mistake regarding correct tuning. Remember that you should not only be able to tune in a signal, but tune it out. In other words, if you get a station on 30° of your variable condenser, you should be able to tune the station out below 30° and also tune it out above 30°. Unless you are able to tune out on both sides, you do not know that you are getting the signal at its maximum strength. Another point to remember is to work on as low a value of your variable condenser as possible, and rather than use a small coil and 150° on your variable condenser, use a larger coil and, say, 20° on your condenser; your signal strength will be louder on the latter adjustment in nearly all cases.

Signal Strength

Remember that this set involves only a single stage of low-frequency amplification, whereas the ST100 involves two stages of low-frequency amplification. You must con-

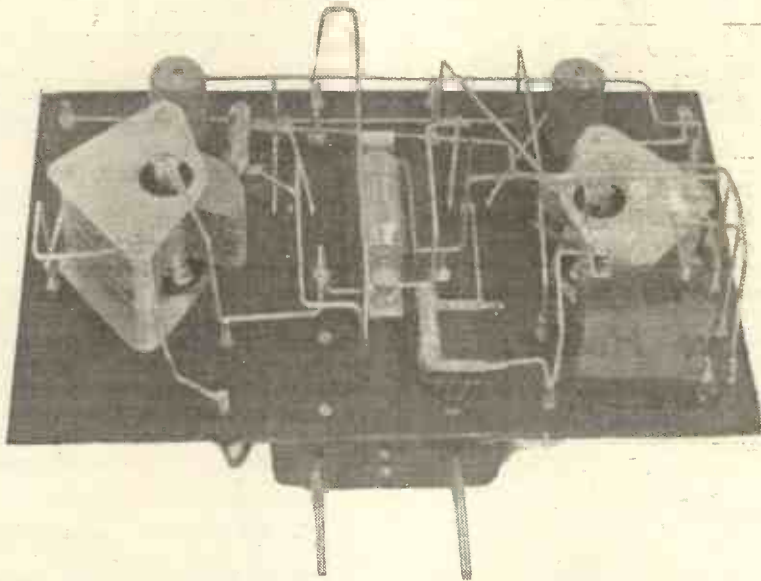


Fig. 8.—A back-of-panel view of the wiring.

set up, try reversing the connections to the aerial coil on the left of Fig. 2. The connections to this coil govern the reaction in the set, although there is always the normal reaction effect, even though the aerial coil is not near the middle coil. If this is experienced to such an extent that self-oscillation occurs, a reversal of the leads may stop the trouble.

Control of Oscillation

A surer method is to loosen the coupling between the middle coil and the right-hand coil of Fig. 7, but this coupling should not be loosened any further than is absolutely necessary to stop the set from oscillating, because it will weaken signal strength somewhat.

You will also probably be able to lessen any tendency to oscillate by turning down the filament current of the first valve, although this, of course, must also be done with caution so as to stop oscillation without affecting signal strength.

Summarising these remarks, I would advise you to try the following arrangement. Keep the left-hand coil of Fig. 7 down and the right-hand coil close to the middle coil. Provided the set does not oscillate when you are tuned in, try reversing the leads to the right-hand coil, and see if signal strength improves.

the coupling between the different coils, always, of course, re-tuning on the two variable condensers whenever any alteration is made.

Try the effect of pulling out one or both of the two plug-in condensers in the middle of the set.

Remember to connect the battery terminals correctly. To begin with, you can connect H.T.₁ to H.T.₂, and join these two terminals to the positive terminal of the high-tension battery of about 100 volts; the negative of this high-tension

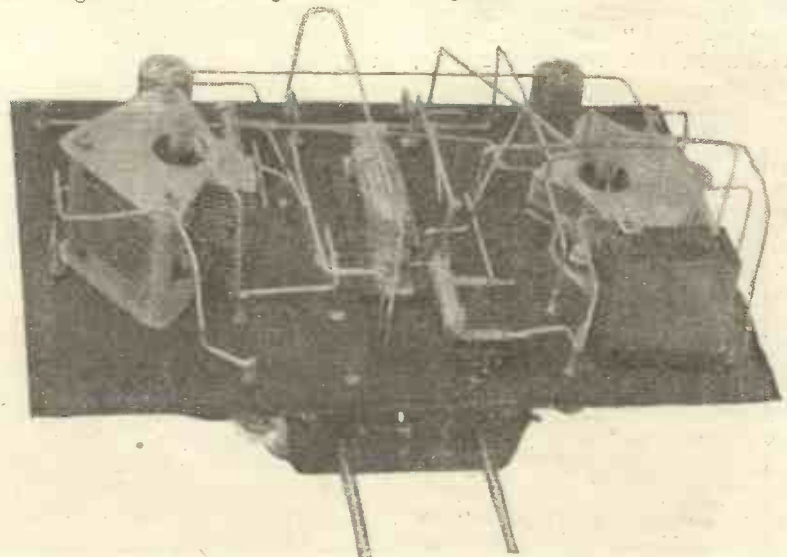


Fig. 9.—The components are adequately spaced.

sequently not expect the same degree of signal strength. Moreover, the resistance method of low-frequency coupling does not give as strong signals as a transformer. These facts, of course, must be borne in mind when the set is being used.

High-Tension Voltage

The high-tension voltage is very important, and I very strongly recommend using nothing short of 100 volts with this receiver. Many readers, I know, will use lower voltages and perhaps be disappointed in the signal strength.

If you like you can try different anode voltages on the two anodes. There are two high-tension positive

terminals on the set, H.T. +₁ and H.T. +₂. You can have two Wander plugs in your high-tension battery, each being connected to one of these high-tension terminals, and you can consequently vary the anode voltage applied to each valve.

**Radio Press
Blueprint
Service**

Write to the Sales Manager, Radio Press Ltd., Bush House, Strand, W.C.2., for list of blueprints available at 1/6 each post free

FAME !

A letter from Czechoslovakia has been delivered to us with the following on the envelope :—

PRAHA VII,
Belskeho Trida Cisko 58,
Czechoslovakia.

To
The scientist and Constructor of Radio receivers, among others, the famous ST 100.

SIR SCOT-TAGARD,
in


LONDON.

I beg the English post to be kind enough and to find the man of the unknown address as soon as possible for which I beg to receive my heartiest thanks in advance. Surely some of the radio enthusiasts will have his plans and constructions at hand and with it the name of the publisher with which the whole riddle will be solved at once.

**An Improved Valve Holder:
with very low capacity.**

MANY improved forms of valve sockets have been placed upon the market with the object of reducing the capacity present between the valve-pins. One hint for instance is to drill a number of holes through the panel between the valve-sockets, allowing an air-space and so reducing the capacity.

A great improvement on all such methods is the simple one illustrated in the sketch. The valve is mounted upside down in a small wooden box packed with soft felt or cotton-wool, and supported by a wire loop. The connecting wires are then soldered directly to the valve-pins. This method of mounting is, of course, not suitable for a cabinet type of receiver, but the experimenter's "bread-board" receiver is easily adaptable, with improved results,

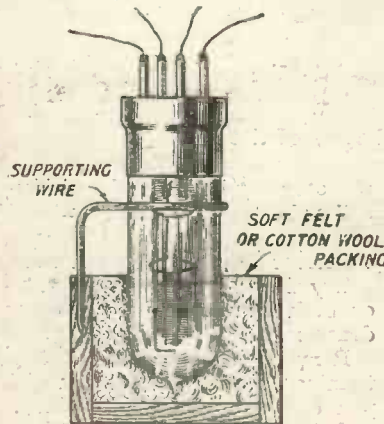

This diagram shows how the valve is held.

especially where, say, two stages of high-frequency amplification are used and the set is at all unstable.

The writer even goes a step further in order to reduce all unwanted capacity. The metal cap round the base of the valve is removed by applying heat from a Bunsen burner, rotating the valve slowly and taking care that the flame does not touch the glass. When the cement softens the cap can be removed and the moulded filling cut away, leaving the glass valve only with its four connections protruding, to which the wires to the set are directly soldered and the valve mounted as described above.

In addition to greater stability on ordinary wavelengths, a very great improvement is, of course, experienced on the extra short wavelengths.

" 2 AUH."



Our photograph shows the pupils of the L.C.C. school at Broadwater Road, Tooting, during a wireless lesson. This subject now forms part of the school's routine.



A description of a station which is arousing great interest among American broadcast listeners.

THE Zenith Portable Broadcasting Station, WJAZ, is a complete self-contained, self-sustaining, battery operated broadcasting station, able to function entirely without any external sources of supply and carrying its own collapsible aerial. The station can be set up in the

The set is of 100-watt power, and uses four 50-watt valves, two as oscillators and two as modulators. All the apparatus is completely panel-mounted. The inductances, capacities and other apparatus are mounted behind these panels in a cabinet equipped with glass sides, allowing easy observation of the

entire construction and interior of the set. Electric lights are provided inside the set for the same purpose.


The entire truck is electrically lighted with spot-lights on the panels, as well as a number of spot-lights designed to illuminate the aerial mast, which is of sectional type such as was used by the Army during the war, and 53 ft. in height.

The aerial is certainly novel, consisting of four heavily braided copper cables made of extremely fine wire, this making them extraordinarily flexible. These wires are provided at each end with snap-hooks which are attached to rings which fasten to two spreaders. Clips are provided on each spreader for connection purposes.



The station is mounted on a lorry.

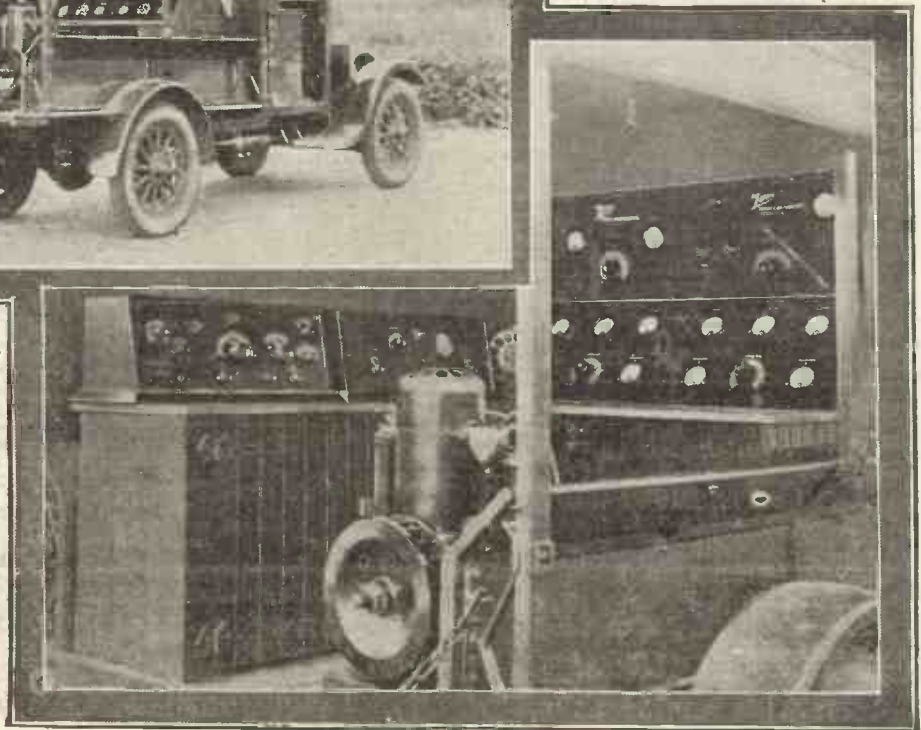middle of a field without any other power supply than its own and without any supports other than its own aerial mast, and can operate indefinitely, since it is equipped with a complete gas engine generator charging outfit which is able to charge the batteries while the station is in broadcasting operation.



Inside, the apparatus is very neatly arranged.

The entire framework and body of the car, including the iron strips on the floor, are connected together and grounded, the grounding strips all being brought to one point at the side of the car, where a heavy connection lug is attached.

The battery supply is 24 volts with a total capacity of 320 ampere hours. This battery arrangement operates a 24-volt to 1,500-volt direct-current generator, which, of course, is equipped with the necessary filter system to eliminate all generator hum. Standard broadcasting microphones, line amplifier, etc., are used. Three microphones may be used, one for announcing,

Switching Arrangements

Special switching arrangements are provided whereby the generating outfit not only charges the 24-volt battery but also charges the lighting and ignition batteries of the truck at the same time and also operates a 24-volt to 350-volt motor generator which serves to charge the high-tension accumulators used on the line amplifier. In this way the one engine charges the complete set of batteries, high and low voltage, all simultaneously. This can be done while the set is in actual operation without in any way disturbing it.

The entire wiring of the set is of the bus-bar type, using gold-plated copper bus-bar.

Three stages of amplification are used in the line amplifier, and the output of this is connected to a 5-watt speech amplifier, and from this connection is made to the two 50-watt modulator valves.

A complete receiving set with loud-speaker is provided for checking the modulation and also for maintaining communication if this is desired at any time.

In the transmitter proper the Hartley oscillator circuit is used, with Heising modulation.



This handsome Primax loud-speaker was one of the features of the recent Albert Hall Exhibition.

one for orchestra and one for studio purposes, where these are necessary. A switching control arrangement is provided whereby each one of these or any of them at once may be used at the will of the announcer. Special armoured cable is provided whereby the microphones can be placed as far as 300 ft. from the truck, allowing the broadcasting of performances in halls, etc., with the car parked outside.

The wave-length is 268 metres. The call letters are WJAZ, and the average aerial current is 4 amperes with an upward modulation of about 1 ampere.

**HINTS ON READING
A BLUEPRINT**

Remember that a blueprint of a wiring diagram represents a view of the underside of the panel, and therefore the order of things is reversed.

Note also that where wires are intended to cross that part of one wire which crosses the other is shown as a small semi-circle.

Intersecting wires intended to be joined or soldered are marked with a small white circle at the intersection.

Since a plan only is given, wires which are parallel and vertically above each other, are shown conveniently spaced side by side, and thus the actual disposition of the wiring is not necessarily as represented. Here the perspective photographs of the descriptive article are a help.

Components such as valve and coil holders, variable condensers, fixed condensers, fixed grid leaks and anode resistances, etc., are shown pictorially, as far as is possible.

Always aim at keeping parallel wires well spaced.

Be very careful not to let adjacent wires touch one another.



A Simply Made Single-Valve Receiver.

By PERCY W. HARRIS.

Last month, in the "Crusoe" Set, we saw how easily a single-valve circuit can be arranged from a few odd parts. This month the construction of a simple, yet efficient and handsome, single-valve receiver is described in full.

FOR the man who is just beginning wireless, the single-valve set has many charms. It can, for example, be run quite economically from a small accumulator, or, if we purchase one of the newer type of valve, burning only .06 of an ampere, even three dry cells of the electric bell type will suffice. The sensitiveness of a good single-valve set, particularly when reaction amplification is used, is considerably higher than that of the best crystal receiver, while the operation is so simple that even the most unskilled can soon learn how to get results. The one disadvantage of such a set—that it may cause interference with one's neighbours' reception—is easily overcome when attention is paid to a few simple rules.

Several pairs of phones

Furthermore, from such a single-valve set, which will operate several pairs of headphones on the nearest broadcasting station, the experimenter may proceed by easy stages to a more elaborate set. Next month, for example, we shall describe the construction of a two-valve amplifier, which when added to this receiver will enable a loud-speaker to be operated at good volume from the nearest station, provided this is not more than 30 or 40 miles away. I am not saying

that a loud-speaker cannot be worked by a single-valve set followed by two note magnifiers at a greater distance than that given, but that one is certain to obtain good results at this distance, after which results are less certain.

If you look at the photographs you will see that the set is mounted in vertical cabinet with the rather unusual feature that the valve is mounted inside the cabinet out of

band, but also Eiffel Tower, Radiola and Chelmsford. Being primarily a receiver for use with headphones on the nearest station, it is yet sufficiently sensitive to give several others when conditions are good, and occasionally all of the others may be received, when adjustments are carefully made to the best advantage.

Components

Let us now see what parts we require to make this set. They are as follows:—

One vertical oak cabinet to take a panel 10 in. by 6½ in. (that illustrated is a standard line of Peto Scott, Ltd.)

One ebonite panel, 10 in. by 6½ in. by ⅜ in. or ¼ in. (It does not much matter which thickness. This panel should be of guaranteed ebonite of one of the well-known brands.)

Eight terminals with nuts.


One filament resistance for bright or dull emitters. (That shown is a Lissenstat. There is scarcely room on the panel for the larger disc type of filament resistance.)

One grid condenser .0003 μF and one grid leak 2 megohms (Dubilier).

One fixed condenser .002 mfd.


(Dubilier).

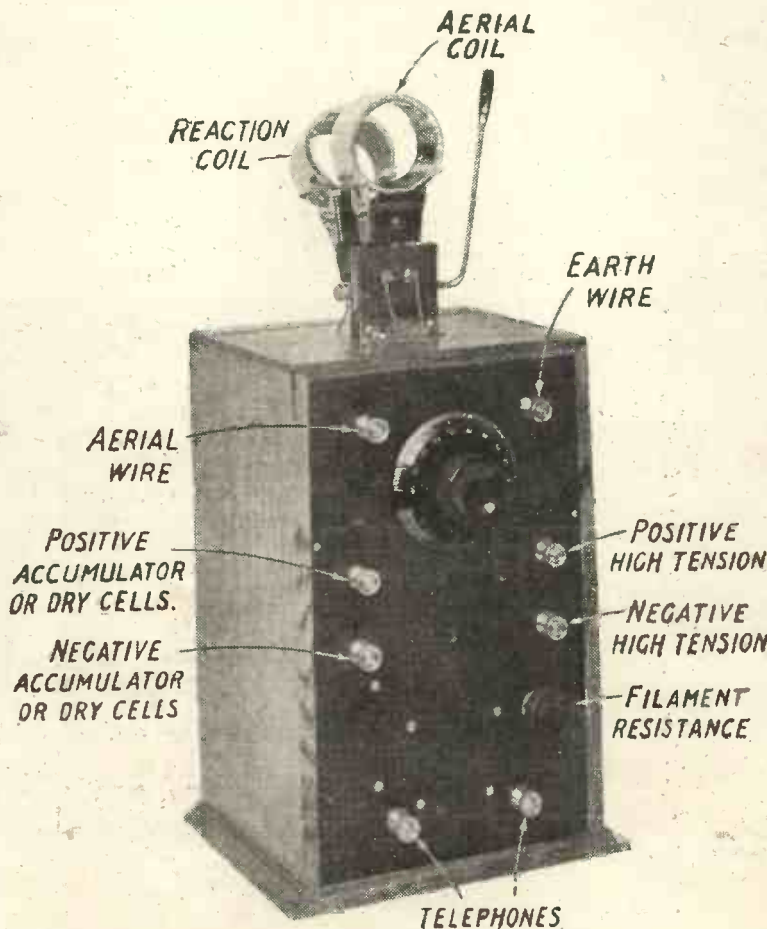One two-coil holder of good make. (There are so many reliable types of two-coil holder for mounting in this fashion that there is no need to specify any individual make.)



How the terminals are used.

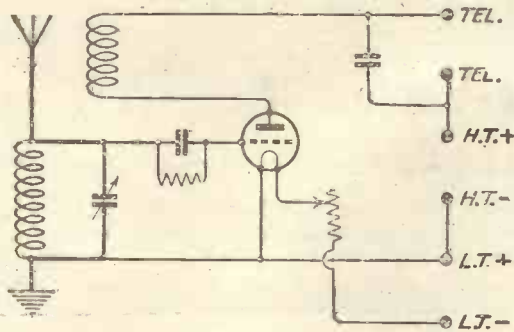harm's way. Plug-in coils, fitted to a two-coil holder on the top of the instrument, enable a rapid change of wavelength to be made, so that not only is it possible to receive any of the stations on the lower broadcast



The theoretical diagram is quite simple.

One variable square law condenser .0005 mfd. (This is preferably of the single hole mounting type if the set is being made by a beginner. That shown was purchased from K. Raymond. Any good square law variable condenser will do here.)

The valve holder

One special valve holder for mounting behind the panel. (That shown is known as the Aermonic, made by V. R. Pleasance, of Sheffield. To the best of my knowledge it is the only make of this type at present sold in this country. In America there are a number of suitable sockets, made, however, to fit their own valves and not ours.)

Accessories.

If you have no other apparatus you will need the following accessories:—

One valve. This may be a bright or dull emitter. There is an excellent article in this issue by Mr. R. W. Hallows, M.A., entitled "When the Beginner Buys A Valve." You will find many useful hints and explanations there. An accumulator, or dry cells, will be required to run the filament of the valve, and one high-tension battery which should be of 60 volts, tapped, so as to use different voltages for adjustment. One or more pairs of telephones will be needed. These should be of the high resistance variety, of which there are many excellent makes at reasonable prices. It is no good buying a loud-speaker for this set as it is not sufficiently powerful to operate even on a near-by station. If you want to run a loud-speaker from it you must add a valve amplifier of the kind which will be described next month.


Having assembled your parts you should lay them out on the panel to see that they will go into the space indicated. If you use parts of a size similar to those illustrated you will have no difficulty. The first step is to mark

out the panel according to the dimensions given (working, of course, on the back so as to avoid spoiling the front surface) and to drill the various holes to take the different components. When you have mounted all of these, take a fine file and file the tops of all screws that have to be soldered. Tin the points carefully, as described in THE WIRELESS CONSTRUCTOR for last month, and wire up carefully from the drawings. The wires which should have particular attention are those which pass between the valve and the panel. These wires must be very carefully placed and should go as close to the panel as possible so as to avoid fouling the valve. At the same time they must be so bent as not to touch one another, or they will tend to short

circuit. If you find difficulty in using the square section wire you may wire up the set with thinner wire, covering it with insulated tubing which can be obtained quite cheaply from any wireless dealers


Wiring hints

There is one other point in wiring which I must mention. Notice, particularly, that the wire which goes from the right hand telephone terminal (this is looking from the back) is connected to one of the soldering lugs of the .002 mfd. condenser and also to the positive high-tension terminals. Notice, too, that long flexible leads are soldered to the plate socket connection of the valve holder, and to the left-hand telephone terminal (looking from the back). These flexible leads are subsequently passed to the top of the cabinet, through holes drilled in the top, and are connected to the two contacts of the movable plug from the two-coil holder. Two other flexible

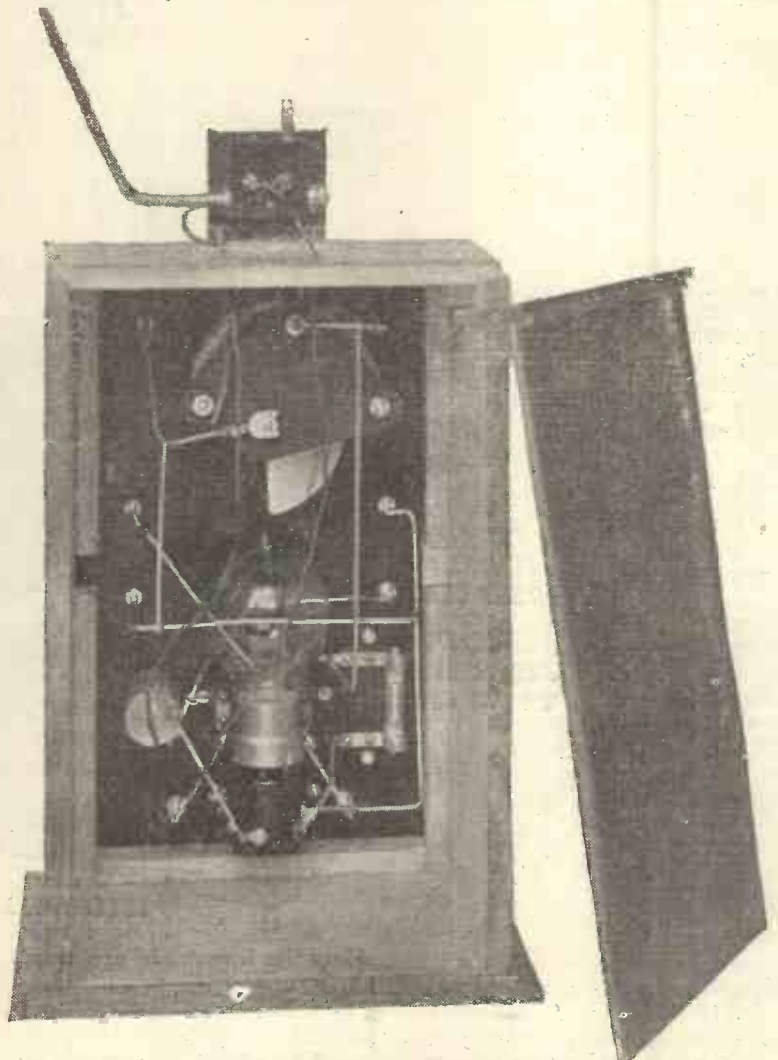

The back of the cabinet can be removed to give access to the valve and wiring.


Britain's Best BROADCASTING SETS

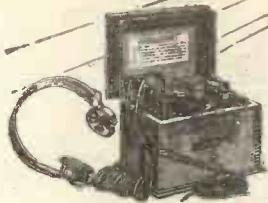


GECOPHONE
Crystal Set



GECOPHONE
Single Valve Set

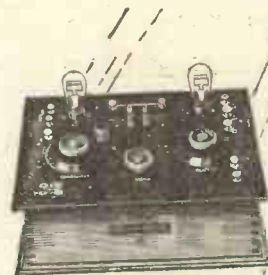

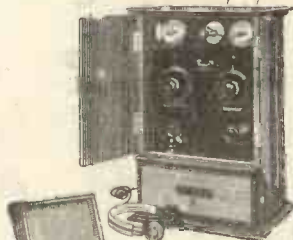GECOPHONE
Two Valve Set (Det. & L.F.)
Table Model



GECOPHONE
Two Valve Cabinet
Set (H.F. & Det.)

1924/5

GECOPHONE

REGISTERED TRADE MARK


MODELS

LET your choice of a Wireless Set be guided by the knowledge and experience of the many thousands of satisfied users of GECOPHONE Sets.


A new range of models has now been introduced, each set embodying all those superlative qualities which have made GECOPHONE famous throughout the World.

The range of GECOPHONE receiving sets now meets every requirement and offers selection to suit the pockets of all sections of the community. Prices from £2 10s. to £120.

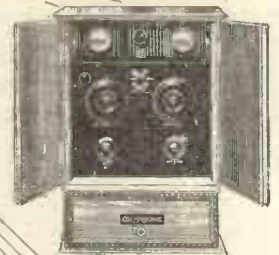
Before you make your choice of a Wireless Set ask your dealer to demonstrate the new GECOPHONE models to you. He will gladly do this without obligation.



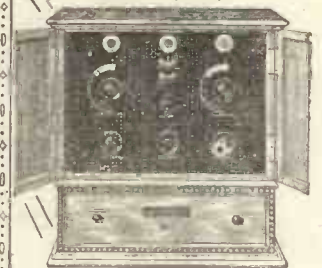GECOPHONE
Two Valve Cabinet Set
(Det. & L.F.)



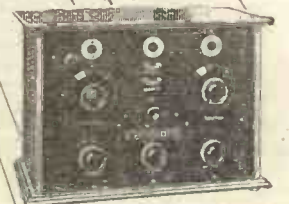GECOPHONE
Three Valve Cabinet
Set (Det. & 2 L.F.)



GECOPHONE
Three Valve Table Set
(Det. & 2 L.F.)

GECOPHONE Sets are sold by
GECOPHONE SERVICE DEPOTS, Electrical
and Wireless Dealers, Stores, etc.
Ask for price list No. B.C. 3425.

Advertisement of The General Electric Co., Ltd.
(Manufacturers and Wholesale only),
Magnet House, Kingsway, London, W.C.2




GECOPHONE
Five Valve Cabinet Set



GECOPHONE
Four Valve Cabinet Set de Luxe

Brandes

TO some people a receiver is merely a piece of mechanism. It has never occurred to them to give it a real chance—to help it become vitally alive. Brandes "Matched Tone" Headphones will exploit the full merit of your set, bringing it to eager life. The *Table-Talker* will make it talk clearly and melodiously. All the liquid tones, the pulsating warmth of a soprano, will come to you unspoiled, without any unnatural harshness. It does not matter—the rioting madness of the violin, the immense grandeur of the organ, or the intoxicating rhythm of a dance band, they all speak to you—ALIVE with their OWN vigorous cadences. Let Brandes products dispense with dull tonelessness, and bring your receiver to vigorous life.

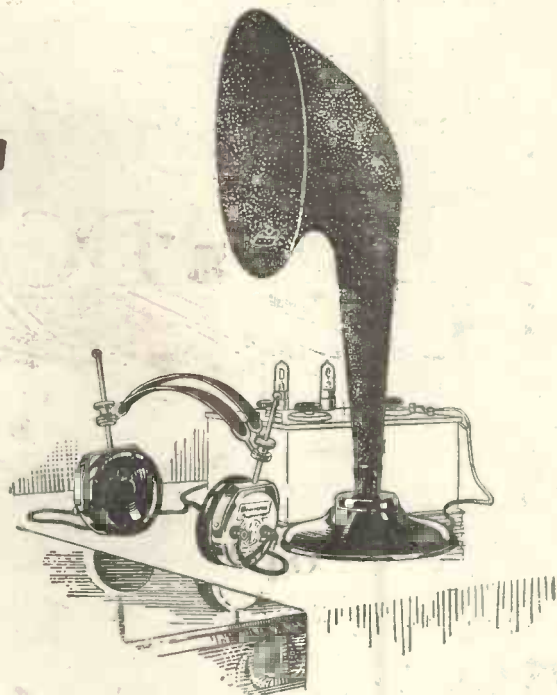

All Brandes products carry our official money-back guarantee, enabling you to return them within 10 days if dissatisfied. This guarantee practically constitutes a free trial.

The "Matched Tone" feature was embodied as the distinctive characteristic of Brandes' Headphones in 1908, and means that both your ears hear exactly the same sound at the same instant—and you learn a new beauty of tone. They are tested and re-tested for just this one vital point, and in addition their strength, long-wearing comfort and reliable efficiency make them undoubtedly superior.

25/-

The *Table-Talker* is a Brandes' quality product at a moderate price. The non-resonant, specially constructed horn is matched to the unit so that the air resistance produced will exactly balance the mechanical power of the diaphragm. This means beautiful sound-balance and remarkable tone qualities. It is twenty-one inches high and has a clear, strong volume of sound sufficient to fill the largest room. It has a self-adjusting diaphragm and is finished a shade of neutral brown—a tasteful and effective addition to the set.

42/-

British Manufacture (B.B.C. Stamped)

Brandes Limited, 296, Regent Street, W.1. Works: Slough, Bucks.



25/-



42/-

Brandes

The name to know in Radio



Tune with Brandes Matched Tone Radio Headphones—Then listen with Brandes Table-Talker.

leads are soldered to the points shown and also pass through the top of the cabinet to the fixed coil of the two-coil holder. These are not connected until the panel has been placed in the cabinet. The fact that in the present cabinet the whole back is removable by sliding upwards, is an advantage when making the final adjustment.

The Aermonic valve socket has four screws passing through holes in the base. These make electrical contact with the filament pins and grid and plate connections. You will find it useful to screw behind these four short soldering lugs.

top of the cabinet as shown. When you have connected up these wires, place the valve in its socket, turn the cabinet round (turn the knob of the Lissenstat anti-clockwise until it comes out almost as far as it will go), and connect the battery wires to the low-tension terminals as indicated. Now turn the Lissenstat gradually in a clockwise direction until the valve begins to light up; this will indicate that all is well with the filament wiring. Turn the valve off again, connect leads from the positive and negative plugs of the high-tension battery to the terminals indicated, and con-

listen in by the telephones. Alter the position of the tuning dial of the variable condenser until you hear signals from your local station, when if all is well you will come in quite clearly. Now with very great care move the moving coil in the coil-holder slowly towards the fixed coil, and unless your station is very near, there should be an increase in strength. In a short time you will hear a "plop" and a breathing in your earpieces, which will indicate that your set is oscillating. Immediately open out the moving coil until it is well away from the fixed coil holder, and try

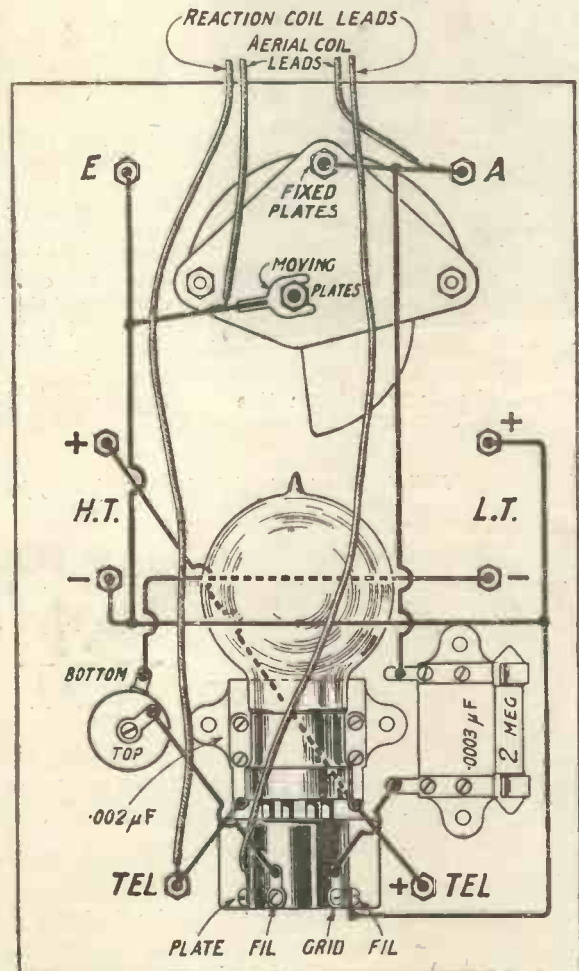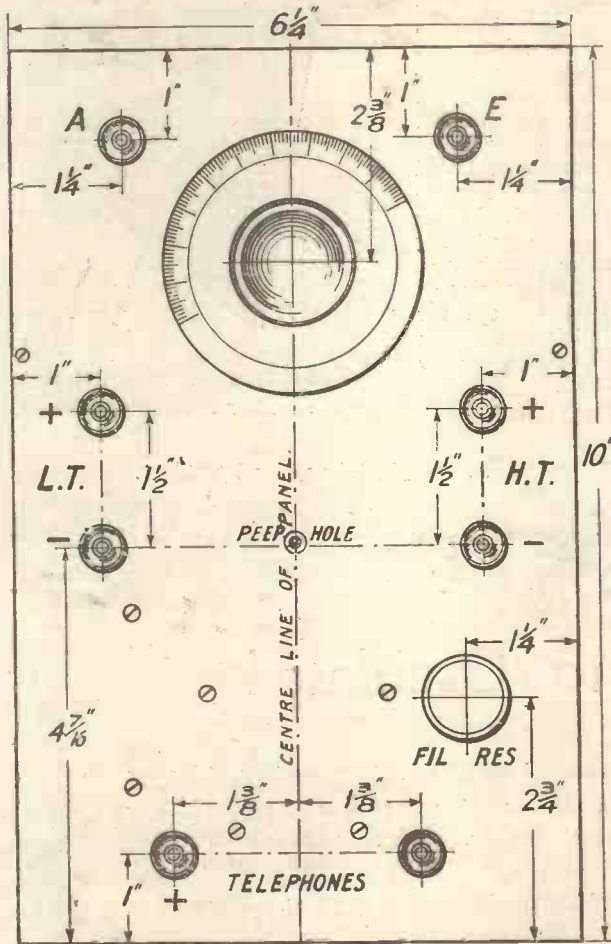


These two pictures show the front and back details quite clearly. The + telephone terminal should be connected to the telephone tag marked with this sign. All telephones, however, are not so marked. If one tag is marked red, this is the + lead. If the 'phones are not marked in any way, try which lead gives better results here.

This will greatly facilitate wiring up with stiff wire. If, however, you are using tinned flexible wire and insulating tubing you can pass the wire behind the screws without fitting any lugs.

As soon as you have wired up the back of the panel push it into the cabinet and thread the four flexible leads through holes made in the top of the cabinet just by the two-coil holder, which is screwed to the

connect your telephones. A pair of coils will now need to be plugged into the two-coil holder. The front coil should be a number 25 or 35 for the British Broadcasting band, and the back coil can be a number 35 or 50. For Chelmsford a number 150 should be put in the fixed socket and a number 200 in the moving. Open up the coil holder so that the coils are at right angles, connect the aerial and earth and


again, very slowly this time, stopping your adjustment a little before the point where the set will break into oscillation. If you have any doubts whether the set is oscillating or not, wet your forefinger and tap it on the aerial terminal. If there is a "plonking" noise when you touch, and also when you withdraw your finger, the set is oscillating, and the reaction coupling should be opened up until it stops. If there

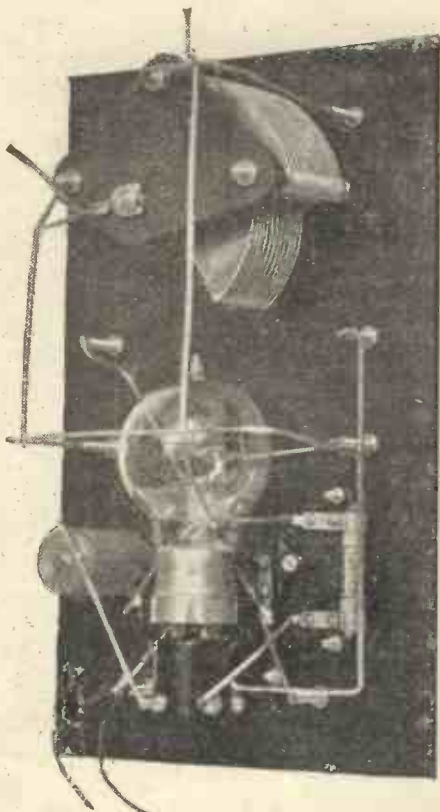

The panel removed from the cabinet.

is no "plop" and if bringing the coil right up against the fixed coil still does not make the set oscillate or does not increase the strength of signals, then reverse the connections to the moving coil and repeat the experiment. One way round is correct, you will find which way by trial. Do not use reaction if the signals are good without it. It is best to take no risks of disturbing your neighbours.

On test this set gave excellent signals from the nearest broadcasting station, and good signals from several others. On a night when conditions were very good all B.B.C. stations, as well as two or three on the Continent, were heard quite clearly in the 'phones. In most circumstances, however, the set is not sufficiently sensitive, save with a very good aerial, to receive all the stations, but two or three other than the local station should be heard quite clearly where a reasonable outdoor aerial is used. On a small indoor aerial made by taking a wire out of the room upstairs and once round the loft, the local signals were still quite loud enough for several pairs of 'phones, when tested seven miles from the 2LO Broadcasting Station.

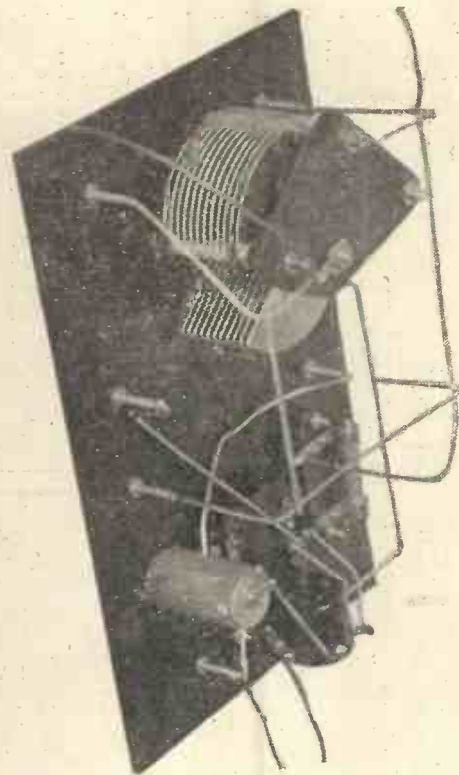

Panel without valve, showing further wiring details.

Full size Blueprints of the front and back of panel (C 1003A and C1003B) price 1/6 each post free.

How NOT to Oscillate!

If when you turn your tuning dial, you hear howls which vary their note as you turn, it is your set that is oscillating. Look at once to see if your reaction coil is too close to the tuning coil, or if your "intensifier" or "reaction" knob is turned too far. This may be the cause.

Don't try to force your set to give the last ounce of strength by reaction coupling. You will get distortion and run a grave risk of becoming a local nuisance.

Don't play with the reaction coupling "to see what happens." If you use reaction at all, use it with the greatest discrimination.

Don't fail to touch the aerial terminal occasionally with a moist finger. If you hear a "plonk" when you touch it and also when you withdraw your finger, the set is oscillating. Loosen reaction immediately.

LISSENIUM COAXING THE VALVE—AT NIGHT TIME

IS YOUR LEAK RESISTANCE RIGHT?—



You can put a resistance in circuit whose value will be so inaccurate and fluctuating that the leak is useless. Though some circuits and valves are not so susceptible to variable grid control as others, it is reassuring to know that one has the means to control grid potential so that the correct value is obtained for any circuit or valve, or the particular conditions under which a valve may be working. With the LISSEN VARIABLE GRID LEAK fitted, the receiver will yield the utmost sensitivity which correct grid potential under all conditions implies.

LISSEN ONE-HOLE FIXING, OF COURSE 2/6

LISSEN VARIABLE ANODE RESISTANCE, 20,000 to 250,000 ohms, same outward appearance as LISSEN Variable Grid Leak 2/6

TO SMOOTH OUT LOUD SPEAKER DISTORTION PUT A LISSEN VARIABLE GRID LEAK ACROSS THE SECONDARY OF THE LAST TRANSFORMER, OR ACROSS THE LOUD SPEAKER ITSELF. FIRST POSITION IS BEST. THE DIFFERENCE WILL BE VERY NOTICEABLE.

PARTS THAT PULL TOGETHER

- Use LISSENAGON COILS for sharp tuning—for strong tuning.
- Use LISSEN TRANSFORMERS and LISSEN CHOKES for fine tone and pleasing volume.
- Use LISSEN H.F. Parts for extending range.
- Use LISSEN TUNER for conveniently covering a wide wave-length.

DON'T MIX YOUR PARTS

A Receiver built with all Lissen parts will give results which would never be possible if you used mixed parts.


LISSEN LIMITED

24-30, Woodger Rd., Gold-hawk Rd., Shepherd's Bush, London, W.12.

Telephones: 3380, 3381, 3382, 1072
Riverside.
Telegrams: "Lissenium, London."

PARTS WITH HIDDEN POWER—BUILD WITH THEM.

SIGNALS THAT PASS IN THE NIGHT!—You get them stronger and from farther away if you are using LISSENSTAT control. After you have tuned in as far as you can go with every other control on your receiver you can still do a great deal more—IF YOU ARE USING LISSENSTAT control. When at last you realise that you are on to an unknown station there is a thrill in the thought that it has been brought in to you by nursing the valve with the turn of a knob that stands out so simply above your panel.

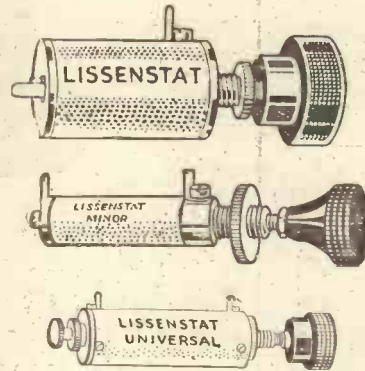

The secret is in the structure of the LISSENSTAT and its composition—so critically is it possible to control electron emission of the valve that you can get right on to the very spot necessary for the finest detection of long distance telephony.

LISSENSTAT (patent pending)—gives the most acute tuning possible 7/6

LISSENSTAT MINOR (patent pending)—is replacing many thousands of discarded and inefficient rheostats. Provides LISSENSTAT control at a popular price 3/6

LISSENSTAT UNIVERSAL (patent pending)—with its protective device for dull emitters 10/6

All types have LISSEN ONE-HOLE FIXING, OF COURSE.


You can feel for fine detection—if you use LISSENSTAT Control

USE A RADIO SWITCH

Many switches sold are undesirable for radio work—they have been designed from the purely electrical point of view, which is not good enough for radio.

LISSEN SWITCHES, on the contrary, have been designed primarily for radio, but they are useful also for other switching purposes. You just gently pull or push them, and you hear them make with a reassuring "click"—and you know they are free from capacity effect.

WHAT LISSEN 5-POINT SWITCH DOES

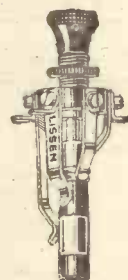


- A. Switches off one stage of L.F. without touching the filament control—a separate switch for each stage.
- B. Connects the telephones to the plate of whichever valve it is desired to use, and at the same time switches off the L.T. current from the unused valve.
- C. Cuts out a stage of H.F. in the same way as it does L.F. (we do not recommend any switching in H.F. circuits where it can be avoided, but where it is decided to use a switch, this is the switch to use).
- D. Will also disconnect both the H.T. and L.T. batteries, and short the aerial to earth so that the receiver can be left adjusted ready for switching instantly into commission next time. With diagram. 4/-

LISSEN REVERSING SWITCH

Particularly useful when the LISSEN 5-point switch is used for cutting out one stage of H.F. When a H.F. stage is cut out, and reaction is being taken off the aerial circuit, it is necessary to reverse the reaction coil connections for each H.F. stage cut out, and this new LISSEN switch conveniently does it. Can also be used anywhere when it is necessary to reverse the connections of a battery, a coil, or a condenser, for instance. VERY USEFUL FOR COMPARATIVE TESTS. With diagram 4/-

TWO OTHER LITTLE SWITCHES.

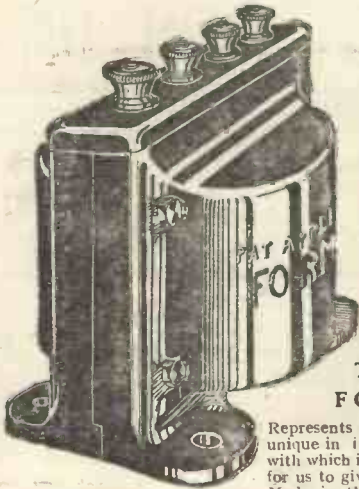LISSEN 2-way switch 2/9 LISSEN Series-parallel switch 3/9



THE
**FAMOUS
FORMO**
RADIO
EQUIPMENT
*Ensures Maximum
Results*

THE WORLD RENOWNED
FORMO TRANSFORMER

Represents the highest value obtainable. It is unique in its qualities, and the meticulous care with which it is made and tested, render it possible for us to give such a comprehensive guarantee. Made in the following ratios:—

- A. ratio 1-2. C. ratio 1-4.
- B. ratio 1-3. D. ratio 1-5.
- Also Telephone 1-1.

18/-

**START
RIGHT**


BY USING FORMO
PARTS, WHICH ARE
UNCONDITIONALLY
GUARANTEED

Formo-Densor Prices :

.001 mfd.	10/6
.00075 mfd.	10/-
.0005 mfd.	9/8
.0003 mfd.	8/6
.0002 mfd.	7/6
Three Plate Vernier	5/6
Dual, with Vernier ..	12/6

SO-CALLED "SQUARE LAW"
SUPERSEDED.

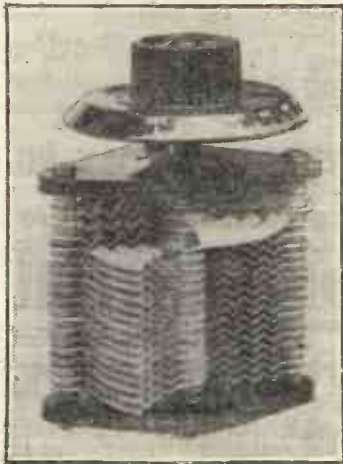With the low inherent capacity and low minimum capacity of the Formo Densor, together with coarse and fine tuning in one movement, a "straight line" is more nearly approached than with the so called "Square Law" condenser.



THE FORMO-DENSOR WITH
INTEGRAL VERNIER.

The Formo
Home
Constructor's
Set

Is composed of Standard Formo Guaranteed Components, packed in cabinet, complete with panel, accurately drilled and tapped, coil holder, wire, etc., and practical wiring diagram. Price 24/12s. Plus Marconi Royalties.

THE FORMO PORTABLE
AERIAL.

For use indoors, out-of-doors, on the car, in fact, anywhere; can be erected or taken down in a moment; complete with insulators, hooks, etc. Can be carried in the pocket.

ELIMINATES STATIC. 7/6.
THE FORMO CO.,

(Arthur Preen & Co., Ltd.),
Contractors to the Admiralty,
War Office, India Office, Air
Ministry and Post Office.

Head Offices & Works :


CROWN WORKS,
CRICKLEWOOD
LANE, N.W.2.

Phone: Hamp 1787.

Scottish Branch—
22, York Place, Edinburgh.


A NEUTRODYNE CONDENSER

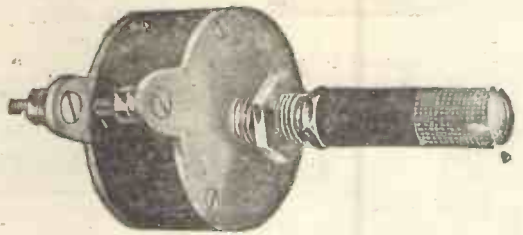is an essential part of a high frequency amplifier if the greatest possible efficiency is to be obtained from the valve. It provides a method whereby the capacity of the valve can be effectively balanced and the circuit made quite stable and free from the tendency to self oscillation.



Price 7/9.

The only additions required to convert the ordinary tuned anode amplifier are the condenser and a coil of similar value to the tuned anode coil. This coil is coupled as tightly as possible to the anode coil and is connected to the grid and filament in the manner shown in the following diagram. If when condenser "C" is adjusted, oscillation cannot be controlled, the connection to the ends of coil "B" should be reversed. The correct connections can be easily found by trial.

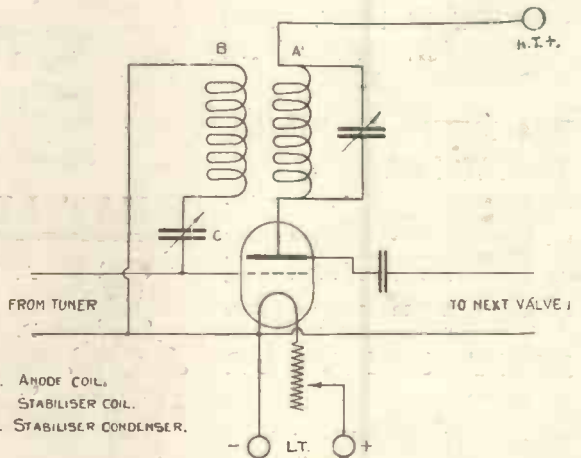

- A. ANODE COIL.
- B. STABILISER COIL.
- C. STABILISER CONDENSER.

The Condenser illustrated occupies a panel space of only 1 3/8 in. diameter and as a single 1/16 in. diameter hole is all that is necessary for fixing, alterations to existing sets can be made with the minimum of trouble. To obtain the best results the coils should be "Gambrell Efficiency Inductances."

GAMBRELL BROS., LTD.

76, Victoria Street, S.W.1.

Works : Southfields.

Phones : Victoria 9938.

Putney 3641-2.





Native Galena (much magnified).

Something about Galena:

How Modern "Ites" are Made.

By CHARLES H. BUTCHER

What it is—Where to find Sensitive Spots—Selecting a Crystal by Appearance—How to fix it—How to Keep it in Good Condition—Contacts for the Best Results—Treated Galena.

The author of this article is an expert mineralogist and has done much research work on crystals for wireless.

GALENA is a natural sulphide of lead crystallising in both cubic and octahedral crystals. In the massive form it occurs widely distributed throughout the world, as primary metallic veins in limestone or as irregular deposits. Almost all natural galena is radio-sensitive to a certain degree.

Hard Crystals

Hard specimens of the mineral are generally more sensitive than softer ones, and those with a slightly striated surface will be found remarkably so. The most sensitive spots are to be found at the very angles of cubic crystals or cleavages, or on minute octahedral cleavage planes. At these points there is a strong unbalanced electrostatic field, very probably due to the presence of atoms of only one kind, either sulphur or lead. In the case of cubic crystals where one particular face is highly sensitive, it will often be found that the adjacent faces are quite insensitive. If therefore a crystal gives poor rectification on one face, a spot on an axis at right angles should be tried in preference to one on the face directly opposite.

Crystals of galena with a brilliant silvery lustre and fine granular appearance are generally considered to be the most highly sensitive, but this is by no means invariably the case. There are many types of natural galena with a smooth dull grey surface, showing distinct cleavage, which are quite equal and in many cases better than the most sensitive of fine grained crystals now obtainable. In a good crystal sensitivity should be

constant and permanent, and should not fall off after a few weeks' continual use. The best results are obtained by connecting the crystal itself to the earth side of the circuit, and the "cat's whisker" or wire contact to the aerial side. This may be explained more clearly by reference to the diagram on the next page.

Fixing

The use of solder is generally considered the most efficient and most desirable method of mounting the crystal in its cup. In this operation, however, considerable care must be exercised to see that the temperature of the molten solder is not too high. However low its fusion point, solder is liable to seriously impair or perhaps



A magnified piece of hertzite. Notice the pin's head which indicates the degree of magnification.

entirely destroy the sensitivity of a crystal, though the risk at temperatures up to 65° C is small. Wood's metal, an alloy of tin (1 part), lead (1 part), bismuth (4 parts) and cadmium (1 part), melting at 60.5° C is generally used. Malleable solders have sometimes been employed, the metal being lightly punched into

contact with the crystal and its cup. This method of fixing is very undesirable, as the shock occasioned in the process of punching tends to shatter the structure of the galena.

Spring Clips

Spring clips are sometimes used for holding crystals. They will be found more satisfactory than cups with set-screws, with which it is not always possible to hold the crystal in any and every position. Where spring clips are used, the pressure exerted on the galena must not be too great owing to the possible presence of weak lines of cleavage. The principal advantage of a spring clip lies in the fact that crystals are readily changed with a minimum of trouble. Highly sensitive natural galenas are liable to become over-exerted by continual use, and if such a specimen is put aside for a week or so it will regain its original rectifying power.

Don't Touch!

On no account should sensitive galena be touched with the fingers, as a minutely thin film of grease is readily imparted to the surface of the crystal. A small pair of forceps should be used to handle crystals where necessary. Should the surface of a crystal become dull by accidentally being touched, or by the accumulation of dust particles, it should be washed in a little ether or alcohol and allowed to dry spontaneously on a piece of clean blotting paper. The surface of galena should never be scraped or scratched in order to expose a fresh sensitive face. If necessary, break off a portion of the crystal by cleavage with



Yesterday

—the explorer braved hardships to chart the seas.

WUNCCELL DULL EMITTERS
 W.1. (For Detector and L.F. use). Operating at 1.8 volts .. 21/-
 W.2. (With red top) for H.F. use. Operating at 1.8 volts .. 21/-
 Types W.R.1 and W.R.2 as above but with resistance incorporated in base to operate off 2, 4 or 6-volt accumulator .. 23/-
The Wuncell is fully described in a comprehensive Folder which will be sent post free to any experimenter on receipt of a postcard. Don't invest in a Dull Emitter Valve until you have read about the Wuncell.


While the explorer of long ago had to set sail and face almost incredible hardships in his praiseworthy efforts to chart the globe, his successor sits by the fireside and logs Foreign Broadcasting Stations with almost absurd ease. From America to the borders of Russia and from Scandinavia to the shores of the Mediterranean the ether is available for his exploration.

amplification, and for his Valves he should use those which have been specially developed for the work.

Undoubtedly the most popular high-frequency amplifier to-day is the Cossor P2—the valve with the red top. Hundreds of thousands of these valves are in use at this moment among all grades of wireless enthusiasts—from the expert to the novice—and everywhere it is giving the most complete satisfaction.

But the man who is enthusiastic over long distance reception will see that he is not handicapped either by his Set or his Valves. His Set should employ at least one stage (and two for preference) of high-frequency

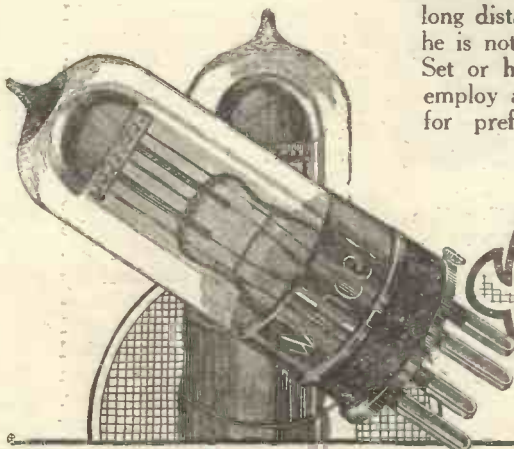Its striking success is undoubtedly due to its design. As every wireless enthusiast knows, the working of a valve depends upon the correct use being made of its electron emission.



Cossor

Get Cossor Valves—they cost no more

Advertisement of H. C. Cossor, Ltd., Highbury Grove, London N. 5



To-day

—he charts the ether from the comfort of his fireside.

You must have noticed that when your accumulator begins to fail and the filaments of your valves grow dim that your Set falls off in sensitiveness and volume. A clear case that the emission from the filaments has decreased.

Obviously, therefore, the quantity of the electron emission is an important factor in valve efficiency.

Now compare the Cossor P2 with an ordinary Valve. Instead of a hood-shaped Anode and Grid totally enclosing an arched filament and almost completely entrapping its electron stream, we see that at each

end of the tubular Anode the filament is exposed and that a large proportion of the electron stream is obviously leaking away. Remember that for high-frequency use you cannot afford to risk inefficiency—feeble oscillations from Stations thousands of miles away will strike your aerial and you'll be none the wiser if your Valves are not sensitive to them.


The remedy is in your hands—for high-frequency use select the Valve specially developed for the purpose and chosen by the vast majority of Valve users in this country—the wonderful Cossor P2.

COSSOR BRIGHT EMITTERS.

- P.1. For Detector and Low-Frequency use 12/6
- P.2. (V with red top). For H.F. use only .. 12/6

TO THE TRADE:

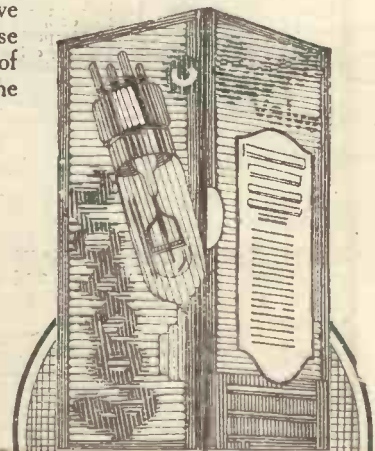Have you received copies of the new Cossor Electrical Testing Showcard? If not, send in your application at once.



Valves

but what a difference in results!

EFESCA

ONE-HOLE FIXING WIRELESS COMPONENTS MEAN EFFICIENCY!

Build your Set with them.

Maximum Efficiency is the aim of every constructor. Building with Efesca Parts enables you to attain your objective the first time you use your Set.

Efesca Wireless Components do much to smooth out difficulties in the construction of Sets, not only for the beginner, but for the more advanced experimenter also, who will at once appreciate the many refinements and unique features embodied in the wide range of Efesca Parts.

Panel-mounting is greatly simplified by the STANDARD ONE-HOLE FIXING.

EFESCA COMPONENTS ARE STOCKED BY ALL WIRELESS DEALERS, IRONMONGERS AND ELECTRICIANS.

Learn more about Efesca Components by writing for Catalogue 522—TO-DAY, or ask your dealer to get it for you.

THE COMPONENTS ILLUSTRATED ARE:



- (1) Efesca High Frequency Transformer.—Specially recommended where more than one stage of High Frequency amplification is required. Can be employed immediately preceding a reactance coupling to form two High Frequency stages or any number of separate transformers may be used in combination. Can also be used as a Tuned Anode Transformer by shunting the primary with a .0003 mfd. variable Condenser in any number of stages. Wavelength range 150-2,600 metres, complete as illustration, wound on Ebonite former, 21/-.
- (2) Efesca Tapped High Frequency Reactance.—The most efficient form for one stage of High Frequency amplification. It is self-tuned, and requires no condenser. Wavelength range 150-2,600 metres. Complete, as illustration, 21/- each, or embodying grid leak and condenser (.0003 mfd.), 25/- each.
- (3) Efesca Vernistat (Pat. applied for).—Of unique construction, the Vernistat gives extremely delicate control, and is smooth and silent in operation, and is specially suited to High Frequency and Detector Valve filament control. Resistance 5 ohms, 6/- each, complete as illustrated.
- (4) Efesca Variable Reaction Coil for use in either Aerial or Anode Circuits. Wound on Ebonite former, totally enclosed, complete as illustration, 17/6.
- (5) Efesca Aerial Tuner.—Wavelength range 150-2,600 metres, in conjunction with .001 condenser. A convenient form of self-contained tapped coil possessing minimum self-capacity, low resistance, and high inductance. Tappings arranged to obviate dead-end effects. Complete as illustration, 19/-.
- (6) Efesca Speech Amplifying Transformer, type "C".—This transformer is designed to give the amplification of a power Transformer without the loss in purity of reproduction generally experienced with power amplification. The coil is wound in a special manner to neutralise resonant effect, while the laminations of the core are extra carefully insulated from each other to localise eddy currents and thus prevent distortion. Ratio 2-1 one-hole fixing, 25/-.

For those not interested in the constructional side of wireless there is a wide range of complete Efesca phone sets from the simple crystal set to the multi-valve receiver for loud speaker and long range work.

FALK STADELMANN & CO., LTD.
Efesca Electrical Works, 83-85-87, Farringdon Road, London, E.C.1.

and at
Glasgow,

Manchester &
Birmingham.

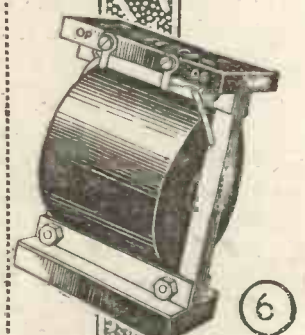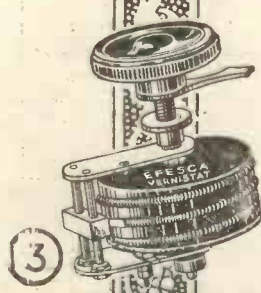



Representatives of Messrs. Heinz, the pickle manufacturers, listening at Bristol to speeches received by wireless.

pressure from the blade of a pocket knife, as this will usually ensure the exposure of sensitive planes.

Stiff "Cat's-whiskers"

The use of the commonly stiff single-pointed contact as "cat's-whisker" is very detrimental to the surface of galena crystals. Most metals have at one time or another been employed as contacts. There is nothing to be said in favour of gold except its non-oxidisable character, as it is only reasonably efficient. Platinum, silver, and pure tin give far better results. Pure aluminium wire, 30 S.W.G., will be found very effective if a slight pressure is applied at the point of contact. Brass wire varies considerably in its composition and hardness, and gives varying results with the same piece of galena. Clean copper wire, 40 S.W.G., gives excellent results when carefully adjusted.

The best contact for use with galena is unquestionably a short length of ordinary copper flex stripped of its protective covering and scraped clean with a knife. This will form a kind of brush with a large number of fine copper points grouped closely together. The brush should be allowed to touch the crystal very lightly, sufficient pressure being found by allowing the free ends of the wire to fall on the surface of the galena by reason of their own weight.


Treated Galena

Crystals of galena which show but slight signs of radio-sensitivity are generally rendered entirely insensitive by artificial treatment. But many quite insensitive specimens may be treated to give crystals of high rectifying power. Artificial sensitive surfaces may be obtained by heating in a sulphur flame, or in sulphur dioxide at a

temperature of 350° C, preferably in the presence of nitrogen. In a current of air at high temperature sensitivity is readily destroyed. From this it would appear that the sensitiveness of natural galena is due to the presence of sulphur atoms on the surface of the lead sulphide.


Surface Sensitivity

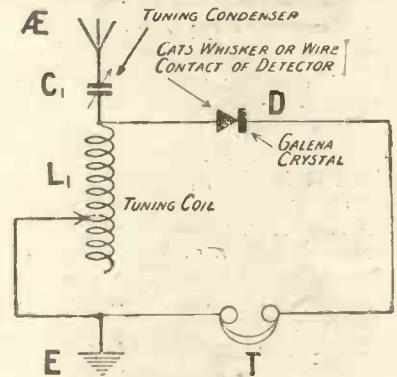Good crystals should be sensitive throughout, yielding equal results wherever fractured. By heating insensitive galena with sulphur in a covered crucible for about thirty minutes it is possible to obtain crystals with a good rectifying power. Finely powdered rock or roll sulphur, and not flowers of sulphur, should be used, as the impurities in the former seem desirable for



Best connections

the process. Fusion and recrystallisation at a temperature of 1120° C to 1150° C will also sensitise natural insensitive galena. The material should be roughly crushed and placed in a fireclay crucible and just sprinkled over with powdered sulphur to prevent undue oxidation. The cover of the crucible should be luted on with clay, and the whole is then heated up in a small gas furnace or in a fire, maintained at the temperature of fusion for about thirty minutes, and cooled as slowly as possible.

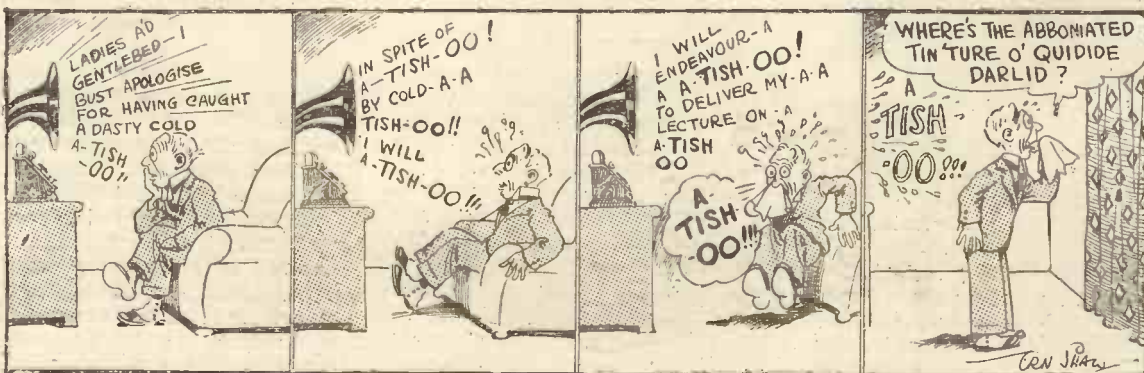

Horrible effects of auto-suggestion.

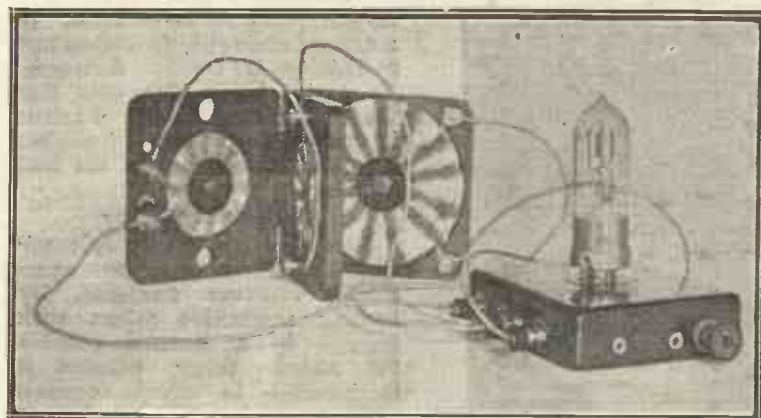


Fig. 1.—The complete set.

A Single Valve Portable Set

by
Norman K. Jackson

An essentially portable broadcast receiver.

A PORTABLE set which can be easily carried on any occasion, and disposed of in any odd corner of one's bag, is a useful addition to the wireless kit.

This design was worked out with that end in view, and the set can, as a matter of fact, be carried in the jacket pocket, without, of course, the H.T. and L.T. batteries and valve, which can easily be stowed away in one's bag when a dull emitter is used.

The various components are designed in such a manner that the principal parts of the set are, in a practical manner, pocketable, and, with that end in view, a variometer was chosen as the tuning component, so avoiding the bulk of a coil and condenser.

For the same reason, and to enable either bright or dull emitter valves to be used at option, a Lissenstat Minor filament control was used in the valve circuit, and also "Clix" terminals and flexible connections.

The Complete Set

The photograph Fig. 1 shows the complete set ready for use, and it will be seen that the variometer used for tuning consists of two basket coils connected in series by a flexible lead, the other leaf of the component being the reaction coil.

Fig. 2 shows the circuit used, being a straight circuit with reaction on to the aerial.

In the photographs Figs. 4 and 5 and drawing Fig. 7 the variometer unit is shown in detail.

It is made up of three wooden leaves hinged together like a book.

This is made in mahogany $\frac{3}{8}$ in. in thickness, and has each coil sunk into the thickness of the wood, the aerial and reaction coils being let in flush with the surface

of the piece; the centre coil is secured in place in a hole of the required diameter, which is bored right through the wood, and the coil held in position by painting the edge of the hole with thick shellac, and when this is "tacky" pressing in the coil.

When dry it will be found to be very firmly held in position.

The aerial and reaction coils are held in place by shellacked card-

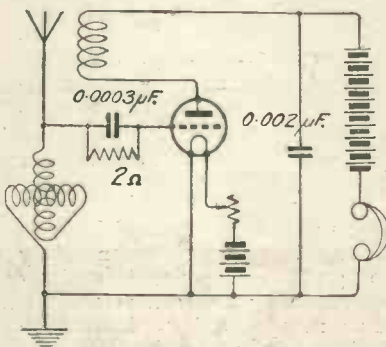


Fig. 2.—Theoretical circuit diagram of the set.

board washers, secured to the wood with a small round-headed brass screw.

The ends of the two aerial coils which form the variometer, and which have to be connected with a flexible wire, are marked with a white or coloured dot made with the point of a drill and filled with paint,



Fig. 3.—The valve unit ready for use.

and the ends of the various coils secured under their various terminals.

The terminals are mounted in $\frac{1}{4}$ in. ebonite bushes let in flush with the surface, a tight fit in the wood leaf, and tapped to receive the terminal shank, a corresponding hole being bored in the adjoining leaf to allow the unit to close flat.

The three leaves are hinged together with small brass hinges.

The edges and corners of the three leaves are rounded, and the whole unit carefully glass-papered and finally french polished.

With the flexible connection to the variometer removed, the whole unit can be closed up like a pocket-book as shown in the photograph.

The Coils

The coils used are designed for reception of 210 and consist of basket coils wound on a 1 in. former having thirteen spokes.

They are wound with No. 22 D.C.C. wire, and are not shellacked except for a touch at each spoke for ease when removing the former.

The coils have the following number of turns: aerial coil (first leaf) 20 turns, single basket type, (i.e., over one spoke and under next), the inner end being connected under the "aerial" terminal, and the outer or finishing end under the other terminal: this terminal is to be marked with a white dot.

This terminal is to be connected by a flexible lead to the terminal connected to the inner end of the centre coil (also marked with a white dot), which is of 20 turns single basket wound, the finishing end of which is connected under the other or "earth" terminal: the ends of the coil windings should be sunk

This portable receiver is essentially practical and will appeal to the constructor who desires extreme portability in his receiver, or who is interested in unique designs.

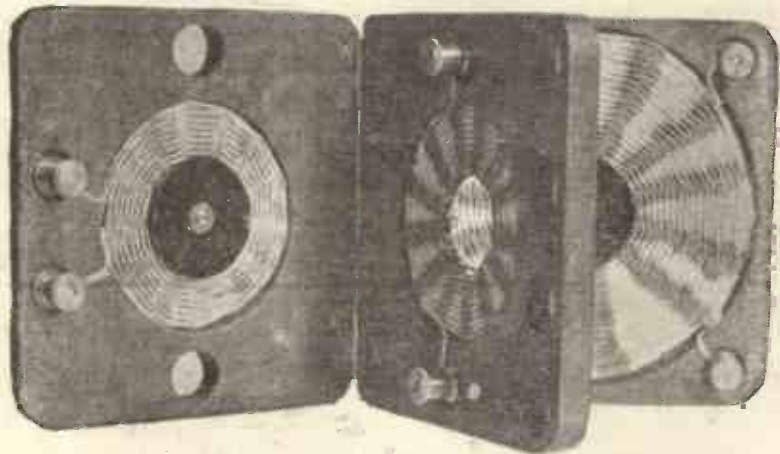


Fig. 4.—The ingenious method of mounting the coils is clearly shown.

in a shallow groove cut in the wood leaf.

The reaction coil (the largest of the three coils) is wound with the same gauge of wire on the same size of former, and has 19 turns wound double basket fashion, *i.e.*, over and under two spokes of the former, to reduce the diameter of the coil.

As each turn counts as four in a coil wound double basket fashion, this coil is equal to a .75 turn single layer coil.

The valve unit is built up in the form of a small box, as shown in Fig. 9 and the photograph Fig. 3; it is made in $\frac{1}{4}$ in. mahogany french-polished, and with rounded edges and corners, and the bottom is



Fig. 5.—The variometer unit closed, with connections detached.

made with a sliding lid, like a child's pencil box, to enable the wiring to be examined.

The valve holder is let in flush with the surface, and consists of a disc of $\frac{1}{4}$ in. ebonite with four valve

sockets pressed into the holes a really tight fit; these should have their screwed shanks cut off to reduce the depth, and the wiring soldered to the actual socket. It is secured in the wood forming the box by making the hole for its reception a tight fit for the disc and the edges shellacked and driven in.

The Lissenstat Minor is provided with a one-hole fixing, making it an easy matter to fix this component.

The "Clix" terminals are just as easily fixed in position, having small ebonite bushes for insulation, one on each side of the hole in the wood sides of the box, and which may be obtained in various colours for their appropriate terminals, red for positive, black for negative, etc., and the "Clix" socket secured in them with the milled nut provided on the shank.

Tabs marking the various connections should be fixed to the sides of the box with shellac, under their proper bushes.

The .003 condenser (a "Dubilier") and two megohm grid leak, and also the .002 condenser, should next be fixed to the bottom of the box in the positions shown.

Before fixing the "Clix" terminals, etc., the ends should be well cleaned and tinned in readiness for wiring up.

Wiring

The wiring is done with soft copper wire cased in systoflex, and in so small a unit requires care, but an examination of the drawings and photograph Fig. 6 of the inside of this unit should make the wiring up quite easy to follow.

The connections between variometer and valve units are made with flexible connections, ordinary


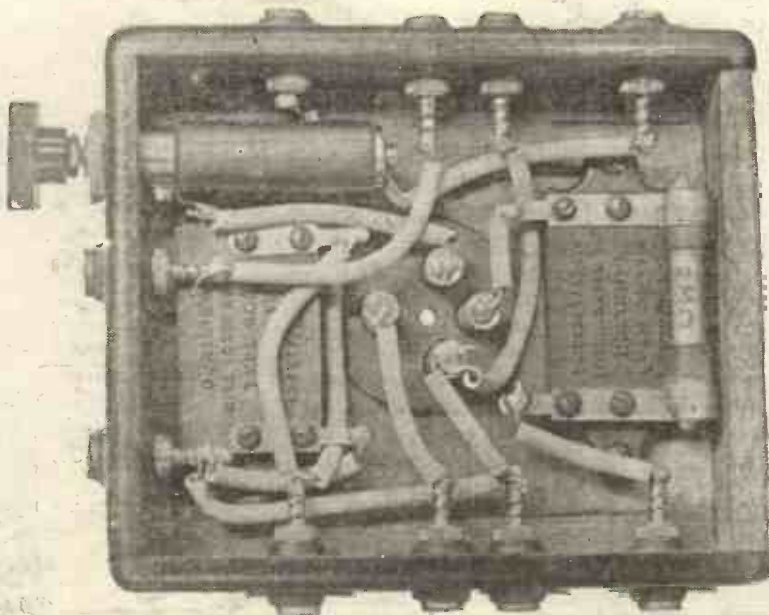


Fig. 6.—The underside of the detector unit, showing the systoflex wiring.

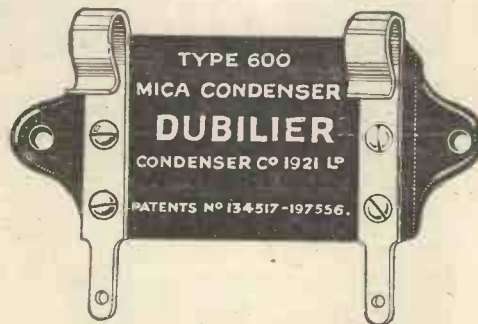

Type 600—For all purposes in connection with receiving apparatus. With or without clips for grid leak.
 0.0001—0.0009 2/6 each
 0.001—0.006 3/- each

Type 6002—As Type 600 but for vertical panel mounting.
 0.0001—0.0009 2/6 each
 0.001—0.006 3/- each

DUBILIER GUARANTEE.

Your only safeguard lies in purchasing the products which carry the guarantee of a firm with a reputation to maintain.

All Dubilier fixed condensers are guaranteed to be within 15 per cent. of their stated capacity, and where desired they can be manufactured and guaranteed within still closer limits. The type 600 illustrated here and the type 600a are practically universal amongst manufacturers of complete sets, whilst experienced home constructors continually assure us that they can feel complete confidence in the working of their sets when—and only when—they have fitted Dubilier Condensers. See that they are in your set as well.



Eucon Works,
 Goldhawk Road,
 London, W. 12.

Telephone :
 Riverside 1084.
 Telegrams :
 Hivolteon, Phone
 London.



To a Hair's Breadth

THE smith demands the highest degree of accuracy from his steam hammer.

It must respond instantly, and deliver a giant blow of twelve tons or a light tap barely sufficient to crack a watch glass, and it must never make a mistake.

The smith gets the best out of his hammer because the best workmanship and materials have been put into it.

You should see that no component finds its way into your wireless set unless you can feel entire confidence in it.

Eighty per cent. of the complete set manufacturers in Britain as well as thousands of experimenters employ Dubilier Condensers and Resistances in their sets.

They know that a product bearing the name Dubilier can be trusted implicitly to do what is expected of it, and they count the few extra pence spent on it as sound insurance against disappointment.

You should specify Dubilier.



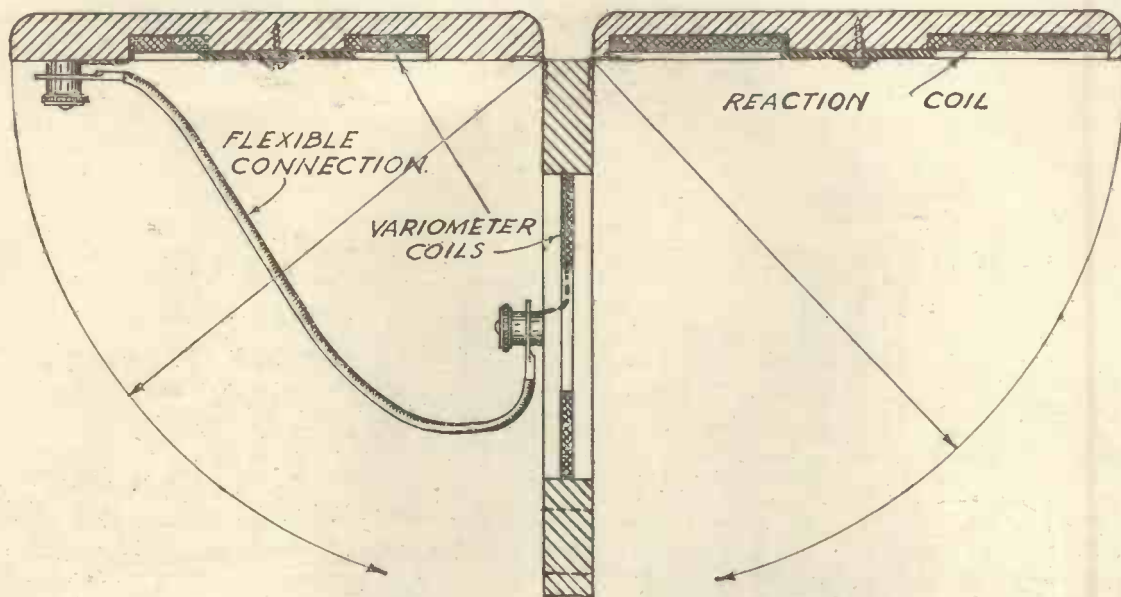


Fig. 7.—The method of mounting the coils in the variometer unit is clearly shown.

single lighting flex being used, with the silk or cotton covering removed.

The ends connected to the valve unit are fitted with "Clix" sockets, and the other ends have spade terminals to go under the screw-down terminals of the variometer and the L.T. battery.

The H.T. connections are, of course, fitted at the battery end with the proper wander plugs.

Operating the Set

The set having been connected up and a valve inserted in its holder, adjust the Lissenstat to the brightness appropriate to the type of valve used.

Keep the leaves of the variometer well apart at first, particularly the reaction coil leaf, to avoid interference with near-by listeners, then adjust the variometer by

bringing the two leaves closer to each other until the best position is found: then carefully bring the reaction coil leaf closer to centre leaf (without moving the other or aerial leaf of variometer) until the best strength is obtained without oscillation, and finally slightly adjust the variometer as may be necessary.

Should no increase in the strength of signals occur when the reaction

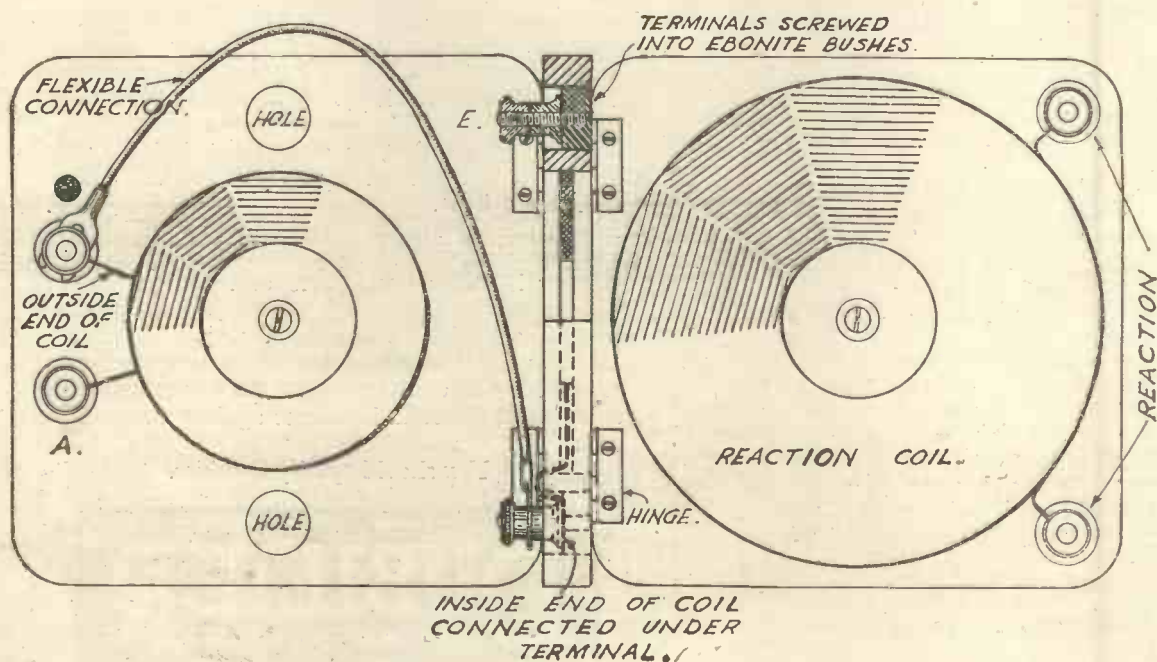


Fig. 8.—Showing the method of mounting the reaction and stationary aerial coils.

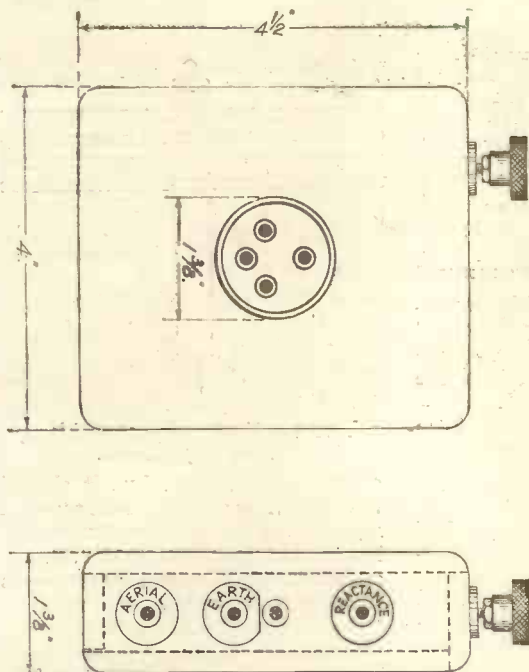


Fig. 9.—Front and side elevations of the detector unit.

coil is brought closer to the variometer coils (showing that the reaction coil is connected the wrong way), reverse the ends of leads, when the desired effect should be obtained.

At twelve miles from 2LO excellent reception is obtained with this set; and its compactness, to say nothing of its portability, should recommend it to those who like tidiness at home.

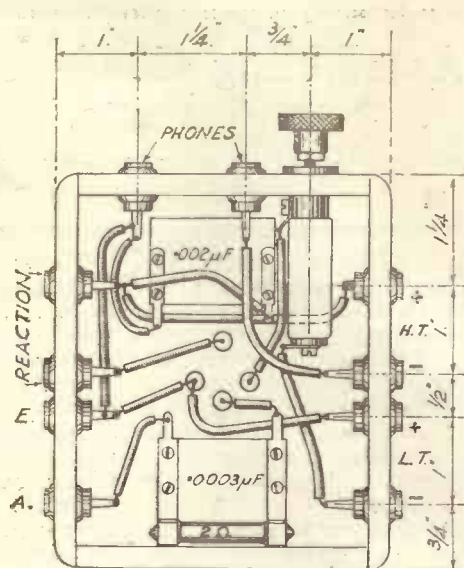


Fig. 10.—The underside of the valve unit, showing wiring.

[EDITOR'S NOTE.—Although designed for 2 LO, this set should suit all waves between that of Cardiff and Newcastle. For longer wave stations we suggest increasing both variometer coils by 6 or 7 turns.]

The S.T. 100 Set

To the Editor of THE WIRELESS CONSTRUCTOR.

SIR,—A short time ago I made up a set as instructed in the Radio Press Envelope No. 1. Using dull emitter valves (B.T.H. B5) with ninety volts on the plates and a three-volt battery across the grid bias terminals, I get all the B.B.C. main stations at splendid signal strength, London, Bournemouth, Manchester and Newcastle coming in especially well. Both Bournemouth and 5XX come in at good loud speaker strength. This is, of course, after sunset, although 5XX comes in equally well by day and night. By day I get Radio Paris at good strength on two pairs of headphones. By night I also get Lyons, Ecole Supérieure and Madrid quite comfortably. The new Belfast station comes in, of course, very well. The other night I picked up Nottingham (testing) direct, which, taking into account the low power of this station,

speaks volumes for the set. My aerial is none too good, being rather badly screened by trees.

I have no hesitation in saying that the ST100 is the best two-

valve set I have ever heard.

Yours truly,

A. J. S. BRADY.

Macroom,
Co. Cork.



Professor Branley, inventor of the wireless coherer, who has just celebrated his eightieth birthday.

Assembling Condensers from Parts.

An article which will assist the constructor who is keen on making his own components.

ALTHOUGH so many excellent condensers are on the market that the wants of the average constructor are amply supplied, yet for reasons of economy or for enthusiasm over home-made apparatus, the amateur may desire to construct his own variable condenser from the many sets of parts that are now available.

Modern parts are more accurate, and the constructor may commence building a variable condenser in

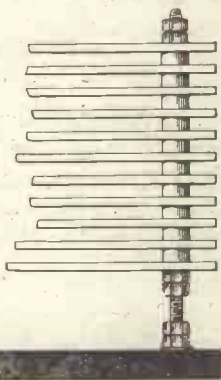


Fig. 1.—Showing how fixed plates are secured.

full confidence that it will, on completion, compare favourably with commercial products.

Fortunately the parts that are now produced may be assembled to form a condenser that has a capacity value at least approximate to the correct theoretical value. This in early sets of parts was not so, and a 0.001 μF condenser assembled from parts often proved on test to have a maximum capacity of only 0.00075 μF .

Drilling Valve Socket Holes. An Emergency Tip.

ALTHOUGH many excellent valve holders that are suitable for all general occasions are obtainable and will obviate difficult drilling of panels, the constructor is sometimes faced


The fixed vanes should be assembled first in the manner indicated in Fig. 1, and the square centre spindle may be inserted into the framework, when mounted.

Connection to the moving plates may be made by a short length of flex—this being the simplest method—but care must be taken that permanent contact is not destroyed by undue rotations of the vanes.

Condenser stops, mounted either on the panel or on the condenser frame, will obviate this difficulty.

Care should be taken when choosing sets that the top and bottom bearing plates are of considerable strength and are accurately drilled, since these plates form the foundation of the condenser. End plates may be either square or triangular; the use of this latter shape of end plate economises space, which is very desirable where panel mounting is considered.

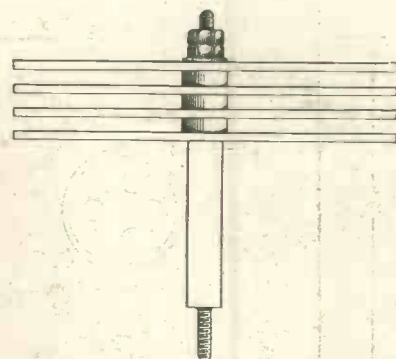The lengths of the supporting rods and centre spindle will, of course, vary with the number



The method of assembling moving vanes.

of plates necessary, but it should be noted that only the best screwed rod should be used, since cheap, light rod will often have the threads stripped off if much pressure is brought to bear on the end nuts.

In Fig. 1 it will be noted that although the holes in the end bearing plates are drilled, additional security and strength is given by the lock nuts screwed in hard against the end piece.

The table given below shows the necessary sizes and number of parts for condensers of the more usual capacities, constructed with plates of $1\frac{1}{2}$ in. radius and $\frac{1}{8}$ in. spacing washers:—

The moving spindles may, of course, be any length, but it will be found most convenient to make them about $1\frac{1}{2}$ in. longer than the corresponding side supports.

Capacity.	No. of plates.		No. of washers.		Length of side rods. Inches.
	Fixed.	Moving.	Fixed.	Moving.	
.0015 ..	43	42	126	41	8
.001 ..	29	28	84	27	6
.0005 ..	15	14	42	13	4
.0003 ..	10	9	27	8	3½
.0002 ..	7	6	18	5	3
.0001 ..	4	3	9	2	2
.00005 ..	2	1	6	0	2

with the problem of drilling holes in a panel for valve sockets.

The "staggered" unequal spacing of British valve legs, although conducive to safety when the valve is inserted, renders the task of drilling difficult. Unfortunately templates are not supplied with valves, and, although a good template is an invaluable possession, there will come a time when a hurried job is on hand, and no template is available.

The simplest method to adopt on such an occasion is to construct a simple template by pressing a

valve firmly on to some soft paper and to drill through these indentations on to the panel.

Trouble may be experienced in fitting, since, unfortunately, valves are not made absolutely to a standard, and considerable displacement of the pins of another valve may be necessary before easy insertion is possible.

There are on the market, however, several excellent templates which greatly facilitate this operation, and the serious constructor is advised to have one always handy.



Buy Sterling Components

Sterling Components are British made from the highest grade materials and have obvious points of advantage in finish and workmanship. They consistently give amazing results, pass any test or comparison and unfailingly satisfy radio enthusiasts.

STERLING VARIOMETER

An instrument of unique design which tunes from 250 to 2,725 metres. Very selective; inductance ratio 9:1. The rotor and stator windings are connected to separate terminals to facilitate connecting in series or parallel as required in conjunction with condensers of appropriate capacity, to cover the wave-ranges as published in the chart supplied with each instrument. Supplied complete with dial and knob as shown.

PRICE 21/-

STERLING SEMI-AUTOMATIC CRYSTAL DETECTOR

Novel in design, easy to adjust and very effective in use. Many sensitive points on the crystal are instantly found by revolving the small milled wheel shown. Entirely enclosed, protecting the crystal and point from dust and oxidation. Complete with screws for panel mounting.

PRICE 8/-

STERLING VARIABLE SQUARE LAW CONDENSERS.

With specially shaped vanes giving uniform wave-length variation and practically zero minimum capacity. The end plates are arranged for either horizontal or vertical mounting. Unrivalled for use in receiving sets and specially recommended for use in the construction of wave-meters and other Radio measuring instruments.

Capacity.	With Vernier Adjustment.		Without Vernier.	
	For Panel Mounting as illustrated.	In Case with Ivorine Dial Mounting.	For Panel Mounting.	In case with Ivorine Dial.
*00025 mfd. ...	£1 3 0	£2 2 6	£1 0 0	£1 19 6
*0005 mfd. ...	£1 5 6	£2 5 0	£1 2 6	£2 2 0
*001 mfd. ...	£1 10 6	£2 10 0	£1 7 6	£2 7 0

FOR CONTROLLING H.F. AMPLIFICATION (Without Vernier)
 *00025 mfd. (each unit) - - - - - £1 7 6
 †00025 mfd. (each unit) - - - - - £1 15 0

*For controlling two stages. †For controlling three stages.


STERLING LIGHTWEIGHT HEADPHONES

Supreme in tone, volume and quality. As light as good headphones can be and as comfortable as good headphones should be. Fitted with polished Duralumin headbands.
 120 ohms the pair £1:2:6 2000 ohms the pair £1:4:0
 4000 ohms the pair £1:5:0

Obtain from your radio dealer.

Advt. of **STERLING TELEPHONE AND ELECTRIC CO., LTD.**

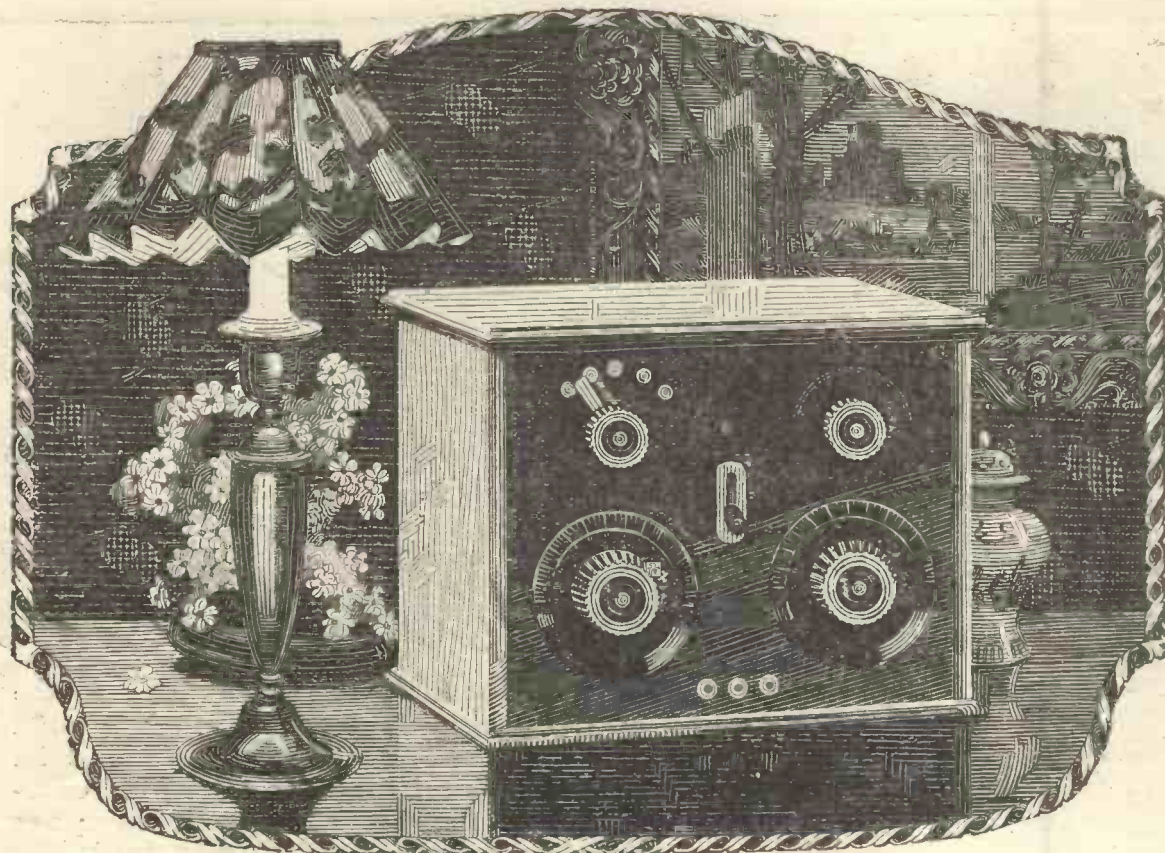Manufacturers of Telephones and Radio Apparatus, etc. Telephone House, 210-212, Tottenham Court Road, London, W.1
 Works - - - - - DAGENHAM, ESSEX.



**A cheap Panel—
may be the most expensive
part of your Receiving Set.**

NOT everything masquerading as ebonite is worth using as a panel—in fact, it is difficult to conceive a greater test for any insulation material than to use it in a Wireless Set. The extremely weak impulses received upon your aerial, when conveyed to your Set, so readily leak away that the greatest care must be taken to preserve them if you are going to receive any signals at all. That is why a cheap panel can be easily proved to be a waste of time and money. Radion is the highest grade of insulation in the world, and has been specially developed for wireless use. Its highly-polished surface, which need not be removed before use, enhances the appearance of the finished instrument and prevents the formation of dust.

Radion is sold in black and mahogany—a beautiful colour, very similar to old mahogany—with dials and knobs to match. It is packed in stout envelopes in the convenient sizes shown below. For your next set choose Radion—every panel is stamped—then you can be certain that it will look better and work better.

Size	Black	Mahogany	Size	Black	Mahogany	Size	Black	Mahogany
6" x 7"	3/6	4/3	7" x 14"	8/-	10/3	8" x 26"	17/6	21/3
6" x 10 1/2"	5/3	6/6	7" x 18"	10/6	12/9	9" x 14"	10/6	12/9
6" x 14"	7/-	8/6	7" x 21"	12/3	15/-	10" x 12"	10/-	12/-
6" x 21"	10/6	12/9	7" x 24"	14/-	17/3	12" x 14"	13/3	16/-
7" x 9"	5/3	6/6	7" x 26"	15/-	18/6	12" x 21"	19/9	24/3
7" x 10"	5/9	7/3	7" x 30"	17/9	21/6	14" x 18"	19/9	24/3
7" x 12"	7/-	8/6	7" x 48"	28/-	34/6	20" x 24"	39/6	48/-

Special Note:—All 1/8" thick—quite sufficient owing to Radion's tremendous strength.

Dealers: If you have not yet received particulars of the Radion proposition write to us to-day.

FROM ALL DEALERS.

RADION  **FOR PANELS**

AMERICAN HARD RUBBER CO. (BRITAIN), LTD.

13a, Fore Street, London, E.C.2.

Gilbert Ad. 169r



More About "The Wireless Constructor" Neutrodyne Set.

Hints on Adjustment and Tuning.

By PERCY W. HARRIS.

(Continued from page 37, last month.)

FOR testing purposes it is just as well to join the three high-tension positives together as shown, a lead being taken from any one of them to the positive side of the high-tension battery, the negative side of which, of course, is connected to the negative H.T. terminal indicated. Connect a pair of telephones to the correct terminals and short the grid bias terminals, or, if you are using a grid bias battery, connect in cells of the right value. Plug in to the secondary socket a suitable coil for the wavelength range (a number 50 coil is recommended for most of the British broadcasting), and short circuit the reaction terminals, without inserting the reaction coil in the socket for the moment. The shorting of the reaction terminals is easily effected by joining a wire between them. Plug in the "Clix" plugs into the sockets so as to obtain the $.0005 \mu F$ value in the aerial tuning condenser, and the $.00025$ in the secondary or closed circuit. Put the switch on the "tune" position.

Neutralising

Set the closed circuit condenser at some intermediate value, say at 30° , plug into the transformer socket of the valve panel a suitable transformer for the wavelength range desired, turn the knob of the neutrodyne condenser in an anti-clockwise direction as far as it will go (this will be upwards). Read the previous remarks through again to make sure you perform these actions in correct order, as this part of the process is important. Now turn the knob of the anode condenser backwards and forwards a few times. You will find that the set will burst into oscillation and will remain in oscillation over a wide range of the condenser readings, perhaps coming out of oscillation again towards one or both ends. When you have found that

the set oscillates over this wide range of condenser readings, turn the knob of the neutralising condenser two or three times and observe that the width of the band over which the oscillation tunes will be reduced. Now turn the condenser knob again and once more rotate the anode tuning condenser. For each adjustment of the neutralising condenser you will find the band over which the anode condenser will oscillate becomes narrower and narrower. As this band reduces in width turn your neutralising condenser more care-

terminal and when you withdraw your finger. If the set is not oscillating there will be only a slight click when you touch it and not at all when you withdraw your finger. Now, having reached the point of adjustment when the set will oscillate on just one degree, give a very slight turn more and you will find the set will not oscillate at all. Leave the neutralising condenser in this position; it will not need to be touched again so long as you are using a particular valve and a particular transformer, although, of course, if you are curious you will



The aerial mast on a lifeboat of the s.s. "Aquitania" fitted with wireless.

fully until a point is reached when perhaps the anode condenser will only oscillate at one degree in its setting. You can tell when the set is oscillating by touching the grid terminal of the valve panel with your wet finger. If the set is oscillating there will be a loud "plonk" both when you touch the

adjust it sometimes just to see what happens! If the neutralising condenser has no effect you may need to reverse the leads to primary of the plug-in H.F. transformer. This is occasionally necessary as transformers are not all wound the same way.

The set is now "neutralised"; the



Winding basket coils at the Broad-water Road L.C.C. School, Tooting.

secondary coil is fairly close to the aerial the set is easier to tune but not so selective. If "standby" adjustment is used you will tune only on aerial and anode condensers. The reaction leads will need to be reversed when using this method.

Results.

The results I have obtained on



All the boys are keen wireless "fans."

next step is to remove the short circuiting wire from the reaction terminals of the valve panel and to plug in a small reaction coil (say a 25). You will now need to insert a coil in the aerial socket and connect the aerial and earth to the set. A 25 or 35 plug-in coil will do in the aerial socket when the condenser is in parallel and a 50 or 75 when the condenser is in series. Some coils are not numbered 50, 75, etc., but have letters such as A, B, C, or S1, S2, etc.

If you are working on the "tuned" side you will need a very small reaction coil, say 25 or its equivalent.

The next step is to see whether the set will oscillate when you move the reaction coil towards the aerial coil. If it does so, well and good; it should do so if you have followed my connections. If it does not, try reversing the leads between the reaction terminals.

The method of operation of the set is rapidly found by trial. Set the anode tuning condenser at about 20 deg. and then vary the

aerial and secondary condensers until you pick up the local station. Keep the reaction coil well away from the aerial coil for the moment. When you have obtained the best adjustment for A.T.C. and C.C.C. circuits, readjust the anode tuning condenser for best results. A slight amount of reaction can then be applied. The potentiometer will give final adjustment and once the best position of this latter has been found it can be left set so long as this particular valve is used.

To pick up other stations, follow the same procedure. I advise you to keep to the tune side, and to work with the secondary coil well away from the aerial coil. If the

this set have been distinctly better than on any other three-valve set I have designed. At various times I have had all the B.B.C. stations on the loud-speaker, and any evening three or four can be heard in this way. Selectivity is very high. For example, Madrid can be heard on the loud-speaker with no interference whatever from Newcastle. This is a difference of only eight metres. London at seven miles can be cut right out when receiving all but Manchester. German stations are frequently of loud-speaker strength and Ecole Superieure is always receivable at L.S. strength. American broadcasting is also heard quite regularly.

Hector and the Witching Waves.



ANYTHING from ANYWHERE The DUODYNE III



A Genuine Long-Distance Receiver
of
Exclusive Merit
Two Stages of High-Frequency Amplification
Automatic Tuning

In the Duodyne III the fullest advantage has been taken of the extraordinary virtues of the Curtis Constant-Tuned High-Frequency Amplifier. The first valve functions through the Curtis High-Frequency Amplifier, the second as an orthodox tuned anode, and the last as a rectifier. Guaranteed perfect reception at full power and of extraordinary purity from anywhere in the United Kingdom of any broadcasting station from Aberdeen to Madrid.

Used in conjunction with the CURTIS EJECTOR will tune in any Broadcasting Station at will!

In spite of a multiplicity of stations operating on a congested wave band, the Duodyne and Curtis Ejector regains that true fascination of wireless of "listening-in" at—where you will and when you like.

PRICE £10

The DUODYNE V

Combines the Duodyne III with a two-stage power Amplifier and constitutes a Receiver of remarkable power and receptivity.

Liverpool or Manchester on a Loud Speaker with 2LO cut out! The DUODYNE V is obviously an ideal demonstrator.

The exquisite purity of loud-speaker (Amplion) reproduction with a Duodyne V is a positive revelation and has never been equalled by any professional model.

PRICE £18 18 0

The DUODYNE Receivers, with their extraordinary range and power make an irresistible appeal to those countries where Broadcasting Stations are not so plentiful as they are in the United Kingdom. The DUODYNE brings the pleasure of "listening-in" to all, wherever situated throughout the world.

Average range in miles of Duodyne Receiver under average conditions on P.M.G. aerial:

	Headphones.	Loud Speaker.
DUODYNE III	3/4,000	1,000/1,200
DUODYNE V	4/5,000	

WAVETRAPS HAVE FAILED.

BUT not because of any inefficiency of the wavetraps, but rather because the receivers with which these were used did not have sufficient reserve of power to stand the loss inherent with a wavetraps and yet "fetch in" the more distant stations.

On a conservative basis the Curtis Ejector with the Duodyne III will cut out principal station (1 1/2 kw.) at one mile and bring in 25 per cent. of the stations; at four miles and bring in 50 per cent. of the remaining stations; at six miles and bring in all British Stations at will.

THE CURTIS EJECTOR - - - - - 35/-
PRACTICALLY ELIMINATES MORSE AND MUSH

THE CURTIS CONSTANT-TUNED HIGH-FREQUENCY AMPLIFIER



**NO CONTROLS
NO CONDENSER**

ABSOLUTELY AUTOMATIC TUNING

IT is quite possible for a signal, practically inaudible on headphones with even one high-frequency and detector valves, to become positively deafening when passed through two stages of low-frequency amplification, but the reproduction will be far more distorted than if the detector signal strength had been twice as loud, when only somewhat less than half the amount of low-frequency amplification would be required to yield the same volume of audibility. It is axiomatic that the louder the signal strength at the detector valve, the less low-frequency amplification required for any given volume of audibility, and correspondingly more natural and tuneful reproduction will result.

YOU CANNOT USE TOO MUCH HIGH-FREQUENCY AMPLIFICATION NOR TOO LITTLE LOW-FREQUENCY AMPLIFICATION FOR PERFECT REPRODUCTION.

BUT the use of more than one stage of high-frequency amplification has hitherto proved to be commercially impracticable, because of the extreme difficulty in tuning, and the need for considerable skill and patience to obtain results which, even at best, would be erratic and unreliable. Designers and Manufacturers have therefore been compelled to rely on the employment of excessive reaction and low-frequency amplification to make up for the weakness of the received signal, with consequent comparative distortion.

The Curtis "Constant Tuned" High Frequency Amplifier is the only automatic high-frequency amplifier on this or any other market which, when connected in circuit, guarantees high efficiency for two stages of radio amplification on any wavelengths between 300 and 3,000 metres, and requires no additional controls, NOR MORE EFFORT, SKILL OR PATIENCE IN TUNING, THAN IS REQUIRED FOR THE OPERATION OF THE USUAL ORTHODOX SINGLE STAGE TUNED ANODE CIRCUIT.

THE CURTIS CONSTANT-TUNED HIGH-FREQUENCY AMPLIFIER CHANGES THE WHOLE CHARACTER AND QUALITY OF WIRELESS REPRODUCTION.

WITH its automatic simplicity, combined with increased selectivity and power, is predestined to make two stages of high-frequency amplification a sine qua non of every Wireless Receiver for the Experimenter and Home Constructor, or the purchaser who prefers to buy a professionally constructed instrument.

For the greater convenience of the constructor, and so as to conform with existing panel design, the Curtis Constant-Tuned High-Frequency Amplifier is designed for use and must be connected up in exactly the same way in which an ordinary High-Frequency Transformer is used.

The Curtis High-Frequency Amplifier may be instantly substituted for any High-Frequency Transformer in any existing circuit or instrument where such is used, but the corresponding condenser of such transformer must be turned to zero or any one wire disconnected therefrom.

The Curtis Constant-Tuned High-Frequency Amplifier guarantees such a reserve of receptivity as to permit the efficient use of a suitably designed wavetraps.

TEN DAYS' FREE TRIAL

So as to give all an immediate opportunity of testing the efficiency of the Curtis Constant Tuned High-Frequency Amplifier, without cost, we undertake to refund your money in full if the Amplifier is returned to us, postage paid, within 10 days of your receipt.

Model A, 300 to 800 metres, 15/-, postage 6d.

Model B, 800 to 3,000 metres, 17/6, postage 6d.

HAVE AT HAND
Our 16 pp. Catalogue of
Raw Materials and accessories
FREE ON REQUEST

PETER CURTIS, LTD.

75, CAMDEN ROAD, N.W.1.

Telegrams: "Paracurtex." Phone: North 866.

BIRMINGHAM: 76, Newall Street. Central 7236.
MANCHESTER: 312, Dean-gate. Central 5095.

In conjunction with

THE PARAGON RUBBER MFG. CO. LTD.

What
Mr William
Le Queux thinks
of the



B.T.H.

B4 Valve

6 VOLTS—0.25 AMPS.

MR. WILLIAM LE QUEUX, the famous novelist, is equally famous in the world of radio technics. He was one of the pioneers of wireless, and has been experimenting for 20 years. His transmitting station 2.A.Z. at Guildford was the first station in the world to broadcast regularly every night.

Mr. William Le Queux, as a result of his Jungfrau experiments, has proved the superiority of the B4 Valve—the first of its kind, and the best

The B.T.H. Type B4 Valve was the first valve taking only 0.25 amperes at 6 volts sold in this country. It is acknowledged as the supreme valve for use as a low frequency power amplifier.

Obtainable from all Electricians & Radio Dealers

TELEGRAMS—
"LUXURIE BECKY, LONDON"
TELEPHONE—PRESENT 8772 (5 Lines)

Sept. 1924

DEVONSHIRE CLUB,
ST. JAMES'S, S.W.1.


To the British Thomson-Houston Co. Ltd.

Sir, It may perhaps interest you to know that during my recent experiments in reception of the B.B.C. stations upon the Jungfrau & other points in the Alps I tested many makes of valves. The ones which gave by far the best all-round results were the B.T.H. B4—one of which in my opinion is equal to two of any other. I strongly advise every amateur to use them.

William Le Queux

Sir,
It may perhaps interest you to know that during my recent experiments in reception of the B.B.C. stations upon the Jungfrau and other points on the Alps I tested many makes of valves. The ones which gave by far the best all-round results were the B.T.H. B4—one of which, I consider, equal to two of any other. I strongly advise every amateur to use them.

(Signed) WILLIAM LE QUEUX

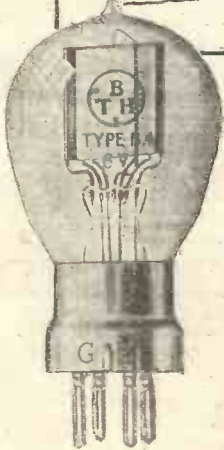

The British Thomson-Houston Co. Ltd.

Works: Coventry. Offices: Crown House, Aldwych, London, W.C.2

Branches at: Belfast, Birmingham, Bristol, Cardiff, Dublin, Glasgow, Leeds, Liverpool, Manchester, Middlesbrough, Newcastle, Sheffield, Swansea

Price 35/-



A Simple and Efficient Method of Winding Coils

By P. BYE

ONE of the most common tasks of the enthusiastic experimenter is the winding of various kinds of coils, such as tuning coils, choke coils, windings for transformers, resistances, etc. Many—probably the majority of amateurs—do not possess winding instruments, and hence have to wind their coils by hand, a process which can hardly be considered satisfactory.

The winding of coils of many turns of fine wire by hand is extremely tiring and the necessity of counting each turn very irksome.


We, therefore, exert our energies towards seeking a cheap and efficient method of winding coils and means of ascertaining the

in diameter cut in the centre of it to a depth of about $\frac{1}{4}$ in. The purpose of this hole is to make a clearance for the hub of the sewing machine wheel. It is immaterial whether the hole is round or square, provided it is large enough to clear the hub. Many readers will find it most convenient to cut a square hole.

Several holes about $\frac{1}{4}$ in. in diameter are drilled all round the wheel about $\frac{1}{2}$ in. from its edge. These holes are for the binding string to pass through.

Mounting the Former

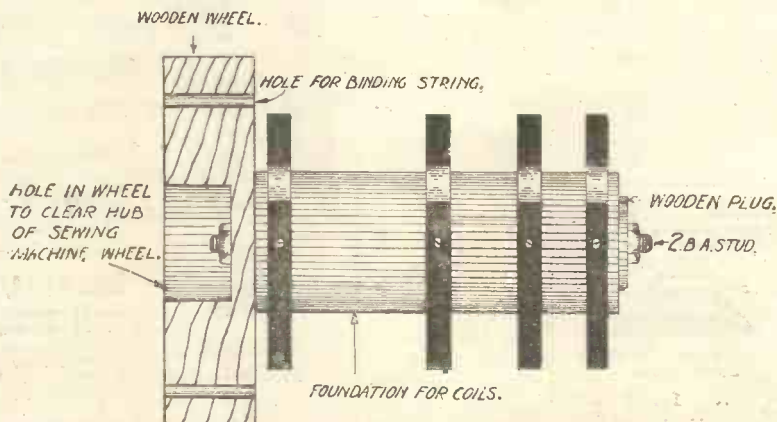The foundation of the coil to be wound is mounted on the wheel by means of a short length



The illustration shows the construction of the wooden block, which is attached to the machine, and a coil former in position.

number of turns without mental effort.

When looking for a cheap method we usually try to adapt to the purpose some instrument already in our possession. The author has long employed an instrument, some make of which is to be found in most homes, and it is hoped the following hints will be useful to many readers.

Those amateurs who are fortunate enough to have the use of a treadle sewing machine have an excellent instrument for both winding and counting.

Adapting the Machine

An improvised wooden wheel (see Figure) about 1 in. thick is made, having a hole about $1\frac{1}{2}$ in.

of 2 B.A. rod passed through the centre of the foundation and through a hole in the exact centre of the wheel. Nuts are put on the ends of the rod and screwed up tightly.

It will be seen that the tubing of the coil foundation illustrated has been plugged with wood. Readers will understand that this process is necessary when tube of large internal diameter is used.

Method of Attachment

The wooden wheel is bound tightly to the spokes of the sewing machine wheel by means of stout string. It is essential that the end of the 2 B.A. rod should be exactly opposite the centre of the hub of the sewing machine

wheel, in order to prevent any wobbling of the coil foundation.


It will be found that on treadling the whole contraption turns very smoothly.

The method of counting the turns is as follows:

For every revolution of the sewing machine wheel a stitch is made, so all we have to do is to proceed as if sewing and count the stitches. The easiest way of doing this is to take the cotton off the machine and adjust the latter to make large stitches. Take a long piece of plain paper and sew from one end to the other in a straight line, count off from one end one hundred holes thus made and cut off the surplus paper beyond the hundred holes. All one has to do then is to sew straight up and down the paper, counting a hundred turns for each complete journey up or down. By this means thousands of turns can be wound in a few minutes and the number of turns is found without calling for any mental effort.

A Valve Shield to Obviate Glare

THE glare of bright emitter valves is often found trying to the eyes. By putting these simple protectors over the valve the glare is reduced to a minimum. A piece of cardboard tube of sufficient diameter to slip over the valve and of sufficient length to just clear the panel is cut, and a circular piece of cardboard glued or scotch-taped to the end. This disc has a small hole cut in the top, which rests on the pip of the valve. The accompanying sketch illustrates the idea.

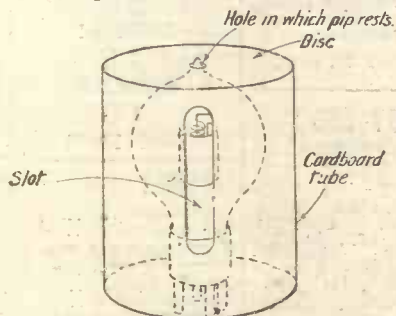

This diagram shows how the shield encloses the valve.

A narrow slot is cut up one side of the tube so that the brilliance of the valve may be examined by turning the device round. The slot can, of course, be turned away from the eyes when required.

HULLO EVERYBODY!

LISSEN.

Variable Grid Leak 2/6
 Anode Resistance 2/0
 Lissen Minor .. 3/6
 Lissenstat .. 7/6
 Do. Universal .. 10/6
 2-way Switch .. 2/9
 Series Parallel .. 3/9
 T1 Transformers.. 33/
 T2, 25/-; T3, 16/6;
 Coils: 25, 4/10; 30, 35,
 40, 4/10; 50, 5/-; 60,
 5/4; 75, 6/4; 100, 6/8

POST 3d. each.

DUBILIER.

.001, .002, .003, .004,
 .005, .006, Fixed, 3/-
 .0001, .0002, .0003,
 .0004, .0005 .. 2/6
 Type 577, .01 .. 7/6
 Grid Leaks each 2/6
 Anode Resistance
 50,000, 70,000,
 80,000, 100,000,
 on stand complete 5/6
 Minicap Switch .. 8/-

POST 3d. each.

IGRANIC.

Coils: 25, 5/-; 35, 5/-;
 50, 5/2; 75, 5/6; 100,
 7/-; 150, 7/10; 200,
 8/8; 250, 8/-; 300,
 9/5; 400, 10/3; 500,
 10/6
 Fil. Rheostat .. 4/6
 Potentiometer .. 7/-
 Vernier Rheostat.. 7/6
 30-ohm Rheostat.. 7/-

POST 3d. each.

STERLING SQUARE LAW CONDENSERS.

with Vernier.
 .001 .. 30/-
 .0005 .. 25/6
 .00025 .. 23/6

EDISON BELL.

.0001 to .0005 Fixed 1/3
 .002 to .009 .. 2/-
 .001 .. 1/3
 .0002 with Grid Leak 2/6
 Variometer .. 10/6
 Twin Detector .. 5/-

POST 2d. each.

WEST END DEPOT FOR

POLAR; JACKSON
 BROS.; R.I.; BURN-
 DEPT.; GOSWELL
 ENG. CO.; SILVER-
 TOWN; IGRANIC;
 LISSEN; RADIO
 PRESS ENVELOPES;
 DUBILIER; EDISON
 BELL; ETC.

POST FREE OFFER.

POST PAGE No. 1. Not Applicable to Foreign Orders.

DELIVERY. Every endeavour is made to despatch goods by return, but sometimes delays occur which are beyond our control and in which cases customers may rest assured that their orders will be executed in the very shortest period. They will therefore realise that it is not possible to have orders cancelled through above causes. All orders over 20/- post free U.F.P.V.

RHEOSTATS.

Ormond .. 2/-
 Raymond .. 1/6
 Do. with dial .. 2/-
 Extra value do. .. 2/6
 T.C.B. 6 ohms .. 4/-
 Potentiometer T.C.B. .. 5/-
 Burndept Dual .. 7/6

POST 3d. each.

TRANSFORMERS (L.F.).

Radio Instruments .. 25/-
 Igranic, Shrouded .. 21/-
 Powquip, Shrouded .. 18/-
 Formo, Shrouded .. 18/-
 General Radio 83 .. 14/11
 Brunet, Shrouded .. 13/6
 Formo, Open .. 12/8
 Powquip, 2-1 or 4-1 .. 14/6
 Raymond .. 10/-
 Eureka Concert Grand .. 30/-
 Ditto, 2nd Stage .. 22/6
 Silvertown .. 21/-

TRANSFORMERS (H.F.).

McMichael, 300/600 .. 7/-
 Ditto 1100/2000 .. 7/-
 Energo, 250/700 .. 3/11
 Ditto 900/2000 .. 4/6
 Raymond, 300/600 .. 2/9
 Others Stocked.

H.T.C. POST 2d.

Special valve holder above panel .. 1/6
 Ditto, for under panel .. 1/6

POLAR POST 6d.

.001 var. Condenser .. 10/6
 .0003 " " .. 10/6
 .0003 " " .. 10/6
 Micrometer Condenser .. 5/6
 Cam Vernier 2-way .. 7/-
 Coil Holder .. 11/-

GRID LEAK.

Dublier 2/6
 McMichael 1/6
 Edison Bell 1/6
 POST FREE


WATMEL

Var. Grid Leak .. 2/6
 Anode Resistance .. 3/6

BRETWOOD (New Model)

Var. Grid Leak .. 3/-
 Anode Resistance .. 3/2

POST 2d. EACH.

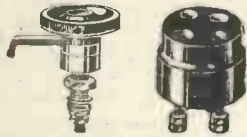

This first-class Switch Arm, with 12 Studs, 12 Nuts, 12 Washers. By Post 1/6 set.
 Ebonite Valve Holder, set from solid rod, hand-turned, 8 nuts and washers. Each. 1/8.

"POWQUIP" L.F. TRANSFORMERS.

POST FREE
 BUCKS. (for Reflex etc.) - 12/6
 MANCHESTER (similar to R.I.) 14/11
 STANDARD - 14/11
 SEROUDED - 18/-

COIL PLUGS.

Single Coil Holder mounted on ebonite base and fitted with terminals .. 1/4
 Ditto, swivel movement .. 1/8
 Post Free.

CRYSTAL Post DETECTORS 4d. each



Enclosed glass. As Sketch. Ebonite Base.

Brass .. 1/-, 1/4, 1/8, 2/-
 Nickel .. 1/6, 2/-
 Ebonite .. 1/8
 Perikon .. 2/3

(With Zincite and Bornite.)

NOTE!

OUR WONDERFUL MICRO-METER ADJUSTMENT GLASS-ENCLOSED DETECTOR. WHY PAY MORE? POST 6d. each. 1/11

"BABY" COIL STANDS (EBONITE)

GRAND VALVE
 2-Way, 2/6; by Post, 8/-
 3-Way, 4/3; by Post, 4/9
 Brass Fittings, Knob Type, on Base.

WATES MICROSTAT

FOR D.E. or R. 2/9
 VALVES .. 2/9
 Post Free.



"ORMOND" L.F. TRANSFORMER

Post Free.

RHEOSTAT (Ebonite Former)

EUREKA WIRE, KNOB, AND DIAL 1/11
 By Post, 2/3



EDISON BELL Shaped Plug


1/- By Post, 1/3
 Also with Base, 1/3
 By Post 1/6

FINE VARIOMETERS

DOUBLE SILK WOUND, Close Coupling, One Hole Fixing, 4/11 and 5/11
 Post 6d. each.

EBONITE—

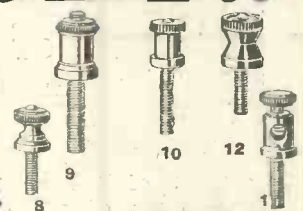4/11 and 5/11
 Post 6d. each.
DUPLIX WAXLESS BASKET COILS
 Min. Self-Capacity Set of 5 1/8
 By Post 2/- Set



TERMINALS

WITH NUT & WASHER
 No. 8 per dozen 1/-
 No. 9 " 1/3
 No. 10 " 1/1
 No. 12 " 1/3
 No. 13 " 1/1
 POST FREE
 All 4 B.A.

"BUCKS" for Reflex 12/6

EBONITE
 2 for 1/2
 2 for 1/4
 2 for 1/8
 3 Qualities.

BASKET HOLDERS

2 for 2/-
 2 for 2/8
 2 Qualities.

FORMO SHROUDED

18/-

RAYMOND FORMO

10/-
 By post 10/6
 12/6
 Post Free.

ONE HOLE FIXING

1/3
 By Post 1/6

PARTS FOR 2-VALVE "UNIDYNE" RECEIVING SET

THE 4-ELECTRODE VALVE
 Thorpe K4 .. each 17/6
 6 Terminals .. for 10d.
 2 Microstat Filament Resistances each 2/9
 1 Variable Grid Leak 2/6
 1 Single-Pole Double-Throw Switch 1/9 or 2/-
 1 .0005 Variable Condenser, with Vernier 7/3
 1 Cam Vernier 2-way Coil Holder .. 9/-
 Panel 5 1/2 in. by 1 1/2 in. by 1 in., drilled to hold 2 5-Pin Valve Holders for 2/-
 2 5-Pin Valve Holders .. each 1/6
 1 Fixed Condenser, .001 .. 1/2, 2/2 3/-
 1 Fixed Condenser, .0002 1/2, 2/2 3/-
 1 Shrouded L.F. Transformer 20/-
 8 yds. No. 18 Gauge Tinned Copper Wire .. 1/2
 Necessary Screws, Nuts, and Washers, Free if above lot purchased. Post extra.

BATTERIES (H.T.) EVER-READY

60v. - 13/6
 180v. - 22/6
 POST FREE

FIBRE STRIP FOR COILS

3 FEET Lengths
 1 inch wide.
 12 feet 1/-
 Post Free.

GOSWELL ENGINEERING

Patent Valve Holder 1/6
 2-Way Cam Vernier Coil Stand 9/-
 1-Way Cam Vernier Coil Stand 12/6
 2-Way Ordinary 7/6
 ALL POST FREE.

HOURS OF BUSINESS:
 DAILY - 9 to 7.45
 SUNDAY - 10 to 1
 Phone GERRARD 4637

K. RAYMOND
 27, LISLE STREET,
 LEICESTER SQUARE, W.C.2

No responsibility accepted on post orders unless cheques and postal orders are crossed and made payable to the firm. Moneys sent must be registered.

RIGHT OPPOSITE
DALY'S
 GALLERY DOOR

TWO PAGES MORE OVERLEAF

ALL OUR CONDENSERS HAVE BEEN TESTED AND RECOMMENDED BY LEADING JOURNALS UNSOLICITED.

BRITISH MADE SPECIALLY ADAPTED FOR

ALL LEADING CIRCUITS

NEW MODEL

WITH VERNIER		WITHOUT VERNIER	
.001	9/3	.001	6/6
.0005	7/3	.0005	5/3
.0003	6/9	.0003	4/11
With EBONITE DIAL and Two Knobs. Post 6d. Set.		.0002	4/6
		Vernier, .00005	3/9



SQUARE LAW

.0005	7/11
.0003	7/6
With Vernier.	
.0005	13/11
.0003	9/11

Post 6d. Knob & Dial included.

RAYMOND VARIABLE CONDENSERS

Exclusive Design. Stout Vanes. Extra Insulation. Very Compact. Narrowest Spaces (Pressed Aluminium). Centre Rod cannot bend. Terminal Connections Wonderful for Portables. Capacity Guaranteed. Perfect Efficiency. Handsome Design. Takes up very little space in panel. Nickelled Fittings. Beautifully Made. New one-hole fixing method.

COSTS A TRIFLE MORE, A Few Pence Only, and is Just what You Want.

NICE DIAL and KNOB included.



'DE LUXE' MODEL

AS SHOWN, WITH DIAL KNOB AND BUSH.

.001	7/3
.0005	5/11
.0003	5/4
.0002	4/11

POST 6d. SET.

John Blair, Esq.
Rexall Pharmacy
says:— Millom.
Your Condensers are a REVELATION to me as a Dealer. Sept., 1924.

C. Walton, Esq., Andover.
Tested your Condensers on Meiger and got "EXCELLENT"

9/- TWIN CONDENSER POST FREE.



Composed of two equal units of .0005 or .0003 m.f., operated by one Knob and Dial, thereby enabling you to tune two circuits by one turn of the Dial. Can be used in series or parallel. Complete as shown with aluminium ends. Knob and dial. For Tuned Anode Circuits.

MANSBRIDGE FIXED CONDENSERS

1 M.F.	4/6	Various others Stocked.
2 M.F.	5/-	
2 1/2 M.F.	4/-	
3 M.F.	4/6	

Delivery very slow from makers.

"RAYMOND" FIXED CONDENSERS.

Ebonite Base. .001, .0001 to	
.0005	1/2
.002 to .004	1/3
.006	1/6
.01 and .02	1/9
.05	3/3

POST FREE.

W Kennard, Sig. Telegraphist, H.M.S. Leamington. 2nd July, 1924. The Condensers are splendid, and superior to any I have ever seen. Please find repeat order. W. Hale, Esq., 3, Gaye St., Walsall. 30th April, 1924. The last 4 Condensers gave every possible satisfaction—highest quality at extremely low prices. Kindly despatch enclosed further order. E. Shepherd, Esq., 23, Warden Street, Dunedin, 12th May, 1924. Everything came to hand in splendid condition, the quality far exceeding my expectations.

The set used by **Miss Evelyn Laye** in her dressing-room at Daly's is made of Raymond parts.

LOUD SPEAKERS

30/-	STERLING "DINKIE"
25/-	DRAGON FLY AMPLIFIER (Baby New Model.)
55/-	BABY STERLING (Brown Floral.)

ALL MODELS OBTAINABLE.

VARIOMETERS

RAYMOND 8/11



Post 3d. each

FALLON IGRANIC OR EDISON-SELL

Post free 10/-

ENERGO

H.F. Plug-in Transformers	
Post, 2d. each.	
No. 1. 150-450	3/6
No. 2. 250-700	3/11
No. 3. 450-1200	4/3
No. 4. 900-2000	4/6
No. 5. 1800-3000	4/9
No. 6. 2200-5000	4/11

BRUNET (genuine)

4000 ohm Double	18/6
4000 ohm Single	8/3
2000 ohm Single	7/6

POST FREE.

From **S. H. COULTER, Esq.,** 55, Court Road, Barry Dock.

30/9/24. Condenser to hand this a.m. No wonder you are snowed under with orders! IT IS AN EXCELLENT COMPONENT. Please find repeat order.

JACKSON BROS. "J.B." VARIABLE CONDENSERS

	Standard	Super.	Microdenser
.001	5/8	9/6	11/6
.00075	5/-	9/-	11/-
.005	7/-	8/-	10/-
.0003	5/9	6/9	8/9
.00025	5/9	6/9	8/9
.0002	5/-	5/8	8/-
.0001	4/9	5/3	7/9
Vernier	4/-	4/6	

Post 3d. s.t.

SQUARE LAW SHORTLY.

HIGH GRADE EBONITE

POST PRICES	3/16 in.	1 in.
6 x 6	1/6	2/-
7 x 5	1/6	2/-
8 x 6	2/-	3/3
9 x 6	2/2	3/3
10 x 8	3/-	4/2
12 x 6	3/3	4/2
12 x 9	4/3	5/8
12 x 12	5/6	7/8
14 x 10	5/3	7/8

Cut to Size, 3/16 in. at 1d. square inch. Post 3d. Foreign Post extra.

CALLERS' PRICES ELSEWHERE.

D.C.C. WIRE POST PRICES

16 D.C.C. 1/2 lb.	2/6	20 D.C.C. 1/2 lb.	1/3
18 " 1/2 lb.	3/6	22 " 1/2 lb.	1/4
18 " 1/2 lb.	2/3	24 " 1/2 lb.	1/6
18 " 1/2 lb.	3/9	26 " 1/2 lb.	1/8
		23 D.C.C. 1/2 lb.	1/10

CALLERS' PRICES ELSEWHERE

FRENCH THOMSON-HOUSTON

4000 ohm Phones
100 pairs at 12/11
POST 6d.

SUNDRIES

Post free

Screw Spade Terminals	doz.	1/-
Pin Screw Terminals	doz.	10d.
Spade Tags	doz.	5d.
Empire Tape, 1/2 in.	12 yds	8d.
Insulating Sleeving	6 yds.	2/-
Ebonite Knobs, 1 1/2 in. 2 B.A.	6d.	
Moulded Knobs 1 1/2 in.	2 for	8d.
Ditto 1 in. 2 B.A.	2 for	8d.
Ebonite ex-handles 6 in.	9d.	
D.C.C., I.R.C. Bell Wire 10 yds.	1/-	
Double 'Phone Cords, 72 in.	1/11	
Porcelain S.P.D.T. Switch	1/11	
Ditto D.P.D.T. Switch	2/6	
Battery Clips	doz.	10d.
Ebonite Valve Holders	1/3 and 1/-	
Lead-in Wire 4 M/M.	10 yds.	2/6
Lead-in Wire	10 yds.	1/6
Twin Flex	12 yds.	1/11
100 ft. 7/22 Aerial Wire with four insulators	3/6	
Engraving Titles or Scales	8d.	
"R.I." Choke Coil	10/-	
Nickel Panel Switches, D.P.D.T.	1/5	
Ditto, S.P.D.T.	1/2	
Insulating Sleeving 3 yds.	1/4	
Tinned copper sq., 16 gauge, 15ft.	1/-	
Spearpoint Whisker, gold	4d.	
Gold Whisker	4d.	
Set of 5 (one gold)	6d.	
Variometer (250/650)	3/3 and 2/6	
Ditto Ebonite	4/11	
Ditto Ball Rotor	6/11	
Burndep Detector	5/8	
Screw Wander Plugs	pair	6d.
Skinderviken Button, Alumin.	5/-	
Seven Twist Drums (H.S.)	1/11	
Taps 0, 2, 4, 6 B.A.	set	2/-
Sorbo Ear Pads	pair	1/9
Neutron Crystal	1/6	
Blue Tungstaitite	1/8	
Geosite (G.E.C.)	1/3	
Tumbler Switches (Ebonite)	1/9	
Valve Sockets, Plain (nut and washer)	doz.	1/-
Sets of Spanners	2/-	

RIGHT OPPOSITE
DALY'S
GALLERY DOOR

Phone: GERRARD 4637.

K. RAYMOND

27, LISLE STREET, LEICESTER SQUARE, W.C.2

No responsibility accepted on post orders unless cheques and postal orders are crossed and made payable to the firm. Moneys sent must be registered

HOURS OF BUSINESS:
DAILY . 9 to 7.45
SUNDAY . 10 to 1

POST PAGES CONTINUED

SEE OVERLEAF EXTRA POSTAGE ON FOREIGN ORDERS. SEE OVERLEAF

The CREAM of the WORLD'S HEADPHONES

4,000 ohms.
STERLING 4,000 ohms
NEW MODEL .. 25/-
BROWN'S (Featherweight) 25/-
B.T.H. (Wonderful Tone) .. 25/-
BRANDES (Matched Tone) 25/-
GENERAL RADIO .. 20/-

TELEFUNKEN 4,000 ohms HEADPHONES
 As light as a Feather .. 17/11

Dr. NESPER HEADPHONES

Genuine Nesperphone, 4,000 ohms. Fitted with adjustable diaphragm, detachable receivers, double leather-covered head-springs, long flexible cords, nickel-plated parts. Very comfortably fitting to the head.
LOOK FOR THE TRADE MARK.
 4,000 ohms .. 12/6
 Post 6d. pair.

GENUINE "N & K" HEADPHONES

Guard against inferior imitations which are "cleverly" got up to deceive. Make sure of the genuine article, the original "N & K," and avoid dissatisfaction. See that the letters "N & K"—and no other—are stamped, 4,000 ohms .. 12/11
 6,000 ohms .. 13/3
 Post 6d. pair.

BEWARE OF "PATTERN" OFFERED (HEAPLY)

ACCUMULATORS

MADE BY WELL-KNOWN FIRM FOR ME.

2 v. 40 amps. 9/6. By post 10/6
 4 v. 40 amps. 16/6. By post 17/6
 4 v. 80 amps. 19/6. By post 20/6
 4 v. 80 amps. 23/6. By post 24/6
 6 v. 60 amps. 27/6. By post 29/-
 6 v. 80 amps. 33/- . By post 34/6
 6 v. 105 amps. 38/6. By post 40/6

UNIVERSAL (FRANCO)

Basket Coil Stand, 2-way

POST FREE 5/9

FRANCO, 2-way (plug-in) .. 12/6
 Ditto 3-way .. 17/6
 The only GEARED COILHOLDER on the market.

CHELMSFORD (5 X X)

D.C.C. Basket, Coil, complete with adapter, specially made to use with 650 variometer, 2/6. By post 2/9
 LOADING PLUG and Socket .. 9d.
 D.C.C. COIL for 5 X X, 1/6. By post 1/9

BRASS FORMER TO MAKE YOUR OWN COILS

DOUBLE, 23 spokes each side.
 POST FREE 3/11

POST PRICE TINNED COPPER

18 Round 1/2 lb. .. 2/6
 20 Round, 1/2 lb. .. 2/6
 16 Square, 12 ft. .. 10d.
 18 Square, 12 ft. .. 9d.

GUIDE FOR CHELMSFORD

On 1,600 Metres

Aerial Reaction
 Coil No. 150 200
 Tuned Anode 250 or 300

"SUCCESS" L.F. TRANSFORMER

21/-

"MURRAY"

(Prov. Pat.)

VALVE HOLDERS

High finish. Absolutely Safe. Low Capacity.

EASILY FIXED.

Exceptionally neat appearance
 1/3 POST FREE.

RADIO PRESS TRANSFERS 6d.

By Post 8d.

POST PRICES
VARIOMETER 250/600
 2/6

Ditto with fixing clips
 3/-

EBONITE BALL ROTOR
 6/11

ALL KINDS STOCKED
 at 2/11 3/6 3/9 4/- 4/6

Leave the selection to me and you won't be disappointed

VALVES

Cossor P.1 and P.2 12/6
 Mullard L.F. & H.F. 12/6
 Mullard D. ra 21/-
 B.T.H. R.4 - - - 12/3
 B.T.H. P.5 '06 - - 25/-
 Idiswan A.R. - - 12/6
 Ediswan A.R.D.E. 21/-
 Ediswan A.R. '06 25/-
 Marconi R. and R.5 12/6
 Marconi D.E.R. - 21 -
 Marconi D.E.3 - 25/-

POST FREE

French "R" - - 6/11
 Phillips "R" - - 7/6
 French '06 - - 15/11

Post 6d. each

ALL VALVES ON POST SENT AT PURCHASER'S RISK.

MYERS VALVES

UNIVERSAL DULL EMITTER

12/6 21/-

POST FREE

PHILLIPS D.E. VALVES

'04 Type 1.5 to 1.8
 each 17/6
 Post 6d. each.

THORPE K4 VALVES

(6-pin) for UNIDYNE 17/6

THORPE K 1 10/-

POST FREE

5-Pin Valve-holder - - 1/6

"OOJAH" GRAPHITE

Pile Rheostat for D.E. or R Valves .. 4/-

N. & K. LOUD SPEAKER

A LITTLE GEM

21/-
 POST 1/-

RADIO PRESS ENVELOPES

No. 1 at 1/6
 2, 3, 4 at 2/6

COIL STANDS

Ebonite 2-way with Extension Handles
 Nickel Fittings

3/3

By Post 3/9

Ditto 3-way
 4/9

By Post 5/3

CAM-VERNIER

(2-way)

POST FREE 7/6

POLAR (2-way)

11/-

GOSWELL

(see elsewhere)



"R.I."

NEW MODEL

IN SEALED BOX

Don't Buy Otherwise

Post 25/- Free

NEW LISSEN LINES

5 Point Switch - 4/-

Auxiliary Res. - - 1/3

Lissen Choke - 10/-

Post Free

RIGHT OPPOSITE
DALY'S
 GALLERY DOOR

'Phone: GERRARD 4637.

K. RAYMOND

27, LISLE STREET,
 LEICESTER SQUARE, W.C.2

No responsibility accepted on post orders unless cheques and postal orders are crossed and made payable to the firm. Moneys sent must be registered.

HOURS
 OF BUSINESS:
 DAILY . 9 to 7.45
 SUNDAY . 10 to 1

THIS PAGE IS FOR CALLERS ONLY

ALL POST ORDERS FROM THE OTHER THREE PAGES

OPEN
WEEKDAYS
9 to 7.45
SUNDAYS
10 to 1

Prices subject to alteration without notice. Every endeavour made to keep large stocks; but am not responsible for manufacturers' non-deliveries.

NO POST ORDERS FROM THIS PAGE.

SWITCHES

- Porcelain D.P.D.T. . . 1/7d
- Porcelain S.P.D.T. . . 1/8
- Ebonite D.P.D.T. . . 1/8
- Ebonite S.P.D.T. . . 1/8
- Min. Panel D.P.D.T. . . 1/-
- Min. Panel S.P.D.T. . . 10½d.

BATTERIES 4-5

- Vulco English 4-5 . . 4d.

H.T. BATTERIES.

- Best Made 30 v. . . 4/6
- Best Made 60 v. . . 7/6
- Best Made 88 v. . . 9/-
- Ever-ready 66 v. . . 13/6
- Ever-ready 108 v. . . 22/6
- Siemens "Q 2, L 5" . . 3/-
- Ever-ready ditto . . 1/9
- B.B.C. 8 volts . . 3/-
- B.B.C. 60 volts . . 9/6
- B.B.C. 36 volts . . 5/6
- B.B.C. 16 volts . . 2/6

RHEOSTATS.

- Small 5 ohms . . 1/3
- One Hole Fixing . . 1/3
- Ormond . . 1/9
- Ebonite Former . . 1/6
- Ditto and Dial . . 1/10
- Igranite, T.G.B., and all known makes.

CRYSTAL

DETECTORS, &c.

- Enclosed Brass, Large 1/3
- Ditto, Nickel or Brass, Large . . 1/6
- Small Brass . . 9½d.
- Ebonite, Enclosed . . 1/-
- Mic. Met-Type . . 2/8
- Barndept . . 5/-
- Easi-Fix Cups 1d. & 1½d.
- Gold Spearpoint . . 3d.
- Neutron Crystal . . 1/6
- Hertzite (Shaw's) 8d. & 1/-
- Midite . . 6d.

VALVES.

- Dutch Detector . . 4/9
- Dutch "R" . . 5/-
- Phillips "R" . . 7/6
- French "Metal" . . 6/11

TOOLS.

- Set of Spanners . . 1/4
- Tags, 0, 2, 4, 6 B.A. set 2/-
- Small Soldering Irons 8½d.
- 7-Twist (H.S.) Drills . . 1/4

MURRAY VALVE HOLDER (Patent) 1/3

- Legless Valve Holder, Solid Ebonite . . 1/-

EBONITE PARTS.

- Good Coil Plugs from 4½d.
- Edison Bell Shaped . . 1/-
- Raymond ditto . . 10½d.
- Basket Adapters . . 8½d.
- Also at 1/- & 1/3
- 2-way Coil Stands . . 2/6
- With Extens. Handle 2/11
- Also at 3/0, 4/-, 4/6
- 3-way . . 4/3, 4/6, 5/-
- Goswell Cam Vernier 9/-
- Franco " " . . 12/6
- Polar " " . . 11/-
- Coil Plug on Stand . . 1/-
- Ditto, Swivel Movement 1/3
- Coil Plug and Clips . . 8½d.

BRASS PARTS.

- W.O. or Pillar Terminals 1d.
- Small Pillar . . 4 for 3½d.
- 'Phone 4 B.A. . . 1d.
- 'Phone 2 B.A., 2 for . . 2½d.
- Valve Sockets 4 for 3d.
- (Above with Nut Washer)
- Valve Pins and Nuts, 2 a 1d.
- Stop Pins and Nuts 2 a 1d.
- Plug and Socket pr. 1d.
- Spring Washers 4 a 1d.
- Spade Screws . . 1d
- Pin Screws . . 2 for 1½d.
- Spade Tags . . 5 a 1d
- Spring Pillar Terminals 2½d.
- Nuts, 2, 4, 5, 6 B.A. doz. 2d.
- Washers (Brass) 12 a 1d.

VARIOMETERS.

- Impregnated Board, Wound D.C.C. and Clips, 200/600 metres 2/6
- Very Good Value, Wound D.C.C. and Knob . . 1/6
- Ebonite D.S. Wound, with Ball Rotor and Knob, 200/700 metres 5/11
- Ebonite, 200/600 . . 3/11
- Raymond Inside Wind- ing . . 8/11

BOXES

- 7 x 5 9 x 6 12 x 9
- 3 x 6 10 x 8 12 x 12

16g D.C.C.

USUALLY IN STOCK.

FIBRE STRIP (For Coils)

- 3ft. long, 1 in. wide.
- 2½d. per length.

BREAST DRILLS

- 0 to ½ chuck
- Cut Bev. 1 a d Gear
- 5/9

SUNDRIES.

- 'Phone Cords (6 feet) 1/5
- Nugraving . . 7½d.
- Similar Sets (Titles or Scales) . . 3d.
- Good Knobs . . 1½d.
- Small Knobs, 2014 B.A. 2d.
- Studs, Nuts and Washers doz. 4½d.
- Switch Arms 8d. to 1/-
- Copper Foil . . ft. 2½d.
- 18g. Sq. Tin Copper 15 ft. 5d.
- 16g. Sq. Tin Copper 12 feet 5d.
- Round Tin Copper, various Sizes.
- Insulated Staples 5 a 1d.
- Insulated Hooks 4 for 3d.
- Rubber Lead in, 30 feet 1/3
- 7/22 Copper Aerial, 100 ft. 1/10
- Extra Heavy Aerial 100 ft. 2/- & 2/3
- Good Valve Holders 8d.
- H.T.C. in Stock 1/8, 1/9
- H.F. Transformers, 300/600 . . 2/9
- Empire Tape, ½ in., 2 yds. . . 1d.
- Ditto, ½ in., 2 yds. 1½d.
- 8 in. Ebonite Anticape Handles . . 8d.
- Battery Clips 2 a 1d.
- Skinderviken Buttons (Aluminium) 4/6
- Connecticut Switches 1/4
- 1,000 ohm Bobbins . . 1/3
- 2,000 ohm Bobbins . . 1/8
- Sorbo Rubber Ear Caps pr. 1/4
- Adhesive Tape Roll . . 2½d.
- Basket Coils . . 1/-
- Waxless ST100 (2) . . 1/-
- Waxless (5) 200/2,000, set 1/8
- Waxed (6), 200/3,600 set 1/8
- Waxed (7), 150/3,600 1/11
- Chelmsford No. 8 Tachon 1/- 1/6
- Chelmsford, D.C.C. . . 1/3
- 1 Complete with Adapter 2/3 (To use with variometer.)
- Allen var. Gd. Lk. . . 1/3
- Alien Anode Res. . . 1/3
- Scales, 0-180. 2d., 3d., 4d.
- Dial and Knob (Ed. Bell) 1/3
- Dial (Ebonite) . . 10d.
- Brunet Headphones . . 14/6
- Twin Flex . . 4 yds. 6d.
- D.C.C. Bell Wire, 10 yds. 5d. (Indiarubber covered)
- Sleeving . . yd. 4d.
- Wander Plugs pr. 3d.
- Coloured Plugs each 1½d. (All screw pattern)
- Electron Aerial . . 1/3
- Polished Boxes, 8 hv 6 3/8

SUNDRIES.

- Tungstelite . . 1/-
- Microstat . . 2/6
- Tumbler Switches (Ebonite) 1/4
- Fibre Strip (for Coils) 3 feet 2½d.
- D.C.C. Wire, per lb.—
- 13 g. . . 9d. 20 g. . 9d
- 22 g. . . 10d. 24 g. . 1/-
- 28 g. . . 1/1 28 g. . 1/3
- 30 g. . . 1/8 Etc., etc.
- Solder . . per stick 2d.
- 2 Color Flex . . yard 2½d.
- Shellac . . 5d.
- Battery Box . . 4/6 (with clips for 36 v.)
- Nickel Pillar Terminals 2d.
- Nickel Contact Studs 2 for 1½d.
- Nickel Switch Arm . . 1/- (one hole fixing)
- Loading Coil and plug 8d.
- Gamages Permanite . . 1/-
- Condenser Brushes . . 6d.

SHAW'S HERTZITE.

BEATS ALL OTHER "ITES." 1/-

Impossible to Advertise All the Goods Stocked.

'Ware Imitations.

N and K

4,000 ohms . . 12/11

GENUINE STAMPED.

MYERS VALVES.

UNIVERSAL D.E. 12/6 21/-

- Strong Valve Template 4d.
- Egg Insulators . . 1d.
- Reel ditto . . 1d.
- Thick Rubber Lead-in per vd. 2d., 3d.
- Ribbon Aerials 100 ft. 1/10
- Panels Drilled
- Radio Press Envelopes.
- Raymond Fixed Condensers '001, '0001 to '0005, 10d.
- '002, '003, '004 . . 1/-
- '006 1/3; '01 1/9; '02 1/9
- Polar Micrometer . . 5/6
- Condenser . . 5/6

PHILLIPS

4 ELECTRODE VALVE 12/6

DUTCH '06

VALVES 12/6

NO POST ORDERS.

BEST SWITCH ARM.

- 12 Studs . . 1 1/2 lb. 10½d.
- 12 Nuts.
- 12 Washers.

CRYSTAL CALLERS

DETECTOR, only.

Glass enclosed. Micrometer adjustment. 1/9

BRASS FORMER

'DOUBLE' 23 spokes 2/11 each side.

Make your own coil—CALLER'S PRICE ONLY.

RAYMOND CRYSTAL SETS

7/11, 9/11, 12/11

EBONITE

STOCK SIZES

6 x 6	1/4
7 x 5	1/4
8 x 6	1-10
9 x 6	2/-
10 x 8	3/-
12 x 6	3/-
12 x 9	4/3
12 x 12	5/6
14 x 10	5/6

CUT TO SIZE ½d. sq. i. WE STOCK ½ in. EBONITE.

"POPULAR WIRELESS."

FREE TO CALLERS. (Limited number, of course.)

DR. NESPER

(SEE TRADE MARK)

4,000 OHM PHONES

12/6

(NOT DR. "ANYTHING!")

BASKET COILS

- Duplex Waxless (5) . . 1/8
- 1,200/2,000 metres
- Waxless Set of 5 . . 1/11
- 25, 35, 50, 75, 100.
- D.C.C. Chelmsford 1/- 1/3
- Enamelled Do. 1/- 1/2
- Waxed (6) . . 1/8
- 200/3,600
- Ditto (7) . . 1/10
- 150/3,600
- Waxless (2) ST100 . . 1/-
- Ditto (2) Unidyne . . 1/- (For Broadcasting only)
- D.C.C. Coil for Chelmsford, complete with adapter 2/3 (to use with 650 variometer)

RIGHT OPPOSITE
DALY'S
GALLERY DOOR

K. RAYMOND

27, LISLE STREET, LEICESTER SQUARE, W.C.2

No responsibility accepted on post orders unless cheques and postal orders are crossed and made payable to the firm. Moneys sent must be registered.

HOURS
OF BUSINESS:
DAILY . . 9 to 7.45
SUNDAY . . 10 to 1



How it Works.

1.—THE RHEOSTAT.

Every beginner should make a point of understanding the purpose of the components in his set. This article clearly explains the why and wherefore of the filament resistance.

ONE of the most important laws in electricity and wireless is that known as Ohm's Law, which tells us that the amount of current flowing in any circuit is governed directly by the voltage applied and by the resistance encountered. We can find the current passing in a circuit by dividing the voltage applied by the resistance of the circuit. In other words, amperes equal volts divided by ohms.

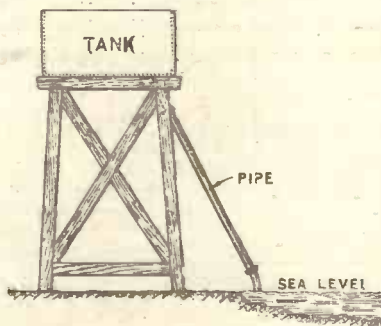


Fig. 1.—The water in the tank flows to the sea because of the pressure.

It will perhaps make an explanation of the working of the rheostat more simple if at the moment we regard the voltage at the positive terminal of the battery as a pressure equivalent to the head of water in a raised tank. Water raised to any height, as in Fig. 1, exerts a downward pressure since its natural tendency is to flow to sea-level. The water in the tank then has a head or potential which falls to zero when it reaches sea-level. Actually electricity flows, as we know now, not from the positive terminal to the negative, but in the reverse direction; but as all the old laws were founded on the assumption that the positive

terminal was the point of highest pressure, it is convenient to retain this idea whilst thinking of electrical pressure. Fig. 2 is the electrical equivalent of Fig. 1. Here the pressure at the positive terminal is six volts, whilst at the negative it is zero. There is thus a voltage drop of six volts round the circuit. It does not matter whether a resistance in the circuit is in millions of ohms or only a tiny fraction of an ohm, the voltage drop will still be the same between positive and negative terminals.

Two Resistances

Now suppose we place in the circuit two resistances of equal value in series as R_1, R_2 in Fig. 3, using for our connections wire of such stout gauge that its resistance is negligible. Then the total resistance of the circuit is the sum of these two—that is, 12 ohms in all. Between point A and point D the voltage drop is six volts, and we shall find that the voltage drop is equally distributed between the two resistances. The drop across each will be three volts. At point A the potential will be six volts, and at B three volts. At C it will be three volts, and at D zero.



A typical filament rheostat for bright emitters.

But suppose that we have two resistances of unequal value as in Fig. 4. Again the total value is 12 ohms and the voltage drop six volts, but eight-twelfths of the total drop will take place between A and B and four-twelfths between C and D. That is, the drop between A and B will be four volts and that between C and D two volts. If now we make R_1 a fixed resistance and R_2 variable, we can vary the voltage drop between A and B by altering the resistance between C

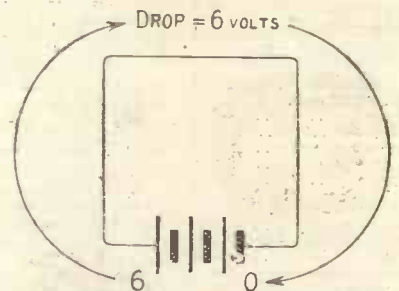


Fig. 2.—A flow of electricity is due to a higher pressure at the positive terminal.

and D. Suppose, for example, we move the slider of R_2 until this resistance has a value of nine ohms, the drop between A and B and between C and D will be three volts. If, however, we give R_2 a value of six ohms, then the total resistance will be 15 ohms and the drop across AB will be $9/15$ ths of six volts, or 3.6 volts. If the maximum value of R_2 is equal to the value of R_1 , we can make the voltage drop between AB anything between three and six volts by adjusting the slider.

Valve Resistance

Now in the valve we have a fixed resistance in the shape of the filament. This is, strictly speaking, not quite a true state-

BROADCAST MESSAGE TO THE TRADE.

THERE ARE MANY SO-CALLED LIGHTWEIGHTS BUT NONE COMPARE IN WEIGHT, QUALITY, AND PRICE WITH THE—

PRICE :

12/6

Trade only Supplied

The HEADQUARTERS OF ALL WIRELESS ACCESSORIES, AND AT THE RIGHT PRICE & QUALITY.

Write for our Illustrated Catalogue, comprising a comprehensive list of all Wireless Accessories.

THE WHOLESALE FITTINGS Co., Ltd.

23, 25 and 27, COMMERCIAL ST., LONDON, E.1.
Phone: London Wall 1191. Telegrams: Calottes, Norton, London.

South London Depot: 65, NEWINGTON BUTTS, LONDON, S.E. 11

Phone: Hop 773.

MANCHESTER: 78-80, High Street.

BRISTOL: 14, North Street, Stokes Croft.




WHY PAY ?

Why spend good money every week to have your accumulators re-charged when you can do them yourself at home, FREE OF ALL COST?

Why suffer the annoyance of being left with accumulators run down and the trouble of carrying them to a charging station, when you can keep them always fully charged and in perfect condition in your own home?

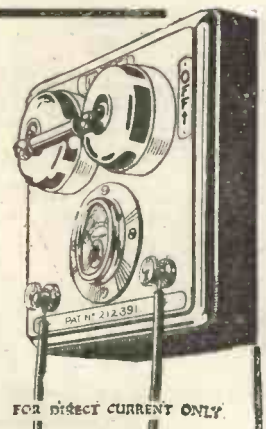If you have a Direct Current supply of electricity of any voltage in your house, either for lighting or heating purposes, all you need to charge your own accumulators at home is the



FOR DIRECT CURRENT ONLY

ULINKIN

PATENT No. 212391.

THE D.C. HOME CHARGER

which charges your batteries automatically whenever you have lights, radiators, electric irons or vacuum cleaners in use in any part of your house, without consuming any extra current, and therefore free of cost.

PRICE **£2 : 2 : 0** CARR. FREE.

Complete with simple instructions

Send 42/- for a ULINKIN To-day, or write for illustrated booklet and fuller particulars.

Trade Enquiries Invited.

The Gran - Goldman Service
(Dept. C.2), 71, Fleet Street, London, E.C.4

See the ULINKIN at the WHITE CITY EXHIBITION STAND No. 53 November 15th to 29th.

AUTOMATIC IN ACTION. Requires no attention. Cannot go wrong.



Type A (above Panel)

This model especially appeals to those who prefer above-panel mounting.



Type C (below panel).

The special advantage of this type is the method of mounting—below panel.

GREAT PARTS SMALL THINGS PLAY

In Radio Receiving sets it is the small things that count. Innocent pieces of apparatus—the valve-holders for instance—are overlooked as having nothing to do with good or bad reception. But you just try a correctly designed valve-holder in place of the very crude socket you are accustomed to use and be convinced that the efficiency of your receiver has been increased more than you can imagine. It is no idle claim to make that no receiver can possibly yield the fullest power, high selectivity, or highest efficiency unless fitted with H.T.C. Valve Holders.

LOW CAPACITY VALVE HOLDERS ESSENTIAL IN H.F. AMPLIFIERS

Little, if any, emphasis can be needed on our part, when so high a technical authority as John Scott-Taggart, F.Inst.P., A.M.I.E.E writes on the Low Capacity Valve Holder: "Quite apart from other merits, the widely-spaced contacts on certain types of special valve holders are particularly suitable for high-frequency work. The ordinary arrangement where the socket pins are very close together, the nuts and washers being frequently only a matter of 1/16 inch apart, are entirely unsuitable for high-frequency OR IN FACT, FOR ANY OTHER WORK."

Type A (above panel)

Template supplied 1/9

Type C (below panel)

Template supplied 1/6

WARNING.

Purchasers of low Capacity Valve Holders are notified to beware of imitations. It is very necessary when buying to look for the name H.T.C. on the template without which no Valve-Holder is the genuine and original H.T.C. It may be taken that colourable imitations—simply because they are imitations—will not cannot give the efficiency which is inherent to the H.T.C.

BRITISH and FOREIGN PATENTS APPLIED FOR.

IF YOUR LOCAL DEALER CANNOT SUPPLY, WRITE DIRECT TO:

H.T.C. ELECTRICAL CO., LTD.


2 and 2a, BOUNDARIES ROAD, BALHAM, S.W.12.

Trade Enquiries Invited

TELEPHONE: Battersea 374

EQUALLY EFFICIENT.

You may buy H.T.C. Transformers with confidence, although the price is low. There is no reason why you should incur greater expense with the hope of securing better results. Extraordinary care expended upon their design, and relentless inspection during their construction and of the materials used preclude any possibility of manufacturing fault. The design of the H.T.C. is such that it operates efficiently in all circuits. They are designed to give power combined with purity 15/- of reproduction. Price Do not be induced to pay more or less. Simply ask for the H.T.C.

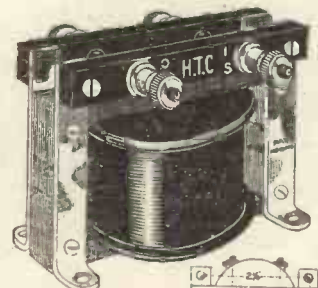


LENGTH - 2 3/4" HEIGHT - 2 1/4"



*“Gold is for the Mistress-Silver for the Maid
Copper for the Craftsman cunning at his trade
Good! said the Baron, sitting in his hall
But Iron-Cold Iron-is master of them all.”*
Rudyard Kipling.

IS IRON YOUR MASTER?

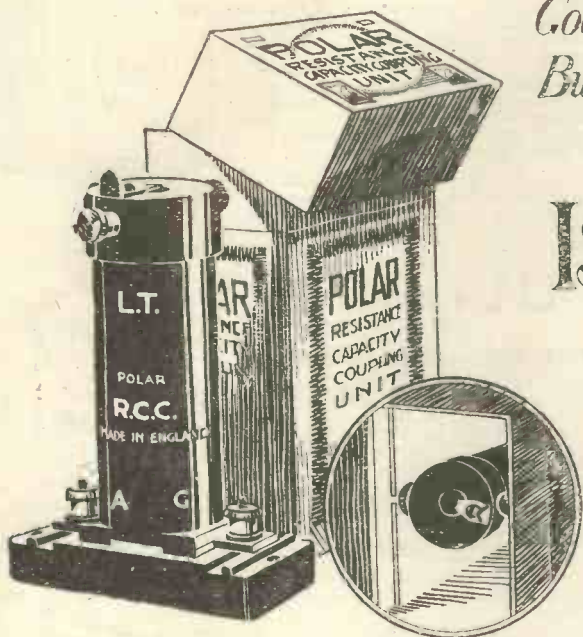

**POLAR
RESISTANCE CAPACITY
COUPLING UNIT
PRICE 15/-**

**ON SALE AT YOUR NEAREST
POLAR STOCKIST**

Distortion of reproduction is invariably present in a wireless receiver incorporating Low Frequency iron-core Transformers. The iron core of the transformers is the chief cause of this, although of course there are contributory distorting factors due to the windings of the transformer. A rapidly increasing number of wireless experimenters and "listeners in" are now seeking purity of reproduction rather than volume of sound.

If you wish to eliminate distortion completely and to obtain pure reception, replace your interval transformers by the POLAR RESISTANCE CAPACITY COUPLING UNIT. This unit consists of an anode resistance, a Dubilier Condenser specially built for the purpose and a grid-leak. It is perfectly self-contained and has four clearly marked terminals corresponding to the four terminals of a transformer. The unit is built by British labour of best British materials throughout and backed by the usual Polar Guarantee. A wiring diagram is included in the 4 pp. explanatory leaflet which is supplied free on request.

In order to obtain the volume of sound equivalent to that given by two first-class transformers three Resistance Capacity Coupling units are required. The comparative cost of the two methods, at first glance, is rather in favour of interval transformer coupling, but considering that the difference is only a few shillings, it is well worth while to spend these few shillings and obtain perfectly distortionless reproduction.

**BEWARE
OF INFERIOR
IMITATIONS.**

Some manufacturers are paying us the usual compliment of imitating Polar products and Polar descriptions. To prevent disappointment see that you get your unit in a box, bearing our trade mark. The box is shown above.

YOU WILL ELIMINATE DISTORTION!



ment, for the resistance of the filament varies to a certain extent with its temperature, but for our purposes, however, we may take it as constant. In the standard bright emitter valve the filament resistance may be taken as six ohms. If the proper working potential is four volts, we shall require to put a resistance of three ohms in series with the filament when a six-volt accumulator is used. This we can do, as shown in Fig. 6, by means of the rheostat. The drop across the filament will then be 6/9ths of six volts, or four volts, whilst that across the rheostat will be 3/9ths of six volts, or two volts. The rheostat thus enables us to adjust the pressure

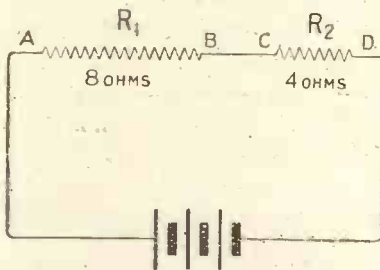


Fig. 4.—Although the resistances are of different values to those in Fig. 3, the potential drop is the same.

exactly until the proper working point is reached.

What would be the effect of using too high a potential? Voltage drives current through a circuit, and the higher the potential we use the greater will the current be. If the current is excessive, the filament will be over-burdened by the load which it is called upon to carry, and though it may not burn out immediately, it will do so long before its time. If the resistance of the filament is six ohms a potential of four volts will, as Ohm's Law shows us, drive 4/6ths of an ampere, or .66 ampere through it. If we increase the potential to five volts the current will be 5/6ths, or .83 ampere, and at six volts a whole ampere passes. The rheostat, then, by regulating the voltage drop across the filament, controls the amount of current passed, and it enables us to make sure that no overloading takes place.

What Resistance ?

The next question about rheostats is: What should the maximum resistance be? This, as we shall see, depends entirely upon the type of valve that is in use and the voltage of the battery employed to heat its filament. With the bright emitter valves which we have been discussing hitherto a


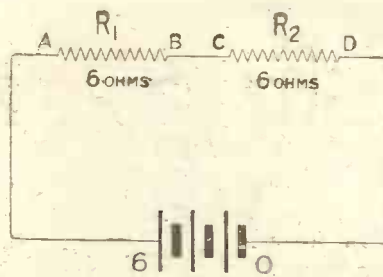


Fig. 3.—The potential drop across the two resistances is 6 volts.

rheostat with a maximum resistance of four ohms will suffice, for this will enable us to cut down the filament potential to 6/10ths of six volts, or 3.6 volts. But with dull emitters things are quite different. Take, for example, a valve rated to work at a potential of one volt and to pass .25 ampere. By applying Ohm's Law we can see that its filament resistance (volts divided by amperes) is 1/.25, or four ohms. If now we were to use such a valve with a six-volt accumulator and a six-ohm rheostat the greatest resistance that we could throw into circuit would be the four ohms of the filament plus the six of the rheostat; that is,

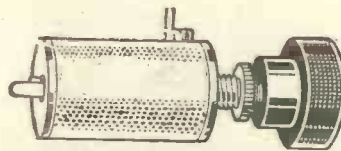

A typical carbon type filament rheostat for bright or dull emitters.

10 ohms in all, and the current passed would be 6/10ths of an ampere, or .6 ampere. This would certainly ruin the valve by destroying the coating of its filament, even if it did not cause an immediate burn out. To find the proper size of the rheostat we

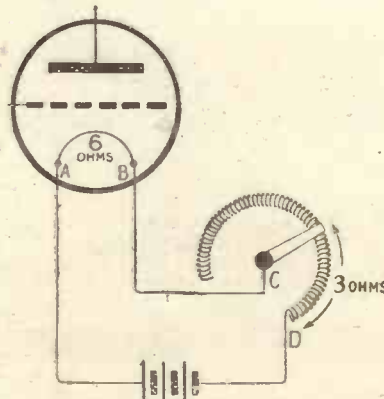


Fig. 6.—Showing how voltage drop across the filament is regulated.

must take the voltage available at the battery terminals and discover the resistance necessary to cut it down to .25 ampere. With a six-volt accumulator the total necessary resistance would be 6/.25, or 24 ohms. The filament provides four of this, so that the rheostat, to be on the safe side, will have to have a resistance of rather more than 20 ohms. With a four-volt accumulator the total resistance needed is 4/.25, or 16 ohms, which indicates a 15-ohm rheostat, and with a two-volt accumulator we require 2/.25, or eight ohms, so

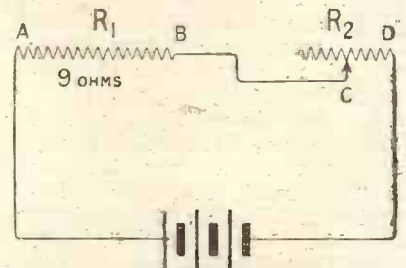


Fig. 5.—For any value of R₂ the potential drop is 6 volts.

that the rheostat should have a resistance of five or six ohms. Working on the same lines, it is easy to discover the amount of added resistance required to cut down the voltage of any low-tension battery to suit a particular dull emitter. The ".06" valves need great care, since their filaments are very easily damaged. Most of them are rated to pass .06 ampere at three volts, hence the filament resistance is 3/.06, or 50 ohms. Simple calculations on the lines indicated will show that with a six-volt accumulator a rheostat must have a resistance of not less than 50 ohms, and that if the battery has an E.M.F. of four volts, the proper value for the rheostat is not less than 20 ohms, and better 30 ohms.

*Are you interested
in Transmitting ?*

"Wireless Weekly"

Publishes many articles
on this phase of Radio.

**6d. Weekly
EVERYWHERE.**





MANY experimenters, constructors and wireless amateurs are now busily engaged in preparing and constructing various sets and pieces of apparatus in anticipation of an interesting and fruitful time during the winter. A new series of articles on "Supersonic Heterodyne Reception in Theory and Practice," by Mr. John Scott-Taggart, F.Inst.P., A.M.I.E.E., appearing in the October 15, 22, 29, etc., issues of *Wireless Weekly*, are of vital interest to the more advanced experimenter. The need for more precise information on such a subject has long been felt in this country, and this series of articles will no doubt open up a wider field, full of interesting possibilities, to a large section of our readers.

Equal attention has been concentrated on the requirements of those who lack such advanced experience, and full details of an efficient single-valve receiver were given by Stanley G. Rattée in the

issue of *Wireless Weekly* of October 15.

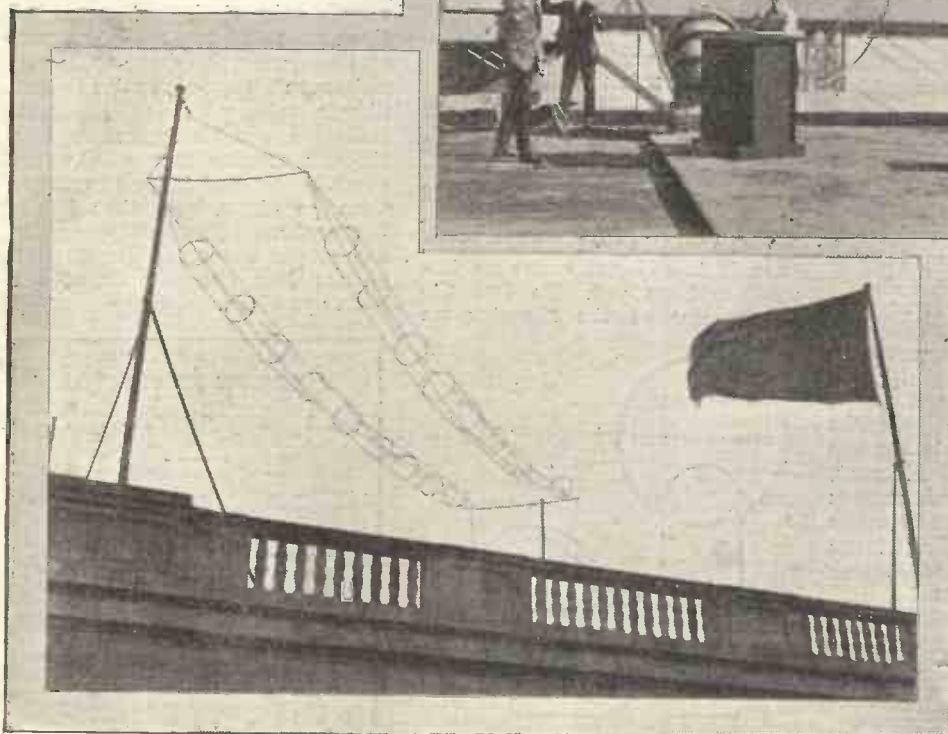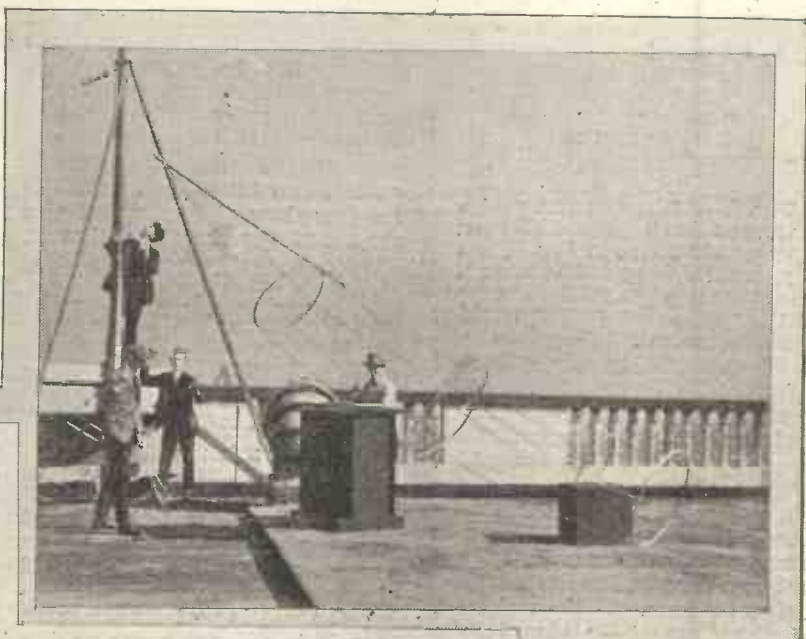The November issue of *Modern Wireless* contains full details for the construction of a Crystal Set for both short and long wavelengths.



This set will appeal to those who desire to receive 5XX without the necessity for external plug-in inductances.

Much interesting and valuable information may be gained by all classes of wireless amateurs, by careful reference to Mr. Percy W. Harris's "Random Technicalities,"

Erecting the Radio Press aerial on Bush House.




SPECIALITIES

The finest results can be only be secured from your set by using the best and nothing but the best British Components. Insist on having "M.H." products.

FILAMENT RESISTANCES

Combined Dull and Bright Emitter Type.

The advantages in this type of resistance are at once apparent. It is the most convenient and economical method of controlling filament current, as the space occupied on the panel is reduced to a minimum, while any valve can be used at an emergency. This rheostat is built up on the same principles as the bright emitter type but it has a double reading on the dial and to safeguard your operation with either type of valve the bright emitter resistance comes into operation first and is added to the dull when the latter comes into operation.

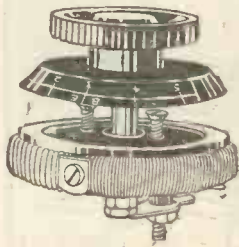

PRICE
7/6

L. F. TRANSFORMERS

—are most efficient.

A high-grade and efficient Transformer of pleasing design for all intervalve purposes, possessing the best possible electrical characteristics. A fixed condenser is nearly always used with an intervalve transformer; provision is made in this model by the clips at the top to take our standard flat type condenser of suitable value.




PRICE
21/-

FILAMENT RESISTANCES

play a most important part in purity and perfection of reception.

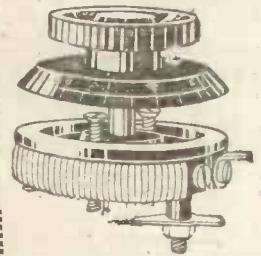The "M.H." Bright Emitter Type are smooth in action, resistance coils are of Eureka wire, the acknowledged best, cleanly engraved dial, finely controlled by milled edged knob, and constructed throughout on the principle that the best and nothing but the best is good enough for satisfactory service.



PRICE
5/6

Certain imitations of our specialities have come to our notice: we therefore expressly advise all customers to insist upon having M.H. products which guarantee efficiency and reliability.

L.M. MICHAEL LTD
IN CONJUNCTION WITH B. HESKETH LTD

WIRELESS ENGINEERS,
Radio Corner, 179, Strand, London, W.C.2.

Barclay, 257

*Put the World
on your Dial.*

Fit MYERS to your receiver and you will enthuse over the ease with which you can then pick up Distant Telephony. Compared to the limited action of your receiver when fitted with ordinary valves, MYERS will truly give you Radio on wings.

In the ordinary valve electrode leads are bunched together in the stem. The success of MYERS in long-distant reception is the outcome of the bringing the grid and anode leads out at opposite ends.

This particular design is confined to the MYERS. The resultant low internal capacity banishes valve distortion, valve noise and hiss. The removal of these paralysing features permits the MYERS to function—perfectly.



Myers
PRACTICALLY UNBREAKABLE
Valves

WIRELESS DEPOTS:—

LONDON—The Dull Emitter Valve Co., 83, Pelham Street, South Kensington, S.W.7 (Kensington 3331).
MANCHESTER—R. Davis & Sons, Wireless Depot, Bilberry St.
LIVERPOOL—Apex Electrical Supply Co., 59, Old Hall Street.
GLASGOW—Milligan's Wireless Co., 50, Sauchiehall Street.
YORKSHIRE—H. Wadsworth Sellers, Standard Buildings, Leeds.
SOUTHERN COUNTIES—D.E.D.A., 4, Tennis Road, Hove.

(Advertisement of Cunningham and Morrison, Windsor House, S.W.1.)

Barclays 273.

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR

**IMPORTANT
NEW
COMPONENTS**

**THE NEUTRODYNE
CONDENSER.**

Mr. Harris's Neutrodyne Circuit demands a Condenser having a minimum capacity practically NIL and a maximum less than the minimum of an ordinary condenser. We have produced an instrument which fills these conditions. Fixing by one screw, with additional 3/8-in. hole for operating spindle. Drilling template supplied. Efficiency guaranteed. Immediate delivery. List No. 168. Price 5/-. Sold only in cartons bearing our name.

ABETTER VALVE WINDOW
For "All-Concert De Luxe" Receiver and others. 1 1/2 in. outside, 1 in. inside diameter. Hand polished, heavily nickel plated, bezel inside and out, complete with Gauge. Each sold in named carton. 9d.



COIL PLUG AND SOCKET.
Designed for panel mounting. Specially useful where single coils are to be mounted separately. Screws and nuts for fixing and fitting connecting wires included. Lacquered finish. Per pair, 9d.



**ANTI-CAPACITY VALVE
HOLDER.**

Made at the suggestion of Mr. P. W. Harris in a form to give increased efficiency, especially on short wavelengths. Fitted to panel without brass nuts, the ebonite base panel being tapped. Lacquered finish, 1/2.



**PLUG-IN H.F. TRANS-
FORMERS.**

Made in all ranges. Each guaranteed in range and to match perfectly every other one in same series. All connections clearly marked. The most efficient H.F. Transformer made. Price, all ranges 7/-.

STUD SWITCH PARTS.

Complete sets of parts to construct Stud Switches with 3/4 in. radius arms. Boxes containing complete Switch Arm with real Ebonite Knob, Bush, Contact Plate, 20 Studs with 2 Nuts to each and 2 Stops, lacquered finish; Drilling Template, enabling purchaser to construct any size switch from 2 to 10 way. Price inclusive, 2/3.

*"I'm setting to work
on the right lines, now"*

Hundreds of wireless workers begin to achieve bigger successes than they had ever thought possible when they start working with Bowyer-Lowe Tested Components. With these trustworthy, guaranteed products the worker knows that every individual portion of his Set is yielding the utmost of which modern science is capable. With Bowyer-Lowe parts you are always on the right lines. Start from the Blue Print—

*with Bowyer-Lowe
Tested Ebonite-*

This Ebonite is Post Office Grade A, guaranteed non-metallic surface and can be used with perfect safety without rubbing down. It is supplied in panels cut exactly to any size, 1/4-in. thick with square edges. Every sheet bears our trade mark on the back, and is sold in a sealed package bearing our label and trade mark, so that our customers are protected against substitution.

A perfect insulating panel is essential in any set. Bowyer-Lowe panels may be accepted without question as being absolutely free from metal and safe for use without preparation. Insist on having them. Order direct from us if your dealer cannot supply.



PRICES OF BOWYER-LOWE TESTED EBONITE.

Semi-Matt Surface, entirely free from Tinfoil, 1/2d. per sq. inch. Hand polished one side and edges, 1d. per sq. inch. Drilled and engraved for any Radio Press Set (except OMNI top panel), hand polished one side, 1 1/2d. per sq. inch.



PF.OV.
PAT.
7213/24

**PRICES OF BOWYER-LOWE SQUARE LAW
CONDENSERS.**

Quotations are for Panel Mounting Type with Dial. Particulars of all types are in our brochure, which is free on application. Write for it to-day.

Standard.	Double.
.0002 M.F. ... 14/-	.00025 M.F. ... 18/-
.00025 M.F. ... 15/-	.0003 M.F. ... 29/-
.0003 M.F. ... 16/-	.0005 M.F. ... 31/-

Drilling templates and calibration charts supplied with all types.

*and Bowyer-Lowe
Tested Square Law
Condensers*

The experimenter who really seeks to make his set as efficient as it can be will use Bowyer-Lowe Square Law Condensers. They are all of guaranteed Maximum capacities. Their minimum capacities are the lowest in wireless. Actual tests by customers show that the e condensers give longer range of reception, greater signal strength and purer tonal quality to every set in which they are used. These illustrated are exactly similar to the set used by Mr. P. W. Harris in the new Neutrodyne Receiver described in the October issue of THE WIRELESS CONSTRUCTOR.

*Capacity Ratio 150 to 1.— Easy to
Calibrate—Big Wavelength Ranges*

These qualities, plus sturdiness of construction, convenience of size (they are no larger than ordinary condensers) and moderation of prices, make Bowyer-Lowe Square Law Condensers unmatched for every tuning purpose of the amateur worker who seeks to obtain the maximum signal strength and range from every one of his sets

**Bowyer-Lowe
Tested Components**

Send postcard asking for particulars of all components in which you are interested. Good dealers stock them. If you cannot obtain locally order direct.

BOWYER-LOWE, Co., Ltd., RADIO WORKS, LETCHWORTH.

which are a distinctive feature of *Wireless Weekly*.

The name of Capt. Round appended to an article is in itself a sufficient guarantee of excellence, and in his articles on "The Design of Resistance-capacity Coupled Low Frequency Amplifiers" in *Wireless Weekly* recently aroused much interest. Those readers who realise the limitations of low-frequency transformer coupling would be well advised to concentrate their attention on these articles.

Efficient high-frequency amplification, combined with stability and ease of control, is the aim of every experimenter requiring satisfactory long-distance reception, and a marked advance in this direction has been provided by Mr. A. D. Cowper, B.Sc., M.Sc., who hands on his information to our readers in an article on "Neutral-Grid Coupling," to be found in the October 29 issue of *Wireless*

Weekly. Practical working details of a 2-valve short-wave broadcast receiver are given in this article.

Mr. Percy W. Harris contributes an article on "A Wavemeter for Amateur Transmitters" in the same issue. This instrument is simple to construct and manipulate,

and information is given regarding the remarkable work of some of our British amateurs in establishing two-way communication with three New Zealand amateurs.

Mr. Percy W. Harris has made a further addition to his long-list of efficient receiving sets, by introducing a new modification of a popular design, which forms the subject matter for a complete article in the November issue of *Modern Wireless*. Those who study efficiency combined with neat and attractive appearance will be interested in this receiver. Long-distance reception will always continue to fascinate a large section of the wireless public, who would be well advised to study the article on a "Long-Range Neutrodyne Receiver," by John Underdown, contained in the same issue.



Mr. John Scott-Taggart, F.Ins.P., A.M.I.E.E., demonstrating his 3-valve dual receiver at Cambridge.

and for those who take advantage of this opportunity to make a reliable wavemeter, it will provide a solution in clearing up the ambiguity which often exists as to the exact value of their wavelength and of that of the station with which they are working.

In this issue some accurate infor-

Multi-Stage H.F. Amplification
A new and highly important

YOUR FIRST VALVE SET

The building of your first valve receiver is a great adventure. But disappointment looms ahead. Low frequency amplification, perhaps for reasons of simplicity, inclines set-builders to ignore the all-important function of L.F. transformers. Inference to the make you incorporate in your first valve set will positively mar your second step into the wonderland of radio.

Months of trial and elimination have alone evolved the SUPER SUCCESS (All Black), an instrument of which we are proud. Experience has shown the need of careful test apart from mere mathematical calculation, and no trouble or expense has been spared to find the "SUPER" METHOD OF DETAIL and CONSTRUCTION.

High impedance, low self-capacity, tested to 1,000 volts between the windings and windings and frame, shrouded to prevent interaction, absolutely damp and dust-proof—fit for a fortnight, but indefinitely—are a few paramount considerations by which the SUPER SUCCESS L.F. Transformer assures your great adventure the success your enthusiasm deserves.

Price **21/-**
Obtainable from all Dealers.



Reg. No. 703507.

Advertisement of Eard & Fitch, Ltd., London, E.C.1.

method of multi-stage high-frequency amplification, known as the T.A.T. system, was introduced in the November issue of *Modern Wireless* by John Scott-Taggart, F.Inst.P., A.M.I.E.E. This will no doubt be of considerable interest to our readers.


A revised and enlarged list of regular programmes from the Continental broadcasting stations, prepared at great trouble, is also to be found in that issue.

Radio Press Envelopes

A further feature of the Radio Press activities is to be found in the Envelopes, four of which are already on sale. When we say that it is not possible to give more detailed information of the construction and manipulation of the set referred to in the Envelope, readers will appreciate the exceptional value of the latter. In fact, we guarantee, that if the set is made up strictly in accordance with the instructions given, perfect results will be obtained.

The Service Department

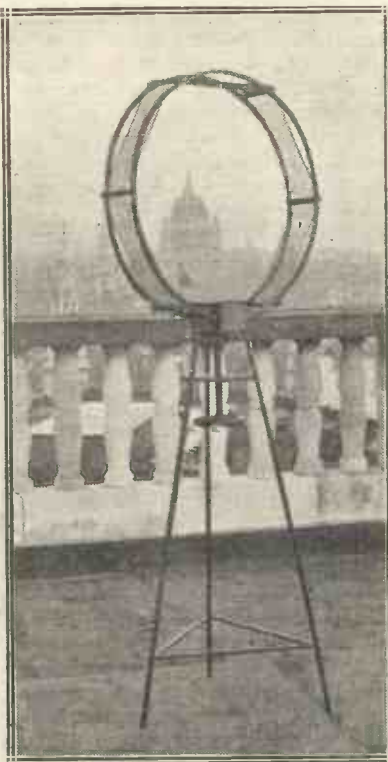Should some slight deviation from the original be made, or some small error or fault introduced with consequent failure of efficient operation, constructors would be



A circular frame aerial of novel design.

advised to consult the Radio Press Service Department, a highly efficient organisation for dealing with defective sets, whose work comprises the thorough examination of sets submitted for test, the location of faults, and the preparation of a complete report on such sets. This work is carried out for a small fee, and constructors have, therefore, a double guarantee that their sets will give good results.

Construction of Sets

A recent innovation of special interest to the set constructor is the Radio Press Panel Card System. Each Panel Card comprises a flat cardboard model of the panel of the set itself, printed upon one side with a photograph of the top of the panel, and upon the other side with a fully detailed drawing of the underside, showing the disposition of the components, and all the wiring, etc. Complete instructions for the building of the set, and a drilling template for the panel are also provided with each Panel Card, No. 1 of which may now be obtained from the usual sources.

Simplex Charts

Yet another aid to the building of a receiver with great ease is furnished by the Simplex Series of

TUNING EFFICIENCY BRINGS RESULTS



Without going into technics to prove our statement, we may say that for the most part bad reception may be tracked to the tuner. Here the weak H.F. currents easily leak away. Bad contacts in the tuning condensers, bad insulating property of the end plates, touching vanes all combine to rob a receiver of selectivity and power.

Primarily, you should only fit good condensers into your sets—Instruments which bear our Regd. Trade Mark.


Secondly, you should only fit the Square Law Type and be sure those you do buy emanate from the house of Jackson. They bear our mark—the sign of good design—an accurate straight line wavelength curve, guaranteed maximum capacity, an extremely low minimum, and many constructional superiorities.

.001	- 9/6	.0025	- 6/9
.00075	- 9/-	.0002	- 5/6
.0005	- 8/-	.0001	- 5/3
.0003	- 6/9	Vernier	- 4/6

There are J.B. Condensers for every tuning purpose. For really very fine tuning ask your dealer to show you the J.B. Microdenser: it incorporates an ingenious mechanical vernier.

J.B. Instruments are obtainable from all dealers or direct from the manufacturers: Post, one, 6d.; two, 9d.; three, 1s.

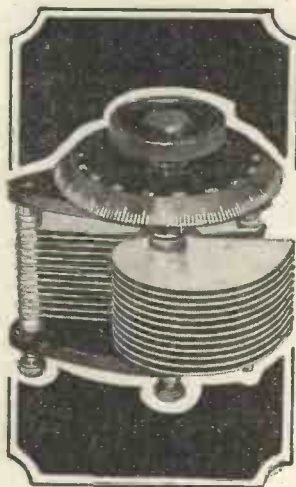JACKSON BROS.
 8, POLAND ST.—OXFORD ST.
 LONDON - W.1
 Telephone: GERRARD 7414
 (First Floor)



The SUPER Transformer
 IN QUALITY—EFFICIENCY and TONE
SUPER U.S. SUPER

COMPARE IT AGAINST ANY OTHER L.F. ON THE MARKET! NOTE ITS PRICE!! NOTE ITS FINISH!!!

MADE and TESTED BY EXPERTS ONLY


Ratio 5-1 AND IS

5 to 1

U.S. No. 1

14/6

Ratio 5-1

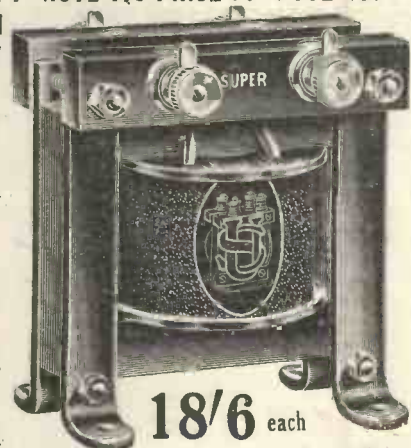

18/6 each

EVERY L.F. BEARING the TRADE MARK of the U.S. RADIO CO., LTD., is Thoroughly Tested and is GUARANTEED

FINISHED and DESIGNED LIKE A GUY!

U.S. No. 2

11/6 Ratio 3-1

THE SECRET OF THE U.S. SUPER'S SUCCESS
 They are wound by experienced winders, with the correct amount of the right gauge wire. They are packed with Stalloy iron of sufficient quantity to allow the transformer its maximum amplification. No part of this exceptionally fine instrument is neglected.

IF YOUR DEALER CANNOT SUPPLY YOU, WRITE TO U.S.

U.S. RADIO CO., LTD. Wireless Component Manufacturers, 155, HIGH STREET, LEWISHAM, LONDON, S.E.13. 'Phone, Lee Green 2404.

Barclays 203.

Charts, three of which are now on sale, price 1s. each. The basic principle of the Simplex Chart is a diagram giving the layout of the panel upon which all the parts are allotted reference numbers. A wiring key is provided which gives, in the clearest possible manner, the connections to each other of all the different parts, simply by quoting the numbers. By this means, the terrors of wiring which the beginner experiences, are materially lessened, and the operation is, in fact, reduced to a mere mechanical process, in which the probability of error, provided a normal amount of care is taken, is practically negligible.

Panel Transfers

Our characteristic attention to the smallest details is reflected in the issue of Radio Press Wireless Panel Transfers, which eliminate the necessity for engraving or otherwise marking a finished panel, and enable the keen constructor, who desires to impart the best possible finish to his work, to do so at the minimum of expense. For the sum of 6d., a set of Radio Press Panel Transfers, sealed in an envelope, can be obtained. A most comprehensive collection of the usual words, lettering, and symbols used for marking panels, is included.

Other Publications

Apart from our periodicals and the publications briefly outlined above, a large number of authoritative books on the many aspects of wireless, books on the design and construction of components, on valves, circuits and many other subjects of vital importance, written by members of the technical staff of the Radio Press, Ltd., and published by us, are available for the amateur. A progressive organisation such as Radio Press, Ltd., never lacks movement in the right direction, and our readers may rest assured that we will continue to advance their interests in every possible way.

DO NOT FORGET
TO ORDER YOUR
NEXT COPY OF

**"The Wireless
Constructor."**

Use a Reservoir Condenser.

MANY a high-tension battery can be made to last much longer if you use what is known as a reservoir condenser.

This is a condenser of about two microfarads capacity which is connected across the high-tension terminals of the set.

There are two reasons for using a reservoir condenser of this value. One is that your high-tension battery, when it is running down, gets crackly owing to small fluctuations in its voltage. Rather than discard your battery you may prolong its useful life by evening up these little fluctuations, and the way to do it is to connect a condenser of large capacity across the battery terminals.

A Helpful Analogy

The effect is very similar to that of an ordinary reservoir into which a stream may be running. If there were no reservoir there, our water supply might come straight from the stream, and the flow of water from the stream might be very irregular. On a rainy day there would be a rush of water, but on a fine day there might be only a trickle. To even things up we run the water into

a big pond, or reservoir, and draw our supply from this by means of pipes. There is consequently a big reserve of water always there to draw from, and the irregularities of the stream do not affect the steady outward flow of water from the reservoir.

Internal Battery Resistance

Another reason for using such a condenser is that a high-tension battery has a certain amount of internal resistance. This may amount to say 100 ohms in some cases, and, when it is remembered that perhaps several valves are all run off a single high-tension battery, the currents flowing through this battery, if it possesses a substantial internal resistance, will interfere with each other and may affect the operation of the set by causing peculiar reaction or reverse reaction effects.

A Useful Remedy

If however, we shunt the battery by a condenser of large capacity, as far as any varying currents are concerned the condenser will act as a short-circuit to them. A condenser of large capacity acts very much like an ordinary wire connection to currents of varying character, even though the condenser will not allow the passage of direct currents. The internal resistance of the high-tension battery is rendered non-effective by connecting a big-capacity condenser across the battery for this reason.

THANK YOU!

A quarter of a million copies of the first number of the WIRELESS CONSTRUCTOR were sold; yet at least thirty thousands of people were disappointed: Letters of congratulation, far too numerous for individual reply, have poured in from all parts of the country.

THE WIRELESS CONSTRUCTOR—The wireless magazine with a new appeal—has proved conclusively that the British public appreciates sound articles, common sense explanations, and really expert advice.

You can rely on the CONSTRUCTOR as you can rely on all Radio Press publications.

Will you please tell your friends who are just beginning wireless that the CONSTRUCTOR is the paper they need? THEY will thank you, too!

PERCY W. HARRIS.



Six Simple Crystal-Valve Circuits in Pictorial Form

A Guide to Wiring for the New Experimenter

THE first step from a crystal receiver involves the addition of a valve, and Fig. 1 shows in pictorial form the addition of a note-magnifying valve, in which reaction is also introduced into the aerial circuit. Constant aerial tuning is employed, C_1 being a fixed condenser of $0.0001 \mu F$ in series with the A.T.I., L_1 , across which is shunted a variable condenser C_2 which may conveniently have a value of $0.0005 \mu F$. Where the telephones would be in a simple crystal receiver is connected the primary T_1 of a step-up intervalve transformer, across the secondary of which is a fixed condenser C_3 of $0.001 \mu F$. The OS of T_2 is connected through L_2 to the grid of the valve V_1 ; and the plate circuit includes the coil L_3 and the 'phones T , shunted by

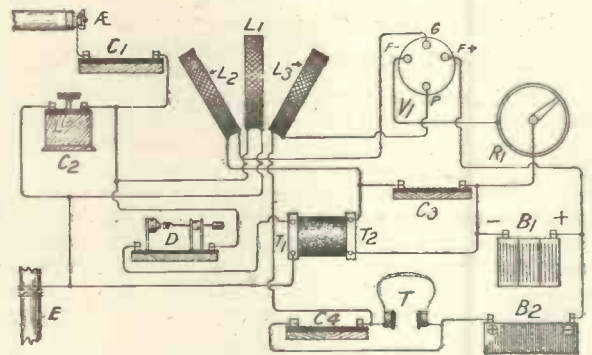


Fig. 1.—A note-magnifier and reaction added to a simple crystal set.

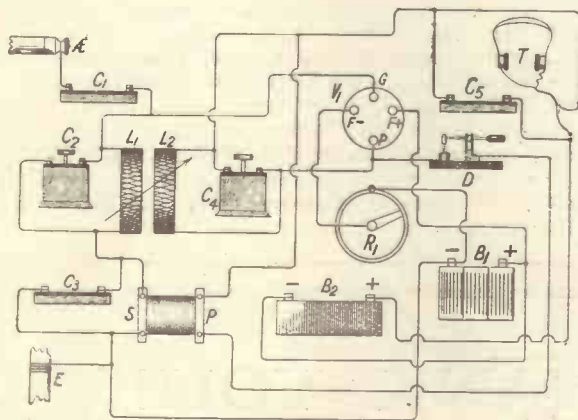


Fig. 2.—A simple reflex circuit.

C_1 of $0.002 \mu F$. In this, and in all the following circuits, R_1 , B_1 , and B_2 represent the filament resistance, fil. battery, and H.T. battery respectively. For broadcast wavelengths L_1 , L_2 and L_3 may be No. 50 honeycomb coils. For 5XX, L_1 may be a No. 200, and L_2 and L_3 both No. 150. Reaction is introduced by varying the coupling between L_3 and L_1 or L_2 and L_1 .

A Reflex Circuit

Proceeding a stage further we come to a reflex circuit illustrated pictorially in Fig. 2. Constant aerial tuning is provided as before by the $0.0001 \mu F$ condenser C_1 in series with the aerial. The incoming oscillations are amplified at high frequency by the valve V_1 , rectified by the crystal D , the resulting low frequency currents being fed back into the grid circuit through the primary P of the

step-up transformer PS, and subsequently amplified as such by the valve. For each of the variable condensers C_2 and C_4 , $0.0005 \mu F$ is a suitable value, whilst the fixed condensers C_3 and C_5 may be $0.001 \mu F$ and $0.002 \mu F$ respectively. The aerial coil L_1 may be a No. 50 coil, and the reaction coil L_2 a No. 75. These values will give efficient reception on the broadcast wavelengths.

A Modification

Fig. 3 illustrates pictorially a slightly modified form of the Fig. 2 circuit, the only essential difference being that the high-frequency oscillations, after being rectified by the crystal D , are fed back to the grid currents as low frequency currents through the transformer T_1 , T_2 and the air core choke coil L_3 , which, for broadcast wavelengths, may be a No. 200 honeycomb coil. The fixed condenser C_3 in Fig. 2 is omitted, and a fixed condenser C_3 , of $0.0003 \mu F$, is connected in the grid circuit as indicated.

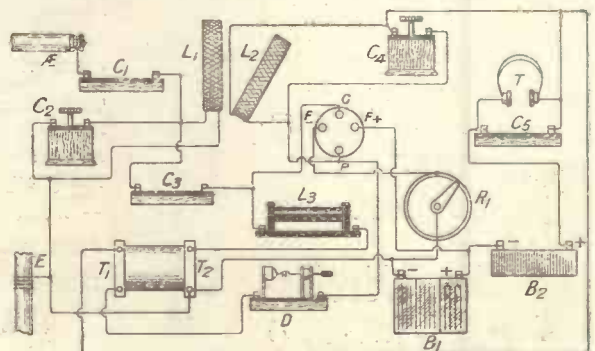


Fig. 3.—A modified form of the Fig. 2 circuit.

An Interesting Circuit

In Fig 4 is illustrated pictorially an interesting circuit incorporating yet another method of reflexing. The amplified H.F. oscillations are passed on to the crystal detector D through the transformer L_2, L_3 , rectified, and the resulting L.F. currents fed into the joint aerial and grid circuits via the condenser C_3 of $0.0003\mu F$ capacity. If the

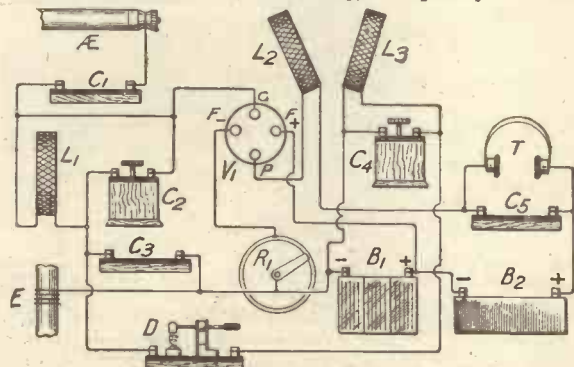


Fig. 4.—An interesting reflex circuit which dispenses with the L.F. transformer.

C.A.T. condenser C_1 is made $0.00025\mu F$, this will, in conjunction with C_3 , produce a resultant approximate capacity of $0.0001\mu F$ in series with the aerial. The transformer L_2, L_3 may consist of two coupled plug-in coils as indicated, L_2 being a No. 50 or a No. 75, and L_3 a No. 50.

Tri-Coil Circuits

The pictorial diagram Fig. 5 illustrates how reaction may be introduced into the aerial circuit by means of the tri-coil method, using however the same method of feed-back as in Fig. 4. The honey-comb coils L_1, L_2, L_3 , may consist of Nos. 50, 75 and 50, which will provide ample wavelength range for the reception of broadcast. L_1 is tuned by the variable condenser C_2 of $0.0005\mu F$ capacity, L_2 is aperiodic, and L_3 is tuned by C_5 , also $0.0005\mu F$. Reaction is provided by coupling L_1 and L_2 , while the coupling between L_2 and L_3 is usually tight, and may

be loosened, but only at the expense of signal strength.

In other respects Figs 4 and 5 are identical. The tri-coil system provides for an easy control of reaction, but it should be observed that a variation in the coupling of the three coils must be accompanied by a corresponding retuning on C_2 and C_5 . Fig. 6 shows pictorially another application of the tri-coil system to a reflex circuit employing transformer feed-back. The step-up L.F. transformer T_1, T_2 functions in place of the condenser C_3 of Fig. 5. In other respects Figs. 5 and 6 are identical. The beginner would be well advised to try-out these circuits in the order given, using an experimental panel. By this means a valuable insight into the principles and manipulation of reflex circuits may be obtained. For the benefit of those to whom the symbols and abbreviations used in the foregoing are unfamiliar, the following list is appended:—

- μF —microfarad,
- A.T.I.—Aerial tuning inductance.
- C.A.T.—Constant aerial tuning.
- L.F.—Low frequency.
- H.F.—High frequency.
- H.T.—High tension.

be loosened, but only at the expense of signal strength. In other respects Figs 4 and 5 are identical.

Reaction Control

The tri-coil system provides for an easy control of reaction, but it should be observed that a variation

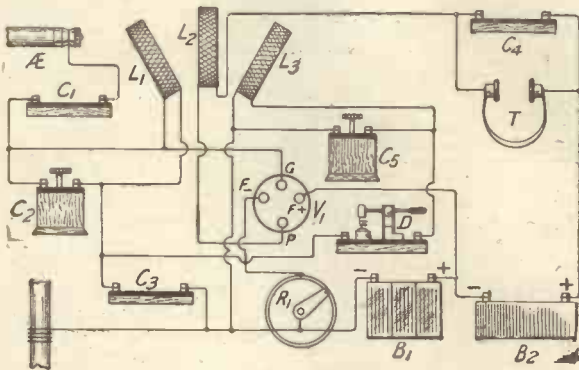


Fig. 5.—The introduction of reaction into the aerial by the Tri-Coil System.

in the coupling of the three coils must be accompanied by a corresponding retuning on C_2 and C_5 .

Fig. 6 shows pictorially another application of the tri-coil system to a reflex circuit employing transformer feed-back. The step-up L.F. transformer T_1, T_2 functions in place of the condenser C_3 of Fig. 5. In other respects Figs. 5 and 6 are identical.

The beginner would be well advised to try-out these circuits in the order given, using an experimental panel. By this means a valuable insight into the principles and manipulation of reflex circuits may be obtained. For the benefit of those to whom the symbols and abbreviations used in the foregoing are unfamiliar, the following list is appended:—



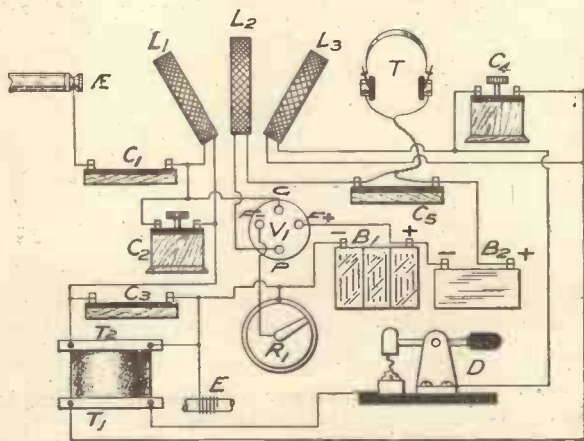


Fig. 6.—A tri-coil reflex using an L.F. transformer.

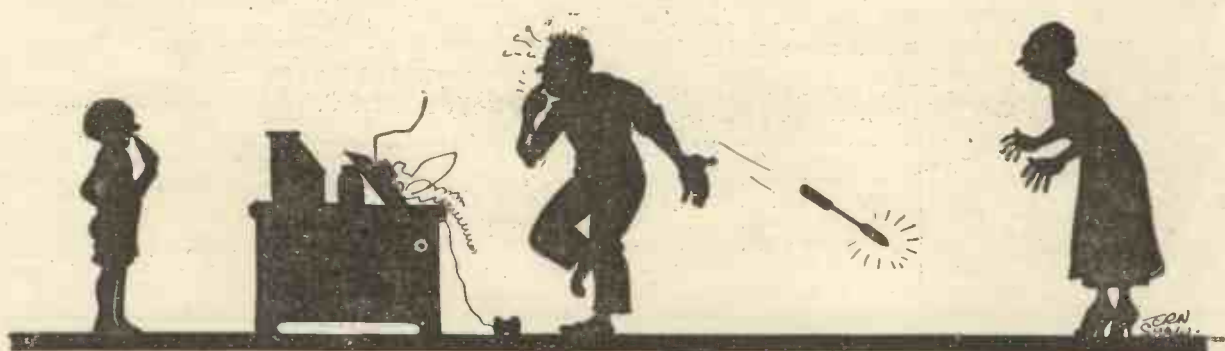

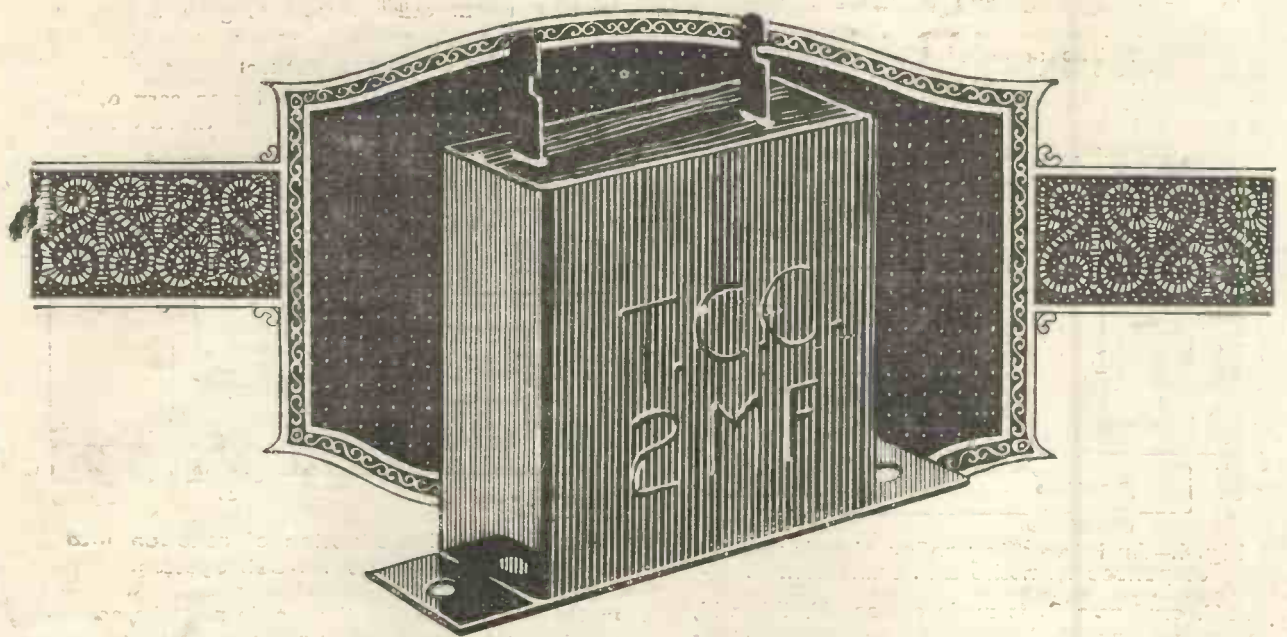

—the famous green Condenser

YEARS before Broadcasting, Wireless enthusiasts knew the T.C.C. green condenser. Hundreds of thousands have been made—in fact, it is recognised everywhere as the standard *fixed* Condenser for wireless use.

Its green metal case is a familiar sight in wireless shops and at Radio demonstrations. There is hardly a manufacturer of note who does not standardise on T.C.C. Condensers for at least some position or other in his Receiving Sets.

The reason for this marked supremacy is that—in spite of its low cost—the T.C.C. Condenser has never been built down to a price. The first consideration has always been quality. A faulty condenser is a snare and a delusion. Put one in your Set and it may cost you the price of a new

H.T. Battery—or at least it will prevent your Set from functioning and probably cause you hours of trouble and worry.

No! a condenser must be bought entirely on faith. Therefore when you buy a T.C.C. Condenser you can be sure that it has been made as well as expert fingers and elaborate machinery can make it. Remember, every T.C.C. Condenser is fully guaranteed and accurately calibrated. Whatever your purpose, use a T.C.C.—it will take up little room on the panel—but be sure it is a T.C.C.

No. 24, 2 mfd.	4/8	No. 28, '1 mfd. and '2 mfd.	2/8
No. 25, 1 mfd.	3/10	No. 30, '01 to '09 mfd.	2/4
No. 26, '5 mfd.	3/4	No. 31, '001 to '009 mfd.	2/-
No. 27, '25 mfd.	3/-	No. 32, '0001 to '0009 mfd.	1/10

FROM ALL DEALERS.

Some Radio Questions Answered

Help for the New Experimenter.



What is meant by a hard valve ?

A hard valve is one having a particularly high degree of vacuum. That is to say, that no appreciable amount of gas remains within the valve, under which condition the current flow through it depends entirely upon the number of electrons passing between the hot filament and the anode. Hard valves may be operated satisfactorily with very much higher anode voltages than soft valves.

How can one test a pair of 'phones suspected of being defective ?

Place their tags across a single dry cell, or two of the adjacent sockets of an H.T. battery, and note whether a click is produced at make and break of the circuit. No click indicates a break in either cords or windings. Replace the cords with temporary leads and try again. If there are still no clicks the fault is in one or both of the earpieces. Short-circuit first one and then the other with a piece of wire, and repeat the

test. If shorting one earpiece enables clicks to be heard in the other, the shorted one is at fault. If no result is obtained by shorting either, both are faulty.

What is the best all-round combination for three Valves ?

Taking the expression "all-round" to mean good average reception of near-by, medium and long-distance signals, a combination consisting of one H.F. detector, and one L.F. valve is constantly

WHAT YOU WILL SEE ON STAND 3, BLOCK F

White City Exhibition, November 15-29.

GAMBRELL "EFFICIENCY" APPARATUS

Coils—wavemeters—valve sets—components of all descriptions and their remarkable H.F. Units fitted with the Neutrodyne. Do not fail to inspect the latest Gambrell product, the SPECIAL NEUTRODYNE CONDENSER so favourably reported on by the Editor of the "Wireless Constructor" (No. 1 issue).

MYERS VALVES.

Bright and Dull Emitters.

We use a GAMBRELL 3-Valve Set, and MYERS Valves for our successful reception at Loud-Speaker strength of the AMERICAN speech from W.G.Y by Capt. Eckersley.

WE ARE LONDON AGENTS FOR ALL THESE PRODUCTS.

J. V. MULHOLLAND,

Consulting Radio Engineer,

4, Blenheim St., New Bond St., W.1

'Phone: Mayfair 2666.

(One minute from Bond Street Tube Station.)


The present popularity of Square Law Condensers and the efficient working of the straight wavelength curve require a coil of very low self-capacity. Any high-capacity coil renders more inaccurate the plotting of the wavelength curve on the principles which are now being advocated. Square Law Condensers are most efficient, but use in conjunction with them



PLUG-IN

This is due to their extremely low self-capacity. Reversion to the old type condenser is only equalled in its inefficiency by employing coils of high self-capacity with Square Law Condensers. Efficiency requires "Diamond Sunflower." Low self-capacity, low H.F. resistance, maximum transference of energy and consequently maximum signal strength, sharper tuning and selectivity, follow the fitting of "Diamond Sunflower" Coils, etc., etc. Prices include the plug.

COILS

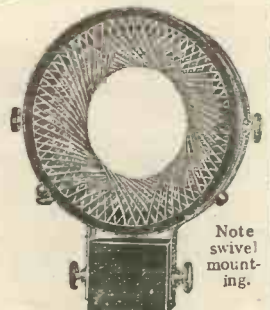

PROV. PAT.

It should be remembered that intermediate sizes are made. This allows for a larger inductance and a lower condenser capacity for any given wavelength—a little consideration which gives better reception. Get "Diamond Sunflower" Coils from your dealer. If not, write or call. Full lists on application. DIAMOND WIRELESS, LTD., 184a, OXFORD STREET, LONDON, W.1. Telephone: Museum 1380. Entrance Et. Titchfield Street.

No. of Coil.	Approx. Wave-length in metres '001 Cond. in Shunt.	Price per Coil.
25	100—290	4/3
*30	142—377	4/8
35	185—465	4/9
*40	216—561	4/11
50	245—653	5/-
*65	310—820	5/3
75	395—1,090	5/6
*85	600—1,350	5/9
100	619—1,495	6/-
*125	671—1,720	6/8
150	720—2,000	7/-
*175	850—2,400	7/3
200	980—2,780	7/6
*225	1,010—3,160	7/9
250	1,240—3,520	8/-

etc., etc. Prices include the plug.

recommended. The H.F. valve enables satisfactory reception to be obtained from signals which without it would be too feeble to actuate the detector valve, whilst the L.F. valve gives a reliable and satisfactory amplification of whatever signals come through the detector valve. If it is desired to increase signal strength in order to operate a loud speaker, the addition of a further L.F. amplifying valve is recommended.

What is reaction and what purpose does it serve?

Reaction, sometimes called retro-action and reactance, although the last-named is incorrect, affords a means of reducing the resistance of an oscillatory circuit, not only to zero point, but beyond that, in which case "negative resistance" is said to be introduced. The received currents in an aerial circuit, connected to the input side of a three-electrode valve, are damped out by the resistance of the circuit and the damping action of the valve. By introducing an additional inductance coil and coupling it to the aerial circuit, some of the

amplified energy in the anode circuit may be transferred back to the aerial grid circuit, and provided the direction of the winding of the reaction and aerial tuning coils is correct, the losses in the aerial cir-

cuit are to a large extent compensated for, with consequent increase in signal strength.


What is the best method of preventing interference from a nearby broadcasting station so that distant stations can be received?

It can scarcely be said that there is one infallible method of accomplishing this, but provided the receiving apparatus is fairly selective in itself, one or other of the following arrangements will no doubt meet the requirements. 1. Much can be done in the avoidance of this type of interference by selective tuning only. By this is meant the use of an inductively coupled tuner, operated always with a very loose coupling between the aerial and closed circuit, and one high-frequency valve with a carefully tuned anode circuit. (See Mr. Harris's neutrodyne.) 2. If careful tuning alone will not eliminate the interference, owing to the comparative closeness of the transmitting station, alternative arrangements of "wave traps" should be tried. In using any of these devices, carefully tune in the desired station with the "trap" in




A giant crystal set at the Plymouth show.

CONSTRUCT YOUR OWN SET

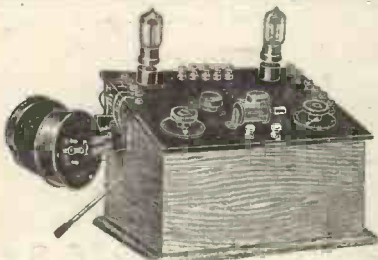

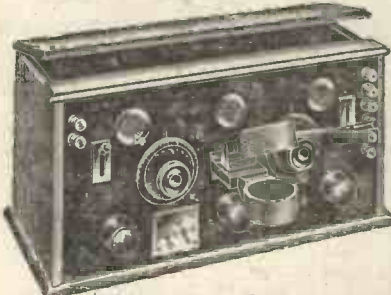CONSTRUCT THE S.T.100 for £7 4s. 2d. (Envelope No. 1.)



CONSTRUCT THE ALL CONCERT de LUXE for £9 8s. 0d., including Sterling Condensers. (Envelope No. 4.)

CONSTRUCT THE 7-CIRCUIT CRYSTAL SET as described in this issue by Mr. Percy W. Harris.

- 1 Polished Cabinet, 10 in. by 9 in. 9 0
- 1 Radion Mahogany Panel, 10 in. by 9 in. 9 6
- 1 Var. Sq. Law Condenser .0005, complete 8 3
- 1 Burndept Crystal Detector, complete 5 0
- 6 Terminals (Lacquered), complete 1 0
- 4 Clix Sockets 1 0
- 3 Clix Plugs 1 0
- 1 Plug and Socket with Shorting Plug 9
- 1 Prepared Cardboard Tube 6
- 1 lb. No. 16 D.C.C. Wire 2 6
- Supply of No. 16 Sq. Sec. T.C. Wire 3
- 1 Set Radio Press Transfers 6

£1 19 3


Complete as above (carr. and pkg. free), £2.

1 lb. Hank No. 16 D.C.C. Wire for P. W. Harris Crystal Set, 3/-, post free.
 All Components supplied for the 3-Valve Neutrodyne, Resistorlex and all Circuits described in WIRELESS CONSTRUCTOR.
 Send stamp for Illustrated Booklet and set of Leaflets dealing with S.T.100, 4-Valve Family, Simplicity 3, All Concert-de-Luxe, Omni Transatlantic 5, Transatlantic 4, Puriflex, 3-Valve Dual, All-Britain, Tri-Cell, Crystal Set, 3-Valve Neutrodyne, etc.

Carriage and Packing Free on Retail Orders value £2 or over.
BURNE-JONES & Co., Ltd.
 Magnum House, 288, Borough High Street,
 LONDON, S.E.1.
 Telephone: HOP 6257.



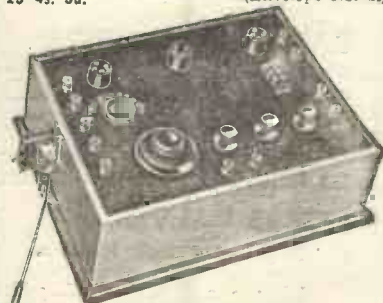CONSTRUCT THE 4-VALVE FAMILY for £9 4s. 5d. (Envelope No. 2.)



CONSTRUCT THE SIMPLICITY 3-VALVE for £4 11s. 8d. (Envelope No. 3.)



CONSTRUCT THE TRANSATLANTIC V. for £11 13s. 11d.

BUY A RADIO PRESS ENVELOPE containing Blue Prints and full instructions for building the following famous Sets:—

No. 1. S.T.100	Post free.
No. 2. 4-Valve Family	1/8
No. 3. 3-Valve Simplicity	2/9
No. 4. All Concert-de-Luxe	2/9
Radio Press Transfers	8d.



**PARAGON
CURTIS
ONE-PIECE
MICA
CONDENSER**



Guaranteed Uniform Capacity.

The duty of fixed condensers in wireless receiving circuits is one of paramount importance. While so small a component may appear innocent of reducing the efficiency of any receiver, the function of a fixed condenser is such that it requires a guaranteed uniform capacity. Considerable manufacturing skill combined with the huge chemical and moulding resources of Britain's largest ebonite manufacturers is represented in every Paragon-Curtis.

Its manufacture is of so precise a nature that two Paragon-Curtis Condensers of the same stated capacity picked out at random are guaranteed to be of uniform capacity. Such uniformity has never before been attained.

Efficiency is only to be gained when fixed condensers are of guaranteed capacity—greater efficiency when guaranteed capacity is uniform throughout production.

'0008 to '006 ... 2/6 each
Grid Condenser with Clips 2/9 each
Grid Leak ... 1/6

**GENUINE SERVICE
WITHOUT PROFIT**

For the benefit of the Home Constructor we have now opened a
CONSTRUCTOR'S DEPARTMENT


Any constructor purchasing a complete set of parts either direct from us or through any of OUR AGENTS for any published circuit whatsoever and experiencing any difficulty therewith may send his effort to the Constructor's Department, Peter Curtis, Ltd., together with a postal order to cover the nominal charge of 2/6 per valve holder. For this sum we shall examine the set, rectify any errors and return carriage forward in perfect order tested under average conditions on P.M.G. Aerial.

- (a) Care should be taken to pack carefully, as all goods will be returned in the same case as received.
- (b) Mention the trader from whom the parts were purchased.
- (c) Unless the charge for passenger carriage is included, the set will be returned carriage forward per goods train.

**CURTIS FILAMENT
RHEOSTAT.**

45 to 50 ohms; Eureka wire; the smooth micrometer adjustment of this Curtis Rheostat places it above any high-resistance rheostat on the market, and assures the finest possible degree of filament control. One hole fixing.

Price 5/-.

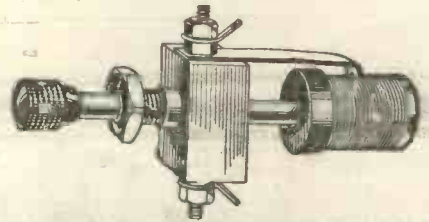

PARAGON Radio Quality
"The Best Post Office Specification
Made." **EBONITE PANELS**

Uniform Fine Grain.
Dead Matt Finish.
Non-metallic surface.

TESTED and RECOMMENDED by "MODERN WIRELESS."

STANDARD SIZES.	
4 1/2 x 4 x 1/8	.. 9/10
6 1/2 x 5 1/2 x 1/8	.. 1/9
8 x 6 x 1/8	.. 2/6
8 x 6 x 1/4	.. 3/3
10 1/2 x 8 1/2 x 1/8	.. 5/3
12 x 10 x 1/8	.. 7/3
12 x 12 x 1/8	.. 8/6
14 x 12 x 1/8	.. 10/-
16 x 12 x 1/8	.. 11/6
18 x 12 x 1/8	.. 13/-
24 x 10 x 1/8	.. 14/6
24 x 12 x 1/8	.. 17/6
8 x 5 1/2 x 1/8	.. 2/9
9 1/2 x 7 x 1/8	.. 4/7
12 x 6 x 1/8	.. 4/3
11 x 11 x 1/8	.. 15/3
9 x 9 x 1/8	.. 9/-
11 x 11 x 1/4	.. 8/3
6 x 6 x 1/8	.. 6/9
8 x 8 x 1/8	.. 6/-
10 x 10 x 1/8	.. 6/9
12 x 12 x 1/8	.. 2/3
14 x 14 x 1/8	.. 5/8
16 x 16 x 1/8	.. 3/5
18 x 18 x 1/8	.. 3/3
24 x 24 x 1/8	.. 7/6

EXTRA PRICE FOR DRILLING AND ENGRAVING:
MODERN WIRELESS PANELS.

To M.W. Specification only.	Delivery from Stock.
S.T. 100 (2 valves) .. 7/-	Experimenter's Tuner .. 9/-
S.T. 100 (3 valves) .. 5/9	Double Reaction .. 4/6
Efficient Single Valve .. 3/6	Crystal Set (Harris) .. 3/6
Transatlantic .. 7/-	All Britain .. 7/-
De Luxe Amplifier .. 6/-	1/2 Portable .. 5/6
Single Valve All Wave 3/6	3 Valve Dual .. 8/6

SPECIAL PANELS for Sets described in the current issue. Similar quality and finish, Cut, Edges Ground and d spatched same day 3d. per sq. in. postage 6d. extra.

PARAGON POLISHED MAHOGANY EBONITE

Is NOT a Composition, but **GUARANTEED POST OFFICE QUALITY EBONITE** and is of similar specification to the now universally used **PARAGON EBONITE**. **PANELS CUT TO SIZE, Squared, Edges Ground, 1d. per sq. inch.**
STOCKED BY ALL REPUTABLE STORES. But it must be in PARAGON SEALED CARTON

**THE
"NU-GRAVING"
PANEL MARKING PROCESS**

You will find **NUGRAVING**

We appreciate the compliment of the increasing competition of spurious imitations. For the moment we would strongly emphasise that **NUGRAVING** is guaranteed against chipping, cracking or any deterioration either before or after use, for an indefinite period.

An interesting announcement of particular interest with reference to **NUGRAVING** will shortly be made.

PETER CURTIS, LTD.
75, CAMDEN ROAD, N.W.1.

Telegrams: "Paracurtx." Phone: North 866.

BIRMINGHAM—76, Newall St. Central 7236.

MANCHESTER—312, Deansgate. Central 5095.

In conjunction with

**THE PARAGON RUBBER
MFG. CO., LTD., HULL.**

**LOCAL BROADCAST
ON THE**


LOUD SPEAKER

THE RADIONETTE No. 4—

Crystal and Two Note Magnifiers.

50% more power than any other

2-Valve Receiver of equal price.

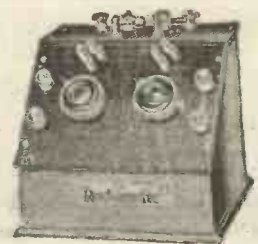

Price £6 0 0

SOLD

MAKES SOLDERING CHILD'S PLAY.

OTHER METHODS



An amateur can solder more easily with "SOLD" than an expert by other methods. *Soldering without Soldo is the constructor's nightmare.*

1/6 NO ACIDS, NO FLUXES, NO FILING: Cleans and Tins and Solders in one operation.

The SOLD CO., Sicilian House, Southampton Row, London, W.C.1.

SOLD METHOD



ULTRA

REGISTERED TRADE MARK

NEW IMPROVED MODEL



"Nothing to touch it"

ASK YOUR DEALER FOR IT

Should you have any difficulty in obtaining same, write direct to

Messrs. EDWARD E. ROSEN & CO.,
158/160, City Road, London, E.C.


with the name of your Dealer.

27/6

REGENERATION IN THE DETECTOR CIRCUIT.

The damping effect of a grid leak having the wrong value is an experience which has to be tried to be fully understood. Damping circuits where Detector Valve Regeneration is employed does actually destroy rather counteracts the gain in signal strength secured by regeneration. Ability to adjust grid leak resistance to just the correct proportion for the full employment of regeneration is only possible with a **VARIABLE GRID LEAK**. By working the detector valve on the correct portion of the curve for perfect rectification—**AND HERE A VARIABLE GRID LEAK IS INDISPENSABLE**—the detector valve may be efficiently controlled to give maximum signal without any possibility of the rectifier tipping the set into self-oscillation.

CHOOSE ALWAYS A WATMEL. IT GIVES DELICATE CONTROL BUT BE SURE YOU FIT A



Watmel
COIL FORMER
For winding inductances.
4/6

All goods of our manufacture bear this mark. It is your only guarantee.

IMPORTANT NOTICE to intending purchasers



Patent 206098

5 to .5 Megohms 2/6
50,000 to 100,000 Ohms. 3/6

Other Resistances to suit any circuit.

Send P.C. for Descriptive Folder. SEE THE TRADE MARK.



ON EVERY GRID LEAK, BEWARE OF IMITATIONS.

The Watmel Wireless Co. wish to notify the trade and public that their Variable Grid Leak Patent Application No. 206098 was contested in the Comptroller's Court and on Appeal; in both instances the Patent Grant was upheld and costs awarded.

It is the aim of this Company to protect traders', customers', and also its own interests by securing Patent protection for the novelties in its specialities, as it is these novelties, invented by experts and exhaustively tested, which are the Hall Mark of all Watmel Products.

THE WATMEL WIRELESS CO.

332a, Goswell Road, London, E.C.1.

Telephone - - - - - CLERKENWELL 7990.

circuit, but not correctly adjusted, and then vary the trap condenser until the unwanted station is satisfactorily tuned out.

What expedient can be adopted to stop self-oscillation in high-frequency amplifiers ?

Assuming that the amplifier has been properly designed, and that the wiring has been carried out so as to separate the various circuits as much as possible, all that is necessary is to adopt one of the methods of stabilising, such as the use of a potentiometer.

What are the respective uses and advantages of the different methods of high-frequency intervalve coupling ?

The method which commonly gives the greatest amplification per valve is that known as the tuned anode method, which consists of a tuning coil and condenser connected in the plate circuit of the valve, tuned to the received wavelength, and coupled to the grid of the succeeding valve by means of a small grid condenser and leak.

this method is probably the best, since it is uniformly efficient upon all broadcast wavelengths and is easy to handle. Where more than one high-frequency valve is used, however, this type becomes somewhat unstable and difficult to operate, and it is then usually preferable to employ the tuned transformer method, which consists of a high-frequency transformer, one of whose windings, either primary or secondary, is tuned by means of a very small variable condenser. Such transformers can be easily designed to introduce a certain amount of damping in the intervalve circuits, and thereby one can stabilise the receiver to any desired degree. Where more than two high-frequency valves are employed, or where it is desired to have a receiver of extreme simplicity, it is usual to employ the semi-aperiodic type of transformer, which is wound with very fine resistance wire to flatten the tuning of the windings so that no tuning condenser is needed. This type does not give so much amplification, but it is very easy to handle. For long wave reception above

about 1,000 metres the resistance-capacity method is extremely useful, since it is very stable and easy to handle, there being no tuned intervalve circuits. This method operates by virtue of the fact that if high resistances are connected in the anode circuits of the valves, fluctuations in the plate current caused by incoming signals will produce fluctuating voltages across the ends of these resistances, which can be transferred to the grid of the next valve by the usual grid condenser and leak. The amount of amplification given by this method, however, is not very high.

How is it possible to tell when the valve set is radiating ?

In the first place, the possibility of actual radiation depends upon the point in the circuit at which the reaction effect is introduced. Reaction, electro-magnetic or electrostatic, may be applied to the aerial or aerial secondary circuit, or there may be one or more valves between the aerial circuit and the point at which reaction is applied. From this it will be gathered that a valve receiving

RADIAX Duplex Basket Coils

Far more efficient than honeycomb or any other type of coil. Exceedingly strong and rigid, mounted on standard ebonite plugs. Brown finish, no wax or shellac used.



No.	Mounted Price.	Unmounted Price.
25	1/6	2/-
35	1/9	2/-
50	2/-	2/6
75	2/3	2/6
100	2/9	2/6
150	3/-	2/6



Variable Condensers.

Knobs deeply fluted, ensuring easy control. Vernier indicator shows position and makes the finest tuning simple. Their high overall efficiency enables hitherto impossible stations to be tuned in readily.

Capacity.	Best Quality. With Vernier.	Best Quality. Without Vernier.	Cheaper Quality. Without Vernier.
.001	12/-	8/6	7/-
.0006	10/-	7/-	5/9
.0003	10/-	6/-	5/-

RADIOSTAT.

A universal filament resistance, infinitely variable. Suitable for ordinary or D.E. valves. Price 2/9. Radiax Fil. Res. for ordinary valves, 1/10.



Crystal Detectors.

No. 320 Radiax New Horizontal, exceedingly well made and finished. 2/3. No. 309, Vertical enclosed splendid value 1/10. No. 670, The Mic-Met. The best yet produced 6/-.



Transformers (H.F. or Tuned Anode Coils).

We specialise in H.F. Couplings and Reaction Units of all kinds. Send for special list, post free, or 3d. for complete Catalogue of Radiax Sets, Components and Accessories.




Wavelength.	Price
300/500	3/6
500/900	4/3
900/1600	4/9
1500/2600	5/6
2600/4000	6/6



Standard Coil Socket 1/6
Standard Coil Plug 9d.



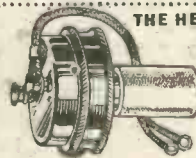The guarantee of THIS crystal is that we use it in our own Receivers on account of its remarkable power, permanence and long life. Price 1/3 per tin, with spearpoint catswhisker.




THE HERALD LOUD-SPEAKER RECEIVER.

For building a loud-speaker in any form. Adaptable to any horn or gramophone instantly attached. Adjustable diaphragm. Perfect tone on speech and music. As illustrated, but with 6 ft. cord. Price ... 29/-

CABINETS POLISHED.

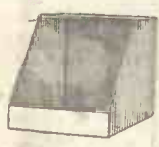Selected Mahogany as illustrated, new, perfect. Block approx. 1 in. square. Limited Stock. Size 13 in. wide, 12 1/2 in. high, bottom 8 in. deep, top 4 in. deep. Price ... 10/6. Postage and Packing 1/- ext. A variety of Cabinets are listed in our Catalogue.



L.F. INTERVALVE TRANSFORMERS.

Powquip	14/6
Ferranti	17/6
R.J.	25/-
Royal	20/-
Telephone Transformers	13/6



VARIOMETERS on tube frames with knob and pointer as illustrated ... 2/8. With ebonite former and ball rotor ... 6/9. Finest quality, with ball stator and rotor ... 10/-.
EARTH SWITCH and LIGHTNING ARRESTER. The newest protective device consists of strong Earth Switch, Lightning Arrester and a Lead-in Tube combined. 5/9 each.
TWIN WIRE for CONNECTIONS (Black and Red). twisted flex, most convenient for battery, loud-speaker, etc., leads. Price, 25 yds. 7/-, or 4d. per yd.

Your dealer can supply all Radiax specialities.

RADIAX, Ltd., 44, Radio House, Percy Street, TOTTENHAM COURT ROAD, LONDON, W.1. Museum 490. 3 min. Tottenham Ct. Rd. & Cooledge St. Tube Stations



AIRMAX

BARE WIRE

Tuning Coils

Use neither Shellac, Tape, Wax, Cotton nor similar coverings between the layers and turns. The "Airmax" Coil being absolutely Air Spaced in every direction provides the theoretically and practically ideal coil.

MAXIMUM INDUCTANCE WITH MINIMUM SELF CAPACITY.



Pat. Appld. for 11983/24.

Coil No.	Wavelength with four mfd. in parallel.	Prices.
25	125 to 380	5/-
35	180 " 600	5/-
50	240 " 780	5/2
60	290 " 1000	5/4
75	350 " 1400	5/8
100	455 " 1600	7/-
150	650 " 2400	7/10
200	900 " 2800	8/8
250	1200 " 3800	9/-

Sent anywhere on approval against cash. **LISTS FREE. AGENTS WANTED.**

RADIO

FRENCH '06 VALVES

Fil. Volt 3: Fil. Amp. '06 HT. 20-100.
14/11 each.

Self praise is no praise. This is entirely unsolicited.

Many thanks for your prompt dispatch of my order. The '06 valve is the best I have ever tried and works well on 2-volts, but gives amazing results on just under 3. I have built over 20 sets this year, so I am not a novice by any means.

All Valves Insured against Breakage in the Post. Ask for Special List.

DEMONSTRATION AGENTS WANTED. See our advt. in Nov. issue MODERN WIRELESS.

H. LLOYD MARSHALL
and CO.,
8, Westmoreland Bdgs., E.C.1.

set may be oscillating and yet not radiating, although it is certainly the safest and most considerate plan to avoid oscillation of any kind on broadcasting wavelengths during broadcast hours. If radiation is suspected, remove the reaction coil to a distance or short-circuit it and touch the aerial terminal with the moist finger tips. Note carefully the sound in the telephones. Replace the reaction coil in its normal position and again touch the aerial terminal. If radiation is occurring a noticeably different sound will be produced in the telephones. (See also a note in this issue on "How not to oscillate.")

Why is it that a continuous subdued rustling and crackling noise is heard in the intervals of the programme of a Broadcasting Station?

Various phenomena may assist in producing this sound, such as microphone-rustles at the broadcasting station, or "line noise" from induction effects in the underground cables used in broadcasting public entertainments, but the usual cause is partial heterodyning of the more or less continuous stream of minor atmospheric by the carrier wave. A similar faint rustling is heard when a receiver is kept in continuous oscillation by means of reaction. If the noise is very pronounced, and is accompanied by occasional louder clicks and bangs, it may indicate either a defective H.T. battery or a bad night for atmospheric. To distinguish between these possible causes, disconnect aerial and earth from the set and note whether the noise continues; if it does the H.T. battery may be implicated, although it may also be due to a loose or otherwise faulty connection somewhere, leaky insulation or a defective grid leak.

What is "double reaction"?

In simple circuits reaction is applied at only one point, but it is possible to react into two or more of the circuits in a receiver with beneficial effects upon the signal strength. Such receivers are apt to be difficult to handle, however.

What is meant by saying that an accumulator is of 60 ampere hours capacity?

This indicates that the battery is of such a size that it will deliver a current of one ampere for 60 hours, 2 amperes for 30 hours, 4 amperes for 15 hours, and so on, before requiring re-charging.

The capacity is sometimes given in "ignition" ampere-hours, which is double the "actual" capacity.

Thus, if an accumulator is described as being of 50 amp. hours ignition capacity, it will only give one amp. for 25 hours.

What is meant by negative grid bias?

When using fairly high voltages upon the anode of an amplifying valve, it is desirable to apply an additional negative potential upon the grid (by means of one or two dry cells included in the grid circuit), to ensure that the average steady current through the valve corresponds to a point about half-way up the straight part of the characteristic curve. This additional grid potential is always negative, and is known as "negative grid bias."

What precautions should be taken to ensure the clearest reproduction by a loud-speaker?

Assuming that distortion has been eliminated as far as possible in the circuits of the receiver itself, first turn the adjusting screw of the loud-speaker until the best result is obtained, and then experiment with various sizes of fixed condenser across its windings. In the case of a low-resistance instrument the requisite capacity will be quite large, an average value being 0.25 μ F, and it will greatly improve the performance of the loud-speaker when provided. The effect is less marked with the high-resistance type, but is nevertheless present, and should be taken into account. A good value in this instance is 0.005 μ F.

A very important adjustment to obtain the most satisfactory results is that of the volume or loudness of the signals; it is utterly useless to apply an input power large enough for a Magnavox Senior to one of the "baby" or "junior" varieties of loud-speaker, for the inevitable result is severe distortion from the ruthless overloading. Always adjust the strength of the signals to such a point that the loud-speaker is taking just as much as it will carry without beginning to distort seriously, and never give it more. It is a most senseless proceeding to pile on valve after valve until the diaphragm is rattling against the pole-pieces and the horn is ringing with all sorts of notes and their harmonics, and yet it is all too common. If it is necessary to reduce the signal strength even when a moderate number of valves are in use, it should be done by slightly de-tuning the receiving circuits, which often reduces distortion, rather than by turning down the valve filaments, which may increase it.

Practical Workshop Hints.

Ebonite—A Panel Tip—Simple Tapping—The Breast Drill

DON'T try to work ebonite with wood tools. You can cut it with a chisel, and you can plane its edges; but both plane and chisel suffer severely in the process. Ebonite, which is made from india-rubber, is an exceedingly tough substance, which blunts even metal tools very rapidly unless care is taken. A little oil or turpentine used as a lubricant when drilling, for example, adds considerably to the useful life of one's twist drills. Never try to put wood screws into ebonite. Amongst other things the pitch of their thread is far too steep to enable them to work their way into it, and if you try to use them you will most certainly twist off their heads and be unable to extract them. The only wood tool which may legitimately be used for ebonite working is the tenon or stiff-backed saw, which is very useful for cutting it, since it enables you to make a perfectly straight edge.

When you are laying out the panel either of a complete set or of some smaller piece of apparatus, it is always best to make a full-sized drawing, unless, of course, a blue print is available. By doing this you avoid any possibility of making mistakes in the positions of holes and so on which you may very easily do when taking your measurements off small drawings. Even the blue print will not be completely satisfactory unless you are using exactly the same components as those with which it is

made. Should you already have components in stock that you propose to use, make a full-sized drawing and cut out paper patterns exactly the size of the bases of these components. You can then move your paper patterns about on the drawing until you find the best positions for fitting them in. A full-sized drawing is very easily made with the aid of a drawing board, a T-square, and a foot-rule. It need not be a beautifully finished piece of work so long as its dimensions are correct.


A beginner at constructional work is often rather at a loss when it comes to marking out ebonite panels. The first thing to do is to cut the panel absolutely square with perfectly straight edges and right-angled corners. This may be done with the help of a set-square and a medium file. There are three quite distinct methods of marking out, each of which has much to recommend it. Perhaps the best of all, at any rate for those who have not had much practice in the workshop, is this. Take a piece of thin white paper and stick it on to the panel with stickphast or some other adhesive. Press the paper well down round the edges and trim it off with a pair of scissors or a sharp knife. Now make use of the set-square and a pencil to do the marking out. When you have got the positions of their centres mark each with a centre punch, and then wash off the paper. In this way there is no chance of injuring the panel by



Quality RADIO

COMPONENTS

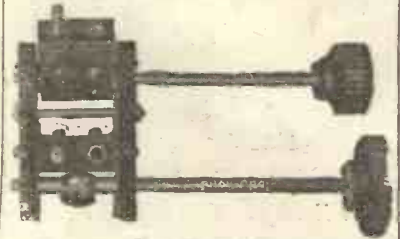Profusely illustrated twelve page CATALOGUE just out. If your dealer cannot give you one send us a card with his name and address to receive it direct FREE and POST FREE.



Prov. Protected.

CAM-VERNIER COIL HOLDER

Price 9/- on base 1/- extra. With Reaction Reverse and Shorting Switch incorporated, 12/6. Postage 4d.



LEGLESS VALVE HOLDERS 1/6 post 2d. Acts as



own drilling jig.

FASKET COIL HOLDER

1/3 postage 2d.




PANEL COIL HOLDER

(no base)

Back connections eliminating flex. 2 way 3/-, 3 way 5/-, N.P. 1/- extra.

Post 3d

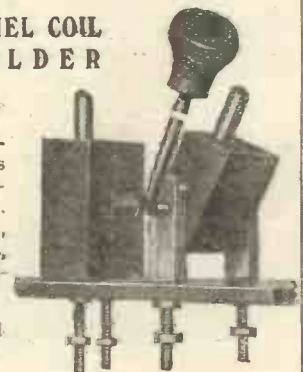

Drilling template with all.

If your dealer has not got them we send post free if you mention his name and address.

GOSWELL ENGINEERING CO., LTD.,

12a, PENTONVILLE RD., LONDON, N.1.
Liberal Trade Terms. Phone: North 3951.



Burndept coils for long-distance short-wave reception

MANY experiments have proved that stations transmitting on short waves can be received at very great distances, and this year more wireless enthusiasts than ever are building receivers for short-wave reception. Burndept Coils are ideal for use in such instruments because their high-frequency resistance and self-capacity are extremely low. The efficiency of Burndept Coils is well known. The complete range covers all wavelengths from 80 to 25,000 metres. The spring socket fittings of Burndept Coils are non-reversible and make perfect electrical contact.


- Set of 4 Extra Short-Wave Coils (8-150 metres) .. 16s.
- Set of 4 Concert Coils (150-800 metres) .. 16s.
- Set of 9 Coils, S. 5 to 1,000 (750-20,000 metres) .. £3 16s. 6d.

Prices of single Coils on application.



Write for full particulars of the newly-designed Burndept Wireless apparatus to Head Offices or to the nearest Provincial Branch:—LEEDS: 12, Basinghall St. (near City Square); CARDIFF: 67, Queen St.; NORTHAMPTON: 10, The Drapery.

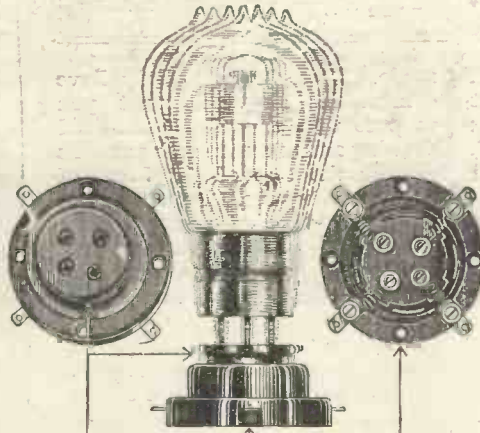Mr. John Scott-Taggart, F. Inst. P., A.M.I.E.E., writing about the Anti-Phonic Valve Holder in the "Wireless Weekly," said, "I consider this new component as an example of enterprise which is curiously lacking in the industry to-day."



SHOWING TOP OF VALVE HOLDER WHICH FLOATS ON SPRINGS


UNDER VIEW SHOWING SPRINGS SUPPORTING VALVE HOLDER PROPER

The Anti-Phonic Valve Holder.

THE Anti-Phonic Valve Holder prolongs the life of any type of valve and eliminates the microphonic noises usually associated with the dull-emitter type. In the long run, the use of this component means less expenditure on valves. As will be seen from the above illustration, the valve holder proper is insulated from mechanical shocks by a four-point spring suspension. The centre sketch shows how a valve vibrates at a touch of the finger. The valve sockets are countersunk, so eliminating the risk of short circuits, and there is no capacity between the sockets, as there are no nuts on them.

The advantages of fitting Anti-Phonic Valve Holders are many, and for use in portable sets they are ideal.

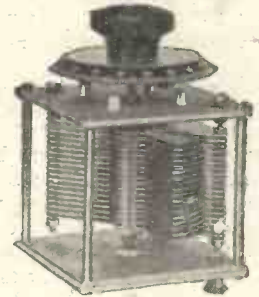No. 401. Anti-Phonic Valve Holder, diameter 2½ in., height just over 1 in. For panel or base mounting. In carton, with screws, 6s.



Burndept Standard Condensers

THE actual capacity of Burndept Standard Variable Condensers is guaranteed to be within a very small percentage of the stated capacity, and of the power applied to them only 0.05 per cent. is lost. Tuning is very sharp and signal strength greatly increased when these efficient condensers are used. Slight wear is automatically taken up without the capacity of the condenser being changed. The movement is very smooth. Steel snap-on dust covers eliminate hand-capacity effects. The upper illustration shows a Standard Condenser without dust covers and the lower illustration, with them.

BURNDEPT STANDARD CONDENSERS

- No.417, capacity .0005 mfd., £1 2s. 6d.
- No.417, capacity .001 mfd., £1 7s. 6d.



BURNDEPT LTD.

Aldine House, Bedford Street, Strand, London, W.C.2.

Telephone: Gerrard 9072. Telegrams: Burndept, Westrand, London.



scratching it, and marking out can be very neatly and accurately done. The second method is to use a lead pencil for marking on the ebonite itself. This is not completely satisfactory for two reasons. In the first place the graphite of which pencil "leads" are composed is a good conductor of high-frequency current, and unless it is entirely removed, the set may not work properly. Secondly, it is not easy to see pencil marks on ebonite in certain lights, and they may become blurred or obliterated by handling. If you wish to use a pencil for marking directly on to the ebonite, do so before removing the shiny outer surface. You are then certain of getting rid of all the graphite when the finishing process takes place. The third method is to make use of a scribe. When this is done marking out should always take place on the underside of the panel, for if it is done on the top the removal of the scratches will be found to be a very laborious business.


In the last paragraph the removal of the polished surface of ebonite was mentioned. It

is essential to do this unless you are using some brand which is guaranteed to have a non-conducting surface. Much of the commercial ebonite on the market receives its high polish by being pressed between sheets of tin foil. In the process some of the metal is apt to adhere to the ebonite, making the surface leaky. The best way of removing the gloss is to use a piece of the finest emery cloth which has previously seen a good deal of wear. New emery cloth is too keen and is apt to make deep scratches. Wrap it round a large flat cork and work over the panel in one direction only, that is, don't go first of all straight away from you and then from side to side. A very little labour will suffice to remove the polish and the panel may then be finished up in the following way. Make a piece of rag into a pad, moisten it with oil and sprinkle it with knife powder. Then work it in the same direction as the emery cloth was worked. When the process is completed wash the panel well to ensure that all fragments of emery and of knife powder are removed. To show how serious are the effects of allowing

the glossy surface to remain, let me mention the results of some tests made recently with various samples of ebonite just as they came from the shop. The method used was to drill pairs of holes an inch apart into which terminals were inserted. A "Megger" (insulation tester) was then attached to the terminals and the insulation resistance read. Of four samples the best resistance found was just under one megohm and the worst rather less than 30,000 ohms. A set made up with ebonite of this kind could never have worked satisfactorily, since there would have been high resistance leaks everywhere between valve legs, terminals and so on. The same tests were repeated with the glossy surface removed, and in every case an "infinity" reading was obtained.

I warned you in an earlier paragraph against attempting to use wood screws in ebonite. Metal screws of the B.A. sizes should always be used, holes for them being threaded with a tap. It is possible to drive metal screws into ebonite by making the holes for them two sizes less than the clearance size. Drilling sizes, by

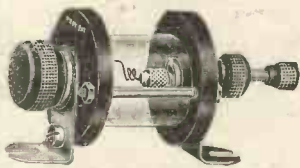The "MIC-MET" (micrometrical) (Regd.) CRYSTAL RECTIFIER



Patent
No. 221943.

British Manufacture.

100% Greater Efficiency

A PERFECT DETECTOR

Recommended on high authority as the pre-eminent detector, and we have had hundreds of unsolicited testimonials as to the perfection of this instrument since placing it on the market. The simplicity of this instrument in adjusting and the result obtained is so perfectly obvious that detailed explanation is unnecessary.

A BOON TO CRYSTAL SETS

To be obtained at most Wireless dealers or for
6/- Postal Order from


C. & J. ARRIGONI & CO., LTD.

8, Compton Passage, Compton Street, Clerkenwell,
LONDON, E.C.1.

Clerkenwell 2985.

FIT INDEPENDENT VERNIERS

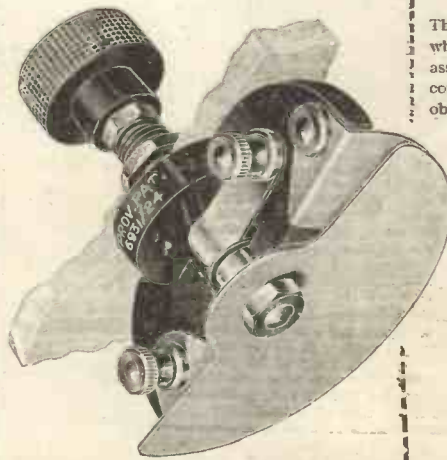The slight variation of capacity when large maximum condensers are employed heterodynes the incoming signal. It would seem that blame is attachable to tight coupling of coils: but you have only to fit the COLVERN to realise that heterodyning happens simply because the large condenser is unwieldy and does not permit the accurate tuning of circuits.



The type of Condenser which fits a vernier in association with the large condenser defeats the object of fitting a vernier.

The low maximum of any vernier is adversely affected by capacity effects, and any vernier which is employed to give fine tuning MUST NOT be in association with the main tuning condenser.

PRICE
2/6

The design of the COLVERN is thoroughly practical. The main structure is moulded from high insulating material. Over-all size is as small as convenience allows. The two plates are dead flat and edges are finished to minimise brush effects. Contact is positive upon centre spindle. The particular design of the COLVERN removes all possibility of bad contact.

For Stabilising Condensers in Neutralising Circuits, see you fit a COLVERN.

COLLINSON'S PRECISIONS REW CO., LTD.

Macdonald Rd., Walthamstow, London, E.17, Tel: Wal: 532.

the way, are a purely arbitrary series, running from 1 to 60. The clearance size, for example, for a 4 B.A. screw—this is the screw most commonly used in wireless constructional work—is No. 26. By making a hole with a No. 24 drill and going carefully, a screw can be turned straight in without any tapping. The process is made easier if turpentine or oil is used as a lubricant. For tapping we require to drill holes a good deal smaller than those through which the screw will pass easily. The tapping size for 4 B.A. is No. 34. The tap to use is of the type known as second cut. Many people think that threading holes is a difficult business. This is probably because they have never tried to do it. If you arm yourself with a tap fixed in a wrench and a few odd pieces of scrap ebonite, you will find that a very small amount of practice enables you to tap holes most successfully.

* * *

One of the wireless constructors' most important allies is the breast drill, with whose help he can make in ebonite or brass any hole required for wireless work. When you are buying a breast drill get

the best that you can obtain. It is very poor economy to pass by a really good drill and to purchase something inferior for a couple of shillings less. A badly made breast drill is a source of endless trouble, for its bearings become loose after a little while and the jaws of its chuck are too soft to stand up properly to the work that they have to perform. When it has been in use for some time they refuse to grip the drill tightly and you may have quite an amount of trouble in getting the drills correctly centred up in them. Exceedingly good work can be done with a breast drill if one takes proper care. Never try to make a hole in ebonite or brass without first of all making a punch mark to indicate its centre. If you omit this precaution the drill will probably slip, with the result that when the hole is made it will be slightly out of place. See that the drill is vertical as it goes in, and do not exercise too much pressure. If you push too hard upon the handle the drill on coming out on the underside of the panel will break away small pieces of the ebonite, making a rough, ragged-looking hole. Don't turn the crank too fast. Ebonite

demands medium speeds. It heats it rapidly if the drill is turned too fast, to the detriment both of the drill and of its insulating qualities. The smaller drills may be run through very quickly, but the larger ones, such as those $\frac{3}{8}$ in. in diameter, required for making the holes for condenser and rheostat spindles, must be allowed to do their work quite slowly.

DO NOT MISS THE
GREAT CHRISTMAS NUMBER
OF

“MODERN WIRELESS,”


Published 1st December,
price 1/6.

Among other special features of this issue will be a description of Mr. John Scott-Taggart's new T.A.T. receiver, using two stages of high frequency—a set of remarkable sensitivity.

MANY NOVEL FEATURES
by well-known Experts.
ORDER YOUR COPY EARLY!

BRETWOOD
GUARANTEED

Anti-Capacity Valve Holder

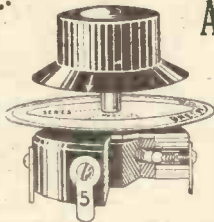

We have pleasure in presenting another first-class speciality, which is the outcome of the famous BRETWOOD ANTI-CAPACITY VALVE HOLDER, which has gained such popularity among the wireless public on account of its scientific design and smart appearance. The Bretwood Switch is constructed on similar lines and we

claim that it is like the Valve Holder absolutely free from capacity effects and we feel confident that this component will meet with the most exacting requirements of the present day experimenter. One of the principal features of the Bretwood Switch is its beautifully smooth action, made possible by the spring loaded balls and the wiping or rolling motion of the Phosphor-Bronze balls always insures clean and perfect electrical contact.

- Features. 1. Absolute freedom from capacity. 2. Perfect contact. 3. Sweet and smooth action. 4. Practically no wear and tear. 5. First-class finish and neat in appearance. 6. Easy to fix (one hole fixing). 7. Very easy to make wire connections. 8. Like our other components it is fully guaranteed. 9. For value offered the price is moderate.

Price
5/-


Postage 3d.

THE “BRETWOOD” PATENT VALVE HOLDER.

Fifty per cent. of your poor reception is caused by faulty valve holders, shooting through dampness, and poor material used, and other reasons.

Eliminate all these troubles by adopting the latest scientific invention of Radio Improvements, Ltd., i.e. the Bretwood Valve Holder. From the design it is evident that there is absolutely no capacity effect, as the metal parts have been reduced to a minimum, contact with valve legs being effected by $\frac{1}{8}$ in. steel balls, which are held in position by powerful steel springs, ensuring a sweet action, a firm hold and yet gently yielding; the balls effectively wipe over the surface of the pins.

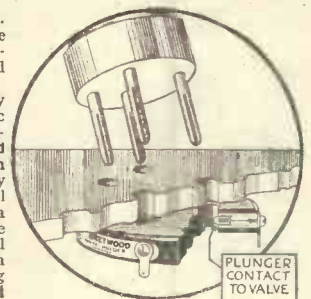Features. The valve is mounted flush to panel. Easy to fix. No capacity. No leakage. Always perfect contact. Saves space on panel. Can be mounted on front or back of same. Impossible to short-circuit valve when inserting same. It affords convenient method of wiring. No soldering necessary. Fit the “Bretwood” Anti-Capacity Valve Holder and obtain 100 per cent. efficiency.



Price
1/9

Postage 3d.



Patent Pending.

IT'S THE LEAK THAT DOES IT.

The “Bretwood” Grid Leak (Guaranteed) tunes a carrier wave from the silent point up. The “Bretwood” is recognised by highest experts and experimenters as the only variable and reliable Grid Leak.

Price
3/-

Postage 3d.

RADIO IMPROVEMENTS, LTD.,
12-18, London Mews, **BRETWOOD** GUARANTEED Maple St., London, W.

All BRETWOOD specialities are

obtainable from most Wireless Dealers.



When the Beginner Buys a Valve.

By R. W. Hallows, M.A.,
Staff Editor.

ONE of the first difficulties which confronts the beginner is to select a valve suitable for his receiving set. I do not know exactly how many different receiving valves there are available at the present moment, but the number is certainly a large one, and as each of them is, of course, "the best," the beginner's task is apt to be rather bewildering. To start with, he must decide whether he is going to use an accumulator or dry cells for heating the filaments.

Choice of Batteries

On this point let me say that if you can possibly use an accumulator do so, for, though dry cells will give passable results, no receiving set will work quite as well with them as with a secondary battery. The reason is that a dry cell of good make starts with a voltage of usually rather more than 1.5 across the cells, and that as soon as it is brought into use its voltage begins to fall off because the resistance within the cell increases

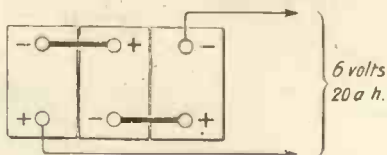


Fig. 1.—3 cells connected in series to give 6 volts.

as current is taken from it. This means that at the end of, say, a couple of hours' use the voltage of the filament battery has decreased to an extent which depends upon the amount of current drawn from it. Reception has, therefore, been growing slowly less and less good, though its decline and quality is so gradual that it is hardly noticeable. If the battery is given a good rest before being brought into use again, it will pick up until it almost reaches its original voltage. Then as it delivers current to the

filament its E.M.F. will fall off until at the end of the second period of two hours it is rather lower than it was after the first. And so it goes on falling off and picking up as it is worked and rested, until finally a point is reached at which it cannot supply the necessary voltage. With an accumulator things are quite different.

Accumulator Voltage

Almost as soon as it is brought into use the voltage falls to a value of approximately two volts per cell, and it remains there without any further drop until the battery is almost discharged. Then it declines rapidly and provides a sure indication that a visit to the charging station is necessary. If you live in the depths of the country where it is impossible to get accumulators charged, then you must perforce decide upon dry cells, ; but supposing that you can get charging done, even though it may entail a little inconvenience, then plump for the accumulator in preference to the dry battery.

Actual Capacity

Now with a six-volt accumulator you have the voltage necessary for operating any ordinary type of receiving valve. Your choice here will be covered only by the capacity of your battery and the number of valves that you desire to use. The capacity of the battery is reckoned in ampere hours, and for wireless purposes we require to know not the intermittent or ignition rating, but the *actual* capacity. The actual capacity is half the intermittent.

Discharge Rates

The safe discharge rate for any well-made accumulator is on the average about one-tenth of its actual ampere hour capacity. Thus we can take two amperes from a

20 a.h. accumulator, five from a 50, and so on. If you already possess, or contemplate buying, a 20 ampere-hour accumulator, then the maximum amount of bright emitter valves that can be used with it is three, and it will be best not to use more than two. Most bright emitters have a filament current consumption when new of about 7 ampere. Should you desire to work a four or five-valve set from an accumulator of the size mentioned, it will be best to go in for valves of the low-consumption type with a rating of not more than .4 ampere apiece. Or, again, we may make certain alterations in your accumulator.

Battery Connections

The cells are usually connected in series as shown in Fig. 1, so that the voltage at the terminals is six. If, however, the connections are made by means of metal strips fixed to terminals, it



Fig. 2.—3 cells in parallel to give 2 volts for dull emitters.

is quite easy to alter them in the way shown in Fig. 2, so that they are in parallel, in which case the voltage will be two, but the rating of the battery in ampere hours will be practically trebled. With the battery arranged in this way you can make use of low-voltage dull emitters such as the D.E.R., the A.R.D.E., the L.F. Ora, the Cossor "Wuncell," and the B.T.H. B3, all of which require between 1.6 and 2 volts and consume from .3 to .4 ampere. These are all robust and efficient valves, very long lived

owing to their comparatively stout filaments and to the low temperature at which they work. There are, again, valves with still smaller requirements such as the Wecovalve, the One Volt Ora, and the Dextraudion, all of which can be used economically from a two-volt battery. Any of these last three will also function with a single dry cell for filament heating purposes. As both the Wecovalve and the One Volt Ora draw .25 ampere, it is desirable that the single cell, if used, should be of large size; a quarter of an ampere is too great a load for any small dry cell to stand up to for more than a short period on end. The Dextraudion, which consumes only about .1 ampere, can be worked satisfactorily off a single bell cell of good make.

Dry Battery Valves

I think, though, that the man who must necessarily use dry cells for providing his low-tension current would do best to confine himself to valves of the "06" type. These are the D.E. 3, the D.F. Ora, the A.R. 06, and the B. 5. All of these require a filament potential of between 2.5 and 3 volts, and take a current of only 60 milliampere. (A milliampere, by the way, is a thousandth of an

ampere.) They, therefore, place a very small strain upon dry cells and can be worked quite well with three of them in series provided that a rheostat with a maximum resistance of about 30 ohms is used.

All of the valves previously mentioned are of the "general purpose" type, that is they can be used in any part of the set and will give good results there. The general purpose valve is most convenient since only a single spare need be kept. If a valve in any part of the set goes wrong the spare can be used to replace it without detriment to results. The beginner would, I think, be well advised to confine himself to general purpose valves, to start with at any rate. Having decided upon the type of valve he requires to suit his purposes, he will not go wrong if he purchases one made by any reliable and well-known firm of makers.

Buy Good Valves

In valves, as in all other wireless goods, you get what you pay for. It is therefore a poor kind of economy to "save" a shilling or two by purchasing cheap or foreign made valves which are usually very greedy in their current requirements, unstable in use, and short lived.

Special Valves

Later on, when the beginner has learned something about the way in which valves work and has had some experience of handling them, he may go in for special valves, such as those designed to function solely as either high-frequency amplifiers or rectifiers. When he is no longer satisfied with head telephones and yearns for a loud-speaker, he may take to the power valve for low-frequency amplifying purposes, and here he will find something to match, in its requirements from the low-tension battery, valves which he already possesses. Such is the range of small-power valves nowadays that whether you use in the rest of the set bright emitters, low-voltage dull emitters or "06" valves, you can obtain a power valve operating at about the same filament voltage and drawing only a little more current from the battery.

ANOTHER
FREE
BLUEPRINT
NEXT
MONTH!

Greco TRADE MARK

A SELECTION
of GUARANTEED Components which are indispensable
To EVERY CONSTRUCTOR.



Highly finished
VALVE WINDOWS.
Another of our products
which has met with
UNIVERSAL APPROVAL.
Brass 3d. each Post 1/2d.
N.P. 4d. "
B.L. Nickel 5d. "



Our famous "CLIP IN"
CONDENSERS guaranteed
ACCURATE. Each is calibrated
after being made. Post 2d.
Mfds. Unmounted Mounted
with clips. as illus.
.0001 to .001 1/9 2/3
.0015 to .03 2/9 3/3



Panel mounting
CGIL PLUGS.
Complete as illustration
Heavy brass parts.
1/3 each. Post 1/4d.



**PANEL MOUNTING
KNIFE SWITCHES**
Best finish, Polished
brass or N.P. S.P.S.T.
1/- Post 1/4d.
D.P.D.T. 1/6, Post 1/4d.



Rewind your own Telephones
Magnet slot. 3/8 x 5/64.
1000' phone 1/-. 2000' phone 1/6
Post 1/4d.

BOX SPANNERS.
Fits all nuts, 2 to 6 B.A.
All inaccessible nuts can be
tightened by their use.
8d. set of 2. Post 2d.



VALVE STAMP. Hardened
points. A most useful
accessory, 1/-, Post 2d.
Have you seen a copy of
our 124 page Catalogue
(1,500 illustrations)
Post free 3d.?

Telephone: MUSEUM 241 Works: SLOUGH

ELECTRIC GRAFTON COMPANY

GRAFTON STREET, TOTTENHAM COURT ROAD,
LONDON.

**The discovery that
doubles your range**

When W. Bennison, F.C.S., and T. Hadley, B.Sc., after long study of the characteristics of minerals in wireless practice, evolved this new crystal, they opened up a new field to Crystal users. Neutron has, in many cases, been found to produce volume of sound equal to a valve without react on. It brings your local station "twenty miles nearer" in volume, and many long-distance records are to the credit of Neutron

A Nottingham correspondent writes:
"I wish to thank you for the crystal, and find it gives wonderful results. I have recommended your crystal to a number of my friends, and they also speak very highly of the clear reception they obtain from same. Excels all other makes. Wishing you every success."
H. B., Nottn.



1/6

Concert Tested & Guaranteed

NEUTRON

TRADE MARK

NEUTRON, LTD., Sicilian House, Southampton Row, London, W.C.1. Phone: Museum 2677.
Sole Distributors: V. ZEITLIN & SONS, 144, Theobald's Road, London, W.C.1. Phone: Museum 315 and 1841.



The Fynetune
Gives
**HAIRSBREADTH
ADJUSTMENT TO
CONDENSERS ETC.**
Three Minute-One Hole Fix

HEIGHT ABOVE PANEL 2 1/2"
TOTAL LENGTH 1 1/2"



ALL BRITISH GOODS FULLY GUARANTEED.

"Fynetune" Micro Adjuster Improved model is perfection. No backlash, increased ratio, 2/6, post free.
"Radiohmite" Crystal. Speaks for itself A.1 for Reflex. 1/6 per box, post free.
2/- with 3 Catwhiskers.
Flush Panel Mounting Valve Sockets with tags. 6d. per set. Post 1 1/2d.

SPECIAL LINES
"Radiohm" Ribbon Aerial, used by American Amateurs. 3/- per 100 ft. on reel. Post 5d.
Engraved 2 B.A. Pillar Terminals, Gold Lacquered. Aerial, Earth, Phones, Phones+, L.T., L.T.+; H.T., H.T.+; L.S., L.S.+; G.B., G.B.+; A., A.1, A.2, B., C., E., D. 3/6 per doz. Post 3d.

"Radiohm" Bus Bar. The original and still the best. Don't buy soft shoddy stuff on reels. 1 doz. 2 ft. lengths, with tags 2/- Post 3d.
Spade Tags, C. and U. shape. 3d. per doz. Post 1 1/2d.
Micro Filament Control. The perfect Resistance for all types of valves. 3/6. Post 2d.

All parts for Receivers described in "Wireless Weekly" and "Modern Wireless." Send for particulars.
SPARKS RADIO SUPPLIES,
43, GREAT PORTLAND STREET, LONDON, W.1. Telephone—Langham 2463.

"GOLTONE" (Regd.)


"GOLTONE" LOW FREQUENCY TRANSFORMERS.



Unsurpassed for silence, efficiency and reliability. Provides remarkable amplification with freedom from noise and distortion. Equally suitable with every type of valve. No make of Transformer gives better results.
Price 17/6.

THE BEST OF ALL CIRCUITS

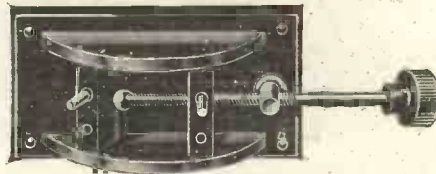is of little value if your components are inefficient. The use of the "Goltone" (Regd.) Transformer, combined with our "Goltone" (Regd.) Micrometer Coil Holder, ensures the maximum possible results.



"GOLTONE" MICROMETER REGULATING COIL HOLDERS. (P. Patent)

A high-grade instrument. Enables the finest possible tuning and considerably increases the selectivity, reliability and efficiency of the receiving set.

- TWO COIL TYPE 9/- each.
- THREE COIL TYPE 12/6 each.

Constructional Wireless Receiving Sets



British Made.

These sets are dispatched with ready-drilled Panels, Assembled Condensers, Wound Transformers, enabling the set to be quickly constructed with ease and simplicity. Full instructions supplied.


- TWO VALVE PANEL, £5 5s. Plus Marconi Patent Royalties, 25/-.
- THREE VALVE PANEL, £6 11s. Plus Marconi Patent Royalties, 37/6.
- FOUR VALVE PANEL, £8 17s. Plus Marconi Patent Royalties, 50/-.
- FIVE VALVE PANEL, £12 10s. 6d. Plus Marconi Patent Royalties, 62/6.



Address all communications to Head Office and Works: **PENDLETON - MANCHESTER**
Stocks also held at Glasgow Depot, 95, Pitt Street.

"GOLTONE" WAVE-TRAP.

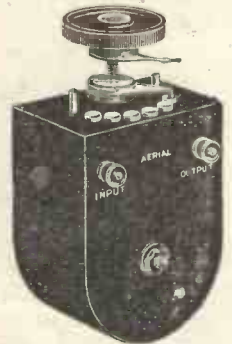An extremely effective instrument for eliminating signal interference up to 600 metres wavelength. Can be easily attached without any alteration to the actual wiring. No. R5/750, 12/6 each. Variable condenser for use in conjunction with above Wave-Trap, .0005 mfd., 6/- each.



"W. & G. EASIFIX" HIGH & LOW TENSION CABLE ASSEMBLY.



64 in. long over all.

Eliminates all ugly loose wiring and minimises the risk of burning out valves. Each conductor is distinctively coloured and enclosed within an outer braiding. Complete with Wander Plugs. Price 3/- Packed in attractive carton. RADIO WIRES of every description, including silk, cotton and enamelled instrument wires, aerial wires, telephone receiver and loud-speaker cords, etc. Keen prices.

Fully illustrated 32 pp. Catalogue, containing full particulars of Crystal and Valve Sets, and Component Parts of every description, post free on request. Enclose Business Card for Trade Terms.

These Lines are stocked by all High-Class Radio and Electrical Stores. Write direct if unobtainable.

MAGNIPLEX GETS CAPT. ECKERSLEY IN NEW YORK ON ONE VALVE.

At 2.48 a.m. on 17th October a user of MAGNIPLEX AERIALS attached to one valve set, in London, distinctly heard Capt. Eckersley speaking in New York and received his broadcast invitation to visit 2LO. This invitation was promptly honoured with great courtesy by the British Broadcasting Co., Ltd., at 2, Savoy Hill.



High tensile phosphor-bronze wire gauze. "Strong as Steel."

Patent Applied for.

If your dealer does not stock them, send direct to us.

Guarantee:—If you are not satisfied that MAGNIPLEX AERIAL is worth the additional cost, return it in good condition and your money will be refunded.

Prices:—3/4 in. wide 3d. per ft.; 1/2 in. wide 2d. per ft. Supplied in lengths of 50, 75, and 100 feet, including fittings, viz.: End Terminal for Down Lead and Insulators ready for erecting. For lengths under 50 ft. fittings charged 1s. 3d. extra. Postage and packing free.

HELIXO LTD., HENRY BUILDINGS, GRESSE STREET, RATHONE PLACE, LONDON, W.1.
Phone: Museum 6039.

WATCH THIS SPACE FOR ADDITIONAL "MAGNIPLEX" RESULTS NEXT MONTH.



Adding a Valve to a Crystal Set

By E. REDPATH.

An instructive article of particular interest to all readers who contemplate improving the performance of their crystal sets by the addition of a valve.

"MINE is only a crystal set, and, although it has served its purpose quite well up to the present, I should like to obtain better results. What do you recommend?"

Although the above query could be answered in a few words by saying: "Add a valve as an amplifier," there are no doubt many readers to whom the matter is not as clear as the proverbial pikestaff and who desire to obtain further information on the subject to enable them to proceed.

In the present article, therefore, the writer will explain two simple

and practical methods of adding a valve to an existing receiving set either as a *low-frequency* amplifier, for the purpose of increasing the volume or strength of signals already received on the crystal set alone, or as a *high-frequency* amplifier, primarily to effect reception over a greater distance.

Low-frequency Amplification

At A, B, C and D (Fig. 1), are shown four typical crystal receiver circuits with the various components illustrated pictorially, so that readers unfamiliar with the conventional signs or "short-

hand" of wireless will have no difficulty in recognising them.

A—represents a single-circuit receiver, the aerial being tuned by means of a slider inductance coil, L.

B—represents a single-circuit receiver with variometer tuning.

C—another single-circuit receiver with fixed inductance L (usually a "plug-in" coil) and variable condenser C, by means of which the aerial tuning is varied.

D—an inductively-coupled receiver comprising an aerial circuit (A, C, L, E) and a "closed" or secondary circuit (L₁, C₁), the


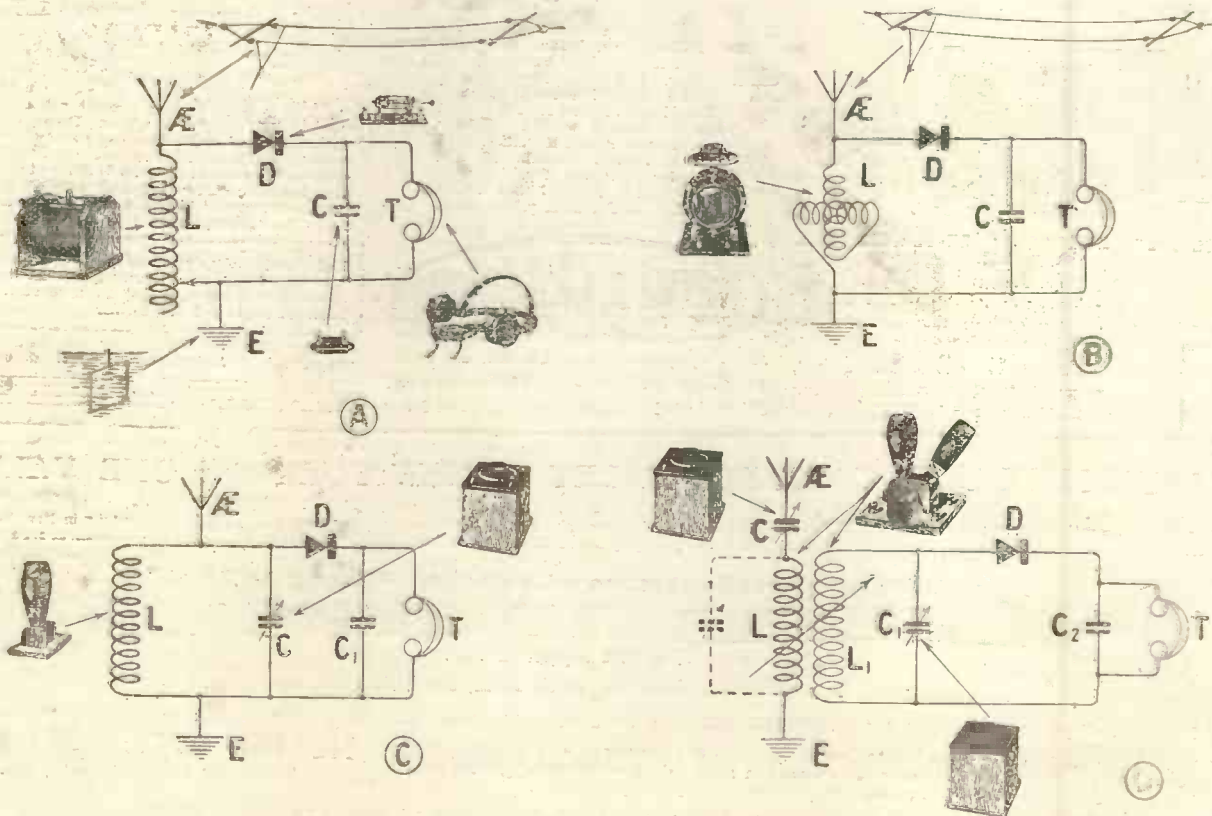


Fig. 1.—Four typical crystal circuits with pictorial representation of the components.

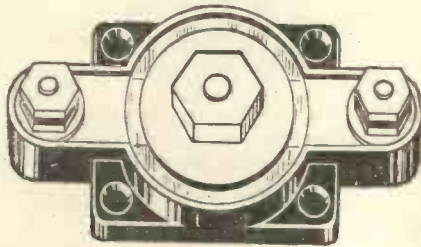

FINSTON FIXED CONDENSERS

are symbolic of Stonehenge because of the everlasting qualities which serve to make them immune from the most exacting and protracted use. They stand the test of time.




FEATURES:

Reliability of Capacity. Finest grade Mica Dielectric. Highest possible quality Copper Foil. Adapted for Terminal or soldered connections.

CAPACITIES:

.0001 to .001 Price 1/3 each.
.002 to .005 Price 2/- each.

PRICE
5/6

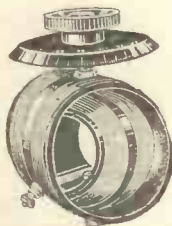

PRICE
5/6

FINSTON STANDARD VARIOMETER

Ebonite stator, high-grade ebonite moulding rotor, engraved dial and knob. Price, 5/6.

FINSTON SQUARE LAW CONDENSERS

Aluminium top and bottom plates, high-grade ebonite composition knob and dial, cleanly engraved 0-150. Values 93 per cent. pure aluminium.

.001	9/-	.0003	7/6
.00075	8/6	.0001	6/6
.0005	8/-	.00005	6/-

BRITISH WIRELESS EXHIBITION

WHITE CITY, NOV 15 to 29.

VISIT OUR STAND No 48

and see all Finston Specialities assembled.

If your local dealer cannot supply, send your order to us together with his name and address.

LIGHTING SUPPLIES Co.

2, FINSBURY AVENUE, LONDON, E.C.2

WIRELESS ON EASY TERMS!

GAMAGES have now extended their easy payment system to Wireless, and you may now secure on payment of first deposit, Wireless Sets and Apparatus from £5 upwards, balance being payable in monthly instalments. Write for details to Wireless Dept.

GAMAGES

The Premier Store for Wireless

Always first in such matters, GAMAGES are offering this famous Rectifier at a hitherto unheard of Price. The Production is of the highest Quality and carries the usual Gamage Guarantee of Efficiency.

GAMAGE "Compacto" RECTIFIER, at a Hitherto Unheard-of Price.

A wonderful Bargain, of which all real enthusiasts will avail themselves immediately.


To USERS OF VALVE SETS IN DISTRICTS served by ALTERNATING CURRENT Keep your batteries charged at home by this device.

The Cheapest, most Efficient and most Reliable means of charging Storage Batteries from an A.C. Circuit.


Charges 6 volt Battery at 2 amps. Consumes no more Current than the Average House Lamp.

Accumulators may be charged overnight ensuring Good Reception of Broadcast Concerts whenever required. Customers ordering this by Post are assured of satisfaction equal to that obtained by a personal visit. We refund your money in full, should goods fail to come up to Specification.

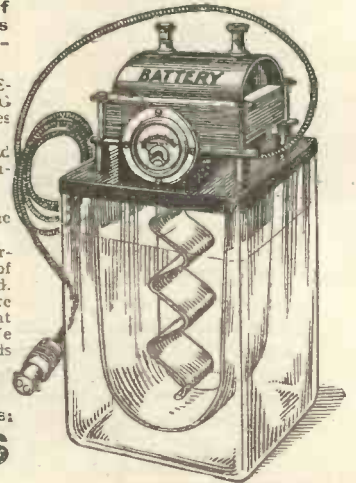Price with Ammeter Fixed **£2 10/-**
Cooling Tank, with Tap..... **10/6**



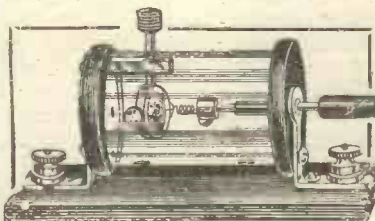
For Standard Voltages and Periodicity between 40-70 Prices quoted for under 40 and over 70 periods and for charging 2 and 4 volt Batteries. Please state Voltage and Periodicity when ordering.



Super Crystal Detector

The striking points about this new detector are the Revolving Crystal, and the silver Cats Whisker. All Brass Parts lacquered. New Crystal easily fitted. - Complete with Gamages famous "Permanite" Crystal.

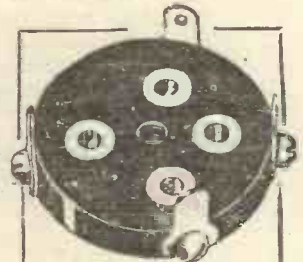Price for Panel Mounting **4/6** Price for Table Mounting **5/6** Post 4d. on each type.



The "Gamage" Under Panel Valve Socket.

STRIKING POINTS—Anticapacity; Positive Protection from burning out valves by incorrect fitting.

Low Price. Post 2d. Gamage-Price **10d.**

Gamages are Stockists for all the best makes of Wireless Sets and Apparatus and are always showing large stocks of Sterling, Bowyer Lowe and Radio Instruments.

GAMAGES, HOLBORN, LONDON, E.C.1.

Also at Benetfinks, Cheapside, E.C.2.

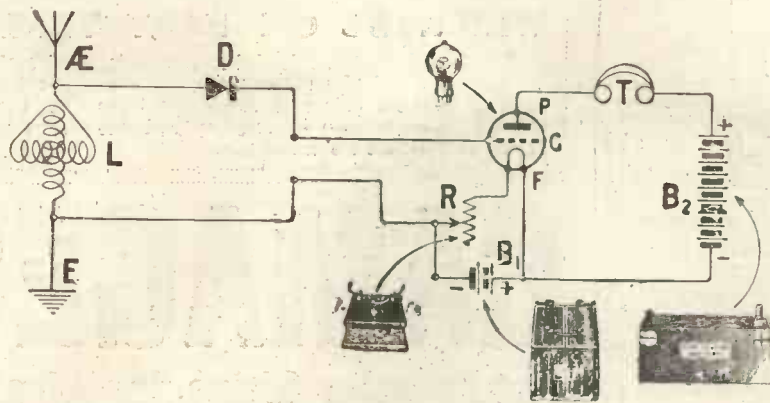


Fig. 2.—The simplest method of note magnification,

electro-magnetic coupling between the coils L and L₁ being variable, as indicated by the arrow drawn through them.

In each of the above circuits the crystal detector D and telephone receivers T (with more or less optional fixed condenser) are connected in series with one another across the aerial tuning inductance (as at A and B), or across the aerial condenser or secondary condenser (as at C and D respectively).

Your Own Arrangement

From inspection of the four diagrams of Fig. 1, the reader will be able to identify the arrangement of his own receiving set and, at the same time, he will notice that the connections of the detector and telephones are the same in each. The oscillatory currents set up in the aerial (or secondary) circuit are rectified by the crystal, and low-frequency pulses, due to the voice modulation at the transmitting station, flow through the windings of the telephones.

To any of these arrangements a valve can be added very easily. All that is necessary is that the low-frequency currents which normally traverse the telephone windings be applied to the grid-filament or "input" side of a three-electrode valve where they undergo amplifi-

fication and may be made to give considerably increased signals in telephone receivers connected in the anode or "output" circuit of the valve.

The Simplest L.F. Amplifier

Fig. 2 illustrates what is possibly

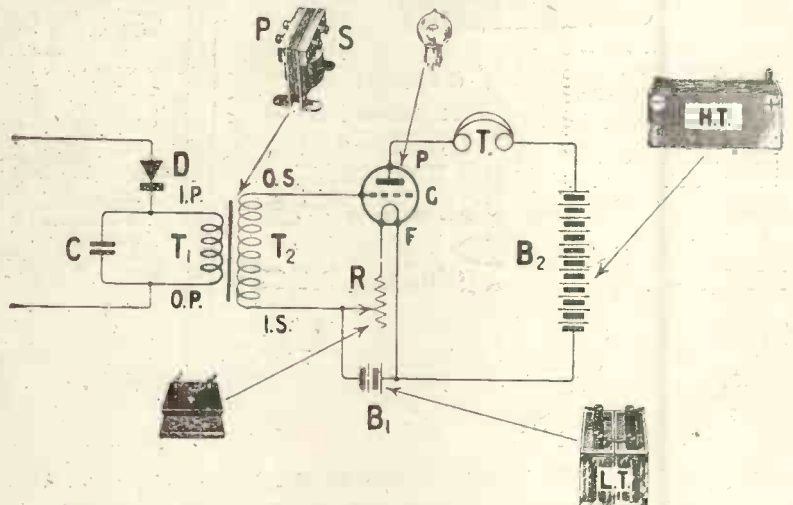


Fig. 3.—More efficient note magnification, using "step-up" transformer coupling.

the simplest application of this principle. The telephone terminals of an ordinary receiving set, with telephone condenser removed, are connected to the grid and negative

side of filament of a valve, whilst the telephones are connected between the plate or anode of the valve and the positive terminal of the high-tension or anode battery.

In this and all following diagrams depicting a valve, the reader should note the three essential "circuits" namely:—

1. The filament circuit, including the valve filament itself (F), the variable resistance (R) which controls the current flow and consequently the temperature of the filament, and the filament-lighting or low-tension battery B₁ (usually a four-volt accumulator).
2. The "grid-filament" or input circuit.
3. The "anode-filament" or output circuit, including the anode or plate (P), the high-tension battery B₂ with positive terminal always connected to the anode of the valve (in this instance via the telephone receivers T).

With the arrangement shown in Fig. 2, the low-frequency pulses of current which originally actuated the telephones now cause a variation of grid potential and consequently, due to the action of the valve, an amplified change of anode-telephone current.

A More Practical Arrangement

It is, however, a fundamental law of the three-electrode valve that the greater the change of grid potential, the greater will be the change in anode current—with in certain limits, of course, depending upon the type of valve, anode voltage, etc.

Accordingly improved results may be obtained by connecting the telephone terminals of the crystal set to the primary winding of a "step-up" transformer, the

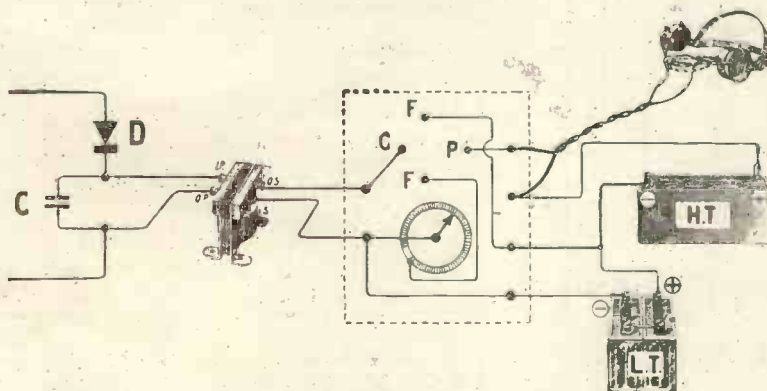


Fig. 4.—Pictorial and wiring diagram of Fig. 3 circuit.

READ THESE WELL-KNOWN RADIO PRESS BOOKS

The Radio Press Series.

No.		Price.
1	Wireless for All ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	9d
2	Simplified Wireless ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	1/-
3	How to Make Your Own Broadcast Receiver ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	1/6
4	How to Erect Your Wireless Aerial ... By B. Muttell, A.M.I.E.E.	1/-
5	The Construction of Wireless Receiving Apparatus ... By P. D. Tyers.	1/6
6	The Construction of Crystal Receivers... By Alan L. M. Douglas.	1/6
7	How to Make a "Unit" Wireless Receiver ... By E. Redpath.	2/6
8	Pictorial Wireless Circuits ... By Oswald J. R. ...	1/6
9	Wireless Valves Simply Explained ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	2/6
10	Practical Wireless Valve Circuits ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	2/6
12	Radio Valves and How to Use Them ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	2/6
13	500 Wireless Questions Answered ... By G. P. Kentall and E. Redpath.	2/6
14	12 Tested Wireless Sets ... By Percy W. Harris	2/6
15	More Practical Valve Circuits ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	3/6
16	Home-Built Wireless Components ...	2/6
17	Wireless Sets for Home Constructors ... By E. Redpath.	2/6
18	Tuning Coils and How to Wind Them ... By G. P. Kentall, B.Sc.	1/6

Radio Press Panel Cards.

1	How to Make the W.I. Receiver ... By Herbert K. Simpson.	1/-
---	---	-----

Radio Press Envelopes.

1	How to Build an S.T.100 Receiver ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	1/6
2	How to Build a 4-Valve Receiver ... By Percy W. Harris.	2/6
3	How to Build the "Simplicity" 3-Valve Set ... By G. P. Kentall, B.Sc.	2/6
4	How to Build the All-Concert-de-Luxe Receiver ... By Percy W. Harris.	2/6

Simplex Wiring Charts.

1	For 2-Valve Set ...	1/-
2	For 3-Valve Set ...	1/-
3	For 4-Valve Set ...	1/-



Radio Press Wireless Panel Transfers ... 6d

The Radio Press Envelopes are the most complete guide to wireless construction ever devised. They contain exact size panel and wiring blue prints, complete working drawings, sheets of instructions regarding construction and working, lists of components; and many photographs on beautiful art paper showing the set and wiring from every possible angle. Every possible detail is explained and you cannot go wrong.

Any of the above publications can be obtained from principal wireless dealers and through any bookseller—or direct (plus ad. postage) from Radio Press Ltd., Bush House, Strand, London, W.C. 2.

Special Activation Process OLDHAM ACCUMULATORS

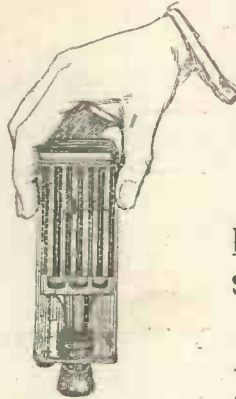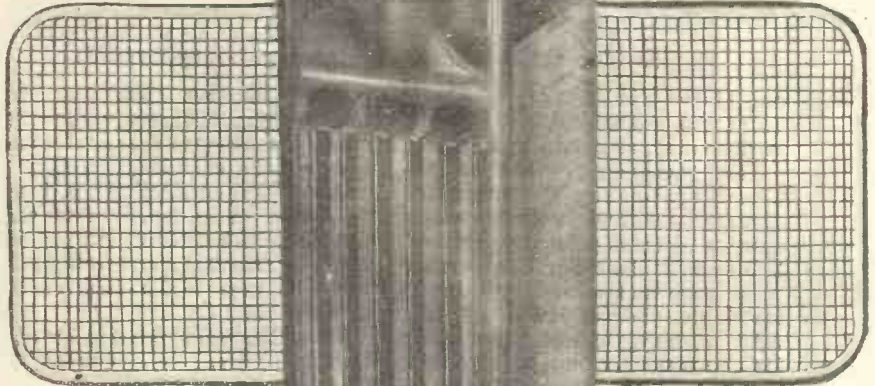London Depot :
Gt. Chapel St., Oxford St., W.1



Dealers: Write for full details of the Oldham proposition—you are missing a valuable amount of business if you are not stocking Oldham Accumulators.

Hold this new Portable Oldham upside down and the acid cannot spill

AT last here is a non-spillable accumulator that can be carried in the pocket without fear of the acid falling out and spoiling the clothes. Just the accumulator for Dull Emitter Valves. Of small size and light weight it is easily the most economical method of lighting Wecos, Wuncells, 1-volt Oras, and two of them in series are absolutely ideal for the .06 amp. type of Valve.

For Dull Emitters

**2 volts
10 amp. hrs.
(actual)**

12/-

Built from seamless celluloid of the highest grade with substantial terminal knobs, it is a typical Oldham product. Actually it is very similar to the accumulator used in the Oldham Miner's Electric Lamp—the most popular lamp in the country.

Its plates are manufactured under the same special activation process, which has the property of ensuring a longer life

and a greater ability to hold the charge when the accumulator is not in use. Remember that it costs only a few pence to charge it—that the charging can be done in a few hours—and that its absolutely constant output is preferable to any type of dry battery. Bearing these points in mind you will realise that the new Oldham Non-spill Accumulator is just the one for your Dull Emitter Valves.

Oldham & Son Ltd.—Denton, Manchester

Gilbert Ad. 1691

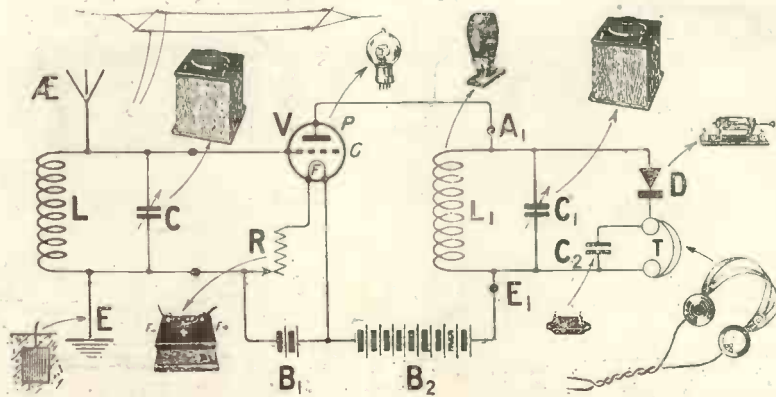


Fig. 5.—The valve used as a high-frequency amplifier.

secondary winding of which is connected to the grid and filament of the valve, as shewn in Fig. 3.

The "step-up" effect is obtained by winding the secondary of the transformer with a greater number of turns than the primary. If the ratio between the number of primary and secondary turns is too high, the variation of grid voltage may exceed the limit for the valve in use, so that the anode current does not vary in strict accordance, giving rise to distortion in the telephones.

Other Causes

There are other causes of distortion, however, and, as a result of much experimental work, several makers have evolved very satisfactory instruments, usually with a "step-up" ratio of 1 to 4, or 1 to 5. Frequently these figures are quoted the other way round, namely, 4 to 1, or 5 to 1, which, although really a "step-down," indicates the ratio between secondary and primary windings just the same.

A combined pictorial and wiring diagram of the Fig. 3 circuit is given in Fig. 4, in which the transformer is shewn with primary winding connected to the telephone terminals of any crystal receiving set.

Components Required for L.F. Amplifier

By means of the arrangement shewn in Fig. 4, the strength of signals may be increased some 4 to 5 times, and the items required are as follows:—

- 1 Iron-core Transformer of reliable make. Step-up ratio 1 : 5 recommended.
- 1 Valveholder.
- 1 Filament Rheostat.
- 1 Filament-lighting Battery. A 4-volt accumulator for bright-emitter valves; a 2-volt accumulator or dry-cells for dull-emitter valves, according to voltage recommended by the valve makers.
- 1 High-tension or Anode Battery, 40 to 80 volts.

Two Simple Rules

By careful observance of the following simple rules, readers who are about to handle valve ap-

paratus for the first time will avoid slight mishaps which may cause considerable annoyance and, occasionally, expense.

A.—When connecting up, insert the valve in its holder first, then connect the filament battery and turn the rheostat so as to light the valve. Connect the high-tension battery last.

B.—After using the set, turn the rheostat so as to *extinguish* the filament; remove both plugs from

the oscillatory currents *before* they are applied to the detector, so that signals which are too feeble to actuate the detector direct may be strengthened sufficiently to do so.

Two Tuned Circuits

Reference to the diagram will show that there are two tuned circuits, the aerial circuit LC and an additional closed circuit introduced between the anode of the valve and the positive terminal of the H.T. battery. The latter circuit, comprising the inductance L_1 and the variable condenser C_1 , is known as the tuned-anode circuit, and the crystal detector D and telephones T (with small fixed condenser C_2) are connected across C_1 , exactly as in a crystal receiving set. There is no need to disturb an existing set, provided that it can be tuned over the desired range of wavelengths without the usual capacity of the aerial.

Plug-in Coils

If the tuning arrangements of the original set comprise a plug-in coil and parallel variable condenser, it will be necessary merely to use a No. 50 or No. 75 coil instead of the

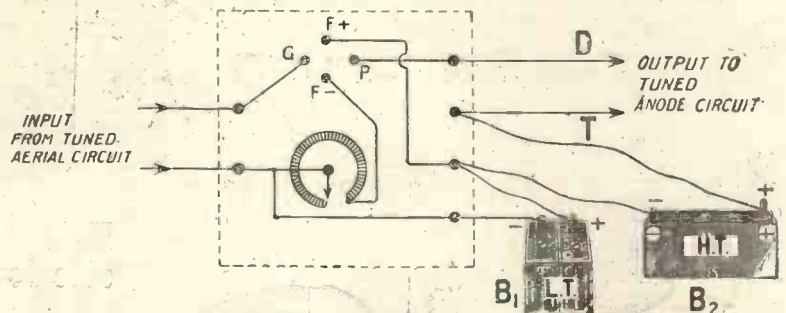


Fig. 6.—The valve connection of the Fig. 5 circuit.

the high-tension battery and disconnect one lead from the filament battery (*at the battery terminal*).

In some cases it may be found that the gain in signal strength is not what it should be. A reversal of the leads from the transformer secondary will probably put matters right.

High-frequency Amplification

A very effective method of employing a single-valve as a high-

No. 35, but if the set is of the type illustrated at A or B in Fig. 1, it will be necessary to connect a "compensating" condenser across the aerial and earth terminals in order to permit of tuning over approximately the same range of wavelengths as when the aerial was connected. A fixed condenser with a capacity of 0.0002 or 0.0003 μF will be found suitable.

Alternatively, the existing tuner (with crystal detector and telephone condenser removed) may be connected in the aerial circuit and to the grid and negative filament of the valve, whilst a plug-in coil in a fixed holder and a 0.0005 μF variable condenser may be purchased and connected at L_1 and C_1 respectively, the crystal and telephones being connected across C_1 as shewn in Fig. 5. The important point to note is, that when operating the complete arrangement, both the aerial and the closed

WIRELESS CONSTRUCTORS OF GREAT BRITAIN!

WE INTRODUCE TO YOU OUR 1925 EDITION,
50-page Illustrated Catalogue.

The most comprehensive Retail Wireless Component Catalogue yet published—backed by a smart postal delivery service, and a firm whose whole energies are devoted to supplying the Home Constructor.

IT'S YOURS FOR THE ASKING.

SEND A POSTCARD NOW TO
THE BRIGHTON RADIO STORES,
163, Western Road, Brighton.

Place your Set on



The FELMATIC Mat


And lose those microphonic noises due to the extreme sensitivity of modern valves. The FELMATIC mat eliminates these disturbances because the combination of insulating qualities of the specially prepared india rubber with the silencer qualities of the other special material used makes the FELMATIC ideal for the purpose.

Size.	Price.	Size.	Price.	Size.	Price.
12 1/2 in. x 11 1/2 in.	5/6	18 in. x 11 1/2 in.	8/6	24 in. x 11 1/2 in.	10/6

OBTAINABLE through your Wireless Dealer or direct from
C. W. CAVE & CO., LTD.
56, Gresham St., London, E.C.2.

Barclays 256

"UTILITY" VARIABLE SQUARE LAW CONDENSERS

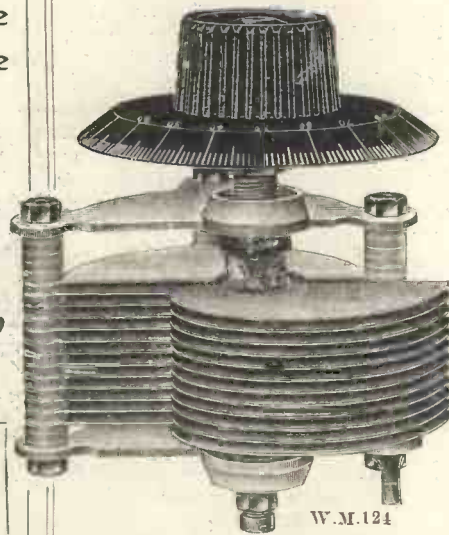

at
same price
as our
ORDINARY

PRICES.

Ref. No	Cap.	Price
WM.123	.001	12/6
WM.144	.00075	11/9
WM.124	.0005	10/6
WM.125	.0003	8/9
WM.145	.0002	7/9

Vernier 2/6 extra.

NO-CAPACITY


The "UTILITY" NO-CAPACITY SWITCH, as used in the constructional articles appearing in this journal.

Specially designed by electrical engineers to reduce the electrostatic capacity, this switch has proved to be exceptionally reliable in action and has self-cleaning contacts.

Size	Knob Type	Price
1 Pole Change over.	WM130/1	3/8
2 " " "	WM130/2	4/-
3 " " "	WM130/3	5/-
4 " " "	WM130/4	6/-
5 " " "	WM130/5	7/-
6 " " "	WM130/6	8/6

Size	Lever Type	Price
1 Pole Change over.	WM147/1	4/6
2 " " "	WM147/2	5/-
3 " " "	WM147/3	6/-
4 " " "	WM147/4	7/6
5 " " "	WM147/5	10/-
6 " " "	WM147/6	10/-

Nickel-plated, sixpence each extra.

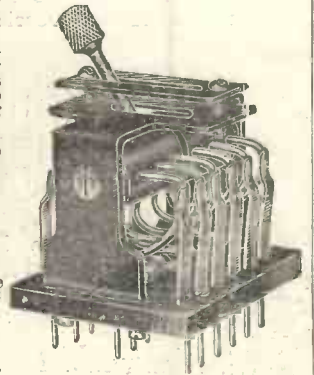

WM. 147/6.

SWITCHES

Manufactured by

WILKINS & WRIGHT LIMITED,
UTILITY Works, Kenyon Street, Birmingham.

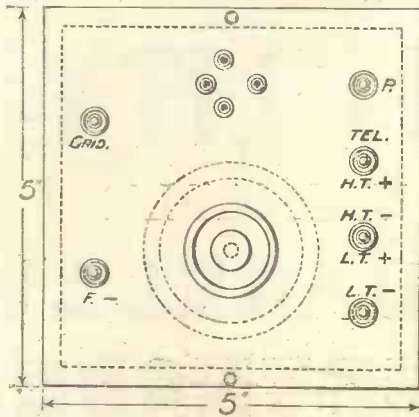


Fig. 7. - A suitable valve panel.

circuit must be tuned to the desired wavelength.

In the case of an inductively-coupled crystal receiving set, as illustrated at (D) in Fig. 1 for instance, the closed circuit $L_1 C_1$ will be suitably proportioned to cover the same wavelengths as the aerial circuit, and no com-

pensating condenser or other addition will be required. A set of this type lends itself very readily to the addition of a high-frequency amplifying valve, which, as shown in Fig. 5, acts as a kind of connecting (and amplifying) link between the aerial and closed circuits of the original set.

Possibly this will be understood more clearly on reference to Fig. 6, which indicates the "input" to the valve panel from the aerial circuit; the actual panel and battery connections; and the "output" to the tuned-anode circuit ($L_1 C_1$ of Fig. 5).

A Convenient Valve Panel

Figs. 7 and 8, a front view and "back-of-panel" wiring diagram respectively, illustrate the construction of an inexpensive, easily constructed and effective valve panel by means of which readers may experiment in both low and high-frequency amplification as explained in this article.

The materials required for the construction of this "panel" are

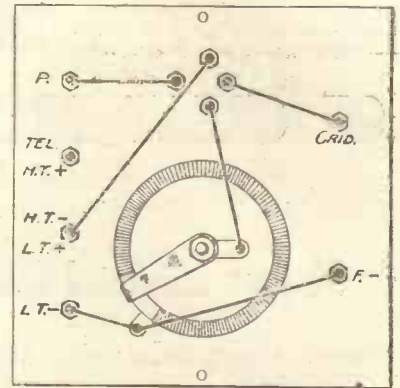



Fig. 8. - Wiring diagram for valve panel.

readily obtainable from almost any wireless dealer, and are as follows: One piece of ebonite 5 in. by 5 in. by $\frac{1}{4}$ in. thick; one filament rheostat; four valve sockets; six terminal; and a shallow containing box to carry the panel, or alternatively, four supports, such as cotton reels, one at each corner of the panel.

An Emergency Filament Battery.


If your accumulator should run down during an interesting programme, there is no necessity to miss the rest if you have a few pocket lamp batteries handy. The H.T. battery, if made up from such cells, may be robbed.

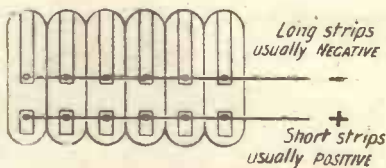As many cells as can be procured are connected up in parallel, *i.e.*, all the positives are joined together and connected to the L.T.+ terminal of the receiver, and the



negatives to the L.T.-. One pocket lamp cell of good make will last one valve if used carefully for about $\frac{1}{3}$ of an hour. The accompanying sketch shows such a makeshift L.T. supply ready for use.

Wireless in Cheko-Slovakia.

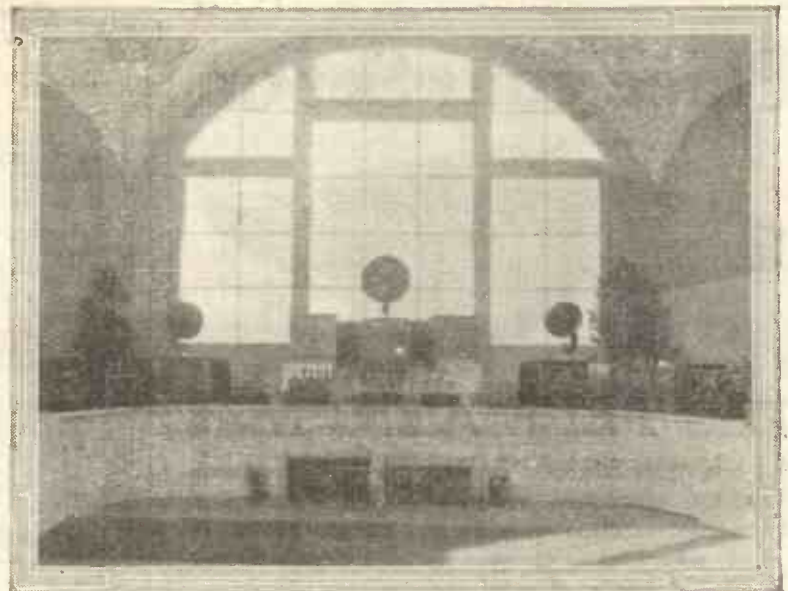

British wireless apparatus on show at the International Sample Fair at Prague.

PRICE	THE SPECIAL CHRISTMAS NUMBER OF MODERN WIRELESS	PRICE
1/6.	WILL BE PUBLISHED ON 1st DECEMBER. ORDER EARLY!	1/6

FOR SECURING YOUR AERIALS
and a thousand purposes where great strength and strain is needed. **FLEXIBLE STEEL WIRE ROPE, Aeroplane Cable** made to Government specification to specified breaking strains. **PRICES BELOW COST.** Orders of 10/- and over carriage paid, otherwise, please add 1/- for postage.

No.	Dia.	Strain.	100 ft.
0	1/16	5 cwt.	4/6
51	5/32	25 cwt.	10/-
52	3/15	35 cwt.	11/-
53	7/32	45 cwt.	12/-
5	1/4	70 cwt.	14/-
7	11/32	100 cwt.	20/-

Strainers for use with above, right and left-hand threads, 9c. each or 8/6 per dozen.
MITH & ELLIS, Ltd. (Dept. 85), 11, Little Britain, E.C.1. Tel.: City 8994.

MAKE YOUR OWN CABINETS.
We supply timber cut accurately to size for amateurs to make their own cabinets. Every part is ready for immediate assembling. Amateurs who use these parts will not have cabinets that look amateurly made, out of square and with jagged edges. Each part is planed smooth, sawn square and fits accurately. Moulding for embellishing cabinets is also provided, cut to size, ready for putting on the body of the cabinet.

Prices for stock sizes of cabinets.

Cabinet.	Parts per set.	Cab. made up and polished.
6 by 6	1/8	3/-
9 " 8	3/-	6/-
10 " 9	3/9	7/6
12 " 10	5/-	10/-
14 " 12	7/-	14/-
16 " 12	8/-	16/-

All postage 6d. extra.
Sloping cabinets 50 per cent. on these prices. We also supply cabinets to fit any size of customers' panels at 1d. per square inch of panel to be used, and at 1/2d. per square inch for made-up cabinets. Sloping cabinets 50 per cent. extra. Nothing but the best oak or mahogany is used in making these parts and cabinets. Send your order on and receive your cabinet without delay.
F. and J. FLETCHER, Ordish Timber Yard, Water Lane, Halifax, Yorks.

TRADE **AERMONIC** MARK.

BACK OF PANEL VALVE HOLDERS.
Exactly as recommended by **Mr. P. W. HARRIS** in his article on the construction of a one valve receiver.
Price 1/6 each. Postage 2d. Obtainable by post direct from
V. R. PLEASANCE,
60, FARGATE, SHEFFIELD.
Telegrams: "Aermonic, Sheffield."

COUPON
QUESTIONS AND ANSWERS
This coupon must be accompanied with a 2s. 6d. P.
"Wireless Constructor"
DECEMBER, 1924

Brown



From the tiniest nut to the finished Loud Speaker

THE non-technical visitor to the works of S. G. Brown, Ltd., will be amazed at the large number of processes and the magnitude of the equipment necessary to produce **BROWN** Loud Speakers and Headphones.

To many, a pair of headphones consists merely of a couple of coils in each ear-piece, together with a circular magnet and a diaphragm. But see even the simplest type of **BROWN** headphones—the famous featherweight F. Type—manufactured under ideal conditions and you will appreciate that parts ground to 1/1000 part of an inch must obviously give infinitely better results.

And it is the same with **BROWN** Loud Speakers. Not only has their design—based on the world-famous A. Type Headphones—been proved superior for sensitiveness and tonal purity—but their success is due in no small degree to the wonderful accuracy of the many manufacturing processes.

Remember that your Loud Speaker should be an investment—the few shillings necessary to obtain a **BROWN** will be more than repaid to you by the increased enjoyment of hearing really true-to-life reproduction and by the knowledge that you own an Instrument capable of giving you many years of service.

Types and Prices :

H.1.	120 ohms	£5 5 0
	2,000 ohms	£5 8 0
	4,000 ohms	£5 10 0
H.2.	120 ohms	£2 5 0
	2,000 ohms	£2 8 0
	4,000 ohms	£2 10 0
Q.	£15 15 0 in all resistance.	

From all Dealers or can be demonstrated at the following Showrooms:
19, Mortimer Street, W.1.
15, Moorfields, Liverpool.
67, High St., Southampton.

S. G. BROWN, LTD. — Victoria Road, N. Acton, W. 3

Gilbert Ad. 1690

THE VERY LATEST INVENTION IN WIRELESS

The
“ENEWAIR”
 (Trade Mark)
VARIOMETER

(Patent No. 220185)

with New Slow Motion Handle

The “Enewair” Variometer is the result of months of careful study and experimental work, and we claim that it is the finest instrument of its kind in the world.

The spherical coils are produced from the very best silk-covered wire, and are pile wound without formers, giving a range of

300 TO 1,800 METRES


Mounted on bevelled ebonite base, as illustrated

12/6

Unmounted for panel one hole fixing

11/6

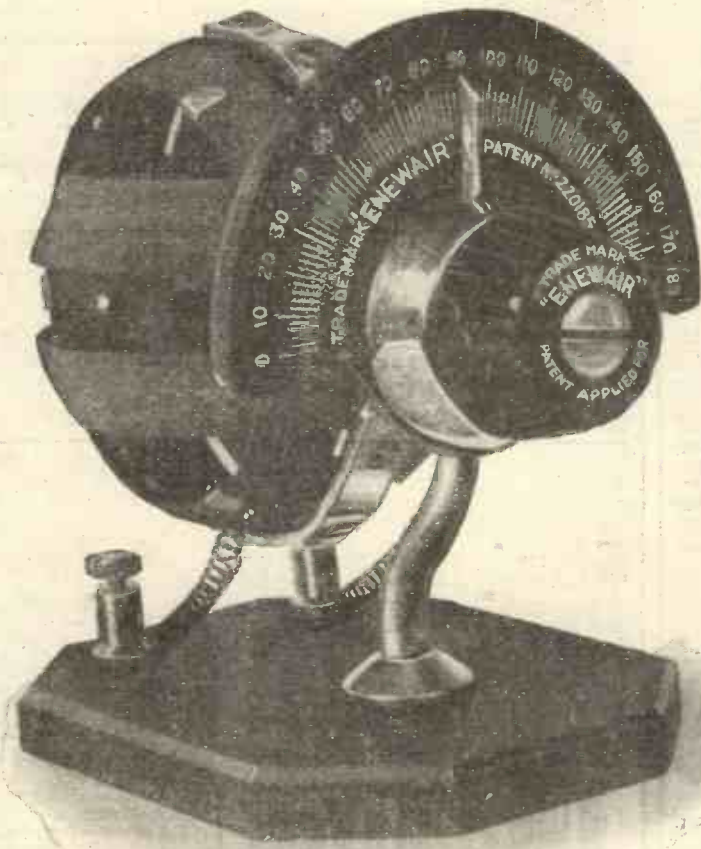The slow Motion Handle as shown below can also be purchased separately.



2/6

You should be able to purchase our goods from your dealer, but should you experience difficulty, please write to us at once.


THE AUTOMATIC COIL WINDER AND ELECTRICAL EQUIPMENT CO., LTD.,

Telephone, T6c. 4350 WELLINGTON HOUSE, BUCKINGHAM GATE, LONDON, S.W.1 Telegrams, "Autovinda
 Sawest, London."

The New Peto-Scott Square Law Condenser

—a delight to use, say the experts

Experts who have seen and used it are frankly amazed that such a well-made condenser can be sold at such a moderate figure. From top to bottom the Peto-Scott Square Law is a good piece of engineering skill. Its plates (registered design No. 707,587) permit the true square law tuning being obtained over the whole of its curve. Standard one hole fixing will enable every experimenter to substitute it for any old-fashioned condenser without alteration to set.

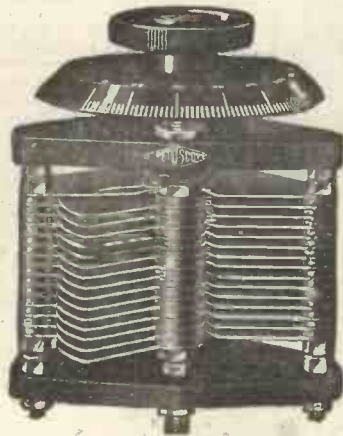

Send for large Catalogue.

Send 3d. in stamps for large 48-page catalogue and other literature invaluable to the experimenter.

PRICES.

'0001 mfd. 7/-	'001 mfd. 11/6
'0002 mfd. 8/6	Dual Condensers
'0003 mfd. 10/-	ser for 2 stages
'0005 mfd. 10/6	of H.F. 15/6



Interchangeable Plug-in Condensers as used in Mr. Scott-Taggart's Resistoflex.

Each condenser is of same standard size and plugs into panel or into another one of different value. Thus, two condensers each of the value of '0005 mfd. become '001 mfd. Every condenser tested, guaranteed and calibrated. The most convenient method of mounting condensers ever invented. Any condenser can be removed and substituted by any other of a different value without disturbing a connection. For mounting above or below the panel.

Price: '0001 to '0009 mfd., 2/6 each; '001 to '004 mfd. 3/- each. Sockets, 2d. per pair.

Our registered design, and made exclusively for us by Dubilier Condenser Co., Ltd.

PETO-SCOTT CO. LTD. Reg. Offices (for all Mail Orders), 77, CITY ROAD, E.C.1.

BRANCHES: LONDON, 62, High Holborn, W.C.1, and 230, Wood Street, Walthamstow.—CARDIFF, 94, Queen Street.—LIVERPOOL, 4, Manchester Street. PLYMOUTH, Near Derry's Clock.

G. A. 1692

DON'T SPOIL YOUR PANEL

BY FITTING IT IN A CHEAP MACHINE-MADE CABINET. INSIST ON A CABINET-MAKER'S JOB THAT WILL ALWAYS GIVE YOU SATISFACTION. THIS WE CAN SUPPLY FOR ALL RADIO PRESS RECEIVERS AND ALSO DRILLED AND ENGRAVED PANELS AND ANY COMPONENTS.

RADION PANEL SUPPLIED IF DESIRED.

SPECIAL CABINETS MADE TO CUSTOMERS' DESIGNS.

EXAMPLES.	Cabinet.	Panel.
FOUR-VALVE FAMILY	18/-	15/6
SIMPLICITY THREE-VALVE	21/-	12/-
ALL CONCERT-DE-LUXE	26/-	15/-

Carriage and packing on post orders 1/6 9d.

Send 2d. stamp for descriptive leaflets and our new 100-page Catalogue.

XMAS IS COMING. Good panels and cabinets make acceptable presents.

"S. A. CUTTERS,"

15, Red Lion Square, London, W.C.1.

'Phone: Chancery 8042.



Ask your LOCAL RETAILER for the "SIMPLEX"

Lead-in Strip. No holes to bore, no tools required. 1/6. Postage 2d.

THE "MORRIS" (all-steel) Valve Template. Saves TIME, TEMPER and EBONITE.


10 1/2d. post free.

J. O. NICHOL & CO.,

46, Lancaster Avenue, Fennel St., Manchester. Tel.: City 1769.

The SHIPTON New Type Strip Rheostat & Potentiometer

protects your valves

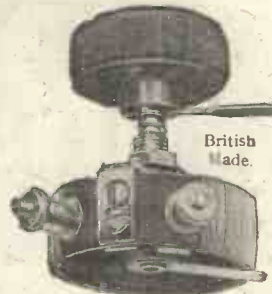

Various devices are available for the protection of valves from accidental short circuit; but fitting is troublesome. When you fit The SHIPTON Rheostat (one hole fixing) your valves are protected, since the SHIPTON 7 ohm model is fitted with a fuse. A spare fuse is contained in every box.

This Rheostat, besides combining a safety fuse, is designed with a special tension spring on the spindle assuring good contact while retaining a silky action, and actually costs no more than the now obsolete rheostat.

THE MOST PERFECT RHEOSTAT YET INTRODUCED

- SHIPTON New Type STRIP RHEOSTAT 7 ohm (with fuse) 3/-
 - SHIPTON New Type STRIP RHEOSTAT 30 ohm 3/-
 - SHIPTON New Type STRIP RHEOSTAT 60 ohm 3/-
 - SHIPTON POTENTIOMETER 600 ohm 4/3
- Packed in neat linenette boxes.

The resistance wire is wound on insulated strip. Noises due to uneven spacing of the wire cannot occur with the SHIPTON. Terminals are standard and connection is a matter of facility.

Three models are available so that whatever valves you may use there is a SHIPTON Rheostat to give you perfect filament control. Ask for it by name. Apply to your local dealer or direct giving your dealer's name and address. Sole agency applications considered for certain territories.

E. SHIPTON & CO., LTD.
37, Tothill Street, Westminster, S.W.1.

Telephone: Victoria 7. Telegrams: "Rentfones, Parl."

Also at 14, King Street, Covent Garden, W.C.

Ba clays 131

Aerial Satisfaction !!

Use clear receptin Radiowire for your aerial, and lead direct to set. Easily fixed, requires no insulators. Only 1/8 for 100 ft. with instructions! Useful for earthing and 'phone extensions and is waterproof insulated.


From your dealer or post free from:

DAVID GREEN & SON,
655, Department, Lytham.

Straight from the Heart of Nature

A wonderful new NATURAL crystal. Thoroughly tested and guaranteed, consistently active, unaffected by atmosphere, and will give loud and clear reception over maximum range.

Uraium
NATURE'S WONDER CRYSTAL

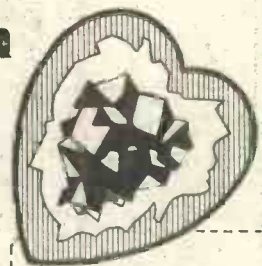

Obtainable in boxes, including silver catwhisker 1/6 of all dealers.

If unable to obtain Locally, send P.O. with name and address of Local Dealer,
BOWER ELECTRIC LTD.,
15, GRAPE STREET, SHAFESBURY AVENUE, W.C.2.

November 15th to 29th
BRITISH
WIRELESS
EXHIBITION
 AT THE
WHITE CITY
 LONDON, W. 12.

A gigantic show of sets and Component Parts, including some wonderful new ideas and improvements. In order to make the Exhibition representative of the

Entire British Wireless Industry every manufacturer of British goods has been invited to exhibit. Come and see ALL that the industry can offer. All goods will be on sale at the stands.

COMPETITIONS FOR AMATEURS.
DEMONSTRATIONS AND OTHER ATTRACTIONS.

Organised by Radio Exhibitions and Wireless Conventions, 46, Cannon St., London, E.C. 4.



RADIO STOCKS (B. HAINE, Sole and New Proprietor),
RADIO HOUSE, NEWMAN STREET,

Phone: MUSEUM 3205. OXFORD ST., LONDON, W. 1.

Accumulators. Best British, 4 Vt. 40 Amp. 17/6, 4 Vt. 60 Amp. 21/0, 4 Vt. 80 Amp. 27/6, 6 Vt. 40 Amp. 25/0, 6 Vt. 60 Amp. 30/0, 6 Vt. 80 Amp. 37/6, 6 Vt. 100 Amp. 45/0.
 Aerial Wire. 7/22; Best H.D. Copper, 2/0. Enamelled, 3/6 per 100 feet. Electron, 1/8.
 Anode Resistances. Allen, variable, 1/6; Wamtel, 3/6; Lissen, 2/6; Dubilier and all makes.
 Batteries. Best British H.T. Batteries, 36 volt 7/0, 63 volt 12/6, 100 volt 16/6.
 Coils. Basket, waxless, duplex set Nos. 25, 35, 50, 75 and 100, 2/0; for Chelmsford station, No. 150 1/3, No. 200 1/6. Ditto (extra large air spacings), Nos. 25, 35, 50, 75 and 100, 3/0.
 Coil Holders. Radstocks quality, solid ebonite, long handles or knobs, two way 2/3, 3/0, 4/0 and 5/0; ditto with Vernier fine adjustment 6/0, 8/6, 10/6. Three way, 3/6, 4/9, 6/9 and 8/6; ditto Vernier, 7/6, 9/6, 12/0. Basket Coil Holders, best, 1/0 and 1/3.
 Ebonite Coil Plugs. 6d. each; curved, 1/0 each.
 Condensers. (Copper and mica.) Fixed: to .001 9d., to .005 1/0, to .01 1/9, to .1 3/0. Edison Bell Fixed Condensers, to .001 1/3, .002 upwards 2/0; Dubilier to .001 2/6, .002 upwards 3/0.
 Crystals. Galite, Hertzite, Talite, Zincite, Midite, 9d. and 1/0; Neutron and Tungstallite 1/6.
 Crystal Detectors. Adjustable Enclosed, glass covered, 1/0, 1/6, 1/9, 2/6 and 3/0. Radstock Special Detector, micrometer movements, 3/0. All detectors stocked; Edison twin 5/0, etc.
 Crystal Sets from 5/6 to 30/0.
 Ebonite. Cut to size 3/6 per lb. Scrap Ebonite 2/0 lb.
 Flex. Twin 3d. yard. Bell wire, 22 yards 6d.
 Filament Resistances, 1/6, 2/0 and 2/6 with engraved dial. "Microstat" for D.E. 2/6 each.
 "Radstock" 30 ohm 2/3, Igranite 4/6, Ormond 2/0. All makes in stock.
 Frame Aerials. Well-made, fold-up, in carrying case, 21/0.

EVERYTHING WIRELESS AT LOWEST PRICES.
Send for Free List.

All goods on 24 hours approval. Send ample postage: surplus refunded.

THE QUALITY OF OUR COMPONENTS IS GUARANTEED, AND OUR PRICES ARE THE BEST OBTAINABLE.

FIRST CLASS VARIABLE CONDENSERS.

Best British Make.

Accurate Spacing. Perfect Finish.
 Absolutely Best Value Obtainable.

	Ordinary.	Square Law.	With 3 Plate Vernier.
	s. d.	s. d.	
.001	7 3	9 6	16 EXTRA.
.00075	6 6	—	
.0005	5 4	8 9	
.0003	5 1	7 6	
.0002	4 5	6 6	
.0001	4 2	—	
.00005	3 1	—	

Postage 6d. one condenser; 3d. each additional instruments.

SPECIAL OFFER OF MANSBRIDGE CONDENSERS.

Octopus B. and. Best Make. New and Guaranteed
SECOND TO NONE.

.05 3/6, .1 3/6, .25 3/6, 1mf. 4/-, 2mf. 4/6

SEND YOUR ORDER WITH CONFIDENCE. IF THE GOODS YOU WANT ARE NOT LISTED ON THIS PAGE, REST ASSURED PRICE AND QUALITY WILL BE THE BEST.

Headphones. "Brandes" 25/0. N. & K. pattern 12/8. "Continental" 12/11. Dr. Nesper's adjustable 12/6.
 Insulators. Egg shape 1d., 2 in reel 2 for 1 1/2. Jack and Plug, 3/0 the pair.
 Leading-in Tubes, 12 in. 9d. each, 9 in. 8d., 6 in. 7d., "Simplex" flat lead-in 1/6.
 Loud-Speakers. All makes stocked: Special Radio Classic, 20/0.
 Sets (Valve). Splendid Selection, open or closed cabinets. From £1 to £30.
 Sleaving. (Insulating), 3 feet lengths, 3 for 10d., finest quality.
 Switch Arms: first quality 9d., Nickel 1/0, second quality 6d.
 Switches. S.P.S.T. 1/0, S.P.D.T. 1/6, D.P.S.T. 1/9, D.P.D.T. 2/0. Panel mounting, S.P.D.T. 1/0, D.P.D.T. 1/8.
 Transformers. L.F. "Powquip" 14/8, "Bucks" 11/6, "Radstock" 13/6, Royal 20/0—Best of all. All makes stocked.
 Transformers. H.F. Plug-in. Nos. 1, 3/6; 2, 3/11; 3, 4/3; 4, 4/8; 5, 4/9; 6, 5/0.
 Terminals. Nickel 2d., Large W.O. & Telephone type 11d. each, Nickel 2d., Small Pillar & W.O. 1d., Nickel 2d., Spade 2 a 1d. Screwed Spade 1d., Screwed Pins 2d.
 Variometers. Double wound 150/550, 2/0, on ebonite 3/0, finest make "Radstock" moulded ebonite ball rotor 6/6. Edison Bell 10/0, Igranite 12/6, G.R.C. 15/0 each, close coupling. All makes stocked.
 Valve Holders. Best turned ebonite, with nuts 10d. Radstock Anti-Capacity, legless, 1/0 each, Murrays 1/3; highly recommended.
 Valve Legs. With nut and washer plain 1d. each, 9d. doz., nickel 1d., 1/3 doz., flanged 11d. each, 1/3 doz., nickel 2d. each, 1/9 doz.
 Valves. Tested before dispatch and sent at purchaser's risk. Dutch "R" ideal for detector (hard or soft) 5/6, French R 6/6. All makes stocked.

EVERYTHING WIRELESS AT LOWEST PRICES. RADIO STOCKS (B. HAINE, Sole and New Proprietor),
Send for Free List.
 RADIO HOUSE, NEWMAN STREET,
 OXFORD ST., LONDON, W. 1.

All goods on 24 hours approval. Send ample postage; surplus refunded. Phone: MUSEUM 3205.



Published every Wednesday by
Radio Press, Ltd., Bush House,
Strand, London, W.C. 2.
6d. WEEKLY.

Why I read "Wireless Weekly"

1. BECAUSE, chiefly, I feel safe. I know that behind this paper is the RADIO PRESS, the largest Wireless Publishing concern in the World, and this is their weekly.
2. BECAUSE the Editor is John Scott-Taggart, F.Inst.P., A.M.I.E.E., and the Assistant Editor is Percy W. Harris, and because this is the only paper which contains articles by such other well-known writers as Cowper, Hallows, Kendall, Itattee, Redpath, etc., etc.
3. BECAUSE it is beautifully printed on the finest quality paper, and all the photographs come out clearly and not as smudges, as is so often the case. A Photogravure Supplement is now appearing, by the way, in every alternate issue.
4. BECAUSE of the regular "Valve Notes" which appear weekly and are written by the Editor. Nothing like these appears anywhere else. WIRELESS WEEKLY appeals to me because I am a valve user, and the paper caters very largely for the valve man.
5. BECAUSE I thoroughly enjoy "Jottings By the Way," a very witty weekly feature (now illustrated, by the way).
6. BECAUSE new circuits and designs appear regularly and many of them never appear elsewhere. I know that if I miss my WIRELESS WEEKLY I shall miss something new.
7. BECAUSE I am pleased to reply WIRELESS WEEKLY when my friends ask me what I read. I know that they know that WIRELESS WEEKLY is a paper in a class by itself. Its price is the highest of the weeklies, and though not a snob, I don't mind my friends knowing that I want the best—and get it.
8. BECAUSE it's a "live" paper. It does things. It's the most virile of the RADIO PRESS periodicals. It criticises fearlessly on wireless topics of the day. Its test reports on wireless apparatus are equally fearless. If something new comes along, whether it is oscillating crystals, a new circuit, a new move by the Post Office, every keen wireless man wants to know "what WIRELESS WEEKLY has to say about it"—and they are never disappointed.

PLACE AN ORDER FOR "WIRELESS WEEKLY" WITH YOUR NEWSAGENT TO-DAY. A FINE SERIES OF ARTICLES ON SUPERSONIC HETERODYNE RECEPTION HAS JUST COMMENCED.

ORDER FORM

Please deliver reserve WIRELESS WEEKLY (6d. weekly) until further notice.

NAME _____

ADDRESS _____



Sole Manufacturers:
**PORTABLE UTILITIES
 CO., LTD.,**
 Fisher St., London, W.C.1.

Scottish Agents:
**FULLER, BLACKIE &
 RUSSELL, LTD.,**
 30, Gordon St., Glasgow.

Dampness—the arch-thief of signal strength.

THE wonderful Eureka Concert Grand was not evolved in a day—nor a week—nor a month—nor, for that matter, in a year. It was the direct outcome of much intensive study of the problem of Low Frequency amplification and the possibility of obtaining "power" results without the necessity of using power valves. From the first, the radio engineers who designed the Eureka worked on original lines. In fact, apart from the fact that the Eureka has a primary winding and a secondary winding it has little in common with ordinary Transformers. Take its superb insulation, for example. In the Faraday House Test Report (sent free of charge to all interested) it is recorded that the tremendous pressure of 2,000 volts was necessary to break down the insulation between windings and between windings and case.

But that is not all. This tremendously high insulation safety factor is permanent. No matter how old your Eureka its insulation will always be perfect because the Transformer is hermetically sealed up after its last test report.

Dampness cannot affect it. Many L.F. Transformers absorb moisture (see Dr. Roberts' article in "Popular Wireless," August 30th) and naturally signal strength is considerably reduced. If your Set is not as loud as it was, say, six months ago it is quite likely that your Transformer is the cause. Discard it and instal a Eureka Concert Grand. You will get greater purity of sound, increased volume, and freedom from trouble. Remember that the Eureka is the only Transformer that can be suspended in water for fourteen days and used immediately without any harmful effects.

Concert Grand 30/-

Eureka No. 2 22/6 (For Second Stage)

From all Dealers.


Transformer De Luxe



Gilbert Ad. 1625

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR

THE IDEAL BOOKS FOR THE BEGINNER

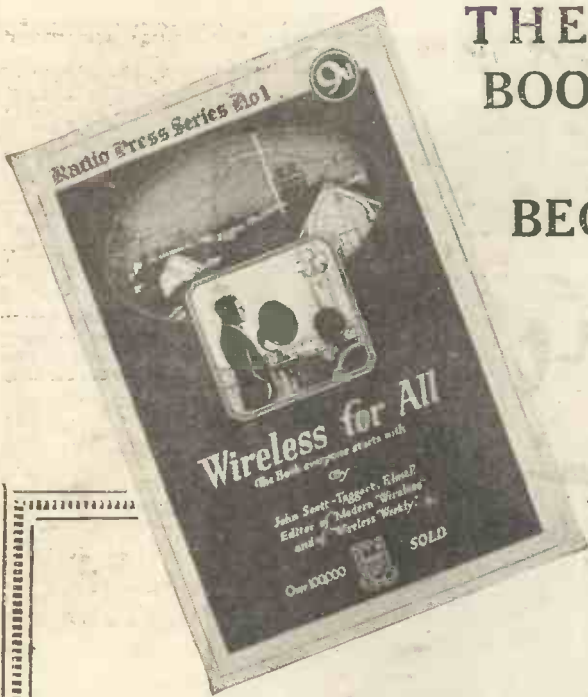

OVER A QUARTER OF A MILLION HAVE BEEN SOLD

of these books which every beginner buys.

"WIRELESS FOR ALL" (9d. net) is No. 1 of the famous Radio Press Series of handbooks. "SIMPLIFIED WIRELESS" (1s. net) is the very popular sequel. Each book, however, is self-contained.

FOR the novice whose knowledge of Wireless is absolutely nil, these are the two books which he will need. Both are from the pen of John Scott-Taggart, F.Inst.P., A.M.I.E.E., a master in the difficult art of explaining technical subjects lucidly and in language everyone can understand. These two books treat the elements of Wireless very thoroughly, and even the more experienced amateur will find them helpful in elucidating any difficult points which may not be absolutely clear to him.

Wireless for All

CONTENTS: Introduction—Morse Code—How to Tell what Station is Working—How Wireless Signals are Actually Sent—Nature of Waves—Light and Wireless Waves Compared—Meaning of Wavelength—How Wireless Waves are Set Up and Detected—How Wireless Stations work at the same time without interfering with each other—Does Weather Affect Wireless—Waves from a Wireless Telephone Station—General Notes on Different Kinds of Waves Received—Some Elementary Instruction in Electricity—How a Wireless Receiver Detects Wireless Waves—The Aerial—The Earth Connection—How a Wireless Set is Tuned to a Certain Wavelength—The Variable Condenser—The Detector—The Crystal Detector—The Complete Wireless Receiving Circuit—Special Tuning Arrangements—The Thermionic Valve—How a Valve Works—How to Start with a Wireless Station—Conclusion—List of Principal Wireless Societies in Great Britain.

9d.

10d. post free.

Published by Radio Press, Ltd., the largest wireless publishers in the world, Bush House, Strand, London, W.C.2.

Simplified Wireless

CONTENTS: Some General Remarks regarding Wireless—Elementary Instruction in Electricity—Sources of Electricity—Effects of a Current of Electricity—Magnetic Effect of an Electric Current—Meaning of Positive and Negative—Electrical Units—How we can vary an Electric Current—Connecting Cells in Series—Connecting Cells in Parallel—Electro-Magnetism—The Telephone Receiver—Transformers—Air-core and Iron-core Transformers—Step-up and Step-down Transformers—Inductances—Condensers—Oscillating Circuits—Frequency and Wavelength—The Aerial Circuit of a Wireless Receiver—The Use of a Variable Condenser when Tuning an Aerial Circuit—The Detector Circuit—The Crystal Detector—A Receiver Using a Variable Condenser—Use of a Series Condenser—Loose-coupled Circuits—Notes on the Erection of Aerials—Twin-wire Aerials—The Earth—Frame Aerials—Loudspeakers—How to Make a Simple Broadcast Receiver—Operation of the Receiver—Second Type of Broadcast Receiver—The Variable Inductance—Another Type of Variable Inductance—Some Simple Forms of Crystal Detector—The Telephone Condenser—The Complete Arrangement of the Apparatus—Operation of the Circuit—Use of Lightning Arresters—Some further Safety Hints.

1/-

1/1½ post free.

THREE POPULAR BOOKS

The CONSTRUCTION of CRYSTAL RECEIVERS

By ALAN L. M. DOUGLAS.

This book deals exclusively with crystal receivers for the reception of signals from the ordinary B.B.C. stations and also the high-powered station.

Price 1/6 net (post free 1/8).



HOW TO ERECT YOUR WIRELESS AERIAL

By B. MITTELL, A.M.I.E.E.

To every newcomer and many "old hands" this book will make all the difference between poor and first-rate reception.

Mr. Mittell is a professional radio engineer, and he has had many years' experience of aerial erecting and knows just those points where beginners go wrong. Incidentally, he took a prominent part in the erection of the huge aerials at Northolt and elsewhere. This is a useful volume which should be found on every wireless bookshelf.

Price 1/- net (post free 1/2).




HOW to MAKE your OWN BROADCAST RECEIVER

By JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.

This book is by the Editor of *Wireless Weekly* and of *Modern Wireless*, and tens of thousands have made their first crystal set from this book, which is a sequel to "Wireless For All" and "Simplified Wireless."

This book contains much valuable data on aerials and how to erect them, and the purchaser can go straight home, make one of the three very simple and cheap sets, erect his aerial, and enjoy the programme from his local station or from the high-powered station.


Price 1/6 net (post free 1/8).

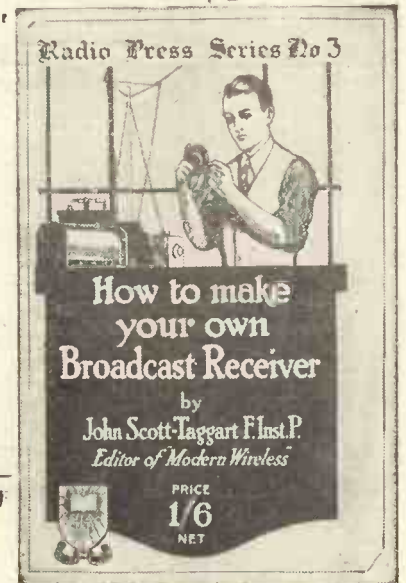

Published by RADIO PRESS, LTD.,
Bush House,

Strand, London, W.C. 2.

Barclays Ad. 1175

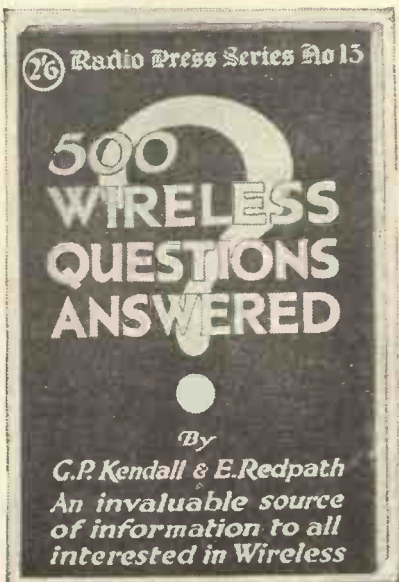

BUY THIS BOOK
AND
Your
Wireless Worries
will Disappear

THIS volume, "500 WIRELESS QUESTIONS ANSWERED" (2/6 net), is a veritable mine of information. Encyclopædic in its scope, it is written so that the veriest novice can understand.

Every section of wireless is dealt with in a highly competent manner by G. P. Kendall, B.Sc., and E. Redpath, the joint authors, both of whom, by long experience, understand just those difficulties which worry the average experimenter.

There are 500 answers to typical questions on the following subjects :


- | | |
|----------------------------|-------------------------|
| Aerials. | Reaction. |
| Amplifiers. | Secondary batteries. |
| Crystals and crystal sets. | Sounds and signals. |
| Earths. | Telephone receivers. |
| Frame Aerials. | Tuning coils. |
| Grid-leaks and condensers. | Tuning condensers. |
| Interference. | Valves. |
| Loud-Speakers. | Wave-lengths. |
| Morse. | Waves. |
| Primary Batteries. | Wire. |
| Ranges. | Miscellaneous problems. |

Buy a copy to-day from your wireless dealer or bookseller, or send 2/8 to the publishers and get the book by return post.

Published by RADIO PRESS, LTD.,
Bush House, Strand, W.C.2.

Barclays Ad. 1174



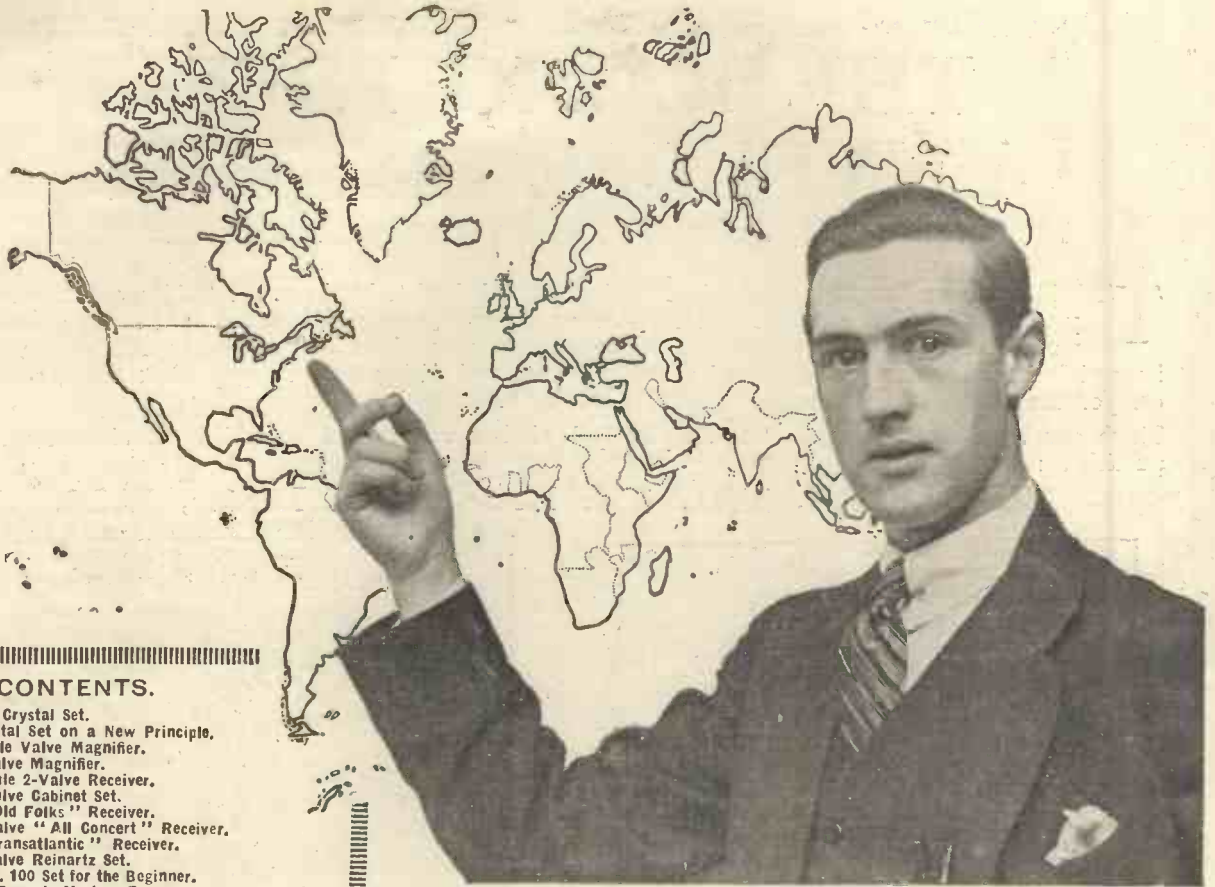

CONTENTS.

- I A 2/6 Crystal Set.
- 2 A Crystal Set on a New Principle.
- 3 A Single Valve Magnifier.
- 4 A 2-Valve Magnifier.
- 5 A Simple 2-Valve Receiver.
- 6 A 2-Valve Cabinet Set.
- 7 An "Old Folks" Receiver.
- 8 A 3-Valve "All Concert" Receiver.
- 9 A "Transatlantic" Receiver.
- 10 A 3-Valve Reinartz Set.
- 11 An S.T. 100 Set for the Beginner.
- 12 Wave Traps in Various Forms.

"I get these stations regularly"

So will you if you buy a copy of

TWELVE TESTED WIRELESS SETS

By PERCY W. HARRIS

2/6 net.
Post Free,
2/8



And make one of the fine multi-valve sets such as the "Transatlantic." This is the season for receiving broadcasting from American and Continental stations, and there is no more fascinating or instructive pastime than searching for those elusive stations.

They will, however, not be elusive if you build a set produced by such an experienced designer as Mr. Harris.

Look at the varied contents and you will realise what a bargain such a cheap but reliable book is. Every set is not merely tested by the author but by hundreds, and sometimes thousands, of readers who have bought this book.

Buy it to-day from your wireless dealer or bookseller (2s. 6d. net) or send 2s. 8d. to the publishers:

RADIO PRESS, LTD., Bush House, Strand, London, W.C.2.

Barclays Ad., 1173

THE RADIO PRESS ENVELOPE SYSTEM

THE Radio Press Envelope System is generally acknowledged to be the greatest aid to the constructor yet evolved. Each envelope contains working diagrams, exact size blue prints of wiring and of the panel (suitable for drilling), a set of photographs printed on real art paper and in a manner impossible in a book or periodical and showing the set and wiring from every possible angle, a list of components and the full instructions for making each set and using it.


These envelopes are obtainable from all principal wireless dealers and booksellers or direct from the publishers:

RADIO PRESS, LTD., Bush House, Strand, London, W.C.2.




R.P. Envelope No. 1. Price 1s. 6d. (1s. 8d. post free). How to Make an Efficient 2-Valve Receiver using the ST. 100 Circuit. By John Scott-Taggart, F.Inst.P., A.M.I.E.E.

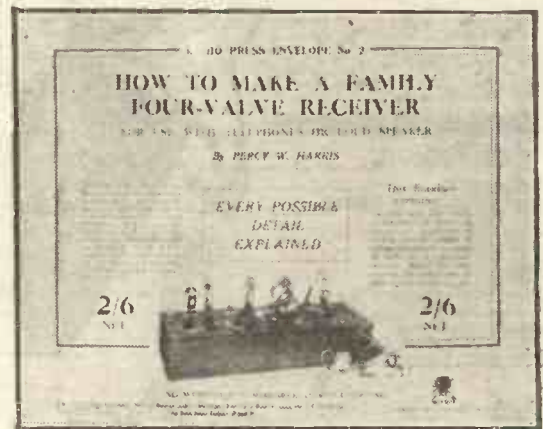A huge number of this ST. 100 envelope has been sold, and practically all the tens of thousands of successful ST. 100 sets in the country have been made from this design, which works a loud-speaker with ease up to 30 to 35 miles.



R.P. Envelope No. 2. Price 2s. 6d. (2s. 8d. post free). How to Make a Family 4-Valve Receiver. By Percy W. Harris.

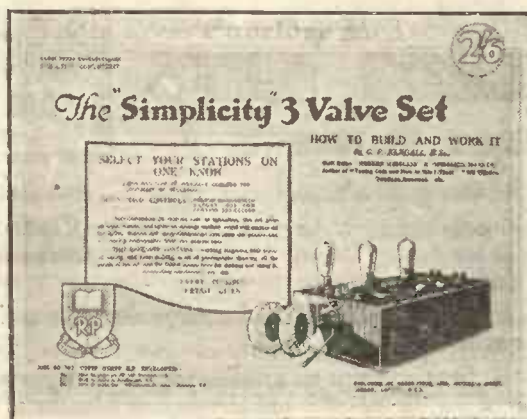This is the ideal easily-handled set for long range loud-speaker work. For those some distance from a station this set is ideal.



R.P. Envelope No. 3. Price 2s. 6d. (2s. 8d. post free). The "Simplicity" 3-Valve Set. By G. P. Kendall, B.Sc.

Notwithstanding extreme ease of operation this set gives excellent results and will receive all the B.B.C. stations and many Continental ones upon the phones and will work a loud-speaker from the nearest ones.



R.P. Envelope No. 4. Price 2s. 6d. (2s. 8d. post free). The "All-Concert de Luxe" Receiver. By Percy W. Harris.

A supremely efficient 3-Valve set with enclosed valves and all the latest technical improvements incorporated.

BOOK ORDER FORM

Cut out this form and hand it to your newsagent or wireless dealer, or post it to RADIO PRESS, LIMITED, Bush House, Strand, London, W.C.2, who will despatch by return post.

PLEASE DO NOT LIMIT YOUR ORDER TO ONE BOOK IF YOU THINK YOU WILL REQUIRE OTHERS.

Please supply a copy of each of the publications against which a tick has been made.

Name.	Author.	Radio Press Series No.	Price.	PRICE PLUS POSTAGE
" WIRELESS FOR ALL."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	1	9d.	11d.
" SIMPLIFIED WIRELESS."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	2	1/-	1/2
" HOW TO MAKE YOUR OWN BROADCAST RECEIVER."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	3	1/6	1/8
" HOW TO ERECT YOUR WIRELESS AERIAL."	B. Mittell, A.M.I.E.E.	4	1/-	1/2
" THE CONSTRUCTION OF WIRELESS RECEIVING APPARATUS."	P. D. Tyers.	5	1/6	1/8
" CONSTRUCTION OF CRYSTAL RECEIVERS."	Alan L. M. Douglas.	6	1/6	1/8
" HOW TO MAKE A 'UNIT' WIRELESS RECEIVER."	E. Redpath.	7	2/6	2/8
" PICTORIAL WIRELESS CIRCUITS."	Oswald J. Rankin.	8	1/8	1/8
" WIRELESS VALVES SIMPLY EXPLAINED."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	9	2/6	2/8
" PRACTICAL WIRELESS VALVE CIRCUITS."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	10	2/6	2/8
" RADIO VALVES AND HOW TO USE THEM."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	12	2/6	2/8
" 500 WIRELESS QUESTIONS ANSWERED."	G. P. Kendall & E. Redpath.	13	2/6	2/8
" 12 TESTED WIRELESS SETS."	Percy W. Harris.	14	2/6	2/8
" MORE PRACTICAL VALVE CIRCUITS."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	15	3/6	3/8
" HOME BUILT WIRELESS COMPONENTS."		16	2/6	2/8
" WIRELESS SETS FOR HOME CONSTRUCTORS."	E. Redpath.	17	2/6	2/8
" TUNING COILS AND HOW TO WIND THEM."	G. P. Kendall.	18	1/6	1/8
RADIO PRESS PANEL CARDS.				
Name.	Author.	Panel Card No.	Price.	Price plus Postage
" HOW TO MAKE THE W.I RECEIVER."	Herbert K. Simpson.	1	1/-	1/2.
RADIO PRESS ENVELOPES.				
Name.	Author.	Envelope No.	Price.	Price plus Postage
" HOW TO BUILD AN ST.100 RECEIVER."	John Scott Taggart, F.Inst.P., A.M.I.E.E.	1	1/6	1/9
" HOW TO BUILD A 4-VALVE RECEIVER."	Percy W. Harris.	2	2/6	2/9
" HOW TO BUILD THE 'SIMPLICITY' 3-VALVE SET."	G. P. Kendall, B.Sc.	3	2/6	2/9
" HOW TO BUILD THE ALL-CONCERT DE LUXE RECEIVER."	Percy W. Harris.	4	2/6	2/9
" A SINGLE VALVE REFLEX RECEIVER."	Herbert K. Simpson.	8	1/6	1/9
" AN EFFICIENT SINGLE VALVE RECEIVER."	Herbert K. Simpson.	9	1/6	1/9
SIMPLEX WIRING CHARTS.				
Name.	Author.	Simplex Chart No.	Price.	Price plus Postage
" FOR 2-VALVE SET."		1	1/-	1/3
" FOR 3-VALVE SET."		2	1/-	1/3
" FOR 4-VALVE SET."		3	1/-	1/3
RADIO PRESS WIRELESS PANEL TRANSFERS				
			6d.	9d.

CUT HERE

I enclose remittance for


(necessary where goods are ordered by post).

NAME

ADDRESS

Index to Advertisers

	PAGE		PAGE		PAGE
American Hard Rubber Co...	124	Fletcher (F. and J.) ..	167	Oldham Accumulators ..	163
Arrigoni (C. & J.) & Co. ..	155	Formo Co. ..	110	Peto-Scott Co. ..	170
Automatic Coil Winder and Elec. Equipment Co. ..	119	Gamage, (A.W.) Ltd. ..	161	Pleasance ..	167
Beard and Fitch, Ltd. ..	141	Gambrell Brothers ..	110	Portable Utilities Co., Ltd. ..	173
Bower Elec., Ltd. ..	170	General Electric Co., Ltd. ..	105	Radiax, Ltd. ..	151
Bowyer-Lowe Co. ..	140	Goswell Engineering Co. ..	153	Radio Communication Co., Ltd. ..	136
Brandes, Ltd. ..	106	Grafton Electric Co. ..	158	Radio Improvements ..	156
Brighton Radio and Elect. Co. ..	165	Gran-Goldman Service ..	135	Radio Stocks ..	171
British Thomson-Houston Co., Ltd. ..	128	Green (David) & Son ..	170	Raymond (K.) ..	130, 131, 132, 133
Brown (S. G.), Ltd. ..	167	Helixo, Ltd. ..	159	Reynolds (Walter) ..	168
Buradep, Ltd. ..	154	H. T. C. Electrical Co. ..	135	Rosen (Ed.) and Co. ..	150
Burne-Jones and Co. ..	148	Hughes and Co. ..	168	'S. A. Cutters' ..	170
Cave and Co. ..	165	Igranic Electric Co. ..	86	Shipton (E.) & Co., Ltd. ..	170
Collinson's Precision Screw Co., Ltd. ..	155	Jackson Brothers ..	142	Smith and Ellis ..	167
Cossor (A. C.), Ltd. ..	112, 113	Lighting Supplies Co. ..	161	Soldo Co. ..	150
Cunningham and Morrison ..	139	Lissen, Ltd. ..	109	Sparks Radio Supplies ..	159
Curtis (Peter), Ltd. ..	127, 149	McMichael (L.), Ltd. ..	139	Sterling Telephone & Elec. Co., Ltd. ..	123
Diamond Wireless, Ltd. ..	147	Marshall (H. Lloyd) ..	152	Telegraph Condensers Co., Ltd. ..	146
Dubilier Condenser Co., Ltd. ..	118, 119	Molback ..	161	"U.S." Radio Co. ..	142
Electrical Equipment Co., Ltd. ..	168	Mulholland (V.) ..	147	Ward and Goldstone, Ltd. ..	159
Express Radio Services ..	168	Mullard Radio Valve Co., Ltd. ..	cover ii	Watmel Wireless Co. ..	150
Falk, Stadelmann and Co., Ltd. ..	114	Neutron, Ltd. ..	158	Wholesale Fittings Co. ..	135
Fallon Condenser Co. ..	85	Nichol (J. O.) and Co. ..	170	Wilkins and Wright, Ltd. ..	165
		Noel (S.A.) ..	168	Wireless Exhibition ..	171
				World's Wireless Stores ..	168

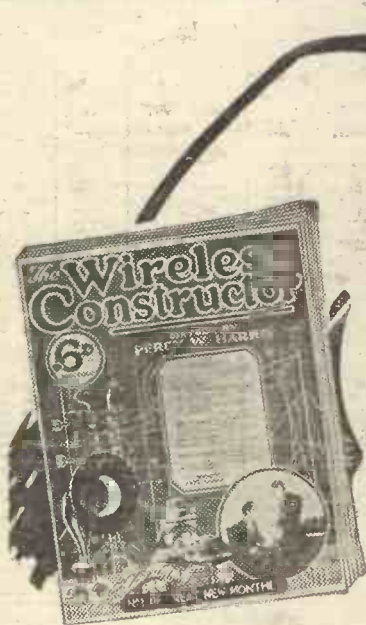

Telephone :
CITY
9911 (Extn. 9).

THREE SOUND MEDIA

for your advertising campaign.


MODERN WIRELESS,
WIRELESS WEEKLY,
AND
THE WIRELESS CONSTRUCTOR
the predominant media for Radio advertising.

You cannot afford to ignore the responsive public that eagerly and consistently studies the advertisements in these journals and which constitutes an excellent established market for your goods.

Write at once for Advertisement rates:

BARCLAYS ADVERTISING LTD.,
Bush House, Strand, London, W.C.2.

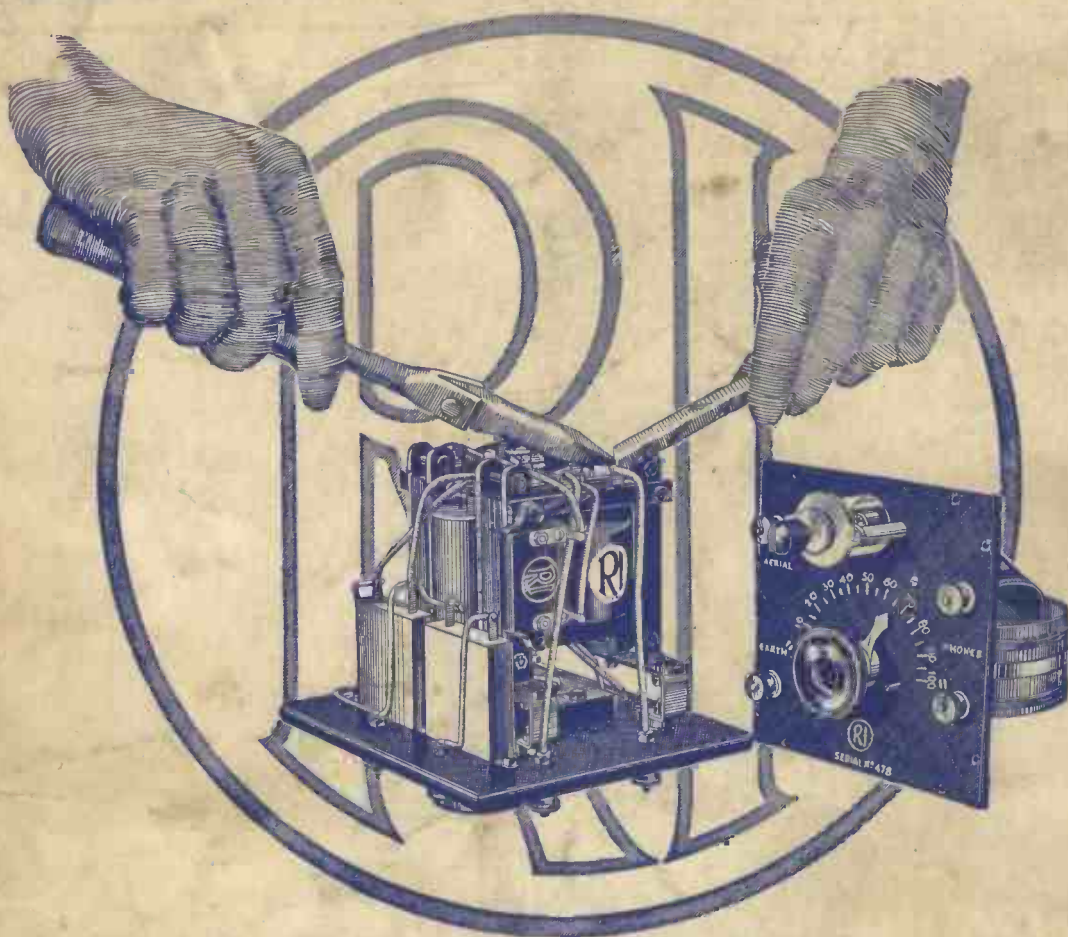Advertisements Managers for Radio Press publications.



IN EVERY DETAIL—

R.I. Components mark the peak of progress in Radio science. Years of experience lies behind them—successful years, in which inventive genius and the finest laboratory resources, were supported to an extreme by public appreciation. Just try the combination :—Two of the new R.I. transformers coupled with the R.I. detector, and results will proclaim the finest amplifying unit possible.

What another enthusiast says—

Messrs. Radio Instruments, Ltd., London.

"I should like to inform you that I am using two of your L.F. Transformers in a loud speaker public address system.

These transformers are giving every satisfaction and are standing up well with 160 volts on the plate using power valves.

The amplification is as good as a seven-valve resistance coupled amplifier and is not distorted.

I may say that within four days I burnt out five transformers of other makes. This will give you some idea of the test that your instruments are undergoing.

I shall be fitting two into my wireless set at a later date.

Yours faithfully,
 (Sgd.) Harry V. McCalla,
 Engineer Palace, Gateshead.

The New R.I. Transformer,
 25/-

With one year's guarantee
 and book of distortionless
 circuit diagrams.

The R.I. Detector, 8/6

Write for the new R.I.
 catalogue, free on application

Telephone: Regent 6214-5-6

Telegrams: "Instradio London"

Radio Instruments Ltd.

12 Hyde Street, Oxford Street W. I.