

Wireless World

RADIO • ELECTRONICS • ELECTRO-ACOUSTICS




AUGUST 1942

1/3

Vol. XLVIII No. 8

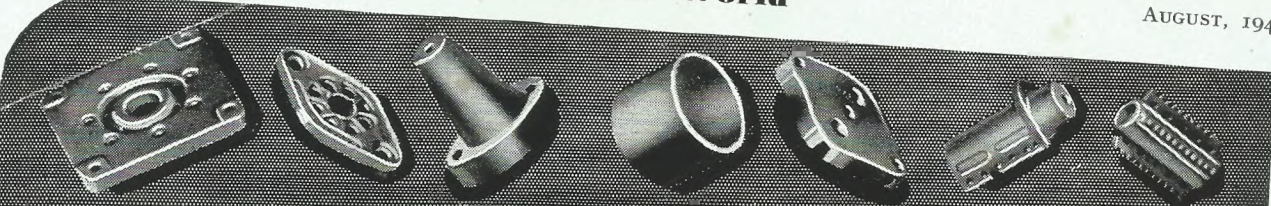TRANSFORMER DISTORTION ✦ IMPROVING THE DIODE



Going one better

IN COMMUNICATIONS



To-day, wherever Bullers Low Loss Ceramics are used, reception is clearer and better than ever before.

Years of research in Bullers Laboratories have developed these materials to such a high level of efficiency that Dielectric Loss is virtually eliminated. Bullers Ceramics are now playing a vital part in maintaining communications under all conditions.

**Made
in Three
Principal
Materials**

FREQUELEX. An Insulating material of Low Dielectric Loss. For Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX. A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX. A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

BULLERS LIMITED
THE HALL, OATLANDS DRIVE, WEYBRIDGE, SURREY
Telephone : Walton-on-Thames 2451
Manchester Office : 196 Deansgate, Manchester.


Bullers

LOW LOSS CERAMICS




46-range Model 7
 Universal AvoMeter

40-range Model 40
 Universal AvoMeter

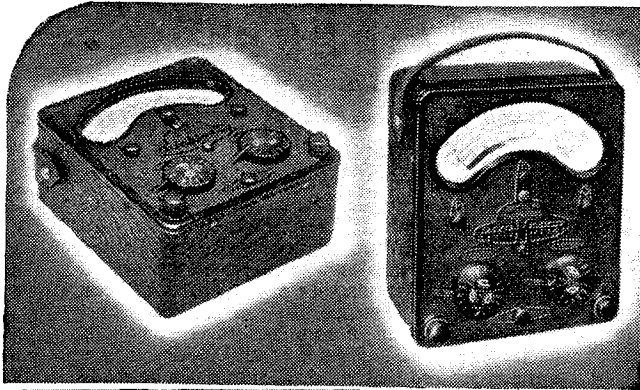

Meters that Matter

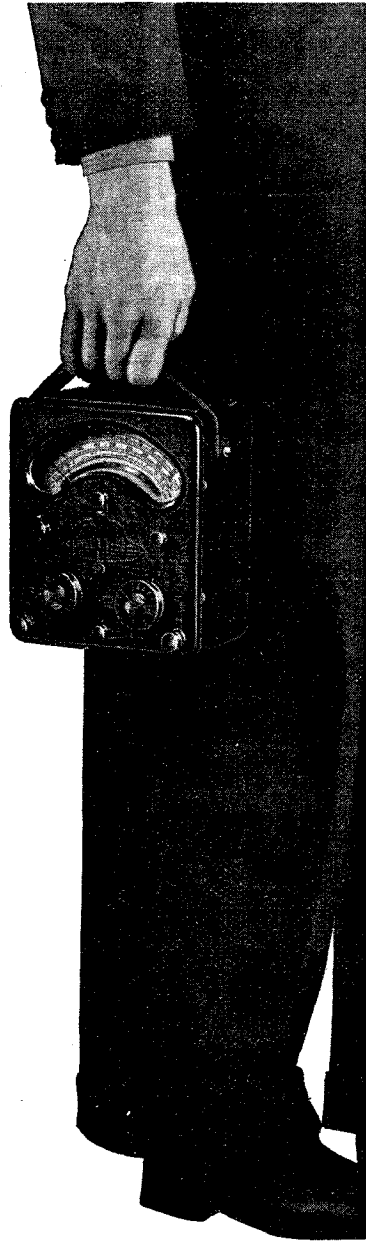

In every sphere of electrical test work . . . in the laboratory, the workshop, the service engineer's bench or "out on a job," . . . the word "AVO" is synonymous with instruments of precision. The "AVO" range embraces instruments for every essential electrical test. By reason of their reliability and maintained accuracy, even under the most searching of workshop conditions, they are frequently used as a standard by which other instruments are judged.

Write for literature fully descriptive of any "AVO" Instrument in which you are interested.


Sole Proprietors and Manufacturers:

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT Co. Ltd.
 Winder House, Douglas Street, London, S.W.1. Phone: VICTORIA 3404-7.

Some delay in delivery of Trade orders is inevitable, but we shall continue to do our best to fulfil your requirements as promptly as possible.


All-Wave "Avo" Oscillator

"Avo" Test Bridge

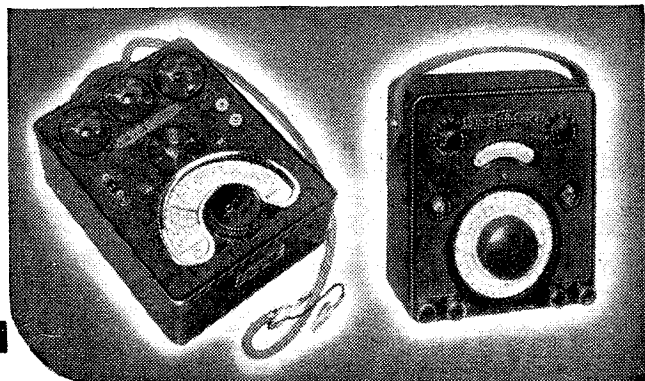

TAYLOR METER

This improved Taylor Model 90 instrument is soundly constructed and carefully adjusted to give accurate measurements over a very wide range. It is particularly suitable for all Radio and Electrical Measurements.

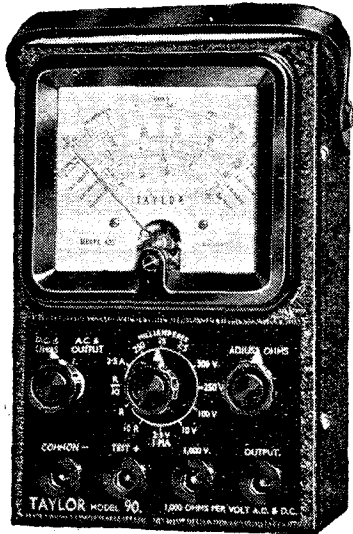

MODEL 90. Sensitivity 1000 Ohms per volt on all voltage ranges

TAYLOR 38 RANGE UNIVERSAL METER

The 38 ranges cover :—

- D.C. VOLTS** 7 ranges from 0-0.25 to 1000 v.
- A.C. VOLTS** 6 ranges from 0-2.5 to 1000 v.
- OUTPUT** 5 ranges from 0-2.5 to 500 v.
- D.C. CURRENT** 5 ranges from 0-1 mA. to 2.5 amps.
- A.C. CURRENT** 5 ranges from 0-1 mA. to 2.5 amps.
- RESISTANCE** 3 ranges from 1 ohm to 1 megohm with internal battery.
- RESISTANCE** 1 range from 1000 ohms to 10 megohms with external 60-volt battery.
- DECIBELS** 6 ranges from -22 db to +60 db.
- METER.** Five scales covering A.C. and D.C. measurements and also ohms and decibels. Scale Length. Outer scale is 3½ in. long.

Supplied complete with lead and test prods, internal battery and instruction book.

£11 - 11 - 0

TAYLOR METERS

In addition to our range of measuring instruments, we also manufacture five types of moving-coil meters from 2 in. to 5 in. in scale length.

Full details of Taylor Instruments and Meters sent on request.

TAYLOR

ELECTRICAL INSTRUMENTS LTD.
419, 422 Montrove Ave., Slough, Bucks.
Phone: Slough 21381.

P. R. MALLORY & CO. Inc. MALLORY

PRECISION RADIO PRODUCTS

It is in the interests of the cause for which the Allies are fighting that we cannot continue to supply you with Mallory precision radio products unless you possess the necessary Import Licences and Priorities. Mallory activities extend far beyond the manufacture of radio parts and our plant is busily engaged on work of National importance. Much of your service equipment is Mallory equipped and when conditions permit you can rest assured that we shall once again be ready to supply you with :—

MALLORY VIBRATORS AND VIBRAPACKS. MALLORY WAVE CHANGE AND CIRCUIT SWITCHES.

MALLORY F.P. ELECTROLYTIC CONDENSERS.

MALLORY TUBULAR AND PAPER CONDENSERS.


MALLORY GRID BIAS CELLS, PLUGS, JACKS AND OTHER PRECISION RADIO PARTS.

★ Register your name with our Representative now. He will forward you information on our products as soon as they become available.


P. R. MALLORY & CO. INC.
INDIANAPOLIS, INDIANA, U.S.A.

Represented exclusively in Gt. Britain by

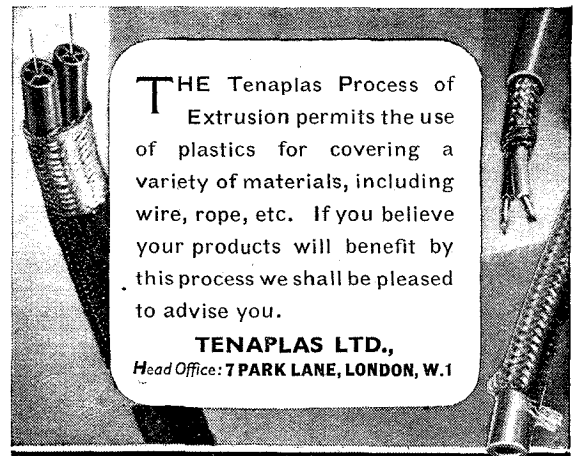
FRANK HEAVER LTD., Kingsley Rd., Bideford, N. Devon, Eng.



TENAPLAS
Extruded Plastics

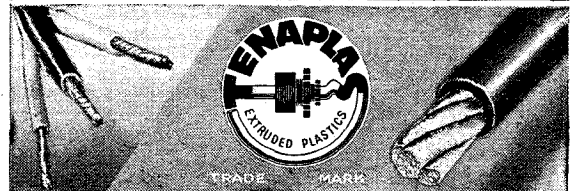

1 2 3 inches

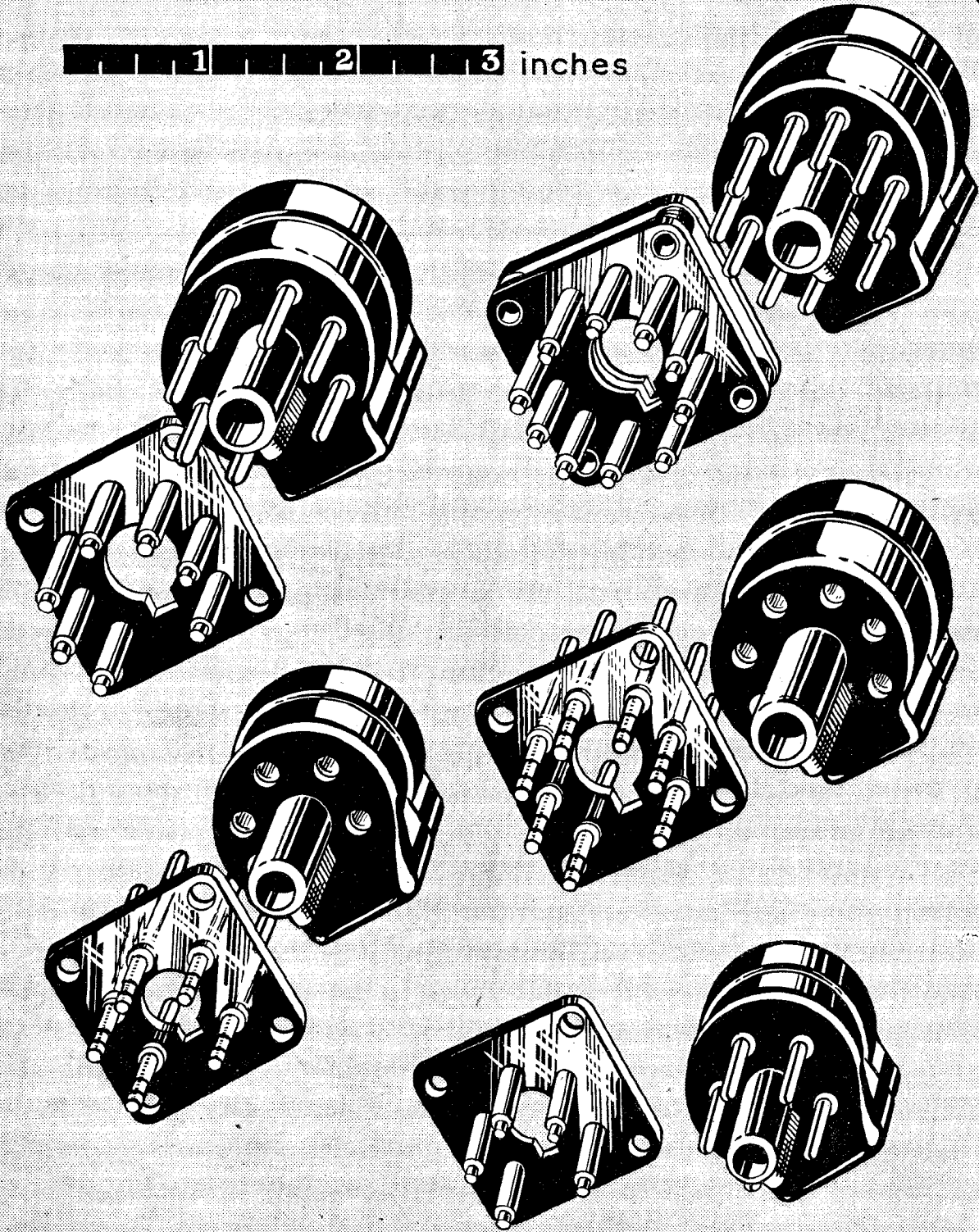

BELLING & LEE LTD
CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDDX

G.P. 5901

WEBB'S *Radio*

SPECIAL LIST OF radio components

Webb's wartime service still affords unique facilities for the radio-man. The following items are part of a large range of components in stock NOW! Call at our showrooms or post your enquiries to-day.

SHORT WAVE VARIABLE CONDENSERS

Cydon Midget 20 mmfd., ceramic end... 3/6
Eddystone Microdenser 18 mmfd., 4/6; 40 mmfd., 5/-; 60 mmfd., 5/6; 100 mmfd., 5/9; 16 mmfd.... 7/-
Wavemaster 250 mf., 150 mf. and 100 mf. ... 3/6
Transmitting Condensers, 40 x 40 split stator. Many types from stock. Slow motion drive condenser .00035 aluminium vanes, heavy type ... 8/6
Ceramic Trimmers, compression type, 250 mmfd., 450 mmfd. and 250 mmfd. ... 1/-
U.I.C. Trimmers and Fixed Condensers, all values in stock.

INTERVALVE TRANSFORMERS

I.F. 465 Kc. square can type ... 6/-
I.F. 465 Kc. small cylindrical ... 4/-

Low Frequency small shrouded, 3:1 ratio, 3 6;
heavier type ... 5/-
Small Ericsson L.F. Transformers, 2 1/4 x 1 3/8 x 1 1/2 ... 3/-

MISCELLANEOUS ITEMS

Push Back Insulated Flex (single), 1/- doz. yds.
Resistance Cord for A.C./D.C. Receivers, 100 ohms per ft. ... 2/-
Flexible Couplers for 1/2 in. shaft rubber insulation, each ... 4d.
80 ohm Concentric Cable (1/2 in. diam.), maximum length 150 ft. ... 8d.
Magic-Eye Adaptor Kit with instructions, 6/6; 6G5 Valve for same ... 11/-

VALVE HOLDERS

American Octal chassis mounting (Paxolin) ... 4d.
Ceramic (Amphenol) 5-pin, U.S.A. ... 2/-
Ceramic 4 and 5 (lemon), British ... 1/-

45-volt Burgess High Tension Batteries, heavy duty... 14/8

Collapsible Microphone Stands ... 42/-
Highest quality Moving Coil Microphone, with transformer ... £5/5

Taylor 0-1 ma. Moving Coil Meters, 3 1/2 in. flush mtg., £4; 4 in. rectangular ... £6/10

Aerovox 40 mfd. 200-volt Condensers, for Midget Receiver, at ... 6/6

Aerovox 30 mfd. + 32 mfd. 175 volts Condenser, for Midget Receiver, at ... 6/6

Aerovox .1 mfd. 1,000-volt Condenser, at ... 6/-


Side Contact Valve Holder, for E series valves... 6d.

Hivac Midget Valves, all types in stock.

Additional charge of 1s. for postage and packing on orders below 10s.

WEBB'S RADIO, 14 SOHO STREET, OXFORD STREET, LONDON, W.1
Telephone: GERrard 2089 Hours of Business 9 a.m. to 5 p.m. Sats. 9 a.m. to 12 noon

Transformers to
TROPICAL
specification

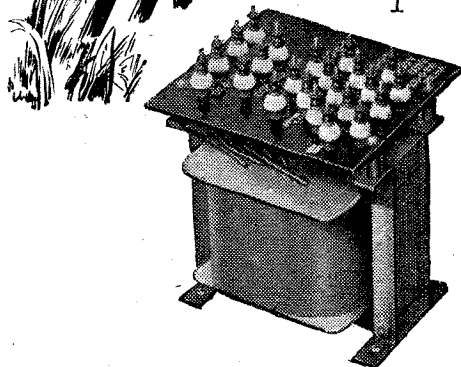

from 10 VA-10 kVA

Every precaution, including vacuum impregnation, special materials and exceptional care in manufacture, is taken to ensure that Woden Transformers made to tropical specification will give reliable service under the most arduous conditions.

WODEN Transformer Co.
THORNLEY STREET · WOLVERHAMPTON
TEL: WOLVERHAMPTON 22829


MAKERS OF TRANSFORMERS, POWER PACKS, & SPECIAL RECEIVING & TRANSMITTING APPARATUS

CELESTION

CELESTION-AMPHENOL


valveholders are preferred by radio engineers because of their Strength, Efficiency, Uniform Contact and exceptional Insulation.

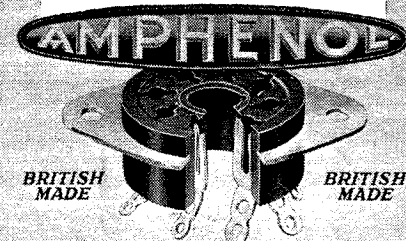All standard British and American types are available.




CELESTION LTD.
(Engineers).
KINGSTON-UPON-THAMES, SURREY.
Telephone: KINGston 5656-7-8.

SYMBOLS OF PRECISION

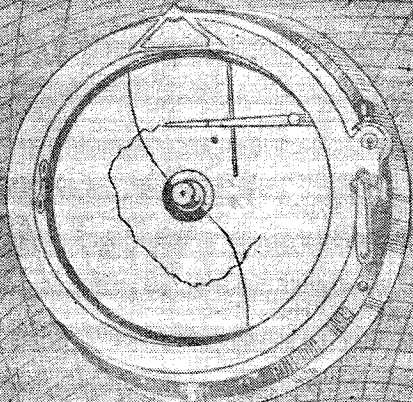

TEMPERATURE RECORDER

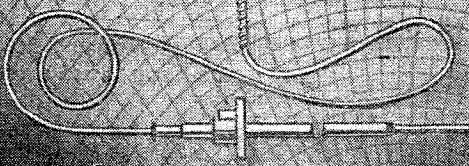


MAZDA RADIO VALVES

Mazda Radio Valves are manufactured in Gt. Britain for the British Thomson-Houston Co. Ltd., London & Rugby, and distributed by

THE EDISON SWAN ELECTRIC CO. LTD  155 CHARING CROSS RD., LONDON, W.C.2

For full particulars write to Technical Service Department

"to Insulate"

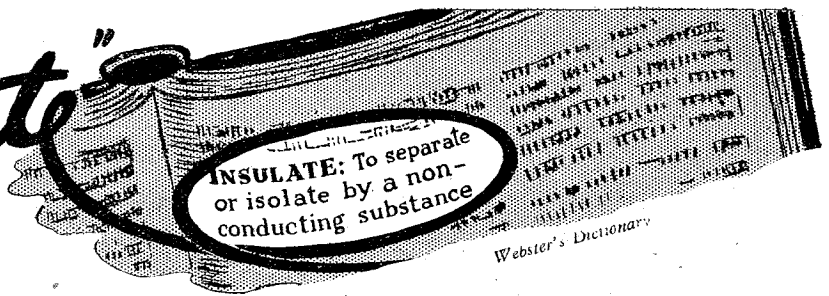

Practically all waxes are used to "separate or isolate," but the degree of insulation provided by the different types of waxes varies enormously.

There is obviously no higher degree of insulation required than that of electrical components and apparatus in intense electrical fields, especially in the extremes of conditions to which they are subjected to-day.

We specialise in the supply of
WAXES *for all*
purposes - under all conditions

Our technical advice is at your disposal.

If you have any problem of

IMPREGNATING—DIPPING—FILLING

we, as consultants to the Industry, shall be glad to offer you a solution.

CLAUD CAMPBELL & CO. LTD.

4, LLOYDS AVENUE — LONDON — E. C. 3.

Telephone Nos. :—ROYAL 5403/4/5.

AMPLIFIERS
MICROPHONES
LOUDSPEAKERS

R'S Spells Quality

Just so long as there is R'S in Public Address Equipment, so long will you be able to rest assured that not only is quality that intangible something that is usually associated with the term, but that it is visible in the appearance, proven in the reliability and audible in the performance of every item we offer.

R'S

Amplifiers Limited

3-4, Highfield Rd., Shepperton, Middlesex
 Telephone: Walton-on-Thames 1019

RAYTHEON

RECEIVING-TRANSMITTING TUBES

Millions of Raytheon tubes are going into Allied defence equipment, yet we are still able to cater for set manufacturers and civilian replacement needs in the U.S.A. As soon as circumstances permit we shall be able to take care of your needs as well and give you those better tubes that you were accustomed to receive before your import restrictions were announced. Raytheon is a name to remember for the future—you can place your complete confidence in Raytheon Radio Receiving and Transmitting Tubes.

Register your name with our Representative now. He will forward you information on our products as soon as they become available.

RAYTHEON PRODUCTION CORPORATION
NEWTON, MASS., U.S.A.

World's Largest Exclusive Radio Tube Manufacturer.

* * *

Represented by
Frank Heaver Ltd. Kingsley Road, Bideford, N. Devon.

RADIO BOOKS

RADIO RECEIVER CIRCUITS HANDBOOK

By E. M. Squire. This book is a useful guide to circuits for members of the radio industry, and radio amateurs, containing practical notes on the operation of basic modern circuits. The text is liberally illustrated with circuit drawings and other diagrams. Second edition. 5s. net.

RADIO RECEIVER SERVICING AND MAINTENANCE

By E. J. G. Lewis. A practical manual specially written to give the radio dealer, salesman and service man up-to-date assistance in the technical details of his work. A handy fault-finding summary, combined with the index, is a feature of the book. Third edition. 8s. 6d. net.

SHORT-WAVE RADIO

By J. H. Reyner, B.Sc. (Hons.), A.C.G.I., etc. This book gives an account of the tremendous progress which has been made in the field of short-wave radio telegraphy during the last few years, and shows how many of the problems formerly regarded as insuperable have been overcome. It gives a comprehensive survey of the available data concerning these waves, and of the practical methods by which they have been harnessed for radio and television transmissions. Second edition. 10s. 6d. net.

PITMAN'S, PARKER STREET, KINGSWAY FOR RADIO MEN

NEVILLE'S

SPECIALISTS

in the design and manufacture of
COIL WINDING MACHINES
TAPING MACHINES
WIRE COVERING MACHINES
ARMATURE AND STATOR
COIL WINDERS

AND SIMILAR SPECIALISED
MACHINERY FOR THE ELECTRICAL
AND ALLIED INDUSTRIES



Contractors to the
Admiralty and . . .

other Government
Departments

NEVILLE'S (LIVERPOOL) LIMITED

SIMMONDS TOWER · GREAT WEST ROAD · LONDON

Please address all enquiries to Western Office:
City House, St. Stephen Street, Bristol, 1.

A DIVISION OF THE SIMMONDS GROUP

U.I.C.

Fixed Condensers with Ceramic Dielectric. Small size. Mechanically and electrically stable.

Type approved.

Full details and advice gladly given.

UNITED INSULATOR CO. LTD.


12-20, LAYSTALL ST., LONDON, E.C.1

Phone: TERminus 7383. Grams: Calanel, Smith, London

Contractors to G.P.O. and Government Departments. On A.I.D. Approved List.

Silvered Ceramic Condensers

HAT TYPE

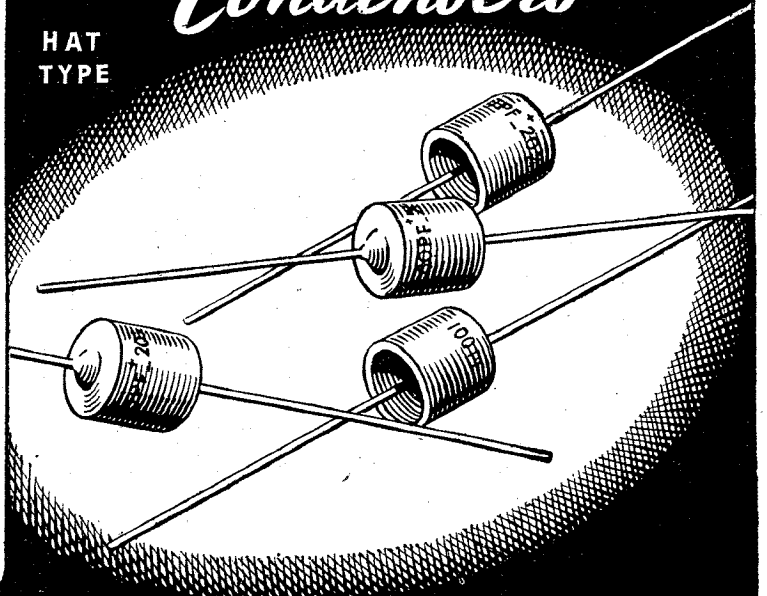

The Pioneers of Low Loss Ceramics

M.R. SUPPLIES


have the following first-class and brand new goods in stock and (subject to no prior bulk clearance) can effect delivery by return. All prices strictly nett.

To-day's Greatest MICROPHONE OPPORTUNITY

Rothermel - Brush Piezo - Crystal

Microphones.

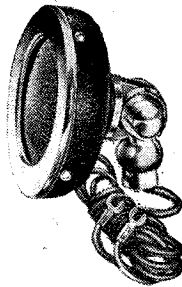Outstanding performance and appearance. Fitted latest piezo-electric generating agent. Level response to about 8,000 c/s. Output—60 d.b. Satin-black housing with plated bezel and knuckle-joint for angle adjustment. Mounting thread is 1/8 in. Complete with 6ft. screened lead. 72/6 nett.



Several hundreds now in use on exacting work for important users.

HAND MICROPHONES. Low resistance carbon type, suitable for use in conjunction with L.R. Phones without amplifier. Ideal for field or factory use. Well-housed in black bakelite with 5in. handle, 22/6.

INDUSTRIAL LOUDSPEAKERS. New 8-watt P.M. moving-coil model, housed in 10in. grey enamelled metal drum with front and rear grille, fitted heavy duty multi-tapped transformer, 49/6. (NOTE.—We have to make a charge of 3/- each for packing and despatch.)

L.F. CHOKES. 10-henries at 200 m.a., 100 ohms D.C. res., 13/6.

SLIDING RHEOSTATS, 100-watts cap. Fully enclosed with smooth, positive action. Full range again in stock: 4 ohms 5 amps., 10 ohms 3 amps., 50 ohms 1.5 amp., 100 ohms 1 amp. and 400 ohms 0.5 amp. Any one, 21/-.

ELECTRIC SOLDERING IRONS, best makes from stock. All industrial models for continuous use. 220/240 volts. Stanelco, 75-watt, 21/-. 150-watt (massive bit), 32/6. Acru (with interchangeable bit—2 1/4 in. pointed bit supplied, others available at 4/- each), 100-watt, 28/6.

RESIN CORED SOLDER, 40/60 alloy 13 s.w.g., on 1 lb. reels, 3/9 per reel, post paid.

HEADPHONES (by best makers). Here in stock—no waiting. 4,000 ohms. Maker-boxed, G.E.C., 22/6 pair. Ericsson's, 25/- pair.

GEARED HIGH TORQUE MOTORS, constant speed induction, 200/250v. A.C., final speed 3 r.p.m. in metal housing 4 1/2 in. dia. and 3in. high, silent running and precision made, with flex and plug, 39/6. Very useful in research depts., etc., for recording instruments.

Please include sufficient for packing and postage—excess refunded.

Will our customers please note that these premises will be closed from the 10th to 15th August (inclusive).

M.R. SUPPLIES, 68, New Oxford St., London, W.C.1

(Phone: MUSEum 2958)

ROLA

LOUD SPEAKERS

THE WORLD'S FINEST REPRODUCERS

TRANSFORMER LAMINATIONS

Core Widths 3/8" to 1 1/2" (E's and I's.)

EIGHT STOCK SIZES



A Comprehensive Bulletin together with details of Associated Covers and Clamps with design data will be sent to manufacturers on request.

BRITISH ROLA LIMITED

MINERVA ROAD · PARK ROYAL · N.W.10 · WILLOden 4322

VACUUM


*The Invisible Protection
for Filament Emission*

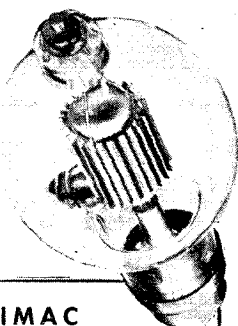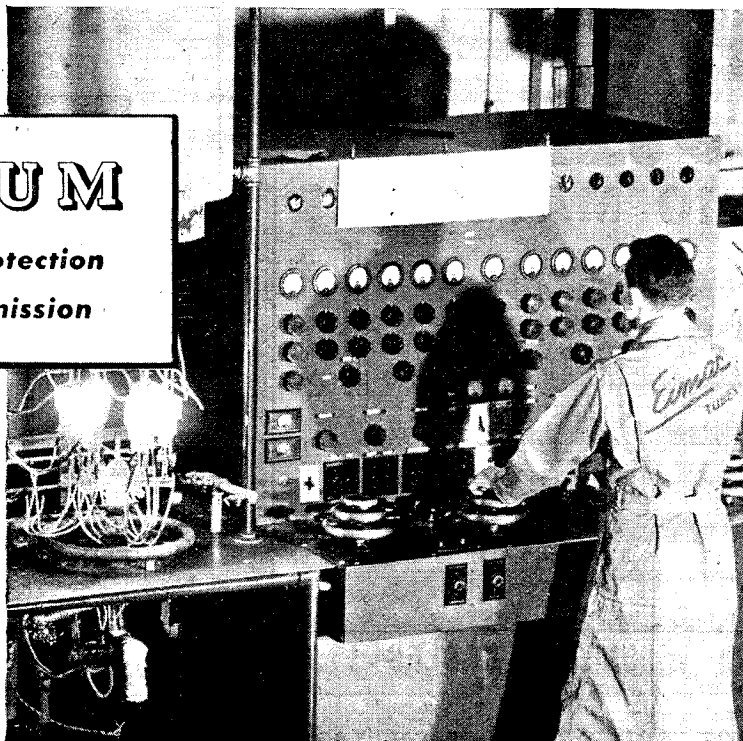


EIMAC 2000T

Filament Voltage 10 volts
Plate Voltage up to 6000 volts
Plate Dissipation - 2000 watts
Power Output (75% eff.)
6000 watts

Like a solid coat of armor-plate, hard, high vacuum protects filament emission in every Eimac valve. Extremely efficient evacuating pumps developed and built in the Eimac laboratories for the precise purpose of producing the highest possible degree of vacuum are shown in action above. It is this excellent vacuum that proved the idea fallacious that plate temperature destroyed emission...caused premature failures. Chiefly because of this processing, Eimac valves today, and in past years, have provided longer life, greater stamina and vastly superior performance.

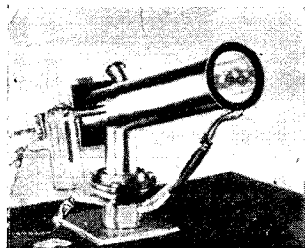

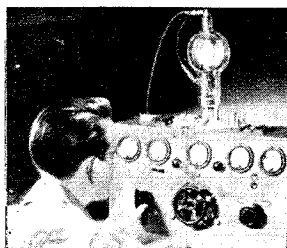ELECTRON MICROSCOPE virtually gives a moving picture projection of the action of electrons being emitted from a heated filament. Such observations enable Eimac engineers to constantly produce better filaments.



PEAK EMISSION TESTER measures the flow of electrons from the filaments of completed Eimac valves. Of the long series of gruelling tests made to insure more efficient filament emission in every Eimac valve, this is the final test.



FLASH FILAMENT TESTER checks filaments before valves are assembled and pumped. Here valves are placed under a temporary vacuum, heated to much higher temperatures than will ever be required in normal use. Only perfect filaments reach the final stages of manufacture.

In Peacetime or Wartime... wherever you look...in the air, on land and at sea... you'll find Eimac valves doing their bit. Right now the Armed Forces get first call on our facilities and Eimac valves are receiving enthusiastic acceptance from all quarters.

Follow the Leaders to

Eimac
VALVES

Manufactured by
Eitel-McCullough, Inc., San Bruno, California, U. S. A.

FOREIGN DIVISION: FRAZAR & CO., LTD., 301 CLAY STREET, SAN FRANCISCO, CALIFORNIA, U. S. A.

B.I.


RADIO MATERIALS

We have had a long experience in the manufacture of all kinds of Cables and Wires, Static Condensers, Insulators and Iron Work, Telephone Cords and Copper Earthing Rods, for Radio use.



U.K. Regd. Trade Mark.

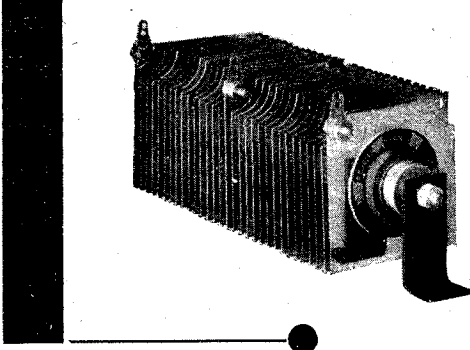BRITISH INSULATED CABLES LTD.
CABLE MAKERS AND ELECTRICAL ENGINEERS
Head Office:
PRESCOT, LANCS. Tel. No. PRESCOT 6571



Designed for **RELIABILITY**
Built for **RELIABILITY**
And *proved* in actual service
to be **THE WORLD'S MOST**
RELIABLE

WESTINGHOUSE


metal rectifiers

Write to Dept. W.W. for a copy of "The All Metal Way," price 3d.

Westinghouse Brake & Signal Co. Ltd., Pew Hill House, Chippenham, Wilts

WHARFEDALE

FACTORY SPEAKER

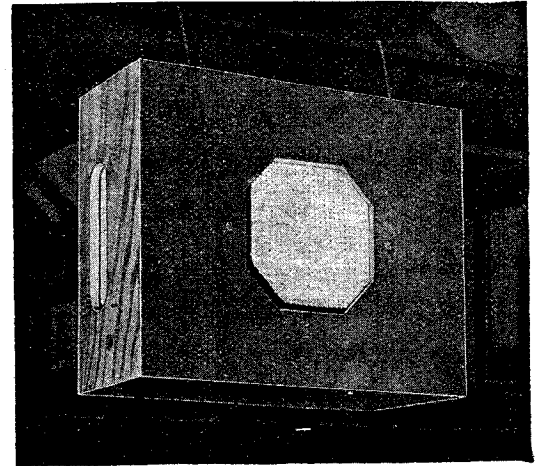

Available with or without Volume Control or Remote Control. REVERSIBLE. Fitted with 10" BRONZE UNIT for 5 Watts input.

PRIORITY ORDERS ONLY.

WHARFEDALE WIRELESS WORKS

SOLE PROPRIETOR: D. E. BRIGGS
HUTCHINSON LANE • BRIGHOUSE • YORKS
PHONE: BRIGHOUSE 50 "GRAMS: "WHARFEDALE"



**EQUIPMENT
AVAILABLE
for
PRIORITY
CONTRACTS**

C.40. Mains- and battery-driven 30-watt amplifier—Twin channels, independently controlled, employing nine standard service valves—Four inputs—Output stage operated as Triodes or Tetrodes—Bass and treble controls—Variable output impedance—etc. (as illustrated).

C.30. 30-watt amplifier for 12-volt operation only—Inputs for microphone and gramophone—Standby switch—Tone control—etc.


M.30. As type C.30, but operated from 200/250-volt 40-100 c.p.s. mains.

for AMPLIFIERS, TRANSFORMERS
AND ALL PA. EQUIPMENT

ACOUSTICAL


MANUFACTURING COMPANY LTD
HUNTINGDON 'TEL: 361

G.P.O. MORSE KEY & BUZZER UNIT

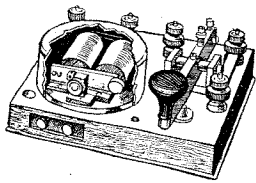

We have only a small number of these instruments left. Made for professional use. All parts of heavy solid brass mounted on mahogany base. The Key is fitted with platinum contacts. An excellent opportunity for those requiring a robust unit which will give years of service Price **45/-**

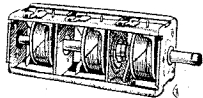
PHILIPS 3-GANG CONCENTRIC SPIRAL VANE VARIABLE CONDENSERS



.0005 mfd. without trimmers. As used in Philips well-known Push Button receivers. Price **4/6**

SPEAKERS

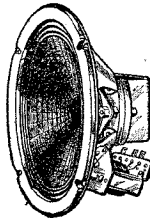ROLA. Brand new 8in. P.M. moving coil, with transformer for super power or pentode valve. Fine cadmium plated chassis **27/6**



CELESTION 8in. P.M. moving coil, pentode output. New... **25/6**

GOODMANS 8in. P.M. moving coil Universal transformer, suitable for all output valves **27/6**

MOVING IRON D.C. VOLTMETERS



A good quality panel mounting meter with clear-reading 2 1/2 in. dial. Voltage measurement 0-9 v. Fitted with terminals at back. Brand new. Price **20/-**

LONDON CENTRAL RADIO Opportunity Column

BELLING & LEE. 5-pin Valveholders. 1/- each.
SCREENED WIRE, 7/026 SWG, rubber covered 1/9 per yard.
ASSORTED RESISTORS. 3/6 per dozen.
REACTION CONDENSERS. Mica spaced. 0.0003 mfd, 2in. spindles. 2/- each.
VALVES are in short supply; stock of Mullard T.S.P. 4's and H.V.R. 2's to be cleared at 15/- each; first come, first served.
CONDENSERS.—Special offer of metal-cased paper condensers, 300 v. working, all brand new and unused 2 mfd. 2/-, 1 mfd. x 1 mfd. 1/9, 1 mfd. 1/9.
VARIABLE CONDENSERS, well made heavy 3-gang superhet condensers, die cast frames in first class condition. 5/6 each.
BULGIN HIGH VOLTAGE ANODE VALVE CAPS. 9d. each.
DECORATIVE CABINET GRILLES, 4-bar 14 1/2 in. x 1 1/2 in. wide. Solid brass chrome plated. 2/6 each.
PHILIPS HIGH VOLTAGE CONDENSERS. 1 mfd. 5,000 v. D.C. working. 10/6 each.
TRIMMERS.—Twin trimmers on ceramic base, brand new; to clear, 6d. each; 5/- doz. Also Bakelite Strip containing 5 Postage Stamp Trimmers, 2/6.
TUBULAR WIRE-END CONDENSERS, brand new first quality components, 0.0003 mfd., 8d.; 0.005 mfd 9d.; 0.01 mfd., 10d.; 0.1 mfd., 1/- each.

★ ONLY A FEW LEFT! ★ BAIRD TELEVISION RECEIVERS

Model T.26. Brand New. Offered at the cost of parts only
 See June advertisement for full details

- **SMALL TRICKLE CHARGERS,** Skeleton Type. Metal rectification. Input 200-220 v. A.C. Output 2 v. 1/2 amp. Reliable and Shockproof Price **17/6**
- **SINGLE R.A.F. EARPHONES,** resistance 750 ohms D.C. approx., 4/- each; ex-Govt. low-resistance single earphones, 2/6 each; microphone buttons, well-known make, 2/- each.
- **MAINS TRANSFORMERS.** Originally made for Television Power Packs where accuracy and robustness are essential. Weight 12 lb. Size 5 1/2 in. x 4 1/2 in. overall. 350-0-350 v. 120 m.a. Tapped. 4 v. 2 a.; 4 v. 8 a.; 3 v. 3 a.; 20 v. 1 a. Diagram free. Post and packing 1/6 **25/-**
- **G.E.C. MOTORS,** 1/100th H.P., A.C. 225 v. 50 **47/6**
- **HEAVY DUTY MAINS TRANSFORMERS.** Input 240 v. A.C. One tapping at approx. 5,000 v. max. 3 m.a., and one for supplying filament of Mullard H.V.R. 2 (6.3 v. at .65 amp.). Shrouded in metal box. Car. fwd. **10/6**
- Also input 200-250 v. A.C., approx. 6,500 volts. Shrouded in metal box. Car. fwd. **20/-**
- **B.I. CONDENSERS.** 1 x 1 mfd. 7,000 volts D.C. test, with porcelain insulators **30/-**

— FOR CALLERS ONLY — PAPER SPEAKER CONES

Less Speech Coil, 7" dia. 9d., 6" dia. 6d.
BAKELITE SPEAKER H.F. DIFFUSER CONES
 2 1/2" dia. x 2 1/2" long, 6d. each.
 3 1/2" dia. x 2 1/2" long, 9d. each.
— MANUFACTURERS PLEASE NOTE! —
 Special prices quoted for large quantities of the above. Enquiries are invited.


BAIRD TELEVISION POWER PACK & AMPLIFIER CHASSIS

Includes heavy mains transformer 350-0-350, 120 m.a., with 4 tappings. High voltage transformer for supplying C.R. tube. Various condensers including 16 x 16 mfd. 550 v. working, 1-16 mfd. 450 v. working, 50 x 50 x 2 mfd. B.I. Electrolytics, etc. Pentode output trans-


former; chokes; resistors; trimmers; bias electrolytics; mica and tubular condensers; short-wave coils, etc. Workmanship and components are of the highest quality. Valve diagram free. Carriage forward. **£3.17.6**
 Add 2/6 for packing.

PLUGS AND JACKS

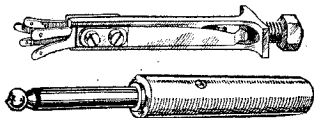These ex-Govt. Jacks have powerful phosphor-bronze springs ensuring a perfect contact. Overall length, including 1/2" threaded shank, 3 1/2 in. Supplied with nut for panel mounting. Price complete with best quality Plug (as illustrated) Plugs only, 2/-, 5/6




PHILIPS HIGH VOLTAGE TRANSFORMERS

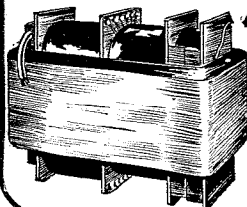

Robust in construction; weight approx. 13 lb. Dimensions: 5 1/2 x 5 1/4 x 4 1/2 in. Specification: 350-0-350 v., 70 m.a. Four tappings giving 4 v. 3 amps., 6.3 v. 4 amps., 4 v. .65 amp. and 4,000 v. at 3 m.a. Input 100/250. Free wiring diagram. Carriage fwd. Price **32/6**


PHILIPS SMOOTHING CHOKES

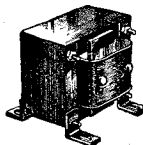Brand new well-built chokes, 60 ohms D.C. resistance 400/120 m.a. Core size: 2 1/2 in. by 2 1/2 in. by 1 1/2 in., 5/6 each. Also 400 ohms D.C. resistance 60 m.a. Core size: 1 1/2 in. by 1 1/2 in. by 3/8 in., 3/6 each.



VARIABLE POTENTIOMETERS

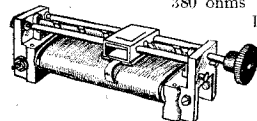380 ohms 10 watts. Low price to clear. **7/6** Each.




● **PLEASE NOTE.** Write your name and address in Block Capitals. You should order only from current advertisement, as many lines soon go out of stock. No orders can be sent C.O.D. Orders cannot be accepted from Eire or Northern Ireland. Postage must be included with all orders.

LONDON CENTRAL RADIO STORES

23, LISLE STREET, LONDON, W.C.2.

Telephone: GEBRard 2969.

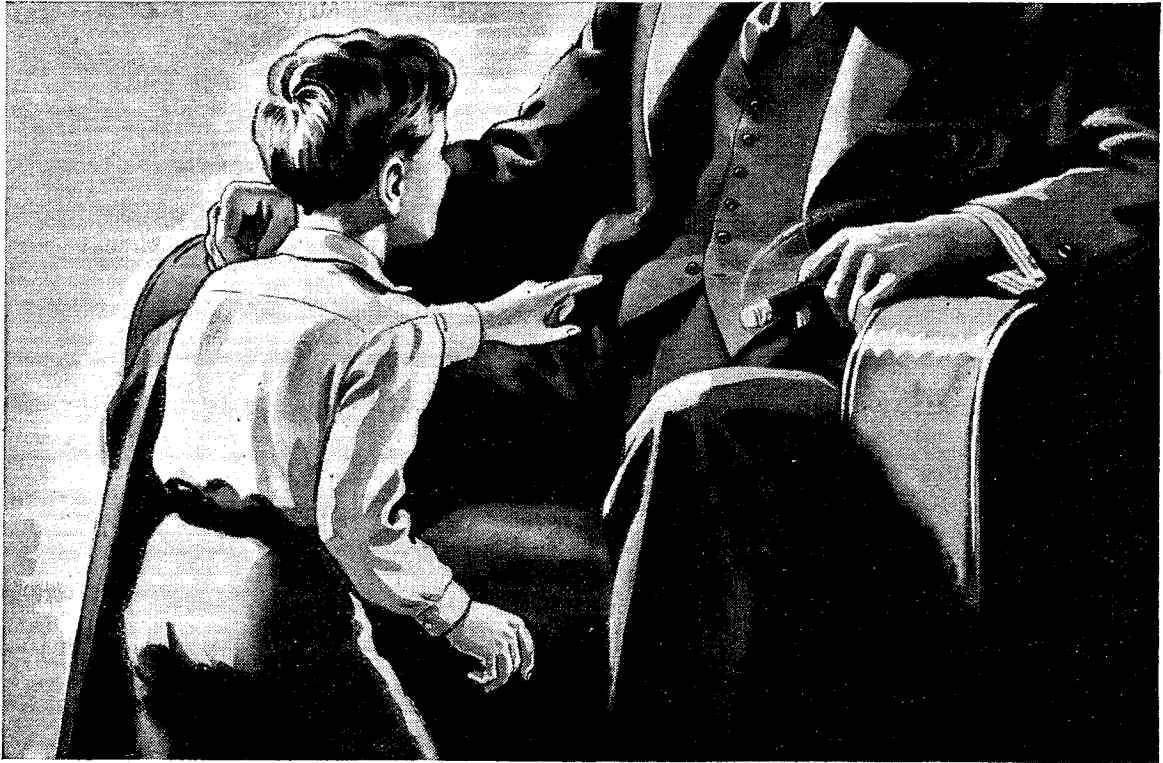

“Pray, what is the reason of that?”

IT has taken a war and an Act of Parliament to remove the bottom waistcoat button from its traditional idleness. Searching minds are likewise demolishing tradition with the vital question—“Why do we go on doing that?”

In many widely separated fields the application of new products by the Simmonds Organisation has achieved the utmost economy in man-hours and costs. The opportunity is there. Looking forward betimes today will spare the pain of disillusioned retrospection tomorrow.

S I M M O N D S

THE SIMMONDS “S.A.” NUT
SIMMONDS-CORSEY CONTROLS
SIMMONDS CONTENTS GAUGES
FOR AIRCRAFT.
SIMMONDS POSITION INDICATORS
SIMMONDS ELECTRIC TEMPERATURE
AND PRESSURE GAUGES
SIMMONDS AIRCRAFT FLOORING



SPIRE “S.A.” NUTS
FRAM OIL & ENGINE CLEANER
SIMMONDS INDUSTRIAL AND
MARINE CONTENTS GAUGES
SIMMONDS JOINTING COMPOUND
SIMMONDS CRYSTAL UNITS
SIMMONDS-GOUDIME
NAVIGATIONAL INSTRUMENTS

SIMMONDS AEROCESSORIES LTD

A COMPANY OF THE SIMMONDS GROUP
LONDON · MELBOURNE · PARIS · NEW YORK

P.7.

ALL ENQUIRIES TO GREAT WEST ROAD, LONDON.

Wireless World

Radio • Electronics • Electro-Acoustics

32nd YEAR OF PUBLICATION

AUGUST 1942

Proprietors :
ILIFFE & SONS LTD.

Managing Editor :
HUGH S. POCKOCK,
M.I.E.E.

Editor :
H. F. SMITH.

Editorial, Advertising
and Publishing Offices :

DORSET HOUSE,
STAMFORD STREET,
LONDON, S.E.1.

Telephone:
Waterloo 3333 (35 lines).

Telegrams:
"Ethaworld, Sedist, London."

△

PUBLISHED
MONTHLY

Price : 1/3

(Publication date 20th
of preceding month)

Subscription Rate
Home and Abroad
17/- per annum.

EDITORIAL	177
TRANSFORMER DISTORTION. By N. Partridge, Ph.D., B.Sc. (Eng.), A.M.I.E.E.	178
INSTRUMENTS—V: BEAT FREQUENCY OSCIL- LATORS. By W. H. Cazaly	183
" WIRELESS WORLD " BRAINS TRUST.—No. 3 ..	185
IMPROVING THE DIODE DETECTOR. By George A. Hay, B.Sc.	186
UNBIASED. By Free Grid	188
MORSE METHODS	189
CONDENSER SMOOTHING. By E. H. W. Banner, M.Sc., M.I.E.E., F.Inst.P.	190
LETTERS TO THE EDITOR	192
RANDOM RADIATIONS. By " Diallist "	196
THE WORLD OF WIRELESS	197
NEWS IN ENGLISH FROM ABROAD	198
RECENT INVENTIONS	200

Branch Offices :

COVENTRY :

8-10, Corporation Street.
Telephone: Coventry 5210.
Telegrams: " Autocar, Coventry."

BIRMINGHAM :

Guildhall Buildings,
Navigation Street, 2.

Telephone:
Midland 2971 (5 lines).

Telegrams:
" Autopress, Birmingham."

MANCHESTER :

260, Deansgate, 3.

Telephone:
Blackbriars 4412 (4 lines).

Telegrams:
" Iliffe, Manchester "

GLASGOW :

26B, Renfield Street, C.2.

Telephone: Central 4857.
Telegrams: " Iliffe, Glasgow."

△

As many of the circuits and apparatus described in these pages are covered by patents, readers are advised before making use of them, to satisfy themselves that they would not be infringing patents.

WEARITE


VIBRATORS

for Dependable Power

Representing the result of several years research into Vibratory technique, they embody the most recent developments of both British and American Design and are manufactured in this country under "OAK Manufacturing Company's" Patents 460470, etc., etc.

• • •

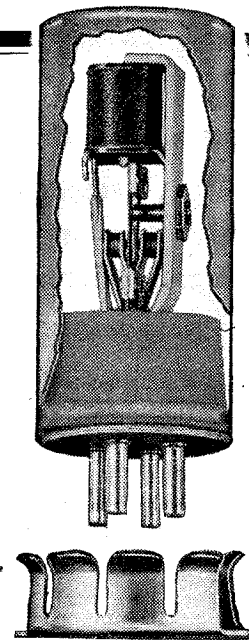
Our technical staff will be pleased to co-operate in the solution of **your** Vibratory problems.



WRIGHT & WEAIRE LTD.

HIGH ROAD, TOTTENHAM, N.17.

Telephones : Tottenham 3847-8-9

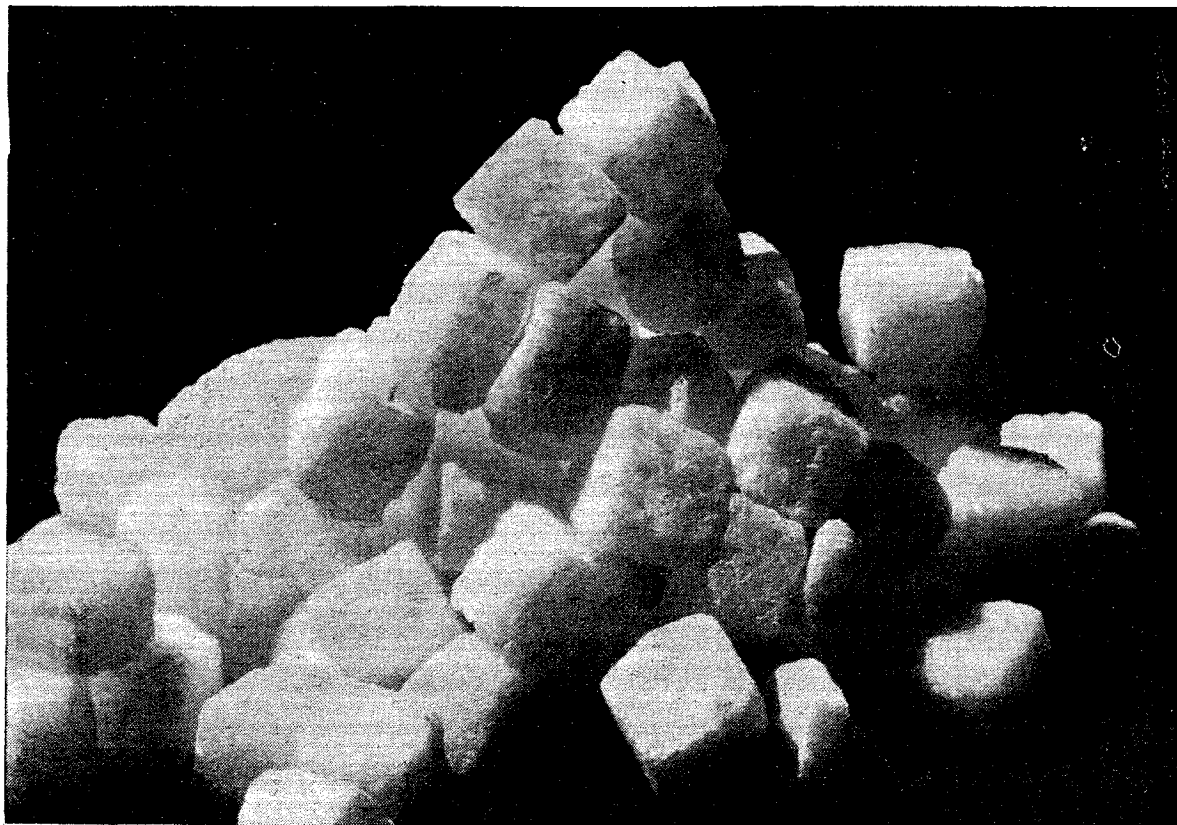

Valves and sugar

To the industrial chemist sugar is a product requiring constant and careful analysis to maintain the prescribed standard of quality. One of the tests is to determine its 'ash content', and a method in common use is to compare the electrical conductivity of a prepared solution against a known standard by using a balanced bridge circuit — and there are Mullard Valves for this purpose.

In every branch of industry and research, problems constantly arise demanding more exacting standards of comparison, more sensitive equipment, and closer control of industrial processes.

In many cases the answer is to be found in the application of the radio valve — and that is where Mullard come into the picture with the right valve for the purpose.

MULLARD
THE MASTER VALVE

A Valve for Every Purpose

DOMESTIC · COMMERCIAL · INDUSTRIAL · SCIENTIFIC · MEDICAL · EXPERIMENTAL

THE MULLARD WIRELESS SERVICE COMPANY LIMITED, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2. (35B)

Wireless World

Radio • Electronics • Electro-Acoustics

Vol. XLVIII. No. 8

AUGUST 1942

Price 1s. 3d.

A British "Austerity" Set ?

Ensuring Continuance of Broadcast Reception

WRITING only a month or two after the outbreak of the present war, we discussed its retarding effect on various branches of wireless development and suggested that, before peace returned, we might be forced to receive the B.B.C. transmissions on apparatus that savoured more of 1922 than of 1939. The time has now come to face that unpleasant possibility squarely.

Broadly speaking, there seems to be two ways of ensuring that the majority of the population may still have facilities for receiving British broadcasting. The first is to devote a sufficient proportion of our wireless productive power to the manufacture of the replacement valves and components necessary to maintain existing receivers. The second is to embark on the large-scale production of a standard receiver of extreme simplicity which will be used to replace existing sets as they go out of commission through breakdown.

Of these alternatives, the policy of providing replacement components is probably the more economical in materials, but more wasteful in everything else, not excluding man-power. The strongest objection that can be urged against it is that the replacement of a defective part calls for a skilled service-man, who in many cases is not available nowadays. Again, the manufacture and distribution of the wide diversity of valves and components needed for the upkeep of old sets is far from being an efficient process. But, while facilities for the maintenance of these old receivers still exist, they should, of course, be used.

The introduction of an ultra-simple and strictly standardised receiver would appear to offer many advantages, in spite of the relatively larger consumption of raw materials involved in such a plan. Given a suitable design, servicing difficulties should be almost non-existent, and any troubles that might develop could be put right by almost any intelligent person after a few weeks of well-planned

intensive and specialised training. The kind of receiver we have in mind would be designed and manufactured as a united effort of the radio industry as a whole, and production on a scale sufficient to meet the need for replacements of inoperative receivers would account for a very small proportion of our total wireless productive capacity. To ensure maximum economy, the work would probably be distributed among a number of firms, each one making those components for the production of which they are best fitted. Similarly, assembly of the receivers could be allocated with a view to efficiency of distribution. Of course, both battery and mains models would be needed, but everything possible should be done to avoid a multiplicity of types.

Limitations of Crude Sets

One objection to a relatively crude, unselective and insensitive set is that it may prove inadequate over wide areas of the country so long as broadcasting is carried out on the present system. That, however, does not seem to be an insuperable objection; it has already been suggested in these columns that the original reasons for adopting our wartime system of broadcasting may no longer apply, and that a change might be made without giving help to the enemy.

The circuit arrangement of a British "austerity" receiver would naturally be chosen after the most careful consideration of all the factors involved. The subject is one on which it is interesting to speculate, but perhaps it may be found that the case is best met by something technically no more exciting than a simple detector—AF combination. But, as we said in 1939, when first discussing the possibility of being compelled to revive out-of-date devices, there is no harm in applying to their improvement the knowledge gained during the intervening years.

TRANSFORMER DISTORTION

SEVERAL years ago the writer contributed to *Wireless World* a series of articles dealing with harmonic distortion in audio frequency transformers. These articles were based upon an original method of attacking the problem, and, at the time of publication, constituted the most complete and constructive review of the subject then available. But much remained to be done before the suggestions presented could be regarded as a definite contribution to knowledge in the scientific sense.

Therefore a rather ambitious research was set in motion. The original plan was developed, modified and expanded, finally to emerge in the form of a new technique to which academic recognition has been accorded.

Those who may wish to study the development of the new method in detail are referred to a recent Brit.I.R.E. paper,¹ and to a further article shortly to be published in *Wireless Engineer*. Here an attempt will be made to show in simple terms how iron distortion comes about, and to indicate how in practice its magnitude may be calculated.

Current and Voltage Distortion

A transformer does not ordinarily produce harmonic distortion within itself. For example, suppose the primary of a transformer to be directly connected to a low impedance sine-wave source such as the 50 c/s. lighting mains. An oscilloscope will readily show that the wave-form of the voltage appearing across the secondary is exactly the same as that applied to the primary.

Nevertheless, we know that transformers *do* cause harmonic distortion in spite of the above demonstration to the contrary. How?

Two factors have to be considered. Returning to our experiment, if instead of examining the secondary voltage we examine the current flowing through the primary, as is shown in Fig. 1 (a) an ample degree of distortion will be revealed. But it is important to appreciate that this distortion of the current, by itself, is of no consequence whatever in the circuit of Fig. 1 (a). A sine-wave voltage is applied directly to the primary winding, hence the magnetic flux within the core behaves in such a way as to induce a back EMF of sine wave-form. This being

Why It Occurs and How to Calculate It

By N. PARTRIDGE,
Ph.D., B.Sc.(Eng.), A.M.I.E.E.

so, it follows that the voltage induced in the secondary winding will also be of sine wave-form. Our present interest is strictly limited to this comparison between the applied primary voltage and the resultant secondary voltage. So long as no distortion occurs between these two points the primary current can adopt whatever wave-form it chooses.

The second factor necessary to produce the phenomenon of voltage distortion has nothing to do with the transformer. It arises from the unhappy fact that audio frequency transformers are not usually connected directly across a low impedance source, but generally have a series impedance between the source of voltage and the primary winding. In the case of an intervalve or output transformer, there is the AC resistance of the associated valve; in the case of a microphone transformer there is the impedance of the microphone, and so on.

In Fig. 1 (b) a resistance R has been introduced to represent this series impedance. The shape of the current wave-form at once assumes

importance. A distorted current will obviously produce a distorted voltage drop across the resistance, and therefore will cause the voltage across the primary of the transformer to be distorted. Thus the distorted primary current and the series resistance conspire to produce voltage distortion on the primary side of the transformer. No further distortion occurs within the transformer between the primary and secondary terminals.

The magnitude of the voltage distortion can be expressed as the ratio of the harmonic voltage across the primary (or secondary) to the fundamental voltage across the primary (or secondary). Let us suppose that in Fig. 1 (b) the impedance of the transformer is Z_f , and let the current through the primary be I_f at the fundamental frequency, plus a harmonic component I_h . The voltage across the primary can be represented by $V_f (= I_f Z_f)$ at the fundamental frequency and V_h at the harmonic frequency. The fractional voltage distortion is clearly V_h/V_f .

The harmonic voltage appearing across R will be (by Ohms Law) $I_h R$. We started with the clear understanding that the source was of pure sine wave-form, and therefore contained no harmonic voltage. Hence the harmonic voltage across R and that across the transformer primary must cancel out. In other words, these two voltages must be equal and opposite. Therefore $V_h = -I_h R$. Also we know that $V_f = I_f Z_f$, and dividing one by the other we find that:—

$$\frac{V_h}{V_f} = -\frac{I_h}{I_f} \cdot \frac{R}{Z_f}$$

Thus we arrive at an expression for the fractional voltage distortion (V_h/V_f) in terms of the current distortion (I_h/I_f), the series resistance (R), and the impedance of the transformer (Z_f).

Variables

Apart from throwing a certain light upon the mechanism of transformer distortion, the equation does not get us very far on account of the elusive nature of the ratio I_h/I_f . This ratio varies with the flux density within the core material, becoming greater the higher the flux density; also, at any constant flux density it varies with R, becoming zero when R is infinite.

The papers already referred to will show the reader how the problem was solved, and in the present article it is proposed to jump in one leap from the present introductory stage straight

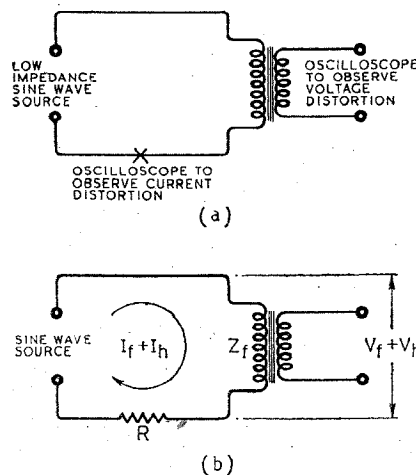


Fig. 1. Circuits employed to show that a series impedance (R) is essential for the production of voltage distortion. A transformer alone does not distort the voltage.

¹ "An Introduction to the Study of Harmonic Distortion in Audio Frequency Transformers," *Journal of the British Institution of Radio Engineers*, Vol. 3, No. 1, July, 1942.

to the application of the solution in practical cases.

Two formulae have been evolved for the calculation of the total RMS harmonic distortion produced by a transformer. They both arrive at precisely the same result, but each

l is the length of the magnetic circuit in centimetres.
 A is the cross sectional area of the magnetic circuit in square centimetres.
 f is the frequency being considered in cycles per sec.

(2) It is accurate only providing that the ratio R/Z_f falls between 0 and 1. This restriction is not a serious one. The bass attenuation of a transformer depends upon the ratio of R to Z_f . If R/Z_f exceeds 1 the attenuation will exceed 3 db. Hence another way of

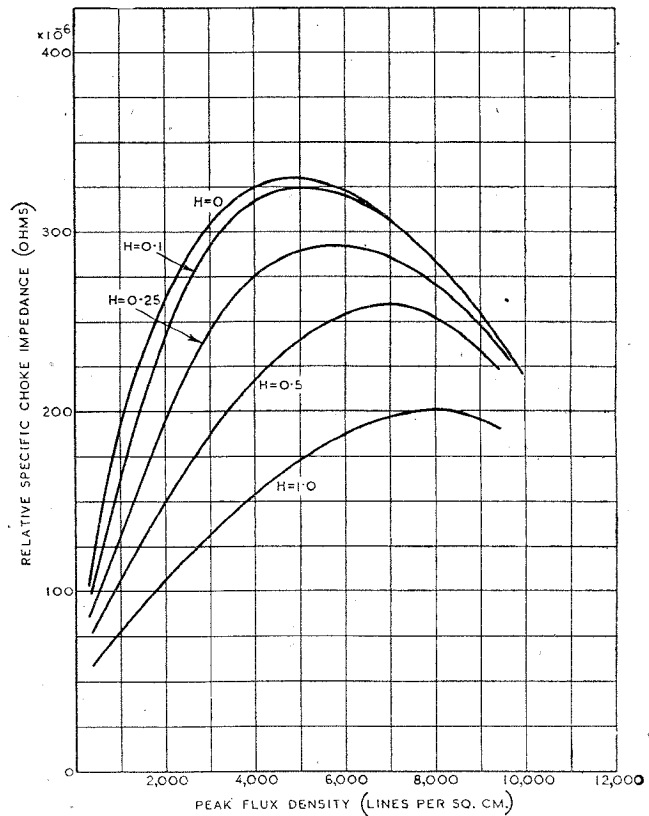
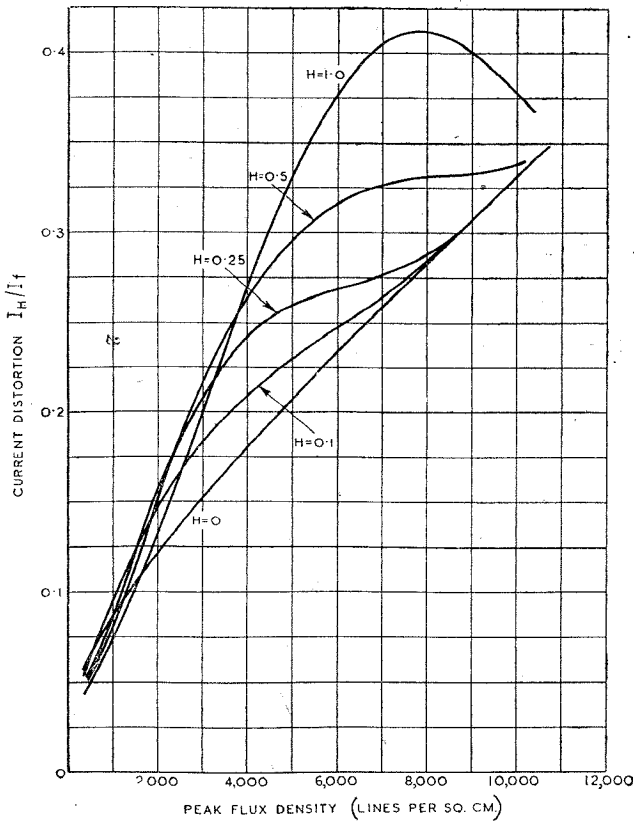


Fig. 2. Values of the factor I_H/I_1 for Silcor 2 in the normal cyclic condition ($H=0$) and in the presence of various polarizing fields ($H=0.1, 0.25, 0.5$ and 1.0 gilbert per cm.). The tests were conducted at 50 c/s upon laminations $0.014''$ thick.

Fig. 3. Values of Z_{sp} relative to the values of I_H/I_1 given in Fig. 2, i.e. the present curves were determined under the same conditions of test as those of Fig. 2.

has its own particular sphere of usefulness. We will deal with these one at a time, first stating the formula, then describing the factors appearing therein, and finally illustrating its employment.

$$\frac{I_H}{I_1} = \frac{V_h}{\sqrt{f}} = \frac{I}{Z_{sp}} \cdot \frac{l}{N^2 A} \cdot \frac{R}{f} \left(1 - \frac{R}{4Z_f} \right) \quad (1)$$

I_H/I_1 and Z_{sp} are two quantities relating to the core material. Both vary with flux density and measured values obtained from samples of silicon steels in common use are given in Table 1. Table 2 gives further information about the particular silicon steels studied. The effect of a polarising field upon Silcor 2 is indicated in Figs. 2 and 3.

N is the number of turns upon the primary winding of the transformer.

R is the combined resistance of the secondary load transferred to the primary in parallel with the resistance in series with the primary.

Z_f is the impedance of the primary as before.

It will be noted that the data concerning the core material is contained in the first two factors, i.e. I_H/I_1 and $1/Z_{sp}$. The third factor ($l/N^2 A$) relates entirely to the physical design of the transformer. The fourth factor (R/f) deals with the conditions in the circuit external to the transformer. The final part of the equation contained within the brackets is an empirical correction factor.

There are three limitations that must be observed when using the formula.

(1) It has been proved to be accurate only in the case of the silicon steels.²

² Preliminary experiments by G. A. V. Sowter, B.Sc., A.M.I.E.E., the authority on the nickel irons and their applications, suggest that the formula holds for these alloys also.

expressing this limitation would be to say that the formula holds good providing the attenuation of the transformer at the considered frequency is not greater than 3 db.

(3) The formula is applicable only when R is resistive. Again the restriction is not serious. The AC resistance of a valve or valves usually forms the major component of R , and this is, of course, purely resistive. The secondary load is often substantially resistive in practice, and in any case specifications of performance are usually framed with reference to a purely resistive load.

A little more must be said about I_H/I_1 and Z_{sp} . Possibly the easiest way of understanding what these factors signify is to consider how they are measured. Take any stack of laminations of the material to be examined, such that the magnetic circuit is a closed one of constant cross-

Transformer Distortion—

sectional area. Suppose the length of the magnetic circuit to be l_1 cms. and the cross-sectional area A_1 sq. cms. Wind a primary coil of any

Dividing the latter by the former we obtain the value of I_h/I_f .

It should be noted that I_h is not the same as I_h mentioned earlier in connection with Fig. 1 (b). I_h is the

I_h/I_f obtained under identical conditions of test. If a sample be tested at a number of different frequencies, the values of I_h/I_f and Z_{sp} so obtained will differ slightly in each case. But

TABLE 1

B_m Lines per sq. cm.	$\frac{I_h}{I_f}$	Z_{sp}	SH	$\frac{I_h}{I_f}$	Z_{sp}	SH	$\frac{I_h}{I_f}$	Z_{sp}	SH	$\frac{I_h}{I_f}$	Z_{sp}	SH	B_m Lines per sq. cm.
	Silcor 1			Silcor 2			Silcor 3			Silcor 4			
		$\times 10^{-6}$	$\times 10^{-6}$		$\times 10^{-6}$	$\times 10^{-6}$		$\times 10^{-6}$	$\times 10^{-6}$		$\times 10^{-6}$	$\times 10^{-6}$	
45	0.036	80	35.5	0.030	60	39.5	0.020	56	28	0.029	33	69	45
90	0.0385	108	28	0.0365	72	40	0.0285	70	32	0.038	36.5	82	90
180	0.041	130	25	0.0445	89	39.5	0.042	92	36	0.058	54	85	180
360	0.052	173	23.5	0.057	112	40	0.050	112	35	0.066	69	75	360
675	0.065	225	22.5	0.073	155	37	0.065	144	35.5	0.075	96	62	675
1,125	0.080	280	22.5	0.093	200	36.5	0.085	182	37	0.091	123	58	1,125
1,575	0.094	315	23.5	0.111	240	36.5	0.105	220	37.5	0.104	146	56	1,575
2,250	0.115	355	25.5	0.130	275	37	0.122	255	37.5	0.116	172	53	2,250
3,600	0.150	385	30.5	0.170	320	42	0.161	315	40	0.143	215	52	3,600
5,400	0.191	370	40.5	0.220	330	53	0.20	330	47.5	0.173	245	56	5,400
7,200	0.23	320	57	0.265	305	69	0.24	320	59	0.21	240	69	7,200
9,000	0.27	255	84	0.315	260	96	0.28	285	78	0.235	215	86	9,000
10,800	0.305	180	133	0.36	200	142	0.33	230	113	0.27	180	118	10,800

The above figures were deduced from tests at 50 c/s and the sheet thicknesses were as stated in Table 2.

convenient number of turns, say N_1 . The next requirement is a source of sinusoidal voltage having negligible impedance and capable of adjustment at will. The frequency is not important so long as it is low; let it be f_1 c/s.

The quantities to be measured are variable with flux density. It must therefore be decided at what peak flux density the test is to be performed. Call the chosen peak flux density B_m . Then the voltage to be applied to the winding to produce this flux density is given by the well-known formula

$$V_f = \frac{4.44 B_m N_1 A_1 f_1}{10^8} \dots (2)$$

Having adjusted the source to this voltage the test sample is connected directly across it, as in Fig. 1 (a). By employing an electrical wave analyser in place of the oscilloscope, the current can be measured at the fundamental frequency, giving I_f , and at the harmonic frequencies, giving I_h .

value of the harmonic current when a series resistance (R) is included in the circuit. I_h is the particular value of I_h when R is zero.

Z_{sp} remains to be evaluated. This is given by the formula:—

$$Z_{sp} = \frac{V_f}{I_f} \cdot \frac{l_1}{N_1^2 A_1 f_1} = Z_f \cdot \frac{l_1}{N_1^2 A_1 f_1}$$

A little consideration will show that, at low frequencies, multiplying Z_f by $l_1/N_1^2 A_1 f_1$ gives (very nearly) the impedance at τ c/s of a choke in which $N = 1$, $A = 1$ and $l = 1$.⁽³⁾ This follows from the fact that at constant peak flux density the impedance is inversely proportional to l and directly proportional to N^2 , A and f (nearly). Z_{sp} has therefore been christened "the relative specific choke impedance," and it is "relative" to the value of

³ The approximation arises as a result of eddy current effects. For a discussion of this point the reader is referred to the forthcoming article in *Wireless Engineer*.

the product $\frac{I_h}{I_f} \cdot \frac{l}{Z_{sp}}$ will always be constant, hence formula (1) is in no way influenced by these variations in the separate members of the relative pairs of values.

Z_{sp} is a useful quantity to know about. It enables a rapid estimate to be made of the impedance at any low frequency of any choke. For example, let a new choke have the parameters N_2 , l_2 and A_2 , and let the frequency be f_2 . A good idea of its impedance is given by:—

$$Z_f \approx Z_{sp} \cdot \frac{N_2^2 A_2 f_2}{l_2} \dots (3)$$

A practical example will clear up any obscure points. Suppose a transformer to be made up of No. 56 stampings (M. & E.A. Ltd., see Fig. 5) in Silcor 2, the number of stampings being such that the centre limb has a square cross-section. Let the primary have 4,000 turns wound in two sections of 2,000 turns each. Next let us

TABLE 2
Silicon Steels to which Table 1 refers
Manufactured by Magnetic & Electrical Alloys, Ltd., of Wembley

Trade Name	Silicon Content* (per cent.)	Sheet Thickness (ins.)	Max. Loss $f = 50$, $B_m = 10,000$ (watts/kilo)	Specific Resistance	Specific Gravity	Equivalent Material by	
						Sankey	Armco
Silcor 1 ...	4	0.014	1.30	56	7.5	Super Stalloy	Tran-Cor 2
Silcor 2 ...	3½	0.014	1.40	56	7.5	Stalloy	Tran-Cor 1
Silcor 3 ...	2¾	0.018	2.14	41	7.5	42 Quality	Special Elec. Armature
Silcor 4 ...	1	0.018	3.17	18	7.7	Lohys	

* The figures quoted for the silicon content were supplied by Magnetic & Electrical Alloys, Ltd.

Imagine that the transformer is to be used in connection with two valves in push-pull, the AC resistance of each valve being 1,500 ohms and the optimum load 3,000 ohms, i.e. 6,000 ohms anode to anode. Assume that the secondary is resistively loaded so that the optimum load for the valves is reflected to the primary, and also that the anode currents of the two valves are exactly balanced. Let us now estimate the attenuation and the harmonic distortion to be expected at 20 c/s when the transformer is delivering (a) 10 watts and (b) 0.1 watt.

First, it is necessary to discover what peak flux densities are involved in the two cases (a) and (b). This can be done in two steps. The voltage across the primary is calculated as follows:—

$$V_f' = \sqrt{\text{Watts} \times \text{load resistance}}$$

$$= \sqrt{10 \times 6,000}$$

$$= 245 \text{ volts RMS (case a)}$$

$$V_f'' = \sqrt{0.1 \times 6,000}$$

$$= 24.5 \text{ volts RMS (case b)}$$

Re-arranging formula (2) and substituting appropriate values, we find:

$$B_m' = \frac{245 \times 10^8}{4.44 \times 4,000 \times 14.5 \times 20}$$

$$= 4,750 \text{ lines per sq. cm. (case a)}$$

It will be noted that the area (A) must be in sq. cms. while the dimensions in Fig. 5 are in inches. The area

is therefore $(1.5 \times 1.5 \times 2.54^2)$ sq. cms. Case (b) can be treated in exactly the same way, substituting 24.5 volts in place of 245 volts. B_m'' is thus found to be 475 lines per sq. cm.

Formula (3) enables us to calculate the impedance of the transformer. N, A and f are known. l is the mean length of the magnetic circuit (shown dotted in Fig. 2) expressed in cms., and is approximately 22 cms. Z_{sp} is found from Table 1 under the heading of Silcon 2. These figures have been plotted in Fig. 3 (upper curve, $H = 0$), from which can be taken the values at (a) 4,750 lines per sq. cm. and (b) 475 lines per sq. cm. These values are roughly (a) 330×10^{-6} and (b) 120×10^{-6} . Substituting in formula (3) we have:—

$$Z_f' = \frac{330 \times 10^{-6} \times 4,000^2 \times 14.5 \times 20}{22}$$

$$= 69,500 \text{ ohms approx. (case a)}$$


$$Z_f'' = 25,300 \text{ ohms approx. (case b)}$$

The next step is to determine R. Neglecting the resistance of the transformer windings, this will be the resistance of the secondary load transferred to the primary, namely, 6,000 ohms, taken in parallel with the resistance in series with the primary, i.e. $1,500 \times 2 = 3,000$ ohms. R is therefore 2,000 ohms.

Since Z_f' and Z_f'' are so large by comparison with R, it follows that (a) the attenuation will be negligible, (b) formula (1) can be used with safety since R/Z_f is less than 1, and (c) the factor appearing within the brackets in equation (1) approximates to unity and can be neglected.

It now remains only to substitute the appropriate values in equation (1) and thus to determine the magnitude of the harmonic distortion. All the factors are known with the exception of I_H/I_f . By plotting the figures given in Table 1 (see Fig. 2, $H = 0$)

Fig. 4. Values of the distortion coefficient (SH) for Silcon 2 in the normal and polarized states. These values are independent of the test frequency and lamination thickness.

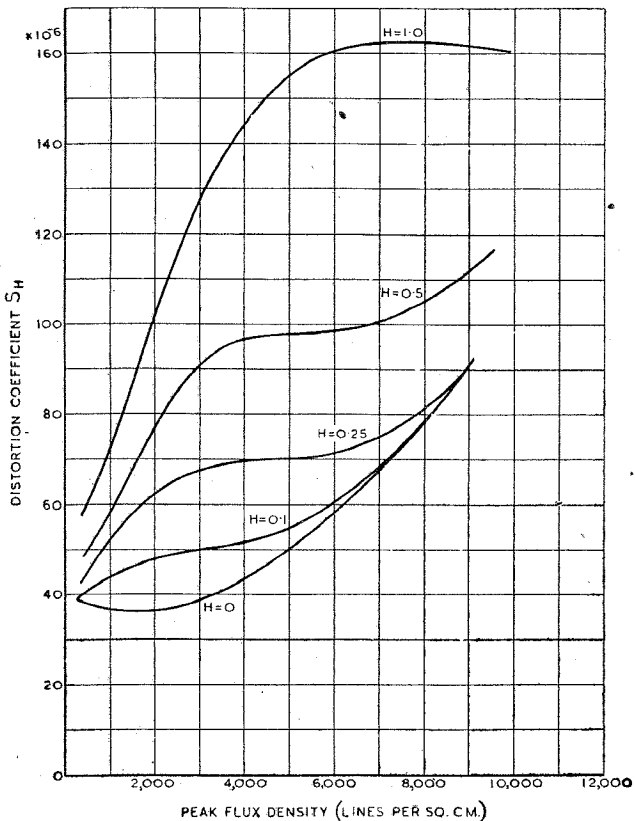

it will be found that at 4,750 and 475 lines per sq. cm. $I_H/I_f = 0.2$ and 0.06 respectively. By substitution in equation (1) the fractional distortion in case (a) is 0.0057 (or 0.57 per cent.), and in case (b) 0.0047 (or 0.47 per cent.).

The example chosen for illustration happens to be a very favourable one, and it must not be assumed that the distortion is always so desirably small.

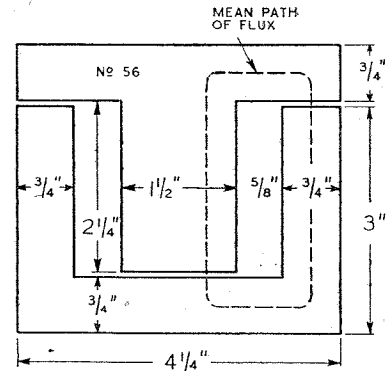


Fig. 5. Dimensions of the M. & E. A. Ltd. stamping No. 56 used in the numerical examples. The mean path of the magnetic flux in one half is indicated by the dotted line.

The second formula for calculating transformer distortion is:—

$$\frac{V_h}{V_f} = S_H \cdot \frac{10^9}{8\pi^2} \cdot \frac{l}{N^2 A} \cdot \frac{R}{f} \left(1 - \frac{R}{4Z_f} \right) \quad (4)$$

This is little more than a variation of equation (1) in which $\frac{I_H}{I_f} \cdot \frac{I}{Z_{sp}}$ has been replaced by $S_H \cdot \frac{10^9}{8\pi^2}$. These two products are, in fact, equal. But special interest centres upon S_H , which is defined as the distortion coefficient of a magnetic material. It can be calculated from the data obtained when measuring I_H/I_f and Z_{sp} , and is given by:—

$$S_H = \frac{I_H N}{0.56 B_m l}$$

It can be shown that this specific quantity is constant for any given material operating at any one value of B_m . It is dependent only upon the shape of the hysteresis loop and is independent of test frequency, lamination thickness, winding data, physical shape or size of the sample tested, etc., always providing the flux density is substantially constant throughout the magnetic circuit and the frequency is below that at which skin effect becomes appreciable.

Values of the distortion coefficient

Transformer Distortion—

(SH) are included in Table 1, and the effect of a polarising current upon the coefficient in the case of Silcor 2 is shown in Fig. 4.

By way of illustrating the use of equation (4) we will answer the following question. Referring to the earlier numerical example, what would be the effect upon the distortion if the two anode currents differed by 6 mA. instead of being balanced?

We have already assigned values to N, l, A, R and f_p , and none of these will be influenced by the polarising field which results from the anode currents being unequal. Neither will the values of the alternating peak flux densities, B_m' and B_m'' , be different. But Z_{sp} (which is wanted to calculate Z_f) and SH are both functions of the polarising field. The strength of this field is therefore the first thing to be decided. For a closed magnetic circuit, i.e. non-gapped, this is given by the well-known formula:—

$$H = \frac{0.4 \pi NI}{l}$$

where N is the effective number of turns traversed by the polarising current I.

In the present instance one half of the primary winding carries 6 mA more than the other half. Therefore the polarising current is 6 mA and the effective turns are 2,000. Hence:—

$$H = \frac{0.4 \times \pi \times 2,000 \times 0.006}{22} = 0.68 \text{ gilbert per centimetre.}$$

Referring to Fig. 3 and interpolating, it will be seen that the relevant values of Z_{sp} are 210×10^{-6} for case (a) and 70×10^{-6} for case (b). Substituting in equation (3) the values of Z_f are found to be 44,000 ohms and 15,000 ohms, respectively. The polarising field has caused the impedance to fall considerably, but in both cases it still remains very large by comparison with R (2,000 ohms), and therefore the attenuation will not be appreciable and the correction factor to the right of equation (4) can be neglected.

Turning now to Fig. 4 and again interpolating, the relevant values of SH are found to be of the order of 120×10^{-6} and 53×10^{-6} . Finally, substituting in equation (4) the two values of the distortion come out to be 0.0145 (or 1.45 per cent.) and 0.0064 (or 0.64 per cent.). Looking back at the original figures it will be seen that the lack of balance between the anode currents has caused the distortion to increase by no less than 155 per cent. at 10 watts output. In other words, the distortion is about $2\frac{1}{2}$ times as great as before. At 0.1 watt output the ill-effect is less marked, being an increase of only 36 per cent.

A very great deal more could be said about this matter of iron distortion in audio frequency transformers. Almost all preconceived ideas about it are now known to have been fundamentally wrong. But space is precious in a monthly journal and must be fairly divided amongst all interests. Perhaps an opportunity to return to the subject will occur later.

Russian Morse

CIRCUMSTANCES may arise where a knowledge of the morse code as used by our Russian Allies will be of value to British wireless operators. Accordingly we give below the symbols corresponding to the Cyrillic alphabet, which is used throughout the greater part of the U.S.S.R.

RUSSIAN LETTER	ENGLISH PHONETIC EQUIVALENT	MORSE SYMBOL
А	A	— · · ·
Б	B	— · · · ·
В	W	— · · · · ·
Г	G	— · · · · · ·
Д	D	— · · · · · · ·
Е, Э	E	— · · · · · · · ·
Ж	V	— · · · · · · · · ·
З	Z	— · · · · · · · · · ·
И	I	— · · · · · · · · · · ·
Й	J	— · · · · · · · · · · · ·
К	K	— · · · · · · · · · · · · ·
Л	L	— · · · · · · · · · · · · · ·
М	M	— · · · · · · · · · · · · · · ·
Н	N	— · · · · · · · · · · · · · · · ·
О	O	— · · · · · · · · · · · · · · · · ·
П	P	— · · · · · · · · · · · · · · · · · ·
Р	R	— · · · · · · · · · · · · · · · · · · ·
С	S	— ·
Т	T	— ·
У	U	— ·
Ф	F	— ·
Х	H	— ·
Ц	C	— ·
Ч	Oe, ö	— ·
Ш	CH	— ·
Щ	Q	— ·
Ъ, б	X	— ·
Ы	Y	— ·
Ю, я	Ue, ü	— ·
Я	Ae, ä	— ·

As will be seen from the table, transliteration from one alphabet to the other presents less difficulty than might be expected, as the morse symbols for each Russian letter are those allotted to the phonetic equivalent letter in the International Code.

Introduction to Valves

IN spite of the fact that the valve is the most important of all modern radio devices most textbooks deal with it as an auxiliary to the circuit in which it is used. In "Introduction to Valves," by F. E. Henderson, A.M.I.E.E., which is expected to be ready some time during the month of August, the normal process is reversed, and the valve comes into the foreground of the picture. As its title implies, the book deals with the subject from the point of view of those who have not previously studied it deeply. The book costs 4s. 6d. (by post 4s. 9d.), and is to be issued by our publishers on behalf of the General Electric Company.

BOOKS ON WIRELESS

issued in conjunction with "Wireless World"

	Net Price	By Post
"FOUNDATIONS OF WIRELESS," by A. L. M. Sowerby, M.Sc. Third Edition revised by M. G. Scroggie, B.Sc., A.M.I.E.E.	6/-	6/4
"RADIO LABORATORY HANDBOOK," by M. G. Scroggie, B.Sc., A.M.I.E.E. Second Edition Revised and Enlarged	12/6	12/11
"WIRELESS SERVICING MANUAL," by W. T. Cocking, A.M.I.E.E. Sixth Edition Revised and Enlarged	7/6	7/10
"HANDBOOK OF TECHNICAL INSTRUCTION FOR WIRELESS TELEGRAPHISTS," by H. M. Dowsett, M.I.E.E., F.Inst.P., M.Inst.R.E., and L. E. Q. Walker, A.R.C.S. Seventh Edition	27/6	28/3
"WIRELESS DIRECTION FINDING," by R. Keen, B.Eng. Hons. Sheffield, A.M.I.E.E. Third Edition	27/6	28/3
"RADIO DATA CHARTS," by R. T. Beatty, M.A., B.E., D.Sc. Second Edition Revised	6/-	6/3
"TELEVISION RECEIVING EQUIPMENT," by W. T. Cocking, A.M.I.E.E.	8/6	9/-
"RADIO INTERFERENCE SUPPRESSION," by Gordon W. Ingram, B.Sc.	5/-	5/4
"LEARNING MORSE," Ninth Edition	6d.	7½d.
"RADIO DESIGNER'S HANDBOOK," Edited by F. Langford Smith, B.Sc., B.E.	10/6	11/1
"WIRELESS WORLD" GREAT "CIRCLE PROJECTION MAP	2/-	2/3
B.V.A. LIST OF EQUIVALENT AND PREFERRED ALTERNATIVE VALVES	1/-	1/1

Obtainable from Leading Booksellers and Railway Bookstalls or by post (remittance with order) from

LIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1

INSTRUMENTS: *Test and Measuring Gear and Its Uses*

By W. H. CAZALY

V.—Beat Frequency Oscillators

IN testing the performance of audio amplifiers and receivers it is often necessary to make use of audio-frequency alternating voltage of which the frequency, the magnitude and the wave-form are precisely known. Moreover, it is very often necessary that the first two factors at least should be easily and accurately altered over wide ranges.

For instance, the response of an AF amplifier may be checked by applying a test input voltage and recording the resultant output on an output meter. In such a case the input voltage may need to be less than a volt in magnitude, but that magnitude must be known; the frequency of this voltage, however, must be variable from (for a first-class amplifier) about 20 c/s to 12,000 c/s, and in most cases it is very important that it should be of pure sine wave-form. A known voltage of this nature, but of much greater amplitude, may be needed to modulate some test RF carrier signal when measuring the performance of a receiver. There is, again, the testing of a loudspeaker for its efficiency and fidelity in converting electrical into acoustical energy, and for this quite considerable power as well as accurately known frequency

and wave-form, may be needed. A little thought will show that a piece of apparatus capable of producing alternating potentials of such widely variable qualities with ease and certainty has to be a fairly complex device.

Sum and Difference Frequencies

Indeed, a good beat frequency oscillator, which is the most commonly used instrument for the purpose, is neither easy nor cheap to construct. Its principles, however, are simple enough. It is well known that if two sine-wave alternating voltages are developed simultaneously across some circuit that will record their resultant effect, that effect will contain not only the two original frequencies but also two more, one equal to the sum of the two originating frequencies and the other equal to their difference. Thus if f_1 and f_2 are the two originating frequencies, the mixing of them will give rise to $f_3 = f_1 + f_2$ and $f_4 = f_1 - f_2$.

To take some figures: if $f_1 = 100$ kc/s and $f_2 = 115$ kc/s, then the resultant of mixing them will contain also $f_3 = 100 + 115$ kc/s = 215 kc/s, and $f_4 = 115 - 100$ kc/s = 15 kc/s.

A glance at the circuit diagram

shown in Fig. 1 will reveal two triode tuned-anode oscillators, V_1 and V_2 , the frequencies of which are determined by the values of L_1 , $C_{1,2,3}$, and L_3 , $C_{4,5,6}$, respectively. The outputs of these two oscillators are mixed in a conventional triode-hexode, so that in the anode circuit of that valve there are present the four frequencies, two from the two oscillators, their sum, and their difference. The frequency of the oscillators themselves is approximately 100 kc/s, and the sum frequency is, therefore, approximately 200 kc/s. These three are of comparatively high frequency and are readily filtered out by chokes and by-pass condensers, leaving only the difference frequency, which is within the audible range. This difference frequency is now handled exactly like an ordinary AF input to the grid of V_4 , which acts as a buffer amplifier, and the signal passes to the output valve V_5 , and is conveyed to the output terminals through a massive and carefully designed iron-cored transformer.

This is a fairly typical and very commonly used form of circuit for a beat frequency oscillator. Before considering other forms of AF generator, it will be worth while to note a few

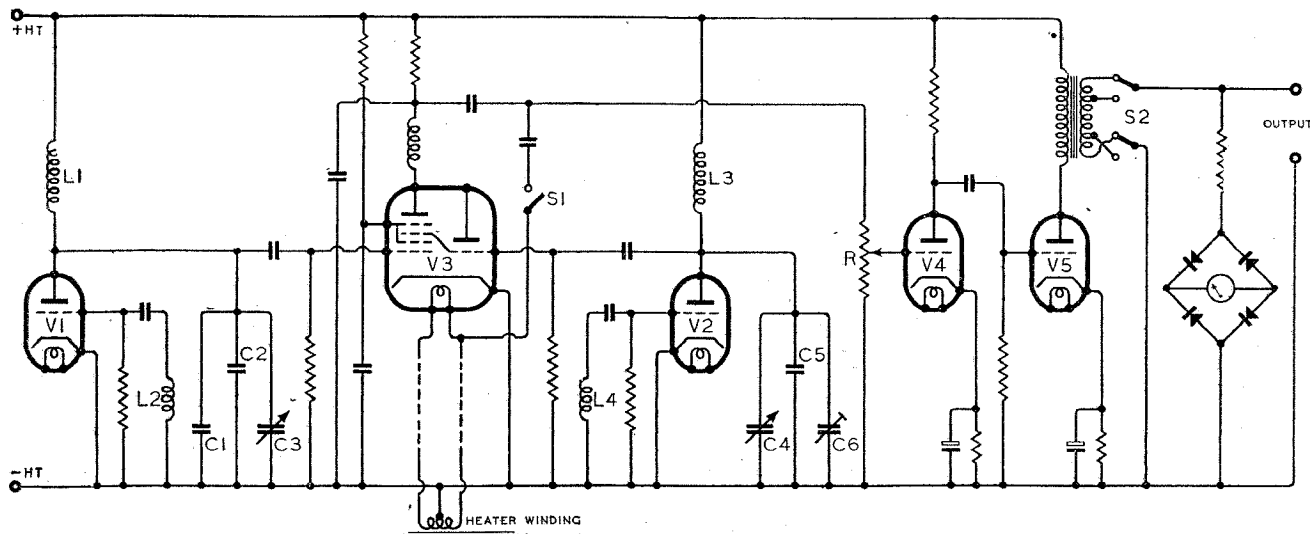


Fig. 1. Basic circuit of a typical beat frequency oscillator. V_1 and V_2 are tuned anode oscillators. $C_3 = 0.00005\mu\text{F}$ (variable), and is used as the "Set Zero" control in adjustments preliminary to use. The output frequency is altered by $C_4 = 0.0005\mu\text{F}$. $C_6 = 0.00005\mu\text{F}$ and is a pre-set trimmer for scale calibration. $C_2 = C_5 = 0.001\mu\text{F}$; these form the major part of the capacities tuning the circuits.

Instruments—

points about the circuit. In the first place, although it is not shown in the diagram, the screening of the two oscillators from each other has to be very complete. They are usually positioned as far away from each other as is practicable in the instrument and the coils at least are encased in cans. This is to avoid "pulling" between the two oscillators when they are on very nearly the same frequency. Those who have handled a "reaction" receiver close to a powerful transmitter will have noticed, perhaps, that when the receiver is oscillating the resulting whistle caused by the heterodyning of the incoming signal with the oscillation of the reacting valve cannot be brought progressively quite to zero. When it has dropped to a few score cycles per second it stops abruptly and a "dead spot" seems to extend over a degree or two of the tuning dial. This is because the powerful incoming signal is forcing the oscillatory currents in the receiver tuned circuits into resonance with itself. Plainly, when the two frequencies of the incoming signal and of the oscillatory currents in the receiver are exactly the same, there is no difference frequency—that is, no audible sound.

Hexode Mixer

The same sort of thing may happen if the two oscillators in the BFO pull into resonance, through stray coupling, at a common frequency; they produce in the anode of the mixer valve V_3 no difference frequency, or a zero beat frequency. This would mean in practice that the BFO, instead of being able to produce alternating output voltage at frequencies covering even the lowest audio extreme (about, perhaps, 30 c/s), would give no output at all below about 100 c/s or so—which would render the BFO useless for quite a number of the more interesting performance tests.

Hence, the two oscillators are most carefully isolated from each other. The use of a triode-hexode mixer aids this—it is a type of valve noted for the small amount of coupling between the triode portion and the control grid circuit even in normal use in super-heterodyne reception—and the very fact that the triode portion of this valve is not used save for the triode grid, but the two frequencies are generated by separate oscillators, enables them to be brought to within very small differences from each other before they tend to pull into resonance.

There is also a reason for picking on neither a very high nor a very low

frequency for the two oscillators. Considering first what would happen if V_1 , say, were fixed at 40 kc/s and V_2 had to be tuneable to produce difference frequencies covering the whole AF range. It is evident that to do so V_2 would have to be tuneable from 40 kc/s to 25 kc/s. It would itself run nearly into the AF range, and an enormous tuning condenser would be required to cover this range of frequency variation. The oscillator frequencies are therefore made high enough to be well outside the AF range and easily tuneable over 15 kc/s, using the almost standard $0.0005 \mu\text{F}$ type of tuning condenser in conjunction with fixed condensers and trimmers.

Optimum Oscillator Frequency

Now, if we consider what would happen if, instead of about 100 kc/s, we were to use frequencies of the order of megacycles per second, it is found that the capacity changes to cover the 15 kc/s range of difference are so slight that they can be brought about by small alterations of stray capacities due to wiring, changes of valves, warping of the case, etc. So that with two high-frequency oscillators, tuning would certainly be easy, but the order or reliability and constancy would be remarkably low. Moreover, owing to the small percentage of difference between two such high frequencies, pulling between their circuits would become much more difficult to avoid. Hence, 100 kc/s seems to be a good working compromise.

In the diagram, V_1 is the fixed oscillator, the trimmer C_3 shown being used only for zero adjustments. V_2 is tuned over a range from 100 kc/s to 115 kc/s by the $0.0005 \mu\text{F}$ variable condenser C_5 , across which there is also a fixed condenser C_5 , which corresponds to C_1 in V_1 , and it, too, has a trimmer that may be adjusted to compensate for changes in strays. The difference frequency is determined by the setting of the condenser C_4 , the dial of which is calibrated in cycles per second.

Although the two voltages are combined, in this case, in a triode-hexode, another triode is often used. With careful design, one of the oscillators itself may function also as a mixer.

In the anode of the mixer, by-pass condensers and filters remove the supersonic components present, leaving the difference frequency, which is then fed to the grid of a buffer-amplifier valve stage and treated as an ordinary AF signal. There may be more than one of these stages.

A point worth noting is that connected to the grid of the buffer-amplifier

there is not only the output control potential divider, but also a switch S_1 that connects this grid at will to one side of the valve heaters. This is done in order that, when setting up the instrument for use, a quick check of accuracy of calibration may be made against the 50 c/s frequency of the AC mains supply that operates the instrument. Normally, "mains hum" is carefully avoided in amplifiers, one of the devices for this purpose being to centre-tap the heater supply windings as shown in Fig. 1 to chassis. However, by connecting the grid of V_4 through a condenser to one side of these heater windings, a volt or two at 50 c/s is applied.

Now, if the difference beat frequency supplied from the anode of V_3 is itself at 50 c/s, it will be exactly in step with this mains frequency and the pointer of the output meter of the instrument will merely indicate a steady output. But if the generated difference frequency is not exactly 50 c/s, the pointer will slowly rise and fall, and the "Set Zero" condenser (C_3) must be adjusted until this wav-

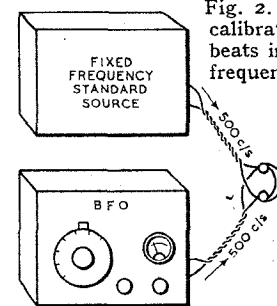


Fig. 2. A method of calibration by audible beats in which a fixed frequency standard and a BFO have their outputs applied simultaneously to a pair of headphones or a loudspeaker.

ing motion ceases and the generated and mains voltages applied to the grid of V_4 are exactly in step. Admittedly this check can only be applied at the 50 c/s mark on the calibrated dial, or, if harmonics are sufficiently strong in the mains supply, at 100 and 150 c/s; but if the rest of the instrument is in good order, it can usually be assumed that the calibration is correct over the rest of the dial.

It will be noted that the only iron in the circuit is in the output transformer, which is usually of massive construction to avoid an approach to saturation, even on high outputs, with consequent distortion and the creation of harmonic frequencies in the output. Provision is shown for only two output impedances obtained by altering the ratio of secondary to primary in the output transformer; but, of course, the design can be adapted to the nature of the work to be done. A rectifier type of AC voltmeter is usually quite accurate enough to indicate the voltage developed across the output terminals.

The calibration of a BFO and of kindred sources of AF may be carried out either by means of comparison with standard fixed generators including tuning forks, or by visual means with a cathode ray oscillograph. Considering the first mentioned, all that is necessary is to combine the standard frequency output acoustically with that of the BFO under test. For instance, at frequencies over 100 c/s (above which the response of headphones is usually sufficient) the arrangement of Fig. 2 will be quite satisfactory. The output of the standard source and that of the BFO will combine as a complex sound output from the phones. The dial of the BFO may now be turned until the BFO output frequency approaches the standard frequency, say, 500 c/s. As coincidence is made closer, the combination of the BFO and the standard outputs will give rise to a beat note or flutter, falling in frequency until finally only a pure 500 c/s tone is heard. In this way, accuracy of the order of a fraction of a cycle per second can be obtained with ease, even at high frequencies of the order of 10 or 12 kc/s. Even with only one standard frequency, the BFO dial may be calibrated by the use of octaves and a good musical ear, with an accuracy quite sufficient for most purposes. If this method of calibration is adopted one should arrange to be at home when the piano-tuner calls!

Good public mains supplies preserve a considerable accuracy of frequency, even if their voltage varies somewhat, and therefore form a very handy standard 50 c/s frequency. With this source at 50 c/s, Lissajous figures obtained on the screen of a cathode ray oscillograph provide a very accurate


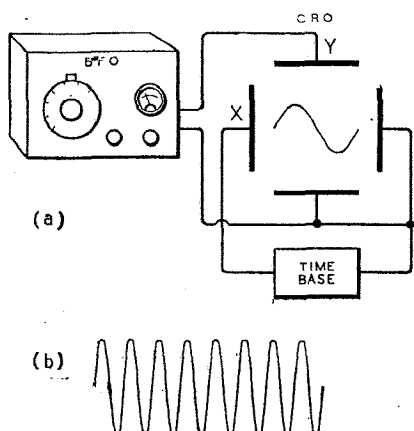


Fig. 3. (a) Shows the picture obtained when the frequency of the time base and the BFO output are the same. (b) Shows the picture obtained when the frequency of the BFO output is increased to 8 times that of the time base. There are 8 complete sine waves.

and easy method of calibrating the dial of a BFO over the whole AF range. The method may be briefly outlined as follows: First, the saw-toothed time base for the "X" sweep is set up at exactly 50 c/s, by applying mains voltage (stepped down by a transformer) to the Y plate and adjusting the time base until a single sine-wave trace is obtained. Now the mains voltage is removed from the Y plate and the output of the BFO is

Fig. 4. An arrangement for taking a frequency response curve of an AF amplifier. R is a resistance equal to the normal load offered by the speaker.

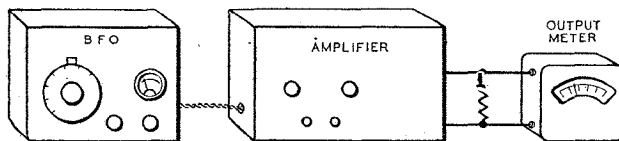

applied in its place. The synchronising control should *not* be used to steady the picture; that must be done by exact control of the time base frequency and BFO output.

If the BFO output is now made 25 c/s, an elliptical figure will be obtained on the CRO screen. If desired, the time base can now be adjusted to run more slowly until the sine-wave is regained, showing the time base to be set at 25 c/s. With this time base, the application of BFO outputs at multiples of 25 c/s can be readily obtained by increasing the BFO frequency and noting the necessarily increasing number of sine-waves in the picture, up to some 200 or 250 c/s. Assuming that the last figure has been obtained with 250 c/s applied to the Y plate from the BFO—10 complete sine-waves on the screen—the time base is then adjusted, leaving the BFO dial untouched, to increase its speed until once more only one sine-wave is seen as the picture. The time base is now running at 250 c/s. Multiples of this can be obtained now, as before, by increasing the frequency of the BFO output so that in succession 2, 3, 4, 5, and up to 10 complete sine-waves are seen. This takes the BFO up to 2,500 c/s. The time base can now be again adjusted to regain a single-wave, showing that it is running at 2,500 c/s, and with that as a base, the BFO output can be taken in frequency right up to the limit of the AF band.

Having obtained a calibration point at, say, 1,000 c/s on the BFO dial, it can be used on similar principles to find a very large number of intermediate points. With care, this can be made an extremely accurate method of calibrating a frequency source up to radio frequencies, the limit being determined by the maximum speed of the time base and the characteristics of the cathode ray tube.

The uses of a good BFO are so many

and varied that it is hard to select a few typical examples. There is, of course, the most obvious use, in checking over an AF amplifier for "frequency response." The arrangement is shown in Fig. 4, the BFO output, maintained at an unvarying level, being applied to the input terminals and the frequency altered to cover the whole AF range desired. The variations in the output of the amplifier as recorded on the output meter are

noted and subsequently plotted against frequency. The effects of various speaker loadings can be observed and also the effects of long connecting leads.

With a signal generator it can be used, as was described in a previous article, for making overall acoustic response tests of a receiver, being then in operation as a modulator of variable frequency, or as a means of accurately tuning a RF carrier a few hundred or thousand cycles away from a mid-frequency for bandpass and adjacent channel tests.

The Wireless Industry

A HARD beryllium-copper alloy (Cu.Be.250) has been added to the range of "Telcon" alloys. Its high tensile and fatigue strength make it suitable for electrical spring contacts and it is easily worked in the soft condition. It is available in strip, wire and rod, and particulars are obtainable from The Telegraph Construction and Maintenance Co., Ltd., 22, Old Broad Street, London, E.C.2.

For delicate instrument work the average electric soldering iron is too heavy and clumsy and a special lightweight electric iron has been introduced by Runbaken Electrical Products, 71-73a, Oxford Road, Manchester, 1. It weighs 5oz., has a copper bit $\frac{3}{8}$ in. \times $\frac{1}{8}$ in., and is fitted with radiating fins to keep the handle cool. The heater is rated at 30 watts and is supplied with current at 12 volts through a mains transformer, which is fitted with a pilot light and is available in sizes suitable for 1 to 50 irons.

Wireless World Brains Trust

Problem No. 3

WHAT is the difference between additive and multiplicative mixing? (Solution on page 194.)

Improving the DIODE DETECTOR

THE widespread use of the diode detector in modern receivers is due to its cheapness, low inherent distortion and ability to provide AVC. It is now realised, however, that it can contribute a large amount of distortion if not used correctly. This may be due either to curvature of the valve characteristic or to the arrangement of the diode in the circuit. The former is easily reduced to negligible proportions by working the diode with a sufficiently large carrier input, so that the curved part of the characteristic forms only a small proportion of the total used. Under normal conditions with a detector efficiency of 80 per cent. the total amplitude distortion in the output has been quoted³ as 2 per cent., which is relatively harmless.

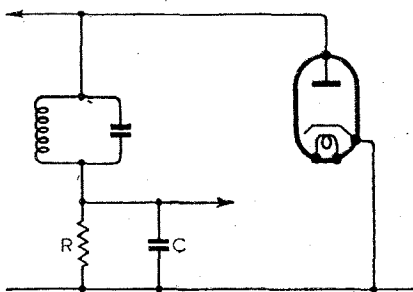


Fig. 1. Diode detector circuit.

Amplitude distortion is by far the more important, and apart from any non-linearity in the valve feeding the diode, is always due to the AC load being unequal to the DC load, causing clipping of the negative peaks at all levels beyond a certain critical modulation depth. The theory of this effect, has been amply treated elsewhere^{1, 2, 3, 4} and it is sufficient to say that the maximum modulation depth handled by a diode detector without distortion is equal to the ratio of AC to DC loads. It will be apparent that if the DC load resistance be shunted by other components offering no DC path, the distortion present at 100 per cent. modulation will be greatly increased.⁵

Fig. 1 shows a conventional diode circuit. In this the DC and AC loads are equal for all low and medium modulation frequencies; at high frequencies, however, the AC load becomes less than the DC load because of the shunt reactance of C. This cannot

Design for Negligible Distortion at All Modulation Levels

By GEORGE A. HAY, B.Sc.


easily be avoided, and is a possible source of amplitude distortion in receivers with a wide frequency response. The maximum modulation

depth m is equal to the ratio $\frac{\text{AC load}}{\text{DC load}}$ i.e.

$$m = \frac{XR}{\sqrt{X^2 + R^2}} = \frac{X}{\sqrt{X^2 + R^2}}$$

If $R = 0.25 \text{ M}\Omega$ and $C = 300 \mu\text{F}$ —common values in practice— X will be about $0.1 \text{ M}\Omega$ at 5,000 c/s, and m will be 0.37; any distortion will therefore result from the detection of any modulation beyond 37 per cent. Actually results are not quite so bad as this because of the demodulating effect of a diode used in this manner.⁶ Evidently the choice of R and C is of some importance, and the deciding factor must be C , as this must be large enough not to reduce substantially the RF input to the diode. A reasonable value is ten times the anode-cathode capacitance of the diode, which, in the case of the Mazda V914, gives a value of $30 \mu\text{F}$, a value considerably lower than the usually quoted figure. R must now be

Fig. 2. Compensated diode detector with negligible amplitude distortion: values of components as given in the text.

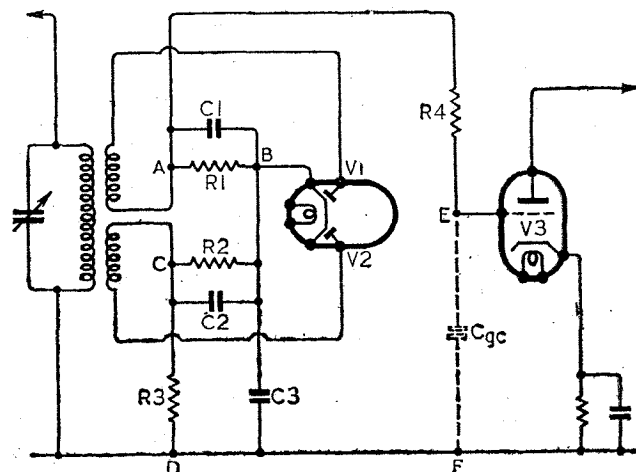

chosen so that the AC load is nearly equal to the DC load. If we assume a maximum m of 0.9 at 5,000 c/s (i.e.

the highest frequency whose second harmonic lies within the reproduced range) we have

$$m = \frac{X}{\sqrt{X^2 + R^2}} = 0.9 \text{ where } X \approx 0.5 \text{ M}\Omega$$

$$\text{and hence } R = X \frac{\sqrt{1 - m^2}}{m} \approx 0.15 \text{ M}\Omega$$

A safe value to adopt will be $0.1 \text{ M}\Omega$.

So far we have not considered the connection of the detector to an AF amplifier. Such a connection in the normal way requires the interposition of a blocking condenser with accompanying grid resistance, in order that the DC component of the detector output will not alter the bias on the amplifier. This, however, forms another shunt circuit which reduces the load impedance to AC at all modulation frequencies. There exist several methods of overcoming this, such as operating the diode with positive bias⁷, using a complex reactive load², or applying negative feedback⁸. It seems to the writer, however, that the only really satisfactory solution lies in abolishing any reactive shunting, and thus removing the trouble at the source. This is done, of course, in the grid detector when used correctly, as the output of the diode, in this case the grid and cathode of the triode, is applied directly to the grid of the AF amplifier. The DC load is thus shunted only by stray capacitance. The great disadvantage of the grid detector is the fact that the working point of the

amplifier depends on the value of the RF input, and thus we may find bottom-bend distortion taking place

^{1, 2, 3, 4} etc.—These and subsequent references are to the Bibliography at the end of the article.

Even if we fix the value of the input by using an anode current meter and a manually adjusted pre-detector gain control, there still remains the difficulty that the RF input which will

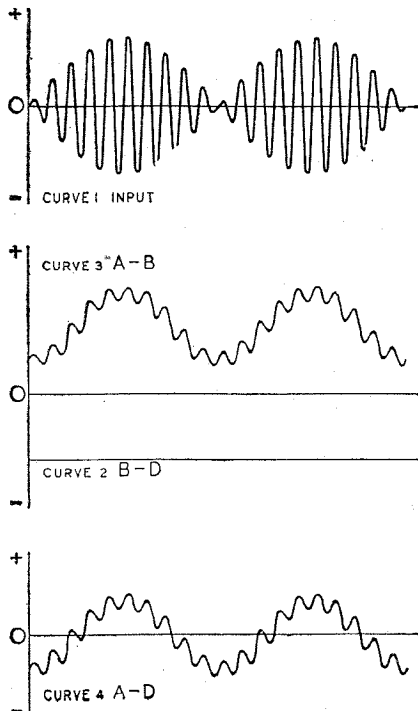


Fig. 3. Graphical illustration of working of Fig. 2.

bias a valve of the small triode class to its correct working point is too small for the avoidance of distortion due to diode curvature. On top of all this is the fact that it is impossible to obtain satisfactory AVC from a grid detector.


If we could connect in series with the detector output a source of direct potential difference which was always equal and opposite to the DC component of the output, the combination could then be connected directly to an AF amplifier without affecting the bias of the latter under any conditions. This has been done in the arrangement shown in Fig. 2. As can be seen, two diodes are used back to back, one, V_1 , connected normally, and the other, V_2 , arranged to supply only the DC component. The output of the detector proper is connected to the grid of V_3 through an RF stopper R_4 . R_1 , R_2 , C_1 and C_2 may have the values worked out earlier in this article, while R_3 and C_3 have values of $1\text{ M}\Omega$ and $1\mu\text{F}$. Assuming a modulated input, the voltages across A and B, and B and C, will contain DC, RF and AF components, such that A and C are negative with respect to B. R_3 and C_3 form a filter which

removes the AF and RF components from the output across B and C, and hence across B and D we have only the steady DC component, D being negative. The results of this are shown graphically in Fig. 3, curve 1 being the input, curve 2 the potential of B relative to D and curve 3 the potential of A relative to B. Now the output is taken from points A and D, and hence the total output is the algebraic sum of curves 2 and 3, curve 4, which contains only AF and RF components. The latter is removed by R_4 acting in conjunction with the input capacitance of V_3 , leaving only the audio frequency across E and F. It is important to realise that this occurs at any carrier input, and V_3 , being separately biased, is independent of the RF input for its working conditions. For this reason we can use any value of detector input, making this as large as necessary to reduce distortion due to diode curvature.

The DC and AC loads on V_1 are substantially equal for all modulation frequencies, while V_2 , which we may call the compensator, is only supplying DC to the output, and hence the slight inequality of AC and DC loads does not matter, as it is insufficient to cause any appreciable distortion in the output of the valve feeding the detector.

If AVC is required, the circuit must be rearranged as shown in Fig. 4, when a negative potential is available from point B without further filtering. This circuit is not so good practically, as the double diode requires separate cathodes, and these are isolated from earth, and thus liable to give rise to hum. If the greatest freedom from background is required, it may be found necessary to use separate heater windings for the two diodes. In any case the AF gain will be low, as the RF input is large, and thus any hum will not be amplified greatly.

Fig. 4. Modification of Fig. 2 to give non-delayed AVC.

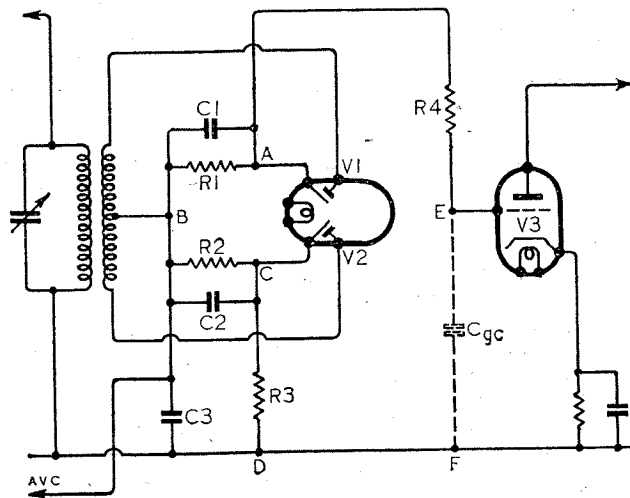

Delayed AVC is impossible with this arrangement, as the two diodes must always be working under identical conditions. This is perhaps just as well, as it has been shown that excessive distortion takes place when the carrier input is equal to the delay

voltage.⁹ The most promising arrangement appears to be some sort of DC amplified AVC using the positive output from point B in Fig. 2.

The coil design calls for some comment. Best results were obtained when each secondary section was given half the number of turns of the tuned primary. The voltage step-down is therefore 2:1, and if we require 5 volts input to each diode the pre-detector amplifier must give 10 volts RMS, which corresponds to about 28 volts peak for a fully modulated signal. This is relatively easy to arrange. The input resistance of each diode is $R/2\eta$ where R is the DC load and η the efficiency. Thus the load imposed by each diode on the secondary is about 50,000 ohms (taking η as unity) which, reflected into the primary, becomes $4 \times 50,000$ ohms or $0.2\text{ M}\Omega$. The total load on the tuned circuit is therefore $0.1\text{ M}\Omega$, which is not excessive. It is advisable to construct the coil to be as symmetrical as possible, in order that the stray capacitances and voltage outputs of each secondary should be equal. It may even be an improvement to earth the centre of the tuned primary where circuit arrangements will allow of this.

The circuit shown in Fig. 2 has been in use for some time in a pre-tuned local station receiver, and while critical judgment is difficult under war-time conditions, it is believed that the quality represents a distinct advance on any other detector so far tried.

Bibliography

- 1 H. L. Kirke, *Wireless World*, April 20th, 1932.
- 2 J. B. Lovell Foot, *Wireless World*, December 28th, 1934.

- 3 F. E. Terman, "Radio Engineering," p. 427.
- 4 W. T. Cocking, *Wireless World*, January 27th, 1933; February 3rd, 1933.
- 5 F. Langford Smith, "Radio Designer's Handbook," p. 161.
- 6 F. E. Terman, "Radio Engineering," p. 430.
- 7 K. R. Sturley, *Wireless World*, March 9th, 1933.
- 8 J. E. Varrall, *Wireless World*, August 3rd, 1933.
- 9 K. R. Sturley, *Wireless World*, December 23rd, 1937.

UNBIASED

This Mechanisation

WE hear such a lot nowadays about the complete mechanisation of the Army that it leaves us old timers of the last war a little bewildered. When we remember the old days on the parade grounds of 1914 as we formed fours to the bellicose bellowings of the Sergeant-Major, it is hard for us to visualise a modern parade ground with its serried ranks of one-man tanks silently forming threes without any apparent command, for, of course, all orders are transmitted by USW wireless from the Sergeant-Major encased in his master-tank with the crown of his rank upon its tractors. Gone are the days when we were told to put soap or special marching powder in our socks. Nowadays, I suppose, it is some other portion of the anatomy that has to be protected against corns and callosities.


It was with such thoughts in my mind that the other day I gave a few words of fatherly advice to one of the little Grid Leaks on the eve of his departure to join one of these mechanised units. I bade him not to forget to let me have a full budget of news concerning his new life with its mechanised this and mechanised that, and I sternly admonished Mrs. Free Grid for her foolishness in insisting on his taking his all-electric portable, his electric blanket, electric shaver and various other electrical devices with which he had been endeavouring to mechanise himself during the past few weeks in readiness for his new life. As I explained to her, these things would be provided by an all-wise and fully mechanised army.

It was with no little indignation, therefore, that I learned from the first letter we received that such things had certainly *not* been provided, and that when he had blandly enquired at bedtime the whereabouts of the power point for his portable and his electric blanket "a mighty shout of laughter from all the troops arose," as Macaulay records in his graphic description of a war which bears a most astonishing resemblance to the present conflict in its record of unpreparedness and hasty improvisation.

Not only was there no issue of all-wave portables whereby each soldier might keep himself informed of the war's progress by ransacking the world for news, but there were no proper facilities for those who had been enterprising enough to provide

By FREE GRID

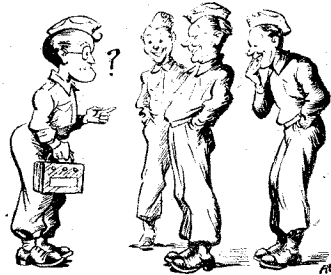their own sets. Electric light there certainly was, but if a set were plugged into a lamp socket it meant doing without the light, and this was frowned upon. The result was that those who did have portables possessed battery-driven ones, thereby wasting the country's supplies of zinc and lead in the construction of HT and J.T bat-



"A mighty shout of laughter."

teries. As for the personal receivers by which each soldier will keep in touch with his unit when out on commando amid the lonely passes of the Black Forest, there has so far been no trace of these.

Nearly a "Yorker"

I HAD a distinctly nasty shock the other morning when I received a somewhat peremptory letter headed "*re* suppression," and signed by a man named Morrison. It took several minutes as well as two cups of coffee and cognac for me to realise that the letter was about electrical interference to broadcasting and that, in any case, the writer's name was not Herbert. It only goes to show how fatal it is to jump to conclusions, and reminds me of a secretary I once had, now married and safely out of the way, I am glad to say, who was singularly addicted to this habit of jumping to conclusions. Her crowning act concerned a letter which I had occasion to write to a correspondent rejoicing in the good old Anglo-Saxon name of Ebor. It was no thanks to her that I did not unwittingly commit a breach of good taste, as the terms used in the letter were, to say the least, very unrestrained, and it was only at the last moment that I noticed that she had addressed it to a very august member of the Upper Chamber.


Babel Confounded

ATTEMPTS have been made from time to time to bring into universal use an international language such as Volapük, Esperanto, Ido, Latinesco and basic English. These attempts have been based on the belief that the adoption of a universal language would abolish war, for according to Dr. Zamenoff, who invented Esperanto, it is ignorance of each others' language and therefore the inability to exchange ideas and aspirations which causes quarrels among individuals and, therefore, among nations which are, after all, merely collections of individuals.

Of course absolutely the opposite is really true, for to quarrel with anybody you must make use of a language which he or she understands, and therefore it follows logically that if we all spoke a different language none of us could quarrel with the other and so all wars would be avoided. I once met with a striking instance of this when motoring in Wales. A native of those parts was walking in the roadway along which my car was coming and it was not altogether inappropriate, therefore, that, like the minstrel boy in the song, he had his harp slung behind him. Naturally I knocked him down, but as neither of us understood the other's language we could not quarrel, but with a polite raising of our hats we passed along on our respective ways.

Despite this I am all in favour of an international language, but to commend itself to me it must be founded on a sound scientific basis, and for this reason I am glad to see the *Wireless World* is tending more and more to follow the example of *Wireless Engineer* and other serious scientific journals in abandoning the use of the King's English in favour of the one international language which is worthy of serious support from men of science. I refer, of course, to mathematics, which, as "Cathode Ray" once told us, is nothing but a sort of shorthand. Thus $\sqrt{\quad}$ is an instruction to do something, and it is understood by men of all nations. It is concise, it is definite and it cannot be twisted from its true meaning by artful luminaries of the law. I am considering the question of writing this page of notes henceforth in mathematics, but I would first like a few comments from the more scientific among you. Postcards only please, and only mathematical symbols to be used.

Heater coating

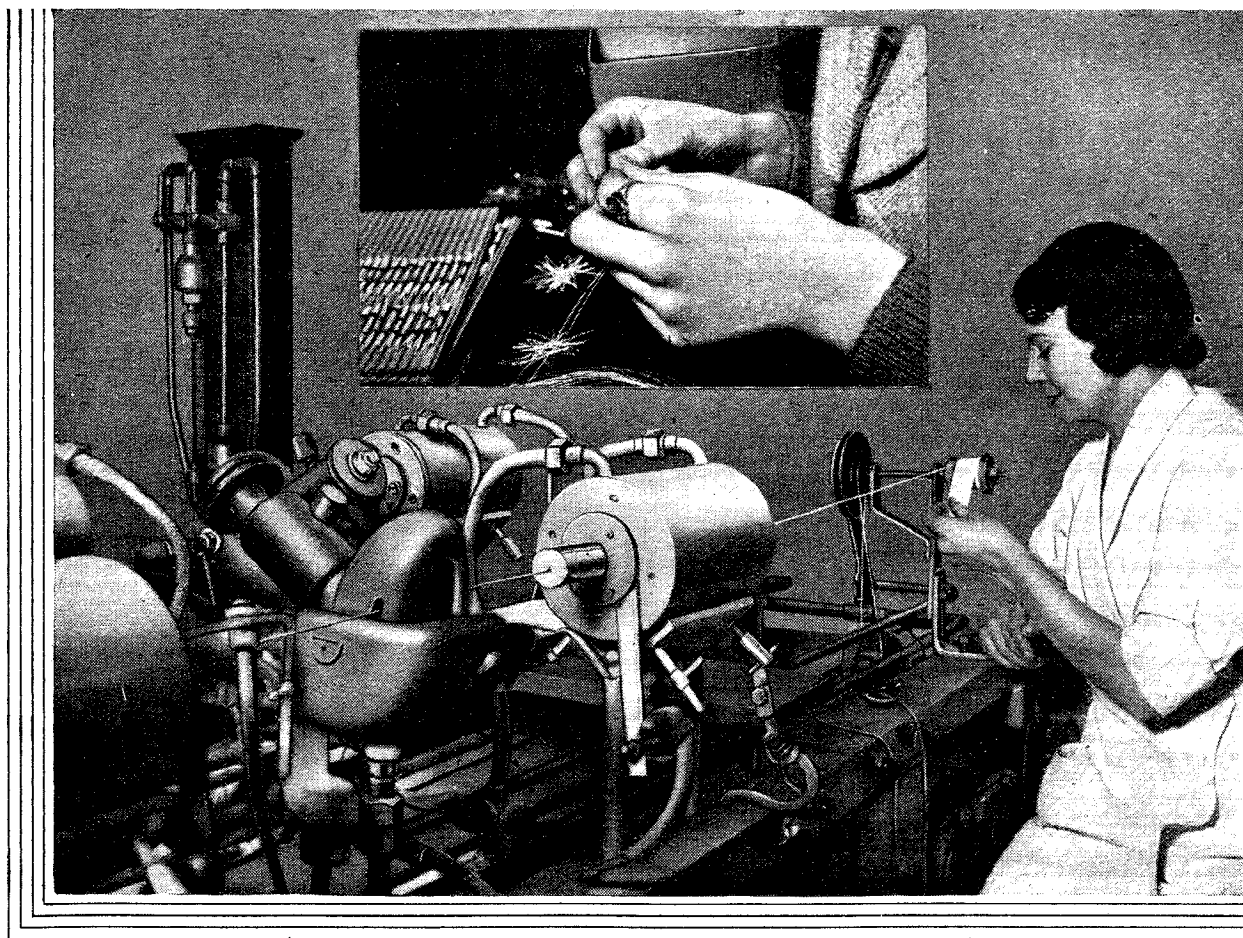

HEATER Coating is a highly specialised process vitally concerned with the life of the valve, the greatest care being taken with this and all other processes to ensure the longevity associated with Brimar Valves.

BRIMAR
BVA
VALVES

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.




The stars

look down . . .

. . . upon the sleeping villages and towns of England. Over the peaceful scene the moon mounts guard with watchful eye. Yet, at any given moment, should the necessity arise, the quietest country village can be in instant communication with the greatest city; can command its resources and enlist its help. Our products for many years have served in spreading human happiness and in forging links between men, and to-day we still proudly play our part in maintaining human fellowship.

DUBILIER
CONDENSER CO. (1925) LTD.

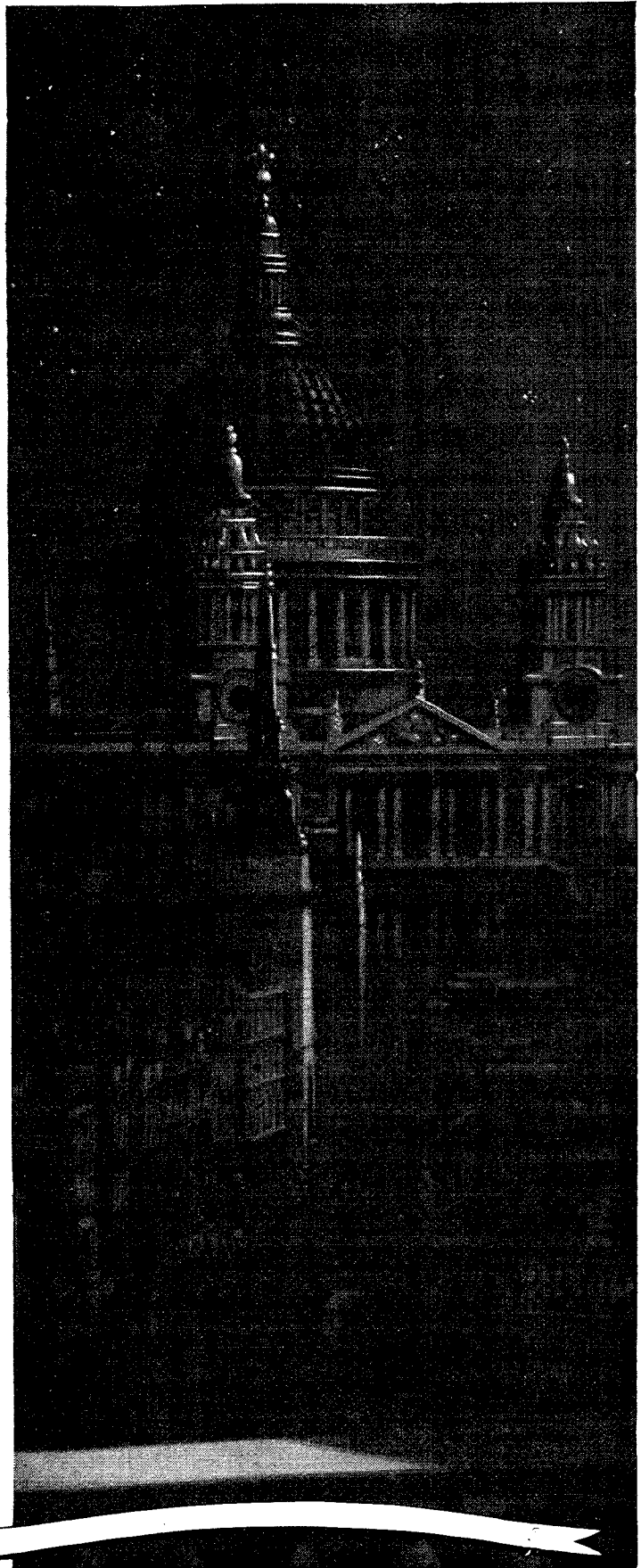

MORSE METHODS

Notes on Learning the Code and Operating Technique

OF late the morse code has been very much in the news. Some indication of the widespread interest in the subject is given by the fact that sales of the *Wireless World* booklet "Learning Morse" have now passed the quarter-million mark. Even the columns of *The Times* have carried a voluminous correspondence on the learning of the code.

Far too much stress has been laid, both in *The Times* correspondence and elsewhere, on the relatively simple matter of learning the code; that is, of memorising the morse symbols corresponding to each letter and figure. Admittedly, the use of some of the ingenious aids to memory that have been suggested may save a few hours in a process that in any case should not take more than a day or two. But the point is that such aids involve an indirect line of thought that is far too slow even for the slowest reception or transmission of signals. It would hardly be an exaggeration to say that the memorising of morse symbols as such is a waste of time, if not worse. What the would-be wireless operator must memorise are, for reception, rhythmic sounds, and, for transmission, rhythmic wrist movements. Until these are firmly impressed on his subconscious mind, he is a long way from becoming competent.


What seems to be a more direct method, and one that is less wasteful of effort in the early stages of instruction, is described by T. R. McElroy, the American champion telegraphist, in the May *QST*. Writing under the title, "Good Morse is Easier," he claims to have succeeded in getting a class of average beginners, none of whom knew a dot from a dash, to copy simple words at 20 words per minute during their first evening's instruction. This is how he did it, in his own words:

"On the ordinary paper slip, in a Mac Recorder, made with an ordinary hand-key, I made about half a dozen dots spaced very widely apart. Then, after a minute or so, I made a half dozen series of two dots, the two dots being right together as they should be, but much space between each group of two dots. Then, after an interval, three dots, the same way. Then four dots. And then five dots. Then two dots again as originally. On the first night I ran that slip through my Mac Auto at 20 words per minute. A dot ran through, and I announced loudly 'That is a dot. One dot, or dit, is the letter E. Now here it is again; write it down with your pencil. Forget that it is dit—it is E.' And the slip meanwhile, running through at 20 words per minute, had come to the

second dot. Each of the 16 persons in the group almost automatically wrote E when they heard it.

"Then we came to the two-dot group. I said 'Now we'll hear two dits. Listen.' And along came dit dit at 20 words per minute. I said 'That is I. Now here it is again. Write it down with your pencils when you hear it.' And the slip, running all the while, came to the two dots, and again automatically the group wrote I. After doing that a half dozen times, they would recognise I when they heard it. Mind you, they had never heard a dot or a dash before. But at 20 words per minute they automatically slapped down I. Then the letter S in the same way. Then we came to the letter H and the figure 5 in the same way. And then back over it again, excepting that this time I said 'Now, remember this is E,' and a single dot ran through. 'This is I,' and two dots ran through. 'This is S, etc. Now then, friends, here is a word. Write it down just as you did the letters. Don't let it fool you.' And then letter S ran through. All of this at 20 words per minute, you understand, but with a lot of space between the letters. Then the letter I and then the letter S again. 'And now, friends, you've copied the word SIS at 20 words per minute. Isn't it easy?' And by showing them how simple the code is, and how easy to copy at 20 words per minute, they had the job licked before they had hardly started. Then came the word HIS and the word SHE, etc.

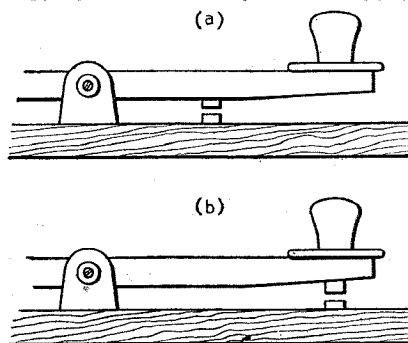"The second lesson, two nights later, I took them to the dash characters, and the third lesson, two nights later, to the combinations. Very easy ones, of course, but words just the same. The entire group, after the first week, or three nights, one hour each night, were copying, automatically and happily,



Courtesy T. and R. Bulletin
Sketch (exaggerated) to show how the contact gap is dependent on key design.

easy words at 20 words per minute, and copying them correctly, too."

On the subject of operating technique, B. W. F. Mainprize makes some useful comments in the June *T and R Bulletin* on details that have seldom, if ever, been discussed in print. Writing on the proper tension of the manipulating key spring, he urges that it should be light, maintaining that the function of the spring is merely to prevent the contacts from closing under the weight of the lever; only slight resistance should be offered to downward pressure. This accords with the theory that the thumb and first finger should play an important part in opening the contacts, and that this operation should not be left almost entirely to the spring. Although some experts will maintain that the lightness of spring tension implied is excessive for regular work, it will probably be generally admitted that the use of a very light tension at the early stages of learning helps to encourage correct methods of manipulation, especially wrist action.

The same writer also advocates a wide gap for the key contacts, particularly in the beginner stage. He rightly points out, however, that it is useless to specify the actual gap unless the type of key is specified as well. Referring to the accompanying diagram, both keys are set to the same gap, but the finger rest of (a) will be depressed through twice the distance of (b). Depression is not only a matter of gap width; the dimensions between fulcrum and gap and fulcrum and finger-rest are also factors. Finger-rest depression is what really matters; from 1/16in. to 1/10in. is suggested for beginners.

Technical Progress Abroad

A SOLUTION to the problem of obtaining exact tracking between signal and oscillator circuits of a superheterodyne receiver at three arbitrary frequencies is given in the second part of an article reprinted from the Australian journal *A.W.A. Technical Review* in the July issue of *Wireless Engineer*. Occasional departures from our sister journal's practice of publishing only original matter are being made to assist those unable to obtain journals from abroad.

The translation of foreign papers of special interest and, occasionally, reprints from certain journals printed in English which are not readily available in this country, are, of course, additional to the many pages of each issue which are devoted to abstracts from the world's technical journals.

CONDENSER SMOOTHING

Performance in Conjunction with Rectifier Circuits

By

E. H. W. BANNER,

M.Sc., M.I.E.E., F.Inst.P.

CONDENSERS act as smoothing agents by virtue of their property of tending to prevent a change of voltage when they are connected directly across a circuit carrying unidirectional current, as in Fig. 1, but not when connected in series in an AC circuit as in Fig. 2. It may be noted here that the addition of a second condenser at B in Fig. 2 results in the Villard circuit used for some X-ray apparatus, where the voltage wave-form is sinusoidal.

The voltage curves for a full-wave rectifier circuit are shown in Fig. 3 where the full line *a* is the sine wave

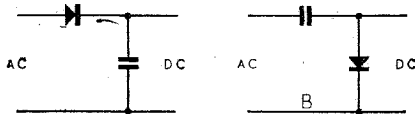


Fig. 1. Half-wave rectifier and condenser smoothing.

Fig. 2. Parallel rectifier, no smoothing.

for perfect rectification (not obtained in practice). Perfect smoothing maintains the voltage at the peak value for the whole cycle as at *b*. This is the case with almost any value of capacitance on no load, but load tends to discharge the condenser and so produce a falling wave-form as at *c*. Approximate calculations for the capacitance necessary for a given volt drop are as follows. With condenser smoothing the drop in voltage is inversely proportional to the resistance (which itself is inversely proportional to load), the frequency and the capacitance. Then

$$dV, \text{ the drop in voltage} = \frac{V}{2RfC}$$

where

- V = load voltage (volts)
- R = load resistance (ohms)
- f = frequency (cycles per sec.)
- C = capacitance (farads).

Alternatively the drop may be expressed in terms of current as $dV =$

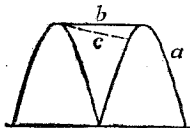


Fig. 3. Full-wave rectification. *a*, *b*, with smoothing on no load; *c*, smoothing on load.

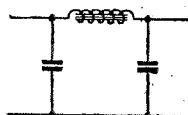


Fig. 4. Inductance and capacitance smoothing.

Calculations for smoothing by condensers are given, with examples, although for low-voltage circuits where condensers are cheap the calculations are often neglected. The measurement of voltage on a rectified supply is not quite the simple matter often assumed, and various measurements are detailed. The uses of metal-rectifier units are included

$$\frac{I}{2fC}, \text{ where } I = \text{load current, amperes.}$$

Since $f = \frac{2}{t}$, where t = time of one-half cycle, the second expression may also be shown as $dV = \frac{Vt}{RC}$ and as

$$I = \frac{V}{R} \text{ a further expression is } dV = \frac{It}{C}$$

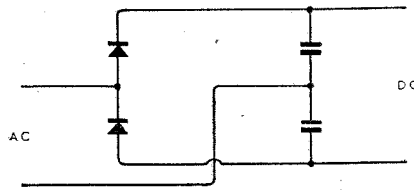


Fig. 5. Greinacher circuit.

Any of these alternative expressions may be used as convenient, with the reservation that they are approximate, the error increasing with the load. The error is partly due to the fact that no rectifier has a perfectly linear characteristic under all conditions.

As an example consider the case of a full-wave rectifier on 50 c/s mains, output voltage 1,000 V, peak; load current 100 mA and drop in voltage per half cycle to be 50 V.

$$\text{Then } dV = \frac{I}{2fC} \text{ or } C = \frac{I}{2fdV} = \frac{0.1}{100 \times 50} = 20 \mu\text{F.}$$

But if the load current is only 10 mA, then for the same capacitance of condenser dV will be only 1/10, or 5V, or alternatively if dV may be 50V with this load current, then the capacitance may be reduced to 1/10, or 2 μF .

Whilst the calculations are necessary for high voltage circuits where condensers are expensive and a small known ripple immaterial, if the supply is required in a radio output circuit such as a directly heated filament, or for anode voltage in a receiving valve, any ripple becomes audible and objectionable as a mains hum and must be eliminated by further smoothing. Consequently for such low voltage circuits simple values of capacitance such as 2, 4 or 8 μF are generally used after trial.

Inductance smoothing alone is generally less satisfactory, as the inductance usually has appreciable resistance, and this causes a permanent power loss, not found with condenser smoothing. Also the voltage drop increases with load, so that "regulation" or $\frac{V(\text{o.c.}) - V(\text{load})}{V(\text{o.c.})}$

is bad, where $V(\text{o.c.})$ is voltage on open circuit and $V(\text{load})$ the voltage on load. A combination of condenser and inductance smoothing is generally the best arrangement, the common case being as in Fig. 4, or with more units similarly connected.

Where a voltage doubling circuit such as the Greinacher in Fig. 5 is used, the wave-form comprises two symmetrical halves about the AC base line as in Fig. 6. In this case let V be the RMS input voltage, then the smoothing will ensure the voltage being maintained at the peak value of the wave, or $\sqrt{2} V$. But because

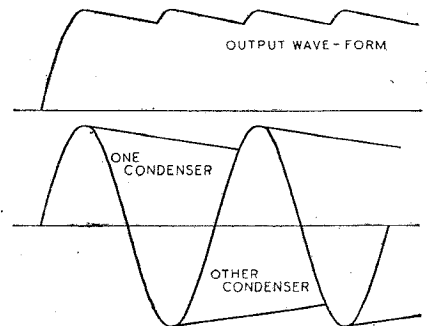


Fig. 6. Wave-forms in the Greinacher circuit.

of the voltage doubling the total line voltage will be $2\sqrt{2} V$, or about 2.8 times the RMS input voltage. Here there are two condensers in series, each subjected to $\sqrt{2} V$. The calcula-

tion for capacitance should be made by assuming there to be one condenser only, then splitting it into two series condensers each of *double* the capacitance. The condensers will only have to withstand half the total voltage so that the energy involved in both condensers is the same as one for the full voltage. A full analysis of this circuit has been given by the author¹. Fig. 7 shows a voltage doubling circuit with a common line, very useful for retaining a common earth point if specially required. Here the capacitance of the condenser is calculable as before.

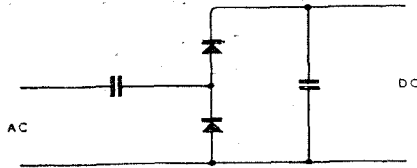


Fig. 7. Voltage doubler with common AC-DC terminal.

From the original expressions for smoothing it will be seen that the frequency is involved. For half-wave rectification the effective frequency is halved and so the condenser voltage drop is approximately doubled. For this reason some circuits, such as radio transmitters, use a frequency higher than 50 c/s. for more economic smoothing. Figs. 8 and 9 show the factors of half- and a full-wave rectifier circuits respectively, and the peak, RMS and mean values are marked. For a fully-smoothed circuit as Fig. 3 b all three values will be equal, and will be read on any suitable voltmeter. The half-wave circuit has a lower RMS and mean value for the same peak value and the resulting values of peak factor (peak/RMS) and form factor (RMS/mean) will differ, as follows:

	Half-wave	Full-wave
Peak factor	2	1.414 ($\sqrt{2}$)
Form factor	1.57	1.11

The peak voltage is not shown directly by any voltmeter, but the addition of a rectifier and condenser to an electrostatic voltmeter forms a suitable peak voltmeter². A spark gap will spark over at a voltage proportional to the peak value. The electrostatic, moving iron, thermal

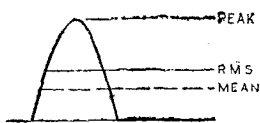


Fig. 8. Half-wave factors.

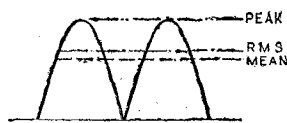


Fig. 9. Full-wave factors.

and induction types all read RMS voltage, more or less accurately, but the rectifier instrument reads the mean value, although it is calibrated in RMS units, on the assumption of a sine wave-form, which may lead to considerable error.

A recent article³ shows various rectifier and condenser circuits to which much of the foregoing may be applied. Rectifiers may in all cases be either valves or metal rectifiers, as convenient. Each has merits and demerits. When metal rectifier units are used (4 elements bridge-connected with two AC and two DC terminals) these may be used for many of the circuits by paralleling two sections and using the resulting two elements in series with up to double the load capacity. The bridge rectifier of Fig. 10 may be connected in the circuits of Figs. 5 and 7 by connecting the AC terminals together as a centre point, the two DC terminals forming the outer terminals for the two rectifiers in series.

Finally, it should be noted that where there is no transformer there is a direct electrical connection between the mains and the output side, which is usually to be avoided for low and medium voltages. A double-wound transformer removes most of the shock risk from live output terminals to earth.

¹ Brit. Journ. Radiology, 6, 1933, p. 360.
² J. Sci. Instr., XI, 7, 1934, p. 218.
³ Wireless World, March, 1942, p. 60.

Book Received

Radio Trouble Shooter's Handbook, by Alfred A. Ghirardi.—This book is essentially one for the serviceman; it contains carefully tabulated data of receivers upon the American market, together with notes concerning clearing faults in them. In this part of the book, over four thousand sets are dealt with. Information is given concerning the suppression of various types of electrical interference most commonly encountered. Special attention is paid to car radio, and full wiring diagrams of the electrical gear are given in a large number of cases. Pp. 710. Published by Radio and Technical Publishing Co., 45, Aston Place, New York, U.S.A. It may be obtained from A. F. Bird, 66, Chandos Street, London, Sherratt and Hughes, 34, Cross Street, Manchester, and Cornish Bros., 39, New Street, Birmingham. Price 3.50 dollars.

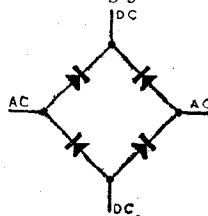


Fig. 10. Bridge rectifier (full-wave).



VARIABLE CONDENSERS
—DRIVES—
AUTOMATIC TUNERS

FOR many years prior to the outbreak of War, it has been our pleasure to supply several of your leading radio receiver manufacturers with the latest designs in variable condensers and vernier drives. We also equipped thousands of your sets with precision mechanical tuners and your portables with midget variable condensers.

Our extensive factory, although still producing vast quantities of radio parts, is also engaged on other work of extreme National importance, and, as a result, both your Country and ours must restrict the manufacture of domestic radio receivers.

The General Instruments Corporation will again be ready to serve you when conditions allow with all that is best in

VARIABLE CONDENSERS—DRIVES
—AUTOMATIC TUNERS

Register your name with our Representative now. He will forward you information on our products as soon as they become available.

THE GENERAL INSTRUMENTS CORPORATION

ELIZABETH, N.J., U.S.A.

Represented by
Frank Heaver Ltd. Kingsley Road, Bideford, N. Devon



CRYSTAL DEVICES

The care and precision with which Astatic Crystal Products are made insures highest operating efficiency and long, satisfactory service. No Astatic instrument ever leaves the factory without first having been thoroughly tested and found to meet the exacting standards of performance that have made these products so desirable. For amateur, studio, public address, inter-communicating sound systems and recording sets Astatic devices are accepted favourites—dependable and yet surprisingly low in cost. Astatic will be ready to supply you again as soon as circumstances permit; in the meantime Astatic crystal devices are doing their part in helping to win the war.

Register your name with our Representative for your future benefit

The
ASTATIC CORPORATION

YOUNGSTOWN, OHIO,
U.S.A.

TORONTO, CANADA

* * *

Represented by
Frank Heaver Ltd. Kingsley Road, Bideford, N. Devon

Letters to the Editor

Pick-up Design : Mass-produced Hearing Aids : Training Operators

Making a Moving Coil Pick-up

I SHOULD like to congratulate Mr. Brierley on the ingenuity of design and excellence of results of his pick-up, as described in the July issue. I have been working on similar lines, and the following remarks may be of interest.

First, I should like to ask Mr. Brierley whether he has tried any experiments to determine the best trailing angle for the needle. I note that he has made his nearly vertical (2 to 3 degrees), and that Mr. Voigt has made a similar recommendation. Most commercial pick-ups have about 30 degrees, and there is presumably some reason for this. So far as the reproduction of the groove waveform is concerned, this angle should be the same as that used in recording, viz., practically vertical. There is, also, however, the problem of ensuring that the point slides smoothly along the groove without chatter. If the case is at all analogous to that of a walking-stick dragged along a rough pavement, then there is no question but that some appreciable trail is necessary, and that the greater it is the better. In the pick-up which I have made the trailing angle is 10 degrees, and satisfactory results have been obtained.

I should also like to ask whether there is any difficulty in changing the needle from the points of view of inserting it the correct distance and of the hole in the celluloid coil former becoming enlarged. What is the order of the needle life obtained?

Mr. Brierley does not mention that to ensure correct tracking the pick-up head must be set on the carrying arm at an angle. I agree that, provided the carrying arm is made fairly rigid, there is little difficulty due to its resonances. Vertical and torsional rigidity are of more importance than the lateral stiffness. I have used a piece of H-section brass curtain rail with a square bar of hardwood screwed along it.

In my experience extreme lightness of arm and head and a spring counterbalance, as opposed to a counterweight, are not essential. The head of my pick-up weighs 105 grams, and the balance weight is nearly 400 grams, yet I have been able to play satisfactorily a markedly warped record with a vertical pressure of only

15 grams ($\frac{1}{2}$ oz.). The warp at the outside of this record is 1 mm., peak to trough. For the simplest kind of warp of this magnitude, the maximum vertical accelerating force is 0.45 gm., which is quite negligible in comparison with the steady weight of 15 gms. Eccentricity of the record ("a swinger") has a similar effect.

The counterweight only adds a small fraction of its mass to the effective mass of the head. The fraction is the square of the ratio of the distances of head and balance from the fulcrum. Thus, in the above example the balance only adds effectively some 25 grams to the head mass. The use of a spring instead would only save this amount. Of more importance, in my opinion, is the freedom of movement of the carrying arm in the vertical and horizontal directions. This depends on the workmanship and design of the pivots, on the total load and on the stiffness of the wires used to carry the pick-up output. The horizontal movement is the more difficult to arrange satisfactorily. The use of a spring counterbalance reduces the total vertical load which the bearing has to carry, but only at the expense of a considerable side thrust. The ball bearings fitted on some commercial pick-ups are very poor. After a very little use, they move in a series of small jerks because the races are made of soft metal, and wear very rapidly. Such a bearing is temporarily in use in my pick-up. A force of 4-5 grams at the needle tip is needed to produce horizontal movement. The vertical pressure for proper tracking may, therefore, need to be increased by about this amount.

The vertical pressure required depends on the mechanical impedance of the needle tip to lateral movement. At low frequencies this depends on the stiffness of the suspension and the bass resonance. The latter occurs where the head mass resonates with the suspension stiffness, and the impedance is then greatly increased. It is sufficient to have this resonance as low as 20 c/s. In my pick-up the suspension stiffness is 19 grams per mm. movement of the needle tip. This gives a bass resonance of 21 c/s with

a head of 105 grams. A vertical pressure of 15 grams is then adequate at all frequencies on the H.M.V. test records except 25 c/s, where 22 grams is necessary.

This pick-up is of the moving iron type, and the "Silent Stylus" needle is held without any clamping screw. Oil damping in the form of a drop of vaseline is applied to the tip of the armature. The construction is more complicated than Mr. Brierley's model, and the frequency response trails off above 5 kc/s. The voltage output is slightly more than his, but no transformer is necessary. This, I think, the principal advantage of the moving iron type. The magnet I have used is not nearly so good as his, and I estimate that with redesign an output of between two and three times the present value could be obtained.

J. H. MOLE.

Dewsbury, Yorks.

"Hearing Aids for the Million"

THE articles and correspondence columns of your excellent paper have rightly expressed a desire for improved hearing-aids for the deaf.

Your Editorial stresses this and chides my profession for lack of ardour in this matter. May I plead on their behalf that the experts are probably too busy to read anything outside their medical journals.

The cause you are sponsoring is one of the most worthy of attention. There is, in my experience, no affliction of the senses that produces the same moroseness, irritability and generally hopeless outlook on life that deafness engenders in its victims. The deaf patient, unlike, say, the blind, frequently treads a path that becomes increasingly miserable, both to himself and to his immediate social contacts.

As regards the apparatus itself, this should be as nearly perfect as possible for the deaf and often suspicious individual (suspicious of the world as a result of his infirmity) can usually be persuaded to try an expensive piece of apparatus on "sale or return" terms, but will be very disappointed if he cannot hear fairly well at once.

A tone corrector with a great deal of emphasis, at maximum, on the higher frequencies should be included, and this should be manually variable by the patient if space, size and weight considerations permit. Alternatively,

The Editor does not necessarily endorse
the opinions of his correspondents

the frequency characteristics might be adjusted by the service man.

As regards distribution, the apparatus might be distributed through the National Health Insurance Scheme with some supervision by Ministry of Health doctors in addition to the usual recommendation from the insurance practitioner, and for the remainder of the population a Government subsidy might well pay for itself in the resulting increased efficiency.

As a medical man my point of view is probably my own, but at least I hope I have removed your charge of too per cent. indifference on the part of my profession.

ROBERT F. E. HARRINGTON,
M.R.C.S. (Eng.), L.R.C.P. (Lond.)
Rochdale, Lancs.

AS a free-lance research worker I am in entire agreement with Mr. R. W. Lowden's views as expressed in the July issue of *Wireless World*.

Deaf-aids cannot be handled by salesmen as an ordinary retail commodity, and it is definitely dangerous to a person suffering from some forms of deafness to attempt to do so.

Not only must the design and operation of an instrument be very accurately understood by the person carrying out tests with a deaf subject, but he must also have a very clear idea and knowledge of the medical side. The human ear, like the eye, is a very delicate and complicated piece of mechanism, and a person showing signs of deafness may easily have what hearing capacity there is destroyed by non-recognition of the factors causing it. It may arise from an acute condition of rheumatoid arthritis in other parts of the anatomy or from an advanced state of catarrh. If a patient has excessive blood pressure it must be known and every precaution taken. A valve aid is liable to do serious injury in a case of this kind, due to the volume irritating the auditory and associated nerves.

In every instance where I am approached regarding a hearing aid I invariably endeavour to first discuss the matter with the medical man in charge of the person concerned. I would strongly recommend that before any attempt is made to mass-produce the equipment, the British Medical Association should be asked to consider the matter.

I would even go so far as to say that no one should be allowed to handle deaf-aids until they have passed some form of examination set by the British Medical Association in collaboration with the Institution of Electrical Engineers.

J. STANLEY JOWITT,
Lytham St. Annes.

THE fears raised by Mr. Lowden in connection with the sale and servicing of hearing-aids by the wireless trade are worthy of consideration.

It is appreciated that the trade at present does not know what is involved, and it is therefore suggested that the policy best suited to the industry is for the companies taking up this matter to appoint only certain dealers in different districts who have the necessary standing and who have agreed to have some training.

It is not essential for an agent to carry any stock, but he should be equipped with what can be termed a predictor. This consists of a small microphone, amplifier and switches, which by easy manipulation can be made to present a number of combinations of different response characteristics required by deaf people. The test would conclusively inform the client what benefit could be obtained from the use of a deaf-aid and an order could be placed for an instrument to give the same performance. I believe that no deaf person would object to paying a small fixed charge for the test.

For maintenance, I suggest an exchange system for defective parts.
C. B.

"Operators in the Making"

I AGREE with all except one of the statements made by "Raw-C.W." in the July issue.

When a learner of telegraphy gets past the morse memorising stage, practice gradually brings up his speed, but it is my experience, having done telegraphy instructional work since 1937, that different speed stages are reached in jumps, i.e., 8's, 10's, 12's, 14's, 16's, 18's, 20's, and so on.

The stale period he mentions—15's—does not require his remedy to counteract it. The only remedy is a rest. This has been proved over and over again in a very practical manner.

At the end of a session of work prior to a holiday, a stale 16's-18's student who could not do 20's, no matter how he strove, found it easy after the holiday period of a week or so. The student returns "fresh" to the job, and sits down to the key, and—there it is.

My remarks above apply to manipulation. Receiving comes more easily.

As a civilian technical instructor to the Air Ministry, I have seen students prior to, and at the beginning of hostilities, driven in some cases nearly frantic, and afraid to touch the key. One particular case had to go into hospital. A rest was the solution.

H. ARMSTRONG.

The North-Eastern School of
Wireless, Newcastle-upon-Tyne.



In the future, as in the past, we shall be ready to offer you the latest designs in:—

**I.F. TRANSFORMERS of all types
AERIAL and OSCILLATOR COILS
TRIMMER and PADDER CONDENSERS
"SILVERCAP" CONDENSERS
COIL FORMS, etc.**

and all that is best where parts of this nature are concerned.

Present day restrictions applying to both exporting and importing are in the interests of our combined war efforts.

We are extensively engaged on Defence work, but when Victory comes and restrictions withdrawn, our parts will be ready to use in your receivers and our Engineering Laboratories will be at your service.

Register your name with our Representative now. He will forward you information on our products as soon as they become available.

**THE F. W. SICKLES CO.
CHICOPEE,
MASS., U.S.A.**

Represented by
Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon



**KURZ - KASCH
RADIO KNOBS—DIALS
INSTRUMENT KNOBS**

Circumstances to-day are such that unless you have the necessary Import Licences and Priorities we cannot continue to serve you. We look forward to the time when these conditions will no longer exist.

In the meantime we are busily engaged on essential war work and it is quite possible that you may still be using Kurz-Kasch mouldings on Lease-Lend instruments and other equipment.

We always appreciated your business prior to the introduction of restrictions and we shall be ready once again to satisfy your most exacting needs as soon as circumstances permit.

Kurz-Kasch will always offer you the finest quality and latest fashions in plastics.

Register your name with our Representative now. He will forward you information on our products as soon as they become available.

KURZ-KASCH INC.
Moulders of Plastics,
DAYTON, OHIO, U.S.A.

Represented by
Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon.

Brains Trust

Solution to Problem No. 3

TO answer your question, it is necessary to go back a little and ask what "mixing" really is. It will then become apparent that you are not so much putting a problem before us as revealing a certain confusion caused by the unscientific use of the terms "additive" and "multiplicative"; it is unfortunately difficult to find the original sinners in this connection.

Fundamentally, mixing for super-heterodyne reception is the same as amplitude modulation. In practice, of course, the electrical raw material fed into a mixer consists of two radio frequency waves, whose frequencies f_1 and f_2 differ by a fairly low radio frequency, the "intermediate frequency" (approximately 460 kc/s in modern receivers for domestic use). The modulating stage of a signal generator or transmitter is supplied with an RF wave and an audio-frequency wave.

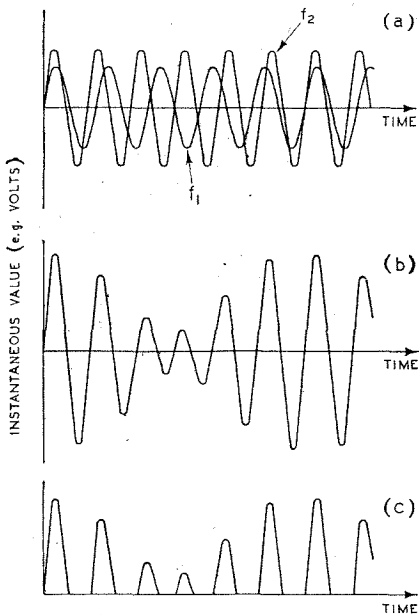


Fig. 1. (a) Two sine waves of frequencies f_1 and f_2 with separate existence. (b) Wave whose value at any instant is the sum of the original waves f_1 and f_2 . (c) Result of rectifying wave-forms of either (a) or (b).

Now, consider what happens when two sine waves co-exist. Fig. 1 (a) deals with the case where this happens: the two waves are shown as being of different frequencies f_1 and f_2 respectively, and their resultant is

(See page 185)

obtained as the sum of the individual values at any instant of time, as shown in Fig. 1 (b). It can be shown that the resultant is a wave of frequency $(f_1 + f_2)/2$ and amplitude changing at frequency $f_2 - f_1$, assuming f_2 to be the higher frequency.

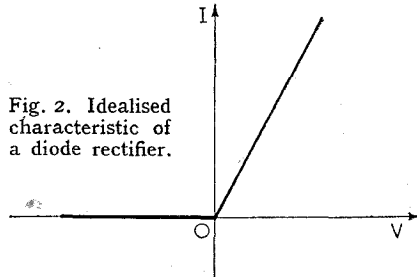


Fig. 2. Idealised characteristic of a diode rectifier.

Where this difference frequency is small compared with f_1 , one speaks of "beat motion." Yet whether the resultant could be described as beat motion or not, it would be incorrect to say that it contained a difference frequency component: it is merely the sum of two sine waves, and no matter how much maths we applied to it, its average value over a few complete cycles of f_1 or f_2 is zero. Physically, a simple check may be obtained with the aid of two audio oscillators (one of which should be variable), a cathode-ray oscilloscope, and a pair of headphones or loudspeakers. On connecting the oscillators to the X-deflector plates and suitably adjusting their frequencies and the time base, a picture of the Fig. 1 (b) type will obtain. Connecting the oscillators to the headphones, the observation will depend on the value of $f_2 - f_1$. If the notes radiated from the sound reproducers be 800 c/s and 1,000 c/s respectively, this is exactly what one will hear, barring outside noises; i.e., there will be no 200 c/s note. On making the difference in pitch smaller, i.e., setting the frequencies to 998 and 1,000 c/s respectively, matters would appear to become slightly different, for a distinct thud-thud noise would become noticeable, a vibration of $1,000 - 998 = 2$ c/s which appears to be almost independent of the carrying note of $\frac{1,000 + 998}{2} = 999$ c/s. Yet there can be but little doubt that the ear is cheating in telling the brain

that an independent difference frequency component is present in the last instance, for it is not possible to hear a note below 20 c/s or so in the normal course of events. The hearing expert would call the difference note heard "subjective," and blame either the nervous system or its inadequate discriminating powers or the mechanism of the ear for non-linear behaviour.

The latter point is the key to the whole problem. To obtain genuine—i.e., sinusoidal—components at the "combination" frequencies, such as $(f_2 - f_1)$, $(f_2 + f_1)$, etc., the original waves may be applied to a non-linear device, i.e., an instrument whose output is not directly proportional to the input. This is the simplest type of modulator, and its simplest and perhaps most useful representative is the diode valve: idealised, the characteristic between voltage and current is the "kinked, straight line" characteristic of Fig. 2. Hence, on applying the voltages of Fig. 1 (a) to the diode, a current of the wave-form of Fig. 1 (c) would result: this may be described as a unidirectional, pulsating current, and contains a DC component and alternating components of frequencies f_1 , f_2 , $(f_2 - f_1)$, $(f_2 + f_1)$, and

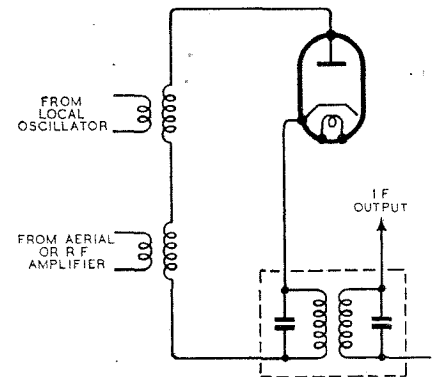


Fig. 3. Circuit of a possible diode mixer stage.

many others of smaller amplitude. These various combination frequencies occur because the output current is proportional to the product of the original waves, among other terms.

While a rigid proof of these last statements requires a certain knowledge of trigonometry, the less mathematical reader may convince himself of their truth by inspecting Fig. 1 (c): this "rectified" wave is evidently

not zero over any significant time interval—its average value clearly varies at the frequencies above mentioned, as may be verified by considering suitable intervals.

In what is usually termed amplitude modulation, the terms f_2 , $(f_2 - f_1)$, $(f_2 + f_1)$ are the carrier and its upper and lower sidebands, and

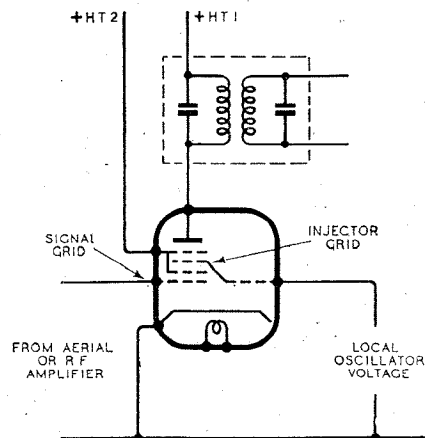


Fig. 4. Schematic diagram of the more efficient hexode mixing stage.

constitute the modulated wave. However, in mixing interest centres on the component $(f_2 - f_1)$, while $(f_2 + f_1)$ represents the unwanted image frequency.

The diode frequency changer is outlined in Fig. 3, including the tuned transformer for developing the output voltage at IF. While used quite a lot for very high frequency work, it suffers from low conversion gain (defined as the ratio IF output voltage signal-frequency input voltage), and interaction between the signal and local oscillator circuits.

Multi-grid valves are frequently used in the hope of overcoming these difficulties, and their fittest survivor seems to be the hexode or heptode, its glass envelope often containing a separate triode for the local oscillator circuit. Mixing takes place through simultaneous application of the signal at the grid nearest the cathode, and the local oscillator voltage to the third or "injector" grid. The IF transformer is, of course, connected in the anode lead. The important point about this mixer is illustrated by Fig. 5, which shows how the ratio

"change in anode current/change in bias of first grid" (the mutual conductance of the first grid relative to the anode), varies with the voltage at the third grid. Hence, with alternating voltages applied to the first and third grids, some of the anode current at least will be proportional to the product "signal volts \times oscillator volts," and hence contain the desired IF component.

You will see, therefore, that all types of modulators or mixers depend on "multiplicative" action, inasmuch the generation of combination frequencies requires (at least part) of the output current to be proportional to the original p.d.'s. While inspection of Figs. 3 and 4 might label one mixing circuit as being additive, because the two input p.d.'s are in series between two electrodes (anode and cathode in Fig. 3), this conclusion is rather meaningless, for the difference between various types of mixer systems depends not on their basic action, but on such finer details as interaction between circuits; input impedances, etc., arising from valve

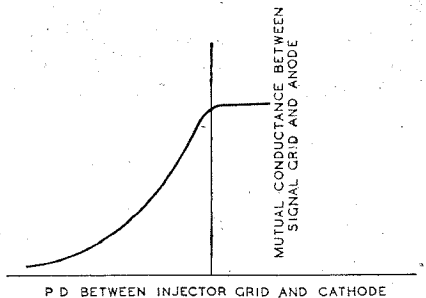



Fig. 5. Indicating the effect of injector grid bias on the mutual conductance from signal grid to anode in a hexode mixer.

structure, as well as circuit design and operating conditions.

These points have been admirably cleared up by E. W. Herold in an excellent descriptive paper entitled, "Frequency Converters for Superheterodyne Reception," appearing in the *Proc. I.R.E.* for February, 1942. T. J. R.

Salvage and Economy

WITH the increasing demands upon the shipping space of the allied nations the need for the salvaging of every scrap of waste paper and rubber becomes greater. It is, however, not only the salvaging of waste paper that is necessary, but the conserving of supplies by economical use. One method of economy is the re-use of envelopes. Statistics, however, show that a large percentage of communications are still enclosed in new envelopes; and we are reminded that care in opening is essential to their re-use.

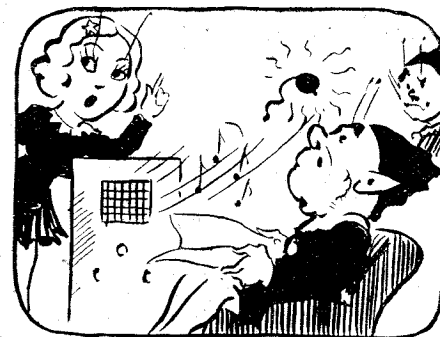

The "Fluxite Quins" at work

Said OO "I bet that's a top 'E,'
'Course maybe it's only a 'D'.
Growled EH "Strike a light!
Why—that set needs FLUXITE,
It sounds like a dead 'C' to me."

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for 30 years in Government works and by leading engineers and manufacturers. Of Ironmongers—in tins, 4d., 8d., 1/4 and 2/8.

Ask to see the FLUXITE SMALL-SPACE SOLDERING SET—compact but substantial—complete with full instructions 7/6.


Write for Free Book on the art of "soft" soldering and ask for Leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE.

TO CYCLISTS! Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT.

THE FLUXITE GUN

puts Fluxite where you want it by a simple pressure. Price 1/6, or filled 2/6.

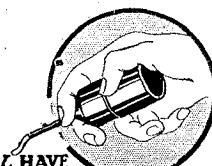FLUXITE LTD.
(Dept. W.W.),
BERMONDSEY
STREET, S.E.1.



ALL MECHANICS WILL HAVE

FLUXITE

IT SIMPLIFIES ALL SOLDERING

GOODS FOR EXPORT

The fact that goods made of raw materials in short supply owing to war conditions are advertised in this journal should not be taken as an indication that they are necessarily available for export

RANDOM RADIATIONS

By "DIALLIST"

Wartime Pruning

THE Americans, I see, have ruthlessly cut down the number of kinds of radio valves that may be manufactured so long as the war lasts. We have done something of the kind, too; and now that this step has been taken on both sides of the Atlantic, is it too much to hope that the two great valve-making industries, our own and that of the U.S.A., will take steps to see that we have no return to a bewildering and unnecessary multiplicity of valve types when peace is with us again? Everyone was agreed, I think, that the pre-war state of affairs was ridiculous. On our own market here were hundreds and hundreds of different types, only a small proportion of which was really needed. The multiplication of types, many with a comparatively small sale, means greatly increased overhead manufacturing costs, and, therefore, high prices all round. It is the nightmare of the wireless shop owner, whose shelves must be packed with a vast number of types.

Too Many Types

The shopkeeper can't very well help himself. Unless he keeps a huge number of types in stock he can't be sure of supplying people readily with what they want. And customers are easily disgruntled if the men behind the counter can't produce what they ask for then and there. One hopes that the bigwigs of the valve industry are already planning a sane, far-sighted policy. There will be a terrific boom in wireless set sales when the war is over, for so many receivers are already long overdue for the scrapheap or the salvage bin. Set makers would have no difficulty in educating the public up to bigger and better radio receivers if only the bugbear of the excessive cost of valve replacements were removed. And it could be removed were valve manufacturers to come to an agreement to confine their main energies to the production of a limited range of essential types.

Cut Out the Out-of-date

Don't think that I'm trying to suggest a brake on progress. Far from it. New and really useful types will be evolved from time to time, and as they are produced there should be a ruthless pruning of the dead wood. Give set owners a reasonable run for their money in the way of valve replacements, but don't keep obsolete

valves in production years and years after they have ceased to be used in new receivers. In any event the pruning suggested wouldn't entail severe hardship, even if out-of-date valves were struck off the list early. Experience of war conditions has taught servicemen to be very clever in adapting existing circuits for valves for which their designers never intended them. And we need more than just cessation of production of obsolete types. We require the early and complete cutting out of the types which have no particularly good reason for existing. At present we have large numbers of, for example, RF pentodes, most of them good, few head and shoulders above the rest in performance, and all differing just a little from each other in their characteristics. For receiving sets two types of RF pentode should suffice. 'Tis much the same story with valves of other classes.

Valve Bases, Too

What I should like to see very much is the adoption of one standard base and one alone for all valves used in receiving sets—everything from diodes to triode-hexodes—and a standard arrangement of the connections. Were the valve industry to announce at the end of the war that as from a certain date no valves would be made with any but one particular base, the thing could be done quite painlessly. When stocks of existing valves with obsolete bases were sold out it would be a matter of small difficulty and small expense to fit new sockets to any receiver that needed re-valving.

Silent Sets

IT is stated that at least one receiving set in ten is out of action nowadays because it has developed a fault and its owner cannot get this put right. From what I see of friends' sets when I go on leave, I should say that this estimate is by no means too high. There are two main reasons for this state of affairs. One is the shortage of skilled servicemen, of whom so many have been called to the Colours; the other is that valves and components for many of the older receiving sets are not now obtainable. Comparatively few of the very old sets that one sees would still be in service in normal times; the need for war saving and the dearth of new receivers have meant that many have been kept in harness long after senile decay had set in. Good servicemen

can often contrive to give a decrepit receiver new life even if they can't get the proper parts to replace those that have failed: I've seen one or two ex-superhets working quite happily as "straights." But to do jobs of that kind servicemen must be good—and have the necessary time. Wireless now plays so important a part in national life that the authorities should pause before they call more trained radio men to the Colours. If they don't, the proportion of sets temporarily or permanently out of action is likely to increase rapidly.

Leave Them to It

Actually it's rather surprising to find how very few fellows who were radio servicemen in civil life one comes across, in branches of the Army at any rate, that are concerned with wireless. I've mentioned before the diversity of civil-life occupations that one finds amongst "other ranks" now skilled in radio and electrical matters. One of the best trouble-spotters in complicated apparatus that I know was a waterworks hand, and he is run close by an ex-bookkeeper. Neither of them knew anything about electricity before enlistment or could have done the simplest of jobs on a radio set. Myself, I'd say leave the remaining wireless servicemen where they are in civil life, except where it can be shown that they aren't really needed—and that, I feel, would not occur very often!

An Improvement

IT'S good to notice that the campaign waged by *Wireless World* against the affected and exaggerated pronunciation of foreign personal and place names by our radio announcers is at last beginning to bear fruit. One of them still offends at times, though he's not so bad as he was. The rest do seem to have seen reason, and it was high time that they did. With the war zones now covering such a large part of the world's surface and embracing so many nations, fresh foreign proper names are always cropping up in the news, and it's a poor business if an announcer overlays them with so thick a coating of would-be correct accent that they become entirely incomprehensible to the listener. I still have a liking for the habit of some U.S.A. announcers, who not only pronounce unfamiliar foreign names carefully and distinctly, but also spell them out.

THE WORLD OF WIRELESS

BRITISH AND AMERICAN BROADCASTS

"BRITISH short-wave broadcasting is as superior to American short-wave efforts as American home broadcasting is to its British counterpart."

In this way Wells Church, who is serving in London as American adviser to the B.B.C. for its North American service, summarizes his observations of the two countries' short-wave services in an article in our American contemporary *Broadcasting*.

He states that the difference so far as short-wave work is concerned, is "that the B.B.C. thinks internationally and speaks with one voice whereas American short-wave radio speaks with half-a-dozen voices and these in terms, largely, of the holding of a (transmitting) licence."

He urges the need for a plan under which all American short-wave stations will operate as a single voice with a unification of programmes. It is inferred that the primary cause of the ineffectiveness of American international transmissions is an inherent insularity.

VALVE PRICES

THE attention of the British Radio Valve Manufacturers' Association has been drawn to the excessive prices being charged for B.V.A. valves, which prices purport to include

carriage and packing. To clarify the Association's policy with regard to valve prices we are asked to state that the B.V.A. prices for valves include carriage and packing. Thus valves reach the consignee free of the expense of carriage or packing.

It is, however, accepted that postage actually incurred by the retailer in forwarding a valve to his customer may be charged, but it will be appreciated that the expenses of such postage can only be from the retailer to his customer.

VALVE SHORTAGE


ASKED in the House of Commons whether he was aware that there was no improvement in the supply of wireless valves (chiefly rectifiers) the President of the Board of Trade said that he was well aware of the importance of securing an increase in the supply of valves for civilian receivers. He stated that short of interfering with the needs of the Services everything possible was being done to release valves of British manufacture and to obtain supplies from the United States.

W.R.N.S. WIRELESS MECHANICS

MEMBERS of the Women's Royal Naval Service can now qualify as wireless mechanics at Fleet Air Arm stations. Their job includes the fitting and repair of radio apparatus in aircraft. Incidentally, they test the apparatus during flight. The training period for these girls is from four to six months. They must have had a secondary school education, have attained


(Continued on next page)

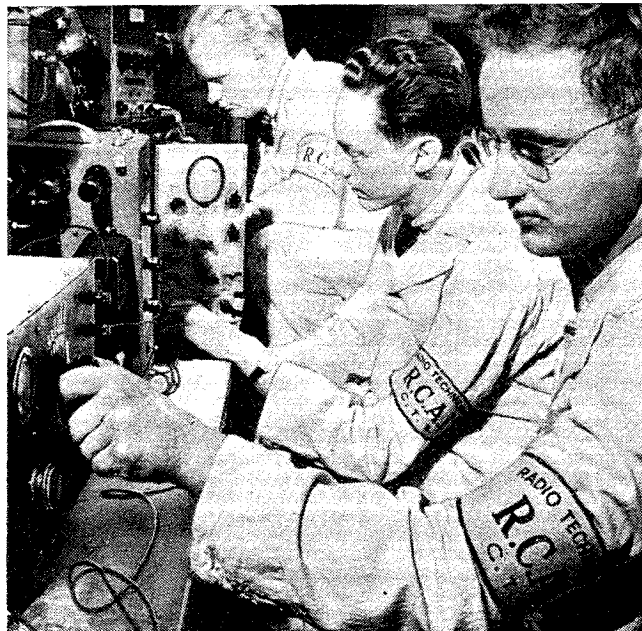PRE-ENLISTMENT classes are now arranged by the Royal Canadian Air Force for prospective radio mechanics, who are given a trade test before entering the Force.



VORTEXION

50w. AMPLIFIER CHASSIS

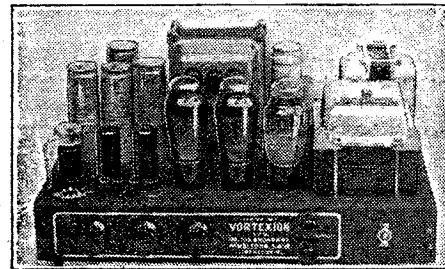


A pair of matched 6L6's with 10 per cent. negative feed-back is fitted in the output stage, and the separate HT supplies to the anode and screen have better than 4 per cent. regulation, while a separate rectifier provides bias.

The 6L6's are driven by a 6F6 triode connected through a driver transformer incorporating feed-back. This is preceded by a 6N7 electronic mixing for pick-up and microphone. The additional 6F6 operating as first stage on microphone only is suitable for any microphone. A tone control is fitted and the large eight-section output transformer is available in three types—2-8-15-30 ohms; 4-16-30-60 ohms or 15-60-125-250 ohms. These output lines can be matched using all sections of windings and will deliver the full response (40-18,000 c/s) to the loud speakers, with extremely low overall harmonic distortion.

CHASSIS with valves and plugs	£17 10 0
Moving Coil Microphones	£5 5 0
Chromium Microphone Stands, from	£1 5 0

Many hundreds already in use

15w. AC & 12-VOLT DC AMPLIFIER

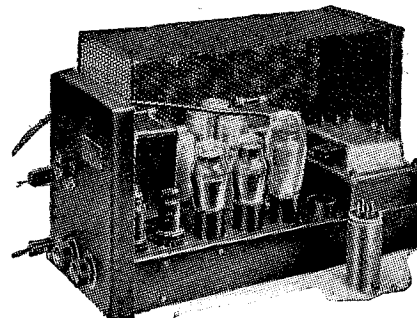

TYPE CP20

This small Portable Amplifier operating either from AC mains or 12-volt battery, was tested by the "WIRELESS WORLD," October 1st, 1937, and has proved so popular that at customers' demand it remains unaltered except that the output has been increased to 17.2 watts and the battery consumption lowered to 6 amperes. Read what the "Wireless World" said :-

"During tests an output of 14.7 watts was obtained without any trace of distortion so that the rating of 15 watts is quite justified. The measured response shows an upper limit of 18,000 c/s and a lower of 30 c/s. Its performance is exceptionally good. Another outstanding feature is its exceptionally low hum level when AC operated even without an earth connection. In order to obtain the maximum undistorted output an input to the microphone jack of 0.037 volt was required. The two independent volume controls enable one to adjust the gain of the amplifier for the same power output from both sources, as well as superimpose one on the other or fade out one and bring the other up to full volume. The secondary of the output transformer is tapped for loud speakers or fine impedances of 4, 7.5 and 15 ohms. Prices

AC and 12-volt CHASSIS with valves, etc....	£12 12 0
AC only CHASSIS with valves, etc.	£8 18 6

Gauze Case for either chassis, 12/6 extra.

Plus 25% War Increase on all above prices.

Orders can only be accepted against Government Contracts.

Vortexion Ltd., 257, The Broadway,
Wimbledon, S.W.19. 'Phone: LIBerty 2814

The World of Wireless—

matriculation standard in mathematics and physics and have a mechanical aptitude.

B.B.C. NEWS

EACH word is now repeated in the B.B.C. morse transmissions of news in English, French and German which are broadcast at 0230, 0300 and 0330 (BDST), respectively, on 261.1 and 49.59 metres.

The news in English broadcast in the overseas services of the B.B.C. is radiated at the following times and on the wavelengths given. The wavelengths used for the two bulletins in the European service at 1000 and 2215 (BDST) are marked with an asterisk.

- 0045: 31.32, 30.53, 25.68, 25.53.
- 0300: 31.32, 30.53, 25.68, 25.53.
- 0445: 31.32, 30.53, 25.68, 25.53.
- 0630: 40.98, 31.32, 30.53, 25.68, 25.53.
- 0815: 49.10, 42.46, 31.53, 31.25, 25.53, 19.82, 19.60, 19.49.
- 1000: 49.59*, 42.46, 41.96*, 41.49*, 31.75*, 31.55, 30.96*, 25.53, 24.92*, 24.80*, 19.82, 19.60, 19.49, 19.42, 16.84.
- 1300: 25.53, 19.82, 19.49, 19.42, 16.84, 16.77, 13.97.
- 1500: 25.53, 19.82, 19.49, 19.42, 16.84, 16.77, 13.97.
- 1800: 31.75, 25.53, 19.82, 19.06, 19.49, 16.84, 16.77.
- 2000: 31.55, 31.25, 25.53, 19.82, 19.06, 16.77.
- 2215: 49.59*, 49.10*, 48.43*, 41.96*, 41.49*.
- 2245: 31.25, 25.68, 25.53, 19.82, 16.77.
- 2315: 31.32, 31.25, 30.53, 25.68, 25.53, 19.82.
- 2345 (ex. Sundays): 31.32, 31.25, 30.53, 25.68, 25.53, 19.82.

IN BRIEF

German Television

It is learned that Germany's television transmissions, which emanate from the station known as "Paul Nipkow," are entirely for the troops. Special theatres are provided with large screens for the reception of the transmissions which, it is believed, are "piped" by low-loss cable from the television studio.

A Westinghouse Promotion

MAJOR L. H. PETER, M.C., A.F.C., M.I.E.E., formerly chief electrical engineer of Westinghouse Brake and Signal Company, has been appointed chief



Major L. H. Peter.

engineer of that company. Major Peter, a one-time chairman of the Radio Manufacturers' Association, is prominent in wireless circles, being specially interested in the training of technicians.

N.B.C. International Division

THE appointment of Fred Bate, who has been director of the National Broadcasting Company's staff in Western Europe since 1932, as head of the N.B.C.'s international division is announced from New York. His experience in Europe, where he has been resident for some 30 years, should be of considerable help to him in his onerous task. He opened the N.B.C. London office in 1932, and, it will be remembered, was injured when the office was bombed in 1940.

Polar Diagram Ready Reckoner

AN award by the American Institute of Electrical Engineering is to be given to Carl E. Smith, chief engineer of stations WHK and WCLE, Cleveland, for his paper on "An Electro-mechanical Antenna Pattern Calculator." In this he gives details of the construction and operation of his invention which mechanically calculates the distances at which a transmission is receivable in any given direction.

New WRUL Beam

THE engineers of the powerful American international short-wave station WRUL, operated by the World Wide Broadcasting Foundation in Boston, Mass., have hurriedly completed a new aerial array which completely covers Madagascar, French Equatorial Africa and the North Coast of Africa.

R.T.R.A.

THE address of the Radio and Television Retailers' Association, which is the combined association merging N.A.R.R. and W.R.A., is Avenue Chambers, 4, Vernon Place, Southampton Row, London, W.C.1 (Tel.: Holborn 8075). J. H. S. Smith, who was president of the W.R.A., has been elected chairman and H. A. Curtis, who has been assistant secretary of N.A.R.R. since 1937, is secretary.

Canadian Spare Parts

ALTHOUGH the production of civilian receivers has been discontinued in Canada, it is hoped that there will not be a shortage of replacement parts for some time at least. So far no restriction has been placed on the manufacture of components. The Radio Manufacturing Association of Canada has stated that manufacturers of components and valves are working on an understanding

NEWS IN ENGLISH FROM ABROAD

REGULAR SHORT-WAVE TRANSMISSIONS

Country : Station	Mc/s	Metres	Daily Bulletins (BDST)	Country : Station	Mc/s	Metres	Daily Bulletins (BDST)
America				China			
WNBI (Bound Brook)	11.890	25.23	5.0.	Chungking	9.410	31.88	4.0.
WNBI	17.780	16.87	3.0†, 3.45‡, 5.0§, 7.0.		11.900	25.21	10 a.m., 11.30 a.m., 12.15, 1.30, 2.0, 4.0, 6.0, 9.15.
WRCA (Bound Brook)	9.670	31.02	5.0.	French Equatorial Africa			
WRCA	15.150	19.80	3.0†, 3.45‡, 5.0§, 7.0.	FZI (Brazzaville) ..	11.970	25.06	5.45 a.m., 9.45.
WGEO (Schenectady)	9.530	31.48	10.45 a.m., 10.0†, 11.55‡.	India			
WGEO (Schenectady)	15.330	19.57	3.0, 4.0, 8.45‡, 10.55‡.	VUD4 (Delhi)	9.590	31.28	10.0 a.m., 2.30, 5.50.
WBOS (Hull)	11.870	25.27	1.0, 1.45, 5.0.	VUD3	11.830	25.36	2.30.
WBOS	15.210	19.72	3.0†, 3.45‡, 5.0§, 7.0.	VUD3	15.290	19.62	10.0 a.m.
WCAB (Philadelphia)	6.060	49.50	7.0 a.m.	Sweden			
WCBX (Wayne) ..	15.270	19.65	12.30, 4.30, 8.30‡, 10.30.	SBU (Motala)	9.535	31.46	11.20.
WCBC (Wayne) ..	11.860	25.30	12.30, 4.30, 8.30‡, 10.30.	Turkey			
WCW (New York) ..	15.870	18.90		TAP (Ankara)	9.465	31.70	9.15.
WRUL (Boston) ..	11.790	25.45	12.45 a.m.‡, 10.30‡.	U.S.S.R.			
WRUL	17.750	16.90	4.0‡, 4.45‡.	Moscow	6.977	43.01	6.15 a.m., 12.45, 7.0, 8.30, 10.0, 11.0, 11.45.
WLWO (Cincinnati) ..	6.080	49.34	7.0 a.m., 8.0 a.m.	Moscow	7.770	38.61	6.15 a.m., 11.0, 11.45.
WLWO	11.710	25.62	4.0, 5.0, 6.0, 7.0, 8.0, 9.0, 10.0, 11.0.	Kuibyshev	10.040	29.88	7.0 a.m., 2.45, 5.30.
Australia				Vatican City			
VLQ6 (Sydney) ..	9.580	31.32	9.0 a.m.	HVJ	5.970	50.25	9.15.
VLG6 (Melbourne) ..	15.230	19.69	9.0 a.m.	MEDIUM-WAVE TRANSMISSIONS			
				Ireland	kc/s	Metres	
				Radio Eireann	565	531	2.40‡, 7.45, 10.0.

It should be noted that the times are Double Summer Time—two hours ahead of GMT—and are p.m. unless otherwise stated. The times of the transmission of news in English in the B.B.C. Short-wave Service are given at the top of the page.
 * Saturdays only. † Saturdays excepted. ‡ Sundays only. § Sundays excepted.

with the Controller of Supplies that they will manufacture a normal quantity of replacements and have undertaken to see that this work does not in any way interfere with their war production.

Canadian Gramophone Records

AN Order recently issued by Canada's Wartime Prices and Trade Board limits the manufacture and distribution of gramophone records and all other products containing natural varnish resin.

Receivers in Canada

CANADIAN manufacturers sold a total of 399,556 receivers in 1941 compared with 438,976 in 1940 and 370,568 in 1939. The number of sets imported by the Dominion was only 4,022, as against 36,062 the year before.

"A Rose by Any Other Name . . ."

WITH the publication of the July issue of the official journal of the Radio Society of Great Britain the familiar title for the past seventeen years of *T & R Bulletin* gives place to *R.S.G.B. Bulletin*. In future the membership badge of the society will include the initials R.S.G.B. instead of T. & R. (which incidentally stood for "Transmitter and Relay" section).

Trans-Pacific Radio Circuit

THE sixth direct radio-telegraph link between the United States and the Far East and the South-western Pacific to be established by R.C.A. Communications since America entered the war was recently opened between San Francisco and Noumea, New Caledonia. The new circuit removes the previous necessity of contacting Noumea via Australia.

New Chairman for B.V.A.

THE Board of Management of the British Radio Valve Manufacturers' Association has elected J. W. Ridgeway, manager of the radio division of the Edison Swan Electric Co., to be chairman of the Association. Mr. Ridgeway retains the chairmanship of the B.V.A. Committee on Production, which office he has held since its creation. In 1924, Mr. Ridgeway joined Metropolitan Vickers Supplies as a radio engineer. In 1930 he was appointed assistant manager of the radio division of Ediswan into which department the radio sales sections of Metropolitan Vickers and the B.T.H. Companies were merged. He became acting manager in 1941, and was this year promoted to manager.



Obituary

WE regret to record the death in America a few months ago of J. C. Wilson, who was formerly with the Baird Company. Mr. Wilson was employed by the Hazeltine Service Corporation, and was the author of "Television Engineering" (1937), one of the first comprehensive textbooks on the subject.

Marconi Instruments

It was revealed by the Chairman of Marconi's Wireless Telegraph Company at the annual meeting recently that the company had purchased the share holding of E. K. Cole, Ltd., in Marconi-Elco Instruments, which is now known as Marconi Instruments, Limited.

COMMUNICATIONS DEPEND....

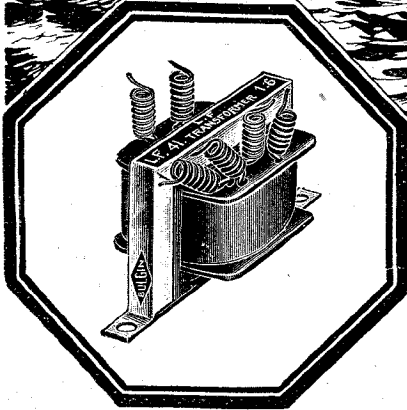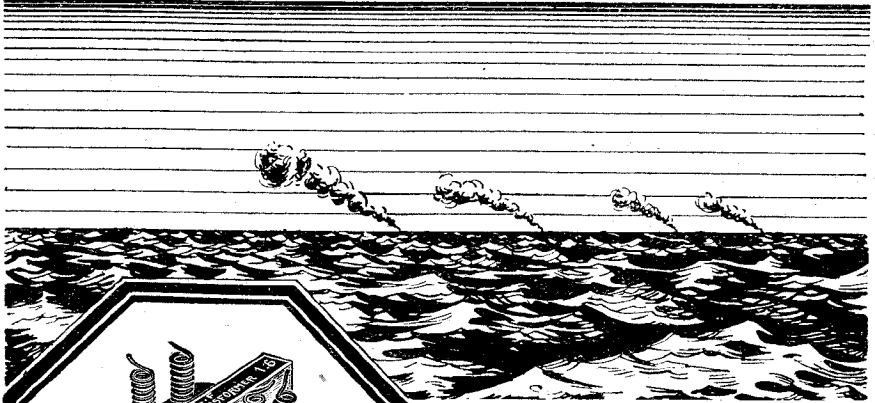

ON SMALL PARTS....

IN countless instances quite intricate pieces of apparatus are wholly dependent on the proved reputation and reliability of their component parts.

All products from the House of Bulgín are pre-eminent for superior design and workmanship and every article bearing our Trade Mark has to pass exacting and exhaustive tests during the course of its production.

We ask the kind indulgence of the Trade on delivery until peaceful conditions return.

*The Choice
of Critics*

BULGIN FOR TRANSFORMERS

THE largest and most extensive range of midget and ultra small intervalve (voltage) transformers in the world. Provided with high- μ cores and carefully proportioned windings of finest enamelled-copper wires. All joints welded; mono-metallic from start to finish for long life under all conditions.

"The Choice of Critics"

BULGIN


REGISTERED • TRADE • MARK

A. F. BULGIN & CO. LTD., BY-PASS RD., BARKING, ESSEX.
TEL.: RIPPLEWAY 3474 (4 lines).

MICRO-WAVE OSCILLATION GENERATORS

THE figure shows the electrode arrangement of a "velocity modulator" for amplifying or generating very high frequencies. The cathode C is followed by two conical control elements and a cylindrical electrode G₂, all carrying increasingly positive potentials. These are followed in turn by two "split" half-wave resonators R₁, R₂, with an intervening conical collector K. At the far end of the tube is a terminal collector K₁ consisting of a disc with radial conical vanes. The tube is surrounded by a main magnetising coil M, with two auxiliary coils M₁, M₂ placed near the gun or cathode.

In the ordinary way the electron stream from the cathode would pass through the tube as a straight beam. The external magnetic field, however, imparts a spiral motion to the electrons so that they "fan out" and enter the electrode G₂ as a hollow rotating cylindrical stream. Input current is applied across the two halves of the resonator R₁ from P through a transmission line T. If the applied currents are of the same frequency as the periodicity

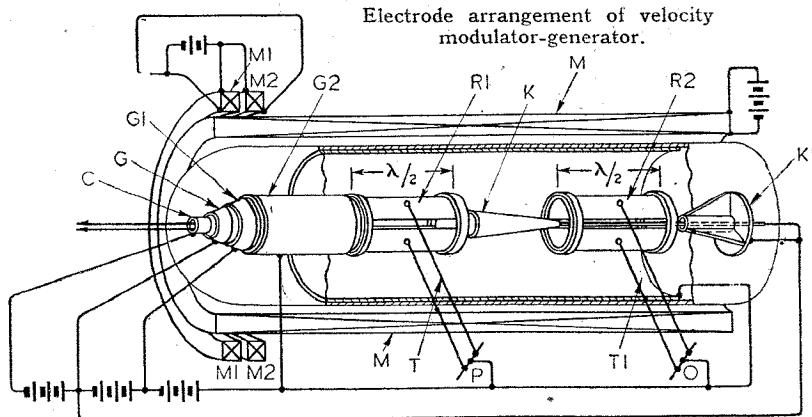

of the rotating stream, some of the electrons will be accelerated and others will be retarded. Certain of the latter will follow a path of diminishing radius and are collected by the conical electrode K. The rest will form a "bunched" stream of varying density, and will deliver power to the resonator R₂, which is coupled through a transmission line T₁ to the output O. If the latter is back-coupled to P, persistent oscillations will be generated. The residue of the stream is collected at K₁, any undesirable secondary emission being trapped between the vanes.

Marconi's Wireless Telegraph Co., Ltd. (assignees of I. Wolff). Convention date (U.S.A.) July 21st, 1939. No. 542182.

PRODUCING INTENSE ELECTRON BEAMS

IN certain discharge devices such as the klystron tube for generating ultra-short waves, it is desirable to produce an electron stream of high density. Diffi-

RECENT INVENTIONS


A Selection of the More Interesting Radio Developments

culty arises in doing so because of the space-charge created by the electrons, which tends not only to disperse, but also to decelerate the individual electrons, and may actually arrest them, so that they form a virtual cathode at a point along the path of the stream.

To overcome this tendency, a beam of positive ions is formed at the far end of the pipe and is directed against the stream of electrons towards the cathode. The positive ions are preferably liberated from a heated layer of some barium compound which is surrounded by a focusing "gun." Barium is preferred, if a barium-heated cathode is used, because the barium ions help to replenish wastage from the cathode. Also, any barium ions

Electrode arrangement of velocity modulator-generator.

The figure shows a method of mounting such a coil and of tuning it by varying the spacing between each of the turns uniformly. One end of the coil L is fixed to a pillar P, and the other end is soldered to the upper surface of a blade spring S. The under surface of the same end of the spring is fitted with a cup-shaped member M which bears against the end of a tuning screw A. The inside surface of the cup is preferably fitted

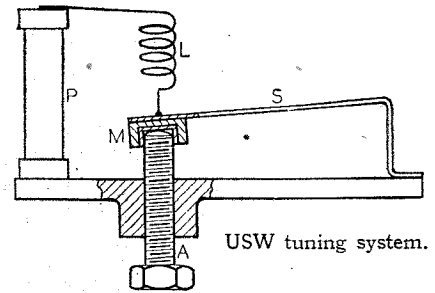

USW tuning system.

with an insulation to avoid the injection of "noise" owing to possible bad contact between the rotating end of the screw and the blade, the latter being electrically connected to the baseplate.

The Mullard Radio Valve Co., Ltd., and C. C. Eaglesfield. Application date August 14th, 1940. No. 542395.

DC VOLTAGE-CONVERTERS

RELATES to circuits for deriving a high-tension voltage from an accumulator or other LT source by using a make-and-break contact to feed a step-up transformer, and rectifying the output from the latter.

In the present arrangement the positive terminal of the accumulator is tapped to the centre of the primary winding of the transformer, and the two outer ends of the same winding are alternately connected to the negative terminal through a trembler switch. A double-diode rectifier is shunted across the secondary of the transformer, and the two opposite ends of this winding are alternately connected to the common cathode of the rectifier through contacts which are operated synchronously with the trembler switch.


The whole of the secondary coil is thus coupled to the rectifier load during each half-cycle, so that a much smaller coil can be used, as compared with known arrangements in which a centre-tapped secondary is employed for full-wave rectification.

Philco Radio and Television Corp'n. (assignees of J. H. Pressley). Convention date (U.S.A.) September 8th, 1939. No. 543032.

HIGH-FREQUENCY TUNING

FOR very short wavelengths there are certain advantages to be gained by using a tuning coil in which the whole of the wire is constantly kept in circuit, and the effective inductance is varied by changing the spacing between the turns. This is particularly so when it is essential to maintain a uniform bandwidth.

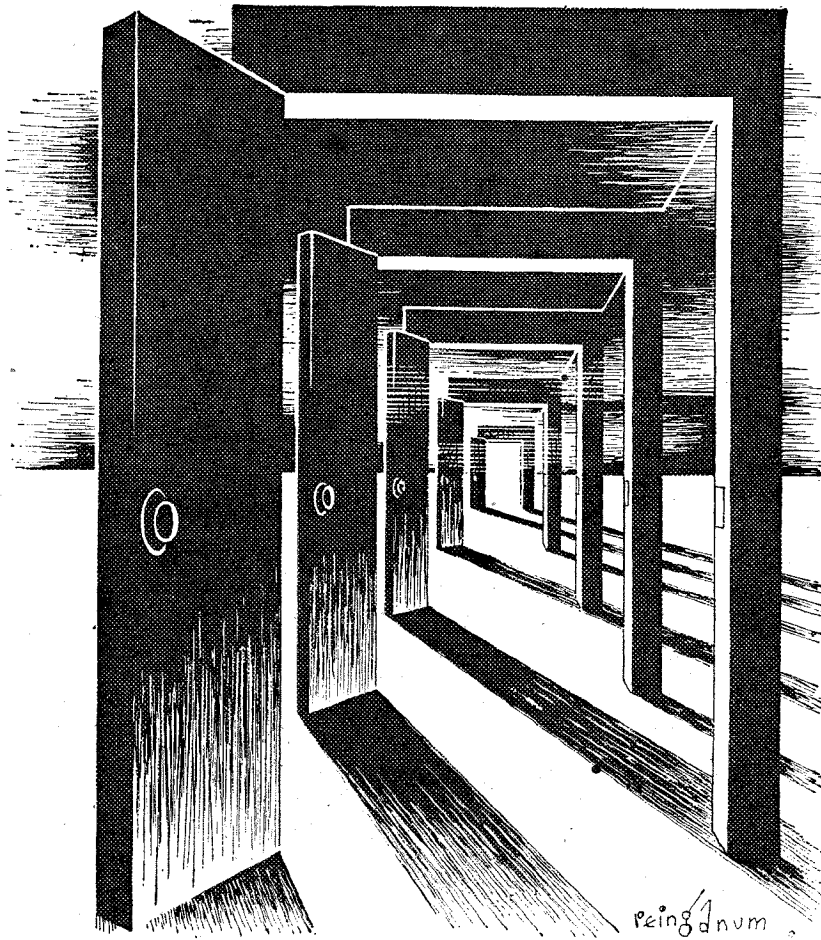The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.



SCOPE . . .

“One could extend almost indefinitely a list of the manifold activities to which Philips products and processes have contributed . . . an ever-widening field of electrical pioneering and achievement.”

PHILIPS



LAMPS · DISCHARGE LIGHTING · RADIO RECEIVERS · TRANSMITTERS · VALVES & THERMIONIC DEVICES · MEDICAL & INDUSTRIAL X-RAY & ELECTRO-MEDICAL EQUIPMENT · ARC WELDING EQUIPMENT & ELECTRODES · LIGHT ALLOY RESISTANCE WELDING PLANT · MAGNETIC OIL FILTERS · MAGNETS · SOUND AMPLIFYING INSTALLATIONS

— VALVES —

AMERICAN AND INTERNATIONAL OCTAL. Mostly glass types, 1A4, 12/6; 1A6, 14/-; 1J5, 15/-; 1C5, 16/-; 1G5, 15/-; 2A6, 14/-; 2A7, 15/-; 2B7, 15/-; 5Y3, 14/-; 1V, 12/-; 6A6, 14/-; 6A8, 14/-; 6AG5, 11/6; 6AC5, 11/6; 6B7, 14/-; 6B8, 16/-; 6C6, 14/-; 6D6, 14/-; 6D7, 15/-; 6F7, 17/-; 6J5, 13/-; 6K7, 13/-; 6K8, 14/-; 6L7, 13/-; 6O7, 13/-; 6S7, 14/-; 6U5, 11/-; 6U7, 13/-; 6V6, 13/-; 6X5, 15/-; 6Z5, 18/-; 7V5, 16/-; 12B8, 15/-; 15, 18/-; 19, 18/-; 24A, 13/-; 26, 11/-; 27, 9/-; 31, 12/-; 32, 15/-; 33, 14/-; 34, 15/-; 35, 13/-; 36, 14/-; 37, 11/-; 38, 12/6; 39/44, 12/6; 46, 15/-; 50, 25/-; 53, 16/-; 52, 22/-; 55, 13/-; 57, 14/-; 58, 14/-; 59, 16/-; 71A, 11/-; 76, 10/-; 77, 15/-; 78, 14/-; 79, 15/-; 80, 14/6; 81/6Z4, 14/6; 85, 12/-; 2101, 15/-; 2103, 15/-.

RECTIFIERS. Non-B.V.A. Replacement Types, all 14/6 each. Replacements for American 80, 5Y3, 5Z4; Marconi Osram, U50, U10, U12, MU12; Mullard, 1W2, 1W3, 1W4, DW2, DW3; Cossor, 422BU, 506BU; Brimar, R1, R2, R3; Philips, 1821, etc., etc.

MAZDA OCTALS. Mullard E. Types, English B.V.A. Types, most numbers in stock.

SERVICE MEN. We make special arrangements for your valve problems. The fact that you do not see the valve you want listed here does not mean we have not got it. We may be able to get it or suggest a suitable alternative.

— SPARES —

VOLUME CONTROLS, with switch, 4/9 each. The following values only in stock: 10,000, 25,000, 50,000, 100,000 ohms; 1 meg., 1 meg., 2 meg. **GLAROSTAT WIREWOUND POTENTIOMETERS,** 200, 500, 600, 1,000, 2,000 and 5,000 ohms, at 5/9 each; 20,000 ohms at 6/11 each; 40,000 and 50,000 ohms at 8/- each; and 100,000 ohms at 9/9 each.

ADJUSTABLE RESISTORS can be used to replace any .2 or .3 amp. Barretter, 7/- each.

SCREENED MIKE CABLE, twin, 1/9 yd. **LINE CORD,** Standard, 110/230, 6/6. **Uncut,** 3 core, 60 ohms, per foot, 4/- a yard; 100 ohms, per foot, 5/- a yard.

BUZZERS, small type, high note; ideal for Morse, 3/9 each. **MAINS TRANSFORMERS.** Fully shrouded, 350-0-35, 120 m.a., 6.3 v. 3 amp., 5 v. 2 amp., for 200/250 mains, 22/6.

CONDENSERS, 8 mfd. electrolytics, 500 v., 4/9; 8x8, ditto, 9/3; paper, 500 v., 5, 1/6; 25, 1/3; .1, 10d.; .06, 9d.; .04, 8d.; .01, 8d.; .005, .003, .002, .001, all 6d.

RESISTORS, 10 watt up to 2,000, 2/6 each. **VOLTAGE DROPPERS,** for most sets, from 4/6 each. **C.I. and C.I.C.** replacements resistors, 6/- each.


CONNECTING WIRE, 2/- 4-lb. reel; sleeving suitable for above, 4d. yd. **SOLDER,** resin cored, 5/6 lb., or 1/- coil.

PUSH BACK, 6d. and 1/- per coil. **VALVE HOLDERS,** English, 5- and 7-pin, 8d.; American, 4-, 5-, 6- and 7-pin, Mazda and ordinary octals, 1/- each.

ROLA P.M. SPEAKERS, 4in., 17/6; 6in., 21/-.

Terms: Cash with order or C.O.D. Postage, etc., extra on orders under £3. Callers and phone orders are not welcomed. Please post your order.

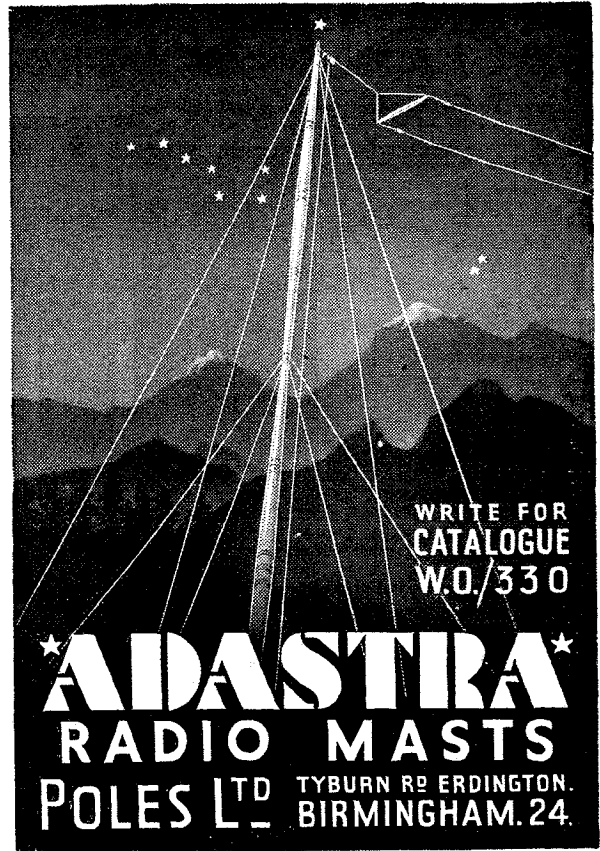J. BULL & SONS, Radio House, Melthorne Drive, Ruislip, Middx.



WRITE FOR CATALOGUE W.O./330

★ ADASTRA ★
RADIO MASTS
POLES LTD TYBURN RD ERDINGTON. BIRMINGHAM. 24.

Enquiries should be accompanied by Government Priority Reference



HIVAC
 THE SCIENTIFIC VALVE
 BRITISH MADE

Specialists in
MIDGET VALVES

HIVAC LIMITED
 Greenhill Crescent,
 Harrow on the Hill, Middx.
 Telephone: Harrow 0895.



THE POWER BEHIND-
MASTERADIO
VIBRATOR PACKS

The Perfect Portable Power Supply in service under arduous conditions in Transmitters, Receivers, Amplifiers, etc.

Masteradio LTD *GRAMS: MASTIOLA *PHONE: WATFORD 9885/9889
VIBRANT WORKS, WATFORD, HERTS.

CLASSIFIED ADVERTISEMENTS. The charge is 6/- for each paragraph of 2 lines or less, and 3/- for every additional line or part thereof, average 7 words to a line. Each paragraph is charged separately.

ADVERTISEMENTS for the September issue are accepted up to First Post on Monday, August 10th, at the Head Offices of Dorset House, Stamford Street, London, S.E.1, or one day earlier at provincial Offices.

THE PROPRIETORS retain the right to refuse or withdraw advertisements at their discretion. They are not responsible for clerical or printers' errors although every care is taken to avoid mistakes. Cheques and postal orders should be made payable to Iliffe & Sons Ltd. and crossed. Notes are legal tender and cannot be traced if lost in transit.

ADVERTISERS may have letters, other than circulars, addressed to numbers at this office. The words Box 000, c/o "WIRELESS WORLD" must be paid for and a further 1/- added for registration and forwarding replies.

DEPOSIT SYSTEM. Full particulars upon application to the Deposit Dept., "Wireless World," Dorset House, Stamford Street, London, S.E.1.

Ode Partridge

No. 18

STOP-GAP

New readers of the "Wireless World" May wonder at our firm Devoting space to poetry (If you'll excuse the term).

In normal times, being normal folk, We simply loved to sell Our Chokes & Mains Transformers, which Old readers know so well.

But now, alas! the times have changed. Our goods are good goods still, And we're making them in thousands, But not for Tom and Bill.

It's no use, therefore, telling you Of "Model No. 9," If we cannot let you have it Or any other line.

So that's why we break into verse On topics somewhat mixed, But it serves as a reminder 'Till Hitler's gang is fixed.

N. Partridge

Makers of Transformers and Chokes
King's Bldgs., Dean Stanley Street,
LONDON, S.W.1. Phone: VICToria 5035

ARMSTRONG

A very limited supply of

EXP48 COIL PACKS

covering 4-wavebands, have now become available and orders will be executed in rotation whilst our stock lasts

Originally designed for use with our export chassis, Model EXP48, which was so favourably reviewed in the October, 1940, issue of *Wireless World*. The Test Report said: "No difficulty was experienced in picking up American stations." This assembly is ideal for constructing a modern receiver using English or Octal valves, or tuning unit to work with an amplifier. The short-wave performance with the EXP48 coils is extremely high. Specification. EXP48 coil and switch assembly covering 13-45, 43-160, 200-550, 1,000-2,000 m. Mounted on cadmium plated sub-chassis with 4 position Yaxley type rotary switch. Medium and long wave adjustable paddlers and fixed paddlers on the short-wave ranges. Each coil fitted with individual trimmer and the whole assembly wired up. Factory Blue Print giving 7-valve EXP48 circuit and values of components FREE with assembly. Price 35/-. Heavy Steel Chassis for use with above, 12in. x 9in. x 3 1/2in. deep, drilled and cadmium plated. Price 10/6. 465 kc. High "Q" I.F. Transformers. Leitz wire wound and fitted with iron cores, in aluminium cans, incorporating trimmers with ceramic insulation. For use with the above. Price 18/6 per pair. Glass Scales. 4 wavebands, calibrated in station names and metres. For use with the above. Price 3/6. A complete chassis, incorporating the above components, will be gladly demonstrated at our Showrooms and any technical advice given.

Deliveries should not exceed 14 to 21 days.

All components advertised in June issue are still available.

★
ARMSTRONG MANUFACTURING CO.
WALTERS ROAD, HOLLOWAY, LONDON, N.7
Phone: NORTH 3213

Advertisers and buyers are reminded that under Defence Regulations 1939, Statutory Rules and Orders 1940, Number 1689, a permit (T 99 G) must be obtained before sale or purchase of certain electrical and wireless apparatus, particularly such valves and apparatus as are applicable to wireless transmission.

RECEIVERS & AMPLIFIERS—SECONDHAND, ETC.

QUALITY Receiver and Amp. 10 valves, including PX25s in P.P.—Humpidge, Borth, Cards. [1159]

SUPER Skyrider S.X.17, perfect; seen by appointment.—Box 2710, c/o *The Wireless World*. [1154]

HAMRAD 13v Communication Receiver, less valves (obtainable octals); £13.—Flude, Wychwood, Park Lane, Slough. [1150]

DX. Plus Feeder Unit (16-2,000 metres), in cabinet with transformer, to feed W.W. p.p. amplifier; £6, as new.—Box 2708, c/o *Wireless World*. [1147]

5-VALVE Ship's Receiver (batt.), T.R.F., 100-200 and 550-3,000 metres by switching, heavy aluminium construction; £12.—Holmes, 795, Borough Rd., Birkenhead. [1156]

R.M.E.69 D.B.20, R.M.E. speaker, painted grey, £56; receiver and speaker only, £43/10; 6 valves and Service Manual, £2/10; no offers or agents; carr. fwd.—Jones, Brixton Mount, Holyhead. [1145]

Wanted

MODERN Superhet Chassis with Valves, 3-wave band.—S. Harris, 37, Edgeworth Crescent, N.W.4. [1117]

MURPHY A76 or A92, working or otherwise, or unaltered chassis only.—Jones, Brixton Mount, Holyhead. [1146]

BY Ham in, and for use of, Forces' Unit; Halli-crafter S.X.17 and speaker.—Box 2705, c/o *Wireless World*. [1142]

WE Offer Cash for Good Modern Communication and All-wave Receivers.—A.C.S. Radio, 44, Widmore Rd., Bromley. [9948]

HIGH-CLASS Communication Receiver: full price paid for suitable model.—G. W., 14, Beaufort Gardens, London, S.W.3. [1151]

NEW or Used Receivers, Amplifiers, Meters, Converters, Radio and Electrical Accessories. Very high prices paid for really clean apparatus.—Phone: Gerrard 4447. [9696]

NATIONAL 1-10 Urgently Wanted in Connection with Important Experimental Work; a very good price will be paid.—Write the Bolton Engineering Co., 106, Queen's Head Rd., Birmingham, 21. Phone: Northern Birmingham 1221. [1148]

LONDON CENTRAL RADIO STORES Will Pay good prices for Receivers, Radiograms, Amplifiers, Dynamos, Converters, Test Equipment, Electric Gramophone Motors, and all Radio and Electrical Accessories.—London Central Radio Stores, 23, Lisle St., London, W.C.2. Gerrard 2969. [9836]

NEW MAINS EQUIPMENT

VORTEXION Mains Transformers, chokes, etc., are supplied to G.P.O., B.B.C., L.P.T.B.; why not you? Imitated but unequalled. Orders can only be accepted against Government contracts.

VORTEXION, Ltd., 257, The Broadway, Wimbledon, London, S.W.19. Phone: Lib. 2814. [9942]

MORSE EQUIPMENT

FULL Range of Transmitting Keys, practice sets and equipment for Morse training.—Webb's Radio, 14, Soho St., London, W.1. Phone: Gerrard 2089. [9553]

TEST EQUIPMENT

PHILCO Mains Oscil., £8; E.M.I. batt. do., £6/10; sundry Ferranti meters; s.a.e. list.—Petty, Bentham, Lancaster. [1157]

TEST Equipment Kits, cabinets and accessories; for new lists please send s.a.e., stating requirements.—MacLachlan and Co., Strathyre. [1153]

TESTOSCOPE, used everywhere by radio service engineers, makes 20 important tests. Send for interesting leaflet "R.I."—Rumbaken, Manchester, 1. [1074]

Wanted

RIDER "Chanalyst," signal tracers, oscillators; in state condition and price.—Box 2706, c/o *Wireless World*. [1143]

WANTED, Audio oscillator, generating accurate wave shape.—State particulars and price to Box 2700, c/o *Wireless World*. [1129]

Reaching for the Stars

We have often been told that our constant striving for perfection is like "reaching for the stars." Naturally, we smile but we go on striving, for just as we know that we shall never reach perfection the effort involved keeps us a few jumps ahead and helps us give you a product just that much better. So when you are required to supply Small Power Transformers up to 4 kva and the specification seems to demand perfection remember that GARDNERS have long experience in "reaching for the stars." Please don't forget to quote priority numbers.



GARDNERS RADIO LIMITED
SOMERFORD • CHRISTCHURCH • HANTS

A few only!!

7-VALVE CHASSIS complete with valves and 10" SPEAKERS

KNOB AND FIXING ACCESSORIES INCLUDED

Specification:

3 wave bands Super-Het. (long, medium and short). Full A.V.C. Split phase. Push-pull output. Radiogram connections. Superb tone. 8 watts output approx. Excellent range. Large full-scale illuminated dial 8" x 5". Stations named.

Price £20 each
including Purchase Tax

MARTINS RADIO

3/4 The Broadway, Edmonton, London, N.9
Phone: Tottenham 4188.

Look to your future...

Trained men get good jobs. Hundreds of our students write to thank us for their successes and increased earnings. Now, more than ever before, men with a good knowledge of radio or mathematics are urgently needed. Even if you are already in the Forces, or engaged on work of National importance, you should think of your future. A sound technical training is the best insurance against the risks of unemployment. Our simplified method of Home-Studying is a proved success. Even if you know nothing about radio or mathematics, you can master these subjects, and you will really enjoy studying. Post coupon now for free details of our Home-Study Courses in Mathematics, Radio Calculations, Radio Reception, Servicing, Transmission, Radiolocation and Television.


T. & C. RADIO COLLEGE 29, Market Place, READING

(Post in unsealed envelope, 1d. stamp.)
Please send me free details of your Home-Study Courses.

NAME.....
ADDRESS.....
W.V.S.....

CODE COURSES

For Beginners and Operators

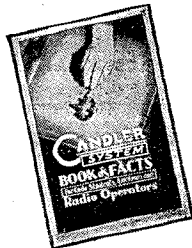

The Candler System of Code training is just what one needs for entering or advancing in Army, Navy, Air Force, Amateur Radio work, or the Commercial side of telegraphy.

JUNIOR AND ADVANCED COURSES

on Cash or Monthly Payment terms.

There's no royal road to learning—but there IS a quick, sure way to genuine CODE skill. Thousands upon thousands of Candler Trained Operators have proved the value of this truly remarkable system of Morse Code instruction.

J. Clarricoats, Sec., Radio Society of Great Britain—says: "I regard the Candler System as being the most important system of its kind and already large numbers of Members of the Radio Society of Great Britain have intimated to me that they are studying the course of instruction with a view to preparing themselves for service in one branch or another of H.M. Forces."

In the "BOOK OF FACTS," which will be sent FREE on request, you will see that full information is given concerning the subjects covered by Morse Code Courses for beginners and also for operators.

COUPON

Please send me a Free Copy of Candler "Book of Facts."

NAME.....
ADDRESS.....

Post Coupon in 1d. unsealed envelope to London Manager
CANDLER SYSTEM CO. (Room 55W), 121, Kingsway, London, W.C.2

Candler System Co., Denver, Colorado, U.S.A. 842

MARCONI-LEKCO, General Radio, or similar Signal Generator; also Coil Winding Machine, power driven.—Full particulars, price to Box 2694, c/o *Wireless World*. [1118]

NEW LOUDSPEAKERS

NEW Rola P.M. Speakers, 50 only, 10in., 19/- each; 100 only, 8in., 18/- each; 100 only, 5in., 12/6 each; postage and packing extra; all orders c.o.d.—Box 2701, c/o *Wireless World*. [1135]

BAKERS SELHURST RADIO, the pioneer manufacturers of moving coil speakers since 1925.—Bakers' brand new surplus speaker bargains; every music lover interested in realistic reproduction should write for free descriptive leaflet now; £3/10, brand new super quality triple cone speaker, permanent magnet model; limited number available under list price, wide frequency range, even response, ideal for quality reproduction; leaflet giving constructional details of an infinite baffle cabinet suitable for use with the above speaker free upon receipt of stamp.—Bakers Selhurst Radio, 75, Sussex Rd., South Croydon. [1138]

SECOND-HAND LOUDSPEAKERS

WANTED, Rola G.12, preferably permanent magnet (energised considered), for experimental purposes.—F/Lt. Lynas, Officers' Mess, R.A.F. Station, Cardington, Bedford. [1152]

Wanted

VOIGT Corner Horn, complete or separately.—Box 2709, c/o *Wireless World*. [1151]

WANTED, quality speaker. Sell S.S. 036 trans., 2 P x 4's.—Box 2698, c/o *Wireless World*. [1126]

VOIGT Speaker Unit, Hartley Turner, Goodmans, infinite baffle.—Box 2702, c/o *Wireless World*. [1136]

DYNAMOS, MOTORS, ETC

WANTED, Small High Frequency Alternator.—Details to Box 2697, c/o *Wireless World*. [1123]

ROTARY Converters by E.D.C., Crypto. G.E.C. etc., all voltages, 30 to 5,000 watts; immediate delivery.—Below.

MOTORS and Dynamos, transformers, resistances, starters and switches for radio and power; many unusual types available.—Below.

LIGHTING Sets and Batteries by Crossley, Pelapone, Lister, etc.; automatic sets by Kohler, Petter, all voltages to 5kW; switchboards and meters, hundreds in stock.—Harris, Strouds, Bradford, Berks. [1149]

ALL Types of Rotary Converters, electric motors, battery chargers, petrol-electric generator sets, etc., in stock, new and second-hand.

WARD, 37, White Post Lane, Hackney Wick, E.9. Tel: Amherst 1393. [0518]

L.T. Dynamos for Charging or Windmill, Lucas-Rotax, 6-12 volts 8 amps. D.C., 3rd brush, weight 11lb., size 8in. x 4 1/2in., unused ex W.D., cost £10, to clear 17/- each, carr. paid; H.P. and L.I. G.E.C. double-end 6 volts and 600 volts, 17lb. ditto, 27/6 carr. paid.—Electradix, 19, Broughton St., London, S.W.8. [9993]

Wanted

CONVERTER, high grade, 200 D.C. to 230 A.C., for television gram. radio.—Robinson, High St., Sonning. [1127]

CABINETS

WE Regret That, owing to all our employees having joined H.M. Forces, we are unable to accept orders for cabinets except to callers. Limited stock only. We have a large stock of radio components.—H. L. Smith and Co., Ltd., 289, Edgware Rd., London, W.2. Tel.: Pad. 5891. [9683]

NEW COMPONENTS

SERVICE Supplies—Condensers, paper, mica, bias, tubular, electrolytic types; Transformers, rectifiers, volume controls, resistors, etc. S.A.E. for lists. Rola 8in. P.M. speakers, 17/6; elect. condrs., 500v., 8 mfd. 4/3, 8 x 8 mfd. 8/6; Push-back wire, 12yd. coils, 1/9; sleeving, 2/6 doz. yds. Gramo. motors, pick-ups, 35/-; valves, etc. (Staff shortage! Mail orders only; postage extra. C.o.d. service available.)—Radio Instrument Service Co., 116, Littleheath Rd., Bexleyheath. [1132]

COMPONENTS—SECONDHAND, SURPLUS, ETC. SOUTHERN RADIO'S Wireless Bargains.


7/6—Assorted components contained in attractive permanent box, 2 volume controls, 9 assorted valve holders, 12 assorted condensers, 6 resistances, choke, wire, plugs, circuits, 7/6, postage 7d.; Ormond loudspeaker units, balanced armature, 4-pole, 6/6; small unshrouded type, 3/-; Ace P.O. microphones, complete with transformer, 6/6; Telsen No. 6 Radio Magazines, complete with 4 circuits, 9d., post free; wireless crystals, 5d. each, 5/6 dozen; Telsen binocular H.F. chokes, 1/6; 75ft. covered wire, suitable for aerials, etc., 2/6.

1/6—Magnets, very powerful, small circular magnets, 1 1/2in. diameter, 3/4in. thick, 1/6 each, 15/- dozen; many more bargains for callers. Please add extra for postage.

SOUTHERN RADIO SUPPLY Co., 46, Lisle St., London, W.C.1. Gerrard 6653. [1102]

COULPHONE Radio, New Longton, nr. Preston.—Brand new goods only; P.M. speakers with transformer, 8in. Rola and Plessey, 24/6; 6 1/2in. Celestion, 21/-; Barretter Resistors, 6/-; electrolytics, 500v., 8mfd. 5/6, 8+8mfd. 9/6, 50mfd. 50-volt 3/3; Erie 1-watt resistors, all values, 9d. each; pushback wire, 100ft. coil, 6/-; S.A.E. for stock list. [1133]

L-R-S has in stock a small number of

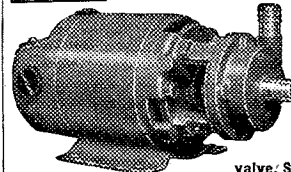

STUART No. 10 Centrifugal PUMPS

Complete with Foot-valve, Strainer & Hose Union.
Capacity 100 gals. per hour. Carr. 2/- extra ... £5 2 6
Suitable for Machine Tool Cooling and all pumping purposes, for hot or cold water.

Please enquire regarding delivery of:
No. 11, 280 gals. per hour. Carr. 2/- extra ... £6 6 0
No. 12, 560 gals. per hour. Carr. 3/- extra ... £7 12 0
Suitable Rubber Hose available from stock.

The STUART AUTOMATIC FLOAT SWITCH is the best method of controlling water-level. Price complete with all fittings... £2 5 0

LONDON RADIO SUPPLY CO.

Est. 1925

"WINDEN," ARDINGLY RD., BALCOMBE, SUSSEX.

ENGINEERING OPPORTUNITIES

This unique Handbook shows the easy way to secure
A. M. I. C. E.,
A. M. I. Mech. E.,
A. M. I. E. E., A. M. I. E. S.,
A. M. Brit. I. R. E. and similar qualifications. **WE GUARANTEE—"NO PASS—NO FEE."** Details are given of over 150 Diploma Courses in all branches of Civil, Mech., Elec., Motor, Tracing, Inspection, Government Employment, BUILDING (great scope), MATRIC., R.A.F. MATHS., etc. Book and subsequent matter sent (post free) on receipt of 2d. stamps. Men with Radio knowledge can obtain attractive posts in the Services.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, 387, Shakespeare House, 17, 18, 19, Stratford Place, London, W.1

Book sent post free



W. BRYAN SAVAGE LTD.

Expert assistance in the solution of problems relating to

- TRANSFORMERS, CHOKES
 - AMPLIFIERS
 - POWER UNITS
- and Specialised Equipment embodying
ELECTRONIC CONTROL

WESTMORELAND RD., N.W.9.
COLINDALE 7131


WARD ROTARY CONVERTERS

Petrol Electric Generating Plants, H.T. Generators, D.C. Motors, Frequency Changers, etc., up to 25 K.V.A.

CHAS. F. WARD 37 WHITE POST LANE,
HACKNEY WICK, E.9.
Phone: Amherst 1393.

TRIX SOUND EQUIPMENT

RELIABLE AMPLIFICATION
The TRIX ELECTRICAL COMPANY LTD.
65, Bolsover St., London, W.1. Euston 5471



E.H. WILSON
for
QUALITY COMPONENTS & ACCESSORIES

SLOW-MOTION DRIVE, 2-speed, 4-waveband (3 short and medium). Complete with dial and 5in. square chromium-plated escutcheon. Price **5/11**.

VARIABLE CONDENSERS, 2-gang, 0.0005 mfd., first-class precision job, ceramic insulation, with special slow-motion drive, no backlash or slip, mounted on metal frame, rubber sprung (no trimmers), new, boxed, **7/6**; 3-gang, 0.0005 mfd. standard type, **4/6**.

MAINS TRANSFORMERS, 350-0-350v. 80-100 m.a., 4v. 4a., 4v. 2a., screened primary, input 200-250v. A.C., **2/1**; 350-0-350v. 80-100 m.a., 6.3v. 4a., 5v. 2a., screened primary, input 200-250v. A.C., **2/1**; Philips 300-0-300v. 80 m.a. 6.3v. 3a., 4v. 1a., input 110-240v. A.C., **17/6**.

TRANSFORMERS, L.F., intervalve, various makes and ratios, **5/-**; I.F. transformers, 465kc., unscreened and without trimmers, new, **3/6**; Philips 160kc. intermediate frequency transformers, air-space trimmers, **1/6**.

SCREENED COILS, Medium and Short-Wave Band (12-17 metres), **2/6**; Long and Short-Wave Band (10-50 metres), **2/6**. Both types fitted with two ceramic trimmers. Circuit free.

SHORT AND MEDIUM-WAVE BAND COIL, in aluminium can, with small ceramic trimmer, new, **2/6**; Philips dual range aerial coils (no reaction), with air-space trimmers, circuit, **1/6**.

DUAL RANGE COILS, Aerial or H.F. (small, unscreened), with circuit, **3/6** each.

BANDPASS COILS, **1/3** each.

MAINS H.F. CHOKES, for interference suppression, **2/6**; L.F. chokes, 20hy. 100 m.a., **15/-**.

SHORT-WAVE CHOKE, 2/-; short-wave double-wound filament choke, **1/-**.

TAPPED MAINS DROPPING RESISTANCES, approx. 800 ohms, standard for Pye, Lissen, etc., 2 amp., **3/6**; Replacement for line cord resistances, 950 ohm, **6/-**; 750 ohm, **4/6**; 360 ohm, **4/3**; 801 Ferguson, 4 amp., **6/6**; 802 Ferguson, 4 amp., **6/6**; Vidor, 3 amp., **4/6**; Ferranti, 3 amp., **4/6**; Belmont, 3 amp., **4/6**.

RESISTORS, different values, 1/2-watt **3d.**, 1/3-watt **4d.**, 1-watt **6d.**, 1-watt **8d.**

B.I. TUBULAR CONDENSERS, N.I., 0.0001, 0.0002, 0.0003, 0.0005, 0.01, 0.05, **6d.**

T.C.C. TUBULAR CONDENSERS, 0.00015, 0.01, 0.05, **5d.**, 0.1, **7d.**, 0.25, 1/-, 0.5, **1/6**; I.C.C. tubular electrolytics, 25 mfd. 25v., **1/9**, 50 mfd. 25v., **2/-**, 25 mfd. 50v., **2/-**, 50 mfd. 12v., **2/-**.

MICA CONDENSERS, 30 m.mfd. and 0.0005 and 0.0001, wire ended, **8d.**; assorted mica condensers, 0.0001 to 0.01, tag or terminal type, **1/-**.

MANSBRIDGE TYPE PAPER CONDENSERS, 0.25 to 4 mfd., various makes, from **9d.** to **3/-**; Ceramic pre-set condensers, **6d.**

LOUD SPEAKERS, extension "Goodmans," no transformer, 8in., **17/6**; "Celestion" with transformer, 7in., **2/1**.

VALVE HOLDERS, English chassis type, 4-pin, **4d.**; 5-pin and 7-pin, **6d.**; English Octal, **6d.**; American U.S. type, 4-, 5-, 6-, and 7-pin, and International Octal, **6d.**

PAXOLIN PANELS, flat, strong, 9in. x 15in., **3/6**; A.E. or P.U. or L.S. Paxolin strips, complete with plugs, **8d.** each; Terminal strips and group boards, from **3d.** to **1/-**.

OCTAL CABLE PLUGS AND SOCKETS, **1/6** complete.

CELLULOID DIALS Only. "Selmer" calibrated 3-wave band, coloured, **3d.**; Slewing, red, black, yellow, blue, green, brown, good quality, **4 1/2d.** per yard length; Screened Cable, single, **1/6** per yard; twin, **1/9** per yard; Terminals, patent spring type for quick attachment of wire, **3d.**

BENJAMIN TRANSFEEDA, brand new, **8/6**; Toggle Switches, s.p.s.t., **1/6**; Dial Lamp Holders, clip-on type, **4d.**; Steel Chassis, used, drilled, strong, **1/3**.

HOURS: 9-6 p.m., Saturdays 1 p.m.; C.O.D. orders accepted; prices subject to alteration without notice; special terms to members of H.M. Forces and Civil Defence workers; licence to export to Northern Ireland and Irish Free State; please add postage for enquiries and mail orders.

51-52 CHANCERY LANE.
LONDON. W.C.2. Telephone **HOLBORN 4631.**

G. A. RYALL, "Arnehurst," Marsh Lane, Taplow, Bucks (late Ryall's Radio, London); offers radio components; post free.

T.C.C. 0.1 Tubular Non-inductive Condensers, 350v. wkg., in Paxolin tubes and waxed, 6/6 dozen.

WEARITE Tuning Coils, in cans, oddments only, aerial, B.P., etc., no sets, 3 for 1/3.

RESISTANCES, well known make, 1/4-watt, 1 meg., 1/3 dozen, 10/- gross. Insulating tape, 2oz. reels, 1/3 lb.

VOLUME Controls: British make 1 meg at 1/6 each; 50,000 2/3 ea., less switches.

G.E.C. "Tuneon" Tuning Indicators, as used in the "AVO Five" neon type, 1/3 each; slow motion (epicyclic) drives, fit 1/4in. shafts, long 1/4in. spindles, well made in brass, with ball bearings, ratio 8-1, 1/3 each.

PAXOLIN Strip, 2 1/2in. wide, as used for group boards, etc., three 12in. lengths for 1/6; group boards, with tags, 12-way, two for 1/3; or drilled, less tags, four for 1/3.

ERIE Resistors, 1/2-watt type, actual values, as used in many well known sets, 220, 680, 3,300, 27,000, 33,000, 1 1/2 meg., 3/- dozen, new goods; Erie resistors, 2-watt type, 150, 560, 800, 3,000, 3,900, 7,500, 8,200, 68,000, 120,000, three for 1/6, new goods; Erie resistors, 3-watt, 680, 1,500, 2,200, 3,300, 4,700, 8,800, two for 1/6, new goods.

CLIX Input Strips, A. and E. P.U., loudspeaker, etc., 2-, 3-, 4-way, 2/3 dozen; Ferranti wire wound resistors, nickel end caps, 4,000, 4 for 1/3.

DOUBLE Trimmers, on Paxolin, ex G.E.C., not joined, 2/6 dozen; single ditto, 1/6 dozen; ditto, not mounted, 1/2 dozen.

VALVES—Europa AC/L 4v. 1 amp., makes good detector or L.F. amplifier, 3/3 each; Europa AC/HP, 5-pin base, 3/3 each (metallising of the AC/HP may be rather soiled, but all O.K.).

WAVE traps, ex K.B., iron core, 1/3; switches for band pass H.F. and dial lights, Wearite type, 1/3.

PLESSEY, 3 gang, screened, with one trimmer only, 3/- straight, no superhet types; condenser drives, with 2-band scale, less escutch., similar Polar VP, 1/9.

INVERTED Type Large Capacity Mansbridge Low Volt for cathode by-pass, pair in one block, 1/6.

CONE Units, large circular magnets, bobbins mostly O.K., rather soiled, no reeds; 2 for 1/6.

TURNTABLES, as used for rotating portables, ball bearing; 1/6 each, soiled.

CERAMIC Type 3-gang Straight Type Condensers, with slow-motion drive, offset, ex Cossor, soiled but useable; 3/9 each.

PLUG and Sockets, 5-pin Paxolin metal shell-holder, 2 1/3. Thimble top caps, "Ali," 24 for 1/3.

SPEAKER "Pots", windings O.K., with face plate, etc., for use as L.F. smoothing chokes, resistances 750ohms, 1,400ohms, 2,000ohms, 7,500ohms, carry 60ma. to 100ma.; 3/9 each.

YAXLEY Switch Screens, 3 1/2 x 3 1/2, with fixing flange, 4 for 1/3. Paxolin sheet, 1/8, 3/16in. thick, 14.16.18in. x 7, 2/9 each, polished and matt, slightly soiled; nearest available to requirements sent.

CONE Units, small type, with long reed, soiled, quite useable, 1/6 each.

DIAL Plates, 3-band, size approx. 6 x 5, scale 4 x 2 1/2, white ground, 2 1/3; Burgoyne dial plate, 3 band, brown ground, 6 x 4, scale 3 x 2, station list printed on, 2 1/3. Dial plate ex Berners, 4-band, in green, red, blue, orange, transparent, brass stiffened edges, 1/6 each, dial and scale, 6 1/2 x 4.

SPECIAL Note—We now confine our business to: Mail Order; prompt attention, in rotation—G. A. Ryall, "Arnehurst," Marsh Lane, Taplow, Bucks. [1140]

RECTIFIERS—L.T. metal rectifiers, 12v 1 amp. with instructions, 7/2, post 4d.; instrument type rectifiers, bridge type for meters, bakelite, 11/6, post 3d.; home chargers, Atlas, 2v, 4v, 6v, 1/2 amp, 35/-; Varley, 2v., 1/2 amp, 21/-, post 7d.; transformer and rectifier for 2v 0.75 amp charger, 14/6, post 7d.; transformer, rectifier and ballast bulb for 2v, 4v, 6v, 1 amp, 25/9, post 8d.; microphones, miniature crystal mike for deaf aids, fitted flexible cord, 42/6; aerodynamic shape crystal mikes for stand mounting, 52/6; Rothenel crystal pick-up, 35/6.—Champion, 42, Howitt Rd., London, N.W.3. [1155]

WE Buy New or Used Radios, amplifiers, meters, converters, radio and electrical accessories, etc.—Phone: Ger. 4447. [9603]

WANTED, Postlethwaite scratch filter for Piezo pick-up; state price.—S. Allen, Rectory Cott., Sulhamstead, Reading. [1160]

WANTED, 18 S.W.G. Enamelled.—Sample, price, quantity available to Bain, 15, Dragon Rd., London, S.E.15. [1124]

URGENTLY Required for a Government Contract of highest priority, only good condition National Tuning Dials, type P.W.O.; current list prices will be paid.—Box 2695, c/o *Wireless World*. [1119]

GRAMOPHONE EQUIPMENT
RECORDING Blanks—Small quantity of acetate recording blanks for sale, standard sizes. Advertisers can also undertake re-coating of suitable blanks.—Write for details, box 2696, c/o *Wireless World*. [1122]

Wanted
AUTOMATIC Record Changer, up to £12.—Box 2704, c/o *Wireless World*. [1141]

GALPINS
ELECTRICAL STORES
21, WILLIAM ST., SLOUGH, BUCKS.
Phone: **SLOUGH 20855** TERMS: Cash with order

DYNAMO, 110 volts 60 amps, shunt wound, interpole ball bearing, speed 1,750 r.p.m., continuous rating. Price **£15**, carriage forward.

EX-G.P.O. MORSE INKER AND TAPE RECORDER, complete with actuating relay and tape reel, mounted on mahogany base, clockwork model, in good clean condition and perfect working order. Price **£12**, carriage paid.

SHEET EBONITE, size 12in. by 11in. by 1/32in., best quality. Price 4/- per doz., post free.

ELECTRIC LIGHT CHECK METERS, well-known makers, first-class condition, electrically guaranteed, for A.C. mains 200/250 volts 50 cy. 1 phase 5 amp. load, **10/-** each; 10 amp. load, **12/6**, carriage 1/-.

D.C. ELECTRIC LIGHT CHECK METERS, 200/250 volts 5 and 10 amps., in new condition and electrically perfect. **7/6**, post 1/-.

AUTO. CHARGING CUT-OUT AND VOLTAGE REGULATOR, ex-R.A.F., suit any dynamo up to 20 v. at 15 amps., fully adjustable, with wiring instructions, complete in metal case. **3/6**, post 9d.

AUTO TRANSFORMER, 1,500 watts, tappings 0-110-200-220 and 240 volts for step-up or step-down. Price **£5**, carriage paid.

LARGE TRANSFORMERS for rewinding, rating unknown, size 1 kW. auto. Price **17/6**, carriage paid.

LARGE TRANSFORMERS for rewinding, size 2 kW. auto., rating unknown. Price **30/-**, carriage forward.

HIGH FREQUENCY TRANSFORMERS, 75 v. A.C. input at 300 cycles; output 5,000-0-5,000 v. at 500 watts. Price **45/-**, carriage forward.

ROTARY CONVERTOR, D.C. to D.C.; input 220 volts D.C.; output 12 volts at 50 amps. D.C., ball bearing, condition as new. Price **£10**, carriage forward, or 17/6 passenger train.

DOUBLE OUTPUT GENERATOR, shunt wound ball bearing, maker "Crypto"; output 60 volts at 5 amps. and 10 volts at 50 amps., condition as new. Price **£10**, carriage forward, or 20/- passenger train.

ALTERNATOR, output 220 volts, 1 ph., 50 cycles at 180 watts, will give 1 amp. easily, speed 3,000 r.p.m.; self-exciting, condition as new. Price **£3**, carriage forward, or 15/- passenger train.

TRANSFORMER, input 230 volts, 50 cycles, 1 ph.; output 1,100-0-1,100 volts, at 220 milliamps. and 6 volts C.T. three times, earth screen, wound to B.S.R., weight 32 lbs. Price **£6**, carriage passenger train 7/6.

MOVING COIL METERS high grade, 2 1/2in. dia., panel mounting, reading 0-1 amp. or 0-1 1/2 amp., full scale deflection 15 milliamps. Price **25/-** either model, post free.

MOVING COIL METERS, high grade, 2 1/2in. dia., panel mounting, reading 0-8 volts, full scale deflection 5 milliamps. Price, either model, **32/6**, post free.

MOVING COIL METERS, high grade, 2in. dia., flush mounting, reading 0-50 milliamps, **50/-**, post free.

INSTRUMENT METAL RECTIFIERS, in good working order, 5 M/A output. **12/6** each, post free.

HEADPHONES, 120 ohm, complete with headband and cord, in perfect working order, highly suitable for H.G. or A.F.S. services. Price **6/-** per pair, post free.

110 V. D.C. KLAXON MOTORS, precision made, ball bearing, variable speed, approx. 1/10th h.p., laminated fields, as new. Price **20/-** each, post free.

20 V. D.C. MOTORS, compound wound, 1/20th h.p., speed 2,000 r.p.m., totally enclosed, ball bearing, rating 3 1/2 amps., a really high-class job in new condition, make good dynamo. Price **30/-**, carriage paid.

BRIDGE MEGGER, by Evershed Vignoles, 250 volt, 20 megohms. Price **£20**, carriage paid.

PORTABLE AMPMETER, reading 0-75 amps. calibrated at 50 cycle, mirror scale, as new. **£5**, carriage paid.

SPRAY GUN, maker B.E.N., high pressure, condition as new, complete with filter and high pressure hose. **£12**, carriage paid.



FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I. C. S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 38, International Buildings, Kingsway, London, W.C.2

Please explain fully about your instruction in the subject marked X.

Complete Radio Engineering
Radio Service Engineers

Elementary Radio Television

If you wish to pass a Radio examination, indicate it below.

Inst. of Wireless Technology


P.M.G. Certificate for Wireless Operators
Provisional Certificate in Radio Telephony and Telegraphy for Aircraft
City and Guilds Telecommunications

Name..... Age.....
Address.....

(Use penny stamp on unsealed envelope)

LONDEX BATTERY CUT-OUT

TYPE L/F/C

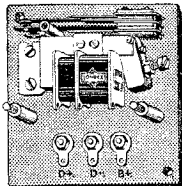

Simple, robust and sensitive. Works in any position. Suitable for ships, vehicles and stationary plants. Heavy silver-to-silver contacts. No mercury.

Ask for Leaflet 98/W.W.

LONDEX LTD
MANUFACTURERS OF RELAYS
ANERLEY 207 ANERLEY ROAD LONDON S E 20
PHONE: SYDENHAM 0226/9

"COSMOCORD" CRYSTAL PICK-UP



LICENSED BY BRUSH CRYSTAL CO., LTD. under Brit. Pat. Nos. 366,252 and 454,595

Retail Price
30/-
Plus Tax

Registered Wholesalers only supplied.

SOLE SELLING AGENTS:
SALE, TILNEY & Co., Ltd.,
3, LLOYD'S AVENUE, LONDON, E.C.3.
Phone: ROYAL 4811.

5 U4G or 5Z3 Rectifiers, automatic record changer.—Box 2703, c/o *Wireless World*. [1139]

WANTED, recording table, tracking gear and head, such as Presto 6-N.—State particulars and price to Box 2699, c/o *Wireless World*. [1128]

VALVES—Thousands in stock; send requirements, s.a.e.—Davies, 28, Mount Vernon Cres., Barnsley. [1073]

Wanted
WANTED, a 50L6GT valve.—Hunt, Chorley Wood Hotel, Herts. [1158]

VALVES Wanted, any quantity from one upwards; also test equipment, service sheets and spares.—J. Bull, 4, Melthorne Drive, Ruislip. [9732]

REPAIRS AND SERVICE
L.T.P. Repair All Mains Transformers and Chokes. Prompt delivery.

LONDON TRANSFORMER PRODUCTS, Ltd., Willesden, N.W.10. Wil. 6486 (3 lines). [9552]

MIDWEST, etc., we are the American experts.—Bennett's, 4, Humberstone Drive, Leicester. [1104]

METROPOLITAN RADIO SERVICE Co. Guarantee Repairs to American and British Receivers.—1,021, Finchley Rd., N.W.11. Spe. 3000. [9641]

TRANSFORMERS, pick-ups, motor rewinds, repairs of all descriptions to the wireless trade.—Marshall, 167, Windmill Lane, Nottingham. [1093]

ANY Type Auto. Record-changing and Elec. Gramo. Motor Repairs. Prompt service.—Barden, 241-3, Cambridge Heath Rd., E.2. Bishopsgate 1105. [1130]

ACCURATE Radio Rewinds, mains transformers. A. Fields O.P. transformers, etc., and all loudspeaker repairs, prompt service.—Southern Trade Services, 75a, George St., Croydon. [1039]

MAINS Transformers Service, repairs, rewinds, or construction to specification of any type, competitive prices and prompt service.—Sturdy Electric Co., Ltd., Dipton, Newcastle-upon-Tyne. [9651]

"SERVICE with a Smile."—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cords.—F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [8934]

SITUATIONS VACANT
LONDON Company, manufacturing valve deaf aids, requires young assistant to production manager, must be exempt military service and have sound electrical knowledge; excellent post-war prospects.—Write, stating age, experience, salary, Box 2707, c/o *Wireless World*. [1144]

TECHNICAL TRAINING
GREAT Possibilities Exist for Technically Qualified Engineers, key men in wartime and afterwards. Through the home-study courses of the T.I.G.B. take a recognised engineering qualifications such as A.M.L.Mech.E., A.M.I.E.E., A.F.R.Ac.S., A.M.I.Chem.E. C. and G., etc., in which examinations the T.I.G.B. students have gained 25 FIRST PLACES and Hundreds of Passes. Write to-day for "The Engineer's Guide to Success"—Free—containing the world's widest choice of engineering courses covering all branches, including Aeronautical, Mechanical, Electrical, Wireless, Chemical, etc.
THE TECHNOLOGICAL INSTITUTE OF GREAT BRITAIN, 82, Temple Bar House, London, E.C.4. [9335]

TUITION
MORSE and Wireless, evening tuition. Parties, stamp.—Hastars, 45, Grove Park Rd., W.4. [1116]

RADIO Training.—P.M.G. exams. and I.E.E. Diploma, prospectus free.—Technical College, Hull. [0611]

MORSE Code Training in Your Own Home; "Book of Facts" free.—Candler System Co. (W.O.), 121, Kingsway, London, W.C.2. [9744]

PRACTICAL Radio Postal Courses, coaching for I.P.R.E., R.A.F., A.I.D. exams; booklet free.—Secretary, I.P.R.E., Bush House, Walton Avenue, Henley-on-Thames [9547]

RADIO Engineering.—Television and Wireless Telegraphy, comprehensive postal courses of instruction. Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. (Estd. 1906). Also instruction at school in wireless for H.M. Merchant Navy and R.A.F. [9249]

BUSINESSES FOR SALE OR WANTED
"The Wireless and Electrical Trader" is an essential part of the equipment of every Wireless Trader, its pages reflect the very latest turn of trade events, and it is read by all the leading dealers and manufacturers, for particulars of businesses offered or wanted. By subscription, to the trade only, 17/6 per annum, post free. Send your trade card for specimen copy to Dorset House, Stamford St., London, S.E.1. [0614]

PATENT NOTICE
THE Proprietors of British Patent No. 465747, relating to "Improvements in variable coils," are desirous of entering into negotiations with one or more firms in Great Britain for the purpose of exploiting the invention either by sale of the patent rights or by the grant of licences on reasonable terms.—Interested parties who desire further particulars should apply to Albert L. Mond & Thiemann, of 14 to 18, Holborn, London, E.C.1. [1157]

CROWE

ESCUTCHEONS TUNING CONTROLS DIALS—REMOTE CONTROLS POINTERS, ETC

Crowe products are known to every British Radio Receiver manufacturer. They will be needed again as soon as Victory is won and Crowe will be happy to supply those needs without undue delay. Our extensive plants and equipment are now devoted to the production of important defence items some of which are assisting in your country's great efforts. You can rely upon us to do all we can for you now and in the future and we thank you for your past co-operation. When you think of smarter receivers remember CROWE.

Register your name now with our British Representative for details as soon as available of Crowe Products.

CROWE NAMEPLATE & MANUFACTURING CO.

3701 RAVENSWOOD AVENUE,
CHICAGO, ILL., U.S.A.

Represented in Great Britain by
Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon

"UNIVERSAL CIRCUITS"

by R. S. Roberts, M.Brit.I.R.E., A.M.I.R.E.

Three folders and a thirty-six page booklet, presenting the main principles of radio circuit operation in a concise and convenient form for the pocket.

- I. The Transmitter
- II. The T.R.F. Receiver
- III. The Superheterodyne Receiver

By means of hinged flaps, the charts give a large number of recognised alternatives for each stage. To assist the student in memorising and understanding these, a logical five-colour scheme has been adopted throughout.

Price complete 6/3½ post free, from

The Bookstall
NORTHERN POLYTECHNIC
HOLLOWAY, LONDON, N.7

THE POLYTECHNIC, REGENT ST., LONDON, W.1. SCHOOL OF ENGINEERING

Head of School: PHILIP KEMP, M.Sc.Tech., M.I.E.E., A.I.Mee.E.
RADIO ENGINEERING: A full-time day course in telecommunications, extending over a period of three years, preparing for all recognised examinations and for the radio and telephone industries.
School re-opens 31st August, 1942
Prospectus on application to Director of Education

1,000 National Union, Philco, Tungram, etc. VALVES in stock, including: 78, 6V6G, 6K7G, 6U5, 6U5G, 35, 51, 6K5G, 1A4, 1B4, 6U7G, 2101, 6H6G, 01A, 15, 1A6, 1C6, 10, SP4, HL13, DD13, YME4, DD4D, EMI, P215, SP220, EABI, DDT13, HP4101, SP4B, EZ2, SP13, VPI3K.
Barretters, British 4-Pin and S.C. American 6-Pin. Philco replacement coils.
Please send stamp and exact requirements for price.

E. H. ROBINS TRADING CO., LTD.
44, Kyle Crescent South, Whitechurch, Glam.

ELECTRADIX

"NITNDAY" MAINS CHARGERS. A range for all jobs. The Leadix Nitdays are the best and cheapest trouble-free chargers. Any A.C. mains voltage to 2, 4, 6 or 12 volts. Steel chassis. Safe for car. Model N.A. 2.1/2 is Radio Home Charger for 2 volts 4 amp. 15/6; Model N.A. 1/2 3-cell Trickle. 6 volts 1 amp. 22/-; Model N.B. 6/1 Car Trickle, 6 volt 1 amp. 30/-; Model N.B. 6/1.1/2 Car Trickle, 6 volts 1 1/2 amps. 34/6; Model N.D. 1.2/1 H.M. Car Charger, 12 volts 1 amp. 47/6; Model N.D. 1.2/1 NK Car Charger, 12 volts 1.6 amps. 68/6. Special Model N.E. 2/2 Double Twin Rate Charger, 6 volts and 12 volts 1.6 amps. 81/6. Tungar Type, 70 volts 6 amps. 81/10/-; Model N.A. 1.2/2 3-cell Trickle. 6 volts 1 amp. 22/-; Westinghouse Chargers for 15 amps. and 32 amps. at 6 to 8 volts in stock. Particulars on application.

PETROL ELECTRIC ENGINE SETS. Pelapone 500-watt 2-stroke water-cooled Engine, 50/70 volts 10 amps. D.C. Shunt Dynamo, Supplies limited now. A.B.C. Twin Air-Cooled Set with 50/70 volt 25 amps. Specially lightweight for portable work. Engines. Petrol Twin-Cyl. Douglas for direct coupling, mag. ignition and governor. 14 h.p., £12; 24 h.p., £15.


PUMPS. Stuart motor-pumps, centrifugal, C.D. shelter 12 volts D.C., or 230 volts A.C., in stock. Twin piston pumps with or without motors for suctions or water.

HIGH CYCLE ALTERNATORS, SINGLE PHASE, HIGH SPEED. Compton, 300 watt, 500 cycles, 50 volts 6 amps. £8; 270-watt, 500 cycles, 50 volts 4 amps. £7/15/-. Newton, 250-watt, 10 volt 20 amps., 500 cycles, £4/5/-. E.C.C. and Newton, 2,000-watt, 180 volts 12 amps., 500 cycles, £18/10/-. Motor Alternators, single phase, 1/2 h.p. type "B", input 15 volts D.C., output 50 volts 1 amp., 500 cycles, £3/10/-.

DYNAMOS, WIND DRIVE AERO. Lucas-Rotax, 6/12 volts 8 1/2 amps. D.C., 3rd brush size, 8in. x 4 1/2in., 11 lb., cost £10, unused, 15/- (carriage 2/- extra). G.E.C. Current Dynamoe, 6 volts and 600 volts, ball-bearings, 17 lbs., new, 25/- (carriage 2/6 extra). Charging Dynamos, 30 volts 15 amps. £8/10/-. AC/DC Motor Gen. Chargers. State wants.

MORSE RECORDERS. Spring drive G.P.O. Inker Morse Recorders, standard 6-volt type, £12. Morse Trainer Recorders, direct acting, with key, £9/10/-.

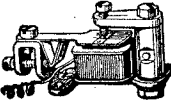THE CAMBRIDGE TOWNSEND BUZZER is the highest note and smallest Buzzer made, used by Government on wave-meters, and has ample platinum contacts. Ident for key work, 10/-; Other Buzzers: Practice, bakelite-cased, 2/-; Square brass-cased Buzzer, 4/6. Heavy type bakelite cased, 5/6. Few D111 Buzzers, multi windings, no contacts, 5/6.



DICTAPHONE SOUND AMPLIFIERS and horn for loud use, with buzzer, 7/6. **MORSE TAPPER SIGNAL KEYS.** Type B1, 5/-; Type M, 6/6; Type R, British-made American type "Speed" key, 8/6; Type PF, 9/6; Type IV, 12/6.

VARIABLE AIR CONDENSERS. .0005 mid. Type F., in maker's carton, 3/6. Twin Trimers, variable, .00012 to .00015 mid. 1/-; RELAYS. No. 6 telephone, twin bobbin, 6-volt 25 m.a., S.P. change-over, 8/6. Other types in stock.

TALKIE SOUNDHEAD CINEPHONE. 35 mm., with meter, £9/10/-; Optical 3-lens unit for 9 mm. Talkie, 4 1/2" long, 1 1/2" dia., 10/6. Ozonezers. 230 volts A.C., for sweet air, 25/-.

D.C. WORKS MOTOR VACUUM CLEANER, on wheels. Powerful 1/2 h.p. motor, £5/15/-.

WORKS SWITCHBOARD PANELS. Fitted circuit breakers, meters and switches. Price on application.

GALVOS, ETC. Circuit testing, G.P.O., vertical, 35/-; Elliott, etc., Army E108, in case with test rheo., M.C. meter, m.a. to 3 amps., 57/6. Bridge Galvos, Sullivan Marine Mirror Galvo, vertical suspension, M.C., £9/10/-; Tinsley Ballistic Susp. Coil Mirror Galvo., as new, £4/10/-; Wheatstone Bridges, incomplete, G.P.O. surplus, less coils and plugs, 45/-.

WAVEMETERS, ETC. Buzzer and Heterodyne, less calibration charts, 45/- to £3/10/-; Radiogoniometer Direction Finders, £4/10/-; Fullograph Spares, new. Chart Drum and Clip, 5/6. Magnetic clutch, 6-volt, complete, 25/-; 9in. Traveller, 8/6; 4in. threaded 120 to inch, with bearings, 12/6; Stylus with carriage rods and brackets, 7/6. 5-pin Plugs, with panel socket and cord, midget type, pair, 4/6. 4in. Drilled Alumina. Panel, 13in. x 6 1/2in., 3/-; Bakelite, ditto, 7in. x 6 1/2in., 2/3.

TESTERS OR AMPLIFIERS. Ex-W.D. Portable Mark IV 3-valve Battery Amplifiers, 9in. x 9in. x 6 1/2in., double doors, mahogany canvas-covered metal-bound case. Fitted 4 transformers, 5-tap switch rheo., terminals and sockets. Suitable for conversion for test set microphone oscillator, etc., unused, 45/-.

HOME GUARD FIELD TELEPHONE CABLE, twin, in 1/2-mile reels. Coiling roses, porcelain, with two Seruit couplers for connect. boxes, 6/6 doz. Old bayonets, make two daggers, 3/6. Relays and drop indicators. Portable Field Telephones.

Please add postage on all mail orders. Send stamped envelope for replies to all enquiries please.

ELECTRADIX RADIOS
19, Broughton St., Battersea, London, S.W.8.

Telephone: Macaulay 2159

SAVE TO SPEND



SEE OUR POST-WAR DELIVERY SCHEME

Why not!

Phone: SYD. 6666

VOIGT PATENTS LTD

"W.W." MAY p. 20
The Courts, Silverdale, London, S.E. 26

CLASSIFIED ADVERTISEMENTS intended for the SEPTEMBER issue can be accepted up to First Post on Monday, August 10th.

THE Proprietors of British Patent No. 475750, dated July 20, 1936, relating to Improvements in Electric Wave Signalling, are desirous of entering into arrangements by way of a license or otherwise on reasonable terms for the purpose of exploiting the above patent and ensuring its practical working in Great Britain.—Enquiries to Singer, Ehlert, Stern and Carlborg, Chrysler Bldg., New York City, N.Y., U.S.A. [1121]

THE Proprietors of British Patent No. 505632, dated November 12, 1937, for "Improvements in and Relating to Cathode-ray Tubes" are desirous of entering into arrangements by way of a license or otherwise on reasonable terms for the purpose of exploiting the above patent and ensuring its practical working in Great Britain.—Enquiries to Singer, Ehlert, Stern and Carlborg, Chrysler Bldg., New York City, N.Y., U.S.A. [1120]

THE Proprietors of British Patent No. 504934, dated November 1, 1937, relating to Improvements in Closures for Evacuated Envelopes and Method of Manufacturing the same, are desirous of entering into arrangements by way of a license or otherwise on reasonable terms for the purpose of exploiting the above patent and ensuring its practical working in Great Britain. Inquiries to Singer, Ehlert, Stern and Carlborg, Chrysler Bldg., New York City, N.Y., U.S.A. [1072]

MISCELLANEOUS

MANUFACTURERS Require Government Sub-contract Work of any Description for their Latex Department, which is being closed down owing to war production restrictions. Factory space and 8-10 female workers available. Willing to purchase new machinery if licence provided.—Please write to Box "A." c/o Dawson's, 129, Cannon St., London, E.C.4. [1125]

BOOKS, INSTRUCTIONS, ETC.

WEBB'S Radio Map of the World Locates any Station Heard. Size 40x30in., 4/6, post 6d.; on linen, 10/6, post 6d.—Webb's Radio, 14, Soho St., London, W.1. 'Phone: Gerrard 2089. [9947]

EVERY Radio Dealer Who is Not a Regular Reader of "The Wireless and Electrical Trader" should send his trade card at once for a specimen copy and full details of the "Trader" Services. "The Wireless and Electrical Trader" has the widest influence, and is read by all the leading manufacturers and traders. Trade only, 17/6 per annum, post free. Published at Dorset House, Stamford St., London, S.E.1. [0615]

A 65-watt SOLON for general use

This 65-watt Industrial type SOLON Electric Soldering Iron is fitted with an oval tapered bit—a shape which is suitable for most general work. For specialised work the pencil bit model is recommended, whilst bigger jobs call for the 125-watt or 240-watt models.

Supplies of these various models are only available for essential war work, of course, and due to heavy demands it is necessary to order well in advance to avoid disappointment in delivery.

Details of this and other models sent on request.



MADE FOR USUAL STANDARD VOLTAGES

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.,
Engineering Dept., Milton Court,
WESTCOTT, DORKING, SURREY.

PREMIER RADIO

PREMIER 4-watt A.C. AMPLIFIER

Each Amplifier is completely wired and tested. Selected components, specially matched valves and 8in. energised speaker, £5/5/-.

PREMIER MICROPHONES

Transverse Current Mike. High-grade large output unit. Response 45-7,500 cycles. Low hiss level, 23/-.

Moving Coil Mike. Permanent magnet model requiring no energising. Response 90-5,200 cycles. Output 25 volt average. Excellent reproduction of speech and music, 63/-.

Super model, £5/5/-.

Microphone Transformers, 10/- each.
MR1 Universal 4-watt output transformer tapped for Power, Pentode and Push Pull, suitable for 2 and 7/9 ohms speech coil, 7/6 each.

I.F. TRANSFORMERS, IRON CORED

450-475 kcs, plain and with flying lead, 5/6 each.

ELECTROLYTIC CONDENSERS

8MF 250 v. Wet Can type, 3/- each.
25MF 25 v. 1/6 50MF 12 v. 1/6
50MF 50 v. 2/6 8MF 125 v. 1/6
15MF 50 v. 1/- 15MF 100 v. 1/3

NEW PREMIER S.W. COILS

4- and 6-pin types now have octal pin spacing, and will fit International Octal valve holders.

4-PIN TYPE			6-PIN TYPE		
Type	Range	Price	Type	Range	Price
04	9-15 m.	2/6	06	9-15 m.	2/6
04A	12-26 m.	2/6	06A	12-26 m.	2/6
04B	22-47 m.	2/6	06B	22-47 m.	2/6
04C	41-94 m.	2/6	06C	41-94 m.	2/6
04D	78-170 m.	2/6	06D	78-170 m.	2/6
04E	150-350 m.	3/-	CHASSIS MOUNTING		
04F	255-550 m.	3/-	OCTAL HOLDERS		
04G	490-1,000 m.	4/-	10 1/2 d. each.		
04H	1,000-2,000 m.	4/-			

S.W. H.F. CHOKES

10-100 m., 10jd.
High-grade Pie-wound type, 5-200 m., 2/6 each.

SHORT WAVE CONDENSERS

Trolital insulation. Certified superior to ceramic. All-brass construction. Easily ganged.
15 m.mfd. 2/6 100 m.mfd. 3/-
25 m.mfd. 2/6 160 m.mfd. 3/7
40 m.mfd. 2/6 250 m.mfd. 4/-
Utility Micro Dials, direct and 100-1 6/6

PREMIER REPLACEMENT VALVES

4-volt A.C. types, 5-pin. ACHL, ACSI, 5/6 each.

RESISTANCES

2,000 ohms 25-watt Res., with 5 Tapping Clips, 2/- each.
1,000 ohm Wire Wound Potentiometers, 3/11 each.
Mains Resistances, 660 ohms .2A Tapped. 360 x 180 x 60 x 60 ohms, 5/6 each.
1,000 ohms .2A Tapped. 900, 800, 700, 600, 500 ohms, 4/6 each.
Valve Screens for International and U.S.A. types, 1/2 each.
H.T. Eliminators, 150 v. 30 mA. output, 41/6; ditto, with 2 v. + A. charger, 52/6.

MOVING COIL SPEAKERS

Celestion 8in. P.M. Speaker, 25/-.
Goodmans 8in. P.M. Speaker, 25/-.
Energised 8in. 2,000 ohms field, 25/-.
Speakers are complete with output transformer.

Send for details of our Morse Equipment, Mains Transformers, Smoothing Chokes and Valves available.

PREMIER BATTERY CHARGERS FOR A.C. MAINS

Westinghouse Rectification, complete and ready for use. To charge 6 volts at 1 amp. (also tapped for 2 and 4 v.), 29/6. 12 v., 1 a. (also tapped for 2 and 6 v.), 37/6. 6 v. at 2 a. (also tapped to charge 2 and 4 volts), 48/-.

MATCHMAKER UNIVERSAL OUTPUT TRANSFORMERS

Will match any output valves to any speaker impedance. 11 ratios from 13-1 to 80-1, 5/7 watts, 20/-; 10/15 watts, 26/-.

ALL ENQUIRIES MUST BE ACCOMPANIED BY d. STAMP.

PREMIER RADIO CO.

ALL POST ORDERS to:

JUBILEE WORKS, 167, LOWER CLAPTON ROAD, LONDON, E.5. (Amherst 4723.)

CALLERS to:

JUBILEE WORKS or 50, HIGH STREET CLAPHAM, S.W.4. (Macaulay 2381.)


169, FLEET STREET, E.C.4. (Central 2833.)

RAYMART "SPEED" KEY

After giving a thorough test to this British-made Raymart "Speed" Key, the "WIRELESS WORLD" said:

"The Key is rigidly constructed and is extremely light in action; being fitted with heavy silver contacts, it is suitable for serious work and can be recommended either for practical purposes or otherwise."

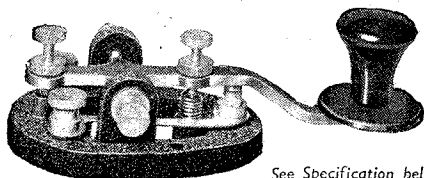This is not a toy: it is a key anyone would be proud to own, and it will give years of useful service.



See Specification below.

The contacts are of 1/4-in. solid sterling silver. A high grade of spring is fitted and gap adjustment is easily and accurately carried out. The base of the key is drilled for two-hole screw fixing. All metal parts are instrument lacquer finished.

Raymart KIT OF PARTS for building a G.P.O. type of Morse Key. This KIT includes:

Solid brass bar 1/4-in. by 3/8-in. Set of pivot bushes. Pair of solid sterling silver contacts. Brass screw with adjusting collar for varying tension on spring. Spring for above. Brass stop screw with locking collar. Bakelite knob, highly polished, fitted with fixing screw. Washer for fitting below knob. Combined template and "erinofort" base which covers the wood base. In addition, you will need as a base a two-way switch block (cost only a few pence) and two terminals. Obtain these from local electricians. Only tools needed are a gimlet and pliers. Anyone can assemble this Kit in 10 to 15 minutes.

GENI'S MANUAL. All interested in Radio Communication should have a copy. It shows you how to build short-wave receivers, transmitters, oscilloscopes, etc. Written by an expert with Air Force and Navy experience. Price only 9d. post free. Please mention the "Wireless World" when ordering.

RAYMART
"SPEED" KEY
8/6
Post Paid.


THE KIT
7/6
Post Free.

RAYMART 48 HOLLOWAY HEAD, BIRMINGHAM, 1
Telephone: Midland 3254.



NORMAN ROSE RADIO COMPONENTS

—EX STOCK

Look for the 'Norman' Trade Mark 

ELECTROLYTIC CONDENSERS

Paper Condensers, Carbon and Wire-wound Resistors. Volume Controls. Dropper Resistors for all makes of Sets, Pye, Ekco, Maestro, Ferguson, Decca, etc., etc. Cartridge Fuses, Pilot Lamps, Transformers, NR Barretters replacing C1 and C1C, Line Cord, Replacement Resistors, 750 ohm with var. slider. Multi-Purpose Dropper Resistor with five 50 ohmappings and one 750 ohm with slider. Insulated sleeveings. High Note Buzzers, etc., etc.

Send 2 1/2d. for list stating special requirements so that up-to-the-minute offers can be submitted.

DON'T MISS YOUR COPY OF THE RADIO TRADE'S MOST FAMOUS SERVICE MANUAL, "RADIO INSIDE OUT."

Hundreds of useful hints when doing repairs, colour codes, valve charts, tabulated list replacement parts for all popular Receivers, Valves, Condensers, etc. **3/6** post paid.

(Available all Booksellers, W. H. Smith, etc.)

Special facilities for Government orders, Radio Trade Wholesalers and Trade Repair Depots.

NORMAN ROSE (ELECTRICAL) LTD.
EIGHTY, ST. MARY'S ROAD, EALING, LONDON, W.5.
Telephone: Ealing 3595.

ACES DEVELOPMENT CO. LTD.

FOR PRECISION HIGH FREQUENCY IRON CORES

37, CITY RD. MANCHESTER, 15

Central 1515

DR. CECILS RADIO CRYSTAL

improves reception on any crystal set.
Send for Sample.

Post **1/6** FREE

AUSTIN CLARKE (LONDON) LTD.
84, NEWMAN ST., LONDON, W.1.

The SIMMONDS GROUP


LONDON
MELBOURNE
PARIS
NEW YORK
LOS ANGELES

INVENTORS

We continually seek new inventions and products in all branches of industry for development and production by the manufacturing companies of the Simmonds Group throughout the world.

SIMMONDS DEVELOPMENT CORPORATION LTD. BUSH HOUSE W C 2

F R E Q U E N T I T E

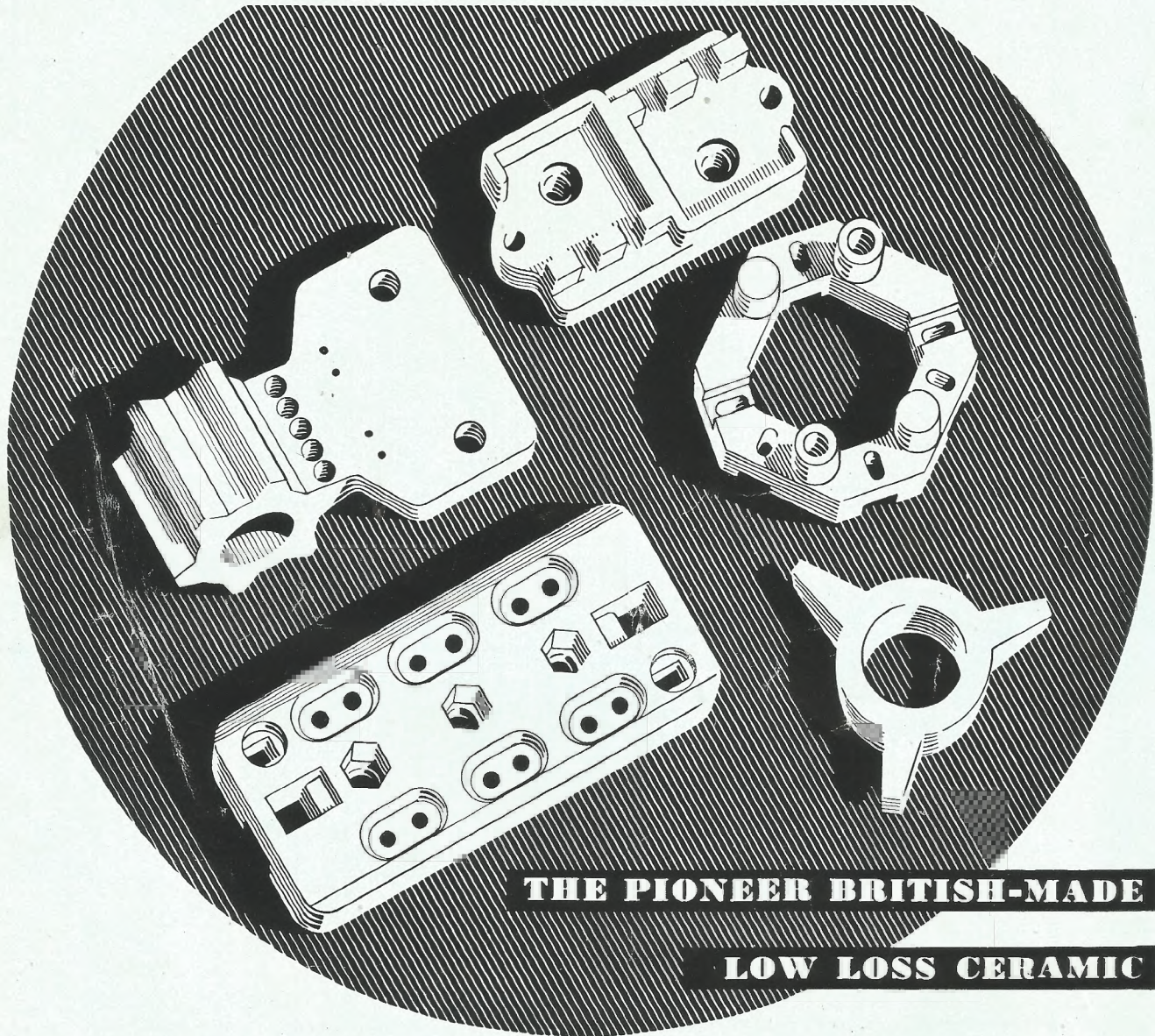

THE PIONEER BRITISH-MADE


LOW LOSS CERAMIC

THE demand for Frequentite, which possesses outstanding properties of Low Loss and High Mechanical Strength, continues to increase rapidly—*and to be met.* Production capacity has been stepped up over a period of years by extensions to plant, the

employment of specialised new equipment, and progressive improvements in manufacturing technique. Bulk supplies of the most intricate designs can be delivered promptly, and all manufacturers are invited to write for Catalogue No. S.P.10.

STEATITE & PORCELAIN PRODUCTS LTD.

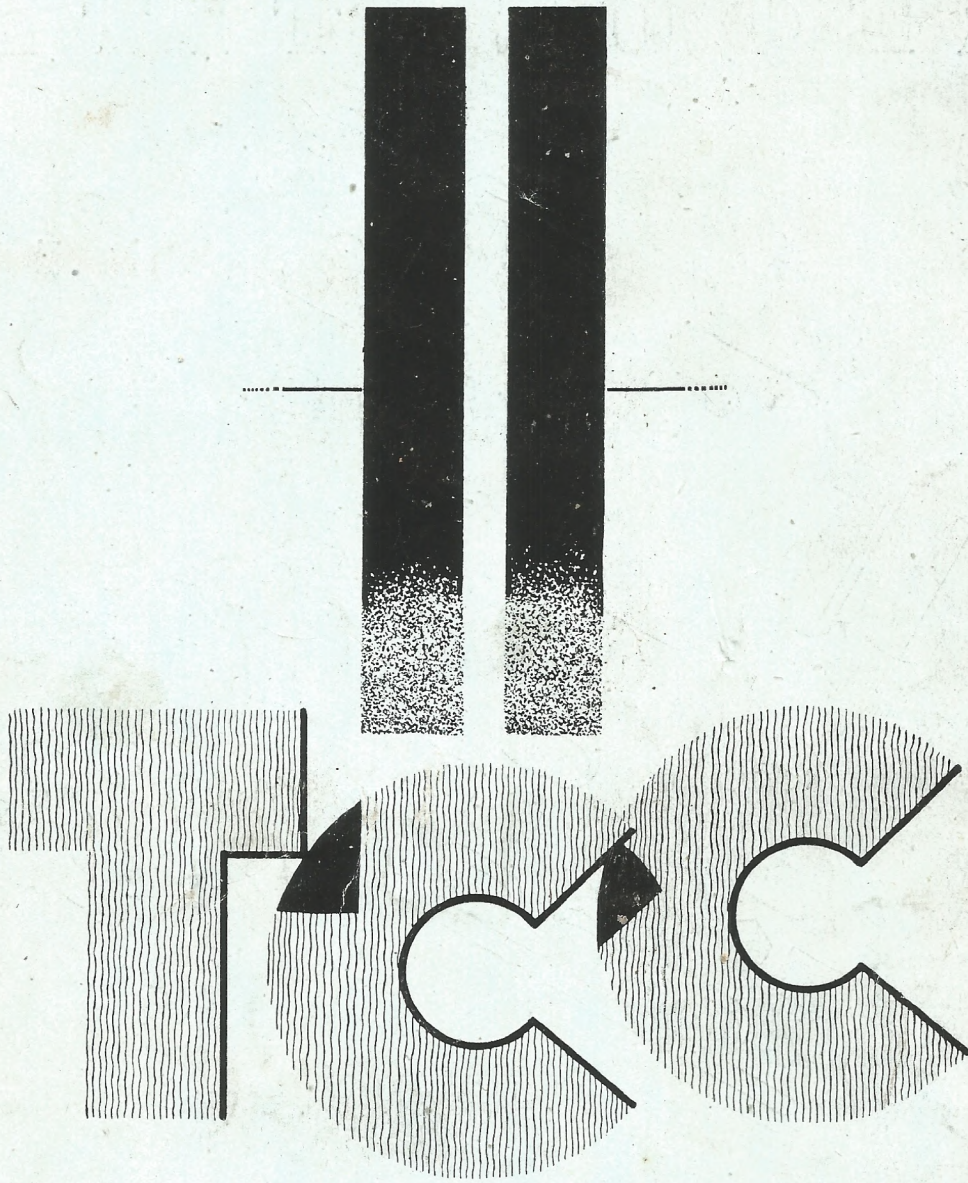Head Office : STOURPORT-ON-SEVERN, WORCS.
 Telephone : Stourport 111. Telegrams : Steatoin, Stourport.



**PRE-EMINENT IN PEACE
INDISPENSABLE IN WAR**

ADVERTISEMENT OF THE TELEGRAPH CONDENSER CO., LTD.

G.P. 5257