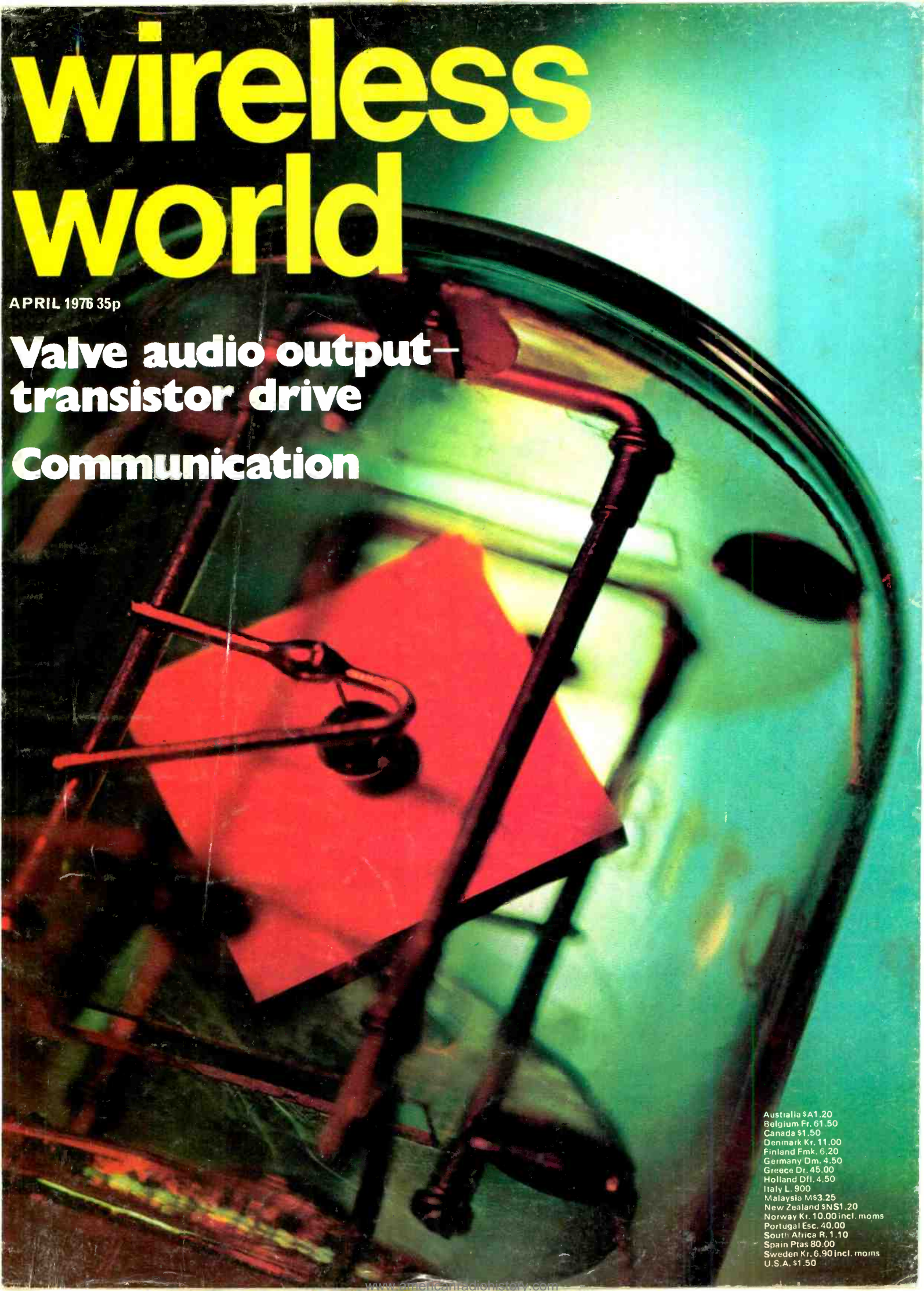


wireless world






APRIL 1976 35p

**Valve audio output—
transistor drive**

Communication

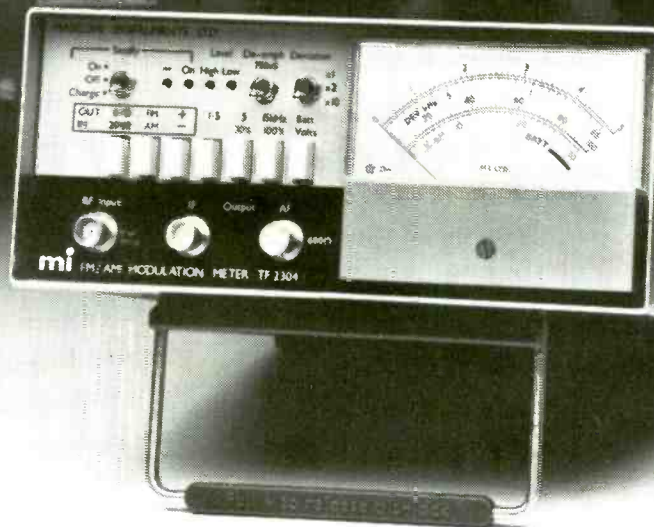Australia \$A1.20
Belgium Fr. 61.50
Canada \$1.50
Denmark Kr. 11.00
Finland Fmk. 6.20
Germany Dm. 4.50
Greece Dr. 45.00
Holland Dfl. 4.50
Italy L. 900
Malaysia M\$3.25
New Zealand \$NS1.20
Norway Kr. 10.00 incl. moms
Portugal Esc. 40.00
South Africa R. 1.10
Spain Ptas 80.00
Sweden Kr. 6.90 incl. moms
U.S.A. \$1.50





IEA·ELECTREX
 International Electronic
 Electrical and Instrument
 and Instrument
 Exhibition
 National Exhibition Centre
 Birmingham 3-7 May 1976

It's always been **mi** for modulation meters. It still is-am/fm style.

Modulation meter expertise has always meant **mi** – ever since we were the only manufacturer. So, if you are in the market for deviation or modulation meters, you could save yourself time and trouble by considering the **mi** range first . . . anything from lowest priced automatic to sophisticated, low noise, high performance instruments.

TF 2303 Compact and lightweight, this manual model is still preferred by many engineers for mobile radio testing on the bench or in the field. FM deviation and AM depth at carrier frequencies up to 520 MHz.

TF 2304 A low priced automatic with high performance. Automatic tuning and level setting with exceptionally good r.f. screening. Eight peak deviation ranges from 1.5 to 150 kHz and a.m. ranges at carrier frequencies from 18 to 1000 MHz.

TF 2300B A high-grade instrument with exceptional low noise performance, TF 2300B is often used as a standard for lower grade types. As a multipurpose instrument it can measure peak deviations up to 500 kHz (at modulating

frequencies up to 200 kHz) for carrier frequencies up to 1200 MHz. Applications include tests on mono and stereo broadcast transmitters, mobile radio type approval and f.m./a.m. production testing. Crystal oscillator **TK 2302** plugs into TF 2300B for extra low noise testing.

TF 2300BM series: A series of specials (e.g. for measuring a.m. on f.m.).

TF 2301A Fully programmable, for use in automatic test systems. Special peak detector designed to follow rapidly increasing or decreasing modulation depths. Deviation ranges 1.5 to 500 kHz and a.m. at carrier frequencies 4 to 1000 MHz.

Accessories A range of accessories specially designed to make your job easier includes a signal sniffer, power attenuators, termination unit, r.f. fuse unit and carrying cases.

Ask for the latest information from the experts who have been in the business for over 30 years.

mi: THE MODULATION EXPERTS

MARCONI INSTRUMENTS LIMITED

Longacres • St. Albans • Hertfordshire AL4 0JN • England • Telephone: St. Albans 59292 • Telex: 23350

A GEC - Marconi Electronics company.

www.americanradiohistory.com

WW-001 FOR FURTHER DETAILS


LOW COST TESTERS



LEVELL

PORTABLE INSTRUMENTS

INSULATION TESTER

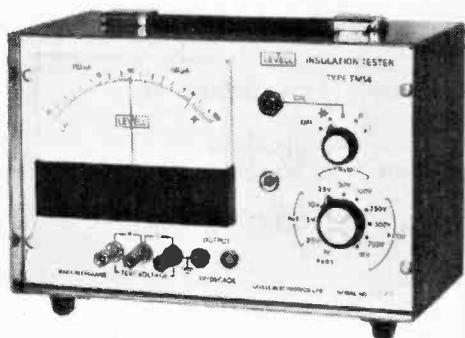

A logarithmic scale covering 6 decades is used to display either insulation resistance or leakage current at a fixed stabilised test voltage. The current available is limited to a maximum value of 3mA for safety and capacitors are automatically discharged when the instrument is switched off or to the CAL condition. The instrument operates from a 9V internal battery.

RESISTANCE RANGES

10M Ω to 10T Ω (10^{13} Ω) at 250V, 500V, 750V and 1kV.

1M Ω to 1T Ω at 25V, 50V and 100V.

100k Ω to 100G Ω at 2.5V, 5V and 10V.

10k Ω to 10G Ω at 1V.

Accuracy $\pm 15\%$ +800 Ω on 6 decade logarithmic scale.

Accuracy of test voltages $\pm 3\%$ ± 50 mV at scale centre.

Fall of test voltages $< 2\%$ at 10 μ A and $< 20\%$ at 100 μ A.

Short circuit current between 500 μ A and 3mA.

CURRENT RANGE

100pA to 100 μ A on 6 decade logarithmic scale.

Accuracy of current measurement $\pm 15\%$ of indicated value.

Input voltage drop is approximately 20mV at 100pA, 200mV at 100nA and 400mV at 100 μ A.

Maximum safe continuous overload is 50mA.

MEASUREMENT TIME

< 3 s for resistance on all ranges relative to CAL position.

< 10 s for resistance of 10G Ω across 1 μ F on 50V to 500V.

Discharge time to 1% is 0.1s per μ F on CAL position.


RECORDER OUTPUT

1V per decade $\pm 2\%$ with zero output at scale centre.

Maximum output ± 3 V. Output resistance 1k Ω .

type
TM14 **£98**

TRANSISTOR TESTER

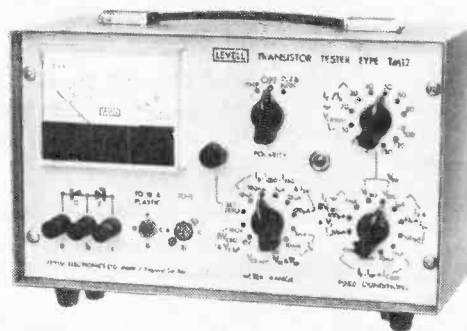

Tests bipolar transistors, diodes and zener diodes. Measures leakage down to 0.5 nA at 2V to 150V. Current gains are checked from 1 μ A to 100mA. Breakdown voltages up to 100V are measured at 10 μ A, 100 μ A and 1mA. Collector to emitter saturation voltage is measured at 1mA, 10mA, 30mA and 100mA for I_C/I_B ratios of 10, 20, 30. The instrument is powered by a 9V battery.

TRANSISTOR RANGES (PNP OR NPN)

I_{CBO} & I_{EBO} : 10nA, 100nA, 1 μ A, 10 μ A and 100 μ A f.s.d. acc. $\pm 2\%$ f.s.d. $\pm 1\%$ at voltages of 2V, 5V, 10V, 20V, 30V, 40V, 50V, 60V, 80V, 100V, 120V, and 150V acc. $\pm 3\%$ ± 100 mV up to 10 μ A with fall at 100 μ A $< 5\%$ +250mV.

BV_{CBO} : 10V or 100V f.s.d. acc. $\pm 2\%$ f.s.d. $\pm 1\%$ at currents of 10 μ A, 100 μ A and 1mA $\pm 20\%$.

I_B : 10nA, 100nA, 1 μ A ... 10mA f.s.d. acc. $\pm 2\%$ f.s.d. $\pm 1\%$ at fixed I_E of 1 μ A, 10 μ A, 100 μ A, 1mA, 10mA, 30mA, and 100mA acc. $\pm 1\%$.

h_{FE} : 3 inverse scales of 2000 to 100, 400 to 30 and 100 to 10 convert I_B into h_{FE} readings.

V_{BE} : 1V f.s.d. acc. ± 20 mV measured at conditions on h_{FE} test.

$V_{CE(sat)}$: 1V f.s.d. acc. ± 20 mV at collector currents of 1mA, 10mA, 30mA and 100mA with I_C/I_B selected at 10, 20 or 30 acc. $\pm 20\%$.

DIODE & ZENER DIODE RANGES

I_{DR} : As I_{EBO} transistor ranges.

V_Z : Breakdown ranges as BV_{CBO} for transistors.

V_{DF} : 1V f.s.d. acc. ± 20 mV at I_{DF} of 1 μ A, 10 μ A, 100 μ A, 1mA, 10mA, 30mA and 100mA.

type
TM12 **£95**

LEVELL ELECTRONICS LTD.

Moxon Street, High Barnet, Herts. EN5 5SD
Tel: 01-449 5028/440 8686


Prices include batteries and U.K. delivery, V.A.T. extra. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.




It is now 2 years since we published this tuner design in the *Wireless World*. Since then it has been admired, sold across the world, built by countless people, talked about and copied, but this is still the best F.M. Tuner available.

Now further improved by the original designers:

- ★ Updated circuitry gives full 88-108 MHz tuning, and reduced hum level.
- ★ New fibreglass P.C.B., fully anotated, drilled and tinned.
- ★ Coil now supplied fully assembled and aligned, leaving NO adjustments after building, for the same price!
- ★ Illustrated booklet gives full description and assembly instructions for 50p, refundable on purchase.
- ★ New REDUCED prices now INCLUDE U.K. postage and packing.
- ★ **Assembled** modules now competitive with **kits** from other sources (Compare our prices!)
- ★ Credit facilities now available via BARCLAYCARD AND ACCESS. Just quote your card number when ordering.
- ★ New illustrated leaflet available, drop us a post card.

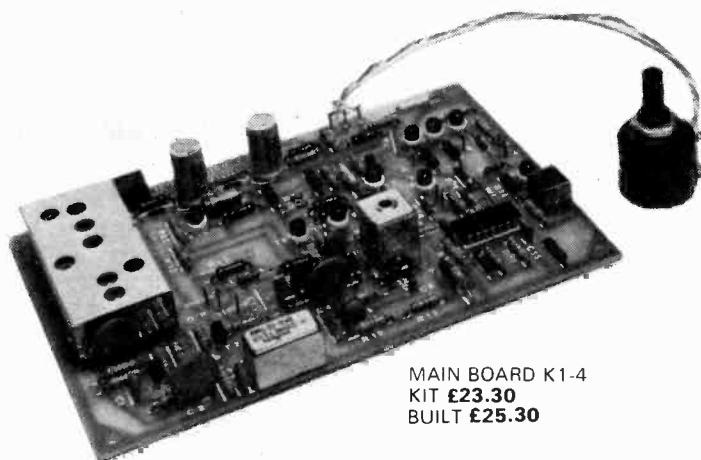

MAIN BOARD K1-4
KIT £23.30
BUILT £25.30

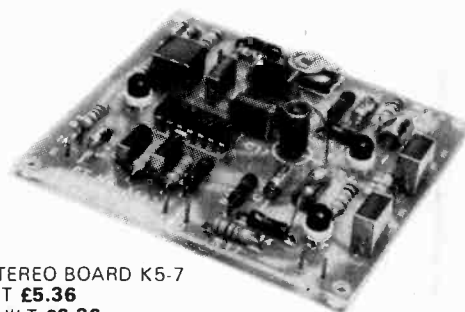

STEREO BOARD K5-7
KIT £5.36
BUILT £6.36

KITS

K1	All main board resistors, including tuning pot	£5.32
K2	All main board capacitors	£1.98
K3	Main board transistors and diodes	£3.00
K4	Main P.C.B. i.c.'s, filter coil and front end	£13.00
K5	Stereo board resistors	£0.76
K6	Stereo board capacitors	£1.05
K7	Stereo P.C.B. i.c. and transistors	£3.55
K8	4 way function switches	£4.59
K9a	6 way channel selector, inc. cermet pots, P.C.B.	£12.75
K10	Power supply, including transformer and P.C.B.	£5.50
K11	Full metalwork set, front panel, cabinet, plugs mains lead, wire, etc.	£25.60
K12	Frequency meter and drive components for K9a	£10.22

SEPARATE ITEMS (inc. in kits)

P.C.B. for main board	£1.95
P.C.B. for stereo	£0.95
P.C.B. for selector	£0.95
P.C.B. for power supply	£0.95
MC1310 or equiv.	£1.95
TBA750B	£1.55
SL301B	£1.10
SL3046	£0.85
TBA625C (reg) & heat sk.	£1.15
LP1186 front end	£5.95
Filter SFG10-7MA	£1.55
Coil. (assembled & adjusted)	£0.50
Ten turn tuning pot	£3.00
Front panel	£1.75
Teak cabinet	£7.75
Meter (scaled 105 or 108 MHz)	£8.85
Scale only (state which)	£0.30

All kits guaranteed to work or free repair!



Use Access here



FULL TUNER KIT £85.00
COMPLETED TUNER £92.50

ALL ORDERS ACKNOWLEDGED — EX STOCK DELIVERY
PLEASE ADD 25% VAT TO ALL ORDERS

Icon Design

33 Restrop View
Purton, WILTS
SN5 9DG

THE 'MISTRAL' 1 DIGITAL CLOCK

★ COMPLETE KIT ★



- Pleasant green display · 12/24 Hour readout
- Silent Synchronous Accuracy · Fully electronic
- Pulsating colon · Push-button setting
- Building time 1 Hr. · Attractive acrylic case
- Easy to follow instructions · Size 10.5x5.7x8 cm
- Ready drilled PCB to accept components

KIT PRICE £11.57
Inc. P&P + £0.93 VAT

THE 'MISTRAL' 2 DIGITAL ALARM CLOCK

WITH SLEEP-OVER FEATURE



- Soft Green Display
- 24 Hour Alarm
- 10 Minute Repetition
- Alarm Set Indicator
- Accurate Silent Timekeeping
- British Designed and Built

COMPLETE PRICE £14.35
Inc. P&P + £1.15 VAT

1419 — ADVANCED



SPECIFICATION

- 14 digit LED display
- 10 digit mantissa with sign and 2-digit exponent with sign for data entry or results (10^{-99} ~ 10^{99})
- Automatic selection of correct notation for result display (scientific or floating point)
- Dome keyboard for excellent response and preventing double entry input
- BASIC FUNCTION (+ - × ÷)
- AND MEMORY
- Algebraic mode operation
- Constant operations
- Repeat operations
- Chain operations
- Change sign operation

- Display and Y-register exchangeable
- One accumulating memory
- Display and memory exchangeable
- SPECIAL FUNCTION
- Trigonometric functions (sin cos tan)
- Inverse trigonometric functions (sin⁻¹ cos⁻¹ tan⁻¹)
- Hyperbolic functions (sinh cosh tanh)
- Inverse-Hyperbolic functions (sinh⁻¹ cosh⁻¹ tanh⁻¹)
- Radian or degree selectable
- Logarithms (ln log)
- Anti-logarithms (e^x 10^x)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})

PRICE £25.89
P&P 75p + VAT £2.13

1420 — SENIOR



- 14 digit LED display
- 10-digit mantissa with sign and 2-digit exponent with sign for data entry or results (10^{-99} ~ 10^{99})
- Automatic selection of correct notation for result display (scientific or floating point)
- Dome keyboard for excellent response and preventing double entry input
- Algebraic mode operation
- Chain operations
- Change sign operation
- Three memories
- Display and memory exchangeable
- Trigonometric functions (sin cos tan)
- Inverse-trigonometric functions (sin⁻¹ cos⁻¹ tan⁻¹)
- Radian or degree selectable
- constant
- Logarithms (ln log)
- Anti-logarithms (e^x 10^x)
- Combinatorial functions (n! (n), nPr, nCr)
- Normal distribution function (Pr(x))
- Gamma function ($\Gamma(x)$)
- Group operations (\sum \prod σ Σ Δ Δ^2)
- X
- Group controls (K⁺ K⁻ Σ Δ Δ^2 CLear)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})
- Square (x^2)
- Sum of squares ($\Delta^2 x^2$)
- Summation (ΣX)
- Item count (n)
- Mean value (X)
- Mixed chain operations with parentheses approach (up to two levels)

PRICE £55.63
P&P 75p + VAT £4.51

1421 — PROGRAMMABLE



BESIDES HAVING THE CAPABILITY OF A SCIENTIFIC CALCULATOR


- 9-digit LED display
- 8 digits capacity for data entry or results (10^{-99} ~ 10^{99})
- Full floating point
- Automatic display blanking
- Three-register operational stack
- Change sign operation
- Reverse polish notation
- Display and Y-register exchangeable
- One accumulating memory (Memory store, Memory recall M + × M - × and M ÷ X)
- Trigonometric functions (sin cos tan)
- Inverse trigonometric functions (sin⁻¹ cos⁻¹ tan⁻¹)
- Radians and degrees exchangeable
- constant
- Logarithms (ln log)
- Anti-logarithms (e^x)
- Power function (y^x)
- Reciprocal ($1/x$)
- Square root (\sqrt{x})
- Square (x^2)

IT CAN LOAD ANY 102 STEPS PROGRAM TO HELP YOU SOLVE THE REPEATED ENORMOUS COMPLEX PROBLEMS

The Qualitron Programmable Calculator can be used to memorize any combination of key entries while in the LOAD mode then automatically plays back the programmed sequences as often as desired in the RUN mode

Up to 102 steps can be stored in multi-program sequence blocks. Each block or program can be executed individually or you can make the decision to branch to specific program, run each in series or perform intermediate calculations from the keyboard

PRICE £40.80
P&P 75p + VAT £3.32

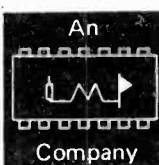


IMTECH PRODUCTS LTD

IMP HOUSE, ASHFORD ROAD
ASHFORD, MIDDX. TW15 1XB
telephone ASHFORD 44211 (4 lines)
telex 936291 WESSIMP ASHFORD

Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.

Viewer's Panel

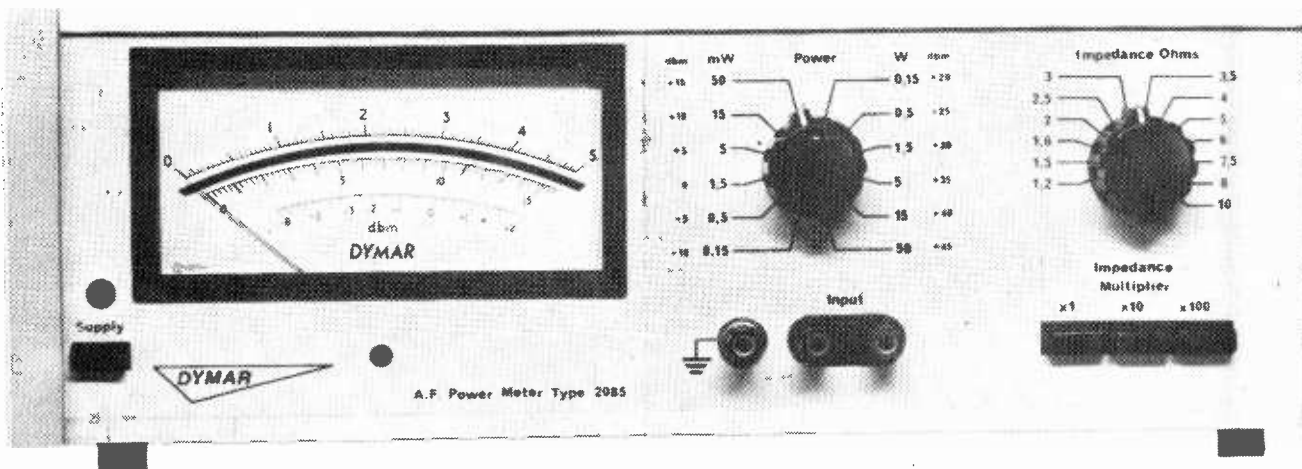

The new Dymar Type 2085. An AF power meter that let's you see what you're doing.

With a mirror-backed 11 cm meter – that's nearly 4½ in. – you are never in doubt about the reading. It's the same with the control settings. Man-sized knobs, click stops and clear markings make this AF power meter a joy to drive. Under the bonnet, of course, there's performance to match appearance.

Like:

Frequency range: 30 Hz to 30 kHz.

Power ranges: Twelve from 150 μ W to 50 W (yes, fifty Watts).

Impedance ranges: 39 values, 1.2 ohms to 1000 ohms.

Plus all the little extras that come as standard with Dymar.

A temperature compensated 'square law' detector for true power reading on the sensibly linear meter scale.

And the battery power option. A simple module which provides integral battery and charger for laboratory standard measurements anywhere.

Measure AF power, AF gain loss or signal to noise, or match source impedances.

Whichever way you use the Dymar Type 2085 the answers come out crystal clear.

On a panel that's meant to be looked at. Not simply admired.

The Type 2085. Designed and made in Britain by Dymar. Write or call for details, or use the Reader Reply Service.

DYMAR

the name in radiotelephones

Dymar Electronics Limited,

Instruments Division, Colonial Way, Radlett Road, Watford, Herts. WD2 4LA, England.

Telephone: Watford 37321. Telex: 923035. Cables: Dymar Watford.

WW — 068 FOR FURTHER DETAILS

We've joined Christopher Wren in the dome business...

... as users of our **Dome Tweeters** will already know

ISOPHON—are a company who have been manufacturing loudspeakers for over fifty years and are internationally known and respected for quality and reliability. They offer a wide range of tweeters, mid-range and bass units.

Owing to shortage of space we are only able to draw your attention to just two of the models currently being manufactured by Isophon.

The KK8

A dome tweeter, well known for its performance and reliability, and chosen by many loudspeaker manufacturers. Two models are available, one up to 50 watts and the other up to 80 watts RMS Power Rating. Frequency range from 800 to over 20,000 Hz.

The PSL 245/60

A new 10" circular loudspeaker, offering up to 50 watts RMS Power Rating.

Our 28 page colour catalogue will give you details of the extremely wide choice of loudspeakers that are available from Isophon.



For your free copy of the catalogue, please post the coupon to...

Hayden Laboratories Limited
Hayden House, Churchfield Road
Chalfont St. Peter, Bucks. SL9 9EW
Tel: Gerrards Cross (028 13) 88447

Please forward your 28 page ISOPHON LOUSPEAKER catalogue to:
Name
Company
Address
Code

Collect wireless world Circards. And build a valuable dossier on circuit design.


Circards is a unique and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable and up-to-the-minute data on circuit design — data not available from any other single source.

Each Circard is 8" x 5" and usually shows a specific tested circuit, a description of the circuit operation; component values and ranges; circuit limitations and modifications; performance data and graphs.

The double-sided format enables the Circard to be filed in standard boxes for easy reference. And the plastic wallet provided keeps the cards well protected.

Circard sets (10 cards) come in wallets and cost £2.00. A subscription for 10 consecutive sets costs £18.

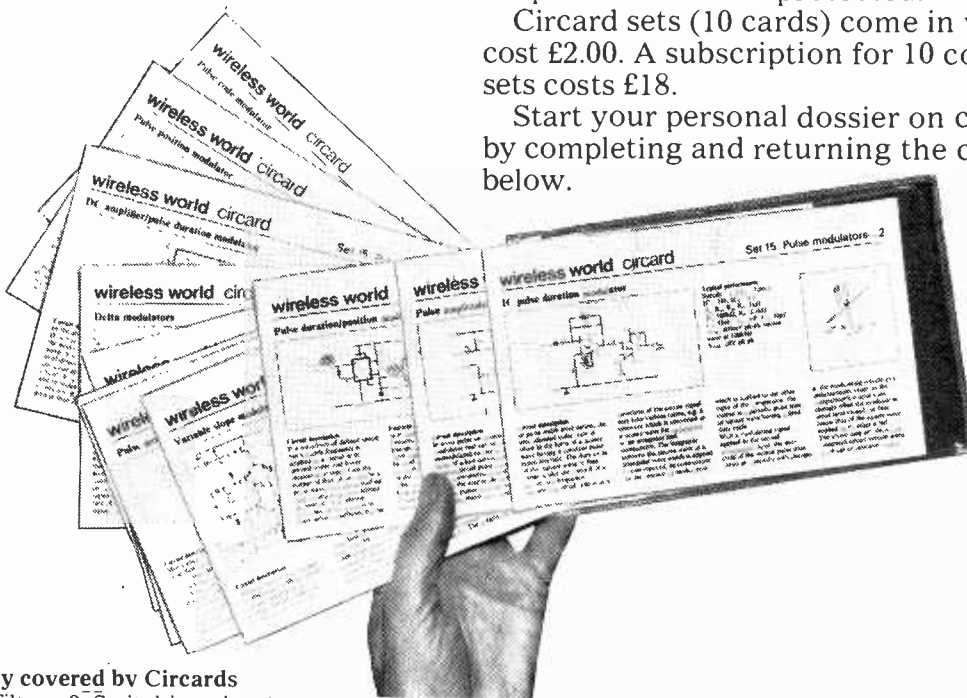Start your personal dossier on circuit design by completing and returning the coupon below.



Subjects already covered by Circards

- 1. Basic active filters. 2. Switching circuits comparators and schmitts.
- 3. Waveform generators. 4. AC measurements.
- 5. Audio circuits: preamplifiers, mixers, filters and tone controls.
- 6. Constant current circuits. 7. Power amplifiers.
- 8. Astables. 9. Opto-electronics.
- 10. Micropower circuits. 11. Basic logic gates.
- 12. Wideband amplifiers. 13. Alarm circuits.
- 14. Digital counters. 15. Pulse modulators.
- 16. Current differencing amplifiers — signal processing.
- 17. Current differencing amplifiers — generation.
- 18. Current differencing amplifiers — measurement and detection.
- 19. Monostable circuits. 20. Transistor pairs.
- 21. Voltage to frequency converters.
- 22. Amplitude modulators. 23. Reference circuits.
- 24. Voltage regulators
- 25. RC oscillators — I. 26. RC oscillators — II.
- 27. Linear C.M.O.S.—I.
- 28. Linear C.M.O.S.—II.
- 29. Analogue multipliers
- 30. Non-linear functions

To: General Sales Dept., IPC Business Press Ltd., Room 11 Dorset House, Stamford Street, London SE1 9LU

Please send me set no(s) @ £2.00 each *
@ £18.00 *

I wish to subscribe, starting with no

I enclose cheque/money order for £
*Tick as required/Cheques to be made payable to IPC Business Press Ltd.

Name

Address

.....
Company registered in England. Registered address, Dorset House Stamford Street, SE1 9LU, England. Registered Number 677128

The Antex Range

All prices include VAT. P.&P. in brackets



MODEL C - 15 watt miniature soldering iron
Bits slide on and off stainless steel shaft. Elements fitted inside steel shaft for efficient heat transfer. Length 16 cm. Complete iron with 2.3 mm. iron-coated bit £2.99 (0.22). Spare elements £1.20 Spare bits £0.35 (nickel) £0.45 (iron-coated).



MODEL G - 18 watt miniature soldering iron
Looks exactly like model C, but because of the extra 3 watts should be kept going all day on repairs or production. Stainless steel shaft - fitted with standard iron-coated bit 2.3 mm. £3.21 (0.22) Spare elements £1.69 Spare bits 2.3, 3 or 4.7 mm. £0.45.



MODEL CCN - 15 watt miniature soldering iron
Unique - ceramic shaft - no measurable leakage - capacitance 30 pf. Tested at 2000 volts A.C. Length 16 cm. Complete with standard iron-coated bit 2.3 mm. £3.21 (0.22). 4 other slide-on and-off bits available from £0.45 Spare elements £1.69. Suitable for the most delicate soldering job imaginable.



MODEL X.50 T.C. - 50 watt temperature controlled soldering iron
Leakage current negligible - Temperature controlled to 2°C either way. Ceramic shaft inside stainless steel shaft. Tested at 2000 volts A.C. Complete with 3 mm. iron-coated bit £10.55 (0.27) Normally set at 370°C Length 20 cm. Weight 50 gr.

MODEL SK.1 - SOLDERING KIT
Fitted with model C miniature iron (see above), 2 spare bits 2.3 and 4 mm., heat sink, reel of solder. Plastic base serves as stand. Booklet "How to Solder" gives useful tips for beginners. Price £4.62 (0.42)

MODEL MLX - 12 volt - 25 watt Soldering iron
with 4½ mtrs. lead and crocodile clips
Useful for repairs on motor cars, boats, model trains, etc. Can be worked off car-type battery. Complete with 3.2 mm. bit £3.53 (0.30) Two other bits available 2.4 and 4.7 mm. £0.47 each. Packed in a plastic wallet with guide "How to Solder".

STAND S.T.3
High grade insulation material, chromium plated steel spring. Suitable for all our models. Replaceable sponges, space for spare bits. Complete £1.21 (0.24)

I enclose cheque/P.O./Cash (Giro No. 258 1000) _____
NAME _____
ADDRESS _____

Model X25

Point 1

Near-perfect insulation
Breakdown voltage 1500 A.C.
Leakage current 3.5 uA

Point 2

Top-efficiency in heat transfer.
Element slides inside the soldering bit
25 watts but equivalent in heat capacity to 60 watts

Point 3

Highgrade phenolic handle (own moulding!)
Stainless steel shaft
- 3 core 0.4 mm flexible lead.

Point 4


Iron-coated bits that do not stick to the shaft but slide on and off easily.
3 tip sizes 2.4, 3.2 and 4.7 mm.

Point 5

Price with standard (3.2 mm) bit £2.99 (0.22)
Spare elements £1.47
Spare bits £0.47 incl. VAT

Point 6

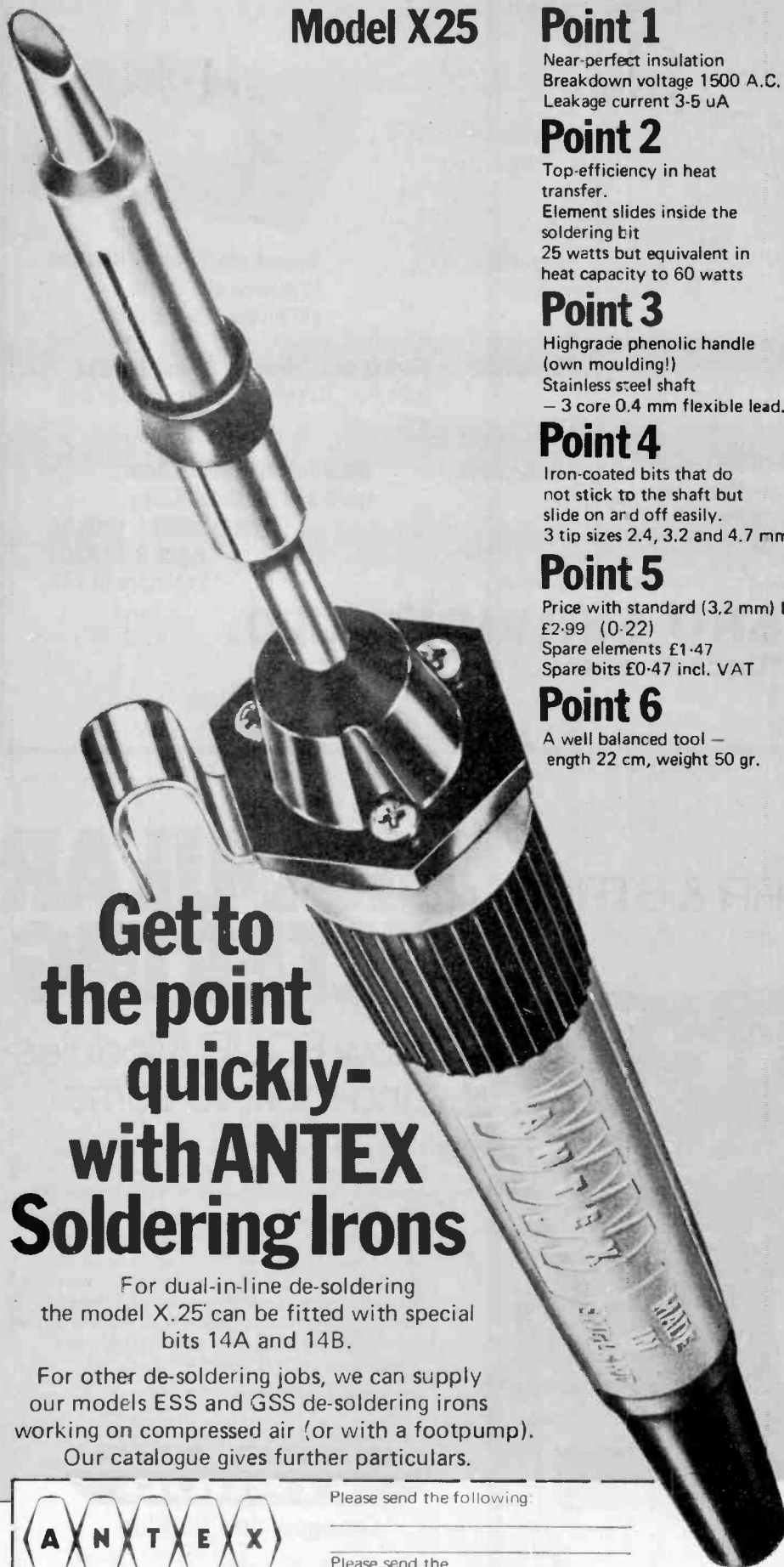A well balanced tool - length 22 cm, weight 50 gr.



Get to the point quickly - with ANTEX Soldering Irons

For dual-in-line de-soldering the model X.25' can be fitted with special bits 14A and 14B.

For other de-soldering jobs, we can supply our models ESS and GSS de-soldering irons working on compressed air (or with a footpump). Our catalogue gives further particulars.




Please send the following: _____
Please send the ANTEX colour catalogue.

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:
ANTEX LTD. FREEPOST, PLYMOUTH PL1 1BR (no stamp required) Tel. 0752 67377.

FAST RESPONSE STRIP CHART RECORDERS


Made in USSR

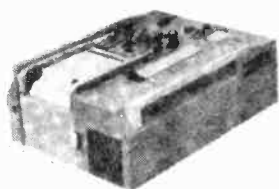

Type H3020-1
Single pen

Specification

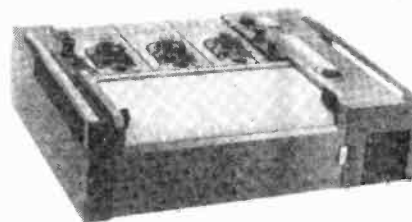Basic error 2.5%
 Sensitivity 8mA F.S.D.
 Response 0.2 sec.
 Width of each channel 80mm
 Chart speeds, selected by
 push buttons 0.1-0.2-0.5-1-2.5-
 -5-12.5-25mm/sec.
 Chart drive 200-250v 50Hz



Type H3020-3
Three-pen

Recording: Syphon pen directly attached to moving coil frame, curvilinear co-ordinates

Equipment: Marker pen, Timerpen, Paper footage indicator, 10 rolls of paper, connectors, etc.

Dimensions: H320-1: 285x384x16.5mm
 H320-3: 475x384x16.5mm

PRICE: H320-1 £108.00
 H320-3 £160.00
 Exclusive of VAT

Available for immediate delivery

Z & I AERO SERVICES LTD.

44A WESTBOURNE GROVE, LONDON W2 5SF

Tel. 01-727 5641

Telex: 261306

WW-066 FOR FURTHER DETAILS

BARR & STROUD

MODULAR FILTERING

EF3-04 Low Pass

Cut-off frequency variable from 0.1Hz to 100kHz

EF3-03 High Pass

Cut-off frequency variable from 0.1Hz to 100kHz

EF3-02 Low Pass

Cut-off frequency variable from 0.01Hz to 10kHz

EF3-01 High Pass

Cut-off frequency variable from 0.01Hz to 10kHz



EF3 Basic Main Frame

Now FOUR Modules—and more to come!

The introduction of our EF3 Electronic Filter System was a breakthrough in electronic filtering, a System with options and interchangeability.

Now we introduce two additional modules to extend the scope and versatility of the EF3. To appreciate fully the technical and economic merits of the EF3 System you ought to have our detailed literature which we will be pleased to send. Continuing development of the EF3 System means that we will be announcing yet more modules in the near future.

Send now for full details to:



Glasgow and London

Barr & Stroud Limited,
 1 Pall Mall East, London SW1Y 5AU.
 Tel: 01-930 1541 Telex: 261877

WW-065 FOR FURTHER DETAILS

A NEW DIMENSION IN SOLDERING

Iso-Tip Cordless Soldering Iron




Ideal for factory, field servicing, laboratory or home, the Iso-Tip Cordless offers a great advance in soldering. It is completely portable, heats in 5 seconds and recharges automatically in its own stand.

The Iso-Tip is powered by long-life nickel cadmium batteries giving tip performance up to 50 watts with a temperature of 370°C. Tips are available in five different sizes ranging from Micro to Heavy Duty to meet all soldering requirements.

Greenwood Electronics
Portman Rd, Reading RG3 1NE, England.
Telephone: Reading (0734) 595844.
Telex: 848659

WW-028 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

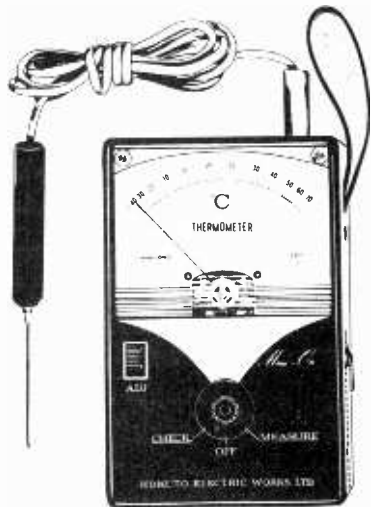

THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied with carrying case, Probe and internal 1 1/2 volt standard size battery.

- Model "Mini-Z 1" measures from -40° C to + 70° C
- Model "Mini-Z 2" measures from -5° C to + 105° C
- Model "Mini-on Hi" measures from + 100° C to + 500° C

PRICE £20.00 each (VAT 8% EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON),
138 GRAY'S INN ROAD, LONDON. WC1X 8AX
(Phone 01-837 7937)

WW-023 FOR FURTHER DETAILS

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 1/4" x 8 1/4" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.



£5.95

plus 50p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£3.95

plus 50p P. & P.

Offer Order both courses for the bargain price £9.25, plus 50p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises, Dept COM
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR
*Please send me set(s) of Design of Digital Systems at £6.45 each, p & p included

'or set(s) of Digital Computer Logic and Electronics at £4.45 each, p & p included

'or combined set(s) at £9.75 each, p & p included

Name

Address


.

.

*delete as applicable
No need to use a stamp — just print FREEPOST on the envelope

WW4

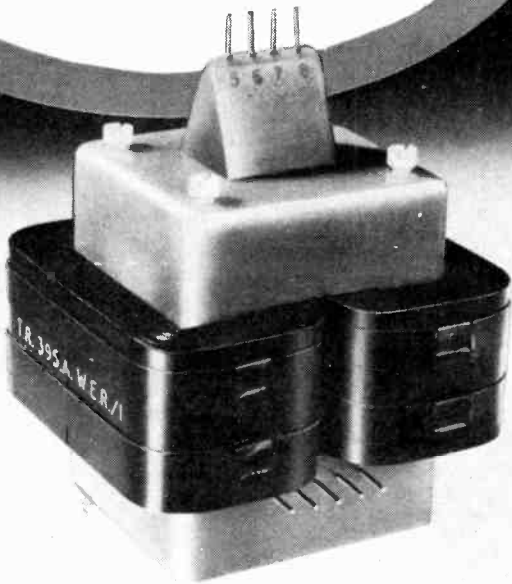"They want safety isolation for their voice band circuits"



One more request item. We met it with a neat little transformer. Now, in two versions, it joins the list of useful Whiteley products, and everyone involved in communications system design will be interested in the protection they provide. Inserted in voice band circuits, they effectively isolate equipment from the hazards of adjacent high voltage power circuits on the 'line' side. High isolation level between line and equipment windings gives protection against voltage surges, lightning strikes and fault conditions. One version is designed for 17Hz signalling circuits, the other with several voltage ratios also suits a 50Hz ringing circuit. All are Post Office and C.E.G.B. approved, and the second version is also approved with extra protection diodes added. Requests for data sheets welcome. Or if you want to request a product spec of your own — we're always interested!

Surprising how often you'll find

**Whiteley
make it.**


Whiteley Electrical Radio Co. Ltd
Mansfield, Notts NG18 5RW, England. Tel: 0623 24762.

WW-061 FOR FURTHER DETAILS

brenell

**PROFESSIONAL
TAPE TRANSPORTS**

and multi-channel electronics
for studio and industrial use

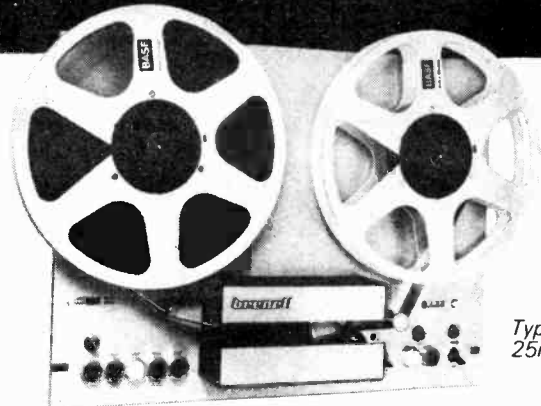

Type 19
25mm model

**Finance
available**

- * Tapewidths up to 25mm
- * Speeds: 3mm/s minimum up to 152cm/s max
2 and 4 speed models
- * Reel Capacity up to 29cm
- * Remote Control Facility
- * Tape Tension Control
- * Automatic Interlock against misuse
- * Special models to customer requirements

BRENELL ENGINEERING CO LTD

231-5 Liverpool Road, London N1 1LY. Tel: 01-607-8271


**HEPWORTH
ELECTRONICS**

Worcester Road, Kidderminster
Tel. 0562 2212 or 3

for

Quick, Clean, Low Cost, No Waste
Breadboarding:

THE SK10 Socket

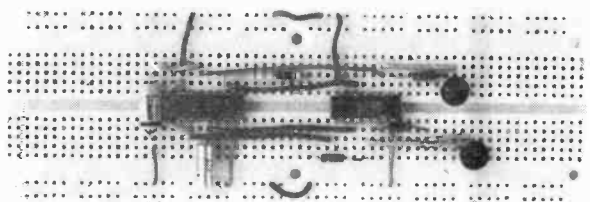

or its little brother the **SK50
Socket**. **SK50** Costs £6.95, the
SK10 Costs £12.07.

VAT and Postage extra or from London and South
East Distributors

ASPEN ELECTRONICS

18A High Street, Northwood, Middlesex
Tel. 27688

WW 035 FOR FURTHER DETAILS

Way out in front!


A great new line of RF-heating triodes from THOMSON-CSF:

- Output power from 100 to 800 kW.
- Superior PYROBLOC™ grids and HYPERVAPOTRON® anode cooling - the latest word in power-grid tube technology.

Specially designed for industrial thermal treatment and built using rugged metal/ceramic technology.

Get the latest advance in the power-grid tube state of the art from the RF-heating leader: THOMSON-CSF!

Contact us today.

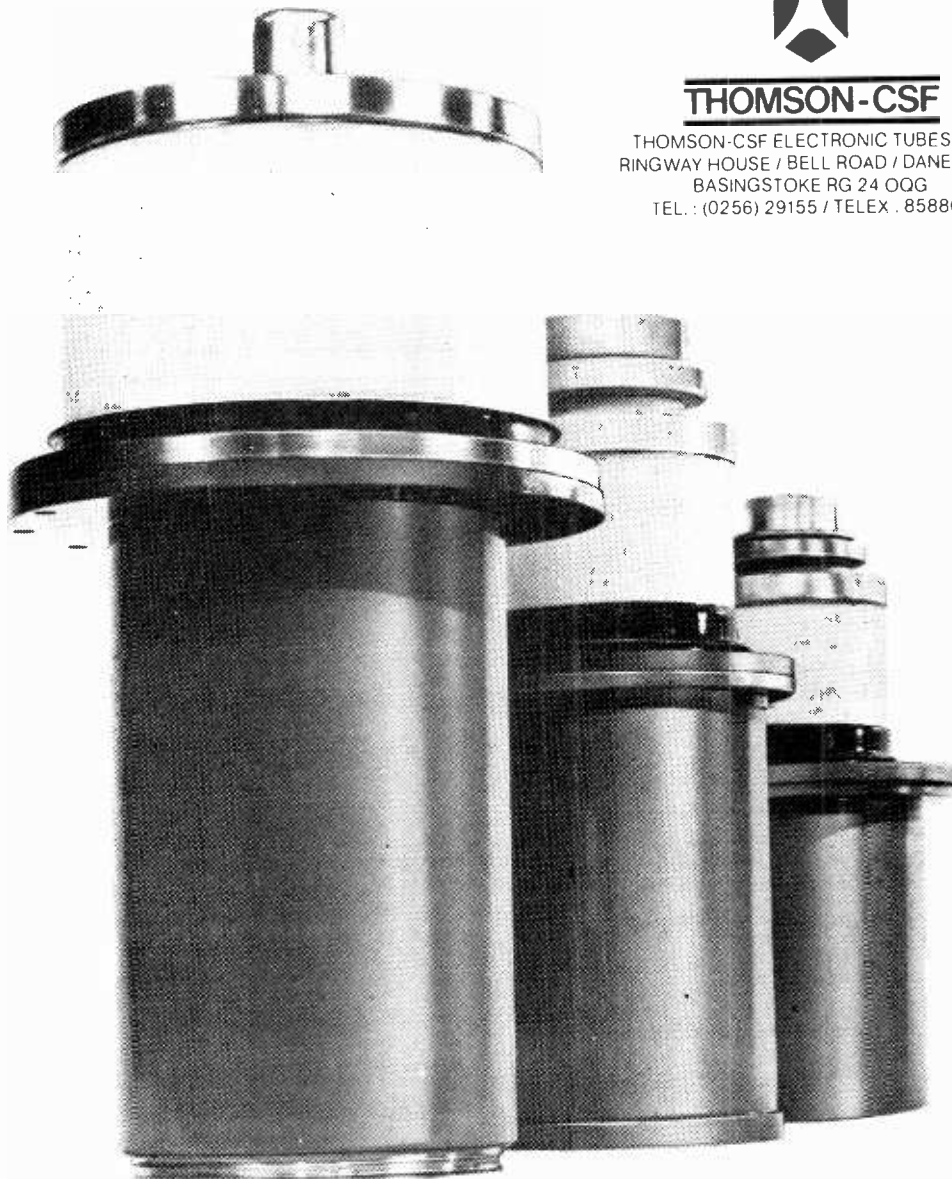

THOMSON-CSF

THOMSON-CSF ELECTRONIC TUBES LTD
RINGWAY HOUSE / BELL ROAD / DANESHILL
BASINGSTOKE RG 24 0QG
TEL. : (0256) 29155 / TELEX . 858865

LITTLE WONDER...THE MINITEST IS PREFERRED

The SEI MINITEST has made a remarkable impact in the pocket-sized multi-range meter market, by making itself a firm favourite with discerning people in the industry.

First, the appearance. Diminutive, neat, wipe-clean plastic cover with pressed steel case.

Controls are simple and easy to use.

Second, the range. The Minitest measures a.c.

and d.c. voltages d.c. current and resistance over 20 ranges to a sensitivity of 20,000 and 2,000 ohms per volt d.c. and a.c. respectively.


Third, High Voltage Probes. Will extend the range to 25kV or 30kV d.c. Ideal for T.V. sets and similar electronic equipment where source impedance is high. Little wonder the Minitest is preferred!

Edgecumbe (Peebles) Limited,
Main Street,
Bothwell,
Scotland.

Havant Instruments Ltd,
Instrument House,
2A Waterloo Road,
Havant, Hampshire

I.T.T. Electronic Services
S.T.C. Ltd.
Edinburgh Way,
Harlow, Essex CM20 2DF.

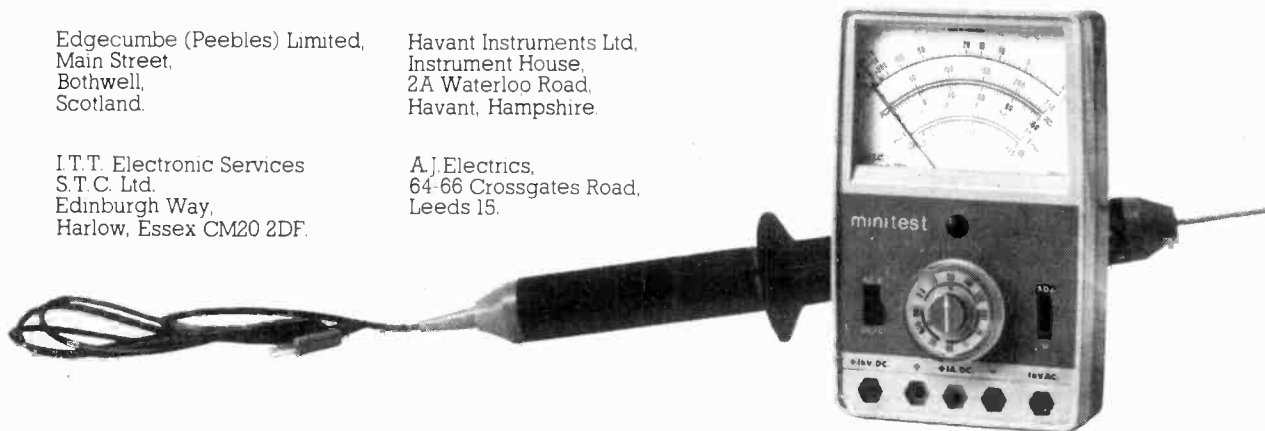A.J. Electronics,
64-66 Crossgates Road,
Leeds 15.



SALFORD ELECTRICAL INSTRUMENTS LIMITED

Peel Works, Barton Lane, Eccles, Manchester M30 0HL
Telephone: 061-789 5081. Telex: 667711

SEC


A member company of GEC Electrical Components Ltd

WW — 057 FOR FURTHER DETAILS

Switching problems? Rely on Zettler.

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

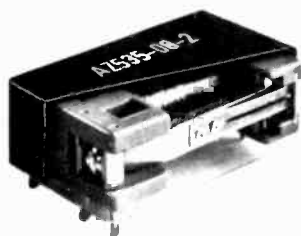Our product range comprises:
Low profile (platform) · Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping · Mains switching · Latching Contact stacks · Solenoids



Platform Relay AZ 535

for reliable insulation between signal and heavy duty circuits.
1 changeover.
Contact material: Silver cadmium oxide, or fine silver.
Printed circuit mounting (32.5 x 20 x 11 mm).
Coil voltages: 6 to 110 V DC.
Contact rating:
240 V max., 3 A max., 500 VA.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



ZETTLER Zettler
UK Division
Brember Road, Harrow, Middx. HA2 8AS
Tel. (01) 4220061

A member of the worldwide ZETTLER electrical engineering group, est. 1877

WW—006 FOR FURTHER DETAILS

DATA AND COMMUNICATIONS TERMINALS

Teletype 28, 32, 33, 35, 40
TermiNet 30, 300 & 1200 (30 and 120 cps)
Teleterm 1030 & 1132 (portable 30 cps
with integral coupler and RS 232C)
Other page printers (by Siemens, ITT Creed, etc.)
TermiNet 120 line printer

- ★ Spares, repairs, overhauls and maintenance
- ★ Other types and models available
- ★ Refurbished units also available
- ★ Short and long period rentals
- ★ Minicomputer interfaces
- ★ Quantity discounts
- ★ Immediate delivery


TELEPRINTER EQUIPMENT LTD.
70-80 AKEMAN STREET,
TRING, HERTS., U.K.

Telephone 0442-82-4011
Cables RAHNO Tring
Telex 82362
A/B Batelcom Tring



WW—009 FOR FURTHER DETAILS

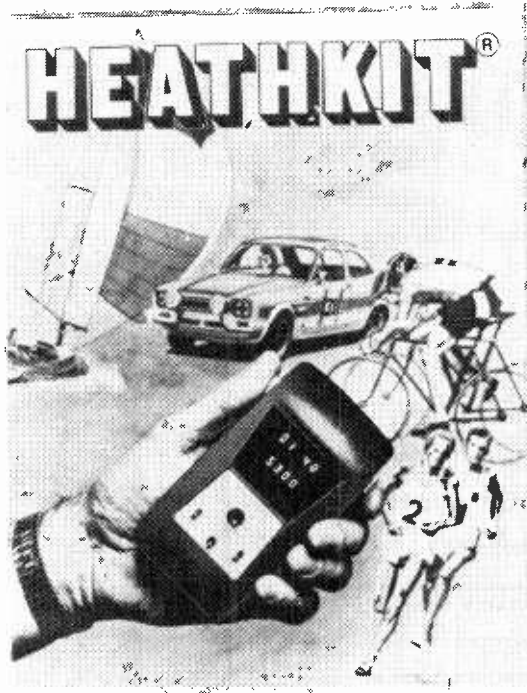Complete the coupon and we'll send you our complete, new catalogue.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now (enclosing a 10p stamp for postage) and we'll send you your copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.


Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

So, when you receive your catalogue you should have hours of pleasant reading. And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.


At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. W/W - 46 Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.


Digital electronic stop watch

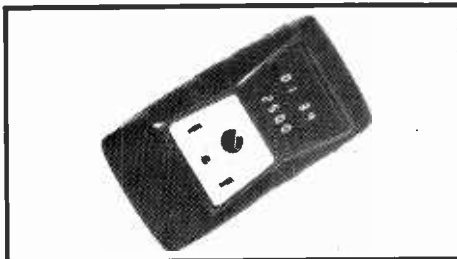

AM/FM 60 watt r.m.s. stereo receiver

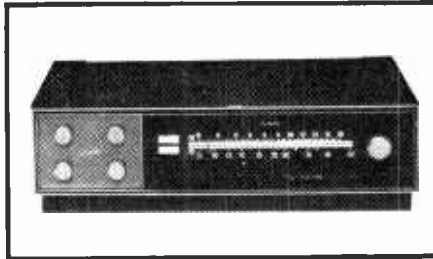

Digital rev counter

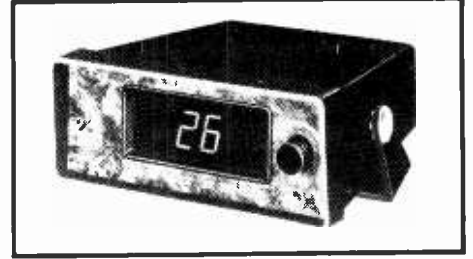

FREE
SOLDERING IRON
 WORTH
£3.50
 with all orders over £30

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. WW-46, Gloucester, GL2 6EE.
Please send me my Heathkit catalogue. I enclose a 10p stamp for postage.



Name _____ Address _____


Postcode _____

Full details in the catalogue. Offer available for limited period only.

EASY TERMS AVAILABLE
WITH HEATHKIT MONTHLY
BUDGET PLAN

ANADEX CF-700

1 GHz COUNTER FOR £475

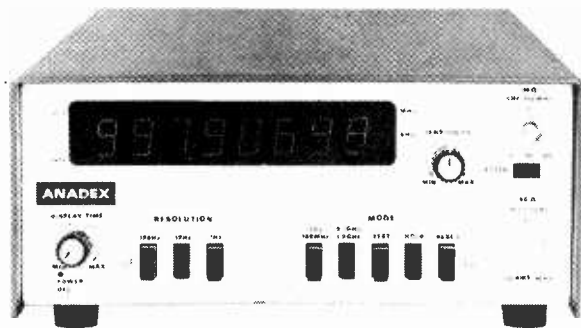

Features include:—

- ★ 1 GHz count rate with 1 Hz resolution
- ★ 30mv sensitivity with high overload capability
- ★ 8 digit 'SPERRY' display


Also: Model CF-710 giving 0.001 Hz resolution up to 10k Hz

aspen *electronics limited*

18a HIGH STREET, NORTHWOOD, MIDDX
HA61BN
TELEPHONE NORTHWOOD 27688

WW—034 FOR FURTHER DETAILS

GROOVAC

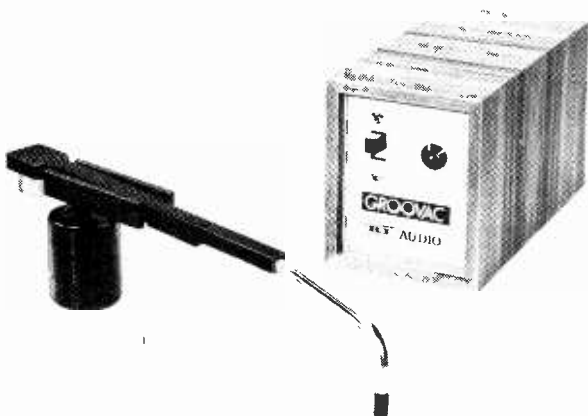

vacuum record cleaner

Vacuum cleaning is the best way to remove dust, especially fine dust. Now with the Groovac, vacuum cleaning is available for extracting the particles from inside record grooves which are responsible for record and stylus wear — while your record is playing.

For full details please write to:—

RI AUDIO

Kernick Road, Penryn
Cornwall TR10 9DQ, England
Telephone: Penryn 72753

WW—049 FOR FURTHER DETAILS

RADFORD

HIGH SENSITIVITY AUDIO VOLTMETERS AND NOISEMETERS

Four instruments are now available for the measurement of audio frequency signals including noise. They are derived from a basic battery operated voltmeter design having 16 measurement ranges from 10 μ V for full scale meter deflection to 300V f.s.d. The Voltmeter has a high input impedance and low inherent noise. It is fitted with a high grade meter having a 5" mirror scale of excellent linearity, calibrated in volts and dBV.

The Audio Voltmeter (HSV 1) become an Audio Noisemeter (ANM1) by the inclusion of frequency contouring networks having characteristics recommended by international organisations concerned with specifications and measurement standards as being suitable for the quantitative measurement of the subjective effect of noise in audio systems. The HSV 1 and ANM 1 instruments respond to the average or mean value of the waveform being measured and are calibrated in r.m.s. values on a sine wave.

In the HSV2 and ANM2 instruments an r.m.s. to d.c. converter module is incorporated which provides a true r.m.s. reading on waveforms with a crest factor in excess of 10. These instruments are also provided with an additional output socket giving 1.00V d.c. output corresponding to 1.00V at nominal full scale meter deflection to operate a chart recorder or d.c. digital voltmeter.

All the instruments are fitted with a socket to enable an external network of any weighting characteristic to be introduced in the measuring circuit. This extends the use of the instruments to vibration and acoustical measurement, as well as to the measurement of gramophone turntable rumble, f.m. receiver noise, etc.

Brief Specification:

Frequency response as Voltmeter: 4Hz to 500kHz \pm 0.5dB
Input impedance: 1M ohm shunted by 30pF
Attenuator accuracy: 0.25%
Meter scale linearity: 1%. Typically better than 0.5%
Waveform error in true r.m.s. instruments: 1% for crest factor 10
Noisemeter included weighting characteristics: Wide band (flat response as voltmeter), DIN, 'Audio Band', IEC/DIN. Curve 'A', and CCIR.

Size: 11 1/4" x 7 1/4" x 8 1/2" deep overall

HSV1	Audio Voltmeter. Average reading	£125.00
HSV2	Audio Voltmeter. True r.m.s. reading	£175.00
ANM1	Audio Noisemeter. Average reading	£150.00
ANM2	Audio Noisemeter. True r.m.s. reading	£200.00

Please write or phone for descriptive leaflet giving details of the design and full performance characteristics of the above instruments, together with a reprint copy of Dolby Laboratories Inc. Engineering Field Bulletin No. 19/2 — 'Noise Measurement on Consumer Equipment'

RADFORD LABORATORY INSTRUMENTS LTD.
Ashton Vale Road, Bristol, BS3 2HZ. Telephone 0272
662301

WW—089 FOR FURTHER DETAILS

EXCLUSIVE — WORLDBEATING

**DIGITAL ALARM
CLOCK KIT★**



NON-ALARM £14 INC. VAT, ETC.

£15

INCL. VAT & DEL.

★ Or Ready Built & Tested £21.50



TEAK Case 70p extra

- Built-in Alarm
- Photo cell controlled brightness
- AM / PM Indicator
- Giant 0.5" LED Display
- 12 / 24 hr. mode
- Mains failure ind.
- Tilt Snooze Sw.
- Separate alarm Control Sw.
- 9 min. Snooze
- No knowledge of electronics to build kit


CWO, PULSE ELECTRONICS, DEPT. WW11, 202 SHEFFORD RD., CLIFTON, SHEFFORD, BEDS.
S.A.E. for complete price list

ELECTRONORGTECHNICA

carbon film

RESISTORS

1/8 and 1/4w 70°C 5% tol. E.12

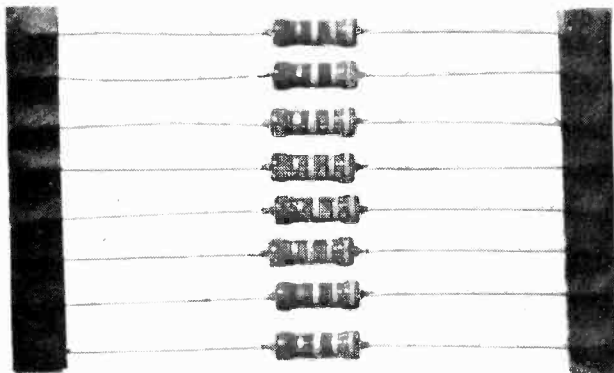

EX-STOCK

£4.00 PER 1,000 PLUS V.A.T.
OF ONE VALUE

Contact John Gingell



AERO SERVICES LTD.

44A Westbourne Grove
London W2 5SF
TEL: 01-727 5641 TELEX 261306

WW-059 FOR FURTHER DETAILS

Reed Relays

**1-10,000 for same
day shipment**

Prices from 49p 100 rate

Military grade-
ask for NATO conversion list


Custom design specials-
7-10 days for samples

15 years experience

**Equivalents to most European
& U.S. type available**

Erg Components Telephone: 0582-62241
Luton Road, Dunstable, Bedfordshire, LU5 4LJ England.

WW-062 FOR FURTHER DETAILS

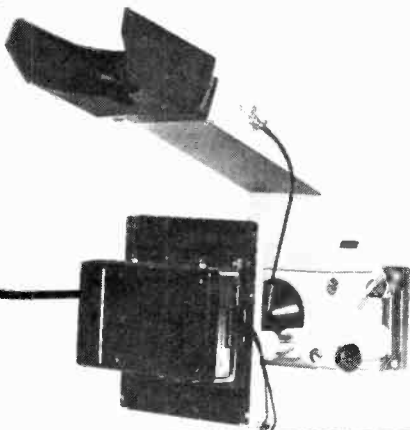

Telford Oscilloscope cameras

Type A modular system with widest range of film backs, lenses, viewing systems and adaptors to meet virtually all requirements.

Plus inexpensive Type P (prices from £50) utilising coaterless Polaroid® film and 'Robot' with economical 35mm film for continuous feed.

More complete details available on request from:

©Reg. Trade Mark.


Telford PRODUCTS LTD.

WADSWORTH ROAD PERIVALE GREENFORD MIDDX. ENGLAND Telephone: 01-998 1011 Telex: 935524

DAVALL A MEMBER COMPANY OF BENTIMA INDUSTRIES LIMITED

WW-012 FOR FURTHER DETAILS

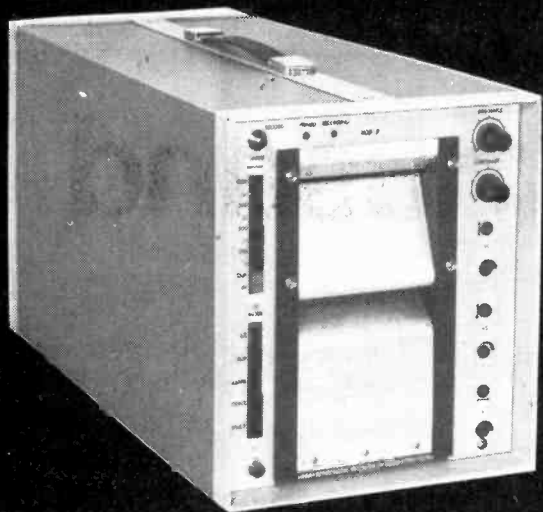THE WORLD'S LOWEST COST FIBRE OPTIC RECORDER



Introduced to meet the demand for a simple, high quality, FOR for those who do not require full recording oscilloscope capabilities; the FOR-7 has a *rectangular* CRT which provides strip chart, X-Y plot and single frame recording on low cost paper.

WIDEBAND BRILLIANCE MODULATION
-for video imaging with *good grey scale*

HIGH FREQUENCY DEFLECTION AMPLIFIERS
-for trace recording with *faithful transient response*

VARIABLE SENSITIVITY AND POLARITY REVERSAL
-for *easy interfacing* with displays and systems

BENCH, RACK OR BUILD-IN VERSIONS
-for general purpose laboratory or *OEM applications*

For further information or a demonstration of the FOR-7 or any other Medelec unit please contact:

MEDELEC LIMITED . Woking . Surrey GU22 9JU
Tel: Woking (048 62) 70331 Telegrams: Medelec Woking


From the Leaders in
Fibre Optic Recording

medelec



WW 008 FOR FURTHER DETAILS

TAKE A CLOSE LOOK

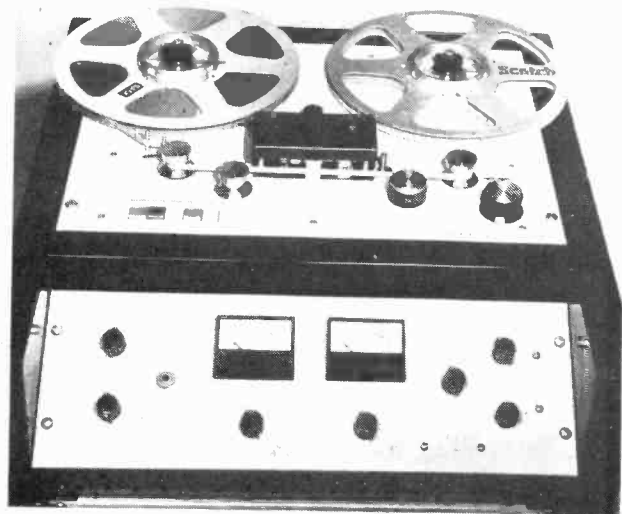

at a professional recorder that offers high performance, excellent reliability and is very easy to maintain. Ask yourself why so many commercial radio stations and recording studios are doing their best to wear them out, and not having much success. Decide if you need mono or stereo, console transportable or rack mounting versions and then inquire about prices.

We are sure you will be very pleasantly surprised.

LEEVERS-RICH EQUIPMENT LTD.
INC. BIAS ELECTRONICS

319 TRINITY RD., LONDON, SW18 3SL

01-874 9054

WW-052 FOR FURTHER DETAILS

servos synchronous steppers dc motors



gearboxes and control systems



Stockists for **IMPEX** Motors

McLennan

McLENNAN ENGINEERING LIMITED

Kings Road Crowthorne Berks Telephone: Crowthorne 5757/8


WW-041 FOR FURTHER DETAILS

PETITE PRECISION!

A 12V DC POWER TOOL FOR THE DESIGN AND RESEARCH ENGINEER
AVAILABLE IN KIT FORM OR SEPARATES

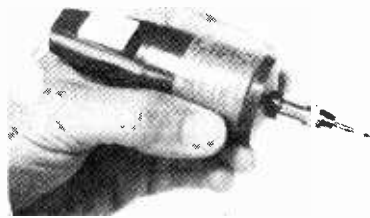EXAMPLE OF FRENCH PRECISION ENGINEERING.

Diameter 33mm
Weight 160g
Length 125mm
Torque 120cmg
RPM
approx. 10,000
at 12V DC
Power 9/14V DC
Batteries
or AC/DC
transformer



Flexible drive.
£5.00
P&P 25p
Now in use by the following:
GPO, BBC, Atomic Energy
Authority, British Nuclear
Fuels, Weekend TV, Ministry
of Defence, Hospitals,
Opticians, etc.



Stand £3.76
P&P 35p

UK DISTRIBUTOR
PRECISION PETITE LTD
119A HIGH STREET
TEDDINGTON, MIDDX. UK
TEL. 01-977 0878
SAE for leaflets, price list and order form

NEW IMPROVED MARK II

£8.00 P&P 35p

Bridge in a thousand




One part in one thousand is the accuracy of Universal Bridge B224 from 10 ohms to 1 gigohm, 0.1pF to 10 microfarads and 1 nanomho to 100 millimhos. Monitor its 1592Hz source frequency and also get 0.1% from 1mH to 10kH. With reducing accuracy, coverage extends above and below the ranges quoted, on R, C, G and L. Resistive and reactive terms read simultaneously. Sockets for 200Hz—50kHz operation. Internal rechargeable battery. Many other valuable features detailed in Data Sheet B224.

WAYNE KERR

A member of the Wilmot Breedon group

For more information phone Bognor (02433) 25811, or write to Wayne Kerr, Durban Rd., Bognor Regis, Sussex PO22 9RL

WW-011 FOR FURTHER DETAILS

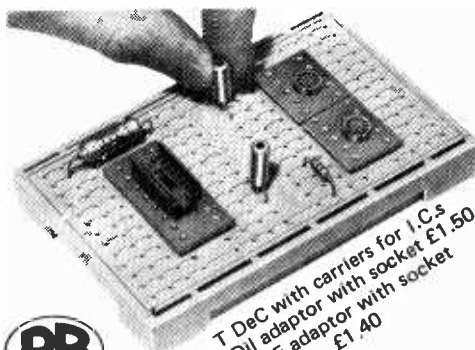

FREE SUPER SOLDER BOARD WITH EVERY DEC BUILD CIRCUITS EASILY PUSH COMPONENT-IN NO SOLDERING

Designing circuits is easy with DeCs, just plug in your components. Each DeC breadboard is complete with step-by-step instructions. When circuit is designed, take components out and use them again OR plug components into SUPER SOLDER BOARDS for a perfect, finished P.C.B.

TO P. B. Electronics (Scotland) Ltd., 57 High Street, Saffron Walden, Essex. Please find enclosed P.C./Cheque value £

- _____ S-DeCs + Free Super Solder Board £1.80
- _____ T-DeCs + Free Super Solder Board £3.87 } Includes postage + VAT.
- _____ U-DeCA + Free Super Solder Board £4.31

FULL POSTAL ADDRESS

Allow 21-28 days delivery.

2452



P.B. Electronics (Scotland) Ltd.,
57 High Street, Saffron Walden, Essex.
Tel: Saffron Walden (0799) 22876.

WW-077 FOR FURTHER DETAILS



sound equipment
by **Grampian**

GRAMPIAN REPRODUCERS LTD. HANWORTH TRADING ESTATE FELTHAM, MIDDLESEX TELEPHONE 01-894 9141

WW-027 FOR FURTHER DETAILS

nombrex



MODEL 40
WIDE RANGE AUDIO GENERATOR
£42.49 + VAT

- ★ 4 RANGES, 10Hz-100 KHz.
- ★ SINE AND SQUARE WAVE OUTPUT.
- ★ DUAL CALIBRATED ATTENUATOR.
- ★ STABILIZED OUTPUT LEVEL 1 V.

*Trade and Export enquiries welcome
Send for full technical leaflets
Post and packing £1 00 extra*

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET
NEWTON ABBOT, DEVON TQ12 1NE
Tel. Newton Abbot 68297**

WW-021 FOR FURTHER DETAILS

**QUARTZ
CRYSTALS
-FAST!**



AEL GATWICK HOUSE, HORLEY, SURREY, ENGLAND
Tel: Horley (02934) 5353
Telex: 87116 (Aerocon Horley) Cables: Aerocon Telex Horley

WW-039 FOR FURTHER DETAILS

**Your choice of
Live Sockets-
Instantly!**

A Lexor DIS-BOARD gives you up to 6 sockets from one power outlet. Portable or permanent fixing, compact units, with safety neon. Over 1,000 socket combinations available from stock. All types of fittings and finishes

Brochure from
LEXOR DIS-BOARDS LIMITED
Allesley Old Road, Coventry
Telephone 72614 or 72207



WW-051 FOR FURTHER DETAILS

In a range of multimeters with pointers whats the point of one without



SEE US ON
STAND No.4306
HALL 4
IEA-ELECTREX

The point is that for some applications, a digital indicator makes a lot of sense. That's why AVO makes the the Digital Avometer DA 114. It offers you a choice of DC, AC and resistance ranges at high accuracy. High input impedance, comprehensive built-in calibration check facilities, two versions—one for mains operation, the other with built-in rechargeable battery and mains operation.

It offers you the best of the traditional AVO features—reliability, ruggedness, range, repairability, readability and, perhaps above all, AVO accuracy. Plus the best of the new generation multimeters.

As you can imagine, our designers took a long hard look at digitals before they produced a Digital Avometer. For instance, they realized that the displays on some digital meters could be a positive nuisance in many applications. After all, you don't always need accuracy to the 'nth degree—so where you'd normally just glance at an analogue pointer you could find yourself screwing your eyes up at a diminutive and

faintly glowing digital. A few hours of that and the average engineer would be begging for the return of his old analogue meter.

That's why we gave the DA 114 numerals big and bright enough to read across a room. And it's the reason that AVO, while producing one of the few 'serious' digital multimeters, still produces what is probably the widest range of analogue multimeters for the electronics engineer.

The AVO range for Electronics Engineers includes Model 8 Mk 5, Model 72, and the high impedance models EM 272 and EA 113.



For full details of the range, contact your distributor or write to:


AVO Limited, Archcliffe Road, Dover,
Kent. CT17 9EN. Telephone: Dover
(0304) 202620. Telex: 96283

Thorn Measurement Control and Automation Division

WW — 102 FOR FURTHER DETAILS



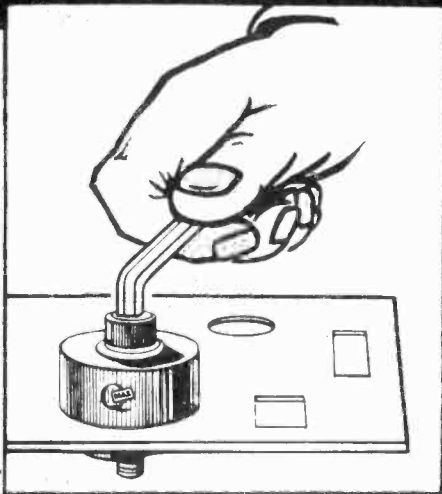SHEET METAL PUNCHES FOR QUICK CLEAN HOLES



- Easiest and quickest way of punching holes in sheet metal (up to 1.625mm).
- Simple operation ● **100% British**
- Burr-free holes — no jagged edges
- **57 Metric and Linear sizes** (Lists on application)


Used all over the world by: Government services — Atomic, Military, Naval, Air, G.P.O. and Ministry of Works; Radio, Motor and Industrial manufacturers, Plumbing and Sheet Metal Trades, Garages, etc.

Obtainable from leading tool factors
Wholesale & Export enquiries to:

"Q·MAX"(ELECTRONICS)LTD
44 PENTON STREET · LONDON N19QA Tel: 01-278 2500

WW—007 FOR FURTHER DETAILS

TPA SERIES - D integrated circuit power amplifier

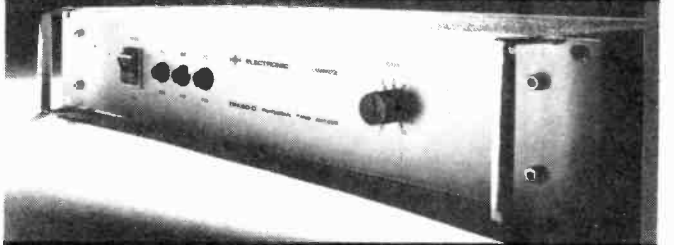

TPA 50 - D Specification

Power Output	100 watts rms into 4 ohms 65 watts rms into 15 ohms
Freq Response	±0.1dB 20Hz to 20KHz into 15 ohms. -1dB at 150KHz
Total harmonic distortion	Less than 0.04% at all levels up to 50 watts rms into 15 ohms
Input sensitivity	0dBm
Noise	-100dB
Rise time	2 u seconds
Price	£77 plus V.A.T.

100V Line (C.T.) and balanced inputs available.


For full technical information contact:

H|H ELECTRONIC

CAMBRIDGE ROAD, MILTON, CAMBS
TELEPHONE CAMBRIDGE 65945/6/7

WW—025 FOR FURTHER DETAILS

Test Equipment

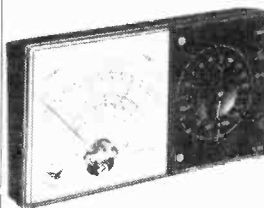

Multimeters


The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment

NAME

ADDRESS

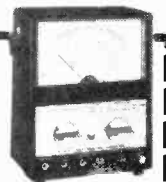

Eagle International Ltd., Precision Centre, Heather Park Drive, Wembley HA0 1SU
Tel(01)-902 8832


Eagle

WW

WW—029 FOR FURTHER DETAILS

FREQUENCY COUNTERS

HIGHER PERFORMANCE INSTRUMENTS FROM 1/10 Hz to 1.2 GHz. MEASURING FREQUENCY, PERIOD, TIME, FREQ./RATIO AND CALIBRATED OUTPUT FACILITY. FAST DELIVERY.

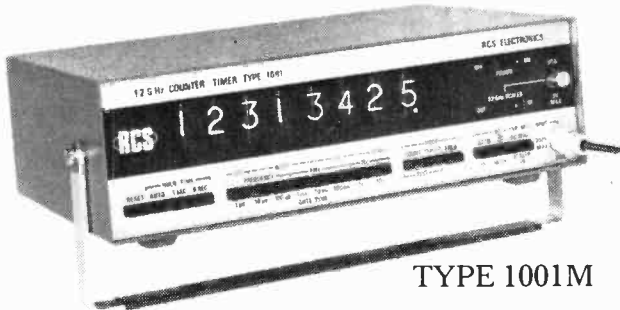

TYPE 1001M

CRYSTAL OVEN
OPERATING MANUAL
TWO TONE BLUE CASE

£670 **1.2** GHz

Sensitivity 10mV. Stability 5 parts 10.¹⁰

301M	32MHz 5 Digit £78	401	32MHz 6 Digit £121
501	32MHz 8 Digit £178	701A	80MHz 8 Digit £195
801A/M	300MHz 8 Digit £305	901M	520MHz 8 Digit £3.75
801B/M	250MHz 8 Digit £262	1001M	1.2GHz 8 Digit £670

Start/Stop versions plus £12

Memory versions available if not suffixed M £25 extra

Type 101 1MHz 100KHz Crystal Standard £80


Type 103 Off/Air Standard £78

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Dept., Crystal Manufacturers and Electronic Laboratories world-wide



R.C.S. ELECTRONICS
NATIONAL WORKS, BATH ROAD
HOUNSLOW, MIDDX. TW4 7EE
Telephone: 01-572 0933/4

WW-095 FOR FURTHER DETAILS

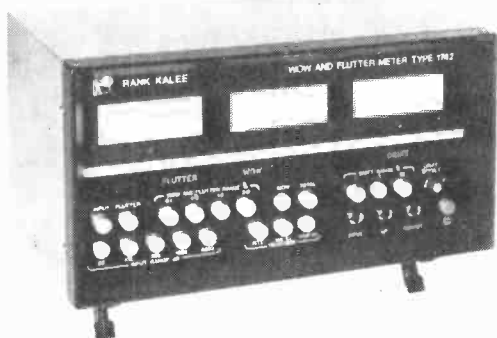

The new Rank

WOW & FLUTTER Meter Type 1742

Fully transistorised for high reliability

Versatile

Meets in every respect all current specifications for measurement of Wow, Flutter and Drift on Optical and Magnetic sound recording/reproduction equipment using film, tape or disc

High accuracy

with crystal controlled oscillator

Simple to use

accepts wide range of input signals with no manual tuning or adjustment

Two models available:

- Type 1742 'A' BS:4847: 1972 DIN 45507 CCI:R 409-2 Specifications
- Type 1742 'B' BS:1988: 1953 Rank Kalee Specifications

For further information please address your enquiry to Mrs B. Nodwell

Rank Film Equipment, PO Box 70
Great West Road, Brentford
Middlesex TW89HR


Tel: 01-568 9222 Telex 24408 Cables Rankaudio Brentford



RANK FILM EQUIPMENT


WW-056 FOR FURTHER DETAILS

LABORATORY POWER SUPPLIES

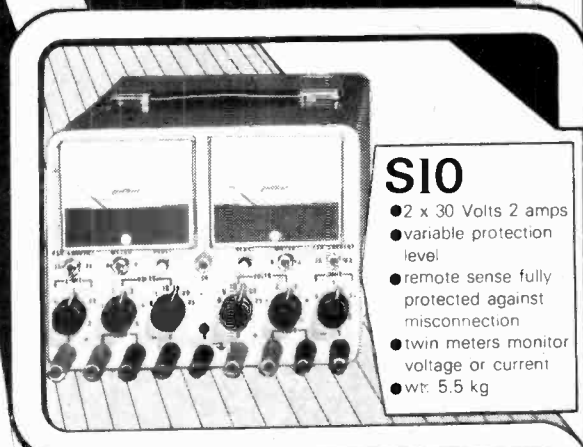

S10

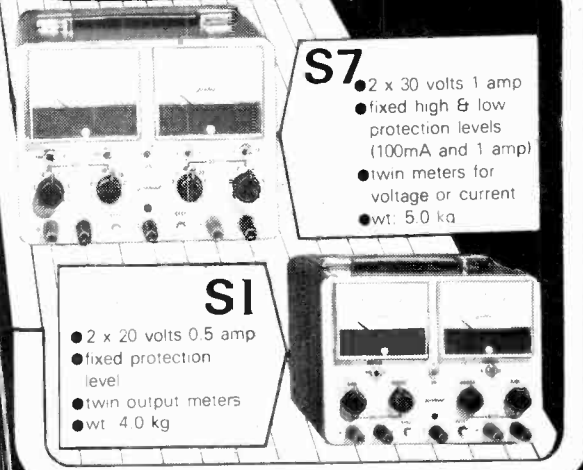- 2 x 30 Volts 2 amps
- variable protection level
- remote sense fully protected against misconnection
- twin meters monitor voltage or current
- wt: 5.5 kg



S7

- 2 x 30 volts 1 amp
- fixed high & low protection levels (100mA and 1 amp)
- twin meters for voltage or current
- wt: 5.0 kg

S1

- 2 x 20 volts 0.5 amp
- fixed protection level
- twin output meters
- wt: 4.0 kg

'S' RANGE

STABILISED TWIN POWER SUPPLIES TO 30V AT 2 AMP

LINSTEAD

MANUFACTURING CO. LTD.
ROSLYN ROAD LONDON N15 5JB
01 - 802 5144

MAIN AGENTS

- IRELAND:** LENNOX LTD, P.O. BOX 212A, DUBLIN 2
- DENMARK:** SCANFYSIK AB, 13/15 HJORRINGGADE DK-2100, COPENHAGEN
- SWEDEN:** EMI SVENSKA AB TRITONVAGEN 17, FACK S-171 19 SOLNA 1
- NORWAY:** EMI NORSK AS POSTBOKS 42, KORSVOLL, OSLO 8
- MALAYSIA:** LEC Sdn Bhd, P.O. BOX 60, BATU-PAHAT.
- SOUTH AFRICA:** PROTEA (PTY), 38 FARADAY STREET, JOHANNESBURG.

WW-054 FOR FURTHER DETAILS

AEL 3030

The AEL 3030 is a compact, fully solid-state 150 watt PEP output Transmitter-Receiver covering 2.16 MHz on 4 or 6 channels.

Rugged construction for today's tough environments. Easily accessible for simple maintenance.

Ten plug-in modules give maximum insurance against loss of service.

The advanced technology used in the AEL 3030 provides unmatched efficiency in point to point or mobile communication, minimises size and cost and maximises reliability!

DESIGNED FOR RELIABILITY



For further information and colour brochure write to:

AEL GATWICK HOUSE
HORLEY, SURREY, ENGLAND
TELEPHONE HORLEY (02934) 5353

Telex 87116 (Aerocon Horley)
Cables Aerocon Telex Horley

WW085—FOR FURTHER DETAILS

SOUND INSTALLATIONS

Design, installation and commissioning of recording and broadcast studios, sound reinforcement equipment, theatre communication and other systems.

SOUND EQUIPMENT

Supply and, where required, manufacture of equipment to customers' specifications.

We also specialise in television, lighting and other systems.

PHILIP DRAKE ELECTRONICS LTD.
165 LANCASTER ROAD, NEW BARNET, HERTS.
Telephone: 01-445 1144

WW—080 FOR FURTHER DETAILS



Audio Connectors

Broadcast pattern jackfields, jackcords, plugs and jacks.

Quick disconnect microphone connectors
Amphenol (Tuchel) miniature connectors with coupling nut.

Hirschmann Banana plugs and test probes
XLR compatible in-line attenuators and reversers.

Low cost slider faders by Ruf.




Future Film Developments Ltd.
90 Wardour Street
London W1V 3LE
01-437 1892/3

WW—070 FOR FURTHER DETAILS

SPECIALISTS IN COIL AND TRANSFORMER WINDING:

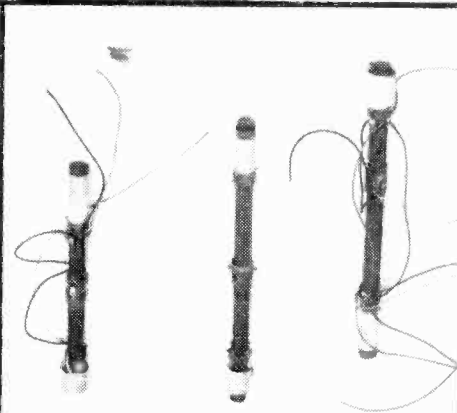Torroidal: c core: high speed high turn bobbin winding: chokes and wave winding
any quantity, any rating.




Send for new catalogue.



27 STATION ROAD
BRIMINGTON
CHESTERFIELD
DERBYSHIRE, ENGLAND
TEL: 0246 70297/8/9
TELEX 54284

WW—004 FOR FURTHER DETAILS

JES AUDIO INSTRUMENTATION

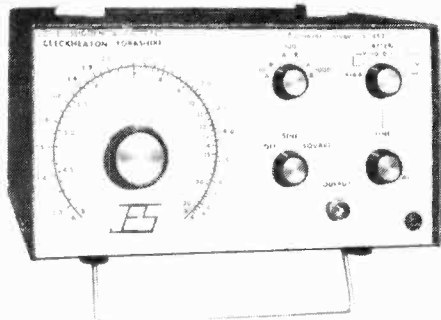

Illustrated the Si453 Audio Oscillator

SPECIAL FEATURES:

- ★ very low distortion content—less than 0.03%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£50.00

also available

Si451 Millivoltmeter

- ★ 20 ranges also with variable control permitting easy reading of relative frequency response

£50.00

Si452 Distortion Measuring Unit

- ★ low cost distortion measurement down to 0.01% with comprehensive facilities including L.F. cut switch, etc.

£40.00


ALL PRICES PLUS VAT

J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, W. YORKS. BD19 5LA.

Tel. 0274-872501

WW—032 FOR FURTHER DETAILS

HIGH POWER DC-COUPLED AMPLIFIER

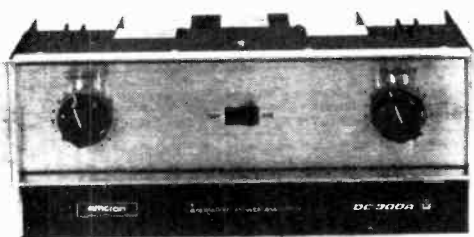

- ★ UP TO 500 WATTS RMS FROM ONE CHANNEL
- ★ DC-COUPLED THROUGHOUT
- ★ OPERATES INTO LOADS AS LOW AS 1 OHM
- ★ FULLY PROTECTED AGAINST SHORT CCT, MISMATCH, ETC.
- ★ 3 YEAR WARRANTY ON PARTS AND LABOUR

The DC300A Power Amplifier is the successor to the world famous DC300 which is so widely used in Industrial, and Research applications in this country. It is DC-coupled throughout so providing a power bandwidth from DC to over 20,000Hz. The ability of the DC300A to operate without fuss into totally reactive loads while delivering its full power, and maintaining its faithful reproduction of Pulse or complex waveforms has established the DC300A as the world's leading power amplifier. Each of the two channels will operate into loads as low as 1 ohm, and the amplifier can be rapidly connected as a single ended amplifier providing over 650 watts RMS into a 4 ohms load, and still providing a bandwidth down to DC. Below is a brief specification of the DC300A, but if you require a data sheet, or a demonstration of this fine equipment please let us know.

Power Bandwidth	DC-20kHz @ 150 watts + 1db. - 0db.	Slewing Rate	8 volts per microsecond
Power at clip point (1 chan)	500 watts rms into 2.5 ohms	Load impedance	1 ohm to infinity
Phase Response	+0. - 15° DC to 20kHz. 1 watt 8Ω	Input sensitivity	1.75 V for 150 watts into 8Ω
Harmonic Distortion	Below 0.05% DC to 20kHz	Input Impedance	10K ohms to 100K ohms
Intermod. Distortion	Below 0.05% 0.01 watt to 150 watts	Protection	Short. mismatch & open cct. protection
Damping Factor	Greater than 200 DC to 1kHz at 8Ω	Power supply	120-256V, 50-400Hz
Hum & Noise (20-20kHz)	At least 110db below 150 watts	Dimensions	19" Rackmount, 7" High, 9 1/4" Deep
Other models in the range: D60 — 60 watts per channel		D150 — 150 watts per channel	



MACINNES LABORATORIES LTD


**MACINNES HOUSE, CARLTON PARK INDUSTRIAL ESTATE,
SAXMUNDHAM, SUFFOLK IP17 2NL
TEL: (0728) 2262 2615**

WW—086 FOR FURTHER DETAILS

Drill with 20 tools. FREE. Super Solder Board with every DeC.



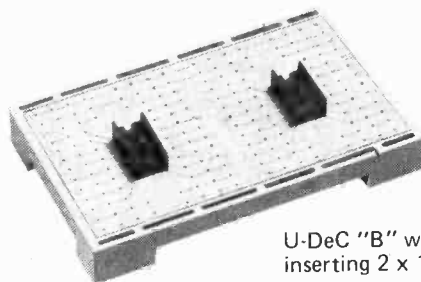PB Reliant drill kit 9000 RPM drill with 20 assorted tools only **£9.40** inclus. post + VAT.



U-DeC "B" with sockets for inserting 2 x 16 DIL Packages.

Building Circuits? IC or Discreet? Use DeC Breadboards. No soldering. 208 Contact points. Step by step instructions. Build hundreds of circuits. Use components over and over again. U-DeC "B" **£6.99** inclusive of postage and VAT.




P.B. Electronics (Scotland) Ltd.
57 High Street, Saffron Walden, Essex, CB10 1AA.
Tel: 0799 22876.

All stockists of DeC Breadboards please note PB are the manufacturers and suppliers, please send all orders, communications direct.

WW—073 FOR FURTHER DETAILS

Alice Broadcasting STM6

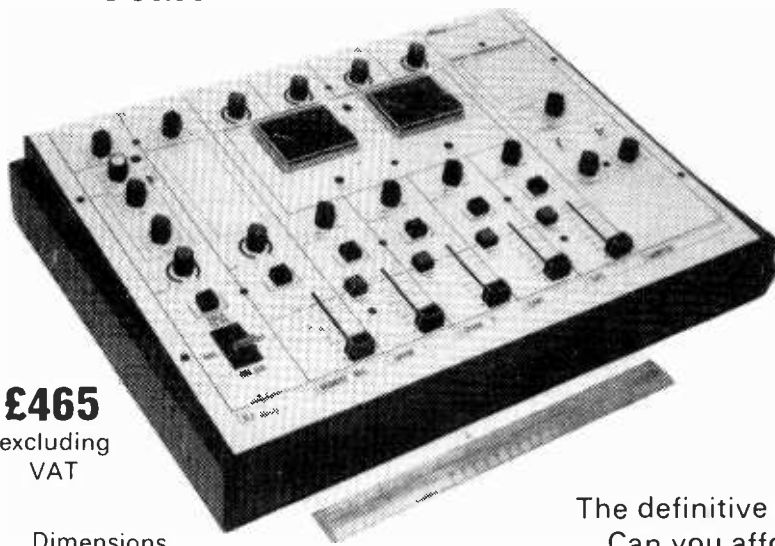

£465

excluding
VAT

Dimensions
20" x 15" x 4½"

Six Channel Stereo Transmission Mixer (ALICE'S BABY)

INPUTS

Microphones
Lines/Tape/Carts
Pick-ups
Off Air

OUTPUTS

Lines
P.A.
Headphones
Recording

The definitive DJ/OB/Production Mixer
Can you afford to use anything use?

Contact Chris Walden on Windsor 51056/7


ALICE (STANCOIL LTD.), 38 ALEXANDRA ROAD, WINDSOR, BERKS, ENGLAND

Also available from Roger Squires, London and Manchester

WW-045 FOR FURTHER DETAILS

tecknowledgery in consumer ICs - and their applications.

SGS Audio ICs

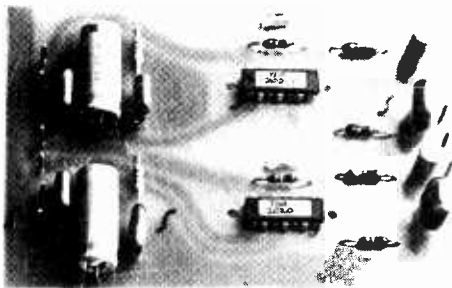

The much heralded TDA2020 is here. And just to make sure that you don't go wrong, so is the SGS application test circuit PCB for a stereo 15 + 15 (RMS) Hi Fi amplifier.

Prices :	IC	AUDIO	DISCRETES
TBA810AS	+HS 1.09	ZTX107/8/9	14p
TCA940E	+HS 1.80	ZTX413(LN)	17p
TDA2020	2.99	ZTX212/3/4	16p
FM LINEAR	ICS	BD 535 npn	7A/60v 52p
MC1350	0.70	BD536 pnp	53p
CA3089	+QC 1.94	BD377 npn	3A/50v 29p
TBA120	+QC 1.00	BD378 pnp	32p
MPX LINEAR	ICS	BD515 npn	2A/45v 27p
MC1310P	+LED 2.20	BD516 pnp	30p
CA3090AQ	+LED 3.75	BD609 npn	10A/90v 70p
		BD610 pnp	102p

We've moved

To accommodate expanded R & D facilities, AMBIT has moved sales and administration to 25 High St. Brentwood. The existing 37 High Street premises are retained for the engineering activities.

One of the first products of this move has been the development of a TV sound tuner, from an "off air" system, using its own varicap UHF TV tuner, with ICIF amplifiers and block filters by TOKO. And then one of our best ever circuits - an electronic touch tuner, with scanning mode, and facilities for 6 preset stations. The unit is suitable for use with FM, and now AM of course, and offers a complete tuner system without any moving parts. Selection is by means of touch tuning in all cases, with manual scan and preset switching automatically interlocked.

Our R&D facilities are available for general consultancy to OEMs: further details on application. Standard project estimation fee, including project evaluation comment data is £15.00 payable in advance.


Modules & Kits

New modules:

8011	Totally touch tuned varicap controller built	£14.99.
8005	Larsholt tuner set accessory unit, with pilot tone filter and audio stages, rectifier, IC stabilizer, meter driver circuits. £4.99 (kit)	
8001	55kHz low pass filter (mpx birdy filter)	£2.35 built £1.75 (kit)
2001	Stereo scratch and rumble filter, with continuously variable operating frequencies.	£5.80 (built) £4.60 (kit)
3000	Stereo control preamp - a wide dynamic range, low distortion AF preamp, with vol, bal, bass and treble controls. kit	£5.78
2020k	The TDA2020 stereo amp kit photographed on the left.	£7.85
7700	TV off air UHF sound tuner - built	£26.00 (4 preset stations)
9000 kit	AM/FM mpx tuner chassis, with mech. tuner	£17.50
7004 kit	MW/LW varicap tuner module, inc. ferrite rod	£9.95
7252	HiFi MOSFET FM tuner module by Larsholt	£24.00
7253	HiFi FET FM tuner module inc decoder	£24.00
5600	Hi Q MOSFET varicap tunerhead by TOKO	£11.25
EC3302	FET tunerhead from TOKO	£5.00

Complete FM Tuner kits, inc case, for use with the above modules: details SAE please. Prices range from £40 - £60.

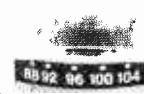Amongst our various accessories for entertainment electronics is a range of FM tuning, frequency and sig. strength meters with 12v, 50mA bulb. £2.50 ea.



ambit international
Trade Mark
25 high street, brentwood,
essex. cm14 4rh.
tel: (0277) 216029
tlx: 995194

Free price list with an SAE, catalogue of modules and parts 40p., including postage and VAT.

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 25%. In stock orders despatched within 48 hours.

WW-036 FOR FURTHER DETAILS

The International Microphone



For over 40 years Beyer Dynamic microphones and headphones have served the needs of professional 'Sound Men' throughout the world.

The M500 (Illustrated) is only one of a range of microphones now serving thousands of users who still demand high quality performance and reliability.

Brochure showing the full range of microphones, headphones and accessories available on request.

BEYER DYNAMIC

BEYER DYNAMIC (GB) LTD

1 Clair Road, Haywards Heath, Sussex. Tel: 51003

WW — 099 FOR FURTHER DETAILS




**When a new one is needed
or the old one needs repairing**

Contact the appointed U.K. distributor
with authorized repair service:-


FARNELL INTERNATIONAL INSTRUMENTS LTD
Sandbeck Way, Wetherby
LS22 4DH
Tel. 0937 3541 or
01 864 7433

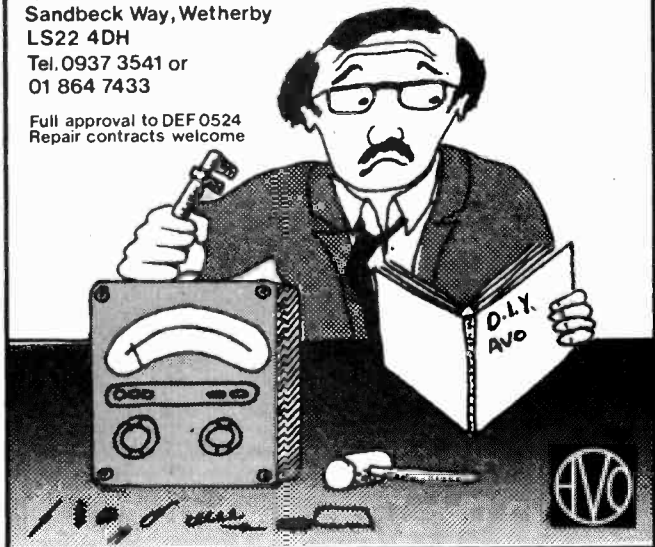Full approval to DEF 0524
Repair contracts welcome



WW—088 FOR FURTHER DETAILS

METER PROBLEMS?

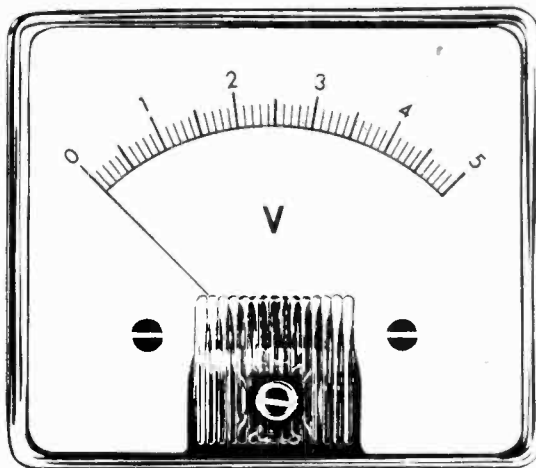

137 Standard Ranges in a variety of
sizes and stylings available for 10-14
days delivery. Other Ranges and
special scales can be made to order.

Full information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW—024 FOR FURTHER DETAILS




Add LUSTRE to every Performance

Lustre Pick-up arms have variable Magnetic anti-skating, stylus overhang adjustment, lateral balance and height adjustment plus an oil damped arm lifter and two plug-in headshells all to add Lustre to your HiFi performance.

The Lustre Pick-up Arm is beautifully finished in satin chrome and black to complement the precision engineering employed in its manufacture and yet it is (approximately) half the recommended price of those few other arms which rival its performance.

SPECIFICATION

- * Bias Compensation: Patented Direct Magnetic Diallying System
- * Two Headshells provided with Gold Plated Contacts
- * Offset angle: 21°
- * Tracking error angle: Less than 1.5°
- * Weight range of suitable cartridge: 5-30g
- * Connecting Leads: Low Capacity - Phono Plug
- * Stylus pressure is by micro adjustment graduated from 0-3g
- * Height Adjustment is from 45-60mm
- * Overall length: 330mm
- * Effective length: 237mm
- * Overhang: 15mm

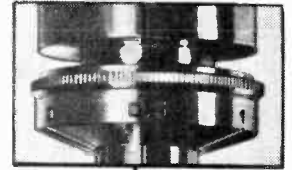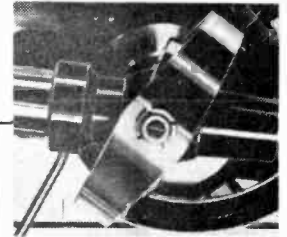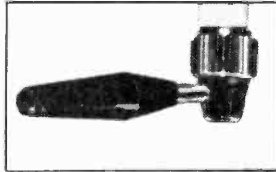


HAKUTO INTERNATIONAL (U.K.) LTD.,

Hakuto


Hakuto House, 557/563 Rayleigh Road, Leigh-on-Sea, Essex, SS9 5HP. Telephone (0703) 526622

WW — 005 FOR FURTHER DETAILS

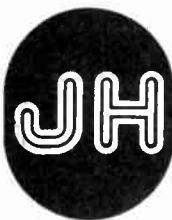

Red & Green LED applied Logic Level Indicator MODEL 320 LOGIC PROBE

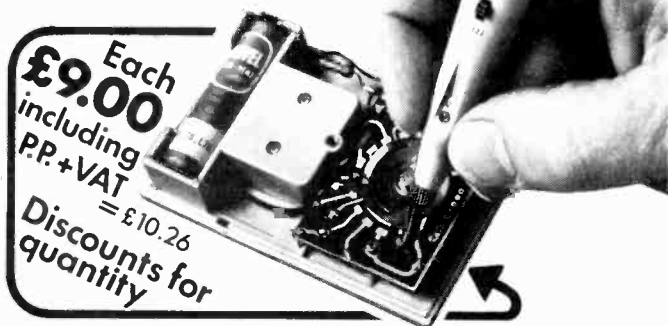- * Wrong polarity and overload protectors provided
- * Detection of the peak value of input waveform
- * Open circuit or faulty IC can be detected
- * All logic levels are visible at a glance
- * Powered from circuit under test
- * Built-in storage circuit
- * Up to 12 MHz



Each £9.00 including P.P.+VAT = £10.26
Discounts for quantity

JH Associates Ltd Sales Office: 52 Silver Street, Stansted, Essex. (0279) 814929

WW—040 FOR FURTHER DETAILS



only
£3.50
+ 8% VAT


The CSP200 offers a good tough and versatile method of housing electronics at a very low cost. The case is constructed from moulded glass fibre with a detachable aluminium front panel & chassis. A choice of colour is also available i.e. Grey, Red or Blue. Size 10 3/4" x 5 1/2" x 5" Available ex-stock direct from our factory

SUPER PROFESSIONAL

Designed for professional use but now also offered direct to the amateur enthusiast, and at a fantastically low price. The main feature of the cases, are the moulded glass fibre side/handle, this being a major safety factor. The cases are all standard sizes and are 3 1/2" high x 1 1/4" deep. Widths are CS101.9 1/4" (£5.25), CS102.12" (£6.25), CS103.17" (£7.25) which when fitted with brackets B103, fits in 19" G.P.O. rack size. All available ex-stock direct from our factory.

More details on request with S.A.F.


from
£5.25
+ 8% VAT

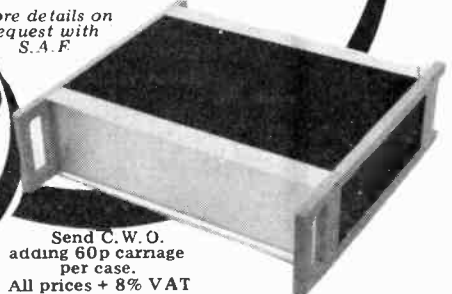

Send C.W.O. adding 60p carriage per case. All prices + 8% VAT

To: Case Systems, 20 Hunt Lane, Chadderton, Lancs. England. Trade Enquires welcome

WW — 079 FOR FURTHER DETAILS

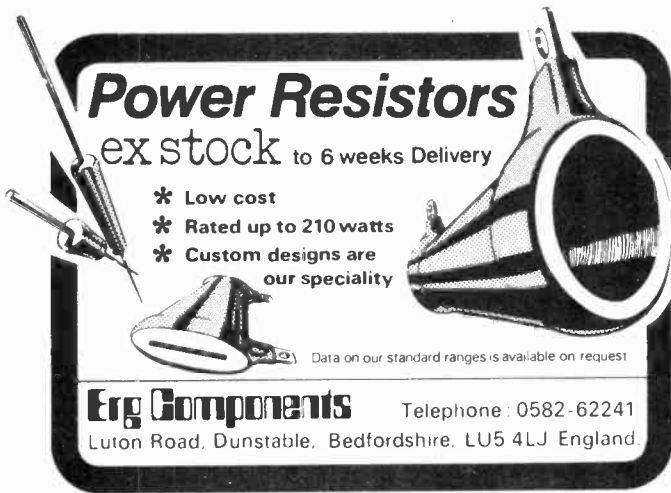

Power Resistors
ex stock to 6 weeks Delivery

- * Low cost
- * Rated up to 210 watts
- * Custom designs are our speciality

Data on our standard ranges is available on request

Erg Components Telephone: 0582-62241
Luton Road, Dunstable, Bedfordshire, LU5 4LJ England.

WW-064 FOR FURTHER DETAILS



AEL SPEEDSERVICE


Hard-to-find tubes and semiconductors are normally included in our quotations. We try to give a complete answer.

AEL GATWICK HOUSE HORLEY SURREY RH6 9SU
Telex 87116 Cables Aerocon Telex Horley Telephone Horley 5353

WW-037 FOR FURTHER DETAILS

FYLDE

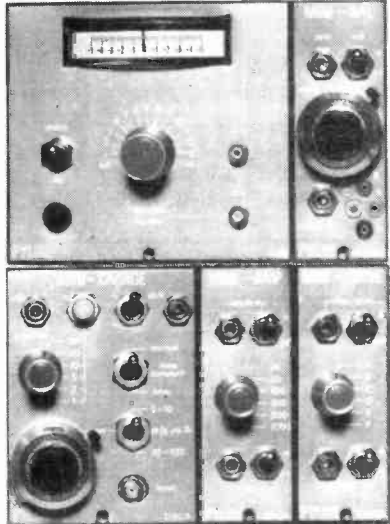TRANSDUCER and RECORDER
AMPLIFIERS and SYSTEMS




reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE Fylde Electronic Laboratories Limited.
49/51 Fylde Road Preston PR1 2XQ
Telephone 0772 57560

WW-047 FOR FURTHER DETAILS

digital arithmetic tutor

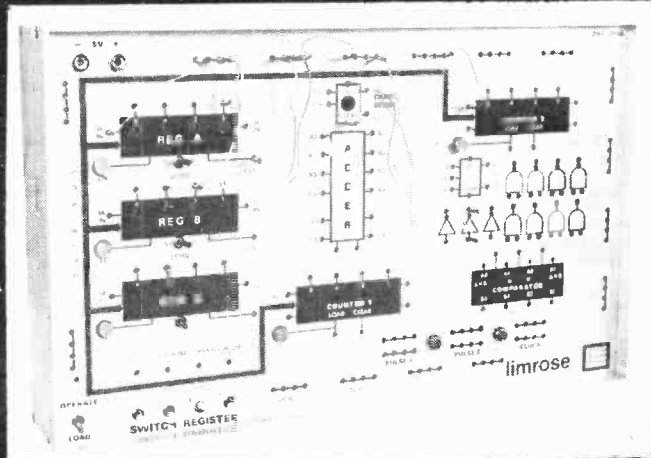Like all it's predecessors, Limrose's Digital Arithmetic Tutor is an extremely versatile and low cost computer training aid. It is very reliable, portable and comes complete with mains operated power supplies for just £174 plus VAT.



For more information, please contact :

limrose electronics ltd.
241-243 Manchester Road, Northwich, CW9 7NE
Tel. 0606 41696 and 0606 41697.


WW-093 FOR FURTHER DETAILS

- P.A. SYSTEMS FOR AIRPORT, HOTEL, FACTORY.
- THEATRE AND LECTURE THEATRE AUDIO SYSTEMS
- AUDIO MIXING EQUIPMENT
- SIMULTANEOUS TRANSLATION SYSTEMS
- RADIO AND T.V. BROADCAST SOUND CONTROL EQUIPMENT
- MARINE INTERCOMMUNICATION AND ENTERTAINMENT EQUIPMENT
- System design, manufacture and installation.

audix AUDIX LIMITED
Wenden, Saffron Walden, Essex CB11 4L9
TEL. Saffron Walden (0799) 40888: TELEX: 817444



COIL WINDING

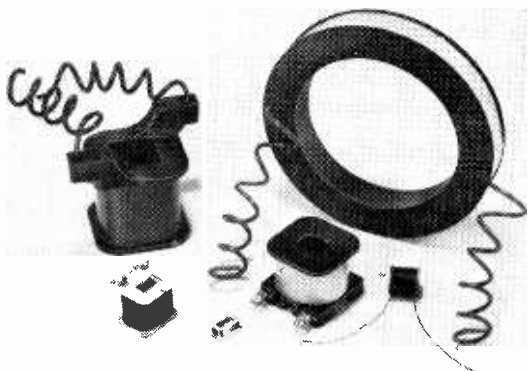

Manufacturers of all wound components including transformers, chokes, stators and armatures. Prototype and design service available.


Electric Windings' factories are equipped to handle large or small volume production. Vacuum impregnation plants provide varnish impregnation for all temperature requirements.

ELECTRIC WINDINGS (LONDON) LTD.
 (Dept. WW) Avenue Works, Gallows Corner
 Romford, ESSEX RM3 0AJ

Ingrebourne 46677

WW-075 FOR FURTHER DETAILS

JOYSTICKS

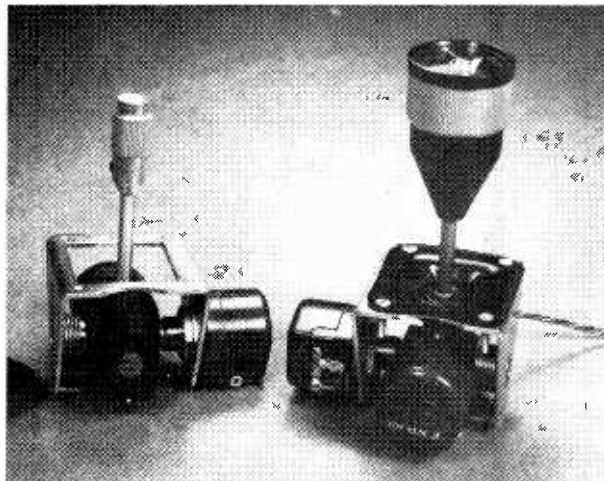

Precise, reliable, long-life Joystick Control Units, in single, dual or triple axis forms. Sprung to centre, or held by adjustable friction locks. Choice of wirewound, cermet or plastic film potentiometers (all standard 3/8" bush types) — or rotary switches.

Already in quantity production for remote control, TV games, electric wheelchairs, audio control panels, etc., etc. Any quantity from one-off to hundreds per month. Typical one-off prices: Single axis £4.50. Dual £6.50. Triple £11.00 + VAT.

See our ad. in January issue for details of all our products.

FLIGHT LINK CONTROL LTD.

Bristow Works, Bristow Road
 Hounslow, Middlesex, 01-570 4065



QUARTZ CHRONOMETER

The range of Electro Systems and Timing electronic chronometers is now available in kit form.

Send S.A.E. for full details.
 Telephone **PENN 4661 (STD code 049481)**.

Trade and overseas enquiries welcome.

PRICES	KIT	ASSEMBLED & TESTED
401-4 (Hours, minutes)	£38.75	£49.40
401-6 (Hours, minutes, seconds)	£43.75	£54.60
401-4-R (As 401-4, with Ni-Cd battery)	£52.50	£63.70
401-6-R (As 401-6, with Ni-Cd battery)	£57.50	£68.90

No VAT required for overseas orders, but add 10% for air parcel post. Add 8% VAT U.K. only; postage and packing included.

OUTSTANDING FEATURES OF THE MODEL 401 DIGITAL CHRONOMETER

- * One second per month accuracy at 20°C
- * 3 MHz AT cut quartz crystal used for best possible temperature stability
- * All versions provide security against timing inaccuracies caused by mains-borne interference and short term mains frequency variations
- * Rechargeable nickel-cadmium battery versions offer not only portability but also protection against outright mains failure, may be left on charge continuously
- * Rugged mechanical design ensures reliability for portable use
- * Large, bright and easy to read LED display; 24 hour or 12 hour modes optional
- * 220/240V mains or external battery operation. 110V version also available
- * Weight 0.5kg. Width 13cm, depth 5cm, height 10cm (12cm with stand)
- * No-cost extras include precision engineered adjustable metal stand and power unit/battery charger
- * 12-month guarantee for correctly assembled kits and ready-built chronometers
- * Low cost "Get-you-going" service for kits, if required
- * All components needed are supplied in kits, including wire, screws and case

COMPREHENSIVE INSTRUCTIONS SUPPLIED WITH KITS

To **ELECTRO SYSTEMS AND TIMING CO.**
 48 Robinson Road, Loudwater, High Wycombe, Bucks., HP13 7BJ
 ENGLAND

Please supply

- 401-4 kit 401-4-R kit 401-4 assemb & tested 401-4-R assemb. & tested
 401-6 kit 401-6-R kit 401-6 assemb & tested 401-6-R assemb. & tested

(U.K. residents add 8% VAT)


Name

Address

I ENCLOSE CHEQUE/P.O. FOR £

—TURNER—

STEREO POWER AMPLIFIERS

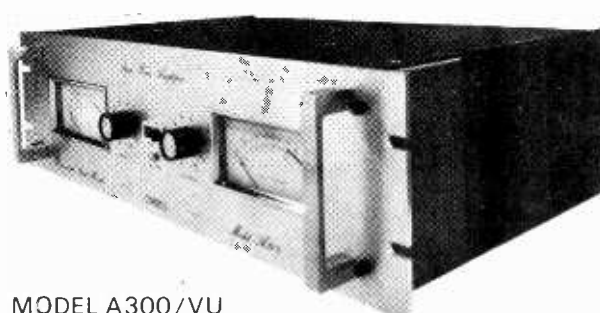

MODEL A300/VU

A range of professional stereo power amplifiers designed and manufactured to a very high standard.

The A Series (Professional Studio Monitor) amplifiers feature dual power supplies to maintain full RMS power on both channels

The B Series (Professional) amplifiers feature single power supplies suitable for most music applications.

		STANDARD	WITH VU's
MODEL A500	250+250 watts RMS 4 ohms	£380.00	£440.00
MODEL A300	150+150 watts RMS 4 ohms	£262.50	£322.00
MODEL B300	150 watts RMS per channel	£210.00	£250.00
MODEL B200	100 watts RMS per channel	£170.00	£210.00

The above prices are list and exclusive of VAT

Overseas Import Agents are invited to make their final applications for allocation of areas for 1976 exports.

TURNER ELECTRONIC INDUSTRIES LTD.
 175 Uxbridge Road, London W7 3TH
 Tel. 01-567 8472

WW-046 FOR FURTHER DETAILS

THE *new* WORLD OF AUDIO

AUDIO FAIR 76

1976 INTERNATIONAL AUDIO FESTIVAL & FAIR OLYMPIA LONDON

13th – 19th September (inclusive)

There is a whole new deal for exhibitors at the 1976 Audio Festival & Fair. A new deal designed to ensure that participation spells success in every way. The formula has been created by a new management team comprising people with a real understanding of Hi-Fi and people possessing deep experience and expertise in staging major exhibitions.



Plans for the 1976 Audio Fair include:—

- new** – earlier dates
- new** – extended trade only period
- new** – floor plans
- new** – cost structure
- new** – Biggest ever all-media promotion

plus –
The backing of all the key IPC Business Press publications

IT'S SOUND SENSE FOR YOUR COMPANY TO BE THERE

Complete and post the coupon below for more details

Please send me a brochure with details for intending exhibitors at the 1976 Audio Festival & Fair.

Name _____ Company _____

Address _____ Telephone number _____

Complete and post to: Audio Festival & Fair, Iliffe Promotions Ltd.,
Dorset House, Stamford Street, London SE1 9LU.
Tel: 01-261 8000

CRYSLON ELECTRONICS LTD.

for

ALL SOUND & COMMUNICATION
EQUIPMENT

SOUND MIXERS CUE SYSTEMS
TALK-BACK ALL ANCILLARY EQUIPMENT

100 WATT POWER AMPLIFIER


FREE STANDING
OR
RACK
MOUNTING



FULL PROTECTION CIRCUITS
SEND OR TELEPHONE FOR DETAILS

CRYSLON ELECTRONIC LTD.
SYDENHAM INDUSTRIAL ESTATE
LEAMINGTON SPA, WARWICKSHIRE
Tel. 37628

WW — 026 FOR FURTHER DETAILS

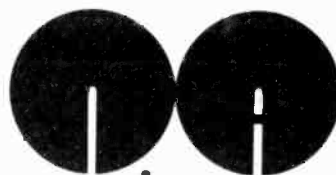

naim audio the power amplifier

BE FAIR TO YOUR MUSIC


Reproduction of sound and its acceptability is dependent on a combination of physical parameters not yet fully explored. We believe that only a compatible combination of specifications will enable a system to

reproduce music. We have taken care that the NAC 12 and NAP 160 pre and power amplifier will do so faithfully, while accepting the output of any pickup cartridge and driving any loudspeaker.



Naim Audio Ltd. 11 Salt Lane, Salisbury, Wilts. Tel: (0722) 3746

WW — 022 FOR FURTHER DETAILS

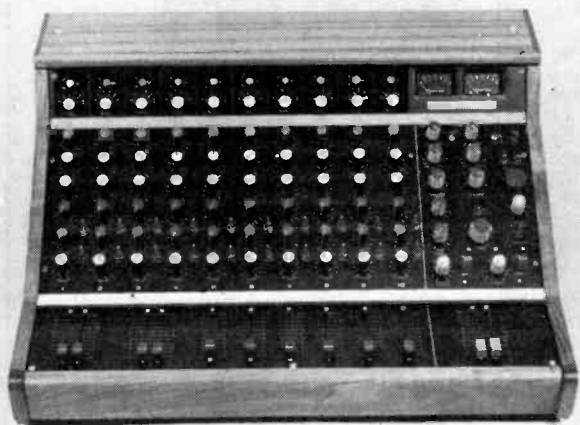

IS CHILTON'S MIXER THE BEST FOR YOUR USE?

Magnetic tapes Ltd make the 10/2 above as well as a 16/2 and a 12/4 with all the inherent flexibility and quality customarily found in big studio mixers. Most of our mixers are constructed to meet the varying demands of the customer, perhaps we can do one for you. Prices start at £400 for the basic 10/2 + VAT @ 8%.

MAGNETIC TAPES LTD.
Chilton Works, Garden Road, Richmond
Surrey TW9 4NS - 01-876 7957

SUBMINIATURE Metal Film Resistors



- * Resistance Range 10Ω to 150KΩ
- * Tolerance from ±1%
- * Nominal Watage @ 70 °C upto 50KΩ 125mW
- * Prices from 9.06p each 100 rate
- * Temperature Coefficients from 50ppm
- * Size 4.1mm long 1.8mm diameter

Erg Components

Telephone: 0582-62241

Luton Road, Dunstable, Bedfordshire, LU5 4LJ England.

WW—063 FOR FURTHER DETAILS

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP
(as in 'W.W.' July '72)

**MOTOROLA MC1310P EX STOCK
DELIVERY SPECIFICATION**

Separation: 40dB 50Hz-15kHz
I/P level: 560mV rms
Input impedance: 50kΩ
Distortion: 0.3%
O/P level: 485mV rms per channel
Power requirements: 8-14V at 16mA
Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB
(Roller tinned), Resistors, I.C., Capacitors,
Preset Potm & Comprehensive Instructions

LIGHT EMITTING DIODE
Suitable as stereo 'on' indicator for above

**ONLY
£3.98
RED
GREEN** WHY PAY
MORE?
post free
29p
59p

MC1310P only £2.15 plus p.p. 10p

NOTE:
As the supplier of the first MC1310P decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

V.A.T.



Please add V.A.T. to all prices

FI-COMP ELECTRONICS
PORTWOOD INDUSTRIAL ESTATE, CHURCH GRESLEY
BURTON-ON-TRENT, STAFFS. DE11 9PT

The new P14 range is designed to meet the demand for a UK source of high quality, low cost 10mm wound components. High quality and low cost has been achieved by designing specifically for automatic production techniques representing a high degree of capital investment.

The range is designed to provide flexible winding and tapping arrangements with adjustable tuning for IF transformers, oscillator coils and RF inductors.

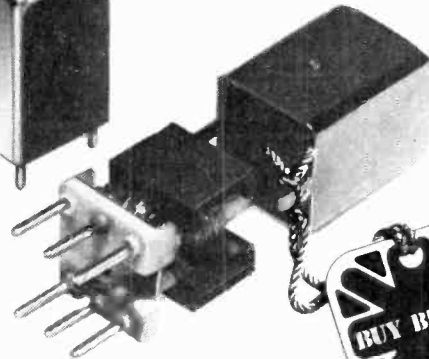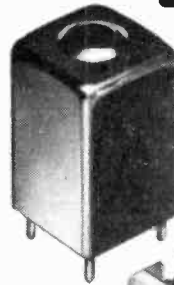Weyrad are manufacturers of wound components and assemblies for the electronics industry. Capabilities include bobbin, layer, and toroidal winding, resin/wave encapsulation, moulding, varnish and wax impregnation and vacuum filling. These manufacturing capabilities are backed by design and development sections which offer industry the widest possible service and flexibility.



Weyrad

Type P14

10mm I.F. coils and transformers

Weyrad (Electronics) Ltd

Head office
Lynch Lane Weymouth Dorset
Telephone (03057) 3801 Telex 41165

WW-091 FOR FURTHER DETAILS

NEW FROM STRUMECH

Electric powered winch (110 volt/5 amp). Bolts directly onto existing towers without modification. Send for leaflet. Price £115 ex works.

VERSATOWER
Strumech Engineering Limited
Coppice Side, Brownhills, Walsall, West Midlands
Telephone: Brownhills 4321

WW-014 FOR FURTHER DETAILS

For those who appreciate Quality...

a complete electronic kit **The Forgestone 400** high quality colour television receiver

A really up-to-the-minute kit, with all these Plus Features . . .

- 9 integrated circuits
- Thick film resistor units
- Ready-built and aligned IF module
- Glass epoxy printed circuit panels
- High quality components
- Fully isolated power supply
- Plugs and sockets for easy panel removal
- Each module kit available separately
- Full technical construction manual
- LT supply regulator

Buy as you build - all Forgestone Kitsets are for the constructor of today, each section of the kit is available separately. Please send stamp for further details of these quality products.

Forgestone Colour Developments Limited


Ketteringham, Wymondham, Norfolk, NR18 9RY, U.K.

Telephone: Norwich 810453 (STD 0603)


MAIL ORDER - Barclaycard & Access accepted



WW-100 FOR FURTHER DETAILS

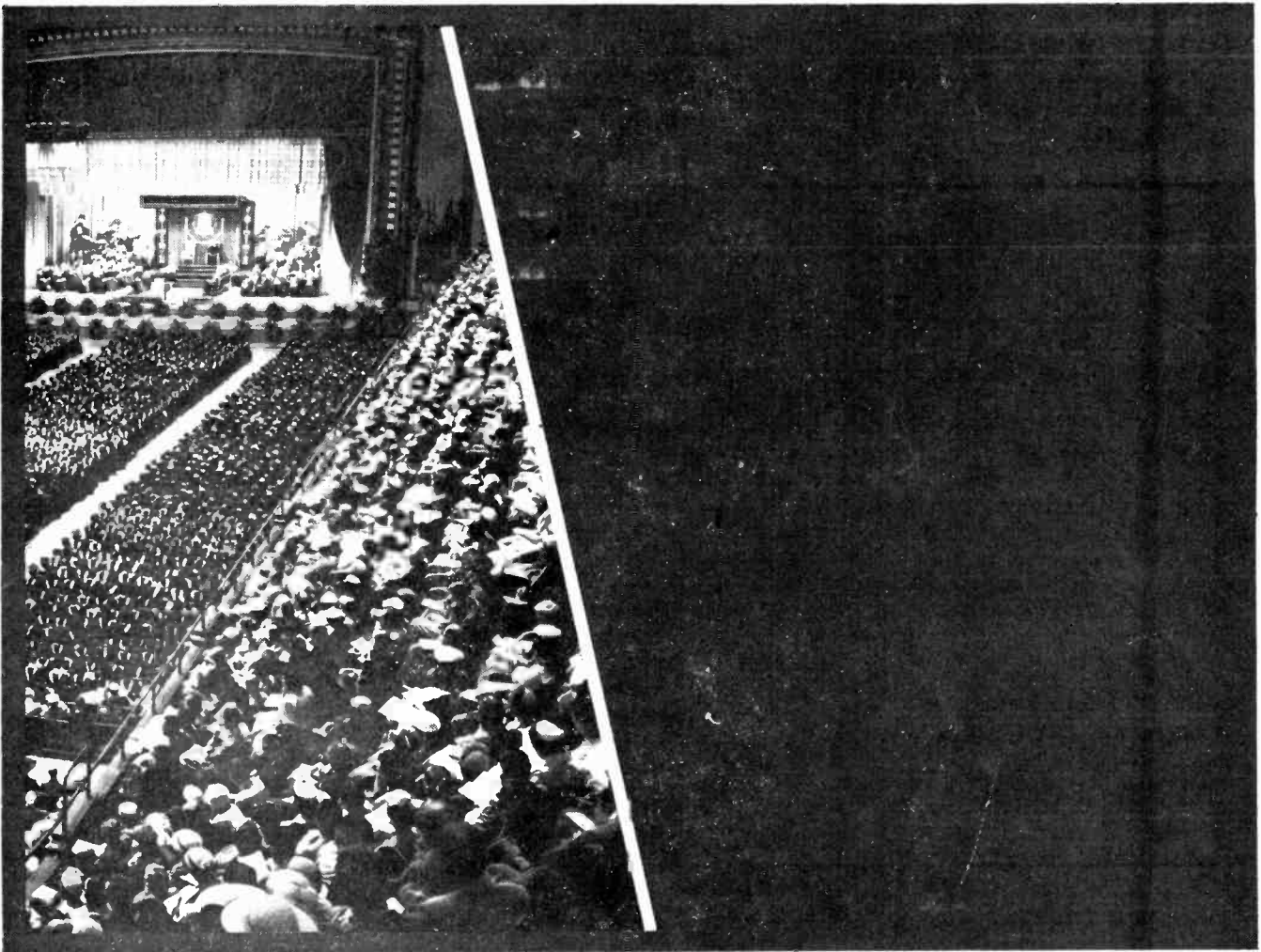

Vocal Master of Ceremonies

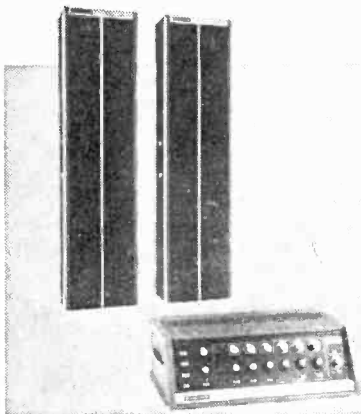

There are precious few ceremonies, functions, meetings or entertainment events that *Shure Vocal Master Sound Systems* can't cover — regardless of room size or apparent acoustic difficulties. The Vocal Master is designed to project the voice with intelligibility and authority to the rear of large areas without overwhelming the listeners up front. It's versatile, easy to operate, and totally reliable. It's the system that earned its reputation for superb sound amplification by meeting the standards of professional entertainers — and is now used in hotels, churches, schools, executive meeting rooms and entertainment facilities from Land's End to John O'Groats in preference to built-in "custom" systems costing *many* times more.

Shure Electronics Limited
 Ecclestone Road, Maidstone ME15 6AU
 Telephone: Maidstone (0622) 59881



WW-072 FOR FURTHER DETAILS

wireless world

Electronics, Television, Radio, Audio


APRIL 1976 Vol 82 No 1484

Contents

- 35 Approach to microwave landing
- 36 Transistor driver for valve amplifiers by *Seth Berglund*
- 41 News of the month
 - Mobile radio price fears
 - Union for engineers?
- 43 Communication theory — 1 by *D. A. Bell*
- 46 Sixty years ago. H.F. predictions
- 47 F.M. tuner designs — 2 by *D. C. Read*
- 51 Research notes
- 52 Letters to the editor
 - Phase effects in loudspeakers
 - Was Baird fooling the public?
 - Current dumping audio amplifier
- 56 Time-code receiver clock — 3 by *A. F. Cross*
- 58 April meetings
- 59 Electronic systems — 3 by *W. E. Anderton*
- 60 Books received
- 61 Circuit ideas
 - Automatic display brightness control
 - Low current source
- 64 Wireless World Teletext decoder — 6 by *J. F. Daniels*
- 73 Phase shift in loudspeakers by *James Moir*
- 76 Automatic battery switch-off circuit by *D. T. Smith*
- 77 Diode model of the m.o.s.f.e.t. by *B. L. Hart*
- 80 World of amateur radio
- 81 Circards 29: analogue multipliers by *J. Carruthers, J. H. Evans, J. Kinsley & P. Williams*.
- 83 Television tuner design notes by *D. C. Read*
- 85 New products
- 88 Real and imaginary by "Vector"
- 129 APPOINTMENTS VACANT
- 144 INDEX TO ADVERTISERS

*Price 35p (Back numbers 50p, from Room 11, Dorset House, Stamford Street, London SE1 9LU.)
Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.
Telephones: Editorial 01-261 8620; Advertising 01-261 8339.
Telegrams/Telex. Wiworld Bisnespres 25137 London. Cables. "Ethaworld, London SE1."
Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50
UK and overseas (\$9.10 USA and Canada).
Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.
Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone
0444 53281. Subscribers are requested to notify a change of address.

© IPC Business Press Ltd, 1976

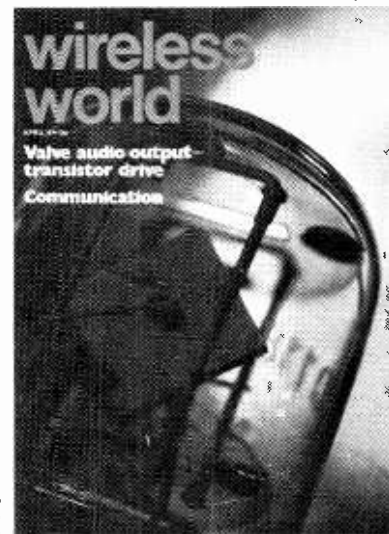

Front cover shows 120kHz quartz crystal, DT-cot, made by the Quartz Crystal Division of ITT Components Group Europe.

(Photographer Paul Brierley)

IN OUR NEXT ISSUE

Cassette deck. Design for a low-noise (s/n 52dB) front-loading cassette deck which can be built for less than £40.

The "walltenna" — an array of metal foil dipoles for v.h.f./f.m. reception, designed to be hidden beneath the wallpaper of your living room.

Loudspeaker sound quality. Little known relationships between design parameters and what is heard — with some new subjective data.


SIXTY-SIXTH YEAR
OF PUBLICATION

ibpa
International Business
Press Associates

ABC
MEMBER OF THE ADVERTISING
BUREAU OF CIRCULATION

Switch to complete protection. Switch to EEV.

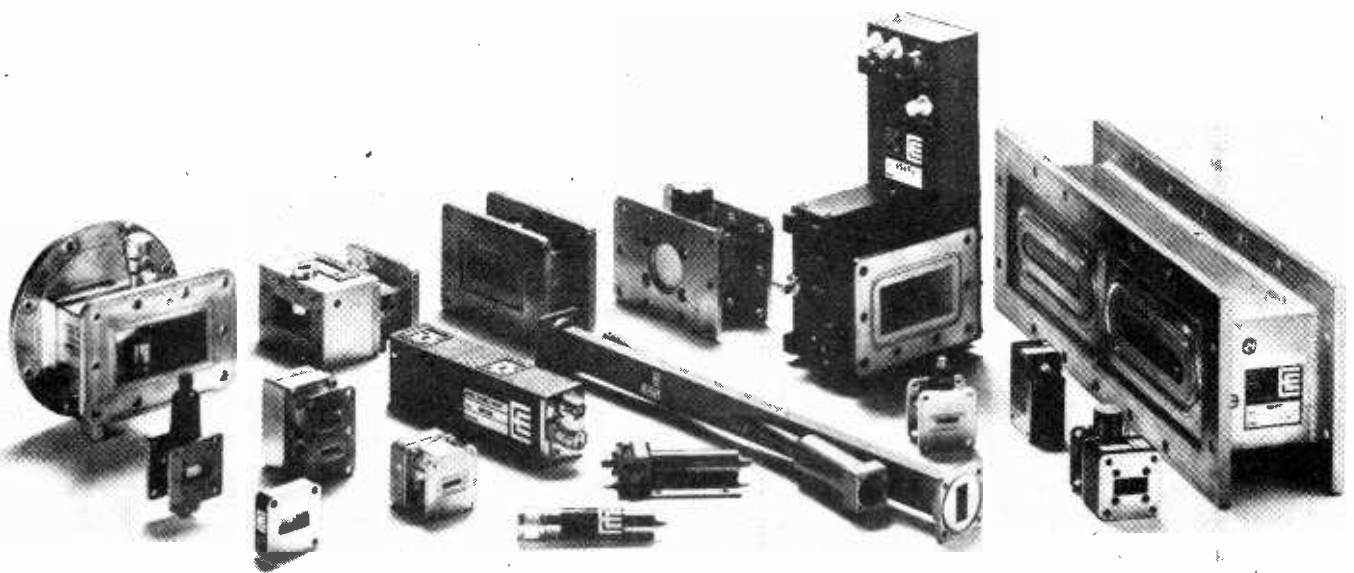A selection from the EEV range. We have more than 300 types of duplexer devices currently in production.



The receiver is one of the most important components in radar equipment. And one of the most delicate.

Unless the receiver is completely protected, sensitivity will be degraded and performance adversely affected.

You can give your receiver the protection it needs – by using EEV duplexer devices.

We can supply high-quality devices for all power levels and radar functions. The EEV range includes:

- TR tubes. ● TR limiters (primed and primerless). ● Pre-TR tubes. ● Protector tubes.

- PIN switches. ● Solid state limiters.
- Balanced duplexers. ● Mixer receivers.
- RF heads. ● Monitor diodes. ● Noise sources.

EEV appreciates the importance of duplexer devices. They are a major part of our total microwave capability.

Backed by Europe's best research, production and test facilities, we can provide devices which exactly meet your needs.

Whatever you want to protect, try EEV's range for size. Write or 'phone for duplexer device data. Or, even better, tell us your precise requirements.

LAP 85

EEV and M-OV know how.

wireless world

Approach to microwave landing

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
Phone 01-261 8435

Technical Editor:
GEOFFREY SHORTER, B.Sc.
Phone 01-261 8443

Assistant Editors:
BILL ANDERTON, B.Sc.
Phone 01-261 8620
MIKE SAGIN
Phone 01-261 8429

Production:
D. R. BRAY

Advertisements:
G. BENTON ROWELL (*Manager*)

KEVIN BURNAL
Phone 01-261 8515

O. BAILEY (*Classified Advertisements*)
Phone 01-261 8508 or 01-261 8423

JOHN GIBBON (*Make-up and copy*)
Phone 01-261 8353

IPC Electrical-Electronic Press Ltd
Publisher: Gordon Henderson

If your holiday beach last year lay at the end of a journey by air the chances are that the last few miles were flown along a narrow radio beam known as ILS – instrument landing system. This has become the standard international approach aid to airfields, and its performance has been steadily improved to the extent that it enables suitably equipped aircraft to be landed in virtually zero visibility. In no other function is the pilot required to put so much trust in the accuracy and reliability of electronics. But a new development known as MLS – microwave landing system – now holds the attention of the policy makers in the International Civil Aviation Organisation. Interest in the possibility of a new approach aid developed in the late 1960s when communications engineers realised that microwaves, digital computing and advanced cockpit displays could be brought together to produce a more accurate and versatile system.

ICAO produced in 1972 a set of technical requirements, and five countries responded: the USA, Britain, France, West Germany and Australia. Their proposals are now being studied, and a decision is expected next year. The schemes fall into two categories: Doppler and scanning beam. Britain, along with two US companies, ITT Gilfillan and Hazeltine, has put forward a Doppler-based system (see March 1974 issue, pp. 25-26) which, supported by the UK Government in collaboration with Plessey, has already been successfully demonstrated in flight tests at the Royal Aircraft Establishment, Bedford. Two other American companies, Texas Instruments and Bendix, pinned their faith on the alternative technique. Last year the US Federal Aviation Administration, in a controversial decision which was hotly contested by Britain and the two losing US companies, chose the scanning-beam system as its proposal to ICAO. The reasons given for this decision – there was no airborne experience of scanning-beam equipment to the technical standard specified by ICAO available for comparison – are not convincing, particularly since the scanning-beam system as it stands probably cannot provide the accuracy needed to level the aircraft and reduce its rate of sink just before it touches the runway. This, of course, is a critical manoeuvre.

America's choice cannot but influence the ICAO's committee, the All Weather Operations Panel, in its deliberations. If it pleads more time for practical experiments, the FAA is likely to go ahead anyway and introduce scanning-beam MLS into some US airfields which cannot be served by ILS. Such a *fait accompli* may very well capture the majority vote of the ICAO's eleven-man AWOP group which will choose one of the five entries as the basis of its recommendation for an international standard.

Apart from the rights and wrongs of the decision, the companies involved stand to make money handsomely. Even those firms which backed the losing method will have the edge over those which have no experience, because the C-band techniques, aerial design, data-processing and many other aspects are similar in both systems. This particularly applies to Britain, whose Government has spent £3.5 million in developing and demonstrating the so far only workable MLS.

Michael Wilson,
Technical Editor, *Flight International*

Transistor driver for valve amplifiers

Design for Williamson and other output stages

by Seth Berglund
Lunds University, Sweden

There are certainly a lot of valve audio amplifiers still in use, and many of them have an inherent quality of performance that makes it reasonable to give them a thorough repair, with or without an accompanying modernization. The work needed for repair may tend to grow, however, since it may not be sufficient to replace valves and a few electrolytic capacitors. A general degradation of components may have taken place, and in nearly all instances of modernization it should be advantageous to replace the rectifying valve by silicon or maybe selenium rectifiers. So there may be some doubt as to what is really needed and what is worthwhile.

For those who are interested in giving their valve amplifier a positive modernization that will result in obvious improvements, a description is here given of a transistor driving amplifier that can replace the voltage amplifying stages of many existing power amplifiers. The Williamson amplifier¹ has been chosen as a typical example for the discussion that follows, because it is a well-known design. Other amplifier designs that have been used for comparison are those designs by Mullard² and by GEC³.

The original idea was to design an amplifier with a bandwidth sufficiently in excess of the output transformer bandwidth, so that the only phase shift to take account of should be that of the transformer. A d.c. amplifier with a bandwidth of about 1MHz was thought to be sufficient. Direct coupling from the input stage to the signal grids of the output valves leaves the output transformer as the only cause of phase shift at the low frequency end, and the shift tends to only 90°. So there are no problems of instability from negative feedback at the low frequency end, provided that the usual precautions as to supply line filtering are taken.

At the high frequency end of the transformer passband there is usually one main resonant frequency, often at about 100kHz, around which the phase shift passes 90° by a considerable amount but does not reach 180°. It was thought therefore that with a bandwidth of at least 1MHz for the driver, the normal amount of 20dB frequency-independent feedback should be

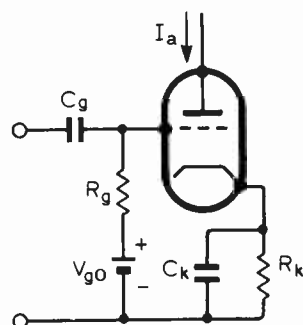


Fig. 1. A constant voltage V_{go} is in this circuit added to a normal cathode bias.

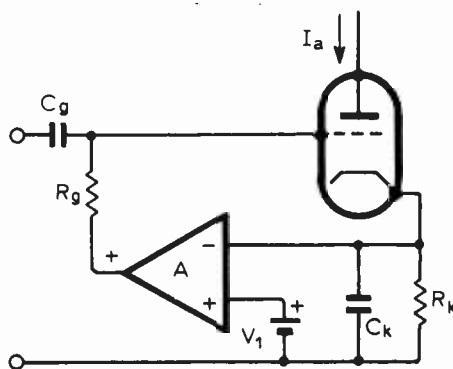


Fig. 2. Further development of the circuit in Fig. 1 by means of a gain function A .

allowable without instability. This was found to be the case for several output transformers, at least with a resistive load. With the Williamson transformer and output stage according to the original design, an essentially flat amplitude-frequency response was obtained up to 1MHz, and there was some stability margin.

If a loudspeaker or some load of a complex nature is inserted, the phase shift tends to become too large, and the only way to stability is then to reduce the closed-loop gain. So extended bandwidth is no radical solution for stability at the high frequency end in the same way as direct coupling is for low frequencies. And after all, the aim should not be amplification up to radio frequencies, but an i.f. amplifier with a defined upper frequency limit. This does not mean that it is a wasted effort to start with a large bandwidth for the

driver. On the contrary, by starting with a bandwidth of 1MHz, the high-frequency response can be exactly formed up to this frequency, using simple operational amplifier techniques, and so it can easily be changed to suit different output transformers. The output voltage of the driver is sufficient even for large output tubes such as the KT88; they are assumed to work in class A or AB in the design that follows.

Output valve biasing

When direct coupling to the output valves is used, the grids can still be kept at zero potential for the quiescent point, with a normal cathode bias for class A or AB operation. But this is not necessary and in my opinion not at all the best way. Let us therefore look at other ways of biasing. For the sake of simplicity, single valve biasing is discussed first, and the valves shown as triodes with the usual assumption of zero grid current, i.e. anode and cathode currents are identical. If thus I_a is the anode current of a triode and R_k the outer cathode resistance, the negative grid voltage with a normal cathode bias is $V_{gk} = I_a R_k$.

It is possible, although not often used in practise, to modify the influence of the anode current on this bias voltage by the addition of a constant voltage to the circuit, either in series with the cathode or, normally with less effort, in the grid circuit, shown as the voltage V_{go} in Fig. 1. The grid bias voltage is now $V_{gk} = V_{go} - I_a R_k$.

It is important to note that V_{go} may be positive as indicated in the figure, or negative. In the first case a larger resistance R_k is required than for simple cathode bias, which makes the grid voltage more dependent on the anode current, i.e. there is a better stabilization of the quiescent point. In the case of negative polarity for V_{go} , the grid voltage becomes less dependent on the anode current, as R_k must be diminished. For growing negative values of V_{go} , it becomes in the limit equal to the desired grid voltage. Then R_k must go to zero and the result is a constant grid voltage.

A grid bias that has exactly the same dependence on the combination of a constant voltage and the anode current

as that of Fig. 1, but with improved means for the choice, can be obtained by a circuit as shown in Fig. 2. With the notations according to this figure, and provided that the operational amplifier of voltage gain A has zero offset, the constant part of the grid bias is $V_{go} = AV_i$, and the total grid bias becomes

$$V_{gr} = AV_i - (1 + A)I_a R_k$$

In this circuit R_k can be a small resistance, which is an advantage for large output tubes where the power dissipated in R_k for a normal bias may be considerable. Most important is, however, the ease of adjustment to a desired bias.

The bypass capacitor C_k has retained its function, and the time constant $R_k C_k$ is chosen as for normal cathode bias. However, if R_k is small, so that it causes only negligible feedback by itself, the bias time-constant may be introduced by a separate RC-link, either before or after the amplifier.

In the foregoing figures the bias and signal voltages have been mixed in the usual way by a grid resistor R_g and a coupling capacitor C_g . If a full signal feedback from R_k is wanted, corresponding to an unbypassed cathode resistance in Fig.1, some other type of mixing circuit is needed. This also holds, if direct coupling of the signal to the valve grid is used.

Arrangement of amplifier

To explain the main features of the complete push-pull amplifier, its layout is first shown by the simplified circuit of Fig. 3. The circuit comprises three differential stages, namely a signal input stage, a biasing stage for the sensing of the currents in the output valves, and between these a mixing and amplifying stage that drives the valves. It is a symmetrical circuit throughout for the input signals, and the necessary d.c. balance is obtained at the emitter side of the input stage, in the figure by means of the potentiometer R_1 . Another important feature is that the differential stages are all supplied by a current source at the emitter side, instead of just by a common emitter resistor. A high common-mode rejection ratio is thereby obtained, which means that the input signal and the negative feedback around the amplifier can be fed differentially to the input stage without danger of adverse secondary effects.

The current source for the mixing stage, a single transistor in Fig.3, acts with the differential pair as a common-mode amplifier for the signals from the preceding biasing stage, so that the two stages together give a common-mode voltage gain from cathodes to grids that corresponds to the gain function denoted by A in Fig. 2. The gain to a sufficiently good approximation is

$$|A| = \frac{R_B}{R_2} \cdot \frac{R_C}{2R_E}$$

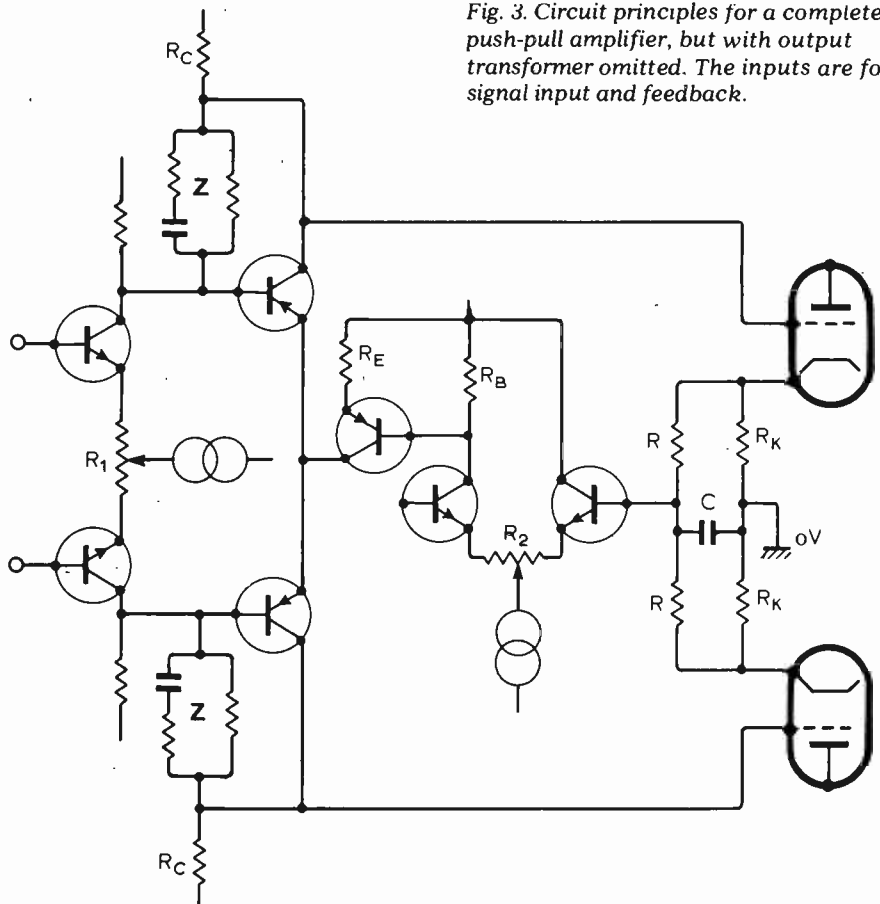


Fig. 3. Circuit principles for a complete push-pull amplifier, but with output transformer omitted. The inputs are for signal input and feedback.

Resistance R_2 is selectable for choice of voltage gain.

As the amplified part of the bias is a common-mode one, it corresponds to a common cathode resistance with the value $R_k A/2$, and the time constant of the RC-link is $RC/2$. The constant part of the grid bias is simply an offset voltage, effected by an adjustment of the potentiometer R_2 , which is therefore found to have the double function of determining the gain by its resistance value and the constant voltage by its adjustment.

The resistances of R_k may be so small that their direct influence on the valve bias becomes negligible. They cause a small lowering of the effective valve transconductances.

Because the collector resistances of the mixing stage become fairly large, there is ample signal amplification available in this stage for local feedback to be applied. This is used in the amplifier for determining the response by means of the impedances Z .

Amplifier design

The complete amplifier is shown in the circuit diagram of Fig. 4. Although the number of components has grown, the fundamental simplicity as evidenced by Fig.3 is retained, and there are not any hidden difficulties such as the need for tricky adjustments or special demands on the power supply voltages, which may vary within large limits. The demands on filtering are not very large either, since the current sources for the

differential stages reduce hum. Only the negative high tension voltage needs a certain stabilization.

The input common-emitter long-tailed pair of Fig. 3 is a dual n-p-n transistor Tr_1 , and it is completed by an n-channel dual f.e.t. Tr_2 , the two transistors of which are used as input source followers. This makes the amplifier compatible with valve amplifiers with regard to input impedance as well as to independency of the characteristics of the driving source. So all that is required of the preamplifier is that it shall give sufficient voltage.

The d.c. balancing potentiometer R_{41} , a 15-turn trimming potentiometer, has been moved away from the main signal path into the f.e.t. source circuit, where it gives a smooth adjustment of the differential balance. By this change the two resistors R_7 and R_8 also become more freely selectable for their function to determine the local feedback of the stage and the gain of the amplifier. They should be matched, so as not to cause additional asymmetry to be balanced out. It is the combination of f.e.t. and bipolar transistor pairs that gives the good input property, together with an easily variable amplification and a large bandwidth. Dual transistors must be used to reduce temperature drift, see later.

The mixing stage has been developed to a cascode configuration, which is very important with regard to harmonic distortion because the output voltage swing is large. It is also important that

the Miller feedback capacitance is kept very low so that the loading on the preceding stage can be controlled as desired, and the amplifier as a whole be given sufficient bandwidth. The main local feedback is by means of the emitter resistors R_{13} and R_{14} , but they need not be matched as their counterparts R_7 and R_8 , as the balancing action of R_{41} is amplified by the input stage.

Local feedback by the two impedances Z starts at a value of about 12dB for low frequencies, but increases within the frequency range 20 to 200kHz to about 26 dB. It forms the amplitude response as shown in Fig.5, curve A. The impedances Z do not cause any common-mode feedback but act together for the differential feedback, so they do not need matching for their action. However, matching is needed for the collector loads of transistors Tr_5 and Tr_6 for symmetry in driving the output valves. The two collector resistors R_{15} and R_{16} should be matched, and also the impedances as they also load the collectors.

As to the valve common-mode biasing, there are only two alterations from the simplified circuit of Fig.3. One is that the potentiometer for adjustment of the constant voltage part has been split up in two fixed resistors, R_{19} and R_{20} , and a 15-turn trimming potentiometer, R_{42} . This makes the selection of resistances for a desired value of the amplification fairly easy, and provides for a smooth adjustment of the constant voltage. The other change, mainly for temperature

drift is that the current source for the mixing stage, Tr_9 and Tr_{10} , is a complementary pair amplifier.

The gain as defined by Fig.2 is nearly 70, which means that the bias circuit corresponds to a common-cathode resistor of 350 ohms. A common-mode constant grid voltage of about +5V is added by adjustment of R_{42} . The quiescent grid-cathode voltage is about -45V and the valves work in class A.

A negative feedback that senses the differential direct voltages across the cathode resistors has also been added to the circuit. It consists of the matched resistor pairs R_{31} , R_{32} and R_5 , R_6 together with the capacitors C_3 , C_4 . This feedback is coupled to the amplifier inputs and has an upper frequency limit of about 1Hz. It has the same stabilizing effect on the balance between the tube currents as two separate cathode resistors of 200 ohms, connected together in a long-tailed pair configuration but without influence on the common-mode bias.

All the above values are easily changed for desired bias conditions, but a general discussion of valve biasing is outside the scope of this article.

A capacitance of 22 μ F was originally used for C_5 , but is omitted in the circuit of Fig. 4. However, output triodes in

class A with a high load impedance is the only case where the capacitance may be omitted to some advantage.

Response and distortion

The amplitude-frequency response of the complete amplifier is shown in Fig. 5: without feedback by curve B, and with 20dB overall negative feedback by curve C. The low-frequency response for small signals is flat down to 10Hz both with and without feedback. Exact curves showing the fall below 10Hz are not interesting, but it is possible to select a value for C_2 that gives an optimum response to square waves at low frequencies.

There is a dip in transformer response at about 50kHz, which cannot be eliminated by simple feedback circuits. It causes some ringing in square-wave tests, which of course has nothing to do with instability. The capacitance of C_6 in the feedback loop has, however, been chosen so large that it has a damping influence on the ringing. The series resistance of R_{36} has been chosen as a compromise to give about the same frequency response when loaded by a certain broadband loudspeaker as with a resistive load. A capacitance inserted as C_6 in the feedback loop without a series resistance often gives a good frequency response with a resistive load, but oscillations when a load-speaker is connected. Its influence on the feedback must therefore always be carefully checked.

The branch R_{22} and C_7 between the

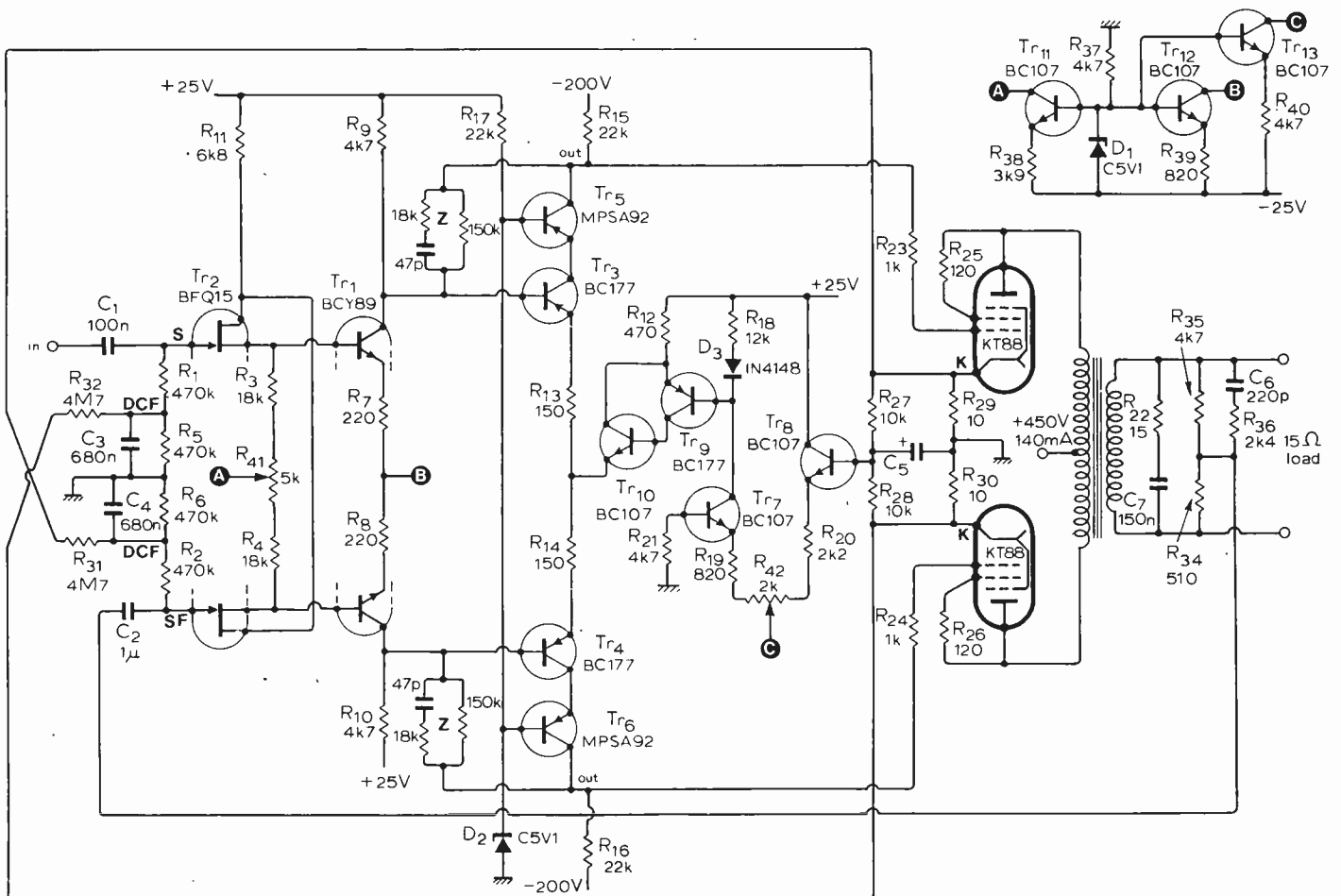


Fig. 4. Complete circuit diagram of the power amplifier. Valves work in class A as C_5 is made zero (see text).

output terminals has been found valuable with several output transformers, and is therefore recommended. It has no effect on the response within the audible band, but represents a resistive load at high frequencies. Values are not critical.

It has been an aim to choose about the same high frequency limit for the response without feedback as in the improved version design by Williamson to make a comparison of the final result fairly easy. It could be an advantage, however, to choose a lower high frequency limit by a change of the impedances Z.

Total harmonic distortion of the driver is quite low. For 30V r.m.s. output on each side it is only about 0.05% at low frequencies and rises to about 0.1% at 20kHz. This leads to a low distortion for the whole amplifier even without overall feedback: at 1kHz this distortion is only 0.08% for 10W and 0.2% for 15W output power.

The overall feedback works fully within the audible band, but the maximum output power falls at the low and high frequency ends. At a distortion of less than a quarter of a percent the available output power with resistive load is 20W at middle frequencies and 15W at 20Hz and 15kHz.

The total harmonic distortion, measured at 20Hz, 1kHz, and 15kHz and with an output power of 10 and 15W is summarized in the table below. The figures are given in percentage distortion, but include what there may be of hum and noise in the prototype amplifier.

Power output (W)	Total harmonic distortion (%)		
	20Hz	1kHz	15kHz
10	0.05	0.01	0.1
15	0.1	0.02	0.25

Circuit working conditions

In all d.c. amplifiers there is a temperature drift that must be taken account of. In this case there are really two, namely a common-mode drift in the biasing circuit and a differential drift for the signal path. Drift in the output valves is not considered.

An obvious cause of common-mode bias drift is the difference in change of base-emitter voltage with temperature for the transistor pair Tr₇ and Tr₈. The two transistors should be of the same current amplification class, BC107A in the prototypes, in which case the difference may be assumed to be 0.1mV/deg C at the most. The drift voltage is equal in its effect to a false reading of the direct input voltage on the base of Tr₈, and results in a corresponding shift of the anode currents of the valves.

If an ambient temperature change as large as ± 20 deg C is assumed, the false reading is not more than ± 2 mV, which is less than 0.3% of the above-

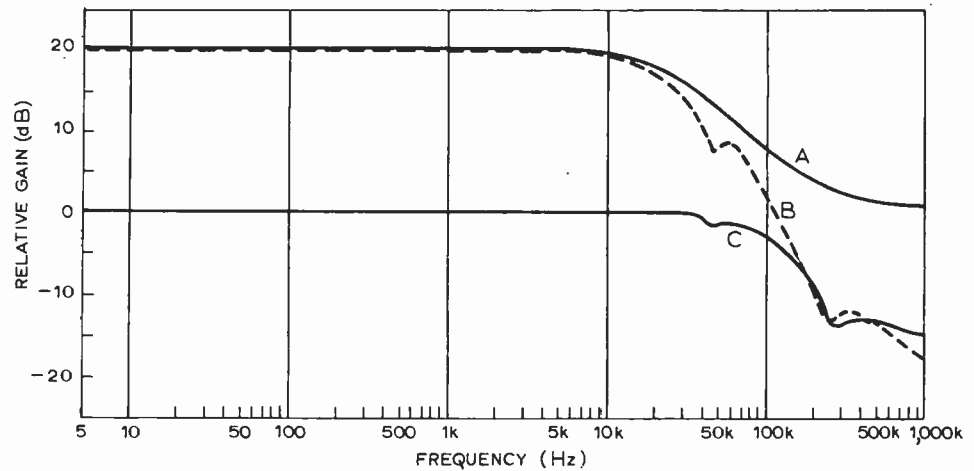


Fig. 5. Amplitude frequency response curves for the driver (A) and for the complete amplifier without (B) and with feedback (C).


mentioned d.c. input voltage, being about 700mV. However, the two transistors must be mounted close together, so that they experience the same ambient temperature change. Preferably they should be plastics transistors and clamped together, but a dual transistor is not necessary.

There is also a temperature drift from differences in the internal heating of the transistors, for instance at power supply variations. This is kept low by means of low collector currents. For the same reason the design assures a small collector current for Tr₉ in the current source, and the transistor drift is partly balanced out by D₃. The balance is not as good as for a couple of equal transistors, but here the drift is inside the feedback loop and has less influence on the valve currents, about one third of that of the preceding transistor pair.

The main cause of differential drift is the input dual f.e.t. Although its thermal drift of gate-source voltage difference for specified working conditions is less than 40 μ V/deg C, its drift in the circuit may be larger, on account of shifts of quiescent points. There is also up to 10 μ V/deg C drift in the dual bipolar transistor, and some additional drift from the transistor pair Tr₃, Tr₄. As a summation a temperature drift of up to 100 μ V/deg C referred to the input of the amplifier will be assumed.

To find what the above drift means as a drift in quiescent current for the valves, the d.c. feedback from the cathodes to the input circuit will first be assumed inoperative. The differential voltage amplification to the grids is 450 and the transconductance is 10mA/V, which gives 0.45mA/deg C differential drift for the anode currents, or ± 9 mA for a change in temperature of ± 20 deg C. This is at the limit of what should be allowable, but, on the other hand, fairly wide limits as to the causes are assumed.

The picture of drift changes radically, however, if the d.c. differential feedback

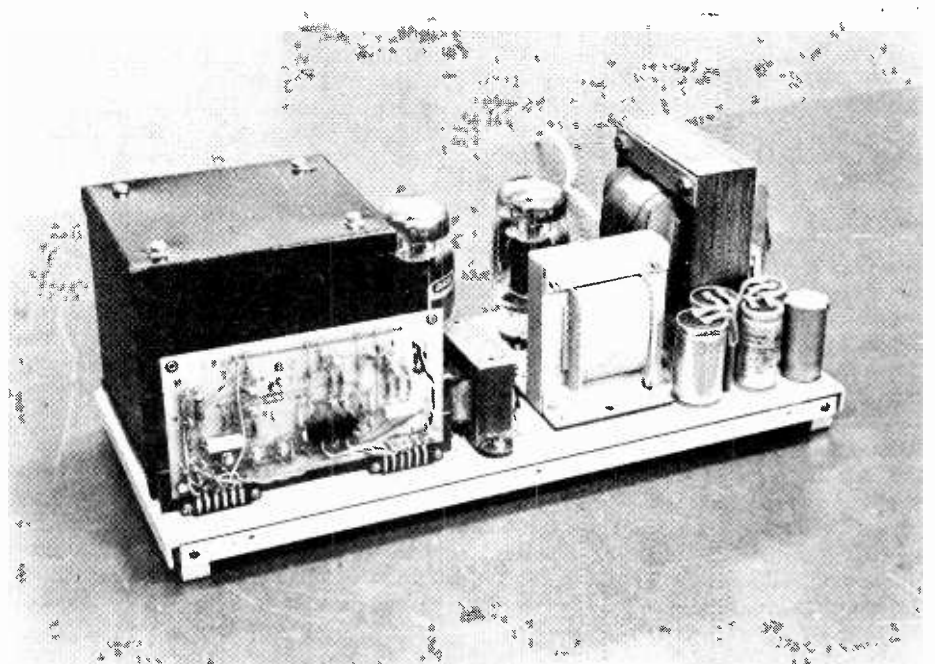

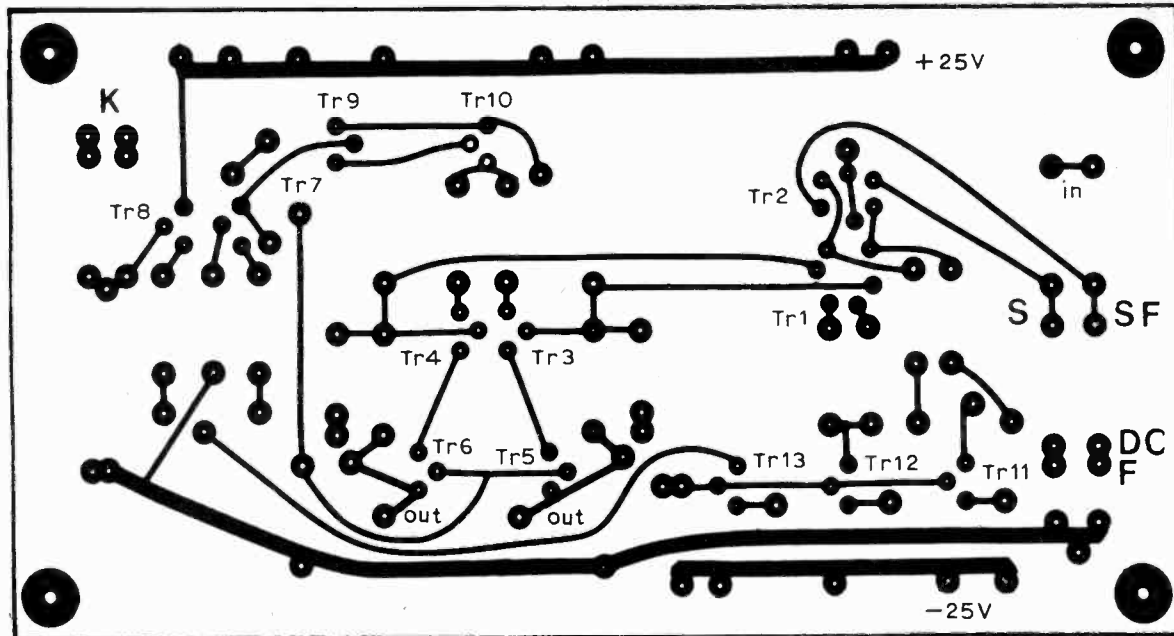


Fig. 6. Components in feedback circuits, R_5 , C_3 , R_6 , C_4 and C_2 are not included on board; neither are R_{15} and R_{16} . Mono printed boards are available for £2 inclusive from M. R. Sagin, 11 Villiers Road, London NW9.

is inserted. The feedback is 14dB from d.c. to about 1Hz, and the above anode drift becomes less than $\pm 2\text{mA}$ for a $\pm 20\text{deg C}$ temperature change. The feedback also reduces d.c. drift from other causes, such as changes of component values with time. Its equivalence to a pair of separate cathode resistances has already been shown.

The above feedback may, on the whole, be regarded as a possibility rather than a necessity, and 14dB is certainly more than necessary. The time constant in the feedback circuit is so large that temporary deviations from symmetry in the signal (musical) voltage should not cause appreciable d.c. shifts.

Stabilization is needed for the negative high tension voltage, because a $\pm 10\%$ variation of this voltage would cause too large variations in the valve bias. A simple stabilization, for instance by means of a series resistance from a -300V supply feeding a chain of six 0.4W, 33V zener diodes is sufficient. The voltage is of course not critical.

Constructional details

The layout of the circuit on a printed circuit board or otherwise is not critical. It has already been mentioned that the two transistors of the pairs Tr_3 , Tr_4 and Tr_7 , Tr_8 should be mounted for close thermal connexion, and so should Tr_9 be with D_3 . To avoid heating effects from the collector resistors R_{15} and R_{16} , mount them with the valves, and not on a p.c. board. The circuit should be mounted away from the mains transformer and filtering choke to avoid induced hum from stray magnetic fields. It should also be kept away from any hot air stream or heat radiation from the valves. These precautions do not cause any problem, as the circuit may be given fairly small dimensions. Simple metal shields have been used in the prototype amplifiers.

Five-percent resistors have been used, and for matched pairs a 2%

difference is acceptable, although a closer tolerance may be required for the resistor pairs in the d.c. feedback, or the value of R_1 may prove not to be sufficient.

In a first construction, the d.c. feedback should be omitted, and put into effect only as a finishing touch.

For the positive and negative supply voltages of 25V in Fig. 4 the recommended values are 25 to 30V, but there is no need for symmetry. The value of collector currents for the cascode stage is 6 to 7mA. The currents of the other stages are evident from the values of the resistors R_{38} , R_{39} and R_{40} , since the voltage across these is about 4.3V.

Any transistor in the Philips BFQ10-16 family may be used at the input, and there are of course also other replacement types, for instance the Siliconix E401. There are also a number of replacements for the Motorola MPS-A92, for instance MPS-U60, BFT19 (RCA), and BFW43 and BFW44 (SGS-Ates). There are numerous replacements for BC107 and BC177, and also for the dual transistor BCY89, which is the least expensive of the BCY87-89 family.

Concluding remarks

One reason for the choice of KT88 valves connected as triodes was that they put high demands on the driver, and so are suitable for presentation of driver qualities. The same valves connected as pentodes or with a distributed load are more easily driven because the Miller capacitance is lower. An obvious conclusion is therefore that the driver should suit most power amplifiers except for very large ones that require several output valves in parallel.

The ratio between the negative high

tension voltage for the cascode stage and the maximum grid peak-to-peak voltage is about two. When smaller output tubes are used, such as EL34, EL506 or EL84, the negative voltage should be lowered, but the above ratio not made smaller — a value between two and three is preferred. The collector currents for the cascode stage should be maintained, and the collector resistors chosen accordingly.

References

1. Williamson, D.T.N. High quality amplifier: new version, *Wireless World*, vol. 55, 1949, p. 282.
Williamson, D.T.N. The Williamson Amplifier, A Wireless World publication, Iliffe & Sons, Ltd.
2. Ferguson, W.A. Design for a 20-watt high quality amplifier, *Wireless World*, vol. 61, 1955, p.223.
High Quality Sound Reproduction, Mullard Ltd.
3. How to Build the Osram 912-PLUS, General Electric Co, Ltd.
Heath, W. Ian and Woodville, G. R. "Design for a 50-watt amplifier," *Wireless World*, vol. 63, 1957, p.158.

Logic design course

Digital System Design is the name of a course to be held at Chelsea College, Pulton Place, London SW6, from May 17 to 21. This course is designed to give practising engineers and scientists a formal approach to the logical design of digital systems and should prove useful to those engineers and scientists working in the field of digital electronics who have had no previous training in methods of logic design. Enquiries should be addressed to Professor J. E. Houldin at the above address.

News of the Month

Mobile radio price fears

According to the Mobile Radio Users' Association, essential public services as well as commerce and industry will experience escalating equipment costs during the next ten years in the use of mobile radio. Proposals made by the Home Office in their preparations for the 1979 World Administrative Radio Conference — which will decide the amount of frequency spectrum required for the 1980s — suggest even greater usage of mobile radio frequencies now available.

Such measures "would entail vastly more expensive equipment and re-organization of the present allocated spectrum at a time when users are already experiencing increasing interference in the main conurbations, as well as being forced to share facilities." The Mobile Radio Users' Association is busy gathering support from its members to prepare a case for the allocation of more of the spectrum to mobile radio. They think that unless this is done, unfair and costly restrictions will be imposed on what is an essential cost-saving and efficiency-improving tool for the country, resulting in the "trebling of costs and the curtailing of growth within the industry."

BS9000 mandatory for military equipment

From February 1 the Ministry of Defence introduced a new contracts clause requiring electronic components used in the design of MOD-sponsored equipment to be approved within the BS9000 standards system. Any necessary exceptions will be kept to the minimum. Military forces rely heavily on electronic equipment, which they expect to function reliably under exacting conditions, and they therefore consider it essential to have an effective system of component specification and quality assurance.

The BS9000 series was formulated by the British Standards Institution in 1967, in collaboration with Government departments, industry and other users,

to specify a range of electronic components meeting levels of quality assurance and performance acceptable for common use in industry and the military services. The Ministry of Defence has supported the scheme, believing that a national system offers greater benefits than one restricted to military requirements. In particular the larger volume of components covered by BS9000 permits economies in reducing wasteful proliferation of component types. Although the use of BS9000 components is growing, progress has been slower than originally hoped. Since the full advantages of the scheme will not be realised until BS9000 is more widely used, the Ministry of Defence is now taking steps to extend its application in the military equipment industries.

Union for engineers?

Professional engineers need a union, with strong and experienced leaders and affiliation to the TUC, according to Dr G. F. Gainsborough, secretary of the Institution of Electrical Engineers. Writing in the February issue of *IEE News* he refers to a recent report* of a Council of Engineering Institutions working party which urges that engineers should join a union, and backs a suggestion that the Electrical Power Engineers' Association (EPEA) should change its name and constitution to make it representative of all engineering disciplines. The March issue of *Wireless World* (p.43) proposed rather a union to be formed on an industry-technology basis for technicians and professional engineers in electronics. (About half of the unions affiliated to

the TUC are based on particular crafts, trades or technologies.)


*"CEI Professional Engineers and Trade Unions"

Direction finder for Cape Gris Nez

Following the successful completion of trials at Cape Gris Nez (between Boulogne and Calais) the French office of lighthouses and maritime signals has ordered a v.h.f. direction finder. The monitoring of shipping in the English Channel by radar has not proved itself to be completely satisfactory as the unambiguous identification of ships is not immediate enough and presumes among other things the manoeuvrability of the ships and that the v.h.f. communication channels are not too crowded. This led to the additional use of a v.h.f. direction finder which was tested out for the task. In contrast to other identification aids, direction finders possess the advantage of requiring no extra aids on board ships except the v.h.f. radio systems which most ships have anyway. Also, in the case of emergencies they can immediately provide the exact position of disabled ships. The Rohde & Schwarz NP7 direction finder used works in the frequency range of maritime radio (156 to 162 or 174MHz) and delivers bearing values with a maximum deviation of only one degree. The NP7 operates on the Doppler principle and uses an antenna system made up of 32 dipoles arranged on a circle plus one antenna in the centre. An antenna commutator simulates the rotation of a single antenna on this circle. The bearing indicator automatically provides a three-digit display of the direction to

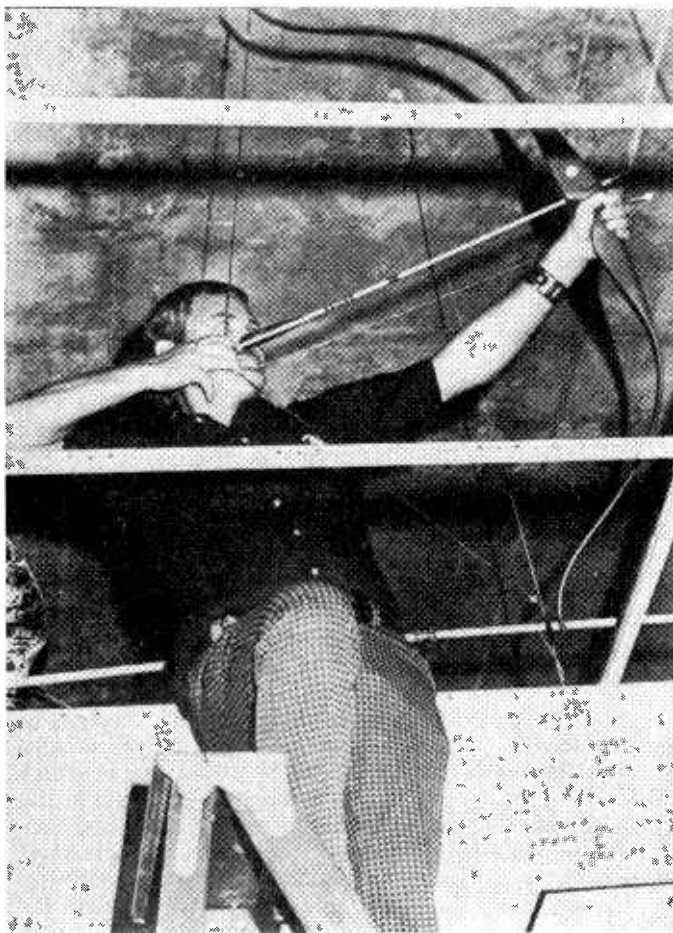In the new Radio London Studio, Marylebone High Street. Picture shows d.j. Robbie Vincent at his control desk.





Not the latest electronic guided weapon but Jim Taylor, an installation supervisor for General Telephone and Electronics Company of Florida who resorts to the bowman's ancient art whenever he has to install telephone lines in inaccessible places.

the transmitter target, the measured value being averaged over 180 simulated rotations of the d.f. antenna.

TV goes underground

Platforms on the new Heathrow Central underground station at London Airport will be monitored with a closed-circuit TV system. This will allow London Transport observers at Earls Court station to view the platforms at the last three stations on the new Piccadilly Line extension – Heathrow Central, Hatton Cross, Hounslow West. The installation consists of a single coaxial cable linking all stations along the line and control cables for switching the selected cameras at the different stations to two monitors at Earls Court. The installation contract, awarded to British Relay TV Ltd, covers video-switching and modulating equipment at the "observed" stations, amplifying equipment for picture transmission, at h.f. and the receiving and switching equipment at Earls Court. The system is capable of carrying three vision channels in the 3 to 30MHz frequency band.

Sun-tan for components

A solar radiation simulator is in use at the Product Assessment Laboratories of

Plessey in Titchfield. The simulator has been introduced to meet new specifications which have been laid down by the International Electro-Technical Commission and the British Standards Institution. Artificially created sunshine can be applied to test samples to determine their ability to withstand both visible and invisible radiation in natural sunlight. The simulator will show the effect of u.v. radiation on rubbers and plastics such as cable forms and plastic assemblies and will also create a temperature rise in equipment to enable designers to check solar radiation protection and the operation of cooling systems. Electronic trackside railway signalling equipment is under investigation at the Plessey laboratories and the facility is expected to be widely used in testing virtually anything that stands in the open air. The sun simulator is claimed to be able to reproduce the worst solar radiation conditions throughout the world.

Secondary radar for MRCA

A secondary radar data display system to be installed at British Aircraft Corporation's military aircraft division flight test centre at Warton is scheduled to be in service within ten months, serving BAC and the development flying programme of the Multi-Role

Combat Aircraft. The design of the system is claimed to provide an economic solution to the surveillance and control problems of any small airfield with radar facilities. It will also increase air safety by providing additional flight data to the air traffic controllers at Warton where full flight envelope testing of supersonic aircraft takes place relatively close to civil air lanes and the busy Manchester control zone.

At present, the air traffic control unit at Warton relies solely on a Marconi S264 primary radar, backed up by a precision approach radar. This has recently been improved by the addition of a digital signal processor and provides primary cover up to a distance of 160 miles. The secondary radar data display system, to be provided under a new contract to Marconi Radar Systems, will take this primary information in its new form and present it to the controller combined with secondary and primary extracted radar data obtained via landline from Civil Aviation Authority's St Anne's facility about four miles away. The ability to revert to a local primary picture is retained. The facilities available at each radar display position include raw local primary radar data, video and digital map data, reference marks, emergency indications plus full control over range, off-centre and presentation parameters.

Colour TV deliveries for '75

Deliveries to UK distributors of UK made and imported colour television receivers reached 150,000 in December, a fall of 7% on December 1974, according to the latest statistics compiled by the British Radio Equipment Manufacturers' Association. This brought the total for the year to 1,590,000, a fall of 28% compared with the same period in 1974. Total monochrome set deliveries for December were 67,000, an increase of 52% compared with December 1974; this brings the year's total to 938,000, a 15% increase on the same period of last year. These figures include deliveries to rental and relay companies.

Leeds electronics exhibition

Visitors to the 1976 Leeds Electronics Exhibition will be able to hear about current technology and applications of microprocessors. Three lectures on this subject are being arranged for day two of the show and one lecture for day three. Also in the programme of lectures which traditionally accompanies the Leeds show is one on switched mode power supplies. The exhibition will take place in the Department of Electrical and Electronic Engineering at Leeds University on June 29, 30 and July 1.

Communication theory

1 — Information is finite

by D. A. Bell

University of Hull

A generation ago one might have said that *language* was one of the main features distinguishing man from the animals. But now it is known that most animals, from chimpanzees to bees, have systematic methods of communication by sounds and gestures; and the unfortunate person who is deaf and dumb (and therefore would a few centuries ago have been regarded as stupid) can communicate by "deaf and dumb language." All of this goes to show that communication can be effected by various means; and the superiority of human speech lies in its speed and flexibility which enable it to convey a very wide range of messages, including abstract ideas.

The introduction of the word *idea* is a cue to point out that the communication or information theory of engineers is not concerned with "ideas": it handles only "messages." This might sound like a severe limitation but in fact it is not, since any set of words, for example, can be regarded as a message; and the "set of words" might be the Bible, the collected works of Shakespeare, or the works of your favourite science-fiction author. By choosing a set of words we have made the number of possible messages finite in the mathematical sense though inconceivably large: there are some 35,000 words in an English dictionary so the number of different sets of, say, 100,000 words is rather more than 10 to the power of 400,000. If I assume that every reader has a copy of the Concise Oxford Dictionary (5th edition, 1964) I can represent any word by a code of the form $n_1 a n_2$ where n_1 is the page number, a is L or R for left-hand or right-hand column and n_2 is the serial number of the word in the column. The opening words of this article would then be represented by: 1L2 509R4 26L13 544R7 767L6.

This is very clumsy and time-consuming as it means looking up every word in the dictionary (though I am sure one would soon get to recognise the codes for common words, like 1L2 and 544R7) but it has several noteworthy features:

(1) It reminds us that communication

requires that sender and receiver agree on the code to be used, even if only on a common language.

(2) It is more precise than words. 767L6 in the dictionary reads "might²". See MAY¹*, thus distinguishing it from "might¹" meaning great strength.

(3) It illustrates the point that words may be represented by all sorts of different symbols during the process of communication.

(4) From the sample given above it would appear that the typical length of a code group is 5 characters, which compares with 5 letters for an average English word. But 4 of the 5 characters are now numerals in the scale 0-9 and the fifth has only two values, L or R. So there is some economy.

It also makes it clear that we are talking about the kind of communication which consists in selecting in turn particular signals from a known set of signals or code; and the kind of information which can be communicated in this way is called selective information. Now most of the information we handle is of this kind: the current price of gold; which of the national contestants became Miss World; which premium bond drew a prize; which airline has just had a plane crash; what are the frequencies and times of BBC stereo broadcasts. These are all questions which can be answered by drawing a particular number or name from the range of numbers and names which was known to exist, and less specific or more complex information can be communicated by a more or less lengthy series of words selected from the dictionary. New ideas, on the other hand, cannot always be specified definitively by existing words or groups of words and may have to be assimilated gradually from the context in which new words or phrases are used. If I look in the dictionary for "meaning" I am referred to "significant" and vice versa. But under "bread" I find "Flour moistened, kneaded and baked, usually with leaven". Thus a concrete object can be broken down into its components or alternatively it can be described in terms of shape, colour, texture etc.;

but an abstract idea like "meaning" can only be learned through experience of the way in which the word is used. It is also a prime principle of communication theory that one should not communicate information which was already known; this means that the amount of information transmitted is measured by the *increase* in amount of information possessed by the recipient. The method of measuring the amount of information will come later.

Communication is never absolutely certain. The hi-fi enthusiast may ask for "perfect" reproduction, but the engineer knows that at least there will be Johnson noise in the circuits, with power kTB^* in bandwidth B . So the engineer must ask "How good is good enough?" Ask him for 60, 70 . . . dB signal-to-noise ratio and he will tell you whether it is possible and how much it will cost; but ask him for perfection and he will either shake his head or decide for himself what standard the customer will accept as perfect. But if we are communicating only selections from a finite set of signals, it is obvious that the s/n ratio required is just enough to prevent one signal being mistaken for another. This idea is usually illustrated by the analogy of representing the several signals by points in space. (It has to be multi-dimensional space with a large number of dimensions.) These points have to be far enough apart that when the co-ordinates of one of the points are given then in spite of the noise in the system a seeker armed with the co-ordinates will arrive within reach of the desired point and of no other. The sort of practical problems to be solved by communication theory are therefore as follows.

(i) Given a set of messages (of known number) from which selections are to be communicated through a channel of given bandwidth and s/n ratio, what are the best shapes of signal to use to represent the messages?

(ii) With the conditions in (i), what will be the reliability of communication, or

* k = Boltzmann's constant and T = circuit temperature.

how should the conditions be altered to achieve some specified standard of reliability?

(iii) How does speed of communication tie in with everything else?

Ignoring derivations and proofs, we can answer questions (ii) and (iii) by quoting Shannon's key formula

$$C \leq W \log (1 + P/N) \quad (1)$$

which is part of the following theorem: By a sufficiently complicated method of encoding it is possible to communicate information at any rate up to C through a channel of bandwidth W and ratio P/N of signal power to noise power with negligible risk of error. This is the channel capacity theorem. Note that this evades question (i) by postulating "a sufficiently complicated system of encoding." The hypothetical system of coding which allows the equality sign to be used in formula (i) is called "ideal coding." Much effort has been devoted to the search for coding methods which approach this ideal. Another point is that where we have loosely said "with negligible risk of error" one should ask "negligible in comparison with what?" To be precise, Shannon showed that the risk of error may be made as small as we wish by making the signals long enough in time. There are therefore advantages in putting the formula in symmetrical form

$$I \leq T W \log (1 + P/N) \quad (2)$$

where I is the amount of information transmitted in time T .

T can be measured in seconds, W in hertz and P/N is a ratio (e.g. of watts); but we have not yet any measure of I .

Now any information can be communicated, between two people using the same code book, by a sufficient number of yes/no questions. This was noted by Francis Bacon in 1623 when he devised a code in which each letter of the alphabet was represented by five binary symbols and said that "And here, by the way, we gain no small advantage, as this contrivance shows a method of expressing and signifying one's mind to any distance by objects that are either visible or audible - provided only the objects are but capable of two differences, as bells, speaking trumpets, fireworks, cannon etc."

A simple example is that about 16 binary decisions should suffice to locate any word in the Concise Oxford Dictionary if I start with first or second half, quarters, eighths . . . and finally down to fractions of a page. (I have to say "about" because the number of pages is not a power of 2 and the number of words per page is not uniform; the Dictionary was not designed for this exercise!) It follows that (selective) information can always be expressed as an equivalent number of binary units; and I in (2) is measured in bits or C in (1) in bits per second. But this is not the whole story. If a "sixteen questions" guessing game with the dictionary leads me to the top half of the right-hand column of p.943 I shall think that the word I am seeking is likely to be *pompous* or *pond*, but unlikely to be *pompano* or *pompier*, for example. So the measure of the amount of informa-

tion which is communicated must take account of the pre-existing probabilities and not merely absolute certainties; and we now take the view that the amount of information communicated is related to the reduction in uncertainty or to the extent to which it allows a reassessment of probabilities at the receiving end of the channel. It can be shown mathematically that the only satisfactory measure of the uncertainty related to a finite group of probabilities is the *entropy*

$$H = - \sum_{i=1}^N p_i \log p_i \quad (3)$$


where the p_i are the individual probabilities in a set of N distinct probabilities. Since probabilities are by definition less than unity, each $\log p_i$ is a negative quantity and H is positive.

Entropy has significance in thermodynamics and statistical mechanics, but the exact relationship between the different applications of entropy need not concern us. It suffices to say that entropy is always associated with ideas of disorder, confusion or indistinguishability of one state of a system from another. It is therefore natural to associate it with uncertainty and use reduction in entropy as a quantitative measure of information.

So far as we are concerned, H in formula (3) is just the weighted mean of all the logarithms of the probabilities, each logarithm being weighted with its own probability of occurrence, and it can be measured in bits. (Readers are probably familiar with the transformation from common logarithms (\log_{10}) to natural logarithms (\log_e) by multiplying by 2.3. Equally one can work in logarithms to base 2 and if the units in formulae (1), (2) and (3) are bits it must be understood that the logarithms are (\log_2). An important property of H is that it has a maximum value of $-\log p$ when all p 's are equal and is zero if one probability is unity and all others zero. For if one probability $p_k = 1$, $\log p_k = 0$ and all the other $p_i = 0$; so $\sum p \log p = 0$ when one possibility can be selected with certainty.

For a simple application to a communication situation, suppose we are watching a Telex machine which we know is going to print a string of letters. Before a letter is printed there is a probability of $1/26$ for each letter of the alphabet and $H = -\log_2 (1/26) = \log_2 26 = 4.7$ bits. If the letter Q is printed, $H = 0$ for this letter; and the information attributed to the communication of one letter is equal to the reduction of entropy of 4.7 bits. But if instead of "a string of letters" the Telex output was known to be English language text, the appearance of Q would be quite improbable but the appearance of E would be probable. This prior knowledge of probabilities constitutes information which we already have at the receiver and thereby reduces the amount of information which has been communicated. This is allowed for by recalculat-

Fig. 1. Identification of a word: (a) the dictionary, (b) the page number, (c) the column, (d) the word.

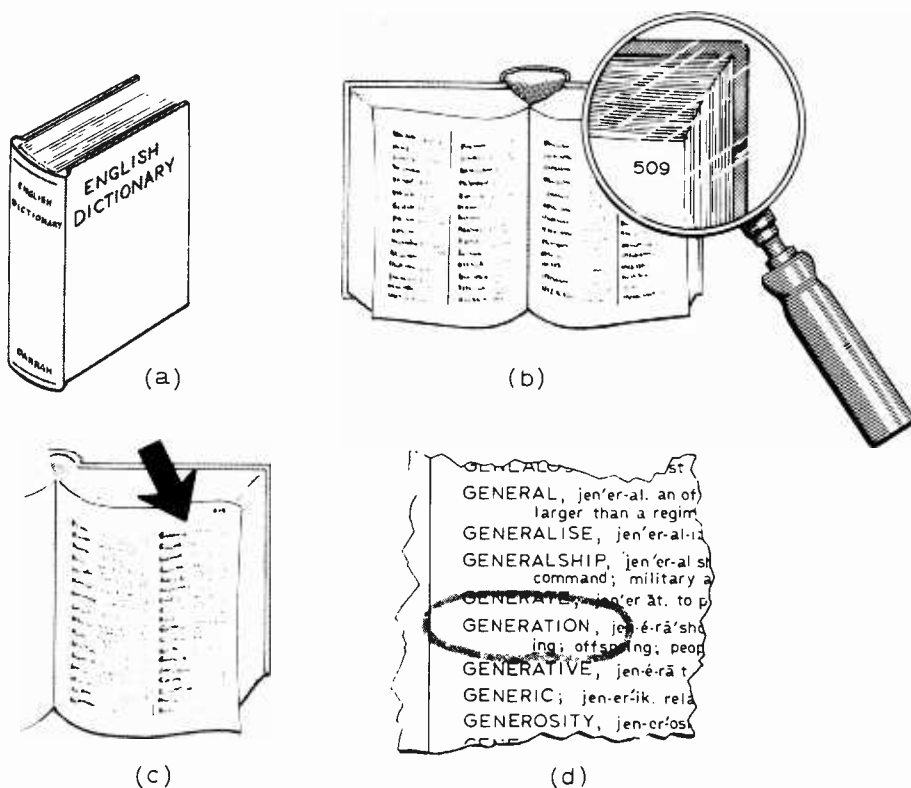

ing the value of H before the letter was received, putting the English-language weighting for each letter in the formula

$$H = -\sum_{i=1}^{26} p_i \log p_i \quad (4)$$

This will necessarily be less than the maximum value obtained when all the p 's are equal and therefore its reduction to zero will represent less increase in information. (Actually the entropy of the English-language-weighted alphabet of 26 letters is reduced only to 4.3 bits per letter.)

But now let us look at the line engineer's view. Each letter is represented by five units (plus some synchronising pulses), and the receiving equipment must be set up with a threshold which decides between mark and space for each of the five units. Suppose the line is noisy so that there is a 10% chance that any one (but only one) of the units will be incorrectly interpreted. Then 5 letters which differ in one unit from the letter sent will each have a $(1/5) \times 0.1$ chance of being printed and the entropy after receipt of the noisy signal will look like this:

$$H = -\sum p \log p = -(5 \times 0.02 \log 0.02 + 0.9 \log 0.9) \quad (5)$$

In binary units this is 0.701 bits. The information transmitted is the difference between the uncertainty before and the uncertainty after transmission, which in this case with English language is nearly 3.6 bits. So now we are able to measure the amount of information which is communicated even when noise in the channel means that nothing is certain. An important result of applying formula (3) to a binary channel ($N=2$) is that a 50% error rate means zero communication of information. For if when 1 is received the chances are 50 - 50 whether 0 or 1 was transmitted, one might as well toss a coin at the receiver and dispense with the communication channel.

Now we have admitted that there will always be noise in the communication channel. If it is random noise it may have any value of instantaneous amplitude up to infinity, but for just over two-thirds of the time it will not exceed the r.m.s. value. How can we reconcile this presence of occasional noise amplitudes which are many times bigger than the r.m.s. value with the channel capacity theorem?

That there is a real problem is shown by the following very crude and approximate interpretation of formula (2). If the signal-to-noise ratio is good, $1 + P/N \approx P/N$ and the amplitude ratio is approximately $\sqrt{(P/N)}$. The logarithm of the square root is half the logarithm of the original quantity, so

$$I \approx 2TW \log [\sqrt{(P/N)}] \quad (6)$$

Now $2TW$ is the number of independent pulses that can be associated with the time-bandwidth product TW and in the

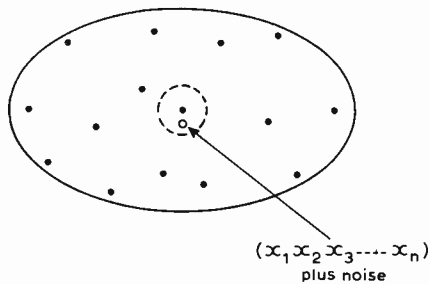


Fig. 2. The distance between signals must be greater than the likely effect of noise.

absence of noise digital information can always be expressed in the form

$$I_D = n \log S \quad (7)$$

where n is the number of digits and S the number of states or amplitude levels for each digit.


Comparing (6) and (7), the channel capacity theorem seems to be saying that the number of amplitude levels can be spaced at intervals equal to the r.m.s. noise; but the instantaneous noise exceeds the r.m.s. value for about one third of the time, so how can errors then be negligible? The answer is in the first few words of the theorem "By a sufficiently complicated method of coding..." A proper derivation of the channel capacity theorem is fairly mathematical, and the further one goes in search of "ideal coding" the more one gets entangled in mathematics; but there are two principles which can be stated non-mathematically:

- (1) Since the number of messages is finite, one has only to choose a finite set of signals which are sufficiently different from each other that even in the presence of noise one is unlikely to pick the wrong one. (This difference is often called the "distance" between signals.)
- (2) A single instantaneous amplitude of noise may have a large value, but it is unlikely that a number of instantaneous values in succession will all have large values, and the more samples you take the nearer their average[†] will come to what we regard as the r.m.s. value of the noise.

An example of the second principle is

[†]Strictly speaking this "average" must be the root-mean-square value of the samples and what we normally call the r.m.s. value of the noise is that which we should obtain with an infinite number of samples.

Fig. 3. (a) signal transmitted, 11010; (b) signal received, 11010 or 11011?

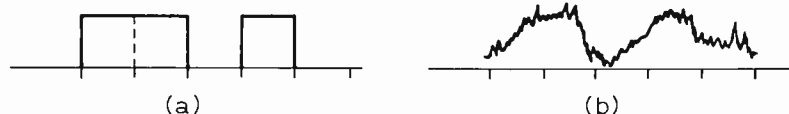

that if you listen to the audio output from a high-gain receiver you will hear noise because the ear can respond to pulses lasting only one tenth of a millisecond; but if you connect an a.c. voltmeter with a response time of about a second, it will probably give a perfectly steady reading. This is because it will have averaged the noise over a TW product of about 10,000.

So "ideal coding" requires first that you construct signals with sufficient mutual differences (or distances) and second that you both construct signals which require a large value of TW and wait until the whole of a signal has been received before you try to identify it. Thus in principle ideal coding involves delay; but if W is of the order of kilohertz then T , and hence the delay, need only be of the order of a second to make TW large.

More recently the question has been put, "Supposing I do exceed the channel capacity defined by formula (1), how bad will the system be?" If we regard all differences between the received and transmitted signals as distortion, it is possible to formulate a relationship between the amount of such distortion and the rate of communication. The latter must take account of the fact that information is not received with certainty. For each received symbol one has only a set of probabilities of the various possible transmitted symbols; and in general different symbols may be made to have different probabilities of error. There results a rather complicated mathematical function called the *rate distortion function* which relates the rate of communication which can be achieved to a specified degree of distortion.

All that we have said so far about finite sets of messages seems to apply readily to telegraphy, where digital signals are natural, but what about telephony, television etc. when the signals are basically in continuous analogue form?

The answer is that continuous analogue signals may be reduced to discrete form by the two processes of quantizing in amplitude and sampling in time. No magnitude is ever known with absolute precision so it can always be equated to the nearest of a number of fixed levels if the latter are at close enough intervals. This process of equating to a pre-selected value is known as quantizing, and is no different from expressing a magnitude by a figure taken to a finite number of decimal places. The fineness of quantizing - the number of decimal places in the analogy - is chosen to give the desired accuracy. The other operation which is needed is sampling in time.

It was mentioned in connection with

formulae (6) and (7) that the maximum rate at which independent pulses can be transmitted through a channel is two per unit of time-bandwidth. This is often called the Nyquist rate, since it was stated by Nyquist in relation to telegraphy in 1928* An equivalent statement in very general terms due to Gabor** is that however one may try to construct a minimum signal element it will obey the law

$$\delta f \cdot \delta t \geq \frac{1}{2} \quad (8)$$

where the equivalent extent of the signal in bandwidth and time, δf and δt , is measured by a statistical formula which can be applied however fast or slowly the signal is cut off in frequency and in time. This is mathematically true because the frequency spectrum of a signal is the Fourier transform of its time waveform; but the cut-off points equivalent to this δf and δt do not correspond in any way with 3dB points. Gabor's theorem of the minimum signal is in close analogy with Heisenberg's principle of indeterminacy in physics, which is generally written as $\delta p \cdot \delta q \approx h$ where h is Planck's quantum and p and q are a pair of conjugate co-ordinates of a particle such as its momentum and position.

The counterpart of the rule about pulse rate is that any waveform of which the Fourier components can be contained in a bandwidth W and of which the duration is T can be reconstructed unambiguously from $2WT$ suitably chosen samples. This is the sampling theorem. If the waveform corresponds to a low-pass band from 0 to W hertz, then evenly spaced samples at two per cycle of the highest frequency are suitable. (This is the form of the sampling theorem which is most commonly used. Other arrangements of $2TW$ samples are possible, and a different sampling pattern is needed for bandpass signals.) The original waveform is reconstructed if the n th sample of amplitude a_n causes the receiver to generate a unit waveform

$$a_n \frac{\sin \pi (2\omega t - n)}{\pi (2\omega t - n)}$$

This method of reconstructing the waveform is open to criticism in theory, though in practice it is good enough provided that TW is large. The difficulty is that the waveform $(\sin x)/x$ extends from $x = -\infty$ to $x = +\infty$ so no one of the waveforms used for reconstruction can be completely contained in the time interval T . But the function is small for x outside $\pm 4\pi$ so the imperfect reconstruction is noticeable only in the neighbourhood of the first and last

samples, and this is unimportant if TW is large. Assuming for the moment that formula (1) is of general application, it says that for a given communication

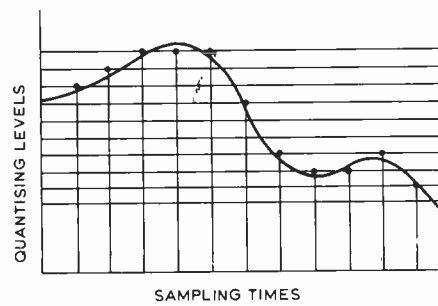


Fig. 4. Digitising a waveform.

rate one can change bandwidth provided one adjusts P/N accordingly, and vice versa. This is a qualitative retrospective justification of systems like f.m. where for a given output the carrier signal-to-noise may be allowed to drop in exchange for the use of a greater bandwidth. The idea of exchanging bandwidth against signal-to-noise was not obvious while we were always thinking of hi-fi transmission of the original sound or other waveform. But it arises naturally from the Shannon approach of communicating signals from a finite and pre-arranged set instead of arbitrary waveforms.

Thus we have shown that information is an objectively measurable quantity; and in consequence communication channels can be designed in terms of the communication of information rather than of the faithful transmission of waveforms.

(Next article: redundancy and the exchange rate)


Sixty Years Ago

The following extracts from the April 1916 issue of *Wireless World* were drawn from an informative article by Wm. S. Purser entitled *The Banjo - A Pastime for Wireless Operators*. "One of the popular fallacies regarding the banjo is that one has to have a black face and sing nigger songs . . . Some talk has been heard in the past of elevating the banjo, and playing classical music upon it . . . The banjo may be regarded as symbolical of good fellowship . . . When purchasing an instrument select a British-made ordinary banjo and you will have a reliable article which will stand any climate . . . Do not be misguided by the expression 'Anything will do to learn on'. The banjo should have five strings . . . Wireless operators and others going on voyages or to out-of-the-way places should purchase strings by the dozen. Having decided on your brand of strings, always get them from the same place . . . After gut strings have been exposed to the sea air for a long time on the instrument they gradually turn green". Follow that.

HF predictions

There are no signs of vigour in current solar activity and expectations of an established upward trend by the end of the year seem optimistic at present.

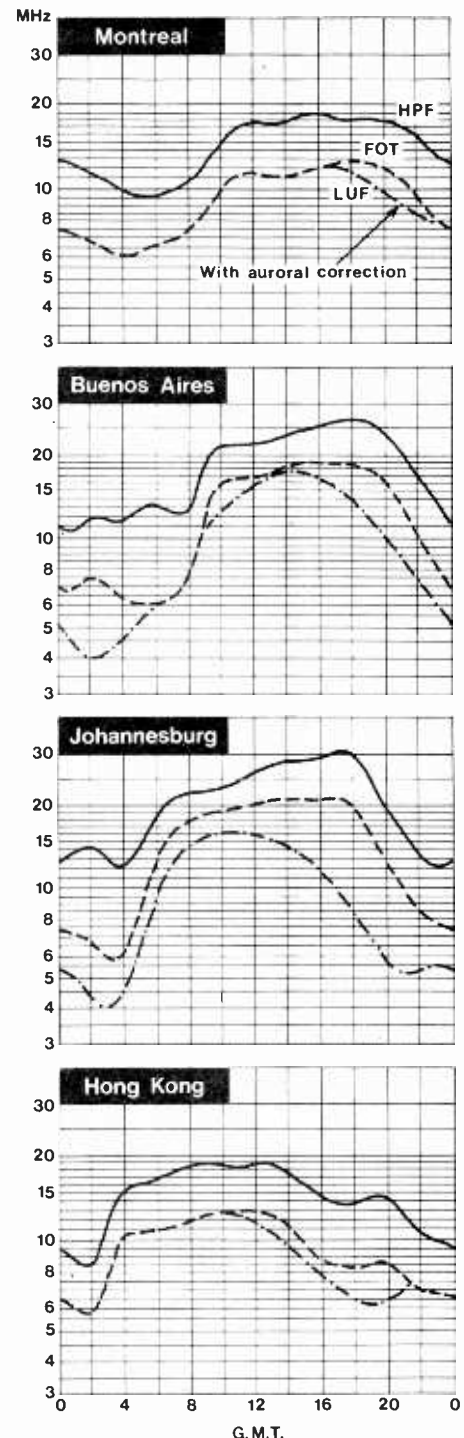Seasonal changes in highest probable frequency (HPF) and optimum working frequency (FOT) curves become evident this month and magnetic disturbances are likely to occur over March 14 to 19 and April 10 to 15.



*H. Nyquist, "Certain Topics in Telegraph Transmission Theory," *Trans. A.I.E.E.* vol. 47, p.617, 1928.

**D. Gabor, "Theory of Communication," *J.I.E.E.*, Part III, vol. 93, p.429, 1946.

FM tuner designs

2 — Improved performance; further facilities

by D. C. Read, B.Sc.

Changes which provide the tuner described in part 1 of this article with some additional control and monitoring facilities and a more flexible input circuit are shown in Fig. 5. The extra gain-controlled r.f. stage comprising the dual-gate m.o.s.f.e.t., Tr_6 , can be arranged to function in different ways according to local reception conditions. Two alternatives are illustrated in the circuit diagram by the indicated possible connection of a $10k\Omega$ resistor between Tr_1 source and the positive supply rail. Circuit operation is as follows.

With $10k\Omega$ resistor. The stage produces either a gain (maximum 6dB) or a loss (maximum 12dB) under the control of the a.g.c. voltage returned from the i.c. This division into two control regions makes the most efficient use of the available 18dB a.g.c. range whereby large incoming signals are reduced in level to prevent oscillator pulling but weak signals are given low-noise amplification before the LP1186 r.f. and mixer stages, so that the noise these produce is added in smaller proportion.

Without resistor. The stage gives low-noise gain with a value between zero and 12dB again depending on the a.g.c. voltage. This arrangement is suitable for tuners used in fringe areas where received signals are low; i.e. where increased sensitivity is required and high-level incoming signals are not normally encountered.

A further possibility makes even more effective use of the m.o.s.f.e.t. characteristics but at the expense of added complexity, particularly in setting up. If the Tr_{10} source is held at a fixed voltage, say by means of a low-value zener between it and the 0-volt rail with a current feed via a resistor to the positive rail, then the a.g.c. range is extended because the source-follower feedback action which modifies the effect of the control voltage on gate 2 is inhibited.

The spread of characteristics for f.e.t. devices is such that, without this stabilizing feedback, the bias on gate 1 needs preset adjustment to give maxi-

● The simpler version described in part 1 comprises tried and trusted circuits, up-dated with refinements intended to make construction, line-up and operation easy; stability and utility are the essential features. The overall design is flexible, and various special facilities can easily be added either during or subsequent to the main construction. These extras include:

- a twin tuned-circuit demodulator which reduces harmonics in the recovered multiplex signal but which needs proper adjustment using a wave analyser or distortion meter
- a stereo-inhibit switch which allows mono reception of weak stereo signals thus giving a 20dB improvement in signal-to-noise
- a buffered and de-emphasized mono feed derived before decoding and intended for tape-recording
- low-pass audio filters to remove unwanted components from the tuner outputs, useful for tape recording either stereo or mono
- a tuning-indicator circuit.

● The more advanced tuner can be provided with any or all of the additions listed above; it also shows further refinements, some optional, which give improved performance in certain respects but which increase the number of necessary adjustments both in setting up the tuner and in its normal operation. These modifications and additions are:

- an extra gain-controlled r.f. stage giving increased sensitivity and stability, and improved signal-to-noise performance. The design of this stage also allows different a.g.c. characteristics to be chosen either as a result of fixed circuit changes or subsequently by adjustment of a panel control to suit various reception conditions
- a more comprehensive a.f.c. system which, like the a.g.c. circuit, can be varied in its effect under external control (R_9 could be a front-panel variable resistor)
- a received signal-strength meter circuit with calibration curve. This meter feed could also be used for stereo-threshold switching.
- adjustable inter-station muting.

mum gain for weak signals. In practice the required bias is easily set by connecting gate 1, actually the earthy end of the input coil, to a variable tapping in a high-resistance potentiometer chain across the zener. Then, with the a.g.c. voltage on gate 2 at its most positive value, the bias is varied until the highest possible stage gain is obtained. The likely performance of such a circuit is a maximum gain of 16dB and a control range of 25 to 30dB.

The circuit which includes the LP1186 module and the impedance-matching stage, Tr_2 , is largely as in the simpler version, the only difference being an additional resistor in the a.f.c. feed. The choice of value for this component, which determines a.f.c. sensitivity, is

dictated by local reception conditions. High sensitivity is given with the value at $47k\Omega$ as shown in Fig. 5. If equal-strength neighbouring-channel signals are present, the degree of control might be too great such that the tuner could be captured by an unwanted station as the local oscillator sweeps through the relevant frequency while changing select the wanted station. If this occurs reduce the resistor value, possibly to low as $5k\Omega$, which still allows a useful amount of control.

Because of the extra gain now available at the tuner front end and the CA3089E module, the i.f. amp IC₂ is not required and the impedance for F_2 is provided in a grounded-base stage, Tr_3 .

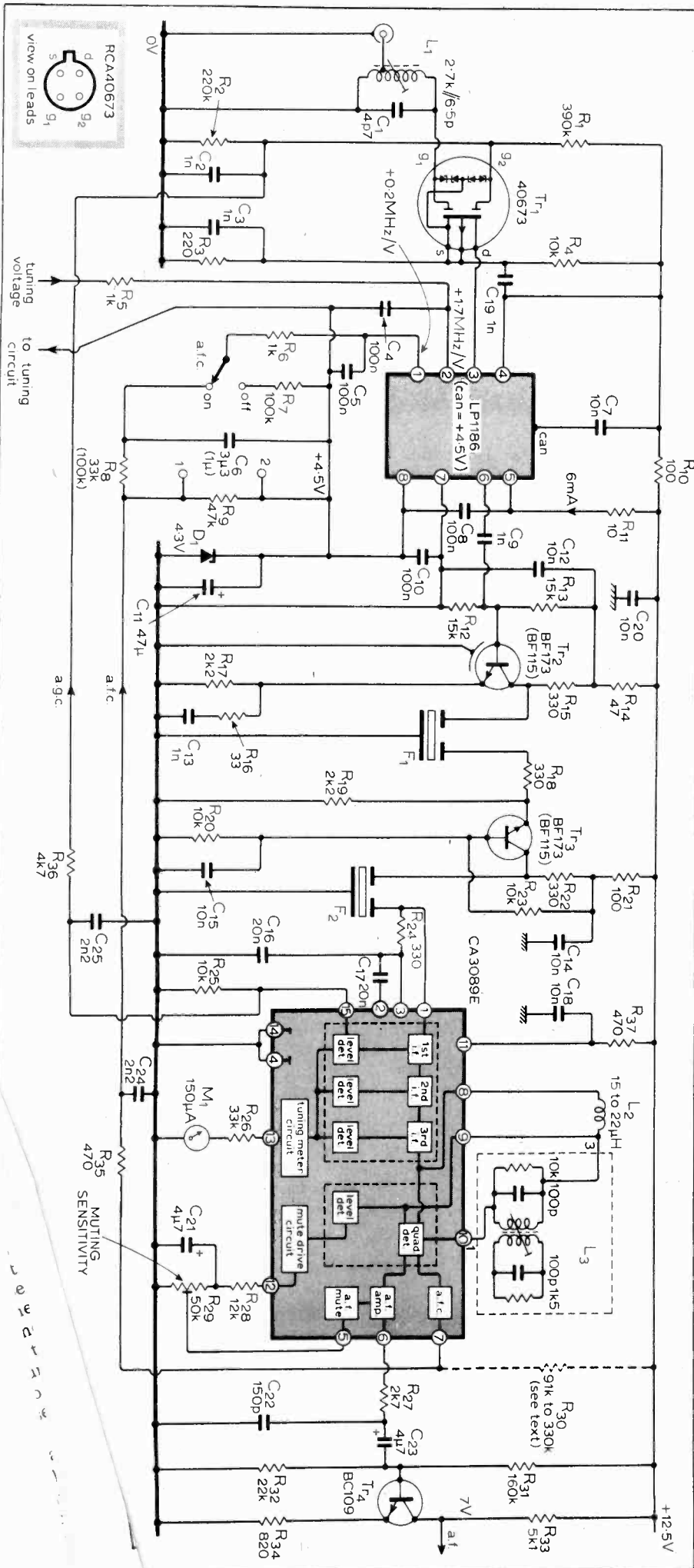


Fig. 5. Improved performance at low signal levels is obtained with this circuit, which uses the tuning and decoder circuits of Fig. 1. Sequence of connections for Tr_2 is b, e, c, screen (on-lead view). On the CA3089E pin 8 corresponds with the tag location.

Although the RCA limiter/demodulator circuit is more complex than its TAA661B counterpart it operates in a similar manner, using an inductive carrier feed to obtain the quadrature reference phase and has the optional dummy tuned circuit to improve linearity of the transfer slope. The external circuit differences mainly concern the use of additional facilities provided by the i.c. Because the a.f.c. signal is derived from a push-pull, open-collector current source in the CA3089E circuit, it is possible that the equal and opposite current condition in a given sample of the i.c. does not occur precisely at the middle of the demodulator S curve. In such a circumstance, a small correcting bias can be provided through a resistor with a value in the 91 to 330kΩ range, connected either to the positive rail, as shown, or to 0 volts, whichever is appropriate. To find the required value and the appropriate supply connection point for this resistor, a method similar to that already described for matching the a.f.c. offset voltage in the simple tuner is suggested; in this instance, however, the S curve is sampled by measuring the voltage across the 150pF capacitor in the pin 6 output circuit.

The completely off-tune condition is used to find the particular voltage value which represents the effective S curve centre and this is then established by tuning to a strong station. Now connect the meter across the a.f.c. sensitivity-controlling resistor, R_9 (points 1 and 2). With the a.f.c. switch off, vary the bias to pin 7 until the measured voltage is zero and remains so with the a.f.c. on. (Note that, as the a.f.c. drive is from a constant-current source, there is automatic compensation for the supply voltage - offset at pin 8 of the LP1186.)

The varying voltage output from pin 13, shown as the meter current in

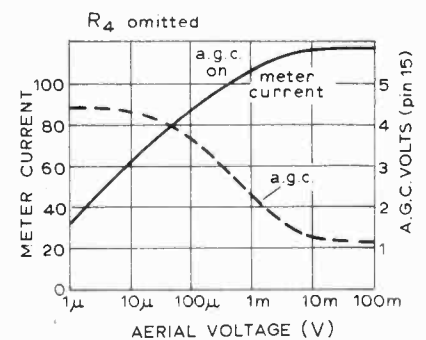


Fig. 6. Curves showing a.g.c. performance and meter current, taken with R_4 omitted. Delayed a.g.c. voltage is at pin 15 on CA3089E.

Fig. 7. Double notch output filter option. Inductors wound on 14mm Mullard Vinkor assembly, with Ferroxcore violet type LA1228. Filter, which has a 6dB loss, should have 25kΩ load.


Fig. 6, is not used in this tuner for stereo threshold switching. It can, however, be fed to a suitable meter circuit to give a received-signal strength measurement by relating the indicated current to the calibration curve shown in Fig. 6.

Setting of the audio muting sensitivity control is done by tuning manually through a number of stations and increasing sensitivity until the noise between these is reduced to a minimum. The demodulated multiplex signal, at about 140mV r.m.s. for ±75kHz incoming-signal deviation, is fed via Tr₁ to the 50kHz low-pass filter, decoder and audio output circuits, already described. An extra stage around Tr₄ provides a small amount of gain to compensate for the lower output from the CA3089E demodulator and presents the correct source impedance to the filter.

Optional 15kHz low-pass filter

The output signals from the tuner contain components at the pilot-tone frequency and the switching frequency. Apart from producing noise, these

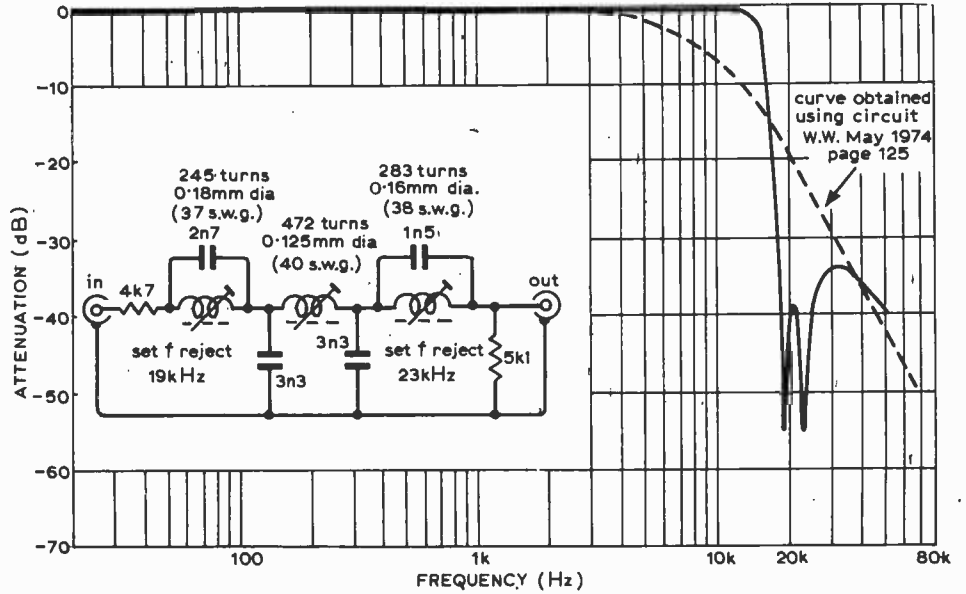Component location and p.c. board layout for Fig. 1. Boards for Fig. 1 and Fig. 5 circuits are available from M. R. Sagin, 11 Villiers Road, London NW2, price £3 inclusive, and parts are available from Manor Supplies, 172 West End Lane, London NW6.



unwanted signals can cause difficulty when the tuner stereo output is tape-recorded. If the recording bias beats with one or other of the out-of-band components, or more probably, with their harmonics, then the product frequency could be within the audio band and the resulting signal would produce interference. Such undesirable effects can be prevented by including a low-pass filter in each of the output circuits.


The audio band transmitted is limited to 15kHz, as a necessary factor in normal pulse-code-modulated signal distribution, so it is reasonable to use a sharp filter cut-off at a frequency just above 15kHz. The circuit of a suitable filter is given in Fig. 7 together with its


response. The second notch, at 23kHz, is at the frequency allotted to a control signal which the BBC uses for distribution-route and transmitter switching. (An active filter would have required a more extensive circuit requiring many more components to achieve the high rates of response change at cut-off and the notch sides.)

Tuner r.f. and i.f. performance

The four most important figures here are those for i.f. and image rejection, which relate to operation in the r.f. section, and for a.m. and adjacent/alternate channel rejection given by the i.f. circuits.

The first two depend on r.f. circuit

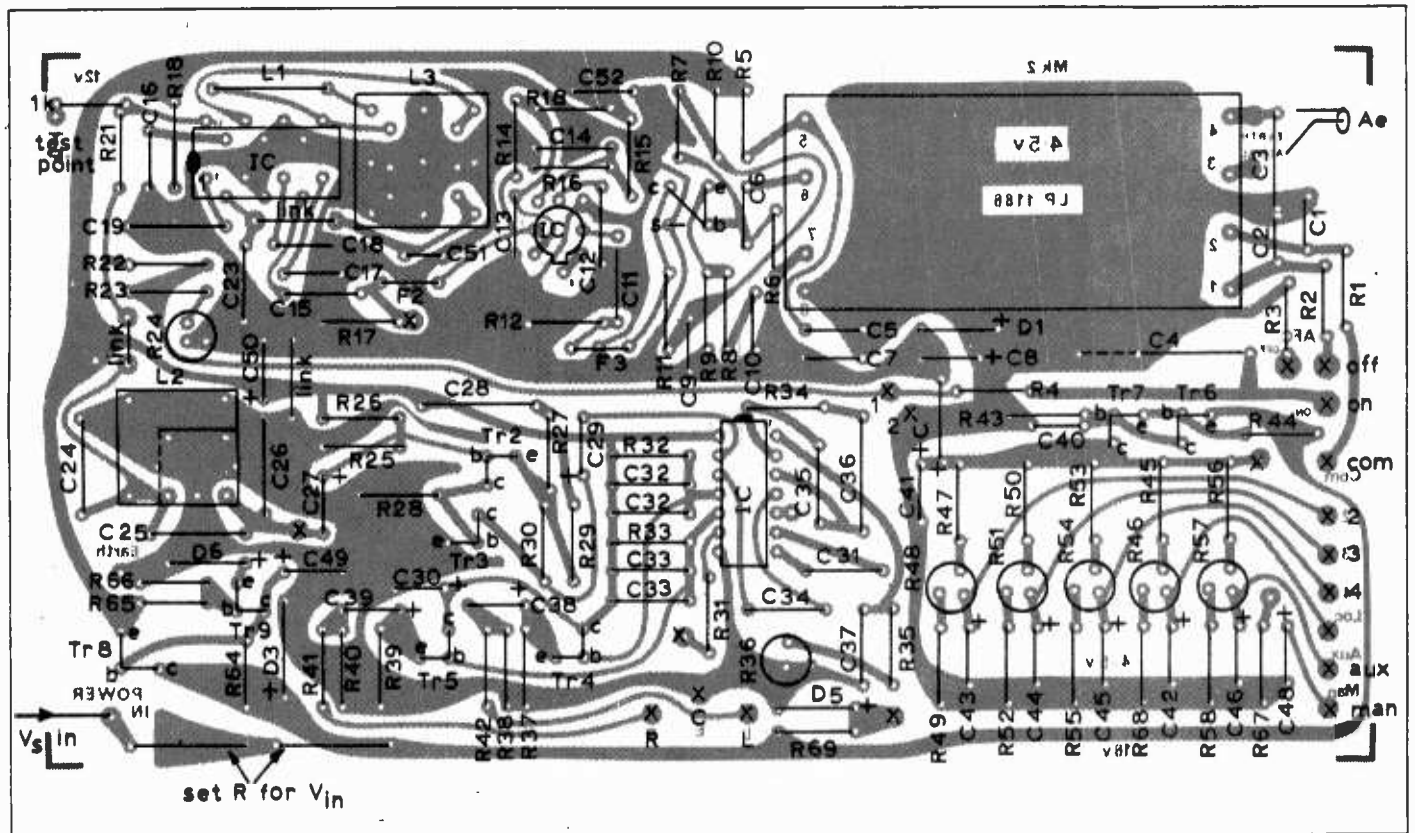

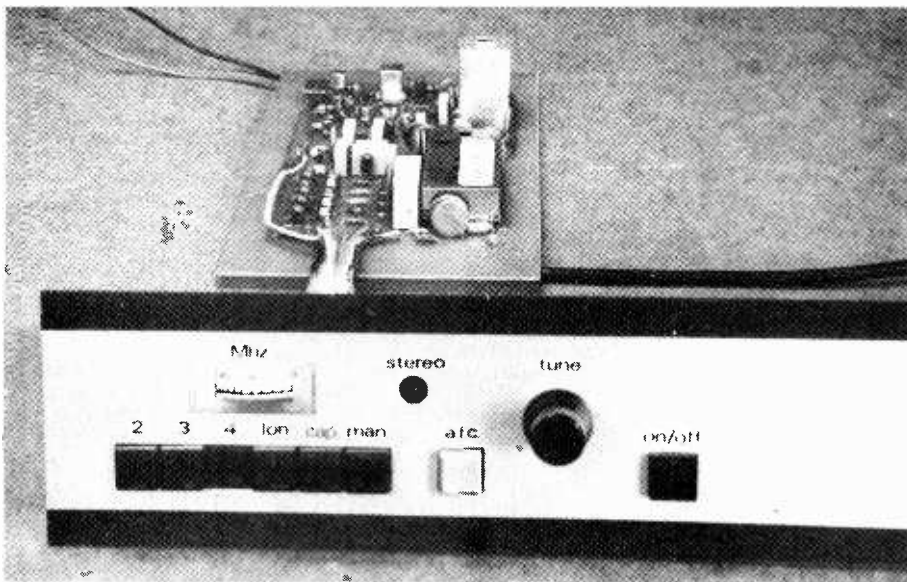

Front panel and controls can be mounted remote from the printed board.


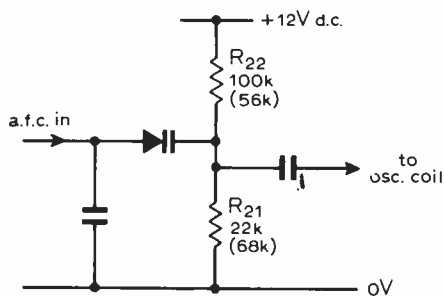


Fig. 8. If Toko EF5600U-1 module is used in place of LP1186 change values of resistors in Toko module to those shown in brackets.

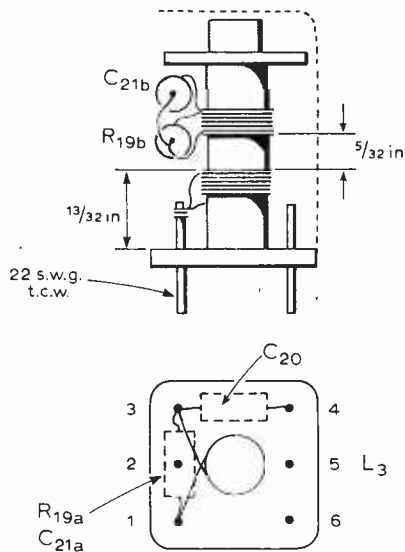

1/4 in former, 6mm (5/32 in dia.) Neosid can 1 3/8 in. high 3/4 in square
 2 violet cores 6 x 1 x 12-7
 both windings 16 turns 34 s.w.g.

L₃ component numbers above as for Fig. 1. Capacitor marked C₂₀ is omitted in Fig. 5. Simpler coil uses 10 turns on Neosid E3 assembly. Phase shift coil is a Sigma SC10 screened r.f. choke, or Painton equivalent. L₂ Fig. 1 is wound on a Mullard Vinkor assembly with 14mm violet core and 172 turns of 38s.w.g. enamelled wire. L₁ in Fig. 5 is 8 1/4 turns, tapped at 1 1/4 turns, on Neosid 6mm former with 22s.w.g. wire.

selectivity and in both versions are determined by the performance of the Mullard LP1186 module. The specification for this quotes an i.f. rejection of 65 dB for 95MHz input and an image rejection of 40 dB.

If better r.f. performance is required, this can be easily obtained but at increased cost by replacing the LP1186 with the Toko type EF5600U-1 tuner module which contains four varicap-controlled tuned circuits and has image and i.f. rejection figures both quoted as 90 dB. A module of this type has been successfully fitted to the author's tuner with some small modifications, as below.

Fitting Toko front-end

Change of tuning voltages. For tuners operated in the London area, the necessary changes to pre-set tuning voltages for stations at the ends of the band are:

	LP 1186 (w.r.t. pin 8)	EF5600U-1 (w.r.t. 0V)
89.1 MHz (Radio 2)	2.4V	3.5V
97.3 MHz (LBC)	6.0V	7.5V

Change of d.c. offset and a.f.c. centre-voltage. The EF5600U-1 tuning voltages are referred to 0 volts instead of the +4.5-volt offset present at pin 8 of the LP1186. This difference necessitates two modifications. First, the 4.3-volt zener, marked D₁ in both diagrams, must be replaced with a shorting link. Second, in the Toko module, the maker's circuit diagram shows that the a.f.c. circuit involves a separate diode with a 2-volt bias obtained from resistors numbered R₂₁ and R₂₂ as illustrated in Fig. 8. Because this circuit is intended for operation with an incoming a.f.c. signal centred on 0 volts, it must be modified to suit the +4.5-volt centre value which obtains in the tuners. The suggested changes are marked in parentheses in Fig. 8, giving an offset of about 6.5 volts.

The figures for a.m. rejection, quoted from the manufacturers' data for 30% a.m., are -45dB for the SGS TAA661B and -55dB for the RCA 3089E. Performance in respect of adjacent/alternate channel rejection is determined by the i.f. pass-band response characteristic which, for both tuner versions, is the resultant of two FM-4 ceramic filters in cascade. These components were also used by Nelson-Jones, and a curve showing the insertion loss for the combination appears in his original article. This gives the 3dB-down bandwidth as ±110 kHz, and off-tune loss figures of 40 dB at ±200 kHz and 60 dB at ±280 kHz. Rejection of unwanted channels is thus more than adequate.

Correction. In Fig. 1, March issue, the value of C₁₂ should be 47nF and not 47µF, R₂ should be 1kΩ and not 100kΩ, and D₆ should be a 6.2V zener diode, labelled C6V2. Supply voltage to Fig. 4 circuit is 13V and not 11V.

Literature Received

Radio-frequency shielding materials and their use are treated in a simple manner in a handbook from Metex. R.f. gaskets are fully described in theory and practical applications data is provided, together with detailed information on shielded enclosure windows and ventilators for shielded cubicles. Walmore Electronics Ltd, 11-15 Betterton Street London WC2H 9BS. WW401

An application note on a thermal r.m.s.-to-d.c. converter is published by Burr-Brown. The device exhibits a thermal time-constant of 65ms and a characteristic which is linear and repeatable to within 0.05% over 30dB. It is still accurate to within 2% at 100MHz. Applications include amplifier gain measurement, thermal protection and r.m.s. voltage regulation. Burr-Brown International Ltd, Permanent House, 1y Exchange Road, Watford WD1 7EB. WW402

Aluminium aerial towers are the subject of a leaflet sent to us by Fred Franke Inc., PO Box 2806, 1639 Old Dixie Highway, Vero Beach, Florida, USA. The towers are crank-up, extending types, forty, fifty or sixty feet in height and of triangular section, and a selection of bases and mounting brackets is described. WW403

The British Standards Institution has published group 09:1976 of part 3 of BS4727, which is a glossary of terms used in waveguide engineering. The publication is obtainable from British Standards Institution, Sales Department, 101 Pentonville Road, London N1 0ND at £3.10 by post. WW404

Relays with mercury-wetted contacts from Elliott are described in a booklet which gives mechanical information and electrical characteristics of twelve ranges of relays. Application information on contact protection, screening, etc. is included. Elliott Relays, 70 Dudden Hill Lane, London NW10 1DJ. WW405

Aerial information for equipment in the m.w., v.h.f. and u.h.f. range is presented by Aerialite. The latest to be published includes a leaflet on indoor aerials, two on u.h.f. types and a description of the mounting accessories made by the company. Aerialite Aerials Ltd, Whitgate, Broadway, Chaderton, Oldham, OL9 9QC. WW406

An f.m. radiotelephone is illustrated and described by Telefunken in a new leaflet. The 10-channel Teleport VII covers the 80MHz, 160MHz and 460 MHz bands at 2.5W r.f. (1W at 460MHz). Bayly Engineering Ltd, 167 Hunt Street, Ajax, Ontario, Canada. WW407

Research Notes

Great balls of fire!

According to a NASA report, glowing spheres have been noticed in almost half the cases where an observer happened to be very close to a stroke of lightning. The nature and indeed the very existence of this ball-lightning has been the subject not only of heated debate among theorists but more recently of some seemingly dangerous research in France.

Scientists at the Commissariat à l'Energie Atomique (CEA) and Electricité de France (EDF) have been photographing lightning discharges caused when rockets trailing thin steel wire were fired into thunder clouds. During the course of these experiments, some twenty artificial lightning strokes were produced and filmed. According to a report in *Nature* (vol. 257, no. 5523), triggered lightning, like upward natural lightning, begins with a slow discharge in the kiloampere range with a rise time longer than $10\mu\text{s}$ and a total duration of several tenths of a second.

But although nothing resembling some of the more exotic stories of ball-lightning was noticed, there is now firm photographic evidence for balls of lesser degree. During some long-lasting lightning strokes ($> \frac{1}{2}$ sec) "luminous spheroids" some 40cm in diameter were observed towards the end of the discharge and, according to the French researchers, their properties are entirely consistent with those of hot blobs of gas. So it seems that lightning folklore and tales of monster blobs of plasma can still thrive on exaggerated stories of the one that got away!

Fibre optics for chemists

Readers of this journal won't need reminding that progress in fibre optics has now reached a point where "light-guides" are very competitive with r.f. waveguides for data transmission. But if the highly critical design criteria for light-guides have provided headaches for some researchers, their less desirable properties have nevertheless resulted in a highly sensitive method of chemical analysis.

It's a form of spectrophotometry developed in the United States in which the transmission properties of a light-guide are intentionally altered by the presence on its surface of microgram quantities of the chemical being evaluated. The refractive indices of the light guide and of a special polymer coating carrying the test chemical are so arranged that light is refracted in and out of the coating as it passes along the guide. In this way a small change in the optical properties of the guide/coating interface are amplified to a very considerable extent. So sensitive is this technique that polymers containing sub-microgram quantities of cyanide ion can alter the light transmission of a guide by over 50% compared with a pure polymer coating. (*Nature*, vol. 257, no. 5528.)

Natural magnetism attracts the birds

Dr William Southern, an American biologist writing in *Science* (vol. 189, no. 143) has evidence to suggest that v.l.f. radio waves affect the migratory pattern of gulls. His experiments were conducted on frequencies around 50Hz using equipment which the US Navy has developed for submarine communication (Project Sanguine). The birds, chicks a few days old, were taken from their colony several miles away and released near the transmitting aerial, some at times when the transmitter was operating and some when it was inactive. The birds released during non-radiating periods were found to migrate in a direction consistent with those in the parent colony, whereas during transmission the migratory pattern became completely random. These results add considerable weight to current theories that birds can orientate themselves to the natural magnetic field. (The writer however, has very little evidence that his amateur transmitting activities in any way deter marauding wood-pigeons!).

Microminiature . . . Picominiature . . . where next?

A comparison of today's microprocessor chips with bipolar transistors of only a decade ago might well convince even the most sceptical that pinhead-sized computers are merely a few years away. But before you go rushing out to buy the latest in 25 microwatt soldering irons (or perhaps commit suicide), be comforted: the end is nigh. A paper by J. T. Wallmark (Inst. of Physics Conf. Ser. No. 25, 133) concludes that by the time present-day circuit elements have been scaled down by about five times, i.e. to around $2\mu\text{m}$, basic laws of physics will step into play and limit any further size reduction. The limitations according to

this author lie not so much in the technology necessary to produce finer and finer patterns, but intrinsic barriers such as insulation breakdown and excessive current density. One other major problem is that with diminishing size, local variations in the concentration of doping atoms result in excessive spread of device characteristics. So, in the absence of any fundamental discoveries in solid state physics, we might as well forget any dreams about unlimited pocket computer power – that is unless we're prepared for it to think slowly – like people.

Grains of metal in an insulator

Mixtures of conducting and non-conducting materials are interesting to solid-state physicists in their own right but are also now beginning to be used to make devices. Dr Ben Abeles and his co-workers at RCA Laboratories, Princeton, USA, have been exploring the conducting properties of films formed when metals, say gold, and insulating materials such as silica are sputtered together. The metal forms well-dispersed spherical particles in an insulating matrix but the particles are close enough together that, even though they do not touch, electrons can tunnel between them. Tunnelling is a quantum-mechanical phenomenon which does not allow high current to flow but can be controlled more effectively than metallic conduction. One new application for these effects is described in the announcement of a "granular metal semiconductor vidicon". In this, the light-sensitive target consists of the following layers deposited on a glass faceplate: transparent conductive tin oxide, cadmium selenide and granular metal, sputtered from a composite gold-silica target, to a thickness of 400nm.

As is usual in a vidicon camera, the target charges up in proportion to the light falling upon it and an electron beam is scanned over it as a means of reading out the charge pattern. The advantage over targets which have been used up to now, such as those which have the semiconductor left bare or others which have a pure silica layer over the semiconductor, is that the granular metal layer prevents blurring of the image (which occurs on the bare target because of excessive conductivity) and it also eases the flow of image information to the electron beam (which is excessively slow for the pure-silica coated target). C. R. Wronski, Ben Abeles and Al Rose, writing in *Applied Physics Letters*, vol. 27, 91-92, put this more precisely, explaining that photo-generated holes have to be forced through the pure insulator under high fields, while tunnelling allows the same process to be done in the metal-filled insulator under much lower fields.

Letters to the Editor

CONSULTANTS, PROSTITUTES AND CHAUFFEURS

There is chalk and cheese, there are prostitutes and wives, there are also in our domain consultants and consulting engineers. As someone who, starting without the aid of either capital or contracts, has run a successful consulting engineering practice in telecommunications and electronics for rising twenty-five years, I feel I must comment on the article "The consultants" in your November issue.

I have always felt that consulting must be done from the background of complete independence from commercial affiliations and any other loyalties. Independence means just that. If you are paid by someone else and/or use their property for your own purposes you have no higher status than the chauffeur who uses his master's Rolls for weddings and funerals while the latter is out of sight.

I am not the least surprised that your correspondent has found such dissatisfaction with "consultants" — highly likely I would say — but give the real chaps a break. We have had clients in all five continents. We have had large public companies in our domain — sometimes for a period of years — and they wouldn't come back if they were not satisfied, but it is true that more often than not they do not wish it to be known that they used us.

The World Bank will not underwrite any engineering project without the *imprimatur* of consulting engineers. Surely this shows the value, the competence and status of the consulting engineer.

C. A. Henn-Collins,
Henn-Collins Associates,
Castel,
Guernsey.

John Dwyer is deserved of high praise for his clearly written, unbiased, frank, fearless and interesting exploration into the ways and means of independent engineering consultants, and for illuminating certain dark corners.

My own consultancy activities stem from a small family business and much of the money it makes is ploughed back into the purchase of new plant and equipment to enhance the value and quality of the work undertaken for our clients and readers of the hi-fi magazines in which our detailed review

and test reports appear. In spite of the expensive plant we are obliged to purchase and maintain from our own resources, our fees are far more modest than those of the consultants referred to in the latter part of the article; and I feel that Derek Bond in his summing-up warning means "... if they're inexpensive (not cheap) and good we'll use them ..."

Like James Moir intimates, we are also experiencing the somewhat unfair competition from college-based consultants, and were very surprised to read that equipment, plant and facilities from the public pocket are, in effect, being used in competition with the consultant who relies essentially on his fees for a living. It is noteworthy that North London Polytechnic at least has blocked one-third of the flow of money from essentially college-financed personal enterprises to private pocket, but this still nevertheless presumes that two-thirds of the money goes as a cheque into the bank account or as pound notes into the pocket of the consulting lecturer, etc. What about other polytechnics and colleges — is it accepted practice for all the income so derived to go to the college official?

One might be inclined to say "so what, good luck to them", except for the startling attitude-reflecting statements, such as "... money isn't the thing that counts ..." (it may not be to the chap getting a fat salary from public funds for his twenty-six-hour week when it is purely pin money, but it certainly is to the professional consultant working his hundred or more hours a week for possibly less money) and "... didn't charge nearly as much as outside consultants ..." (a blatant admission of unfair competition based on public money at the expense of the professional).

Clearly, if all this is true, then the private consultant not in a position to command the use of thousands of pounds worth of equipment, plant and facilities at public cost for nothing is faced with overwhelming and singularly unfair competition. The depreciation and running costs of a small lab could well be up to £10,000 per annum. Apart from having this sort of yearly expenditure immediately available for free the college chap would appear to acquire at least two-thirds of the consulting fee for himself (perhaps the whole lot apart from NLP) plus his normal salary. What an incredible situation if it is really a fact!

From the article, it appears as though it could be. The implication being that provided the NLP chap puts about one-third in the pool all is well. The article fails to say what happens to the pool of money — whether it is returned to the public funds or shared out at Christmas time!

Perhaps officials from colleges other than NLP who undertake such consultancies with the college's plant, facilities, etc. would care to clarify the scene, saying exactly where the client's money goes, and whether any charge is made to the consultant.

I also often wonder what happens to the fees received by the technician, etc. for equipment reviews, he undertakes for the hi-fi magazines using college plant, equipment and facilities, as often indicated by the review. Does he charge less for the review than could a reviewer relying upon the income to live and pocket all the fee? Does he charge the full amount and return it to the public kitty; or does he keep some for himself and return some of the college? Then there are all the other researches written up in the magazines and paid for. Who gets the fees?

Answers to questions like these are very

important to the private consultant who has to purchase and maintain his own lab and premises, pay the rates and rent, pay his own telephone bills, pay for his own heating, his own office and secretarial staff, who cannot advertise for business and cannot belong to a trade union, giving him some idea of the unfair competition he is now facing and how long he will be able to stay in business.

Gordon J. King,
Gordon J. King (Enterprises) Ltd,
Brixham,
Devon.

WAS BAIRD FOOLING THE PUBLIC?

The plea in your January issue for a "serious study of the business and technical aspects" of the 30-line Baird activity may well serve to put an end to this confused affair. ("John Logie Baird and the Falkirk transmitter," pp 43-46). Annotated references in the article to reputable proceedings about achievements are intended to convince but give to today's reader a false picture of the happenings of 50 years ago. It should be appreciated that Baird never successfully demonstrated television. Being without a method of synchronisation over a distance, there could be no such event. At every attempted demonstration this primary need had to be faced and contrived. The bringing together of radio transmission, in itself having ideal properties for television purposes, and the trundling mechanical image analyser, was quite incongruous.

Proper electrical circuits for conveying the light values were not to be found in the various Baird set-ups. This was the time of early talking films and picture telegraphy when the stable photocell and bright recording lamp were both readily available. Baird claimed to use visual purple as the light sensitive material.

"Fibre optics," a modern term of wide application, is brought into the article. True, the possibility of using a bundle of fine internally reflecting glass fibres for channeling an image falling on a closely divided grid was well known, a scheme which avoids synchronising and light handling difficulties. The modern plastics as used in optical cables give a high degree of light insulation with but little loss. Fibre optics offer high definition remote viewing with the possibilities of image intensification. These things were not part of the Baird programme, being generally inapplicable to a radio service.

Baird hoped to convey to the public with his inadequate devices that he was in possession of a commercial proposition of considerable potential value. This he aimed to sell by pretence and to that end demonstrations had to be conjured and reports by staff contributors commissioned for publication. The pattern of the *Wireless World* article, almost line by line, shows the marks of this policy. Displayed advertisements in the daily press of the time said "Television is Here." A "Home Televisor" appeared, so here all was revealed for public judgement. The "Televisor" was a typical well made. Plessey product. With a monitored signal input (Big Ben clock face) and in an equipped laboratory where auxiliary gear, by way of a heavy duty synchronising and vision amplifier was to hand, the Baird Televisor was shown to be a failure in fulfilling its intended purpose.

This was the end of the 30-line part of the story which is as far as your article goes. No

radio enthusiast was fooled. Radio societies, then much attended, were amused. *Wireless World*, always ready to pursue and report, remained silent.

F. H. Haynes,
Bovey Tracey,
Devon.

PHASE EFFECTS IN LOUDSPEAKERS

It is, I think, generally accepted that phase distortion exists, inasmuch as it can be mathematically proven, or perhaps better, displayed on a c.r.t. It is also, I believe, generally accepted that the human brain in some mysterious way "integrates" the incoming signal in the same way as it does a harmonic interval, say a major third, to sound as it does and not as a c.r.t. shows that it should. In the same way (broadly speaking) a received mixture of primary colours is seen as a specific hue. At least, by most of us it is: there are those who do not have this ability visually, and it does not seem beyond belief that there are those who, similarly, lack the audio integrating function which most take for granted, but is not easily quantified in the same way as, say aural frequency response.

I know, for instance, that my hearing cuts off above 17kHz, whereas 20 years ago it was 22kHz (when it was still kc/s) but this is an easily measured function. Perhaps we need a consultant neurologist to enter the discussion?

A. J. Gamble
Ormskirck
Lancs

The long dead and buried question of square waves not being heard differently when considerable phaseshift is applied to the different harmonics, is disinterred again. This despite the fact that no designer of linear phase speakers uses the argument that *because* of the ability of a speaker to reproduce a square wave it will sound better. This is always presented as just one means — and no more — to show that it really possesses phase linearity. It is a "tool" and nothing but a tool and presented as such.

As to audibility of linear phase, Mr. Harwood (conveniently?) completely ignores the articles on "Aural Phase Detection" in the *Journal of the AES* (vol. 22, Nos. 1 and 10) by V. Hansen and E. R. Madsen, which go a long way indeed to proving the importance of investigating this aspect in sound reproduction.

Quite different signals than square waves were extensively used, far more related to musical transient sounds. Altogether it was a very thorough investigation into human perception, with particular regard to the desirability of phase linearity in music reproduction. Far more convincing indeed than the questionable experiments by Mr. Harwood in which only NON linear phase seems to have played a part.

Personally I had the opportunity of investigating loudspeakers that laid claim to phase linearity, to a greater or lesser degree, from France, Germany, Denmark, Japan and England. Most of them first as prototypes and later on as the finished product.

Perhaps the most striking experience was the first in which I and a few other selected people were able to compare two identical loudspeakers, identical as to size and units used, where the first was equipped with a carefully designed, but conventional 3-way crossover filter, and the second with a filter that ensured linear phase from about 300Hz upwards.

Although the first was judged to be a very good speaker of very wide response and an extremely well balanced sound, the difference could be called enormous. Especially transient response was improved to an incredible extent. This concerns pure quality, but the other aspect, the stereo image, also changed in a startling way. By comparison the first pair (for pure quality only single speakers were compared) suddenly gave the impression of presenting a confused though reasonably wide stereo-stage with little depth.

In the meantime I have listened to, and tested extensively, the other ones mentioned. It cannot just be a coincidence that five (!) loudspeakers from five different countries ALL showed the same striking improvement in transient response. The last, one of British origin (this cannot be any other than the DM-6 of course) being an absolute winner and in some ways even beating an electrostatic speaker.

Yes, square waves too! In all cases I was able to make oscillograms in an ordinary, but well damped room, of square waves with the microphone at 1 m distance. Again, no proof of better music, but of linear phase. Single sinewave pulses, and/or half waves have proven to be of more use to confirm in technical tests, qualities heard with music. Symmetry and ringing can be judged over the whole frequency range and in my experience are in 90% of the tests, consistent with subjective experiences. In the case of p.l. it is moreover remarkable to observe the steady position of the reproduced pulse when the microphone is moved vertically, no significant phaseshift can be observed, even in crossover regions.

The transfer function of any link in a reproduction chain should be described by its frequency and phase response; without linear phase accurate reproduction of waveshapes, and envelopes is impossible. To state that this is of no importance takes someone of perhaps great bravery, but more likely, one with prejudices who still thinks of music in terms of simple sinewave structures in which simple evenly related harmonics play a part only. It is of course, in particular, the transient nature of most musical sounds, with its highly complicated structure that is so important to reproduce well. Any system that shows large improvements in transient handling should be taken very seriously indeed, if of course all the other long known important parameters are not neglected. Signs of this were found in some of the prototypes, where some preoccupation with phase made bass or treble suffer. Not however apparent in most of the finalized designs. No, if Mr. Harwood were right, a lot of music should be rescored to fit his conclusions!

The linear phase loudspeakers I was privileged to handle proved to me and all my "guinea pigs" beyond all reasonable doubt that it is an important step forward in striving for perfection.

J. Kool,
Technical Editor,
Luister
Amersfoort,
Holland.

While I have to admit that H. D. Harwood's article on the Audibility of Phase Effects in Loudspeakers (*Wireless World*, January 1976) was scrupulously fair with regard to the facts, I would venture to suggest that a good deal of emotional weight went behind the thesis that phase-linear speakers are a 'con'. For readers interested in the other side of the coin, could I perhaps publicize an article of mine (1976, *Hi-Fi News Annual*) in which some of the recent evidence demonstrating the ears' sensitivity to phase effects is presented in detail. I have also outlined there the way in which this evidence has modified current thinking about the mechanisms involved in the ear/brain hearing system.

However, rather than becoming entrenched in our own respective camps and flinging mud at the opposite side, it seems to me that the way forward is to accept the findings of both sets of experimenters, and look for an explanation which admits of both results.

Let me summarise the two, apparently mutually exclusive viewpoints. On the one hand the psycho-acousticians (if they'll forgive the phrase!) have shown that in special circumstances and with special kinds of signals, the ear is capable of detecting 'phase distortion'. The audio-engineers, on the other hand, have demonstrated many times that on typical programme music, phase shifts go unnoticed. Could there be an explanation which is consistent with both these results? Consider the following. Suppose that the transmitting of information is a bit like playing 'Scrabble' (to steal a Magnus Pyke-ism), and suppose that phase shifting is a bit like rearranging the orders of the letters in the words. If I were now to ask my audience to compare the sequence SEPAH with the phase-shifted sequence ASHEP, they might well retort that the information conveyed by both sequences is zero, and that therefore, in information terms, both these sequences are identical. If, however, I presented them with the sequence PHASE, comprehension might dawn!

In other words, if the phase information in a signal is already jumbled, a re-jumbling could well make no difference at all to our perception of the signal — the brain just rejects the phase-information channel, and derives instead, as much information as it can from other channels. If though, the phase channel is pregnant with information (e.g. the phase relationships are undistorted from source to detector) the brain might just be able to put this information to good use.

In terms of audio-programme material, the initial jumbling of phase information occurs long before the signal reaches the speaker — it occurs whenever a multi-mike recording technique (with its attendant mixer desks and pan-potted imaging) is used. What does a bit more phase-jumbling at the speaker end matter here?!

It has been argued that phase distortion occurs even before the microphone stage, because multiple room-wall reflections (the ingredients which make for a satisfactory reverberent acoustic) generate a resultant pressure wave at the microphone (or ear) which has a time profile dependent on the position of the source, the properties and positioning of the reflecting surfaces in the room, and the position of the listener. If the phase information really is lost at this stage, then phase-linear-anthings really are a con. (And that includes square-wave tested amplifiers too!) It would appear, however, (even though the experimental evidence is as yet very tentative), that the ear/brain is.

capable of distinguishing between direct and reflected sound. If this result is confirmed, we can see that the relative phase of the source's harmonics is preserved in the direct sound reaching the ear. What is more, comparison of the phase information in the direct sound with that in the reflected sound might be an important direction-locating mechanism in the 'live' acoustic of the concert hall.

In the meantime, I'm not averse to any development which reduces the phase distortion properties of the recording chain, as long as I am not charged exorbitantly for the privilege.

K. A. Hodgkinson,
Open University,
Milton Keynes.

In Mr Harwood's article, and in the view of many other eminent men in the audio field in the "anti-phase" lobby, one factor stands out as the fundamental argument — that until someone can demonstrate that phase response is important to sound quality on musical signals, they will continue to believe that phase is unimportant. Often this is accompanied by details of experiments "proving" that phase distortion is inaudible, and sometimes the nature and conditions of the experiment give the impression that the proof of a predetermined objective was the purpose of the test. The debate on phase is not going to end unless those who are primarily interested in high quality sound reproduction rather than pro- or anti-phase arguments, come to conclusions based on unbiased listening tests conducted under fair conditions.

There can be no doubt that since linearity of phase response is fundamental to recreating the original wave shape received at the microphone, it can be no disadvantage to eliminate phase distortion throughout the reproducing chain, including the loudspeaker. It can conceivably be argued that a limited amount of phase distortion is not detectable by the ear, but it has been conclusively established by, amongst others, telephone companies that large amounts of frequency dependant time delay (phase distortion) can not only distort speech, but make the human voice totally unintelligible, and phase correctors have to be used in long-distance cable communications. Thus, the debate really centres on how much phase distortion is detectable by the ear, and especially whether the amount and quality of phase distortion in conventional loudspeakers is above or below this limit. It will serve no purpose to add to the debate by quoting experiments, or arguments about phase distortion. But a certain amount of care must be taken in listening tests, without which tests would not be valid.

To start with, testing for wave shape distortion with a microphone in a living room is extremely misleading. Reflections from room walls picked up by the microphone are indistinguishable from the direct sound, whereas the ear finds it quite easy to concentrate on the direct sound, presumably because of the slight delays that occur. Thus while we prefer certain acoustic conditions to others in particular cases, one can always recognise a voice or instrument, irrespective of its environment. In order to test with musical signals, a primary condition must be that the source, together with the reproducing chain, must have a linear phase response. If one were conducting a test to find the limits in variation of frequency response in a loudspeaker, before the difference became

audible compared to a flat frequency response, one would naturally arrange for the music source to be recorded with microphones that also had a flat frequency response.

Similarly, if phase distortion is under test, a sound source and reproducing chain which do not have a linear phase response will mask the phase distortion originating in the loudspeakers. If in addition one is used to the type of sound reproduced by a high quality system, one can quite easily be misled into believing that phase is unimportant. This is not to say, as everyone will agree, that reproduction is perfect. No one, to the best of my knowledge, has any doubt that the finest system in existence is still imperfect.

It is, however, unwise to reject phase, as one of the factors giving rise to imperfections without comprehensive tests under relevant conditions. A musical source with undistorted phase response may be difficult to find among commercial sources. One suitable method of recording such a signal for test purposes would be a mono recording using a single high quality microphone and a high quality tape recorder.

Finally, as the purpose is to judge the effect of phase distortion only, and not the quality of the reproducing chain, it is relevant to point out that no two loudspeakers sound exactly alike. To make an A-B comparison, therefore, only one loudspeaker should be used, and this must be one with a minimum of conventional faults. In addition, it must have linear phase response. Phase distortion can be added easily by an electronic phase shift unit, at a high impedance stage of the amplifier.

Phase distortion, artificially introduced, should reflect the characteristics of conventional loudspeakers. Thus, with conventional crossover, or non-staggered units, phase rotation is limited in angle and the frequency region it occurs. Thus a second order filter network has a 180° rotation and a third order 360°, in both cases the rotation occurs mainly in the two octaves on either side of the crossover frequency. Mr Harwood's all-pass networks have a constant rotation of 30°, 60°, and 90° per octave, which do not have the same characteristics as any known loudspeaker. This alone invalidates Mr Harwood's tests as far as loudspeakers are concerned, but experience in this field shows that even this kind of steady rotation can be heard under the right test conditions.

It should be noted that phase distortion is not something that is easily recognised, as we are not conditioned to listen for phase-distorted sound. Differences between live and reproduced sound can too easily be attributed to other causes, without recognising the influence of phase. The relevant criterion, in the first instance, must therefore be that a difference should be heard in an A-B test between distorted and undistorted sound. The relevance of phase distortion in sound reproduction will then have been established. S. K. Pramanik,
Bang and Olufsen a/s,
Denmark.

CURRENT DUMPING AUDIO AMPLIFIER

Mr Walker's ingenious "current dumping circuit" (*Wireless World*, December 1975, p.560) undoubtedly is one way of solving the difficult problem of cross-over distortion in

amplifiers. The only claim I would reject is that it is "feedforward".

An essential feature of feedforward is freedom from interaction; i.e. the voltage at the emitters of Tr₁, Tr₂ (Fig 2, p.561, December 1975, WW) should have no effect at the output point of amplifier A. This basic criterion is not met.

The equation given in Fig. 1:

$$I_3 = (V_{in} - I_4 Z_4) \frac{Z_2}{Z_1 Z_3} + \frac{V_{in}}{Z_3}$$

confirms this.

Feedforward can very easily make distortion worse; indeed I have no doubt that Black found this when his amplifiers went out of adjustment, which may be why when he discovered negative feedback he abandoned feedforward.

To make feedforward work another ingredient is necessary — that of "rigidity of interconnection" (Fig. 2, October 1974, WW p.367), i.e. that the error voltage at the output of the main amplifier A₁ should be rigidly interconnected to the output of the subsidiary amplifier A₂ V_d so that its waveshape is accurately reproduced. For this reason it is important not to add transformers outside the negative feedback loop.

These two principles together produce "error takeoff" which has the ability to reduce distortion by an arbitrary amount and at the same time maintain stability.

Mr Walker's circuit in my view is an effective application of negative feedback. A. Sandman,
Royal College of Surgeons,
London, WC2.

Mr Walker replies:

The feedforward ancestry of current dumping can be clearly seen if we disentangle the circuit to show the error amplifier and the main amplifier as separate entities. This is shown below.


The bottom amplifier has a mutual conductance, G_{m2}, feeding current into the load via resistor R. Current feedback developed across R is fed back to its input. The top amplifier is the "error" amplifier and has a mutual conductance G_{m1}, feeding into the same load. The differential inputs of the two amplifiers are commoned.

The total current in load is V'G_{m1} + V'G_{m2}. But V' = V_{in} - V'G_{m2}R. Therefore we can write the load current as (V_{in} - V'G_{m2}R)G_{m1} + V'G_{m2}. If we now arrange that R = 1/G_{m1} we then have a load current: -V_{in}G_{m1} - V'G_{m2} + V'G_{m2} = V_{in}G_{m1}. Note that dependence on G_{m2} has completely disappeared.


If G_{m2} is very much larger than G_{m1}, the bottom amplifier will provide most of the current and hence the power to the load. Since its mutual conductance does not appear in the transfer characteristics its own distortion will not appear in the load. This is not a result than can be expected from conventional feedback. We call it feedforward because the error correcting current is added in the load outside the feedback loop. (There is no current interaction).

Now suppose the top amplifier is replaced by an amplifier of rigidly fixed voltage gain feeding its output into the load via a resistor. It will still have a fully defined overall G_m and operate as before. However, the top amplifier now has an accessible output point of fixed voltage gain relative to its input and this can therefore usefully be used as the drive point for the bottom amplifier.

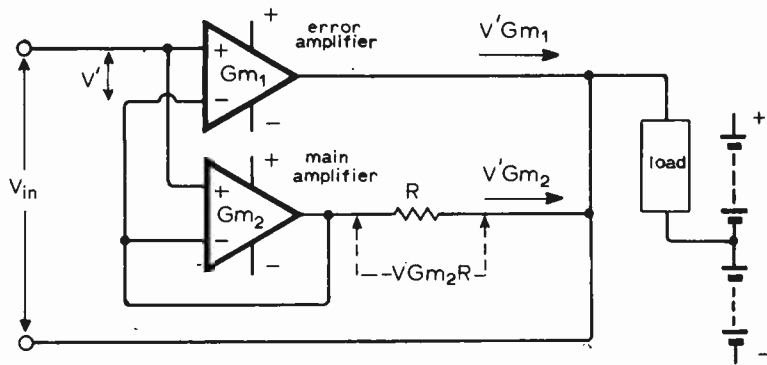THIS combining of error amplifier and drive amplifier brings us to Fig. 1 of the original article. I believe the reasoning to be clear from that point on.



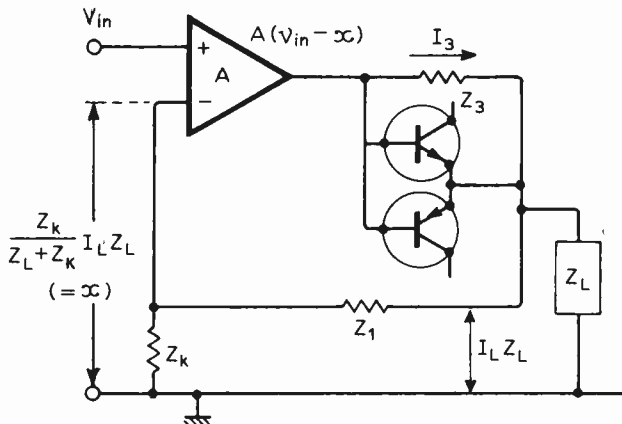Mr Walker's amplifier shown in basic form.



Mr Bennett's suggested circuit.

I have recently made a more rigorous analysis of the behaviour of the "current dumping" amplifier than that presented by Mr P. J. Walker in his December article, and several interesting properties were brought out.

First there are distortion terms which are not removed by setting $Z_1 Z_3 = Z_2 Z_4$ using the notation of Mr Walker's article. For Fig. 1 of that article,

$$I_L = \frac{AV_{in}(Z_1 + Z_2) + A(Z_2 Z_3 - Z_1 Z_4)I_4}{Z_3(A+1)Z_1 + Z_2} + \frac{Z_3(Z_1 + Z_2)I_4}{Z_3(A+1)Z_1 + Z_2}$$

To obtain some judgement of the importance of the third term, use the circuit values in the original Fig. 2, and worst-case 5% tolerance components, as suggested by Mr Walker. If $A = 10^4$, then the third term dominates distortion below 2.5kHz. Incidentally, another distortion term would be introduced in Fig. 2 by the use of voltage gain as indicated.

Now the situation is not so severe in the Quad 405 where inspection reveals A is of the order of 10^6 . Also it is important to note that the contribution of I_4 is not the same as cross-over distortion, for in this case the problem may be reduced by feedback, whereas when the output transistors of a class B amplifier are switched off, the feedback loop is powerless to compensate.

The final point, and perhaps the most interesting, is to consider what happens when Z_2 and Z_4 are removed and short-circuited respectively, thus:

$$I_L Z_L = A \left(V_{in} - \frac{Z_k I_L Z_L}{Z_L + Z_k} \right) - I_3 Z_3$$

$$= \frac{(Z_L + Z_k)(A V_{in} - I_3 Z_3)}{(A+1)Z_k + Z_L}$$

Thus this configuration has no feedback components tolerance problems, does not need a power inductor, and there is no third distortion term due to the presence of Z_k .

The $Z_3 I_3$ term is of equivalent effect to the $Z_4(Z_1 + Z_2)I_4$ term in (1), and thus, given an A of order 10^6 may be reduced to similar insignificance.

J. G. Bennett,
Cambridge

There appears to be some mystification surrounding Mr Walker's new amplifier circuit described in the December 1975 issue, pp. 560-562. Consider his Fig. 1. It is a power amplifier in which part of the load current (I_L) comes from the unbiased emitter-followers via Z_4 and the remainder (I_3) from the driver amplifier via Z_3 . At the central junction of the potential divider $Z_1 - Z_2$ a feedback voltage is derived, which if the divider ratio is correct ($Z_2 Z_3 = Z_1 Z_4$) depends only on $I_3 + I_4$, i.e. on the total output current. This is not a very special achievement - normally such a voltage would be obtained more straightforwardly across a small resistor in series with the load below the junction of Z_3 and Z_4 .

Having established that the voltage fed back is linearly related to the output current, he proceeds by implication to the quite different claim that the forward response is linear. There seem to be no grounds for this assertion. In the basic amplifier without feedback it is far from true - in the floating input configuration of Fig. 1 (with the values suggested) the transconductance increases by up to a hundredfold when the transistors turn on - and the application of feedback will reduce the distortion only to the extent expected in any feedback amplifier.

The various voltages marked on Fig. 1 do

appear to support the claim; they are, however, correct only if there is no p.d. between the inputs of the driver amplifier A , i.e. if it has infinite gain. The text implies that this is indeed the intended assumption. In that case the benefits attributed to the circuit reduce to the familiar assertion that the distortion can be made negligible by huge amounts of feedback, and it has yet to be shown that Fig. 1 possesses any unique property making it easier than usual to do this.

J. Halliday,
Winchester,
Hants.

Mr Walker replies:

Asking the reader "for the time being" to assume the gain of amplifier A to be completely defined by its external impedances Z_1 and Z_2 was, I thought, a convenient way of defining a finite gain (of around 100 in Fig. 1) and was not intended to imply infinite loop gain in a practical case. For any finite gain for amplifier A it is necessary to change the component equation to give the equivalent of a true "virtual earth". Thus for a gain of A , the real equation for balance becomes

$$\frac{Z_3}{Z_4} = \frac{Z_2 A}{Z_1(A+1) + Z_2}$$

and indeed if this is applied to Mr Bennett's formula for the load current, it will be found that terms involving I_4 disappear.

It is this possibility of reducing the output stage distortion to zero (without calling on infinite loop gain) that distinguishes this circuit from those in which feedback only is applied.

Mr Bennett's suggested circuit employs feedback in the conventional manner. The circuit principle is found in several excellent commercial amplifiers and, as Mr Bennett rightly points out, if enough feedback is applied the distortion becomes acceptably low.

SUPPRESSOR FOR TV COMMERCIALS?

On reading about Ceefax and Oracle it occurred to me that there are some other useful pieces of information which could be added to TV signals. I refer to the nature of the transmission, especially advertisements. It would be possible to have various codes for different types of advertisement, and for sets to be fitted with a fairly simple decoder which would, at the selection of the viewers, mute the sound and/or blank the vision during transmissions.

Supporters of commercial TV have for long assured us that viewers enjoy advertisements. Now is an opportunity for them to show that they believe what they say, as if they oppose this suggestion it will be clear evidence that their policy is to take our minds by force.

Robin A. Hoare,
Howick,
Auckland,
New Zealand.

Editor's note: Correspondence on "Electrodynamically induced e.m.f." will be resumed in a later issue.

Time-code receiver clock — 3

Construction, alignment and operation

by A. F. Cross, B.Sc.

Thames Television Ltd

The power supply for the time-code receiver clock, shown in Fig. 15, requires little explanation. The nominal d.c. voltage across C_{37} is 10V on load, and this can be used to supply the display. The 10V rail feeds the monolithic voltage regulator IC_{40} , which has an output preset to 5V, and a current output capability in excess of 1A. A heat-sink is required for the regulator.

Construction

The author's aim was a conveniently small clock, and for this reason a compact layout has been adopted. Apart from the power supply, the clock has been constructed on one matrix board 10in \times 6in, resulting in overall dimensions of 14in \times 7in \times 2½in.

Care should be taken with the layout, and the power supply connections should be as short and substantial as practical e.g. at least 20 s.w.g. on the board. It is good practice to decouple the supply rail to the integrated circuits at regular intervals; a 10nF ceramic disc per integrated circuit is ideal. Logic wiring should be no longer than necessary, and compact construction of the receiver will minimise the effect of interference from the logic. Earthing of the zero-volt line is important, preferably to a single point on the chassis. For this reason it is desirable to isolate the aerial coaxial socket, the 5V regulator

can then become the common earth point.

The displays are mounted in d.i.l. sockets fitted to a small piece of matrix board, and interconnected using thin single strand insulated wire. The wiring details of the ferrite-rod aerial are shown in Fig. 16. The rod may be housed in a plastic or cardboard tube, along with the tuning capacitors which should have short connections to the coil. A screened cable should be connected as shown, close to the coupling coil. The siting of the aerial should not

be critical except in areas of low signal strength; however, placing it within six inches or so of the clock does result in a degradation of the signal due to interference from the power supply. Generally it is more convenient to separate the aerial from the clock so that it may be independently rotated for the best signal. The capacitors across the primary windings are a parallel combination of a nominal 4n7 capacitor plus a smaller value for trimming. The final adjustment of resonant frequency is made with the coil adjuster core.

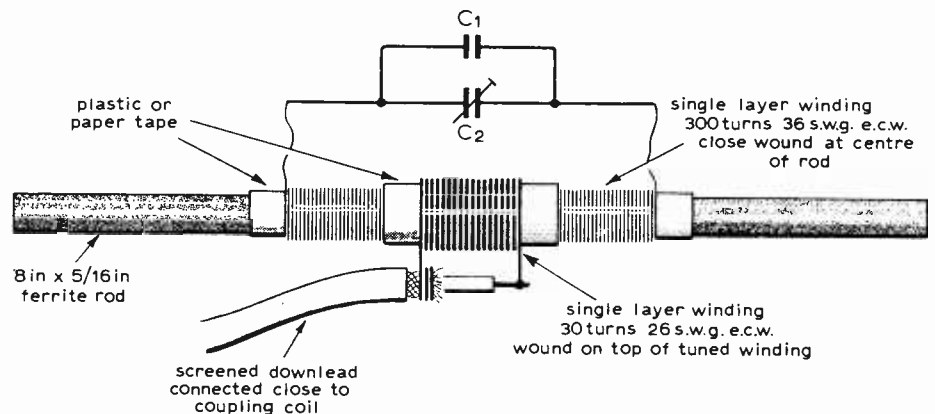


Fig. 16. Ferrite-rod aerial constructional details.

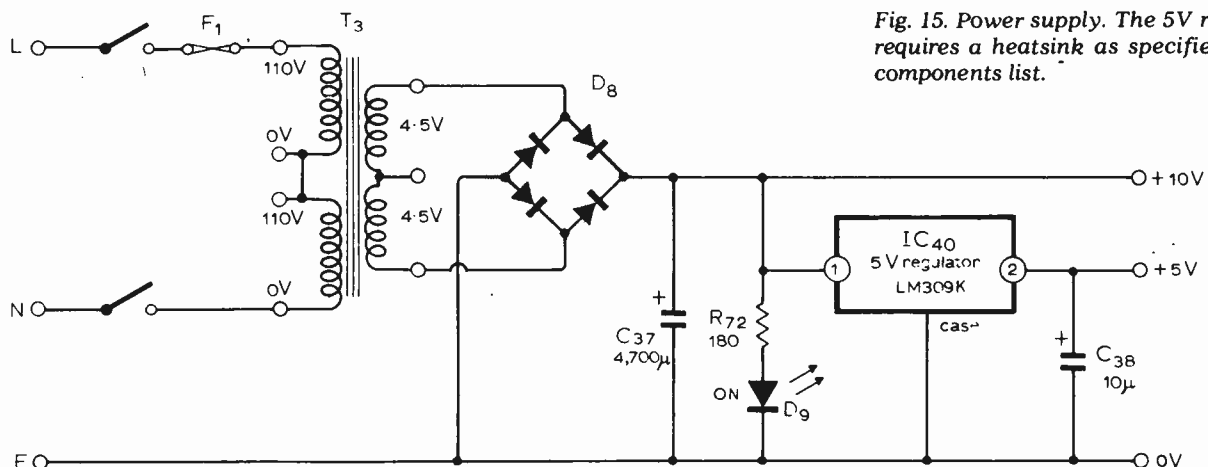


Fig. 15. Power supply. The 5V regulator requires a heatsink as specified in the components list.

Alignment

There are several adjustments to be made before the clock will function correctly. These are; tuning of the ferrite-rod aerial, alignment of the two tuned amplifier stages, adjustment of the muting level, adjustment of the crystal oscillator frequency, and the setting of the two monostable periods.

The a.g.c. used in the receiver must be disabled before accurate alignment is possible. For the initial tuning, however, there will probably be insufficient output to operate the a.g.c. system and the amplifier will be operating at maximum gain. An oscilloscope should be connected to the collector of Tr₃. The adjusters for T₁ and T₂ should be set about half way. With the ferrite rod placed roughly "broadside" to Rugby, the aerial trimmer C₂ should be adjusted over its range until a 60kHz signal is observed on the oscilloscope (this may be only a few millivolts). T₁ and T₂ are now adjusted for maximum output. When the output has reached about 600mV peak-to-peak, the a.g.c. loop will start to operate. To disable this a 47kΩ potentiometer should be connected between the collector of Tr₄ and zero volts. This is now adjusted to give an output between 100 and 200mV peak-to-peak. Fine adjustments to all three tuned circuits can now be made, adjusting the potentiometer as necessary to maintain the output below 200mV. When tuning is complete the potentiometer is removed; the output should increase to between 600mV and 800mV peak-to-peak. (The positive peaks will be somewhat flattened due to non-linear loading of the output.)

Muting level is set by adjusting R₇₃. (With the receiver correctly aligned, the carrier indicator lamp should be flashing with the breaks in the carrier.) When R₇₃ is set to maximum resistance the muting level is at a minimum, i.e. relatively weak signals can be received without the muting circuit inhibiting the demodulator. This means, however, that in areas prone to radio interference, such interference may be of a level which prevents the muting circuit from operating when Rugby is not transmitting. If the normal signal strength is good, the muting level can be raised to reject the interference.


The oscillator is easily set to the correct operating frequency, using the received 60kHz carrier as a reference. The output of the first decade divider after the oscillator (pin 11, IC₂₁) provides a 10kHz signal; this is used to trigger an oscilloscope with the timebase set at about 5μs/cm. Displaying the signal on the collector of Tr₃ in the receiver should produce a stable 60kHz trace which drifts slowly across the screen. The trimmer, C₂₈, is now adjusted for minimum drift. Because one cycle of the 60kHz carrier has a period of 16.7μs, a figure for the accuracy can be determined. A relative drift of one cycle per second represents 16.7μs per second or 16.7 parts per million. Ideally the

oscillator should be set up to better than one part per million which requires that the relative drift be one cycle of carrier in not less than about 17 seconds (the breaks in the displayed carrier provide convenient one second pulses for timing).

The adjustable monostable periods can be set up using an oscilloscope with a well-calibrated time base (an excellent calibrator is the crystal oscillator and

divider chain). The demodulated carrier will normally trigger the monostables once per second. The final adjustment should be made by comparison with the received control pulse once per minute. The end of the 25ms off period (preceding the control pulse) should fall in the middle of the 4ms low pulse on the collector of Tr₁₂; R₇₄ is adjusted to achieve this. The end of the 20ms control pulse should fall in the middle of the 4ms high pulse on the collector of Tr₁₀; only R₇₅ should be adjusted for this.

Fig. 17. Connection details for integrated circuits.

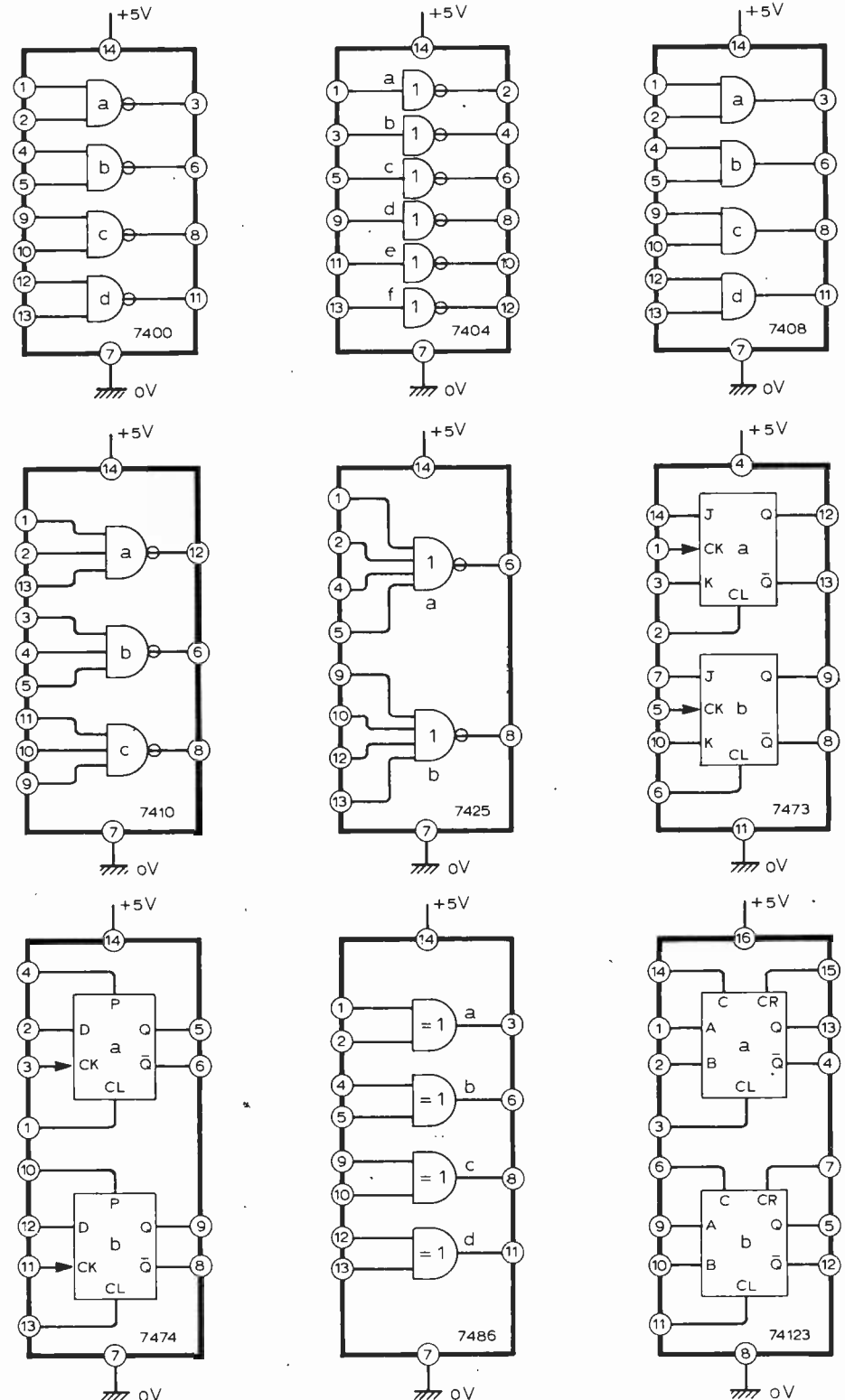

Operating the clock

When the clock is switched on the disparity lamp should light, along with the carrier lamp which flashes in sympathy with the signal. Besides the one-second pulses, the time code should be seen as a brief flicker each minute. The other coded information may also be noticed: firstly, the atomic/astronomic time-difference code, which is transmitted as a double break in the carrier in some of the seconds in the first quarter of each minute. This code changes from week to week as the difference varies. Secondly, in the last five seconds of every hour, the modulation is changed to the station call sign (MSF) transmitted twice in Morse code. Until the first code is correctly received, the clock display remains blanked. Upon recognising a control pulse the code lamp should flash, the disparity lamp should go off, and the display should show the received time code (subject to the GMT/BST switch). The disparity light may come on again if either a spurious signal is recognised as a control pulse (followed by correct spurious parity), or if the time code is incorrectly received (but again with the correct detected parity), or if the contents of the display dividers become corrupted by, for instance, momentary loss of power. For the displayed time to become corrupted by received interference, several coincidences must occur; two false control pulses need to be recognised with no intervening correct code, also, both false pulses must be followed by correct parity before they are acknowledged by the control logic. Although the chance of this happening is increased when the transmitter is switched off, the system has been found to give satisfactory results in most environments.

The author wishes to thank Mr J S Sansom, OBE, former director of Studios and Engineering, Thames Television, for permission to publish this article, and Mr B G Scott, chief engineer, for his encouragement and the use of facilities for the project.

Points arising

Because of a change in the transmission specification the following points should be noted. In Fig. 1 the parity bit was shown as a 1, this is now a 0 and, as a result, the parity check from IC_{12a} (Fig. 7) is taken from the Q output. If the received parity in the flip-flop is correct the final state is now Q = 0.

In the parts list IC₂ was shown as a quad two-input NAND gate package. In Fig. 9, 11 sections a and b of IC₂ are shown as inverters. These are realised by connecting the two inputs of the gates together which then function as inverters.

Meetings

LONDON

- 1st. IEE — "Electrical engineering and medicine" by Dr D. W. Hill at 18.30 at Savoy Pl., WC2.
- 6th. IEE — "Position control of floating structures" by P. H. Barton at 17.30 at Savoy Pl., WC2.
- 7th. IEE — "The history of transmitters — some aspects of early radio" by R. F. Pocock at 17.30 at Savoy Pl., WC2.
- 7th. BKSTS — "What are audio visuals?" at 19.30 at Thames Television Theatre, 308-316 Euston Road, NW1.
- 12th. IEE — "Digital systems representation" by S. Y. Foo at 18.30 at Savoy Pl., WC2.
- 13th. IEE — Colloquium on "Earth leakage protective devices" at 10.30 at Savoy Pl., WC2.
- 13th. IEE — Colloquium on "Theory and operation of Read type IMPATTs" at 14.30 at Savoy Pl., WC2.
- 13th. AES — "Developments in noise reduction techniques" by speaker from Dolby Laboratories Inc. at 19.15 at the IEE, Savoy Place, WC2.
- 14th. IEE — Colloquium on "Evaluation and experience of high level languages for process control computers" at 10.30 at Savoy Pl., WC2.
- 20th. SERT — One-day seminar on "Applications of computers" at the IEE, Savoy Pl., WC2.
- 21st. IERE — Colloquium on "Automatic production" at 14.00.
- 21st. BKSTS — "Video tape recording today and tomorrow" by L. H. Griffiths at 19.30 at Thames Television Theatre, 308-316 Euston Road, NW1.
- 26th. IEE — "History of magnetic sound recording" by B. Lane at 17.30 at Savoy Pl., WC2.
- 27th. IEE — Colloquium on "Paging systems" at Savoy Pl., WC2.
- 29th. IEE — Colloquium on "Parallel digital computing methods: d.d.as and stochastic computing" at 10.30 at Savoy Pl., WC2.
- 29th. IERE — "A novel approach to marine surveying" by J. M. Thompson at 9 Bedford Sq., WC1.
- 30th. IEE — Discussion on "Part-time undergraduate degree courses in electrical engineering" at 17.30 at Savoy Pl., WC2.

BELFAST

- 13th. IEE — "Integrated circuits for communications" by S. J. Laverty at 18.30 at Ashby Institute.

BIRMINGHAM

- 7th. IEE — "Train control, developments on British Rail" by J. W. Birkby at 18.30 at Sumpner Building, University of Aston, Gosta Green.
- 14th. RTS — "The other side of the camera" by Tom Coyne at 19.00 at BBC Broadcasting Centre, Pebble Mill Road.

BLETCHLEY

- 8th. IEE — "Tomorrow's world and microwave communications" by P. J. Mountain at 19.30 at Post Office Training Centre, Horwood House.

BRIGHTON

- 13th. IEE — "Electro-acoustics" by Prof. E. Ash at 19.30 at the University of Sussex.

BRISTOL

- 5th. IEE — "Automobile Electronics" by C. S. Rayner at 18.00 at Mercury House, Bond Street.
- 8th. IEE — "Electronic calculators" by B. Clarke at 19.30 at Queens Building, Bristol University.
- 28th. IEE/IERE — "Marine electronics" by speaker from Marconi International Marine Ltd.
- 28th. IEETE — "Programmable logic controllers" by C. C. Cargill at 19.30 at Royal Hotel, College Green.

BURY ST EDMUNDS

- 7th. IEE — "Police Research" by B. J. Blain at the Angel Hotel.

DERBY

- 6th. IEE — "Automobile electronics" by D. B. Hodgson at 19.00 at the Lecture Theatre, College of Art and Technology, Kedleston Road.

DUBLIN

- 8th. IEE — "Electronic aids for medical studies" by Dr E. T. Powner and P. J. Best at 18.00 at Physics Laboratory, Trinity College.

DURHAM

- 5th. IEE — Exhibition and "Telecommunications; past, present and future" by W. J. Bray at Durham Castle.

EASTBOURNE

- 8th. IEETE — "Royal Greenwich Observatory" by G. H. Gill at 19.30 at The Drive Hotel, Victoria Drive.

EDINBURGH

- 8th. IEE — Symposium on "Further developments of applications of micro-computer systems" at 9.30 at Heriot Watt University, Grassmarket.
- 23rd. IEE — Faraday Lecture on "The entertaining electron" by F. H. Steele, afternoon and evening at The Usher Hall.

GLASGOW

- 21st. IEE — Faraday Lecture on "The entertaining electron" by F. H. Steele in the evening at The Kelvin Hall.

HATFIELD

- 6th. IEETE — EASCON 76 one-day conference "Links: education — employment" at Hatfield Polytechnic.

KINGSTON-UPON-THAMES

- 1st. IEETE — "The testing of electrical household appliances" by M. H. Hewett at 19.30 at Kingston Polytechnic, Penrhyn Road.

LIVERPOOL

- 5th. IEE — "Music hath charms . . ." at 18.30 at the Department of Electrical Engineering, Liverpool University.

LOUGHBOROUGH

- 27th. IEE — "Introduction of adaptive control techniques into areas of classical control" by J. R. Wolton at 19.30 at Lecture Theatre J002 Ed., Herbert Building, Loughborough University.

MANCHESTER

- 14th. IEE — "Microprocessors" by Prof. D. Aspinall at 18.15 at the University of Manchester.

MIDDLESBROUGH

- 7th. IEE — "Rapid fault finding techniques to minimise down time" by R. H. Baulk at 18.30 at Cleveland Scientific Institute, Corporation Road.

NEWCASTLE-UPON-TYNE

- 12th. IEE — "Colour TV — a popular approach" by G. D. Barnes at 18.30 at Room L101 Merz Court, University of Newcastle-upon-Tyne.
- 27th. IEE — Faraday Lecture on "The entertaining electron" by F. H. Steele, 19.15 at City Hall.

NOTTINGHAM

- 6th. IEETE — "Computerised control of Nottingham traffic" by M. B. Tate at 19.00 at New Mechanics Institute, St Trinity Square.

PORTSMOUTH

- 6th. IEETE — "Oracle — the teletext data broadcasting system" by G. A. McKenzie at 19.30 at Highbury Technical College, Cosham.

RUGBY

- 7th. IEE — "The future of the IEE" by R. J. Clayton at 18.30 at Lanchester Polytechnic, Rugby.

SHEFFIELD

- 20th. IEE — "Future role of the IEE" by Dr E. Laverick at 19.30 at Sheffield University.
- 28th. IEE — "Electronic techniques in Archaeology" by Dr E. T. Hall at 18.30 at Sheffield Telephone House.

SWANSEA

- 8th. IEE — "Transducers for modern automobile systems" by J. Moore at 18.15 at University College.

SWINDON

- 6th. IEE — "Sonar and underwater acoustic communication" by V. G. Welsby at 18.15 at The College, Regent Circus.

Electronic systems — 3

Modulation and transmitting signals

by W. E. Anderton

Assistant Editor, *Wireless World*



Modulation is a principle fundamental to all communication systems — speech is a modulation of sound waveforms, pictures are modulations of light intensity and communication within the human body itself relies on modulation of the rate of firing of electro-chemical pulses in the nerves. The fast transmission of information over long distances is only possible using a high speed carrier which will travel for large distances without attenuation; hence electromagnetic radio waves are of prime importance for distant communication. In the case of transmitted radio waves, the process of modulation is to vary some parameter of the basic electromagnetic wave, which is usually called the carrier. Over the years, various modulating methods have been devised and are aimed at transmitting the required information as effectively as possible with the minimum amount of distortion. The primary factors to be considered are signal power, baseband, distortion and noise power — each of these will be described later. Ultimately, it is the ratio of signal power to noise power or output “signal-to-noise ratio” specified for the system which determines its performance.

Baseband

The baseband is defined as the range of frequencies which is to be communicated, e.g., the speech baseband is approximately 300Hz to 4kHz. The ear can perceive sounds outside this defined speech baseband but experiments have shown that adequate intelligibility is achieved using this contracted range. Consequently all telephone systems use this baseband.

Baseband communication (i.e. with no modulation of carrier signal) has a very limited transmission distance. Without electrical assistance, acoustic communication is not possible over distances greater than half a mile. This range may be further restricted by environmental conditions. In fact, the limitations of baseband telephone communication are many and the following list gives some of the more obvious and important of these: (a) the communica-

tion link can be made only between fixed locations; (b) a complex switching system must be designed to allow any subscriber to contact any other subscriber; (c) long distance links require amplification in order to overcome cable losses; (d) simultaneous communication with large audiences is impossible; (e) the system’s cost is largely in the laying of individual cables to each subscriber.

The development of a “wire-less” system has overcome most of these disadvantages.

Electromagnetic propagation

Early experimenters in electromagnetic propagation discovered that some energy from a high energy spark could be transmitted to a suitable receiver without the use of wires. The spark’s energy was coupled to an aerial and propagated through “space” to the receiver. The receiver often being a crude tuned circuit consisting of a coil and another smaller spark gap. This process was termed “impulsive electromagnetic propagation”.

Later experiments were performed which, instead of using the impulsive spark energy, used an oscillatory waveform. This waveform (represented as in Fig. 1) could also be propagated from transmitter to receiver.

Wavelength, frequency, wavebands

Sound waves travelling in air do so at a velocity of approximately 343m.s⁻¹, but radio waves travelling through space do so at the speed of light, i.e. at approximately 300 million m.s⁻¹. The frequency of an electromagnetic wave is defined as the number of complete cycles transmitted per second and because we know the speed of the radio wave we can calculate the length of any one complete cycle in space. This length is known as the wavelength of the radio wave. The formula linking these two quantities is

$$\text{wavelength} = \frac{\text{speed of light}}{\text{frequency}}$$

or $\lambda = c/f$

Electromagnetic propagation is affected by the Earth’s atmosphere in various ways which are dependent on the transmission frequency and the distance between transmitter and receiver. Fig. 2 shows a convenient classification of the frequency bands.


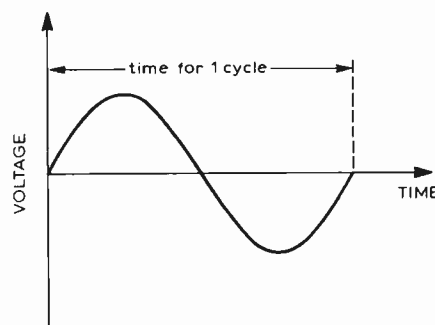


Fig. 1. Oscillatory waveform — the basic carrier wave.

Fig. 2. Frequency bands may be classified as shown here.

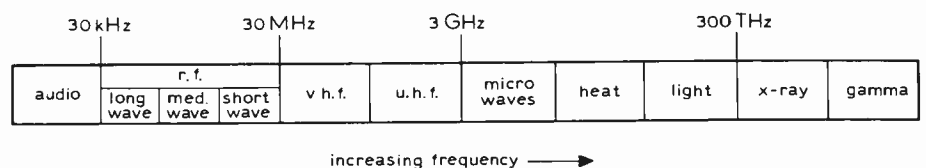

Modulation

To send information from transmitter to receiver, the carrier wave must be varied in sympathy with the information to be transmitted. This process is termed “modulation” and the information that is being transmitted is termed the “modulating signal”. Modulation occurs whenever a “carrier” is affected by a signal which has to be transmitted. For example, the frequencies and

amplitudes of sound waves are modulated by the speech information which is transmitted from person to person whilst the intensity of a light is modulated by a signaller using an Aldis lamp.

The two most important analogue methods are amplitude modulation and angle modulation. Amplitude modulation is most common for applications such as radio broadcasting and radio telephony. The process of amplitude modulation is illustrated in Fig. 3. The a.m. systems are essentially narrow-band and suffer from limitations due to noise which has a direct effect on signal amplitude, and is therefore reproduced as interference.

In competition with a.m. some systems use angle modulation because of its immunity to amplitude varying noise. In angle modulation, the instantaneous angle of the carrier wave is varied and it leads to two forms of modulation known respectively as frequency modulation (f.m.) and phase modulation (p.m.). These two are closely related though practical systems tend to favour f.m. Typical examples are v.h.f. broadcasting, satellite communications and f.m. radar. The frequency modulated carrier wave shown in Fig. 4 requires a much greater available band of frequencies than its a.m. counterpart and an f.m. system is capable of giving a much better signal-to-noise performance than the corresponding a.m. system, or alternatively a considerable economy in power if required.

Carrier keying

If a transmitter is tuned to transmit a carrier wave at frequency f and a receiver at a distant location is tuned to receive this frequency then one would expect that the man at the receiver would be able to detect if the man at the transmitter switched his transmitter on and off. This is the most basic form of modulation and information transmission via a carrier wave. The technique is termed "carrier keying". This simple system can be extended to enable it to convey messages by keying the carrier in a predetermined code sequence. Morse code wireless telegraphy uses a system of long and short pulses. Fig. 5 shows the signal transmitted by a carrier keying system for the morse character "Y". The long bursts of carrier denote a dash and the short bursts a dot.

Amplitude modulation

In a linear amplitude modulation system, the amplitude of the transmitted carrier wave is made to be instantaneously proportional to the amplitude of the modulating signal. The modulation can be sinusoidal, square or any other shape which it is found necessary to transmit. The modulator is similar to a linear multiplier, the inputs being the carrier and the modulation signals. The output is the signal to be transmitted.

$$\text{transmitted signal} = \text{carrier} \times \text{modulation signal}$$

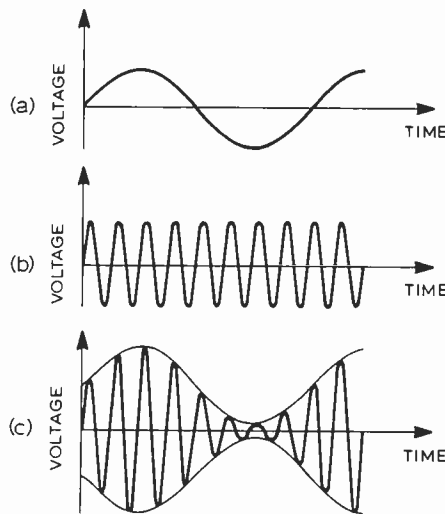


Fig. 3. Illustrating the basic process of amplitude modulation.

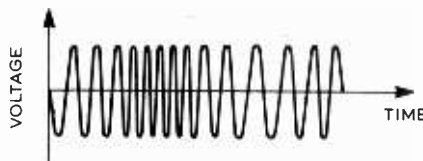


Fig. 4. Frequency-modulated carrier wave.

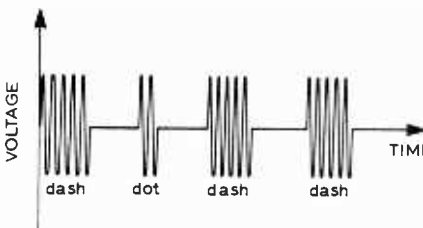


Fig. 5. Signal transmitted by a carrier keying system for the morse character "Y".

If the carrier is modulated with a 400Hz sine wave then the receiver will receive a carrier signal whose amplitude is varying at 400Hz and the variations will be sinusoidal. In the last section we discussed carrier keying as a method of transmitting morse code. There are complications involved when one wants to switch a high power transmitter rapidly on and off. This problem is easily overcome in the amplitude modulation system — one simply switches the modulating signal on and off. The result at the receiver is 400Hz tone bursts which will represent the dashes and dots of the code, while the carrier wave is transmitted continuously. The 400Hz modulation frequency can be replaced by a speech waveform, in which case the carrier will now be amplitude modulated so as to correspond with the speech signal. This system is used widely, an example being the programmes broadcast on the long and medium wavebands.

The next part of this series will examine a.m. and f.m. in more detail. An

outline of the basic electronic systems course which this series of articles will cover was published in the first part appearing in the January 1976 issue.

This article was prepared in consultation with Professor G. B. B. Chaplin, University of Essex.

Further reading

Connor, F. R., "Modulation," Edward Arnold, London.

Obtainable from Mr R. A. Smith, Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ, Essex, are the teaching texts for the electronic systems pilot A-level course, price £4.50; communication systems section only, £2.00; computer systems section only, £2.00; feedback systems section only, £2.00; basic electronics section only, £1.50.

Books Received

Handbook of Electronic Circuits by G. J. Scoles. In the authors words "instead of first, dealing with electronic theory in some detail and then proceeding to a mathematical analysis of a small number of selected circuits, it assumes that with the help of a simple explanation the reader already knows sufficient of the theory for him to understand the operation of virtually any electronic circuit. In this way it becomes possible to describe the uses and functioning of more than 200 different circuits, either using non-mathematical explanation or, where relevant, simplified formulae only". A wide cross section of circuits are discussed, under 26 general categories purposely omitting r.f. amplifiers and t.v. receiver details because, in the authors opinion, these have been adequately covered in other publications. Price £13.50. Pp. 370. John Wiley & Sons Ltd, Baffins Lane, Chichester, Sussex.


Diode characteristics, equivalents and substitutes by B. B. Babani contains more than 25,000 separate entries including military types. The pocket book also contains a contents page in nine different languages for our overseas friends. Price 95p. Pp. 159. Bernard's Publishers Ltd, The Grampians, Shepherds Bush Road, London W6 7NF.

Electronic and switching circuits by S. M. Bozic, R. M. H. Chery and J. D. Parsons. This book is based on lectures given by the authors to undergraduate students. An intermediate level of mathematical knowledge is assumed together with the basic principles of a.c. circuit theory. After explaining physical electronics, the principles of amplification, switching devices, oscillators and power supplies are covered. Final chapters discuss data processing and transmission, industrial applications and electronic instruments. The book also contains problems and solutions which are designed to test whether the reader has understood the text. Price £4.95 paperback, £10.00 hard back. Pp. 380. Edward Arnold Publishers Ltd, 25 Hill Street, London W1X 8LL.

Circuit Ideas

Low-current source

It is possible to use a reverse-biased germanium diode as a voltage independent current source for loading silicon transistors. Advantages of this method are less voltage lost across the source when compared with f.e.t.s and similar sources, it is cheap, and the diode I_R increases with temperature in much the same manner as the h_{fe} , I_{cbo} in a transistor. The last point allows reliable micropower circuits to operate over a wide temperature range at

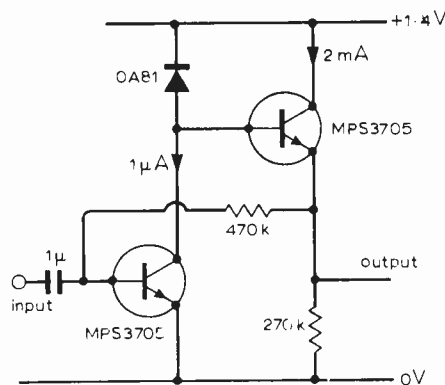

optimum current drain. This principle was applied in the amplifier circuit shown. The diode leakage current is arranged to be greater than the collector-emitter leakage of the transistor, permitting linear operation. Performance figures are: a voltage gain of 50, a -3dB bandwidth from 16Hz to 4kHz, a maximum output into 1MΩ of 500mV pk-pk (at 300Hz), an input impedance of 10kΩ (at 500Hz), and a consumption at 20°C of 4mW.

Owing to manufacturing tolerances the operating point can only be guaranteed to within a decade or two, and the diode capacitance is extremely non-linear at low reverse voltages.


M. G. Baker,
Beaminster,
Dorset.

Automatic display-brightness control

It is quite easy to modulate the intensity of a display by switching it on and off with a varying duty cycle. With single-chip clocks where multiplexing is used, the display on time must be synchronised to the multiplex frequency. This circuit was designed around an MM5314 clock chip but should be usable wherever there are external multiplex-oscillator and strobe-enable outputs. The 555 timer is used in the monostable mode, triggered by the multiplex oscillator to determine the display off time. In bright conditions the ORP12 resistance is low and the display is on most of the time. It is

necessary to set an upper limit to the pulse length, otherwise the 555 will not retrigger on each cycle of the multiplex oscillator and only alternate digits will be displayed. The potentiometer should be set to give low light output without mistriggering in dark conditions. The simplest way to control the rate of brightness increase with ambient light is to partially obscure the ORP12 surface. The 555 can also drive a decimal point directly, giving a matched brightness.

M. G. Martin,
Maybush,
Southampton.

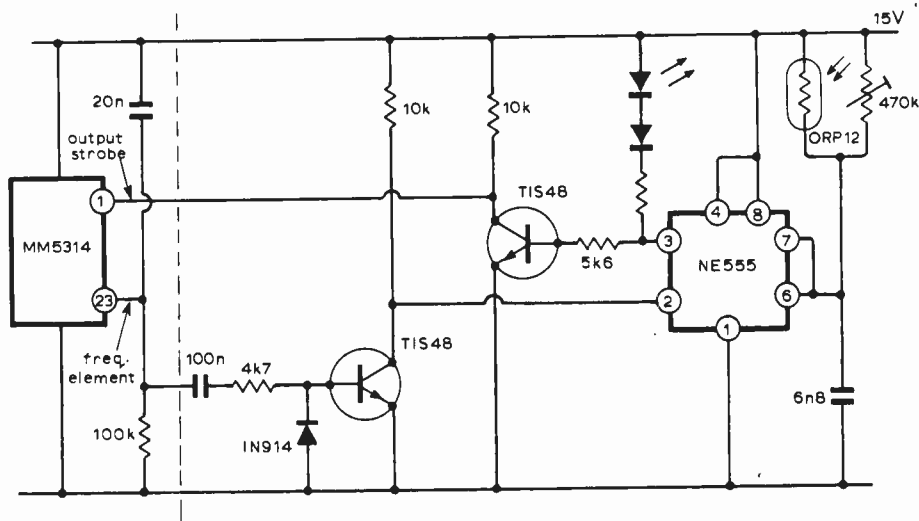


Bias supply for r.f. power amplifiers

Many designers resort to the use of a single forward-biased diode voltage source when attempting to operate transistor r.f. power amplifiers in the class AB linear mode. This can require the selection of a suitable diode and thus does not lend itself to reproducible design.

The circuit shown not only offers improved performance, typically 1Ω output impedance and ±3% output voltage change for ±2½V input change, but also allows adjustment of the quiescent collector current. A p-n-p


silicon device is used as an amplified diode variable voltage source. If this is in thermal contact with the r.f. device's heatsink, a significant degree of thermal stabilization is obtained. The emitter follower lowers the supply output impedance. The devices shown can be replaced by similar readily available transistors.

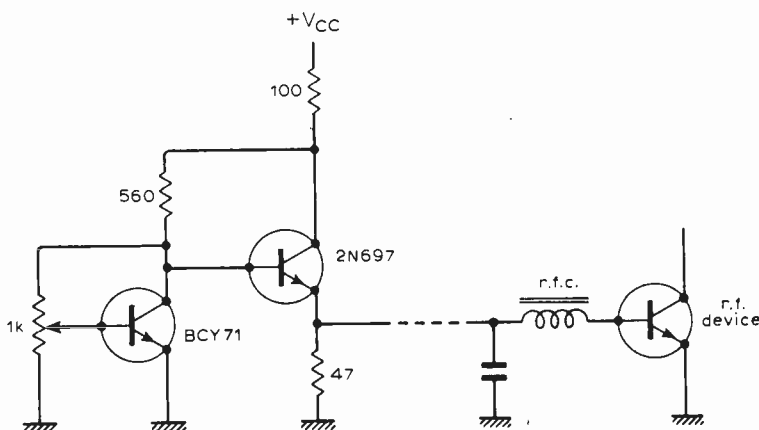C. P. Bartram,
Dept. of Metallurgy
and Science of Materials,
Oxford.



Simple current controlled pulse generator

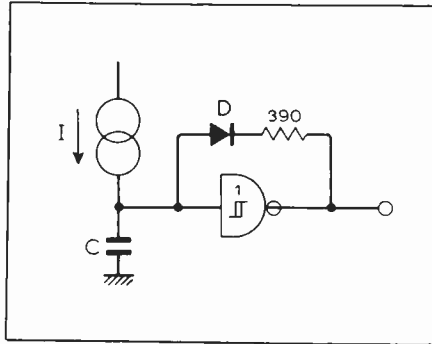This simple circuit generates pulses to operate t.t.l. at a variable rate between about 100Hz and several MHz. The diode should be a germanium type of low capacitance and must be able to carry current *I* continuously. The capacitor can be any value from picofarads to millifarads. Suitable inverters are SN7413/14/132 or the Schottky clamped variety for higher speed. Care



must be taken in choosing the current to avoid damaging the inverter and diode. The control current can be obtained by a resistor to +5V. There is an internal resistor of about 4kΩ connected to +5V on the input of the inverter, which gives a minimum pulse rate for any value of *C*. For further information about such oscillators see *T.I. Applications report B81*.

G. W. Haywood,
Bingham,
Notts.

Synchronous-motor phase control


The requirement was for accurate phasing of a 51 pole pair phonic/synchronous motor in a facsimile transmitter. This circuit can be readily adapted for similar applications. A sixteen stage shift register loaded with one bit and connected as a ring counter is clocked at sixteen times the required motor drive frequency. Thus, the output of any one stage is a pulse train with a 1:15 mark/space ratio and a repetition rate equal to the drive frequency. A single pole sixteen way switch can select the output from any stage of the shift register. For every clockwise step of the switch there will be a 360/16 degree phase retard of the output. Similarly for every anticlockwise step there will be a 360/16 degree phase advance. Smaller steps may be achieved


by extra stages in the shift register. In terms of shaft rotation each step is $360/16 \times 51 = 0.44^\circ$. In the circuit shown a sixteen line-to-one multiplexer acts as the sixteen-way switch. The position of the switch is determined by the data select input. To make the switch rotate uniformly either clockwise or anticlockwise, the data select is connected to a four-bit binary up/down counter. The clock drive for the counter is derived from a gated multivibrator, the rate of which determines the rate at which the phase advances or retards. If necessary another counter can be used to monitor the number of pulses from the multivibrator.

The 1:15 mark/space ratio at the multiplexer output can be improved by a monostable with a period set at half

the period of the drive frequency. This puts less demand on the bandpass filter if a sinusoidal output is required. Sixteen clock pulses to the up/down counter produce one complete rotation of the sixteen way switch which means one complete cycle subtracted from or added to the motor drive. In terms of shaft rotation in a 51 pole pair machine, the phase is retarded or advanced $360/51 (7.05^\circ)$ in sixteen 0.44° steps. In other words, if the gated multivibrator output frequency is *N* pulses/s, the motor speed alters by $N/7.05$ degrees/second.

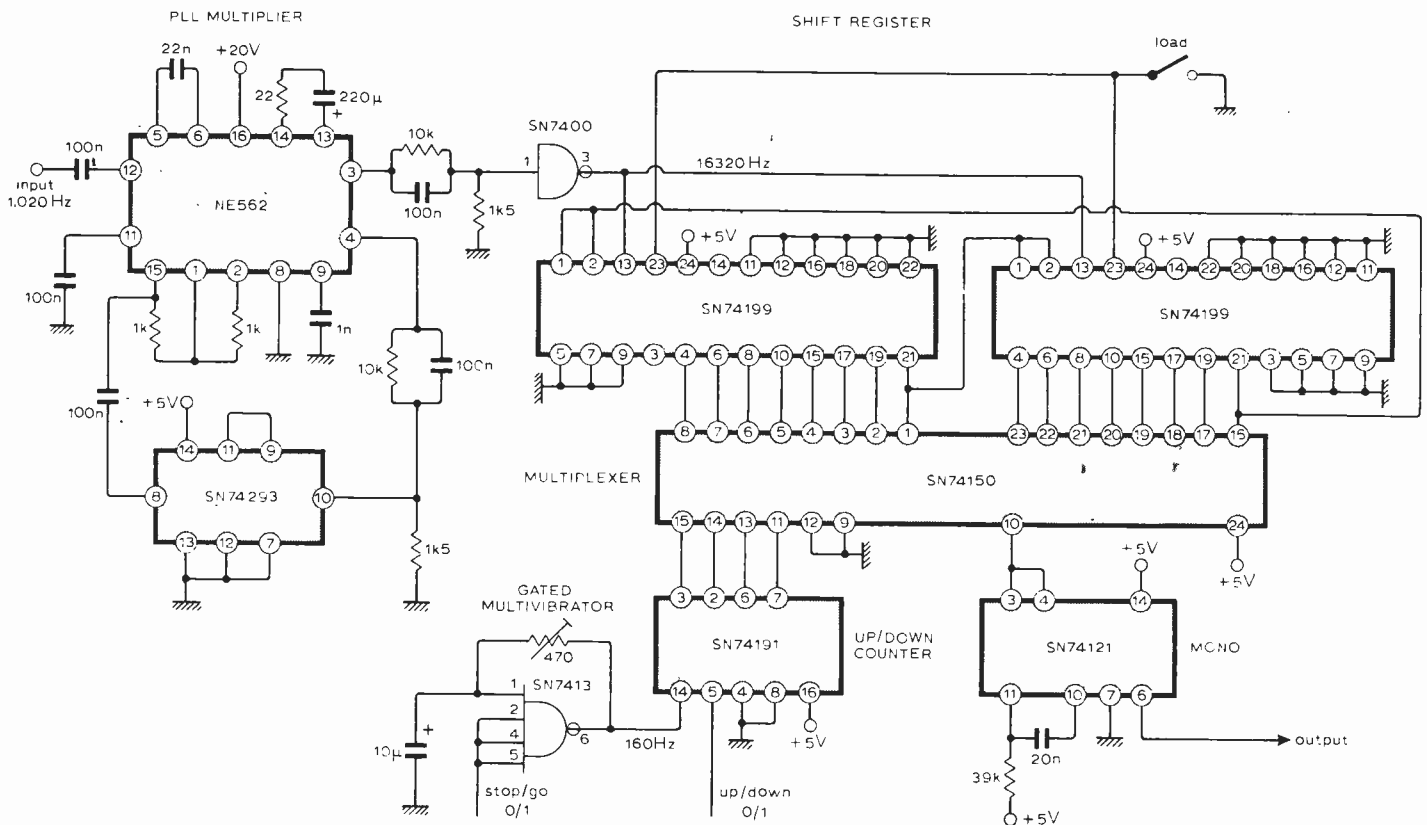P. E. Baylis and R. J. H. Brush,
Dept. of Electrical Engineering
and Electronics,
University of Dundee.



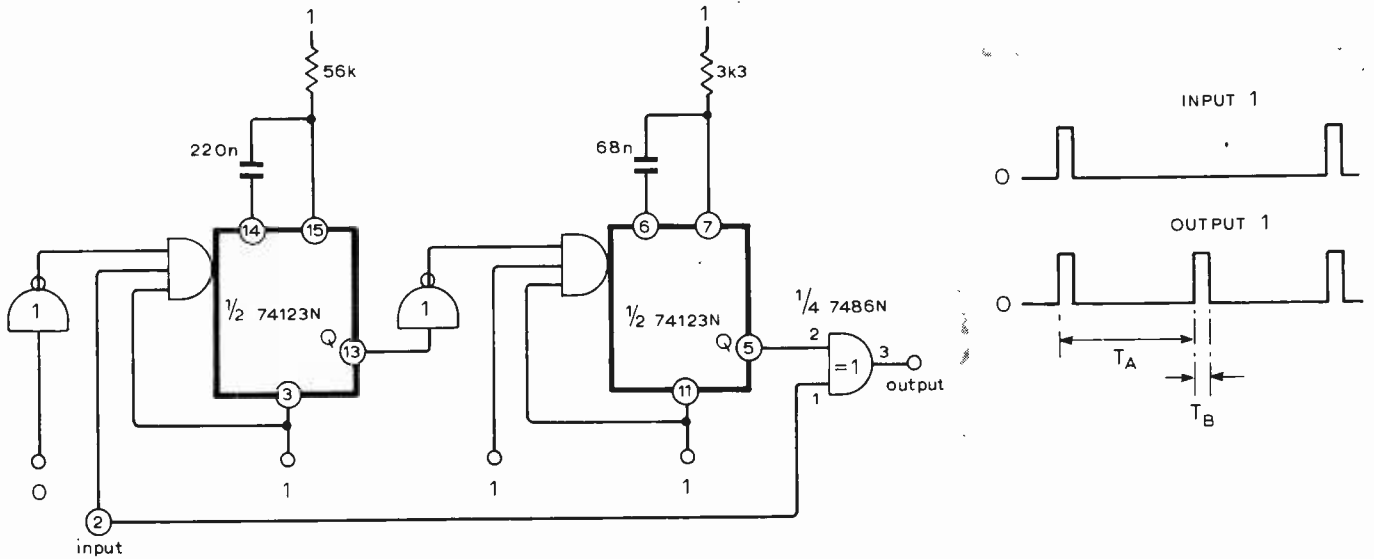

Pulse rate doubler

The circuit shown will generate pulses at twice the input frequency. A pulse is applied to the first monostable in the 74123N, which runs for time T_A . The negative edge, terminating T_A , triggers

the second monostable which runs for time T_B . Thus, if T_A equals half the input period and T_B equals the width of the input pulse, an additional pulse is generated between each input pulse. An exclusive-OR gate combines both


pulses to produce the output. Using R and C values as shown, the circuit will double a pulse of width $800\mu\text{s}$ and repetition rate about 130 per sec.

K. R. Brooks,
University of Bristol.

Simple staircase generator

The circuit provides a simple means of generating a repetitive staircase waveform. A total of seven steps is generated before the waveform is repeated. This may be increased by cascading several SN74 164 shift registers or decreased by providing the clear pulse from an earlier Q output.


P. Cochrane,
Ipswich,
Suffolk.

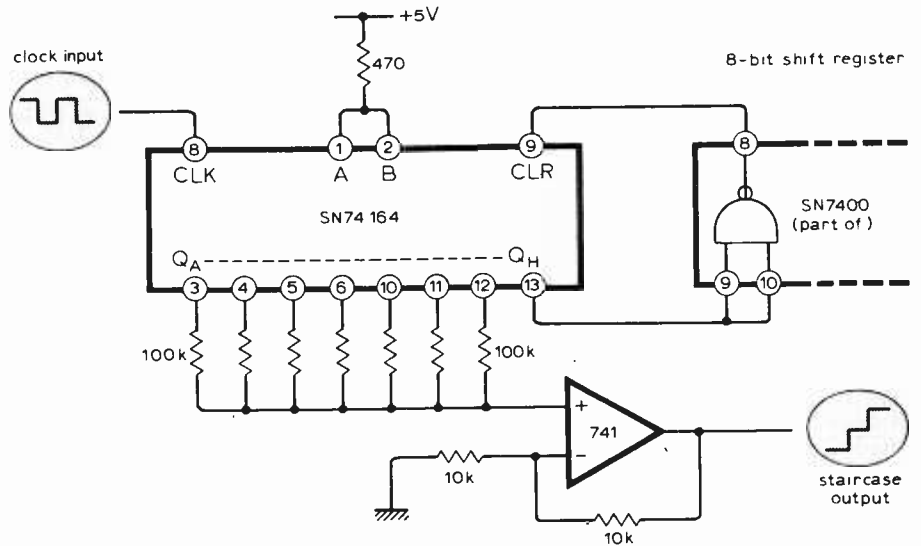

F.m. discriminator

To produce a high quality f.m. tuner I surveyed a number of design techniques using discrete components. After some research I became interested in an article by J. C. Hopkins (*Wireless World*, Sept. 1965). This circuit uses a transistor pump discriminator operating around a 200kHz i.f. This technique, used with a conventional 10.7MHz i.f. strip, produced very good results.

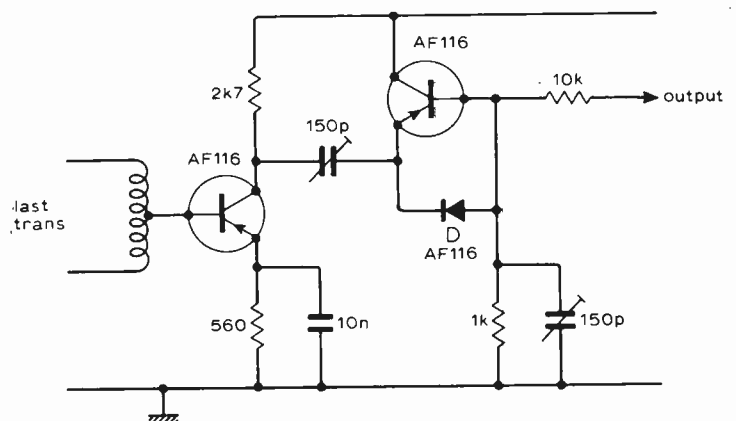The circuit is similar to J. C. Hopkins's design and requires modifications only to the capacitor values and transistors. The last i.f. stage was modified and the load made resistive. The signal was then coupled to the discriminator which, in turn, was connected to a stereo decoder. W. Anderson,
Portland,
Dorset.



Wireless World Teletext decoder

6--Lower-case characters and analogue circuits

by J. F. Daniels

The control-codes detection is based on six D-type flip-flops. The first three of these (52,6), (52,8) and (53,6) detect codes which mean "go to red display, green display and blue display" respectively. The fourth one dictates whether the display should be in the alphanumeric or graphics mode, and the fifth one (51,6) indicates when characters should be flashing. The final one is used to derive a waveform to switch between the TV and Teletext displays during the insert or boxed mode.

The Teletext specification says that all rows should begin in the steady, alphanumeric white, unboxed condition, and this is achieved by presetting the outputs of the six flip-flops to the required state with the output pulse from (59,8), which is a combined line and field blanking waveform.

Considering first the codes which indicate a change in colour of the display, it can be seen from the code table that bit 1 is always at 1 when a red output is required, bit 2 is at 1 when a green output is required and bit 3 is at 1 when a blue display is required. Combinations of these three bits will also give the complementary colours correctly such as yellow when bits 1 and 2 are both at 1, and also white when all three bits are at 1. The way in which this is achieved in the decoder is to feed bits 1, 2 and 3 respectively to the D inputs of the three flip-flops, (52,6), (52,8) and (53,6) and feed the clock inputs in parallel, with clock pulses occurring only during the fourteen colouring codes in the code table.

The clock pulse gating is achieved in (41,10), (49,8), (43,13), (44,6), (58,6) and (49,6). The actual clock pulses are narrow negative-going pulses obtained from decoder (42,2) and are fed into gate (43,13). The other gates merely serve to inhibit the clock pulses at all times other than when a change in colour of the display is required. The input to IC₄₉, pin 9 can be changed by means of the link, from IC₂₈, pin 7 to IC₅₉, pin 2, altering the Clock-pulse-allow waveform to cater for the new code allocations.

The changeover between graphics and alphanumeric operation is obtained in a very similar way to that already

described for colours. Flip-flop (53,8) obtains its clock pulses from the same place as the colour changing i.cs and its D input is fed either from (66,12) or (28,10) according to which transmission standard is being received.

Flashing and boxing codes are dealt with, again in a similar way to that already described. Clock pulses are only allowed during the two code positions allocated to flashing and boxing respectively. The D inputs are fed with bit 1 information, and in this way the output of each flip-flop is set either to the on or off condition depending upon which of the control codes is received. Normally, of course, the flip-flops are set to the off condition by the line-blanking waveform, and then somewhere along the character row a flashing code may be received which will set the flip-flop to the on condition. A further code may be received to turn off the flashing or, if no code is received, the line-blanking waveform will again set the flip-flop to the off condition at the end of the row.

Switching between the alphanumeric and graphic displays (both types of character are actually generated for each character box in the display) is achieved with gates (57,8), (57,11), (58,8) and (58,12). Alphanumeric characters are fed into IC₅₈, pin 2 and graphic characters into IC₅₇, pin 10. A feed of bit 6 is also connected into IC₅₈, pin 1 and IC₅₇, pin 13. This is to enable the "blast through" mode of operation, in the following manner. Normally when graphics are being displayed, bit 6 is in the 1 condition. If, however, bit 6 is made 0 as for instance in the transmission of upper-case letters, this can be made to switch away from the graphics mode, and into the alphanumeric mode for the duration of the character. In this way switching between graphics and alphanumerics can be obtained very economically, without the need for a separate control character (which would be displayed as a space). The slight disadvantage of this is that only upper-case characters in columns 4 and 5 of the code table may be displayed in this way.

Gate (58,8) is fed with the outputs of

gates (57,8) and (58,12), containing the graphics and alphanumeric characters respectively. A third input to this gate is fed with a composite blanking waveform which contains both line and field blanking, and also information to blank the control characters. Gate (44,12) adds together the line and field blanking waveforms, and a third blanking input is provided here which may be used to blank the Teletext display output while watching TV programmes. (It is possible that the Teletext waveform could break through onto the TV picture under some circumstances, if the leads were not properly screened, for instance.) The output of this gate is delayed by capacitor C₁₁ to allow for delays in the r.a.ms and r.o.m. This output is added to the control-character blanking waveform in gate (41,13) and the output of this gate is then fed into (58,8) where it serves to blank the video display waveform.

The output of (58,8) is then inverted and gated with the output of the flashing oscillator formed from (67,2) and (67,4). This flashing oscillator is allowed by the D type flip flop (51,6) and gates the display waveform in (57,6). At this point the composite display waveform exists in monochrome form, and then the colours are incorporated by gating this monochrome waveform in the 2-input NOR gates (54,4), (54,13) and (54,1). The three D-type flip-flops enable or disable these gates to form the red, green and blue outputs.

Finally the output of the flip-flop (51,8) is gated with the line and field blanking waveforms to give an output which can be used as a switching waveform when a "boxed" display is wanted.

Lower-case characters

The character-generation circuit already described is capable of generating only upper case, or capital letters. Although this does not detract in any way from the information-carrying capabilities of the system, some people may consider it worthwhile to add the extra circuitry required to display lower case characters.

The method is exactly the same as that described last month for upper case characters, except that some lower case letters, i.e. g,j,p,q,y, drop below the line of normal characters. Provision has already been made for this as the character box is ten lines high and only the top eight lines are used for the upper-case characters and a space line between characters. This leaves two unused lines available to display lower-case descenders.

The same type of r.o.m. is used to contain the lower-case characters, the only difference being that the lower-case memory only contains the thirty two characters in columns six and seven of the code table, the other thirty two spaces being left blank. The complication arises from the fact that characters stored in the memory can only occupy up to eight lines of the display, as the row-address information to the r.o.m. consists of only three bits of information. Fortunately, however, none of the characters having descenders contains information in the top two rows of the character box, and this enables the character to be stored in the r.o.m. two rows higher than its intended display position, as shown in Fig. 1. This means that when the row addresses are applied to the r.o.m. they must be changed for those characters which have descenders, in order to lower the display position by two TV lines.

Figure 2 shows the extra circuitry needed to produce lower-case characters, and in practice these additional i.c.s are mounted on a small board which fits above digital board 1 at the opposite end to the analogue board. I.c.s 87, 88, 89, and 90 are used to detect the characters which require lowering by two rows, and this information is available at gate (89,4) where a 0 denotes a normal character and a 1 indicates a character that should be lowered by two rows.

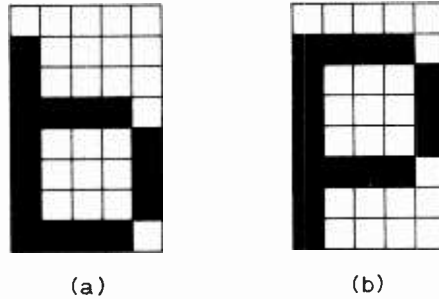


Fig. 1. Lower-case letters with "tails" are stored in the same memory rows as ordinary letters. Row addresses are changed during readout to lower the letters by two rows.

The character generator, IC₈₅ is of the same type as the upper case one, a 2513, but its suffix CM3021 indicates that it is programmed with lower case characters. (The upper-case version is suffixed CM2140). Switching between the outputs of the two character generators is facilitated by their "tri-state" outputs. This means that as well as having the normal states of 0 and 1 at the output pins, a third condition can be obtained where the output pin is effectively open-circuited from the rest of the i.c. This third state is controlled by the "chip enable" input, and by suitable control of this input, any number of 2513's may be connected to the same five output rails. In this circuit, switching between the two r.o.m.s is controlled by gate (90,3). The output of this gate goes to 0 only during columns 6 and 7 of the code table, enabling IC₈₅, and the inverse of this waveform is fed to the chip enable pin of the upper-case character generator IC₇₃, enabling it during columns 0-5 of the code table.


The row addresses to IC₈₅ are fed from IC₈₆, which is a four-bit binary full adder, type 7483. The A inputs are fed with the four-bit row-address information from the line counter IC₅, and the B

inputs are fed either with a binary zero, during normal characters, or the binary number fourteen during characters which require descending by two rows. Sum outputs one, two and three are fed to the row address inputs of the r.o.m. and these will change for a descended character in such a way that the character will be lowered by two TV lines. Sum output four can be used as a blanking waveform to inhibit the generation of characters during the top two rows of the character box, when a descended character is displayed. The blanking is achieved by means of gate (89,13) which switches the character generator to one of the blank character spaces during the required blanking period. This method of achieving the blanking is extremely useful, as the delay applied to the blanking waveform will be similar to the delay of the character read-out of the r.o.m. (about 400ns). If the blanking had to be added externally to the r.o.m. then some means of delaying the waveform by a suitable amount would have to be found. A useful feature of the lower-case circuitry is that only one track on the upper-case printed board has to be cut when adding the extra board (the chip-enable pin of IC₇₃) and all the connections to the existing boards may be made to the underside of digital board two, which entails a minimum amount of disturbance to the existing upper-case circuitry. For this reason also, I would suggest that the decoder should be built and tested as an "upper-case only" unit initially. The lower-case board can be added later as there is no extra line-up procedure required when this board is fitted.

Analogue board

This board serves three main functions, namely to provide feeds to the digital boards of mixed syncs, separated data,

Fig. 2. Extra circuits to obtain lower-case letters.

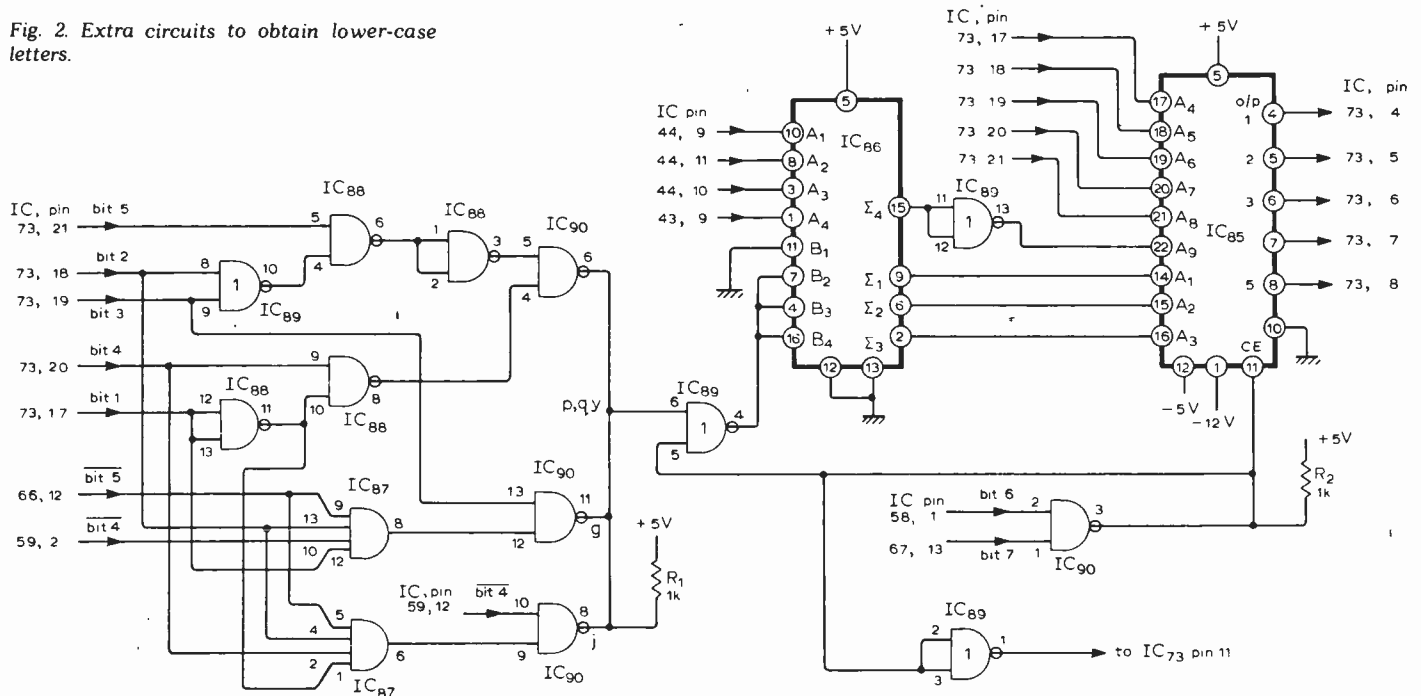

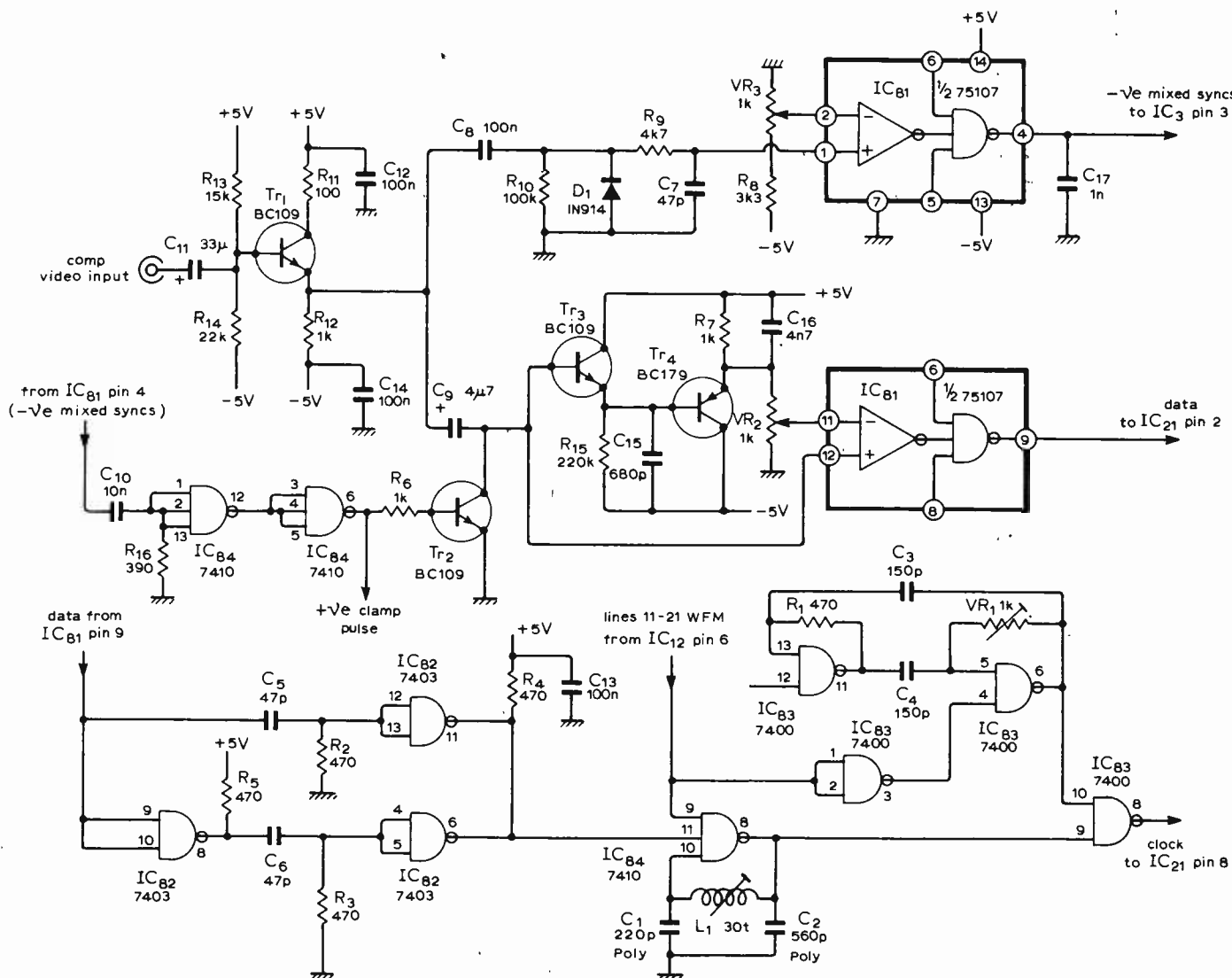


Fig. 3. The analogue circuitry to produce syncs, data and clock.

and a switched clock waveform which is suitable both for the writing of data into the store and for reading it out during the display period. The input to the analogue board, the circuit of which is shown in Fig. 3, should consist of a composite positive-going video waveform of between about 1 volt and 5 volts peak to peak. Tr_1 is an emitter-follower buffer which provides a suitable low-impedance source to drive the d.c. restorer formed from C_8 , R_{10} and D_1 . This restores the sync tips of the video waveform to a potential of about -1 volt. Chrominance information is then removed by the low-pass filter R_9 , C_7 , and the remaining video signal is fed to the positive input of a difference amplifier. The negative input is connected to a potentiometer which controls the point at which the video waveform is sliced. The best setting will depend on the amplitude of the video waveform, but the range of the potentiometer should be great enough to cover the whole of the sync portion of the video waveform and enable separated syncs to be obtained at the output of the difference amplifier. This i.c. is in fact a high-speed dual line receiver with fully t.t.l.-compatible outputs and is ideal for use in this type of circuit.

A mixed sync waveform could, of

course, be obtained from the TV receiver in which the decoder is to be installed, but it was felt that it would be better to include one in the decoder if only to reduce the number of connections to the TV set. It also has another advantage in that the decoder may be fed from a "video ring main" where a separate feed of syncs may not be available.

As well as feeding the digital boards, the feed of mixed syncs is used to generate a clamp-pulse waveform which is used both on the analogue board and the video switching interface board in the TV receiver. The positive going trailing edge of the line sync waveform is differentiated by C_{10} and R_{16} and coupled into gate (84,12). The resulting negative-going pulse is inverted by gate (84,6) and a positive going clamp pulse is obtained which is about $4\mu s$ wide, and occurs during the back porch of the video waveform.

This pulse is used in the analogue board to clamp the video waveform before slicing the Teletext-data in a similar way to that used in the sync separator. Before describing this in

great detail, however, it would be as well to discuss some of the problems involved in successfully slicing the data signal.

Data slicing

In the simplest possible system, the video waveform could be fed via a capacitor into the positive input of a differential amplifier and by varying the direct voltage level on the negative input by means of a potentiometer, sliced video and data would be obtained at the output. The fact that picture information is sliced, and present at the output, is immaterial as precautions against this causing trouble have been taken elsewhere in the digital circuitry. However, because of the nature of the video waveform, the varying picture information will cause the average voltage of the signal to vary, and thus alter the position at which the video (and data) is sliced. If the data information were transmitted as perfect square-shaped pulses this would not matter because the output mark/space ratio of the data information would remain unaltered. However, the data cannot be transmitted in this way because the bandwidth requirements would become infinite, and the transmission system must be tailored to suit the normal TV band-

width of 5.5 MHz. The data is in fact transmitted in the form of raised cosine pulses, and this implies that the data must be sliced fairly close to the halfway point between its positive and negative peaks, if the mark/space ratio of the received data is to be close enough to the original for correct decoding. This is the case even if the received signal is completely undistorted by the receiver tuner and i.f. strip. In cases where the receiver i.f. amplifier has insufficient bandwidth or large group-delay errors, or the aerial is mismatched into the receiver, the setting of the slice level will be even more critical and in very severe cases of "ghosting" or i.f. misalignment it may be impossible to find a suitable point at which to slice the video waveform and obtain error-free readouts. The simple system described above could only be adjusted to give satisfactory results during periods of static transmission such as test card, where the picture information is constant and the slice level would remain unaltered.

One way to overcome the problem of changing level of the video waveform would be to use the d.c.-restored video present at the cathode end of D₁. However, a better system is to clamp the video during the back porch, and this method is used in this design. Tr₂ is

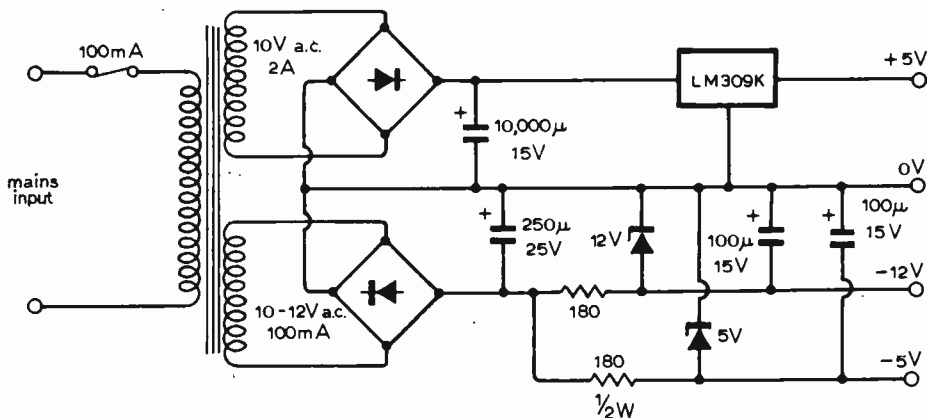


Fig. 4. A suggested power supply circuit.

turned on during the back porch by the clamp pulse, thus holding black level to approximately 0 volts regardless of the average level of the signal. Purists may point out that the clamp action will be upset by the colour burst. In practice, however, this only becomes a problem if large variations in level of the chrominance information occur, which will in turn cause the clamping point to vary slightly. If this is really a problem that cannot be solved by improving the aerial installation, then a 4.43MHz tuned circuit should be included in series with the collector of Tr₂. It has not been included as a standard feature in the circuit, partly because it has not proved necessary, but mainly because it would be rather difficult to set up correctly without expensive test gear.

The system described so far, consisting of a clamped video signal, sliced by means of a differential amplifier having a variable voltage level at its second input, is capable of giving very good results under most reception conditions. The slice level setting can be fairly critical under adverse conditions, however, and although the black level end of the waveform is maintained at a fixed level by the clamp, variations in amplitude of the video signal will also cause unwanted movement of the data level.

Small variations between the signal amplitude of different TV channels which may occur with some types of i.f. strip can be enough to prevent correct decoder operation. A more likely cause of video amplitude variations will occur in TV sets where the contrast control operates in the a.g.c. line. In this type of set the detected video information will vary as the contrast control is changed and nowhere in the circuit will a video waveform be available that does not vary with contrast control changes. It is obviously undesirable to have to alter the slice level whenever the contrast control is adjusted and some form of compensation must be provided to automatically keep the slice level correct. One method would be to have a variable gain video amplifier which was automatically adjusted to keep the data amplitude constant. However, this


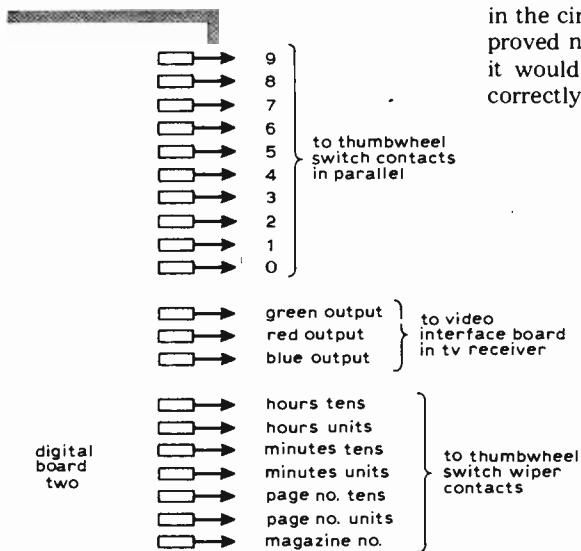


Fig. 5. Function switching. The "CLEAR" switch is a push, non-locking type, the "TIME" button is a push-push, locking switch and the rest are interlocking. Further constructional information appears in the next article.

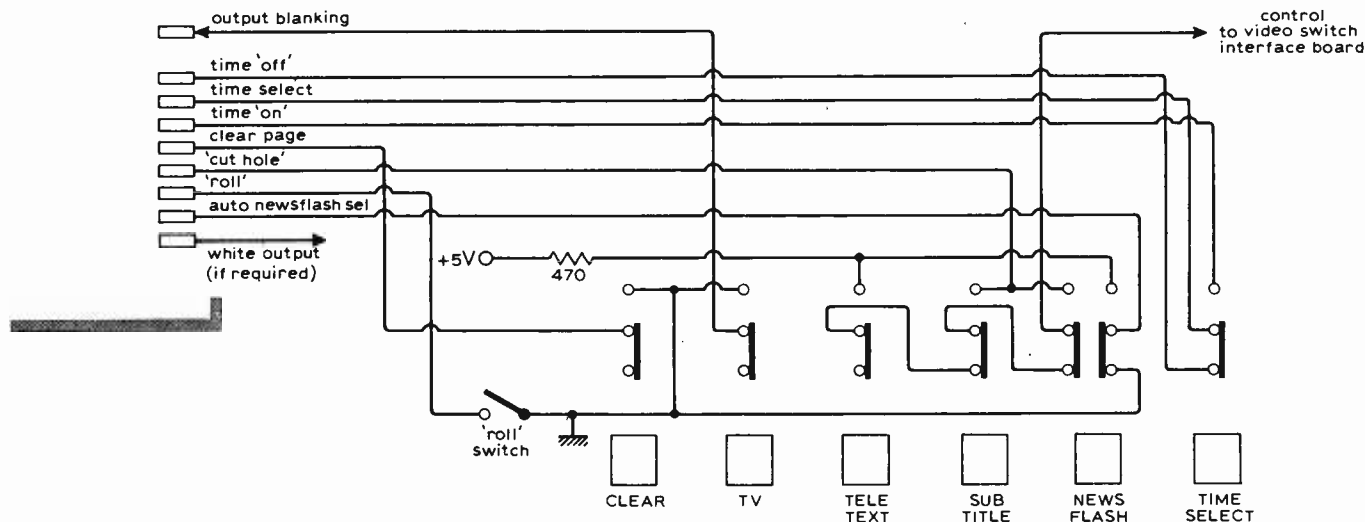

would undoubtedly be expensive, and a much simpler way of achieving the same end is to alter the slice level automatically, to enable it to follow the varying data amplitude. This is done by detecting the data amplitude with a peak-detector circuit and then using this information to set the slice level midway between the data peaks and black level.

Tr_3 forms the positive-data peak detection circuit with the decay time set by the time constant R_{15}, C_{15} . This time constant is made fairly long compared to the data bytes to prevent too much decay during the worst case condition of fourteen consecutive zeros. TR_4 then serves to offset the base-emitter voltage drop of Tr_3 and the shorter time constant R_7, C_{16} , increases the rise time of the peak detector circuit to reduce the effect of large noise spikes. The actual slice level is adjustable by means of VR_2 over the full range from 0 volts to the positive data peak level. Although theoretically this potentiometer should be in its mid position for correct data slicing, non-linearity distortion introduced by certain types of vision detector circuit will mean that the best results may be obtained if the slice level is not mid-way between the positive and negative peaks of the data. The difference amplifier used to perform the actual data slicing is the other half of the dual line receiver, IC_{81} .

Clock generation

It has already been explained that the clock waveform generated on the analogue board consists of the outputs of two oscillators, one locked to the incoming data, and the other adjustable in frequency to enable the display width to be adjusted. Switching between the two clock generators is performed by the 'lines 11-21' waveform. Gates (83,11) and (83,6) are cross coupled to form a free running oscillator. Oscillation is inhibited during lines 11-21 by the waveform present at gate (83,3), and by also inhibiting oscillation at the start of each TV line - Q of monostable 3 is fed into gate (83,11) - the oscillator is phase-locked to the TV lines. This ensures that the characters will have "clean" verticals. If the oscillator was merely free running the phase would alter at random from one TV line to the next, and ragged verticals would result. VR_1 adjusts the frequency of oscillation and forms the display width control.

Gate (84,8) forms the active part of the data clock oscillator. The frequency of oscillation is determined by L_1, C_1 and C_2 . The waveform on pin 9 of the i.c. only allows oscillation to take place during lines 11-21, and at all other times the gate output is held at 1 allowing the display clock through gate (83,8) to the output line. The oscillator is locked to the incoming data by means of narrow, negative going spikes fed into the third input of (84,8). These spikes occur at every data transition, gate (82,11)

providing the spikes derived from positive-going data transitions, and gate (82,6) spikes derived from negative-going data transitions. Although the oscillator circuit may appear rather crude, it has been found to give excellent results in practice. The main point in its favour is that it is extremely easy to set up, as there is only one adjustment, that being L_1 . The specified coil former is the Neosid A6 assembly, but in practice equally good results will be obtained with any former of approximately 3/16in diameter, containing an adjustable ferrite core, so long as it can be tuned in to the correct frequency of about 7MHz. The frequency stability of the circuit has been found to be perfectly adequate so long as polystyrene capacitors are used for C_1 and C_2 . The preferred method of adjusting the oscillator frequency will be dealt with later in the article, as will the rest of the decoder line up.

Power supply

The power requirements of the decoder are fairly modest. Five volts for the t.t.l. circuitry is required at approximately 1.3A, and this can most conveniently be obtained from a three-terminal regulator of the LM309K variety. The input voltage to the regulator must not be too great, however, as the device will be working fairly close to its limits and may exceed its maximum power dissipation figure. For this reason, the regulator must be mounted on a suitable heatsink.

A negative five-volt supply is required at a current of about 25mA, and a negative 12-volt supply for the character-generator i.c. at only a few milliamps. Both negative supplies may be derived from simple zener-diode type stabilizers, and a suitable power supply circuit is shown in Fig. 4.

Constructors should see that the connecting wires between the power supply and the decoder are of a suitable gauge to prevent excessive voltage drop of the plus five-volt rail. At a current of something greater than one amp, it only takes a few feet of thin connecting wire to cause a voltage drop of greater than 0.25 volts which will be sufficient to bring the five-volt rail outside the recommended specification for t.t.l. devices.

(To be continued)

The next article in this series will give constructional details of the teletext decoder. Subsequently there will be an article on interfacing the decoder with various colour television sets in common use.

Who thought up the synchronous satellite?

Dr Harold A. Rosen, a vice-president of Hughes Aircraft Company and a pioneer developer of synchronous communications satellites, has won the first L.M. Ericsson International Prize for "proposing the introduction of geostationary communications satellites and for his scientific and technological contributions to their development, design and operation." The prize, of 100,000 Swedish crowns (about £11,000) will be presented by King Carl XVI Gustaf at ceremonies in Stockholm in May. To be awarded every three years, the prize honours the memory of Lars Magnus Ericsson, founder of the L.M. Ericsson Telephone Company.

Dr Hakan Sterky, chairman of the prize committee, says "Dr Rosen proposed that a single satellite could be orbited at an altitude where it matches the earth's rotation and appear to be stationary, thereby simplifying connection with earth stations and providing 24-hour-a-day service". British readers, in particular, will be surprised that no acknowledgement is made to Arthur C. Clarke, who is widely considered to be the originator of the idea of satellites in synchronous orbit. Clarke pointed out in the October 1945 issue of *Wireless World* (eleven years before Dr Rosen joined Hughes) that a space-station orbit with a radius of 42,000km "has a period of exactly 24 hours. A body in such an orbit, if its plane coincided with that of the earth's equator, would revolve with the earth and would thus be stationary above the same spot on the planet. It would remain fixed in the sky of a whole hemisphere and unlike all other heavenly bodies would neither rise nor set." Further, a satellite in this orbit "could be provided with receiving and transmitting equipment . . . and could act as a repeater to relay transmissions between any two points on the hemisphere beneath . . ." (See "Extra-terrestrial relays", October 1945, pp. 305-308).

Hughes Aircraft state that all of the Intelsat communications satellites "are a result of Dr Rosen's synchronous-orbit concept." This is strange in view of the fact that it was a vice-president of Hughes Aircraft Company, Dr F. P. Adler, who gave public acknowledgement to Clarke's proposal more than a decade ago (June 1965 issue, p.269). Moreover, L. M. Ericsson have indicated that they know of Clarke (although they do not seem to be aware of the thoroughness of his 1945 proposal). Readers may be forgiven for questioning whether it really was Dr Rosen's concept.

Radio Telephones?



Ask Nolton!

Key-men keep in touch by radio-telephone. For the planning of these sophisticated installations, for the supply and installation of equipment, for advice and help in procuring licenses, for maintenance and servicing, key-men keep in touch with Nolton.

Nolton supply major radio-telephone users in the UK and overseas ... Nolton advise impartially on the suitability of equipment (of their own manufacture and also other leading brands) ... Nolton are represented throughout the UK. For all radio-telephone enquiries, write, ring, or telex Nolton.

Nolton Communications Ltd

Radiotelephone Division
 Fieldings Road Cheshunt Herts EN8 9TX
 Telephone Waltham Cross 33555
 Telex 28952




The Black Watch kit

£14.95!

★ **Practical**—easily built by anyone in an evening's straightforward assembly.

★ **Complete**—right down to strap and batteries.

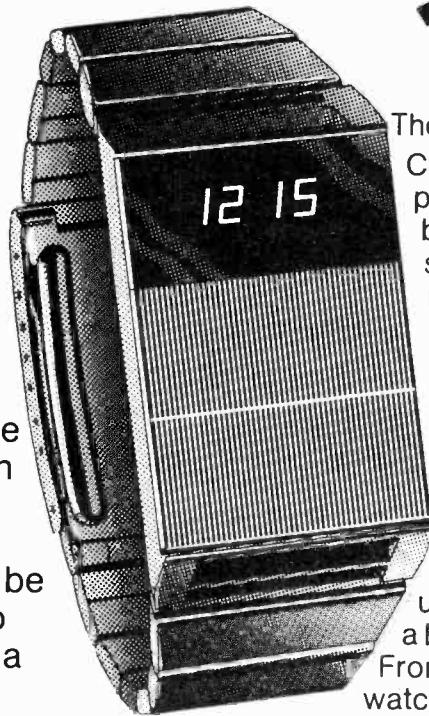★ **Guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day—but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.





The Black Watch by Sinclair is unique. Controlled by a quartz crystal, and powered by two hearing aid batteries, it uses bright red LEDs to show hours and minutes, and minutes and seconds. And it's styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.


The Black Watch kit is unique, too. It's rational—Sinclair have reduced the separate components to just four—and it's simple: anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.

Touch and tell

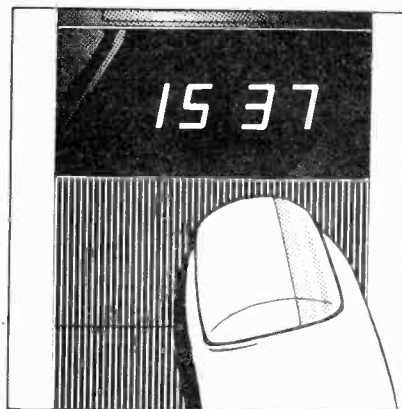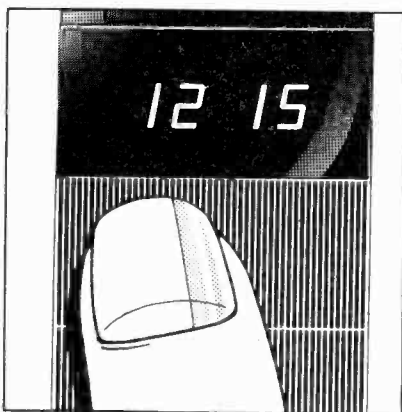Press here for hours and minutes... here for minutes and seconds.



Batteries easily replaced at home.

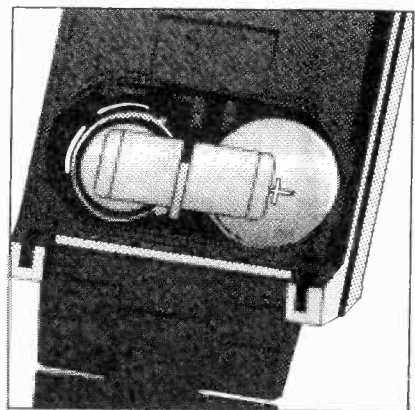

The specialist features of the Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra—see order form.)

Large, bright, red display—easily read at night. Touch-and-see case—no unprofessional buttons.

Runs on two hearing-aid batteries (supplied). Easily re-set using special button—no expensive jeweller's service.

The Black Watch – using the unique Sinclair-designed state-of-the-art IC.

The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology – integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate all circuitry for a digital watch on a single chip.

...and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

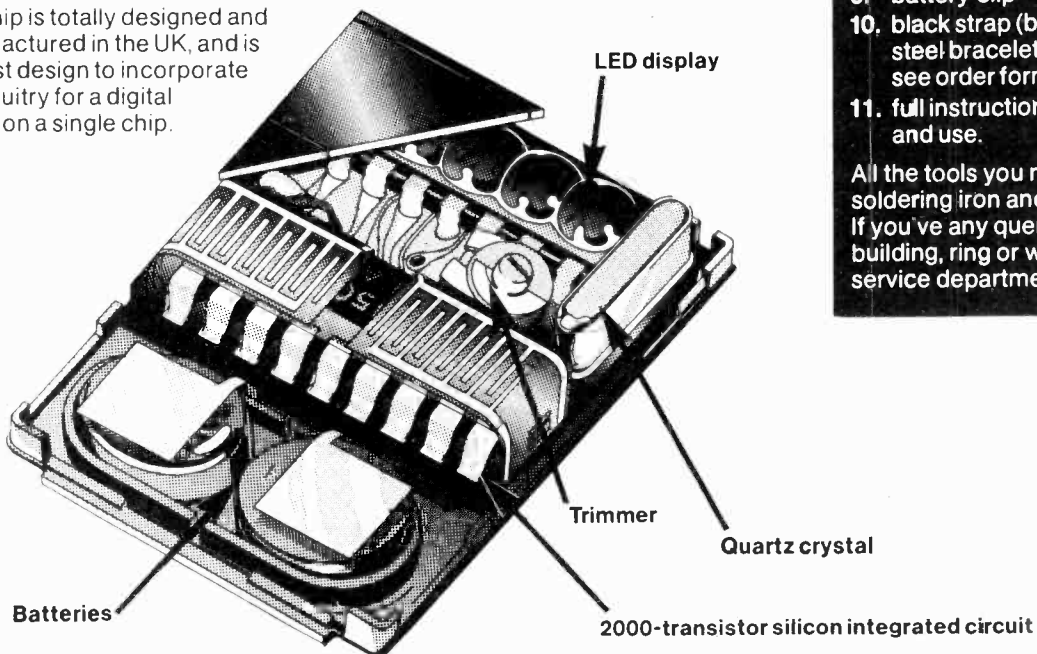

Complete kit £14.95!

The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra – see order form)
11. full instructions for building and use.

All the tools you need are a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to Sinclair service department for help.

Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit in original condition within 10 days and we'll refund your money without question. All parts are tested and checked before despatch - and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it - today!

Price in kit form: £14.95 (inc. black strap, VAT, p & p).

Price in built form: £24.95 (inc. black strap, VAT, p&p).

sinclair

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me	Total £	
..... (qty) Sinclair Black Watch kit(s) at £14.95 (inc. black strap, VAT, p&p).	* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.
..... (qty) Sinclair Black Watch(es) built at £24.95 (inc. black strap, VAT, p&p).	* Please debit my *Barclaycard/Access/ American Express account number
..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p).	

Name (please print) _____

Address _____

Signature _____ WW/4

FREEPOST – no stamp required. * Delete as required

S

single source makes

six way sense

- 1** **CONSERVES YOUR CASH.** No need to lock up capital in slow moving stocks.
- 2** **SAVES TIME.** Parts usually despatched by return. Orders phoned before midday are often on the way same day.
- 3** **A PROTOTYPE SERVICE.** Invaluable when assorted alternative experimental parts are required.
- 4** **SOLVES BUFFER STOCK PROBLEMS.** Eliminates need for heavy stock holding. *Our* stocks are at *your* immediate disposal.
- 5** **SIMPLIFIES ORDERING.** One transaction for a variety of parts saves bookkeeping and paper work.
- 6** **NO ORDER TOO SMALL.** Every enquiry is of equal importance and dealt with expeditiously.

Obviously Single Source Service can solve a lot of your day to day problems. As the first step get the relevant U-C S catalogue, which illustrates and describes hundreds of parts any of which you may want at any moment. Write, or better still phone 06072 78711, for it now.

So make United-Carr Supplies your SINGLE SOURCE for:-





It makes sense to use the United-Carr Supply Service when you require smaller or mixed quantities of any of the following:-

CINCH

Barrier terminal strips.	Audio sockets.
Fanning strips.	Group boards.
Marker strips.	Valve holders.
Printed circuit board edge connectors.	Fuse holders.
D Subminiatures.	Battery connectors.
Multi way plugs and sockets.	

DOT

Electrical Components.	Industrial Fastenings.
Single and double pole rocker switches.	Tee nuts.
Mains and low voltage indicator lights.	DOTLOC single thread lock nuts.
Plunger switches.	Lift the Dot fastenings.
Mains connector blocks.	Turnbuttons.
Automotive lamp holders.	Plugs and grommets.
Push on terminations.	Metal and plastic components.
Fuse holders.	Press studs.

FT

Edge clips.	W buttons.
Cable clips.	Door catches.
Cover plates.	Cable straps.
Turnbuckles.	Metal and plastic components.
Knob clips.	

Separate catalogues are available for:-

**Electronic Components,
Electrical Components
& Industrial Fasteners.**

Write or phone for your free copy, stating possible requirements.

Phase shift in loudspeakers

Considering the cause and measurement of phase shifts

by James Moir

James Moir & Associates

When the sound pressure maxima immediately in front of a loudspeaker do not occur at exactly the same instants in time as the corresponding maxima in the voltage across the loudspeaker voice coil, they are said to differ in phase. The phase shifts that actually occur in some typical current speaker systems were measured to obtain objective data.

The time delays or phase shifts produced by loudspeakers arise for several reasons which we will consider, starting with the simplest example, a single-unit wide-range loudspeaker. The mechanical force exerted on the adjacent section of the coil former by the current in the voice coil is in phase with that current, but the phase of the current with respect to the voltage across the voice coil varies throughout the frequency band because of the reactances present in the moving coil system. Typical measured values of the phase difference between the applied voltage and the resulting current for a simple single cone loudspeaker are shown in Fig. 1. The phase shift in the region of the bass resonance is critically dependent upon the type of enclosure. Below the bass resonance frequency the current in the voice coil is seen to be inductive with the current lagging the voltage, the phase angle approaching 40°; but the phase changes rapidly as the resonant frequency is passed, the current and voltage being in phase at resonance (100Hz), but the current leads the voltage above the resonant frequency where the voice coil behaves as a capacitor. In this particular example the current is in phase with the voltage again just below 300Hz but above this frequency the coil is generally inductive, the phase angle increasing continuously. Thus it will be seen that the mechanical force on the voice coil former is only rarely in phase with the applied voltage.

This effect is of greater significance in multi-unit speaker systems. These must incorporate electrical filters that protect the relatively fragile high frequency units from the powerful low frequency signals and channel the electrical signals into the speaker units best able to handle them. In a three or four unit system the filters are often of considerable complexity.



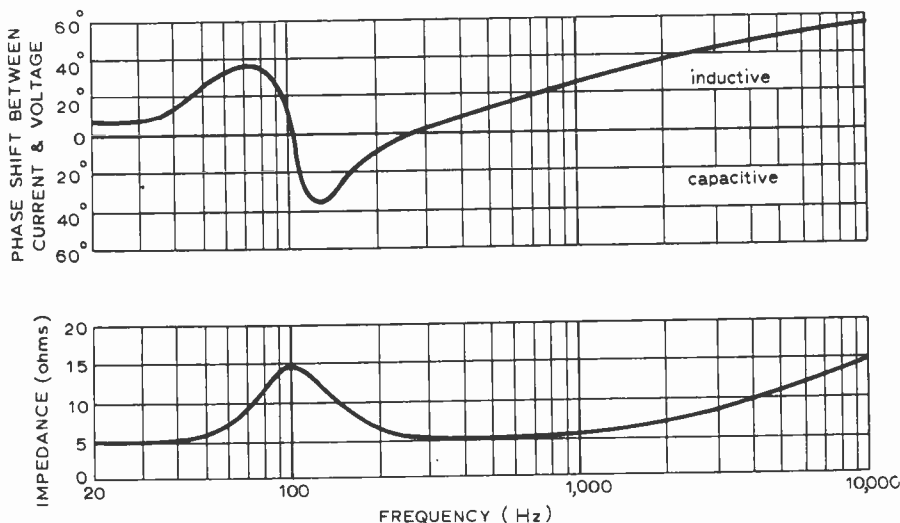


Fig. 1. Typical phase difference between applied voltage and resulting current for a single cone loudspeaker. The corresponding impedance curve is shown below.

Fig. 2. Phase angle and impedance curves for a three-unit loudspeaker system.

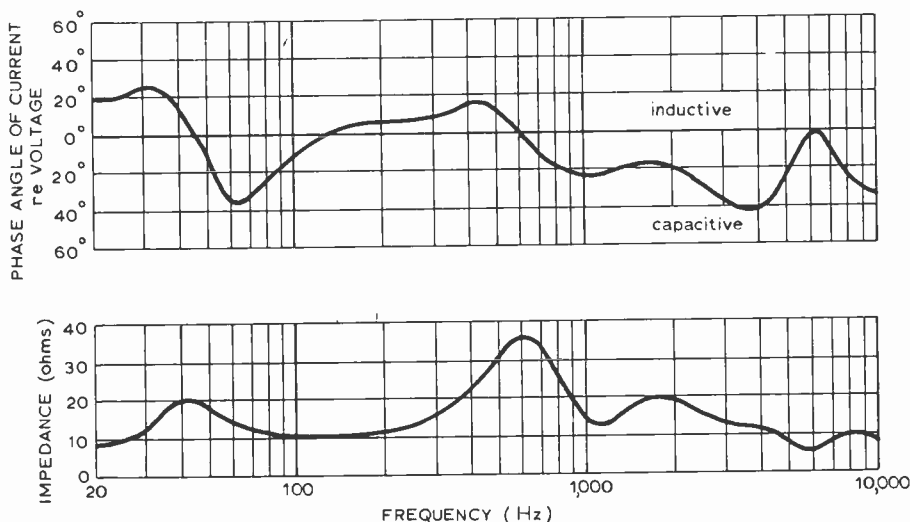

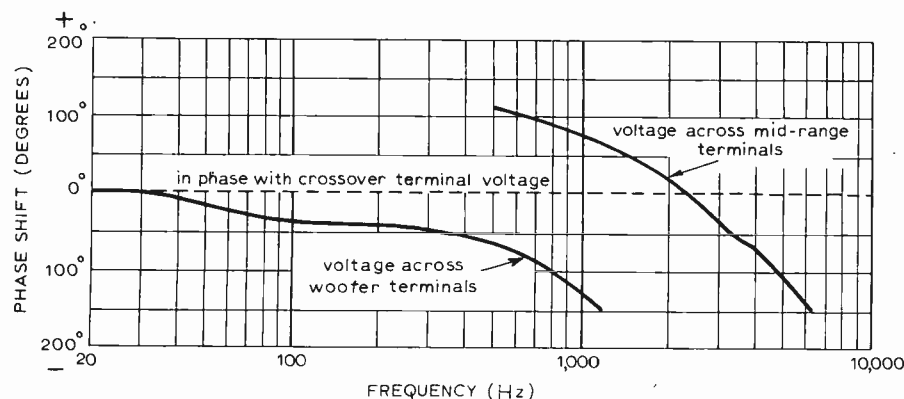

The curves of Fig. 2 illustrate the phase difference between the applied voltage and the current into the speaker system, but the voltage across the individual speaker units is not in phase with the voltage across the system terminals as a result of the reactance present in the crossover filters. Fig. 3 illustrates the phase shift between the voltage applied to the system terminals and the voltage across the terminals of the woofer and mid-range units in a well known multiple unit system having an excellent reputation. It will be seen that the filter networks introduce a considerable additional phase shift. In the cross-over region the voltage across the higher frequency unit is generally shifting in phase in the opposite direction to that across the lower frequency unit.

These phase shifts are all introduced by the electrical system but there are additional phase shifts in the mechanical coupling between the voice coil and the apex of the cone and between the apex of the cone and the remainder of the cone and surround. These are difficult to quantify but an approximate analysis shows that they are very frequency dependent and significant.

Acoustic phase shifts

The major phase shifts appear when sound waves are launched into the air. In a single cone wide range loudspeaker unit, the high frequency components of the acoustic signal are generally radiated from a small area near the cone apex, there being little high frequency radiation from the areas of cone near the surround. At frequencies below about 1kHz the whole cone tends increasingly to act as a more or less rigid piston and the signals are radiated by the whole of the cone and part of the surround. Thus the area radiating the high frequencies is usually about an inch behind the effective centre of the low frequency radiation and in consequence signals in the high frequency band will appear a fraction of a millisecond behind the low frequency signal radiated by the whole area of the cone.

These phase shifts due to the variation in the effective position of the source are much more serious in a multiple unit system employing separate speaker units for the low, mid

Fig. 3. Phase shift through a typical crossover network.

and high frequency ranges. In the usual type of enclosure the 'tweeter' handling the frequencies above 4-5 kHz will be mounted near the top of the enclosure, adjacent to the mid-range unit and perhaps 12-14 inches away from the centre of the l.f. unit. Generally the radiating surface of the tweeter will be a few inches in front of the effective radiation centre of the l.f. cone, so the higher frequencies will travel through the air a fraction of a millisecond before the frequencies handled by the woofer.

In practice the listener will sit two to four metres away from the loudspeaker enclosure and unless he is on the median line between the h.f. and l.f. units the path length between his ears and the h.f. unit will differ from the path length between his ears and the l.f. unit. In consequence, the signals from one unit will arrive before those from the other unit, or in conventional terms, there will be a phase difference between the signals from the two loudspeakers. This is of special significance in the changeover region when phase interference results in the appearance of peaks and dips in the frequency response, though the effect of phase shift on frequency response is not the real aspect of the present discussion.

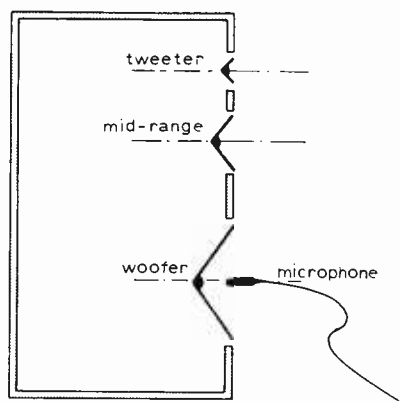


Fig. 4. Measurement of a woofer's phase shift with the microphone mounted in the plane of the front baffle.

Several recent speaker system designs attempt to minimize the phase shifts due to the cross-over networks and the lack of coincidence in the vertical plane of the emitting surfaces, by displacing the units, the high frequency radiators generally being set back behind the plane of the woofer. The exact positions of the various units are difficult to determine by measurements of the relative phase of the acoustic outputs of the units, but the "correct" positions can be found experimentally by adjustment of the unit location with a square voltage waveform applied. The adjustment must be done either in the open air or in an anechoic chamber to avoid the gross phase shifts that characterize any ordinary room.

Phase shift measurements

Measurements of the overall phase shift between the system input voltage that has been adopted as the reference and the sound pressure in front of the loudspeaker is not as simple as it might appear at first thought. While the position of the microphone diaphragm is obvious, the effective centre of the acoustic radiation from the speaker diaphragm is not known and cannot be determined with the required accuracy. Moreover the effective centre of radiation varies with frequency.

The microphone must be mounted in front of the loudspeaker and the spacing between speaker and microphone introduces a fixed time delay, or in phase shift terms, a phase shift linearly proportional to frequency. As this time delay is constant at all frequencies it does not introduce phase distortion, so any measurement of the phase shift should ignore that fraction of the total phase difference that is due to the physical spacing between microphone and loudspeaker.

This ambiguity in deciding on the actual part of the loudspeaker cone that emits the signal at any specific frequency limits the upper frequency to which phase shifts can be measured with an adequate degree of accuracy. At a frequency of 5kHz for example, the wavelength in air is 6.86cm and in consequence the phase nominally changes by 360 degrees for each 6.86cm increase in spacing between microphone and loudspeaker unit. If the phase shift measurements are to be really accurate the distance between the diaphragm of the measuring microphone and the point on the diaphragm for which the signal is emitted must be known with an accuracy that can rarely be achieved.

A first choice for the position of the measuring microphone would be the speaker/microphone spacing standardized for frequency response measurements, one metre. At a frequency of 5kHz this is $100/6.86 = 14.6$ wavelengths and an equivalent phase shift of $14.6 \times 360 = 5260$ degrees approximately, due

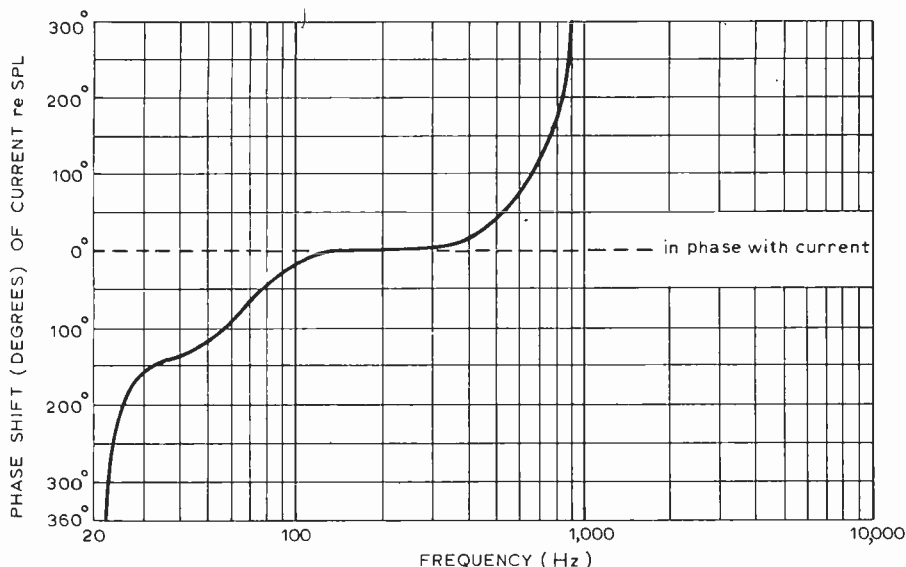


Fig. 5. Phase versus frequency response of a moving coil loudspeaker measured as shown in Fig. 4.

only to the distance between microphone and loudspeaker, and in consequence, a phase shift that does not introduce any waveshape distortion. It will be seen from Fig. 1 that a typical single unit speaker system will introduce a phase shift of about 30° - 60° at this frequency. Thus if the phase shift due to the speaker unit itself is to be measured to an accuracy as poor as 20%, it is necessary to measure the overall phase shift between input voltage and the sound pressure at the microphone one metre away, to an accuracy of about 5° - 10° in 5000° i.e. about 0.1%. This is just not possible for the effective centre of radiation in the speaker diaphragms, the point from which the one metre spacing is to be measured, is not known.

Nominally the constant time delay due to the speaker/microphone spacing of one metre can be compensated by the insertion of a delay line having a delay time of about 0.3ms. In practice this is not satisfactory for the speaker/microphone distance of one metre cannot be determined when the centre of the acoustic radiation from the speaker cone is not known with any accuracy.

An alternative solution to the problem is to minimize the spacing between microphone and loudspeaker, for this minimizes the time delay that must be compensated. Consideration suggests that the best compromise may be to mount the microphone with its diaphragm in the plane of the speaker opening (Fig. 4). At this position the phase shifts due to spacing time delay are of no significance at low frequency and only become of consequence at frequencies above about 10kHz where the wavelength is about 3.5cm. The microphone can probably be located with a positional accuracy that is perhaps one tenth of this, limiting the accuracy to which the overall phase shift can be measured to about ± 15 degrees at a frequency of 10kHz. Fig. 5 indicates the phase shift/frequency response of a typical wide range single unit loudspeaker when the measuring

microphone is mounted in the plane of the diaphragm opening.

Choosing a microphone location close to the loudspeaker unit may be the best compromise but it is not without its limitations, apart from that of accuracy mentioned earlier. As far as a listener is concerned the effective phase shift is that at his ears about two to three metres away from the loudspeaker. This cannot be directly measured if a multi-unit speaker system is employed. At any listening position there is in addition to the phase shifts discussed, another and generally more significant cause of phase shift, that due to the difference in the length of the air path between the listener's ears and the two sources of the acoustic signal. If there are only two units in the system the listener can eliminate these differences by sitting exactly on the medium line between the two units, but this is not possible if a three unit system is employed. If the phase shift at the listener's ears must be known, it must be separately measured for each unit, and if the total resultant phase shift at the distant listening point is to be obtained, it must be calculated from geometric considerations. This is clearly a tedious piece of simple arithmetic, but the writer has gone on record many times as saying that these phase shifts are of no consequence.

Value of phase shift measurement

Measurements of the phase shifts to a point in the diaphragm plane is of real use to the speaker development engineer when he is assessing the effect of design changes. Phase changes more rapidly in the vicinity of a resonance that does the amplitude and is a more sensitive indication of the resonant frequency and its Q. Thus the effect of such changes as cone or surround doping can be rapidly assessed even

though the effect of such a change is small and in the midst of a lot of other irregularities.

When a stereo system is employed, the absolute values of phase shift in the loudspeakers are of little significance, but it is important to ensure that the phase shifts do not change too rapidly with frequency and that there is uniformity of phase shift between the speakers coming off the production line. Rapid changes in the phase/frequency response of nominally identical samples leads to unstable positioning of the stereo image.

My thanks are due to Mr W. R. Stevens of our laboratory for the measurements of phase response which have been quoted.

Announcements

Papers presented at the second international conference on software engineering for telecommunication switching systems held in February in Salzburg, Austria are to be published as "Software engineering for telecommunication switching systems", IEE Conference Publication 135. Further information can be obtained from The Marketing Department, The Institution of Electrical Engineers, PO Box 8, Southgate House, Stevenage, Herts. SG1 1HQ.

A service for the design of I.S.I. circuits is available from Smiths Industries Ltd, Aviation Division, Cheltenham. A computer aided design and testing facility has been established to provide a design service for the low-volume market.

The Duddell medal and prize has been awarded by the Institute of Physics to Mr G. N. Hounsfeld of EMI Ltd for his development in the use of X-rays for the examination of three dimensional structures.

The National Closed Circuit Television Association's Annual Conference at University College, Cardiff is to be held from April 5th to 8th. Further information can be obtained from V. Ginn, College of Education, Cyncoed Road, Cardiff.

Sonab Ltd has moved to 214 Harlequin Avenue, Brentford, Middlesex TW8 9DW.

Cathodeon Crystals Ltd, Linton, Cambridge CB1 9JU, has received BS9000 approval for the manufacture of crystal based components for the telecommunications and electronics industries.

British Relay TV, Overline House, Crawley, Sussex is now relaying Southern-TV as a fourth channel to viewers connected to its cable-TV networks in the London regions of Bow, Fulham, Hammersmith, North Kensington, Paddington and Poplar.

Wound Electronic Components Ltd, Excelsis Works, Gogmore Lane, Chertsey, Surrey KT16 9AP are offering toroidal transformers designed and manufactured to customers specification.

Belmont A/V Ltd, Fircroft Way, Edenbridge, Kent TN8 6HA, UK distributors of the B.I.C. range of loudspeakers, have announced the granting of a US patent to B.I.C. for their application of the venturi principle in the field of acoustics.

Automatic battery switch-off circuit

Extending the life of small instrument batteries

by D. T. Smith

Clarendon Laboratory, University of Oxford

Nowadays, many small electronic instruments are powered by batteries. Battery prices have risen in recent years, and with the increasing prices of raw materials such as zinc, costs are likely to rise further. Moreover, it is frustrating to find equipment out of action due to flat batteries just when it is needed.

Much laboratory equipment is used intermittently and batteries then have a long life if the equipment is always switched off after use. However, people often forget to switch off, particularly when there is no obvious reminder (such as a light or noise) that the equipment is on. In practice, instruments are frequently left on for days or weeks when not in use. The circuit described here was designed so that it can be built into equipment without affecting performance or the normal controls, but will switch off the battery after a reasonable time if it not switched off manually. We chose a time of about 10 hours so that the equipment would operate for a full working day without interruption. Normal operation can be restored by moving the manual switch to off and back to on.

Circuit operation

Both capacitors discharge when the battery is off. When the battery is switched on, C_1 charges and gives a pulse of current to the base of Tr_1 , which conducts and feeds current to the base of Tr_3 to allow current to flow to the load. Initially, C_2 remains uncharged, and with the bias on the gate of Tr_4 , the tail current of the pair $Tr_4, 5$ is all taken

by Tr_4 . Base current is fed to Tr_2 which in turn drives Tr_3 into saturation. Voltage drop across Tr_3 is, therefore, quite small. Capacitor C_2 is slowly charged via R_7 until Tr_5 is conducting and drawing tail current. Current through Tr_4 is decreased together with the base current of Tr_2 , and Tr_3 is no longer saturated. The output voltage then falls and the bias on Tr_4 falls, while the bias of Tr_5 remains constant, so that a regenerative feedback loop is formed and the circuit snaps off.

When the circuit has switched off, the only drain on the battery is the current through R_1 ($10M\Omega$) and transistor leakage, and this is a negligible drain to normal batteries. With the output off, C_2 discharges rapidly through the gate of Tr_5 . When the operator switches off, C_1 discharges through D_1 and R_1 with a time constant of one second, so that the circuit is ready to be switched on again without delay.

The circuit switches off when the voltages on the gates of the f.e.t.s are about equal, that is, when C_2 has charged to about half of the output voltage. This gives an operating time $T = \log_2 2 \cdot C_2 R_7 \approx 0.7 C_2 R_7$.

The values shown give a calculated time of just under 10 hours. Other periods can be obtained by altering C_2 or R_7 .

The value of R_2 is chosen to suit the working current and battery voltage. A

low value of R_2 increases the battery drain, while a high value limits the working current; a suitable value is


$$R_2 = \frac{15V_b}{I_{out}}$$

Construction

The circuit was built as a printed circuit board with a p.t.f.e. insulated tag for the junction of R_7 , C_2 and the gate of Tr_5 . This extra insulation is necessary to give a leakage resistance large compared with the high resistance of R_7 ($10 G\Omega$), and care should be taken to keep this part of the circuit clean and dry to prevent the insulation from deteriorating. The circuit is not critical, as accurate timing is not required. A polycarbonate capacitor was used for C_2 to ensure low internal leakage. A maximum gate current of $2nA$ as quoted in manufacturers data for the 2N3819 would be disastrous, but in practice the gate current for this device is usually below $10 pA$.

This circuit has been fitted to a number of a.f. oscillators without any inconvenience to normal operation. Users need not be aware of the presence of the circuit.

Fig. 1. Circuit diagram of the switch-off unit.

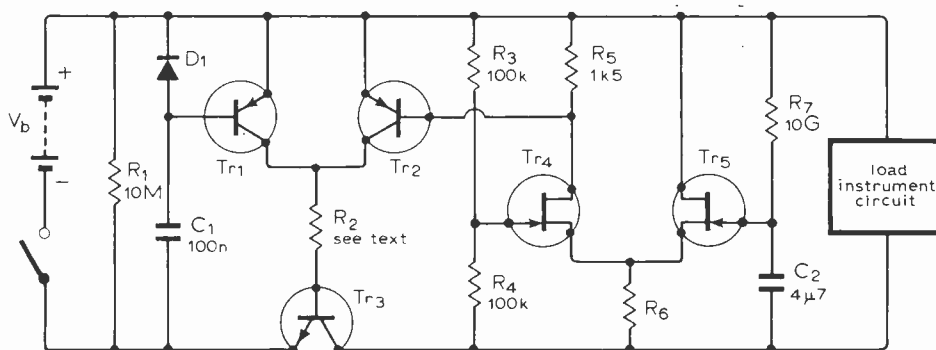

Components

- $Tr_{1,2}$ 2N4061, BC478 or similar small silicon p-n-p type
- Tr_3 2N3053, BC142 or a similar medium power silicon n-p-n type
- $Tr_{4,5}$ 2N3819 (n-channel silicon f.e.t.)
- D_1 any small silicon diode
- R_6 4k7 (9 or 12V battery)
- R_7 10k (15 to 27V battery)
- R_7 $10G\Omega \pm 20\%$ H13. Welwyn Electric Ltd, Bedlington, Northumbria NE22 7AA. (£1.08 in small quantities)

Diode model of the m.o.s.f.e.t.

An insight into device operation to clear up some of the difficulties encountered in its initial study

by B. L. Hart

North East London Polytechnic

From the point of view of the circuit engineer the d.c. model, for a given application, of an active device can be classified as "good" if it is as simple as possible, and easy to use on both pencil-and-paper and computer aided designs. Also it should be characterized by parameters that are readily obtainable by measurements at the device terminals and that relate circuit performance potentialities and limitations to device design choices and fabrication process technology.

The classic Ebers-Moll¹ (E-M) d.c. model of a bipolar junction transistor (b.j.t.) certainly fulfills these criteria. There can be little doubt that the E-M model has clarified the operation of a number of circuit designs and been responsible for the generation of some new ones. The advent of the equally classic Beaufoy-Sparkes² charge-control model of a b.j.t. facilitated the paper design, and predictable practical performance, of saturated b.j.t. switching circuits such as inverters, bistables, etc. and led to the formulation of various figures-of-merit for fast switching b.j.t.s.

Recently, work by Gibson³, Wedlock⁴, and others has led to the development of a simple d.c. m.o.s.f.e.t. model which is analogous to the E-M model of a b.j.t. The aim of this article is twofold: to clarify — at a level comprehensible by the circuit engineer, rather than the device physicist — the basic operation of a m.o.s.f.e.t.; to introduce the Gibson-Wedlock model and show how it meets the criteria of "goodness" outlined above.

Basic operation

Because of its importance in digital electronics we consider, throughout, an enhancement-mode⁵ device. The symbolic representation, together with schematic cross-sectional views of the n-channel device selected for discussion are shown in Fig.1(a), (b) and (c) respectively. The source(S) — drain (D) spacing is L and, by definition, the gate(G) "width" is W . The S and D diffusions — richly doped by comparison with the p-type substrate — are designated n^+ and have a plentiful supply of

electrons. Let us see what happens for the bias conditions $V_{GS} = V_{BS} \neq 0$. The action of the device may, for the time being, be represented by two p.n junction diodes — the source-substrate junction, and the drain-substrate junction — connected back-to-back. Irrespective of the polarity of V_{DS} there can be no significant drain current, I_{DS} . This

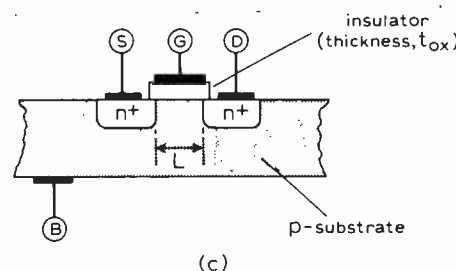
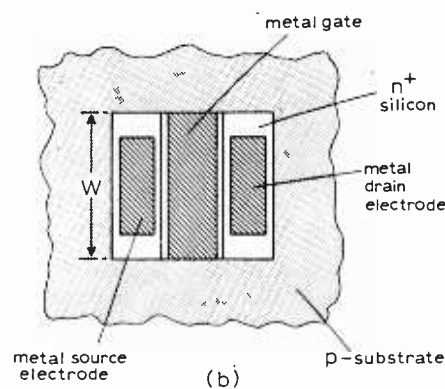
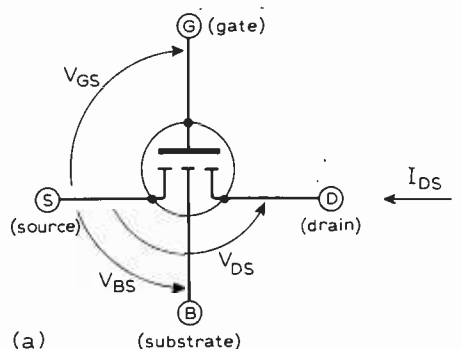


Fig. 1. N-channel enhancement-mode m.o.s.f.e.t. (a) symbolic representation and terminal voltage designation (b) plan view of physical construction (c) cross-section corresponding to (b)

is also the case if the substrate connection, B, is left floating (though this is an operating condition not recommended) because one or the other of the two diodes is always reverse-biased.

Suppose, instead, that $V_{BS} = V_{DS} = 0$ but $V_{GS} > 0$. Under d.c. conditions there is no current in the gate lead, i.e. $I_G = 0$, because of the insulating properties of the oxide layer. Gate G acquires a positive charge and a corresponding negative charge is induced in the substrate surface layer beneath the gate. This arises as a result of electrons, drawn in from S and D, that are attracted to this region by the field in the oxide and holes that are repelled away from it. When V_{GS} is sufficiently positive — by an amount known as the threshold voltage, V_T — enough electrons are concentrated in the substrate surface layer to compensate the positive charge due to substrate doping and device processing. Thus, when $V_{GS} = V_T$ the phenomenon of "inversion" is said to occur: the substrate just under the gate changes its polarity from p to n or "inverts." It must be borne in mind that the designation "n" means, basically, that the majority carriers are electrons, whether this be due to the fixed initial doping of the substrate wafer, or the induced doping from device biasing.

After inversion has occurred a continuous conducting layer or "channel" links the S and D diffusions. This channel, which is of uniform shape throughout its length, is normally only a few angstroms thick i.e. much less than the thickness, t_{ox} , of the oxide insulating layer (typically, 100nm). The n-channel forms with the p-substrate an induced p.n junction and, as with any conventionally fabricated junction there is an associated depletion region (see Fig.2(a), in which the thickness of the channel is exaggerated for clarity) and this serves to make the device self-isolating. Thus, built-in junction-isolation is not required, and a consequent saving in chip area is achieved, when a number of similar devices share a common substrate as in single-polarity m.o.s.f.e.t. memory systems such as those used in pocket calculators.

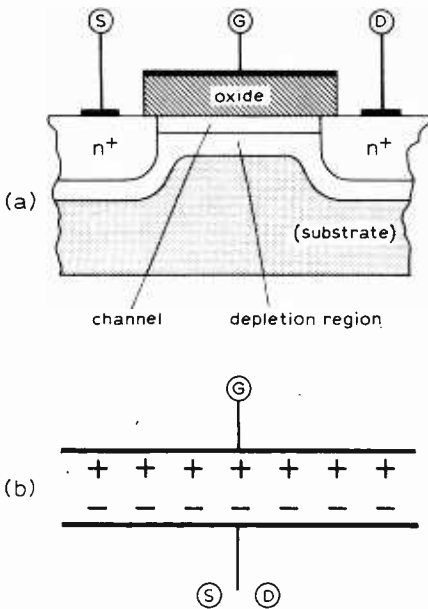


Fig. 2 (a) Showing the presence of channel and depletion regions (b) equivalent circuit of 2(a)

Under conditions of strong inversion ($V_{GS} - V_T > V_T$, say) and with $V_{DS} = 0$ the m.o.s.f.e.t. behaves physically as a parallel plate capacitor system (Fig.2(b)), in which one plate is G and the other, accessible via the source-drain connection, is the channel. The magnitude of the charge density on each plate is $C_0(V_{GS} - V_T)$, where C_0 is the gate-oxide capacitance per unit area. Let us now keep $V_{GS} > V_T$ and arrange that $0 < V_{DS} \ll V_{GS}$. The charge of majority carriers on the lower plate of the capacitor is able to drift, under the influence of the x -directed field: there is no reverse-biased p.n junction to impede the flow of electrons from S to D because the channel carriers have the same polarity as the S and D diffusions, hence $I_{DS} > 0$. Variations in V_{GS} cause variations in the density of charge carriers available for conduction, and it is the modulation of I_{DS} by the perpendicular field which gives the name field effect to the control function of this type of structure. (We have chosen $V_{DS} > 0$ for convenience. The choice $V_{DS} < 0$ leads to a negative value for I_{DS} : once a channel is established the induced majority carrier charge can drift from S to D or with equal ease – provided $|V_{DS}| \ll V_{GS}$ – from D to S, the particular direction being dependent on the polarity of V_{DS} .)

The assumed condition $V_{DS} \ll V_{GS}$ ensures that the field in the oxide – and the channel charge density – varies only slowly throughout the channel length, and is perpendicular to the substrate surface. This is the 'gradual-channel approximation' used in first-order mathematical treatments. The existence of a finite V_{DS} , and hence I_{DS} , means that the channel charge density $\sigma(x)$ is non-uniform. The x - directed field in the channel produces a potential difference $V(x)$ between S and some

point in the channel distance x away from it.

$$\text{Thus, } \sigma(x) = -C_0 \{ V_{GS} - V_T - V(x) \} \quad (1)$$

If $V_{DS} \ll V_{GS}$, $\sigma(0 < x < L) \approx -C_0 \{ V_{GS} - V_T \}$, and the channel depth varies only slowly along its length – see Fig.3(a). When V_{DS} is comparable with V_{GS} , $\sigma(x)$ varies significantly along the channel and this leads to a more pronounced wedge-shaped profile; however, a conducting channel always links S and D providing $|\sigma(0 \leq x < L)| > 0$. A limiting condition exists when $V_{GS} - V_T - V_{DS} = 0$ because, then, $|\sigma(x)|$ falls to zero at the drain end, i.e. $V(x) = V_{DS}$, where the field in the oxide is least (Fig.3(b) – full line for channel outline). When $V_{DS} > (V_{GS} - V_T)$ the channel does not extend along the full length of the source-drain separation but terminates (is pinched-off) at some point P distant x_p from S, at which $|\sigma(x_p)| \approx 0$. (Fig.3(b), dotted curve).

The choice of the term pinch-off for this mode of operation is not a completely happy one since it suggests that $I_{DS} = 0$ which is clearly not possible here because it is the presence of I_{DS} which is responsible for $V(x_p)$. A self-limiting process is established in which the current remains sensibly constant at that value corresponding to $x_p = L$, despite further increases in V_{DS} . Obviously $|\sigma(x_p \leq x < L)|$ cannot be precisely zero because that would mean the absence of charge carriers in the surface substrate layer for $x_p \leq x < L$. That part of V_{DS} in excess of $(V_{GS} - V_T)$ appears across the virtually depleted region between P and D and the field there helps speed the small, but finite, number of electrons at P on the remainder of their journey to D. Current continuity in the path from S to D is maintained because I_{DS} is dependent on the product $\sigma(x)v(x)$, where $v(x)$ is the mean carrier velocity. As $|\sigma(x)|$ decreases with x , $|v(x)|$ increases. A self-limiting process, such as the one mentioned, is not unfamiliar in electronic devices and

Fig. 3. (a) Channel conditions for $V_{DS} < V_{GS}$ (depletion layer omitted) (b) Channel conditions for $V_{DS} = (V_{GS} - V_T)$, full-curve; $V_{DS} > (V_{GS} - V_T)$, dotted curve.

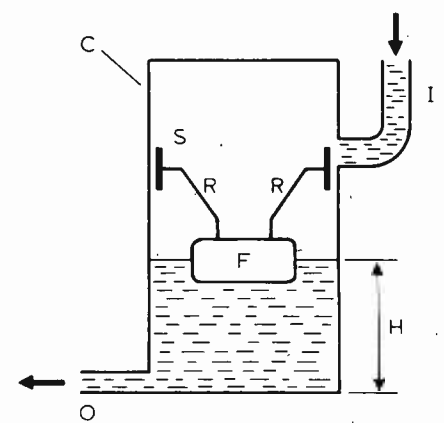
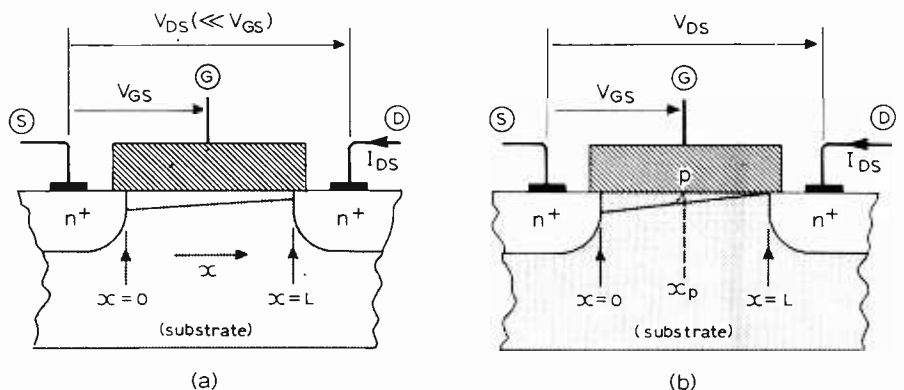


Fig. 4. An hydraulic analogy to m.o.s.f.e.t. pinch-off mode operation

suggests the existence of some internal negative feedback mechanism. A simple hydraulic analogy will help to clarify this for the case of the m.o.s.f.e.t.

Fig. 4 shows the cross-section of a possible self-limiting water flow system. C is a cylindrical chamber with an inlet pipe I, the diameter of which is much greater than that of the outlet tube, O, located at the bottom. Cylindrical sleeve, S, attached by rigid support rods, R, to a float unit, F, slides up and down the internal wall of C and – in one position – is capable of completely covering the inlet port. Under steady-state conditions (hydrodynamic equilibrium) F floats to a level, H, above O causing S to partially cover the inlet port. In likening this condition to pinch off in a m.o.s.f.e.t. we note that a flow rate (channel current), which is a function of the bore of O, is associated with a head, H (channel voltage) that, in itself, restricts the flow rate to a sensibly constant value dependent on the mechanical dimensions (electrical parameters) of the component parts. Other, and more precise, hydraulic analysis could be envisaged, but the one mentioned serves well enough for our discussion. The ideal constant-current characteristic of pinch-off operation is not observed practically because of the dependence of I_{DS} on conducting channel length, which is a weak function, usually, of V_{DS} . Though this effect is understood, and can be allowed for, it is neglected in the d.c. model now presented.

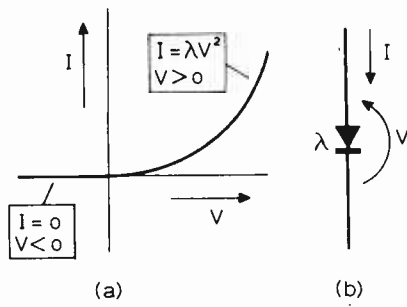


Fig. 5. (a) Characteristics of a square-law-diode (b) symbolic representation of (a)

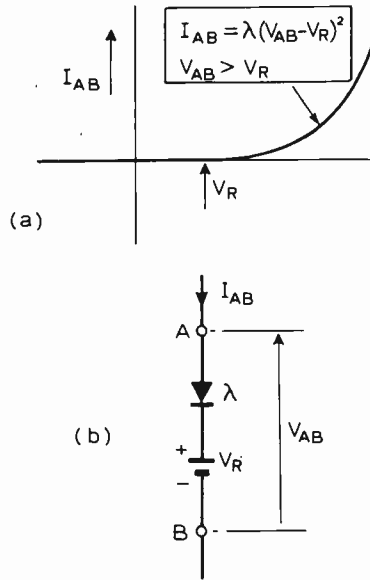


Fig. 6 An equivalent circuit of (a) is shown in (b)

Fig. 7. M.o.s.f.e.t. square-law-diode d.c. model (a) form based on equation (4) of text (b) arrangement of (a) (c), development of (b)


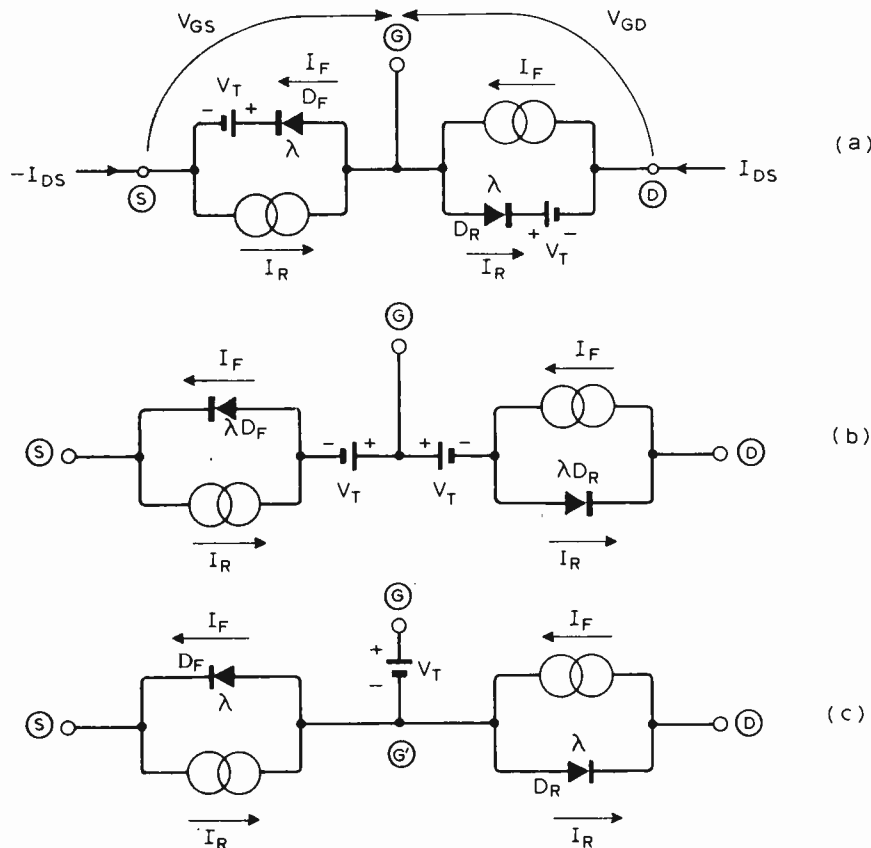


Fig. 8. Final d.c. model for Fig. 1(a)

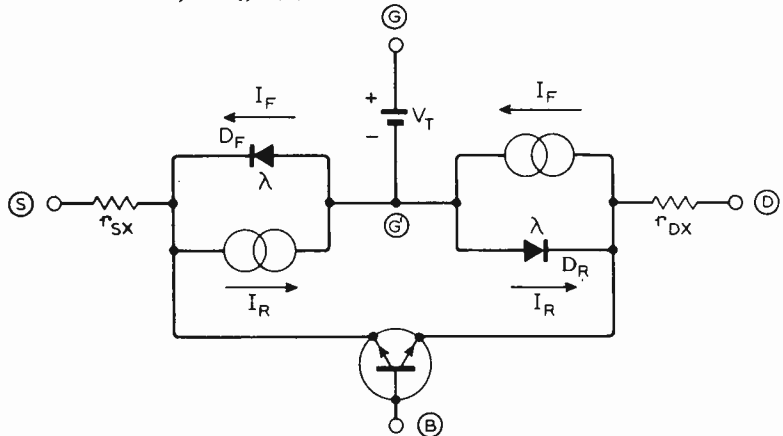

M.o.s.f.e.t. d.c. model

For $V_{GS} < V_T$, $V_{DS} < (V_{GS} - V_T)$, the d.c. characteristic of the n-channel m.o.s.-f.e.t. shown in Fig. 8 can be expressed mathematically in the form,

$$I_{DS} = \lambda [2V_{DS} (V_{GS} - V_T) - V_{DS}^2] \quad (2)$$

where λ is a conductance coefficient (with dimensions A/V^2) given by,

$$\lambda = \mu_e \epsilon_{ox} (W/2)L t_{ox} \quad (3)$$

in which: ϵ = permittivity of free space; ϵ_{ox} = relative permittivity of oxide; μ_e = effective mobility of electrons in the substrate surface layer.

A simple derivation of (2), based on a quantitative discussion of the physical electronics of device operation outlined above will be given in Part 2.

For the present purposes we can put (2) into a more convenient form by making the temporary substitutions:

$$a \equiv (V_{GS} - V_T) \quad b \equiv V_{DS}$$

Then, $I_{DS} = \lambda [2ab - b^2] = \lambda [a^2 - (a-b)^2] \quad (3)$

Now, $(a-b) = (V_{GS} - V_T - V_{DS}) = (V_{GD} - V_T) \quad (4)$

Hence, substituting back into (3), (2) becomes,

$$I_{DS} = \lambda [(V_{GS} - V_T)^2 - (V_{GD} - V_T)^2] \quad (5)$$

Equation (5) can now be used, directly, in the construction of a d.c. model by imagining a fictitious square-law diode with the d.c. characteristic in Fig. 5(a).

There is no standard symbol for such a device: the one proposed here, and favoured by this author, for its simplicity is shown in Fig. 5(b). Clearly, the d.c. circuit model for a square law characteristic offset from the origin by an amount V_R , Fig. 6(a), is an ideal square-law diode with an inbuilt opposing battery V_R (see Fig. 6(b)).

By an extension of this argument the model representing equation (5) and hence (2), is shown in Fig. 7(a). The intermediate form Fig. 7(b) and the final form, Fig. 7(c), both have terminal voltages and currents respectively identical to those of Fig. 7(a) and are thus - from a circuit theory and application standpoint - equivalent to Fig. 7(a). Two effects have been ignored, substrate bias and bulk resistance, but these will be considered in Part 2.

(To be continued)

References

1. Ebers, J. J. and Moll J. L., "Large signal behaviour of junction transistors" *Proc. I.R.E.*, Dec. 1954, pp 1761-72.
2. Beaufoy R., and Sparkes J. J., "The junction transistor as a charge controlled device," *A.T.E. Journal* 317, Oct. 1957.
3. Lo A. W. and Gibson J. J., "Simple MOSFET modelling for Digital Applications", *IEEE Journal of Solid State Circuits*, Oct. 1973, pp 391-393.
4. Wedlock B. D., "Static large signal field effect junction transistor models" *Proc. IEEE*, April 1970, pp. 593-595.
5. Hart, B. L., "Classifying f.e.t.s", *Wireless World*, Jan. 1975, pp 2-3.

World of Amateur Radio

Integrated-circuit transceivers

Back in 1970, Tich Ryan, G3VJN, found that the linear integrated circuit amplifiers types CA3020 and CA3020A, usually regarded as intended for audio frequency applications, were generally capable of providing significant r.f. output at frequencies as high as 21MHz. On 7MHz the CA3020 will usually provide 500mW output and the CA3020A over 1-watt.

A number of British amateurs have since used such devices in conjunction with the SL600 series of integrated circuits to provide compact, all-solid-state s.s.b./c.w. transceivers. One of those who have recently been interested in this approach is Leslie Moxon, G6XN, who has built an equipment which includes two of the recent SL613 devices to provide r.f. clipping of the speech. Powered by a 6-volt lantern battery, his transceiver provides an output of about 250mW on 14MHz from a CA3020A and is capable of working quite easily into Eastern Europe. He has also been developing a 2-watt "linear" amplifier for use when higher power is needed for long-distance contacts.

More repeaters

Two more v.h.f. repeaters have been authorized by the Home Office: Moely-Parc, GB3MP, and Burnley, GB3RF, both intended primarily for use by n.b.f.m. mobile and portable stations. GB3MP is expected to open during March or April on channel R6 (145.15MHz in, 145.75MHz out) and is sited at the IBA's television station near Clywd, North Wales. Under normal propagation conditions, it is expected to provide coverage of much of North Wales and North-west England, including Manchester, Liverpool, Preston and the coastal strip up to the Morecambe Bay area as well as parts of the Isle of Man. The repeater, under the aegis of the UK FM Group (Western), has been financed largely by contributions from over 125 licensed members. The vertically polarized aerials, between 200 to

300 ft up the IBA mast, are over 1300 ft above sea level. Applications have also been submitted by this group for 70cm u.h.f. repeaters at Manchester (GB3MR), Colwyn Bay (GB3LL), Liverpool (GB3LI) and Stoke-on-Trent (GB3ST). A linear repeater project is also being considered.

The very high usage of the London repeater, GB3LO, has been measured by W. Blanchard, G3JKV, and amounts to an average of between 51 to 58 minutes per hour throughout the period 0800 in the morning to midnight and remains substantial at all times except between 0400 and 0600.

The latest IARU list of repeaters in the German Federal Republic includes over 120 operational stations including some cross-band (432/144 MHz), r.t.t.y., 1260MHz and amateur TV repeaters. A 70cm amateur TV repeater in Alexandria, Virginia, has a vision output of 800 watts e.r.p. and handles both vision and sound signals conforming to the US 525-line specification.

Random communication?

There seems among some British amateurs a growing degree of disillusion with the way that amateur phone communication is developing, arising from the widespread adoption of the popular and effective Japanese s.s.b. transceivers for h.f. and increasingly for v.h.f. Operation of these units, unless carried out with specific aims or as part of an interest in aereals or propagation, often fails to retain the interest of amateurs who previously spent part of their time testing home-built equipment or "assembling" highly individual stations based on commercial and surplus units. Often — as in the classic Tony Hancock record — amateurs who acquire the current all-swinging little boxes show a burst of eager activity followed by fewer and fewer appearances on the bands. Is there any morale to be drawn from the fact that similar fading interest does not seem to affect those who pursue specific operating interests such as low-power (QRP) operation, the various specialist modes or even c.w.? One has the impression (or is it merely prejudice?) that amateur operating activity that involves some degree of personal effort or skill or training or with a definite technical or other aim results in far more dedication than random radiotelephone operation based on one specific piece of equipment. Few people would wish for long to sit beside an ordinary telephone dialling random numbers — or would they?

On the bands

The Home Office has approved the start of the GB2ATG r.t.t.y. news bulletin broadcasts from March 7, following four

weeks of trial transmissions. The bulletins are transmitted on Sundays at 1200 (3590kHz, F1, 170Hz shift); 1215 (144.6MHz beaming north from London, F1, 850Hz shift); and 1230 (London area only, 144.6MHz, F2, 170Hz shift).

The Royal Signals Institution has made a grant of £200 to the Royal Signals Amateur Radio Society towards the cost of new aereals, including a ten-element crossed-Yagi, to allow the headquarters station, G4RS, at Blandford Camp, Dorset, to operate through the Oscar beacons.

The Home Office has refused an RSGB request to lift or modify the restrictions applying to the use of 430 to 432 MHz by amateurs living within the area 53-55° north, 2-3° west and has stated that these are likely to continue for many years.

During December/January a number of contacts were made on 1.8MHz by European stations (including some in the UK) with Australian stations in Victoria and Western Australia. The "twilight boundary" or "Grey line" technique (working along the great circle route representing the dawn/dusk or dusk/dawn boundary) has also brought good long-distance contacts to many stations on 3.5MHz during recent months.

The RSGB has recommended that QSL cards should not exceed about 5½ by 3½ inches as larger cards cause handling problems for the QSL Bureaux.

In brief

Class A licences in the series G4FAA are likely to be issued soon. Over 21,750 people held UK Class A, B or amateur TV licences on November 30, 1975 and there were almost 6000 mobile licences

... The British Amateur Radio-Teleprinter Group are holding a "Spring r.t.t.y. contest" between 0200 GMT on March 27 to 0200 GMT on March 29... The Norwegian national society, NRRL, has a membership of just over 2500 with about 3700 licensed amateurs in the country and with some 18 repeaters in operation... "World Radio Club", the BBC World Service weekly programme for short-wave listeners, has recently enrolled its 25,000th member... The RSGB are providing an examination centre in Central London for the next Radio Amateurs' Examination on May 20... Among recent new ITU prefix allocations are: D2A to D3Z Angola; D4A to D4Z Cape Verde; and D5A to D5Z Liberia... The Emley Moor beacon station (February issue) is under the aegis of the Northern Heights Amateur Radio Society and is not yet in regular operation... A mobile rally is being held for the North Midlands at Drayton Manor Park, Tamworth on April 25; the White Rose Rally is at Lawnswood School, Leeds on March 28.

PAT HAWKER, G3VA

Introducing analogue multipliers

This article is complemented with the practical circuits of set 29 of Circards


by J. Carruthers, J. H. Evans, J. Kinsler & P. Williams

Paisley College of Technology

In the processing of electrical signals there is a need for circuits that can perform all the standard arithmetical processes – addition, subtraction, multiplication and division. The first two fall into the domain of linear amplifiers and present no great difficulty; the last-mentioned pair provide a real challenge to the ingenuity of circuit designers. Fig. 1 shows the waveforms of a particular example where an input signal Y is to be under the control of a second input X, the output being of the form XY. This is a gain-controlled amplifier and is one of the simpler forms of multiplier since usually the gain is required to be either positive or negative and not both. Hence X takes up only one polarity, and Fig. 2 shows the multiplier as needing to operate in only two of the four quadrants viz X positive, Y positive and X positive, Y negative. Such a system can be realized as in Fig. 3 where v_1 corresponds to Y and v_2 to X. In many such circuits it is not even essential that the gain be a linear function of v_2 , in which case the circuit ceases to be a multiplier. A problem with circuits based on this idea is that of finding a resistor having negligible non-linearity over a suitable range of currents and voltages, while being controllable by an external signal.

While true and direct multiplication would be ideal, and can be obtained by using suitable transducers such as Hall-effect devices (see card 9), the designer often has to resort to devices and circuits obeying other laws. These are then manipulated until some combination of them yields a term which is proportional to the product of two signals.

It can be very difficult to eliminate all unwanted terms consistently and over a wide range of temperatures and supply voltages. One well-established technique is to use a circuit with a square-law voltage transfer function. This can be synthesized by a "piece-wise linear" technique, where a network of diodes, resistors and reference voltages, provides a slope that changes progressively as the input increases (see card 1). With a large enough number of segments, a power law can be approached

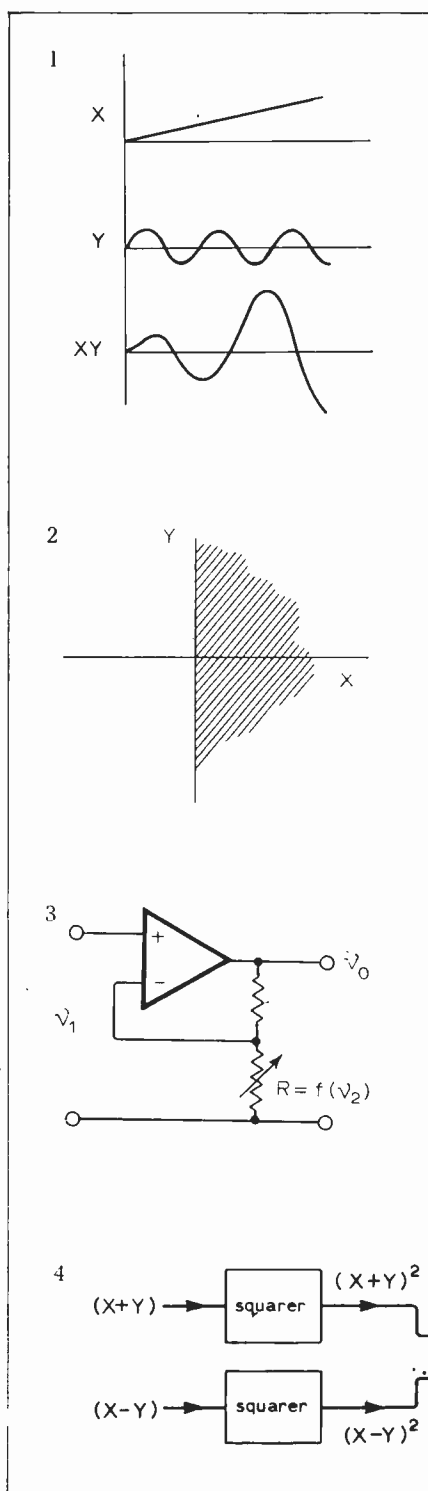


to any desired degree of accuracy. For economy the number of segments has to be restricted particularly if both polarities of input have to be accommodated – twenty or so might be needed in such a case.

The quarter-squares multiplier applied in analogue computing uses two such squaring circuits as shown in Fig. 4. The sum of the two input signals is fed to one squarer, and the difference to a second. Each output contains a product term but also the square of each input signal. By subtracting the two outputs, these square terms cancel leaving only the product term, in this case $4XY$ i.e. a quarter of the output giving the desired multiplication of X by Y (card 1).

Of considerable interest in this respect are the characteristics of field-effect transistors. Both junction and m.o.s. devices have an on-resistance below pinch-off that is controlled by the gate-source voltage. The resistance is non-linear but can be linearized with feedback, while the control-law contains a square-law term (card 10).

Although bipolar transistors have output current/input voltage transfer characteristics which include square-law terms, their true nature is exponential with all their higher-order terms. It would be pointless to try to manipulate these transfer functions in the same way as above. Instead the exponential function is exploited directly in various ways. The exponential equation is reasonably accurate for p-n junctions over a few decades of currents. To ensure that the current in the diode/transistor is well-controlled the device can be placed in the feedback path of an operational amplifier, Fig. 5.

One problem introduced by the use of a transistor is that of the increased loop gain, the transistor operating effectively in common-base with a voltage gain dependent on the input voltage. This leads to h.f. oscillation unless the amplitude-frequency response is carefully controlled by means of external compensation — one possibility being capacitive feedback from output to inverting input, by-passing the transistor at high frequencies. To use this logarithmic function for multiplication (as in card 4) the system shown in block diagram form in Fig. 6 may be used. The antilog circuit is simply a log circuit with input (resistor) and feedback (diode/transistor) elements interchanged. Similar systems can be devised to provide other power law and ratio circuits by expressing the desired function in log/antilog forms first.

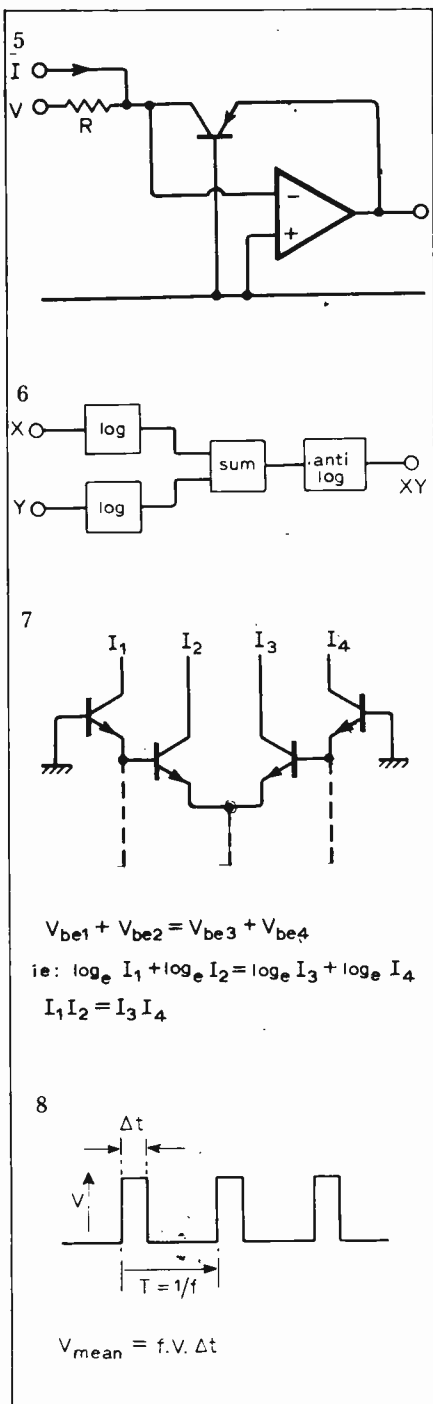

A related technique uses multiple transistors (card 8), shown in a general configuration in Fig. 7. It is assumed that the currents are controlled by external generators and/or feedback with one of them, or the difference between two of them, as the output. In the example shown, for I_2 maintained constant, $I_1 \propto I_3 I_4$ i.e. a multiplier. As shown, operation would be restricted to a single quadrant, but a large number of circuits have been published both to extend the operation into all four quadrants and to produce a range of interrelationships such as those based on the log approach.

A totally different approach yielded many ingenious and effective multipliers, prior to the ready availability of matched transistors. It stems from the concept that the terms to be multiplied need not remain in the same physical domain while being processed e.g. the variables of interest may both be voltages and the output may also be required as a voltage but each input may be used separately to control a different parameter of an output waveform, while a third property might be proportional to the product of the other two.

Consider the pulse waveform shown in Fig. 8. The pulse height is V , the repetition frequency $f=1/T$ and the pulse width of Δt . The mean output voltage as would be indicated on a moving coil meter is given by the product of these three variables, increases in each individually producing a proportional change in that mean value. Thus if any pair of these variables (f, V), ($f, \Delta t$) or ($V, \Delta t$) is brought under the separate and linear control of two input voltages, then the mean output voltage is a measure of the input product (card 2). There is a close relationship between these circuits and various forms of pulse modulators in the same way that the analogue multipliers described earlier are related to amplitude modulators.

There are purely digital methods of multiplication, but an intermediate solution is offered by the multiplying d.-to-a. converter. For a given binary input the converter has a number of output switches activated. If these operate on an external reference voltage the final output depends on the product of that reference voltage and the binary number. A class of digital circuits called binary-rate-multipliers is used to operate on a pulse train, producing a second train of pulses at a slower rate, card 3. At first sight this must cast doubts on the terminology since we associate multiplication with outputs greater than the inputs. The property of the circuit is however to multiply the input pulse rate by a factor such as $n/100$ where $n < 100$ and n can take up any value between 1 and 100, i.e. it is equivalent to multiplying by n but shifting the decimal point by two places.

The variety of methods available for achieving the multiplication of two

variables electronically is growing, and modules are readily available to a high degree of accuracy. As the methods vary widely in both properties and in the physical processes involved it is important to consider the options carefully — it is a field where the opportunities to place one's foot firmly in it (unspecified) are remarkably high.

Topics of set 29 Circards

Quarter-squares multiplier
 V-f converter multiplier
 Delta-sigma modulator/multiplier
 Log-antilog multiplier
 Triangle-wave averaging multiplier
 Four-quadrant multiplier — characteristics
 Four-quadrant multiplier — applications
 Translinear multiplier
 Hall-effect multiplier
 F.e.t. analogue multiplier

Tested circuits on the above topics are given in set 29, obtainable for £2 post free from:

IPC Electrical-Electronic Press Ltd
 General Sales Dept, Room 11
 Dorset House
 Stamford Street
 London SE1 9LU

Subscriptions cost £18 for ten sets (100 cards minimum). When ordering specify which set your order should start with, and make cheques, postal orders or money orders payable to IPC Business Press Ltd. See advertisement on page 6).

Topics covered so far in Circards are:

- 1 active filters
- 2 switching circuits (comparator and Schmitt circuits)
- 3 waveform generators
- 4 a.c. measurement
- 5 audio circuits (equalizers, etc.)
- 6 constant-current circuits
- 7 power amplifiers (classes A, B, C, D).
- 8 astable multivibrator circuits
- 9 optoelectronics: devices and uses
- 10 micropower circuits
- 11 basic logic gates
- 12 wideband amplifiers
- 13 alarm circuits
- 14 digital counters
- 15 pulse modulators
- 16 current-differencing amplifiers — signal processing
- 17 c.d.as — signal generation
- 18 c.d.as — measurement and detection
- 19 monostable circuits
- 20 transistor pairs
- 21 voltage to frequency converters
- 22 amplitude modulators
- 23 reference circuits
- 24 voltage regulators
- 25 RC oscillators-1
- 26 RC oscillators-2
- 27 Linear c.m.o.s.-1
- 28 Linear c.m.o.s.-2
- 29 Analogue multipliers
- 30 Non-linear functions (available April)

Television tuner design notes

Constructional hints in the light of experience


by D. C. Read, B.Sc.

Following publication of the TV tuner design details (WW, October, November, December 1975 and January 1976), a number of aspects of construction and operation have been queried. Happily, none of the questions suggest faulty design; most are concerned with minor effects, and the problems that have occurred have been easy to solve. For readers who are at present building the tuner or perhaps thinking of doing so, the various points are discussed below.


Modification to accommodate 05 version of ELC1043 module

As shown in Fig. 17 (part 3), the tuning-voltage spread for the ELC1043/05 is about 1 volt at the lower frequencies. If a module on the low side of this spread is installed, the tuning voltage required to select channel 21 (471.25MHz) would probably be about 0.5 volt. But with the circuit as in Fig. 14 (part 3) the least voltage which can be fed from IC_{2b} to the u.h.f. tuner (point C in Fig. 2 Part 1) is appreciably more than 1 volt.

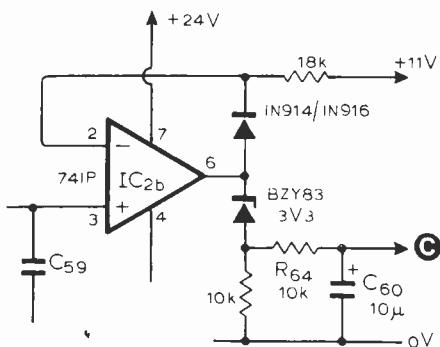To obtain the necessary lower voltage, the IC_{2b} circuit modification suggested below would be suitable. It provides a voltage offset for IC_{2b} output which is maintained at a constant value over a considerable range of ambient temperature.



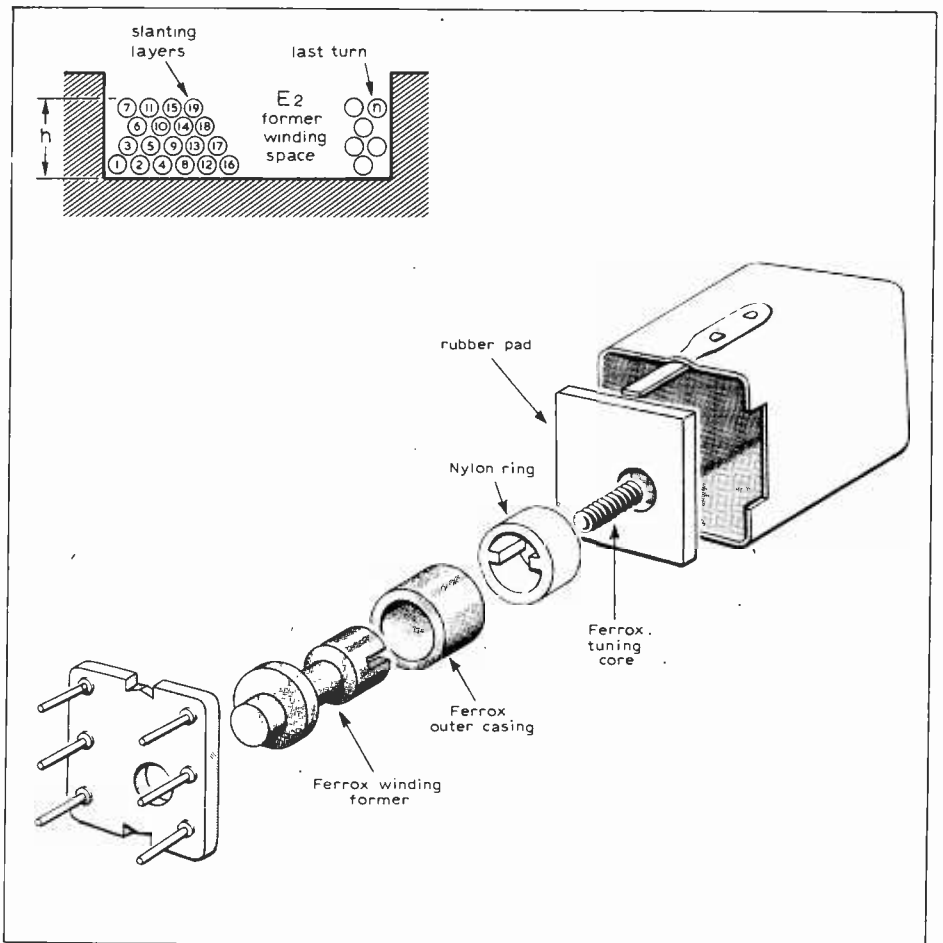In this modified circuit, the 3.3 volt zener diode draws a low bias current through the 18kΩ and 10kΩ resistors from the 11-volt supply rail, and holds point C at a constant 2 volts negative with respect to the IC_{2b} output. Given



this standing bias, the tuning voltage fed to the u.h.f. module can be reduced to zero or even below, and therefore enables selection of channel 21. The silicon junction diode connected between IC_{2b} output (pin 6) and the inverting input (pin 2) provides an overall positive voltage-versus-temperature variation which matches and counteracts the negative-going drift in the zener.

A tuner modified in this way has been tested over an ambient temperature range much greater than would be experienced in practice. The trial showed that voltage tracking between the diodes was quite effective so that the a.f.c. system does not have to adjust for variation in the added bias.

Pile-winding of Neosid type-E2 coils

The components list in part 3 shows that inductors L₈ - L₁₃ are pile-wound on type-E2 formers. Pile winding is an effective way of reducing self-capacitance in coils, particularly those with a relatively large number of turns e.g. L₁₀. It prevents spurious resonances occurring and is generally used to ensure that the larger part of the designed circuit capacitance is obtained from known, discrete components rather than from indeterminate strays in the winding.

The accompanying diagram illustrates how the windings are started and then gradually stacked, as it were, in vertically-slanted layers across the former winding space. The winding height (h) must be judged to suit the

number of turns. The basic aim, of course, is to keep turns with the largest r.f. voltage difference as far apart as possible. With care it is not a difficult construction technique to master; the friction of silk-covered litz wire eases the slant stacking. Failing its use, it may be found that tuning capacitance values as shown in the Fig. 2 circuit will have to be reduced to accommodate the extra winding capacitance which will result; in this event, the specified tuner performance might be difficult to achieve.

As shown in the exploded diagram on p.83, a rubber "cushion" with an offset hole is included in the necessary fitments and is laid between the top of the former and the shielding can. It is a most important item. If the tuning core is screwed fully "home" with the cushion omitted, it could reach, and press against, the former base. When this happens, further rotation of the core lifts the nylon collar clear of the ferrite ring, allowing it to move up and down with the resulting random changes of inductance. It might then be necessary to remove the inductor screening can from the board, dismantle it and re-seat the collar.

The rubber cushion fills the gap between the collar and the can top and so restricts any such movement. To help it do this, remember to push each can firmly down on to the board before soldering the lugs to the earth plane; this action compresses the rubber.

Adjustment of L_{14}/L_{15} coupling capacitor

In Fig. 2, it is shown that the "top-C" coupling for L_{14}/L_{15} is provided on the printed-wiring board by track capacitance. Because of variation in the etching process, some of the boards supplied have a value of capacitance which is too large (too little space between tracks). In this event, the sound i.f. response as exemplified in Fig. 20 of part 4 might be difficult to achieve, and the value would have to be reduced.

Adjustment is easily made by carefully scraping a small amount of copper from the board so as to widen the gap between tracks until the response is correct. As explained in step 9 of the line-up instructions (part 4), satisfactory response obtains when the transfer of energy by the L_{14}/L_{15} circuit is equal about the carrier frequency. For a value of coupling C which is too large, the tendency will be for more energy to be transferred on the high-frequency side of the carrier i.e. the part of the spectrum towards the vision-frequencies.

Pre-set tuning arrangements

The photograph in part 4 shows a push-button assembly connected to a tuner board equipped for sound-only

reception; the full vision and sound version can also be fitted with push-button control. But, in adding this facility, the high-value variable resistors provided in these assemblies for pre-set adjustment are not suitable as direct replacements for the components (R_{91} , R_{94} , R_{97} , R_{100}) specified for the tuning-voltage supply circuit given in Fig. 2.

The difference in resistance value creates two problems, both involving the $22\mu\text{F}$ tantalum capacitors (C_{70} to C_{73}) connected across each pre-set. Referring to Fig. 2, the R_{61}/C_{59} combination at the input to IC_{2b} is needed to reduce a.f. modulation present in the discriminator output feed used for a.f.c. But when channel reselection takes place, the voltage on C_{59} must be appropriately increased or reduced as quickly as possible to complete the re-tuning process. Mainly, voltage change results from the charge transfer between C_{59} and whichever of the $22\mu\text{F}$ tuning-supply reservoir capacitors is connected into circuit at the instant of reselection. The feed of current from the d.c. supply through the relevant pre-set resistor then completes the change. The effective time constant is determined by the pre-set chain resistance, which is $10\text{ k}\Omega$ in the original (published) circuit as compared with $100\text{ k}\Omega$ for the push-button assemblies. Thus with the push-button unit, the time taken to bring the voltage within the range covered by a.f.c. and so re-establish settled tuning conditions is increased by up to 10 times.

The other problem concerns the leakage current taken by tantalum capacitors and the variation of this with temperature. For these capacitors, leakage can double for every 10 deg C change in temperature; for a d.c. source impedance of $2.5\text{ k}\Omega$, as in the original circuit, this represents a voltage change of about 5 mV . Such a voltage applied to the ELC1043 u.h.f. module causes a frequency change of about 0.1 MHz , which is easily corrected by a.f.c. With a d.c. source of $25\text{ k}\Omega$ as presented by the push-button pre-sets, however, the frequency bias resulting from capacitor leakage could be as much as 1 MHz . Although this is still within the a.f.c. range, the offset is unacceptably large because in one direction the degree of control then remaining to counteract all other tuning change effects is severely limited.

In practice, an elegant arrangement is possible: the two pre-set chains – high and low resistance – can be connected in parallel. If this is done, the high-resistance push-button pre-sets are initially put to mid-range and coarse adjustment for the required channels is carried out using the original low-value resistors. Subsequently, fine tuning is completed by means of the high-value controls so that the a.f.c. system is then arranged to operate exactly in the middle of its range for each selected station.

Component-location diagram

The following are errors in the location diagram supplied with the printed wiring board.

- The tantalum capacitor C_{74} across zener diode D_{14} at the base of T_{14} is shown reversed. As indicated in the circuit diagram of Fig. 2, the C_{74} positive terminal should be connected to the transistor base and to the positive end of the parallel zener.
- The positions marked IC_{2a} and IC_{2b} are inverted in the diagram although the component type numbers are correct. The SN72741P, IC_{2b} , is at the top and the SN72748P, IC_{2a} , at the bottom.

Finally, the ELC1043/05 module can be obtained from Manor Supplies, who also offer an alignment service.

T. C. Owen

Many of the long standing advertisers in *Wireless World* will be saddened to hear of the death of T. Charles Owen, who was advertisement manager of the journal from 1925 to 1959. Born in 1894 (the year Heinrich Hertz died), Tommy Owen made his career among the pioneers of radio. He joined Marconi's Wireless Telegraph Company in 1912 as an assistant in the cashier's department, and knew Marconi personally. He handled the cash side of *The Marconigraph*, and when this became *The Wireless World* in 1913, began his long, 47 years' association with the journal.

At the outbreak of the First World War in 1914 he joined the Royal Welch Fusiliers and saw service in France, but was invalided out in 1916. He returned to *Wireless World* in 1917 and subsequently was put in charge of the office, sales and despatch department of Wireless Press Ltd, then at Marconi House in the Strand, London. Iliffe bought this company in 1924 and shortly afterwards Mr Owen was made advertisement manager of *Wireless World*. It was in the early 1920's that he got to know E. K. Cole, J. L. Baird and many other pioneers of radio and television in the U.K. The old 2LO broadcasting station in London was familiar ground to him.


A genial, greatly respected figure, he conducted the advertisement business of *Wireless World* with continuing success until his retirement in 1959, when he was succeeded by G. Benton Rowell. Mr. Owen died in February, aged 81.

G.B.R.

New Products

Function generator

The model 119 voltage-controlled frequency function generator has been added to the range produced by Exact Electronics Ltd. This unit has a frequency range from 0.02Hz to 2.2MHz with sine, square, triangle and variable time symmetry of all waveforms for ramp and pulse operation. A v.c.f. input is provided to allow the generator frequency to be varied either up or down over a total range of 1,000:1. Minus 10V d.c. will increase the frequency by three decades from a minimum multiplier setting, and plus 10V d.c. will decrease it by a similar amount from a maximum multiplier setting. The "high" output delivers 20V pk-pk on open circuit, or 10V pk-pk into 50 ohms whilst the "low" output gives 632mV pk-pk open circuit or 316mV pk-pk into 50 ohms. An amplitude control provides a 30dB attenuator for both high and low

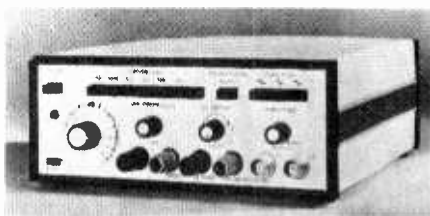

WW 301 for further details

outputs which are available simultaneously. An invert switch allows the pulse and ramp waveforms to be reversed in polarity and a d.c. offset control gives up to $\pm 10V$ adjustment. A t.t.l.-compatible pulse output is provided in the front panel. Dana Electronics Ltd, Collingdon Street, Luton, Beds.

WW 301 for further details


Infrared oven

For reflow soldering, drying thick-film paste, curing photo-resists and sprays and many other small-scale heating, drying, soldering and curing applications, a new infrared oven has been introduced to this country by Dage Intersem Ltd. Called the TR-91, it is manufactured by Glo-Quartz Ovens Inc, California and is suitable for bench-top use. It incorporates a variable speed (0-4ft per minute) stainless steel conveyor belt and may be integrated into existing production lines. Dage Intersen Ltd, Haywood House, Pinner, Middlesex.

WW 302 for further details

Inverter for TV sets

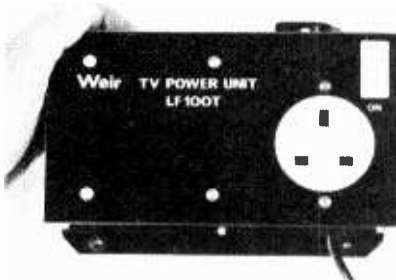Inverter LF100T has been designed to operate mains-driven TV sets from a 12-volt car battery or similar d.c. source. The inverter delivers a rectangular output waveform with a form factor suited to models relying on r.m.s. or peak voltage values. The maximum power output is 100W at a nominal 240V a.c. Input must be within 11 to 16V d.c. Full protection against output short



WW 303 for further details

circuits or overloads is incorporated and the unit is fuse protected against incorrect input polarity connection. Further protection is provided by an electronic trip circuit which shuts down the power unit should the battery voltage fall below 11V, thereby preventing undue battery drain. The unit also trips should over heating occur. Dimensions are 180 x 130 x 90mm, it is mechanically robust and will withstand electrical surges of up to 20V for 80ms or spikes up to $\pm 300V$ for 15 μ s. Weir Instrumentation Ltd, Durban Road, Bognor Regis, Sussex.


WW 303 for further details

Spark tester for defects

Designed for the detection of flaws, defects or porosity in non-conductive materials, the Goodburn model GBP20 portable h.f. spark tester incorporates a replaceable plug-in coil. The tester has a variable output control which adjusts the spark length to suit different applications, combining optimum frequency with safety in use. The unit will test such materials as rubber, plastics, ebonite and bituminous coatings up to 25mm thick. Voltage input can be set to 100/125V or 220/250V at 30W power consumption. Output frequency is 200kHz and maximum output voltage 55kV. The generator is housed in a compact pistol-shaped moulded polythene case. In testing, the surface of an object is systematically checked by passing over it with the correct probe. Voids and defects will be recognized by the passage of a bright spark accom-



WW 302 for further details

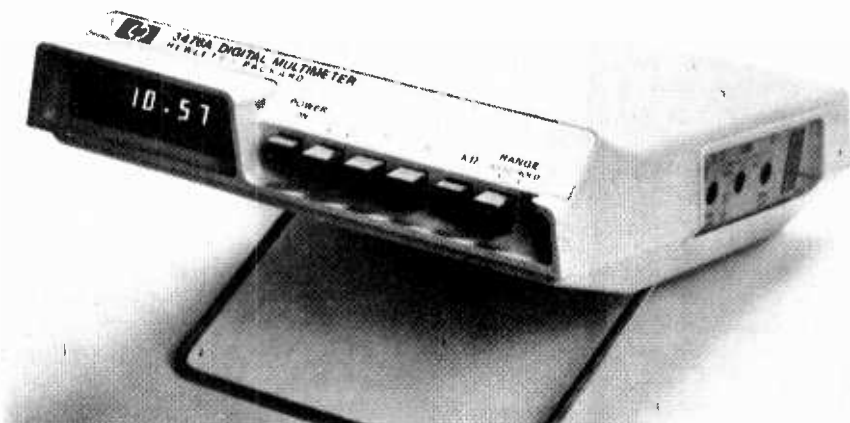

WW 305 for further details



WW 304 for further details

panied by an audible hissing noise. Goodburn, The Welding Centre, Arundel Road, Trading Estate, Uxbridge, Middlesex UB8 2SE.

WW 304 for further details

Digital multimeter

A new 3½-digit, five function, auto-ranging digital multimeter from Hewlett-Packard measures voltages from $\pm 0.1\text{mV}$ to 1kV d.c. and from 0.3mV to 700V r.m.s. a.c. Resistance is measured from $1\text{m}\Omega$ to $1\text{M}\Omega$ whilst current can be measured from 0.1mA to 1.1A d.c. and 0.3mA to 1.1A a.c. Autozero, autopolarity and autoranging are built in. Typical accuracy for direct voltage measurements is 0.5% and direct current accuracy is 1%. On alternating voltage ranges, frequency is specified to 10kHz, while a.c. measurement is to 5kHz. Accuracy of resistance measurements is within 0.6% on the three highest ranges and 0.4% on the two lower ranges. Open circuit voltage is less than 4V. Input resistance on all voltage ranges is $10\text{M}\Omega$ with input capacitance of less than 30pF . The model 3476 is protected to 1100 volts peak on all ranges. A range hold feature is included that allows the instrument to be locked to any desired range. Hewlett Packard Ltd, King Street Lane, Winnersh, Wokingham, Berkshire RG11 5AR.

WW 305 for further details

Integrator

The D-block integrator from Lee-Dickens Ltd operates by providing a pulse rate which is linearly proportional to an input amplitude. The pulses are then amplified to drive a separate electro-magnetic counter. The unit accepts signals with a minimum span of 100mV and input currents of 0-10 and 4-20mA. The output pulse is 24V d.c., 40ms wide and the output, at minimum input, may be up to any count rate between 120 and 12,000 counts per hour. The module will operate from either 100-120V or 210-250V and the power requirement is approximately 2VA. Each instrument is supplied factory calibrated from Lee-Dickens Ltd, Desborough, Kettering, Northants.

WW 306 for further details

Instrument case

Boss Industrial Mouldings has recently introduced the BIM300 instrument case. The unit measures $250 \times 167.5 \times 68.5\text{mm}$ and has a volume of 2000cu.cm . The case has two similar covers screwed onto an 18 s.w.g. chassis which is pre-punched to accept an IEC mains socket. Internal upper and lower brackets are also provided for mounting printed circuits boards. The top and bottom covers are constructed from s.w.g. aluminium which is stove ena-

melled in either red, grey or orange. The cases are priced at around £12.50 in one off quantities from Boss Industrial Mouldings Ltd, Higgs Industrial Estate, 2 Herne Hill Road, London SE25 0AU.

WW 307 for further details

Automatic millivoltmeter

An analogue, alternating millivoltmeter from the NF Circuit Design Block Co., the Model M-176, will change ranges automatically from 1mV to 300V full-scale. A hold mode is provided and with this in use the ranges can be changed manually. Range-change switching points are at 25% f.s.d. in the downward direction and slightly over 100% upwards, although provision is made for variations. A row of l.e.d.s indicates the range in use. A sensitivity control is fitted for convenience in making ratio measurements. The stated error is $\pm 3\%$ or less; frequency/indication response is within 0.3dB from 20Hz to 500kHz and 1dB from 10Hz to 1MHz and a 1V output is taken to front panel sockets. Lyons Instruments, Hoddesdon, Herts.

WW 308 for further details

Flexible jumperlinks


The latest ribbon cabling product to be offered by Tekdata Ltd is CK Jumperlinks. These are sections of flat interconnections for short-distance connection of p.c.bs and connectors. They are custom made in rolls ready to be cut by the user, and consist of tinned copper wires or self-fluxing enamel wires held at the required pitch by woven supporting strips. Any wire pitch or length up to 8cm can be ordered in quantity and coloured bands at stipulated separations can indicate the cutting points. The maximum wire gauge is 30 s.w.g. After a section has been cut from the strip of sections and the ends trimmed, it is ready for termination at lay-on joints or poke-through holes and it may be reflow soldered. Tekdata Ltd, Westport Lake, Canal Lane, Tunstall, Stoke on Trent, Staffs.

WW 309 for further details


Logic-state indicator

The Ryley Logic Clip is a dual-in-line instrument which provides a simultaneous display of the logic state at each pin of an i.c. Indication is by means of l.e.d.s which have a numerical-slide for pin number identification. The clip has high impedance inputs each with a 1.5V threshold for use on t.t.l., d.t.l. and c.m.o.s. devices operating at 5V. Power for the logic clip is derived automatically from the i.c. under test. The device costs £25 + v.a.t. and is available from Electroplan Ltd, P.O. Box 19, Orchard Rd, Royston, Herts. SG8 5HH.


WW 310 for further details

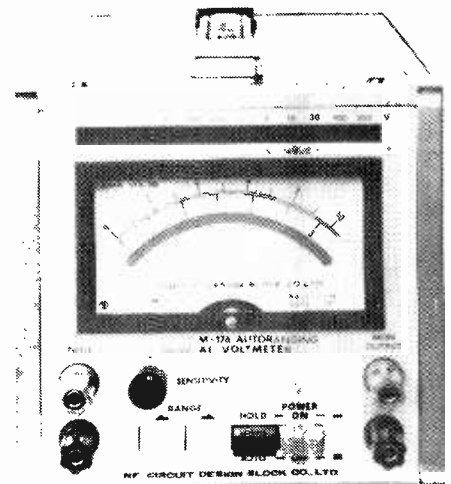


WW 308 for further details

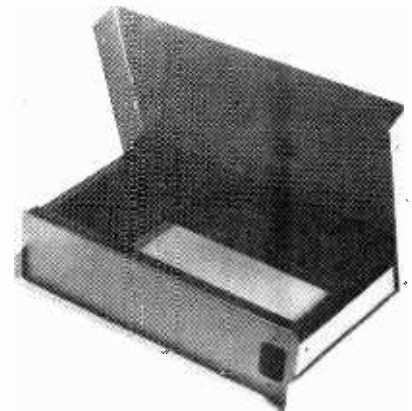

WW 307 for further details

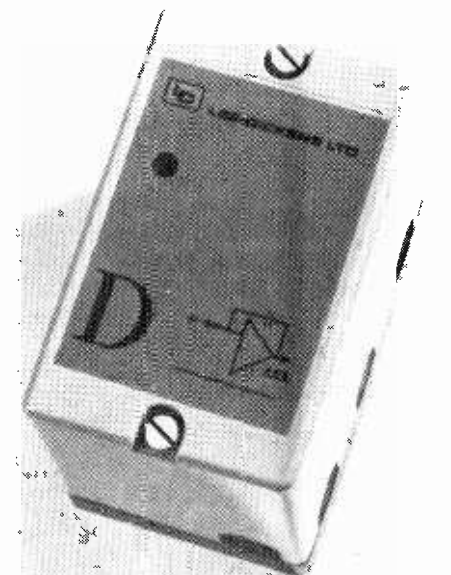

WW 306 for further details

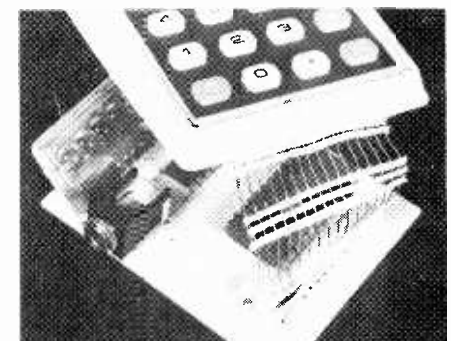

WW 309 for further details

Solid State Devices

Names of suppliers of devices in this section are given in abbreviation after each entry and in full at the end of the section.

Microcomputer kit

A microcomputer kit called the SDK-80 incorporates all of the l.s.i. integrated circuits, crystal, sockets, printed circuit board and auxiliary components necessary to build an 8-bit n.m.o.s. microcomputer system. The kit uses the 8080A c.p.u., the 8228 system controller and the 8224 clock generator with 256 bytes of read/write memory, 2k bytes of programmable read only memory, a programmable serial communications input/output port and 24 other programmable input/output lines. The kit is also supplied with a detailed set of instructions together with system and software manuals.

Intel

WW 311 for further details

Microprocessor

An eight-bit microprocessor set developed by GIM of Glenrothes, the series 8000 is available as a set of five integrated circuits, as a microcomputer or as a set of plug-in circuit boards. Software support is available. The cost (£17.50 for the c.p.u. - one-off) makes it practicable to use the set for relatively mundane work, as in weighing machines, typewriters and cash registers. The use of the GIM p-channel nitride process used in equipment which is approved to Post Office D4000 means that it can be used in a telecommunications role.

GIM

WW 312 for further details

Divide-by-four

A 1GHz divide-by-four circuit from Motorola, the MC1699 requires only 160mV pk-pk input from 50MHz to 1GHz. Below 50MHz, the device is best triggered by 1 or 2ns rise time pulses, such as those from emitter-coupled logic. Clock enable and reset inputs are provided and the circuit needs +2V and -5V supplies. The package is currently a flat ceramic type, but the d.i.l. ceramic variety is soon to be used in addition.

Motorola

WW 313 for further details

Watch calendar circuit

A 12-hour watch circuit in the c.m.o.s. family of devices is announced by RCA. The 32-terminal, leadless package is a watch/calendar unit, designed for use with external display drives and intended for a 32.768kHz drive. The TA6342 will display hours and minutes, with seconds or month, a.m. or p.m. or date. The date display is compensated for 30 and 31 day months, but not 28-day Februaries so that annual re-setting is

needed. By the provision of separate photocell, R and C the display can be made to vary in brightness to accommodate ambient lighting changes. Supply voltage is between 2.2V and 3.2V.

RCA

WW 314 for further details

Microwave i.c. amplifiers

The Avantek range of thin film microwave amplifiers is now available in the UK. The devices are designated the UTO-500 series and are housed in the TO-8 packages suitable for operation in microstrip circuits. There are ten devices ranging in gain from 6 to 27dB and output powers from -2 to +17dBm. Maximum noise figures range from 2.5 to 11dB. All of the amplifiers have a bandwidth of 5 to 500MHz flat within ± 1 dB. Inputs and outputs have a 50 Ω impedance with a v.s.w.r. of less than 2.

Walmore

WW 315 for further details

Precision voltage source

The ZN423T provides a 1.26V source and is suitable for use in stabilised power supplies d-a-d converters and instruments. The device, which is encapsulated in a two-pin TO18 package, offers a slope impedance of 5.5 Ω , a temperature coefficient of 100 p.p.m. per deg C, and an operating temperature range from 0 to +70°C. The 100+ price is £0.70 each.

Ferranti

WW 316 for further details

Precision op-amp

The AD510 is a laser-trimmed op-amp offering a maximum offset voltage of 25 μ V, a 10nA bias current, 1 μ V pk-pk input noise for a 0.01 to 10Hz bandwidth and an open-loop gain of over 1×10^4 . The device is available for operation between 0 and +70°C or in the military temperature range of -55 to +125°C. Both types are packaged in a TO-99 can.

Analog Devices

WW 317 for further details

Transistor for s.m.p.s.

Mullard have recently extended their range of high-voltage, high-speed switching transistors with the addition of the BUX86. The device is an n-p-n type with a power rating of 20W, a V_{ces} of 800V and a V_{ceo} of 400V. Applications include switched-mode power supplies, inverters and converters.

Mullard

WW 318 for further details

Micro circuit oscillator

The latest addition to the range of standard microcircuit products produced by Redac Software Ltd is the TF105 audio oscillator, a hybrid thick-film oscillator which can be used for either analogue or digital clock application. The unit is a ± 10 p.p.m./deg C sine wave oscillator, the frequency of which can be set by the user in the range 100Hz to 100kHz. It will operate

between 5 and 30V with split or single supplies and over the temperature range -20 to +85°C with a high amplitude stability. The output is d.c. coupled with a low offset voltage. With the addition of a dual ganged potentiometer a wide range RC oscillator can be constructed. Dimensions of the unit are 2.5 x 3.5 x 0.8cm.

Racal.

WW 319 for further details

Low-pass filters

A range of low-pass filters in standard 16-pin d.i.l. packages is available. The filters, manufactured by the American E.S.C. Electronics Corporation provide a cut-off frequency range from 200kHz to 1MHz and an impedance range from 75 Ω to 1k Ω . Insertion loss is less than 0.5dB. The operating temperature range is -55°C to +125°C and the device conforms to applicable portions of MIL-F-18327C.

G.E. Electronics

WW 320 for further details

Telephone relay drivers

Two new i.c.s from National Semiconductor, DS3686 and DS3687 will drive 48V telephone relays without the need for external circuit protection. Both devices convert standard bipolar and c.m.o.s. logic signals to the high voltage, high current levels required by telephone relays. The DS3686 is a positive-voltage driver; DS3687 a negative-voltage driver. Outputs are rated at 65V and the devices will sink 300mA per channel.

National

WW 321 for further details

Suppliers

RCA Ltd, Sunbury-on-Thames, Middx.
Mullard Ltd, Mullard House, Torrington Place, London, WC1.

Walmore Electronics Ltd, 11 Betterton Street, London WC2H 9BS.

Ferranti Ltd, Gem Mill, Chadderton, Oldham, Lancashire.

Analog Devices Ltd, Central Ave, East Molesey, Surrey.

Intel Corporation (UK) Ltd, Broadfield House, 4 Between Towns Road, Cowley, Oxford OX4 3NB.

National Semiconductor UK Ltd, 19 Goldington Road, Bedford MK403LF.

Motorola Ltd, Semiconductor Products Division, York House, Empire Way, Wembley, Middx HA9 OPR.

General Instrument Microelectronics Ltd, 57 Mortimer Street, London W1N.

G. E. Electronics (London) Ltd, Eardley House, 182/4 Campden Hill Road, Kensington, London W8 7AS.

Racal-Redac Ltd, Newtown, Tewkesbury, Gloucestershire, GL20 8HE.

Advanced Microdevices have informed us that they are now at Room 322, Ebury Gate, 23 Lower Belgrave St, London SW1W 0NS.

Real and Imaginary

by "Vector"

FIFTY YEARS
OF THE BEAM

Holiday-makers in Cornwall may have discovered the charming little Poldhu Cove, a few miles west of Mullion. Relatively few visitors, however, make the short pilgrimage up a cliff path and round the headland to a spot which, if it had been in the United States, would surely have become a shrine long before this. For here was the cradle of long-distance radio communications.

But this is England (if the Cornish Nationalists will pardon the expression) so, apart from the magnificent views, there isn't much else to see. Some traces of building foundations, a granite obelisk and that's all, except for a plaque recording the bridging of the Atlantic by wireless signals in 1901 and the evolution of the beam system half a century ago. Of the mighty Poldhu station itself, scarcely a vestige remains.

Wireless telegraphy generated centimetric waves which were directed — well, more or less — by forms of parabolic reflector; then Marconi discovered that an elevated antenna wire gave better ranges than the Hertzian dipole mounted on the transmitting or receiving instrument and this ushered in a phase of omnidirectional working in which the reflector sank into oblivion.

Gradually the operating ranges increased to line-of-sight and somewhat beyond and it was found that the longer the wavelength that was used, the further the signals reached, until at length ranges were being recorded that were utterly inconsistent with theory.

Voltaire's comment that "If God did not exist it would be necessary to invent him" fitted the situation perfectly, except that in this case it was the ionosphere that had to be invented. It was a concept which was still being hotly debated twenty years later, until its existence was proved by the work of Appleton, Breit and Tuve, T. L. Eckersley *et al* in the 1920s.

Ionosphere or no ionosphere, the practical workers in the field evolved the golden rule that long distances could be achieved only by using long wavelengths and high power. It worked. By the 1920s wavelengths of the order of thousands of metres were the norm for long-distance working and the use of reflectors was in any case physically

impracticable because of the huge sizes which would be involved. But by this time the reflector approach had long since been forgotten and plans were under way for a chain of longwave high-power stations to link the Empire.

In 1916, Marconi, who had largely been responsible for the trend toward long wavelengths, reverted to experiments on 2 metres but only for short range working. His personal assistant on this occasion, Charles Samuel Franklin, having an antenna of manageable size to work with, added a reflector and thereby concentrated the signal into a beam with consequent economies in power and an increase of privacy (the work was for the Italian Navy). Subsequently Franklin continued his short-wave experiments and in the immediate post-war period built a 15-metre link between Birmingham and Hendon which also used reflectors. This was also highly successful.

Every now and then reports would come in of the signals being received over long distances. There was also the matter of the amateurs who, confined to the then despised and "useless" bands below 200 metres, were occasionally reporting that their signals had been picked up in the USA and even further afield. Franklin pondered over these circumstances; true, reception was erratic in the extreme but that it occurred at all was remarkable. He persuaded Marconi to let him investigate and in due course installed himself at the existing long-wave station at Poldhu. Here, working at astonishing speed, he built an 8-valve transmitter to operate at 97 metres, and a half-wave antenna with a reflector that could be switched in and out at will.

Aboard Marconi's yacht *Elettra* special receiving gear had been fitted and on April 11, 1923, the ship set out from Falmouth heading for Madeira and, eventually, St. Vincent in the Cape Verde Islands, with Marconi aboard. At first, it seemed, the experiment was a failure, for the Poldhu signals attenuated rapidly then disappeared altogether. This was the now familiar (but then unknown) "skip distance effect". Fortunately the voyage continued and, after some hundreds of miles, Marconi was able to record good reception.

The results were spectacular but left room for improvement. As it turned out later, 97 metres was a bad choice for daylight reception, while the reflector wasn't providing the anticipated increase in gain. But more than enough had been done to show the enormous potential in short-wave long-haul radio communication.

With all speed Franklin redesigned the transmitter for 92 metres working at a power of 17kW and at the same time improved the reflector, although this wasn't ready in time for the next series of tests. Even so, on May 30, 1924, Marconi was able to telephone direct to Sydney from Poldhu. Subsequent tests on various wavelengths between 32 and

92 metres showed that the daylight range increased as the wavelength decreased; on 32 metres, reception at Sydney was possible for 23½ out of the 24 hours. All the data from these tests were rigorously examined and formed the foundation of our present knowledge of the ionosphere.

The story of how the long-projected plan for a long-wave, high power chain of stations throughout the British Empire was abandoned in favour of the beam system is well-known. Perhaps less well-known is the magnitude of the gamble which Marconi took in offering the stations to the British Post Office and the Empire Governments. At the time of the contract, no fully engineered version of the beam transmitter existed; serious teething troubles were being experienced with the transmitting valves; neither the antennas nor the reflectors were fully engineered, while the problem of how to transfer the energy from the transmitter to the antenna without undue losses had still to be solved. To cap it all, Marconi had no means of knowing whether the long ranges obtained in the tests would continue or not. For all he knew, transient freak conditions might have been responsible — circumstances which might never be repeated. Although the contract was wholly conditional upon successful performance, he took the risk.

His decision was a measure of his faith in Franklin. And Franklin performed wonders. To overcome the valve problem he personally designed the first "CAT" (Cooled Anode Transmitter) valves in which the copper anode was also the envelope. Next, he re-engineered the transmitters, antennas and reflectors (and, with no precedents to guide him, the antennas themselves were no mean problem, consisting as they did of a large number of elements, all of which had to be fed in a common phase relationship).

Then came the matter of an efficient power transfer. Franklin solved this by the invention of the concentric feeder, or coaxial cable. And he did the whole lot in a matter of months — he had to, because construction of some of the stations had already begun! Let's be honest with ourselves for a moment. How many electronics engineers of today have the capability of tackling an entirely new system and designing and engineering its transmitters, valves and antennas from scratch? And Franklin's end-products were no lashups, either. Forty years later one or two of his original transmitters were still in regular traffic service and in some part of the world may still be so — and that's engineering by any standards.

On October 18, 1926 the first beam circuit came officially into service, linking Britain and Canada.

Fifty years ago, Poldhu station has since disappeared almost without trace and I suspect that C. S. Franklin is all but forgotten.

More than just a catalogue!

PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .


Really good value for money at just 40p.



132 pages!

The 3600 SYNTHESISER

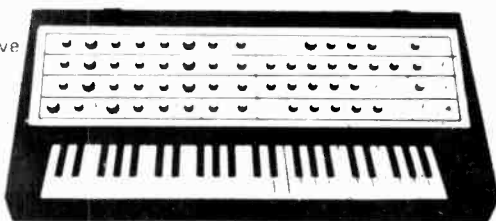
The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.



S.A.E. please for price list


The 4600 SYNTHESISER

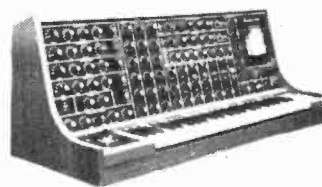We stock all the parts for this brilliantly designed synthesiser, including all the PCBs, metalwork and a drilled and printed front panel, giving a superb professional finish.



Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details available now in our booklet price £1.50, or S.A.E. please for specification.

GRAPHIC EQUALIZER

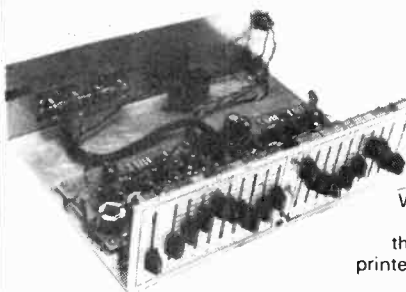

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCBs. Complete reprint of article — price 15p.

ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.



Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, price 35p. (Pre-publication price 15p).

NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p


NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff on Sea, Essex. Please address all mail to

MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3 Rayleigh Essex SS6 8LR

I enclose Cheque/P.O. value _____ ww
 For _____ copy/copies of your Catalogue
 Name _____
 Address _____

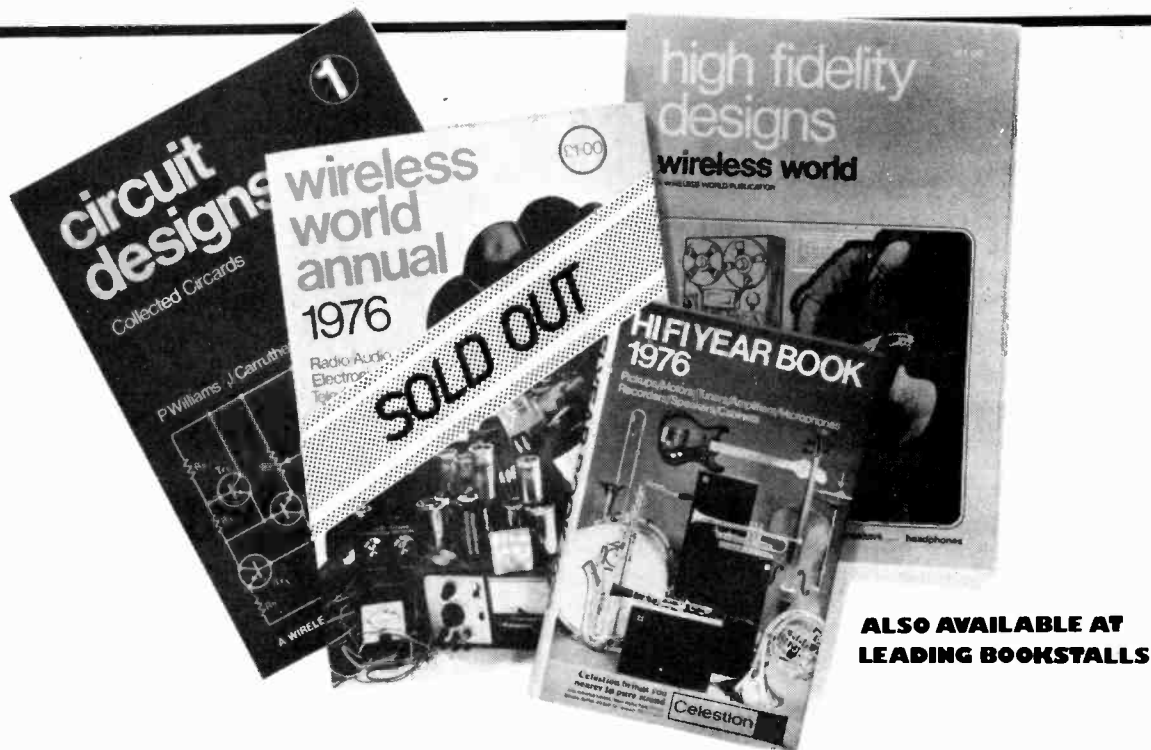MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR



The big four from Wireless World

Wireless World Annual 1976

1 The world of electronics, television, radio/audio is on parade in the second great Wireless World annual. Constructional articles include making a photographic timer. Surveys cover video, magnetic tape compatibility, electronic ignition and radio astronomy in schools.

Hi-Fi Year Book 1976

2 This is the book that tells you everything you need to know about the hi-fi equipment on the market. Separate illustrated sections cover every major category, together giving prices and specifications of over 2,000 products.

High Fidelity Designs

3 In response to demand for reprints of Wireless World constructional projects, we have collected fifteen of the most popular designs in one book.

Circuit Designs (1)

4 A compilation of the first ten sets of Wireless World Circards and including additional circuits. Each set in this hard back book is preceded by an explanatory introduction.

Order coupon
To General Sales Dept. Room 11,
Dorset House, Stamford St., SE1 9LU

Please send me books as indicated below (state number of copies of each)

Hi-Fi Yearbook 1976 " £2.35 incl. _____
High Fidelity Designs " £1.35 incl. _____
Circuit Designs (1) " £10.40 incl. _____

I enclose remittance value £ _____
(cheques payable to IPC Business Press Ltd)


Name _____

Address _____

Regd. in England No. 677128 Regd. Office: Dorset House, Stamford St.
SE1 9LU

HART ELECTRONICS

Audio Kit Specialists since 1961

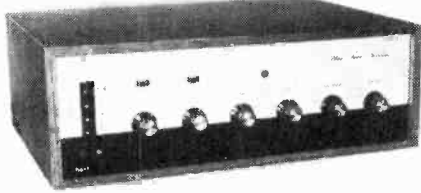

STEREO BAILEY 30 WATT TUNER AMP.

This complete tuner/amp unit is of the very highest quality and is the amalgam of our Compact FM Tuner, Bailey 30watt power amps and the Bailey/Burrows/Quilter pre amp. The wooden sleeve is available in either teak or sapele finish to blend with existing equipment or furnishings.

The combination of our excellently designed printed circuits and the high quality components used makes this unit unequalled on the kit market and approached in quality of performance and durability by few made up tuner amps. Full details are in our free lists.

STUART TAPE CIRCUITS. Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre amp. Total cost varies but around £35 is all you need. We can offer tape heads as well if you want new ones.

All above kits have fibreglass PCB's. Prices exclude VAT but P&P is included.

FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in. x 4 in. S.A.E.

REPRINTS Post free, no VAT.

Bailey 30W 18p.

STUART TAPE RECORDER. All 3 articles under one cover 30p.

BAILEY/BURROWS/QUILTER Preamp circuits, layouts and assembly notes 15p.

All prices exclude VAT.

Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday


SINCLAIR CALCULATORS★

Cambridge £7.95. Cam Mem £11.20. Scientific £8.95. Oxford 100 £6.95. Oxford 200 £13.45. Oxford 300 £16.95. Programmable Scientific £25.95. Mains adaptor for Programmable and Oxford £3.19. Mains adaptor for Cambridge and Scientific £3.15.

S-DECS AND T-DECS★

Special Offer: 25p or 50p off orders accompanied by 25p or 50p PB Electronics adverts.

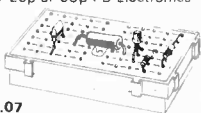
S-DeC £2.24
T-DeC A £4.05
u-DeC A £4.45
u-DeC B £7.85



16 dit. plain £1.07
With socket £2.21
10 T05 plain 99p. With socket £1.95.
SST1 60p. SSUI 60p. SSNI 80p.

BATTERY ELIMINATORS

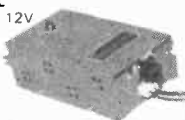6-WAY SPECIAL
3. 4½. 6. 7½. 9. 12V at 500mA with unique 4-way multi-jack connector and free matching socket £5.80.



6-WAY DOUBLE RADIO MODEL
Similar to above, but with press-stud battery connectors. 3+3. 4½+4½. 6+6. 7½+7½. 9+9. 12+12V at 250mA. Can also be used to give 15. 18 and 24V single. £6.80.

3-WAY MODEL★
Switched output of 6. 7½ and 9V at 250mA with 4-way multi-jack connector and free matching socket £2.95.

RADIO MODELS
50mA with press-stud battery connectors for radios, etc. 6V £2.95. 9V £2.95. 4½+4½V £4.45. 6+6V £4.45. 9+9V £4.45.

CASSETTE MAINS UNITS
7½V output to run cassette tape recorders from the mains. Complete with 5 pin DIN plug £3.45.

CAR CONVERTERS
Input 12V DC. Output 6/7½/9V DC 1A regulated. £3.95★.

SINCLAIR BLACK

WATCH★
Fully assembled with black strap £20.95. Braçolet £2.



DIGITAL CLOCK KIT★

24 Hr. display. Includes pcb, mains power supply, attractive case, 0.5in jumbo green display, clock chip and all other parts. Displays hours and minutes separated by pulsating colon. Kit £12.50. Built £13.50.

SINCLAIR IC20

IC20 10W+10W stereo amp kit with printed circuit £6.95.
PS20 Power supply for above £4.95.
VP20 Volume, tone control and preamp kit £7.95.
SP20 10W 4 Ohm speaker £2.95. Send sae for free leaflet.

SINCLAIR PROJECT 80

Q16 £10.15. FM tuner £13.25. P25 £3.95. P26 £8.70. P28 £8.20. Trans for P28 £5.40. Z40 £5.75. Stereo 80 £10.95. Project 805 £20.95. Project 805Q £18.95.

JC12 AMPLIFIER

6W IC audio amp with free data and printed circuit £1.95★



DELUXE KIT FOR JC12

Includes extra parts for the pcb and volume and tone controls. Mono £2.29. Stereo £4.95.

JC12 POWER KIT

Supplies 25V 1 Amp. £2.95

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono £1.55. Stereo £3.0. Type 2 for ceramic or crystal pickups. Mono 85p. Stereo £1.70.

LOUDSPEAKERS

FOR JC12 5in x 5in 8 Ohms 5W £2.50.

Post 20p on orders under £2, otherwise free. Prices include VAT. (Overseas customers deduct 7% on items marked ★, otherwise 20%). Official orders from schools, etc. welcome.

SWANLEY ELECTRONICS
DEPT. WW, PO BOX 68, SWANLEY, KENT BR8 8TQ

Look AT THESE PRICES AND BUY QUALITY

VALVES		Price		Price	
Type	Price (p)	Type	Each (p)	Type	Each (p)
DY87	30 0	BC125B	15	R2008B	£2 00
DY802	30 0	BC132	25	R2010B	£2 00
ECC82	28 0	BC135	15	RCA16334	80
EF80	29 5	BC137	19	RCA16335	80
EF183	34 5	BC138	26	TIP31A	57
EF184	34 5	BC142	23	TIP32A	67
EH90	35 5	BC143	25	TIP41A	67
PC900	24 5	BC147	11	TIP42A	80
PCC89	40 0	BC147A	11	2N3055	55
PCC189	41 0	BC148	10	DIODES	
PCF80	31 5	BC149	10	BA115	7
PCF86	39 0	BC153	15	BA145	14
PCF801	42 0	BC154	15	BA148	19
PCF802	40 0	BC157	14	BA154/201	11
PCL82	39 0	BC158	10	BY126	11
PCL84	39 0	BC159	11	BY127	12
PCL85	44 5	BC173	18	BY199	27
PCL86	41 0	BC178B	20	BY206	21
PFL200	59 5	BC182L	12	BY238	25
PL36	55 5	BC183L	12	OA90	6
PL84	25 0	BC187	25	QA202	7 5
PL504	64 5	BC214L	15	IN60/OA91	5
PL508	67 0	BC328	28	IN914	6
PL519	£1 20	BC337	19	IN4002	5
PY88	35 5	BD124	75	INTEGRATED CIRCUITS	
PY800	33 0	BD131	45	Type	Price
PY500A	85 0	BD132	39	Each (p)	
		BD160	£1 39	E1TR6016	£2 00
		BD235	49	MC1351P	70
		BD237	52	SN76003N	£2 35
		BDX32	£2 40	SN76013N	£1 50
		BF115	20	SN76013ND	£1 50
		BF160	15	SN76023N	£1 50
		BF167	20	SN76023ND	£1 45
		BF173	20	SN76033N	£2 35
		BF178	35	SN76227N	£1 45
		BF179	40	SN76532N	£1 45
		BF180	31	SN76660N	58
		BF181	32	SN76666N	87
		BF184	25	TAA550	49
		BF185	25	TAA700	£2 95
		BF194	9	TBA120AS	£1 00
		BF195	8	TBA120SQ	£1 00
		BF196	10	TBA480Q	£1 40
		BF197	12	TBA520Q	£2 35
		BF198	23	TBA530Q	£1 75
		BF200	25	TBA540Q	£1 75
		BF218	30	TBA550Q	£2 90
		BF224	23	TBA560CQ	£2 40
		BF258	34	TBA800	£1 50
		BF336	28	TBA920Q	£2 90
		BF337	35	TBA99CQ	£2 90
		BF355	54	TCA270Q	£2 90
		BFX86	28	EHT MULTIPLIERS MONOCHROME (BRC) Price Each	
		BFY50	19	2HD 950MK1	960
		BFY52	20	2TQ 950MK2	1400
		BSY52	35		£1 85
		BT106	£1 20	2DAK 1500	
		BU105/02	£1 95	(17" & 19")	£1 85
		BU108	£2 10	2TAK 1500	
		BU208	£2 95	(23" & 24")	£2 00
		E1222	30		
		MJE340	45		
		OC71	15		
		OC72	16		



PRICE QUALITY SERVICE



COMBINED PRECISION COMPONENTS (PRESTON) LTD

Department W.
194-200 North Rd.
Preston PR1 1YP
Tel: 55034
Telex: 677122.

EHT MULTIPLIERS COLOUR

Type	Price Each
11TAQ ITT CVC 1, 2 & 3	£4 50
11N GEC Schell	£4 50
11TAZ GEC 2110	£4 85
11TAM Philips G8	£4 50
11TBD Philips 550	£4 50
3TCW Pye 691/693	£3 50
11H Decca 30 Series	£4 50
11TAQ Decca Bradford	£4 50
3TCU Thorn 3000/3500	£5 00
11HAA Thorn 8000	£1 90
11HAB Thorn 8500	£4 25

New TOSHIBA TUBES

with 12 months in service guarantee

19" A49-191X equivalent	
A49-192 and A49-120X	£48 95
20" 510D JB22 equivalent	
A51-110X	£50 75
22" A56/120X	£54 25

PRICES SUBJECT TO 25% V.A.T.


All goods subject to settlement discount of 5% 7 days and 2% monthly. No postage charges or minimum order values. Write or phone for full details now.

For the musician who wants the best in recording.

10XD — Our Studio Class, 15 IPS, Cross Field, Dolby B Recorder. At 15 IPS, the advantage of Tandberg Cross Field recording and the Dolby B Noise Reduction System must be heard to be believed. You don't have to be a perfectionist to appreciate this quality, but it may make you into one.

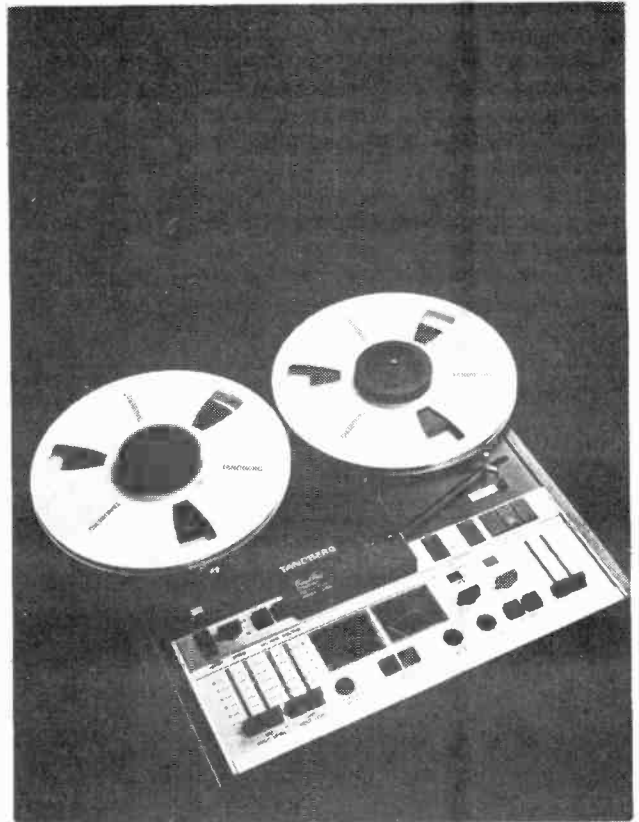1. 10½" spool capacity, 3 speeds and remote control.
2. A, B Monitoring with easy editing facility.
3. Sound on Sound, add-a-track, echo, mixing, etc.
4. Peak level record/playback meters
5. Balanced microphone inputs.
6. Superb logic control circuits.
7. Electronic servo controlled speed regulation.


See the 10XD and other Tandberg recording equipment at REW's new professional department.




REW Audio Visual Co., 146 Charing Cross Road, London WC2. Tel. 01 240 3064/5

WW — 098 FOR FURTHER DETAILS

WEST HYDE COMPONENTS

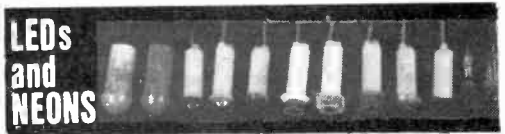

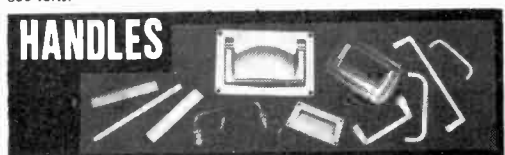LEDs and NEONS
Above: Red LED, R Threaded chrome LED, Q, S, PCG, PCE, PCH, PCI, PCF, PCC, PCB, PCA, PPA, PPB. LEDs in red, green on own or in threaded chromium housing, 5.5mm d. hole. S neon 5.5mm Ø. Q neon 7mm d. Neons in PC housings 9.5mm d. 3 cap colours, dome, top-hat, square. PP 12.5mm d. 6" leads std., 30" extra cost; neon only, 110, 220 or 500 volts.



HANDLES
On L., extruded PVC and anod. al. Centre: heavy duty carrying handles. On R. anod. & chromium. Wide range (47 different) in PVC, nylon, chromium, anodised, flush, extruded and carrying.



TEST METERS
Pop-up 20,000 ohms/v., LT801, 17 ranges. Pocket LT101 low-cost, 12 ranges, 1,000 ohms/v. TS141, 66 ranges, 20,000 ohms/v, incl. nylon case, 115mm scale, 5amps AC & DC, 2,500 v. AC, well damped, many accessories.



BRADRAD CONECUT ADEL
L. to R. 2½" Bradrad, drills and deburrs. ¼"/1½" 11 diameters Bradrad. 4 Conecuts, ¼"/2". Adel nibbling tool, square or round holes. 11mm d. entry. Underneath: 2 reamers, ¼"/1". To make round holes with no vibration.

THE INSTRUMENT

WEST HYDE COMPONENTS

Neon prices include P. & P.

LEDs	1	10	50	100	500	1000
Red (LED 32)	21p	19p	17p	16p	15p	14p
Green (LED 35)	33p	30p	26p	25p	23p	21p
Red (Thread) (LED 12)	55p	50p	44p	41p	39p	36p
Green ... (LED 15)	65p	59p	52p	49p	46p	42p

NEONS, 110 or 230V	1	10	100	500	1000	10000
PCA/I & PP. 6"	27.5p	19.3p	18.2p	17.1p	16p	14.9p
PCA/I & PP. 30"	27.5p	21.5p	20.4p	19.3p	18.2p	17.1p
Q	38.5p	31.9p	29.7p	28.6p	27.5p	25.3p
S	33p	25.3p	23.1p	22p	20.9p	19.8p
N per 10 (neon only)	75p	66p	55p	48.4p	45.1p	41.8p

PRICES — 1 off inc. P & P but not VAT. Discounts for quantities. Minimum order £2.00.

HANDLES		KNOBs	
Chromium from	54p	See Catalogue for Prices	
Extruded from	107p		
Nylon from	55p	PANAVICE	
PVC from	41p	(Photo. L to R)	
Pivoting	132p	301. base plus vice	£13.00
Flush precision	£3.34	306. 1.65mm opening	£6.50
Very Heavy duty		300. Screw base	£7.80
150 Kg	£4.47	380. Vacuum base	£11.50
		315. PC holder	£11.25
		311. Bench clamp	£6.50
		303. Vertical vice	£5.50

TEST METERS		ORyx SOLDERING	
LT101	£4.25	Solder pot	£10.50
LT801	£9.10	Oryx 75	£13.50
TS141	£21.00	Oryx 50	£7.25
141/30A Shunt	£4.00	SR2 desolder	£6.95
141/Lux	£18.00	SR3A desolder	£5.35
141/Thermometer	£16.00	SR3S desolder	£4.95
141/25KV	£7.50	Soldersuck	£1.50

BRADRAD, CONECUT, ADEL		PROFESSIONAL SWITCHES	
Bradrad 1½" or 36mm	£13.00	197.111	£1.99
Bradrad 2½" or 60mm	£33.00	199.112	£1.76
Conecut No. 1	£4.25	196.2	£1.97
Conecut No. 2	£6.90	198.1	£3.51
Conecut No. 3	£10.30	197.212	£1.99
Conecut No. 4	£12.60	224.6	£2.24
Set 1 2 3	£19.40	212.13	£2.84
Adel	£6.88	195.22	£2.03
Reamer, small	£5.90	195.2	£1.28
Reamer, large	£6.90	195.14	£2.54
Reamer, pair	£11.50	189.2	£1.54

OVER 250 DIFFERENT CASES IN STOCK — SIZE RANGE OVER 5000:1 IN VOLUME


Send for catalogue
WEST HYDE
DEVELOPMENTS LIMITED
Ryefield Cres., Northwood Hills, Northwood, Middx., HA6 1NN
Telephone: Northwood 24941/26732/27051
Telex: 923231 West Hyde Nthwd.

WW — 081 FOR FURTHER DETAILS

WEST HYDE COMPONENTS



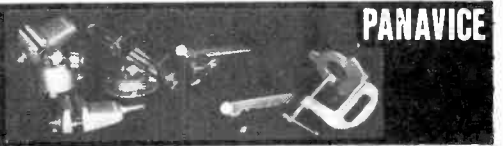
KNOBs
Hundreds of knobs, collet or screw fixing, plastic or aluminium, fluted, textured, smooth, wing, pointer, insulated, slow-motion, digital, crank-handle, heavy-duty, wing, contemporary, dual, & diamond turned. Shafts from 3mm to 10mm. Dia. from 8mm to 58mm.



PANAVICE
A very good holding system. Four vices, 3 different bases, all interchangeable. Many vice jaws to hold PCs or available in steel, neoprene, nylon etc. Max. opening 6". Table mounting, Screw mount or Vacuum base.



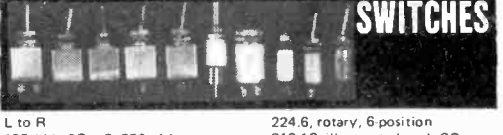ORyx
Solder pots incl. neons, temp. controlled irons, Oryx 75 silicone leads, solid state control with dial in handle. Oryx 50 thermostat in handle. Desoldering tools, all with PTFE nozzle. On right, solder suck at minimum cost.




SWITCHES
L to R
197.111, CO x 2, 220v 1A
199.112, CO, 220v 1A
196.2, CO x 2, 220v. 2A
198.1, 5-position toggle
197.212, spring return (197.111)
224.6, rotary, 6 position
212.13, illuminated push CO
195.22, push snap CO, 220v. 2A
195.2, CO, 220v. 2A
195.14, water-tight, 195.2
189.2, 6.5mm d. CO toggle

CASE SPECIALISTS

CATRONICS

WW TELETEXT DECODER

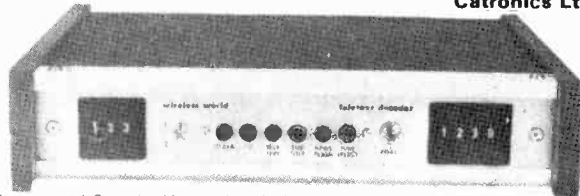The design of this decoder is being described in a series of articles being published by 'Wireless World' (from last November). All the components are available from Catronics Ltd.



The approved Catronics kit contains all the printed circuit boards and components necessary to build the complete decoder. Signal input required is a minimum of 0.5V detected video. The output is approximately 4V of R, G and B drive suitable for driving most types of colour Television sets. PLUS a luminance output for black and white sets.

The power supply and video switching circuitry are normally installed within the television cabinet and the main decoding control and memory circuitry in a separate cabinet positioned on top of the television.

PRICES ARE AS FOLLOWS:

- Set of 3 main PCBs only **£12.00+VAT (£3.00)**
- Component Kit (inc. PCBs) — for upper case only **£91.45+VAT (£9.70)**
- Add-on Kit for lower case characters **£12.95+VAT (£1.35)**
- Cabinet and Front Panel (styling may vary) **£11.60+VAT (£2.95)**

Ready-built and Tested Decoders add **£32.00 + V.A.T. (£8.00)**


Post & Packing PCBs are post free — but add £1 for component kit and/or cabinet

A wide range of other components are also available, including **SL600** series i.c.s, **KVG** and **MURATA** filters, **AERIALS** for Commercial Mobile and Radio Amateur bands, **IGNITION** Interference Suppression Components plus, of course, the famous **Catronics Frequency Counters and Prescalers** — including an exclusive new 500MHz version

Send S.A.E. for current price lists (stating requirements)

CATRONICS LTD. (Dept. 624)

39 Pound Street
Carshalton, Surrey
Tel: 01-669 6700

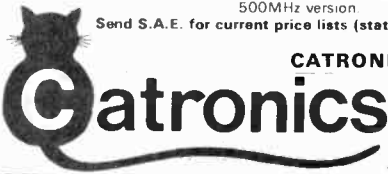

WW 622 — FOR FURTHER DETAILS

ADVANCED CLOCK KIT

Complete kit including attractive slim case for 6 digit alarm clock with bleep alarm, snooze and automatic intensity control, high brightness display driving with optional touch switch controls and crystal control/battery-back-up (both extra) using MK50253 and LED displays. Kit also includes PCBs, active and passive components, IC socket, miniature cool transformer, switches, flat cable, loudspeaker, mains plug and lead, perspex panel, and full instructions. With 0.5" JUMBO FND500 Displays **£27.31**

P.E. CAR CLOCK with Journey Timer

6 digit clock for use in any car with 12V battery with an independent journey timer incorporated. Bright Jumbo LED display comes on with ignition — automatic intensity control. Complete kit of all parts needed including case, PCBs and all components. Full instructions **£39.50**
Easy to build **E.E. DIGITAL CLOCK** (Jan issue) Kit of all components including case etc for this attractive clock with 12mm green display. Full instructions **£15.70**
50 Hz Xtal Timebase Kit for clocks (incl. advanced kit above) **£6.28**

CMOS ICs	CD4031	1.82	CD4062	7.33	CD4518	1.03	DISPLAY INT.
RCA MOT. ONLY	CD4032	0.88	CD4063	0.90	CD4520	1.03	SN75491
CD4000	0.17	CD4033	1.14	CD4066	0.58	CD4527	1.30
CD4001	0.17	CD4034	1.56	CD4067	2.95	CD4532	1.16
CD4002	0.17	CD4035	0.97	CD4068	0.18	CD4535	0.74
CD4006	0.97	CD4036	1.82	CD4069	0.18	CD4556	0.74
CD4007	0.17	CD4037	0.78	CD4070	0.18	MC14528	0.86
CD4008	0.79	CD4038	0.88	CD4071	0.18	MC14534	6.04
CD4009	0.46	CD4039	2.86	CD4072	0.18	MC14553	4.07
CD4010	0.46	CD4040	0.88	CD4073	0.18	MC14566	1.21
CD4011	0.17	CD4041	0.69	CD4075	0.18	MCM14552	8.05
CD4012	0.17	CD4042	0.69	CD4076	1.27		
CD4013	0.46	CD4043	0.83	CD4077	0.18		
CD4014	0.83	CD4044	0.77	CD4078	0.18	CLOCK CHIPS	
CD4015	0.83	CD4045	1.15	CD4081	0.18	MK50253	5.60
CD4016	0.46	CD4046	1.10	CD4082	0.18	MM5314	4.44
CD4017	0.83	CD4047	0.74	CD4085	0.59	AY51224	3.66
CD4018	0.83	CD4048	0.46	CD4086	0.59	AY51202	4.76
CD4019	0.46	CD4049	0.46	CD4089	1.27		
CD4020	0.92	CD4050	0.46	CD4093	0.66	IC SOCKET PINS	
CD4021	0.83	CD4051	0.77	CD4094	1.53	100	0.50
CD4022	0.79	CD4052	0.77	CD4095	0.86	1000	4.00
CD4023	0.17	CD4053	0.77	CD4096	0.86	3000	10.50
CD4024	0.64	CD4054	0.95	CD4099	1.50	MCM14552	8.05
CD4025	0.17	CD4055	1.08	CD4502	0.98		
CD4026	1.42	CD4056	1.08	CD4510	1.12	VEROCASES	
CD4027	0.46	CD4057	20.35	CD4511	1.28	751410J	2.64
CD4028	0.74	CD4058	3.64	CD4514	2.56	751411D	3.04
CD4029	0.94	CD4060	0.92	CD4515	2.56	751412K	4.00
CD4030	0.46	CD4061	16.43	CD4516	1.12	CA3130	0.88

FND500 Jumbo 0.5in. CC Red LED now only **£1.02**. This full specification prime unit from Fairchild offers outstanding value — compare its price with other digits of comparable size and high quality. DL704E 0.3" CC Red LED now only **75p**.

ADD VAT at 9% (Higher rate does not apply to any of above) 15p P&P on orders under £3 — Despatch is by 1st Class post. Price list and data sent FREE with an order — or on request (an SAE helps). Official orders welcomed (written or phoned) — Univs. Poly's. Govt. Cos. etc. Export orders No VAT! Add 35p (Europe) + 1 (Overseas) for Airmail P&P. (No export outside Europe for databooks and transformers.)

SINTEL 53C ASTON STREET, OXFORD
TEL. 0865 49791

WW — 048 FOR FURTHER DETAILS

Build it yourself!

Designed by **TEXAS**

Featured by **PRACTICAL WIRELESS**
SOLE U.K. DISTRIBUTORS - HENRY'S

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

- ★ Can be built Stage by stage
- ★ Ask for leaflet 20.
- ★ Everything necessary supplied. Full after sales service and guarantees.

Look at the Texan specification

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardeners low-field low-line mains transformer, all facilities and controls. Slim design, chassis 14½" x 6" x 2" overall, 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

KIT PRICE
£35.00
inc. VAT + £1 p&p

Built and tested **£45.00 inc. VAT**
+ £1.00 p&p.

THE NATURAL FOLLOW-ON — THE TEXAN FM TUNER KIT!

KIT PRICE
£25.95
inc. VAT +
50p p&p.

Build the matching Texan stereo tuner! Features advanced varicap tuning, Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec. 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

Built and tested **£30.95 inc. VAT + 50p p&p**

VIDEO SPORT

all the electronic excitement you could wish for!

★ OVER 10,000 ALREADY SOLD ★ IDEAL GIFT

An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game — football, tennis or hole-in-the-wall. Absolutely safe. For you, your children. And your TV. Mains powered. List Price **£42.50**



HENRY'S PRICE—ONLY £29.50 inc. VAT + 50p p&p

WHATEVER YOU DO, DON'T FORGET YOUR LATEST HENRY'S CATALOGUE!



For this new edition, we have made hundreds of changes and additions. It has over 200 pages, containing virtually everything for amateurs and professionals. And you'll have no bother at all finding everything you want, because there's a complete alphabetical index as well as a section index. Together, they put you right on course for the items you need. From Sinclair projects to educational kits. Oscilloscopes to panel meters. Coils to capacitors. Transistors to valves. Loudspeakers to microphones — all at competitive prices. Over 200 pages of vital statistics — just for you! So send now for your copy.

- Over 5000 items inside!
- Every copy contains a free 50p voucher.
- Many new items.
- Over 200 pages.

FREE to Educational Establishments when ordered on official headed notepaper.

ONLY 50p + 20p carr / pack

Henry's

SELF-SERVICE CENTRES 404 and 309 EDGWARE ROAD, LONDON W2
Bargains galore — Call in and see for yourself!

404/6 EDGWARE ROAD, LONDON W2 01-402 8381
LOWER SALES FLOOR, 231, TOTTENHAM CT. RD., LONDON W1 01-636 6681
NEW MIDLANDS STORE 94/96 UPPER PARLIAMENT STREET, NOTTINGHAM. 0602-40403
All mail to Henry's Radio, 303 Edgware Road, London W2

WW—053 FOR FURTHER DETAILS

AIRMEC FREQUENCY METER TYPE 265: 0-6000 rpm and 0-100Kc/s £35. Carr. £2.
RACAL L.F. CONVERTER UNIT RA-37B : £35. Carr. £1.
RACAL I.S.B. ADAPTOR RA-95A: £65. Carr. £2.
MUIRHEAD ATTENUATORS: 75 ohms 0-8 Mc/s 3V MAK 3 ranges 0-5, 0-25, 0-50 DB £3.00 + 75p post.
CREED MODEL 54 TELEPRINTER: £37.50 each. Carr. £4.
CREED MODEL 75 TELEPRINTER: Receiver only £30.00. Carr. £3.
MULLARD VALVE VOLTMETER: E/7555/3 A.C./D.C. 2 ranges 0-5 and 0-500v. £35. Carr. £2.
EDDYSTONE TELEPRINTER ADAPTOR TYPE 937: £45. Carr. £1.
WAVEMETER CLASS 'D' NO. 2: 1.2 to 20Mc/s 12 volts d.c. input or 240v a.c. £12.50. Carr. £3.
WILD BARFIELD ELECTRIC FURNACE MODEL CCI.22X: With ether indicating temperature controllers Model 990. 0-1400° C. £250. Carr. £5.
METROVAC IONIZATION GAUGE MODEL V.C.3: £55. Carr. £3.
AVO VALVE TESTER CT.160: (Portable) similar to Avo Mk. 3 Characteristic meter. Good condition. £45.00. Carr. £2.00.
ANTENNA MAST: 30ft. consisting of 10 x 3ft tubular screw sections (7/8" dia.) with base, guyropes and stays, etc. £7.50 each. Carr. £2.00.
REDIFON TELEPRINTER RELAY UNIT No. 12: ZA-41196 and power supply 200-250V a.c. Polarised relay type 3SEITR. 80-0V 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. x 8in. New condition. £107 Carr. 75p.
SOLARTRON PULSE GENERATOR TYPE G1101-2: £75.00 each. Carr. £2.00.
TELEPRINTER TYPE 7B: Pageprinter 24V d.c. power supply, speed 50 bauds per min. second hand cond. (excellent order) no parts broken. £20 each. Carriage £3.
AUTO TRANSFORMER: 230V 50c/s, 1000 watts. Mounted in strong steel case 5" x 6 1/2" x 7". Bitumen impregnated. £12.00. Carr. £1.50.
BRIDGE MEGGER: 250V. (Evershed Vignoles) series 2. £30 each. Carr. £1.
BRIDGE MEGGER: 2,500V, series 1. £30 each. Carr. £1.
CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. £25. Carr. £1.50.
SOLARTRON VARIABLE POWER UNIT S.R.S. 1535: 0-500 volts at 100 mA and 6.3 volts C.T. 3 amps d.c. 110/250 volts a.c. input. £18.50. Carr. £1.50.
CLASS 'D' WAVEMETER NO. 1: Crystal controlled heterodyne frequency meter covering 2-8 MHz. Power supply 6V d.c. Good secondhand condition. £8.50. Carr. £1.50.
PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microseconds 0-0.1c. 115V input. £55 each. Carr. £1.
MUIRHEAD PHASEMETER D-729: A.M. £85. Carr. £3.
ALL CARRIAGE QUOTES GIVEN ARE FOR 50-MILE RADIUS OF LONDON ONLY.

RACAL RA17 Front Panels: £5. £1 post.
Q METER: 30MHz-200MHz. £55. Carr. £1.
MUIRHEAD PHASEMETER TYPE D729: A.M. £95.00. Carr. £3.00.
CT.420 SIGNAL GENERATOR: 200-8000c/s Variable tuning. Two fixed frequencies 9000 and 10,000. Internal calibrator 100 & 500 c/s. £75 each carr. £2.
NOISE GENERATOR TF-1106: Frequency 1 to 200 Mc/s Direct noise factor calibration. Output impedance 70 ohms £65 each. Carr. £1.50.
MW-59 UNIVERSAL KLYSTRON POWER SUPPLY: £85. Carr. £3.
TF-1278/1 TRAVELLING TUBE WAVE AMPLIFIER: £125. Carr. £2.
BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1.
CAWKELL REMSCOPE TYPE 741 : Memory scope, 'as new' cond. £150.00.
MANSON SYNTHESISER Q115-URC: 2-30 mc/s. £175.00.
FIREPROOF TELEPHONES: £25.00 each, carr. £1.50.
POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30.00 each. Carr. £3.00.
SMOOTHING UNIT (for the above): £10.00 each. Carr. £2.00.
X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 each. Carr. £1.
BACKWARD WAVE OSCILLATOR TYPE SE-125: 6.3 heater, 105V Anode, 7.9mA. Mnfr. Watkins & Johnson. £85 each. Carr. £1.
TEKTRONIX TIME MARK GENERATOR TYPE 180-S1: 5, 10, 50 MHz. £65. Carr. £2.
ROTARY INVERTERS: TYPE PE.218E — input 24-28V d.c., 80 Amps. 4,800 rpm. Output 115V a.c. 13 Amp 400 c/s. 1Ph. P.F.9. £200.00 each. Carr. £2.50.
FREQUENCY METER BC-221: 125-20,000 Kc/s complete with original calibration charts. Checked out, working order £20 + £1.50 carr.
COMPUTER STABILISED POWER SUPPLY: 19" rack fitting. Input 200-240v a.c. Output 6 volts at 25 amps. 4" meter 0-8 volts 0-25 amps. £35.00 each. Carr. £3.00.
SORENSEN VOLTAGE REGULATOR: Input 190/260 volts a.c. Output 220/240 volts a.c. 1000 watts. £40.00, carr. £3.00.
EVERSHED SAFETY OHM. METER: Max 10Ma. Test pressure 30v. Complete in leather case. £25.00 each. post £1.00.
AVO SIGNAL GENERATOR: 200/250 volts a.c. Frequency range 6 bands 50Hz to 80MHz. £25.00, carriage £2.00.
FYLDE AMPLIFIERS TYPE 154 BDM: Rack mounted 3v d.c. and power supply FE.500.TP. £65.00, carr. £2.00.
STC ATTENUATORS 74600A & B: Push-button selectors 0-9 db 75ohm. and 0-90 db 75 ohm. Housed in steel case 11" x 8" x 7". £25.00 each. Carr. £1.50.
AUTOMATIC VOLTAGE STABILIZERS: Input 207-242v a.c. Output 230v a.c. at 2.80 amps. £17.50, carriage £1.50.

ALL U.K. ORDERS SUBJECT TO VALUE ADDED TAX.

If wishing to call at stores, please telephone for appointment

W. MILLS

3 & 3a BALDOCK STREET, WARE, HERTS. SG12 9DT
 WARE 66312 (STD 0920)
 and at ELSTOW STORAGE DEPOT. Phone: Bedford 740605 (STD 0234)

TAUT SUSPENSION MULTIMETERS
 Made in USSR



U4312: 41 ranges 0.3mA — 6A D.C., 1.5mA — 6A A.C., 0.3-900v A.C./D.C., 0.2-50kΩ; Mirror scale. Sensitivity 667Ω/v; Accuracy 1% D.C., 1.5% A.C. £11.50.
 U4313: 40 ranges 0.06mA — 1.5A D.C., 0.6-1.5A A.C.; 1.5-600v A.C./D.C., 0.06-60kΩ; Mirror scale. Sensitivity 20kΩ/v D.C.; 2kΩ/v A.C. Accuracy 1.5% D.C., 2.5% A.C. £14.90.
 U4315: 43 ranges 0.05mA-2.5A D.C.; 0.5mA-2.5A A.C.; 1-1000v D.C./A.C.; 0.3-500kΩ; Sensitivity 20kΩ/v D.C., 2kΩ/v A.C. Accuracy 2.5% D.C., 4% A.C. £11.25.



U4324: 33 ranges 0.06mA — 3A D.C., 0.3mA — 3A A.C., 0.6-1200v D.C., 3-900v A.C., 0.5-500kΩ; Sensitivity 20,000Ω/v D.C., 4000Ω/v A.C. Accuracy 2.5% D.C., 4% A.C. Re-chargeable cadmium cell operation. £10.85.

LINEAR I.C. AMPLIFIERS

TAA263 — 3 stage low level amplifier. Bandwidth DC to 600KHz. Supply voltage 6-8V Output power 10mW To 72 4-lead £0.65.
 TAA293 — Med freq. amplifier up to 600KHz. Supply voltage 6V Output 10mW into 150Ω. TO 74 10-lead case £0.65.
 TAA320 — Most stage followed by a bi-polar transistor Gate-to-source voltage 9-14V Power dissipation 200mW Drain current 1μA. TO 18 3-lead £0.60.


DIGITAL 7400 SERIES I.C.

Made in USSR			
7400	£0.14	7440	£0.14
7401	£0.14	7450	£0.14
7410	£0.14	7453	£0.14
7420	£0.14	7455	£0.14
7422	£0.20	7460	£0.14
7430	£0.14	7472	£0.30
		7474	£0.25

TEXAS BC517


Silicon Darlington pair in three-lead plastic case Average current gain 30,000 Max V_{ceo} 40V; Max I_c 400mA. Max. I_{co} 10 nA. £0.80

OSCILLOSCOPE CI-5
 Made in USSR

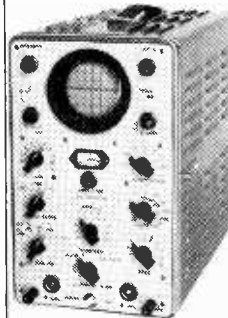

Extremely simple and easy to use single beam oscilloscope. Well proved design based on standard octal valves makes servicing and maintenance straightforward and inexpensive. Because of its bandwidth of 10 MHz the instrument is suitable for general electronic applications and educational purposes where a sophisticated instrument would be both too expensive and delicate. 3-in. tube giving a 50 x 50mm clear display. Amplitude and time base calibrations. Sensitivity 30mm/v max. Triggered and free-running time base, suitable for displaying pulses from 0.1 μ sec. to 3 m sec. A.C. mains operation.
Price £55.00 ex. works
 Packing and carriage (U.K. only £2.50)

EDUCATIONAL METERS
 Made in USSR

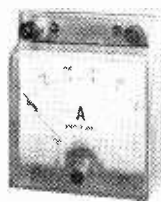

A range of small portable free-standing meters suitable for experiments and demonstration work. Moving coil movements with centre-pole pieces. 69mm long open scale. Basic calibration accuracy 4% The following ranges are available: 1, 2, 5, 10 Amps D.C., 6, 15, 30 Volts D.C. Overall dimensions: 80 x 100 x 48mm.
Price £1.90 ex. works
 Packing and postage £0.20 per meter

SPECIAL TELEVISION BARGAINS

FIRST GRADE TRANSISTORS

R2008B	£0.95
R2010B	£1.65
BU126	£1.55
BU133	£1.55
BU208	£2.00

Have you already got our illustrated 1975 catalogue/price list of valves, semiconductor test equipment and passive components? If not, please send £0.20 for your copy now

Prices are exclusive of VAT and unless stated otherwise packing and postage. When remitting cash with order please add £1.00 per multimeter, or £0.20 in £ for other items, as well as VAT (25% for valves, semiconductors and linear I.C.s and 8% for other equipment)

Z & I AERO SERVICES LTD.

Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF
 Tel.: 727 5641 Telex: 261306

Retail Branch:
 85 Tottenham Court Road
 London W1. Tel: 580 8403


CHROMASONIC electronics

Dept. 5, 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C - MOS

	1-24	25-99	100up
CD4000AE	19p	17p	14p
CD4001AE	19p	17p	14p
CD4002AE	19p	17p	14p
CD4006AE	E1.59	E1.33	E1.06
CD4007AE	23p	19p	15p
CD4008AE	E1.75	E1.46	E1.17
CD4009AE	Use	CD4049*	
CD4010AE	Use	CD4050*	
CD4011AE	Use	17p	14p
CD4012AE	19p	17p	14p
CD4013AE	59p	50p	46p
CD4014AE	E1.75	E1.46	E1.17
CD4015AE	E1.75	E1.46	E1.17
CD4016AE	55p	48p	44p
CD4017AE	E1.29	E1.07	93p
CD4018AE	E1.89	E1.56	E1.25
CD4019AE	80p	60p	53p
CD4020AE	E1.97	E1.64	E1.31
CD4021AE	E1.75	E1.46	E1.17p
CD4023AE	19p	17p	14p
CD4027AE	E1.83	E1.53	E1.27
CD4028AE	E1.26	E1.05	84p
CD4025AE	19p	17p	14p
CD4026AE	E2.79	E2.32	E1.86
CD4027AE	98p	82p	65p
CD4028AE	E1.53	E1.28	E1.02
CD4029AE	E1.89	E1.56	E1.15
CD4030AE	71p	59p	47p
CD4035AE	E1.75	E1.46	E1.17
CD4040AE	E2.01	E1.69	E1.34
CD4042AE	E1.49	E1.24	99p
CD4046AE	E2.15	E1.79	E1.44
CD4049AE	69p	59p	46p
CD4050AE	69p	59p	46p
CD4051AE	E2.78	E2.32	E1.85
CD4052AE	E2.78	E2.32	E1.85
CD4056AE	E2.12	E1.76	E1.41
CD4060AE	E2.39	E1.99	E1.55
CD4066AE	E1.13	94p	75p
CD4068AE	28p	24p	19p
CD4069AE	28p	24p	19p
CD4070AE	28p	24p	19p
CD4071AE	28p	24p	19p
CD4077AE	71p	59p	47p
CD4081AE	28p	24p	19p
CD4082AE	28p	24p	19p
CD4085AE	E1.28	E1.06	85p
CD4086AE	E1.28	E1.06	85p
CD4093AE	E1.56	E1.20	E1.04
CD4099AE	E2.95	E2.46	E1.96
CD4111AE	E2.36	E1.79	E1.44
CD4528AE	E1.30	E1.08	87p

I.C. SOCKETS



Pin Sockets, pins in strips of 100. Just snip off what you need. 65p per strip

Dual in line

8 pin 13p.	24 pin 26p.	10S
14 pin 15p	28 pin 30p.	8 pin 31p.
16 pin 15p	36 pin 39p.	10 pin 35p.

FREE CIRCUITS

Our 8 Page A4 Audio I.C. Booklet is supplied FREE with purchases of Linear I.C.'s worth £1. or more (35p. if sold alone) Contains circuits and pin connections

- 15 Amplifiers 250 mW to 20 watts
- 5 Audio Pre-Amplifiers
- 1 Tape Pre-Amplifier
- 1 Power Driver
- 1 Instrument Amplifier (Bifet)
- 1 General Purpose Mini Amplifier
- 1 D.C. Controlled Gain Control
- 1 Micro-mini radio (2 I.C.'s)

PHOTO-DARLINGTON



V_{ceo} 25v 2N5777
V_{ceo} 25v
V_{beo} 8v
I_I 250 mA
P_d 200 mW
Hfe 2500

35p

LINE-O-LIGHT



NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20 pin dual-in-line package. Ideal for solid state analogue meters or dials. Type 101 RED. £2.26. Complete with leaflet.

74 TTL

	1-24	25-99	100*
7400	14p*	12p	10p*
7401	14p*	12p	10p*
7402	14p*	12p	10p*
7403	15p*	12p*	10p*
7404	16p*	13p*	11p*
7408	16p*	13p*	11p*
7409	16p*	13p*	11p*
7410	16p*	13p*	11p*
7413	29p*	24p*	20p*
7417	27p*	22p*	20p*
7420	16p*	13p*	11p*
7427	27p*	22p*	18p*
7430	16p*	13p*	11p*
7432	27p*	22p*	18p*
7437	27p*	22p*	18p*
7441	75p*	67p*	50p*
7442	65p*	55p*	43p*
7445	85p*	71p*	57p*
7447	81p*	75p*	65p*
7448	75p*	67p*	50p*
7447A	95p*	83p*	67p*
7470	30p*	25p*	20p*
7472	25p*	21p*	17p*
7473	30p*	25p*	20p*
7474	32p*	26p*	21p*
7475	47p*	39p*	31p*
7476	32p*	26p*	21p*
7482	75p*	62p*	50p*
7485	E1.30	E1.09	87p
7486	32p*	26p*	21p*
7489	E2.92	E2.80	E2.10
7490	49p*	40p*	33p*
7491	65p*	55p*	45p*
7492	57p*	46p*	36p*
7493	45p*	40p*	33p*
7495	67p*	55p*	45p*
74100	E1.08	89p*	72p*
74107	35p*	28p*	23p*
74121	34p*	28p*	23p*
74122	47p*	39p*	31p*
74141	78p*	63p*	53p*
74145	68p*	58p*	48p*
74154	E1.62	E1.48	86p*
74174	E1.00	83p*	67p*
74180	E1.06	89p*	72p*
74181	E3.20	E2.50	E1.90
74192	E1.35	E1.14	90p*
74193	E1.35	E1.14	90p*
74196	E1.64	E1.34	99p*

LINEAR I.C.'s

555 (8 pin dip)	55p*
555 (10-99T)	81p*
556 (14 pin dip)	E1.29*
703 (RF/IF Amp)	68p
707 (8 pin dip)	38p
709 (10-99)	45p
709 (14 pin dip)	39p
710 (8 pin dip)	39p
710 (10-99)	45p
710 (14 pin dip)	44p
711 (10-99)	51p
711 (14 pin dip)	44p
720 (A.M. Radio)	E1.76
723 (10-99)	E1.09
723 (14 pin dip)	55p
741 (8 pin dip)	30p
741 (10-99)	43p
741 (14 pin dip)	39p
747 (14 pin dip)	E1.04
748 (8 pin dip)	42p
748 (10-99)	46p
748 (14 pin dip)	49p
753 (F.M. 1st. I. F)	E1.08
75491	88p*
75492	E1.10*

Regulators 100 mA

78105WC (10-92)	60p*
78112WC (10-92)	60p*
78115WC (10-92)	60p*

Regulators 100mA

78L05AWC (TBA625A)	90p*
78L12AWC (TBA625B)	90p*
78L15AWC (TBA625C)	90p*

Regulators 500mA

78M05HC	E1.35
78M12HC	E1.35
78M15HC	E1.35
78M18HC	E1.35
78M24HC	E1.35

Regulators 1A

7805KC (10-3)	E2.09
7812KC (10-3)	E2.09
7815KC (10-3)	E2.09
7818KC (10-3)	E2.09
7824KC (10-3)	E2.09

Regulator 1A

7805UC (10-220)	E1.72
7812UC (10-220)	E1.72
7815UC (10-220)	E1.72
7818UC (10-220)	E1.72
7824UC (10-220)	E1.72


IC L8030 E3.52

LM2111	E1.12	SN76001N (TAA611)	E1.82
LM3900	69p	SN76003N	E3.30
LM3909	66p*	SN76013N	E1.98
MC1303L	E1.94	SN76023N	E1.98
MC1306P	85p	SN76227N(MC1327)	E1.89
MC1310P	E2.10	SN76532N	E1.81
MC1312P	E2.52	SN76544N	E1.86
MC1314P	E4.34	SN76550-2(TAA550)	89p
MC1315P	E4.85	SN76552-2	81p
MC1327P	E1.48	SN76660N(TBA120)	75p
MC1330P	89p	SN76660N (CA3065)	E1.12
MC3401P	81p	TAA263	E1.50
MC1339P	E1.60	TAA300	E2.16
MC1350	68p	TAA310A	E1.87
MC1351	92p	TAA320	E1.44
MC1352	92p	TAA350	E2.43
MC1357	E1.60	TAA370	E3.45
MC1358(CA3065)	E1.23	TAA550	75
MC1375	E1.56	TAA570	E2.75
MC1455 (555T)	65p*	TAA700	E5.03
MC1456CQ	E1.77	TBA120S	E1.25
MC1458CP1	89p	TBA231	E1.02
MC1468G	E2.30	TBA281 (723)	E2.59
MC1495L	E4.48	TBA500Q	E3.16
MC1496G	E1.01	TBA520Q	E3.85
MC3302P	E1.65	TBA530Q	E3.27
MC3401P	81p	TBA540Q	E3.72
MFC4000B	87p	TBA550Q	E5.29
MFC4060A	85p*	TBA560CQ	E5.29
MFC6030A	85p*	TBA625A	E1.03
MFC6040	E1.01	TBA625B	E1.03
MMS314	E4.80	TBA625C	E1.03
MMS316	E9.99	TBA651	E1.87
MVRSV (10-3)	E1.45	TBA720Q	E2.79
MVRSV2 (10-3)	E1.45	TBA750Q	E2.79
MVRSV3 (10-3)	E1.45	TBA800	E1.11
NE5401	E1.25	TBA810S	E1.24
NE546A	E1.16	TBA810AS	E1.24
NE555V	69p*	TBA820	80p
NE556	E1.29	TBA920Q	E4.71
NE5608	E5.06	TBA990Q	E4.71
NE5618	E5.06	TCA270Q	E5.24
NE5628	E5.06	TCA760	E2.16
NE563	E2.96	TCA800Q	E7.24
NE565N	E2.63	TCA830S	E1.04
NE566V	E1.87	TCA940	E2.25
NE567V	E2.63	TDA1054	E1.50
SD6000	E1.22	TDA1200	E2.43
SL414A	E2.09	TDA1405	80p*
SL415A	E2.75	TDA1412	80p*
SL437D	E7.50	TDA1415	80p*
SL440	E2.84	TDA2010	E3.00
SN75491N	88p*	TDA2020	E3.75
SN75492N	E1.10	ULN2111A	E1.52
SN75492N	E1.10	ZN414	E1.26

ZN414 Leaflet free with devices (10p alone)

MC1310; 2, 4 & 5 Leaflet free with devices (10p alone)

3 1/2 DECADE DVM I.C.

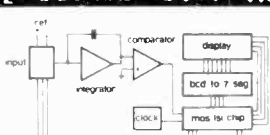

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 1/2 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507

OUR PRICE ONLY £6.59.*


(Data and Circuit Booklets alone 20p.)

The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet E3.95p*(inc. VAT) (Leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone Clive for details.

MULLARD MODULES

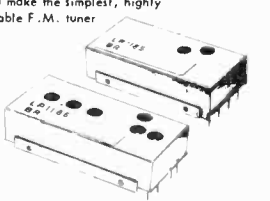Still make the simplest, highly reliable F.M. tuner



LP1186 Varactor front end £8.60
LP1185 I.F. Strip £8.95
LP1400 Multiplex decoder £9.02

LED DISPLAYS

Litronix Double Digit Displays

0.5" Common Anode, 2 R/H
Decimal Points
DL721 ±1.9
DL727 0.0 to 9.9
Suitable for Clocks, Meters, Instruments, Channel Indicators
Our price £4.75 * each

NEW



Low cost Red GoASP Motorola MLED 500 in a T092 package

0.33"	Litronix DL 707 Series
0.33"	Monsanto MAN 50/70/80/3600
0.33"	Xciron XAN 70 Series
0.43"	Monsanto MAN 4000 Series
0.63"	Litronix DL747 'Jumbo' Series


15p.*

NOTE: MAN 4000 Series pin outs are 14 pin dip the same as MAN 50; 70 and 80 series.

DIGITAL SWITCH

BCD encoded digital switch Reading 0 to 9. Suitable for digital clock alarm setting DVM input scaling etc.

1 to 9. £1.49 each *



all £1.82* each (Red only)
all £1.82* Each (Red, green, yellow, Orange)
all £1.49* Each (Red, Green, yellow)
all £2.32* Each (Red, Green, Yellow, Orange)
all £2.42* Each (Red only)

Common Cathode as Common Anode (Red only)

LIGHT EMITTING DIODES

Free snap-on plastic retainer

0.125"			0.16"			0.2"			
dia. lens	(TIL 209)		dia. lens			dia. lens	(MLED 650)		
1+	10+	100+	1+	10+	100+	1+	10+	100+	
Red	1p	15p	13p*	27p	24p	23p*	18p	16p	14p*
Green	27p	24p	22p*	33p	30p	27p*	30p	27p	25p*
Orange	27p	24p	22p*	33p	30p	27p*	30p	27p	25p*
Yellow	34p	31p	29p*	35p	32p	29p*	35p	33p	30p*

..... Cont'd

Our Bulk Buying Power enables a repeat of our Special Offer:

0.33" (LIT 707) 90p.* (inc. VAT)
0.63" (LIT 747) £1.99.* (inc. VAT)

OPTO-ISOLATORS

T11 4N25 or T11116
6 pin industry standard package
2.5KV isolation £1.00.*

MAINS TRANSFORMERS

Secondaries			1A	1A	2A	4A
6-0-6V	100 mA	97p.*	0-9-17 V	-	-	-
9-0-9V	100 mA	97p.*	0-12-15-20-24-30V	-	E1.95 *	E2.27
12-0-12V	100 mA	97p.*	0-24-30-40-48-60V	-	E2.48 *	E4.15.
20-0-20V	1 A	E4.55	0-24-30-40-48-60V	-	E5.18 *	E7.02
24-0-24V	500 mA	E2.48	0-19-25-33-40-50V	E2.70 *	E3.40 *	E4.25
28-0-28V	1 A	E6.18				

p.p. on transformers 10% of price min. 20p

VAT INC


Items followed by * inc. VAT at 8% all others include 25%

Overseas Customers deduct 2/27 from * items. 1/5 from others

postage & packing 20p. Orders for over £6. post free. Except transformers


Data Sheet and photocopy service available 10p. per page
Advert No. 1A of Series B
CALLERS WELCOME

Looking for...

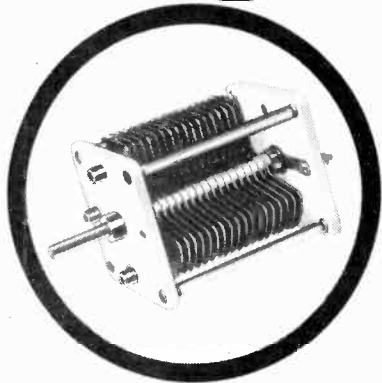


...high voltage air dielectric capacitors

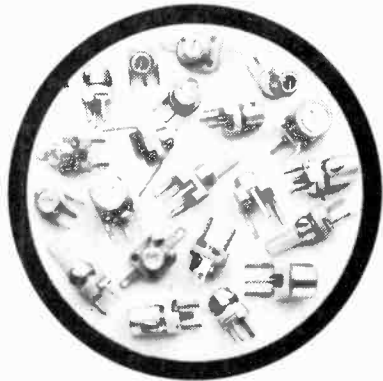Specially developed for modern transmitting and aerial tuning applications.



...an extensive and versatile range of trimmers

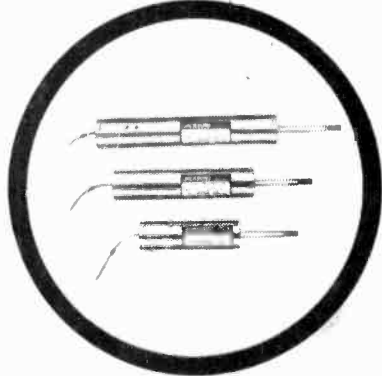With an extra edge of capability to a host of applications in professional communications and instrumentation equipment.



...a new approach to linear displacement measurement

High sensitivity and linearity coupled with infinite resolution make these linear and angular displacement transducers ideal for a wide variety of control and measurement applications.

See them on Stand 32 at the "All Electronics Show",
Grosvenor House, April 13th-15th.



All Jackson products are backed by 50 years' experience in the communications field. Highly skilled men, and Jackson Brothers' good name.
JACKSON BROTHERS (LONDON) LIMITED
Kingsway, Waddon, Croydon CR9 4DG. Tel: 01-681 2754/7 Telex: 946849.

B. S. 9000 Approved. DEF. STAN. 05 - 21 REG. No. 48020/1/01.

WW-083 FOR FURTHER DETAILS

"Ampex and WHAT?..."

The JAMES SCOTT Alignment Units for D.R. and F.M. Multi-Channel Tape Recorders.




The F.M. Alignment Unit Type FMU/1 illustrated was designed at the Royal Radar Establishment, Malvern, to suit Ampex Recorders working on the IRIG intermediate band specification (using ES 100 Electronics) e.g. Model Numbers FR 1200, FR 1260, FR 1300, FR 1800L, FB 400, PR 500

If you have a sophisticated Ampex Recorder—Align it to the Manufacturers specification using our Alignment Units for D.R. & F.M. Systems.

Speedy and inexpensive

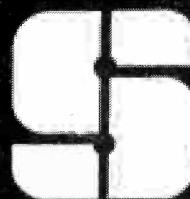For Further information and Technical Literature Write or telephone.



**JAMES
SCOTT**
(Electronic Engineering) Ltd

CARNTYNE INDUSTRIAL ESTATE
GLASGOW G32 6AB
Tel: 041 778 4206

WW-030 FOR FURTHER DETAILS

To obtain further details of any of the coded items mentioned in the Editorial or Advertisement pages of this issue, please complete one or more of the attached cards entering the reference number(s). Your enquiries will be passed on to the manufacturers concerned and you can expect to hear from them direct in due course. Cards posted from abroad require a stamp. These Service Cards are valid for six months from the date of publication.

Please Use Capital Letters

If you are way down on the circulation list, you may not be getting the information you require from the journal as soon as you should. Why not have your own copy?

To start a one year's subscription, place a tick in the box on one of the postage-free cards opposite and fill in your name and address.

Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt. Britain, Channel Islands or N. Ireland

BUSINESS REPLY SERVICE
Licence No. 12045

**WIRELESS WORLD,
READER ENQUIRY SERVICE,
429 BRIGHTON ROAD,
SOUTH CROYDON,
SURREY
CR2 9PS**

2

CUT HERE

CUT HERE

CUT HERE

Enquiry Service for Professional Readers

WIRELESS WORLD

Wireless World, April 1976

WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

Name

Name of Company

Address

Telephone Number

PUBLISHERS USE ONLY			A/E			
---------------------	--	--	-----	--	--	--

Position in Company

Nature of Company/Business

No. of employees at this establishment

I wish to subscribe to Wireless World

VALID FOR SIX MONTHS ONLY

CUT HERE

CUT HERE

Wireless World: Subscription Order Form

To become a subscriber to Wireless World please complete the reverse side of this form and return it with your remittance to:

**Wireless World, Room 15,
Dorset House, Stamford Street,
London SE1 9LU, England**

WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

Name

Name of Company

Address

Telephone Number

PUBLISHERS USE ONLY			A/E		
------------------------	--	--	-----	--	--

Position in Company

Nature of Company/Business

No. of employees at this establishment

I wish to subscribe to Wireless World

VALID FOR SIX MONTHS ONLY


CUT HERE

Do not affix Postage Stamps if posted in Gt. Britain, Channel Islands or N. Ireland

Postage will be paid by Licensee

BUSINESS REPLY SERVICE
Licence No. 12045

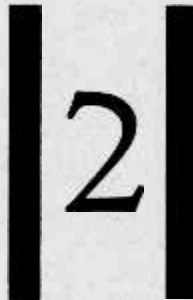**WIRELESS WORLD,
READER ENQUIRY SERVICE,
429 BRIGHTON ROAD,
SOUTH CROYDON,
SURREY
CR2 9PS**



CUT HERE

Wireless World Subscription Order Form

Wireless World, April 1976

UK subscription rates
1 year: £7.00

USA & Canada subscription rates
1 year: \$18.20

Please enter my subscription to Wireless World for 1 year

I enclose remittance value.....made payable to
IPC BUSINESS PRESS Ltd.

Name.....

Address.....

**HARMSWORTH TOWNLEY
FOR FASTENERS**

The quickest way of putting things together

METAL ANCHOR NUTS

with threads up to 3/8" or 10 mm



SYSTEM J for sheet metal and other work up to 1/4" thick




SYSTEM X for materials from 0.038" upwards.

These internally threaded fasteners are set into work like a blind rivet with hand and power tools.



WIRE TIES

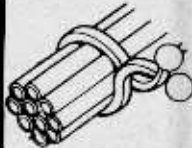


Colour coded plastic wire ties. Twist-on, Twist-off, use over and over again.

PLASTIC RIVETS




Self expanding plastic rivets, set with simple hand tools or a light hammer.

DRESSING CLIPS

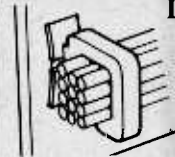


Semi-rigid panel-mounted clips for flat, compact looms.

**SELF-ADHESIVE
CABLE CLIPS**

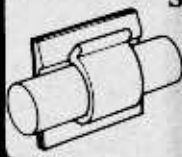

Three sizes of plastic clips with self-adhesive backing.

**P.C. BOARD
FITTINGS**

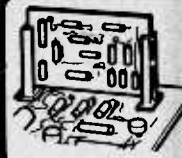

Guides, Stand-offs, spacers in various sizes, all in non-conductive plastic.

To get information on hundreds of fastener types please ask for leaflets!
Harmsworth, Townley & Co. Ltd.
2 Harehill, Todmorden, Lancs.
Phone 070 681 2601

Celestion Dittons get the best out of any system

Buy a really good set of speakers and you've got yourself a better hi-fi system... buy a set of Celestion Dittons and you've got one of the best!

Whether you already own or are thinking of buying either a 'package' hi-fi system or are selecting your own individual units, a pair of good speakers will pay dividends in terms of sound quality.

Some people pay least attention to selecting the speakers. Given first priority they will vastly improve the performance of most systems.

Celestion Dittons have a long standing reputation among enthusiasts for their outstanding achievements in high quality sound reproduction.

From left to right the Ditton 11, 44 and 33.

Visit your Celestion Dealer. See the beautiful appearance and hear the new sounds of the very latest Dittons.

Full details on request.



Celestion



Rola Celestion Limited, Ditton Works,
Foxhall Road, Ipswich, Suffolk IP3 8JP.
Telephone: Ipswich (0473) 73131.
Cables: Voicecoil Ipswich. Telex: 98365.

Please send full details of Ditton 11 Ditton 33 Ditton 44 W10
(tick appropriate box/boxes)

Name _____

Address _____

15 — 240 Watts!

HY5 Preamplifier


The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi function equalization — Low noise — Low distortion — High overload — Two simply combined for stereo

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:

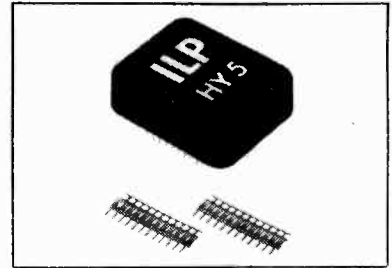INPUTS: Magnetic Pick-up 3mV, Ceramic Pick-up 30mV, Tuner 100mV, Microphone 10mV, Auxiliary 3-100mV, input impedance 47k Ω at 1kHz
 OUTPUTS: Tape 100mV, Main output 500mV R.M.S.
 ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz, Bass \pm at 100Hz
 DISTORTION: 0.1% at 1kHz, Signal/Noise Ratio 68dB
 OVERLOAD: 38dB on Magnetic Pick-up, SUPPLY VOLTAGE \pm 16-50V
Price £4.75 + £1.19 VAT P&P free.



HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build
APPLICATIONS: Updating audio equipment — Guitar practice amplifier — Test amplifier — audio oscillator.

SPECIFICATIONS

OUTPUT POWER 15W R.M.S. into 8 Ω , DISTORTION 0.1% at 15W
 INPUT SENSITIVITY 500mV FREQUENCY RESPONSE 10Hz-16kHz — 3dB
 SUPPLY VOLTAGE \pm 18V

Price £4.75 + £1.19 VAT P&P free.

**Available
June '76**

HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS:

INPUT SENSITIVITY 500mV
 OUTPUT POWER 25W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.04% at 25W at 1kHz
 SIGNAL/NOISE RATIO 75dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB
 SUPPLY VOLTAGE = 25V, SIZE 105 50 25mm

Price £6.20 + £1.55 VAT P&P free.



HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.


FEATURES: Very low distortion — Integral heatsink — Load line protection — Thermal protection — Five connections — No external components

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

SPECIFICATIONS

INPUT SENSITIVITY 500mV
 OUTPUT POWER 60W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.04% at 60W at 1kHz
 SIGNAL/NOISE RATIO 90dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB SUPPLY VOLTAGE = 35V
 SIZE 114 50 85mm

Price £14.40 + £1.16 VAT P&P free.

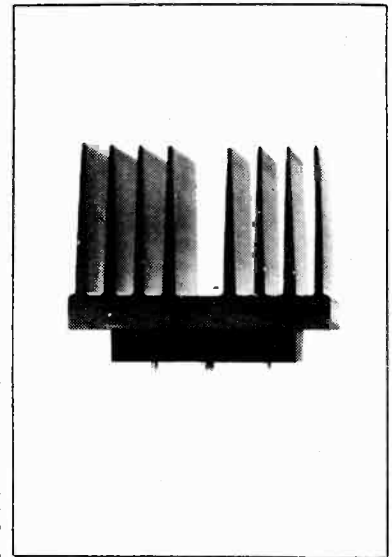

HY200 120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral heatsink — No external components

APPLICATIONS: Hi-Fi — Disco — Monitor — Power slave — Industrial — Public Address

SPECIFICATIONS

INPUT SENSITIVITY 500mV
 OUTPUT POWER 120W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.05% at 100W at 1kHz
 SIGNAL/NOISE RATIO 96 dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB SUPPLY VOLTAGE = 45V
 SIZE 114 100 85mm

Price £21.20 + £1.70 VAT P&P free.

HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.


FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components

APPLICATIONS: Public address — Disco — Power slave — Industrial

SPECIFICATIONS

OUTPUT POWER 240W RMS into 4 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.1% at 240W at 1kHz
 SIGNAL/NOISE RATIO 94dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB SUPPLY VOLTAGE = 45V
 INPUT SENSITIVITY 500mV SIZE 114x100x85mm

Price £29.25 + £2.34 VAT P&P free.

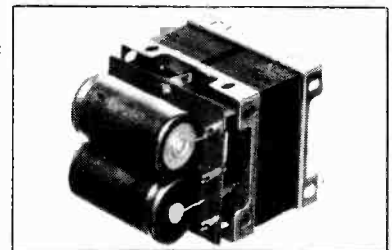

POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus £1.19 VAT P/P free
 PSU50 suitable for two HY50's £6.20 plus £1.55 VAT P/P free
 PSU70 suitable for two HY120's £12.50 plus £1.00 VAT P/P free
 PSU90 suitable for one HY200 £11.50 plus £0.92 VAT P/P free
 PSU180 suitable for two HY200's or one HY400 £21.00 plus £1.68 VAT P/P free

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please Supply _____
 Total Purchase Price _____
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number _____
 Name & Address _____
 Signature _____

Marshall's

A. Marshall (London) Ltd Dept: WW
 42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2
 Telex: 21492
 & 85 West Regent St Glasgow G2 2OD Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol BS16 2LX
 Tel: 0272 654201/2
 & 27 Rue Danton Issy Les Moulinaux Paris 92 Tel: 644 2356
 Catalogue price 25p Trade and export enquiries welcome

OUR RANGE COVERS OVER 7,000 ITEMS THE LARGEST SELECTION IN BRITAIN TOP 200 IC'S TTL, CMOS & LINEARS

CA3020A	1.80	CD4050	0.45	NE561	4.48	SN7448	0.90	SN74160	0.88
CA3028A	0.75	CD4510	1.25	NE565	4.48	SN7450	0.16	SN74161	0.88
CA3035	1.37	CD4511	1.94	SL1414	2.35	SN7451	0.16	SN74162	0.88
CA3046	0.70	CD4516	1.25	SL610C	2.35	SN7453	0.16	SN74163	0.88
CA3048	2.11	CD4518	1.87	SL611C	2.35	SN7454	0.16	SN74164	1.60
CA3052	1.62	CD4520	1.87	SL612C	2.35	SN7460	0.16	SN74165	1.60
CA3089E	1.96	LM301A	0.48	SL620C	3.50	SN7470	0.29	SN74167	3.30
CA3090Q	4.23	LM308	1.17	SL621C	3.50	SN7472	0.21	SN74174	0.99
CA3130	0.88	LM309K	1.88	SL6230	5.26	SN7473	0.31	SN74175	0.70
CD4000	0.18	LM380	98	SL640C	4.00	SN7474	0.31	SN74176	1.14
CD4001	0.18	LM381	2.07	SN7400	0.16	SN7475	0.45	SN74180	1.10
CD4002	0.18	LM702C	0.75	SN7401	0.16	SN7476	0.30	SN74181	1.95
CD4006	0.98	LM709	0.29	SN7401AN	0.29	SN7480	0.42	SN74190	1.86
CD4007	0.18	T099	0.38	SN7417	0.28	SN7481	1.00	SN74191	1.86
CD4008	0.82	8DIL	0.45	SN7403	0.16	SN7482	0.65	SN74192	1.15
CD4009	0.52	14DIL	0.38	SN7404	0.19	SN7483	0.82	SN74193	1.15
CD4010	0.52	LM710	0.47	SN7405	0.19	SN7484	0.95	SN74196	1.60
CD4011	0.18	LM723C	0.66	SN7406	0.36	SN7485	1.00	SN74197	1.58
CD4012	0.18	LM741C	0.40	SN7407	0.36	SN7486	0.29	SN74198	1.80
CD4013	0.45	T099	0.40	SN7408	0.19	SN7490	0.42	SN74199	1.80
CD4014	0.89	8DIL	0.45	SN7409	0.18	SN7491	0.75	SN76003N	2.92
CD4015	0.89	14DIL	0.38	SN7410	0.16	SN7492	0.45	SN76013N	1.95
CD4016	0.45	LM747	1.05	SN7411	0.20	SN7493	0.45	SN76023N	1.60
CD4017	0.88	LM748	0.88	SN7412	0.22	SN7494	0.75	SN76033N	2.92
CD4018	0.88	8DIL	0.44	SN7413	0.28	SN7495	0.68	TAA263	1.20
CD4019	0.52	14DIL	0.41	SN7416	0.28	SN7496	0.68	TAA300	1.84
CD4020	0.98	LM7900	0.61	SN7417	0.28	SN74107	1.10	TAA350A	2.10
CD4021	0.88	LM7805	1.88	SN7420	0.16	SN74107	0.30	TAA550	0.32
CD4022	0.85	LM7812	1.99	SN7423	0.23	SN74118	0.85	TAA611C	2.18
CD4023	0.18	LM7815	1.99	SN7425	0.23	SN74119	1.75	TAA621	2.02
CD4024	0.72	LM7824	1.99	SN7427	0.23	SN74121	0.32	TAA661B	1.03
CD4025	0.19	MC1303L	1.50	SN7430	0.15	SN74122	0.42	TBA641B	2.25
CD4027	0.41	MC1303	2.50	SN7432	0.22	SN74123	0.65	TBA651	1.68
CD4028	0.83	MC1330P	0.90	SN7437	0.28	SN74141	0.75	TBA800	0.89
CD4029	1.06	MC1351P	0.80	SN7438	0.28	SN74145	0.72	TBA810	0.98
CD4030	0.52	MC1466L	3.50	SN7440	0.16	SN74150	1.20	TBA820	0.80
CD4031	0.98	MC1469R	2.75	SN7441AN	0.68	SN74151	0.68	TBA920	1.79
CD4037	0.88	MC14553	4.07	SN7442	0.65	SN74153	0.68	14DILSKT	0.12
CD4041	0.70	NE555V	4.70	SN7445	0.78	SN74154	1.20	16DILSKT	0.13
CD4042	1.83	NE565	1.30	SN7446	0.84	SN74155	0.78		
CD4049	0.45	NE560	4.48	SN7447	0.80	SN74157	0.76		

LONDON, GLASGOW, PARIS — AND NOW BRISTOL IT'S OUR SERVICE THAT MAKES US GROW

POPULAR SEMICONDUCTORS

2N696	0.22	2N3906	0.19	AFJ39	0.65	BD139	0.71	MPSA56	0.31
2N697	0.16	2N4037	0.42	AFJ239	0.65	BD140	0.87	OC2B	1.48
2N698	0.82	2N4036	0.67	AFJ240	0.90	BF115	0.29	OC32	1.16
2N699	0.59	2N4058	0.18	AFJ279	0.70	BF117	0.55	OC42	0.50
2N706	0.14	2N4062	0.15	AFJ280	0.79	BF154	0.20	OC45	0.32
2N708	0.28	2N4289	0.34	AL102	1.00	BF159	0.27	TIP29A	0.49
2N916	0.14	2N4920	1.10	BC107	0.14	BF180	0.35	TIP29C	0.80
2N918	0.32	2N4921	0.83	BC108	0.14	BF181	0.36	TIP31A	0.62
2N1302	0.185	2N4923	1.00	BC109	0.14	BF184	0.30	TIP32A	0.74
2N1304	0.26	2N5245	0.29	BC147B	0.10	BF194	0.12	TIP33A	1.01
2N1306	0.47	2N5294	0.45	BC148B	0.09	BF195	0.12	TIP34A	1.51
2N1308	0.47	2N5296	0.48	BC149B	0.11	BF196	0.13	TIP35A	2.90
2N1711	0.27	2N5457	0.29	BC157A	0.16	BF197	0.15	TIP36A	3.70
2N2102	0.60	2N5458	0.26	BC158A	0.16	BF198	0.18	TIP41A	0.79
2N2147	0.78	2N5459	0.29	BC167B	0.15	BF244	0.21	TIP42A	0.90
2N2148	0.94	2N6027	0.45	BC168B	0.15	BF257	0.47	TIP295S	0.98
2N2218A	0.12	2N6062	0.74	BC169B	0.15	BF258	0.12	TIP305S	0.50
2N2219A	0.52	3N140	1.00	BC182	0.12	BF259	0.55	TIS43	0.28
2N2220	0.25	3N141	0.81	BC182L	0.12	BF561	0.27	ZTX300	0.13
2N2221	0.18	3N200	2.49	BC183	0.12	BF598	0.25	ZTX301	0.13
2N2222	0.20	40361	0.40	BC183L	0.13	BF939	0.24	ZTX500	0.15
2N2369	0.20	40362	0.45	BC184	0.13	BF979	0.24	ZTX501	0.13
2N2646	0.55	40406	0.44	BC184L	0.13	BF980	0.12	TIP34A	1.51
2N2904	0.40	40407	0.35	BC212A	0.16	BF930	0.34	1N914	0.35
2N2905	0.47	40408	0.50	BC212LA	0.16	BF984	0.30	1N3754	0.15
2N2906	0.33	40409	0.52	BC213LA	0.15	BF985	0.30	1N4007	0.10
2N2907	0.22	40410	0.52	BC214LB	0.18	BF988	0.30	1N4148	0.04
2N2924	0.20	40411	2.00	BC237B	0.16	BF950	0.30	1N4504	0.22
2N2926G	0.12	40592	0.74	BC238C	0.15	BF951	0.28	1N5408	0.30
2N3053	0.22	40595	0.84	BC239C	0.15	BF952	0.205	AA119	0.08
2N3054	0.60	40636	1.10	BC257A	0.16	BRY39	0.48	BA102	0.25
2N3055	0.65	40673	0.73	BC258R	0.16	ME0402	0.20	BA145	0.18
2N3391	0.28	AC126	0.20	BC259B	0.17	ME0412	0.18	BA154	0.12
2N3392	0.15	AC127	0.40	BC301	0.34	ME4102	0.11	BA155	0.12
2N3393	0.15	AC128	0.35	BC307B	0.17	MJ180	0.95	BB103B	0.23
2N3440	0.59	AC151	0.27	BC308A	0.15	NJ481	1.20	BR104B	0.45
2N3442	1.40	AC152	0.49	BC309C	0.20	MJ490	1.05	BY126	0.12
2N3638	0.15	AC153	0.35	BC327	0.23	MJ491	1.45	BY127	0.15
2N3702	0.12	AC176	0.41	BC32R	0.22	MJ2955	1.00	BY211	0.51
2N3703	0.13	AC187K	0.35	BC370	0.17	MJE340	0.48	BY212	0.51
2N3704	0.45	AC188K	0.49	BC371	0.22	MJE370	0.63	BY217	0.66
2N3706	0.15	AD143	0.68	BC372	0.18	MJE371	0.75	OAR1	0.18
2N3708	0.14	AD161	0.69	BD121	1.00	MJE520	0.60	OA90	0.06
2N3714	1.38	AD162	0.69	BD123	0.82	MJE521	0.70	OA91	0.06
2N3716	1.80	AF106	0.40	BD124	0.67	MJE2955	1.20	OA200	0.08
2N3771	2.20	AF109	0.40	BD131	0.40	MJE3055	0.75	BY164	0.57
2N3773	2.65	AF115	0.35	BD132	0.50	MPF113	0.47	SI2	diac
2N3789	2.06	AF116	0.35	BD133	0.21	MPF102	0.39	40669	1.50
2N3819	0.37	AF117	0.35	BD136	0.22	MPSA05	0.25	TC44	0.29
2N3820	0.29	AF118	0.35	BD137	0.24	MPSA06	0.31	CI06D	0.65
2N3904	0.19	AF124	0.30	BD138	0.26	MPSA55	0.21	OPR12	0.60

Prices correct at March 1976 but all exclusive of V A T Post & Packing 25p

TRANSFORMERS ALL EX-STOCK — SAME-DAY DESPATCH

MAINS ISOLATING 12 and/or 24-VOLT
 PRI 120/240V SEC 120/240V V.A.T 8% PRIMARY 220-240 VOLTS
 CENTRE TAPPED AND SCREENED

Ref. No.	VA (Watts)	£	P&P	Ref. No.	12v	24v	£	P&P
07-	20	£3.10	58	111	0.5	0.25	1.54	28
149	60	4.69	72	213	1.0	0.5	1.86	58
150	100	5.33	85	71	2	1	2.41	58
151	200	8.54	112	18	4	2	2.97	72
152	250	10.32	141	70	6	3	4.43	72
153	350	12.47	141	108	8	4	5.09	85
154	500	14.33	161	72	10	5	5.50	85
155	750	21.94	BRS	116	12	6	5.80	97
156	1000	30.51	BRS	17	16	8	7.48	97
157	1500	34.89	BRS	115	20	10	10.91	161
158	2000	38.92	BRS	187	30	15	14.20	141
159	3000	61.48	BRS	226	60	30	17.67	BRS


*115 or 240 sec only

50 VOLT RANGE
 SEC TAPS 0-19-25-33-40-50V

Ref. No.	Amps.	£	P&P
102	0.5	2.71	58
103	1.0	3.55	72
104	2.0	4.95	85
105	3.0	6.10	97
106	4.0	7.98	112
107	6.0	12.71	125
118	8.0	13.63	161
119	10.0	17.75	BRS

30 VOLT RANGE
 SEC. TAPS 0-12-15-20-25-30V

Ref. No.	Amps.	£	P&P
112	0.5	1.90	58
79	1.0	2.52	72
3	2.0	3.77	72
20	3.0	4.70	85
21	4.0	5.56	85
51	5.0	6.73	97
117	6.0	7.52	112
88	8.0	10.20	125
89			

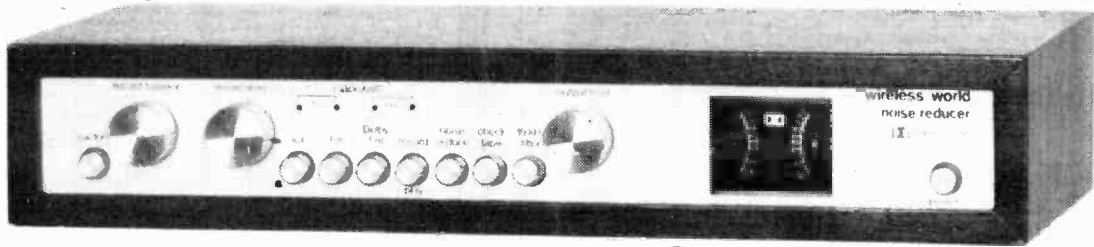

Wireless World DolbyTM noise reducer

Trademark of Dolby Laboratories Inc.

We are proud to announce the latest addition to our range of matching high fidelity units.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

Typical performance

Noise reduction: better than 9dB weighted

Clipping level: 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%.

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output.

Dynamic Range > 90dB

30mV sensitivity.

PRICE: £34.40 + VAT

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £1.80 + VAT***

Single channel plug-in DolbyTM PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components **Price £6.50 + VAT**

Single channel board with selected fet **Price £2.00 + VAT**

Gold plated edge connector **Price £1.27 + VAT***

Selected FET's **54p** each + VAT, **96p** + VAT for two, **£1.76** + VAT for four

Please add VAT at 25% unless marked thus*, when 8% applies
We guarantee full after sales technical and servicing facilities on all our kits



INTEGREX LTD.


Please send SAE for complete lists and specifications
**Portwood Industrial Estate, Church Gresley,
Burton-on-Trent, Staffs DE11 9PT
Tel. Swadlincote (0283 87) 5432. Telex 377106**

INTEGRIX

S-2020TA STEREO TUNER / AMPLIFIER KIT

SOLID MAHOGANY CABINET

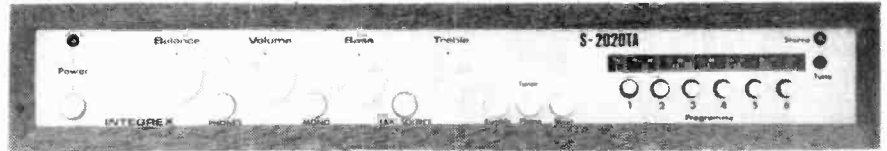A high-quality push-button FM Varicap Stereo Tuner combined with a 20W r.m.s. per channel Stereo Amplifier.




Brief Spec. Amplifier: Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc), THD less than 0.1% at 20W into 8 ohms. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section: uses Mullard LP1186 module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88—104MHz. 30dB mono S/N @ 1.8µV. THD typ. 0.4%

PRICE: £48.95 + VAT

NELSON-JONES STEREO FM TUNER KIT

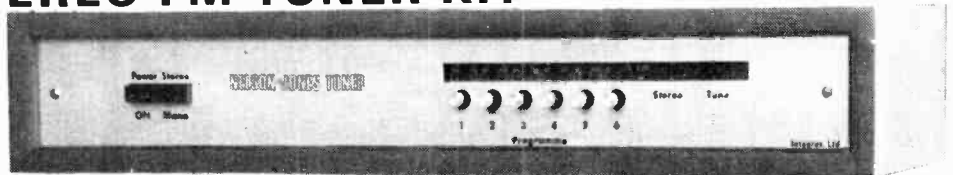A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter / dual IC IF amp.



Brief Spec. Tuning range 88—104MHz. 20dB mono quieting @ 0.75µV. Image rejection — 70dB. IF rejection—85dB. THD typically 0.4%. IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

Compare this spec. with tuners costing twice the price

Mono £26.31 + VAT

With ICPL Decoder £30.58 + VAT

**With Portus-Haywood Decoder
£32.81 + VAT**



Sens. 30dB S/N mono @ 1.8µV
THD typically 0.4%
Tuning range 88—104MHz
LED sig. strength and stereo indicator

STEREO MODULE TUNER KIT


A low-cost Stereo Tuner based on the Mullard LP1186 RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC

PRICE: Mono £25.55 + VAT

Stereo £28.65 + VAT

S-2020A AMPLIFIER KIT

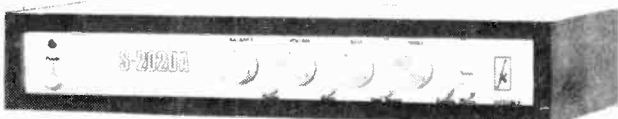Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring



Typ. Spec. 20+20W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

PRICE: £30.94 + VAT

ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS

BASIC NELSON-JONES TUNER KIT . . . £13.13 + VAT
BASIC MODULE TUNER KIT (Mono) . . . £13.25 + VAT
BASIC MODULE TUNER KIT (stereo) . . . £15.25 + VAT

PHASE-LOCKED IC DECODER KIT . . . £4.47 + VAT
PUSH-BUTTON UNIT . . . £3.50 + VAT

PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT . . . £7.93 + VAT

WW—042 FOR FURTHER DETAILS

<h3>TTLs by TEXAS</h3> <table border="0"> <tr><td>7400</td><td>13p</td><td>7486</td><td>30p</td></tr> <tr><td>74H00</td><td>20p</td><td>7489</td><td>270p</td></tr> <tr><td>7401</td><td>14p</td><td>7490</td><td>40p</td></tr> <tr><td>7402</td><td>14p</td><td>7491</td><td>75p</td></tr> <tr><td>7403</td><td>16p</td><td>7492</td><td>45p</td></tr> <tr><td>7404</td><td>16p</td><td>7493</td><td>40p</td></tr> <tr><td>74H04</td><td>22p</td><td>7494</td><td>75p</td></tr> <tr><td>7405</td><td>16p</td><td>7495</td><td>65p</td></tr> <tr><td>7406</td><td>38p</td><td>7496</td><td>78p</td></tr> <tr><td>7407</td><td>36p</td><td>7497</td><td>270p</td></tr> <tr><td>7408</td><td>16p</td><td>74100</td><td>108p</td></tr> <tr><td>7409</td><td>20p</td><td>74107</td><td>30p</td></tr> <tr><td>7410</td><td>13p</td><td>74118</td><td>84p</td></tr> <tr><td>74H10</td><td>20p</td><td>74121</td><td>30p</td></tr> <tr><td>7411</td><td>22p</td><td>74122</td><td>46p</td></tr> <tr><td>7412</td><td>23p</td><td>74123</td><td>68p</td></tr> <tr><td>7413</td><td>32p</td><td>74126</td><td>70p</td></tr> <tr><td>7414</td><td>60p</td><td>74132</td><td>70p</td></tr> <tr><td>7416</td><td>33p</td><td>74136</td><td>75p</td></tr> <tr><td>7417</td><td>30p</td><td>74141</td><td>65p</td></tr> <tr><td>7420</td><td>14p</td><td>74145</td><td>70p</td></tr> <tr><td>7421</td><td>40p</td><td>74148</td><td>160p</td></tr> <tr><td>7422</td><td>15p</td><td>74150</td><td>125p</td></tr> <tr><td>7423</td><td>34p</td><td>74151</td><td>72p</td></tr> <tr><td>7425</td><td>30p</td><td>74153</td><td>85p</td></tr> <tr><td>7427</td><td>37p</td><td>74154</td><td>150p</td></tr> <tr><td>7428</td><td>36p</td><td>74155</td><td>76p</td></tr> <tr><td>7430</td><td>14p</td><td>74156</td><td>76p</td></tr> <tr><td>7432</td><td>25p</td><td>74160</td><td>99p</td></tr> <tr><td>7437</td><td>25p</td><td>74161</td><td>99p</td></tr> <tr><td>7440</td><td>14p</td><td>74162</td><td>99p</td></tr> <tr><td>7441</td><td>65p</td><td>74163</td><td>99p</td></tr> <tr><td>7442</td><td>60p</td><td>74164</td><td>120p</td></tr> <tr><td>7447</td><td>75p</td><td>74166</td><td>126p</td></tr> <tr><td>7448</td><td>70p</td><td>74174</td><td>120p</td></tr> <tr><td>7450</td><td>15p</td><td>74175</td><td>85p</td></tr> <tr><td>7451</td><td>16p</td><td>74176</td><td>120p</td></tr> <tr><td>7453</td><td>16p</td><td>74177</td><td>100p</td></tr> <tr><td>7454</td><td>16p</td><td>74180</td><td>100p</td></tr> <tr><td>7460</td><td>15p</td><td>74181</td><td>298p</td></tr> <tr><td>7470</td><td>27p</td><td>74182</td><td>82p</td></tr> <tr><td>7472</td><td>25p</td><td>74185</td><td>135p</td></tr> <tr><td>7473</td><td>30p</td><td>74190</td><td>144p</td></tr> <tr><td>7474</td><td>30p</td><td>74191</td><td>144p</td></tr> <tr><td>7475</td><td>45p</td><td>74192</td><td>120p</td></tr> <tr><td>7476</td><td>30p</td><td>74193</td><td>120p</td></tr> <tr><td>7480</td><td>50p</td><td>74194</td><td>108p</td></tr> <tr><td>7481</td><td>95p</td><td>74195</td><td>75p</td></tr> <tr><td>7482</td><td>70p</td><td>74196</td><td>100p</td></tr> <tr><td>7483</td><td>80p</td><td>74197</td><td>100p</td></tr> <tr><td>7484</td><td>95p</td><td>74198</td><td>198p</td></tr> <tr><td>7485</td><td>120p</td><td>74199</td><td>180p</td></tr> </table>		7400	13p	7486	30p	74H00	20p	7489	270p	7401	14p	7490	40p	7402	14p	7491	75p	7403	16p	7492	45p	7404	16p	7493	40p	74H04	22p	7494	75p	7405	16p	7495	65p	7406	38p	7496	78p	7407	36p	7497	270p	7408	16p	74100	108p	7409	20p	74107	30p	7410	13p	74118	84p	74H10	20p	74121	30p	7411	22p	74122	46p	7412	23p	74123	68p	7413	32p	74126	70p	7414	60p	74132	70p	7416	33p	74136	75p	7417	30p	74141	65p	7420	14p	74145	70p	7421	40p	74148	160p	7422	15p	74150	125p	7423	34p	74151	72p	7425	30p	74153	85p	7427	37p	74154	150p	7428	36p	74155	76p	7430	14p	74156	76p	7432	25p	74160	99p	7437	25p	74161	99p	7440	14p	74162	99p	7441	65p	74163	99p	7442	60p	74164	120p	7447	75p	74166	126p	7448	70p	74174	120p	7450	15p	74175	85p	7451	16p	74176	120p	7453	16p	74177	100p	7454	16p	74180	100p	7460	15p	74181	298p	7470	27p	74182	82p	7472	25p	74185	135p	7473	30p	74190	144p	7474	30p	74191	144p	7475	45p	74192	120p	7476	30p	74193	120p	7480	50p	74194	108p	7481	95p	74195	75p	7482	70p	74196	100p	7483	80p	74197	100p	7484	95p	74198	198p	7485	120p	74199	180p	<h3>C-MOS I.C.s</h3> <table border="0"> <tr><td>CD4000AE</td><td>19p</td></tr> <tr><td>CD4001AE</td><td>19p</td></tr> <tr><td>CD4002AE</td><td>19p</td></tr> <tr><td>CD4007AE</td><td>19p</td></tr> <tr><td>CD4009AE</td><td>67p</td></tr> <tr><td>CD4011AE</td><td>19p</td></tr> <tr><td>CD4012AE</td><td>19p</td></tr> <tr><td>CD4013AE</td><td>19p</td></tr> <tr><td>CD4016AE</td><td>50p</td></tr> <tr><td>CD4017AE</td><td>120p</td></tr> <tr><td>CD4018AE</td><td>175p</td></tr> <tr><td>CD4020AE</td><td>250p</td></tr> <tr><td>CD4022AE</td><td>170p</td></tr> <tr><td>CD4023AE</td><td>19p</td></tr> <tr><td>CD4024AE</td><td>120p</td></tr> <tr><td>CD4025AE</td><td>19p</td></tr> <tr><td>CD4026AE</td><td>196p</td></tr> <tr><td>CD4027AE</td><td>75p</td></tr> <tr><td>CD4028AE</td><td>140p</td></tr> <tr><td>CD4029AE</td><td>175p</td></tr> <tr><td>CD4030AE</td><td>55p</td></tr> <tr><td>CD4034AE</td><td>137p</td></tr> <tr><td>CD4038AE</td><td>202p</td></tr> <tr><td>CD4046AE</td><td>140p</td></tr> <tr><td>CD4047AE</td><td>154p</td></tr> <tr><td>CD4049AE</td><td>63p</td></tr> <tr><td>CD4054AE</td><td>196p</td></tr> <tr><td>CD4055AE</td><td>196p</td></tr> <tr><td>CD4056AE</td><td>135p</td></tr> <tr><td>CD4060AE</td><td>229p</td></tr> <tr><td>CD4069AE</td><td>37p</td></tr> <tr><td>CD4071AE</td><td>27p</td></tr> <tr><td>CD4072AE</td><td>27p</td></tr> <tr><td>CD4081AE</td><td>19p</td></tr> <tr><td>CD4082AE</td><td>27p</td></tr> <tr><td>CD4510AE</td><td>130p</td></tr> <tr><td>CD4511AE</td><td>200p</td></tr> <tr><td>CD4518AE</td><td>100p</td></tr> <tr><td>CD4528AE</td><td>120p</td></tr> </table>		CD4000AE	19p	CD4001AE	19p	CD4002AE	19p	CD4007AE	19p	CD4009AE	67p	CD4011AE	19p	CD4012AE	19p	CD4013AE	19p	CD4016AE	50p	CD4017AE	120p	CD4018AE	175p	CD4020AE	250p	CD4022AE	170p	CD4023AE	19p	CD4024AE	120p	CD4025AE	19p	CD4026AE	196p	CD4027AE	75p	CD4028AE	140p	CD4029AE	175p	CD4030AE	55p	CD4034AE	137p	CD4038AE	202p	CD4046AE	140p	CD4047AE	154p	CD4049AE	63p	CD4054AE	196p	CD4055AE	196p	CD4056AE	135p	CD4060AE	229p	CD4069AE	37p	CD4071AE	27p	CD4072AE	27p	CD4081AE	19p	CD4082AE	27p	CD4510AE	130p	CD4511AE	200p	CD4518AE	100p	CD4528AE	120p	<h3>OP. AMPS</h3> <table border="0"> <tr><td>1458</td><td>Dual Op Amp Int. Comp</td><td>8 pin DIL</td><td>70p</td></tr> <tr><td>301A</td><td>Ext. Comp</td><td>8 pin DIL</td><td>36p</td></tr> <tr><td>3130</td><td>COSMOS/Bi-Polar MosFet</td><td>8 pin DIL</td><td>100p</td></tr> <tr><td>3900</td><td>Quad. Op. Amp</td><td>14 pin DIL</td><td>70p</td></tr> <tr><td>536T</td><td>FET Op Amp</td><td>TO-99</td><td>275p</td></tr> <tr><td>709</td><td>Ext. Comp.</td><td>8/14 pin DIL</td><td>30p</td></tr> <tr><td>741</td><td>Int. Comp.</td><td>8/14 pin DIL</td><td>22p</td></tr> <tr><td>747</td><td>Dual 741</td><td>14 pin DIL</td><td>70p</td></tr> <tr><td>748</td><td>Ext. Comp.</td><td>8/14 pin DIL</td><td>36p</td></tr> <tr><td>776</td><td>Programmable Cp. Amp</td><td>TO-5</td><td>140p</td></tr> </table>		1458	Dual Op Amp Int. Comp	8 pin DIL	70p	301A	Ext. Comp	8 pin DIL	36p	3130	COSMOS/Bi-Polar MosFet	8 pin DIL	100p	3900	Quad. Op. Amp	14 pin DIL	70p	536T	FET Op Amp	TO-99	275p	709	Ext. Comp.	8/14 pin DIL	30p	741	Int. Comp.	8/14 pin DIL	22p	747	Dual 741	14 pin DIL	70p	748	Ext. Comp.	8/14 pin DIL	36p	776	Programmable Cp. Amp	TO-5	140p	<h3>TRANSISTORS</h3> <table border="0"> <tr><td>AC125</td><td>16p</td><td>BFX85</td><td>25p</td><td>2N3439</td><td>67p</td></tr> <tr><td>AC126</td><td>12p</td><td>BFX86</td><td>25p</td><td>2N3442</td><td>140p</td></tr> <tr><td>AC127</td><td>12p</td><td>BFX87</td><td>20p</td><td>*2N3702</td><td>11p</td></tr> <tr><td>AC128</td><td>11p</td><td>BFX88</td><td>24p</td><td>*2N3703</td><td>11p</td></tr> <tr><td>AC141</td><td>18p</td><td>BFY50</td><td>16p</td><td>*2N3704</td><td>11p</td></tr> <tr><td>AC142</td><td>18p</td><td>BFY51</td><td>15p</td><td>*2N3705</td><td>11p</td></tr> <tr><td>AC176</td><td>11p</td><td>BFY52</td><td>16p</td><td>*2N3706</td><td>10p</td></tr> <tr><td>AC187</td><td>13p</td><td>BRV39</td><td>34p</td><td>*2N3707</td><td>11p</td></tr> <tr><td>AC188</td><td>12p</td><td>BSX19</td><td>16p</td><td>*2N3708</td><td>9p</td></tr> <tr><td>AD149</td><td>43p</td><td>BSX20</td><td>18p</td><td>*2N3709</td><td>9p</td></tr> <tr><td>AD161</td><td>36p</td><td>*BU105</td><td>140p</td><td>2N3773</td><td>220p</td></tr> <tr><td>AD162</td><td>36p</td><td>BU108</td><td>250p</td><td>2N3866</td><td>90p</td></tr> <tr><td>AF114</td><td>18p</td><td>*MJ340</td><td>45p</td><td>*2N3903</td><td>18p</td></tr> <tr><td>AF115</td><td>18p</td><td>MJ2955</td><td>70p</td><td>*2N3904</td><td>16p</td></tr> <tr><td>AF116</td><td>18p</td><td>MJE2955</td><td>99p</td><td>*2N3905</td><td>18p</td></tr> <tr><td>AF117</td><td>18p</td><td>MJE3055</td><td>65p</td><td>*2N3906</td><td>16p</td></tr> <tr><td>AF139</td><td>33p</td><td>*MPS534</td><td>18p</td><td>*2N4058</td><td>15p</td></tr> <tr><td>AF239</td><td>38p</td><td>*MPSA06</td><td>30p</td><td>*2N4059</td><td>10p</td></tr> <tr><td>BC107</td><td>9p</td><td>*MPSA12</td><td>50p</td><td>*2N4060</td><td>13p</td></tr> <tr><td>BC108</td><td>9p</td><td>*MPSA56</td><td>32p</td><td>*2N4123</td><td>18p</td></tr> <tr><td>BC109</td><td>10p</td><td>*MPSA06</td><td>62p</td><td>*2N4124</td><td>18p</td></tr> <tr><td>BC109C</td><td>12p</td><td>*MPSU56</td><td>78p</td><td>*2N4125</td><td>18p</td></tr> <tr><td>*BC117</td><td>22p</td><td>OC28</td><td>65p</td><td>*2N4126</td><td>18p</td></tr> <tr><td>*BC147</td><td>7p</td><td>OC35</td><td>55p</td><td>*2N4289</td><td>20p</td></tr> <tr><td>*BC148</td><td>7p</td><td>OC36</td><td>60p</td><td>2N4347</td><td>130p</td></tr> <tr><td>*BC149C</td><td>8p</td><td>*OC41/2</td><td>15p</td><td>2N4348</td><td>160p</td></tr> <tr><td>*BC157</td><td>11p</td><td>*OC45</td><td>15p</td><td>*2N4401</td><td>27p</td></tr> <tr><td>*BC158</td><td>10p</td><td>*OC71</td><td>20p</td><td>*2N4403</td><td>27p</td></tr> <tr><td>*BC159</td><td>11p</td><td>*TIP29A</td><td>40p</td><td>*2N5089</td><td>27p</td></tr> <tr><td>*BC169C</td><td>12p</td><td>*TIP30A</td><td>48p</td><td>*2N5401</td><td>50p</td></tr> <tr><td>BC177</td><td>18p</td><td>TIP31A</td><td>52p</td><td>40360</td><td>40p</td></tr> <tr><td>BC178</td><td>17p</td><td>TIP32A</td><td>58p</td><td>40361</td><td>38p</td></tr> <tr><td>BC179</td><td>18p</td><td>TIP33A</td><td>90p</td><td>40362</td><td>40p</td></tr> <tr><td>*BC182</td><td>11p</td><td>TIP34A</td><td>115p</td><td>40364</td><td>120p</td></tr> <tr><td>*BC183</td><td>10p</td><td>TIP35A</td><td>225p</td><td>40409</td><td>55p</td></tr> <tr><td>*BC184</td><td>11p</td><td>TIP36A</td><td>270p</td><td>40410</td><td>55p</td></tr> <tr><td>BC187</td><td>30p</td><td>1P41A</td><td>65p</td><td>40411</td><td>225p</td></tr> <tr><td>*BC212</td><td>11p</td><td>TIP42A</td><td>70p</td><td>40594</td><td>75p</td></tr> <tr><td>*BC213</td><td>10p</td><td>TIP2955</td><td>70p</td><td>40595</td><td>85p</td></tr> <tr><td>*BC214</td><td>14p</td><td>*ZTX108</td><td>10p</td><td></td><td></td></tr> <tr><td>*BC373</td><td>20p</td><td>*ZTX300</td><td>13p</td><td></td><td></td></tr> <tr><td>BC478</td><td>30p</td><td>*CX500</td><td>15p</td><td></td><td></td></tr> <tr><td>BCY70</td><td>18p</td><td>*CX502</td><td>18p</td><td></td><td></td></tr> <tr><td>BCY71</td><td>22p</td><td>2N697</td><td>13p</td><td></td><td></td></tr> <tr><td>BD123</td><td>100p</td><td>2N698</td><td>30p</td><td></td><td></td></tr> <tr><td>BD124</td><td>65p</td><td>2N706</td><td>12p</td><td></td><td></td></tr> <tr><td>BD131</td><td>36p</td><td>2N708</td><td>15p</td><td></td><td></td></tr> <tr><td>BD132</td><td>40p</td><td>2N918</td><td>40p</td><td></td><td></td></tr> <tr><td>*BD135</td><td>43p</td><td>2N930</td><td>18p</td><td></td><td></td></tr> <tr><td>*BD139</td><td>63p</td><td>2N1131</td><td>18p</td><td></td><td></td></tr> <tr><td>*BD140</td><td>70p</td><td>2N1132</td><td>18p</td><td></td><td></td></tr> <tr><td>BF115</td><td>22p</td><td>2N1304</td><td>21p</td><td></td><td></td></tr> <tr><td>BF167</td><td>23p</td><td>2N1305</td><td>21p</td><td></td><td></td></tr> <tr><td>BF170</td><td>23p</td><td>2N1306</td><td>28p</td><td></td><td></td></tr> <tr><td>BF173</td><td>25p</td><td>2N1307</td><td>28p</td><td></td><td></td></tr> <tr><td>BF177</td><td>26p</td><td>2N1308</td><td>28p</td><td></td><td></td></tr> <tr><td>BF178</td><td>28p</td><td>2N1309</td><td>28p</td><td></td><td></td></tr> <tr><td>BF179</td><td>33p</td><td>2N1613</td><td>20p</td><td></td><td></td></tr> <tr><td>BF180</td><td>33p</td><td>2N1711</td><td>20p</td><td></td><td></td></tr> <tr><td>BF181</td><td>33p</td><td>2N1893</td><td>30p</td><td></td><td></td></tr> <tr><td>BF182</td><td>33p</td><td>2N2219</td><td>20p</td><td></td><td></td></tr> <tr><td>BF184</td><td>22p</td><td>2N2220</td><td>19p</td><td></td><td></td></tr> <tr><td>BF185</td><td>22p</td><td>2N2221</td><td>20p</td><td></td><td></td></tr> <tr><td>*BF194</td><td>10p</td><td>2N2222</td><td>20p</td><td></td><td></td></tr> <tr><td>*BF195</td><td>9p</td><td>2N2369</td><td>18p</td><td></td><td></td></tr> <tr><td>*BF196</td><td>14p</td><td>2N2484</td><td>30p</td><td></td><td></td></tr> <tr><td>*BF197</td><td>15p</td><td>2N2904</td><td>20p</td><td></td><td></td></tr> <tr><td>BF200</td><td>32p</td><td>2N2905</td><td>20p</td><td></td><td></td></tr> <tr><td>BF257</td><td>32p</td><td>2N2906</td><td>20p</td><td></td><td></td></tr> <tr><td>BF258</td><td>36p</td><td>*2N2926R</td><td>7p</td><td></td><td></td></tr> <tr><td>*BF259</td><td>30p</td><td>*2N2926S</td><td>7p</td><td></td><td></td></tr> <tr><td>*BF260</td><td>30p</td><td>*2N2926O</td><td>8p</td><td></td><td></td></tr> <tr><td>*BF279</td><td>30p</td><td>*2N2926Y</td><td>9p</td><td></td><td></td></tr> <tr><td>*BF280</td><td>30p</td><td>*2N2926G</td><td>9p</td><td></td><td></td></tr> <tr><td>*BF288</td><td>30p</td><td>2N3053</td><td>18p</td><td></td><td></td></tr> <tr><td>*BF288</td><td>30p</td><td>2N3054</td><td>45p</td><td></td><td></td></tr> <tr><td>BFX30</td><td>30p</td><td>2N3055</td><td>50p</td><td></td><td></td></tr> <tr><td>BFX84</td><td>26p</td><td></td><td></td><td></td><td></td></tr> </table>		AC125	16p	BFX85	25p	2N3439	67p	AC126	12p	BFX86	25p	2N3442	140p	AC127	12p	BFX87	20p	*2N3702	11p	AC128	11p	BFX88	24p	*2N3703	11p	AC141	18p	BFY50	16p	*2N3704	11p	AC142	18p	BFY51	15p	*2N3705	11p	AC176	11p	BFY52	16p	*2N3706	10p	AC187	13p	BRV39	34p	*2N3707	11p	AC188	12p	BSX19	16p	*2N3708	9p	AD149	43p	BSX20	18p	*2N3709	9p	AD161	36p	*BU105	140p	2N3773	220p	AD162	36p	BU108	250p	2N3866	90p	AF114	18p	*MJ340	45p	*2N3903	18p	AF115	18p	MJ2955	70p	*2N3904	16p	AF116	18p	MJE2955	99p	*2N3905	18p	AF117	18p	MJE3055	65p	*2N3906	16p	AF139	33p	*MPS534	18p	*2N4058	15p	AF239	38p	*MPSA06	30p	*2N4059	10p	BC107	9p	*MPSA12	50p	*2N4060	13p	BC108	9p	*MPSA56	32p	*2N4123	18p	BC109	10p	*MPSA06	62p	*2N4124	18p	BC109C	12p	*MPSU56	78p	*2N4125	18p	*BC117	22p	OC28	65p	*2N4126	18p	*BC147	7p	OC35	55p	*2N4289	20p	*BC148	7p	OC36	60p	2N4347	130p	*BC149C	8p	*OC41/2	15p	2N4348	160p	*BC157	11p	*OC45	15p	*2N4401	27p	*BC158	10p	*OC71	20p	*2N4403	27p	*BC159	11p	*TIP29A	40p	*2N5089	27p	*BC169C	12p	*TIP30A	48p	*2N5401	50p	BC177	18p	TIP31A	52p	40360	40p	BC178	17p	TIP32A	58p	40361	38p	BC179	18p	TIP33A	90p	40362	40p	*BC182	11p	TIP34A	115p	40364	120p	*BC183	10p	TIP35A	225p	40409	55p	*BC184	11p	TIP36A	270p	40410	55p	BC187	30p	1P41A	65p	40411	225p	*BC212	11p	TIP42A	70p	40594	75p	*BC213	10p	TIP2955	70p	40595	85p	*BC214	14p	*ZTX108	10p			*BC373	20p	*ZTX300	13p			BC478	30p	*CX500	15p			BCY70	18p	*CX502	18p			BCY71	22p	2N697	13p			BD123	100p	2N698	30p			BD124	65p	2N706	12p			BD131	36p	2N708	15p			BD132	40p	2N918	40p			*BD135	43p	2N930	18p			*BD139	63p	2N1131	18p			*BD140	70p	2N1132	18p			BF115	22p	2N1304	21p			BF167	23p	2N1305	21p			BF170	23p	2N1306	28p			BF173	25p	2N1307	28p			BF177	26p	2N1308	28p			BF178	28p	2N1309	28p			BF179	33p	2N1613	20p			BF180	33p	2N1711	20p			BF181	33p	2N1893	30p			BF182	33p	2N2219	20p			BF184	22p	2N2220	19p			BF185	22p	2N2221	20p			*BF194	10p	2N2222	20p			*BF195	9p	2N2369	18p			*BF196	14p	2N2484	30p			*BF197	15p	2N2904	20p			BF200	32p	2N2905	20p			BF257	32p	2N2906	20p			BF258	36p	*2N2926R	7p			*BF259	30p	*2N2926S	7p			*BF260	30p	*2N2926O	8p			*BF279	30p	*2N2926Y	9p			*BF280	30p	*2N2926G	9p			*BF288	30p	2N3053	18p			*BF288	30p	2N3054	45p			BFX30	30p	2N3055	50p			BFX84	26p					<h3>DIODES</h3> <table border="0"> <tr><td colspan="2">SIGNAL*</td><td></td></tr> <tr><td>0A47</td><td>7p</td><td></td></tr> <tr><td>0A70</td><td>9p</td><td></td></tr> <tr><td>0A81</td><td>8p</td><td></td></tr> <tr><td>0A85</td><td>10p</td><td></td></tr> <tr><td>0A90</td><td>7p</td><td></td></tr> <tr><td>0A91</td><td>7p</td><td></td></tr> <tr><td>0A95</td><td>8p</td><td></td></tr> <tr><td>0A200</td><td>8p</td><td></td></tr> <tr><td>0A202</td><td>10p</td><td></td></tr> <tr><td>IN914</td><td>4p</td><td></td></tr> <tr><td>IN916</td><td>4p</td><td></td></tr> <tr><td>IN4148</td><td>4p</td><td></td></tr> <tr><td colspan="2">RECTIFIER</td><td></td></tr> <tr><td>*BY100</td><td>25p</td><td></td></tr> <tr><td>*BY126</td><td>12p</td><td></td></tr> <tr><td>*BY127</td><td>12p</td><td></td></tr> <tr><td>IN4001</td><td>5p</td><td></td></tr> <tr><td>IN4002</td><td>5p</td><td></td></tr> <tr><td>IN4004</td><td>6p</td><td></td></tr> <tr><td>IN4005</td><td>6p</td><td></td></tr> <tr><td>IN4007</td><td>7p</td><td></td></tr> <tr><td colspan="2">ZENER</td><td></td></tr> <tr><td colspan="3">3.3V to 33V*</td></tr> <tr><td>*400mW</td><td>9p</td><td></td></tr> <tr><td>*1W</td><td>18p</td><td></td></tr> <tr><td colspan="2">TUNNEL</td><td></td></tr> <tr><td>AEY11</td><td>70p</td><td></td></tr> <tr><td colspan="2">VARICAP</td><td></td></tr> <tr><td>*MB105</td><td>25p</td><td></td></tr> <tr><td colspan="2">NOISE</td><td></td></tr> <tr><td>*Z5J</td><td>110p</td><td></td></tr> <tr><td colspan="2">BRIDGE RECTIFIERS</td><td></td></tr> <tr><td>*2SA100V</td><td>20p</td><td></td></tr> <tr><td>*1A 50V</td><td>20p</td><td></td></tr> <tr><td>*1A 100V</td><td>22p</td><td></td></tr> <tr><td>*1A 400V</td><td>25p</td><td></td></tr> <tr><td>*1A 600V</td><td>30p</td><td></td></tr> <tr><td>*2A 50V</td><td>30p</td><td></td></tr> <tr><td>*2A 100V</td><td>35p</td><td></td></tr> <tr><td>*2A 400V</td><td>45p</td><td></td></tr> <tr><td>*4A 100V</td><td>60p</td><td></td></tr> <tr><td>6A 100V</td><td>65p</td><td></td></tr> <tr><td colspan="2">TRIACS</td><td></td></tr> <tr><td colspan="3">Amp Volts</td></tr> <tr><td>3 400</td><td>120p</td><td></td></tr> <tr><td>6 400</td><td>150p</td><td></td></tr> <tr><td>6 500</td><td>180p</td><td></td></tr> <tr><td>10 400</td><td>185p</td><td></td></tr> <tr><td>10 500</td><td>195p</td><td></td></tr> <tr><td>15 400</td><td>210p</td><td></td></tr> <tr><td>15 500</td><td>250p</td><td></td></tr> <tr><td>40 430</td><td>99p</td><td></td></tr> <tr><td>40 486</td><td>99p</td><td></td></tr> <tr><td>40 669</td><td>99p</td><td></td></tr> <tr><td>DIAC</td><td></td><td></td></tr> <tr><td>BR100</td><td>25p</td><td></td></tr> </table>		SIGNAL*			0A47	7p		0A70	9p		0A81	8p		0A85	10p		0A90	7p		0A91	7p		0A95	8p		0A200	8p		0A202	10p		IN914	4p		IN916	4p		IN4148	4p		RECTIFIER			*BY100	25p		*BY126	12p		*BY127	12p		IN4001	5p		IN4002	5p		IN4004	6p		IN4005	6p		IN4007	7p		ZENER			3.3V to 33V*			*400mW	9p		*1W	18p		TUNNEL			AEY11	70p		VARICAP			*MB105	25p		NOISE			*Z5J	110p		BRIDGE RECTIFIERS			*2SA100V	20p		*1A 50V	20p		*1A 100V	22p		*1A 400V	25p		*1A 600V	30p		*2A 50V	30p		*2A 100V	35p		*2A 400V	45p		*4A 100V	60p		6A 100V	65p		TRIACS			Amp Volts			3 400	120p		6 400	150p		6 500	180p		10 400	185p		10 500	195p		15 400	210p		15 500	250p		40 430	99p		40 486	99p		40 669	99p		DIAC			BR100	25p	
7400	13p	7486	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
74H00	20p	7489	270p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7401	14p	7490	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7402	14p	7491	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7403	16p	7492	45p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7404	16p	7493	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
74H04	22p	7494	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7405	16p	7495	65p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7406	38p	7496	78p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7407	36p	7497	270p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7408	16p	74100	108p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7409	20p	74107	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7410	13p	74118	84p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
74H10	20p	74121	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7411	22p	74122	46p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7412	23p	74123	68p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7413	32p	74126	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7414	60p	74132	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7416	33p	74136	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7417	30p	74141	65p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7420	14p	74145	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7421	40p	74148	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7422	15p	74150	125p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7423	34p	74151	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7425	30p	74153	85p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7427	37p	74154	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7428	36p	74155	76p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7430	14p	74156	76p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7432	25p	74160	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7437	25p	74161	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7440	14p	74162	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7441	65p	74163	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7442	60p	74164	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7447	75p	74166	126p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7448	70p	74174	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7450	15p	74175	85p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7451	16p	74176	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7453	16p	74177	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7454	16p	74180	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7460	15p	74181	298p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7470	27p	74182	82p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7472	25p	74185	135p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7473	30p	74190	144p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7474	30p	74191	144p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7475	45p	74192	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7476	30p	74193	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7480	50p	74194	108p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7481	95p	74195	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7482	70p	74196	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7483	80p	74197	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7484	95p	74198	198p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7485	120p	74199	180p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
CD4000AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4001AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4002AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4007AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4009AE	67p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4011AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4012AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4013AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4016AE	50p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4017AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4018AE	175p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4020AE	250p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4022AE	170p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4023AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4024AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4025AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4026AE	196p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4027AE	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4028AE	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4029AE	175p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4030AE	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4034AE	137p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4038AE	202p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4046AE	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4047AE	154p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4049AE	63p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4054AE	196p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4055AE	196p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4056AE	135p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4060AE	229p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4069AE	37p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4071AE	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4072AE	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4081AE	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4082AE	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4510AE	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4511AE	200p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4518AE	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
CD4528AE	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
1458	Dual Op Amp Int. Comp	8 pin DIL	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
301A	Ext. Comp	8 pin DIL	36p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
3130	COSMOS/Bi-Polar MosFet	8 pin DIL	100p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
3900	Quad. Op. Amp	14 pin DIL	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
536T	FET Op Amp	TO-99	275p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
709	Ext. Comp.	8/14 pin DIL	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
741	Int. Comp.	8/14 pin DIL	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
747	Dual 741	14 pin DIL	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
748	Ext. Comp.	8/14 pin DIL	36p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
776	Programmable Cp. Amp	TO-5	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
AC125	16p	BFX85	25p	2N3439	67p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC126	12p	BFX86	25p	2N3442	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC127	12p	BFX87	20p	*2N3702	11p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC128	11p	BFX88	24p	*2N3703	11p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC141	18p	BFY50	16p	*2N3704	11p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC142	18p	BFY51	15p	*2N3705	11p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC176	11p	BFY52	16p	*2N3706	10p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC187	13p	BRV39	34p	*2N3707	11p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AC188	12p	BSX19	16p	*2N3708	9p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AD149	43p	BSX20	18p	*2N3709	9p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AD161	36p	*BU105	140p	2N3773	220p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AD162	36p	BU108	250p	2N3866	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AF114	18p	*MJ340	45p	*2N3903	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AF115	18p	MJ2955	70p	*2N3904	16p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AF116	18p	MJE2955	99p	*2N3905	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AF117	18p	MJE3055	65p	*2N3906	16p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AF139	33p	*MPS534	18p	*2N4058	15p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
AF239	38p	*MPSA06	30p	*2N4059	10p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC107	9p	*MPSA12	50p	*2N4060	13p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC108	9p	*MPSA56	32p	*2N4123	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC109	10p	*MPSA06	62p	*2N4124	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC109C	12p	*MPSU56	78p	*2N4125	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC117	22p	OC28	65p	*2N4126	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC147	7p	OC35	55p	*2N4289	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC148	7p	OC36	60p	2N4347	130p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC149C	8p	*OC41/2	15p	2N4348	160p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC157	11p	*OC45	15p	*2N4401	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC158	10p	*OC71	20p	*2N4403	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC159	11p	*TIP29A	40p	*2N5089	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC169C	12p	*TIP30A	48p	*2N5401	50p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC177	18p	TIP31A	52p	40360	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC178	17p	TIP32A	58p	40361	38p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC179	18p	TIP33A	90p	40362	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC182	11p	TIP34A	115p	40364	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC183	10p	TIP35A	225p	40409	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC184	11p	TIP36A	270p	40410	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
BC187	30p	1P41A	65p	40411	225p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC212	11p	TIP42A	70p	40594	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC213	10p	TIP2955	70p	40595	85p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
*BC214	14p	*ZTX108	10p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BC373	20p	*ZTX300	13p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BC478	30p	*CX500	15p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BCY70	18p	*CX502	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BCY71	22p	2N697	13p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BD123	100p	2N698	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BD124	65p	2N706	12p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BD131	36p	2N708	15p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BD132	40p	2N918	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BD135	43p	2N930	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BD139	63p	2N1131	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BD140	70p	2N1132	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF115	22p	2N1304	21p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF167	23p	2N1305	21p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF170	23p	2N1306	28p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF173	25p	2N1307	28p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF177	26p	2N1308	28p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF178	28p	2N1309	28p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF179	33p	2N1613	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF180	33p	2N1711	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF181	33p	2N1893	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF182	33p	2N2219	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF184	22p	2N2220	19p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF185	22p	2N2221	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF194	10p	2N2222	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF195	9p	2N2369	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF196	14p	2N2484	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF197	15p	2N2904	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF200	32p	2N2905	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF257	32p	2N2906	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BF258	36p	*2N2926R	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF259	30p	*2N2926S	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF260	30p	*2N2926O	8p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF279	30p	*2N2926Y	9p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF280	30p	*2N2926G	9p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF288	30p	2N3053	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*BF288	30p	2N3054	45p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BFX30	30p	2N3055	50p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
BFX84	26p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
SIGNAL*																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0A47	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A70	9p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A81	8p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A85	10p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A90	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A91	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A95	8p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A200	8p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0A202	10p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN914	4p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN916	4p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN4148	4p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
RECTIFIER																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
*BY100	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*BY126	12p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*BY127	12p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN4001	5p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN4002	5p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN4004	6p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN4005	6p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
IN4007	7p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
ZENER																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
3.3V to 33V*																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
*400mW	9p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*1W	18p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
TUNNEL																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
AEY11	70p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
VARICAP																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
*MB105	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
NOISE																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
*Z5J	110p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
BRIDGE RECTIFIERS																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
*2SA100V	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*1A 50V	20p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*1A 100V	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*1A 400V	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*1A 600V	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2A 50V	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2A 100V	35p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2A 400V	45p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*4A 100V	60p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
6A 100V	65p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
TRIACS																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
Amp Volts																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
3 400	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
6 400	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
6 500	180p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
10 400	185p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
10 500	195p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
15 400	210p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
15 500	250p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
40 430	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
40 486	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
40 669	99p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
DIAC																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
BR100	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
<h3>MEMORIES</h3> <table border="0"> <tr><td>2602B</td><td>1924 bit RAM</td><td>£2.75</td></tr> <tr><td>2513(UC)</td><td>Character Generator</td><td>£10.00</td></tr> <tr><td>2513(LC)</td><td>Character Generator</td><td>£10.00</td></tr> </table>		2602B	1924 bit RAM	£2.75	2513(UC)	Character Generator	£10.00	2513(LC)	Character Generator	£10.00	<h3>OPTO-ELECTRONICS</h3> <table border="0"> <tr><td>Phototransistors</td><td>I.D.Rs</td><td></td></tr> <tr><td>OCPT70</td><td>ORP12</td><td>50p</td></tr> <tr><td>OCPT71</td><td>ORP60</td><td>75p</td></tr> <tr><td>2N5777</td><td>ORP61</td><td>75p</td></tr> </table>		Phototransistors	I.D.Rs		OCPT70	ORP12	50p	OCPT71	ORP60	75p	2N5777	ORP61	75p	<h3>MOSFETS</h3> <table border="0"> <tr><td>*BF244</td><td>25p</td></tr> <tr><td>*MPF102</td><td>30p</td></tr> <tr><td>*MPF103</td><td>30p</td></tr> <tr><td>*MPF104</td><td>30p</td></tr> <tr><td>*MPF105</td><td>30p</td></tr> <tr><td>*2N3819</td><td>22p</td></tr> <tr><td>*2N3820</td><td>57p</td></tr> <tr><td>*2N3823</td><td>50p</td></tr> <tr><td>*2N5457</td><td>30p</td></tr> <tr><td>*2N5458</td><td>30p</td></tr> <tr><td>*2N5459</td><td>30p</td></tr> </table>		*BF244	25p	*MPF102	30p	*MPF103	30p	*MPF104	30p	*MPF105	30p	*2N3819	22p	*2N3820	57p	*2N3823	50p	*2N5457	30p	*2N5458	30p	*2N5459	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
2602B	1924 bit RAM	£2.75																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
2513(UC)	Character Generator	£10.00																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
2513(LC)	Character Generator	£10.00																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
Phototransistors	I.D.Rs																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
OCPT70	ORP12	50p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
OCPT71	ORP60	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
2N5777	ORP61	75p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
*BF244	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*MPF102	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*MPF103	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*MPF104	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*MPF105	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N3819	22p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N3820	57p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N3823	50p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N5457	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N5458	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N5459	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
<h3>MULLARD MODULE</h3> <p>LP1186 Varicap FM Tuner £6.50</p>		<h3>SEVEN SEGMENT DISPLAYS</h3> <table border="0"> <tr><td>3015F</td><td>Minitron 0.3 in</td><td>120p</td></tr> <tr><td>DL704</td><td>Com. Cathode 0.3 in</td><td>150p</td></tr> <tr><td>DL707</td><td>Com. Anode 0.3 in</td><td>150p</td></tr> <tr><td>DL747</td><td>Com. Anode 0.6 in</td><td>225p</td></tr> </table>		3015F	Minitron 0.3 in	120p	DL704	Com. Cathode 0.3 in	150p	DL707	Com. Anode 0.3 in	150p	DL747	Com. Anode 0.6 in	225p	<h3>SCR-THYRISTORS</h3> <table border="0"> <tr><td>1A 50V</td><td>TO5</td><td>40p</td><td>4A/400V</td><td>Plastic</td><td>55p</td></tr> <tr><td>1A100V</td><td>TO5</td><td>42p</td><td>*MCR101</td><td></td><td></td></tr> <tr><td>1A400V</td><td>TO5</td><td>45p</td><td>0.5A/15V</td><td>TO-92</td><td>25p</td></tr> <tr><td>1A600V</td><td>TO5</td><td>70p</td><td>2N3525</td><td></td><td></td></tr> <tr><td>3A100V</td><td>Stud</td><td>49p</td><td>5A/400V</td><td>TO-66</td><td>90p</td></tr> <tr><td>3A400V</td><td>Stud</td><td>75p</td><td>2N4444</td><td></td><td></td></tr> <tr><td>7A100V</td><td>TO5+HS</td><td>84p</td><td>8A/600V</td><td>Plastic</td><td>185p</td></tr> <tr><td>7A400V</td><td>TO5+HS</td><td>90p</td><td>*2N5060</td><td></td><td></td></tr> <tr><td>8A 50V</td><td>Plastic</td><td>130p</td><td>0.8A/30V</td><td>TO-92</td><td>34p</td></tr> <tr><td>12A400V</td><td>Plastic</td><td>160p</td><td>*2N5062</td><td></td><td></td></tr> <tr><td>16A100V</td><td>Plastic</td><td>160p</td><td>0.8A/100V</td><td>TO-92</td><td>37p</td></tr> <tr><td>16A400V</td><td>Plastic</td><td>180p</td><td>*2N5064</td><td></td><td></td></tr> <tr><td>16A600V</td><td>Plastic</td><td>220p</td><td>0.8A/200V</td><td>TO-92</td><td>40p</td></tr> </table>		1A 50V	TO5	40p	4A/400V	Plastic	55p	1A100V	TO5	42p	*MCR101			1A400V	TO5	45p	0.5A/15V	TO-92	25p	1A600V	TO5	70p	2N3525			3A100V	Stud	49p	5A/400V	TO-66	90p	3A400V	Stud	75p	2N4444			7A100V	TO5+HS	84p	8A/600V	Plastic	185p	7A400V	TO5+HS	90p	*2N5060			8A 50V	Plastic	130p	0.8A/30V	TO-92	34p	12A400V	Plastic	160p	*2N5062			16A100V	Plastic	160p	0.8A/100V	TO-92	37p	16A400V	Plastic	180p	*2N5064			16A600V	Plastic	220p	0.8A/200V	TO-92	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																															
3015F	Minitron 0.3 in	120p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
DL704	Com. Cathode 0.3 in	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
DL707	Com. Anode 0.3 in	150p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
DL747	Com. Anode 0.6 in	225p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
1A 50V	TO5	40p	4A/400V	Plastic	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
1A100V	TO5	42p	*MCR101																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
1A400V	TO5	45p	0.5A/15V	TO-92	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
1A600V	TO5	70p	2N3525																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
3A100V	Stud	49p	5A/400V	TO-66	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
3A400V	Stud	75p	2N4444																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
7A100V	TO5+HS	84p	8A/600V	Plastic	185p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
7A400V	TO5+HS	90p	*2N5060																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
8A 50V	Plastic	130p	0.8A/30V	TO-92	34p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
12A400V	Plastic	160p	*2N5062																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
16A100V	Plastic	160p	0.8A/100V	TO-92	37p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
16A400V	Plastic	180p	*2N5064																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
16A600V	Plastic	220p	0.8A/200V	TO-92	40p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
<h3>LOW PROFILE DIL SOCKETS BY TEXAS</h3> <p>8 pin 13p, 14 pin 14p, 16 pin 15p, 24 pin 50p. INSULATORS Mica + 2 Bushes for TO3 & TO66 5p</p>		<h3>OPTO-ISOLATORS</h3> <table border="0"> <tr><td>Phototransistor TIL 112 (IL 12)</td><td>6 pin DIL</td><td>140p</td></tr> <tr><td>Photodarlington: ILCA-55</td><td>6 pin DIL</td><td>250p</td></tr> </table>		Phototransistor TIL 112 (IL 12)	6 pin DIL	140p	Photodarlington: ILCA-55	6 pin DIL	250p	<h3>UJTs</h3> <table border="0"> <tr><td>*1T543</td><td>27p</td></tr> <tr><td>*2N1260</td><td>80p</td></tr> <tr><td>*2N2646</td><td>38p</td></tr> <tr><td>*2N4871</td><td>30p</td></tr> </table>		*1T543	27p	*2N1260	80p	*2N2646	38p	*2N4871	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
Phototransistor TIL 112 (IL 12)	6 pin DIL	140p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
Photodarlington: ILCA-55	6 pin DIL	250p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
*1T543	27p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N1260	80p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N2646	38p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
*2N4871	30p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
<h3>VOLTAGE REGULATORS</h3> <p>FIXED - Plastic 3 Terminals</p> <table border="0"> <tr><td>1 Amp Positive</td><td>1 Amp Negative</td></tr> <tr><td>5V 7805</td><td>5V 7905</td></tr> <tr><td>12V 7812</td><td>12V 7912</td></tr> <tr><td>15V 7815</td><td>15V 7915</td></tr> <tr><td>18V 7818</td><td>18V 7918</td></tr> <tr><td>24V 7824</td><td>24V 7924</td></tr> </table> <p>LM309K 1 Amp 5V TO3 140p</p>		1 Amp Positive	1 Amp Negative	5V 7805	5V 7905	12V 7812	12V 7912	15V 7815	15V 7915	18V 7818	18V 7918	24V 7824	24V 7924	<h3>DRIVERS</h3> <table border="0"> <tr><td>75491</td><td>Quad Segment Driver</td><td>14 pin DIL</td><td>72p</td></tr> <tr><td>75492</td><td>Hex Digit Driver</td><td>14 pin DIL</td><td>90p</td></tr> </table>		75491	Quad Segment Driver	14 pin DIL	72p	75492	Hex Digit Driver	14 pin DIL	90p	<h3>PUJTs</h3> <table border="0"> <tr><td>*2N6027</td><td>48p</td></tr> </table>		*2N6027	48p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																			
1 Amp Positive	1 Amp Negative																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
5V 7805	5V 7905																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
12V 7812	12V 7912																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
15V 7815	15V 7915																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
18V 7818	18V 7918																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
24V 7824	24V 7924																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
75491	Quad Segment Driver	14 pin DIL	72p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
75492	Hex Digit Driver	14 pin DIL	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
*2N6027	48p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
<h3>DUAL VOLTAGE REGULATOR</h3> <p>1468 ±15V 100mA 16 pin DIL 300p. (Adjustable by resistors from ± 8V min. to ± 20V max.)</p>		<h3>SCR-THYRISTORS</h3> <p>BT106 1A/700V Stud 140p C106D 4A/400V Plastic 55p</p>		<h3>DIAC</h3> <table border="0"> <tr><td>BR100</td><td>25p</td></tr> </table>		BR100	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
BR100	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
<h3>VARIABLE VOLTAGE REGULATOR</h3> <p>723 2V to 37V 150mA 14 pin DIL 45p Basic Data Sheets on Vol. Regs. at 10p each + SAE</p>		<h3>SCR-THYRISTORS</h3> <table border="0"> <tr><td>1A 50V</td><td>TO5</td><td>40p</td><td>4A/400V</td><td>Plastic</td><td>55p</td></tr> <tr><td>1A100V</td><td>TO5</td><td>42p</td><td>*MCR101</td><td></td><td></td></tr> <tr><td>1A400V</td><td>TO5</td><td>45p</td><td>0.5A/15V</td><td>TO-92</td><td>25p</td></tr> <tr><td>1A600V</td><td>TO5</td><td>70p</td><td>2N3525</td><td></td><td></td></tr> <tr><td>3A100V</td><td>Stud</td><td>49p</td><td>5A/400V</td><td>TO-66</td><td>90p</td></tr> <tr><td>3A400V</td><td>Stud</td><td>75p</td><td>2N4444</td><td></td><td></td></tr> </table>		1A 50V	TO5	40p	4A/400V	Plastic	55p	1A100V	TO5	42p	*MCR101			1A400V	TO5	45p	0.5A/15V	TO-92	25p	1A600V	TO5	70p	2N3525			3A100V	Stud	49p	5A/400V	TO-66	90p	3A400V	Stud	75p	2N4444																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
1A 50V	TO5	40p	4A/400V	Plastic	55p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
1A100V	TO5	42p	*MCR101																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
1A400V	TO5	45p	0.5A/15V	TO-92	25p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
1A600V	TO5	70p	2N3525																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
3A100V	Stud	49p	5A/400V	TO-66	90p																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
3A400V	Stud	75p	2N4444																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

B-P-P Packs

Originated in 1959 by the Company's managing director, his were the first semi-conductor and component packs to be marketed in this country, and indeed, the company's name grew out of "British Industrial Pre-Pack Components". Today, Bi-Pre-Pak continues to occupy a position of pre-eminence in the supply of packs as well as a vastly extended range of products detailed in our latest 24-page A.4 size free catalogue. Send 10p stamped large addressed envelope for your copy by return.

IT'S ALL IN OUR FREE CATALOGUE

Component Packs

- CP1 150 Capacitors mixed bag of paper, silver mica electrolytic's etc. Approx. quantity counted by weight (post and packing) **60p**
- CP2 200 Resistors mixed bag of different types, values, wattages etc. Approx. quantity counted by weight **60p**
- CP3 40 Wirewound resistors, mixed types, values and wattages **60p**
- CP4 12 Potentiometers pre-sets w/wound carbon etc. Mixed types and values **60p**
- CP5 5 Earphones, single low impedance for transistor radios, cassettes etc. Less plugs for suitable plugs see PAKs CP9 and CP10 **60p**
- CP6 50 10-5 mounting pads, fits between transistor and board for that pin finish **60p**
- CP8 500 Cable clips for G.P.O. 1/8" dia. cable. Nylon with hardened steel pin (probably tungsten) per sealed box of 500 **60p**
- CP9 5 3.5mm plugs, miniature jack, to fit earphones in PAK CP5 **60p**
- CP10 5 2.5mm sub-miniature jack plugs, to fit earphones in PAK CP5 **60p**
- CP11 6 Screwdrivers, 1 x mains neon tester, 5 x grub screwdrivers **60p**
- CP12 10 Reed relay inserts, 1" long 1/4" dia. These will operate from an external magnet or coil. For magnets see PAK CP13 **60p**
- CP13 10 Magnets of various sizes for operating reed switches on PAK CP12. Ideal for burglar alarms on doors and windows etc. **60p**
- CP14 40 Potentiometers, pre-sets, wirewounds, carbons, dual gangs, with and without switches etc. Mixed values and wattages **£1.20**
- CP15 12 Standard crocodile clips, screw fixing, good quality **60p**
- CP16 5 P.C. boards each containing a BF180 UHF amplifier transistor. A good basis for building a T.V. aerial pre-amp as various parts inc. **60p**
- CP17 25 Electrolytic Capacitors, various values and voltages, many useful types from T.V. to transistor radio and Hi-Fi (post and packing 23p) **60p**
- CP18 1 Light activated SCR 50 volts 1.6 amps type L9F. Ready mounted on P.C. board with gate resistor and leads fitted. Full data and circuit diagrams for 14 projects includes slave photo flash unit, burglar alarm, etc. **60p**
- CP19 3 Micro switches 1 pole change over, standard model 1 1/2" x 1/4" **60p**
- CP20 10 Relays assorted types Ex-G.P.O. and others mixed voltages **£1.20**
- CP21 200 Square inches of copper laminate P.C. board in approx. 8 pieces **60p**
- CP22 3 Fibreglass plain printed circuit boards, approx. 2 1/2" x 14" **60p**
- CP23 4 Switches, miniature push to make, single pole **60p**

YOUR SUPPLIERS FOR:

Semi-conductors, all popular types, Opto electronic devices inc. Nixie Tubes, Solder Tools, Terminals, Switches, Knobs, Ex-G.P.O. items, Aluminium Boxes, Triacs, Thyristors, Zener Diodes and much more in our catalogue and shop



Semi-Conductors

TESTED AND GUARANTEED PACKS

- TP4 3 SN7490 integrated circuits, 14 pin dual in line TTL type Decade counter. Get one FREE, these are 60p each in singles **£1.20p**
- ALL THE FOLLOWING ARE AT 60p EACH PACK**
- TP9 5 SN7400 integrated circuits, 14 pin dual in line TTL type Quad 2 input NAND gate. Get one FREE, these are 15p each
- TP10 2 Light dependant resistors, 400 ohms light, 1 megohm dark, 1/4" dia
- TP11 10 Transistors XB102 and XB112 equivalent to AC126, AC156, OC81, 2, OC72 etc
- TP12 4 BY127 Silicon rectifiers 1000 piv 1 amp Plastic 1 V rectifier
- TP13 5 OCP71 Light sensitive transistors
- TP14 20 OC71 germanium PNP audio pre amp transistor, black glass type
- TP15 20 OC81 Germanium PNP audio output transistor, white glass type
- TP16 20 OC200, 1/2/3 transistors, PNP silicon 10-5, unmarked
- TP17 20 1 watt zener diodes, mixed voltages 6.8 to 43 volts
- TP18 20 2N3707/B, 9/10 transistors, NPN silicon plastic, unmarked
- TP19 100 Diodes, mixture of germanium, gold bonded, silicon etc. a useful selection of many types, marked and unmarked
- TP20 10 Mullard OC45 transistors, 1F amp PNP germanium
- TP23 20 BFY50, 1, 2, 2N898, 7, 2N1813 etc. NPN silicon 10-5 unmarked, COMPLEMENTARY TO PAK TP24
- TP24 20 BFY64, 2N2904/5 etc. PNP silicon 10-5 unmarked, COMPLEMENTARY TO PAK TP23
- TP30 20 NPN silicon planar transistors, TO-18 similar to BC108, etc. unmarked
- TP31 20 PNP silicon planar transistors, TO-18 similar to BC178, etc. unmarked
- TP32 20 2N2926 silicon plastic transistors, unmarked and ungraded for colours

UNTESTED PACKS — 60p each Specially for keen bargain hunters

- UT1 50 PNP germanium transistors, AF and RF, very good yield
- UT2 150 Germanium diodes, miniature glass type
- UT5 40 Zener diodes, 250 mW OA2240 range, average 50% good
- UT6 25 Zener diodes, 1-1 1/2 watt top hat type, mixed voltages
- UT9 40 NPN silicon planar transistors, of the 2N3707-11 range, low noise amp
- UT10 15 Power transistors, PNP germanium and NPN silicon, mostly TO-3 but some plastic and some marked
- UT13 15 Integrated circuits, experimenters pak, dual in line TO-5, TTL, OTL, marked and unmarked, some definitely good but old types

FOR FULL RANGES — SEE CATALOGUE

Singles

BRIDGE RECTIFIERS Plastic encapsulated

P.V.	50v	100v	400v
1 amp	35p	35p	45p
2 amp	35p	45p	55p
4 amp	45p	50p	80p
6 amp	50p	60p	90p
RY164 equiv SKB2/O2	400v 1.5 amp	45p	

FETs		UNI-JUNCTION TRANSISTORS	
2N3919	18p	2N2160	65p
2N4416	20p	2N2646	48p
MOS F.E.T.s		TIS43	31p
3N141/MEM616	50p		

PUTs	2N26027	50p
LEDs	TIL209—Red	18p
	TIL211—Green	33p

Also Power Diodes, Thyristors, Triacs, Diacs-Zener Diodes, Opto-Electronics, etc.

X-44 POCKET SIZE R.F. CROSS HATCH GENERATOR

Improved version of our famous Mk 2 model, of which thousands are in regular use. Size 150 x 75 x 50mm, strong plastic case with handle/stand, 4 push button operation, 4 patterns. Self-contained line and frame generator and synchro pulse. Preset adjust for R.F. output and line/frame synch. Uses 4 alkaline type 1600 batts. Blank raster facility. **FOR COLOUR AND MONO.** (P/P add 35p) **£25** in kit form **£27.50** Built & tested

LOOK OUT NEXT MONTH FOR THE NEW STERLING SOUND MODULES

	Vce	Watts	1cAmps	Price
40P1	15	20	3	30p
40N2	40	40	4	30p
40P2	40	40	4	30p
90N1	15	45	4	25p
90P1	15	45	4	25p
90N2	40	90	8	35p
90P2	40	90	8	35p

Many other types available from 3 to 115 watts

INTEGRATED CIRCUITS

MM5314	Dual in line clock chip	£3
LMS380	SL60745 Dual in line 2w. audio amp. with data etc.	75p
	Dual in line I.C. sockets 8 pin 14p; 14 pin 15p; 16 pin 16p.	

Sundry

SIGNAL GENERATOR

For MW and LF. Covers 550 KHz to 1.6 MHz for MW and 400 to 550KHz for LF. Fully portable. Invaluable in AM repair and alignment jobs (P/p 40p) **£4.25**

POCKET SIGNAL INJECTOR

Fourteen-pin type. Invaluable for fault tracing in radio sets, amplifiers, TVs, tape recorders etc. Takes one HP7 battery **£2.00**

EX-G.P.O. 5in SIDECUTTERS

Not new but in perfect order, per pair **50p**

EX-G.P.O. 6" LONG NOSE PLIERS

Not new, but in perfect order, per pair **60p**

MAINS TRANSFORMERS

MT6	6V 0.6v 100mA	£1.22
MT12	12V 0.12v 50mA	£1.22
SST9/1	9v 1amp	£1.67
SST12/1	12v 1amp	£2.05
SST18/1	18v 1amp	£2.50
SST25/2	25v 2amp	£3.00
SST30/2	30v 2amp	£4.25
SST35/4	35v 4amp	£5.50

(P/P 50p any one)

PC EDGE CONNECTORS

Type	Sizes	Pitch	
SSEC 6-wBY	1 1/2"	156"	32p
SSEC 10	1 3/4"	156"	50p
SSEC 12	2"	156"	60p
SSEC 16	2 1/2"	156"	75p
SSEC 18	3"	156"	85p
SSEC 22	3 1/2"	156"	1.00

UHF TUNER UNITS

Brand new, by famous manufacturer, 625 lines, Channels 21-65, ideal for use as TV sound receiver. With data **£2.50**

BOOKS

All free of VAT. We carry very large stocks of technical books by Babani & Bernard Publishers, by Newnes and Butterworth as well as reference books from the Common Market in English/German/Italian. All detailed in our catalogue

MONEY SAVER FOR CAR OWNERS

The "Super Spark" Capacity Discharge Ignition Unit, developed out of our original ETI model (of which we have sold well over 9,000) enables you to enjoy this system at a truly economic price. Facilities include simple adaption to pos or neg earth, immediate switch back to conventional ignition, anti-burglar immobilisation with all parts in totally enclosed strong metal case. Very easy to fit and install. With full instructions (P/P add 50p)

KIT £7.95+ READY-BUILT £10.50

B-P-P SECURITY CHECK POINT

- Write your own name and address clearly in block capital letters.
- Check that your order is correct for description, quantity and price.
- Don't forget VAT at 25% of total value of order unless otherwise stated.
- MAKE SURE YOU GET OUR NAME AND ADDRESS RIGHT WHEN ORDERING.
- Cash (cheque, money or postal order) with your order, please.
- Mention this journal when ordering if you don't want to cut out the coupon

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order, except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. **POST & PACKING** Add 30p for UK orders except where shown otherwise. Minimum mail order acceptable — £1. Overseas orders, add £1 for postage. And difference will be credited or charged. **PRICES** Subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

To: BI-PRE-PAK, 220/222 WEST RD. WESTCLIFF-ON-SEA, ESSEX SS0 9DF

Please send _____ inc. VAT
for which I enclose _____
NAME _____
ADDRESS _____
AW-

BI-PRE-PAK LTD

Co Reg No 820919

222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF.

TELEPHONE: SOUTHWEND (0702) 46344.

• FIRST IN U.K. WITH PACKS FOR ELECTRONICS USERS

LYNX ELECTRONICS (LONDON) LTD.

AC126 0.15	BC301 0.32	BY206 0.15	1N4003 0.06*
AC127 0.16	BC323 0.60	BY207 0.20*	1N4003 0.07*
AC128 0.13	BC327 0.18*	BYX36-300 0.12*	1N4005 0.08*
AC128K 0.25	BC328 0.16*	BYX36-600 0.16*	1N4006 0.09*
AC141 0.18	BC337 0.17*	BYX36-900 0.18*	1N4007 0.10*
AC141K 0.28	BC338 0.17*	BYX36-12000.21*	2N696 0.14
AC142 0.18	BCY70 0.12	BYX38-300 0.60	2N697 0.12
AC142K 0.18	BCY71 0.18	BYX38-600 0.65	2N706 0.10
AC176 0.16	BCY72 0.12	BYX38-900 0.80	2N929 0.14
AC176K 0.25	BD115 0.55	BYX38-12000.65	2N930 0.14
AC187 0.18	BD131 0.36	BZK61 Series	2N1131 0.15
AC187K 0.25	BD132 0.40	Zeners 0.20	2N1132 0.16
AC188 0.18	BD135 0.36	BZX83 or BZX88	2N1304 0.20
AC188K 0.25	BD136 0.38	Series	2N1305 0.20
AD140 0.50	BD137 0.40	Zeners 0.11	2N1711 0.18
AD142 0.50	BD138 0.48	C106A 0.40	2N2102 0.44
AD143 0.46	BD139 0.48	C106B 0.45	2N2369 0.14
AD149 0.45	BD181 0.86	C106D 0.50	2N2369A 0.14
AD161 0.35	BD182 0.92	C106F 0.35	2N2484 0.16
AD162 0.35	BD183 0.97	CRS1/05 0.25	2N2646 0.90
AL102 0.95	BD232 0.60*	CRS1/10 0.25	2N2905 0.18
AL103 0.93	BD233 0.48*	CRS1/20 0.35	2N2905A 0.22
AF114 0.20	BD237 0.65*	CRS1/40 0.40	2N2926R 0.10*
AF115 0.20	BD238 0.60*	CRS1/60 0.65	2N2926G 0.09*
AF116 0.20	BD184 1.20	CRS3-05 0.34	2N29267 0.09*
AF117 0.20	BDY20 0.80	CRS3-10 0.45	2N2926G 0.10*
AF118 0.50	BDY38 0.60	CRS3-20 0.50	2N3053 0.15
AF139 0.33	BDY60 0.60	CRS3-40 0.60	2N3054 0.40
AF239 0.37	BDY61 0.65	CRS3-60 0.85	2N3055 0.50
BC107 0.14	BDY62 0.55	MJ480 0.80	2N3440 0.98
BC107B 0.16	BF178 0.28	MJ481 1.05	2N3442 1.20
BC108 0.13	BF179 0.30	MJ490 0.90	2N3525 0.75
BC109 0.14	BF194 0.10*	MJ491 1.15	2N3570 0.80
BC109C 0.16	BF195 0.10*	MJ340 0.40*	2N3702 0.10*
BC117 0.19*	BF196 0.12*	MJ371 0.60*	2N3703 0.10*
BC125 0.18*	BF197 0.12*	MJ520 0.45	2N3704 0.10*
BC126 0.20*	BF224J 0.11*	MJ521 0.55	2N3705 0.10*
BC141 0.28	BF244 0.17*	OAS 0.50*	2N3706 0.10*
BC142 0.23	BF257 0.30*	OAS90 0.08	2N3707 0.10*
BC143 0.23	BF258 0.35	OAS1 0.08	2N3714 1.05
BC144 0.30	BF337 0.32*	OC41 0.15	2N3715 1.15
BC147 0.09*	BFV60 0.17*	OC42 0.15	2N3716 1.25
BC148 0.09*	BFX29 0.26	OC44 0.12	2N3771 1.60
BC149 0.09*	BFX30 0.30	OC45 0.10	2N3772 1.60
BC152 0.25*	BFX64 0.23	OC70 0.10	2N3773 2.10
BC153 0.18*	BFX65 0.25	OC71 0.10	2N3819 0.28*
BC157 0.09*	BFX88 0.22	OC72 0.22	2N3904 0.16*
BC158 0.09*	BFY50 0.20	OC84 0.14	2N3906 0.16*
BC159 0.09*	BFY51 0.18	SC40A 0.73	2N4124 0.12*
BC160 0.32	BFY52 0.19	SC40B 0.81	2N4290 1.2*
BC161 0.38	BFY64 0.35	SC40D 0.98	2N4348 0.98
BC168B 0.09*	BFY90 0.65	SC40F 0.85	2N4870 0.35
BC182 0.11*	BR100 0.20	SC41A 0.68	2N4871 0.35
BC182L 0.11*	BRV39 0.40	SC41B 0.70	2N4919 0.70*
BC183 0.10*	BSX19 0.16	SC41D 0.85	2N4920 0.50*
BC183L 0.10*	BSX20 0.18	SC41F 0.60	2N4922 0.58*
BC184 0.11*	BSX21 0.20	ST2 0.20	2N4923 0.64*
BC184L 0.11*	BSX95A 0.12	TIP29A 0.44	2N5060 0.20*
BC207B 0.12	BT106 1.00	TIP30A 0.52	2N5061 0.25*
BC212 0.11*	BT107 1.60	TIP31A 0.54	2N5062 0.27*
BC212L 0.11*	BT108 1.80	TIP32A 0.64	2N5064 0.30*
BC213 0.12*	BT109 1.00	TIP34 1.05	2N5496 0.85
BC213L 0.12*	BT116 1.00	TIP41A 0.68	
BC214 0.14*	BU105 1.80*	TIP42A 0.72	
BC214L 0.14*	BU105/	IN2069 0.14	
BC237 0.16*	O2 1.90*	IN2070 0.18	
BC238 0.16*	BU126 1.60*	1N4001 0.04*	
BC300 0.34		1N4002 0.05*	

DIGITAL DISPLAYS & LED'S

DL704	99p	DL747	£1.75	2 RED LED ONLY	13p
DL707	99p	DL750	£1.75	GREEN CLEAR	15p

THYRISTORS

	8A	1A	3A	6A	8A	10A
	(T092)	(T05)	(C106 type)	(T0220)	(T0220)	
50	20	25	35	41	47	47
100	25	25	40	48	48	54
200	27	35	45	58	60	68
400	30	40	50	87	88	98
600		65	70	1.09	1.19	1.26

TRIACS (PLASTIC TO-220 PKG. ISOLATED TAB)

	4A		6.5A		8.5A		10A		15A	
	(a)	(b)	(a)	(b)	(a)	(b)	(a)	(b)	(a)	(b)
100V	0.60	0.60	0.70	0.70	0.78	0.78	0.83	0.83	1.01	1.01
200V	0.84	0.84	0.75	0.75	0.87	0.87	0.87	0.87	1.17	1.17
400V	0.77	0.78	0.80	0.83	0.97	1.01	1.13	1.19	1.70	1.74
600V	0.96	0.99	0.87	1.01	1.21	1.26	1.42	1.50	2.11	2.17

N B Triacs without internal trigger diac are priced under column (a) Triacs with internal trigger diac are priced under column (b) When ordering please indicate clearly the type required

74 TTL mixed prices

7400	1.24	25.99	100+	7445	1.24	25.99	100+	7493	1.24	25.99	100+
7401	14p	12p	10p	7446	85p	71p	57p	7495	45p	40p	32p
7402	14p	12p	10p	7447	81p	75p	65p	7496	67p	55p	45p
7403	15p	12 1/2p	10p	7448	75p	62p	50p	74100	£1.08	89p	72p
7404	16p	13p	11p	7447A	95p	83p	67p	74107	35p	28p	22p
7408	16p	13p	11p	7470	30p	29p	20p	74121	34p	28p	23p
7409	16p	13p	11p	7472	25p	21p	17p	74122	47p	39p	31p
7410	16p	13p	11p	7473	30p	25p	20p	74131	78p	63p	53p
7413	29p	24p	20p	7474	32p	26p	21p	74145	68p	58p	48p
7417	27p	22 1/2p	20p	7475	47p	39p	31p	74154	£1.62	£1.48	86p
7420	16p	13p	11p	7476	32p	28p	21p	74174	£1.00	83p	67p
7427	27p	22 1/2p	18p	7482	75p	62p	50p	74180	£1.06	88p	71p
7430	16p	13p	11p	7485	£1.30	£1.09	87p	74181	£2.20	£2.50	£1.90
7432	27p	22 1/2p	18p	7486	32p	26p	21p	74192	£1.35	£1.14	90p
7437	27p	22 1/2p	18p	7489	£2.92	£2.80	£2.10	74193	£1.35	£1.14	90p
7441	75p	62p	50p	7490	49p	40p	32p	74196	£1.64	£1.34	99p
7442	65p	55p	43p	7491	65p	55p	45p				
				7492	57p	45p	36p				

LINEAR IC'S


301A 8 pin DIL	35p*	3900 14 pin DIL	70p*	565 14 pin DIL	£2.00*						
307	55p*	709 8/14 pin DIL	35p*	566 8 pin DIL	£1.50*						
309K	£1.60	741 8 pin DIL	28p*	567 8 pin DIL	£2.00*						
381 14 pin DIL	90p	741 14 pin DIL	28p*	CA3046 14 pin DIL	50p*						
381 14 pin DIL	£1.80*	748 8 pin DIL	36p*	CA3045	85p*						
		555 8 pin DIL	45p								

HIGHAM MEED, CHESHAM, BUCKS. Tel. (02405) 75151

VAT - Please add 8% except items marked * which are 25%

Servodata Limited

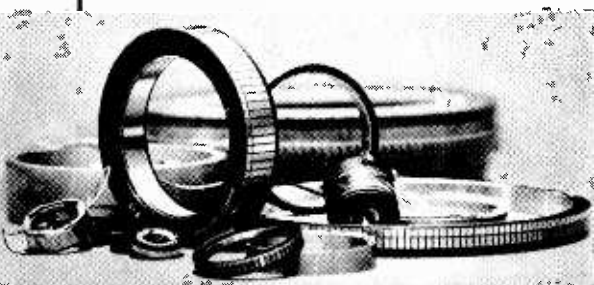Advanced Technology in Servo Control Components



DC Torque Motors and Tachometers

- ★ High performance, brush and brushless versions and complementary tachometers.
- ★ 840 Standard Models ranging from 15 oz-in to 120 lb-ft.
- ★ Military, Industrial or Space Qualified models are already used by most European Nations.

Servodata

is able to offer a technical design service utilising these devices in control systems as well as supplying amplifiers, solid state synchro/resolver to digital converters, readouts and other servo control transducers.

Servodata Limited

Highclere, Newbury
Berkshire RG15 9PU
Telephone: Highclere (STD 0635) 253579
Telex: 847054

WW-050 FOR FURTHER DETAILS

THE RADIO SHOP

16 CHERRY LANE
BRISTOL BS1 3NG



TELEPHONE
0272-421196

OFFICIAL ORDERS WELCOMED GOVT / EDUCATIONAL DEPTS. . ETC

TRIACS

1.6 AMP PLASTIC		6 AMP ISOLATED TAB		10 AMP ISOLATED TAB	
NAS0161W	100V .29	NAS0651W	100V .62	NAS1001W	100V .73
NAS011X	100V .28	NAS0651X	100V .61	NAS1001X	100V .72
NAS012W	200V .30	NAS0652W	200V .66	NAS1002W	200V .78
NAS011X	200V .29	NAS0652X	200V .65	NAS1002X	200V .76
NAS011W	400V .40	NAS0654W	400V .72	NAS1004W	400V 1.09
NAS011X	400V .38	NAS0654X	400V .70	NAS1004X	400V 1.04
NAS016W	600V .50	NAS0656W	600V .88	NAS1006W	600V 1.36
NAS016X	600V .48	NAS0656X	600V .78	NAS1006X	600V 1.34

3.5 AMP CLIPPED TAB		8.5 AMP ISOLATED TAB		15 AMP ISOLATED TAB	
NAS0351W	100V .53	NAS0851W	100V .69	NAS1501W	100V 1.05
NAS0351X	100V .52	NAS0851X	100V .68	NAS1501X	100V .95
NAS0352W	200V .58	NAS0852W	200V .78	NAS1502W	200V 1.04
NAS0352X	200V .56	NAS0852X	200V .76	NAS1502X	200V 1.02
NAS0354W	400V .68	NAS0854W	400V .88	NAS1504W	400V 1.51
NAS0354X	400V .67	NAS0854X	400V .85	NAS1504X	400V 1.48
NAS0356W	600V .86	NAS0856W	600V 1.10	NAS1506W	600V 1.89
NAS0356X	600V .84	NAS0856X	600V 1.06	NAS1506X	600V 1.84

Devices with internal trigger have "W" suffix. "X" denotes standard Triac.

THYRISTORS

1.6 AMP TO 5		4 AMP ISOLATED TAB		6 AMP ISOLATED TAB					
NAS006P	50V .25	NAS106Q	50V .26	NAS206P	50V .37				
NAS006Q	100V .28	NAS106Q	100V .30	NAS206Q	100V .42				
NAS006R	200V .31	NAS106R	200V .36	NAS206R	200V .50				
NAS006S	400V .40	NAS106S	400V .57	NAS206S	400V .77				
NAS006T	600V .52	NAS106T	600V .90						

8 AMP ISOLATED TAB		16 AMP TO 48	
NAS306P	50V .41	16A	50V .55
NAS306Q	100V .47	16A	100V .59
NAS306R	200V .59	16A	200V .65
NAS306S	400V .85	16A	400V .78
		16A	600V 1.08

INTEGRATED CIRCUITS

TAA550	TO18	54	●TBA800	78	●709	1 1/2 IN	.37	
TAA263	TO18	62	●TBA10AS	108	●741	8 IN	.35	
555	8 DIL	.40	●ZNA14	TO18	1.10	●748	1 1/2 IN	.50
556	8 DIL	1.05				723	1 1/2 IN	.67

CLOCK CHIPS

CT7001	28 Pin	4.95	AY-5-1224	16 Pin	3.75
28 Pin Skt		50	16 Pin Skt		16
Data		15	Data		15

707 LED 3" Common Anode Display	.90
704 LED 3" Common Cathode Display	1.00
747 LED 6" Common Anode Display	1.65

● Please add 25% VAT Remainder 8% P&P 20p
Phone in your Access or Barclaycard order. Catalogue 20p. Callers welcome

INTRODUCTORY PRICES

In addition to National, Mostek and Caltex clock chips, we are now selling a range of General Instrument chips.

Until 30th April '76 we are pleased to offer the following special prices.

AY-5-1202 + Futaba 5LT01.

AY-5-1202 interfaces directly with 5LT01 to provide the basis for a very simple electronic clock. The hours and minutes can be in 12 or 24 hour format and 50 or 60 Hz can be used as the timing source. 5LT01 is a green phosphor diode display. Special price £9.50.

AY-5-1230 + Futaba 5LT01

This chip similar to 1202. It has an ON/OFF programmable alarm which can be used in 7 segment mode to drive the 5LT01 or in BCD format to drive logic or TV display chips. Special price £10.00.

MK50253 + Futaba 5LT01

12 or 24 hour, 6 digit alarm chip. Snooze facility. Special price £10.50.

COME AND SEE US AT SEMINEX MARCH 22nd-26th.

STAND 11, Imperial College SW7.
Please send SAE for free ticket and new catalogue.

MISTRAL CLOCK KIT

Uses AY-5-1202 + Futaba 5LT01. Complete kit including case. £11.58.

CHEVIOT ALARM CLOCK

24 Hour 4 digit alarm clock. 0.5" green display, tilt to snooze. Finished clock — not kit. £21.85.

Terms: C.W.O. Access, Barclaycard (simply quote your number and sign)
Credit facilities to Accredited account holders
ALL PRICES EXCLUDE VAT AT 8%

BYWOOD BYWOOD ELECTRONICS
68 Ebbw Road
Hemel Hempstead, HP3 9RDF
Tel. 0442 62757

DEMA ELECTRONICS INTERNATIONAL

ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

MONTHLY SPECIALS

— Close out Sale Special Purchase While They Last —

CT 5001 12 Digit 4 Funct.	59	CT 5005 12 Digit 4 Funct. w/Mem	.79
CT 5002 Batt Oper 5001	69	CT 7001 4 or 6 Digit Alarm	3.50

— Memories Are Made of These Specials —

1101 256-Bit Ram Mos	.99	5262 2048-Bit Ram	3.95
1103 1024-Bit Ram Mos	1.45	1702A 2048-Bit Prom	9.95
5260 1024-Bit Ram	1.45	5203 2048-Bit w/Violet Proms	8.95
5261 1024-Bit Ram L/power	1.45	2102 1024-Bit Status Ram	2.75

TTL				ICL 8038 Funct. Gen Volt Contr	1.95
7447	59	74123	39	Oscillator Sine Sq	
7475	.29	74145	49	9-Digit LEO display Comm.	
7490	.35			Cathodes Comp w/8-digit	
				Clk Chps 12" Char	1.95

TTL 7400 SERIES

7400	£ 0.11	7440	£ 0.11	7485	£ 0.85	74155	£ 0.69
7401	0.11	7441	1.60	7486	0.24	74156	0.69
7402	0.11	7442	0.55	7488	2.50	74157	0.69
7403	0.11	7443	0.55	7489	1.50	74158	0.69
7404	0.13	7444	0.60	7490	0.40	74160	0.89
7405	0.13	7445	0.75	7491	0.55	74162	0.89
7406	0.22	7446	0.85	7492	0.43	74163	0.89
7407	0.22	7447	0.75	7493	0.43	74164	1.05
7408	0.14	7448	0.65	7494	0.49	74165	1.05
7409	0.14	7450	0.12	7495	0.49	74166	1.05
7410	0.11	7451	0.13	7496	0.55	74170	1.65
7411	0.16	7453	0.13	74100	0.89	74175	0.90
7413	0.26	7454	0.14	74107	0.27	74180	0.80
7416	0.22	7460	0.11	74121	0.37	74181	2.50
7417	0.22	7470	0.24	74122	0.27	74182	0.80
7420	0.11	7472	0.21	74123	0.49	74192	0.90
7426	0.23	7473	0.25	74145	0.57	74193	0.85
7430	0.12	7474	0.25	74150	0.59	74194	0.85
7432	0.22	7475	0.37	74151	0.59	74195	0.80
7437	0.25	7476	0.26	74153	0.69	74198	1.70
7438	0.25	7483	0.69	74154	1.05	74199	1.70

HIGH SPEED 74H00

74H00	£ 0.16	74H20	£ 0.16	74H52	£ 0.16	74H71	£ 0.21
74H01	0.16	74H21	0.16	74H53	0.16	74H72	0.26
74H04	0.16	74H22	0.16	74H54	0.21	74H74	0.28
74H05	0.21	74H30	0.16	74H55	0.16	74H76	0.28
74H08	0.16	74H40	0.16	74H60	0.16		
74H10	0.16	74H50	0.16	74H61	0.16		
74H11	0.16	74H51	0.21	74H62	0.16		

CMOS 4000 SERIES

4000A	£ 0.19	4014	£ 1.10	4028	£ 0.95	4071	£ 0.23
4001	0.19	4015	1.10	4030	0.50	4072	0.25
4002	0.19	4016	0.55	4042	0.95	4073	0.25
4006	0.90	4019	0.67	4043	1.20	4075	0.25
4007	0.19	4020	1.15	4044	1.20	4078	0.25
4008	1.30	4021	1.10	4049	0.48	4081	0.25
4009	0.49	4023	0.19	4050	0.48	4082	0.29
4010	0.49	4024	0.85	4066	0.75	4528	0.85
4011	0.19	4025	0.19	4068	0.23	4585	1.25
4013	0.39	4027	0.75	4069	0.23		

DTL

930	£ 0.10	936	£ 0.10	944	£ 0.10	962	£ 0.10
932	0.10	937	0.10	946	0.10	963	0.10

LINEARS

LM300	TO99	£ 0.45	340U	TO92	£ 1.25	739	A DIP	£ 0.65
301	V DIP	0.29	380	A DIP	80	741	V DIP	0.22
302	TO99	0.45	381	A DIP	1.05	747	A DIP	0.44
304	TO100	0.50	546	V DIP	0.51	748	V DIP	0.27
305	TO99	0.60	550	A DIP	0.55	5556 (1456)	V DIP	0.65
307	V DIP	0.38	555	V DIP	0.45	5558 (1458)	V DIP	0.65
	TO99	0.45	556	B DIP	0.75	ULN 2111	A DIP	0.95
308	A DIP	0.59	560	B DIP	2.55	LM3900	A DIP	0.35
	TO99	0.79	561	B DIP	2.55	75450	V DIP	0.45
309K	TO3	1.45	562	B DIP	2.55	75451	V DIP	0.45
310	T pkg	0.65	565	A DIP	1.25	75452	V DIP	0.45
311	V DIP	0.90	566	V DIP	1.20	75453	V DIP	0.45
320K	TD 3 NEG		567	V DIP	1.25	75454	V DIP	0.45
	5.2, 12, 15	1.25	709	A DIP	0.22	75491	A pkg	0.65
324	A DIP	1.07	710	A DIP	0.25	75492	A pkg	0.75
339	A DIP	1.49	711	A DIP	0.30	ICL 8038 Funct. Gen	1.95	
340K	TO3	2.10	723	A DIP	0.38	Volt Contr Oscillator, Sine Sq		
	12V 1 AMP					8864 22 Pin pkg	1.45	

V - Mini Dip A - 14L Dip B - 16L DIP TO99 8-Pin Header TO100 10-Pin Header
Data sheets supplied on request Add 20 ea. excepted as noted.

MEMORIES w/DATA	CALCULATORS & CLOCKS w/DATA
1101 256 Bit Ram Mos £ 1.79	5001 Cal Chip £ 0.99
1103 1024 Bit Ram Mos 2.25	5002 Cal Chip 1.19
7489 (8225) 64 Bit Ram TTL 1.50	5005 Cal Chip 1.49
8223 Programmable ROM 2.50	5311 Clock Chip 2.95
5260 1024 Bit Ram Low Power 1.95	5312 Clock Chip 2.95
	5313 Clock Chip 2.95
	5316 Clock Chip 3.95
	Data only for any of above 0.50
	Refundable Against Purchase
LEDS	TRANSISTORS
MY 5020 Jumbo Red or Clear £ 0.15	2N 2219A TO5 £ 0.32 2N 4124 TO92 0.10
MAN 1 Red 7 Seg 270 1.30	2N 2222 TO18 0.15 2N 4126 TO92 0.10
MAN 3A Red Seg 127 35	2N 2369 TO18 0.10 2N 4401 TO92 0.10
MAN 5 Green 7 Seg 270 1.75	2N 2905A TO5 0.38 2N 5225 TO92 0.10
MAN 6 6 Solid Seg 2.50	2N 3227 TO18 0.32 2N 5226 TO92 0.10
9 Digit Array Fairchild 37 with clear magnifying lens 2.95	


DISCOUNTS:	MIN ORDER	All Items New Branded Guaranteed By DEMA ELECTRONICS
10% on orders over £ 10	£ 2.5	
15% on orders over £ 25		

TERMS: PRICES LISTED ARE BRITISH POUNDS & PENCE. SEND CHEQUE WITH ORDER. MASTERCARD, BANKAMERICARD, BARCLAY CARD ACCEPTED. (Card # and expiration date requested). TERMS OFFERED TO SCHOOLS & INSTITUTIONS.

POSTAL AND HANDLING CHARGES SHIPMENT VIA AIR MAIL		
under 4.99	add .45	£ 10 and over
5.00-9.99	add .35	No Charge

DEMA ELECTRONICS INTERNATIONAL
P.O. Box 407 San Ramon, Ca. 94583 USA
Cable DEMAELINTL

ELECTROVALUE

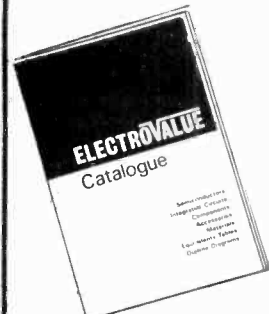

CATALOGUE 8

ISSUE No. 2
NOW READY

- 144 pages
- UP-DATED PRODUCT & PRICE INFORMATION
- 40p POST PAID + 40p REFUND VOUCHER

We have made it just about as comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 40p for spending on orders list value £5 or more. SEND NOW FOR YOUR COPY OF CATALOGUE 8, ISSUE No. 2 BY RETURN. It's an investment in practical money-saving and reliability!

+ E.V. PRICE STABILIZATION POLICY FOR 1976

This is one of reviewing prices every 3 months rather than trying to keep up with day by day changes as they occur. We have on the whole held prices better than anticipated in following this plan. Next review period starts April 1st.

+ E.V. DISCOUNT PLAN

Applies to all items except the few where prices are shown NETT 5% on orders from £5 to £14.99 10% on orders value £15 or more.

+ FREE POST & PACKING

In UK for pre-paid mail orders over £2. If under there is an additional handling charge of 15p.

+ QUALITY GUARANTEE

All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Dept 4, 3
28 ST. JUDES ROAD, ENGELFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603, Telex 264475. Shop hours 9-5.30 daily, 9-1 p.m. Sats
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945. Shop hours Daily 9-5.30 p.m., 9-1 p.m. Sats
In U.S.A. you are invited to contact ELECTROVALUE AMERICA, P.O. 337 Peterborough NH03458

RETURN OF POST MAIL ORDER SERVICE

BSR HI-FI AUTOCHANGER

STEREO AND MONO
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 1 1/2 x 1 1/4 in., 3 speeds. Above motor board 3 1/2 in. Below motor board 2 1/2 in. with STEREO and MONO CARTRIDGE



£10.95 Post 75p

PORTABLE PLAYER CABINET

Modern design. Rexine covered. Vynar front grille. Chrome fittings. Size 17 x 15 x 8 in. approx

£4.50 Post 50p

HEAVY METAL PLINTHS

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A" Size 1 1/2 x 1 1/4 x 7 1/2 in. Model "B". Size 1 1/2 x 1 1/4 x 7 in.

£5.95 Post 75p

COMPLETE STEREO SYSTEM

Two full size loudspeakers 1 3/4 x 10 x 3 3/4 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 3/4 x 10 x 8 1/2 in.. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls

£25 Post 50p



SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

0-60 MINUTES £2.50 Post 35p
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed.



TEAKWOOD LOUDSPEAKER GRILLES will easily fit to baffle board. Size 10 1/2 x 7 1/4 in.—45p.

WEYRAN P50 — TRANSISTOR COILS

RA2W Ferrite Aerial 85p	Driver Trans. LFD14 65p
1.F. P50/2CC 470 kc/s 40p	Printed Circuit, PCA1 65p
3rd I.F. P50/3CC 40p	J.B. Tuning Gang £2.00
P50/1AC 60p	OPT1 65p

Ferrite Rod 8 x 3/8 in., 20p. 6 x 5/16 in., 20p. 3 x 3/8 in., 10p

VOLUME CONTROLS

5KΩ to 2MΩ. LOG or LIN. L/S 25p. D.P. 40p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 30p.

80 Ohm Coax 8p yd.

BRITISH AERIALITE
AERAXIAL-AIR SPACED
40 yd. £3; 60 yd. £4.50
FRINGE LOW LOSS
Ideal 625 and colour yd.

ELAC HI-FI SPEAKER

8 in. or 10 x 6 in.

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 10 watts. music power. £4.35 Post 35p




E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With tweeter and crossover 10 watt. State 3 or 8 ohm. As illustrated

£5.25 Post 35p Post 45p

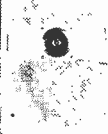With flared tweeter cone and ceramic magnet 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. 8 ohm. 40 to 11,000 c/s. Post 35p



Bookshelf Cabinet

Teak finish 16 x 10 x 9 in. For EMI 13 x 8 speakers.

£6.95 Post 75p

THE "INSTANT" BULK TAPE ERASER

AND HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. Will also demagnetise small tools.

£4.35 Post 30p



BLANK ALUMINIUM CHASSIS. 6 x 4—70p; 8 x 6—90p; 10 x 7—£1.15; 12 x 8—£1.35; 14 x 9—£1.50; 16x6—£1.45; 16 x 10—£1.70.

ALUMINIUM PANELS. 6 x 4—17p; 8 x 6—24p; 14 x 3—25p; 10 x 7—35p; 12 x 8—43p; 12 x 5—30p; 16 x 6—43p; 14 x 9—52p; 12 x 12—68p; 16 x 10—75p.

ELAC 9 x 5 in HI-FI SPEAKER TYPE 59RM

This famous unit now available. 10 watts. 8 ohm.
£3.45 Post 35p

RCS LOW VOLTAGE STABILISED POWER PACK KITS

All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available. 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required.
£2.95 Post 45p

RCS POWER PACK KIT

12 VOLT. 750mA. Complete with printed circuit board and assembly instructions.
£3.35 Post 30p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER — BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size. 1 1/4 x 1 1/4 x 3/4 in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment.
£1.45 Post 30p

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc.
95p Post 30p

R.C.S. "MINOR" 10 watt AMPLIFIER KIT

This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available: Mono. £12.50; Stereo. £20. Post 45p. Specification 10W per channel; input 100mV; size 9 1/2 x 3 x 2 in. approx. S.A.E. details. Full instructions supplied. AC mains powered.

MAINS TRANSFORMERS

250-0-250V 70mA, 6.5V, 2A	£3.45
250-0-250 80mA, 6.3V 3.5A, 6.3V 1A or 5V 2A	£4.60
350-0-350 80mA, 6.3V 3.5A, 6.3V 1A or 5V 2A	£5.80
300-0-300V 120mA, 6.3V 4A CT, 6.3V 2A	£7.00
MIDGET 220V 45mA, 6.3V 2A	£1.40
HEATED TRANS. 6.3V 1/2 amp £1; 3 amp	£1.40
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£4.60.
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£4.60.
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£7.00.
3 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8.70.
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11.25.
6.06V 500mA £1, 9V 1 amp. £1, 12V 300mA £1, 12V 500mA £1, 12V 750mA £1, 10V, 30V, 40V, 2 amp. £2.75, 20V, 3 amp. £2.45, 40V, 2 amp. £2.95, 22-0-22V, 4 amp. d.c. £3.45, 16V, 1/2 amp. £1, 16V, 2 amp. £2.20, 0, 5, 8, 10, 16V, 1/2 amp. £1.95, 20V 1/2 amp. £1.75, 20V, 1 amp. £2.20.	
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £5; 250W £6; 400W £7; 500W £8.	
FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.	
CHARGER TRANSFORMERS 1 1/2 amp £2.75; 4 amp £4.60. 12V. 1 1/2A HALF WAVE Selenium Rectifier, 25p.	

GOODMANS 8-inch HI-FI BASS WOOFER

8 ohm. 10W. Large ceramic magnet. Special Rubber cone surround. Frequency response, 30-8000 c/s.
Ideal Hi-Fi Enclosure Systems. £6.75



NEW ELECTROLYTIC CONDENSERS

2/350V 20p	250/25V 20p	50+50/300V 50p
4/350V 20p	500/25V 25p	900/350V 95p
8/350V 28p	100+100/275V 65p	32+32/250V 20p
16/350V 35p	150+200/275V 70p	32+32/450V 80p
32/500V 60p	8+8/350V 50p	350+50/325V 85p
25/25V 15p	8+16/350V 50p	100+50+50/350V 85p
50/50V 15p	16+16/350V 60p	32+32+32/350V 65p
100/25V 15p	32+32/350V 60p	4700/63V 95p

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

SHORT WAVE 100pF air spaced gangable tuner. 95p.

TRIMMERS 10pF, 30pF, 50pF, 5p. 100pF, 150pF, 15p.
CERAMIC, 1pF to 0.01mF, 5p. Silver Mica 2 to 5000pF, 5p.
PAPER 350V-0.1 7p; 0.5 13p; 1mf 150V 15p; 2mf 150V 15p; 500V-0.001 to 0.05 5p; 0.1 10p; 0.25 13p; 0.47 25p.
MICRO SWITCH SINGLE POLE CHANGEOVER 20p.
SUB-MIN MICRO SWITCH, 25p. Single pole change over
TWIN GANG, "0-0" 208pF + 176pF £2.00; 500pF standard
75p; 365 + 365 + 25 + 25pF. Slow motion drive 50p.
120pF TWIN GANG, 50p; 365pF TWIN GANG, 50p.
NEON PANEL INDICATORS 250V AC/D.C. Amber or red, 30p.
RESISTORS. 1/4W, 1/2W, 20% 2p; 2W, 10p; 10Ω to 10M
HIGH STABILITY. 1/2W 2% 10 ohms to 6 meg. 12p.
Ditto 5%. Preferred values 10 ohms to 10 meg. 5p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each
TAPE OSCILLATOR COIL Valve type. 35p.
BRIDGE RECTIFIER 200V PIV 1/2 amp 50p.

BAKER MAJOR 12" £11.50



30-14,500 c/s. 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell's. Bass resonance 40 c/s. Rated 25W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions.

£14.50 Post 60p each
Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS. Post 50p each.

'Group 25'	'Group 35'	'Group 50/15'
12in	12in	15in
30W £8.95	40W £10.50	75W £19.50
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

NEW MODEL BAKER LOUDSPEAKER, 12-inch 60 WATT GROUP 50/12, 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. 30-16,000 CPS MASSIVE CERAMIC MAGNET. Post 80p ALUMINIUM PRESENCE CENTRE DOME. £14.50

TEAK VENEERED HI-FI SPEAKERS AND CABINETS

For 12 in or 10 in speaker 20x13x12 in. £12.50 Post 95p
For 13x8 in or 8 in, speaker 16x10x7 in. £6.95 Post 75p
For 8x5 in, speaker 12x8x6 in. £4.95 Post 50p
LOUDSPEAKER CABINET WADDING 18 in. wide 20p ft.

R.C.S. 100 watt VALVE AMPLIFIER CHASSIS



Four inputs Four way mixing, master volume, treble and bass controls Suits all speakers This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required, 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier.
Send for leaflet Price £85 carr £2.50

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £3.60
De Luxe Horn Tweeters 2-18kc/s, 15W, 15 ohm £4.50
CROSSOVERS, TWO-WAY 3000 c/s 3 or 8 or 15 ohm £1.90. 3-way 950 cps/3000 cps £2.20.
LOUDSPEAKERS P.M. 3 OHMS. 7x4 in. £1.50; 6 1/2 in. £1.80; 8x5 in. £1.90; 8 in. £1.95.
SPECIAL OFFER: 80 ohm. 2 1/2 in., 2 3/4 in., 35 ohm, 2 in., 3 in., 25 ohm, 2 1/2 in. dia., 3 in. dia., 5 in. dia., 8 ohm, 2 1/2 in., 3 in., 3 1/2 in., 15 ohm, 3 1/4 in. dia., 6x4 in., 7x4 in., 8x5 in., 3 ohm, 2 1/2 in., 2 3/4 in., 3 1/2 in. 5 in. dia. £1.25 each.
PHILIPS LOUDSPEAKER, 8 in., 4 ohms, 4 watts, ceramic magnet £1.95
RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8 in. diameter 4W £2.50. 10 in. diameter 5W £2.95; 12 in. diameter 6W £3.50. 3/8/15 ohms, please state.
VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50 p, 40p. *like trans. mu metal 100-1 £1.25.

Loudspeaker Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting. 1/4 in. spindle. 65p

BAKER 100 WATT ALL PURPOSE AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music, 4 way mixing. Output 8/15 ohm. a.c. Mains Separate treble and bass controls. £65 Carr. £1.00 each
Guaranteed. Details S.A.E.
NEW MODEL MAJOR—50 watt, 4 input, 2 vol. Treble and bass. Ideal disco amplifier. £49.95



100 WATT DISCO AMPLIFIER CHASSIS

volume, treble, bass controls 500 M V input
Four loudspeaker outputs 4 to 16 ohm. £52

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output, 9V. £5.20

TWO STEREO CHANNEL VERSION £6.85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready Built, with volume, Treble and bass controls 18 volt d.c. Mains Power Pack £3.45

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES, SURFACE 40p. FLUSH 60p. TWIN 85p. BALANCED TWIN RIBBON FEEDER 300 ohms. 7p yd. JACK SOCKET Std. open-circuit 20p, closed circuit 25p; Chrome Lead-Socket 45p. Mono or Stereo. Phono Plugs 8p. Phono Socket 8p. JACK PLUGS Std. Chrome 30p; 3.5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p. 5-pin 10p. DIN SOCKETS FREE 3-pin 25p; 5-pin 25p. DIN PLUGS 3-pin 25p; 5-pin 25p. VALVE HOLDERS, 10p; CANS, 10p.

R.C.S. SOUND TO LIGHT KIT

*Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. £12.50. Post 35p. Easy to build. Full instructions supplied, cabinet £3. As featured in December Practical Wireless.

E.M.I. TAPE MOTORS. 240V a.c. 1,200 r.p.m. 4 pole 185mA Spindle 0.187x0.75 in. Size 3 1/4 x 2 1/4 in £2. Post 40p
120V Model, £1



RADIO COMPONENT SPECIALISTS


Radio Books and Components Lists 10p. (Minimum posting charge 30p) All prices include VAT (We accept Access or Barclaycard) Tel. 01-684 1665

For all who want to know about electronic circuits

Here's a book of very special appeal to all concerned with designing, using or understanding electronic circuits. It comprises information previously included in the first ten sets of Wireless World's highly successful Circards — regularly published cards giving *selected* and *tested* circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of the ten sets — including additional circuits — in this magazine size hard cover book has been updated where necessary, and is preceded by an explanatory introduction. Circuit designs (1) is the first collection of its kind.

Circuits covered are:

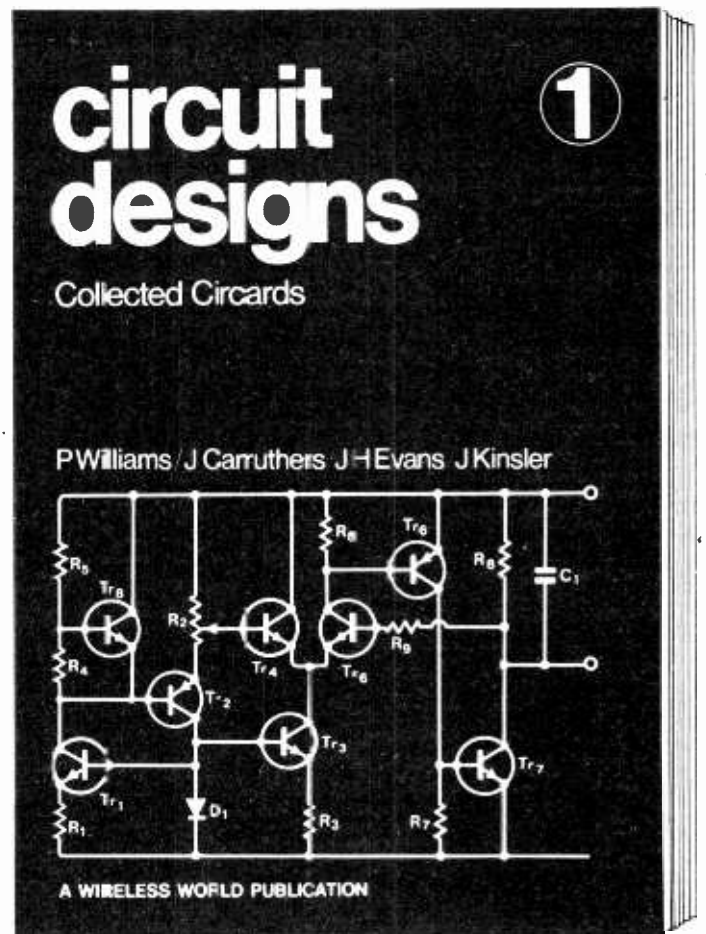- Basic active filters**
- Switching circuits**
- Waveform generators**
- AC measurements**
- Audio circuits**
- Constant-current circuits**
- Power amplifiers**
- Astable circuits**
- Optoelectronics**
- Micropower circuits**



A new book from Wireless World

ORDER FORM

To: General Sales Department,
IPC Business Press Limited,
Room 11, Dorset House,
Stamford Street, London SE1 9LU.

Please send me copy/copies of
Circuit Designs — Number 1 at £10.40
each inclusive. I enclose remittance
value £. (cheques payable to
IPC Business Press Ltd.)

NAME (please print)

ADDRESS

Company registered in England and a subsidiary of Reed
International Limited Registered No 677128 Regd. office
Dorset House, Stamford Street, London SE1 9LU.

KINNIE COMPONENTS

10, NELMES WAY, HORNCHURCH
ESSEX RM11 2OZ
HORNCHURCH 45167

CIRCUIT BOARD

P.C.B. 1/16. 1 oz. COPPER

FORMICA

Dim. 8.4 x 7.7 in 3 pcs., **75p**
Dim. 9.4 x 8.1 in 3 pcs., **90p**
Dim. 10.1 x 7.9 in 3 pcs., **£1.00**
Dim. 13.1 x 9.4 in 3 pcs., **£1.20**
Dim. 17.0 x 9.0 in 2 pcs., **£1.20**
Post & Packing 30p each pack.

BARGAIN PACK

10 pcs. 10.1 x 7.9 in. Plus free 1/2 lb etching
Xtals **£3.00** P.P. 55p.

FIBRE GLASS P.C.B.

Dim. 6 x 6 in. **35p** each
Dim. 12 x 6 in. **60p** each
Dim. 12 x 12 in. **£1.00** each
Equals less than **1p** sq. in.
Post & Packing 10p per sheet.

RESIST COATED P.C.B. FORMICA

10.1 x 7.9 in. **55p** ea.
13.1 x 9.4 in **70p** ea.

RESIST COATED P.C.B. FIBRE GLASS

6 x 6 in. **50p** ea.
12 x 6 in. **90p** ea.
12 x 12 in. **£1.50** ea.
Post & Packing 10p per sheet.

BLUE P.C.B. INK

Etch resist use with any pen. Much cheaper than ready loaded pens.
50c.c **55p.** P.P. 10p.

FERRIC CHLORIDE ETCHING XTALS

1 lb - 1 litre pack, **60p** P.P. 25p.
5 lb - 5 litre pack, **£1.95** P.P. 55p.

EDGE CONNECTORS. 54 WAY

1 Vero size etc. Can be cut to any length,
55p P.P. 10p

QUADROPHONIC DECODER MODULE

C.B.S./S.Q. Type using I.C. MC 1312P.
With slight modification direct substitute for P.E. "RONDO" Board. Complete with Data.
£4.60 each. P.P. 25p.

PRINTED CIRCUIT KIT

The no frills all value kit. Containing 4 pcs 8 x 7 Formica laminate. 1 pce 6 x 6 Fibre glass laminate, 1 lb Etching Crystals, 50 c.c. Resist ink, with instructions.
£2.30 P.P. 50p.

TELEPHONE DIALS

(New) **£1** P.P. 25p.

EXTENSION TELEPHONES

(Type 706) Various colours.
£3.95 P.P. 75p.

12V MINIATURE

UNISELECTOR

11 ways. 4 bank (3 non bridging, 1 homing).
£2.50 P.P. 35p.



UNISELECTORS

(New) 25 way. 12 Bank (Non bridging), 68 ohms. **£6.50** P.P. 50p.

MINIATURE UNISELECTOR

(Ex. Equip.) 6 Bank (5 non bridging, 1 bridging) 100 ohms 24-30 V.D.C. **£1.50** P.P. 50p.

1,000 TYPE KEY SWITCHES

Single 2 x 2 c/o Locking. **50p.** P.P. 10p
Bank of 4-2 x 4 c/o each switch (one biased).
£1.20 P.P. 25p.

MULTICORE CABLE

6-core (6 colours) 14/0076 Screened P.V.C. **30p** per yard; 100 yards at **£16.50** P.P. 2p a yard, 7-core (7 colours) 7/22 mm. Screened P.V.C. **30p** per yard; 100 yards **£16.50** P.P. 2p per yard.

RIBBON CABLE

(8 colours); 10m. **£1.65.** P.P. 20p. 100m. 8-core x 14/0.19mm. Bonded side by side **£11.50** P.P. £1.

P.T.F.E. CONNECTING WIRE

1/20 Black or White 100 m. Drum **£2.50** P.P. 30p.

H.D. ALARM BELLS

6in. Dome. 6/8v, d.c. Heavy cast housing for exterior/interior use. **£3.75** P.P. £1.
Connecting wire (twin/twisted) 220yd. reel **£3** P.P. 75p.

HIGH CAPACITY ELECTROLYTICS

250mfd/63 volt, **20p** P.P. 8p.
1,000mfd/100 volt, **70p** P.P. 25p.
2,200mfd/100 volt, **90p.** P.P. 25p.
4,700mfd/25 volt, **65p.** P.P. 20p.
6,800mfd/16 volt, **50p.** P.P. 15p.
10,000mfd/25 volt, **75p.** P.P. 25p.
25,000mfd/40 volt, **£1.25.** P.P. 30p.
47,000mfd/40 volt, **£2.00.** P.P. 50p.
100,000mfd/10 volt, **£1.50.** P.P. 50p.
160,000mfd/10 volt, **£2.00.** P.P. 50p.

OVERLOAD CUT OUTS

Panel mounting 800 M/A 1.8 amp. 10 amp. **55p** ea.

SMITHS GEARED MOTORS 240V AC

3 rev. per min. **£1.50.** P.P. 25p.
4 rev. per min. **£1.50.** P.P. 25p.
6 rev. per min. **£1.50.** P.P. 25p.
2 rev. per hour. **£1.50.** P.P. 25p.
6 rev. per hour. **£1.50.** P.P. 25p.

HIGH-SPEED MAGNETIC COUNTERS

4 digit (non reset) 24v or 48v (state which)
4 x 1 x 1 in. **£1.** P.P. 20p.
5 digit (non reset) 24v **1.50.** P.P. 20p.
3 digit 12v (Rotary Reset) 2 1/4 x 1 3/4 x 1 1/4 **£1.40.** P.P. 15p.
6 digit (Reset) 220v. a.c. **£3.50.** P.P. 25p.



S-DECS AND T-DECS

S-DEC **£1.90** T-DEC **£3.60**
U-DEC A **£4.20** U-DEC B **£6.90**
Post & Packing 25p.

MINIATURE METERS

500 micro-amp (level stereo beacon, etc) scaled half back/half red. Size 1 x 1 in. **65p.** P.P. 15p.

PANEL METERS

T1 50µA	T8 500mA
T2 100µA	T9 1Amp
T3 500µA	T10 50v.a.c.
T4 1mA	T11 300v.a.c.
T5 10mA	T12 50/0/50fIA
T6 50mA	T13 100/0/100µA
T7 100mA	T14 500/0/500µA

All at **£3.75.** P.P. 15p.



PANEL METERS

4 1/2 ins. x 3 1/4	D3 200µA
D1 50µA	D4 500µA
D2 100µA	All at £4.60. P.P. 15p.

S.T.C. CRYSTAL FILTERS

(10.7Mhz) 445-LQU-901A (50 Khz spacing). **£3.** P.P. 20p.
445-LQU-901B (25Khz spacing). **£4.** P.P. 20p. 10.7Mhz Canned I.F.s. Size 1 x 1/2 x 1/2 in. (with data) **65p.** P.P. 10p.

3 GANG TUNING CAPACITOR

8.5 PF, to 320 P.F. **80p.** P.P. 20p.

V.H.F./U.H.F. POWER TRANSISTORS

(type BLY 38). 3 watt output at 100-500 Mhz. **£2.25.** P.P. 10p.

SIEMENS MINIATURE RELAYS

6v.4 c/o **65p.** 24v.2 c/o **50p.**

MINIATURE RELAYS

(1 1/8 x 1 1/4 x 1/2) 24 v.4 c/o **35p.** P.P. 5p.

MAINS RELAY 240v.a.c.

3 c/o 10 amp. contacts **80p.** with base P.P. 20p

24v a.c. RELAY (PLUG IN)

3 pole c/o **75p.** P.P. 15p.
2-pole c/o **55p.** P.P. 15p.

S.C.R.

1 amp. 400 P.I.V. **35p.**
5 amp. 400 P.I.V. **40p**

MINIATURE "ELAPSED TIME" INDICATORS

(0.5000 hours) 45 x 8mm **75p.** P.P. 15p.

BULK COMPONENTS OFFER

Resistors/capacitors 600 new components **£2.75.** P.P. 36p.
Trial order 100 pcs **75p.** P.P. 20p.

D.C. SUPPLY

Input 240v. a.c. giving 17 1/2 v.d.c. at 1 1/2 amp (unsmoothed) 2 3/4 x 2 1/2 x 2 1/4 in. **£2.25.** P.P. 45p.

ADVANCE TRANSFORMERS

"VOLSTAT"

Input 240v. a.c. C.V.50. 38v. at 1 amp; 25v. at 100/m/a; 75v. at 200 m/a **£3.** P.P. 65p.
C.V. 75.25v. at 2 1/2 amp. **£3.25.** P.P. 75p.
C.V. 100.50v. at 2 amp; 50v. at 100 m/a **£4.** P.P. 75p.
C.V. 250.25v. at 8 amp; 75v. at 1/2 amp. **£6.50.** P.P. £1.50.
C.V. 500.45v. at 3 amp; 35v at 2 amp. **£12.** P.P. £1.75.

H.T. TRANSFORMERS. Prim. 110/240v. Sec. 400v. 100 m/a **£3.** P.P. 65p.
L.T. TRANSFORMER. Prim. 240v. Sec. 27-0-27 at 800 m/a **£2.25.** P.P. 50p.
L.T. TRANSFORMER. Prim. 110/240v. Sec. 50v. at 10 amp. **£10.** P.P. £1.50.
L.T. TRANSFORMER. Prim. 240v. Sec. 18v. at 1.5 amp. & 12v. at 1 amp. **£2.25.** P.P. 50p.
L.T. TRANSFORMER. Prim. 240v. Sec. 18v. 1 amp. **£1.** P.P. 30p.
L.T. TRANSFORMER. Prim. 240v. Sec. 12v. at 1 amp. **80p.** P.P. 25p.
L.T. TRANSFORMER. Prim. 110/240v. Sec. 23/24/25v. at 10 amps **£7.** P.P. £1.
L.T. TRANSFORMER. Prim. 110/240v.

TRANSFORMERS

Sec. 20/21/22v. at 8 amp. **£6.** P.P. £1.
L.T. TRANSFORMER. Prim. 110/240v. Sec. 0/24/40v. at 1 1/2 amp. (Shrouded). **£1.95.** P.P. 50p.
L.T. TRANSFORMER. Prim. 200/250v. Sec. 20/40/60v. at 2 amp. (Shrouded). **£3.** P.P. 70p.
L.T. TRANSFORMER. (H.D.) Prim. 200/250v. Sec. 18v. at 27 amp; 40v at 9.8 amp; 40v. at 3.6 amp; 52v. at 1 amp; 25v. at 3.7 amp. **£17.50.** P.P. £2.50.
L.T. TRANSFORMER. Prim. 240v. Sec. 20v. at 2.5 amp. **£2.** P.P. 50p.
L.T. TRANSFORMER ("C" CORE)

200/240v. Secs. 1-3-8-9c. All at 1.5 amp. 50v. at 1 amp. **£2.50.** P.P. 50p.
L.T. TRANSFORMER ("C" CORE) 200/240v. Secs. 1-3-9-27v. All at 4 amp. **£4.** P.P. 50p.
L.T. TRANSFORMER ("C" CORE) 200/240v. Secs. 1-3-9-27v. All at 10 amp. **£7.50.** P.P. £1.50
L.T. TRANSFORMER ("C" CORE) 200/240v. Secs. 1-3-9-20v. All at 4 amp. **£5.50.** P.P. 75p.
L.T. TRANSFORMER ("C" CORE) 120/120v. Secs. 1-3-9-9v. All at 10 amp. **£6.50.** P.P. £1.50.
L.T. TRANSFORMERS ("C" CORE) 110/240v. Secs. 1-3-9v. 10 amp. 35v. 1 amp; 50v. 750 M/A. **£6.50.** P.P. £1.50.

MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT

BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743
ALL PRICES SHOWN INCLUDE V.A.T.

0B2 0.45	6B8G 0.35	6L8C 0.68	12A2V6 0.58	30P4MR 1.05	ARKP3 0.60	EBF89 0.40
0B4 0.55	6BA6 0.41	6L7M 0.59	12A2X7 0.39	30P12 0.20	ATP4 0.50	EHL21 2.30
1A3 0.85	6BCR 0.80	6L12 0.47	12A7 0.94	30P4 0.88	AT4 0.50	EC52 1.00
1ASGT 0.59	6BE6 0.41	6L18 0.64	12B48 0.53	30P19 0.88	AZ31 0.60	EC53 1.00
1ATGT 0.60	6BC6G 1.23	6L19 2.80	12B58 0.59	30P18 0.43	AZ41 0.50	EC54 1.00
1B3GT 0.59	6B8H 0.75	6L20 0.48	12B57 0.85	30P18 0.50	BLB3 2.34	EC86 0.90
1C2 1.15	6B16 0.64	6L20 0.58	12B77 0.85	30P11 1.00	CL33 1.85	EC88 0.90
1D6 0.75	6BK7A 0.65	6NTG7 0.70	12E1 3.51	30P12 0.45	CV6 0.62	EC92 0.55
1G6 1.17	6B05 0.36	6P12 0.45	12J5GT 0.39	30P13 1.20	CV63 1.00	EC92 1.00
1HSGT 0.80	6B07A 0.64	6P15 0.36	12J7GT 0.70	30P14 1.29	CY88 0.29	EC93 1.00
1LA 0.25	6BR7 1.20	6Q7G 1.20	12K65 1.17	30P15 0.90	CY11 1.00	EC93 2.00
1LD5 0.70	6BR8 1.25	6Q7GT 0.60	12K7GT 0.50	35A3 0.78	CC10 0.70	EC94 1.00
1LN5 0.70	6BS7 1.84	6Q7M 0.64	12K7 0.85	35C5 0.85	D1 0.50	EC94 1.00
1INSGT 0.76	6BW6 1.00	6R7G 1.00	12Q7GT 0.50	35D5 0.90	D63 0.30	EC98 0.40
1R5 0.50	6BWX 0.65	6RTM 0.88	12SA7GT 0.88	35L6GT 0.88	DAC32 0.80	EC98 0.39
1S4 0.39	6BX6 0.30	6SA7 0.55	0.70 35W4 0.60	DAF9 0.40	EC98 0.40	EC98 0.40
1S5 0.40	6BY7 0.40	6SC7GT 0.50	12SC7 0.55	35Z3 0.88	DAF9 0.40	EC98 0.40
1TA 0.39	6BZ6 0.57	6SG7 0.55	12SG7 0.55	35Z4GT 0.88	DAF9 0.40	EC98 0.40
1U4 0.70	6C4 0.47	6SH7 0.55	12SH7 0.50	35Z5GT 0.80	DD4 0.80	EC98 0.40
1U5 0.88	6C5G 0.59	6S17 0.64	12SJ7 0.60	4.00 DF33 0.76	EC98 0.40	EC98 0.40
2D2 0.60	6C6 0.47	6SK7GT 0.52	12SJ7 0.64	50B5 1.00	DF91 0.30	EC98 0.40
2GK5 0.75	6C9 2.00	6S07 0.50	12SN7GT 0.50	50C5 0.70	DF96 0.65	EC98 0.40
2X2 0.70	6C10 0.80	6U4GT 0.82	12SJ7 0.75	50C6DG 1.46	DH63 0.50	EC98 0.40
3A4 0.82	6CB8A 0.47	6U7G 0.52	12SG7 0.76	50EH5 0.88	DF96 0.65	EC98 0.40
3B7 0.53	6C8 0.76	6V6GT 0.39	12SQ7GT 0.72	50G7 0.80	DH77 0.53	EC98 0.40
3D6 0.47	6C12 2.34	6V8GT 0.53	0.70 7.00	DH81 0.88	ECF84 0.23	EC98 0.40
3Q4 0.85	6CD6G 1.80	6X4 0.47	12SR7 0.75	77 0.70	DK32 0.60	EC98 0.40
3QSGT 0.70	6CGB8 0.88	6X5GT 0.50	14H7 0.64	85A2 0.75	DK40 0.82	EC98 0.40
3S4 0.47	6CL6 0.76	6Y6G 0.94	1A57 1.10	85A3 0.75	DK91 0.50	EC98 0.40
3V4 0.82	6CL8A 0.94	6Y7G 1.17	1.17 90AG 2.83	DK92 1.15	DK92 1.15	EC98 0.40
4C86 0.75	6CM7 0.88	7A7 1.00	18A9X5 0.65	90CG 2.81	DK96 0.70	EC98 0.40
5C8 0.75	6C85 0.88	7B6 0.88	18B6G 1.17	90CV 2.81	DL52 0.47	EC98 0.40
5R4GY 0.94	6CW4 1.17	7B8 0.82	18G7 1.00	90C1 0.88	DL94 0.82	EC98 0.40
5T4 0.47	6D3 0.75	7D6 2.00	19H1 4.00	150B2 1.00	DL96 0.84	EC98 0.40
5U4 0.50	6DE7 0.88	7F8 1.76	20D1 0.90	215SG 0.59	DM70 0.80	EC98 0.40
5V4G 0.50	6D7BA 0.88	7H7 0.88	20D4 2.34	301 1.17	DM71 1.17	EC98 0.40
5YGT 0.55	6E6W 0.65	7R7 2.00	20P2 0.88	302 1.17	DW4/350 0.70	EC98 0.40
5Z3 0.88	6E5 1.17	7V7 1.76	20L1 1.29	303 1.17	1.76	EC98 0.40
5Z4G 0.55	6F1 0.90	7Y4 0.80	20P1 1.00	305 1.17	DY87/6 0.41	EC98 0.40
5Z4GT 0.55	6F6G 0.60	7Z4 0.80	20P3 0.94	807 1.17	DY802 0.47	EC98 0.40
6/30L2 0.80	6F12 0.50	8D8 0.50	20P4 1.17	956 0.60	E80CC 2.57	EC98 0.40
6A8G 1.46	6F13 0.90	9HW6 0.88	20P5 1.50	921 1.17	E80F 2.00	EC98 0.40
6A7 0.80	6F14 0.88	7R7 0.78	25A6G 0.78	4033X 7.61	ES3T 1.60	EC98 0.40
6A85 0.35	6F15 0.75	10C2 0.76	25L6G 0.70	5702 1.20	E88CC 1.20	EC98 0.40
6A86 0.80	6F18 0.64	10D1 0.82	25Y5 0.80	5783 1.76	E82CC 0.70	EC98 0.40
6A95 0.76	6F23 0.80	10DE7 0.88	25Y5G 0.60	6057 1.00	E180CC 0.82	EC98 0.40
6A9 0.40	6F24 1.00	10F1 0.88	25Z4G 0.50	6060 1.00	E180F 1.17	EC98 0.40
6AK5 0.47	6F25 1.17	10F3 1.17	25Z5 0.75	6067 1.00	E182CC 3.00	EC98 0.40
6AK6 0.70	6F26 0.40	10F9 0.76	25Z6G 2.00	7193 0.62	E80F 2.00	EC98 0.40
6AK8 0.45	6F28 0.78	10F18 0.60	27 0.70	7197 1.17	E1148 0.82	EC98 0.40
6AL5 0.23	6F32 0.70	10L14 0.53	30A5 0.78	9002 0.59	E450 0.40	EC98 0.40
6AM6 0.50	6G6G 0.60	10LD11 0.82	30C1 0.47	9006 0.50	E476 1.40	EC98 0.40
6AM8A 0.70	6G8BA 0.88	10LP12 0.45	30C15 0.80	A1834 1.17	EAC80 0.45	EC98 0.40
6AN8 0.82	6CK5 0.76	10P13 0.88	30C17 0.85	A2134 3.06	EA91 0.65	EC98 0.40
6AQ5 0.53	6C6GT 0.88	10P14 2.34	30C18 0.85	A3042 0.66	EA92 0.68	EC98 0.40
6AV6 0.47	6H8GT 0.47	12A18 0.12	30F5 0.75	AC29EN 1.17	EA90 0.80	EC98 0.40
6ARS 0.80	6S5T 0.53	12A6 0.75	30F11 1.10	AC2PENDD	EB34 0.35	EC98 0.40
6AR6 1.17	6J6 0.35	12AC6 0.90	30F12 1.10	1.00	EB91 0.23	EC98 0.40
6AS7 1.17	6J7G 0.35	12AD6 0.90	30F13 1.05	AC6/PEN	EB41 0.88	EC98 0.40
6AT6 0.53	6J7M 0.65	12AE6 0.90	30F13 0.64	0.60	EB80 0.45	EC98 0.40
6AU6 0.40	6JU8A 0.88	12AT6 0.47	30FL14 0.82	AC/PEN(7)	EB91 0.53	EC98 0.40
6AV6 0.53	6K7G 0.35	12AT7 0.40	30L1 1.17	0.60	EB91 0.53	EC98 0.40
6AW8A 0.80	6K8G 0.53	12A18 0.53	30L15 0.82	AC/THI 1.00	EBF80 0.40	EC98 0.40
6AX4 0.88	6L1 2.34	12AU7 0.39	30L17 0.76	AL60 1.17	EBF83 0.50	EC98 0.40
					EL41 0.60	EC98 0.40

EL81 0.70	PC88 0.70	PY83 0.45	U17 0.90	1N4952 0.64	AF180 0.82	GD11 0.26	OC45 0.14
EL83 0.70	PC95 0.70	PY88 0.47	U18/20 1.17	2N404 0.23	AF186 0.71	GD12 0.26	OC46 0.26
EL84 0.36	PC97 0.42	PY90 0.59	U19 2.85	2N406 0.86	AF239 0.49	GD13 0.64	OC68 1.45
EL86 0.80	PC90 0.50	PY90A 1.11	U25 0.70	2N2147 1.10	ASV27 0.55	GD15 0.52	OC70 0.16
EL90 0.53	PC94 0.40	PY80 0.45	U26 0.85	2N2147 1.10	ASV28 0.42	GD16 0.26	OC71 0.14
EL95 0.70	PCC85 0.50	PY80 0.45	U31 0.30	2N2369A 0.18	AT102 0.59	GD18 0.26	OC72 0.14
EL360 1.20	PCC88 0.65	PY80 0.45	U33 1.75	2N2613 0.50	BA110 0.58	GET18 0.26	OC74 0.29
EM80 0.53	PCC89 0.60	QP21 1.10	U35 1.75	2N3053 0.42	BA116 0.23	GET19 0.33	OC75 0.29
EM81 0.76	PCC805 0.82	QQV03/10 1.17	U42 2.85	2N3121 3.22	BCY33 0.64	GET30 0.29	OC76 0.29
EM84 0.64	PCC806 0.76	2.10	U45 1.17	2N3073 0.25	BA130 0.13	GET32 1.23	OC77 0.35
EM85 1.20	PCF80 0.47	Q575/20 1.00	U47 0.70	2N3079 0.26	BA153 0.20	GET33 0.20	OC78 0.29
EM87 1.10	PCF84 0.70	Q585/10 1.00	U49 0.85	2N3866 1.20	BCY30 0.58	GET34 0.64	OC79 0.52
EMM803 2.50	PCF86 0.50	Q590/10 1.00	U50 0.55	2N3988 0.64	BCY32 0.64	GET37 0.29	OC81 0.14
EY51 0.50	PCF87 0.90	QV04/7 1.17	U78 0.80	AA1129 0.20	BCY38 0.29	GET38 0.29	OC82 0.14
EY81 0.50	PCF80 1.05	QV06/20 3.50	U153 0.40	AA1129 0.20	BCY38 0.29	GET39 0.29	OC83 0.26
EY83 0.70	PCF80 0.82	R11 0.80	U191 0.50	AA213 0.23	BC108 0.16	GET39 0.29	OC84 0.31
EY84 0.92	PCF80 0.65	R16 2.05	U192 0.40	AC107 0.20	BC109 0.16	GET39 0.29	OC84 0.31
EY87/6 1.00	PCF80 0.82	R17 1.00	U193 0.45	AC113 0.33	BC113 0.33	GET39 0.29	OC84 0.31
EY88 0.80	PCF80 0.85	R18 0.92	U251 0.94	AC114 0.32	BC115 0.20	GET39 0.29	OC84 0.31
EY91 0.50	PCF905 0.85	R19 0.75	U281 0.75	AC126 0.16	BC116 0.33	GET39 0.29	OC84 0.31
EZ30 0.50	PCF906 0.80	R20 0.65	U282 0.70	AC127 0.22	BC118 0.29	GET39 0.29	OC84 0.31
EZ40 0.40	PCF906 0.82	R22 0.55	U291 0.50	AC128 0.26	BF154 0.33	GET39 0.29	OC84 0.31
EZ41 0.55	PCH200 1.00	R52 0.55	U291 0.50	AC132 0.26	BF158 0.33	GET39 0.29	OC84 0.31
EZ80 0.35	PCL82 0.45	RK34 1.00	U301 0.65	AC132 0.26	BF158 0.33	GET39 0.29	OC84 0.31
EZ81 0.35	PCL83 0.50	SP13C 0.74	U329 0.94	AC154 0.33	BF159 0.33	GET39 0.29	OC84 0.31
EZ90 0.47	PCL84 0.50	TH4B 1.00	U339 0.50	AC136 0.26	BF163 0.28	GET39 0.29	OC84 0.31
FC4 1.00	PCL86 0.55	TH233 1.00	U381 0.50	AC137 0.33	BF173 0.40	GET39 0.29	OC84 0.31
FW4/500 1.17	PCL88 1.29	TP2620 1.00	U403 0.80	AC165 0.33	BF173 0.40	GET39 0.29	OC84 0.31
FW4/90 1.17	PCL80 1.11	TP22 1.00	U404 0.75	AC166 0.33	BF181 0.52	GET39 0.29	OC84 0.31
GW301 0.82	PCL805/5 1.17	TP25 1.00	U801 0.80	AC167 0.33	BF185 0.52	GET39 0.29	OC84 0.31
GZ30 0.55	PCL85 0.70	UABC8 0.67	U4020 0.75	AC168 0.40	BFY50 0.29	GET39 0.29	OC84 0.31
GZ32 0.59	PEN4DD 2.00	UAF 4.24	VP13C 0.60	AC169 0.42	BFY51 0.25	GET39 0.29	OC84 0.31
GZ33 1.46	PEN25 1.00	UBC41 0.80	VP23 0.85	AC176 0.71	BFY52 0.28	GET39 0.29	OC84 0.31
GZ34 0.90	PEN45 1.00	UBC81 0.80	VP41 0.86	AC178 0.33	BFY52 0.28	GET39 0.29	OC84 0.31
GZ37 1.20	PEN45DD 1.00	UBF80 0.47	VR105 0.59	ACY17 0.33	BTX34/400 2.57	GET39 0.29	OC84 0.31
HL480 0.80	PEN46 0.60	UBL21 2.34	VU111 0.80	ACY18 0.36	BY100 0.23	GET39 0.29	OC84 0.31
HL13C 0.80	PEN45DD 1.00	UC92 0.60	VU120 1.17	ACY20 0.23	BY105 0.23	GET39 0.29	OC84 0.31
HL23 0.70	PEN44 1.17	UCC34 0.90	VU120A 1.17	ACY21 0.25	BY113 0.23	GET39 0.29	OC84 0.31
HL23DD 0.80	PEN44 1.17	UCC35 0.88	VU133 0.86	ACY22 0.20	BY126 0.20	GET39 0.29	OC84 0.31
HL41 1.00	PEN44 1.17	UCF80 0.80	W78 0.50	ACY28 0.23	BY127 0.23	GET39 0.29	OC84 0.31
HL41DD 1.00	A020 1.00	UCH21 2.34	WR1M 1.17	AD140 0.47	BY213 1.29	GET39 0.29	OC84 0.31
HL42DD 1.00	PFL200 0.82	UCH42 0.88	W107 0.75	AD149 0.64	BY210 0.33	GET39 0.29	OC84 0.31
HN309 1.76	PL33 0.50	UCH81 0.47	W29 1.17	AD161 0.50	BY211 0.33	GET39 0.29	OC84 0.31
HVR2 1.00	PL38 0.70	UCL82 0.45	XE3 5.85	AD162 0.50	BY212 0.33	GET39 0.29	OC84 0.31
HVR2A 1.17	PL41 0.53	UCF83 0.56	XFY12 0.56	AF102 1.18	BY213 0.33	GET39 0.29	OC84 0.31
K72 0.88	PL82 0.43	UF80 0.82	X41 1.00	AF106 0.84	BY217 0.28	GET39 0.29	OC84 0.31
K78 2.93	PL83 0.50	UF85 0.52	X65 1.46	AF115 0.20	CG42 0.28	GET39 0.29	OC84 0.31
KT41 1.17	PL84 0.50	UF89 0.47	X66 1.46	AF121 0.29	FSY41A 0.28	GET39 0.29	OC84 0.31
KT44 1.17	PL302 0.88	UL41 0.75	X76M 0.85	AF125 0.33	GD4 0.42	GET39 0.29	OC84 0.31
KT63 0.80	PL304/500 1.00	UL84 0.49	XG515 1.17	AF126 0.22	GD5 0.36	GET39 0.29	OC84 0.31

BI-PAK SEMICONDUCTORS

COMPONENTS

CARBON RESISTOR PAKS
These Paks contain a range of Carbon Resistors, assorted into the following groups:-

- R1 50 Mixed 100 ohms — 820 ohms 1/4 W 0.60
- R2 50 Mixed 10K ohms — 82K ohms 1/4 W 0.60
- R3 50 Mixed 100K ohms — 820K ohms 1/4 W 0.60
- R4 50 Mixed 100 ohms — 820K ohms 1/4 W 0.60
- R5 30 Mixed 100 ohms — 820 ohms 1/2 W 0.60
- R6 30 Mixed 10K ohms — 82K ohms 1/2 W 0.60
- R7 30 Mixed 10K ohms — 82K ohms 1/2 W 0.60
- R8 30 Mixed 100K ohms — 820K ohms 1/2 W 0.60

These are unbeatable prices.

LOW COST CAPACITORS

500 µF	50V Elect	0.09 each
01 µF	400V	0.03 each

REPANCO CHOKES & COILS

RF Chokes	CHI 2.5mH	0.27
	CH3 7.5mH	0.29
	CH5 1.5mH	0.26
	CH2 5.0mH	0.28
	CH4 10mH	0.31

COILS

DRX1 Crystal set 0.29
DRR2 Dual range 0.42

CARBON POTENTIOMETERS

Log and Lin 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M.

- VC 1 Single Less Switch 0.20
- VC 2 Single D.P. Switch 0.40
- VC 3 Tandem Less Switch 0.60
- VC 4 1K Lin Less Switch 0.20
- VC 5 100K Log anti-Log 0.60

HORIZONTAL CARBON PRESETS

0.1 Watt 0.09 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M.

REPANCO TRANSFORMERS *

240V. Primary. Secondary voltages available from selected tappings 4V, 7V, 8V, 10V, 40V, 50V and 25V-0-25V.

Type	Amps	Price	P&P
MT50/1/2	1/2	£1.79	0.45
MT50/1	1	£2.24	0.48
MT50/2	2	£3.06	0.60

COIL FORMERS & CORES

NORMAN 1/2" Cores & Formers 0.07p
1/4" Cores & Formers 0.09p

SWITCHES

DP/DT Toggle 0.28p
SP/ST Toggle 0.22p

FUSES

20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A QUICK BLOW
Anti-surge 20mm only 0.05p each
0.8p each

VEROBOARDS *

VB 1 containing approx. 50sq. ins. various sizes all 0.1 matrix 0.60p
VB 2 containing approx. 50 sq. ins. various sizes all 0.15 matrix 0.60p

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen. Full instructions supplied with each pen 0.92p

BATTERY HOLDERS *

Takes 6 H.P. 7's complete with terminal clip and lead 0.31p each

V.A.T.

ALL PRICES EXCLUDE V.A.T.

Please add 8% to all prices marked *. Remainder add 25%. Do NOT add V.A.T. to prices marked †.

INSTRUMENT CASES



(In 2 sections. Black Vinyl covered top and sides and bezel)

No.	Length	Width	Height	Price
BV1	8" x 5 1/4"	x 2"		*£1.25
BV2	11" x 6"	x 3"		*£1.62
BV3	6" x 4 3/4"	x 1 1/2"		*£0.92
BV4	9" x 5 1/4"	x 2 1/2"		*£1.39

ALUMINIUM BOXES

No.	Length	Width	Height	Price
BA1	5 1/4" x 2 1/4"	x 1 1/2"		*0.45
BA2	4" x 4"	x 1 1/2"		*0.45
BA3	4" x 2 1/4"	x 1 1/2"		*0.45
BA4	5 1/4" x 4"	x 1 1/2"		*0.54
BA5	4" x 2 1/2"	x 2"		*0.45
BA6	3" x 2"	x 1"		*0.39
BA7	7" x 5"	x 2 1/2"		*0.79
BA8	8" x 6"	x 3"		*£1.02
BA9	6" x 4"	x 2"		*0.65

(Each complete with 1/2" deep lids & screws)

PLEASE ADD 20p POSTAGE AND PACKING FOR EACH BOX

COMPONENT PAKS

Pak No.	Qty	Description	Price
C1	200	Resistors mixed values approx. count by weight	.60
C2	150	Capacitors mixed values approx. count by weight	.60
C3	50	Precision Resistors mixed values	.60
C4	75	1/4 W Resistors mixed preferred values	.60
C5	5	Pieces assorted Ferrite Rods	.60
C6	2	Tuning Gangs. MW/LW VHF	.60
C7	1	Pak Wire 50 metres assorted colours	.60
C8	10	Reed Switches	.60
C9	3	Micro Switches	.60
C10	15	Assorted Pots & Pre-Sets	.60
C11	5	Jack Sockets 3 x 3.5m. 2 x standard Switch Type	.60
C12	30	Paper Condensers preferred types mixed values	.60
C13	20	Electrolytics Trans. types	.60
C14	1	Pack assorted Hardware: Nuts/Bolts, Grommets, etc.	.60
C15	5	Mains Slide Switches, 2 Amp	.60
C16	20	Assorted Tag Strips Panels	.60
C17	10	Assorted Control Knobs	.60
C18	4	Rotary Wave Change Switches	.60
C19	2	Relays 6-24V Operating Sheets Copper Laminate.	.60
C20		approx. 200 sq. ins.	.60

Please add 20p post and packing on all component packs, plus a further 10p on pack nos. C1, C2, C19 & C20.

AVDEL BOND



SOLVE THOSE STICKY PROBLEMS!
with
CYANOACRYLATE G2 ADHESIVE
The wonder bond which works in seconds. Bonds plastic, rubber, transistors, components, permanently, immediately!

OUR PRICE ONLY 70p *
for 2 gm phial

CABLES

CP	Description	Per Metre
CP 1	Single lapped screen	*0.08
CP 2	Twin Common Screen	*0.11
CP 3	Stereo Screened	*0.12
CP 4	Four Core Common Screen	*0.21
CP 5	Four Core individually screened	*0.28
CP 6	Microphone Fully Braided Cable	*0.11
CP 7	Three Core Mains Cable	*0.11
CP 8	Twin Oval Mains Cable	*0.08
CP 9	Speaker Cable	*0.06
CP 10	Low Loss Co-Axial	*0.14



Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.00

ANTEX EQUIPMENT

SOLDERING IRONS
x25. 25 watt £2.45
Model G. 18 watt £2.70
CCN 240. 15 watt £2.90
SK2.Soldering Kit £3.90

BITS AND ANOLEMENTS *

Bit No.	Model	Price
102	for model CN240	3/32" *42p
104	for model CN240	3/16" *42p
1100	for model CCN240	3/32" *42p
1101	for model CCN240	3/8" *42p
1102	for model CCN240	1/4" *42p
1020	for model G240	3/32" *42p
1021	for model G240	1/8" *42p
1022	for model G240	3/16" *42p
50	for model X25	3/32" *44p
51	for model X25	1/8" *44p
52	for model X25	3/16" *44p

ELEMENTS *

Model ECN	£1.10
Model EG 240	£1.35*
Model ECCN 240	£1.55*
Model EX 25	£1.20*

SOLDERING IRON STAND

ST3 Suitable for all models *£1.10
Antex heat shunt *10p

PLUGS

PS	Description	Price
PS 1	D.I.N. 2 Pin (Speaker)	0.10
PS 2	D.I.N. 3 Pin	0.11
PS 3	D.I.N. 4 Pin	0.14
PS 4	D.I.N. 5 Pin 180°	0.15
PS 5	D.I.N. 5 Pin 240°	0.15
PS 6	D.I.N. 6 Pin	0.16
PS 7	D.I.N. 7 Pin	0.17
PS 8	Jack 2.5mm Screened	0.17
PS 9	Jack 3.5mm Plastic	0.11
PS 10	Jack 3.5mm Screened	0.17
PS 11	Jack 1/4" Plastic	0.14
PS 12	Jack 1/4" Screened	0.20
PS 13	Jack Stereo Screened	0.33
PS 14	Phono	0.09
PS 15	Car Aerial	0.14
PS 16	Co-Axial	0.14

INLINE SOCKETS

PS	Description	Price
PS 21	D.I.N. 2 Pin (Speaker)	0.13
PS 22	D.I.N. 3 Pin	0.19
PS 23	D.I.N. 5 Pin 180°	0.19
PS 24	D.I.N. 5 Pin 240°	0.19
PS 25	Jack 2.5mm Plastic	0.15
PS 26	Jack 3.5mm Plastic	0.15
PS 27	Jack 1/4" Plastic	0.28
PS 28	Jack 1/4" Screened	0.32
PS 29	Jack Stereo Plastic	0.28
PS 30	Jack Stereo Screened	0.35
PS 31	Phono Screened	0.17
PS 32	Car Aerial	0.20
PS 33	Co-Axial	0.20

SOCKETS

PS	Description	Price
PS 35	D.I.N. 2 Pin (Speaker)	0.07
PS 36	D.I.N. 3 Pin	0.09
PS 37	D.I.N. 5 Pin 180°	0.09
PS 38	D.I.N. 5 Pin 240°	0.10
PS 39	Jack 2.5mm Switched	0.11
PS 40	Jack 3.5mm Switched	0.11
PS 41	Jack 1/4" Switched	0.19
PS 42	Jack Stereo Switched	0.28
PS 43	Phono Single	0.07
PS 44	Phono Double	0.09
PS 46	Co-Axial Surface	0.09
PS 47	Co-Axial Flush	0.19

P.C.B. KITS & PENS

PROFESSIONAL D.I.Y. PRINTED CIRCUIT KIT

Containing 6 sheets of 6" x 4" single sided laminate, a generous supply of etchant powder, etching dish, etchant measure, tweezers, etch resistant marking pen, high quality pump drill with spares, cutting knife with spare blades, 6" metal ruler, plus full easy to follow instructions. *£7.80 per kit

Spare container of etchant for above, complete with instructions *70p

P.C.B. MARKING PENS

2 x quality market pens, specifically designed for drawing fine etchant resistant circuits on copper laminate. Complete with full instructions *£1.53 per pair

LOW-NOISE CASSETTES

C60	*33p
C90	*44p
C120	*56p

SLIDER PAK

Containing a range of slider pots.
SP1 6 mixed values sliders 0.60
SP2 6 470R Lin. sliders 0.60
SP3 6 10K Lin. slider 0.60
SP4 6 22K Lin. sliders 0.60
SP5 6 47K Log. sliders 0.60
SP6 6 47K Lin. sliders 0.60

AUDIO LEADS

- S221 5 pin DIN plug to 4 phono plugs length 1.5m £1.08
- S222 5 pin DIN plug to 5 pin DIN socket length 1.5m .68p
- S237 5 pin DIN plug to 5 pin DIN plug mirror image length 1.5m £1.20
- S238 2 pin DIN plug to 2 pin DIN socket length 5m .68p
- S268 5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 length 1.5m £1.00
- S270 2 pin DIN plug to 2 pin DIN socket length 10m .80p
- S271 5 pin DIN plug to 2 phono plugs connected to pins 3 & 5 length 1.5m .70p
- S275 5 pin DIN plug to 2 phono sockets connected to pins 3 & 5 length 23cm .68p
- S318 5 pin DIN socket to 2 phono plugs connected to pins 3 & 5 length 23cm .68p
- S404 Coiled stereo headphones extension cord extends to 7m £1.40
- S217 3 pin DIN plug to 3 pin DIN plug length 1.5m .80p
- S219 5 pin DIN plug to 5 pin DIN plug length 1.5m .80p
- S474 3.5mm Jack to 3.5mm Jack length 1.5m .68p
- S600 5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m .80p
- S700 5 pin DIN plug to 3.5 Jack connected to pins 1 & 4 length 1.5m .80p

CROSSOVER NETWORK

K4007 1/P Impedance 8 ohms.
(2-way) Insertion Loss 3dB.
Crossover Frequency 3 KHz.
PRICE £1.12

3-WAY-STEREO H/PHONE JUNCT BOX

H 1012 Enables change-over from loudspeaker to headphone listening. Also has a centre position for both outputs. PRICE £1.73

HANDBOOKS

- TRANSISTOR DATA BOOK, DTE 2 227 Pages packed with information on European Transistors. Full specification including outlines. Price † £2.95 each
- TRANSISTOR EQUIVALENT BOOK BPE 75 256 Pages of cross references and equivalents for European, American and Japanese Transistors. This is the most comprehensive equivalents book on the market today and has an introduction in 13 languages. Price † £2.68 each
- DIODE EQUIVALENT BOOK DE 74 144 Pages of cross references and equivalents for European, American and Japanese Diodes, Zeners, Thyristors, Triacs, Diacs and L.E.D.'s. Price † £1.98 each
- MULLARD DATA BOOK 1976 MDB 74 The latest edition of this popular handbook contains information on Semiconductors, Integrated Circuits, Television Picture Tubes, Valves, Capacitors and Resistors. Included in the 161 informative pages are 21 pages on Semiconductor Comparables Price † £0.50 each
- TTL DATA BOOK DIC 75 Now complete Data book of 74 series TTL (7400-74132). Covering 13 main manufacturers in U.S.A. and Europe, this book gives full data as well as equivalents. Price † £3.74
- THE WORLD'S BROADCASTING STATIONS WBS 75 An up-to-the-minute guide for those interested in DX-ing. Contains all the world's broadcasters on SW, MW and LW, as well as European FM/TV stations. Price † £3.56

A full range of technical books available on request.

INDICATORS *

3013F Minitron 7 Segment Indicator *£1.11

SIL G.P. DIODES

300 mW 40 PIV(min) SUB-MIN FULLY TESTED
Ideal for Organ builders
30 for 50p*, 100 for £1.50*, 500 for £5*, 1,000 for £9*

CERAMIC PAKS

Containing a range of miniature ceramic capacitors in mixed values, unrepeatable value.

- MC1 24 ceramic capacitors: 22pF, 27pF, 33pF, 39pF, 47pF, 56pF, 68pF, and 82pF 0.60
- MC2 24 ceramic capacitors: 100pF, 120pF, 150pF, 180pF, 220pF, 270pF, 330pF, and 390pF 0.60
- MC3 24 ceramic capacitors: 470pF, 560pF, 680pF, 830pF, 1000pF, 1500pF, 2200pF, and 3300pF 0.60
- MC4 21 ceramic capacitors: 4700pF, 6800pF, 0.1µF, 0.15µF, 0.22µF, 0.33µF and 0.47µF 0.60

MAMMOTH I.C. PAK *

APPROX. 200 PIECES

Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked — you to identify. OUR SPECIAL PRICE £1.00

WORLD SCOOP *

JUMBO SEMICONDUCTOR PAK
Transistors — Germ. and Silicon. Rectifiers — Diodes — Triacs — Thyristors — I.C.'s and Zeners. ALL NEW AND CODED.


APPROX. 100 PIECES

Offering the amateur a fantastic bargain PAK and an enormous saving — identification and data sheet in every pak. ONLY £1.85 each

BIB HI-FI ACCESSORIES

REF	PRICE
'D' 2 Hi-Fi Cable & Flex Tidy	*34p
'J' Tape Head Cleaning Kit	72p
'P' Hi-Fi Cleaner	*30p
Model 9 Wire Stripper	*£1.00
23 1/4" Tape Editing Kit	*£1.80
24 1/4" Cassette Editing Kit	*£1.84
29A Salvage Cassette	*44p
32A	

BI-PAK

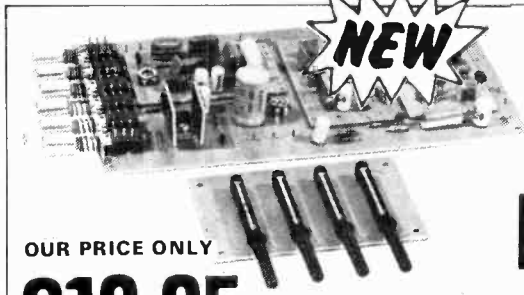

OUR PRICE ONLY

£19.95 Fitted with Phase Lock-loop Decoder


The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls. Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461. The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

PUSH-BUTTON STEREO FM TUNER

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v at 90 Ma max.

MPA 30

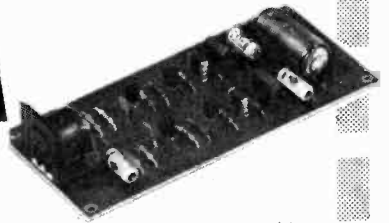

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

£2.65

STEREO PRE-AMPLIFIER



A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

MK. 60 AUDIO KIT: Comprising 2 x AL60's, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55.**

TEAK 60 AUDIO KIT: plus 62p postage. Comprising Teak veneered cabinet size 16 3/4" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £9.20** plus 62p postage.

Frequency Response + 1dB 20Hz 20KHz. Sensitivity of inputs
1 Tape Input 100mV into 100K ohms
2 Radio Tuner 100mV into 100K ohms
3 Magnetic P.U. 3mV into 50K ohms
P.U. Input equalises to R1AA curve with 1dB from 20Hz to 20KHz.
Supply - 20-35V at 20mA.

Dimensions 299mm x 89mm x 35mm

PA 100

OUR PRICE **£13.50**

AL10-20-30 AUDIO AMPLIFIER MODULES

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

SPECIFICATION:

- Harmonic Distortion Po = 3 watts f = 4 KHz 02.5%
- Load Impedance 8-16ohm
- Frequency response ± 3dB Po = 2 watts 50Hz-25Hz
- Sensitivity for Rated O/P - Vs = 25v, RL = 8ohm f = 1KHz 75mV.RMS

AL10 3w R.M.S. **£2.30** AL20 5w R.M.S. **£2.65** AL30 10w R.M.S. **£2.95**

VAT ADD 25%

POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

STEREO 30

COMPLETE AUDIO CHASSIS
7+7 WATTS R.M.S.



£15.75

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).

TRANSFORMER £2.45 plus 62p p & p
TEAK CASE £3.65 plus 62p p & p.



AL 60 25 Watts (RMS)

- ★ Max Heat Sink temp 90C.
- ★ Frequency response 20Hz to 100KHz
- ★ Distortion better than 0.1 at 1KHz
- ★ Supply voltage 15-50v
- ★ Thermal Feedback
- ★ Latest Design Improvements
- ★ Load - 3,4,8, or 16 ohms
- ★ Signal to noise ratio 80db
- ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast

£3.95



PA12

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL10/20/30 Amplifier

Modules. Features include on/off volume. Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

£6.50

PS12

Input voltage 15-20v A.C. Output voltage 22-30v D.C. Output current 800 mA Max. Size 60mm x 43mm x 26mm.

Transformer T538 **£2.30**

OUR PRICE **£1.20**

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size 63mm. 105mm. 30mm. Incorporating short circuit protection.


Transformer BMT80 **£2.60 + 62p postage**

£3.00

BI-PAK

P.O. BOX 6, WARE, HERTS.


TOYA

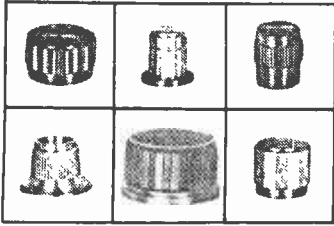

High quality competitively priced Knobs in production quantities only. Min. order 1000 Pcs of any one of 266 types!

KNOB CAT.: WW124 FOR FURTHER DETAILS

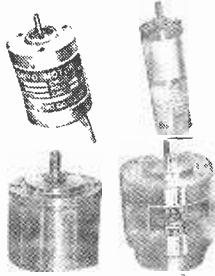We can now offer a range of Mini and Micro Motors with or without gear heads for AC and DC operation.



MOTORIZED ZOOM LENSES FOR TV & CCTV USE

DC pulse driven Turntable Units of especially high performance.

NDK CAT.: WW125 FOR FURTHER DETAILS

TABAI

ENVIRONMENTAL TEST EQUIPMENT

A Standard Range offering the following facilities:

- High temperatures to 500° C
- Low temperatures to -75° C
- Humidity Cycling
- Thermal Shock
- Vibration
- Pressure Cycling
- Sand and Dust exposure
- Corrosive Gas exposure
- Explosion Test




Also embraced in the range of manufacture are:

VACUUM DRYING EQUIPMENT HYPERBARIC OXYGEN SURGERY CHAMBERS

TABAI INFO.: WW126 FOR FURTHER DETAILS

ALPS LABORATORY TYPE SE65E

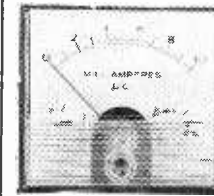

TYPE TAD

Dim's	48	66	85	118	150
in	x	x	x	x	x
mm	42	50	70	106	110
50µA	£3.73	£3.91	£4.10	£5.00	£5.55
500µA	£3.44	£3.61	£3.82	£4.72	£5.25
1mA	£3.37	£3.54	£3.74	£4.63	£5.33
15VDC	£3.40	£3.59	£3.77	£4.67	£5.36
300VAC	£3.87	£3.76	£3.94	£4.83	£5.40

VU METERS AVAILABLE.

TYPE SA

Dim's	43	51	61	82
in	x	x	x	x
mm	43	51	61	78
50µA	£3.62	£3.69	£3.97	£4.22
500µA	£3.31	£3.38	£3.63	£3.86
1mA	£3.21	£3.28	£3.53	£3.82
15VDC	£3.25	£3.32	£3.60	£3.86
300VAC	£3.49	£3.56	£3.77	£4.02




VU METERS AVAILABLE.

FOR YOUR PRODUCTION REQUIREMENTS USE

ALPS PANEL METERS

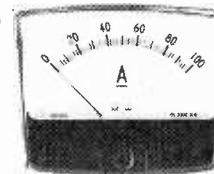Substantial quantity discounts to manufacturers
Remember! We are the sole importers!



TYPE SR

Dim's	73	78	92
in	x	x	x
mm	56	63	72
50µA	£4.03	£4.28	£4.52
500µA	£3.68	£3.93	£4.18
1mA	£3.58	£3.83	£4.08
15VDC	£3.70	£3.94	£4.19
300VAC	£3.93	£3.97	£4.32

SPECIALIST STOCKISTS OF SERVOMOTORS, SYNCHROS, TEST EQUIPMENT, METERS AND CONNECTORS

Servo and Electronic Sales Ltd

24 HIGH ST., LYDD, KENT TN29 9AJ. Tel. Lydd 20252 (STD 0679) VAT No. 201-1296-23. TELEX 965265



LEMANIA AIRCREW CHRONOGRAPHS

Stainless steel case with screw back, luminous hands and markings. One-fifth sec. sweep hand controlled and independently of main movement by press to start stop and return to zero button. 15-jewel movement. Many of these watches are as new but all have been completely overhauled and checked for accuracy. Fitted strap. White face £18.80. Black face £19.75 inc. P & P.

GS WATCHES

All with brushed stainless steel case with screw back and black faces. Manufactured by TIMOR, ETERNA, LEMANIA, VERTEX RECORD, CYMA, etc. to a standard specification. Completely overhauled. Fitted strap £9.05 (inc. P & P). We also have limited quantities of these watches, by BUREN, HAMILTON and IWC at £18.50 inc. P & P. SMITHS GS watch with sweep second hand £9.25 inc. P & P. VAT. All watches: Inspection against remittance.




PANEL DISPLAY RECORDING CAMERA

Manufactured A.G.I. Specifically for the recording of complex instrument displays on 2 1/4" x 2 1/4" shots. Fitted 80mm F3.5 lens. Shutter speeds 1/100, 1/50, 1/25 sec. and time exp. Focusing at 1.75 to 50ft. in 18 steps. Aperture settings F3.5 to F22. Prismatic viewfinder and facility for viewing direct on ground glass screen. Rotating filter attachment. Cord film advance and shutter cock with separate Button control and electrical release facility (24V DC). Spool holds 40 exposures. Camera may be wall mounted on bracket supplied. Tripod mounting socket provided. In wooden case. Two grades available as new. Grade A £35.50 (inc. P & P and VAT). Somewhat used but serviceable Grade B £28.40 (inc. P & P and VAT).

NEW ADDITIONS to our range of PANEL METERS available at present only in MANUFACTURING QUANTITIES

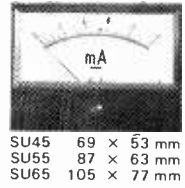- SE45 64 x 52 mm
- SE52 80 x 60 mm
- SE65 100 x 80 mm
- SE85 120 x 100 mm



- SU45 69 x 53 mm
- SU55 87 x 63 mm
- SU65 105 x 77 mm

Above meter forms are for moving coil movements only and may house S-meter and VU-meter instruments.

MIL SYNCHROS AND SERVOMOTORS

COMPUTERS AND PERIPHERALS

ICL 1904 CPU (complete) - documentation will be available - with 32k 2uS Plessey core store £1000. ICL 7070/2 UNIPLEXER (Complete) £150. BRPE 110 ch/sec. 8-channel paper tape punches - some silence covers £120. Plessey 68/1339 16K (13 bit) 1uS corestores £35. Mullard AW 3331 16K (25 bit) 2uS corestores £40. Mullard AW 3795 corestores £30. IBM 729/IV M-TUJ - documentation available £200. ICL mainframe PSUs 6V 25A and 28V 20A (p.40) £25. ICL peripheral PSUs - 10V and -20V £20. Ampex & DRI digital tape heads (7 & 9 track) P.O.A. ICL 1971 & 1973 servo motors & vacuum blowers P.O.A. CDC/ICL 2802 (EDS8) disc drives - mechanical spares P.O.A. RCA/ICL 1500 series - electrical & mechanical spares P.O.A. Belling Lee R F I suppressors - 30 20A (50Hz) £30. STC Sentrycal fire (smoke) detectors - data available £15. Vactric Shaft position encoders type 110P101 (10 bit) £15. Tolana 8-channel FM instrumentation recorder (complete) £350.

We can also design and construct non-standard interfaces between computers instrumentation and control equipment and we have a large number of one-off pieces of test equipment. If you have any problems in this field do not hesitate to get in touch with us. Contact D.P. Manager Chms Seton (Ext'n 3) GE Optical Tape Readers 5 7 and B-track 300 ch/sec. built-in amps and contacts. Excellent condition. Tested £70 inc. P & P and VAT.

OVER 300,000 RF AND MULTIWAY CONNECTORS IN STOCK. TELEX YOUR REQUIREMENTS NOW!

LEMANIA STOPWATCHES

Fitted with one red and one black sweep hands independently controlled enabling elapsed periods forming part of the main period to be measured separately without stopping the measurement of the main time period. Absolutely mint condition but cleaned and checked. £18 inc. P & P. & VAT.

1/10 SEC. STOPWATCHES

Overhauled, £8.50 (inc. P & P. & VAT).

1/100 SEC. STOPWATCHES

0-6 sec., £8.60 (inc. P & P. & VAT).

CAMBRIDGE INST. MIRROR GALVOS

4.50 ohm. £10 (inc. P & P. & VAT).

500-WATT CW TRANSMITTERS

1.5 to 26MHz. P.O.A.

HEAVY DUTY FLEXIBLE POWER CABLES


Type A 2 core each 750A 440 VAC. Type B 4 core each 200A 440 VAC 100 ft lengths.

REED SWITCH INSERTS

Overall length 1.85in (Body length 1.1in) Diameter 0.14in to switch up to 500mA or 250VDC Gold clad contacts 74p per doz. £4.15 per 100 £28.85 per 1,000. All carriage paid U.K. Operating Coils for 12v supply to accept up to four standard reeds £2.50 per doz. £12.60 per 100. All carriage paid U.K. Heavy duty type (Body length 2in) Diameter 0.22in to switch up to 1A at up to 250VAC Gold clad contacts £1.45 per doz. £6.95 per 100. £52.00 per 1,000. Changeover Heavy Duty type £2.80 per doz. All carriage paid U.K. Magnets for HD reeds £1.50 per doz. A few coils available for HD reeds.

FORTHCOMING EXHIBITIONS IEA-Electrex 1976 National Exhibition Centre, Birmingham, 3-7 May 1976
Leetronex 1976, Leeds University, 29-30 June, 1 July, 1976
Tickets free on receipt of SAE (1 for each Exhibition please)

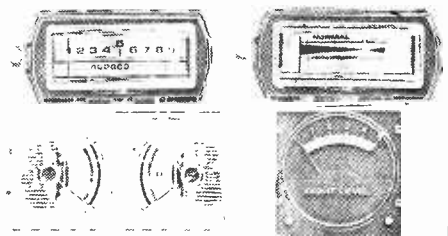
MULTIRANGE TEST METERS & LOW-PRICE INDICATORS AND PANEL METERS AVAILABLE WITH PERSONALISED SCALES



METERS CAT.: WW127 FOR FURTHER DETAILS

TEAC

TEAC A3340(S)
4-CHANNEL
RECORDER

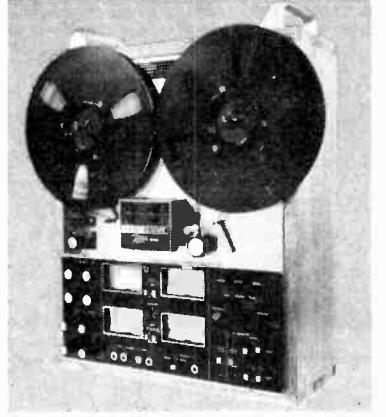

Industrial version upgraded to studio requirements, with increased signal to noise performance and improved reliability. Four totally independent channels each with sel sync, input mixing, switchable VU's and all the facilities for easy multitracking. This industrial model is in more studios than any other version.

Available only from ITA
(Semi-pro version also available)
IMMEDIATE DELIVERY

REVOX

REVOX A-700 SERIES



The new big Revox — ideal for all studio requirements. Highly sophisticated design features include servo tape tension, full deck logic, crystal controlled servo electronics, 3 speeds, tape footage counter.

£635 IMMEDIATE DELIVERY

The famous A-77 SERIES Mk 4




The famous A-77 has been consistently improved over the past 8 years and is now available in the latest Mk 4 version. The wide choice of specifications includes versions for duplicating and logging applications. Backed by UK's latest fastest service.

Hire service Check our prices from **£298**
IMMEDIATE DELIVERY

ITA

ITA 10-4
MODULAR MIXER

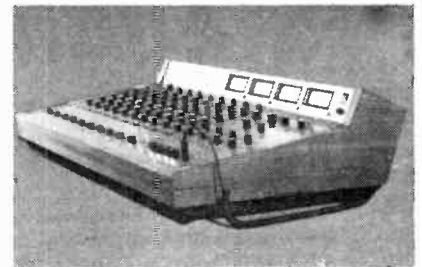

Ten balanced inputs, four output groups, 4 limiters, bass mid and treble EQ, modular construction, headphone monitoring. Extremely high quality construction only matched by mixers costing around £1,000.

10-4 **£647**
20-4 **£1095**
EIGHT OUTPUT **£1260**

IMMEDIATE DELIVERY

Also available for hire

PRICES EXCLUSIVE OF V.A.T.

Industrial Tape Applications



5 Pratt Street, London NW1 0AE
Telephone: 01-485 6162. Telex: 21879

WW — 104 FOR FURTHER DETAILS

Samson's

(ELECTRONICS) LTD.

9 & 10 CHAPEL ST., LONDON, N.W.1
01-723 7851 01-262 5125
ADJACENT TO EDGWARE ROAD MET. LINE STATION

CURRENT RANGE OF NEW L.T. TRANSFORMERS OPEN TYPE TAG CONNECTIONS ALL PRIMARIES 220-240V

Type	Sec. Taps	Amps	Price	Carr
1	24.30-40-48-60v	12	£20.25	12.00
2	24.30-40-48-60v	10	£19.40	12.00
3	24.30-40-48-60v	8	£15.75	11.50
4	24.30-40-48-60v	5	£10.24	11.00
5	24.30-40-48-60v	3	£7.90	7.5p
6	24.30-40-48-60v	2	£5.53	7.5p
6.8-10-12-16-18-20-24-36-40-48-60v CAN BE OBTAINED FROM THE ABOVE RANGE				
7	19.25-33-40-50v	10	£17.75	12.00
8	19.25-33-40-50v	6	£12.00	11.25
9	19.25-33-40-50v	3	£6.00	7.5p
10	19.25-33-40-50v	2	£4.95	7.5p
5-7-8-10-13-15-17-20-25-30-40-50v OR 25-0-25v or 20-0-20v CAN BE OBTAINED FROM THE ABOVE RANGE				
11	12.15-20-25-30v	10	£10.35	11.25
12	12.15-20-25-30v	5	£6.70	11.00
13	12.15-20-25-30v	2	£3.75	7.5p
3-4-5-6-8-9-10-12-15-18-20-24-30v or 12-0-12v or 15-0-15v CAN BE OBTAINED FROM THE ABOVE RANGE				
14	12.24v	12v 60A 24v 30A	£17.50	12.00
15	12.24v	17v 30A 24v 15A	£14.25	11.50
16	12.24v	12v 20A 24v 10A	£10.75	11.25
17	12.24v	12v 10A 24v 5A	£5.50	7.5p
18	12.24v	12v 4A 24v 2A	£2.95	60p

FULLY SHROUDED TYPE TERMINAL CONNECTIONS

19	4.16-24-32v	4	£6.95	7.5p
20	4.16-24-32v	2	£4.65	6.5p
21	1.20-24v	10	£9.50	11.00
22	12.20-24v	5	£6.50	7.5p
23	24.30-36v	10	£12.00	11.25
24	24.30-36v	5	£9.50	11.00
25	24.30-36v	2	£4.50	6.5p

WOODEN AUTO TRANSFORMERS

3000 watts tapped 105-115-125-135-200-215-230-245-260 open type terminal block connections, £19.50, carr. £2.00. Isolation type 750 watts P.P. tapped 220-220-240v Sec. tapped 100-110-150v Terminal block connections, £15.00, carr. £2.00

PLEASE ADD 3% TO ALL ORDERS INC. CARR.

AUTO TRANSFORMERS FOR AMERICAN EQUIPMENT

240/110v 80-3000 watts fitted with 2-3 pin sockets and 3 core mains lead. Send sae for price list. We have England's largest selection of American electrical accessories: 2-3 pin plugs, recessed and surface type 2-3 sockets multi-way adaptors 2-3 pin grounding adaptors Cable type sockets Extension cords 240v Edison screw type light bulbs Industrial plugs and sockets. Let us know your requirements

PARMEKO 240/115V ISOLATION TRANSFORMERS

P.P. tapped +10v 10v 0-115-200-225-250v 7v x 115v 13.5A conservatively rated. Shrouded table top connections. Size 12 x 9 1/2 x 8 1/2 ins. £32.50, carr. £3. P.P. tapped +10v 10v 0-200-220-240v Sec. tapped +10v 0-90-110v 7.5 A conservatively rated. Shrouded table top connections. Size 7 1/2 x 8 x 8 ins. £19.50 + carr. £3. T.E.C. isolation transformers. P.P. 240v. Sec. tapped 265-270-275v 1400 watts conservatively rated. Size 8 x 8 x 7 ins. £25.00, carr. £3.

GRESHAM L.T. TRANSFORMERS

All primaries tapped 10-0-200-220-240v open type tropicalised Terminal block connections fraction of maker's price. No 1 sec. tapped 0.4-16-17-18-19-20v 20A £7.00. No 2 4.7-11-31-32-33-34v 20A £8.50. No 3 4.7-11-32-33-34-35v 10A £6.50. No 4 6-13-20-54-56-58-59v 5A £6.50. Carr. on all types. L.C. core types, all primaries, 200-220-240v. No 1 4 separate secs 1v, 3v, 9v, 27v. All at 15A £12.00. No 2 3 separate secs 29-30-33v, 15A. £23-24-26v 5A 14-15-17v 5A £12.00, carr. £2.

PARMEKO L.T. TRANSFORMERS

No 1 Open Type P.P. 110-220-240v Sec. 30v 5.5A and 12v 2.2A and 115v 250 M.A. £4.95, P.P. 95p. No 2 Potted type P.P. 115-230v Sec. tapped 24-30-32v 2A £2.95, P.P. 50p. No 3 Potted type P.P. 115-230v 6.3v 1.8A, 5.3v 1A £2.00, P.P. 50p. No 4 Shrouded type P.P. 220-240-250v Sec. 6.4-0-6.4v 12A £4.50, P.P. 50p. No 5 P.P. 115-220-230v Sec. 6.6v 6A twice and 5v 6A will give 13.2v 6A and 5v 6A or 6.6v 12A and 5v 6A or 18.2v 6A Potted type £4.95, P.P. 95p. No 6 P.P. 200-220-240v Sec. 39v 8.6A and 38v 2.6A and 127v 25M.A. Potted type £6.00, carr. £1.50. No 7 P.P. 110-230v Sec. Tapped 40-45-50v 5A Potted type £6.50, P.P. £1.50

GARDNER HIGH VOLTAGE ISOLATION TRANSFORMERS

P.P. 230-240v Screen Sec. 2-0-2v 11 amps conservatively rated 25Kv insulation Encapsulated type £6.50 carr. £1.50

A.E.I. 240V AC CONTACTORS

Type	Contacts	Price
0656	6M 2B	£1.50
0659	3M 1B	£1.25
0658	2M 2B	£1.25
AC 110v Types		
0651	3M 1B	£1.25
0654	2M 2B	£1.25
0653	4M	£1.25

Brand new and boxed offered at a fraction of maker's price P.P. all types 25p

MINIATURE RELAYS PLESSEY VARLEY

52v 4 CO 75p, 52v 2 CO 60p, 280v 4 CO 60p, 430v 4 CO 60p, 430v 2 CO 50p, 1250v 4 CO 60p. Postage 10p per Open type size 1 1/4 x 1 1/4 ins 6v DC 1 CO 35p, P.P. 10p

BENSON SOLENOIDS

AC 240v 25% duty Approx 2 ins 1/2 in pull Size 2 1/2 x 1 1/2 ins Res 350v 75p, P.P. 25p

HIGH VOLTAGE BLOCK CAPACITORS

Jensen 0.22mfd 7000v AC Wkg £2.00, P.P. 75p Wago 0.215mfd 1250v RMS Pulse Wkg £1.50, P.P. 50p T.C.C. 8mfd 2500v DC Wkg £3.00, P.P. 75p 0.5mfd 10,000v DC Wkg £3.00, P.P. 75p 0.5mfd 5000v DC Wkg £2.00, P.P. 50p 0.5mfd 2500v DC Wkg 65p, P.P. 20p

AC WKG BLOCK CAPACITORS

Dublier 15mfd 330v AC Wkg £1.25, P.P. 25p 10mfd 350v AC Wkg £1.00, P.P. 25p 5mfd 300v AC Wkg 75p, P.P. 25p 4mfd 650v AC Wkg £1.50, P.P. 25p 4mfd 500v AC Wkg 75p, P.P. 25p T.C.C. 4mfd 250v AC Wkg 50p, P.P. 20p 2.5mfd 300v AC Wkg 50p, P.P. 20p 1.5mfd 400v AC Wkg 75p, P.P. 20p 0.4mfd 440v AC Wkg 50p, P.P. 20p Bosch 1mfd 800v AC £1.00, P.P. 20p

DC WKG BLOCK CAPS

TCC 2mfd 100v DC Wkg ideal for crossover circuits 10 for £1.50, P.P. 25p 2mfd 500v DC Wkg 5 for £1.50, P.P. 50p BICC 4mfd 800v DC Wkg 50p, P.P. 20p TCC 8mfd 350v DC Wkg 50p, 8mfd 200v DC Wkg 35p, P.P. all types 20p 4mfd 1250v DC Wkg £1.00, 4mfd 600v DC Wkg 50p, 4mfd 350v DC Wkg 40p, 2mfd 2000v DC Wkg 65p, 1mfd 2500v DC Wkg 65p, 1mfd 2000v DC Wkg 60p, 1mfd 600v DC Wkg 25p, 0.5mfd 2500v DC Wkg 50p, 0.1mfd 3000v DC Wkg 50p, P.P. all types 20p All wkg. voltages are at 60 C.

HEAVY DUTY BALLAST RESISTORS

Enclosed type 1 1/2 x 1 1/2 A Size 19 x 3 1/2 ins £3.00, BSJ 1 1/2 A Size 15 x 3 ins £2.00, P.P. either type High volt 500 Megohm 25Kv Resistors length 17 ins dia 2 1/2 ins £3.00, P.P. 75p Berco Tubular v resistors 30j 1 1/2 A right angle geared drive control £1.50, P.P. 50p Widen and Simular 7-10 watt WW resistors (10-15K) 25 assorted £1.25, P.P. 20p

VENNER INDUSTRIAL TYPE

Time switch motors AC 240v 1 rev per 24 hours housed in metal case 5 ins dia £2.00, P.P. 50p

L.T. TRANSFORMERS BY FAMOUS MAKERS

Open types No 1 P.P. 240, Sec. 26v 10A and 12v 0.1A £5.50, No 2 P.P. 220-240v Sec. Tapped 51-61-65-67-69, 10A £10.00, carr. £1.50 No 3 P.P. 220-240v Sec. Tapped 58-63-69-74 3A, £4.75, carr. £1 No 4 P.P. 117-220-240v Sec. 28-0-28v 3A and 30-0-30v 100MVA and 6v 1A £3.50, P.P. 75p No 4 P.P. 115-230v Sec. 30-0-30v 4A and 10-0-10v 1/2A, £3.75, P.P. 75p No 5 P.P. 115-230v Sec. 33v 6A and 18-0-18v 1A, £3.00, P.P. 75p No 6 P.P. 110-200-220-240v Sec. 14v 5A 14v 2.5A, 12v 10A 8v 10A 24v 750MVA, 200v 500MVA Separate windings £10.00, carr. £1.50 No 7 P.P. 200-220-240v Sec. 4v 6A 4v 3A, £3.50, P.P. 75p No 8 P.P. 110-220-235v Sec. 12v 2.2A and 12v 1A and 200v 35MVA £2.50, P.P. 75p No 9 P.P. 200-220-240v Sec. 37v 5.5A and 37v 2A and 21v 11A £8.50, carr. £1.50 No 10 P.P. 200-220-240v Sec. 31v 7A 26v 5A 16v 4A 25v 2A Separate windings £8.50, carr. £2.00 No 11, C core types P.P. 220-240v Sec. 18-0-18v 21A £10.00, No 12 P.P. 230v Sec. 1.25-0-1.25v 10A £2.00, P.P. 50p No 13 Potted types, P.P. 110-220-240v Sec. 70v 1A and 30v 1A, £3.50, carr. £1 No 14 P.P. 115-220-240v Sec. 43v 0.75A and 43v 0.5A and 6.3v 1A, £3.50, P.P. £1 No 15 P.P. 110-220-240v Sec. 29.7v 5A 23v 1/2A 78v 60MVA 181v 100MVA Separate windings £6.00, carr. £1.50 No 16 P.P. 220-240v Sec. 12v 6A and 15.6v 1.5A £4.00, carr. £1.50 No 17 P.P. 220-240v Sec. 50v 2A £3.00, P.P. 75p No 18 P.P. 110-220-240v Sec. Tapped 4.3-3-3v 3v 10-11-12-22-23-24-25-26-26-26-26v 45MVA £4.00, P.P. £1 No 19 P.P. 200-220-240v Sec. 60v 1A twice £2.00, P.P. 75p No 20 P.P. 200-220-240v Sec. 105v 2A £2.00, P.P. 75p No 21 P.P. 200-220-240v Sec. Tapped 4.5v 8A £2.00, P.P. 75p No 22 P.P. 220-240v Sec. 22 25v 3.5A and 26v 45MVA £4.50, P.P. £1 No 23 P.P. 110-220-240v Sec. 62v 1A and 6v 6A £4.50, P.P. £1 No 24 P.P. 110-220-240v Sec. 6.7v 3.8A twice 7v 2.4A twice 6.7v 0.6A £3.50, P.P. £1 Open type No 25 P.P. 220-240v Sec. 55v 1A £2.00, P.P. 50p No 26 P.P. 110-220-240v Sec. 50v 1/2A and 10v 1.5A £2.50, P.P. 75p No 27 P.P. 110-220-240v Sec. 4v 2A £1.00, P.P. 35p No 28 P.P. 240v Sec. 24v 2A, £1.50, P.P. 50p No 29 P.P. 240v Sec. 30v 1A twice £2.00, P.P. 50p No 30 P.P. 240v Sec. 40v 50MVA and 60v 50MVA No 31 P.P. 115-220-240v Sec. 17-0-17v 1.2A and 36v 50MVA No 32 P.P. 240v Sec. 40v 6A and 5-0-5v 2A and 5-0-5v 1/2A £4.75, carr. £1.75p High Voltage Transformers Gresham P.P. 240v Sec. 2300v 10MVA 3-1.5A Open type Table top connections £3.50, P.P. 50p Woden P.P. 230v Sec. 890-710-0-710-890 120 MVA Open type T.T. connections £3.75, P.P. 75p Parmeko potted type P.P. 110v 220-240v Sec. 187.5v 60 MVA £4.4v 6.5v 3A £4.50, carr. £1.50 All transformers are offered at a fraction of maker's price. Guaranteed in perfect condition. As supplied to the electronic industries, universities, schools, etc.

YOU COULD SAVE UP TO **€1,000** *pa* PER ENGINEER * With THIS BOOK


* With the Colour Faults Guide system of rapid, on-the-spot diagnosis of colour set faults the originating firm, Colour Vision Rentals Ltd, reported savings of the order of **well over €1,000 per engineer per year.**

HOW IT IS DONE . . . A tabulated index of fault symptoms and the most common circuit troubles causing them quickly enables the engineer in the customer's home to locate the cause of the breakdown and the panel or assembly in which it has occurred. He can then change the panel (etc) on the spot from his van stock and return the faulty item for repair subsequently, and return to stock. The originating firm calculates that an average of about 3 hours a week per engineer is saved, plus an average of one workshop uplift less per engineer — hence the €1,000-plus per year saving.

The Colour Faults Guides, E R T's top innovation of 1974-5, covering 14 widely used chassis, are now collected in book form for sale at €1.70 inclusive per issue.

CAN YOU AFFORD YOUR MEN NOT TO HAVE A COPY WITH THEM ON EVERY JOB?

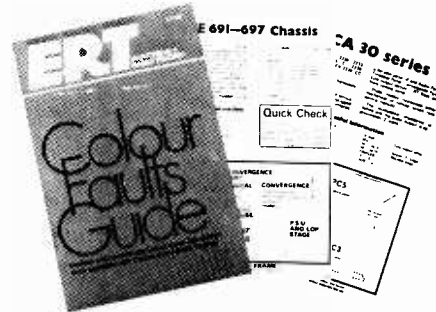The fourteen chassis covered in the book comprise:- Decca 30 series; GEC 2210 series; GEC Hybrid 2040 series; Hitachi range — CAP 160, CEP 180, CNP 190; ITT CVC5; Philips G8; Pye CT200 series, Pye 691-697; Rank R I A823/A; Thorn C E 3000 & 3500; Thorn (BRC) 8000/8500 series; Bang & Olufsen 39 series — Beovision 3500, 3600, 400, 600; Skantic — all models except earlier 22in. hybrid.



Order Coupon
 To General Sales Dept., Room 11, ERT, Dorset House, Stamford St., London SE1 9LU

Please send me copy/copies of Colour Faults Guide at €1.65 inclusive


I enclose remittance value € (Cheques payable to IPC Business Press Ltd.)

Name (please print)

Address

Company regd. in England No. 677128
 Regd. office: Dorset House, Stamford St., London SE1 9LU

PRINTED CIRCUIT BOARD TRANSFER SYSTEMS

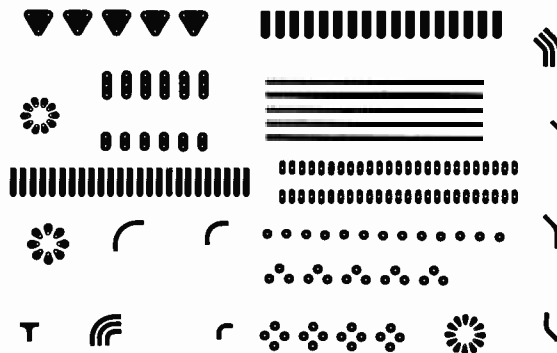

Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes — i.e. edge connectors, lines, pads, dual in line I.C.s, 8-10-12. T.O.5 Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry. A full money back guarantee is sent with each order, trade prices on application.

List of Prices

Complete system including post and VAT	€2.95
Individual sheets	30p
Sample sheet	30p
Ex. U.K. Post Extra	€1.00

Printed circuit board PCB transfer systems patent applied for

E. R. NICHOLLS, 46 LOWFIELD ROAD, STOCKPORT, CHESHIRE
TELEPHONE NUMBER 061-480 2179


P. F. RALFE 10 CHAPEL ST. LONDON N.W.T.
Phone 01-723 8753

SIGNAL GENERATORS



MARCONI TF801D/1S. 10-480 mHz P.O.A.
MARCONI TF801B/2S. 10-480 mHz £225.
HGN MS3/U. 9.7-11.9 and 77-109 mHz. AM/FM.
ADVANCE SG63D. AM/FM 7.5-230mHz £125.
RACAL/AIRMEC 201A. 30kHz-30mHz. As new. P.O.A.
ADVANCE SG21 VHF Square-wave generator 9kHz-100mHz. £25.

OSCILLOSCOPES

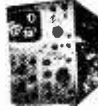

SOLARTRON CD1400 DC-15mHz
COSSOR CDU110. DC-80mHz
TEKTRONIX 545A with CA unit. DC-30mHz. Price only £295.00
TEKTRONIX 531 DC-15mHz with L type plug-in
TEKTRONIX 535 DC-15mHz with L type plug-in
TEKTRONIX 545B DC-30mHz with 'CA' plug-in.
TEKTRONIX 585A. DC-80mHz with type 82 plug-in.
TEKTRONIX 654B. Storage oscilloscope.
TEKTRONIX 502. 200uV. Sens. X-Y.
TEKTRONIX C27 Polaroid Camera. Series 125 with 560 series adapter.

CO-AXIAL CHANGE OVER RELAYS. Terminated in N-type sockets (3 off) Suitable for frequencies up to 1GHz 48 V D C coil Plugs available at 50p each Relay only £5.50 each

PRINTED CIRCUIT MOTORS. Manufactured in U S by Photocircuits Corp 24 V D C 2,000 rpm 14 cms diameter. These are quality made, high precision motors offered at a fraction of list price. Only £8.50 each

"WEE MEGGERS". 250V Insulation Testers Good working condition £8.50.

'MUFFIN' INSTRUMENT FANS. Manufactured in Holland by Rotron Dims 4.5x4.5x1.5 ins This is a precision cooling fan, very quiet running specially designed for the cooling of electronic equipment, amplifiers, etc 115V.50Hz operation, drawing only 11 Watts. The list price from Rotrons is over £10 each. Our price, brand new, only £4.50 each

MINIATURE DEAC NI-CADMIUM batteries, type 70CK 3 cells in package making 3.7 Volts 25x17x15mm only 75p post paid

E.M.I. oscilloscopes type RMO15 Response to 40mHz. 5 inch CRT 10KV E.H.T. We can offer these quality oscilloscopes at the exceptional price of only £35 each to callers only

ADVANCE type 63A AM/FM R.F. Signal generators 7.5-230mHz Deviation 0-22.5 and 0-75 kHz. X-sweep output. Crystal calibrator, scope output. £75.00.

MARCONI TF995A2/M AM/FM R.F. SIGNAL GENERATORS. 1.5-220mHz. 0-100kHz Deviation. 1µV-100mV output. Sold in excellent condition, P.O.A.

METRIX 210 WOBBLATORS. 0-25mHz Sweep width 0.5-20mHz Output 100mV attenuable in steps of 10 to 10uV. Last few of these left at only £15.00 each to callers only.

E.M.I. oscilloscopes model WM16 with type 7/1 W.B.A. plug-in unit Supplied in perfect condition complete with trolley £125.00.

20-way BPO Jack strips to accept 316 type Jack plugs. Also quantity of 316 plugs available. All good condition.

Centrifugal blowers by **WOODS** 8 inch snail type Outlet 2 3/4 x 2 in 24V DC 2.8A 2400 r.p.m. Grey stove finish All brand new. Price is £10.50 + carriage

GENTS/FRIEDLAND fire alarm bells Operating voltages 12v dc/24v dc All in as new condition and tested before despatch. Sizes 6/8/12 inch Prices £4.80, £5.20 and £6.50 resp.

COMPUTER PERIPHERALS. Tape punches 8 hole by Westrex and other well known manufacturers. Tape readers by Elliot. All virtually brand new. Prices are better than one half the maker's. Write or phone for quotation.

An exceptional buy enables us to offer stabilised and regulated power supplies by APT at a very cheap price. 16-24v dc @ 10 Amps, and 8-10v dc @ A. Both supplies are extremely stable with low ripple voltage. Price each £18.50 + carriage

MISCELLANEOUS TEST EQUIPMENT

MARCONI TF1400S double pulse generator with TM6600/S secondary pulse unit. £105.
MARCONI TF791D deviation meter. 4-1024mHz 0-100kHz deviation.
MARCONI 455E Wave Analyser £120.
MARCONI TF2600 Valve Voltmeter 1mV-300V. Excellent £75.
ROHDE & SCHWARZ USVD calibrated receiver 280-940mHz (4600mHz)
LEVELL TG200 DM. RC Oscillator. c/w case. £65.
ROHDE & SCHWARZ URV milli-voltmeter BN10913 (late type) 1mV-10V. With 'T' type insertion unit, free probe and attenuator heads. 1kHz-1.600mHz. £175.
COSSOR 1453 True RMS milli-voltmeter Excellent £75.
AIRMEC TYPE 210 modulation meter. Excellent condition.
ROHDE & SCHWARZ 'SCR' V H F. Signal Generator 1000-1900 mHz.
MARCONI type TF936 Impedance Bridge. £85.00.
GERTCH Phase Angle V. Meters. Range 1mV-300V. in 12 ranges
SOLARTRON oscillator type CO 546 25Hz-500kHz. £30.00.
GAMBRELL Precision 4 Decade Resistance Box. 1-11, 110 ohms. £24.50.

PLEASE ADD 8% V.A.T. TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH. THANK YOU.



With our New
ORYX SUPER 30
soldering iron
we have a slight
problem
at £2.95* how
do we convince
you that it is a
precision tool.

Our reputation for professional soldering equipment has been built on our precision products, so we have taken extreme care to see that our new ORYX Super 30 iron at, dare we repeat it, only £2.95, is going to be the best at its price.

* plus VAT at 8%

Here are some of the features you get as standard:

- A neon Safety Light,
- A long life element,
- Iron coated screw-on tip,
- Stainless steel shaft,
- Styled handle,
- A two-minute element change, and a Stainless steel clip-on hook.

You can have further technical information, or by ordering one now you will see why we call it the Super 30.

Illustration actual size.

Greenwood Electronics


Greenwood Electronics Portman Road Reading, RG3 1NE
Telephone: 0734-595844 Telex 848659

Attenuate with Hatfield

Now with the latest additions to the range, you can select for ALL your needs from the following:

2100 Series:

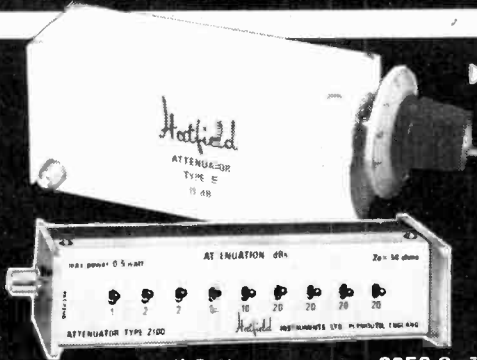8 models covering impedances of 50Ω, 75Ω, 600Ω unbalanced and 600Ω balanced. 0-100dB in 1 dB steps. Frequency range D.C. to 250MHz. NEW 2100 style Attenuators, 50Ω with 0.1dB steps to 10dB which may be combined with standard 1dB units on a common panel.



'L' and 'S' Band Attenuators:

Small, compact Attenuators with designed-in reliability. Fitted with SMA connectors 'L' band units, 50Ω, D.C. to 2GHz. 'S' band units 50Ω, D.C. to 4GHz. 1 watt power rating. 'L' Band Attenuators with 1 dB and 10dB steps can be supplied together in a case for laboratory use.

'O' Series:

High accuracy Attenuators with low insertion loss. 6 Models covering impedances of 50Ω and 75Ω with 0.1dB, 1.0dB and 10dB steps. NOW with frequency range extended to cover D.C. to 750MHz with increased accuracy Useful to 1GHz.

708 Series:

Low cost rotary Attenuators. Models with 50Ω and 75Ω impedance in 0.1, 1.0, and 10 dB steps and frequency range to 100MHz. Combinations of these units can be supplied in a robust case for laboratory use.

'RV' Series:

Ladder network Attenuators suitable for controlling output signal levels where high accuracy is not essential. Separate units provide 1.0 and 10dB steps and the two units can be supplied mechanically linked as a tandem pair. Frequency range to 150 MHz.

2050 Series:

High discrimination 600Ω balanced Attenuator with 0.1 dB increments to a total of 121dB. Frequency range DC to 1MHz. NEW 140Ω balanced Attenuator to similar design. 0.1 dB dB increments to 91dB.

2010 Series:

Rack mounting programmable Attenuators providing 0.1dB, 1.0dB and 10dB steps for use primarily in automatic/computer-controlled test systems. Programming modes: (1) 4-line compatible BCD, (2) 1 out of 10 line code (3) local front panel thumb wheel switches.

Send for full particulars of the complete range of Hatfield Attenuators

HATFIELD

forward thinking in electronics

HATFIELD INSTRUMENTS LIMITED,
Burrington Way, Plymouth PL5 3LZ, Devon.
Telephone: Plymouth (0752) 772773
Telex: 45592. Grams: Sigjen, Plymouth.

WW — 108 FOR FURTHER DETAILS

A.S.P. TRANSFORMERS

(Dept. WW4), SIMMONDS ROAD WINCHEAP, CANTERBURY, KENT Tel: (0227) 52436

CASED TRANSFORMERS

Housed in smart resin coated steel cases with 3 core power cable and outlet socket. fused primary winding, isolation types are fitted with 3-pin outlet sockets and are available with 110 volt or 240 volt output (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and isolation sections for prices. Plugs extra.

VA (WATTS)	Ref No	PRICE Cased	PRICE Plugs 2 Pin + 1 Earth	PRICE Open	Post
60	149	9.03	0.98	4.70	0.72
200	151	12.29	0.98	8.61	0.97
250	152	13.81	0.98	10.31	1.18

TRANSFORMERS

30 VOLTS		See catalogue for full range	
PRIMARY 200/240V		SECONDARY 12, 15, 20, 24, 30V	
AMPS	Ref No.	PRICE	Post
0.5	112	2.04	0.61

50 VOLTS		See catalogue for full range	
PRIMARY 200/240V		SECONDARY 19, 25, 33, 40, 50V	
AMPS	Ref No.	PRICE	Post
1	103	3.58	0.76
2	104	5.30	0.85

60 VOLTS		See catalogue for full range	
PRIMARY 200/240V		SECONDARY 24, 30, 40, 48, 60V	
AMPS	Ref No.	PRICE	Post
0.5	124	2.51	0.72
1	125	3.75	0.75
2	127	5.36	0.82

SAFETY ISOLATING

See catalogue for full range
Prim 120, 240V. Sec. 120/240V. Centre Tap with screen

VA (WATTS)	Ref No	PRICE Cased	PRICE Plugs 2 Pin + 1 Earth	PRICE Open	Post
60	149	9.03	0.98	4.70	0.72
200	151	12.29	0.98	8.61	0.97
250	152	13.81	0.98	10.31	1.18

AUTO TRANSFORMERS

See catalogue for full range

VA (Watts)	Ref No	PRICE Cased	PRICE Plugs 2 Pin + 3 pin	PRICE Open	Post
1500	93	23.26	0.95	19.22	0A

MINIATURE & EQUIPMENT

See catalogue for full range
Primary 240V with Screen

VOLTS		MILLIAMPS		REF No.	PRICE	Post
Sec. 1	Sec. 2	Sec. 1	Sec. 2		£	£
3-0.3	—	200	—	238	1.56	0.34
0.6	0.6	500	500	239	1.56	0.34
0.6	0.6	1000	1000	212	2.12	0.46
9-0.9	—	100	—	113	1.60	0.34
0.9	0.9	330	330	235	1.62	0.34

12 and 24 VOLTS PRIMARY 200-240 Volts

See catalogue for full range

12V	AMPS	24V	REF No.	PRICE	Post
0.3	0.15	242	111	1.66	0.34
0.5	0.25	111	111	1.60	0.46
1	0.5	213	71	1.90	0.61
2	1	18	71	2.47	0.61
4	2	18	71	3.07	0.62
6	3	70	70	4.50	0.72
8	4	108	108	5.11	0.85

BRIDGE RECTIFIERS

ONE AMP	Price	FOUR AMP	Price
50 P.I.V.	0.25	100 P.I.V.	0.55
100 P.I.V.	0.25	200 P.I.V.	0.59
200 P.I.V.	0.28	400 P.I.V.	0.65
600 P.I.V.	0.30	600 P.I.V.	0.75

TWO AMP	Price	SIX AMP	Price
50 P.I.V.	0.35	50 P.I.V.	0.65
100 P.I.V.	0.40	100 P.I.V.	0.70
200 P.I.V.	0.45	200 P.I.V.	0.80
400 P.I.V.	0.50	400 P.I.V.	0.90

Add 25% VAT on all prices

SPECIAL OFFER!

2 KVA ISOLATORS

Fully impregnated & screened
2 primary windings 110V each
2 secondary windings 115V each
(2 matching transformers)
£29.50 plus carr. & VAT.

NEW! 2" AND 4" PANEL METERS

See catalogue for full range

2" SIZE: 60mm Wide x 45mm High x 40mm Deep. 4" SIZE: 110mm Wide x 82mm High x 43mm Deep.

VU Meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00. Post 10p. Lamps 40p per set. Plus 8% VAT

RADFORD HD250

High Definition Stereo Amplifier

A new standard for sound reproduction in the home! We believe that no other amplifier in the world can match the overall specification of the HD250.

Rated power output: 50 watts av. continuous per channel into any impedance from 4 to 8 ohms, both channels driven.

Maximum power output: 90 watts av. per channel into 5 ohms.

Distortion, preamplifier: Virtually zero (cannot be identified or measured as it is below inherent circuit noise.)

Distortion, power amplifier: Typically 0.006% at 25 watts, less than 0.02% at rated output (Typically 0.01% at 1 Khz)

Hum and noise: Disc.—83dBV measured flat with noise band width 23 Khz (ref 5mV); —88dBV "A" weighted (ref. 5mV)

Line —85 dBV measured flat (ref 100v)
—88dBV "A" weighted (ref 100v)

Hear the HD250 at

SWIFT OF WILMSLOW

Dept. WW

5 Swan Street, Wilmslow, Cheshire (Tel. 26213)

Mail Order and Personal Export enquiries: Wilmslow Audio, Swan Works, Bank Square, Wilmslow (Tel. 29599)

Also in stock: All Radford speaker drive units and crossovers, ZD22 preamp, Low Distortion oscillator LE03 and Distortion Measuring set DMS3.


WW—015 FOR FURTHER DETAILS

ELECTRONIC BROKERS

Electronic Brokers Ltd. are one of the leading electronic instrumentation companies in the UK, providing a full range of services to Universities, Industry, Colleges and Governments both at home and overseas.

We have the largest stocks of secondhand test equipment in Europe as well

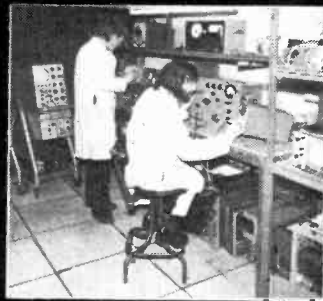as a selected range of new products. These are on display at our London showrooms where customers can examine the equipment of their choice and see it working.



Electronic Brokers Ltd. have fully equipped workshops on the premises to test and report on the majority of equipment we sell.



1uV-10mV in 10dB steps 1KHz A.F. Oscillator a l
Power ranges 10mV 100mW & 1W £70.00
Wide range RC Oscillator TF1370 Sine wave
10Hz-10MHz Square wave 10Hz-100KHz Direct
outputs up to 31.6V Attenuator with 75ohms
100ohms & 600ohms ixance £110.00
Phase A M Signal Generator TF2003
0.4-12MHz
V.H.F. Mobile Radio Test Set TF1064B 5M £300
Signal Generator TF144H 4 Late models in superb
condition. £500 to £650
AM FM Generator TF995B/5 (Brand new -
unused) £750

HEATHKIT
10-12 µ Scope Single Beam 50MV/cm DC-4.5MHz
5" Tube Assembled Refurbished Our price £49.50

ROBAND
25MHz Scope R 050 c/w 5C Plug in £200
25MHz Scope R 050A c/w 5C Plug in £225

TEKTRONIX
Sampling Scope 661 c/w plug ins £450
453 DC 50MHz Solid state & portable £650
Storage Scope 564B with MOD 121N Auto Erase c/w
3A74 (4 trace) & 383 plug ins (Immaculate
condition) £725

MUIRHEAD
LF Decade Oscillator D880A 2 phase
0.01Hz-1.2KHz £295.00
Decade Oscillator D890A 1Hz-11.2KHz £335.00

RADIOMETER
Stereo signal generator SMG1C Full spec on request
Superb condition £400
AM FM Generator Type MS27G £315

RHODE & SCHWARZ
Frequency Synthesiser Type XUC (BN444466) c/w
XSU Power Supply & Calibrator (Brand new
condition) P.O.A.

WAYNE KERR
Video Oscillator O 222 7KHz-8MHz in 6
ranges £75.00
Video Oscillator O 22D 10 KHz-10MHz £150.00

OSCILLOSCOPES

COSSOR
CDU110 DC - 20MHz c/w CAM 111 Plug in £245

HEWLETT PACKARD
Oscilloscope 140A c/w 1415A time domain
reflector-fer for testing of cables connectors
striplines & transmission lines £750
Sampling Scope 185B DC 3.5 GHz £395.00
Oscilloscope 175A DC-50MHz Main Frame £150.00
Plug ins available from £25-£55.00
50MHz single channel 1751A Time Mark Gen 1783
Aux Plug-In 1780A Display Scanner 1782A Sweep
Delay Gen 1781B Dual Trace Vert Amp 1750A
Delay Gen 1781A

MARCONI
T.V. Scope TF 2200A/1 c/w TV Off plug in TM
6457A DC 30MHz £190
Portable Scope TF2203 15MHz Bandwidth DC
coupled 50mV/cm sensitivity £125.00

SOLARTRON
Portable Scope DC-6MHz Double Beam £95
CD 10 14 3 DC 5MHz £90
Portable Scope CD 1400 DC-15MHz Plug ins available
CX 1441 1443 £180
Wide Band General Purpose Scope CD-1212 (Min
Type CT484) Plug ins CX1251 & CX1252 £149.50

VOLTMETERS

ADVANCE
7.8 Millivoltmeter 50Hz 4.5MHz 0.001V to 300V
FSD Input impedance 10Mohms £42
Voltmeter VM 80 AV Volts 0-500V (ranges 6) DC Volts
0-1.5KV 7 ranges Resistance 0-1000Mohms £45

DAVE
Valve Voltmeter Type 613B 0.03 300V
(RMS) £125.00

ELECTRONIC BROKERS TEST EQUIPMENT CATALOGUE

The most comprehensive catalogue of its kind ever compiled in the UK. Send 50p towards printing, postage, etc. (Overseas customers £1) and a catalogue will be sent by return. Electronic Brokers Ltd. will then keep the catalogue updated by forwarding revision sheets free of charge.

TELEPHONE TEST EQUIPMENT

SIEMENS
Level Meter 3D 332 0.3-1200KHz £250
Level Meter 3D 335 10KHz-17MHz £300
Level Oscillator 3W29 0.3-1200KHz £250
Level Oscillator 3W518 £300

Carrier Frequency Sweep measuring set up Type Ref
32 M710 (to 15MHz) Comprising Level Oscillator
Ref 3W 518 Level Meter Ref 3D 335 Sweep
Attachment Ref 3W 933 Tracing Receiver Ref 3D
346 Used for measurement on carrier telephone
equipment for coaxial systems (ie V960 V1200 &
V2700) and wideband radio relay systems (e.g.
FM600 FM900 FM1800) P.O.A.

Octave Filter 74143A 37.5-12 800Hz For
analysing noise & interference on comms systems
Particularly useful with Psophometer 74142 P.O.A.

Selective Level Measuring Set 74184B 60-1364
KHz £125.00 P.O.A.

Measuring Set 74831A P.O.A.
Milliwatt Test Sets 74166 £50-£65.00
Noise Generator 74126 20Hz-4KHz £120-£200.00

Selective Level Measuring Sets 74832B
50KHz-800MHz 0.3-3V 0-500mV & dB scale
60mV-120mV FSD (adjustable) on dB scale Will
function also as Beat Frequency Indicator & as a Freq.
Deviation Meter Transistorised & Portable operates
from an internal battery Impedance 75ohms £140.00

White Noise Generator 74262B Measures basic noise
& intermodulation on multicircuit telephone systems
(up to 960 ccts.) in terms of Noise Power Ratio P.O.A.

WANDEL & GOLTERMAN
Level Transmitter TFPS 42 10KHz-14MHz £375
Level Meter TFFM 43 10KHz-14MHz £375
Wandel & Golterman VZM 2 Distortion measuring set
for phase and amplitude mod. For multichannel FM
Radio Systems up to 12MHz base bands £350

SIGNAL SOURCES

ADVANCE
V.H.F. Square Wave Generator SG21
10 KHz-100MHz Max p 2V £35.00

AIRMEC
H.F. Signal Generator 201 30KHz-30MHz (7 bands)
Int. Xtal Calibrator o/p level variable 1uV-1V 75ohms
impedance Int Mod at 1KHz Ext Mod 30Hz-
10KHz £215.00 £60-115.00

GENERAL RADIO
Unit Oscillator 1209C Freq 250-920MHz Accuracy
1% Drift 0.2% O/p in to 50ohms=150mW supplied
with Power Supply Type 1201-CO1B as
illustrated £450

Unit Oscillator 1218A 900-2000MHz Power output
of 200mW across band £140.00
Unit oscillator 1363 Spec on request £495.00

HEWLETT PACKARD
V.H.F. Signal Generator 202H F.M. A.M. C.W. &
pulse coverage 54 to 216 MHz R.F. o/p 0.1µV-0.2V
50ohms Impedance £450

Univerter 207H for use with above £100

U.H.F. Signal Generator 612A 450-1200MHz £495

V.H.F. Signal Generator 608E 10-480MHz (5 band)
Accuracy ±0.5% o/p 0.1µV-1V (variable) 50ohms
Int A.M. 400 & 1000Hz Ext A.M. 20Hz-20KHz
Superb condition £895

Signal Generator 614A 900-2100MHz o/p
0.1µV-0.2V (50ohms) £395.00

S.H.F. Signal Generator 618C 2.8-7.6GHz ±1%
50ohms £550.00

U.H.F. Signal Generator 616A 1.8-4.2GHz £475.00

MARCONI INSTRS.
F.M. A.M. Signal Generator TF 995A 3S Ministry
Type No CT402 1.5MHz-220MHz R.F. o/p
2µV-200mV Internal & External Mod Facilities V.
good condition £385

F.M. A.M. Signal Generator TF 995A S 1.5-220MHz
in 5 bands 0.1µV-200mV F.M. up to ±120KHz from
50Hz-15KHz A.M. up to 50% from 100Hz-10KHz
o/p (1) 2µV-200mV (2) with terminating unit
1µV-100mV Int mod freqs 400Hz 1KHz & 1.5KHz
Distortion (1) on internal F.M. -25Hz (2) on internal
A.M. 6% at 30% mod £450.00

A.M. Signal Generator TF801D 1 Freq range
10-470MHz R.F. output 0.1µV-1V Piston attenuator
50ohms Impedance Modulation Int A.M. 1KHz Ext
A.M. 30 Hz-20KHz Low spurious F.M. & drift
V.S.W.R. 1.2 or less £400-£800

A.M. Signal Generator TF801D 1S Military Version
10-485MHz £450-£800

RC Oscillator TF1370A 10Hz-10MHz Square Wave
up to 100KHz High Outputs up to 31.6V £285

Phase A.M. Signal Generator TF 2003
0.4-12MHz £150

A.M. Signal Generator TF 801B/3S 12 485MHz
0.1µV-1V £195.00

RC Oscillator TF1101 Frequency range
20Hz-200KHz Output Direct into 600Ω 20V
variable Attenuator 0.6dB in 10dB steps Impedance
600Ω Distortion Via 1KHz Filter less than 0.1%
Direct or via Attenuator Less than 0.5% 50Hz-20KHz
Less than 1% 20Hz-200KHz Superb condition £175

U.H.F. & S.H.F. Signal Generator TF105B
1600-4000MHz 0.1µV-445mV 50ohms Impedance
£295.00

Heterodyne Generator TF1221
2MHz-100MHz £45.00

F.M. A.M. signal Generator TF937 1 CT320
35KHz-18 3MHz As seen condition £80.00

Portable Receiver Tester TF888 3 Freq
70KHz-70MHz Xtal check 500KHz & 5MHz Output

PULSE GENERATORS

ADVANCE
Double Pulse Generator PG 56 Pulse Amplitude
0.1V-10V Sq wave 0-10V Rise Time 10nsec
(typical) £87.50 P.O.A.

Pulse Generator PG 55 P.O.A.
Modular Pulse Generator Advance Type PG 52
System of 5 Signal Generating & Processing Units
Repetition freq. up to 20MHz & Output Pulses to 20V
(50ohms) Rise & Fall times 5nsec. Its versatility enables
the production of complex pulse & ramp waveforms not
obtainable from pulse generators £250

SWEEP GENERATORS


HEWLETT PACKARD
Sweep Oscillator 692D 2.4GHz Sweeps from start
to stop freq. SPECIAL OFFER £300

Sweep Oscillator 692B 4.8GHz SPECIAL OFFER £325

Sweep Oscillator 693D 4.8GHz £325

JERROLD
Sweep Signal Generator 900B Central Freqs
500KHz-1200MHz Sweeps widths narrow as 10KHz to
400MHz wide 50ohms o/p impedance £400

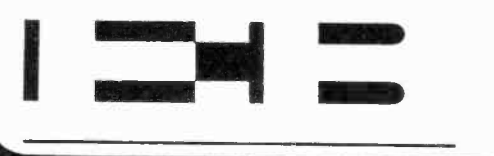M.E.S.L.
Sweep Signal Source MH883 7-12.5GHz £480.00



ELECTRONIC

A member of the EB group

ADD 8% VAT TO ALL PRICES

WW-105 FOR FURTHER DETAILS

the test equipment people




On these pages you will find just the briefest selection from the vast range which we hold in stock at any one time.

If you are seeking a specific item and it is not listed, it will pay you to ring us first — we believe we offer the best prices and the best service.

WORLD WIDE EXPORT.
Enquiries and tenders welcome from any part of the world.

HOW TO REACH US
We are easy to reach, no matter where you live. Minutes away from Kings Cross or St. Pancras main-line stations, and a bus ride from Euston; only just over half an hour from Heathrow Airport. Parking is easy too.

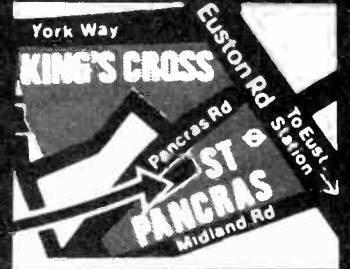49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781



VOLTMETERS

HEWLETT PACKARD
DC Vacuum Tube Voltmeter 412A 1mV-1000V 1% Accuracy. Can also be used as Ohmmeter & Ammeter. £75
VTVM 400D 1mV to 300V FSD. 12 ranges 10Hz to 4MHz. 2% accuracy. Input Impedance 10Mohms. £85
VTVM 400L Logarithmic version of 400D Reads RMS value of sine wave. Log. voltage scale 0.3 to 1 & 0.8 to 3 Linear dB scale. Input Impedance 10Mohms. £90
Vacuum Tube Voltmeter 410B Freq. Range 20Hz-700MHz AC 1-600V (6 ranges) DC 1V-1KV ohmmeter 0.2 ohms to 500Mohms (7 ranges). Accuracy ± 3%. £65.00
D.C. Microvoltmeter 425A. Voltage range +ve & -ve from 10µV and scale to 1V end scale 11 steps 1, 3, 10 sequences. Current +ve & -ve from 10µA to 3mA Amplifier Gain 1000/000. £95.00
Vacuum Tube Voltmeter 400H Freq. Range 10Hz-4MHz Volts 1.0mV-300V F.S. (12 ranges). Accuracy ± 1% (50Hz-500KHz) ± 2% (20Hz-1MHz). P.O.A.
AV Voltmeter 400E Solid state AC volts 1mV-300V F.S. (12 ranges) Freq. 10Hz-10MHz Accuracy 1%. P.O.A.
MARCONI
Sensitive Valve Voltmeter TF 1100 100µV-300V AC Freq. coverage 10Hz-10MHz. Meter has dB scale facility. £85
Valve Voltmeter TF 1041B General Spec. 0-300V AC (1KV DC Resistance up to 500Mohms) £60.95
Voltmeter No. 3 CT 20B TF 95B AC 100mV-150V multiplier extends AC range to 1.5KV DC 50mV-100V Freq. Range 20Hz-100MHz. £55.00 TF 2600 unused condition. £175
PHILIPS
L.F. Millivoltmeter GM 6012 12 ranges 1mV-300V dB scale on meter. Accuracy 2Hz-5Hz 5% 100KHz 2.5% 100KHz-1MHz 0.5% Amplifier option available 50/70. £65.00
H.F. Millivoltmeter GM 6014 Measuring Ranges 1mV-300mV in 6 ranges Accuracy at 30KHz ± 3% of FSD = Amplitude Char. 1KHz-30KHz flat within ± 5%. £55.00
DC Microvoltmeter GM6020 10-V-1KV Current 10µA-10A Accuracy 5% (FSD) 0-100µV 3% (FSD) AU other ranges. Recorder option facility. £65.00
SIGN ELECTRONICS
A.F. Voltmeter AM324 £60
SOLARTRON
D.C. Digital Voltmeter LM1420 2 2.5V-1KV in 6 ranges 0 Ohms DC accuracy. £235.00
D.V.M. Type LM1420 2Ba DC true R.M.S. & mean A.C. sensing. Accurate measurement irrespective of harmonic distortion accuracy ± 0.25% Freq. 40Hz-20KHz P.O.A.

A.C. Converter LM1219 30mV-300V mean reading Freq. range 10Hz-10KHz P.O.A.
D.V.M. LM 1480 3 Autorange version of LM 1440 3. Max reading 39999 5V-2KV DC Full spec on request P.O.A.

FLUKE
Differential type Voltmeter 821A For calibration testing stability measurements of regulated power supplies DC Voltmeter calibration ± 0.01% absolute accuracy infinite input resistance at null over entire 0-500V range standard cell reference. Polarity switch in-line readout with automatic lighted decimal. No zero controls. Usable as conventional V.T.M. (3% FSD). £165

MISCELLANEOUS


ADVANCE
Recorder Calibrator HC20 £15.00
AVO
Valve Tester CT160 For testing of receiving & low power valves. Mutual conductance. Emission Electrode. Insulation & anode current can be measured. Ministry approved. £60.00
AIRMEC/RACAL
Wave Analyser 24BA 5-300MHz £195-£300
Wave Analyser 8a3 30KHz-30MHz Sensitivity 1µV to 1V up to 20 MHz 4µV to 4V up to 30MHz £95.00
Wave Analyser 24B Freq. Range 5MHz-300MHz £90.00
AIRMEC
Modulation Meter 210 £75 to £100
AMPEX
F.M. Direct Recorder Reproducer SP 300 4 Channels Speed 1 1/2, 3 1/2, 7 1/2, 15 ips Freq. response Instrumentation 50Hz-40Hz at 15 ips. Audio 50Hz-18KHz at 15 ips. Special offer £850
BECKMAN
Transfer Oscillator 7580B DC-15GHz with counter 7.5MHz-15GHz without counter. Sensitivity 100mV (R.M.S.) £350
BELL
Gaussmeter Type 120 complete with Probes P.O.A.
B & K
Oscillation Bridge 1505 P.O.A.
BURNOPT
Battery Charger BE370 £30.00
B.P.L.
Electrolytic Capacitance Bridge CB 154-D Q.F. 22 000 F Freq. 50Hz £35.00
COSSOR
Battery Charger CC 99 £15.00
DECCA
Power Supply for Noise Source MW 61 P.O.A.
GENERAL RADIO
Impedance Bridge 1607A Immaculate Condition in Wooden Transit Case. £1000
Unit Null Detector 1212A 20Hz-5MHz Log Response with 120dB scale. P.O.A.

- | | |
|--|--------|
| HEWLETT PACKARD | £210 |
| Distortion Analyser 331A | £110 |
| Digital Recorder 580A | £140 |
| Digital Recorder 561B | |
| MARCONI INSTS. | |
| Attenuator TF 1073A 2S | £85 |
| Distortion Factor Meter TF 2331 Brand New Condition | £300 |
| Brink & Sync Mixer TF 290B | £90 |
| Quantization Distortion Tester TF 2343 | P.O.A. |
| R.F. Power Meter TF 1152 1 | £75 |
| Q Meter TF 329G | £200 |
| RADIOMETER | |
| Stereo signal Generator SMG 1 | P.O.A. |
| RHODE & SCHWARTZ | |
| Stereo Caster MSCGN 4192 2 | P.O.A. |
| Poly or Switch II | £1450 |
| Attenuator type DPR 2-60 ohms BN 18042 | P.O.A. |
| TELEON | |
| Sweep Generator SM 7000 c/w Plug Ins E 3M S R & S 3M | P.O.A. |

STROBOSCOPES & TACHOMETERS

STROBOSCOPIC TACHOMETER

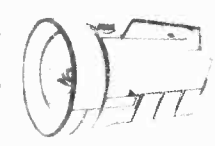Two units in one
STROBOSCOPIC FLASH RATE 200 to 6 000
flashes per minute
TACHOMETER
SPEED RATE As above ACCURACY 3% better
FLASH DURATION ~ Approx 10 to 25 µsec HIGH IMPACT CASE WEIGHT 27 oz 22 Volts
£49.50



"TOUCHLESS" RETRO-REFLECTIVE TACHOMETER

Reads RPM from as far as 12 in. away! Four ranges 0-1 000 3 000 10 000 30 000 RPM Battery powered. Mirror Scale Accuracy 1% of full scale. Push-button reading.
£89.50
Carrying Case £12.50 extra. Send for full literature.



MULTIMETERS

MICROTEST 80 — I.C.E.
20,000 OHMS/VOLT 40 RANGES
20 000 ohms Volt 4 000 ohms Volt (AC) 2% accuracy V DC 100mV to 1KV (6 Ranges) V AC 1.5V to 1KV (5 Ranges) DC 50-A to 5A (6 Ranges) 1 AC 250µA to 2.5A (6 Ranges) Ohms low ohms ohms x 1 ohms x 10 ohms x 100 Power Output Measurements 1.5V to 1000V (5 Ranges) ± 6dB to 62dB (5 Ranges) Capacitance 25-pF to 25 000 µF (4 Ranges) 1,000 times overload protection (on ohm ranges) Meter movement diode protection size (Without case) 90 X 70 X 18 mm. Electronic zero non-parallel mirror scale. Unbreakable carrying case and probes supplied. Full After Sales Service available.



Price £11.95
Post & Packing 50p VAT at 8% £1.00 SEND TOTAL £13.45


SUPERTESTER 680R — I.C.E.

20 000 OHMS/VOLTS 80 RANGES
20 000 ohms Volt 1% DC 2% AC V DC 100mV to 2KV (13 Ranges) V AC 2 to 2KV (11 Ranges) 1 DC 50-A to 10A (12 Ranges) 1 AC 250µA to 5A (10 Ranges) R x 1 x 100 x 1 000 x 10 000 and Low ohms Detector. Resistance 0.10 M ohms Freq. Measurement 0.5 0.01 Hz (2 Ranges) Power Output 10-2 000V (9 Ranges) Decibels -24 to +70 dB (10 Ranges) Capacitance 0.5 000 000 pF (2 Ranges using mains supply) 0.2 000 µF (4 Ranges using internal 3 Volt battery) 1 000 times overload protection on ohms ranges and meter movement diode protection 10 Fields of Measurement and 80 ranges. Size 128 X 95 X 32 mm. Non parallel mirror scale. Unbreakable carrying case supplied which contains probes, mains lead crocodile clips and shorting link.

Price £18.50
Post & Packing 75p VAT at 8% £1.54 SEND TOTAL £20.79

ACCESSORIES FOR 680R AND MICROTTEST 80 (EXTRA)

(I denotes item not usable on Microtest 80)
AMBERCLAMP A.C. 2.5A to 500A (6 Ranges) 3% £11.95 H.V. PROBE MOD. 1B 25KV (MAX) I.P. Z=500 M ohms (Nom) £5.95 LIGHT METER PROBE MOD. 24 2 20 000 Lux £11.95 RESISTANCE MULTIPLIER MOD. 25 Multiplying Factor x 100 000 R. Range (with 680R) 0-100M £5.95 GAUSSMETER PROBE MOD. 27 0-15 Kilogauss £11.95 PHASE SEQUENCE INDICATOR MOD. 28 100/400V (A.C.) 50-60 Hz. £5.95 D.C. CURRENT SHUNTS MOD. 32 SERIES 10A 25A 50A and 100A £4.50 each TEMPERATURE PROBE MOD. 36 -50°C to +200°C £11.95 SIGNAL INJECTOR MOD. 33 Basic D.P. Freq. 500KHz and 1 KHz. £5.95 CURRENT TRANSFORMER MOD. 61B 250mA to 100A £7.00

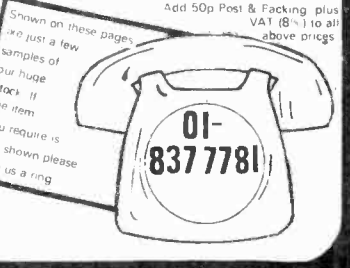

BROKERS LTD


Carriage and packing charge extra on all items unless otherwise stated.

Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated.

Hong Kong Jersey Australia St. Lucia India Barbados Antigua Jordan Spain Israel Mauritius St. Vincent Uganda Ascension Island Malta Sierra Leone Somalia New Guinea Italy Kuwait Netherlands Canada Trinidad Malaya Austria

AUDIO KIT SUPPLIERS TO THE WORLD

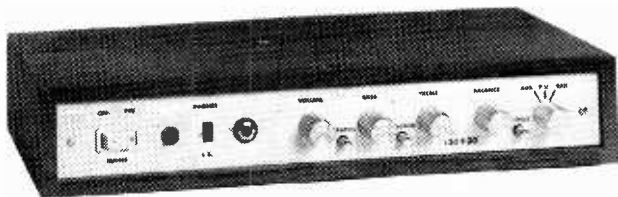T20+20 and our new T30+30 20W, 30W AMPLIFIERS



Designed by Texas engineers and described in Practical Wireless the Texan was an immediate success. Now developed further in our laboratories to include a Toroidal transformer and additional improvements, the slimline T20 + 20 delivers 20W per channel of true Hi-Fi at exceptionally low cost. The design is based on a single F/Glass PCB and features all the normal facilities found on quality amplifiers, including scratch and rumble filters, adaptable input selector and head phones socket. In a follow up article in Practical Wireless further modifications were suggested and these have been incorporated into the T30 + 30. These include RF interference filters and a tape monitor facility. Power output of this new model is 30W per channel.

Pack	T20	T30
1. Set of low noise resistors	0.95	1.05
2. Set of small capacitors	1.50	2.10
3. Set of power supply capacitors	1.40	2.05
4. Set of miscellaneous parts	1.90	1.90
5. Set of slide, mains, P.B. switches	1.20	1.20
6. Set of pots, selector switch	2.00	2.00
7. Set of semiconductors, ICs, skts.	7.25	7.75

Pack	T20	T30
8. Toroidal transformer - 240V prim. a.s. screen	4.95	6.80
9. Fibreglass PCB	2.50	2.90
10. Set of metalwork, fixing parts	4.20	4.80
11. Set of cables, mains lead	0.40	0.40
12. Handbook (free with complete kit)	0.25	0.25
13. Teak cabinet 15.4" x 6.7" x 2.8"	4.50	4.50

FREE TEAK CASE WITH FULL KITS


T20+20
KIT PRICE only **£28.25**

T30+30
KIT PRICE only **£32.95**

2 NEW TUNERS!

WW SFMT II


Following the success of our Wireless World FM Tuner kit we are now pleased to introduce our new cost reduced model, designed to complement the T20 and T30 amplifiers. The frequency meter of the more advanced model has been omitted and the mechanics simplified, however the circuitry is identical and this new kit offers most exceptional value for money. Facilities included are switchable afc, adjustable, switchable muting, channel selection by slider or readily adjustable pre-set push-button controls and LED tuning indication. Individual pack prices in our free list.

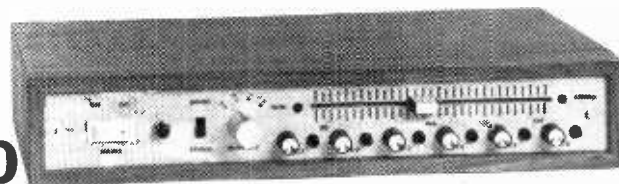

KIT PRICE
£47.40

POWERTRAN SFMT

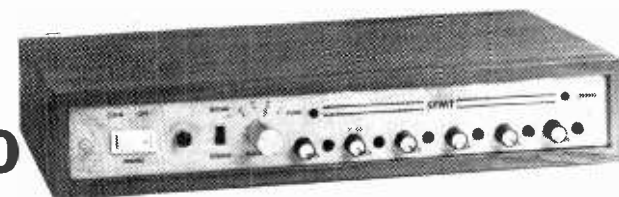This easy to construct tuner using our own circuit design includes a pre-aligned front end module, PLL stereo decoder, adjustable, switchable muting, switchable afc and push-button channel selection. As with all our full kits, all components down to the last nut and bolt are supplied together with full constructional details.




KIT PRICE
£32.60

CONVERT NOW TO QUADRAPHONICS

With 100s of titles now available no longer is there any problem over suitable software. No problems with hardware either. Our new unit the SQM1-30 simply plugs into the tape monitor socket of your existing amplifier and drives two additional speakers at 30W per channel. A full complement of controls including volume, bass, treble and balance are provided as are comprehensive switching facilities enabling the unit to be used for either front or rear channels, by-passing the decoder for stereo-only use and exchanging left and right channels. The SQ matrix decoder is based upon a single integrated circuit and was designed by CBS whilst the power and tone control sections are identical to those used in our T30 + 30 amplifier which the SQM1-30 matches perfectly. Kit price includes CBS licence fee.

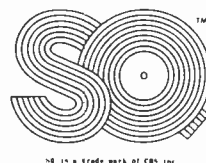Special offer to T20 + 20 and Texan owners! Owners of T20 + 20 and Texan amplifiers, which have no tape monitor outlet, purchasing an SQM1-30 will be supplied, on request, a free conversion kit to fit a tape monitoring facility to the existing amplifier. This makes simple the connection to the highly adaptable SQM1-30 quadrasonic decoder/rear channel amplifier.




KIT PRICE **£37.15**

SEMICONDUCTORS

as used in our range of quality audio equipment.

2N699	£0.20	BC212K	£0.12	MPSA65	£0.35
2N1613	£0.20	BC182L	£0.10	MPSA66	£0.40
2N1711	£0.25	BC184L	£0.11	MPSU05	£0.60
2N2926G	£0.10	BC212L	£0.12	MPSU55	£0.70
2N3055	£0.45	BC214L	£0.14	SBA750A	£2.50
2N3442	£1.20	BCY72	£0.13	SL301	£1.30
2N3711	£0.09	BD529	£0.85	SL3045	£1.60
2N3904	£0.17	BD530	£0.85	SN72741P	£0.40
2N3906	£0.20	BDY56	£1.60	SN72748P	£0.40
2N4062	£0.11	BF257	£0.40	TIL209	£0.30
2N4302	£0.60	BF259	£0.47	TIP29A	£0.50
2N5087	£0.42	BFR39	£0.25	TIP30A	£0.60
2N5210	£0.54	BFR79	£0.25	TIP29C	£0.71
2N5457	£0.45	BFV51	£0.20	TIP30C	£0.78
2N5459	£0.45	BFV52	£0.20	TIP41A	£0.74
2N5461	£0.50	CA3046	£0.70	TIP42A	£0.90
2N5830	£0.35	LC1186	£5.50	TIP41B	£0.82
40361	£0.40	MCI310	£2.90	TIP42B	£0.98
40362	£0.45	MC1351	£1.05	1N914	£0.07
BC107	£0.10	MFC4010	£0.95	1N916	£0.07
BC108	£0.10	NJ491	£1.20	1S820	£0.10
BC109	£0.10	NJ491	£1.30	5B05	£1.20
BC109C	£0.12	MJE521	£0.60		
BC125	£0.15	MPSA05	£0.25		
BC126	£0.15	MPSA12	£0.55	FILTERS	£0.80
BC182	£0.10	MPSA14	£0.35	FM4	£2.80
BC212	£0.12	MPSA55	£0.25	SFG10 7MA	£2.80
BC182K	£0.10				

SQ QUADRAPHONIC DECODERS

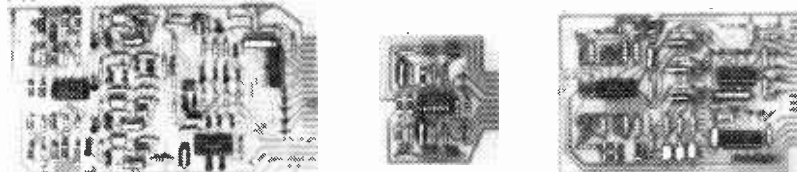

Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers or amplifier tape monitor outlets) into any one of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front-Back, LF-RF balance, LB-RB balance and Dimension controls can all be implemented by simple single gang potentiometers. These state-of-the-art circuits used under licence from CBS are offered in kits of superior quality with close tolerance capacitors, metal oxide resistors and fibre-glass PCBs designed for edge connector insertion. All kit prices include CBS licence fee.

M1 Basic matrix decoder with fixed 10-40 blend. All components, PCB **£5.90**
L1 Full logic controlled decoder with wave matching and front back logic for enhanced channel separation. All components PCB **£17.20**
L2A More advanced full logic decoder with variable blend, extended frequency response, increased front back separation. All components, PCB **£24.60**

EXPORT NO PROBLEM

Our Export Department will be pleased to advise on postal costs to any country in the world. Some of the countries to which we sent kits in 1975 are shown surrounding this advertisement.

Kenya France St. Martin, Java New Zealand Borneo South Africa Denmark Nigeria Anguilla Finland

NEW PRODUCTS

PROTO BOARDS

Build & test circuits as fast as you think!

PB100	10 IC Cap breadboard kit	4 5 x 6 x 1 3/4"	£17.45
PB101	10 14-DIP cap 5-way post	940 solderless tie points 5 8 x 4 5/8"	£26.15
PB102	12 14-DIP cap like PB101 with 1 240 tie points	7 0 x 4 5/8"	£34.90
PB103	24 14-DIP cap 4 5-way posts	2 250 tie points 6 0 x 9 0"	£52.35
PB104	32 14-DIP cap 3 060 solderless tie points	8 0 x 9 7/8"	£69.80



LOGIC MONITOR


Simultaneously displays static and dynamic logic states of DTL, TTL, HTL or CMOS DIP ICs. Pocket size LM-1. **£59.95.**

PROTO-CLIP

For power on hands off signal tracing. Bring IC leads up from PC board surface for fast trouble shooting. PC14 14-pin **£3.25**, PC16 16-pin **£3.40**

SOCKETS & BUS STRIPS

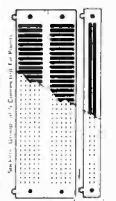Plug-in wire, test, modify or expand without patch cords or solder. Snap together to form breadboard mounted.



PN/Description	Hole to Hole	Term ls	Price
Q15/S	1 3/4"	118	£10.90
Q15/SB Bus	6 5/8"	20	£2.20
Q14/S	Socket	5 3/8" 5 0"	£8.75
Q15/S	Socket	5 3/8" 5 0"	£2.00
Q15/SB Bus	4 1/8" 3 8"	12	£7.45
Q15/S	Socket	4 1/8" 3 8"	£1.75
Q15/S	Socket	2 4/8" 2 1/8"	£4.15
Q11/S	Socket	1 8/8" 1 5/8"	£3.30
Q18/S	Socket	1 4/8" 1 1/8"	£2.85
Q17/S	Socket	1 3/8" 1 0/8"	£2.65

7400 Series TTL

25		100+		SN7494		0.48	0.45	0.46
SN7400	0.14	0.13	0.12	SN7495	0.60	0.56	0.50	
SN7401	0.14	0.13	0.12	SN7496	0.70	0.67	0.60	
SN7402	0.14	0.13	0.12	SN7497	2.90	2.50	2.35	
SN7403	0.14	0.13	0.12	SN74100	1.35	1.30	1.25	
SN7404	0.15	0.14	0.13	SN74104	0.31	0.29	0.26	
SN7405	0.15	0.14	0.13	SN74105	0.31	0.29	0.26	
SN7406	0.30	0.29	0.28	SN74107	0.31	0.29	0.26	
SN7407	0.30	0.29	0.28	SN74109	0.31	0.29	0.26	
SN7408	0.15	0.13	0.12	SN74110	0.55	0.50	0.45	
SN7409	0.15	0.13	0.12	SN74111	0.81	0.80	0.76	
SN7410	0.14	0.13	0.12	SN74114	1.00	0.97	0.95	
SN7411	0.23	0.22	0.21	SN74115	1.00	0.97	0.95	
SN7412	0.19	0.18	0.17	SN74118	1.00	0.95	0.90	
SN7413	0.30	0.29	0.28	SN74121	1.31	0.29	0.25	
SN7414	0.71	0.70	0.69	SN74122	0.44	0.41	0.37	
SN7415	0.30	0.29	0.27	SN74123	0.62	0.58	0.50	
SN7416	0.28	0.27	0.26	SN74125	0.70	0.65	0.60	
SN7417	0.28	0.27	0.26	SN74126	0.75	0.70	0.65	
SN7420	0.14	0.13	0.12	SN74128	1.40	1.35	1.30	
SN7421	0.95	0.94	0.93	SN74132	2.10	2.05	2.00	
SN7422	0.25	0.24	0.23	SN74136	0.95	0.90	0.85	
SN7423	0.26	0.25	0.22	SN74140	2.50	2.45	2.40	
SN7425	0.26	0.25	0.22	SN74141	0.75	0.70	0.62	
SN7426	0.26	0.25	0.22	SN74145	1.15	1.10	1.05	
SN7427	0.27	0.26	0.22	SN74147	2.95	2.90	2.85	
SN7428	0.39	0.38	0.37	SN74151	0.68	0.62	0.55	
SN7430	0.14	0.13	0.12	SN74150	1.35	1.30	1.25	
SN7432	0.25	0.24	0.22	SN74151	0.68	0.62	0.55	
SN7433	0.36	0.35	0.34	SN74152	1.55	1.50	1.45	
SN7437	0.27	0.26	0.22	SN74153	0.68	0.62	0.55	
SN7438	0.27	0.26	0.22	SN74154	1.55	1.50	1.45	
SN7439	1.10	1.08	1.06	SN74155	0.68	0.62	0.55	
SN7440	0.14	0.13	0.12	SN74156	0.68	0.62	0.55	
SN7441	0.70	0.69	0.66	SN74157	0.90	0.85	0.80	
SN7442	0.63	0.60	0.53	SN74158	1.50	1.45	1.40	
SN7443	1.00	0.99	0.90	SN74160	0.95	0.90	0.80	
SN7444	1.08	1.07	1.05	SN74161	0.95	0.90	0.80	
SN7445	0.85	0.83	0.70	SN74162	0.95	0.90	0.80	
SN7446	1.03	1.00	0.85	SN74163	0.95	0.90	0.80	
SN7447	1.03	1.00	0.85	SN74164	1.60	1.55	1.50	
SN7448	0.85	0.83	0.70	SN74165	1.60	1.55	1.50	
SN7450	0.14	0.13	0.12	SN74166	1.40	1.30	1.15	
SN7451	0.14	0.13	0.12	SN74170	2.40	2.30	2.20	
SN7453	0.14	0.13	0.12	SN74173	1.65	1.60	1.55	
SN7454	0.14	0.13	0.12	SN74174	1.15	1.10	1.00	
SN7455	0.40	0.39	0.38	SN74175	0.97	0.90	0.80	
SN7460	0.14	0.13	0.12	SN74176	1.10	1.05	1.00	
SN7462	0.45	0.44	0.42	SN74177	1.10	1.05	1.00	
SN7464	0.45	0.44	0.42	SN74180	1.10	1.05	1.00	
SN7465	0.45	0.44	0.42	SN74181	3.50	3.45	3.35	
SN7470	0.30	0.27	0.25	SN74182	1.10	1.05	1.00	
SN7471	0.60	0.59	0.58	SN74184	1.60	1.55	1.50	
SN7472	0.25	0.24	0.21	SN74185	2.30	2.25	2.20	
SN7473	0.30	0.27	0.26	SN74188	4.90	4.85	4.80	
SN7474	0.31	0.29	0.26	SN74191	1.75	1.70	1.65	
SN7475	0.40	0.39	0.38	SN74191	1.70	1.65	1.60	
SN7476	0.31	0.29	0.26	SN74192	1.25	1.05	1.00	
SN7478	0.65	0.63	0.61	SN74193	1.25	1.05	1.00	
SN7480	0.43	0.41	0.36	SN74194	1.10	1.05	1.00	
SN7481	1.00	0.95	0.90	SN74195	0.90	0.85	0.80	
SN7482	0.75	0.70	0.62	SN74196	1.05	1.00	0.95	
SN7483	0.81	0.80	0.68	SN74197	1.05	1.00	0.95	
SN7484	0.90	0.86	0.85	SN74198	2.05	2.00	1.70	
SN7485	1.25	1.15	1.00	SN74199	2.05	2.00	1.70	
SN7486	0.31	0.28	0.25	SN74200	6.00	5.95	5.80	
SN7489	3.50	3.20	3.00	SN74221	1.80	1.75	1.70	
SN7490	0.45	0.42	0.35	SN74251	1.80	1.75	1.70	
SN7491	1.00	0.95	0.90	SN74278	3.00	2.90	2.80	
SN7492	0.45	0.42	0.35	SN74279	1.20	1.15	1.10	
SN7493	0.45	0.42	0.35	SN74293	1.00	0.95	0.90	
				SN74298	2.60	2.55	2.40	

'LS' and 'S' Series TTL also available

All goods new, to full manufacturer's spec. No standard parts sold. Visitors welcome, by appointment. Colleges, Govt. and Account orders welcomed.

HIGH-SPEED TTL

1		25		100+			
SN74H00	0.34	0.33	0.30	SN74H51	0.36	0.35	0.33
SN74H01	0.34	0.33	0.30	SN74H52	0.36	0.35	0.33
SN74H02	0.34	0.33	0.30	SN74H53	0.36	0.35	0.33
SN74H05	0.37	0.36	0.33	SN74H54	0.36	0.35	0.33
SN74H08	0.40	0.39	0.37	SN74H55	0.36	0.35	0.33
SN74H10	0.36	0.35	0.33	SN74H60	0.36	0.35	0.33
SN74H11	0.36	0.35	0.33	SN74H61	0.36	0.35	0.33
SN74H20	0.36	0.35	0.33	SN74H71	0.80	0.78	0.75
SN74H21	0.34	0.33	0.30	SN74H72	0.74	0.73	0.70
SN74H22	0.36	0.35	0.33	SN74H73	0.90	0.88	0.85
SN74H30	0.36	0.35	0.33	SN74H74	0.87	0.85	0.81
SN74H40	0.36	0.35	0.33	SN74H76	0.90	0.88	0.85
SN74H50	0.36	0.35	0.33	SN74H77	0.80	0.78	0.75
				SN74H101	0.80	0.78	0.75
				SN74H103	1.10	1.09	1.05
				SN74H106	0.95	0.93	0.90

LOW-POWER TTL

1		25		100+			
SN74L00	0.34	0.33	0.30	SN74L73	0.74	0.71	0.68
SN74L02	0.34	0.33	0.30	SN74L74	0.89	0.87	0.80
SN74L03	0.39	0.37	0.34	SN74L90	1.62	1.58	1.50
SN74L04	0.39	0.37	0.34	SN74L91	1.74	1.71	1.65
SN74L10	0.39	0.37	0.34	SN74L95	1.62	1.58	1.50
SN74L20	0.34	0.33	0.30				
SN74L52	1.62	1.58	1.50				
SN74L51	0.34	0.33	0.30				

WIRELESS WORLD

TELETEXT DECODER

1024-bit Static N-Channel Ram Type 2602 B (1000 ns) 16-pin Moulded Dip **£2.75 each**

WAVEFORM GENERATOR KITS



Here's a highly versatile instrument at a fraction of the cost of conventional units. It includes two XR2025 IC's, data & applications, PC boardetcher & drill & ready for assembly) and detailed instructions.

XR 205K **£12.30**

The Function Generator Kit features sine, triangle and square wave, THD 0.5% typ., AM/FM capability.

XR-2206KA FUNCTION GENERATOR KIT

Includes monolithic function generator IC, PC board, and assembly instruction manual. **£11.50**

XR-2206KB FUNCTION GENERATOR KIT

Same as XR-2206KA above and includes components for PC board. **£16.00**

PICO-PAC

THE SMALLEST AC/DC POWER SUPPLY EVER!		Volts	mA
		5	140
		8	115
		10	100
		12	90
		15	70
		18	50
		20	35
		22	25
		24	15

£15.00 each

PREMIUM QUALITY COMPONENTS


We've been buying and selling top quality components for nearly ten years. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies. Now you can take advantage of our component buying skills and power and select from a broad range of advanced circuits.



NEW

Solar Powered Watch

with 100-YEAR CALENDAR

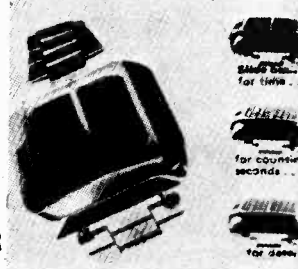

Solar cells draw power from the sun (10 to 15 minutes per day) or from ambient light (slightly longer) to keep batteries fully charged. Batteries operate up to 10 years. IS1 circuitry is programmed to provide a calendar to the year 2100, automatically adjusting for 30 and 31 day months, even leap years. Automatic brightness control adjusts LED for perfect viewing even in outdoors. Shows minutes and hours, counts out seconds or shows the date. Easily adjusts to reset hour or date without affecting calendar. Shock and water resistant. Accurate to 5 seconds per month. **Price: £298.50 each.**

HIGH-BRIGHTNESS L.E.D.s

200" dia.		125" dia.		
ED5053	= RED	100+	ED2099 = RED	100+
ED5053Y	= YELLOW	20p	ED2099Y = YELLOW	19p
ED5053G	= GREEN	20p	ED2099G = GREEN	19p
ED5053O	= ORANGE	20p	OC-1 = CLIP FOR ED5053	31p

STANDARD MICROSYSTEMS

1-up		25-up		100-up	
COM2502	£6.80	£5.30	£4.62		
COM2502P	£4.65	£3.95	£3.50		
COM2017	£7.05	£6.00	£5.00		
COM2017P	£4.75	£4.15	£3.75		
COM2502H	£12.80	£11.25	£10.30		
COM2017H	£12.80	£11.25	£10.30		
COM2601	£16.40	£14.25	£13.15		
COM5016	£6.70	£6.15	£5.60		
KR2376 ST	£11.50	£9.20	£8.19		
KR3600 ST	£12.00	£10.20	£9.25		
1:MX-010	£6.70	£6.15	£5.55		

INTERFACE MODULES

PN	Instr	Amp	Bipolar input	Price
CY1010	Instr	Amp	Bipolar input	

The SECOND-USER Computer Specialists

Peripherals and Systems for Data Processing Systems, Equipment and Components

COMPUTER SALES AND SERVICES

Mini-Computer Exchange

PDP11/20 24K Processor with RF11/RS11 Disk Drive & Control and Remex High Speed Reader/Punch & Control
 Tektronix Graphics Display & Control (for PDP11 series)
 PDP81 16K Processor, rack-mounted, with Teletype Control
 PC81 High Speed Reader Punch
 RK05 Disk Drive (no controller)
 DF32 Disk Drive & Control (for PDP8E series)
 TU60 DUAL Cassette Drive & Control (for PDP8E series)
 RT02 Single-line Alphanumeric Display & Control (for PDP8E series)
 DEC 6ft. Cabinets

IMMEDIATE EX STOCK DELIVERY OF ASR33 TELETYPE, ALSO ASR35 and KSR33

IBM PUNCHED CARD EQUIPMENT

EX STOCK DELIVERY OF IBM 024, 056, 026, 077

Add 8% VAT to all prices shown. Carriage extra - details on request.

PAPER TAPE PUNCHES & READERS



TELETYPE BRPE 110 cps Synchronous Punch 5 7/8 channel Self-contained mains-operated unit consisting of punch unit base motor and tape supply spool Price £145.00 Sound reducing cabinet available at £25.00

FACIT 406B rack-mounting heavy-duty punch 5/8 channel maximum operating speed 150 cps Complete with supply and take-up spools tape low/out sensor and large built-in chad box £595.00. Control unit also available

TALLY P.120 panel-mounted perforator Asynchronous operation up to 120 cps Integral tape supply and take-up spools Price £150.00
 TALLY 420 Rack mounting perforator Asynchronous operation up to 60 cps Integral supply and take-up spools Complete with Model 5088 transistorised drive package £495.00

WELMEC LOW-SPEED PUNCH. Magnetically driven up to 17 cps Ideal for data logging Large chad box £45.00

FACIT 4001 Rack mounting high-speed reader A very high quality unit with dielectric reading and capstan drive Reading speed up to 500 cps for 1000 cps using separate spooler! Can be stopped between two consecutive characters. £650.00

TALLY R150A READER. 150 cps Fast rewind Suitable for rack-mounting Complete with supply and take-up spools £200.00

TALLY 424 rack-mounting starwheel reader Bidirectional operation up to 600 cps Complete with supply and take up spools Price £125.00, WELMEC R82 solenoid-operated mechanical reader Low-cost low-speed reader for speeds up to 17 cps Compact free-standing unit £45.00


DIGITAL PRINTING MECHANISM TYPE EP 101

Capacity 21 columns 16 print positions (0-9 + - L \$) Parallel data entry Column spacing 3.5mm Line spacing 5.1mm Character dimensions 1.8mm wide x 2.9mm high Power requirements 15V DC Current 150mA non-printing up to 410mA maximum printing load Very compact unit measuring 6 x 5 x 4 OUR BARGAIN PRICE £49.00 (P&P £1) Input Output connector also available price £2.00



Keyboards

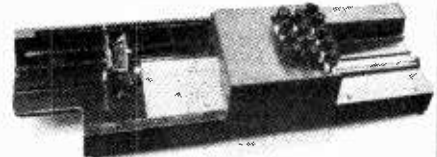NEW ECONOMY 80 COLUMN HAND PUNCH Completely redesigned with many important new features - send for brochure from £69.50



NEW STOCK JUST RECEIVED:

16-Key Japanese Keyboard. BRAND NEW SURPLUS! Magnetically operated relay switches mounted on PCB 9 white keys 4 black 2 yellow 1 red. Dimensions 3' x 3' x 1/2" Price £3.50 (P&P 30p)

4 BANK HONEYWELL ALPHANUMERIC KEYBOARD - BRAND NEW Mounted on printed circuit board (non-coded) 53 character keys + 10 instruction keys and 2 space bars Layout can be re-arranged as required Ideal for prototypes and special applications Hall-effect switches Power requirement + 5V 420 mA Price £20.00 (P&P £1)

REED-SWITCH 4-BANK ALPHANUMERIC KEYBOARD mounted on printed circuit board with ASCII coded output. 43 character keys + 2 shift keys and 12 instructional keys Ideal for data displays computer programming, etc (a) Ex-equipment housed in metal case £30.00 + £3.00 P&P. (b) Brand new mounted on PC board only £30.00 + £1.00 P&P

Callers welcome Monday to Friday 9 a.m. to 5 p.m.

COMPUTER SALES & SERVICES (EQUIPMENT) LIMITED
 49/53 Pancras Road, London NW1 2QB. Tel. 01-278 5571

WW-107 FOR FURTHER DETAILS

VOLTAGE REGULATORS				DIODES				MOTOROLA • MULLARD • SIGNETICS			
Variable Output				Rectifier Diodes				MONTAGNO • FERRANTI • GIM			
MC 1469 R 500 mA 2.5-37.0 V Positive			£1.83	1N 4001 Series 1 AMP			£0.04	from			
MC 1463 R 500 mA 3.6-37.0 V Negative			£2.50	1N 4002			£0.06	MOTOROLA • MULLARD • SIGNETICS			
MC 1723 CP2 150 mA 2.0-37.0 V Positive			£0.50	1N 4003			£0.07	MONTAGNO • FERRANTI • GIM			
MLM 305 G 20 mA 4.5-40.0 V Positive			£1.25	1N 4004			£0.08	Mullard Audio and Radio Modules			
MLM 304 G 20 mA 0.1-40.0 V Negative			£1.25	1N 4005			£0.09	*LP 1173 10 Watt Audio Amp £7.54			
MC 1466 L Floating Current Voltage regulator			£3.53	1N 4006			£0.10	*LP 1184 2 Very low distortion stereo pre amp £8.18			
Fixed Output				1N 4007			£0.13	*LP 1185 FM IF Amplifier £6.28			
1 Amp	MC 7805 CP	Negative Voltage -£1.60		MR 501 Series 3 AMP			£0.16	*P 1186 FM Tuner Module £7.78			
5 volt	MC 7812 CP	MC 7905 CP		MR 501			£0.17	*LP 1400 Stereo Decoder Module £8.02			
12 volt	MC 7815 CP	MC 7912 CP		MR 502			£0.18				
15 volt	MC 7818 CP	MC 7915 CP		MR 504			£0.20				
18 volt	MC 7824 CP	MC 7918 CP		MR 506			£0.25				
24 volt	MC 7824 CP	MC 7924 CP		MR 508			£0.29				
0.7 Amp	MC 7705 CP			MR 750 Series 6 AMP			£0.27				
5 V	MC 7715 CP			MR 750			£0.28				
15 V	MC 7718 CP			MR 751			£0.29				
18 V	MC 7718 CP			MR 752			£0.33				
				MR 755			£0.40				
				MR 756			£0.54				
DISPLAYS AND LED'S				Zener Diodes 400 mW BZY 88 Series				MULLARD TRANSISTORS/DIODES			
All from Monsanto MAN Series				2.7 to 33 volts				AC 126 £0.21			
7 segment displays - Red yellow green orange								AC 127 £0.18			
Type 1 Common anode RH decimal		0.3 inch	£1.34					AC 128 £0.13			
Type 2 Common anode overflow (-1)		0.4 inch	£1.66					AC 153 £0.08			
Type 3 Common cathode LH decimal								AC 176 £0.18			
Please specify colour height and type number read								AC 188 £0.32			
Type 4 0.12" Red display - £0.35								AC 191 £0.30			
Light emitting diodes - Red, yellow, green orange								AC 200 £0.17			
Type 1 0.2 inch diameter panel mounting			£0.38					AC 222 £0.08			
Type 2 0.125 inch diameter PCB mounting			£0.15					AC 220 £0.08			
Type 3 0.125 inch diameter high intensity			£0.32					AD 140 £0.36			
Please specify colour and type number read								AD 149 £0.50			
Unless otherwise specified alternate colours will be shipped if ordered colour is not available								AF 114 £0.25			
7 segment decoder drivers -								AF 115 £0.22			
CMOS common cathode MC 14511 CP			£1.23					AF 116 £0.20			
TTL common anode N 7447 B			£0.75					AF 117 £0.19			
TTL common cathode N 7448 B			£0.85					AF 121 £0.10			
DATA BOOKS								AF 125 £0.24			
Motorola								AF 126 £0.20			
Diodes Transistors etc over 3500 pgs			£10.50					AF 139 £0.31			
CMOS over 400 pgs			£1.50					AF 178 £0.40			
Linear integrated circuits over 800 pgs			£2.50					AF 239 £0.60			
Signetics								AF 102 £0.16			
Data/Applications book over 1600 pgs			£4.00					BA 154 £0.06			
Booklets on CMOS DMOS, 74LS, Consumer IC shift registers RAM S (specify title)			£0.20 each					BA 155 £0.07			
No V.A.T. this section								BA 182 £0.17			
RESISTORS								BAT 10 £0.65			
1/2 Watt Carbon resistors Mullard CR 37			1p each					BAW 10 £0.68			
1/2 Watt Metal film resistors Welwyn MR 5			5p each					BAW 62 £0.06			
8 Watt Wirewound resistors Welwyn W 22			37p each					BAX 13 £0.06			
12 Watt Wirewound resistors Welwyn W 23			39p each								
20 Watt Wirewound resistors Welwyn W 24			41p each								
W23 and W24 are available up to 27 kΩ all other standard values available											
I.C. SOCKETS											
14 pin	£0.12	16 pin	£0.15								
24 pin	£0.26	28 pin	£0.27								
40 pin	£0.30										
INTEGRATED CIRCUITS											
MC 1458 V Dual comp op amp											
NE 540 L Audio power driver											
NE 555 V Timer											
NE 556 A Dual Timer											
NE 561 B P L L with AM demod											
NE 562 B P L L with V.C.O											
NE 566 V P L L function gen											
Sigmetics Linear											
MC 1458 V Dual comp op amp											
NE 540 L Audio power driver											
NE 555 V Timer											
NE 556 A Dual Timer											
NE 561 B P L L with AM demod											
NE 562 B P L L with V.C.O											
NE 566 V P L L function gen											
Sigmetics Linear											
MC 1458 V Dual comp op amp											
NE 540 L Audio power driver											
NE 555 V Timer											
NE 556 A Dual Timer											
NE 561 B P L L with AM demod											
NE 562 B P L L with V.C.O											
NE 566 V P L L function gen											
Sigmetics Linear											
MC 1458 V Dual comp op amp											
NE 540 L Audio power driver											
NE 555 V Timer											
NE 556 A Dual Timer											
NE 561 B P L L with AM demod											
NE 562 B P L L with V.C.O											
NE 566 V P L L function gen											
Sigmetics Linear											

VALVES

A1065	1.25	EF36	0.65	G237	1.00
ARR	0.80	EF37A	1.10	K166	2.90
ARF3	0.60	EF40	0.70	K188	3.85
AT74	0.50	EF41	0.75	MH4	1.00
A12H	3.00	EF80	0.35	ML6	0.75
DAF96	0.60	EF83	1.25	OA2	0.45
DF96	0.60	EF85	0.40	OB2	0.45
DK96	0.75	EF86	0.45	PABC80	0.40
DL92	0.50	EF89	0.35	PC86	0.65
DL96	0.70	EF91	0.60	PC88	0.65
DY86/87	0.45	EF92	0.50	PC87	0.55
DY802	0.45	EF95	0.45	PC900	0.55
E88CC/011.30	0.40	EF183	0.40	PC84	0.45
E180CC	1.00	EF184	0.40	PC89	0.60
E182CC	3.00	EFL200	0.75	PC189	0.65
EAS0	0.40	EL34	0.70	PCF80	0.40
EABC80	0.40	EL35	0.70	PCF82	0.40
EAF42	0.70	EL37	2.20	PCF84	0.65
EB91	0.30	EL41	0.80	PCF86	0.65
EBC33	1.00	EL81	0.60	PCF200	0.90
EBC41	0.75	EL84	0.35	PCF201	0.90
EBF80	0.40	EL85	0.60	PCF801	0.55
EBF83	0.45	EL86	0.50	PCF802	0.55
EBF89	0.40	EL90	0.50	PCF805	1.10
EC52	0.40	EL91	1.00	PCF806	0.90
ECC81	0.85	EL95	0.70	PCH200	0.80
ECC82	0.35	EL504	0.80	PCL81	0.60
ECC83	0.35	EL821	1.80	PCL82	0.40
ECC84	0.35	EL831	0.70	PCL83	0.70
ECC85	0.45	EM80	0.55	PCL84	0.60
ECC86	1.25	EM84	0.40	PCL86	0.60
ECC88	0.55	EM87	1.00	PCL805/85	
ECC189	0.80	EY51	0.45		0.60
ECF80	0.45	EY81	0.45	PFL200	0.70
ECF82	0.45	EY86/87	0.45	PL36	0.60
ECF801	0.75	EY98	0.50	PL81	0.55
ECF804	2.50	EZ40	0.70	PL82	0.50
ECH42	0.85	EZ41	0.75	PL83	0.50
ECH81	0.40	EZ80	0.30	PLR4	0.50
ECH84	0.80	EZ81	0.35	PLR4	0.50
ECL80	0.60	GY1C	0.50	PL504	0.85
ECL82	0.40	GY501	0.80	PL508	0.95
ECL83	0.75	GZ32	0.65	PL509	1.35
ECL86	0.60	GZ34	0.80	PL802	1.85

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable

PLUMBICON TUBES TYPE XO 1071 Mullard £150.00

Py33	0.35	U25	1.00	UCL83	0.70	Z900T	1.50	5R4GY	1.00	8A05	0.55
Py80	0.80	U26	0.80	UF80	0.40	1A3	0.55	5U4G	0.55	8A6SW	0.70
Py/81/800	1.00	U27	1.00	UF85	0.50	IR5	0.50	5V4G	0.65	8A6S	0.80
		U191	0.75	UF89	0.50	IS4	0.35	5Y3GT	0.60	6A57G	1.00
Py82	0.45	U801	0.80	UL41	0.70	IS5	0.35	5Z4G	0.60	6A6	0.60
Py83	0.50	UABC80	0.45	UL84	0.50	IT4	0.35	5Z4GT	0.65	6A6V6	0.50
Py88	0.50	UAF42	0.70	UV41	0.50	IX2B	0.75	6A87	0.60	6A44GT	0.75
UBC41	1.10	UBC41	0.60	UV85	0.50	ZD21	0.50	6A67	0.60	6A45GT	1.00
UBF80	0.55	UBF80	0.50	VR105/30		ZK25	9.00	6A6H	0.70	6B7	0.70
QV03/101.50		UBF89	0.50	VR150/30	0.45	3A4	0.60	6AK5	0.45	6BA6	0.40
QV06.40A		UBL1	1.00			3D6	0.40	6AK8	0.40	6BE6	1.00
QV06.40		UBL21	0.75	VR150/30	0.45	3S4	0.50	6AL5	0.30	6B66G	0.40
QV03-12	8.00	UCC85	0.50			3V4	0.85	6AL5W	0.60	6B86	0.75
SC1/400	3.60	UCF90	0.80	X61M	1.50	5B/254M	5.00	6AM5	1.00	6B37A	0.60
SC17600	5.50	UCH42	0.80	X66	0.75	5B/255M	5.00	6AM6	0.60	6BR7	1.30
SP61	0.80	UCH81	0.50	Z900U	3.00	5B/256M	5.50	6AN8	0.70	6BW6	1.10
TT21	1.00	UCL82	0.45	Z801U	3.00						

VIDECON TUBE TYPE P 864 B English Electric £20.00


Please write or phone for current price of any of the transistors diodes shown below

TRANSISTORS

AAZ12-8AV10	AF186	BCY33	CRS25/25	OC26	OC170	2N3054
AF239	BCY72	GET115	OC28	OC172	2N3055	
AF126	BF115	GET116	OC29	OC200	2N3391	
AC127	BF167	GEK66	OC35	OC204	2N3730	
AC128	BF173	NKT222	OC36	OC206	2N3819	
AC176	BF185	NKT304	OC42	ZR11	2N4038	
AC107	BFY51	NKT404	OC44	ZR21	2N4058	
AC18	BFY52	OA5	OC45	ZR22	2N4061	
AC19	BFY27	OA7	OC70	2N456A	2N4172	
AC20	BSY38	OP70	OC73	2N525	2N5295	
AC39	BSY95A	OA71	OC75	2N696	3N126	
AC118	BY100	OA73	OC78	2N708	3N128	
BC136	BYZ16	OA79	OC78D	2N918	6Y6	
BC137	CRS1/20	OA91	OC81	2N1305	3N154	
BC148A	CRS1/30	OA200	OC82	2N1307	5X754	
AD211	CRS3/10	OA202	OC82DM	2N1309	2S303	
AD212	CRS3/20	OA2200	OC83	2N2062	112082	
AF114	CRS3/30	OC22	OC83B	2N2411	40235	
AF115	CRS3/40	OC25	OC139	2N2989	40250	
AF116			OC140	2N3053		
AF117						
AF118						
AF124						
AF125						
AF126						
AF127						
AF139						
AF178						

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc retail 749 3934 trade and export 743 0899



THE VALVE WITH A GUARANTEE


12E1	3.75	931A	6.00
12K5	1.50	954	0.60
12K7GT	0.55	955	0.50
12K8GT	0.75	956	0.50
12Q7GT	0.90	957	0.50
12SA7GT	0.80	1629	0.70
12SG7	0.55	2051	1.00
12SJ7	0.55	5933	3.00
12Y4	0.40	6057	0.80
14S7	1.00	6060	0.70
19A05	0.70	6064	0.60
19G3	8.00	6065	1.00
19G6	8.50	6067	2.50
19H5	15.00	6080	2.50
20P3	0.80	6146	3.35
20P4	1.10	6146B	4.00
25L6GT	1.70	8020	5.00
30C15	1.00	9001	0.40
30C17	1.10	9002	0.55
30C18	1.10	9003	0.70
30F5	1.00	9004	0.40
30FL1	1.10	9006	0.40
30FL2	1.10		
30L15	1.00		
30L17	1.00		
30P12	1.00		
30P19	1.00	DG7-5	12.00
30PL1	1.10	DG13-2	18.00
30PL13	1.10	MW13-35	
30PL14	1.10		35.00
35L6GT	0.80	VCR139A	8.00
35W4	0.55	5FP7	8.00
35Z4GT	0.70	8BJ	9.00
50C5	0.65	88L	9.00
50C6	0.60		
50D6G	1.20		
90E	0.50		
11E2	6.00		
75C1	0.75		
76	0.75		
78	0.75		
78	0.75		
78	0.75		
80	0.75		
85A2	0.75		
903	6.00		
905	18.00		
907	8.00		
908	8.00		
909	6.50		
913	6.50		
866A	1.60		

C.R. TUBES

DG7-5 12.00
DG13-2 18.00
MW13-35
VCR139A 8.00
5FP7 8.00
8BJ 9.00
88L 9.00

SPECIAL VALVES


CV2339 45.00
M503-2J4L
K301 7.00
KRN2A 6.00
725A 25.00
TY4-500 30.00
2J/192 140.00
2J/52A 75.00



MARCONI TF 867 SIGNAL GENERATOR
Range: 15KHz to 30MHz. Output 0.4uV to 4V at 13 or 75 ohms. Impedance with termination (supplied). Built in crystal check facility with handbook. £138 including carriage.



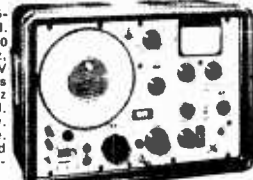RACAL COMMUNICATION EQUIPMENT. On top of the above we are able to offer a comprehensive selection of this modern high class equipment including LF Converters, panoramic adaptors, transmitter driver units (export only) linear amplifiers can be built to customer's requirements



TF 526B OSCILLATOR AND DETECTOR UNIT £59.00.

CINTIL TYPE 1873 SQUARE WAVE & PULSE GENERATOR. Freq 5c/s to 250Kc/s Pulse 0.5 uSec, 0.3uA Output to 50v for 1000Ω to 5v for 100Ω P.O.A

RADIOMETER TYPE MS111 SIGNAL GENERATOR. High quality Danish production 10KHz-110MHz £200 carriage £5 00

CT480 SIGNAL GENERATOR, 7 KMC/S to 12 KMC/S mod CW, F.M. Pulse £160 carriage £5 00

AVO NOISE GENERATOR CT 410 £30 carriage £2 00

BRIDGE IMPEDANCE NO 5. 0.10-10MΩ 1pF-1uF 1uH-H £85 carriage £4 00

EDISWAN STABILIZED POWER UNITS. To 100v, 50MA Type R1280 to 300v-150MA and, 300v 75mA

TEKTRONIX OSCILLOSCOPES 535 & 545. With plug in units. CA (33MHz) (double beam). G20MHz differential 50mv-20v) and D high gain differential 1MV-50v Price on application

BEST PRICES PAID FOR TEST AND COMMUNICATION EQUIPMENT. Single items or quantities. Private or Industrial.



TF 801B/2. Spec as for 801D but minor circuit differences. Few only left £120 carriage £5 00

TF 867 SIGNAL GENERATOR. Range 15KHz to 30MHz Output 0.4uV to 4v at 13 or 75 ohms Impedance with termination (supplied) Built in crystal check facilities With hand book £135.00 carriage £5 00

TF 144H SIGNAL GENERATOR. Freq range 10KHz-72MHz R.F. output 2uV to 2V at 50 ohms 400 and 1000Hz internal mod. Limited quantity only available. Full spec. and price on request

TF 801D/1/5 SIGNAL GENERATOR. Range 10KHz-72MHz R.F. output 0.1uV 1V source 400 and 1000Hz internal mod. Limited quantity only available. Full spec. and price on request

TF 893 AUDIO OUTPUT METERS. Up to 10W £55 carriage £3 00

TF 995A/1 or A/2 or A/2M or A5 SIGNAL GENERATORS. Very high class AM/FM 1.5MHz to 220MHz. Detailed spec. and price on application

EM1 OSCILLOSCOPE WMB AC/DC to 15 mc/s Time base 0.15Msec 15Msec £70 carriage £5 00

HR 23 TRIPLE DIVERSITY SSB RECEIVERS. Freq 3-27.5MHz V.F.O. at 6 Xtal positions Reception of independent single or double side band transmitters Full spec on application £350 carriage £35 00

TF 885A/1 VIDEO OSCILLATOR. 0-30KHz 5MHz 1Mv-31 6v £85 carriage £4 00

TF 934 DEVIATION METER. 250MHz £55 carriage £3 00

TF 1400S DOUBLE PULSE GENERATOR WITH TM 8600 SECONDARY PULSE UNIT for testing radar nucleosonic scopes counters filters etc £775 carriage £5 00

500/250 MEDIUM WAVE BROADCAST TRANSMITTERS. Export only Price and details on application

RACAL RECEIVERS MODELS. RA17L RA17W in fully working and tuned condition Prices on application RA98A SSB ADAPTOR £85.00.

HEWLETT-PACKARD OSCILLOSCOPES 175A with 1750A dual trace vertically plug-in and 1781B delay time base plug-in, 50MHz mini-meter band switch at 50 MV/cm Modes of operation Single, mixed delaying Full spec and price on application

BOONTON AM/FM SIGNAL GENERATOR. TYPE 202E & 202H 54-216MHz in 2 ranges £275.00.

BOONTON SIGNAL GENERATOR TS. 497/URS 2.5MHz 13MHz 30MHz 78MHz 180MHz 400MHz 0.1v-1.1v £150 carriage £3.00

TECHNICAL MATERIAL CORP EXCITER/TRANSMITTER MODE SELECTOR. Freq 2.32MHz M D and 10 crystal positions Vernier tuning USB, LSB var carrier insertion etc £200 carriage £10 00

FSK EXCITER. Freq 1-6 5MHz to 100Hz continued frequency shift up to 600Hz switched freq correction Modes FAX, FS, MSC, CW £50.00 carriage £5 00

AMPLIFIER UNIT TYPE 1430. Dynatron Production. Pulse amplifier with control Differential and "Integration" time constant 0.08 u-s to Bus Attenuation to 20db P.O.A

PULSE ANALYZER. Made by Dynatron with discriminator all meter reads, channel width threshold level P.O.A

RHOE & SCHWARZ, Z-g DIRECT GRAPH TYPE ZDU 30-420MHz 50Ω Directly measures multiterminal networks, phase shift, phase angle with complementary POWER SIGNAL GENERATOR TYPE SWLM high freq resolution, internal external mod up to 3v out £750.

FREQUENCY SYNTHESIZER TYPE XUA. 30Hz-30MHz with FREQUENCY INDICATOR TYPE FKM 15-30MHz 30-100MHz £1,000.

SIGNAL GENERATOR NO 16. 8cm-11cm £85 carriage £4 00

SIGNAL GENERATOR NO 13. 20MHz-80MHz AM FM CW 1uv-1v £65 carriage £4 00

KAHN SSB ADAPTOR TYPE RSSB - 62 - 18. Designed for receivers with 455-500KHz IF at 100mV (max) input Features electronic AFC carrier freq diversity to combat fading 20 sec R.C. memory to maintain tuning during severe fading individual carrier meters, nullifiers 10W distortion production demodulator £65 carriage £5 00

PLEASE NOTE
Unless offered as "as seen"
ALL EQUIPMENT
ordered from us is completely overhauled mechanically and electrically in our own laboratories

SOLARTRON CD1400 OSCILLOSCOPE with wide band amplifier CX 1441 and general purpose time base x-amplifier CX 1443 Up to 15MHz d.c. 750KHz on X10 gain Sensitivity 1mX mV/cm 10v/cm on X10 gain £130 carriage £3 00

DIGITAL VOLTMETERS
LM 14202. 2.2 5uv-1000v in 6 ranges Accuracy 0.05% of range i.e. ±1 digit. Sensitivity 2.5uv per digit £320.
LM 1426 25mV-1000v in 6 ranges. Acc range 1 in 0.2. £170.00.
Also available CD 1420 £170.00. CD 1440 2 £220.

ARR8 D & LF SPARES. We hold the largest stock in UK write for list

RF METERS. 0.8 amp 2 1/2" (USA) brand new £150 P&P 25p

TELEPHONE TYPE "J" tropicalised 10 LINE MAGNETO SWITCHBOARDS 50 LINE AUTOMATIC PRIVATE TELEPHONE SWITCHBOARDS

Open 9-12.30, 1.30-5.30 p.m. except Thursday 9-1 p.m.

FOR EXPORT ONLY.
RCA ET 4336 TRANSMITTERS
Also modified version of increased output to 700W COLLINS TYPE 231D 4/5KW TRANS-MITTER
10 channel. Autotone and manual tuning
C13 TRANSMITTERS, 3B 6Z TRANSCIVERS
NO 53 TRANSMITTERS, REDIFON 100SW SSB TRANSCIVERS, MULLARD C11 HIGH POWER INSTALLATION (1.000W)

PLEASE ADD APPROPRIATE VAT (8% or 25%)

COLOMOR (ELECTRONICS) LTD.
170 Goldhawk Rd., London, W.12
Tel. 01 - 743 0899

SERVICE TRADING CO

RELAYS

SIEMENS PLESSEY, etc.		MINIATURE RELAYS	
1	2	3	4
52	4-8	2c/o	75p*
58	5-9	6c/o	85p*
185	8-12	6M	85p*
230	9-18	2c/oHD	75p*
430	15-24	4c/o	85p*
600	10-20	6M	85p*
700	12-24	2c/o	65*

(*) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price HD=Heavy Duty, All Post Paid. (*Including Base)

OPEN TYPE RELAYS

- 6 VOLT D.C.** 1 make con 45p. Post 15p
- 9 VOLT D.C. RELAY**
3 c/o 5 amp contacts 70 ohm coil 85p. Post 15p
- 12 VOLT D.C. RELAY**
3 c/o 5 amp contacts 120 ohm coil 85p. Post 15p
- 24 VOLT D.C.**
2 HD c/o 700 ohm coil 85p. Post 15p
4 c/o 300 ohm coil 95p. Post 15p
100 VOLT a.c. 2 c/o 75p 3 c/o 85p. Post 15p

ENCLOSED TYPE RELAYS

- 6 VOLT DC** 3 c/o 85p. Post 15p
- 24V DC** 3 c/o 85p. Post 20p Base 15p
- 24 VOLT A.C.** Mfg ITT 3 h d. c/o contacts 65p. Post 20p. Base 15p extra.
- 55 VOLT A.C.**
3 heavy duty c/o contacts Price 65p. Post 20p Base 15p

230 VOLT A.C. RELAY

240V A.C. heavy duty 3 c/o contacts. Price 85p. Post 20p Octal base 15p extra

220/240 VOLT A.C. RELAY

3 c/o 5 amp cont Sealed M.f.g ISKRA £1.35. Post 20p Base 15p extra

ARROW 230/240V AC 2 c/o 15 amp contacts

Amp connectors £1.10. Post 20p

110 VOLT A.C. 2 c/o 20 amp £1.35. Post 15p

CLARE-ELLIOT Type RP 7641 G8

Miniature relay 675 ohm coil 24 volt D.C. 2 c/o 80p P.P

MANY OTHERS FROM STOCK. PHONE FOR DETAILS

LATCHING RELAY

Twin latching relay, flip-flop 2c/o each relay. Mains contacts 115 volts A.C. or 50 volt D.C. operation or 240 volts A.C. with 2.5K resistor. 85p. Post 20p



PRECISION CENTRIGUAL BLOWERS

Mfg by Smiths Industries. Miniature model. Series SF/200 Size 95mm x 82mm x 82mm. Aperture 38mm x 31mm 12 c.f.m. £2.75. Post 50p
Mfg by Airflow Developments Ltd. Precision made, continuously rated smooth running 230/240v A.C. motor 80C.f.m. As illustrated but with round aperture. £6.50. Post 75p.
Mfg by Woods
Extremely powerful 220 250v A.C. 0.3 amp 2,700 r.p.m. continuously rated Capacitor start. Cast construction Aperture 66mm x 50mm. O/A 200mm. £12.00. Post £1.00




230 VOLT FAN ASSEMBLY

Continuously rated, removable aluminium blades. Price £1.25. Post 50p.
VAT 25%



C/O MICRO SWITCH

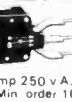VERY SPECIAL OFFER Mfg by C.E.M. 3 amp 250 volt 10 amp 125 volt .50 for £3. Post 36 100 for £5. Post 50p. 1,000 for £45. Post paid
DOUBLE POLE C/O or 2 make/2 break micro switch 10 amp 250 v A.C. With detachable roller assembly 10 for £2.50. Post 50p (Min order 10)



MINIATURE ROLLER

M switch OMRON type V15 FL 22-1C 10 for £2.00 post 50p (Min order 10)



230-250 VOLT A.C. SOLENOID

Similar in appearance to illustration. Approximately 1 1/2 lb. pull. Size of feet 1 1/2" x 1 1/2". Price £1.00. Post 25p.



SOLENOID HEAVY DUTY MODEL

230/250V A.C. Apprx. 10lb pull, 4" long x 2 3/4" wide x 3 1/2" high. £2.50. Post 50p

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx 25 lb pull at 1 in. travel. 2 solenoids of approx. 1 lb. pull at 1/2 in. travel. 6 solenoids of approx. 4 oz. pull at 1/2 in. travel. Plus 1 24V D.C. 1 heavy duty 1 make relay. Price £2.50. Post £1.00. ABSOLUTE BARGAIN.

240 V.A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body stainless steel core and spring in b.s.p. inlet outlet. Precision made British mfg. PRICE £2.25. Post 50p. NEW original packing



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600 watts of all lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p

1000 watt model	£4.00. Post 25p
2000 watt model	£8.00. Post 40p

VARIABLE VOLTAGE TRANSFORMERS

Carriage extra INPUT 230 v. A.C. 50/60 OUTPUT VARIABLE 0/260v. A.C.

- BRAND NEW. All types.
- 200W (1 Amp) £10.00
- 0.5 KVA (Max. 2 1/2 Amp) £11.50
- 1 KVA (Max. 5 Amp) £16.50
- 2 KVA (Max. 10 Amp) £30.00
- 3 KVA (Max. 15 Amp) £33.00
- 4 KVA (Max. 20 Amp) £60.00
- (max. 37.5 Amp) £102.50

LT TRANSFORMERS

- 0 6 12 volt a 10 amp £5.60 Post 70p
- 0 10 17 18 volt a 10 amp £7.90 Post £1.00
- 0 6 12 volt a 20 amp £9.00 Post £1.00
- 0 12 24 volt a 10 amp £9.20 Post £1.00
- 0 4 6 24 32 volt a 12 amp £9.80 Post £1.00
- 0 6 12 17 18 20 volt a 20 amp £10.40 Post £1.00

AUTO TRANSFORMERS

Step up step down 0 115 200 220 240 volts
At 75 watt £3.00 Post 40p. 150 watt £4.30 Post 50p. 300 watt £6.20. Post 60p. 500 watt £9.20 Post 75p. 1000 watt £13.50 Post 90p.

RING TRANSFORMERS

Functional Versatile Educational
These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer. By simply hand winding the required number of turns through the centre opening. E.g. Using the RT 100 V.A. Model the output could be wound to give 8V @ 12 1/2 Amp. 4V @ 25 Amp. or 2V @ 50 Amp. etc Price
RT 100VA 3 1/8 turns per volt. £5.00. Post 75p
RT 2KVA 1 5 turns per volt. £21.00. Post £1 50
RT 3KVA 1 5 turns per volt. £28.00. Post £1 50



STROBE! STROBE! STROBE!

- * HY-LIGHT STROBE Mk. IV *
- * Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s. *
- * Designed for large rooms, halls, etc. Light output greater than many so called 4 Joule strobes. Price £15.40. Post 75p. *
- * XENON FLASH GUN TUBES *
- * Range of Xenon tubes available from stock. S.A.E. for full details. *
- *****
- * ULTRA VIOLET BIG BLACK LIGHT *
- * 400 Watt. Mercury vapour ultra violet lamp. Extremely compact and powerful source of u.v. Innumerable industrial applications also ideal for stage display, discos etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £24.00. Post £1 50. Spare bulb £8.00. Post 65p. *
- *****
- * ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES *
- * 4ft. 40 watt £6.00 (callers only). 2ft. 20 watt £4 60. Post 60p (For use in sw. o. pin (stings) MINI 12in. 8 watt £1.75. Post 25p. 9in. 6 watt £1.40. Post 25p. Complete ballast unit and holders for either 9" or 12" tube. £1.70. Post 30p (9" x 12" measures approx.) *
- *****

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights, or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Price only £58.00 Post 75p S.A.E. (Footscap) for further details



WHY PAY MORE?!

MULTI RANGE METER A.C. volts 2.5-500 D.C. volts 2.5-500 (Sensitivity 20000Ω/V DC & AC) DC current 0/1/10/100 mA. Ohms range Sturdy compact moving coil instrument with 21 ranges. dimensions 120 x 80 x 44mm. Weight 0.32 kg SERVICE TRADING CO Price £5.00. incl leads and battery Post 50p (Total price inc. VAT & Post. £5.94).



METERS NEW

90mm Diameter
Type 65C5 2A D.C. M/C 5A D.C. M/C 10A D.C. M/C.
20A D.C. M/C
Type 62T2 1A A.C. M/I 20A A.C. M/I 300V A.C. M/I ALL ABOVE
£2.50. Post 30p
Type 65L5 300V A.C. R/M/C. £2.75. Post 30p



VAT VAT AT 8% MUST BE ADDED TO ALL ORDERS
FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

NICKEL CADMIUM BATTERY

Type V022: 1.2V 22Ah height 210mm width 55mm depth 25mm weight 1050 gms £17.75. post 50p + 25p extra each additional cell.

GEARED MOTORS

100 R.P.M.
115 lb. ins. 110 volt. 50Hz. 2.8 amp., single phase, split capacitor motor. Emense power. Continuously rated. Totally enclosed. Fan cooled. In-line gear box. Length 250mm. Dia 135mm. Spindle Dia 15.5mm. Length 145mm. ex-equipment £14.00. Post £1 50. Suitable transformer 230/240 volts tested £8.00. Post 75p

15 R.P.M.
Type SD48 15 r.p.m. 80 lb. ins. input 100/120 volt A.C. Length incl gearbox 270mm. Height 135mm. Width 150mm. Shaft drive 16mm. Weight 8.5 Kilos. BRAND NEW. Price £10.00. carr. £1 00. Suitable transformer for use on 220/240 volt A.C. £3.85. Post 50p.

60 R.P.M. REVERSIBLE

220/240 volt A.C. Small, powerful, continuously rated motor. Mfg. BERGER (Germany). Size 80mm x 65mm x 65mm. Spindle dia. 6mm. Length 155mm. Weight 725 grams. £6.50. Post 50p



BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle .38 amp.
(Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/30th h.p. 50 cycle 2.8 amp. The above two precision made U.S.A. motors are offered in as new condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. input.
Price, either type £6.25. Post 75p or less transformer £3.75. Post 65p
These motors are ideal for rotating aeriels, drawing curtains, display stands, vending machines, etc etc

20 r.p.m. GEARED MOTOR


230/240 volt 20 r.p.m. motor. £1.00. Post 20p.

REVERSIBLE MOTOR 230V A.C.

General Electric. 230v A.C. 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 95mm. Spindle 5/16" dia. 20mm long. Ex-equipment tested £3.00. Post 50p.


BENDIX MAGNETIC CLUTCH

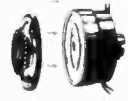A superb example of Electro-mechanics! The main body is in two sections. The coil section is fixed and has a 3/8 in. sleeve. The drive section rotating on the outer perimeters. The uniting plate has 3/8 in. ID bearing concentric with main section and 18-tooth cog wheel.
When energized transmission is extremely powerful. 24V d.c. at 240MA. OUR PRICE JUST £3.50. Post 45p



ROTARY VACUUM AIR COMPRESSOR AND PUMP

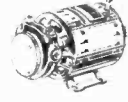Carbon vane, oil-less 100/115V A.C. 1.12 h.p. motor. 50/60 cycles. 28.5/3450 r.p.m. 20" vacuum 1.25 c.f.m. 10 p.s.i. (approx. figures). New unused surplus stock, with exact connection data. Fraction of maker's price. £12.00. Post £1 00. Suitable transformer £3.50. Post 50p



TIME SWITCH

Horstmann Type V Mk II Time Switch 200/250 volt A.C. Two on/two off every 24 hours, at any manually pre-set time. 30 amp contacts. 36-hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case, with glass observation window. Built to highest Electricity Board spec. individually tested. Price £7.75. Post 50p (Total inc. VAT £8.91)



A.C. MAINS TIMER UNIT

Based on an electric clock with 25 amp. single-pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p (Total inc. VAT & Post £2.87.)



POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
25 WATT 10 25 100 150 250 500 1k 1.5k ohm
£1.70. Post 20p. 50 WATT 1 5 10 25 50 100 500 1k ohm
£2.10. Post 25p. 100 WATT
1/10/25/50/100/250/500/1k/1.5k/2.5k/5k ohm. £3.30. Post 35p
Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above Rheostats, 22p ea.

INSULATION TESTERS (NEW)

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in., W. 4 in., H. 6 in., weight 6 lb.
500 VOLTS 500 megohms £36.00. Post 80p.
1000 VOLTS 1000 megohms £14.00. Post 80p.



ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560. Closed Saturdays.

SERVICE TRADING CO.

SHOWROOMS NOW OPEN AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ. Tel.: 01-437 0576

MULLARD THYRISTOR TRIGGER MODULE

This product produces phase control triggering it has two isolated outputs so one thyristor or two thyristor (in separate arms of bridge) may be controlled by one module. The timing circuit is synchronised to the mains frequency and control is by an external variable resistor or from a voltage or current source. Provision is made for feed-back where automatic control is required. Price £5.95.



MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v 9v 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries PP1 PP3 PP4 PP6 PP7 PP9 and others. Kit comprises main transformer rectifier smoothing and load resistor condensers and instructions. Real snip at only £1.50. VAT and postage 60p.

MULTI-SPEED MOTOR

Six speeds are available 500 850 and 1 100 r.p.m. and 8,000 12,000 and 15 500 r.p.m. Shaft is 1/4in diameter and approximately 1in long. 230V/240V its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx 2in dia x 5in long. Price £1.40 + 45p post and VAT.



PEED CONTROL SWITCH 50p + 4

DC HIGH CURRENT PANEL METERS

3 1/2in wound wide angle 240 movement meters flush mounting fitted with external shunts made by Crompton Parkinson brand new still in maker's cartons. These are a real bargain at 1.50 each. Reasonable quantities available in the following ranges: 0-10 amps 0-20 amps 0-30 amps 0-40 amps 0-50 amps. Post and VAT 80p each.



TAPE DECK

In metal case with carrying handle heavy fly wheel and capstan drive. Tape speed 3 3/4. Mains operated on metal platform with tape head and guide. Not new but guaranteed good working order. Price £1.50 plus VAT and postage £1.50.



SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450v). Unit in Box all ready to work. £7.95 plus 95p VAT and postage.




OVEN THERMOSTAT

Made by the famous Diamond H Company this has a sensor joined by a capillary to a variable control and when fitted with a knob is ideal for many ovens or processes. 50p each + post and VAT 15p.



HONEYWELL PROGRAMMER

This is a drum timing device the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro-switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control boiler firing dispensing and vending machines. Display lighting animated and signs. Signalling etc. Price from makers probably over £20 each. Special snip price £9.95. £1 00 post and VAT. Don't miss this terrific bargain.

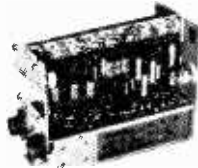

BREAK-DOWN UNIT

Contains hundreds of useful parts some of which are as follows - 66 silicon diodes equivalent OA 911 68 resistors mostly 1/2 watt 5% covering a wide range of values. 4 x 1 mfd 400v mfd condensers. 15 x 0.1 mfd 100v condensers. 2 RF chokes. 8 x B9 valve holders. 1 x 4H choke. 1 x 115v transformer. 1 boxed unit containing 4 delay lines also tag panels trimmer condensers suppressors etc. on a useful chassis sized approx 9in x 5in x 7in. Only 75p (the 66 diodes would cost at least 10 times this amount). This is a snip not to be missed. Post and VAT 75p.

THIS MONTH'S SNIP

250 watt Transformer is a very versatile transformer which can be used for many purposes. Rated at 250 watts it is very well built with frames for upright mounting and is varnish impregnated. Its primary is for 230 240 volts 50 cycles it has four secondaries each 10v very high current windings. Just a few of the circuits it can power are: 10 0 10v at up to 12 amps. 20 0 20v at up to 6 amps. single 10v at 25 amps. single 20v at 12 1/2 amps. single 30v at 9 amps. single 40v at 6 1/2 amps. The transformer can be used for power circuits (charging etc) or for amplifiers there being an earth screen between primary and secondaries. A transformer like this today would cost at least 15 from the makers however we are making a special offer at £3.50 + 28p post + 1 + 8p each. Grab some while you can our stock may not last long.

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one. In easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30 - but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £15.50 including VAT and postage.



TWIN OUTPUT POWER PACKS

These have two separately R.C. smoothed outputs so can operate two battery radios on a stereo amp without cross modulation (they will of course operate one radio/tape cassette/calculator in fact any battery appliance and will save their cost in a few months). Specs: Full wave rectification double insulated mains transformer - total enclosed in a hard P.V.C. case - three core mains lead terminal output - when ordering please state output voltage. 4 1/2v 6v 7 1/2v 9v 12v or 24v. Price £3.95. Post and VAT included.



TERMS. Where order is under £5 please add 30p surcharge to offset packing expenses.

J. BULL (ELECTRICAL) LTD.

(Dept. W.W.), 103 TAMWORTH ROAD
CROYDON CRO 1XX

YOU MAY BE IN TIME

for a valve volt-meter at £7.50 - a signal generator at £8.50, a frequency standard at £19.50. As these and many other good buys were offered in our December Advanced Advertising News Send S.A.E. for a copy today.

RELAY BARGAIN

Type 600 relay. 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable or closing off DC 6v DC 12v DC 24v or AC mains using resistor and rectifier. 40p each. Resistor and rectifier 20p extra. Post and VAT 20p.


MAINS TRANSFORMERS

All standard 230-250 volt primaries	£	p
1v	1 amp (special)	1.75
2.4	5 amp	.85
6.3v	2 amp	1.25
6.3v	3 amp	1.75
9v	1 amp	.95
9v	3.5 amp	2.50
12v	1 1/2 amp	1.50
12v	1 amp	1.00
6.5v 0.6 5v	1 amp	1.50
18v	1 amp	1.50
24v	2 amp	2.25
24v	3 amp	3.50
12 0 12v	50mA	1.20
6 0 6v	50mA	1.20
8 0v 8v	1/2 amp	1.50
18 0 18v	2 amps	3.50
25v	1 1/2 amp	1.95
50v 2 amp & 6.3v	1 amp	4.50
60v 5 amp & 5v	1 amp	7.50
27v	8 amp	4.50
30v	37 amp	22.00
80v tapped 75v & 70v	4 amp	5.50
230v 60mA & 6.3v	1.5 amps	1.75
275 0 275v at 90mA & 604v	3 amps	2.35
EHT Transformer 5000v 23mA (intermittent)		5.50
Charger Transformers		
6v and 12v	2 amps	1.50
6v and 12v	3 amps	2.25
6v and 12v	5 amps	3.50

Add 30p per l. to cover postage and VAT 25% And 25% except for industrial types.

ONLY £1.50 FOR SEVEN ELECTRIC MOTORS

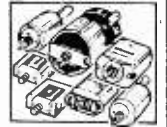7 powerful batt motors as used in racing cars and power models. Output and types vary for use in hundreds of projects - Tools toys models etc. All brand new reversible and for 1 1/2-12v. Wiring diagrams inc. VAT and post. 40p. FREE plan for min. power station.




1 R.P.M. MOTOR + GEAR BOX
Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit. Price £1.50 + 30p post and VAT.

BLACK LIGHT

As used in discotheques and for stage effects etc. Virtually no white light appears until the rays impinge on luminous paint or white shirts etc. We offer 9in. 6w tubes complete with starter choke lamp-holders and starter holder. Price £2.75 + 30p post. Tubes only £2. Post and VAT 50p.

230 volt/175 watt model £6.50. Post & VAT 92p.

NEW OLSON SLOPING CASES



Type	Panel Dim	Depth	Height	Price
1	150 m/m x 100 m/m	95 m/m	95 m/m	£1.55p
2	200 m/m x 100 m/m	95 m/m	95 m/m	£1.75p
3	250 m/m x 100 m/m	95 m/m	95 m/m	£1.95p

New range of cases at 45° sloping panels, attractively designed of robust construction and finished in two tone colour. Supplied complete with four rubber feet, available from stock in three different widths.

Materials
Cases made from 20G. steel.
Front panels made from 20G. aluminium.

Colours
Cases sprayed in light brown hammer finish, front panels sprayed in light grey semi-gloss enamel.

PORTABLE POWER DISTRIBUTION

COMPLETE WITH 6FT CABLE AND 13-AMP PLUG

4 Sockets 13A	8.80
6 Sockets 13A	10.45
4 Sockets 13A/SW	10.06
6 Sockets 13A/SW	11.11


PLEASE ADD 8% FOR V.A.T. PLUS P & P

Trade Counter is open for personal callers from 9 a.m. to 5.00 p.m. Monday-Friday

OLSON ELECTRONICS LTD. 5-7 LONG ST., LONDON. E.2
TEL: 01-739 2343

WW-084 FOR FURTHER DETAILS

New range of ILLUMINATED SWITCHES

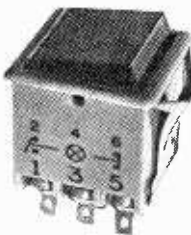

Here's a new illuminated switch from the famous Finnish ESMI range. Strong grey plastic case (cut-out size 21 mm sq.), contacts for make/break, make/make and break/break, capacity 1A (60V AC), 1/2A (48V DC). Takes variety of "push-in" miniature bulbs. Screw, soldering or AMP connections. Built-in panel-grip fixing, 4 lens colours, engraved if required. Rocker or push-button versions, with matching signal lamps.

CONTARNEX LIMITED

252 MARTIN WAY, MORDEN
SURREY SM4 4AW, ENGLAND TEL. 01-540 1034/5

Send for details of complete range

AC/DC MULTIMETER TYPE U4324*

With taut band suspension movement

High sensitivity movement and full coverage of AC and DC current and voltage ranges

0 06 0 6 6 60 600mA 3 Amps DC
0 3-30-300mA 3 Amps AC
0 6-1 2 3 17 30 60 120 600 1200 Volts DC
3 6 15-60-150-300-600 900 Volts AC
45 to 20 000 Hz Freq. Range
50uV: 5-50 500kΩ!
25Ω: 0 5 50kΩ!
5MΩ! Rev. Range

Price £9.95 + 8% VAT

*** STAR OFFER BC 207**
50 for £2.50 + 25% VAT
Plastic BC 107

*** STAR OFFER 2N 3055A**
8 for £2.50 + 8% VAT

*** STAR OFFER IN 4002**
100 for £2.50 + 8% VAT
Silicon rectifier
1 amp 100 volt

Please add VAT and 20p P.&P.

Send Stamped Addressed Envelope for FREE Catalogue of over 2,000 Items

AMATEUR COMPONENTS

ORCHARD WORKS, CHURCH LANE, WALLINGTON, SURREY SM6 7NF



the audio amateur ?

What a trip old Richard's Rhine journey could have become had he built his own mixers, 900 watt amps, octave equalizers, 24 inch woofers, electronic crossovers, and home brew electrostatics. Zounds what sounds!

Ask our Rhine maidens for details.


the Audio Amateur Yellow Oak Cottage
Tillington nr. Hereford HR48LQ

Send now for a free prospectus.

Craig Stark of STEREO REVIEW says: "Top quality, only U.S. publication devoted to the serious audiophile constructor."

Name _____

Address _____



OVER 25 PROJECTS

ETI TOP PROJECTS No. 3

COMPLETE DETAILS FOR BUILDING:

GRAPHIC EQUALISER	DIGITAL VOLTMETER
IMPEDANCE METER	STEREO FM TUNER
25W STEREO AMP	TACHO TIMING LIGHT
COLOUR ORGAN	RADAR ALARM
DIGITAL DISPLAY	LINE AMPLIFIER
ELECTRONIC IGNITION	LIGHT DIMMER

ON SALE AT YOUR NEWSAGENTS NOW: £1.00

IN CASE OF DIFFICULTY SEND £1.20 (INC. POSTAGE) TO: ETI TOP PROJECTS No. 3, 36 EBURY ST. LONDON SW1W 0LW

Now the European electronics industry is an open book


It's the European Electronics Suppliers Guide—the only reference book of its kind you can buy (And, in fact, the only multi-lingual, multi-national buyers guide in the electronics world.)

Every feature is designed to take you fast to the name of the supplier you need, whatever the country, whatever the product concerned.

Products and manufacturers are broken down into 26 distinct market sectors. Over 600 types of products are listed, cross-referenced with over 1700 manufacturers. Principal Trade Associations in every country are included too. And all essential information appears in three languages—English, German and French.

The price is £18.50, including post and packaging. Not much for opening up a continent.

Post this coupon—with your cheque—today.

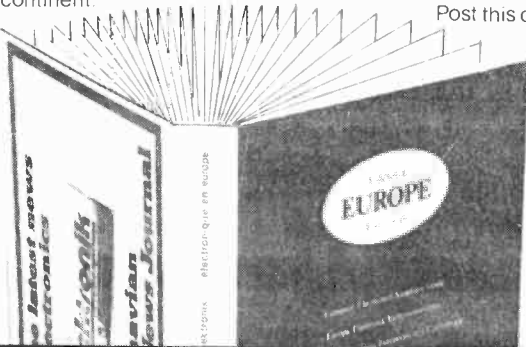

To: General Sales Dept., IPC Electrical-Electronic Press Ltd., Room 11, Dorset House, Stamford St., London SE1 9LU, England.

Please send me a copy of The European Electronics Suppliers Guide. I enclose cheque/money order for £18.50 (100 Swiss Francs) inclusive.

Name _____

Address _____

*Cheques should be made payable to IPC Business Press Ltd.

Registered in England, No. 677128
Registered Office: Dorset House, Stamford Street, London SE1 9LU, England.

EXCLUSIVE OFFERS

WORLD-WIDE RANGE NEVER BEFORE OFFERED

COMPLETE TRANSPORTABLE H.F. COMMUNICATIONS CENTRE housed in Air Conditioned TRAILER fitted two COLLINS KWT-6 500W S.S.B. Transmitter-Receiver and one COLLINS Receiver all fully tuneable 2 to 30 mcs digital readout synthesised frequency control, with line amplifiers and inputs, operating position and remote control facilities and ancillary equipment. Power input 115V or 230V A.C. Full details on application.

PHILCO HC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS 2/30 mcs. Ten fully tuneable channels to 9.5 mcs with synthesizer. Single and diversity reception on 1SH, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS

Table with columns: Our Ref, Height in inches, Width in inches, Depth in inches, Rack Panel in ins, Price. Lists various cabinet models like CR, FA, FC, FH, FI, LL6, LL7, LL8, LL9, LL10, MM.

Table with columns: Our Ref, Height in inches, Channel, Rack Panel, Base, Price. Lists console models like RG.

Full details of all above on request. We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

- List of electronic components and their prices: Lavoie OS-62 Oscilloscopes, S.T.C. Rx 5 Receivers, 45 feet Uniratio 4 Co-ax 50 ohms, Furzehill Spectrum Analysers, 25 ft Telescopic Aerial Mast, Bausch & Lomb Episcopes, Advance L1 Signal Generator, etc.

We have a quantity of Power Transformers 250 watts to 15KVA at voltages up to 40KV. Best quality at low prices. List available.

- List of power supplies and adaptors: Racal RA-63 SSB Adaptors, Racal RA-237 L-W Converters, 19" Blank Rack Panels, Apeco Dial a Copy Photo Copier, etc.

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

- List of tape recorders: Ampex TM2 4 speeds, 7 tracks 1/2", Ampex FR-1100, 6 speeds, 2 tracks 1/2", Ampex FR600, 4 speeds, 7 tracks 1/2", etc.

Prices of above £70 to £400

Also Transport Decks only available

COMPUTER HARDWARE

- List of computer hardware: PRINTER, High speed 1000 lines p.m., TAPE READER, High-speed 5/8 track 800 c.p.m., CARD READER 80 col. 600 c.p.m.

Prices on Application

PLEASE ADD CARRIAGE AND V.A.T. AT APPROPRIATE RATE TO ABOVE

P. HARRIS ORGANFORD-DORSET BH16 6BR BOURNEMOUTH-765051 (0202)

GIRO NO. 331 7056. Access and Barclaycard accepted. C.W.O. only. Terms of business: as in our catalogue. Export Order enquiries welcome (£5 min.). Official Orders accepted from Educational & Government Departments. ALL PRICES INCLUDE VAT & P. & P. Shop hours: 9-12.30, 1.30-5 p.m. 5 days except Wednesday.

1976 ISSUE 66 PAGES - 3000 ITEMS FULLY ILLUSTRATED. Includes 20p plus 10p postage. Lists categories: TRANSFORMERS, SEMICONDUCTORS, MODULES - AUDIO, HEATSINKS - S-OEC, AUDIO ACCESSORIES, TOOLS - TEST METERS, CALCULATORS - AUDIO, LEADS - BATTERIES - KITS, RESISTORS - CAPACITORS, CASES - COILS - BOOKS, CONNECTORS - VEROBARD, PC MATERIALS - HARDWARE, BOXES - SCREWS - KNOBS, POTS - STORAGE UNITS, ETC., ETC.

SPECIAL RESISTOR KITS (CARBON FILM 5%) (Prices include post & packing). 10E12 1/4W or 1/4W KIT 10 of each E12 value 22ohms-1M, a total of 570 £5.29 net. 25E12 1/4W or 1/4W KIT 25 of each E12 value. 22 ohms-1M a total of 1425 £12.64 net.

SPECIAL CAPACITOR KITS C280 Kit-PC Mounting polyester 250V 5 of each value 0.01, 0.022, 0.047, 0.1, 22µF, 2 of 0.47, 1µF £1.98 net. C296 Kit-Tubular polyester 400V 5 of each value 0.01, 0.022, 0.047, 0.1, 0.22µF, 2 of 0.47, £2.67 net. Ceramic Kit-square plaque 50V 5 of each value 22, 33, 47, 100, 220, 330, 470, 1000µF, 2200, 4700µF, 0.01µF £1.86 net. 250V Paper Kit-Tubular metal case, 3 of each value 0.05, 0.1, 0.25, 0.5 1µF £1.41 net. 500V Paper Kit-Tubular metal case, 3 of each value 0.025, 0.05, 0.1, 0.025, 0.5µF £1.41 net. 1000V Paper Kit-Tubular metal case, 3 of each value 0.01, 0.025, 0.05, 0.1µF £1.63 net.


B.H. COMPONENT FACTORS LTD.

MULTIMETER U4341 27 Ranges plus Transistor Tester 16 700Ω/Volt Vdc -0.3 -900V in 8 ranges Vac -1.5 -750V in 6 ranges Idc -0.06 -600mA in 5 ranges Iac -0.3 -300mA in 4 ranges Resistance -2K Ω -2M Ω in 4 ranges Accuracy -dc -2 1/2% ac -4% of F S D Iafe 10 -350 in 2 ranges Size -115 x 215 x 90mm Complete with steel carrying case, test leads and battery PRICE £12.10 net P&P 75p



U4341

MULTIMETER U4313 33 ranges Knife edge with mirror scale 20 000Ω/Volt High accuracy, mVdc -25mV Vdc -1.5 -600V in 9 ranges Vac -1.5 -600V in 9 ranges Idc 60 -120 microamps in 2 Idc -0.6 -1500mA in 6 ranges Iac -0.6 -1500mA in 6 ranges Resistance -1K Ω -1M Ω in 4 ranges db scale -10 to +12db Accuracy -dc -1 1/2%, ac -2 1/2% Size -115 x 215 x 90mm Complete with steel carrying case, test leads and battery PRICE £16.09 net P&P 75p

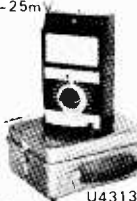

U4313

MULTIMETER U4323 22 Ranges plus AF-IF Oscillator 20 000Ω/Volt Vdc -0.5 -1000V in 7 ranges Vac -2.5 -1000V in 6 ranges Idc -0.05 -500mA in 5 ranges Resistance -5Ω -1M Ω in 4 ranges Accuracy -5% of F S D OSCILLATOR -1 KHz and 465 KHz (A M) at approx 1 volt Size -160 x 97 x 40mm Supplied complete with carrying case test leads and battery PRICE £9.95 net P&P 75p



U4323

MULTIMETER U4324 34 Ranges High sensitivity 20 000 Ω/Volt Vdc -0.6 -1200V in 9 ranges Vac -3 -900V in 8 ranges Idc -0.06 -3A in 6 ranges Iac -0.3 -3A in 5 ranges Resistance -25Ω -5M Ω in 5 ranges Accuracy -dc and R -2 1/2% of F S D ac and db 4% of F S D Size -167 x 98 x 63mm Supplied complete with storage case test leads spare diode and battery PRICE £11.72 net P&P 75p



U4324

(WWW), LEIGHTON ELECTRONICS CENTRE, 59 Leighton Buzzard, LU7 7EG. Leighton Buzzard 2316 (Std code 05253)

Wilmslow Audio THE firm for speakers!



- Speaker list: Baker Group 25, 3, 8, or 15 ohm £8.64, Baker Group 35, 3, 8 or 15 ohm £10.25, Baker Deluxe, 8 or 15 ohm £13.75, Baker Major, 3, 8 or 15 ohm £11.87, Baker Regent, 8 or 15 ohm £10.00, Baker Superb, 8 or 15 ohm £18.12, Celestion HF1300 8 or 15 ohm £7.75, Celestion MH 1000 horn, 8 or 15 ohm £13.50, Decca London and X over £42.25, Decca DK30 and X over £24.06, EMI 5" Mid range £3.50, EMI 6 1/2" d/c cone roll surr. 8 ohm £4.37, EMI 8 x 5, 10 watt, d/c, roll/s 8 ohm £3.95, EMI 14" x 9" Base 80 £13.25, Elac 59RM 109 15 ohm, 59RM 1148 ohm £3.44, Elac 6 1/2" d/c roll/s 8 ohm £4.06, Fane Pop 15 watt 12" £5.25, Fane Pop 25T 30 watt 12" £7.50, Fane Pop 50 watt, 12" £12.00, Fane Pop 55, 12" 60 watt £15.50, Fane Pop 60 watt, 15" £17.25, Fane Pop 70 watt 15" £18.75, Fane Pop 100 watt, 18" £29.95, Fane Crescendo 12A or B, 8 or 15 ohm £34.50, Fane Crescendo 15, 8 or 15 ohm £47.50, Fane Crescendo 18, 8 or 15 ohm £62.95, Fane 807T 8" d/c roll/s, 8 or 15 ohm £5.75, Fane 801T 8" d/c roll/s 8 ohm £9.95, Goodmans 8P 8 or 15 ohm £5.95, Goodmans 10P 8 or 15 ohm £6.25, Goodmans 12P 8 or 15 ohm £13.95, Goodmans 12P-D 8 or 15 ohms £16.95, Goodmans 12P-G 8 or 15 ohms £15.95, Goodmans Audiom 100 15-ohm £13.90, Goodmans Audiom 200 8 ohm £13.90, Goodmans Axent 100 8 ohm £8.44, Goodmans Axiom 402 8 or 15 ohm £20.00, Goodmans Twinaxiom 8" 8 or 15 ohm £10.55, Goodmans Twinaxiom 10" 8 or 15 ohm £10.95, Kef T27 £6.06, Kef T15 £6.94, Kef B110 £8.37, Kef B200 £9.50, Kef B139 £16.95, Kef DN8 £2.31, Kef DN12 £5.99, Kef DN13 £4.50, Richard Allan HP88 8" 45 watt £13.25, Richard Allan CG8T 8" d/c roll/s £7.50, STC 400 1 G super tweeter £6.56, Baker Major Module, each £14.75, Goodmans Mezzo Twinkit, pair £47.19, Goodmans DIN 20, 4 ohm, each £14.75, Helme XLK35, pair £24.00, Helme XLK40, pair £35.00, Helme XLK30, pair £19.00, Helme XLK50, pair £56.00, Kefkit 1, pair £53.00, Kefkit III, each £48.00, Richard Allan Twinkit, each £14.95, Richard Allan Triple 8, each £22.50, Richard Allan Triple, each £27.95, Richard Allan Super Triple, each £32.50, Richard Allan RA8 kit, pair £42.00, Richard Allan RA82 kit, pair £66.00, Wharfedale Linton 2 kit (pair) £23.12, Wharfedale Glendale 3 XP kit, pair £58.00, Wharfedale Dove Dale 3 kit, pair £63.12, All Radford, Gauss, Castle, Jordan Watts, Eagle, Lowther, Peerless Tannoy units in stock

Prices correct at 3 2 76 INCLUDING VAT AT 25% ON HI-FI 8% ON PRO & P.A.

Cabinets for PA AND HiFi, wadding, Vynair, etc. Send stamp for free booklet "Choosing a Speaker" FREE with all orders over £10 - HiFi Loudspeaker Enclosures Book All units are guaranteed new and perfect Prompt despatch Carriage Speakers 50p each, 12" and up 75p each, tweeters and crossovers 30p each, kits 80p each (£1.60 pair).

WILMSLOW AUDIO Dept. WW Loudspeakers & Export Dept: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Discount HiFi, PA etc: 10 Swan Street, Wilmslow. Radio, Hi Fi, TV: Swift of Wilmslow, 5 Swan Street, Wilmslow. Tel. (Loudspeakers) Wilmslow 29599, (HiFi, etc.) Wilmslow 26213.

WW-010 FOR FURTHER DETAILS

SPECIAL LOW PRICE ARRANGEMENTS FOR VISITING OVERSEAS TRADE FAIRS

wireless
world



IPC Electrical-Electronic Press Ltd., the world's largest publishers of computer, electrical and electronic journals, have made special arrangements for readers wishing to visit important overseas trade fairs. The cost, in most cases, is little more than the normal air fare but includes – travel by scheduled airline from Heathrow and Manchester * first-class hotel accommodation * arrival and departure transfers * admission to the trade fair * services of an experienced tour manager. The current programme comprises the following tours.

To obtain a brochure and booking form, tick the box against the tours in which you are interested, complete the coupon and post to the exclusively appointed travel agent, Commercial Trade Travel Ltd., Carlisle House, 8 Southampton Row, London WC1. Telephone 01-405-8666 or 01-405-5469.

International Electronic Components Exhibition Paris, April 5-10 1976. Two nights at the de luxe Meridien Hotel. Fully inclusive price £86.50, extra nights as required.

International Electrical and Electronics Engineers Exhibition – I.E.E.E. ELECTRO. – Boston – May 11-14, 1976. 10 nights at the de luxe Statler Hilton Hotel. Fully inclusive price – £283.00.

Compec Europe Exhibition – Brussels – May 18-20, 1976. 2 nights at the first class Royal Windsor Hotel. Fully inclusive price – £108.60.

National Computer Congress – New York – June 7-11, 1976. 10 nights at the de luxe Hilton Hotel at Rockefeller Centre. Fully inclusive price – £320.00.

Exhibition of Electrical Equipment – EIEE. Measurement and Control Exhibition – MESUCORA Paris. June 10-17 1976. Two nights at the de luxe Meridien Hotel. Fully inclusive price £86.50, extra nights as required.

Consumer Electronics Show and Video Expo – Chicago – June 13-16, 1976. 10 nights at the de luxe Palmer House Hotel. Fully inclusive price £340.00.

Western Electronic Show and Convention – WESCON – Los Angeles – September 14-17, 1976. 10 nights at the de luxe Downtown Hilton Hotel. Fully inclusive price – £399.00.

International Exhibition of Data Processing, Communication and Office Organisation – SICOB Paris, September 23 – October 10 1976. Two nights at the de luxe Meridien Hotel. Fully inclusive price £86.50, extra nights as required.

Hifi International Exhibition and Festival – Dusseldorf – September 24-29, 1976. 2 nights at the first class Quality Inn Hotel. – Ratingen (8 km from the Fair Ground). Fully inclusive price – £99.90.

International Trade Fair for Production in the Electronics Industry – ELECTRONICA – Munich, November 25-December 1, 1976. Two nights at the first class Hotel Der Konigshof. Fully inclusive price £118.00, extra nights as required.

Please send details of the tours indicated above.

NAME

COMPANY

ADDRESS

Telephone

Appointments

Advertisements accepted up to 12 noon Monday, April 5th for the May issue subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £6.50 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £1 per line, minimum three lines.
BOX NUMBERS: 45p extra. (Replies should be addressed to the Box Number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.)
PHONE: Owen Bailey on 01-261 8508 or 01-261 8423.
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

TEST AND LIAISON ENGINEERS

Ferranti in Edinburgh have a number of Ministry of Defence contracts involving the design and development of advanced avionic equipment for military aircraft in an international market.

We have vacancies for test and liaison engineers who will probably be qualified to HND level in electronic engineering with some years' experience in design, test or support of modern avionic equipment. A knowledge of digital and analogue techniques is essential.

Close liaison with design/development teams currently engaged on inertial navigation and display systems will be necessary and the work will entail factory acceptance testing, fault diagnosis and system commissioning on a variety of sophisticated equipment.

There will be opportunities for some of these engineers after a period of in-house training to be selected for technical liaison duties at locations in the U.K., Europe, Middle and Far East.

The Company offers an attractive employment package which includes 22 days holiday and membership of a life assurance and pension scheme. Incoming personnel will qualify for housing under the Scottish Special Housing Association scheme and realistic assistance will be given with relocation expenses where applicable.

Apply in writing giving details of age, experience and qualifications to:

THE STAFF APPOINTMENTS OFFICER
 FERRANTI LIMITED
 FERRY ROAD
 EDINBURGH EH52XS

(5123)

FERRANTI

YOUNG ELECTRONICS LTD.

We are a manufacturer of lighting control systems and signal detection equipment, and are looking for a

WIREMAN-TESTER

(male or female) for the construction, testing and servicing of the equipment at our works in N.W.1. Very varied work. Qualifications: ONC or C&G or ex-apprentice (electronics or mechanical) or similar desirable. A wide practical experience is essential involving both electronics and mechanical work. We are a small expanding company and will offer a good salary to the right person.

Please write for an application form to:—Young Electronics Ltd, 184 Royal College St, London NW1 9NN.

(5238)

LORD MAYOR TRELOAR COLLEGE

ELECTRONICS INSTRUCTOR

required for September, 1976, to take charge of full-time Radio, Television & Electronics Course and teach both theory and craft practical to parts 1 and 2 standard of the City & Guilds Mechanics 222 Course.


Qualifications: Radio, Television & Electronics (272) Technician Part III Certificate including Colour TV Endorsement and experience, or equivalent.

Salary: £4,000+ p.a. if fully qualified and experienced. Superannuation. Accommodation at reasonable rent.

Students are physically handicapped. Good record of results.

Further details and application form from the Headmaster, Lord Mayor Treloar College, Froyle, Alton, Hampshire GU34 4LA.

(5200)

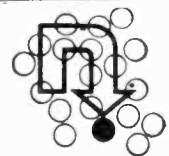


Opportunities in the ELECTRONICS FIELD

People with analogue or digital qualifications / experience seeking higher paid posts in TEST - SERVICE - DESIGN - SALES.

Phone Mike Gernat, Ref. W.W.

NEWMAN APPOINTMENTS
 360 Oxford Street, W.1.
 01-629 0501

(94)

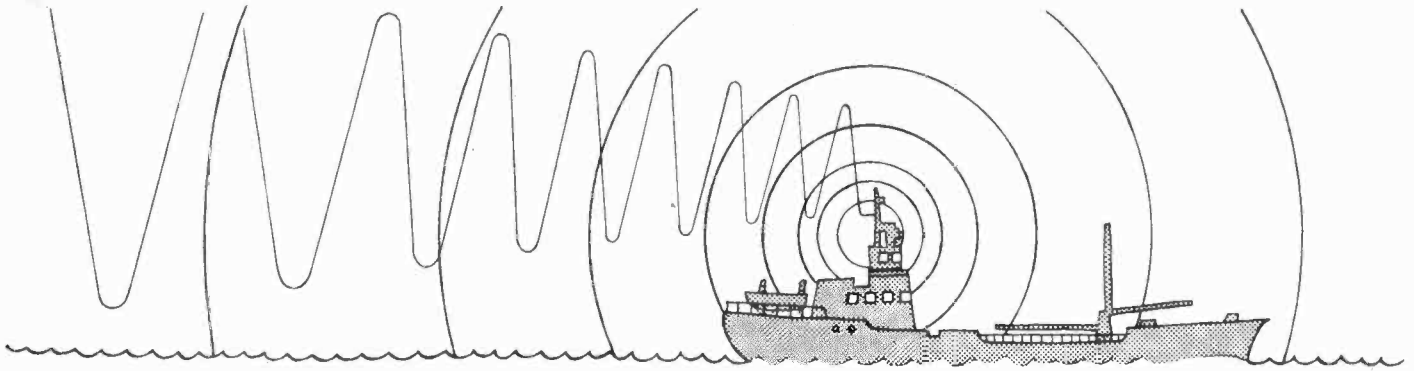

Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627

according to age. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.


Right now we have vacancies at some of our coastal radio stations, so if you're 19 or over, write to ETE Maritime Radio Services Division (R/B/1), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

93

mi

Careers in Professional Electronics

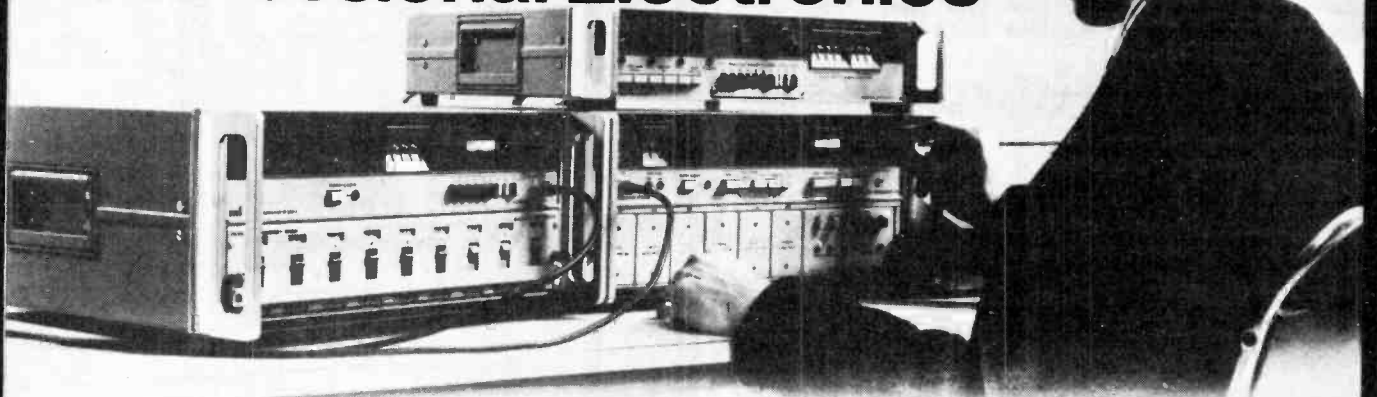

Your experience could open the door to a range of interesting and rewarding opportunities in the Design, Production or Service departments of a Company whose products complement the most advanced modern electronic techniques.

For more information apply in confidence to:— John Prodger,
MARCONI INSTRUMENTS LIMITED
 Longacres, St. Albans, Herts. Tel: St. Albans 59292

A GEC-Marconi Electronics Company

(5208)

Professionally frustrated? We can find you a new job.

You know you're good but your present employers are apparently ignorant of the fact. Enough to make you look for a new job. Put your name on the Lansdowne Appointments Register and make it easy on yourself. Hundreds of employers use our register to fill their key jobs. And remember the best jobs are not always advertised.

It costs nothing to take advantage of our help so you've nothing to lose and everything to gain. And our service is conducted in strictest confidence.

So make sure you're 'in the know' by phoning 01-579 6585 or writing to Stuart Tait, Lansdowne Appointments Register, Design House, The Mall, London W5 5LS.

Name _____

Address _____

WW 15/3

Lansdowne Appointments Register

(5257)

A leading US Manufacturer of TV Products requires

ELECTRONICS ENGINEERS

with extensive experience in digital techniques in one or more of the following areas:

- Synchronisers
- Time Base Correctors
- TV Related Software Development
- Data Reduction Systems
- Standards Conversion

These senior appointments would be based in the U.S.A., salary and benefits commensurate with experience. Initial interview in U.K.

Please send résumé to Box No. 5256.

SYSTEMS ENGINEER

Due to the rapid expansion of our Systems Group we have an excellent vacancy for a top grade Systems Engineer.


The post is for a person to design and commission minicomputer systems utilising a wide range of computer hardware. This is an excellent opportunity for the go-ahead engineer capable of solving system problems. A sound knowledge of minicomputer systems is essential and a working knowledge of software would be a distinct advantage.

For the right person this is a real opportunity for career advancement.

Qualifications: HNC/BSc in Electronics/Electrical Engineering.
A most competitive salary will be paid for the right person.

Salary: In the first instance contact Mrs. Jay Dee

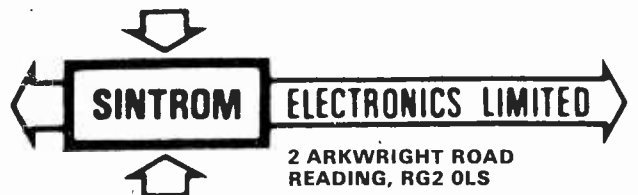In the first instance contact Mrs. Jay Dee



(5255)

Applications Engineers

Audio Systems

Tannoy, the internationally famous name in the field of industrial and high fidelity audio electronics, are engaged in a major programme of growth and development

To assist in this expansion the Company wish to recruit additional suitably experienced Applications Engineers. Application Engineers form part of the Engineering Division and are responsible for the interpretation of customer requirements in the audio communications field and the translation of these into engineering systems. There is a total involvement in the project from inception to completion and site visits may occasionally be necessary.

Applicants, aged over 25, should have had experience in the design of audio and communication systems and should be qualified at least to ONC standard in electronic engineering

The company is in a particularly interesting stage of development and career prospects, for those able to accept responsibility and work conscientiously, are excellent. Salary is negotiable at an attractive level and normal company benefits apply including four weeks' holiday.

For an application form, please write to or telephone Peter Fletcher, Personnel Manager, Tannoy Products Ltd., 348 Norwood Road, West Norwood, London, SE27. Tel. 01-670 1131

(5242)

TANNOY



North Midland Co-operative Society Ltd.

require

SENIOR AUDIO ENGINEER

A grand opportunity for a suitable, capable engineer to co-ordinate the activities of our Audio service department, which undertake the wide service aspect across the consumer spectrum.

The person appointed will be directly responsible to the Group Service Manager, and would not normally be expected to work on television or other equipment, but will be capable of dealing with customer inquiries and complaints.

The initial wage rate is £58 per week, and accommodation may be available on rental.

We are situated at the county border of Staffordshire, Cheshire and Derbyshire, which is a very attractive residential environment.

If you desire a change with opportunities, and wish to join an organisation with sales in excess of £34 million per year, apply in the first instance giving details of career to date by letter to the:

Personnel Officer
10 Newcastle Street
Burslem
Stoke-on-Trent
ST6 3QG


*Looking
for
a
new
job?*

Perhaps we can help!

We have regular contact with hundreds of electronics and electrical companies needing qualified electronics engineers and technicians and TV service engineers.

We can, therefore, help you to find an interesting and well paid job. All you need to do is to return the coupon below or give us a ring. Our service is confidential and costs you nothing.

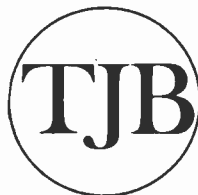TJB Technical Services Bureau,
3A South Bar,
Banbury, Oxfordshire.
Banbury (0295) 53529



Technical Services Bureau is a division of Technical & Executive Personnel Ltd and is solely concerned with job placement in the Electronics and Electrical Industries

Please note that this service is available only for engineers who are (or will be) available in the U.K. for interview.

Please send me an "Application for Registration" form

NAME

ADDRESS

.....

..... (90)

You have a vital role to play as a Test Engineer with Pye

Vital because many of our products are used in situations in which their efficient operation may make all the difference between life and death. Much of our VHF radio equipment is used widely by police, fire and ambulance services throughout the country and overseas too. And that's why you, as a Test Engineer with Pye in Cambridge, have an important part to play.

Pye Telecom are one of the largest companies within the Pye Group. We're involved in the development and manufacture of a wide range of fixed, mobile and portable radio communications equipment and can, therefore, provide exceptional scope to experienced and ambitious engineers.

As a Test Engineer, you'll be carrying out unit and systems testing and fault finding, utilising the most modern equipment and techniques in a highly sophisticated quality control operation.

We'd like you to have sound relevant test experience, preferably but not necessarily on communications equipment, and this experience might well have been gained in the Services. If you have an ONC or City & Guilds qualification, so much the better.

You can look forward to a good salary and excellent career opportunities, both within the Company and the Pye Group as a whole. Attractive additional benefits include contributory pension scheme, a good canteen, sports and social activities and assistance with relocation expenses where appropriate.

To find out more, telephone or write to Mrs. Audrey Darkin at Pye Telecommunications Ltd., Cambridge Works, Elizabeth Way, Cambridge CB4 1DW. Tel. Cambridge 58985; or Mrs. T. White, at Pye Telecommunications Ltd., Colne Valley Road, Haverhill, Suffolk. Tel. Haverhill 4422.



Pye Telecommunications Ltd

Newmarket Road, Cambridge, England CB5 8PD
Tel. Cambridge (0223) 61222 Telex: 81166 PYTELECOM CAMBGE

A member of the Pye of Cambridge Group

(5209)

OVERSEAS APPOINTMENTS

ELECTRONICS TECHNICIANS

Petty-Ray is one of the leading Companies in the field of oil exploration and due to our ever increasing workload require young single personnel, who are looking for varied and interesting career working overseas.

You should be educated to HNC / ONC in Electronics of C & G radio and TV Technician level, and on appointment you will be assigned to one of our field crews either in Africa or the Middle East for on the job training in the operation and maintenance of digital seismic recording equipment.

Candidates must be in possession of a current driving licence.

We offer a good starting salary which is tax free, food and accommodation will be provided and rest leaves are generous.

If you would like to have more information about these challenging positions why not write giving brief career details to -

**THE PERSONNEL OFFICER
PETTY-RAY LTD.
106 Coldharbour Lane
Hayes, Middlesex
UB3 3HL**

(5241)



— first in Sound and Vibration

require

ELECTRONIC TECHNICIANS

for interesting and varied work in the fields of sound and vibration measuring instrumentation. This involves fault-finding, practical mechanical and electronic repairs and calibration. Previous experience with audio frequency equipment and a sound knowledge of current analogue and digital techniques is essential. (Valves to CMOS). We are looking for experienced engineers with both adaptability and enthusiasm and an understanding of the need to maintain the highest possible standards at all times.

Write, stating age, experience and present salary, to: Mr. Alan Gibson,

B & K LABORATORIES LTD.

Cross Lances Road, Hounslow, Middx.

(5224)

UNIVERSITY OF LEICESTER Department of Chemistry

Applications are invited for a post of

EXPERIMENTAL OFFICER

in the field of electronics. Candidates should be graduates or have equivalent professional qualifications. The post concerns the maintenance of analytical instrumentation, design and development of electronic equipment and a knowledge of modern electronics including digital, data logging and R.F. circuitry. Salary on an incremental scale £2766 to £4602 a year. Applications should be forwarded to the head of the Department of Chemistry, The University, Leicester LE1 7RH, as soon as possible.

(5245)

MANAGEMENT TRAINEE C. £2,500

A young, technically orientated self-starter is required to train for Management in Fields, based initially with our instrument and Ancillaries Division at Croydon.

The successful candidate will be in the early to mid-twenties, with a basic engineering knowledge, probably gained in an indentured apprenticeship, and at least two years' experience in purchasing or production management in the engineering industry.

Prospects are excellent and the salary is negotiable in the region of £2,500.

Please apply for application form to -

**COMPANY PERSONNEL MANAGER
FIELD AIRCRAFT SERVICES**

HEATHROW AIRPORT — LONDON
HOUNSLOW, MIDDLESEX, TW6 3AE
TELEPHONE: 01-759 2141, ext. 56

5254

CCTV ENGINEER

A top London Advertising Agency with the most sophisticated closed circuit T.V. facilities and a thorough understanding of the importance of good engineering has a vacancy for a young engineer.

Applicants must have some experience in this field, and should be studying towards HNC. Day release is allowed for further study and a salary is offered in keeping with experience and qualifications.

Please write giving information of experience and qualifications, to:

**Neville Smith
Television Department
FOOTE, CONE &
BELDING LTD.
82 Baker Street
London, W1
Tel. 01-935 4426**

(5249)

The Polytechnic of North London

DEPARTMENT OF PHYSICS

Electronics or Physics?

A difficult choice — for a clear understanding of electronics you must know a great deal of basic physics; for experimental physics you need to be familiar with modern electronic devices. The Physics Department offers a sandwich course, with 2 industrial training periods totalling 15 months, in the CNAH Honours degree.

The Physics and Technology of Electronics

This course combines both subjects and can satisfy the academic requirements for corporate membership of both the Institute of Physics and the Institution of Electrical Engineers. Obtain this degree first — you will then be better able to make your final choice of profession.

MSc Course — The Physical Basis of Electronics

This course is designed for graduates in either physics or electrical engineering who have realised the need to study the fundamentals of electronics. Full-time, part-time and evening only courses are available.

Details of all courses from:

The Head of the Physics Dept. (Ref. WW1)

THE POLYTECHNIC OF NORTH LONDON

Holloway Road, London N7 8DB

(Tel. 01-607 6767, Ext. 305) (5201)



MALLA TECHNICAL STAFF

334 Euston Road
London NW1 3BG
01-387 1043

ELECTRONICS AND COMPUTER PERSONNEL, QUALIFIED AND EXPERIENCED ALL SPECIALITIES, ALL AREAS. (5243)

T.V. ENGINEERS FOR NEW ZEALAND

Due to the rapid development of colour T.V. and the introduction of a second channel, we are in need of experienced T.V. servicemen. Who are we? N.Z.'s largest T.V. service company with over 30 branches and a staff of approximately 350.

Single Men: 2 Year Contract — Return Fares Guaranteed.

Married Men: Subsidy provided to cover major part of air fares.

Interested? Then write now enclosing a recent photograph, details of past experience and any qualifications to the Technical Staff Supervisor, Tisco Ltd., Private Bag, Royal Oak, Auckland, NEW ZEALAND.

(5263)

ELECTRONIC TECHNICIANS. Required for fault finding diagnosis and testing of aircraft electronic equipment. Applicants should be qualified or studying H.N.C. or C.G. technicians or have considerable experience in circuit fault finding and operation of standard test instruments. Apply in writing to:— Canford Aircraft Equipment Limited, Stansted Airport, Stansted, Essex. (5274)

MARINE ELECTRONIC INSTALLATION REPAIR FIELD ENGINEER for work on Yachts UK and abroad. Must have experience radar communication. Auto pilots instruments, etc. Must live in or near London. Apply to: Telesonic Marine Limited, 243 Euston Road, London NW1. Telephone: 01-387 7467. (5244)



RHM MANAGEMENT SERVICES LIMITED

RHM Management Services Ltd., a company within the RHM Group, require a Telecommunications Engineer at Harlow to assist in the planning and implementation of their Tandem Switching Network, which will carry speech, data and facsimile traffic between many group locations.

The Engineer will be a member of a team responsible for many aspects of computing and telecommunications including data transmission, equipment development, computer system installation and fault diagnosis. This role will be primarily concerned with Strowger and Crossbar switching, signalling, wide-band transmission, PABX/PMBX/PAX systems, facsimile and telex, plus conducting traffic surveys and liaison with suppliers, Post Office, Group Management.

TELECOMMUNICATIONS ENGINEER

There will also be opportunities to gain experience in other areas such as computer peripherals, terminals and data transmission.

Experience in the primary areas together with possession of a City & Guilds Intermediate Certificate, or higher, in Telecommunications is essential. Salary negotiable.

If you would like to know more about this unique opportunity to join a really progressive outfit, please write or telephone for an application form to: **Mrs. M. E. Saunders, Personnel Manager, RHM Management Services Limited**, Joseph Rank House Northgate, The High Harlow, Essex CM20 1LX Tel. Harlow 26831 ext. 113 (5258)

DEVON AREA HEALTH AUTHORITY (PLYMOUTH HEALTH CARE) CORNWALL & ISLES OF SCILLY AREA HEALTH AUTHORITY

Medical Physics Department
Plymouth General Hospital, Freedom Fields

ELECTRONICS TECHNICIAN

required for further expansion of the electronics service. The person appointed will join a small team in a well-equipped laboratory. He will be responsible to a graduate electronics engineer for maintenance of a wide range of patient-oriented electronic equipment. Development of special-purpose systems is undertaken, and safety and purchase decisions are made on new equipment.

Minimum qualifications: ONC or HNC. Some travel in S. Devon and Cornwall necessitates a current driving licence. The appointment will be in either of the following grades depending on experience:

Medical Physics Technician III £2,931-£3,834
Medical Physics Technician IV £2,346-£3,267

Further details of the work may be obtained by telephoning Mr. L. R. Jenkin, Plymouth 68080, ext. 369. Application forms are available from Miss E. J. Coggins, Senior Administrative Assistant, North Friary House, Greenbank Terrace, Plymouth, PL4 8QQ.

(5260)

AGENTS WANTED

RADIO-TELEPHONE Service Engineer Wanted for workshops in S. London, must be reliable and experienced. Salary neg. 680 1010. (5141)

AGENTS required to sell quality electric soldering instruments and ancillary equipment to Industry. Commission only basis. Suit persons selling allied products who require additional income. Good potential. Box No. 5227.

APPOINTMENTS

ELECTROSONIC, S.E. LONDON

Microprocessor Applications Engineer

Salary not a limiting factor

Project Engineer £3,000-£3600

Test Engineer £2500-£3100

The Company has vacancies in its design, manufacturing and service division as outlined below. Electrosonic Ltd., is leader in the rapidly expanding fields of lighting control, audio and audio visual systems and offers a wide range of interesting work in an attractive environment with excellent conditions of employment.

Microprocessor Applications Engineer

A Programming/Development Engineer is required to assist in the development of a range of audio visual and lighting control products based on the Intel 4040 microprocessor. Preference will be given towards experience gained in the design of software for real time applications using microprocessors together with some experience and knowledge of current digital techniques. A well equipped laboratory is available including a development computer, high speed reader, teletype and VDU. Projects already in hand will involve the applicant in both hardware and software aspects of product design but it is anticipated that eventually the applicant will specialise in software and advise the Company in other areas of Computer application.

AUDIO PROJECT ENGINEER

An Engineer is required with experience of planning and detailing special projects. He will be required to handle projects from initial concept to on-site commissioning and should have the ability to liaise with customer sales and production departments. ONC with a minimum of three years' experience in an electronics company essential, preferably with an audio background. Willingness to travel and a current driver's licence essential. This is an important post and remuneration will reflect qualifications and experience.

TEST/SERVICE ENGINEERS

Vacancies exist in both these departments for Electronic Engineers with at least two years' continuous experience in Industry additional to Industrial Training periods. On the job training will be given in the company's products and opportunities for advancement are available. Service Engineers will be required to work both in the factory and on site and the holding of a current driving licence is desirable.

Applications should be made by telephone or in writing to:

Mr. R. D. Naisbitt, Personnel Director
Electrosonic Ltd., 815 Woolwich Road, Charlton, London, SE7 8LT.
Tel: 01-855 1101.

ARTICLES FOR SALE

QUARTZ CRYSTAL UNITS from

- 1.0-90.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 6271-A

WRITE FOR LEAFLET AT 1

McKNIGHT CRYSTAL Co. Ltd.

HARDLEY INDUSTRIAL ESTATE, MYTHE, SOUTHAMPTON SD4 6ZY

TEL. HYTHE 848961
STD CODE 0703

Quartz Crystal Units
ACCURATE RELIABLE

Private enquiries, send 10p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT,
NEW MALDEN, SURREY 01 942 0314 & 2988

VG Scientific

A division of one of Britain's most rapidly expanding Scientific Companies require top people to work in RESEARCH and DEVELOPMENT. Attractive salaries are offered for the following positions based at East Grinstead

**ELECTRONIC ENGINEERS
TEST ENGINEERS
PRINTED CIRCUIT
DRAUGHTSMAN**

We require several young people men and women to work with an active research and development team engaged in the design of surface physics instruments. The successful applicants would require to have a sound knowledge of fundamental principles and a physics appreciation. The work entails the design and development of equipment working over a wide range of voltage current and frequency using a large variety of circuitry.

Please write stating qualifications and experience to Mrs S Sutton, The Birches Industrial Estate, Imberhorne Lane, East Grinstead, Sussex.

(5201)

CA CAPITAL APPOINTMENTS LTD.

FIELD SERVICE ENGINEERS (ELECTRONICS)

If you're not earning over £3,500 p.a. plus a car — then you had better contact us!

(5203)

34 Percy Street, London, W.1
01-636 9658 (day) or
550 0836 (evening)

KING'S COLLEGE HOSPITAL MEDICAL SCHOOL (University of London) Denmark Hill, London SE5 8RX

ELECTRONICS TECHNICIAN

Required to join the Department of Biomedical Engineering, to assist research groups within the department with the design, development and maintenance of electronic signal processing equipment using analogue digital and radio-frequency techniques.

Applicants should have experience in the field and possess an HNC or equivalent in electronics as a minimum.

The post is tenable for one year in the first instance, but is renewable up to a maximum of three years. Initial salary will be within the range £2823-£4050 including London Allowance, commensurate with experience and qualifications.

Applications giving details of age, qualifications and experience, together with the names of two referees, should be sent to the Secretary, King's College Hospital Medical School, London SE5, as soon as possible.

(5273)

ARTICLES FOR SALE

THE SCIENTIFIC WIRE CO

Copper — Nickel — Chrome — Eureka — Litz — Manganin Wires
Enamelled — Silk — cotton — Tinned Coverings

- ★ No minimum charges or quantities
- ★ Trade and export enquiries welcome
- ★ S.A.E. brings List

P.O. BOX 30, LONDON E4 9BW

For Sale 2 off PDP 11/05 (16K); RK11 RK05 disc and bootstrap; LA 36 Dec Writer £9,900. Other peripherals possible.

CETEC Systems Limited, Tel. (0494) 446311 — P. Herke, Managing Director.

(5225)

ARTICLES FOR SALE



MIXED MINIATURE ELECTROLYTIC CAPACITORS

6V-63V

- 50 PACK 1.68 MFD £1.00
- 100 PACK 1.68 MFD £1.84
- 50 PACK 10-1000 MFD £1.52
- 100 PACK 10-1000 MFD £2.52

CASH WITH ORDER PLUS 25% VAT



M.C.L. (DEPT. C)
12 DAKINGTON AVE.
RAYNERS LANE
HARROW, MIDDXX.

(5259)

fibre optic suppliers

MARE'S TAIL 22" dia. 7.000 + Fibres £10.00. Glass fibres requires cover.
FIBROFLEX SIZE 1 440 Strand Flexible Glass Light Conduit, 1.14mm Active Dia. Black Sheath. 10m £3.00; 100m £21.00.
FIBROFLEX SIZE 4 1760 strand £1.50.
GROFROW 1610 Flexible 64 Strand Plastic Light Conduit. Active Dia. 1.5mm. O.D. 3.3mm £1.20 per M.; 10m £9.00.
PLASTIC OPTICAL MONOFIBRE Flexible Light Guide Dia. 10, 20, 40, 60 thou, PP10 100m £4.00, PP20 20.5mm 100m £8.00; FP40 10m £4.00; 100m £32.00, FP60 10m £8.00; 100m £65.00.
OPTIKIT 103 2m CHOPON 1610 + 3m each FP20, FP40, FP60 + Polishing Compound, ideal laboratory pack £5.50.
OPTIKIT 1.6 6 Convex Glass Lenses Dia. 7/14/21/26/47/51mm £3.00. (Lenses also available separately).
OPTIKITS RRS Five Retro Reflectors for Optical/beam systems. Dia. 22/36/44/83mm + 150mm Strip. £2.50.
ULTRASONIC TRANSDUCERS SE05B-40T/R Sensitive 40kHz Tx/Rx pair (Suitable for Doppler/Ramette Control) £3.50.
ULTRASONIC TRANSDUCERS SED48-25T/R 25 Hz Tx/Rx Pair. (Better Sensitivity, Lower Bandwidth than SE05B-40) £3.50.
CIRCULAR POLARISERS Reduce glare on all types of instrument. RED/AMBER or NEUTRAL 50 mm sq. 70p; 75 mm sq. £1.40; 150 mm sq. £4.50. Linear Polarizers also available.
OPTOELECTRONICS LIGHT SOURCES & DETECTORS
W54 2mm Red LED 20p, W5350 TORQ Red LED 20p.
IC209 Red (3mm) 20p, IC209-Y, IC209-G (amber, green) 30p.
MLED92 Infra Red Emitter 30p, MLED203 Photo-Thyristor £1.20.
MS777 High Sensitivity Photo-Darlington 25V 50p.
MRO 150 2mm High Speed Photo-Transistor (4-45) 40p 70p.
Please add 8% VAT to prices. S.A.E. please for sheet form/data.
FIBRE OPTIC SUPPLIERS (NW)
6 CHIPPENHAM MEWS, LONDON, W9 (5206)

IBM GOLFBALL COMPUTER INPUT/OUTPUT TYPEWRITERS

STANDARD EBCDIC CODING
Will accept normal or sprocketed paper. Supplied in working order with data sheets, circuit diagram and application notes. Each machine serviced and tested.

£100 + 8% VAT

- As above but modified to take office range of Golf Balls £110 + 8% VAT
- 100 c.f.m. 50/60 c/s £4 (40p)
- PAPST FANS Type 7576, new, 6" dia x 2 3/16 deep £5 (45p)
- LIGHT DIMMERS 250w £2.70 (16p)
- BC107/8/9, BC147/8/9, BC157/8/9 all 9p ea (11p)
- ELECTROLYTICS
10,000µ 63v £1 (28p), 280µ 100v 80p (25p), 2240µ 100, 75p (25p), 1000µ 63v £1 (25p), 4500µ 35v 60p (15p), 2000µ 50v 35p (11p), 4000µ 70v 50p (20p), 4700µ 63v 80p (15p), 2500µ 60v 50p (12p).
- EX-COMPUTER PC PANELS, 2 x 4" 50 boards for £2.40 (62p)
- OPCOA SCA7 7mm 7-seg led display £1 (12p)
- QH bulbs 12v 55µ 60p (10p)
- 250 mixed resistors 60p (18p)
- 250 mixed capacitors 60p (18p)
- Si recs 60A 100piv 4 for £1 (15p)
- SN3055 equiv 4 for £1 (15p)
- EXTRUDED HEAT SINK for 2 x T03 50p (15p)
- SMALL ELECTROLYTICS 50p (15p)
- 2.2µ 10v 10µ 35v, 50µ 40v, 100µ 40v, 100µ 6v 150µ 10v, 64µ 10v, 300µ 10v 200µ 10v, 12 for 45p (12p)
- PIHER PRESETS 100mW
220 470 1k, 4k7, 10k, 47k, 100k, 220k, 12 for 50p (12p)
- 6v 0.5A Transformer 75p (18p)
- ALMA REED RELAY CPRI/A 18-30v 50p (10p)
- REED RELAYS 6v coil h/d contacts 5 for £1 (15p)
- REED INSERTS h/d contacts 10 for £1 (12p)
- WATER-COOLED HEATSINKS ex eqpt £1.20 (40p)
- CHROMED HANDLES
5" mtg centres per pair £1 (20p)
8" mtg centres per pair £1.50 (25p)

P&P shown in brackets

ADD 25% VAT to TOTAL
8% VAT on PSUs, FANS, DIMMERS, ROARDS

KEYTRONICS

Shop open Monday-Saturday, 9-2
332 LEY STREET, ILFORD, ESSEX
01-553 1863 till 2 p.m.
01-478 8499 after 2 p.m. (5220)

ARTICLES FOR SALE


Electrotime

THE TIME HAS ARRIVED FOR YOU TO JOIN THE DIGITAL REVOLUTION

INTRODUCING A NEW RANGE OF QUARTZ CRYSTAL DIGITAL ELECTRONIC WATCHES

CONTINUOUS LIQUID CRYSTAL DISPLAY MODEL TLC 4

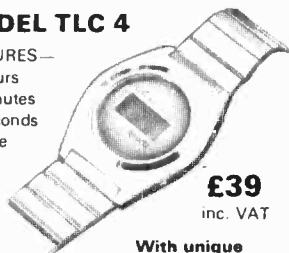- FEATURES—
- ★ Hours
 - ★ Minutes
 - ★ Seconds
 - ★ Date



£39
inc. VAT

With unique
Backlight feature
for Night Reading

THE BLACK WATCH



£17.99
inc. VAT

LED DISPLAY MODEL TLE3

Jet Black Stainless Steel Bracelet
(not plastic)

- FEATURES —
- ★ Hours
 - ★ Minutes
 - ★ Seconds

ALL MODELS EXCEPT
THE BLACK WATCH
WITH GOLD PLATED
OR RHODIUM
BRACELET

LED MODEL TLE 5



£34.95
inc. VAT

- FEATURES—
- ★ Hours
 - ★ Minutes
 - ★ Seconds
 - ★ Date
 - ★ Alpha Day

ALL WATCHES FEATURE—

- ★ Solid State — No moving parts
- ★ Quartz Crystal Controlled, accurate to 5 secs. per month
- ★ Attractive Presentation Gift Box

ADD TO THE SOPHISTICATION OF YOUR LIFE WITH THIS UNIQUE DIGITAL ELECTRONIC CLOCK

FEATURES —

- ★ Large 4-digit Easy Read Display
- ★ Variable Display Intensity
- ★ AM/PM Indicator
- ★ 24-hour Alarm
- ★ 5-minute Repeating Snooze Alarm
- ★ Power Interrupt Indication
- ★ Tilt Operation for Alarm Cancel
- ★ Pulsing Seconds Indicator
- ★ Attractive White Case




Complete
fully tested
cased clock

£14.50
inc. VAT



GENERAL CALCULATOR MODEL 1437

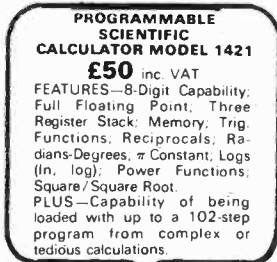- FEATURES—
- 8-Digit Capability
 - Full Floating Point
 - Basic Functions (+, -, X, ÷, %)
 - Automatic Power-on
 - Clear
 - Leading Zero Suppression
- £13.80**
inc. VAT



PROGRAMMABLE SCIENTIFIC CALCULATOR MODEL 1421

- £50** inc. VAT
- FEATURES—8-Digit Capability, Full Floating Point, Three Register Stack, Memory, Trig Functions, Reciprocals, Radians-Degrees, π Constant, Logs (ln, log), Power Functions, Square/Square Root.
- PLUS—Capability of being loaded with up to a 102-step program from complex or tedious calculations.



*Money back if not completely satisfied
One-year guarantee with all models*

**ELECTROTIME, 111 Storforth Lane Trading Estate
Chesterfield, Derbyshire - Tel: 35804**

Please supply

I enclose cheque/postal order/money order

Name

Address

and NOW

from ONE source

SEEN & SEEN

If you are an Engineer or Buyer in any of the following, write for our Catalogues

Manufacturing, Public Authorities, Laboratories, Universities, Contracting, Maintenance.

SERVICE, you can obtain many other Technical Products including **Electrical, Mechanical and Tools** in addition to the **Electronic** components that we have been distributing to Industry for over 30 years.

Large duplicate stocks are kept in **LONDON** and **SCOTLAND** to give you quick service.



CABLES & COMPONENTS LTD

Park Avenue, London NW10 7XN

SEMICONDUCTOR CIRCUIT ELEMENTS

Towers, T. D. Price: £6.00

ELECTRONIC CIRCUIT DESIGN HANDBOOK by EEE Magazine PRICE **£5.10**

RADIO VALVE & SEMICONDUCTOR DATA by A. M. Ball PRICE **£2.50**

ELECTRONIC CIRCUITS & SYSTEMS by R. King PRICE **£5.45**

HOW TO BUILD ELECTRONIC KITS by V. Capel PRICE **£1.95**

ELECTRONIC TEST EQUIPMENT by H. T. Kitchen PRICE **£4.90**

HI-FI LOUDSPEAKERS & ENCLOSURES by A. B. Cohen PRICE **£6.30**

DESIGNING CIRCUITS WITH IC OPERATIONAL AMPLIFIERS by R. G. Seippel PRICE **£3.45**

VIDEOTAPE RECORDING by J. F. Robinson PRICE **£6.25**

FOUNDATION OF WIRELESS & ELECTRONICS by M. G. Scroggie PRICE **£4.25**

HI-FI YEAR BOOK 1976 by K. Ellmore PRICE **£2.60**

* PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO
SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS

19-21 PRAED STREET
LONDON W2 1NP

Phone 723 4185
Closed Sat. 1 p.m.

Economise on Semiconductors

All prices include VAT — by return service

- * Lower price CMOS
- * Lower price 741C

- * Low price DIL sockets
- * Low price NE555

	TTL Mixed			prices		CMOS Mixed prices			
	1+	10+	25+	1+	25+	1+	25+	+	
723C + data 14 pin DIL	70	68	64	7400	13	12	4000	17	16
741C + data 8 pin DIL	23	22	22	7402	13	12	4001	16	15
748C + data 8 pin DIL	36	34	32	7403	13	12	4002	16	15
LM308 + data 8 pin DIL	110	99	95	7404	15	13	4006	104	95
NE555 + data 8 pin DIL	44	42	40	7405	15	13	4007	17	16
CA3046 14 pin OIL	84	81	77	7410	13	12	4008	95	88
TDA1405 5V 650mA	80	76	74	7413	28	24	4009	50	46
TDA1412 12V 500mA	80	76	74	7420	13	12	4010	50	46
TDA1415 15V 450mA	75	72	70	7430	13	12	4011	16	15
BC107, 108, 109, 109C	11	10.5	10	7442	60	54	4012	16	15
BC182, 184	12	11.5	11	7447	85	80	4013	45	40
BC212, 214	13	12.5	12	7473	28	24	4014	90	82
H-P 0.2" LED red + clip	19	18	17	7474	30	26	4015	85	80
H-P 1/4" LED red	18	17	16	7476	30	26	4016	48	44
DIL low profile sockets	8 pin 11	10	9	7486	28	24	4017	85	80
	14 pin 12	11	10	7490	45	38	4020	99	93
	16 pin 13	12	11	7492	55	50	4023	16	15
H-P 5082-7740 cc digit	180			7493	45	38	4024	68	62
MT242CS Transformer	150			74121	33	28	4025	16	15
							4027	48	44
							4028	78	71
							4030	48	44
							4040	93	85
							4046	117	107
							4049	48	44
							4050	48	44
							4068	17	16
							4071	16	15
							4078	17	16
							4081	16	15
							4507	50	45
							4511	136	126
							4518	110	101
							4520	112	103
							4527	138	126

BC177	21	2N3702	12	1N4001	4
BC179	22	2N3708	10	1N4002	4.5
BF244B	30	2N3055	49	1N4003	5
BFY51	15	1N914	4	1N4004	6
BZ788C				1N4006	7
3V3-15	11			1N4148	4

AY-5-1224 16 pin DIL clock IC + data + circuit	4.00
Clock IC + 4 H-P D.3" red digits	11.00
Clock IC + 4 digits + transformer + transistors	13.00
TBA81DAS 7W Audio Amp + circuit + data	1.15
TCA940 10W Audio Amp + circuits + data	2.00
TAD100 radio IC + IF filter + circuit + data	1.70
Carbon Film high stab. resistor. 1% W 5% E12 values 10ohm - 2M2. 1.1p ea. 10 for 10p. 100 90p. Same value.	

All prices include VAT. P&P (UK) 12p. Overseas at cost. SAE enquiries. All goods new. Full spec. devices from Motorola, Mullard, TI, SGS, etc. Schools, colleges, etc. supplied. By return service.

SILICON SEMICONDUCTOR SERVICES
41 Dunstable Road, Caddington, Luton LU1 4AL

(40)

BRIDGE ELECTRONICS COMPONENTS

AC126	13	BF180	25	2N604	18
AC127	13	BF181	25	2N2905	18
AC128	11	BF200	25	2N2906	18
AC151	14	BF194	09	2N2907	18
AC152	15	BF195	09	2N2926	20
AC153	17	BF198	12	2N3633	20
AC116	14	BF199	13	2N3054	18
AC187K	27	BF257	25	2N3055	18
AC188K	27	BF258	24	2N3933	18
AD162	25	BF259	24	2N3441	18
AD162	25	BF259	24	2N3442	18
BA102	10	BF330	22	2N3638	18
BA113	10	BF334	22	2N358A	18
BA116	14	BF305	27	2N3702	18
BC107	10	BF368	20	2N3703	18
BC108	10	BF375	19	2N3704	18
BC109	10	BF375	19	2N3705	18
BC107	10	BF375	19	2N3706	18
BC148	09	BY122	11	2N3708	18
BC149	09	BY122	11	2N3711	1.25
BC167	10	0A47	06	2N3772	1.35
BC168	10	0A90	04	2N3773	2.00
BC169	10	0A91	04	2N3904	11
BC182	10	0A200	05	2N3906	12
BC183	10	0A202	06	2N3904	12
BC184	10	0A201	04	2N5296	15
BC212	095	1N4004	05	2N5298	35
BC213	09	1N4007	05	2N3794	21
BC214	095	1N4148	03	2N3819	30
BC137	08	1S920	08	2N3820	55
BC138	08	1S921	08	2N4036	55
BC239	08	1S923	05	2N4037	10
BC307	09	2N697	15	2N4286	20
BC308	09	2N698	14	2N4921	60
BC309	09	2N706	13	2N5086	25
BC327	12	1N708	10	2N4293	25
BC315	12	2N616	23	2N5447	12
BC370	13	2N1305	25	2N5449	12
BC377	12	2N1307	25	2N5457	10
BC377	12	2N1308	25	2N5458	27
BC131	30	2N1613	15	2N6027	30
BC132	30	2N1711	13	30361	45
BC135	25	2N2218	25	40382	60
BC136	25	2N2218A	18	40408	62
BC137	25	2N2219	175	40409	64
BC138	28	2N2219A	18	40410	64
BC139	29	2N2221	275	40682	55
BC140	25	2N2221A	13	40636	100
BOY56	100	2N2222	175	40673	60
BC133	20	2N2546	30		

(5222)

FULLY GUARANTEED


Mail order only VAT extra p&p 20p
B. S. Electronics
PO Box No. 10 Fishponds Bristol BS16 2LX

INSCO ELECTRONICS

POWER SUPPLY MANUFACTURER

Whitehill Industrial Estate, Glenrothes, Fife
Other information Telephone (0592) 771959

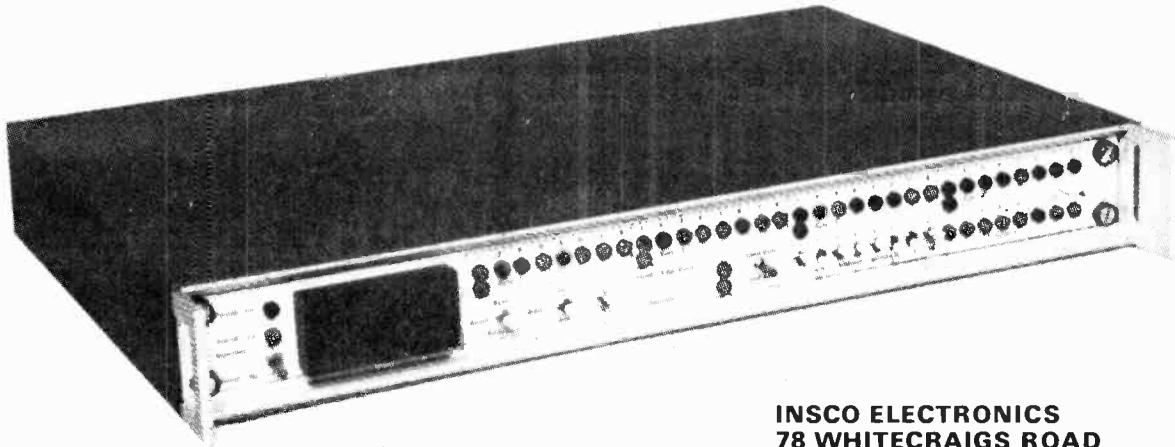Scolab series to provide Designers with complete Lab capability in one instrument.
0-30V 1A + Balance. Tracking
0-30V — 1A Sim/Triangular/Square £128.00
Wave. Form Generator Adjustable between 1 Hz and 1mHz 0-10V
Same as above, but inclusive 16-BIT. 10mHz Digital Word Generator. (TTL) £166.00.



INSCO ELECTRONICS
78 WHITECRAIGS ROAD
WHITEHILL INDUSTRIAL ESTATE
GLENROTHES, FIFE

(5204)

DIRECT COMMUNICATIONS

Division of Direct Electronics Ltd. INTERCOMMS & TELEPHONES

- Simple 2-way wall/desk with 100ft cable. 6v batt. or power supply. £16 (£1 p&p)
 - Similar but 2- to 7-way instrument only. Installation diagram. 18.50 each (50p)
 - Superior 2- to 6-way Siemens & Halske. Wall-desk conversion kit, term. block and cord per instrument £10 (50p)
 - AUTOMATIC INSTRUMENTS Strouger compatible or PX working. New/refurbished/2nd hand 232 332 706 746 722 (Trimfone), etc. Special and foreign types
 - ULTRA MODERN TYPES "Gondola" International Touch-button dial; Charleston (candlestick), etc. from £32.85
 - Plain & Key Phones for home and export
 - Jacks, Plugs, Cords, Term. Blocks, Cables (up to 25-way and 50 pair) etc
 - Entrance Phones and Electric Latches, with or without intercomm facility
 - Telephone Amplifier (1-way), £6.95 (35p), hands-free tele amp. (two-way conversation), £9.50 (50p)
 - TRANSISTORISED UNITS Simple 2-way batt intercomm. £7.75 (50p); Batt Baby Alarm £5.25 (50p); Intercomm with roving master £9.50 (50p)
 - Wireless Intercomm (just plug into mains), 2-way £20 (£1), batt. op. 3-way (master + 2 subs) £23.95 (£1); 4-way (master + 3 subs) £28.50 (£1)
 - Mains adaptor 6v/7.5v/9v dc £3.75 (35p)
- Add VAT ● = 8% ★ = 25% on post paid price
- TRADE ENQUIRIES WELCOMED
MANY SURPLUS ELECTRONIC BARGAINS FROM OLD STOCK STILL LEFT — COME AND DO A DEAL!

34 LISLE STREET, LONDON WC2H 7BD
Tel: 01-437 2524

(5216)

SONAR IND UNITS. Modern style unit with 5in sq. flat face electrostatic tube with dual beam and blue/yell phosfor, module construction with approx 40 min & sub min valves as int eht unit osc type giving 2.7Kv reqs ext HT supplies. CRT as two separate deflection & gun systems normally gives slow speed scan from bottom to top of crt. Ex equipment with circ £13. Trimmers 3/10pf ceramic 10x9mm 5 for 50p. Feedthrough conds Erie type CDF100 1000pf 500v solder in type 20 for £1. Erie type 1214 Filtercons 1750pf 250v solder in type good to 10Ghz 10 for £1. Horn speaker unit for M/cycle 3 ohm size 5x3in. with mt brk £2.50. Recording paper heart sensitive sprocket feed drive centres approx 9 3/4in. £1.30 per roll. Remote 6 chan TX Rc crystal selector with holders for Hc6/u crystals also 6x BC108, 6xTrim 6x Coils etc. £1.60. Handsets with low imp earpiece & 4K imp mike have small push button at rear of earpiece with ext cable £1.50. Crystal filters all 10.7Mc/s c.f. size 38x16x18mm 30Kc b.p. £1.30. 15Kc £1.60. 12Kc £1.60. Integrated Circs three types CA3014 w.b. amp & disc. ULN211A w.b. amp & product det. TAA300 a.f. amp 1 watt into 8 ohms one of ea with data shts £1.50. Dish Aes 18in. dia. 4 1/2in. deep at centre in 16g dural plain finish £3.80. Pwr Transis Lucas type DT6106 sil npl Vc 500v Ic 10a £3.50. Filters TPL high pass fits into down lead rear of set standard coax fittings 4 for £1.30. Coax leads BNC to BNC 1.5mts 50 ohm £2.30. Min rot swt 2p 5w 3/4 shaft 2 for 60p. Atten units STC 0 to .9Db in .1 steps 75 ohm cal at DC & 50Mc/s £5. Sig Gens CT478 mains 1.3 to 4.2KMc/s in two bands int mod etc ex equip £35. Decca marine scanner X band on base approx size 5ft x 4ft 6in with qty of w.g. x equip £45 plus carr. All prices inc. VAT and post. all items are new, unused, unless stated ex. equip. A. H. SUPPLIES, 122 Handsworth Rd., Sheffield S9 4AE. Tel. 0742-444278. (5265)

TIDY PACK with 6 different sizes of heat shrink sleeving each 1M in length 100 self-locking cable ties and a roll of black PVC tape. All for only £2 inc. VAT & PP. B.D.O. Products Ltd., Retail Division, 13A Heath Road, St Albans, Herts. (5090)

WE INVITE ENQUIRIES from anywhere in the World. We have in stock several million carbon resistors with 1/4, 1/2, and 1 watt. 1/2 million wire wound resistors 5 and 10 watt — 1 million capacitors — 1 million electrolytic condensers — 1/2 million transistors and diodes, thousands of potentiometers, and hosts of other components. Write, phone or call at our warehouse — Broadfields & Mayco Disposals Ltd., 21 Lodge Lane, N. Finchley, London, N.12. 01-445 0749, 445 2713. (5097)

★ MINICOMPUTERS ★ PERIPHERALS ★ INSTRUMENTATION

For fastest, best CASH offer, phone

COMPUTER APPRECIATION
Godstone (088 384) 3106

CRYSTALS

Fast delivery of prototype and production quantities to your specification. EG

100 KHz	0.005%	HC13/0	£2.50 each	£1,900 per 1,000
1 MHz	0.005%	HC5/U	£2.50 each	£1,600 per 1,000
2,097,152 MHz	0.0025%	HC5/U	£3.05 each	£1,500 per 1,000
3,276,800 MHz	0.0025%	HC5/U	£2.70 each	£1,500 per 1,000
10 MHz	0.002%	HC18/U	£2.00 each	£1,100 per 1,000

Also, Stattek LF crystals in TO-5 package, many stock frequencies in the range 10-240 KHz, e.g. 10, 12.8, 16, 38.4, 32, 768 & 100 KHz, prices from £2.55 each £1,400 per 1,000. Please send for further details. **INTERFACE QUARTZ DEVICES LTD.,** 29 Market Street, Grewkerne, Somerset. Telephone: (046031) 2578 Telex: 46283

MICROPHONE PREAMPLIFIER

Small pc board (70x90mm) accepting two 30-600 ohm microphones (balanced inputs) and feeding loads down to 5 Kohm. Board plugs into 12-way gold edge connector (supplied) and has presets for gain, 1.5db noise figure. Supply + 24V. Board built and tested. £37. Kit £29.

STEREO DISC AMP

FOR BROADCASTING AND DISC MONITORING. Magnetic cartridge to balanced lines with HF and LF filtering. Excellent distortion and overload performance. MEETS IBA SPECIFICATION. £105.

10-OUTLET DISTRIBUTION AMP

One balanced input — 10 isolated balanced outputs. GENERAL STUDIO WORK ★ FEEDING MULTIPLE SLAVE PA AMPLIFIERS ★ DRIVING FOLDBACK HEADPHONES. Meets IBA signal path specification. Complete and boxed unit £100. Set of parts excluding case and all XLR connectors £62.

PEAK PROGRAM METERS TO BS4297

also 200KHz version for high speed copying. Drive circuit, 35 x 80mm for 1mA L.H. zero meter to BBC ED1499. Gold 8-way edge con. supplied. Built and aligned £19.00. Complete kit £13. ERNEST TURNER PPM meters, scalings 1/7 OR-22/+4 Types 642; 71 x 56mm £14; 643; 102 x 79mm £16.70; twin movement, scale 86 x 54mm £42.00.

STABILIZER

FOR HOWL REDUCTION, BALANCED AND UNBALANCED VERSIONS BOXED OR RACK MOUNTING

PUBLIC ADDRESS : SOUND REINFORCEMENT



+ 5Hz Fixed Shift Circuit Boards for WW July 1973 article.

Small enough to be built inside the cabinets of many amplifiers. Complete kit and board £24 including PSU & designer. DESIGNER Board built and aligned £31 mains transformer approved. APPROVED SPECTRUM SHIFTER. Variable shifts 0.1 — 1000Hz for weird special effects on speech or music.

SURREY ELECTRONICS

The Forge, Luck Green, Cranleigh Surrey GU6 7BG (STD 04663) 5997. CASH WITH ORDER less 5%. UK POST FREE ADD VAT at 8%

ARTICLES FOR SALE

PRECISION POLYCARBONATE CAPACITORS

All High Stability - Extremely Low Leakage

Table with columns: RANGE, VALL, DIMENSIONS, PRICE, 63V Range, 1%, 2%, 5%

*TANTALUM BEAD CAPACITORS - Values available...

TRANSISTORS & IC's

Table listing various transistors and ICs with part numbers and prices.

POPULAR DIODES - IN914 6p, N for 45p, 18 for 90p...

LOW PRICE ZENER DIODES - 400MW Tol ±5% at 5mA...

MARCO TRADING (Dept. D1) The Old School, Edstaston, Nr. Wem Shropshire...

FREELANCE TECHNICAL AUTHOR and design engineer seeks commissions for handbook writing...

"COLLECTORS" ITEM: Bundles of "Wireless World" etc. going back to 1929...

COMPUTER SYSTEM PDP11-20 with PC11 high speed reader and punch and ASR33 teletype...

COMPONENT BARGAINS. Full spec. 741 20p, 555 37p, 7447 decoders 58p...

TELERADIO HI FI OFFER L. LINSLEY HOOD HIGH QUALITY AMPLIFIERS AND TEST EQUIPMENT

FM Tuner, Hi Q Amp 75 watt, Millivoltmeter

OSCILLOSCOPE. Dual Trace type CI-16 D.C. to 5 MHz.

V.H.F. A.M. radio installation consisting of the following G.E.C. equipment...

LOUDSPEAKER UNITS - UK's lowest prices for KEF, Celestion, Peerless, etc.

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram.

C.R.T. REGUNNING PLANT. New and secondhand reconditioned training, demonstration, colour or B/W.

16MM B & H 631 Sound projectors c/w speaker and transformers £135.

500 DUAL STANDARD COLOUR TV's. In stock from £30. Contact: S.H.C. Television.

LINSLEY-HOOD 75 watt amplifier spares by return. Sescoseni BDY56 £1.75...

FOR SOUND SENSE BUDGET KITS MIX WITH PARTRIDGE ELECTRONICS OR CUSTOM BUILT MANUFACTURERS OF AUDIO MIXERS, BIG AND SMALL, FOR ALL PURPOSES

FERRANTI J4 GYRO'S (Four) cased. 55 m/m x 30 m/m rotor.

DISCO & LIGHTING by Citronic, FAL ESE, PULSAR, OPTIKENETICS, EAGLE, etc.

TF144G, 85 KHz to 25 MHz Signal Generator. Offers - 6 Ashtree Close.

18 OLD COPIES OF WIRELESS WORLD. 1920 to 1938. £7.50.

RANK STUDIO FLUTTER METER type 1740 - £175. Heathkit laboratory oscilloscope model 10-18U - £25.

EVERSHED & VIGNOLES MURDAY twin pen chart recorder complete with 2 x 6in paper rolls.

AVO TRANSISTOR ANALYSER CT446. Complete with battery pack and service manual.

IBM GOLFBALL TYPEWRITER, computer terminal in excellent condition with TTL interface to transmit and receive 7 bit parallel A.S.C. code.

STELLAVOX SP7 portable tape recorder. 4.8 - 76 CMS/SEC, variable head and amplifier configuration by plug in modules.

AUDIX MXT200 MIXER. 10 MIC and 2 Line inputs, 2 output Groups, monitor. £350.

DISCO UNIT, consisting of two. KF speakers, output 50w, two turntables, one Garrard the other BSR plus D.J. Disco amplifier with microphone and headphones.

COLOUR UHF and TV SPARES. Lists available on request "Wireless World" TV tuner project, by D. C. Read.

Colour UHF and TV Spares. Lists available on request "Wireless World" TV tuner project, by D. C. Read.

Colour UHF and TV Spares. Lists available on request "Wireless World" TV tuner project, by D. C. Read.

Colour UHF and TV Spares. Lists available on request "Wireless World" TV tuner project, by D. C. Read.

BURGLAR AND FIRE Alarms. extinguishers, emergency lighting. Comprehensive range of DIY and professional equipment.

POWER SUPPLIES. 12vDC lamp smoothed supply £3.00 0-17vDC 1Amp variable supply, regulated, filtered. £8.50.

ARTICLES WANTED

WANTED!

all types of scrap and **REDUNDANT ELECTRONIC & COMPUTER MATERIALS** with precious metal content

TRANSISTORS & PRINTED CIRCUIT BOARDS TO COMPLETE COMPUTERS

The COMMERCIAL SMELTING & REFINING Co. Ltd.
171 FARRINGDON ROAD
LONDON EC1R 3AL
Tel. 01-837 1475.
Cables: COMSMELT, ECI
Works: FLECKNEY, nr. LEICESTER (5116)

WANTED, all types of communication receivers and test equipment. Details to R. T. & I. Electronics Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (63)

B-D ELECTRONICS offer prompt settlement for your surplus components. Our main field of interest is consumer electronics. Please telephone our Miss Hughes, Sandy (0767) 81616. (22)

SURPLUS COMPONENTS, Equipment and Computer panels wanted for cash. Ring Southampton 772501. (16)

WANTED NEW 705A VALVES. Details to P. Norgate; GV Planer Ltd., Sunbury-on-Thames 86262.

WANTED — ITT radio telephones type M5, AM7 and SF1. Good prices paid, any condition considered. Please telephone Rowhams (042 123) 4285. (5277)

ARTICLES FOR SALE

VACUUM is our speciality, new and secondhand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from E40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. (24)

60 KHz MSF RUGBY RECEIVERS. BCD TIME-OF-DAY OUTPUT. High performance, phase locked loop radio receiver. 5V operation with LED indication. Kit complete £9.50; assembled and tested unit £11.12 (prices include postage and V.A.T.) Also available low power receiver with signal and audio outputs. Send for details Toolex, Sherborne (4359) Dorset. (21)

MULLARD LP1400 high performance stereo decoder modules. Limited quantity to clear, only £6 including p & p. Mr Cook, 39 Barrett Road, London, E.17. Mail order only.

DISCO CONSOLE consisting of two 100 watt DJ Power Amplifiers with SDL mixer Mk II. 2 Garrard SP25 MKIII Turntables with Shure. Magnetic cartridges housed in compact mobile unit. 4 speaker units; 2 containing four 12" 50 watt Goodman speakers. 2 containing 18" EMI speakers. 100 watt Pluto light projector, microphone (including stand and boom). Speaker leads, Bank lights. All perfect and ready for use. £800. 01-805 3898.

TELEVISION double beam oscilloscope model D56. Delayed sweep. Little used manual £180. Spec. available. Parmeko transformer 7500V — 0 0 7500 20mA, unused, £10. — Erith 30556. (5267)

WANTED

black and white, dual standard televisions. Preferably Thorn 1400's or similar sets. In large or small quantities. Collection arranged. Reply to Box No 5239 5239

5239

WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.

SPOT CASH
CHILTMead LTD.
7, 9, 11 Arthur Road
Reading, Berks.
Tel. 582 605

REQUIRED from Ministry of Defence and other sources Plessey models P.T.R. 371 also 691, 692 and 693. Please post fullest details to John F. Learney, 16 Pine Walk, Carshalton Beeches, Surrey. (5226)

WANTED. FLUKE 8000A, Advance DMM3 or similar digital volt meter. Also X-Y Recorder any make or condition considered. Tel: Brighton 684286. (5250)

ARTICLES FOR SALE

SOWTER TRANSFORMERS

FOR SOUND RECORDING AND REPRODUCING EQUIPMENT
We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large of small quantities. List on quote.
A recent release
SOWTER TYPE 3078 MULTITAP MICROPHONE TRANSFORMER
Primary windings for 100 ohm, 250 ohm and 600 ohm with Secondary loadings from 2k ohm to 10 k ohm. Frequency response plus minus 1dB 25 Hz to 25 kHz. Constructed in well finished metal case. 35mm diameter by 22mm high, with colour coded end leads, low distortion DELTA I signal quantities. EX-STOCK. HIGHLY COMPETITIVE PRICE. FULL DETAILS ON REQUEST.

E. A. SOWTER LTD.
Transformer Manufacturers and Designers
7 Dedham Place, Fore Street
Ipswich IP4 1JP. Tel. 0473 52794 (5215)

ENAMELLED COPPER WIRE

S.W.G.	1 lb reel	1/2 lb reel.
10 to 19	2 40	1 35
20 to 29	2 45	1 40
30 to 34	2 60	1 50
35 to 40	2 85	1 60

All the above prices are inclusive of postage and packing in UK

COPPER SUPPLIES
102 Parrswood Road, Withington,
Manchester 20
Telephone 061-445 8753

EURO CIRCUITS

Printed Circuit Boards — Master layouts — Photography — Legend printing — Roller tinning — Gold plating — Flexible films — Conventional fibre glass — No order too large or too small — Fast turnaround on prototypes. All or part service available NOW

EURO CIRCUITS TD.
Highfield House
West Kingsdown
Nr. Sevenoaks, Kent. WK2344

SAVE IT! BARGAIN 500 WATT DIMMER SWITCH

(Not suitable for fluorescent lights)
Basic Module with 1" Knob £2 00
Complete on MK switch plate £2 50
Large 2" knob (BULGIN) 25p extra.
P&P 25p
Please add 8% VAT to all orders inc P&P
FRASER-MANNING LTD.
40 TUDDENHAM ROAD, IPSWICH IP4 2SL (35)

CAPACITY AVAILABLE

CAPACITY AVAILABLE

General Sheet Metal Work including Fabrication of Chassis Panels, Boxes and Guards. Large and Small Runs at highly Competitive Rates. Let us quote you now.

ANTEC ENGINEERING LTD.
6 Sunny Place, Sunny Garden Road
London NW4 1RS. Tel. 01-203 4822 (5086)

DESIGN, development, repair, test and small production of electronic equipment. Specialist in production of printed circuit assemblies. **YOUNG ELECTRONICS LTD.**, 184 Royal College Street, London NW1 9NN. 01-267 0201. (20)

AIRTRONICS LTD., for Coil Winding — large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed, 3a Walerand Road, London SE13 7PE. Tel: 01-852 1706. (61)

PRINTED CIRCUIT BOARDS — Quick deliveries, competitive prices, quotations on request, roller tinning, drilling, etc., speciality small batches, larger quantities available Jamiesons Automatics Ltd., 1-5 Westgate, Bridlington, N. Humber-side, for the attention of Mr. J. Harrison, Tel: (0262) 4738/77877. (18)

A.A.A. SERVICE. Small batch production wiring, assembly to sample or drawings. Specialists in printed circuit assembly. Cableforms to order. Rock Electronics Ltd., 42 Bishopsfield, Harlow, Essex. Tel. Harlow (0279) 33018. (19)

BATCH Production Wiring and Assembly to sample or drawings. Deane Electricals, 19B Station Parade, Ealing Common, London, W.5. Tel: 01-992 8976. (13)

CAPACITY available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 jig borer. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel: 01-985 7057. (14)

CRYSTAL TECHNOLOGY

For quartz growing, cutting, lapping and finishing. Designs for crystal devices.

CLARK EXPORT IMPORT COMPANY
MATTAPOISETT
MASS., U.S.A.

Crystal specialists since 1941 (5207)

ELECTRO MECHANICAL DRAWING FACILITIES. Production standard drawings from Engineer's sketches; printed circuit artworks from your layouts or circuit diagrams. Rapid turnaround. Roger Jeffery, 39 Bunyon Close, Pirton, Nr. Hitching, Herts Tel: Pirton 482. (5274)

CAPACITY AVAILABLE for assembling large or small quantities of P.C.B.'s Electronic and Electro-Mechanical equipment from drawings or prototype. Overseas enquiries welcome. Horizon Electronics, 100 Sandfield Road, Arnold, Nottm. Tel: 0602-606980. (5230)

DESIGN DEVELOPMENT and small production of electronic equipment. No job too small. — Holts Electronics, 223 Pole Lane Court, Unsworth, Bury, Lancs. BL9 8QD. (5281)

DESIGN. YOUNG C. ENG. (Electronics) Physicist, university based, offers individuals and small firms design work, consultancy and instrument construction. Novelty's to Microprocessors Systems. Tel: 0293 45132. (5279)

COURSES

GRADUATED OR GRADUATING?

Join the postgraduates at

BRUNEL UNIVERSITY

Department of Electrical Engineering and Electronics

Applications are invited from graduates or graduands in Electrical Engineering, Electronics, Mathematics, Computer Science or Physics who wish to obtain a higher degree by joining research teams working on:

COMPUTER AIDS TO DIGITAL SYSTEM DESIGN
INFORMATION PROCESSING SYSTEMS
INTELLIGENT AUTOMATA
POWER ELECTRONICS SYSTEMS
CONTROL SYSTEM DESIGN
COMMUNICATION SYSTEMS

Studentships are available for suitably qualified candidates.

Please write to Professor Igor Aleksander, Dept. of Electrical Engineering and Electronics, Brunel University, Uxbridge, Middlesex. (5272)

RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. (25)

VALVES WANTED

WE BUY new valves, transistors and clean new components, large or small quantities, all details, quotations by return. — Walton's, 55 Worcester St., Wolverhampton. (62)

ARTICLES FOR SALE

CRYSTAL OSCILLATORS

- 16 pin DIL package 4-25 MHz
 - Low frequency range from 150 Hz
 - CMOS & TTL compatible
 - Prototype service available
 - Fast delivery (some items ex-stock)
 - Competitive quantity discounts
- Meon Electronics Ltd., Savoy Works, Swan Street, Petersfield, Hants. Tel. 0730 2306/7. Telex: 86181.** (5286)

BOOKS

TELECOMMUNICATIONS:

A Systems Approach by G. Smol, M. P. R. Hamer and M. T. Hills covers the application of a number of signalling and transmission techniques in telecommunication systems at a higher level than most books on the subject. It takes account of the needs of the users of the systems and the economic constraints which affect the choice of techniques and overall system structure. This is an **Open University set book** for the T321 course. Price: Hardback £8.50; Paperback £4.25 from bookshops.

Published by **George Allen & Unwin Ltd., Park Lane, Hemel Hempstead, Herts. HP2 4TE.**

(5232)

**START YOUR OWN BUSINESS
REWINDING ELECTRIC MOTORS**

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience

Everything you need to know easily explained including where to obtain materials, how to get all the work you need, etc. etc.

A goldmine of information and knowledge

Only £3 65 + 25p P & P from

**Magnum Publications Dept. ME5
Brinksway Trading Estate
Brinksway, Stockport SK3 0BZ**

WIRELESS WORLD WANTED.
November 1975 issue. High price offered for a clean complete copy.
— Please telephone 01-888 1909.
(5253)

TAPE RECORDING ETC.**RECORDS MADE TO
ORDER**

DEMO DISCS
MASTERS FOR
RECORD COMPANIES

VINYLLITE
PRESSINGS

Single disc. 1 20. Mono or Stereo. delivery 4 days from your tapes. Quantity runs 25 to 1,000 records PRESSED IN VINYLLITE IN OUR OWN PLANT. Delivery 3-4 weeks. Sleeves/Labels. Finest quality NEUMANN STEREO/Mono Lathes. We cut for many studios UK/OVERSEAS SAE list

DEROY RECORDS

PO Box 3, Hawk Street, Carnforth
Lancs
Tel: 2273

(82)

APPOINTMENTS**THE ROYAL NORTHERN
COLLEGE OF MUSIC**

Applications are invited for the post of

**AUDIO VISUAL
AIDS
TECHNICIAN
GRADE T.1.C**

Salary £2,277 - £2529

The Technician will be responsible under the direction of the Recording Manager for the provision of the highest quality of Audio Visual reproduction and recording techniques in connection with public performances, broadcasting, commercial purposes and most important, involves close liaison with the tutorial staff and assistance in their tutorial programmes. Experience of tape editing sound mixing CCTV and the maintenance of recording and electronic equipment to a high standard should be combined with an appreciation of music and the ability to read musical score. Further details and application forms can be obtained from the Administration Registrar, The Royal Northern College of Music, 124 Oxford Road, Manchester. Closing date for applications 1st April, 1976

(5287)

EQUIPMENT WANTED**BROADFIELDS AND
MAYCO DISPOSALS**

21 Lodge Lane, N. Finchley
London, N12 8JG

Telephone:

01-445 2713

01-445 0749

01-958 7624

MAY WE ASSIST YOU TO
DISPOSE OF YOUR SURPLUS
AND REDUNDANT STOCKS.

We will call anywhere in the British Isles, and pay **SPOT CASH** for Electronic Components and Equipment.

(5234)

18IN FACSIMILE. Muirhead weather receiver required urgently. Please contact Sea & Storm Service Specialists. Tel. 01-723 8466.

(5237)

NEW GRAM EQUIPMENT

GLASGOW. Hi Fi. Cassette Decks. Tape Recorders. Video Equipment. always available we buy, sell and exchange for Hi Fi sets and photographic equipment. **VICTOR MORRIS** Audio Visual Ltd., 340 Argyle Street, Glasgow, G1, 8/10 Glassford Street, Glasgow, G1, 8/10 Sauchiehall Street. Tel: 041-221 8958. (11)

**RING
YOUR
CLASSIFIEDS
TO
OWEN
BAILEY
ON
01-261 8508
OR
01-261 8423**

SERVICE

When you need to hire Video-
it pays to contact the most experienced
video company in the business

REW

R.E.W. HOUSE
10, 12 HIGH STREET
COLLIERS WOOD
LONDON SW19 2BE
PHONE: 01-540 9684

Also at **CENTRE POINT**
20/21 ST. GILES HIGH STREET
LONDON, WC2
PHONE: 01-240 3066

(5212)

**PRINTED CIRCUITS
and HARDWARE**

Readily available supplies of Constructors hardware Aluminum sheet and sections Printed circuit board, top quality for individual or published designs

Prompt service

Send 15p for catalogue

**RAMAR CONSTRUCTOR
SERVICES**

Masons Road, Stratford-on-Avon
Warwicks. Tel: 4879

(38)

AUDIOMASTER . . . service, sales. Tape programmes. P. J. Equipments, 3 Onslow Street, Guildford 4801. (12)

RECEIVERS AND AMPLIFIERS

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (65)

SIGNAL Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (64)

THOR-HOLE CONVENTIONAL P.C.B.'s gold plating, roller tinning, prototypes, silk screening, drilling. All or part service. — **ELECTRO-CIRCUITS (P.C.) LTD.**, Delamare Road, Cheshunt, Herts. Tel. Waltham Cross 38600 or 20344. (84)

TUBE POLISHING, mono, £5.63, colour £5.94. C.W.O. Return carriage and VAT paid. Phone: N.S. 300, Retube Limited, North Somercotes, Lough, Lincs. (27)



**Instruments
well worth servicing
and worth
servicing well**

And now it's even easier because you can bring or send your AVO, MEGGER or SULLIVAN instruments for service or repair direct to the manufacturers' joint service and spares centre in-house BCS certification facility, London Instrument Repair Centre, *Repairs* Cunnington Street Acton Lane Works Chiswick, London W4 5HJ Tel 01-995 9212. Telex. 22583 *Enquires* Archcliffe Road DOVER, Kent CT17 9EN Tel 0304 202620 Telex 96283 AVO-MEGGER-SULLIVAN



(5248)

WANTED

WE BUY

All sorts of computers, peripherals, automatic typewriters, etc. Top prices paid.

Autotype, at East Hill, Otford, Kent. Otford 3256 or Otford 43393.

(5288)

FOUNDATIONS OF WIRELESS AND ELECTRONICS

M. G. Scroggie, B.Sc., C.Eng., F.I.E.E.

— 9th Edition

- ★ Since the first edition was first published in 1936 over a quarter of a million copies have been sold.
- ★ Has proved to be of great assistance to many thousands of enthusiasts and students making acquaintance with the principles of radio and electronics.
- ★ It has been written clearly and concisely in Mr. Scroggie's well-known and often humorous style.

CONTENTS: General View of a System. Electricity and Circuits. Capacitance. Inductance. Alternating Currents. Capacitance in a.c. circuits. The Triode at Work. Transistor Equivalent Circuits. The Working Point. Oscillation. Radio Senders. Transmission Lines. Radiation and Aerials. Detection. Low-Frequency Amplification. Selectivity and Tuning. The Superheterodyne Receiver. High-Frequency Amplification. Cathode-Ray Tubes; Television and Radar. Electronic Waveform Generators and Switches. Computers. Power Supplies. Appendices.

The cost of this very useful text is £3.75 which you will agree is tremendous value for a book of 521 pages. 0 408 001 88 7.

If you purchase a copy you could be the winner of a beautiful leatherbound copy, personally autographed by the author. Details of 'The ¼-million Competition' appear in the book.

For details of other books in this field please write

NEWNES TECHNICAL, Borough Green, Nr. Sevenoaks, Kent



CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

To "Wireless World" Classified Advertisement Dept., Dorset House, Stamford Street, London, SE1 9LU

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

- Rate: 99p PER LINE. Average seven words per line. Minimum THREE lines.
- Name and address to be included in charge if used in advertisement.
- Box No. Allow two words plus 40p.
- Cheques, etc., payable to "Wireless World" and crossed "& Co."

NAME.....

ADDRESS.....

.....

.....

			REMITTANCE VALUE..... ENCLOSED

PLEASE WRITE IN BLOCK LETTERS. CLASSIFICATION..... NUMBER OF INSERTIONS.....

Newnes Technical Books

The Newest name in Technical Books

For details of all the books in our list please write to:

**Newnes-Butterworths, Borough Green
Nr. Sevenoaks, Kent**


Telephone: Borough Green (0732) 884567



INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 130-142

	PAGE		PAGE		PAGE
Aero Electronics Ltd.	18, 22, 27	Grampian Reproducers Ltd.	18	Q Max Electronics Ltd.	20
Alice (Stancoil) Ltd.	24	Greenwood Electronics Ltd.	9, 115	Radford Laboratories Ltd.	14
Amateur Components	126	Hakuto Int. (U.K.) Ltd.	26	Radio Component Specialists	106
Ambit International Ltd.	24	Harmsworth Townley & Co. Ltd.	Readers Card	Radio Shop, The	104
Antex Products Ltd.	7	Harris Electronics (London) Ltd.	9, 25	Ralfe, P.	115
A.S.P. Ltd.	117	Harris P.	128	Rank Film Equipment	21
Aspen Electronics Ltd.	14	Hart Electronics	91	Rastra Electronics Ltd.	122
Audio Amateur	127	Hatfield Instruments Ltd.	117	R.C.S. Electronics	21
Avo Ltd.	19	Hayden Laboratories Ltd.	5	R.E.W. Audio Visual Co.	92
Audio Fair	29	Heath (Gloucester) Ltd.	13	R.I. Instruments	14
Audix Ltd.	27	Henry's Radio Ltd.	93	Rola Celestion Ltd.	97
Avant	102	Hepworth Electronics	10	R.S.T. Valves Ltd.	116
Barr & Stroud	8	H/H Electronic	20		
Barrie Electronics Ltd.	99	Icon Designs	2	Salford Electrical Insts. Ltd.	12
Bentley Acoustic Corp. Ltd.	109	I.L.P. (Electronics) Ltd.	98	Samsons (Electronics) Ltd.	113
Beyer Dynamic (G.B.) Ltd.	25	Imtech Products Ltd.	3	S.C.S. Components	123
B.H. Component Factors Ltd.	128	Industrial Tape Applications Ltd.	113	Scott, James (Electronic Eng.) Ltd.	96
Bi-Pak Semiconductors Ltd.	110, 111	Integrex Ltd.	100, 101	Semiconductor Supplies Ltd.	126
Bi-Pre Pak Ltd.	103	Jackson Bros. (Ldn) Ltd.	96	Service Trading Co.	125
Bradley, G. & E. Ltd.	cover iii	J.H. Associates Ltd.	26	Servodata Ltd.	104
Bradley, G. & E. Ltd.	cover iii	Kinnie Components Ltd.	108	Servo & Electronic Sales Ltd.	112
Brenell Eng.	10	Leevers Rich Equipment	16	Shure Electronics Ltd.	32
Bull, J., Electrical Ltd.	126	Levell Electronics Ltd.	1	Sinclair Radionics Ltd.	70, 71
Bywood Electronics	105	Lexor Electronics Ltd.	18	Sintel	93
Cambridge Learning	9	Limrose Electronics Ltd.	27	Strumech Eng. Ltd.	31
Case Systems	26	Linstead Electronics	21	Sugden, J. E. & Co. Ltd.	23
Catronics	93	Lynx (Electronics) London Ltd.	104	Swanley Electronics Ltd.	91
Chromasonic Electronics	95	MacInnes Laboratories Ltd.	23	Swift of Wilmslow	117
Colomor (Electronics) Ltd.	124	Magnetic Tapes Ltd.	30	Tandberg (U.K.) Ltd.	92
Combined Precision Components Ltd.	91	Maplin Electronic Supplies	89	Technomatic Ltd.	102
Computer Appreciation	116	McLennan Eng. Ltd.	16	Teleprinter Equipment Ltd.	12
Computer Sales & Service	123	Marconi Instruments Ltd.	Cover ii	Telford Products Ltd.	15
Contarnex Ltd.	126	Marshall, A., & Sons (London) Ltd.	99	Thomson CSF.	11
Crofton Electronics Ltd.	102	Medelec Ltd.	16	Trampus Electronics	109
Cryslon Electronics Ltd.	30	Mills, W.	94	Turner Electronics	28
Dema Electronics International	105	Multicore Solders Ltd.	Cover iv	United-Carr Supplies Ltd.	72
Dolby Noise Unit	100, 101	Naim Audio	30	Wayne, Kerr, The, Co. Ltd.	17
Drake, Philip, Electronic Ltd.	22	Nicholls, E. R.	114	West Hyde Developments Ltd.	92
Dymar Electronics Ltd.	4	Nolton Communications Ltd.	69	Weyrad (Electronics) Ltd.	31
Eagle International Ltd.	20	Nombrex Ltd.	18	Whiteley Electrical Radio Co. Ltd.	10
Electro Systems & Timing	28	Olson Electronics Ltd.	126	Wilmslow Audio	128
Electronic Brokers Ltd.	118, 119	Orchard Electronics	109	Wireless World Circards	6
Electronics Today International	127	Overseas Trade Fair	129	Wireless World (Circuit Designs)	107
Electrovalue Ltd.	105	PB Electronics Ltd.	17, 23	Wireless World (The Big Four)	90
Electronic Windings	28	Powertran Electronics	120, 121	Wye Electronics Ltd.	22
English Electric Valve Co. Ltd.	34	Precision Petite Ltd.	17	Z. & I. Aero Services Ltd.	8, 15, 94
ERG Components Ltd.	15, 27, 30	Pulse Electronics Ltd.	15	Zettler (U.K.) Division	12
ER/T Colour Faults Guide	114				
European Electronic Systems Ltd.	127				
Farnell Instruments Ltd.	25				
Fj-Comp Electronics	30				
Flight Link Control	28				
Forgestone Components	31				
Future Film Developments Ltd.	22				
Fyde Electronic Labs. Ltd.	27				



We're experts on all of these



HEWLETT



PACKARD

SOLARTRON

Schlumberger

RACAL instruments



ADVANCE
and many more.

For the Great Names a Great Service

Bradley Electronics are well known as manufacturers of precision electronic instrumentation. But there's another important aspect of our business – we're also experts on other people's products.

For 21 years our Services Division has been providing a first-class repair and recalibration service for all types and makes of electronic test and measuring equipment – from simple meters to complicated systems. Any manufacturer's instrument in the frequency range DC to 18 GHz – and to

36 GHz in some cases – collected and delivered back to your door ready to plug-in.

The Services Division has its own 35,000 sq ft factory, expert staff, comprehensive spares, and a Standards Laboratory approved by the British Calibration Service. It will supply calibration certificates for AC, DC and RF measurements. And, of course, our standards are directly traceable to NPL and NBS.

So – when your calibrator won't calibrate anymore, your generator

refuses to generate, or your counter stops counting – you know who to contact.

G & E BRADLEY LIMITED
Electrical House, Neasden Lane,
London NW10 1RR
Telephone: 01-450 7811
Telex: 225583

A Lucas Company

BRADLEY
electronics

WW-002 FOR FURTHER DETAILS

www.americanradiohistory.com

8 Hill Lane

Ersin Multicore- the international solder

Ersin Multicore 5-Core Solder


The proved superiority of ERSIN Multicore Solder for over thirty years is due to many factors. We have specialised throughout this period in the manufacture of cored solders. Consequently our research and manufacturing staff have been able to devote all their energies to the development of Multicore Solders. All alloys are of highest purity, carefully formulated and checked.

Our unsurpassed ERSIN flux is rigorously tested before and after it is incorporated in the solder wire. Our five separate cores of flux ensure flux continuity, leave only an ultra-thin layer of solder separating flux from work for instant wetting and provide a more accurate ratio of flux to solder. It is therefore possible to

use less solder and obtain greater reliability.

Our Quality Control at all stages of manufacture is guaranteed and recorded by the batch number on every reel.


Needle fine gauges

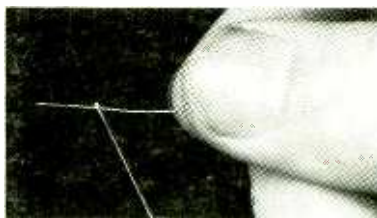

In addition to our standard range of wire diameters (10-22 swg: 3.2-0.7 mm) supplied on 2½ kg and ½ kg reels we also mass-produce needle-fine gauges (24-34 swg: 0.56-0.23 mm) on 250 g reels for microminiature soldering applications—still with 5 Cores of flux.

Savbit Solder

One of our most popular special ERSIN Multicore Solder alloys is SAVBIT alloy. Compared with ordinary tin/lead solders it dramatically reduces the erosion of soldering iron bits, copper wires and printed circuit conductors. It also saves costs and increases reliability. SAVBIT alloy containing 5-Cores ERSIN 362 flux has received special Ministry approval—under DTD. 900/4535 for Military applications.

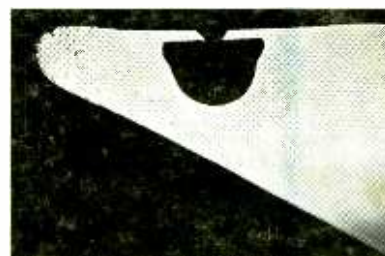

Sectioned iron-plated bit, after 40,000 simulated operations using 60/40 Solder.



Sectioned iron-plated bit, after 40,000 simulated operations using SAVBIT Solder.

ALLOY

Composition (nominal major elements)	Grade	Melting Temperature		Specification
		Solidus °C	Liquidus °C	
50/33/17 Sn/Pb/Cd	TLC	145	145	DIN 1707
62/36/2 Sn/Pb/Ag	LMP	179	179	DIN 1707
62/35.7/2/0.3 Sn/Pb/Ag/Sb	Sn62	179	179	QQ-S-57 1E
63/36.7/0.3 Sn/Pb/Sb	Sn63	183	183	QQ-S-57 1E
60/40 Sn/Pb	K	183	188	B.S. 219
60/39.7/0.3 Sn/Pb/Sb	Sn60	183	188	QQ-S-57 1E
50/50 Sn/Pb	F	183	212	B.S.219
50/49.7/0.3 Sn/Pb/Sb	Sn50	183	212	QQ-S-57 1E
50/48.5/1.5 Sn/Pb/Cu	Savbit 1	183	215	DTD 900/4535 DIN 1707
45/55 Sn/Pb	R	183	224	B.S.219
40/60 Sn/Pb	G	183	234	B.S.219
40/59.7/0.3 Sn/Pb/Sb	Sn40	183	234	QQ-S-57 1E
30/70 Sn/Pb	J	183	255	B.S.219
20/80 Sn/Pb	V	183	275	B.S.219
15/85 Sn/Pb	—	225	290	—
Pure Tin	P.T.	232	232	B.S.3252
95/5 Sn/Sb	95A	236	243	B.S.219
5/93.5/1.5 Sn/Pb/Ag	H.M.P.	296	301	B.S.219



For full information on these and a Selector Guide to other MULTICORE products please write on your Company's letterhead direct to:

Multicore Solders Limited, Maylands Avenue, Hemel Hempstead, Hertfordshire HP2 7EP.
Tel: Hemel Hempstead 3636 Telex: 82363