

ELECTRONICS & Wireless World

MARCH 1984

85p




ESTABLISHMENT

2 MAY 1984

AUCKLAND

Oscilloscopes

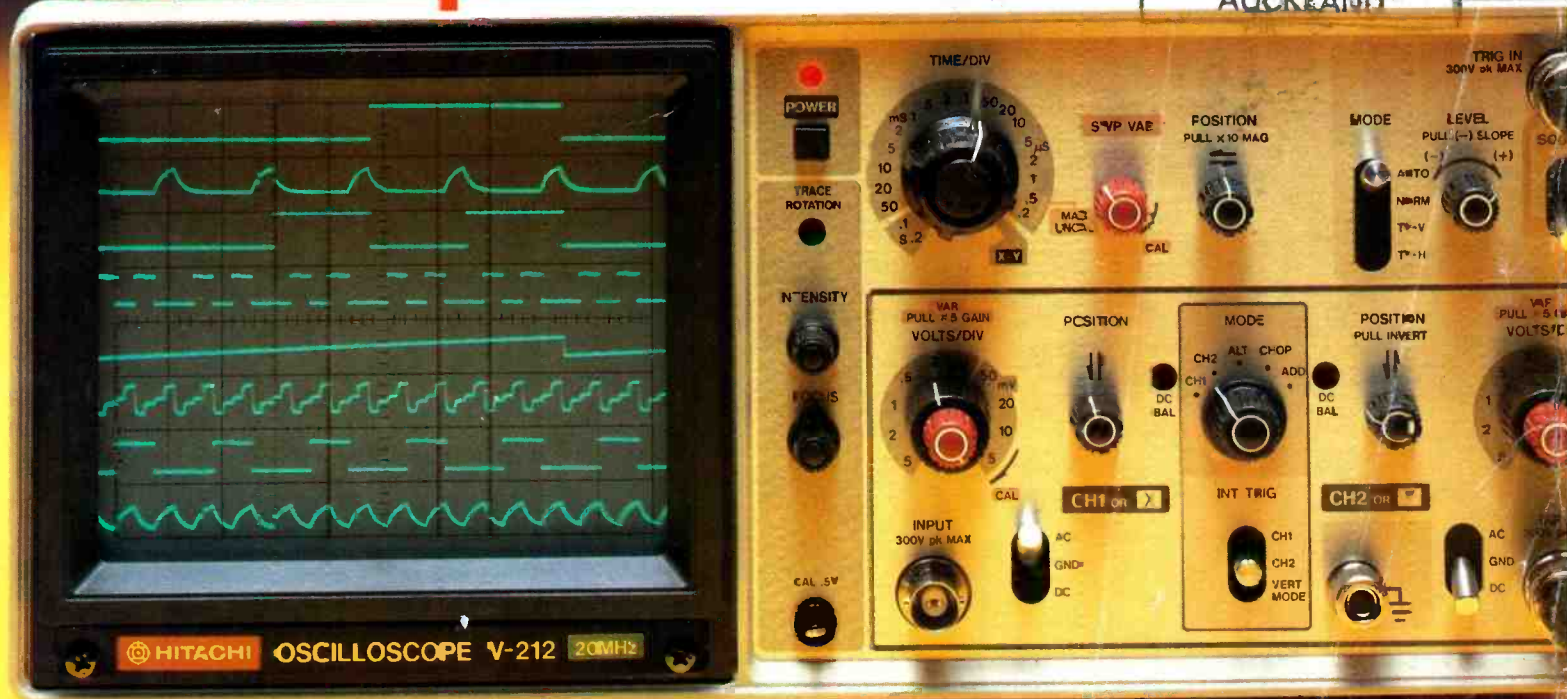

Typewriter interface

Colour tv decoder

Frequency response analyser

Digital filtering

Australia	A\$	3.00
Denmark	DKr	34.50
Germany	Dm	7.00
Greece	Dra	220.00
Holland	DFL	8.50
Italy	L	3800
Norway	Nkr	29.20
Singapore	M\$	5.50
Spain	Pts	340.00
Switzerland	SFr	7.00
U.S.A.	\$	3.75

dual trace oscilloscopes

LOW COST, COMPACT BRITISH MANUFACTURED OSCILLOSCOPES
FOR TEST, SERVICE OR DEVELOPMENT ENGINEERS



DT12-5 Dual trace, 12MHz, general use

DTV12-14 As above plus differential mode etc.
– useful in any service applications

DTC12 As above plus component tester
– a really versatile 'scope at a bargain price

DTS12 Our new digital storage 'scope
– at a remarkably low price

Free colour brochure describes the range.
Send for your copy now!



from



Farnell

FARNELL INSTRUMENTS LIMITED · WETHERBY · WEST YORKSHIRE LS22 4DH · TEL. (0937) 61961 · TELEX 557294


REGIONAL OFFICE SOUTH: TEL. HARPENDEN (05827) 66123/4

WW-001 FOR FURTHER DETAILS

ELECTRONICS & Wireless world

MARCH 1984

VOL 90 NO 1578

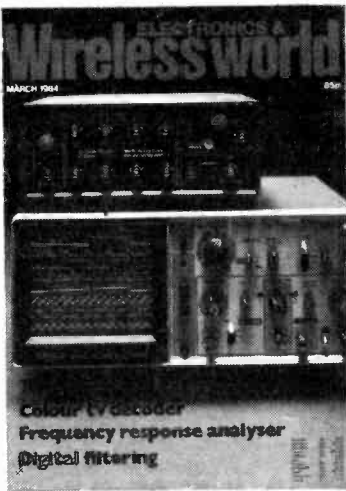

Front cover shows a Thurlby OM358 eight-trace multiplexer in use with a Hitachi V121 dual-trace oscilloscope to introduce our oscilloscope survey on page 57. Picture supplied by Thurlby.

NEXT MONTH

Bob Coates turns the Picotutor's 68705 microprocessor into a simple, low-cost interface for driving a teletypewriter from a microcomputer Centronics port.

As well as providing 5.5 and 6MHz sound, a synthesized tv modulator can be accurately switched to any u.h.f. channel.

Testing microprocessor systems is not so simple for the first-time builder without access to logic analysers or emulators. Carson gives some simple procedures that highlight hardware and software problems.

Surface wave, charge transfer and digital v.l.s.i. devices have enabled complex and powerful matched filters to be made. Geoffrey Robinson describes some examples that illustrate their different forms and uses.

Current issue price 85p, back issues (if available) £1.06, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.30, back issues (if available) £1.40, order and payments to Sundry Sales Dept, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Tel: 01-661 8668.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3614. Advertising 01-661 3130. See leader page. **Telex:** 892084 BISPRS G.

Subscription rates: 1 year £15 UK and £19 outside UK.

Student rates: 1 year £10 UK, and £12.70 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone: 01-661 3248.

Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone: 0444 459188. Please notify a change of address.


USA: \$49.40 surface mail, \$102.60 air. Business Press International (USA). Subscriptions Office, 205 E.42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd class postage paid at New York.

© Business Press International Ltd 1984
ISSN 0043 6062.

-
- 23 SOFTWARE COPYRIGHT**
-
- 24 COMMUNICATIONS COMMENTARY**
Brown's biography AM stereo 50MHz class A permits
-
- 26 ADAPTABLE TYPEWRITER INTERFACE**
by C. Fortesque-Webb
-
- 29 IMPROVING COLOUR TELEVISION DECODING**
by D. C. A. Read
-
- 35 ELECTRONIC DEVICES FOR THE DISABLED**
Winners of the Wireless World competition
-
- 36 DIFFERENTIAL TEMPERATURE INTEGRATOR**
by R. Everett
-
- 40 CIRCUIT IDEAS**
Opto circuits Moving-coil amplifier 15bit d.a.c.
-
- 43 PARALLEL-FED VOLTAGE MULTIPLIER**
by R. D. Purves and C. Prescott
-
- 44 FREQUENCY RESPONSE ANALYSER**
by R. Parta, K. Srivastava and S. L. Sridharmurthy
-
- 46 DIGITAL FILTER DESIGN PROCEDURE-3**
by J. T. R. Sylvester-Bradley
-
- 49 NEWS OF THE MONTH**
TAT8 is optical DSP algorithms Compressed f.m.
-
- 51 LETTERS TO THE EDITOR**
Radio software Energy saving Logic noise
-
- 57 OSCILLOSCOPE SURVEY**
Non-storage oscilloscopes up to 100MHz
-
- 66 DESIGNING WITH THE 68008 MICROPROCESSOR**
by A. J. Barth
-
- 69 16 LINE PABX WITH OPTIONS**
by J. H. Kuiper
-
- 70 NEW PRODUCTS**
Diode laser New computers Transistor tester
-
- 92 APPOINTMENTS**
-
- 104 ADVERTISERS INDEX**
-

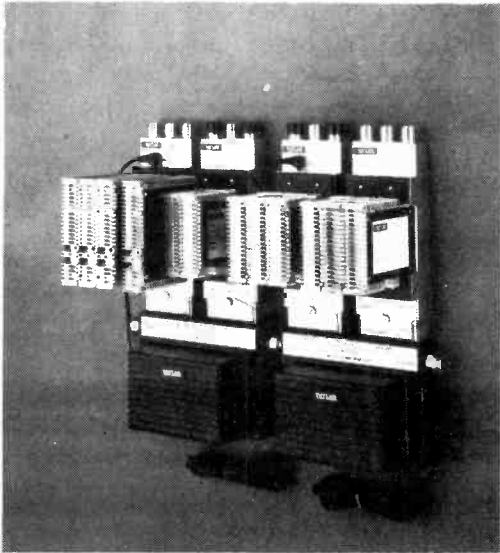CABLE T.V. HEAD END AND REPEATER AMPLIFIERS



CHANNEL CONVERTERS

TCUU UHF-UHF Single channel converter. Gain adjustable +2dB-16dB. Maximum output +26dBmV. Crystal controlled oscillator. Power requirement 14V 25mA. (Quote Channels required).
TCUV As TCUU except UHF to VHF converter. (Quote Channels required).
TCVU As TCUU except VHF to UHF converter. (Quote Channels required).

SINGLE CHANNEL AUTOMATIC GAIN CONTROL AMPLIFIERS

TAG4863 Gain 48dB, maximum output 63dBmV. Regulator + or - 8dB. Power requirement 14V 210mA.
TAG4063 Gain 40dB, maximum output 64dBmV. Regulator + or - 16dB. Power requirement 14V 210mA.

SINGLE CHANNEL AMPLIFIERS

TSS4663 Gain 28-46dB adjustable. Maximum output 63dBmV. Power requirement 14V 170mA.
TSS3062 Gain 12-30dB adjustable. Maximum output 62dBmV. Power requirement 14V 26mA.

DRIVER AMPLIFIERS

TS1030FM FM driver amplifier. 10dB Gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1030B3 Band III driver amplifier. 10dB gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1030UHF UHF driver amplifier. 10dB gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1040S Single channel UHF driver amplifier. 10dB gain. Maximum output 40dBmV. Power requirement 14V 10mA. (Quote channel required).

DISTRIBUTION AMPLIFIERS

TE2042 Domestic distribution amplifier. 1 input, 1 output. Gain 20dB. Maximum output 42dBmV.
TE1638 Domestic distribution amplifier. 1 input, 2 outputs. Gain 16dB. Maximum output: 2 at 38dBmV.
TS2046 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 46dBmV.
TS2846 40-860MHz. Gain 28dB UHF, 22dB VHF. Maximum output 46dBmV.
TS2845 Separate UHF/UHF inputs. Gain 28dB UHF, 22dB VHF. Maximum output 46dBmV.
TS2054 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 54dBmV.
TS2060 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 60dBmV.
TS5565 Gain 55dB UHF, 55dB VHF, 42dB FM. Maximum output 65dBmV.

REPEATER AMPLIFIERS


TSC3660 Repeater. Gain 16-36dB UHF, 10-30dB VHF. Maximum output 60dBmV.
TSC3665 Repeater. Gain 16-36dB UHF, 10-30dB VHF. Maximum output 65dBmV.
TSC3060 Repeater. Gain 10-30dB VHF. Maximum output 60dBmV.

QUALITY AT LOW COST

TAYLOR BROS (OLDHAM) LTD

LEE STREET, OLDHAM - TEL. 061-652 3221 - TELEX 669911


WW - 056 FOR FURTHER DETAILS

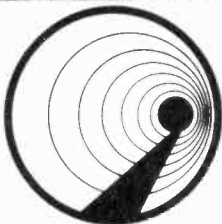

**INSIGHT
VISION
SYSTEMS
LIMITED**

Unit 1, Merebrook,
Hanley Road, Malvern,
Worcs WR13 6NP, England
Tel (0684) 310001
Telex 334480 INSIGTG

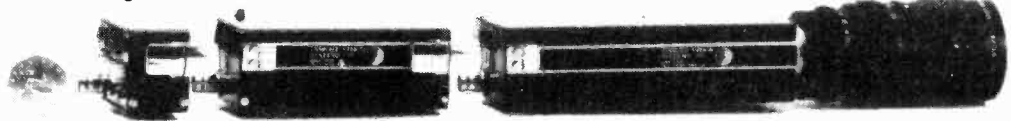DESIGNERS AND MANUFACTURERS OF HIGH QUALITY CCTV CAMERAS & SYSTEMS



This self-contained black and white camera has been developed for use in situations where space is at a premium but the need for high quality is of paramount importance. Features include:

- LOW POWER CONSUMPTION
- UNPROCESSED VIDEO OUT TO EE LENS
- EXTERNAL LOCK
- AUTOMATIC VIDEO BLACK LEVEL
- INBUILT IRIS DRIVE SERVO
- HIGH RESOLUTION, LOW NOISE PICTURE
- MOTORISED VIDICON RACKING
- 10 TO 32 VOLT DC OPERATION
- PLUG ON BATTERY AND REMOTE CONTROL MODULES
- EDGE ENHANCEMENT CORRECTION

We believe this is the smallest self-contained black and white TV camera available.
Contact Andrew Smith on (0684) 310001

WW - 068 FOR FURTHER DETAILS

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner

Telephone 445 2713/0749

WW - 025 FOR FURTHER DETAILS

RECHARGEABLE BATTERIES

EXPORT & TRADE ENQUIRIES WELCOME

Full range of Ni-Cads to replace 1.5 volt dry cells and 9 volt PP type batteries. S.A.E. for lists and prices. £1.45 for booklet, "Nickel Cadmium Power." Sealed lead range stocked. Chargers and multi-chargers to suit.

★ TRADE PRICES FOR SCHOOLS AND COLLEGES ★


Sandwell Plant Ltd, 656 Chester Road
Erdington, Birmingham B23 5TE

Tel: 021-373 9487

After hours Lichfield 57977

Southern Office - Hitchin 733254

WW - 007 FOR FURTHER DETAILS

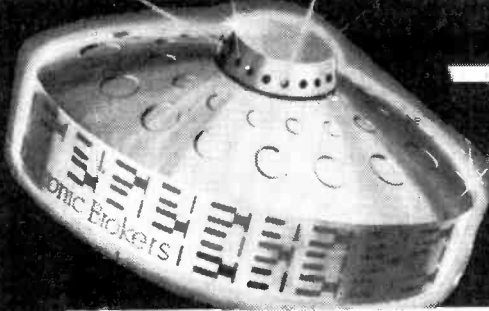


THE SOURCE OF ALL GOOD USED TEST EQUIPMENT

Electronic Brokers are Europe's largest specialists in quality second user test equipment, computers and associated peripherals. All second user test equipment offered by Electronic Brokers is calibrated to meet the original manufacturer's sales specifications and guaranteed for 12 months. Our latest catalogue contains full details of our extensive inventory. Contact us for your free copy now.

HEWLETT PACKARD Storage Oscilloscope 1744A

100MHz Dual Trace
Portable
1800 cm/ μ s
Variable Persistence
Superb Condition
Price: **£3,000**


Save **£2,586**
On New Price

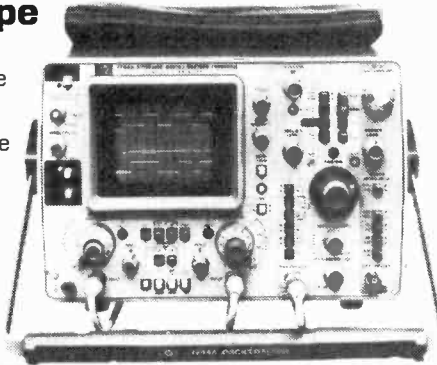

TEKTRONIX Oscilloscope Mainframe 7704A


200MHz Bandwidth
For use with 7000 series Plug Ins
As New Condition
Price: **£2,850**

Save **£1,068**
On New Price

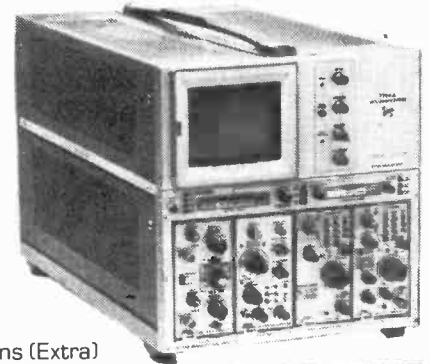

Illustrated with Plug Ins (Extra)

TEKTRONIX Data Comms Tester 833

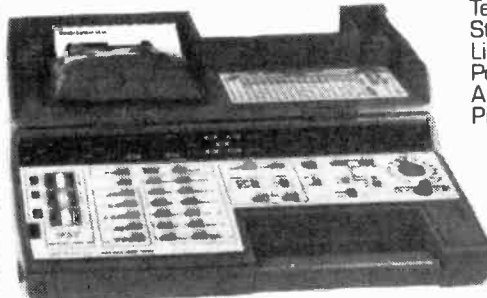

Bit Error Rate Testing
String Search
Lightweight and Portable
As New Condition
Price: **£995**


Save **£1,619**
On New Price

(30 Day Warranty Only)

RACAL-DANA Counter/Timer 9514

0.100MHz Counter
100ns to 10³ Sec Period
IEEE Interface

Superb Condition
Price: **£850**

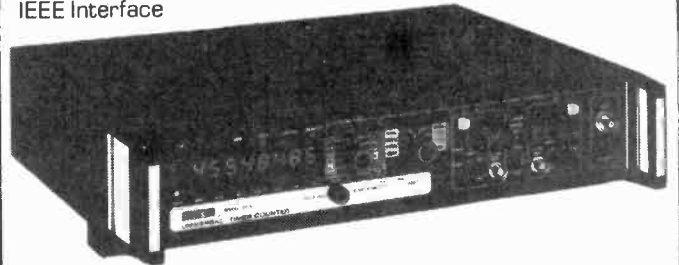

ANALYSERS

- Hewlett Packard**
334A Distortion Analyser **£1,200.00**
3581A Wave Analyser **£1,800.00**
3582A Dual-Channel Spectrum Analyser
0.02Hz-25.5KHz **£6,650.00**
- Tektronix**
AA501 opt 01. Distortion 10Hz-100KHz
to Less than 0.0025% **£1,450.00**
DAS 9103 opt 01 02. Logic Analyser
..... **£11,000.00**
DF1 Display Formatter For 7D01
..... **£500.00**
308 Portable 8 Channel 20MHz Data
Analyser **£2,100.00**
492 (opt 01, 08) Spectrum Analyser
50KHz-21GHz **£13,000.00**
7L12 Spectrum Analyser
100KHz-1.8GHz **£6,000.00**
7L13 Spectrum Analyser
1KHz-1.8GHz **£7,500.00**
7L18 Spectrum Analyser
1.5GHz-60GHz **£3,950.00**
TR503 Tracking Generator
(for 492/496 series) **£3,250.00**
7D01 16 Channel 100MHz
Sample Rate **£1,500.00**
7D02/01 Logic Analyser **£3,950.00**

OSCILLOSCOPES

- Hewlett Packard**
1332A High Quality CRT Display
9.6 x 11.9cm **£1,250.00**
1741A 100MHz Variable Persistence
..... **£2,850.00**
1744A 100MHz Variable Persistence
Storage **£3,000.00**
1809A 100MHz 4 Channel Plug In
..... **£2,000.00**
1821A Timebase Plug in **£1,000.00**
- Philips**
PM3232 Dual Beam 10MHz **£495.00**
PM3244 50MHz 4 channel **£1,500.00**

- Tektronix**
305 Portable battery scope/DMM. DT
5MHz **£1,200.00**
335 Dual Trace 35MHz Small portable
with delay T Base **£1,300.00**
200C Trolley for 400 Series **£1,120.00**
465 100MHz Portable **£1,500.00**
466 100MHz Storage **£3,750.00**
7313 100MHz Storage Mainframe
..... **£2,225.00**
7603 100MHz Mainframe **£1,950.00**
7623 100MHz Storage **£2,500.00**
7704A Scope DC-200MHz Mainframe
..... **£2,850.00**
7613 Storage Scope Mainframe
DC-100MHz **£3,250.00**
7844 Dual Beam 400MHz Mainframe
..... **£8,000.00**
5110 Mainframe 2MHz **£1,095.00**
C12 Camera
..... **POA**
- Tequipment**
D34 15MHz DT Battery Portable
..... **£350.00**
CT71 Curve Tracer **£550.00**
- Gould**
OS4000 10MHz Digital Storage
..... **£995.00**

SIGNAL SOURCES

- EH Labs**
132A Pulse Gen. **£1,200.00**
139B Pulse Gen. **£950.00**
- Hewlett Packard**
204C Oscillator **£200.00**
204D Oscillator **£240.00**
214A Pulse Gen. **£950.00**
11720A Pulse Modulator **£1,950.00**
612A Sig Gen. **£1,500.00**
8004A Pulse Gen. **£450.00**
8011A-01 Pulse Gen. **£695.00**
8013B Pulse Gen. **£750.00**
8620C Sweeper Mainframe **£2,100.00**
86240B Sweeper Plug In 2-8.4GHz
..... **£4,200.00**

- 862228 Sweeper Plug In 0.1-2.4GHz
..... **£4,000.00**
8640A Sig Gen. **£2,750.00**
8640B opt 1 2.3 AM/FM Sig Gen.
0.5-1024MHz **£4,950.00**
- Marconi**
TF2008 Sig Gen. **£3,000.00**
TF2015 Sig Gen. **£1,350.00**
TF2015/1 Sig Gen. **£1,350.00**
TF2016 AM/FM Sig Gen.
10KHz-120MHz **£950.00**
TF2173 Digital Sync for TF2016
..... **£600.00**
TF2169 Pulse Modulator **£200.00**
TF2120 Waveform Gen **£850.00**
- Wavetek**
148 Funct Gen. **£650.00**

TEKTRONIX PLUG INS

We stock a complete range of Plug Ins for use with 7000 and 5000 series Mainframes.

TEKTRONIX TM500 SERIES

We stock a very wide range of these versatile modular equipments

MISCELLANEOUS

- Avo**
Model 8 Multimeters **£80.00**
7 Electronic's Multimeter **£65.00**
- Bruel & Kjaer**
2209 Sound Level Meter **£850.00**
1613 Filter **£400.00**
- Datlabs**
DL901 Transient Recorder **£750.00**
- Fiske**
515A Portable Calibrator **£1,750.00**
8050A 4 1/2 Digit DMM **£200.00**
8502A DMM **£1,200.00**

- 931B Diff V/Meter **£1,000.00**
2020A-3-6 Printer **£500.00**
5205A Precision Power Amplifier
..... **£3,500.00**
8921A DMM **£695.00**
- Hewlett Packard**
461A Amp 20/40DB 1KHz-150MHz
..... **£120.00**
467A Amplifier **£725.00**
415E VSWR Meter **£950.00**
3556A Psophometer **£850.00**
3552A Trans Test Set **£1,500.00**
4815A Vector Impedance Meter
..... **£3,850.00**
59308A HP1B Timing Generator
..... **£300.00**
- Marconi**
TF1313A LCR Bridge **£775.00**
TF2603 RF Millivoltmeter **£750.00**
TF2604 Electronic Voltmeter **£350.00**
TF2700 LCR Bridge **£295.00**
- Racal**
9514 Counter/Timer IEEE **£850.00**
- Tektronix**
106 Square Wave Generator 1ns
risetime 10Hz-1MHz without
accessories **£175.00**
191 Constant Amplitude Generator
..... **£250.00**
832 Data Comms Tester **£395.00**
833 Data Comms Tester **£995.00**
2701 Step Attenuator 50n to 0.79dB in
1dB steps. DC to 2GHz **£295.00**

SPECIAL OFFER

TEKTRONIX. A complete Measurement System.
TM506 c/w FG501, PG501,
PS501-1, DM501, SC501,
DC503. 1 YEAR WARRANTY.
£2000 THE LOT

ADD 15% VAT TO ALL PRICES

Carriage and Packing extra




**Electronic Brokers Ltd., 61/65 Kings Cross Road,
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**

Essex Tiny Basic System

The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal. Instant ROM modules may be used both during development and for program storage.

£198

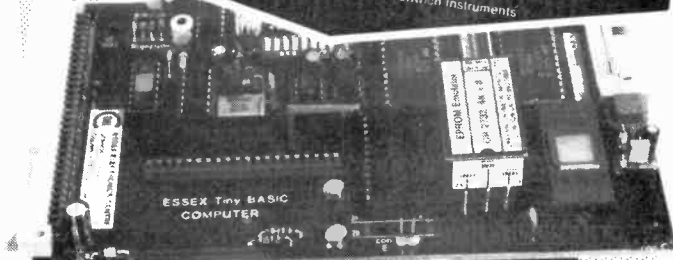
INSTANT ROM is the trademark of Greenwich Instruments



Essex Buffer Timer

A convenient means of buffering the I/O lines of the Essex Tiny BASIC Computer provides 24 inputs, 16 outputs and four hardware timers.


£96

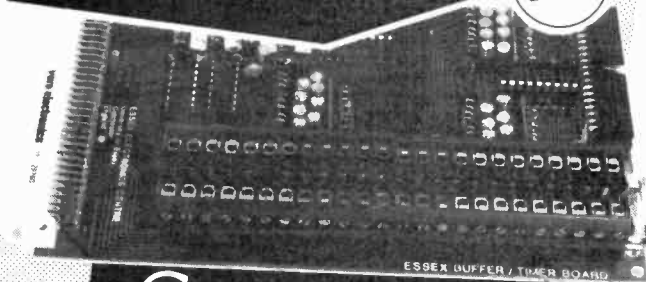

Essex Opto-Isolator

Connects to the Essex Tiny BASIC System bus to provide an additional 12 opto-isolated inputs and 12 opto-isolated outputs per card for safe connection to external equipment, isolation voltage = 1500 volts.

£165

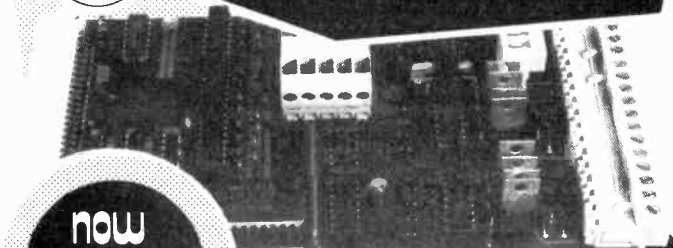

now available...

Essex Backplane

A four slot backplane with printer and terminal connectors to accept these cards.

£61

'Alex'

A powerful software utilities package that provides the user with an enhanced editor and all the tools needed to program efficiently in assembly language.

* Text Editor * Assembler
* Disassembler * Debug Monitor

£65

Supplied as a 4K EPROM with comprehensive manual.

all prices exclude V.A.T.
* substantial quantity discounts available
* carriage within U.K. £2


Essex Electronics Centre
Wivenhoe Park, Colchester, Essex CO4 3SQ
Telephone: Colchester (0206) 865089

WW - 054 FOR FURTHER DETAILS

Patchcords?



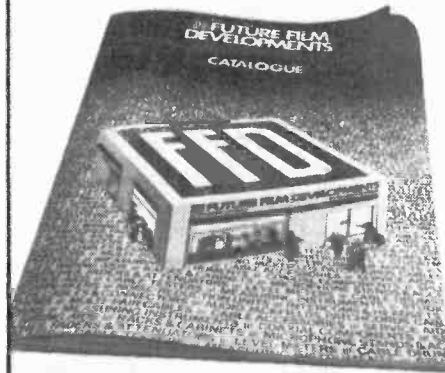Audio, Video and Data cords listed in our Catalogue.



Write or call for your free copy.

FFD FUTURE FILM DEVELOPMENTS
114 Wardour Street, London W1V 3LP, England.
Telephone: 01-434 3344 & 01-437 1892. Telex: 21624 ALOFFD G.

WW - 040 FOR FURTHER DETAILS



Orange aid!

No! It's not a floating drinks dispenser, it's the Neptune hand-held radio case. Neptune is brilliant orange, it floats, it's waterproof and could save your life if your ICOM hand-held fell in the drink. Neptune cases are easily retrieved from:

Thanet Electronics Ltd.
143 Reculver Road Herne Bay Kent.
Tel: (02273) 63859/63850.
Sole U.K. Importers of ICOM equipment.

WW - 028 FOR FURTHER DETAILS

Electronic Brokers Ltd


*Authorised
Distributor*

FOR
Philips • Fluke
Hameg • Ice
Test Equipment



Full Colour Catalogue
Send for your free copy now.



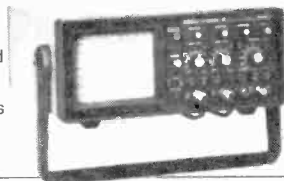
Philips PM3207 15MHz Oscilloscope £325
Compact, portable, lightweight oscilloscope designed for field and workshop use. 15MHz bandwidth with 5mV sensitivity. TV and auto triggering from either channel, with adjustable level. Add and invert facilities and X-Y mode. Large screen with internal graticule.



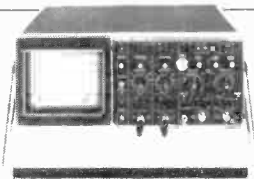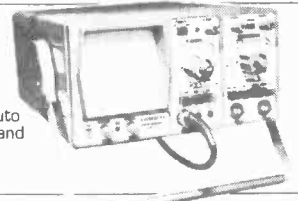Hameg HM103 10MHz Oscilloscope £158
This small oscilloscope has been designed specifically for field service personnel and advanced electronic hobbyists. Single trace, 10MHz bandwidth with 2mV sensitivity. TV and auto triggering with adjustable level. Internal graticule and in-built component tester.




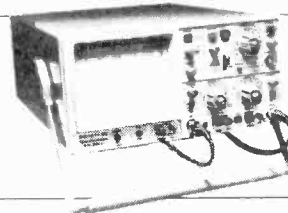Philips PM3217 50MHz Oscilloscope £850
High 2mV sensitivity, dual trace, 8 x 10cm display with small spot size, high light output, and illuminated graticule, auto trigger mode, TV triggering on line and frame. Full X-Y display facilities. Comprehensive second time base facility. Compact dimensions and low weight.
Philips PM 3215 Single time base £695




Hameg HM203-4 20MHz Oscilloscope £264
Designed for general purpose applications in industry and education. Versatile triggering performance to at least 40MHz. Dual trace X-Y operation, TV triggering, add and invert mode and component tester make the price/performance ratio of this scope most attractive.

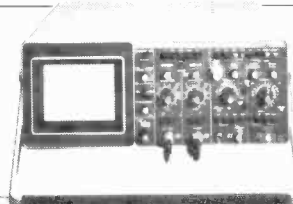
Philips PM3219 Storage Oscilloscope £2675
Provides comprehensive, cost effective storage of single-shot transients and low frequency events. Variable persistence and variable storage. Auto erase between 1 and 10 seconds, and read button facility. Auto store up to 1 minute, up to 24 hours in 'baby sit' mode. 2mV sensitivity at 50MHz.



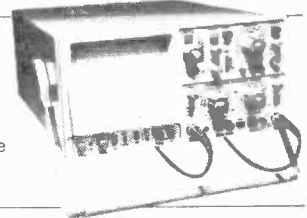Hameg HM204 20MHz Oscilloscope £365
High performance scope with peak value triggering up to 50MHz. Versatile triggering facilities and variable hold off control. Dual trace, delayed sweep mode, Z modulation, X-Y operation, internal illuminated graticule and component tester complete the attractive specification.




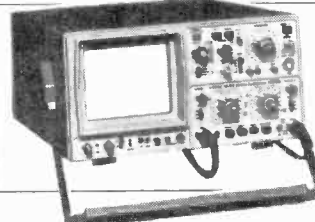Philips PM3256 75MHz Oscilloscope £1245
Tough, light-weight ruggedised unit, with shoulder strap, that can be used in harsh service environments. Fast trigger circuits to over 100MHz. TTL triggering is standard. Trigger view third channel and full X-Y display. Dual trace with 2mV sensitivity and delayed time base.
Philips PM 3254 Single time base £1145




Hameg HM605 60MHz Oscilloscope £487
Outstanding performance with versatile triggering to 80MHz. Sensitivity 1mV to 30MHz and 2mV above. Bright display from 14kV CRT. Switchable 1kHz/1MHz probe calibrator. Dual trace, delayed sweep, X-Y operation, Z modulation, internal illuminated graticule and component tester.

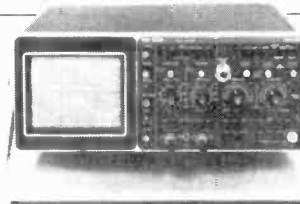Philips PM3267 100MHz Oscilloscope £1250
Versatile and economic instrument designed for advanced electronic environments. Separate main and delayed time base controls with comprehensive triggering facilities and trigger view third channel. Dual trace, 2mV sensitivity, full X-Y display, Z modulation and internal illuminated graticule.



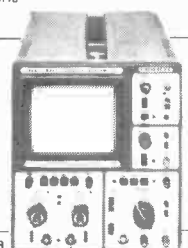Hameg HM705 70MHz Oscilloscope £588
General purpose scope with multitude of operating modes and trigger facilities. Extremely bright and well defined displays, with 8 x 10 cm. screen and internal illuminated graticule. TV triggering, Z modulation, X-Y display facilities and sweep delay mode. Dual trace.




ADD 15% VAT TO ALL PRICES. Carriage and Packing extra.

**Electronic Brokers Ltd., 61/65 Kings Cross Road,
London WC1X 9LN. Tel 01-833 1166. Telex 298694**

RADIOCODE CLOCKS SOLVE PROBLEMS

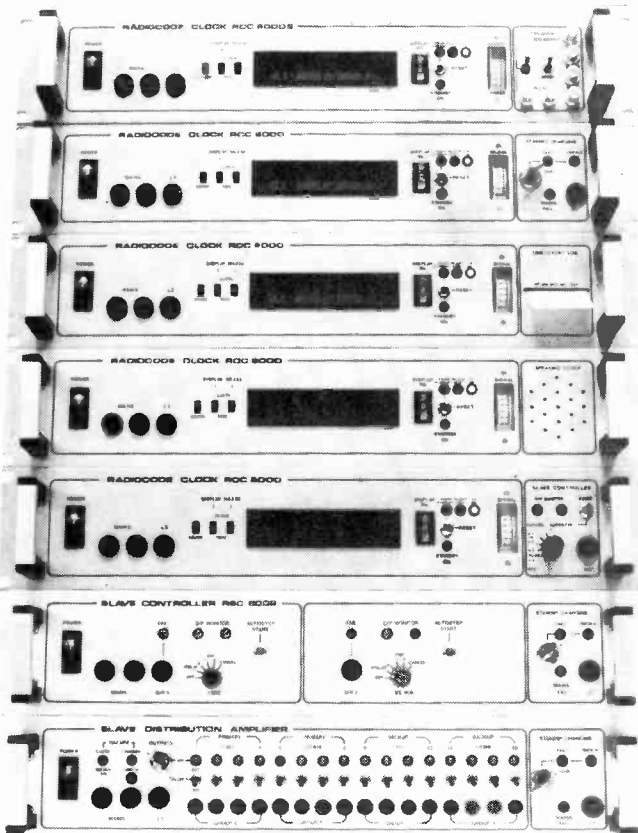ATOMIC TIME, FREQUENCY AND SYNCHRONISATION EQUIPMENT



NEW PHASE-MODULATION SYSTEMS

Until recently, atomic time and date information was only available on v.l.f. transmissions using amplitude modulation. The RCC 8000AM series of equipment uses these transmissions to offer high noise immunity and high accuracy, particularly at very long range.

The new RCC 8000PM series of equipment uses, for the first time, phase modulated transmissions with massive radiated powers of up to 2 Mega-Watts to offer long range, excellent noise immunity and no scheduled maintenance periods.

NEW PRODUCTS

The AM and PM series of Radiocode Clock equipment has been further expanded to include seven new models (from top) **8000S** – combined clock, frequency standard and optional stopclock. **Internal standby power supply** – with dual rate constant current charger. **Time-event log** – prints hours, minutes, seconds, milliseconds and day of year, on receipt of a log pulse. **Speaking clock** – time announcement or audio recording. **Slave controller** – total control of single-standard master/slave systems ie one pulse/sec. **Dual standard slave controller** – total control of two different and independent slave systems, ie. one pulse/sec and one pulse/half min. **Slave distribution amplifier** – maximum flexibility for the largest master/slave installations requiring dual standard operation, multiple circuits and complete master/slave backup.

NEW OPTIONS

A continuously expanding range of fully integrated software and hardware is available for both series of Radiocode Clock equipment. Standard options now include:

- IRIG B precision serial o/p
- RS232/V24 1mS resolution
- General purpose parallel o/p
- FSK record/replay system
- Keypad entry of alarm times
- Keypad entry of time/date
- Time code generators
- Intelligent slave systems
- Standard frequency outputs
- Stopclock operation
- Calibrated systems for increased accuracy

Radiocode Clocks Ltd*

Unit 19, Parkengue, Kernick Road Industrial Estate
Penryn, Falmouth, Cornwall. Tel: Falmouth (0326) 76007
(*A Circuit Services Associate Co.)

WW – 034 FOR FURTHER DETAILS



If you have trouble understanding chopper circuits and protection arrangements, want to know about flywheel line sync, are deeply interested in all things from pattern generators to satellite TV receiving techniques—well, have we got the magazine for you.

What would you say to a unique specialist magazine which offers guidance to enthusiasts as well as electronics technicians on all aspects of TV and Video, including servicing, news and developments?

It's well worth a closer look...
March issue on sale 15 Feb.

SWITCH ON TO...

TELEVISION
SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS
£1.00

SALE*

P.&R. COMPUTER SHOP

SALE*

IBM GOLFBALL PRINTERS from £70 EACH + V.A.T.

INTERFACE FOR IBM GOLFBALL £40 + V.A.T.
CENTRONIC 779 PRINTERS – £200 + V.A.T.
CENTRONIC 781 PRINTER – £225 + V.A.T.
POWER UNITS 15 VOLT 10 AMP – £20 EACH
FANS, PCBs, KEYBOARDS AND LOTS MORE
8-INCH BURROUGHS FLOPPY DISC DRIVES

COME AND LOOK AROUND

SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, MALDON, ESSEX
PHONE MALDON (0621) 57440

Hours: Mon-Fri. 9am to 5pm. Sat. till 1pm

WW – 036 FOR FURTHER DETAILS

FILTERS

Custom-built to YOUR requirements

Solent Electronic Services Ltd. specialize in the custom design and manufacture of L/C and crystal filters in the 0-40 MHz range (0-1000 MHz under development).

Filters are designed, built and tested to meet the highest specifications, including those for telecommunications and defence.

Production is specifically geared to small quantities - from single units to small batches - at relatively low cost.

Phone or write for further information.



Solent Electronic Services Ltd.

15 Abshot Close Titchfield Common
Fareham Hants PO14 4LZ
Tel. 04895-82094

WW – 037 FOR FURTHER DETAILS

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns.....	1.25	1.15	1.10
4164 200ns.....	4.95	4.40	4.20
2016 150ns.....	3.85	3.45	3.30
6116 150ns Low power.....	5.25	4.70	4.50
6264 150ns.....	28.00	25.00	24.00
2716 450ns 5 volt.....	3.85	3.45	3.30
2732 450ns Intel type.....	3.85	3.45	3.30
2532 450ns Texas type.....	3.85	3.45	3.30
2764 250ns.....	Call	Call	Call
27128 300ns.....	Call	Call	Call

Z80A-CPU.....£2.99	Z80A-P10.....£2.99	Z80A-CTC.....£2.99
6522 PIA.....£3.70	7805 reg.....£0.50	7812 reg.....£0.50

Low-profile IC sockets:	Pins:	8	14	16	18	20	22	24	28	40
	Pence	12	13	14	16	18	22	24	27	38

Soft-sectored floppy discs per 10 in plastic library case:
 5 inch SSSD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00
 5 inch SSQD £23.95 5 inch DSQD £26.35

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.

*Please add 50p post & packing to orders under £15 and VAT to total
 Access & Visa welcome. 24-hr 'phone service on (054 422) 618
 Government & Educational orders welcome, £15 minimum
 Trade accounts operated, 'phone or write for details*

HAPPY MEMORIES (WW)
Gladestry, Kington
Herefordshire HR5 3NY
Tel: (054 422) 618 or 628

E.M.S. POWER SYSTEMS



Solve all your Power Problems by contacting E.M.S.

E.M.S. specialise in systems to eliminate your power problems.

Products range from 35VA switched square wave Power Packs to 1KVA fully uninterruptible sine wave systems.

E.M.S. also manufacture chargers which range up to 60 amps.

For further details please contact:

E.M.S. Manufacturing Limited
Chairborough Road
High Wycombe
Bucks
Tel: (0494) 448484

WW - 020 FOR FURTHER DETAILS

DEC SALE

a selection from our huge stocks. All items reconditioned unless otherwise stated.

WINTER '83/'84 CATALOGUE NOW OUT
 Send for your Free copy now.

UNIBUS OPTIONS

AR11KT A/D Converter	£750
DB11A Bus Repeater	£250
DD11A Backplane	£125
DD11CK Backplane	£275
DL11E Interface	from £395
DL11W Interface	from £395
DMC11AL I/P Link	£975
DMC11AR Network Link	£895
DMC11DA EIA Link	£575
DMC11MD Modem Link	£875
DMF32 Multiplexor	£2,750
DD11DA Synch Ctl	£1,250
DR11B DMA Interface	£550
DR11C Gen. Purpose I/F	£350
DR780-AB DMA Interface	£7,500
DUI10A Synch I/F	£195
FP11C Floating Point	£2,750
KE11B Ext. Arithmetic	£595
KE44A EIS	£395
KG11A CRC Module	£350
KJ11A Stack Limit Module	£75
KMC11A Aux. Processor	£695
KT11C Memory Management	£750
KT11D Memory Management	£425
KW11L Real Time Clock	£75
KW11P Programmable RTC	£345
M9301 Bootstrap	£125
M9312 Bootstrap	£395
XY11 Plotter Interface	£450

LSI 11

11/03 Processor 32KW	from £1,495
11/23 Processor 128KB	from £2,950
AAV11A D/A Converter	£950
ADV11A A/D Converter	£725
BA11MF 3 5in Expander Box	£595
DIV11 Asynch Interface	£125
DIV11F Asynch Interface	£150
DIV11J 4-line Interface	£350
DRV11B Parallel I/O	£295
DUV11A Synch Interface	£395
IBV11A IEEE Interface	£325
KDF11AA CPU Module	£900
KDF11AC CPU Module	£695
MRV11C Prom Module	£175
MSV11DC 16KW MOS Memory	£150

MSV110D 32KW MOS Memory	£225
MSV11LK 256KB MOS Memory	£750
MSV11PL 512KB MOS Memory	£1,395
VTV01 A/D Controller	£475

PERIPHERALS

CR11 Card Reader	£500
PC11A Reader Punch and Ctl	£925
PR11 Reader and Ctl	£675
RK05F 5MB Disk Drive	£850
RK05J 2 5MB Disk Drive	£975
RK06 14MB Disk Drive	£1,225
RK07 28MB Disk Drive	from £1,750
RL01A 10MB Disk Drive	£995
RM03 67MB Disk Drive	£6,250
RP04 88MB Disk Drive	£2,750
RP06 256MB Disk Drive	£7,500
TE10 Tape Deck incl Cabinet	£2,500
TE16 Tape Deck	from £2,500
TU16 Tape Deck	from £1,500
TU77 Tape Deck incl TM03	£14,500

CONTROLLERS

RH70 Massbus Controller	£3,000
RH780 VAX780 Controller	£3,500
RK110 RK05 Disk Ctl (Unibus)	£395
RKV11DA RK05 Disk Ctl (LSI11)	£395
RK611/RK711 RK06/RK07 Disk Ctl	£750
RL11/RL211 RL01/RL02 Disk Ctl (Unibus)	£1,500
RVL11 RL01/RL02 Disk Ctl (LSI11)	£750
RL8A RL01/RL02 Disk Ctl (POP8)	£750
TMB11 Tape Controller	£625

PRINTERS

LA34 KSR 30 cps	from £425
LA35 RD 30 cps	from £250
LA36 KSR 30 cps	from £295
LA120DA KSR 120 cps	£1,500
LA180PD RD 180 cps	£495
LP04 RD 1200 Lpm	£5,500
LP05 RD 300 Lpm	£2,500
LS120 KSR 120 cps	£750

VDUS

Hazeltine 1500	£325
DEC VT100	£775


TEKTRONIX COLOUR GRAPHICS

Ex-Demonstration Stock in Original Manufacturer's Packaging

Colour Graphics Terminal Model 4027A

Providing full colour graphics and alphanumerics. Plot 10 compatible. 8 displayable colours from palette of 64. Full screen crosshair cursor 34 x 80 display (2720 characters). 120 user-defined patterns. RS232 Interface with up to 9600 baud transmission.

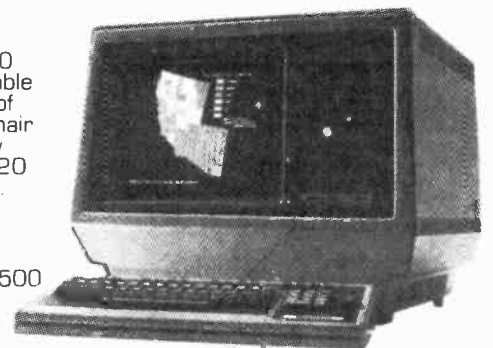Original List Price £9,500
 Our Amazing Price
 Only **£1,995**




ADD 15% VAT TO ALL PRICES Carriage and Packing extra

Electronic Brokers Ltd., 61/65 Kings Cross Rd
London WC1X 9LN. Tel: 01-278 3461

Electronic Brokers

WW - 203 FOR FURTHER DETAILS

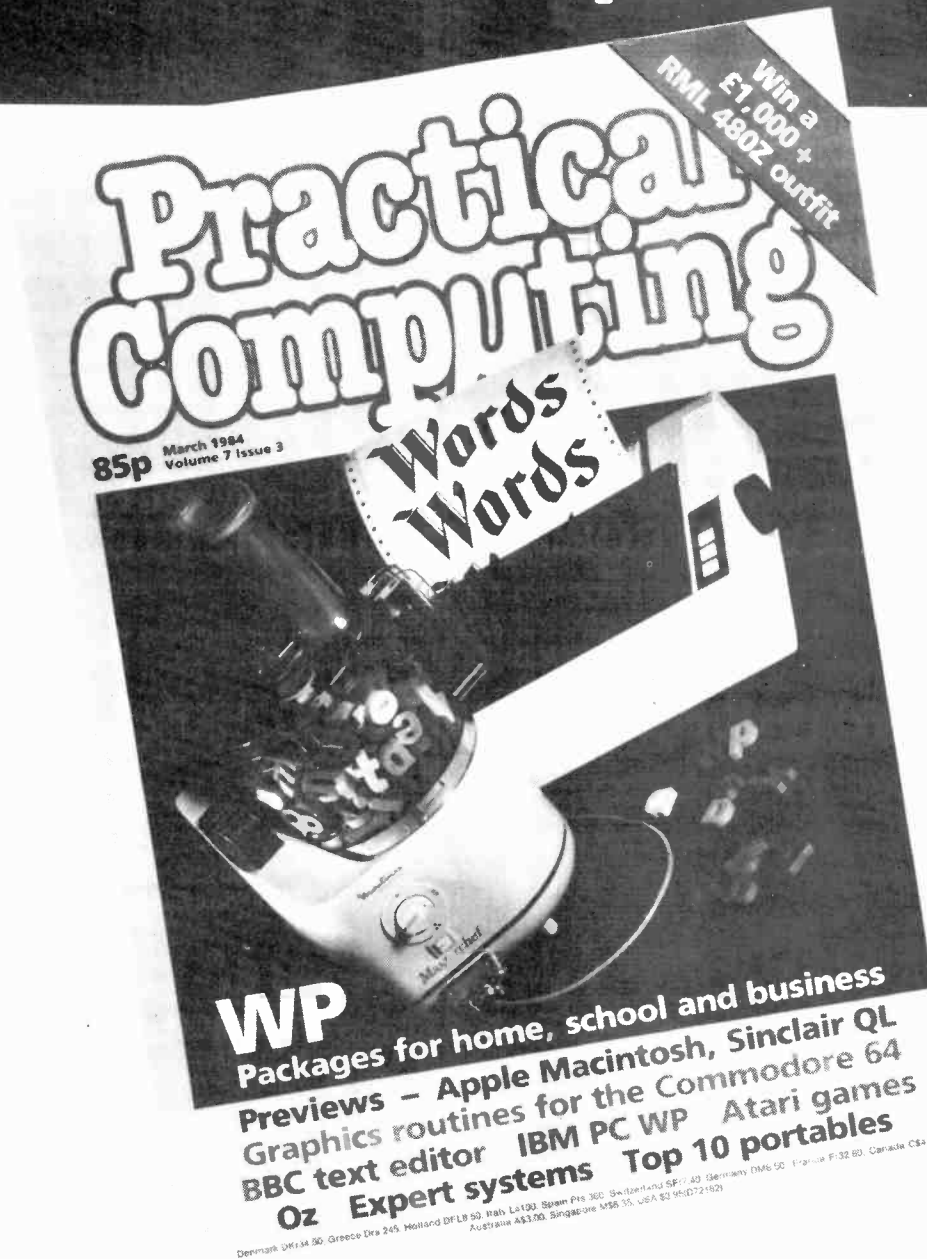**This month's Practical Computing
processes the
facts on word processing.**



This month we include a guide to the range of word processing packages available and give the pros and cons of each. Plus previews of the new, user friendly, Apple Macintosh and the Sinclair QL. A survey of the growing number of portable computers. Latest software reports on OZ, Expert-Ease and Atari Games. A benchtest of the Research Machines 480Z. The chance to win a computer and peripherals worth £1000. And lots more. All in the March issue of Practical Computing. Out now, 85p.

Practical Computing
At work. At home

ELECTRICAL-ELECTRONIC PRESS

WIRELESS WORLD MARCH 1984

The lightweight mast with 101 applications

25 years in this specialist field



The smoothly operated QTM Mast comes fitted with handpump or can be vehicle mounted with 'Power Pack' for extension and retraction. Available in a range of heights up to 15 metres, the QTM mast can provide the ideal answer for:

- Mobile Radio Telephone
- Police Mobile HQ (UHF)
- Field Telecommunications
- Floodlighting
- Anemometer and Wind Measurement
- Environmental - gas sampling collector
- High level photography
- Meteorology
- And a host of other uses

CLARK MASTS

Find out more about the QTM series by writing or phoning:-

U.K.
CLARK MASTS LTD. (W.W.)
Evergreen House, Ringwood Road,
Binstead, Isle of Wight,
England PO33 3PA
Tel: Isle of Wight (0983) 63691
Telex 86686

EUROPE
GENK TECHNICAL PRODUCTS N.V. (W.W.)
Woudstraat 21, 3600 Genk,
Belgium
Telefoon 011-380831
Telex 39354 Genant B

WW - 017 FOR FURTHER DETAILS

MIDWICH

COMPUTER COMPANY LIMITED

RICKINGHALL HOUSE, HINDERCLAY ROAD, RICKINGHALL, SUFFOLK IP22 1HH. TEL. DISS (0379) 896781.

BBC Microcomputers

Model B 348.26
Model B + Disc Int 433.21
NB Credit cards are not accepted in payment for BBC Microcomputers

BBC Micro Econet

Full range of products available Installation service available

BBC Compatible Disc Drives

Cased drives, finished to match the BBC Micro are supplied complete with connecting cables, manual and utilities disc.

All single cased drives may be expanded to dual configuration by the addition of the appropriate uncased mechanism

Disc capacity	Single	Dual	Uncased
100K 40T	150.83	291.95	130.00
400K 40/80T D S	284.35	479.15	215.00

Trade/quantity discounts are available

BBC3 Disc Interface 84.95
Please send for our BBC Micro price list. Full range of accessories available

Memories

2114L-20	D1	0.92
4116-15	D2	1.05
4116-20	D2	0.88
4118-15	D1	3.75
4164-15	D2	4.33
4164-20	D2	3.95
4416-20	D2	6.60
4564-15		5.25
5516-25		7.73
6116-3	D1	3.72
6116-LP3	D2	4.67
2532-45	D2	3.50
2708-45	D2	3.25
2716-35	D1	4.50
2716-45	D1	3.50
2716-3	D1	4.50
2732-35	D1	4.58
2732-45	D1	3.75
2764-30	D1	3.92
2764-250NS TI		3.92
2764-250NS BBC		5.95
2564-30	D2	6.00
27128-30	D2	24.50

Buffers

81LS95	0.95	
81LS96	0.95	
81LS97	0.95	
81LS98	0.95	
8T26A (6880AP)	0.78	
8T28A (6889)	0.78	
8T35 (6885)	0.78	
8T97A (6887)	0.78	
8T98 (6888)	0.78	
6821	D3	1.31
6840	D4	3.92
6843L	D3	20.88
6845	D5	5.88
6850	D2	1.31
6862		0.00
6871-A1		14.17
68488	D2	7.78
6875	D2	7.13
68800	D7	4.30
68B09	D6	9.96
68B21	D3	1.88
68B10	D1	1.80
68B40	D4	5.50
68B50	D2	1.83
MC68B54P		7.75

Data Convertors

ZN435	D1	3.70
UPD7002	D1	4.65
ZN425E-8	D1	3.13
ZN426E-8	D1	1.67
ZN427E-8	D1	5.75
ZN428E-8	D1	4.38
ZN429E-8	D1	1.33
ZN432CJ-10	D1	25.98
ZN432E-10	D1	10.88
ZN433CJ-10	D1	20.98
ZN440	D1	47.43
ZN447	D1	6.70
ZN448	D1	5.75
ZN449	D1	2.35
ZN441	D1	40.32

Crystals

A111B 1MHz	4.22
A112A 1.008MHz	4.12
A113A 1.0432MHz	2.88
A116A 2.4576MHz	1.00
A169A 3.6864MHz	1.55
A120B 4MHz	0.85
A132A 6MHz	0.72
A140A 8MHz	1.00
A173A 9.8304MHz	1.40
A182A 19.6608MHz	2.07

UHF Modulators

UM1111 6MHz	2.17
UM1233 8MHz	3.25

Floppy Disc Controllers

8271P	53.33	
FD1771P	D5	21.25
FD1791	D6	17.00
FD1793	D6	17.00
FD1795	D6	24.35
FD1797	D6	24.35
WD1691	D2	12.00
WD2143.01	D2	7.90

Prices: all prices exclude V.A.T. and carriage. Please add these to your order.

All prices correct at time of going to press.

Prices: all prices exclude V.A.T. and carriage. Please add these to your order.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

All prices correct at time of going to press.

5500 Family

6502	D3	4.40
6502A	D3	4.67
6520	D1	2.67
6520A	D1	2.80
6522	D5	3.47
6522A	D5	4.40
6532	D2	5.33
6532A	D2	5.87

Linear & Interface Devices

6402		6.00
AY3-1015	D2	2.92
AY3-1270		6.50
AY3-8910	D6	4.48
AY5-3600	D2	7.37
DP8304	D1	1.92
L203		0.80
LF398		3.17
LM301 AN		0.24
LM308AN		0.73
LM308N		0.47
LM311N		0.84
LM319		2.23
LM324N		0.32
LM339N		0.37
LM348N		0.53
LM358N		0.28
LM393N		0.34
LM725CN		1.33
LM741CP		0.18
LM747CP		0.48
LM748CP		0.22
MC1413P	D1	0.66
MC1416	D1	0.66
MC1458CPL		0.26
MC1495L		7.13
MC1496P		0.65
MC1723P		0.32
MC3242A		5.25
MC3302P		0.40
MC3340P		1.97
MC3357P		1.56
MC3423PL		0.67
MC3441AP		2.40
MC3446AP	D1	2.40
MC3447P		3.58
MC3448AP	D1	3.32
MC3470P		5.23
MC3480P	D5	6.47
MC3497P	D1	1.50
MC14411	D1	8.52
MC14412		11.87
NE555P		0.19
NE556CP		0.45
RO3-2513L	D1	7.82
RO3-2513U	D1	7.82
SN75107BN		0.58
SN75110AN		0.68
SN75150P		0.72
SN75154N		0.87
SN75159N		1.19
SN75160AN		2.15
SN75161AN		2.35
SN75162AN		3.31
SN75172NG		1.64
SN75173N		1.21
SN75174		1.64
SN75175		1.21
SN75182		0.82
SN75183		0.62
SN75188		0.44
SN75189		0.44
SN75451BP		0.24
SN75452BP		0.24
SN75453BP		0.24

SN75454BP

SN75468N	1.08
SN75491AN	0.46
SN75492AN	0.61
TL010CP	0.38
TL061CLP	0.28
TL062CP	0.47
TL064CN	0.89
TL066CP	0.28
TL071CP	0.28
TL072CP	0.47
TL074CN	0.91
TL081CP	0.24
TL082CP	0.41
TL084CN	0.85
TL091CP	0.41
TL092CP	0.60
TL094CN	1.37
TL487CP	0.55
TL489CP	0.55
TL494CN	1.66
TL496CP	0.30
TL507CP	1.02
ZN450E	5.25
ZN451E	6.38
ZN451KIT	25.65

DIL Sockets

Pin	Tin	Gold W/W
8	0.10	0.24 0.58
14	0.12	0.28 0.77
16	0.13	0.32 0.86
18	0.16	0.32 1.08
20	0.17	0.41 1.23
22	0.17	0.48 1.31
24	0.20	0.63 1.44
28	0.23	0.57 1.59
40	0.33	0.99 1.96

ZIF Sockets

24 Pin	5.80
28 Pin	6.35
40 Pin	8.45

Data sheets are available on items marked D.

Prices are as follows
D1 0.75 D5 2.50
D2 1.00 D6 3.00
D3 1.25 D7 4.00
D4 2.00

A full range of the following products is carried in stock and is listed in our FREE catalogue

- ★ 74LS Series TTC
- ★ 4000 Series CMOS
- ★ TI Bipolar Memories
- ★ 9900 Series Micros
- ★ Crystals
- ★ IDC Card Edge & D-Type Connectors
- ★ Dip Jumpers
- ★ Monochrome & Colour Monitors (NEC & KAGA)
- ★ Eprom Programmers
- ★ Erasable
- ★ Custom Cable Assemblies

SPECIAL OFFER! SPECTRUM 32K UPGRADE KIT £24.95

Carriage Orders up to £199 are sent by 1st class post and £200+ by Securcor

£0-£100 0.50 £100-£199 1.25 £200+ 5.00 by Securcor

Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice

Quantity Discounts are available on many products, please ring for details.

Official Orders are welcome from Education Establishments, Government Bodies and Public Companies

Credit Accounts are available to others subject to status. Payment is due strictly net by the 15th of the month.

Credit Cards are accepted (Access and Visa) for telephone and postal orders and NO SURCHARGE is made

Out of stock items will follow automatically, at our discretion, or a refund will be given if requested



SPECIAL TELEPHONE NUMBER FOR FAST, IMMEDIATE SERVICE, TELEPHONE YOUR ORDER TO: DISS (0379) 898751

For FREE CATALOGUE post to Midwich Computer Company Limited, Rickinghall House, Hinderclay Road, Rickinghall, Suffolk IP22 1HH

Name


Address

Telephone

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I. L. P., PRICE.

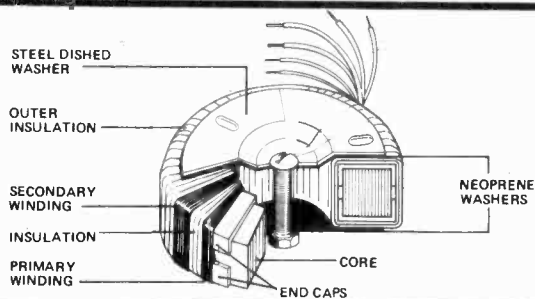Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm 0.35Kg Regulation 19%	50 VA 80 x 35mm 0.9Kg Regulation 13%	120 VA 90 x 40mm 1.2Kg Regulation 11%	225 VA 110 x 45mm 2.2Kg Regulation 7%	500 VA 140 x 60mm 4Kg Regulation 4%
SERIES SECONDARY RMS No Volts Current	2x010 6+6 4.16 2x011 9-9 2.77 2x012 12+12 2.08 2x013 15+15 1.66 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83	4x010 6+6 10.00 4x011 9-9 6.66 4x012 12+12 5.00 4x013 15+15 4.00 4x014 18+18 3.33 4x015 22+22 2.72 4x016 25+25 2.40 4x017 30+30 2.00 4x018 35+35 1.71 4x019 40+40 1.50 4x020 45+45 1.33 4x021 50+50 1.20 4x022 60+60 1.00	6x012 12+12 9.38 6x013 15+15 7.50 6x014 18+18 6.25 6x015 22+22 5.11 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x019 40+40 2.81 6x020 45+45 2.50 6x021 50+50 2.25 6x022 60+60 2.00 6x023 70+70 1.75 6x024 80+80 1.50	8x016 25+25 10.00 8x017 30+30 8.33 8x018 35+35 7.14 8x019 40+40 6.25 8x020 45+45 5.56 8x021 50+50 5.00 8x022 55+55 4.54 8x023 60+60 4.07 8x024 65+65 3.70 8x025 70+70 3.33 8x026 75+75 3.00 8x027 80+80 2.72 8x028 85+85 2.47 8x029 90+90 2.22 8x030 95+95 2.00
(encased in ABS plastic)	80 VA 90 x 30mm 1Kg Regulation 12%	160 VA 110 x 40mm 1.8Kg Regulation 8%	300 VA 110 x 50mm 2.6Kg Regulation 6%	625 VA 140 x 75mm 5Kg Regulation 4%
30 VA 70 x 30mm 0.45Kg Regulation 18%	3x010 6+6 6.64 3x011 9-9 4.44 3x012 12+12 3.33 3x013 15+15 2.66 3x014 18+18 2.22 3x015 22+22 1.81 3x016 25+25 1.60 3x017 30+30 1.33 3x018 35+35 1.11 3x019 40+40 0.94 3x020 45+45 0.80 3x021 50+50 0.72 3x022 60+60 0.60	5x011 9-9 8.89 5x012 12+12 6.66 5x013 15+15 5.33 5x014 18+18 4.44 5x015 22+22 3.63 5x016 25+25 3.20 5x017 30+30 2.66 5x018 35+35 2.28 5x019 40+40 2.00 5x020 45+45 1.78 5x021 50+50 1.57 5x022 60+60 1.39 5x023 70+70 1.22 5x024 80+80 1.08	7x013 15+15 10.00 7x014 18+18 8.33 7x015 22+22 6.82 7x016 25+25 6.00 7x017 30+30 5.00 7x018 35+35 4.28 7x019 40+40 3.75 7x020 45+45 3.33 7x021 50+50 3.00 7x022 60+60 2.67 7x023 70+70 2.33 7x024 80+80 2.00 7x025 90+90 1.78 7x026 100+100 1.57	9x017 30+30 10.41 9x018 35+35 8.92 9x019 40+40 7.81 9x020 45+45 6.94 9x021 50+50 6.25 9x022 55+55 5.68 9x023 60+60 5.11 9x024 65+65 4.63 9x025 70+70 4.17 9x026 75+75 3.81 9x027 80+80 3.46 9x028 85+85 3.12 9x029 90+90 2.79 9x030 95+95 2.48

Why a Toroid?

- * Smaller size & weight to meet modern 'slimline' requirements.
- * Low electrically induced noise demanded by compact equipment.
- * High efficiency enabling conservative rating whilst maintaining size advantages.
- * Lower operating temperature.

Why ILP?

- * Ex-stock delivery for small quantities.
- * Gold service available. 21 days manufacture for urgent deliveries.
- * 5 year no quibble guarantee.
- * Realistic delivery for volume orders.
- * No price penalty for call off orders.

Prices including P&P and VAT

VA	Size	£	VA	Size	£
15	0	7.43	160	5	12.90
30	1	8.08	225	6	16.30
50	2	10.10	300	7	18.55
80	3	10.81	500	8	25.73
120	4	11.73	625	9	31.63

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.
Trade - We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 3
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 54778 Telex: 965780



ELECTRONICS LTD.

WW - 014 FOR FURTHER DETAILS

TEST EQUIPMENT

Marconi TF2002B 10KHz-88MHz Signal Generator.....	£795
Fluke 8600A 4 1/2 digit Digital Multimeter.....	£150
Fluke 8020A 3 1/2 digit Digital Multimeter (Unused).....	£60
Case for Fluke 8020A (Unused).....	£12
Philips PM 2554 Millivoltmeter.....	£75
Sullivan AC Test Sets.....	£150
Philips 2522A Digital Multimeter.....	£145
Sanwa Multimeters.....	£10
Pantec 'Electro' Multimeters.....	£20
25A/600 Volt Clampmeters.....	£10
Houston DP10 Incremental XY Plotter.....	£175
Hewlett-Packard 9815A Desk Top Computer with manuals.....	£195
Advance OS1000B 20MHz. Dual Trace Oscilloscope.....	£95
Leader LB0510B 4MHz. Single Channel Oscilloscope (New).....	£95
Leader Lfr 5600 Frequency Response Recorder.....	£565
J. J. Lloyd PL100 X-Y Plotter with spare amplifier.....	£250
Hewlett-Packard 9815A Desk Top Computer with manuals.....	£195
Hewlett-Packard Directional Couplers 940-1900 MHz (New).....	£150
Syston Donner 6250A 50MHz. Timer Counter.....	£135
Syston Donner 7344A 4 1/2 digit DMM IEEE Interfaced.....	£195
Pecker 5000A Prom Programmers.....	£250
Tektronix 191 Constant Amplitude Generators.....	£115
Tektronix 106 Fast rise time Pulse Generators.....	£95
Tektronix Amplitude Calibrators.....	£95
R. & S. SMAF 300MHz. AM/FM Signal Generator.....	£195
Hewlett-Packard 181C Storage Oscilloscope with 1803A and 1821A.....	£295
DEC PDP8- Computer in rack with tape reader and Cartrifile.....	£195
DEC PDP8- Computer.....	£100
Tektronix 7603 100MHz. Mainframe.....	£750
Tektronix 7A18 Dual Trace 75MHz. Plug in.....	£225
Tektronix 7B53N Timebase Plug in.....	£115
Tektronix 7B50A Timebase Plug in.....	£115
Tektronix 7D01 Logic Analyser Plug in.....	£995
Tektronix DF1 Display Formatter.....	£399
Tektronix 7313 25MHz. Storage Mainframe.....	£895
Mitsubishi Dual Density Dual Sided Disk Drives 5 1/4" As new.....	£150
Mitsubishi Dual Density Dual Sided Disk Drives 8" As new.....	£199
Honeywell 20Megabyte Disk Drive with interface board.....	£375
5 1/4" Winchester Disk Drive 20 Megabyte.....	£395
Telegroup S64 10 MHz. Single Channel Oscilloscopes.....	£75
H.P. P.I's for 5245L Counter. 5267A, 5265A, 5263A.....	each £50
Telegroup D61 10 MHz. Dual Trace Oscilloscopes.....	£125
Wavetek VHF/UHF Sweep Generators 950MHz.....	£215
Telonic 1006A Sweep Generator.....	£215
Texscan Sweep Generators.....	£215
Telegroup D52 Dual Channel Oscilloscopes.....	£60
Telonic 121 12" Display Oscilloscope.....	£175
Leader 150MHz. AM Signal Generator (New).....	£50
Leader Audio Signal Generator (New).....	£70
Leader Video Head Checker VHS or Beta (New).....	£45
Avometer Model 8 Mark 5 with leads and case.....	£75
Avometer Model 8X Panclimatic with leads.....	£60
Avometer Model 7X with leads.....	£50
Model VB Megger with case.....	£50
Hewlett-Packard 141A with 1410A and 1425A Sampling Plug ins.....	£199
Racal-Dana 9905 Timer Counter.....	£199
Hewlett-Packard 8002A Pulse Generator.....	£195
Hewlett-Packard 182C with 1801A and 1821A Plug ins.....	£295
R. & S. Polyskop II.....	£295


TIMEBASE Q-TEQ

94 ALFRISTON GARDENS, SHOLING, SOUTHAMPTON SO2 8FU
TELEPHONE: 431323 (0703)
Callers welcome. Access/Barclaycard Telephone your order



WW - 052 FOR FURTHER DETAILS

METER PROBLEMS?

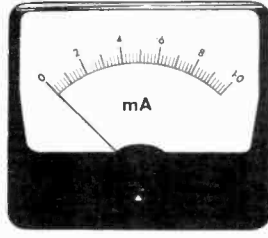

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:
HARRIS ELECTRONICS (London)
138 GRAY'S INN ROAD, W.C.1 Phone: 01-837 9737
Telex: 892301 HARTRO G

WW - 026 FOR FURTHER DETAILS



Audio Measuring Instruments,
Audio Amplifiers, Loudspeakers and
Loudspeaker Components for the
professional and enthusiast

RADFORD AUDIO LTD.

10 BEACH ROAD
WESTON-S-MARE, AVON BS23 2AU
TEL. 0934 416033

WW - 024 FOR FURTHER DETAILS

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished **DIABLO/DRE** series 30 2.5 Mb disk drives.
DEC RK05, NOVA, TEXAS compatible.
Front load. Free stand or rack mount
Exchangeable type (via lid removal)
me3029 PSU unit for 2 drives
DIABLO/DRE 44-4000A/B 5+5 ex stock from 1000's of spares for £30, 4000, 3200, HAWK ex stock. Plus in house repair, refurbishing service. Call for details or quotation.

£550.00
£295.00
£125.00

£995.00

SOLID STATE SWITCHES

Matchbox size solid state switch type **IR D2402** enables on off control of 240 V AC loads up to 600 watts, direct from your micro etc. Fully isolated 3-32 v DC input with zero voltage switching. Complete with data £6.99 + pp
250,000 other relays **EX STOCK** call for details.

COOLING FANS

Keep your hot parts **COOL** and **RELIABLE** with our range of **BRAND NEW** professional cooling fans.
ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95
BUHLER 69.11.22, 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. **OUR PRICE ONLY £12.95** complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested **EX EQUIPMENT** 240 v at £6.25 or 110 v at £4.95 or **BRAND NEW** 240 v at £10.50. 1000's of other fans **EX STOCK**. Call for Details. Post & Packing on all fans £1.60

HOT LINE DATA BASE DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base. 1000's of stock items and one off bargains.
ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit word, no parity.
01-679 1888

MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference.
SD5A As recommended by Z X81 news letter, matchbox size up to 1000 watt load £5.95
L2127 compact completely cased unit with 3 pin fitted socket. Up to 750 watts £9.99

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous **DEC PDP8** computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on All front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. **Give your system that professional finish for only £249.95 + Carr.** Dim. 19" wide 16" deep 10.5" high. Useable area 16" w 10.5" h 11.5" d. Also available **LESS PSU**, with **FANS** etc. Internal dim. 19" w, 16" d, 10.5" h. £19.95. Carriage & insurance £9.50.

SAVE £250 SUPER PRINTER SCOOP BRAND NEW CENTRONICS 739-2



ONLY £199

The "Do Everything Printer" at a price that will NEVER be repeated. Standard **CENTRONICS** parallel interface for direct connection to **BBC, ORIC, DRAGON** etc. Superb print quality with full pin addressable graphics and 4 type fonts plus **HIGH DEFINITION INTERNAL PROPORTIONAL SPACED MODE** for **WORD PROCESSOR** applications. 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available **ONLY** from **DISPLAY ELECTRONICS** at the ridiculous price of **ONLY £199.00 + VAT** Complete with full manual etc. Limited quantity - Hurry while stocks last.
Options: interface cable (specify) for **BBC, ORIC, DRAGON** or **CENTRONICS 36** way plug £12.50. Spare ribbon £3.00 each. **BBC** graphics screen dump utility program £8.50.

VIDEO MONITORS

5" CASED Superb little unit made by **HITACHI** in ergonomically designed free standing case. Very high definition will play small but readable 132 columns wide! 12v DC opp. @ 800 ma, so ideal for mobile use. Supplied in **AS NEW** condition complete with data. Composite 75 ohm vid in. Black & White CRT £45.00 or Green CRT £55.00 Carr & Ins £5.00.
12" CASED. Made by the British **KGM Co**. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with **ON-OFF, BRIGHTNESS** and **CONTRAST** controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via **SO239** socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**
24" CASED. Again made by the **KGM Co** with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs, shops etc. Supplied in a used but working condition. **ONLY £55.00 PLUS £9.50 CARR & INS.**

8" WINCHESTERS

BASF 6172 23 mb 8" winchester disk drive. Complete unit consists of sealed cavity with 3 x 8" platters and CPU based control logic on 3 pcb's. Multiplexed i/o with the **BASF "DISK BUS"** interface is via a single 40 way cable. Units have been carefully removed from believed working equipment - but at the staggering price of **ONLY £125.00** are sold without guarantee. Supplied complete with 200 + page tech manual. Additional +5V DC, -12VDC, +24VDC £65.00 Carriage & Ins £10.00

GE TERMIPRINTER

A massive purchase of these desk top printer - terminals enables us to offer you these quality 30 cps printers at a **SUPER LOW PRICE** against their original cost of over £1000. Unit comprises of full **QWERTY**, electronic keyboard and printer mech with print face similar to correspondence quality typewriter. Variable forms tractor unit enables full width - up to 13.5" 120 column paper, upper - lower case, standard **RS232** serial interface, internal vertical and horizontal tab settings, standard ribbon adjustable baud rates, quiet operation plus many other features. Supplied complete with manual. Guaranteed working **£130.00** or untested **£85.00**, optional floor stand £12.50 Carr & Ins £10.00.

TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR + VAT
Fully fledged industry standard **ASR33** data terminal. Many features including **ASCII** keyboard and printer for data I/O auto data detect circuitry. **RS232** serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order.
Options: Floor stand **£12.50 + VAT**
KSR33 with 20ma loop interface **£125.00 +**
Sound proof enclosure **£25.00 + VAT**

PROFESSIONAL KEYBOARD OFFER

An advantageous purchase of brand new surplus allows a great **QWERTY**, full travel, chassis keyboard offer at fractions of their original costs.
ALPHAMERIC 7204/60 full **ASCII** 60 key, upper, lower + control key, parallel TTL output plus strobe. Dim 12" x 6" x 5 + 5 - 12 DC. **£39.50**.
DEC LA36 Unencoded keyboard with 67 quality, **GOLD**, normally open switches on standard X, Y matrix. Complete with 3 LED indicators & i/o cable - ideal micro conversions etc. pcb DIM 15" x 4.5" **£20.95** Carriage on keyboards £3.00.

SOFTY 2

The amazing **SOFTY 2**. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator. Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00** pp £1.95 Data sheet on request

DATA MODEMS

Join the communications revolution with our range of **EX TELECOM** data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the **CCITT** tone spec. With **RS232** i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 2B "Hackers Special" fully fledged up to 300 baud full duplex, **ANSWER** or **CALL** modes. **AUTO ANSWER**. Data i/o via standard **RS232 25 way 'D'** socket. Just 2 wire connection to comms line. Ideal networks etc. Complete with data, tested, ready to run at a **NEW SUPER LOW PRICE** of **ONLY £65.00 + VAT + Carr.**
MODEM 20-1 Compact unit for use with **MICRONET, PRESTEL** or **TELECOM GOLD** etc. 2 wire direct connect. 75 baud transmit 1200 baud receive. Data i/o via **RS232 'D'** socket. Guaranteed working with data **£49.95**
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit **£130.00**
DATel 4800 sync service. **RACAL** type **MPS4800** ex **TELECOM** good condition. **£395.00 + VAT.**
NEW DLS12123 Multi Standard modem selectable V21 300-300 bps, V23 75-1200, V23 1200-75 full duplex. Or 1200-1200 half duplex modes. Full auto answer via modem or CPU. LED status indicators. **CALL** or **ANS** modes. Switchable **CCITT** or **BELL 103 & 202**. Housed in **ABS** case size only 2.5" x 8.5" x 9". **£286.00 + VAT.**
For further data or details on other **EX STOCK** modems contact sales office.
Carriage on all modems £10.00 + VAT.

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter BRAND NEW AT ONLY £499 + VAT



Made to the very highest spec the **TEC Starwriter FP1500-25** features a heavy duty die cast chassis and **DIABLO** type print mechanism giving superb registration and print quality. Micro-processor electronics offer full **DIABLO/QUEM** command compatibility and full control via **CPM Wordstar** etc. Many other features include bidirectional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard **RS232** serial interface with handshake. Supplied absolutely **BRAND NEW** with 90 day guarantee and **FREE** daisy wheel and dust cover. Order **NOW** or contact sales office for more information.
Optional extras: **RS232** data cable **£10.00**. Tech manual **£7.50**. Tractor feed **£140.00**. Spare daisy wheel **£3.00**. Carriage & Ins. (UK Mainland) **£10.00**.

66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of **I.C.s**, Transistors, Relays, Caps, P.C.B.s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.
2.5kls **£4.25** + pp **£1.25** 5kls **£5.90** + **£1.80**
10kls **£10.25** + pp **£2.25** 20 kls **£17.50** + **£4.75**

SEMICONDUCTOR 'GRAB BAGS'

Mixed **Semls** amazing value contents include transistors, digital, linear, I.C.s triacs, diodes, bridge recs., etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed, 50+ **£2.95** 100+ **£5.15**.
TTL 74 Series A gigantic purchase of an "across the board" range of 74 **TTL** series I.C.s enables us to offer 100+ mixed "mostly **TTL**" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ **£6.90** 200+ **£12.30** 300+ **£19.50**

DEC CORNER

MOSTEK CRT 80E Brand new dual eurocard, Z80 based **VT100 PLUS** emulator with graphics etc
BAT1-MB 3.5" Box, **PSU, LTC** **£385.00**
DLV11-J 4 x EIA interface **£310.00**
RK05-J 2.5 Mb disk drives **£650.00**
PDP1105 Cpu, Ram, i/o, etc. **£450.00**
RT11 ver. 3B doc kit **£70.00**
LA36 Decwriter **EIA** or **20 ma** **£270.00**
KLBJA PDP 8 async i/o **£175.00**
MIBE PDP 8 Bootstrap option **£75.00**
DILOG DQ100 **RK05 LSI 4 x RK05** disk controller **£450.00**
LAXX-NW LA180 **RS232** serial interface and buffer option **£230.00**
LAX34-AL LA34 tractor feed **£85.00**
1000's of **EX STOCK** spares for **DEC PDP8 PDP11 PDP15** & peripherals. Call for details. All types of Computer equipment and spares wanted for prompt **CASH PAYMENT**

ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum **BONA FIDE** account orders from Government depts., Schools, Universities and established companies **£20.00** Where post and packing not indicated please ADD **£1.00**. + **VAT** Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

32 Biggin Way, Upper Norwood, London SE19 3XF Telephone 01-679 4414 Telex 27924



WW - 038 FOR FURTHER DETAILS

Twilight locator

Construct your own aid to choosing suitable frequency bands for long distance radio communication. All you need is a globe.

Special pull-out

PW Radio Data—Part I, "ABBREVIATIONS". Most comprehensive listing of abbreviations frequently used by Radio Hobbyists. Ideal beginner's guide.

Feature articles


Orienteering by Radio!!
See how to build and use a Top-Band
Direction Finder.

Practical Wireless

THE RADIO MAGAZINE

March issue 90p in your Newsagents now

KONTAKT

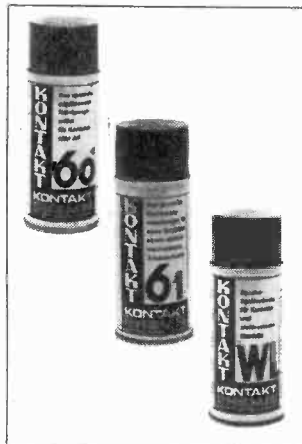

NEW from Kontakt

The capability and effect of compressed air in a handy can. TENSION 67 efficiently removes dust and deposits from electronic components, electronic and electrical apparatus, microscopes, medical equipment, cabinets, etc. Absolutely no spray residues. No compressed airline needed. With plug-in nozzle even blows around corners. Ready for use in the service kit.

Kontakt 60

Dissolves oxides and sulphides, removes dirt, oil, resin and traces of metal abrasion. Protects against erosion. Ensures perfect contacts.

Kontakt 61

Special cleaning, lubricating and anti-corrosion fluid for NEW (non oxidised) and specially sensitive contacts. An excellent lubricant for all electrical and electro-mechanical systems.

Spray Wash WL

A rapid cleaner for reliable washing and degreasing of electrical equipment and components. For removal of dirt, grease, oil, soldering residues and other impurities.

ALSO AVAILABLE:

A COMPLETE RANGE OF INDUSTRIAL AEROSOL SPRAYS

SK10 Soldering Lacquer, K75 Cold Spray, K70 Plastic Spray, K88 Oil Spray, K701 Vaseline Spray, K90 Video Spray, K33 Graphite Spray, K100 Antistatic Spray, K101 Fluid Spray and, of course, Positiv 20 positive photo resist for printed circuits.


Details from:

Special Products Distributors Ltd.

81 Piccadilly, London W1V 0HL
Tel: 01-629 9556. Telex: 28500 (answerback RACEN)
Cables: Speciproduct, London W1

WW - 073 FOR FURTHER DETAILS

APOLLO

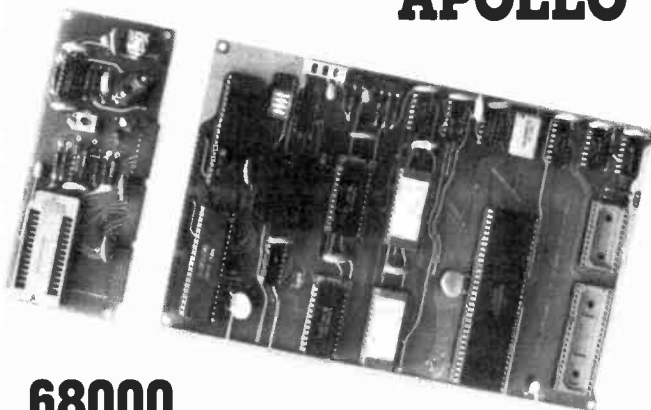

68000

Development system

Powerful 68000 runs at 10MHz without wait states. 16KB EPROM and 4KB fast static RAM, expandable. 24 line programmable parallel I/O port. RS232 programmable serial port. Comprehensive monitor in 2764 Eproms. Optional plug-in Eprom programmer card. Cross Assemblers for Z80 based microcomputers. Code can be developed downline loaded to 68000, debugged, and then written into Eprom.

- ★ 10MHz 68000 CPU Board £295 + VAT
- ★ EPROM PROGRAMMER card £95 + VAT
- ★ CROSS ASSEMBLER for Z80 hosts from £55 + VAT

APOLLO SOFTWARE. Tel: (0635) 201150

The Alley, Cold Ash, Newbury, Berkshire RG16 9NN

WW - 051 FOR FURTHER DETAILS

VISIT OR PHONE
OPEN 6 DAYS A WEEK
ALL STOCK ON DISPLAY

HENRY'S AUDIO ELECTRONICS

Electronics Specialists
Quantity Enquiries Invited


COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

THERMAL • MATRIX • LINE PRINTER

150 to 180 LPM • Full 96 CH ASCII • 40 CPL • 280 Dots P/L • Auto-underline • 50 Graphic Symbols • Back Space • Self Test • VU/HOR TABS • 7 x 10 Matrix • 4.4" Wide Paper • Bidirectional • 220/240V AC • Size Approx. 9.8 x 2.8 x 7.2" • SUITABLE FOR: TANDY • BBC • ORIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc. (Your enquiries invited).
Complete with 3 rolls paper
Incl VAT £69.95
List price approx. £187 with paper (UK C/P £1.05)



NEW LOW PRICE

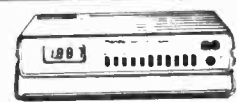

ALL MODELS 3 1/2 DIGIT UNLESS STATED

DIGITAL MULTIMETERS

Free carry case (rotary controls)
Carry case £2.95 (slide buttons)
HAND HELD
KD25C 13 range 0.2A DC 2 meg ohm £28.95
KD30C 16 range 10A DC 2 meg ohm £27.95
KD30C 26 range 1A AC/DC 20 meg ohm £33.50
KD55C 28 range 10A AC/DC 20 meg ohm £38.95
METEX 3000 30 range 10A AC/DC 20 meg ohm £37.95
6010 28 range 10A AC/DC 20 meg ohm £37.95
7030 As 6010 but 0.1% basic £47.50
K0615 16 range 10A DC 2 meg plus Hfe tester £39.95
DM2350 21 range 10A AC/DC 20 meg ohm miniature hand held auto range with case £62.95
Beckman T100 34 range 10A AC/DC 20 meg ohm £56.35
Beckman T110 As T100 plus Cont. test etc £67.85
DM3350 19 range 10A AC/DC 2 meg ohm autorange £49.95


SK6330 24 range P-B autorange 10A AC/DC buzzer, with case £90.85
Matrix (ITT) £77.00
MX522 21 range 10A AC/DC £178.25
MX522 24 range 10A AC/DC Plus continuity buzzer £109.25
MX575 4 1/2 Digit true RMS £201.25
BENCH MODELS
TM356 27 range LCO 10A AC/DC 20 meg £119.25
TM355 29 range LEO 10A AC/DC 20 meg £97.75
TM351 29 range LCO 10A AC/DC 20 meg £132.25
Optional carry case £6.84
TM45 1 1/4 digit LCO every facility (0.02%) £184.00
1503a 4 1/2 digit LCO every facility (0.05%) £171.00
1503Ha 0.03% basic version of above £189.00
1504 True RMS version £201.25

SANYO DM2112 HIGH RESOLUTION MONITOR

12" green display. Composite video. 1280 characters. Over 15 MBZ B/W. 240V AC 34 w. 16" x 11 1/2" x 12 1/2". Alphanumeric and Graphic display.
Usually £89.95 - £99.95 Price **£69.95** (Incl VAT UK C/P & ins £2.05)



SAVE £20 TO £30

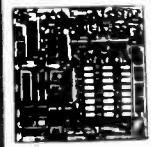


PROFESSIONAL SERIES COMPUTERS IN STOCK
GEMINI • GALAXY • NASCOM • 80-Bus multiboards.
Complete and part systems to suit your needs. Frames boards, power supplies, keyboards, disc systems, etc FOR THE PROFESSIONAL USER - SEND FOR DETAILS



DELUXE 69 KEY ASCII KEYBOARD

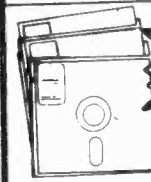General purpose, steel plate, output reddefinable, +5 and -12 volt, neg. strobe pulse, 4 user definable keys. Shift and control keys, etc.
Incl VAT £42.95
ALSO Type 756A £51 Type 771 £66 (Incl VAT)



3 NEW SOFTWARE PRODUCTS

MOIS (C) INTELLIGENT DIS ASSEMBLER For all CP/M based machines £57.50 (Incl VAT)
IWC HI-RES (C) For Gemini and others (please enquire) provides pseudo high resolution graphics. £17.25 (Incl VAT)
DISKPEN (C) Version 3. Lost cost word processor. For Gemini and others (please enquire) £57.50 (Incl VAT)
PLUS range of overlays available for Diskpen. Send for details of all above
(C) Copyright Cubegate Ltd. 1983. All rights reserved)

I.T.T. 2020 CABINET

Complete PROFESSIONAL Case beautifully constructed with cut out for one CHERRY keyboard plus ample room to house a COMPLETE SYSTEM and power supply. Complete with fittings (Case top detachable). Units in silver grey in colour. Robust construction. Sloping front with side ventilation. Ideal for NASCOM, ACORN, TANGERINE or your own system. Size 18" x 15" x 4 1/2" (front slopes).
£27.50 (Incl VAT UK C/P £2.50)



FREQUENCY COUNTERS

MET - TF series UK made PFM 200A 200 MHz hand held pocket 8 digit LED with batteries £78.93
MET Series, 8 digit LED with AC Adaptors
100 100 MHz 2 ranges £102.35
600 600 MHz 3 ranges £132.35
1000 1 GHz 3 ranges £182.85
TFD40 8 digit LCO 40 MHz with batteries £138.00
TF200 8 digit LCO 200 MHz with batteries £186.75
Optional carry case £6.84 AC adaptor £7.90
8110A 8 digit LED 100 MHz £90.85
8610E 9 digit LED 600 MHz £125.35
8000B 8 digit LED 1 GHz £171.35
8500E 9 digit LED 1.5 GHz £274.85

COMPUTER POWER SUPPLY

Switched mode, stabilised, self protecting S/C protected etc. 220/240V AC -5V 3.3A -12V 2.4A 40% cycle -5V 0.5A -12V 0.5A Suitable Apple replacement
£57.50 (Incl VAT UK C/P £1.50)

PRESTEL ADAPTOR

3 card set with data etc (P/S +/- 12V and +5V) £69.95 (Incl VAT)

CHERRY ADD-ON KEYPAD

16 button pad non-encoded £5.95

MODEM CARD

BT approved ready assembled unit with data and accessories £39.95 (Incl VAT)

ELECTRONIC INSULATION TESTER

YF501 500V/0-100m with carry case Large range stocked. Ask for leaflet £68.00

OSCILLOSCOPES

Full specification any model on request. SAE by post.
HM Series NAMEG: SC THANDAR: CS TRIO: 3' CROTECH: W HITACHI SINGLE TRACE UK C/P £3.00
3030 15 MHz 5mV, 95mm tube plus component tester £177.10
SC110A Miniature 10 MHz battery portable Post free Nicads £12.50 AC adaptor £7.99
HM10310 MHz 2mV, 6 x 7 display plus component tester C/P £3.00
DUAL TRACE UK C/P £4.00
HM203/4 Dual 20 MHz plus component tester £303.60
HM605 Dual 80 MHz, 1mV £580.00
CS1562A Dual 10 MHz (List £321.00) £275.50
3132 Dual 20 MHz + component tester £235.45
CS1566A Dual 20 MHz All facilities (List £401.35) £349.50

SIGNAL GENERATORS

(220/240V AC) (UK C/P £1.00)
FUNCTION: All sine/square/triangle/TTL etc.
TG101 0.02HZ-200KHZ £120.75
TG102 0.2HZ-2 MHz £178.75
PULSE
TG105 Various facilities 5 Hz-5 MHz £120.75
AUDIO: Multiband Sine/Square
LAG27 10 KHz to 1 MHz £106.95
AG202 20 Hz to 200 KHz (List £94.50) £94.50
LAG1 20A 10 KHz-1MHz Low Distortion RF £166.75
SG402 100 KHz to 30 MHz (List £79.50) £79.50
LSG17 100 KHz to 150 MHz (450 MHz HARM) £108.25

MULTIMETERS (UK C/P 65p)

M200 20K/volt, 30 ranges AC/DC 20 KHz (List £21.85) £22.95
HM102BZ 20K/V 10A DC 22 range + cont. buzzer £13.50
HC1015 10K/V 15 range pocket meter £8.50
TMK500 23 ranges 30K/V 12A DC plus cont. buzzer £23.95 £11.95
NH56R 20K/V 22 range pocket £23.95
B30A 26 range 30K/V 10A AC/DC overload protection, etc £39.95
360TR 23 range 100 K/V. Large scale 10A AC/DC plus Hfe £39.95
AT2100 10A AC/DC 31 range 100 K/V deluxe £33.50
AT1020 18 range 20K/V. Deluxe plus Hfe tester £21.00
YN360TR 19 range 20K/V plus Hfe tester £13.95
Matrix Professional multimeters in-stock 3 models from £74.75

VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP241 0/12/24V 0/1A £35.00
PP243 3 amp version £32.90
230M 0/30V 1A Twin meter £99.50

LOGIC PROBES

LP10 10 MHz £22.95
DLP50 50 MHz with carry case and accessories £49.95

HIGH VOLTAGE METERS

Direct reading 0/40 KV 20K/Volt £28.00 (UK C/P 65p)
Also 0/30, 0/45KV version £39.95

DIGITAL CAPACITANCE METER

0.1 pF to 2000 mfd LCO B Ranges (UK C/P 65p) £28.95

TOROIDAL TRANSFORMER
100 watts isolation 230/240 V AC plus 8-0-8V 4A 15-0-15V 0.645A 30V 0.16A Size approx 4" dia x 1 1/2"
£7.95 (UK C/P 75p)

RADIO INTERFERENCE FREE

24 hr 230/240V AC digital clock movements with alarm by Braun £4.50 (UK C/P 50p)

CENTAUR FANS
CU7983 115V 50/60HZ 12/13W Impedance protected fuse 2 in series for 230V/4, x 4, x 1.
Two for £10.00 (UK C/P 70p)
220/240V as new £5.50 each (UK C/P 50p)

POCKET RADIATION DETECTORS
Dosimeter for Gamma and X-Rays 0-5r
£6.95
Quantities available

ASTEC UHF MODULATORS

UM1233 cased for computers, etc. £3.50 (UK C/P 40p)

CASSETTE MECHANISMS
Fitted counter, motor, record and erase heads, solenoid, etc. Brand new available 6V DC or 12V DC (state which)
£5.95 (UK C/P 65p)

TRANSISTOR TESTER

Direct reading PNP/NPN, etc. TCI £22.95 (UK C/P 65p)

DIGITAL THERMOMETER

TH301 LCO -50 C to +750 with thermocouple £68.43

TOROIDAL POWER SUPPLY

12V and 5V 1 amp max stabilised 6" x 2" x 1 1/2"
£5.95 (UK C/P 65p)

ULTRASONIC TRANSDUCERS

with cables, 40 KHZ £2.95 per pair (UK C/P 40p)

MILLAR MODULES

(UK C/P 65p per 1-3) pr £5.75
LP1171 IF and LP1179 AM/FM Tuner £5.00
LP1186 Varicap Tuner £2.50
LP1157 AM Tuner

HM204 Dual 20 MHz plus component tester sweep delay

£419.75

HM705 Dual 70 MHz sweep delay

£676.00

V212 Dual 20 MHz

£399.25

V422 Dual 40 MHz plus extra facilities

£391.00

V203F Dual Trace 20 MHz sweep delay

£586.50

V353F Dual 35 MHz Sweep delay

£408.25

V134 Dual Trace 10 MHz storage

£569.25

All HITACHI, CROTECH & TRIO MODELS AVAILABLE

OPTIONAL PROBE KITS • With probes £1092.50
X1 £7.95 X10 £9.45 X11 £10.50 X100 £12.95
With carry case (UK C/P 65p) £29.95

AC CLAMP METER

ST300 0/300A, 0/600 V AC 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £29.95

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • COMMERCIAL • EDUCATIONAL

Official orders welcome. (Subject to confirmation)

FREE CATALOGUES

Please state type required. Send large SAE (20p UK) Test Equipment Computers Audio Communications Components Schools, Colleges, Companies etc. Export Free on Written Request

ORDER BY PHONE OR BY POST OR CALL IN AND SEE FOR YOURSELF



Order by Post with CHEQUES/ACCESS/VISA or you can telephone your orders
CREDIT FACILITIES AVAILABLE (Tricity Finance) Ask for details.

HENRY'S 404-406 Edgware Road, London, W2 1ED
Computers 01-402 6822 • Equipment 01-724 0323 • Components 01-723 1008
AUDIO ELECTRONICS 301 Edgware Road, London, W2 1BN
01-724 3564
All mail to Cubegate Ltd, 1st floor, 406 Edgware Road, London, W2 1ED

WW - 044 FOR FURTHER DETAILS

BBC Micro Computer System OFFICIAL DEALER

Please phone for availability



Software from ACORNSOFT/
PROGRAM POWER/GEMINI in
stock

- BBC Model B £348
B + Econet £389
B + DFS £409
B + DFS + Econet £450
Carr £7
Model A to Model B
Upgrade Kit £75
Installation £15
LANGUAGE ROMS
BCPL Rom + Disc + Manual £87
PASCAL-T Rom £44
WORD PROCESSOR ROMS
VIEW 16k Rom £52
WORDWISE 8k Rom £32
Carr £1.50
UTILITY ROMS
BBC Ultracalc £65
EXMON £24 DISC DOCTOR £28
FX Dump £15 Graphics ROM £30
Termi ROM £29

FLOPPY DISC INTERFACE £84 & £15 installation

BBC COMPATIBLE DISC DRIVES

All drives are supplied with manual, form disc and cables.

Single Drive: 100k £150; 200k £215*; 400k £235.
Single Drive with PSU: 100k £185; 200k £260; 400k £275.
Dual Drive with PSU: 2 x 100k £330; 2 x 200k £450*;
2 x 400k £495.

*These drives are switchable between 40/80 tracks.
40/80 Switch Module for 1 x 400k and 2 x 400k Drive
£32.

DISKETTES: Packet of 10
40 track SSSD £15 40 track DSDD £22
80 track SSDD £24 80 track DSDD £26
Carriage £2/box.

FLOPPICLENE Drive Head Cleaning Kit £14.50

Phone or send for our BBC leaflet

CASSETTE RECORDERS

SANYO DR101 Data Recorder £34 + £2.50 carriage
BBC Tape Recorder £28.50 + £2.50 carriage
Cassette Lead £3 + £1 carriage
HOBBIT Floppy Tale £135 + £2.50 carriage
HOBBIT Zero Memory Option £25 + £1 carriage
Computer Grade C12 cassette 50p each. £4.50 for 10 £1 carriage

MONITORS


MICROVITEC 1431 14" RGB Std Res £215
MICROVITEC 1431P 14" RGB/PAL Std Res £249
MICROVITEC 1451 14" RGB Med Res £320
MICROVITEC 1441 14" RGB Hi Res £440
MICROVITEC 2031 20" RGB Std Res £287
KAGA VISION 12" RGB Std Res £230
KAGA VISION III 12" RGB Hi Res £385
KAGA 12" GREEN Hi Res £106
SANYO DM8112CX 12" Green Hi Res £99
All leads included. Carriage £7

TORCH Z80 DISC PACK

Your BBC computer can be converted into a business machine with the addition of a TORCH Z80 disc pack. The Torch pack with twin disc drive and the Z80 processor card greatly enhances the computer's data storage and processing capability. Z80 card comes complete with 64K RAM and a CP/M compatible operating system. In addition to BBC owner's user guide and a systems disc the package is supplied with PERFECT software package comprising of DATABASE, WORD PROCESSOR & SPREADSHEET and COMANEX, an interactive business management game. Complete Package for £738 + £8 carr.

PRINTERS & PLOTTERS

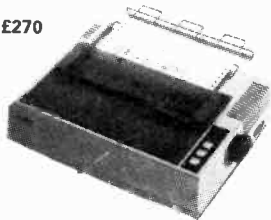EPSON FX80 £350. EPSON RX80 FT £270
EPSON FX-100 £555
NECPC80 23BE-N £310
SEIKOSHA GP 100A £170
SEIKOSHA GP 250X £199
SEIKOSHA GP 700A Colour £375
JUKI 6100 Daisy Wheel £365
MCP 40 Col Printer/Plotter £129
Colour Graphics Plotter A3 size £270
GRAFPAD Graphics Tablet £120
Carriage £7



ACCESSORIES

Parallel Printer Lead £10 + £1 carriage
Serial Printer Lead £8 + £1 carriage
Epson Serial Interface 2K £60 + £1 carriage
Epson Serial Interface £50 + £1 carriage
NEC Serial Interface £42 + £1.50 carriage
Epson Paper Roll Holder £17 + £1.50 carriage
FX80 Tractor Attachment £37 + £1.50 carriage
Paper Fanfold 2000 sheets £13.50 + £2.50 carriage

'TIME-WARP' REAL-TIME-CLOCK/CALENDAR

A low cost unit that opens up the full range of Real-Time applications. With its full battery backup, possibilities include an Electronic Diary, automatic document dating, precise timing and control in scientific applications, recreational use in games, etc - its uses are endless and are simply limited by one's imagination. Simply plugs into the user port - no specialist installation required - No ROMS. Supplied with extensive applications software. £29.

BBC EPROM PROGRAMMER

A fully self-contained Eprom Programmer with its own power supply, able to program 2516, 2716/32/32A/64/128 single rail Eproms.
★ Personality selection is simplified by a single rotary switch.
★ Programming voltage selector switch is provided with a safe position.
★ Warning indicator to show programming in progress.
★ Programmer can read, blank check, program and verify at any address/addresses on the EPROM.
★ Simple menu driven software supplied on cassette (transferable to disc).
★ Full editor with ASCII disassembler.
★ Programmer complete with cables, software and operating instructions: £79.50 + £2 p. & p.

BOOKS (no VAT; p&p £1)

Advanced User Guide (£2 p & p) £12.95
Assembly Lang Prog. for BBC £8.95
Assembly Lang programming on BBC
Micro by Ferguson and Shaw £7.95
Basic Prog. for BBC £5.95
BBC An Expert Guide £6.95
Easy Programming on BBC £5.95
Further Programming on BBC £5.95
Introducing BBC Micro £5.95
Programming the BBC £6.50
30 Hour Basic £5.95
35 Educational Programs £6.95
BBC Sound & Graphics £7.95
Creating Adventure Programs £6.95
Discovering Machine Code £6.95
Structured Programming £6.50
The Friendly Computer Book BBC £4.50
Beyond Basic BBC £7.25

Large number of other titles stocked

EPROM ERASERS

UV1T Eraser with a built-in timer and mains indicator. Built-in safety interlock to avoid accidental exposure to the harmful UV rays. It can handle up to 5 eproms at a time with an average erasing time of about 20 mins. £59 + £2 p&p.
UV1 as above but without the timer £47 + £2 p&p.
UV140 up to 14 Eproms £61.
UV141 as above but with timer £79.

PRODUCTION PROGRAMMER: P8000

P8000 provides reliable gang programming of up to 8 EPROMS simultaneously with device sizes up to 16k x 8 bytes. Devices supported range from 2704 to 27128 in single and three rail versions. Simple menu driven operation ensures easy eprom selection and reliable programming in minimum programming times. £695 + £6 carriage.

★★ ATTENTION ★★

All prices in this double page spread are subject to change without notice.

ACORN IEEE INTERFACE

This IEEE 488 standard interface is a general purpose system for exchanging digital data between a number of devices in a local area. The interface complies with the IEC 625-1 standard and can be connected to up to 14 other devices. Interface board is supplied complete with software in ROM, interconnecting cables, IEEE cable for connection to an external device and a comprehensive manual. £282.50 + £2.50 carr.

SMARTMOUTH

The 'infinite vocabulary' self-contained speech synthesiser unit. Uses only 5-10 bytes per word - no ROMs required - simply plugs into the user port. (Has Aux. Audio output skt.). Supplied with Demo/Development programs and simple software instructions, £37 + £2 p. & p.

NEW COMPREHENSIVE CATALOGUE AVAILABLE - PLEASE SEND FOR PRICE LIST

CONNECTOR SYSTEMS

I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header Plug	Receptacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

	No. of ways			
	9	15	25	37
MALE				
Solder	80p	105p	160p	250p
Angled	150p	210p	250p	365p
FEMALE				
Solder	105p	160p	200p	335p
Angled	165p	215p	290p	440p
Hoods	90p	85p	90p	100p
IDC 15-way plug	340p	Socket 400p		
IDC 25-way plug	385p	Socket 450p		

TEXTPOOL ZIF

SOCKETS	24-pin	£5.75
28-pin	£8.00	40-pin £9.75

DIL SWITCHES

4-way 70p	8-way 90p
6-way 85p	10-way 140p

JUMPER LEADS

24" Ribbon Cable with Headers				
	14-pin	16-pin	24-pin	40-pin
1 end	145p	165p	240p	350p
2 ends	210p	230p	345p	540p

24" Ribbon Cable with Sockets				
	20-pin	26-pin	34-pin	40-pin
1 end	160p	200p	280p	300p
2 ends	290p	370p	480p	525p

Ribbon Cable with D. Conn.	
	Female 550p
25-way Male	500p

RS 232 JUMPERS

(25-way D)		
24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female-Female	£10.00
24" Male-Male	£9.50
24" Male-Female	£9.50

DIL HEADERS

	Solder Type		IDC Type
	40p	100p	
14pin	40p	100p	
16pin	50p	110p	
24pin	100p	150p	
40pin	200p	225p	

AMPHENOL CONNECTORS

36-way plug Centronics Parallel Solder £5.25 IDC £4.95
36-way socket Centronics Parallel Solder £5.50 IDC £5.20
24-way plug IEEE Solder £5 IDC £4.75
24-way socket IEEE Solder £5

RIBBON CABLE

(Grey/meter)	
10-way	40p
16-way	80p
20-way	85p
26-way	120p
34-way	180p
40-way	180p
50-way	200p
64-way	280p

EURO CONNECTORS

DIN 41617	Plug	Skt
21-way	160p	165p
31-way	170p	170p
DIN 41612		
2x32-way St. Pin	220p	275p
2x32-way Ang. Pin	275p	320p
3x32-way St. Pin	260p	300p
3x32-way Ang. Pin	375p	350p

EDGE CONNECTORS

		0.1"'	0.156"'
2x12-way (Vic)	350p	-	-
2x18-way	-	140p	-
2x22-way	190p	240p	-
2x23-way	175p	-	-
2x25-way	225p	220p	-
2x28-way	190p	-	-
1x43-way	260p	-	-
2x43-way	365p	-	-
1x77-way	600p	-	-
S100 Conn			600p

TEST CLIPS

14-pin 275p	40-pin £6	16-pin £3
-------------	-----------	-----------

74 SERIES

7400	25p	74259	150p
7401	25p	74265	55p
7402	25p	74273	150p
7403	25p	74278	100p
7404	25p	74279	55p
7405	25p	74283	50p
7406	25p	74285	160p
7407	25p	74286	180p
7408	25p	74289	90p
7409	25p	74298	120p
7410	25p	74351	150p
7411	25p	74365A	48p
7412	25p	74366A	48p
7413	40p	74367A	48p
7414	60p	74368A	48p
7415	60p	74370A	48p
7416	60p	74390	90p
7417	60p	74393	150p
7418	60p	74490	120p

74LS SERIES

74LS00	25p	74LS275	175p
74LS01	20p	74LS279	180p
74LS02	20p	74LS280	46p
74LS03	20p	74LS283	50p
74LS04	20p	74LS290	55p
74LS05	20p	74LS292	90p
74LS06	20p	74LS293	50p
74LS07	20p	74LS297	90p
74LS08	20p	74LS298	90p
74LS09	20p	74LS299	200p
74LS10	20p	74LS321	240p
74LS11	20p	74LS322	240p
74LS12	20p	74LS323	240p
74LS13	20p	74LS324/624	403p
74LS14	20p	74LS348	150p
74LS15	20p	74LS348	150p
74LS16	20p	74LS352	70p
74LS17	20p	74LS353	70p
74LS18	20p	74LS356	175p
74LS19	20p	74LS363	180p
74LS20	20p	74LS364	180p
74LS21	20p	74LS366A	36p
74LS22	20p	74LS367A	36p
74LS23	20p	74LS368A	36p
74LS24	20p	74LS373	120p
74LS25	20p	74LS374	120p
74LS26	20p	74LS377	120p
74LS27	20p	74LS377	120p
74LS28	20p	74LS378	85p
74LS29	20p	74LS379	120p
74LS30	20p	74LS390	100p
74LS31	20p	74LS393	120p
74LS32	20p	74LS399	120p
74LS33	20p	74LS445	100p
74LS34	20p	74LS465	120p
74LS35	20p	74LS466	120p
74LS36	20p	74LS467	120p
74LS37	20p	74LS467	120p
74LS38	20p	74LS468	120p
74LS39	20p	74LS469	120p
74LS40	20p	74LS470	120p
74LS41	20p	74LS471	120p
74LS42	20p	74LS472	120p
74LS43	20p	74LS473	120p
74LS44	20p	74LS474	120p
74LS45	20p	74LS475	120p
74LS46	20p	74LS476	120p
74LS47	20p	74LS477	120p
74LS48	20p	74LS478	120p
74LS49	20p	74LS479	120p
74LS50	20p	74LS480	120p
74LS51	20p	74LS481	120p
74LS52	20p	74LS482	120p
74LS53	20p	74LS483	120p
74LS54	20p	74LS484	120p
74LS55	20p	74LS485	120p
74LS56	20p	74LS486	120p
74LS57	20p	74LS487	120p
74LS58	20p	74LS488	120p
74LS59	20p	74LS489	120p
74LS60	20p	74LS490	120p
74LS61	20p	74LS491	120p
74LS62	20p	74LS492	120p
74LS63	20p	74LS493	120p
74LS64	20p	74LS494	120p
74LS65	20p	74LS495	120p
74LS66	20p	74LS496	120p
74LS67	20p	74LS497	120p
74LS68	20p	74LS498	120p
74LS69	20p	74LS499	120p
74LS70	20p	74LS500	120p

74ALS SERIES

74ALS00	25p	74ALS275	175p
74ALS01	20p	74ALS279	180p
74ALS02	20p	74ALS280	46p
74ALS03	20p	74ALS283	50p
74ALS04	20p	74ALS290	55p
74ALS05	20p	74ALS292	90p
74ALS06	20p	74ALS293	50p
74ALS07	20p	74ALS297	90p
74ALS08	20p	74ALS298	90p
74ALS09	20p	74ALS299	200p
74ALS10	20p	74ALS321	240p
74ALS11	20p	74ALS322	240p
74ALS12	20p	74ALS323	240p
74ALS13	20p	74ALS324/624	403p
74ALS14	20p	74ALS348	150p
74ALS15	20p	74ALS348	150p
74ALS16	20p	74ALS352	70p
74ALS17	20p	74ALS353	70p
74ALS18	20p	74ALS356	175p
74ALS19	20p	74ALS363	180p
74ALS20	20p	74ALS364	180p
74ALS21	20p	74ALS366A	36p
74ALS22	20p	74ALS367A	36p
74ALS23	20p	74ALS368A	36p
74ALS24	20p	74ALS373	120p
74ALS25	20p	74ALS374	120p
74ALS26	20p	74ALS377	120p
74ALS27	20p	74ALS377	120p
74ALS28	20p	74ALS378	85p
74ALS29	20p	74ALS379	120p
74ALS30	20p	74ALS390	100p
74ALS31	20p	74ALS393	120p
74ALS32	20p	74ALS399	120p
74ALS33	20p	74ALS445	100p
74ALS34	20p	74ALS465	120p
74ALS35	20p	74ALS466	120p
74ALS36	20p	74ALS467	120p
74ALS37	20p	74ALS467	120p
74ALS38	20p	74ALS468	120p
74ALS39	20p	74ALS469	120p
74ALS40	20p	74ALS470	120p
74ALS41	20p	74ALS471	120p
74ALS42	20p	74ALS472	120p
74ALS43	20p	74ALS473	120p
74ALS44	20p	74ALS474	120p
74ALS45	20p	74ALS475	120p
74ALS46	20p	74ALS476	120p
74ALS47	20p	74ALS477	120p
74ALS48	20p	74ALS478	120p
74ALS49	20p	74ALS479	120p
74ALS50	20p	74ALS480	120p
74ALS51	20p	74ALS481	120p
74ALS52	20p	74ALS482	120p
74ALS53	20p	74ALS483	120p
74ALS54	20p	74ALS484	120p
74ALS55	20p	74ALS485	120p
74ALS56	20p	74ALS486	120p
74ALS57	20p	74ALS487	120p
74ALS58	20p	74ALS488	120p
74ALS59	20p	74ALS489	120p
74ALS60	20p	74ALS490	120p
74ALS61	20p	74ALS491	120p
74ALS62	20p	74ALS492	120p
74ALS63	20p	74ALS493	120p
74ALS64	20p	74ALS494	120p
74ALS65	20p	74ALS495	120p
74ALS66	20p	74ALS496	120p
74ALS67	20p	74ALS497	120p
74ALS68	20p	74ALS498	120p
74ALS69	20p	74ALS499	120p
74ALS70	20p	74ALS500	120p

74ALS SERIES

74ALS00	25p	74ALS275	175p
74ALS01	20p	74ALS279	180p
74ALS02	20p	74ALS280	46p
74ALS03	20p	74ALS283	50p
74ALS04	20p	74ALS290	55p
74ALS05	20p	74ALS292	90p
74ALS06	20p	74ALS293	50p
74ALS07	20p	74ALS297	90p
74ALS08	20p	74ALS298	90p
74ALS09	20p	74ALS299	200p
74ALS10	20p	74ALS321	240p
74ALS11	20p	74ALS322	240p
74ALS12	20p	74ALS323	240p
74ALS13	20p	74ALS324/624	403p
74ALS14	20p	74ALS348	150p
74ALS15	20p	74ALS348	150p
74ALS16	20p	74ALS352	70p
74ALS17	20p	74ALS353	70p
74ALS18	20p	74ALS356	175p
74ALS19	20p	74ALS363	180p
74ALS20	20p	74ALS364	180p
74ALS21	20p	74ALS366A	36p
74ALS22	20p	74ALS367A	36p
74ALS23	20p	74ALS368A	36p
74ALS24	20p	74ALS373	120p
74ALS25	20p	74ALS374	120p
74ALS26	20p	74ALS377	120p
74ALS27	20p	74ALS377	120p
74ALS28	20p	74ALS378	85p
74ALS29	20p	74ALS379	120p
74ALS30	20p	74ALS390	100p
74ALS31	20p	74ALS393	120p
74ALS32	20p	74ALS399	120p
74ALS33	20p	74ALS445	100p
74ALS34	20p	74ALS465	120p
74ALS35	20p	74ALS466	120p
74ALS36	20p	74ALS467	120p
74ALS37	20p	74ALS467	120p
74ALS38	20p	74ALS468	120p
74ALS39	20p	74ALS469	120p
74ALS40	20p	74ALS470	120p
74ALS41	20p	74ALS471	120p
74ALS42	20p	74ALS472	120p
74ALS43	20p	74ALS473	120p
74ALS44	20p	74ALS474	120p
74ALS45	20p	74ALS475	120p
74ALS46	20p	74ALS476	120p
74ALS47	20p	74ALS477	120p
74ALS48	20p	74ALS478	120p
74ALS49	20p	74ALS479	120p
74ALS50	20p	74ALS480	120p
74ALS51	20p	74ALS481	120p
74ALS52	20p	74ALS482	120p
74ALS53	20p	74ALS483	120p
74ALS54	20p	74ALS484	120p
74ALS55	20p	74ALS485	120p
74ALS56	20p	74ALS486	120p
74ALS57	20p	74ALS487	120p
74ALS58	20p	74ALS488	120p
74ALS59	20p	74ALS489	120p
74ALS60	20p	74ALS490	120p
74ALS61	20p	74ALS491	120p
74ALS62	20p	74ALS492	120p
74ALS63	20p	74ALS493	120p
74ALS64	20p	74ALS494	120p
74ALS65	20p	74ALS495	120p
74ALS66	20p	74ALS496	120p
74ALS67	20p	74ALS497	120p
74ALS68	20p	74ALS498	120p
74ALS69	20p	74ALS499	120p
74ALS70	20p	74ALS500	120p

4000 CMOS

74VHC00	150p	74VHC275	175p
74VHC01	150p	74VHC279	180p
74VHC02	150p	74VHC280	46p
74VHC03	150p	74VHC283	50p
74VHC04	150p	74VHC290	55p
74VHC05	150p	74VHC292	90p
74VHC06	150p	74VHC293	50p
74VHC07	150p	74VHC297	90p
74VHC08	150p	74VHC298	90p
74VHC09	150p	74VHC299	200p
74VHC10	150p	74VHC321	240p
74VHC11	150p	74VHC322	240p
74VHC12	150p	74VHC323	240p
74VHC13	150p	74VHC324/624	403p
74VHC14	150p	74VHC348	150p
74VHC15	150p	74VHC348	150p
74VHC16	150p	74VHC352	70p
74VHC17	150p	74VHC353	70p
74VHC18	150p	74VHC356	175p
74VHC19	150p	74VHC363	180p
74VHC20	150p	74VHC364	180p
74VHC21	150p	74VHC366A	36p
74VHC22	150p	74VHC367A	36p
74VHC23	150p	74VHC368A	36p
74VHC24	150p	74VHC373	120p
74VHC25	150p	74VHC374	120p
74VHC26	150p	74VHC377	120p
74VHC27	150p	74VHC377	120p
74VHC28	150p	74VHC378	85p
74VHC29	150p	74VHC379	120p
74VHC30	150p	74VHC390	100p
74VHC31	150p	74VHC393	120p
74VHC32	150p	74VHC399	120p
74VHC33	150p	74VHC445	100p
74VHC34	150p	74VHC465	120p
74VHC35	150p	74VHC466	120p
74VHC36	150p	74VHC467	120p
74VHC37	150p	74VHC467	120p
74VHC38	150p	74VHC468	120p
74VHC39	150p	74VHC469	120p
74VHC40	150p	74VHC470	120p
74VHC41	150p	74VHC471	120p
74VHC42	150p	74VHC472	120p
74VHC43	150p	74VHC473	120p
74VHC44	150p	74VHC474	120p

JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail-Order Prices.

EC50 Mains Electronic Iron. £26.19




Features spike-free, solid state

proportional electronic temperature control inside the handle. Adjustable 280° to 400°C. Burn-proof 3-wire mains lead. Fitted 3.2mm Long-Life bit. 1.6, 2.4 and 4.7mm available. 240v a.c.

SK18 Soldering Kit. £15.24

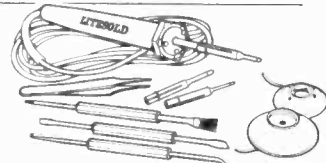Build or repair any electronic project. LC18 240v 18w iron with 3.2, 2.4, and 1.6mm bits. Pack of 18 swg flux-cored 60/40 solder. Tweezers. 3 soldering aids. Reel of De-Solder braid. In PVC presentation wallet.



ADAMIN Miniature Iron. £5.97




Possibly smallest mains iron in the world. Ideal for fine work. Slim

nylon handle with finger grip. Interchangeable bits available 1.2, 1.6, 2.4, 3.4 and 4.7mm. Fitted with 2.4mm. 240v 12w (12v available). Presentation wallet.

'L' Series Lightweight Irons. 12w £6.23.

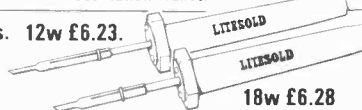High efficiency irons for all electronic hobby work. Non-roll handles with finger guards.




18w £6.28

Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12

model, 12w, 2.4mm bit. LC 18 Model, 18w, 3.2mm bit. 240v Std - 12v available. Presentation wallet.

Soldering Iron Stands. £5.11

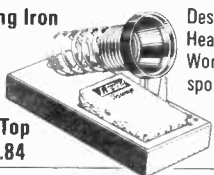

Designed specially for LITESOLD irons. Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits.

No 5 stand for EC50 iron No 4 stand for ADAMIN miniature Iron No 3 stand for LA12 and LC18 Irons All same price

Spring/Top only, £1.84

Replacement Bits

For all above irons. Non-stick designs, machined from special copper alloy, with Inconel retaining rings. Two types - Chromium plated with copper face (for economy and ease of use) and Iron plated with

Pre-tinned face (Long Life). State tip size, iron and type.

	Copper	I/L
EC50	£1.58	
Adamin 12 and		
LA12	92p	£1.56
LC18	£1.01	£1.70

BRADEWICK De-Solder Braid.



£1.05 per Reel

For simple, safe and effective de-soldering of all types of joint, using a standard soldering iron. Handy colour-coded packs of 1.5 metres in 3 widths: Yellow - 1.5mm, Green - 2mm, Blue - 3mm.

De-Solder Pumps. £6.19

High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy



thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.

Miniature Tool Sets



Top quality Japanese metric hardened and tempered tools. Swivel-top chrome plated brass handles. Fitted plastic cases. 113 set - 6 miniature

screwdrivers 0.9 to 3.5mm £2.70

227 set 5 socket spanners 3 to 5mm £2.80


305 set 2 crosspoint and 3 hex wrenches 1.5 to 2.5mm £2.70

228 set 20 piece combination: 5 open, 5 skt spanners, 2 crosspoint, 3 hex and 3 plain drivers, scriber, handle/holder £4.83

Microcutters. £3.21 Light weight hardened and precision ground. Flush cutting. Screw joint, return spring, cushion-grip handles. Safety wire-retaining clip.



Soldering Aids.

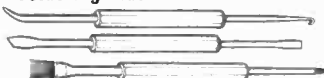

Set of 3 £3.63

Scraper/Knife, Hook/Probe, Brush/Fork. 3 useful double-ended aids to soldering/desoldering/assembly. In plastic wallet.

Solder. £0.90

Top grade resin flux cored 60/40 wire, 18 swg, in handy plastic dispenser. Approximately 3 metres (26gm).



ADAMIN Electric Stylus. £15.04

Writes like a ballpoint in Gold, Silver, Copper or 6 colours, on card, plastics, leather etc. Personalise wallets, bags, albums, books, electronic equipment, models... Operates at 4.5v from its own plug/transformer - totally safe. Supplied with coloured foils.




Prices include p&p and VAT. Send order with Cheque/PD. Ring for Access/Visa sales, or ask for order forms.

LIGHT SOLDERING DEVELOPMENTS LTD. DEPT. W
97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 01 689 0574

WW - 035 FOR FURTHER DETAILS

SATELLITE RECEIVING EQUIPMENT

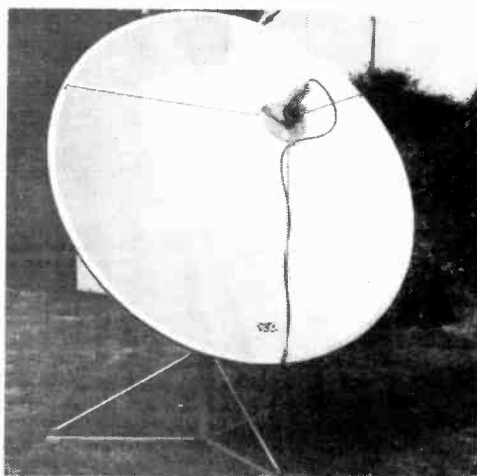

1.9M, 2.5M and 5M Harrison Dishes. Sat-Tec R5000 4GHz Receivers. Avcom COM-2B 4GHz Receivers. California Amplifier 4GHz LNAs. Chaparral Horns. Harrison Feed Horns.

Demonstrations by appointment only.


Dealer enquiries welcome

For further details contact: **Harrison Electronics**,
22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX.
Telephone: Southend (0702) 332338.

WW - 013 FOR FURTHER DETAILS

FYLDE

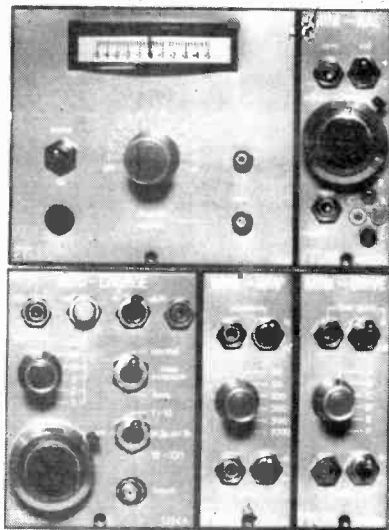TRANSDUCER and RECORDER
AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules - mains or dc option single cases and up to 17 modules in standard 19" crates small size - low weight - realistic prices.

FYLDE


Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

WW - 023 FOR FURTHER DETAILS



TYPE 9051

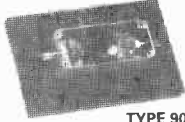

TYPE 9046

VMOs WIDEBAND LINEAR POWER AMPLIFIERS. 4 watts RF output. Without tuning. Power gain 10 dB. 24V+ supply

TYPE 9046 100 KHz - 100 MHz £54.50 + £3.50 p&p
TYPE 9051 20 MHz - 200 MHz £64.50 + £3.50 p&p




TYPE 9152




TYPE 9159

TELEVISION LINEAR POWER AMPLIFIERS. Tuned to your specified channels in bands IV or V

TYPE 9061 150 mV. input, 10 mW. output £120 + £5 p&p
TYPE 9152 10 mW. input, 500 mW. output £160 + 5 p&p
TYPE 9159 500 mW. input, 5 watts output £180 + £5 p&p

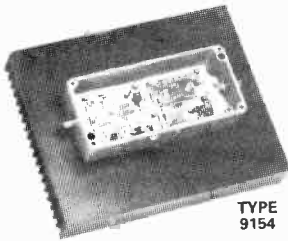


TYPE 9154

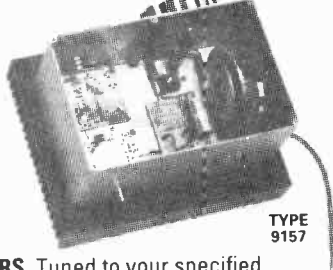

TYPE 9157

VMOs LINEAR POWER AMPLIFIERS. Tuned to your specified frequency in the range 10-250 MHz


TYPE 9154 200 mW. - 2 watts input, 20 watts output £180 + £10 p&p
TYPE 9160 As above with integral mains power supply unit £240 + £15 p&p
TYPE 9168 8 watts input, 80 watts output £240 + £10 p&p
TYPE 9157 As above with integral mains power supply unit £295 + £15 p&p
TYPE 9086 FM TRANSMITTER 88-108 MHz. 50 watts RF output. 24V+ supply. Complete modular system £380 + £20 p&p
TYPE 9087 As above with integral mains power supply unit £440 + £25 p&p

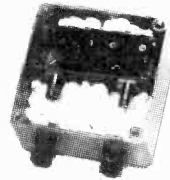

TYPE 9010

TWO STAGE GASFET STRIPLINE PREAMPLIFIERS
Tuned to your specified channels in bands IV or V

TYPE 9002 Two stage Gasfet preamplifier. N.F. 0.7 dB. Gain 25 dB. High Q filter. 15V. + DC £85 + £2 p&p
TYPE 9004 UHF two stage Gasfet preamplifier. N.F. 0.6 dB. Gain 25 dB. Aligned to your specified frequency in the range 250-500 MHz. High Q filter. 15V. + DC £85 + £2 p&p
TYPE 9012 Gasfet preamplifier mains power supply unit £24.50 + £3 p&p
TYPE 9010 Masthead weatherproof unit £6.50 + £2 p&p

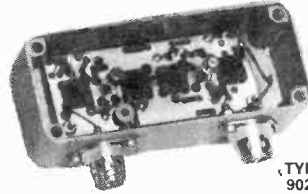

TYPE 9026



TYPE 9035

GASFET/MOSFET RF PREAMPLIFIERS. Aligned to your specified frequency in the range 30-250 MHz. Masthead/local use

TYPE 9026 N.F. 1.0 dB. Gain 10-40 dB. variable £39.50 + £2 p&p
TYPE 9026FM As above. Band II 88-108 MHz £39.50 + £2 p&p
TYPE 9006 Gasfet. N.F. 0.6 dB. Gain 10-40 dB. variable £65 + £2 p&p
TYPE 9035 Mains power supply unit for above types £24.50 + £3 p&p





TYPE 8034

TYPE 8034 PHASE LOCKED SIGNAL SOURCE using low frequency reference crystal. Specify output in the range 1-600 MHz. Output 10 mW. + 10 dBm £79.50 + £2 p&p
TYPE 9113 TELEVISION FREQUENCY CONVERTER. Changes channels in the range 40-1000 MHz £242 + £5 p&p
TYPE 9056 1500 MHz. PRESCALER. Divides 100-1500 MHz. by 10 £69.50 + £2 p&p

RESEARCH COMMUNICATIONS LTD.
UNIT 3, DANE JOHN WORKS, GORDON ROAD, CANTERBURY, KENT CT1 3PP
TELEPHONE: CANTERBURY (0227) 56489

PLEASE ADD 15% V.A.T. ON TOTAL

WW - 048 FOR FURTHER DETAILS

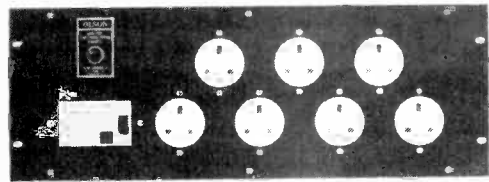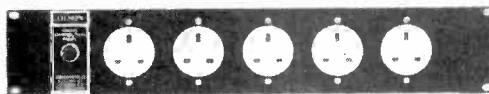

**V
E
R
T
I
C
A
L**



**WHEN
IT COMES
TO POWER
FOR RACKS
IT MUST BE OLSON**

HORIZONTAL OR

**VERTICAL RANGE FROM 3-10 SOCKETS
ALL EX-STOCK!
SPECIALS TO ORDER**

OLSON ELECTRONICS LIMITED

5-7 LONG STREET LONDON E2 8HJ
TEL: 01-739 2343 TELEX 296797

WW - 018 FOR FURTHER DETAILS

LEADER GENERATORS

A complete range of generators including audio, function, RF, pattern, etc. In each type several models are available offering specifications suitable for most requirements and excellent value.

Audio

LAG-27 10Hz to 1MHz
LAG-120A 10Hz to 1MHz
LAG-125 10Hz to 1MHz

Function

LFG-1300 .002Hz to 2MHz
Sine, Triangle, Square + Int. Sweep

RF

LSG-17 0.1 to 150MHz
LSG-216 0.1 to 30MHz and 70 to 115MHz
Programmable, PLL Synthesized
LSW-250 2 to 260MHz Swemar

Pattern

LCG-399A PAL, Colour Bar, RF and Video outputs, Patterns.

For further information contact:-



thandar
ELECTRONICS LIMITED

Thandar Electronics Limited,
London Road, St. Ives, Huntingdon,
Cambridgeshire PE17 4HJ, England
Telephone (0480) 64646 Telex 32250 Test

THE LOGICAL CHOICE

WW - 005 FOR FURTHER DETAILS



MITSUBISHI

MGF-1400
MGF-1402
MGF-1412

GaAs FETs


FROM STOCK

Aspen Electronics Limited

UK representative for Mitsubishi Electric

2/3 Kildare Close, Eastcote, Ruislip
Middlesex HA4 9UR

Tel: 01-868 1188 Tlx: 8812727

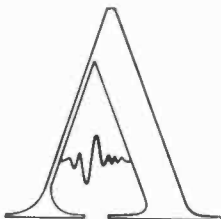

WW - 027 FOR FURTHER DETAILS

AMBISONIC SURROUND SOUND DECODERS

Ambisonic surround sound gives a realism in the reproduction of music that is hard to describe without using hackneyed expressions like 'natural' and 'being there'. Positioning of the performer becomes obvious and the acoustic of the original environment comes through to the listening room. The Minim decoders also provide enhanced results from conventional stereo material. We can now supply UHF encoded records, tapes and compact discs.

And don't forget our other products:

**PROGRAMMABLE WEEKLY TIME SWITCHES
TELEVISION SOUND TUNERS**

Please send me information on Timeswitches/Television Tuners/Ambisonics

Name

Address


Minim Electronics Limited, Lent Rise Road
Burnham, Slough SL1 7NY. Tel. Burnham 63724

ww3

WW - 076 FOR FURTHER DETAILS

TDS900

FORTH COMPUTER

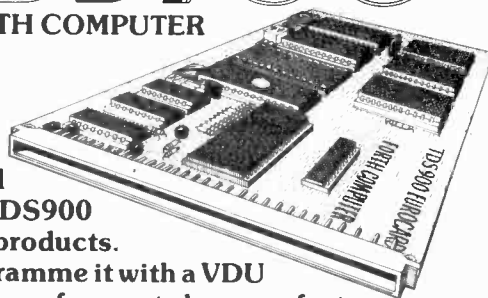

**Build
the TDS900
into products.
Programme it with a VDU
and your forecasts become fact.**

Software costs are significant in all industrial applications of microprocessors. They cannot be amortised over the large quantities associated with personal computers and electronic games. This C-MOS embedded computer card aims at resolving this problem by including FORTH high level language programming and developmental facilities. The software can be written quickly and made to work correctly at lowest possible expense. Using a high level programming language rather than assembler gives a fast reaction time to market opportunities. Production products use the same board as employed in the prototypes.

No microprocessor development system is needed since the card contains a screen editor working with simple visual display units (VDUs). It also has the compiler for the FORTH source code. Debugging is inherent in the FORTH language and once the code is working, this can be output to a PROM programmer.

Use of C-MOS throughout has brought the power consumption down to 28mA, making the TDS900 especially suitable for portable and battery-driven applications.



Triangle Digital Services Limited

100a Wood Street, Walthamstow, London E17 3HX Tel: 01-520 0442

Visitors to our laboratories are welcome by appointment

WW - 055 FOR FURTHER DETAILS

LANGRFX SUPPLIES LTD

Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

RST

Tel: 01-677 2424 Telex: 946703

RST

SEMICONDUCTORS

AA119 0.10	AS215 1.20	BC173 0.11	BD132 0.48	BF257 0.27	GEX541 5.00	OA2207 1.50	OC205 2.75	ZTX504 0.21	2N1671 5.00	2N3819 0.30
AA130 0.17	AS216 1.10	BC177 0.28	BD135 0.40	BF258 0.27	GJ3M 1.50	OC206 2.50	OC207 2.50	ZTX550 0.25	2N1893 0.32	2N3820 0.39
AA130 0.17	AS217 1.00	BC178 0.28	BD137 0.40	BF259 0.27	GM0378A 1.75	OC210 2.50	OC211 2.50	IN914 0.05	2N1917 0.40	2N3823 0.60
AA133 0.15	AS220 2.30	BC179 0.28	BD138 0.48	BF338 0.36	KS100A 0.45	OC22 2.50	OC23 4.00	IN916 0.05	2N2148 3.75	2N3866 1.00
AA135 0.15	AS221 2.50	BC182 0.11	BD139 0.48	BF337 0.34	MJE340 0.60	OC24 3.00	OC25 1.00	R2008B 2.00	2N2218 0.32	2N3904 0.17
AA171 0.15	AU113 2.50	BC183 0.11	BD140 0.50	BF328 2.25	MJE371 0.73	OC26 1.00	OC27 2.50	IN4001 0.06	2N2219 0.32	2N3905 0.17
AC107 0.55	AU110 3.00	BC184 0.11	BD144 2.00	BF361 0.20	MJE520 0.47	OC28 1.50	OC29 2.00	IN4002 0.06	2N2220 0.20	2N3906 0.17
AC126 0.25	BA145 0.13	BC212 0.11	BD181 1.20	BF398 0.20	MJE2955 1.70	OC32 2.00	OC35 1.50	R2010B 2.00	2N2221 0.20	2N4058 0.20
AC127 0.25	BA148 0.15	BC213 0.11	BD183 0.80	BF399 0.20	MJE3055 1.10	OC36 1.50	OC37 1.50	TIC226D 1.27	2N2222 0.20	2N4059 0.20
AC128 0.30	BA154 0.10	BC214 0.11	BD217 0.54	BF411 0.97	MPE102 0.35	OC41 1.50	OC42 0.90	TIC226D 1.27	2N2223 4.25	2N4060 0.16
AC128 0.30	BA155 0.11	BC237 0.11	BD238 0.54	BF438 0.46	MPE104 0.35	OC43 1.50	OC44 0.85	TIP299A 0.43	2N2368 0.25	2N4061 0.16
AC141 0.28	BA156 0.10	BC238 0.11	BDX10 0.91	BF485 0.30	MPE105 0.35	OC45 1.50	OC46 0.85	TIP300 0.45	2N2484 0.25	2N4062 0.16
AC141K 0.35	BAW62 0.05	BC303 0.34	BDX32 2.00	BF490 0.30	MPE106 0.26	OC47 1.50	OC48 0.85	TIP310 0.33	2N2646 0.50	2N4124 0.16
AC142 0.42	BAW62 0.05	BC307 0.11	BDY20 1.50	BF499 0.25	MPSA56 0.28	OC49 1.50	OC50 1.50	TIP32A 0.36	2N2904 0.32	2N4126 0.17
AC142K 0.35	BAX16 0.06	BC307 0.11	BDY60 2.75	BF520 0.25	MPSA56 0.28	OC51 1.50	OC52 1.50	TIP33A 0.54	2N2905 0.32	2N4286 0.15
AC176 0.30	BC107 0.16	BC308 0.11	BF115 0.35	BF521 0.25	MPSU01 0.53	OC53 1.50	OC54 1.50	TIP34A 0.67	2N2906 0.21	2N4288 0.18
AC176 0.30	BC108 0.16	BC327 0.12	BF152 0.16	BF522 0.25	MPSU06 0.65	OC55 1.50	OC56 1.50	TIP34A 0.67	2N2907 0.21	2N4289 0.18
AC176 0.30	BC109 0.16	BC328 0.12	BF153 0.16	BF523 0.25	MPSU06 0.65	OC57 1.50	OC58 1.50	TIP34A 0.67	2N2908 0.21	2N4400 0.11
AC176 0.30	BC110 0.16	BC329 0.12	BF154 0.17	BF524 0.25	MPSU06 0.65	OC59 1.50	OC60 1.50	TIP34A 0.67	2N2909 0.21	2N4401 0.11
AC176 0.30	BC111 0.16	BC330 0.12	BF155 0.17	BF525 0.25	MPSU06 0.65	OC61 1.50	OC62 1.50	TIP34A 0.67	2N2910 0.21	2N4402 0.11
AC176 0.30	BC112 0.16	BC331 0.12	BF156 0.17	BF526 0.25	MPSU06 0.65	OC63 1.50	OC64 1.50	TIP34A 0.67	2N2911 0.21	2N4403 0.11
AC176 0.30	BC113 0.16	BC332 0.12	BF157 0.17	BF527 0.25	MPSU06 0.65	OC65 1.50	OC66 1.50	TIP34A 0.67	2N2912 0.21	2N4404 0.11
AC176 0.30	BC114 0.15	BC333 0.12	BF158 0.17	BF528 0.25	MPSU06 0.65	OC67 1.50	OC68 1.50	TIP34A 0.67	2N2913 0.21	2N4405 0.11
AC176 0.30	BC115 0.18	BC334 0.12	BF159 0.17	BF529 0.25	MPSU06 0.65	OC69 1.50	OC70 1.50	TIP34A 0.67	2N2914 0.21	2N4406 0.11
AC176 0.30	BC116 0.19	BC335 0.12	BF160 0.17	BF530 0.25	MPSU06 0.65	OC71 1.50	OC72 1.50	TIP34A 0.67	2N2915 0.21	2N4407 0.11
AC176 0.30	BC117 0.23	BC336 0.12	BF161 0.17	BF531 0.25	MPSU06 0.65	OC73 1.50	OC74 1.50	TIP34A 0.67	2N2916 0.21	2N4408 0.11
AC176 0.30	BC118 0.18	BC337 0.12	BF162 0.17	BF532 0.25	MPSU06 0.65	OC75 1.50	OC76 1.50	TIP34A 0.67	2N2917 0.21	2N4409 0.11
AD149 0.75	BC125 0.18	BC338 0.12	BF163 0.17	BF533 0.25	MPSU06 0.65	OC77 1.50	OC78 1.50	TIP34A 0.67	2N2918 0.21	2N4410 0.11
AD161 0.35	BC126 0.18	BC339 0.12	BF164 0.17	BF534 0.25	MPSU06 0.65	OC79 1.50	OC80 1.50	TIP34A 0.67	2N2919 0.21	2N4411 0.11
AD162 0.35	BC127 0.18	BC340 0.12	BF165 0.17	BF535 0.25	MPSU06 0.65	OC81 1.50	OC82 1.50	TIP34A 0.67	2N2920 0.21	2N4412 0.11
AF106 0.35	BC136 0.19	BCY42 0.30	BF181 0.28	BF182 0.30	BY100 2.40	OC83 1.00	OC84 1.00	ZTX107 0.12	2N708 0.25	2N3053 0.25
AF114 0.75	BC137 0.19	BCY43 0.30	BF183 0.28	BF184 0.28	BY100 2.40	OC85 1.00	OC86 1.00	ZTX107 0.12	2N708 0.25	2N3054 0.25
AF115 0.75	BC147 0.12	BCY58 0.18	BF185 0.28	BF186 0.28	BY100 2.40	OC87 1.00	OC88 1.00	ZTX107 0.12	2N708 0.25	2N3055 0.25
AF116 0.75	BC148 0.12	BCY59 0.18	BF187 0.28	BF188 0.28	BY100 2.40	OC89 1.00	OC90 1.00	ZTX107 0.12	2N708 0.25	2N3056 0.25
AF117 0.75	BC149 0.12	BCY60 0.18	BF189 0.28	BF190 0.28	BY100 2.40	OC91 1.00	OC92 1.00	ZTX107 0.12	2N708 0.25	2N3057 0.25
AF118 0.75	BC150 0.12	BCY61 0.18	BF191 0.28	BF192 0.28	BY100 2.40	OC93 1.00	OC94 1.00	ZTX107 0.12	2N708 0.25	2N3058 0.25
AF119 0.75	BC151 0.12	BCY62 0.18	BF193 0.28	BF194 0.28	BY100 2.40	OC95 1.00	OC96 1.00	ZTX107 0.12	2N708 0.25	2N3059 0.25
AF186 1.00	BC158 0.13	BCZ11 0.17	BF195 0.14	BF196 0.14	Series 0.17	OC97 1.00	OC98 1.00	ZTX107 0.12	2N708 0.25	2N3060 0.25
AF239 0.39	BC159 0.13	BD115 0.42	BF197 0.14	BF198 0.14	Series 0.17	OC99 1.00	OC100 1.00	ZTX107 0.12	2N708 0.25	2N3061 0.25
AF211 4.00	BC167 0.11	BD121 1.70	BF199 0.17	BF200 0.17	CRS140 0.60	OC101 1.00	OC102 1.00	ZTX107 0.12	2N708 0.25	2N3062 0.25
AF212 4.00	BC170 0.11	BD123 2.80	BF201 0.17	BF202 0.17	CRS340 0.75	OC103 1.00	OC104 1.00	ZTX107 0.12	2N708 0.25	2N3063 0.25
ASV26 1.40	BC171 0.11	BD124 2.80	BF203 0.17	BF204 0.17	CRS340 0.75	OC105 1.00	OC106 1.00	ZTX107 0.12	2N708 0.25	2N3064 0.25
ASV27 0.90	BC172 0.11	BD131 0.44	BF244 0.48	GEX66 3.00	GEX66 3.00	OC107 1.00	OC108 1.00	ZTX107 0.12	2N708 0.25	2N3065 0.25

VALVES

A1834 9.00	E130L 18.50	EF85 1.75	GU51 20.00	QD3 2.50	QY3-65 59.86	UF41 2.00	4-250A 80.00	6CG7 2.50	12AX7 1.75	5642 9.00
A2087 13.50	E180C 10.50	EF86 1.75	GXU1 15.35	QZ4 3.50	QY3-125 66.50	UF42 2.10	4-400A 87.00	6CH6 13.00	12AY7A 4.00	6524 3.00
A2134 17.50	E180C 10.50	EF91 2.95	GXU2 30.00	PC86 2.50	QY4-250 68.00	UF80 1.75	4B32 20.00	6CL6 3.75	12B4A 3.50	6561 4.45
A2293 16.00	E180C 10.50	EF92 6.37	GXU4 44.50	PC88 2.50	QY4-400 74.20	UF89 2.00	4C35 28.00	6CW4 8.00	12BA6 2.50	6570 4.50
A2426 27.50	E280C 12.00	EF93 1.50	GXU5 20.00	PC95 1.75	QY5-3000A 1.75	UL41 3.50	4X150A 60.00	6D2 1.50	12B6 3.00	6575 28.00
A2521 22.50	E280C 12.00	EF94 2.50	GY501 3.00	PC97 1.75	QY6-200 32.70	UL84 1.75	4X150D 36.00	6D2 1.50	12B7 2.75	6577 6.00
A2900 15.00	E280C 12.00	EF98 2.00	GY502 3.00	PC98 1.75	R10 6.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6578 6.00
A3343 45.00	E280C 12.00	EF183 2.00	GY503 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6579 6.00
A3343 45.00	E280C 12.00	EF184 2.00	GY504 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6580 6.00
A3343 45.00	E280C 12.00	EF185 2.00	GY505 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6581 6.00
A3343 45.00	E280C 12.00	EF186 2.00	GY506 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6582 6.00
A3343 45.00	E280C 12.00	EF187 2.00	GY507 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6583 6.00
A3343 45.00	E280C 12.00	EF188 2.00	GY508 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6584 6.00
A3343 45.00	E280C 12.00	EF189 2.00	GY509 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6585 6.00
A3343 45.00	E280C 12.00	EF190 2.00	GY510 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6586 6.00
A3343 45.00	E280C 12.00	EF191 2.00	GY511 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6587 6.00
A3343 45.00	E280C 12.00	EF192 2.00	GY512 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6588 6.00
A3343 45.00	E280C 12.00	EF193 2.00	GY513 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6589 6.00
A3343 45.00	E280C 12.00	EF194 2.00	GY514 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6590 6.00
A3343 45.00	E280C 12.00	EF195 2.00	GY515 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6591 6.00
A3343 45.00	E280C 12.00	EF196 2.00	GY516 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6592 6.00
A3343 45.00	E280C 12.00	EF197 2.00	GY517 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6593 6.00
A3343 45.00	E280C 12.00	EF198 2.00	GY518 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6594 6.00
A3343 45.00	E280C 12.00	EF199 2.00	GY519 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6595 6.00
A3343 45.00	E280C 12.00	EF200 2.00	GY520 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6596 6.00
A3343 45.00	E280C 12.00	EF201 2.00	GY521 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6597 6.00
A3343 45.00	E280C 12.00	EF202 2.00	GY522 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6598 6.00
A3343 45.00	E280C 12.00	EF203 2.00	GY523 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6599 6.00
A3343 45.00	E280C 12.00	EF204 2.00	GY524 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6600 6.00
A3343 45.00	E280C 12.00	EF205 2.00	GY525 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6601 6.00
A3343 45.00	E280C 12.00	EF206 2.00	GY526 3.00	PC98 1.75	R17 3.00	UL84 1.75	4X250A 55.00	6D2 1.50	12B7 2.75	6602 6.00

AFFORDABLE PERIPHERALS.

Opus peripherals are the best buys in the whole peripherals market—bar none.

Just compare the prices below with anything else in this magazine. And note just what our prices include: VAT, all necessary leads, carriage and a full one year's guarantee.

All products are suitable for use with the BBC and most other leading Micros. And all are of the very highest quality—a fact endorsed by the

enthusiasm of dealers all over the country to carry OPUS brands.

WH Smith, for example, carry the 3" micro-drive, while Spectrum dealers offer our 5401 and 5402 5¼" Disc Drive.

All products offered here, —and many more, are on display in our showroom. Trade enquiries welcome and discounts are available for Government and Educational authorities.

OPUS 3" MICRODRIVE.

Opus 3402 Double Sided 40 Track Drive ½ Megabyte Unformatted.


- Twice the capacity on line of other available drives
- 200K Single Density—400K. Double Density
- Ex-stock delivery ● 3ms. access time
- Lowest power consumption—direct drive
- Includes case, leads and utilities disc
- Totally compatible with 5¼" drives

Single Drive. _____

£229.95

Dual Drive. _____

£459.95

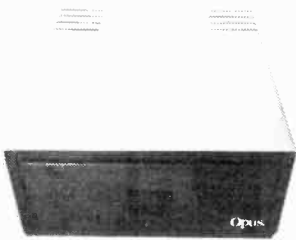

5¼" JAPANESE DISC DRIVES. SINGLE DRIVE.

Opus 5401 Single Sided 40 Track—250k. Unformatted. Formatted:
100K. Single Density. 200K. Double Density. _____

£179.95

Opus 5402 Double Sided 40 Track—500K. Unformatted.

Formatted: 200K. Single Density. 400K. Double Density. _____

£229.95

Opus 5800 Double Sided 80 Track: 1 Megabyte Unformatted.

Formatted: 400K Single Density. 800K Double Density. _____

£259.95

Opus 5802 Double Sided 80 Track—1 Megabyte Unformatted.

Formatted: 800K. Single Density, Switchable 80/40 Track. _____

£299.95

- ½ Height ● Includes case, leads and utilities disc ● Fast access time ● State of the Art Technology ● Ex-stock delivery ● Low power consumption.

DUAL DRIVES.

All Dual Drives are metal cased with separate power supply.

Opus Dual 5401D. Single Sided 40 Track.

200K./400K. on line. _____

£379.50

Opus Dual 5402D. Double Sided 40 Track.

400K./800K. on line. _____

£459.95

Opus Dual 5800 Double Sided 80 Track.


800K./1.6 Megabyte on line. _____

£499.95

Opus Dual 5802D. Double Sided 80 Track.

800K./1.6 Megabyte on line. Switchable 80/40 Track. _____

£599.95

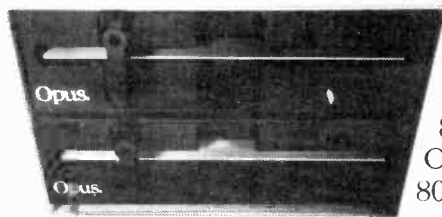

FLOPPY DISCS. DOUBLE DENSITY FILING SYSTEM.

3" Cartridge **£5.75** each or **£25.95** for 5.

5¼" Discs with full 5 year warranty + free plastic library case.

S/SS/D **£19.95** for 10.

S/S 80 Track **£29.00** for 10.

S/SD/D **£23.95** for 10.

D/S 80 Track **£31.95** for 10.

D/SD/D **£26.95** for 10.

8" Discs.

S/SS/D **£21.50**

S/SD/D **£28.50**

D/SD/D **£29.95**

Double Density
filing system.

£100.00

WIRELESS WORLD MARCH 1984




14" RGB JVC COLOUR MONITORS.

High Resolution (580 × 470 pixels) and Medium Resolution (370 × 470 pixels) Models available.

- Robustly constructed
- Handsome Cream Casing
- RGB Analogue/TTL input
- 80 Characters × 25 lines
- EHT: Min: 19.5kv MAX 22.5kv
- Supply -220/240v 50/60Hz

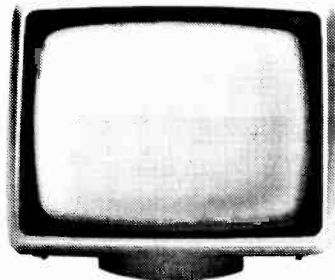High Resolution Model _____ **£279.39**
 Medium Resolution Model _____ **£187.39**




12" MONOCHROME MONITORS.

Superb units, optimised for high resolution and excellent geometry.

- Sturdy lightweight metal frame
- Easily accessible boards and modules
- Composite video input ● Video response 24MHz
- 800 lines horizontal at centre
- EHT 13.0kv ● Supply 220-240V.

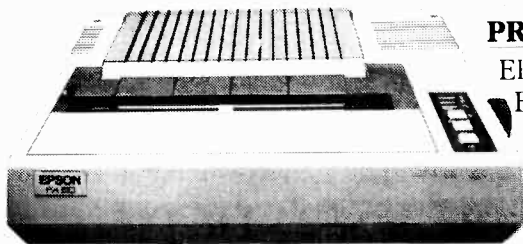Green Screen _____ **£89.95**
 Amber Screen _____ **£99.95**




PRINTERS.

EPSON FX80 F/T _____ **£410.00**
 EPSON FX100 _____ **£549.00**
 EPSON RX80 F/T _____ **£315.00**
 JUKI 6100 Daisywheel _____ **£435.00**
 Parallel printer leads to BBC _____ **£13.50**



THE ORGANISER DESK.

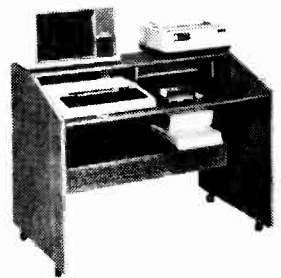- Top shelf for Monitor/Printer
- Large Desk Top Area
- Lower shelf for Paper/Book Storage
- Teak Finish ● On Castors
- Self Assembly
- Ample room in front of the shelf for you to sit comfortably
- Assembled Dimensions: H.31" W. 40¼" D. 26" Only **£59.95**



THE BUSINESS DESK RANGE.

Opus produce a range of 10 Business desks ideally suited for education, home or the professional user. Illustrated is the Model 10 desk.

- Units are finished in cream and brown
- Sturdy steel underframes ● Castors have lockable brakes
- Different models are available to suit many leading computer systems.

All are on display in our showroom and are available from us or dealers throughout the U.K. Prices start from **£100**
 For further details please telephone.

OPUS SUPPLIES LTD. 158 Camberwell Road, London SE5 0EE. **GOVERNMENT & EDUCATION DISCOUNTS GIVEN. QUANTITY DISCOUNTS GIVEN. DEALER ENQUIRIES INVITED.**
 01-701 8668. Opening hours: 9.00-6.00 Monday-Friday. 01-703 6155. 9.00-1.30p.m. Saturday.

To: Opus Supplies Ltd., 158 Camberwell Road, London SE5 0EE. Please rush me the following: **(ALL PRICES INCLUDE VAT & CARRIAGE.)**

Quantity	Description	Price
	TOTAL:	

I enclose a cheque for £ _____
 Or please debit my credit card account with the amount of £ _____
 My Access/Barclaycard (please tick) No. is _____

Name _____
 Address _____

Tel _____



WW 8

Keithley's 175.



Data Logger

Relative Reference

dB/Rel dB Function

Min/Max Hold

Fast Autoranging

Digital Calibration

LCD Annunciators

IEEE-488 Option

Extended Range

Battery Option

A new benchmark for portable DMMs.

The Keithley 175 Autoranging DMM — sets new standards in bench/portable technology.

It out-performs every other unit in its class and has all the features you'd expect of a full function multimeter — 4½ digits, 10 μV, 10 nA, 10 mΩ, TRMS AC — as well as many more you wouldn't expect even on some meters costing twice as much. For instance...

Fast Autoranging on DC volts, ohms, AC volts and dB. Manual range selection too.

100-Point Data Logger stores readings at six different rates from three per second to one every hour.

Digital Calibration for increased reliability and ease of calibration. All calibration constants are stored digitally.

Min/Max Reading Hold stores both highest and lowest readings — over lunch, overnight, over weekends.

dB/Relative dB makes direct dB readings over a wide dynamic range and frequency spectrum.

Relative Reference used to null or zero the display — ideal for monitoring small changes in input signal.

Add **IEEE** bus and **battery** options and see for yourself how well the 175 comes up to the mark on your own bench — phone our hotline now for further information.

KEITHLEY

Keithley Instruments Limited
1 Boulton Road
Reading Berkshire RG2 0NL
Telex 847047

0734 861287

WW - 012 FOR FURTHER DETAILS

Editor

PHILIP DARRINGTON
01-661 3128

Deputy Editor

GEOFFREY SHORTER, B.Sc.
01-661 8639

Technical Editor

MARTIN ECCLES
01-661 8638

Projects Editor

RICHARD LAMBLEY
01-661 3039

News Editor

DAVID SCOBIE
01-661 8632

Drawing Office Manager

ROGER GOODMAN
01-661 8690

Technical Illustrator

BETTY PALMER

Advertisement Manager

BOB NIBBS, A.C.I.I.
01-661 3130

BARBARA MILLER
01-661 8640

ASHLEY WALLIS
01-661 8641

Northern Sales

HARRY AIKEN
061-872 8861

Midland Sales

BASIL MCGOWAN
021-356 4838

Classified Manager

BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production

BRIAN BANNISTER
(Make-up and copy)
01-661 8648

Publishing Director

DAVID MONTGOMERY
01-661 3241

Software copyright and piracy

The issue of software copyright is a vexed and intractable one. On the one hand, there is the undoubted need to provide a living for programmers and maximum distribution of valuable software. On the other hand, one must consider that software is not an art form and can be derived independently from situation logic; furthermore, if a processor contains many equivalent registers, any change in the use of registers means a new program, therefore people desirous of stealing the work of a programmer for commercial gain and having the time to do it and the backup to pay lawyers, presumably can. As Dean Swift pointed out, that the lawyer is interested in "whether the said cow be black or white" not in what title the claimant has to the cow.

There are two alternatives to ensure a proper return. Either every user must pay a fee to the inventor of the program, or the state must use the award-to-inventor system. Attempts have been made to shame users into the former course by writing on software packages the fact that the programmer must live and asking all users to buy their own expensive copy, for the fact is that popular material will always tend to be expensive, providing quite unjustified returns, like a best-selling book, while the minority-interest material will with the greatest difficulty recover costs. A book or program concerned with sewage cannot sell more copies than there are sewage works, yet may affect the lives

of every citizen. Thus authorship of all kinds is grossly ill-rewarded by the commercial system.

This problem is entirely new, because in the past technical authors might be reasonably expected to have academic jobs and programs be published free. There is no way that the cottage industry of software production can protect its copyright. It must rely on honourable treatment. If it doesn't get it and if as a nation we want this industry to continue we will have to pay the workers from central funds.

This will distress the computer retail industry who naturally want to sell information in a physical object with a limited life and accident prone condition, like a paperback book.

Anyone who wants to pirate a very valuable program need only buy enough battery backed-up ram to hold it, for there is no way anyone can argue that software can't be copied into ram: similarly it would be very hard to argue that paper tape cannot be cut from this ram.

If one uses selective-bit inversion no one could ever prove a tape was their program; it is foolish to contemplate it. In the end people will pay for convenience if the software creators aren't greedy and shops take reasonable mark-ups. Blatant commercial pirates ought to be prosecuted, but talk of prosecuting friends for exchanging one's own copies is nonsense.

COMMUNICATIONS

History in the making

Apart from those few radio and television pioneers who are regarded by the public as the great inventors – Marconi, Armstrong, Baird, Watson-Watt etc. – the bulk of engineers and scientists who have followed in their wake and contributed enormously to the technology have remained virtually unrecognised. Few engineers, let alone the public, associate the coaxial cable with Franklyn, the waveguide with Southworth, the optical fibre pipe with Kao . . . etc. Very few engineers write readable autobiographies, fewer still form the subject of in-depth studies by historians who can appreciate the precise value of the contributions they made to the state-of-art.

Occasionally one comes across exhortations to technologists such as “It isn’t enough in any science to do things. It is necessary to communicate what has been done . . . not only your scientific or engineering results but also talk about how they arose, who was involved, all those things that are too often unrecorded. People’s memories are not precise. But that does not matter because the essence of historical scholarship is to use memoirs and other primary sources with discretion. A person who has participated shouldn’t worry about that bias he has due to his participation. The historians will take care of that in due time by comparing sources and checking dates.”

Excellent advice – provided always that those later historians actually start digging, and manage to produce books that can be read with interest!

These thoughts have been generated by reading two recent exceptions to the general rule: Dr George Brown’s lively and outspoken recollections of his life as a research engineer “and part of which I was” (Angus Cupar Publishers) that covers not only his pioneer work on aerials, r.f. heating and colour television but the familiar problems of an engineer caught up in commercial and political struggles to gain acceptance for his ideas. The second book was Andrew Hodges’ excellent 600-page study of “Alan Turing – The Enigma” (Burnett Books, 1983) that provides a detailed study of the life and tragic early death of the brilliant mathematician who in 1936 first outlined the concept of the ‘universal machine’ from which was to spring the digital computer. He was a gifted member of that formidable team of cryptoanalysts who in the “creative anarchy” of Bletchley Park successfully tackled the difficult German naval enigma machine code; taught himself electronic and radio engineering in a couple of months at Hanslope Park; and struggled at NPL to get built the stored program computer ACE but found bureaucracy too strongly entrenched. In fairness to NPL, Turing was clearly not the easiest or most

diplomatic person to work in harness with, though capable of attracting intense loyalty from those who assisted him during wartime.

A few years ago I received a letter from a technician who had worked alongside Turing at Hanslope when, with Donald Bayley, he was developing the never-to-be-used Delilah speech encryption system. Alan Turing was then advising the whole laboratory on circuit calculations, he had picked up practical radio engineering in less than three months, claiming “When I first looked at radio I could see it was 100% mathematics anyway so it was no problem.”

Andrew Hodges has amassed an enormous amount of information on Turing, but the reason for his suicide in June 1954 remains a mystery. Hodges shows that the often-mentioned prosecution of Turing on homosexual charges was by then two years behind him. He speculates on the continued involvement of Turing with GCHQ in an era when the security investigations following the Burgess, MacLean, the third and fourth man scandals were still rumbling on, but provides no evidence of any link between these events and Turing’s untimely death. Certainly there can be no evidence that Turing, patriot that he was, was ever a real security risk.

NTSC, PAL and SECAM

Dr Brown is particularly revealing about the bitter struggle in the period 1945-1955 between RCA and CBS over the sequential and compatible colour television systems, and the subsequent struggle in Europe over NTSC (which was basically the RCA system), PAL and SECAM. He shows clearly, though from an American viewpoint, that politics rather than engineering dominated the CCIR meetings at Vienna and Oslo, and the similarity of Russian, American, French and British skulduggery in the form of overnight changes of policy, suppression of technical reports, rigging of delegations and the like. As one retired British television engineer put it to me, in recommending George Brown’s lively account of his struggles with RCA’s management, “Just change the name of the firm, and you have the story of my life”. For any young engineer who wishes to understand how things really happen, this is essential reading – though I noted that even the politically-conscious Dr Brown apparently failed to note one of the most astonishing events of the Oslo CCIR meeting in 1966. In April of that year, a member of the British delegation returned (unsuccessfully) to the UK during the event for the express purpose of trying to have the Post Office man in charge of the British delegation removed, leading later to an off-the-record press briefing in which the leader of the British team bitterly attacked the broadcasting delegates.

Data security

Presumably we shall never know whether Turing was under pressure from the security people in 1954 though one has no doubt that, as a wartime member of the Government School of Codes and Ciphers, he would have figured in those secret files that will remain inviolate under both the 30-year rule and the Data Protection Bill. Yet there is plenty of evidence that such files frequently contain information confused by mistaken identification etc. This might not matter so much were it not for the evidence that the Security Service advise outside organizations, including commercial firms, when recruiting engineers for sensitive posts. With such information now fully computerized, the effects on people’s careers can be far-reaching. Unlike many other countries not even the registrar, who will administer the British Act, will have power of inspection or supervision of either security or police files.

Clandestine war plans

Surprisingly one of the official files of 1953 now opened under the 30-year-rule details plans then proposed for clandestine activities in the event of war. The 1982 Falklands campaign showed that such activities still form an important part of British military planning. The 1953 proposals covered “stay-behind”, evader and coup-de-main activities. Sir John Sinclair, then head of the Special Intelligence Service, requested the use of 15 fast patrol boats, three trawlers, 42 fishing boats, 8 long-range aircraft, use of a submarine, and no less than 400 specially trained signals operators. Britain, France and the USA were each expected to provide 500 agents and 50 aircraft for the first three weeks following the outbreak of war. It was recognized that such activities were a gamble, possibly paying a high dividend or “next to none”. One wonders if the agents knew that they were to be part of a high risk gamble.

Costly clangers

Governments can and do make bad mistakes on their assessment of new electronics technology in addition to grossly underestimating the development costs. Now, the French Government and their nationalised Elf-Aquitaine oil company has been forced into revealing that they were “taken” to the tune of some £60million by the so-called Omega and Delta oil-sniffing systems that purported to reveal deeply buried geological strata to aircraft flying overhead, but was eventually shown to depend on prepared sketches fed into the machine. By surrounding the invention with an air of mystery, the Panamanian-registered company, Fisalma, was able to block all attempts to examine the costly prototypes. But it is not only the French

COMMENTARY

Government that has been known to back the wrong horse in electronics and telecommunications.

Recently Americans have become increasingly uneasy that the electronics equipment put into military aircraft, flight simulators etc can cost up to ten times its civilian counterpart. The electronics can cost many times more than basic aircraft. As one writer put it recently: "In the necessary secrecy that shrouds weapons development, a pipe dream can be pursued for years — and for billions of dollars — before someone catches on to its futility." The solution, it is suggested, would be to introduce independent technical monitoring of projects by a watchdog committee of top-notch engineers. But, one wonders, who would watch the watch-dogs? Engineers, as well as administrators, have been known to get it wrong.

The AM-stereo struggle

At the end of 1983 there was still no clear outcome to the "market-place" struggle in the USA between the four competing systems of a.m. stereo. In terms of transmitters, Harris had lost the lead to Kahn's independent sideband system used by some 80 stations including several major NBC music stations. Harris was stuck at about 65 stations, resulting from the FCC decision to restrain the company from marketing any more exciters until the type-acceptance dispute had been fully cleared up. Motorola was up to about 50 and their system has been endorsed by some large car radio firms. Trailing with single-figures was the Magnavox system, despite it being the original choice of FCC in 1979. Meanwhile Sony has marketed a \$90 combined a.m./f.m. portable that can receive any of the four a.m.-stereo systems and including a switch to widen the m.f. bandwidth to 12kHz. A multimode set has also been marketed by Sansui.

AMATEUR RADIO

50MHz extension

The Department of Trade and Industry has agreed to a substantial extension of the special research permits for 50MHz operation by British amateurs holding Class A licences. The number will go from 40 to 100. DTI have asked the RSGB to recommend additional names by March 31. With all British 405-line television broadcasting in bands 1 and 3 now due to end in the first week of January 1985, British amateurs are hoping that the DTI will make an early announcement about any plans to implement the recommendation in the interim Merriman Report in 1982 that an alloca-

tion in this part of the spectrum should be made available to all British amateurs. There remains the problem that this part of the frequency spectrum (except channel 1) is likely to remain in use for television in virtually all other European countries.

RTTY

Ian Wade, G3NRW, the current editor of the British Amateur Radio Teleprinter Group newsletter, estimates that about one half of BARTG members are still using mechanical teleprinters but many are in process of adopting computer-based electronic systems with over two-thirds of the membership owning home computers. Interest in the Amtor system with automatic correction of errors is also increasing rapidly and expected to really take off during 1984 with commercially manufactured units increasingly available. He also forecasts more amateur interest in digital data techniques including the "packet" systems. But there seems to be no end in sight to various problems of different technical standards, including the long standing problem of 45 versus 50 baud transmission, though some teleprinters, such as the Creed 444 will cope with both speeds. Bob Sayers, G8IYK is seeking contact with radio amateurs interested in adapting compact telephone-line facsimile equipments for h.f. transmission or for using such machines for other applications. He also points out that a special Met Office licence is needed to receive weather messages in r.t.t.y. format. Application forms for DTI licences can be obtained from Meteorological Office (Licensing) London Road, Bracknell, Berks, RG12 2SZ. Full title of the licence is "Receiving licence for the reception of meteorological information transmitted from special service stations".

During 1984 BARTG celebrates its Silver Jubilee having been founded in 1959. The group caters for those interested in most forms of data transmission, including r.t.t.y., Amtor, Fax, weather forecasting, satellites and telemetry. Current membership is about 1300. Membership details from John Beedie, G6MOK, 161 Tudor Road, Hayes, Middlesex UB3 2QG (telephone 01-561 0010). Apart from the quarterly newsletter BARTG publish "RTTY, the easy way".

Low power activity

Although extreme low-power operation is not an activity I would recommend to newcomers to the h.f. bands, it holds much interest for those with the necessary experience and patience. Indeed on some h.f. bands signals can come in at good strength from transmitters using power inputs of less than 5 watts over many thousands of miles. Low-power (QRP) operation in the UK has for a number of years been en-

couraged by the "G-QRP Club", formed in late-1974, and now having almost 2500 members. Rev George Dobbs, G3RJV, editor of its quarterly journal "Sprat" admits to being concerned that the fall-off of conditions on the h.f. bands due to the declining sunspot activity may make it more difficult to achieve good contacts on the higher of the h.f. bands but urges more activity on the "low-power calling frequencies" of 3560kHz and 7030kHz. He notes that low-power operation on these bands has not kept pace with the increasing number of members. He reports, however, an increasing interest in home construction of low power transmitters and compact direct-conversion receivers.

In brief . . .

George Stratton Loughton, founder in the 1920s of Eddystone Radio, died during December 1983. Eddystone was one of the first British firms to cater specifically for short-wave enthusiasts and radio amateurs with their "All World" series of receivers and components for home construction . . . RSGB membership has exceeded 35,000 for the first time . . . The RSGB National VHF convention is being held on March 24 at Sandown Park Racecourse, Esher, Surrey . . . A mobile rally is being held at the Carelon Community Centre by the Pontefract society on March 18 . . . An increasing number of amateurs in many parts of the world are now equipped for earth-moon-earth (moonbounce) contacts on the 1.3 and 2.3GHz band but Z25JJ, representing Africa, is closed for the time being while his equipment, including a massive 32ft dish reflector, is transported from Zimbabwe to South Africa . . . Much effort is being put into the rush building at the University of Surrey of its second spacecraft, UOSAT-B, which it hoped will be launched this Spring . . . Of the various Russian amateur satellites, RS6 and RS8 remain in operation. The problem on the L-band Oscar 10 transponder seems to have been successfully overcome . . . The IARU Region 1 Triennial Conference, bringing together the national IARU societies in Europe and Africa, is to be held in Sicily between April 7 and 14 . . . The installation of the RSGB's 50th President, R. G. Barrett, GW8HEZ, was at Cardiff Castle on January 14 . . . A number of changes affecting the British CB licence were introduced on February 1. No further licences are being issued to persons under 14 years of age but they can operate CB equipment under supervision. There is now an explicit ban on the playing of music and the re-transmission of radio and television broadcast material (both of which have always been illegal) and DTI draw attention to the CB Code of Practice in particular highlighting the recommendation that Channel 9 should be used for emergencies and assistance only.

PAT HAWKER, G3VA

Adaptable typewriter interface

Simple interface connects electronic typewriter to computer parallel output port. Self-documenting Pascal code facilitates translation into other languages that might be used in the target processor, and demonstrates how a printing routine is constructed rather than provides a rigid routine for only one situation.

Acquisition of a home-based computer requires a decision as to the type of printed output needed. The provision of a fully-formed letter printer allows a system to be used for word processing with a degree of professionalism that is absent from the usual low-definition dot-matrix machine. If an electronic typewriter is available then the simple interface described here enables it to be driven from a Centronics or other parallel output port.

The interface is in principle applicable to any typewriter mechanism that uses electronic-style switches to complete a circuit when a key is depressed. Virtually all daisy wheel printers use this type of mechanism. Since the majority of small computer systems do not have printer spooling (i.e. the system is dedicated to driving the printer whilst the printer is active) the computer is used to provide as much as possible of the intelligence of the interface.

Although the interface itself is simple it is necessary to do some investigation to determine the correct connection points for the various wires – and then further work to find the correct data for each printed character. The interface was actually connected to an Olivetti Praxis 35 and the specific data as to connection points and character data refer to this machine. Enough information is included to enable adaption to any other machine.

General considerations

In operation the printer sequentially grounds one of the lines marked A through H and reads the data appearing on all the lines a through h, Fig. 1. If no keys are closed then the data will be read as all high but otherwise the occurrence of a low will allow the closed key to be detected and decoded. Two points about this – first, a number of reads must give the same data for the printer to register the key closure and to avoid errors due to contact bounce. Second, not all possible crossing points on the matrix are used and so there are a number of possible data codes that may have no meaning to the printer as they should not be generated by the keyboard. Also there are two connections outside the matrix (I to i and J to j) used to tell the printer about keys that are pressed in conjunction with the main keyboard. Examples of this on the Praxis are Shift

by
C. M. Fortescue-Webb M.Sc.

and Keyboard 1 or Keyboard 2.

To simulate a key closure the circuit of Fig. 2 could be used. When the select key line is true then the low-going pulse on the input line be coupled through to the output. By using open collector gates there will be no interaction between the various keys. The difficulty of such a scheme is that a key select line is needed for every key and this requires a lot of hardware. By using a multiplexer and demultiplexer coupled with open collector drivers the final arrangement shown in Fig. 3 is realised. Now three lines are used to select the input row and a further three to select the output column. The remaining two lines on the eight-line computer output are used for the shift and keyboard 1/2 switches. Incidentally, if your computer will only output a seven-bit character on the parallel port then the keyboard 1/2 or equivalent line will have to be operated manually.

It is also necessary to prevent the computer passing data to the printer at a rate in excess of that at which it can accept the data. The interface shown here uses a software delay loop in the driving routine to ensure that the character rate is within specifications. A longer delay is used for those functions on the typewriter that take longest – carriage return (up to two seconds on the Praxis), fast return (timing as carriage return) and tab. The alternative is to use hardware consisting of something like a 555 timer with a variable current source depending on the character being printed, with the output from the timer being the busy line and used for character separation. To achieve a maximum transmission rate it would be necessary to find an internal (to the printer processor system) status line that will show if the printer can accept a character and then use this line for the BUSY/ACKnowledge reply to the computer.

When the computer outputs data on a Centronics interface the strobe line is made low for a short time (a few microseconds) to tell the printer that data is available.

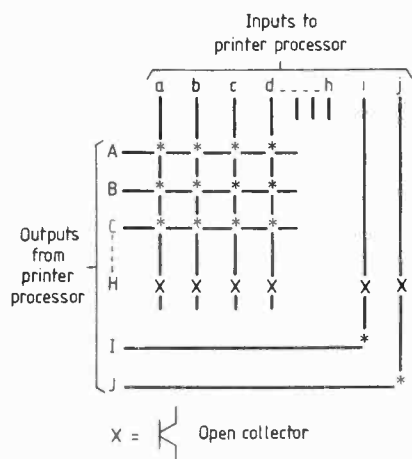


Fig. 1. Schematic of the matrix switching layout of typewriter keyboard. A keyswitch is present, normally open at intersections marked*. Pull-up resistors to V_{cc} are connected to lines a to j inclusive.

The printer responds by asserting BUSY and should pulse ACKnowledge low to signify that the character was accepted. When the printer is ready to accept another character it will drop BUSY. Many computer systems are content to ignore either BUSY or ACKnowledge but printers requiring line buffering (normally line printers) may use ACKnowledge to fill the line buffer and then assert BUSY whilst the characters are printing. Strictly the computer is not permitted to change the data on the Centronics port between the assertion of STROBE and the receipt

Charles Fortescue-Webb has been designing and producing microcomputer systems and electronic interfaces for eight years, with experience as chief engineer for a turnkey systems house in Ireland and as an independent consultant in microcomputer applications. His primary degree is in experimental physics and was followed by applied biological research for a M.Sc. degree. Application of minicomputers to the analysis and costing of civil engineering structures led onto work with microprocessor systems. His hobbies include sailing, bridge, woodworking and tinkering with cars and electronics.

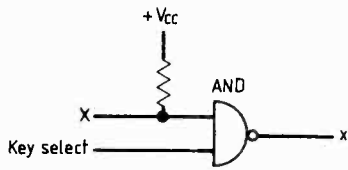


Fig. 2. Possible connection method to simulate a key switch connection when key-select is high. This circuit would be substituted at each * in Fig. 1, in which case a low on X will be coupled through to x via the open collector gate.

of an ACKnowledge, nor to assert STROBE whilst the printer is BUSY.

Circuit details

The functioning of the actual circuit is straightforward and the full schematic is shown in Fig. 4. The layout corresponds to that used in Fig. 3. The monostable between the strobe and busy lines is used to separate a multiple sequence of the same character into separate 'key depressions' by enabling the LS138 for a set time after each strobe pulse. The period of the monostable must be adjusted to be sufficient for the printer to recognise the character yet less than the intercharacter delay and the shown values provide a good starting point. The maximum R value is about 5kΩ due to limitations of the LS t.t.l. inputs.

The original was constructed on Vero d.i.p. breadboard using ribbon cable to couple the inputs and outputs. If a small system is being used then it may be more convenient to add on a eight-bit latch to the computer address/data lines rather than construct or purchase a specific parallel port.

If the keyboard uses greater than five volts then a small 5V supply will be needed for the logic and the inputs to the LS151 should be isolated using diodes connected in series with the lines to the LS151 from the keyboard with the anode connected to the interface. If a key is pressed on the keyboard whilst the interface is connected then the keyboard supply voltage can be coupled through to the multiplexer unless isolation from higher voltages is implemented.

The typewriter/printer lines are shown with the connection schematic for the Praxis. It is possible that your warranty on the typewriter could be effected by connecting this modification and so it is perhaps wise to wait until it is out of the warranty period. When making connections to this main board be aware that mos chips may be used internally and so static should be avoided (no nylon carpets, plastics worktops etc.). A soldering iron with low leakage or securely grounded would be a wise precaution if using soldered connections. If using a mains-powered wire-wrap tool then do not work on the interface whilst it is connected to the keyboard.

Detective work

One of the first operations is to examine the keyboard connections of the selected machine to ensure that it is possible to

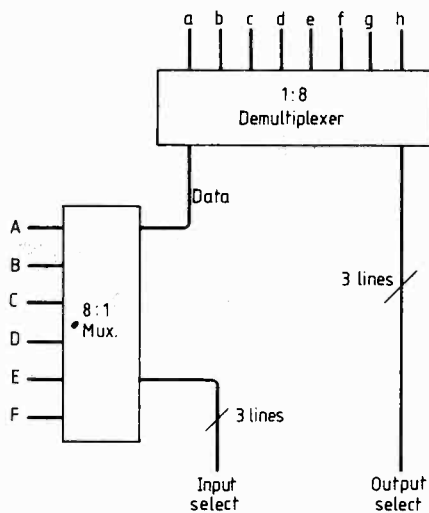


Fig. 3. Using a multiplexer and demultiplexer to replace a keyboard.

make the connections without having to, for instance, replace the complete case. First be quite sure that the mains cable is removed from the machine - a surprise jolt when you are probing inside the machine can do much damage to man and machine. On the Praxis after unscrewing the two platen knobs, without losing the small disc in the left hand one, four screws in the underneath of the case can be removed. Turning the case right side up again should enable the top section to be lifted off over the back of the machine. Be careful of the paper-holding bar. The keyboard can now be removed by undoing the two screws, one at either end, that hold the metal backing plate to the base of the typewriter case.

Lifting it off gently brings to light a number of connectors and these can be parted without putting any tension on the wires. At this stage the printer processor and electronics will be exposed to view along with three brass nuts positioned on the processor board that hold grounding straps and the processor board to the keyboard sub assembly. After noting the way in which the grounding straps are positioned the nuts can be undone and the keyboard and processor unfolded to show the printed circuit traces of the keyboard and processor connections. A drawing of the two boards opened out is shown at Fig. 5 with the connection points numbered to correspond with the schematic diagram Fig. 4.

Suppose that the typewriter is a different model from that used above. Then some investigation is necessary to find the connecting lines. Without the manufacturer's service manual the best method is to follow the printed circuit traces to the various keys. Keyboard switches may have either three connections (with the outer two commoned-check with a meter) or just two. The key connection traces should either end up on a chip with open collector drivers (in which case they are being driven from the printer processor) or else be connected to pull-up resistors if an input to the processor. If the keyboard processor combination can be 'powered up' whilst access is retained to the keyboard traces then processor output wire should have no or small voltages on them whilst processor input traces should be at 5V due to the pull-up resistors. In any event, provided that the keyboard is powered from five volts, an incorrect connection of the traces

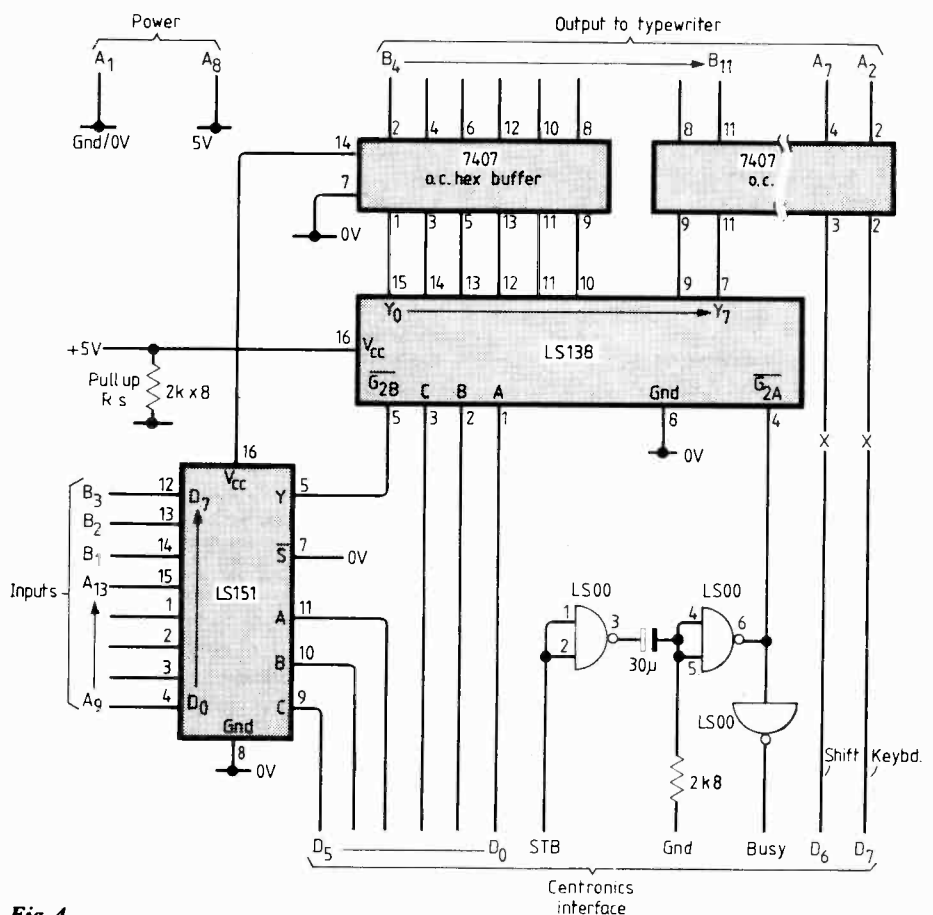


Fig. 4.

to the interface will not cause damage but prevent the interface and/or the typewriter working properly. There is no need to assign specific assignments to each of the input/output connections on the interface since a software routine is used later to determine the actual data required to

simulate a specific key closure.

The next stage is to determine the output data required for each simulated key closure. Connect up the computer-interface-typewriter combination and then run a program to output characters (with data values in the range of 0 to 255) and see

List 1. Program to produce a file 'Trans. text' of ascii character and corresponding code to operate printer.

```

Program Decode; (* Pascal under UCSD Version 4 *)

var Translation_file : text; (* data and character file *)
    Printer          : text; (* Treated as a file *)
    j                : integer; (* loop variable *)
    ch               : char; (* character read from vdu *)
Begin; (* program from hereon *)
Rewrite( Translation_file,'Trans.text'); (*Open Output file *)
Rewrite( Printer,'Printer:'); (*Open Printer*)

For j := 0 to 255 do begin; (* main loop *)
    Write(printer,chr(j)); (* data to printer *)
    Write(' Enter character printed ( ^ for non printing)');
    Read(ch); (* read character inputted from vdu *)
    writeln; (* new line on vdu *)
    writeln(Translation_file,j:5,ord(ch):5); (* write to file *)
end; (* end of main j loop *)

Close(Translation_file,Lock); (* keep the translation file *)
end.

```

List 2. Program to show how translation data can be used to run typewriter using codes from program in List 1.

```

Program Encode; (* Uses translation file to print on typewriter *)
Const cr = 13; (* carriage return ascii value *)
Var Printer : text;
    Decode : Array(0..255) of 0..255; (* holds printer codes *)
    k      : char; (* only used in demonstration program *)

Procedure PRINT_INIT; (* Initialises for the Printer *)

Var Translation_file : text; (* data setup in program DECODE *)
    data, code, j : integer;

Begin; (* procedure Print_init *)
Reset ( Translation_file, 'trans.text'); (* Open file *)
For j := 0 to 255 do Decode(j) := 0; (* initialise Decode array *)
For j := 0 to 255 do begin; (* file data to decode *)
    Read (translation_file, data, code ); (* read a line from file *)
    Decode(code) := Data; (* and put to decode *)
End; (* of the j loop *)
Close(Translation_file); (* no further need for this *)
Rewrite(Printer,'Printer:'); (* open printer for output *)
end; (* of procedure Print_init *)

procedure delay(ticks:integer); (* gives a 'ticks' milliseconds delay *)
var i,j,k:integer;
begin;
    For i := 1 to ticks do
        For j := 1 to 8 do k := k+1; (* 1 ms delay *)
        end;
end;

Procedure PRINT ( ch: Char ); (* accepts a character for printing *)

Var i : integer;

Begin; (* Procedure PRINT *)
i := ord(ch); (* find integer value of ascii character *)
i := decode(i); (* and use to get printer data *)
write(Printer,chr(i)); (* and output to Printer *)
if ch = chr(cr) then delay(1000) else delay(90); (* 11 c/sec *)
end;
End; (* of Procedure Print *)

Procedure PRINT_EXIT; (* called after finished with printer *)

Begin; (* start of Print_exit *)
print(chr(cr)); (* Carriage return to Printer *)
Write(Printer,chr(255)); (* Holds interface out of action to
enable all typewriter functions *)
Close(Printer); (* No further use for printer *)
End; (* of Procedure Print_Exit *)

BEGIN;

(* This is where your main routine would be. The following
is a short sample Program that can be used to test the
interface, and would not be present for normal use *)

Print_init; (* initialise the printer channel *)

For k := 'A' to 'z' do begin;
    write( k ); (* put out the character on vdu *)
    print ( k ); (* and on the printer to check correct action *)
end;

Print_Exit; (* and close up the channels *)
END.

```

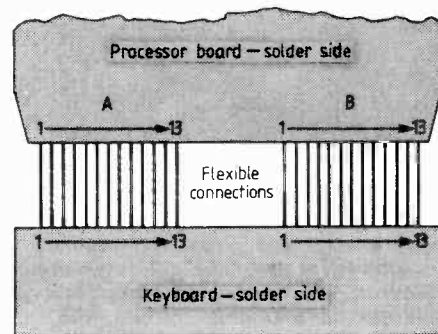


Fig. 5. Connection points on the opened out Praxis processor and keyboard.

what the response is from the typewriter. Be aware that some of the unused code can cause the typewriter to 'lock out' and not accept any more input. If this should happen the easiest way to recover is to turn the typewriter off then on again to reset the internal mechanism. Also some software driving parallel output ports will only output seven bits, the most significant bit being masked off as it is not used by many printers. If this is the case with your system then either the driving software can be altered or alternatively one of the dedicated lines (I...i, J...j) in Fig. 1) can be deleted.

In the case of the Praxis this would mean that keyboard 2 was not available but for many applications this would be quite acceptable. The program in Fig. 6 which is written in Pascal will provide you with a file of the data and corresponding characters printed. If you find that the interface is behaving badly, for instance by not printing all characters then check both the interface and connections to the keyboard traces. It is easy to have 95% functionality even though the shift line say is not connected.

Operation

The final step is to generate a small program that takes any character that you wish to output to the printer, translates this to the appropriate data code, and then outputs it on the parallel interface. The best method of implementing such a routine is in assembly language and then to incorporate it into the bios (basic input-output system) so that the operation is transparent to the host program. To give an idea of what is required and to provide a basis for further experimentation the small routine shown in Fig. 7 is written in Pascal and can be incorporated into an applications routine. The routine is broken up into three procedures: Print-init to open the printer channel, Print to actually translate and output the characters and Print-over to perform any closing tasks. Note that the main translation array TRANS must be declared in the main routine since Pascal cannot hold local variables from call to call of a sub routine. If you wish to use the printer for word processing then you will probably want to extend this program to enable such things as underlining and printing both £,p and \$,c.

continued on page 39

Improving colour television decoding

4 – Simple one-line comb decoder on a small single board can be added to existing receivers

Much of the background material and illustrations in these articles derives from the author's BBC work and that of his colleagues in the Research and Designs Departments. The particular proposal for a domestic receiver decoder described here is the author's own rather than a BBC concept.

Considering now the actual electronics, Fig. 34 shows a circuit diagram of the video path built to incorporate the

The full extent of picture improvement can only be achieved if the suggested modifications are incorporated into a receiver in which attention has been paid to a number of other aspects of performance, a similar experience to improving high quality audio. These would include the use of a 26in tube (preferably high resolution), an efficient aerial (possibly with a down-lead amplifier), a tuner and i.f. amplifier response flat to 5.5MHz and with the demodulated video group-delay equalized to give minimum phase errors. It would also be beneficial to receive the incoming r.f. signal from a transmitter of good performance.

The performance of the modifier used to comb chroma from the composite signal (to provide clean luminance) is degraded in the presence of phase errors. These errors are largely introduced by the video signal modulation and demodulation processes and mainly comprise poor group delay response across the chroma bandwidth ($f_{cc} \pm 1.3\text{MHz}$) and by differential phase (chroma phase shift with the change of luminance level).

Further information on transmitter performance and alternative circuits to place between the i.f. output and the PAL decoder will be given in a later article. These alternative circuits would be preferable for smaller screen sizes (assuming the standard tv receiver tube).

Some other developments which will be of relevance if the time delay for their introduction and cost are not too great are ITT's digital tv i.cs and the Philips n-mos memory chips. Philips also make a high resolution 26in tube (which will probably double the standard tube price) that can be operated at twice the normal line and field scanning rate. Memory chips store the incoming signal over a field or picture period; video information is thus available for scanning twice in the period of one input picture. This double scanning removes flicker and enables other decoding methods to be used, as outlined in the December and January articles. (See also the German Radio Show report, November 1983 issue pages 74, 75.)

by D. C. A. Read
B.Sc. (Eng), M.I.E.E.

foregoing principles (part 2, January issue). Composite video (1V pk-pk) is applied to the circuit to produce outputs that are suitable for the various decoder chips now readily available. Output pins can directly feed the decoder chips TDA3516A or 3560 from Mullard.

Transistors Tr_1 and Tr_2 are complementary emitter followers providing low-impedance drives, appropriate resistors being fitted to match the delay-line characteristic impedance and the chroma bandpass filter impedance. Also, a low-impedance feed is available for the sync filter which is an optional extra. The three coils and capacitors (L_{1-3} , C_{5-7}) form a symmetrical gaussian bandpass filter (described later) set up by adjusting all three inductors so that maximum subcarrier level occurs at the output, also with minimum 7.8kHz at chroma transitions.

The filtered chroma signal is fed out via Tr_{18} to provide low-impedance drive to the chroma input pin of the demodulator chip or chips. PAL decoding i.cs normally use a

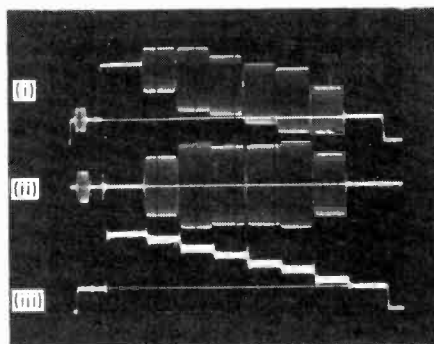


Fig. 35. Modifier comb-circuit waveforms. Top trace is the input composite PAL video signal, middle trace shows the chroma envelope after the Tr_1 , Tr_2 buffer and gaussian bandpass filter. After a further buffer this signal is fed out to pin 3 of the decoder TDA 3561A (or 3560) (if the one-chip decoder is used). Minimum 7.8kHz twitter at chroma transition indicates good group delay symmetry in the gaussian filter. Bottom trace is the luminance signal as fed to pin 10 of the one chip decoder.

chroma-length line (64 μ s–56ns) to provide delay-line PAL decoding for enhanced U/V separation in the chroma circuits. Colour prints 7, 8 and 9 are screen photographs with luminance off, showing, in print 7, the chroma demodulation performance using the field sweep skew test waveform for line-by-line decoding. Print 8 shows one chroma line in use i.e. combing the chroma over two lines; this is the standard method in most television sets. Using two-line delays, print 9 shows three-line combing in the ratio 1/4:1/2:1/4. The third line has no offset whereas the centre line has a 56ns offset. No further chroma work was felt necessary on this add-on card and this design will use one chroma line. This is a reasonable compromise which provides some comb filtering of the luminance, a 3-dB reduction of fine cross-colour, and, by adding and subtracting equal amplitude from the two lines, a 3dB reduction of random noise occurs. The slight loss of vertical resolution is only apparent when viewing computer graphics. Spatially, on horizontal transitions, the luminance and chroma are displaced by half a line in the field, but this is only seen on electronically generated signals.

In the circuit of Fig. 34, Tr_3 amplifies the signal from the chroma bandpass filter to provide a high level input for the DL60 delay line, which has a typical insertion loss of 11dB. The output transducer of this delay line is floating and can therefore provide a balanced push-pull drive to the MC1596 balanced modulator input with the d.c. supply bias provided by resistors


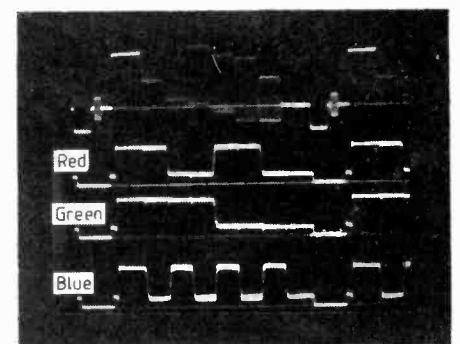


Fig. 37. Signal waveforms for the complete decoder. Top trace is 1V composite video input. The lower three traces are red, green and blue outputs from the modifier comb and TDA3516A (or TDA 3560) chroma chip.

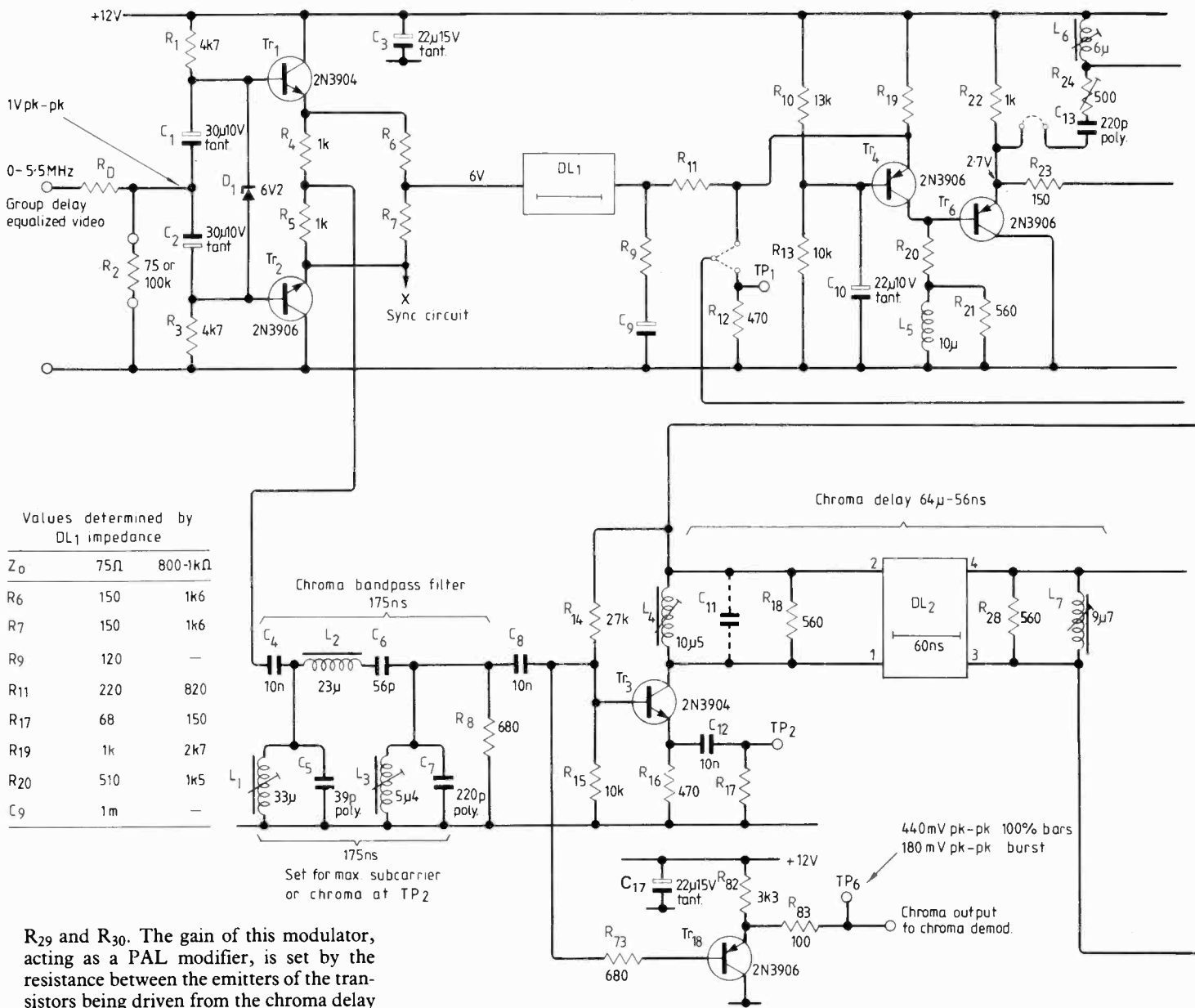

R₂₉ and R₃₀. The gain of this modulator, acting as a PAL modifier, is set by the resistance between the emitters of the transistors being driven from the chroma delay line. Pins 7 and 8 have suitably phased and d.c. balanced (R₄₂, 5kΩ pot.) drives of 8.8MHz (twice colour subcarrier) taken from the chroma demodulator chips via buffer stages Tr₈, Tr₉ which also provides phase shift. The two phase shifters plus the changeover shown adjacent to C₂₈ and C₂₉ mean that the change in phase setting available to the modulator is in excess of 360°. Thus a setting will always be found, regardless of the decoder chips being used, to obtain the correct phase in the overall system. Pin 9, the demodulator output is fed directly to a grounded base stage via 10nF blocking capacitor (C₂₁). Therefore no signal can be seen at pin 9. Also summed at the grounded base stage is the composite PAL video from the luminance delay line. The delay of this, compared with the delay time through the gaussian bandpass filter plus the DL60 delay line and the modifier, is such that the two signals summing at the grounded-base stage are exactly 64µs apart.

The collector load of Tr₄, R₂₀, gives sufficient gain to provide a suitable level to the output filter, this being buffered by emitter follower Tr₆ and R₂₃ (150Ω) representing the characteristic impedance to the output filter.

The first sections L₈ and L₉, form a

phase/group delay equalizer as is L₁₀. The filter itself is formed by L₁₁ and L₁₂; the last element in the filter L₁₂ has an additional capacitor switched in by the f.e.t. to bring it to resonance at subcarrier frequency when the notch is needed, such as at a horizontal colour transition. As the notch switches in and L₁₂ becomes resonant, the input impedance to the filter rises. The small resulting increase in voltage available at Tr₆ emitter therefore drives Tr₅ harder and the notch 'snaps in' with a positive-feedback effect. Components L₆ and C₁₃, with variable resistor R₂₄ are in series resonance at subcarrier frequency; R₂₄ is adjusted to set the threshold of the notch. The notch will switch in very quickly with Tr₅ bottoming on the peaks of the 4.43MHz oscillations developed across L₆. With R₂₅ of 10MΩ the decay is slow, switching the f.e.t. off about half a line later.

If the voltage supplied to the gate of this f.e.t. is displayed on a black and white receiver with an external sync feed and viewed adjacent to the colour receiver, the amount of time the notch is in is shown to represent a very small proportion of the total picture area. The loss of resolution

can therefore be considered slight. It is also statistically unlikely that fine luminance detail will occur on horizontal colour transitions when the notch is switched in.

If luminance detail is continually present at 4.43MHz, the notch will be introduced and detail lost; it is as if the notch were always present. But the delay in operation of the adaptive notch switch will allow luminance edges through unscathed and this gives subjective improvement to the picture resolution.

It has been found in practice that with an input of test card F from a slide scanner, the threshold control resistor is best set so that the 4.5MHz gratings pass through with minimal degradation. Subcarrier from horizontal coloured edges will then cause the notch to switch in if the amplitude increases above the equivalent amplitude of this 4.5MHz grating. The 4.5MHz grating on the analogue test card (about to be replaced by a digital one) is well below the 0.7V black-to-white amplitude. However, switching to the electronically generated signal Channel 4 test card, the notch is permanently in during the 4.5MHz grating. But on pictures, the notch switches in when horizontal dot

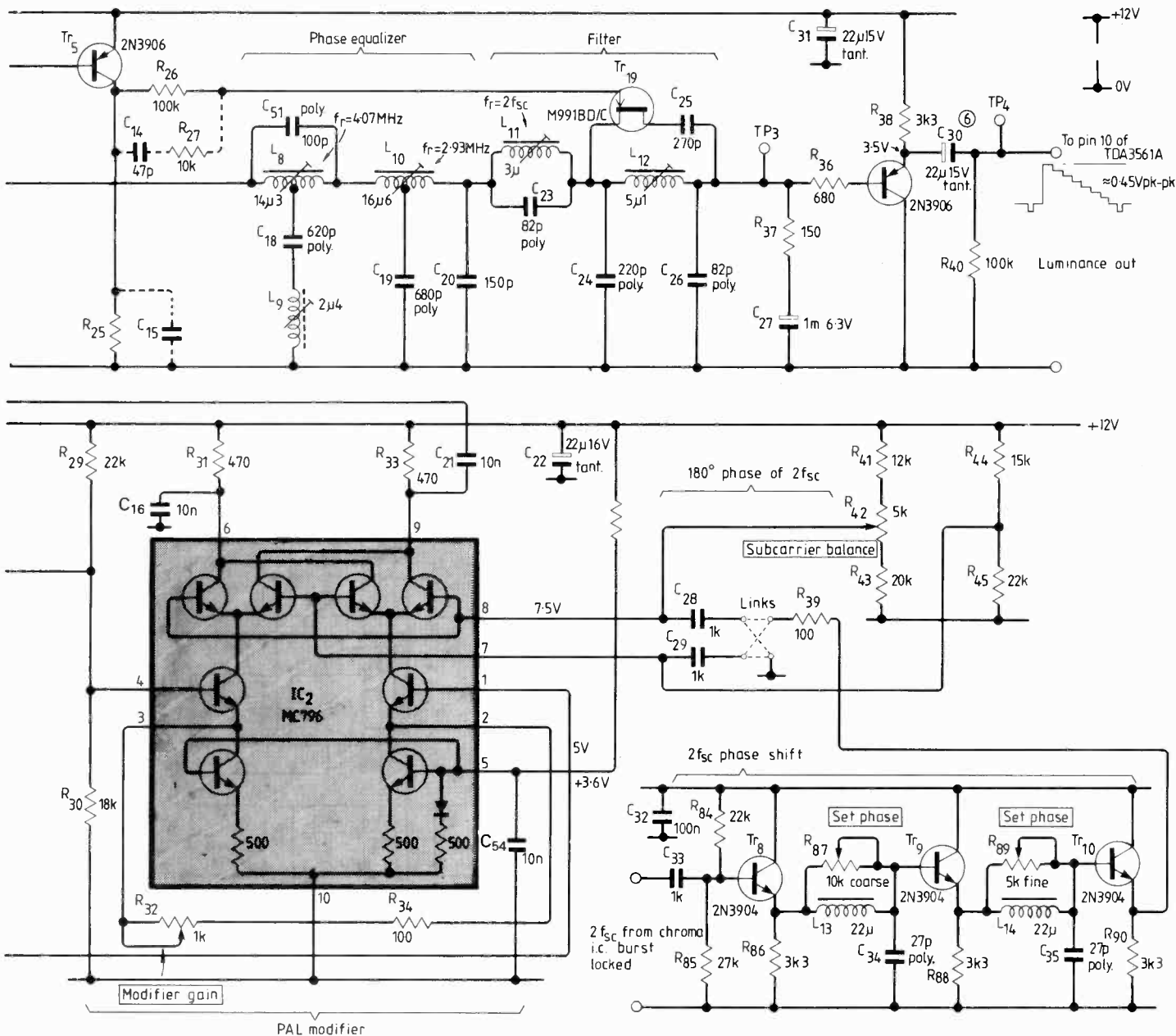


Fig. 34. Diagram of circuit that processes chroma and luminance signals.

Notes

- ① L₅ and R₂₁ can provide 1 to 3dB h.f. lift, normally shorted by link.
- ② R₂₅ 10MΩ for slow turn-off of adaptive notch, 100kΩ for fast turn-off
- ③ C₁₄, R₂₇ slightly speed-up switch-on but need not be fitted. Set for best 2T lobes
- ④ C₁₁ not fitted but can be used to trim phase
- ⑤ Poly = 2% polystyrene Cer = ceramic disc or Redcap/Bluecap
- ⑥ C₃₀ 100μ 12V Mullard for three-chip decoder. Lum. input has 2k7 in series & 22k to 12V. Remove R₄₀
- ⑦ Refer to next installment for filter adjustments
- ⑧ Inductors are wound with Sor6-strand 48s.w.g. Litz or 38s.w.g. (0.16 or 0.14mm dia.) enamelled copper wire

crawl becomes just visible at normal viewing distance, assuming $\leq 3.5 \times$ screen diameter. This seems a suitable criterion for determining the threshold of the notch. It may be considered that a slightly lower threshold which degrades 4.5MHz gratings on the test card will further reduce visibility of horizontal dot crawl. This is a setting which will be made subjectively to suit the individual.

At the output of the filter the signal is terminated (R₃₇, 150Ω) and buffered. Transistor Tr₇ provides a low-impedance drive output as many clamps in decoder


chips require a low-impedance point. The coupling capacitor may have to be changed to suit the time constant of such clamps, depending on whether the extra circuit board is fitted to a three, two or one-chip decoder.

Setting-up procedure (luminance)

In the first place, it is required to obtain a timing difference between the two signals summed at Tr₄ emitter of exactly 64μs. 100% colour bars are used as the test signal, although 95%, 75% or EBU bars would be suitable.

Inductor details

No.	Value (μH)	Turns	
		Neosid E2	Toko 10K
1	33	37	55
2	23	34	42
3	54	15	18
4	10.5	21	27
5	5	Painton or Sigma choke	
6	6	16	21
7	9.7 or 10	20.5 or 13+13	26 or Sigma choke
8	14.3	13+13	16 16
9	2.4	10	13
10	16.6	14+14	17+17
11	3.8	13.5	16
12	5.1	15	18
15	150	Painton or Sigma choke	

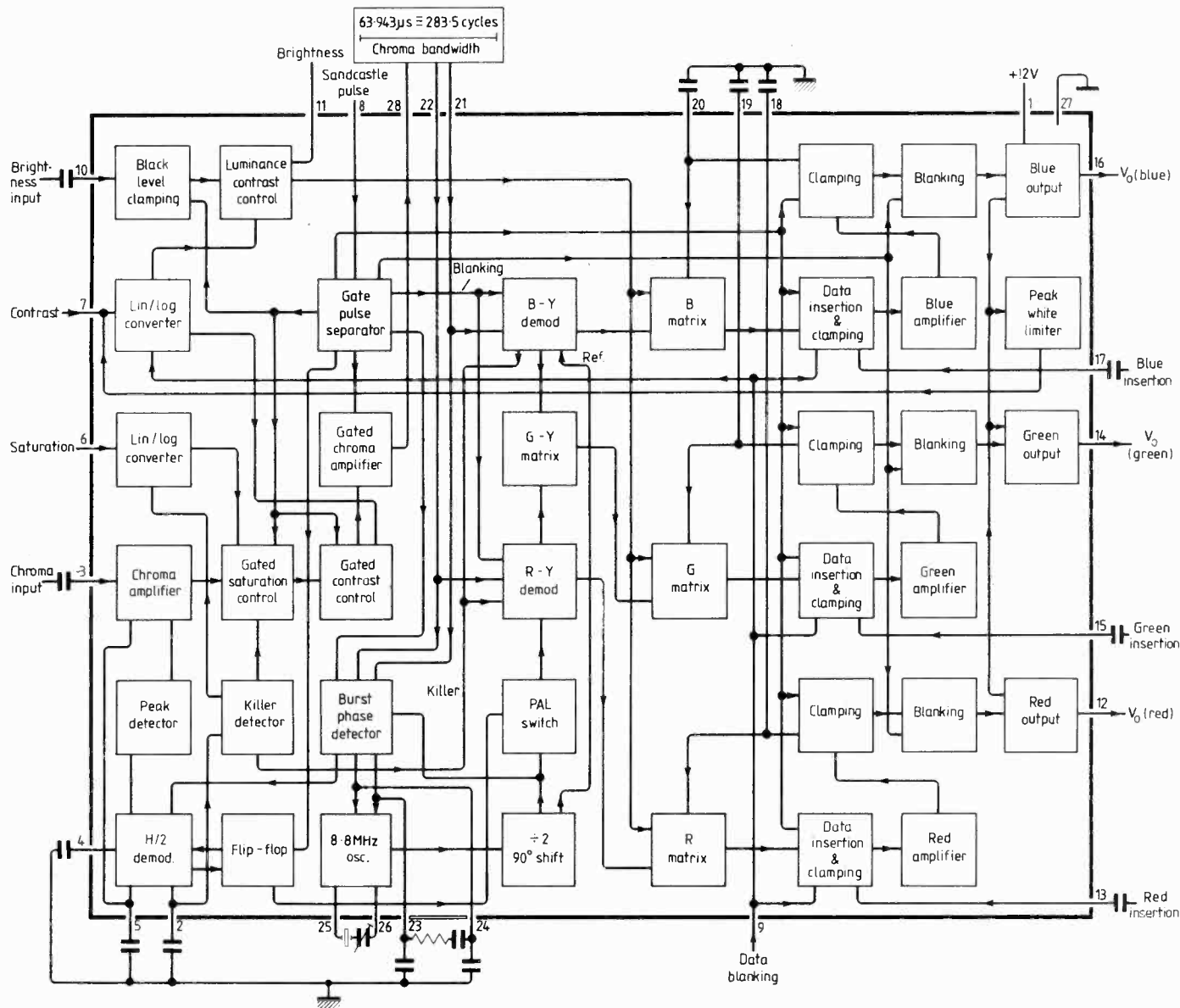


1. Disconnect either the input or output end of DL₁, and with the 2f_{sc} feed also disconnected (by removing the links adjacent to C₂₈ and C₂₉) unbalance the modifier pins 7 and 8 (R₄₂ turned to an end-stop).
2. With the output of the modifier linked to R₁₂, TP₁, the chrominance passing through the gaussian filter and DL60 delay line can be displayed on an oscilloscope and the signal path checked.
3. Reconnect the modifier Tr₄ emitter so that the chroma envelope can be seen at the output test point TP₄ (Fig. 34). The waveform appearance should be as shown in Fig. 35, middle trace. The green/magenta centre transition, will need to be expanded on the oscilloscope so that the signal is resolved down to 50ns (see Fig. 24, January).
4. The link at TP₁ is switched so that the modifier output is across R₁₂ and is not fed into Tr₄ emitter. Reconnect 2f_{sc}, put the oscilloscope probe on TP₁ and rebalance pins 7 and 8 on the modifier so that the carrier (2f_{sc}) is nulled to zero. This represents carrier balance of the modulator/modifier.
5. Again feed the direct composite PAL

The normal functions expected of a PAL decoder are adequately provided by the Mullard one-chip decoder TDA3561A. The chip requires separate chroma and luminance inputs - the circuit of Fig. 34 provides these in enhanced form. Pin 25 feeds PAL modifier via Tr₁₅ in Fig. 34.

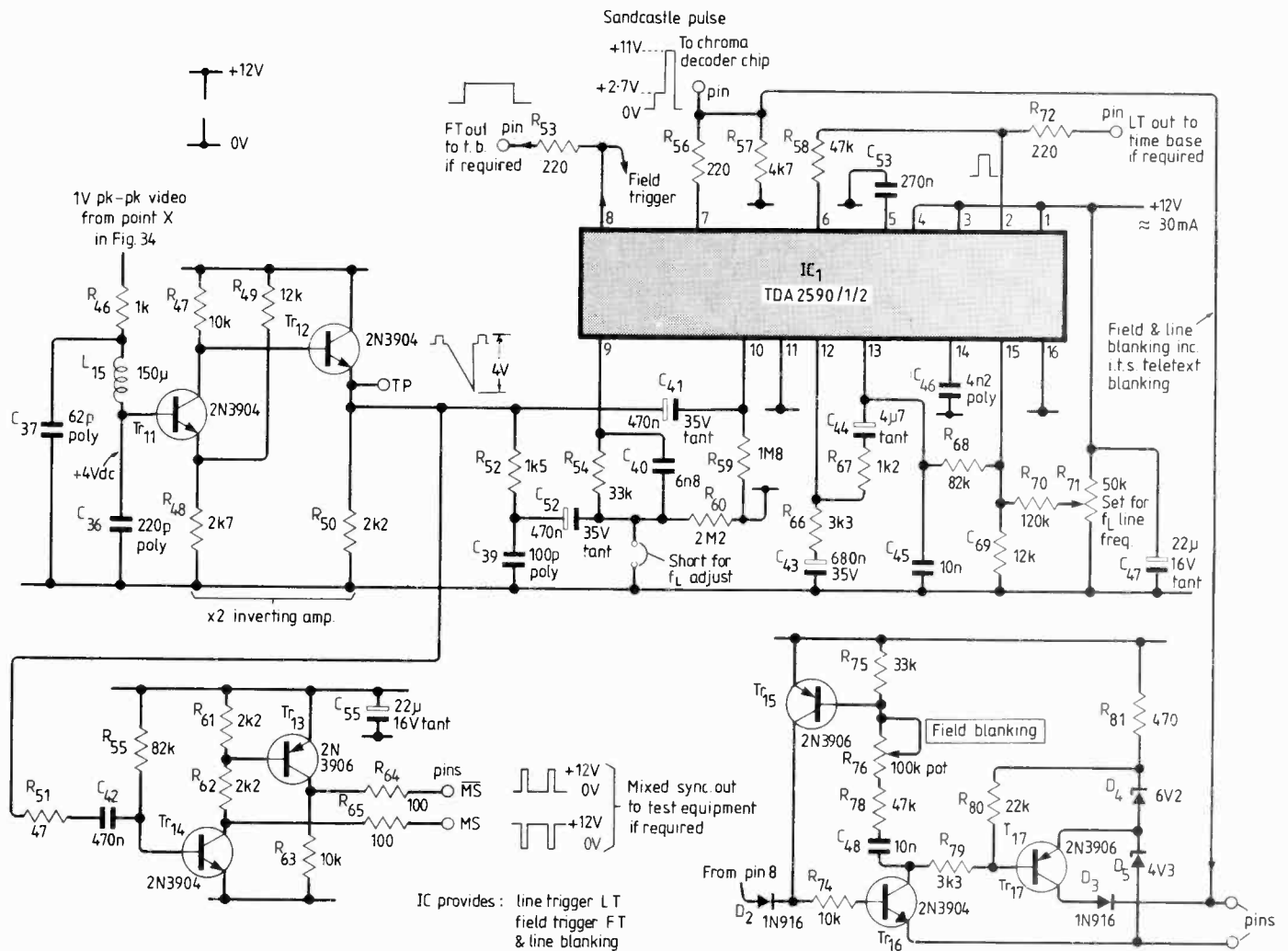6. Disconnect either the input or output lead of DL₁ as before, re-connect the modifier (link at Tr₄ emitter), adjust the gain of the modifier with R₃₂ (1kΩ pot.) to obtain the same chrominance amplitude as in preceding step.
7. Reconnect the luminance (link at DL₁), with the chrominance from the modifier also being summed at Tr₄ emitter, it only remains to adjust the phase of

- the modifier output. Using R₈₆ (10k pot.) and R₈₉ (5k pot.), the coarse and fine phase adjustments in the 2f_{sc} feed (and, possibly, the links adjacent to C₂₈ and C₂₉ for 180° change), a point will be reached where the phase of the chroma from the modifier will cancel the chroma of the composite PAL signal.
 8. The amplitude of the 2f_{sc} feed from the phase shifting stages Tr_{8,9,10} can be from 0.3 to 1.3V pk-pk and it may be necessary to adjust C₃₄ and/or C₃₅ to obtain reasonably constant amplitude as the appropriate 'set phase' controls are taken between end stops. Check at Tr₉ emitter first and adjust C₃₄ on test for constant amplitude over the full range of R₈₆. Repeat for C₃₅ and R₈₉.
 9. Finally to achieve the best null and to optimise the chroma cancellation on all levels (steps) of the resulting luminance, a small adjustment on the gain will be required. It is as well to use the gain pot (R₃₂ 1k) the phase pot (R₈₉ 5k) with the modifier balance pot (R₄₂ 10k) in a converging sequence to minimize residual subcarrier for all the steps in the luminance signal.
- The trace in Fig. 35 shows the composite PAL signal as measured across R₂ (input



terminating resistor), the middle trace is the chrominance at TP₂ which is being fed out to the chroma circuits of the demodulator (external to this additional circuitry), and the lower trace at TP₄ shows that the chroma from the modifier output is cancelling the composite PAL chroma to leave a clean luminance signal.

Fig. 36 shows some optional additional circuitry that may be used depending on the receiver to be modified. Point X is taken from the emitter of the input buffering pair in Fig. 34, Tr₂. This feeds a filter with a characteristic impedance of 1kΩ provided by R₄₆. The high-impedance terminated filter has a low-pass linear amplitude response which removes all the subcarrier and highband luminance energy but retains the sync risetimes with optimum shape. The filter design will be detailed later with group delay/phase and amplitude responses. Transistor Tr₁₁ amplifies the signal and Tr₁₂ emitter follower drives the sync separator chip IC₁, (TDA2590). There are other versions i.e. 2591, 2592, 2593 but in this application the available alternatives are not important. All the chips are capable of driving line output stages and field scan i.cs directly.

The chip has a sync-slicing system which is self-adjusting, according to the video amplitude, to maintain a 50% slice on sync edges. The line frequency can be set to approximately 15.625kHz using R₇₁ (50kΩ pot) with the input signal shorted at the points shown adjacent to C₅₂, R₆₀.

Fig. 36. Diagram of circuit of sync processor chip providing field blanking and other pulses.

When the short is removed, the phase locked loop is centralized. This chip also provides field triggers and line triggers. By feeding the line trigger output pulse back into the chip (on pin 6 via R₅₈) a 'sandcastle' pulse is generated which, if necessary, is then available for the chroma decoder chip. In most of the receivers, however a sandcastle pulse is already available and this circuitry would not be required.

The line and field trigger pulse trains could both be used to drive line and frame time bases if the whole receiver is being engineered. There is another optional circuit available. This widens field trigger pulses via the monostable (Tr₁₅/Tr₁₆) and thus provides blanking of the IFS (insertion test signal), and teletext (Ceefax and Oracle) and other data signals in the field block. See Fig. 38.

On the author's attic workroom receiver, the picture is underscanned so that all four corners can be seen and the 'business' at the top of the picture becomes unacceptable without widened blanking. The extra blanking circuit ensures that only active picture lines are displayed. The other optional extra, formed by Tr₁₃ and Tr₁₄, is solely used to drive test gear which needs to be locked to mixed syncs.

The luminance output of the board from Tr₇ can be coupled into the Mullard one-

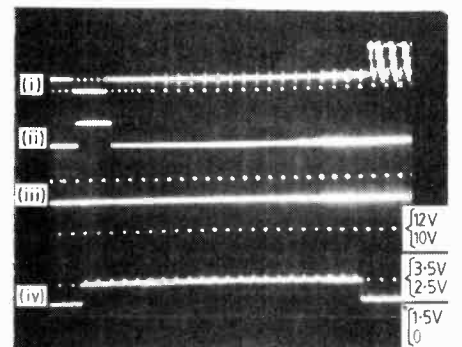


Fig. 36(b). Some of the waveforms occurring in Fig. 36 circuit. Trace (i) is video signal fed to pre-sync separator filter C₃₇, L₁₅ and C₃₆. (ii) is field trigger from pin 8 of TDA2592 and (iii) line trigger from pin 2. (iv) shows RGB clamping (top), output picture blanked (middle) and active picture - line and field blanking off (bottom).

chip TDA3561A (or 3560) which is mainly used as a colour decoder (see Fig. 20, January issue pages 54, 55). The coupling component feeding the luminance input, on pin 10 can be a 0.47μF non-polarized ceramic/polyester capacitor. The chrominance input on pin 3 fed from Tr₁₈ also requires d.c. blocking; 10nF is suitable. The d.c. on both pins 3 and 10 of the decoder chip are typically 2.2V and the output on Tr₇ is typically 3.5V. If a small tantalum capacitor is used, check for polarization particularly where other chips are employed.

Full amplitude levels in ITS and the high levels of teletext plus ICE signals (internal communications equipment) need to be fully blanked.

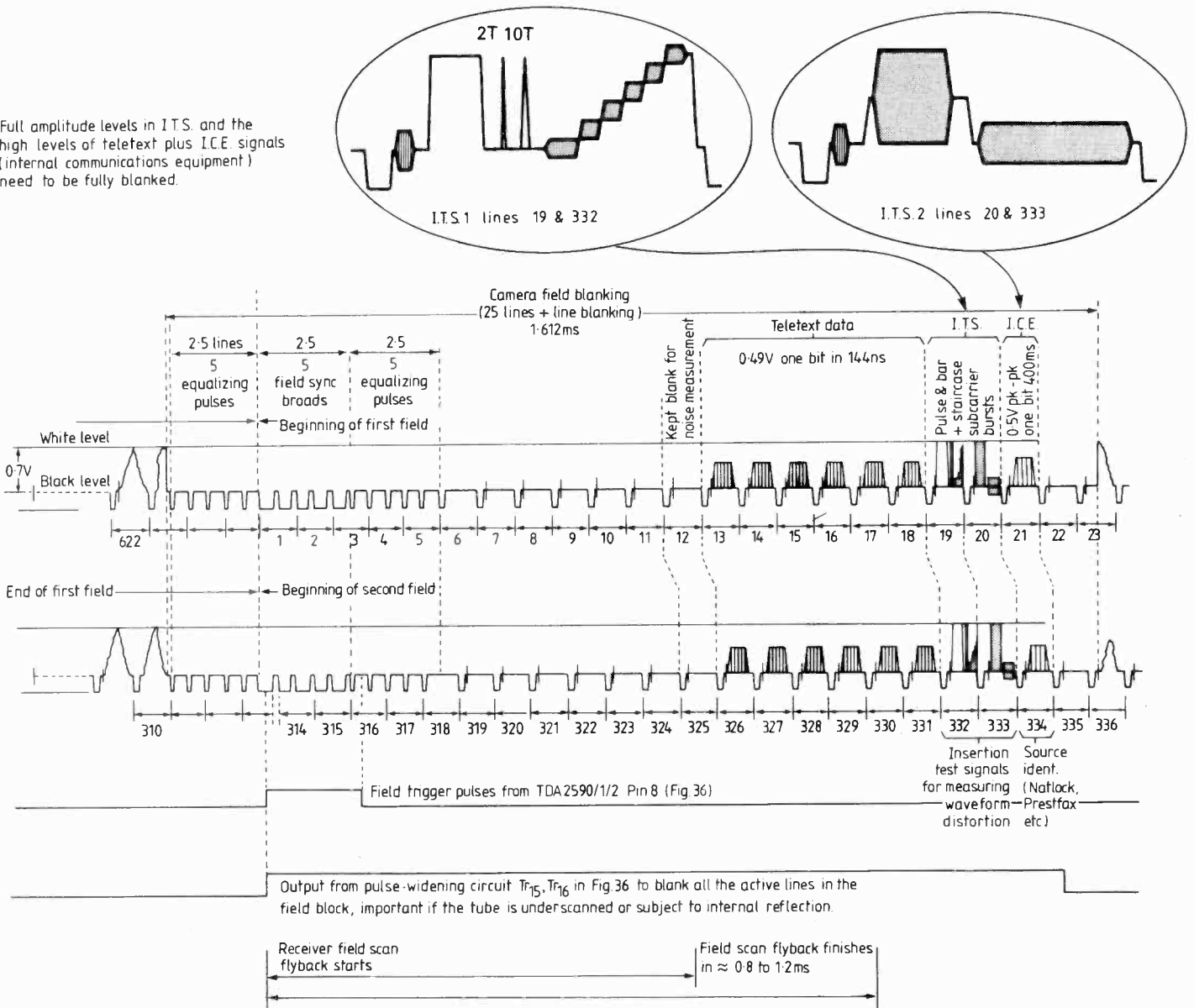


Fig. 38. Vertical synchronizing and blanking waveforms. As shown, field blanking interval lines are also used for teletext, ICE (internal communications equipment), ITS (insertion test signals), and clear lines for noise measurement. TDA2562A also uses lines 21, 22, 23 for RGB tube black-level stabilizing.

insertion test signal (two lines per field), teletext information (four lines per field or six lines on some channels), and the ICE signal (internal communications equipment coding line), will then all be blanked by the widened field pulse.

With the extra board (modifier etc.), set up, the picture will attain a horizontal resolution which is close to the vertical resolution. The equivalent vertical and horizontal resolutions can be calculated as follows. There are 625 lines transmitted in each picture period (40ms) but as 25 lines are blanked in each field (20ms) there are only 575 active lines in each picture or 287.5 active lines per field. These 287.5 lines determine the vertical resolution, i.e. the maximum number of cycles that can occur within the picture height. The transmitted pictures has a horizontal to vertical aspect ratio of 4:3, so 287.5 vertical cycles are equivalent to 383.3 horizontal cycles. Given that the active line period is 52μs (64μs less 12μs blanking), the period for each cycle of this maximum equivalent horizontal resolution then is 135.62ns (52/383.3). The frequency is to equivalent to 7.37MHz. This is the justification for improving the horizontal resolution.

WW


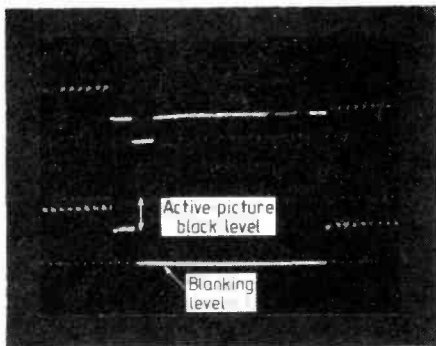


Fig. 38(b). Off-air video signal and extra blanking to prevent any adverse visibility at the picture top. Top trace shows some lines in use in the field blanking period. Bottom trace is final green drive to display tube, indicating line blanking and extra field blanking provided by the circuit of Fig. 36.

Provision was at one time made to adjust the chroma level output with a pair of resistors attenuating the feed to Tr₁₈ base. When adjusting the level feeding the decoder chip TDA3561A or the equivalent two and three-chip versions, it was found to be difficult to determine which chroma level suited the decoder to obtain maximum chroma linearity (the linearity being somewhat poor). Also the matrix which produces the red, green and blue signals

from the luminance and colour-difference signals can have up to 10% and amplitude errors. By optimizing the chroma level and averaging out the matrix errors across the RGB outputs a fairly good compromise can be achieved as is shown in the photograph, Fig. 37.

The blanking as generated by the extra circuitry Tr₁₆, Tr₁₇ and IC₁ (TDA 2590/1/2/3) is applied to the blanking input of the TDA3561A chroma demodulator chip. A line-rate trace of the blanking component is shown in Fig. 37 in which the fainter line represents the field blanking. Using this trace and with the oscilloscope timebase switched to field lock, the pot R₇₆ is adjusted so that the field blanking ends at the beginning of the first line in the active picture. The blanking should end half way through line 23 in the first (even) field, and at the beginning of line 336 on the second (odd) field; see Fig. 38. The

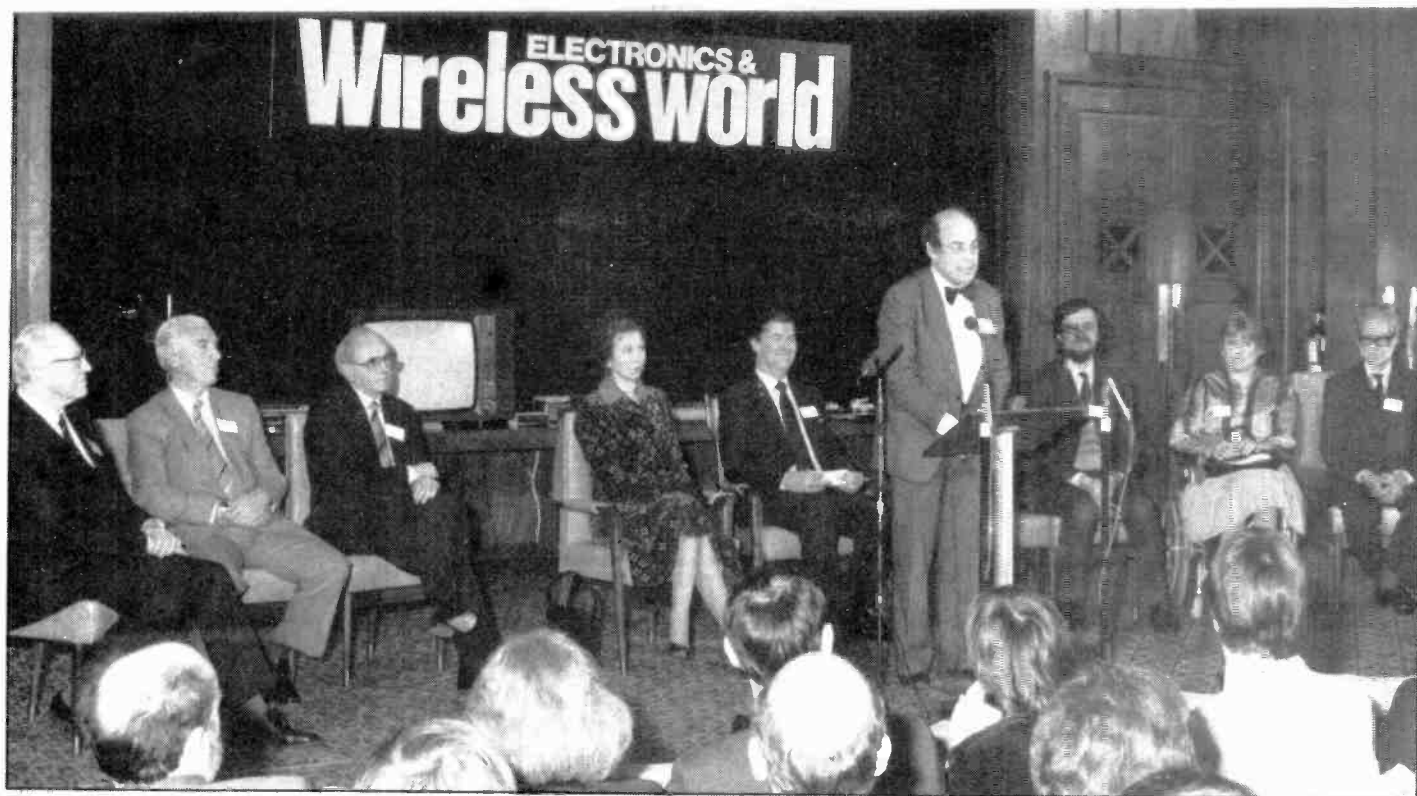

Left to right: Bill Bond (judge), David Gemmell (judge), Philip Darrington, H.R.H. Princess Anne, Sir Keith Skinner (chairman of Business Press International), Heinz Wolff (judge), Richard Lambley, Elizabeth Fanshawe (judge), Meredith Thring (judge).

Electronic devices for the disabled

First prize in *Wireless World's* recent competition was won by Tony Heyes of Nottingham University for his *Sonic Pathfinder*, a navigation aid for the blind. Dr Heyes received his award of £2,500 from Princess Anne at a presentation on January 30. Second prize, £1,500, went to Phil Pickersgill and Nic Stewart of Wokingham for a speech training device which they named *Pausaid*.

The four £1,000 prizes for runners-up went to

- David Battison and David Palmer of Cambridge, for their *Miaphone*, a speakback facility for blind, disabled typists.
- Michael Bolton and Alastair Taylor of Aberbeen, for their computer interface for the disabled.
- William McCarthy of Edinburgh, for his depth gauge for the visually handicapped.
- Ian Mitchell of Hull, for his *Talking Box*, a communication aid designed initially for speech-impaired children.

Judging and presentation of the awards took place on January 30th at the Institution of Electrical Engineers in London. Twelve entries selected for the final stage of the competition were demonstrated to the judges by their authors, who were Elizabeth Fanshawe of the Disabled Living Foundation, David Gemmell of Possum Controls Ltd, Bill Bond of the Polytechnic of the South Bank, Professor Heinz Wolff of the Brunel Institute for Bioengineering and Professor Meredith Thring, Queen Mary College, London University.

Princess Anne spent more than half an hour examining the devices and discussing them with their designers. In an address afterwards, she spoke of the ingenuity and inventiveness of those who had entered the competition. She said "Your enthusiasm and your efforts may not make you household names, but will certainly earn

you the sincere gratitude of a highly individual and progressively independent group of people". Princess Anne spoke also of those who had not reached the finals, whose entries might still warrant development and possible future production. "If they do that", she said, "they will have their own reward".

Speaking on behalf of the judges, Professor Wolff praised the designers for their cost-consciousness. They recognised that technical aids had to be paid for by someone. "A competition of this kind as a stimulus for technically knowledgeable people to exercise their compassion and think about people less fortunate than themselves is itself very valuable".

An article by Dr Heyes describing his prize-winning entry will appear in *Wireless World* shortly, and we plan to include details of other interesting entries during the next few months.



Dr Tony Heyes receives his prize from Princess Anne.



Philip Darrington (right), *Wireless World* editor, with Dr Heyes and a *Sonic Pathfinder*. Left is Richard Lambley, projects editor.

Dr Michael Bolton (right) shows Princess Anne his computer interface.



Differential temperature integrator

Battery-powered remote-reading integrating thermometer has application in energy-conservation schemes

As much as 25% of the UK's primary energy consumption is in domestic buildings, yet relatively little is known about the details of its use. Individual tastes vary wildly and variations of annual energy consumption of 3:1 or more between identical houses are quite common. Because of this, testing out some new insulation measure or heating system requires monitoring a large number of houses. This can be a very expensive business.

The traditional instrument for temperature recording has been the thermograph, a kind of clockwork chart recorder, still to be seen ticking away in the corners of art galleries and museums. More recently memory-based electronic recorders have appeared that can be read out into a computer.

For most housing work all that is re-

R. Everett

quired are weekly or monthly averages of temperature plus the opportunity to sample spot values, such as the evening living-room temperature. Most importantly, this must be done without disturbing the house occupants and without spending vast sums on cabling back to a central datalogger. The differential temperature integrator was specifically developed for the Pennyland field trial in Milton Keynes, one of many sponsored by the UK Departments of Environment and Energy in recent years, and involved monitoring 80 houses of varying insulation level and south-facing window area¹.

Why a 'differential' integrator?

The heating energy consumption of a house is roughly proportional to the average inside-outside temperature difference (ΔT), the constant of proportionality being an indication of the insulation level of the house. To evaluate the effectiveness of insulation, weekly heating energy consumption needs to be correlated with weekly ΔT . We can extend the process to include solar radiation to make an estimate of the 'passive' solar gains into a house. ('Passive' as opposed to the 'active' solar energy that you get from solar panels.)

As various zones of a house are at different temperatures, a weighted average of


the different temperatures of different rooms is required. Thus the job of the d.t.i. is simply to generate cumulative integrals of the difference in temperature between each of three sensors inside the house, two downstairs and one upstairs, and a fourth on the outside, preferably on the north side out of the sun's rays. The temperatures are sampled every 8 minutes and the cumulative integrals are clocked up on three liquid-crystal displays, in units of degree-days (i.e. 1degC for one day, commonly used in building work). For the Pennyland field trial the integrator was mounted alongside the gas and electricity meters in an external meter cupboard where it could be read by the researchers without entering the house. The d.t.i. also has a hold mode allowing any of the four temperatures to be sampled on a test point with a d.v.m.

This device is a logical solution to a monitoring problem; I was not surprised therefore to find a paper proposing such a device after completing the prototype².

Circuit design

The temperature sensors used are thin-film platinum resistance types (such as RS 158-238), effectively precalibrated to $\pm 0.3\text{degC}$. This type of sensor has a resis-

Designed for temperature monitoring in energy conservation field trials at Milton Keynes this thermometer provides weekly average temperature differences between each of three zones of a house and the outside air temperature. Put crudely, heating energy consumption to a house is proportional to the temperature difference and the constant of proportionality is a measure of the quality of house insulation. The device requires three platinum resistance thermometers installed in the house, nominally one each in living room, kitchen and a bedroom, and an outside air temperature sensor. These four sensors are wired to the integrator box located in some convenient place, such as a meter or bin cupboard on the outside of the house, where it can be read weekly along with gas and electricity meters without disturbing the house occupants.

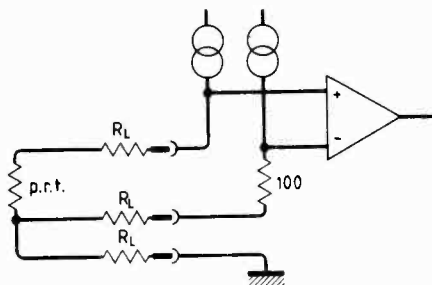

Note: Positions of heat meters may vary from house to house

Fig. 1. Three-wire bridge circuit puts equal lead resistance in each arm, with one lead in common.


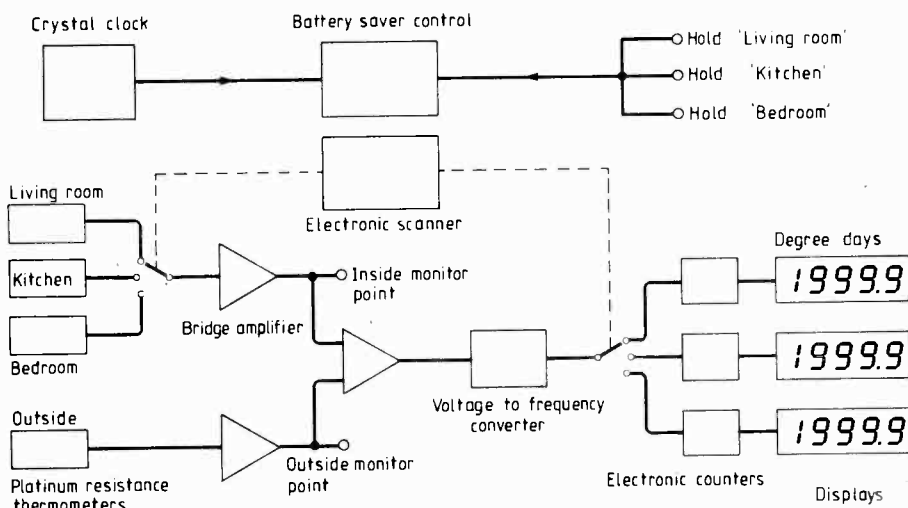


Fig. 2. Battery-saving circuitry samples temperatures every few minutes - the amplifier and v. to f. converter are multiplexed between sensors.

Fig. 3. Temperature integrator is mounted in the house external meter cupboard with other meters — the sensors are up to 10 metres away.

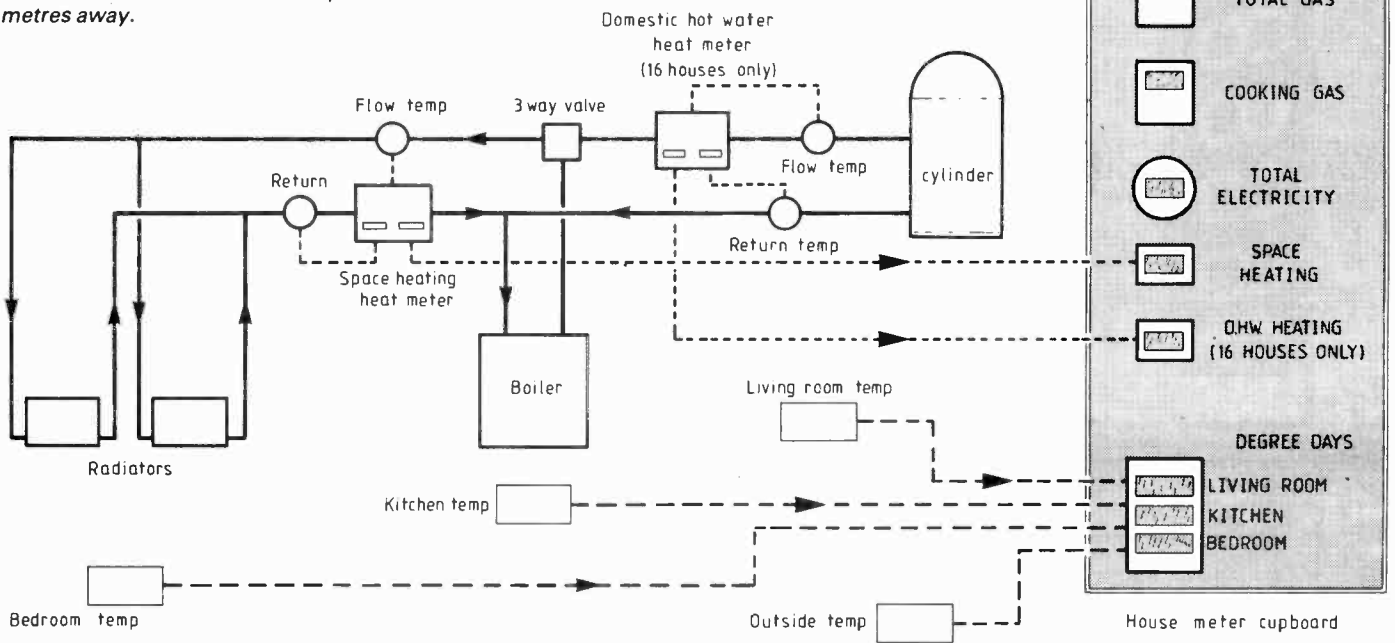

tance of 100 ohms at 0°C rising to 138.5 ohms at 100°C.

Because lead resistances are likely to be significant it is usual to use them in a bridge arrangement, as in Fig. 1. Here the p.r.t. is compared with a precision 100 ohm resistor (e.g. RS158-086) and the bridge ensures that equal lead resistances appear in each arm, with one resistance in common.

I wouldn't recommend the use of i.c.

constant-current sources in this type of bridge. Many have large temperature coefficients (read the fine print for long-term drift characteristics!) and more than one is sold as a dual-purpose constant-current source/temperature sensor! More recently, precalibrated thermistors have become available cheaply and these are now a better choice for temperature measurement than p.r.t.s because of their higher output.

The temperature integration process is

achieved by feeding the difference between the inside and outside temperatures to a voltage-to-frequency converter and then counting and displaying the resulting pulses. To minimize drift, the bridge amplifiers are ICL7600 commutating auto-zero types. To keep the component-count down the internal temperatures are multiplexed into a single bridge amplifier and v-to-f converter (see block diagram).

Much of the circuitry is devoted to battery saving. This allows four D-size and six AA-size alkaline cells to last up to six months.


The 32.768kHz crystal oscillator is counted down by 4040 counters and decoded with the 4068 and gate to wake up the sleeping system for two seconds in 512 (about eight minutes). In the off state, battery consumption is essentially that of the three liquid crystal displays (about 300µA). The circuit cycles through four phases of 500ms each, starting with a settling period with the amplifier inputs grounded. Then each of the sensors in turn is routed through the input multiplexer and the bridge amplifier to the v-to-f converter. The resulting pulse train is routed to the appropriate 4040 counter and 7224 counter/display driver.

The v-to-f converter (Teledyne 7400 or RS307-070) requires a stabilized negative voltage rail as a reference, the stability of

Designed by Bob Everett and engineered by the OU Electronics Common Facility, 100 of these temperature integrators were made and installed in houses at Milton Keynes in the summer of 1981.



Bob Everett is currently a Research Fellow in the energy research group of the Open University. He studied mechanical and electrical engineering at Cambridge University, graduating in 1970, and subsequently worked on computer phototypesetting development for the (then) International Publishing Corporation. Since 1976 he has worked on the monitoring and computer analysis of a number of solar energy projects in Milton Keynes. He is embarrassingly fond of his ZX81.

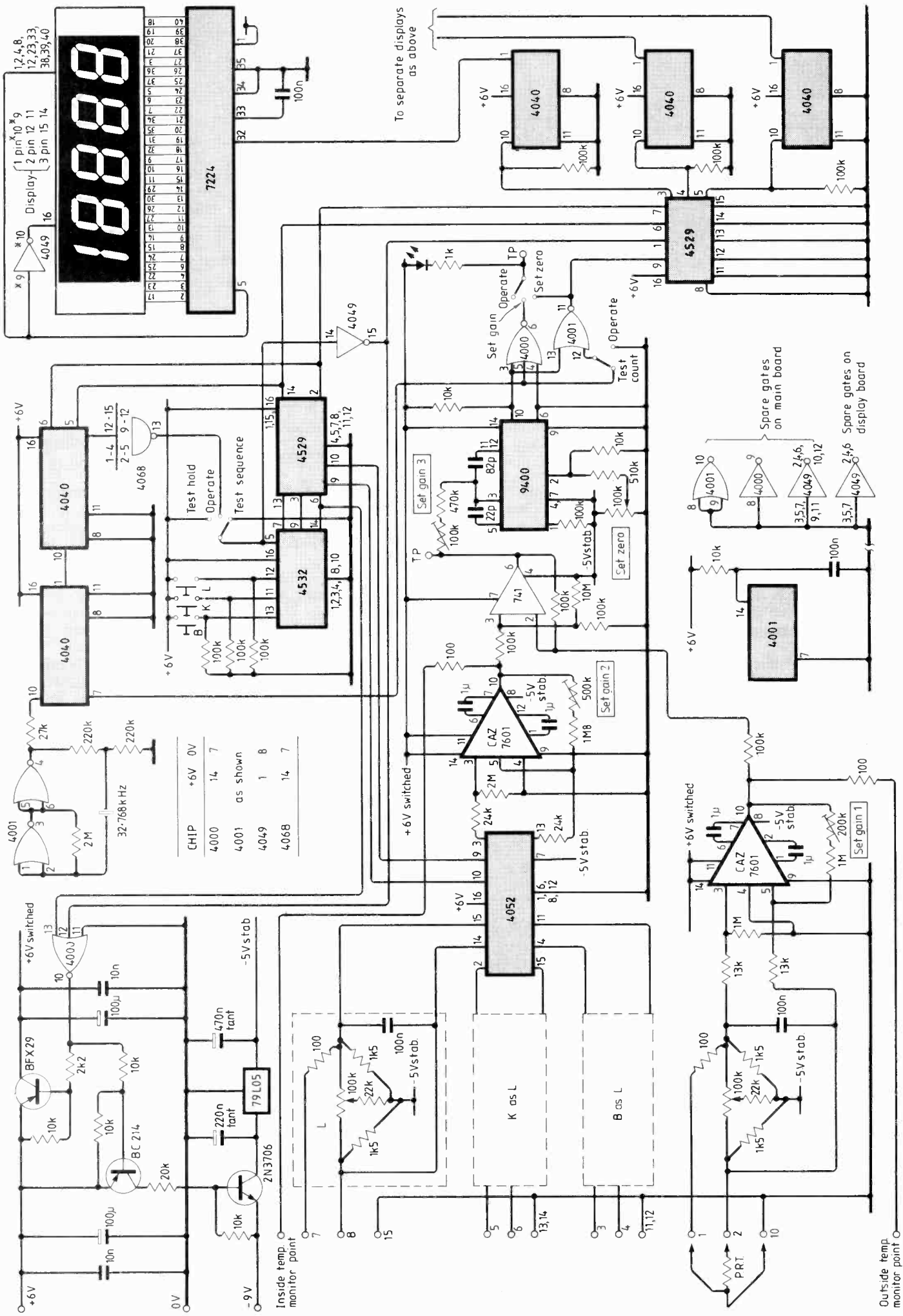

◀ **Fig. 4.** Light-emitting diode and associated switches were included for production testing and could be omitted. The l.e.d. was an idea to set the v. to f. converter gain without an oscilloscope by beating the output against the crystal clock, but the 'scope is a lot easier in practice.

the positive rail being not nearly so critical. Hence the use of a 9V battery regulated to 5V to drive v-to-f converter, bridge amplifiers and the bridge.

Pressing any one of the individual hold buttons powers the system. The 4532 priority encoder selects the appropriate two-bit address and also allows the normal integration mode priority should the counter time out. The bridge amplifiers are powered and the appropriate temperature can be sampled on the two test points with a d.v.m. (1 volt=10degC).

Setting up


The design contains a rather confusing array of switch settings for testing and setting up, most of which turned out to be unnecessary. The bridge amplifier gains

and offsets can easily be set up in the hold mode using standard resistors (100Ω=0°C and 110Ω=26.0°C). The v-to-f offset is set to give a 5Hz tickover at zero ΔT (visible on the l.e.d. in the set-zero switch position). The v-to-f gain is set by adjusting the output to 8.192kHz at a ΔT of 16.9°C. The beat between the v-to-f output and the reference signal from the clock chain should be visible on the l.e.d. with the test switches set to set-gain. Alas, in practice it is far more visible on a 'scope.

One vital ingredient missing from the design is a way of detecting leaky c-mos chips. With complex battery powered equipment, one leaky chip or a floating gate can mean the difference between microamps and milliamps of battery consumption. But which chip is it? Desoldering them at random from a double-sided printed circuit board is a recipe for disaster, and yet a few 100ohm resistors in the power rails to localize the fault could have saved many boards from the bin.

This design dates from 1980. A production run of 100 were made in 1981 and have performed reliably since then. With

the close of the Pennyland field trial they are likely to be passed on to further trials. Although the design is a little dated, it is still difficult to get the same performance at the price from a micro design (the components excluding board and box come to about £120), but it is only a matter of time.

Members of the Open University Electronics Common Facility transformed the scruffy prototype into a production device. Funding for the Pennyland project came from the Department of Energy, through their Passive Solar Energy Programme, and the Department of Environment as an extension of their 'Better Insulated House' programme. 

References

1. Energy Projects in Milton Keynes, S. Fuller, J. Daggart & R. Everett, 1982. Available from Milton Keynes Development Corporation.
2. Simple data-logging instrumentation for monitoring the thermal performance of buildings, Charles Newcomb, Proc. 5th Passive Solar Conference, University of Massachusetts, 1980.

Adaptable typewriter interface continued from page 28

Table 1. Small sample of the output of program of List 1.

Data to printer	Ascii decimal equivalent
12	82
13	77
14	64
15	75
16	94
17	94
18	80
19	83
20	87

Table 2 shows the ascii code in binary for a character (written in left hand side of column) and decimal data representation of the binary code to be sent to the printer (right hand side). For example ascii code 1100100 is found from intersection of column 100 and row 1100 giving character 'd' translated to decimal code 123 for the printer. Non-printing characters are shown by blank entries.

Bits 7654	321							
	000	001	010	011	100	101	110	111
0000	nul							bel
0001	bs 114	ht 70	uf	vt	ff	cr 48	so 71	si 98
0010		dc1 68	dc2 67	dc3 65	dc4 66			
0011				esc 96			rs 69	
0100	sp 113	! 154	" 22	# 158	£ 54	% 29	& 52	' 40
0101	(8) 56	* 30	+ 26	, 125	- 80	. 85	/ 62
0110	0 120	1 94	2 86	3 126	4 78	5 118	6 110	7 116
0111	8 104	9 72	: 23	; 87	(8	= 90) 56	? 144
1000	@ 14	A 27	B 53	C 57	D 59	E 60	F 11	G 41
1001	H 55	I 10	J 47	K 15	L 63	M 13	N 45	O 58
1010	P 18	Q 28	R 12	S 19	T 44	U 42	V 9	W 20
1011	X 17	Y 43	Z 25	(8) 56			46
1100	Y 40	a 91	b 117	c 121	d 123	e 124	f 75	g 105
1101	h 119	i 74	j 111	k 79	l 127	m 77	n 109	o 122
1110	p 82	q 92	r 76	s 83	t 108	u 106	v 73	w 84
1111	x 81	y 107	z 89	8	157	56		

Notes and limitations

Some residual problems exist such as the fact that the ascii code does not allow for characters such as half-space or ÷ which are available from the typewriter keyboard. One possible solution to this is to define characters in the code range 128 to 255 and then to use software to substitute these special codes when the alternate character set is required. A decision to include or discard such codes will have a bearing on the complexity of your final program as will, for instance, forcing your non-proportional spacing typewriter to right-margin justify text.


Note that the Praxis does not seem to read the keyboard 1/keyboard 2 status unless the character buffer is empty and so it is necessary to delay before changing the keyboard status if the printing rate is above about ten characters per second.

A more serious limitation is the amount of time that the printer can run continu-

ously until it needs a cooling off period. Typewriters are seldom driven by people who type virtually continuously and so they tend to overheat with this kind of use. For example the Praxis is not really up to printing more than 40 minutes continuously without say a 20 minute rest for the mechanism to cool down a bit. If the printer does get overheated it tends to skip characters and generally mess up the text, thus necessitating a reprint. A lot of printing can be done in 40 minutes but for really long and hard use it is probably more effective to purchase a heavy-duty daisy wheel printer in the first instance.

The problem of feeding single sheets of paper into the printer can be overcome

either by forcing a software delay (the simplest method) at the start of each new page or else detecting the form feed character, then setting a latch to hold BUSY high until manually reset.



There are of course plenty of hardware options to add on if desired. A uart can be added to accept serial input but be careful about drawing too much current from the printer power supply. A preprogrammed eprom inserted into the data lines will enable the printer to accept straight ascii character data rather than the modified set used here. By this stage you are probably considering one of those single-chip eprom-based processors to produce an interface with all the 'bells and whistles'. 

CIRCUIT IDEAS



Optical-fibre measurements

Used with an optical-fibre directional coupler, these circuits allow backscatter measurements on fibres with >10dB one-way insertion loss. Light pulses of 50ns are used in the avalanche photodiode pre-amplifier which, when carefully constructed, has a 10-40MHz bandwidth. Small-signal Schottky diode D stops $Tr_{1,2}$ saturating when strong optical reflections occur. Resistor R should be as high as possible, depending on the required bandwidth. When displaying fibre backscatter curves on an oscilloscope, the second amplifier circuit may be useful (b). Oscilloscope bandwidth should be equal to or greater than 40MHz.

In the GaAs laser-diode pulse circuit, (c) capacitor C charges through the transistors and is discharged through the Siemens fast-recovery thyristor and the RCA SG2004/5/6 laser diode. These 904nm laser devices suit the C30921 avalanche photodiode. Capacitor C, chosen to give 50% light-on time, depends on the laser diode and supply voltage and is typically around 8nF. Pulse repetition rates higher than 10kHz are possible. Using a ferrite pulse transformer to drive the thyristor provides isolation (shown separately).

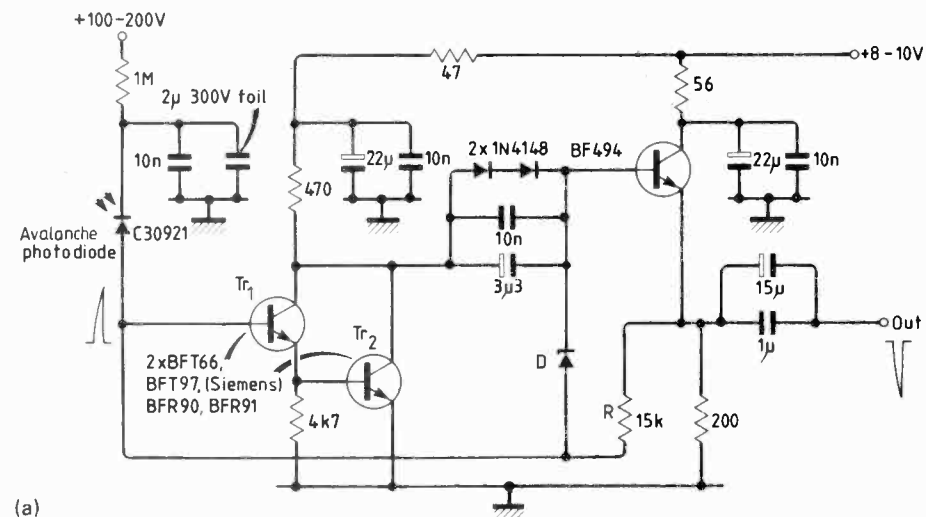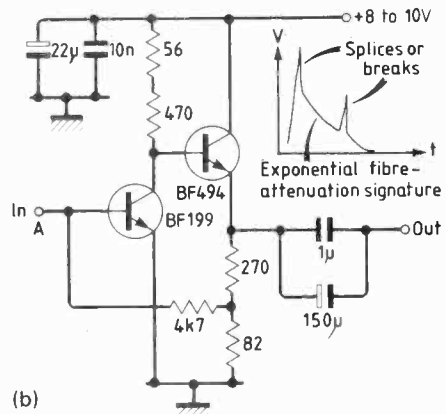

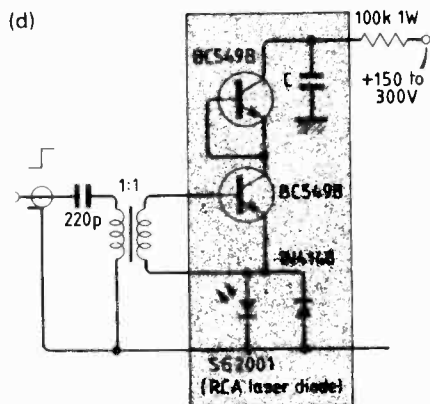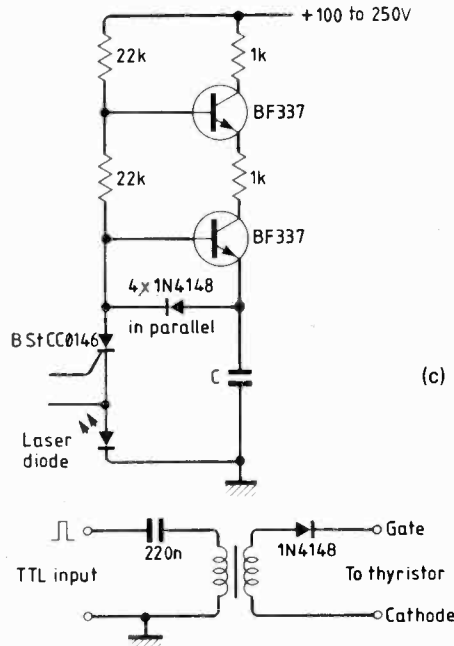
As an aid to optical-fibre bandwidth measurement, final circuit (d) can produce light pulses as short as 200ps with capacitor C at 45pF and using selected transistors in avalanche mode. Input pulse-repetition frequencies between 100Hz and 100kHz



are possible. Siemens BC549s showed avalanche effect at $V_{CEO} > 70V$ and $V_{BR(CES)} > 140V$ d.c. Each of the transistors must be above these limits and only small-signal devices may be used. Wiring within the boxed section should be as short as possible.


Chopped-light amplifier

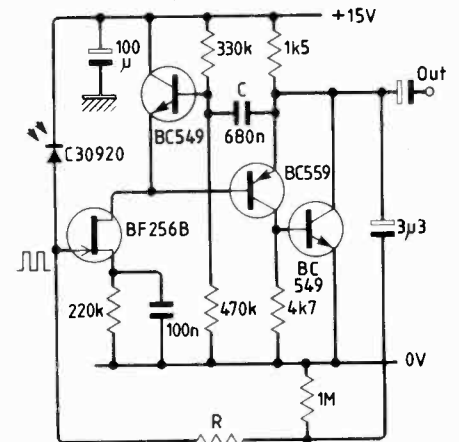Filtering the output of this amplifier to within 100Hz of the chopping frequency of say 1kHz allows light levels down to 10pW to be detected when $R = 10M\Omega$. A bipolar transistor fixes the fet drain voltage so



selection is not required; drain current may be altered by adjusting the source resistor. Voltage gain of the fet is high through inclusion of capacitor C which provides a high dynamic-load impedance. Amplifier noise is 0.04pA r.m.s./ \sqrt{Hz} and noise of the RCA C30920 p-i-n diode is 0.06pA r.m.s./ \sqrt{Hz} .

Schmitt-trigger opto-coupler

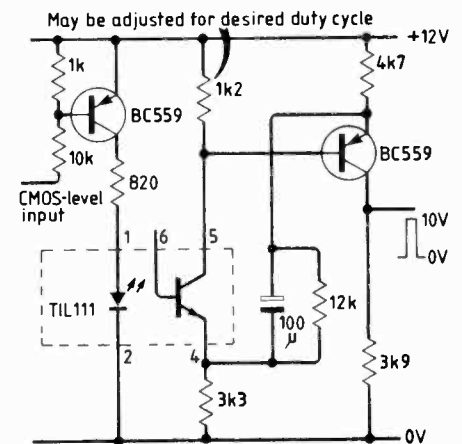


J. Vandeweghe
Ghent University
Belgium

Aligning four frequencies

Four a.c. signals may be compared on a four-channel oscilloscope, but a more graphic representation can be obtained using an oscilloscope in XY mode and adding pseudo-Z and Z modulation signals. This is particularly useful when testing phase-locked loops or tuning several signals simultaneously.

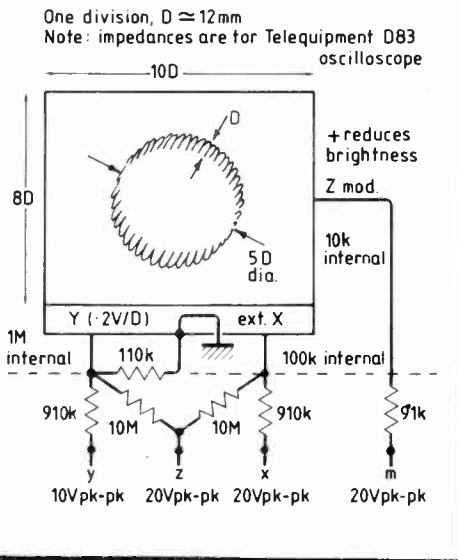This arrangement, originally devised for a Telequipment D83 oscilloscope, was used to set up two 50Hz sinewaves in quadrature (at x and y) by means of a Lissajous circle. A 2.5kHz signal introduced at z causes the circle to take on a crown shape; this signal appears stationary when its frequency is an exact multiple of the



Programmable pulses with delay

On triggering, this programmable circuit produces a pulse after a delay. Accuracy of the pulse and delay periods is determined by the accuracy of the clock so the design doesn't suffer from drift associated with monostable circuits and works reliably at high frequencies.

The first counter determines delay and the second one pulse width. Counter Q_D outputs are used as these change synchronously with the clock and don't produce glitches at the output but it means that the maximum count is half of that possible using the ripple-carry output. Eight-bit counters are shown but any number of bits may be used by cascading more or fewer 74S163 i.cs. Delay D for a load value L is given by

$$D = (2^n - 1) - L$$

where n is the number of counter bits. In this case, n is seven.

A. D. Hackett
Salisbury
Wiltshire


fundamental signal. The highest frequency, 5kHz in this instance, is applied at m to modulate brightness and results in a stationary stripe when synchronized.

With practice, z and m can be adjusted simultaneously. For lower multiples applied to z characteristic shapes are obtained, i.e., three lobes at 2f and four lobes at 3f. If frequencies at x and y are not the same, as usual, Lissajous figures are stationary when the frequencies are exact multiples of each other. For digital signals, sensitivity may be increased by reducing series-resistor values.

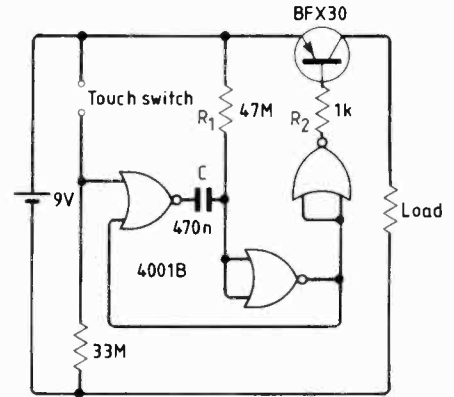C. J. D. Catto
Cambridge


Simplified battery timeout

This contribution is a cheap and simple means of conserving battery power using only six components. After the touch switch is activated, power is applied to the




load for a period equal to $0.69CR_1$. Resistor R_2 determines current limiting and may be changed. Quiescent leakage current is less than 100nA and with values shown, the power-on period is 13s and current limiting is at about 450mA. At 200mA, voltage drop is only 200mV.

S. Whitt
Ipswich
Suffolk

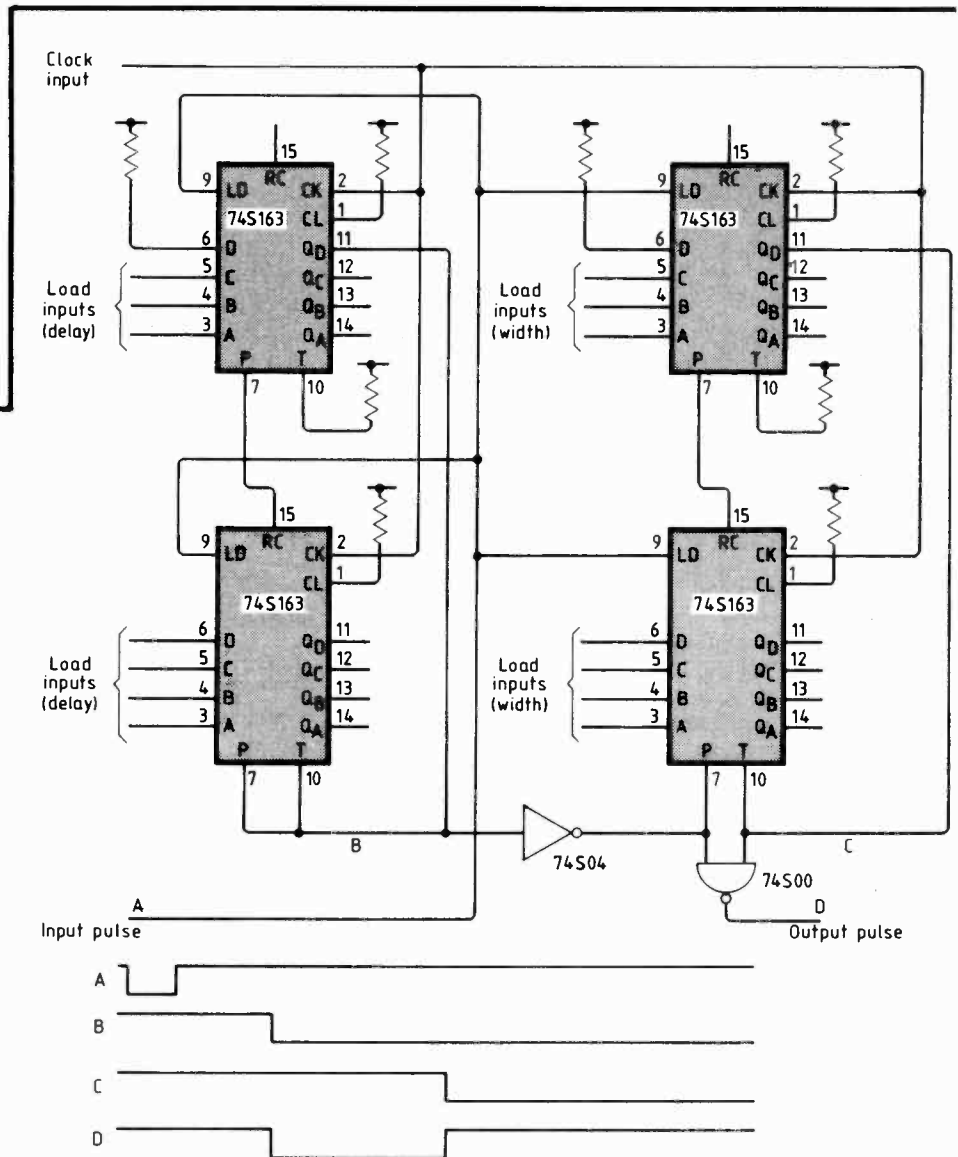

CIRCUIT IDEAS

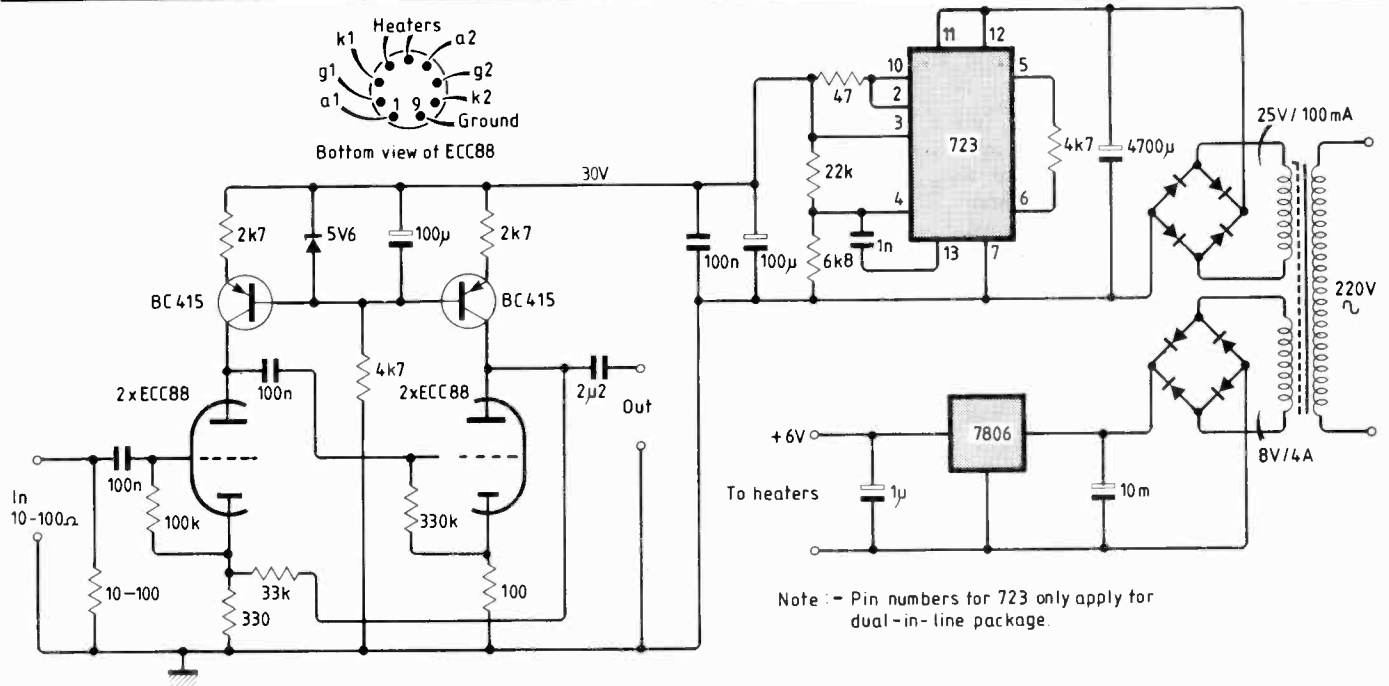

Moving-coil amplifier

I find that this moving-coil cartridge amplifier using valves gives a more natural sound than many circuits using transistors and it is easy to construct. Anode voltage rating of the ECC88 dual triode is only 90V but it may be taken as low as 10V so

power-supply design is simplified. The two sections of each ECC88 are connected in series and low-noise transistors connected as constant-current sources form anode loads for the two stages. Gain of each stage is about 30.

A 723 regulator is used for the main supply because signal-to-noise ratio of the

amplifier depends on noise, output impedance and ripple rejection of the supply. Popular 78-series regulators are not good enough. Valve heater supply must be regulated for the same reasons but in this case a 7806 suffices. Overall closed-loop gain of 100 is determined by the 33kΩ resistor, which may be lowered to reduce gain. Open-loop gain is 600. Loading required for different makes of cartridge varies but is usually between 10 and 100Ω. Capacitors are critical and high-quality polycarbonate or polypropylene types should be used throughout, except for power-supply smoothing.


Per Hojlev
Copenhagen
Denmark

15-bit d-to-a using ZN425 converters

Two cheap eight-bit d-to-a converters are combined to form a 15-bit converter in this circuit. Output of the left-hand converter is calibrated for all input values (0 to 255) and a correction value is programmed into the 28L22 prom with 00 corresponding to -511/512 l.s.b. and FF₁₆ corresponding to +511/512 l.s.b. This correction is added to the seven least-significant bits of the input data to provide an eight-bit input to the second converter. Reference voltage for both converters is derived from one i.c. to reduce errors due to ageing and temperature fluctuations.

Resistors R_{3,5} are adjusted to give correct scaling factors for the two d-to-a converter outputs and R₇ corrects for output offset. Component values are not shown since these will depend on the application and output voltage range required. Temperature compensation can be applied through R₉ and by using an external reference voltage.

S. W. Beet
Merseyside

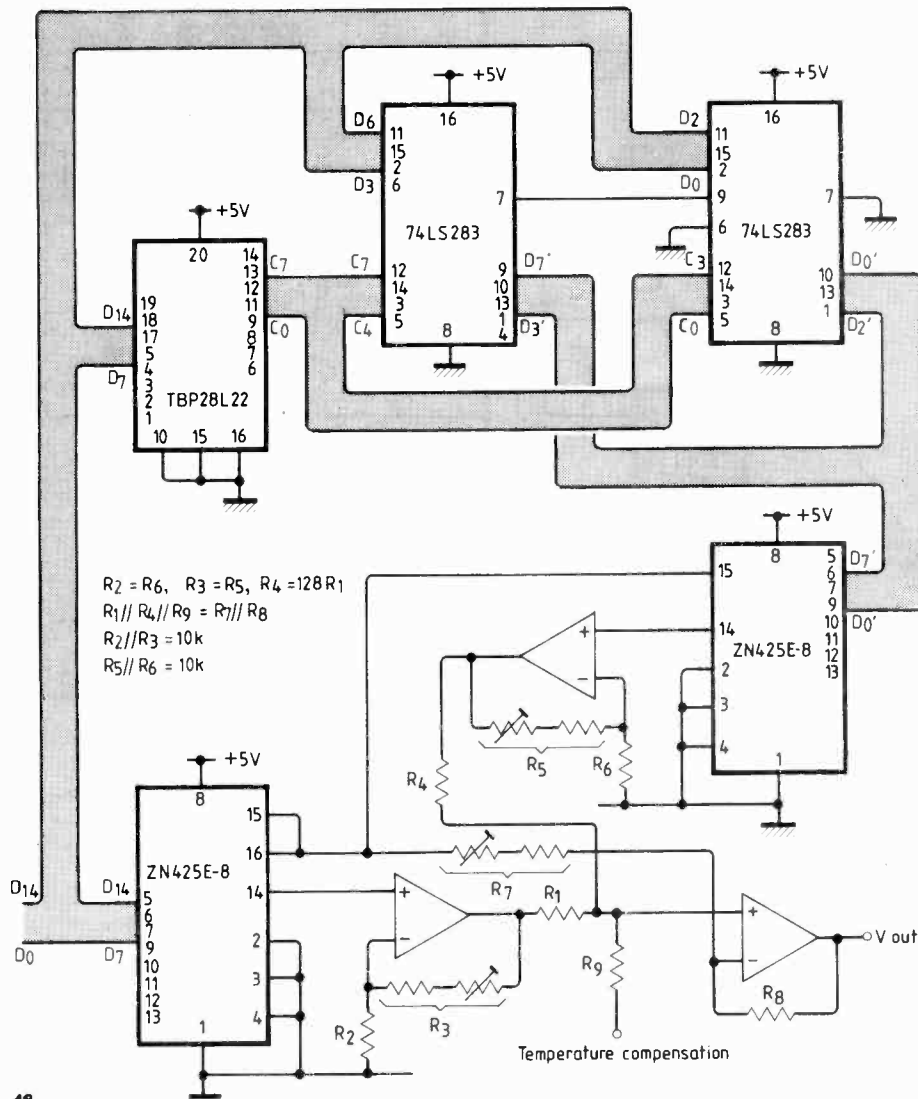

The parallel-fed voltage multiplier

Although any desired voltage may be obtained by stringing together a sufficient number of cells, a voltage converter has many advantages. Battery testing and replacement are simpler, and there is the option of using a single rechargeable device to power the whole of the circuitry.

Our particular need arose during the design of a portable muscle stimulator for biomedical use. The initial specification called for a unit to give output pulses at 10Hz, of 200 μ s duration and amplitude 15mA maximum into a load of approximately 8k Ω , representing the resistance of electrodes placed on skin over the muscle. The stimulator was to be carried about in a pocket or on a belt, and would be used for 6 to 12 hours per day. The power source was to be a single PP3 9V battery, and we hoped to keep the current drain below 1mA to ensure long battery life.

The specification evidently requires a voltage supply of at least 120V. As the output energy per pulse is 0.36mJ, the average power drawn from the supply is 3.6mW. If voltage conversion could be achieved with 100% efficiency, the current drain from the battery would be only 0.4mA. Thus the target value of 1mA seemed approachable. However at power levels below 10mW a conversion efficiency of even 50% is hard to achieve, as we found by examining a commercial stimulator with broadly similar specifications. It employed the conventional oscillator and step-up transformer, rectifier approach to voltage conversion, and its current drain was several milliamps. This poor efficiency, less than 20%, encouraged us to consider an alternative method.

Fig. 1 shows the well-known Cockroft-Walton cascade voltage multiplier in the form commonly used when an alternating voltage is available to drive it. A minor modification at (b) enables it to be driven by antiphase square waves which do not have to swing below 0V. These circuits are series-fed: the a.c. or square-wave driving voltage is applied to the end of a chain of capacitors in series. Design and analysis are notoriously difficult, because the current and voltage waveforms for each stage are different. It is known that with optimal allocation of resources the capacitor values should not all be equal, but should increase from C at the output end to NC at the driven end. Another disadvantage is that the additional output voltage per stage is not constant, but diminishes by one diode drop V_f for each stage in the circuit.

R. D. Purves and C. Prescott

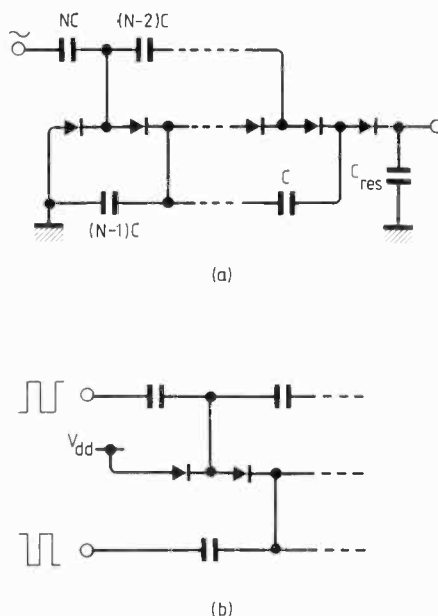


Fig. 1. In the Cockroft-Walton series-fed voltage multiplier the output reservoir capacitor C_{res} is chosen to have a reactance, that is much less than the load impedance at the working frequency. (a) is the single-ended version, while (b) is a modification for push-pull input where antiphase square waves do not have to swing below 0V.

Thus in Fig. 1 (b) with a driving swing from 0 to V_{dd} of 9V and V_f taken as 0.6V, one stage provides $9+8.4=17.4V$, two stages provide $9+8.4+7.8=25.2V$, and so on up to 14 stages which provide 72V. Beyond this limit extra stages contribute nothing.

While pondering these deficiencies we discovered that some remarkable improvements result if the configuration is changed to the parallel-driven form of Fig. 2. The N capacitors now all take the same

value, which simplifies construction. The open-circuit output voltage per stage has the constant value $V_{dd}-V_f$ and so the total output voltage $(N+1)(V_{dd}-V_f)$ can be increased without limit. Finally, the analysis is facilitated by the fact that apart from a step-wise increase in d.c. level, the current and voltage waveforms for each stage are identical (this is strictly true only if N is even, so that points X and Y see the same total capacitance).

The most important design parameter of a power supply, after its open-circuit output voltage, is the equivalent output resistance. The parallel-fed multiplier's output resistance can be derived directly as the ratio of open-circuit output voltage to short-circuit output current. For calculation only, it is convenient to return point Z of Fig. 2 to earth instead of to V_{dd} and to treat the diodes as having zero forward voltage drop. With these assumptions the output voltage becomes NV_{dd} . A further assumption, which will later be relaxed, is that square wave sources X and Y have negligible internal resistance and thus provide a full swing from 0 to V_{dd} regardless of the load. Now if the output terminal is earthed the diodes and capacitors act in 'bucket brigade' fashion to transfer a charge CV_{dd} from one stage to the next in each cycle. The average short-circuit current is therefore CV_{dd}/T where T is the square-wave period; it follows that the multiplier output resistance is NT/C .

A more general expression for output resistance, derived in the appendix, is

$$(NT/C) \coth(T/2NRC)$$

in which the hyperbolic term corrects for the finite resistance R of the square-wave

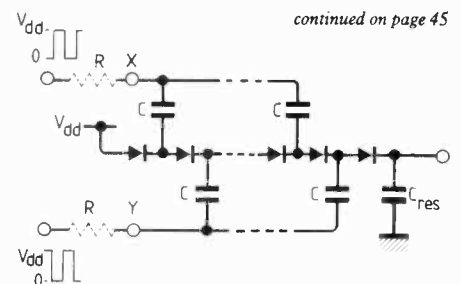


Fig. 2. Parallel-fed voltage multiplier. Resistors R represent the equivalent resistance of the square wave sources.

* Battery-powered instruments, by Ian Hickman, *Wireless World*, vol. 87, 1981, pp.57-61.

Dr Purves is with the department of pharmacology, University of Otago, New Zealand, and Mr Prescott is at the department of anatomy & embryology, University College, London.

Frequency response analyser


Using an oscilloscope to display response, this educational aid to understanding frequency response of amplifiers and tuned circuits covers the band 40Hz to 400kHz.

The heart of the analyser is a voltage-controlled oscillator, Fig. 1, whose ramp voltage varies the frequency. The v.c.o. used, the Intersil 8038, has a linear relationship between control voltage and frequency with the required range of 1:10,000 covered in four sweeps, each sweep causing a decade change in frequency. A given frequency range depends on external resistances and a capacitor. In our scheme, four different timing capacitors are used, one for each sweep range, switched in a repetitive sequence. The switching circuit shown in Fig. 1 is also used for providing retrace pulses for the bootstrap ramp generator and external trigger input for stabilized oscilloscope display. For a large frequency sweep, the v.c.o. requires a control voltage decreasing from V_{max} to V_{min} of V_{cc} to $2V_{cc}/3 + 2$. The level shifter with inversion after the ramp generator shown in Fig. 1 solves this problem.

The v.c.o. output is attenuated and fed to the input of the device under test (d.u.t.), say an RC-coupled amplifier. The frequency-dependent output of the device under test is passed to the oscilloscope Y-input.

K. Srivatsa, with a B.E. and M.Tech. in electronics, lectured at the University Visvesvaraya College of Engineering, Bangalore, before becoming senior engineer (software) at Processor Systems Pty Ltd, Bangalore. His co-authors graduated from UVCE in 1982 with B. E. (Electronics) and have taken up jobs in power electronics (Sridhara Murthy) and digital microwave communication (R. Partha).

Fig. 1. 8038 v.c.o. covers four frequency ranges, and uses a switching circuit that also provides retrace pulses for the ramp generator and external trigger input. Numbered nodes have waveforms shown in Fig. 2.

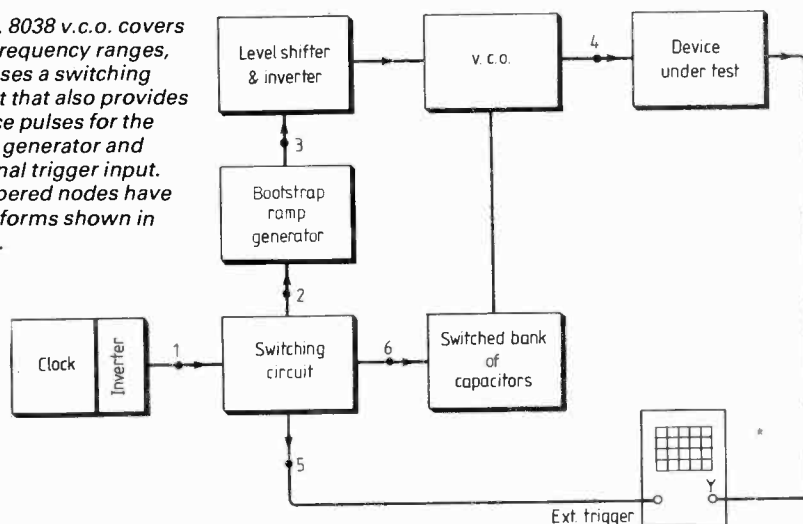

by K. Srivatsa, R. Partha and S. L. Sridharmurthy

Figure (2a) shows the clock input to the switching circuit, with a duty cycle of about 10%. Waveform (b) is derived from (a) with a period equal to four times the clock period. These pulses are passed to the bootstrap ramp generator circuit causing retrace.

The ramp at (c) has a frequency of

Fig. 2. Waveforms (a) to (f) are found at the nodes 1 to 6 in Fig. 1.

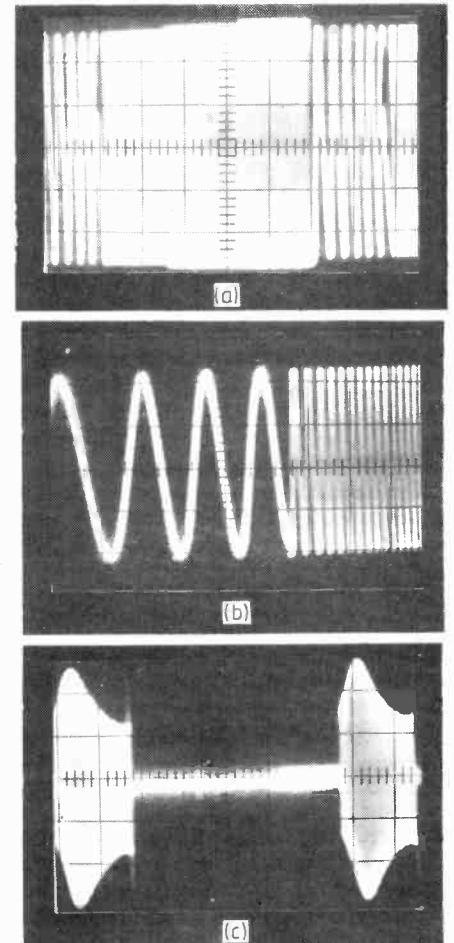
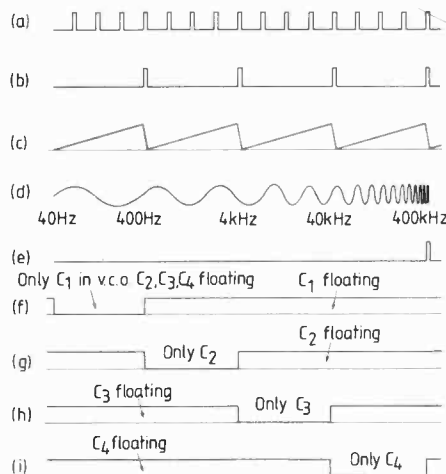


Fig. 3. Full range of analyser is shown at (a), with an expansion at (b). Lower trace shows typical output from a tuned amplifier.

400Hz. This waveform is inverted and level shifted before the v.c.o., whose output is shown in (d). Waveform at (e) has a period of four times the ramp period used for external sweep triggering to give a flicker-free display. Waveforms (f) to (i) switch the required capacitor into the v.c.o.

The performance of the analyser is demonstrated in Fig. 3. Photograph (a) shows the full range of v.c.o. and (b) is an expanded partial range. With this as the input to a tuned amplifier, the resulting output was as shown in (c). The detailed circuit is shown in Fig. 4. Design procedure is easily obtained from the data sheets¹.

Improvements

For higher resolution, as in a tuned amplifier which requires a part of the frequency

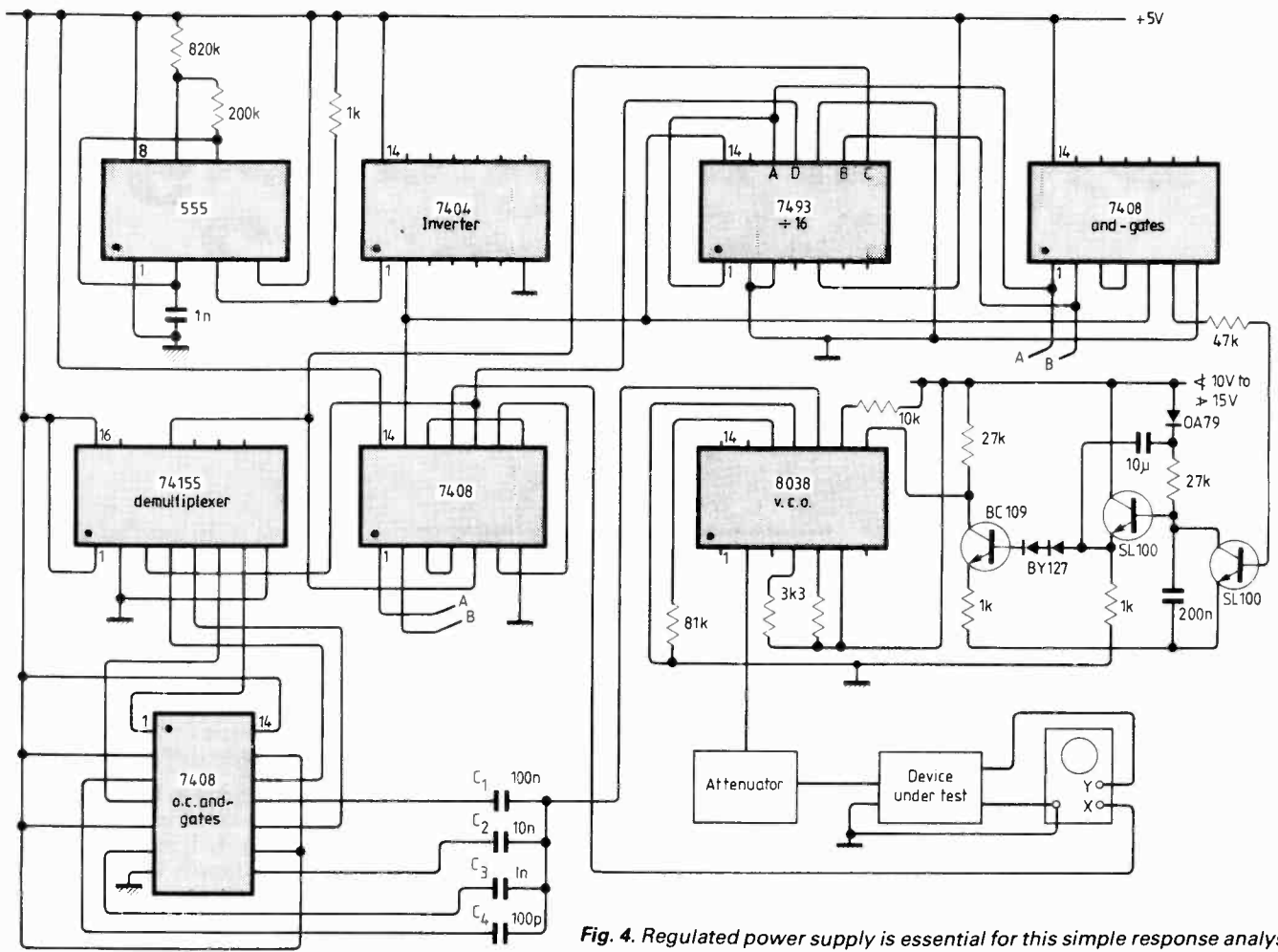


Fig. 4. Regulated power supply is essential for this simple response analyser.

range, it must be possible to divide the entire sweep range into programmable sub ranges, and the above multisweep technique repeated within each sub range.

In the analyser, the sinewave output of the d.u.t. is fed directly to the Y input. For a proper plot a direct voltage must be

given to the Y input. It will be necessary to use a wideband average detector with a switched filter for a d.c. output. Switching of filter capacitors is done using the waveforms for switching the v.c.o. capacitors. Other techniques for improving the display can be found in reference 2.

References

- 1 Intersil application note ICL 8038.
- 2 Logarithmic audio sweep generator, by A. C. Ainslie. *Wireless World* Sept. 1979.

Parallel-fed voltage multiplier continued from page 43

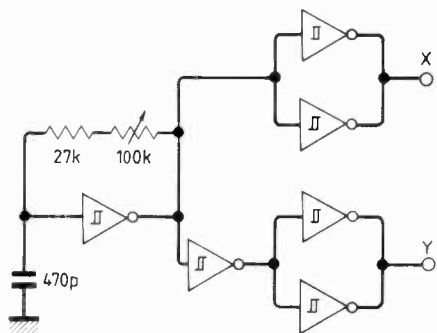


Fig. 3. A simple low power square wave source, using a CMOS hex Schmitt inverter (40106B or 74C14).

sources. For fixed R the output resistance falls with decreasing T or increasing C until $T \ll NCR$, when a limiting minimum value $2N^2R$ is reached. The actual value of capacitance used is largely immaterial, as a compensatory change in T can always be made.

In low power operation c-mos gates have sufficiently low output resistance (a few hundred ohms) to act as drivers, espe-

cially if two or more gates are paralleled, Fig. 3. More effective buffering is needed at power levels greater than about 10mW. A 15-stage multiplier driven by this circuit with $T=50\mu s$ and $C=10nF$ provided an open-circuit voltage of 137V with a battery drain of 0.27mA. The measured output resistance was 130k Ω . With 30 μA drawn from the output, total battery drain was 0.72mA. Overall conversion efficiency (load power/battery power) is 60%, a very satisfactory result in view of the low power level. If miniature polyester layer capacitors are used in the multiplier chain the entire circuit occupies little more volume than the 9V PP3 battery supplying it.

Appendix

When the resistance R of the square-wave sources is not negligible, the waveform at X or Y with the multiplier output short-circuited takes the shape indicated in Fig. 4, in which the amplitude of the swing $V_2 - V_1$ is less than its maximum value V_{dd} , owing to incomplete charging and discharging of the capacitors in

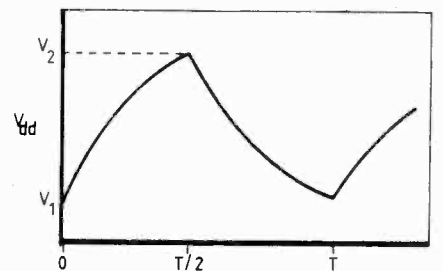


Fig. 4. The waveform seen at point X or Y of Fig 2 when R is not negligible.

each half cycle. The charge transferred from stage to stage in one cycle is $C(V_2 - V_1)$ and the average short-circuit current is therefore $C(V_2 - V_1)/T$. By inspection of Fig. 4:

$$V_1 = V_2 e^{-1/NRC}$$

$$V_2 = V_{dd} - V_1$$

$$\text{Hence } V_2 - V_1 = V_{dd}(1 - e^{-T/NRC}) / (1 + e^{-T/NRC}) = V_{dd} \tanh(T/2NRC)$$

With ideal diodes the open-circuit output voltage is NV_{dd} and so the output resistance is given by

$$NV_{dd} T / C(V_2 - V_1) = (NT/C) \coth(T/2NRC).$$

Digital filter design procedure – 3

Despite its limitations a high-pass digital filter is easily designed by 'inverting' its equivalent low-pass version (July issue). Except for sign changes, pole and zero parameters are the same.

Previous articles with this title were in the May and July 1983 issues, the first outlining how to design the digital equivalent of an analogue filter where the transfer function can be simply formulated. As an example, the article derived in detail the digital equivalent of a parallel tuned circuit, and one case had pole positions chosen with a simple microprocessor in mind. The second article covered the case where the z-plane transfer function had to be derived from an analogue filter using a bilinear transformation, and a fourth-order low-pass Butterworth filter was used as an example.

One can argue that even in the analogue world a high-pass filter cannot really exist as it is not possible for a circuit to pass signals of an infinite frequency. The Butterworth low-pass filter has a flat response from zero up to its cut-off, but the flat response of the equivalent high-pass filter cannot possibly extend from

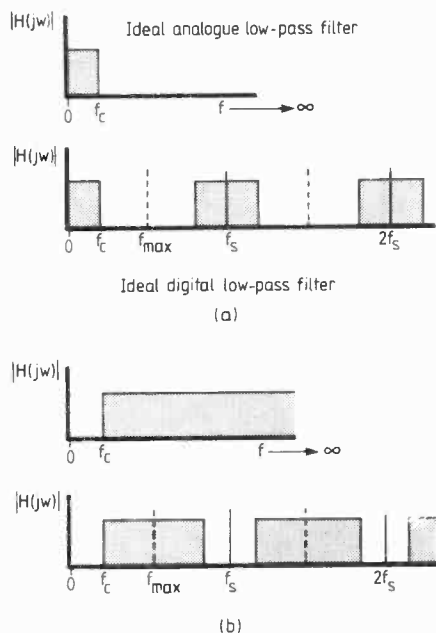


Fig. 1. Spectra of ideal analogue and digital low-pass filters compare as at top diagram (a), while ideal analogue and digital high-pass filters compare at bottom (b). Frequency f_{max} is the digital equivalent to an infinite analogue frequency.

by J. T. R.
Sylvester-Bradley M.A.

cut-off to infinity. However, as explained in the previous article, with the digital version of the Butterworth low-pass filter, the digital equivalent to an infinite frequency is the maximum frequency that the digital filter can handle, that is half the sampling frequency.

The same applies to the high-pass digital filter, and within this limitation it can have a flat response from its cut-off frequency up to the digital equivalent of an infinite frequency (f_{max}), see Fig. 1, where the spectra (or more precisely, the Fourier transforms of the impulse responses) of both low-pass and high-pass ideal analogue filters are compared with their digital equivalents. In the last mentioned the spectra are repeated at multiples (harmonics) of the sampling frequency.

Once the limitations of the high-pass filter are recognized, a filter which is the precise equivalent to its low-pass version is easily designed by inverting the position of the low-pass poles and zeros on the Z plane.

Figure 2 shows the spectrum and Z-plane diagram of the high-pass filter designed in this way to be an exact

equivalent of the low-pass filter designed in the previous article (Fig. 10 of that article).

Pole and zero positions

The pole positions for the low-pass filter were

$$\begin{aligned} \text{pole 1 } r_1/\omega_1 T &= 0.758 \angle 137.2^\circ \\ \text{pole 2 } r_2/\omega_2 T &= 0.458 \angle 159.1^\circ, \end{aligned}$$

with poles 3 & 4 as their conjugates. The four zeros were all located at $1.0 \angle 180^\circ$.

The pole and zero positions for the high-pass filter are found by adding 180° to the above positions, giving

$$\begin{aligned} \text{pole 1 } r_1/\omega_1 T &= 0.758 \angle 42.8^\circ \\ \text{pole 2 } r_2/\omega_2 T &= 0.458 \angle 20.9^\circ, \end{aligned}$$


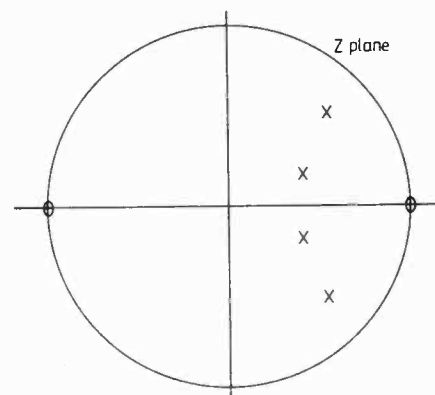


Fig. 2. Spectrum and Z-plane diagram and $|H(j\omega)|$ of digital equivalent of high-pass Butterworth filter.

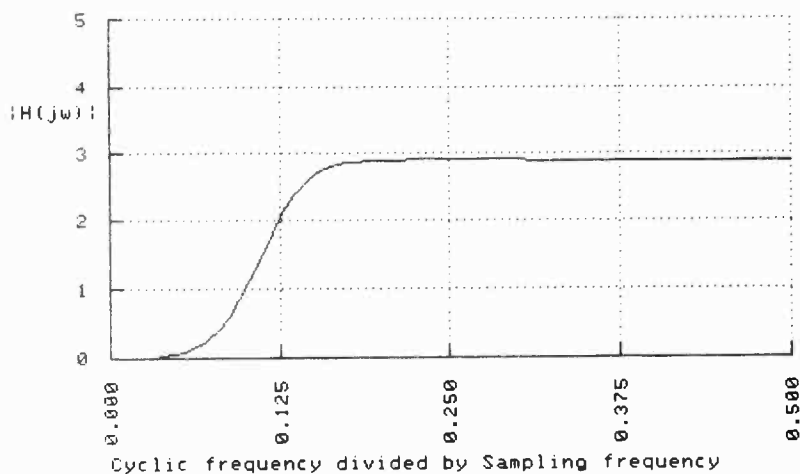

with poles 3 & 4 as their conjugates, and with the four zeros located at $1.0 \angle 0^\circ$.

The spectrum of Fig. 2 shows a flat response from just above the cut-off frequency (f_c) up to f_{max} and

$$f_c = 1/8f_s = 1/4f_{max}$$

Transfer function

For the high-pass filter $H(z) = \frac{(z-1)^4}{(z-r_1e^{j\omega_1 T})(z-r_1e^{-j\omega_1 T})(z-r_2e^{j\omega_2 T})(z-r_2e^{-j\omega_2 T})}$

$$(z-r_1e^{j\omega_1 T})(z-r_1e^{-j\omega_1 T})(z-r_2e^{j\omega_2 T})(z-r_2e^{-j\omega_2 T}) \quad (1)$$

multiply the denominator to evaluate the pole parameters:

$$(z^2 - 2zr_1\cos\omega_1 T + r_1^2)(z^2 - 2zr_2\cos\omega_2 T + r_2^2) = z^4 - 2z^3r_1\cos\omega_1 T + z^2r_1^2 - 2z^3r_2\cos\omega_2 T + 4z^2r_1r_2\cos\omega_1 T\cos\omega_2 T - 2zr_1r_2\cos\omega_2 T + z^2r_2^2 - 2zr_1r_2^2\cos\omega_1 T + r_1^2r_2^2$$

Collect like terms:

z^4	z^3	z^2	z^1	z^0
1	$-2r_1\cos\omega_1 T$ $-2r_2\cos\omega_2 T$	r_1^2 $4r_1r_2\cos\omega_1 T\cos\omega_2 T$ r_2^2	$-2r_1r_2\cos\omega_2 T$ $-2r_1r_2^2\cos\omega_1 T$	$r_1^2r_2^2$

From the pole positions,

$$r_1 = 0.758$$

$$\omega_1 T = 42.8^\circ \quad \cos\omega_1 T = 0.7337$$

$$r_2 = 0.458$$

$$\omega_2 T = 20.9^\circ \quad \cos\omega_2 T = 0.9342$$

Therefore the pole parameters are

z^4	z^3	z^2	z	z^0
a_0	a_1	a_2	a_3	a_4
1	-1.1123	0.5746		
	-0.8557	0.9518	-0.4917	
		0.2098	-0.2333	0.1205
$\Sigma 1$	-1.968	1.7362	-0.725	0.1205

The pole parameters, a_n ($n=0$ to 4) for the high-pass filter above are the same, except for sign changes, as for the low-pass filter designed in the previous article. Some paperwork would therefore be avoidable if the high-pass filter is designed as the inverse of low-pass filter already designed.

The transfer function can now be written to include the pole parameters, and assuming unity gain, $H(z) =$

$$\frac{(z-1)^4}{z^4 - 1.968z^3 + 1.7362z^2 - 0.725z + 0.1205} = \frac{Y(z)}{X(z)} \quad (2)$$

In the numerator the zero parameters b_0 to b_4 can be found by expanding $(z-1)^4$ (or from Pascal's triangle):

$$(z-1)^4 = z^4 - 4z^3 + 6z^2 - 4z + 1$$

Values for b_n are the same as for the low-pass filter, except for sign changes in b_1

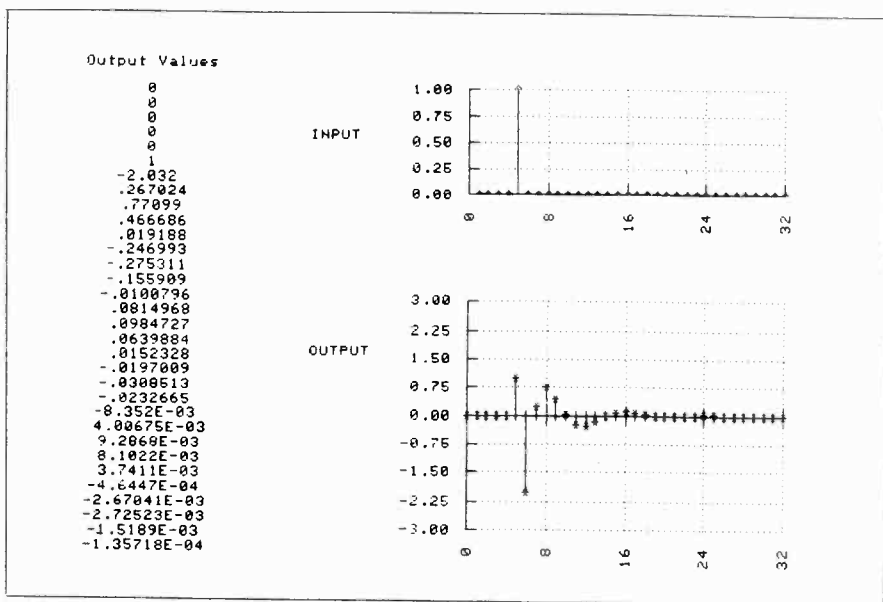


Fig. 4. Impulse response of high-pass digital filter showing "ringing" at $1/8f_s$ (top).

Fig. 5. Output of high-pass digital filter with a long (16 samples) input pulse (below).


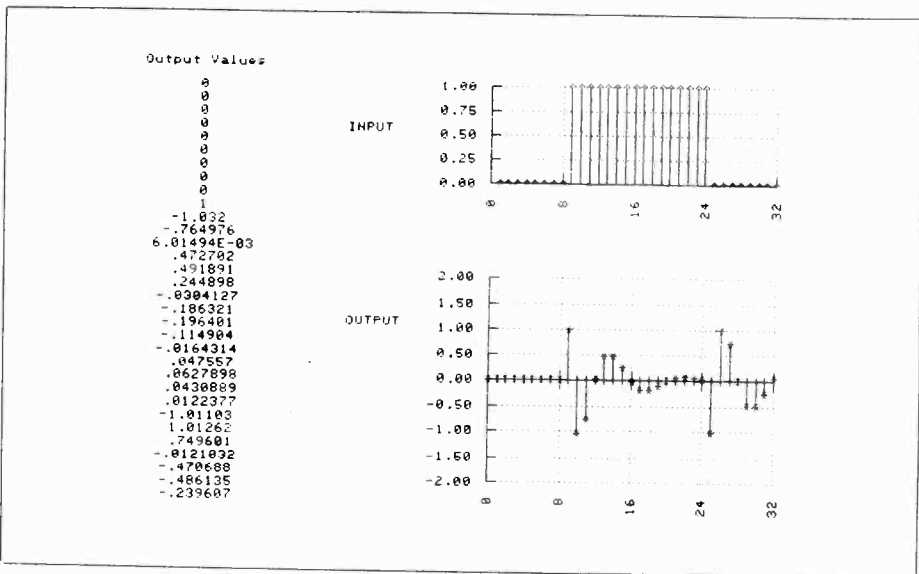


Fig. 3. Realization diagram for the 4th-order Butterworth high-pass digital filter (bottom).

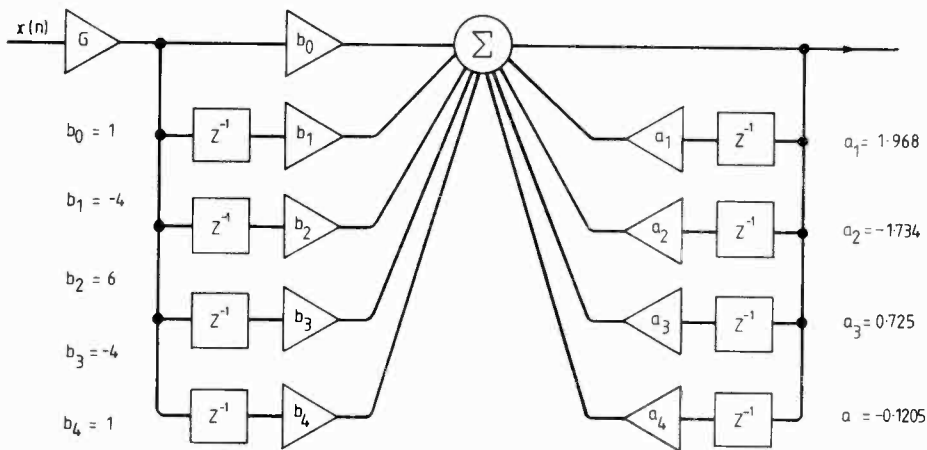

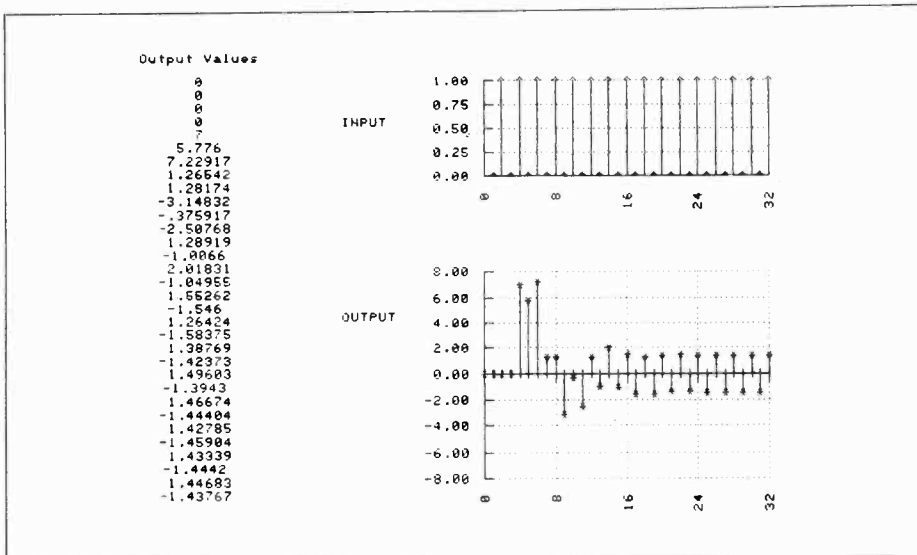


Fig. 6. After the switching transient, pulses are transmitted but with no d.c. component. Input is at f_{max} .


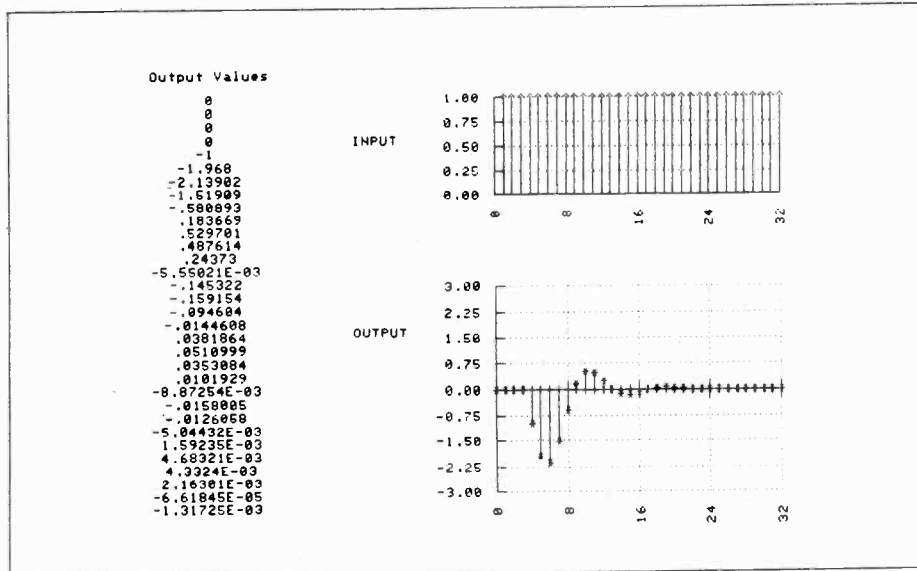


Fig. 7. In spite of being a "high-pass" filter, it cannot pass frequencies above f_{max} . Here the input is zero (after switching transient) with an input at the sampling frequency.

Fig. 8. Pulse train within the passband of the filter passed without distortion but with no d.c. component.

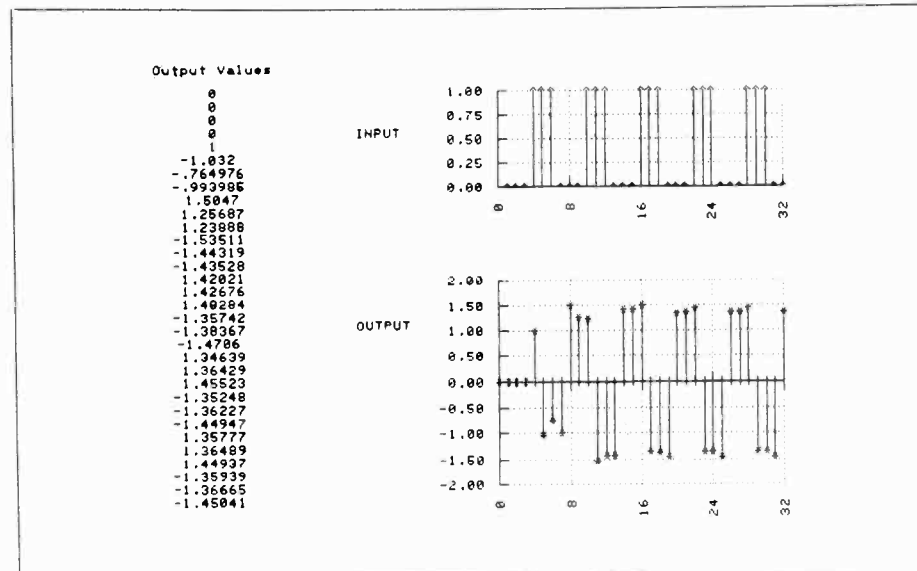

and b_3 . Cross multiplying in the equation for $H(z)$ and dividing by z^4 gives the expression for $Y(z)$:

$$Y(z) = 1.968Y(z)z^{-1} - 1.734Y(z)z^{-2} + 0.725Y(z)z^{-3} + 0.1205Y(z)z^{-4} + X(z) - 4X(z)z^{-1} + 6X(z)z^{-2} - 4X(z)z^{-3} + z^{-4}$$

The recurrence formula is therefore

$$y(n) = 1.968y(n-1) - 1.734y(n-2) + 0.725y(n-3) - 0.1205y(n-4) + x(n) - 4x(n-1) + 6x(n-2) - 4x(n-3) + x(n-4)$$

which can be written directly into a computer program to realize the filter. The realization diagram and impulse response are shown in Figs 3 and 4.

The output with a long rectangular input pulse, as in Fig. 5, clearly shows the differentiating effect of the filter, together with some ringing at the cut-off frequency.

With an input at f_{max} , (in Fig. 6 the on/off pulses are at half the sampling frequency) the output soon settles down to passing the pulses, but with their d.c. component removed. The output settles down after the ringing effect of the switching transient is over.

The filter is unable to pass a frequency equal to f_s , Fig. 7.

With a series of rectangular pulses three samples long their frequencies are well within the pass-band of the filter, and at Fig. 8 the pulse train is passed without much distortion (after the switching transient) but with the d.c. component removed. WWW

In the July 1983 article, a slip occurred on page 43, in which $X(z)$ was inadvertently repeated in the penultimate line.

If you read that article you will no doubt have spotted that the last two lines of text in column one on page 44 should have followed the recurrence formula. — dep. ed.

Who was Fessenden?

When J. D. Parker received the Fessenden Award from the National Marine Electronic Association, he had to confess that he did not know of Fessenden. So the NMEA provided him with an article from the January 1930 issue of *Radio-Craft*. Reginald A. Fessenden, it turned out, worked with Edison as an electrical engineer and as chief chemist. He later became professor of electrical engineering at Western University, Pittsburg and as early as 1895 began experimental work with radio waves. Through his knowledge of sound waves he conceived the idea of modulating a continuously oscillating radio wave and his was the first voice ever to be heard on radio. He invented the rectifying electrolytic detector, the successor to the coherer, and his other inventions included the r.f. alternator and the rotary spark-gap. He suggested the principle of heterodyning but was unable to go further until the development of suitable oscillator valves. He also spent a considerable time working on navigation and signalling at sea.

DSP, the next big step

Digital signal processing does the same things that are familiar to computer users. It executes algorithms. However in most computer applications relatively small batches of data are processed and they often do not require immediate processing. Many are familiar with the 'printout will be available next Tuesday' system. D.s.p. offers the ability to process great volumes of data with no observable delay, in 'real time'.

The technique is not particularly new. It has been used in specialized military and aerospace programmes where ultra-fast real-time computation is said to be needed, and used very expensive array processors. What is new is the production of integrated circuits that make it feasible to perform tasks previously too expensive for general use or only possible on analogue equipment.

An example of the use of d.s.p. is spectrum analysis of the vibrations in an engine on test. A d.s.p. spectrum analyser receives signals from transducers attached to the engine. It converts the analogue signals to digital signals, processed through filters to analyse the frequency content of the vibrations and provide an instant printout or display on the current state-of-health of the engine. Such equipment might now be the size of a personal computer but the new integrated circuits will reduce this to a handful of chips. A car, for example, might be fitted with a self-diagnosed module and a collision-avoidance system. Similarly small packages could be used for speech analysis, speech synthesis or for helping to compensate for hearing, speech or sight impairments.

All d.s.p. algorithms have similar structures. They typically require the multiplication and totalling of strings of numbers. This structure is similar to the totalling of a bill where data (e.g. quantities) and coefficients (e.g. prices) are multiplied together to give subtotals which are, in turn, all added to give a grand total.

Such multiplication of data and coefficients is known as array processing. Typical algorithms are digital filtering, which may be used for improving the signal-to-noise ratio; spectral analysis, which uses fast Fourier transforms to determine the frequency content of a signal; correlation, to compare signals; estimation, to decide on the validity of a signal that is incomplete or obscured by noise; and control.

A typical d.s.p. multiplier can complete a multiplication in 150ns, about 1000 times faster than a standard microprocessor. Multipliers are typical building blocks for d.s.p. hardware, others are arithmetic logic units and sequencers.

Belying their name, Analog Devices have launched a 16 by 16-bit multiplier accumulator (mac), the ADSP-1110. This c.mos device provides a 40-bit internal accumulator and yet fits onto a standard 28-pin dual in-line package. This is because it uses only a single port but operating from a 10MHz clock, the mac can alternately load x and y operands and, when instructed, output the result.

The mac can be used as a low-cost computational accelerator in graphics systems where matrix multiplications are used in image manipulation to translate, rotate or zoom the image. Under control of the system's processor, the mac can multiply a four-by-four matrix and a four-by-one vector, requiring 16 operations in less than 4µs. It operates on six-bit instruction words, there are two control lines and an overflow flag. In the event of an overflow there is an eight-bit accumulator overflow register. The ceramic version of the ADSP-1110 is available in sample quantities. It can operate over the temperature range -55 to 125°C. A plastics-housed version with a more modest temperature range, 0 to 75°C will be available soon. Prices are thought to be about £75 each if bought in quantities over 100. Analog Devices Ltd, East Molesey, Surrey KT8 0SN.

Electronic potato

If you have noticed that the potatoes you buy are less battered than before, this may be due to research carried out by the Scottish Institute for Agricultural Engineering (SIAE). They developed an electronic potato made out of plastic foam enclosing an Entran accelerometer, a transmitter and small rechargeable batteries. The transmitter sends out a v.h.f. radio signal, modulated when the transducer is activated. This potato is handled during harvesting and potato grading along with a batch of real potatoes and the stages when the is at

most risk from damage can be monitored. A battery operated receiver and tape recorder are used to record the signals transmitted from the potato and 'voice-over' commentary may be recorded at the same time to identify the stages actually taking place. Machine adjustments, modifications or alterations to the operating speed can all be assessed with the electronic spud. Moreover it can also disguise itself as an apple or an onion which are also subject to mechanical handling. A similar technique has been used to monitor raspberry harvesting with electronic raspberries.

Do you remember Baird tv?

If you do, the Royal Television Society would like to get in touch with you. They are planning an event to mark the 50 years that have passed since the 30-line service was terminated. They would like to identify as many of those 'pioneer viewers' as possible. The honorary secretary of the midland centre of the RTS is John Grant-ham, at BBC Network Production Centre, Pebble Mill Road, Birmingham, B5 7QQ.

Briton honoured

The tenth Marconi International Fellowship has been awarded to Professor Eric Ash. Dr Ash, Professor of Electronics at University College, London, has been made "in recognition of his outstanding leadership and pioneering work in the emerging technologies of acoustic surface wave device, optical fibre-based communications, acoustic optics and acoustic imaging".

Marconi International Fellowships were founded by Guglielmo Marconi's family and are awarded each year to further research by "a leading world scientist who has made a distinguished contribution to those areas of science and technology that improve the quality of life". Readers may recall that in 1982 the fellowship was awarded to Dr Arthur C. Clarke for first specifying the potentialities and technical requirements for the use of synchronous orbiting satellites for global communications.

High-Com stereo radio

A three month public trial of compressed f.m. broadcasts is under way in Federal Germany. The system had to offer no reduction in quality to the listener without an expander in the receiver and yet when an expander fitted there should be a noticeable difference. Not surprisingly, ARD chose a home-grown product - AEG-Telefunken's High-Com compander system. The system had to be modified to fit the requirements (see German radio show report, November 1983, page 75). After modification only two out of 13 'guinea pigs' could tell any difference between the compressed and uncompressed signal and then only in direct comparisons. Moreover, tests in cars showed that there was an audible improvement in v.h.f. reception of the compressed but unexpanded signals. It is thought that this was because the compressed signal increased the volume of quieter passages which were then more easily heard above the noise background.

Interface to be made in bulk

Swamped by the orders for the IEEE488 Procyon interface for the Acorn/BBC microcomputer, Cambridge Systems Technology have been forced to award an assembly contract for the unit to an outside manufacturer. The contract has gone to CVO Electronics of Stevenage.

The device has found a considerable number of customers in professional, scientific and educational users. A high proportion of scientific test instruments use 488 interfacing especially from such manufacturers as Hewlett Packard, CBM, Philips, and Tektronix, and therefore can be monitored or controlled through a BBC computer fitted with the Procyon unit.

TAT-8 will be optical

International agreement between 28 telecommunications authorities has given the go-ahead for TAT-8, which will use hair-thin glass fibres. Two pairs of fibres will be incorporated in the cable. Each pair will operate digitally at 280Mbit/s to give a total capacity of 8000 telephone circuits. This basic capacity can be increased by digital circuit multiplying equipment up to 40 000, although initially only a small proportion of this potential capacity will be used. Monomode transmission will give the cable this high capacity and allow a long spacing, 30 to 55km, between light regenerators, the equivalent of repeaters on wire cables which are needed every 5km.

The American end of the cable will start at Tuckerton, New Jersey and the main part, 5 800km will be provided by AT&T Communications. Near the European continental shelf, a junction box will allow the cable to be split two ways. 520km of cable will be laid by STC to join the junction box to Widemouth Bay, Cornwall, while another 310km will branch off to Penmarche on the Brittany coast of France. The French branch will be the responsibility of a French company, Submarcom.

Cables and satellites share about half each the total capacity of telecommunications across the ocean. At present, including TAT-7, the cable capacity is about 11 200 telephone circuits. TAT-8, expected to come into operation in 1988, will more than double this.

Home energy monitor

On page 36 of this issue is a project to build a differential temperature integrator to monitor temperature differences in a house. Designed by Bob Everett, a research fellow at the Open University, and engineered by the OU Electronics Com-



Amongst the facilities at the Daresbury Laboratory of the Science and Engineering Research Council are the world's largest tandem Van der Graaff accelerator and the world's first high energy electron accelerator dedicated to the production and use of synchrotron radiation. In experiments to study the details of atomic nuclei, ions are accelerated to energy levels up to 20MeV. Synchrotron radiation is emitted when electron have been accelerated to a peak level of 2GeV and then deflected by the fields of storage ring magnets. It is used in atomic and molecular spectroscopy, X-ray spectroscopy and surface science. Microprocessor monitoring and alarm systems are provided by Sattcontrol of Aldershot.

mon Facility, 100 of them were made and installed in houses in Milton Keynes in the summer of 1981 as part of a series of energy conservation field trials. The Building Research Establishment put the device on its list of equipment suitable for such monitoring.

The device has proved to be useful and reliable and the OU has had a continuous stream of letters from architects and research students who would like to borrow one or have the circuit. But the potential for making them commercially is small: "The design will surely be superseded within a year or so by a suitable c.mos processor," says Bob Everett. The current cost of the components for the integrator excluding the p.c.b. and the box is a little over £100, whereas current competitive commercial systems is mainly restricted to microprocessor systems for ten or single channel ram-based devices at £400. "Although the world is full of well-intentioned people who would like to monitor the energy performance of their houses," says Everett, "there are few who are prepared to fork out that much money or harness the i/o port of their home computers to temperature monitoring for six months solid.

"It would be nice if it were possible to get the integrator as a kit," he commented, "the Open University would have no problems in selling the two double-sided circuit boards required, and the whole thing

would have the blessing of the Department of Energy, though it could be of more interest to countries such as Denmark and France where energy conservation research is not quite as unfashionable as it is here."

In brief

Giotto, the space probe which is to intercept Halley's Comet in 1986, has undergone a comprehensive check-out on its electrical and electromagnetic characteristics. The tests, on this European Space Agency project, have been carried out by British Aerospace Dynamics group, Bristol. The circular test chamber is 14m in diameter and 12m high, where the vehicle has been subjected to r.f. tests from 0.1Hz to 18GHz.

The formation of a new computer company and a new computer has been announced. The first product of Compass Computers, of Tetbury, Gloucestershire, will be the Compass 32. This is a multi-user computer which will run CP/M, MS-Dos, or Unix under the DEC operating systems. Each user will have a Z80 or an 8088 processor and 64KBytes of ram. Winchester disc memory will be available. The company is also planning a variety of add-on devices for the DEC range of computers which will include communications boards, mass storage systems, etc.

LETTERS

AMATEUR BAND JAMMING

Under the heading "Moral persuasion" (Communications Commentary, August issue) the claim is made that China has ceased to operate broadcast stations in the 7000 to 7100kHz amateur band. Whilst it may well be true that Chinese broadcast stations in this band are not heard in Europe, it is completely incorrect to say that these stations have quit the so-called amateur-exclusive band at 7000-7100kHz.

As coordinator of the New Zealand Intruder Watch, and as coordinator for the Region 3 IARU Monitoring Service, I daily handle many complaints from amateurs regarding the use of this band by the Chinese broadcasting services – and others! My records for September and October show the following frequencies to be in current usage by the Chinese Service: 7010, 7025, 7030, 7035, 7040, 7045, 7050, 7055 and 7095kHz.

With reference to the 7010kHz frequency it appears that some rearrangement of schedules may have been made but the frequency is still used by China. The People's Liberation Army station on the nominal frequency of 7025kHz, and the regular Radio Beijing station on 7055kHz, hop around between the above noted frequencies depending on the degree of jamming they are being subjected to by the Russians.

The "hopping" from one frequency to another, without warning and often in the middle of an item, brings into question – at least in my mind – the value, if any, of this type of broadcasting.

Resolution 641 of WARC 1979 calls upon stations using this band to vacate it. To date this resolution has been ignored by China – using the "reservations" procedure of the ITU Convention, and simply ignored by Albania with its Radio Tirana on 7065, 7075 & 7090kHz.

Albania at least does have the excuse that it is not a signatory to the ITU Convention, not so China and the USSR, although we "down under" do wish somebody "up there" would show the Albanians how to operate their transmitters without the resultant daily high level 2nd harmonics on 20 metres.

The USSR at times re-broadcasts one of its Mayac (home service) programmes on top of Radio Beijing – grossly over modulated – as a jamming technique, and has the lower sideband of its 7100kHz transmissions in the amateur band. To say nothing of the intense jamming, with 2nd and 3rd harmonics appearing on other amateur bands.

The "footnoting" into the 7000-7050kHz portion of this band by the fixed services of 13 countries plus its unauthorized use by the Russian fixed service, and the broadcast service as noted above, brings into mockery the whole concept of an "exclusive" band for the amateur service.

A recent random check of this band by the WIA Intruder Watch, and later confirmed by the NZART Intruder Watch, showed that between the hours of 1900 to 1925 u.t.c. on the 13th July 1983 there were 11 broadcast stations present in this band plus seven jammers, and that the activities of these stations accounted for 70.7% of the available 100kHz. At this date (28-11-83) the situation has not changed appreciably!

We can only hope that the 1984 WARC for

h.f. broadcasters will go some way to alleviate the current situation on this band.

R. E. Knowles, ZL1BAD/ZL61W
Coordinator NZART Intruder Watch
Tuakau
New Zealand

RADIO SOFTWARE

With regard to your picture coverage of our Computer Programme, Datarama, and the subsequent reponse from our colleagues at BBC Radio Leeds claiming that they were the true pioneers of Radiosoftware, I should like to make a few salient points.

Firstly, we are not in the business of claiming firsts: we believe the true originators of Radiosoftware as a broadcasting fact to be The Dutch Hobby Scoop Programme,* which began doing it in 1978.

Secondly the Datarama team, unlike it would seem the BBC Leeds team and others who've followed suit, conducted its own 'experimental data transmissions' under controlled conditions and out of broadcasting hours, i.e. not during programme time. When the first series of Datarama went on air in March 1983, Radiosoftware, at least in our hands had passed beyond the stage of experiment and was a properly researched piece of broadcast material. Within the current series, Radiosoftware forms as natural a part of the programme, as does conversation. There is no more experimentation necessary. It is time to get on with it.

Thirdly, in conjunction with the IBA, we have produced outline specifications which we hope will form the basis of future technical specifications for any station wishing to broadcast Radiosoftware. These should be available from local IBA officers in all regions.

Datarama is broadcast weekly on Radio West (in the Avon area), and on Wiltshire Radio (Swindon/W. Wilts) and very shortly on CBC Radio (Cardiff). Since its inception, each programme has included Radiosoftware for at least one microcomputer.

On the RW transmission, Datarama is supplemented by longer programmes for more micros transmitted after the stations closedown. These 'Nightfile' tapes are repeated at ¼ hour intervals throughout the night, a technique copied by Barry Norman's excellent 'Chip shop take-away service,' except that ours are free, and theirs require you to spend £3.95 on a translator kit, which is still not available at the time of writing!

Tim Lyons
Chief Engineer
Radio West
Bristol

*See also News, November, 1982.

ENERGY SAVING

I read Mr MacHarg's article and the subsequent correspondence with interest. Several of my colleagues have an interest in optimizing heating systems, and many lunch-time conversations have taken place, during which useful exchanges of ideas occur. Many different ideas are aired; individuals rate different aspects of a system with varied importance. To my mind it is necessary to get back to basics if we are to make decisions which enable us to optimize a system.


The object of a heating system is to burn fuel, thereby warming the house. A stable situation exists when heat input equals heat loss. Therefore the better insulated the property, the less energy we have to put in. This may seem very obvious, but is the first step.


Assuming, for the moment, that boiler efficiency is not affected by flame height, then in theory we could adjust the flame height to provide water at a constant temperature, so that the heat lost by the radiators was equal to the heat lost by the house to the outside world.

The usual type of system does not work this way; we rely on a variable burner duty cycle followed by the integrating effect of large thermal masses to iron out the discontinuity. Having said this we next need to define the areas of waste. There is the basic loss of heat from the building, and there is heat loss up the boiler flue. If the boiler was 100% efficient, all the heat would go into the house. Because of the effects of integration, the temperature will rise before a control thermostat operates, but continue to do so afterwards. It is recognised that the thermal inertia is normally too great to allow a simple thermostat to be used, which is why the "accelerator" heating resistor is fitted into the majority of room thermostats.

Taken in isolation, this arrangement, if operating in a constant temperature, is a duty-cycle control device. By allowing a passage of air through this device the duty cycle is modified by ambient temperature as well as by manipulation of the control. Provided that the rate of heating by the accelerator resistor can be adjusted to suit the thermal inertia of the system, a simple means of optimization is available. Unfortunately, most proprietary items do not have such a facility, so a basically sound principle is nearly always subject to maladjustment in a particular installation.

I believe that it is undesirable to have a boiler cycle continuously, particularly when only the pump is controlled by a thermostat. Unfortunately Mr Ball, whose system employs a room thermostat to control both pump and boiler simultaneously, seems to have received short shrift from Mr MacHarg in the correspondence column. This is probably because Mr Ball has not gone into as much analysis of his simple system as is desirable. I have used a similar, but not identical, system for several years. The system operates successfully because not only does it avoid excessive cycling of the boiler, but also keeps the boiler temperature as low as possible consistent with providing adequate heat, as advocated by Mr Hargis. The less required, the shorter the duty cycle becomes (controlled by the thermostat with accelerator resistor) and consequently, the lower is the maximum water temperature attained throughout the cycle. Therefore the heating effect on the surrounding air is a function of both time and rising water temperature – a point which did not emerge in Mr Ball's letter.

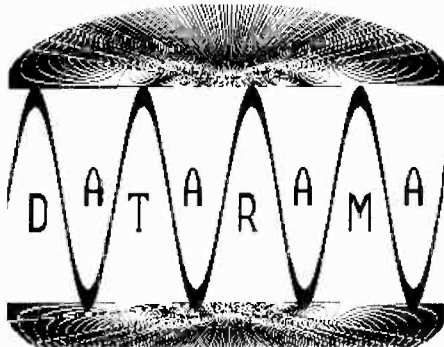

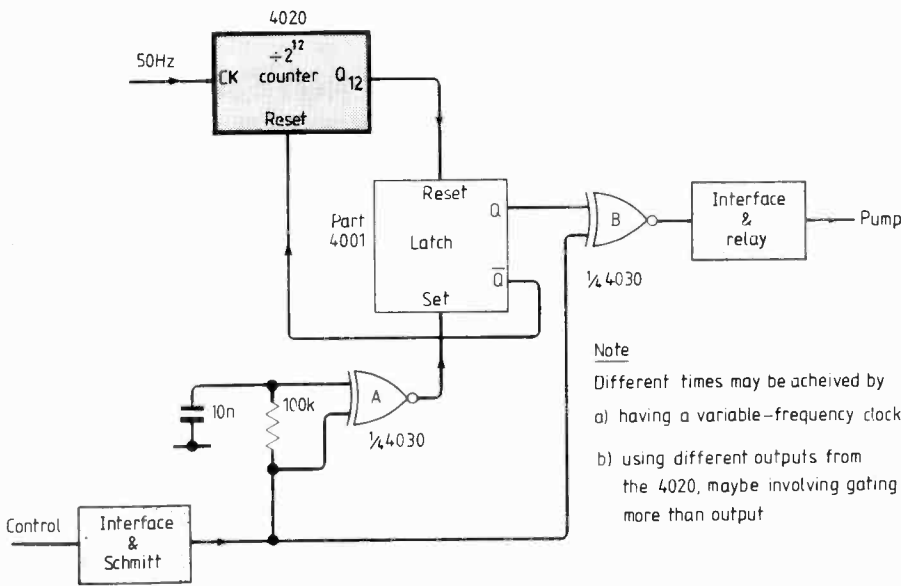

The colder the weather, the greater the heat loss from the house, the longer will be the thermostat (and therefore, boiler) on duty cycle and the hotter the radiators become. To my mind, this is exactly what a sensible system should do. It is only under the most adverse conditions that I have known the boiler thermostat (set to 77°C) to operate. The system works well because I have taken care to "tune" the accelerator resistor as mentioned earlier, using a modified commercial thermostat, placed in a carefully chosen position.

Economies can be made by modifying simple systems as described. First, I have delayed the pump start and stop relative to the controlled boiler cycle. The boiler has a cast-iron heat exchanger, and a pump delay of about 82 seconds enables the boiler temperature to rise quickly, but without overshoot, after ignition and also enables a substantial amount of heat to be extracted from the iron after the flame is extinguished.

Another economy is made by designing the domestic hot water heating facility to latch up, so it is not defeated by the clock. This enables the water heating cycle to be completed before the boiler is turned off. The facility is particularly helpful in summer, when it prevents the need for re-ignition of the boiler at the start of the following day.

I should also point out that I heat the whole house consistently; radiator valves have been adjusted and are never normally touched. Furthermore I use no supplementary heating; this would upset the balance of the system. If supplementary heating is to be used, the subject of control becomes more complex and thermostatic radiator valves are likely to be needed. This would result in changes of heat output in other areas if the duty-cycle system I have described is used.

Finally, I believe long electrical time constants to be a potential problem because of the large values of resistance and capacitance needed. The diagram shows the bare bones of the 82 second delay referred to earlier. A $\div 2^{12}$ counter counts 50Hz mains pulses, but is normally held in the reset condition. The "go" control signal (which has also fired the boiler) causes the output from the interface and Schmitt to go high. A high or low excursion on this line results in a pulse emerging from 4030A, which sets the latch. Output goes high, maintaining a low at the output of B. Output Q goes low and removes the reset from the counter,


which then counts $2^{12} = 4096$ pulses at 50 per second; this takes 81.92 seconds. The output from Q12 goes high and resets the latch; B now has only one high on its inputs - its output goes high and the pump starts. Conversely, when the control input goes low, the counter is started again which sets Q high. As the other input to 4030B is now low, the pump keeps running until the circuit times out.

Keith Cummins
Southampton
Hampshire

LOGIC NOISE MARGINS

It is standard practice to talk of noise margins in terms of noise voltage. The meaning of this is, to say the least, vague, although it has its uses. For instance t.t.l. is quoted as having a noise margin of 0.9 volts, so it is obviously asking for trouble to use discrete diodes to expand the fan in, a reasonably common malpractice, because it reduces the margin to 0.2 volts.

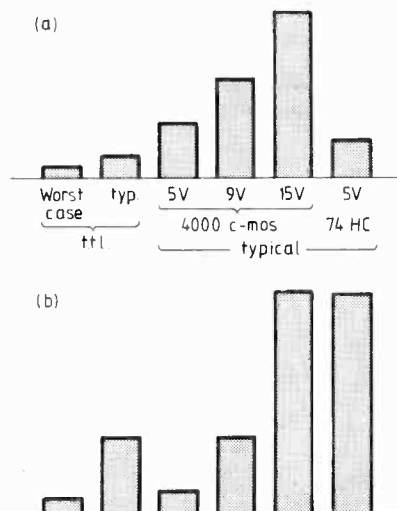The c-mos 4000 series is quoted as having a noise margin of 45% of the supply voltage - clearly superior as compared with t.t.l. - but this is only half the story. When signal lines are short as is desirable and likely within a piece of equipment, they take their impedance from the driving output according to the slogan "Low Z rules, OK?"



Short lines driven by t.t.l. are at an impedance of about 100 and the noise power necessary to overcome the noise voltage margin is $V^2/R = 0.9^2/100$ or about 8mW. The output resistance of 4000 series c-mos is 1.5kΩ to 2kΩ, so with a supply voltage of 5V the power needed to raise (or lower) the potential on the line by 45% is $2.25^2/2000 \approx 2.5$ mW. The noise power margin of t.t.l. is over three times as great at this supply voltage, see diagram.

It is worth noting that 54HC and 74HC logic has a much lower output resistance and a noise voltage margin of about 1.5 volts. Taking output resistance as 100Ω - it is in that parish though I have not seen it quoted - this requires a noise power of $1.5^2/100 = 22.5$ mW to overcome the noise voltage margin.

Using the same noise power concept, 4000 series c-mos requires a supply voltage of 9 volts to match the t.t.l. margin of 8mW, and only at a supply voltage of 15V does it achieve a noise power margin of 23mW, the equal in this respect of 74HCXX.

So far I have been considering short lines which take their impedance from the driving output. Long lines are a different matter. Correct termination is vital to establish the designed (low) impedance of the line and therefore confirm the designed noise power margin of the receiver device. It also performs its well known task of minimising reflection and radiation, two most potent causes of noise and crosstalk. Once again we are specifying and maximizing the noise power margin.

Our evaluation is not yet quite complete. An additional factor to be taken into account is the frequency response of the logic. 4000 c-mos just does not have time to propagate a noise spike of width 10ns, so its tardiness has considerable advantage if the system can be run at a frequency suitable to this logic family. The noise is effectively band limited and this is where 4000 c-mos really scores in noise immunity. The old 4049 buffer was particularly good in this respect, having a frequency limit of about 180kHz. Updated versions have a propagation delay of 60ns. Modern fast logic has a much greater bandwidth and is therefore vulnerable also to high frequency noise. So we are concerned with a balance of two factors; the noise power margin and the noise power bandwidth, both here defined by the characteristics of the logic. It is desirable to arrive at a figure of merit for noise immunity, taking both factors into account and expressed in terms which are, ideally, self-explanatory. I would welcome comments on the subject.

Tim Hartigan
Ballsbridge
Dublin

FORTH PROCESSORS

In his article and letter in November Wireless World Mr Woodroffe is less scrupulous than the Intel benchmark report that he obliquely criticises. This report, which compares the 68B09 with the 8088, can only really be faulted on the grounds that no allowance is made for code frequency in averaging out relative execution times and code sizes. It indicates, quite correctly, that re-entrancy is handled faster by the 6809.

By contrast, the table presented in his article by Mr Woodroffe can be faulted on several grounds. First, it omits the Texas 9995 processor, which competes in the same market sector as the 6809 (64k address, nonsegmented). I wonder why? The 9995 has a non-multiplexed bus and fast 16-bit parallel onboard ram; for 450ns access time its bus cycle is 670ns, versus

800 for the 8088 and 1000 for the 6809. It also makes use of prefetch.

Second, and more serious, some funny arithmetic occurs before the bottom line. The relative speeds for the 6809 and the 8088 are given as 4.11 and 3.19 respectively although the 8088 actually executes its code faster. This is derived from this "speed for 450 nanosecond access memory." I have news for Mr Woodroffe; in the real world it is not desirable to run a processor with a bus cycle allowing 695ns access at a speed which gives 450ns access. It tends not to work. In the real world the 8088 is faster by nearly 30%. Of course it would be perfectly practical to use a faster 6809 – the 68A or B 09 options – but then he should say so. If he is not actually using these faster devices in his own computer, he should tell us what access time his hardware actually requires, and recalculate his last line on that basis.

The third objection, however, is that in reality the 8088 programmer is unlikely to use the "JMP NEXT", as this requires that NEXT be within 127 bytes, necessitating numerous NEXTs scattered throughout the code rather like Underground stations (I nearly wrote public conveniences) in London. He or she will accept the 9-byte inline code (typical 6809 code is twice as long as typical 8088 code), losing 15 clocks and giving 8.6 microseconds. This execution time is slightly less than for the 6809 running at 1.5MHz with a comparable memory access time. The point, surely, is that the 8088 is the more expensive device, and the time and effort required to use features like segmentation mean that they are likely to be wasted in a small domestic microcomputer. There is no point in buying unused silicon.

The comments about code usage I agree with, except as regards the very arbitrary 80/20 ratio, seen quoted elsewhere as 75/25, $\frac{1}{3}/\frac{2}{3}$ – it is true that in most high level languages most of the time is spent pushing garbage to keep the system happy. This is why high level languages waste silicon and time while keeping programmers employed. However, the picture can change dramatically as soon as real arithmetic starts to happen, especially when trigonometry is involved. The makers of home computers assume, generally correctly, that most users will never stretch the resources of the mathematics. I would have thought, however, that electronic engineers differed in this respect; in the days when I was limited to a programmable calculator I remember calculations that exercised the poor little thing for hours on end, leading me to wish a bleeper had been fitted to announce the result. For this reason I would have thought that, again, the TMS9995 would have been a strong contender for a CPU because of its ability to handle 16 bit signed and unsigned multiplication and division in the instruction set.

Perhaps I should add that I am in no way connected with any semiconductor manufacturer.

Martin D. Bacon
Taunton
Somerset

WORLD TIMING

I am pleased that Dr J. D. H. Pilkington, head of the time department at Royal Greenwich Observatory, provided better background to the subject of "World Timing" than we were authorized to in our article on the subject; *WW* October 1983.

In our laboratory we make use of the special transmissions which disseminate UTC and CAT (co-ordinated atomic time) for calibrating and monitoring frequency sources and transmis-

sions. Therefore, one of the purposes of our article was to draw attention to the less tightly co-ordinated h.f. broadcast (and m.f.) frequencies by broadcasters since as we said, "errors of frequency can in fact be more of a nuisance than an error of time".

Indeed, in an European Broadcasting Union Report (SEBP66) entitled "A study of technical questions of interest to the WARC 1979", it was pointed out (paragraph 1.4) that the then frequency tolerance of l.f./m.f. and h.f. transmitters was unnecessarily generous, and that the stability of all carriers should be within 1Hz of the nominal assigned frequency by 31 December, 1984. It would appear from Dr Pilkington's letter that some broadcast authorities could have a busy year.

R. C. V. Macario
Department of Electrical and Electronic
Engineering
University College of Swansea

IMPLANT FOR BLADDER CONTROL

You may be interested to know that since the article on the electronic implant for bladder control was published (January issue) the device is continuing to be used to help paraplegic patients. The MRC workers who developed the implant tell me that 36 patients have now been fitted with this neurological prosthesis.

May I please correct a couple of small errors which came into the article during your preparation for publication? First, the article should have stated that the patient's hand-held transmitter (Fig. 8) was developed by T. A. Perkins of the MRC Neurological Prostheses Unit. Secondly, reference 3 should be to *Proc. IEE*, and not *IEEE*.

Tom Ivall
Staines
Middlesex

BEHIND THE MICRO

I've just read your articles 'Behind the micro' with interest, since I am thinking of expanding my interests in that direction.

Interesting . . . Well, yes, but I feel the writers haven't ever been in an actual shop to make enquiries!

The problem is, alas, compatibility. It's all very well to say that peripherals are available, but if I plug a device made by X into Y's computer, will it work – or will I get a cloud of smoke?

Don't tell me to 'consult the literature'!
So far as I can see, it is deliberately written in such a way as to discourage any such experiments!

I know what I want . . . but to do it I need to join together gadgets from SIX different makers! But can I, I just don't know!

Ronald G. Young
Peacehaven
East Sussex

DEAD WATCH TIMERS

To cope with just the sort of situation referred to by A. Roscoe under "Thunderstruck" (*Letters* February) we routinely include a "dead watch timer" in most of our new products. We also recommend our clients to use a power supply that outputs an advance warning of impending failure. These two hardware features when well integrated into the software enable

mains-related problems to be dramatically reduced, provided a third and equally vital facility is incorporated: an area of battery-backed ram to hold critical variables.

The basic idea of the dead watch timer is to have the software periodically trigger a, retriggerable monostable. As long as the software does this the monostable is prevented from reaching time out. If this happens a maskable interrupt is forced into the microprocessor. This causes activation of a special restart routine.

These facilities are essential when the system is required to "remember" long-term accumulating variables e.g. p-i-d controllers.

Steven Harris
Lodge Associates
Portslade
East Sussex

INDUCTANCE MEASUREMENT

I don't know whether the subtitle 'Simple practical method, hard to find in the textbooks' is due to the author, D. R. Fownes, or to you, but while I agree with the first half of it I think I have reason to be surprised by the second. From the sales and library loans, I venture to claim that the obvious textbook in which to look for simple practical methods of measuring inductance is my 'Radio & Electronic Laboratory Handbook', and Mr Fownes's method has been described in every edition of it from the first in 1938 (issued then by WW) to the 9th dated 1980. It was entitled 'The Three-voltages Method'.

I am obliged to Mr Fownes for deriving a simple formula for calculating the inductance. On the other hand most iron-cored inductors need to be measured with known variable amounts of d.c. flowing through them, and my measuring circuit has always shown this. Perhaps nowadays my stress on the voltmeter taking negligible current is no longer needed.

By the way, my letter in your October issue questioning the appropriateness of the term 'current dumping' having evoked no defence of it, I infer that there is no defence, and it is yet another misuse of a word in electronic terminology (e.g. 'slew rate', 'mixer' and 'attenuation distortion').

M. G. Scroggie
Bexhill
East Sussex

THE NEW BUREAUCRACY

Engineers will be regretful, but not surprised, that only one programmer in the country failed the von Neumann loyalty test. (*Wireless World* Letters, August and October 1983.)

However, D. W. Scott then writes,

"He – and MAPCON – still have not realised that machine architecture need have little to do with its technological implementation."

This statement beautifully illustrates the blocking position taken by programmers, preventing advances in the art. If, for instance, we can simulate a cam in a ram, then why should we ever want to build a cam? (If we can get there by horse and carriage, then why do we need a motor car?)

Ivor Catt
St. Albans
Hertfordshire

MICRO PRODUCTS

Apple Macintosh

The latest Apple computer is to be launched in the UK in April. Known as the Macintosh, it offers similar facilities to the Apple Lisa; it is menu driven from a display resembling a desk top where the facilities that a business executive may need can be pointed to with a cursor and selected for use by the push of a button. So notes may be scribbled on a pad, memos, expenses sheets, calculator, graph pad etc. are all available on the screen. They are selected by moving the cursor with a 'mouse', a small rolling box whose movements across the desk top are reproduced on the notional desk-top on the screen.

Macintosh uses a 16/32-bit Motorola MC68000 processor and includes 64K of rom and 128K of ram. A 512K version is due later in the year. The operating system is both rom and disc based and the computer includes a 3.5in disc drive. Each disk has a capacity of up to 400Kbytes. There is a port for an optional additional disc drive, two RS232C/422 serial ports for attaching printers or for communicating through a modem. Sound facilities give polyphonic sound over more than 12 octaves and are capable of reproducing human speech through the built-in speaker. Apple is developing a point-to-point interconnection bus and the interface is already built in to Macintosh. The integral 9in c.r.t display offers a bit-mapped 512 by 342 pixel resolution. There is a clock/calendar chip. Although not intended as a portable computer, it does have a carrying handle and at 7.7kg it weighs less than many so-called portables.

The price of Macintosh has not yet been fixed, though in the US it is likely to be about \$3,000.

Apple have produced two software packages for Macintosh; MacWrite word processing and MacDraw graphics. Lotus have developed a Macintosh version of 1-2-3, a spread-sheet and filing system and a number of software houses are preparing programs. Apple Computer (UK) Ltd, Eastman Way, Hemel Hempstead, Herts HP2 7HQ.

WW 303

Oric Atmos

The Oric 1 computer at the cheap home computer end of the market was never very successful. The



WW 303

makers made a mistake in providing prototypes rather than complete machines to the computer press who were very unkind to it. A cynical definition of the Oric 1 was "prototype for the Oric 2". The faults were compounded by the non-appearance of many promised additions and peripherals; a disc drive, a communications modem with a teletextdecoder, a rom cartridge with "super extended Basic as powerful as the BBC".

The principal difference between the Oric 1 and the Atmos is the new version of the rom operating system which has, according to Oric, not only ironed out the Oric bugs but also some others inherent in the Microsoft software. A number of additional commands have been added; especially to the cassette routines so that programs can now be verified after they have been saved. Arrays can now be stored and recalled without recourse to machine code.

The Basic is adequate and most of the commands that you would expect to find are there. We were surprised to note that there has been no attempt to improve on the abysmal line editing facility. In this respect many other computers also claiming to use 'extended Microsoft Basic' are much better (for example the Dragon and the Tandy Color Computer). Serial attributes, to change the colour or style of

characters on the screen, take some getting used to but have the advantage of taking up very little memory space.

Also provided is a cassette which has a graphics display program showing how good the display facilities are. Included is an animation of a flying duck which is very impressive especially as it is written in Basic. The program may be broken in to and listed to show how a particular effect is achieved. Also on the tape is a machine-code facility to overcome some of the frustrations of program loading mentioned above; it enables the user to override the error-checking routine. This overcomes the most common problems caused by errors in the 'header' and leading portion of the tape, which have no relevance to the actual program.

The specification for the Atmos includes a 6502A processor running at 1MHz, 48K ram, 16K rom, 57 keys and a concealed reset button for a 'warm' reset; i.e. one that does not lose any data. The screen format offers eight foreground and the same eight background colours for a text screen of 40 columns of 28 lines and a character set very similar to teletext (and BBC Mode 7) with standard ascii characters, double height and flashing characters and up to 80 user-defineable characters. High-resolution graphics offer 240 by 200

pixels in eight colours and there are line, circle and point facilities. Areas of the screen may be "filled" with a chosen colour. Three channels of sound over eight octaves with additional white noise and envelope control are output through a powerful internal speaker or may be output to a hi-fi system. There is an expansion port for the addition of some peripheral equipment, such as disc drives or a-to-d converters, a Centronics printer port, a modulated tv output as well as an RGB output for a colour monitor.

The Oric printer/plotter using four-coloured ball point pens has been re-styled to match the Atmos colour scheme and the long-promised 3in disc drive with 160Kbytes per side and a transfer rate of 250Kbit/s has been announced but at the time of writing we have not been able to get hold of one.

Those who already have an Oric 1 need not despair or throw it in the bin. Oric are looking "very seriously" at the possibility of providing an upgrade kit to turn an Oric 1 into an Atmos. This could cost about £50. 160 000 Oric 1s were sold so this could be a major operation. Oric Products International Ltd, Coworth Park, London Road, Ascot, Berks SL5 7SE.

WW 304

20MHz + 5mV/Division

TRIO


● 5mV/div Sensitivity over the Entire Bandwidth.

● Addition and Subtraction of Waveforms.

● Bright, High Resolution Display.

● Observation of Video Signals.

● Wide Sweep Time Range.

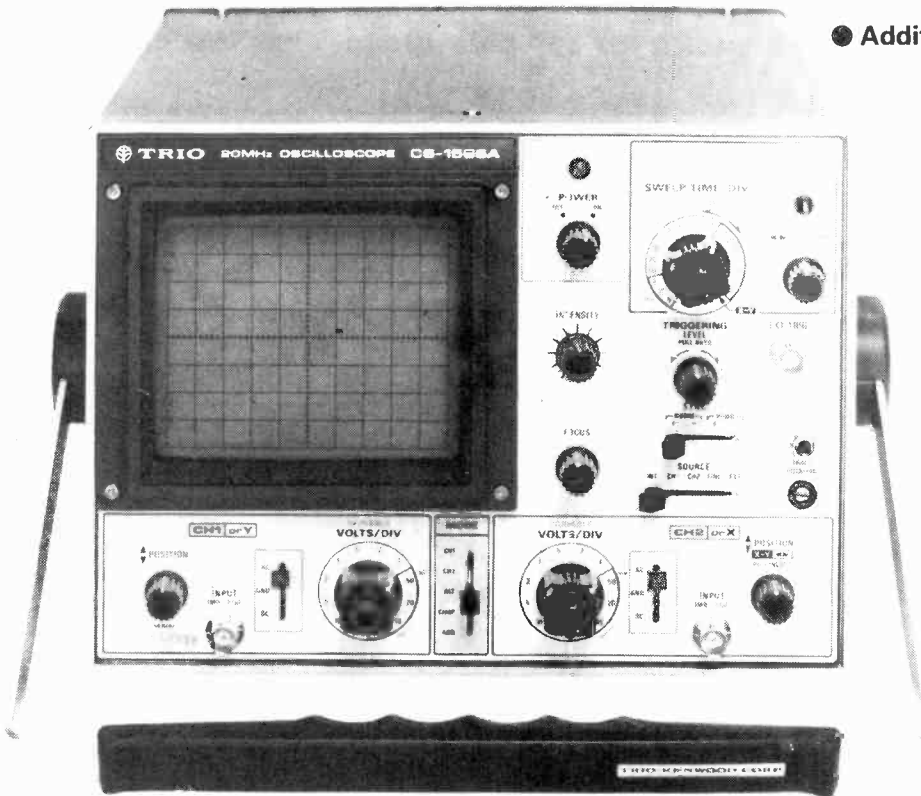

WW - 066 FOR FURTHER DETAILS

hi!

House of Instruments Ltd.
Clifton Chambers, 62 High Street
Saffron Walden, Essex CB10 1EE
Tel: (0799) 24922 Telex: 818750

TEST INSTRUMENTS

A wide range of high performance instruments that put professional test capability on your bench.

COUNTERS — TF200 10Hz to 200MHz, TF040 10Hz to 40MHz; PF M200A 20Hz to 200MHz (hand-held model); TP600 prescales to 600MHz, TP1000 prescales to 1000MHz.

MULTIMETERS — TM351 0.1% 3½ digit LCD; TM356 0.25% 3½ digit LCD; TM355 0.25% 3½ digit LED; TM354 0.75% 3½ digit LCD (hand-held model); TM451 0.03% 4½ digit LCD digit with autoranging and sample hold.

OSCILLOSCOPE — SC110A 10MHz, 10mV sensitivity, 40mm CRT with 6mm graticule divisions.

THERMOMETERS TH301 -50°C to +750°C, 1° resolution; TH302 -40°C to +1100°C and -40°F to +2000°F, 0.1° and 1° resolution. Both accept any type K thermocouple.

GENERATORS — TG101 0.2Hz to 200kHz Function Generator, Sine, Square, Triangle Waveforms; TG102 0.2Hz to 2MHz Function Generator, Sine, Square, Triangle Waveforms; TG105 5Hz to 5MHz Pulse Generator, Free-Run, Gated or Triggered Modes.

LOGIC ANALYSERS — TA2080 8 channel 20MHz, TA2160 16 channel 20MHz.

ACCESSORIES — Bench rack, test leads, carrying cases, mains adaptors, probes, thermocouple probes, microprocessor disassembly options.

For further information contact:-


Thandar Electronics Ltd, London Road, St Ives,
Huntingdon, Cambridgeshire PE17 4HJ
Telephone: (0480) 64646 Telex: 32250

 **thandar**
ELECTRONICS LIMITED

WW - 006 FOR FURTHER DETAILS




THE GOULD OS300 DUAL-TRACE 20MHz 'SCOPE

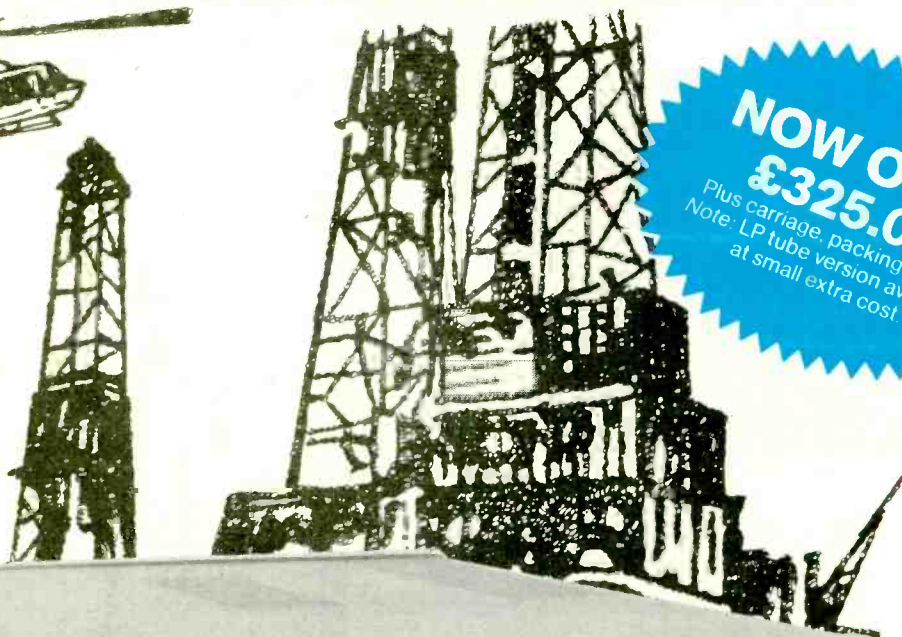

The OS300: as tough as the environment you use it in, e.g. measuring vibration characteristics of rotating machinery and mechanical structures on site.

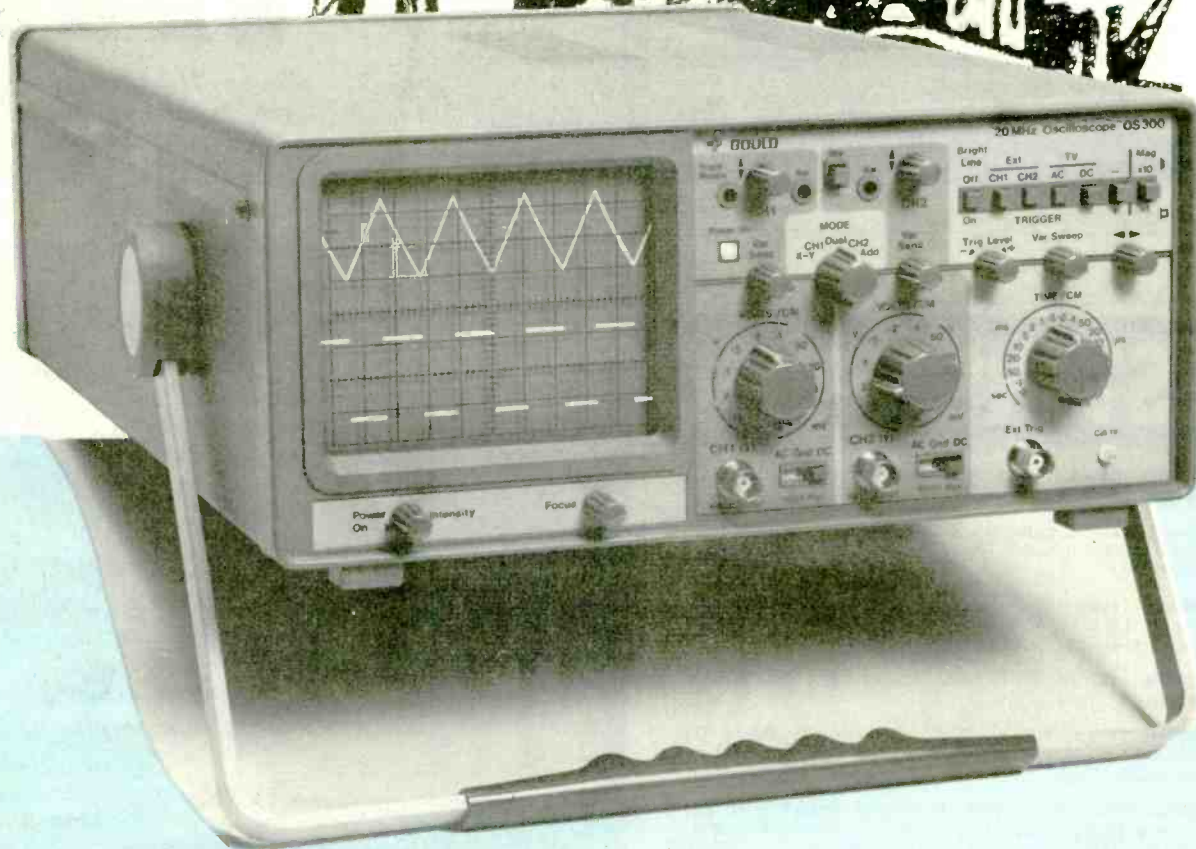**NOW ONLY
£325.00**
Plus carriage, packing + VAT
Note: LP tube version available
at small extra cost.



A tough, professional instrument you can trust – at a price you can afford! Built to do more – safely, reliably and longer.

Complete with a 2-year guarantee. This robust and highly portable oscilloscope has obvious applications in test, production, service and R & D areas.

As some of the specification highlights make clear: ★ True 20MHz operation – compare its maximum display amplitude at full bandwidth

with competitors; ★ Continuously variable amplifier sensitivity with no loss of bandwidth from 2mV/cm to 25V/cm; ★ Differential measurements can be made using the channel 2 'add' and 'invert' controls; ★ X-Y operation for frequency and phase shift measurements; ★ New type CRT with quick-heat cathode to reduce operational delays and P43 phosphor for a brighter display.

And many other features designed specifically for you!

Comprehensive data is yours for the asking. On this tough little 'scope.

Sales Department, Design & Test Systems Division, Gould Instruments Ltd., Roebuck Road, Hainault, Ilford, Essex IG6 3UE. Telephone: 01-500 1000. Telex: 26375.



GOULD
Electronics

Non-storage oscilloscopes up to 100MHz

Instruments currently available on the UK market

In the time since the last oscilloscope review appeared in *Wireless World* – a survey of portable types – it has become unnecessary to classify them in such a way, since the majority are now easily portable. Indeed, it is becoming increasingly difficult to classify oscilloscopes in any way at all: some of the functions of the more modern test instruments are those of an oscilloscope, but in some cases form only a small part of the instrument's repertoire. Logic analysis, spectrum analysis, waveform recording and even computing are now taken in hand by the latest, high-end equipment and the distinctions become blurred.

Not many instruments now exist of the type intended solely for displaying a trace. Very extensive measuring facilities in both axes are offered and, in the case of digital oscilloscopes, these can be made to an extremely high level of accuracy, sometimes with the result displayed on the screen.


To enable readers who may be out of touch with modern oscilloscope design and the characteristics and facilities provided, the terms used in manufacturers' data sheets need explanation. The first part of this survey is therefore devoted to a glossary of terms.

Signal path

Bandwidth is the passband of the Y amplifier or amplifiers, measured at the -3dB points. Normally, oscilloscope amplifiers are directly coupled, so that the amplitude response extends to zero frequency: a capacitor can usually be switched in to allow small events on a large d.c. level to appear on the screen, the bandwidth then being limited to around 10Hz rather than zero.

In some cases, it is possible to offset the d.c. by means of a panel control to achieve the same effect without loss of low frequencies. The bandwidth of the Y amplifier is the characteristic used to indicate the kind of oscilloscope under consideration.

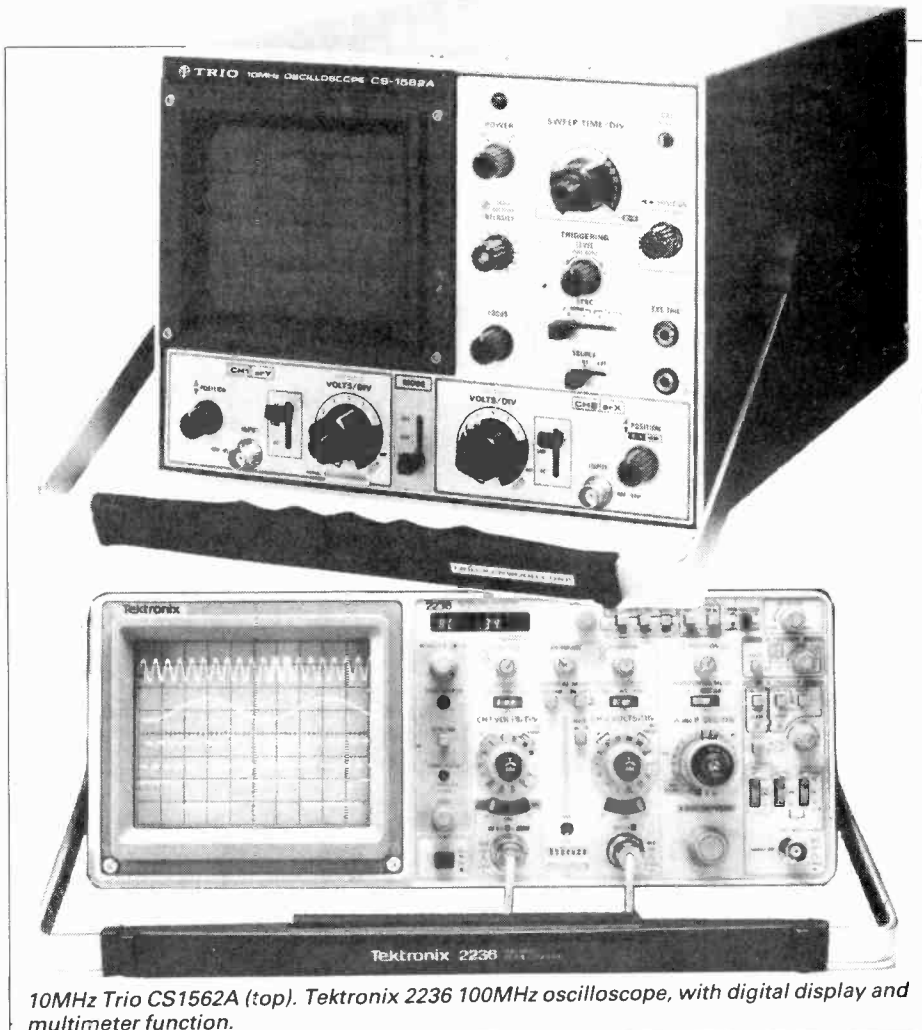Rise-time is the response time of the Y amplifier to an infinitely steep step. If the amplifier's frequency/amplitude response has a smooth roll-off at high frequencies, as they all do, then the rise time in nanoseconds can be found from the bandwidth in megahertz by the expression $t_r = 350/f$. A



10MHz Trio CS1562A (top). Tektronix 2236 100MHz oscilloscope, with digital display and multimeter function.

bandwidth of 100MHz will give rise to an amplifier rise time of 3.5ns. Since, however, voltage steps are not infinitely steep, the displayed rise time (taken from 10% to 90% of the excursion) will always be longer than this, and is equal to $\sqrt{t_{ra}^2 + t_{rs}^2}$, where t_{ra} is the amplifier rise time and t_{rs} is that of the step itself.

Deflection factor is often termed Y sensitivity and is the amount of vertical deflection of the spot on the screen for a given input voltage to the amplifier. It is measured in millivolts per division of the graticule or per centimetre. A common figure is 5mV/div and may not be constant over the whole bandwidth of the amplifier: sometimes an increased sensitivity can be

obtained by sacrificing bandwidth and rise time. The sensitivity is controlled at the front panel by a switch, working in the 1, 2, 5 sequence, and often there is a two-position auxiliary switch to increase the sensitivity by a factor of 10. When a continuously variable gain control is fitted, the amplifier is not calibrated unless the control is at the end of its travel.

Display modes describe the way in which the input signals are presented on screen, in dual-trace oscilloscopes. A front-panel control selects for display channel 1, channel 2 (one of which can often be inverted), ch1 and ch2 alternately, ch1 and ch2 effectively simultaneously by chopping from one to the other at high speed so that


Model	Y bandwidth (MHz)	Y sensitivity (mV/div)	Channels	Max sweep rate (ns/div)	Dual sweep sweep delay Y delay line	TV sync	Screen	Acceleration potential	Price		Reply card number
BK/Dynascan											
1590	100	5 (x5)	4	20 (x10)	● ● ●		8x10cm	16kV	1780	V-mode trigger	WW501
1570	80	5 (x5)	4	50 (x10)	● ● ● ●		8x10cm	12kV	1285	V-mode trigger	
1560	60	1 (CH3-0.1)	3	500 (x10)	● ● ● ●		8x10cm	16kV	1139	Trig. holdoff. Auto focus. XY operation. V-mode	
1540	40	1	2	100 (x10)	● ● ● ●		8x10cm	12kV	941	XY. V-mode	
1522	20	1	2	200	● ● ● ●		8x10cm	6kV	670	XY. V-mode	
1466A	10	1	1	500 (x10)	● ● ● ●		8x10cm	2kV	380	XY	
1476A	10	1	2	500 (x10)	● ● ● ●		8x10cm	2kV	460	Dual-trace version of 1466A	
1535A	35	2	2	100 (x5)	● ● ● ●		8x10cm	6kV	745	Variable trigger hold off. Differential	
1479B	30	5	2	200 (x5)	● ● ● ●		8x10cm	6kV	700	XY. R.f. detector triggering	
1477	15	10	2	500 (x5)	● ● ● ●		8x10cm	2kV	453	XY	
1405	5	10	1	1000 aprx.					188	Free-running time base, synchronized	
1420	15	10	2	1000 (x10)			4x5cm	1kV	650	Mains/battery	
1435	15	2	2	500 (x5)	● ● ● ●		4.8x6cm	1.5kV	677		
Crotech											
3337	30	5	2	200 (x5)	● ● ● ●		8x10cm	10kV	405	XY	WW502
3132	20	2	2	500 (x5)	● ● ● ●		8x10cm		283	XY. Tester for passive and active components	
3034	15	5	2	500 (x2.5)	● ● ● ●		5.3x6.6cm	2kV	370	Battery. XY. Battery saver	
3033	15	5	1	500 (x2.5)	● ● ● ●		5.3x6.6cm	1kV	287	Battery saver	
3030	15	5	1	500 (x2.5)	● ● ● ●		5.3x6.6cm	1kV	154	Component tester	
3035	10	5	1	500 (x2.5)	● ● ● ●		8x10cm	2kV	174	Component tester	
Datacheck											
1200B	2.5	50	1	2000 (x10)			5x4.2cm	1.8kV	4223	Modular. Up to 7 units plugged into rack.	WW518
1200B(S)	2.5	50	1	20,000 (x10)			5x4.2cm	1.8kV	4545	Dual, selectable inputs	
Farnell											
DT12-5	12	5	2	500 (x5)	● ● ● ●		8x10cm	2kV	245	XY	WW503
DTV 12-14	12	5	2	500 (x5)	● ● ● ●		8x10cm	2kV	265	More flexible Y display options.	
DTC-12	12	5	2	500 (x5)	● ● ● ●		8x10cm	2kV	359	Fine X and Y controls	
DTS-12	12	5	2	500 (x5)	● ● ● ●		8x10cm	2kV	795	Component tester	
										Digital storage version of DT12-5. Max. event speed 100kHz. Max. sample rate 0.5MHz.	
Gould											
OS300	20	2	2	500 (x10)	● ● ● ●		8x10cm		325		WW504
OS8100	100	2	2	50	● ● ● ●		8x10cm	16kV	8400	Micro-controlled. Menu display. Auto calculations	
Hameg											
HM103	10	5 (x2.5)	1	500 (x2.5)	● ● ● ●		6x7cm	1.8kV	158	Component tester	WW505
HM203	20	5 (x2.5)	2	500 (x12.5)	● ● ● ●		8x10cm	2kV	264	Component Tester	
HM204	20	5 (x2.5)	2	500 (x2.5)	● ● ● ●		8x10cm	2kV	365	Trig. delay	
HM605	60	5 (x5)	2	50 (x10)	● ● ● ●		8x10cm	14kV	487	Trig. Delay. Trig. hold off	
HM705	70	5 (x2.5)	2	50 (x10)	● ● ● ●		8x10cm	14kV	588	Trig. delay	
Hewlett-Packard											
1980	100	2	2	5	● ● ● ●		10x12cm	22kV	8516	XY Trig-view. Trig delay. Auto-ranging trig-level, deflection factor and sweep speed	WW521
Hitachi											
V-212	20	5(x5)	2	200 (x10)	● ● ● ●		8x10cm	2kV	295	XY. V-mode	WW506
V-222	20	5(x5)	2	200 (x10)	● ● ● ●		8x10cm	2kV	340	D.c. offset for small signal viewing in presence of d.c. Avoids a.c. coupling. V-mode	
V-422	40	5 (x5)	2	200 (x10)	● ● ● ●		8x10cm	12kV	510		
V-203F	20	5 (x5)	2	200 (x10)	● ● ● ●		7.5x9.5cm	2kV	355	Trig. delay	
V-353F	35	5 (x5)	2	200 (x10)	● ● ● ●		7.5x9.5cm	5.2kV	495	Trig delay	
V-1050F	100	5 (x10)	4	20 (x10)	● ● ● ●		8x10cm	20kV	1200		
V-650F	50	5 (x5)	3	50 (x10)	● ● ● ●		8x10cm	10kV	750	A-trigger view on third channel	
V-509	50	5 (x5)	2	100 (x10)	● ● ● ●		5x6.3cm	12kV	995	A.c.-d.c. Trig. delay	
V-209	20	5 (x5)	2	500 (x5)	● ● ● ●		5x6.3cm	1.5kV	525	A.c.-d.c.	
Iwatsu											
SS5702	20	5(x5)	2	100 (x5)	● ● ● ●		8x10cm	2kV	290	XY. Ac/dc	WW519
SS3510	50	2 (x5)	2	100 (x10)	● ● ● ●		5x6.4cm	12kV	1250	Batt/mains, 8.25x4x11.875in. 8.6lb	
SS5710	100	1	4	20 (x10)	● ● ● ●		8x10cm	20kV	745		
SS5711	60	1	4	50 (x10)	● ● ● ●		8x10cm	15kV	1150		
Kikusui											
COS6100	100	5 (x5)	5	20 (x10)	● ● ● ●		8x10cm	20kV	1145	XY. Displays CH1, CH2, CH3, A trig, B trig. and add simultaneously. Trig. hold off	WW511
COS3010	15	5 (x5)	2	500 (x5)	● ● ● ●		7.6x6.4cm	1.5kV	395	Mains/battery. Trig. hold off. XY	
COS5060	60	5 (x5)	3	50 (x10)	● ● ● ●		6in rect.	12kV	735	8 traces. XY	
COS5041	40	5 (x5)	2	200 (x10)	● ● ● ●		6in rect.	12kV	535		
COS5040	40	5 (x5)	2	200 (x10)	● ● ● ●		6 in rect	12kV	445	XY. Trig. hold off	
COS5021	20	5 (x5)	2	200 (x10)	● ● ● ●		6in rect	2kV	395	Trig. hold off. XY	
COS5020	20	5 (x5)	2	200 (x10)	● ● ● ●		6in rect	2kV	280	XY	
Leader											
LBO514A	15	5 (x5)	2	500 (x5)	● ● ● ●		8x10cm	1.8kV	323		WW507
LBO522	20	5 (x10)	2	200 (x5)	● ● ● ●		8x10cm	2	349	Trig. hold off	
LBO523	35	5 (x10)	2	200 (x10)	● ● ● ●		8x10cm	7kV	501	XY	
LBO524	35	5 (x10)	2	200 (x10)	● ● ● ●		8x10cm	7kV	615	XY	
Non-Linear											
MS215	15	10	2	100			2.5x3.2cm	700V	445	Batt/mains (110V a.c.) Measures 2.9x6.4x8in.	WW520
MS230	30	10	2	50			2.5x3.2cm	700V	540	Batt/mains (110V a.c.)	
Philips											
PM3262	100	2	3	50 (x10)	● ● ● ●		8x10cm	17kV	1695	Trig. hold off. Trig. view	WW512
PM3267	100	2	3	50 (x10)	● ● ● ●		8x10cm	10kV	1250		
PM3264	100	2	4	50 (x10)	● ● ● ●		8x10cm	17kV	3550	Trig. view on fifth channel	
PM3263	100	2	2	50 (x10)	● ● ● ●		8x10cm	17kV	3030	Trig. view. Dual delay for time interval measurement	
PM3254	75	2	1	50 (x10)	● ● ● ●		8x10cm	10kV	1145	Trig. view on third channel	
PM3256			2						1245	As3254 with two channels	
PM3215	50	2	2	100 (x10)	● ● ● ●		8x10cm	10kV	695	XY. Trig. hold off	
PM3217	50	2	2	100 (x10)	● ● ● ●		8x10cm	10kV	850	As 3215 with delayed time base	
PM3233	10	2	2	200 (x5)	● ● ● ●		8x10cm	10kV	960	Dual beam	
PM3211	15	2	2	500	● ● ● ●		8x10cm	4kV	660		
PM3207	15	5	2	500 (x5)	● ● ● ●		8x10cm	2kV	325	X and Y sensitivity equal	continued on page 61

WELL WORTH A SECOND LOOK...

NEW!!!

No — you're not seeing double, just the Crotech 3132's Component Comparator in action. This unique feature, using two Crotech component testers, gives you the benefit of checking an active or passive component against a known standard. Complete circuits can also be checked using signature techniques.

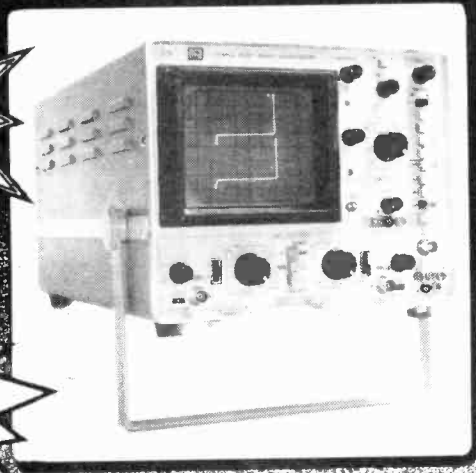But that's not the only new feature. The 3132 has three DC source outlets available on the front panel, capable of powering most solid state circuits. Dare we say that the 3132 is the nearest affordable 'scope to come near to being a complete test system?



14 Trigger Functions
Triggering up to 40MHz

2mV/div

X-Y Mode

DC — 20MHz

40ns — 0.2s/div

PLUS

COMPONENT COMPARATOR and DC SOURCE OUTLETS

Add & Subtract


Crotech Instruments Limited
5 Nimrod Way, Elgar Road, Reading, Berkshire, RG2 0EB.
Telephone: (0734) 866945

For full data sheet and a copy of our Highlight brochure — all free — just give us a call or fill in the enquiry card

WW — 050 FOR FURTHER DETAILS

THE HM 605 ~ BEYOND COMPARISON ~THE CHOICE IS HAMEG

NEW PRODUCT

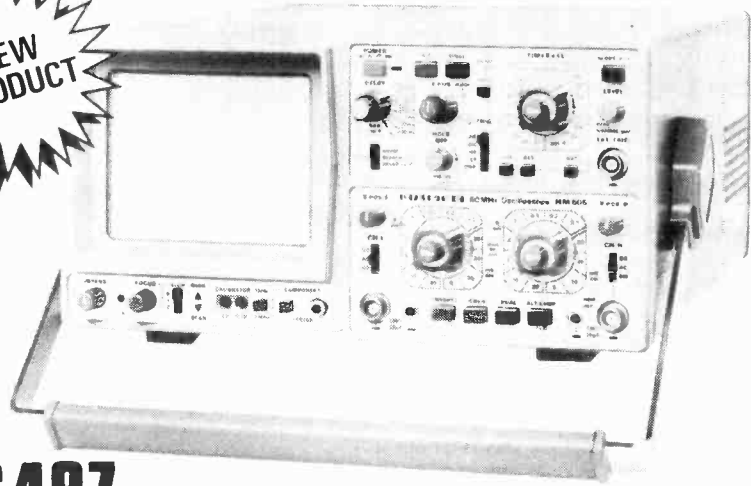

£487 Prices U.K. list ex. VAT

Ideally Suitable for Computer Systems Applications

- 60 MHz Bandwidth
- 5mV—20V Sensitivity at 60MHz
- 1mV Sensitivity at 30MHz
- Timebase Range 5ns—2.5s/cm
- Reliable Triggering to 80MHz
- Normal and Peak Value Triggering
- Alternate Triggering
- Variable Sweep Delay
- 14kV Rectangular CRT
- Y-Output
- 1kHz/1MHz Calibrator
- Component Tester
- 2 Year Warranty

For free data sheet of the full range contact:

HAMEG

74-78 Collingdon St. Luton Beds, LU1 1RX
Tel: (0582) 413174 Telex 5

WW — 015 FOR FURTHER DETAILS

Out of this world for value!

ET Not our extra-terrestrial friend, but a versatile bench power supply –

– the ET30/2

For a modest price it will provide you with:

2 outputs at 0 to 30 volts d.c. at 1 amp or
2 outputs at 0 to 15 volts d.c. at 2 amps or
0 to 30 volts d.c. at 2 amps or 0 to 60 volts
d.c. at 1 amp or 0 to 15 volts d.c. at 4 amps.

from



Farnell



Send for details now from: FARNELL INSTRUMENTS LIMITED · WETHERBY · WEST YORKSHIRE LS22 4DH
TELEPHONE (0937) 61961 · TELEX 557294 FARIST G | REGIONAL OFFICE TELEPHONE (05827) 66123/4 · TELEX 826307

WW – 033 FOR FURTHER DETAILS

SCOPEX 14D10V VITAL FOR VIDEO

A high sensitivity (2mV) oscilloscope with an advanced digital delay system for TV line selection providing an exceptionally stable and inherently jitter-free display from inherently unstable mechanically reproduced video recording systems, whether tape or disc. The digital counting system operates on line numbers (selected by a 10-turn vernier delay control), not on elapsed time thus guaranteeing jitter-free traces even after a delay of almost a full field.

Designed primarily for the video service market, the 14D10V with its large screen and advanced facilities also offers considerable advantages to Technical Colleges and Polytechnics for demonstrating modern TV methods and for work on video, text and digital techniques.

Outstanding value at only **£365** plus VAT. Send for full specification details today. British designed and made. Agents required worldwide.



SCOPEX
the oscilloscope people

Scopex Electronics Limited
63-65 High Street, Skipton, North Yorkshire BD23 1EF
Tel: Skipton (0756) 69511

NEW

WW – 087 FOR FURTHER DETAILS

WIRELESS WORLD MARCH 1984

Model	Y bandwidth (MHz)	Y sensitivity (mV/div)	Channels	Max sweep rate (ns/div)	Dual sweep sweep delay Y delay line	TV sync	Screen	Acceleration potential	Price	Reply card number
Rohde & Schwarz										WW508
BOP	30	5	2	200 (x10)	● ● ●		8x10cm	6kV		
BOL	100	5	4	20 (x10)	● ● ● ●		8x10cm	18kV	Displays eight traces, with trig. view	
Scopex										WW509
14D-10V	10	2	2	1000 (x5)		●	8x10cm		325 XY. Tv line delay. Tv & video servicing	
14D-15	15	5	2	1000 (x10)		●	8x10cm	2kV	285 XY	
Scopextra FC	15	5	2	1000 (x10)		●	8x10cm	2kV	365 As 14D-15 with add-on function generator	
Scopextra PS	15	5	2	1000 (x10)		●	8x10cm	2kV	385 As 14D-15 with add-on dual power supply	
Bridage SB121	5	50	1	1000			5x6cm		175	
DB242	5	50	2	1000			5x6cm		195 As SB121 but two channels	
Siemens										WW513
D1004	50	2	2	10	● ● ●		8x10cm	11kV	1150 XY	
Rest of Siemens range under revision										
Solartron										WW510
5220	100	5	2	50 (x10)	● ● ●		8x10cm	12kV	1545 Dig. time measurement	
5224	100	5	4	50 (x10)	● ● ● ●		8x10cm	12kV	1881 As 5220 but four channels	
5222	50	5	2	100 (x10)	● ● ●		8x10cm	10kV	1279 XY. Trig. delay	
5013	15	5	2	1000 (x5)		●	8x10cm	2kV	477 XY	
5023	15	5	2	1000 (x5)		●	8x10cm	2kV	448 As 5013, with fine gain adj. and A±B	
5024	10	5	4	1000 (x5)		●	8x10cm	2kV	988 A.c./d.c. XY	
5025	25	5	2	200 (x5)	● ● ●		8x10cm	4kV	778 XY	
5500					●		10x12.5cm	20kV	2633 XY. Mainframe with probe power. R version rack mount	
5522	175	5	2						1208 D.c. offset. 5500 plug-in	
5532	85	2 (x5)	2						895 5500 plug-in	
5523	1	0.02	2						778 Differential amp. for 5500. C.m.r.r. 100dB at 20µV and 100kHz	
5533	85	1	2						1416 Diff. comparator for 5500. C.m.r.r. 86dB at 1mV and 100kHz	
5546				20 (x10)	●				964 Dual time base for 5500	
5539	>1GHz	2 (x2.5)	2	0.02	●				2264 Sampling plug-in for 5500	
Tektronix										WW514
2337	100	5 (x2.5)	2	50 (x10)	● ● ●		6.4x8cm	18kV	2695 Trig. view. Trig. hold off. XY. D.v.m. Diff. time	
2336	100	5 (x2.5)	2	50 (x10)	● ● ●		6.4x8cm	18kV	2274 As 2337 without d.v.m.	
2235	100	5 (x2.5)	2	50 (x10)	● ● ●		6.4x8cm	18kV	2122 As 2336 without diff. time measurement	
2213	60	2	2	50 (x10)	● ● ● ●		8x10cm	10kV	880 Trig. hold off. Trig. delay	
2215	60	2	2	50 (x10)	● ● ● ●		8x10cm	10kV	1063	
335	35	10	2	200 (x10)	● ● ● ●		6.4x8cm	12kV	2796	
T422R	15	2	2	200 (x10)	● ● ● ●		8x10cm	12kV	765 XY. Rackmount	
308	5	5	2	1000 (x10)	● ● ● ●		5x6.3cm	2kV	333 D.v.m.	
221	5	5	1	1000 (x10)	● ● ● ●		3.1x5.2cm	1kV	1826 Mains/battery	
213	1	5	1	2000 (x5)	● ● ● ●		3.1x5.2cm	1kV	2327 D.v.m. display on screen. Mains/battery	
212	0.5	1	2	5000 (x5)	● ● ● ●		3.1x5.2cm	1kV	1645 Mains/battery	
7104	1GHz		2	0.2 max	●		6.8x8.5cm	12.5kV	19821 Mainframe. V and I calibrator	
Y plug-ins from 75 MHz to 1GHz, from 1m V/div.										
Y plug-ins from 0.2ns/div, delayed sweep, programmable										
5440	50 max		2	10max	●		9x12cm	15kV	2438 Mainframe	
5A38	35	10 (x2.5)	2						596 5440 Y plug-in	
5A48	50	1 (x2.5)	2						879 5440 Y plug-in	
5B40				100 (x10)	●				614 5440 X plug-in	
5B42				100 (x10)	●				1131 5440 X plug-in	
465	100	5	2	200 (x10)	● ●		8x10cm	18kV	2852 Trig. view	
Thandar										WW515
SC110A	10	10	1	100		●	3.2x2.6cm		D.c. or a.c. adaptor	
Trio										WW516
CS2110	100	5 (x5)	4	20(x10)	● ● ● ●		8x10cm	20kV	1499 Four channels, eight traces	
CS2070	70	5 (x5)	4	50 (x10)	● ● ● ●		8x10cm	12kV	949 V.c.r. and video disc work	
CS1577A	35	2	2	100 (x5)	● ● ● ●		140mm tube	6kV	499 Trig. hold off. XY	
CS1830	30	5 (x2.5)	2	200 (x5)	● ● ● ●		140mm tube	6kV	583 Trig. delay. Trig. hold off. XY	
CS1010	10	1	1	500 (x10)	● ● ● ●		8x10cm	2kV	269 V-mode	
CS1012	10	1	2	500 (x10)	● ● ● ●		8x10cm	2kV	289 As 1010, but two channels	
CS1020	20	1	1	200 (x10)	● ● ● ●		8x10cm	6kV	339	
CS1022	20	1	2	200 (x10)	● ● ● ●		8x10cm	6kV	359 As 1020, but two channels	
CS1566A	20	5	2	500 (x10)	● ● ● ●		140mm tube	2kV	349 XY	
CS1820	20	5 (x2.5)	2	200 (x5)	● ● ● ●		140mm tube	6kV	442 Trig. hold off. Trig. delay	
CS1720	20	2	2	200 (x5)	● ● ● ●		7.6x9.5cm	6kV	1674 Programmable functions	
CS1352	15	2	2	500 (x5)	● ● ● ●		75mm tube	1.5kV	431 Mains/batt. XY	
CS1560A	15	10	2	500 (x5)	● ● ● ●		130mm tube	2kV	325	
CS1562A	10	10	2	1000 (x5)	● ● ● ●		130mm tube	2kV	279	
CS1559A	10	10	1	1000 (x5)	● ● ● ●		130mm tube	2kV	265	
CS1575	5	10	2	500	● ● ● ●		130mm tube		358 Displays CH1, CH2, Lissajou and 0° phase simultaneously	
Vu-data										WW517
4100	100	5	2	50 (x10)	●		2x2.5cm	6kV	1850	

the chopping is invisible, ch1 minus ch2 and ch1 plus ch2.

The 'alternate' and 'chopped' presentations perform roughly the same function. At low and middle frequencies, chopping between channels occurs many times during the time-base sweep and is generally not phase-related: it cannot, therefore, be seen and the two traces appear simultaneously. At higher frequencies, the chopping may occur only a few times during a sweep and may become visible, so that each trace must then be triggered alternately to give once again an effective simultaneous display of the two signal channels.

Input impedance at the Y inputs is usually $1M\Omega$ with 20-30pF in parallel. In the event that the signal under inspection is from a high-impedance source and would be deformed by this input arrangement, most makers provide as an accessory a probe which, at the expense of a decrease in sensitivity by a factor of 10, gives $10M\Omega$ and 2pF at the probe tip. Even better performance is provided by probes with a field-effect transistor source-follower, which can give $1M\Omega$ and around 1pF even when the input of the oscilloscope is a 50Ω coupling – often found with high-frequency instruments.

Input coupling selects a coupling capacitor when the d.c. component of a signal is too high to allow inspection of small features which need a high sensitivity. It is usually marked AC, DC and GND, the latter earthing the input to provide a 0V reference on the display.

Delay line allows inspection of the leading edge of a transient. Since the signal itself normally triggers the time-base, and since the time-base takes a certain amount of time to fire after the trigger, the leading edge would have occurred before the sweep started, without the delay line.

With the line in the signal path, the signal is delayed by a fraction of a microsecond until the time-base is operative. The delay line does not deform the signal.

Time-base

Modern time-bases are of the triggered variety – they run when triggered by a pulse. The rate at which the spot sweeps across the screen is controlled from a front-panel switch, usually in a 1-2-5 sequence, and by an uncalibrated variable control. The fastest sweep provided must spread the rise-time of the Y amplifier over a useful part of the screen; for example, if the bandwidth is 100MHz, giving a rise time of 3.5ns, the highest sweep speed should be around 2 to 5ns per division or per centimetre. It may be that the fastest sweep on the control is ten times slower than this, at around 50ns per division, in which case there will probably be provision to magnify the sweep amplitude to overscan the screen by a factor of 10, effectively multiplying the sweep speed by 10. The result is roughly the same.

Horizontal modes

In dual-trace instruments, delayed sweeps with a number of display modes are commonplace. In essence, the main (A) sweep

traverses the whole area of investigation relatively slowly, small events being identifiable but not easily seen. By means of a delay control, the second (B) sweep is triggered just before the area of interest and, since it is set to run much faster than the A sweep, covers only that part. During this time the A sweep only is displayed, the part covered by the B sweep being brightened up.

When the delay and the duration of the B sweep are adjusted as required, the B sweep is displayed across the whole screen, the aforementioned small event now being magnified horizontally. The front-panel mode selector is labelled A, A intensified by B, B, or words to that effect. On some instruments, the delayed and delaying sweeps can be mixed to display both simultaneously. It might be possible to see the small occurrence in the normal way with sweep magnification, if it were near the trigger pulse, but a large magnification on a small trace would almost certainly result in a jittery display: the delaying method avoids this problem.

Triggering

A variety of triggering modes is usually provided. 'Normal' is the condition when the Y signal provides a trigger pulse for the time-base, which does not sweep unless the trigger is present. In the 'automatic' mode, the time-base free runs, providing a base-line on the screen in the absence of a Y signal, and locks to an applied signal: it is somewhat similar to the method used many years ago when free-running time-bases were synchronized with the Y signal. A 'single-sweep' facility is sometimes provided, when the timebase fires once on the next trigger after a front-panel button is pressed. Trigger hold-off is useful when, say, one cycle in a long train is to be viewed. It would normally not be easy to trigger the sweep just before the wanted cycle, since as far as the trigger circuit is concerned, all the cycles are identical. With trigger hold-off, pulses can be inhibited until the part to be investigated is reached, whereupon the next trigger fires the time-base, which can then run at the desired speed.

Since the Y signal itself normally provides the trigger, it is necessary to select the exact point on a waveform at which the trigger pulse is generated. The 'level' control sets this in the vertical direction and the 'slope' determines whether the trigger is taken from a positive or negative-going edge. It is usually possible to use an external trigger, selectable from the front panel. Vertical-mode triggering (V mode) enables two traces of differing frequencies to be viewed alternately – normally, triggering from one would give an unlocked display of the other.

In the table, sensitivity and sweep-speed figures are given without taking into account the multipliers shown in brackets. Prices quoted are exclusive of v.a.t.

For more complete information, insert the **WW No** on the Reader Service Card facing page ££.



Manufacturers

BK/Dynascan. B & K Precision, P.O. Box 27, 39 Whitby Street, Hartlepool, Cleveland TS24 7BR. 0429 75750.

Crotech. Crotech Instruments Ltd, 5 Nimrod Way, Elgar Road, Reading, Berks. RG2 OEB. 0734 866945.

Datacheck. RMR Measurements, 138 Lime Crescent, Cumbernauld G67 3PQ. 02367 28170.

Farnell. Farnell Instruments Ltd, Sandbeck Way, Wetherby, West Yorks. LS22 4DH. 0937 61961.

Gould. Gould Instruments Division, Roebuck Road, Hainault, Essex IG6 3UE. 01-500 1000. Electroplan Ltd, P.O. Box 19, Orchard Road, Royston, Herts ST8 5HH. 0763 45145.

Hameg. Hameg Oscilloscopes Ltd, 74-78 Collingdon Street, Luton, Beds LU1 1RX. 0582 413174. Lawtronics Ltd, 139 High Street, Edenbridge, Kent TN8 5AX. 0732 865191.

Hewlett-Packard. H.P. Ltd, Nine Mile Ride, Easthampstead, Wokingham, Berks RG11 3LL. 03446 3100.

Hitachi. Hitachi Denshi (UK) Ltd, 13-14 Garrick Industrial Centre, Garrick Road, Hendon, London NW9 9AP. 01-202 4311.

Reltech Instruments. New Road, St. Ives, Huntingdon, Cambs. PE17 4BG. 0480 63570.

Iwatsu. STC Instrument Services, Edinburgh Way, Harlow, Essex CM20 2DF. 0279 29522.

Kikusui. Telonic Instruments Ltd, 2 Castle Hill Terrace, Maidenhead, Berks SL6 4JP. 0628 73933.

Non-Linear Systems. Lawtronics Ltd, 139 High Street, Edenbridge, Kent TN8 5AX. 0732 865191.

Leader. Thandar Electronics Ltd, London Road, St. Ives, Huntingdon, Cambs PE17 4HJ. 0480 64646. Also Electroplan Ltd, P.O. Box 19, Orchard Road, Royston, Herts. SG8 5HH. 0763 45145.

Philips. Pye Unicam Ltd, York Street, Cambridge, CB1 2PX. 0223 358866.

Electronic Brokers Ltd, 61/65 Kings Cross Road, London WC1X 9LN. 01-278 3461.

Rohde und Schwarz. R & S GmbH & Co KG, D-8000 Munchen 80, Muhlendorfstrasse 115, West Germany. (089) 4129-1.

Scopex. Scopex Electronics Ltd, 63-65 High Street, Skipton, N. Yorks. BD23 1EF. 0756 69511.

Siemens. Siemens Ltd, Siemens House, Windmill Road, Sunbury-on-Thames, Middlesex TW16 7HS. 09327 85691.

Solartron. Solartron Schlumberger, Victoria Road, Farnborough, Hants GU14 7PW. 0252 544433.

Tektronix. Tektronix UK Ltd, P.O. Box 69, 36/38 Coldharbour Lane, Harpenden, Herts, AL5 4UP. 05827 63141. Also Electroplan Ltd, P.O. Box 19, Orchard Road, Royston, Herts SG8 5HH. 0763 45145.

Thandar. Thandar Electronics Ltd, London Road, St. Ives, Huntingdon, Cambs. PE17 4HJ. 0480 64646.

Trio. House of Instruments, Clifton Chambers, 62 High Street, Saffron Walden, Essex CB10 1EE. 0799 24922. Also Lawtronics Ltd, 139 High Street, Edenbridge, Kent TN8 5AX. 0732 865191.

Vu-data. RMR Measurements, 138 Lime Crescent, Cumbernauld G67 3PG. 02367 28170.

Give your oscilloscope 8 channels with the *NEW* 8001 SCOPE MULTIPLEXER



Now, GSC offers every scope user the ability to view eight traces simultaneously. With the new 8001 scope multiplexer, any single-channel or two-channel oscilloscope is transformed into an 8-channel instrument, opening up whole new areas of digital and analogue measurement. With the 8001, you can use an ordinary scope for measurements that previously needed a logic analyser — whether you are comparing simultaneous events or looking at cause and effect relationships in complex digital circuits.

And the 8001 is so simple to use, with clearly labelled front-panel controls and a comprehensive instruction manual. Input is via eight BNC connectors, and the 8001 will accept signals of $\pm 5V$ (10V peak-to-peak) with a 3dB frequency response which is flat to 12MHz — ample for most general-purpose oscilloscope measurements.


It's versatile, too. You can look at all eight channels at once, or just channels 1 - 4 or 5 - 8, and then zero in on a single channel for closer examination using the instrument's manual control mode.

All the usual trigger features are present, and a simple pushbutton control allows easy calibration by adjusting the vertical gain.

Whether your application is in the development laboratory or field service, the 8001 is a valuable new tool that extends your measurement capabilities.

And the price is right, too — as you'll see from the coupon. Why not fill it in right away.

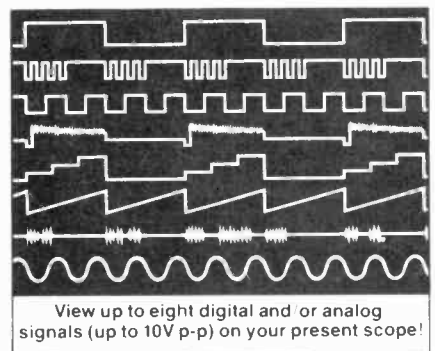LOW COST
£225
(£263.35 inc. P & P and 15% VAT)



GLOBAL SPECIALTIES CORPORATION



G.S.C (UK) LIMITED 7F

UNIT 1, SHIRE HILL INDUSTRIAL ESTATE
SAFFRON WALDEN, ESSEX CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

GLOBAL SPECIALTIES CORPORATION (UK) LIMITED, DEPT. 7F

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

8001 SCOPE MULTIPLEXER	£263.35 (inc. P & P) and 15% VAT	Quantity Req'd.	For FREE catalog tick box
------------------------	----------------------------------	-----------------	---------------------------

Name _____ Address _____

I enclose PO/Cheque for £ _____ or _____

Barclaycard/Access/American Express. No. _____ exp date _____

HIGH CAPABILITY. LOW PRICE.


There's never been
better value, anywhere

£735

Like Kikusui's COS5060.
A really professional 60MHz dual
channel, dual timebase delayed
sweep oscilloscope.

Just part of Kikusui's COS5000 dual
channel oscilloscope range, including
20MHz and 40MHz single and dual
timebase models from less than £300
+ VAT, including probes
and delivery.

Mostly ex stock.
Ask for data.

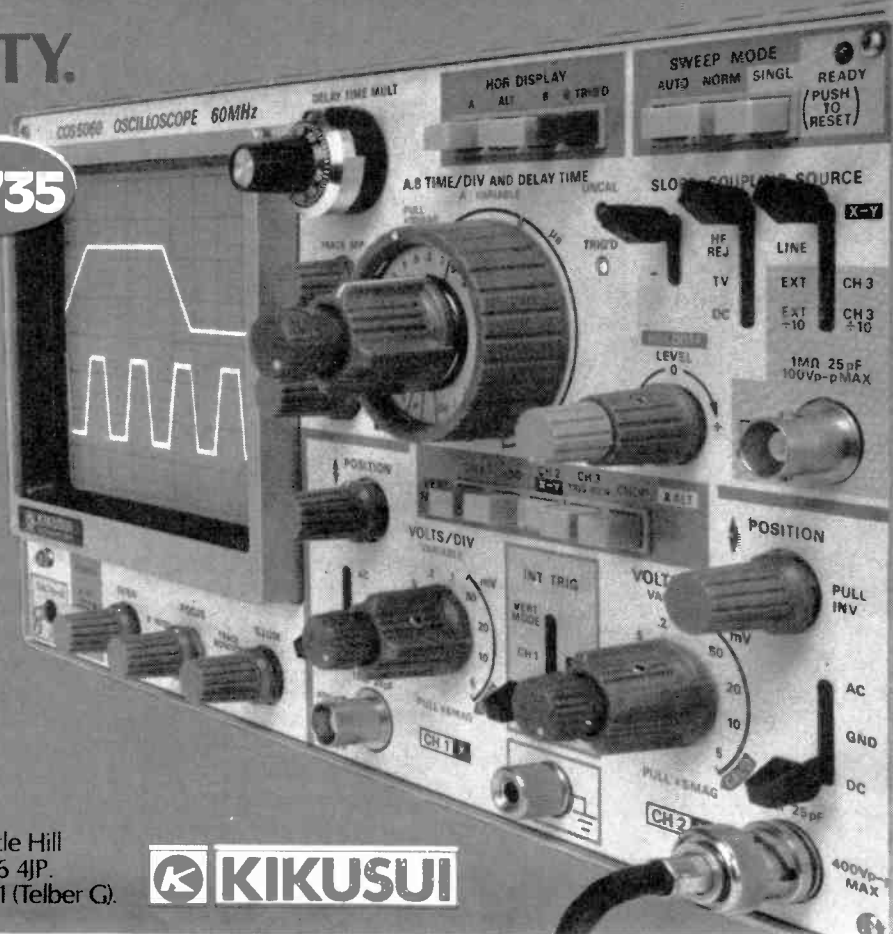

Telonic Instruments Ltd, 2 Castle Hill
Terrace, Maidenhead, Berks, SL6 4JP.
Tel: (0628) 739333. Telex: 849131 (Telber G).




No Project Is Complete Without The Right Housing ...

KMT

The unique new modular enclosure.

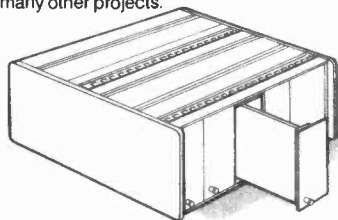Suitable for alarm systems, counters,
interfaces amplifiers, model control units
and many other projects.



Easy to assemble - just 10 screws.

Easy on the pocket - house your projects
economically and professionally.


For full size eurocards (100 x 160mm)
mounted horizontally in the 35TE front
panel kit.

Half size eurocards (100 x 80mm)
mounted vertically included as part of all
front panel kits (except 35TE), with
connector included.

Hi-Style Desk Top Case

Designed to house keyboards and
displays on two 1,6mm silver anodised
aluminium panels. The light brown case
is manufactured from high impact polystyrene
and has a textured finish.

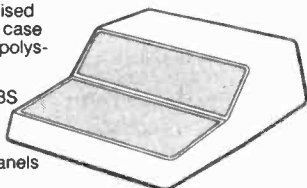- Casing-High impact textured ABS
- Colour-Brown, front and base panels
1,6mm satin anodised aluminium



Hand Held Box



This box is moulded in two sections and
has a textured finish. The battery
compartment accepts a PP3 or nickel cadmium
stack 25 x 45mm long. A circuit
board 56 x 105mm may be mounted on
three pillars in the base, location being
provided by a 3mm spigot. The top
moulding will accept a circuit board 71
x 107mm.

- Material-Textured ABS
- Colour-Dark brown

Plastic Boxes Type A

Plastic boxes consisting of a top and
bottom moulding with front and rear
aluminium panels, positively retained in
the two halves.



- Top and bottom moulding-High
ABS.
- Colour-Light grey top: dark grey base.
- Front and rear panels-Satin anodised
aluminium 1,6mm thick.

Type B

Constructed of high impact polystyrene,
these handsome two-toned grey boxes
are suitable for wall mounting and free
standing instruments. The two halves of
the box are held together by screws
inserted from the base.

- Material-High impact polystyrene
- Colour-Top light grey: base dark grey
- Panels-Satin anodised aluminium

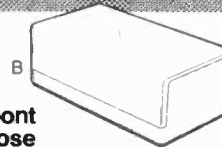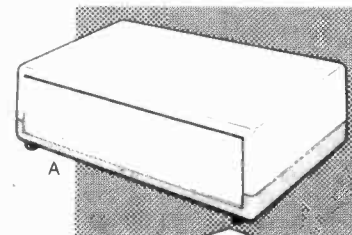Send 50p for a copy of the catalogue with
details of the full range available.



... Why don't
you choose
BICC-Vero Enclosures.
A complete range where
quality and economy are
combined.

BICC-VERO ELECTRONICS LIMITED


Retail Department,
Industrial Estate,
Chandlers Ford,
Hants SO5 3ZR
Tel (04215) 62829



WW - 053 FOR FURTHER DETAILS

Hitachi Oscilloscopes

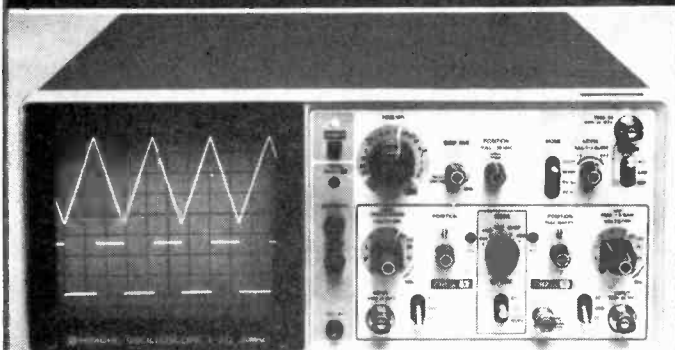performance, reliability, value
and immediate delivery!



Hitachi Oscilloscopes provide the quality and performance that you'd expect from such a famous name, with a newly-extended range that represents the best value for money available anywhere.

V-212	20MHz Dual Trace	V-209	20MHz Mini-Portable
V-222	20MHz (illustrated)	V-509	50MHz Mini-Portable
V-203F	20MHz Sweep Delay	V-1050F	100MHz Quad Trace
V-353F	35MHz Sweep Delay	V-134	10MHz Tube Storage
V-422	40MHz Dual Trace	VC-6015	10MHz Digital
V-650F	60MHz Dual Timebase	VC-6041	40MHz Digital

Prices start at around £300 plus VAT including two probes and two year warranty. We hold the range in stock for immediate delivery.

For colour brochure giving specifications and prices ring (0480) 63570 Thurlby-Reltech, 46 High Street, Solihull, W. Midlands B91 3TB.

WW - 021 FOR FURTHER DETAILS

ELECTRONICS & Wirelessworld


EDITORIAL FEATURES 1984

ISSUE DATE	PUBLICATION DATE	FEATURE
June 1984	May 16th	Emulators
July 1984	June 20th	2m Transceivers
Sep. 1984	Aug. 15th	Digital Multimeters
Dec. 1984	Nov. 21st	Components Buyers Guide
Jan. 1985	Dec. 19th	Single Board Computers

For more details regarding advertising contact Bob Nibbs
01-661 3130

Nicolet 3091 Portable Digital Oscilloscope

Portable Precision

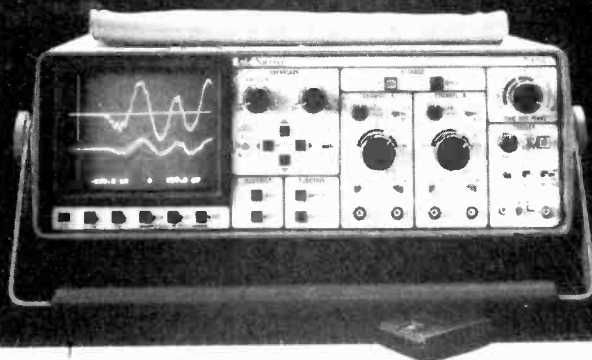

Measure With Accuracy

Precision is simple with the new 3091 digital oscilloscope. High resolution digitizers (12-bit) improve accuracy 10 times over analog scopes. Clear numeric readouts eliminate human error and guesswork in critical situations. Extremely high dynamic range is at your fingertips with zoom expansion for any waveform section up to X60.

Capture Transients With Push-Button Ease

Hold one-time events in each 4k memory and on the screen. You can examine signals from an intermittent problem minutes or even days after the occurrence. Using self-explanatory controls, set the scope to capture pre- and post-trigger information. View what led up to an event as well as what occurred afterwards.

Store Signals In A Bubble

The 3091's unique bubble memory option provides reliable non-volatile storage in a handy cassette. Controls are simple read-write buttons on the front panel. Store up to ten 2000-point waveforms on each cassette.

Display Mode Options

Select the display mode to suit your measurement needs: YT, XY, or ROLL mode can be combined with either a CURSOR or GRID display. In all modes reference signals may be displayed for comparison with incoming signals. These references may be recently acquired waveforms or signals recalled from bubble memory.

Price-Performance

The 3091 offers many of the advantages of Nicolet's more powerful benchtop models—high resolution, ease of use, data storage and computer interfaces. But it is small (18 lbs.), and so is the price.

30-Day Trial Offer

Discover for yourself how the 3091 can benefit you. Try one for 30 days. All we need is a purchase order. If the Oscilloscope doesn't suit your application, you may return it at no charge.

Nicolet

Nicolet Instruments Limited

Budbrooke Road Warwick CV34 5XH
Telephone (0926) 494111 Telex 311135

WW - 010 FOR FURTHER DETAILS

Designing with the 68008 microprocessor

Ideal for use in low-cost, high-volume applications like personal computers and small business machines, the 68008 is an eight-bit microprocessor with a 32-bit architecture.

This two-part article describes its main features and how it's used with other microcomputer components like rom, ram and peripheral devices.

All of the microprocessors in the M68000 family of high-performance processors and peripherals, including the 68008, are based on the same 32-bit architecture. The 68008 has an eight-bit external data bus; others have 16 or 32-bit buses. The once-clear divisions between eight, 16 and 32-bit microprocessors are becoming blurred; with the 68008 the designer is now able to have a high-performance microprocessor with a 32-bit architecture in small cost-effective systems using eight-bit data buses.

The architecture of the 68008 is identical to the original member of the family, the 68000, a processor with a 16-bit external data bus. From the programmer's point of view the two processors look identical, so that the 68008 is completely code-compatible with the 68000. This means that any program developed for one processor will run on the other. This is true for object code as well as source code. Other 68000-family microprocessors such as the 68010, virtual memory version of the 68000, and the 68020, very high performance 32-bit mpu, have architectures which are upward-compatible with that of the 68008, making it easier to upgrade 68008-based systems. For example, any user program written for the 68008 will execute correctly on the 68000, 68010 and 68020 without need for modification.

Using standard rams and roms a smaller minimum-sized system can be constructed with the 68008 than with the 68000. Cost savings are made by producing the 68008 in a 48-pin dual-in-line package as opposed to the 64-pin version for the 68000. Eight pins are saved by halving the reduced data bus. Other minor hardware differences allow more pins to be shed (Fig. 1), for instance a few of the high-order address lines of the 68000 are not brought off-chip on the 68008. Even so, this still allows direct addressing of over one megabyte of memory — huge compared to that of conventional eight-bit microprocessors and more than enough for the low-end applications for which the 68008 is intended.

The 68008 is as fast as the 68000 when

by A. J. Barth

accessing byte-sized operands. However, because of its byte-sized data bus the 68008 needs to access 16-bit words as two successive bytes. As a result, the overall throughput of the 68008 is less than that of the 68000. For the same processor clock and for a typical mix of instructions, the 68008's performance is about 60% of that of the 68000. This is still a lot of raw processing power and will meet a need for low-end applications.

Because the architectures of the 68000-family microprocessors are so similar, knowing the 68008 means knowing much about the other processors. The 68008 is characterized by its 'clean', regular and consistent structure and in particular, emphasis was given to the architecture to make it regular with respect to the registers, instructions, addressing modes and data types.

Register set

The 68008 programming model has a large number of general-purpose 32-bit data and address registers, Fig. 2. There are eight

general-purpose 32-bit data registers, D₀-D₇, for byte (8-bit), word (16-bit), and long word (32-bit) operations. Seven address registers A₀-A₆ and two system stack pointers A₇, may be used as software stack pointers and base address registers. In addition these registers may be used for word and long-word address operations. All 17 registers may be used as index registers.

High-performance microprocessors are expected to rapidly handle complex functions having a large number of parameters. The 68008 can maintain most or all of these parameters in processor registers, which is both fast and makes the programs efficient and elegant. Microprocessors with only a few registers in such situations need to continuously swap parameters between registers and external memory.

As the 68008 has general-purpose registers, the programmer and not the microprocessor-chip designer decides which registers are used. It does not dictate that certain instructions use certain registers. This not only eases the task of the assembler language programmer but also makes high-level language compiler-generated code more efficient. Many of the instructions and addressing modes which

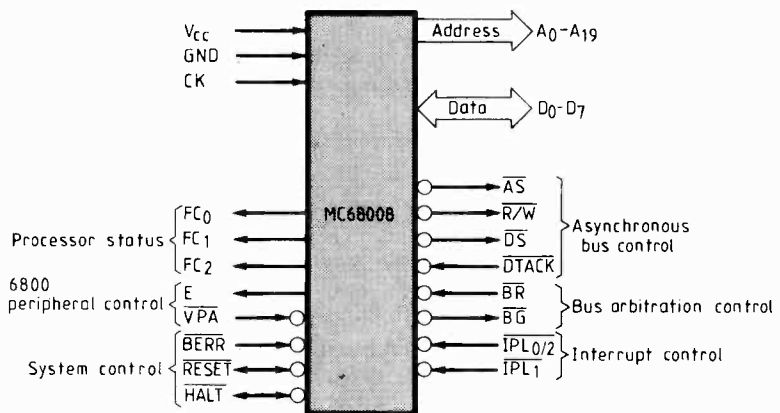


Fig. 1 68008 signal lines. The microprocessor has an internal 32-bit architecture and an eight-bit external data bus. Packaged in a 48-pin package the 68008 has non-multiplexed buses and a non-segmented 1 megabyte address space.

operate on the address registers may also be used with the 32-bit program counter. This makes it easy to write position-independent software that will execute correctly no matter where the code is loaded in memory.

The 68008 has a 16-bit status register which consists of two parts: a user byte and a system byte. The user byte is accessible by any program and contains the usual condition code flags associated with the execution of instructions, condition like Negative, Zero, Carry, Overflow, etc. The system byte of the status register is accessible only by a supervisory program (usually the operating system) and is used to control the operating mode.

Addressing range

The 68008 has a large linear addressing range. It can directly access one megabyte of external memory without paging or segmentation. Many microprocessors are able to access fairly large memory space but need to do so via a narrow window called a segment or page. This may be useful in a few applications, but in most situations it is an irritating handicap because the programmer is obliged to keep repositioning the window to access the desired location.

Like other Motorola microprocessors the 68008 has memory-mapped i/o. This enables the programmer to use the m.p.u's sophisticated instructions and addressing modes to operate on i/o as well as memory.

Instruction set

The 68008 has a powerful, flexible and easy-to-use instruction set. There are 56 basic instructions (Table 1). This is actually less than the ten-year-old 6800 microprocessor. However because of the regularity of the 68008 architecture, those instructions which use registers may use any register with almost any addressing mode and data type. These permutations yield many thousands of useful operations, compared to less than 100 for the 6800; the 68000 family philosophy being to provide a small number of easy-to-remember and flexible general-purpose instructions.

The instruction set covers the following classes of operations:

- data movement
- integer arithmetic
- logic
- shift and rotate
- bit manipulation
- binary-coded decimal
- high-level language support
- program control and
- system control.

Operations on data in registers and memory are independent of the data size and usually involve a source and a destination operand. The programmer need only remember one mnemonic for each type of operation and then specify data size and addressing modes for both the source and destination operands. Consistency is maintained as all data registers and memory locations may be a source or destination for most operations on integer data.

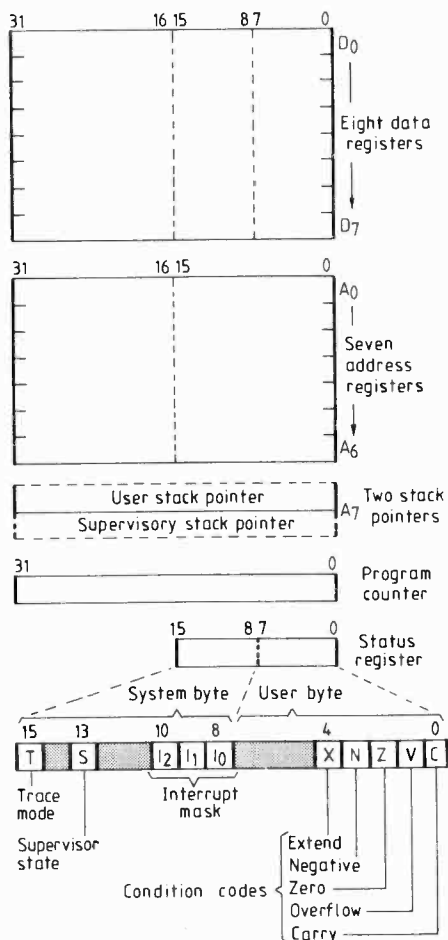


Fig. 2 68008 programming model: eight general-purpose data registers for 8, 16 and 32-bit operations, seven address registers, and two system stack pointers for software stack pointers and base address register. All 17 maybe used as index registers.

Like all M68000 microprocessors the 68008 instructions are implemented by microcode rather than random logic, so that, for example, the execution of undefined instructions no longer leads to unpredictable results.

Data types

The 68008 operates on five main data types. Operations may be on bits, b.c.d. digits, bytes, words and long-words. For integer arithmetic the programmer need not remember different instructions for different data sizes. The required data size is simply appended to the instruction as the program is written.

Addressing modes

An addressing mode is the method by which the data or other operand is accessed by the processor. The availability of powerful and flexible modes usually means performing an operation with just one instruction which would otherwise take many. This results in programs executing faster, being smaller, easier to read and to maintain. The 68008 has 14 powerful addressing modes (See Table 2). They operate consistently and are independent of the instruction itself.

Program privilege scheme

A two-level program privilege scheme


provides security and high reliability. Programs should access only their own code and data areas, and ought to be restricted from accessing the information which they do not need and must not modify. Such a scheme not only prevents the deliberate tampering with data but also guards against a faulty program running wild and altering other programs.

The 68008 operates at one of two privilege levels, the supervisor level or at the user level. At the supervisor level programs have access to all processor resources and can execute any instruction or access any register. Normally, only the controlling operating system or its kernel runs at this level. This code is normally relatively small, well-tested and therefore reliable. All the rest of the software, which includes both the utility and application programs, executes at the user level and has access only to a subset of the total processor unit resources, the resources governing control of the system being protected from these programs. If a user-level program attempts to execute a 'privileged' instruction or to access a supervisor register, control is immediately taken away and given to the controlling supervisor program which can take some corrective action.

Interrupt structure

In most applications, programs are seldom executed instruction-after-instruction without a break. The need frequently arises to respond to an event or exception. Such exceptions may be the hardware interrupts caused by external logic, or the software interrupts caused by the recognition of some condition internal to the processor unit. High-performance microprocessors must be able to respond rapidly to a large variety of exceptions with varying degrees of priority.

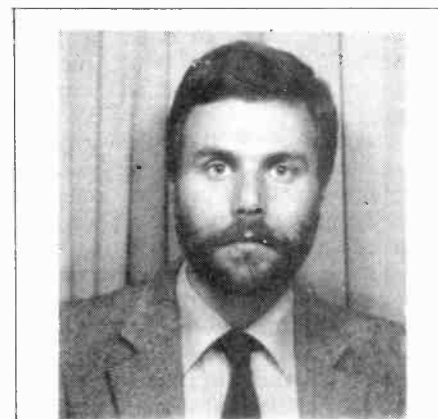Three levels of priority are provided for external hardware interrupts. By use of the three-bit interrupt mask in the 68008 status register (Fig. 2) the supervisor program may postpone handling external interrupts with priorities less than that contained in the mask. When an interrupt



Andrew Barth is a senior staff engineer with Motorola's systems engineering group in East Kilbride. He graduated in physics from Leeds University and since 1976 has worked in microprocessor systems design in Germany and the USA, as well as in the UK.

Table 1. 68008 instruction set

Mnemonic	Description
ADBC	add decimal with extend
ADD	add
AND	logical and
ASL	arithmetic shift left
ASR	arithmetic shift right
B _{CC}	branch conditionally
BCHQ	bit test and change
BCLR	bit test and clear
BRA	branch always
BSET	bit test and set
BSR	branch to subroutine
BTST	bit test
CHK	check register against bounds
CLR	clear operand
CMP	compare
DB _{CC}	test condition, decrement & branch
DIVS	signed divide
DIVU	unsigned divide
EOR	exclusive or
EXG	exchange registers
EXT	sign extend
JMP	jump
JSR	jump to subroutine
LEA	load to effective address
LINK	link stack
LSL	logical shift left
LSR	logical shift right
MOVE	move

is recognised the processor performs an interrupt acknowledgement sequence (IACK). During IACK the peripheral being acknowledged may indicate that program control should be given to any one of 256 interrupt service routines (vectored interrupt method), or to one of three service routines corresponding with the hardware interrupt priority level (autovector interrupt method). Most of the M68000-family peripherals use the vectored interrupt method in which the peripheral provides an eight-bit vector number on the data bus. The 68008 uses this vector number to determine which of the 256 interrupt routine addresses in its interrupt vector table to use. The less sophisticated peripherals use the autovector interrupt method which have seven vectors reserved for them. In either case the external hardware needed to interface both kinds of peripherals to the 68008 is minimal.

Some 68008 instructions are designed to cause internal interrupts, some always and others only upon detection of certain conditions. An example of the last is the execution of a 'privileged' instruction. If a supervisor-level program executes such an instruction, the instruction will execute normally and no exception will occur. However, if a user-level program attempts to execute it, a privilege violation exception occurs and program control is given immediately to the appropriate interrupt service routine.

A number of exceptions correspond to error conditions, either those detected by external hardware or by the processor itself. For example, the Bus Error input (BERR) may be used by external hardware to cause the 68008 to abandon the current bus cycle and give program control to the Bus Error interrupt routine, or, by the simultaneous use of BERR and HALT, to retry the current bus cycle.

A very useful feature is the trace exception, which enables a supervisor-level program to step through a target program on an instruction-by-instruction

Mnemonic	Description
MOVEM	move multiple registers
MOVEP	move peripheral data
MULS	signed multiply
MULU	unsigned multiply
NBCD	negate decimal with extend
NEG	negate
NOP	no operation
NOT	one's complement
OR	logical or
PEA	push effective address
RESET	reset external devices
ROL	rotate left without extend
ROR	rotate right without extend
ROXL	rotate left with extend
ROXR	rotate right with extend
RTE	return from exception
RTR	return and restore
RTS	return from subroutine
SBCD	subtract decimal with extend
S _{CC}	set conditional
STOP	stop
SUB	subtract
SWAP	swap data register halves
TAS	test and set operand
TRAP	trap
TRAPV	trap on overflow
TST	test
UNLK	unlink

basis. Each time the target program executes an instruction, no matter which instruction it may be, control is returned to the supervisory program. No external hardware is required to implement the program tracing as it is part of the processor architecture.

Asynchronous data bus

Like most of the other Motorola microprocessors, the 68008 data bus is not multiplexed – the m.p.u. pins used for the data bus are not shared with other signals. Some microprocessors multiplex the data and address buses onto the same pins to reduce the total number of pins. Non-multiplexed microprocessors such as the 68008 require more pins and sometimes a more expensive package. However, non-multiplexed buses have many advantages: they can operate much

faster, dissipate less chip power, and do not require external demultiplexing hardware. Analysis shows that multiplexed microprocessor systems are more costly than non-multiplexed systems because the microprocessor and demultiplexing i.c.s together cost more, occupy more board space and have more pins overall.

The 68008 has an asynchronous data bus. The time taken to transfer data to or from a memory or peripheral device via the data bus is variable. The memory or peripheral device signals the processor when it is ready to make the data transfer by use of a special handshake line called data transfer acknowledge (DTACK). The advantage of this asynchronous scheme is that each bus cycle can be fine-tuned to the speed of the particular device being accessed. If the device is rather slow, the processor simply marks time until the device is ready. In this way the 68008 runs at the fastest rate that memory and peripherals can go, which maximizes system throughput.

Most M68000-family peripherals have a pin for the DTACK handshake signal, and interfacing such parts to the 68008 microprocessor is simple. Even those peripherals originally designed to work with synchronous processors, like the 6800 or 6809 microprocessor units, may be interfaced to the 68008 with minimal hardware. This is because the 68008 has several signal pins specially for this purpose. By use of these signals, the M6800-type peripheral device signals the processor to perform the current bus cycle synchronously, making the 68008 behave like a synchronous microprocessor for this one bus cycle.

The 68008 m.p.u. uses a two-line bus arbitration scheme which enables the data bus to be shared efficiently with other microprocessors units in a multiprocessor system and with other bus masters such as d.m.a. controllers.

To be continued with interfacing details.

Table 2. 68008 addressing modes

Mode	Generation
Register direct addressing	
Data register direct	EA=D _n
Address register direct	EA=A _n
Absolute data addressing	
Absolute short	EA=(next word)
Absolute long	EA=(next two words)
Program counter relative addressing	
Relative with offset	EA=(PC)+d ₁₆
Relative with index and offset	EA=(PC)+(X _n)+d ₈
Register indirect addressing	
Register indirect	EA=(A _n)
Postincrement register indirect	EA=(A _n), A _n ←A _n +N
Predecrement register indirect	A _n ←A _n -N, EA=(A _n)
Register indirect with offset	EA=(A _n)+d ₁₆
Indexed register indirect with offset	EA=(A _n)+(X _n)+d ₈
Immediate data addressing	
Immediate	Data=next word(s)
Quick immediate	Inherent data
Implied addressing	
Implied register	EA=SR, USP, SP, PC

EA effective address
 A_n address register
 D_n data register
 X_n address or data register used as index register
 SR status register PC program counter
 d₈ eight-bit offset (displacement)
 d₁₆ sixteen-bit offset (displacement)
 N=1 for byte 2 for words and 4 for long words
 () contents of
 ← replaces

16-line p.a.b.x with options

Hints on construction complete Jaap Kuiper's description of a versatile electronic/electromechanical exchange

Current passing through the telephones has to be kept within acceptable limits. Having used 700Ω relays throughout the O relay requires a 470Ω, 1W series resistor (at 45V supply). As relays O, G, II, EI and R are all controlled from the individual stations they must switch positively. Typical values for limiting resistors turned out to be 390Ω, 1W for II, EI and R, and 1kΩ, 1W for G relays and others working off the 45V supply. Relays using the 12V rail don't need series resistors and so operate economically and reliably. The limiting resistor for G relays, if required fits between the G-bus and contacts gh₂/gi₂ in the external control section.

Most Continental telephones include a ground key but where not, momentary push-buttons may be fitted and connected directly to the set's a-line. The original switches, if available, may be fitted in the space provided on top of UK sets in front of the cradle. Holes for the leds have to be drilled or melted in a suitable position and are also connected directly to the a-line. Previous diagrams gave details for both Continental and UK sets.

Special mounting plates (RS Components RS349-119) are available for fitting Siemens/Varley type relays. Each plate holds six relays. Joining these plates together allows daisy-chain wiring of the bussed contacts. The mounting plates have each station's O, T and G relays grouped together for ease of wiring with ribbon cables running to the T-drivers. Terminator, oscillators and line interface were constructed on home-made p.c.bs and 30-way connectors were used to plug in the various telephones.

Resistors in the ground-key toggle have to be approximately the same value as the relay coil and must be capable of dissipating the full power during switching (1kΩ, 5W). The muting i.c. is an LM311 which is rated at 36V maximum, so a voltage divider was included to reduce the supply. These are resistors ra and rb. The reference point is connected through a 1MΩ

resistor so as not to affect proper operation of EI which has to follow dial pulses. At 700Ω EI coil value and a telephone presenting 300Ω when operating, the reference voltage will be approximately 31.5V. Therefore divider rc/rd has to be adjusted to provide around 35V. As soon as the dial is moved the reference point goes to the full supply voltage; the 1MΩ resistor protects the i.c. The LM311 will switch up


by J. H. Kuiper

to 40V so the additional transistor was included for protection.

With the introduction of more and more d.t.m.f. (system X) exchanges it is sensible to construct the line interface on a separate p.c.b. so that when change-over is required only the line interface needs replacing. A dual tone circuit (Exar application note AN-08) then feeds the 4514 latch. Wiring to the individual sets is by standard four-core cable as each station's b and




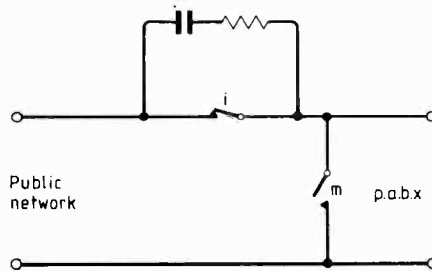Born in Friesland in 1949 and having lived in Holland since 1960, Jaap Kuiper completed his study of electrical engineering and electronics at Alkmaar Polytechnic in 1970 after which he worked as a buyer re-exporting equipment to Indonesia and Singapore. Since 1977 he has run a small import/wholesale business specialising in audio accessories and computer peripherals.



Automatic dialling by computer requires two buffered output ports each driving a relay. Additional hardware requirements are minimal as shown here.

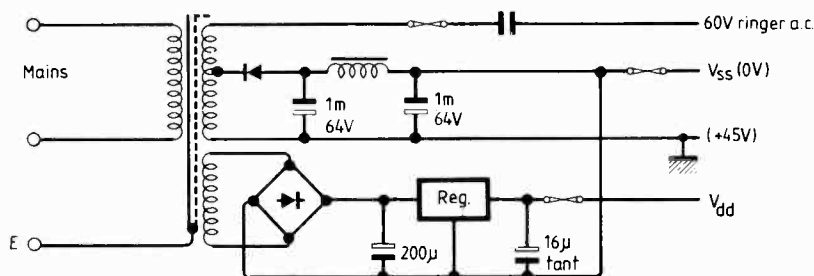Power supply diagram. Current of the 33V secondary producing 45V direct is 1.5A. Using higher impedance coils will reduce this. Current from the 9V secondary is 100mA; a 12V regulator is used on this supply. The 1μF, 250V ringer-line capacitor is not needed for UK sets.



ground-key wire have to be discrete throughout. This largely applies to the a-wire as well to avoid speech induction to unwanted sets. Led-lines may, however, be joined together at convenient places to reduce the number of leads.

The line isolating and matching transformer is available from RS Components (RS217-826). The RC shunt across the interruptor contact consists of a 1μF, 250V capacitor and a 560Ω, 1W resistor on the Continent and 2μF, 250V and 600Ω, 1W in the UK. In view of interface requirements relays EI and M should be new types as they must have a contact bounce of less than 4ms and contact resistance of less than 200mΩ. All other relays may be surplus types. Diodes are general-purpose high-speed silicon types. Many diodes used combine or separate switching actions to reduce the number of relay contacts; these are rated at 100mA (BA155). Diodes used in the oscillator circuits and sections working at 12V may be rated lower.

Note that in stations not requiring the muting-inhibit action the g₄ contact becomes redundant. Since relays usually come with two or four contacts, a component can be reduced by omitting the diode between contact t₂ and the G coil and connecting spare contact g₄ directly from t₂ to ground (marked with asterisk on page 63 of November issue).



NEW PRODUCTS



WW 305

Micro-floppy

Following other Japanese manufacturers, Teac have announced the availability of FD-30A, a 3in floppy disc drive that has all the same characteristics as their 5.25in drives; capacity, format, density, disc rotation speed, transfer rate and power and data interface connections are all identical. This makes it fully compatible and a direct replacement for its larger cousin. With a brushless d.c. direct-drive motor, the drive is claimed to be very durable and electrical noise is eliminated. Available in the UK through Tekdata Electronics, Federation Road, Burslem, Stoke-on-Trent ST6 4HY. WW 305

Transistor tester

An addition to their range of hand-held test units is the Osgorne 4500 transistor tester. Completely self-contained, it can be used easily to check p-n junctions of discrete semiconductors whether in or out of circuit. It features a series of leds which indicate the junction status; p-n-p or n-p-n, open or short circuit can be instantly identified and it will work reliably even when parallel circuits have values approaching 270 ohms or 33 microfarads. Osborne Electronics, Binstead Road, Ryde, Isle-of-Wight. WW 306

Voice digitizer

A voice digitizer may be used to enable the transmission of voice and data down the same telephone line. An American model, the Switchco TSP series 1000 works at a very low data rate of 2400bit/s which makes it easy to use with data modems or, by using a multi-

port modem it can transmit four voice conversations over the same line. It is distributed by Vanderhoff Communications Ltd, Haunchwood Estate, Bermuda Road, Nuneaton, Warwicks CV10 7QF. WW 307

Conduct heat — not current

Another American product is a thermally-conductive dry filled silicone rubber that provides 2000V isolation between power semiconductors and heat sinks. The low-cost Aarvid Rubber-Duc pads are vulcanised onto the heatsinks in the factory and eliminate mica washers and grease or silicone rubber pads and adhesives, while offering better thermal conductivity than either. Configurations suitable for TO-3, TO-66 and plastic power devices as well as DO-4 and DO-5 diode washers. Warth International Ltd, Oxted, Surrey. WW 308

Shaft cutter

The cutting of shafts on potentiometers, rotary switches and variable capacitors has been made much easier by the introduction of the Telpro shaft shear. This guillotine-type tool will cut copper, aluminium, mild and stainless steel, and plastics rods of diameters up to 0.25in or 6mm. It does not transmit any shock or vibration and may be used on such delicate components as helical trimmers, providing a clean cut


with no need for further filing or finishing. It is claimed that the tool will pay for itself by cutting as few as half-a-dozen shafts because of the reduction in time and damage to components. Electronic and Computer Workshop Ltd., 171 Broomfield Road, Chelmsford, Essex CM1 1RY. WW 309

Laser for communication

A new high-frequency GaAlAs diode laser with a modulation bandwidth of 6GHz is mounted in an impedance matched high frequency module which includes an integral power-monitoring photodiode for the automatic control of carrier wave output power. The laser diode can be used for the transmission of analogue or digital signals from d.c. up to microwave frequencies over long or short optical links. For a complete high-speed link, there is a matching photodiode with a 7GHz detection bandwidth. The small size, light weight and very low power consumption of the laser make it suitable for airborne or remotely powered system use. Typical applications include multi-channel communications, phased array antennae, or radar signal transmission. Walmore Electronics Ltd, 11 Betterton Street, London WC2H 9BS. WW 310

Polyester capacitors

An alternative to the multi-layered ceramic capacitor in decoupling application is offered by the Suflex range of metallized polyester capacitors. The SUF168 is a sub-miniature device that allows for high packing density and is printed on the top to allow identification of values when closely mounted. Values range from 1000pF to 1 μ F with ratings of 50, 60 and 100V d.c. Suflex Ltd, Risca, Newport, Gwent NP1 6YD. WW 311

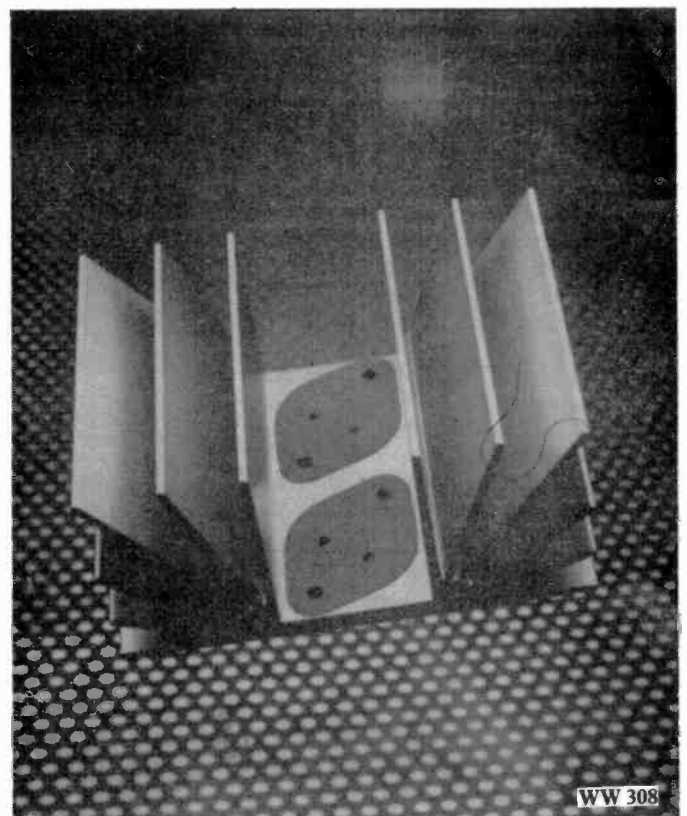

WW 308

Sinclair goes into business

No modesty has been exercised by Sinclair Research in the naming of their latest computer which they have called the QL for Quantum Leap. It certainly is a leap into an entirely different world from that occupied by the ZX81 or the Spectrum. The QL is being promoted as a purely business machine and is provided with four business-oriented software packages; a word processor, a database, a spreadsheet and a graphics program for the production of graphs and charts.

The computer is based on Motorola MC68000 processor which Sinclair claim is a 32-bit processor. The 68000 has 32-bit internal architecture but uses 16-bits externally and the 68008 version used in the QL has an 8-bit data bus. So it's really an 8/16/32-bit processor depending from where you look at it. A second processor, Intel 8049, is used to control the keyboard, generate the sound and act as an RS232C receiver. QL has 128K of ram and there will be a 0.5Mbyte plug-in ram module as an optional extra. Program storage is on Sinclair Microdrive, a tape cartridge medium with 100Kbytes of storage on each of the two built-in drives. There is an expansion slot for up to six further drives.

Sinclair have designed their own operating system, called QDOS, although no discs are involved. QDOS is a single user, multi-tasking system which has the ability to run several programmes concurrently and to display the result simultaneously in different windows on the screen. The operating system uses a new version of Sinclair Basic, called SuperBasic, which is claimed to be so superior to 'normal' Basic as to constitute a different language. It has the ability to define procedures written in individual blocks. A 'constant execution speed' is claimed, that does not get slower if a program is longer.

The computer has a full typewriter-pitch keyboard with 'real' keys, 65 of them, including cursor-control keys and five programmable function keys.

The display facilities are from a wide choice of character sets with a normal format of 84 columns by 25 lines. Two modes of high-resolution graphics are offered; 512 by 256 pixels with four-colour (red, green, black and white) display, and 256 by 256 with an eight-colour display. A 'stipple' command allows the mixing of foreground and background colours to add to the palette. In both modes a varying grey scale is produced on a monochrome monitor. The quality



WW 301

of the display is such that a high-resolution monitor is necessary to take full advantage of the system. Much would be lost by using a tv receiver even though a tv modulated output is provided.

A number of interfaces are built in; two RS232C interfaces, two analogue joystick ports, a rom-cartridge slot, a u.h.f modulated tv output as well as an RGB monitor output. There is a general-purpose expansion slot which may be used to plug in a ram module, or other peripherals as they become available. There are also two local area network ports and up to 64QLs and/or ZX Spectrums may be daisy-chained together sharing such facilities as a printer or a data base. Data may be transmitted along the QLAN at 100K baud and there is a handshake protocol to ensure that a receiver station is 'listening'.

The QL is due to be issued to customers toward the end of February. As is usual with Sinclair new products, it will be available on mail-order only and may appear in retail shop after about six months. There is a £7.95 charge for postage and packing and users are invited to join a users' group or QLUB, for an additional £35 a year. Members will get software up-dates and news of all additions.

Planned enhancements already under development include a C compiler, 6800 assembler, emulation of a main-frame terminal, a-to-d converter, a hard disc interface, a modem, a parallel printer interface, and an IEEE-488 interface.

Sinclair Research Ltd, Computer Division, Stanhope Road, Camberley, Surrey GU15 3PS.

WW 301

Wren for £1,000

Designed by Transam for Prism Business Systems, the Wren computer is based around a Z80B processor running at 6MHz. It has 64K or ram expandable to 256K, with a diagnostics rom of 8K. A real-time clock is included as is a 50byte c.mos ram, both with battery back-up. It includes a 7in monochrome amber display c.r.t with 36K of screen memory, three selectable screen formats; 80 columns by 24 lines, 40 columns by 24 lines Prestel format, or 512 by 256 elements high-resolution graphics. Although the internal display is monochrome, full colour graphics are supported and there is an RGB output to a colour monitor. The keyboard, which is not detachable, has 67 full size qwerty keys with separate cursor keys and five function keys which allow up to 15 different programmable operations. Two 5.25in disc drives are included with 200Kbyte storage for each drive.

There are a number of interfaces; an RS232 serial port, a Centronics parallel printer port, two analogue inputs for paddle cursor controls, a hard disc interface, and a built in autodial modem which is Prestel and CCITT compatible. Software may be downloaded from Micronet 800 through the inbuilt download facility. For transport, the screen and disc drives in the upper section slide forward over the keyboard, revealing a sturdy carrying handle at the back, it weighs "under 20 lb" (9kg).

The software includes a Z80 version of BBC Basic, a desk-top facility which includes a diary, an address file, a system for creating simple documents such as memos, or expense forms, a filing system, a calculator and it may be used in conjunction with a printer as a typewriter. Perfect Writer, Perfect Calc and Perfect Filer are included along with CP/M 3. Prism Business Systems Ltd, 18 Mora Street, London EC1V 8BT. WW 302



WW 302

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical uses, etc.
Approx 16 joules. Adjustable speed. Price £45 + £2 p&p (Total inc. VAT £54.05). Case and reflector price £15 + £2 p&p (total incl. VAT £19.55). Footscap SAE for further details including Hy-Light and Industrial Strobe Kits

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £8.70 + VAT (Callers only)
2ft 20 watt £6.20 + £1.25 p&p (£8.57 inc. VAT)
18in. 15 watt £3.50 + 75p p&p (£4.88 inc. VAT)
13in. 10 watt £3.25 + 75p p&p (£4.50 inc. VAT)
12in. 8 watt £3.00 + 45p p&p (£3.97 inc. VAT)
9in. 5 watt £2.50 + 45p p&p (£3.39 inc. VAT)
6in. 4 watt £2.50 + 45p p&p (£3.39 inc. VAT)



230V AC Ballast Kit for either 6in., 9in. or 12in. tubes £5.50 p&p 55p (£6.96 inc. VAT)
For 13in. & 18in. Tubes £6 p&p 75p (£7.76 inc. VAT)
For 12V DC op. 12in. & 13in. tubes only £5.50 p&p 75p (£7.18 inc. VAT)

175 WATT SELF-BALLASTED MERCURY BULBS Available for either B C or E S fitting price £11.79 inc. p&p and VAT

400W UV LAMP AND BALLAST complete £38 post £3.50 (£47.73 inc. VAT & p&p) **400W UV LAMP only** £14 post £2 (£18.40 inc. VAT & p&p)

2KV VOLTAGE CHANGING TRANSFORMER. Auto wound with taps 0.5-100 125-150-175-190-200-225-230-240-250 Volt Price £22 + £4 p&p (total incl. VAT £29.90) N.M.S.

Comprehensive range of TRANSFORMERS LT ISOLATION & AUTO (110-240V). Either cased with American socket and mains lead or open frame type available for immediate delivery. Leaflet on request

12V DC SOLENOIDS
Approx 1lb pull £1.50 40p p&p (£2.18 inc. VAT) N.M.S.
Approx 2lb pull £2.50 50p p&p (£3.45 inc. VAT) N.M.S.

240V AC SOLENOID
Approx 6lb pull £4.75p p&p (£5.46 inc. VAT) N.M.S.

HEAVY DUTY SOLENOID, mf. by Magne-tic Devices. 240V A.C. intermittent operation. Approx 20lb pull at 1.25 in. Ex equipt. Tested Price £7.50 p&p £1.50 (£9.05 incl. VAT). R & T



VORTEX BLOWER & SUCTION UNIT
Powerful multi stage dynamically balanced, totally enclosed 9 dia. Rotators. 3,500 rpm 1/2" ID inlet and outlet, 110V A.C. Price £20 Suitable transformer for 240V A.C. £5 + £3 p&p (total incl. VAT £32.20) N.M.S.

Quiet smooth running COOLING or EXTRAC-TOR FAN. Size 4 3/4x4 3/4x1 1/2. Supplied for 240V a.c. operation Price £4.75 + £1 p&p (total incl. VAT £6.62) N.M.S.



240V A.C. SOLENOID VALVE
Designed for Air/Gas at 0.7 Water 5 psi Inlet/outlet 3/8" Forged brass body. Manul. Dewraswitch Asco. Price £5.50 + £1 p&p (£7.48 inc. VAT) N.M.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230, 240V a.c. 50/60 OUTPUT 0-260V.
200W 1A. Max. £15.00
0.5KVA 2A Max. £19.00
1KVA 5A Max. £27.00
2KVA 10A Max. £41.00
3KVA 15A Max. £54.00
5KVA 25A Max. £95.00
10KVA 50A Max. £181.00
15KVA 75A Max. £275.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS
Dual Input 200-240V or 380-415V. Star connected
3KVA 5amp per phase max £113.40
6KVA 10amp per phase max £170.10
10KVA 16amp per phase max £275.45

All V.V.Ts plus carriage and VAT

12V D.C. BILGE PUMPS
700 G.P.H. 10ft head, 3.5amp. £7.50 + £1.50 p&p (£10.35 inc. VAT)
1750 G.P.H. 15ft head, 9amp. £14 + £1.75 p&p (£18.11 inc. VAT)



SINGLE DIAPHRAGM COMPRESSOR
Max 20 PSI. One CFM approx. 240 volts A.C. £18 + £2 p&p (£23 inc. VAT)

EPROM ERASURE KIT

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case to include 12.8 watt 2537 Argon Tube. Ballast unit pair of bi-pin leads, Neon indicator, safety microswitch, on/off switch and circuit.
LESS CASE Price £13.60 + 75p p&p (Total incl. VAT £16.50)
Warning: Tube used in this circuit is highly dangerous to the eyes. Unit must be fitted in suitable case

FROM STOCK AT PRICES THAT DEFY COMPETITION!

- AC GEARED MOTORS
- DC MOTORS
- MICROSWITCHES
- RELAYS
- REED SWITCHES
- SOLENOIDS A.C. or D.C.
- PROGRAMME TIMERS
- C.F. BLOWERS
- AC CAPACITORS
- STROBE KITS
- FLASHTUBES
- CONTACTORS
- SYNCHRONOUS MOTORS

Phone in your enquiries

Stockists for Finnings Hammerite paint and Waxoyl products. Good normally despatched within 7 days.

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, heavy duty brush assembly, continuously rated.
25 WATT 5/10/25/50/100/150/250/300/500/1K Ω
1.5k Ω £3.80 + 30p p&p (£4.71 inc. VAT)
50 WATT £7.20 (£8.50 p&p £9.90 inc. VAT)
100 WATT 1/5/10/25/50/100/250/500/1K Ω 1.5k Ω £12.5k (£13.5k Ω)
£7.75 + 75p p&p (£8.77 inc. VAT)
Black Silver Skirted Knob calibrated in Nos 1-9, 1 1/2 in. dia. brass bush. Ideal for above Rheostats 30p ea. + VAT.

WHY PAY MORE?

MULTI RANGE METER. Type MF15A, a.c. d.c. volts 10, 50, 250, 500, 1000. Ma 0.5-0.10 0-100 Sensitivity 2000V. 24 range diameter 133 by 93 by 46mm including test leads Price £10.35 inc. VAT & p&p



INSULATED TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work constant speed clutch. Size L 8in. W 4in. H 6in. weight 6lb. 500V, 300 megohms. £49.9 p&p £2 (£53.65 incl. VAT) 1000V 1000M Ω £55.9 p&p £2 (£65.55 incl. VAT) SAE for leaflet




GEARED MOTORS

5 rpm 240V A.C. MI by Carter. £6.05 £1 p&p (£8.11 inc. VAT) N.M.S.
38.3 rpm GEARED MOTOR. Torque 35lb in reversible 115V AC inc. start capacity. Price £11.55 + p&p (total incl. VAT £15.58) N.M.S.
Suitable TRANSFORMER 230V A.C. operation. Price £4.50 + 50p p&p (total incl. VAT £5.75)

CROWN 37 rpm 200lb in. approx. 110V AC, reversible geared motor. Price £35 p&p £1.50 (£36.50 inc. VAT) N.M.S.
Suitable transformer for above £10 p&p £1.50 (£13.22 inc. VAT)
CROWN 42 rpm 110/230V A.C. 50 Hz, 100 lb.in. approx. Reversible geared Motor. Price £18.15 + £2.50 p&p (total incl. VAT £23.75)

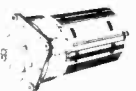120 RPM 1/10 HP APPROX. 15 lb.in. 230V A.C. Cont. Rating Non-reversible. Size 150mm x 90mm x 85mm spindle 8mm dia x 30mm long. Complete with capacitor and relay for max load starting. Offered at mere fraction of mfrs price - £11.50 inc. p&p & VAT. N.M.S.



CHECK METER

200-240V A.C. 50amp, fully reconditioned. £7.50 + £1.75 p&p (total incl. VAT £10.64)

SANGAMO WESTON TIME SWITCH
Type S251 200/250 A.C. 2 on/2 off every 24 hours. 20 amps contacts with override switch. Diameter 4 x 3. Price £9.50 + £1.50 p&p (£12.65 inc. VAT) & p&p. Also available with solar dia R&T. Other types available from stock

N.M.S. New Manufacturers' Surplus R&T Reconditioned and tested

Ample parking space
Showroom open
Monday-Friday




SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB. 01-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only Open Saturdays
9 Little Newport Street
London WC2H 7JJ
Tel: 01-437 0576

WW - 077 FOR FURTHER DETAILS

CHUM ONE Industrial Computer

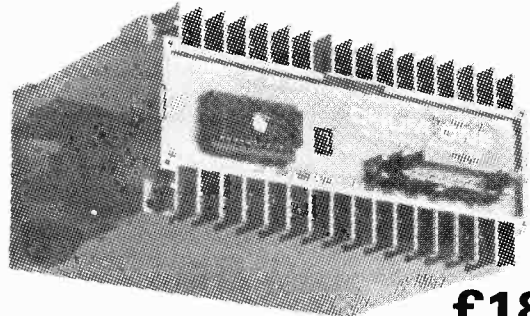

£189

- ★ BASIC, Z80 Assembler and PLC Language
- ★ Detachable Hand-held Keyboard and Display
- ★ 8K Bytes of non-volatile Memory
- ★ Eight Analogue Inputs
- ★ One Analogue Output
- ★ Up to 512 Optical Coupled Inputs/Outputs
- ★ Four Programmable Frequency/Timers
- ★ RS 232 Serial Input/Output Port
- ★ Cassette Back-up Memory
- ★ Real Time Clock

Simply by changing the EPROM in the top socket a Chum One can be used for such functions as:

- Machine Control
- Temperature Control
- Computer Outstations
- Data Logging
- Weighing Machine
- Programmable Timer

WARWICK DESIGN GROUP, 12 ST. GEORGE'S ROAD LEAMINGTON SPA CV31 3AY (0926) 34311

WW - 074 FOR FURTHER DETAILS

COMMERCIAL CONTINENTAL/CRADLE RELAYS

Medium-duty miniature plug-in relays, fully interchangeable with other British and Continental types, gold flashed silver contacts.

TYPE 24A02C18A. 2-pole changeover rated at 1 amp with a coil resistance of 430ohm, nominal voltage 12V DC, approx. dimensions, length 24mm, width 19mm, height 30mm. Price £15 for 10, £135 for 100, £615 for 500. Sample sent for £2 + 35p P&P (£2.10 inc. VAT).

TYPE 25A04C18A. 4-pole changeover relay rated at 1 amp with a coil resistance of 430R, nominal voltage 12V DC, approx. dimensions, length 24mm, width 19mm, height 30mm. Price £17.50 for 10, £158 for 100, £711 for 500. Sample sent for £2.15 + 35p P&P (£2.82 inc. VAT).

TYPE 25A04C20A. 4-pole changeover rated at 1 amp with a coil resistance of 700R, nominal voltage 24V DC, approx. dimensions, length 24mm, width 19mm, height 30mm. Price £18 for 10, £160 for 100, £720 for 500. Sample sent for £2.25 + 35p P&P (£2.99 inc. VAT).

CONTINENTAL/CRADLE SERIES SOCKET

TYPE FR10. Cradle including clip manufactured for Type 24 relay listed above PCB mounting. Price £5 for 10, £22 for 50, £40 for 100, £180 for 500, £325 for 1,000. Sample sent for 75p + 25p P&P (£1.15 inc. VAT).

TYPE FR16. Cradle including clip manufactured for Type 25 relay as listed above, PCB mounting. Price £6 for 10, £27 for 50, £49 for 100, £220 for 500. Sample sent for 75p + 25p P&P (£1.15 inc. VAT).

METAL FILM RESISTOR TYPE FZ4

Manufactured by C.G.S., semi-precision with a standard tolerance of ±2% and a temperature coefficient of better than 100 PPM/°C. We have a full range in stock from 100R to 1MΩ. All bandoleried. £2.50 per 1,000 any one value.

WIRE WOUND RESISTORS

Manufactured by E.R.G., Type 16 ES with a standard tolerance ±5% of nominal resistance value. All values in stock.

3 WATT SERIES. £3.50 per 100 any one value + £1 P&P (£4.83 inc. VAT).
6 WATT SERIES. £6.50 per 100 any one value + £1 P&P (£8.63 inc. VAT).
10 WATT SERIES. £10.50 per 100 any one value + £1 P&P (£13.23 inc. VAT).

POLARISED ALUMINIUM ELECTROLYTIC CAPACITOR

Designed for application in power supply filters and similar applications in instrumentation radio communications and industrial control equipment, rated at 22,000µF 16V with a capacitance tolerance of +10% +50% and a temperature range of -40°C +95°C IECF (100Hz), 13 BA (50°C), solder tags dia. width 40mm, height inc. tags 30mm. 50 sent for £45 + VAT, 100 sent for £75 + VAT, 500 sent for £250 + VAT. Sample sent for £1.25 + £1 P&P (£2.58 inc. VAT).

HUNTS THERMILIN CAPACITOR

List No. 2528 EDA, rated at 2µF 440V AC cont. and a temp. range of -30°C to +70°C. Approx. diameter length 118mm, width 44mm, width including attachment plate 75mm, lead length 195mm. 50 sent for £92.50 + VAT, 100 sent for £150 + VAT, 500 sent for £500 + VAT. Sample sent for £2 + £1 P&P (£3.45 inc. VAT).

WIMA MKS METALLISED POLYESTER CAPACITORS

With an epoxy resin moulding, temp range -55°C + 100°C. Capacitance temp. co-efficient non linear curve 30 PPM per degree C within +20°C to -40°C. AC voltage rating for frequencies greater than 50Hz de-rating is necessary. Divide peak AC voltage by 1.4 for RMS rating assuming sinusoidal waveform climatic category 55/100/21.

CAP	VOLTS	%	
0.01 µF	100V		100 sent for £4.80 + £1 P&P (£6.67 inc. VAT)
0.068µF	100V		100 sent for £5.60 + £1 P&P (£7.59 inc. VAT)
0.1 µF	100V	5%	100 sent for £6.00 + £1 P&P (£8.05 inc. VAT)
0.33 µF	100V		100 sent for £8.20 + £1 P&P (£10.58 inc. VAT)
0.47 µF	100V		100 sent for £10.00 + £1 P&P (£12.65 inc. VAT)
0.68 µF	100V	10%	100 sent for £12.00 + £1 P&P (£14.95 inc. VAT)
0.068µF	250V	5%	100 sent for £5.50 + £1 P&P (£7.48 inc. VAT)
0.11 µF	250V		100 sent for £5.50 + £1 P&P (£7.48 inc. VAT)
0.47 µF	250V		100 sent for £12.00 + £1 P&P (£14.95 inc. VAT)
0.22 µF	400V		100 sent for £11.50 + £1 P&P (£14.38 inc. VAT)

Many other values in stock. Also full range of Seatronics, Electrolytics and Polyester in stock.
BERG low profile 14 pin dual in line IC socket manufactured from glass-filled polyester to UL94V-0. £7 for 100, £31 for 500, £56 for 1,000, £256 for 5,000, £460 for 10,000, £2,100 for 50,000, £3,700 for 100,000. Sample 10 sent for £1.20 + 30p P&P (£1.37 inc. VAT)

ELECTRONIC EQUIPMENT Co.

SPRINGFIELD HOUSE
TYSSON STREET, LONDON, E 8
TELEPHONE: 01-249 5217
TELEX: 9853906 EECO.G

WW - 082 FOR FURTHER INFORMATION

TELEDIGITAL COMPUTER



Sales Office:

42 Gorst Road, Park Royal
London NW10 6LD, UK
Telephone: 01-965 0627 Telex: 24708
and Telephone: Esher 67282

Member of the **PCML** Group

COMPARE OUR PRICES



COME TO US LAST!!!

CDC DISKETTES AT CRAZY PRICES!

Code	Type	Price
TD1	5 1/4" 40 TRK single sided	£1.95
TD2	5 1/4" 40 TRK double sided	£2.40
TD3	5 1/4" 80 TRK single sided	£2.86
TD4	5 1/4" 80 TRK double sided	£3.50
TD5	8" 40 TRK SS-SD	£2.20
TD6	8" 40 TRK SS-DD	£3.05
TD7	8" 40 TRK DS-SD	£3.05
TD8	8" 40 TRK DS-DD	£3.05

10 per box. Prices per diskette quoted. Discounts for quantity
ADD 15% VAT + £1.50 P&P

LARGE RANGES OF LISTING PAPER AND RIBBONS AT GREAT PRICES

Code	Type	Price
TD9	11" x 8 1/2" 60 GSM Plain	per 1000 £3.75
TD10	11" x 9 1/2" 60 GSM Perf'd Margins	per 1000 £3.95
TD11	11" x 14 1/2" 70 GSM Music Ruled	per 1000 £5.95
TD12	11" x 450mm 60 GSM Music Ruled	per 1000 £5.95
RIBBONS:	10 off EPSON FX-80	£49.95
	10 off EPSON FX-100	£42.50

(Refill for metal cartridges)
ADD 15% VAT + £1.50 CARR. PER ITEM (PAPER)
OR BOX OF 10 RIBBONS.

MANY MORE AVAILABLE - PHONE FOR DETAILS NOW!
01-965 0627

ECONOMICAL DRIVE POWER

Very powerful and versatile, from Rade Systems the R150 multiprocessor SBC **£385!** (ex. VAT + carr). Amazing spec. Look what you get: Z80A at 4MHz with 64K RAM 5 1/4" 8" disk controller, Z80A CTC, Z80A DMA, Z80A P10, memory mapped VDU uses M6845 CRTX 25x80 char display, you can use all the TD8 option cards to build your own powerful system, or build your own TD8! Suitable power supply **£95**. Keyboard from **£85**. Cased Video Monitors from **£95**. Supplied with full technical documentation. Demand for this excellent machine is high! Order now! Power requirements: +5V @ 1.5A, +12V @ 25A. -12V required for RS232 option - available on our standard PSU. Uncased drives also available with/without PSU.



EXCLUSIVE OF VAT & CARRIAGE

DON'T WASTE MONEY! ON OTHER COMPUTERS: COMPARE THE TD8 WITH OTHERS - COME TO US LAST!!

FROM **£995**
(ex. VAT and monitor)
PHILIPS 12" VDU 25x80 char display



£149

TD8 SYSTEM PROC SSOR

Dual Serial Ports



TD8 Keyboard

For dual 250KB disk system with 25x80 char. VDU, 93-key keyboard, user definable char. set, 128KB RAM (no upper limit to expansion, due to our unique bus structure. This also allows CPUs to be mixed). 4KB ROM with M/C monitor, bootstrap, dual RS232 ports to 19.2K baud, software controlled. Unique 'stackable' option modules allow easy and cheap expansion of your system - the first rational development from S-100 bus based machines!

CHOOSE YOUR SOFTWARE FIRST THEN
COMPARE OUR HARDWARE...



CP/M80 **£139**. CP/M86 **£225**. 8086/7 with 128KB **£495** extra gives you THE most powerful machine in its class. You could spend £6,000 for a machine of this specification.
Other options include: 64KB RAM expansion **£135**. 192KB RAM **£249**. IEEE488 **£97.50**. Sync comms **£78**. Dual Parallel Ports **£59**. Dual RS232 **£59**. 68000 CPU **£TBA**. 16032 CPU **£TBA**. A to D and D to A converters, high res. graphics, floppy and hard disk controllers and drives, tracker ball, real-time clock/calendar with BBU and more on the way!

PHONE TO ARRANGE DEMO
01-965 0627
24 HOURS - SEVEN DAYS

Complete TD8 system (as illust.) with Keystar, Epson RX-80, disk filling box, CPM 2.2 and WordStar, VDU and keyboard

ONLY **£1895!**

OR with HR15 Daisy Wheel - **£1995**

EXCLUSIVE OF VAT & CARRIAGE

NEW!

PERSONAL TYPE SETTING

For use with your CP/M 80, CP/M 86, MS-DOS, and most other systems.

Provide you with the ability to produce customised letter heads, invoices, delivery notes, price lists.

Do you own printing on your EPSON or compatible printer. No modifications to hardware. PRICE includes comprehensive MANUAL and MASTER DISK.

Call us now to receive some sample output of...


FANCY FONT™
your personal typesetter

£150 exc. VAT & CARR.

INCREDIBLE!

A high quality daisy wheel printer with RS232 interface, 3KB character buffer, and a host of other features like full WordStar function support dual colour (red/black) printing

ONLY **£395**

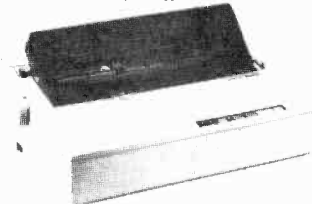

FREE DATA CABLE WITH EVERY BROTHER HR15!
Use this printer with the low-cost TD8 micro for the ultimate in low-cost WP systems

DATA CABLES

Made to your specification
Off shelf from **£12**
Exclusive of VAT & CARR.

The most

ECONOMICAL VIDEO MONITOR


you can buy...

PHILIPS 12" 25 x 80 character, green phosphor anti-glare screen, attractive case

ONLY **£69.95**

Exclusive VAT & CARR.

CASED DRIVES WITH PSU

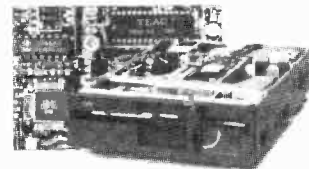

BBC COMPATIBLE SINGLE DISK DRIVES

TD 100 5 1/4" x SS 40TK 100K	£181
TD 200 5 1/4" x SS 80TK 200K	£223
TD 400 5 1/4" x DS 80TK 400K	£248

BBC COMPATIBLE DUAL DISK DRIVES

TD 200 2 x 5 1/4" SS 40TK 208K	£339
TD 400 2 x 5 1/4" SS 80TK 40K	£379
TD 800 2 x 5 1/4" DS 80TK 800K	£451

BBC COMPATIBLE DUAL SWITCHABLE DISK DRIVES


TD 400S 2 x 5 1/4" SS 80TK 400K	£457
TD 800S 2 x 5 1/4" DS 80TK 800K	£510

The drives include connecting cables, user manual, disk formatter ex of VAT & CARR.

WW - 079 FOR FURTHER DETAILS

Vigilant **micon** HF Communications Receivers MICROPROCESSOR CONTROLLED RECEIVERS

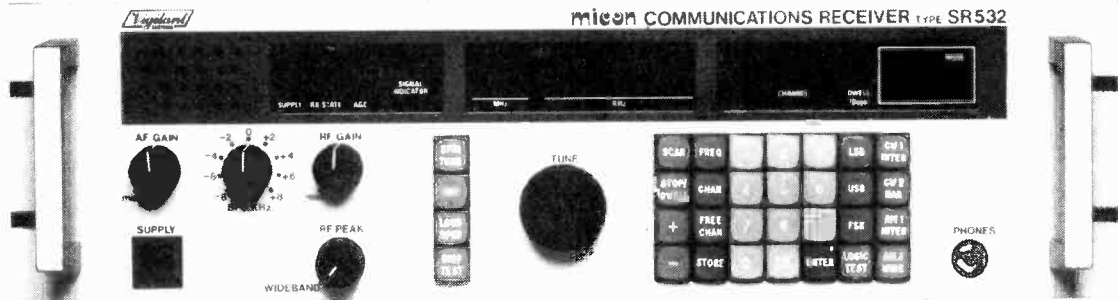Type SR 530 USB/CW/AM/Telex – 10 Hz Steps (Marine)
Type SR 532 USB/LSB/AM/CW – 10 Hz Steps (Static/Transportable)
Type SR 531 USB/LSB/AM/CW – 100 Hz Steps (Static/Transportable)



DESIGNED AND MANUFACTURED TO HIGHEST INTERNATIONAL SPECS

Freq. Range : 50 KHz to 30 MHz
Increments : 10 Hz or 100 Hz Steps
Stability : ± 1 Part in $10^7/^\circ\text{C}$
Tuning : Keypad and Spin Wheel
Power Supplies : 110/240V AC and 24V DC
FULLY MODULAR 'PLUG IN' CONSTRUCTION

Memory : 200 Channels Freq/Mode/Filter
Scanning : Full memory or discreet parts
Automatic or Manual Stop
Manual step on or Reverse
Dwell : Variable from Keypad 1 to 9 seconds
KEYPAD FUNCTIONS INDICATED BY DISPLAYS

NOW AVAILABLE AT HIGHLY COMPETITIVE PRICES

Send for Technical Brochure to:
Vigilant Communications Ltd.
Unit 5, Pontiac Works, Fernbank Road, Ascot, Berks SL5 8JH, England

Tel: (0344) 885656
Telex: 849769 Vigcom G

WW – 016 FOR FURTHER DETAILS

HOME CONTROL CENTRE

This kit enables you to control up to 16 different appliances by means of coded pulses in the mains wiring which may be decoded by special receivers anywhere in the house. The transmitter may be controlled manually or by the computer interface enabling your favourite micro to make your coffee in the morning, switch lights anywhere in the house, or your electric blanket in your bedroom. Just think of the possibilities — and no wiring!

The Kit comprises a transmitter with pre drilled box and two receivers. **XXK112 £42.00**

XXK111 (additional receivers) £10

REMOTE CONTROL KITS

FOR A DETAILED BOOKLET ON REMOTE CONTROL — send 30p + 6" x 9" S.A.E

These kits have been designed to enable infra red remote control to be incorporated into virtually any application from switching carlocks to alarms to controlling hi-fi or TV. The exact application will determine the interface circuitry (not supplied) between the receiver and the device to be controlled. In many cases this could be a relay or triac. General instructions and applications are supplied with the kits. The kits are coded and provide a high degree of noise immunity and security.

MK18 Transmitter Kit For use with MK11 MK12 Receivers and MK9 10 13 keyboards. Requires PP3 battery. Size 8 x 2.13 cms. Range approximately 60ft. **£6.80**
MK11 Receiver Kit Mains powered. Provides 10 latched plus 3 analogue outputs. Ideal for controlling audio amplifiers, TV or lighting circuits where control of lamp brightness is required. **£13.50**
MK12 Transmitter Keyboard **£4.35**
MK19 DC Controlled Stereo Amplifier Kit If control of stereo amplifier is required the MK19 may be used providing for remote control of base, treble and volume (or balance). This kit also includes a one of 10 decoder with LEDs for remote selection of programme or channel. May be connected between the pre-amp and power amp sections of almost any audio amplifier. **£10.70**

MK12 Receiver Kit
MK12 (state latched or momentary) **£13.50**
MK9 4 way Transmitter Keyboard **£1.90**
MK10 16 way Transmitter Keyboard **£5.40**
MK15 Dual Latched Solid State Relay **£4.50**

SEND SAE 9" x 6" for FREE YELLOW CATALOGUE

MICROPROCESSOR CONTROLLED MULTI-PURPOSE TIMER

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre set times over a seven-day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set and forget it — the clock will do the rest. **£39.00**



XXK114 OPTIONAL RELAY KIT £3.90

Kit includes one relay, PCB to accommodate up to four relays, terminal blocks, etc. to fit inside CT6000 box. Provides up to four 3amp 240V changeover contacts. Additional relays £1.65 each.

Add 65p postage & packing +15% VAT to total Overseas Customers. Add £2.50 (Europe), £6.00 (elsewhere) for p&p. Send SAE for further STOCK DETAILS. Goods by return subject to availability. 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)

COMPUTER SHOWROOM
TOP HARDWARE, LATEST SOFTWARE
PERIPHERALS, ACCESSORIES AND MUCH, MUCH MORE!

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to

TK ELECTRONICS
11-13 Boston Road
London W7 3SJ

TEL 01-567 8910 ORDERS
01-578 7744 ENQUIRIES
01-578 2842 TECHNICAL AFTER 5PM

WW – 071 FOR FURTHER DETAILS

METAL FILM RESISTORS

1% Tolerance, 1/4 Watt

High quality, British made 89 (E24) values, only 3p each. VAT, p&p inclusive.

SPECIAL OFFER
5 of each 445 resistors
£12.60

SPECIAL 'POP' PACK

50 pcs: 100R, 1K, 4K7, 10K, 47K, 100K,
1M. 25 pcs: 330R, 470R, 1K5, 2K2, 3K3,
22K. Total 500 pcs. £11.50.

Extra special 1 of each kit £22

ORION SCIENTIFIC LTD - 16 Orange Street - London WC2H 7ED

WW – 067 FOR FURTHER DETAILS

TIME WRONG?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, 24 hour format, larger digit Hours and Minutes for easy QUICK GLANCE time, auto GMT/BST and Leap Year, can expand to Years, Months and Milliseconds, also audio to record and show time on playback, receives Rugby 60kHz atomic time signals, only 15x5x8cm, built-in antenna, 1000km range, GET the TIME RIGHT, £72.70.

TUNABLE AUDIO NOTCH FILTER £16.40.

Each fun-to-build kit (ready made to order) includes all parts, printed circuit, case, instructions, by-return postage, etc, full catalogue, money back assurance, SEND away NOW.

CAMBRIDGE KITS

45 (WB) Old School Lane, Milton, Cambridge. Tel: 860150



SALE of TEST EQUIPMENT

1/2 PRICE!



YC1000L DATA PROCESSOR OBSERVE & RECORD: FREQUENCY PERIOD PULSES TEMPERATURE VOLTAGES & TIMES
£365 +15% VAT +£5 Securitor

The YC1000L is a laboratory grade instrument with versatile microprocessor control. It includes: a frequency (10Hz-600MHz, 0.02 ppm), a period (0.1S to 0.1uS), and a pulse counter (0-99,999,999, TTL level), a voltmeter (AC or DC to 999V, 3 ranges), a thermometer (remote sensor -29.0 to +99.9°C) plus a precision timer (24 hour clock providing; event or period, (local or remote) and alarm functions). Display is via 8 large fluorescent green digits and/or the inbuilt 5X7 (20 characters line 2 line second) Dot Matrix thermal printer.


You will wonder how your laboratory or workshops ever coped without



LCD MULTIMETER 3 1/2 DIGIT HANDHELD (Auto range/pol) KD200
£25 +15% VAT +£1 postage



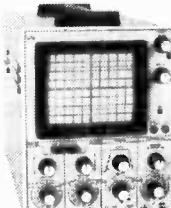VSWR-POWER METER INTERNAL 50Ω LOAD 2-150 MHz 6/30/150W 35 models stocked F5800
£99 +15% VAT +£3 postage



OSCILLOSCOPE 4" 20 MHz DUAL TRACE (DT520 5" E229+) DT420
£199 +15% VAT +£5 Securitor

S.M. HOUSE, TOTTEN, SOUTHAMPTON SO4 4DP, ENGLAND
 Tel: SOUTHAMPTON [+44] ([0]703) 867333. Telex: 477351 SMCMM G

WW - 057 FOR FURTHER DETAILS

SURPLUS STOCK SALE

Compact Switch Mode Power Supplies (50 watt)

	SIZE	STATUS	PRICE
Model SR5-10 5v @ 10A	5 1/2" x 4 1/2" x 1 1/2"	Unused	
Model SR12-4 12v @ 4A	5 1/2" x 4 1/2" x 1 1/2"	Unused	
Prices each			£75
Lots of 10			£65
Lots of 20			£49

5 1/4" Floppy Disc Drives

Pertec FD250 48 TPI	Double Sided	Unused	£140
Pertec FD200 48TPI	Single Sided	Used*	£50
YE-Data YD274 48 TPI	Double Sided	Unused	£180

Cartridge Disc Drives

Pertec D3341 2.5 mbyte fixed and 2.5 mbyte removable	Unused	£500
Pertec D3481 5 mbyte fixed and 15.0 mbyte removable	Unused	£1,500
CDC9448 Cartridge Disc Drive	Used*	£1,750

Terminals

Mael 502 VDU/Terminal	Unused	£350
Mael 502 VDU/Terminal	Used*	£150
Televideo Model 950 VDU/Terminal	Used*	£375
Data Type DT22	New	£495

Paper Tape Reader

EECO 2001-2 200CPS Read Head and Electronics	Unused	£190
--	--------	------

Items marked * are used products and cannot be guaranteed free from defect.



Dicoll Electronics Limited
 Bond Close, Kingsland Estate, Basingstoke, Hampshire, RG24 0QB.
 Telephone: Basingstoke 61551
 Telex: 858769

WW - 046 FOR FURTHER DETAILS



PM COMPONENTS LTD VALVE & COMPONENTS SPECIALISTS

INTEGRATED CIRCUITS

AN124 2.50	MC1350P 0.95	SN76660N 0.80	TBA530 1.10	TDA2030 2.80
AN214Q 2.50	MC1351P 1.50	STK014 7.95	TBA530Q 1.10	TDA2522 1.95
AN240P 2.80	MC1352P 1.25	STK015 7.95	TBA540 1.25	TDA2524 1.95
AN612 2.15	MC1357 2.35	STK433 7.95	TBA550Q 1.45	TDA2530 1.95
AN7140 3.50	MC1358 1.58	STK437 7.95	TBA560C 1.45	TDA2532 1.95
AN7145 3.50	MC1495 3.00	TA7061AP 3.95	TBA560CQ 1.45	TDA2540 1.25
AN7150 2.95	MC1496 1.25	TA7108P 1.80	TBA570 1.00	TDA2541 2.15
BA521 3.35	MC145106P 1.65	TA7120P 1.80	TBA641A12 2.50	TDA2560 2.15
CA1352E 1.75		TA7130P 1.50		TDA2571 1.95
CA3086 0.48	MC1723 0.50	TA7146 2.95	TBA651R 2.50	TDA2581 2.25
ET76016 2.50	MC3357 2.75	TA7176AP 2.95	TBA720A 2.45	TDA2593 2.95
HA11377 3.50	ML2318 1.75	TA7203 2.95	TBA750Q 2.65	TDA2600 5.50
HA1156W 1.50	ML2328 2.50	TA7204P 2.15	TBA800 0.89	TDA2610 2.50
HA1339A 2.95	MSM5807 6.75	TA7205AP 1.50	TBA810AS 1.65	TDA2611A 1.95
HA1551 2.95	MSM5807 6.75	TA7222AP 1.80	TBA810T 1.65	TDA2640 2.80
LA1230 1.15	SAA500A 3.50	TA7272P 4.25	TBA820M 0.75	TDA2680A 2.75
LA4102 2.95	SAA1025 7.25	TA7310P 1.80	TBA820Q 1.45	TDA2690A 2.45
LA4250 2.95	SAA5010 6.35	TA7313AP 2.95	TBA890 2.50	TDA3660 5.50
LA4400 4.15	SAS560S 7.75	TA7321P 2.25	TBA920 1.65	UPC566H 2.95
LA4420 1.95	SAS570S 1.75	TA7609P 3.15	TBA950/2X 2.35	UPC575C2 2.75
LA4422 2.50	SAS580 2.85	TA7611AP 2.95	TBA970 2.95	UPC1025H 2.50
LA4430 2.50	SL901B 4.85	TAA550 0.25	TBA820M 0.75	UPC1028H 1.95
LC7120 3.25	SL917B 6.65	TAA570 1.95	TBA1441 2.15	UPC1032H 2.75
LC7130 3.50	TC1210 1.80	TAA621AX1 2.50	TCA270 1.10	UPC1156H 1.50
LC7131 5.50	TC1327 1.10	TAA661B 1.20	TCA270S 1.10	UPC1158H 0.75
LC7137 1.00	TC1327Q 1.10	TAA700 1.70	TCA850 2.50	UPC1181H 1.25
LM324N 0.45	SN76003N 1.95	TBA120B 0.95	TCA900 1.65	UPC1182H 2.95
LM380N 0.95	SN76013N 1.95	TBA120C 1.15	TDA440 2.20	UPC1185H 3.95
LM383T 2.95	SN76023N 1.95	TBA120T 1.05	TDA1001 1.95	UPC1191V 1.50
M51513L 2.30	SN76033N 1.95	TBA120U 1.00	TDA1004A 3.25	UPC1350C 2.95
M51515L 2.95	SN76110N 0.85	TBA231 1.25	TDA1006A 2.50	UPC1353C 2.45
M51521L 1.50	SN76115N 1.25	TBA395 1.50	TDA1010 2.15	UPC1365C 3.95
MB3712 1.00	SN76131N 1.30	TBA396 0.75	TDA1035 2.50	UPC2002H 1.95
MC1307P 2.00	SN76226DN 1.55	TBA440N 2.55	TDA1037 1.95	555 0.35
MC1310P 1.80	SN76227N 1.95	TBA480Q 1.25	TDA1170 1.95	556 0.42
MC1327 0.95	SN76533N 1.95	TDA1200 1.90	TDA1190 2.15	723 0.50
MC1327Q 0.95	SN76544N 1.05	TBA510Q 2.50	TD01270Q 3.95	741 0.35
MC1330P 0.76	SN76570N 1.00	TBA520 1.10	TDA1327 1.70	747 0.50
MC1349P 1.20	SN76650N 1.15	TBA520Q 1.10	TDA2002 1.95	748 0.35
			TDA2020 2.45	7805 0.80

SEMICONDUCTORS

AA12 0.25	BC174 0.09	BD202 0.85	BF457 0.32	RC11633A 0.90
AC126 0.22	BC174A 0.09	BD203 0.78	BF458 0.36	RC11633S 1.45
AC127 0.20	BC177 0.15	BD222 0.48	BF459 0.40	SK55F 1.45
AC128 0.28	BC178 0.15	BD225 0.48	BF597 0.25	TIP29C 0.42
AC128K 0.32	BC182 0.10	BD232 0.35	BF840 0.23	TIP30C 0.42
AC141 0.28	BC182BL 0.10	BD233 0.35	BF841 0.28	TIP32C 0.42
AC141K 0.34	BC183 0.10	BD237 0.35	BF842 0.35	TIP33C 0.75
AC142K 0.30	BC183L 0.09	BD236 0.45	BF888 0.30	TIP34B 0.75
AC176 0.22	BC184BL 0.09	BD237 0.40	BF890 1.50	TIP41A 0.45
AC176K 0.31	BC204 0.10	BD238 0.40	BF891 1.75	TIP41C 0.45
AC178 0.25	BC204B 0.13	BD241 0.40	BF892 1.75	TIP42C 0.47
AC187 0.28	BC208B 1.13	BD242 0.40	BF893 1.75	TIP42T 0.65
AC187K 0.28	BC212 0.09	BD246 0.50	BF894 0.80	TIP43 0.80
AC188 0.25	BC212L 0.09	BD246 0.50	BF929 0.30	TIP125 0.65
AC188K 0.37	BC212LA 0.09	BD410 0.55	BF929 0.30	TIP142 1.75
AD142 0.79	BC213 0.09	BD434 0.55	BF929 0.30	TIP146 2.75
AD143 0.79	BC213L 0.09	BD437 0.50	BF929 0.30	TIP161 2.95
AD149 0.70	BC214 0.09	BD438 0.80	BF929 0.30	TIP165 0.80
AD161 0.39	BC214C 0.09	BD506 0.50	BF929 0.30	TIP205S 0.55
AD162 0.39	BC214L 0.09	BD508 0.40	BF951 0.21	TIS91 0.20
AD161/2 0.90	BC237B 0.09	BD520 0.65	BFY52 0.25	TV106/2 1.50
AF114 1.80	BC238 0.09	BD538 0.85	BFY90 0.75	2N2219 0.28
AF124 0.34	BC239 0.12	BD597 0.75	BLV48 1.77	2N2905 0.40
AF125 0.35	BC251A 0.12	BD597 0.75	BLV48 1.77	2N305 0.12
AF126 0.32	BC252A 0.15	BD698 1.10	BR101 0.30	2N3054 0.59
AF127 0.32	BC258 0.25	BD707 0.80	BRC4443 0.85	2N3055 0.52
AF139 0.40	BC258A 0.39	BDX32 1.50	BT106 1.49	2N3702 0.12
AF178 1.95	BC264 0.10	BDY57 1.65	BT108 1.89	2N3703 0.12
AF239 0.42	BC300 0.30	BF115 0.35	BT116 1.20	2N3704 0.12
AU106 2.00	BC301 0.30	BF117 0.24	BT119 1.85	2N3705 0.12
AU110 2.00	BC303 0.26	BF154 0.12	BT120 1.85	2N3706 0.12
AU113 2.95	BC307 0.09	BF158 0.22	BU105 1.22	2N3708 0.12
BC107A 0.11	BC307A 0.09	BF160 0.27	BU108 1.69	2N3773 1.95
BC107B 0.11	BC307B 0.09	BF167 0.28	BU124 1.25	2N3792 1.36
BC108 0.10	BC327 0.10	BF173 0.22	BU125 1.25	2N4427 1.50
BC108A 0.11	BC328 0.10	BF177 0.38	BU126 1.44	2N4444 1.15
BC108B 0.12	BC337 0.10	BF178 0.28	BU204 1.55	2N5294 0.42
BC109 0.10	BC338 0.09	BF179 0.34	BU205 1.30	2N5296 0.48
BC109B 0.12	BC347A 0.13	BF180 0.29	BU208 1.39	2N5298 0.60
BC109C 0.12	BC347B 0.13	BF181 0.29	BU208A 1.52	2N5496 0.65
BC114 0.11	BC478 0.20	BF182 0.29	BU326 1.20	2SA715 0.60
BC116A 0.15	BC527 0.20	BF183 0.29	BU407 1.24	2SC1995 0.80
BC117 0.19	BC547 0.10	BF184 0.28	BU500 2.25	2SC496 0.80
BC119 0.24	BC548 0.10	BF185 0.28	BU526 1.90	2SC1096 0.80
BC125 0.25	BC549A 0.06	BF194 0.11	BUY698 1.70	2SC1106 2.50
BC139 0.20	BC550 0.10	BF195 0.11	MJ3000 1.98	2SC1172 2.20
BC140 0.31	BC557 0.08	BF196 0.11	MJE340 0.40	2SC1173 1.15
BC141 0.25	BC557B 0.08	BF197 0.11	MJE520 0.48	2SC1306 1.00
BC142 0.21	BC558 0.10	BF198 0.16	MPSA12 0.20	2SC1307 1.50
BC143 0.24	BCY33A 1.80	BF199 0.14	MPSA13 0.20	2SC1449 0.80
BC147 0.09	BD115 0.30	BF200 0.16	MPSA92 0.30	2SC1678 1.25
BC147B 0.09	BD116 0.60	BF201 0.40	MRF453 17.50	2SC1909 1.95
BC148A 0.09	BD124P 0.59	BF245 0.30	MRF454 23.50	2SC1945 2.10
BC148B 0.09	BD131 0.32	BF256/LC 0.28	MRF475 2.50	2SC1953 0.95
BC149 0.09	BD132 0.35	BF257 0.28	MRF477 10.00	2SC1957 0.80
BC157 0.12	BD133 0.40	BF258 0.28	OC23 1.80	2SC2028 1.15
BC158 0.09	BD135 0.30	BF259 0.28	OC42 0.55	2SC2029 1.95
BC159 0.09	BD136 0.30	BF271 0.28	OC44 0.75	2SC2078 1.45
BC160 0.28	BD137 0.32	BF273 0.13	OC45 0.55	2SC2091 0.85
BC161 0.28	BD138 0.30	BF336 0.34	OC70 0.45	2SC2098 2.50
BC170B 0.15	BD139 0.32	BF337 0.29	OC71 0.40	2SC2166 1.95
BC171 0.09	BD140 0.30	BF338 0.32	OC81 1.80	2SC2314 0.80
BC171A 0.10	BD144 1.10	BF355 0.37	R2008B 1.70	2SD234 0.50
BC171B 0.10	BD159 0.65	BF362 0.38	R2010B 1.70	3N211 1.95
BC172 0.10	BD166 0.55	BF363 0.38	R2322 0.58	3SK45 0.70
BC172B 0.10	BD179 0.72	BF371 0.20	R2323 0.66	3SK88 0.55
BC172C 0.10	BD182 0.70	BF394 0.19	R2540 2.48	
BC173B 0.10	BD201 0.83	BF422 0.32		

DIODES

AA119 0.08	BY199 0.40	IN4004 0.05	CRT TUBES
BA102 0.17	BY206 0.14	IN4005 0.06	A selection available. Prices on request.
BA115 0.13	BY208-80		

SOUND EIGHTY FOUR

London's premier exhibition of public address, sound reinforcement and communications equipment will be another exciting show!

a unique opportunity to see the very latest equipment and systems – to meet and talk with specialists of vast experience in sound installations

**CUNARD INTERNATIONAL HOTEL
HAMMERSMITH, LONDON**

FEBRUARY 21-22-23, 1984

10 am-5pm Daily – Admission Free

Association of Sound and Communications Engineers Limited
4B High Street, Burnham, Slough SL1 7JH Telephone: 06286 67633

WW – 058 FOR FURTHER DETAILS

EASIBINDERS

Quick, neat and easy!



It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold six issues and is attractively bound and blocked with the WIRELESS WORLD logo.

Price U.K. £4.30 including postage, packing and V.A.T.

Overseas orders add 35p per binder
Nat. Giro No. 5157552.


Please allow 3/4 weeks for fulfilment of order.

Payment by ACCESS/BARCLAYCARD/VISA. Send coupon below detailing credit card no. and signature.

Why not place your order now? Send the completed coupon below with remittance payable to:

EASIBIND 42 Hoxton Square
London N1 6NS

Order Form WIRELESS WORLD

I enclose P.O./cheque value..... for.....binders
Years required.....
BLOCK LETTERS PLEASE
Name.....
Address.....
Date..... Registration No. 735718 

ELECTROVALUE

**Your
SPECIALIST SUPPLIERS
for SWITCHES**



MINIATURE TOGGLES, 7000 Series
250V/2A, 120 V/5A. Single, double, three and four pole configurations inc. Centre Off/On and biased.


CK WAVECHANGE with adjustable stops. 1P/12 way, 2P/6W, 3P/4W, 4P/3W, 6P/2W.

SWITCH KITS
RA Shaft Assemblies up to 6 wafers.
DP Mains switch. Screens; Spacers.



PUSH BUTTON
Miniature
Single and Double Pole Changeover
Standard
Latching and momentary

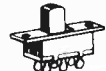SLIDERS
Miniature & Standard. SP and DP in 1, 2 or 3 positions.
Many other types such as for timing and other special applications.



**BRITAIN'S LEADING QUALITY COMPONENT
SUPPLIERS - SEND FOR FREE 32 PAGE A-Z LIST
ATTRACTIVE DISCOUNTS-FREE POSTAGE-GOOD SERVICE & DELIVERY**

ELECTROVALUE LTD

28 St. Jude's Road
Englefield Green
Egham, Surrey
TW20 0HB

Tel: (0784) 33603. Telex: 264475. North: 680 Burnage Lane,
Manchester (061-432 4945). EV Computing Shop, 700
Burnage Lane, Manchester (061-431 4866).

**ACCESS AND
BARCLAYCARD
Phoned Orders
Welcome**

2

WW – 030 FOR FURTHER DETAILS

CONNECTION PATTERN TESTER



DATAMAN I.C.T.

£1 PER POINT approx.

FOR CABLES LOOMS, BARE PCBS, ETC.

(Picture shows 1, 144 Point tester, measuring 10.5 x 11.75 x 1.5 inches) If an array has N connection nodes, then (N-1) + (N-2) + (N-3) ... + 1 tests are required to discover its connection pattern. An old-fashioned method would be to use a buzzer, with a probe in each hand to complete the circuit, and check each node with the remainder. The formula simplifies to $N(N-1)/2$ which means that 653,796 tests are required to check a PCB with 1,144 component pads.

DATAMAN's ICT performs in the same way — but finishes the task in seconds. The results can be compared with a previously learned pattern or formed into a standard ASCII file (a list of what-is-connected-with-what) and transmitted to a printer, terminal or computer in serial (RS232) or parallel (CENTRONICS) format.

ICT uses CUSTOM LSI designed by DATAMAN. A tester of the size and format you need can be BUILT-TO-ORDER. DATAMAN can also provide a COMPLETE SOLUTION with fixtures, beds-of-nails, N.C. drilling from your artworks etc.

BUS EXERCISER/DIAGNOSTIC AID



£295

+ VAT

Plugs into microprocessor socket, reads and writes to system ROM, RAM and I/O.

Prints memory contents in HEX, ASCII or ASSEMBLER MNEMONICS.

Prints MEMORY MAP of addressing space.

Performs CHECKSUMS, TESTS RAM, prints addresses and bits which default.

Tests data lines for SHORTS to rails, other data or address lines.

Tells engineer of address/data faults impossible to find with other tools

Easy to program: retains sequences for testing up to fifteen different products in permanent memory.

Microdoctor is supplied in Z80, 6500, 6800 and 8085 format with appropriate disassembler (say which you want).

MICRODOCTOR £295.00

Conversion card & ROM (Changes configuration and disassembler e.g. Z80 to 6500 say which) £35.00

Clip-over PROBE (only needed if uP is soldered-in) £35.00

10 Rolls Thermal Paper £9.00

FAST EPROM PROGRAMMER

£395

+ VAT



NINE TEXTTOOL ZIPDIP SOCKETS

LCD ALPHA DISPLAY

PROGRAMS ALL SINGLE RAIL EPROMS TO 27256

80% CUT IN PROGRAMMING TIME USING MANUFACTURERS' SUGGESTED ALGORITHMS (e.g. 2764 takes 1.25 mins not 7 mins typical)

SWITCH-SELECT OF EPROM TYPE (NO MODULES)

Z80 TEACHING AID

£99

+ VAT

MENTA

GIVES REAL INSIGHT

TV DISPLAY of program, register and stack.

Outstanding editing, debugging, single-step, set breakpoint etc. Very useful on-line ASSEMBLER — also DISASSEMBLER to serial output. Cassette interface.

24 I/O ports. Good for ROBOTICS.

Designed for British schools-council to teach micro-control — appears in GCE syllabus.

MENTA complete with power-supply, leads, manual etc. £99.00

Module for Course in Microprocessor control:

Teachers' Guide £2.50

Pupil Reader £3.00

Universal I/O Module £21.00

Analogue to Digital Module £18.00


Digital to Analogue Module £14.00

D.C. Motor & control Module £12.00

Switched Input Module Analogue/Digital £10.00

Complete set of all above including MENTA £160.00

EPROM PROGRAMMER/EMULATOR

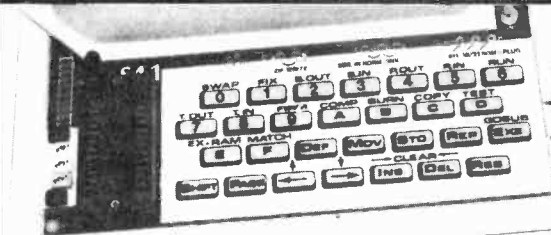

£169

+ VAT

SOFTY programs

2716, 2732 and 2532 EPROMS

Will copy any EPROM to any other — same

type or different. Uses TV for display of

features. Has standard serial and parallel I/O routines for communication with

computers and printers — and cassette interface.

Also popular as in-circuit ROM emulator for product development.

2764/128 ADAPTOR for SOFTY

With 28 pin Zero-Force Textool socket.

Rotary switch selects bank to be programmed £25.00

EPSON thandar NEC H/H TIGER

WE HAVE COMPUTERS, LOGIC ANALYSERS, PRINTERS, SOFTWARE IN STOCK INCLUDING QX10, HX20, TA2080 £ call us for a good deal.

THANDAR TA2080 — DATAMAN ADDS RS232 OUTPUT AND DISASSEMBLERS

12K of retrofit ROM and interface board allows printing complete D or R store in STATE or TIMING diagrams — also DISASSEMBLES in Z80, 6502 or 6800 MNEMONICS on-screen or to printer. You fit or we fit — no fitting charge but you pay carriage £295

OLIVETTI TYPEWRITER INTERFACES

For ET121 and ET221 machines which permit the typewriter to be used as a DAISY WHEEL PRINTER for computers implementing the RS232, IEEE 488 (PET) or CENTRONICS PARALLEL busses, almost all computers in fact. Great for word processing and letter-writing! Same price, fitting free if requested (you pay carriage on typewriter if we fit) £195

ULTRA-VIOLET EPROM ERASERS from £39

DATAMAN PRODUCTS ARE USED IN INDUSTRY AND EDUCATION ALL OVER THE WORLD. GET FREE LIT PACK — PHONE NOW OR ANYTIME (24 HR answering)

NO RIP-OFF GUARANTEE
MONEY BACK WITHOUT QUESTION IF PRODUCT RETURNED V. THIN 14 DAYS (less p & p)
ALL GOODS HAVE 12 MONTHS WARRANTY, PARTS AND LABOUR

**LOMBARD HOUSE,
CORNWALL ROAD,
DORCHESTER, DORSET DT1 1RX.
Telephone: Dorchester (0305) 68066**

Telex 418442 DATAMAN

Prepaid orders normally shipped by return

Prices include first-class recorded post in UK

Securicor, Red Star, etc. at extra cost.

VAT should be added at current rates.

Carriage Free on Orders in

excess of £50.00

Add £2.50 if less


WW - 032 FOR FURTHER DETAILS

CUBE

TOTAL COMPUTER SYSTEM

**6502+assembler+BBC BASIC
6809+FLEX→cross assemble anything**

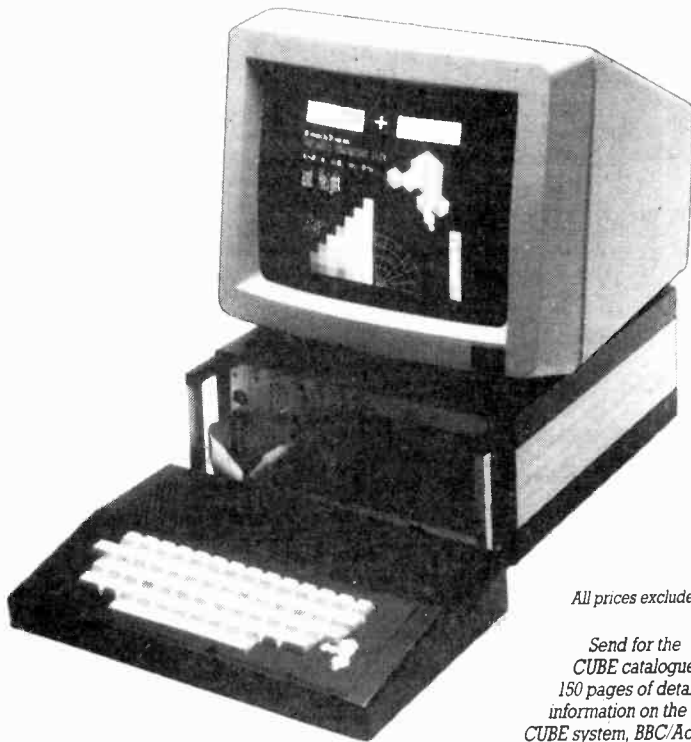SPECIAL SUPPORT FOR 6809, 6801, (SINGLE CHIP) AND 68000



All prices exclude VAT

Send for the
CUBE catalogue –
150 pages of detailed
information on the
CUBE system, BBC/Acorn
Computers and accessories.

**Complete disk development system from £1276
Target single board computer card from £139**

Here is an exciting concept, based on the demands of working engineers who are called on to provide computer solutions, often at short notice.



These flexible, robust and easy-to-use development systems are based on CUBE Eurocard modules, and can be extended to include as many interfaces of as many types as the ultimate application demands, and yet which can also be reduced after development to a minimum cost unit, leaving off every unnecessary feature.

6502 systems support Atom and BBC BASIC, both on disk systems and on the 6502 EuroCUBE SBC.

£139 buys this single board computer, which is also the cpu card of the development system. It carries serial and digital interfaces, a standard CUBE bus connector and four byte-wide memory sockets with battery back-up for CMOS RAM.

6809 systems support FLEX, and under FLEX support assembler for 6809 and cross assemblers for all popular processors. Control Universal especially support 6801 (single chip computer) and 68000. High level compiling languages such as "C" and PL/9 provide code to run on the 6809 EuroCUBE which costs the same and has the same specification as the 6502 EuroCUBE.

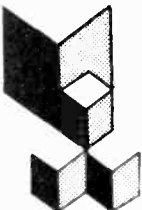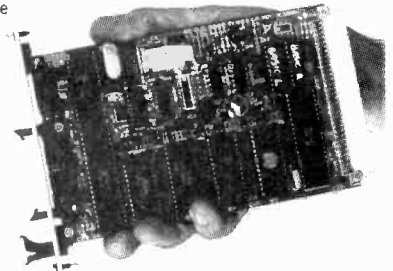UniCUBE is a carrier for the 6801 single chip computer, which has a serial interface, 4KB masked ROM or piggy-back EPROM, 128 bytes of RAM and 29 i/o lines. It costs less than £35 in quantity, and the single chip micro itself is just a few pounds for the masked ROM version, or can be used in the EPROM version with no commitment to quantity.



Control Universal Ltd
Anderson's Court
Newnham Road,
Cambridge CB3 9EZ
Tel 0223 358757 Telex 995801

WW - 062 FOR FURTHER DETAILS

FREQUENCY COUNTERS

**HIGH PERFORMANCE
HIGH RELIABILITY
LOW COST**


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz – 1.2GHz
- ★ Sensitivity <50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100	(100MHz)	£104.36
METEOR 600	(600MHz)	£134.26
METEOR 1000	(1GHz)	£184.36

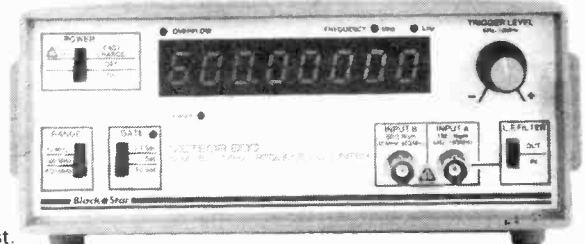Illustrated colour brochure with technical specification and prices available on request.



Designed and
manufactured
in Britain

Black★Star

**BLACK STAR LTD, Dept. WW, 9A Crown Street, St Ives
Huntingdon, Cambs PE17 4EB, England
Tel: (0480) 62440 Telex: 32339**

WW - 022 FOR FURTHER DETAILS

STEREO DISC AMPLIFIER 4

THE MOST THOROUGHLY RESEARCHED DISC AMPLIFIER THERE IS
for Broadcasting, Disc Monitoring and Transfer



Magnetic cartridge to balanced lines. Unique Response Variable Filter provides, through a single control knob, a 3dB turnover frequency variable between 13 and 4kHz but always with an appropriate phase and amplitude characteristic for psychoacoustic considerations. Also unbalanced version and Moving Coil Pre-amplifier.

SURREY ELECTRONICS LTD., The Forge, Lucks Green, Cranleigh
Surrey GU6 7BG - Telephone: 0483 275997

TOROIDAL TRANSFORMERS

We are now able to offer a range of high quality Toroidal transformers at very competitive prices:

30VA £6.27, 50VA £7.73, 80VA £8.51
120VA £9.33, 160VA £11.43, 300VA £15.27

Prices include P&P and VAT

Available in the following voltages: 6-0-6, 9-0-9, 12-0-12, 15-0-15, 18-0-18, 22-0-22, 25-0-25, 30-0-30, 35-0-35, 40-0-40, 45-0-45, 50-0-50.

Qty. discount 50 plus 10%, 100 plus 20%.

TRADE ENQUIRIES WELCOME

AIRLINK TRANSFORMERS LTD
28 Bullfields, Sawbridgeworth, Herts. Tel: 0279-724425

WW - 047 FOR FURTHER DETAILS

WIRELESS WORLD MARCH 1984

To obtain further details of any of the coded items mentioned in the editorial or advertisement pages of this issue, please complete one or more of the attached cards entering the reference number(s). Your enquiries will be passed on to the manufacturers concerned and you can expect to hear from them direct in due course. Cards posted from abroad require a stamp. These service cards are valid for six months from the date of publication.

Please use capital letters

If you are way down on the circulation list, you may not be getting the information you require from the journal as soon as you should. Why not have your own copy?

To start a one year's subscription you may apply direct to us by using the card at the bottom of this page. You may also apply to the agent nearest to you: their address is shown below.

OVERSEAS SUBSCRIPTION AGENTS

Australia: Gordon & Gotch (Australasia) Ltd, 380 Lonsdale Street, Melbourne 3000, Victoria

Japan: Western Publications Distribution Agency, 170 Nishi-Okubo 4-chome, Shinjuku-Ku, Tokyo 160

Belgium: Agence et Messageries de la Presse, 1 Rue de la Petite-ILE Brussels 7

Lebanon: Levant Distributors Co., P.O. Box 1181, Makdesi Street, Halim Hanna Bldg, Beirut

Canada: Davis Circulation Agency, 153 St. Clair Avenue West, Toronto 195, Ontario

Malaysia: Times Distributors Sdn. Bhd., Times House, 390 Kim Seng Road, Singapore 9, Malaysia.

Cyprus: General Press Agency Ltd, 131 Prodromou Street, P.O. Box 4528, Nicosia

Malta: W. H. Smith Continental Ltd, 18a Scots Street, Valletta

Denmark: Dansk Bladdistribution, Hovedvagtsgade 8, Dk. 1103 Kobenhavn.

New Zealand: Gordon & Gotch (New Zealand) Ltd, 102 Adelaide Road, Wellington 2

Finland: Rautakirja OY, Koivuvaarankuja 2, 01640 Vantaa 64, Finland.

Nigeria: Daily Times of Nigeria Ltd, 3 Kakawa Street, P.O. Box 139, Lagos

France: Dawson-France S.A., B.P.40, F-91121, Palaiseau

Norway: A/S Narvesens Kioskkompani, Bertrand Narvesens vei 2, Oslo 6

Germany: W. E. Saarbach GmbH, 5 Kolin 1, Follerstrasse 2

Portugal: Livaria Bertrand s.a.r.l Apartado 37, Amadora

Greece: Hellenic Distribution Agency, P.O. Box 315, 245 Syngrou Avenue, Nea Smyrni, Greece.

South Africa: Central News Agency Ltd, P.O. Box 1033, Johannesburg

Holland: Van Ditmar N.V., Oostelijke Handelskade 11, Amsterdam 1004

Spain: Comercial Athenum s.a. Consejo de Ciento, 130-136 Barcelona 15

India: International Book House, Indian Mercantile Mansion Ext, Madame Cama Road, Bombay 1

Sweden: Wennegren Williams A. B. Fack S-104, 25 Stockholm 30

Iran: A.D.A., 151 Khasban Soraya, Tehran

Switzerland: Neville & Cie SA, Rue Levrier 5-7, CH-1211 Geneve 1 Schmidt Agence AG, Savogelstrasse 34, 4002 Basle

Israel: Stelmatsky's Agency Ltd, Citrus House, P.O. Box 628, Tel Aviv

U.S.A.: John Barrios, Business Press International, 205 East 42nd Street, New York, N.Y. 10017

Italy: Intercontinental s.a.s. Via Veracini 9, 20124 Milano

Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
Licence No CY258

Wireless World
Reader Enquiry Service
Oakfield House
Perrymount Road
Haywards Heath
Sussex RH16 3DH

2

CUT HERE

CUT HERE

CUT HERE

Enquiry Service for Professional Readers

Wireless World

Wireless World, March 1984 WW 8463

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW

Name

Name of Company

Address

Telephone Number

PUBLISHERS USE ONLY			A/E		
------------------------	--	--	-----	--	--

Position in Company

Nature of Company/Business

No. of employees at this establishment

I wish to subscribe to Wireless World


VALID FOR SIX MONTHS ONLY

ELECTRONICS & Wireless World
Subscription Order Form

To become a subscriber to Wireless World please complete the reverse side of this form and return it with your remittance to:

**Subscription Manager,
Business Press International Ltd,
Oakfield House, Perrymouth Road
Haywards Heath, Sussex RH16 3DH
United Kingdom**

DC MICROVOLTMETER

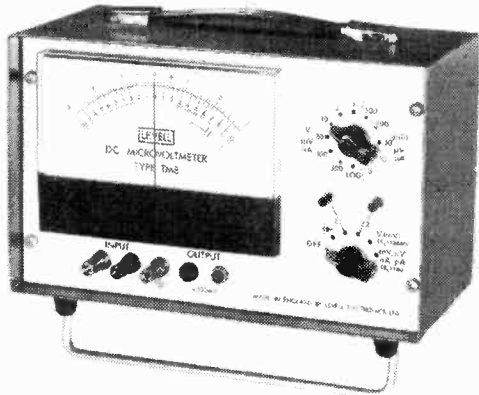

TYPE TM8 £120
+ p&p + VAT

Send for data covering our range of instruments

VOLTAGE RANGES

±3µV, ±10µV, ±30µV..... ±300V.
Accuracy ±1.5% rdg. ±1.5% range ±0.15µV.
Drift <0.1µV/°C. Noise <0.3µV p-p on 3µV.
Input resistance 100M on V, (mV); 1M on mV, µV.

CURRENT RANGES

±3pA, ±10pA, ±30pA..... ±300nA.
Accuracy ±2% rdg. ±1.5% range ±0.2pA.
Drift <0.3pA/°C. Noise <0.5pA p-p on 3pA.

LIN/LOG RANGES

On mV, µV and nA, pA LOG ranges
±30% fsd equals ±3µV and ±3pA approx.
±60% fsd equals ±30µV and ±30pA approx.
±100% fsd equals ±300mV and ±300nA approx.
On V LOG the voltages are 1000 times greater.

RECORDER OUTPUT

±300mV at fsd. Source resistance 4.7kΩ

POWER SUPPLY

One type PP9 battery or equivalent, life 1000 hrs.

SIZE & WEIGHT

180 × 260 × 140mm. 3kg. Meter scale 120mm.

LEVEL ELECTRONICS LTD.

Moxon Street, Barnet, Herts. EN5 5SD, England.
Telephone: 01-440 8686/449 5028.

ESTABLISHED 30 YEARS. U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

RECORD DECKS 240 volt AC. Post £2

Make	Model	Drive	Cartridge	Price
BSR	P170	Rim	Ceramic	£22
GARRARD	6200	Rim	Ceramic	£24
BSR	P207	Rim	Ceramic	£20
BSR	P232	Belt	Magnetic	£28

AUTOCHANGERS 240 VOLT
Budget Rim Ceramic £18
Deluxe Rim Ceramic £20
BSR Deluxe Rim Magnetic £26
GARRARD 6200 Rim Ceramic £22

THE "INSTANT" BULK TAPE ERASER £11.50 Post 95p
Suitable for cassettes and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools. **Tape Head Demagnetiser** £5.

ALUMINIUM CHASSIS. 2 1/2in. deep 6x4 £1.75; 8x6 £2.20; 10x7 £2.75; 12x8 £3.20; 14x9 £3.60; 16x6 £3; 16x10 £3.80; 12x3 £2.80; 14x3 £2.50; 13x9 £2.80.
ALUMINIUM PANELS. 6x4 55p; 8x6 90p; 14x3 90p; 10x7 £1.15; 12x8 £1.30; 16x6 £1.30; 14x9 £1.75; 12x12 £1.80; 16x10 £2.10.
ALUMINIUM BOXES. 4x4x1 1/2 £1.20, 4x2 1/2x2 £1.20, 3x2x1 £1.20, 6x4x2 £1.90, 7x5x3 £2.90, 8x6x3 £3, 10x7x3 £3.60, 12x5x3 £3.60, 12x8x3 £4.30; 9x4x4 £3.
POTENTIOMETERS 5k/2meg. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5L SP 45p.

MINI-MULTI TESTER £7.50 Post 65p
Pocket size moving coil instrument. 4000 o.p.v. 11 ranges. DC volts 5.25, 250, 500. AC volts 10, 50, 500, 1000. DC amps 0-250µA, 0-250mA. Resistance 0 to 600K

De Luxe Range Doubler MULTI-METER £19.50
50,000 o.p.v. 7x5x2in. 50 Micro Amp
43 Ranges, 1,000V, AC-DC, 20 MEG 10 amp DC Post £1

PANEL METERS 50µA, 100µA, 500µA, 1mA, 5mA, 50mA, 100mA, 500mA, 1 amp, 2 amp, 25 volt, VU 2 1/4x2x1 1/4. Stereo VU 3 1/4x1 1/2x1in. £5. p.p. 50p

RCS SOUND TO LIGHT CONTROL BOX £27 Post £1
Complete ready to use with cabinet size 9x3x5in.
3 channel, 1000 watt each. For home hi-fi or disco
OR KIT OF PARTS £19.50

BATTERY ELIMINATOR Mains to 9 volt DC. 400MA.
Stabilised, safety cutout, 5x3 1/4x2 1/2in. £5. Post £1.

DISCO GRAPHIC MIXER EQUALISER £108. Post £2.
4 channel stereo, 5 band graphic, red + green LED. VU display, headphone monitor, or Deluxe Model, 5 channel 7 band graphic. £119.

FAMOUS LOUDSPEAKERS

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
AUDAX	WOOFER	5in	25	8	£10.50	£1
GOODMANS	HIFAX	7 1/2x4 1/4	100	4/8/16	£30	£2
GOODMANS	HB WOOFER	8in	60	8	£12.50	£1
WHARFEDALE	WOOFER	8in	30	8	£9.50	£2
CELESTION	DISCO/GROUP	10in	50	8/16	£21	£2
GOODMANS	HPG/GROUP	12in	120	8/15	£29.50	£2
GOODMANS	HPD/DISCO	12in	120	8/15	£29.50	£2
GOODMANS	HP/BASS	15in	250	8	£72	£3
GOODMANS	HPO/BASS	18in	230	8	£84	£4

RCS STEREO PRE-AMP KIT. To build. Inputs for high, medium or low imp volume control and PC Board. Can be ganged for mono-channel £3.50 Post 65p

MAINS TRANSFORMERS Post
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A £7.00 £2
350-0-350V 250mA, 6.3V 6A CT £14.00 £2
220V 25ma 6V lamp £3.00 220V 45ma 6V 2 Amp £4.00 £1
250V 60mA, 6V 2A £5 £1

Step-Down 115v to 240V 150W £9. 250W £12. 500W £14 £2

GENERAL PURPOSE LOW VOLTAGE			Price Post		
Tapped outputs available					
2 amp	3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V		£5.00	£2	
1 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£6.00	£2	
2 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£10.50	£2	
3 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£12.50	£2	
5.8-10-16V	1/2 amp	£2.50 £1	0-8-12V 5 amp	£5.00 £1	
6V 1/2 amp	£2.80 £1	15-0-15V 1 amp	£4.00 £1		
6-0-6V 1 1/2 amp	£3.50 £1	15-0-15V 2 amp	£5.00 £1		
9V 400ma	£1.50 £1	20V 1 amp	£4.00 £1		
9V 3 amp	£5.00 £1	20-0-20V 1 amp	£4.50 £1		
9-0-9V 50ma	£1.50 £1	0-12-27V 1 amp	£5.00 £1		
9-0-9V 1 amp	£3.50 £1	20-40-60V 1 amp	£4.50 £2		
10-0-10V 2 amp	£4.00 £1	25-0-25V 2 amp	£5.50 £1		
10-30-40V 2 amp	£5.50 £1	28V 1 amp twice	£7.00 £2		
12V 100mA	£1.50 £1	30V 1 1/2 amp	£5.00 £1		
12V 750 ma	£2.50 £1	30V 5 amp and			
12V 3 amp	£4.50 £1	17-0-17 2a	£5.50 £2		
12-0-12V 2 amp	£5.50 £1	35V 2 amp	£5.00 £1		

500mF 12V 15p; 25V 20p; 50V 30p. 1200mF 76V 80p.
1000mF 12V 20p; 25V 35p; 50V 50p; 100V 120p.
2000mF 30V 42p; 40V 60p; 100V £1.40; 1500mF 100V £1.20.
2250mF 50V 70p; 3000mF 50V 65p; 4700mF 40V £1.

CAPACITORS WIRE END High Voltage
.001, .002, .003 .005, .01, .02, .03, .05 mfd 400V 10p.
.1MF 400V 14p. 600V 15p. 1000V 25p.
22MF 350V 12p. 600V 20p. 1000V 30p. 1750V 60p.
47MF 150V 10p. 400V 25p. 630V 30p.

HIGH VOLTAGE ELECTROLYTICS			
2/500V	45p	32+32+16/350V	90p
16/450V	45p	100+100/275V	50p
20/500V	75p	150+200/275V	50p
32/350V	45p	32+32+32/450V	95p
32/500V	95p	50+50+50/350V	95p
125/500V	£2	8+8/500V	£1
		8+16/450V	75p
		16+16/350V	80p
		32+32/350V	85p
		32+32/500V	£2
		50+50/300V	50p
		50+50/350V	80p

BAKER AMPLIFIERS BRITISH MADE

PA150 Watt MICROPHONE VOCAL AMPLIFIER £129
4 channel mixing, 8 inputs, dual impedance, 50K-600 ohm, volume, treble, bass. Presence controls on each channel. Master volume control, echo send return socket. Slave sockets. Post £3.
150 Watt MIXER AMPLIFIER 4 Inputs £99
Discotheque, Vocal, Public Address. Speaker outlets for 4, 8 or 16 ohms. Four inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. Slave output. 16" x 8" x 5 1/2". Wt - 14lb. Master volume control. British made. 12 months' guarantee. 240V A.C. 120V to order. All transistor and solid state. Post £2.
100 Volt Line Model, 150 watt £114. MONO SLAVE, 150 watt £80. Baker Stereo Slave 150 + 150 watt 300 watt Mono £125. Post £4.

BAKER MOBILE PA AMPLIFIER. All transistor. 60 watt RMS, 12V DC & 240V AC, 4 inputs 50k. Aux + 2 mics + 1 phono. Output 4-8-16 ohm + 100 volt line. **£89 Post £2**

BAKER PORTABLE DISCO 150 watt. Twin console + amplifier + mike and headphones + twin speakers £330, 300 watt £399. Carr. £30. Console + decks + pre-amp £95. Carr. £12.

PA CABINET SPEAKERS. Complete. 8 ohm 60 watt 17x15x9in. £27. Post £4. 4 or 8 or 16 ohm 75 watt 23x15x11in. £52. 90 watt 32x15x11in. £71. 150 watt £80. Carr. £10. Black vinyl covered.

BAKER LOUDSPEAKERS

MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£16	£2
SUPERB	12	8-16	30	HI-FI	£26	£2
AUDITORIUM	12	8-16	45	HI-FI	£24	£2
AUDITORIUM	15	8-16	60	Woofer	£37	£2
GROUP 45	12	4-8-16	45	PA	£16	£2
DG 75	12	4-8-16	75	PA	£20	£2
GRUP 100	12	8-16	100	PA	£26	£2
DISCO 100	12	8-16	100	Disco	£26	£2
GROUP 100	15	8-16	100	PA	£35	£2
DISCO 100	15	8-16	100	Disco	£35	£2

REPAIR service available to most Baker loudspeakers.
SPEAKER COVERING MATERIALS. Samples Large S A E
B.A.F. LOUDSPEAKER CABINET WADDING 18in wide 35p ft.

MOTOROLA PIEZO ELECTRIC HORN TWEETER, 3 3/4in. square £5
100 watts. No crossover required. 4-8-16 ohm, 7 3/4x3 3/8in. £10
HORN BOXES, complete 200 watt £30. 300 watt £35. Size 16x6x6in. Black vinyl covered with handle Post £4

CROSSOVERS. TWO-WAY 3000 cps 30 watt £3. 100W £4.
THREE-WAY 950 cps/3000 cps. 40 watt rating. £4. 60 watt £6. 100W £8.
LOUDSPEAKER BARGAINS. Please enquire, many others in stock.
4 ohm, 5in. 7x4in. £2.50; 6 1/2in, 8x5in, £3; 8in, £3.50. 6 1/2in 20W £7.50.
8 ohm, 2 3/8in, 3in, £2; 5x3in, 6x4in, 7x4in, 5in, £2.50; 3in, 10W £4.
8x5in, £3; 8in, £4.50; 10in, £5; 12in, £6. 8in 25W £6.50. 60W £12.50.
15 ohm, 2 1/4in, 3 1/2in, 5x3in, 6x4in, £2.50. 6 1/2in 10W £5. 8in £4. 10in £7.
25 ohm, 3in, £2; 5x3in, 6x4in, 7x4in, £2.50. 120 ohm, 3 1/4in dia. £1.
EMI 13 1/2x8in. Bass & Tweeter 4 or 8 ohm 10 watt £8 pp. £1

RADIO COMPONENT SPECIALISTS

Books and Components Lists 32p stamps. (Minimum post/packing charge 65p.) Access or Barclaycard Visa. Tel: 01-684 1665 for SAME DAY DESPATCH. Cash prices include VAT. WWW-7

HART


LINSLEY-HOOD 300 SERIES AMPLIFIERS

- 30 Watt Complete Kit £72
- 35 Watt Complete Kit MosFet O/P £79.50
- 45 Watt Complete Kit MosFet O/P £83.50
- Reprints of 30 Watt Article from 'Hi-Fi News' 50p
- Reprints of MosFet Postscript to above 30p

LINSLEY-HOOD 100-WATT MOSFET POWER AMPLIFIER

The very latest amplifier design, published in 'Wireless World' by the renowned John Linsley-Hood. This may now be taken as the standard by which the rest are judged! Our kit, approved by the designer, has massive heat sinks and power supply and includes all components needed to build. Case size 412mm wide, 254mm deep and 145mm high. Automatic switched speaker protection is included as standard. Cost of all parts is over £120. Our complete stereo kit price £105.50.

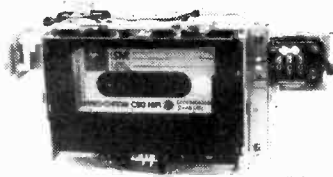SOLENOID CONTROLLED HI FI/DIGITAL CASSETTE MECHANISM



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

THIS MONTH'S SPECIAL OFFERS

HIGH-SPEED DIGITAL CASSETTE RECORDER

A really super buy for the computer enthusiast. These decks, made by Burroughs, use a capacitorless cassette mechanism to record and replay data at 10 and 30 inches per second. The read after write head uses an NRZ system with separate tracks for clock and data. Power supplies of 5v, -12v and +12v are required. Front panel is 137mm square and the unit is 200mm deep including rear connector. Offered in good export condition at a fraction of original cost, ONLY £44.50 inc. VAT and postage. Data inc. circuits and layouts of PCBs £3.50.

DOLBY 'B' NOISE REDUCTION IC LM1011

Magnificent opportunity for home experimenters, build your own noise reduction system. Supplied complete with circuit showing typical application. Absolute knockout price only £3.50 for two inc. VAT and post.


COMPLETE STEREO CASSETTE DECK

Brand new high quality top-loading Cassette Deck complete with Record/Play electronics. Supplied with connection data and circuit diagram. Automatic chrome/ferrie switching. Only needs 9v DC supply. Total price only £18.34 inc. VAT and post.

COMPLETE STEREO TUNER MODULE

Three band LW/MW/FM Stereo Tuner fully assembled on PCB 165 x 85mm. Supplied with Ferrite rod aerial and band switch fully wired. Facility provided to drive tuning meter and stereo LED. Only needs 12v DC supply. FM sensitivity. 2.5uV. Price only £7.99 inc. VAT and post.

HALF HEIGHT 5 1/4" FLOPPY DISK

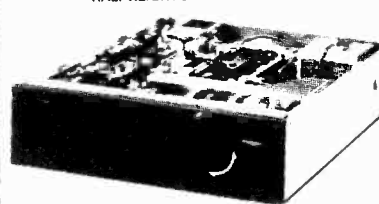

Latest MPU controlled 80 Track Drives, support single or double density. Fully compatible with Teac, Shugart and many other full and half height drives. £179 80 Track, Single side £225 80 Track, Double side Full manual for each type £14.50. No VAT.

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

- HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £5.11
 - HM50 High Beta Permalloy Head. A hard-wearing, higher performance head with metal capability £8.06
 - HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £9.91
 - HO551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £9.73
- Please consult our list for technical data on these and other Special Purpose Heads.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build-up of residual head magnetisation causing noise on playback £4.54

Curved Pole Type for inaccessible heads £4.85

COMPONENTS

We now list a wide range of individual components many of which are not available elsewhere. Send for your copy of our latest list which also gives further information on our Kits.

Please add part cost of post, packing and insurance as follows:

INLAND
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50

OVERSEAS
Please send sufficient to cover Surface or Air Post as required.

ALL PRICES EXCLUDE VAT UNLESS STATED



Personal callers are always very welcome but please note that we are closed all day Saturday (0691) 652894

AA117	0.090	BC140	0.130	BD138	0.200	BF244	0.200	BW200	0.200	BY200	0.200	ZZ200	0.200	AAA117	0.090	BB117	0.130	CC117	0.130	DD117	0.130	EE117	0.130	FF117	0.130	GG117	0.130	HH117	0.130	II117	0.130	JJ117	0.130	KK117	0.130	LL117	0.130	MM117	0.130	NN117	0.130	OO117	0.130	PP117	0.130	QQ117	0.130	RR117	0.130	SS117	0.130	TT117	0.130	UU117	0.130	VV117	0.130	WW117	0.130	XX117	0.130	YY117	0.130	ZZ117	0.130	AAA222	0.090	BB222	0.130	CC222	0.130	DD222	0.130	EE222	0.130	FF222	0.130	GG222	0.130	HH222	0.130	II222	0.130	JJ222	0.130	KK222	0.130	LL222	0.130	MM222	0.130	NN222	0.130	OO222	0.130	PP222	0.130	QQ222	0.130	RR222	0.130	SS222	0.130	TT222	0.130	UU222	0.130	VV222	0.130	WW222	0.130	XX222	0.130	YY222	0.130	ZZ222	0.130	AAA333	0.090	BB333	0.130	CC333	0.130	DD333	0.130	EE333	0.130	FF333	0.130	GG333	0.130	HH333	0.130	II333	0.130	JJ333	0.130	KK333	0.130	LL333	0.130	MM333	0.130	NN333	0.130	OO333	0.130	PP333	0.130	QQ333	0.130	RR333	0.130	SS333	0.130	TT333	0.130	UU333	0.130	VV333	0.130	WW333	0.130	XX333	0.130	YY333	0.130	ZZ333	0.130	AAA444	0.090	BB444	0.130	CC444	0.130	DD444	0.130	EE444	0.130	FF444	0.130	GG444	0.130	HH444	0.130	II444	0.130	JJ444	0.130	KK444	0.130	LL444	0.130	MM444	0.130	NN444	0.130	OO444	0.130	PP444	0.130	QQ444	0.130	RR444	0.130	SS444	0.130	TT444	0.130	UU444	0.130	VV444	0.130	WW444	0.130	XX444	0.130	YY444	0.130	ZZ444	0.130	AAA555	0.090	BB555	0.130	CC555	0.130	DD555	0.130	EE555	0.130	FF555	0.130	GG555	0.130	HH555	0.130	II555	0.130	JJ555	0.130	KK555	0.130	LL555	0.130	MM555	0.130	NN555	0.130	OO555	0.130	PP555	0.130	QQ555	0.130	RR555	0.130	SS555	0.130	TT555	0.130	UU555	0.130	VV555	0.130	WW555	0.130	XX555	0.130	YY555	0.130	ZZ555	0.130	AAA666	0.090	BB666	0.130	CC666	0.130	DD666	0.130	EE666	0.130	FF666	0.130	GG666	0.130	HH666	0.130	II666	0.130	JJ666	0.130	KK666	0.130	LL666	0.130	MM666	0.130	NN666	0.130	OO666	0.130	PP666	0.130	QQ666	0.130	RR666	0.130	SS666	0.130	TT666	0.130	UU666	0.130	VV666	0.130	WW666	0.130	XX666	0.130	YY666	0.130	ZZ666	0.130	AAA777	0.090	BB777	0.130	CC777	0.130	DD777	0.130	EE777	0.130	FF777	0.130	GG777	0.130	HH777	0.130	II777	0.130	JJ777	0.130	KK777	0.130	LL777	0.130	MM777	0.130	NN777	0.130	OO777	0.130	PP777	0.130	QQ777	0.130	RR777	0.130	SS777	0.130	TT777	0.130	UU777	0.130	VV777	0.130	WW777	0.130	XX777	0.130	YY777	0.130	ZZ777	0.130	AAA888	0.090	BB888	0.130	CC888	0.130	DD888	0.130	EE888	0.130	FF888	0.130	GG888	0.130	HH888	0.130	II888	0.130	JJ888	0.130	KK888	0.130	LL888	0.130	MM888	0.130	NN888	0.130	OO888	0.130	PP888	0.130	QQ888	0.130	RR888	0.130	SS888	0.130	TT888	0.130	UU888	0.130	VV888	0.130	WW888	0.130	XX888	0.130	YY888	0.130	ZZ888	0.130	AAA999	0.090	BB999	0.130	CC999	0.130	DD999	0.130	EE999	0.130	FF999	0.130	GG999	0.130	HH999	0.130	II999	0.130	JJ999	0.130	KK999	0.130	LL999	0.130	MM999	0.130	NN999	0.130	OO999	0.130	PP999	0.130	QQ999	0.130	RR999	0.130	SS999	0.130	TT999	0.130	UU999	0.130	VV999	0.130	WW999	0.130	XX999	0.130	YY999	0.130	ZZ999	0.130	AAA000	0.090	BB000	0.130	CC000	0.130	DD000	0.130	EE000	0.130	FF000	0.130	GG000	0.130	HH000	0.130	II000	0.130	JJ000	0.130	KK000	0.130	LL000	0.130	MM000	0.130	NN000	0.130	OO000	0.130	PP000	0.130	QQ000	0.130	RR000	0.130	SS000	0.130	TT000	0.130	UU000	0.130	VV000	0.130	WW000	0.130	XX000	0.130	YY000	0.130	ZZ000	0.130
-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	--------	-------	-------	-------	-------	-------

PHILIPS P2000 DAISY WHEEL PRINTER. RS232	£375 ea	44 HP SWEEP OSC H01-694B. 7-12.4gHz.	£350
SHUGART 801 FLOPPY DISK DRIVES 8"	£100 ea	45 JP VHF SIG GEN 608D 10-480MHz	£150
TRANSELT DOT MATRIX PRINTER Compact Serial Interface 230V. With info	£65 ea	48 HP WAVE ANALYSER 302A. 20Hz-50kHz	£35
TELETYPE ASR33 (Printer, Keyboard, Punch and Reader) RS232	£50 ea	49 B&K BEAT FREQ OSC 1022 20Hz-20kHz	£400
CREDO 75 TELEPRINTER. Very good condition	£25 ea	51 B&K LEVEL RECORDER 2305. Solid state	£200
9" MONITOR. Cased. Non-standard, with info	£20 ea	52 B&K LEVEL RECORDER 2305. valve	£200
12" MONITOR. Cased. Non-standard, with info	£15 ea	53 B&K MICROPHONE AMPLIFIER 2603	£100
AZTEC 20" Black and white MONITOR. Video In	£50 ea	54 B&K RANDOM NOISE GEN 1402	£125
TV Style 20" MONITOR. Black and white	£30 ea	56 B&K RMS AUDIO VOLTMETER 2410	£40
		59 B&K MICROPHONE 4111 with stand and cable	£35
		61 B&K AUDIO FREQ SPECTROMETER 2109 with level recorder 2304	£150
		63 TEK TIME MARK GENERATOR 184	£125
		64 TEK SQUARE WAVE GEN 106 10Hz-1MHz rep rate	£35
		65 WAYNE KERR UNIVERSAL BRIDGE B221 Mk 3 (meter indicator) with low imp adaptor	£175
		67 WAYNE KERR UNIVERSAL BRIDGE B221 with low imp adaptor Q221	£35
		68 WAYNE KERR COMPONENT BRIDGE B521	£45
		69 WAYNE KERR VHF ADMITTANCE BRIDGE B801	£125
		70 WAYNE KERR VHF ADMITTANCE BRIDGE B801 Mk 3 (meter indicator) with low imp adaptor	£30
		71 ADVANCE SIG GEN SB62B 150Hz-220MHz CW/Mod	£60
		72 ADVANCE PULSE GENERATOR PG52B	£350
		74 ADVANCE DUAL STAB DB PS P.3 0-30V-1A twice Metered.	£50
		75 SOLARTRON DVM A223. AC/DC/Ohm 4 1/2 digit	£30
		78 AVO MULTIMETER CT41A (Ex-Ministry)	£40
		79 AVO MULTIMETER 7X	£25
		80 AVO MULTIMETER 8s from	£45
		81 AVO TRANSISTOR TESTER TT169 with leads. As new (P&P £2)	£20
		82 AVO VALVE CHARACTERISTIC METER VCM163 with data	£250
		84 FARNELL STAB PS TSV30/SEC 0-5amps	£80
		86 FARNELL STAB PS TSV30/2EC 0-30V 2 Amps	£40
		87 FARNELL L.F. SINE/SQUARE OSCILLATOR 1Hz-100kHz. Solid state	£75
		88 AIRMEC MODULATION METER 2103 300MHz AM/FM	£150
		90 BRANDENBURG POWER SUPPLY 37A5E0 0-1000V	£75
		91 BRANDENBURG POWER SUPPLY PM2500R 0-2.5kv	£125
		92 LEVEL TRANSISTOR AC VOLTMETER TM2A 1.5mV-500V (with leather case)	£30
		93 LEVEL TRANSISTOR AC MICROVOLTMETER TM3B 15 microVolt - 500V full scale	£45
		95 TAYLOR INSULATION TESTER 130C 500VMax (P&P £3)	£25
		96 GREEN TRANSMITTER OUTPUT ANALYSER TG2400	£50
		97 GREEN SYNTHESISED DIGITAL SIGNAL GENERATOR TG1800 1Hz-9.9MHz Sine/Square	£600

EXECUTIVE TELEPHONES - PUSH BUTTON
Many functions including 10 number memory, repeat dialling, etc. Will connect to GPD System. Brand New £25 each. P&P £4

SAMPLE OF STOCK - SAE or telephone for LISTS
Please check availability before ordering. Carriage all units £7. VAT to be added to total of Goods and Carriage. SAE for LISTS

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 68041

Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

WW - 083 FOR FURTHER DETAILS

WW - 080 FOR FURTHER DETAILS

YOU HAVEN'T SEEN ANYTHING LIKE THIS ON A COLOUR MONITOR BEFORE.

An RGB monitor from JVC offering a resolution of 370x470 pixels for less than £150?

We guarantee you won't see another bargain like that in this or any other micro mag—or in any other supplier's showroom.

For we've managed to acquire the sole distribution rights to these superb machines and we are able to offer them at an unbeatable price.

There are two models available: medium resolution (370x470 pixels) at £149.95; and high resolution (580x470 pixels) at £229.95. (Both excluding VAT.)

The units have a 14" screen and are suitable for the BBC Micro, Lynx, Oric, Apple, IBM and most other leading micros.

They are robustly constructed in a handsome cream casing. And come with a full year's guarantee.

Delivery is good: your monitor should arrive by courier service within ten days of our receiving your order.

You can order by filling in the coupon below and posting to: Opus Supplies Ltd., 158 Camberwell Road, London SE5 0EE. Or by telephoning 01-701 8668 quoting your credit card number. Or, of course, you can buy in person at our showroom between 9-5.30pm, Monday-Saturday.



MODEL REFERENCE	1302-1 Medium Resolution	1302-2 High Resolution
RESOLUTION	370 x 470 Pixels	580 x 470 Pixels
C.R.T.	14"	14"
SUPPLY	220/240v. 50/60Hz.	220/240v. 50/60Hz.
E.H.T.	Minimum 19.5kv Maximum 22.5kv	Minimum 19.5kv Maximum 22.5kv
VIDEO BAND WIDTH	6MHz.	10MHz
DISPLAY	80 characters by 25 lines	80 characters by 25 lines
SLOT PITCH	0.63mm	0.41mm
INPUT. VIDEO	R.G.B. Analogue/ TTL Input	R.G.B. Analogue/ TTL Input
SYNC	Separate Sync on R.G.B. Positive or Negative	Separate Sync on R.G.B. Positive or Negative
EXTERNAL CONTROLS	On/off switch and brightness control	On/off switch and brightness control

To Opus Supplies Ltd., 158 Camberwell Road, London SE5 0EE.

Please send me _____ Medium Resolution Colour Monitor(s)
at £149.95 each (ex. VAT).

_____ High Resolution Colour Monitor(s) at
£229.95 each (ex. VAT).

_____ Connection lead(s) at £6.00 each.

I understand carriage per monitor will cost an extra £7.00.

(N.B. A Medium Resolution Monitor including VAT, lead, and carriage costs £187.39. A High Resolution Monitor including VAT, lead, and carriage costs £279.39.)

I enclose a cheque for £_____. Or please debit my credit card
account with the amount of £_____. My Access/Barclaycard
(please tick) no. is _____

Name _____

Address _____

Telephone: _____

Opus.
Opus Supplies Ltd.

WW8

WW - 031 FOR FURTHER DETAILS

B. BAMBER ELECTRONICS

SURPLUS & EX-EQUIPMENT VALVES

Rohde & Schwarz Enograph Type BN 18531, £60.
 Rohde & Schwarz Sweep Signal Generator Type BN 4242/2, 50 kHz to 12 MHz, £85.
 Rohde & Schwarz U.H.F. Signal Generator Type BN 41026, 1000 to 1900 MHz, £125.
 Rohde & Schwarz Group Delay Measuring Equipment Indicator, £50.
 Rohde & Schwarz Group Delay Measuring Equipment Modulator/Demodulator, £50.
 Rohde & Schwarz Power Signal Generator Type BN 4105, 30 kHz to 300 MHz, £125.
 Rohde & Schwarz U.H.F. Millivolt Meter Type BN 1091, 20mV to 10V, £50.
 Airmec Modulation Meter Type 210, 3 to 300 MHz, £95.
 Hewlett Packard S.H.F. Signal Generator Model 618 B, 3.8 to 7.6 GHz, £120.
 Hewlett Packard Square Wave Generator Model 211 A, £60.
 Pye 12V Power Unit Type AC 15, £25.
 Wandel Goltermann Carrier Frequency Level Meter, Type TFPM 76, £60.
 Rohde & Schwarz Video Skop Type BN 4241, £250.
 Schomantal Frequency Meter Type FD1, 30 to 900 MHz, £50.
 Tektronix Delay Cable Type 113, £50.
 Bruel & Kjoer Vibration Meter Type 2502, £50.
 Advance Pulse Generator Type PG 54, £40.
 Systron Donne L.F. Spectrum Analyzer Model 805, 200 Hz to 1.6 MHz, £550.
 Ministry Oscilloscope Type CT 436 Dual Beam D.C. to 6 MHz, £85.
 Marconi Signal Generator Type TF 995A/3/S (CT402), £95.
 Marconi 100-Watt 7dB Attenuator Type TM 5280, 150 to 185 MHz, £40.
 Pye Aerial Tuner Unit Type ATU 4, 2 to 9 MHz, Pre-set, £15.
 A.I.M. Electronics Pulse Generator with Clock Generator, £65.
 Marconi V.H.F. Signal Generator Type TF 1064B/5M, £125.
 Marconi Tx & Rx Output Test Set Type TF 1065, £85.
 Marconi 1/4 Universal Bridge Type TF 1313, £220.
 Tektronix L-C Meter Type 130, £65.
 Heathkit Harmonic Distortion Meter Type 1M-12U, £20.
 Rohde & Schwarz Polyskop 11 Type BN 425/50, £350.
 A.E.W. Process Cycling Oven, £600.
 Twin Clothes Lockers, nests of 2 with keys, £20.
 Louverd Lin Bin Panels, 4'6" x 4'6", £20.
 Kodak Roll Film Drying Cabinet with Hangers, £150.
 Potter Line Printer Type LP 3000, £150.

Digital Decwriter 11 Printer with keyboard, £100.
 Rohde & Schwarz Z-g Diagraph Type BN 3562, 300 to 2430 MHz, £85.
 Marconi V.H.F. Alignment Oscilloscope Type TF 1104/1, £150.
 Tektronix Sampling Oscilloscope Type 661 with 4S2 plug in, £120.
 Avo Valve Tester Type CT160, £30.
 Advance Oscilloscope Type DS25A, DC to 3 MHz, £120.
 Tequipment Oscilloscope Type D43, DC to 10 MHz, £100.
 Tequipment Oscilloscope Type S43, DC to 10 MHz, £85.
 Tequipment Oscilloscope Type S51, £75.
 Tequipment Oscilloscope Type S32A, DC to 3 MHz, £65.
 Tektronix Rack Mount Oscilloscope RM17, DC to 10 MHz, £85.
 Tektronix Oscilloscope Type 317, DC to 15 MHz, £120.
 Marconi R.C. Oscilloscope Type TF1101, £65.
 Airmec Millivolt Meter Type 301A, £20.
 Advance Audio Generator Type H1, £20.
 Tektronix Oscilloscope Type 543A with Type B plug in, £160.
 Tektronix Oscilloscope Type 531A with Type H plug in, £160.
 Sander Oscillator Type CLC 2-4, 2 to 4.5 GHz, £95.
 Bruel & Kjoer Microphone Amplifier Type 2604, £50.
 Bruel & Kjoer Microphone Amplifier Type 2603, £50.
 EMI Oscilloscope Wide Band Amplifier Type 7/1, £25.
 Airmec Sweep Signal Generator Type 352, 20 Hz to 200 kHz, £45.
 Belix Variable Power Unit, 0 to 50V at 2 amp, £40.
 BTR Silvertown Anti-Static and Conductive Footwear Tester, £25.
 E995 £1.00 S11E12 £19.00 £20.00
 Dawe True RMS Valve Voltmeter Type 612A, £20.
 Rohde & Schwarz Power Signal Generator Type BN41001, 0.1 to 30 MHz, £75.
 Marconi Distortion Factor Meter Type TF142F, £85.
 Marconi A.M. Signal Generator Type TF144H/4S, £125.
 Tektronix Time Mark Generator Type 180A, £125.
 Marconi F.M. Signal Generator Type TF 1066B/1, £280.
 Marconi F.M. Signal Generator Type TF 1066B/6, £300.
 Marconi Carrier Deviation Meter Type TF 791 D, £95.
 Airmec Modulation Meter Type 409, £120.
 Marconi Universal Bridge Type TF 868, £50.
 Marconi A.M./F.M. Signal Generator Type TF 995A/5, £230.
 Marconi R.F. Power Meter Type TF 1020A/4, 300W, 75 ohm, £65.
 Marconi R.F. Power Meter Type TF 1020A/1, 100W, 50 ohm, £65.

A2293	£6.50	6AU6	£1.00
DA41	£21.50	6AV6	£1.00
DF61	£4.00	6BA6	£1.00
DY70	£9.00	6B66	£1.25
E182CC	£9.00	6BH6	£1.95
E282F	£19.00	EY81	£1.50
EAC91	£2.50	EY84	£6.50
EBC90	£1.00	GZ32	£1.00
EC88	£1.00	GZ34	£2.00
EC91	£7.00	GZ37	£4.00
ECC35	£3.50	KT66	£6.50
ECC85	£1.00	KT88	£8.00
ECC88	£1.00	N78	£14.00
ECC91	£2.00	DA2	£1.00
ECF80	£1.00	PL82	£1.00
ECF804	£6.00	QQV03-10	6SL7
ECL80	£1.00	QQV03-20A	6U4
ECL82	£1.00	15L00	6X4
EF39	£1.00	QQV06-40A	7Y4
EF54	£2.50	18L00	12AT7
EF86	£1.25	QV04-7	12AU6
EF91	£1.25	QZ06-20	12AU7
EF92	£2.50	R18	12AV7
EF95	£1.00	S11E12	12AX7
EF184	£1.00	U403	12B4
EF732	£1.80	5B254M	12BH7
EK90	£1.00	5B255M	12BY7
EL34	£2.25	5R4G	12E1
EL37	£9.00	5V4	25L6GT
EL71	£2.50	5Y3GT	1.00
EL81	£6.75	6AG5	1.50
EL84	£1.00	6AG6G	£2.00
EL85	£4.50	6AG7	£2.00
EL86	£1.00	6AN5	£3.95
EL90	£1.25	6AS6	£1.50
EL91	£6.00	6AS7G	£7.50
EL360	£7.75	6AL5	£1.00

PYE POCKETPHONE PF1 UHF RECEIVER

440-470 MHz, Single Channel, int. speaker and aerial. Supplied complete with rechargeable battery and service manual. £6 each plus £1 p.p. plus V.A.T.

BREAKING TEK 545A SCOPES FOR SPARES

CRT type T543 P2 £12 each. Mains Transformers T601 £15. High Volume Transformer T801 with valves £25. Also Switches, Knobs, Fans, Capacitors and Metalwork.

RADIOSONDE RS21 METEOROLOGICAL BALLOON TRANSMITTER

with Water Activated Battery, contains all-weather sensors, fully solid state, £5 each plus £1 p.p. plus V.A.T.

P. & P. or Carriage and V.A.T. at 15% on total must be added to all orders.
 Callers very welcome, strictly between 9 a.m. and 1 p.m and 2 and 5 p.m. Monday to Friday inc. Barclaycard and Access taken
 Official orders welcome ww27




5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE
 PHONE: ELY (0353) 860185



WW - 060 FOR FURTHER DETAILS

SINGLE BOARD 6809 2nd PROCESSOR FOR THE BBC MICRO.

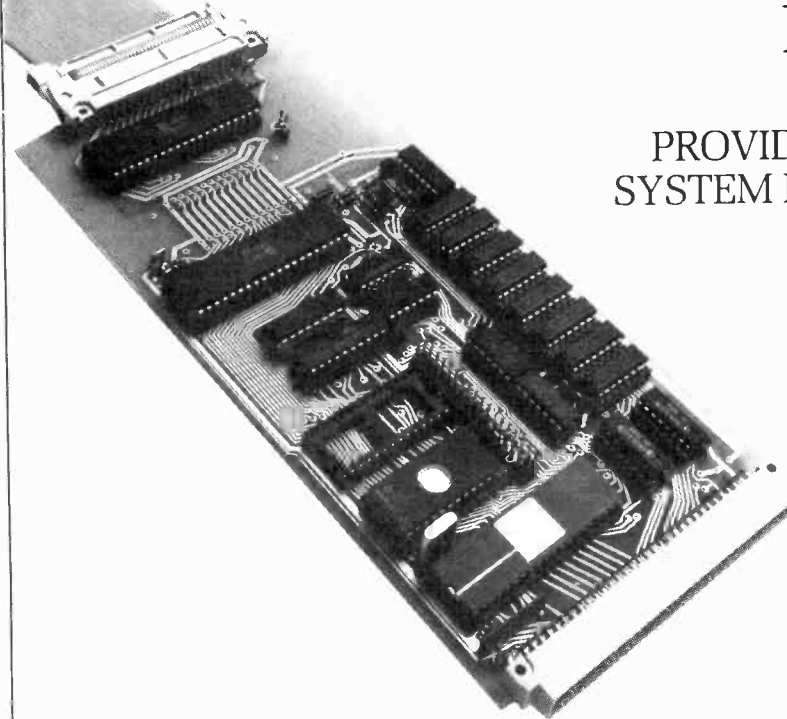PROVIDES A LOW-COST DEVELOPMENT SYSTEM FOR INDUSTRIAL APPLICATIONS.



- Sits inside the BBC or plugs into an extension rack
- Enables standard Flex format Discs to run on BBC
- Supports High Level Language Compilers
- Cross Assemblers and Disassemblers for most micros
- Connects directly on to the tube
- 64k DRAM on board
- Two 28 pin byte wide memory sockets
- Acorn Bus compatible DIN 41612 Bus interface
- Also available as a single board controller

For full information contact Phil Taylor at:



11 St Margarets Road
 Girton, Cambridge CB3 0LT
 (0223) 276791

Cambridge
 Microprocessor
 Systems Limited

WW - 086 FOR FURTHER DETAILS

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

AUDIO FREQUENCY TRANSFORMERS OF EVERY TYPE

YOU NAME IT! WE MAKE IT!

OUR RANGE INCLUDES

Microphone transformers (all types), Microphone Splitter/Combiner transformers, Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.


We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E.E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.

E. A. Sowter Ltd.

Manufacturers and Designers

E. A. SOWTER LTD. (Established 1941) : Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
P.O. Box 36, Ipswich, IP1 2EL, England
Phone: 0473 52794 and 0473 219390
Telex 987703G Sowter

WW - 063 FOR FURTHER DETAILS

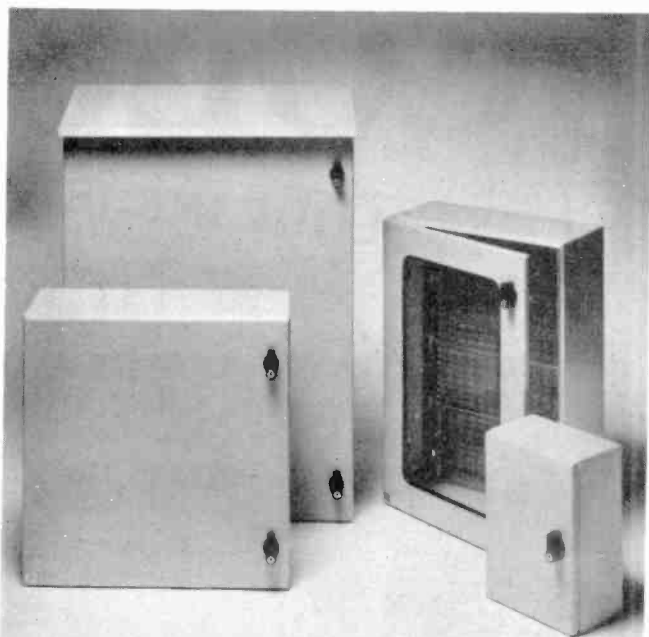

SAREL'S 8000 SERIES SET THE STANDARD

- Protects against ingress of dust and liquids IP55 (BS5490 1977, IEC 529 1976).
- 1.5 and 1.75mm steel bodies and 2mm steel doors.
- Smaller sizes fitted with advanced polyurethane gaskets. Larger sizes (600 x 600 and above) fitted with neoprene gaskets.
- Wide range of chassis systems including plates DIN rail, telequick and gland plates.
- Standard finish is textured beige polyester powder paint.
- Glazed doors — wide choice from stock.



sarel

Think big — think Sarel

Sarel Limited

Cosgrove Way, Luton, Beds. Tel: Luton 20121

Please send me full details of how Sarel's 8000 Series of cabinets and accessories set the standard.

Name _____

Position _____

Company _____

Address _____

Tel: _____

Sarel Limited, Cosgrove Way, Luton, Beds

WW3/84

WW - 060 FOR FURTHER DETAILS

pantechnic

THE POWERFET
SPECIALISTS

OEM USERS

Pantechnic present the most adaptable high-powered amplifier ever.

FET SYSTEM AMP

Features:

- HIGH POWER up to 1.2kW (single ended)
 - LOW VOLUME. 1/15 Cubic foot inc. Heatsink
 - VERSATILE. Delivers more than 1kW into 1/2 to 8 ohms
- OR 2 x 600W into 2 to 8Ω
OR 4 x 300W into 2 to 4Ω (200W into 8Ω)
- OR { 1 x 600W into 2 to 8Ω
1 x 300W into 2 to 4Ω
1 x 150W into 4 to 8Ω
- Etc., etc.

Having been closely involved in a wide variety of OEM applications of their amp boards, Pantechnic became aware of numerous implementation problems often left untackled by other amp board manufacturers. These problems specifically of size and thermal efficiency became particularly aggravated at high powers and considerably lengthened OEM product development time.

By including thermal design in the totality of board design it has been possible to reduce the size of the electronics, and increase the efficiency of the transistor to heatsink thermal circuit. The combined effect of this has been to dramatically increase the volumetric efficiency of the amplifier/heatsink assembly. The SYSTEM Amp offers 1.2kW of power in a space of 180mm x 102mm x 77mm, excluding PSU and Fan.

The basis of this considerable advance is the PANTECH 74 Heat Exchanger, designed and manufactured by us. By eliminating the laminar air flow found in conventional, extruded heatsinks, heat transfer to the environment is greatly enhanced.

The flexibility of the 1.2kW amp stems from its division into 4 potentially separate amplifiers of 300W each (downrateable with cost savings to 150W). These can be paralleled, increasing current capability or seriesed (bridged in pairs) doubling voltage capability. In consequence a large variety of amplifier/load strategies can be implemented.

As ever Pantechnic offer a full range of customising options including DC coupling, ultra-high slew, etc. Contact Phil Rimmer on 01-361 8715 with your particular application problem.

P.S. Specs, as ever, are exemplary.

A wide range of other amplifiers and other modules available.

Price and Delivery

PANTECHNIC (Dept. WW3)
17A WOOLTON STREET
LIVERPOOL L25 5NH
Tel: 051-428 8485

Technical Enquiries
contact
Phil Rimmer
on
01-361 8715

WW - 072 FOR FURTHER DETAILS

COLOURJET

7 COLOUR INK JET PRINTER

Logic seeking in dot address mode

£499 + VAT

With Centronics parallel interface and free BBC Micro dump listing


also: prints OVERHEAD TRANSPARENCIES

Options available

- Buffered RS232/Viewdata interface
- Apple II & IIe interface
- IBM pc dump

Specifications:

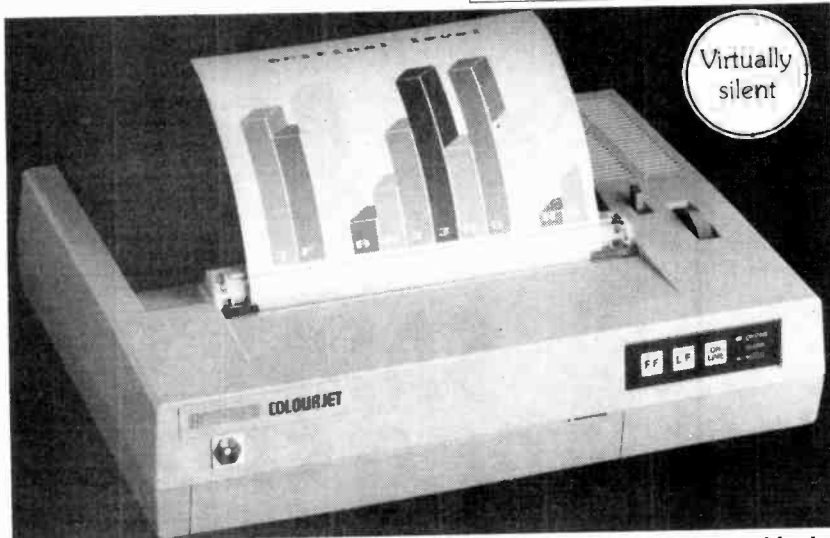- 1280 dots/line in double res. mode
- 37cps in full colour
- Friction feed roll paper and single sheet feed A4
- Ink cartridges 4 million character life



INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432. Telex: 377106



ELECTRIC SHOCK

NEW AIDS TO RECOVERY

ELECTRIC SHOCK ACT AT ONCE—DELAY IS FATAL

1. make sure it is safe to approach
The cable has it. If this is not possible stand on any insulating material such as a mat, newspaper or a rubber mat and use the pencil or pen to disconnect the casualty from the contact using a brush or stick. Do not touch the casualty with bare hands but if nothing else is available then you may have to touch them under the armpits and get the casualty away from the source.

2. check for signs of breathing
Place a casualty in the recovery position and call medical aid.
if NOT breathing
Get someone to call medical aid while you begin mouth-to-mouth ventilation.

3. mouth to mouth ventilation—Speed is essential
Open the airway by tilting the head and lifting the neck. Place the heel of your hand on the forehead and the back of your hand on the chin and push upwards. Breathing should be restored.

4. if AFTER FOUR VENTILATIONS the casualty does not respond, start external chest compression
Kneel alongside the casualty facing the head. Place the heel of your hand on the centre of the lower part of the breastbone. Press down with the heel of your other hand and lock the fingers together. With arms straight press vertically down on the lower part of the breastbone to depress chest about 1.5 in. Do this 15 times at the rate of 80 per minute. Repeat the arms and give two ventilations. Repeat this 15 compressions and two ventilations for one minute and check for a pulse. If a pulse is restored, continue until normal breathing is restored.

● manual artificial ventilation method
If mouth-to-mouth ventilation is not possible or if there are several casualties the manual resuscitator should be used. Place the hands placed under the head. Turn the

doctor
phone
ambulance
phone
hospital
phone
nearest first aid
phone

Prepare with the assistance of the British Red Cross Society

Enclose with your name or a vertical one for your name. Pack backwards allowing for name and full address. The casualty's name just above the name of the person to be contacted. Have the name and full address written on the envelope. Repeat this for each casualty. After the exercise continue for 15 minutes.

WALLCHART 340 x 438mm
POCKET CARD 92 x 126mm

ELECTRICAL TIMES' FIRST AID CHARTS

To the Cashier, Business Press International Ltd., Sales and Distribution, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, England. Tel: 01-661 8438.

- Please send me:
- ... pocket cards at 70p each
 - ... paper charts at £1.00 each
 - ... card charts at £2.00 each
 - ... plastic charts at £3.00 each

I enclose cheque/money order for £..... payable to BUSINESS PRESS INTERNATIONAL LTD

Name _____
Address _____

BE READY TO SAVE LIFE. SOMEONE MIGHT SAVE YOU.

Co. Reg. No. 151537. Reg. Office: Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.



PRICES ARE SUBJECT TO ALTERATION. PLEASE CONTACT SALES DESK FOR CURRENT PRICES. AND BEST U.K. DELIVERY TIMES

CRICKLEWOOD ELECTRONICS LTD

40 CRICKLEWOOD BROADWAY LONDON NW2 3ET
01-452 0161/01-450 0995 Tlx:914977

This list contains only a fraction of CRICKLEWOOD'S stock. Please add 60p p&p & 15% VAT to all orders. Official orders from schools, colleges, Govt. Depts. etc. welcome.

RESISTORS	AXIALS (wires each/ind)	7491 7492 7493	7494 7495 7496	7497 7498 7499	7995 7996 7997	7998 7999 8000
------------------	--------------------------------	----------------------	----------------------	----------------------	----------------------	----------------------

IMMEDIATE DELIVERY - PHONE FOR LATEST PRICES

IMMEDIATE DELIVERY - PHONE FOR LATEST PRICES

4072	19p	10mp	40412	70p	BC338	15p	BFY50	23p	6amp type	SL480	2.99	Single sided
4073	19p	790957	40873	70p	BC440	32p	BFY51	23p	Square with hole	SL490	3.47	100 x 180 2.10
4074	19p	79121	40874	70p	BC441	32p	BFY52	23p	PW06 1000 95p	SN76003	2.95	100 x 220 2.50
4075	45p	79157	40875	70p	BC460	32p	BFY53	23p	PW02 1200 99p	SN76013	2.95	203 x 114 2.40
4076	45p	79247	40876	70p	BC461	32p	BFY54	23p	PW04 4000 130p	SN76023	2.95	233 x 220 2.50
4077	19p		40877	70p	BC462	32p	BFY55	23p	PW06 6000 139p	SN76033	2.95	Double Sided
4078	19p		40878	70p	BC516	40p	BSX21	40p	25amp type	TA7220	2.95	150 x 160 2.20
4079	19p		40879	70p	BC546E	15p	BU014	22p	Metal clad with hole	TA7221	2.95	100 x 200 2.80
4080	19p		40880	70p	BC547	15p	BU015	22p	RO11100 2.62	TA7222	2.95	203 x 114 2.90
4081	49p		40881	70p	BC556B	15p	BU018	3.95	K02 1200 2.75	TA7223	2.95	233 x 220 5.90
4082	19p		40882	70p	BC548	12p	BU020	1.75	NB21	TBA5000	3.1	1 above ldn
4083	49p		40883	70p	BC549	12p	BU021	1.75	NB22	TBA5010	3.1	use Sodium
4084	60p		40884	70p	BC548B	14p	BU022	1.75	NB23	TBA5100	3.05	Hydrexel
4085	49p		40885	70p	BC548C	14p	BU023	1.75	NB24	TBA5200	2.75	500ml
4086	49p		40886	70p	BC548D	14p	BU024	1.75	NB25	TBA5300	2.56	
4087	19p		40887	70p	BC548E	14p	BU025	1.75	NB26	TBA5500	2.77	
4088	19p		40888	70p	BC548F	14p	BU026	1.75	NB27	TBA5600	2.87	
4089	19p		40889	70p	BC548G	14p	BU027	1.75	NB28	TBA5700	2.74	
4090	19p		40890	70p	BC548H	14p	BU028	1.75	NB29	TBA5800	2.74	
4091	19p		40891	70p	BC548I	14p	BU029	1.75	NB30	TBA5900	2.74	
4092	19p		40892	70p	BC548J	14p	BU030	1.75	NB31	TBA6000	2.74	
4093	19p		40893	70p	BC548K	14p	BU031	1.75	NB32	TBA6100	2.74	
4094	69p		40894	70p	BC548L	14p	BU032	1.75	NB33	TBA6200	2.74	
4095	71p		40895	70p	BC548M	14p	BU033	1.75	NB34	TBA6300	2.74	
4096	71p		40896	70p	BC548N	14p	BU034	1.75	NB35	TBA6400	2.74	
4097	2.88p		40897	70p	BC548O	14p	BU035	1.75	NB36	TBA6500	2.74	
4098	74p		40898	70p	BC548P	14p	BU036	1.75	NB37	TBA6600	2.74	
4099	89p		40899	70p	BC548Q	14p	BU037	1.75	NB38	TBA6700	2.74	
4502	39p		4502	39p	BC548R	14p	BU038	1.75	NB39	TBA6800	2.74	
4503	39p		4503	39p	BC548S	14p	BU039	1.75	NB40	TBA6900	2.74	
4507	33p		4507	33p	BC548T	14p	BU040	1.75	NB41	TBA7000	2.74	
4508	1.26		4508	1.26	BC548U	14p	BU041	1.75	NB42	TBA7100	2.74	
4510	4.4p		4510	4.4p	BC548V	14p	BU042	1.75	NB43	TBA7200	2.74	
4511	4.4p		4511	4.4p	BC548W	14p	BU043	1.75	NB44	TBA7300	2.74	
4512	4.4p		4512	4.4p	BC548X	14p	BU044	1.75	NB45	TBA7400	2.74	
4513	1.3		4513	1.3	BC548Y	14p	BU045	1.75	NB46	TBA7500	2.74	
4514	1.3		4514	1.3	BC548Z	14p	BU046	1.75	NB47	TBA7600	2.74	
4515	1.3		4515	1.3	BC548AA	14p	BU047	1.75	NB48	TBA7700	2.74	
4516	5.5p		4516	5.5p	BC548AB	14p	BU048	1.75	NB49	TBA7800	2.74	
4518	3.9p		4518	3.9p	BC548AC	14p	BU049	1.75	NB50	TBA7900	2.74	
4519	2.9p		4519	2.9p	BC548AD	14p	BU050	1.75	NB51	TBA8000	2.74	
4520	4.8p		4520	4.8p	BC548AE	14p	BU051	1.75	NB52	TBA8100	2.74	
4521	6.8p		4521	6.8p	BC548AF	14p	BU052	1.75	NB53	TBA8200	2.74	
4526	6.8p		4526	6.8p	BC548AG	14p	BU053	1.75	NB54	TBA8300	2.74	
4527	6.2p		4527	6.2p	BC548AH	14p	BU054	1.75	NB55	TBA8400	2.74	
4528	74p		4528	74p	BC548AJ	14p	BU055	1.75	NB56	TBA8500	2.74	
4529	6.8p		4529	6.8p	BC548AK	14p	BU056	1.75	NB57	TBA8600	2.74	
4534	3.9p		4534	3.9p	BC548AL	14p	BU057	1.75	NB58	TBA8700	2.74	
4536	2.9p		4536	2.9p	BC548AM	14p	BU058	1.75	NB59	TBA8800	2.74	
4538	7.8p		4538	7.8p	BC548AN	14p	BU059	1.75	NB60	TBA8900	2.74	
4539	8.9p		4539	8.9p	BC548AO	14p	BU060	1.75	NB61	TBA9000	2.74	
4543	6.8p		4543	6.8p	BC548AP	14p	BU061	1.75	NB62	TBA9100	2.74	
4545	2.25		4545	2.25	BC548AQ	14p	BU062	1.75	NB63	TBA9200	2.74	
4555	3.5p		4555	3.5p	BC548AR	14p	BU063	1.75	NB64	TBA9300	2.74	
4556	3.5p		4556	3.5p	BC548AS	14p	BU064	1.75	NB65	TBA9400	2.74	
4560	1.9p		4560	1.9p	BC548AT	14p	BU065	1.75	NB66	TBA9500	2.74	
4566	1.4p		4566	1.4p	BC548AU	14p	BU066	1.75	NB67	TBA9600	2.74	
4569	1.65		4569	1.65	BC548AV	14p	BU067	1.75	NB68	TBA9700	2.74	
4570	3.9p		4570	3.9p	BC548AW	14p	BU068	1.75	NB69	TBA9800	2.74	
4585	5.5p		4585	5.5p	BC548AX	14p	BU069	1.75	NB70	TBA9900	2.74	

40412	70p	BC338	15p	BFY50	23p	6amp type	SL480	2.99	Single sided
40873	70p	BC440	32p	BFY51	23p	Square with hole	SL490	3.47	100 x 180 2.10
40874	70p	BC441	32p	BFY52	23				

CIRCUIT MODELLER for CP/M

by Harcourt Systems

An engineering package for CP/M* and MS DOS* microcomputers to carry out accurate, fast designs of linear circuits.

CIRCUIT MODELLER can find voltage gain, phase shift, Z_{in} and Z_{out} for most linear electrical and electronic circuits. The limits of capacity are set by the microcomputer RAM, which must be at least 60 KBytes. This gives a capacity of 32 nodes, 101 resistors, 101 capacitors, 101 inductors, 31 mutual inductors, 31 simple operational amplifiers and 31 controlled sources.

Features include:

- ADD & EDIT** to construct and alter circuit
- LOAD & SAVE** to save and recover circuit from disk
- GAIN** to display gain and phase
- ZIN** to display input and output impedances
- BW** to find centre frequency and $-3dB$ Av points of circuit
- SEARCH** to find frequency corresponding to given gain
- PRINT** to print synopsis of circuit diagram sufficient for its precise reproduction.

Operating Speed

CIRCUIT MODELLER is an all-compiled package with seven overlays in which the inner two loops of pivotal condensation are written in Z80 assembler. This means that whereas microcomputer CAD is usually slow, **CIRCUIT MODELLER** can solve a four hybrid-pi amplifier in a few seconds.

Graphics

PLOT is an extension to **CIRCUIT MODELLER** enabling an ordinary 132 column printer to plot both dB gain and phase angle against frequency for the circuit. A log/log plot is obtained with automatic axis scaling.

Themselves designers of high performance electronic equipment, Seasim Controls have recognised the importance of **CIRCUIT MODELLER** which they are making available in association with Harcourt Systems. **CIRCUIT MODELLER** is priced at £160+VAT. Prices for MS DOS on application. Order, or send for more details from


SEASIM CONTROLS LIMITED

The Paddocks, Frith Lane, Mill Hill, London NW7 1PS

Telephone: (01) 346 9271 - Telex: 21189

*CP/M is a trademark of Digital Research

*MS DOS is a trade mark of Microsoft

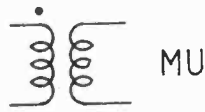

MU




R




L




C

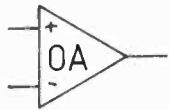

CS

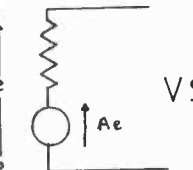

VS

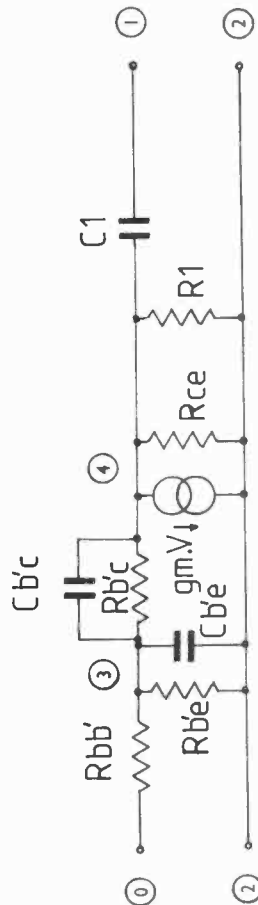

BULK PURCHASE BARGAINS CAPACITORS

AXIAL		Price each per 100	Price each per 1K	Price each per 10K	RADIAL		Price each per 100	Price each per 1K	Price each per 10K
Value/Volts	Qty.				Value/Volts	Qty.			
100/10	89000	0.07	0.04	.025	47/10	3600	0.04	0.03	
220/10	5000	0.08	0.05		330/10	69500	0.05	0.03	0.02
2200/10	10000	0.19	0.10	0.07	1000/10	7400	0.08	0.05	
4700/10	4000	0.32	0.20		33/16	47000	0.04	0.03	0.02
100/16	4000	0.07	0.04		33/25	19600	0.04	0.025	0.02
470/16	400	0.11			330/25	3000	0.07	0.05	
47/40	9000	0.09	0.05		100/40	9200	0.06	0.04	
100/40	2500	0.11	0.07		47/40	3000	0.05	0.03	
150/40	7000	0.11	0.07		100/63	23400	0.11	0.07	0.05
4700/40	400	0.55			2.2/100	2800	0.03	0.02	
4.7/50	2800	0.05	0.03		330/40	850	0.09	0.05	
3.3/63	1400	0.06	0.04		22/100	1900	0.05	0.03	
4.7/63	300	0.06	0.04		220/100	8400	0.18	0.11	
.47/63	6000	0.04	0.025		47/160	1000	0.12	0.07	
1000/63	450	0.32			10/200	1000	0.04	0.025	
100/100	450	0.15			47/250	1500	0.05	0.03	
1/160	2000	0.05	0.025		4.7/450	550	0.03		
10/160	18000	0.08	0.05	0.04	CERAMICS				
4.7/450	4000	0.07	0.045		10pf	24000	All one price		
22/500	1500	0.05	0.04		39pf	56000			
4.7/500	350	0.06			47pf	118000	£10 per 100		
470/6.3	900	0.11			20pf	16000	£25 per 10K		
1/250	1000	0.07			51pf	100000	£125 per 100K		
CERAMIC FILTERS					33pf	48000			
10.7 Mhz	15000	0.15	0.10	0.05	120pf	16000	Any mix		
INDUCTORS					12pf	16000			
82µH	35000	0.15	0.10	0.05	6800pf	36500			
33µH	16000	0.15	0.10	0.05	4700pf	6000			
					120pf	1800			
					150pf	75000			
					15pf	40000			
					12pf	16000			
					68pf	20000			
					22pf	2000			
					39pf	5000			
					47pf	14000			

All components are new and boxed. Carriage additional. All prices exc. V.A.T.

TIMEBASE

94 ALFRISTON GARDENS, SHOLING, SOUTHAMPTON SO2 8FU
TEL. 431323 (0703)

Callers welcome


Access, Barclaycard. Telephone your order



WW 088 - FOR FURTHER DETAILS

P. F. RALFE ELECTRONICS

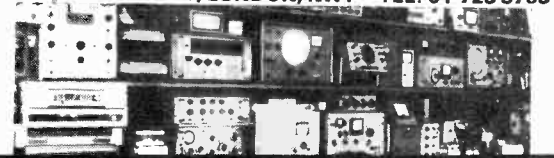
10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753



'OSCILLOSCOPES'

PLEASE PHONE FOR CURRENT STOCK

TEKTRONIX 453. Dual-trace 50MHz.
 TEKTRONIX 565. Dual time-base. Differential plug-ins.
 SOLARTRON CD1740. 50MHz sweep-delay £350.
 MARCONI TF2210 Dual-trace, 100MHz, sweep-delay £350.
 MARCONI TF2604 Electronic Multi-Meter
 MARCONI TF893A Audio Power Meters £85.
 MARCONI TF2502 3F Power Meters. DC-1GHz. 10w fsd £350.
 MARCONI TF2701 In-Situ Universal Component Bridge £250.
 MEGGER-5KV Insulation Tester. Hand-crank.
 MARCONI TF2343A Quantization Distortion Meter £150.
 HEWLETT-PACKARD 3450A Multi-Function Digital Multi-Meter.
 ROHDE & SCHWARZ 'SDR' AM Signal Generator 0.3-1GHz.
 TEKTRONIX 2901 Time-mark Generator.
 GOULD J3B Signal Generator £150.
 ROHDE & SCHWARZ Resonance Frequency Meter 470MHz-2.5GHz.
 HEATHKIT AW1U Audio Power Meters 5mW-50W £25 pp £1.
 METROHM 500V Insulation Testers Transistorised £40 pp £1.50.
 BRUEL & KJAER Heterodyne Voltmeter 0.5-240MHz.
 AIRMEC Display Oscilloscope 279, 4-trace, 14x10" CRT £195.
 RIKADENKI 3-channel Chart Recorder, Model B-341.

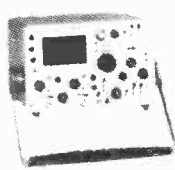

★ AVO SIGNAL GENERATORS AFM2 ★

We have in stock a quantity of AVO type AFM2 signal generators supplied in fully tested working condition complete with accessories. Spec as follows: 0.45MHz-225MHz in 8 bands. AM all bands plus FM on two bands covering 20-100MHz. Output 1uV-50mV and 200mV High D/P setting, m/c set level meter, scale shift for accurate frequency calibration, variable mod etc. PRICE EACH JUST £55 + VAT. Carriage each + £4.



★ SWEEPERS ★

TELEONIC Sweep generator system type 2003. Fitted with Marker, attenuator, Detector plug-in units and Generator covering 800-1500MHz. £325

★ MUIRHEAD FACSIMILE UNITS ★

MUFAX 'COURIER' facsimile receiver type K441-CH and transmitters K400 AMCH in stock in excellent condition £250 per pair.

PLEASE NOTE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months' guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES.

★ COMPUTER PERIPHERALS ★

8" FLOPPY DISK DRIVES

DRE (Data Recording Equipment) Model 7100 Single-sided floppy disk drives in stock now at vastly reduced prices. Supplied BRAND NEW in manufacturers sealed cartons. CAPACITY 0.8MBytes. Hard/Soft sectoring ANSI/ECMA Standards compatible. Measures 4 1/2 x 8 1/2 x 14". Weight 13lbs. PRICE £150 + VAT. Securicor despatch if required + £10 + VAT. 7200 (Double-sided) £250

8" WINCHESTER DRIVES

United Peripherals type 3100 Minidisk Drives CAPACITY over 19MBytes. Power supply requirements 5V DC at 4A. +24V DC at 3A. Measures 17 x 8 x 7". Limited quantity only available in BRAND NEW condition. £250 each + VAT. Carriage details as above.

4000-SERIES HARD DISK DRIVES

Data Recording Equipment 4000-Series exchangeable IBM-type 5440 Disks. Units available ex-stock and BRAND NEW. Please call us for our lowest ever quotation.

★ DISK CARTRIDGES ★

Surplus BASF 12-Sector RK05 cartridges available in small quantity only remaining at £15 each. Carriage each £1.50.

★ SWITCHING POWER SUPPLIES ★

The following DC power supplies are available now from stock in limited quantities. All fully tested and guaranteed.
 3.5V @ 10 Amps £15 5V @ 10 Amps £15
 5V @ 20 Amps £20 5V @ 40 Amps £30
 5V @ 60 Amps £40 19V @ 30 Amps £40
 +15V, -12V +5V @ 11A, 4A and 40A £50
 All prices + VAT please. Carriage + £2 each

★ CENTRIFUGAL BLOWERS ★

'TORIN' Type U62B1. 230V Cap'Start (supplied), very powerful (200W, 3,000rpm) centrifugal fans for large rack cooling or enclosure extraction applications. Overall dimensions 20x12 cms, outlet 6x4 cms. BRAND NEW. Surplus stock. £15 each inc. VAT, pp £1.50.

★ ROTRON INSTRUMENT COOLING FANS ★

Supplied in fully tested excellent condition, as follows:
 115V, 4 1/2 x 4 1/2 x 1 1/2" £5. 230V same size £5.50.
 115V 3 x 3 x 1 1/2" £4. 230V 3" size, brand new £6. Also small quantity 115V 4 1/2" size, brand new £6. Postage each + 50p please. ww10

MARCONI SIGNAL GENERATORS

TF2002A/S (illustrated) 10kHz-72MHz AM/FM. £750
 TF2002. As above but AM only. £450
 MARCONI TF1066B. AM/FM Generator. 10-470MHz. 0.2uV-200mV output. FM Deviation up to ±100kHz.
 MARCONI TF995A/S. AM/FM Generator. Narrow deviation model 995 covering 1.5-220MHz. £450.
 TF2015. 10-520MHz AM/FM. TF144H. AM 10kHz-72MHz £295.
 MARCONI TF1064B/S. AM/FM Signal generator covering in three ranges 68-108, 118-185 and 450-470MHz. FM fixed deviations of 3.5 & 10kHz. AM fixed 30%. £225

★ 'DOLBY' NOISE WEIGHTING FILTERS ★

Cat. No. 98A. Noise weighting filters for CCIR/ARM signal-to-noise ratio measurements. As new units. £40 each (+£1 p&p).

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.

RFI RECEIVER

Stoddart Model NM52A. RF Noise & Field intensity measuring receiver. 375MHz-1GHz c/w power supply unit.

KAY SOUND SPECTROGRAPH

Model 6061B with Amplitude Display, scale magnifier. 85Hz-16kHz. Complete sound spectrograph in excellent condition.

★ STEPPER MOTORS ★

Brand new stock of 'ASTROSYN' Type 20PM-A055 stepper motors. 28V DC. 24 steps per rev. 15 oz-in torque @ 100PPS. Body length 2 1/2", diameter 2", shaft 1/4" diam x 4 1/2" spirally threaded. Weight 16oz. Price each £15 (p&p 50p). Connections supplied.

★ MULTI-VOLT MEASUREMENT, ANALOGUE ★

MARCONI TF2600. Twelve ranges 1mV-300V FSD. Wide-band to 10MHz.
 MARCONI TF2603. Frequency range 50kHz-1.5GHz. High Sensitivity from 300uV.
 MARCONI TF2604. Electronic Multi-meter. AC/DC 300mV Full scale to 300V (1kV DC). Resistance ranged. AC Frequency range 20Hz-1500MHz.

★ CONSTANT VOLTAGE TRANSFORMERS ★

'ADVANCE VOLSTAT'; Type. Model MT140A. Mains input 190-260V AC. Output 230V AC @ 150W. Price each £20 + VAT + £2 carriage.

WW - 059 FOR FURTHER DETAILS

Gateways to the World Outside

The CST PROCYON opens a lot of doors to your BBC microcomputer - lifting it right out of the "home computer" league. The CST PROCYON provides full IEEE 488 interface, enabling your BBC micro to operate professional plotters and printers, frequency counters, voltmeters, disc drives etc, and to communicate with other IEEE-ported machines, such as Commodore, Sirius, Osborne, Hewlett-Packard or Tectronix computers.

The CST PROCYON comes with a highly efficient IEEE filing system, supplied in EPROM, and responds to any high level language, including LISP, FORTRAN, FORTH, APL and BASIC. A specially-written Commodore data-exchange routine, allows you to link your BBC micro to CBM machines and disc drives.


At 70k bytes of information per second, the CST PROCYON channels data quickly and efficiently between up to sixteen devices, responding to standard system commands as well as specialised filing instructions. Its capabilities are fully documented in a straightforward but comprehensive manual.

Isn't it time you started taking your BBC micro seriously?

- Full multiple controller implementation
- Extensive "HELP" facilities
- Interactive debugging
- Visual Display of operating status
- Internal switched and socketed power supply
- Comprehensive error checking and indicating

The CST PROCYON from
 Cambridge Systems Technology
 30 Regent Street, Cambridge
 Tel: (0223) 323302

ENQUIRIES FROM DEALERS WELCOME

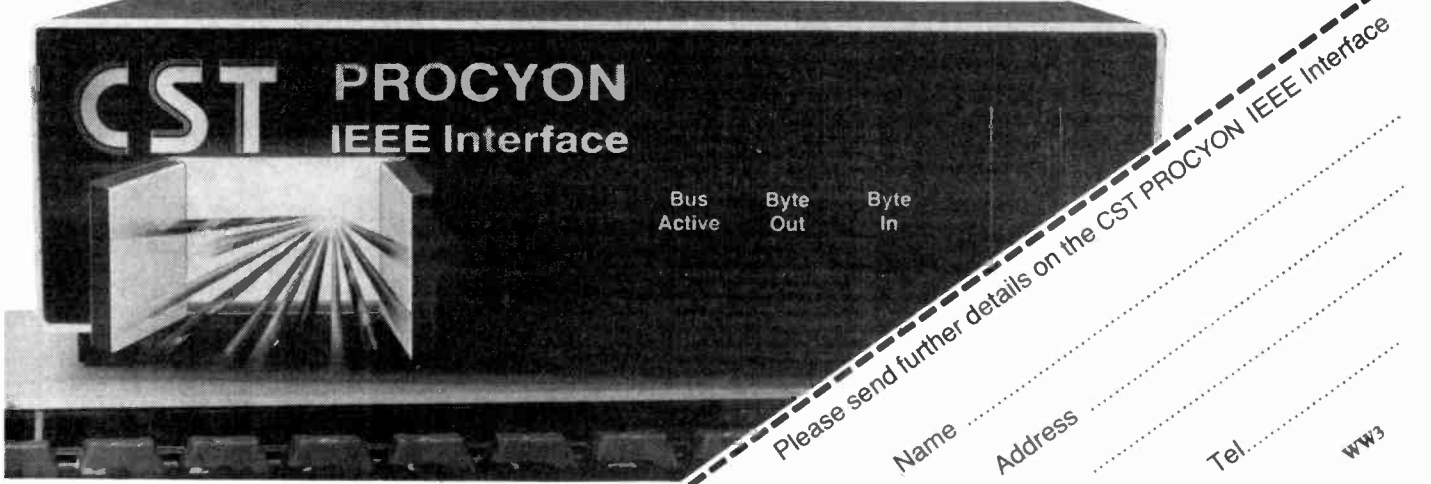

WW - 069 FOR FURTHER DETAILS

Modem Filters

INDUSTRY STANDARD

New Low Prices in OEM Quantities From Stock

- R5630** Full-duplex 300 baud, 103 compatible filter in 16 pin DIP.
- R5631** Full-duplex 200/300 baud, V.21 CCITT compatible filter in 16 pin DIP, pin-for-pin compatible with R5630.
- R5632** Full-duplex 1200 baud, 212/V.22 combo filter.
- R5633** General purpose programmable filter array for full-duplex 103, V.21, DTMF and Videotex.
- R5626** Mask programmable to your specification.

Reticon also provides a wide variety of other standard and specialised custom filters and signal processing devices using Reticon's proven NMOS Switched-Capacitor Technology.

Contact us on your needs at Chicago (312) 640-7713; Boston (617) 745-7400; Japan 03-343-4411; England (0734) 790 7722; Germany (089) 918-060.

Head Office: EG&G Reticon, 345 Potrero Avenue, Sunnyvale, California 94086 (408) 738-4266; TWX 910-339-9343.



34/35 MARKET PLACE, WOKINGHAM, BERKSHIRE RG11 2PP
Telephone: Wokingham (0734) 788666 Telex: 847510 EGGUK


WW - 086 FOR FURTHER DETAILS

Valradio

DC-AC Inverters
(30W up to 1kW)
sine wave or square
wave output
AC-DC power units
Frequency
changers
Emergency
standby
systems
No-break
systems
Crystal
controlled
units

POWER UNITS

NOW AVAILABLE
WITH 3 VARIABLE
OUTPUTS

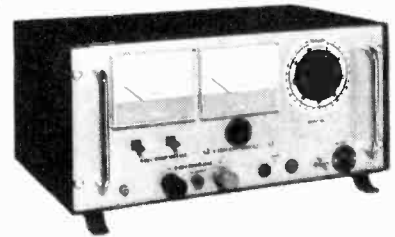

Input 200-250V. 50Hz or 100-120V
60Hz to order.
Output 1:0-30V. 25A. D.C.
Output 2:0-70V. 10A. A.C.
Output 3:0-250V4A. D.C.

ALL CONTINUOUSLY VARIABLE

Other units are also available
with outputs of:

0-60V 12A
0-120V 6A
0-240V 3A

SERVICING
EDUCATION
DEVELOPMENT
PRODUCTION
TESTING

SEND FOR FURTHER DETAILS
OF THESE VERSATILE UNITS
TO

Valradio POWER LIMITED
A.K. INTERNATIONAL BUILDING
LAWRENCE ESTATE, GREEN LANE
HOUNSLOW, MIDDX. TW4 6DU
ENGLAND 01-570 5622

WW - 078 FOR FURTHER DETAILS

Lynwood GD1 VDUs: Intelligent Green micro controlled, RS232, printer port, 101 key k/b. Full Video enhancements. ONLY £149 + £15 P&P (S/H)
Burroughs MT686/7/TD710: Intelligent Green 12" VDU with 3 micros and 64K store. RS232. Programmable. Only £199 new or £149 S/H + £15 P&P
Videocom Apollo VDUs: Stylish 15" Green Z80 controlled VDU with printer port and lots of very advanced features. Only £399 new or £249 S/H + £15 P&P
Centronics 306 Line printers: Professional fast (120 cps), superb quality, 80 column printer. Parallel i/f. ONLY £149 + £17.50 P&P
Computhink Act 800 Computer system. Dual floppies (2.4Mb) with Qume Sprint daisywheel and lots of business software ONLY £1,200.
Diablo 630 Daisywheel printer. RS232, NEW £599 + £15 P&P.
Diablo Hitype 2 Daisywheel, Tractor unit, S/H £399 + £15 P&P



BECKENHAM PERIPHERALS LTD

Callers welcome
by appointment

01-778 3600
124 Lennard Road, Beckenham
Kent BR3 1QP

SAE for LIST
and enquiries

WW - 009 FOR FURTHER DETAILS

Mfrs.	Device	Price	Mfrs.	Device	Price
OPCDA	OPB 815 OPTO each.....	£1.00	ITT	937 50 DTL GATE CER.....	£0.20
LMDA	PMD 11K 80 Power Dar- lington each.....	£1.00	ISKRA	47pf 160V Polystyrene per 200.....	£2.00
TI	2S 103NPN TO 18 KILSPEC each.....	£1.00	TCSF	470pf 50V DISC CER per 1000.....	£10.00
MUL	RW 153P each.....	£5.00	ITT	3300pf 500V DISC CER per 1000.....	£10.00
TI	2N 1302 NPN GE T05 each.....	£0.48	MUL	344 0.022mf 400V Poly- ester per 250.....	£5.00
GE	2N 2711 PNP S/Signal each.....	£0.06		0.1mf 400V Polyester Ax per 100.....	£2.50
TI	2N 5450 Small Signal each.....	£0.05	PLESSEY	0.47mf 250V 'X' Radial Poly each.....	£0.25
TI	2N 5838 NPN Power T03 each.....	£1.00		10mf 25V Bead Tant per 100.....	£10.00
M&T	MC 14433 each.....	£5.00	LORLIN	10000mf 40V Comp Grade each.....	£2.00
TCSF	27pf 63V CER Plate per 1000.....	£10.00			


LARGER QUANTITIES QUOTED BY RETURN
All good, brand-new and perfect
48-hour Service : C.W.O. to:

AC/DC Electronic Components
Dept. WW, 43 Church Street, Enfield, Middlesex

WW - 081 FOR FURTHER DETAILS

ambit INTERNATIONAL

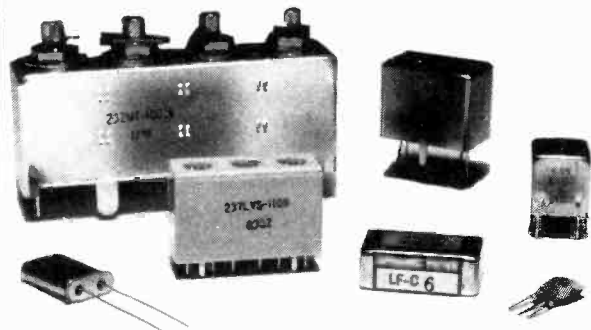PRACTICALLY ALL THE WIRELESS PARTS YOU'LL EVER NEED, GATHERED TOGETHER IN ONE CATALOGUE...




Coils, crystals, filters

TOKO coils, filters chokes. UNI crystals, filters, NTK and Murata ceramic filters. Probably the broadest stock ranges of these types of component in the world, and a full service from AMBIT INDUSTRIAL MARKETING to support the OEM with custom requirements.

Semiconductors for radio communications

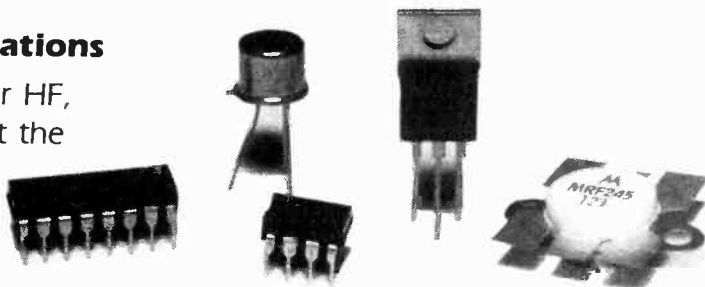
ICs, Varicaps, FETS, MOSFETS, RF Power for HF, VHF, UHF. A broad selection that will meet the majority of requirements in receiver and transmitter designs



High Performance Coax Relays, switches etc. PC and connector relays engineered to the highest standards, plus a broad range of electro-mechanical support including push, toggle, and keyboard switches, rotary switches, plugs sockets etc.

Test Gear and Tools

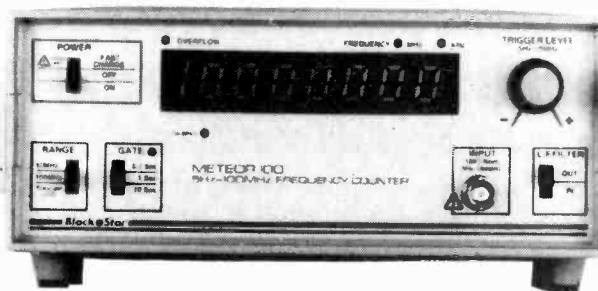New Black Star Frequency counters, Weller and Antex soldering tools, plus a wide selection of all types of equipment and tools for home and work.



Communications Technology

for the enthusiast
(and professional)

200 North Service Road, Brentwood, Essex CM14 4SG
Tel: Consumer (0277) 230909. Industrial (0277) 231616
Telex: 995194 AMBIT G.
Data: (0277) 232628 REWTEL» (300 baud duplex)

★ **REGIONAL SALES COUNTERS**
Solent Component Supplies, 53 Burrfields Road,
Portsmouth
Broxlea, Park Lane, Broxbourne, Herts

★ **SPRING CATALOGUE**
Parts, Project Packs, Test Gear
Info and 3 x £1 discount vouchers!
ORDER NOW for FEB Shipment — 80p



WW - 084 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Tuesday, March 6, for April issue subject to space available.

DISPLAYED APPOINTMENTS VACANT: £17 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £3.50 per line, minimum £25 (prepayable).
BOX NUMBERS: £5 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS).
PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to BUSINESS PRESS INTERNATIONAL LTD. and crossed.



ALWAYS AHEAD WITH THE BEST!

£7,000-£20,000

- ★ **Where does your interest lie:** Communications; Computers; Weapons; Radar; Sonar; Data-Comms; Signal Processing; Medical; Telemetry; Simulation; Satcom; Local Area Nets; ATE?
- ★ **Experienced in:** Microprocessor Hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ **There are hundreds of opportunities in:** Design; Test; Sales and Service for Engineers and Managers
- ★ **Act now:** Just call **0763 84676/7** (until 8 p.m. most evenings)

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
 Freeport, Barkway, Royston, Herts SG8 8BR

(1926)

Applications Engineering (Dolby Stereo sound consultant)

Dolby Laboratories Inc. require a young sound engineer with solid technical background and the ability to deal with people. Practical experience as a mixing or recording engineer is essential. A foreign language would be useful. Based in London with some international travelling.

Competitive salary according to experience and good general benefits.

Apply in writing to John Iles.

Technician

With audio experience, probably City and Guilds electronics or similar education. Ability to work without day-to-day supervision is important for this in-house position within the marketing department.

Competitive salary according to experience and good general benefits.

Apply in writing to David Watts.



Dolby Laboratories Inc.
 346 Clapham Road
 London SW9 9AP
 Tel No. 01-720 1111

(2457)

London College

ilea of

Furniture

HEAD OF DEPARTMENT OF MUSICAL INSTRUMENT TECHNOLOGY (BURNHAM GRADE IV)

Applications are invited for the above post. The position demands an appropriately qualified person in the field of music and instrument making, coupled to organisational ability and an understanding of the developments in further and higher education. The College's Department of Musical Instrument Technology has become a unique establishment, offering an expanding range of advanced and non-advanced courses in instrument making validated by BTEC and the City and Guilds.

Salary: On an incremental scale within the range of £14,148 - £15,849 plus £987 Inner London Allowance.

Further details and application forms are available from The Clerk of the Governors at the College.

LONDON COLLEGE OF FURNITURE
 41/71 Commercial Road, London E1 1LA. Tel: 01-247 1953
 ILEA is an equal opportunities employer.

Box number replies should be addressed to:

Box No.....
 c/o Wireless World
 Quadrant House
 The Quadrant
 Sutton, Surrey, SM2 5AS

AN OPPORTUNITY FOR SELF-EMPLOYED ENGINEERS

We have a steady flow of customers seeking repairs to Hi-Fi, Radio, TV and Video equipment.

If you offer a service in London in these fields call:

MR PATTERSON
242 4000

(2465)

TARGET CHARACTERISTICS

CHARACTERISTICS OF ENVIRONMENT

SYSTEM FEATURES

HARDWARE PARAMETERS

SIGNAL PROCESSING

COMPUTATION

Progress your career as a

SYSTEMS OR HARDWARE ENGINEER
in the development of high technology

ELECTRONIC WEAPON SYSTEMS to £17.5k

Our client is able to offer you unequalled opportunities to further your career if you have a Degree/HNC qualification and experience of radar, missiles, underwater systems, avionics, control systems or mathematical modelling. This is because this highly successful, progressive company is growing more rapidly than any other company in the defence industry today. Their constantly expanding product range includes total defence and weapons systems as well as intelligent weapons and electronic countermeasures.

The majority of products are at an early stage of development and many are PV funded. Your technical knowledge would be fully utilised and expanded because, in order to retain technical supremacy, our client has a policy of ensuring that the latest and most effective technology is embodied in its products. You would work in a fast moving environment and would have access to first-class CAD, computing and VLSI facilities.

The company recognises that to maintain its position of world leadership it relies above all else on the excellence of its engineering staff and this is reflected in a highly attractive package of rewards and conditions, including generous assistance with relocation where appropriate and **starting salaries of up to £17,500.**

As a Systems Engineer you could be involved with Electronic Sub-systems in respect of one or more of the following: theoretical studies; computer simulation and mathematical modelling; performance evaluation; algorithm development; the assessment and analysis of weapon and hardware performance.

As an Electronic Design/Development Engineer you could be involved with either digital or analogue design in the early development of equipment. The equipment can involve novel advanced transducer techniques; sophisticated signal processing; advanced microprocessor technology; recording & instrumentation; power conditioning for high power densities and high efficiency; VLSI and high density packaging.

To find out more and to obtain an early interview please telephone FRED JEFFRIES, C.Eng., M.I.E.R.E. in complete confidence on Hemel Hempstead (0442) 212655 during office hours or one of our duty consultants on Hemel Hempstead (0442) 212650 evenings or weekends. Alternatively write to him at the address below.



Executive Recruitment Services

THE SPECIALISTS IN RECRUITMENT FOR THE ELECTRONICS COMPUTING AND DEFENCE INDUSTRIES

29-33 Bridge Street, Hemel Hempstead, Herts., HP1 1EG.

(2473)

Electronics Engineers

£9561

Communications Design in High Tech Country

At H.M. Government Communications Centre we're using the very latest ideas in electronics technology to design and develop sophisticated communications systems and installations for special Government needs at home and overseas.

With full technical support facilities on hand, it's an environment where you can see your ideas progress from initial concepts through prototype construction, tests and evaluation, to the pre-production phase, with a chance to influence every stage. Working conditions are pleasant, the surroundings are attractive, and the career prospects are excellent.

Ideally we're looking for men and women who have studied electronics to degree level or equivalent and have had some experience of design, whether obtained at work or through hobby activities. Appointments will be made as Higher Scientific Officer (£7149-£9561) or Scientific Officer (£5682-£7765) according to qualifications and experience.

For further details please write to the address given below. As our careful selection process takes some time, it would be particularly helpful if you could detail your qualifications, your personal fields of interest and practical experience, and describe the type of working environment most suited to your career plans.

The Recruitment Officer, HMGCC, Hanslope Park, Buckinghamshire MK19 7BH.

(2448)

Appointments

Antenna Test Specialists

The Satellite Division of Marconi Space and Defence Systems is about to commission the UK's most advanced satellite test facilities. There is an immediate requirement for an Antenna Range Test Superintendent and for an Antenna Test Systems Supervisor

The Superintendent will institute test runs and be responsible for range personnel, test procedures, safety, the integrity of test equipments, and will also contribute to the development of the test range facility. Applicants should have an HNC as a minimum qualification and at least 5 years experience of R.F. and antenna testing utilising computer based systems.

The Supervisor will be responsible to the Range Superintendent for the implementation of test runs and generally contribute as a member of the range test team. Applicants for this should possess ONC in electronics plus at least 3 years computer based test experience of R.F. equipments.

Appropriate salaries and other attractive benefits form a first-class package anticipated from a large market-leader employer.

Telephone Portsmouth (0705) 674019 for an application form or write direct to Derek Withers, Marconi Space and Defence Systems Limited, Browns Lane, The Airport, Portsmouth, Hants PO3 5PQ quoting reference BL 152.

(All posts are open to men and women)

Marconi
Space & Defence Systems



(2458)

WANDSWORTH HEALTH AUTHORITY

Atkinson Morley's
Hospital: Department
of Medical Physics

ELECTRONICS TECHNICIAN

A technician is required to design, build and develop microprocessor-based instruments including both associated hardware and software.

The person appointed will join a small team of scientists and technologists providing a service to Atkinson Morley's Hospital and to other Hospitals in the District and Region.

Educational standard will be at least H-TEC or HNC with a minimum of five years' appropriate experience, including work with microprocessors. The appointment will be in the grade of Medical Physics Technician II.

The starting salary will be £8,009, with increments up to a maximum of £9,835 including London Weighting. Post available from April 1984.

For further information please contact Ian Eversden, Principal Physicist.

Application form and job description available from:

Hospital Administrator
Atkinson Morley's Hospital
Copse Hill, Wimbledon
London SW20. Tel: 01-946 7711
(2479)

Electronic Opportunities !

- ★ RF and DIGITAL DESIGN
- ★ ATE APPLICATIONS
- ★ SALES and MARKETING
- ★ TEST and REPAIR

For details of these and our many other permanent and contract vacancies apply to:

D M Technical Services
13 Station Approach
Northwood
STD: 09274 21622

(2489)

PICCADILLY RADIO seeks an ENGINEER

Qualified to HNC/HND to perform varied tasks in a friendly and challenging environment. No broadcasting experience required - training will be given. Good salary, shift allowance and bonus.

Apply:
Chief Engineer, Piccadilly Radio
P.O. Box 261, Manchester

Piccadilly Radio - An Equal
Opportunities Employer (2449)

CAPITAL APPOINTMENTS LTD

THE UK's No. 1 ELECTRONICS AGENCY

If you have HNC/TEC or higher qualifications and are looking for a job in design, test, customer service, technical sales or similar fields:

Telephone now for our free jobs list
We have vacancies in all areas of the UK
Salaries to £15,000 pa

01-637 5551 or 01-636 9659
(24 hours)

CAPITAL APPOINTMENTS LTD
29-30 WINDMILL STREET, LONDON W1P 1HG

(291)

UNIVERSITY OF ABERDEEN

Department of Bio-Medical Physics and Bio-Engineering

ELECTRONIC ENGINEER or PHYSICIST

of practical bent required in department of international reputation, to maintain electronic imaging equipment containing computers, particularly two X-ray CT Scanners in modern teaching hospital. Training will be provided.

Salary within Grade 1A Scale for Other Related Staff, £7,190 - £11,615 per annum, depending on qualifications and experience.

Further particulars and application forms from The Secretary, The University, Aberdeen with whom applications (2 copies) should be lodged by 15 March 1984. (2461)

ELECTRONIC ENGINEERS

Due to promotion, two Electronic Engineers, qualified to a minimum of HNC level, are required for our Electronic Maintenance Department.

Electronic Maintenance

One opportunity is to join the section responsible for repair to component level of studio broadcast equipment, including Video Switching and Processor Systems, Field Synchronisers, Telecine and Cameras. Applicants should be familiar with colour television technology and have experience in fault finding on analogue, digital or microprocessor based hardware.

Routine Maintenance

The second vacancy is within a team which ensures that the Industry Code of Practice is met through a comprehensive policy of measurement and routine maintenance of the electronic broadcast systems on the station. Test engineering experience on such systems with a television company or equipment manufacture is essential.

Starting salaries will be in a range up to £13,000, depending on qualifications and experience, plus overtime payments.

Applications in writing to:

Personnel Officer (Recruitment)
Yorkshire Television Limited
The Television Centre, Leeds LS3 1JS

(2475)

YORKSHIRE TELEVISION

VIDEO ENGINEERS

Rediffusion Consumer Manufacturing Ltd is seeking an intermediate and a senior video engineer with OND, HND or similar qualifications, together with a knowledge of modern consumer electronics circuitry techniques, to join a small team looking after Rediffusion's mammoth investment in domestic video recorders and video disc players.

In addition to analysis of performance and long term reliability factors, assessment reporting is an important part of the team's function and the ability to express oneself verbally and in writing is essential. Our laboratories are situated at Chessington within easy commuting distance of the Surrey countryside. Attractive salaries and the usual big company benefits, which include assistance with relocation expenses, are offered to suitably qualified and experienced engineers. If you believe you can make a significant contribution to our video projects please write to or phone:-

Harry Brearley,
Rediffusion Consumer Manufacturing Ltd.,
Fullers Way South,
Chessington, Surrey. KT9 1HJ.
Telephone: 01-397-5411.

REDIFFUSION

(2407)

Advanced telecommunications:

careers with extensive scope at Cheltenham

Join the Government Communications Headquarters, one of the world's foremost centres for R & D and production in voice/data communications ranging from HF to satellite - and their security. Some of GCHQ's facilities are unique and there is substantial emphasis on creative solutions for solving complex communications problems using state-of-the-art techniques including computer/microprocessor applications. Current opportunities are for:

Telecommunication Technical Officers

Two levels of entry providing two salary scales: £6262-£8580 & £8420-£9522

Minimum qualifications are TEC/SCOTEC in Electronics/Telecommunications or a similar discipline or C & G Part II Telecommunications Technicians Certificate or Part I plus Maths B, Telecommunication Principles B and either Radio Line Transmission B or Computers B or equivalent: ONC in Electrical, Electronics or Telecommunications Engineering or a CIE Part I Pass, or formal approved Service technical training. Additionally, at least four years' (lower level) or seven years' (higher level) appropriate experience is essential in either radio communications or radar, data, computer or similar electronic systems. At the lower entry level first line technical/supervisory control of technicians involves "hands-on" participation and may involve individual work of a highly technical nature. The higher level involves application of technical knowledge and experience to work planning including implementation of medium to large scale projects.

Radio Technicians — £5485-£7818

To provide all aspects of technical support. Promotion prospects are good and linked with active encouragement to acquire further skills and experience. Minimum qualifications are a TEC Certificate in Telecommunications or equivalent plus two or more years' practical experience.

Cheltenham, a handsome Regency town, is finely endowed with cultural, sports and other facilities which are equally available in nearby Gloucester. Close to some of Britain's most magnificent countryside, the area also offers reasonably priced housing. Relocation assistance may be available.

For further information and your application form, please telephone Cheltenham (0242) 32912/3 or write to:



Recruitment Office, Government Communications Headquarters,
Oakley, Priors Road, Cheltenham,
Gloucestershire, GL52 5AJ. (2452)

CAREER IN MUSIC ELECTRONICS

Music Electronics company specialising in the design of electronics for music industry requires an engineer to join design team.

Duties will include design and test, knowledge of digital, analogue, C.A.D., microprocessors.

Ability to work on own initiative. Knowledge of music and sound would be appreciated but not necessary. Ideal candidate will have HTC or HTD, HNC/HND degree or equivalent.

Sound knowledge of business administration will be expected. Excellent promotional prospects.

Salary negotiable. Position would suit ambitious graduate.

Applicants write with full C.V. to:

MUSIC ELECTRONICS CO.
c/o Kynastons (Business Consultants)
Block D, Metropolitan Wharf
Wapping High Street, London, E.1
Telephone: 01-265 0722 (24-hour phone)
or 01-806 5127 (Evenings)

(2418)

Move up with a world leader

We have designed, developed and manufactured a series of products which have brought enormous advancements in data communications and established our dominance in international markets.

Now, due to expansion, we're looking for highly competent Repair Engineers to fill the following positions:

Senior Base Repair Engineer (Message Switching Equipment)

Experience in the repair and testing, down to component level, of mini-computers and peripherals, micro-processors on 6800 and Winchester tech. disc systems is preferable.

Senior Base Repair Engineer (Data Communications)

A sound background in data communications and experience of repairing and testing equipment, down to component level, is essential. The ability to program and some knowledge of Texas 9900 and Motorola 6800 micro-processors would be advantageous.

Probably in your mid 20's you must be able to demonstrate sufficient experience in a similar environment to equip you for these demanding and responsible positions. Competitive negotiable salaries, depending on the extent and relevance of your experience, are offered.

Our company's continuing success and exciting plans for the future create excellent prospects for career advancement and mean that we can offer a generous range of benefits, including bonus and profit share.

To apply, please write to, or telephone, Chris Burns at:

CASE Computer and Systems, Engineering plc, Caxton Way, Watford Business Park, Watford WD1 8XH. Hertfordshire. Tel: Watford 33500.

(2488)

GUY'S HOSPITAL DEPARTMENT OF CLINICAL PHYSICS AND BIOENGINEERING

This active, well-established and well-equipped Department provides a physical sciences service for a number of clinical departments in the hospital. We require a technician to join our electronics servicing group. This work includes the maintenance and servicing of a varied range of medical electronic equipment, and covers all aspects of patient orientated equipment from fixed installations to small portable instruments.

Experience in this type of work would be an advantage, but candidates with HM Forces experience, or a good background of TV servicing are encouraged to apply.

An ONC/HNC or equivalent qualification, plus at least three years' technical experience is essential.

The appointment will be on the Medical Physics Technician Grade 3 scale.

Salary: £7,174 to £8,968 p.a. inclusive.

Application forms are available from the Personnel Department, Guy's Hospital, London SE1 9RT. Tel: 01-407 7600, Ext. 3471. Please quote Ref: P/2. Closing date for completed application forms, March 30, 1984.

(2482)

LOGEX ELECTRONICS RECRUITMENT

Specialists in Field & Customer Engineering appointments, all locations and disciplines.

Logex House, Burleigh, Stroud
Gloucestershire GL5 2PW
0453 883264 & 01-290 0267

(24 hours)

Inner London Education Authority
LEARNING RESOURCES BRANCH
Television Centre, Thackeray Road, London SW8 3TB

TECHNICIAN (ST1/2)

A Technician is required to work in the Schools TV Workshop to share in the operation and maintenance of its facilities. The colour studio enables students to make practical use of television equipment.

Candidates should have educational as well as relevant technical experience and should be able easily and quickly to establish a helpful relationship with visitors.

Salary £5,517-£8,316 plus £1,284 London Weighting

Further details and application form from EO/Estab 1b, Inner London Education Authority, Room 365, The County Hall, London SE1 7PB.

The closing date for receipt of completed application forms is 29th February, 1984.

This vacancy is suitable for job sharing.

All applicants will be given equal consideration irrespective of sex, age, disabilities, race, colour, ethnic or national origins, marital status, sexual orientation, family responsibility, trade union activity or political belief.

(2456)

British Antarctic Survey Radio Officers (Marine)

Vacancies exist for Radio Officers (Marine) to serve on the Survey's research vessels. Successful applicants would be required to commence duties on August 1, 1984. Voyages are normally seven months long and vessels sail from the United Kingdom in the autumn.

The Survey's vessels re-supply Antarctic land stations, support scientific parties in the field and in addition undertake shipborne research.

Candidates should possess valid certificates of proficiency recognised by the Department of Trade and have served the necessary sea time to work a single-handed station.

Starting salary in a scale up to £8,640, rising to £10,917 per annum. In addition an allowance of £1,200 per annum is payable for periods of service spent south of Montevideo.

For further details and an application form, please write, stating full qualifications and experience, to: The Establishment Officer, British Antarctic Survey, High Cross, Madingley Road, Cambridge CB3 0ET. Please quote ref: BAS 5. Closing date: March 14, 1984.

NATURAL ENVIRONMENT RESEARCH COUNCIL

(2492)

Cameron Communications, an expanding division of C W Cameron Ltd, is a well established leader in the Visual Communications market, with high quality products for the professional and industrial users, including — Colour Graphic Displays — Interactive Video Systems — Video Projection — Videotex Terminals — Broadcast and Industrial Video Equipment — Touch Screen Displays — Computer Graphics Projectors.

The continuing growth and success of the company has resulted in the creation of further career opportunities based in our new Reading Office.

SENIOR ENGINEER

Video/Computer Products (Ref: RE1)

Salary: £ Negotiable Based: Reading Plus: Car

A Senior Engineer is required to head a team of engineers operating in a modern well equipped department providing technical assistance to the Sales Group, OEM Customers, Dealer Network and End Users. Key activities will include the organisation of documentation system to cope with the expanding product line and installed equipment base. Provide and maintain a technical interface with the company's suppliers and its customers and introduce equipment training and acceptance facilities.

EUROPEAN SERVICE ENGINEER

(Ref: RE2)

Interactive Video — Computer Products

Salary: £ Negotiable Based: Reading Plus: Car

An adaptable and self motivated person is required to provide service support and practical training on the above display systems at our distributors and customers premises in the UK, Europe and certain other countries.

Formal qualifications in electronics are required and service experience on video displays and some knowledge of personal computers or microprocessor based equipment would be a distinct advantage as would a foreign language.

TEST/SERVICE TECHNICIAN

(Ref: RE3)

Interactive Video — Computer Products

Salary: £ Negotiable Based: Reading Plus: Car

An interesting position is offered which will involve carrying out regular quality control checks on pre-manufactured 'Interact' systems passing through our Reading distribution and service depot. The post will also involve service and update of display units returned from the field and the preparation of fault investigation reports. Formal qualifications in electronics would be an advantage.

A small amount of UK and overseas travel may also be required.

We offer an attractive remuneration package with competitive salaries and company profit sharing scheme. All replies will be dealt with in the strictest confidence.



Cameron

Write for an Application Form quoting the position reference number to: —
Mr J F Cowan
Personnel Department at
Company Head Office
C W Cameron Ltd
Communications Division
Burnfield Road
Glasgow G46 7TH
Tel: 041-633 0077

(2460)

TECHNICAL MANAGER

Laser Sporting Products Limited are looking for an Electronics Engineer based at their office in North Yorkshire. The company is about to launch a new product and package on to the Game Shooting scene.

The applicant should have a sound knowledge of electronic and sonic technology together with a flare for innovation. An interest in fire-arms and shooting would also be a great advantage.

Please send applications together with curriculum vitae to:

The Managing Director, Laser Sporting Products Ltd
Manor Farm House
Garriston
Leyburn
N. Yorkshire DL8 5JT

(2467)

TEST EQUIPMENT DESIGN ENGINEERS

Rediffusion Consumer Manufacturing design and manufacture a full range of advanced specification colour television receivers and monitors.

We are looking for experienced Electronic Design Engineers to help us maintain our industry lead in sophisticated computer controlled test gear for production testing of our products. Future test equipment will be an interesting mix of digital and analogue circuitry aimed at increasing the automation of the production testing operation.

If you are able to conceive, design and implement production test equipment with minimal supervision, we'd like to hear from you.

These positions are based in our Chessington Engineering Centre but some visits to our factories in the North East and Lancashire will be required at infrequent intervals. Salaries are obviously dependent on qualifications and experience, but will reflect the importance of future test gear projects to the Company's long term development.

Interested ? ... Then write or phone :

Harry Brearley,
Rediffusion Consumer Manufacturing Ltd.,
Fullers Way South,
Chessington, Surrey. KT9 1HJ.
Telephone: 01-397-5411.



REDIFFUSION

(2408)

DOES THIS COMPANY EXCITE YOUR IMAGINATION?

All-British with American backing. Winner of £20,000,000 contract to supply one of the most advanced type Mobile Radio Systems.

THEY REQUIRE

RF CIRCUIT ENGINEERS and DESIGN/DEVELOPMENT ENGINEERS

to design a very wide range of mobile radio products — including those for commercial users, public bodies and other professional users. Technology includes RX, TX, frequency synthesisers, hybrid and microprocessor circuitry, frequency right up to microwave bands.

SOFTWARE ENGINEER — GROUND-FLOOR OPPORTUNITY

required to provide the necessary SW expertise in support of the above project including the use of 6800 family microprocessors. The candidate will be required to advise on latest techniques. Knowledge of Assembler and Pascal essential.

Location:

Rural fringe of Britain's Silicon Valley — motorway to South Coast and London. Outstanding scenic beauty nearby.

Salaries:

Ranging from £9,000 to £15,000 plus excellent relocation package.

FOR FURTHER DETAILS PLEASE CONTACT

Charles Airey Associates

Tempo House, 30 Fairfield Street, London SW18 1DW
Telephone: 01-870 4504

(2453)

Appointments

Engineering Opportunities

As world leaders in the supply of communications, navigation and entertainment equipment to the mercantile marine and offshore industry, we need additional professional men and women to help us meet the demand for our expanding product range.

SYSTEMS PLANNING/ PROJECT ENGINEER

Would you like to be technically involved with the planning of communication systems to meet specific marketing requirements? If so this position has good prospects with an ultimate objective to engineer and manage major projects. You should be aged 30 to 40, a good organiser, of graduate level or equivalent, with a sound knowledge of communication systems both in a practical and theoretical sense.

DEVELOPMENT ENGINEERS

Radio Communications

You will need to be a degree level/HNC or equivalent engineer with experience of radio communication development work, with particular regard to transmitters, modems, ancillary units, control and RF circuitry. Experience of digital and microprocessor work is highly desirable.

Radar Systems

A graduate with sound industrial experience, preferably including digital circuit design, is needed for the design of marine electronics equipment, initially radar. Your tasks would involve the detailed design of analogue and digital circuits over a wide range of speeds and power levels, together with associated software, overall systems design and equipment evaluation including sea trials.

The preferred age range for both these positions is 23-40.

We offer good working conditions, attractive salaries and other benefits usual within the thriving Marconi group of companies.

Please send full personal and career details, indicating which position interests you, to John Ellis, Marconi International Marine Company Limited, Elettra House, Westway, Chelmsford, Essex. Telephone: Chelmsford 261701.

Marconi
International Marine



(2486)

CUT THIS OUT!

Clip this advert and you can stop hunting for your next appointment. We have a wide selection of the best appointments in Digital, Analogue, RF, Microwave, Micro processor, Computer, Data Comms and Medical Electronics and we're here to serve *your* interests.

Call us now for posts in Design, Sales, Applications or Field Service, at all levels from £6,000-£16,000



Technomark
Engineering & Technical Recruitment

11 Westbourne Grove, London W2 Tel 01 229 9239

(1935)

Opportunities in Field Service

PROFESSIONAL BROADCAST PRODUCTS

£ Neg. Plus Car.

We are a highly successful and rapidly expanding world leader in the professional broadcast industry, with our international headquarters based in North Hampshire. Our wide range of products includes Cameras, VTR's, sophisticated editing control systems and the exciting new Betacam range.

Applications are now invited from engineers with a minimum of 2 years' experience gained either in operational television or its allied manufacturing industry. There are opportunities at all levels within the Department.

Responsibilities will include the commissioning, service and repair of our full range of video products. This will involve travel throughout our marketing area of Europe, the Middle East and Africa. Full product training will be given where necessary.

We offer an excellent benefits package including an attractive salary, Company car, free private medical cover and a Company Pension/Life Assurance Scheme.

If you are interested please write to, or telephone:

David Parry, Assistant Personnel Officer, Sony Broadcast Limited, City Wall House, Basing View, Basingstoke, Hants RG21 2LA. Tel: (0256) 55011

SONY
Broadcast



Sony Broadcast Ltd.

City Wall House
Basing View, Basingstoke
Hampshire RG21 2LA
United Kingdom
Telephone (0256) 550 11

(2469)

SENIOR ELECTRONICS DESIGN ENGINEER

THE JOB: Electronics and Instrumentation design for the rehabilitation and medical markets: signal processing, digital circuits, microprocessors, small servo systems.

THE REWARDS: An opportunity to be involved from conception to production in a company with a good working atmosphere. Salary £9,000-£12,500 depending on ability.

THE PERSON: Age: Preferably 26-40 years. Qualification: Degree or equivalent. Experience: At least three or four years of relevant design work needing a creative approach.

THE COMPANY: The post is in our Roehampton Research Department which is part of a company which has supplied rehabilitation services to the disabled for over 60 years.

Apply with full c.v. to:

Mr D. Hawkins
Hugh Steeper Ltd
237 Roehampton Lane
London SW15
Tel: 01-788 8165

(2472)

ARTICLES FOR SALE

WAVEGUIDE, Flanges and Dishes. All standard sizes and alloys (new material only) from stock. Special sizes to order. Call Earth Stations, 01-228 7876, 22 Howie Street, London SW11 4AR. (2099)

AVO 8 SERIES. Fully refurbished and calibrated Avo 8 Mark 3,4,5. Price including Avo type leads, prods, erocs and VAT £70. Also digital meters from £29. Telephone for details BELA ELECTRONIC DESIGNS, Bedford 257171. (2468)

VACUUM EQUIPMENT for encapsulation. Degassing of silicones and resins. CRT regunning plant, bw and colour. Barrets. Mayo Road, Grovdon CR0 2QP. 01-684 9917. (9678)

PAIR VOIGT/LAWDHER corner speakers and drive units required. Mr. Holdsworth, 021-705 1060. (2474)

BRIDGES, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236.

WIRELESS WORLD MARCH 1984

SITUATIONS VACANT

"In 3 days, 27 employers approached me. That's some form, Lansdowne."

The Lansdowne profile form is like no other application form. It's so brief and easy to fill in. But it tells employers just what they need to know to pick you out for a job offer.

In just 3 days, one Lansdowne job-seeker was approached by 27 employers. No real surprise considering we've spent 12 years introducing employers to job-seekers. At the same time trimming and shaping the information we ask for into the lean fighting form employers welcome and use.

Our computer instantly memorises your form and compares it with the vast number of vacancies we've been asked to help fill in 283 different job categories. Speed is important because we scan the Register every day to see which of the latest incoming vacancies might suit you.

We need to do this because the Lansdowne team is talking to employers about job vacancies day in, day out by phone, mail and face to face. So new vacancies are constantly being added to Lansdowne Appointments Register.

We could have one in there for you right now. And if you think it will cost you to find out, think again.

It costs you nothing.

NOW SHORTLISTING
ENGINEERS ·
SERVICE · TEST · Q.A. ·
CUSTOMER SUPPORT

01-743 6321 (24 hours)

All posts are open to men and women and our service is completely confidential for companies and job-seekers. (2466)



Lansdowne Appointments Register

To Stuart Tait,
Lansdowne Appointments Register,
Park House, 207-211 The Vale,
London W3 7QB.
Please send me a Lansdowne
Appointments Register job-finding pack.

NAME _____

JOB TITLE _____

ADDRESS _____

WW 15/2/84D

ARTICLES FOR SALE

ENCAPSULATING EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regunning metalising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

SERVICE SHEETS. C.T.V.s Music C £3 - others £2 plus I.s.a.e. Repair data including all circuits - any named TV or video £9.50. L.s.a.e. for quotation, free 50p mag and service sheet, etc. World's largest service repair manual stockists. [TIS/W] 76 Church St., Larkhall, Lanarkshire ML9 1HE. (For fast quotes phone 0698 883334).

EP 4000 EPROM emulator/programmer with 2764 adaptor £325. UV14 Eprom eraser with timer £45. BP4 (Texas) B Polar programmer £100. A1 size drawing board and folio £10. PCB Assembly jg £15. All prices exclude VAT. Telephone St Albans (0727) 31831 evenings. (2480)

FACSIMILE SYSTEM in first class condition, comprising Muirhead K-400D transmitter, K-401D receiver, K-346 crystal control units, K-404D line switching unit, cables and paper rolls, £225. Morris, Bolton 52384. (2490)

EK WD Radio equipment and test equipment. Over 500 sets in stock from £8. Send 50p for illustrated catalogue (including £1 voucher). Weirhead Ltd. 129 St. Albans Road, Watford, Herts. Tel: Watford (0923) 49456. (1974)

INSTRUMENT & EQUIPMENT FASCIA PANELS - Prototype and small batch production, photo-dyed anodised aluminium, 1.0 to 3.0mm from your positive master film. Also labels-dials-mimics in most plastics and metals. ESENCO, Peppercorns W, Eaton Socon, St Neots, Cambs. PE19 3JE. Telephone: (0480) 74454. (2493)

F.F.T. COMPUTER ANALYSERS, full specification with manuals, HP 3582A, dual channel, 85dB, 0-25kHz, zoom, G.P.I.B., £4,950 (list £8,600). Nicolet 444, 0-100kHz 400-line, fully annotated display, math functions, log/in, 1/2 and 1/4 octave, parallel interface, £4,450 (list £12,000). Also personally owned hi-fi equipment: Linn Linnk m.c. pre-equaliser, £105 inc.; Naim Nait integrated amplifier adapted for direct CD link to power stage, £140 inc.; Thorens TD125 electronic belt-drive turntable with tone arm, £125 inc. Telephone 01-794 2839. (2477)

VALVES, PROJECTOR Lamps, 6000 types, list 75p, world wide export. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Phone (024) 366 2023. (1991)

PYE GPO car telephone. Phone anywhere from your car for £295. Complete with number. Phone 061-764 8158. (2476)

FOR SALE. - Bound Wireless Worlds 1940-1962 in excellent condition. Telephone Braintree (0376) 24763. (2471)

1) Computer Terminals

Field support and service of microprocessor-based equipment. 2 yrs. exp. min. to £9,500 + car - London.

2) Marine Communications

HF/VHF and logic experience. Occasional work offshore/abroad. EVG - Glasgow

3) Satellite Communications

Senior test engineers with a knowledge of digital and analog or radar techniques. Circa £10,000 - Surrey/Middx./S. Coast

4) Service Personnel

(RAF, RN, Army)

We have many clients interested in employing ex-service fitters and technicians at sites throughout the UK. Phone for details.

5) £500 per week

We are paying very high rates for contract design and test engineers who have a background in RF, MICROWAVE, DIGITAL, ANALOGUE or SOFTWARE, at sites throughout the UK.

Hundreds of other Electronic and Computer Vacancies to £12,500

Phone or write:

Roger Howard
C.Eng., M.I.E.E., M.I.E.R.E.

CLIVEDEN CONSULTANTS

92 The Broadway, Bracknell, Berkshire
Tel. 0344 489489

(1640)

CLIVEDEN

**MEDICAL RESEARCH COUNCIL
NEUROENDOCRINOLOGY UNIT**
Newcastle upon Tyne

RESEARCH OFFICER (Electronics)

The appointee will be responsible for the design, construction and maintenance of electronic equipment to be used in biophysical investigations of the properties of neurones and neurosecretory cells. Design tasks will include: very low-level current detection circuitry; high-speed multichannel optical recording devices; computer-controlled stimulation equipment; instrumentation amplifiers; analog signal transformation circuitry. The appointee should have some experience of computer interfacing.

Minimum requirement is a university degree, HNC or equivalent qualification, with two years' relevant experience after qualification. Salary scale (due for revision) Research Officer £6,204-£8,126; Senior Research Officer £8,204-£10,467.

For further information contact:

Dr R. N. McBurney
MRC Neuroendocrinology Unit
Newcastle General Hospital
Westgate Road
Newcastle upon Tyne NE4 6BE
Telephone (0632) 735251

(2464)

ROYAL FREE HOSPITAL MEDICAL PHYSICS TECHNICIAN III (ELECTRONICS)

Salary on scale £7,174 - £8,968 incl.

An Electronics Technician is required for the Medical Electronics Department to assist with the development and maintenance of electronic circuits and systems.

Applicants should hold the Ordinary Tec Certificate in appropriate subjects, or an equivalent or higher qualification, and have good practical experience in the design of electronic circuits using state-of-the-art techniques.

Application form and job description available from the Personnel Dept., Royal Free Hospital, Pond Street, Hampstead NW3 2QG. Quote ref. 0758

Closing date - 2nd March 1984

HAMPSTEAD HEALTH AUTHORITY (2459)

University of Leeds

An

Electronics Technician Grade 7

is required to take charge of the electronics workshop that jointly serves three departments. He/she would be assisted by a Grade 5 Technician already in post. The duties include the construction of new instruments for the research and teaching activities of the department, together with the maintenance of existing instruments. It is essential that the person appointed should be familiar with, and keep abreast of, the latest developments in electronic circuitry (including microprocessors) and that he should also be prepared to keep going older equipment. There is a very interesting wide spread of applications. Applicants should be qualified to at least HNC or equivalent level and have had a minimum of ten years' relevant experience. Salary is in the range £8,385 - £9,418pa.

Applications to Professor A C T North, Astbury Department of Biophysics, The University, Leeds LS2 9JT. (2462)

TEST ENGINEERS

For real involvement in electronic equipment

Automation is taking much of the initiative out of a test engineer's role. But not here at Marconi Radar, where we need you to make a major contribution to the constant refinement of our complex electronic modules, units and systems, incorporated in advanced radar equipment. As world leaders in this technology, our performance and quality standards are stringent which is why we are looking for Test Engineers to work on a wide range of small quantity items.

You will need to have previous experience in a test or related field, possibly gained in HM forces or the electronics industry. In return, we offer an attractive salary and a range of benefits including assistance with relocation to this attractive part of the South East.

Write with full details of your experience and qualifications to Mr. B. Walsh, Marconi Radar Systems Limited, Writtle Road, Chelmsford, Essex. Telephone Chelmsford (0245) 267111, ext. 2484.

Marconi

Radar Systems



ARTICLES FOR SALE

COMMUNICATION RECEIVERS

RACAL 500C/S TO 30M/C/S IN 30 BANDS 1M/C/S WIDE
RA17 MW11 £100 • RA17L £150 • RA17E £225 • NEW
METAL LIDUVED CASES FOR ABOVE £20 ALL RE-
CEIVERS ARE AIR TESTED AND CALIBRATED IN OUR
WORKSHOP SUPPLIED WITH DUST COVER • OPERA-
TION INSTRUCTIONS - CIRCUIT IN FAIR USED CON-
DITION • RACAL SYNTHESISERS (DECADE FREQUENCY
GENERATORS) MA350B SOLID STATE FOR USE WITH
MA79 RA117 - RA217 - RA1218, ETC. £100 TO £150
• MA250 - 1.6M/C/S TO 31.6M/C/S £100 • MA1350 FOR
USE WITH RA17 RECEIVER - £100 TO £150 • MA259G -
PRECISION FREQUENCY STANDARD 5M/C/S 1M/C/S
100KHZ £100 TO £150 • PANORAMIC ADAPTOR
RA66 £150 • RA137 LF CONVERTOR - 10 TO 380K/C/S
£75 - RA218 INDEPENDENT SSB UNIT £50 - RA153
AND RA253 TWIN-CHANNEL RECEIVER 1 TO 30 M/C/S
- THIS IS VIRTUALLY TWO RA1715 IN ONE CASE £150
TO £200 • RA1218 SOLID STATE RECEIVER WITH
ELECTRONIC FREQUENCY DISPLAY TO 10KHZ FRE-
QUENCY 1 TO 30M/C/S - £500 • RA6217 RECEIVER
SOLID STATE COMPLETE WITH SEPARATE SYNTHES-
ISER - INCLUDES FM - A VERY HIGH-GAIN, SENSIT-
IVE AND EXTREMELY STABLE RECEIVER NORTH
AMERICAN RACAL MADE £400 • RA337 LF CONVERTOR
£100 TO £150 FOR USE WITH SOLID STATE RECEIVERS -
£150 • EDYSTONE COMMUNICATION RECEIVERS
EC958 - SOLID STATE HIGH STABILITY 10KHZ TO
30M/C/S £350 TO £400 EC964/7K SOLID STATE -
SINGLE CHANNEL - SSB - MAINS OR BATTERY - 1.6
TO 27.5M/C/S AND 400 TO 535KHZ £100 WITH MANUAL •
REDIFON SSB RECEIVER - R495 - SOLID STATE - 10
FIXED CHANNELS - RANGE 5 TO 30M/C/S AND 255KHZ
TO 525KHZ - MAINS OR BATTERY - COMPLETE WITH
ISB ADAPTOR ARU10A - £100 WITH MANUAL • CREED
75 TELEPRINTERS - FITTED TAPE PUNCH AND GEAR-
BOX FOR 50 AND 75 BAUDS - 110VOLT AC SUPPLY
IN ORIGINAL TRANSPORT TRAY SEALED IN POLYTHENE
LIKE NEW £15 EA • REDIFON TT11 AUDIO
TELEPRINTER CONVERTOR RECEIVER SOLID STATE
SUPPLY 110 OR 240 AC - MADE FOR USE WITH ABOVE
TELEPRINTER ENABLING PRINT-OUT OF MESSAGES
RECEIVED FROM AUDIO OUTPUT OF COMMUNICATION
RECEIVER - £15 WITH CIRCUIT TESTED, REDIFON TT10
CONVERTOR AS ABOVE BUT INCLUDES TRANSMIT
FACILITIES - £20 • OSCILLOSCOPES - STOCKS AL-
WAYS CHANGING - SELAB'S 111 SOLID STATE -
25M/C/S £175 • COSSOR CDU150 - 35M/C/S £200 •
TELEQUIPMENT D75 - 50M/C/S £300 • TEKTRONIX 465
100M/C/S £1000 • SOLDERING CD1740 - 50M/C/S £300
• FM RECORDER SANGHMD SABBRE 114 CHANNELS
£350 • TRANSEL MATRIX PRINTERS - AF11R 5-
LEVEL BAUDOT CODE - UP TO 300 BAUDS - FOR
PRINT-OUT ON PLAIN TELEPRINTER PAPER £50 TO £100
• TRANSEL AH11R AS ABOVE BUT ALSO 8-LEVEL
ASC11 (COTT NO. 2 AND COTT NO. 5) LIKE NEW £200 •
ARMY FIELD TELEPHONE SETS, TYPE F AND J
LARGE QUANTITY IN STOCK £6 TO £15 DEPENDING ON
TYPE AND QUANTITY • G.P.O. TYPE 26 HAND GENERA-
TORS - LARGE QUANTITY AVAILABLE P.O.R. • DON 10
TELEPHONE CABLE HALF-MILE CANVAS CONTAINERS
£20 • NIGHT VIEWING INFRARED AFV PERISCOPE
TWIN EYEPIECE - 24-VOLT DC SUPPLY - £100 EA.
ORIGINAL COST TO GOVERNMENT OVER £11,000 EA.
STATIC INVERTORS - 12 OR 24-VOLT INPUT - 240-
VOLT AC SINEWAVE OUTPUT VARIOUS WATTAGES
P.O.R. • XY PLOTTERS AND PEN RECORDERS VARIOUS
P.O.R. • FERROGRAPH SERIES 7 TAPE RECORDERS
MDNO £100 - STEREO £150 • LOW-NOISE AMPLIFIERS
500M/C/S TO 40G/CS IN VARIOUS RANGES MADE BY
WATKINS JOHNSON, 110- OR 240-VOLT MAINS INPUT
£25 TO £50 • SIGNAL GENERATORS VARIOUS -
TF995A3 £80 • TF995A5 £120 • TF144H £100 • TF1660/2
£75 • HP606A AND B £100 • B £150 • HP608 £100 •
HP614A £100 • HP618B £100 • HP620A £100 • TELONIC
SM 2000 SWEEP GENERATORS L3 AND L5 PLUG-INS 4
TO 75M/C/S £60 • TELONIC SWEEP GENERATORS 2003
850 TO 2150M/C/S £275 • MARCONI TF2212 XY SCOPE
£150 • TF1313 BRIDGE £100 • TF919 DEVIATION METER
£100 • TR83A POWER METER £50 • TF1245 AND 1246
CIRCUIT MAGNIFICATION METER £150 • BOX OF PLUG-
IN STANDARDS FOR TF1245 £100 • AERIAL MAST AS-
SEMBLY 30FT. HIGH COMPLETE WITH 16FT WHIP
AERIAL TO MOUNT ON TOP GUYROPES - INSULA-
TORS - BASE AND SPIRES, ETC. IN HEAVY-DUTY
CARRYING BAG - NEW £30 • RACAL FREQUENCY
COUNTERS TYPE 801 AND 836 £50 EA • TEKTRONIX
PLUG-INS - 1A1 £50, 1A2 £40, 1A4 £100, M £50
All items are bought direct from H.M. Government, being
surplus equipment, price is ex-works S.A.E. for en-
quiries. Phone for appointment for demonstration of any
item. V.A.T. AND CARRIAGE EXTRA
EXPORT TRADE AND QUANTITY DISCOUNTS GIVEN

JOHN'S RADIO
WHITEHALL WORKS, 84 WHITEHALL ROAD EAST
BIRKENSHAW, BRADFORD B011 2ER
TEL: (0274) 584007
WANTED: REDUNDANT TEST EQUIPMENT - RE-
CEIVING AND TRANSMITTING EQUIPMENT VALVES,
PLUGS SOCKETS - SYNCHROS, ETC. (848)

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC.

LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS,
DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc.
CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERA-
MICS, PLATE CERAMICS, etc.

ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE,
CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFOR-
MERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE.

TELEPHONE: 445 0749/445 2713

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, North Finchley, London, N.12
(5 minutes from Tally Ho Corner)

(1613)

BULK COMPONENTS

Resistors - ideal for making into packs or just to
increase stocks at a very low price. We're selling
new, full lead length resistors in original boxes/
packets/rolls. Because most are packed in
thousands (some are 100s) you'll need to buy a
large quantity to get a reasonable mix. You'll get
carbon/film/oxide mixed tolerances 1% to 20% in
1/8W, 1/4W and 1/2W. 20,000 £26, 50,000 £60,
100,000 £110, 1/4 million £250, 1 million £950. All
prices inclusive. S.A.E. for samples. We also stock
capacitors, semiconductors, verbosard etc. in
bulk.

SAE for latest list
PC ELECTRONICS, 2 THORNHILL
ROMSEY ROAD, WHITEPARISH, SALISBURY
WILTS SP5 2SD (2380)

B&T ELECTRONICS

13 TANNERS HILL
DEPTFORD, LONDON, S.E.8

TEL: 01-692 1441

1,000s ELECTRONIC, ELECTRICAL
MECHANICAL ITEMS

Xenon Tubes, Type XBLU 50.00 Eclatron £2.50
each P&P 60p. Quantity discounts P.O.A.

Xenon Flashers. Complete panel with dual flash
rate, 12-18 volts DC, inc. Tube, Base Fuse -
Holder, 10 metres connecting wire. Full instruc-
tions. 3 months' guarantee. Complete package
only £10 - £1.80 P&P Discounts P.O.A.

Enamelled Copper Wire. .090, .080, 180 MM £5
per 1kg Reel + £1.80 P&P

AVO 8 Movements, Mk 3 plus spares, plus
damaged Meters P.O.A. Will sell as one lot
£400

Measured Pressure Transducers £25 each
S.A.E. LISTS

Meters Mcooil, dc plastic, as used in Japanese
and 10 units, app. size 5mmx4.5mm. We have
Power W.V.U. Signal, or Battery level 100 or
200 micro amp Isd £1.50 each P&P 60p

MULTITURN

CERMET TRIMMERS 3/4 INCH

Make Allan Bradley	100	1K+
Type 94P non transparent	£22p	18p
Type 95P transparent	£22p	18p
Values 10-470R, 2K 500K, 1M, 2M, 2M2, 18 pin low profile I.C. socket	10p	7p

Please phone or telex
DIW MARKETING

3 Whitney Avenue, Ilford, Essex

Tel: 01-445 6645/550 4774

Telex 896 559 Att. DIW (2324)

LINSLEY HOOD DESIGNS

75Watt and 100W amps
Audio Signal Generators

75Watt amp p.c.b.	£2.30
100Watt Mosfet p.c.b.	£4.00

p&p 50p

S.A.E. for leaflets

TELERADIO ELECTRONICS

325 Fore Street, London N9 0PE

(1762)

Quartz Crystal Units
ACCURATE
RELIABLE

Private enquiries send 13p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY 01-942 0334 & 2988

Two essentials for every video test engineer.

VIDEO LINE SELECTOR
converts your cheap scope into a video
waveform monitor.

PATTERN GENERATOR
ALSO 12 VOLT ADAPTIONS OF
IKEGAMI 9" & 12" MONITORS

Contact Andrew Smith
INSIGHT VISION SYSTEMS LTD

Unit 1, Merebrook, Hanley Road, Malvern
Worcs WR13 6NP. Tel (0684) 310001 (2353)

SITUATIONS VACANT

CAPITAL APPOINTMENTS LTD

THE UK's No. 1 ELECTRONICS AGENCY
ELECTRONICS ENGINEERS

If your career is stagnating, if you are unemployed, or just starting your career in the most dynamic industry this country has to offer, then Capital Appointments can help. Our client companies have immediate and long term requirements throughout the UK for most categories of staff including: TECHNICAL MANAGEMENT, DESIGN, SOFTWARE, TEST, FIELD SERVICE, SALES, ETC. with salaries from £6,900 to £16,000 p.a.

Ours is a FREE SERVICE for applicants and you are assured of complete confidentiality. For immediate attention to your career requirements, complete the form below now and post to: CAPITAL APPOINTMENTS LTD, 29/30 WINDMILL STREET, LONDON W1P 1HG

If you would prefer to telephone us to discuss your situation in more detail, one of our consultants will be pleased to help.
TELEPHONE 01-637 5551

CUT FORM AND RETURN

CONFIDENTIAL

NAME ADDRESS

Tel. (Home): (Office):

Date of Birth: Place of Birth: Nationality now:

If not British, is a Work Permit required?

Marital Status: Car Driver: Car Owner:

Type of Position required: Approx. Salary level:

Please indicate areas in which you are prepared to work:				Are you a houseowner?	Are you willing to relocate?
Cent. London	S. Coast	E. Midlands		Are you prepared to travel - In UK?	Overseas?
S.E. London	West Country	W. Midlands		State of health:	
S.W. London	N.E. England	E. Anglia		Notice Period required:	
N.E. London	N.W. England	Wales		Availability for Interview:	
N.W. London	Scotland	Overseas			
Home Counties: N.W.		N.E.	S.W.	S.E.	

EDUCATION:

Secondary School Qualifications:

College or University Qualifications:

Any Professional Membership:

CAREER HISTORY

From/To	Company	Job Title/Description	Salary

Please indicate any Companies you do not wish us to contact.

If you wish to detail further aspects of your experience or job requirements, please enclose on a separate sheet. (2450)

ARTICLES FOR SALE

WORLD RADIO TV HANDBOOK

1984 ed. £12

1984 THE RADIO AMATEUR'S H/B by A.R.R.L. Price £12.50

BEGINNER'S GUIDE TO INTEGRATED CIRCUITS by I. R. Sinclair Price £4.50

ELECTRONIC PROTOTYPE CONSTRUCTION by S. D. Kasten Price £15.95

UNDERSTANDING ELECTRONIC SECURITY SYSTEMS by M. D. Lamont Price £2.30

UNDERSTANDING DIGITAL ELECTRONICS by G. McWhorter Price £4.30

INTRODUCTION TO ELECTRONIC SPEECH SYNTHESIS by N. Sclater Price £8

ELECTRONICS FOR HIGHER TECH by S. A. Knight Price £10

DOMESTIC VIDEO CASSETTE RECORDERS. A SERVICING GUIDE by S. Beeching Price £15.50

SEMICONDUCTOR DATA BOOK by A. M. Ball Price £7.50

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Telephone: 01-402 9176

Closed Saturday 1 p.m.

Please allow 14 days for reply or delivery

(2245)

USED ELECTRONIC INSTRUMENTATION

Avo 8 Mk.III. No Leads £55
 Avo 215L Breakdown & Ionisation Tester £200
 Croptic RBBA Resistance Boxes 0.10hm-1K0hm £20
 0.1% Hilgar & Watts. Optic Bench £195
 Halstrom 2'x18" x18" Oven. 300°F £400
 I.C.I. ULV 2518 Ultra Sonic cleaner £2000
 Keithley 135 4 1/2 digit Handheld D.V.M. £95
 Hewlett-Packard 1332A X-Y Display £250
 Hewlett-Packard CRT's for 1332A £100
 Laminair Clean Air Bench £400
 Unitek 2-127-05 Microbond Parallel Gap Welder £400
 Marconi TF.995A/3 AM/FM Signal Generator £200
 Philips PM.6465 Stereo Generator R.F. 100MHz £95
 Solatron 16045 Digi D.C. Voltmeter Sens 1uV £150
 Wayne Kerr B901/R261/S261 Admittance Bridge £95

VAT & Carriage Extra

MARTIN ASSOCIATES
 PARTHA HOUSE, BECKHAMPTON
 NR. MARLBOROUGH, WILTS.
 TEL: AVEBURY (067 23) 219

(2480)

ARTICLES FOR SALE

Kodak Stereoscan (stereoscopic scanning of picture pairs), £50. Reversible Gearboxes, speed reduction or increase, £4.50. PCM Simulator (Schlumberger), £250. PCM Decommutator, Infra-red Gas Analyser, £125. Philips FM/AM Generator, £89. Modulation Meter, £89. Clare Flash/Insulation Tester, £60. Sullivan 0.1% Decade Potentiometer, £35. Chart Recorder, £35. 24v. Stabilized PSU, £20. NiCad Multi-Charger, £20. FM Deviation meter, £45. Centrifuge, £49. Pulse Generator, Audio Generator, EHT Supply, EHT Meter, Wow/Flutter, RCL Deviation Bridge, Television Alignment Generator, Pulse Analyser, Oxygen Meter, Photo-multiplier Microphotometer, Mutual and Self Inductance Bridge, Television Sweep/Marker Generator, Valve Tester, Rohde & Schwarz Audio Spectrograph, £75. Stabilized PSU (variable). Books (various).

040-376236

(2016)

THE FOWBERRY ENERGY SAVER

(Patent Pending)

As described in the December Issue of Wireless World

Printed Circuit Board, fully silk-screen printed with component positions; component specifications and sources of supply; assembly instructions; drilling template for box-lid; window material and self-adhesive label, fully printed. Board to fit Bimbox 2006.

£7.50 inc. postage and VAT
MACHARG PARTNERSHIP
 Fowberry Tower, Wooler
 Northumberland NE71 6ER

(2470)

ARTICLES WANTED

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO
 86 Bishopsgate Street
 Leeds LS1 4BB
 0532 435649

(9956)

WANTED

SURPLUS ELECTRONIC COMPONENTS AND EQUIPMENT

We also welcome the opportunity to quote for complete factory clearance

B. BAMBER ELECTRONICS
 5 STATION ROAD, LITTLEPORT, CAMBS.
 Phone: Ely (0353) 860185

(2483)

SCIENCE OF CAMBRIDGE MK 14 micro-computer any condition. Box No. 2484. (2484)

SCIENCE OF CAMBRIDGE MK 14 micro-computer any condition. Box No. 2484. (2484)

SURPLUS

We offer good prices for test equipment, components, redundant computers, PCB's connectors. Immediate settlement.

TIMEBASE

94 Alfriston Gardens
 Sholing, Southampton SO2 8FU
 Telephone: (0703) 431 323

(1832)

VERBGATE LTD.

We buy large and small parcels of surplus I/C, transistors, capacitors and related electronic stock. Immediate settlement

Tel: 01-452 9769

Telex: 8814998

(2478)

Box number replies should be addressed to:

Box No.
 c/o Wireless World
 Quadrant House
 The Quadrant
 Sutton, Surrey, SM2 5AS

COMPONENT SCOOP PURCHASE

ONE MILLION C280 MULLARD PHILIPS POLYESTER CAPACITORS. Ideal for the trade or manufacturing. 0.01 to 0.47 mfd. 100v wkg. Assorted values £10 per 1,000 lot, p.p. £1. 1,000 of one value £12.50, p.p. £1. 5,000 assorted £42, p.p. £2. Please add VAT. MAINS TRANSFORMERS. Famous manufacturer TYPE 1. Midget clamped type. Input 200-250/250 c.s. Output 250-0-250 50 ma. 5.3v at 2 amps. £2.50 each, p.p. £1.50. Ten transformers £17.50, carriage £4. TYPE 2. Mains input. Output 35V at 1 1/4 amp. Price £2.75 each, carriage £1.50. Ten for £16, carriage £6. Larger discounts for larger quantities. Ten thousand valves, 1925 to 1975, modern and obsolete types. Send 50p (refundable). VERSATILE BENCH POWER SUPPLY UNITS. Contains high quality transformer made to exacting specifications giving one 20v output and one 20-0-20v output. D.C. output fused at 3amps but will easily give 5 amps. Input AC 110 250v 50 c.s. Bridge rectification. Contained on metal chassis with robust compact case size 7x5x4. Easily modified to give 40v and 80v. Makes ideal variable power supply. Usual cost around £60. Our price as new with circuit £8.50 each, p.p. £3. Two units £20 post free. XENON FLASHER UNITS. Complete panel with dual flash rate (slow/fast). 12v to 18v D.C. Includes tube, base, fuseholder, 10 metres of connecting wire. Full instructions and guarantee. As used on police vehicles. Ideal for boats and cars. Should be £40 each. Our price £12 each, p.p. £1.50. Two units £23 post free. Ideal emergency beacons for boats and cars.

DEPT. WW. MYERS ELECTRONIC DEVICES
 12-14 Harper Street, Leeds LS2 7EA. Tel: 452045

SYSTEM PROJECT ENGINEERS

The Ampex Broadcast Systems Group based in Reading, Berkshire, supplies complete television studio and mobile systems to broadcast installations worldwide.

Owing to expansion of the group's activities, we are now looking for Systems Project Engineers to join our innovative project teams involved in the design installation and commissioning of television studio and outside broadcast vehicle projects.

These appointments involve occasional overseas travel for on-site commissioning.

Key requirements are:

- * Thorough knowledge of video and audio principles – HNC/Degree in Electronics preferred.
- * Experience in broadcast television industry.
- * Previous knowledge of TV systems an advantage.

Attractive salaries and benefits, which include pension, life assurance, permanent health scheme, BUPA care option, product training, overseas allowances and relocation expenses where appropriate.

AMPEX

Please contact Maureen Brake for an application form:

AMPEX GREAT BRITAIN LIMITED
ACRE ROAD
READING RG2 0QR
TEL. READING (0734) 875200

(2447)

UWIST

University of Wales

**MSc/Diploma Course
in Electronics
M Eng Course in
Systems Engineering
(Automation, Robotics and
Information Systems)**

Applications are invited for places on the above full-time, one-year courses commencing in October 1984.

Further details and application forms (returnable as soon as possible) may be obtained from the Assistant Registrar, UWIST, PO Box 68, Cardiff CF1 3XA.

CAPACITY AVAILABLE

P.C.B.'s

Printed Circuit Boards
to your specification
from artwork through to
finished board

QUICK DELIVERY -
COMPETITIVE PRICES

CROFTON ELECTRONICS LIMITED

35 Grosvenor Road,
Twickenham, Middlesex
TEL 01-891 1923/1513 Telex 295093

PCB/ELECTRONIC ASSEMBLY

- ★ Circuit Design & Development
- ★ Prototyping
- ★ Pre-production Consultancy
- ★ Full Production Capability
- ★ Component Sourcing & Stocking
- ★ Complete Test Facilities

STAGECRAFT (ELECTRONICS) LTD
3 Churchfield Road
Acton Central, W3 6BH
Tel: 01-993 1852/3660

(2203)

TW ELECTRONICS LTD THE PCB ASSEMBLERS

More and more companies are investigating the advantages of using a professional subcontractor. Such an undertaking requires certain assurances.

TW are able to satisfy all of them – quality, competitive pricing, firm delivery and close co-operation with the customer.

Assembled boards at 100% inspected before flow soldering and reinspected after automatic cropping and cleaning.

Every batch of completed boards is issued with a signed certificate of conformity and quality – our final assurance.

For further details, contact us at our new works:

**Blenheim Industrial Park
Bury St. Edmunds
Suffolk IP33 3UT**

Telephone: 0284 3931 (1466)

FREE PROTOTYPE of the finest quality with EVERY P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited. Tel: Halstead (0787) 477408. (2126)

BATCH PRODUCTION wiring and assembly to sample or drawings. McDeane Electricals L., 19b Station Parade, Ealing Common, London W5. Tel: 01-992 8976. (169)

Box number replies should be addressed to:

Box No.
c/o Wireless World
Quadrant House
The Quadrant
Sutton, Surrey, SM2 5AS

Accurate Digital Multimeters at Exceptional Prices

28 RANGES EACH WITH FULL OVERLOAD PROTECTION

**7030
1% Accuracy
£35.95**



**6010
0.5% Accuracy
£29.95**

6010 & 7030 MODELS SPECIFICATION

- 10 amp AC/DC
- Battery: single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm
- Weight: 400g inc. battery
- Mode Select: Push Button
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 20MΩ
- Input Impedance: 10MΩ
- Display: 3 1/2 Digit 13mm LCD
- O/Load Protection: All ranges



**NEW
HM102 BZ
£13.00**

ANALOGUE HM102BZ WITH CONTINUITY BUZZER AND BATTERY SCALE

- DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500µA, 0-5, 50, 50mA 10A.
- Ohmmeter: 0-6 Meg ohms in 4 ranges
30 ohms Centre Scale.
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.

OTHER features: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road
Wembley, Middlesex HA9 8BH, England
Telephone: 01-902 4321 (3 lines). TELEX No. 923985

Quantity discount for trade on application
Please Add 15% to your order for V.A.T. P&P is free of charge
Offer applies only to mainland U.K.

Payment by cheque with order
accepted

WWW - 019 FOR FURTHER DETAILS

ELECTRONICS & Wireless World

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 92-103

PAGE	PAGE	PAGE
AC DC Electronics 90	Global Instruments Corporations 63	Radford Laboratory 10
Airlink Transformers 80	Gould Instruments 56	Radiocode Clocks Ltd 6
Ambit International 91	G.P. Industrial III, IV	Radio Components Specialities 81
Apollo 12	Grandata Ltd. 82	Ralfe, PF Electronics 89
Armon Electronics Ltd. 104		Research Communications 17
Aspen Electronics 18		
Association of Sound and Communication Engineers Ltd. 78	Hameg 59	
Audio Electronics 13	Happy Memories 7	
	Harris Electronics (London) 10	
B. Bamber Electronics 84	Harrison Bros. Electronic Dist. 16	Sandwell Plant Ltd. 2
Barrie Electronics Ltd. 75	Hart Electronics Kits 82	Sarel Electric Ltd. 85
Beckenham Peripherals 90	House of Instruments 55	Scopex Electronics Ltd. 60
BICC Vero 64		Seasims Controls 88
Black Star Ltd. 80	ILP Electronics Ltd. 10	Service Trading Co. 72
Broadfield & Mayco 2	Insight Vision Systems Ltd. 2	Solent Elect 6
	Intergrex Ltd. 86	South Midlands Communications 76
Cambridge Kits 74		Sower EA 85
Cambridge Microprocessor Systems 84	Keithley Instruments 22	Special Products Distribution Ltd. 12
Cambridge Systems Technology 89		Stewart of Reading 82
Clark Masts Ltd. 9	Langrex Supplies Ltd. RST 19	Strumtech Engineering 75
Cricklewood Electronics 87	Levell Electronics Ltd. 81	Surrey Electric 80
Crimson Elektrik Stoke 75	Light Soldering Development 16	
Crotech Instruments 59	Midwich Computer Co. 9	Taylor Bros. (Oldham) Ltd 2
Control Universal Ltd. 80	Minim Electronics 18	Technomatic Ltd. 14/15
		Teledigital Computer 73
Dataman Designs 79	Nicolet Instruments 65	Television 6
Dicoll Electronics 76	Olson Electronics Ltd. 17	Telonic Instruments 64
Display Electronics 11	Opus Supplies 20/21, 83	Thandar 18, 55
	Orion Scientific Products 74	Thanet Electronics (Reltech) 4
Easibind 78	Pantechnic 85	Thurby Electronics (Reltech) 65
EG & G Reticon 90	PM Components 76, 77	Timebase 88
Electrical Times First-Aid Chart 86	Practical Computer 8	Timebase Q Teq 10
Electronic Broker 3, 5, 7	Practical Wireless 12	TK Electronics 74
Electronic Equipment Co. 72	P & R Computer Shop 6	Triangle Digital Service 18
Electrovalve 78		
EMS Manufacturing 7		Valradio Power Ltd. 90
Essex Electronics 4		Vigilant Communications 74
Farnell Instruments 60		Warwick Design Group 72
Future Film Development 4		Wireless World Feature Ed 65
Fyde Electronics Ltd. 16		

OVERSEAS ADVERTISEMENT AGENTS
France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Ms Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget.
Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106.
Telephone: (03) 585 0581.

United States of America: Ray Barnes, Business Press International Ltd, 205 East 42nd Street, New York, NY 10017 - Telephone (212) 867-2080 - Telex: 238327.


Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone (312) 63074.
Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Jack Mantel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone (216) 621 1919.
Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone (404) 237 7432.
Mike Loughlin Business Press International, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.

Canada: Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
* Also subscription agents.

EP8000 EPROM EMULATOR PROGRAMMER

**NEW
PRODUCT**

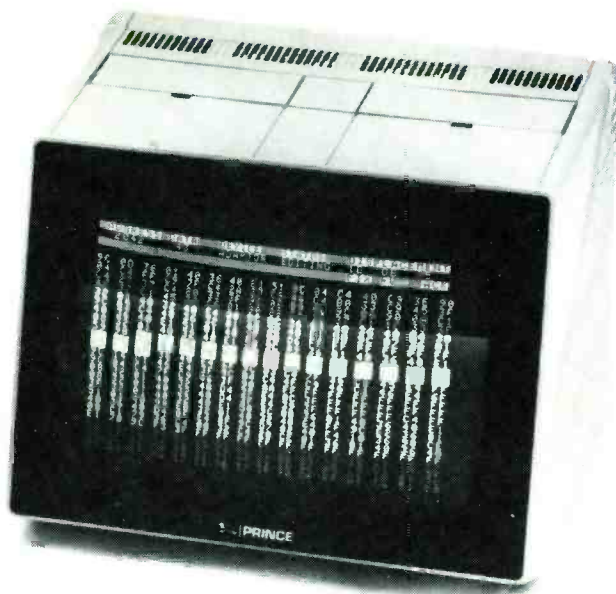

The new microprocessor controlled EP8000 Emulator Programmer will program and emulate all EPROMs up to 8k x 8 sizes, and can be extended to program other devices such as 16k x 8 EPROMs, Bipolar PROMs, single chip microprocessors with external modules.

Personality cards and hardware changes are not required as the machine configures itself for the different devices.

The EP4000 with 4k x 8 static RAM is still available with EPROM programming and emulation capacity up to 4k x 8 sizes.

● EP8000 8k x 8 Emulator Programmer – £695 + £12 delivery ● BSC8 Buffered emulation cable – £49 ● SA27128 Programming adaptor – £69 ● SA25128 Programming adaptor – £69 ● EP4000 4k x 8 Emulator Programmer – £545 + £12 de-

FEATURES

- Software personality programming/emulation of all EPROMs up to 8k x 8 bytes including 2704, 2708, 2716(3), 2508, 2758A, 2758B, 2516, 2716, 2532, 2732, 2732A, 68732-0, 68732-1, 68766, 68764, 2564, 2764. Programs 25128, 27128 with adaptors.
- No personality cards/characterisers required.
- Use as stand alone programmer, slave programmer, or EPROM development system.
- Checks for misplaced and reversed insertion, and shorts on data lines.
- Memory mapped video output allows full use of powerful editing facilities.
- Built-in LED display for field use.
- Powerful editing facilities include: Block/Byte move, insert, delete, match, highlight, etc.
- Comprehensive input/output – RS232C serial port, parallel port, cassette, printer O/P, DMA.
- Extra 1k x 8 scratchpad RAM for block moving.

livery ● BSC4 Buffered emulation cable – £39 ● BP4 (TEXAS) Bipolar PROM Module – £190 ● Prinz video monitor – £99 ● UV141 EPROM Eraser with timer – £78 ● GP100A 80 column printer – £225 ● GR1 Centronics interface – £65

VAT should be added to all prices

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961

Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW-002 FOR FURTHER DETAILS

P8000 – THE PRODUCTION PROGRAMMER THAT HANDLES ALL NMOS EPROMS



**NEW
PRODUCT**

- Checks, Programs, Compares up to 8 devices simultaneously
- Handles all NMOS EPROMS up to projected 128K designs with no personality modules or characterisers – See list
- Easy to use, menu driven operation for blankcheck, program, verify, illegal bit check, checksum, self-test
- Constant display of device type, mode and fault codings
- Individual socket LED indicators for EPROM status
- Comprehensive EPROM integrity checks – Illegal bit check, data and address shorts, constant power line monitoring
- Full safeguard protection on all sockets
- Automatic machine self-test routine
- RS232C interface supplied as standard
- Powered down sockets
- Cost effective price – £695 + VAT
- Available from stock

Write or phone for more details

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

2704
2708
2716(3)
2508
2758A
2758B
2516
2716
48016
2532
2732
2732A
68732-0
68732-1
68766
68764
2764
2564
MK2764
25128
27128