

# ELECTRONICS WORLD

Denmark DKr. 70.00  
Germany DM 15.00  
Greece Dra. 760  
Holland Dfl. 14  
Italy L. 7300  
IR £3.30  
Spain Pts. 780  
Singapore S\$ 12.60  
USA \$6.70

## + WIRELESS WORLD

SOR DISTRIBUTION

A REED BUSINESS PUBLICATION

MAY 1994 £1.95

### AUDIO

Ultra-low distortion  
test oscillator

### CIRCUITRY

Working with  
current mode  
amplifiers

### APPLICATIONS

Three-chip pager  
system

### RF ENGINEERING

Microstrip design,  
instability and  
mismatch

### PC ENGINEERING

Schematic entry:  
good starting point?

### COMPONENTS

SOT23 transistor  
switches 100W



## DESIGNER'S GUIDE TO OPTOELECTRONICS



9 770959 833004



# THE WORLDS No.1 BEST SELLING UNIVERSAL PROGRAMMING AND TESTING SYSTEM.

The PC82 Universal Programmer and Tester is a PC-based development tool designed to program and test more than 1500 ICs. The latest version of the PC82 is based on the experience gained after a 7 year production run of over 100,000 units.

The PC82 is the US version of the Sunshine Expro 60, and therefore can be offered at a very competitive price for a product of such high quality. The PC82 has undergone extensive testing and inspection by various major IC manufacturers and has won their professional approval and support. Many do in fact use the PC82 for their own use!

The PC82 can program E/EPROM, Serial PROM, BPROM, MPU, DSP, PLD, EPLD, PEEL, GAL, FPL, MACH, MAX, and many more. It comes with a 40 pin DIP socket capable of programming devices with 8 to 40 pins. Adding special adaptors, the PC82 can program devices up to 84 pins in DIP, PLCC, LCC, QFP, SOP and PGA packages.

The unit can also test digital ICs such as the TTL 74/54 series, CMOS 40/45 series, DRAM (even SIMM/SIP modules) and SRAM. The PC82 can even check and identify unmarked devices.

Customers can write their own test vectors to program non standard devices. Furthermore it can perform functional vector testing of PLDs using the JEDEC standard test vectors created by PLD compilers such as PALASM, OPALjr, ABLE, CUPL etc. or by the user.

The PC82's hardware circuits are composed of 40 set pin-driver circuits each with TTL I/O control, D/A voltage output control, ground control, noise filter circuit control, and OSC crystal frequency control. The PC82 shares all the PC's resources such as CPU, memory, I/O hard disk, keyboard, display and power supply.

A dedicated plug in card with rugged connecting cable ensures fast transfer of data to the programmer without tying up a standard parallel or serial port. Will work in all PC compatibles from PC XT to 486.

The pull-down menus of the software makes the PC82 one of the easiest and most user-friendly programmers available. A full library of file conversion utilities is supplied as standard.

The frequent software updates provided by Sunshine enables the customer to immediately program newly released ICs. It even supports EPROMs to 16Mbit.

Over 20 engineers are employed by Sunshine to develop new software and hardware for the PC82. Not many competitors can boast of similar support!

Citadel, a 32 year old company are the UK agents and service centre for the Sunshine range of programmers, testers and in circuit emulators and have a team of engineers trained to give local support in Europe.

- \* More sold worldwide than any other of its type.
- \* UK users include BT, IBM, MOD, THORN EMI, MOTOROLA, SANYO, RACAL
- \* High quality Textool or Yamaichi zero insertion force sockets.
- \* Rugged screened cabling.
- \* High speed PC interface card designed for use with all PC models from XT to 486.
- \* Over 1500 different devices (including more than 100 MPU's) supported.
- \* Tests and or identifies a wide range of logic devices.
- \* Software supplied to write own test vectors for custom ICs and ASICs etc.
- \* Protection circuitry to protect against wrong insertion of devices.
- \* Ground control circuitry using relay switching.
- \* One model covers the widest range of devices, at the lowest cost.
- \* No need to tie up a slow parallel port.
- \* Two year free software update.
- \* Speed optimised range of programming algorithms.



**NOW SUPPLIED WITH SPECIAL VALUE ADDED SOFTWARE** (worth over £300 if bought seperately):

- \* MICROTEC disassemblers for Z8, 8085, 8048, 8051, 6809 & 68HC11.

- \* NATIONAL SEMICONDUCTOR OPALjr PAL/PLD development software.

- \* BATCH SOFTWARE for production programming.

Our stocked range of own manufactured and imported Sunshine products include:

- \* Super fast EPROM Erasers.
- \* 1, 4 & 8 gang EPROM 8Mbit production programmers.
- \* Battery operated portable EPROM programmers.
- \* "In circuit" Emulators.
- \* Handy pocket IC testers.



## ORDERING INFORMATION

PC82 complete with interface card, cable, software and manual only **£395**

Please add £7 carriage (by overnight courier) for UK orders, £20 for export orders, and VAT where applicable.

ACCESS, MASTERCARD, VISA or CWO. Official orders are welcome from Government bodies & local authorities.

Free demo disk with device list available.



**CITADEL PRODUCTS LTD**  
DEPT. WW, 50 HIGH ST.,  
EDGWARE, MIDDX. HA8 7EP.

Phone now on: 081 951 1848/9





# CONTENTS

## FEATURES



### OPTO-ELECTRONICS .....364

Opto-electronics components find wide usage in measurement, production control, scientific and consumer applications. Nearly all uses have a common requirement for photodetection in the presence of ambient light. Tore Nielsen presents a circuit designer's guide to opto-electronics.

### LOW DISTORTION AUDIO OSCILLATOR.....370

You may wish to design the ultimate in distortion free audio equipment but can you be sure that you are measuring residual from the equipment under test or an artifact from the test oscillator or distortion meter? The test oscillator design presented here by Ian Hickman could break the dilemma.

### SURFACE MOUNT POWER SWITCHING.....377

Superior bipolar chip technology and better leadframe design have been used to create an SOT device which has double the power handling performance of comparable devices. By Martin Eccles.

### USING RF TRANSISTORS.....381

Instability in solid state amplifiers may well be the most difficult problem a designer must face. Norm Dye and Helge Granberg review some common causes. The authors also examine the measurement and control of excessive VSWR.

### BIG BROTHER'S PROTECTION RACKET.....388

The Government is worried that it won't be able to eavesdrop on your telephone conversations or your computer traffic. It would have you use a chip which will make personal surveillance easier. Robert Shifreen reports.

### CIRCUIT CAPTURE AND PCB DESIGN.....391

The inclusion of schematic capture with PCB edit provides a powerful productivity design tool. John Anderson reviews the latest addition to Tsien's Boardmaker software which adds full schematic capture.

### MATHS FUNCTIONALITY FOR MATHS-PHOBICS.....395

Mathematic analysis can give valuable insight at the initial circuit design stage. Lionel Snell reports on two packages – Mathematica and Nodal – which give engineers the power of maths without the pain.

### NEW WAVE MICROWAVES.....410

Microstrip engineering more than any other technique provides the foundation to modern microwave design. Mike Hosking spells out the design rules which turn unwanted reactance into a positive asset.

### PATENTLY UNCLEAR.....433

Just because it's patented doesn't make it good. And just because it's good doesn't mean it will be successful. Barrie Blake-Coleman explains how big companies play by the unwritten rules of the patent.

## REGULARS

### COMMENT.....355

Lack of initiative

### NEWS.....356

Radar for buried bodies; plastic battery; optical amplifiers; report backs digital TV; PowerPC outperforms Pentium

### RESEARCH NOTES.....360

Smallest piece of metal in the world; Satellites shot from a gun; Electrons show brittle behaviour; Computer disks use magneto-resistive storage.

### DESIGN BRIEF.....402

There are unique benefits to current conveyor ICs in applications from lf to rf. Take a precision rectifier needing only two resistors and two diodes for example. Ian Hickman looks at this new class of component.

### BOOK REVIEWS.....406

Works on DSP, multiplexing and radio history.

### CIRCUIT IDEAS.....416

SCR based AC power inverter; OTA oscillator; Voltage independent time delay; Comparator extends alarm system; Analogue switch with memory; Variable frequency generator has switchable duty cycle; Inductance meter.

**Doug Self power amplifier PCBs are now available. Ordering details on page 358**

### LETTERS.....420

Self vs Duncan over hot audio; Virtual travel; Diagram as a language; Appaling editor; O frabjous days.

### NEW PRODUCTS.....423

Comprehensive round-up of the industry's new products presented in the industry's most readable format.

### APPLICATIONS.....428

Low drop-out regulators; Designing with dc to dc converters; Radio pager design.

### IN NEXT MONTH'S ISSUE

Selective calling for mobile radio. The telephone dial or keyboard and its power to summon up a specific connection is taken for granted. Not so with radio. Individual radio services have each evolved their own calling codes; the aeronautical service uses a different set of codes from maritime networks. James Vincent presents both protocol and circuitry for selective radio calling

**THE JUNE ISSUE IS ON SALE FROM MAY 26**

## Technologies change

## Our commitment to Training does not

Commitment to training is essential in the rapidly changing communications world. At Ericsson the importance of training has long been recognised. Since the early 1980s Ericsson has developed Technology Based Training (TBT) which allows personnel to be trained where and when the user needs it.

Ericsson's TBT presents complex and difficult training material in an interesting and exciting way. It is a self-paced, interactive, user-friendly and cost effective method of enhancing technical competence.

### Ericsson's generic range of IBM PC™ compatible courseware includes the following courses:-

- Introduction to Telecommunications
- ISDN Overview and ISDN Advanced
- OSI & Data Networks and OSI Advanced
- X.25 and Related Protocols and X.25 Advanced
- C7 Signalling System Part 1 and Part 2
- Understanding Modems
- PCM Principles
- Cellular Mobile Radio
- X.400 Overview

For further information please contact your local Ericsson office or

**Marketing Department,**  
Ericsson Systems Expertise Limited,  
Adelphi Centre, Upper George's Street, Dun Laoghaire, Co. Dublin, Ireland.  
Tel: + 353 1 2800455. After 5pm: + 353 1 2843030. Fax: + 353 1 2805914.

*Ericsson's TBT is used in over  
50 countries world-wide*

CIRCLE NO. 103 ON REPLY CARD

**ERICSSON** 

Finally an upgradeable PCB CAD system to suit any budget ...

## Board Capture

### BoardCapture - Schematic Capture

- Direct raster link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

E395

NEW

## Board Maker

### BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surfaces mount support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

E395

### BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus:
- Full netlist support - OrCAD, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

E295

## Board Router

### BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

E200

### Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)

Call for info or full  
evaluation kit  
Tsien (UK) Limited  
Tel (0354) 695959  
Fax (0354) 695957



**tsien**

Tsien (UK) Ltd, Aynsby House, Wexley Road, Chatteris, Cambridge PE16 6UT

CIRCLE NO. 104 ON REPLY CARD

**EDITOR**

Frank Ogden  
081-652 3128

**DEPUTY EDITOR**

Martin Eccles  
081-652 8638

**CONSULTANT**

Derek Rowe

**DESIGN & PRODUCTION**

Alan Kerr

**EDITORIAL ADMINISTRATION**

Lorraine Spindler  
081-652 3614

**ADVERTISEMENT MANAGER**

Richard Napier  
081-652 3620

**DISPLAY SALES EXECUTIVE**

Malcolm Wells  
081-652 3620

**ADVERTISING PRODUCTION**

Paul Burgess  
081-652 8355

**PUBLISHER**

Susan Downey

**EDITORIAL FAX**

081-652 8956

**CLASSIFIED FAX**

081-652 8931

**SUBSCRIPTION HOTLINE**

0622 721666  
Quote ref INJ

**NEWSTRADE DISTRIBUTION**

Martin Parr  
081 652 8171

**BACK ISSUES**

Available at £2.50  
081 652 3614

ISSN 0959-8332



## No place for initiative

Industry minister Tim Sainsbury has indicated that there will be no more government cash in the pot to stimulate the UK's microelectronics industry when the £3m *Microelectronics in Business* initiative has run its course. This is both right and wrong.

It is right because the description "electronics industry" covers such a wide range of activity that it would be positively wrong to single out one facet for special economic treatment. After all, "Microelectronics in Business" strikes me as a particularly fatuous subdivision; why not "software design tools for industry" or, perhaps, "tax credits on automated test equipment"?

But why concentrate on the sharp end of the product design process? Companies and consultancies pay their staff to be well informed about design and process technology and, if these people can't hack it, they should consider a job in hair dressing or the legal profession. The Government has no place in persuading people to do what should naturally be part of their job.

It makes sense to stimulate the health of the infrastructure by ensuring a supply of well educated and motivated people who leave college with a training that fits more closely the needs of employers. Seed money should be used to forge

additional links between education and industry: personnel exchange programmes between the two, joint sponsorship of final year projects and applications oriented postgraduate research come to mind.

I appreciate that such things already happen but the electronics industry would benefit from more of them, much more so than by the simple funding of a few non-recurring engineering charges.

But if business currently fails to appreciate the importance of modern electronics in general design – which the Government seems to think is the case – then it is for reasons other than a specific lack of knowledge about ASIC chips. I suggest that industry generally fails to appreciate the worth of competent and qualified electronics engineers, an indifference which it matches in remuneration. This shortfall is definitely the responsibility of industry, not the Government.

It has to look to itself for a solution. It could begin by appointing engineers to control the plague of lawyers and accountants in company boardrooms.

When industry (and government) is prepared to pay engineering graduates (and maths and science teachers) more than this deeply unimaginative group of business professionals, we will begin to see a real change in our industrial fortune. **Frank Ogden**

*Electronics World + Wireless World* is published monthly. By post, current issue £2.25, back issues (if available) £2.50. Orders, payments and general correspondence to **L333 Electronics World + Wireless World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tlx: 892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group

**Newstrade:** IPC Marketforce, 071 261-5108.  
**Subscriptions:** Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 445566. Please notify change of address. Subscription rates 1 year (normal rate) £30 UK and £43 outside UK

**USA:** \$52.00 air mail. Reed Business Publishing (USA), Subscriptions office, 205 E. 42nd Street, NY 10117.

**Overseas advertising agents:** France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 205 E. 42nd Street, NY 10117. Telephone (212) 867-2080. Tlx 23827.

**USA mailing agents:** Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

**Printed by** BPC Magazines (Carlisle) Ltd, Newtown Trading Estate, Carlisle Cumbria, CA2 7NR  
Typeset by Marlin Graphics 2-4 Powerscroft Road, Sidcup, Kent CA14 5DT

©Reed Business Publishing Ltd 1992 ISSN 0959 8330

## Radar helps police look for bodies

As the horror of 25 Cromwell Road unfurled, one could not help but be impressed with the apparent ease in which long decayed remains were discovered.

Thermal imaging systems can find living people under mounds of rubble and debris after plane crashes or earthquakes. But in Gloucestershire the remains were long dead.


Searchers reverted to a method designed during the Falklands war for finding plastic mines. Called surface penetrating radar it has since found applications in archaeology, civil engineering and searching for victims of snow avalanches.

A major advantage of this type of radar over other nondestructive testing methods such as ultrasound is that an antenna can be used that is not in physical contact with the material being tested. It is therefore possible to scan large areas quickly.


Wideband radar pulses directed into the ground give rise to back-scattered energy from a target buried in a material. Anomalies in density or dielectric constant produce reflections which are detected by the receiving antenna. A conventional radar is stationary and its target mobile. Surface penetrating radar moves and its targets are stationary.

A typical system consists of an antenna head, transmitter-receiver and a purpose designed real-time processor, storage and display unit.

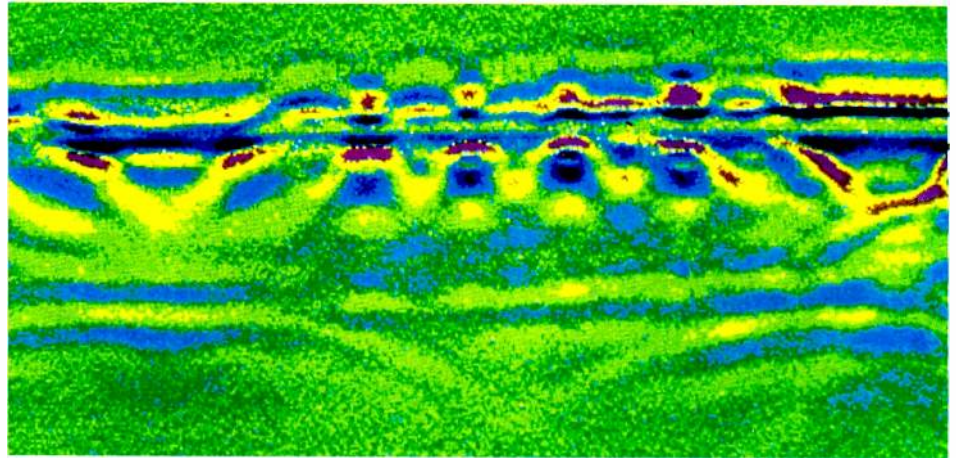Transmitting and receiving antennas are housed in an ABS plastic antenna head measuring about 50x50cm. This assembly is moved in a regular pattern over the surface of interest. A pulse of energy – as narrow as



*A typical colour enhanced image using surface penetrating radar. This civil engineering application shows petrol tanks buried under reinforced concrete. By comparing the line drawing and the colour image you can see the concrete layer shown by the false colour line near the top. The dark patches denote the reinforcement. Below that deviations in the soil (coloured green) provide the outline of the tanks.*

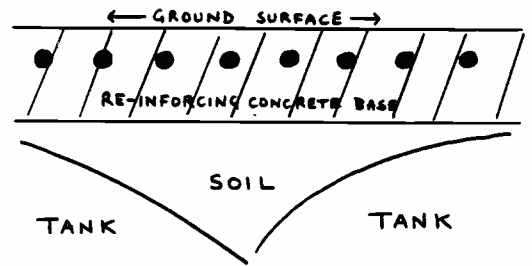

1ns – is repetitively transmitted into the sub-surface material at an average power level of 5mW.

A PC based processor provides an image of the internal composition of the structure in real time. A trained operator can see what is happening as the scan progresses. The system produces an enhanced image with different types of structure density being

shown in different colours.

This was good enough to give a 100% hit rate in Cromwell Road because the structure of the foundations of the building was known as was the type of soil.

In use, each measurement consists of about 256 samples, each to 12-bit resolution, and each averaged four times before being transferred every 6ms to the processing unit. The time interval between samples may be set to provide a range between 6.4 and 1048ns, corresponding to depths of 0.3 to 53m. In the wet soil conditions of the UK – which are heavily attenuating – a depth of 2 or 3m is achievable.

As well as presenting the data as a cross section, the radar can build up an area scan by taking a grid of correctly registered line scans. Selected depths may also be viewed.

The choice of bandwidth dictates the compromise between depth and detail. The equipment covers the 50MHz to 5GHz range and involves several octaves of bandwidth. Low frequencies are normally used for deep probing, say 50m, and high frequencies for shallow probing.

The wavelength of the transmission decreases as the velocity of propagation slows within the material, a process governed by the relative dielectric constant of the material. If the propagation velocity can be measured or derived, an absolute measurement of depth or thickness is possible.

## Flexible battery charged to plastic

Researchers at Bellcore say they have created a revolutionary new type of battery that is as flexible and as light as a plastic credit card yet delivers high-energy and is rechargeable.

The lithium-ion battery offers equal or better performance than rechargeable nickel-cadmium and lead-acid batteries at half the weight. Bellcore says that the flexible battery can be shaped for virtually any application from small hand-held video games to large sizes capable of powering electric cars.

"This is the first plastic, rechargeable battery," says Jean-Marie Tarascon, leader of Bellcore's battery team. "It does not contain toxic metals, like lead, cadmium, mercury or cobalt. What's more, no liquid will leak out if the battery is cut or punctured, making it safe to install and use."

Jeff Dahn, a battery research expert and professor at Simon Fraser University says, Bellcore's plastic lithium-ion battery appears suited for portable electronics applications where a lightweight, high energy, thin battery is preferred."

The Bellcore battery does not have any liquid electrolytes and can be recharged hundreds of times without losing capacity at the same rate as comparable liquid lithium-ion batteries. The batteries' elements are permanently bonded together and covered in a waterproof barrier.

Bellcore, which is funded by US telephone companies, says that one of the first applications of the new battery will be to provide back-up electricity for central switching offices. Bellcore says it will license the battery technology to other firms.



Once the signal has been received, it has to be processed for display. This requires deconvolving the unprocessed waveform in time and space. With surface penetrating radar, the initial transmitted impulse becomes convolved with a series of responses due to the antenna, the ground and so on. The only part of the signal of interest is the target impulse response. The processing techniques used to isolate this are similar to those used in seismic exploration, ultrasonic imaging and medical tomography.

The equipment was designed and operated by a team from ERA Technology. Speaking about the Cromwell Road events Keith Cheshire from the company said: "We knew what the subsoil was like. If you bury something in soil, the soil gets disturbed so its not uniform."

Another advantage the searchers had came from the way a buried body decays. The missing flesh is not necessarily replaced by the surrounding soil. This especially true for areas like the skull where, once the brain has rotted away, a tell-tale void remains which is easily picked up by the radar. When voids are discovered, grid pattern analysis can be used to measure the size of the void and make judgements about its likely cause.

For searches more complex than Cromwell Road, the data can be stored and post-processed to get rid of clutter and enhance interesting parts. Up to 2Gbyte of data can be stored by the assembly. Fully processed data can be continuously displayed at a measurement rate of one point every 300mm at a traverse speed of 25km/h.

Post processing is useful in archaeology for detecting ancient burials and artifacts, or in civil engineering for assessing the condition of roads or tunnel linings.

Looking for pipes and cables may be done on the spot as can finding people trapped under snow avalanches. This last task is particularly easy for the system as snow is a uniform conductor which reflects well from changes in conductivity.

Ground penetrating radar has more difficulty with collapsed buildings because of excessive clutter and an irregular antenna datum.

**Spheres of influence:** This electron microscope view shows an electrically conductive light weight elastomer comprising silver coated glass spheres in a matrix of silicone rubber. The material can be used for screening electromagnetic interference from telecommunications equipment, UHF and microwave radio systems, and computer controlled devices. It is claimed to provide 100dB of shielding between 20MHz and 10GHz. James Walker 0483-757575.

## Report backs digital TV

Channel 5, the proposed new TV channel, should be put on hold while the economics of launching a digital TV service are investigated, according to a report from Convergent Decisions, a specialist consultancy.

The report gives a boost to those in the BBC and elsewhere lobbying behind the scenes for channels 35 and 37 to be allocated to a new digital TV service.

A study produced last year by the Independent Television Commission suggested that the addition of these channels would not make much difference to the potential coverage of digital TV. But digital TV backers point out that channels 35 and 37 are unique because they are available across the whole country. This means they

could be used for a 'single frequency network', where one frequency is used to transmit the same digital TV channel across the whole country. Existing analogue terrestrial TV stations each require 44 frequency channels for national coverage.

● IBM Microelectronics unveiled a single chip MPEG-2 decoder at last month's National Association of Broadcasters conference in Las Vegas. The firm joins a highly competitive market already involving several major semiconductor firms including C-Cube, SGS Thomson and AT&T.

"You will not find anyone with a better price at the end of this year," said an IBM spokesman. He expects the price to fall to \$30 or less in volume production.

## Opto amplifier with bright prospects

BT has claimed a breakthrough in the transmission of broadband services direct to the home with the development of an optical amplifier which will work with optical pulses with a 1.3µm wavelength.

BT claims that the optical amplifier, developed in conjunction with Hewlett-Packard, will boost the optical signal by a factor of 1000 (30dB). According to group leader Dr Colin Millar, that will make it possible to transmit a 5Gbit/s data stream over 100km. "But these are very new results and it will be between two and five years before the amplifier is put into commercial service," said Millar.


The significance of this development compared to erbium-doped optical amplifiers, which are already in commercial service, is that because it boosts light at a wavelength of 1.3µm, it will work on the optical fibre systems commonly used in BT's national network. Erbium doped amplifiers operate at the less commonly used 1.55µm optical fibre window.

Operation at 1.3µm has been achieved by using a new type of optical fibre known as fluoride fibre. The amplifier incorporates a

20m length of fluoride fibre which has been chemically doped to promote energy transfer from one wavelength to a higher one. The dopant used is praseodymium (Pr<sup>3+</sup>).

The optical energy is transferred from a local source at 1.047µm to light at a wavelength of 1.3µm which may be used to boost the carrier signal. The energy transfer is mediated by the praseodymium ions which are incorporated into the core of the fluoride fibre. The local source is a Nd:YLF solid state laser, pumped by a low power diode laser, which emits the light at a wavelength of 1.047µm. The energy in light of this wavelength matches the energy needed to excite the Pr<sup>3+</sup> ions in the fibre.

The two optical signals, one from the local source and the signal to be amplified, travel together along the length of doped fibre. The photon energy of the 1.047µm pump light matches the energy difference between the low and excitation energy levels of the Pr<sup>3+</sup> dopant and the light is absorbed by the ions in the fibre. The excited ions are unstable, and the presence of the signal light at 1.3µm is sufficient to force the Pr<sup>3+</sup> ions to fall to a lower level and emit additional light at the

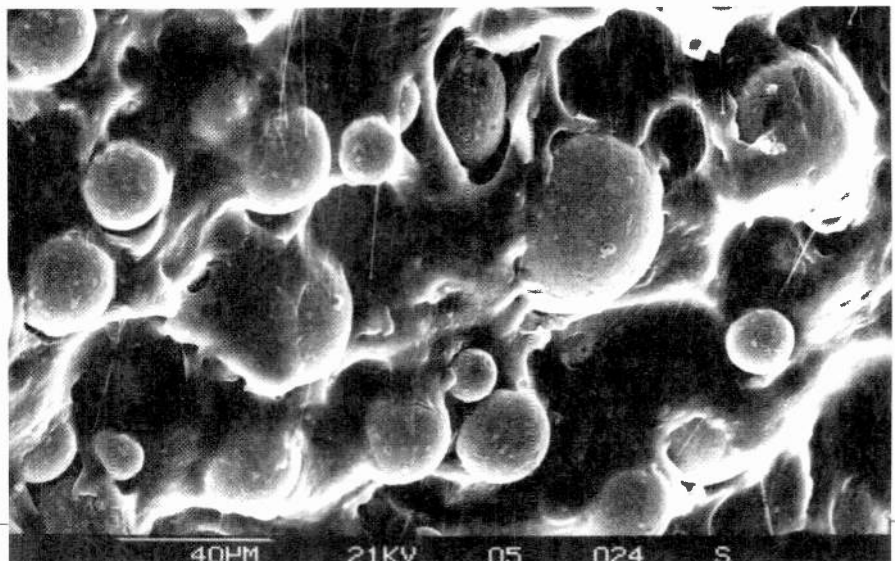

signal wavelength of 1.3 $\mu$ m.

The BT group's amplifier uses 500mW pump power to amplify the information signal by 30dB.

One problem BT found with using Pr<sup>3+</sup> doping ions in conventional silica fibre was that the excitation lifetime of the ions was too short for the secondary excitation to work. Hence the fluoride fibre with its longer excitation lifetime.

Although the 100 $\mu$ s lifetime in the fluoride fibre is still along way short of the 10ms lifetime of erbium dopant ions in conventional 1.55 $\mu$ m optical amplifiers, it was sufficient to support amplification.

The optical amplifier, which will work on BT's three million km of 1.3 $\mu$ m fibre, will enable the operator to increase capacity and reduce equipment costs on its trunk network. Using the amplifier on a single high bit rate carrier, BT is confident that it can support 5Gbit/s data transmission over 100km of fibre. This would extend the reach and capacity of BT's trunk network which currently uses 140 and 565Mbit/s data rates over 30km spans.

In addition, the amplifier's 40nm bandwidth will enable multiple signals, generated by wavelength division multiplexing, to be amplified by over 20dB.

**Richard Wilson**, *Electronics Weekly*

## PowerPC: "Pentium performance at half the price"

Growing support for the new PowerPC microprocessor from Motorola and IBM was demonstrated at Cebit last month, with systems on display from Germany's three largest indigenous PC makers, and new motherboard reference designs from Taiwanese and American companies.

The German trio of Vobis, Escom and Peacock are the first mass-market PC makers apart from Apple, to demonstrate systems containing the new chip. Although

none is shipping now, all were running early versions of Windows NT on the new microprocessor.

Peacock showed a server machine based on the Sandalford reference design from IBM. Asked why Peacock had opted for PowerPC, Peacock's marketing manager Christof Basener said: "We are not married to anyone in microprocessors. The PowerPC gives the performance of Pentium at half the price." **David Darcy**, *Electronics Weekly*

## PCBs for Douglas Self's power amplifier series

Circuit boards for Douglas Self's high-performance power amplifier are now available via *EW+WW*.

Detailed on page 139 of the February issue, Douglas Self's state-of-the-art power amplifier is the culmination of ideas from one of the most detailed studies of power amplifier design ever published in a monthly magazine. Capable of delivering up to 100W into 8 $\Omega$ , the amplifier features a distortion figure of 0.0015% at 50W and is designed around a new approach to feedback.


Designed by Douglas himself, the fibreglass boards have silk-screened component IDs and solder masking to minimise the possibility of shorts. Sold in pairs, the boards are supplied with additional detailed constructional notes.

Each board pair costs £45, which includes VAT and postage, UK and overseas. Credit card orders can be placed 24 hours on 081 652 8956. Alternatively, send a postal order or cheque made payable to Reed Business Publishing to *EW+WW*, The Quadrant, Sutton, Surrey SM2 5AS.

## SEETRAX CAE - RANGER - PCB DESIGN
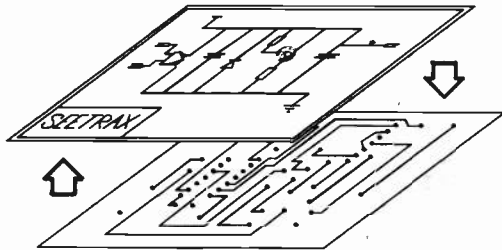
### Ranger1 £100

- \* Schematic capture linked to PCB
- \* Parts and wiring list entry
- \* Outline (footprint) library editor
- \* Manual board layout
- \* Full design rule checker
- \* Back annotation (linked to schematic)
- \* Power, memory and signal autorouter - £50



All systems upward compatible. Trade-in deals available.

Call **Seetrax CAE** for further information/demo packs.  
Tel 0705 591037 Fax 0705 599036

Seetrax CAE, Hinton Daubnay House, Broadway Lane,  
Lovedean, Hampshire, PO8 0SG

All trademarks acknowledged.

### Ranger2 £599

- All the features of Ranger1 plus**
- \* Gate & pin swapping (linked to schematic)
- \* Track highlighting
- \* Auto track necking
- \* Copper flood fill
- \* Power planes (heat-relief & anti-pads)
- \* Rip-up & retry autorouter

### Ranger3 £3500

- All the features of Ranger2 plus**
- \* UNIX or DOS versions
- \* 1 Micron resolution and angles to 1/10th degree
- \* Hierarchical or flat schematic
- \* Unlimited design size
- \* Any-shaped pad
- \* Split power planes
- \* Optional on-line DRC
- \* 100% rip-up & retry, push & shove autorouter

### Outputs to:

- \* 8/9 and 24 pin dot-matrix printers
- \* HP Desk/Laser Jet, Canon BJet, Postscript (R3 only)
- \* HP-GL, Houston Instruments plotters
- \* Gerber photoplotters
- \* NC Drill Excellon. Sieb & Meyer
- \* AutoCAD DXF

CIRCLE NO. 114 ON REPLY CARD



**VIEWDATA RETURNS** £6 made by Tandata, includes 1200.75 modem, k/bd, RGB and comp o/p, printer port. No PSU £6 MAG6P7

**IBM PC CASE AND PSU** Ideal base for building your own PC. Ex equipment but OK. £14.00 each REF: MAG14P2

**SOLAR POWER LAB SPECIAL** You get TWO 6"x6" 6v 130mA solar cells, 4 LEDs, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8

**SOLID STATE RELAYS** Will switch 25A mains. Input 3.5-26V DC 57x43x21mm with terminal screws £3.99 REF MAG4P10

**300DPI A4 DTP MONITOR** Brand new, TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £24.99. REF MAG25P1

**ULTRAMINI BUG MIC** 6mmx3.5mm made by AKG. 5-12v electret condenser. Cost £12 ea, Our? four for £9.99 REF MAG10P2

**RGB/CGA/EGA/TTL COLOUR MONITORS** 12" in good condition. Back anodised metal case. £99 each REF MAG99P1

**GX4000 GAMES MACHINES** returns so ok for spares or repair £9 each (no games). REF MAG9P1

**C64 COMPUTERS** Returns, so ok for spares etc £9 ref MAG9P2

**FUSELAGE LIGHTS** 3 foot by 4" panel 1/8" thick with 3 panels that glow green when a voltage is applied. Good for nightlights, front panels, signs, disco etc. 50-100v per strip. £25 ref MAG25P2

**ANSWER PHONES** Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF MAG18P1, BT Response 400's £25 ea REF MAG25P3 Suitable power supply £5 REF MAG25P12

**SWITCHED MODE PSU** ex equip, 60w +5v @ 5A, -5v @ 5A, +12v @ 2A, -12v @ 5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF MAG7P1

**PLUG IN PSU 9V** 200mA DC £2.99 each REF MAG3P9

**PLUG IN ACORN PSU** 19v AC 14w. £2.99 REF MAG3P10

**POWER SUPPLY** fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9

**ACORN ARCHEDES PSU** +5v @ 4.4A, on/off sw uncased, selectable mains input, 145x100x45mm £7 REF MAG7P2

**GEIGER COUNTER KIT** Low cost professional twin tube, complete with PCB and components. £29 REF MAG29P1

**SINCLAIR C6 13"** wheels complete with tube, tyre and cycle style bearing £6 ea REF MAG6P10

**AA NICAD PACK** encapsulated pack of 8 AA nicad batteries (tagged) ex equip. 55x32x32mm. £3 a pack. REF MAG3P11

**13.8V 1.9A** psu cased with leads. Just £9.99 REF MAG10P3

**360K 6.25** brand new half height floppy drives IBM compatible industry standard. Just £6.99 REF MAG7P3

**PPC MODEM CARDS** These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

**INFRA RED REMOTE CONTROLLERS** Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

**TOWERS INTERNATIONAL TRANSISTOR GUIDE.** A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: MAG20P1

**SINCLAIR C6 MOTORS** We have a few left without gearboxes. These are 12v DC 3,300 rpm 6"x4", 1/4" OP shaft. £25 REF: MAG25

**UNIVERSAL SPEED CONTROLLER KIT** Designed by us for the above motor but suitable for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

**VIDEO SENDER UNIT.** Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

**\*FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

**LOW COST WALKIE TALKIES** Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd

**\*MINATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x5x2155mm. Complete with cases and earpieces. 2xPP3 req'd. £30.00 pair REF: MAG30.

**COMPOSITE VIDEO KIT.** Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

**LQ3600 PRINTER ASSEMBLIES** Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc etc. In fact everything bar the case and electronics, a good stepper £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

**SPEAKER WIRE** Brown 2 core 100 foot hank £2 REF: MAG2P1

**LED PACK** of 100 standard red 5m leds £5 REF MAG5P4

**JUG KETTLE ELEMENT** good general purpose heating element (about 2kw) ideal for heating projects 2 for £3 REF: MAG3

**UNIVERSAL PC POWER SUPPLY** complete with flyleads, switch, fan etc. Two types available 150w at £15 REF: MAG15P2 (23x23x23mm) and 200w at £20 REF: MAG20P3 (23x23x23mm)

**\*FM TRANSMITTER** housed in a standard working 13A adapter!! the bug runs directly off the mains so lasts forever why pay £700? or price is £26 REF: MAG26 Transmits to any FM radio

**\*FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd. £5 REF: MAG5P5

**\*FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

**TALKING COINBOX STRIPPER** originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just £3 REF: MAG3P1

**100 WATT MOSFET PAIR** Same specs 2SK343 and 2SJ413 (8A, 140v, 100w) 1 N channel, 1 P channel, £3 a pair REF: MAG3P2

**VELCRO** 1 metre length of each side 20mm wide (quick way of fixing for temporary jobs etc) £2 REF: MAG2P3

**MAGNETIC AGITATORS** Consisting of a cased mains motor with lead. The motor has two magnets fixed to a rotor that spin round inside. There are also 2 plastic covered magnets supplied. Made for remotely stirring liquidst you may have a use? £3 each REF: MAG3P3

## BULL'S BULLSETN BOARD

**100MHZ DUAL TRACE  
OSCILLOSCOPES  
JUST £259  
RING FOR DETAILS**

**MASSIVE  
WAREHOUSE CLEARANCE  
FANTASTIC £20.00 REDUCTION  
REFURBISHED PC BASE UNITS  
COMPLETE WITH KEYBOARD**

**FROM ONLY £29.00  
AMSTRAD 1512 BASE UNITS  
GUARANTEED  
PERFECT WORKING ORDER.**

A LOW COST INTRODUCTION TO THE HOME COMPUTER MARKET.

**AMSTRAD 1512SD**  
1512 BASE UNIT, 5.25" FLOPPY DRIVE AND  
KEYBOARD. ALL YOU NEED IS A MONITOR AND  
POWER SUPPLY. WAS £49.00

NOW ONLY £29.00  
REF: MAG29

**AMSTRAD 1512DD**  
1512 BASE UNIT AND KEYBOARD AND TWO  
5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR  
AND POWER SUPPLY. WAS £59.00

NOW ONLY £39.00  
REF: MAG39

## SOLAR POWER PANELS

**3FT X 1FT 10WATT GLASS PANELS  
14.5v/700mA  
NOW AVAILABLE BY MAIL ORDER  
£33.95**

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A  
TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE  
APPLICATIONS. SOME OF WHICH MAY BE CAR BATTERY  
CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANY  
WHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

## FREE SOFTWARE!

Brand new, UNUSED top quality Famous brand  
licensed software discs. Available in 5.25" DSD or 5.25"  
HD only. You buy the disk and it comes with free BRAND  
NEW UNUSED SOFTWARE. We are actually selling you the  
floppy disc for your own "MEGA CHEAP" storage facilities,  
if you happen to get software that you want/need/like as  
well..... you get a "MEGA BARGAIN" too!

DSD or PKTIC £2.99 REF: MAG37 PKT100 £15.00 REF: MAG16

\*\*\*\*\*WE BUY SURPLUS STOCK\*\*\*\*\*

TURN YOUR SURPLUS STOCK INTO CASH.  
IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR  
COMPLETE FACTORY CLEARANCE.

## 1994 CATALOGUE.

PLEASE SEND 45P, A4 SIZED SAE FOR YOUR FREE COPY.  
MINIMUM GOODS ORDER £5.00 TRADE ORDERS FROM GOVERNMENT, SCHOOLS,  
UNIVERSITIES, & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO  
OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30  
DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR  
NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILL ONLY BE GIVEN FOR QUANTITIES  
HIGHER THAN THOSE STATED.

\*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

## BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX  
BN3 5QT

MAIL ORDER TERMS: CASH PO OR CHEQUE  
WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY

TELEPHONE ORDERS WELCOME

TEL: 0273 203500

FAX: 0273 323077



CIRCLE NO. 106 ON REPLY CARD

**TOP QUALITY SPEAKERS** Made for HI FI televisions  
these are 10 watt 4R Jap made 4" round with large  
shielded magnets. Good quality general purpose speaker.  
£2 each REF: MAG2P4 or 4 for £6 REF: MAG8P2

**TWEETERS** 2" diameter good quality tweeter 140R (ok with the  
above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

**AT KEYBOARDS** Made by Apricot these quality keyboards need  
just a small modification to run on any AT, they work perfectly but you  
will have to put up with 1 or 2 foreign keycaps! Price £6 REF:  
MAG4P3

**XT KEYBOARDS** Mixed types, some returns, some good, some  
foreign etc but all good for spares! Price is £2 each REF: MAG2P6  
or 4 for £6 REF: MAG8P4

**PC CASES** Again mixed types so you take a chance next one off  
the pile £12 REF: MAG12 or two the same for £20 REF: MAG20P4

**COMMODORE MICRODRIVE SYSTEM** mini storage  
device for C64's 4 times faster than disc drives, 10 times faster  
than tapes. Complete unit just £12 REF: MAG12P1

**SCHOOL STRIPPERS** We have quite a few of the above  
units which are 'returns' as they are quite comprehensive units  
they could be used for other projects etc. Let us know how many you  
need at just 50p a unit (minimum 10).

**HEADPHONES 16P** These are ex Virgin Atlantic. You can have  
8 pairs for £2 REF: MAG2P8

**PROXIMITY SENSORS** These are small PCB's with what look  
like a source and sensor LED on one end and lots of components on  
the rest of the PCB. Complete with flyleads. Pack of 5 £3 REF: MAG:  
3P5 or 20 for £8 REF: MAG8P4

**SNCOOPERS EAR?** Original made to dip over the earpiece of  
telephone to amplify the sound-it also works quite well on the cable  
ringing along the wall! Price is £5 REF: MAG5P7

**DOS PACKS** Microsoft version 3.3 or higher complete with all  
manuals or price just £5 REF: MAG5P8 Worth it just for the very  
comprehensive manual! 5.25" only.

**DOS PACK** Microsoft version 5 Original software but no manu-  
als hence only £3 REF: MAG3P6 5.25" only

**FOREIGN DOS** 3.3-German, French, Italian etc £2 a pack with  
manual. 5.25" only. REF: MAG2P9

**CTN 644 COLOUR MONITOR.** Made to work with the CPC464  
home computer. Standard RGB input so will work with other ma-  
chines. Refurbished £59.00 REF: MAG59

**PIR DETECTOR** Made by famous UK alarm manufacturer these  
are hi spec, long range internal units. 12v operation. Slight marks on  
case and unboxed (although brand new) £8 REF: MAG8P5

**WINDUP SOLAR POWERED RADIO** AM/FM radio complete  
with hand charger and solar panel! £14 REF: MAG14P1

**COMMODORE 64 TAPE DRIVES** Customer returns at £4  
REF: MAG4P9 Fully tested and working units are £12 REF: MAG12P5

**COMPUTER TERMINALS** complete with screen, keyboard and  
RS232C input/output. Ex equipment. Price is £27 REF: MAG27

**MAINS CABLES** These are 2 core standard black 2 metre mains  
cables fitted with a 13A plug on one end, cable the other. Ideal for  
projects, low cost manufacturing etc. Pack of 10 for £3 REF: MAG3P8  
Pack of 100 £20 REF: MAG20P5

**SURFACE MOUNT STRIPPER** Originally made as some form  
of high frequency amplifier (main chip is a TSA5511T 1.3GHz  
synthesiser) but good stripper value, an excellent way to play with  
surface mount components £1.00 REF: MAG1P1.

**MICROWAVE TIMER** Electronic timer with relay output suitable  
to make enlarger timer etc £4 REF: MAG4P4

**MOBILE CAR PHONE £6.99** Well almost! complete in car  
phone excluding the box of electronics normally hidden under seat.  
Can be made to illuminate with 12v also has built in light sensor so  
display only illuminates when dark. Totally convincing! REF: MAG6P6

**ALARM BEACONS** Zenon strobe made to mount on an external  
bell box but could be used for caravans etc. 12v operation. Just  
connect up and it flashes regularly! £5 REF: MAG5P11

**FIRE ALARM CONTROL PANEL** High quality metal cased  
alarm panel 350x165x80mm. With key. Comes with electronics but  
no information. sale price 7.99 REF: MAG8P6

**SUPER SIZE HEATSINK** Superb quality aluminium heatsink.  
365 x 183 x 61mm, 15 fins enable high heat dissipation. No holes!  
sale price £5.99 REF: MAG6P11

**REMOTE CONTROL PCB** These are receiver boards for  
garage door opening systems. You may have another use? £4 ea  
REF: MAG4P5

**6"x12" AMORPHOUS SOLAR PANEL** 12v 155x310mm  
130mA. Bargain price just £5.99 ea REF: MAG6P12.

**FIBRE OPTIC CABLE BUMPER PACK** 10 metres for £4.99  
ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

**LOPTX** Line output transformers believed to be for hi res colour  
monitors but useful for getting high voltages from low ones! £2 each  
REF: MAG2P12 bumper pack of 10 for £12 REF: MAG12P3

**SHOP OPEN 9-5.30 SIX  
DAYS A WEEK**

## PORTABLE RADIATION DETECTOR

**£49.99**

A Hand held personal Gamma and X Ray detec-  
tor. This unit contains two Geiger Tubes, has a 4  
digit LCD display with a Piezo speaker, giving an  
audio visual indication. The unit detects high  
energy electromagnetic quanta with an energy  
from 30K eV to over 1.2M eV and a measuring  
range of 5-9999 UR/h or 10-99990 Nr/h. Supplied  
complete with handbook.

REF: MAG50

# RESEARCH NOTES

## Smallest piece of metal in the world

A single atom of a metallic element behaves very differently from the bulk metal. But at what size does that transformation start to happen? Workers at the Universities of Leiden in Holland and Essen in Germany have been searching for an answer which could have important ramifications for electronic devices.

Most of us are familiar with some of the strange quantum effects that occur as structures get smaller and smaller. Many electronic and opto-electronic devices depend for their function on such counter-intuitive phenomena as electron tunnelling.

But it is not just that ultra-small structures behave in a different way: in many respects they are different.

Any school child knows that one atom is the smallest unit of a chemical element. But if scientists were able to isolate a single atom of, say platinum (which is virtually possible thanks to scanning tunnelling microscopy), it would certainly not look or behave like a metal.


Bulk metallic properties depend essentially on the highest energy bands of electrons – the conduction and valence bands – from which electrons are shared freely between all the atoms in the lump. It is these relatively free electrons that are responsible for such features as metallic

appearance and electrical conductivity. But if a lump of metal were progressively chopped up into smaller pieces, there would come a point when the electrons would lose their mobility and the metal would stop being a metal.

The team from Leiden and Essen performed experiments (*Nature*, Vol 367, No 6465) to try to discover the number of atoms below which this metal to non-metal transition occurs. Reducing the number of atoms in a lump of platinum was achieved, not with a knife, but by clever chemical synthesis of platinum cluster compounds.

Under professor Leenert de Jongh, the researchers created a whole range of compounds built round a central polyhedral cluster of platinum atoms. The atoms exist only in complete onion-like shells with well defined numbers. The Pt<sub>309</sub> cluster is a four-shell member of an *n*-shell magic number series that goes 1, 13, 55, 147, 309, 561...

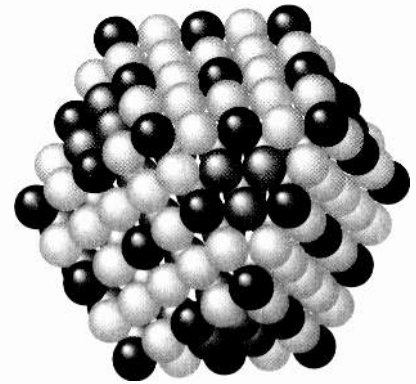Using Mössbauer spectroscopy to examine each shell of the platinum onion, de Jongh and his team were able to discover something of the electronic environment of the atoms in each shell – this being a sensitive test of 'metallicity'. What they found was that the electrons associated with the 147 atom cluster behaved with the same freedom as they do in a piece of bulk



**At somewhere below 147 atoms, platinum clusters stop behaving like a metal.**

platinum: a 147-atom chunk of platinum behaves as a metal.

But in an earlier experiment, with gold clusters, de Jongh found that a 13-atom cluster did *not* exhibit metallic properties. So he concludes that, somewhere between 147 and 13 atoms, there is a transition between metal and non-metal.

It all may look extremely esoteric and theoretical. Until we remember that the properties of very small quantities of materials are becoming increasingly important, not just for electronic devices, but also for environmentally important chemical devices such as catalysis.

## Shooting at the stars

Jules Verne's idea of shooting a satellite into space from the muzzle of a gun, looks like becoming science fact, thanks to the efforts of a group working at the Lawrence Livermore National Laboratory in California.

The continuing attractiveness of Verne's idea, dreamed up more than a century ago, stems from the extraordinary inefficiency of today's rockets, 95% of whose take-off weight consists of fuel. To put a kilogram of human into orbit costs about \$20,000 – or about half that for an unmanned launch.

As John Hunter of LLNL put it rather graphically on a BBC *World Service* programme: "Right now, the cost of putting any object into low Earth orbit is the object's weight in gold."

Using a huge gun to shoot an object into space has a wonderful simplicity about it, at least from the theoretical point of view. It would have far fewer moving parts than the now-standard three-stage rocket.


Verne clearly had in mind something like the ill-fated Iraqi supergun, powered by conventional gunpowder. All very simple – until you try the calculations. Even back-of-envelope sums show that to reach escape

velocity with a conventional type of gun would require impossibly-oversized engineering.

So Hunter and his team at LLNL have adopted a different approach, albeit with slightly more modest immediate objectives. They have developed what amounts to the biggest air-pistol in the world, extending the principles used in current high-velocity laboratory gas guns.

The basic idea behind such guns – many of which can accelerate a rifle bullet-sized object to 25,000 mile/h – is to compress hydrogen gas behind a rupture valve which suddenly releases the gas, propelling the projectile down a barrel.

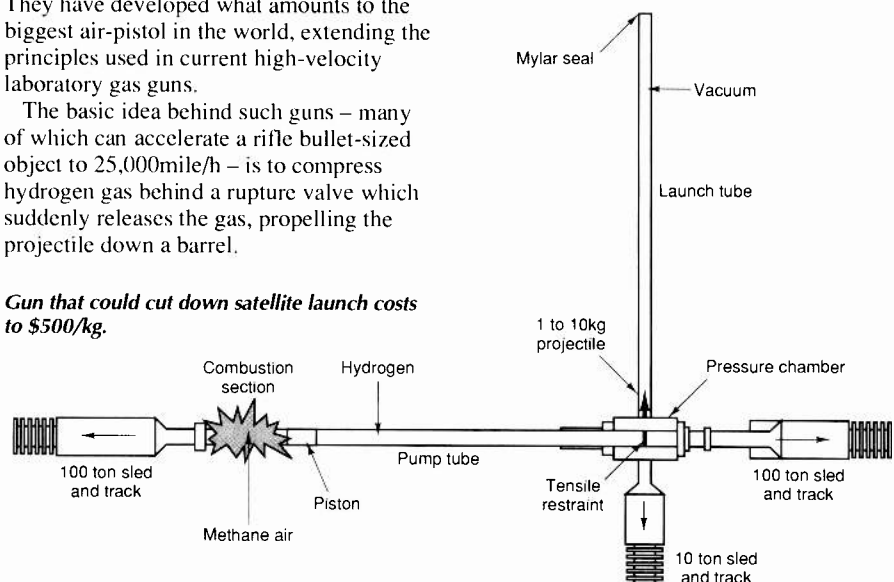**Gun that could cut down satellite launch costs to \$500/kg.**





*Supersonic launch from a light-gas gun, right and a projectile – a scramjet – in flight at Mach 8 just before entering a retaining bunker, above. In-flight glow is caused by the engine's hydrogen fuel and air friction. Flames on the right are hydrogen used to accelerate the jet along the 4in launch tube.*

piston is propelled by a methane/air charge. This rapidly heats the hydrogen in the tube, compressing it to 7000lb/in<sup>2</sup> and rupturing a tensile restraint. The hydrogen then rushes into the launch tube, driving the projectile up the tube at 9000mile/h (10 and 100t sleds are designed to absorb the recoil forces).

So far projectiles up to 10kg have been flung into the hillside with the launch tube horizontal, though the team are hoping to conduct vertical launch tests at sites such as the Vandenberg Air Force Base in California. In the course of these tests they want to discover, for example, how their projectiles fare during their high velocity transit through the atmosphere. There would be little point in shooting satellites into space if they burnt out on the way up!

Parallel research is aimed at scaling up even this monster gun to something that would enable the team to launch a missile into orbit. Success will demand a yet-newer and more advanced approach, such as the development of a piston-less pump tube. Calculations show that while the necessary 3km-long launch tube could be made, the



existing style of pump-tube exceeds current engineering limits. One idea being explored is a launch tube in which hot compressed hydrogen is injected at various intervals along the tube, just behind the passing projectile. This would provide progressive acceleration to around 25,000mile/h without exceeding engineering limits.

Obviously such a system, if it ever comes to fruition, would not be able to launch people (or even fragile satellites) into orbit.

The acceleration would be destructively great. But as Hunter points out, much of the material that would be needed to construct a space station would not be at all delicate. He also estimates that, at a rate of one launch per day, the cost of shooting material into orbit with a gun would be a mere \$500/kg – vastly less than with today's rocketry – with less than 10s needed to get into orbit.

Simple satellites, says Hunter, will be shot into space by the year 2001.

## Electrons exhibit brittle behaviour

**M**etals are soft and malleable: non-metals on the other hand – whether elements or composites – are comparatively hard and brittle. Now scientists in California think they can use electronic behaviour to explain why.

At a superficial level, hardness is explained by the mobility of electrons associated with atoms. In metals these move relatively freely, whereas in covalent solids the electrons are tightly paired up.

At a structural level, the hardness of a material such as silicon is a feature of the slowness with which natural dislocations propagate through the material. Dislocations are lines in a crystal where the atoms are not perfectly arranged – a bit like a wrinkle in a

carpet. For a material to deform plastically without breaking, dislocations must propagate relatively quickly, as they do in most pure metals. But, until recently, no-one has been able to understand (at the electronic level) why the propagation of dislocations is so slow in hard materials like silicon.

John Gilman of the Lawrence Berkeley Laboratory in California has now analysed how the electronic structure of silicon changes as a dislocation slowly moves its way through the crystal.

Gilman says (*Science*, Vol 261, 1436) that dislocation lines do not move in a concerted fashion; instead they move through kinks that lie along their length. The overall rate at which a dislocation moves is determined by

the mobility of the kinks. For a kink to move, says Gilman, it has to separate a pair of electrons that lie in its way.

In the case of a hard solid like silicon, the relative slowness with which dislocations propagate is now seen to be a feature of the strength with which pairs of electrons are bound together. The greater the bonding energy, the harder the material.

By calculating the relationship between kink mobility and the electronic structure of a material Gilman has now been able to determine in detail why other important materials such as germanium and silicon carbide have the physical properties they do, and how these properties vary with temperature.



## Disk technology's resistance to change

Scientists at Argonne National Laboratory in Illinois have established what they claim is a record for 'giant magnetoresistance'. The effect – an unprecedented change in bulk resistance as a magnetic field is applied – has been produced by

manufacturing a superlattice of iron and chromium consisting of alternate layers of each material. The layers are about a million times thinner than a sheet of paper and are produced by magnetron sputtering — a process already employed industrially.

*Using a cone-shaped electromagnet to apply a strong magnetic field to Argonne's record breaking giant magnetoresistant material. A 250% decrease in resistance is the result.*



When a magnetic field is applied to the structure, cooled with liquid helium, its resistance drops by a factor of 2.5, beating the previous record of a two-fold reduction. Argonne's figure can also be compared with the 1-2% change typical of most magnetoresistive materials.

The potential value of material exhibiting such a large change of resistance is in the measurement of tiny magnetic fields. Any given change in magnetic field produces a proportionately bigger electrical signal.

'Read' heads for extracting data from magnetic disks is one of the applications envisaged by the Argonne team. For this purpose, the new material is said to be about 75 times more sensitive than the nickel-iron alloys currently in use. The benefit would be that disks could be spun faster and memory access time reduced. Other possible applications include position sensors in robotics and industrial automation.

The Argonne researchers are now concentrating on creating materials that will exhibit the same giant magnetoresistive effect with lower magnetic fields. ■

*Research Notes is written by John Wilson of the BBC World Service.*

# KENWOOD

TEST & MEASURING INSTRUMENTS  
A SUPERB RANGE OF OVER 100  
QUALITY INSTRUMENTS.

Available from  
**B.K. ELECTRONICS**



- FM-AM Signal Generators ★ Colour Pattern Generators ★ Video Signal Analyser ★ Video Timing Analyser ★ Video Noise Meter
- ★ Distortion Meter ★ Waveform Monitors
- ★ Vectorscopes ★ Audio Generators ★ Wow and Flutter Meters ★ Electronic Voltmeters
- ★ Digital Multimeters ★ Function Generators
- ★ Frequency Counters ★ Bus Analyser
- ★ Resistance Attenuator ★ Oscilloscopes ★ Fully Programmable Digital Storage Oscilloscopes
- ★ Regulated D.C. Power Supplies

A free, 50 page colour brochure, including price list, is available on request. Please make your request on company headed notepaper, by post or by fax, to:

**B.K. ELECTRONICS**  
Unit 1 Comet Way,  
SOUTHEND-ON-SEA,  
Essex, SS2 6TR.  
Tel.: 0702-527572  
Fax: 0702-420243



CIRCLE NO. 107 ON REPLY CARD

Z8 Z80 Super8

6502 65816

68HC11

68000...

8051...

from only **£69**

and many more

COMPILERS  
CROSS-  
ASSEMBLERS  
SIMULATORS

Call for data sheets

Tel: 081-441 3890  
Fax: 081-441 1843

**SMART**  
COMMUNICATIONS

CIRCLE NO. 108 ON REPLY CARD

**COMPUTER ICs**

Table listing various computer ICs such as P8271 BBC DISC CONTROLLER CHIP, SAA5050 TELETEXT CHIP, and others with their respective prices.

Table listing various electronic components like 100nF 63V X7R PHILIPS SURFACE MOUNT, 10Nf 63V X7R PHILIPS SURFACE MOUNT, and other resistors and capacitors.

Table listing bridge rectifiers like 6A 100V SIMILAR MR751, 1A 600V BRIDGE RECTIFIER, etc.

**SCFS**

Table listing Pulse Transformers like PULSE TRANSFORMERS 1.1 + 1, 2P4M EQUIV C106D.

**TRIACS**

Table listing Triacs like NEC TRIAC AC08F 8A 600V TO220, TXAL225 8A 500V 5mA GATE.

**CONNECTORS**

Table listing various connectors like D25 IDC PLUG OR SOCKET, 34-way card edge IDCCONNECTOR, etc.

**PHOTO DEVICES**

Table listing photo devices like HI BRIGHTNESS LEDs COX24 RED, SLOTTED OPTO-SWITCH OPCOA OPB615.

**STC NTC BEAD THERMISTORS**

Table listing NTC bead thermistors like G22 220R, G13 1K, G23 2K, etc.

**CERMET MULTI TURN PRESETS 3/4"**

Table listing Cermet multi-turn presets like 10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K 50K.

**IC SOCKETS**

Table listing IC sockets like 14/16/18/20/24/28/40-WAY DIL SKTS, 8-WAY DIL SKTS.

**POLYESTER/POLYCAP CAPS**

Table listing polyester/polycap capacitors like 330nF 10% 250V AC X2 RATED PHILIPS TYPE 330, 100nF 200nF 63V 5mm.

**RF BITS**

Table listing RF bits like MARCONI MICROWAVE DIODES TYPES DC2929, DC2962, DC4229F1/2.

**CERAMIC FILTERS 4M5/6M/9M/10M7**

Table listing ceramic filters like FEED THRU CERAMIC CAPS 1000pF, SL610, 6 VOLT TELEDYNE RELAYS 2 POLE CHANGEOVER.

**PLESSEY ICs EX-STOCK**

Table listing Plessey ICs like SL350G SL360G SL362C SL403D SL423A.

**MONOLITHIC CERAMIC CAPACITORS**

Table listing monolithic ceramic capacitors like 10n 50V 2.5mm, 100n 50V 2.5mm or 5mm.

**KEYTRONICS**

TEL. 0279-505543  
FAX. 0279-757656

P O BOX 634  
BISHOPS STORTFORD  
HERTFORDSHIRE CM23 2RX

SEND £1 STAMPS FOR CURRENT IC + SEMI STOCK LIST - ALSO AVAILABLE ON  
3 1/2" FLOPPY DISK

**MAIL ORDER ONLY**

MIN CASH ORDER £5.00 OFFICIAL ORDERS WELCOME  
UNIVERSITIES/COLLEGES/SCHOOLS/GOVT DEPT.MENTS  
MIN. ACCOUNT ORDER £10.00  
P&P AS SHOWN IN BRACKETS (HEAVY ITEMS) OTHERWISE 99p

ADD 17 1/2% VAT TO TOTAL  
ELECTRONIC COMPONENTS BOUGHT FOR CASH







*Opto-electronic components find wide usage in measurement, production control, scientific and consumer applications. Nearly all uses have a common requirement for photodetection in the presence of ambient lighting while others must preserve system bandwidth. **Tore Nielsen** presents a circuit designer's guide to opto-electronics.*

# OPTO-ELECTRONICS BY DESIGN

**L**ight sensitivity is common to all semiconductors but the effect is optimised in the photodiode. It may be thought of as a current generator controlled by light. The current generator aspect is almost ideal: the main limitation is the parallel capacitor intrinsic to the relatively large semiconductor junction, and the diode characteristic if the diode is forward biased. The latter may even be considered a feature in some applications.

Silicon photodiodes are sensitive to wavelengths from 400nm to 1100nm which takes in the visible spectrum from 400nm to 700nm, but the sensitivity peaks at 900nm in the near infrared spectrum. Germanium photo devices operate from 400nm to 1800nm with a peak around 1500nm. They exhibit a lower sensitivity in the visible range than the silicon diode.

The photo current is proportional to the illumination for eight or more decades, and is downward limited only by the dark current (leakage current) which may be as low as 5pA for some diodes. **Fig. 1** shows the equivalent circuit for a photodiode

## Photodiode interface

The photodiode is easily interfaced to an inverting amplifier (**Fig. 2**). The low input resistance at the inverting input effectively shorts the diode thus reducing the

influence of the parallel capacitor. The output voltage, the product of  $R_1 \times I_p$ , is proportional to light and positive with respect to ground.

Typical device sensitivity would be about 80nA/lx (*see box for an explanation of the lux unit*). With feedback resistor  $R_1$  set at 120k $\Omega$  the output voltage equals 10mV/lx, saturating the amplifier at 1000lx. The output could feed a comparator to initiate some action when the input exceeds a certain level, or the circuit could be used in a feedback loop to control illumination.

The classic use for an infrared receiver is to detect an optical pulse stream from a remote control handset or whatever. The absolute level of the illumination is unimportant and is rejected with a differentiating network. This is the idea behind **Fig. 3** where the photodiode is reverse biased and capacitively coupled to the amplifier. High pass filter time constant  $CR_2$  could also be used to suppress low frequency interference. Reverse biasing may increase the sensitivity slightly for some photodiodes, but the main purpose is to accept the photo current emerging from the absolute level of illumination without affecting the function. If  $R_2$  is 10k $\Omega$ , the circuit would accept some 15000lx before forward biasing the diode.

The bias resistor may inject noise from the power sup-



ply into the amplifier input with a gain of  $R_1/R_2$ . The photodiode power supply should be decoupled to reduce this effect.

The transient response of the circuit tends to be limited by amplifier performance rather than the response of the photodiode; risetime of the photodiode is typically 20ns when feeding a 50Ω load.

If the photodiode is connected to the high impedance input of the amplifier (Fig. 4), the photo current develops a voltage across the diode, creating a forward voltage across the junction. This varies logarithmically with current – some 60 to 100mV/decade – and would typically be about 450mV at 1000lx effectively compressing the useful luminance range to a convenient scale. A microprocessor fitted with a suitable a to d converter can convert this directly to light measurement units.

The following design originated from this basic circuit.

**Light meter**

The light meter in Fig. 5 uses two photodiodes with different optical filters, to create an instrument for measurement in the visible light or near infrared spectrum. The sensitivity characteristics of the two photodiodes are shown in Fig. 6. The optical bandpass filters are centred at 550nm (green) and 950nm (infrared) and are approximately 200nm wide.

The instrument features a peak hold rectifier for pulse measurement and an output for an oscilloscope. The logarithmic conversion could have used the photodiodes, but the pulse response was too slow to be of practical use. Logarithmic conversion diodes were used instead. If the instrument is intended for operation below 1lx then the 1N4148 diode should be substituted with a low leakage type. The instrument is calibrated by the injection of a known (negative) current at the virtual ground node of the input amplifiers.

The Siemens BPW21 has a sensitivity of 10nA/lx, so 1mA should read 100000lx on the instrument scale. The current is reduced in decade steps for the other readings down to 1lx. The BPW21 is specified to 0.01lx.

The Siemens BP104 has a sensitivity of 17µA at 0.5mW/cm<sup>2</sup> and 950nm. This corresponds to 3.4µA at an irradiance of 1W/m<sup>2</sup>. For 1kW/m<sup>2</sup> the current is 3.4mA, and read-

ings are obtained in decade steps down to 1mW/m<sup>2</sup>.

Bright sunlight has the equivalent radiance of 1kW/m<sup>2</sup>.

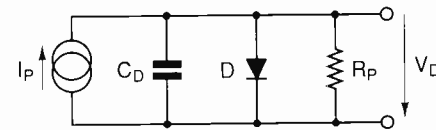


Fig. 1. Equivalent circuit for the photodiode. The capacitance is 10 to 500pF, and the resistance represents the leakage current.

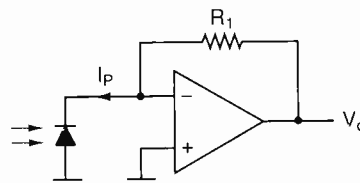


Fig. 2. Photo detector for high speed operation. Output is proportional to illumination level.

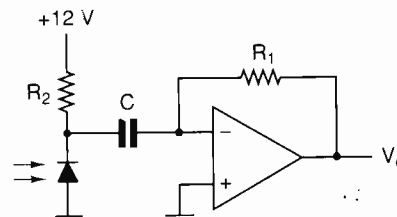


Fig. 3. Photo diode capacitively coupled to increase the amount of extraneous light accepted and to suppress low frequency interference.

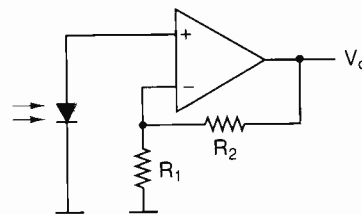


Fig. 4. Photo detector with output voltage proportional to the logarithm of the photo current for eight or more decades.

The circuit exhibits a temperature coefficient of approximately -0.5 %/°C, primarily caused by the 1N4148 diode forward voltage change with temperature. It thus requires some form of temperature compensation for serious use. The basic instrument read correctly over the range 1 to 5000lx compared to a Gossen luxmeter using a tungsten filament lamp source. Fluorescent lamps illuminating 2000lx read some 50% low.

This is because the BPW21 is specified for use with a tungsten filament lamp. The photodiode sensitivity above 700nm adds extra energy from the filament lamp infrared radiation. This radiation is missing in the fluorescent lamp, leading to under reading.

No comparison against a reference has been performed in the infrared spectrum.

**The infrared emitter diode**

Popular infrared emitting diodes come in two sorts: 880nm GaAlAs diode and the 950nm GaAs diode. The emitted spectrum (Fig. 7) indicates a good match between a GaAlAs emitter and the unfiltered photodiode, and between a GaAs emitter and the IR filtered photodiode.


Visible leds may of course be used as light sources, but the photodiode efficiency is reduced significantly below 900nm and the current rating of the visible light emitting diode is lower. In addition the interference from visible light sources, such as fluorescent lamps, are hard to eliminate without filtration.

Detection of objects on a conveyer belt represents a typical application. Fig. 8 shows a minimalist interrupter circuit. The Telefunken CQX47 IR led develops a radiant intensity of 0.033W/sr at 950nm at 100mA, giving an irradiance of 0.033W/m<sup>2</sup> at 1m distance.

The receiving diode photocurrent develops a voltage across the 33kΩ series resistor. To reach the 3.3V needed to switch the 74HC14 Schmitt gate, the photocurrent should reach 100µA. The Telefunken BPV23F photodiode sensitivity is 6µA at 1W/m<sup>2</sup>. This equates to an irradiation of 16W/m<sup>2</sup> to produce 100µA photocurrent.

The required distance between emitter and photodiode is easily found by iteration. Reducing the distance to a tenth of the previous distance increases the irradiation one hun-

Fig. 5. Battery powered light meter with selectable visible light or near infrared light filters. Optional peak hold rectifier (minimum 50µs pulse width) and output to oscilloscope.

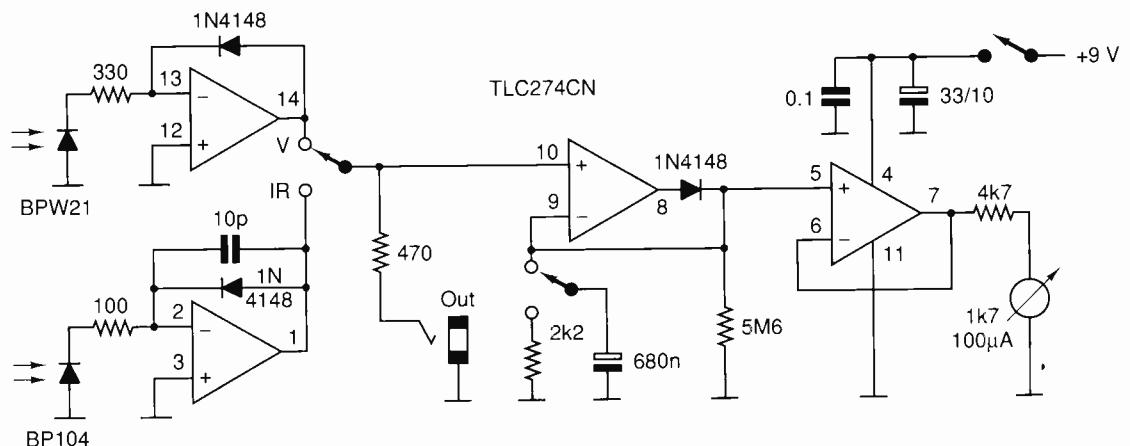

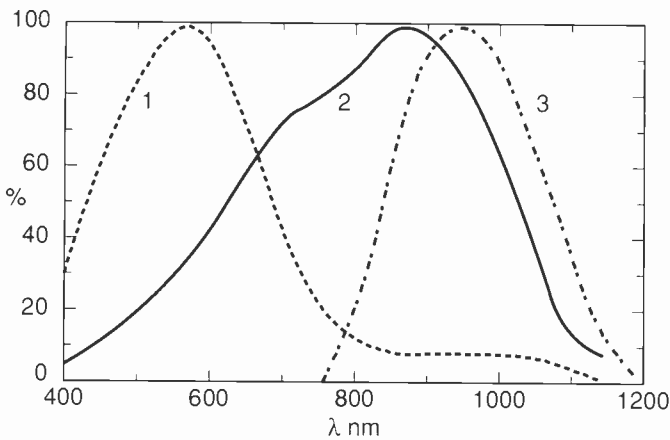


Fig. 6. Relative sensitivity of (1) BPW21 photodiode with daylight filter, (2) BPX43 photo transistor without filter and (3) BP104 photodiode with infrared filter.

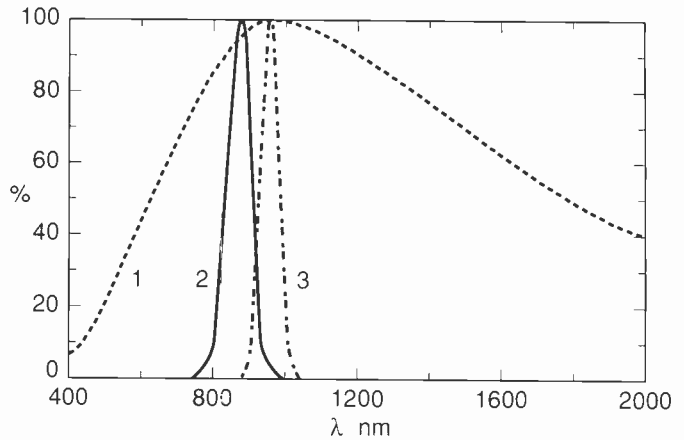


Fig. 7. Power distribution of (1) a tungsten filament lamp, (2) GaAlAs infrared emitting diode at 880nm and (3) GaAs infra red emitting diode at 950nm.

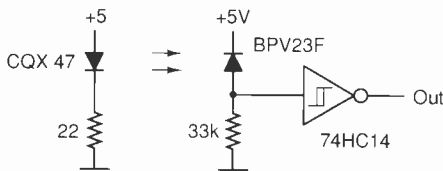


Fig. 8. Optical reader with 45mm detection range. See text for a discussion of the power dissipation.

dred times to 3.3W/m<sup>2</sup> at 100mm. Reducing the distance by a half increases the irradiation four times to 13.2W/m<sup>2</sup> at 50mm. Reducing the distance 10% increases it by 21% to the required 16W/m<sup>2</sup> at 45mm distance.

Calculated distance is based on typical val-

ues of emitter diode efficiency and photodiode sensitivity. The tolerance is approximately +50, -30% for both the led and photodiode.

Increasing separation distance between led and photodiode requires a square law power increase. Two series connected diodes would double the radiated power, increasing maximum separation by 1.4 times the distance available with one diode. Doubling the separation requires four diodes, etc.

The speed of the reader is set by the diode capacitance (20pF), the 74HC14 input capacitance (7pF) and the load resistor (33kΩ), a time constant of 1μs, so the reader should catch up with almost any moving object.

With 100mA forward current and a terminal voltage of 2.8V the power dissipation in the led is 0.28W, and with a thermal resistance of

270°C/W, the resulting temperature rise is 76°C. The led exhibits a power output temperature coefficient of -0.8%/°C resulting in a loss of some 60% of the emission. The diode should not normally be used in continuous mode at 100mA forward current.

At higher output intensity the led must be pulsed. This opens possibilities for modulated carrier systems.

**Pulsed transmitter**

The transmitter circuit shown in Fig. 9 produces high intensity pulses. The radiant intensity of the Siemens LD274-2 IR led is between 50 and 100mW/sr at 100mA, producing a typical 0.33W/sr at the peak current level of 450mA. The pulse width of 5μs is a practical lower limit for pulsed operation since the

**Power, radiation and calibration**

The earth receives approximately 1 kW/m<sup>2</sup> from the sun at the surface of the earth. Photodiode conversion efficiency is approximately 0.6A/W at wavelengths approaching the maximum sensitivity. If the photodiode has an active area of 1mm<sup>2</sup>, the received power would equal 1mW, generating 0.6mA of current.

A BPX43 photo transistor with a glass lens generated 2mA in the collector-base diode (and 1mA in the emitter-base diode) when subjected to direct sunshine. With an active area of 0.675mm<sup>2</sup> this indicated an effective magnification of about five times due to the lens action.


A tungsten lamp filament is heated with the intention of creating visible light. Most of the radiation is infrared, invisible to the human eye. Just one tenth falls inside the visible range. A third is radiation below 1100nm, useful to the photodiode, while the remaining two thirds are wasted as heat.

The radiated power from a domestic 40W bulb can be considered equally distributed in any direction. If this light source is placed at the centre of a sphere of radius R (Fig. a), the power P is distributed across the sphere surface of 4πR<sup>2</sup>, creating an irradiation of,

$$E_e = P/4\pi R^2 = 3.2W/m^2$$

at a radius of 1m. At wavelengths visible to the photodiode the useful irradiation is approximately one third of the total or 1W/m<sup>2</sup>.

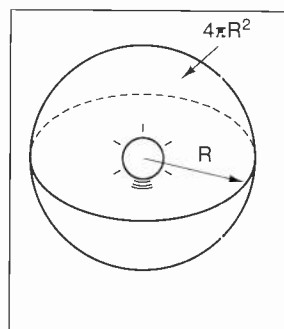The illumination from the 40W bulb was measured to 400lx at



0.3m, indicating a correlation between illumination and irradiation of 40lx to 1W/m<sup>2</sup>. This correlation is valid only for filament lamps operating at the same filament temperature, approximately 2500K.

A higher filament temperature will produce more visible light. At 3000K the correlation is 60lx to 1W/m<sup>2</sup>, at 4000K 100lx to 1W/m<sup>2</sup>. Photo components are usually specified at a filament

temperature (colour temperature) of 2856K (standard light A) and the above correlation enables one to perform an approximate conversion between lx and W/m<sup>2</sup>. These figures should not be used for sources other than incandescent lamps.

Mains ac modulates lamp output to a depth of approximately 30% with a ripple frequency of 100Hz. This should be borne in mind when designing opto-electronics.

The fluorescent lamp produces mainly visible light although some infrared radiation will be present, probably below 10% of the total. The light may be amplitude modulated by a frequency of 5 to 40kHz from electronic ballasts. Interference from fluorescent lamps may be reduced by optical filters.

device switching time is 1µs.

The led has a half power angle of ±10° but the main intensity is concentrated in a narrow beam within ±4°. This often causes alignment problems at extreme range.

Input gating switches the transmitter on or off. The 4.7µF filter capacitor may be omitted for decreased switching time. However, this results in a slightly distorted pulse waveform.

With the receiver shown in Fig. 8, the pulsed transmitter switches the 74HC14 buffer at 140mm (170mm actually measured) as compared to the calculated 45mm distance attainable with the linear system. The pulsed operation will of course introduce some circuit complications notably some sort of sample/hold which increases the system response time to 500µs.

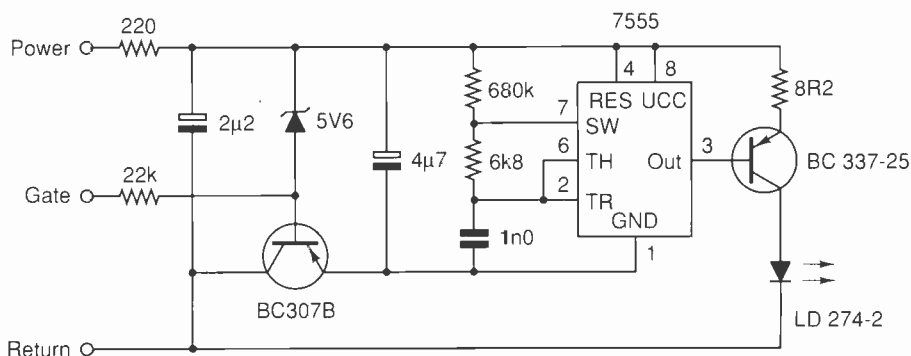


Fig. 9. Pulsed transmitter for 10 to 30V operation with 6mA current consumption. The 555 cms timer is oscillating at 2kHz with 6µs pulse width and 450mA peak led current producing some 0.33W/sr radiant intensity at 950nm. The gate input is connected to the return path to operate the transmitter.

### Active loads

A simple resistive load's maximum value is restricted by bandwidth limitations and overload problems from background light sources. Background light can cause enough photocurrent to forward bias the diode leading to severe losses in sensitivity.

Since most background light sources are either steady-state or have outputs which flicker at low frequencies, a load which is low impedance at these frequencies but high impedance at the desired signal frequency would be ideal. Such characteristics can be achieved with an inductor.

The inductive load shown in (1) can provide a signal frequency impedance of 100kΩ while giving a very low resistance path for background lighting photocurrent. Consequently it will operate over a wide range of light levels.

The circuit's output waveform (2) consists of a damped sine-wave whose frequency is dependent on the inductance used and the sum of the photodiode capacitance, the inductor's stray capacitance as well as the indicated capacitor. This ringing can cause multiple pulse detection if delays are not included in the receiver logic.

Inductors have been used in remote controls where good sensitivity and high background light tolerance has been required but the problems highlighted have limited the popularity of this approach.

The optimum characteristics provided by the inductive load can be obtained without the disadvantages mentioned by using an active circuit. Two configurations of the same basic active load circuit but with differing output polarities are given in (3) and (4).

In the first, photocurrent from the BPW41 raises the base voltage of the low noise ZTX384 via the 330kΩ resistor until the transistor's base-emitter voltage reaches about 0.7V and it starts to conduct. An equilibrium point is quickly reached where the transistor holds its collector voltage at around 0.8V by acting as a current generator; that matches the photodiode current. This equilibrium is maintained for DC or slowly varying photocurrents thus providing the photodiode with a low impedance load at these frequencies. For the component values shown in (3), the load impedance presented to the photodiode changes from around 1kΩ at DC to approach 250kΩ at 50kHz.

Load impedance of this circuit falls a little at high light levels but its main disadvantages are noise and interference rejection. Although at first sight it appears that high-frequency inputs to the transistor are shorted by the capacitor, this does not apply to the small noise voltage generator within the device. These low level signals are amplified by the transistor. Voltage gain is given approximately by:

$$\text{Voltage gain} = \frac{R_c}{r_e} = \frac{\text{collector load impedance}}{\text{intrinsic emitter resistance}}$$

$$\text{where } r_e = \frac{26}{I_e} \quad (I_e \text{ in mA})$$


with low background light levels. For instance, in a dimly lit room yielding 5µA of photocurrent, the voltage gain given to these signals will be around 50, leaving their level too low to be of consequence.

Unfortunately, at light levels approaching direct sunlight, the resulting background photocurrent of 1mA will raise the circuit's voltage gain up as high as 10,000 making the noise and interference significant.

However, the problem is easily dealt with. The extra emitter resistor included in the second active load circuit changes this behavior dramatically. The voltage gain of the circuit now approximates to:

$$\text{Voltage gain} = \frac{R_c}{r_e + R_e}$$

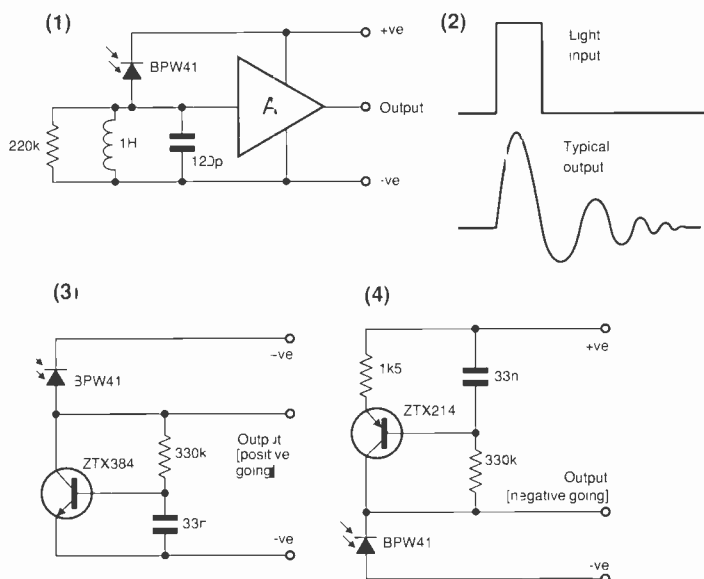At 1mA the voltage gain of the circuit has been reduced to less than 160, leaving the noise contributions from other sources larger than those generated by the load circuit. The added resistor does increase the low frequency impedance of the circuit a little but it will still operate in direct sunlight. David Bradbury, Zetex plc





**The photo transistor**

In principle the photo transistor corresponds to a photodiode (collector-base diode) with a series connected transistor as amplifier. Gain is normally between 100 and 1000. Rise time is significantly slower than the photodiode due to reverse transfer capacitance which is multiplied by the gain of the device (Miller effect).

A typical photo transistor circuit for direct microcontroller interface is shown in Fig. 10, a photo-interrupter. The IR emitter is gated from the microcontroller and the current is limited by a series resistor. The microcontroller repeatedly activates the led and, after a short delay, the photo transistor status is read back, and the transmitter is deactivated to reduce the power dissipation. A delay of 100µs is necessary to switch the Siemens SFH303F-3 photo transistor.

The transistor develops a collector current of 0.5mA at 1W/m<sup>2</sup> and 870nm and is reduced to 0.35mA at 950nm. To switch the transistor requires an irradiation of 3W/m<sup>2</sup>. Since the led is the same as that used in Fig. 8, the maximum separation between transmitter and receiver readily calculates out as 100mm.

The photo transistor is a slow switch, because the photodiode capacitor C<sub>cb</sub> is amplified by the transistor current amplification factor B. The resulting time constant equals B x C<sub>cb</sub> x R<sub>c</sub>, where R<sub>c</sub> is the collector load. For the Fig. 10 circuit the time constant is approximately 30µs.

The only accessible factor in the equation for the photo transistor time constant is the collector load, R<sub>c</sub>. Sensitivity too is proportional to R<sub>c</sub>, so a trade off between distance and speed is necessary.

**Fibre transmission**

Data transmission with fibre optics is useful because of the freedom from electrical connection, crosstalk between channels and electro magnetic interference. The Fig.10 circuit provides a useful basis for experiments with fibre technology if the series resistor is changed to 100Ω to reduce the transmitter diode current to a safe level. The Siemens 660nm transmitter diode SFH750V and photo transistor receiver SFH350V were used, connected to a 3.5m cable of 2.2mm diameter (1mm core diameter).

The system operated with a minimum pulse width of 50µs, indicating suitability for data transmission to 9600 bit/s. The speed limita-

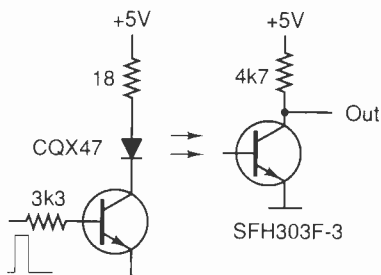


Fig. 10. Optical reader with 100mm detection range. The circuit could be used for data transmission with fibre optics.

**Units and meanings**

Illuminance (E<sub>v</sub>) is expressed in lux (lx). The illuminance is related to the spectral sensitivity of the human eye, and is zero by definition outside the visible range. An illuminance of 1lx is sufficient to read a paper and 100lx is a common indoor illumination level. Starlight is some 0.001lx and sunshine is approximately 100000lx. At 0.25m distance from a 60W tungsten filament lamp (with reflector) the illumination is approximately 1000lx.

For components intended to operate outside the visible spectrum, or at specific wavelengths, the irradiation (E<sub>e</sub>) is expressed in W/m<sup>2</sup>.

Photo current (I<sub>p</sub>) from the photodiode or photo transistor, when exposed to an illumination E<sub>v</sub> or irradiation E<sub>e</sub>, is:

$$I_p = S \times E_v \text{ or } e \dots (1)$$

where S is the sensitivity of the photo component. A typical photodiode sensitivity is 80nA/lx or 5µAxm<sup>2</sup>/W (both Siemens SFH206).

Radiant intensity (I<sub>e</sub>) is the radiant power from an infrared emitting diode solid angle and is expressed in watt/steradian (W/sr).

The solid angle is A/R<sup>2</sup> where A is area and R radius of the sphere (see Fig. a). The full sphere is A = 4πR<sup>2</sup> and 1sr corresponds to a cone angle of approximately 60°.

The radiant intensity I<sub>e</sub> is power P per solid angle A/d<sup>2</sup> (Fig. b), the power is thus the intensity multiplied by the solid angle: P = I<sub>e</sub> x A/d<sup>2</sup>. The irradiation E<sub>e</sub> is power P per area A, thus the power is: P = E<sub>e</sub> x A. The relation between radiant intensity and irradiation is thus:

$$E_e = I_e/d^2 \dots (2)$$

The irradiation is inversely proportional to distance squared, and at a distance of 1m the radiant intensity in W/sr equals the irradiance in W/m<sup>2</sup>. The distance d should be at least 10 times the diameter of the diodes to minimize errors.

The radiant intensity for an IR led is approximately proportional to the forward current and is usually specified at 100mA. The diodes can typically accept pulse currents at 1A, but light emitting diodes exist with ratings above 10A.


The led does not distribute the emitted power evenly within the 1sr solid angle. The half power angle is typically ±15°.

The radiant power declines with increasing length of operation. The life of the component is defined as the time after which the radiant power has fallen to half the initial value. The average life, dependent on the operation current and ambient temperature, is approximately 10 years.

The photo receiver output voltage (U<sub>r</sub>) (Fig. c) is the voltage amplitude of the pulsed signal at the output of the amplifier. The photo current I<sub>p</sub> is converted to voltage, and amplified to an output voltage of I<sub>p</sub> x R<sub>c</sub> x G. With equations (1) and (2) the receiver output voltage becomes;

$$U_r = S.R.G.I_e/d^2 \dots (3)$$

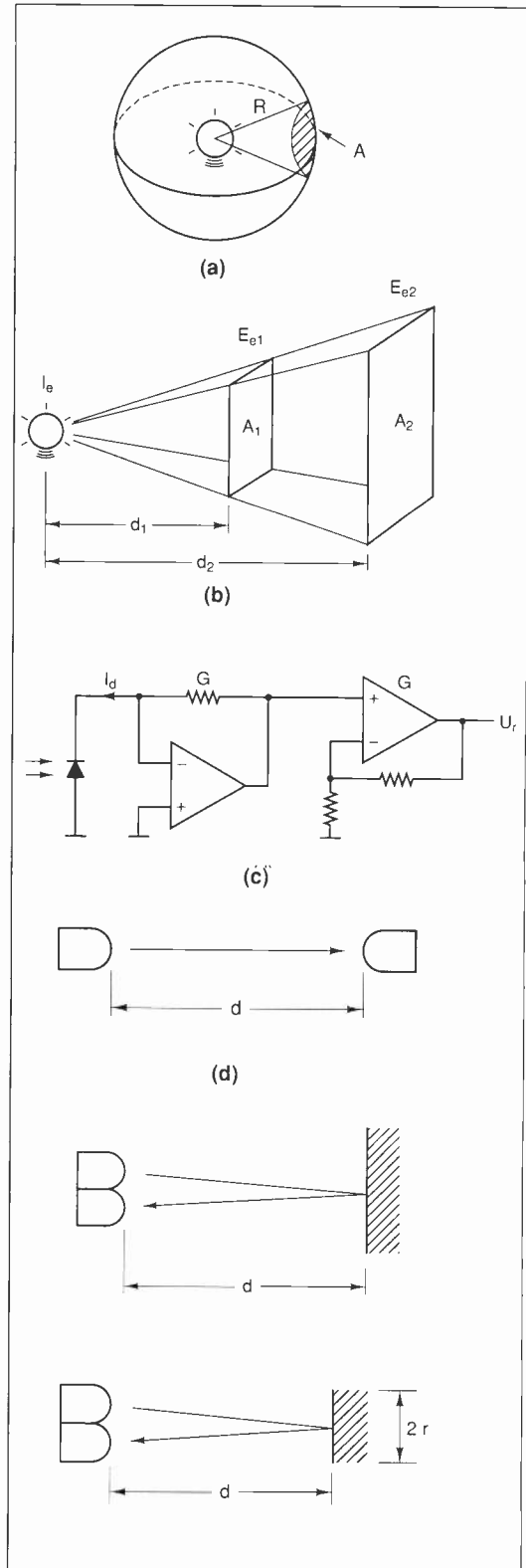With a receiver sensitivity of 5µA at 1W/m<sup>2</sup>, a photodiode load resistance of 100kΩ, an amplifier gain of 100, the receiver delivers 1.5V at an led radiant intensity of 0.03W/sr and a distance of 1m (Fig. d).



tion is the photo transistor collector-base capacitor. For high speed operation a photodiode must be used at the receiver.

### Photo transistor receiver

Photo transistors may be used in fast circuits if the impedance level at the basis is relatively low, as shown in the typical input stage of Fig. 11. The base network has a dual purpose. Besides biasing, the network resistance provides the collector-base photodiode load (150kΩ). The transistor acts as an impedance transformer reducing the output impedance below 1kΩ.

Using the BPX43 photo transistor the value of  $C_{cb}$  is 20pF at 2V leading to a bandwidth of 35kHz if the stray capacitance is assumed to be 10pF. The bandwidth could be increased if the network resistance is reduced. A similar design operated at 100kHz with 20kΩ network resistance and a Honeywell SD5443 photo transistor.

The circuit exhibits a sensitivity of 5mV/lx or 330mV at 1W/m<sup>2</sup> with the resistors shown. The photo transistor will accept 500lx before saturation (the base is driven above the positive supply forward biasing the collector-base diode).

The output voltage at the emitter replicates the intensity of the incident light and should be amplified further before detection. The pulsed transmitter of Fig. 9 produces an output voltage of 110mV at 1m distance.

The collector of a metal can photo transistor is electrically connected to the case. This provides a potential pickup point for interference in collector output circuits and this should be taken account of at the design stage. Grounding the can to rf with the transistor configured as an emitter follower overcomes this potential problem.

### Photo diode receiver

A photodiode receiver intended for analogue signal processing or microprocessor interface is shown in Fig. 12. The design operates at 5V and connects to the system with a screened coaxial cable.

The first transistor acts as a common emitter amplifier with a boot strapped collector load, providing a voltage amplification of 200. The amplifier presents an input impedance of 600Ω providing a fast diode interface. The amplifier limits bandwidth to approximately 80kHz.

The collector of the first transistor is fixed at 0.6V providing a bias for the two-transistor output stage, the open loop gain of which is 650. This is reduced to 100 by feedback. The emitter of the pnp transistor is fixed at 1.2V providing a bias for the photodiode without interference from the power supply. The relatively high value of the biasing resistor limits the extraneous light to some 100lx and thus the application area to dim environments. The resistor value could be lowered at the expense of sensitivity or replaced by a suitable inductor. An inductor of suitable impedance at the prf allows the full ac signal voltage to be developed across it while providing a sink for the static photocurrent due to ambient light.

A suitable detector for a simple microprocessor interface could be a comparator adjusted to accept pulses 1V above the amplifier dc level. The irradiation needed for 1V output is 0.014W/m<sup>2</sup> and with the Fig. 9 transmitter radiant intensity of typically 0.33W/sr, the system should work comfortably at 5m distance.

The output noise voltage is 0.1V peak, mainly due to the illumination level. It could be reduced by increasing the cut off frequency of the high pass filters (hum suppression) and by reducing the amplifier bandwidth. Semiconductor noise is not usually a limiting

factor in opto-electronics. Detection at a 0.1V threshold voltage (which corresponds to a range of 15m) would be possible using a synchronous detector to integrate several received pulses.

### Proximity sensors

Sensitive receivers are used in proximity sensors (the optical equivalent to radar). The sensor detects reflections from objects within the sensor proximity. A combination of the Fig. 9 transmitter and the Fig. 12 receiver provides a useful proximity detector. Using reflection from the roof the pair produced an output voltage of 0.2V at 1.8m distance.

The circuit of Fig. 13 is a complete proximity sensor with 0.35m detection range and low power consumption. The 4069UB hex-inverter is used as six inverting amplifiers self-biasing at half supply voltage.

The transmitter is a free running oscillator with 1% duty cycle and a pulse amplitude of 100mA.

The photo transistor is used as a photodiode with internal lens, and with the metal enclosure connected to ground for shielding purpose. The collector and emitter leads are shorted to use the photo current from the emitter diode as well, increasing the sensitivity some 50% to approximately 3μA at 1W/m<sup>2</sup>.

The first amplifier stage performs the conversion from current to voltage while the second stage provides a gain of 30. The amplified pulse is rectified and smoothed, a pulse amplitude of approximately 1V turning off the output transistor.

This pulse amplitude was reached at 0.35m distance with a large object. As shown in the panel the receiver voltage should reach the required pulse amplitude at approximately 0.25m. The transmitter half power angle should be 15°. ■

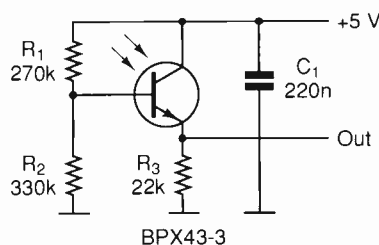


Fig. 11. Photo transistor input stage for high speed operation. The photo transistor enclosure is grounded to reduce sensitivity to electro magnetic interference.

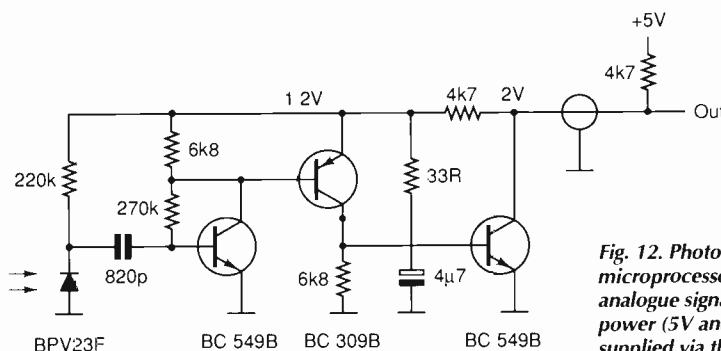


Fig. 12. Photo receiver for microprocessor interface or analogue signal processing. The power (5V and 0.6mA) is supplied via the coax cable.

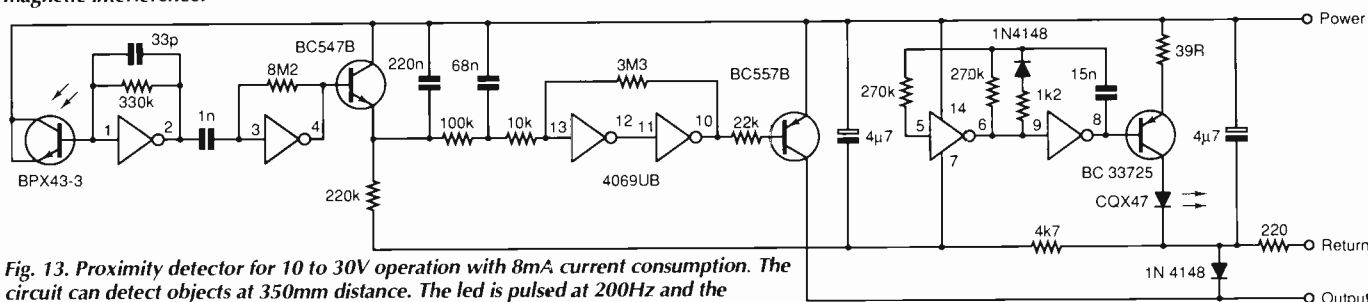


Fig. 13. Proximity detector for 10 to 30V operation with 8mA current consumption. The circuit can detect objects at 350mm distance. The led is pulsed at 200Hz and the reflected pulse is amplified and rectified. The output is active in absence from light and has a reaction time of 30ms.

# LOW DISTORTION AUDIO OSCILLATOR

*It is a chicken and egg situation. You may wish to design the ultimate in distortion free audio equipment but can you be sure that you are measuring a residual from the equipment under test or an artifact from the test oscillator (or distortion meter) itself? This test oscillator design presented here by Ian Hickman could break the dilemma.*

This magazine has a long tradition of interest in audio design and measurement. Central to this are low distortion oscillators and distortion meters, and examples of both of these have appeared from time to time<sup>1,2</sup>.

The oscillator in the first reference has a claimed performance of <0.005% THD from 20Hz-20kHz and as low as 0.0005% typical (or even 0.0002% at 1kHz, actually lower than the commonly accepted typical distortion figures for the NE5532 op-amps used), would be very suitable for evaluating the performance of a THD measuring system as described in Ref. 2. In fact, low distortion oscillators and matching THD meters form a chicken-and-egg pair, with each being (ideally) tested with a sample of the other having a level of internal distortion much lower than its own.

This aspect has prompted me to experiment


with various AF oscillators and THD meters. A trawl through my files unearthed a circuit from 1966, shown in Fig. 1; even the required layout, using turret tagstrip, is there. This circuit was designed for use with a separate external AF millivoltmeter, which would have been average responding, scaled to rms on a sine wave. Thus the indicated distortion would only approximate the true figure. See Box.

A new THD meter was designed around a state variable filter some ten years ago. This offered ranges in a 30 - 10 - 3 - 1 sequence down to 0.01% fsd permitting measurements down to 0.001% or less. Its residual noise level corresponds to 0.0009% in a 20kHz

bandwidth, 0.003% in 80kHz, far too high) and it had a built-in true rms responding indicating section using the AD536 rms to dc converter. This instrument worked well and is still in use although, when making measurements at the 0.001% level, it requires suppression of the fundamental in excess of 100dB. This is a tall order for a single notch.

This is especially the case in a THD meter where the notch must not depress signal level at twice the notch frequency where the second harmonic is encountered. The result is that any slight frequency instability in the test source, appearing as noise sidebands, will cause energy to appear either side of the notch and raise the level of the measured residual. Negative feedback, necessary to ensure a virtually flat response at second and higher harmonics of the rejected fundamental, actually causes a bit of a design problem. The flattening of the fre-

**Fig. 1. Circuit of a THD monitor designed by the author and dating from the mid sixties. Like that in Ref. 2 it was designed to be used with a separate external AF millivoltmeter**

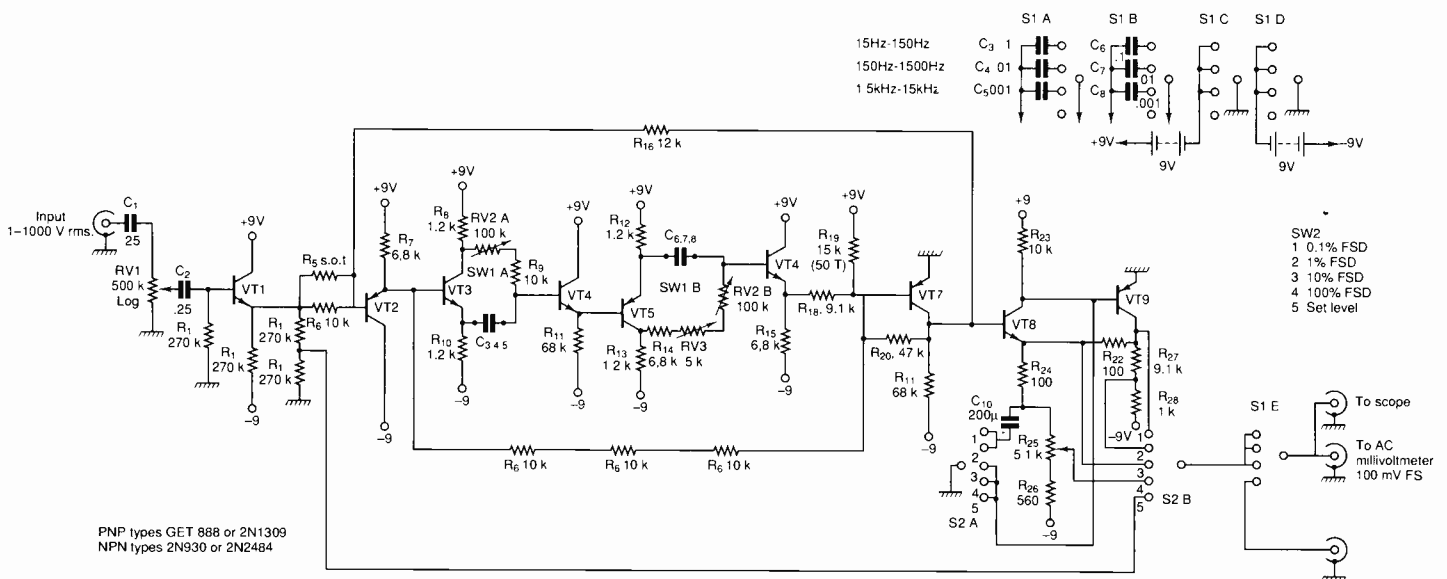



quency response is bought at the price of an increase in gain at the fundamental at an internal circuit node, as shown in Fig. 2. This is based around a Wien bridge, though a very similar argument applies whatever circuit is used to implement the sharpened-up notch.

The level of the enhanced fundamental component must of course be kept well below clipping level, limiting the permissible input level to the notch stage. This in turn reduces the dynamic range due to the reduced clearance of the signal above the wideband noise floor, providing another factor, in addition to the instrument's own residual internal distortion, limiting the lowest level of distortion that can be observed. Despite this, a high performance THD meter *should* be easier to design than an oscillator, since all circuitry within the former can be linear, whereas the latter requires an amplitude control mechanism which involves some non-linearity.

The SVF-based instrument mentioned above actually, like many THD meters, responds to harmonics of the input, hum and the wideband noise floor, as well as significant spectral noise sidebands surrounding the fundamental which fall outside the notch. Useful as this instrument proved, initially there was no way

of knowing what was the level of residual distortion in the instrument itself. Thus a very low distortion oscillator was designed to provide a test source.

Some nonlinearity is needed to constrain an oscillator's output amplitude at a suitable constant level. This non-linearity can operate on a cycle-by-cycle basis or over many cycles as with thermistor control. Having a thermal time constant of nearer to a second than a millisecond, the thermistor's resistance remains sensibly constant over each cycle of the output, except at frequencies below 100Hz. Here, it leads to 20Hz distortion figures in the range 1% or worse for a typical design, down to 0.1% in the case of Ref. 1 (reduced at the output to <0.005% by a distortion cancelling technique described in the article).


**Fig. 2a Circuit providing a notch at one frequency  $f$ . The response at  $2f$  is still 4.77dB down, eventually returning to the dc value at a much higher frequency.**


**b. By enclosing the notch circuit within an NFB loop, the response can be sharpened up to be no more than a fraction of a dB down at second harmonic. However, internal to the loop, the response at the fundamental is actually peaked up significantly.**

### Chicken and egg measurement

It is very difficult to design a really low distortion oscillator using this approach. It was therefore decided to use an SVF-based system incorporating nonlinearity operating over many cycles, effectively adjusting the loop gain. In fact, it is actually the loop phaseshift which is adjusted since, with the two integrator loop of the SVF, there is always a frequency at which the loop gain is unity. This contrasts with the approach in Ref. 2 which uses an all-pass filter based oscillator: here there is always a frequency at which the loop phase shift is  $360^\circ$ , so it is the loop gain which has to be adjusted to obtain a stable output. The circuit adopted is shown in block diagram form in Fig. 3a, with the operating principle explained in 3b.

Initial breadboard results were promising, which immediately reintroduced the chicken and egg problem of measurements. This required a further piece of equipment to resolve it. As Fig. 4 shows, this comprises a passive twin-T notch filter followed by a second order Chebychev active highpass filter, forming a fourth order elliptic highpass filter. The peaking of the Chebychev highpass filter is set to compensate for the attenuation of the

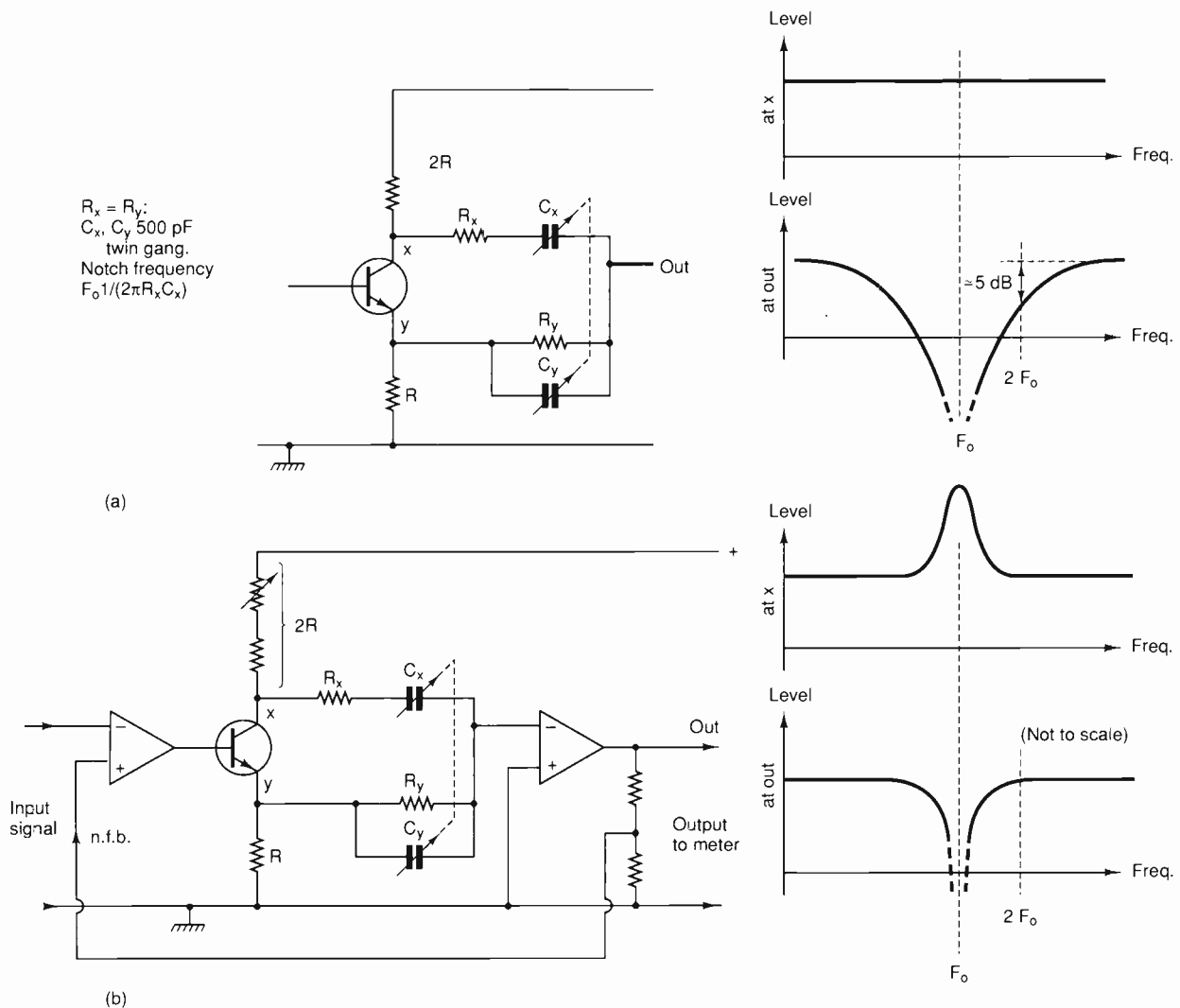

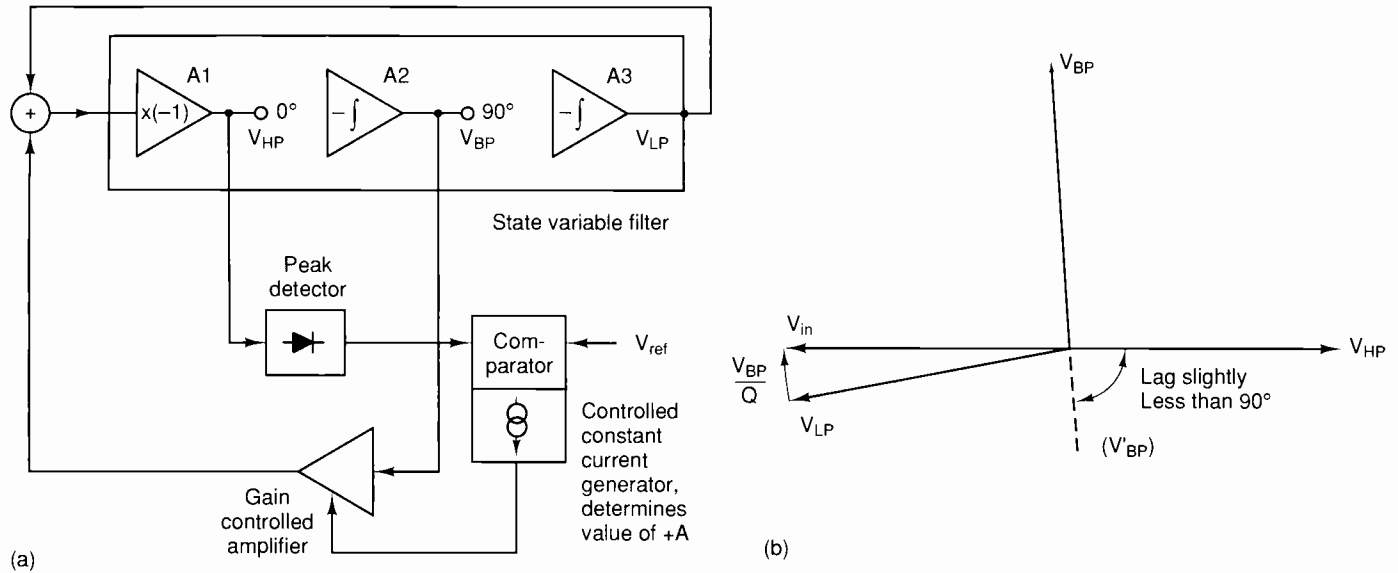

**Fig. 3a. Block diagram of the SVF-filter based low distortion oscillator described in this article. The filter selectively amplifies the fundamental component of the output of the variable gain amplifier, discriminating against any harmonic distortion present.**  
**b. Showing how the BP output, lagging the HP by a fraction less than 90° (much exaggerated for clarity), looks as though it is leading by just over 90°, as A2 is an inverting integrator. Similarly LP with respect to BP, so LP lags HP by slightly less than 180° and cannot by itself provide the necessary input to the filter  $V_{in}$  to produce the output shown. Addition of a fraction  $1/Q$  of the BP output increases the phaseshift to 180° and gives a voltage equal to the required  $V_{in}$ , causing oscillation.**

passive notch filter at twice the notch frequency, amounting to some 8dB relative to the 0Hz and far-out high frequency response. In the case of channel 2 (600Hz) shown, the LF roll-off of this elliptic highpass filter also discriminates against 50Hz and its harmonics. The Chebychev highpass filter section is followed by a lowpass filter designed, in the case of the 600Hz notch channel, to cut off beyond 3kHz. With this in circuit, THD up to and including the fifth harmonic is measured, very low levels being easily seen due to the reduction in wideband noise afforded by the lowpass section. In the case of a low distortion oscillator circuit, the design will be such that often only the lower orders of harmonics are significant. But in other cases, such as a high power amplifier using a push-pull output stage, higher order distortion components due to, say, crossover effects may be present. In this case, the lowpass section would be inappropriate, so provision is made to switch it out.

The adjustments shown provide a sensibly flat response from the second harmonic of 600Hz upwards (or from the second to fifth harmonics, inclusive). The through gain in the flat position is approximately unity (actually somewhat higher), while it is arranged that with a notch channel in circuit, the gain over the specified range of harmonics is increased by exactly 40dB. Thus when used in conjunction with an existing THD meter, the 10% distortion range becomes 0.1% fsd, the 1% range becomes 0.01% etc.

Clearly, when making measurements using a notch channel, the effect of any internal noise or distortion in an associated THD meter is reduced by a factor of 100, while due to the protection afforded by the passive twin T notch there should be a negligible contribution to distortion from the notch channel itself, though it will of course contribute its own noise.

The 20Hz channel uses exactly the same circuit arrangement as the 600Hz channel, with again the option of switching the lowpass section in or out as desired. However, the 10kHz

channel is somewhat different. The twin T section is followed by a buffer/10dB gain stage like the others, but this drives two state variable filters, one tuned to 20kHz and the other to 30kHz. The outputs of these are combined in the output buffer amplifier.

With this notch box in use ahead of a conventional THD meter, the measurement is no longer an "everything else" measurement, especially with the lowpass section in circuit. The great disadvantage is that measurements are confined to the three test frequencies catered for. Of course, additional channels could be provided, but the added complexity rapidly becomes cumbersome.

**The low distortion oscillator**

With means to hand to examine distortion levels below -115dB relative to the fundamental (<0.00018%) work on the development of the low distortion oscillator became possible. When working at low levels of distortion, layout becomes just as important as it is in an RF circuit, so breadboarding was abandoned in favour of discrete wiring on a commercial prototyping PCB.

The intention was to use the state variable filter running at the highest practicable value of Q, to filter a low level, low distortion sinewave drive. The SVF circuit was therefore tested running without any intentional quadra-

ture feedback, either negative or positive, providing in theory a filter with an infinite Q. At low and middle frequencies, the inevitable fractional shortfall of phaseshift in each integrator meant that the loop phaseshift fell fractionally short of 360° and the circuit was stable. But on switching to the 2-20kHz range, at the higher frequency settings the three op-amps in the loop were beginning to contribute a mite of phaseshift each, leading to oscillation when the frequency was set to 17kHz or higher. This was compensated out by providing a touch of phase advance, which turned out to be not quite so simple.

A single capacitor between the lowpass (LP) output and the virtual earth of the highpass (HP) stage will certainly stabilise the circuit, suppressing any tendency to oscillate at 17kHz or above, but the damping it provides becomes quite excessive at 20kHz, leading to a low Q at this frequency. The phase advance was therefore distributed between all three stages within the basic loop, each capacitor being provided with a series resistor to limit the phase advance as shown in the full circuit diagram, Fig. 5. The required value of capacitance at the HP stage virtual earth, 5a was so small that it was provided by two 20mm lengths of wire-wrap wire, twisted more, or less, as required.

Now, a small quadrature (negative damping) term was taken from the BP output via an operational transconductance amplifier (OTA) and added in at the HP stage virtual earth. When this is just sufficient to bring the loop phaseshift up to 360°, the circuit will oscillate (Fig. 3b). A current source provides the  $I_{abc}$  bias current required by the OTA, but it is arranged that as the amplitude of the oscillation increases beyond a certain threshold, the peak detected voltage causes a reduction of  $I_{abc}$ , reducing the loop phaseshift back to exactly 360° and stabilizing the amplitude at that level.

OTAs are not renowned as the lowest of low distortion devices, so the voltage applied to its non-inverting input is kept to a very low level by the 100kΩ/27R potential divider  $R_{17}$ ,  $R_{18}$ .

The OTA's output current is divided between two 100kΩ resistors, one grounded to ensure that its output voltage remains centred within its voltage compliance range, and one providing dc-blocked "negative damping" to the HP stage virtual earth. The voltage set by the 10kΩ/4.7kΩ resistors R<sub>15</sub> and R<sub>16</sub> at the base of the pnp long-tailed pair provides a +5V reference voltage. If the detected peak voltage is more or less than this value, I<sub>abc</sub> will be reduced/increased respectively, adjusting the negative damping term as required to maintain a constant amplitude of oscillation.

The peak detector time constant of 1s (10MΩ x 1μF) is long enough to do duty on all three frequency ranges, covering 20Hz-20kHz, though it is responsible for some rise in distortion at 20Hz. However, increasing this time constant is not without its problems, so the values shown have been retained.

**Estimating the Q**

To see just what Q the filter runs at, I<sub>abc</sub> was reduced to zero and the value of resistance required between BP output and HP virtual earth input to just cause oscillation was determined: this value divided by the value of the resistance from LP output to HP virtual earth (R<sub>3</sub>, 100kΩ) gives the filter Q. The circuit oscillated over the whole 20Hz-20kHz range with quadrature feedback via 10MΩ; over most of the range with 20MΩ and some of the range with 30MΩ. Thus the operating Q of the loop, considered as an SVF, is generally between 200 and 300.

In an active filter operating at such a high Q, the output amplitude would normally be very sensitive to temperature and other external factors. Here, however, the narrow range of level needed to change I<sub>abc</sub> from zero to maximum results in very tight amplitude control. With a gain at the fundamental of, say, 250 times and an attenuation of three at third harmonic in each of the integrator stages, any third harmonic in the signal from the OTA should be reduced by a factor 2250 or 67dB (a factor of -60dB at second harmonic). So if the distortion introduced by the OTA can be held below 0.1%, the output distortion should be <0.0001% at second harmonic, and the third even smaller... provided the op-amps in the loop have zero distortion themselves. The op-amp A<sub>6a</sub> with its gain of 11 was included to provide a buffered amplified version of the OTA output as an aid during circuit development and testing. The voltage measured here confirms the estimate of operating Q, being 0.5Vpk/pk at 10kHz. This corresponds to 45mVpk/pk at the OTA output as against 10Vpk/pk at the LP output, indicating a Q of 220.

The oscillator lowpass output labelled LP in Fig. 5a was used to drive an output section as shown in 5b, being fed to the virtual earth of op-amp A<sub>2b</sub>. It can be seen that there is also a contribution from the HP oscillator output, via

Assuming E<sub>1</sub> stands for the rms value of the fundamental of a distorted sinewave, E<sub>2</sub> for that of the second harmonic component, etc., then the total harmonic distortion is given by:

$$\text{Total THD} = \frac{\sum E_2^2 + E_3^2 + E_4^2 \dots}{\sum E_1^2 + E_2^2 + E_3^2 + E_4^2 \dots} \dots 1$$

By setting a reference level with a flat frequency response, corresponding to the denominator of (1), and then measuring the relative level of the signal with the fundamental component E<sub>1</sub> notched out, this is exactly what a THD Meter measures - except that in the measurements, any noise, hum or other signal present is also inevitably included.

Ideally, we might prefer to measure:

$$\frac{\sum E_2^2 + E_3^2 + E_4^2 \dots}{E_1} \dots 2$$

but if all components E<sub>2</sub>, E<sub>3</sub>, E<sub>4</sub> etc. are less than 10% of the amplitude of E<sub>1</sub>, then the difference due to each is less than 1%. In low distortion measurements, where the harmonics are all much less than 1%, then in practical terms (1) and (2) are identical.

R<sub>31</sub> + R<sub>35</sub>. This was included so that R<sub>31</sub> could be adjusted to suppress any third harmonic component in the output, as described in Ref. 3. The output of A<sub>2b</sub> drives A<sub>3b</sub>, whose feedback resistor is variable, providing fine output level adjustment. Coarse adjustment in 10dB steps is provided by the 600Ω bridged T attenuator associated with S<sub>4</sub>, and by the 0 or 50dB pad, S<sub>5</sub>. The odd value resistors R<sub>44</sub> - 48 and R<sub>53</sub> - 57 were made up by paralleling standard values to get within 1%.

S<sub>3</sub> provides a choice of a 600Ω output impedance or (with the step attenuators set to 0dB) a low impedance. This provides twice the maximum available peak to peak output voltage into 600Ω, but if the step attenuators are used, the first 10dB step will no longer be accurate. Note that great care is

required in the earth routing, as indicated in Fig. 5b, if the distortion is to go down pro rata with the output. screened lead should be used between the main output socket, S<sub>5</sub>, S<sub>4</sub> and the main circuit board.

**Performance**

When set up, the oscillator provided the following performance, all measurements being taken with S<sub>3</sub> set to low output impedance, S<sub>4</sub> and S<sub>5</sub> to 0dB, and using the notch box.

20Hz	0.00062%	(20kHz bandwidth, notch box LPF out, Fig. 6a)
20Hz	0.00059%	(20kHz bandwidth, notch box LPF in)
600Hz	0.00034%	(20kHz bandwidth, notch box LPF out)
600Hz	0.00022%	(20kHz bandwidth, notch box LPF in)
10kHz	0.00092%	(80kHz bandwidth, Fig. 6b)
10kHz	0.00062%	(20kHz bandwidth, Fig. 6c)

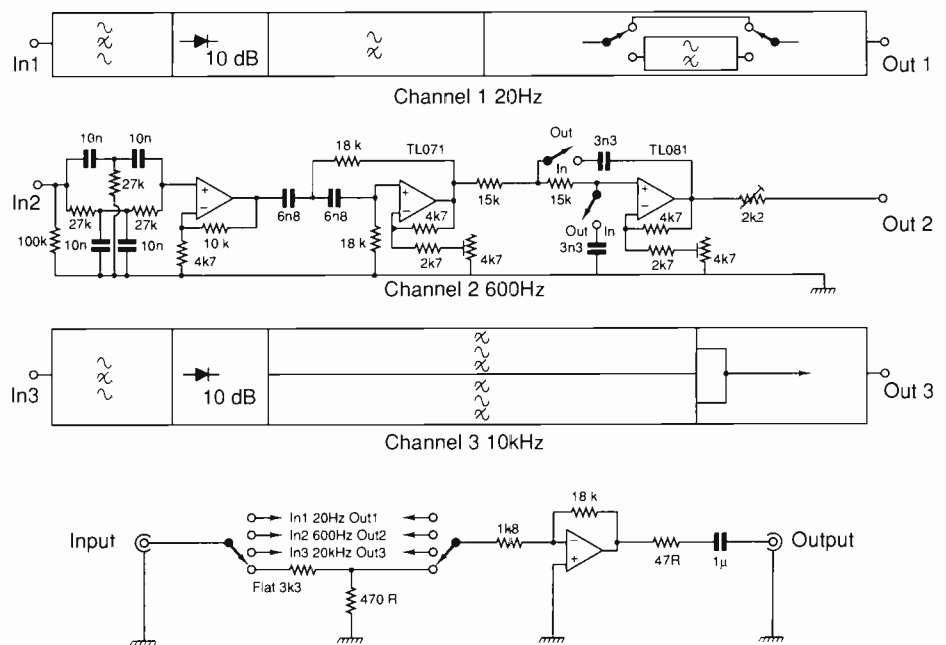


Fig. 4. Circuit of the "Notch Box" used to extend the measurement range of a THD Meter, providing three spot measurement frequencies of (approx) 20Hz, 600Hz and 10kHz.


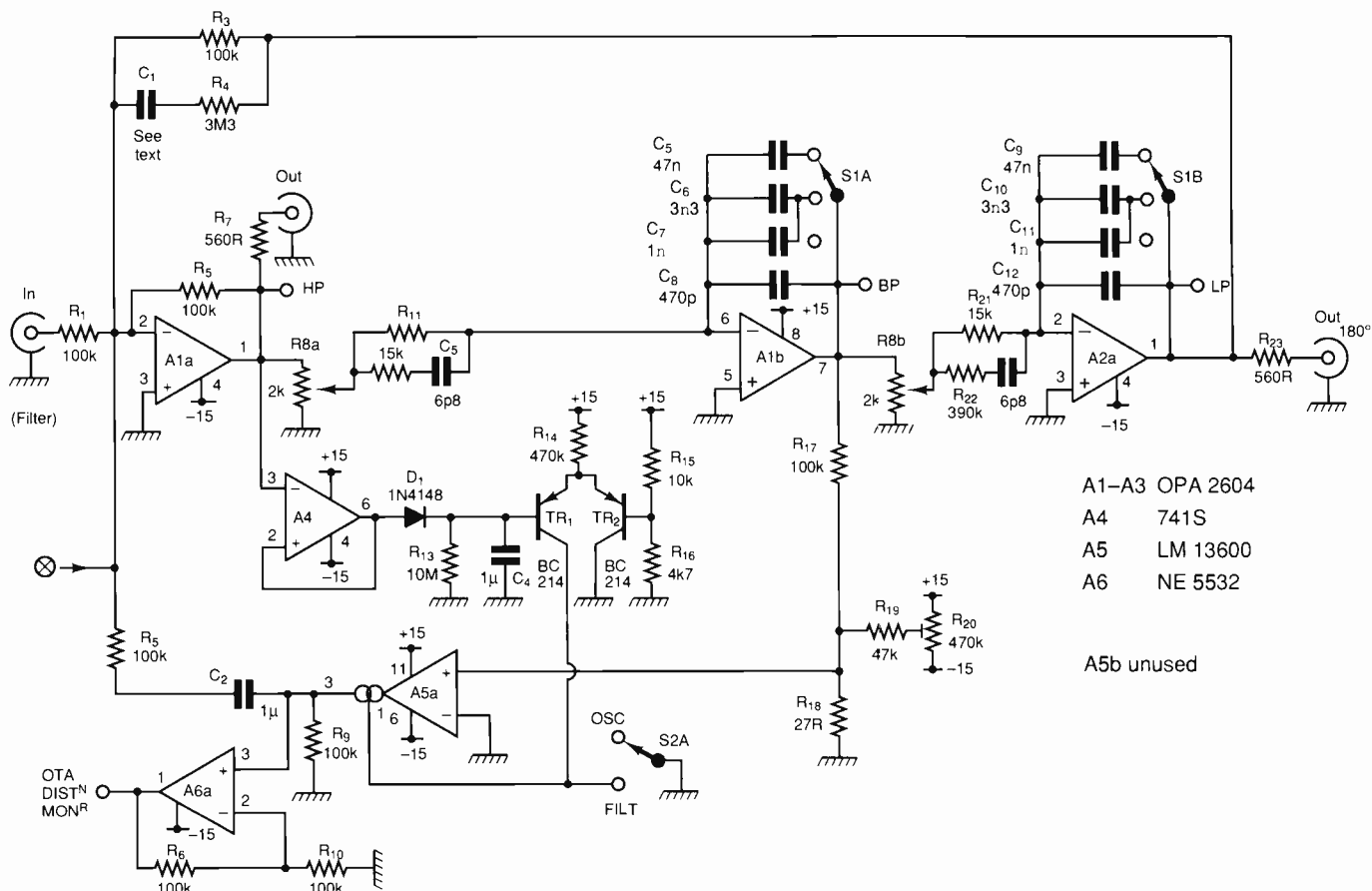


Fig. 5a. Part circuit of the SVF-filter based low distortion oscillator: oscillator section.

(a)

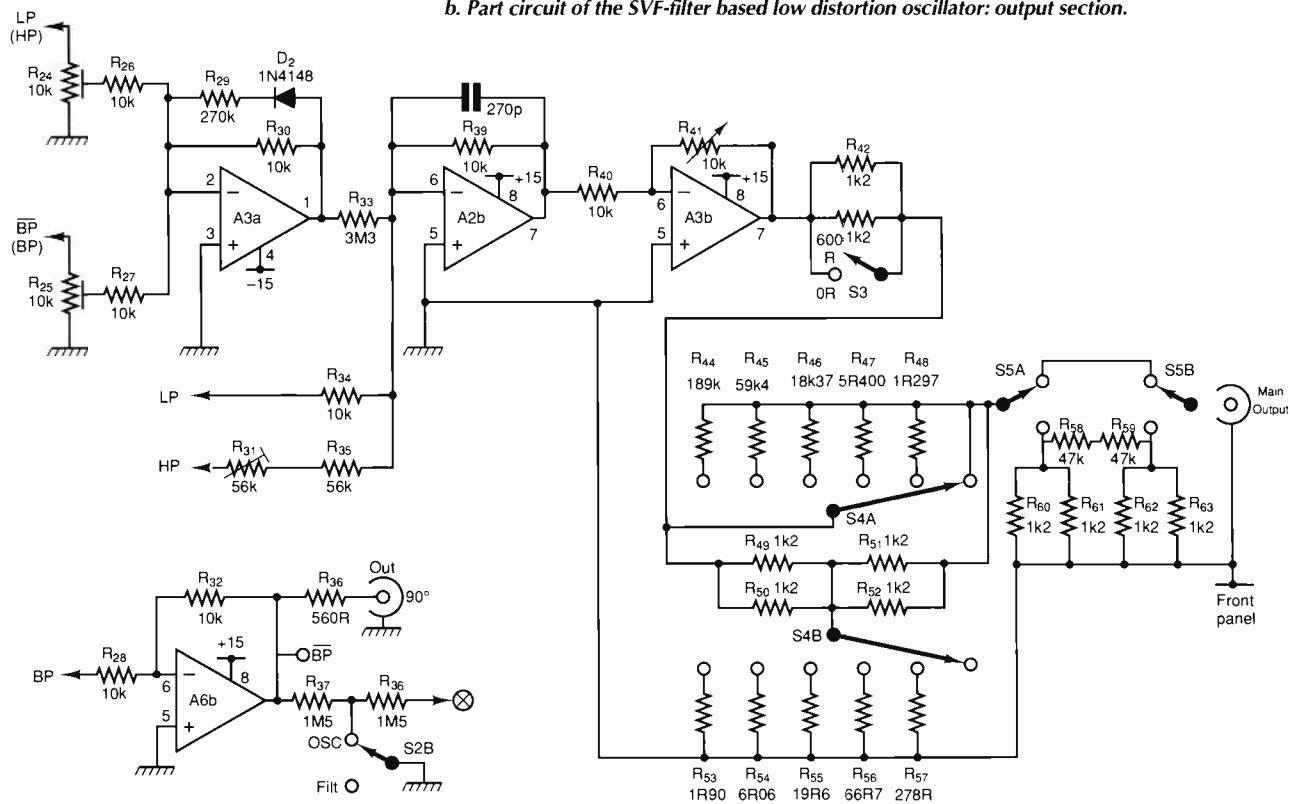b. Part circuit of the SVF-filter based low distortion oscillator: output section.



(b)



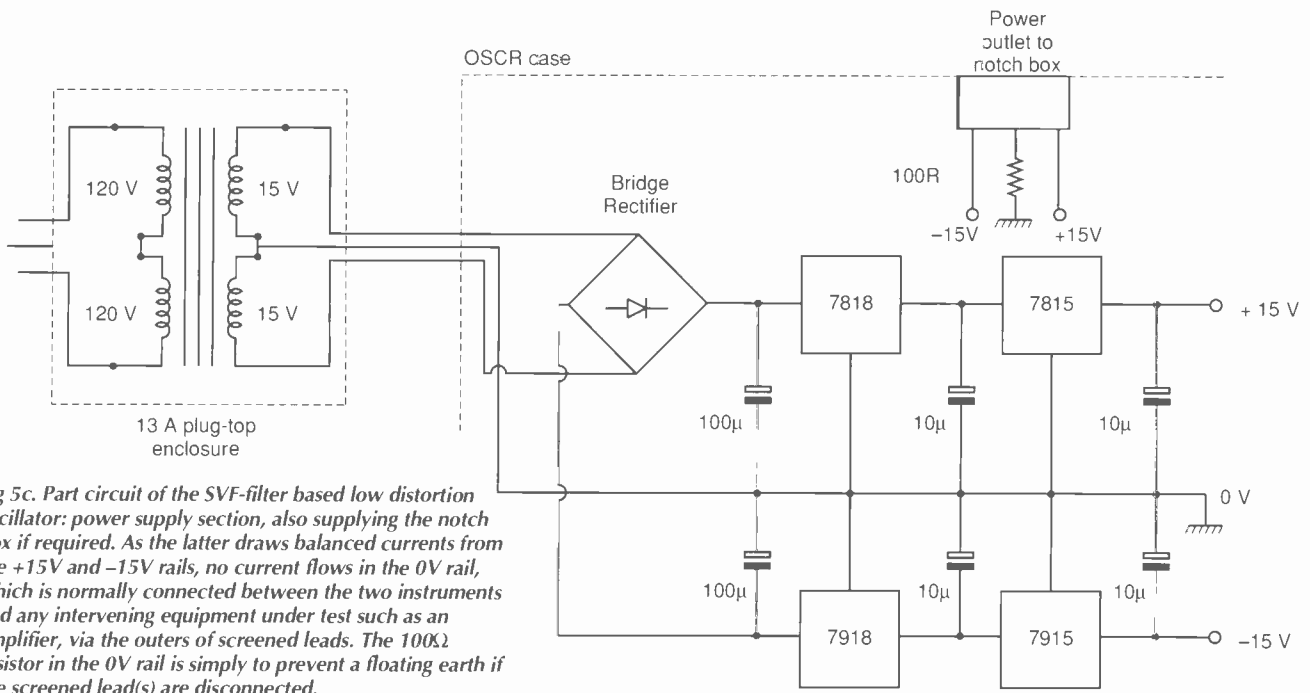


Fig 5c. Part circuit of the SVF-filter based low distortion oscillator: power supply section, also supplying the notch box if required. As the latter draws balanced currents from the +15V and -15V rails, no current flows in the 0V rail, which is normally connected between the two instruments and any intervening equipment under test such as an amplifier, via the outs of screened leads. The 100Ω resistor in the 0V rail is simply to prevent a floating earth if the screened lead(s) are disconnected.

At 600Hz, the residual distortion can be clearly seen when directly viewing the THD meter's residual output on an oscilloscope, but with the 20s exposure required by the scope camera, it was totally obscured by the broadband noise when photographed. In fact, the distortion is visibly virtually pure second harmonic, the figure of 0.00034% being higher due solely to the extra noise admitted in the absence of the notch box's 3kHz lowpass filter.

I will not pretend that the above performance will automatically result from the circuit shown: a number of stages of setting up are required. Firstly, the Burr Brown OPA2604 op-amps were not specially selected – only three samples were to hand – but they were swapped around for best results. (With a manufacturer's quoted typical THD + noise of 0.0003% at 1kHz, the OPA2604 fet input dual op-amp is not the lowest distortion device available. Analog Devices AD797 is supposed to deliver 0.0001% THD (-120dB) at 20kHz. But this is a bipolar input type, optimized for source impedances less than 1kΩ, which is not convenient in the present application.

Next (with the wipers of  $R_{24}$  and  $R_{25}$  set to ground),  $R_{20}$  was adjusted for minimum distortion at 20Hz, this control proving the most critical at low frequencies. It compensates for the input offset in the OTA, centring the signal in the latter and thus minimizing second harmonic distortion. It should not be left too far off centre, as there is then the possibility of control signal breakthrough appearing at the OTA output, leading to instability of the control loop in the 2-20kHz range.

The next adjustment was of  $R_{31}$ , which as already stated was included as a way of out-phasing any third harmonic at the output. However, as noted in an earlier design brief<sup>4</sup> the main distortion mechanism in the op-amps used is second order, and there was no visible

third harmonic to cancel  $R_{31}$  was therefore set to minimise the second harmonic content at 10kHz. This just leaves the circuitry associated with  $R_{24}$  and  $R_{25}$ , which has not been mentioned up till now.

Op-amp  $A_{3a}$  provides a means of deliberately producing an element of second harmonic distortion of any amplitude and at any relative phase angle over the full 360° of the fundamental to cancel residuals. This is added in via  $R_{35}$  to the virtual earth at the input of  $A_{2b}$ . With suitable settings of  $R_{24}$  and  $R_{25}$ , the distortion at the main output at 600Hz can be driven down to the point where the residual reads the same as circuit noise but this is an academic exercise. A better overall result was obtained by a compromise setting which resulted in somewhat more distortion at 600Hz but a substantial improvement (down from 0.0016%) at 10kHz.

It might be thought that the presence of  $D_2$  would make the performance unduly temperature sensitive, so a test was undertaken with the oscillator's top cover removed. The 600Hz distortion residual was monitored and hot air blown into the case, monitoring the temperature adjacent to  $D_2$ . At 50°C the distortion was unchanged from the room temperature value. The particular settings of  $R_{24}$  and  $R_{25}$  used resulted in 1.5V pk-pk at the output of  $A_{3a}$ , the waveform exhibiting a percent or so of second harmonic distortion. This is diluted by a factor of about 300 by the ratio of  $R_{33}$  to  $R_{34}$  and a

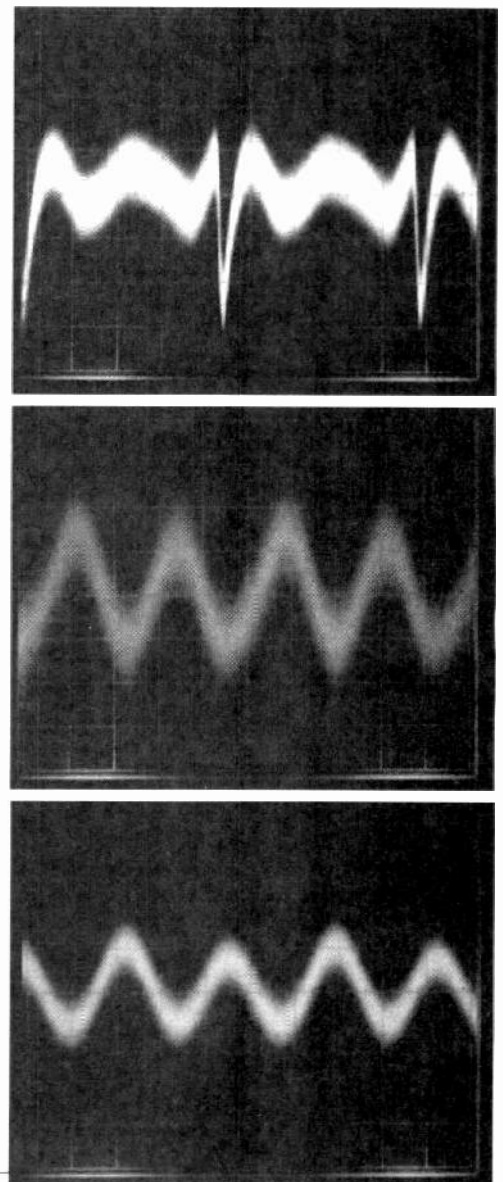


Fig. 6a. Residual distortion plus noise at 20Hz is 0.00062%.  
 b. Residual noise and 2nd + 3rd harmonic distortion with THD Meter bandwidth set to 80kHz measured 0.00092%. Note: no significant 3rd harmonic observable.  
 c. As b, but THD meter bandwidth set to 20kHz; reading 0.00062%.

# AUDIO

further factor set by the ratio of 1.5V pk-pk at  $A_{3a}$  output to the 10V pk-pk at LP, to around 0.0003%.

## Other matters

A number of practical details which arose may be of interest. An attempt to include a power supply within the case of the oscillator was a resounding failure, due to hum from the mains transformer's stray magnetic field.

Having produced a basic oscillator, it seemed sensible to include other facilities. The first of these enables the unit to be used as a quadrature oscillator - very conveniently done with an SVF based circuit. The HP output forms the 0° phase output, taken via a 560Ω resistor to a front panel BNC socket. The inverted BP output, obtained from BP by inverting stage  $A_{6b}$ , provides an output lagging by 90° - note that although  $A_{1b}$  and  $A_{2a}$ , the two integrators within the loop, each provide 90° lag, the BP waveform actually leads that at HP, as they are *inverting* integrators.

Another 560Ω resistor driven from LP provides the 180° output at a third front panel BNC socket. The instrument is also provided with an input, via a front panel socket and  $R_1$ . This may be used in two different ways. Firstly, with the oscillator running, its fre-

quency can be locked to a low level signal injected via  $R_1$ , simply by tuning it to the frequency of the injected signal.

Secondly, the oscillator can be disabled by setting  $S_2$  to the "filter" position. This has the effect of spilling  $I_{abc}$  to the negative rail, disabling the positive feedback via the OTA and stopping the oscillation. At the same time, damping is applied from inverted BP via  $R_{37}$  and  $R_{38}$ , defining the Q of the filter as  $(R_{37}+R_{38})/R_3=30$ . Since  $R_1=R_3$ , the bandpass gain from IN to the 90° OUT socket (inverted BP) should simply equal Q, the measured value at 600Hz actually being 27.

$R_8$  is a 2K wirewound two gang potentiometer fitted with a ten turn counting dial. As 10 on the dial corresponds to 200Hz, 2kHz or 20kHz it can act as a frequency readout if the dial reading is simply doubled. A dial reading of 10 can be arranged to correspond exactly to 2kHz by fitting a select on test resistor between the top end of  $R_{8a}$  (and  $R_{8b}$ ) and the op-amp output driving it. By selecting different a resistor for each frequency range (using additional poles on  $S_1$ ), the top frequency on each range can be correct, without requiring exact close tolerance values for  $C_5-C_{12}$ . Frequency readout will be almost linear, with a maximum error of -3% at five

turns, due to the loading of  $R_{11}$  ( $R_{21}$ ) on the wiper.

This parabolic error can be reduced to a much smaller cubic error by connecting a 15K resistor from the top of  $R_{8a}$  to its wiper (and likewise  $R_{8b}$ ). Some further development of the design is planned, notably affecting the fine output level control. Even using a high quality conductive plastic or cermet type,  $R_{41}$  is a possible source of excess noise in the output. A better arrangement would be a switch providing 1dB steps, with a 0-1dB continuously variable control provided by a potentiometer varying the reference voltage at the junction of  $R_{15}$ ,  $R_{16}$ . ■

## References.

1. *Phase-shifting oscillator* Roger Rosens *Wireless World* Feb. 1982 pp. 38-41
2. *Portable Distortion Monitor* J L Linsley Hood *Wireless World* July 1972 pp. 306-308
3. *Design Brief: Low distortion audio frequency oscillators* Ian Hickman *EW+WW* April 1992 pp. 345, 346.
4. *Design Brief: Audio op amp with its head in the clouds?* Ian Hickman *EW+WW* July 1992 pp. 579, 580.



**8 CAVANS WAY,  
BINLEY INDUSTRIAL ESTATE,  
COVENTRY CV3 2SF**  
Tel: 0203 650702  
Fax: 0203 650773  
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

### OSCILLOSCOPES

Gould 400 - 20MHz D.S.O. 100 Ms/s	£1000
Gould D20 - 100MHz D.S.O. 400 Ms/s	£2000
Gould OS4000, OS4200, OS4020, OS245	from £125
Hewlett Packard 1707A, 1707B - 75MHz dual ch.	from £275
Hewlett Packard 1715A - 200MHz with DMM dual ch.	£650
Hewlett Packard 1740A, 1741A, 1744A, 1744A - 100MHz dual ch.	from £350
Hewlett Packard 1745A - 100MHz dual ch. (DMM)	£450
Hewlett Packard 182C - 100MHz 4 ch.	£350
Tektronix 2201 - 20MHz D.S.O. dual ch.	£675
Tektronix 2215 - 50MHz dual ch.	£450
Tektronix 2235 - 100MHz dual ch. (portable)	£800
Tektronix 2246 - 100MHz 4 channel (as new)	£995
Tektronix 2335 - 100MHz dual ch. (portable)	£750
Tektronix 465/465B - 100MHz dual ch.	from £350
Tektronix 475 - 200MHz dual ch.	£450
Tektronix 468 - 100MHz D.S.O. dual ch.	£850
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch.	from £300
Tektronix 7704 - 250MHz 4 ch.	from £650
Tektronix 7834/7844 - 400MHz 4 ch.	from £750
Tektronix 7904 - 500MHz	from £850
Phillips 3070 - 100MHz 2 + 1 channel + cursors, as new	£900
Phillips 3206, 3211, 3212, 3217, 3226, 3240, 3243	from £125 to £350
3244, 3261, 3262 (2ch + 4 ch.)	
Solartron Schlumberger CD1740 - 20MHz 4 ch.	£250

Other scopes available too

### SPECTRUM ANALYSERS

Alltech 727 - 20GHz	£2200
Advantest TR4131 - 10KHz - 3.5GHz	£4500
Hewlett Packard 3580A - 5Hz - 50KHz	£1250
Hewlett Packard 3585A - 20Hz - 40MHz (GPIB)	£4250
Hewlett Packard 8590A - 10MHz - 1.5GHz (as new)	£4500
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
£4500	
Hewlett Packard 141T with 8554B/8552B - (1250MHz)	£1500
Marconi 2370 - 110MHz	£1250
Hewlett Packard 4953 Protocol analyser	£2500
Tescan AL51A - 1GHz	£1300

### MISCELLANEOUS

Anritsu ML93B/ML92B Optical power meter with sensor	£2000
Anritsu ME538C Microwave system analyser (Rx + Tx)	£3500
B&K 2511 + 1621 Vibration test set	£2000
B&K 2511 Vibration meter	£1500
B&K 2515 Vibration analyser	£4500
Datron 1061A Autocal digital multimeter (6 1/2 digits)	£850
Datron 1071 Autocal digital multimeter (7 1/2 digits)	£1150
Daymarc 1735 Transistor tester/sorter (with all jigs)	£5000
Dranetz 305 Phase meter	£250
Dymar 1585 AF Power meter	£175
Dymar 2085 AF Power meter	£200
Farnell RB 1030-35 Electronic load 1Kw	£450

Farnell AMM/B Automatic modulation meter	£150
Farnell 2081 R/F Power meter	POA
Feedback TWG300 Test waveform generator	£200
Fischer Betascope 2040/2060 Coating thickness computer & non destructive coating measurement instrument & many jigs and extras	all for £2000
Fluke 8840A Multimeter (1EEE)	£300
Fluke 515A Portable calibrator	£500
Fluke 5200A Programmable AC calibrator	POA
Fluke 8010A Digital multimeter	£125
Fluke 8922A True RMS voltmeter	POA
Fluke 95020 Current shunt	POA
Gay Milano FTMC/FTMSC - FTM - Fast transient monitor	£250
General Rad 1658 LCR Digital bridge	£250
General Rad 1621 Precision capacitance measurement system	POA
Hewlett Packard 180TR Display unit with 87555 swept. amp. an.	£375
Hewlett Packard 3200B VHF oscillator, 10-500MHz	£175
Hewlett Packard 3325A Synthesizer/Function generator	£1450
Hewlett Packard 3400A RMS voltmeter	£150
Hewlett Packard 3406A Broadband sampling voltmeter	£175
Hewlett Packard 3437A System voltmeter	£350
Hewlett Packard 3476A Digital multimeter	£100
Hewlett Packard 3478A Digital voltmeter, 4 wire system, 1EEE	£650
Hewlett Packard 3490 Digital multimeter	POA
Hewlett Packard 3702B/3705A/3710A/3716A Microwave link analyser	£1500
Hewlett Packard 3730A Down converter (with 3738A or 3737A)	£250
Hewlett Packard 3760/3761 Data gen + error detector	each £300
Hewlett Packard 3762/3763 Data gen + error detector	each £350
Hewlett Packard 3777A Channel selector	£250
Hewlett Packard 3779A Primary multiplex analyser	£800
Hewlett Packard 400E/F AC voltmeter	£150
Hewlett Packard 4193A Vector impedance meter	£3500
Hewlett Packard 4204A Oscillator 10Hz - 1MHz	£250
Hewlett Packard 435A Power meter (less sensor)	£350
Hewlett Packard 456A AC current probe	POA
Hewlett Packard 415E SWR meter	£275
Hewlett Packard 5335A Universal counter with 1EEE	£1800
Hewlett Packard 5342A Microwave freq. count. 18GHz	£1400
Hewlett Packard 7402 Recorder with 17401A x 2 plug-ins	£300
Hewlett Packard 8005B Pulse generator	£250
Hewlett Packard 8011A Pulse gen 0.1Hz - 20MHz	£500
Hewlett Packard 8012B Pulse generator	£750
Hewlett Packard 8013B Pulse gen. 1Hz - 50MHz	£750
Hewlett Packard 8406A Frequency comb generator	£500
Hewlett Packard 8443A Tracking gen/counter with 1EEE	£450
Hewlett Packard 8445B Automatic presetter	£700
Hewlett Packard 8601A 110MHz Gen/sweeper 110MHz	£350
Hewlett Packard 8620C Sweep oscillator mainframe	£250
Hewlett Packard 8750A Storage normaliser	£400
Hewlett Packard 938A Freq. doubler	£250
Hewlett Packard 8640B with opt 001	£825
Kethley 197 20MHz with 1EEE	£400
Lytone PG75N/PG75/PG28/PG Pulse generator	from £225
Marconi 2019A 80KHz - 1040MHz sig. gen.	£1800
Marconi 2306 Programmable interface	£500
Marconi 2337 Automatic dist. meter	POA
Marconi 2356 20MHz level oscillator	£300
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2610 True RMS voltmeter	£900
Marconi 2820 Multiplex tester	£1250
Marconi 2831 Channel access switch	£500
Marconi 5390 1GHz signal gen.	£1250
Marconi 6920 Power sensor	£400
Marconi 2022E (10KHz-1.01GHz) sig. gen.	£1850

Marconi 2019A (10KHz-1.04GHz) sig. gen.	£1850
Phillips PM 2525 Multimeter WF 1EEE	£850
Phillips PM 5167 10MHz functiongen	£400
Phillips PM 5190 LF synthesizer with GPIB	£800
Phillips PM 5519 Colour TV pattern gen	£400
Phillips PM 5716 Pulse generator high freq. mos	£600
Phillips PM 5770 Pulse gen. - 1MHz - 100MHz	£150
Phillips PM 6672 1GHz timer/counter WF 1EEE	£650
Phillips PM 8272 XYT chart recorder	£500
Photodyne 800 Fibre optic attenuator	£350
Projectline CH9345 Microscope	£800
Racal Dana 202 Logic analyser + 68000 disassembler	£250
Racal Dana 3100 46-130MHz synthesiser	£750
Racal Dana 5002 Midband level meter	£650
Racal Dana 5003 Digital micrometer	£150
Racal Dana 9000 Microprocessing timer/count. 52MHz	£250
Racal Dana 9009 Modulation meter	£225
Racal Dana 9081 Synth. sig. gen. 520MHz	£550
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9246S Programmable PSU 25V-10A	£400
Racal Dana 9303 True RMS/RF level meter	£650
Racal Dana 9347 LCR databridge	£250
Racal Dana 9500 Universal timer/counter 100MHz	£200
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9919 UHF frequency meter 1GHz	£275
Rohde & Schwarz BK36711 Digital Q meter	£400
Solartron Schlumb 1170 Freq. response analyser	£500
Tektronix TM503, SC503, PG506, TG501 Scope calibrator	£2200
Tektronix 834 Data comms analyser	£500
W&G SPM12 Level meter 200Hz-6MHz	£500
W&G PS12 Level generator 20Hz-6MHz	£500
W&G SPM60 Level meter 6KHz-18.6MHz	£500
W&G PS60 Level generator 6KHz-18.6MHz	£500
W&G PS6 Level generator 6KHz-18.6MHz	£250
W&G SPM6 Level meter 6KHz-18.6MHz	£250
Watanabe WTR211 3 pen plotter	£250
Wavetek 157 Programmable waveform synthesiser	£300
Wayne Kerr B42N/LCR Component meter set	£200
Wayne Kerr 4250 LCR meter (as new)	£1000
Wayne Kerr 642 Autobalance universal bridge	£200
Wayne Kerr B905 Automatic precision bridge	£800
Weller D800/D801 Desoldering station	£175
Weller D900 Desoldering station	£150
Wiltron 352 Low freq. differential input phase meter	£350

**SPECIAL OFFERS - Phoenix 5500A Telecoms analyser, ex. demo, as new with 12 months calibration + 12 months guarantee fitted with V24 interface. A variety of interface options available - Ring/Fax for details. Navtel 9440 Protocol analyser, ex. demo, as new £8000 new - cost now £3500. Navtel 9410 PCB based protocol analyser ex. demo, as new £3000 new - cost now £1500.**

**MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS**

CIRCLE NO. 109 ON REPLY CARD

# Power switching in SM packaging

Working towards maximum reliability, designers try to minimise the number of moving parts in their products. Nevertheless there is boom in tiny mechanisms. Hard and floppy disk drives, laptop printers, CD drives, cassette players and fax machines are just a few examples where miniature motors and solenoids are found in abundance.

Proportional to the boom in miniature moving electrical parts is the rise in demand for transistors to switch them. Even small motors, solenoids and lamps can demand significant power, particularly at switch on. High power dissipation and surface-mount PCBs however are incompatible. In SM applications, adding heat sinking or moving the power switching transistor to a cooler location is expensive. As a result, demand is highest for SM transistors that can switch more power without dissipating more heat.

A perfect transistor switches gigawatt loads without heating up. In practice, a number of parameters influence heat dissipation in switching transistors, saturation voltage being the primary factor. Mounted in traditional SOT23 surface-mount packaging, a transistor with a typical 0.5V saturation voltage is limited to a continuous current capability of less than an amp. Any further current causes the device's dissipation capability of less than half a watt to be exceeded.

By reducing saturation voltage and increasing power dissipation, Zetex has produced surface-mount transistors capable of switching resistive loads up to 100W with almost double the efficiency of conventional SOT23 devices.

Gain hold-up can also affect dissipation. As current through a transistor increases, its gain falls. This means that base current needed to achieve full saturation rises disproportionately with increasing collector current. If base current falls below the level needed to turn the transistor hard on at high currents, dissipation increases rapidly. The table and Fig. 1 show that gain of the *FMMT* transistors is significantly higher than other popular devices which also have much larger packages.

**Superior bipolar chip technology and enhanced lead-frame design have contributed to Super SOT – a new surface-mount transistor family with almost double the performance of its contemporaries. Martin Eccles reports.**

	FMMT618	FMMT619	BCX54	BCP54
Package	SOT23	SOT23	SOT89	SOT223
$V_{CE0}$	20V	50V	45V	45V
$I_C$	2.5A	2A	1A	1A
$I_{C(max)}$	6A	6A	1.5A	1.5A
$h_{FE(min)}$	200@2A	200@1A	25@0.5A	25@0.5A
$V_{CE(sat)}$	50mV	200mV	500mV	500mV
max @ $I_C$	@1A	@1A	@0.5A	@0.5A
$P_{tot}$	625mW	625mW	1W	1.5W

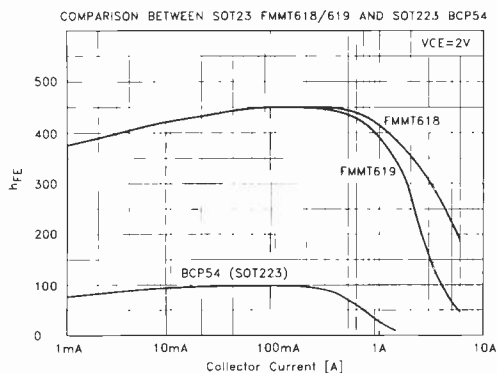


Fig. 1. Large-chip SM transistors like the BCP54 can handle the current but at a little over an amp their gain is no longer useful. The curve for the BCX54 is similar to that of the BCP device shown.

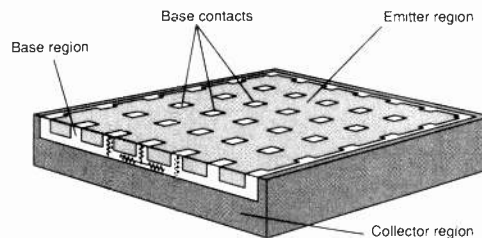


Fig. 2. In the matrix design, tiny current sinks are distributed evenly throughout the emitter region to ensure uniform current distribution without loss of emitter area. Saturation resistance is significantly reduced.

## Advanced lead-frame design

By optimising thermal conductivity of the SOT23 package lead frame, Zetex has arrived at a SOT23 package with performance. To achieve this, the standard silver or gold patch plating of the lead form has been replaced by highly conductive plating. This reduces junction-to-case thermal resistance from 280°C/W to only 100°C/W.

This improvement in thermal resistance allows the package to dissipate 625mW when mounted on a ceramic substrate measuring only 15 by 15 by 0.6mm, or 1.25W on an infinite heatsink. The industry norm for SOT23 packaged devices is 300mW. For a given power dissipation, the devices run cooler than comparable products due to their low saturation voltage. Cooler operation allows increased packing densities, and in turn higher reliability and lower costs.

## Matrix design


Pioneered by Zetex, the matrix chip design has had an important influence on performance, achieving even better results than large-emitter designs but without the inherent disadvantages.

In the matrix design, current distribution is uniform across the chip but there is no loss of emitter area. The ideal matrix chip is composed of an infinite matrix of vanishingly small current sinks distributed evenly throughout the emitter region, Fig. 2.


Base current is extracted through the current sinks. It is possible to fill over 90% of the base region with active emitter, achieving at the same time uniform current distribution. This reduces the saturation resistance of the transistor to such an extent that previously insignificant components of resistance become dominant. Detailed analysis of these components has led to reduction in saturation resistance.

## Applications


Having a low saturation voltage and high current capability, the 20V *FMMT618* is useful in battery-powered applications. It can carry up

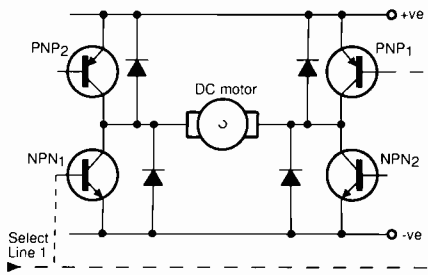


**Fig. 3.** Typical H-bridge driver allows full single-rail supply voltage to be applied to the motor in either polarity. Diodes may be needed to protect the transistors from transients.

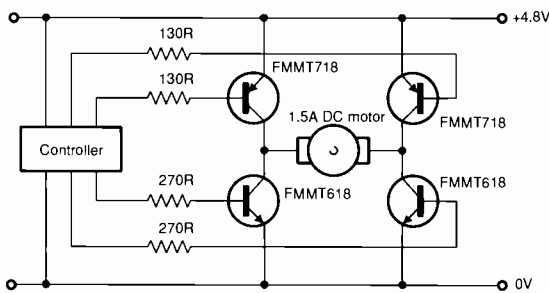


**Fig. 4.** Base resistors in this H-bridge motor controller are selected to suit maximum output current expected. Protection diodes are not needed since the transistors can absorb inductive transients.

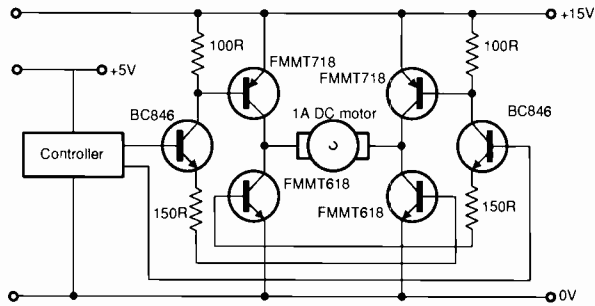

**Fig. 5.** A transistor's gain falls as its  $V_{CE}$  rises so current needed to drive the H-bridge pairs can increase above that available from logic ICs. With this arrangement, only two extra transistors are needed to buffer all four bridge devices.

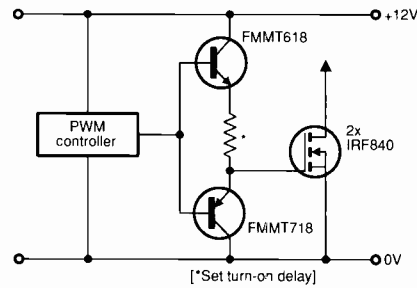

**Fig. 6.** Real input capacitance of a power mosfet gate can rise to nanofarad levels, causing significant problems if fast switching is needed. A driver pair combining high gain and high current capability can overcome this problem with a minimum of components.

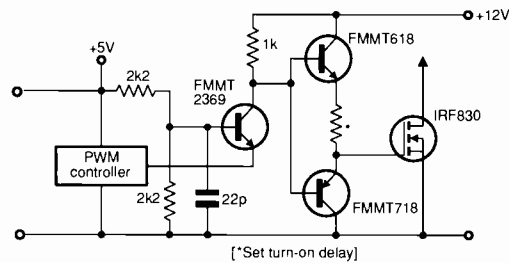

**Fig. 7.** In some cases, 5V logic levels cannot provide enough gate voltage swing for efficient switching. The pre-driver transistor has to have a very low storage time, resulting in a total-circuit turn-on time of only 20ns when driving a 2nF-input mosfet.

to 2.5A continuously and has a typical saturation rating of 130mV. Minimum gain at 2A is 200. Even at the device's peak current rating of 6A, gain is still more than 100.

Further devices in the current *SuperSOT* range are the 50V *FM619* and four pnp types with 20, 40, 70 and 100V ratings and current handling capabilities between 1 and 1.5A.

**H-bridge motor drive.** Motor drivers in H-bridge format are used in a wide range of products such as disk drives, toys, coin-control mechanisms and servo systems. They provide bidirectional outputs from single-polarity supplies, usually under digital logic control.

Two npn/pnp pairs are normally used, all operating in grounded-emitter mode. By turning on one npn device and its diametrically-opposed opposite pnp device, virtually all the supply voltage can be applied across the motor. Switching the second pair reverses the supply to the motor, **Fig. 3**. Often, H-bridge transistors need collector-emitter diodes to protect them from regenerative currents and transients stemming from the motor.

In battery-powered applications, it is vital that as much of the supply voltage as possible is applied across the load. This maximises battery life through greater efficiency and minimises the effects of falling battery voltage.

With an *FM618/718* pair, the circuit of **Fig. 4** will handle load or stall currents to

1.5A. Adapting the circuit for lower current motors is simply a matter of increasing the base resistor values. Base current at maximum load should be 2% of collector current for the pnp types and 1% for the npns.

Saturation losses at 1.5A total only 0.3V and can easily be halved for lower load currents. If the circuit is used to deliver high current, logic drivers need to be able to deliver 30mA. The diodes are unnecessary since the transistor reverse voltage rating is high enough to handle transients.

**Figure 5** is for higher supply voltages or applications where logic output drive is insufficient to drive the previous circuit. Low-cost buffer/level-translators have been added. These compensate for the fall-off in gain with increasing supply voltage, which is inherent in all transistors.

**Mosfet gate drive.** Input capacitances of power mosfets and igbts can rise as high as tens of nanofarads. When Miller effects – i.e. amplification of feedback capacitance – are taken into account, by using the more valid method of evaluating gate charge as opposed to  $C_{iss}$  for calculating effective input capacitance, values around three times higher are obtained.

To minimise switching losses, particularly in high frequency converters, it is vital that the gate capacitances are charged and discharged as rapidly as possible. Consequently driver cir-

cuits must act as low impedance voltage sources, capable of supplying large transient charge currents.

Since standard switching power supply control ICs are rarely able to drive larger capacitance mosfets adequately, a high speed buffer is often used.

Complementary emitter followers as shown in **Fig. 6** can act as an ideal buffer provided that transistors of high current capability combined with high  $f_T$  are used. Combined, the *FM618* and *FM718* have these characteristics. The 10nF effective capacitance of two *IRF840* mosfets in parallel can be charged to 12V in under 30ns – a feat requiring a peak current of around 4A. Included in the circuit is a resistor for introducing a turn-on delay without affecting turn-off performance. This component is sometimes needed to avoid cross conduction problems in push-pull output stages.

Where 5V logic provides a pulse-width modulation, a buffer can be necessary to translate level, giving 10V or greater gate drive for the power switches. By using an *FM2369* switching transistor, the circuit shown in **Fig. 7** converts 5V logic drive to a 12V gate drive signal. Driving the emitter of the 2369 from the logic output avoids signal inversion.

Storage time of the switching transistor is very short. This combines with the high gain *FM618* to give the circuit a turn-on time of only 20ns when driving a mosfet with an

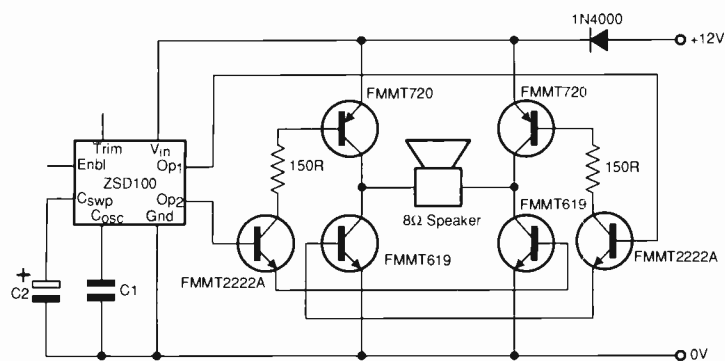


Fig. 8. Burglar-alarm siren drive for an 8Ω loudspeaker is normally provided by large TO126 or TO220 packaged transistors. Using FMMT transistors not only reduces cost and size but also eliminates the need for protection diodes.

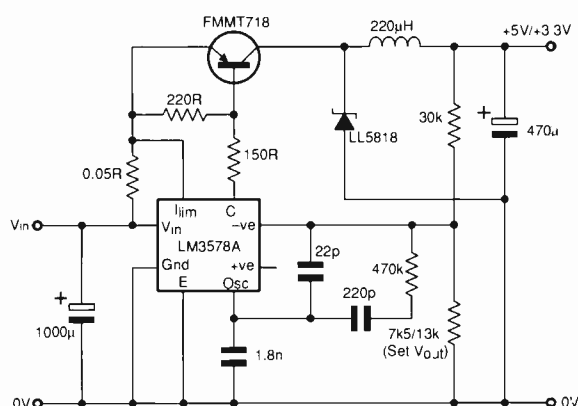


Fig. 9. In battery-powered DC converters, the key to maximising efficiency is to minimise voltage drops over all high-current paths. Next to the inductor, saturation voltage in the switching transistor is usually the biggest loss contributor.

effective input capacitance of 2nF. The FMMT718 helps make turn-off times even shorter, leading to reduced cross-conduction problems in bridge or push-pull converters.

By providing excellent high-current performance in a SOT23 package, the FMMT618 and FMMT718 replace SOT223 and SOT89 transistors in these gate drive circuits leading to cost and PCB area savings – particularly in very high frequency converters.

**H-Bridge Siren Driver.** Many modern burglar and automotive alarm sirens employ an 8Ω moving coil loudspeaker driven by a bipolar H-bridge. Handling peak output currents of 2A, traditional TO126 or TO220 packaged output transistors require parallel collector-emitter diodes. These are needed to divert destructive reverse transients generated by the inductive load.

In Fig. 8, FMMT619 and FMMT720 transistors in SOT23 packaging replace these bulky and expensive leaded transistors, giving other savings too. High reverse  $h_{FE}$ , inherent in matrix technology, eliminates the need for parallel collector-emitter protection diodes. Both FMMT619 and FMMT720 transistors conduct reverse collector current sufficiently well to clamp any inductive transients generated by the load.

A specially designed Zetex ASIC provides a variable frequency drive to the SOT23 H-bridge ensuring a very loud and irritating

noise. The combination of an ASIC signal generator and SOT23 H-bridge produces a compact and inexpensive module.

**DC-DC Converter.** Using standard PWM controllers, it is easy to construct buck-type step-down converters with low component counts. Harder to achieve are designs that are both simple and efficient – as required for modern battery-operated equipment. The key to maximising efficiency is eliminating voltage drops in all high current areas.

In the buck converter shown in Fig. 9, the high current paths are via the 50mΩ sense resistor, the series switching transistor output inductor  $L_1$  and the schottky diode. Once resistance of the output inductor has been minimised the most critical aspect is the saturation voltage drop of the switching transistor. Saturation is particularly important when  $V_{IN}$  approaches  $V_{OUT}$ .

By using an FMMT718, which drops only 200mV @ 1.5A, this converter can operate at an efficiency of over 90% at minimum input voltage and an  $I_{OUT}$  of 1.5A. Even when output current has fallen to 200mA, efficiency is still around 80%.

As input voltage increases, the operating gain of the switching transistor becomes more important. The high gain of this transistor minimises base drive losses, leading to high efficiencies over a wide supply range.

Fast rise and fall times of the FMMT718

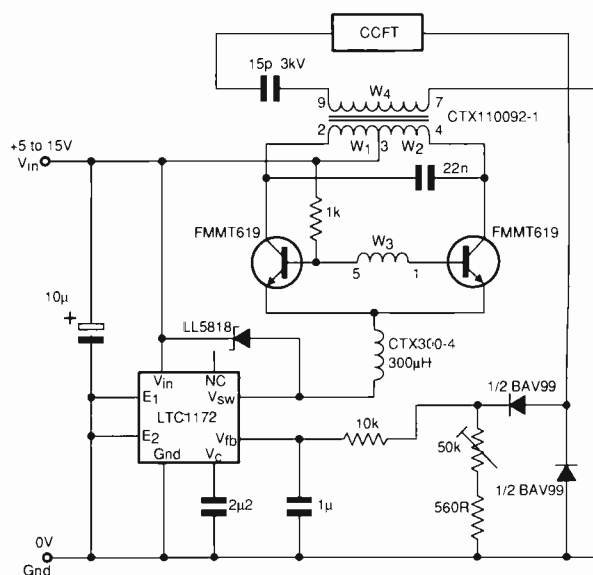


Fig. 10. Driving a cold-cathode fluorescent lamp used in, say, computer backlighting, needs an efficient, compact converter. This design originally had SOT223 BCP65 transistors. Replacing them with smaller FMMT types reduced saturation voltage by half.

allow the converter to operate at 50kHz with minimal switching losses. At this frequency it is essential to use low ESR input and output capacitors and keep any wires carrying switched high currents very short so as to minimise rfi and output ripple.


The converter will operate from a supply of  $V_{OUT}+0.5V$  up to 16V. Its output voltage can be set to 5V or 3.3V by altering the value of  $R_1$ . The circuit will supply loads from 0 to 1.5A, current limiting to around 2A with a shorted output.

**LCD backlighting converter.** Cold-cathode fluorescent lamps used for portable computer led backlighting and similar applications require a converter generating between 1 and 2kV to strike and run.

Standard circuits provide control of tube brightness against input supply variations and other factors such as temperature, tube ageing etc. These circuits commonly use SOT223 transistors in the high voltage converter. This is because high currents must be passed with minimal saturation losses if good efficiency is to be achieved.

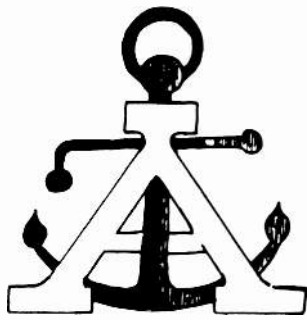In Fig. 10, SOT223 BCP56 transistors have been replaced with smaller FMMT619 SOT23 types. Exhibiting a saturation voltage of only 125mV at 1A – less than half that of the BCP56 – the FMMT619 not only reduces cost and PCB area, but also raises efficiency of the converter. ■





**ANCHOR SURPLUS LTD  
THE CATTLE MARKET  
NOTTINGHAM  
NG2 3GY**



**TEL: (0602) 864902 & 864041  
FAX: (0602) 864667**

## **SPECIAL OFFERS**

### **HEWLETT PACKARD SPECTRUM ANALYSERS**

1KHz - 110MHz (HP141T+8552B+8553A)=**£545.00**  
 100KHz - 1250MHz (HP141T+8552B+8554B)=**£995.00**  
 10MHz - 18GHz (HP141T+8552B+8555A)=**£1295.00**  
 8565A - 10MHz-22.9GHz Synthesised digital=**£3250.00**

### **FARNELL DSG2 Digital Signal Generators**

0.1mHz-110KHz Synthesised, Sine/Square, md GPIB ..... **£150.00**

**ALL SYSTEMS TESTED WITH VERIFIED CALIBRATION**

**MARCONI TF2018 Signal Generators 80KHz - 520MHz Synthesised ..... £650.00**

**MARCONI TF2019 Signal Generators 80KHz - 1040MHz Synthesised ..... £1250.00**

**HEWLETT PACKARD 8616A MicroWave Generators 1.8GHz - 4.5GHz ..... £175.00**

**GIGA GR1101A MicroWave Synthesised Generators 12.0GHz - 18GHz ..... £450.00**

**BIRD 4381 Digital RF Analyser ..... £175.00**

**HEWLETT PACKARD 5256A Frequency Converters 8GHz - 18GHz for HP Counters ..... £75.00**

### **COUNTER TIMERS**

**FLUKE 1952B Universal counter timers 7 digit LED tested to 80MHz ..... £65.00**

**FLUKE 1953A Universal counter timers 8 digit LED tested to 175MHz ..... £75.00**

### **RACAL DANA 9904 50MHz Universal Counter Timers**

LED Readout with TXO Reference Oscillators ..... **now only £75.00**

### **RACAL DANA 9915M 600MHz UHF Frequency Counters**

8 Digit LED Readout with TXO ..... **£125.00**

### **SYSTRON DONNER 6053 UHF Digital Frequency Counters**

20Hz to 3000MHz Tube Readout ..... **£275.00**

**ALL EQUIPMENT IS FULLY TESTED WITH VERIFIED CALIBRATION  
AND COMES WITH OUR 30 DAY UNCONDITIONAL WARRANTY.**

**ALL PRICES EXCLUDE VAT AND CARRIAGE**



CIRCLE NO. 110 ON REPLY CARD

# USING RF TRANSISTORS

## Getting a grip on instability and load mismatch

*Instability in solid state amplifiers may well be the most difficult problem a designer must face. Norm Dye and Helge Granberg review some common causes. The authors also explain the practical implications of using the vswr bridge to handle load mismatching. From the book RF Transistors: principles and practical applications.*

Engineers sometimes talk about unconditional stability, where no matter what the load is, the amplifier does not exhibit spurious oscillations even with drive levels and supply voltages outside nominal values. But such conditions rarely exist with rf amplifiers – except possibly in low power class A designs.

Instabilities can be observed in several ways. Some types may be too low in amplitude to be detected with anything but a spectrum analyser, or may appear only outside the nominal level of drive power and supply voltage. But others may become apparent through erratic tuning (if tuning elements are provided) or if current is being drawn when the drive power is removed.

At least three variables affect amplifier stability: the load ( $R$  and  $X$ ); drive level and supply voltage. In mobile communications the nominal supply voltage is 12.5V, but can vary down to as 10.5V or as high as 16V.

With low level amplitude modulation and ssb, effective drive power varies with modulation. High level AM collector/drain voltage varies between zero and the maximum.

Taking into account the two latter variables, plus the  $R$  and phase angle ( $X$ ) of the load, we can see how difficult it is to design a stable rf amplifier operating under these conditions. Many designers have spent hundreds of hours trying to get an amplifier to meet a stability specification even at 3:1 load mismatch.

Putting aside the drive level and supply voltage variables for a moment, it is relatively easy to reach stability in an amplifier operating into a resistive (usually  $50\Omega$ ) load.

But in real life, there is always some load mismatch. In communications, for example, the load is an antenna connected to the amplifier output through a harmonic filter. In industrial and medical applications the load can

consist of various types of matching networks presenting, at least momentarily, an undefinable load to the amplifier.


Amplifiers designed for frequency modulated communications have one fewer variable because the power input remains constant. This should make design of stable amplifiers for FM somewhat easier than for AM. Several types of instability can be identified in rf amplifiers, some are circuit or layout oriented; some are device oriented or may be a combination of both.

Many oscillation modes depend strongly on non-linear effects. So they can be very difficult to analyse compared with the small-signal feedback type oscillations that are adaptable to linear circuit analysis.

Ratio of feedback capacitance to input impedance (feedback capacitance to input capacitance in a mosfet) in a power transistor determines much of its stability criteria. The higher the ratio, the greater the possibility for device stability. Normally feedback capacitance introduces negative feedback, reducing power gain. But at certain frequencies the feedback will turn positive due to phase delays. Clearly, devices with higher ratios of feedback capacitance to input impedance will exhibit the most stability.

Transistors processed for low voltage operation generally have lower ratios, making stability in 12.5V systems more elusive than in, say, a 50V design. For bipolar transistors, feedback capacitance is not given in data sheets because it is not easy to measure. It is a function of many parameters such as device geometry, types and values of emitter ballast resistors and the silicon material resistivity. The ratio of input impedance/capacitance to feedback capacitance is somewhat higher with mosfets rather than bjts, and so mosfets are more stable in this respect.

*Fig. 1. Low frequency instability. Frequency  $f_1$  is mixed with the carrier ( $f_0$ ) which produces a series of sidebands around  $f_0$ .*

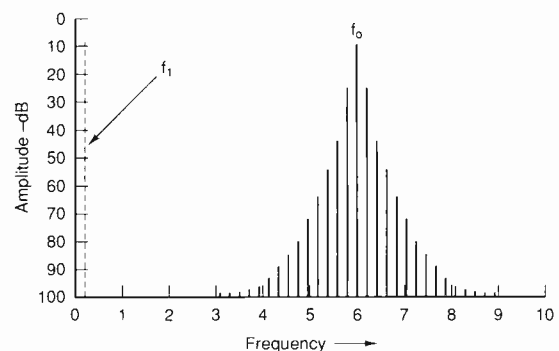

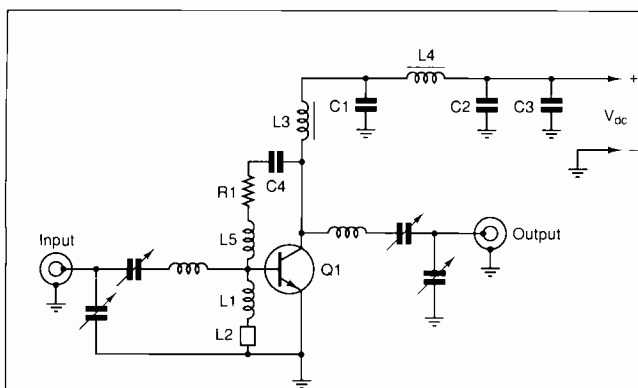


Fig. 2. Typical rf amplifier showing the appropriate dc feed structures and a negative feedback network.

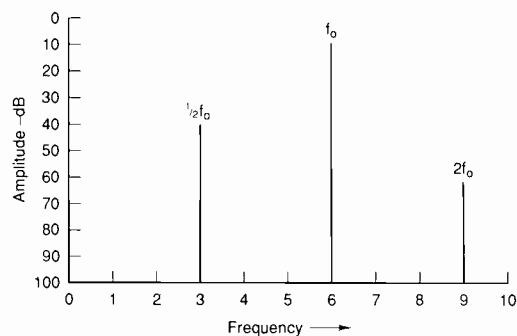


Fig. 3. Display of half  $f_0$  instability, caused by varactor effects primarily in the base-emitter junction.

**Low frequency factors**

One of the most common instabilities occurs at low frequencies (1-10MHz), where device power gain – assuming use of vhf or higher frequency transistors – can be as high as 30-40dB.

Oscillation can be strong, but noticeable only by its mixing products with fundamental  $f_0$  (Fig. 1). In professional circles this display is referred to as a Christmas tree, the width of its skirts depending on amplifier bandwidth.

Frequency of oscillation,  $f_1$ , (Fig. 1) can be high in amplitude, but may not be detected on a spectrum analyser because of bandwidth limitations of the circuit. In some instances this low frequency oscillation can be strong enough to cause a transistor to exceed its dissipation limits and destroy itself.

It is a mode of instability that is almost completely circuit-oriented and is mostly preventable by controlling the low frequency power gain of the amplifier.

Selecting a transistor with low  $h_{FE}$ , controls low frequency gain, but has a minimal effect at high frequencies. Conversely, the emitter/source inductance and resistance have a larger effect in the device's high frequency gain and a lesser effect at low frequencies. Keep these values at their minimum for best amplifier high frequency performance.

Low frequency gain of the amplifier can be lowered by certain simple design practices – though the available gain of the device itself remains unchanged. In a typical rf amplifier, values of the most critical dc feed elements ( $L_1$  and  $L_3$ , Fig. 2) should be selected to block the low frequencies, where device gain is considerably higher than it is at the frequency to be amplified. Values should be as low as possible without resulting in any loss in power gain or efficiency.

To be on the safe side, reactances should not exceed 5-10 times the impedances at the base and collector.

$Q$  values of  $L_1$  and  $L_3$  must also be controllable. If this cannot be done with lossy ferrite beads ( $L_2$  for example), parallel resistances can be used.

Common practice is to wind the chokes ( $L_1$  and  $L_3$ ) over low valued (10-50Ω) non-inductive resistors. This is particularly so for the collector feed choke ( $L_3$ ) where a lossy ferrite

head may face excessive heating at the high power level.

$C_1$  (Fig. 2) must have a large enough value to bypass these low frequencies to ground. To avoid possible resonances, multiple capacitors of different values (0.01 and 0.1μF for example) are sometimes paralleled.

Reactance of  $L_4$  is high enough to pass a minimum of the low frequencies. In fact, it should be as large as possible up to the point where its losses start producing excessive dc voltage drop.

Capacitors  $C_2$  and  $C_3$  again are two different values and paralleled to avoid resonances. Their values should be large enough to bypass all low frequencies to ground.

The  $L_4/C_2/C_3$  network should prevent any rf from feeding back to the dc power source.

Another more effective means of reducing low frequency gain of an rf amplifier is to introduce negative feedback – the purpose of  $C_4/R_1/L_5$  network in Fig. 2.  $C_4$  is merely a dc blocking capacitor. Its value is not critical, except it must be large enough to provide a low reactance at low frequencies.

Feedback slope is controlled by  $L_5$ , whose function is based on its increasing reactance with frequency.  $L_5$  is determined to produce minimum feedback at the operating frequency and maximum feedback at low frequencies, where its reactance is low.

Resistor  $R_1$  controls the overall level of the feedback, and its value is normally very low, except where it is used in conjunction with  $L_5$  to control the gain slope.

Another cause for low frequency instabilities can be the physical layout of the circuit.

**Benefits of good layout**

The most important point in rf amplifier layout is to provide a solid ground plane. A good ground plane will minimise generation of rf ground loops that can feed rf energy back to the input in a phase that would make an oscillator out of the amplifier.

In most cases this problem can be fixed only by making a new circuit layout – which generally proves costly.

Excessively high matching network  $Q$ s, and high  $Q$ s of the dc feed networks (if the input and output networks happen to resonate) can also result in self-oscillations at some inter-

mediate frequency. But these high  $Q$ s can be prevented by following proper design guidelines.

Proper design can also prevent inductively induced feedback. Such instability is more common in hf and vhf amplifiers, with lumped constant matching elements than in, for example, microstrip designs. Enough rf energy can be coupled to the inductor(s) of the input matching network, from the output, to trigger an oscillation.

Oscillation occurs at a frequency where the input-output phases approach  $360^\circ$  – though it may not be enough to destroy the transistor. It usually disappears and snaps to the driven frequency when input drive is applied.

A way to prevent oscillations, is to locate the input and output matching networks physically as far apart as possible, while orienting the inductors of the input and output networks in  $90^\circ$  angles. Electrostatic shielding may also be useful, though it has only proven effective in small-signal designs.

**Varactor effect instability**

In addition to multiplication, a varactor multiplier can also generate sub-frequencies if a selective circuit is provided for those frequencies. The effect is known as varactor instability, and implies that there are  $2.f_0$  and  $3.f_0$  products present, though they would fall on the harmonics and would be hard to distinguish. Their amplitudes are probably much lower than that of the  $0.5 \times f_0$ , since system power gain is much lower at these higher frequencies.

Instead, a stronger  $0.5 \times f_0$  spur is generated since in most cases the bandwidth extends to those frequencies and sufficient power gain is available (Fig. 3). The  $0.5 \times f_0$  oscillation is usually of a fairly low amplitude and does not noticeably affect amplifier performance. There is no real cure for it, and it is most likely to occur in low gain amplifiers of classes B and C. One possibility may be to add a half frequency band reject filter to the amplifier output. But this only works in relatively narrow band designs.

In classes AB and A, the diode junctions do not go out of forward-conduction and the  $0.5 \times f_0$  phenomenon does not usually occur.

The ideal approach is to use a diplexer to

provide a proper resistive load for the amplifier at its harmonic frequencies even if there is a load mismatch at  $f_0$ .

Another common practice in rf amplifier stabilisation is to insert a resistive attenuator between amplifier output and load. The attenuation need only be 1-2dB. But there is always a power loss and so the technique is practical only where stability is more important than system efficiency.

Advantage of resistive loading is that in addition to isolation, the resistive load (although not  $50\Omega$ ) is provided for the amplifier at all frequencies.

For 1dB attenuation, the resistor would have a value of  $440\Omega$ , while for 2dB the value would become  $220\Omega$ .

### Testing stability

Testing an amplifier for instabilities can be accomplished by using a spectrum analyser to see the spurious responses (if any). An LC network can simulate a load mismatch having a reflection coefficient of near unity in magnitude and all possible phase angles. Any value of load mismatch can be realised by inserting an attenuator between the amplifier output and the complete mismatch simulator (Fig. 4).

Generally, at uhf and microwave frequencies, the desired magnitude of reflection coefficient is achieved by a transmission line attenuator terminated in a short circuit. Variation in phase angle of the load reflection coefficient is accomplished with a line stretcher.

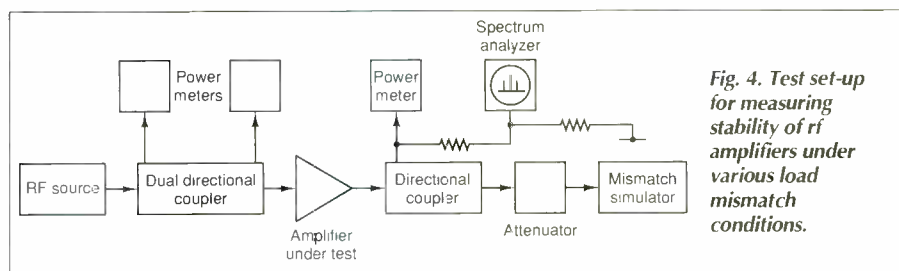


Fig. 4. Test set-up for measuring stability of rf amplifiers under various load mismatch conditions.

Class C amplifiers operating at low voltages are the least stable and high voltage units of classes A and AB exhibit the best stability. Complete stability (no spurious oscillations) of a low voltage class C amplifier into a 3:1 load mismatch would be acceptable, and into 5:1 would be excellent.

Stability of an amplifier can be analysed using large-scale S-parameters. But this will not help in design. Many variables affect stability and since it is largely circuit-layout and component dependent, computer-aided design gives no guarantee of a stable amplifier. If stability measurements are unacceptable, there is little to be done except go back to the drawing board. Circuit design must be re-examined, including board layout, following the proven guidelines.

### VSWR protection in load mismatching

Most transistors fail in solid state amplifiers at load mismatch phase angles that present a high current mode of operation to the output

transistor(s). The result is an increase in power dissipated by the transistor(s).

Since the temperature time constant of a typical rf power transistor die is 0.5-1.0ms, any protection system (including all delays in the agc/alc loop) must react faster than this.

Several methods can be used for protecting solid state rf power amplifiers against load mismatches, but reflectometer vswr sensing is most common.

The reflectometer is usually located in series between amplifier-output and load, and produces a voltage proportional to the amount of output mismatch. This voltage is processed and then fed back to either the power amplifier input, or one of the preceding stages, gradually reducing the power gain or completely shutting down the amplifier.

The standard reflectometer principle used here to detect rf power amplifier output mismatch is commonly known as a vswr bridge. With proper mechanical design, its use can be extended to microwave frequencies (greater

## Matching networks in practice

Design calculations for matching networks can become completely meaningless unless the network components are measured at the operating frequency. For example, a 100pF silver mica capacitor that meets all specifications at 1MHz can have an effective capacitance of 300pF at 100MHz, due to its series inductance. At some frequency, this inductance will tune out the capacitance altogether leaving the capacitor with a net inductive reactance.

Values of inductance in the low nanohenry range are also difficult to achieve, since the inductance of a 25mm straight piece of AWG #20 solid copper wire is approximately 20nH. Component tolerances have no meaning at vhf frequencies and above, unless they are specified at the operating frequency.

Unencapsulated mica capacitors – Unelco, Underwood, Standec, Imenco, Semco – are widely used in rf designs, from low band to uhf. They are more rugged than ceramic chip capacitors but have higher series inductances.

Unelco is a common name for these capacitors, coming in two basic physical sizes. At vhf or uhf, their real values must be adjusted according to the frequency of operation. Parasitic inductances for Unelco and Miniunelco are 1.5-2nH and 1-1.2nH respectively.

The following equation has sufficient accuracy for determining the required low frequency value when the effective value and frequency are known:


$$C_{\text{nom}} = C / (1 + ((2\pi f)^2 L C) 10^{-9})$$

where C is the effective capacitance in pF, L is the parasitic series inductance in nH and f is frequency in MHz. Assuming a capacitance of 100pF is required at 400MHz, and we wish to use a Miniunelco:

$$C_{\text{actual}} = 100 / (1 + (2512^2 \cdot 1.0 \cdot 100 \cdot 10^{-9})) = 61.3\text{pF.}$$

So the actual low frequency value of the capacitor required for a 100pF effective value is almost 40% lower. The nominal value at 150MHz would be 91.8pF (as a comparison), which is well within the standard 10% tolerance limits for these components.

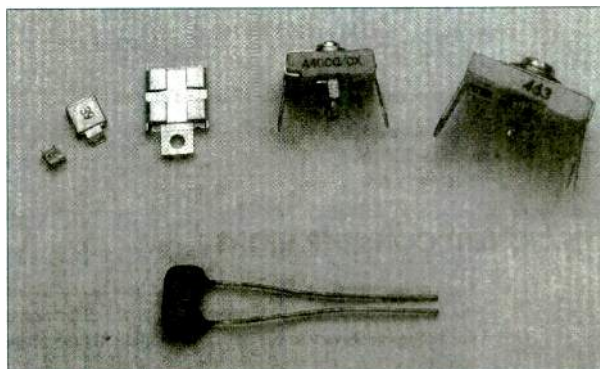Any type of capacitor's nominal value can be calculated with this equation, as long as its parasitic inductance is known.



Various types of capacitors used in rf power circuits. From left to right (upper): a multi-layer ceramic chip, Miniunelco, standard Unelco, and two types of compression mica variables. Lower centre is a dipped mica or silver mica suitable for use up to vhf with very short leads.



# M & B RADIO (LEEDS)

## THE NORTH'S LEADING USED TEST/EQUIPMENT DEALER

### SIGNAL GENERATORS

MARCONI 2018 80KHZ TO 520MHZ SYNTHESIZED	£750
MARCONI 2020 50KHZ TO 520MHZ SYNTHESIZED	£500
MARCONI 2008 10KHZ TO 520MHZ INC RF PROBE KIT	£300
MARCONI 2015/21 71 SYNCRONIZER 10MHZ TO 520MHZ	£325
MARCONI 2016 10KHZ TO 120MHZ AM FM	£195
MARCONI 2015 10MHZ TO 520MHZ AM FM	£195
ADRET 740A 100KHZ TO 1120MHZ SYNTHESIZED	£1450
HP8481D 2.3GHZ TO 13GHZ OPT001/003 SOLID STATE GENERATOR	£4750
HP3336A SYNTHESIZER/LEVEL GENERATOR	£650
HP8640A 500KHZ TO 512MHZ OPT001	£550
HP8640B 500KHZ TO 512MHZ OPT001	£550
HP8640B 500KHZ TO 512MHZ OPT004 AVIONICS VERSION	£1000
HP8620C SWEEPER MAINFRAMES (AS NEW)	£300
HP8620C/86220A RF PLUG-IN 10MHZ TO 1300MHZ	£1200
HP8620C/86290B RF PLUG-IN 2GHZ TO 18.6GHZ	£2750
HP4204A 10KHZ TO 1MHZ OSCILLATOR	£250
FARNELL S5G1000 10KHZ TO 100MHZ SYNTHESIZED (AS NEW)	£1500
FARNELL S5G2000 10KHZ TO 2000MHZ SYNTHESIZED (AS NEW)	£2250
FARNELL S5G520 10MHZ TO 520KHZ SYNTHESIZED	£400
POLRAD 1106ET 1.8GHZ TO 4.6GHZ WITH MODULATOR	£400
GIGA GR1101A 12GHZ TO 18GHZ PULSE GENERATOR (AS NEW)	£750
SAYROSA MA30 FREQUENCY OSCILLATOR 10HZ TO 0KHZ	£450
RHODE & SCHWARZ SMC1 4.8GHZ TO 12.6GHZ	£450
HP8616A 1.8GHZ TO 4.5GHZ	£295
TEKTRONIX 141A PAL TELEVISION TEST SIGNAL GENERATOR	£500
ADRET 20230A 1MHZ SYNTHESIZED SOURCE	£195
HP8672A SYNTHESIZED SIGNAL GENERATOR 2GHZ TO 18GHZ	£6200
HP3586A SELECTIVE LEVEL METER 50HZ TO 32.5MHZ	£1850
TEXSCAN VS-60C SWEEPER GENERATOR 1000MHZ	£450

### SPECTRUM ANALYSERS

B&K 2033 1HZ TO 20KHZ AUDIO ANALYSER	£2750
HP3581A WAVE ANALYSER 15HZ TO 50KHZ (AS NEW)	£850
HP3582A 0.02HZ TO 25.5KHZ DUAL CHANNEL AUDIO ANALYSER	£3000
HP8558B 10MHZ TO 1500MHZ WITH 182T MAINFRAME	£2000
HP141T 8552B/8553B 110MHZ WITH 8433A TRACKING GENERATOR	£2000
HP141T 8552A/8554B 10KHZ TO 1250MHZ (AS NEW)	£2000
HP141T 8555A/8552B 10MHZ TO 18GHZ SPECTRUM ANALYSER SUPPLIED WITH ADDITIONAL HP8553B 1KHZ TO 110MHZ RF PLUG IN	£2000
HP8444A TRACKING GENERATOR OPT058	£1500
HP8553B 1HZ TO 110MHZ LATE MODEL ANALYSER PLUG-INS	£200
WAYNE KERR RA200 FREQUENCY RESPONSE ANALYSER	£400
HP3580A 5KHZ TO 50KHZ AUDIO ANALYSER	£1500
HP3581C SELECTIVE VOLT METER 15HZ TO 50KHZ	£750
TEXSCAN ALS1 4MHZ TO 1000MHZ ANALYSER	£750
EATON 2075B NOISE GAIN ANALYSER 10MHZ TO 2GHZ	£2000

### OSCILLOSCOPES

TEKTRONIX SC504/TM503/DM501 PORTABLE 80MHZ SCOPE/DVM	£600
TEKTRONIX 475 200MHZ DUAL TRACE	£400
TEKTRONIX 465 100MHZ DUAL TRACE	£345
TEKTRONIX 465B 100MHZ OSCILLOSCOPE	£400
TEKTRONIX 466 100MHZ STORAGE	£395

### HP1722B 275MHZ MICROPROCESSOR CAL MEASUREMENTS (AS NEW)

HP1725A 275MHZ DELTA TIME AND DELAYED SWEEP (AS NEW)	£550
TEKTRONIX 7633/7A26/7A13/7B53 200MHZ 4 CHANNEL STORAGE	£600
TEKTRONIX 7603/7A26/7A29/7B53A 1GHZ OSCILLOSCOPE	£750
PHILIPS PM3217 50MHZ 2 CHANNEL DELAYED TIMEBASE	£375
IWATSUI S58122 100MHZ 2 CHANNEL CURSOR READOUT	£900
KIKUSUI C06100 100MHZ 2 CHANNEL	£500
NICOLET 4094A DIGITAL OSCILLOSCOPE (TO CLEAR)	£250
TELEQUIPMENT D34 15MHZ PORTABLE NICADS FITTED	£150
GOULD 05200 10MHZ DIGITAL STORAGE	£495
GOULD 05208 15MHZ 2 CHANNEL	£500
TEKTRONIX 7704/7A13/7A26/7B15/7B53AN 4 CHANNEL	£500
TEKTRONIX 5103N/5B10N/5A20N/5A20N OSCILLOSCOPE	£250

### TEST EQUIPMENT

EFRAIM OPT FRT ATOMIC FREQUENCY STANDARD	£2500
HP3779A PRIMARY MULTIPLEX ANALYSER	£600
HP3780A PATTERN GENERATOR/ERROR DETECTOR	£350
HP3782A DATA GENERATOR	£350
HP3468D DIGITAL MULTIMETER LED	£400
HP3466A DIGITAL MULTIMETER LED	£200
HP8750A STORAGE NORMALISER	£650
HP450A VECTOR VOLTMETER & ACCESSORIES 1000MHZ	£145
HP3400A TRUE RMS VOLTMETER ANALOGUE	£150
HP3403C TRUE RMS VOLTMETER DIGITAL	£225
HP3406A BROADBAND SAMPLING VOLTMETER	£195
HP11638A RANGE CALIBRATOR	£500
HP11667A POWER SPLITTER 18GHZ (NEW)	£85
HP10529A LOGIC COMPARATOR	£85
HP394A VARIABLE ATTENUATOR 1GHZ TO 2GHZ	£250
HP334A DISTORTION METER OPT 1HS	£450
HP3488A SWITCH CONTROL UNIT	£125
HP5382A 225MHZ FREQUENCY COUNTER	£300
MARCONI 2300B MODULATION METER 1200MHZ	£200
MARCONI 2311A DISTORTION FACTOR METER	£150
MARCONI 2432 560MHZ FREQUENCY COUNTER	£200
MARCONI 2432A 560MHZ FREQUENCY COUNTER	£65
MARCONI 2603 RF MILLIVOLT METER 1500MHZ	£95
MARCONI 2910/4 TV LINEAR DISTORTION ANALYSER	£600
HP11638A RANGE CALIBRATOR	£600
MARCONI 2914A INSERTION SIGNAL GENERATOR	£450
MARCONI 2306 PROGRAMMABLE INTERFACE UNIT	prices from £95
MARCONI 2700 LCR BRIDGE BATTERY	£225
FARNELL RB 1030/35 ELECTRONIC LOAD	£495
FARNELL TOPS 3D TRIPLE OUTPUT DIGITAL PSU	£225
FARNELL L50/500mA POWER SUPPLY	£95
FARNELL B30/5 POWER SUPPLY TO 30 VOLTS 5 AMP	£45
FARNELL B30/20 POWER SUPPLY 0-30 VOLT 20 AMP	£100
FARNELL LA520 RF AMPLIFIER 15MHZ TO 520MHZ	£155
FARNELL TMB TRUE RMS SAMPLING RF METER (AS NEW) 1 GHZ	£350
FLUKE 3330B PROG CONSTANT CURRENT/VOLTAGE CALIBRATOR	£750
FLUKE 103A FREQUENCY COMPARATOR	£295
ROTEK AC/DC PRECISION CALIBRATOR	£650
EXACT 334 PRECISION CURRENT CALIBRATOR	£195
BALLANTINE 6125C PROG TIME/AMPLITUDE TEST SET	£500
HALCYON 500B/521A UNIVERSAL CALIBRATOR	£500
AVO RM215 L/2 AC/DC BREAKDOWN/IONISATION TESTER	£300

### AILTECH 533X-11 CALIBRATOR 1 HP355C//HP355D ATTENUATORS

BIRD TENULINE 818 80W COAXIAL RESISTOR	£100
BIRD TERMINAL 818 80W COAXIAL RESISTOR	£85
NARDA 748 150W 6DB ATTENUATORS	£100
NARDA 3001-30 DIRECTIONAL COUPLER 40MHZ TO 950MHZ	£250
NARDA 3002 BI-DIRECTIONAL COUPLER 1GHZ TO 4GHZ	£65
KEMO DP1 PHASE METER 1HZ TO 100KHZ (NEW)	£150
IWATSUI SC7104 10HZ TO 1000MHZ FREQUENCY COUNTER	£325
RACAL 9009 MODULATION METER 30MHZ TO 1500MHZ	£275
RACAL 9903 50MHZ TIMER COUNTER	£95
RACAL 9904 50MHZ TIMER COUNTER	£145
RACAL 9915 10MHZ TO 500MHZ FREQUENCY COUNTER	£150
RACAL 9919 10HZ TO 1100MHZ FREQUENCY COUNTER	£300
RACAL DANA 1998 10HZ TO 1300MHZ FREQ/TIMER COUNTER	£500
RACAL DANA 9009 520MHZ MICROPROCESSING TIMER COUNTER	£250
RACAL DANA 6000 MICROPROCESSING DVM	£300
RACAL DANA 5002 WIDEBAND LEVEL METER	£700
RACAL DANA 1902 THERMAL PRINTER	£150
RACAL DANA 488 IEEE STD BUS ANALYSER	£200
RACAL DANA 9302 RF MILLIVOLT METER 10KHZ TO 1500MHZ	£400
RACAL DANA 1902 THERMAL PRINTER	£150
RACAL 9063 TWO TONE GENERATOR SYNTHESIZED	£250
WAYNE KERR CT 496 LCR BRIDGE BATTERY PORTABLE	£95
PHILIPS PM8252A DUAL PEN RECORDER	£295
DYMAR 2085 AF POWER METER	£200
TEKTRONIX 528A VIDEO WAVEFORM MONITOR	£300
TEKTRONIX 576 CURVE TRACER/72 PROG TEST FIXTURE	£650
TEKTRONIX 338 LOGIC ANALYSER 32 CHANNEL 20MHZ	£400
TEKTRONIX 318 LOGIC ANALYSER 16 CHANNEL 50MHZ	£450
SIEMENS U2231 P50PH METER (NEW)	£500
SIEMENS D2108 LEVEL METER 200HZ TO 30MHZ	£650
SIEMENS W2108 LEVEL OSCILLATOR 30MHZ	£650
WANDEL & GOLTERMAN SPM 19 LEVEL METER 50HZ TO 25MHZ	£650
WANDEL & GOLTERMAN P519 LEVEL GENERATOR 25MHZ	£200
SAYROSA AMH AUTOMATIC MODULATION METER 2GHZ	£200
BRUEL & KJOER 2425 ELECTRONIC VOLTMETER 0.5HZ TO 500KHZ	£195
DRANEZ 626A MAINS DISTURBANCE ANALYSER FITTED WITH 6036 INTERFACE/6002A DC MONITOR/6001 LINE ANALYSER/6006 AC MONITOR/6020 BROADBAND MONITOR	£1250
SCHLUMBERGER 7702 DIGITAL TRANSMISSION ANALYSER	£1250
MARCONI 6950/6910 POWER METER 10MHZ TO 20GHZ	£850
MARCONI 6593A VSWR INDICATOR	£495
HP432A/478A RF POWER METER 10MHZ TO 10GHZ	£400
HP435A/8482H RF POWER METER TO KHZ TO 42GHZ	£850
HP435B/8482H RF POWER METER 100KHZ TO 42GHZ	£850
HP435B/8481A RF POWER METER 10MHZ TO 18GHZ	£1000
HP436A DIGITAL POWER METER	£650
HP447D AMPLIFIER 0.1MHZ TO 1300MHZ	£500
HP432A CRYSTAL DETECTOR	£150
SCD RF AMPLIFIER 10MHZ TO 1000MHZ 10 WATT 46dB	£1000
BIRD COAXIAL ATTENUATOR 500W 30dB	£200

### BULK PURCHASE SPECIALS

BECKMAN DM110 DIGITAL MULTIMETERS WITH CASE/PROBES	£50
SOLARTRON 7045 HIGH SPECIFICATION BENCH DVM	£60
AVO 8 HKV MULTIMETERS	£60
BIRD 43 THRU LINE WATTMETERS	£75
SIEMENS PDRM82 PORTABLE LCD RADIATION METER (NEW)	£45
EX GERMAN ARMY PORTABLE RADIATION METERS	£35

ALL PRICES PLUS VAT AND CARRIAGE - ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY

**86 Bishopgate Street, Leeds LS1 4BB**  
**Tel: (0532) 435649 Fax: (0532) 426881**

CIRCLE NO. 111 ON REPLY CARD

## HEWLETT PACKARD Spectrum Analysers



**HP 141T / 8555A 10 MHz to 18 GHz System**  
 Complete with 8552B IF Section  
 High Sensitivity to - 125 dBm  
 Resolve to 100 Hz  
 Scan up to 8 GHz full screen £2000.00

**HP 141T / 8554B 100 KHz to 1250 MHz System**  
 Complete with 8552B IF Section  
 High Sensitivity to - 122 dBm  
 Resolve to 100 Hz £1250.00

With the purchase of any of the above systems we will supply FREE of charge one HP 8553B 1 kHz to 110 MHz RF section. Normal retail price of £350.00.

All systems covered by 30 day warranty  
 All prices plus Vat and carriage



# M & B RADIO (LEEDS)

**86 Bishopgate Street, Leeds LS1 4BB**  
**Tel: (0532) 435649 Fax: (0532) 426881**

CIRCLE NO. 112 ON REPLY CARD

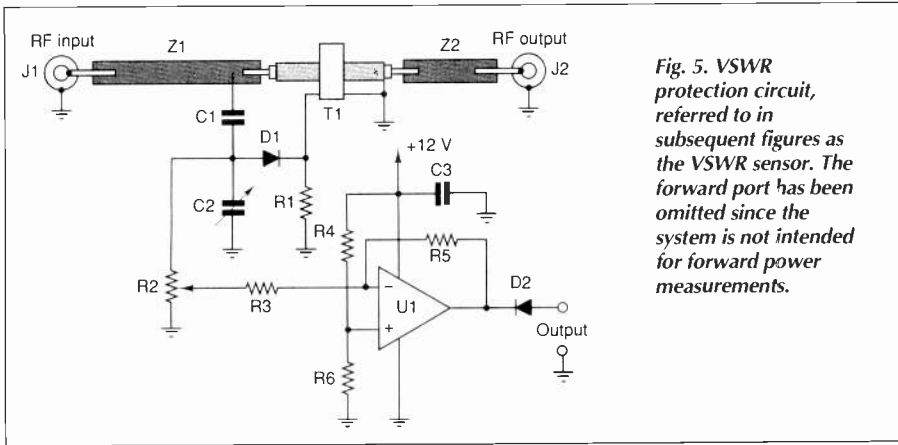


Fig. 5. VSWR protection circuit, referred to in subsequent figures as the VSWR sensor. The forward port has been omitted since the system is not intended for forward power measurements.

than 1GHz). UHF and microwave designs usually employ microstrip transmission line techniques, whereas lower frequency circuits favour lumped constant implementations.

In fact, up to uhf, the lumped constant concept is probably the most practical way to approach the coupling coefficient required between current line (amplifier output) and sample line to produce an output voltage of moderate amplitude. Passing the current line through a multi-turn pick-up coil achieves a tight coupling in a lumped constant system. The effect is of a transformer, with the current line as the primary and the multi-turn coil the secondary. The multi-turn winding is usually toroidal allowing magnetic material to be used as the core, increasing low frequency response.

Inductive reactance of the multi-turn winding must be greater than the load impedance of the current line at the lowest frequency of operation. But the ports are usually terminated into low reactance dummy loads equal to the characteristic impedance of the system – in most cases 50Ω.

High frequency limits of the vswr bridge are determined by leakage inductances and physical length of the multi-turn winding. Whenever the length of the secondary winding (sample line) equals a wavelength divided by 2<sup>n</sup>, where n is an integer 1, 2, 3, etc., there will be resonances. But their amplitudes diminish as n increases. Keeping sample line length shorter than λ/16 ensures amplitudes of any resonances are negligible.

### Bridge operating principle

Voltage across the multi-turn secondary of the transformer is proportional to the current passing through the current line and number of turns in the sample line. When the amplifier has a perfect load (at J2, Fig. 5) the rms rf voltage measured across the forward port (terminated with 50Ω) would be  $V_{rms}/R_L$  decreased by the amount of coupling ( $C_p$ ) between the current line and sample line.

Similarly, the rf voltage at the reflected port relates to the rf power reflected at the output port (J2).

If the load at the output port is totally mismatched – open or shorted – voltage at the reflected port will equal the voltage at the forward port.

To produce a useable voltage in either the forward or reflected port, coupling coefficient  $C_p$  should not be higher than 30-40dB for power levels in the main line of 100-1000W. For example, if  $C_p = 30\text{dB}$  and we have a 100W amplifier, the power appearing at the forward port of the sample line will be 100mW and the voltage will be  $(PRL)^{0.5} = (0.1 \times 50)^{0.5} = 2.24\text{V}$ .

Coupling coefficient  $C_p$  can be figured as  $C_p = 20\log[(1 + [1/(2N^2)])/(1/N)]$ . N is the number of turns in the sample line.

Reversing the equation gives  $N = 10^{C_p/20}$  where  $C_p$  is the required port coupling coefficient in dB.

Then if  $C_p = 30\text{dB}$ :  $N = 10^{30/20} = 32$  turns (for one-turn primary).

Input-output insertion loss =  $20\log[1 + (1/2N^2)] = 0.0042\text{dB}$ , and input return loss =  $20\log[2N^2 + 1] = 66\text{dB}$ .

In addition to the voltage derived from the secondary of the toroidal transformer, a voltage sample is taken from the current line using a capacitive divider ( $C_1$ - $C_2$ , Fig. 5). Half wave rectified voltages are created at the junction of  $C_1$  and  $C_2$  by the transformer secondary, 180° out of phase in the case of a non-mismatched load.

Amplitudes are made equal with  $C_2$ , reducing the voltage to near zero at the junction of  $C_1$  and  $C_2$  until a mismatch in the load causes the phase shift to deviate from 180°.

Mechanical restrictions clearly place a limit on the circuit bandwidth. Design of extremely wide-band and high power systems is difficult since, for high frequencies, the toroidal pick-up coil should be as small as possible, while low frequencies require it to be large enough for the minimum reactance required.

High permeability ( $\mu = 100$  and higher) ferrites in the toroid are usually too lossy at high frequencies and will heat up even at moderate power levels. For example, at 150MHz, materials with  $\mu = 15$  or less have been found acceptable.

A Faraday shield employed between the current line and toroidal winding, preventing capacitive coupling between the two, can best be accomplished with a length of coaxial cable of proper characteristic impedance. The inner conductor forms the current line and the outer conductor the Faraday shield.

Normally, only one end of the Faraday

shield is grounded to prevent formation of a shorted rf loop. But if the length of the Faraday shield is considerably smaller than the ground loop, it can be grounded at both ends – for mechanical reasons, for instance.

Good high frequency performance calls for a solid ground plane in the 'current line' and 'sample line' area. Otherwise the resulting ground loops may reduce the circuit frequency response or produce uneven response characteristics as a function of frequency.

### Practical circuits

The circuit shown has been tested simulating a load mismatch of 5:1 at a power level of 1kW at 30MHz, and up to 200W at 220MHz (Figs. 6 and 7).

A fast operational amplifier such as the MC34071 – 13V/μs slew rate – will allow output switching at 2ms, rapid enough to protect the majority of rf power amplifiers.

Most operational amplifiers can sink currents up to 20mA, sufficient to turn off directly the bias voltage of an enhancement mode mosfet for example; or an emitter follower can be added for higher current requirements. In fact the op-amp output can be made the main bias source to provide the mosfet gate bias voltage.

Controlling the gate voltage of a mosfet for a gradual gain reduction would not be possible in linear operation since a steady idle current has to be used. Such cases require use of some type of voltage or current controlled rf atten-

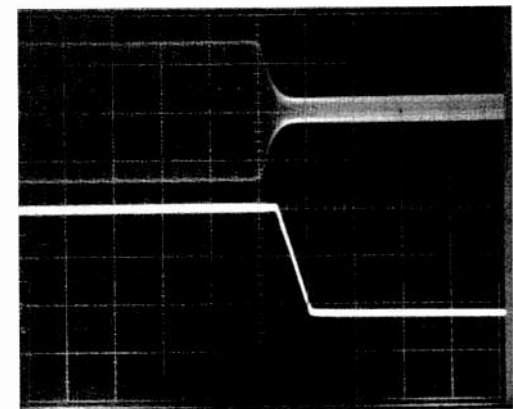


Fig. 6. RF envelope and amplifier output of vswr sensor. Horizontal scale is 2μs/div. Vertical scale is 5V/div.

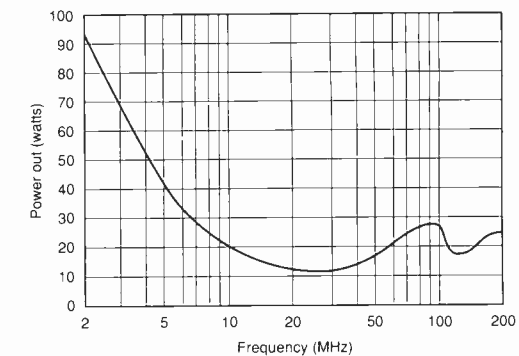


Fig. 7. Sensitivity vs frequency response of the VSWR sensor at 5:1 load mismatch.

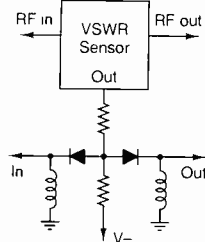


Fig. 8. A pin diode switch is used here and is adaptable with either mosfet or bjt amplifiers. A current boost for the diodes may be necessary to drive them into full conduction, depending on the type of diodes used and the signal level.

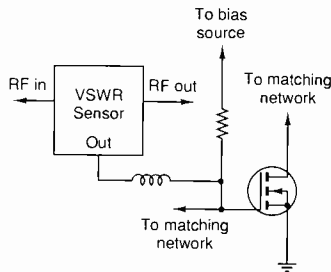


Fig. 9. Typical application for the VSWR sensor (shown in Fig. 5), where its output directly controls a mosfet gate bias voltage at a low level stage.

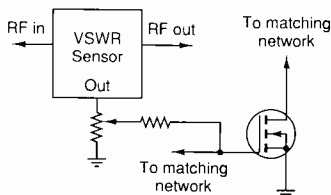


Fig. 10. Similar to Fig. 9, except that the VSWR sensor acts as the gate bias voltage source for the fet in addition to providing a shut-off function.

uator, preferably in the low level pre-stages (usually operating in class A), which are insensitive to variations in output load.

Attenuators, such as a pin diode (Fig. 8), are the only way to control the power gain of bipolar transistor amplifiers since the mosfet age function is not available.

Depending on attenuator characteristics and power level, the power output can be adjusted, for a given output mismatch, using a combination of  $R_2$  and  $R_5$  (Fig. 5). For this, and the circuit given in Fig. 10,  $D_2$  must be shorted to use the output of  $IC_1$  for a voltage pull-up function.

Fast shut down of the amplifier, without linearity requirements, can be achieved simply and adequately with the circuits given in Figs. 9 and 10. For best results, an early stage in the amplifier chain should be controlled, since low power mosfets have low gate input capacitances, speeding up shut off.

**Circuit testing**

Specific amounts of load mismatch must be developed for testing a system. For example, in some applications a fold-back may be

desired at 3:1 or 5:1 output vswr, whereas in others a load vswr of 10:1 may be tolerable.

Component losses make an infinite mismatch impossible, so a value of 30:1 has been adapted as a standard for "infinite mismatch" by the industry. The scale is logarithmic so there is not much practical difference between 30:1 (or even 20:1) and infinite.

A 30:1 mismatch covering all phase angles and  $R$  from nearly zero to open circuit can be simulated with an LC network (Fig. 11). In the diagram,  $C$  consists of two similar variable (air) capacitors whose voltage ratings depend on rf power level.  $C$  can also be a butterfly dual capacitor, where the wiper can be used for the ground contact.

Minimum-maximum capacitance ratio should be at least 5-6 to obtain a coverage for all phase angles and values of  $R$ . The initial maximum capacitance values are not critical and will only slightly affect the circuit  $Q$  and the values of  $L$ . Typical values for 30MHz are 300-400pF; for 100MHz 40-50pF; and for 200MHz 10-15pF.  $L$ s are usually air-wound inductors, physically large enough to handle rf currents at the power level in question,  $L$  values can be calculated as:

$$L_1 = 1/[(2\pi f)^2 C_{(min)}]$$

$$L_2 = 1/[(2\pi f)^2 C_{(max)}]$$

For example, if  $f$  is 100MHz,  $C_{(min)}$  is 7pF and  $C_{(max)}$  is 40pF, then:  $L_1 = 1/[628^2 \times 7] = 362nH$ ; and  $L_2 = 1/[628^2 \times 40] = 63nH$ . The same function can be accomplished with a single inductor and a differential capacitor, where one section is at its minimum capacitance while the other is at its maximum. Their capacitance ratios are roughly the same as the inductance ratios in the network previously described.

The circuit is in the familiar pi network configuration and is widely used for testing amplifier stability. 30:1 mismatch can be reduced by inserting a power attenuator between the circuit and the amplifier output through the vswr sensor.

The attenuator must, of course, be able to handle the power level in question. But remember that an attenuator only dissipates part of the power fed into it. A 1dB attenuator, for example, dissipates only 10% of the power. So one with a 100W rating could be used at a power level of 1kW, providing its resistor elements can handle the current.

Attenuation in dB to produce a specific vswr between a signal source and a 30:1 load mismatch can be calculated. First obtain a value for the magnitude of the voltage reflection coefficient ( $\Gamma$ ) as  $|\Gamma| = (VSWR-1)/(VSWR+1)$ . Then,  $RL = 10\log_{10}(1/|\Gamma|^2)$ , where  $RL$  is the return loss.

For the condition of a load return loss of 0dB (load is open or shorted), the value of attenuation in front of the open/shorted load needed to achieve a particular vswr is equal to one-half the return loss created by the desired vswr. For example, if we wish to create a 5:1 'load' vswr when the actual load is a short circuit,  $|\Gamma| = 4/6 = 0.67$ , and  $RL = 10\log_{10}[1/(0.67)^2]$

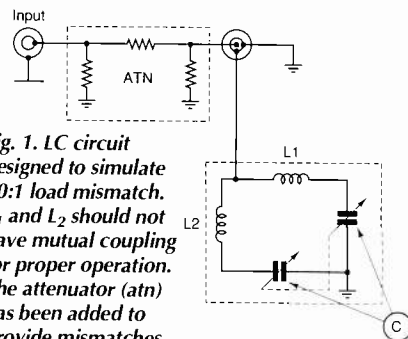


Fig. 1. LC circuit designed to simulate 30:1 load mismatch.  $L_1$  and  $L_2$  should not have mutual coupling for proper operation. The attenuator (atn) has been added to provide mismatches at various levels of swr.


= 3.5dB. Then the value of the attenuation is  $3.5dB/2 = 1.75dB$ .

The vswr simulator can be made to function over about 30% bandwidth, and with such a broad band design,  $L_1$  should be calculated for the high frequency limit and  $L_2$  for the low frequency limit. Several networks would be needed to test multi-octave bandwidth amplifiers.

An advantage of this type of set-up to create load mismatches is that it can be adjusted to any phase angle: different phase angles are needed to simulate loads in laser drivers, plasma generators, communications equipment, and certain medical instrumentation.

## Radio Frequency Transistors

*Principles and Practical Applications*

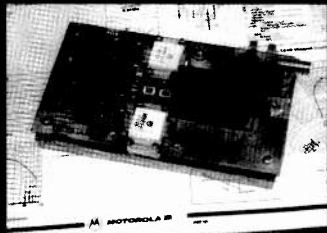

Norm Dye and Helge Granberg

Norm Dye is Motorola's product planning manager in the Semiconductor Products Sector, and Helge Granberg is Member of Technical Staff, Radio Frequency Power Group (Semiconductor Products) at Motorola. Their rf transistors book includes practical examples from the frequency spectrum from 2MHz to microwaves, with special emphasis on the uhf frequencies.

*RF Transistors: Principles and practical applications* is available by postal application to room L333 EW+WW, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Cheques made payable to Reed Books Services. Credit card orders accepted by phone (081 652 3614).

288pp HARDBACK 07506 9059 3 Cost £19.95 + Postage £2.50

**NEW LOW PRICE - NEW COLOUR**  
**HP141T**  
**SPECTRUM ANALYSERS**  
**TESTED**

- HP141T** + 8552A or B IF - 8553B RF - 1kHz - 110Mc/s - A IF £600 or B IF - £700.  
**HP141T** + 8552A or B IF - 8554B RF - 100kHz - 1250Mc/s - A IF £800 or B IF - £900.  
**HP141T** + 8552A or B IF - 8555A RF - 10Mc/s - 18GHz - A IF £1400 or B IF - £1600. The mixer in this unit costs £1000, we test every one for correct gain before despatch.  
**HP141T** + 8552A or B IF - 8556A RF - 20Hz - 300kHz - A IF £600 or B IF - £700.

**HP ANZ UNITS**  
**AVAILABLE SEPARATELY**  
**NEW COLOUR - TESTED**

- HP141T** Mainframe - £350 - 8552A IF - £200 - 8552B IF - £300 - 8553B RF - 1kHz - 110Mc/s - £200 - 8554B RF - 100kHz - 1250Mc/s - £400. 8555A RF - 10Mc/s - 18GHz - £1000. 8556A RF - 20Hz - 300kHz - £250.  
**HP8443A** Tracking Generator Counter - 100kHz - 110Mc/s - £300 - £400.  
**HP8445B** Tracking Pre-selector DC - 18GHz - £400-£600.  
**HP8444A** Tracking Generator - £750 - 1300Mc/s.  
**HP8444A** Opt 059 Tracking Generator - £1000 - 1500Mc/s.

**SPECIAL OFFER - 14 ONLY**  
**HP140T (NON-STORAGE)**

- Mainframe Plus 8552A IF Plug-In Plus 8556A RF Plug-In 20Hz - 300kHz Plus 8553B RF Plug-In 1kHz - 110Mc/s. Tested with instructions - £700.**

Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kc/s - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box  
 HP Frequency comb generator type 8406 - £400.  
 HP Vector Voltmeter type 8405A - £400 to £600 - old or new colour.  
 HP Sweep Oscillators type 8690 A & B - plug-ins from 10Mc/s to 18GHz also 18-40GHz P.O.R..  
 HP Network Analyzer type 8407A - 8412A + 8501A - 100Kc/s - 110Mc/s - £500 - £1000.  
 HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447F. 1-1300Mc/s £400.  
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.  
 HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set up - 8411a - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.  
 Racal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.  
 Racal/Dava Counters 9915M - 9916 - 9917 - 9921 - £150 to £450. Fitted FX standards.  
 Racal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.  
 Marconi RCL Bridge type TF2700 - £150.  
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.  
 Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.  
 Marconi microwave 6600A sweep osc. mainframe with 6650 PI - 18.26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.  
 Marconi distortion meter type TF2331 - £150. TF2331A - 200.  
 Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7B80 + 857B92A  
 Gould J3B test oscillator + manual - £200.  
 Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904 - 7834 - 7104 - 7623 - 7633.  
 Alltech 757 Spectrum Analyser - 001 22GHz - Digital storage + readout - £2000.  
 Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.  
 Barr & Stroud Variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.  
 Marconi TF2163S attenuator - 1GHz. £200.  
 Farnell power unit H60/50 - £400 tested. H60/25 - £250.  
 Racal/Dana 9300 RMS voltmeter - £250.  
 HP 8750A storage normalizer - £400 with lead + S.A or N.A Interface.  
 Marconi TF2330 - or TF2330A wave analysers - £100-£150.  
 Racal/Dana signal generator 9082 - 1.5-520Mc/s - £500.  
 Racal/Dana signal generator 9082H - 1.5-520Mc/s - £600.  
 Tektronix - 7514 - 7111 - 7511 - 7512 - S1 - S2 - S39 - S47 - S51 - S52 - S53.  
 Marconi mod meters type TF2304 - £250.  
 HP 5065A rubidium vapour FX standard - £2.5k.  
 Systron Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.  
 Racal/Dana 9083 signal source - two tone - £250.  
 Systron Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600  
 Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.  
 Rhodes & Schwartz power signal generator SLRD-280 - 2750Mc/s - £250-£600.  
 Ball Efratom rubidium standard PT256B-FRKL - £1000.  
 Farnell electronic load type RB1030-35 - £350.  
 Racal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.  
 HP4815A RF vector impedance meter d/w probe - £500-£600  
 Marconi TF2092 noise receiver. A, B or C plus filters.


Marconi TF2091 noise generator. A, B or C plus filters.  
 HP180TR, HP182T mainframes £300-£500.  
 Fluke 8506A thermal RMS digital multimeter. £400.  
 Philips panoramic receiver type PM790C - 1 to 20GHz - £400.  
 Marconi 6700A sweep oscillator + 6730A - 1 to 2GHz - £500.  
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k  
 Racal/Dana VLF frequency standard equipment. Tracer receiver type 90CA + difference meter type 527E + rubidium standard type 9475 - £2750.  
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz.  
 HP 432A - 435A or B - 436A - power meters + powerheads - Mc/s - 40GHz - £200-£1000  
 Bradley oscilloscope calibrator type 132 - £600.  
 Barr & Stroud variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.  
 Marconi TF2370 spectrum ANZ - 110Mc/s - £900.  
 Marconi TF2370 spectrum ANZ + TK2375 FX extender 1250Mc/s + 1st gen - £1.5k  
 HP8614A signal generator 800Mc/s - 2.4GHz, new colour £400.  
 HP8616A signal gen 1.8GHz - 4.5GHz, new colour £400.  
 HP 3325A syn function gen 20Mc/s - £1500.  
 HP 3336A or B syn level generator - £500-£600.  
 HP 3586B or C selective level meter - £750-£1000.  
 HP 3575A gain phase meter 1Hz - 13Mc/s - £400.  
 HP 8671A syn microwave 2 - 6.2GHz - £2k.  
 HP 8683D S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.  
 HP 8660 A.B.C syn S/G. AM + FM + 10Kc/s to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2500Mc/s - £750-£2800.  
 HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.  
 HP 8656A S/G AM-FM 0.1 - 990Mc/s - £1500.  
 HP 8622B Sweep PI - 01 - 2.4GHz + ATT - £1750.  
 HP 8629A Sweep PI - 2 - 18GHz - £1000.  
 HP 86290B Sweep PI - 2 - 18GHz - £1250.  
 HP 86 Series PIs in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.  
 HP 6620C Mainframe - £250. IEEE - £500.  
 HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.  
 HP 8601A Sweep generator 1 - 110Mc/s - £300.  
 HP 4261A LCR meter + 16038A test leads - £400.  
 HP 4271B LCR meter 1MHz digital meter + 16063A test adaptor - £850.  
 HP 4342A Q meter 22kHz - 70Mc/s 16462A + qty of 10 inductors - £850  
 HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.  
 HP 3561A Dynamic signal ANZ - £3k.  
 HP 8160A 50Mc/s programmable pulse generator - £1400.  
 HP 853A MF ANZ + 8558B - 0.1 - 1500Mc/s - £2500.  
 HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500  
 HP 3585A Analyser 20Hz - 40Mc/s - £4k.  
 HP 8569B Analyser 01 - 22GHz - £5k.  
 HP 3580A Analyser 5Hz - 50kHz - £1k.  
 HP 1980B Oscilloscope measurement system - £600  
 HP 3455A Digital voltmeter - £500.  
 HP 3437A System voltmeter - £300.  
 HP 3581C Selective voltmeter - £500.  
 HP 5370A Universal time interval counter - £450.  
 HP 5335A Universal counter - 200Mc/s - £500.  
 HP 5328A Universal counter - 500Mc/s - £250.  
 HP 6034A System power supply - 0 - 60V - 0 - 10 amps - £500.  
 HP 3960A 3964A Instrumentation tape recorders - £300-£500.  
 HP 5150A Thermal printer - £250.  
 HP 1645A Data error analyser - £150.  
 HP 4437A Attenuator - £150.  
 HP 3717A 70Mc/s modulator - £400.  
 HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.  
 HP 3730A - B RF down converter - P.O.R.  
 HP 3552A Transmission test set - £400.  
 HP 3763A Error detector - £500.  
 HP 3764A Digital transmission analyser - £600.  
 HP 3770A Amp delay distortion analyser - £400.  
 HP 3780A Pattern generator detector - £400.  
 HP 3781A Pattern generator - £400.  
 HP 3781B Pattern generator (bell) - £300.  
 HP 3782A Error detector - £400.  
 HP 3782B Error detector (bell) - £300.  
 HP 3785A Jitter generator + receiver.  
 HP 8006A Word generator - £100.  
 HP 8016A Word generator - £250.  
 HP 8170A Logic pattern generator - £500.  
 HP 59401A Bus system analyser - £350.  
 HP 59500A Multiprogrammer HP - IB - £300  
 Phillips PM5390 RF syn - 0.1 - 1GHz - AM + FM - £1250  
 Phillips PM5519 Colour T.V. pattern generator - £250.  
 S.A. Spectral Dynamics SD345 spectroscope 111 - LF ANZ - £2500.  
 Tektronix R7912 Transient waveform digitizer - programmable - £400  
 Tektronix 496 Analyzer 1kHz - 1.8GHz - £3.5k.  
 Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.  
 Tektronix 576 Curve tracer + adaptors - £900.  
 Tektronix 577 Curve tracer + adaptors - £900.  
 Tektronix 1502/1503 TDR cable test set - £1000.  
 Tektronix 7L5 LF analyser - 0 - 5Mc/s - £800. OPT 25 - £1000  
 Tektronix AM503 Current probe + TM501 m/frame - £1000.  
 Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.  
 Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - £250-£1000  
 Kikusui 100Mc/s Oscilloscope COS6100M - £350.  
 Farnell PSG520 Signal generator - £400.  
 Nicolet 3091 LF oscilloscope - £1000.  
 Racal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£900.  
 Tek 2415 150Mc/s oscilloscope - £1400.  
 Fluke 80K-40 High voltage probe in case - BN - £100.  
 Racal Recorders - Store 4 - 4D - 7 - 4 channels in stock - £250 - £500  
 Racal Store Horse Recorder & control - £400.  
 EIP 545 microwave 18GHz counter - £1200.  
 Fluke 510A AC ref standard - 400Hz - £200.  
 Fluke 355A DC voltage standard - £300.  
 Schlumberger 5229 Oscilloscope - 500Mc/s - £500.  
 Solartron 1170 FX response ANZ - LED display - £280.  
 Wiltron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.  
 Wiltron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.  
 Time Electronics 9814 Voltage calibrator - £750  
 Time Electronics 9811 Programmable resistance - £600.  
 Time Electronics 2004 D.C. voltage standard - £1000.  
 HP 8699P Sweep PI YIG oscillator 01 - 4GHz - £300. 8690B MF - £250.  
 Schlumberger 1250 Frequency response ANZ - £2500.  
 Dummy Loads & power att up to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex equip - relays - attenuators - switches - waveguides - Yigs - SMA - APC7 plugs - adaptors, etc  
 B&K Items in stock - ask for list.  
 W&G Items in stock - ask for list.  
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Racal etc. Ask for list.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA  
 ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANT TO TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

**Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (0274) 684007. Fax: 651 660**

CIRCLE NO. 113 ON REPLY CARD



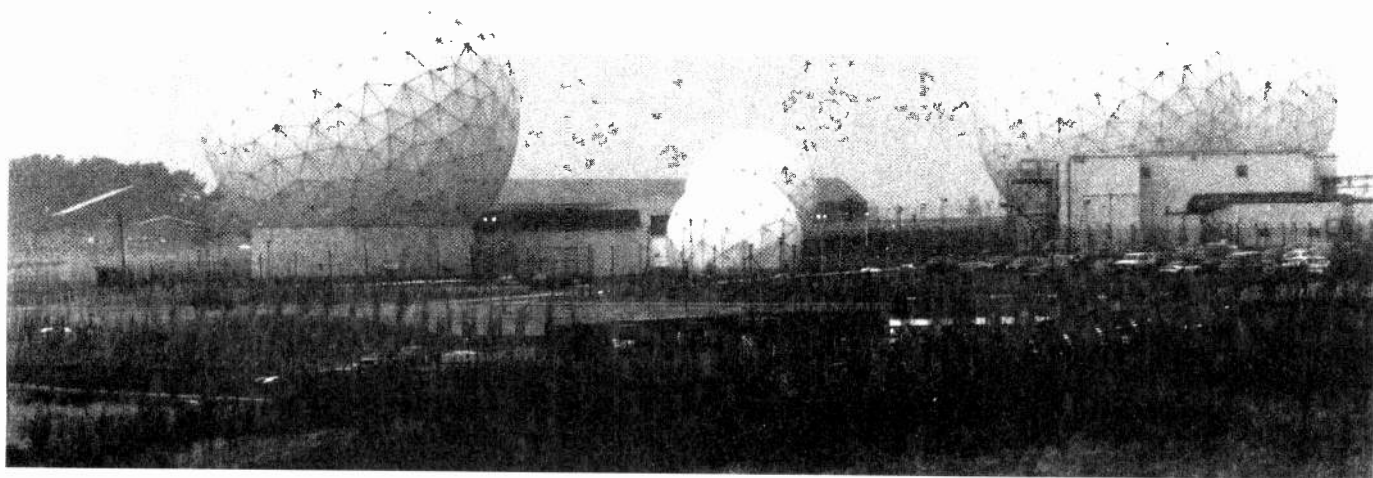

Jon Mitchell

# Big Brother's protection racket

Protecting computer data from hackers and tappers is a difficult task. But there's one method of protection that is just about unhackable and the major financial companies have been using it for years: DES encryption.

Any hacker who would tap a phone line or hack into a computer knows that it's not worth trying to unscramble information so encrypted. Algorithms like DES (the Data Encryption Standard, developed by IBM and much-used in government and financial circles) and RSA (also known as public-key encryption) are still as near to 100% secure as it is possible to get.

The beauty of DES and RSA lies in the fact that everyone knows how they work, but no one can crack them – not even government agencies. For a simple explanation of how RSA works, think of two prime numbers. Make them big ones, with at least 500 digits. Now multiply them together and you get a very large number. Now try reversing the process. Take the very large number and try to find out which two 500-digit prime numbers were used. There's only one solution (that's a feature of prime numbers) and it would take literally hundreds of years of computing power to do. Double-encryption (encrypting already-encrypted data a second time, with a different password) adds to the security.

With DES-like encryption available easily and cheaply to anyone who wants it, it was only a matter of time before criminals came to appreciate its advantages. Any drug dealer worth his salt now keeps his customer list on a PC and protects it with an encryption program. And any gang that's planning a bank job via electronic mail makes sure that all its messages are so encrypted.

Not surprisingly, governments all over the world are worried. It used to be possible for organisations like GCHQ or the NSA to tap almost any voice or data conversation and decipher the contents. Nowadays, even the most sophisticated systems can't cope with DES encrypted information.

So, in the US, the Clinton administration has come up with a plan. If the President can get the necessary legislation through Congress, further use of DES, RSA and any other encryption system within the US will be outlawed. There's even talk of Europe going down the same route.

Under the proposed new laws, if a user wants to encrypt data or voice traffic, they will have to do so with a system based on a new device called the Clipper chip. As the name suggests, Clipper is a hardware device which, according to the US government, provides totally unbreakable encryption... unbreakable that is by anyone other than the Government. It will be made available to any manufacturer wishing to incorporate encryption in their products.

So far so good. But the computing and electronics community is objecting to two aspects of Clipper. First, it's a proprietary algorithm designed by the intelligence agencies in the US. No one knows the algorithm, or anything about its functioning. Potential users are simply being asked by the National Security Agency to trust them when they say it's safe. So is it really secure? Will

someone be able to crack it? No one is telling.

The second objection is more serious, and it is all to do with Clinton's desire to stop criminals encrypting their data. Basically, there is a special password which can crack all Clipper-encrypted data. Any data whatsoever – without access to the original password used for encryption.

This "back door" key will, say Clinton's team, be held securely by the US Government and used only when a judge grants a warrant. But the mere fact that such a key exists is worrying a lot of people. What if the key should fall into the wrong hands? What if someone else manages to make their own version of the key? Can any encryption algorithm be considered secure if it's possible to crack it with a back-door key?

Even now, those who will potentially be forced to use the system are investigating possible methods of beefing up the protection. There are ways of doing this, of course, such as encrypting the data with DES before passing it through the Clipper chip. Then, even if the Clipper encryption is removed, the resulting information will still be safe. But as intentions currently stand, this process will become illegal in the US.

Many US citizens and companies are surprised that, in a country which espouses human rights, the Clinton administration is now attempting to deny the basic right of privacy.

There's much legal argument currently taking place. As yet, it's unclear whether the legislation will make it through without amendment. Most observers suspect that, if Clipper becomes mandatory, it will be in a watered-down form. Its opponents, which include many of America's largest and richest companies as well as its drug dealers, have not yet given up the fight for totally secure data.

**Robert Schifreen**

...governments  
all over the  
world are  
worried...


## Security not guaranteed

There are, of course, encryption algorithms other than DES or RSA which are less secure. Vendors of PC application software packages have been using these for a long time... For instance the encryption system which password-protects wordprocessor files. These are anything but secure. There are at least two commercial cracker products available which will break files saved with the password feature on the industry's leading wordprocessor package. One costs \$15 and takes around half a second to do its job while the other costs \$185 and takes half a minute. The delay in the second program is probably deliberate, as no one would pay \$185 for a job which

takes half a second. There is a third class of encryption algorithm: proprietary systems. They are typified by the adverts in the computer press for a certain software protection dongle. "What makes our system so secure?", asks the headline. "We'll never tell", it goes on to say. Maybe they won't, but as soon as someone finds out, or a disgruntled employee leaks the secret, the product, and everything protected with it, becomes open to the world. Contrast this with DES and RSA, whose algorithms are public and which can thus be proved to be secure.
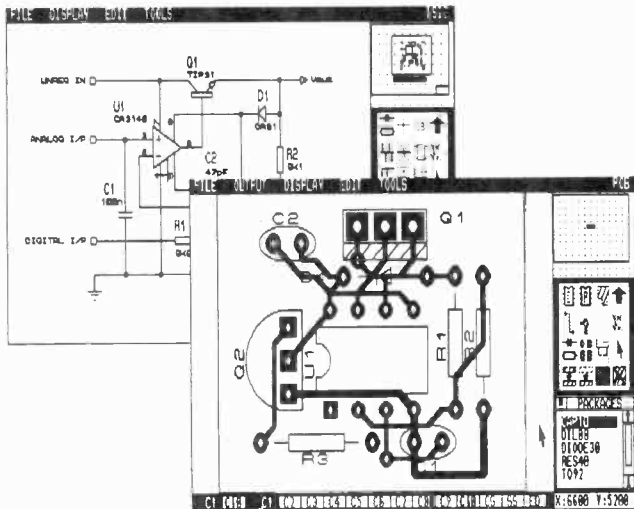
# POWERFUL SCHEMATIC CAPTURE, PCB DESIGN AND AUTOROUTING ALL FOR JUST £395...

**PROPAK AR** for DOS provides all the features you need to create complex PCB designs quickly and easily. Draw the circuit diagram using the powerful facilities of ISIS DESIGNER+ and then netlist into ARES AUTOROUTE for placement, autorouting and tidy up. Advanced real time design rule checks guarantee that the final PCB will correspond exactly with the schematic thus saving you from costly layout errors and time consuming debugging.



- Attractive, easy to use graphical interface.
- Object oriented schematic editor with automatic wire routing, dot placement and mouse driven place/edit/move/delete.
- Netlist generation for most popular CAD software.
- Bill of Materials and Electrical Rules Check reports.
- Two schemes for hierarchical design.
- Automatic component annotation and packaging.
- Comprehensive device libraries and package libraries including both through hole and SMT parts.
- User definable snap grids (imperial and metric) and Real Time Snap to deal with tricky SMT spacings.
- Manual route editing features include Auto Track Necking, Topological editing and Curved tracks.
- Autorouting for single, double and multi-layer boards.
- Non autorouting PROPAK is available for just £250 if you do not need or want the router.
- Full connectivity and design rule checking.
- Power plane generator with thermal relief necking.
- Graphics support to 300x600 Super VGA.
- Output to dot matrix and laser printers, HP and Houston plotters, Postscript devices, Gerber and Excellon NC machines plus DXF and other DTP file formats.

## CADPAK

**Two Programs for the Price of One**

### ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

**Only  
£79**

Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.


### PCB II

High performance yet easy to use manual PCB layout package. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

*Alan Chadwick writing in ETI (January 94) concluded... "At £79 I thought this was an excellent buy."*

## ISIS ILLUSTRATOR

**Schematic Drawing for Windows**

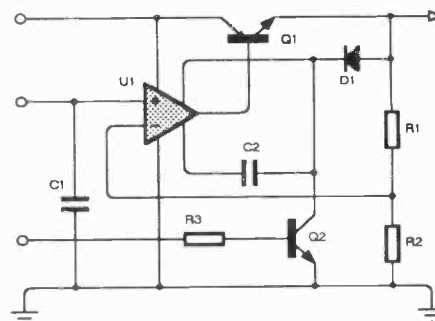


**From  
£99**

Running under Windows 3.1, ISIS ILLUSTRATOR lets you create presentation quality schematic drawings like you see in the magazines. Furthermore, when the drawing is done, transferring it to another document is just a matter of pasting it through the Clipboard.

Now used by a number of prominent technical authors to illustrate their latest books and magazine articles.

**Labcenter**  
Electronics

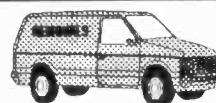

Call us today on 0756 753440 or fax 0756 752857 for a demo pack - state DOS or Windows. Multi-copy and educational discounts available.

WE HAVE MOVED - NOTE NEW ADDRESS

Prices exclude p&p (£5 for U.K.) and VAT. All manufacturers' trademarks acknowledged.


53-55 Main St, Grassington, North Yorks. BD23 5AA.

CIRCLE NO. 114 ON REPLY CARD


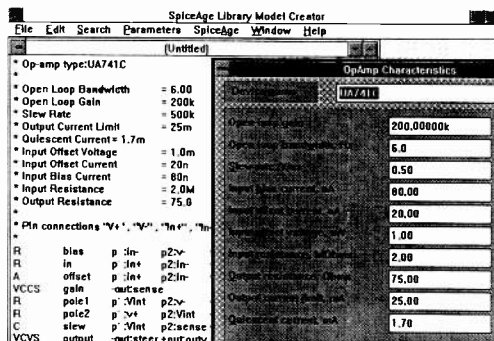
# DESIGN AND BUILD YOUR OWN OPAMP WITH OPAMP CREATOR FOR JUST £30 + VAT.

You have heard about SpiceAge for Windows being able to simulate in any manner of useful conditions in a circuit. Now with OPAMP CREATOR, you can invent or model opamps, some ideal, others with maybe large offsets and non-linearities to check how your circuit behaves. OPAMP CREATOR works via DDE with Level 3 (or higher) of SpiceAge for Windows to create a library circuit that conforms to your defining parameters. The model synthesized is usually as accurate as SPICE models (which may be used in level 7 or higher) but because it exploits SpiceAge's special polynomial pragmas to give account of non-linear behaviour, it calculates typically 5 times faster.



Do you really need such an expensive opamp or were you just lucky when it worked that once?

These are just some of the questions SpiceAge users are now finding out for themselves. For more information, contact Those Engineers, specialists in circuit simulation since 1982. Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP. Tel 081-906 0155, FAX 081-906 0969

CIRCLE NO. 115 ON REPLY CARD

## JPG Electronics

Inverter toroidal transformers 225VA 10.5-0-10.5 primary 0.260-285 secondary.....£29.95  
 LEDs 3mm or 5mm, red or green..... 6p each  
 Yellow..... 11p each  
 High intensity red, green or yellow 5mm..... 30p each  
 Cable ties, 1p each, £5.95 per 1000, £19.50 per 10,000  
 High quality photo resist copper clad epoxy glass boards  
 Dimensions single sided double sided  
 3x4 inches £1.09 £1.23  
 4x8 inches £2.75 £2.99  
 6x12 inches £6.20  
 12x12 inches £12.25  
 Rechargeable batteries  
 AA (HP7) AA 500mAh with solder tags.....£1.55  
 AA 700mAh.....£1.75 C(HP11) 1.8AH.....£2.20  
 C 2AH with solder D(HP2) 1.2 AH.....£2.60  
 £3.60 P 3 8.4V  
 D 1AH with solder 110mAh.....£1.95  
 tags.....£4.95 Sub C with solder  
 1/2 AA with solder tags.....£2.50  
 tags.....£1.95 1/3 AA with tags (Philips  
 A A A (HP16) GTV).....£1.95  
 180mAh.....£1.75  
 Standard charger charges 4 AA cells in 5 hours or  
 16 or Ds in 2-14 hours + 1xPP3 (1, 2, 3 or 4 cells  
 may be charged at a time).....£5.95  
 High power charger as above but charges the Cs and  
 Ds in 5 hours. AAs, Cs and Ds must be charged in  
 25 min. £10.95  
 Nickel Metal Hydride AA cells high capacity with no  
 memory. 1000mAh £3.85 1200mAh £4.40  
 Special offers, please check for availability  
 42 x 16mm dia 1.2v.....£1.45  
 Stick of 4 171mm 16mm dia with red & black leads  
 1.8v.....£5.95  
 Computer grade capacitors with screw terminals  
 3800uf 20v.....£2.50  
 87 0 0 0 u f 1 0 v.....£1.95 6 8 0 0 0 u f  
 15v.....£2.95 10000uf 16v.....£1.50 58000uf  
 60v.....£4.95  
 7 segment common anode led display 12mm.....£0.45  
 LM2951 AT5.0 low drop out 5v regulator 10220  
 package.....£0.85  
 7812 and 7912 12v 1A regulators.....£26.00 per 100  
 LM337K 103 case variable regulator.....£1.95 (£1.44  
 100+)  
 GaAs FET low leakage (current 58873.....£12.95 each  
 (£9.95 10+, £7.95 100+)  
 BS250 P channel mosfet.....£0.45 BC559  
 transistor.....£3.95 per 100  
 741505 hex inverter £10.00 per 100 Used 8748  
 Microcontroller.....£3.50  
 SI952 UHF Limiting amplifier LC 16 surface  
 mounting package with data sheet.....£1.95  
 A M 2 7 5 0 2.....£1.25 each 9 0 p 1 0 0 +  
 CD4007UB.....£1.00 per 100  
 100+(5p. 1000+)

Sinclair light gun terminated with a jack plug and  
 PP3 clip gives a signal when pointed at 50Hz  
 flickering light with output wave form  
 chart.....£3.95  
 DC-DC converter Reliable model V12P5 12v in 5v  
 200ma out 300v input to output Isolation with  
 data.....£4.95 each or pack of 10.....£39.50  
 Hour counter used 7 digit 240v ac 50 Hz.....£1.45  
 QWERTY keyboard 58 key good quality switches  
 new.....£5.00  
 Airpax A82903-C large stepping motor 14v 7.5 step  
 270ohm 68mm dia body 6 3mm shaft.....£8.95 or  
 £200.00 for a box of 30  
 Polyester capacitors box type 22.5mm lead pitch  
 0.9uf 250vdc 18p each 14p.....100+ 9p.....1000+  
 1uf 250Vdc..... 20p each 15p.....100+ 10p.....1000+  
 2.2uf 250vdc (27.5mm pitch)..... 30p each 20p 100+  
 15p.....1000+  
 3.3uf 100vdc..... 30p each 20p.....100+ 15p.....1000+  
 1uf 50v bipolar electrolytic axial leads..... 15p  
 each 7.5p.....1000+  
 0.22uf 250v polyester axial leads..... 15p each, 7.5p  
 100+  
 Polypropylene luf 400vdc (Wima MKP10) 27 5mm  
 pitch 32x29x17mm case 75p each 60p 100+  
 Philips 125 series solid aluminium axial leads - 33uf  
 10v & 2uf 40v..... 40p each 25p 100+  
 Philips 108 series 22uf 63v axial..... 30p each  
 15p  
 Multilayer AVX ceramic capacitors all 5mm pitch  
 100v 100pf, 150pf, 220pf, 10,000pf (10n)..... 10p  
 each 5p.....100+ 3.5p.....1000+  
 500pf compression trimmer..... 60p  
 40 uf 370vac motor start capacitor (dielectric type  
 containing no PCBs)..... £5.95 or £49.50 for 10  
 Welwyn W23 9W 120ohm..... 35p each 20p 100+  
 680 ohm 2W metal film resistor 4p 100+ 2p 1000+  
 Solid carbon resistors very low inductance ideal for  
 RF circuits - 27ohm 2W, 68ohm 2W..... 25p  
 each 15p each 100+  
 We have a range of 0.25w 0.5w 1w and 2w solid  
 carbon resistors, please send SAE for list  
 P.C. 400W PSU (Intel part 201035-001) with stan-  
 dard motherboard and 5 disk drive connectors,  
 fans and mains inlet/outlet connectors on back  
 and switch on the side (top for tower case) dims  
 212x149x149mm excluding switch. £26.00 each  
 £38.00 for 6  
 MX180 Digital multimeter 17 ranges 1000vdc  
 750vac 2Mohm 200mA transient FHe 9v and  
 1.5v battery test.....£12.95  
 AMD 27256-3 Eproms.....£2.00 each £1.25.....100+  
 DIP switch 3PC/12 pin (ERG SDC-3-023)..... 60p  
 each 40p.....100+  
 Disk drive boxes for 5.25 disk drive with room for a  
 power supply, light grey plastic,  
 67x268x247mm.....£7.95 £49.50 for 10  
 Hand held ultrasonic remote control.....£3.95  
 CV2486 gas relay, 30x10mm dia with 3 wire termi-  
 nals, will also work as a neon light..... 20p  
 each £7.50 per 100  
 A23 12v battery for car alarms or lighters..... 75p  
 each £50.00 per 100

All products advertised are new and unused unless otherwise stated.  
 Wide range of CMOS TTL 74HC 74F Linear Transistors kits. Rechargeable batteries, capacitors, tools etc  
 always in stock. Please add £1.95 towards p&p. VAT included in all prices.

JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH  
 Access/Visa (0246) 211202 Callers welcome

CIRCLE NO. 116 ON REPLY CARD

## KESTREL ELECTRONIC COMPONENTS LTD

☆ All items guaranteed to manufacturers' spec.  
 ☆ Many other items available.

'Exclusive of V.A.T. and post and package'

	1+	100+		1+	100+
<b>EPROMS</b>			<b>STATIC RAMS</b>		
2764A	2.50	2.20	62256ALP-10	3.00	2.30
27C64-150	2.30	1.90	6264ALP-10	1.85	1.40
27128A-250	2.40	2.10	6116ALP-10	1.10	0.70
27256-250	2.40	1.90	6522P	2.40	1.80
27C256-150	2.90	2.30	65C02P2	2.90	2.50
27C512-150	3.30	2.50	65C21P2	2.90	2.50
27C010-150	5.80	4.00	65C22P2	2.80	2.40
MAX232	1.35	0.95	146818AP	2.20	1.65
D8748	4.20	3.20	75176BP	1.60	0.80
D8749H	4.40	3.40	Z80A CPU	1.33	0.99
80C31-12	2.60	2.10	Z80A CTC	1.20	0.75
80C39P	2.80	2.20	Z80A DAR7	2.10	1.40
82C55-2	1.95	1.58	ULN2803A	0.70	0.46

74LS, 74HC, 74HCT Series available

Phone for full price list

All memory prices are fluctuating daily, please phone to confirm prices

178 Brighton Road,  
 Purley, Surrey CR8 4HA

Tel: 081-668 7522. Fax: 081-668 4190.

CIRCLE NO. 117 ON REPLY CARD



# Circuit capture and pcb design: a winning combination?

*The inclusion of schematic capture with PCB edit provides a powerful productivity design tool.*

*John Anderson reviews the latest addition to Tsien's Boardmaker software which adds full schematic capture.*


**B**oard Capture is the new schematic capture program from UK company Tsien. It is designed to work with Boardmaker 2.51 the latest version of the pcb design product. Last reviewed for *Electronics World* in 1991, the conclusions were that Boardmaker was slow and compromised by embedding the functionality of library editing, schematic capture and pcb edit all in notionally the same operating environment.

The requirements of the three functions are rather different and the package did not take good account of this, particularly in respect of the schematic capture. Now it has its own schematic capture program, have things improved?
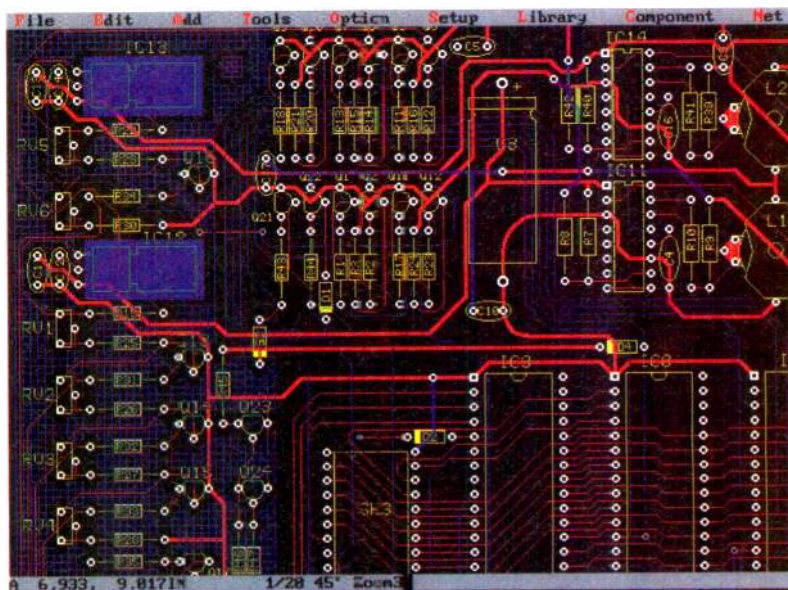
## What you get

The software is provided on both 5.25 and 3.5in media together with two professionally printed manuals and a parallel port dongle. Product support for Boardmaker and Board Capture is free for three months. Additional support is available for a further year at a cost of £60 plus VAT per product.

The installation process is straightforward with an install program moving the files onto hard disk and exhuming




Boardmaker PCB edit screen.




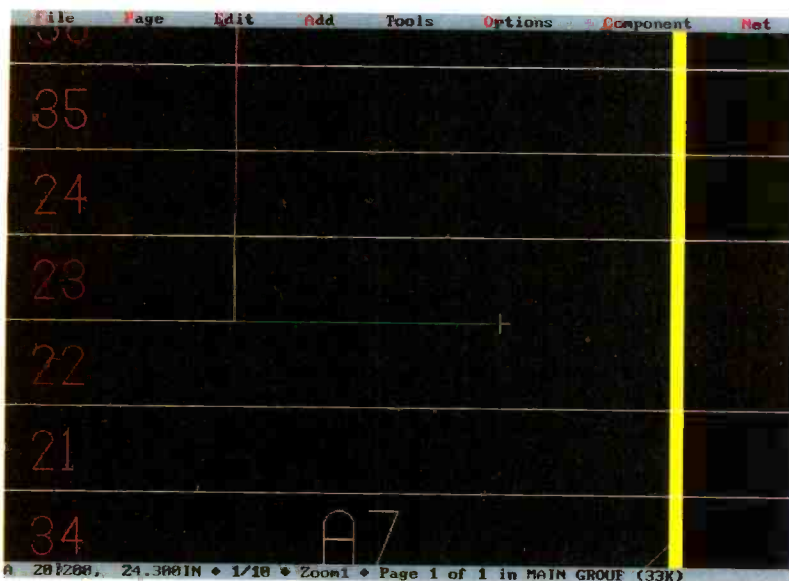File load screen - note the miniature schematic shown for the selected file.






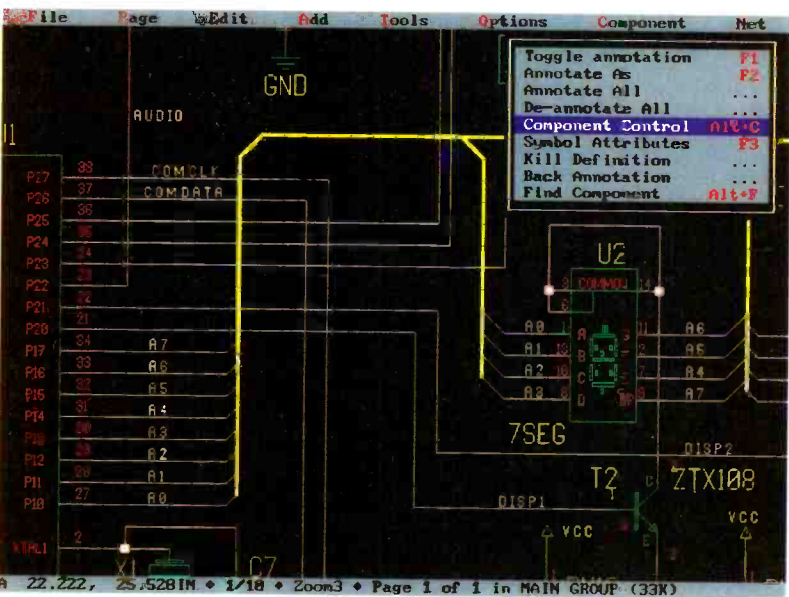Line drawing – the left mouse button starts drawing from the nearest grid position.



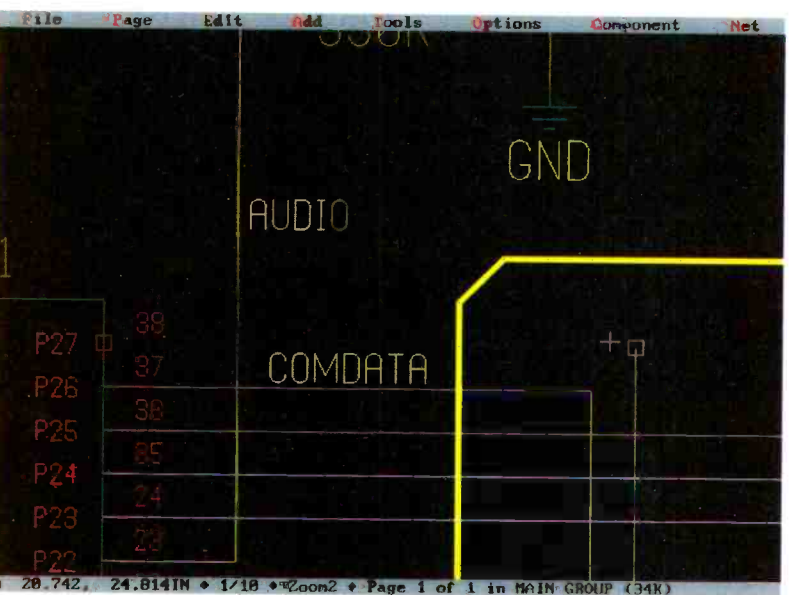Loaded file and user interface with pull down menus.



Schematic close-up. Note how unconnected nodes and wires are clearly marked with a small square.

(ugh!) the compressed files. The files, which include the libraries take about 1.5M bytes of disk space for each product. Board Capture may be configured for either standard VGA or super VGA 800x600. Many other aspects may be configured from the regularity of automatic backups to the way in which the mouse is used to pan the screen.

The Boardmaker manual is really the manual for the original Boardmaker 2 product with a few additional leaves describing the updates for versions 2.4 and 2.5. Even the discs are supplied as version 2.4 with a second disk which overwrites the data with that for version 2.5.1.

Bearing in mind that neither product has on line help, it was particularly annoying that the Board Capture manual hasn't got an index – so learning how to do something depends on remembering what you have read.

### Starting up

On starting Boardmaker, you are presented with an initial menu offering schematic, PCB or library editors. Selection of any one of these leads to an almost identical working environment of a standard banner and pull down windows, and a data line across the bottom of the screen. Access to the functions at the banner is either by clicking with the mouse or by typing control with the key letter of that menu. The schematic capture referred to in this menu is the original "pcb" version and Board Capture has to be executed separately. This software has the same simple banner and menu format.

### Board Capture

This is the new product, and although it initially looks like the old pcb version, this software offers much of what a schematic should. The zoom, pan and redraw are fast with panning occurring if the mouse is moved to the edge of the screen. The system supports a multi-page hierarchical design with a very effective simple page-up or page-down to jump between pages. There is a further level of abstraction with a tree of multiple nodes, each node may have multiple pages. It is not clear whether this system is memory or disk size limited. Thus the software could potentially handle very large designs.

The file load command menu provides a conventional file selector, but with the addition of a useful preview window which gives a (somewhat unclear) representation of the schematic.

Editing follows the normal scheme for any CAD system, with items being selected and added as required. Symbols are loaded by selecting this feature and then selecting either from the existing symbol list or a symbol from one of the libraries.

One particularly useful feature of the editor is that components are initially loaded with a small square on each unconnected node. As the connections are made, the square disappears making any misalignment of line and node obvious. Deletion is fast using the delete key, but as this is a single key press without a query delete, users must take care.

### Annotation


Annotation is rather different to any other schematic capture system. When symbols are placed on the drawing they are not annotated (i.e. R<sub>1</sub> or U<sub>9</sub>, etc.). Annotation can be added individually as the component is added. There are annotation commands which can annotate and de-annotate all the symbols on the drawing.

Boardmaker provides a component renumber function based on layout position, to aid fast component location. During this process, it creates a changes file for each component whose designator has been changed. This file may be read by Board Capture and used to back-annotate the schematic(s).



F Loading a TTL symbol.

The symbol pin editor.

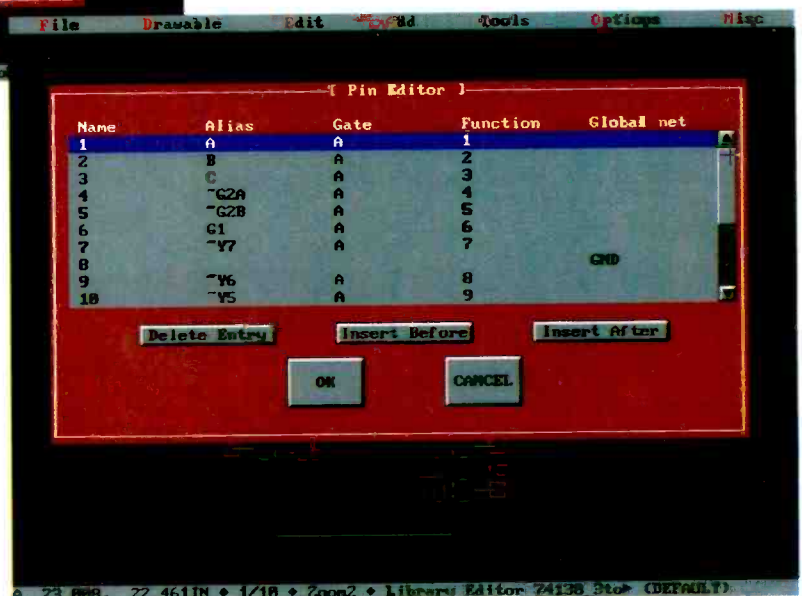

## SYSTEM REQUIREMENTS

Requires: A PC, XT or AT compatible computer  
640KB RAM, running DOS 3.0 or later.  
A parallel printer port (for the dongle)  
Graphics screen supported are: CGA, EGA, VGA and Hercules  
Options: Epson compatible printer  
Mouse  
HP LaserJet II or compatible  
HPGL plotter  
Gerber photoplotter and Excellon NC drilling supported

## PRICE

Prices (ex VAT)  
Boardmaker 2.51 £295  
Board Router 1.08 £200  
Board Capture 1.10 £395  
Extended support £60 for Boardmaker  
and £60 for Board Capture  
Carr. £5.00

## SUPPLIER DETAILS

Product: Board Capture 1.10 and BoardMaker 2.51  
Supplier: Tsien (UK) Ltd.  
Aylesby House, Wenny Road, Chatteris, Cambs.  
PE16 6UT  
Phone 0354-695959

## Library editor

A wide range of standard components are provided in a series of function divided libraries. New components may be added and new libraries created using the library editor. Symbols are created within the Board Capture program by accessing the Library Editor accessed from the file menu. The format of this editor is very similar to the Board Capture editor itself. In the same way as before, when loading a symbol, a miniature version of the component is shown in the preview window. During the symbol editing process, there is access to a separate pin editor. This allows editing of separate

records describing the pins. The pin attributes include the pin number, an alias, the gate to which it belongs, its function, global use (e.g. power supplies) and others.

## Conclusions

So have things improved for the Tsien products with the advent of the new board Capture program? I must give this a definite yes, because the system now offers a properly integrated solution from circuit to hardware. However the product still shows some problems. The Boardmaker pcb product still has vestiges of the old design methodology, which for newcomers at least will cause confusion. The annotation method is both powerful and confusing and rather different in approach to any other pcb cad systems. The speed of routing remains very slow, but in these days of 486 and beyond perhaps this is not so important.

Users these days expect on-line help and for newcomers the omission of this will slow the learning process. The Board Capture program is rich in features and has an excellent user interface. This will eventually result in the programme providing a high level of productivity.


At £395 Board Capture is not cheap, but it does represent one of the best dos based schematic capture programs. Its companion PCB editor, Boardmaker, remains in need of updating. It is however competitively priced so the combination of the two products does represent excellent value for money. ■



# PROMulators

ROM/RAM Emulators

Fast Flexible

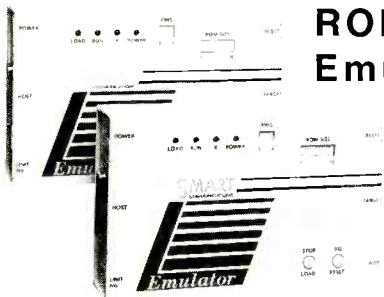

from only **£99**

- ✓ Emulate up to 4 by 8 Mbit EPROMs via one standard printer port
- ✓ Download 4 Mbit in 10 seconds
- ✓ Accepts Intel Hex, Motorola S-Records and Binary files
- ✓ Emulates 24, 28, 32, 40 and 42 pin devices
- ✓ Full screen editor
- ✓ Bi-directional communications between your target board and the PC

CALL FOR FULL DATA SHEETS

Tel: 081-441 3890  
Fax: 081-441 1843

**SMART**  
COMMUNICATIONS

CIRCLE NO. 118 ON REPLY CARD

## SYSTEM 200 DEVICE PROGRAMMER



**SYSTEM:** Programs 24, 28, 32 pin EPROMS, EEPROMS, FLASH and Emulators as standard, quickly, reliably and at low cost.

Expandable to cover virtually any programmable part including serial EEPROMs, PALs, GALs, EPLDs and microcontrollers, in many different packages.

**DESIGN:** Not a plug in card but connecting to the PC serial or parallel port; it comes complete with powerful yet easy to control software, cable and manual.

**SUPPORT:** UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.

**ASK FOR FREE INFORMATION PACK**



MQP ELECTRONICS Ltd.  
Park Road Centre  
Malmesbury, Wiltshire. SN16 0BX. UK  
TEL. 0666 825146 FAX. 0666 825141

IRELAND 1-2800395  
GERMANY 089/4602071  
NORWAY 0702-17890  
ITALY 02 92 10 35 54  
FRANCE 1 69 30 13 79  
SWEDEN 08 590 32185  
Also from ELECTROSPEED UK

CIRCLE NO. 119 ON REPLY CARD

## Field Electric Ltd.

Tel: 0438-353781 Fax: 0438 359397

Mobile: 0836-640328/0860-213370

Unit 2, Marymead Workshops,  
Willows Link, Stevenage, Herts, SG2 8AB.

- 1 44Mb Laptop floppy disk drives new £16 C/P £3
- 16 bit Ram cards with Ram from £25 C/P £3
- 72 pin Simms for PS2 Compaq Dell etc
- Parallel & Serial data switches up to 8 ways - Ring for details
- Compaq enhanced at keyboards (no cable) £11 C/P £5
- 4Mb Sipp Mother board with various chips £19 C/P £6
- MC68451L10: MC68010FN10: SRM2264C12 etc. £60 C/P £6
- PC power supplies up to 600w. in stock - Prices start from £12.00 C/P £3
- IBM 3363 optical disk drive £100 C/P £20
- 102 key AT enhanced keyboard with PS2 type plug £13.95 PS2 to 5 pin Din adpt-plug £3.25 C/P £3.50
- Toshiba external 5.25" F.D. drive PA7225E new and boxed £45 C/P £7.50
- TEAC 5.25" BBC compatible F.D. drives 360K/720K refurbis £8.95 C/P £3.75
- 16 bit hard disk/F. disk controller card £12.00 C/P £3
- SCSI hard disk drive's new CDC 344Mb £350.00 C/P £10.00
- New and boxed 286/16 Motherboards, on board, hard and floppy cont. serial/para ports on board VGA etc. takes Simms £21.00 C/P £4.00
- Yuasa maintenance-free rechargeable battery NP7-12 12v 7.0Ah £12 C/P £4.50
- Rose die-cast box 17.5x5.6x7.8 new £4.25 C/P £1.80
- Sony 7" colour monitor KTX-9000UB 240vAC input with manual, inbuilt modem, needs to be converted to RGB etc £85 C/P £16.00

### TEST AND MEASUREMENT EQUIPMENT

- Sorensen SRL 40-12 0-40 VDC 0-12A metered 115 VAC input £125
- Marconi TF 124SA circuit magnification meter £60
- KSM SC1-200 15 power supply 0-200V 0-15A £200
- HML 411 high voltage 0-20kV gap charger new £120
- Lambda LK 342A FMV 0-36v 5.2A £50
- AVO RM 215F3 AC Breakdown Tester £95
- Schlumberger 4000 Precision Sig. Gen. £150
- Schlumberger 4900 RF-AF Measuring Unit £150
- Wyse 60A Terminals new & boxed with keyboards £195
- Datatruck 7 short haul multiplexer £50
- HP 2671A Printer £125
- Fluke 335A DC voltage standard: differential voltmeter: null detector £350
- Marconi TF 2330 wave analyzer £70
- Marconi TF 2600 valve volt meter £35
- Marconi TF 2904 colour gain and delay test set £50
- Marconi TF 2600A video voltmeter £50
- Farnell B30/20 0-30VDC @ 20A £117
- AEI Gauss meter FB22 form with probe £217
- HP 432A Power meter and cable £120
- FMI Rotary attenuator 27/11 POA
- HP Frequency meter X532B POA
- HP 1740A 100MHz oscilloscope. Dual CHN with 3rd CHN, trigger view etc £325
- AS Elitek switch mode variable PSU 250vAC input. 0-60vDC 25A max metered 17x12 5x5" with manual £325
- HP 8170A logic pattern gen £120
- HP 9872c plotter £175

All above equipment + 17.5% VAT - Please ring for c/p prices



We would like the opportunity to tender for surplus equipment  
Official orders, credit card telephone orders accepted with  
Access, Amex, Diners, Visa cards. Overseas enquiries welcome  
c/p rates UK mainland only. Please ring for c/p rates not shown  
All prices inc VAT unless stated. Stock list available

CIRCLE NO. 120 ON REPLY CARD

## THE DEFINITIVE 'OFF-AIR' FREQUENCY STANDARD



Still Only  
**£195** + VAT  
carriage extra

- \* Provides 10MHz, 5MHz & 1MHz
- \* Use it for calibrating equipment that relies on quartz crystals. TCXOs, VXCOS, oven crystals
- \* Phase locks to DROITWICH (rubidium controlled and traceable to NPL) and traceable to OP - French eq to NPL)
- \* For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP - French eq to NPL)
- \* British designed and British manufactured
- \* Sine wave option of 10, 5 & 1MHz. Nominal 1V into 50Ω
- \* 13MHz option for G.S.M.

Output frequencies -  
10MHz, 5MHz, 1MHz  
Short term stability - better than 1x10<sup>-8</sup> (1 sec)  
Typical - 4x10<sup>-9</sup> (1 sec)  
Long term - tends to 2x10<sup>-12</sup> (1000 sec)

IDEAL BEGINNERS SCOPE, SCOPEX 436 AQUILASCOPE 6MHz SINGLE TRACE, INT/EXT TRIG, TRACE LOCATE, BRIGHT LINE AUTO, 10mV SENSITIVITY, 1µs-100ms/cm, etc. £95

- |   |   |
|---|---|
| QUAD 303 STEREO POWER AMPS £95                            | LEADER LCG396 MTSC COL. PATT. GEN £395        |
| DRAKE MN2700 MATCHING NETWORK & PS7 PSU POA               | UD10206 SONAR SCANNER, SURFACE UNIT £975      |
| PHILIPS PM3065 100MHz DUAL TRACE & T/B £750               | 7SEG 12x9 DISPLAYS DIGITEX/SIGNALX £15 & £10  |
| PLESSEY TCT10 SIG GEN ANAL 50-300 BDS £95                 | RADIOMETER BK6F DIST. METER 20Hz-20KHz £POA   |
| LEADER LBO3C ALIGNMENT SCOPE FROM £195                    | C10H CX6000 6-PEN A4 PLOTTER, CENT/RS232 £135 |
| TELEQUIPMENT D67A 10MHz DUAL TRACE £175                   | BACHARACH MV2 MERCURY SNIFFERS £69            |
| IWATSU SS5116 DUAL TRACE 10MHz £295                       | FISONS FJ MONITORS LIO LEVEL SENSORS £85      |
| TELEQUIPMENT D1011 10MHz DUAL TRACE £165                  | COMMODORE PETS, D, DRIVES, PRINTERS £29.99    |
| IWATSU SS-5802 DIGITAL STORAGE £249                       | INTRON IFG422 FUNC GEN 0.1Hz-2MHz £125        |
| TEKTRONIX 2215 60MHz DUAL TRACE DEL T/B £450              | COMARC 2303 MV SOURCES, DUAL RANGE £49        |
| TEKTRONIX 453A 50MHz DUAL TRACE DEL T/B £249              | INTRON IFG422 FUNC GEN 0.1Hz-2MHz £125        |
| H.P. 8405A VECTOR V/METER 1GHz £395                       | GOULD 2400 4-PEN CHART RECORDER £149          |
| H.P. 8405A VECTOR V/METER 1GHz £215                       | X-Y RECORDERS A3 & A4 FROM £35 TO £139        |
| HITACHI VC 6015 10MHz DIGITAL STORAGE £295                | PHILIPS PM4556 FM STEREO GENERATOR £175       |
| HP1340A X-Y DISPLAYS £149                                 | MARCONI TF2300 FM/AM MODULATION METER £195    |
| OEPLING V20 SINGLE PAN BAL 0.1mg/200g £69                 | MCKENZIE 7DAY TEMP/HUMIDITY RECORDER £95      |
| ANALYTICAL BALANCES WITH WEIGHTS 250g £125 & £149         | VACUUM PUMPS 1.5 & 2.8m <sup>3</sup> /hr £195 |
| FARNELL E350 PSU S 0-350V 100mA 2 x 6.3V £59 to £69       | COMMUNICATIONS RECEIVERS, HF, LF, VHF £79     |
| KINGSHILL NS1540 15V 40A PSU, CASED, AS NEW £195          | LCR BRIDGE WAYNE KERR CT492 £195              |
| ACRON 405P SYNCHRONISING PULSE GEN & 605P £375ea. £695/pr | LCRO BRIDGE AVO B151 £195                     |
| MARCONI TF2330 WAVE ANALYSER 20Hz-50KHz £149              | LCR BRIDGE MARCONI TF2700 £195                |
| H.P. S315A 1GHz F/CTR, OPTS 1, 2, & 3 £595                | LCR BRIDGE MARCONI TF2701 £125                |
| LEVELL TM68 MICRO V-METER 450MHz £95                      | LCR MARCONI TF1313 0.25% £95                  |
| LEVELL TM38 MICRO V-METER 3MHz £85                        | LCR COMPONENT COMPARATOR AVO C2457/S £95      |

LIST AVAILABLE BUT 1000'S OF UNLISTED BARGAINS FOR CALLERS. ALL PRICES EXC. OF P&P AND VAT  
QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED

**HALCYON ELECTRONICS**  
423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR  
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383. FAX 081-542 0340

CIRCLE NO. 121 ON REPLY CARD

# Maths functionality for maths-phobics

*Mathematical analysis can give valuable insight at the initial circuit design stage. Lionel Snell reports on how Mathematica and Nodal can give engineers the power of maths without the pain.*

**M**athematica from Wolfram Research and Macallan Consulting's *Nodal* could be just what is needed to put mathematical analysis at the fingertips of every engineer.

Wolfram describes *Mathematica* as "a system for doing mathematics". That makes it very much more than a system for doing calculations, because it can manipulate equations and formulas containing variables like  $x$  and  $y$  even before specific values have been assigned to those variables.

As with most computer applications, the package does require a special language to be learnt for input and output. But every effort has been made to ensure the language follows familiar mathematical notation. It has simply been designed to get round the problems of inputting mathematical symbols via a standard computer keyboard which does not allow for superscripts, subscripts and other maths symbols.

For example,  $\int x^2 \sin^2 x dx$  would be input as:

```
Integrate[x^2 Sin[x]^2, x]
```

and would result in the output:

$$\frac{4x^3 - 6x \cos[2x] + 3\sin[2x] - 6x^2 \sin[2x]}{24}$$

The straightforward language soon becomes second nature and can be used to find roots, solve simultaneous equations, manipulate polynomials and matrices, invert functions and perform many other operations – as well as process numerical values. What is more, new rules or notations can be defined by the user and consistently applied – a flexibility that has allowed third parties to provide specialist packages, such as *Nodal*, to extend the power of *Mathematica* into practical applications.

Graphical output can be particularly useful for engineering applications. Compare, for example, the transfer function in **Fig. 1** with its 3-d graph which shows how the function ( $tf$ ) blows up for certain values of  $s$  and  $\omega$ . The graph gives an immediate visual image of performance and offers far greater insight.

Extensive plotting functions, in two or three dimensions, also include specific engineering forms such as the Smith chart for relating reflection to impedance.

## **Nodal electronic Interface**

*Mathematica* is a mathematics tool: input equations and


## Do engineers need maths?

A senior engineer I knew in the early 70s used to throw scorn on academic qualifications, insisting that no amount of mathematical training could replace years of experience. He had a reputation for being able to "read" a complex circuit diagram the way experienced musicians can read a score: he could predict its performance and see weak points in design that would be confirmed when it was built and tested.

Yet anyone with a couple of years of A-level maths and physics could have written down the relevant equations and would eventually have reached many of the same conclusions. They would have demonstrated at least half as much insight as all the engineer's years of experience, but would also have actual figures to quantify their conclusions.

His attitude was not untypical in the years when computers were first appearing in R&D departments, and apprenticeship schemes were giving way to more academic training.

But even now, people who opt for engineering as a career are attracted by practical work with tangible end products. Such engineers often have far less interest in the abstract processes of mathematics.

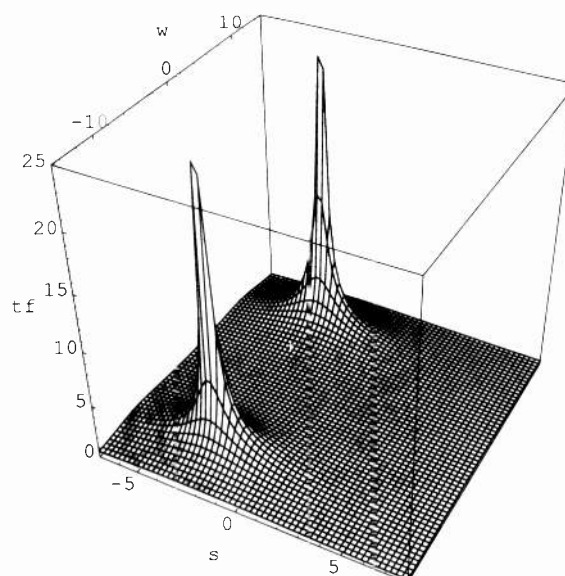

**Fig 1.** 3-D plot of the s-domain transfer function  $tf = (1 + (s/w)2 + s/qw0) - 1$  for values of  $s$  from  $-5$  to  $+5$  and  $w$  from  $0$  to  $15$ . Just one of many different ways that *Mathematica* can create immediate visual images of system performance – in this case showing the poles where the function 'blows up'.

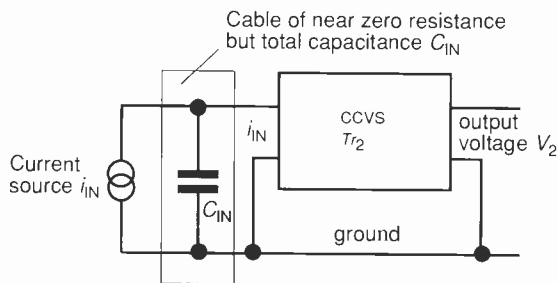


Fig 2. Simple circuit containing a current controlled voltage source. This can be used to model current differencing (Norton) and charge-sensitive amplifiers using Mathematica.

formulas and it returns solutions, graphs or numerical answers. But the user must give it the necessary equations in the first place.

*Nodal* extends the software into the world of electronic circuits, so that actual circuit descriptions can be entered, causing immediate generation of formulas for manipulation via *Mathematica*.

The two packages are seamlessly integrated so that *Nodal* appears as an extra set of commands within the main program. *Nodal*'s commands amount to a special language formulated to allow two- or three-dimensional circuits to be described through the keyboard. Again, it is logical, based on clearly understandable terminology, and describes any circuit in terms of a number of "nodes" separated by various electrical components.

In Fig. 2, for example, there are just three nodes in this sense. All the junctions along the bottom are directly connected and so count as a single node. Between nodes 0 and 1 there are two parallel components, a current source ( $i_{IN}$ ) and a capacitor ( $c_{IN}$ ). There is also a "current controlled voltage source" used here to model a charge sensitive amplifier – it has four connections to nodes 1, 2 and twice to 0.

Giving the circuit the name *chAmp*, it is defined as:

```
chAmp = NodalNetwork[Current
Source[{1,0},iIN],
Capacitor[{1,0},cIN],
CCVS[{1,0,0,2}],tr2]
```

Let us say we want to know the output voltage, that is voltage at node 2 ( $V_2$  in *Nodal*-speak). The basic command is:

```
NodalAnalyze[chAmp,Result->V2]
```

Remembering that Americans write analyse with a z is the only demanding part. The actual response to this command would be a somewhat untidy first draft formula. But it can be cleaned up with *Mathematica*'s *simplify* command. In practice the two stages are easily combined as:

```
Simplify[NodalAnalyze[chAmp,Result->V2]]
```

resulting in:

```
iIN tr2
```

revealing that output is independent of capacitance.

**Practical application**

If you need to connect a current source – an avalanche diode detector maybe – to an amplifier, how critical is the connecting cable capacitance?

The last example modelled the situation for a cable of negligible resistance but total capacitance  $c_{IN}$ . It showed that output voltage was unaffected by the capacitance.

Replacing the current controlled amplifier by a voltage controlled one defines a new circuit we will call *vAmp*. The input simply replaces the CCVS with a VCVS as follows

```
vAmp=NodalNetwork[CurrentSource[{1,0},iIN],
Capacitor[{1,0},cIN],
VCVS[{1,0,0,2}],gain]]
Simplify[NodalAnalyze[vAmp,Result->V2]]
```

giving

```
-I
--- gain
2
-----
Pi cIN f
```

**Mathematical insight**

Circuit modelling software such as *Spice* plays an important role in electronics development, because it allows circuit prototypes to be simulated on a computer. So the performance of various designs can be evaluated quickly and accurately before a single wire has been connected.

The drawback is that this easy trial and error development is at the expense of "insightful" development which takes a more direct route to an optimal solution.

Cad software based on *Mathematica* allows symbolic manipulation of models, leading directly to better design by reinforcing the engineer's intuitive understanding of circuit behaviour.

*Mathematica* can help engineers at several levels.

Firstly, it performs mathematical manipulation.

What is the point in writing down equations based on Kirchhoff's Laws if you don't trust yourself to solve them or draw a graph of performance without making mistakes? This basic lack of confidence in one's own maths undermines any amount of engineering education. Given simple commands *Mathematica* solves equations, plots graphs, simplifies complex formulas and provides a host of features such as Fourier and Laplace domain analysis. Even the most accomplished

mathematician would be glad to hand over such spade-work to a computer not prone to human error. For the engineer it frees the mind to concentrate on actual design principles.

Secondly, *Mathematica* can analyse a real life situation mathematically.

Writing down the initial equations may be just a process of following simple rules, but it becomes a challenge in more complex or unfamiliar cases. Although the software was originally designed purely as a mathematical tool, it has earned such a following that packages are now being created to apply this engine to a host of practical applications. In the case of electronic engineering, *Nodal* allows the engineer to type in a simple circuit description and the relevant equations are instantly generated in *Mathematica* form.

Thirdly, working with *Mathematica* is an education in itself. The creativity required for pure maths research is a rare ability not directly relevant to engineering. All the same, practical experience with *Mathematica* does encourage latent mathematical skills and understanding that can lead in the longer term towards more confident research and development.



where  $I$  is the square root of  $-1$ ,  $\pi$  is  $\pi$  and  $f$  is frequency.

Here cable capacitance does affect the result. Whether this is serious or not can be readily understood by graphing for appropriate values. Options include a simple plot of output voltage against capacitance at a given frequency; or a 3-d plot of output voltage against frequency and cable capacitance; or a contour plot. For example, the commands:

```
Plot3D[output /. {gain->100, iIN-> pA, f->10^x, cIN->y pF}
  {x,0,9},{y,1,1000},
  AxesLabel->{"log(f)", "
  c(pF)", "log(output)"},
  PlotRange->All]
```

define a 3-d graph between chosen values (Fig. 3) giving an immediate visual grasp of the situation.

The example is very simple, and a more complex problem would take longer to input. But the saving in manual calculation and mathematics skills would be all the greater – without the risk of human error in calculation.

Graph the result, and the engineer immediately gets the full picture for informed design decisions.

### Scope of Mathematica and Nodal

*Mathematica* itself is a well established mathematical toolkit, and at the time of writing the *Nodal* electronic application package costs around £310 + VAT. Version 2 contains about thirty component descriptions for analogue circuits handling anything from audio to microwave frequencies.

Updates are promised which will include allowance for thermal effects as the temperature of the circuit alters. There is also talk of "mechanical" additions to take into account the mechanical properties of, say, a gramophone pick-up (it is already possible to define certain components in geometric terms, eg capacitance by gap width and plate overlap).

What cannot be handled is non-linear effects or digital circuits. Of course, these are included in the full version of *Spice*, but there is little competition between these two.

*Spice* is designed to model the most complex circuits at

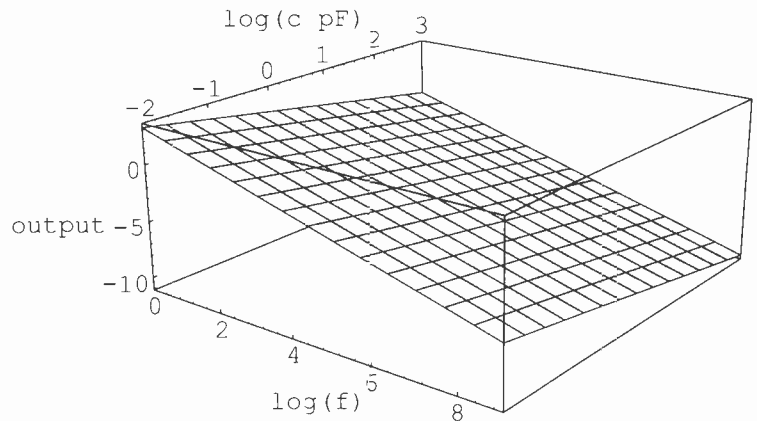


Fig 3. 3-d plot showing effect of replacing the charge sensitive amplifier in Fig. 2 with a voltage amplifier. The output is now seen to be dependent upon the cable capacitance and the frequency.

the prototype stage when all the numerical values are known. It can provide accurate performance figures and even quantify the circuit sensitivity around those values.

What *Spice* does not do is provide the symbolic description of overall performance provided by *Mathematica* at a fraction of the cost of the full *Spice* package.

One limitation, is that the output equations are rather clumsy. The input language for *Mathematica* is restricted by the need to enter mathematical symbols on a standard keyboard. For output there is a little more choice of formats. But there is nothing like the clear mathematical output available from a dtp system. As a working tool for design engineering, this is no problem, though it could become tiresome when being used in the preparation of design reports. Proper mathematical typesetting would be welcome.

### Unique flexibility

Symbolic analysis of circuits balances the "try it and see" approach by developing insight at the early design stage. Until now this has required mathematical confidence, if not actual skill. But *Mathematica* undoubtedly provides an easy and attractive alternative.

No other system to my knowledge offers anything like the same flexibility for electronic design support – even the *Mathcad* electronics support package is little more than a collection of useful formulas or example circuits.

If there is any other software offering this sort of support to the electronic designer, I would like to find it. ■

## Supplier details

### Mathematica

Mac: Student version £149; standard version (no coprocessor) £375; Enhanced version (needs 68020 or higher and uses coprocessor) £575.

Windows: Student £149; Standard (386 or higher, no coprocessor) £375; Enhanced (coprocessor) £645.

dos: Student £149; Standard £375; Enhanced £575.

Available from Wolfram Research Europe Ltd, Long Hanborough, Oxon OX8 2LA. Tel: 0993 883400 Tel: 0993 883800

### Nodal

£310 + £6 p&p + £55.30 VAT available from Goth, Goth & Chandleri Ltd, 36 Victoria Park, Cambridge CB4 3EL. Tel 0223 321748 Fax: 0223 323804. More information from Macallan Consulting, Tel: 010 1 408 262 3575.


## System requirements

Dos 3.0 or later  
Can use coprocessor  
4Mbyte extended ram  
386 or higher  
CGA/EGA/VGA display  
Most printers supported

"... there is no doubt that running under *Windows* puts it ahead of the field and makes it a visually attractive package." *Electronics World + Wireless World July 1993*

*High Quality PCB and Schematic Design for Windows 3/3.1 and DOS*

- Supports over 150 printers/plotters including 9 or 24 pin dot-matrix, DeskJet, LaserJet, Postscript, and HPGL. Professional Edition imports GERBER files, and exports GERBER and NC-DRILL files.
- Up to 200,000 pads/track nodes depending on memory. Simple auto-router and schematic capture tools with SPICE compatible net-list output.
- Low cost DOS version (reduced features) also available. Ring for full details!

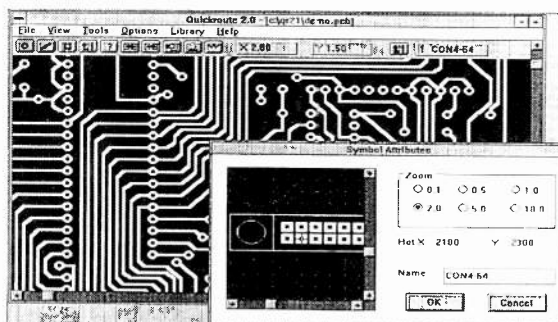

"Quickroute provides a comprehensive and effective introduction to PCB design which is a pleasure to use" *Radio Communication May 1993.*

# Quickroute



POWERware, Dept EW, 14 Ley Lane, Marple Bridge, Stockport, SK6 5DD, UK.  
Ring us on 061 449 7101 or write, for a full information pack.

Quickroute is available for Windows 3/3.1 in Professional (£99.00) and Standard (£59.00) editions, and for DOS with reduced features (£49.00). All prices inclusive. Add £5 P+P outside UK.

from  
**£49**

CIRCLE NO. 122 ON REPLY CARD

PCB & SCHEMATIC CAD	DIGITAL SIMULATION	ANALOGUE SIMULATION	SMITH CHART CAD
EASY-PC <b>£98</b>	PULSAR <b>£98</b>	ANALYSER III <b>£98</b>	Z-MATCH II <b>£195</b>
<ul style="list-style-type: none"> <li>● Design Single sided, Double sided and Multilayer boards.</li> <li>● One software package for Schematics and PCB's.</li> <li>● Standard output includes Dot Matrix / Laser / Inkjet printers, Pen Plotters, Photo-plotters and NC Drill.</li> <li>● Award Winning EASY-PC is in use in over 18,000 installations in 80 Countries World-Wide.</li> <li>● Runs on PC/XT/AT/286/386 with Herc, CGA, EGA, VGA.</li> <li>● Optional libraries S.M. Components etc. From £38.00</li> </ul>	<ul style="list-style-type: none"> <li>● At last! A full featured Digital Circuit Simulator for less than £1000!</li> <li>● Pulsar allows you to test your logic designs without the need for expensive test equipment.</li> <li>● Catch glitches down to a pico-second per week!</li> <li>● Includes 4000 Series CMOS and 74LS Libraries.</li> <li>● Runs on PC/XT/AT/286/386/486 with EGA or VGA. Hard disk recommended.</li> <li>● 74HC / HCT Libraries optional at £48.00 each.</li> </ul>	<ul style="list-style-type: none"> <li>● NEW powerful ANALYSER III has full graphical output.</li> <li>● Handles R's, L's, C's, Bipolar Transistors, FET's, Op-Amp's, Tapped and Untapped Transformers, and Microstrip and Co-axial Transmission Lines.</li> <li>● Plots Input and Output Impedances, Gain, Phase and Group Delay.</li> <li>● Covers 0.001 Hz to &gt;10GHz</li> <li>● Runs on PC/XT/AT/286/386/486 with EGA or VGA displays.</li> <li>● Very fast computation.</li> </ul>	<ul style="list-style-type: none"> <li>● Z-MATCH II takes the drudgery out of RF matching problems and includes many more features than the standard Smith Chart.</li> <li>● Provides quick accurate solutions to many matching problems using transmission line transformers, stubs, discrete components etc.etc..</li> <li>● Supplied with comprehensive user instructions including many worked examples.</li> <li>● Runs on PC/XT/AT/386/486, CGA, EGA, VGA.</li> <li>● Ideal for both education and industry.</li> </ul>

For full info' Phone, Fax or use Enquiry card!

**Number One Systems Ltd.**  
The Electronics CAD Specialists



Technical support free for life!  
Programs not copy protected.  
Special prices for Education.


REF: WW, HARDING WAY, ST.IVES, HUNTINGDON, CAMBS, PE17 4WR, ENGLAND.

Telephone: 0480 461778 (7 lines) Fax: 0480 494042 International: +44-480-461778 Fax: +44-480-494042

Prices Exclude P&P and VAT

ACCESS, AMEX, MASTERCARD, VISA Welcome.

CIRCLE NO. 123 ON REPLY CARD

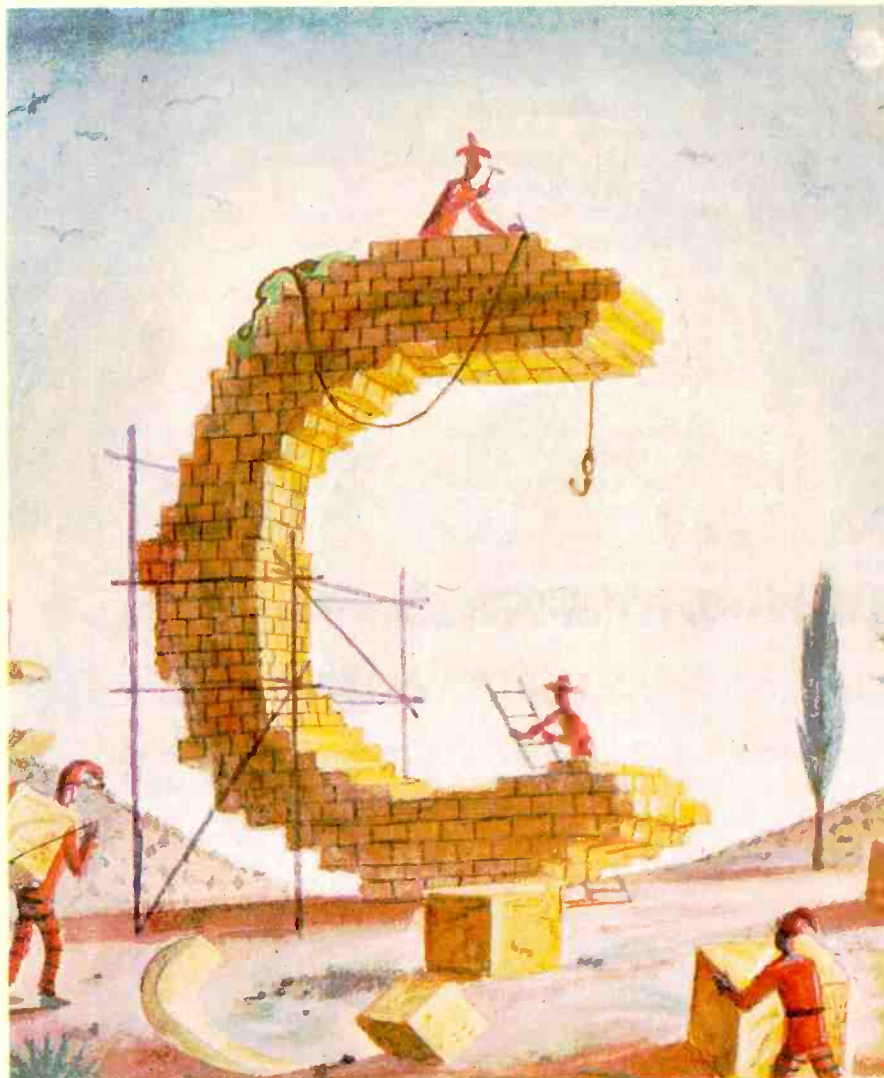

# INTERFACING WITH C

by  
HOWARD HUTCHINGS

Interfacing with C can be obtained from Lorraine Spindler, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM5 2AS.

Please make cheques for £14.95 (which includes postage and packing) payable to Reed Business Publishing Group.

Alternatively, you can telephone your order, quoting a credit card number. Telephone 081-652 3614.

A disk containing all the example listings used in this book is available at £29.96. Please specify size required.

## C HERE!

If you have followed our series on the use of the C programming language, then you will recognise its value to the practising engineer.

But, rather than turning up old issues of the journal to check your design for a digital filter, why not have all the articles collected together in one book, *Interfacing with C*?

The book is a storehouse of information that will be of lasting value to anyone involved in the design of filters, A-to-D conversion, convolution, Fourier and many other applications, with not a soldering iron in sight.


To complement the published series, Howard Hutchings has written additional chapters on D-to-A and A-to-D conversion, waveform synthesis and audio special effects, including echo and reverberation. An appendix provides a "getting started" introduction to the running of the many programs scattered throughout the book.

This is a practical guide to real-time programming, the programs provided having been tested and proved. It is a distillation of the teaching of computer-assisted engineering at Humberside Polytechnic, at which Dr Hutchings is a senior lecturer.

Source code listings for the programs described in the book are available on disk.



# BOOKS TO BUY

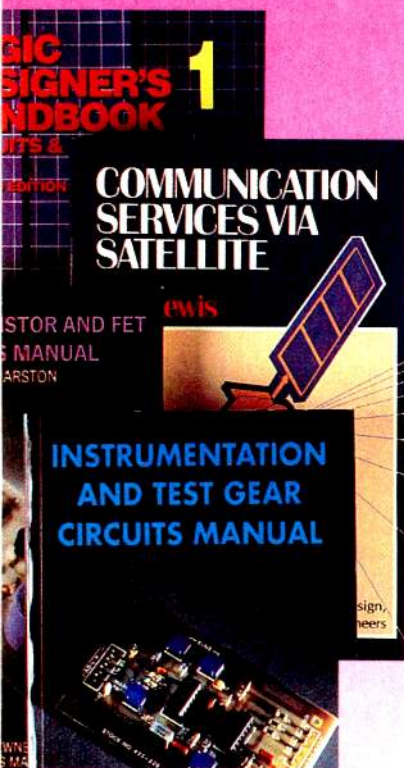

in grasping electrical and electronics theory. This book has been written to help such students to understand the mathematical principles underlying their subject so that they can go on with confidence to tackle problems in practical circuits. Paperback 256 pages.  
**Price £14.95 0 7506 0924 9**

## CIRCUIT MANUALS

**Ray Marston**

A series of books dealing with their subjects in an easy-to-read and non-mathematical manner, presenting the reader with many practical applications and circuits. They are specifically written, for the design engineer, technician and the experimenter, as well as the electronics student and amateur. All the titles are written by Ray Marston, a freelance electronics design engineer and international writer.

### Op-amp Circuits Manual

**Paperback 224 pages**  
**Price £13.95 0 434 912077**

### Audio IC Circuits Manual

**Paperback 168 pages**  
**Price £13.95 0 434 912107**

### CMOS Circuits Manual

**Paperback 192 pages**  
**Price £13.95 0 434 912123**

### Electronic Alarm Circuits Manual

**Paperback 144 pages**  
**Price £13.95 0 7506 00640**

### Timer/Generator Circuits Manual

**Paperback 224 pages**  
**Price £13.95 0 434 912913**

### Diode, Transistor and FET Circuits Manual

**Paperback 240 pages**  
**Price £13.95 0 7506 0228 7**

### Instrumentation and Test Gear Circuits Manual

**Ray Marston**  
Modern instrumentation and test gear circuits of value to the industrial, commercial, or amateur electronic engineer or designer make up this book. Almost 500 outstandingly useful and carefully selected practical circuits are in here. This is one book you must have if you need access to practical working circuits ranging from simple attenuators and bridges to complex digital panel meters, waveform generators, and scope trace doublers. Paperback 400 pages.  
**Price £16.95 0 7506 0758 0**

### Logic Designers Handbook

**Andrew Parr**  
Easy to read, but none the less thorough, this book on digital circuits is for use by students and engineers and provides an accessible source of data on devices in the TTL and CMOS families. It's a 'Designers Handbook' that will live on the designer's bench rather than on the bookshelf. The basic theory is explained and then supported with specific practical examples. Paperback 488 pages.  
**Price £25.00 0 7506 0535 9**

### Digital Audio and Compact Disc Technology

**Luc Baert, Luc Theunissen & Guido Vergult**  
Essential reading for audio engineers, students and hi-fi enthusiasts. A clear and easy-to-follow introduction and includes a technical description of DAT (digital audio tape). Contents includes principles of digital signal processing, sampling, quantization, A/D conversion systems, codes for digital magnetic recording, principles of error correction, the compact disc, CD encoding, opto-electronics and the optical block, servo circuits in CD players, signal processing, digital audio recording systems, PCM, Video 8, R-DAT and S-DAT. Paperback 240 pages.  
**Price £16.95 0 7506 0614 2**

### NEWNES POCKET BOOKS

A series of handy, inexpensive, pocket sized books to be kept by your side and used every day. Their size makes them an ideal 'travelling' companion as well.

### Newnes Electronics Engineer's Pocket Book

**Keith Brindley**  
**Hardback 319 pages**  
**Price £12.95 0 7506 0937 0**

### Newnes Electronics Assembly Pocket Book

**Keith Brindley**  
**Hardback 304 pages**  
**Price £10.95 0 7506 0222 8**

### Newnes Television and Video Engineer's Pocket Book

**Eugene Trundle**  
**Hardback 384 pages**  
**Price £12.95 0 7506 0677 0**

### Newnes Circuit Calculations Pocket Book

**T Davies**  
**Hardback 300 pages**  
**Price £10.95 0 7506 0195 7**

### Newnes Data Communications Pocket Book

**Michael Tooley**  
**Hardback 192 pages**  
**Price £12.95 0 7506 0427 1**

### Newnes Telecommunications Pocket Book

**JE Varrall & EA Edis**  
**Hardback 400 pages**  
**Price £12.95 0 7506 0307 0**

### Newnes Z80 Pocket Book

**Chris Roberts**  
**Hardback 185 pages**  
**Price £12.95 0 7506 0308 9**

### Newnes 68000 Pocket Book

**Mike Tooley**  
**Hardback 257 pages**  
**Price £12.95 0 7506 0309 7**

### Newnes Electrical Pocket Book

**21st edition**  
**E A Parr**  
**Paperback 526 pages**  
**£12.95 0 7506 05138**

### Newnes Electric Circuits Pocket Book Linear IC

**Ray Marston**  
**Hardback 336 pages**  
**Price £12.95 0 7506 0132 9**

### Newnes Guide to Satellite TV

**D J Stephenson**  
A practical guide, without excessive theory of mathematics, to the installation and servicing of satellite TV receiving equipment for those professionally employed in the aerial rigging/TV trades. Hardback 256 pages.  
**Price £17.95 0 7506 0215 5**

### Newnes Practical RF Handbook

**Ian Hickman**  
Pressure on the RF spectrum has never been greater and it's people with knowledge and skills of RF design who are now in demand in the electronics industry to design, produce, maintain and use equipment capable of working in this crowded environment. This practical introduction to modern RF circuit design will equip you with the necessary RF knowledge and skills to enable you to compete effectively in the industry. Paperback 320 pages.  
**Price £16.95 0 7506 0871 4**

### Troubleshooting Analog Circuits

**R A Pease**  
Bob Pease is one of the legends of analog design. Over the years, he's developed techniques and methods to expedite the often-difficult tasks of debugging and

### Programmable Logic Handbook

**Geoff Bostock**  
Logic circuit designers are increasingly turning to programmable logic devices as a means of solving problems. This book, for the established electronics engineer, student and technician, is a thorough introduction to programmable logic. Geoff Bostock will take you to a level where you, as a designer, can take full advantage of the growing product range of ASICs and other self-programmable arrays used in computer and control systems. Paperback 256 pages.  
**Price £19.95 0 7506 0808 0**

### Understand Electrical and Electronic Maths

**Owen Bishop**  
People who find maths difficult often have, as a result, difficulty

troubleshooting analog circuits. Now, Bob has compiled his 'battle-tested' methods in the pages of this book. Based on his immensely popular series in EDN Magazine, the book contains a wealth of new material and advice for Digital/Analog electronics engineers on using simple equipment to troubleshoot. Paperback 217 pages.

**Price £14.95 0 7506 16326**

**PC-Based Instrumentation and Control**

**M Tooley**

Do you need information to enable you to select the necessary hardware and software to implement a wide range of practical PC-based instrumentation and control systems? Then this book is for you. Paperback 320 pages.

**Price £14.95 0 7506 1631 8**

**Electronic Circuits Handbook**

**M Tooley**

Provides you with a unique collection of practical working circuits together with supporting information so that circuits can be produced in the shortest possible time and without recourse to theoretical texts. Paperback 345 pages.

**Price £24.95 0 7506 0750 5**

**Communication Services via Satellite**

**G E Lewis**

DBS is already with us, and will create a series of new technical problems for engineers/technicians in television and communication services. This book gives you the solutions to these problems by:

explaining how the system functions; describing several actual systems and giving several analyses and design rules. You can't afford to be without this invaluable technology update if you're a systems design engineer, service engineer or technician. Paperback 400 pages.

**Price £25.00 0 7506 0437 9**

**Digital Logic Design**  
**Brian Holdsworth**

As one of the most successful and well established electronics textbooks on digital logic design, this book reflects recent developments in the digital fields. The book also covers new functional logic symbols and logic design using MSI and programmable logic arrays. Paperback 448 pages.

**Price £19.50 0 7506 0501 4**

**The Circuit Designers Companion**

**T Williams**

This compendium of practical wisdom concerning the real-world aspects of electronic circuit design is invaluable for linear and digital designers alike. Hardback 320 pages.

**Price £25.00 0 7506 1142 1**

**Credit card orders accepted by phone**  
**081 652 3614**

**Return to: Lorraine Spindler, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**

**Please supply the following titles:**

Qty	Title	ISBN	Price
	Programmable Logic Handbook	07506 0808 0	19.95
	Understanding Electrical & Elec Maths	07506 0924 9	14.95
	Op-amp Circuits Manual	0434 912077	13.95
	Audio IC Circuits Manual	0434 912107	13.95
	CMOS Circuit Manual	0434 912123	13.95
	Electronic Alarm Circuits Manual	07506 0064 0	13.95
	Power Control Circuits Manual	07506 06908	13.95
	Timer/Generator Circuits Manual	0434 91291 3	13.95
	Diode, Transistor & FET Circuits Man	07506 0228 7	13.95
	Instrumentation & Test Gear Circuits Man	07506 0758 0	16.95
	Logic Designers Handbook	07506 0614 2	16.95
	Digital Audio and Compact Disc	07506 0614 2	16.95
	Newnes Elec Engineers Pkt Bk	07506 0937 0	12.95
	Newnes Elec Assembly Pkt Bk	07506 0222 8	10.95
	Newnes TV and Video Eng Pkt Bk	07506 0677 0	12.95
	Newnes Circuit Calculations Pkt Bk	07506 0427 1	10.95
	Newnes Data Communications Pkt Bk	07506 0308 9	12.95
	Newnes Telecommunications Pkt Bk	07506 0307 0	12.95
	Newnes Z80 Pkt Bk	07506 0308 9	12.95
	Newnes 68000 Pkt Bk	07506 0309 7	12.95
	Newnes Electrical Pkt Bk	07506 05138	12.95
	Newnes Electric Circuits Pocket Bk	07506 0132 9	12.95
	Newnes Guide to Satellite TV	07506 0215 5	17.95
	Newnes Practical RF Handbook	07506 0871 4	16.95
	Troubleshooting Analog Circuits	07506 16326	14.95
	PC-Based Instrumentation and Control	07506 1631 8	14.95
	Electronic Circuits Handbook	07506 0750 5	24.95
	Communication Services via Satellite	07506 0437 9	25.00
	Digital Logic Design	07506 05014	19.50

PLEASE ADD £2.50 FOR POSTAGE  
Add VAT at local rate  
NB ZERO RATE FOR UK & IRE  
TOTAL

**Business purchase:** Please send me the books listed with an invoice. I will arrange for my company to pay the accompanying invoice within 30 days. I will attach my business card letterhead and have signed the form below.  
**Guarantee:** If you are not completely satisfied, books may be returned within 30 days in a resaleable condition for a full refund.

Remittance enclosed £  
Cheques should be made payable to **Reed Book Services Ltd.**  
Please debit my credit card as follows:

Access/Master      Barclay/Visa      Amex      Diners

Credit Card No.      Exp date

NAME (Please print)

ORGANISATION

STREET

TOWN

COUNTY      POST CODE      COUNTRY


DATE      TELEPHONE NUMBER

SIGNATURE

T3000

**VAT RATES**  
6% Belgium, 25% Denmark, 5.5% France, 7% Germany, 4% Greece, 4% Italy, 3% Luxembourg, 6% Netherlands, 5% Portugal, 3% Spain. FOR COMPANIES REGISTERED FOR VAT, PLEASE SUPPLY YOUR REGISTRATION NUMBER BELOW (customers outside the EEC should leave this part blank)  
VAT NO.

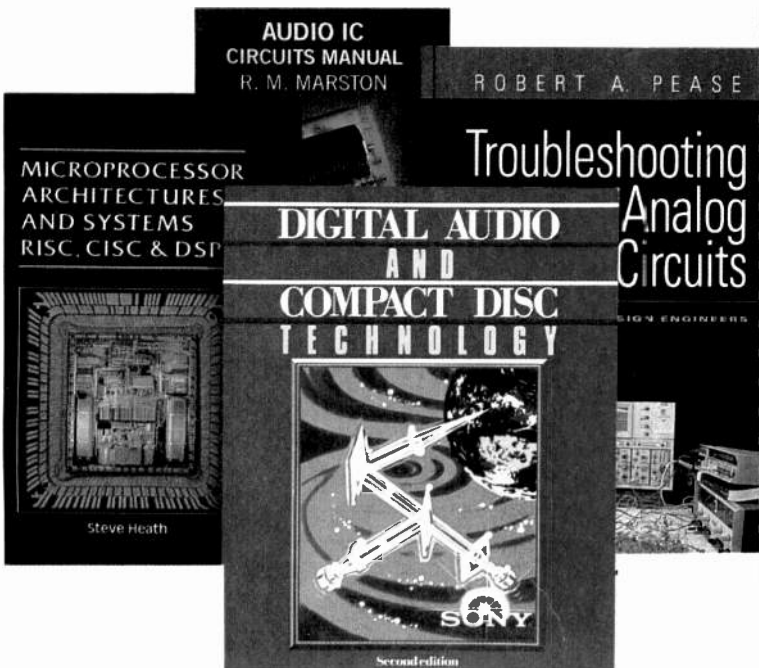If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.  
Please delete as appropriate. I do/do not wish to receive further details about books, journals and information services.  
Reed Business Publishing - Registered Office - Quadrant House The Quadrant Sutton Surrey SM2 5AS      Registered in England 151537





# Current conveyor ICs - a new building block

*There are unique benefits to current conveyor ICs in applications from lf to rf. Take a precision rectifier needing only two resistors and two diodes for example. Ian Hickman describes his experience with this new type of component.*

At first glance, the simplified circuit in **Fig. 1a** looks like an op-amp. An input to bias the tail current has to be provided externally, but the circuit has the usual npn input long tail pair, feeding current mirrors connected to the positive supply rail.

With complementary emitter followers to provide a low output impedance unity gain buffer at the output, it would simply be an op-amp with facility for trading off supply current against speed. In fact, the buffer is missing. Output is taken directly from two complementary transistors arranged as current sources fighting each other. This circuit is a common operational transconductance amplifier, or OTA.

**Figure 1b** shows a close relative of the transconductance amplifier. With a unity gain buffer at its output, this circuit becomes a current feedback op-amp. Since the buffer is missing, the device has a high impedance current source output as does an OTA. But instead of inverting and non-inverting inputs both of high impedance, this device has a high impedance non-inverting input and a low impedance inverting input.

Known as a current conveyor, the device is similar to a current feedback op-amp. Unlike the traditional voltage feedback op-amp, the transconductance amplifier is usually used without feedback. Similarly, unlike a current feedback op-amp, so is the current conveyor.

Absence of a feedback path avoids the stability problems that can plague voltage or current-feedback op-amp designs. This is a welcome feature of the current conveyor, providing complete stability when driving reactive loads of either sign. But the device's current output requires a different approach to circuit

applications, which cover the frequency range from dc up to 100MHz.

**Figure 2a** shows a simplified a current conveyor, the relation between the terminal currents and voltages, and pin-out of the *CCII01* integrated circuit. As with a current feedback op-amp, the current conveyor's non-inverting *Y* input is high impedance – 80kΩ at 1kHz – while its inverting *X* input is low impedance, **Fig. 2b**.

Packaged in eight-pin DIL, the *CCII01* contains two current conveyors. Conveniently, these can be combined to produce an enhanced composite conveyor. This configuration provides an input impedance of less than 200mΩ at the *X* input up to 1MHz or so, **Fig. 2c**.


With its low input impedance, the *X* node of either a standard or enhanced current conveyor can be used as a current summing junction for two or more signals. Its high *Z*-port output impedance – typically 1MΩ at a frequency of 1kHz – means that signals from several current conveyors can be combined simply by hard wiring their outputs together.

Numerous other applications, including differentiators and integrators, voltage and current-controlled negative-impedance converters, precision half and full-wave rectifiers, double terminated amplifiers are presented in the device data sheet.

## Filter

One application is as a biquad filter. Results obtained with the *CCII01* configured as a 5MHz bandpass filter<sup>1</sup> are shown in the data sheet<sup>2</sup>. Equations defining performance of the filter are presented in the panel.

I experimented with the bandpass circuit at audio

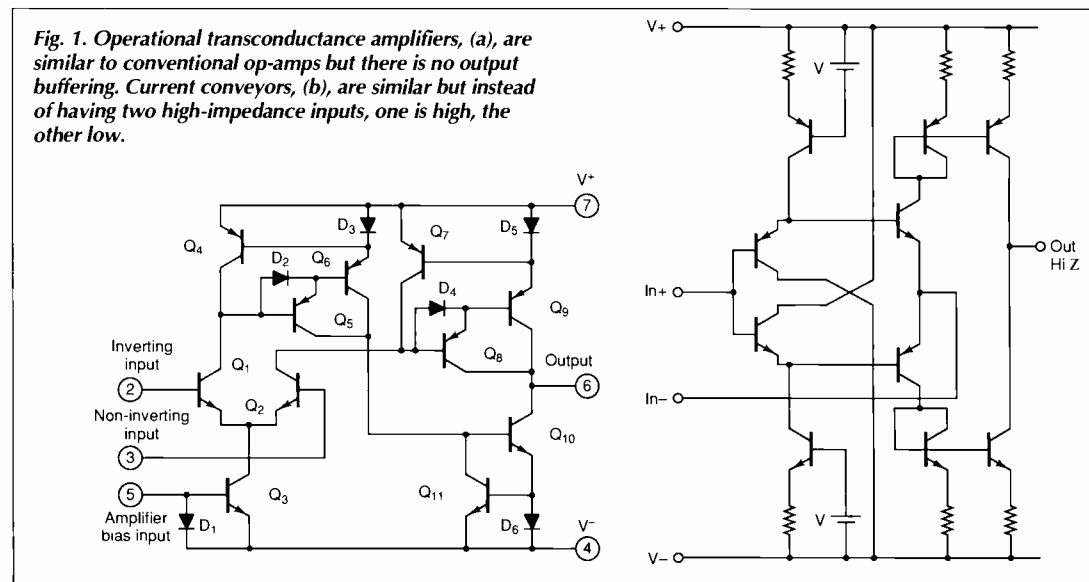

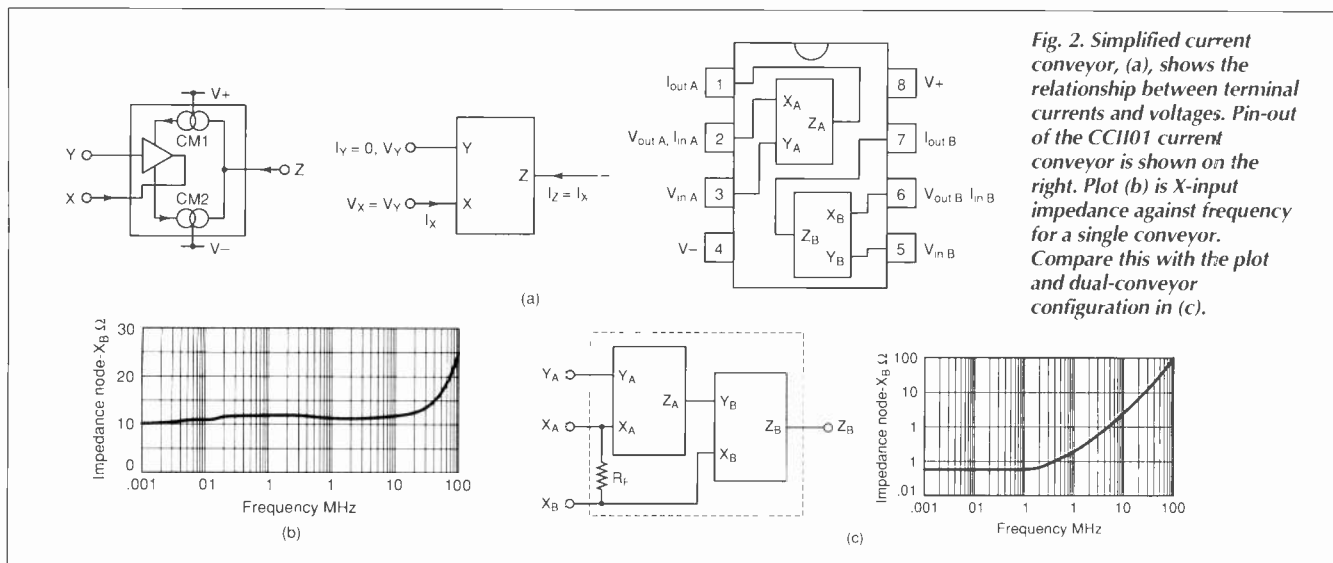


Fig. 2. Simplified current conveyor, (a), shows the relationship between terminal currents and voltages. Pin-out of the CCI101 current conveyor is shown on the right. Plot (b) is X-input impedance against frequency for a single conveyor. Compare this with the plot and dual-conveyor configuration in (c).

frequency, deliberately using extreme values of components to verify the equations and performance. Figure 3a shows this version. Component  $Y_2$  is 0.1S, i.e.  $R_2$  is non-existent but there is 10Ω of input impedance from X input of the first current conveyor.

From the equations in the panel, the expected frequency peak was at 2250Hz while the measured peak occurred at 2267Hz. As the circuit had 20% tolerance capacitors, the close agreement was more luck than good engineering. No such close agreement was found for  $Q$ . The theoretical value was 7.03 whereas the

points at 2052Hz and 2495Hz indicated  $Q=5.1$ .

I used the filter to pick out the seventh harmonic of a 324Hz squarewave. Fig. 3b. Derived from the panel equations, the value of the filter's centre-frequency gain is 9950 or nearly 80dB. This is reflected in the large difference in Y deflection factors for the two traces. Given that amplitude of the seventh harmonic of the 4mV pk-pk squarewave is about 0.73mV pk-pk, the 7V pk-pk average value of the filter output is as expected.

In the time-domain, the damped wavetrain from the filter decays logarithmically after excitation by each

### Current conveyor filter performance

A lowpass/bandpass filter using current conveyors is shown here. Interchanging the resistors and capacitors produces a highpass version. In terms of the admittances of the passive components, the transfer function of the circuit is,

$$\frac{V_{BPF}}{V_{IN}} = \frac{-Y_2 Y_3}{Y_5(Y_2 + Y_3 + Y_4) + Y_3 Y_4}$$

where  $Y_2$  is the conductance  $1/R_2$ ,  $Y_3$  is the susceptance  $sC_3$ , etc, and  $s$  is the complex frequency variable. For analysing the steady state,  $s$  may be replaced by  $j\omega$ . Rewriting the equations in terms of C and R gives,

$$\frac{V_{BPF}}{V_{IN}} = \frac{-sC_3 R_5}{s^2 R_2 R_5 C_3 C_4 + sR_2(C_3 + C_4) + 1}$$

Comparing this with the archetypal form for a bandpass filter,

$$\frac{V_{BPF}}{V_{IN}} = \frac{As}{s^2 + Ds + 1}$$

peak response occurs when phase shift is zero. In this case, phase shift can also be 180° due to the minus sign in the numerator. The circuit is an inverting filter. This is so when the outer terms in

the denominator add to zero, leaving just a  $j\omega$  term to cancel top and bottom, i.e. a real negative number.

Since  $s^2 = (j\omega)^2 = -\omega^2$ , this occurs when;

$$\omega^2 R_2 R_5 C_3 C_4 = 1$$

Feeding in component values from Fig. 3a produces  $\omega = 2\pi f = 14142$  in which resonant frequency  $f_r$  is 2250Hz. At this frequency gain is,

$$\frac{-C_3 R_5}{R_2(C_3 + C_4)} = -9950$$

and  $Q$  is given by

$$\frac{1}{Q} = D = sR_2(C_3 + C_4)$$

In this instance,  $1/Q$  is 0.142 and  $Q$  is 7.03


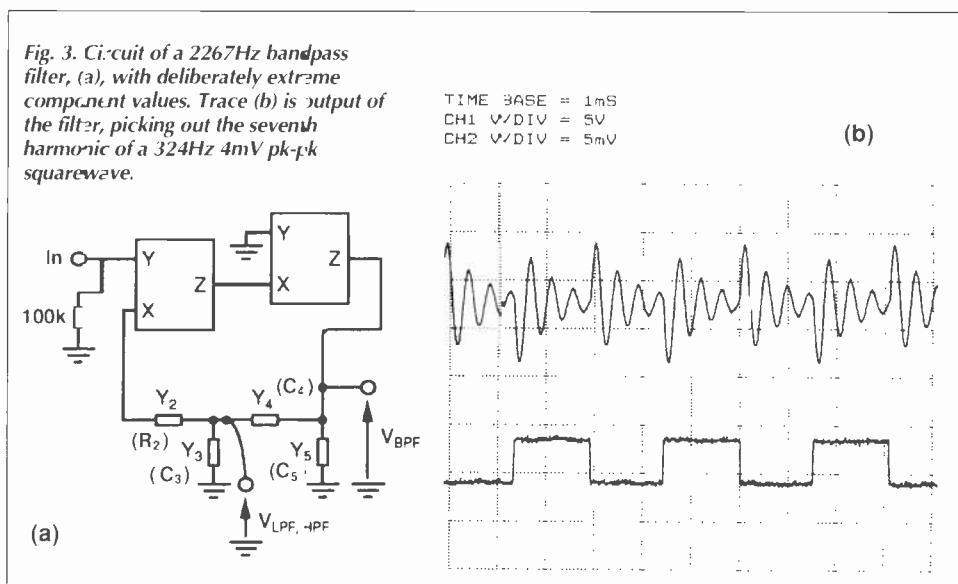


Fig. 3. Circuit of a 2267Hz bandpass filter, (a), with deliberately extreme component values. Trace (b) is output of the filter, picking out the seventh harmonic of a 324Hz 4mV pk-pk squarewave.

TIME BASE = 1ms  
CH1 V/DIV = 5V  
CH2 V/DIV = 5mV

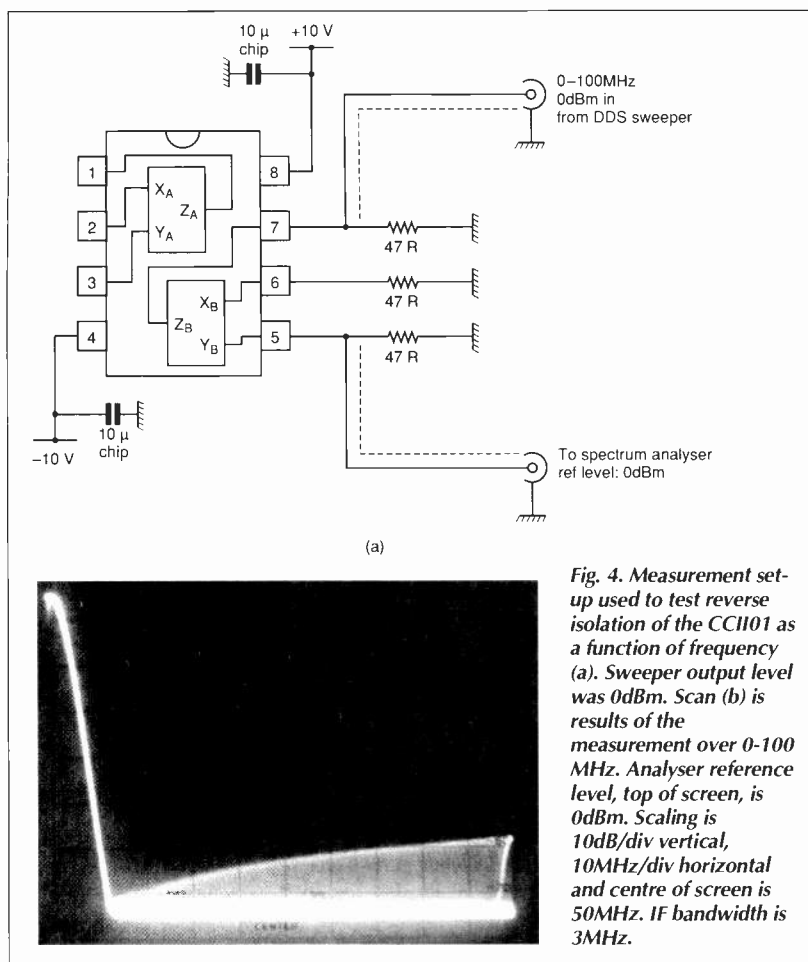

**Fig. 4. Measurement set-up used to test reverse isolation of the CCI101 as a function of frequency (a). Sweeper output level was 0dBm. Scan (b) is results of the measurement over 0-100 MHz. Analyser reference level, top of screen, is 0dBm. Scaling is 10dB/div vertical, 10MHz/div horizontal and centre of screen is 50MHz. IF bandwidth is 3MHz.**

edge of the squarewave. From this, applying the useful relationship between  $Q$  and energy stored over energy lost per radian you can calculate  $Q$ .

Careful measurements of successive peaks of the filter output waveform in Fig. 3b show that amplitude falls to 50% over each successive cycle. Energy stored falls to 25% per cycle, or to 80% per radian. Using an approximation only valid for high values,  $Q$  is about 100%/20%. This agrees with the measured value, mentioned earlier. I am not clear why centre frequency and gain should agree with the theoretical values but  $Q$  not.

Figure 3a is curious. At 0Hz, reactance of each capacitor is infinite, so they effectively no longer appear in the circuit. Gain at the lowpass output is then unity. This is because it is taken via  $R_2$  from the  $X$  port of the first current conveyor, the output of the device's unity gain input buffer.

At dc, the circuit is completely open loop, so some output offset might be expected at the bandpass output, given the high value of  $R_5$ . In fact, the output offset was zero, even with the 50Ω source disconnected leaving the  $Y$  input of the first current conveyor grounded via 100kΩ.

This says something for the accuracy of the device's fabrication, which is carried out by a manufacturer of advanced linear ICs, Elantec. With its 2000V/μs slew rate and 700MHz equivalent gain-bandwidth product, the device is specified for use up to 100MHz.

For any active device intended to be used at high frequencies, an important parameter is reverse isolation. For stable operation – especially in tuned circuits – this should comfortably exceed the forward gain expected from any amplifier using the device.

I measured reverse isolation as a function of frequency using the test set-up of Fig. 4a. Output of the DDS-based sweeper was 0dBm at low frequencies, falling linearly by no more than 1dB up to 100MHz.

### RF amplifier

Figure 4b shows reverse isolation over that frequency range. Reference level of the spectrum analyser was 0dBm and IF bandwidth set wide to 3MHz. This was done to produce a bright enough trace to register at each step of the sweep. Reverse isolation exceeds 70dB below 15MHz, greater than 60dB below 70MHz and still 56dB at 100MHz.

With this sort of performance, the CCI101 should enable stable, high gain rf amplifier stages to be readily realised. I tested this hypothesis via Fig. 5a. Here, a series tuned circuit at a current conveyor's  $X$  port and a parallel tuned circuit, also 10.7MHz, at its  $Z$  output is used to provide a two-pole response.

Appropriate values of  $L/C$  ratio were selected for the two tuned circuits. The second current conveyor in the package formed a high input impedance buffer to avoid loading the parallel tuned circuit.

Attenuated -50dBm output of the sweeper was applied to the circuit, output from which is shown in Fig. 5b. This scan indicates a gain of 30dB and a rather useful but unintentional bandpass response.

With a part having a response extending to the best part of a gigahertz, I used compact layout and a groundplane. As a result there was some coupling between the unshielded coils. Symmetry of the response indicates a lack of internal feedback. This leads to the question - can the circuit be pushed for even more gain and selectivity, without incurring instability?

The 47Ω resistor at the  $X$  input of the second current conveyor in the package was replaced by another 10.7MHz series tuned circuit. All coils were screened. I noticed some occasional oscillation at around 400MHz which was cured by inserting a 10Ω resistor between the  $X$  port pin 6 and the second series tuned circuit as shown in Fig. 5c.


Response, shown in Fig. 5d, indicates that the screened coils prevented unintentional coupling. Output of the circuit is now -7dBm and gain around 43dB. As shown in Fig. 5a however, the circuit does not provide 50Ω input termination.

Slight asymmetry in the response, with a faster fall-off on the high frequency side, indicates some internal feedback. This is not surprising, since although the reverse isolation of the current conveyor at pins 5, 6 and 7 exceeded 70dB at 10MHz the two current conveyors are physically very close.

The remarkable aspect of Fig. 5c is the almost total absence of discrete components, apart from the tuned circuits. Presumably additional tuned circuits, providing 50Ω interfaces to the chip, at input and output, would produce a five-pole response.

In practice, you would probably never need to design a 10.7MHz amplifier using individual tuned circuits as in Fig. 5c. A wide range of block filters covering almost any conceivable requirement is available from numerous suppliers. But if an IF amplifier operating at a non-standard frequency is needed, then current conveyor ICs provide a convenient way of producing the gain and selectivity necessary with a minimum of components.

Figure 6 demonstrates two further current-conveyor applications. Configuration 6a is synonymous with

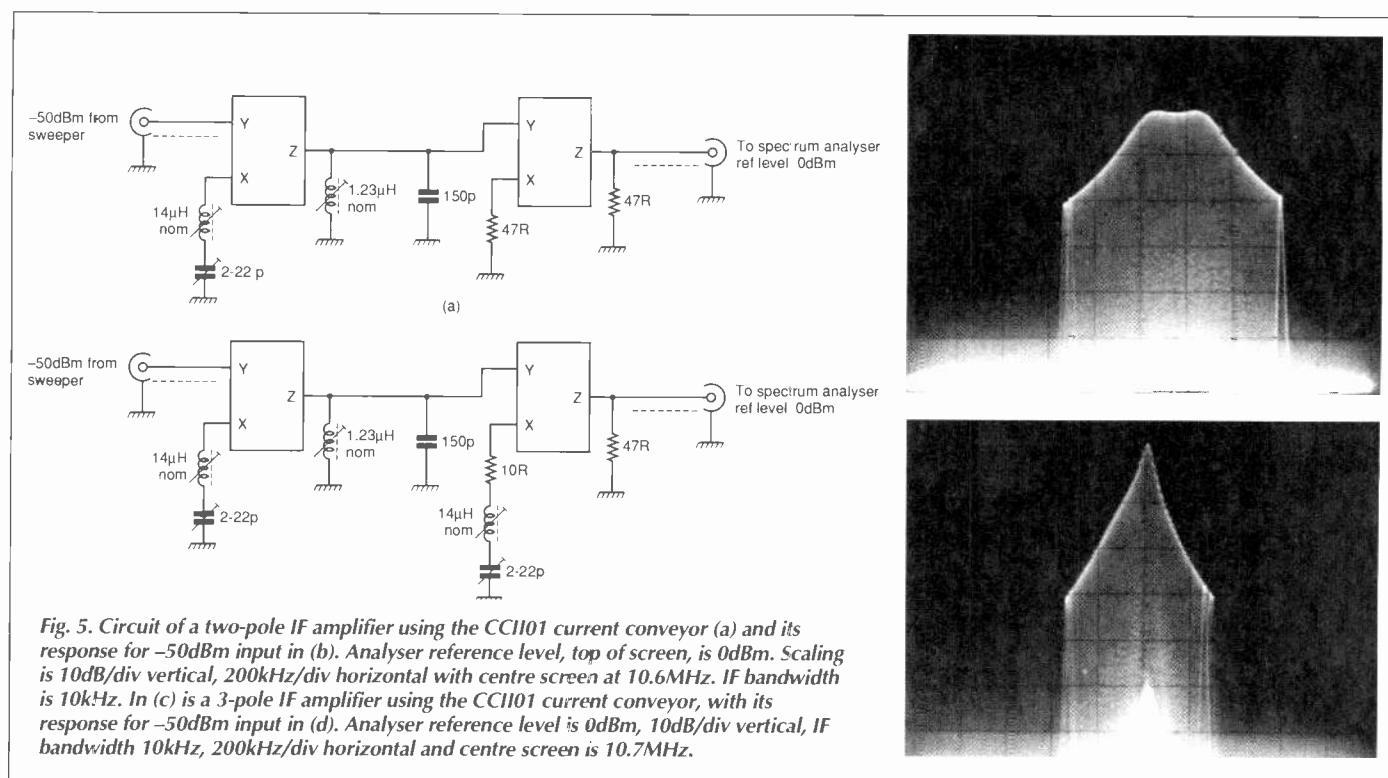

the voltage-controlled or short-circuit stable negative-impedance converter. Being a current-controlled impedance converter it is open-circuit stable.

To see how the converter works, imagine Z is a 1kΩ resistor with its lower end grounded. Voltages at ports X, Y and Z are all initially zero and relationships between the port voltages and currents are defined in Fig. 2a. Raise X to +1V. Since  $V_x = V_y$ , port Y must also be at +1V so there must be +1V at the top end of the 1kΩ resistor. A 1mA current flows out of port Z but also out of X since  $I_z = I_x$ . As a result, port X exhibits a resistance of -1kΩ.

The lower end of Z was assumed grounded solely to simplify the explanation: in view of the device's high common mode rejection - greater than 53dB up to 1MHz - neither end of Z need be grounded. The circuit offers a floating negative impedance.

High output resistance of the Z port, typically 1MΩ at 1kHz, makes it behave like an almost perfect current source. Current passing through the load is not related to the voltage-drop across it. This situation is ideal for biasing diodes in a precision rectifier circuit.

Figure 6b shows a half-wave rectifier. If  $R_1$  equals  $R_2$ , then output is identical to the input for positive voltages and is zero for negative voltages, regardless of waveform or mark/space ratio. Results obtained for a sine wave input are shown in Fig. 6c. Full-wave precision rectification is also covered in the data sheet.

If you experiment with the CCI101, you should be wary of the simulated grounded inductance shown in the data sheet and covered in the first reference. As expected, this set up draws a lagging current from a zero resistance source. Since both current conveyors in the loop are non-inverting, however, the circuit looks like a *negative* resistor at dc - unlike a real inductor. In other words, the circuit is not open-circuit stable and will lock up at one or other supply rail. ■

#### References

- 1 *Current conveyor circuits*, Electronics World and Wireless World, Nov., 1993 pp 962-963.
- 2 *CCI101 data sheet*, LTP Electronics Ltd, 2 Quarry Road, Headington, Oxford OX3 8NU. Tel. 0865 744232.

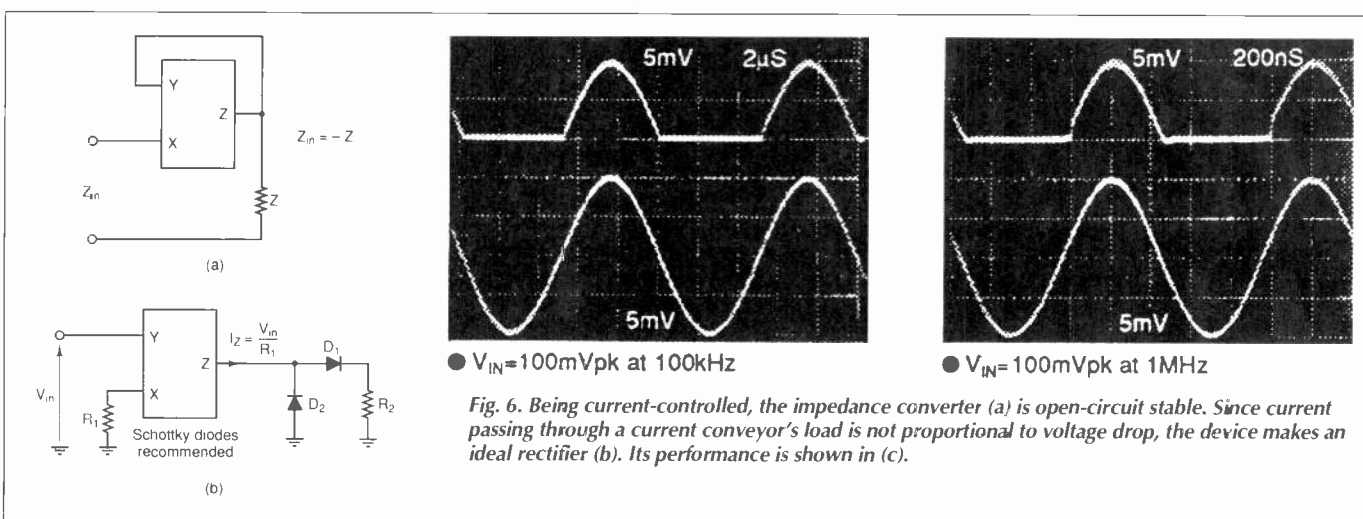


Fig. 6. Being current-controlled, the impedance converter (a) is open-circuit stable. Since current passing through a current conveyor's load is not proportional to voltage drop, the device makes an ideal rectifier (b). Its performance is shown in (c).

# BOOK REVIEWS

## A simple approach to digital signal processing

Over the past ten years, digital signal processing has attracted a lot of attention. This is reflected by the wealth of text books on the topic.

With subjects such as digital filters and FFTs so well worn it would be difficult to find an area which has not been adequately covered in depth – several times over. However Marven and Ewers have identified a deficiency in the standard book range. There is little to cater for the first time reader who is just starting out on the demanding subject of DSP.

*A Simple Approach to DSP* begins from ground zero and covers the majority of DSP subjects in sufficient depth to enable the new reader to gain a flavour of what the subject is about without getting bogged down in the maths and the algorithms. In this respect the book succeeds. It is very readable and the page layout is pleasant – a lesson that many other British publishers have yet to learn.

Maths is kept to a minimum and the diagrams are informative. The style is approachable and should maintain the interest of the new reader. Many introductory texts on DSP fail so often to sustain the reader's interest. Mainly, this is because they delve into the complexity of the subject too early with little regard for the struggling reader whose maths may be a little shaky.


This is clearly not the case with this book. On establishing the reader's confidence in the first few chapters, the book succeeds on building on that confidence to introduce the more demanding aspects of DSP – digital filtering and spectral analysis. Each chapter is supported by a reasonable list of references for further reading. However when discussing processor hardware the

authors have not presented a balanced overview of commercial products. Since the authors are with Texas Instruments, one would naturally assume a discussion on TI's processors, but not to the exclusion of their competitors. Although there is a brief mention at the start of Chapter 7, a discussion of competitors' products would have provided a useful prospective of hardware performance.

On the whole the book should provide a basic understanding of DSP and should serve as a useful introduction to the subject. If its cost could be reduced to less than £10 it would probably find a wider readership among students as an auxiliary text.

Allen Brown

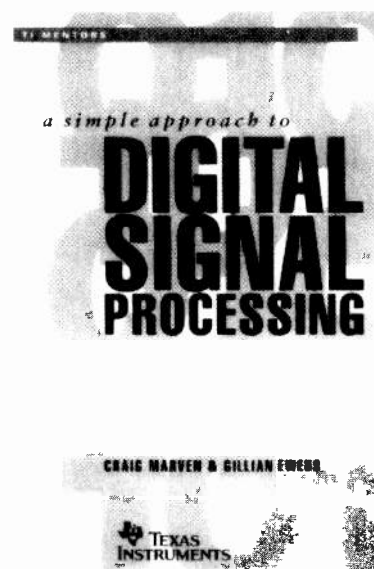Craig Marven & Gillian Ewers, Texas Instruments  
1993. ISBN 0-904 047-00-8, price £19.



## The multiplexer reference manual

Written by Gilbert Held, *The multiplexer reference manual*, is concerned with the multiplexer in communications, rather than the more usual connotation in our field of input multiplexers for signal processing.

The first chapter sets the scene, describing the reasons for the existence of the devices. It proceeds to recount the early uses of multiplexing in telephony and to specify the evolutionary development of the subject from frequency division to optical fibre time division. Each of the methods of multiplexing is given a chapter to itself: frequency and time division, statistical multiplexers, packet assemblers/disassemblers, T-carrier multiplexers and optical fibres. In all cases the alternatives are compared.

In the last chapter, Held looks at currently

evolving methods, including fast packet multiplexing and low bit-rate voice digitisation. Networks are, of course, an important aspect of multiplexing and are accorded their rightful share of attention. Perhaps the most important sections are those on statistical and T1 multiplexers, which are given extensive treatment. Engineers concerned in any way – however peripherally – with communications and networking will find the book a valuable reference, although the style is rather unattractive. A more extensive use of the active voice would have helped to make it a little more appealing, but this is a personal preference and in no way detracts from the value of the work.

Philip Darrington

John Wiley, 188 pages, hardback, £24.95.

## The Early History of Radio, from Faraday to Marconi

This work, by GRM Garratt is the outcome of a career spent mostly at the Science Museum, much of that time in charge of the Communications Collection. After early work at Metrovick and RAE Farnborough on blind landing, Gerald Garratt joined the Museum in 1934 and, except for a wartime period as Senior Engineer Staff Officer with the Royal Indian Air Force, remained there and made the history of radio his special interest.

Each of the six chapters after the introductory piece, on invention in general and electromagnetic theory in particular, is each concerned with one major figure in this field. The last one, on Marconi, was written by his daughter Susan, after Garratt's death in 1989, using lecture notes and other published work by her father.

As the author reiterates throughout, no single person could be called the inventor of radio communication. Each of the scientists mentioned here prepared the way for Marconi's work by discovering or clarifying a part of the puzzle. On one point, Garratt is adamant: Popov merely used the circuit described by Lodge to detect distant lightning flashes and expressed the 'hope' that

such equipment might eventually be used for communication. He made no significant contribution to the subject and his subsequent elevation to the ranks of those who did was engineered by the Soviet authorities for propaganda reasons. They did him a disservice, because he was a good physicist and needed no such false reputation. One is compelled to wonder why, if Popov was a negligible contributor, it was thought necessary to include him in the book.

It seems that leaders in scientific thought were not, even a couple of hundred years ago, automatically able to command respect. Faraday, who was later to become one of the most brilliant scientists of his time, was the son of a blacksmith, understood very little of mathematics and was regarded with extreme caution, being considered a "green-fingered" experimenter with an empirical approach to science, even though his contribution to field theory was seminal. Even Clerk Maxwell's contemporaries were sceptical until he was able to prove mathematically that both the "action-at-a-distance" fraternity and those who worked from Faraday's lines of force had the right answer.

Some of these people were untaught and felt their way in the face of disbelief and often ridicule from the establishment – a familiar story to the present day. Others approached the subject in a rigorously scientific manner and knew exactly what they were doing, but even they were in virgin territory with no one to consult when difficulties appeared: many of them discovered important processes without recognising what they had done. Their courage and determination to go on when the very cornerstones of the work were being questioned by their peers seem almost unbelievable.

This is a valuable little book (96 pages) in that it pulls together all the important names of the period up to and including Marconi: Faraday, Maxwell, Hertz, Lodge, Popov and Marconi. It is not a dull "history book", but is nonetheless complete with all the relevant scientific detail and a little light relief in the form of personal background. It is No 20 in the IEE History of Technology series, published in hard back at £19.00 in association with the Science Museum. ISBN 0 85296 845 0.

Philip Darrington



# THE BEST LOW COST PROGRAMMERS DESIGNED & MANUFACTURED IN THE UK

## **SPEEDMASTER 1000 SPEEDMASTER 1000E**

UNIVERSAL PROGRAMMER

- Superfast PC based programmer
- Programmes; EPROMS UP TO 8M BIT, FLASH EPROMS, EEPROMS, BPROMS, NVRAMs, MICROs (8748/51), PALs, GALs, EPLDs, PEELS, MACHS, MAPLs, MAX
- Plugs directly into parallel port
- 1000E Version has ROM/RAM emulator built in: 128k (1 Mbit) standard, optional 512K (4Mbit)

**only  
£445**

**only  
£525**

## **MICROMASTER 1000 MICROMASTER 1000E**

UNIVERSAL PROGRAMMER

- Programmes: EPROMS UP TO 8M BIT. FLASH EPROMS, EEPROMS, BPROMS, NVRAMs, PALs, GALs, EPLDs, PEELs, MACHs, MAPLs, MAX etc.
- PLUS over 80 different Micros including 8748/51, 68HC705, 68HC711, PICs, Z86, TMS320, TMS370 etc DIPs WITHOUT ADAPTORS OR PERSONALITY MODULES!
- Package adaptors available.
- 1000E Version has ROM/RAM emulator built in: 128K (1Mbit) standard, optional 512K (4 Mbit)

**only  
£575**

**only  
£645**

## **SPEEDMASTER 8000 GANG/SET PROGRAMMER**

- 8 way, Pc or stand alone
- Super-fast programming times, manufacturer recommended algorithms
- 32 pin devices as standard
- Support for 8748,51, TMS370, PIC Micros and 40 pins.

**only  
£645**

Now  
Includes:  
digital IC and RAM tester




**WHY BUY AN INFERIOR IMPORTED PROGRAMMER WHEN YOU CAN HAVE A MANUFACTURER APPROVED UNIVERSAL PROGRAMMER/EMULATOR DIRECT FROM ICE TECHNOLOGY!**

- We offer the best range of low-cost programmers available, now including our unique **UNIVERSAL PROGRAMMERS WITH BUILT IN EMULATORS**
- Unrivalled device support, for example the Micromaster 1000 programmes PICS, Z86, 87C705, 68HC705, TMS370, 77C82 ETC WITHOUT ADAPTORS, as well as the full range of Eproms, PLDs etc supported by all our universal programmers.
- Approved by National Semiconductor** for their full range of PALs, GALs, and MAPLs - other programmers claiming approval are often only approved for EPROMs - a much less exacting specification!
- All our programmers and programme/emulators work off the standard parallel port with any IBM compatible PC, even laptops
- Unbeaten programming times: Programme a 27256 in just 5 SECONDS including download and verify.
- Easy upgrade path between Models.

**FOR MORE DETAILS, DEVICE LIST AND DEMO DISK CALL NOW ON  
TEL +44 (0)226 767404 FAX +44 (0)226 370434**

ICE TECHNOLOGY LTD, UNIT 4, PENISTONE COURT, STATION BUILDINGS, PENISTONE, S. YORKS, S30 6HG, UK.

CIRCLE NO. 124 ON REPLY CARD

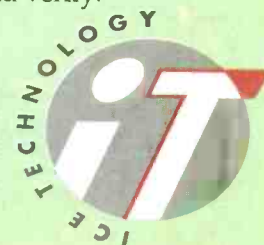

Surplus always wanted for cash!


# THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTHS SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

## LOW COST PC's - ALL EXPANDABLE - ALL PC COMPATIBLE

## THE OFFER OF 1994!

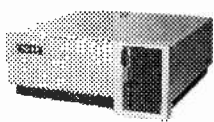


### SPECIAL BUY

**AT 286**  
40Mb HD + 3Mb Ram

LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems made in the USA to an industrial specification, the system was designed for reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 5.0 and 90 DAY Full Guarantee. *Ready to Run!*  
Order as HIGRADE 286 **Only £169.00 (E)**
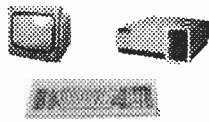
### PC SCOOP

COMPLETE  
COLOUR SYSTEM  
**ONLY £99.00**



A massive bulk purchase enables us to bring you a COMPLETE ready to run colour PC system at an unheard of price! The Display Electronics PC99 system comprises of fully compatible and expandable XT PC with 256k of RAM, 5 1/4" 360k floppy disk drive, 12" CGA colour monitor, standard 84 key keyboard, MS DOS and all connecting cables - just plug in and go! Ideal students, schools or anybody wishing to learn the world of PC's on an ultra low budget. Don't miss this opportunity. Fully guaranteed for 90 Days.  
Order as PC99COL **£99.00 (E)**



### Computer Controlled Laser Video Disk Player

One of the most amazing surplus deals that we ever been able to offer you! The Philips VP410 LaserVision player, in as new condition, unit features full computer control, Plays standard 12" LaserVision disks with starting visual and audio quality in two channel stereo or mono. When controlled by a computer, it may also be used as a versatile high quality storage / retrieval medium. It will play back either LaserVision CAV (active play) or CLV (Long Play) discs (which covers most types of commercially available video discs). Some of the many features of this incredible machine are:  
RS-232 INTERFACE RGB / COMPOSITE VIDEO OUTPUT  
BNC-SCART INTERFACE PAL / RGB DECODER  
IR+WIRED REMOTE CONTROL FAST RANDOM ACCESS

**SPECIAL PURCHASE** Only **£399.00 (F)**

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£32.95
NE2000 Ethernet (thick, thin or twisted) network card	£49.00

Optional Fitted extras: 640k RAM	£29.00
2nd floppy drive, specify 5 1/4" 360k or 3 1/2" 720k	£29.95
Above prices for PC99 offer ONLY.	

## FLOPPY DISK DRIVES 3.5" - 8"

5.25" from £22.95 - 3.5" from £24.95  
Massive purchases of standard 5.25" and 3.5" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3.5" supported on your PC).  
3.5" Panasonic JU363/4 720K or equivalent £24.95(B)  
3.5" Mitsubishi MF355C-L 1.4 Meg. Laptops only \* £36.95(B)  
3.5" Mitsubishi MF355C-D 1.4 Meg. Non laptop £29.95(B)  
5.25" Teac FD-55GFR 1.2 Meg £29.95(B)  
5.25" BRAND NEW Mitsubishi MF501B 360K £22.95(B)  
\* Data cable included in price.  
Shugart 800/801 8" SS refurbished & tested £195.00(E)  
Shugart 851 8" double sided refurbished & tested £250.00(E)  
Mitsubishi M2894-63 8" sided switchable NEW £50.00(E)  
Mitsubishi M2896-63-02U 8" DS slimline NEW £285.00(E)  
Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply. Ideal as exterior drives! £499.00(F)

## VIDEO MONITOR SPECIALS

Superb quality 14" FOREFRONT MTS-9600 SVGA Multisync - Multimode monitor 0.28" dot pitch with resolution of 1024 x 768. The multi mode input allows direct connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES etc. The H version will also function with the ATARI in all modes inc HI RES monochrome. Complete with 'text' switching for WP use. Syncs down to 15 kHz. Supplied in EXCELLENT little used condition with full 90 day guarantee.  
Order as MTS9600/H for ATARI £159.00(E)  
All modes as above Order as MTS9600/S £139.00(E)  
ELECTROHOME ECM-12115BU 12" VGA multisync monitor with resolution 640 x 480. Multi input selection; 9pin CGA/EGA; 15 pin VGA or 5 BNC connectors. 0.31 pitch. Compatible with PCs, Amiga, Atari and others. In good used condition (possible minor screen burns). 90 day guarantee. .... £99.00(E)  
KME 10" high definition colour monitors. Nice tight 0.28" dot pitch for superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13.5" x 12" x 11". Only £125 (E)  
Good used condition. 90 day guarantee.  
KME 10" as above for PC EGA standard £145.00 (E)  
NEC CGA 12" colour IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" x 13" W x 12" H. The front cosmetic bezel has been removed for contractual reasons. **Only £49.00(E)**

### 20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, Point of Sale etc. In EXCELLENT little used condition with full 90 day guarantee.  
20"....£135 22"....£155 26"....£185 (F)  
9" Mono cased, Black & White for CCTV Used / Tested £49.00 (C)

## HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte of hard disk storage! Full industry standard SMJD interface. Ultra hi speed data transfer and access time, replaces Fujitsu equivalent model. complete with manual. Only £299.00(E)  
3.5" FUJII FK-309-26 20mb MFM I/F £59.95(C)  
3.5" CONNER CP3024 20 mb IDE I/F (or equiv.) £69.95(C)  
3.5" CONNER CP3044 40mb IDE I/F (or equiv.) £99.00(C)  
3.5" RODIME R03085S 70mb SCSI I/F (Mac & Acorn) £129.00(C)  
5.25" MINISCRIBE 3425 20mb MFM I/F (or equiv.) £49.95(C)  
5.25" SEAGATE ST-238R 30 mb MLT I/F £69.95(C)  
5.25" CDC 94205-51 40mb HH MFM I/F £89.95(C)  
8" Fujitsu 160 Mb SMD I/F RFE tested £195.00(D)  
Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95

## THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



### TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.  
TELEBOX ST for composite video input type monitors £32.95  
TELEBOX STL as ST but with integral speaker £36.50  
TELEBOX MB Multiband VHF-UHF-Cable- Hyperband tuner £69.95  
For overseas PAL versions state 5.5 or 6mhz sound specification.  
\*For cable / hyperband reception Telebox MB should be connected to cable type socket. Shipping code on all Teleboxes is (B)

## FANS & BLOWERS

3.5" FUJITSU MF-06D12DL 60 x 25 mm 12v DC £4.95 10 / £42  
3.5" FUJITSU MF-09B12DH 92 x 25 mm 12v DC £5.95 10 / £53  
PANCAKE 12-3.5 92 x 18 mm 12v DC £7.95 10 / £69  
EX-EQUIP 120 x 38mm AC fans - tested specify 110 or 240 v £6.95  
EX-EQUIP 80 x 38mm AC fans - tested specify 110 or 240v £5.95  
VERO rack mount 1U x 19" fan tray specify 110 or 240v £45.95  
IHOF B26 1900 rack mnt 3U x 19" Blower 110/240v NEW £79.95  
Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

## IC'S TRANSISTORS DIODES

OBSOLETE - SHORT SUPPLY - BULK  
**5,000,000 items EX STOCK**  
For MAJOR SAVINGS - SAE or CALL FOR LATEST LIST

## Issue 12 of Display News now available - send large SAE - PACKED with bargains!

Display Electronics logo and name.

**LONDON SHOP**  
Open Mon-Sat 9:00-5:30  
215 Whitehorse Lane  
South Norwood  
LONDON SE25

**DISTEL © The Original**  
FREE On line Database  
Info on 1000's of items  
V21,V22, V22 BIS  
081 679 1888

**ALL MAIL & OFFICES**  
Open Mon-Fri 9.00-5.30  
Dept WW. 32 Biggin Way  
Upper Norwood  
LONDON SE19 3XF

**ALL ENQUIRIES**  
**081 679 4414**  
FAX 081 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools Universities and Local Authorities - minimum account order £40. Carriage charges (A)=£3, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1994. E & O E.



## MOTORS - BATTERY 1-12V

3 different model motors, £1, Order Ref 35.  
**Spin to start 3v DC motors** for model aircraft etc, 5 for £1, Order Ref 134.  
**Cassette Motor** 1.5v, powerful, speed increases with voltage, £1, Order Ref 224.  
**Mini Cassette Motor** 6-9v working, £1, Order Ref 944.  
**High Efficiency Motor** for solar cell working, £1, Order Ref 643.  
**12V Motor** ex BSR record player, £1, Order Ref 687.  
**9V Cassette Motor**, brushless, £1.50, Order Ref 1.5P14.  
**1/10HP 12V DC Motor**, Smiths, £4, Order Ref 4P22.  
**1/8HP 12V Motor**, Smiths, £6, Order Ref 6P1.  
**1/6HP 12V Motor**, Smiths, £8, Order Ref 8P14.  
**1/3HP Motor** (Sinclair C5) £18, Order Ref 18P7.

## MAINS MOTORS WITH GEARBOXES

**5RPM 60W**, £5, Order Ref 5P54.  
**25RPM 60W**, £6, Order Ref 6P35.  
**50RPM 60W**, £5, Order Ref 5P168.  
**110RPM 60W**, £5, Order Ref 5P172.  
**150RPM 60W**, £5, Order Ref 5P169.  
**200RPM 60W**, £5, Order Ref 5P216.  
**500W Motor** with gearbox & variable speed selection, 100rpm upwards, £5, Order Ref 5P220.  
**1 Rev per 24hrs 2W Motor**, £1, Order Ref 89.  
**1 Rev per 12hrs 2W Motor**, £1, Order Ref 90.  
**1 Rev per 4hrs 2W Motor**, £1, Order Ref 2P239.  
**1 Rev per hour 2W Extra Small Motor**, 2 for £1, Order Ref 500.  
**12RPH Motor**, £2, Order Ref 2P342.  
**20RPH Motor**, £1, Order Ref 1010.  
**1/3RPM 2W Motor**, £2, Order Ref 2P346.  
**1RPM Motor**, £2, Order Ref 2P328.  
**4RPM 2W Motor**, £1, Order Ref 446.  
**15RPM 2W Motor**, £2, Order Ref 2P321.  
**25RPM 2W Motor**, £2, Order Ref 2P322.  
**200RPM 2W Motor**, £1, Order Ref 175.  
**250RPM 2W Motor**, £1, Order Ref 750.

## MAINS MOTORS

**3/4 Stack Motor** with 1/4" spindle, £1, Order Ref 85.  
**Motor 1 1/2" Stack** with good length spindle from each side, £2, Order Ref 2P55.  
**Motor 1 1/4" Stack** with 4" long spindle, £2, Order Ref 2P203.  
**Motor by Crompton**. .06HP but little soiled, £3, Order Ref 3P4.  
**JAP made Precision Motor** balanced rotor reversible, 1500rpm, £2, Order Ref 2P12.  
**Tape Motor by EMI** 2 speed & reversible, £2, Order Ref 2P70.  
**Very Powerful Mains Motor** with extra long (2 1/2") shafts extending out each side. Makes it ideal for a reversing arrangement for, as you know, shaded pole motors are not reversible, £3, Order Ref 3P157.

## MOTORS - STEPPER

**Mini Motor by Philips** 12V-7.5 degree step, quite standard, data supplied, only £1, Order Ref 910.  
**Medium Powered Jap made** 1.5 degree step, £3, Order Ref 3P162.  
**Very Powerful Motor** by American Philips 10-14V 7.5 degree step, £5, Order Ref 5P81.

## MAINS TRANSFORMERS

**5V 45A**, £20, Order Ref 20P16.  
**6V 1A**, 2 for £1, Order 9.  
**8V 1A**, £1, Order Ref 212.  
**9V 1/2A**, 2 for £1, Order Ref 266.  
**9V 1A**, £1, Order Ref 236.  
**10V 1A**, £1, Order Ref 492.  
**12V 1/2A**, 2 for £1, Order Ref 10.  
**12V 1A**, £1, Order Ref 436.  
**12V 2A**, £2, Order Ref 2P337.  
**15V 1A**, £1, Order Ref 267.  
**17V 1A**, £1, Order Ref 492.  
**18V 1/2A**, £1, Order Ref 491.  
**20V 4A**, £3, Order Ref 3P106.  
**24V 1/2A**, £1, Order Ref 337.  
**30V 2 1/2A**, £4, Order Ref 4P24.  
**36V 3A**, £3, Order Ref 3P14.  
**40V 2A**, £3, Order Ref 3P107.  
**43V 3 1/2A**, £4, Order Ref 4P14.  
**50V** fully shrouded, £5, Order Ref 5P139.  
**50V 15A**, £20, Order Ref 20P2.  
**90V 1A**, £4, Order Ref 4P39.  
**675V 100mA**, £5, Order Ref 5P166.  
**3kV 3mA**, £7, Order Ref 7P7.  
**4kV 2mA**, £5, Order Ref 5P139.  
**6-0-6V 10VA**, £1, Order Ref 281.  
**9-0-9V 5VA**, £1, Order Ref 661.  
**12-0-12V 2V 3VA**, £1, Order Ref 636.  
**12-0-12V 6VA**, £1, Order Ref 811.  
**15-0-15V 1VA**, £1, Order Ref 937.  
**15-0-15V 15VA**, £2, Order Ref 2P68.  
**18-0-18V 10VA**, £1, Order Ref 813.  
**20-0-20V 10VA**, £1, Order Ref 812.  
**20-0-20V 10VA**, £2, Order Ref 2P85.  
**20-0-20V 20VA**, £2, Order Ref 2P138.  
**20-0-20V 80VA**, £4, Order Ref 4P36.  
**36-0-36V 20VA**, £2, Order Ref 2P156.  
**90-0-90V 100VA**, £4, Order Ref 4P39.

## SPECIAL TRANSFORMERS

**15VA** gives 1%V, 7V, 8V, 9V or 10V, £1, Order Ref 744.  
**8V+8V 10VA**, £15, Order Ref 15P51.  
**38-0-38V 15VA** with regulator winding, £10, Order Ref 10P36.  
**250-0-250V 6mA** with 6.3V 5A additional winding made for valve circuits, £5, Order Ref 5P167.  
**230-115V** auto transformer 100VA, £2, Order Ref 2P6.  
**Ditto** but 10VA, £1, Order Ref 822.  
**Ditto** but 250VA, £3, Order Ref 3P142.  
**Ditto** but 1kVA, £20, Order Ref 20P.

## ISOLATION TRANSFORMERS

**230-230V 10VA**, £1, Order Ref 821.  
**230-230V 150VA**, £7.50, Order Ref 7.5P  
**230-230V** with adjustable tappings 250VA, £10, Order Ref 10P97.  
**440-240V 200VA**, £10, Order Ref 10P115.

## SELECTIVE BARGAINS

**Medicine Cupboard Alarm**. Or it could be used to warn when any cupboard door is opened. The light shining on the unit makes the bell ring. Completely built and neatly cased, requires only a battery. £3, Order Ref: 3P155.

**Don't Let it Overflow!** Be it bath, sink, cellar, sump or any other thing that could flood. This device will tell you when the water has risen to the pre-set level. Adjustable over quite a useful range. Neatly cased for wall mounting, ready to work when battery fitted. £3, Order Ref: 3P156.

**Solar Panel Bargain**. Gives 3v at 200mA. Order Ref: 2P324.

**Amstrad 3" Disk Drive**. Brand new and standard replacement for many Amstrad and other machines. £20, Order Ref: 20P28.

**Movement Alarm**. Goes off with the slightest touch. Ideal to protect car, cycle, doorway, window, stairway, etc. Complete with Piezo shrieker, ready to use, only £2, (PP3 battery not supplied). Order Ref: 2P282.

**AM-FM Radio Chassis**. With separate LCD module to display date and time. This is complete with loudspeaker, £3.50, Order Ref 3.5P5.

**20W 5" 4 Ohm Speaker**. Mounted on baffle with front grille, £3, Order Ref: 3P145. Matching 4 ohm 20W tweeter on separate baffle, £1.50, Order Ref: 1.5P9.

**You Can Stand On It!** Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools in, internal size approx. 10 1/2"x4 1/2"x6" high. Complete with carrying strap, price £2, Order Ref: 2P283B.

**Ultra Sonic Transducers**. Two metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref: 1.5P4.

You will receive our current newsletter and two lists giving details of well over 1,000 of our special bargains, with your goods when you order this month

**Philips 9" High Resolution Monitor**. Black and white in metal frame for easy mounting. Brand new, still in maker's packing, offered at less than price of tube alone, only £15. Order Ref: 15P1.

**Insulation Tester and Multimeter**. Internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges, AC/DC volts, 3 ranges DC milliamperes, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50, yours for only £7.50 with leads, carrying case £2 extra, Order Ref: 7.5P4.

**Mains Isolation Transformer**. Stops you getting "to earth" shocks. 230V in and 230V out. 150 watt, £7.50, Order Ref: 7.5P5 and a 250W version is £10, Order Ref: 10P97.

**0-1mA Full Vision Panel Meter**. 2 3/4" square, scaled 0-100 but scale easily removed for re-wiring. £1 each, Order Ref 756.

**40W-250W Light Dimmers**. On standard plate to put directly in place of flush switch. Available in colours, green, red, blue and yellow. £2.50, Order Ref. 2.5P9. Or on standard 3x3 cream metal switch plate, £3, Order Ref: 3P174.

**Touch Dimmers 40W-250W**, no knob to turn, just finger on front plate, will give more, or less light, or off. Silver plate on white background, right size to replace normal switch £5, Order Ref. 5P230.

**LCD 3 1/2 Digit Panel Meter**. This is a small multi range voltmeter/ammeter using the A-D converter chip 7106 to provide 5 ranges each of volts and amps. Supplied with full data sheet. Special snip price of £12, Order Ref: 12P19.

## POWER SUPPLIES - SWITCH MODE

(all 230v mains operated)

**Astec ref B51052** with outputs +12v .5A, -12v .1A, +5v 3A, +10v .05A, +5v .02A unboxed on pcb size 180x130mm, £5, Order Ref 5P188.  
**Astec ref BM41004** with outputs +5v 3 1/2A, +12v 1.3A, -12v .2A, £5, Order Ref 5P199.  
**Astec No 12530** +12v 1A, -12v .1A, +5v 3A, uncased on pcb size 160x100mm, £3, Order Ref 3P141.  
**Astec No BM41001** 110W 38v 2.5A, 25.1v 3A part metal cased with instrument type main input socket & on/off dp rocker switch size 354x118x84mm, £8.50, Order Ref 8.5P2  
**Astec model no BM135-3302** +12v 4A, +5v 16A, -12v 0.5A, totally encased in plated steel with mains input plug, mains output socket & double pole on/off switch size 400x130x65mm, £9.50, Order Ref 9.5P4.

## POWER SUPPLIES - LINEAR

(all cased unless stated)

**4.5v dc 150mA**, £1, Order Ref 104  
**5v dc 2 1/2A psu** with filtering & volt regulation, uncased, £4, Order Ref 4P63.  
**6v dc 700mA**, £1, Order Ref 103.  
**6v dc 200mA** output in 13A case. £2, Order Ref 2P112.  
**6-12v dc** for models with switch to vary voltage and reverse polarity, £2, Order Ref 2P3.  
**9v dc 150mA**, £1, Order Ref 762.  
**9v dc 2.1A** by Sinclair, £3, Order Ref 3P151  
**9v dc 100mA** £1, Order Ref 733.  
**12v dc 200mA** output in 13A case, £2, Order Ref 2P114  
**12v 500mA** on 13A base, £2.50, Order Ref 2.5P4  
**12v dc 1A** filtered & regulated on pcb with relays & piezo sounder, uncased, £3, Order Ref 3P80.  
**Amstrad 13.5v dc** at 1.8A or 12v dc at 2A, £6, Order Ref 6P23.  
**24v dc at 200mA** twice for stereo amplifiers, £2, Ref 2P4  
**9.5v ac 60mA** made for BT, £1.50, Order Ref 1.5P7.  
**15v 320mA ac** on 13A base, £2, Order Ref 2P281  
**AC out 9.8v @ 60mA & 15.3v @ 150mA**, £1, Order Ref 751.  
**BT power supply unit 206AS**, charges 12v battery and cuts off output should voltage fall below pre-set, £16, Order Ref 16P6  
**Sinclair microvision psu**, £5, Order Ref 5P148

## LASERS & LASER BITS


**2MW Laser**. Helium neon by Philips, full spec, £30, Order Ref: 30P1. **Power supply** for this in kit form with case is £15, Order Ref: 15P16, or in larger case to house tube as well £18, Order Ref: 18P2. **The larger unit**, made up, tested and ready to use, complete with laser tube £69, Order Ref: 69P1

## SOLAR CELLS & PROJECTS

**100mA solar cell**, £1, Order Ref 631.  
**400mA solar cell**, £2, Order Ref 2P119.  
**700mA solar cell**, £3, Order Ref 3P42  
**1A solar cell**, £3.50, Order Ref 3.5P2.  
**3V 200mA solar cell**, £2, Order Ref 2P324.  
**15V 200mA solar cell**, £15, Order Ref 15P47  
**Solar Educational Kit** with parts to make solar fan, £8, Order Ref 8P42.  
**Solar kits** - make vintage gramophone, £7.50, Order Ref 7.5P2  
Make helicopter, £7.50, Order Ref 7.5P17.  
Make monoplane, £7.50, Order Ref 7.5P18.

The above prices include VAT but please add £3 towards our packing and carriage if your order is under £25. Send cheque or postal orders or phone & quote credit card number.

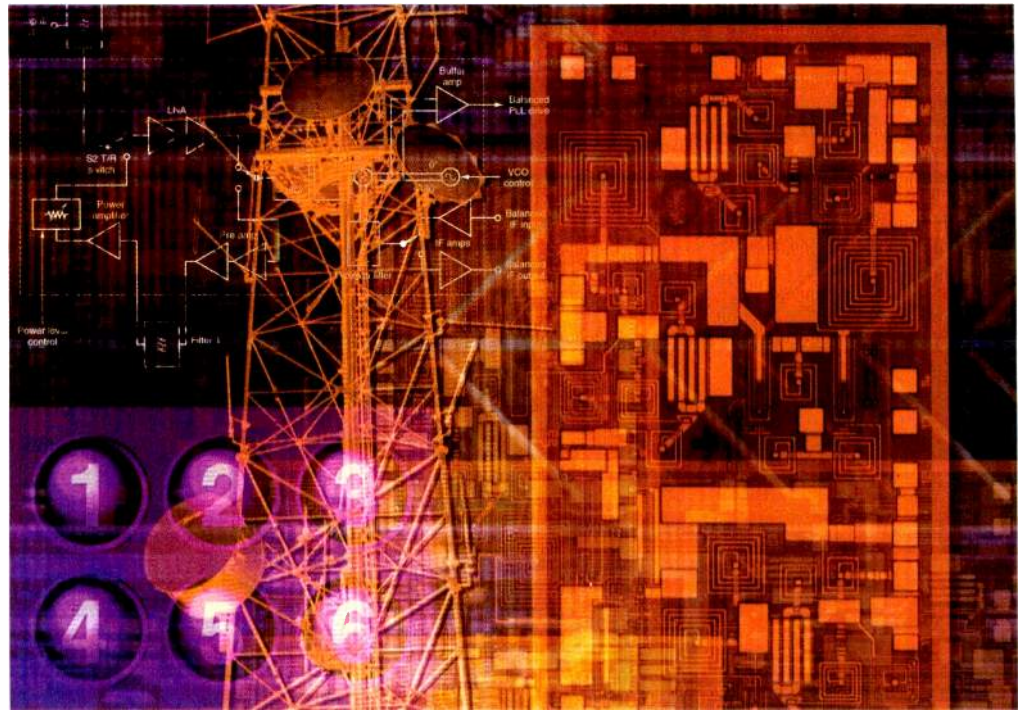**M&B ELECTRICAL SUPPLIES LTD**  
Pilgrim Works (Dept. WW),  
Stairbridge Lane, Bolney,  
Sussex RH17 5PA  
Telephone (0444) 881965 -  
phone for Fax  
Callers to 12 Boundary Road,  
Hove, Sussex.



# MICROWAVES

## 2: The laws of microstrip

**M**ost currently designed microwave circuitry is based upon microstrip transmission line. This consists of a conducting track separated from a ground plane by a dielectric layer. The electromagnetic fields propagate and interact but are confined to the region in the vicinity of conducting track and ground plane. One cannot, of course, confine 100% of these fields within the dielectric and some portion will extend into the air above the circuit. Besides affecting the propagation characteristics, such fringing fields will also couple to any adjacent portions of circuit. This latter effect is not always a disadvantage and, as we shall see later, enables a variety of passive components to be realised. **Fig. 1** shows the general structure of a transmission line.

The microwave circuit designer initially needs to know two main circuit parameters: the wavelength within the microstrip circuit (or, equivalently, the dielectric constant or the phase velocity) and the characteristic impedance of the transmission line. Unfortunately, although the configuration of the transmission line appears simple, the

**Microstrip engineering, more than any other technique, provides the foundation to modern microwave design.**

**Mike Hosking\* spells out the design rules which turn unwanted reactance into a positive asset.**

*Mike Hosking is a lecturer in telecommunications and microwaves at the University of Portsmouth.*

answers are deceptively difficult to obtain accurately.

Unlike waveguide or coaxial line, the conducting boundaries are not easily or uniquely definable and an exact synthesis can only be made using, typically, conformal mapping or finite element techniques. The results of such analyses are not convenient, closed-form design equations for engineering use and, in fact, much of the design effort over the past two decades has been spent on developing and improving such closed-form solutions derived from the larger models. The result has been a steady improvement in the accuracy to which circuit designs may be made and the evolution of comprehensive, internationally used CAD tools such as the *Eesof* (recently merged with H-P) and *Super Compact* suites.

The wavelength within the circuit itself (the guide wavelength) must be known, because all designs are based on the electrical dimensions of small sections of circuit. The essence of high frequency circuit design lies in the determination of the inductive, capacitive, or impedance transforming effects produced when an electromagnetic field 'sees' dimen-



sional changes in its transmission line. If all of the field was confined to the dielectric medium then the velocity of propagation, would simply be the velocity of light  $c$  divided by  $\sqrt{\epsilon_r}$  where  $\epsilon_r$  is the intrinsic dielectric constant (relative permittivity) of the substrate material. However, due to the fact that some portion of the field travels in air (for which  $\epsilon_r = 1$ ) an effective dielectric constant  $\epsilon_e$  must be used and  $\epsilon_e$  depends upon several circuit parameters, including frequency. All transmission circuits including free space, present an impedance to the electromagnetic wave, the characteristic impedance,  $Z_0$ . Its value must be known in order to design circuits with optimum power transfer and minimised internal reflections.

**Microstrip design equations**

The velocity of propagation, hence wavelength, within the microstrip circuit depends upon an effective dielectric constant  $\epsilon_e$ . In turn,  $\epsilon_e$  depends upon the proportion of field within the substrate to that travelling outside. Both of these depend upon the actual dimensions of the line, together with the substrate material and frequency. For example, we may intuitively appreciate that as the top conducting track becomes wider and wider, then more of the fields can be contained within the substrate. Conversely, for narrow lines, more of the field extends to the air. Thus, the effective dielectric constant must lie somewhere between the extremes of unity and the intrinsic value  $\epsilon_r$ .

In practice, the effects of frequency on  $\epsilon_e$  can often be neglected below 1 or 2 GHz and, in this case, we have a 'quasi-static' solution to the design (see further reading) where, for example:

$$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left[ 1 + \frac{10h}{w} - \frac{t/h}{\sqrt{w/h}} \right]^{-0.555}$$

within a certain range of  $w/h$  and  $\epsilon_r$ .

Thus, the guide wavelength is a function of track width and substrate thickness. For thin metal films, their thickness  $t$  can be neglected. Similarly, the characteristic impedance is also a function of  $w$  and  $h$ , shown graphically in Fig. 2.

As a design example, take the two cases of a 50Ω characteristic impedance microstrip line, one on a 1.25mm thick plastic substrate having  $\epsilon_r=2.2$  and the other on 0.125 mm thick GaAs having  $\epsilon_r=13.1$ . The former circuit would have  $\epsilon_e=1.9$  and a track width of 3.85mm, while the respective values for the latter would be  $\epsilon_e=8.4$  and  $w=0.09$ mm. At frequencies where dispersion must be taken into account (accuracies of <0.5% are usually required) the effective dielectric constant can usually be described by an expression of the form:

$$\epsilon_c(f) = \epsilon_r - \frac{\epsilon_r - \epsilon_c}{1 + P(f)}$$

where  $P(f)$  is a semi-empirical modelled term which varies with frequency.

At frequencies higher than those indicated


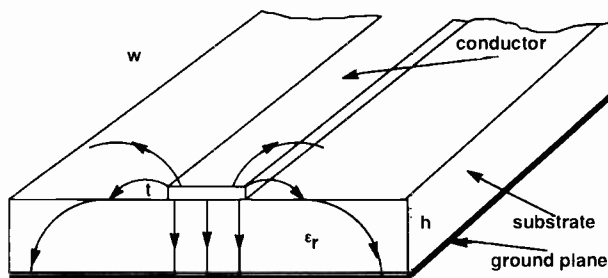


Fig. 1a. General form of microstrip transmission line, showing the electric field pattern with substrate and ground plane.

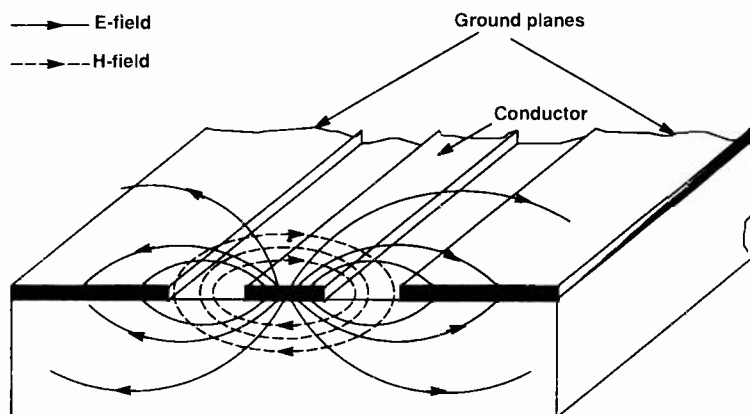

b. Coplanar waveguide, where conductor and ground planes are all on the same surface, showing typical field configuration.

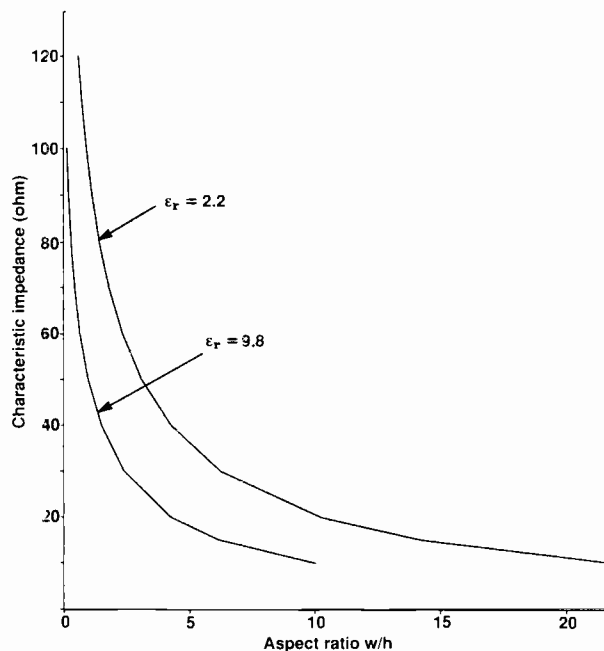


Fig. 2. Graphs of the characteristic impedance of a microstrip line as a function of the line width to substrate thickness ratio for two substrate dielectric constants. It shows that the line width decreases as  $\epsilon_r$  increases and that higher values of impedance require narrower lines.

above, account must be taken of what is termed dispersion. In addition to the wavelength changing with frequency, the actual propagation velocity of the fields changes as well.

Other important design parameters are the signal losses which occur within a circuit (caused by dissipative losses within the conductors), dielectric loss (caused by the substrate) and radiation loss. There is also an

upper frequency limit for microstrip, dependant on thickness and  $\epsilon_r$  beyond which a higher mode occurs; this would typically be above 100GHz. Finally, practical circuits must be packaged within some form of enclosure, the sides and top of which can modify their performance by interaction with the fringing fields. Such effects may either be taken into account from analysis of fields within a box, or by ensuring that the enclosing walls are

spaced far enough away from the circuit so as to avoid interaction.

**Substrate materials**

Virtuosity in circuit design accuracy would be of little account if not matched by a corresponding quality of manufacture, particularly in the area of substrate technology. Not only must a choice of materials be available, but

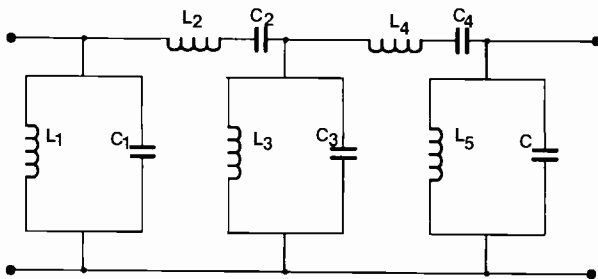
their dimensional accuracy, stability and homogeneity must lie within tight tolerances. Table 1 lists the dielectric constant and loss tangent for some of the more prevalent substrate materials. A wide range of the plastic materials is available. Many of these are based on PTFE, filled with either fine glass or ceramic, although irradiated polyolefin is also used.

**Table 1**

Material	Tand (10GHz)	$\epsilon_r$
PTFE/glass	$10^{-4}$	2.1-2.6
PTFE/ceramic	$4 \times 10^{-4}$	9-11
Alumina (AlO <sub>2</sub> , 99.5%)	$2 \times 10^{-4}$	9.8
Fused quartz	$10^{-4}$	3.8
Irradiated polyolefin	$5 \times 10^{-4}$	2.3
Sapphire (anisotropic)	$5 \times 10^{-5}$	9.4&11.6
Semi-insulating GaAs	$6 \times 10^{-4}$	13.1

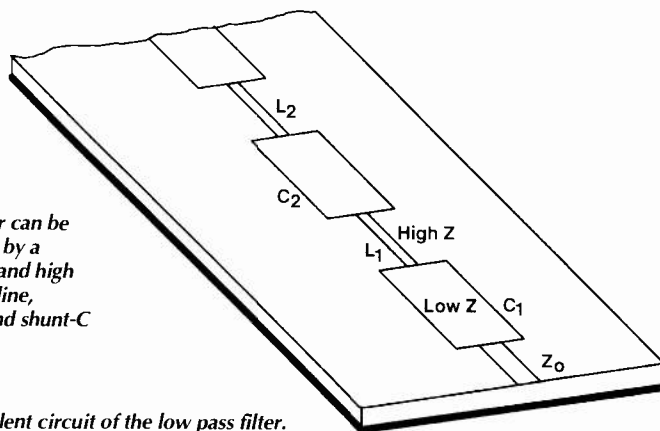


Fig. 3a. Four designs of an 18GHz microstrip bandpass filter on an alumina substrate. The length of each short section of line is approximately  $\lambda_g/2$  and the amount of overlap between adjacent lines is  $\lambda_g/4$ .




b. The bandpass filter equivalent circuit is realised in practice by the parallel resonances due to the  $\lambda_g/2$  sections and the series resonances caused by the coupling of the fields between lines.

Fig. 4a. A low pass filter can be produced in microstrip by a cascaded series of low and high impedance sections of line, appearing as series-L and shunt-C elements



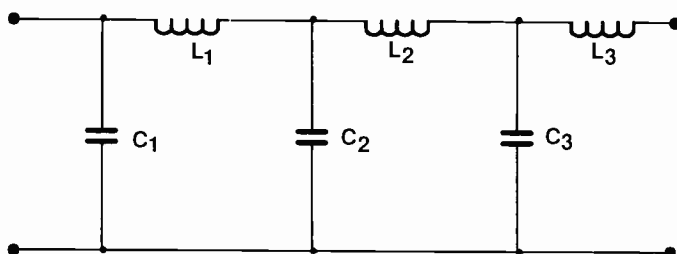b. Conventional equivalent circuit of the low pass filter.



**Reactance with a difference**

If we take a length,  $l$ , of transmission line having a characteristic impedance  $Z_0$  and we terminate the line with some impedance  $Z_L$ , where  $Z_L \neq Z_0$ , then a portion of any input signal will be reflected, due to the impedance mismatch. We can analyse the circuit in terms of those incident and reflected waves and may eventually express the input impedance (neglecting line losses) as:

$$Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] \dots 1$$

where  $\beta$  is called the phase constant  $= 2\pi/\lambda_g$  where  $\lambda_g$  is the guide wavelength.

Equation 1 leads to some very interesting results. Take the two extreme cases of making  $Z_L$  either a short circuit or an open circuit. In the former case,  $Z_L=0$  and equation 1 reduces to:

$$Z_{in} = j Z_0 \tan \beta l \dots 2$$

This is the expression for a pure reactance, the value of which depends on the length of line  $l$ . It can be seen that, for values of  $l$ , up to one quarter wavelength ( $l_g/4$ ),  $Z_{in}$  is inductive and can have any value between zero and infinity. From  $l_g/4$  to  $l_g/2$ ,  $Z_{in}$  becomes capacitive and can vary between  $-\infty$  and 0. A similar situation exists for an open circuit termination, for which  $Z_L = \infty$ . In this case  $Z_{in} = -j Z_0 \cot \beta l$  and may again take on any value between  $\pm\infty$  as  $l$  varies between 0 and  $l_g/2$ . Thus, we can make a capacitor or inductor from a simple length of open or short circuited transmission line. Two special lengths of line are also of interest: when  $l$  is a quarter wavelength (or odd multiples thereof) then equation 1 gives:

$$\frac{Z_{in}}{Z_0} = \frac{Z_0}{Z_L} \text{ or } Z_0 = \sqrt{Z_{in} Z_L} \dots 3$$

This is an impedance transforming function, as it has converted the load impedance  $Z_L$  into an admittance  $1/Z_L$ . Alternatively, equation 3 shows that the magnitudes of an input and output impedance may be matched by inserting a quarter wavelength section of transmission line between them, of a characteristic impedance equal to their geometric mean.

The other special length is when  $l = \lambda_g/2$ ; then  $Z_{in} = Z_L$ . In other words, we could move backwards from the load in half wavelength steps and it would appear as if  $Z_L$  was connected at these points. This is a useful aid in designing impedance matching circuitry, a fet amplifier for example, as the circuit elements need not all be crowded together (probably physically impossible anyway) at the actual terminals of the fet.

Actual circuit fabrication is usually a photo-etching process similar to normal printed-circuit board manufacture, the substrates being supplied with a 1/2oz or 1oz copper coating. High purity alumina is a popular substrate and can be obtained with gold metallisation on both surfaces ready for selective etching. Alternatively, screen printing using conductive thick-film inks which are then fired, may be used with alumina. Thick films are ultimately limited by the edge definition, due to the screen, but are successfully used to above 10GHz in frequency. In both of the above types of material, active devices such as diodes and transistors can be bonded to the circuits to produce hybrid components.

Monolithic circuitry with GaAs as the substrate requires a semiconductor manufacturing technology to produce deposited conductor patterns with diffused or implanted regions forming the active devices.

### Passive component design

The fact that the physical dimensions of microwave transmission lines are comparable in size to the wavelength itself (typically cm or mm) means that the very presence of a section of line, or of a change in dimension, can locally change the phase of the electromagnetic fields and can appear as inductive or capacitive elements. We thus have the concept of "distributed" circuit design. If a conventional type of lower frequency inductor or capacitor were placed into a microwave circuit, it would not behave in accordance with its value. It would appear rather as some complicated discontinuity with a complex equivalent circuit.

A further design technique makes use of the field coupling which occurs when two sections of microstrip line are brought close

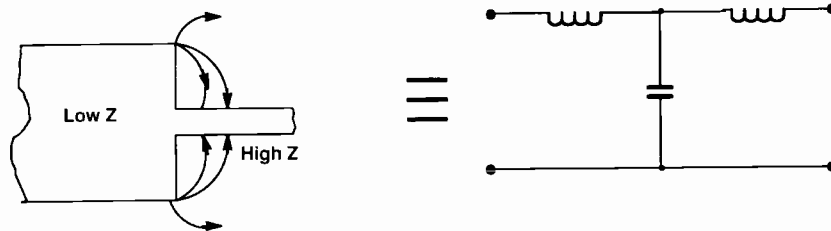


Fig. 5. An abrupt change in conductor width causes a local distortion of the electromagnetic fields to which it appears as an LC circuit in this example. Hence, reactive circuit elements may be produced from physical changes in the line geometry.

together. "Close" typically means between 0.025mm and 5mm depending upon the substrate material and the particular application. With a combination of these design tools, components such as resonators, low pass, high pass, band pass and band stop filters, hybrid directional couplers, power splitters, impedance matching networks and delay lines may be realised. All of these appear as innocuous lines on a substrate but are, in reality, the distributed counterparts of lower frequency discrete-element circuits.

As an example of a passive microwave circuit, Fig. 3a shows four microstrip bandpass filters on an alumina substrate operating at about 18GHz.

Each filter has the normal equivalent circuit of cascaded LC networks, as in Fig. 3b, and indeed, the individual filter elements are calculated in the same way as for lower frequency designs to provide bandpass responses such as Butterworth, Chebyshev, elliptic function; with a trade-off between stop-band attenuation, rate of cutoff, insertion loss and number of poles.

In Fig 3(a), each of the shorter lengths of line is approximately a 1/2λ long and appears,

electrically, as a parallel LC resonant circuit. Individual lines overlap each other by a nominal 1/4λ wavelength and mutually couple, thereby appearing as series LC combinations. In practice, an open circuit microstrip line radiates slightly and has fringing fields from the line ends, with the result that it appears slightly capacitive. Thus, a length correction must be made.


A slightly different approach to a filter design, in this case lowpass, is illustrated in Fig. 4a with its conventional, electronic equivalent circuit in Fig. 4b.

A length of microstrip line much narrower (high impedance) than another section of line loading it, will appear as a series inductance, whilst a wide (low impedance) section will appear largely as a parallel capacitance. Thus, the desired response can be produced by cascading L and C sections. One typical use of such a filter is in the bias circuit to an active device: dc connections have to be made without allowing the microwave signal to travel into the supply circuit or introducing mismatch.

In practice, this particular type of filter is restricted to frequencies below a few GHz due

Fig. 6. Four types of microstrip directional coupler in common use:

- a. A 90° hybrid branch line;
- b. A 180° hybrid ring ("rat race");
- c. Edge-coupled strip having a coupling dependant upon the gap;
- d. A Lange coupler used on wideband circuits, giving a 3dB power split with a 90° phase difference.

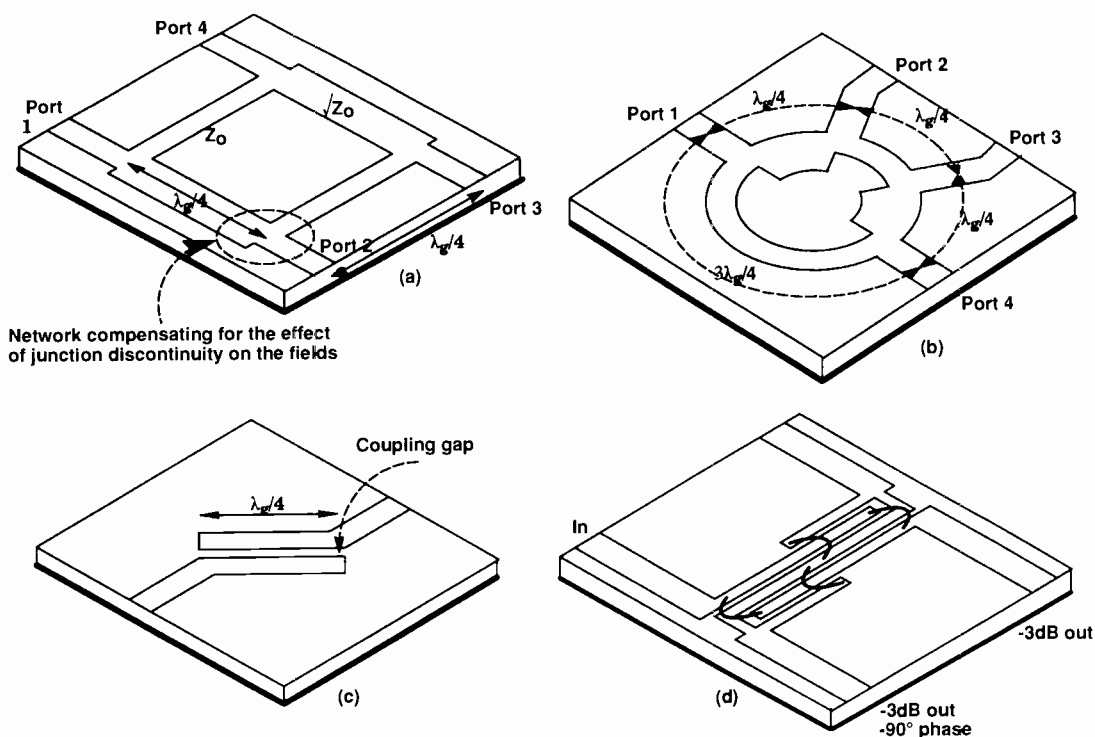

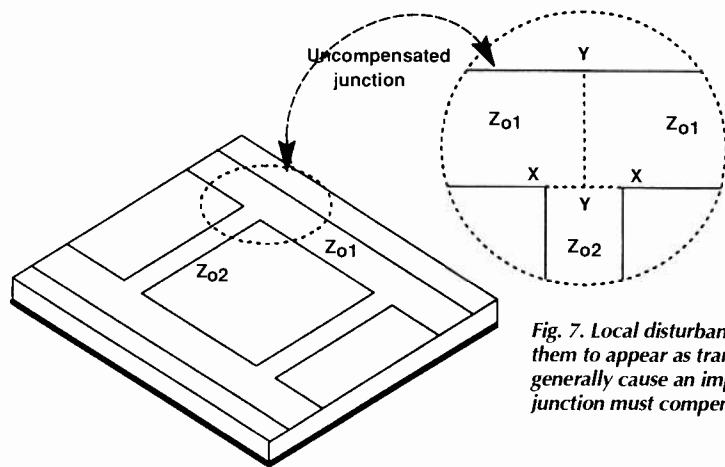


Fig. 7. Local disturbance of the fields at each T-junction causes them to appear as transformer-coupled LC circuits. This would generally cause an impedance mismatch and in practice, each junction must compensate for this with additional design detail.

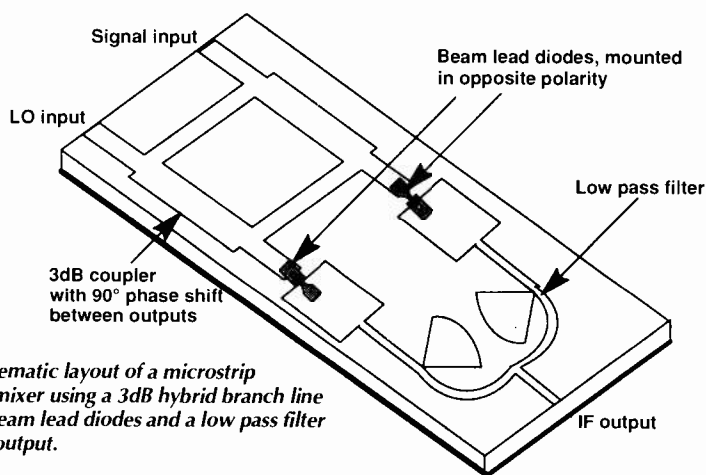
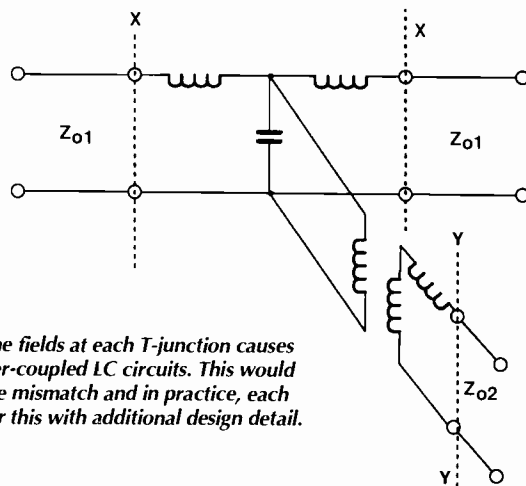


Fig. 8. Schematic layout of a microstrip balanced mixer using a 3dB hybrid branch line coupler, beam lead diodes and a low pass filter for the IF output.

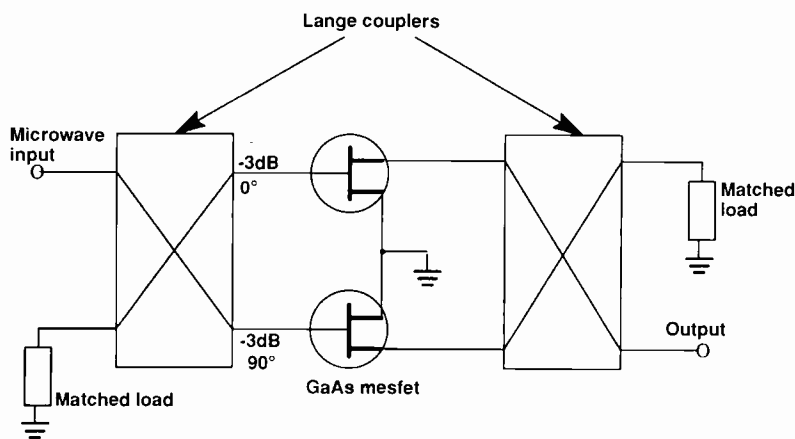


Fig. 9. A balanced amplifier configuration used for wideband circuits reduces the problems of internal mismatch and provides continuous operation should one fet fail.

to fringing fields from the step discontinuity. As shown in Fig. 5, these cause the local dimensional change to appear as another form of LC network, degrading the filter performance. This latter point serves to illustrate the fine detail which has to be taken into account in the design of high frequency circuits.

**Directional couplers**

This device is a basic circuit building block used in applications such as balanced, double balanced and image-rejection mixers, balanced

amplifiers and certain antenna feed networks. The coupler performs a power splitting function, ie one input and two outputs, but with usually a 90° or 180° phase shift between the two outputs. Fig. 6 shows four types of commonly used coupler in microstrip form.

Type (a) is a 90° hybrid branch line coupler so called because of its ability to provide an equal power split with a 90° phase shift between outputs. Each section of the coupler is normally  $\frac{1}{4}\lambda$  long and the branched design has the property that a signal input at Port 1,

say, will split equally with half going to Port 2 and half to Port 3. However, the output at Port 2 has travelled a distance of  $\frac{\lambda_g}{4}$ , while that at Port 3 has travelled  $\frac{\lambda_g}{2}$ , thereby introducing a 90° phase difference.

In practice, the T-junctions of the lines have an equivalent circuit shown in Fig. 7 and thus the local detail around the "T" must be altered, in order to introduce additional reactances for matching. Again, this is an example of the design detail required for microwave circuits.

This type of coupler is widely used in balanced mixer design, shown schematically in Fig. 8. The two mixer diodes are connected in opposite polarity and their outputs are combined via low pass filters to give the IF, while the overall effect of the phase shift introduced by the coupler is to produce cancellation of the local oscillator AM noise.

The coupler shown in Fig. 6b is also used in mixer circuits and is called a hybrid ring or rat-race coupler. A phase shift of 180° is introduced between outputs with, usually, an equal power split, although this can be changed by varying the characteristic impedance of the coupler sections.

An input at Port 1 will split equally, say, at the ring junction and the two components will travel in opposite directions around the ring. At Port 2, one component will have travelled  $\frac{\lambda_g}{4}$  and the other  $\frac{5\lambda_g}{4}$  so they will both be in phase at this port and will thus partially couple out.

At Port 3, one signal will have travelled  $\frac{\lambda_g}{2}$  and the other  $\lambda_g$  so they will be 180° out of phase and will cancel, giving no output.

At port 4, the two components will again be in phase and can, therefore, exit but, because they have travelled an extra  $\frac{\lambda_g}{2}$  compared with those at Port 2, the coupler outputs have a 180° phase difference.

Instead of forcing the microwave fields to split into two parts at a junction, couplers may be designed just by bringing two tracks into close proximity as in Fig. 6c. Even and odd mode waves are generated, each having a different impedance and phase velocity. The amount of coupling depends upon the proximity of the lines. However, it is difficult to



achieve a coupling of more than about -10dB.

The previous coupler types have the disadvantage that they are inherently narrow band designs, although the bandwidth of the branch line hybrid and side coupler can be increased by adding more sections at the expense of greater substrate area and insertion loss. A design which avoids these problems is the Lange coupler of Fig. 6d.

Of interdigital construction, it uses bond wires to equalise the even and odd mode phase velocities and gives a 3dB power split with a 90° phase difference between outputs. However, the big difference is that the amplitude and phase balance is maintained over frequency bands in excess of an octave, leading to widespread use in balanced amplifiers, as in Fig. 9. See also Fig. 4 in Part 1.

A microstrip receiver circuit which brings together several of these elements is shown in Fig. 10. The substrate is alumina, about 0.6mm thick and most of the tracks are 50Ω transmission lines. The hybrid ring style of mixer can be seen, with the microwave input signal passing through a coupled line bandpass filter. A single, edge coupled strip is used to sample power from an external source to provide the local oscillator signal. The discs in the foreground are bias magnets for circulators on ferrite substrates.

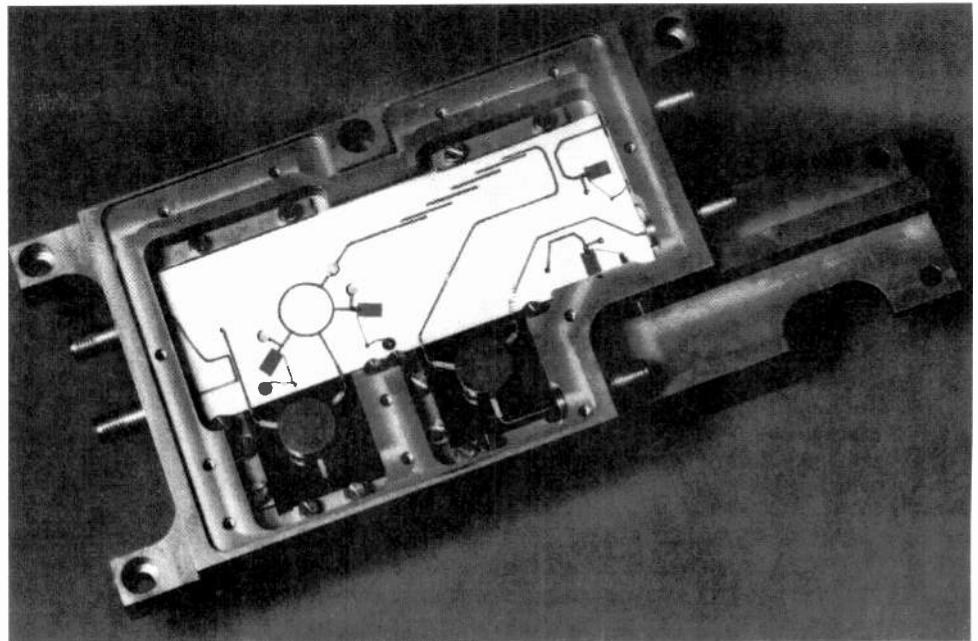


Fig. 10. A complete receiver circuit showing hybrid ring mixer, bandpass filter, edge coupled strips and ferrite circulators.

Further reading

Foundations for Microstrip Circuit Design, 2nd. edition, 1992, T Edwards, Wiley.

Next Month:

lumped components and waveguides.

**WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY**

**TEKTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200. PLUG-INS SOLD SEPARATELY**

TEKTRONIX 2235 Dual Trace 100MHz Delay Sweep.....	£800
PHILIPS 3065 2+1 Channels 100MHz Dual TB Delay Sweep	£700
TEKTRONIX 475 Dual Trace 200 MHz Delay Sweep .....	£550
TEKTRONIX 455 Dual Trace 200 MHz Delay Sweep .....	£450
H.P. 1715A Dual Trace 200MHz Delay Sweep .....	£500
HAMEG 605 Dual Trace 50MHz Delay .....	£400
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep.....	£400
TEKTRONIX SC504 Dual Trace 80MHz in TMS03 .....	£500
TEKTRONIX 2215 Dual Trace 60MHz Delay Sweep .....	£450
TEKTRONIX 455 Dual Trace 50MHz Delay Sweep .....	£400
INTACHI V605F Dual Trace 60MHz Delay Sweep .....	£400
TRIO CS1830 Dual Trace 30MHz Delay Sweep .....	£300
GOULD DS1100 Dual Trace 30MHz .....	£160
IWATSU SS5702 Dual Trace 20MHz .....	£225
GOULD OS300 Dual Trace 20MHz .....	£200
GOULD OS2500 Dual Trace 15MHz .....	£125
TEKTRONIX 2430 Dual Trace 150MHz Digital Storage .....	£1000
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep Analogue Storage .....	£450
H.P. 1741A Dual Trace 100MHz Delay Sweep Analogue Storage .....	£450

THIS IS JUST A SAMPLE. MANY OTHERS AVAILABLE

PHILIPS PM5193 Programmable synthesizer/function Generator 0.1MHz-50MHz IEEE-488. As new .....	£1500
MARCONI 2018 Synthesised AM/FM Sig Gen 80kHz-520MHz .....	£900
RACAL 9081 Synthesised AM/FM Sig Gen 1.5-520MHz .....	£800
EIP/DAMA 3510 Microwave Frequency Counter 20Hz-18GHz .....	£950
RACAL 9521 Frequency Counter 3GHz .....	£300
RACAL/DAMA 1931 Nanosecond Universal Counter .....	£300
RACAL 9302 Millivoltmeter True RMS 10kHz-1.5GHz .....	£450
RACAL 9301A RF Millivoltmeter True RMS 10kHz-1.5GHz .....	£300
RACAL 9009 Automatic Mod. Meter 10MHz-1.5GHz Wide Deviation .....	£250
LYONS PG73N Pulse Gen. PRF 1Hz-20MHz .....	£150
FARNELL P6G520H Synthesised Sig Gen AM/FM 100kHz-520MHz .....	£600
PHILIPS PM6309 Distortion Meter 0.01% .....	£300

**OTHER B&K EQUIPMENT AVAILABLE**

**SPECTRUM ANALYSERS**

HP 1411 with 8555A & IF Plug-in 10MHz-18GHz .....	£2000
HP 1411 with 8554B & 8552B 500kHz-1250MHz .....	£1300
HP 1401 with 8554L & 8552A 500kHz-1250MHz .....	£1000
HP 1411 with 8556A & 8552B 20Hz-300kHz .....	£1000
HP 1401 with 8553L & 8552A 1kHz-110MHz .....	£800
MARCONI TF2370 30Hz-110MHz .....	£1500
HP 1820 with 8558B 100kHz-1500MHz .....	£1500
HP 5582A 0.02Hz-25.5MHz .....	£2000

**Used Equipment - GUARANTEED. Manuals supplied if possible.**  
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

**STEWART of READING**  
110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
Telephone: (0734) 268041. Fax: (0734) 351696  
Callers Welcome 9am-5.30pm Monday to Friday (until 8pm Thursday)

**CIRCLE NO. 127 ON REPLY CARD**

# STEREO STABILIZER 5

- Rack mounting frequency shifter for howl reduction in public address and sound reinforcement.
- Mono version, box types and 5Hz fixed shift boards also available.

★ Broadcast Monitor Receiver 150kHz-30MHz.  
★ Advanced Active Aerial 4kHz-30MHz.  
★ Stereo Variable Emphasis Limiter 3.  
★ 10-Outlet Audio Distribution Amplifier 4.  
★ PPM10 In-vision PPM and chart recorder, also as expansion board for Acorn Computers.  
★ Twin Twin PPM Rack and Box Units.  
★ PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements.  
★ Broadcast Stereo Coders.  
★ Stereo Disc Amplifiers.

**SURREY ELECTRONICS LTD**  
The Forge, Lucks Green, Cranleigh, GU6 7BG  
Telephone: 0483 275997. Fax: 276477.

# CIRCUIT IDEAS


SEND YOUR CIRCUIT IDEAS TO THE EDITOR, ELECTRONICS WORLD, QUADRANT HOUSE, THE QUADRANT, SUTTON, SURREY SM2 5AS

**DO YOU HAVE A £100 CIRCUIT? EACH MONTH'S TOP CIRCUIT IDEA AUTHOR WILL RECEIVE £100. ALL OTHER PUBLISHED IDEAS WILL BE WORTH £25. WE ARE LOOKING FOR INGENUITY AND ORIGINALITY IN THE USE OF MODERN COMPONENTS**

**£100  
WINNER**
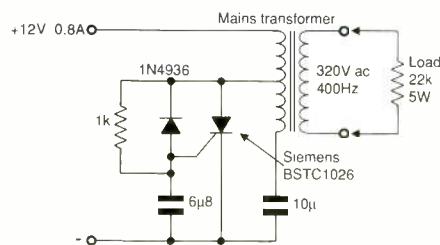
## SCR inverter

With one or two drawbacks, the saving grace of this single-SCR inverter is its simplicity. It produces a vaguely sinusoidal waveform of around 320V AC at 400Hz, the



*Very simple inverter, whose output is virtually unaffected by supply voltage, produces about 320V AC at 15mA.*


frequency being only slightly affected by supply voltage and load. Losses in the RS 209-847 transformer dictate an efficiency of 50% with a resistive load.

At switch on, oscillations must be allowed to build up slowly on a light load, since a heavy load would cause latch-up in the conducting state, necessitating some kind of current limiting.

The only variable is the resistor, which will affect the output voltage to some extent and allow lower or higher supply-voltage working. A lower frequency requires a larger resonating capacitor, which should not be an electrolytic type.

**D Di Mario**  
Milan  
Italy

## OTA oscillator

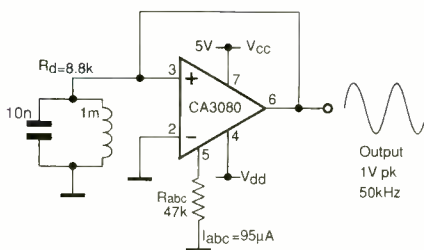

*Simple oscillator for up to 100kHz, using an operational transconductance amplifier to give a 1V pk output at 50kHz.*

In non-linear mode, an operational transconductance amplifier will function as an LC oscillator in the circuit originally described by Baxandall in 1959.

The parallel LC circuit on the non-inverting input of the 3080 OTA receives feedback from the output. At resonance, the tuned circuit appears as a resistive load  $R_d = 2\pi f_0 LQ$ . Bias current in the OTA, set by  $R_{abc}$ , determines  $g_m$ , which is about 2mA/V for an  $I_{abc}$  of 1mA. Oscillation at  $f_0$  takes place when  $g_m R_d > 1$ ,

increasing in amplitude until the amplifier limits, acting as a switch to drive constant  $I_{abc}$  and  $-I_{abc}$  into the tuned circuit, the waveform across it being sinusoidal with an amplitude of  $4R_d I_{abc} / \pi$  and third-harmonic distortion of  $(100/8Q)\%$ .

The circuit works to about 100kHz, although distortion rises at higher frequencies.

**J Willis**  
Macclesfield  
Cheshire


## YOU COULD BE USING A 1GHz SPECTRUM ANALYSER ADAPTOR!

**Got a good idea? Then this Thurlby-Thandar Instruments TSA1000 spectrum analyser adaptor could be yours.**

Covering the frequency range 400kHz to over 1GHz with a logarithmic display range of 70dB  $\pm$ 1.5dB, it turns a basic oscilloscope into a precision spectrum analyser with digital readout calibration.

Recognising the importance of good design, TTI will be giving away one of these excellent instruments every six months to the best circuit idea published in the preceding period until further notice. This incentive will be in addition to our £100 monthly star author's fee together with £25 for all other ideas published.

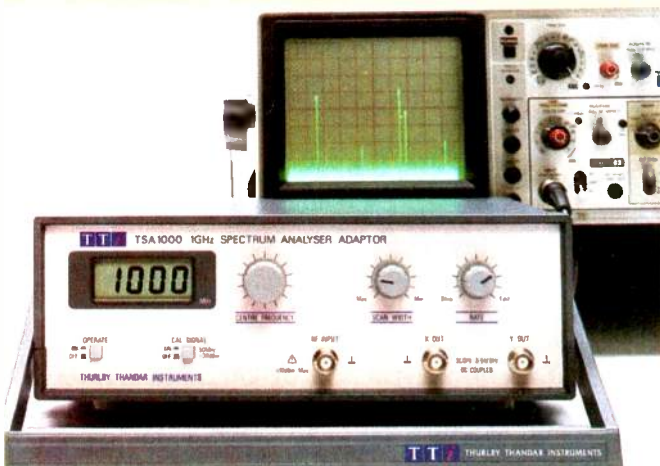Our judging criteria are ingenuity and originality in the use of modern components with simplicity particularly valued.



## Voltage-independent time delay

Although this is an RC time-delay, no adjustment is needed and supply variations have no effect, since such variations affect both inputs to a voltage comparator equally.

Input pulses cause a '1' at the output of IC<sub>1b</sub>, this being applied to the RC and to R<sub>2,3</sub>, so that

$$v_{C1} = v_1 (1 - e^{-t_0/R_1C_1})$$

$$v_{R3} = v_1 R_3 (R_2 - R_3)$$

Since the delay is determined by the time needed for v<sub>C1</sub> to become equal to v<sub>R3</sub>, solving that equation for t<sub>0</sub> produces



$$t_0 = -R_1 C_1 \ln(1 - R_3 / (R_2 + R_3))$$

where t<sub>0</sub> depends only on the RC combination, and voltage plays no part.

The diodes avoid the possibility of two zeros on the comparator inputs, when the input is zero. Inverting input is always high, since either IC<sub>1a</sub> output or IC<sub>1b</sub> output is always present.

**N I Lavrentiev**  
Kaliningrad  
Moscow Region  
Russia

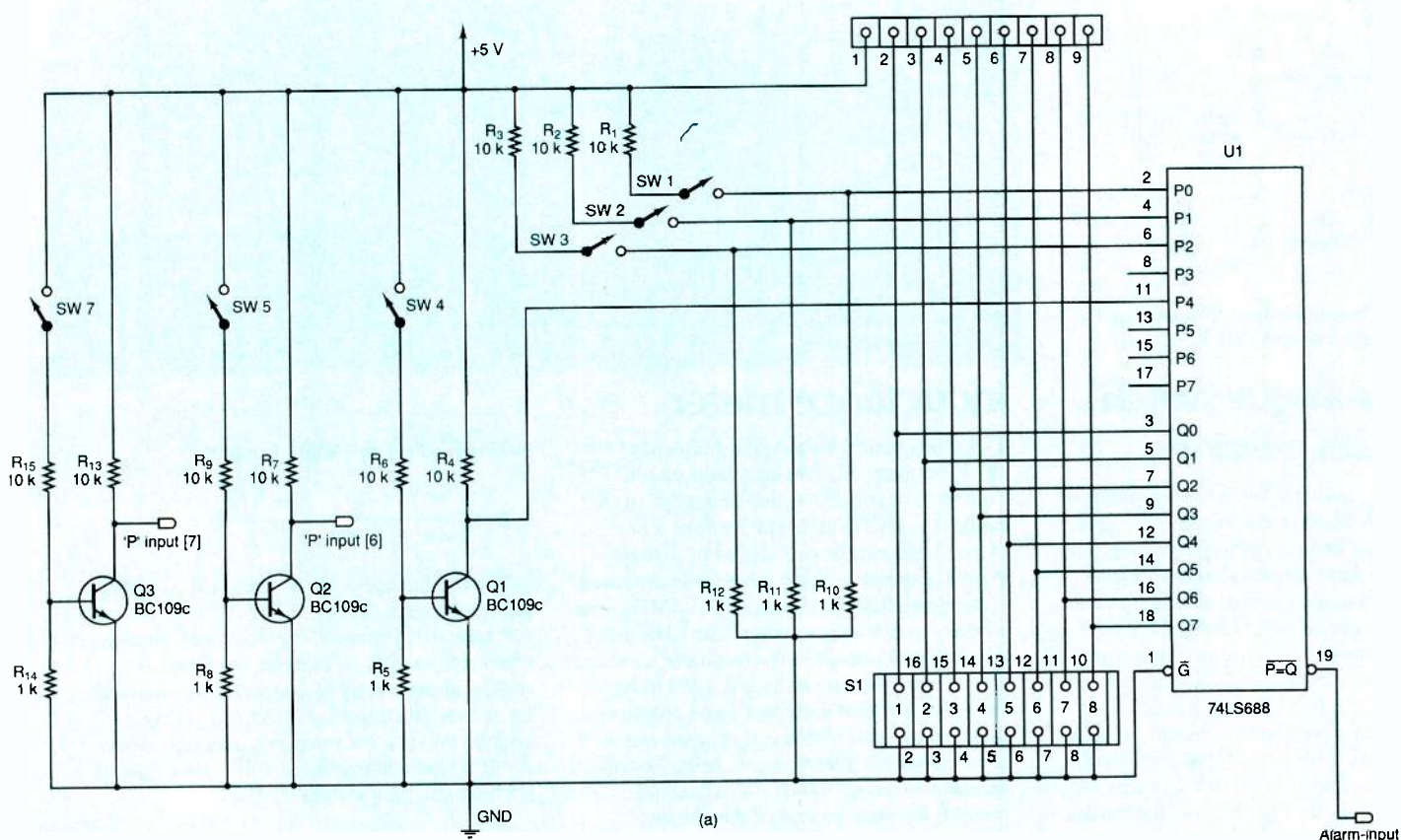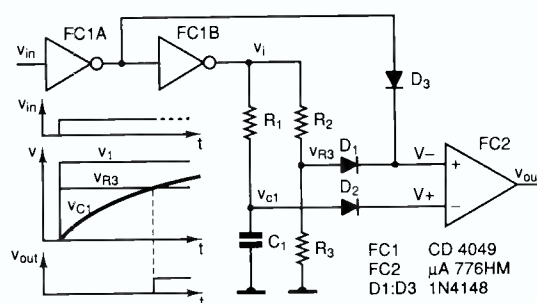*This time delay is independent of supply-voltage variations, even though delay is determined by an RC circuit.*



## Comparator extends alarm system

Several alarm sensors, presenting either normally open or normally closed contacts, are used as inputs to a digital comparator, which emits an enable to an alarm system when any sensor contact changes state.

A 74LS688 has two sets of eight inputs, P and Q, and one P = Q output; when all P inputs are equal to all Q inputs, P = Q is low, otherwise it remains high.


Any Q input may be set at 0 or 1 by the dil switches and the 10kΩ sil resistors. On the P side, normally closed contacts such as that on P0 pull the inputs high, an opened switch

taking the input low via its 1kΩ resistor. Normally open contacts allow transistor switches to provide normally high inputs to their P inputs, closing switches again taking the P input low; the use of transistors avoids trouble with varying supply voltages. For low-level sensors, the contact could feed the transistor base directly, as in (b).

Connecting eight 688s to a summing 688 would extend the number of possible sensors to 64.

**M Saunders**  
Leicester

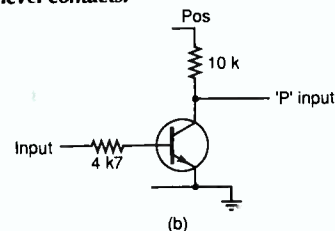*Up to eight contact sensors connected to one 74LS688 generate an alarm enable when one sensor is actuated, whether the sensors are normally open or closed contacts. At (b) is a simplified transistor feed for low-level contacts.*






## Variable-frequency generator has switchable duty cycle

At any frequency up to around 330kHz, the duty cycle of this generator is settable between 3:1 and 1:3.


Four stages of ripple counter 4040 drive the 74C154 16-line decoder, clock input to the 4MHz counter being divided by 12. When output 12 of the decoder goes low, it sets the output flip-flop, resetting the counter, which

starts to count again from zero. As the count reaches that corresponding to the decoder output selected by the switch, the flip-flop is reset. Maximum input frequency is about 4MHz.

**Alberto R Marino**  
Madrid  
Spain

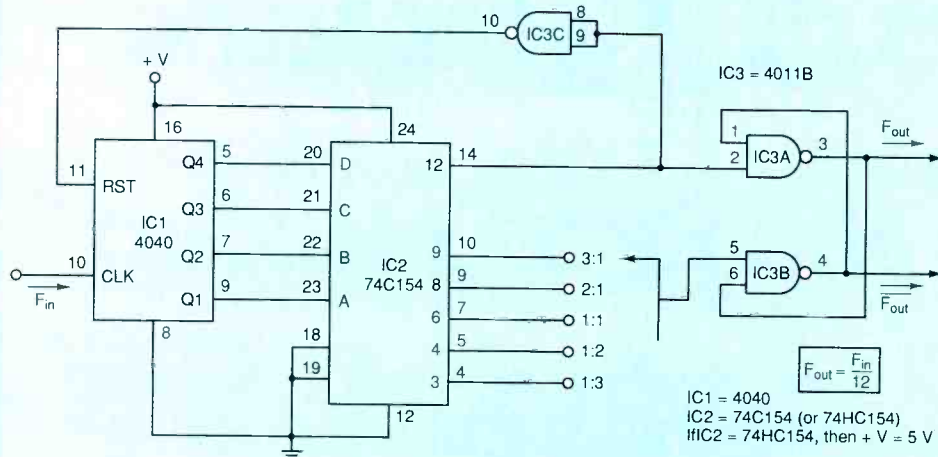

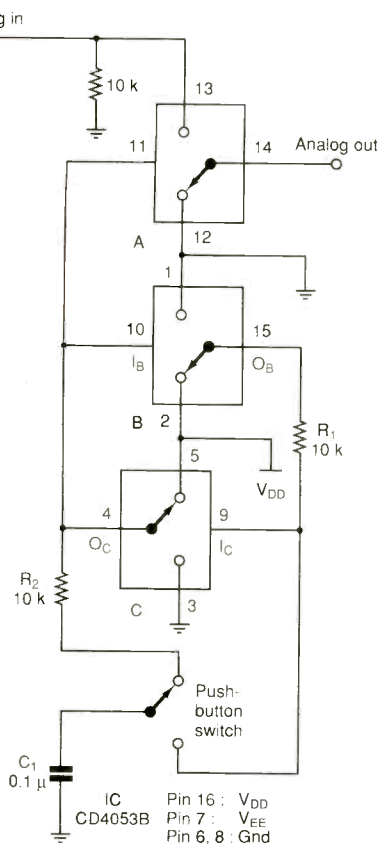At one-twelfth of the clock frequency, this rectangular-wave generator has a duty cycle selected between 3:1 and 1:3.



Push-button alternately opens and closes analogue switch.

## Analogue switch with memory

A push-button switch connects or disconnects an analogue signal in successive operations, using one IC, three resistors and a capacitor.

Analogue signals go through one channel of a 4053B three-channel multiplexer, the other two being connected as a bistable flip-flop so that outputs  $O_B$  and  $O_C$  are alternately 1 or 0. When  $O_C$  is 0, the capacitor is also at 0V; pressing the button connects it to the input  $I_C$  and triggers the flip-flop. As the button is released, the capacitor charges again to  $V_{DD}$ .

A second operation causes the capacitor to apply  $V_{CC}$  to  $I_C$ , which retriggers the flip-flop so that the capacitor is once again discharged when the button is released. Since the flip-flop is toggled each time the button is pressed, output  $O_C$  opens and closes the top channel to the analogue signal.

Requirements are  $V_{DD} = 5V-15V$ , negative supply  $V_{EE} = -13.5V-0V$  and  $(V_{DD}-V_{EE}) = 15V$  maximum.

**M S Nagaraj**  
ISRO Satellite Centre  
Bangalore  
India

## Inductance meter

When used with a digital frequency counter, this two-transistor circuit indicates inductance within about 5% in the range 0.1µH-2000µH. The reading is not direct, but a simple calculation or perhaps even a graph or look-up table gives the result.

An rf oscillator operating at 3.5-4MHz feeds a buffer to drive the counter. The terminals  $L_x$ , when shorted, result in the oscillator's natural frequency; connecting the unknown inductor increases the total inductance and produces a lower frequency, which is displayed and used to calculate the inductance.  $C$  being known. A receiver covering 300kHz-4MHz could possibly be used instead of the counter.

The value of the rf choke must be subtracted from the calculation, which, since the total value of the two 470pF capacitors and the


0.001µF comes to 190pF, becomes

$$L_x = \left( \frac{1}{4\pi^2 f^2 \times 190 \times 10^{-6}} \right) - 10$$

where inductance is in µH, frequency in MHz and capacitance in µF.

Practically, the usual rf precautions must be observed, namely rigid metal enclosure, regulated supply, good-quality capacitors, and the use of short, rigid connections. These include those to the unknown inductor. Any small-signal npn transistor will suffice and the rf choke can be a standard type.

**Peter Parker**  
Bentley  
Australia

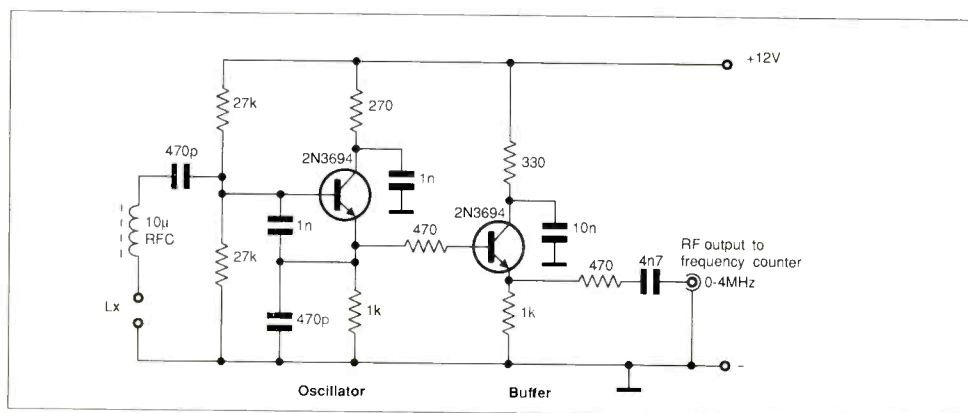



## Easy to use mains timer

Together with a thousand or so others, our household is currently part of an electricity tariff experiment. During the day, electricity is much more expensive than standard rate, at 12.6p a unit but in the evenings it drops to 5.6p and between 12:30 and 07:30 at night it is only 2.6p. This easy to use timer was designed to run the washing machine and dryer after 12:30 at night.


Two outlets are needed because the dryer and washer cannot be run together from one 13A socket. There is only one control, a switch, which allows manual selection of either of the two sockets. Switching to either resets the timer while switching back to the centre position initiates the timing sequence.

A red LED signals the timer's wait period while a green one signals the end of the cycle. Set up as shown, the first socket turns on

about 3h 40m after reset and stays on for just under an hour and a half, after which the second socket turns on for the same period. These periods mean that the timer can be initiated at any time between 8:53 and 12:55 in the evening. Using jumpers allows the on and delay periods to be altered.

Reset must be initiated in both switch positions to eliminate the possibility of having both sockets on at once, overloading the outlet. How long the capacitor can supply the CMOS ICs during mains failure is difficult to determine since connecting a voltmeter to the supply increases the discharge rate. It should be at least a few minutes.

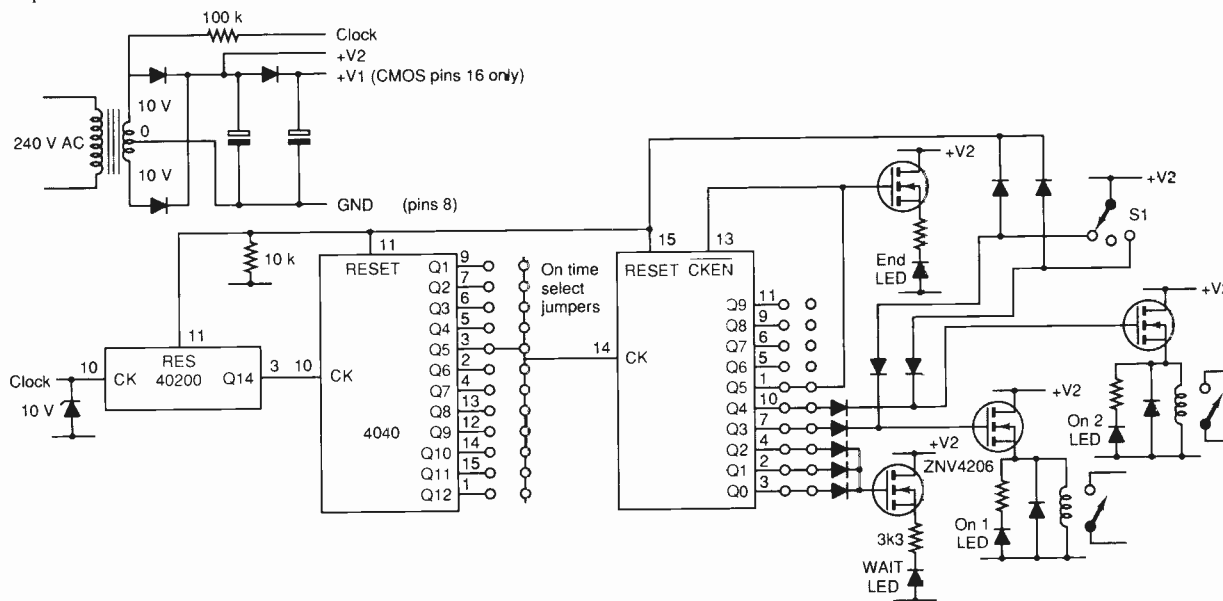**James Stevenson**  
Newcastle-u-Lyme  
Staffordshire



## Soft-start filament driver


Two power mosfets with a ramped gate voltage switch on slowly and eliminate a current surge into a cold filament.

The mosfets act as variable resistors, two charge pumps applying a slow-rising DC bias to the gates. Initially, the mosfets are off and the 22µF and 1µF capacitors charge through the 330Ω resistors and the internal drain/source diodes of the opposite mosfets. During this time, the load receives drive from one mosfet and the substrate diode of the other during each half cycle. When the capacitors are fully charged, both mosfets are on, voltage drop through the circuit being determined by the mosfet  $R_{DS(on)}$  of about 0.2Ω. The gate drivers give a slow charge, fast discharge characteristic.

Mosfets without the substrate diode can

be used, but must have a diode such as the 1N4002 between source and drain.

**Joel Setton**  
Crolles  
France

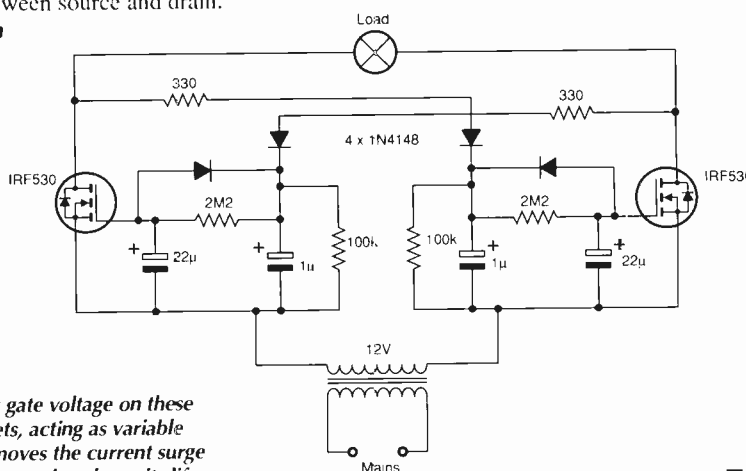

Slowly rising gate voltage on these power mosfets, acting as variable resistors, removes the current surge into a filament and prolongs its life.

# LETTERS

## Self challenges Duncan over hot audio

Having read Ben Duncan's article *Spirit of Bass* (*EW* + *WW*, February) I felt there were a few too many unsupported assertions to let them all go.

The alleged benefits of regulated supplies for power amplifiers may have been covered in some depth in previous articles, but this is different from proving that these benefits exist. Ben's previous contribution (*EW* + *WW*, October) concludes that distortion introduced by ripple and signal on supply lines is a serious problem. But to reach this conclusion he found it necessary to assume that the PSRR of the amplifier in question was about 25dB, which is unrealistically awful even for an unsophisticated circuit.

I question the statement that some sort of "envelope modulation" results between the 100/120Hz reservoir charging frequency and bass frequencies. This obviously occurs when an amplifier with an unregulated supply is driven into continuous clipping, but what has this to do with the finer nuances of

reproduction? I can think of no other way for such modulation to happen: perhaps Ben can enlighten me.

I also winced when I read that "bass clarity has been shown to be improved by... exchanging linear and 80kHz switching PSUs". Has it? When and by whom? And what definition of "bass clarity" are we using here? Is it intermodulation distortion, or something so magically non-measurable that only subjectivist hi-fi reviewers can perceive it?

However, my main concern is the reference to "thermal distortion" at the end of the article. Ben seems to take it as given that such a distortion mechanism exists in power amplifiers, but having studied the subject in some depth I have yet to see the effect, and frankly I don't think it exists.

I do agree that it happens in op amps, because of having output and input devices on the same chip, so there is very close thermal coupling between them. But this has nothing to do with amplifiers constructed from discrete devices. I note that his reference 13 deals with op amps only, and even then it seems necessary to measure the thermal

	10Hz AP out	Amp out	1kHz AP out	Amp out
<b>Fundamental</b>	.00013%	.00031%	.00012%	.00035%
<b>Second</b>	.00033%	.00092%	.00008%	.00060%
<b>Third</b>	.00035%	.00050%	.000013%	.00024%
<b>Fourth</b>	<.000002%	.00035%	<.000008%	.00048%
<b>Fifth</b>	<.00025%	<.00045%	.000014%	.00024%
<b>Sixth</b>	<.000006%	.00030%	.000008%	.00021%
<b>Seventh</b>	<.000006%	<.00008%	.000009%	.00009%
<b>Eighth</b>	<.000003%	.00003%	.000008%	.00016%
<b>Ninth</b>	<.000004%	.00011%	.000007%	<.00008%
<b>AP THD reading (80kHz bandwidth)</b>	.00046%	.00095%	.00060%	.00117%

**NB: The rejection of the fundamental is not perfect, and this is shown as it contributes to the THD figure.**

distortion effect at 1Hz, well outside the audio band.

While there have been odd mentions of thermal distortion in power amps in some of the hi-fi press, I have never seen any explanation of how it might work, any estimate of the magnitude of the effect, and a circuit that will

demonstrate its production.

In the usual absence of specifics, I can only assume that the alleged mechanism induces parameter changes in semiconductors whose power dissipation varies over a cycle. If this happens, it would presumably manifest itself as a rise in second or third harmonic distortion at very low frequencies, but this simply does not happen. The largest effects would be expected in Class B output stages where dissipation varies wildly over a cycle; the effect is still wholly absent.

One reason for this may be that drivers and output devices have relatively large junctions with high thermal inertia. A few minutes work with hammer and chisel revealed that an *MJE340* driver has a chip with four times the total area of a *TL072*. Given this thermal mass, parameters presumably cannot change much even at 10Hz. Low frequencies are also where the global NFB factor is at its maximum; it is perfectly possible to design an amplifier with 100dB of feedback at 10Hz, though much more modest figures are sufficient to make distortion unmeasurably low up to 1kHz or so. Using my design methodology, a blameless amplifier can be straightforwardly designed to produce less than 0.0006% THD at 10Hz (1.50W/8Ω) without even thinking about thermal distortion. I think this suggests that we have here a non-problem.

I accept that it is not uncommon to see amplifier TH plots that rise at low frequencies; but whenever I could investigate this, the LF rise could be eliminated by attending to either defective decoupling or feedback-capacitor distortion. Ben says he accepts the effect must be at a very low level as it is invisible at 0.0006%; remember that this is the level of a THD reading that is visually pure noise, though there are

## Virtual travel

Compared to previous booms in brown goods, the relatively highly priced camcorder may have been less exciting than video recorders or colour televisions. But the industry must look for a new product, and the buzz is about virtual reality.

A number of new technologies have appeared recently that can be put together to make a remarkable family of devices, which will probably be as near as we will ever get to Star Trek's transporter.

The initial or basic offering will be relatively crude and consist of a transmitter and receiver that can be plugged into telephone sockets anywhere. The receiver will be a virtual reality helmet, with stereo headphones and two video displays with arrangements to focus them as a stereo pair to the viewer. It will be connected to a box that decodes the video and audio data from the fractal compression system used to send it down the telephone system.

The transmitter will be a head sized object with binaural microphones and a pair of television cameras, and the data will be fed via a fractal compression unit to the telephone line. It will probably be sold at high prices to business users so that, for example, someone can be shown round an office or factory to decide whether they are sufficiently interested in buying it before visiting it in person.

Being shown round with this set up would be a bit like a quadriplegic being wheeled around in a wheelchair. Although you would have the feel of being there, you would have to look where your head was pointed.

The next development would be to arrange for the receiver to send to the transmitter signals representing the azimuth and bearing of the head, so that the viewer could turn his or her head around and look where he or she wants. But the head's location would still be moved by the people the other end. This would be more like a

paraplegic being wheeled around in a wheelchair.

The stage on from this would be to mount the head on a small airship-type flying machine, and set its computer to keep it at head height. Then directional signals could also be sent to it from the receiving person. I suggest that a flying machine would be easier and cheaper to make than a walking machine. The buoyancy could still be obtained by a cylinder, held vertically by its flight control system, equal in volume to a body and legs and it only need float a few inches above the ground. It may look a bit like an Dalek or animated dustbin, but it would do the job and should be easy enough to mass produce.

However, as it stands people would not be able to use this product to visit each other, as the person receiving the visit would still see the animated dustbin rather than the person.

But a simple trick could be used to get over this. A camera at the terminal of the subscriber making the virtual visit would record his or her appearance, and the person being visited could also wear a virtual reality helmet. However, this helmet would display the home image, except instead of the animated dustbin it would display the image of the person making the visit. It could not be impossible to edit out the VR helmets the two people would be wearing, so each would see the other as if they were a real person.

Of course there will be those who will suggest that this can never replace travel and it would be bad for the soul and so on. However, I can see no technical reason why it would not happen, and in reality it could well have uses to enhance travel rather than suppress it. Never again could the travel agent suppress the fact that the hotel is between the crematorium and the abattoir if customers expect a quick VR tour before laying out their money for the tickets!

**John de Rivas**  
Truro,  
Cornwall

real amplifier distortion products buried in it.

I have therefore done some deeper investigation by spectrum analysis of the residual, which enables the harmonics to be extracted from the noise. The test amplifier was an optimally biased Class B machine very similar to that in part 7, except with a CFP output. The Audio Precision oscillator is very clean but this amplifier tests it to its limits, and so the table shows harmonics in a before-and-after-amplifier comparison. The spectrum analyser bandwidth was 1Hz for 10Hz tests, and 4.5Hz for 1kHz, to discriminate against wideband noise.

This further peeling of the distortion onion shows several things: that the Audio Precision is a brilliant piece of machinery, and that the amplifier is really quite linear too. However, there is nothing resembling evidence for thermal distortion effects.

As a final argument, consider the distortion residual of a slightly underbiased power amp, using a CFP output configuration so output device junction temperatures do not affect the quiescent current. It therefore depends only on the driver temperatures. When the amplifier is switched on and begins to apply sine wave power to a load, the crossover spikes (generated by the deliberate underbiasing) will be seen to slowly shrink in height over a couple of minutes as the drivers warm up. This occurs even with the usual temperature compensation system, because of the delays and losses in heating up the  $V_{be}$  multiplier transistor.

The size of these crossover spikes gives in effect a continuous readout of driver temperature, and the slow variations seen imply time constants measured in tens of seconds or more. This must mean a negligible response at 10Hz.

There is no doubt that long-term thermal effects can alter Class B amplifier distortion, because as I have written elsewhere, the quiescent current setting is critical for the lowest possible high-frequency THD. However, this is strictly a slow (several minutes) phenomenon, whereas Duncan's comments about "even-harmonic residues" show that he is thinking of the usual sort of per-cycle distortion.

The above arguments lead me to conclude that thermal distortion as usually described does not exist at a detectable level. Nonetheless, if anyone has any hard evidence in rebuttal, I would be interested to hear it. Subjectivist impressions, however, are not required.

**Douglas Self.**  
Forest Gate,  
London

## Duncan replies

Douglas Self is being economical with the facts. Regulation improved the %THD+N performance of the amplifier for which I developed the regulator (see Fig. 2, p822, *EW + WW*, October 1992), by up to tenfold above 1kHz.

His guidance on PSRR, while correct in the circumstances, has no relevance to the topology I used (the driver stage had a 100% separate and ground isolated regulated supply) and having many years' experience in power audio, I resent any implication that my 0V nodding or NFB takeoff were anything other than blameless, long before I even considered improving performance with a regulator.

At 650W/4 $\Omega$  the amplifier in question also had considerably larger currents flying about and regulation dramatically cleaned up residue on the supply wires, which makes the black art of lead dress and twist less of an issue, opening new possibilities for ultra-compact packaging of high power without runaway noise induction.

More generally, Douglas is attempting to show that supply regulation is just not needed – ever, without even trying it, and based on idealised experience with just one classic topology. Simultaneously, he implies it has never been needed. The latter appears to be an unsupported assertion of his own, as he shows no measurements of PSR vs frequency or the supply residue of commercial products.

My -25dB PSRR figure was clearly intended as a worst case baseline at 20kHz, and not a wholly unrealistic one with some topologies and real-world PSR-reducing compromises found in PA and up-market hi-fi amplifiers.

Douglas Self has shown supply regulation may not be needed to get quite low static %THD+N figures when driving an 8 $\Omega$  resistor with his own idealistically laid out 50W development of the Lin topology (1956). But where are those measurements demonstrating the extent to which the blameless performance won't be disrupted by RFI on the mains supply or perturbations caused by the transient demands of a hungry, capacitive loudspeaker?

Self's own words are forked, if, as he says in part 1, a power amplifier really is just an op-amp with boots on. So if all power amplifiers can work blamelessly with a raw supply, then why does he and everyone else bother to use regulated supplies for IC op amps in, say, mixing consoles?

Concerning improvements in bass clarity, the MSL-Rauch P600 is a 600W/4 $\Omega$ /channel amplifier with an

80kHz switching supply, but otherwise its audio path replicates Rauch Precision's older DVT 250's model, which has a conventional supply.

Both amplifiers have had an enduring presence in the UK and European live performance, rehearsal and recording studio circuit, and over the past seven years, a number of experienced sound engineers have noted the improved sonics when changing between the two models.

Subjectivists yes, but also top professionals, and here Douglas ignores reality if he cannot accept that humans necessarily have the final say about equipment intended to communicate with most people who have a right brain, capable of measuring music – something machines are still too daft to even recognise.

As the improvement occurs across a wide range of units, artistes, microphones, venues and speaker systems, it has been robustly demonstrated. The relative absence of 50Hz harmonics and intermod products goes some way to accounting for differences. These and others can doubtless be identified and validated, if someone wishes (is Douglas volunteering?) to sponsor the research effort.

As to looking for thermal distortion in monolithic ICs, the JG Graeme test I cited naturally uses 1Hz to create a fairly gross (say > 3%) error for visibility's sake on a curve tracer, and to overcome display hysteresis. As most low to mid market domestic power amplifiers are nowadays monolithic ICs, the very kind of thermal distortion that even Douglas Self admits is more rife than ever!

Inside his own discrete circuitry, my adversary is wasting his time looking for thermal errors by minutely analysing harmonics with a uniform low crest test signal – and in sluggish output devices of all places.

His figures merely demonstrate that any thermal distortion is not contributing much to %THD with a specific topology and specific devices. This is not the same as proving it doesn't exist, ever, anywhere. Showing that 10Hz %THD did or did not change when the device's thermal inertia is say quadrupled, would be more daring.

If Douglas scrutinised the hated hi-fi press more carefully, he might gather that thermal distortion is the industry's best working hypothesis with regard to certain A-B tests between notionally equivalent components.

Superb as it is, the Audio Precision SYS-22 is completely the wrong tool for this kind of detective

assignment. Measuring a heat wobble will happen one day; wait until the professionals get there.

Turning over fully to Douglas Self's own series, it on the one hand deserves praise for writing style and content, for engineering pragmatism and clarity of thought, for organising formerly sporadic, diverse and oft half-baked information into simplicity, and not using the infamous seasickness capacitor location to compensate. His series is indeed excellent stuff for teaching.

But anyone bothered about musical accuracy should be cautioned that Self's entire presentation is limited to honing the original transistor amplifier topology for minimum static %THD+N. His reductionist shears have cut too far. I understand the profound satisfaction he gets from steady linearity, and it may have been smart electronics two decades ago when the Space Shuttle was on the drawing board, but today, the real audio design process hasn't even begun.

By the time a truly modern design (likely employing one of the other, more recent, principal topologies with very different rules) has been optimised according to listening tests and %IMD, %DIM and the various AP, Belcher, NMR and other SOTA DSP-based measurements, and after real world requirements like packaging and making it abuse proof have been attended to, then the %THD+N residue will likely be adjusted away from its minima.

**Ben Duncan**  
Lincoln

## Diagram as a language

I agree with your editorial remarks in the March issue. It is indeed a pity that the circuit diagram is so rarely accorded its true status as a powerful language.

It can be used at many different yet compatible levels from the briefest block diagram representing a whole system at one extreme to a complete schedule of parts at the other.

Even the final board layout is no more than a topological transformation of the same set of relationships.

Circuit sketches enable instant communication of ideas in a manner that has no equal.

Attempts to replace the concept are to be welcomed if they offer at least the same virtues, but so far have been no more successful than those intended to replace the similarly highly developed and subtle representation of music by a printed score.

**RH Pearson**  
Bourne, Lincs

## Sagnac sensors

It may be relevant to mention that the Sagnac effect (1913), referred to by Gerardus Bouw (*EW + WW*, March), is the basis of the laser gyro and other rotation sensing devices.

A laser beam is split into two parts, which are sent in opposite directions round a common optical transmission circuit. Rotation of the structure causes an apparent lengthening of the transmission path in one direction relative to the other (actually a transmission time difference).

This changes the interference pattern between the two sets of coherent light waves and the result is sensed by a photoelectric detector.

**Tom Ivall**  
Staines, Middlesex

## c the light

Martin Berner's question (*EW + WW*, March) on relative speeds versus the light barrier can be best understood by considering the velocity of a particle in three dimensions.

If the particle travels at  $c$  in each direction the classical result would be to add the squares and take the square root, resulting in a speed faster than  $c$ .

By contrast the correct relativistic calculations result in the overall speed being  $c$  - effectively one can

travel at  $c$  in each direction and still only be travelling at  $c$ . Also there is nothing wrong with having two observers whose relative velocity exceeds  $c$ , the result will only be that they cannot communicate with any device limited to  $c$ , like a photon.

Changing subject, AJ Quinton (*EW + WW*, March) is on the right lines with his ideas about linking permanent magnets and superconductors, but misses the point in connecting with room-temperature effects.

Magnetism is caused by charges in motion, and to have a north and south requires an area to be traversed by such charges. If one takes the simplest area - that of the circle - and the simplest particle with a magnetic field - the electron, then I would argue that the electron consists of a number of smaller particles, all chasing each other around the circumference of a circle. This would be, in effect, a permanent magnet and a superconductor at any temperature.

**Mike Lawrence**  
Montgomeryshire

## O frabjous days

I am surprised by the neo-rejectionism of modern physicists put forth in your magazine.

Anyone who listens to Lewis

Carroll, Monty Python and Douglas Hofstadter will most likely contend that everything is screwed up nowadays and that there must be something wrong with a scientific theory that doesn't contain some seemingly paradoxical feature.

This reaction coincides with the closure of all Israeli universities until the end of this semester because the new so-called socialist government tried to reduce the salary of professors, who of course were too intelligent to accept this offer.

Some loony Chabadnik named Amnon Goldberg (I hope he's not a relative of Barukh Goldstein's because he might kill me for this) insinuates that many attempted proofs of the theory of relativity have been shown to be based on fudged evidence. Well I suppose that if physicists keep eating fudge while making measurements, the chewing activity and high sugar content of the fudge may distract their attention from the correct adjustment of their instruments.

Fortunately for physics, no experiment is taken for granted by the scientific community unless it is repeatable in all laboratories.

You are certainly prejudiced if you think that Newton's theory of gravitation has been proven to be universally valid, or even that this validity isn't inflicted with paradox.

I was once told by a nuclear physicist that Newton's formula conflicts with the hypothesis that the universe is uniformly filled with matter. If a stone is dropped, the gravitational attraction from stars can certainly be neglected by approximation, and the more distant they are the less their influence.

But near space is not typical of the universe in general. If spherical shells are considered, the mass contained in those shells grows quadratically with distance while gravitation grows inverse quadratically. The net effect of these shells when integrated over the entire mass contained in the universe is to counteract the interaction of the system of the stone and the Earth almost entirely so that the observed constant of gravity must be less than the real by a factor of 50, as was already calculated by Laplace (or was that Poincaré).

He made the same argument re the dispersion of sunlight in the universe. I have been unable to find these statements anywhere in university textbooks on physics, but as it probably is correct, Einstein may very well have had this in mind when he devised his general theory of relativity.

**Michael Williams**  
Beth Shemesh, Israel

## Short agreement

Regarding your editorial comment on VHDL in March issue: Here! Here!

**Richard Ashwell**  
Newbury, Berkshire

## Life is easier with Dos

Jason Ross (*EW + WW*, April) claims naive users have less to remember with Windows and will find it much easier to use than Dos.

In fact a well designed Dos system is far easier to use. It also avoids the confusing and cluttered Windows screen and the difficulties of memorising the meanings of small differences between numerous icons. Icons may be fine for work involving a narrow range of software but are hardly ideal for users with wide and complex interests.

My systems use a single small control file M.bat - I find 8K sufficient. This automatically displays a full screen descriptive menu of 36 subject groups - on booting or at any time from any point in the system by typing M.

This method potentially eliminates the need to remember or type any file names or Dos commands.

A single character - figure or letter - identifies each menu item. Typing the chosen item - for example M B - either runs a program, performs a system operation, lists a full or partial directory tree, lists a directory in alphabetical order or displays a secondary menu with similar facilities. Menu choices may combine these and other possibilities in most combinations.

The method allows the user an efficient structure to describe any requirement simple, specialised or highly complex.

Secondary menus - with two character codes - permit more than 1,000 choices. Tertiary menus - using three characters - expand to 30,000 or more.

Major uses obviously go into the primary directory. The user has no need to remember any details but may at any time go direct to any point in the whole menu tree by typing the appropriate short menu code in full.

Joel Sciamma (*EW + WW*, April) asks why bother about saving a few milliseconds. The greatly increased speed of systems not using a gui can allow real time operation for many program operations, without killing time waiting for completion. At the other extreme gui slowness may mean the expense of extra computers to meet a work load.

**RG Silson**  
Tring, Herts



# NEW PRODUCTS CLASSIFIED

## ACTIVE

### Asics

**3V embedded array.** Toshiba's new 0.5µm cmos embedded array combines the functionality and performance of standard cells with the faster turnround times of gate arrays. With a typical gate propagation delay of 0.25ns and gate power consumption of 2.2µW/MHz, *TC180E* outperforms 0.8µm 5V asics on 3.3V supplies. The device contains up to 340,000 usable gates. Toshiba Electronics (UK) Ltd. Tel., 0276 694600; fax, 0276 691583.

**Multi-product wafers.** A capability known as Multi-Product Wafer (MPW) Train in 0.8, 1, 1.2 and 2µm cmos and 1.2µm BiCMOS is being used by Austria Mikro Systeme to allow the processing of several different devices on one wafer. Development charges are thereby reduced by up to 50% and AMS points out that, at a small extra cost, customers can have several versions of a design at once, saving waiting time for evaluation. AMS takes a tape from the customer and delivers finished, packaged parts. Austria Mikro Systeme International. Tel., 0276 23399; fax, 0276 29353.

### A-to-D and D-to-A converters

**Stereo codecs.** *AD1847* and *AD1846* single-chip, sigma-delta, stereo, digital audio codecs from Analog both support the Windows Sound System 2.0 and Compaq Business Audio. The 1847's serial port allows direct interface to a DSP or system i/o chip, needing fewer pins than a parallel port and costing less. *AD1846* is a reduced-cost version of the *AD 1848K* industry standard Soundport and is pin and register-compatible, offering

**Linear integrated circuits.** Two new voltage-feedback op-amps from National, the *LMC6572* and *LMC6574* dual and quad devices, were released early in the year and are intended for use in current-to-voltage conversion or amplification in mobile radio or instrumentation. They offer 2.7V and 3V operation at 40µA for each amplifier, an input current of 20fA and 120dB gain on a 2.7V rail.

These amplifiers are therefore well suited to battery power and will cope with either 3.3V digital logic regulated supplies or unregulated rails. Since the output swing is virtually rail-to-rail, within 20mV of the supply with a 5kΩ load, enhanced signal-to-noise ratio and dynamic range make the devices highly suitable for interfacing with A-to-D converters. They will drive heavy loads and their high voltage gain reduces the need for cascaded amplifiers, resulting in better accuracy. Both amplifiers have guaranteed performance over the -40°C to 85°C temperature range and are available in 8-pin and 14-pin plastic dips and 8-pin or 14-pin plastic SOICs. National Semiconductor GmbH. Tel., 01049 814110382; fax, 01049 814103515.

up to 70dB of dynamic range. Both devices provide CD-quality audio on an ISA or EISA add-in card. Analog Devices Ltd. Tel., 0932 253320; fax, 0932 247401.

### Discrete active devices

**Low-resistance power fets.** Two new TO-220 Hexfet power mosfets by International Rectifier, the 30V *IRL2203* and the 50V *IRL3705* offer  $R_{DS(on)}$  values of 10mΩ and 12mΩ respectively, both devices operating from a 5V logic-level drive as well as the standard 10V. International Rectifier. Tel., 0883 7132\*5; fax, 0883 714234.


**Dmos power mosfets** In the 14-member *NDS9XXX* family of dmos power mosfets from National Semiconductor are single and dual n-channel and p-channel types and complementary n-p dual mosfets. All are in SO-8 surface-mounted packages and the devices are pin-to-pin compatible with other SM dmos mosfets, but with better performance at 4.5V  $V_{GS}$ . National Semiconductor. Tel., 01049 8141 103300, fax, 01049 8141 103515.

**Switching diode.** A fast silicon epitaxial switching diode from ITT, the *BAL99*, has a leakage current of only 2.5µA at 70V and a recovery time of 6ns. Forward voltage at 1mA is 0.715V and 1.25V at 150mA. Power dissipation is 350mW at up to 25°C ambient. The diodes are designed for automatic insertion. ITT Semiconductors. Tel., 0932 336116; fax, 0932 33148.
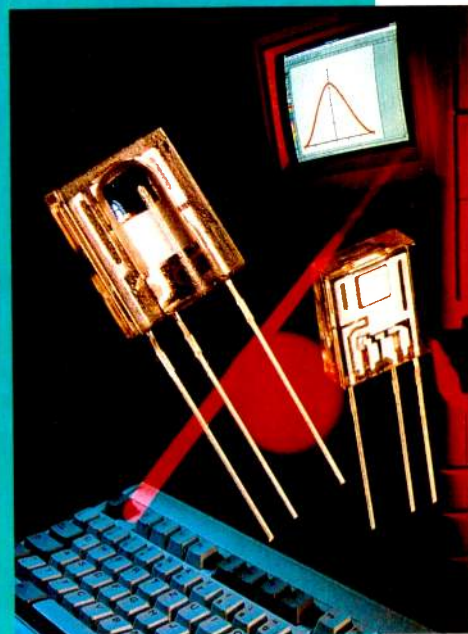
### Linear integrated circuits

**3V low dropout regulators.** Four new low-voltage, 100mA micropower, low dropout regulators from National feature 380mV dropout voltage at full load. *LP2950-3.0* and *-3.3* are fixed-

**Low-power Rx IC.** Temic Telefunken has a family of low-power UHF receiver ICs intended for car security, wireless lans and appliance control that take a standby current of only 1mA. The *U 431X B* series operate at 433MHz. A modulated carrier is converted by a UHF stage to 10.7MHz IF and amplified by the *U 431X B*, its log. amplifier acting as demodulator for AM, FM being handled by a quadrature detector. Digital data is regenerated in the baseband by a clamping comparator and op-amp, the universal output interfacing to a decoder. Temic Telefunken GmbH. Tel., 01049 7131 672747; fax, 01049 7131 993342.



voltage, three-terminal types, the *LP2951-3.0* and *-3.3* being adjustable and fitted with 3V and 3.3V taps, which avoid external resistors. Quiescent current at light loads is 75µA and there is a shutdown facility and an error flag to indicate when the regulator falls out of regulation by over 5%. National Semiconductor GmbH. Tel., 0104 981 4110 3382; fax, 0104 981 4110 3515.

**Precision references.** 1.26V, 2.5V and 5V (Refs 12, 25 and 50) micropower references by GEC Plessey use the bandgap principle and thereby avoid the need for an external shaping capacitor. Knee currents are 40µA and 80µA, battery operating power 113µW, 150µW and 300µW and initial voltage tolerance ±1%. Gothic Crellon Ltd. Tel., 0734 788878; fax, 0734 776095.


**3V RF amplifiers.** 1.9GHz, 3V amplifiers in NEC's *µPC2745T-2749T* range consume 50% less power than others available, running from a supply as low as 1.8V. They are meant for use in receiver buffer amplifiers and exhibit a noise figure of 2.8dB at a gain of 9 to 21dB. Packaging is a six-pin mini-mould measuring 2.9 by 1.5 by 1.1mm and are made in NEC's 20GHz NESAT III silicon bipolar process. NEC Electronics (UK) Ltd. Tel., 0908 691133; fax, 0908 670290.

**Variable-gain amplifier.** *CLC522* by Comlinear is a DC-coupled, two-quadrant multiplier with differential voltage inputs and a single-ended voltage output and forms a complete variable-gain system containing two input buffers and an output op-amp. Signal channel and gain-control bandwidth is 165MHz at a gain of 10, maximum gain is set externally over the range 2 to 100, the gain control giving more than 40dB variation. At the smallest maximum gain of 2, bandwidth is 350MHz and gain control non-linearity 0.5%. Comlinear Europe Ltd. Tel., 0203 422958; fax, 0203 422961.

**FM IF amplifiers.** Sony has a family of low-voltage, low-power FM IF amplifiers for cordless and cellular telephones. The newest model is the *CXA1683M/N*, which is a 100MHz wide bandwidth double balanced mixer design for cordless telephones operating on 1.8-to 6V DC. The chip has a programmable low-pass filter at the detection output stage, a squelch filter operational amplifier and a signal strength indicator with a 70dB dynamic range. Typical current drain is 4mA from 2.3V. The *CXA1293M/N* is similar, but with features for cellular telephones. Sony Semiconductor Europe. Tel., 0256 478771; fax, 0256 818194.

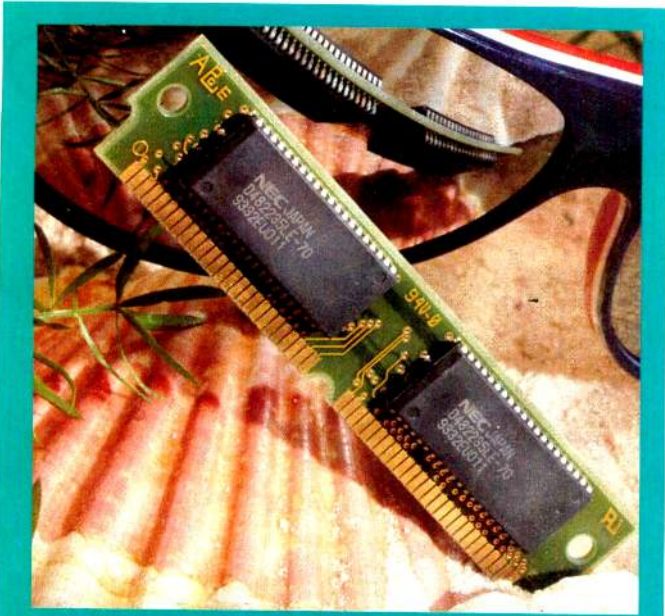**3.3V references.** Knee currents down to 15µA, with a temperature





**Video ram simm.** Video ram MC-250 is a 256K by 32bit device made up of four  $\mu$ PD482235 video rams in a simm format, with two decoupling capacitors for each device, the whole module measuring 82.5mm by 17mm. Each ram has a random-access port and a serial read/write port connected to an internal 16384-bit data register. The device has a split serial buffer, so that data is transferred into one half as serial data is being read from the other half, avoiding flyback noise or flicker in video systems. All i/o is at TTL levels. Sunrise Electronics Ltd. Tel., 0908 263999; fax, 0908 263003.

coefficient of 15ppm/°C are obtained from the Zetex ZRC330 3.3V precision references, which use a bandgap technique needing no external capacitor. Operating current is 20 $\mu$ A-5mA and the device tolerates temperatures from -40°C to 85°C. Since the device is based on an asic, metal mask programming allows Zetex to offer any voltage between 2V and 10V and voltage trimming does not affect temperature coefficient trim. Zetex plc. Tel., 061 627 5105; fax, 061 627 5467.

**5GHz dual differential amplifier.** A dual amplifier for RF and IF down and up converters. Harris's HFA3102 is a dual long-tailed pair with a transistor in each tail, giving a power gain-bandwidth product of 5GHz. Current gain is 70 and is matched between the halves to within 10%. Noise figure is 3.5dB, collector cutoff current is 10nA and collector leakage current 0.01nA. The IC is pin-compatible with other available devices. Spice models are available. Harris Semiconductor UK. Tel., 0276 686886; fax, 0276 682323.

**Infrared receivers.** Infrared communication inside offices, say between computers and printers, is the province of Temic Telefunken's new receiver modules, which are required to work in conditions of high visual and electrical interference. TFMS 5.0 and TFMT 5.0 operate on carriers between 30 and 56kHz, special versions being made for 20 to 60kHz. A pin diode detects the carrier and is followed by signal processing

and a Schmitt output. Shielding by the housing reduces the effects of both visual and electrical interference on paths of up to 40m. Temic Telefunken GmbH. Tel., 01049 7131 672747; fax, 01049 7131 993342.

**Battery charger/monitor.** The Microchip TrueGauge MTA11200 monitors the state of health of rechargeable batteries and recharges them. The device provides information on remaining capacity measured during discharge only, total capacity, voltage, current and temperature, a single-wire to the host microcontroller allowing a module with a Truegauge to stay in the battery pack. There are 35 programmable system parameters from battery warning levels to end-of-discharge voltage, and the device is optimised for different battery types by specifying negative delta peak detection and protection against thermal overcharge, time-out overcharge and peak voltage. Development software is available. Polar Electronics. Tel., 0525 377093; fax, 0525 378367.

**Femtoamp-input op-amp.** Guaranteed input current of National's LMC6001 op-amp is  $25 \times 10^{-15}$ A, other characteristics including an offset voltage of 350 $\mu$ V, 10 $\mu$ V/°C maximum drift and input-referred noise of 22nV/Hz, which allows a better signal-to-noise ratio than jfet electrometer amplifiers. Versions are available with input currents of 25fA and 100fA. Thame Components Ltd. Tel., 0844 261188; fax, 0844 261681.

### Logic building blocks

**Fibre-channel transceiver.** METL's RCC700 is a cmos transceiver, operating at up to 265Mbaud, which integrates 8B/10B encoder/decoder, serialiser and deserialiser, a PLL synthesiser, a PLL clock and data recovery and a byte alignment circuit. PCB evaluation assemblies are available for fibre or coaxial interfaces. Microelectronics Technology Ltd. Tel., 9844 278781; fax, 0844 278746.

### Memory chips

**Fast srams.** Cmos srams in the Alliance Semiconductor 7C256 256K series are fast - 12 to 25ns - and sparing of power, maximum active power in the 15ns type being 605mW. Standby power levels as low as 1.1mW are achieved and data is retained down to 2V. Supply is 5V or 3.3V. Hunter Electronic Components Ltd. Tel., 0628 759111; fax, 0628 756111.

### Microprocessors and controllers

**Embedded 386.** AMD is offering the Am386 processor in two embedded versions, the Am386DE and Am386SE. Any X86 PC can be used as a development platform, the FusionE86 support program providing software and hardware from more than 60 suppliers, including Microsoft's Microsoft At Work operating software. Both versions work at either 3V or 5V, with standby modes. Am386DE, the 33MHz type, is available now, the SE following in a few weeks. Advanced Micro Devices (UK) Ltd. Tel., 0483 740440; fax, 0483 756196.

**16-bit V-series micro.** NEC's V55PI is a 16-bit, single-chip microcomputer with 16Mbyte of address space and 64Kbyte i/o space; the CPU is 8086-compatible, so that existing software is usable. The CPU executes instruction about twice as quickly as the V35 and higher-performance peripherals include two uarts, operating at 780kbit/s asynchronous and up to 3.125Mbit/s clock synchronous, and an 8-bit parallel

### Mixed-signal ICs

**Consumer chips.** ITT's Digital Systems 3000 is effectively the next generation of digital consumer electronics, building on the earlier, self-contained, television-oriented DIGIT2000 system of ICs to become a structure for virtually unlimited application in multimedia systems. Most Digital Systems 3000 ICs are self-contained and combine analogue and digital techniques. The system copes with functions beyond the current consumer area: services such as telefax, videotext and modem functions take the system into telecommunications and picture compression and transmission, computer audio and graphic user interfaces link consumer electronics, telecomms and computers in the area of multimedia services. Since all the modules are small and powerful and are produced by the same technology, tailor-made, one-chip implementations for special applications can be made relatively cheaply.

The company says it is ready to put into practice the idea of single-chip systems for the new, extended area of consumer electronics. For example, ITT is able to integrate several DSP kernels and their ram and rom on one chip, whereas the existing practice is to use an MCU and an interface chip, taking up more space and requiring more extensive interfacing. ITT Semiconductors. Tel., 0932 336116; fax, 0932 33148.

interface configures as either a general-purpose 8-bit i/o port or as a Centronics type giving high-speed bidirectional parallel communications as a slave or as a driver. There are also a four-channel DMA controller, a 4-channel 8-bit A-to-D converter, a PWM operating up to 24.4kHz, a watchdog timer, four 16-bit timers and a 16-bit software interval timer. Sunrise Electronics Ltd. Tel., 0908 263999; fax, 0908 263003.

**32-bit risc microcontrollers.** The SH series of microcontrollers by Hitachi use a 32-bit risc core, the first to be available operating with cycle times of 50ns on a 5V supply or 83ns on 3.3V. Most instructions execute in a single cycle using a 5-stage pipeline to give a 16 Dhrystone Mips performance. Other features include 16, 32-bit wide general-purpose registers and a hardware multiplier performing 16 by 16-bit plus 42-bit multiply and accumulate operations in 100 to 150ns. Current consumption is 100mA at 20MHz and 40mA at 12.5MHz for the 3.3V type, several sleep modes being provided. First models to appear are the SH7032, which is romless with 8Kbyte of on-chip ram, and the SH7034 with 64Kbyte of rom/prom and 4Kbyte of ram. Hitachi Europe Ltd. Tel., 0628 585000; fax, 0628 585200.

### Mixed-signal ICs

**MPEG2 decoder.** Toshiba's new single-chip video decoder meets the MPEG2 standard and decodes compressed 1153 by 1024 line, 30 frames/s digital signals with HDTV-level resolution. Parallel decoding in the variable-length decoder and the risc microprocessor allows both to decode data bit streams at the same time to provide the necessary speed. Toshiba Electronics UK Ltd. Tel., 0276 694600; fax, 0276 691583.

### Optical devices

**Miniature leds.** Seven-segment leds in HP's new HDSP-U series have grey or black surfaces for better contrast and provide an 8mm character height in a 11mm by 7.1mm by 5mm package. Red, orange,



yellow or green character colours are available at luminous intensities of 480mcd for yellow to over 1000mcd for the red and green. Hewlett-Packard Ltd. Tel., 0344 362277; fax, 0344 362269.

#### Laser diode for optical memory.

Intended for use with optical disk memory or memory cards, Mitsubishi's *HS01* high-power HF Super-Imposition laser diode operates from 5V and is in a steel packing-in-shield case for low noise; RIN figure is  $-125\text{dB/Hz}$ . Maximum output is 35mW continuous and 45mW pulsed. Mitsubishi Electric UK Ltd. Tel., 0707 276100; fax, 0707 278692.

#### Two-colour photodiode.

The *Tandem* two-colour photodiode detector combines a 2.5mm diameter silicon diode and a 1mm diameter InGaAs diode in a single TO-5 package to provide sensitivity over the 400 to 1700nm spectral range, each detector being individually addressed. It can be optimised at 820, 880 and 940nm. Different InGaAs diode diameters can be specified. Aerotech World Trade Ltd. Tel., 0628 34555; fax, 0628 781070.

### Oscillators

**Clock oscillators.** *Faltron C04810* and *C04910* clock oscillators are only 2mm high, with a footprint of 7.5mm by 5mm. Frequency stability is 50ppm and power consumption of the 04810, depending on frequency, is 20 to 35mA, driving 10 LSTTL loads or 15pF mos. The *C04910* drives 10 TTL loads or 50pF mos, but still takes only 25 to 60mA. Frequency range is up to 60MHz, a 3.3V version being also available. The *H-13* is a low-profile SM device, with a height of 1.3mm and consuming 0.1mW. Flint Distribution. Tel., 0530 510333; fax, 0530 510275.

### Power semiconductors

**High-voltage mosfets.** Motorola has upgraded its entire 400 to 600V range of power mosfets to 800V and 1000V, using a new technique in which multiple rings provide a better field

#### 40GHz YIG-tuned oscillator.

Avantek, an HP subsidiary, offers the *AV-20040*, which it believes to be the first YIG-tuned oscillator to cover 20 to 40GHz without filters, multipliers or amplifiers to produce a minimum of 10dBm, with  $-60\text{dBc}$  spurious output. It is hermetically sealed and operates from a single 15V supply. Frequency drift is 60MHz maximum. Hewlett-Packard Ltd. Tel., 0344 362277; fax, 0344 362269.



shaping towards the edge of the mosfet die. This gives improved voltage blocking to protect against surface charges at high voltages. As examples, *MTY10N100E*, a 1000V type, has an  $R_{ds(on)}$  of 1.3 $\Omega$  at 10A and the 800V *MTP4N80E* has a 3 $\Omega$   $R_{ds(on)}$  at 4A. Motorola Inc. Tel., 0908 614614; fax, 0908 618650.

**1500W suppressor.** Semtech's *SMCJ* transient voltage suppressors are either unidirectional or bidirectional and are in a DO-214AB plastic package. Response time is 1ps and forward surge rating 200A. Having a voltage range of 5 to 170V, the devices have a steady-state power dissipation of 3W (1500W peak). Semtech Ltd. Tel., 0592 773520; fax, 0592 774781.

**Fast power diode.** Ten members of Harris's *Hyperfast RHR* series of power diodes exhibit reverse recovery times of 60 to 100ns. Three of the devices have breakdown voltages of 1200V and  $t_r$  of 75ns at 30A, one of them being offered as a dual device. Two 75A types are 1200V rated and have  $t_r$  of 100ns; three lower-voltage types recovering in 60ns. A 150A type breaks down at 1000V, with a  $t_r$  of 100ns. Harris Semiconductor UK. Tel., 0276 686886; fax, 0276 682323.


**Reverse blocking switch.** Replacing two mosfets and their drive circuit, the Siliconix *Si9718CY* is a reverse blocking switch for battery disconnect application in dual-battery notebook computers, allowing the computer to switch from one battery pack to the other before cells completely discharge. A new process eliminates the parasitic diode found in standard mosfets, reducing on resistance to 80m $\Omega$  at 3.5A. The device also includes a charge pump and enable circuitry, and undervoltage lockout protects the system. Siliconix/Temic Marketing. Tel., 0344 485757; fax, 0344 427371.

#### Low-power PWM controller.

Unitrode claims a first for its *UCC3570* BiCMOS voltage-mode PWM controller for use in isolated, high-frequency switched-mode power supplies. It features an 85 $\mu\text{A}$  start up current, 1mA run current and the ability to drive a 1A mosfet gate at up to 500kHz. Using voltage feedforward, the device responds accurately and within one clock cycle to wide line-voltage variations and is not noise sensitive. Unitrode (UK) Ltd. Tel., 081 318 1431; fax, 081 318 2549.
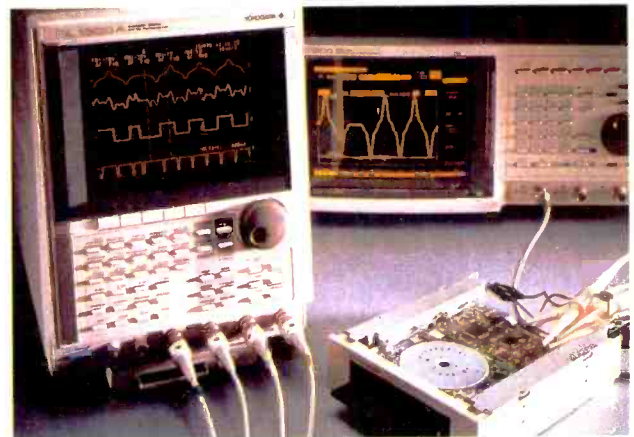
#### 300W transient suppressors.

Semtech's *SM* series of surface-mounted silicon transient voltage suppressors are low-cost devices for data line or supply rail use, having a peak pulse power of 300W, a response time of 1ps and unidirectional or bidirectional operation, depending on type. Voltage range is 5 to 24V, breakdown 5 to 26.7V minimum, clamping voltage at 5A, 11 to 55V and leakage current 1 to 100 $\mu\text{A}$ . Semtech Ltd. Tel., 0592 773520; fax, 0592 774781.



**Waveform generator.** Yokogawa's *AG1200* arbitrary waveform generator captures and reproduces signals from digital storage oscilloscopes. It interfaces to the DSO via a GPIB port and has a 3.5in floppy drive for waveform storage. Waveforms loaded from the DSO are reproduced, displayed and output directly, or modified and edited on screen. Output is 4-channel with a 10MHz clock and 12-bit resolution, instruments perhaps being combined to give 16 channels or channels combined to provide 32-bit patterns. Waveforms are also produced from functions and/or generated by the Scope Draw technique in which the waveform is sketched and edited on screen. Martron Instruments Ltd. Tel., 0494 459200; fax, 0494 535002.

## PASSIVE

### Passive components

**Crossover electrolytics.** Bipolar electrolytic capacitors in Nichicon's *DB.GB* series are meant for use in audio crossover networks and have values from 1 $\mu\text{F}$  to 68 $\mu\text{F}$  in  $\pm 20\%$  (DB) and  $\pm 10\%$  (GB) tolerance. Working voltage is 50V, leakage current 3 $\mu\text{A}$  and allowable ripple 205 to 1200mA (DB), 760 to 1120mA (GB). The radial-lead components resist most halogenous cleaning fluids. Nichicon (Europe) Ltd. Tel., 0276 685393; fax, 0276 686531.

**High-temperature ceramic capacitors.** Vitramon's *H* range of chip capacitors uses the X8R dielectric, which has the stability of

X7R but withstands temperatures up to 150°C, making them suitable for unfriendly environments such as under the bonnet of a car. Sizes 0805, 1206, 1210, 1812 and 2225 are available in values from 470pF to 1 $\mu\text{F}$  at 50V DC and in tolerances from  $\pm 5\%$  to  $\pm 20\%$ . Insulation resistance at 25°C is 100G $\Omega$  and a minimum of 10G $\Omega$  at 150°C. Vitramon Ltd. Tel., 0628 524933; fax, 0628 525435.

**Vertical inductors.** In values of 0.47 $\mu\text{H}$  to 1000 $\mu\text{H}$  at  $\pm 10\%$  standard tolerance, *microSpire MIVI-PK 0455* series of vertically mounted inductors save board space by offering diameters of 5 to 13mm and a height of 11 to 17mm. Self-resonant

**Hand-held IC tester.** Capable of testing 74/74LS/74HC TTL and 4000 series CMOS logic devices and 41/44 series dynamic RAMs, the *Polar D320* is hand-held and is powered by a 9V PP3 cell. More than 350 devices are in its built-in library and it can be switched into a search mode to compare an unknown device with available data. Components are placed in a 20-pin zif socket. Polar Instruments Ltd. Tel., 0481 53081; fax, 0481 52476.





## NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

frequencies are 2.5MHz for the 1000pH version up to 145MHz for the 0.47µH type. Surtech Interconnection Ltd. Tel., 0256 51221; fax, 0256 471180.

**Multilayer ceramics.** Multilayer ceramic capacitors in AVX's CM series are in 0603, 0805 and 1206 cases sizes at working voltages of 16V. Values up to 100nF for the 0603, 470nF in the 0805 and 1µF for the 1206 types are available, all with leakage currents given by an insulation resistance of over 10GΩ or 500MΩ/µF, whichever is the smallest. AVX Ltd. Tel., 0252 336868; fax, 0252 346643.

**Resistor networks.** Made to the customer's specification of values, tolerance and circuit configuration, Beyschlag surface-mounted resistor networks are available in quantities down to 100 pieces. The thin-film resistors are the Beyschlag Micro-MELF type, welded to a metal frame which is shaped to form the circuit. Values in the range 10Ω to 2MΩ are used to tolerances of 1% or better and with temperature coefficients of 50ppm/°C or better. The networks are said to possess a high pulse load capability. Flint Distribution. Tel., 0530 510333; fax, 0530 510275.

### Connectors and cabling

**Adaptable board connector.** 65,536 different connection patterns are possible in a housing smaller than a di1 package with the Erg system. The two-part component is a pin header and matching jumper block which is selectively loaded to obtain the required pattern of contacts. The multi-jumper block fits over the 1-16

three-pin rows of gold-plated header pins, enclosing and protecting them and setting up the interconnection pattern. Standard blocks are fully loaded, but Erg can supply any pattern to order. Blocks are either polarised or reversible. Erg Components. Tel., 0582 662241; fax, 0582 600767.


### Filters

**Notch filters.** A new approach to temperature compensation in cavity filters has been adopted by Wainwright Instruments GmbH in Germany in their range of ultra-stable notch filters for GSM, PCN and other mobile comms systems. Drift is less than ±1ppm/°C. The technique has also been applied to filters for other frequencies and characteristics. Wainwright Instruments GmbH. Tel., 01049 8152 2245; fax, 01049 8152 5174.
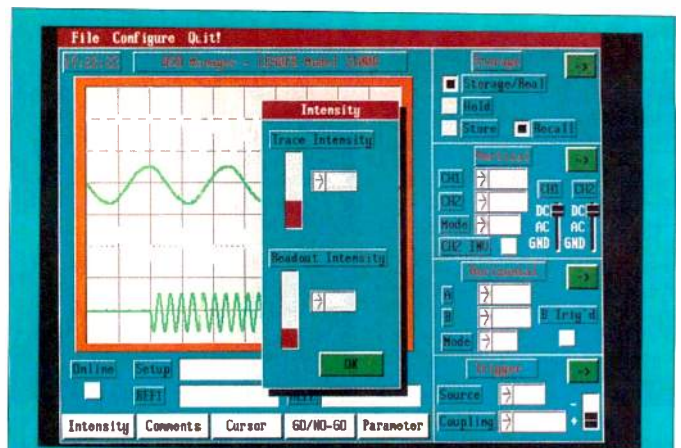
### Hardware

**Conductive keypad.** The Grayhill Series 90 conductive rubber keypad is now available from Highland. The pads are available in 3 by 3 and 4 by 4 forms with matrix circuitry and are rated at 12V DC and 5mA for 0.5s. Contact resistance is 100Ω and bounce time less than 12ms. Highland Electronics Ltd. Tel., 0444 236000; fax, 0444 236641.

**Shielding can.** Made in tin-plated steel, West Hyde's Isolator is a board-mounted shield attached to the board by four solder prongs set on 0.1in pitch. The one-piece unit is fully soldered on the internal faces to provide efficient sealing. It comes in a range of sizes and can be made to



**PC oscilloscope control.** DSO Manager is a package by FemtoTek for the control of a Leader Instruments 3100D digital storage oscilloscope from a PC, using a GUI and a mouse. It is based on National's LabWindows software and comes as the software only or as a complete system including a GPIB interface board. All the oscilloscope functions are settable from the PC and waveforms can be stored on and retrieved from disk, plotted on a printer and sent to Ascii files for later use. National Instruments UK. Tel., 0635 523545; fax, 0635 523154.

order in seven days. It is also available at lower cost without soldering. West Hyde Enclosures. Tel., 0453 731831; fax, 0453 886637.

### Instrumentation

**GPIB test gear.** Thurlby Thandar has additions to its range of rack-mounted, GPIB test equipment, including power supplies, multimeters, generators, logic analysers and oscilloscopes, which are in 2U cases. All instruments conform to IEEE-488.2 in addition to IEEE-488.1. Thurlby Thandar Instruments Ltd. Tel., 0480 412451; fax, 0480 450409.

**Loop-powered process meters.** Models 81 and 82 3.5 and 4.5 digit process meters are powered by the 4-20mA current loop process signal, offset and scale values being adjustable to allow the use of a range of engineering units. Accuracies are ±0.1% and ±0.02% respectively and the signal input can be set to 4-20mA or 10-50mA. Panel-mounting hardware is included. Amplicon Liveline Ltd. Tel., 0800 525 335 (free); fax, 0273 570215.

**Clean RF generators.** Designed to be used as either bench-top instruments or as part of an ATE system, the Giga-tronics 606X series of RF signal generators covers the 100kHz-2.1GHz range in three models; 6060/1/2, the 60602 having fast-rise pulse modulation for transponder and radar testing. As standard, a 10MHz crystal oscillator ages at <±5X10<sup>-10</sup> and warms up in an hour. Alternatively, an optional oven-controlled reference ages at <±5X10<sup>-10</sup> and warms up in 30min. Sematron UK Ltd. Tel., 0734 819970; fax, 0734 819786.

**Micro-based thermometers.** ETI's Microtherma thermometers are lightweight, handheld instruments

based on microprocessors to allow continuous and automatic recalibration. Temperature range is -200°C to 1370°C with either 0.1°C or 1°C resolution. Each has a 4-digit display with open-circuit and low battery indication. Type K,J,T, E or N sensors can be selected by the keypad, and there is a conversion facility from celsius to fahrenheit. Electronic Temperature Instruments Ltd. Tel., 0903 202151; fax, 0903 202445.

**Auto timebase oscilloscopes.** Hitachi's V1065 and V665, 60MHz and 100MHz oscilloscopes, in a new family of compact instruments, provide automatic timebase setting, with manual override, and on-screen display of A and B sweep time, delay time and hold-off. Channel sensitivities are also displayed and the instruments have a cursor readout for voltage, time difference and frequency. Two models in the range feature a 4-digit frequency meter and all models have delayed sweep and autotrigger in the usual modes. Thurlby Thandar Instruments Ltd. Tel., 0480 412451; fax, 0480 450409.

**Vibration analyser/data collector.** A technique developed by SKF, spectral emitted energy technology (SEE), is used in the Microlog CMVA10 single-channel vibration analyser to give a true multi-parameter capability. The technique is an acoustic enveloping process that helps to detect rolling element defects and predict bearing failure at an early stage. The instrument has 4Mbyte of on-board ram to allow the use of a multi-plane balancing routine in the unit. It is also compatible with the PRISM computer-aided condition monitoring software. Endevo UK Ltd. Tel., 0763 261311; fax, 0763 261120.

**Lan cable tester.** For the use of lan installers and maintenance people,



### Computer peripheral

**Contactless smart card.** Measuring 43mm by 54mm and 5mm thick, Mitsubishi's new contactless MelCard is tough enough to stand wear and will withstand being made into a key fob. The cards operate a read/write device linked to a computer network for data i/o, read and write operations, the device automatically transmitting data at up to 455kHz; the frequency can be customised for specific applications such as operating a ticket barrier or recognising parts in a factory. Cards are read at a distance up to 800mm in less than 0.2s. They contain a single-chip, 8-bit microcontroller which uses little power, the use of sram for user memory also takes little power and enables high-speed read and write. RF transmission avoids the problems associated with dirty contacts and facilitates volume throughput. The cards have been thoroughly tested while being bent and twisted at temperatures from -20°C to 60°C and, should the occasion arise, they will survive being immersed in 1m of water for 30 minutes. Mitsubishi Electric UK Ltd. Tel., 0707 276100; fax, 0707 278692.



the *Fluke 650 Cablemeter* tests either coaxial cables or unshielded twisted pairs in both Ethernet and Token-ring lans. A single function knob and a four-line display, together with display and storage of up to 50 results, make for ease of use. It tests a circuit's characteristic impedance and will monitor Ethernet traffic and measure inherent noise over time to locate intermittent trouble. An autotest feature performs a set of tests, compares the results against standards and gives indication of a problem by a tone and fail message. Jensen Tools. Tel., 0604 787060; fax, 0604 785573.

## Literature

**Audio products.** Crystal's complete range of audio ICs is described in a 1072 page book. Information includes all specifications, block diagrams, theory of operation, applications and schematics. Devices detailed are data converters and codecs, DSPs and synthesiser, digital audio transmitters and receivers and volume controls. Crystal Semiconductor Corporation. Tel., 0101 512 442 7555; fax, 0101 5512 445 7581.

## Power supplies

**Rechargeable 996.** A direct replacement for the 996 dry battery, Power-Sonic's 6V, 5Ah sealed lead-acid battery type *PS650* can be recharged up to 1000 times and includes an overload self-resetting cut-out. The company now has more than 100 models of SLA rechargeables with capacities in the range 0.5Ah to 4800Ah. Power-Sonic Europe Ltd. Tel., 0268 560686; fax, 0268 560902.

## Radio communications products

**GaAs fet amplifiers.** Multi-octave and narrow-band GaAs fet amplifiers by Lucas covering the 0.1-40GHz range are based on a library of modules for rapid development and modification and low cost. They use mesfet or hemt devices and most of them incorporate temperature compensation. Many are in the low-cost quasi-MMIC form, in which all passive components are integrated and the active devices bonded separately. Custom designs incorporating limiters, special filters, variable gain, etc., are undertaken. Connection options include standard waveguide, coaxial and microstrip. Anglia Microwaves Ltd. Tel., 0277 630000; fax, 0277 631111.

## Switches and relays

**Solid-state relays.** *Series RA* relays from Teledyne handle loads voltages up to 250V RMS from 40Hz to 440Hz, with reactive loads at power factors down to 0.2. Inverse parallel SCRs, configured for zero-voltage turn-on, handle current surges to 250A. If temperature exceeds set limits, the relays shut down and latch off until the input recycles and case temperature returns to normal, the trip being signalled by a status output. Teledyne Electronic Technologies. Tel., 081 571 9596; fax, 081 571 9637.

# COMPUTER

## Computer board-level products

**Vision inspection system.** *PAC-Scan* by Pro-Active Control is an inspection system quality control, on-line inspection and component identification, using a range of standard cameras and monitors. It is based on a Eurocard and three processors are offered for large or small frame stores, monochrome camera and a toolkit. Resolution is 512 by 576 pixels and there are 256 greyscale levels. Examples of the system's application are a PCB positioner, accurate to within 50µm and a canning factory system in which cans are checked for damage. Pro-Active Control Ltd. Tel., 0223 300801; fax, 0223 300979.

**Thermocouple data acquisition.** *DI-221TC* from Dataq is a 12-bit, 16-channel portable data acquisition system, optimised for grounded thermocouples but suitable for other analogue inputs to the built-in signal i/o panel, a sensor on the PCB signal terminal receptacles providing cold junction compensation. The instrument linearises thermocouple signals in real time with DSP-based, 10th-order polynomial calculation software, voltage inputs being automatically converted to temperature indications in the user's choice of range, either  $\pm 1200^{\circ}\text{C}$  or  $\pm 120^{\circ}\text{C}$ . It plugs into the printer port of a PC and has its own battery. Keithley Instruments Ltd. Tel., 0734 575666; fax, 0734 536469.


**40MHz DSP board.** LSI says its *PC/C31-40* applications board is the first to be based on the Texas Instruments TMS320C31 40MHz digital signal processor. It is a two-thirds-length PC AT card and comes with a complete Windows 3 development and integration software package, the Hypersignal Block Diagram software automatically generating ANSI C code and providing real-time support for the board. There is also the TI floating-point C compiler and debugging is assisted by LSI's Windows-based View31 tool and libraries of C-called DSP and maths functions. Loughborough Sound Images Ltd. Tel., 0509 231843; fax, 0509 262433.

## Computer systems

**Industrial computers.** *SealTouch* computers by the American Deeco company are high-performance units in panel-mounting configuration and proof against hostile environments. CPUs are 486DX or DX-2 and control is by an infrared system that "looks" like a mouse to the computer. The system includes a sealec active-matrix 10.4in VGA display, a 3.5in drive, a 120MB hard disk, four expansion slots, on-board dram and dos. Deeco Systems. Tel., 0101 471 4700; fax, 0101 489 3500.
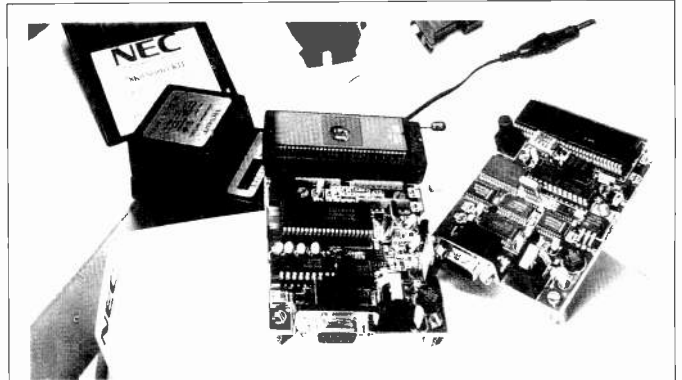
## Data communications

**Parallel port data acquisition.** About the size of a laptop computer, *Parallel*



**Controller design kit.** A starter kit for embedded system design from NEC costs only 5% the price of a full kit, but still contains everything needed to design systems based on the NEC 78K0 range of microcontrollers. It includes an assembler and full-screen debugger for use on a PC, an evaluation board with 32K ram, a programmer for UV and one-time-programmable devices, a UV-erasable 78K0 microcontroller and all necessary hardware. NEC Electronics (UK) Ltd. Tel., 0908 691133; fax, 0908 670290.

*Pad* by Computer Instrumentation acquires data for a PC or notebook computer at up to 100kHz. Its 12-bit converter has programmable ranges from  $\pm 10\text{mV}$  to  $\pm 10\text{V}$ . Additionally, a screw terminal block may be plugged in to provide eight 4-wire inputs for thermocouples, PRTs, accelerometers and other sensors. There are 32 programmable logic i/o channels and a pair of counter timers. A stand-alone logging mode allows the unit to continue collecting data when its notebook computer has gone home. Computer Instrumentation Ltd. Tel., 0903 700755; fax, 0903 700788.

## Portable data acquisition.

Containing not only analogue interfacing circuitry for on-site data acquisition, but also a 486 25MHz PC, Onsite's *Techstation -ci* series are 16-channel, 100kHz analogue signal recorders based on a notebook PC, offering on-line spectrum analysis while logging data to disk. The whole thing measures 15in by 12in by 3.5in and weighs 6kg. Everything works under Windows, so that no programming is needed and the data can be output in common formats for transfer to other software or loading to mainframes. Software supplied as standard is Windows, dos and Onsite's *DasyLab* acquisition software. Laplace Instruments Ltd. Tel., 0692 500777; fax, 0692 406177.

## Development and evaluation

**386CX/EX ICE.** Hitex announces full in-circuit emulators for the Intel *80386CX* and *EX* embedded microprocessors, using the existing PC-based T32/386SX emulator as a base to allow true ICE of the central processor at up to 25MHz in 100PQFP and MQFP packages. The *HITOP386* debugger is now extended to support the CX's new peripherals and C compilers by Microsoft, Borland and Intel are supported. Real-time debugging and analysis are enabled. Hitek (UK) Ltd. Tel., 0203 692066; fax, 0203 692131

**Cheaper Checkmate.** *Checkmate's* Intel 80C186EA in-circuit emulator has been reduced to £3500, including the *Paradigm Debug* debugger. The emulator does not interfere with the target hardware's operation and does not use the target's stack or insert wait-states when running from overlay memory and is guaranteed to run in the user's target. Great Western Instruments Ltd. Tel., 0272 860400; fax, 0272 860401.

## Programming hardware

**Field programmer.** *Sprint Plus 48* by Concentrated Programming is a low-cost device programmer supporting more than 3000 devices, including most popular FPGAs, CPLDs, PLDs, microcontrollers, eeproms and eproms. It uses the ram, CPU and hard disk of the user's PC via a parallel port for menu-driven read, blank check, program, verify, sum check and ID check, the use of a notebook or laptop giving portability. Software is updated when required. Concentrated Programming Ltd. Tel., 0279 600313; fax, 0279 600322.

## Software

**RISCOS software.** Steve Hunt offers software applications for the Acorn RISCOS computers, with the needs of RF engineers in mind, including a filter designer, a receiver noise figure/intercept point analysis tool, an inductance ready reckoner and a Smith chart design aid. Steve Hunt. 0604 858090 (evenings).

**Mathcad updates.** Two new versions of *Mathcad* technical calculation software have appeared: *Mathcad 5.0* and *Mathcad PLUS 5.0*. The former has been made easier to use, with easier equation and text editing and pull-down menus, yet offers new functions such as trace and zoom for graphics, print preview and a spell checker for document preparation. *Mathcad PLUS* has the same ease of use, but also provides a new set of functions, including differential equation solvers and advanced matrix algebra. Mathsoft Europe. Tel., 0344 23491; fax, 0344 873461. ■

# APPLICATIONS

Please mention *Electronics World + Wireless World* when seeking further information.

## Low drop-out regulators

Given a 250mA load, early linear voltage regulating ICs like the *LM78xx* series needed an input supply at least 1.5V higher than their output before their regulators started to function properly.

Two recent ICs produced by National Semiconductor need an input-to-output differential of only 470mV to achieve the same output current. One of these devices is specifically for microprocessor applications, the other a more general-purpose type designed to consume very little quiescent power.

Called *LP2957*, the IC for microprocessor applications has a fixed 5V output. Being designed for minimal energy losses, this IC can compete with switching regulators in battery powered applications. For this reason, reverse battery protection is incorporated. Via its integral power transistor, the IC can deliver up to 250mA yet its quiescent current is only 150 $\mu$ A.

As the first set of diagrams show, the TO220-packaged *LP2957* can act as a basic 5V three-terminal regulator but with shut-

**Dropout Characteristics**

Input Voltage (V)	Output Voltage (V) at $I_L = 1\text{ mA}$	Output Voltage (V) at $I_L = 250\text{ mA}$
1	1.0	1.0
2	2.0	2.0
3	3.0	3.0
4	4.0	4.0
5	5.0	5.0
6	6.0	6.0

Producing a fixed 5V output with low energy losses, the *LP2957* low drop-out regulator is designed specifically for microprocessor and microcontroller applications. Adding a few passive components to the basic regulator circuit provides snap-on/snap-off output. This ensures that, as input voltage falls, supply to the microprocessor cannot linger at a level that might cause it to operate unpredictably.

At light loads, quiescent current of the *LP2956A* low drop-out regulator is 170 $\mu$ A, making it suitable for battery-power applications. Shown here are both 5V fixed and 1.2 to 29V variable output configurations. Fixed-voltage circuit shows the auxiliary supply which remains on when the main supply is disabled.

**Dropout Characteristics (Main Regulator)**

Input Voltage (V)	Output Voltage (V) at $I_{L\text{main}} = 1\text{ mA}$	Output Voltage (V) at $I_{L\text{main}} = 250\text{ mA}$
1	1.0	1.0
2	2.0	2.0
3	3.0	3.0
4	4.0	4.0
5	5.0	5.0
6	6.0	6.0

The variable output circuit includes a 6V EAD (EAD) input, a 348k resistor, a 1 $\mu$ F capacitor, a 100k resistor, a 5V MAIN OUT ( $I_L \leq 250\text{ mA}$ ), a 5V TAP, a 1M resistor, a 1M resistor, a 2.2 $\mu$ F capacitor, an ERROR output, a LOW BATT output, a 5V MEMORY OUT ( $I_L \leq 75\text{ mA}$ ), a 309k resistor, a 100k resistor, and a 10 $\mu$ F capacitor.

down input and error output features added. The error output drives low whenever the output falls out of regulation by more than about 5%.

In the same set of illustrations is a snap-on/snap-off configuration. This arrangement is used to prevent the unpredictable microprocessor operation that occurs when supply input voltage falls below a preset level. If input to the regulator falls below the threshold, supply to the microprocessor

'snaps' off, causing a clean power down.

Housed in a 16-pin DIL or surface-mount package, the general-purpose LP2956 shown in the second set of diagrams is more flexible than the five-pin LP2957. Its output is adjustable from 1.23 to 29V and it has an auxiliary output that can be used, say, for powering memory when the main supply is turned off via its shut-down pin

Again, this device has a comparator that signals when the main output falls more than

5% out of its regulation limits. Output voltage of the 75mA auxiliary regulator – which also features low drop-out capability – is independently adjustable.

Comprehensive performance curves and applications data are presented for both devices in their individual data sheets.

**National Semiconductor**, The Maple, Kembrey Park, Swindon, Wiltshire SN2 6UT. Tel. 0793 614 141, fax 697522.

## Designing with DC-to-DC converters

Possibly the most comprehensive book on using and selecting DC-to-DC converters and power supply systems has been produced by the Energy Systems Division of Ericsson. Comprising over a hundred A4 pages, the *Powerbook* covers topics ranging from circuit needs to electrical and thermal design of decentralised power systems.

Particularly popular in telecomms, decentralised power systems have a number of advantages over traditional alternatives involving a single central power supply. Heat caused by power supply regulation is evenly distributed throughout the enclosure. Regulation is carried out local to the PCB being served so cable voltage drop is minimised.


Upgrading a 100W centralised PSU to 110W, say, would involve replacing an expensive unit. Upgrading a system with ten 10W converters involves simply adding another 10W converter. Likewise, the failure

of a distributed regulator is less drastic than the failure of a central PSU. In some cases, a distributed regulator can even be replaced while the system is powered up.

Finally, the cost of holding replacement power supplies for maintenance is also lower and energy consumption can be reduced since converters designed for distributed power can usually be turned on and off under microprocessor control.


In a section on converter topologies, clarification of the various types of converter is provided. Because different names can be used to describe the same topology, and since there are so many different types, describing topologies often causes confusion. According to the book, there are hundreds of different topologies and variations but no universally accepted classification scheme exists; but one option is presented on the next page.

Most widely used in commercial DC-to-

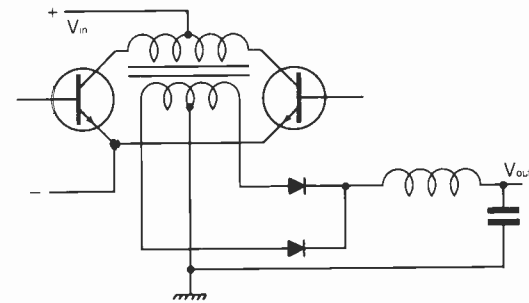


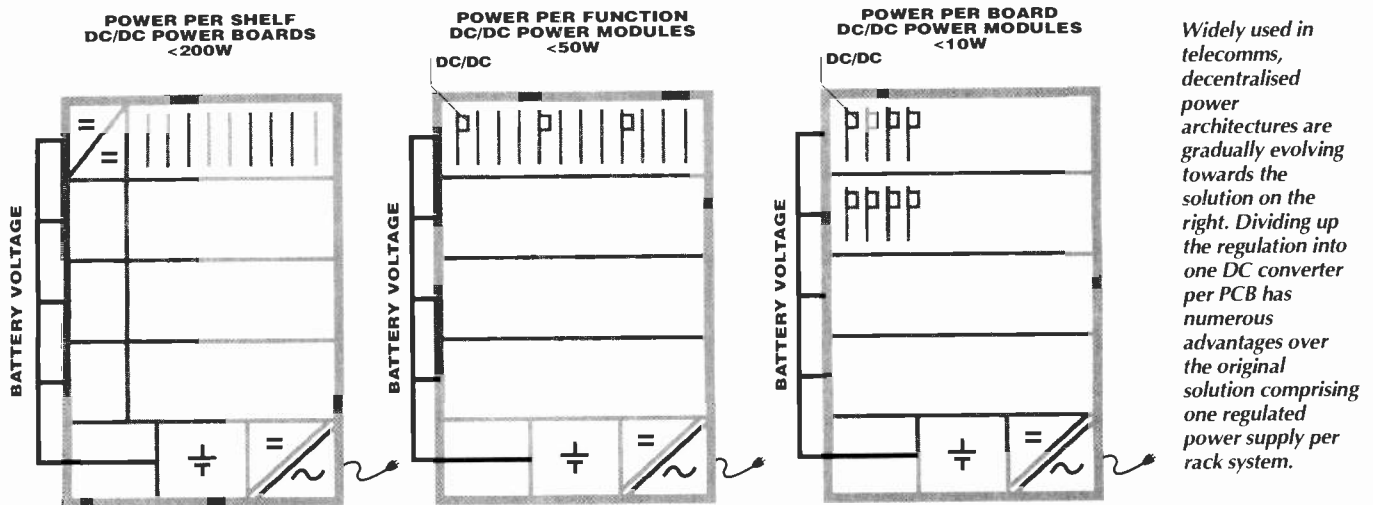**Push-pull DC converters are most useful for lower input voltages since each of the power switches sees a voltage twice that of the supply rail due to the tapped transformer primary.**


DC converters are flyback, push-pull, half-bridge and full bridge topologies. In the flyback converter, not shown here due to its simplicity, transformer voltage 'flies back'




TOPOLOGY	NUMBER OF SWITCHING DEVICES	DEVICE VOLTAGE STRESS (VOLTS)	OPTIMAL POWER LEVEL (WATTS)	COMMENTS
Flyback	1	$V_N + N V_o$	5 to 50	N = Transformer turns ratio Low complexity Low cost
Push-Pull	2	$2 V_N$	15 to 150	
Half bridge	2	$V_N$	15 to 200	
Full bridge	4	$V_N$	150 to 1500	

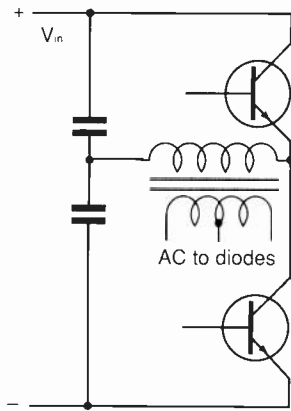

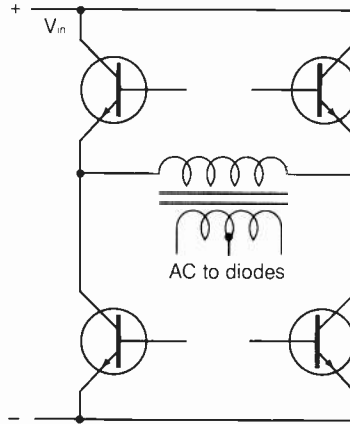In the half-bridge topology, two capacitors keep one side of the primary half way between the supply rails so the power switches only experience half the voltage stress of those in the push-pull converter. Component count is the penalty.



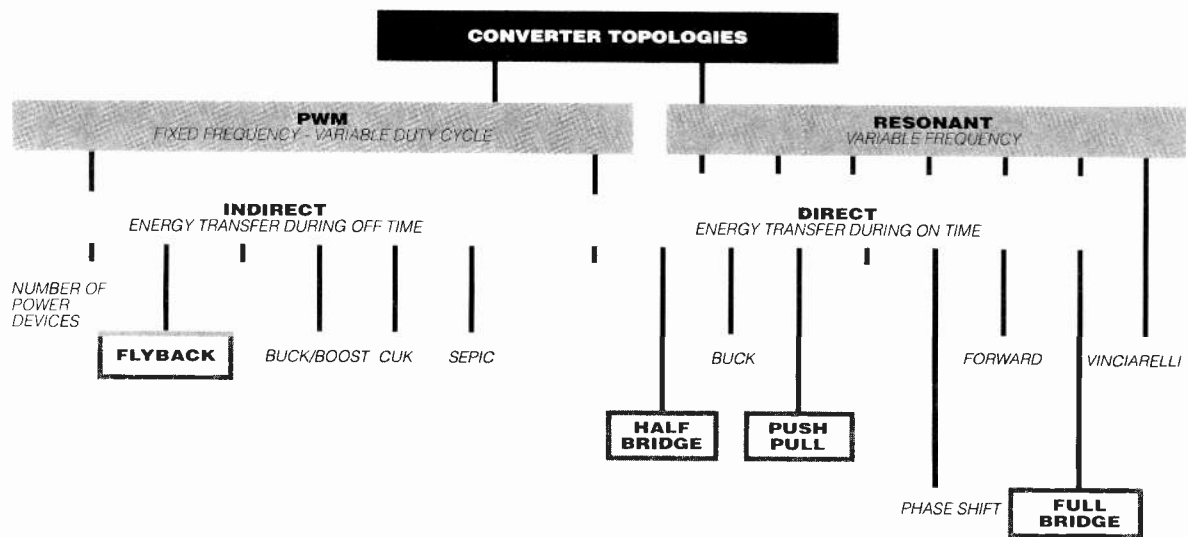Full-bridge circuits, mainly used for converters delivering more than 150W, have four switches each seeing the full supply voltage but experiencing only half the current of their counterparts in the half bridge.



when the power switch turns off. Of the four types mentioned, this is the only one where the transformer acts as an energy storage device. It comprises a single transistor driving a transformer primary winding and rectification together with smoothing

following the isolated secondary winding.

All four topologies are reviewed but the book points out that topology should not be a major criterion when selecting a DC converter for a particular application. No one topology is best, as the table on the

previous page indicates.

**Ericsson Components AB, Energy Systems Division, S16481 Kista-Stockholm, Sweden. Tel. +468 721 6356, fax 721 7001**

## Radio pager design

Full circuit details, PCB layout and adjustment procedures for an fsk radio pager are presented in GEC Plessey's note AN172. *Radio pager design using the SL6649-1 and MV6639.*

Operating at 153MHz, the system is a direct-conversion receiver that converts frequency-shift-keyed rf into digital data for decoding. Output data is 512baud tone data. All filtering is carried out on chip and two reference voltages are available for rf amplifier biasing.

Within the MV6639 POCSAG\* decoder, which is capable of operating from a supply as low as 1V, is a voltage doubler intended to drive an LCD.

In the circuit shown, two references within the SL6649 bias an external cascode rf amplifier. This amplifier then feeds differential inputs of the mixer through a transformer. Input networking to the

amplifier,  $L_4$ ,  $C_{31}$  and  $C_{32}$ , is optimised for noise figure and best overall device sensitivity.

In the local oscillator,  $L_1$  tunes out the crystal capacitance and suppresses oscillation at the fundamental frequency. It may need tuning to suit the crystal.

Circuitry around  $Tr_3$ 's collector is designed for resonance at 153MHz. Output feeds an RC quadrature network comprising  $R_7/C_{18}$  with  $R_6/C_{17}$  and subsequently the mixer local oscillator input ports. Screening is important around the oscillator to prevent sensitivity fall-off due to feed-through to the rf input.

Buffering is provided by  $Tr_{4,5}$  to isolate receiver data output and the POCSAG decoder data input. On leaving the buffer, POCSAG data feeds the MV6639 decoder whose reference is a 32kHz watch crystal. Radio identification code, bit rate selection

### \*POCSAG

Covered also by CCIR RPC No1, Pocsag is the most widely accepted radio paging standard. It accommodates over two-million pager IDs, two of which can be recognised by each MV6639 Pocsag decoder.

An acronym for Post-Office Code Standardisation Advisory Group, Pocsag transmission code comprises at least 576 bits of alternate one, zero sequence preamble followed by batches of code words. Each batch starts with a sync string followed by eight frames dual 32bit code words.

In addition to simple beeping, Pocsag also allows simple messages to be transmitted.



Complete three-chip radio pager for 153MHz uses three ICs. Output is tone only but included in the MV6639 POCSAG decoder is a voltage doubler for powering LCD-readout.

and housekeeping information is held in eeprom. At switch-on, the decoder resets and reads information from this prom.




On receiving a correct message, the sounder receives a low level for 4s then a high level for 12s, unless the signal is terminated via SW<sub>2</sub>.

Antenna matching shown provides the necessary 50Ω source impedance. With it is a curve showing the dip it produces at 153MHz. Variable capacitor VC<sub>1</sub> is capable of tuning the dip to within at least ±5MHz of the resonant frequency. Coupling capacitor C<sub>9</sub> also contributes to the tuning but it should be kept small to maximise Q.

Antenna material should have a high conductivity. This is because the radiation resistance of this type of antenna is very low. Any ohmic loss will degrade efficiency.

Within the note is a description of the procedure for finding the pager's terminal sensitivity, which should be -126dBm or lower.

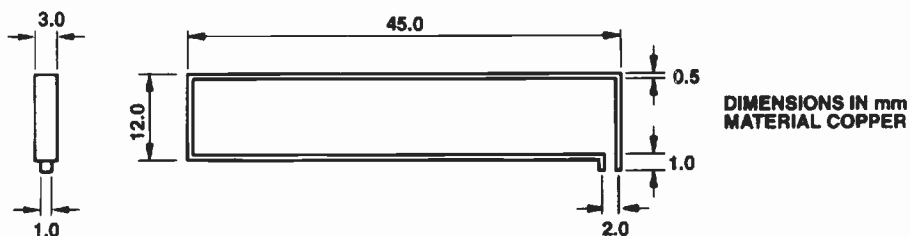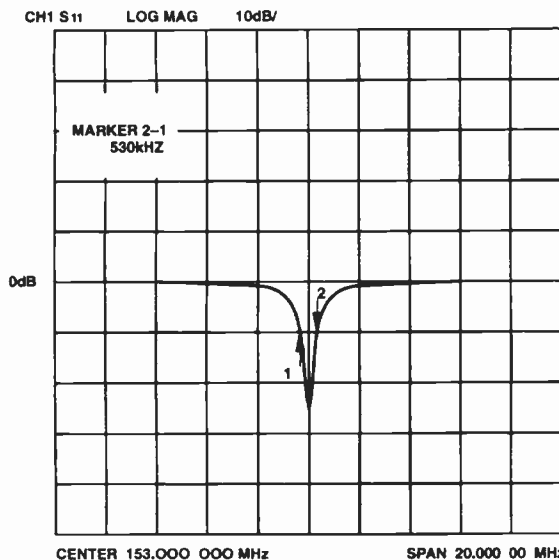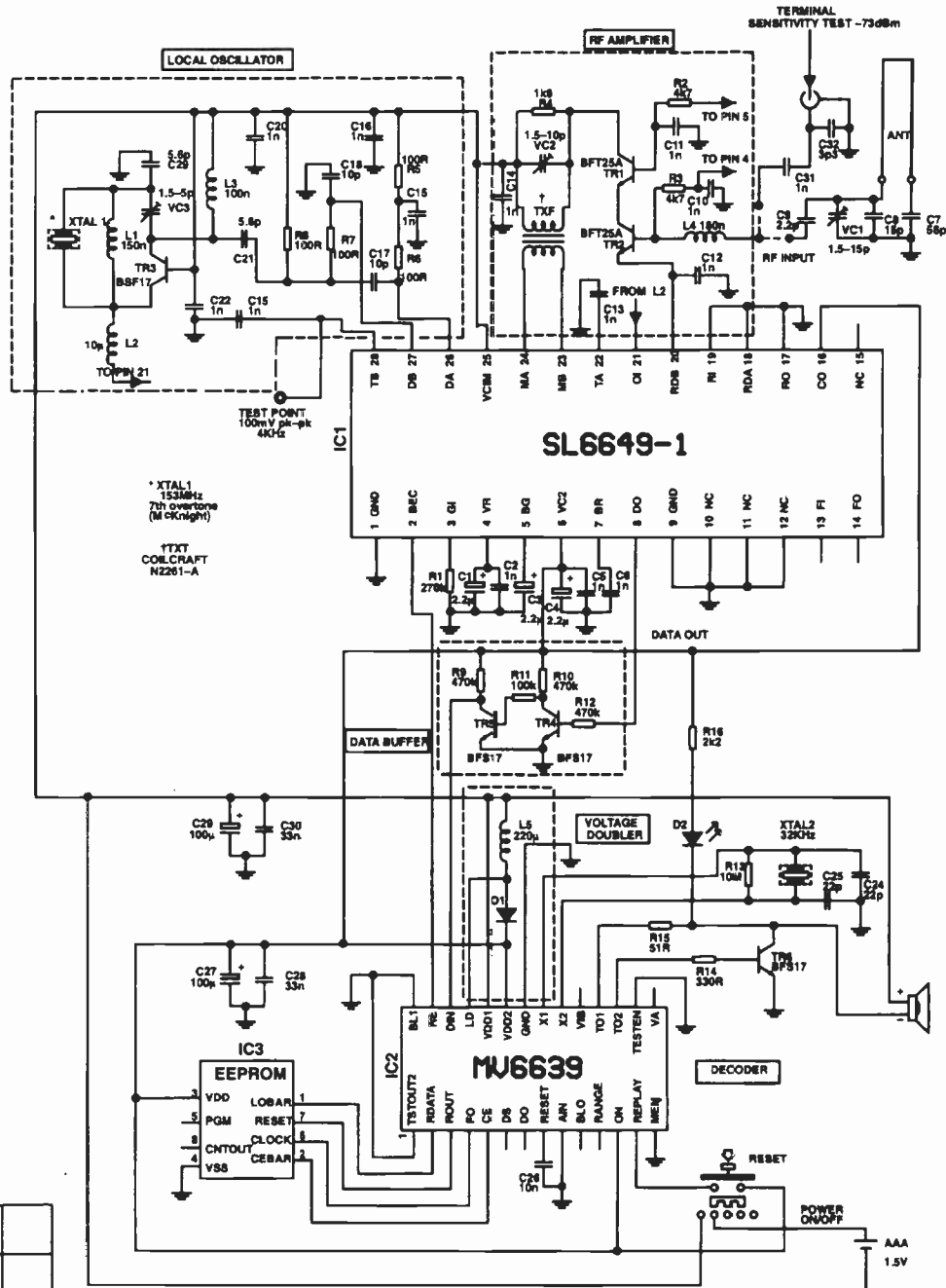GEC Plessey Semiconductors, Cheney Manor, Swindon, Wiltshire SN2 2QW. Tel. 0793 518 000, fax 518 550.



Loop antenna for the 153MHz pager. When combined with the matching components shown on the circuit diagram, its terminal impedance is 50Ω. High-conductivity material such as copper must be used to minimise ohmic losses.

# B&K EQUIPMENT IN STOCK NOW

**Sencore SC61** Waveform Anz-Microprocessor Controlled-60Mc/s Useable 100Mc/S – £350.

**Schlumberger 3531D** – Date Acquisition System – £300.

**Fluke 335A** DC Voltage Standard – £250.

**Marconi Sweep Oscillator 6700A** with 1-2GHZ PI 6730A – £400.

**B&K Sound Level Meter** – Type 2218 – £600.

**EIP 331 18GHz Counter-Microwave** – Led – £700.

**EIP 351D 18GHz Dounter-Microwave** – Led – £800.

**EIP 451 18GHz Counter-Microwave** – Led – £900.

**EIP 545 18GHz Counter-Microwave** – Led – £1,200.

**Systron Donner 6054D** 18GHz Counter – Led – £800.

**Systron Donner 6057** 18GHz Counter – Microwave-Nixey – £600.

**HP5340A 18GHz Counter Microwave** – Led – £1,200.

**HP5340A 18GHz Counter Microwave** – Nixey – £800.

**Systron Donner** – Type 6016 18GHz Counter-Microwave – Nixey – £500.

**Austron Frequency Multiplier** Type 6014 – £250.

**Austron Receiver Loran** – Type 2004 – £250.

**Austron Linear Phase Recorder** Type 1201A – £250.

**Austron Disciplined FX Standard** Type 2010A – £250.

**Microtel MSR-903 Microwave Receiver** – 0.03–18GHz–AM–FM – £2,000.

**Microtel MSR-903 Microwave Receiver** – 0.1–18GHz–AM–FM – £2,000.

**Microtel FC903A** 18GHz FX Counter for above – £1,000.

**Ailtech NM17/27** EMI/Field Intensity Meter – 0.01–32mc/s.

**Ailtech NM37/57** EMI/Field Intensity Meter – 30–1000MC/s.

**Ailtech NM65T** – 1–10GHz.

**Fluke 5205A** Power Amp – £1,200.

**B&K1623** Tracing Filter.

**B&K2607** Measuring Amp.

**B&K2134** Sound Intensity Analyser.

**B&K280** Microphone power supply.

**B&K4408** Two Channel Microphone selector.

**B&K4910** Stroboscope.

**B&K1606** Pre-Amp Vibration.

**B&K4420** Distribution analyser.

**B&K1014** B.F.O. Oscillator.

**B&K2707** Power Amplifier.

**B&K2305** Level Reorders.

**B&K2307** Level Recorders.

**B&K7003** Tape Recorders.

**B&K2615** Charge Amplifier.

**Fluke 9010A** Micro-systems trouble shooter + many pods – £350 + pods or probe.

**Racal/Dana 5002** Wide Band Level Meter.

**Racal/Dana 5006** Digital Multimeter.

**Racal/Dana 5005-4622** Digital Multimeter.

**AVO RM215** – L/2 AC/DC Breakdown Leakage & Ionisation Tester.

**Fluke 80K** – 40 High Voltage Probes – New in Case – £100.

**Watkins Johnson 340A** – 340A–4 RX LF–1–800KC/s AM–FM–CW – Led Readout.

**Watkins Johnson DMS** – 105A Demodulator–AM–FM–SSB – Led Readout.

**Watkins Johnson RS-111-1B-40** VHF Receiver – 30MC/s–1000MC/s – AM–FM–CW – Pan Display.

**Watkins Johnson 373A-2** HF Receiver – 0.5–30MC/s – AM–FM–CW.

**Watkins Johnson Receivers** from 1KC/s to 10,000MC/s also Tuning Heads – Amps–Counter Readouts – Signal Displays – Distribution Amps – HF Multicouplers – IF Demodulators – Signal Monitors etc.


**Racal MA1720** TX Drive Units 1–30MC/s – £500–£750.

**Racal MA1723** TX Drive Units 1–30MC/s – £1,000–£1,500.

**Racal MA1724** TX Drive Units 1.6–25MC/s – £500.

**Racal RA1792** HF RX-100KC/s–30MC/s – £1,000.

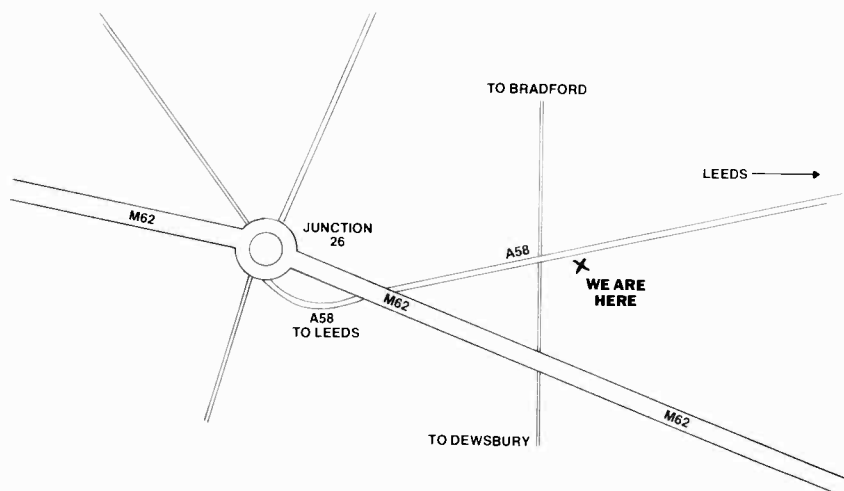**Racal RA1772** HF RX-15KC/s–30MC/s – £600.



## TEKTRONIX 7000 SERIES OSCILLOSCOPES

We can supply all variations of Mainframes and Plug-Ins for this range from stock up to 500MC/S – £300 to £1000.

All items in this advert are in stock at time of printing, most items are held in quantity at both our warehouses which is probably the largest stock of electronic surplus in the UK.

Bulk and trade buyers from UK and abroad are welcome by appointment to bring own transport for quick purchasing and loading of listed and non-listed items.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No. (0274) 684007. Fax (0274) 651160.



Illustration Tracy Martin

# Patently unclear

*Just because it's patented doesn't make it good. And just because it's good doesn't mean it will be successful. **Barrie Blake-Coleman\*** explains how big companies play by the unwritten rules of the patent game.*

***"Anything that won't sell I don't want to invent – a sale is proof of utility and utility is success".  
Thomas Alva Edison  
1847-1931.***

*\*Barrie Blake-Coleman is Industrial Liaison Officer at CAMR, Porton Down.*

A single patent can often embody, in unemotive terms, years of toil and accumulated genius. Eventually, it may become the only accessible record of a project, representing a huge commitment in time, facilities, money and intellectual effort.

Patents emanating from corporate resource-hungry exercises fall into this category. They are usually the outcome of dogged, but straightforward problem solving by large corporate machines able to throw capital at a particular project.

In contrast, there is the patent based on a moment's revelation by a gifted individual. Like the team effort, the inspirational pathway to invention is just as likely to originate in a corporate environment as from the perseverance of an individual.

Whatever the source, the result can be a patent specification worth a lot of money. A successful patent can gain substantial intrinsic

value by virtue of what it cost to attain the information contained in it.

On the other hand, many patents are never tested technically or for their commercial potential and there is no real intention of exploiting their merits. These come about for a number of reasons, not least that of corporate bodies defending current, or future, trading positions.

In the case of the typical gizmo, a device of impressive cleverness stamped all over with "World Patents", we see something that fills a need few of us had spotted, and we stand in admiration at the commercial perception that created it.

But probably greater wealth is buried in the deep undercurrents of industrial technology – and here the patenting game is far more serious. With vast sums committed to r&d, the most important innovations are typically those which reduce production costs. Unfortunately,

## Going for brokers

The person least likely to arrive at a realistic assessment of the business difficulties of promoting an invention is the inventor. Some are street wise and become highly skilled at getting their product off the ground. But most find it difficult to sell their idea, lacking the time, experience and negotiating skills.

The alternative to hawking a patent about is to look for professional help. Reputable brokers for ip (intellectual property) tend to operate on their best estimation of the likely returns on the venture. Some require 'a small fee now and a large piece of the action when I make you rich'. Others will waive the initial fee and simply settle for a percentage when the idea generates

creative product or process engineering enshrined in patents is seldom without risk.

### A strategy for defence

Only a fool would hand a competitor a route to a competing technology, particularly if they haven't paid for it. Even more foolish would be to patent – and so publish – a method showing competitors precisely which technology you have chosen to pursue. This is particularly true if a patent fails to protect procedures that might do the same thing. Thus is born the defensive patent, part of the new policy of strategic patenting.

Organisations committed to aggressive competition may look on strategic patenting as a way of maintaining a product lead. For example, blanket patenting entails patenting a preferred primary technology or process, then filing other patent applications describing procedures which conceivably could do the same thing. No-one needs to establish the validity of these parallel methods, the aim is simply to think up all other possible variations which could bypass the primary patent.

Success in obtaining patents on all your applications means competitors will (supposedly) be technically isolated. Of course, strategic patenting is perfectly legal. It has only one immediate drawback – cost.

Single-nation patenting costs can be modest. But to be truly effective a patent must be filed universally. One "International" patent (Patent Cooperation Treaty), assuming no hiccups, might soak up between £15,000 and £45,000, and servicing/renewal costs are prohibitive. The expense gives perspective to the comparison of patents granted to the leading industrial nations.

The patenting record of the Japanese as compared to the UK, US, France and Germany reflects a willingness to spend money on patents, rather than their technical and commercial value. We should never presume that all patents are viable. Statistics give only the number of patents filed, but give no clue as to commercial fitness. The true value of a patent lies in its ability to be exploited.

income. Yet others will not charge an inventor who can not afford the starting fee but will use the shotgun approach: "I won't make a formal, systematic search, but if I happen to pass a target that needs your invention I'll shoot the idea at them".

All are reasonable methods of sharing the load and in most cases have the merit of giving the broker or agent an incentive to make a real effort.

As a rule, a broker will tell an individual inventor the hard truth about the value of a patent. After all, he or she has the none too difficult task of finding outlets for the manifestly marketable ideas let alone those categorised as a solution looking for a problem.

Falling numbers of British patents say less about the decay of British inventiveness than about the decline of British industrial solvency. In recent times, not only has government and industry neglected to resource the r&d that generates ideas worth protecting, there has been a marked reluctance to finance exploitation – even when lucrative ideas are on offer.

Unless we use our creative talents to create wealth, the wherewithal to protect our ideas will dwindle. With it will go the incentive to patent at all.

### Keeping ahead of the competition

It is naive to believe that competitors will not poach on an originator's "natural" right to monopolise an invention. Patents are designed to protect an idea, but they can invite competition at a time when it could best be done without.

One lesson is that – strategic reasons apart – if you can't afford to do it right with a full inviolate patent portfolio, don't do it at all. As a result, there are probably more technical breakthroughs left unpublished than there are locked up in the patent office.

Indeed, this catch-me-if-you-can policy is an alternative to strategic patenting, though it calls for a lot of confidence in an ability to run faster than the opposition.

An application that fails or is abandoned still constitutes a publication and so can impede a competitor's chances of acquiring a similar patent. It may also cause a collision at some later date with subsequent patents filed by the original applicant.

Nevertheless, the guiding rule should be that if the idea makes commercial sense and has the realistic potential to generate income – then the wise decision is to proceed. Like accident insurance, owning the right patent means you are unlucky if you have to rely on it.

But if the application is for less sound reasons, the maxim remains – a patent is only as strong as the litigation that tests it. A patent grant says only that the examiner is prepared to allow it, not that the examiner is infallible and guarantees the legal invulnerability of the

patent. Furthermore, the rights conferred on an inventor tend to focus on preventing others from profiting from the method embodied in the patent and have little influence on manufacturing rights.

### Finding an interested party

Let's assume you have found someone reputable to pick up your intellectual property (see box **Going for brokers**) and run with it – beware of cowboy patent shops and never sign over rights to an agent.

To attract, the idea must appeal to the recipient and make commercial sense. But any professional involved with ipr (intellectual property rights) can cite a massive array of negative, as well as positive, reasons why a business will or won't acquire patents.

Seldom is it obvious why a company declines interest in a technical acquisition of apparent value to it. Even some of the positive reasons tend to be defensive. For example, a patent might be acquired by a company to ensure it does not impede parallel "in house" development; or the company might want to keep the idea out of the hands of competitors. Or it may want to be certain that no other factor could change the commercial life expectancy of its products.

There are many subtle technical and manufacturing reasons that can prompt companies to turn down a patent. For example:

- failure to understand the implications of a technical development;
- existing product range viewed as sufficient without inviting undue competition;
- appropriate pre-production development/design facilities are lacking;
- new idea departs from core business;
- idea not seen as technically feasible or production orientated (ie requires too many ex-house skills), or
- client has technical confidence but is unfamiliar with or lacks marketing skills to make new idea successful.

But internal politics is by far the most dangerous area for new ideas. Jobs go with products and a new idea may mean changes of responsibilities and skills. It could signal future security for some, but perhaps not for those linked to an old product.

There are also risks in adopting a new product. Those responsible for deciding an acquisition will want it to succeed, perhaps bleeding resource from other areas or depleting already overstretched budgets.

For these reasons, many new ventures never see the light of day and the inventor receives yet another refusal.

### Right decision, right reasons?

Of the positive reasons for acquiring a patent, the most compelling concerns the wish to use it as a major source for income generation or saving money.

The ideal vehicle for a new idea is one with the technical and financial resource quickly to



extract the full value of the patent. Willingness to do so depends on whether the patent is properly understood in terms of a marketing and manufacturing strategy.

A good agent will establish a pyramid of prospective takers for an invention. At the top will be those with an industrial interest that aligns itself with the invention. Then there are those who are evidently diverse in their business strategy and will be open to persuasion as to the business merits of taking on the idea.

Below them comes the option of an entirely fresh business venture, requiring complete start-up from scratch. This clearly would be indicated where finance could be acquired to begin a new manufacturing operation.

In many cases, a company's existing technical expertise in a related area bodes well for a new idea – making it easier to evaluate in terms of the potential commercial worth.

A good agent will pick out the appropriate decision makers in an organisation and put up a convincing argument in favour of acceptance. The aim will be to show that the new idea is technically sound; aligns itself with the company's business interests; demonstrates a return on investment that justifies pre-production and marketing costs; does not divert resource from existing profitable operations, and that the terms of acquisition are not unacceptable.

In short, the sale of the ip must be with a full and sympathetic understanding of the factors that need to be satisfied in the business and manufacturing environment.

### A deal is a deal?

Inventors usually become frustrated with the tedious business of ipr transfer and the apparent inability of prospective takers to appreciate the breathtaking revelations detailed in their patent specification. But the more experienced inventor knows that any recipient of an idea is placing a heavy commitment on themselves.

Many factors have to be satisfied, particularly if rights and licensing agreements are coupled to dates when production is to begin.

Typically, a patent is acquired as a primary risk venture, on a royalty basis or as a split risk (see box **Patent agreements**). The advantage to the recipient in buying out the inventor under a primary risk venture is obvious. In accepting a once-only payment, the inventor surrenders control and interest in the patent. As such, the organisation acquiring the invention is not obliged to use it. Similarly, "option" deals pay the inventor a retainer for exclusive use by the recipient at some future, indeterminate, date.

To win the best deals, inventors must realise they are an integral part of the acquisition. Peddling ipr is as much a public relations exercise as a conveyancing of technical information. Few companies are likely to want an unfamiliar technical process without direct access to the originator. The patent is seldom enough and it is not uncommon for inventors to be overly defensive about their ideas, not even trusting the safety of a patent. So, by

## Patent agreements

**Primary risk venture:** the recipient agrees direct purchase of ownership and the inventor relinquishes all rights and control for a lump sum.

**Royalty:** the inventor is paid a substantial royalty (or moderate lump sum + royalty) on a "shared risk" basis, giving a licence to the recipient and placing a duty on them to go into production.

**'Split risk':** a substantial lump sum is paid upfront for a licence (or ownership) and the inventor takes a chance on when/if use,

deliberate omission or oversight, many specifications are deficient in essential technical features, making it very difficult to repeat the work.

Granted, in certain circumstances the mere exposure to an idea is enough for a technically-competent individual to succeed in producing the same end product. Likewise, the merit of a patent may be in its ability to identify a new application for a well established procedure.

But, whatever the situation, the inventor is usually seen as important to the success of the undertaking. An acquisition should be seen as an exchange: the inventor gets the chance to see his or her idea used – with a possible financial benefit – in exchange giving expert knowledge and a patent.

### Hard negotiation

Having negotiated a half-decent deal, should we think twice before refusing it? The offer could have been long in coming, following years of tramping around the country listening to constant refusals.

Companies usually move cautiously and a decision not to proceed after months of negotiation can take the fight out of even the most enthusiastic of inventors.

The bird in the hand, though not good policy, is all too common and the burden of personal involvement and sundry costs can quickly exhaust the patentee.

But instead of despair the exercise should be reconsidered in terms of whether the objectives are sound. Open-minded applicants will learn from the observations made at various meetings. Perhaps opinion agrees that the idea embodied in the patent is heavily flawed. For the inventor, the facts can be hard to swallow but the more quickly they are, the less painful it will be.

The consensus could be that the idea is good, but the application or approach is in error. Perhaps the industrial sector targeted is actually inappropriate.

But the positive side of getting used to "no" is that it can teach how to get a "yes". Edison (1093 patents) knew the game very well: "It is

manufacture and any royalty on sales commences. Whatever happens, royalties will be at a much reduced percentage.

Royalty agreements are generally exclusive to the recipient or pre-defined in terms of the industrial and marketing area covered. Sometimes, where the invention may spawn other novel products, or where the recipient wants absolute market control, the licensing arrangement may include sub-licensing conditions. In the case of a non-product orientated deal (process or cost saving ideas) the inventor receives a part of the cost saving.

easy enough to invent things and set the newspapers talking, but the trouble comes when you try to perfect your inventions so as to give them a commercial value."

Inventors need to cultivate pragmatism and good business sense to profit by their efforts. Put another way, vendors of ipr need to be able to say no too. If a thing is valuable, it shouldn't be given away. Again, professional help is advisable – if only to suggest where to invest the money.

### On what terms?

Corporate r&d now accounts for the greater proportion of patents and the day of the amateur inventor is past its zenith. Nevertheless, patents are still bartered, exchanged and sold and it is as well to consider how terms are agreed and what constrains typical negotiation.

Few people realise just how much resource is needed when investing in a new idea, particularly if it represents a new product. The importance of the intellectual contribution can easily be overestimated and the mechanics of turning the concept into a reality, underestimated.

Risks can be large, with costs ranging from the staff needed, to the set-up costs. Time spent by personnel in establishing the production and marketing operations must also be included.

So when negotiating a licence for ipr or the transfer of rights, it is in the vendor's interests to agree terms which are favourable to the recipient in the first instance. Recipients should not have their chances of success marginalised because of an over-demanding "money now" agreement. This epitomises the reason for the shared risk approach. Better to wait for long-term rewards than risk short term failure, as can happen when small firms take on new patents requiring substantial investment in time and equipment.

It is a salutary lesson that most of the familiar patented processes took a long time to make it. Typically, the period for a concept to materialise as a product is seven years.

Float glass took seven years to perfect; major advances in petroleum cracking needed

twelve years; nylon was only perfected after six years and, even with an effective recovery process, large scale production of penicillin took twelve years. The transistor only became reality five years after the first crude demonstration of the effect, and production of crease-resistant fibres required another five years of work following the first patent disclosure of the method.

For the invention to succeed, it has to be possible for the user to succeed. That does not mean concluding a bad deal for the vendor.

Some agreements are immensely beneficial to the vendors immediately. But these are generally where the rights transfer instantly confers some financial advantage to the recipient. Being able to market without hinderance a product whose launch would infringe the patent in question is just one example. The further proportionately-smaller investment needed to acquire a licence frees the company to continue profitable trading and eliminates the need to write off the original manufacturing investment.

Unencumbered exchange of licences, where two competitors have both invested in nearly identical products, is another and precludes costly litigation or mutually destructive price wars.

**Rewards of success**

As we have seen, the delay before a product

based on a patent makes its mark commercially can be protracted. The individual inventor has, on past records at least, tended to produce ideas "before their time" and must face an uphill struggle to convince others. Often, too, inventors see economic advantages as secondary to the pleasure of conceiving and demonstrating a novel concept.

But the problems faced in converting ideas into industrial reality remain essentially the same today as in the inventive heyday of the 19th century – as do the rewards if successful. The Black and Decker *Workmate* made its inventor Ron Hickman very wealthy. But, as is now part of inventor folklore, when he first approached B&D they declined to pursue the idea because they thought that too few would be sold to warrant volume manufacture. He set up his own manufacturing operation and when sales clearly started to pick up he offered the idea to B&D again.

A redesign for cost effective mass manufacture resulted in massive sales. In this case, Hickman needed to prove his idea commercially, beyond its technical merits. In the end, the popularity of his product proved that his marketing perception was better than that of the professionals.

It is possible to win and lose at the same time. At the end of the 19th century Westinghouse, desperate to break the hold that his arch rival, Edison, had in dc electrical gen-

eration offered a straight million dollars for Tesla's patents on ac electricity supply. They shook hands on the offer just minutes after their first meeting started. As it turned out, the patents were actually to be worth much more than the fabulous sum agreed. Though Tesla was delighted, Westinghouse later confided that had Tesla demurred, he would have been prepared to go as high as three million dollars.

However, Westinghouse was unsure how his board of directors would react. They were unclear of Westinghouse's intentions and on hearing about the million offered to Tesla thought Westinghouse had taken leave of his senses. Tesla believed he had done extraordinarily well but, ultimately, nearly exhausted all his money on a fine lifestyle and virtually sterile experimentation. Curious, then, that in retrospect Tesla was content with far less than he could have got, Westinghouse achieved more than he expected, while the Westinghouse board thought the whole arrangement was foolhardy as it stood, without realising how bad it could have been. In the end Westinghouse was vindicated but might not have been had he committed the full three million, making it difficult for the company to develop Tesla's technology. A lesson for us all? ■

**R.S.T. LANGREX SUPPLIES LTD R.S.T.**

**One of the largest stockists and distributors of electronic valves, tubes and semiconductors in this country**

Over 5 million items in stock covering more than 6,000 different types, including CRT's camera tubes, diodes, ignitrons, image intensifiers, IC's, klystrons, magnetrons, microwave devices, opto electronics, photomultipliers, receiving tubes, rectifiers, tetrodes, thyratons, transistors, transmitting tubes, triodes, vidicons.

All from major UK & USA manufacturers.

Where still available.

Obsolete items a speciality. Quotations by return. Telephone/telex or fax despatch within 24 hours on stock items. Accounts to approved customers. Mail order service available.

**LANGREX SUPPLIES LTD**  
**1 Mayo Road, Croydon, Surrey CR0 2QP**  
**Tel: 081-684 1166**  
**Telex: 946708**  
**Fax: 081-684 3056**

CIRCLE NO. 129 ON REPLY CARD



**Chelmer Valve Company**

**Worldwide supplier with 30 year's experience**

- **Electron tubes: Transmitting, Industrial, Microwave, Audio, Receiving, Display, etc, etc.**
- **For Maintenance, Spares or Production.**
- **Semiconductors: Transistors, Thyristors, Diodes, RF, Power I/C's, etc.**
- **We have one of the largest stocks in the U.K.**

★ TRY US! ★

FAX, PHONE, POST OR TELEX YOUR REQUIREMENTS  
**1 30 NEW LONDON ROAD, CHELMSFORD, ESSEX CM2 0RG, ENGLAND**

Telephone: (0245) 355296/265865  
 Telex: 995398 SEVEVE G Fax: (0245) 490064

CIRCLE NO. 130 ON REPLY CARD

# CLASSIFIED

TEL 081 652 8339

FAX 081 652 8931

## ARTICLES FOR SALE

### VALVES AND CRTS

#### ALSO MAGNETRONS, KLYSTRONS, VALVE SOCKETS ETC

One million valves in stock for audio industry, receiving, transmitting etc. West European manufactured types a speciality. Fax or phone for quote. Special prices for wholesale quantities. Obsolete sockets available from stock or we can manufacture these in the UK for a minimum of 500 pieces per type. Monthly imports arriving from Russia, China and East Europe.

Testing to special quality - military low microphony etc available on request.

Phone or fax for quotation on any items or send SAE for new 40-page catalogue.

CATHODE RAY TYPES 400 DIFFERENT TYPES IN STOCK. PLEASE ENQUIRE IF YOUR REQUIREMENTS ARE NOT LISTED BELOW.

#### CATHODE RAY TUBES

Please enquire if your requirements are not listed below.

3UP1	£18.00	D 13 630GH	£33.00	F 28-130LDS	£41.00	M31 182GV	£41.00
12CSP4	£27.00	D 14 200GM	£79.50	F31 12LD	£132.00	M31 184W	£41.00
1074H	£43.50	D 16 100GH97	£79.50	LD708	£61.50	M31 190GR	£61.50
1396P	£43.50	DG 7-5	£53.00	M7 120W	£15.75	M31 191W	£61.50
CME1523W	£27.00	DG 7-6	£81.50	M14 100GM	£18.00	M31 325GH	£29.00
CPE1400	£27.00	DG 7-32	£28.80	M17 151GVR	£112.00	M38 100W	£138.00
D9 110GH	£81.50	DG 7-36	£12.00	M23 112GV	£61.50	M40 120W	£61.50
CME1431W	£21.00	DH 7-91	£97.50	M24 121GH	£61.50	MVE-5 (Mul)	£47.00
D 13 611GH	£33.00	F21-12LC	£125.00	M24 122WA	£61.50	SE5FF31	£41.00
4CX250B1TT used but fully tested	£27.00		£27.00	M28 13LG	£61.50	VLS429AG	£26.00
4CX350A Eimac used but fully tested	£29.00						

WANTED: Valves, especially KT66, KT77, KT88, PX4, PX25, Quad, Leak & other Valve Hi-Fi's. Also Transistors & IC's. If poss, send written list.

### BILLINGTON EXPORT Ltd

Unit 1E, Gillmans Industrial Estate, Billingshurst, Sussex RH14 9EZ.

Callers strictly by appointment only.

Tel: 0403 784961 Fax: 0403 783519

Min. UK order £50 + VAT. Min. Export order £100

### PURCHASE FOR CASH

SURPLUS - OBSOLETE - REDUNDANT - EXCESS stocks of electronic, electrical components/accessories, part processed and/or finished products. Please submit preliminary information or lists for immediate response to:

**K.B. COMPONENTS, 21 Playle Chase, Gt Totham, Maldon, Essex CM9 8UT**

Telephone 0621-893204. Facsimile 0621-893180.

### 19" RACK-MOUNT EQUIPMENT?

Frames, cabinets and flight cases for rack and non-rack equipment. A wide range of accessories available. For further information and brochure contact:

GROVESTREAM ENGINEERING SERVICES

29, Silverdale Road, Tadley, Hants, RG26 6JJ

PHONE/FAX 0734 813395

### TURN YOUR SURPLUS TRANSISTORS, IC'S ETC, INTO CASH

Immediate settlement. We also welcome the opportunity to quote for complete factory clearance.

Contact:

COLES-HARDING & CO. 103 South Brink

Wisbech, Cambs PE14 0RJ.

ESTABLISHED OVER 15 YEARS

Buyers of Surplus Inventory

Tel: 0945 584188 Fax: 0945 475216

### TOP PRICES PAID

For all your valves, tubes, semi conductors and IC's.

Langrex Supplies Ltd,  
1, Mayo Road, Croydon,  
Surrey, CRO 2QP  
TEL: 081 684 1166  
FAX 081 684 3056

### ADVERTISERS PLEASE NOTE

For all your future enquiries on advertising rates, please contact

**Malcolm Wells on:  
Tel: 081-652-3620**

## ARTICLES WANTED

### STEWART OF READING

110 WYKEHAM ROAD,  
READING, RG6 1PL.  
TEL. 0734 268041  
FAX: 0734 351696

TOP PRICES PAID FOR ALL TYPES OF SURPLUS TEST EQUIPMENT, COMPUTER EQUIPMENT, COMPONENTS, etc. ANY QUANTITY

103

### WANTED

Receivers, Transmitters, Test Equipment, Components, Cable and Electronic, Scrap, Boxes, PCB's, Plugs and Sockets, Computers, Edge Connectors. TOP PRICES PAID FOR ALL TYPES OF ELECTRONICS EQUIPMENT

A.R. Sinclair, Electronics, Stockholders, 2 Normans Lane, Rabley Heath, Welwyn, Herts AL6 9TQ. Telephone: 0438 812 193. Mobile: 0860 214302. Fax: 0438 812 387. Telephone: 0763 246939

780

### WANTED

High-end Test Equipment, only brand names as Hewlett-Packard, Tektronix, Rhode & Schwarz, Marconi etc. Top prices paid.

Please send or fax your offer to:

HTB ELEKTRONIK

Alter Apeler Weg 5, 2858 Schiffdorf, West Germany

TEL: 01049 4706 7044

FAX: 01049 4706 7049

### WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity. Prompt service and cash.

M & B RADIO  
86 Bishopgate Street,  
Leeds LS1 4BB

Tel: 0532 435649

Fax: 0532 426881

9956



## Cooke International SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS, GENERATORS, OSCILLOSCOPES, POWER METERS, ETC. ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE  
COPIES ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME,  
SEND LARGE "A3" S.A.E. + 50P POSTAGE FOR LISTS  
OF EQUIPMENT AND MANUALS.

ALL PRICES EXCLUDE VAT AND CARRIAGE  
DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY-FRIDAY 9AM-5PM

### Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham,  
Bognor Regis, West Sussex, PO22 0EB

Tel: (+44) 0243 545111/2 Fax: (+44) 0243 542457

HIGH END TEST & COMMUNICATIONS  
EQUIPMENT PURCHASED

## FREE CLASSIFIED

DRANETZ 305c Phase meter for sale 2Hz to 7KHz, 0.01 degrees resolution fully working with plug-ins. O.I.R.O £360. Ask for Mike after 7pm 0483 487189.

WANTED: Very old Philips televisions. Jac Janssen, Hogeham 117D, NL-5104 JD Dongen (Netherlands). Tel: +311623 18158; Fax (office): +3113 624664.

## TENDERS

NORTHAMPTONSHIRE  
COUNTY COUNCIL

COUNTY SUPPLIES

**Police Radio  
Communications  
Equipment  
Maintenance**

Applications are invited from service providers for the maintenance of a wide range of communications equipment for Northamptonshire Police.

Full details obtainable from the Project Co-ordinator, County Supplies, Northamptonshire County Council, PO Box 202, John Dryden House, 8-10 The Lakes, Northampton, NN4 7DB. Tel: 0604-236800 Fax: 0604-237168

Applicants will be required to complete a pre-tender questionnaire, which must be requested by 10th May 1994.

### FOR SALE

16 bit ADC AD13761D analog devices, 62 pieces. Also CS5326 crystal semi, 16 bit ADC. Offers considered. Contact

**Russ Trayling  
0734 311405.**

WANTED: WW2 suitcase/Grandestine sets - German ex-service receivers, transmitters. WHYZ OZ8RO. RA5 Otterstad, Hosterkobuej, 10 DK-3460 Birkerod, Denmark. Tel: 010-45-42815205.

FOR SALE. Dranetz 305C Phasemeter 2Hz - 700KHz, 0.01° resolution fully working £340 ovno. Tel: 0276 682841 Day 0483 487189 Eves. Ask for Mike.

WANTED: One or more, 128 kilobit, ("pick-a-back"), memory chips for original I.B.M. AT computer. Tony Bishop. 071-624 0687.






# ELECTRONIC UPDATE

Contact Pat Bunce on  
081-652 8339

A regular advertising feature enabling  
readers to obtain more information  
on companies' products or services.



**MQP**  
UNIVERSAL PROGRAMMING SYSTEM 2000

Models S2200 and S2400

Gang and Set Programmers for  
24, 28 & 32 pin EPROMs, EEPROMs,  
FLASH, Emulators and OTPs up to 8M bit.

The system 2000 is an ideal programmer for the production environment. Fast programming results in high throughput and rigorous verification leads to improved quality control. Single key functions and checks against misoperation facilitates its use by unskilled staff.

**MQP ELECTRONICS LTD.**  
Tel: 0666 825146  
Fax: 0666 825141  
CIRCLE NO. 142 ON REPLY CARD



## FREE VXI BROCHURE

The National Instruments VXI brochure describes the company's embedded PC and GPIB controllers, MXIbus interface kits for multiple platforms, and NI-VXI, LabWindows, and LabVIEW software for developing and controlling VXI instrumentation systems.

**NATIONAL INSTRUMENTS**  
Tel: 0800 289877  
CIRCLE NO. 146 ON REPLY CARD



**OLSON** FUSED SUPER SLIM  
MAINS DISTRIBUTION PANELS  
WITH DOUBLE POLE  
SWITCHED SOCKETS

**OLSON ELECTRONICS LIMITED**


OLSON ELECTRONICS LIMITED is a leading manufacturer in the field of mains distribution panels of every shape and size to suit a variety of needs. For use in Broadcasting, Computing, Data Communications, Defence, Education, Finance, Health etc. All panels are manufactured to BS5733. BRITISH AMERICAN, FRENCH, GERMAN CEE22/IEC and many other sockets. Most countries catered for.

All panels are available ex-stock and can be bought direct from OLSON.

**Olson Electronics Limited**  
Tel: 081 885 2884  
Fax: 081 885 2496

CIRCLE NO. 143 ON REPLY CARD

## SPICE A/D Simulation

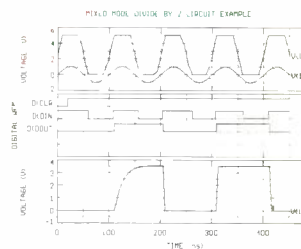

- Mixed Analogue and Digital
- All SPICE 2G6 analyses
- Behavioural Modelling
- Graphical post-processor
- FREE 10 transistor version
- 640K version £395
- 32 bit extd. mem. ver. £695
- Schematic front-end £149

To receive your FREE working evaluation version just send a 1.44MB HD 3.5in disk to: EW+WW Orfer, CRaG Systems, 8 Shakespeare Rd, Thatcham, Newbury, Berks RG13 4DG, Tel (0635) 873670

CIRCLE NO. 147 ON REPLY CARD



**ENGINEERING & SCIENTIFIC PC**

Total Solution for PC-based Industrial and Lab Automation


**ADANTECH**

## ENGINEERING & SCIENTIFIC PC

The new 230 page 1994 PC-LAB catalogue covers an extensive range of PC-based data acquisition, measurement, control, and interface plug-in cards plus supporting software packages for engineering & scientific applications. Also includes 19" rack mounting industrial PCS, custom OEM PC chassis and associated sub-systems.

Please contact integrated measurement systems for a free catalogue copy.

Tel: (0703) 771143  
Fax: (0703) 704301

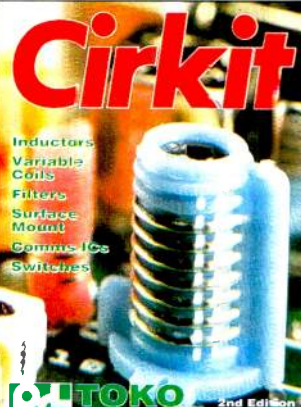

**Cirkit**

Inductors  
Variable Coils  
Filters  
Surface Mount  
Comms ICs  
Switches

**TOKO RF CATALOGUE** 2nd Edition


## 2nd EDITION TOKO RF CATALOGUE

Cirkit have just published the 2nd Edition of the Toko RF Catalogue, featuring details of Tokos' extensive range of RF coils, inductors, filters and comms ICs.

The 128 page catalogue includes many new products such as; Surface mount high current inductors, surface mount multilayer inductors, helical filters at 2.5GHz and a new section of push button and tact switches.

**Cirkit Distribution Ltd, Park Lane, Broxbourne, Herts, EN10 7NQ**  
Tel: (0992) 441306  
Fax: (0992) 441306

CIRCLE NO. 148 ON REPLY CARD

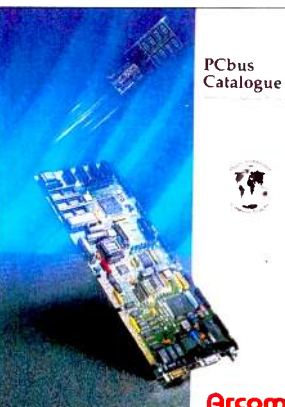

**PCbus Catalogue**

**Arcom**

## INDUSTRIAL PCs

Arcom's PCbus range is expressly developed for embedded control and data acquisition, providing high integrity industrial solutions with:

- \* full range of CPU and I/O functions
- \* industrial EMC enclosures
- \* mezzanine bus expansion
- \* industry standard signal conditioning
- \* Windows I/O drivers with predictable performance.

Arcom Control Systems makes plug-together PC solutions for industry a reality!

Please forward all enquiries to Alan Timmins at: Arcom Control Systems Ltd, Units 8-10 Clifton Road, Cambridge CB1 4WH, UK. Tel: + 44 (0)233 411200 Fax: 410457



**£295.00 + vat**

**High Speed EPROM & FLASH Programming from your PC**

- Programs EPROMs to 4 Mbits/32-pins
- Superfast 8, 16 & 32-bit programming
- Approved algorithms
- Menu driven software included
- Sophisticated editor functions
- Easy file management
- FREE demo disk available

**Stag Programmers Limited**  
Marlfield Welwyn Garden City, Hertfordshire, AL7 1JT UK  
Tel: (0707) 332148  
Fax: (0707) 371503

CIRCLE NO. 149 ON REPLY CARD

**SPECTRUM ANALYSERS**



**\* HP8569B 10MHz-22GHz MICROWAVE SPECTRUM ANALYSERS \***

High-Performance features include external mixing to 115GHz, Internal Preselection  
1.7-22GHz. Wide resolution range 100Hz-3MHz. On-screen readout, direct plotter output. Digital storage. RF Input from -123 to +30dbm. HPIB.

**PRICE.....£5950**

- ADVANTEST TR4133A 199kHz-200GHz Hi-spec spectrum analyser £8500
- TEKTRONIX 492 22GHz spectrum analyser £5000
- IFR A7550 1GHz analyser synthesized, with tracking gen opt £5000

**MARCONI INSTRUMENTS**

2017 **signal generator 10kHz-1024MHz**  
microprocessor-controlled cavity-tuned low-noise AM/FM, +194dbm output. Few only FREE CALIBRATION INCLUDING FREE CALIBRATION - £2000 each.



2019 synthesized AM/FM signal generator 80kHz-1040MHz £1950

**6 to CLEAR £1500 EACH**

- 2030 1.35GHz AM/FM synthesized signal generator £4000
- 6460 6423 power meter 10MHz-12.4GHz 0.3mW-3W £400
- 2040 hi-specification signal generator, w options 1&3 £6000
- 6960 6910 digital RF power meter 10MHz-20GHz 6PIB £1000
- 6912 power sensor 30kHz-4.2GHz for above series £150
- 893B audio power meter £350
- 0A2805A PCM regenerator test set £750
- TF2370 110MHz spectrum analyser £1750
- TF2910-4 non-linear distortion (video) analyser £1000
- TF2914A TV insertion signal analyser £1250
- TF2910 TV interval timer £500

**RALFE ELECTRONICS**

36 EASTCOTE LANE, S. HARROW, MIDDLESEX HA2 8DB  
TEL: 081-422 3593. FAX: 081-423 4009

**NOW IN 40th YEAR**



DISTRIBUZIONE E ASSISTENZA, ITALY: TCL RADIO, ROMA. (06)890763

**TEST EQUIPMENT**

- ANRITSU ME518A PCM portable error rate test set £3000
- BRUEL & KJAER 2511 vibration meter set 1621 filter £2250
- BRUEL & KJAER 2610 measuring amplifier £1000
- BRUEL & KJAER 2307 level recorder £1000
- BRUEL & KJAER 2317 portable level recorder £1850
- BRUEL & KJAER 1616 band pass filter £750
- BRUEL & KJAER 3204 tapping machine £1000
- BRUEL & KJAER 3513 portable vibration analyser £3500
- BRUEL & KJAER 2515 vibration analyser £5000
- AVO RM215L-2 insulation & breakdown tester £650

**2955A/2960 RADIO COMMUNICATIONS TEST SET**

with cellular adaptor with TACS & BAND III software.....£6000

**MUCH MORE, FULLY RE-FURBISHED, FULLY GUARANTEED TEST EQUIPMENT AVAILABLE FROM STOCK. PLEASE REQUEST OUR CURRENT LISTINGS. WE CAN FAX LISTS & SHIP GOODS WORLD-WIDE. HIGH-END EQUIPMENT ALWAYS WANTED FOR STOCK.**

■ CALL US NOW ■

- MAURY MICROWAVE 8650C TNC-calibration kit £1500
- NAGRA IV - S3 tape recorder £2000
- PHILIPS PM5193 synthesized function generator £1500
- PHILIPS PM2534 digital multimeter £450
- PHILIPS PM8272 XY & XI dual-pen analogue plotter £350
- RACAL 2101 frequency counter 21GHz £1600
- RACAL 9038 automatic modulation meter £325, 9009 £300
- RACAL 9038 synthesized AM-FM sig gen 5-520MHz £850
- RACAL 9300 RMS voltmeter -80dB to +50dB £325
- RACAL 9341 LCR catalogue component tester £350
- RACAL-DANA 9302 RF millivoltmeter 1.5GHz £450
- RACAL-DANA 9303 level meter, digital £1000
- ROBERTS & ARMSTRONG 110-cable end-cut-measure unit £500
- TEKTRONIX TM503 SCS03/TG501 PDS06 scope calibrator £2250
- TEKTRONIX 116 digital photometer £250
- TEKTRONIX AM503 current amplifier TM501/A6302 20A probe £1250
- TEKTRONIX AM503/A6303/TM501 100A current probe £1500
- TEKTRONIX 2235 100MHz oscilloscope £950
- TELEONIC 1205A 1-1500MHz sweep generator £1000
- WAVETEK 2000 0-1400MHz sweep generator £750

**HEWLETT PACKARD**



- 331A distortion meter £200
- 339A distortion meter £1500
- 3406A sampling voltmeter £250
- 355C attenuator DC-1GHz 0-11db & 355D 0-120db £125
- 3325A synthesizer/function generator £1500
- 3335A synthesizer/level generator with option 01 £1500
- 3562A transmission test set £1250
- 3562A dynamic signal analyser £7000
- 3711A/3712A microwave link analyser (MLA) with 3793B & 3730B 3736B RF down-converter (1.7-4.2GHz) £4000
- 4192A LF impedance analyser £7000
- 4275A multifrequency LCR meter £5500
- 400FL mV-Meter 100uV-300V/Is 20Hz-4MHz £325
- 415E swr meter £350
- 4274A multi-frequency (100Hz-100kHz) LCR component meter £4000
- 4276A/001 LCZ meter £1750
- 432A/478A microwave power meter 10MHz-10GHz £400
- 432A/R486A uwave power meter 26.5-40GHz (waveguide) £600
- 5342A 18GHz frequency counter £1250
- 5343A 26GHz frequency counter £2250
- 6253A dual power supply 0-20V 0-3A twice £225
- 6825A bipolar power supply/amp -20 to +20vdc 0-1A £350
- 70300A tracking generator plug-in unit £2000
- 70907A external mixer for 7000-ser spectrum analyser £1750
- 7035B X-Y single pen analogue chart recorder £350
- 7790 dual-directional coupler 1.7-12.4GHz (also others) £350
- 8112A pulse generator £250
- 8011A pulse generator 0.1Hz-20MHz £500
- 816A slotted line 1.8-18GHz with carriage 809C & 447B £500
- 8405A vector voltmeter, voltage & phase to 1000MHz £950
- 8406A comb generator £1000
- 8447A RF amplifier 0.1-1300MHz, 22db gain, 0.1W o/p £500
- 8505A network analyser system including 8503A S-parameter test set and 8501A storage normaliser £5000
- 8601A 110MHz sweep generator £500
- 8620C sweep generator, many plug-in units available £call
- 8671A synthesized signal generator 2-6.2GHz £2500
- 8673 2-18GHz synthesized signal generator £7500

**PLEASE NOTE: ALL OUR EQUIPMENT IS NOW OPERATION-VERIFICATION TESTED BEFORE DESPATCH BY INDEPENDENT LABORATORY**

We would be pleased to handle all grades of calibration or NAMAS certification by same laboratory at cost price. All items covered by our 90-day parts and labour guarantee and 7-day 'Right to Refuse' (money back) warranty.

**ALL PRICES SUBJECT TO ADDITIONAL VAT AND CARRIAGE**

CIRCLE NO. 131 ON REPLY CARD

**INDEX TO ADVERTISERS**

	PAGE		PAGE
Anchor Surplus Ltd	380	Lab Center	389
BK Electronics	362	Langrex Supplies Ltd	436
Bull Electrical	359	M & B Electrical	409
Chelmer Valve Company	436	M B Radio (Leeds)	384
Citadel Products Ltd	IFC	M B Radio (Leeds)	384
Dataman Designs	OBC	MQP Electronics	394
Display Electronics Ltd	408	Number One Systems	398
Eriasson Systems	354	Powerware	398
Field Electric Ltd	394	Ralfe Electronics	440
Haleyon Electronics Ltd	394	Seetrax Ltd	358
ICE Technology Ltd	407	Smart Communications	362
John's Radio	387	Smart Communications	394
Johns Radio	432	Stewart of Reading	415
JPG Electronics	390	Surrey Electronics	415
Kare Electronics	440	Telnet	376
Kestral Electronics	390	Those Engineers Ltd	390
Keytronics	363	Tsien Ltd	354

**8051 In-Circuit Emulator £225**

**Cost-effective ICE, Assembler and Source-Level Symbolic Debugger for 8051 family devices**



**Supported Devices:**  
8051/52  
80C51/52  
8031/32  
80C31/32  
(EA\*=0)

**colour catalogue available**

- Adapters for 8751, 8051 (EA\*=1), 80C451, 80C552, 80C562, 80C652, 87C751, 87C752
- Up to 48K emulation memory for program or data
- Powerful windowed menu-driven symbolic debugger
- Built-in assembler - output loads directly to emulator
- Source-level debug ASM, PL/M-51 and C programs
- Optional EPROM and 8751, 8752, 87C552, 87C751, 87C752 programmers available from £39
- 10 day money back guarantee
- Call us today for further information

**KARE ELECTRONICS**  
32 Pear Tree Avenue, Ditton, Aylesford  
Kent ME20 6EB Tel: 0732 844633




CIRCLE NO. 132 ON REPLY CARD



# LIVELINES
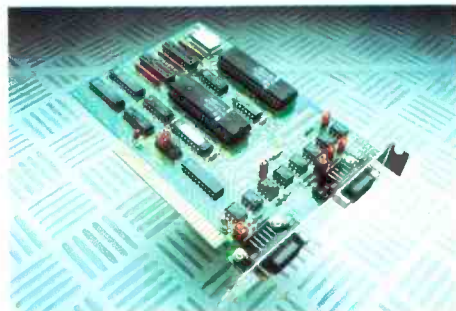
## Dual port serial communications for your PC



The PC 47, 48 and 49AT boards each provide two independent serial ports for any PC/XT/AT(ISA) computer. RS232, RS422 and RS485 standards are supported and all combinations are possible with this range of low power boards.

9 pin D connectors are provided for the RS422 and 485 ports. RS232 can be connected via 9 or 25 way D connectors and charge pump circuitry ensures signal levels in excess of 7V are transmitted.

Interrupt and base addresses are independently selectable for each port, full, half duplex and multidrop communications are fully supported and all boards use the industry standard 82C450, UART.

Designed and manufactured by Amplicon Liveline each board is supplied with a comprehensive technical manual and interrupt driven device driver software is available.

**Write in number 1**

## 750kHz professional data acquisition with Windows support

PC226 from Amplicon Liveline provides 16 true differential 12 bit analog inputs each with dynamically programmable gain. PC226 has sample rates up to 400kHz multichannel and 750kHz single channel, programmable scanning hardware, flexible triggers and a 2048 sample FIFO to ease programming in high speed applications.

PC 226 is supplied with menu driven software for DOS and Windows, LabTech Notebook drivers and comprehensive well documented libraries for most popular high level languages.

Optional software support for Microsoft Windows includes a complete Dynamic Link Library (DLL) and two icon driven packages, Signal Centre for signal capture and analysis and TRACS for process monitoring, visualisation and control.

**Write in number 2**




## 48 lines TTL I/O with 16bit counter timers

PC 14AT available from Amplicon Liveline is a high quality general purpose interface board for PC/XT/AT(ISA) computers.

The board has 48 lines of TTL compatible digital I/O provided as six 8 bit ports four of which can be programmed to be all inputs or all outputs and two which can be split to be 4 inputs and 4 outputs if required. There are also three 16bit counter timers which can be used to generate and measure pulses at up to 5MHz.

An on board 4MHz crystal oscillator is also included on PC 14AT along with LEDs showing the status of a selection of the I/O ports, these can be used as programming and debugging aids.

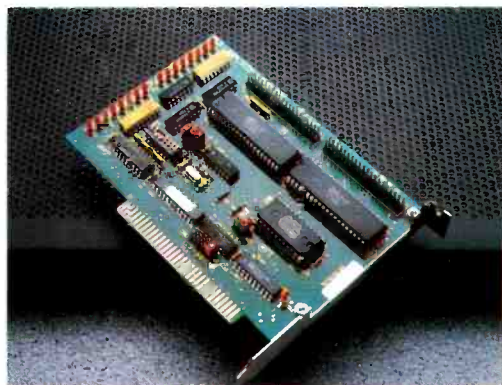PC 14AT is suitable for a wide variety of interface, monitoring and control applications



and an LP (low power) version PC 14LP is available for installation in laptop computers, both boards have flexible base address and interrupt support. **Write in number 3**

# THE WINNING LINE.

-  Large colour catalogue - free
-  24 hour phone and fax lines
-  Knowledgeable engineers for help
-  Same day despatch
-  Excellent support material
-  Certified quality FM 15094
-  After sales support

For up to the minute information on over 1,000 high quality, high specification electronic products, make sure you've got the latest AMPLICON catalogue.

It's not just first class equipment that makes AMPLICON your first choice- we provide outstanding service too: like telesales engineers for pre and post sales support. Easy to manage corporate accounts. Excellent documentation... and same day despatch for orders received before 5 pm.

To order your free catalogue, simply phone the winning line today.

# AMPLICON

## LIVELINE

### 0800 52 53 35

**GET ON... WITH AMPLICON.**

DATA ACQUISITION    POWER SUPPLIES  
INSTRUMENTATION    INDUSTRIAL DATACOMMS  
TEST AND MEASUREMENT



# I want it. What does it do?

- ✓ **8-BIT EPROM**
- ✓ **16-BIT EPROM\***
- ✓ **EEPROM**
- ✓ **SERIAL EEPROM\***
- ✓ **FLASH**
- ✓ **PIC\***
- ✓ **8751\***
- ✓ **EMULATION**
- ✓ **FREE UPGRADES**
- ✓ **TOTALLY HANDHELD**
- ✓ **3 YEAR GUARANTEE**
- ✓ **AVAILABLE TODAY!**

*\*Requires optional modules.*

A 32 pin ZIF socket programs a huge library of EPROMs, EEPROMs and FLASH devices up to 8Mbit. And our unique user loadable Library means that new parts can be added quickly, and at no cost. All software upgrades are free and available for 24hr download from our high speed bulletin boards.

## Emulation

See your code running before committing yourself to an EPROM. With S4's powerful and easy-to-use internal emulation system, download your code to S4, press 'EMULATE', and your target system runs in real time as if an EPROM was plugged in to the socket. Use S4's 'EDIT' command to make minor alterations to your code and see the changes happen *immediately* - just one reason why S4 is used by the world's car manufacturers to develop advanced engine management systems in real time! With S4 emulation there's no need for trailing cables or external power sources; earth loop problems are a thing of the past. S4 even emulates RAM.

## Remote Control

As well as being totally stand alone and self contained, S4 can be operated remotely via it's serial port at speeds up to 115,200 Baud. We supply you with a FREE disk containing custom terminal software and a pop-up TSR communications utility.

## The Company

If you are looking for a supplier with longevity and stability, then you'll be pleased to learn that



Dataman has been designing and selling innovative programmers world-wide for over 15 years. As well as having sales and support offices in both the UK and the USA, we supply the world demand for our products via a network of approved dealers stretching from Norway to Australia.

Size:  
186 x 111 x 46mm  
Weight: 515g

## The Package

S4 comes fully charged and configured for immediate use. You get a mains charger, emulation lead, write lead, personal organiser instruction manual, MS-DOS communications software and a spare Library ROM. Optional modules available for Serial EEPROMS, 40-pin EPROMS, 8751's and PIC's.

## Availability

S4 is always in stock. Phone through your credit card details to ensure *next working day* delivery. Full 30 day no-risk refund.

**DATAMAN**  
Dataman Programmers Ltd

**Credit card hotline:**  
**0300 320719**  
for same-day dispatch

