
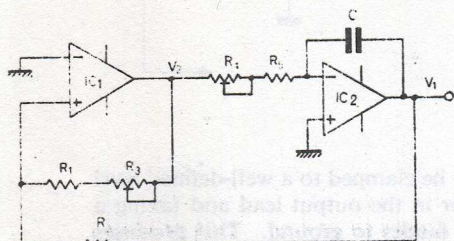


# Wireless World Circard Series 3: Waveform Generators-1
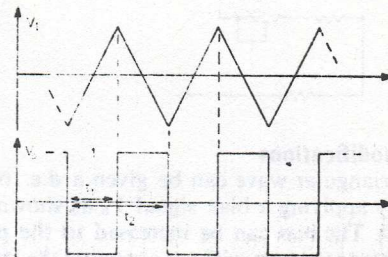
## Basic op-amp square/triangle generator



**Data**  
 IC<sub>1</sub>, IC<sub>2</sub>: 741  
 Supplies:  $\pm 6$  to  $\pm 15$ V  
 $V_2$ :  $\pm 0.9$ V  
 $V_1$ : 1 to 20V pk-pk  
 Frequency: zero to 3kHz  
 $R_1$ : 10k $\Omega$ ;  $R_2$ : 8.2k $\Omega$   
 $R_3$ : 1M $\Omega$ ;  $R_4$ : 220k $\Omega$   
 $R_5$ : 1.2k $\Omega$ ; C: 0.1 $\mu$ F



### Circuit description

When a positive voltage is applied to the input of the inverting integrator, consisting of  $R_4$ ,  $R_5$ , C and IC<sub>2</sub>, the current flow causes C to charge, with its input end positive w.r.t. its output end. Negative feedback through C and the high gain of the amplifier jointly ensure that the inverting terminal retains a potential very close to that of the non-inverting terminal. The output must therefore go negative and provided the amplified input current is much less than the constant current in  $R_5$  and  $R_4$  the output voltage rises linearly with time. At the value of  $V_1$  the negative current fed back through  $R_2$  will overcome the positive current in  $R_1$  and  $R_3$ , and the resulting negative current in the non-inverting input of IC<sub>1</sub> initiates a negative going transition in  $V_2$ . This allows the negative current in the non-inverting input to further enhance the output swing by this positive feedback action. The integrator output then reverses its slope and eventually becomes positive and finally switches  $V_2$  back to its original positive value.


Hence  $V_2$  is a square wave and  $V_1$  a triangular wave. Resistor  $R_4$  gives independent frequency control and  $R_3$  varies the frequency and the magnitude of  $V_1$ .

### Component changes

- The low frequency of operation of this circuit is due mainly to the limited slew-rate of a 741 op-amp as the active element IC<sub>1</sub>. A 301 op-amp will permit frequencies of up to 10kHz to be achieved, the square wave degenerating visibly before the triangle.
- $R_1$  and  $R_5$  limit the current drawn from IC<sub>1</sub> when  $R_4$  and  $R_3$  are in their minimum positions and could possibly be omitted.
- $R_2$  may be varied widely but must not be so low that IC<sub>2</sub> is heavily loaded and not so high that IC<sub>1</sub> does not switch before IC<sub>2</sub> reaches saturation.
- C can also be changed, bearing in mind that the slope of the triangle is inversely proportional to  $C(R_4 + R_5)$ .

# Wireless World Circard Series 3: Waveform Generators-2
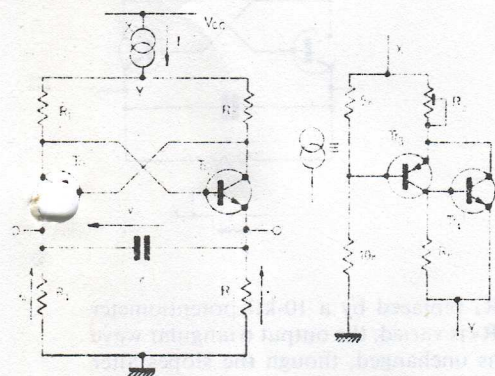
## Emitter-coupled triangular wave generator



### Circuit description

The circuit is an emitter-coupled astable circuit normally fed from a voltage source. This results in sharp transitions in the voltages across  $R_3$  and  $R_4$  at the circuit switching points. These can be eliminated by driving from a constant-current source, so that only the direction of charging current in capacitor C is reversed, the magnitude varying little throughout the cycle. Consider  $Tr_1$  fully conducting,  $Tr_2$  off. The charging circuit is then as shown in the above diagram. Provided the conditions  $v < v_3$  and  $v < v_4$  are maintained, the capacitor charges linearly, but in any case for  $R_3 = R_4$ , any rise in  $v_4$  must be accompanied by an identical fall in  $v_3$ , to maintain a constant total current. Hence there are two outputs  $v_3$  and  $v_4$  which are of identical shape but anti-phase, and are

### Typical performance




$Tr_1, Tr_2$ : BC125  
 $Tr_3$ : BC126  
 $V_{CC}$ : +15V  
 C: 0.1 $\mu$ F  
 $R_5$ : 2.2k $\Omega$   
 $R_1, R_2$ : 330 $\Omega$   
 $R_3, R_4$ : 4.7k $\Omega$   
 $R_6$ : 10k $\Omega$   
 $f$ : 5.3kHz  
 $f \propto 1/C$

$v_3 = v_4$ : Antiphase triangular waveforms 0.4V pk-pk on a d.c. level of 4V. As  $R_5$  is reduced, d.c. level rises towards 8V; frequency increases to 7kHz, as long as triangular waveform is maintained. A ramp voltage at  $2f$  is available at Y.

also good approximations to triangular waveforms. The transition will occur in the above example when  $v \approx -0.5$ V at which condition  $Tr_2$  begins to conduct, positive feedback rapidly completing the transition. Increasing the source current increases the charging rate, and hence frequency, with little change in amplitude. The output has an amplitude of  $\sim 1$ V pk-pk at a mean level of  $\sim 5$ V, depending on the controlled supply current. Supply current is defined by the constant-current source connected between X and Y, where  $R_5$  determines the value of I.
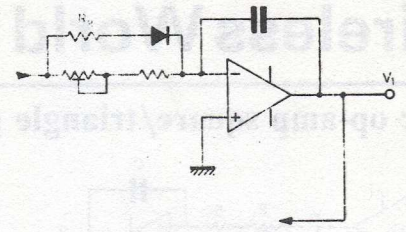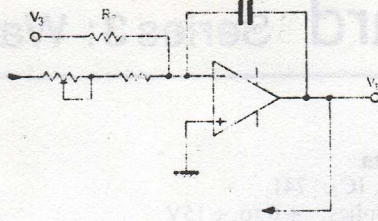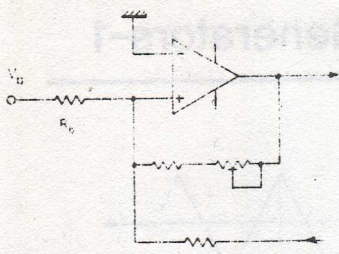
### Component changes

Useful range of C: 1 $\mu$ F to 3.6 nF  
 Frequency range: 0.5 to 130kHz  
 A 20% reduction in  $V_{CC}$  varies frequency by about 5%.



### Circuit modifications

● The triangular wave can be given a d.c. offset of either polarity by applying a bias signal  $V_6$  as shown left in which  $R_6 = 10k\Omega$ . The bias can be increased to the point at which the integrator saturates without changing the state of  $IC_1$ .

● A sawtooth waveform can be achieved by adding a d.c. signal  $V_3$  to the integrator output, as shown middle. The magnitude of  $V_3/R_7$  must be less than  $[V_2/(R_5 + R_4)]$  otherwise the integrator output will not change direction as  $V_3$  changes sign. Time  $t_1$  is greater than  $t_2/2$  if  $V_3$  is positive and  $t_1$  is less than  $t_2/2$  if  $V_3$  is negative. The ratio  $V_3/R_7$  must be comparable to  $V_2/(R_5 + R_4)$  if a large mark-space ratio is required. Independent frequency control through  $R_4$  is lost when this is done but may be regained by varying  $C$ .

● A sawtooth waveform can also be produced by the circuit, right, which does not require an external signal. Any general purpose diode will do. With the diode as shown  $t_1 < t_2$ , but  $t_1 = t_2$  if the diode is reversed. As shown, the integration rate on the negative-going side of the triangle is controlled with  $R_4 + R_5$  and on the positive-going side by  $R_4$  in parallel with  $R_5$ .

● The output of  $IC_1$  may be clamped to a well-defined level by inserting a series resistor in the output lead and taking a pair of back-to-back zener diodes to ground. This produces a better defined integration rate and makes  $t_1$  more nearly equal to  $t_2/2$ . Drive point for the circuits is taken as the junction of the resistor and zeners. Clamping on many i.c.s is possible at low signal levels by means of terminals on the i.c.s (cross ref. 2).




### Further reading

Clayton, G. B. Triangular square wave generator *Wireless World*, vol. 75, 1969, pp.586/7.  
Tobey, G. E., Graeme, J. G. & Huelsman, L. P., *Operational Amplifiers*, McGraw Hill 1971, pp.373-81.  
*Linear Applications Handbook*, National Semiconductor application note AN31-6, 1972.

### Cross references

1. Series 3 cards 2 & 11.
2. Series 2 cards 1 & 3.

© 1972 IPC Business Press Ltd.

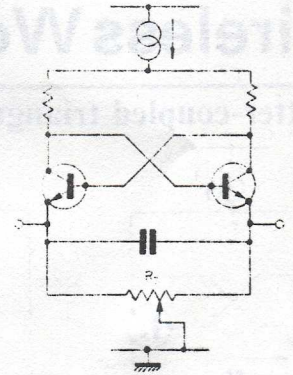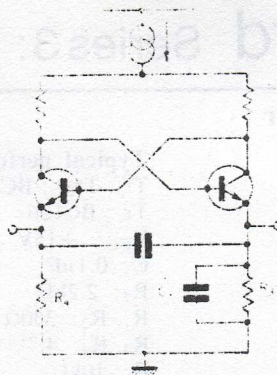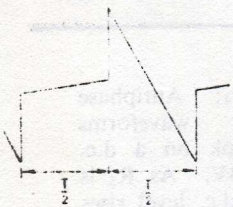

### Circuit modifications

● With  $R_5 = 0$ ,  $C = 0.1\mu F$ , a condition arises where the drive is not from a constant-current source, but the circuit is connected as an oscillator with d.c. supply  $\approx 15V$ . The shape of the output waveform is then as shown left which has a d.c. level of 11V and a swing of 6V pk-pk.

● Voltage spikes occur at the positive and negative peaks of the normal triangular waveforms, due to the change in p.d. across the oscillator causing sharp current spikes from stray capacitance existing across the oscillator: i.e. circuit is temporarily operated from a constant voltage rather than a constant-current source. These can be eliminated by connecting capacitor  $C_x$  in the range 3 to  $10C$ , as shown middle. Typically, for  $C = 0.1\mu F$ ,  $R_5 = 2.2k\Omega$ ,  $C_x = 1\mu F$ . The waveform across  $R_4$  is doubled, the frequency change being  $< 1\%$ .

● Resistors  $R_3$  and  $R_4$  replaced by a 10-k $\Omega$  potentiometer  $R$  as shown right. As  $R_7$  is varied, the output triangular wave peak amplitude remains unchanged, though the slopes alter asymmetrically. Typically for  $C = 1\mu F$ ,  $R_5 = 2.2k\Omega$ ,  $f = 0.5kHz$  when  $R_7$  is set at mid-point. For a setting of 2:1, frequency reduces by 10%.

### Further reading

Hemingway, T. K. *Electronic Designer's Handbook*, Business Publications 1966, pp.191-4.  
Transistorized all-waveform generator, in *Electronic Circuit Design Handbook*, Tab 1971, p.252.


### Cross references

Series 3 card 1.

© 1972 IPC Business Press Ltd.

# Wireless World Circard Series 3: Waveform Generators-3

## Diode-pump staircase generator

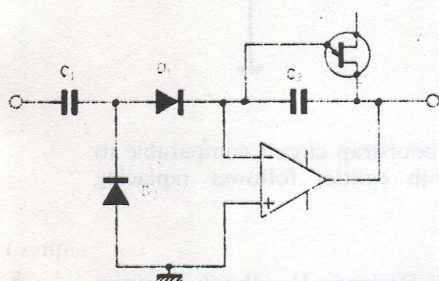

### Typical performance


IC: 741  
 Tr: 2N2160  
 $C_1$ :  $3.3\text{nF} \pm 10\%$   
 $C_2$ :  $3.3\text{nF} \pm 10\%$   
 $D_1, D_2$ : 1N914  
 $V_{in}$ : +3.6V pulses  
 repetition rate: 1kHz/  
 pulse width: 200 $\mu$ s  
 Output step  $\sim 0.28\text{V}$   
 Ramp height  $\sim 8\text{V}$   
 No. of steps  $\sim 28$

Supplies:  $\pm 15\text{V}$   
 $V'$ : +4V

$$\text{Step size} \approx \frac{(V_{in} - 1) C_1}{C_2} V'$$

$$\text{No. of steps} = \frac{\text{height}}{\text{step size}}$$

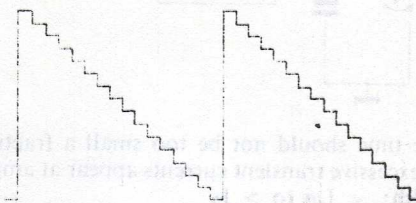Ramp height dependent on unijunction but  $\sim 2V'$



### Circuit description

The basic diode pump has diode  $D_2$  feeding capacitor  $C_2$  (grounded), and without the amplifier. On the first positive input pulse  $D_1$  conducts and provided the pulse duration is long enough the pulse amplitude is shared between  $C_1$  and  $C_2$  - the same charge producing the larger portion of the p.d. across the smaller capacitance. On each succeeding pulse the p.d. established across  $C_2$  opposes any fresh flow of charge, and the step in the output voltage diminishes progressively to zero when the p.d. across  $C_2$  equals the input pulse amplitude. In the circuit shown, the amplifier virtual earth prevents the p.d. across  $C_2$  from influencing the charge flow on successive cycles and the p.d. builds up in equal steps. In each case the charge acquired by  $C_1$  during the pulse is lost to ground through  $D_1$  when the input returns to zero i.e.  $C_1$  commences


each cycle in an uncharged state. Departures from the ideal are: p.d. across each diode when conducting is  $\sim 0.6\text{V}$  for silicon, reducing the effective input pulse amplitude by  $\sim 1.2\text{V}$ ; amplifier input draws a small but finite current that adds a continually varying output due to integration via  $C_2$ ; to make the circuit free-running a device such as a unijunction transistor must be added to provide periodic discharge of  $C_2$ , and such devices contribute additional leakage currents.

### Component changes

$C_1$ : 100pF to  $1\mu\text{F}$   
 $C_2$ : 100 pF to  $1\mu\text{F}$   
 $D_1, D_2$ : general-purpose Si diodes  
 IC: any general-purpose compensated op-amp e.g. 307.  
 $V_{in}$ : 1 to 20V pk


# Wireless World Circard Series 3: Waveform Generators-4

## Unijunction sawtooth generator

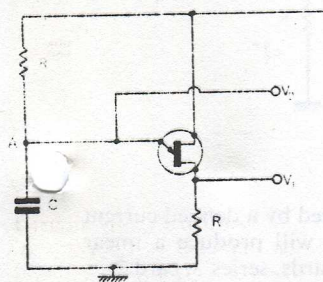
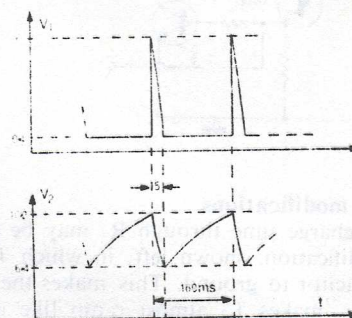
### Data

Typical output waveforms obtained with  
 $R_1$ :  $100\Omega \pm 5\%$   
 $R_2$ :  $10\text{k}\Omega \pm 5\%$   
 $C$ :  $1\mu\text{F} \pm 5\%$   
 $V$ : +15V  
 Tr: 2N2160  
 Supply range can be 4 to 20V at least.



### Circuit description




Circuit is used as a sawtooth ( $V_2$ ) or a trigger pulse generator ( $V_1$ ). Capacitor  $C$  charges through  $R_2$  until the unijunction transistor  $V_p$  is reached and then discharges via  $R_1$  until the transistor changes made at approximately  $0.5V_E$  (sat.);  $C$  then starts charging through  $R_2$  again. Waveform frequency  $\propto 1/R_2C$ . With  $R_2$  fixed at  $10\text{k}\Omega$  and  $C$  varied, the waveform details (apart from the period) remain identical as  $C$  is reduced down to 220 nF. At 10nF,  $V_1$  is reduced to half its previous value and the pulse width increases to approximately 1/10th of the period. At 1nF the pulse height is further reduced and  $V_2$  becomes rounded.

Emitter leakage current modifies the charging waveform and places an upper limit on the value of  $R_2$  for guaranteed operation. The firing potential is temperature dependent

because of the p-n junction p.d. at the emitter junction. This leads to temperature-induced frequency instability which can be compensated for by the insertion of a small series resistor in series with  $B_2$ . The rise in the  $B_1, B_2$  path resistivity with temperature reduces the current and hence the p.d. across this resistor, leaving a larger part of the supply voltage at the junction.
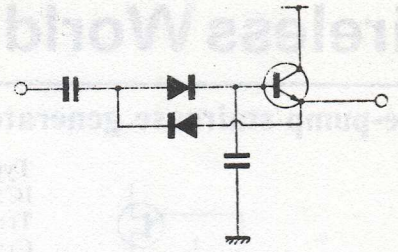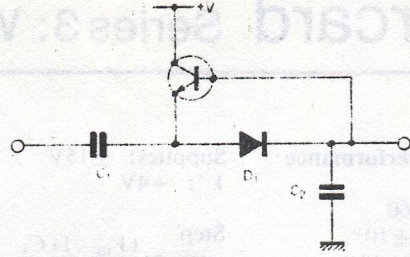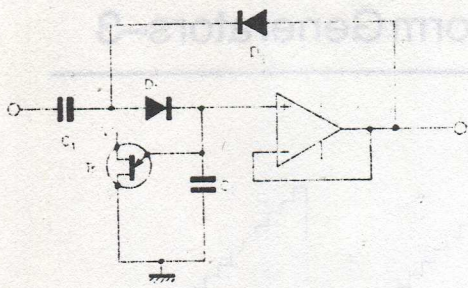
### Component changes

Reduction of  $R_1$  to zero causes  $V_1$  to become zero but has little effect on  $V_2$ . Any standard unijunction transistor may be used. Motorola 2N2646 will produce a smaller lower limit on  $V_2$  and consequently reduced frequency for the same  $C$  &  $R$ .



Pulse rise time should not be too small a fraction of pulse width or excessive transient currents appear at amplifier input.  
Pulse width:  $< 1\mu\text{s}$  to  $> 1\text{s}$   
Mark/space ratio: 1:100 to 100:1  
Repetition rate: 1Hz to 100kHz.

#### Circuit modifications

- Use of bootstrap technique returns r.h. end of  $C_1$  to output through  $D_2$  at end of each positive pulse. This ensures that on next positive pulse  $D_1$  begins to conduct at start of pulse even if p.d. across  $C_2$  and hence at output is greater than pulse height in. Ramp steps of constant size and ramp height limited only by amplifier. Again unijunction may be used to end ramp.
- An alternative range of transistor-pump circuits may be devised. On the positive edge,  $D_1$  conducts and  $C_1$  and  $C_2$  charge with p.d. shared between them in inverse ratio to capacitance. On negative edge,  $Tr_1$  conducts clamping  $C_1$  to just below output while discharging  $C_2$  only by base current of  $Tr_1$ .

- An alternative form of bootstrap circuit comparable to first modification above with emitter follower replacing voltage follower.




#### Further reading

Hemingway, T. K., *Electronic Designers Handbook*, Business Publications 1966, pp.215-24.  
Staircase wave generator, in *GE Transistor Manual*, 7th edition, p.345.  
Clayton, G. B., Resistive feedback networks, *Wireless World*, Aug. 1972, pp.391-3.

#### Cross references

Series 3, cards 4 & 5.

© 1972 IPC Business Press Ltd.

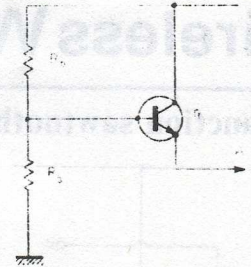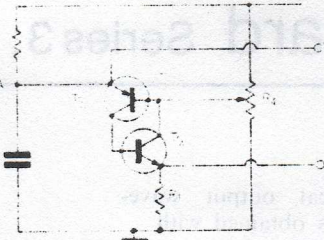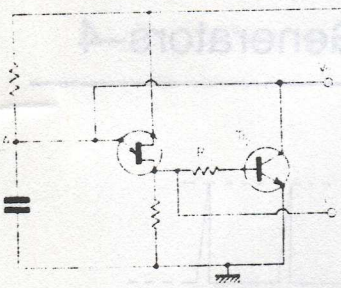

#### Circuit modifications

- Discharge time through  $R_1$  may be greatly reduced by the modification, shown left, in which  $V_2$  is used to short the capacitor to ground. This makes the pulses of  $V_1$  much narrower, makes  $V_2$  almost ramp like and also alters the frequency slightly.
- The unijunction transistor may be replaced by the two transistor version, shown middle, with  $R_1$  100 $\Omega$ ,  $Tr_3$  BC126,  $Tr_4$  BC125 and the potentiometer 2.2k $\Omega$ . The lower value of  $V_2$  in this case comes much closer to zero. The potentiometer is set to the maximum value of  $V_2$  required plus  $V_{be}$ .
- Circuit shown right may be attached to any of the circuits to remove the error arising when the supply is switched on, at which point  $V_2$  is at 0V rather than the minimum value it later achieves on the first discharge cycle. Resistors  $R_5$  and  $R_6$  are chosen so that the transistor conducts, connecting the capacitor directly to the supply, provided the capacitor voltage is less than the eventual minimum value of  $V_2$  (ref. 2).

- Charging resistor  $R_2$  can be replaced by a defined current source e.g. a constant-current source will produce a linear ramp instead of an 'exponential'. (Circards, series 3, card 2).

#### Further reading

- 1 Ultra-linear ramp generator uses UJT to drive Darlington, in *400 Ideas for Design*, Hayden, p.119.
- 2 *Electronic Circuit Design Handbook*, Tab 1971, p.173.
- 3 Triac, UJT & FET give linear ramps, in *400 Ideas for Design*, Hayden, p.128.


#### Cross references

Series 3, cards 2 & 8.

© 1972 IPC Business Press Ltd.


# Wireless World Circard Series 3: Waveform Generators-5
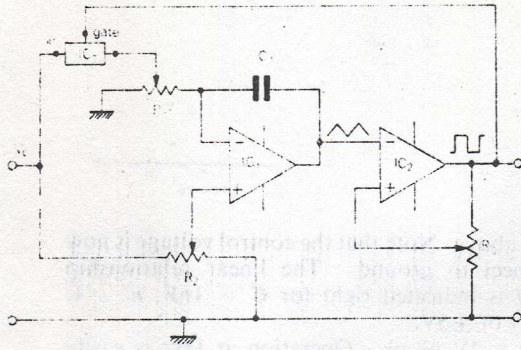
## Voltage-controlled square/triangle generator


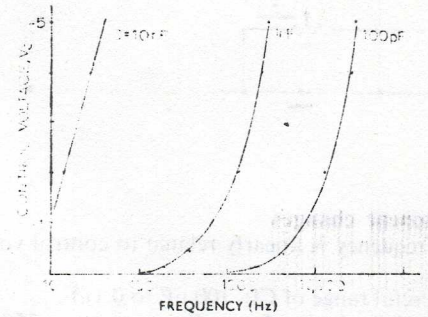
### Typical performance

IC<sub>1</sub>: 741  
 IC<sub>2</sub>: 301  
 IC<sub>3</sub>: 1 (CD4016)  
 Supplies:  $\pm 1V$   
 Control voltage  $V_C$ :  $-1V$   
 Frequency: 660Hz  
 Square wave: 8V pk-pk  
 Triangular wave:  
 4V pk-pk  
 C<sub>1</sub>: 1nF  
 R<sub>1</sub>, R<sub>2</sub>: 100k $\Omega$  (mid-position)  
 R<sub>3</sub>: 10k $\Omega$




### Circuit description

The basic idea of an integrator feeding a Schmitt trigger may be adapted to allow voltage control of oscillator frequency. The square wave output of IC<sub>2</sub> controls an electronic switch (in this case a c.m.o.s. transmission gate) which operates directly on the integrator without need for an additional reversible gain amplifier. A fixed portion of the control voltage is applied to IC<sub>1</sub> non-inverting input through R<sub>2</sub>, while the tap on R<sub>1</sub> is alternately open-circuited and connected to the input. With the switch closed, the inverting input receives a negative current as the full input is applied via part of R<sub>1</sub> to the inverting input, while the non-inverting input is

held at some fraction of  $V_C$ . For an open switch the inverting input is returned to ground via R<sub>1</sub> while the inverting input is still maintained at a constant negative voltage. A convenient setting, if the switch is ideal, is for R<sub>1</sub> to be centre-tapped with the non-inverting input tapped onto R<sub>2</sub> at  $\frac{1}{2}V_C$ . Either can be replaced by corresponding fixed resistors with the other varied to obtain best symmetry i.e. compensating for finite resistance. The Schmitt circuit is conventional while the particular switch may be replaced by any series or series-parallel switch that can make the potential of the inverting input resistor alternate between ground and  $V_C$ .


# Wireless World Circard Series 3: Waveform Generators-6
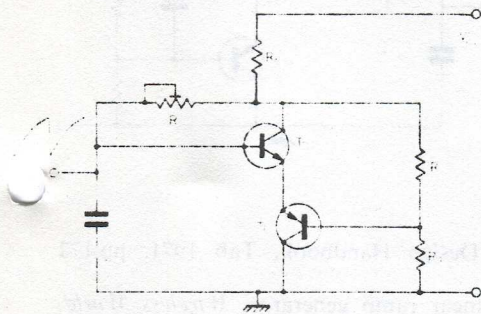
## Complementary transistor sawtooth generator


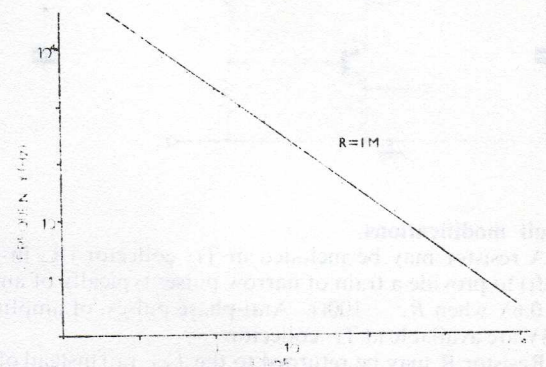
### Typical performance

$V_{CC}$ : +15V  
 Tr<sub>1</sub>: BC125, Tr<sub>2</sub>: BC126  
 R<sub>1</sub>: 2.2k $\Omega$ , R<sub>2</sub>: 22k $\Omega$   
 R<sub>3</sub>: 15k $\Omega$ , R<sub>4</sub>: 1M $\Omega$  (pot)  
 C: 10nF  
 $V_{out}$  oscillates from 2.8V to 7V at 1kHz.  
 Supply current: 0.5mA



### Circuit description


This circuit is related to the corresponding trigger circuit described in Circards series 2. Consider the capacitor in an initially uncharged state. The base potential of Tr<sub>1</sub> is zero and no current flows in either Tr<sub>1</sub> or Tr<sub>2</sub>. The p.d. across R is a large fraction of  $V_{CC}$  provided the current in it and in the potential divider are small enough to avoid a large drop across R<sub>1</sub>. As the capacitor charges the p.d. across R falls and with it the rate of charge. When the potential at the base of Tr<sub>1</sub> exceeds that at the base of Tr<sub>2</sub> by  $\sim 1V$  the transistors begin to conduct. This reduces the potential at Tr<sub>2</sub> collector and at the base of Tr<sub>2</sub> through the potential divider. The increased p.d. between the bases that results completes the positive feedback action, ensuring a rapid switching, with the

p.d. across the capacitor falling to a low value (determined by the saturation characteristics of Tr<sub>1</sub>). Similarly the potential at Tr<sub>1</sub> collector falls. After the switching transient, the recharging cycle begins. Returning R to the collector rather than  $V_{CC}$  provides negative feedback that reduces risk of circuit latching into permanently stable d.c. state.
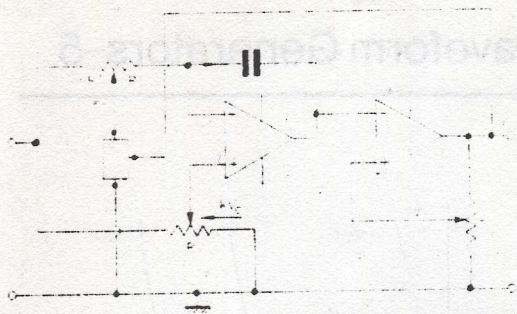
### Component changes

Minimum  $V_{CC}$  = 4V, oscillation ceases at 3.4V. With C = 1nF,  $R_{min} \approx 47k\Omega$ ,  $R_{max} \approx 2.6M\Omega$ . Useful range of C: 47pF to 32 $\mu$ F (tantalum bead). Maximum useful frequency  $\approx 70kHz$ .

Changing the ratio  $R_3/R_2$  alters the voltage to which C charges.




For switch open  $I = \frac{V_C - kV_C}{(n+1)R}$

For switch closed  $I = \frac{kV_C}{R}$

For equal slopes:  $(n+1)k = 1 - k$

$$n = \frac{1}{k} - 2$$

∴ For  $n = 1$ ,  $k = \frac{1}{3}$ .

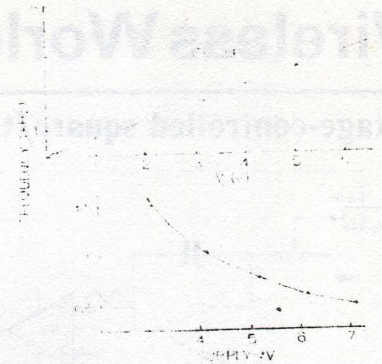

**Component changes**

- Frequency is linearly related to control voltage  $V_C$  up to 4V.
- Useful range of  $C_1$ : 100 pF to 0.1  $\mu$ F.
- Positive feedback via  $R_3$  must be  $< 75\%$  to maintain triangular shape, because of saturation of the IC<sub>1</sub> for the low supply voltage used.
- Adjustment of  $R_2$  controls the mark space of the square wave and slopes of the triangular wave, without altering the amplitude. Typically,  $C = 1nF$ ,  $V_C = -4V$ , mark space can be 1:1.5 at  $f = 1250Hz$  to 17:1 at  $f = 460Hz$ .

**Circuit modifications**

In the circuit shown left, the basic form of the integrator and Schmitt circuit remains the same, but the electronic switch now operates in a shunt mode. A simple analysis to indicate appropriate potentiometer settings to ensure symmetrical

triangles is shown above. Note that the control voltage is now positive with respect to ground. The linear relationship between  $V_C$  and  $f$  is indicated right for  $C = 1nF$ ,  $n = 1$ ,  $k = \frac{1}{3}$  and a supply of  $\pm 5V$ . Triangular output is 4V pk-pk. Operation at 1Hz is easily achieved, but some readjustment of  $R_2$  necessary to retain symmetry. Effect of supply voltage on frequency for the above components is also indicated.




**Further reading**

- LM311 Voltage Comparator. National Semiconductor data 1970.
- 2. Tidley, R. J., Voltage-controlled triangle/square generator. *Wireless World*, May 1972, p.239.

**Cross references**

Series 3, card 11.

© 1972 IPC Business Press Ltd.

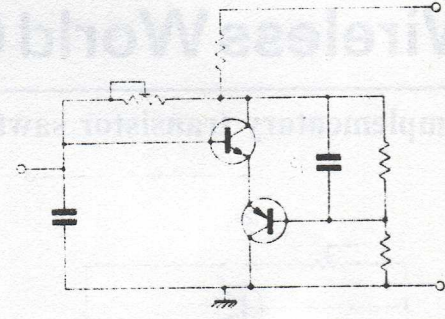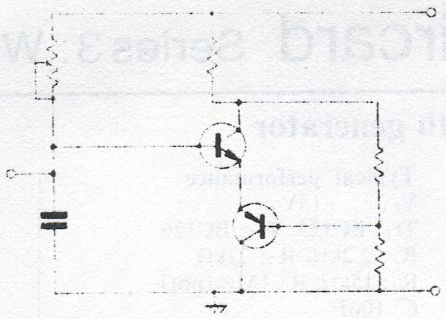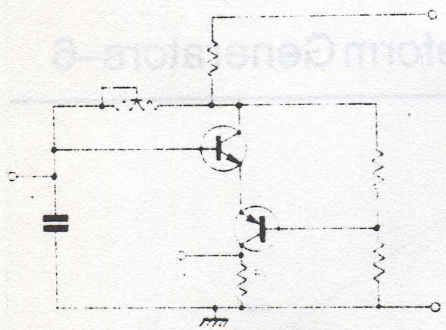

**Circuit modifications**

- A resistor may be included in  $Tr_2$  collector ( $R_2$  in Fig. on left) to provide a train of narrow pulses typically of amplitude 0.6V when  $R_2 = 100\Omega$ . Anti-phase pulses, of amplitude  $\approx 14V$  are available at  $Tr_1$  collector.
- Resistor  $R$  may be returned to the  $V_{CC}$  rail instead of  $Tr_1$  collector, as shown middle. To increase  $R$  above 2.6M $\Omega$ , current gain of  $Tr_1$  could be increased by replacing it with a Darlington unit.
- Speed-up capacitor  $C_1$  may be added, as shown right, to increase the maximum repetition rate.
- The complementary pair may be replaced by a BFR41-BFR81 pair and all resistors can be scaled down by a factor of about ten to give higher current operation, for example, larger output pulses at  $R_4$ . A  $V_{CC}$  up to about 90V may then be used.

**Further reading**

- Electronic Circuit Design Handbook, Tab 1971, pp.172 & 184.
- Cairns, J. B. F., Linear ramp generator. *Wireless World*, vol. 77 1971, p.604.


**Cross references**

Series 2 card 12.  
Series 3 card 9.

© 1972 IPC Business Press Ltd.

# Wireless World Circard Series 3: Waveform Generators—7

## D/A convertor waveform generator

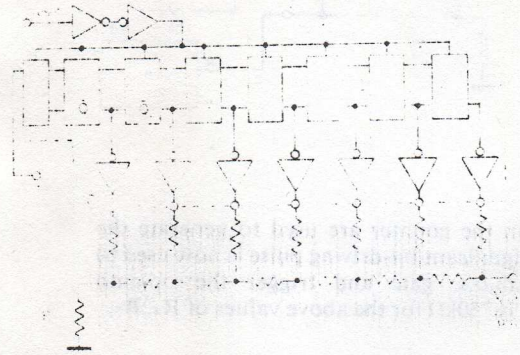

### Typical performance

IC: CD4024A

Supply: +5V

$R_1$ : 94k $\Omega$

$R_2$ : 47k $\Omega$


$f_{in}$ : 12.8kHz

$f_{out}$ : 100Hz i.e. for waveform shown,  $T$  10ms.

For a 7-bit counter, waveform comprises 128 steps.

Minimum input level: 1V

Minimum input pulse: 3.5 $\mu$ s

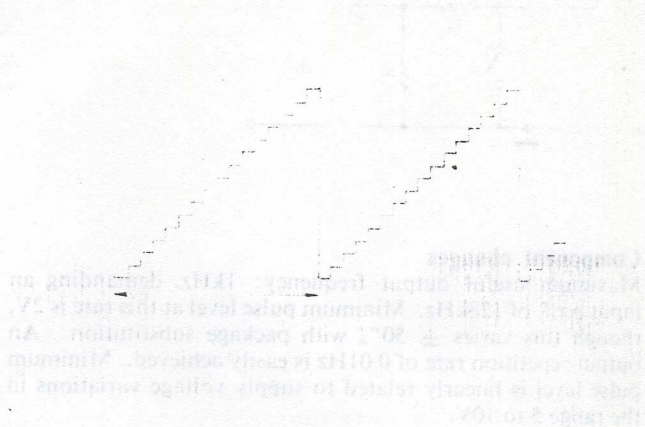


### Circuit description

If the output of a binary counter is used via buffer stages to drive a resistor network, a stepped output voltage is obtained which repeats for each cycle of the counter. If the counter is clocked at a definite frequency then the output frequency is fixed by the division ratio introduced by the counter. If the clock rate is variable so is the output voltage with no change in wave-shape, while modifying the network changes the shape without affecting the frequency. The circuit shown is one example where a seven-stage binary counter feeds a resistive ladder network. The buffer elements are contained within the

IC package and provide a drive voltage which is accurately defined for light loading. Using identical resistors along the chain, the change from logical '0' to logical '1' at  $Q_1$  causes a change at the input to the ladder which is progressively attenuated, halving for each succeeding stage in the counter provided  $R_1 = 2R_2$ . Thus the least significant bit from the counter contributes only half the output contributed by the next bit. The result is an output voltage that is an analogue representation of the total number of bits stored in the counter, and for constant repetition rate and  $n$  stages, staircase waveform results with  $2^n$  equal steps.

# Wireless World Circard Series 3: Waveform Generators—8

## Triggered ramp/trapezium generator

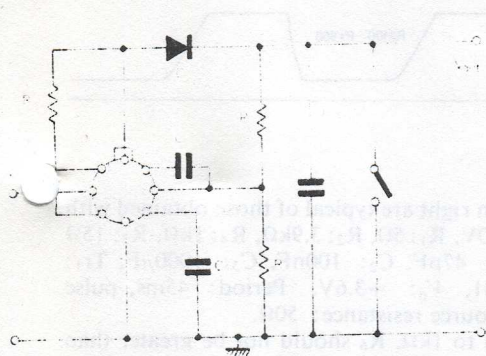

### Typical performance

Supply (V): +10V

IC: LM305


$R_1$ : 220 $\Omega$

$R_2$   $R_3$ : 100k $\Omega$

$C_1$ : 47pF;  $C_2$ : 100nF

$C_3$ : 22 $\mu$ F; D: SD2

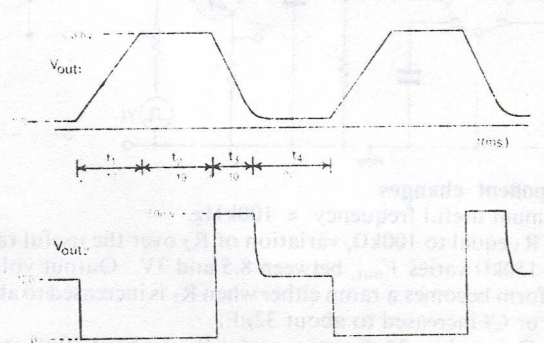
With transistor version (over, left), where  $Tr_1$  is BFR41,  $R_4$  1k $\Omega$ ,  $R_5$  47 $\Omega$ ,  $V_p = +1V$ , period is 66ms, width is 30ms, and source res. 50 $\Omega$ ; waveforms are typically as shown right.


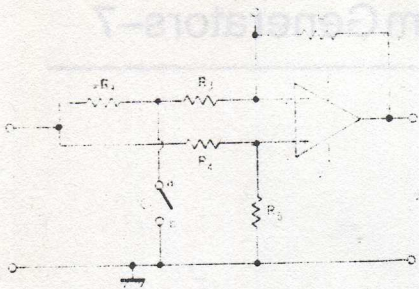
### Circuit description

A ramp with an accurately defined maximum value may be desirable for some applications. This can be provided simultaneously with good control of ramp slope, by using an i.c. voltage regulator having internal current limiting. At switch on, capacitor  $C_3$  is uncharged and the switch is open. The regulator remains in its constant-current mode, charging  $C_3$  until the p.d. across it produces a potential at the junction of  $R_2$  and  $R_3$  that matches the internal reference of the regulator. At this point the regulator reverts to its constant-voltage mode and the output voltage remains constant at a

value that may be controlled by the ratio  $R_2/R_3$ . During the ramp, the current drawn by the potential divider increases as the p.d. across it rises and this, combined with variation in the current-limiting action at different load p.d.s, gives rise to some non-linearity. For this reason  $R_2$  and  $R_3$  are increased though this marginally reduces output voltage stability. Any convenient means may be used to discharge the capacitor to initiate a following cycle and  $Tr_1$  driver from a pulse source is one example.




### Component changes

Maximum useful output frequency: 1kHz, demanding an input p.r.f. of 128kHz. Minimum pulse level at this rate is 2V, though this varies  $\pm 50\%$  with package substitution. An output repetition rate of 0.01Hz is easily achieved. Minimum pulse level is linearly related to supply voltage variations in the range 5 to 10V.

### Circuit modifications

An up and down staircase waveform may be generated by inverting each alternate cycle. A suitable inverting amplifier is shown left. Resistor  $R_3$  is 33k $\Omega$ ; IC<sub>1</sub>:  $\frac{1}{4}$  (CD4016) c.m.o.s. transmission gate. Resistors  $R_4$  and  $R_5$  are 100k $\Omega$ .  $R_4$ : 84k $\Omega$  and  $R_5$ : 16k $\Omega$ .

Diagram on right indicates the overall connection, where

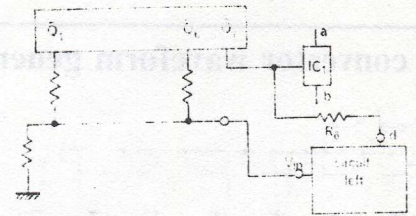

only six outputs from the counter are used to generate the staircase. The most significant bit-driving pulse is now used to switch both the c.m.o.s. gate and trigger the op-amp inverter. Resistor  $R_6$  is 750k $\Omega$  for the above values of  $R_4$ ,  $R_5$ .




### Further reading

COS/MOS Digital Integrated Circuits, RCA, 1972, p.113.  
Naylor, J. R., Digital and analog signal applications of operational amplifiers, *IEEE Spectrum*, May 1971, pp.82-4.  
Staircase-wave generator uses integrated circuits, in 400 Ideas for Design, Hayden, 1971, p.111.  
COS/MOS Integrated Circuits RCA, 1971, pp.72-81.

### Cross references

Series 3, cards 3, 11 & 12.

© 1972 IPC Business Press Ltd.

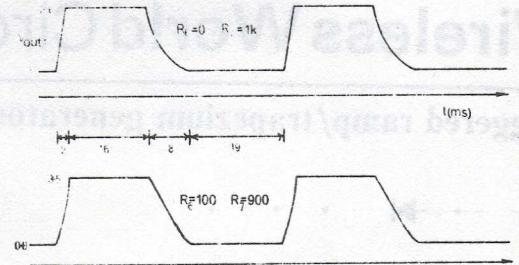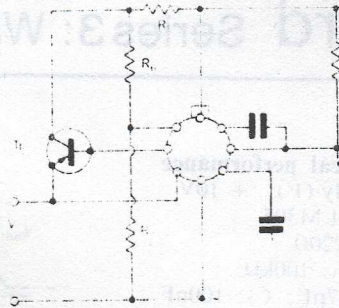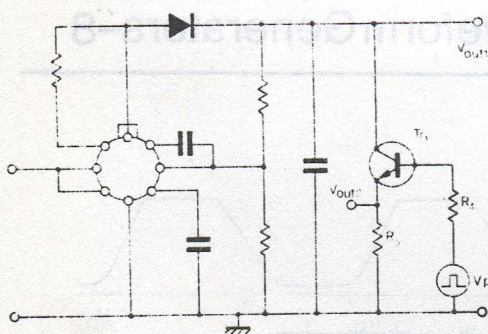

### Component changes

Maximum useful frequency  $\approx 100$ kHz.  
With  $R_3$  equal to 100k $\Omega$ , variation of  $R_2$  over the useful range 22 to 150k $\Omega$  varies  $V_{out}$  between 8.5 and 3V. Output voltage waveform becomes a ramp either when  $R_1$  is increased to about 470 $\Omega$  or  $C_3$  increased to about 32 $\mu$ F.

With  $C_3$  equal to 22 $\mu$ F, max. useful  $R_1$  is about 10k $\Omega$  (ramp amplitude no longer defined by regulator feedback resistors  $R_2$  and  $R_3$ ).

With  $R_1$  equal to 1 $\Omega$ , max. useful  $C_3$  value is about 3000 $\mu$ F.

With  $R_1$  set at 220 $\Omega$ ,  $V_{out}$  becomes a square wave with  $C_3$  of 1nF.

Output voltage waveform can be made triangular by adjustment of time constants, e.g. triangle is 1.2V pk-pk, clamped at 3.6V with  $R_1$ : 330 $\Omega$ ,  $C_3$ : 1000 $\mu$ F &  $R_3$ : 100 $\Omega$ .

### Circuit modifications

To give a higher output current rating and to provide a fold-back (negative resistance region) to the regulator, the circuit can be modified to the form shown in the middle diagram.

The waveforms shown right are typical of those obtained with the following  $V$ : +10V,  $R_1$ : 5 $\Omega$ ,  $R_2$ : 3.9k $\Omega$ ,  $R_4$ : 1k $\Omega$ ,  $R_5$ : 15 $\Omega$ ,  $R_6 + R_7$ : 1k $\Omega$ ,  $C_1$ : 47pF,  $C_2$ : 100nF,  $C_3$ : 1000 $\mu$ F,  $Tr_1$ : BFR41,  $Tr_2$ : BFR81,  $V_p$ : +3.6V. Period: 45ms, pulse width: 26ms, pulse source resistance: 50 $\Omega$ .

With  $R_6 + R_7$  equal to 1k $\Omega$ ,  $R_6$  should not be greater than about 200 $\Omega$  to obviate excessive instability of the regulator due to the negative resistance characteristic. Lower level of  $V_{out}$  is less well-defined than its upper level due to dependence on  $V_{CE(sat)}$  of  $Tr_1$  and  $V_p$  amplitude.

### Further reading

Elmgren, K., *Journal of Physics E: Scientific Instruments* (Letters), vol. 5 1972, p.296.

Linear Integrated Circuits Data Book, National Semiconductor 1971, p.31.

### Cross reference


Series 3, card 4.

© 1972 IPC Business Press Ltd.



# Wireless World Circard Series 3: Waveform Generators-9
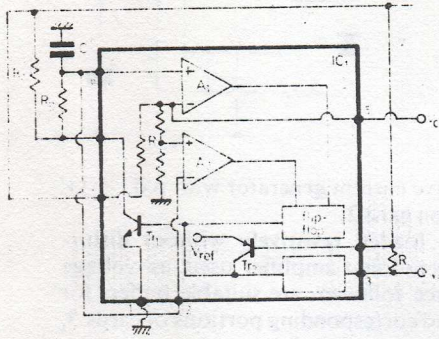
## Stable waveform generator using single i.c.



### Typical performance

IC: NE555V (Signetics)

V: +5V

$R_A$ :  $1\text{ k}\Omega \pm 5\%$

$R_B$ :  $100\text{ k}\Omega \pm 5\%$

C:  $10\text{ nF} \pm 5\%$

f: 710Hz

Charge time  $\sim 0.69 \times$


$(R_A + R_B)C$

Discharge time  $\sim 0.69 \times$

$R_B C$

Period  $\sim 0.69(R_A + 2R_B)C$

Duty cycle:  $R_B / (R_A + 2R_B)$

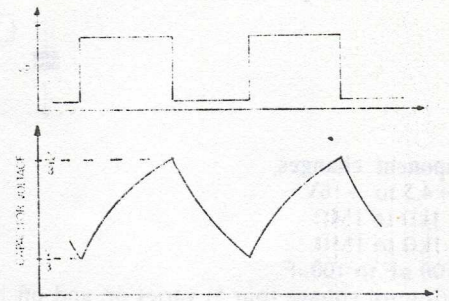

### Circuit description

The i.c. was designed as a versatile timer capable of operation in the astable mode. Frequency and amplitude of the waveform across the capacitor are very stable, and the waveshape can be modified by changing the charge/discharge circuit. Consider the flip-flop in the state that leaves  $Tr_1$  non-conducting. The capacitor charges through  $R_A + R_B$  until the high-level comparator reverses the flip-flop. Transistor  $Tr_1$  conducts, discharging C through  $R_B$  until the low-level comparator returns the flip-flop to its initial state allowing the cycle to re-start.


For  $R_B \ll R_A$  the flyback time is very short, and sawtooth waveforms are possible. Conversely for  $R_B \gg R_A$ , the time-

constants for the two sections of the cycle become comparable. Comparator input currents are low and high values of  $R_A$  and  $R_B$  may be used without deterioration of the waveform or loss of timing accuracy. Capacitor waveform is defined by the comparator levels to lie between  $1/3$  and  $2/3$ .

Unless the load resistance is  $\gg R_A$  and  $R_B$ , buffering of the output from the capacitor is required. A square pulse output is available which can supply load currents of  $> 100\text{mA}$  with respect to either supply line and without disturbing frequency. A reset function is available that over-rides the charging action and a control voltage that changes the comparators' reference potentials i.e. allows modulation.

# Wireless World Circard Series 3: Waveform Generators-10

## Simple multi-waveform generator

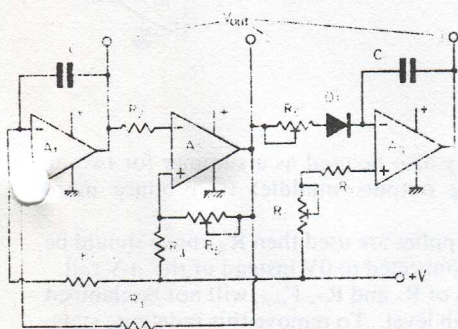

### Typical performance

Supply: +5V

$A_1$ - $A_3$ : LM3900

$R_1$ :  $1\text{ M}\Omega$ ;  $R_2$ :  $100\text{ k}\Omega$

$R_3$ :  $1.2\text{ m}\Omega$ ;  $R_4$ :  $470\text{ k}\Omega$

$R_5$ ,  $R_6$ ,  $R_7$ :  $1\text{ M}\Omega$  pot.

$R_8$ :  $22\text{ k}\Omega$ ;  $C_1$ ,  $C_2$ :  $1\text{ nF}$


$D_1$ : PS101

With  $R_5$ ,  $R_7$ :  $1\text{ M}\Omega$  &

$R_6$ : 0 output wave-

forms are typically as




shown right.

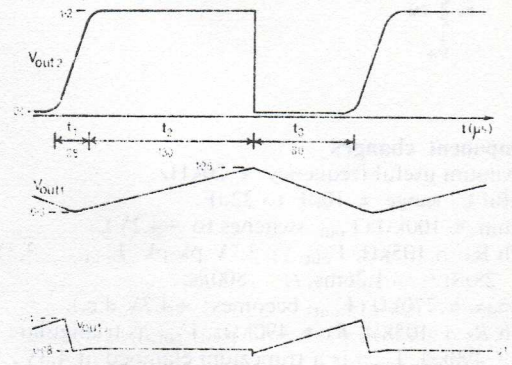
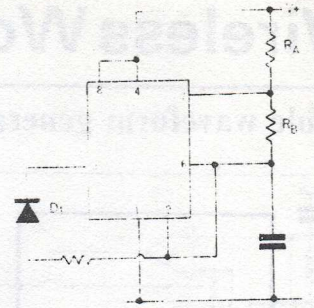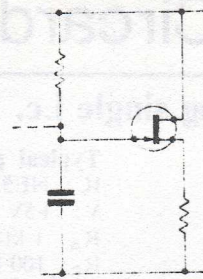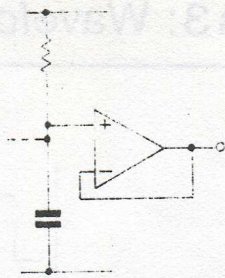
### Circuit description

Operational amplifiers whose output depends on the difference between two input currents can be used as novel waveform generators. Thus  $A_1$  integrates the difference in current in  $R_1$  and  $R_4$ . The former is constant and the latter switches between some positive value and substantially zero (the potentials at the inputs of all these amplifiers are about  $+0.6\text{V}$  w.r.t. the common line, using a single-ended positive supply). If the on-current in  $R_4$  is double that sustained in  $R_1$ , the difference then changes polarity with equal magnitude for the two polarities. The output of  $A_1$  is a linear ramp that at some potential provides a current in the inverting

input of  $A_2$  that initiates a switching action, reverses the output of  $A_2$  and causes the integration to proceed with opposite slope. Resistor  $R_5$  controls hysteresis on  $A_2$ , amplitude of the triangular wave and also frequency. Control of frequency with a single resistor is more difficult than for circuits using conventional op-amp circuits as the ratio  $R_1/R_2$  has to be maintained for symmetrical triangular waves. The output is fed to a second integrator  $A_3$  but at an amplitude sufficient to ensure eventual saturation. Slopes of the edges can be varied by  $R_6$  and  $R_7$ .



### Component changes

V: +4.5 to +16V

RA: 1kΩ to 1MΩ

RB: 1kΩ to 1MΩ

C: 100 pF to 100μF

● Control voltage (pin 5) varies on and off levels in same ratio, allows modulation of frequency, but also changes amplitude of capacitor waveform.

● Addition of silicon diode in parallel with RB, conducting on forward stroke makes charge time dependent mainly on RA. Discharge still depends on RB i.e. Duty cycle adjustable  $\geq 1$ . Diode drop affects accuracy, particularly for low V.

● Output may be synchronized with external waveform fed to control input (pin 5) or triggered by input to trigger point (pin 2).

### Circuit modifications

● For linear ramp generation, constant-current charging is required. Matched transistors (as in RCA CA3084) form current mirror in which collector current of Tr<sub>2</sub> (left) is set by current in Tr<sub>1</sub>, with only small influence of collector-

emitter p.d. Any alternative current generator with p.d.  $< 1V$  may be used such as that on card 2.

● Capacitor cannot be loaded resistively without disturbance to waveform. Operational amplifier used as voltage follower, or f.e.t. as source follower, are suitable buffers for this (middle diagrams), and corresponding portions of cards 3, 4 & 6 may benefit from the same technique.

● For minimum flyback time the discharge current must be increased. If the flyback time is negligible compared to ramp time, then linear voltage control of the latter gives linear control of frequency. Diagram right shows the main output returned through D<sub>1</sub> to the capacitor i.e. using output current capability to reduce flyback time. Fall-time of  $< 1\mu s$  for C = 0.1μF is possible at V = +10V.




### Further reading

Application report: 555 timer, Signetics.

### Cross references

Series 3 cards 2, 4 & 6.

© 1972 IPC Business Press Ltd.

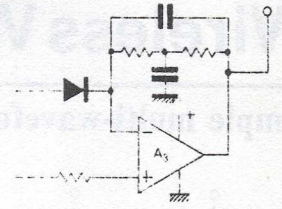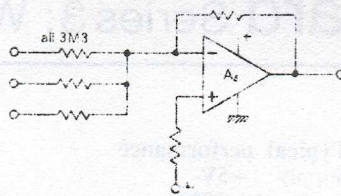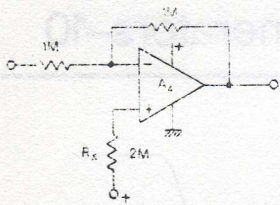

### Component changes

Maximum useful frequency  $\approx 20kHz$ .

Useful C<sub>1</sub> range  $\approx 10pF$  to  $22\mu F$ .

R<sub>5</sub> min  $\approx 100k\Omega$  (V<sub>out1</sub> switches to +4.2V).

With R<sub>5</sub> = 105kΩ, V<sub>out1</sub> = 3.7V pk-pk, V<sub>out2</sub> = 3.3V pk-pk.

t<sub>1</sub> = 28μs, t<sub>2</sub> = 1.26ms, t<sub>3</sub> = 800μs.

R<sub>1</sub> max  $\approx 770k\Omega$  (V<sub>out2</sub> becomes: +4.3V d.c.).

With R<sub>5</sub> = 105kΩ, R<sub>6</sub>  $\approx 490k\Omega$ : V<sub>out2</sub> is triangular.

R<sub>5</sub> > 490kΩ, V<sub>out2</sub> is a trapezium clamped at 4.3V:

R<sub>7</sub> = 0, R<sub>8</sub> = 433kΩ to 1MΩ, V<sub>out2</sub> is a ramp;

R<sub>6</sub> = 0, R<sub>8</sub> = 11 to 433kΩ, V<sub>out2</sub> is a trapezium;

R<sub>6</sub> = 0, R<sub>8</sub> = 5kΩ, V<sub>out2</sub> is a square wave (anti-phase with V<sub>out1</sub>) and may be made a trapezium or a ramp waveform by selecting C<sub>2</sub> between 10pF and 100nF.

### Circuit modifications

● Remaining amplifier in the LM3900 package may be used as an inverter (see left) fed from any one of the existing outputs to provide a pair of antiphase triangular, square, ramp or trapezoidal outputs.

● This amplifier may also be used as a summer for two or more, of the existing outputs (middle) to produce more complex waveshapes.

● If dual polarity supplies are used then R<sub>x</sub> above should be reduced to 1MΩ and connected to 0V instead of the +V rail.

● For certain values of R<sub>6</sub> and R<sub>7</sub>, V<sub>out2</sub> will not be clamped to either a low or a high level. To remove this indefinite state, d.c. feedback can be added to A<sub>3</sub> as shown right.

### Further reading

LM3900 Quad Amplifier, data sheet and application note, National Semiconductor, 1972.

Gledhill, B., Analogue module applications. *Electronic Engineering*, March 1970, pp.64/5.


### Cross reference

Series 3, card 11.

© 1972 IPC Business Press Ltd.

# Wireless World Circard Series 3: Waveform Generators-11

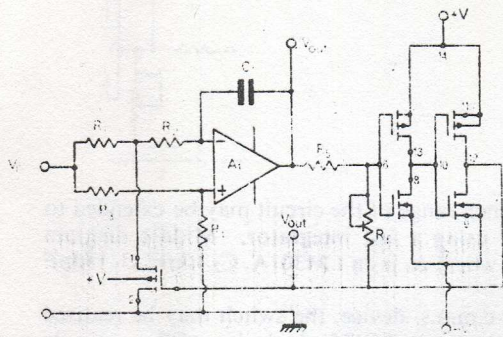
## Op-amp/c.m.o.s. square/triangle generator


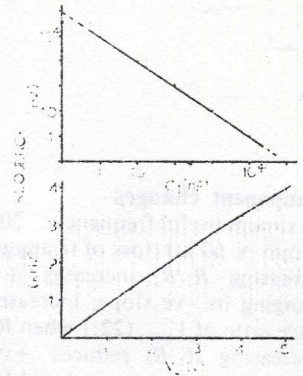
### Typical performance

Supplies: +5V  
 A<sub>1</sub>: 741  
 c.m.o.s. inverters: 1 ×  
 CD4007AE  
 c.m.o.s. switch: 1 ×  
 CD4007AE  
 (R<sub>1</sub> + R<sub>2</sub>): (R<sub>3</sub> + R<sub>4</sub>): 47kΩ  
 R<sub>5</sub>: 100kΩ, R<sub>6</sub>: 1MΩ pot.  
 C<sub>1</sub>: 1nF

Variation of frequency as function of C<sub>1</sub> (V<sub>C</sub> = +1V) and of V<sub>C</sub> (C<sub>1</sub> = 1nF) shown right, with R<sub>1</sub> = 2R<sub>2</sub>, R<sub>3</sub> = 2R<sub>4</sub> and R<sub>6</sub> = 1MΩ. At 10kHz, V<sub>out1</sub> is symmetrical triangular wave of 1.3V pk-pk and V<sub>out2</sub> is 1:1 square wave, 10V pk-pk.



### Circuit description


One limitation to the basic triangle-square generator is that the output amplitude of the Schmitt depends on the saturation limits of the amplifier/comparator used—the hysteresis and the triangular wave amplitude and frequency are device-temperature variable. The circuit shown uses a c.m.o.s. Schmitt whose output swings almost exactly to the supply limits provided it is lightly loaded. Such a circuit can be provided by a single c.m.o.s. package while leaving at least one m.o.s. device free to act as a switch driven by the Schmitt output. The switch may be used to invert the current flow within the integrator, or to invert the gain of a preceding

amplifier where the circuit is to be used as a voltage-controlled oscillator.

The circuit makes very economical use of the lowest-cost c.m.o.s. package to provide triangular and square waves whose amplitudes are constant for constant supply voltage. A further advantage is that the Schmitt current is negligible except at the switching point. The main disadvantage is that the c.m.o.s. threshold voltage, while close to  $V/2$ , has some tolerance and the triangular wave will have a non-zero mean potential.

# Wireless World Circard Series 3: Waveform Generators-12


## Simple wave-shaping circuits

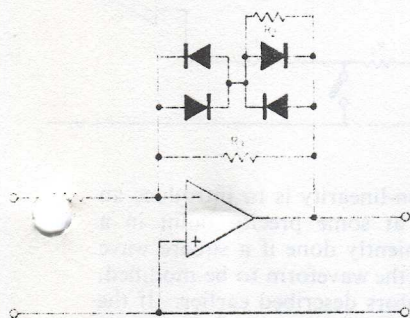




f: 1kHz  
 R<sub>1</sub>: 22kΩ ± 5%  
 R<sub>2</sub>: 100kΩ ± 5%  
 R<sub>3</sub>: 27kΩ ± 5%  
 Diodes 1N914  
 Adjust input triangular wave amplitude for minimum output distortion (~ 2V pk-pk) Distortion < -43dB using distortion factor meter. Visual adjustment possible to -35dB to 40dB.

If a repetitive waveform is fed to an amplifier with a non-linear transfer function, the output waveform differs from that of the input. In the circuit shown the diodes across the feedback resistors are non-conducting for small signals and the output waveform is an inverted version of the input. As the amplitude increases, the diodes are progressively brought into conduction and the output increases more slowly than the input. With the values shown an input triangular wave produces a sinusoidal output with total harmonic distortion < 1% on two conditions: that the input contains no significant d.c. component, and that the input resistor is adjusted for the particular value of input voltage. Component values were determined empirically with the diode non-linearities smoothing the transitions between the defined regions of the transfer function.

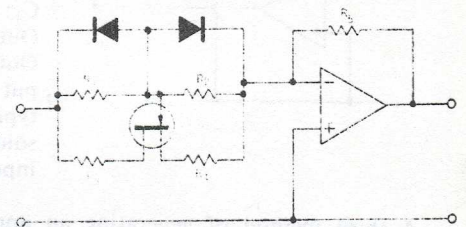f: 1kHz  
 R<sub>1</sub>: 1MΩ ± 5%  
 R<sub>2</sub>: 1MΩ ± 5%  
 R<sub>3</sub>: 470Ω } matched  
 R<sub>4</sub>: 470Ω } to ± 2%  
 Diodes 1N914  
 Adjust input triangular wave amplitude as for 1. Distortion < -40dB. Select R<sub>5</sub> for desired output, typically 1 to 10kΩ.



Placing a non-linear element in the input path also modifies the output, and to convert a triangular wave into an approximate sinusoidal wave an f.e.t. may be used. The source and drain are interchangeable and the diodes ensure that for either polarity of input the f.e.t. is effectively separated with low V<sub>gs</sub>. At low input voltages, the f.e.t. has a low and relatively constant slope resistance, rising progressively as the input brings it towards pinch-off. If the input voltage has  $V \approx V_p$  for the f.e.t., the output peak is just flattened and distortion of less than < 1% is again possible. The gate bias resistors should be large and the source and drain resistors equal. If the f.e.t. or diode networks are reversed, so is their action—the magnitude of the transfer function increases as the input amplitude rises. Any other devices with controlled non-linearities may replace the above.

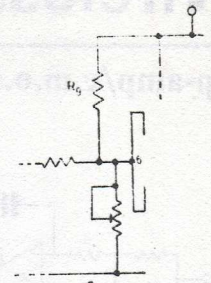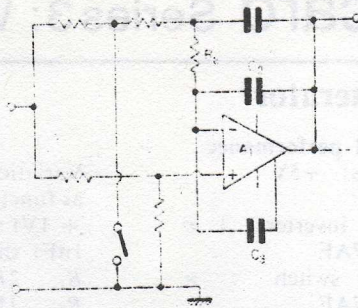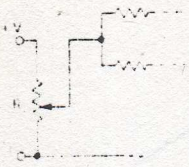

### Component changes

Maximum useful frequency: 50kHz ( $C_1 = 1nF$ ;  $V_C = +1V$ )  
 $R_6$  min  $\approx 60k\Omega$  (loss of triangular wave).  
 Increasing  $R_1/R_2$  increases +ve slope of  $V_{out1}$ , without changing its -ve slope, increases  $V_{out1}$ , and increases mark-space ratio of  $V_{out1}$  (22:1 when  $R_2$  zero).  
 Decreasing  $R_1/R_2$  reduces +ve slopes of  $V_{out1}$ , without affecting its -ve slope, reduced frequency ( $f_{min} \approx 600Hz$ ), and reduces mark-space ratio of  $V_{out1}$  (1:32 min at  $f \approx 700Hz$ ).  
 Increasing  $R_3/R_4$  reduces +ve and increases -ve slopes of  $V_{out1}$ , reduces frequency ( $f_{min} \approx 300Hz$ ), and reduces mark-space ratio of  $V_{out1}$  (1:60 min at  $f \approx 400Hz$ ).  
 Reducing  $R_3/R_4$  increases +ve and decreases -ve slopes of  $V_{out1}$ , reduces frequency ( $f_{min} \approx 20Hz$ ), and increases mark-space ratio of  $V_{out1}$  (500:1 max. at  $f \approx 100Hz$ ).

### Circuit modifications

- Variable voltage control input ( $V_C$ ) may be derived from a potentiometer ( $R_7 \approx 5k\Omega$ , left) connected between +V and 0V rails, which provides first-order compensation for supply voltage changes.

- Useful frequency range of the circuit may be extended to about 250kHz by using a fast integrator. Middle diagram shows an example where  $A_1$  is an LM301A,  $C_2$  10pF,  $C_3$  150pF and  $R_8$  5k $\Omega$ .

- In place of a c.m.o.s. device, the switch may be realized by a discrete transistor e.g. BC125. Inclusion of  $R_9$ , typically 10k $\Omega$ , as shown right allows the triangular output to swing symmetrically with respect to 0V.

- A third output is available at pin 10 of the CD4007AE which provides a square wave in push-pull with  $V_{out1}$ .

### Further reading


Simple square-triangle waveform generator. *Electronic Engineering*, Oct 1972, p.29.

Smith, J. L. *Modern Operational Circuit Design*, 1971, p.224/5.

### Cross references

Series 3 cards 1, 2, 5, 7 & 10.


© 1972 IPC Business Press Ltd.

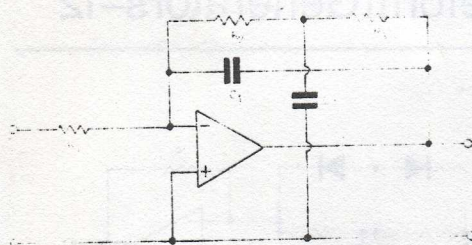

$f$ : 1kHz  
 $R_1$ :  $15k\Omega \pm 5\%$   
 $R_2$ :  $100k\Omega \pm 5\%$   
 $R_3$ :  $100k\Omega \pm 5\%$   
 $C_2$ :  $1\mu F \pm 10\%$   
 $C_1$ :  $10nF \pm 10\%$   
 Output  $\propto (1/fR_1C_1)$   
 Output amplitude  $\approx$  input amplitude for above typical values and sinusoidal/triangular wave inputs.

A third method of generating an approximate sine wave which is not strictly wave-shaping in the above sense is to apply a triangular wave to an integrator with overall decoupled d.c. negative feedback to define the mean output voltage. The integral of a linear ramp is parabolic in form, and the combination of two successive parabolas corresponding to the positive and negative slopes of the triangular waves gives a crude approximation to a sine wave with harmonic distortion of about 4%. The one advantage of this circuit over the previous is that the wave shape is frequency independent, though the amplitude is inversely to frequency.

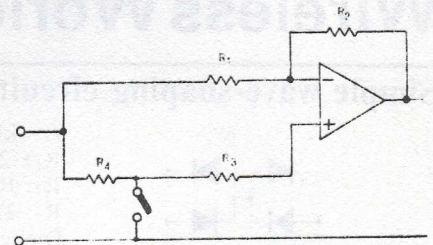Using an ideal switch and  $R_1 = R_3$ , gain is exactly inverted. Switch may be driven by the squarewave of a square/triangle generator, and the circuit then inverts alternate ramps to give saw-tooth.  
 $R_1$  to  $R_4$ : 100k $\Omega$ .



An alternative to controlled non-linearity is to introduce an instantaneous change in gain at some precise point in a waveform. This can be conveniently done if a square wave is available simultaneously with the waveform to be modified, as in the triangle/square generators described earlier. If the triangular waveform is passed through an amplifier whose gain is inverted at each peak of the triangular wave, the result is a sawtooth wave at twice the frequency. The switching of the amplifier gain may be carried out using f.e.t. switches as described in previous cards. A further modification involves the superposition of a portion of the square wave on the sawtooth, producing a sawtooth at the original frequency but with a transient at the ramp mid-point.

### Further reading

Tobey, G. E., Graeme, J. G. & Huelsman, L. P., *Operational Amplifiers*, McGraw Hill 1971, pp.236-81.

Smith, J. *Modern Operational Circuit Design*, Wiley 1971, pp.229-31.

### Cross reference

Series 3, card 7.

© 1972 IPC Business Press Ltd.