

of the voltage divider will evidently be a resistance to cut the 301 volts down to 180. It will have to cause a 121 volt fall of potential with 44 mils flowing thru it. Hence its resistance, according to Ohm's law, is E/I equals $121/.044$, or 2750 ohms. This part of the voltage divider is represented by "R1" of Fig. 2. At the 180-volt tap, the current divides, 20 mils going to the external load, and 24 mils going to the 90-volt tap thru "R2." "R2" will have to cause a 90-volt drop with 24 mils flowing thru it. Hence its resistance is $90/.024$ or 3750 ohms. At the 90-

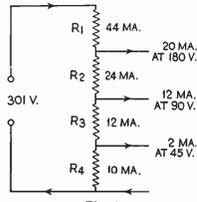


Fig. 2

volt tap, the current divides again, 12 mils going to the external load and 12 mils to the 45-volt tap thru "R3." Figuring "R3" as before, its value is $45/.012$ or 3750 ohms. At the 45-volt tap, the current divides again, finally, 2 mils going to the external load, and 10 mils being "wasted" in "R4," whose resistance is $45/.010$ or 4500 ohms.

This method of calculation is the only correct one, and it is employed by every engineer worthy of the name. The other method, and quaint variations of it, are correct only when no current is drawn from the eliminator; but we cannot see the use of making up an eliminator and then not drawing any current from it.

Now that we have described the proper method of calculating voltage dividers, we will next consider the proper allowances for current at each tap. As we have said before, there is a total lack of uniformity in the amount of current allowed for each tap. There is very little engineering information available, and designers seem to work more on the basis of personal opinion than anything else. Some engineers will allow a current drain of 2 mils at 45 volts, 10 mils at 90 volts, and 20 mils at 180 volts as the average set load. Others will claim that this is all wrong,

and that it should be 5 mils at 45 volts and 20 mils at 90 volts, and 15 mils at 180 volts for the same set. And since no one can present the authoritative figures showing the current drain for 50,000 sets

TABLE 1
5 Mil Voltage Divider

Tap	45V.	90V.	180V.
45V.	4.25	1.37	negligible
90V.	2.20	3.98	1.88
180V.	0.53	1.40	1.25

TABLE 2
10 Mil Voltage Divider

Tap	45V.	90V.	180V.
45V.	3.02	1.30	negligible
90V.	1.53	2.95	1.30
180V.	.38	1.05	.87

TABLE 3
20 Mil Voltage Divider

Tap	45V.	90V.	180V.
45V.	2.05	.96	negligible
90V.	1.12	2.03	.93
180V.	.25	.73	.63

TABLE 4
30 Mil Voltage Divider

Tap	45V.	90V.	180V.
45V.	1.75	.75	negligible
90V.	.92	1.17	.67
180V.	.21	.50	.50

TABLE 5
Currents in the Voltage Divider (See Fig. 4)

I ₁	I ₂	I ₃	I ₄	I ₅	I ₆
10	48	38	37	32.5	1
20	53	33	32	31.5	1
30	58	28	27	30.5	1
40	63	23	22	29.5	1

selected at random over the country, any argument is useless, and eliminators are made more or less on an arbitrary basis. It should be said at this point that this criticism applies to general purpose battery eliminators, which may be used on anything from a two to a twelve tube power supply built into an electric set, and hence can be designed in a correct manner.

The importance of approximately correct current allowance is brought out by a study of voltage variation at the various taps of a divider as the load at each tap is changed. A detailed study of this phenomenon was made with the apparatus shown in Fig. 3. By means of jacks "J1," "J2" and "J3," the current flowing thru each section of the voltage divider could be ascertained. By means of jacks "J4," "J5," "J6" and "J7," the cur-

rent at each tap could be determined. "M1" is a 0-50 d.c. milliammeter, and "M2" a vacuum tube voltmeter to determine the voltage at the various taps. This type of meter was used because it was found that even a high resistance d'Arsonval type voltmeter drawing but one mill at full scale would pull down the voltage more than was tolerable for this study.

The procedure of the experiments was as follows: the load was simulated by means of variable resistors, which were adjusted to take the calculated load. Then, holding all other conditions con-

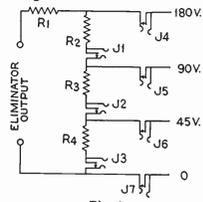


Fig. 3

stant, the 45-volt load was varied, and the effect upon the current and voltage of all taps was measured by means of "M1" and "M2." The same procedure was then repeated with the 90- and the 180-volt taps.

These studies were made with eliminators having a wide range of regulation curves, and with voltage dividers having waste currents of 5 to 30 milliamperes. In all cases the calculated load was assumed to be 20 mils at 180 volts, 12 mils at 90 volts, and 2 mils at 45 volts.

Some of the results obtained are shown in Fig. 4, and Tables 1 to 5. Tables 1 to 4 show the regulation at various taps for voltage dividers having bleed currents of 5, 10, 20 and 30 mils respectively. The figures in these tables show the voltage change produced at any tap of the voltage divider by an increase or decrease of the load by one milliamper. It may be seen for instance in Table 1, that increasing the load resistance at the 45-volt tap to produce a decrease of one milliamper at the 45-volt tap, will cause an increase of 4.25 volts at the 45-volt tap, an increase of 2.20 volts at the 90-volt tap and an increase of .53 volts at the 180-volt tap. A decrease in the load resistance at the 45-volt tap will produce corresponding increases in current of one milliamper will produce drops in voltage instead of increases. These tables

bring out several interesting points. Firstly, they show that better regulation may be obtained by increasing the amount of waste current. Table 1, for instance, shows that a 5 mil voltage divider is very sensitive to any unbalance. Increasing the waste current to 10 mils makes the divider appreciably more stable, and increasing the current to 20 mils almost doubles the stability. The reason for this behavior will be explained below. These tables also show that the 90-volt tap is the one most easily and most greatly disturbed by any change in the load. The tap least disturbed is the 180-volt tap, which feeds directly from the filter without passing thru the divider; and the 45-volt tap is between the two in sensitivity. This tap, however, is very sensitive to change of load values. It is for this reason that many eliminators fail to work satisfactorily when feeding a super-heterodyne or other type of set which has an unusually large 45-volt load.

Table 5 and Fig. 4 show how the voltage divider functions when a change in load takes place. Currents of 10, 20, 30 and 40 mils were drawn from the 90-volt tap, and the changes in the system were measured. The following changes were found to take place in the system:

1. The total current drawn from the eliminator increased, but not as much as the current at the 90-volt tap.
2. The current supplied to the 180-volt tap decreased, and this extra current, together with the extra current that has been assumed, itself, flows to the 90-volt load thru "R1."
3. The waste current flowing thru "R3" decreased, and this extra current flows to the 90-volt load through "R2."
4. The current at the 45-volt tap, then, that only part of the increased load current comes from the eliminator itself. The remainder of the increased current comes from the external system at the expense of the other taps and the waste current. This manner of functioning of the voltage divider explains why the voltages decrease as the load is increased. For, the voltage at any tap depends upon the "IR" drop in the voltage divider, and since the current in sections "R2" and "R3" is a regulator tube with increased load, the "IR" drops are correspondingly reduced. Altho the current thru "R1" is increased, the voltage at this tap, neverthe-

less, is also decreased, for this voltage is the sum of "R3xI3," "R2xI2" and "R1xI1." Since the first two drops decrease more than the last one increases, the net result is a drop in voltage. However, this increase in "R1xI1" serves to make the regulation at this tap much better than it would otherwise be.

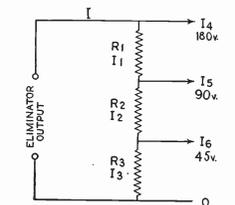


Fig. 4

This manner of functioning also offers an explanation of the superior regulation of high-current, low-resistance dividers. We have seen that the extra current for an increased load is obtained in large part from the waste current. Now, when the waste current is the same in two resistances of different value, it is obvious that the smaller change will occur in the smaller resistance—in this case the low resistance divider.

These results show the extreme importance of fitting the eliminator to the load. For instance, referring to Table 2, we see that the current-voltage slope at the 90-volt tap is 2.95 volts per milliamper. That is, for every milliamper more or less than has been assumed, the voltage at the 90-volt tap will be 2.95 volts lower or higher than has been calculated. It is evident that a miscalculation of 4 or 5 milliamperes will throw the voltage off at the 90-volt tap very badly, and also affect the other taps appreciably. It is also evident that statements like the following are absurd: "This eliminator will deliver up to 40 mils at 90 volts and up to 20 mils at 45 volts." A correct statement would be "This eliminator will deliver up to 40 mils AT THE 90-VOLT TAP and up to 20 mils AT THE 45-VOLT TAP; but the ACTUAL voltages will depend entirely upon the load." While at this point, it may be said by a regulator tube will maintain the voltages at the 45- and 90-volt taps almost absolutely constant within a considerable load variation. The use of these tubes

will be discussed in a forthcoming article.

The conclusions to be drawn from this study are as follows:

1. The voltages obtained from battery eliminators not equipped with regulator tubes are variable, and equal to the nominal voltages only when the presupposed conditions assumed in design are obtained. For other conditions, the voltages will be higher or lower than the nominal voltages, depending upon the amount and nature of the variation from normal.
2. These voltage variations are not due to the regulation of the battery eliminator alone, but are mostly due to the inherent nature of the voltage divider. This is proved by the fact that a voltage divider connected directly to a 220-volt power line has appreciable regulation even though the line itself had perfect regulation for the load that was being drawn.
3. The variations due to variable loads may be minimized by using as heavy a waste current as possible. A waste current of 20 mils or more will produce a quite tolerable regulation, and also introduce other desirable characteristics in the eliminator. It will require a low resistance voltage divider, which is cheaper and easier to make than one of high resistance. At the same time, the heavy current pulls down the eliminator voltage, so that the strain on the filter condensers is materially lessened. In addition, the rise in voltage due to removing the load is minimized.
4. When the current at any tap is increased, the extra current comes mostly from the waste current and the other taps, and the rest is supplied from the eliminator itself.

If you wish to receive the **Aerovox Research Worker** regularly, Free of Charge, fill in and mail this coupon.

Aerovox Wireless Corporation,
70 Washington Street,
Brooklyn, N. Y.

Please put me on the free mailing list for the **Aerovox Research Worker**.

Name _____
Address _____
City _____ State _____