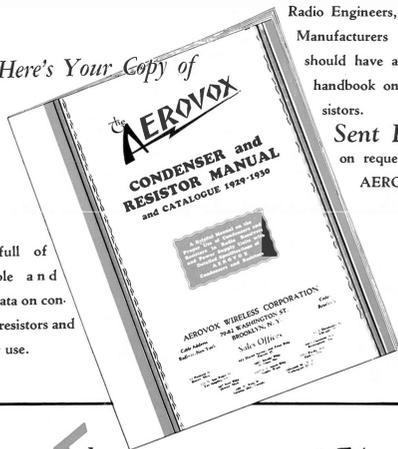


# Just Off the Press!

Here's Your Copy of



32 pages full of new, valuable and interesting data on condensers and resistors and their proper use.

Radio Engineers, Purchasing Agents, Manufacturers and Experimenters should have a copy of this latest handbook on condensers and resistors.

**Sent Free**

on request to

AEROVOX WIRELESS CORP.,  
70 Washington St.  
Brooklyn, N. Y.



**T**HE AeroVox Research Worker is a free publication issued monthly by the AeroVox Wireless Corporation, to keep radio experimenters, engineers and manufacturers abreast of the latest developments in radio.

Special attention is given each month to design problems in connection with radio receivers and power supply units, with special attention on the proper use of resistors and condensers.

During the past year such subjects as the "Measurement of the A.C. Component of Composite Voltages"; the "Construction of a Peak Voltmeter"; "Latest Developments in "A" Condensers"; "Notes on the Design of Filters"; "Principles of Voltage Divider Design"; "How

to Test Condenser Capacities"; "Trouble Shooting in A.C. Receivers"; the "Selection of Resistors for Power Supply Work" and other such subjects have been treated in detail.

If you are not a subscriber, a request to be placed on the mailing list for the Research Worker will bring you this interesting monthly without charge or obligation. Address your request to:

**THE AEROVOX RESEARCH WORKER,**  
AeroVox Wireless Corporation,  
70 Washington Street  
Brooklyn, N. Y.

Radio Editors of magazines and newspapers are hereby given permission to reprint in whole or in part, with proper credit to the AeroVox Wireless Corporation, the contents of this issue of the AeroVox Research Worker.

# The AEROVOX

## Research Worker

The AeroVox Research Worker is a monthly magazine organ of the AeroVox Wireless Corporation. It is published to bring to the Radio Experimenter and Engineer authoritative, first hand information on condensers and resistances for radio work.

Vol. 2 July-August, 1929 No. 7

## How to Increase Efficiency of Circuits by Proper Bypassing and Filtering

Part 1

By the Engineering Department, AeroVox Wireless Corp.


**T**HE subject of metal shielding to prevent coupling effects and their attendant troubles such as oscillation, distortion, motor-boating and generally poor performance of radio circuits has been given considerable attention during the past few years. The equally important subject of preventing coupling by means of filtering to keep signal currents in the circuits where they belong and out of circuits where they are bound to cause trouble has, however, been given but scant attention. In those comparatively few instances where the evils of allowing signal currents to "fraternize" with the direct and alternating currents in the power sources have been recognized, attempts to disassociate them have been more or less half-hearted and doomed to failure.

The evils following the failure to keep these currents in their proper channels were first brought home to the author by George Crom, Jr., of the American Transformer Co., makers of the Amer-Tran line of transformers and power supply units.

To get a clear picture of the effects of coupling in the various circuits of a radio receiver, due to the use of common sources of power in the various circuits, it is necessary to understand the fundamental relations existing in the

circuits of a vacuum tube amplifier.

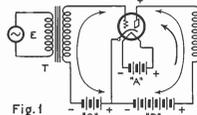The fundamental circuit of a radio amplifier tube is shown in Fig. 1. The tube used is the type in which the cathode is indirectly heated by means of a filament placed within it, but the principle applies equally to all other types of tubes. The current from the "A" battery or A.C. line heats the filament, and the heat developed in



the filament in turn heats the cathode or electron emitting element of the tube. If continuous current, such as is obtained from a storage battery is used to heat the filament, the temperature of the filament and of the cathode will attain a constant temperature, the ideal condition required for best operation of the vacuum tube.

A "C" battery is used in the grid circuit to maintain the grid of the tube at a constant negative potential with respect to the cathode. A "B" battery is used in the plate circuit to maintain the plate or anode, at a positive potential with

respect to the cathode.

If we disregard the grid, we know that current will flow in the plate circuit as long as the "B" battery maintains the plate at a positive potential with respect to the cathode and that the current in the plate circuit will depend on the voltage of the "B" battery (which determines the extent to which the plate is positive with respect to the cathode), and the temperature of the cathode (which determines the electron emission from the cathode).

The use of the grid, however, limits the current in the plate circuit by interposing a negatively charged element between the cathode and the plate. The grid repels to some extent the negative electrons from the filament and prevents them from reaching the plate. The extent to which the grid acts as a controlling "gate" depends on its potential with respect to the cathode.

If it is very negative, its repelling power will be large. If it is only slightly negative, its repelling power will be correspondingly smaller. If it becomes positive with respect to the cathode, it will itself attract electrons instead of repelling them and in that event current will flow in the grid circuit.

The extent to which the grid must be kept negative with respect

**"AEROVOX" PRODUCTS ARE "BUILT BETTER"**

