

Read the Amazing 'HAM RADIO CONFIDENTIAL'

# ELECTRONICS ILLUSTRATED®

By the Publishers of MECHANIX ILLUSTRATED

JANUARY • 35¢

**NEW DX AWARDS FOR  
HAMS, SWLs, BCBers**

**That Amateur  
Radio Brawl—*Wow!***

[Latest Reports  
From The Fight Camps]

See **SWAP SHOP** for  
Big Bargains in  
Electronic Equipment

***Build:***

**CB Channel Slicer**


**2-Tube VHF Receiver**

**Souped-Up Phone Tap**

**Electronic Metronome**

**All-Band SWL Preselector**

**Parasite CW Monitor**

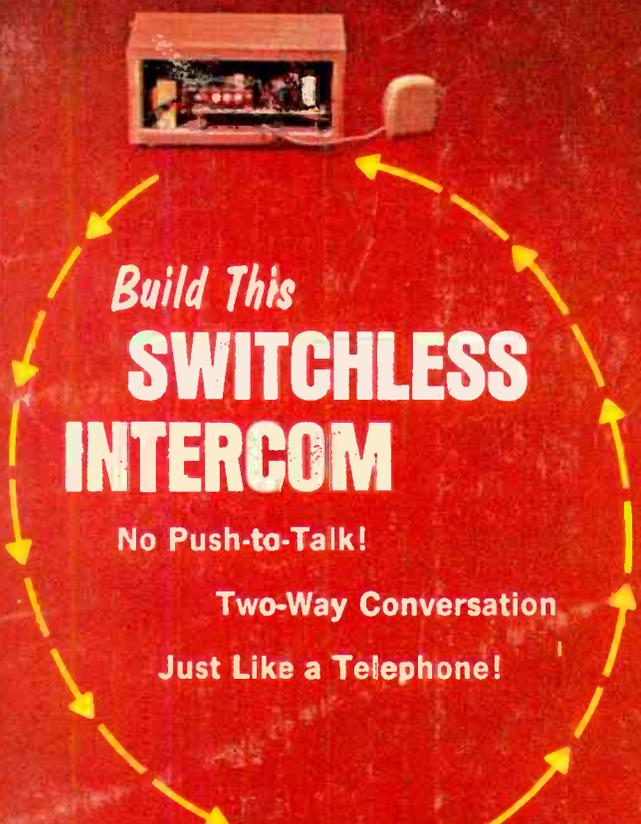

*Build This*  
**SWITCHLESS  
INTERCOM**

No Push-to-Talk!

Two-Way Conversation

Just Like a Telephone!



COMPARE. You'll find—as have tens of thousands of NRI graduates—that NRI training gives you more value than any other home-study Electronics school. From the delivery of your first lessons in the remarkable NRI Achievement Kit we send you on enrolling, to “bite size” easily-read texts carefully programmed with custom-designed training kits . . . NRI can't be beat. Text for text, kit for kit, dollar for dollar—your best home-study buy is unquestionably NRI. (And NRI training costs you less than one semester's tuition at most colleges.)

### New Achievement Kit Starts You Fast

The day we receive your enrollment application we mail out your new NRI Achievement Kit. This attractive starter kit is an outstanding, logical way to help you get an easier, faster start in the training of your choice. It is the first of a number of special training aids developed in the NRI laboratories to make your adventure into Electronics exciting, meaningful. What's

in it? Your first group of lesson texts; a rich, vinyl desk folder to hold your material; the industry's most complete Radio-TV Electronics Dictionary; valuable reference texts; lesson answer sheets; envelopes; pencils; pen; engineer's ruler; even postage. No other school has anything like it.

### Build, Discover with NRI Equipment

Electronics comes alive with NRI training kits. What better way to learn than by *doing*? NRI pioneered and perfected the “home lab” technique of training at home in spare time. You get your hands on actual parts to build, experiment, explore, discover. NRI invites comparison with training equipment offered by any other school. Begin *now* this exciting program of practical learning. Whatever your need . . . whatever your education . . . there's an NRI instruction plan for you, at low tuition rates. Get all the facts. Fill in and mail the postage-free card today. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016

## NOW 10 WAYS to Train at Home with the Leader

### 1. TELEVISION-RADIO SERVICING

—Learn to fix black-and-white and color sets, AM-FM radios, stereo hi-fi, etc. A profitable field for part or full-time business of your own.

### 2. COMPLETE COMMUNICATIONS\*

—Teaches and gives actual practice in operation, service, maintenance of AM, FM, and TV broadcasting stations. Also covers marine, aviation, mobile radio, facsimile, microwave, radar.

### 3. INDUSTRIAL-MILITARY ELECTRONICS

—From basic principles to computers. A comprehensive training plan that starts with fundamentals, then covers servos, telemetry, multiplexing, phase circuitry, other subjects.

### 4. FCC LICENSE\*

—Specifically designed to prepare you for First Class FCC Radiotelephone License exams. You

begin with Electronic fundamentals, advance to required subjects covering equipment, procedures.

**5. MATH FOR ELECTRONICS** —A brief course for engineers and technicians who need a quick review of math used in industry, communications, government jobs. Short-cut formulas, digital number systems, much more.

**6. BASIC ELECTRONICS** — Concise course in modern Electronic terminology and components. Practical, useful information to help you understand the field, give you some technical knowledge of Radio-TV, Electronics.

### 7. AVIATION COMMUNICATIONS\*

—Prepares you to install, maintain, service aircraft equipment like direction finders, ranges, markers, Loran, Shoran, Radar, landing systems. Prepares you for

FCC License exams.

### 8. MOBILE COMMUNICATIONS\*

— Learn to install, maintain mobile equipment and associated base stations. Covers transmitters and receivers used by police, fire departments, taxi companies, etc. Prepares for FCC exams.

### 9. MARINE COMMUNICATIONS\*


— Covers transmitters, direction finders, depth indicators, Radar, Sonar, other equipment used on commercial ships and pleasure boats. Prepares you for FCC License exams.

### 10. ELECTRONICS FOR AUTOMATION

—Not for beginners, but for men with some fundamental knowledge of Electronics who want an understanding of Automation. Process control, ultrasonics, telemetering and remote control, etc.

\*NOTE: You must pass your FCC License exams (any Communications course) or NRI refunds in full the tuition you have paid.

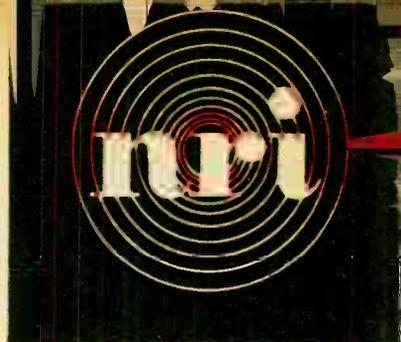*The Oldest and Largest  
School of its Kind  
in America*



**WHERE YOU TRAIN IS AS IMPORTANT  
AS YOUR DECISION TO TRAIN**

# At NRI you are backed by 50 Years of leadership in home-study training for Electronics • Automation • TV • Radio



**J. E. Smith,  
Founder—1914.**

Fifty years ago, a school teacher named James E. Smith started giving extra instruction to four of his students in the "mysterious" new field of radio. From that small beginning, National Radio Institute has grown to be America's largest home-study school in the many fields of Electronics. Nearly three-quarters of a million students have enrolled over the years. This vast experience is behind NRI's

meaningful, interesting, easy-to-understand methods of training; methods that make Electronics a practical subject for almost anyone to learn no matter how much or how little formal education he has.

But experience is only the *base* upon which NRI is built. Today there is a staff of more than 150 dedicated people working with you as a "class" of one, keeping training material up-to-the-minute, providing consultation services as you train, advising you about new developments in Electronics, even helping you with job placement when you're ready. Ask men whose judgment you respect about NRI training. And send for the catalog we offer. Read about opportunities in Electronics, about new developments, about NRI itself and the variety of training plans open to you at reasonable cost. Mail the postage-free card today.

**JOIN MEN LIKE THESE—  
TRAIN FOR SUCCESS WITH NRI**

"I went into my own business six months after finishing the NRI Radio-TV Servicing Course. It makes my family of six a good living. We repair any TV or Radio. I would not take anything for my training with NRI. It is the finest."

**DON HOUSE, Lubbock, Texas**



"Many thanks to NRI for the Electronics training I received. I hold a first class FCC License and am employed as a studio and master control engineer/technician with KXJB-TV."

**RONALD L. WOOD, Fargo, N.D.**

"I am a Senior Engineering Aide at Litton Systems, in charge of checkout of magnetic recording devices for our computers. Without the help of NRI I would probably still be working in a factory at a lower standard of living."

**DAVID F. CONRAD, Reseda, Calif.**



"NRI training enabled me to land a very good job as Electronic Technician with the Post Office Dept. I also have a very profitable spare-time business fixing Radios and TV."


**NORMAN RALSTON,  
Cincinnati, Ohio**

# ELECTRONICS ILLUSTRATED

JANUARY, 1965

A Fawcett Publication

Vol. 8, No. 1

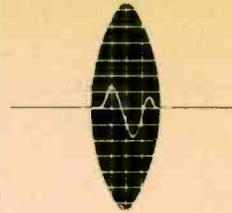

## General Features

Radio's Iron Curtain.....Tom Kneitel, K3FLL/WB2AAI & Stanley Leinwoll	29
Radio Control for Model Trains.....Howard G. McEntee	33
Confessions of an FCC Examiner.....Howard S. Pyle, W7OE	75
Look What's Happened to Home-Study Electronics!.....J. K. Locke	92

## Special Construction Projects

Switchless Intercom.....David Walker	41
VHF Broadspanner.....Charles Green, W3IKH	45
Modular Metronome.....Fred Blechman, K6UGT	64
Automatic Impulse Switch.....Lawrence Glenn	73
Souped-Up Phone Tap.....Gregg Bruce, Jr.	96

## Radio: CB • Amateur • SWL

A New Look for CB?.....Len Buckwalter, KBA4480	38
Amateur Radio Confidential.....Anonymous	50
New Awards for Hams, SWLs, BCBers!.....	53
S-Niner Preselector.....Herb Friedman, W2ZLF	57
The Listener.....C. M. Stanbury II	63
Parasite CW Monitor.....Herb Friedman	66
Slide-Rule CB.....Alex F. Burr, 16W2941	69
CB Channel Slicer.....Bert Mann	79
That Ham Radio Brawl.....Nicholas Rosa, WB6TJ/W1BPQ	83
Behind the Scenes in CB.....	90
Notes From EI's DX Club.....	97
Is NA Really for CB Radio?.....Len Buckwalter	100
Ham Shack.....Robert Hertzberg, W2DJJ	103

## Audio & Hi-Fi

Hi-Fi Today.....John Milder	40
3 Parts=3rd Channel.....Walter G. Salm	72
Kit Report: All-Transistor Preamplifier.....	98

## Theory & Practice

Beginner's Page: The Wheatstone Bridge.....H. B. Morris	101
---	-----

## Regular Departments

Feedback From Our Readers.....	6
Electronics in the News.....	10
Electronic Marketplace.....	16
Broad­sides.....	27
Good Reading.....Tim Cartwright	78
Subscription Blank.....	89
1964 INDEX.....	110
Electronic Swap Shop.....	114
Over & Out.....Rodrigues	118

Audit Bureau of Circulations





MEMBERSHIPS



Magazine Publishers Association, Inc.



COVER — Ektachromes by  
R. J. Capotosto

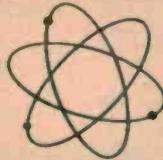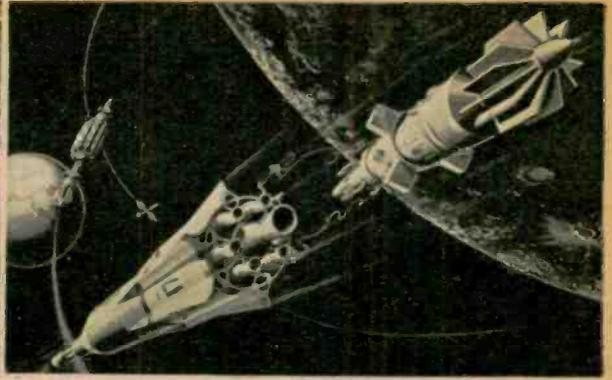

**High pay...exciting, steady work...the great feeling of doing something important. It's all yours with a job in electronics.**

Look around. There's never been anything to match the career opportunities you'll find in electronics. In government, in industry . . . thousands of good, high-paying jobs —just waiting for the right men to fill them. AND YOU CAN HAVE ONE OF THESE JOBS. Regardless of what you're doing today . . . a Cleveland Institute Training Program will give you the necessary electronics skills and knowledge. You'll learn all about Transistors, Communications, Aerospace Electronics. What's more, you'll learn quickly and economically . . . at home, in your spare time. Why wait? There will never be a better time to get started. Send the coupon for complete details.

There's no cost . . . no obligation. Do it now.

**Cleveland Institute  
of Electronics**



1776 E. 17th St., Dept. EI-55, Cleveland, Ohio 44114 Accredited Member

**Mail Coupon TODAY For FREE Catalog**

**Cleveland Institute of Electronics**

1776 E. 17th St., Dept. EI-55  
Cleveland, Ohio 44114

**How to Succeed  
in Electronics**

Please send me your FREE catalog, "How to Succeed in Electronics." I am over 17 years of age and interested in (check one):

- |   |  |
|---|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> First Class FCC License   |
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering  | <input type="checkbox"/> Advanced Engineering      |


Your present occupation \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_  
(please print)

Address \_\_\_\_\_ County \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

January, 1965

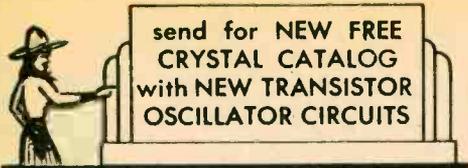

## Citizen Band Class "D" Crystals

### CITIZEN BAND CLASS "D" CRYSTALS

3rd overtone — .005% tolerance — to meet all FCC requirements. Hermetically sealed HC6/U holders. 1/2" pin spacing. .050 pins. (Add 15c per crystal for .093 pins).

**\$2.95**  
EACH

All 23 channels frequencies in stock: 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.155, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225, 27.255.

Matched crystal sets for ALL CB units (Specify equipment make and model numbers) \$5.90 per set

### CRYSTALS IN HC6/U HOLDERS

**SEALED OVERTONE** .486 pin spacing — .050 diameter — .005% tolerance  
15 to 30 MC ..... \$3.85 — 30 to 40 MC ..... \$4.10 — 40 MC to 65 MC ..... \$4.50 — 65 MC to 100 MC ..... \$6.00 ea.

**FUNDAMENTAL FREQ. SEALED** From 1601 KC to 2000 KC \$5.00; from 2001 KC to 2500 KC \$4.00; 2501 KC to 5000 KC \$3.50; 5001 KC to 7000 KC \$3.90; 7001 KC to 10,000 KC \$3.25.

**RADIO CONTROL** Specify frequency. .05 pins spaced 1/2" (Add 15c for .093 pins) \$2.95 ea.



### QUARTZ CRYSTALS FOR EVERY SERVICE

All crystals made from Grade "A" imported quartz—ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:

**FT-243 holders** MC-7 holders  
Pin spacing 1/2" Pin spacing 3/4"  
Pin diameter .093 Pin diameter .125

**CR1A/AR holders** FT-171 holders  
Pin spacing 1/2" Pin spacing 3/4"  
Pin diameter .125 Banana pins

**MADE TO ORDER CRYSTALS** . . . Specify holder wanted  
1001 KC to 1600 KC: .005% tolerance ..... \$4.50 ea.  
1601 KC to 2000 KC: .005% tolerance ..... \$3.55 ea.  
2001 KC to 2500 KC: .005% tolerance ..... \$2.75 ea.  
2501 KC to 9000 KC: .005% tolerance ..... \$2.50 ea.  
9001 KC to 11,000 KC: .005% tolerance ..... \$3.00 ea.

### Amateur, Novice, Technician Band Crystals

.01% Tolerance . . . \$1.50 ea. — 80 meters (3701-3749 KC)  
40 meters (7152-7198 KC), 15 meters (7034-7082 KC), 6 meters (8335-8650 KC) within 1 KC


FT-241 Lattice Crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC) ..... \$1.25 ea.  
Pin spacing 1/2" Pin diameter .093

Matched pairs — 15 cycles \$2.50 per pair  
200 KC Crystals, \$2.00 ea.; 455 KC Crystals, \$1.25 ea.; 500 KC Crystals, \$1.25 ea.; 100 KC Frequency Standard Crystals in HC13/U holders \$4.50 ea.; Socket for FT-243 Crystal 15c ea.; Dual Socket for FT-243 Crystals, 15c ea.; Sockets for MC-7 and FT-171 Crystals 25c ea.; Ceramic Socket for HC6/U Crystals 20c ea.

## 3 PLANTS TO SERVE YOU BETTER ORDER FROM CLOSER PLANT TEXAS CRYSTALS

DEPT. E-15  
1000 Crystal Drive  
FORT MYERS, FLORIDA  
Phone 813 WE 6-2109

Division of

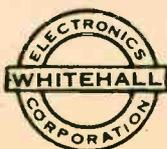

AND  
4117 W. Jefferson Blvd.  
LOS ANGELES, CALIF.  
Phone 213-731-2258

# ELECTRONICS ILLUSTRATED

By the Publishers of MECHANIX ILLUSTRATED

editor **ROBERT G. BEASON**  
managing editor **Robert D. Freed**  
feature editor **Richard A. Flanagan**  
art editor **Lou Rubsamen**  
editorial associate **William C. Fuller**  
production editor **Rosanne Walsh**  
advertising mgr. **John F. Webster**  
eastern adv. mgr. **Don Daily**

### CONTRIBUTING EDITORS

amateur radio **Robert Hertzberg, W2DJJ**  
citizens band **Len Buckwalter, KBA4480**  
swl-dx **C. M. Stanbury II**  
special projects **Herb Friedman, W2ZLF/KBI9457**  
audio **Harry Kolbe**  
audio **John Milder**  
audio **David Muirhead**

### EXECUTIVE STAFF

art director **Al Allard**  
associate art director **Ralph Mattison**  
advertising director **Mortimer Berkowitz, Jr.**  
production director **George H. Carl**

### ADDRESSES


Editorial and Advertising Offices: 67 West 44th St., New York, N.Y. 10036. Subscriptions: Change of address Form 3579 to Subscription Dept., Fawcett Bldg., Greenwich, Conn. 06830.

ELECTRONICS ILLUSTRATED is published bi-monthly by Fawcett Publications, Inc., Fawcett Place, Greenwich, Conn. W. H. Fawcett, Jr., President; Gordon Fawcett, Secretary and Treasurer; Roger Fawcett, General Manager; Roscoe K. Fawcett, Circulation Director; Donald P. Hanson, Assistant General Manager.

Second-class postage paid at Greenwich, Conn., and at additional mailing offices.

Subscription price \$4 for 12 issues in U.S. and possessions and Canada. All other countries \$6 for 12 issues. Foreign subscriptions and sales should be remitted by International Money Order in U.S. funds payable at Greenwich, Conn.

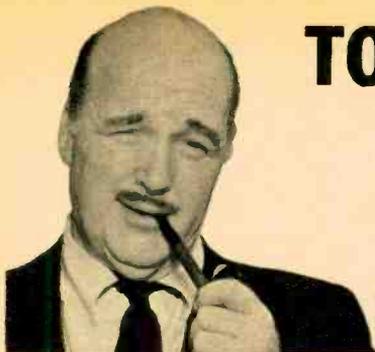Printed in U.S.A. Copyright © 1964 by Fawcett Publications, Inc. Permission hereby granted to quote from this issue of this magazine on radio or television provided a total of not more than 1,000 words is quoted and credit is given to the title of the magazine and issue, as well as the statement, copyright 1964 by Fawcett Publications, Inc.



# TOM McCAHILL SAYS:

## “A lot of people could make themselves valuable FAST”

Everyone talks about high school dropouts and automation changing jobs and what to do after retirement. I know some full grown high school students who can't find summer jobs. I have known family men who thought the end of the world had come when the plant moved out of town.

I hope this doesn't sound like a two-bit sermon, but there are solutions to remedy almost any situation. A lot of people could make themselves valuable fast in a job field that nobody seems to know much about—yet, and that's fixing electrical appliances.

As you know, the day is long past when the average home had only one or two electrical appliances. Most homes today are loaded with electrical gadgets that are used for everything from drying milady's hair to cooking dinner and cooling or heating the house.

These appliances break down and that's where you come in.

Appliances have become a major part in our living habits, and in most areas, good appliance repairmen are as scarce as old maids in Corvettes.

What makes sense about this field is that it offers opportunities to men of any age. You'd be surprised at the extra income you can pick up doing good appliance servicing for your neighbors—or the possibilities of starting your own business with little or no investment. There are also good jobs to be had working for some one else who's already in the business.

How easy is it to break into this field?

A lot easier than you think, if you take a look at

the home-study course offered by the Appliance Division of the National Radio Institute. You've probably seen the NRI ads. They've been one of the biggest and best schools around since 1914.

The course is good. It's easy. It costs less than many people shell out for one month's payment on that Detroit monster parked in the driveway. They train you fast, in an interesting way, to do some real professional appliance servicing on just about every type of appliance from small to large, including most farm and commercial appliances. It even covers small gasoline engines. And they have a separate arrangement to teach you air conditioning and refrigeration.

The point I want to make is this: About the worst thing anyone can do is to sit down and worry about where the extra bucks are coming from. It's not good for your digestive system. It isn't good for those who have to live with you. About the best thing any man can do is help himself.

Do a favor for the guy you see in the mirror every day. Get the details about this course. They send you some books that are worth reading—FREE. Send the coupon below or drop them a note.

No need to tell them I recommended the course. Get the details and see for yourself. Might be a whale of a smart move to do this today.

TOM McCAHILL

APPLIANCE DIV., NATIONAL RADIO INSTITUTE  
WASHINGTON, D. C. 20016

504-015

OK—prove to me this training is as good as McCahill says. Send me the Free Book on Professional Appliance Servicing and Sample Text. No salesman.

NAME .....


ADDRESS .....

CITY..... STATE..... ZIPCODE.....

Accredited Member National Home Study Council

# FEEDBACK


## from our readers

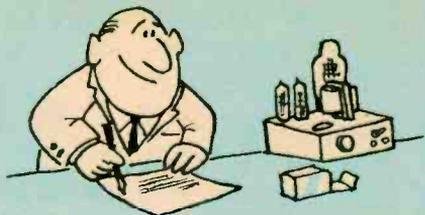

Write to: Letters Editor, Electronics Illustrated, 67 West 44th Street,

New York, N.Y. 10036

### ● OVER THERE

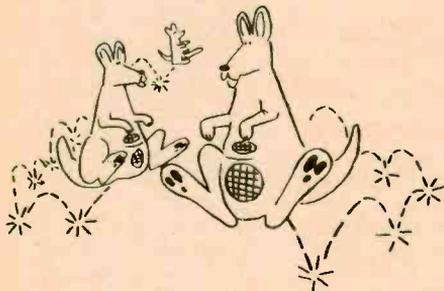

I couldn't agree more that that's a way-out name for a speaker system (THE NOVO TWO KANGAROO, November '64 EI). And as soon as I save up enough for the fare I'm going to retrieve mine from Australia—that's the direction I last saw them heading. Wish you had been more explicit in your instructions and said something about closing the windows. As it happens, my speaker system went way, way out.

Ray Stevenson  
Montreal, Que.

### ● THE REMEMBERER

You have a cartoon in your November issue where a kit builder tells a friend that his new amplifier is heavier than most 20-watters because of six pounds of solder. I don't remember the issue, but I'm sure you published that same cartoon a couple of years ago. What happened? Are you: 1) too chintzy to buy new cartoons, or 2) still laughing at old ideas?

James Bartlett  
Miami, Fla.

3) *Forgetful.*

### ● THE VOICE-MAKER

I have heard from several people that they think it would be possible to build a device that could bring back voices from the past. I don't know if it would be possible, but I

would like to know what you think of it.

Robert Harris  
Carthage, Mo.

*Depends on whose voices.*

### ● CENTENNIAL

Thank you for the treatment you gave to Mahlon Loomis as the inventor of radio (WHO REALLY INVENTED RADIO?, September '64 EI). I am continuing the drive for Loomis recognition in the centennial year of 1966.

Otis B. Young  
Carbondale, Ill.

### ● DXer



Love in its many flowerings has always fascinated me. I, of course, possess a rather extensive library on the subject and I view myself, somewhat unshamedly, as an expert on the aforementioned matter. In speaking of the heart (NEW WAY TO KEEP TABS ON TICKERS, November '64 EI) you discuss several new devices; however, most would appear to require some physical attachment to the person concerned, thus making known their presence. I would hope to assess the cardiacal functions of a person in love remotely.

P. J. Stewart  
Chicago, Ill.

*What?*

[Continued on page 8]

# How To Get 4 New CB Features At The Same Low Price...



## Buy The New Heathkit® MW-34... Only \$89.95!

4 New Advanced Features For Greater Operating Convenience! That's the new Heathkit MW-34 Citizen's Band Transceiver. Boasts 5 crystal-controlled transmit & receive channels with a new front-panel crystal socket to allow quick, easy changing of one transmit crystal *without* the fuss of removing the cabinet! Utilizes variable receiver tuning with another new feature—a spotting switch—for receive function. The spotting switch turns on the transmitter oscillator without going on the air, thus generating a signal for tuning the receiver to exactly the same transmit frequency.

In addition, a TVI filter is incorporated to minimize interference with TV sets. And a new calibrated "S" meter automatically shifts from transmitter to receiver to indicate strength of received signals or relative power output during transmit.

**Ideal For Boat, Home & Car!** The MW-34's compact size, 3-way power supply (6 & 12 v. DC, 117 v. AC) and gimbal mounting bracket allow installation just about anywhere . . . under your car's dash, on top of your boat's instrument panel, or anywhere in your home. And you enjoy the convenience of variable receiver tuning with vernier action and lighted dial to receive all 23 channels . . . superhet receiver with RF stage for sensitive, long-distance reception . . . adjustable squelch to silence receiver during standby . . . automatic noise limiter to reduce electrical ignition interference . . . efficient transmitter circuit for extra-range transmissions. Attractively styled in rust-resistant black & white metal cabinet . . . matches Heathkit marine gear.

**Quick & Easy To Assemble!** With new Heathkit 2-color step-by-step instructions. Requires no special talents, background or tools. Kit includes push-to-talk microphone for ease of operation, AC & DC power cord, and crystals for one channel (specify frequency). Get the most for your money . . . more performance, more savings . . . get the new Heathkit MW-34. Tear out the coupon & order yours now!

Kit MW-34, 16 lbs. . . . . \$89.95



### FREE CATALOG

See these and over 250 other exciting Heathkits available in easy-to-build kit form. Save 50% or more by doing the easy assembly yourself. Send for your Free Catalog today!



**HEATH COMPANY, Dept. 39-1-1**  
Benton Harbor, Michigan 49023

- Enclosed is \$89.95, plus postage. Please send kit MW-34 CB Transceiver.
- Please send Free 1965 Heathkit Catalog.

Name \_\_\_\_\_ (Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Prices & specifications subject to change without notice. GX-136

# GREAT NEW CHRISTMAS GIFT

## Solve Electronics Problems Fast With Special New Slide Rule

Professional, high quality instrument . . . specifically designed for electronic engineers and technicians . . . made to our rigid specs by Pickett & Eckel. Has special scales for solving reactance and resonance frequency problems. Accurately and quickly locates decimal points. Carries widely used formulas and conversion factors not found on any other slide rule. Comes complete with top-grain leather carrying case, illustrated instruction manual, 90 day consultation service — all for just \$14.95. Carries lifetime guarantee against defects in material and workmanship.



### SEND COUPON TODAY

#### TO: CLEVELAND INSTITUTE OF ELECTRONICS

1776 E. 17th St., Dept. EI-102 . Cleveland, Ohio 44114

Please send me your electronics slide rule.

I am enclosing \$14.95. (If not fully satisfied after 10 day trial, CIE will refund payment.)

Please send additional descriptive literature.

Name \_\_\_\_\_  
(Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



BRAND NAMES FOUNDATION, INC.

# FEEDBACK

Continued from page 6

### ● THE DREAMER

I wonder if you could find a schematic for a short-wave set which would include the list of parts I have enclosed. I would like directions for a set which would include these parts. I would like to use these parts because of the technical challenge involved and to get experience.

M. R. Strathkoetler  
Binghamton, N.Y.

*Afraid the challenge and experience would be all ours, M.R.S. And anyway, you don't have the makings of a short-wave receiver in your list.*


### ● DEMODULATED

I read a story once about rocks, hairpins, fillings in teeth and a cigarette lighter that could receive radio broadcasts. Is there anything to this?

Mel Van Pelt  
Salisbury, Mo.


*Could be.*

### ● BEAT ART

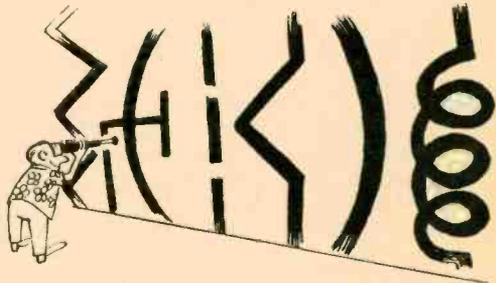

You sure missed the boat in that story about man-size schematics beating ordinary squiggles any day of the week (SUPER-SIZE SCHEMATICS, November '64 EI). Who cares about putting projects together, anyway? Enlarge a squiggle to mural size, slap it on the wall and you've got the best pop art since the Brillo box came round.

Stanley Seigel  
Chicago, Ill.

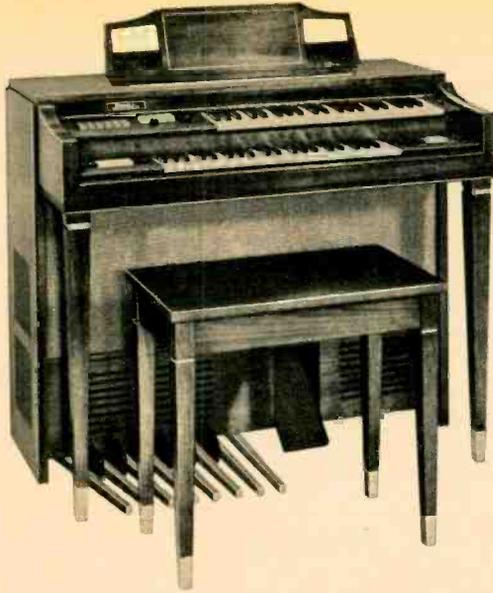

# SAVE \$449...

Kit GD-983  
**\$849<sup>00</sup>**  
Includes  
Bench

## On This NEW Heathkit® Version Of The Thomas "Coronado" All-Transistor Organ!

A Professional Organist's Dream With A Beginner's Simplicity! Has every deluxe organ feature you've ever dreamed of for complete playing versatility . . . 17 beautiful true organ voices, plus chimes, reverb, sustain, vibrato, attack & repeat percussion and treble accent to create an infinite number of thrilling musical effects! And it's all wrapped up in a luxurious piece of walnut furniture that enriches any surroundings. It's all yours to enjoy at a savings of \$449.

**Simple To Build, Simple To Play!** You don't have to be an electronics wizard to build it, nor a professional organist to play it! Famous Heath "Engi-nuity" has reduced assembly to simple-to-perform steps that require *no* special talents, background or tools. And the famous Thomas "Musical Fun Book" starts you easily playing many favorites. Get the full story free—tear out & mail the coupon now!

Kit GD-983, 290 lbs., organ & bench . . . . . \$849.00

### COMPARE THESE FEATURES!

- 17 rich organ voices • Two full-size 44-note keyboards
- Built-in 2-speed Leslie plus 2-unit main speaker systems
- 28 notes of chimes • 13-note heel & toe pedal board, range C thru C • New stereo chorus for exciting "stereo" effects • Color-tone Attack & Repeat Percussion • Sustain • Treble Accent • Reverb • Manual Balance • Pedal Volume • Expression pedal • Headset outlet for private play • 5-year warranty on transistor tone generators, the heart of the organ • 75-watt peak power amplifier • Hand-crafted, full-bodied, walnut-finished cabinet, completely assembled • Matching bench included

### HEAR IT YOURSELF!

Convince yourself by sending for a 7", 33-1/3 demonstration record! Order No. GDA-983-2 for Deluxe GD-983 organ, GDA-232-5 for low-cost GD-232A organ. Each record 50c. Do it now!



### SAVE \$150 ON HEATHKIT/THOMAS "LARGO" ORGAN!



- 10 true organ voices • Variable Repeat Percussion • Two 37-note keyboards • 20-watt peak power amplifier • 13-note heel & toe bass pedals • Walnut cabinet.
- Kit GD-232A, organ, 158 lbs. . . . . \$349.95

**HEATH COMPANY, Dept. 39-1-2**  
Benton Harbor, Michigan 49023

- Please reserve GD-983 Organ for Nov. delivery.
- Enclosed is \_\_\_\_\_ . Please send demo record (s) \_\_\_\_\_
- Please send Free 1965 Heathkit Catalog.


Name \_\_\_\_\_  
(Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
CL-192


Prices & specifications subject to change without notice.

**S**PACE-ACE . . . Unfurling like a sunflower on a summer morn is this unusual 9-foot parabolic antenna. Goodyear designed the oddster for the California Institute of Technology's Jet Propulsion Lab, which will use it for communications between spacecraft and ground stations. Labeled a swirlabola by design engineers, the antenna consists mainly of curved ribs that fold around a circular hub. Thread-thin Invar metal woven in a raschel pattern provides the reflective surface.

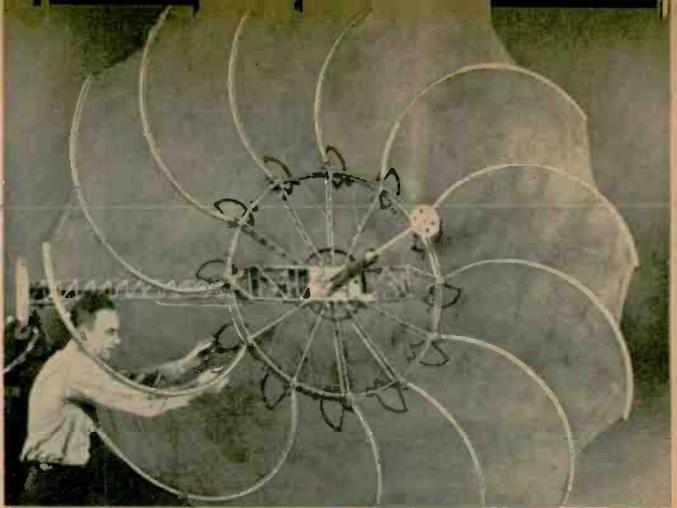


...electronics in the news

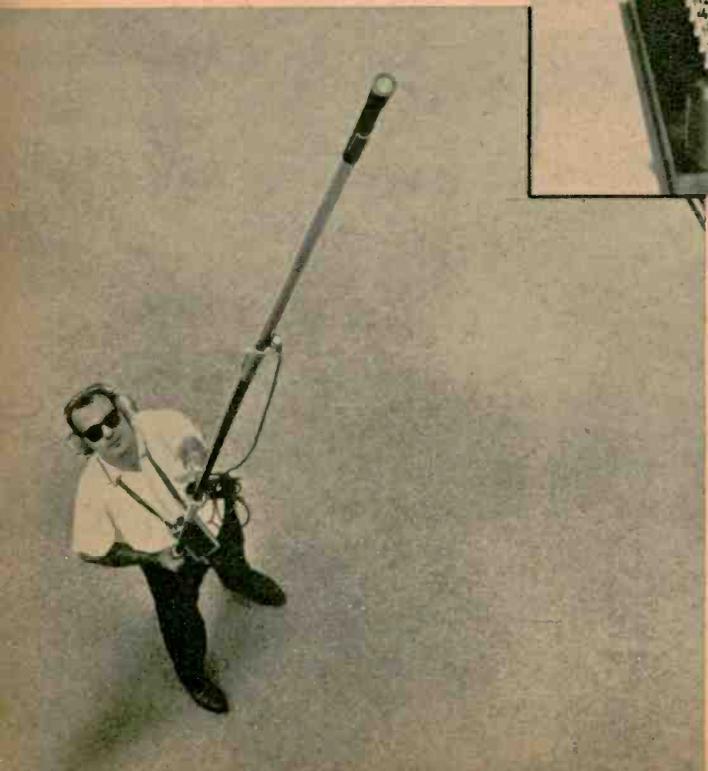**Mock Rock . . .** Diamonds used to be a girl's best friend—until man got into the act, that is. Now they're almost everyone's friend, at least where phonographs are concerned. The man-made diamond needles in our photo are the outcome of four years of research. And General Electric, the manufacturer, thinks so much of its new diamonds that they come with a full lifetime warranty.




**Ssssss Sniffer . . .** What might pass for an electronic tree pruner is nothing more than Delcon's new ultrasonic leak detector. Designated the Quik-Search Wand, it detects ultrasonic energy in the 35- to 45-kc range and translates this energy into audible sounds. Basic uses are for detecting leaks in telephone cable, industrial manifolds of compressed gasses or pressure and vacuum systems. The battery-powered instrument is completely transistorized and has a range of up to 60 ft.
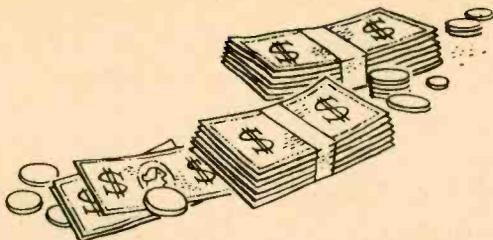
# Regardless of what you pay for other Color TV



it can't perform as well as this one...

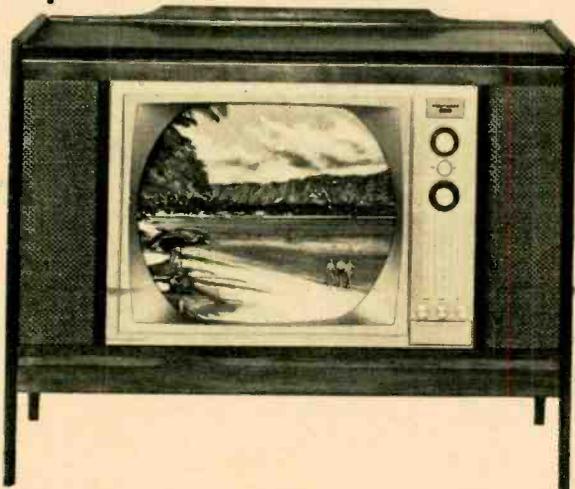

## and yet a Heathkit set costs as little as \$399!

**Exclusive Heath Features For Unequaled Performance!** That's right. No matter how many of your hard-earned dollars you pay for another brand of color TV, *none* can equal the performance of the Heathkit All-Channel, High Fidelity 21" Color TV! Why? *All* color sets require minor periodic adjustments to maintain peak picture performance. The Heathkit GR-53A is the *only* set with a "built-in service center" that provides facilities for perfect picture adjustments. Heath's simple-to-follow instructions and detailed color photos show you exactly what to look for and how to achieve it . . . quickly, easily! You become the expert! Results? Beautiful, true-to-life color pictures day in and day out . . . and *no* costly color TV service calls for simple picture alignment.

But don't take our word for it. See the special articles on the Heathkit GR-53A in the May issue of *Popular Electronics*, June issue of *Radio-TV Experimenter*, February issue of *Popular Mechanics*, April issue of *Science & Mechanics*, and the August issue of *Radio-Electronics*.

Then tear out the coupon and order yours now!

Kit GR-53A, chassis, tubes, mask, VHF & UHF tuners, mounting kit, speaker, 127 lbs. . . . . \$399.00

### THE ONLY COLOR TV YOU CAN INSTALL 3 WAYS!

1. In Heathkit walnut-finished hardboard cabinet (Illustr. opposite), Model GRA-53-6, 52 lbs. . . . \$49.00
2. In Heathkit Deluxe Walnut Cabinet (Illustr. above), Model GRA-53-7, 85 lbs. . . . . \$115.00
3. In a wall, bookshelf, or custom cabinet!



**HEATH COMPANY, Dept. 39-1-3**  
 Benton Harbor, Michigan 49023

Enclosed is \$ \_\_\_\_\_, plus shipping.  
 Please send Model(s) \_\_\_\_\_.

Please send FREE 1965 Heathkit Catalog.

Name \_\_\_\_\_


Address \_\_\_\_\_ (Please Print)

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Prices & specifications subject to change without notice. CL-193R



## 2.7 Db. Gain 6 Meter Mobile Whip

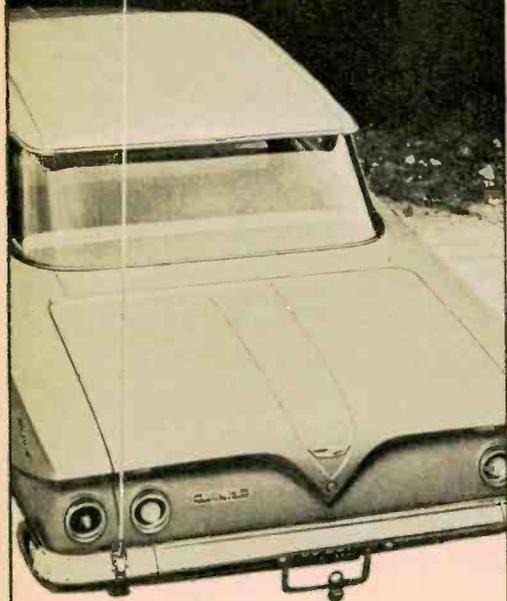

— Looking for streamlined good looks and superior performance for 6 meters?

This sleek, handsome sheath of white fiberglass delivers a solid 2.7 db. average gain over a quarter wave whip in a conventional automobile installation. Our exclusive **WONDERSHAFT** fiberglass construction provides this antenna with a precipitation static barrier over the 108" max. length; exceptional impact and flexural strength; corrosion resistance.

STYLE 238 — End fed,  $\frac{3}{4}$  wave electrical length antenna with physical length shortened through use of built-in coil.

See your local CB dealer or write



**COLUMBIA PRODUCTS CO.**  
Subsidiary of Shakespeare Co.  
Route 3, Columbia, South Carolina

## ...electronics in the news

**Mighty Magnetism . . .** From little acorns oaks shall grow, or so goes the saying. But the process seems to be reversed at RCA's System Center where mounds of paper are being reduced to handfuls of magnetic tape




almost daily. The workhorses of Wall Street paperwork are the RCA 501 and 301 computers. Presently, the Center is capable of handling some 40,000 stock transactions each business day.

**Organ Grinder? . . .** Not exactly, but it's one up on the old music-maker—this one listens at the same time it's making with the sounds. In reality, the gadget is an emergency radio transmitter/receiver for use in lifeboats. Developed by ITT's British Subsidiary, the



transistorized Solas II transmits on three different frequencies. Its receiver tunes continuously over the 8-mc marine band, and its transmitter can broadcast manual or automatic code, a two-tone alarm signal or speech. Power can be supplied by a built-in hand generator or optional 16 $\frac{1}{2}$ -volt battery.

# For The Stereophile With An Eye...

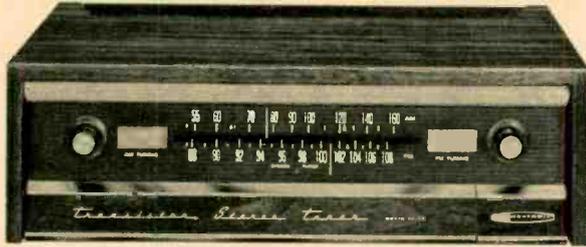

## As Appreciative As His Ear...



# New Heathkit Deluxe Transistor Stereo!

### Luxurious New Walnut Cabinet Styling!

Do you consider appearance as carefully as performance when choosing stereo components? If you do, then you'll delight in this new look of Heathkit Deluxe Transistor Stereo. Sleek, richly warm walnut cabinets. Clean, uncluttered charcoal gray upper front panels. Soft refracted panel lighting. Hinged lower front panels (to neatly conceal all secondary controls and avoid accidental system setting changes). Beautiful enough to capture the spotlight in any room!

### And The Sound?

As modern and beautiful as the new styling. Transistor sound with its broad, crisp, clean, unmodified response ... no compromising here! Add cool, instant operation, simplicity of assembly, and Heath's low prices ... you have the best value in transistor stereo today!

### Inside These Beautiful Cabinets ...

In the magnificent Heathkit AJ-43 Stereo Tuner, you'll find advanced solid-state circuitry ... 25 transistors & 9 diodes in all! You'll find wide-band AM, FM, FM Stereo ... automatic switching to stereo ... filtered left & right channel outputs for direct, beat-free stereo recording ... automatic stereo indicator ... separate

AM & FM tuning meters ... automatic frequency control ... automatic gain control ... adjustable FM squelch ... and stereo phase control for maximum separation, minimum distortion.

The matching Heathkit AA-21 Stereo Amplifier features 26 transistor, 10-diode circuitry to produce 70 watts continuous, 100 watts IHF music power at  $\pm 1$  db from 13 to 25,000 cps ... complete freedom from microphonics, effortless transient response, cool, quick operation. In addition, there are complete controls, plus all inputs & outputs to handle any program source and most speaker impedances. With its encapsulated, epoxy-covered circuit modules and five stable circuit boards, assembly is fast, simple and fun ... requires *no* special skills or knowledge!

### Please Your Ear, Your Eye & Your Sense Of Value!

Choose this matched Heathkit Transistor Stereo pair now for better appearance and better performance at lower cost!

Kit AJ-43C, tuner, 19 lbs. .... \$129.95

Kit AA-21C, amplifier, 29 lbs. .... \$149.95



### FREE 1965 HEATHKIT CATALOG

See these and over 250 other exciting Heathkits available in easy-to-build kit form. Save 50% or more by doing the easy assembly yourself! Send for your free catalog today!

HEATH COMPANY, Dept. 39-1-4  
Benton Harbor, Michigan 49023

In Canada: Daystrom, Ltd., Cooksville, Ontario

Enclosed is \$ \_\_\_\_\_, plus shipping.

Please send Kit \_\_\_\_\_

Please send FREE 1965 Heathkit Catalog.

Name \_\_\_\_\_  
(Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Prices & specifications subject to change without notice.

HF-177R

**In any CB application . . .  
you'll outperform 'em all with a  
MESSENGER<sup>®</sup>**



**Your own 2-way radio for  
Business or Personal use!**



**"PERSONAL MESSENGERS"**—Compact, hand-held 100 milliwatt or 1½ watt units! Rugged and reliable—11 transistors, 4 diodes. Twice the sensitivity and 40% more range than similar units with conventional circuitry—more output than similar units with same rated inputs!

Cat. No. 242-101... 100 Milliwatts... \$109.50 Net  
Cat. No. 242-102... 1½ Watts... \$129.50 Net



**"MESSENGER"; "MESSENGER TWO"**  
For mobile, base station. High efficiency makes full use of maximum allowable legal power. Excellent receiver sensitivity and selectivity. Automatic "squelch" control. 5 crystal controlled channels on the "Messenger" and 10 crystal controlled channels plus tunable receiver on the "Messenger Two".

**"MESSENGER"** — \$114.95 Net  
Cat. No. 242-127... 115 VAC/6 VDC  
Cat. No. 242-128... 115 VAC/12 VDC



**"MESSENGER TWO"** — \$169.95 Net  
Cat. No. 242-162... 115 VAC/6 VDC  
Cat. No. 242-163... 115 VAC/12 VDC



**"MESSENGER III"**—Everything you want in a CB transceiver—a husky signal, extreme sensitivity, razor-sharp selectivity—and complete flexibility for base station, mobile, public address, or battery powered portable use! Double conversion receiver—set-and-forget "Volume" and "Squelch" controls—11 channel coverage—"Tone Alert" Selective Calling System available as accessory.

Cat. No. 242-150  
12 Volts DC Messenger III... \$189.95 Net  
Cat. No. 250-823  
117 Volt AC Power Supply... \$ 29.95 Net

The nation's most popular Citizens Radio equipment line!

Rated BEST by Distributor Salesmen in National Survey!

WRITE TODAY for full color brochure, or see your Dealer/Distributor and ask for a demonstration!



**E. F. JOHNSON COMPANY**  
2242 TENTH AVE. S.W. • WASECA, MINNESOTA

**...electronics in the news**

**Narrow Novel?** . . . Judging a book by its cover is pretty much like selecting canned goods without labels. And this is especially true when there's a six-transistor radio lurk-



ing behind the book's covers. By mounting the transistors folded down rather than in their usual vertical position, Toshiba has come up with a novelette sort of radio that measures a mere 11/16-inch deep. A plastic book-jacket case rounds off the book motif.

**Time Checker Upper** . . . Back in the days of sundials, our ancestors were satisfied with knowing little more than the hour. Seconds hardly existed. But in the age of space, quantum physics and such, nothing less than microseconds can satiate our want of ac-



curacy. Fact is, scientists at Hewlett-Packard have developed a couple of atomic clocks that'll vary nary a second in hundreds of years. Our photo shows the clocks being flown to Switzerland where official U.S. time will be compared with that on the Continent. One use for the clocks will be to measure radio propagation time between countries.

TV-RADIO Servicemen or Beginners . . .

# Send for *Coyne's* 7-Volume Job-Training Set on 14-day **FREE TRIAL!**



The First  
Practical  
TV-RADIO-  
ELECTRONICS  
Shop  
Library!

Answers **ALL** Servicing Problems **QUICKLY** . . .  
Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 14 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams, 10,000 facts!

**SEND NO MONEY!** Just mail coupon for 7-Volume TV-Radio Set on 14-Day **FREE TRIAL!** We'll include the **FREE BOOK** below. If you keep the set, pay only \$5 in 14 days and \$4 per month until \$39.95 plus postage is paid. Cash price only \$29.95. Or return set at our expense in 14 days and owe nothing. Either way, the **FREE BOOK** is yours to keep. Offer limited, so act **NOW!**

Like Having An Electronics Expert Right At Your Side!

**VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES!** 300 pages of practical explanations; hundreds of illustrations.

**VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS;** 403 pages; fully illustrated.

**VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS!** 336 pages; hundreds of illustrations, circuit diagrams.

**VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS!** New they work, how to use them. 368 pages; illustrated.

**VOL. 5—EVERYTHING ON TV TROUBLESHOOTING!** Covers all types of sets. 437 pages; illustrations, diagrams.

**VOL. 6—TV CYCLOPEDIA!** Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 588 pages.

**VOL. 7—TRANSISTOR CIRCUIT HANDBOOK!** Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

BOOKS HAVE BRIGHT, VINYL CLOTH WASHABLE COVERS

## FREE BOOK—FREE TRIAL COUPON!

**COYNE SCHOOL PUBLICATIONS**

1455 W. Congress Parkway, Dept. 15-E1, Chicago 7, Ill.

Yes! Send me **COYNE'S** 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 14-Days **FREE TRIAL** per offer. Include "Patterns & Diagrams" book **FREE!**

Name  Age

Address

City  Zone  State

Check here if you are sending \$29.95 in full payment. Same 2 Week Money Back Guarantee applies.

### "LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."  
—Guy Bliss, New York  
"Well set for either the serviceman or the beginner. Every service bench should have one."  
—Melvin Masbruch, Iowa

### FREE DIAGRAM BOOK!


We'll send you this big book, "160 Radio-Television Picture Patterns and Diagrams Explained" **ABSOLUTELY FREE** just for examining Coyne's 7-Volume Shop Library on 14-day **FREE TRIAL!** Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours **FREE** whether you keep the 7-Volume Set or not! Mail coupon **TODAY!**



*Coyne*

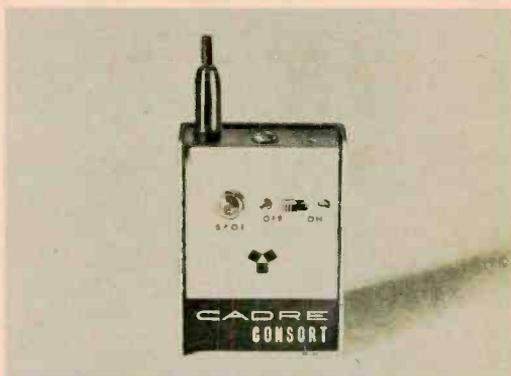**SCHOOL PUBLICATIONS INC.**

1455 W. Congress Parkway, Dept. 15-E1, Chicago 7, Illinois



## Pocketful of power...

## New FM Wireless Microphone

Put the new Cadre Consort in your pocket, or stand it on a table. Set up an FM radio. Zero in the Consort on any open channel in the 88 to 108 mc band with a special pushbutton tone signal—and talk. You've got the finest, most portable PA system available—a wireless short range FM transmitter effective up to 200 feet from the FM radio. Walk free from wires and cables. Stand and speak comfortably with your hands free. The Cadre Consort has many features—built-in dynamic microphone; built-in antenna; 4 silicon transistors for excellent stability; a jack for external microphone. FCC type approval No. WM-104. Operates up to 300 hours on a mercury battery. Less battery only \$44.95.



See the Consort at dealers. For free brochure, write:

**CADRE INDUSTRIES CORP. COMMERCIAL PRODUCTS DIVISION ENDICOTT, N.Y.**  
Canada: Tri-Tel Associates Ltd., 81 Sheppard Ave. W., Willowdale, Ont. 416-222-2529  
Export: Morhan Exporting Corp., 458 Broadway, New York 13, N.Y. 212-925-1257

Assemble the finest instrument your money can buy

# NEW ALL-TRANSISTOR Schober® ELECTRONIC ORGAN



meets AGO specifications

New Recital Model compares musically to instruments costing 4 times the price!



**PIPE ORGAN VOICING**—separate, distinct—32 in Recital Model. LIBRARY OF STOPST™ Kit feature adds extra plug-in voices



ALL TRANSISTOR Models give instant response, easier assembly, full 5 year guarantee



**PIPE ORGAN TONE**—all four families of pipe tone in all models



**REVERBATAPE® Unit**—adds "auditorium" depth and power

plus FULL THEATRE AND CHURCH VOICING, PERCUSSION, many other quality features!

How is it possible to acquire the skill needed to build a splendid organ—without any previous knowledge of electronics or music?

While the complete organ is a complex instrument, Schober Organ kits are specially designed for do-it-yourselfers. Printed circuitry eliminates a lot of the work and makes errors almost impossible. Many parts come preassembled. You simply follow detailed illustrated instructions for easy assembly, then place in assembled and pre-finished cabinet.

You save costly factory assembly, retail store mark-up—put every penny into fine musical parts. You enjoy the finest instrument your money can buy.

Schober Organ kits cost as little as \$550 in kit form, and you may spread this cost by ordering in sections.

THE *Schober Organ* CORPORATION  
NEW YORK, N. Y. 10023

SEND FOR FREE CATALOG WITH FREE "SAMPLER" RECORD

The Schober Organ Corp., Dept. EI-7  
43 West 61st Street, New York, N. Y. 10023

Please send me without cost or obligation FREE SCHOBER ORGAN Booklet describing models. FREE 7-inch "sampler" record included.

Enclosed find \$2 for high-quality LP 10" SCHOBER RECORD DEMONSTRATING all three models with different music (\$2 refunded with purchase of first kit).

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP NO. \_\_\_\_\_



**S**TEREO TESTER . . . Whether you need monophonic or stereo FM test signals, Heath's new stereo-FM generator kit should



fill the bill. The IG-112 generates audio, composite stereo and simulated on-the-air signals. Kit, \$99. Heath Co., Benton Harbor, Mich. 49022

**Lightweight** . . . Snap in a cartridge, flip a switch and you're set for 60 minutes of sound. Powered by five C-type batteries, the Norelco Cartridge-Tape Carry-Corder 150



goes anywhere. And it comes complete with case, mike, cartridges and patch cord. About \$125. North American Philips Co., 100 E. 42nd St., New York, N.Y. 10017

# Choose Your Tailor-Made Course in N.T.S. "PROJECT METHOD" ELECTRONICS!

Now! N.T.S. — one of America's oldest leading home-study and resident technical schools — offers you **GREATER CAREER OPPORTUNITIES IN ELECTRONICS**. N.T.S. "Project Method" home training lessons are shop-tested in the Resident School in Los Angeles. The Schools' practical methods, plus more than 60 years of experience, have helped thousands of students all over the world to successful careers. Choose your field and prepare now for a secure future with one of 8 N.T.S. Electronics Courses designed to fit your own particular needs.



**SEE OTHER SIDE**

## 1 **ELECTRONICS-TV-RADIO-SERVICING & COMMUNICATIONS**

A basic course thoroughly covering fundamentals of electronics, radio, TV servicing and communications.

## 2 **MASTER COURSE IN ELECTRONICS-TV-RADIO, PLUS ADVANCED TV & INDUSTRIAL ELECTRONICS**

This course covers everything included in Course No. 1 plus Automation and every phase of the Electronics industry.

## 3 **FCC LICENSE**

Preparation for this government license essential for interesting jobs in radar, radio, television, communications, guided missiles, many others. Upon completion of this course, if you do not pass the FCC exam for a 1st Class Commercial Radiotelephone License your tuition will be refunded.

## 4 **RADIO SERVICING (AM-FM-Transistors)**

Train for radio sales and service with dealer or distributor.

## 5 **TELEVISION SERVICING (Including Color)**

Covers installation, adjustment, repair and servicing of black and white and color television . . . prepares you for your own sales and service business.

## 6 **STEREO, HI-FI AND SOUND SYSTEMS**

A growing field. Prepares you to build, install and service modern sound equipment for home or industry.

## 7 **BASIC ELECTRONICS**

Gives you the fundamentals you must know to build on for a future Electronics career. Also offers an excellent background for Salesmen, Purchasing Agents, and others in Electronics.

## 8 **ELECTRONICS MATH**

Simple easy-to-follow instructions in the specialized math you need in many electronics jobs.

### HIGH SCHOOL AT HOME

Learn easily. New modern method. National offers accredited high school programs for men and women. Take only subjects you need. Study at your own pace. Latest approved textbooks — yours to keep — everything included at one low tuition. Check High School box in coupon for information.

### CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training in our famous Resident School at Los Angeles in Sunny Southern California. N.T.S. is the oldest and largest school of its kind. Associate in Science Degree also offered in our Resident Program. Check Resident School box in coupon for full details.



**NATIONAL TECHNICAL SCHOOLS**  
WORLD-WIDE TRAINING SINCE 1905

Send Postcard for Free Book & Sample Lesson.



**CUT OUT & MAIL TODAY. NO POSTAGE NECESSARY.**

Please Rush **FREE** Electronics "Opportunity Book" and sample lesson on course checked below:

- |   |   |
|---|---|
| <input type="checkbox"/> Electronics-TV-Radio Servicing & Communications                            | <input type="checkbox"/> Television Servicing (Including Color) |
| <input type="checkbox"/> Master Course in Electronics-TV-Radio Advanced TV & Industrial Electronics | <input type="checkbox"/> Stereo, Hi-Fi and Sound Systems        |
| <input type="checkbox"/> FCC License  | <input type="checkbox"/> Basic Electronics                      |
| <input type="checkbox"/> Radio Servicing (AM-FM-Transistors)  | <input type="checkbox"/> Electronics Math                       |
- Dept. R4Y-124




Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

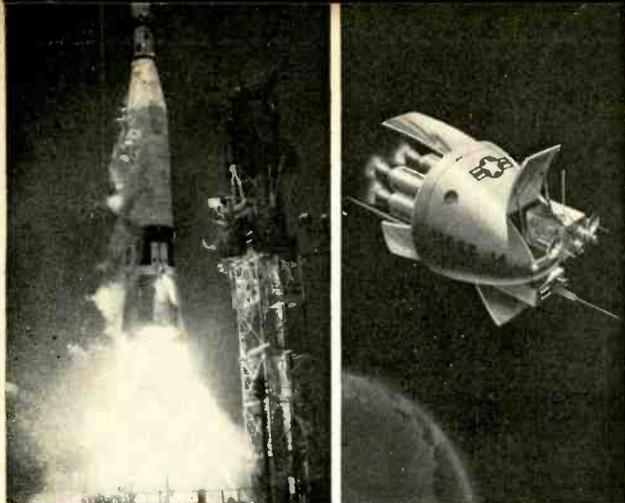- Check here for High School Department Catalog only.  
 Check here if interested **ONLY** in Classroom training at L.A.



You can install and maintain electronic circuitry in missiles and rockets . . . specialize in microwaves, radar, and sonar, or succeed in your own business.

You can succeed in TV-Radio Communications . . . prepare for F.C.C. License, service advanced satellites for industry and defense.

Most courses include Equipment Kits. THERE ARE NO KIT DEPOSITS. Everything included in your low tuition.



**CLIP & MAIL POSTAGE FREE CARD TODAY FOR FREE BOOK AND SAMPLE LESSON**

in Field of Your Choice. You enroll by mail under N.T.S. "No Obligation" Plan. We have No Salesmen; This means lower tuition for you.

# TAKE THE QUICK WAY TO HIGHER PAY, LIFELONG BENEFITS, WITH N.T.S. HOME TRAINING!

N.T.S. "Project Method" Courses can help you get

a new and better job — or move up to higher pay in your present one. You work on practical job projects, learn to use shop manuals and schematics. Your N.T.S. training is individual. You proceed at your own pace.

## BENEFIT NOW AND ALL YOUR LIFE WITH N.T.S. HOME TRAINING

The personal guidance you receive during your training can be very helpful to your progress. Many N.T.S. students are able to earn more money within a few months. You can pick and choose your career. Work in industry or go into business for yourself. Your services will always be in demand wherever you go — and you can pick your spot!

N.T.S. Graduate Advisory Service can help you answer technical questions in establishing your own business and in countless other ways after you've completed your training.

FIRST CLASS

Permit No. 3087  
Los Angeles, Calif.

## BUSINESS REPLY MAIL

No Postage Stamp Necessary If Mailed in the United States

—POSTAGE WILL BE PAID BY—

**NATIONAL TECHNICAL SCHOOLS**

WORLD-WIDE TRAINING SINCE 1905

4000 South Figueroa Street  
Los Angeles, California 90037

See other side of this card for description of all courses.



Accredited Member  
National Home Study Council



**NATIONAL TECHNICAL SCHOOLS**  
WORLD-WIDE TRAINING SINCE 1905  
4000 So. Figueroa  
Los Angeles, California 90037

# MARKETPLACE

**Powerful Pygmy . . .** Though compact in size, the Galaxy III SSB/CW ham transceiver packs a real wallop—300 watts PEP, to be exact. Furthermore, this pint-size power-




house covers 80, 40 and 20 meters with a choice of either upper or lower sideband. Designed for fixed or mobile operation, the Galaxy III makes use of some hybrid circuitry to achieve its compactness (6x10¼ x-11¼ in.) and light weight (14 lbs.). Accessories include AC and DC supplies, a remote VFO, a speaker console and a second console incorporating such extras as a phone patch and a 24-hour clock. \$349.95. Galaxy Electronics, 10 S. 34th St., Council Bluffs, Iowa. 51501.

**Easy Threader . . .** No longer must you engage in finger gymnastics just to thread a reel of tape. With Kodak's Thread-Easy reel.



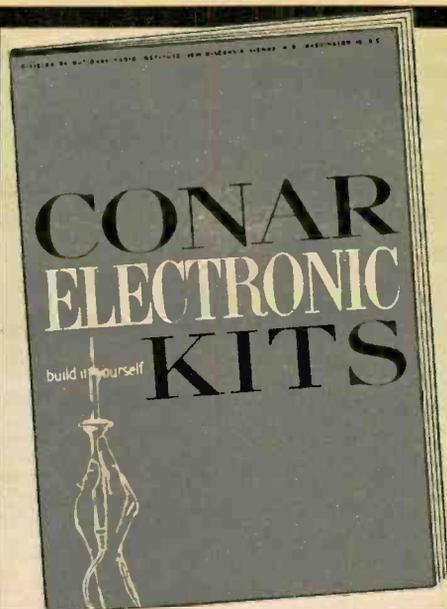all you do is draw the tape through a slotted flange, and bingo! You're in business for the next couple of hours. As a bonus, a built-in splicing jig on the flange gives you on-the-reel splicing. Other features include an index scale and write-on panels. 60 cents. Eastman Kodak Co., 343 State St., Rochester, N.Y. 14654.



*Your copy is waiting*  
**The do-it-yourselfer's  
 newest catalog**

Here's your new catalog of quality electronic kits and assembled equipment . . . your shopping guide for TV set kits, transistor radios, voltmeters, scopes, tube testers, ham gear, PA systems, and a host of other carefully engineered products. Every item in the Conar catalog is backed by a no-loopholes, money-back guarantee. It's not the biggest catalog, but once you shop its pages you'll agree it's among the best. For years of pleasurable performance, for fun and pride in assembly, mail the coupon. Discover why Conar, a division of National Radio Institute, is just about the fastest growing name in the kit and equipment business.

## CONAR

**MAIL NOW!**

CONAR

AESC

3939 Wisconsin Avenue, Washington, D.C. 20016

Please send me your new catalog.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Z-code \_\_\_\_\_

# "Use it



## with any 12 volt CB transceiver"

**New Cadre Selective Call encoder-decoder**  
Put an end to meaningless chatter at the home base and in the mobile units. Contact only the stations you want to talk to. 3-tone, fool-proof selective call system provides up to 24 different tone codes. Code can be changed in field easily with no special relay needed. Easy connection to any of the famous Cadre 5-watt CB transceivers—works with all 12 volt transceivers, regardless of make. Cadre 524, only \$69.95.

**CADRE INDUSTRIES CORP.**  
Commercial Products Div., Endicott, N.Y.



studying antenna system in Tri-State's electronics lab

## B.S. degree in 36 months

Small professionally-oriented college. Four-quarter year permits completion of B. S. degree in three years. Summer attendance optional. **Engineering:** Electrical (electronics or power option), Mechanical, Civil, Chemical, Aeronautical. **Business Administration:** Accounting, General Business, Motor Transport Administration. One-year Drafting-Design Certificate program. Graduate placement outstanding. Founded 1884. Rich heritage. Excellent faculty. Small classes. Well-equipped labs. New library. Residence halls. Pleasant community. Attractive 200-acre campus. **Modest costs.** Enter Mar., June, Sept., Jan. For Catalog and View Book, write Director of Admissions.




## MARKETPLACE

**Living Color . . .** Color-TV servicing calls for a color-coded signal generator. And the Model 980 is designed to provide just about everything you need to put a color-TV set in order. The unit generates ten keyed color



bars, a pattern of 54 dots, a crosshatch pattern, a vertical bar pattern and a horizontal bar pattern. Clip-on leads couple the generator to the TV set. Seco Electronics Inc., 1210 S. Clover Dr., Minneapolis, Minn. 55420

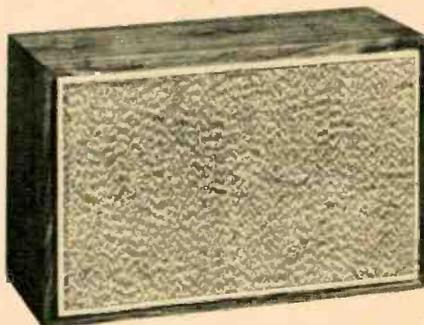**Two for the Money . . .** Though designed for use at the N.Y. World's Fair, the S-5 two-way speaker system sounds good most



anywhere. And while it measures only 10 x 16 x 6 3/4 in. and weighs a mere 12 lbs., the S-5 is no little leaguer. Housed in its attractive cabinet is a low-resonance woofer, a high-frequency tweeter, a crossover network and a level control. Response is within 5db all the way from 60 to 15,000 cps. About \$60. H. H. Scott Inc., 111 Powermill Rd., Maynard, Mass. 01754

# BUILD YOUR OWN RADIO

## CIRCUITS AT HOME

with the Deluxe

### PROGRESSIVE RADIO "EDU-KIT"®

A Practical Home Radio Course

Reg. U. S.  
Pat. Off.



Training Electronics Technicians Since 1946

#### Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ SCHOOL INQUIRIES INVITED
- ★ Sold in 79 Countries

# \$26.95

**YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice Code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the low price you pay. The Signal Tracer alone is worth more than the price of the Kit.

### THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

### PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

### THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build twenty different radios and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc.

In addition you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to FCC Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book on radio. Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

### PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automatic Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

### UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD — RECEIVE FREE BONUS RADIO & TV PARTS JACKPOT WORTH \$15

- Send "Edu-Kit" Postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name \_\_\_\_\_

Address \_\_\_\_\_

### PROGRESSIVE "EDU-KITS" INC.

(ATT: GOODMAN, M. in Ed. PRES.)  
1186 Broadway, Dept. 560AE, Hewlett, N. Y.

LEARN

# ELECTRONICS

TELEVISION

ELECTRICITY

Two Year  
Electronics  
Engineering  
Technology Program



Founded  
1899

## COYNE ELECTRONICS INSTITUTE

on a quarter of a million dollars worth of equipment for top salaries and an Exciting Career. Special finance plans. Part time employment service while in school. Also Free graduate employment service.



Use this coupon to get our FREE BOOK  
"YOUR OPPORTUNITIES IN ELECTRONICS"

COYNE ELECTRONICS INSTITUTE, Dept. of Electronics 15-A  
1501 W. Congress Parkway, Chicago, Illinois 60607

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Phone \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

*Unlike most other schools, we do not employ salesman*

# FREE GIANT NEW 1965 CATALOG

**B-A**  
SINCE 1927  
RADIO TV ELECTRONICS  
1965 Annual Catalog

100'S OF BIG PAGES  
CRAMMED WITH SAVINGS

100'S OF BARGAINS  
NOT IN ANY OTHER  
CATALOG

EVERYTHING  
IN HI-FI  
AND  
STEREO

TOP  
VALUES IN  
POWER  
& HAND  
TOOLS

SAVE UP TO  
50% ON  
CHOICE  
KITS

TUBES, PARTS  
ETC. AT  
LOWEST  
PRICES

### BURSTEIN-APPLEBEE CO.

Dept. 34, 1012 McGeo St., Kansas City 6, Mo.

Rush me FREE 1965 B-A Catalog

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

SEND FOR IT  
TODAY

FREE

# MARKETPLACE

**One Control . . .** Handy as a flashlight (and powered by ten flashlight cells), the S-700 amplifier can be used indoors or out for music, paging or public address. Rated at 25 watts, the S-700 features one-knob control



of on/off and volume. And its two inputs permit using the unit with mike, phono, tuner, tape recorder or what have you. Weight, complete with batteries, is 7 lbs. \$69.95. Perma-Power Co., 5740 N. Tripp Ave., Chicago, Ill. 60646


**Power Pack . . .** Put a couple nickel-cadmium batteries in Gould-National's Action Pack. Plug the little charger into the nearest 117-



VAC outlet, and what've you got? Well, give or take a few hours, and you have batteries good as new. Developed primarily for toys, bicycle lamps, flashlights and the like, the nickel-cadmium batteries can be used anywhere flashlight cells presently are employed. \$5.95. Gould-National, E-1201 First National Bank Bldg., St. Paul, Minn. 55101

*Electronics Illustrated*
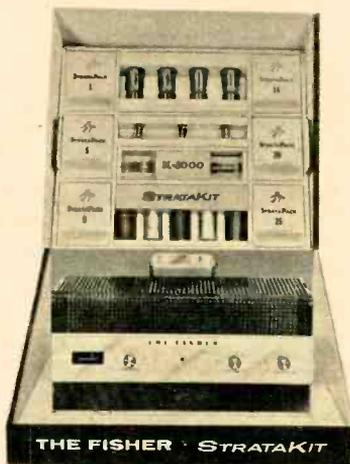
# Don't just talk about the ideal amplifier.



## Build it!

A virtually distortionless basic amplifier of virtually unlimited power is no longer just a conversational gambit among audiophiles. Now they can *build one*—with the Fisher K-1000 StrataKit.

Here is the most advanced and most powerful stereo power amplifier ever produced by Fisher. Its IHF music power rating is 150 watts with *both* channels driven. The RMS power rating, again with both channels driven, is 130 watts (65 watts per channel). However, each channel will deliver 80 watts at 0.5% 1M distortion and even lower 1-kc harmonic distortion, thus indicating the extreme conservativeness of the official rating. A home installation requiring even greater amplifier power is virtually unimaginable.

The circuitry of the K-1000 is completely original in concept and features a host of engineering subtleties that will delight the technically sophisticated. Yet the unique Fisher StrataKit method of kit construction makes it so easy to build that your young son can complete it just as successfully as a skilled electronic technician.

With the laboratory-type calibration meter on the front panel, the K-1000 can be precisely adjusted by the builder to operate under optimum specifications and to maintain these at all times. The exclusive Fisher Strata-Balance—a simple, foolproof invention—makes it possible to balance the push-pull circuitry for minimum distortion by means of an ordinary light bulb!

Size: 15 $\frac{1}{4}$ " wide x 7 $\frac{3}{4}$ " high x 12"

deep. Weight: 70 lbs. Price: \$279.50. (Also available factory-assembled and tested: Model SA-1000; \$329.50.)

### FREE! \$1.00 VALUE!

Mail this coupon for The Kit Builder's Manual, an illustrated guide to high fidelity kit construction, complete with detailed specifications of all Fisher StrataKits.

Fisher Radio, 21-40 44th Drive, Long Island City, N. Y. 11101

Name


Address

City  State

The  
Kit Builder's  
Manual

21111

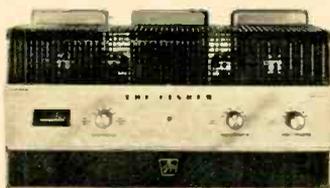OVERSEAS RESIDENTS PLEASE WRITE TO FISHER RADIO INTERNATIONAL, INC., LONG ISLAND CITY, N. Y. 11101. CANADIAN RESIDENTS WRITE TO TRI-TEL ASSOCIATES, LTD., WILLOWDALE, ONT.



## The Fisher K-1000 StrataKit

150-Watt Laboratory Standard Stereo Power Amplifier

# Olson

\* **FREE**

Fill in coupon for a **FREE One Year Subscription to OLSON ELECTRONICS' Fantastic Value Packed Catalog—Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, and other Values. Credit plan available.**

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

**OLSON ELECTRONICS**  
 INCORPORATED

338 S. Forge Street Akron, Ohio 44308

## BIG MONEY

IN THE **4** CORNERS OF THE WORLD!

in TELEVISION, RADIO, ELECTRONICS, RADAR, SONAR

**ONLY CHRISTY OFFERS COMPLETE TRAINING!**

Investigate the Christy Complete Course. Why be satisfied with less? CTS Shop Method. Home Training makes learning easy. You learn by working with actual equipment. You receive Comprehensive training from the start. **CAN EARN AS YOU LEARN.** You become qualified to open your own Electronics Repair business or to gain high pay as a TV, Radio, Electronics, etc., Technician.

**19 TRAINING KITS INCLUDED!** You receive a Multi-Tester, Oscillator, Signal Tracer, Oscilloscope, Signal Generator, Electronic Timer, Regenerative Radio, 24" TV set (optional) and other valuable testing equipment. **FREE BOOK and TWO FREE LESSONS** yours for the asking! No obligation.

**CHRISTY TRADES SCHOOL**  
 Dept. T-2513 3714 W. Lawrence Ave.  
 Chicago, Illinois 60625



**Send for 3 FREE BOOKS**



**CHRISTY TRADES SCHOOL, Dept. T-2513**  
 3714 W. Lawrence Ave., Chicago, Illinois 60625  
 Please send me the 3 **FREE BOOKS** and Special Form for **PAYING LATER** from **EARNINGS MADE WHILE LEARNING.**

NAME ..... AGE.....  
 ADDRESS .....  
 CITY ..... ZONE ..... STATE .....


## MARKETPLACE

**Solid-Staters . . .** Whether you're next door to the studio or way out in the fringes, there's no need to miss out on UHF TV. All it takes is a converter, and JFD now offers two. The CR1-J is a one-transistor unit intended for city dwellers, while the CR2-J contains two



transistors and is aimed at fringe-area listeners. Both converters are completely solid-state and measure only 6 x 7 x 2½ in. CR1-J, \$29.95; CR2-J, \$39.95. JFD Electronics Corp., 15th Ave. @ 62nd St., Brooklyn, N.Y. 11219.

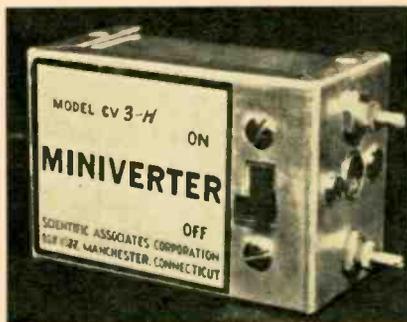**SW Con Box . . .** Any car radio will tune short-wave once you've hooked up the Mini-verter. Installation is child's play, requiring no more than a couple of simple connections. And, once installed, a flick of a switch will let you choose either broadcast-band or



short-wave reception. Since each model is designed to cover a separate 1-mc-wide band, the model you pick will depend on the frequencies you want to tune. The unit measures only 3 x 2½ x 1½ in. \$14.95 and up. Scientific Associates Corp., Dept. 42, P.O. Box 1027, Manchester, Conn. 06040.

# IT'S TOTALLY NEW!

International's Executive 750-HB2 Transceiver with 24 built-in test circuits, is truly the most versatile transceiver manufactured for Citizens Radio communication. ● At the turn of a switch, the 750-HB2 test circuits provide a fast and positive check on the operating performance of receiving and transmitting circuits within the set. ● This "years ahead" test feature checks the filament, plate and input voltages, transmitter forward and reflected power, modulation, etc. Tune-up and servicing is easy. ● The transceiver has a sensitive and selective dual conversion receiver combined with a highly stable and efficient transmitter. The 23-channel crystal controlled transmit and receive frequency selector circuits are housed in the functionally designed remote console. ● Additional features include a new delayed/expanded AVC, new simplified cabling, new built-in S/meter and transmit meter (as standard equipment), and a new speech clipper/filter amplifier. Operates on 115 vac, 6 or 12 vdc. ● Write today for the name of your nearest International dealer. Ask him about his trade-in/trade-up plan.



Remote Console

24-position switch, located on transmitter/receiver unit, is used for checking circuits during tune-up or servicing.

## TEST CIRCUITS WILL CHECK . . .

- Receiver Signal Strength and Transmit Audio Monitor
- Receiver RF Amplifier
- Receiver 1st Mixer
- Receiver 2nd Mixer
- Receiver 1st Oscillator
- Receiver 2nd Oscillator
- Receiver 1st IF Amplifier
- Receiver 2nd Amplifier
- Receiver Detector
- Receiver Squelch
- Receiver Audio
- Microphone Audio
- Power Audio
- Transmitter Buffer
- Transmitter Power Amplifier
- Transmitter Oscillator
- Transmitter Frequency Adder
- Plate Voltage
- AC Filament
- DC Hot +
- DC Hot -
- Transmitter Forward Power
- Transmitter Reflected Power
- Transmitter Modulation



This equipment is intended for personal or business radio communications as authorized by FCC Citizens Radio Service rules and regulations.

# DYNAKIT high fidelity



SCA-35  
stereo amplifier—\$99.95

For the cost-conscious perfectionist

- AMPLIFIERS • TUNERS
- PREAMPLIFIERS

Write for detailed specifications  
and impartial test reports

DYNACO INC., 3912 Powelton Ave., Phila. 4, Pa.  
Please send specifications and test reports to:

Name .....

Address .....

City ..... State .....

EL-115

## 80,000 CANDLEPOWER

as low as \$6.95 ea. ppd.



### UNDERWATER BEAM LIGHTS

Used by skin divers, hunters, fishermen, shipners, watchmen. "Too bright to read by," says one enthusiast. Special die-casting process gives reflector the most distance, greatest brilliance of any flashlight made.

### TREMENDOUS PIERCING BEAM ON LAND — CUTS thru FOG & SMOKE

Made to pierce murky depths and withstand pressures of underwater operation. On land its beam leaps out for twenty miles. 80,000 candlepower illuminates objects clearly a mile away. Pierces smoke-filled areas. Stands alone on special foot. Floats in water. Unbreakable lens. You can jump on this flashlight.

1 at \$10.95..... 2 at \$9.95 ea.  
3 at \$8.95 ea..... 6 at \$6.95 ea.

All Prices Postpaid

## 4000 VOLTS at the End of a 10-oz. 29" Cane

The Police "Shock-Rod" has power to control the most stubborn adversary. It is the most effective protection from nasty dogs. Also effective in riot work. **SAFE TO USER**

FULLY TRANSISTORIZED

Circuit converts electricity into safe but huge voltage. No moving parts. Rugged. Absolutely guaranteed.

Harmless to adversary. The current is tiny (from two small c-size cells) but 2 for \$27 high voltage gives Bats., Inc. kick. Shocky Model same price as regular aluminum walking stick.

**COUNTRY CLUB PRODUCTS**  
349 Manufacturers Exchange Bldg.

KANSAS CITY,  
SP, MO.



From only six regular flashlight batteries in 3-cell length

## WANT A JOB? PART TIME— FULL TIME?

No Boss! No Experience!

No Capital! Your Own Hours!

### WHAT A JOB ! ! ! !

And yet selling subscriptions to ELECTRONICS ILLUSTRATED and other leading publications is just like being in business for yourself.

But no business requires less tal, stock and space. The time you devote and the money you make is up to you. You need no experience to earn steady profits and you keep a cash commission on every sale. You operate in your own community by phone or personal calls. You will be authorized to sell new and renewal subscriptions along with special offers made by the publishers. You'll be amazed at the number of people wanting to take advantage of the convenience, service and savings you can offer them.

To get started immediately—send us your name (on a postal card) requesting free supplies and selling materials.

Write to: Subscription Dept. DE  
ELECTRONICS ILLUSTRATED  
Fawcett Bldg., Greenwich, Conn. 06830

## FOR SPEEDY SERVICE

1102171 647 98 24 0664

T M BROWN

5936 23rd PARKWAY

WASHINGTON, D. C. 20031

## WE'RE LOST WITHOUT THIS LABEL

Well, not really lost — but we can do things faster for you if you send along the ADDRESS LABEL from your magazine any time you write to us about your subscription.

attach  
label  
here

### CHANGE OF ADDRESS

If you're moving, please let us know six weeks before changing your address. Better still, attach the magazine address label to this form, and print your new address here.

name

street

city

state zip

ELECTRONICS ILLUSTRATED Sub. Dept., Greenwich, Conn. 06830

# BROADSIDES

Pamphlets, booklets, flyers, application notes and bulletins available free or at low cost.


Neophyte and seasoned audiophile alike will find much of value in an Information Kit on **hi-fi and stereo**. The package contains an Introduction to Hi-Fi and Stereo; a Photo File of hi-fi component systems; an FM & FM Stereo Station Finder of current stations and a Time Saver Shopping Guide for components of major manufacturers. The entire packet can be yours by sending 25 cents to Sherwood Electronics Laboratories Inc., 43 N. California Ave., Chicago, Ill. 60618.

A new 20-page catalog talks about the latest models of thermal and magnetic circuit breakers. What's more, an easy-to-use chart gives finger-tip information for choosing the model best-suited for your needs. A copy of CB-7-64 is yours for the asking from Wood Electric Corp., 244 Broad St., Lynn, Mass. 01901.

Here we go again—it's time for the new 1965 **electronic catalogs**. And if you're wondering what's what in fresh equipment, copies are free of charge from Allied Radio Corp., 100 N. Western Ave., Chicago, Ill. 60680; Arrow Electronics, 900 Broad Hollow Rd., Farmingdale, N.Y. 11735; Walter Ashe Radio Co., 1125 Pine St., St. Louis, Mo. 63101; Burstein-Applebee Co., 1012-14 McGee St., Kansas City, Mo. 64100; Harvey Radio Co., 103 W. 43rd St., New York, N.Y. 10036; Heath Co., Benton Harbor, Mich. 49022; Lafayette Radio Electronics, 111 Jericho Tpke., Syosset, N.Y. 11791; Newark Electronics Corp., 223 W. Madison St., Chicago, Ill. 60606; Radio Shack Corp., 730 Commonwealth Ave., Boston, Mass. 02117; World Radio Lab., 3415 W. Broadway, Council Bluffs, Iowa 51501.

Refraction, absorption and polarization really can make sense when you see the 28-page booklet entitled **Light Measurement and Control**. For a free copy, write General Electric Co., Nela Park, Cleveland, Ohio 44112.

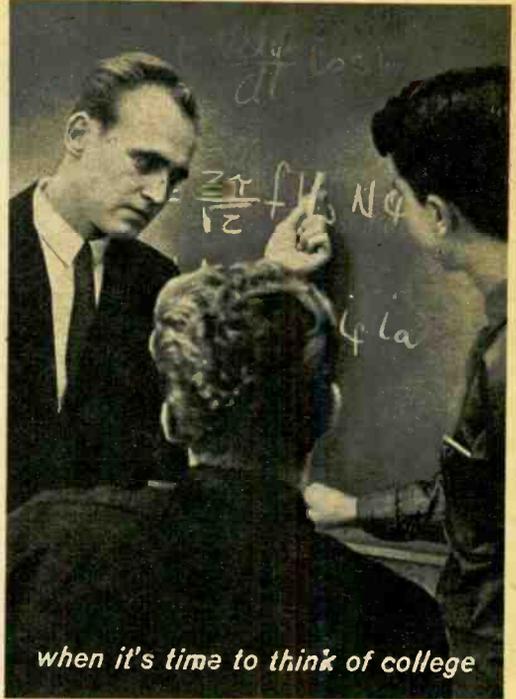A 20-page color booklet shows you all of Scott's **stereo consoles**. A copy can be had by writing H. H. Scott Inc., Dept. P, 111 Powdermill Rd., Maynard, Mass. 01754.



## inquire about Electronics at MSOE

Planning your space age engineering education now, will enhance your career later. Find out about MSOE programs in Electronics, Computers, and Electrical Engineering.

Obtain all the facts about courses leading to 4-year Bachelor of Science and 2-year Associate in Applied Science degrees. Find out about MSOE scholarships, financial aids, job placement opportunities, and other services.

Assure yourself of a bright future in the exciting field of space age engineering and technology. Write for your Free "Career" booklet which will tell you about educational advantages at MSOE.



# MSOE

MILWAUKEE MS-217  
SCHOOL OF ENGINEERING  
Dept. EI-165 1025 N. Milwaukee St.  
Milwaukee, Wisconsin 53201

Tell me about a career through residence study:  
 Electronics field     Mechanical field  
 2-years or  4-years

Name.....Age.....

Address.....

City, State.....


# EICO

# BEST VALUES IN KITS and wired equipment


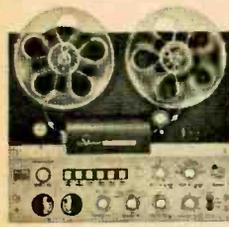
### 3566 SOLID STATE FM MPX AUTOMATIC STEREO TUNER/AMPLIFIER.

Finest all-transistor kit value, equal to \$500-600 class instruments. Kit comes with pre-wired and prealigned RF, IF & MPX circuit boards plus transistor sockets. Outstanding 2 UV IHF sensitivity, automatic FM stereo-mono switching, muting, 40 db FM stereo separation. Total 66 watts IHF music power, only \$229.95 semi-kit (recommended to beginners!); optional walnut cabinet \$9.95—also \$349.95 factory wired including cabinet.



### RP 100 SOLID STATE 4-TRACK STEREO TAPE DECK

Top professional quality—independent record and play—transistor electronics—used by industry in computer and communications systems • 3-motor drive including hysteresis synchronous capstan motor • 3 high-performance heads • Kit only \$299.95. Wired \$450.



**2536 FM MPX STEREO TUNER/AMPLIFIER** Superb FM stereo-MPX tuner, plus a 36-watt stereo amplifier. "In tuning ease, general handling, and sound quality... leaves little to be desired." HIRCH-HOUCK LABS in ELECTRONICS WORLD. Kit only \$154.95. Wired \$209.95.



**ST 70-WATT INTEGRATED STEREO AMPLIFIER.** Best buy of highest ranked stereo amplifiers according to independent testing. Kit \$99.95. Wired \$149.95. **ST40 40-WATT INTEGRATED STEREO AMPLIFIER.** Kit \$79.95. Wired \$129.95.

**HF-90A FM TUNER.** Pre-wired and aligned FM front end. Most popular FM tuner kit ever made—"Without question an extraordinary value." American Record Guide. Kit \$44.95. Wired \$69.95.



**HF-12A 12-WATT MONO AMPLIFIER.** 18 watts IHF power. "Packs a bigger wallop than is apparent from the specifications." POPULAR ELECTRONICS. Kit \$39.95. Wired \$59.95.



**435 DC WIDEBAND 3" SCOPE** Sensational performance in a compact 15-lb. package. Flat-face 3-inch CRT with V and H trace expansion. Flat from DC to 4.5 Mc/s, useful to above 10 Mc/s. Zener diode calibrator. Equal to scopes costing many times more. Kit only \$99.95. Wired \$149.95.

**324 RF Signal Generator** Covers 150 Kc/s to 435 Mc/± 1.5% frequency accuracy. Internal 0-50% 400-cycle modulation. Kit \$28.95. Wired \$39.95.



### 232 PEAK-TO-PEAK VTVM

For color and B&W TV servicing, experimenters and laboratories. 7 non-skip ranges on every function. Measures AC peak-to-peak and RMS as well as DC. Response 30 Cp/s to 3 Mc/s with HVP probe. Kit \$29.95. Wired \$49.95.



### 369 SWEEP/POST INJECTION MARKER GENERATOR

For the "pro" service engineer, experimenters and laboratories. For aligning TV, FM and communications receivers. Sweeps cover 3-220 Mc/s. Markers cover 2-225 Mc/s. Kit \$89.95. Wired \$139.95.

**667 TUBE/TRANSISTOR TESTER** Dynamic conductance tube tester • 14 combinations of 3 plate and 3 screen voltages and 3 ranges of grid voltage • Interelement ohms. Checks all new tube types • Two step transistor test • Kit \$79.95, wired \$129.95. Model 628 Emission tube tester • Checks all new tube types • Kit \$44.95, wired \$59.95. Model CRU—adapts 667 or 628 for testing B&W & Color TV picture tubes. Wired \$9.95.



**EICO** EICO Electronic Instrument Co., Inc. 131-01 39th Avenue, Flushing, N.Y. 11352

Send new 1965 catalog featuring more than 230 EICO Products.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



# RADIO'S IRON CURTAIN

**H**UDDLED AROUND a radio in an eastern European country, a family listens to the crackle of static. Suddenly a voice is heard in the family's native language: "This is Radio Liberty, broadcasting the news to . . ."

The voice continues, though it isn't understood. For just as suddenly as it appeared, it is swamped by a sound that has all the piercing raucousness of a buzz saw. To radio listeners in countries under Communist control, this sound is as familiar as the hammer and sickle. It is the sound of a jamming station, a sound which bespeaks international propaganda and politics, Twentieth-Century style.

In essence, jamming is radio interference so severe that it's intended to do more than block out normal reception. Gratey and raspy, its unsettling sound has all the musicality of a piece of chalk scraping on a

By **TOM KNEITEL**  
KGFL/WB2AA1  
and  
**STANLEY LEINWALL**  
Radio Free Europe

blackboard. The would-be listener's only out is to turn off his radio.

In jamming, the interference is broadcast on the same frequency as the program which is the target for obliteration. Occasionally such jamming is accidental—two radio stations inadvertently broadcasting on or near the same frequency. But most jamming is well-thought-out and purposeful.

The sounds of jamming are numerous and both listeners and engineers have created their own names for each type. Gulls, bagpipes, grunts, single tones, multi-tones, pulses, babbles and buzz-saws are in the picture. But all jamming boils down to one thing—noise, unlistenable and insufferable.

**How It Started.** Though this assortment of noises is very much part of the Twentieth Century, it isn't simply a development of the Iron Curtain. Radio jamming actually goes back some 30 years, when the Austrian government jammed Nazi programs beamed to the Austrian people.

Large-scale jamming began in 1938, when Russia attempted to jam anti-Communist broadcasts from Nazi Germany. Hitler's government retaliated by jamming all Russian broadcasts directed to the German people. In addition, the Italians jammed Russian programs in the Italian language as well as Ethiopian radio appeals for aid during the Abyssinian war.

When World War II erupted, propaganda broadcasts were stepped up immeasurably.

So, too, were efforts to stop them from reaching their intended destinations.


Jamming was used by Germany, Italy and, to a lesser extent, Japan. Each country was feeding its populace a particular brand of propaganda. None wanted Allied broadcasts carrying our version of defeats and victories to be heard. Especially hard-hit were BBC broadcasts, which were jammed by the Nazis through most of the war years.

When the war ended it was thought that the days of jamming were over. This, as we now know, was a premature decision.

**Post-War Jamming.** Since 1945 jamming has had an overwhelmingly Red tinge. For with few exceptions, the Soviet Union and its satellites have been the biggest exporters of radio noise. The Russians and the Spaniards seem to have rekindled the sparks in 1946 by jamming each other's external services. Russia added BBC broadcasts to its jamming schedule in April, 1949. American broadcasts were jammed by the Russians starting about a year later.

From the dozen or so Soviet jamming transmitters in operation in 1946, there were at least 150 on the air four years later. And jamming grew more and more intense as the number of transmitters increased. Worse yet, as the satellite countries set up their own jamming stations, a jamming system or complex was established.

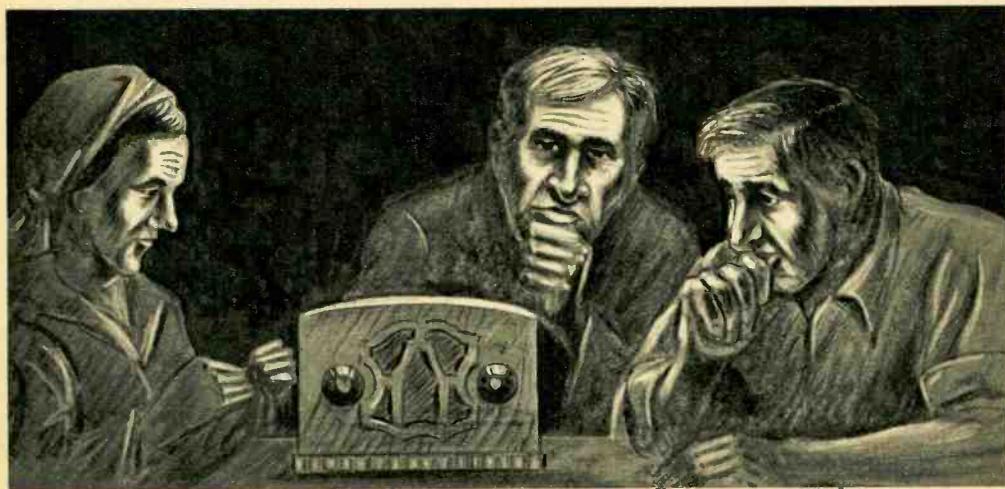The buildup continued. By 1951, all free-world broadcasts beamed to the Soviet Union



Radio listening in the Soviet bloc is fraught with frustration. Though jammers vary in effectiveness, they often totally obliterate programs of news and information transmitted from points outside the Iron Curtain.

and its satellites were subject to intense jamming.

And even this wasn't the end. As the free world increased the number of broadcasts to the Communists, more and more jammers were brought into operation. The number of jamming transmitters increased from something like 1,500 in 1952 to some 2,000 in 1956.

In the spring of 1956, coincident with the visits of Khrushchev and Bulganin to Great Britain, interference with BBC broadcasts to Russia ceased. But jamming of BBC programs in the languages of the satellites continued.

Jamming of broadcasts to the Soviet Union suddenly was resumed during the October 1956 Hungarian Revolution. And early in 1957 came first reports of determined efforts by the Chinese Communists to jam.

**Who Else Jams?** The United States never has used jamming as an instrument of peacetime national policy. All broadcasts from overseas are permitted to enter this country without interference. Similarly, none of the western-alliance countries has used jamming on a permanent basis.


True, there were reports that the British jammed Egyptian and Greek programs during the Suez and Crete crises. In addition, the French were accused of jamming Algerian programs during some phases of the fighting in Algeria. To our knowledge, no free-world jamming presently is taking place.

**How Effective Is Jamming?** The effectiveness of deliberate radio interference varies with geographical location within a country, as well as from country to country. For the most part, reception in large urban population centers (such as Prague and Sofia, where jamming networks are located) is poor. Jamming in such cities is almost 100% effective. In smaller urban centers, as well as in rural and suburban areas, reasonable reception is possible at least 50% of the time. And this condition exists despite all-out efforts to jam.


By locating monitoring stations on the periphery of the Soviet orbit, it's possible to determine reception patterns over wide areas of adjacent Communist territory. This is because the behavior of high-frequency radio signals can be charted in much the same manner as the weather. If it's sunny in New York, for example, it also is likely that the sun will be shining within several hundred miles of the city.

Similarly, conditions affecting a given radio signal will differ only slightly over wide areas. If a signal, say, is getting through the jamming in southern Finland, then it probably is getting through to a good part of northern Russia—provided there are no local (ground-wave) jammers in the vicinity.

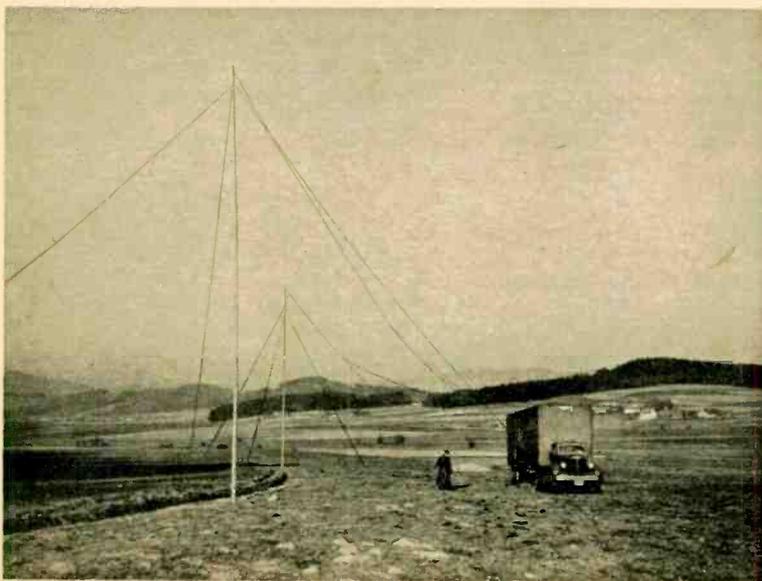In addition to technical monitoring reports, information about reception is obtained from escapees who listened to free-world broadcasts before their flight. Then, too, letters from listeners behind the Cur-



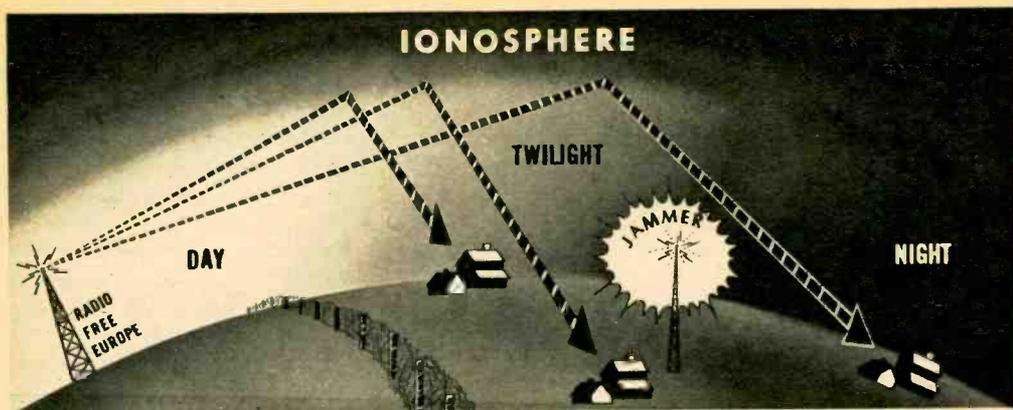Both fixed and mobile jammers are employed throughout the Soviet Union and in many of the satellite countries. Truck in this photo houses mobile jammer, which feeds fixed antennas at left. Guard with rifle can be seen in center of photograph.



Because of sun's effect on ionosphere, jammers located to the east of main transmitting site lose their effectiveness at twilight. This condition is known as twilight immunity and is explained further in text.

tain sometimes come to light. Furthermore, attacks by various Communist regimes on free-world broadcasters often appear in the Soviet and satellite press. Sometimes there even is mention of such broadcasts over the Red radio, proof indeed that free-world transmissions are getting through.

**Anti-Jamming Techniques.** There is no single magic solution to jamming and no black box a would-be listener can attach to a receiver to eliminate the unwanted signal. Even so, several techniques have proven useful against jammers. Most successful of these is brute-force, in which transmitter power and antenna gain are increased until the signal is so strong it simply overrides the jammer.

On the other side of the ledger, the trend toward increased power among all of the world's broadcasters has overshadowed this technique to some extent. Further, though high power and increased antenna gain can deliver signals that are strong enough to override jamming in many areas, there is nothing to prevent the opponent from increasing his jamming power.

Fortunately, economics enters the picture in a helpful way. For each free-world transmitter whose power is increased, many jammers must hike their power to counter the effect. Reason is that propagation from a single jamming location simply isn't capable of delivering comparably stronger signals to all target areas.

A second anti-jamming technique might be called saturation programming. Essential-

ly, it consists of having a great many transmitters simultaneously carry the same program in the same language. This puts an added strain on any jamming system. In many instances, it forces jammers to spread their facilities extremely thin. As a result, effectiveness of the saturation-type programs generally is quite high. R. Free Europe uses up to 12 transmitters simultaneously during its severely jammed Czech programs. Effectiveness of these programs consistently is over 90%.

In an effort to counter the effects of jamming, free-world broadcasters sometimes have scheduled transmissions adjacent to or co-channel with Russian and satellite transmissions. This hasn't mattered in the least to the Soviet bloc. They have shown no hesitancy in putting jammers on frequencies carrying their own broadcasts. If a free-world broadcast is being transmitted on that frequency, then the interference gets top priority, whether or not a Russian broadcast also will be jammed.

Another device tried during the early days of jamming is called jumping. A broadcast would start on one frequency, then jump to another when the jammers opened on the first. When the jammers moved to the second frequency, a third and then a fourth would be tried.

Trouble with this approach was the Red monitoring system. Highly efficient, it usually was able to find the new frequency within minutes. Worse yet, this cat-and-mouse game

[Continued on page 102]

**T**HERE'S SOMETHING new on the market for the dedicated model-train hobbyist, and it's a safe bet he'll go for it with every whistle blowing. Add this factory-wired radio-control transmitter and some receivers to your railroad-in-miniature, and you can have a freight yard or rail network that's as realistic as the B&O's. Reason: the R/C setup enables you to control as many as five trains simultaneously and individually—all on a single track. Trains can be made to rest dead on the track or move at any speed, forward or reverse. What's more, all train and accessory lights stay at full brilliance at all times.

**AC for DC.** A GE development, this all-electronic system is called ASTRAC (for Automatic Simultaneous Train Controls). It's adaptable to any model-train system whose engines have permanent-magnet (DC) motors. And here's an offbeat angle: though the motors must operate on DC, the ASTRAC system puts AC on the track. This eliminates the relatively inefficient rectifier and rheostat in the power supply and it provides more realistic slow-speed operation. In fact, with ASTRAC, trains can be made to creep along with plenty of power and absolute smoothness.


The ASTRAC system requires one or more transmitters plus several receivers, one of

# RADIO CONTROL FOR MODEL TRAINS

By HOWARD G. MCENTEE

which is placed in each engine. Big change you make in your setup to switch over to ASTRAC is to put AC on the track—even though you know PM motors won't run on it. Fortunately, most power packs have AC terminals. If yours doesn't, you simply bypass the rheostat and rectifier and feed the transformer output directly to the track. The receivers will operate on 6 to 30 VAC, but from 16 to 20 VAC will give you about the same speed and power you obtain with conventional DC systems.

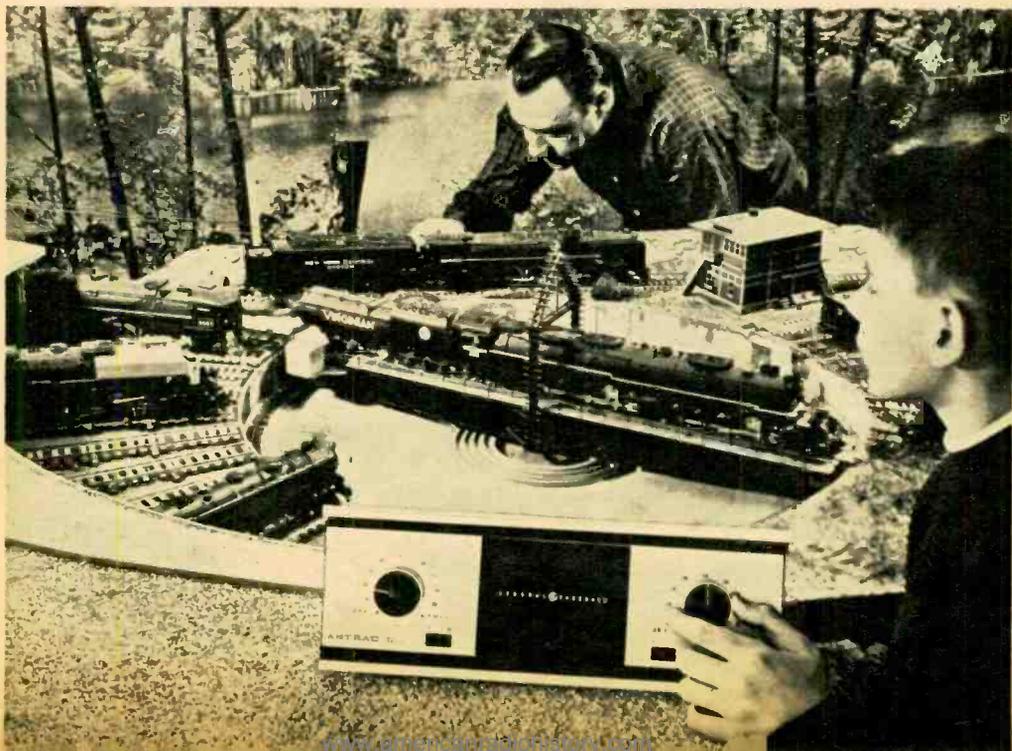**Five Channels.** The basic ASTRAC transmitter is a dual-control unit (Model K2 or K4), which has a panel knob and a switch for regulating the speed and direction of two locomotives. Hook a K2 and a K4 together, and you're all set to handle four trains at




# RADIO CONTROL FOR MODEL TRAINS

once. What about five trains? A third unit, the Model K5 transmitter, is a single-channel device with a similar speed knob and forward/reverse switch—plus a channel selector that allows you to control any of five trains, one at a time. Add the K5 to the K2/K4 combo and you have the full-house, five-train system.

As you may have gathered, five radio frequencies—one for each channel—turn the trick. The transistorized transmitters put out one or more of these frequencies, depending on which model you select. Model K2 operates on 100 and 255 kc, while Model K4 radiates on 140 and 220 kc. The Model K5 puts out 180 kc, but its selector switch will pick any one of the five frequencies.

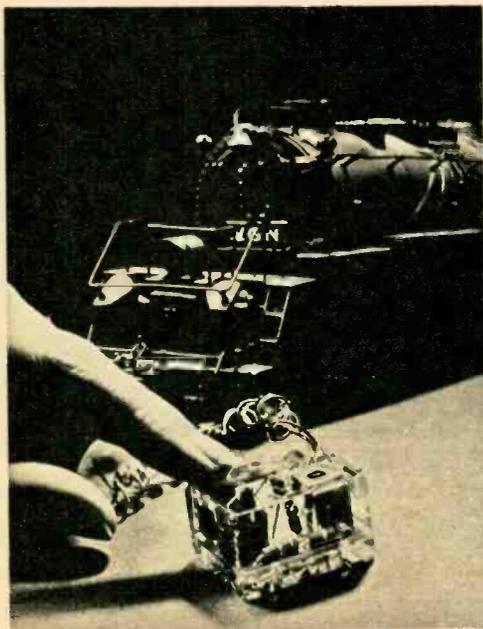No engine ever should be operated on an ASTRAC-equipped track without a receiver,



Receiver for ASTRAC system picks up one of five channels, can be mounted inside locomotive.

of course, since it is the receiver that prevents AC from reaching the engine motor. Five receivers are available, one for each frequency, and they're small enough to fit into most engines. As supplied, they measure  $\frac{7}{8}$  x  $1\frac{1}{2}$  x  $1\text{-}3/16$  inches, but a little whittling here and there can shrink even these miniscule dimensions.

Transmitters in the ASTRAC system are pretty straightforward, though there is a basic requirement that the AC on the track and the AC input to the transmitter be synchronized. However, since both come from the same socket, they have to be. In addition, a line-sync unit takes care of the all-important phasing and ensures that each RF burst from the transmitter starts at the desired point on the track AC cycle.

**Two SCR's.** The ASTRAC receivers, in contrast, are not nearly as simple as their size would suggest. Each is housed in clear silicone rubber, both to protect it from shock and to act as a heat-sink for the two silicon controlled rectifiers (SCR's) inside. An L-C circuit is tuned carefully to the desired frequency and the signal is fed to the gates of both SCR's. However, only one SCR conducts at a time.

Here's why. The first SCR is set up so it conducts every time it receives a positive pulse. Since the SCR rectifies the AC on the tracks, the motor can utilize its output. And, since the SCR gets these pulses only for about the last quarter of each cycle, it sends rather short positive pulses to the engine-drive motor. Due to its own inertia, however, the motor doesn't rotate in a series of jerks but turns smoothly at a fairly slow speed. Longer pulses from the transmitter hold the SCR on longer and the motor goes faster.

The second SCR works much the same, but it's set up to respond to negative pulses. Reversal of the 60-cycle input to the line-sync unit causes this SCR to feed negative pulses to the motor so the train will back up.

Though it's largely foolproof, there are a few things to watch out for with ASTRAC. Since the track voltage is higher than that from an ordinary DC supply, resistors should be placed in series with all lamps or the lamps should be wired in series. Further, if too many lamps are connected across the track the transmitter signals can be attenuated seriously. Remedy here is to insert 1- or 2-mh RF chokes in series with each lamp in the circuit.

# Master Electronics faster with RCA Home Training

NEW, EASY WAY TO BEGIN WITH "AUTOTEXT" PROGRAMMED INSTRUCTION  
HERE'S WHAT YOU GET!

**40** fascinating  
**THEORY LESSONS.**



Here are all the basic principles of radio and electronics in easy-to-understand language, fully illustrated!

**40** exciting  
**EXPERIMENT LESSONS.**



Each contains hundreds of absorbing, experiments and construction techniques to help you learn easier!

**40** complete  
**SERVICE PRACTICES.**



Filled with practical, time-saving, money-saving servicing tips to use throughout your training!

PLUS ALL THIS AT NO EXTRA COST...

**15 KITS!**

to build a Multimeter, AM Receiver and Signal Generator. Kits contain new parts for experiments, integrated so as to demonstrate what you learn in the lessons and to help you develop technical skills. Each kit is fun to put together! Compare what RCA gives you with any other school!



### MULTIMETER

A sensitive precision measuring instrument you build and use on the job. Big 4½" meter with 50 micro-amp meter movement. 20,000 ohms-per-volt sensitivity d-c, 6,667 a-c.



### AM RECEIVER

Have the satisfaction of building your own AM radio with this high quality 6-tube superheterodyne set. Big 5" speaker, fine tone!



### SIGNAL GENERATOR

A "must" for aligning and trouble-shooting receivers. Build it for your own use. 170 KC to 50 MC fundamental frequencies for all radio and TV work.

Begin your training the faster, easier way with new "Autotext" programmed instruction. You learn almost automatically—and go on to advanced training sooner than you ever thought possible! Practical work with the very first lesson. Liberal Tuition Plan. Pay only as you learn. No long term contracts to sign! No monthly installments required!

Complete selection of Home Training Courses to choose from: TV Servicing • Color TV • Transistors • Communications Electronics • FCC License Preparation • Mobile Communications • Automation Electronics • Digital Techniques • Nuclear Instrumentation • Automatic Controls • Industrial Applications • Drafting • Computer Programming.

### CLASSROOM TRAINING ALSO AVAILABLE

RCA Institutes Resident School in New York City offers training that will prepare you to work in rewarding positions in fields such as automation, communications, television, computers, and other industrial and advanced electronic applications. You are eligible even if you haven't completed high school. Check Classroom training and information will be rushed to you.

**Send postcard for free illustrated book today!**  
**Specify home training or classroom training!**

**RCA INSTITUTES, INC.,** Dept. EI-15  
350 West 4th St., New York 14, N. Y.



**THE MOST TRUSTED NAME  
IN ELECTRONICS**

By LEN BUCKWALTER, KBA4480

# A NEW LOOK

**C**ITIZENS BAND radio just mightn't be what it once was. Those rules changes the FCC has been hatching so long just may mean a new look and then some for CB. The band is still in the same place, of course, but that's about all.

To get some perspective on what's happening, you have to boil down 28 pages of legal and technical jargon, which is just what we've done here. Our version is meant to show you what's on the horizon for CB. The complete edition soon will be appearing in the FCC's official Rules and Regulations under the section numbers we indicate.

● **Use of Channels (Sec. 95.41).** Biggest change occurs here. Units of the same station (your base and mobile rigs, for example) still can communicate on any of the 23 channels. But units of different stations (i.e., those operated by other licensees) can communicate only on these seven channels: 9, 10, 11, 12, 13, 14 and 23.

● **Talking Time (Sec. 95.91).** As a general restriction, all transmissions must be kept as short as possible. And as a specific restriction, communications between different stations must not be more than 5 consecutive minutes in length. Furthermore, such stations must remain silent for a period of at least 5 minutes after each transmission and monitor the frequencies involved. One exception: a station observing its silent period can transmit to acknowledge a call from another station, though the message can consist of nothing more than a request to stand by until the silent period is over (silent periods apply even if you change channels).

● **Range (Sec. 95.83).** No station can communicate with any other over a distance of more than 150 miles.

● **10 Codes (Sec. 95.83).** Use them as before. However, you now are required to keep a list of 10 Codes and their meanings on hand in your station.

● **Station Identification (Sec. 95.95).** Call signs must be given in English even if you speak only Latvian. However, you don't have

to say "this is" or "from" when identifying. Units of the same station (which can talk for more than 5 minutes at a time) now can exchange transmissions for as long as 15 minutes before identifying. No abbreviated calls are allowed; the full call-sign of all stations involved must be transmitted and each unit must identify itself separately. You can make up your own special calls for tactical reasons but these can be used only in addition to your regular, assigned call.

● **Equipment Connection (Sec. 95.83).** A transceiver can't be hooked directly into a public-address system but, of course, you still can inform a public-address announcer of information picked up via the receiver. Phone patches aren't specifically ix-nayed by the new rules; however, the Commission points out that many telephone companies prohibit such attachments. Turkey Calls and Q-Birds are out. But selective-call systems are all right so long as the tone signal is kept to less than 15 seconds in duration and actually is used to unlock the squelch of another unit similarly equipped.

● **Equipment (Sec. 95.43).** Power now is defined by more than just the old 5-watt input limitation. The rules add that output can't exceed 4 watts (a daydream, since even the Commission doubts that any rig can produce 4 watts output—80% efficiency—and still be legal). Sideband comes into its own in the new regulations, rated by average power (and not its higher-than-5-watt peak power). Also spelled out is the amount of time you can transmit a test signal. It's pegged at 1 minute during any 5-minute period.

● **Permissible Communications (Sec. 95.83).** Hold on to your db's—there's a new provision which forbids discussion over the air of the technical performance of radio equipment. An exception: you can inform another station when his signal isn't clear or understandable. Another part of this same section makes it illegal to talk to Canadian stations. (Canada, however, does approve certain business communications between U.S.

# FOR CB?



and Canadian operators when a U.S. citizen is in Canada.)

● **Other Changes.** Many organizations—Civil-Defense teams, volunteer fire departments and the like—now can operate units under one call. If you change your address you still can operate while waiting for the new license, provided you notify the local FCC office. A club or association won't be granted a license unless it's incorporated. However, there is a chance of an unincorporated club receiving a license if the Commission recognizes a special need. Lending out call-signs is specifically prohibited. Even CB dealers can't permit a customer to operate under the dealer's license, though the dealer himself can demonstrate equipment over the air.

**The Why of It.** Now that prophets of doom and the alarmists have had their day, the proposed CB rules can be reviewed in the pure light of fact. The rules provoke one inescapable conclusion. If you were operating in accordance with the old rules, the new ones should produce barely a ripple in your activities. The reasons aren't hard to find.

Purpose of the new rules seems twofold: 1) to cut down on hobby-type, hamming activities, and 2) to clarify vague features of the old law.

As any ragchewing kilocycle-killer knows, CB radio as an end in itself never was condoned. Consider the most sweeping change on the books—confining traffic among stations of different call-signs to seven channels. Just about all abuse occurred between different stations (as opposed to units of the same call), so the Commission packed them into a narrower orbit.

A peculiar logic can be applied. Some speculate that the new rule really puts the free-wheeling operator into a side pocket, isolating him in a sort of electronic Pandora's Box. Confined to seven channels, he can swallow himself in meaningless babble. The upright citizen, meanwhile, is free to conduct

orderly communications on the other 16 channels. A cynical interpretation? Yes, but this new arrangement\* could provide a delicate balance which just might keep the service viable.


The rest of the new regulations are reminiscent of a mother-daughter conversation about dating. Daughter already knows, but mother further develops the points. For example, the old rules said an antenna couldn't be more than 20 feet higher than a natural or man-made structure. But the way around that one was obvious, as everyone soon recognized. As one man we know put it, "Anyone can raise a 40-foot tower (a man-made structure), then mount a CB antenna on it."

The rewritten regs nip such tricks by stating that a man-made structure is any construction other than a tower, mast or pole. Similarly, while the old version forbade transmitting music, the new one also tosses in whistling and sound effects. In much the same vein, the false-signal clause now includes a warning about saying MAYDAY. And salty language or blue-tinted gags won't go, either. The new rules not only forbid obscene or profane words but their meanings as well.

In short, the new rules have made for some major changes and picked up some loose ends. And what about the future? Some sage once said that a study of history can help prevent future mistakes. Sounds reasonable, and this same thought applies to CB. Just consider what happened when the rules traveled from mere proposals toward the force of law. Back in November 1962 the Commission first suggested the changes and invited comments. Reports said FCC offices were flooded with mail.

Not so when you look at the real figures. Approximately 2,500 comments were received over a period of more than a year. No flood, this—it was more like a leaky faucet,

[Continued on page 116]

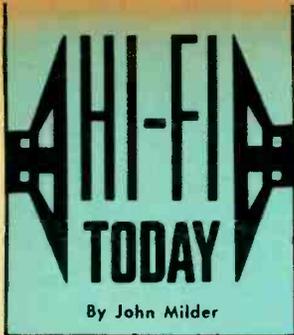

- ✓ *Big-time sound in small-time packages*
- ✓ *What to watch out for with elliptical tips*
- ✓ *Second thoughts on solid-state tuners*

**I**T'S A BIT EARLY to make predictions, but it looks as though packaged hi-fi systems just might be the real show-stealer in 1965. By *packaged* I don't mean those pre-selected component systems some of the mail-order houses put together. Nor am I thinking of those old-style consoles that sound like banshees screaming in the night.

The new-style packages I'm talking about are compact, three-piece sound systems. They're built around a transistor amplifier and two speaker systems of bookshelf-or-smaller size. Such sound packages already are offered by Fisher, KLH, Scott and Shure. And other manufacturers expect to get into the act shortly.

What's behind this new idea in hi-fi design? Well, the transistor, mostly, and here's why. The transistor makes for small-scale (if not subminiature) equipment. This being the case, a system with one control section (containing a record changer and stereo amp/preamp) and two flanking speaker cabinets is right down the transistor's alley.

**Interesting angle here** is what can be done with transistors once you've given up the idea of matching a transistor amplifier to any and all speakers. Since transistor output stages tend to favor only one speaker impedance, having a specific speaker in the setup means you do away with the problem of accommodating speakers of differing impedances.

Then, too, toss out the need for matching more than one kind of pickup at the other end of the hi-fi chain and you can come up with a lot of performance in a neat, reasonably priced little package. Furthermore, design the amplifier for one particular speaker and you can match amplifier and speaker more precisely than in most any standard component stereo system. The speaker, by the way, also becomes a known quantity in the amplifier's distortion-reducing feedback circuitry.

Over the past year, we've seen these ideas reflected in J. B. Lansing's amplifier/speaker

combos (which Lansing calls Energizer/Transducers). But now we're getting the "compleat package"—supplied both as portable phonographs and as ultra-compact non-portable systems. Each offers surprisingly good sound.

Most expensive so far is Shure's M100, which is built around the Dual 1009 automatic turntable and Shure's premium-quality V-15 cartridge. In its portable version, the M100 goes for \$389.50; the non-portable Library system costs \$450. Fisher's portable and stationary packages (the Models 50 and 75) are priced at \$209.50 and \$269.50, respectively. Scott's Stereo Compact (non-portable) is \$299.50, while KLH's new package, the Model Twenty, includes a miniaturized stereo-FM tuner and sells for \$399.50.

**As the prices indicate**, none of the new packages is exactly a bargain-basement item. But all the companies involved claim these new systems can stand their ground against component systems of much higher price. And they also argue that the small speakers sound big enough to satisfy all but the most gilded of golden ears.

Could this mean that components themselves are on the way out? Huh-uh. Matter  
[Continued on page 116]



One example of non-portable package stereo is Shure's M100. All-transistor, it sells for \$450.



# Now! Hands-free conversation with our **SWITCHLESS INTERCOM**

By DAVID WALKER

**H**OW many times have you watched a conversation between two people that never mastered the art? Before long they're both talking at once. And what happens if these same people try to talk to each other over an ordinary intercom? You guessed it—they'll be tied in knots after two minutes of fiddling around with the push-to-talk switches.

The answer is not a course in the fine art of conversation but a switchless intercom like ours. Such an intercom lets each party break into the conversation at any time. It's like the telephone, but with loudspeaker volume. While one person is yacking, the other can start talking and will be heard instantly. You can even interrupt while your friend is interrupting you!

There are no voice-operated relays or other switches to delay the back-and-forth action. Everything is done electronically. But before you set about ordering parts, consider carefully the end use of such an intercom. Though fun to operate, its special design requires plenty of construction and parts.

Unlike push-to-talk intercoms, the switchless intercom requires two complete amplifiers instead of the usual one. Total cost of parts is about \$30 to \$35 if everything is purchased new. But for certain applications, you can't beat it.

Say the boss is dictating a letter to his secretary in another room. She can stop him and ask how to spell *phthisis* without a lot of distracting button pressing.

**Construction.** Since both units are identical, we show the diagrams of only one and the power supply. Most of the parts are mounted on a  $3\frac{1}{2} \times 5\frac{1}{2}$ -inch piece of perforated board. Mount all parts on the board before fastening it in the U-section of an  $8 \times 6 \times 3\frac{1}{2}$  inch Minibox. Flea clips or other small push-in terminals serve as tie points. Transformer T1 and transistor Q4 are installed

on the board as shown in the pictorial.

Grounds are important. Notice that a piece of heavy bare wire runs along two edges of the board. One point on this wire must connect to the solder lug which is attached to a long machine screw near C2. This screw also supports the front edge of the board about  $\frac{3}{4}$  inch above the bottom of the cabinet. A third nut on the top of the board locks it in place. The rear of the board is held to the case with two small L-brackets.



Another ground point is binding post J3. It is not necessary to use a fiber insulating

washer for this post since it must make contact with the case. Binding posts J1 and J2 must be insulated from the case. The solder lug at one side of transistor Q4 is not for grounding. It is for T2's connection to Q4's collector (the case).

**Set-Up and Operation.** After both units and power supply are complete, connect all similarly marked terminals (*gnd, sig, -9V*) with a length of 3-conductor wire (No. 20 plastic-insulated hookup wire). The *aud* terminal that appears in the photo of the power supply has no internal connection to the
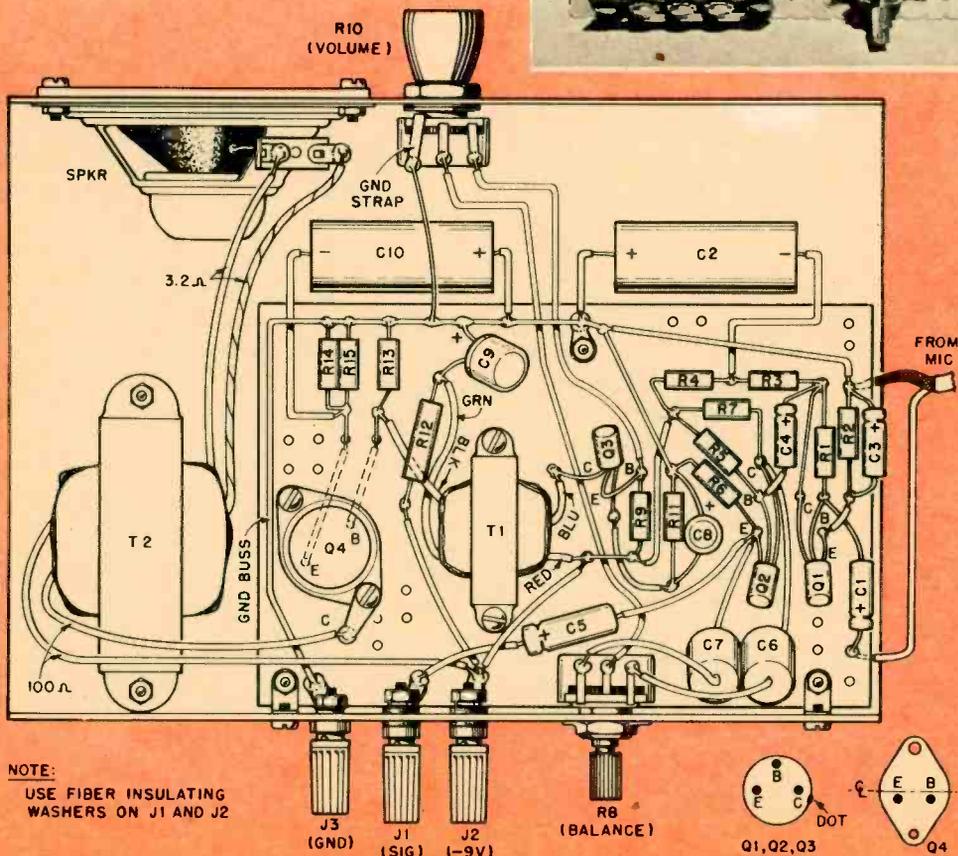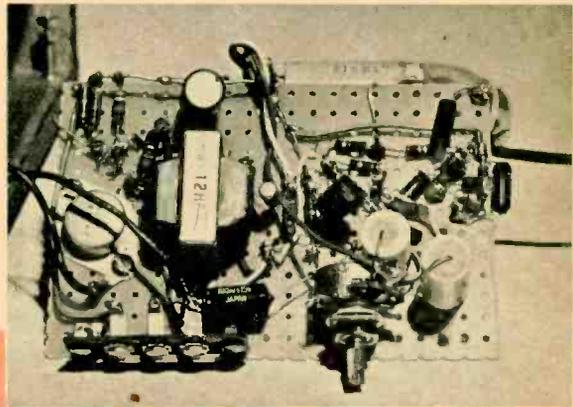
## SWITCHLESS INTERCOM

First model was built in metal cabinet, hence J1, J2, J3, R8, R10 and the speaker are mounted as shown below. Circuit board is held in place with angle brackets at rear and machine screw at front. Later model (photo at right) was built for installation in wood cabinet shown on first and last pages of story. For this construction, mount R8 and screw-type terminal strip with angle brackets.



### PARTS LIST

Capacitors: all electrolytic unless otherwise indicated

C1, C3—10 mf, 15 V  
C2, C10—500 mf, 12 V  
C4—10 mf, 6 V

C5, C9—100 mf, 15 V  
C6, C7—.1 mf, 200 V tubular  
C8—30 mf, 12 V

\*C11—1,000 mf, 25 V  
\*C12—1,000 mf, 15 V

J1-J5—Five-way binding posts

Transistors: all RCA

Q1—2N2613 Q2—2N217  
Q3—2N408 Q4—2N2147

Resistors: 1/2 watt, 10% unless otherwise indicated  
R1—1 megohm


R2, R4—1,000 ohms  
R3—10,000 ohms  
R5—150,000 ohms  
R6, R7—820 ohms  
R8—10,000 ohm linear-taper pot  
R9—47,000 ohms  
R10—5,000 ohm audio-taper pot  
R11—82 ohms  
R12—270 ohms, 1 watt  
R13—39 ohms  
R14, R15—2 ohms, 5%  
\*R16—32 ohms  
\*S1—SPST toggle switch  
\*SR1, SR2—Silicon rectifier: 500 ma, 100 PIV  
SPKR—3x5-inch speaker

T1—Driver transformer: primary, 8,000 ohms; secondary, 3.2 ohms (Allied 62 G 093)  
T2—Output transformer: primary, 100 ohms; secondary, 3.2, 8, 16 ohms (Allied 64 G 149)

\*T3—Power transformer: primary, 117 V; secondary, 26.5 V @ .6 A (Allied 61 G 476)

Misc.—8x6x3 1/2 and \*5x2 1/4 x2 1/4-inch Miniboxes, perforated board, flea clips, crystal microphone

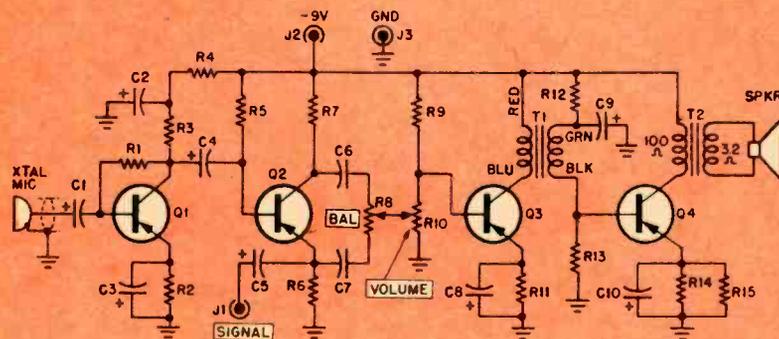\*Note: Order twice the quantity of all parts except those marked with an asterisk (\*)



Signal from mike is amplified by Q1 and fed to Q2. Out of phase signals at Q2's emitter and collector cancel in R8 and very little signal gets to speaker. Hence, no feedback from mike to speaker at same unit. Signal at Q2's emitter is coupled by C5 to J1 and other intercom. Signal from other intercom is fed by C5, C7, R8 and R10 to Q3 where it is further amplified and fed to the speaker.

supply. It is just a tie point for the sig wires of the two intercoms. The location of the power supply may be anywhere along the line.

First thing to do is place the intercoms in separate rooms and close the door. (Feedback will occur if the two stations "hear" each other.) The mike should be located about two feet to the side of each intercom's cabinet. With power turned on, turn the volume control on one unit all the way up. Chances are you'll hear howling feedback. Reduce this by slowly turning balance control R8.

At some point near the middle of R8's rotation, the feedback should stop or become very weak. Now repeat this procedure at the other unit. (Note: this adjustment must be always made with both units connected.) If there is no feedback hold the mike a few inches from the speaker.

It is possible that feedback cannot be killed with the R8 because of mechanical feedback between mike and speaker through the table surface. You can determine this by holding




the mike in your hand. If this stops it, place some soft material under the mike. Feedback may also occur if the mike is placed atop the intercom case or if it is too close to the speaker.

Some experimentation will be required to determine the best speaking level and setting of the volume control. Talking too close to the mike will produce distortion at the other unit. With our model, speaking at a distance of about one foot from the mike produced good intelligibility at the other unit.


**How it Works.** It's easy enough to use two wires with a telephone communications system, since there's no problem in having signals travel two ways simultaneously on one pair of wires. And there's no feedback at either end because the microphone and earphone are separated by the handset and because the gain is low.

With most conventional intercoms, the speaker is not used as a microphone and a speaker at the same time because there'd be feedback. Okay, you say, why not build an

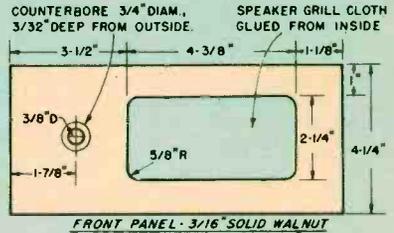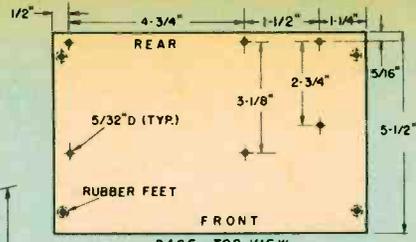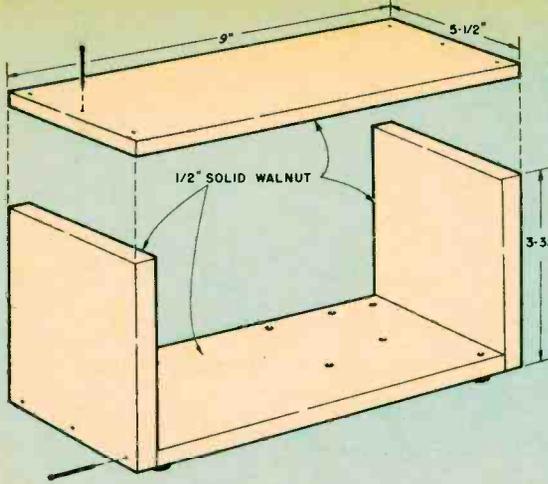NOTE: ASSEMBLE WITH GLUE & FINISHING NAILS



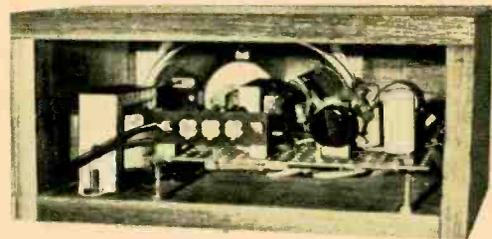If you install intercom in wood cabinet, mount speaker first, then output transformer. Attach volume control to front panel with long leads then mount circuit board atop machine screws. Connect one lead of output transformer's primary to collector of Q4, and other lead to the terminal strip.



## SWITCHLESS INTERCOM


intercom with a speaker and mike at each end? Fine, except that you'd get feedback between them because of the high gain required to produce room volume.

The switchless intercom solves this problem. Here's how. Take a look at the schematic. When you talk into the mike, you want your signal to go to the other unit but not to your speaker. Watch what happens. The signal from your mike is amplified by Q1 and fed to Q2. This signal now appears at both Q2's emitter and collector. These two signals, which are 180 degrees out of phase, are fed to balance potentiometer R8, and at some point on R8 they cancel each other out. That point is where R8 must be set for minimum feedback, as we explained earlier. Since there's hardly any of the signal from your mike at this point none of it gets through to Q3, Q4 and to your speaker. Hence, there

won't be any feedback at your unit.

Remember that we said your signal also appears at Q2's emitter. At this point the signal is not cancelled out. It is coupled through C5 to J1 and fed to the other intercom. Let's see what happens at the other intercom which is identical to yours.

The incoming signal at J1 goes through C5 to the emitter of Q2. Since this signal never goes through Q2 from its base, it is not cancelled out. Therefore it continues through C7 to R8 and goes on to Q3, Q4 and the speaker. In a nutshell, then, your signal to your own speaker is cancelled out at R8. But it is fed to the other intercom through C5. The signal passes through C7 to R8 and goes on to Q3, Q4 and to the speaker.

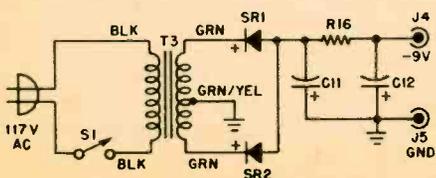

Power supply right, and schematic, left. Lug marked "aud" on chassis is not shown in schematic as it is merely a tie point. Be sure you hook up SR1 and SR2 correctly.



LISTEN TO



Pilots



Firemen




Police



Ambulances



Service Trucks

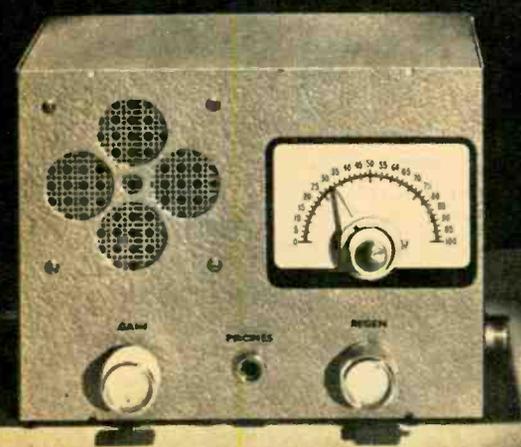

# VHF Broadspanner

*Two tubes and a really hot reflex hookup give you exciting listening all the way from 26 up to 173 mc!*

By CHARLES GREEN, W3IKH


**T**HERE'S real excitement and adventure in the VHF radio spectrum, which begins at 30 mc and runs up to 300 mc. Sure, it may be lots of fun to tune in the *world* on a short-wave receiver. But on VHF there's so much activity in your own back yard and in the sky above that you'll be glued to your seat for days listening to it all.

Take a quick look at some of the things you'll be able to hear with EI's VHF Broadspanner, a really hot, two-tube VHF receiver. Starting at about 26 mc, you find the Citizens Band and then the 10-meter amateurs. Between 30 and 50 mc you hear police cars, fire departments, telephone paging, intra-airport communications and other conversations between public-safety vehicles.


From 50-54 mc, you can eavesdrop on the 6-meter hams. The Broadspanner also tunes the 88-108 mc FM broadcast band. Plug in another coil and listen to commercial and private aircraft and airport control towers. Put in the highest-frequency coil and you are able to tune from 140 to 173 mc for more public-safety listening and the 2-meter ham band at 144-148 mc. For more detailed information about what you can hear and where, take a look at the chart at the end of this article.

VHF is a big world. And the easiest and most economical way to listen is with the VHF Broadspanner.

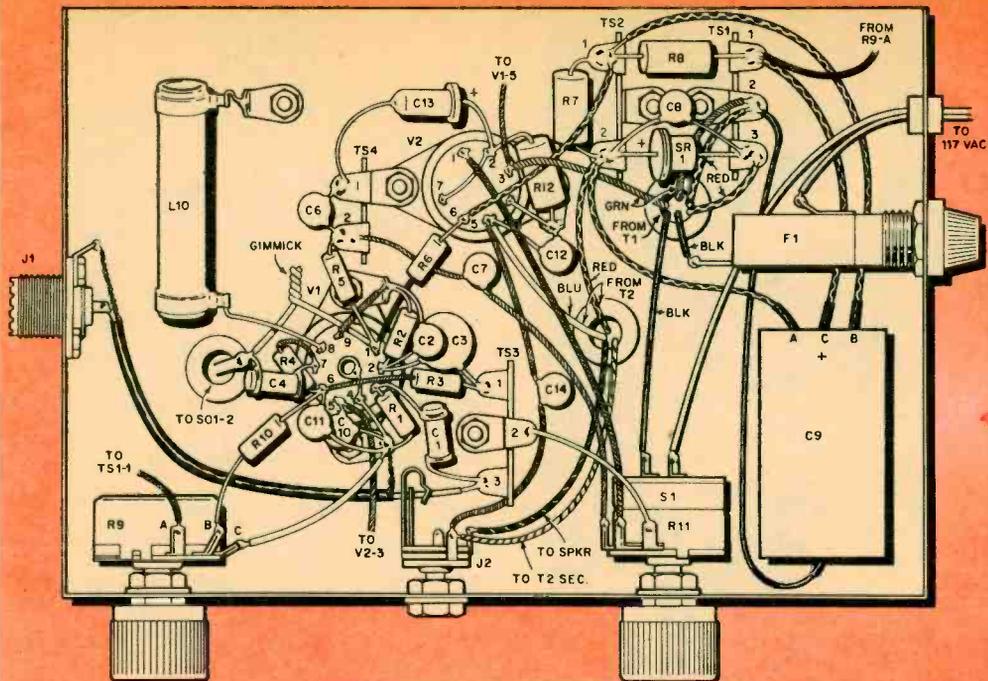The Broadspanner uses only two tubes in a reflex circuit that has a grounded-grid RF stage followed by a superregenerative detector. And there's plenty of audio power to drive its 3½-inch speaker to room volume.



Author's receiver is built in an 8x6x4½-inch LMB utility box (see Parts List). If you have difficulty getting this size, use a 8x6x3½ or a 12x7x4-inch box. Smaller size will mean crowding, so be careful. But whether you use larger or smaller box, keep all parts in same relative location. Chassis in photo at right is 4¾x8 inches. Mount it with angle brackets or cut it 9 inches long and then bend edges ½ inch.

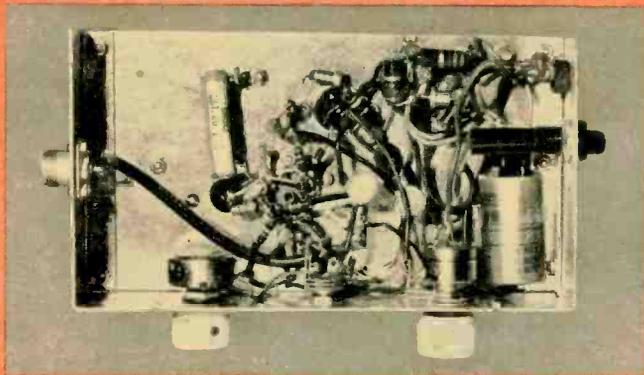

## VHF Broadspanner

The receiver and its power supply fit in a compact metal cabinet. Using all new parts, the Broadspanner can be built for about \$25. The nine coils that cover 26 to 50 mc and 88 to 173 mc aren't at all difficult to wind.


The coils are plugged in through an opening in the rear of the receiver so they can be changed easily. Assembly and wiring are straight-forward and you shouldn't have much trouble with construction.

### Construction

The author's receiver is built in the main

section of an LMB 8x6x4½-inch aluminum utility box. The name of a distributor where you can buy this box is listed in the Parts List. But if you prefer, use a 12x7x4-inch cabinet, which should be easier to get. Just because this box is wider, do not spread out the parts. Because of the high frequencies at which the receiver operates, parts placement and wiring are critical. Therefore, follow exactly the layout shown in the pictorial.

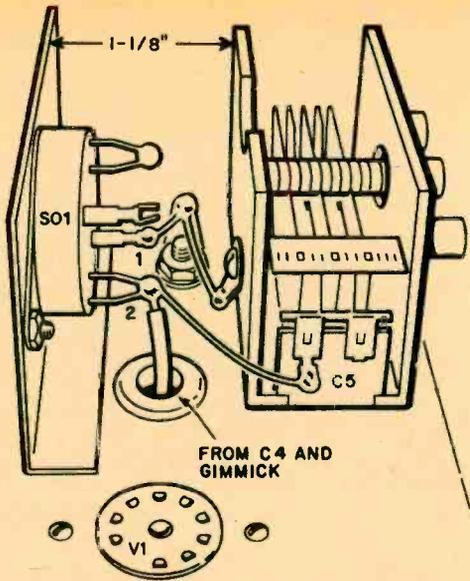Before installing the chassis, which can be cut from a piece of aluminum, drill and punch all holes for the components and tube sockets. You can mount the chassis either with four angle brackets at the corners or by bending the edges on the ends to form ½-inch lips. Either way, install the chassis 2



Coil socket mounting details. The lead that goes from pin No. 2 on SO1 to the junction of C4 and the gimmeck capacitor must be No. 12 buss wire.

inches above the bottom of the box to allow plenty of room for input jack J1, the fuse holder and other parts.

The bracket for the coil socket can be made from a piece of aluminum left over from the stock from which you cut the chassis. The author's bracket is 2 inches wide and 1 3/4 inches high. Since the mounting lip is 1/2-inch wide, start off with a 2x2-inch piece of aluminum. Before installing the bracket, use a 1 1/8-inch punch to put a hole in it for coil socket SO1.

Because tuning capacitor C5 has concen-


### PARTS LIST

#### Capacitors:

- C1, C4—47 mmf, 600 V tubular ceramic
- C2, C6, C8, C10, C11—.001 mf, 600 V ceramic disc
- C3, C7, C14—.005 mf, 600 V ceramic disc
- C5—13 mmf variable capacitor (Lafayette HP-72. Concentric knobs Nos. 18-77 and 18-79; 36¢ and 25¢ respectively)
- C9A, B, C—20/20/20 mf, 150 V electrolytic
- C12—.01 mf, 600 V ceramic disc
- C13—6 mf, 15 V electrolytic
- F1—1/2 A fuse and holder
- Gimmick—4 turns plastic hookup wire (see text)
- J1—SO-239 chassis-type coax connector (Amphenol 83-1R)
- J2—Closed-circuit phone jack
- L1-L9—Coils (see chart and text)
- L10—21 uhy RF choke (Ohmite Z-28 or equiv.)
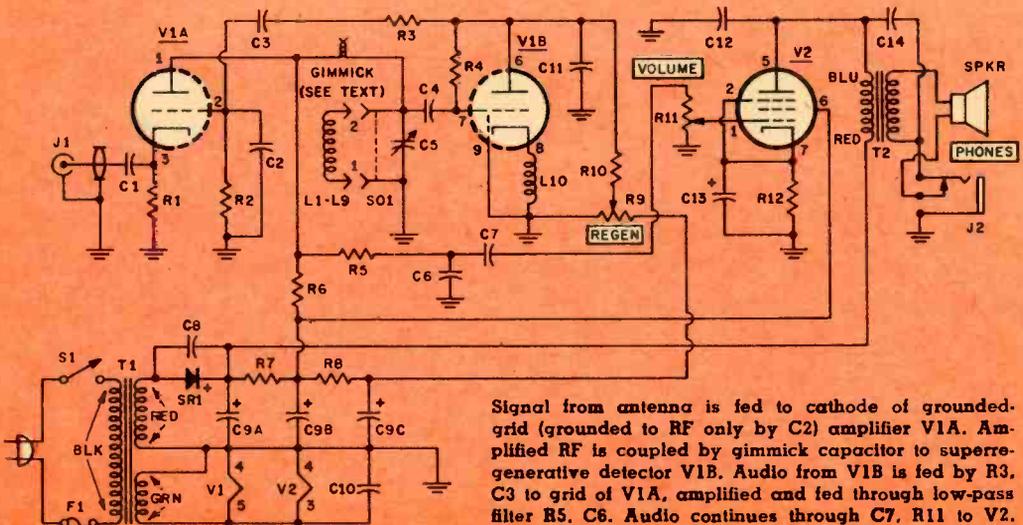
#### Resistors: 1/2 watt, 10% unless otherwise indicated

- R1—560 ohms
- R2—1 megohm
- R3, R5—47,000 ohms
- R4—8.2 megohms
- R6, R10—100,000 ohms
- R7, R8—1,800 ohms, 2 watts
- R9—150,000 ohm linear-taper pot
- R11—500,000 ohm audio-taper pot
- R12—380 ohms, 1 watt
- S1—SPST switch on R11
- SO1—4-pin tube socket (Amphenol 77MIP4)
- SPKR—3 1/2 inch, 3.2-ohm speaker
- SR1—Silicon diode: 500 ma, 400 PIV
- T1—Power transformer: 125 V @ 15 ma, 6.3 V @ 0.6 A (Stancor PS-8415 or equiv.)
- T2—Output transformer: 10,000-ohm primary, 4-ohm secondary (Stancor A3879 or equiv.)
- V1—6BZ7 tube
- V2—6AK6 tube
- Misc.—7- and 9-pin tube sockets, RG58/U coax, 8x6x4 1/2-inch aluminum cabinet (LMB-146; Newark Electronics Corp. stock No. 91F1014). Or 12-7-4-inch aluminum cabinet (Bud CU-2111A) or 8x6x3 1/2-inch aluminum cabinet (Bud CU-2109A).
- Terminal strips, knobs, AC line cord, piece of sheet aluminum for chassis.



Signal from antenna is fed to cathode of grounded-grid (grounded to RF only by C2) amplifier V1A. Amplified RF is coupled by gimmeck capacitor to superregenerative detector V1B. Audio from V1B is fed by R3, C3 to grid of V1A, amplified and fed through low-pass filter R5, C6. Audio continues through C7, R11 to V2.

# VHF Broadspanner

tric shafts for vernier operation, the shafts cannot be cut. Therefore, mount C5 behind the front panel with  $\frac{3}{8}$ -inch-long spacers. This will keep the tuning knobs close to the dial.

Then install a solder lug on the rear of C5 with a 6-32x $\frac{1}{8}$ -inch machine screw. Also mount a solder lug on the chassis as shown in the diagram on top of the third page of this article. Mount C5 so the bottom of its frame is  $\frac{3}{8}$  inch above the chassis.

Install the coil-socket bracket directly behind C5. This will make for short leads from pin 2 on SO1 to C5 and to the gimmick capacitor and C4 (under the chassis). Solder short pieces of wire from the ground lug on the rear of C5 and pin 1 on SO1 to the nearby chassis ground lug.

The author used a piece of perforated aluminum to protect the speaker's cone. And it's a good idea to use a 1-inch bracket between the speaker's lower left mounting hole and the chassis for extra rigidity.

To make the gimmick capacitor, solder a short length of No. 20 plastic-covered solid hookup wire to pin 1 of V1. Solder another short piece of the same wire to the junction of the No. 12 buss wire from pin 2 of SO1 and C4. Twist the wires tightly for 4 turns and cut off the excess. Position the gimmick as shown in the pictorial.

Connect input jack J1 to lug 3 on terminal strip TS3 with a short length of RG58/U coaxial cable. Make sure the shield is grounded at both ends as shown in the pictorial.

After the last part has been installed, cut a 3- or 4-inch hole in the back (the U-section) of the cabinet. Locate the hole directly behind the coil socket so the coils can be inserted and removed easily.

Rubber feet on the bottom of the cabinet finish the job and will prevent the receiver from scratching table surfaces.

Because of the many bands covered by the Broadspanner, you'll find it easier to use a logging scale calibrated from 0 to 100 for the dial, rather than a scale calibrated in frequencies.

Make and cement a long pointer to the back of the larger tuning knob and ink a line down the center of the pointer to make tuning easier. The longer the pointer and the larger the dial, the less trouble there will

be in returning the receiver to a station previously logged. Attach the dial to the front of the cabinet with glue or tape.

## Winding the Coils


The frequencies covered by each coil (indicated in our diagram) are only approximate and depend on how carefully you do the winding. Coils L1 to L4 are made with No. 14 nyclad wire tightly scramblewound on a  $\frac{3}{4}$ -inch-diameter form (such as a dowel). After the coil is wound, remove it and wrap it tightly with plastic tape to hold the turns together. Then cut the leads to the lengths specified. Coils L5-L9 are made with No. 12 tinned copper wire and are wound on  $\frac{1}{2}$ -inch forms. The pins for all coils can be obtained from the base of a discarded 4, 5 or 6 pin tube.

Two dimensions on the coil diagram are worth talking more about. On the sketches for coils L5 and L9, the *spacing* dimension ( $\frac{1}{4}$  inches for L5,  $\frac{1}{2}$  inch for L6,  $\frac{3}{16}$  inch for L8) is the distance between the first and last turns. All lead lengths are measured from the body of the coil to the end of the *contact pin*.


Remember: be careful when winding the coils and be accurate with your measurements. Sloppy construction could mean that a coil will tune only part of the band for which it is designed.
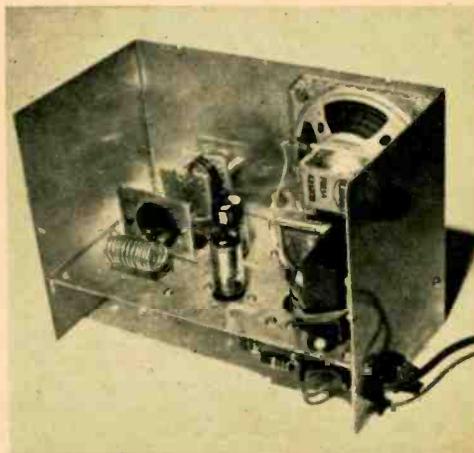
## Testing and Operation

After all coils have been wound, install the




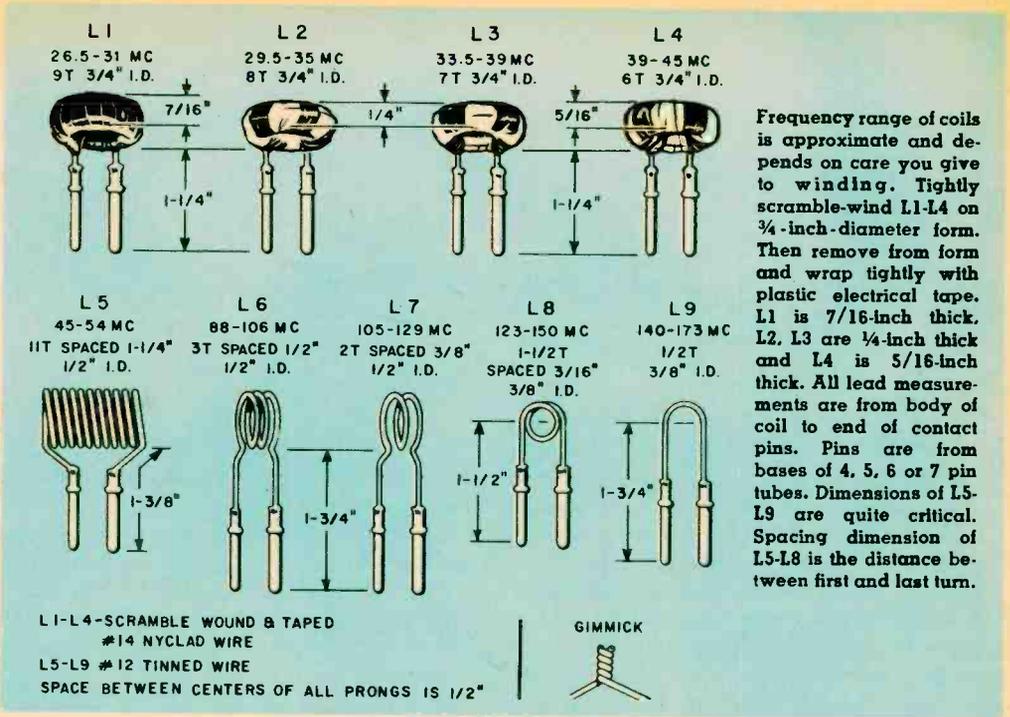Use  $\frac{3}{8}$ -inch spacers between tuning capacitor and panel and mount coil socket exactly as shown.



Frequency range of coils is approximate and depends on care you give to winding. Tightly scramble-wind L1-L4 on 3/4-inch-diameter form. Then remove from form and wrap tightly with plastic electrical tape. L1 is 7/16-inch thick. L2, L3 are 1/4-inch thick and L4 is 5/16-inch thick. All lead measurements are from body of coil to end of contact pins. Pins are from bases of 4, 5, 6 or 7 pin tubes. Dimensions of L5-L9 are quite critical. Spacing dimension of L5-L8 is the distance between first and last turn.

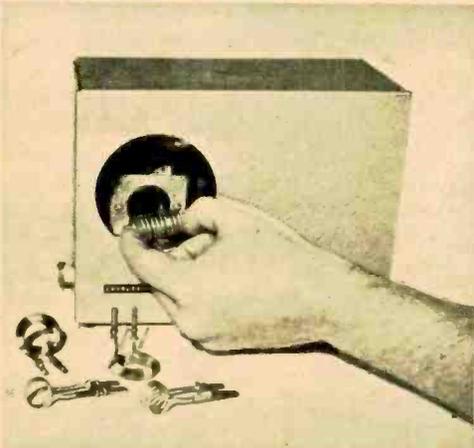tubes and turn on the receiver. Set the volume control to maximum, plug in a coil for a fairly active band, such as CB, and allow a few minutes for warm-up. Check the receiver's operation by rotating the *regen* control until you hear a hissing sound.



A 3- or 4-inch hole in back of cabinet behind the coil socket makes coil changing an easy job.

The Broadspanner does not require alignment but coils L5-L9 may have to be compressed or spread apart slightly to get them to cover the band for which they're designed. The frequency covered by a particular coil also depends on the wiring and layout of the receiver. If you want great dial accuracy, calibrate the receiver and trim the coils with the aid of a grid-dip meter or a signal generator.

To tune a station, turn the *regen* control until you hear a loud hiss, then tune the band. Back off on the control for the best sound, once you've found a station. It's a bit more difficult to tune an FM signal than an AM signal. The best way to go about it is to tune the Broadspanner slightly to one side of the station's center frequency (this detection method for FM is called slope detection). The setting of the *regen* control is tricky and critical for FM, but a little practice and you'll get the feel of it.

Local high-power VHF stations can be pulled in easily with a short hank of antenna wire or a whip antenna. But for best reception, a good VHF antenna is required. Matter of fact, a 2-meter commercial job will do

[Continued on page 117]

# AMATEUR RADIO CONFIDENTIAL

*The untold story about some fun & frolic that you might be surprised to find on the ham bands—but it happened!*

Anonymous

A FEW issues back we were treated to a report on the wild goings-on that could be observed on the Citizens Band. It was billed as a confidential history of CB and the guffaws echoed all the way to Washington.

"Those crazy Cbers," the hams could be heard saying, "they're all going to get booted off the air the way they're going."

"Boy, I'm glad the hams never did anything like that. Policing ourselves has really saved us."

People are funny that way, especially hams. At times we have memories so short we have to look at our QSL cards to find out what our calls are. And while we were getting charley horses in the shoulder blade from patting ourselves on the back we just couldn't remember a one of those wild times back in the late Forties when Hiram Percy Maxim's ghost tried to turn in his ticket every night at the Pearly Gates FCC office.

The truth is, friend, in their own way the hams made latter-day Cbers look like children playing with smoke signals.

Back in the middle Forties when I got my ticket I just couldn't wait to get on the air. So the day my license arrived I fired up the rig, hit the key and called CQ—for four straight hours. All I heard was a few cricket chirps from south Jersey and a couple of guys on phone trying to ignore this nut with the Morse.

I'd been in such a rush to make my first QSO that I hadn't checked anything out and my signal sounded like a V-12 Lincoln hitting on two. Then I remembered what the old-timers said. So I cut my power way down and called again. I happened to be (we'll say) W1XGO but only a looney would have signed that way. XU1A, I signed, slanting



my eyes slightly and turning a pale yellow. Suddenly I was in China.

I signed just once. That was enough. Twenty meters got as quiet as a quiz show when somebody says "payola." Then 40 bolts of lightning struck and guys that had never worked 20 before piled up like a regiment of lemming on a death march, all calling XU1A.

So I knew the transmitter worked.

A strange thing about that Chinese station. I never could understand the 599X reports I kept getting on the air. I was running a whole watt plate input, with enough key clicks to cover all of 20 and most of 10 meters. And my hum would have put the Wabash Cannonball to shame. 599X, they kept saying. Crazy hams.

The fun of making like a Chinaman with a spark gap eventually paled so I decided to reform. I cleaned up the signal, developed a better fist—and worked as bootleg DX for six months. But I was not just any DX call. I was the rare one. It took less work that way because I never had to sign more than once. EP1 in Iran. VR5 on Tonga Island. XZ4 in Burma. Pretty soon the lists in QST of phony DX calls were all mine. It was a game. Think up new ones faster than they could print them.

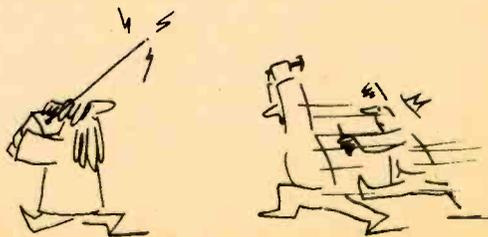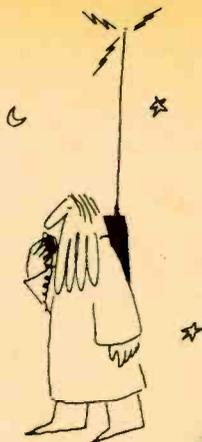


## AMATEUR RADIO CONFIDENTIAL

In case you get the idea that I was the only wild hair on the band, ponder some more. I just happened to specialize in rare DX of the seven-dollar-bill type. The bands were loaded in my big-city area with antics that gave me a halo by comparison.

When I finally realized that all my dubious ingenuity wasn't bringing me in any QSL's I had to find another challenge. It turned out to be that mysterious enigma known as Public Service. I joined our 10-meter Civil Defense net. Let me tell you what big-city CD was like back then. Think of a group of grown men and no-talent adolescents playing at disaster and you have it. The only disaster that happened was when the outfit met.

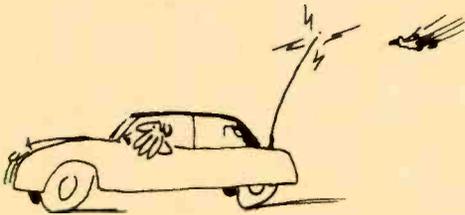The typical CD crew got together once a week, fired up a three-rack kilowatt and made believe they were mobile, rescuing victims of bombings and giving safe harbor to maidens fleeing from overly amorous males. All this was accomplished, of course, while the gang lounged around the shack amid enough



equipment to send the chief engineer at a broadcast station off his rocker. Obviously, I figured, something had to be done to improve CD's public image.

So one evening I cranked my power down to a flea's whisper. "Help! Help!" I panted. "My car ran off the road and turned over." The hard-hitting, efficient net swung into action. Net control took only 15 minutes to decide who would go out in mobiles in that terrible weather (it was about 60 degrees at the time) to rescue the poor slob.

Meanwhile, the big boys with their gallons and four-element rotaries were triangulating to get a fix on my signal and, in typical disaster style, looked at the map and gave my position in latitude and longitude. The mobiles, now careening around town like ants with hot tailpipes, had no maps but that didn't stop them from getting into a squabble about where so many degrees of latitude and longitude would be.

I naturally was helping things along. "There's a fire starting in the engine," I reported breathlessly. "Hurry!"

They finally got the triangulation deciphered. One fix had me ten miles out in the Atlantic. One put me 300 miles away at the Canadian border. The brain of the outfit topped them all, though. He figured my signal was coming in the long way around from Okinawa.

"Help," I said. "The whole car's going up. I'm being burned alive!"

"Actually," said the brain, "it's a skip signal. A soldier on Okinawa. Probably in a Jeep accident. It's out of our territory."



"It's getting hotter and ho. . . ." My signal cut off with dread finality.

"Well, it's too late now, anyway," somebody said. "Too bad he wasn't around here so we could help him."

It took three days for the trusty gang to realize that maybe everything hadn't been on the up and up. But the episode did have one good result. We tried to form a *real* CD organization, one that had mobility as well as all that equipment. Everyone who checked in (except control) was required to be in a car. Besides getting fresh air, we were ready to go into action immediately. It finally dawned on the big wheels that all the cars were parked in their own driveways—but fresh air was fresh air.

The true ham, it is said, is forever an experimenter. Which reminds me of the affair of the balloon. One morning WIXKK wandered by the house, looking like a refugee from the Signal Corps.

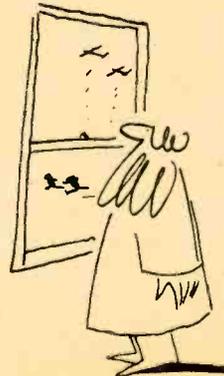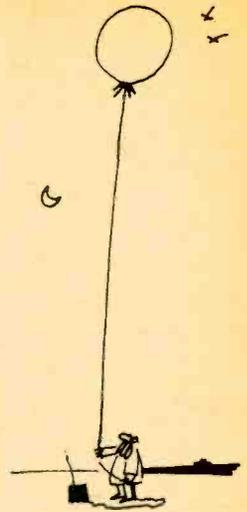"What did you do?" I ask, blandly. "Get a Marshall Plan



package from Ft. Monmouth or something?" "We have here," says XKK, "a little roll of wire, or maybe a roll of little wire—like 5,000 feet of No. 93. And over here in this pretty metal canister is a balloon. This other stuff is radio junk. Come with me."

We walk down to the beach and hook his radio junk (an apt term) to one end of the wire and rig the reel of wire to the canister. The canister happened to be a surplus type that you plunged into the water. The balloon then inflated automatically with a light gas and took off.

XKK is ready. "Today," he says, "you and I will have the world's highest antenna. Ever hear of a 5,000-foot tower?" With that he plunges the canister into the salt water and funny things start happening. Suddenly XKK is no longer on the ground. He can fly. I grab for him and then we're both making like Peter Pan. Before we quite know what is going on we are in 30 feet of water, and we swim like half-looped mud turtles. The difficult part came later, though. How do you explain to a police captain that a big red balloon pushed you into the water?

Being true-blue ham experimenter types, we had another go at it a week later with a slightly smaller balloon. That day modest miracles happened. We did get the wire up and we worked out like crazy. It's the middle of summer and we're working 500-mile ground wave on 10 meters (which nobody ever has believed).

We're having so much fun that we fail to notice that our position is being surrounded by police like in the siege of Ft. Apache by the Indians. The leader of the gang remembers us from the week before. Why in hell, he wants to know, if we are going to fly balloons do we have to get them right in the airport's flight pattern?

Frequency control in those days, as you may remember, was a little like holding your finger on Old Faithful and trying to squirt a passing spider in the eye. After the Iowa outfit came out with its rig you could believe it if someone said you were off frequency. Until then, you only guessed.

One of the big trouble spots was the bottom of the 10-meter band. Everybody wanted to work 5 kc inside, with the sidebands going right up to the edge, because that was where all the foreign DX was. The overseas boys were permitted to work lower than we were and so they



invariably came sliding up the band from the bottom. The DX chasers wrestled like a flock of cats with a dead fish, each one trying to get lower than the others so he could be the first one heard by the foreigners.

There was no rule-breaking in those nightly heave-hos, for a while. But then one wise guy stamped the herd by moving deliberately below the band edge. The result could have been predicted. Seven other guys moved below XGO (as if you didn't know who it was) and then a whole herd of lids moved below *them*. There were all kinds of stories about QSO's with passing airplanes and dog sleds in Alaska.

The arguments about who was or wasn't outside the band was acrimonious. "He was, too, outside the band," you'd hear. "I know he was because I was 10 kc out and he was below *me!*"

In those early post-war years mobile operation probably was the biggest challenge to the amateur. It usually involved a trunkful of surplus gear and mobile modulation sounded as if someone had pushed the RCA pooch into the horn. Then suddenly one manufacturer hit gold with a 30-watt hand-ful that mounted under the dash and it was unusual to hear a W station that wasn't mobile. All the lover's lanes around the suburbs were split between romance and DX, since both did best in deserted spots on high hills.

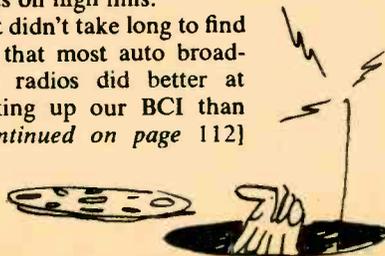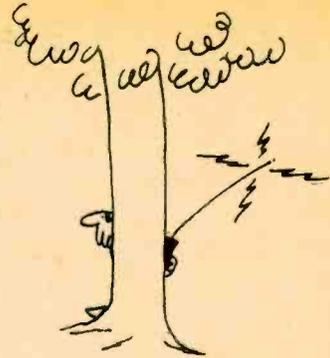It didn't take long to find out that most auto broadcast radios did better at picking up our BCI than [Continued on page 112]





# AWARDS

## for HAMS, SWLs, BCBers!

Fourth Award Period declared officially open

New BCB Award is based on states or provinces QSLed

**W**ITH THE OPENING of its Fourth Award Period, EI's DX Club also celebrates a birthday, and a happy one at that. In the few short years of its existence, the Club has seen its membership grow by leaps and bounds. The Third Award Period, which ended April 30 of 1964, saw more applications for Awards roll into Club offices than during any previous award period. Further, because this was the first time the Club offered an Award specifically for radio amateurs, the Third Award Period saw Club membership more than double.

Since some newcomers may not be familiar with the place and purpose of EI's DX Club, a few words about the Club itself seem in order. To begin, EI's DX Club is a club with a difference. It holds no meetings, collects no dues, elects no officers. Matter of fact, it conducts only one sort of business. And that consists of awarding attractive-looking certificates to radio listeners and amateur radio operators for proven proficiency in the radio art.

Proof, in this instance, takes the form of official QSL cards or letters from stations which have been heard or contacted. In other words, EI's DX Club exists solely to issue certificates—certificates which serve as Awards to dedicated radio listeners and amateur radio operators who can prove that they have heard or communicated with a given number of distant stations.

**Types of Awards.** As you perhaps already have gathered, EI's DX Club offers two major types of Awards. One, though it has come to be known as the SWL Type, actually is subject to no frequency limitations whatsoever (save for the two BCB classes, which we'll discuss shortly). But it is a *listener's* certificate nonetheless, awarded to individ-

uals who have documented proof that they have received transmissions from a given number of stations.

The second type of Award, known as the Ham type, is issued only to radio amateurs. As is the case with the so-called SWL type of Award, hams must have documented proof of transmissions involving a given number of stations. But in the case of the Ham award, such stations must be ham stations, and the applicant must have conducted *two-way* communications with the stations concerned.

**Classes of Awards.** When you come right down to it, both types of Awards really comprise a series. The HAM Award is issued in three different classes, while the SWL Award is issued in five classes. And, except for one class of SWL Award, the governing factor which determines the particular class of Award to which an SWL or a ham is entitled is the number of countries which the applicant has proof of having received transmissions from or conducted communications with.

Easiest type of Award for an SWL or a ham to qualify for is the 10-country Award, also called the SPECIAL. SWLs need have proof only of having received transmissions from stations in ten different countries. Hams, likewise, must have proof of having communicated with other ham stations in ten different countries.

Next class of Award for which both SWLs and hams may apply is the 50-Country Award, also called the GENERAL 50. And for those who want to try for the most coveted DX Club Award of all, there is that champion of awards — the 100-Country Award, also known as the DX CENTURY. As is the case with the SPECIAL Award, SWLs must prove reception of, while hams

# AWARDS

## for HAMS, SWLs, BCBers!

must prove two-way communications with stations in each country concerned.

As stated earlier, there are no frequency limitations for the 10-, 50- and 100-Country SWL Awards, though the frequency of the station always must be indicated clearly on the official application form. Hams naturally are limited to the various international ham bands for their transmissions, so they necessarily do have some obvious restrictions as to frequency. However, hams need not state a specific frequency on the application form. Simply mentioning the ham band on which the two-way communications took place is sufficient.

A fourth class of Awards—available only to SWLs—is known as the BROADCAST BAND Award. One of the two classes of SWL Award which are subject to frequency limitations, the BROADCAST BAND Award requires reception of stations in at least 15 different countries on the standard broadcast band (535-1605 kc).

Also available to SWLs is the Club's fifth and newest class of Award—the BROADCAST BAND STATESIDE SPECIAL. Unlike every other Award the Club offers, the BCB STATESIDE SPECIAL is *not* based on the number of countries an applicant has been able to enter in his log book. Instead, it is governed by the number of U.S. states or Canadian provinces for which the applicant has logged stations. Like the older BROADCAST BAND Award, the BCB STATESIDE SPECIAL is available only to SWLs. Similarly, being a BCB Award, only stations on the standard broadcast band (535-1605 kc) may be counted.

To be eligible for a STATESIDE SPECIAL Award, an applicant must have received transmissions from BCB stations in at least 25 U.S. states or Canadian provinces. In other words, since there are only two countries involved, countries are not the deciding factor. It is the number of states or provinces in those two countries that determines whether a BCB STATESIDE SPECIAL Award will be granted.

**How To Apply.** Our Fourth Award Period now is in progress, and all applications must

be received during the time it is in effect. Official closing date for the Period is April 30, 1965, and all applications must be post-marked on or before that date to be eligible.

Official entry blank for an Award from EI's DX Club is the EI DX CLUB LOG which appears on the following pages. Full instructions are given at the top of this LOG, so it is not necessary to repeat them here. However, there are three things to keep in mind when filling in your DX CLUB LOG. Completeness, neatness and accuracy all are of utmost importance if your application is to win you an Award.

By completeness, we mean that every line and every blank must be filled in, and filled in in its entirety. By neatness, we mean that your application must be tidy and clearly legible if it is to be of value to the Club secretary or to you. And by accuracy, we mean that each and every entry—whether it be your own Zip Code, a station's call letters or the time at which a station was heard—must be correct in every respect. Failure to prepare a complete, neat and accurate application only can delay or perhaps negate your chances of receiving an Award.

To remove the LOG from the magazine, clip neatly along the dotted line with a pair of scissors. And for filling in the form itself, a ball-point pen is recommended.

A word of advice about the blank called CLASS OF AWARD: be certain to apply for the highest class of Award to which you are entitled. For example, a ham who has proof of two-way communications with stations in over 50 different countries naturally would apply for the GENERAL 50 Award rather than the SPECIAL.

Do *not* send your QSLs with your application. However, keep them on hand, since you may be asked to furnish any or all of them to prove the entries on your DX CLUB LOG actually are valid.

When you have checked and double-checked your DX CLUB LOG and satisfied yourself that it is complete, neat and accurate in every respect, place it in an envelope and mail it to

EI's DX CLUB  
67 West 44th Street  
New York, N.Y. 10036

If all is in order, your attractive EI DX Club Award will reach you after processing, ready for framing and hanging on the wall of your shack.

# EI DX CLUB LOG

NAME ..... (last name) ..... (first name and initial) ..... HAM CALL .....

ADDRESS .....

CITY ..... STATE AND ZIP .....  
(or country)

TYPE OF }  SWL  
AWARD }  HAM

CLASS OF  
AWARD .....

INSTRUCTIONS. Clip along broken line at left. Under *Type of Award*, check *SWL* or *HAM*, depending on the type of award you are applying for. Under *Class of Award*, write class of award you are applying for (see text). Fill in *all* items on each entry line below. Under *Date*, use figures (such as 10-1-63); all log entries must be dated January 1, 1950, or later. Under *Time*, use local standard time and 24-hour clock (0000 to 2359 hours). To list second 50 countries, make up additional log pages in similar style. Fourth Award Period ends April 30, 1965.

	DATE (local)	TIME (local)	FREQUENCY (kc)	STATION	LOCATION (city)	COUNTRY	TYPE OF QSL (check one)
1							card <input type="checkbox"/> letter <input type="checkbox"/>
2							card <input type="checkbox"/> letter <input type="checkbox"/>
3							card <input type="checkbox"/> letter <input type="checkbox"/>
4							card <input type="checkbox"/> letter <input type="checkbox"/>
5							card <input type="checkbox"/> letter <input type="checkbox"/>
6							card <input type="checkbox"/> letter <input type="checkbox"/>
7							card <input type="checkbox"/> letter <input type="checkbox"/>
8							card <input type="checkbox"/> letter <input type="checkbox"/>
9							card <input type="checkbox"/> letter <input type="checkbox"/>
10							card <input type="checkbox"/> letter <input type="checkbox"/>
11							card <input type="checkbox"/> letter <input type="checkbox"/>
12							card <input type="checkbox"/> letter <input type="checkbox"/>
13							card <input type="checkbox"/> letter <input type="checkbox"/>
14							card <input type="checkbox"/> letter <input type="checkbox"/>
15							card <input type="checkbox"/> letter <input type="checkbox"/>
16							card <input type="checkbox"/> letter <input type="checkbox"/>
17							card <input type="checkbox"/> letter <input type="checkbox"/>
18							card <input type="checkbox"/> letter <input type="checkbox"/>
19							card <input type="checkbox"/> letter <input type="checkbox"/>
20							card <input type="checkbox"/> letter <input type="checkbox"/>
21							card <input type="checkbox"/> letter <input type="checkbox"/>

	DATE (local)	TIME (local)	FREQUENCY (kc)	STATION	LOCATION (city)	COUNTRY	TYPE OF QSL (check one)
22							card <input type="checkbox"/> letter <input type="checkbox"/>
23							card <input type="checkbox"/> letter <input type="checkbox"/>
24							card <input type="checkbox"/> letter <input type="checkbox"/>
25							card <input type="checkbox"/> letter <input type="checkbox"/>
26							card <input type="checkbox"/> letter <input type="checkbox"/>
27							card <input type="checkbox"/> letter <input type="checkbox"/>
28							card <input type="checkbox"/> letter <input type="checkbox"/>
29							card <input type="checkbox"/> letter <input type="checkbox"/>
30							card <input type="checkbox"/> letter <input type="checkbox"/>
31							card <input type="checkbox"/> letter <input type="checkbox"/>
32							card <input type="checkbox"/> letter <input type="checkbox"/>
33							card <input type="checkbox"/> letter <input type="checkbox"/>
34							card <input type="checkbox"/> letter <input type="checkbox"/>
35							card <input type="checkbox"/> letter <input type="checkbox"/>
36							card <input type="checkbox"/> letter <input type="checkbox"/>
37							card <input type="checkbox"/> letter <input type="checkbox"/>
38							card <input type="checkbox"/> letter <input type="checkbox"/>
39							card <input type="checkbox"/> letter <input type="checkbox"/>
40							card <input type="checkbox"/> letter <input type="checkbox"/>
41							card <input type="checkbox"/> letter <input type="checkbox"/>
42							card <input type="checkbox"/> letter <input type="checkbox"/>
43							card <input type="checkbox"/> letter <input type="checkbox"/>
44							card <input type="checkbox"/> letter <input type="checkbox"/>
45							card <input type="checkbox"/> letter <input type="checkbox"/>
46							card <input type="checkbox"/> letter <input type="checkbox"/>
47							card <input type="checkbox"/> letter <input type="checkbox"/>
48							card <input type="checkbox"/> letter <input type="checkbox"/>
49							card <input type="checkbox"/> letter <input type="checkbox"/>
50							card <input type="checkbox"/> letter <input type="checkbox"/>

# The S-NINER

*Hook our tuned preamp on the front of an all-band rig and watch the S-meter jump!*

By HERB FRIEDMAN  
W2ZLF



**W**HEN it comes to receivers, it's what's up front that counts. And those budget all-band rigs have precious little up front. A receiver must have a tuned RF stage if you want to join the big-league DXers. Sure, some low-cost receivers with a tuned RF stage give pretty good performance for the price. But they always can use a little extra sensitivity and selectivity to dig out those rare flea-power stations.


Put a preselector in front of a receiver and you will say goodbye to the times you tried to get another ten-degree twist out of the sensitivity or volume control.

The easiest and best way to pep up a budget receiver's performance is with EI's S-Niner. The S-Niner is a tunable, high-gain RF preamplifier that covers the ham bands, short-wave bands and the Citizens Band. You just connect it between the antenna and the receiver's input. Depending on the receiver's input circuit (an antenna trimmer capacitor) you'll get another 3 to 5 S-units (18 to 30db gain). And that's a lot of added sensitivity in anyone's book.

But before you go out to buy the parts, a word about the dial assembly. The National dial we specify in the Parts List has a vernier. Don't use an inexpensive imported vernier. The slightest misalignment between tuning capacitor C1 and an inexpensive vernier will cause the vernier to bind. The S-Niner tunes sharply and a binding vernier will cause problems.

**Construction.** The S-Niner should be built on a 5x7x2-inch aluminum chassis. The 5¼x7-inch front panel, which is held to the chassis by S1, S3 and NL1, can be cut from an aluminum chassis bottom plate.

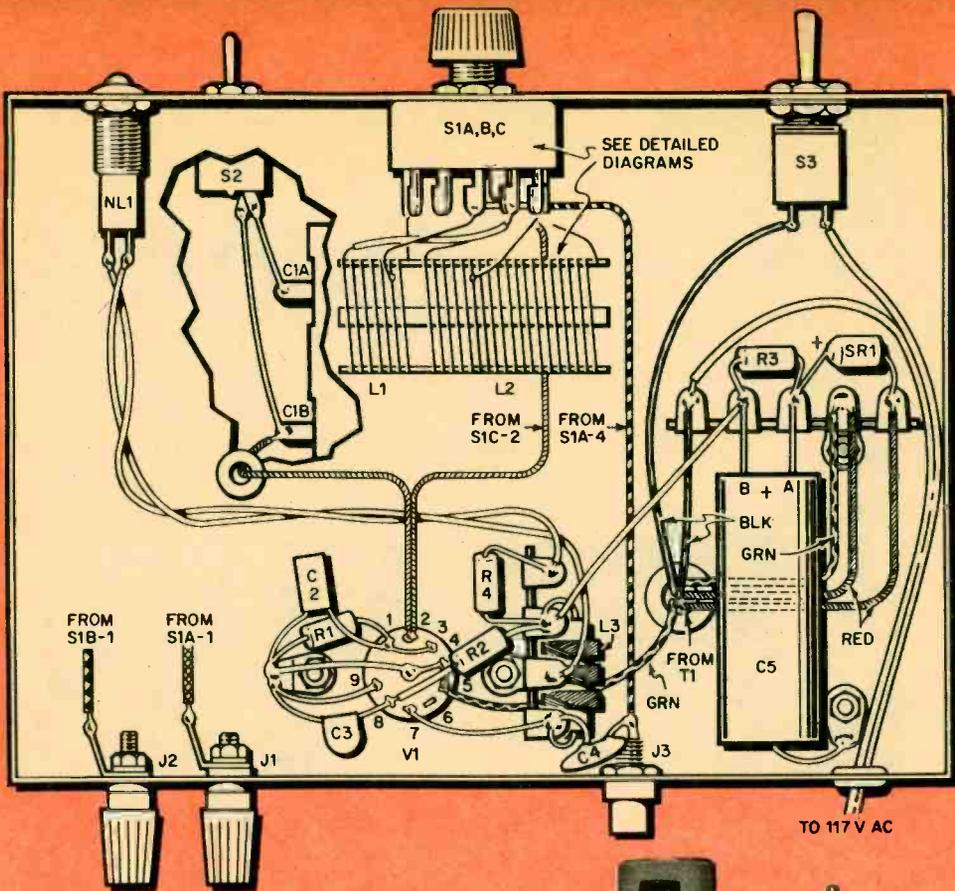
First, hold the front panel against the front of the chassis and temporarily mount C1 on the center of the top of the chassis. Put the dial vernier on C1's



TO 117 V AC

Because there's RF all over the place, you must follow exactly the layout shown here. The placement of the lead from S1 to J3 is quite critical. It should be near the chassis and to the right of L2. Keep all component leads as short as possible. Chassis is shown cut away at upper left for a better look at connections to C1 and to S2.

# The S-NINER

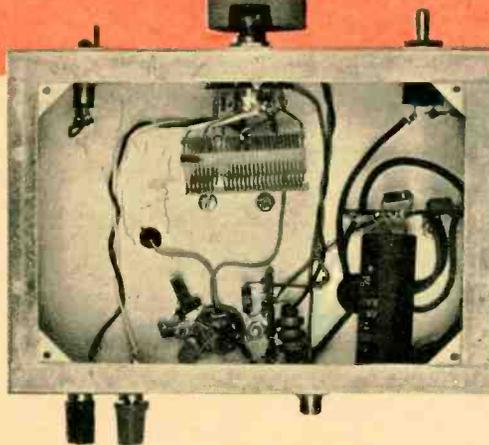

shaft (cut to 1/2-inch length) to determine where to cut a hole in the front panel for the vernier. Remove C1 from the chassis and then cut all the holes in the front panel for S1, S2, S3 and NL1. File away the bottom of the vernier so it clears the top of the chassis.

Coils L1 and L2 are made from a section of Barker and Williamson No. 3011 Mini-inductor coil stock. Before you start cutting

and unwinding turns, carefully study the pictorial of the coils on the last page of this article.

Best place to start is with L2. Unwind one turn at the right of the stock by *rolling*, not pulling, the wire out of the plastic supports with needle-nose pliers. Count off 19 turns and cut the wire at the left side of the 20th turn's support. Unwind the 20th turn and you have a 19-turn coil. Cut only the 20th turn

of wire, not the plastic supports.

Unwind the 21st turn, which is the start of L1. Count 7 turns to the left, cut the wire and roll it out of the plastic support. Discard the remainder of the Miniductor by cutting through the plastic supports.

Connect taps to the 14th turn from the right end of L2 and the 5th turn from the left end of L1. Press in the turns on each side of the tapped turn. Then solder No. 20 or No. 22 solid wire to the tapped turn. Take care when soldering that a solder blob doesn't short two turns—the wires are close.


All leads from S1 that connect to other points in the circuit should be installed before connecting L1 and L2 to S1. Make certain all connections to S1 are correct since it will be almost impossible to change them after the coil is installed on the back of S1. Note that each section of S1 has an unused lug.

After the coil/switch assembly is mounted in the chassis, route the lead from S1 to J3 far away from other wires and V1's socket. Note that the lead from C1B to S2 is above the chassis.


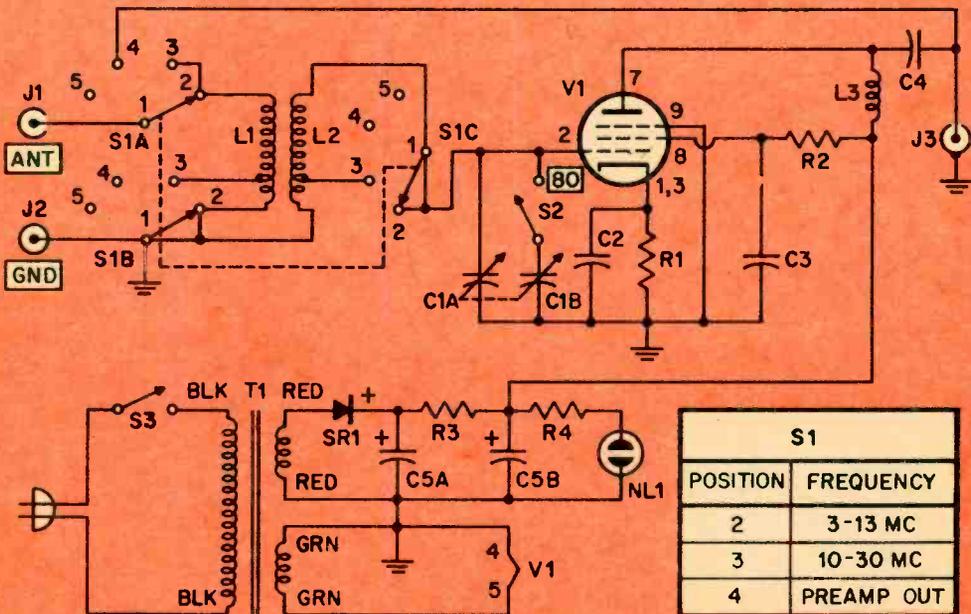
#### PARTS LIST

- C1A, C1B—2 gang, TRF variable capacitor  
10-365 mmf per section (Lafayette MS-142 or equiv.)  
C2—.01 mf, 75 V or higher capacitor  
C3—.001 mf, 600 V ceramic disc capacitor  
C4—.01 mf, 600 V ceramic disc capacitor  
C5A, C5B—20/20 mf, 150 V electrolytic capacitor  
J1, J2—5-way binding posts  
J3—Phono jack  
L1, L2—Barker & Williamson No. 3011 Miniductor (Newark Electronics Catalog No. 40F940)  
L3—1 mh. RF choke (National R-50 or equiv.)  
NL1—NE-2 neon lamp and holder
- Resistors: 1/2 watt, 10%  
R1—150 ohms  
R2—5,600 ohms  
R3—1,000 ohms  
R4—220,000 ohms  
S1A, B, C—3-pole, 4-position rotary switch (Mallory 3234J)  
S2, S3—SPST toggle switches  
SR1—Silicon diode; minimum ratings: 100 ma, 500 PIV  
T1—Power transformer; secondaries: 125 V @ 15 ma, 6.3 V @ .6 A (Lafayette TR-121)  
V1—6EJ7 tube  
Misc.—National type MCN vernier dial, 5x7x2-inch aluminum chassis, tube socket with shield

V1 is a high-gain ( $\mu m = 15,000$ ) frame-grid pentode whose input is tuned by C1A, B. S1 selects appropriate taps on L1, L2 for 3-13 or 10-30 mc ranges. In position 4, S1 feeds signal directly from antenna to receiver. When tuning the 80-meter band, close S2. Leave S2 open when tuning all other frequencies.



Position switch S2 as shown, draw section-dividing lines and connect jumpers as well as leads that go to J1, J2, J3 and V1. Cut 4 turns off coil stock, then push in turns on each side of 6th turn of L1 and 5th turn of L2. Solder leads to 6th and 5th turns, being careful not to apply too much heat. Side of coil shown should be mounted so it faces the rear of S1. Keep L1's and L2's leads short so that L1 is close to S1

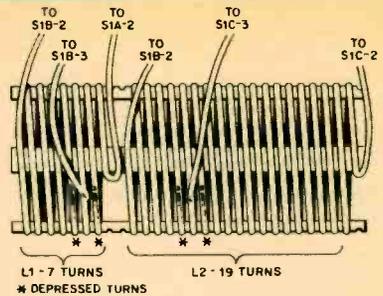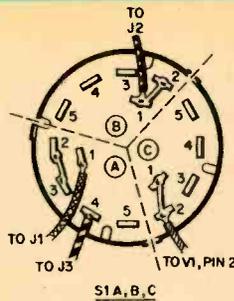

## The S-NINER

The last assembly step is the mounting of the front panel and C1B's connection to pin 2 on V1. Don't force the vernier on C1's shaft since it may bind and prevent precise tuning. First tighten the vernier setscrew on C1's shaft, then attach the panel to the chassis by tightening S1, S3 and NLI's mounting nuts.

**Aligning and Using the S-Niner.** Connect your antenna feedline to binding posts J1 and J2 and connect the receiver to J3 with RG58/U coaxial cable. If the receiver is an AC/DC job, do not connect the coax shield directly to the receiver's ground terminal. Connect a .01 mf, 500 V capacitor between the shield and the ground lug on the receiver.


S1's extreme counterclockwise position (position No. 2 on the schematic) is the low band—4 to 13 mc. When tuning 3 to 5 mc (80 meters) with S1 in this position, close S2. This connects both sections of C1 in parallel. Rotate S1 one position clockwise (position No. 3 on the schematic) to tune 10 to 30 mc (make certain S2 is open when using this band). S1's third position (4 on the schematic) connects the antenna directly to the receiver.

Set switch S3 to *on* and set S1 to position 4 to connect the antenna to the receiver directly. Tune in a signal near 4 mc, then set S1 to the low band and adjust C1 for maximum S-meter indication or highest volume (if you have a VTVM, connect it to the receiver's AVC buss and tune C1 for highest negative voltage). Mark 4 mc on the dial (or whatever frequency you're receiving). Simi-


larly tune frequencies up to 13 mc and mark the dial scale accordingly. Calibrate the high band the same way. The 80-meter calibration should be made with S1 set to the low band and with S2 closed. Use a separate dial scale for the 80-meter band.

Always keep the S-Niner on when the receiver is on and set S1 to position 4. When tuning a station that needs extra gain, set the S-Niner's dial and S1 for the same frequency to which the receiver is set. Then adjust C1 for maximum signal. If your receiver has an antenna trimmer, adjust it for maximum gain.

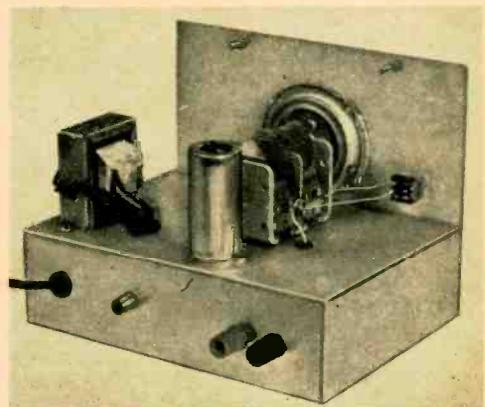Some higher-priced receivers have sharply tuned input circuits which might cause the S-Niner to break into oscillation. This will be evidenced by a pinned S-meter. A slight detuning of the receiver's antenna trimmer will solve this problem. If it doesn't, tune the S-Niner to the *exact* signal frequency to stop oscillation. —



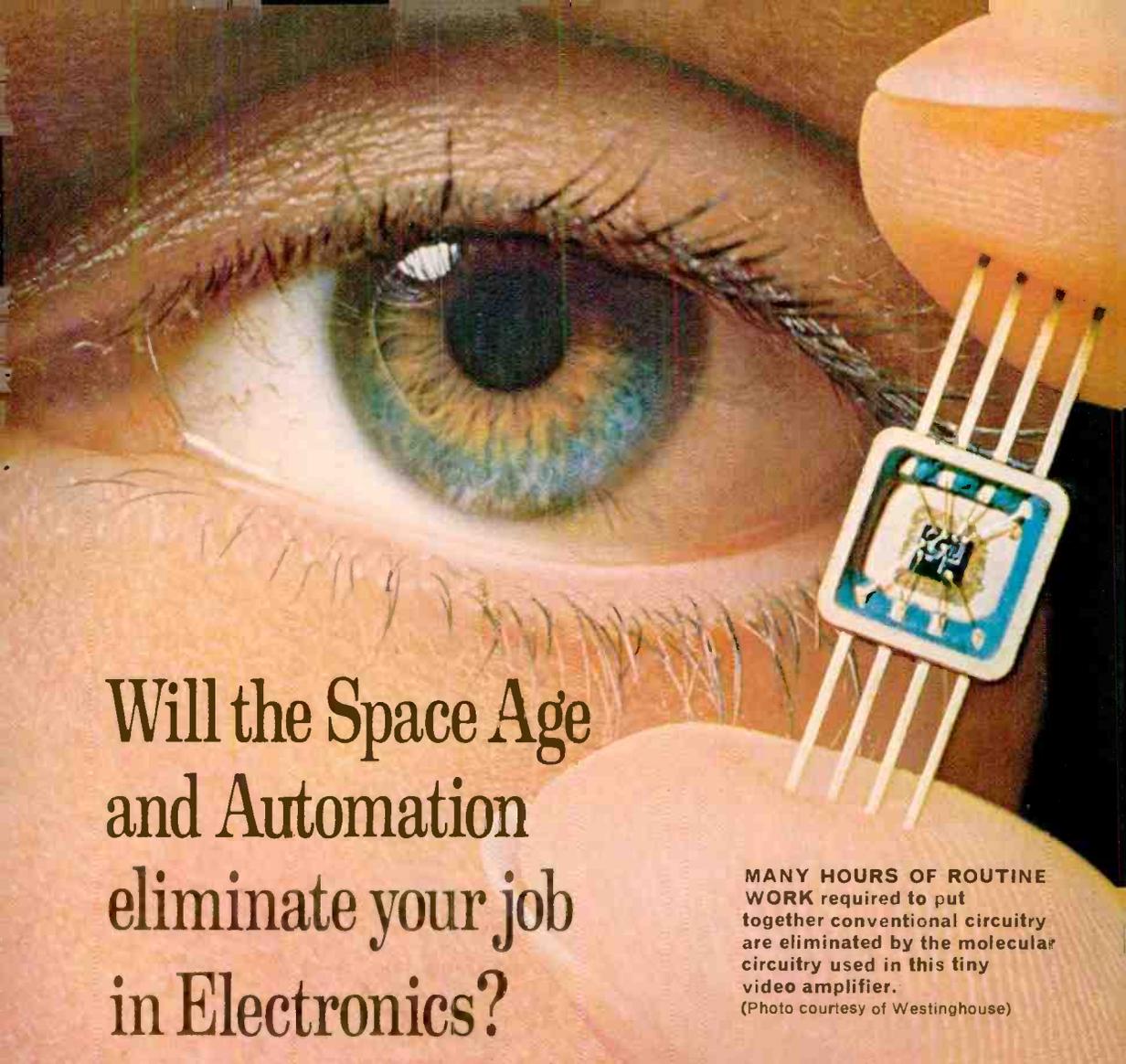Note short, direct connections between switch S2 (right) and each section of tuning capacitor. And be sure that you use a shield-base socket for V1.



# Will the Space Age and Automation eliminate your job in Electronics?

MANY HOURS OF ROUTINE WORK required to put together conventional circuitry are eliminated by the molecular circuitry used in this tiny video amplifier.

(Photo courtesy of Westinghouse)



**YOUR JOB IS IN DANGER** if you work on the routine level where new automated manufacturing techniques are rapidly replacing men. And your job is in danger if you haven't learned enough about new developments in electronics to be of real value to your employer in the space age.



FIRST CLASS  
Permit No. 288-R  
Washington, D.C.

**BUSINESS REPLY MAIL**

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

Postage will be paid by




**The Capitol Radio Engineering Institute**

3224 Sixteenth Street, N.W.

Washington, D.C. 20010

VIA AIR MAIL



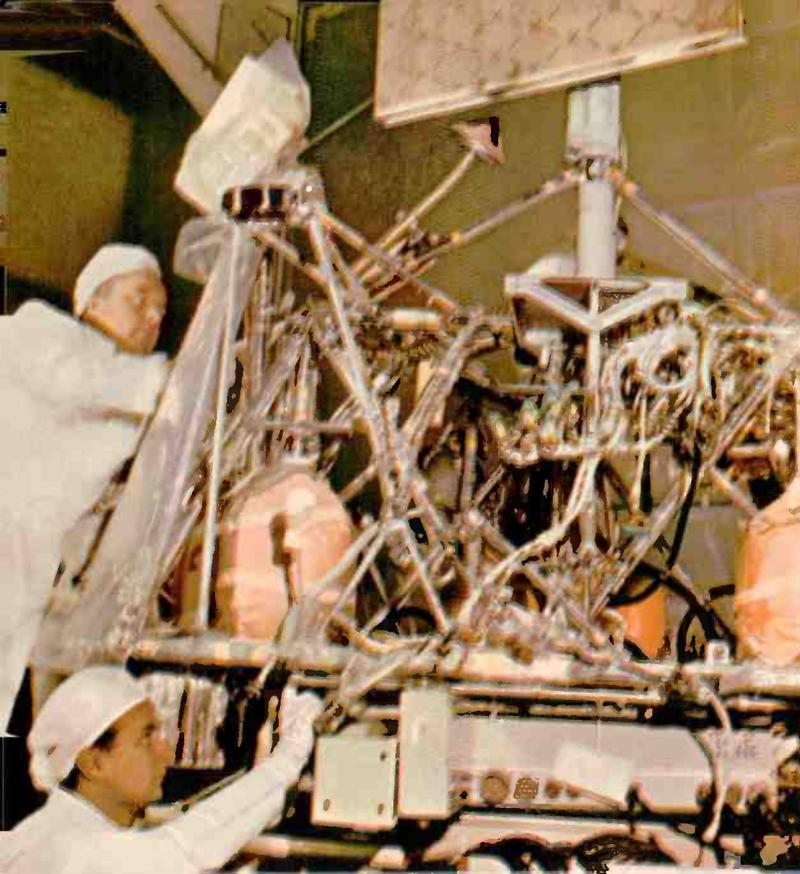

## Protect your future through the New CREI Programs in Space Electronics

**SPACE DATA SYSTEMS**—Includes multi-channel recording, analog to digital conversion systems, data acquisition and processing.

**SPACECRAFT TRACKING AND CONTROL**—Includes such areas as orbit calculation and prediction, inertial guidance, electromagnetic wave generation, space surveillance and environment.

**AEROSPACE RADAR ENGINEERING**—Includes surveillance radar, antennas, receivers, components and microwave equipment used in space applications.

■ The first extension programs developed specifically to help men in electronics apply their experience to the space effort.


■ Content developed to meet employment requirements as determined by government and private organizations in the space field. Text material prepared in leading space-oriented organizations.

CREI also offers specialized education in these important areas of electronics: **Automation, Industrial, Nuclear, Servomechanisms, Computers, Radar, Communications, Aeronautical, Navigational and Television.**

You are eligible for these programs if you work in electronics and have a high school education.

**FREE BOOK**  
GIVES FULL INFORMATION ON CREI PROGRAMS.

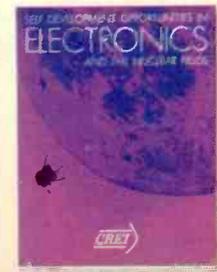For your copy, mail postpaid card or write: CREI, Dept. 1701-C, 3224 16th St., N.W., Washington, D.C. 20010



**CREI** Will the space age end your career in electronics? Or will it open up new opportunities for you? What happens depends on whether or not you supplement your education in electronics with the new knowledge needed to make you a valuable employee today. The new CREI Programs in Space Electronics offer you the up-to-date knowledge employers want and need.

**FILL OUT AND AIR MAIL TODAY—NO POSTAGE REQUIRED**

### The Capitol Radio Engineering Institute

DEPT. 1701-C, 3224 Sixteenth St., N.W., Washington, D.C. 20010

Please send me FREE book describing CREI Home Study Programs including Programs in Space Electronics. I am employed in electronics and have a high school education.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

Employed by \_\_\_\_\_

Type of present work \_\_\_\_\_

Check:  Home Study  Residence School  G.I. Bill E-33



**SPACEBOUND...** All set for Transit DX? It's here, and you even have an option or two on how to get in on the fun.

When fully operational, the U.S. Navy's satellite navigation system will provide accurate, all-weather position-finding data anywhere on earth. And for DXers, these four satellites will produce a sure-fire space logging at least once every three hours—and with even the crudest of receivers.

Since one Transit frequency is on the lower edge of TV channel 2 (54 mc), you'll have no trouble setting up appropriate equipment. All you need is a 6-meter converter for use along with your regular SW set. Or a TV set with an IF around 27 mc (some old Philcos had them), an SW receiver which will tune that IF and a 100-kc frequency standard also will do the trick.

To use this latter combination, first wrap the SW receiver's antenna around the TV set's last video IF tube to determine exactly where the TV IF falls on your SW dial. This can be done best by tuning in a local TV station (preferably channel 6 or lower), then locating the video carrier (strongest buzz) on your receiver. Next, switch on the marker,

put the TV on channel 2, tune the radio down approximately 1.25 mc and locate the marker.

Except for occasional minor frequency adjustments to compensate for drifting, all you have to do now is wait. While waiting, it's a good idea to reduce brightness so the picture tube won't distract you or unnecessarily strain your eyes. But be sure the contrast stays on full.

Though the Transit system is supposed to be operational in the near future, there's only one satellite on 54 mc as of this writing. And while obviously part of the Transit program, it's designated simply as 1963 satellite launch 49C. Matter of fact, all the U.S. Navy told EI was that, "The signals you mention are from an experimental vehicle. . . . The mission of the vehicle was the gathering of environmental data."


Further, while the basic Transit signal will be a continuous time marker, 1963 49C seems to have a more complex transmission pattern. Could be that the Navy and NASA are killing several birds with one satellite.

So long as there's just one satellite on 54 mc you might have to wait 12 hours before bagging it. And if you have a channel 2 station in your area you'll have to try after midnight or at whatever hour this station leaves the air.

*[Continued on page 121]*



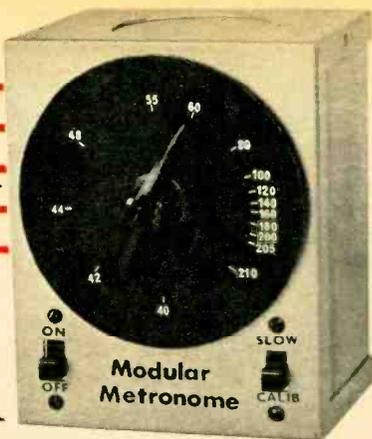A television set is one way into Transit DX, assuming you don't have a 6-meter converter and don't mind doing things the kooky way. As explained in text, the set must sport a 27-mc video IF, and the only time you can do your Transit DXing is after local channel 2 packs up for the night.



# MODULAR METRONOME

*Potted parts, an hour's time and you've got the beat.*

"**T**IME is the stuff life is made of," someone once said. And if you've studied a musical instrument you know how true this is since timing and rhythm are as important as hitting the right note. To get the music really swinging you've just gotta have the beat. Best way to develop it is with a metronome.

Most standard spring-wound metronomes cost around \$12. Commercially-made electronic metronomes could run a lot more. However our Modular Metronome (MM) can be built for about \$6. Its construction is so simple that all you have to know is the difference between black and white piano keys to get it together.

Secret of its simplicity is a module designed specifically for the application. It's a potted black cube that contains transistors, capacitors and resistors; five leads extend from it.


Add batteries, a potentiometer, switches, a resistor and a speaker and you've got a two-speed metronome that counts from 20 to 200 beats per minute. And besides being useful to musicians, it can also be used as an audible timer in a darkroom. For this application you'd just set the MM to 60 beats per minute and count off the seconds. This will allow you to pay full attention to other operations instead of watching a sweep-second hand on a clock. You could even use the MM to help you count sheep when you're trying to fall off to sleep.

**Construction.** A 3x4x5-inch Minibox will house the MM perfectly. The speaker is mounted in the top of the box. Use a piece of grille cloth or perforated metal to protect the speaker's cone from dirt or damage.

Potentiometer R1 should be mounted in the upper center of the front panel as shown in the photo on the next page. *On-off* switch S2 should be mounted on the lower left side of the front panel, and *slow-calibrate* switch S1 should be mounted at the lower right.

Switch S1 and resistor R2 aren't really necessary, but their added expense is worth it for two reasons: 1) They produce an extra slow speed of about 20 beats per minute, and 2) they spread out the calibration markings. Even if you don't want the two-speed feature, it's a good idea to use R2 for the second reason. If you don't use S1, place S2 in the center of the front panel.

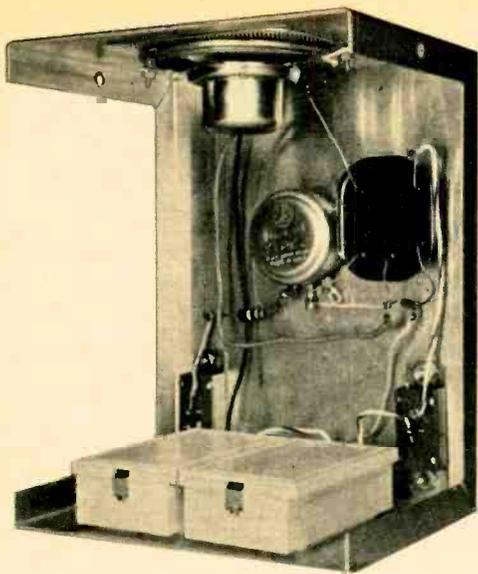All wiring is straightforward and not critical. Terminal strips are not required



Instructions supplied with metronome module specify a 2-megohm potentiometer for R1. However we used a 1/2-megohm potentiometer to get the unit to operate at about one beat every three seconds when S1 is open. Close S1 and slowest speed is about 40 beats per minute. Speed increases as R1's wiper approaches R2.

since the module leads can be used for tie points.


It's a good idea to mark calibrations on a separate circular disc rather than on the front panel since calibration is affected by battery voltage and, to some extent, by temperature. Cut the disc from a thin sheet of soft aluminum and paint it dull black or dark gray. It should be about 3 1/2-inches in diameter to allow the use of a large pointer knob and so there will be plenty of room for all markings. By sandwiching the disc between an extra set of nuts and washers on R1's shaft, the disc can be turned to correct calibration.

**Calibration** requires a sweep-second hand watch and patience. With the disc mounted in position, turn on the MM and close S1. Rotate R1's shaft full counterclockwise, aim the pointer knob straight down and tighten it on the shaft. Now, simply count the number of beats in one minute. There should be
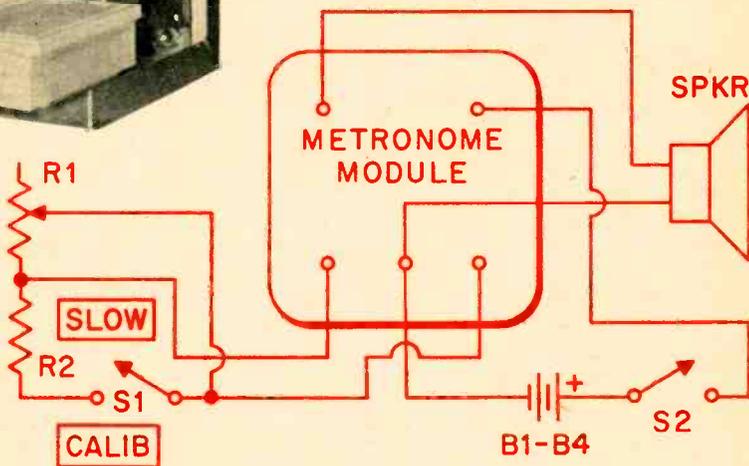
#### PARTS LIST

B1-B4—1.5-volt penlite battery  
 R1—500,000-ohm linear-taper potentiometer  
 R2—330,000-ohm, 1/2-watt resistor  
 S1, S2—SPST slide switch  
 SPKR—2-inch PM speaker  
 Metronome module (Lafayette SP-298)  
 Misc.—3x4x5-inch Minibox, pointer knob, battery holder


Mount the speaker on top of the cabinet and glue the module in place. Author used plastic boxes for batteries, but a Keystone type 182 battery holder (Allied 55 J 904) will do the job just as well. Cover the module leads with spaghetti.




around 40, but this may vary with individual modules.

Great accuracy is not required or attainable with the MM, so count to the nearest round number. Rotate the knob about 45 degrees and count for one minute. Put a light pencil mark on the disc opposite the pointer and keep track of the number of beats for each mark on a separate sheet of paper. You'll find after about 180 degrees of rotation that the speed increases more rapidly with only a small change in knob position, therefore pick out numbers about 20 beats apart.

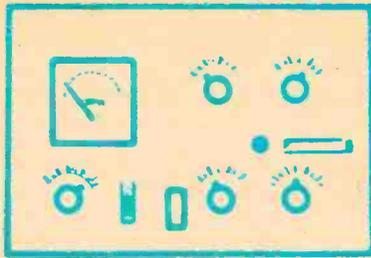When calibration is completed remove the disc and mark it with transfer-type numbers. The easiest way to check the calibration is at 60 beats per minute. Always move this marking on the disc under the pointer knob when it is set for this speed. The rest of the scale will now be pretty close. 



By HERB FRIEDMAN, W2ZLF

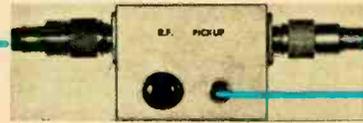

# PARASITE CW MONITOR

**Y**OU really can't tell what your fist sounds like if you don't hear it. Ask any Old Timer at CW or a Navy man who has spent several years pounding brass and he'll agree to that mighty quickly. And the best way to keep close tabs on your fist is with a keying monitor. This simple but valuable shack accessory reproduces your CW signal just as it would sound at the receiving end.

Oh sure, there are hams who claim they can judge their fist by the clickety-click of the key. But their code probably sounds like a fifty-caliber machine gun. There's irregular spacing between characters, halting and choppy dots and dashes. To have a fist that invites replies to your CQ's, a keying monitor is a must.

EI's Parasite CW Monitor fills this bill and has several features not found in many other keying monitors. To avoid being caught with a dead battery, the monitor has been designed to be powered by your transmitted RF. A pitch control allows you to select a pleasant tone in the range of about 400 to 1,000 cycles.

And a volume control has been included to spare the household of the noise when you're sending. The volume control also affects the output level at the phone jack for either high- or low-efficiency phones. And it doesn't make any difference whether the phones are high or low impedance—even hi-fi phones can be used. To prevent the volume control from changing the tone's pitch, an L-pad is used instead of a rheostat or potentiometer.

Another big feature is the remote RF pickup box. Instead of running an extra transmis-

sion line over the operating table to the Monitor, as is usually done with many other RF-powered units, our separate RF pickup box is connected in your antenna feedline. And best of all, the Monitor can be used with any transmitter all the way from a 1 watter up to a 1 kilowatt rig.



## Construction

While the parts layout in a 4x5x6-inch Minibox is not critical, try to follow our arrangement as shown in the pictorial and photo. T1 must be the exact type specified. The Monitor most likely won't work if you substitute another transformer. To avoid a complicated L-pad connection we suggest you use the three-terminal pad specified. It looks and is wired just like a standard potentiometer.

Take particular note of the connections to phone jack J5, which is a shorting-type jack. When the phone plug is removed, the speaker is connected through the jack to T1. Make certain you do not use a grounding-type jack which will short T1 to ground when the plug is removed. To avoid damage to the speaker cone, install a piece of screen or perforated board between the speaker and the cabinet.

The RF pickup unit (built in a 2¾x2½x1½-inch Minibox) is designed for coaxial transmission line, therefore J1 and J2 should match your existing connectors. If you use twinlead, eliminate J1 and J2 and use a two-lug, screw-type terminal strip. Connect one lug to the cabinet (ground) and connect resistor R1 to the other lug.

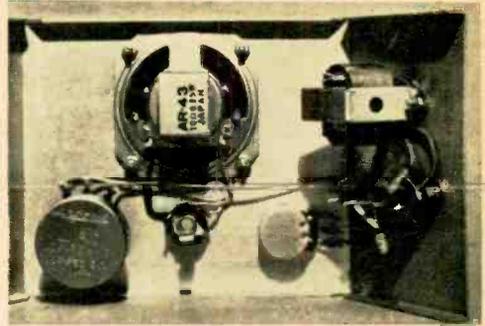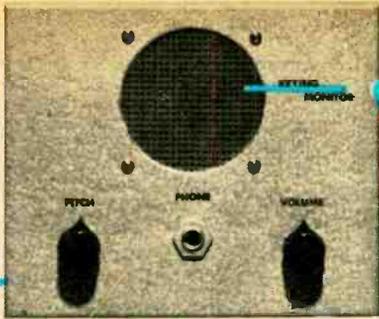The value of resistor R1 is determined by your transmitter's input power. To keep cal-



culations simple, use this formula:

$$R1 = \sqrt{W \times 10} / 0.007$$

W equals your transmitter's input power in watts. For example, if your transmitter has an input power of 10 watts,  $R = \sqrt{10 \times 10} / 0.007$  which is 1,429 ohms. Since 1,429 ohms isn't a standard value, use the closest lower standard value—1,300 ohms.

### Checkout and Use

Be absolutely certain the wiring of the Monitor and RF pickup is correct. A single improper connection could result in Q1 going up in smoke.


Connect the RF pickup in series with your coax transmission line and connect J3 to J4 with a piece of shielded cable. Set R2 full counterclockwise (*off*) and set R5 to its mid-position. Temporarily connect a VOM or VTVM from J4 to ground (negative probe on J4). Tune up your transmitter to normal

power output and then slowly advance R2. As R2 is advanced, the meter should deflect up-scale. If the needle deflects to the left, D1 is installed in reverse.

At about  $-2$  V you should hear a tone in the speaker. Since cleanest tone will be obtained between  $-4$  and  $-7$  volts, keep turning R2 until the meter indicates  $-6$  volts. Rotate pitch control R3 from one end to the other; you should hear clean tone through the entire range. If the transistor's leakage is high the tone may cut out at *one* end, which

power output and then slowly advance R2. As R2 is advanced, the meter should deflect up-scale. If the needle deflects to the left, D1 is installed in reverse.

Easiest way to wire the monitor is to install all small parts on the side first. Solder the transistor leads directly to the terminal strip being careful not to apply too much heat to them. Though R5 looks like an ordinary potentiometer, it is an L-pad whose two resistance elements are contained in one case. The lugs are numbered and connections must be made to them as shown. Don't use a potentiometer for R5 or the tone will be affected when you change volume level. And do not substitute some other transformer for the type specified for T1 in the Parts List or the unit will not work properly. Watch the wiring to phone jack J5.

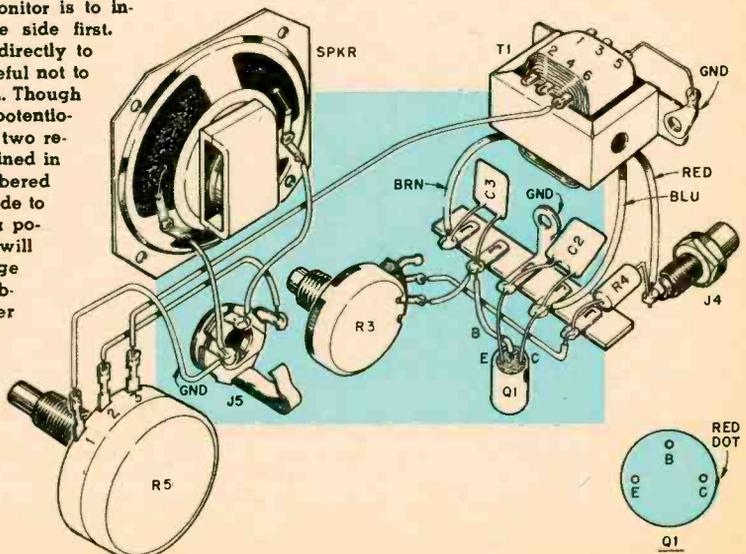

# PARASITE CW MONITOR


would be normal. If the tone drops out long before you reach *both* ends, adjust R2 for a slightly higher voltage until pitch control is constant. Under no circumstances should the voltage at J4 be more than  $-9$  V.

If the transmission line SWR exceeds 3:1 it is possible that insufficient voltage will be developed in the pickup to power the Monitor. If this is the case try reducing R1's value in small increments of about 20 per cent. For example, if the calculated value for R1 is 1,000 ohms try 800 ohms.

As a bonus the Monitor can indicate antenna intermittents. Since the tone depends on both the supply voltage and SWR, any change in the antenna system, such as loose elements, will be indicated by a change in pitch during keying (this applies only to coax transmission lines).

If you use twinlead transmission line the RF pickup connection is slightly different. Set R2 full counterclockwise. Then connect a length of wire to one lug on the terminal strip. Wrap the wire around the transmission line a few times and connect the other end to the other terminal-strip lug. Key the transmitter and slowly advance R2 while watching the meter connected to J4. If you cannot obtain the proper voltage with R2 full-open try increasing the number of turns wrapped around the line. Sometimes a high SWR will prevent sufficient RF pickup. If this happens place the pickup coil near the transmitter's output tank coil. If you have a high-power transmitter and prefer to not fool around near the output coil, place the pickup loop near the driver stage. And make sure it is firmly held in position.

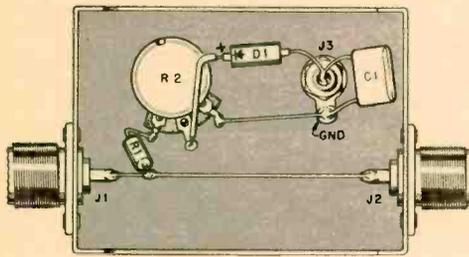
Whether you use coax or twinlead transmission line, once you've adjusted R2 the setting is good for life.



RF pickup box. If you use twinlead transmission line, eliminate J1 and J2 and install a two-lug screw-type terminal strip near R2. Connect one lug to ground and connect R1 to the other lug.
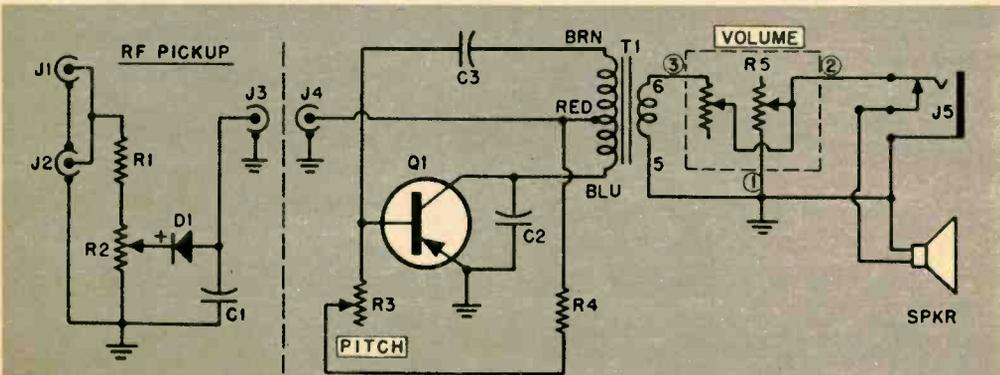
## PARTS LIST

- C1,C2—.25 mf, 15 V or higher capacitor
- C3—.05 mf, 15 V or higher capacitor
- D1—1N34A diode
- J1,J2—SO-239 connector (see text)
- J3,J4—Phono jack
- J5—Shorting-type phone jack
- Q1—2N217 transistor
- R1— $\frac{1}{2}$  watt, 10% resistor (see text for value)
- R2—1,000 ohm, linear-taper potentiometer
- R3—100,000 ohm, linear-taper potentiometer
- R4—22,000 ohm,  $\frac{1}{2}$  watt resistor
- R5—8-ohm L-pad (Lafayette VC-49)
- SPKR—2 $\frac{1}{2}$ -inch, 8- or 10-ohm speaker
- T1—4-watt universal output transformer (Lafayette TR-12)



Portion of RF in transmission line is rectified by D1 and applied to transformer T1. Oscillator, comprising C2, C3, R3, R4 and Q1, starts and its output is coupled by T1 to L-pad R5 and speaker.

Buy now, think later. Bad business? Sure. And what better reason for a CBer to plan ahead?

By ALEX F. BURR, 16W2941

**T**HINK QUICKLY. How many CBers do you know who ran right out, plunked down several hundred smackeroos for a couple of installations and later became unhappy with the selection they had made? You probably could chalk up as many names as you have fingers in ten seconds flat. And even this wouldn't complete your listing of CBers who grabbed the wrong gear.

No, selecting the right CB equipment is more than thumbing through a dog-eared catalog. In one sense, the 200 or 300 bucks you shell out is on a par with the several-hundred-million the government spends for each item of rocket hardware. But does the government pick at random? Not when they're spending your money.

To get every last buck's worth, the government develops rocket systems where each component is selected specifically for optimum performance from the next component. It's sort of like a pyramid. Each part, or block, offers support for the next block.

While you probably aren't going to launch any rockets to the moon in the near future, the same principles of *system engineering* can be used to make sure you get the most CB performance for the least money. And systems engineering starts off with you deciding exactly what your reason is for going CB. Sure, it'll be for either personal or business communications. But right there lies a whale of a difference.

**Let's start with business use.** In any business the entire effort is directed toward one end—making money. Therefore, business-oriented CB gear *has* to make money. It can do this by stimulating enough new business to pay for the cost of the equipment, and then some. Or it can reduce your present operating expenses and thus justify the initial outlay.

First thing the business user has to do is figure out CB vs non-CB expenses. As an example, let's consider one radio-equipped pickup with a driver and helper. Suppose that CB radio saves the truck one five-mile trip to the base station every day. This is a total of ten miles on a round trip and, what with city traffic, probably half an hour of the driver's time. In cold cash, this stacks up as

10 miles at 10 cents per mile.....	\$1.00
30 minutes at \$3 per hour for the driver....	1.50
30 minutes at 1.20 per hour for the helper. .	.60


Total savings for one radio call.....\$3.10

At the rate of one trip a day for twenty days, this gives a savings of about \$60 per month or more than \$700 per year. Result is that you now have \$700 to play with. And so long as your equipment sets you back less than \$700, you're ahead of the game.

Savings of this type are easy to spot and estimate, but there are still other, less-tangible benefits. A radio may mean better,



# SLIDE RULE CB

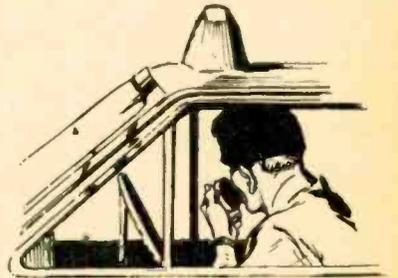

**TAXI**



quicker service for your customers. And better service means more business. You'll find that you can keep better track of vehicles, permitting closer scheduling of work. And if you know your own business you'll be able to see still other advantages of this sort.

A different set of conditions exists for the personal CB user. The primary reason for personal CB has nothing to do with making money. Instead, CB becomes a convenience. Whether it's talking to your buddy on another fishing boat or calling your wife to tell her you're stuck in traffic, CB simply makes life a lot less difficult.

Here, selecting the right CB gear gets a bit sticky. In a big metropolis like New York City, it would take an investment of at least \$400 (for two units) just to tell your wife the car has boiled over. Reason is that everybody and his brother is likely to be using CB during the rush hour and super-selective equipment, which the situation demands, comes high. On the other hand, if you live in a small town in Idaho you could do the same job—and do it well—with \$150 worth of gear.

But whether you want CB for business or pleasure, you'll get the most CB value per dollar by selecting a system which meets your needs. And a system isn't individual components tied together by connectors. Rather, it should be a complementary grouping of components which will do exactly what you need done.

**Next step** in the systems approach is finding out where you want to talk to. A good map, perhaps from a gas station, will be useful. Most base-to-mobile networks call for circular coverage around the base station. But if your store or home is on a lake or on the edge of the city, perhaps a directional beam which concentrates your signal over the city will suit your system better.

Write down your requirements so they always are in front of you. This done, you are ready to look into the equipment you'll need. A good place to start is with the antenna,

since the type you will want depends on the decisions which have just been made. If your system is to include any mobiles you'll need a vertical antenna layout. On the other hand, if you desire only point-to-point work, a horizontal system may fit your needs better.

Reason that this basic decision must be made now is that there is a large signal loss (about 24db) when a vertical antenna is used to receive a signal from a horizontal antenna or vice versa. Since mobile stations always use vertical antennas, any system which has mobile units should have a vertically polarized antenna system.

But for point-to-point work horizontal antennas often are preferred, primarily because a horizontal beam is easier to install. In terms of working range there is essentially no difference between vertical and horizontal polarization.

The best all-round CB antenna is the ground-plane or its cousin in terms of performance, the coaxial antenna. These antennas are easiest to mount and cost in the vicinity of \$15. They have a non-directional pattern, meaning the signal can be received equally well in all directions.

On the vehicles to be radio-equipped you almost certainly will use vertical whips. The standard 108-inch bumper-mounted type will fill most needs. For trucks with high bodies or cars which for some reason cannot use a long whip, the shortened, loaded jobs are available. Though some are only about 3 feet in length, these antennas approach the efficiency of full-size whips because they can be mounted on the vehicle for optimum radiation.

Perhaps the most difficult decision will be what to put at the bottom of the antenna. So far as the transmitter section of CB transceivers is concerned, there is no problem. The easiest thing to design is a 5-watt AM transmitter. And a CB transmitter is like a dragon; if you've seen one, you've seen them all. So whether you spend \$60 or \$200, you'll likely

get a transmitter that's blood brother to every other 5-watter known.

Of course, some (a few) transceivers offer speech compression or clipping—a technique which simulates a transmitter running in excess of 5 watts by boosting the modulation. And when you must squeeze out every drop of operating range, a clipper or compressor certainly is worth looking into.

**The receiver section**, however, varies considerably with price. In fact, eliminating the few transceivers which throw in features just to boost the cost (like a chrome-plated panel), the transceiver's price largely is determined by the receiver.

The most important receiver characteristic is selectivity—the ability to reject interference caused by stations on channels other than the one you are using. For example, if you're communicating on channel 7, it's a bit annoying also to hear the yakking on channels 5, 6, 8 and 9.

Your requirements for selectivity depend on where you live and why you are using CB. Certainly, in a little backwoods California town with only five active Cbers around there won't be much interference. And there's no sense in paying hundreds of dollars for selectivity you're never going to need. But in a big city, where there may be five simultaneous conversations on each channel, selectivity is the one big consideration.

One of the best ways of finding what demands your system will make on a receiver is to borrow a rig and tune across the band. There are several things to look for. What is the occupancy in your area? If the band is crowded you will need a selective model. But do you really need more than one channel? Would two or three channels suffice? Should you pay for 23 channels unless you really are going to use them?

There are a few other items such as power supplies and accessory or specialized equipment that should be considered briefly. Some sets have universal power supplies for 6 VDC, 12 VDC and 117 VAC operation. Others have supplies good for only one volt-


age and are to be preferred if it is unlikely that the supply voltage will be changed or the set moved from one vehicle to another.


If your requirement is for portable sets, you can consider the walkie-talkies, which are hand-held. They come in three sizes: 25 milliwatts, 100 milliwatts and 1 watt or more. The smallest ones are cheap and, of course, have a limited range—a few blocks at the best. In fact, they are little more than toys. But they can be useful in some activities such as antenna erection where you can't shout quite loud enough. The larger rigs are perhaps more practical for communications when more reliability and a range of a mile or more is desired.

In most large cities there are more active stations on each channel than most Cbers want to listen to. But if you're interested in hearing calls from your station only you can buy selective-calling devices which allow a transceiver to hear only those transmitters in the same system. These devices work by turning on your receiver only when it receives a special audio tone sent from one of your own transmitters. Result is that you hear nothing on your channel except when one of your own transmitters is active.

**Final choice** of your CB setup will hinge on operating convenience, price and overall quality. And for help in evaluating these characteristics, you can turn to equipment reviews, personal inspections of samples and the experience of other users. If you talk to a user, be sure that his requirements are similar to yours or his judgment likely won't be applicable to your system.

Next comes the really interesting part—evaluation of the system, which is the real heart of the systems approach. This evaluation consists merely of adding up the cost of the system and comparing it to the benefits to be derived. Will the system save you money? Will it help you make money? Will it make your job easier—or make life better? Will it contribute to better utilization of your leisure time? Only by a systems analysis can you know. ●

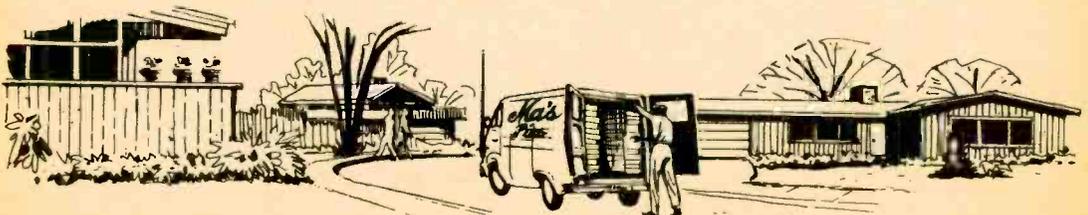

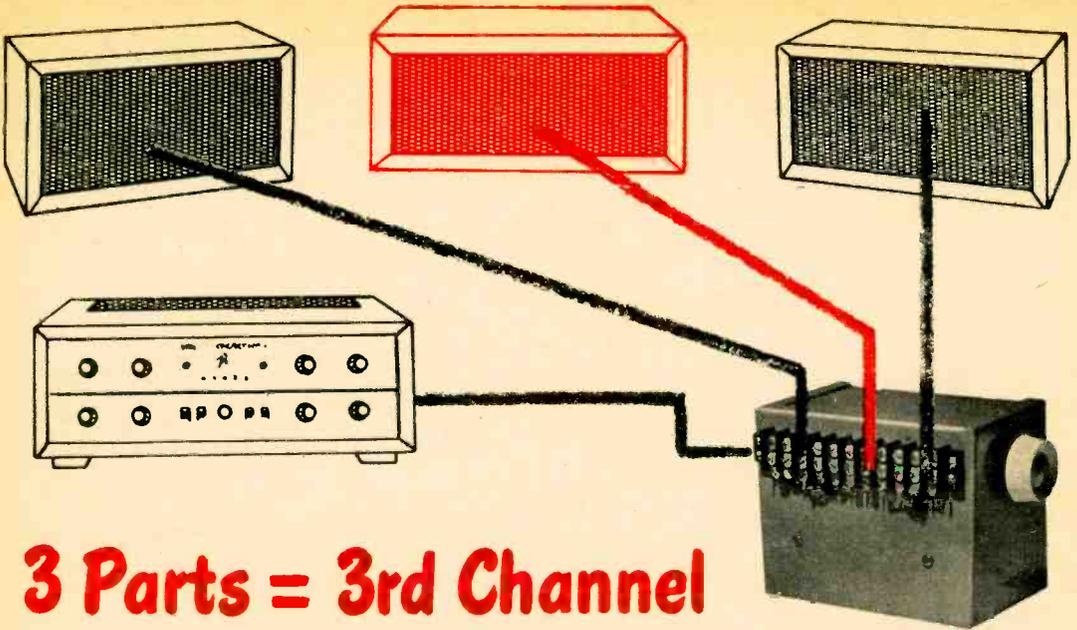

## 3 Parts = 3rd Channel

A GREAT deal of stereo sound suffers from excessive separation because the speakers are located too far apart. This means that instead of hearing a wall of sound you end up with the undersirable ping-pong effect.

Easiest way to fill the hole in the middle is with a center speaker. But you just can't connect each lead from the center speaker to the amplifier's left- and right-channel output terminals. A special transformer is required to do the job.


The transformer takes equal amounts of left- and right-channel signals and adds them to provide a balanced L + R signal. The transformer also matches impedances.

An L-pad should be installed in the center-channel speaker line to control the speaker's volume, should it be louder than the left and right speakers. If the left and right speakers are louder than the center speaker, install a dual L-pad in their lines.


The transformer, a Microtran Model HM-90, is available from Lafayette Radio (stock No. 32-4301Y) for \$6.33 plus postage. It is not listed in the catalog. Single and dual 8-ohm L-pads are available from Lafayette with stock Nos. VC-49 and VC-55 respectively.

The transformer and L-pad can be housed in a Minibox on the outside of which should be mounted a barrier-type terminal strip for connections.


—Walter G. Salm

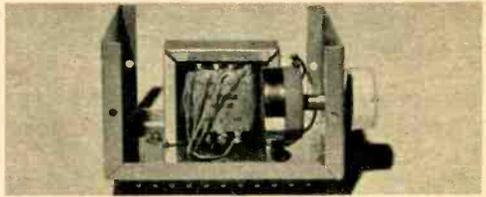

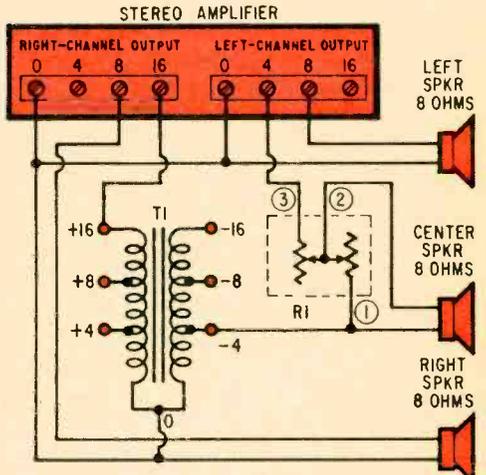All parts fit easily in a 3x4x5-inch Minibox.



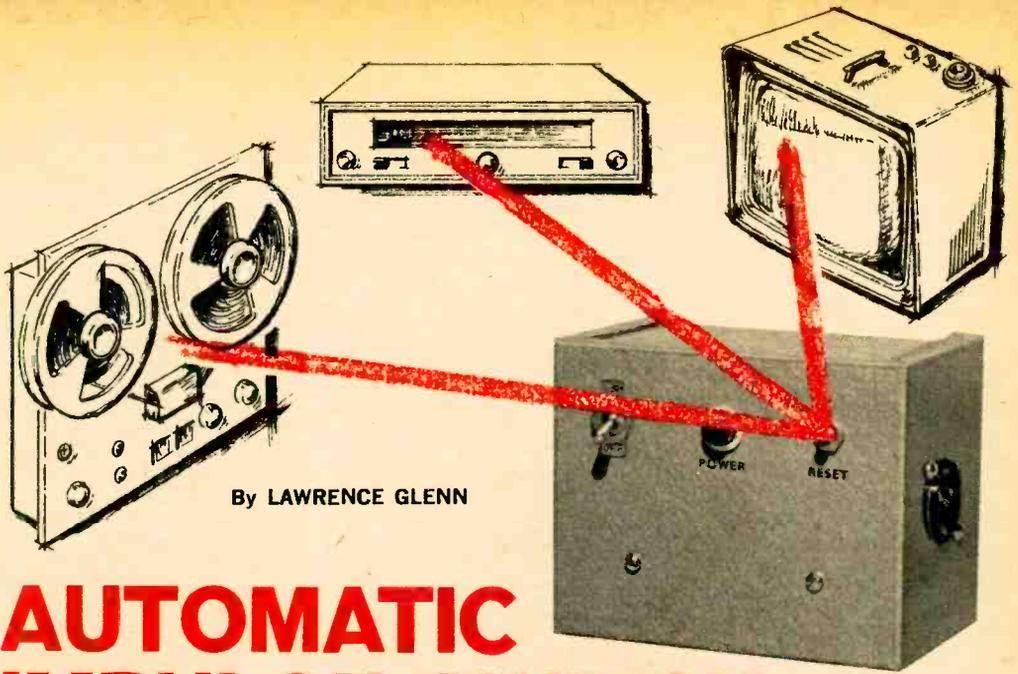Connections are for 8-ohm speakers. The transformer instruction sheet shows connections for other speaker impedances. The center speaker can also be used as a mono extension elsewhere.



By LAWRENCE GLENN

# AUTOMATIC IMPULSE SWITCH

**P**USH, it's on. Push again, it's off. Sounds almost like what you'd do with *any* switch to control power. But the Automatic Impulse Switch (AIS) is different. Its 6.3-volt AC control power is *not* applied to its control circuit continuously—it's present only in the instant the push button is pressed. And low voltage means that if you want to remote-control equipment such as a TV set, hi-fi or practically any electrical device, you can run ordinary zip cord through the walls without violating building codes. You could almost call it powerless control.

If you want to use a tape recorder to lull you to sleep, the AIS can put the tape recorder to bed, too, at the end of the tape. All you have to do is mount a set of contacts on the tape recorder so they touch the back of the tape as shown in the photo. Leads from the contacts plug into the J1. Then place a small piece of Scotch type 51 sensing tape (metallic foil with an adhesive back) at the end of the reel. When the foil touches the contacts, relay RY1 flips off and the tape recorder goes to sleep.

To see how all this is done, take a look at the schematic. Heart of the AIS is RY1—a special relay called an impulse relay. The instant current is applied to RY1 by push button PB1 (or a remotely located push button plugged into J1) RY1's contacts transfer and

*stay* transferred even after current is removed. The next impulse of current switches RY1 the other way (such as *off* to *on*) where it also remains after current is removed. All it takes is that quick spurt of current to turn something on or off. At other times the AIS just sits there.



The AIS also can be used to add push-to-talk (PTT) to ham or CB equipment. Often when PTT wires carrying AC are run in the mike cable some hum gets into the mike leads. Since the AIS requires power *only* at the instant the control switch is pressed, there will be no hum when you talk.

**Construction.** There are no special construction problems. Therefore, you can follow our layout or one of your own design. Our model was built in a 3x4x5-inch Mini-box. Be sure the wires to SO1 can carry the current required by the load.

Push button PB1 is required only if you use the AIS for remote control (it allows you to reset the AIS at the equipment location) or in conjunction with a tape recorder. That is, after the tape recorder turns itself off, you must press PB1 to turn the machine on.

S1 controls power to T1 only—not to the equipment connected to SO1. It allows you to turn off the AIS when not in use. For example, you can apply power to SO1 with PB1 and then set S1 to off. Power still will be


# AUTOMATIC IMPULSE SWITCH

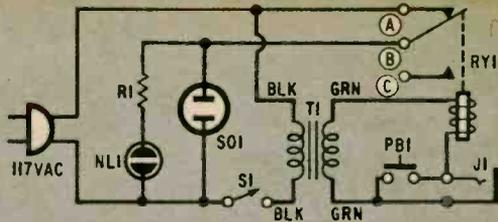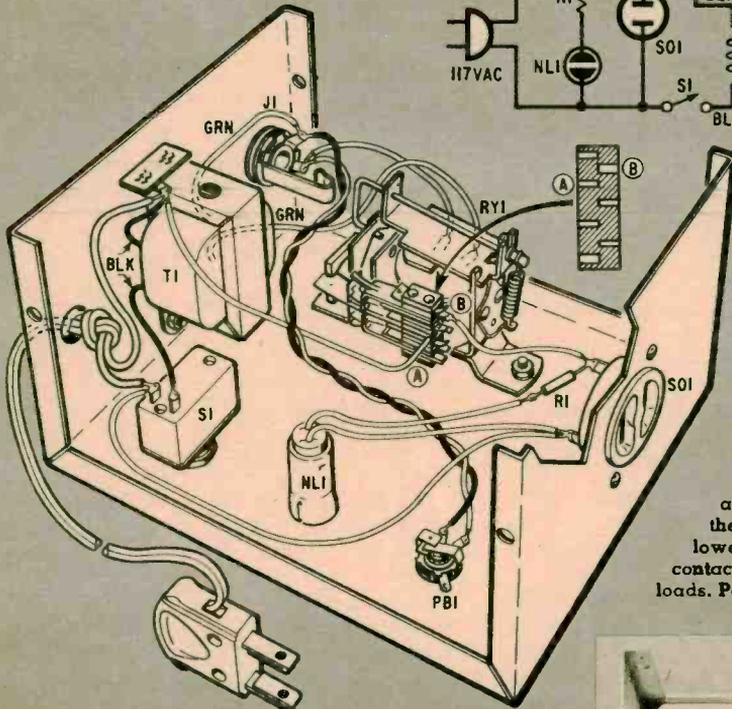

Press PB1 or a push button plugged into J1 and contacts B and C (see above) close and stay closed after PB1 is released. Push again and A and B close. Watch RY1 in operation to see how it works. RY1's contacts are rated at 7.5 amps; therefore, connect the two contacts at the lower left in parallel with contacts A and B for heavier loads. Parts layout isn't critical.
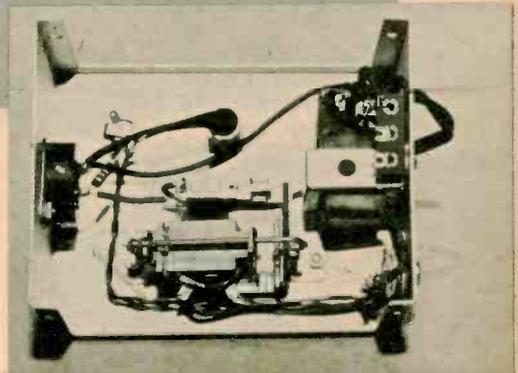
## PARTS LIST

- J1—Phone or phono jack
- NL1—NE-51 or NE-2 neon lamp and holder
- PB1—Normally-open push button switch (see text)
- R1—180,000 ohm,  $\frac{1}{2}$ -watt resistor
- RY1—Impulse relay: 6.3 VAC, DPDT. Potter & Brumfield type PC11A latching
- S1—SPST switch
- SO1—AC chassis receptacle (Amphenol 61-F1)
- T1—Filament transformer: 6.3 V @ 1 A.



applied to SO1.

Neon pilot lamp NL1 indicates that power is applied to SO1 only. It remains on even when S1 is off. Any lamp assembly using an NE-51 or NE-2 can be used. If the assembly contains a current-limiting resistor, omit R1.

When using the AIS with a tape recorder remember that contact need be made only for a brief instant. Therefore, the sensing tape must be short so it coasts on across the contacts after the recorder is shut off. If the foil is too long it will stop on the contacts and apply power to RY1 continuously, causing it to overheat.



To get a tape recorder to turn itself off, make contacts as shown and mount against back of tape. Metallic tape at end energizes relay RY1.

# CONFESSIONS OF AN FCC EXAMINER

**J**UST TO SET the record straight, the letters FCC in that title above don't mean what you think they do. Fact is, there wasn't any Federal Communications Commission until 1934, and the experiences we're about to delve into took place a decade earlier.

In those days, it was the U.S. Dept. of Commerce that looked after the airwaves. But I like to think of myself as an FCC examiner nonetheless—one of those Friendly Patriots of Communication whose job it was to check up on the hams of yesteryear. Care to reminisce?

For several weeks we had been receiving rather consistent complaints of amateur interference with reception in the Buffalo, N.Y., area. Even some bona-fide hams up that way had filed protests with us. They stated that a rather powerful sounding spark was not only breaking up broadcast reception but legitimate amateur operations as well.

Since I drew the assignment to investigate this one, I proceeded to Buffalo in the dead of winter (January) and contacted complainants. Listening for a couple of evenings at both broadcast listeners' homes and at amateur stations, I too heard the mysterious transmissions. There were no call letters or identifying conversation . . . just general ragchew communications.

One of the broadcast listeners possessed a so-called loop receiver—a Murad I think it was—so we decided to see if it could give us any kind of a bearing on the culprit. To some extent, it did. Loop broadcast receivers weren't much for direction finding,

but we pretty well established the general direction the signals were coming from.

Loading the receiver, complete with batteries and loudspeaker, into the car of one of the local hams, we proceeded about a mile in the direction indicated. This done, we set up the equipment on the sidewalk under a corner street light and did some tuning. We apparently were on the right track. The signals were considerably louder, though the direction had shifted some 15 degrees. We were glad to pack the gear in the car again; Buffalo isn't exactly balmy in January at 2 below zero!

We proceeded another mile on the new course and again set up our DF station on a street corner. The signals were much louder and the direction hadn't altered. Evidently the offender was a college student, since much of his conversation had to do with home work involving higher mathematics. But no names were transmitted and there still were no calls. We never did hear the station he was talking to.

The signals were of sufficient strength to lead us to believe that we were pretty close to the source. We decided to load the gear and cruise the streets in the neighborhood while I sat in back listening to the receiver. But this didn't prove too successful; shielding from the car body apparently obstructed most of our direction finding. So we proceeded up one street and down another, peering through the semi-darkness of a moonlit night for signs of ham antenna installations.

Though there were obviously plenty of broadcast-type antennas, there was noth-

By HOWARD S. PYLE, W7OE



A ham since 1908, Howard S. Pyle has spent his entire career in the field of professional radio operating and engineering. World War I saw him as chief radioman in the U.S. Navy. And following that war, he served as assistant U.S. radio inspector in the 8th Radio District. It is his experiences in this post that he brings to life again in this article.

# CONFESSIONS OF AN FCC EXAMINER

ing which appeared to be conventionally ham. We gave up for the night when one of the hams volunteered to take me around for a more intent visual search the following day. This, too, proved unproductive, so we decided to try again that evening. The signals never were on in the daytime.

Returning to the sidewalk site we previously had tried, we set up the gear. Tune as I did, swinging the loop from side-to-side, I heard nary a signal from the suspected station! Working in shifts to try to keep warm, we gave up in favor of hot coffee and warm beds for that night.

The following night also turned out to be a dud. And since I had been away from the office a goodly time, I decided to return to Detroit the next day. Local Buffalo hams and the owner of the loop receiver promised to report the results of other observations which they might make.

In about a week we received a letter from one of the prominent Buffalo hams who had assisted us, advising that the station hadn't been heard for an entire week! Two weeks later we again received a similar letter. Since we had had no indication that the station would be going off the air, we district officers

only could shrug and await developments.

But we never again received a complaint on that particular station. Had he been tipped off that he was under surveillance by someone who had seen our street-corner installations? A number of curious passers-by had stopped, of course. And though we brushed them off with vague explanations, one of them *could* have been friendly ham. . .

One of my routine duties comprised the regular inspection of vessels docking at Detroit. These usually were conducted at intervals of about a week. This way, we caught the Great Lakes cruise ships, those on the Detroit-Cleveland overnight runs, grain carriers and the ore ships of Henry Ford (Detroit to Duluth).

Shortly after I had entered up such inspections, I drove onto the dock of the Detroit-Cleveland Navigation Co. I was in my own little Maxwell roadster, since we had no official Government cars in those days. And I was feeling rather conspicuous, what with my Maxwell painted bright fire-engine red! Since the weather was mild, I had the top folded down.

Suddenly a barrage of small round tin cans fell on me and on the seat! Looking up, I saw several girls in canvas bib aprons, framed in a second-story window, over the covered dock. Lettering on the glass indicated that those loft quarters were occupied by a rub-



Spark gaps and CW ruled the roost decades ago, and radio inspectors relied on an instrument called a decremeter to check up on those sparks. Reason was that a signal which decayed too rapidly when the key was open likely would cause severe interference. Our photo shows students testing out a Kolster decremeter in the laboratory of a Seattle, Wash. radio school back in the early 1920's.

ber products manufacturing company. I assumed that these giggling young women were in its employ.

Ignoring rubber products and the women for the moment, I picked up the little tin containers and boarded the vessel. There the quartermaster met me with a grin and said, "Quite a shower the hussies gave you, eh?" I laughed it off, gave him a couple of the cans and proceeded with my inspection.

The incident was repeated the following week. I was a bit discomfited to receive the horse laugh from several longshoremen and ships' crewmen who apparently had been tipped off by the quartermaster. Several asked me for cans and I told them, "Help yourself; they're all over the car seat!"

My dignity was beginning to suffer. Nevertheless, I was determined to make one more trip before protesting to the rubber company, if it occurred again. Sure enough, the third week brought another hail of cans. Rather than cause a fuss, though, my subsequent trips to the pier found me parked on the opposite side of the building—out of sight and range of the rubber company's windows. I never was so saluted again!

On one major inspection, which included the famous Westinghouse station, KDKA in Pittsburgh, the Inspector-in-Charge of the Detroit district office accompanied me. As KDKA wound up the broadcast stations we

were scheduled to visit, we proceeded to a small western Pennsylvania town, whose name I don't recall.

Reason for our visit was a considerable number of complaints involving violation of quiet hours—a period of the day when all hams were supposed to be off the air. The alleged offenders were a group of amateurs who jointly owned a rather powerful ham station located on a high hill just outside of town.

We checked in with one of the more persistent of the complainants and listened to his broadcast receiver. Sure enough, at about 9:30 p.m., loud signals from an amateur station broke through, though the official silent period would continue in effect for another hour. There was no attempt on the part of the station to withhold call letters. And checking our records, we found that they were bona-fide and listed with correct address. The broadcast listener, who was our host, said that he could take us directly to the station. Seems most of the town was familiar with its isolated location on the hilltop.

Perhaps five minutes' drive brought us to the foot of the hill. My cohort suggested that we leave the car there and proceed by foot to the station which could be seen, brightly lighted, a few hundred yards up the hill. The broadcast listener elected to remain in the car.

As we climbed the slope we could make  
*[Continued on page 109]*

Automation has been around longer than most people realize, at least when it comes to code tests for ham radio applicants. Mounted in a hardwood cabinet in front of each applicant was the famous Omnigraph, a device intended to insure uniform transmission of code characters. Applicants soon dubbed it the infernal machine, since even its presence was unsettling enough, let alone its iron fist.





# GOOD READING

By Tim Cartwright

**SPACE COMMUNICATIONS.** By Stanley Leinwoll. John F. Rider, New York. 166 pages. \$3.95

It'll be a while yet before the first spacecab driver gets his calls over the Citizens Band. It's also going to take a few moons before hams on different planets make contact with one another. These facts notwithstanding, it's certainly not too early for radio hobbyists to make sure they have the ABC's of space communications down pat.

Space listening already is quite a hobby, of course. Both the U.S. and the U.S.S.R. have been sending out a stream of QSL's to verify reception of satellite transmissions. And there's good reason for anyone with reasonable curiosity to keep abreast of what's on the airwaves in the wild blue (or is it transparent?) yonder.

Stanley Leinwoll's book is about as thorough an introduction to the subject as anyone could ask for. Beginning with a short summary of present world communications systems, the author goes on to outline the basics of space communications. This done, he even delves into the whys and wherefores of the various special-purpose communications satellites amateurs have been keeping tabs on. In short, this stacks up as an interesting

and well-written book, with plenty of excellent illustrations.


**ELECTRONIC GADGETS FOR THE CONSTRUCTOR.** By E.N. Bradley. Norman Price, London, England. Distributed by Sim-Tech Book Co., Box 69, Agincourt, Ont. 64 pages. 90 cents.

In case you've been out of touch since that Revolution of a few years ago, it may be interesting to discover a few things about our British cousins. And guess what. They also fool around with breadboards, chassis punches and all that jazz.

The inexpensive little volume we're concerned with here shows precisely what transatlantic tinkerers are up to. And if some of the projects (the theremin, say) are familiar, others—including some mystery display gadgets—will be brand-new and highly interesting. Just substitute tube for valve and ground for earth, and you'll be ready to tackle some worthwhile projects.

Incidentally, if it's not available in your book or parts store, try ordering the book direct from the Canadian distributor. It'll be worth the trouble, and who knows? You even might pick up a few Canadian stamps for your collection.

Though the Mariner II spacecraft was lost in space some 54 million miles from earth, it earlier had passed within 22,000 miles of our sister planet, Venus. And in doing so, it told scientists facts about Venus they could have learned in no other way. Our illustration, taken from the book, *Space Communications*, discussed above, shows how the Mariner was stabilized by radio command from earth at a distance of more than a million miles.

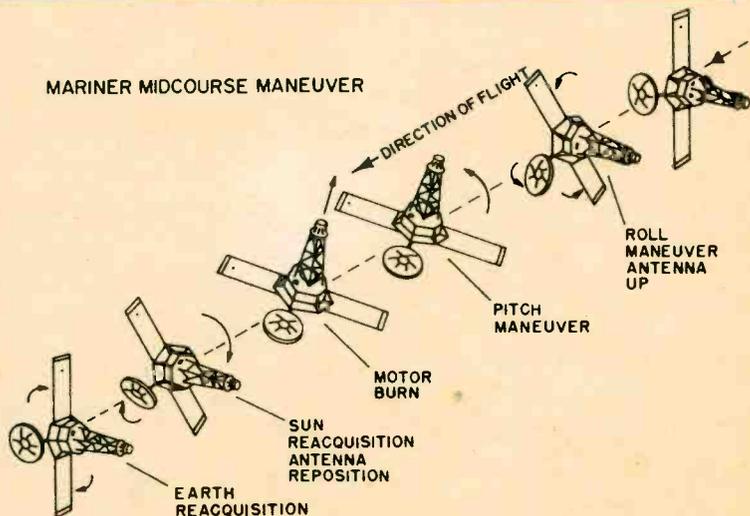



# CB CHANNEL SLICER



CHANNEL 9

By BERT MANN

*Jam-packed channels are wide open when a rig has razor-sharp tuning.*

**W**ITH the new FCC rules crowding all communications between stations of different licenses (or calls) into only seven channels, CBers are likely to find the going rougher than ever. Getting a clear spot on the band will be like looking for a seat on the subway at rush hour.

One of the few good antidotes to the crowding malady will be a receiver with extremely sharp selectivity. Luckily, you don't have to throw out that budget transceiver and then spring for a high-price double-conversion job. Instead, keep the low-cost rig and merely add EI's CB Channel Slicer as an accessory. The Slicer makes adjacent-channel interference a thing of the past, giving you selectivity so sharp that you can separate two stations on the same channel if they are slightly off frequency.

In fact, if you're working a roundtable and everyone isn't in the center of the channel you'll have to trim the tuning each time a different station comes on.

The Slicer is a double-conversion adaptor which adds a 100-kc IF amplifier to transceivers whose IF is around 1,600 kc. The Slicer is not designed for transceivers with a

455-kc IF because the selectivity of these rigs is quite sharp, anyway.

The Slicer has an option. You can either cut a channel in two with 100-kc IF transformers or you can use 262-kc transformers. While not as sharp as 100 kc, selectivity still will be excellent. If an audio-frequency signal generator with a 100-kc output is not available do not use 100-kc transformers; alignment will be almost impossible without a generator. The 262-kc transformers are factory aligned and a reasonably good alignment job can be done by ear. Just adjust T1 as described later on, tune in a station and adjust T2 and T3 for maximum meter indication. Whichever you choose, construction is the same.

Since the 100-kc IF transformers are not stocked by many distributors, you will have to order them directly from Miller. To satisfy Miller's minimum-order requirement it will be necessary to order a complete set of transformers, consisting of oscillator transformer T1 and the two IF transformers, T2 and T3. Further ordering information appears at the end of the Parts List.

Because the power supplies of many trans-

# CB CHANNEL SLICER

ceivers already may be overloaded with accessories, the Slicer has its own power supply—which means its operation is confined to base stations. It can't go mobile.

**Construction.** The Slicer fits easily on a 7x7x2-inch aluminum chassis. Component placement and values are critical so changes and substitutions should not be made.

IF transformers T2 and T3—whether 100 kc or 262 kc—are mounted with the adaptor plate supplied with them. The adaptor hole should be cut with a 1 1/8-inch chassis punch. Take care that you position them exactly as shown: pin 1 is color-coded green.

T2 and T3 are held in place by a U-clip (supplied with them) which fits through the adaptor plate and into the transformer cans. Using your thumb, first press one side of the clip into position and then the other. *Do not* try to force both sides of the clip in place at once. Note that T2 and T3 are *not* connected

Capacitors: 600 V ceramic disc unless otherwise indicated

C1—240 mmf C2—47 mmf

C3—33 mmf (see text)

C4, C5, C11—.005 mmf

C6A, C6B—40/40 mf, 150 V electrolytic

C7—.05 mf, 75 V or higher

C8—.1 mf, 75 V or higher

C9—20 mf, 150 V electrolytic

C10—.1 mf

D1—1N34A diode

F1—1/2 A fuse and holder

J1, J2—phono jack

P1—6-V pilot lamp and holder

Resistors: 1/2-watt, 10%

## PARTS LIST

R1—1 megohm

R2, R6—22,000 ohms

R3—470 ohms R4—100 ohms

R5—2.2 megohms

R7—1,000 ohms

S1—SPST toggle switch

SR1, SR2—Silicon diode: 50 ma, 500 PIV minimum ratings

\*T1—540-1,600 kc miniature adjustable oscillator coil (Miller 70-OSC.)

\*T2—IF transformer: 100 kc, Miller No. 1710; 262 kc, Miller No. 12H-1


\*T3—IF transformer: 100 kc, Miller No. 1710; 262 kc, Miller No. 12H-2

T4—Power transformer: 250 V center tapped @ 25 ma; 6.3 V @ 1 A (Stancor PS-8416 or equiv.)

V1—6BE6 tube V2—6BJ6 tube

\*Available as a group only from J. W. Miller Co., 5917 S. Main St., Los Angeles, Calif. 90003. 1—No. 70-OSC and 2—No. 1710, \$5.34 plus postage. 1—No. 70-OSC, 1—No. 12H-1 and 1—No. 12H-2, \$4.62 plus postage.

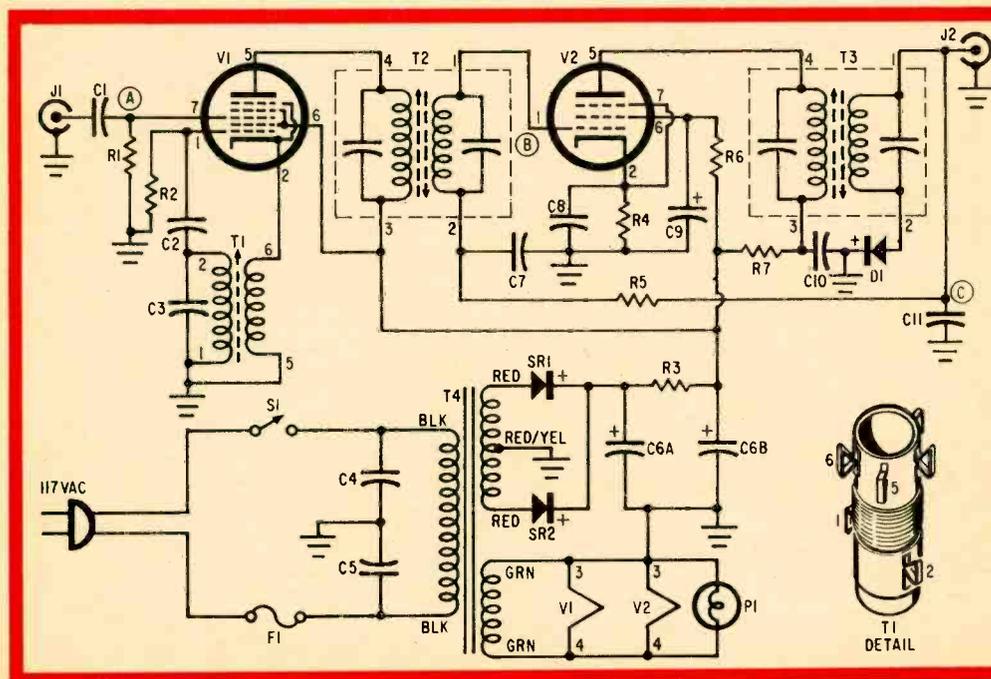Output (1,600 kc) of CB rig's IF strip is fed to pentagrid converter V1. Output of V1 (100 kc or 262 kc depending on the value of C3) then goes to IF stage (100 kc or 262 kc) consisting of T2, V2 and T3. Circled letters are test and alignment points and are referred to in text. Watch the lug numbers on T1.



as specified in the instruction sheet supplied with them; use our connections.

Take extreme care when connecting oscillator transformer T1 since the Slicer will not work if just one set of leads to T1 is reversed. If you employ 262-kc IF transformers, use a 24 mmf capacitor for C3. [C3 in any case should be an NPO disc or tubular ceramic.]

**Connecting the Channel Slicer.** The Slicer is connected between the transceiver's last IF transformer and the detector circuit. The modification to the CB rig is shown in the schematic directly below. To facilitate future transceiver servicing, connections for the Slicer should be brought to phono jacks on the transceiver's rear apron.

The IF transformer lug to which a diode (semiconductor or tube element) is now connected, is connected to the Slicer's input (J1). Next, unsolder the components from the IF transformer lug that feeds the AVC/audio line. Twist the leads together and connect them to the Slicer's output (J2). Then ground the IF transformer terminal which fed the AVC/audio line.

The connecting cables between the transceiver and Slicer should be made with short lengths of RG58/U coaxial cable.

**Alignment.** In order to align the IF trans-

formers you must use the proper alignment tool. Attempts to use a screwdriver will damage the transformers. The 100-kc transformers require a hexagonal alignment tool whose parallel sides are 1/8-inch apart. The 262-kc transformers require a K-Tran alignment tool.

Temporarily disconnect the cable to the Slicer's input (J1). Connect a VTVM set to about -15 VDC to point C (C11) and connect an audio-frequency generator set to 100 kc to point B (pin 1 of V2). If you are using 262-kc transformers use an RF signal generator set to 262 kc.


Adjust the generator's output for the lowest readable meter indication; if necessary, switch to a lower meter range. Turn T3's bottom slug full counterclockwise. Then slowly turn the slug clockwise until the meter peaks. There will be two peaks but the correct one is with the slug nearest full counterclockwise. Align T3's top slug the same way. Then repeat the procedure. As you adjust the slugs the meter may go off scale. Rather than change the meter's setting, reduce the generator's output. Connect the signal generator output to point A (pin 7 of V1) and repeat the procedure on T2.

Now connect an RF signal generator set to the transceiver's IF frequency to J1. Adjust T1's slug—starting from full counterclockwise—for maximum meter indication. Disconnect the generator and connect the transceiver's output cable to J1.


Tune in a station on, let's say, channel 10 to check dial calibration. If the calibration is off, turn the tuning knob so the channel 10 dial marking is directly under the pointer. Now adjust T1 so you receive channel 10 right on the nose. This will be the point of highest meter indication.

Finally, tune in a strong station and adjust the transceiver's last IF transformer for a maximum meter indication. Disconnect the VTVM and the Channel Slicer is ready to go.

Just so you don't think that something's wrong we'd better warn you of what reception will sound like with the Slicer. The volume will be about that of an unmodified transceiver but everything will sound unusually quiet. This is normal. The less IF bandwidth, the less noise. With 100-kc transformers tuning will be razor sharp. In fact, if you're tuned to the center of the channel and someone comes in 3 kc off frequency, it's quite likely you won't hear him. With 100-kc

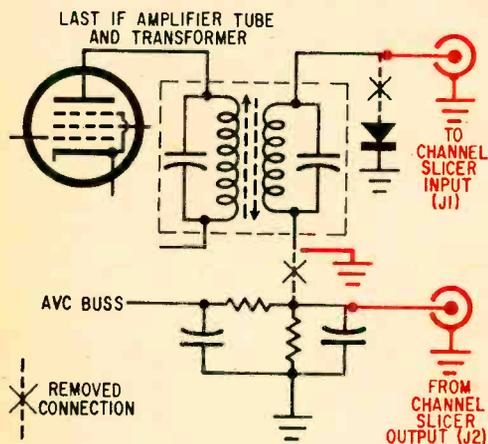

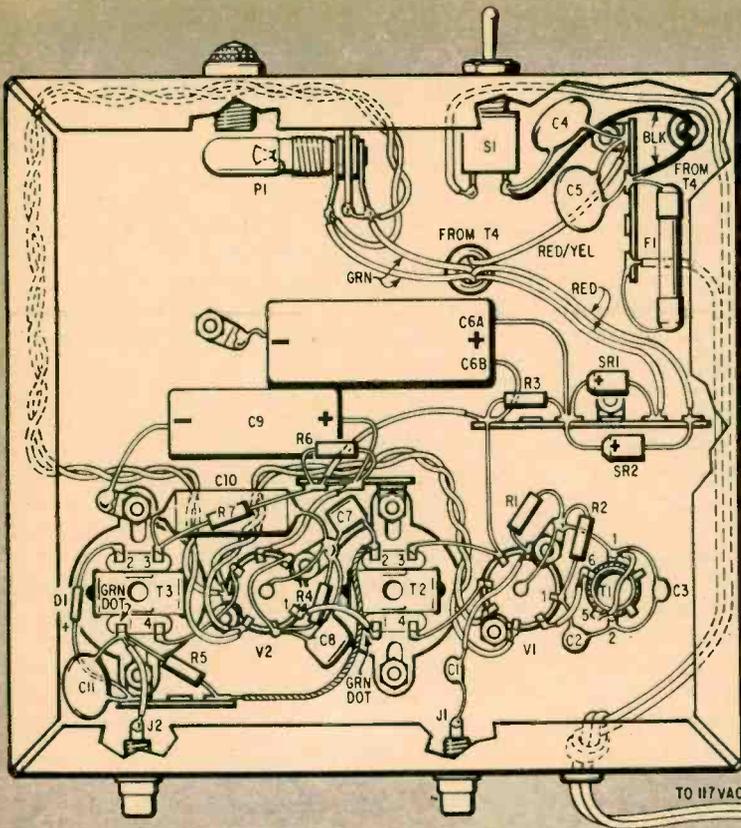Modification of CB rig. Disconnect top lead of secondary of last IF transformer and connect to phono jack on the rear of chassis. Disconnect bottom secondary lead and ground it; run all AVC line leads to secondary to another jack installed on rear of transceiver chassis.




Because of the frequency at which the Channel Slicer operates, layout is important. Duplicate the arrangement shown here and you won't run into trouble later on. Install capacitor C3 on oscillator transformer T1 before you mount the transformer. Center lug on PI's socket is frame and is grounded. If your socket doesn't have such a lug, ground one of the filament leads to the socket's frame. Use heat sinks on D1's leads when soldering in place.

## CB CHANNEL SLICER

transformers, and to a lesser degree with 262-kc transformers, speech will sound somewhat muffled. This also is normal.

**Service Hints.** If T2 and T3 can be aligned but the IF signal cannot be pushed through the Slicer, the oscillator may be inoperative. Check this with the VTVM connected to pin 1 of V1. If the oscillator is working you will get an indication in excess of -10 VDC. If you fail to get the correct indication, check to see if a pair of T1's leads is reversed.

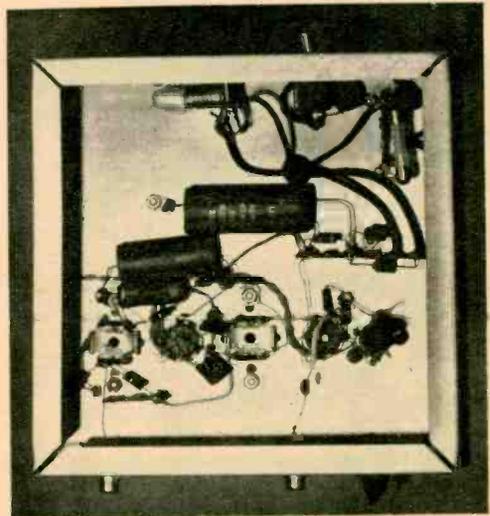If the Slicer is working—as evidenced by your ability to align it and feed a signal through—but won't work when connected to the transceiver, either T1 is adjusted incorrectly or the connections to the transceiver's last IF transformer are incorrect. ⚡



Chassis is wide open; therefore, you shouldn't have difficulty getting everything in place. Long leads will cause trouble, so keep them short.

# THAT HAM RADIO BRAWL

Three fight camps develop in the ham world and barbs & brickbats fill the air as they battle over personalities, publications . . . even an issue or two.

By NICHOLAS ROSA, WB6JTJ/W1BPQ

**R**OT . . . crud . . . vulgar . . . dope . . . slur . . .

With words like that flying about, where would you expect to be? In a pier brawl? At a beer bust for ex-cons? You certainly wouldn't be likely to hear the likes in the staid and sometimes stuffy world of amateur radio. After all, Golden Rule No. 1 in The Amateur's Code says, *The Amateur Is Gentlemanly*.

But those exact words and others of the same breed are, indeed, peppering the ham landscape these days. They're the ammunition in a donnybrook that has shaken amateur ranks from antenna to ground. Conservative brass-pounders and mike-grippers are by turns awed, surprised, shocked . . . and entertained. Clearly, the free-for-all is one of the more remarkable events for hams since they all got kicked off the air in World War I.

Involved in the brawl are personalities, publications and even an issue or two. There are three fight camps, though, in the manner of pugilistic heavyweights, each has friends, diehard supporters, hangers-on and camp followers. In the corners of this fire-and-brimstone triangle can be found:

The Connecticut-based American Radio Relay League; its publication, QST, and John Huntoon, W1LVQ, ARRL general manager and editor of the publication.

The Cowan Publishing Corp. of New York and its ham magazine, CQ.

Wayne Green, W2NSD/1, who edits and publishes an all-ham journal called 73 out of Peterborough, N. H.

All principals have bearded each other to a greater or lesser degree in the past several months, though Green has been by far the most active whisker-puller. W2NSD put together the slogan, Never Say Die, to fit his call letters, and he's gone to great lengths to follow the motto.

The New Hampshireite possess the fastest

typewriter in the East and has become the maverick of ham radio, kicking sacred cows in the stomach and stomping on toes all over the place. His penchant for controversy and far-out ideas has made him easily the most colorful editor in the field, and also the most-talked-about spokesman for the hobby.

Green was not always at outs with one of the principal targets for his barbs—CQ Magazine. In fact, he was once its editor, and during a span of a few years he fairly set its pages ablaze. Then he disappeared from the Cowan fold in a row that—contrary to usual practice in the business world—got a full public airing from both parties. If there was




Ironical cover for CQ of January 1953 pictures Wayne Green (arrow) with celebrities; he and the magazine are now two principals in big brawl.

© 1953 by Cowan Publishing Corp.

a single starting point for the brawl now raging, that unquiet break-up probably was it.

After he resigned or was fired (depending on which version you preferred) Green was not without a voice for long. A few months later he began publication of a new ham magazine called 73 (Best Regards, in ham parlance). The publication first saw life in Brooklyn, was later moved to the New Hampshire hills. "We are not mad at anybody," Green announced, and then let fly. Some of his barbs were good natured but, nevertheless, few in his audience could mistake his targets. Green's way with controversy and his method of combining humor with acid made his followers laugh while they gaped at the holes he burned in his victims.

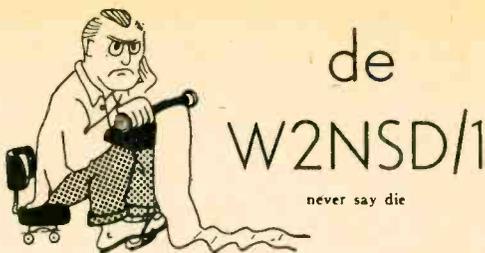Green next proved himself to be a veritable dynamo, stumping up and down the countryside and attending almost all conventions and hamfests. His magazine would revolutionize the ham world, he said. He won many followers. Meanwhile, he was busy with his broadsides at the other two ham camps, Cowan Publishing and the ARRL. Paper that went into his typewriter came out smelling



Most of Green's attacks on adversaries appear in his personal column, which carries the heading shown here; column is a mixture of humor and acid.

of fire.

Green had other ways of giving chuckles to his readers. His original cover price was 37¢, reversing the numerals in the title, and later he was not content with merely listing his new price. "A Steal at 40¢," he put on the cover, and, "a miniscule 40¢." Inside there were other yuks. In tiny type at the bottom of the indicia was this advice: "Readers should stop reading the fine print and stick to the articles and editorial." Through several issues Green's name got turned into Wayne Grein, Wayne Grn and Wain Green, who was listed simply as "Editor, etcetera."


Noses were tweaked all around when 73 vented irritation at the multiplicity and lack of originality in ham awards by announcing its own series of certificates. The big one was the Certificate Haters Club certificate (which sounded strangely like CQ's Certificate *Hunters Club*). Other awards included the WAAS (Worked *Almost All States*) and the Real Rag Chewers certificate, which could be won only if you conducted communications with another ham for six solid hours with no breaks.

During all this, and much more, both the ARRL and Cowan Publishing maintained a stony silence, even when 73 talked blithely about how much it offered in comparison to Brand X and Brand Y and when Green referred to one of his competitors as that "near-bankrupt" ham magazine. A little later, 73 came out with a cover that bore a striking resemblance to QST's long-standing format, though the famed QST line, "devoted entirely to amateur radio," now read, "devoted wholeheartedly to amateur radio."

The sniping went on several months before there was return fire from the other two garisons. It was not until somewhat over a year ago that pot shots became a real battle. The



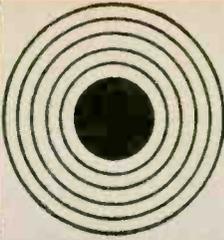John Huntoon, W1LVO, as general manager of the ARRL and editor of its publication, has caught many barbs resulting from controversial proposal.



# ZERO BIAS

**A**LAS—our noble vice-presidential candidate from New Hampshire has done it again—stuck his big foot in his very big mouth, that is. Although his April editorial quietly backed off on his March innuendos, in May he was back at it insisting that 73 contains: “a lot more flagrant information than flagrant misinformation.”

We were almost in hysterics, when directly under this memorable quote we noted that *Auto-Call* (a very fine Washington, D.C. club paper, edited by W3NL): “devoted considerable space to my editorial. . . .” Dear readers, *Auto-* they tore him up in

and we vaguely remember Mr. Huntoon’s salary as being considerably less than \$25,000. We hope 73’s comments won’t cause Mr. Huntoon any undue hardship with the Bureau of Internal Revenue. By the way—couldn’t 73 and the “Institute” operate more effectively as a two-man team?

73’s editor has, in past issues spoken of the abundance of his rejected manuscripts showing up in *CQ*. It is rather ironic that an article prepared for *CQ* has now shown up in 73. *CQ* required that this article, written by one of his “Institute” Directors, be held over a while to correct some of the inaccuracies contained therein. Impatient for

Cowan Publishing’s main blast in ham war appeared in Zero Bias editorial column in *CQ* magazine.

immediate cause for the turn in events was supplied by the ARRL itself which, early in 1963, announced that it was submitting a rules-changing proposal to the Federal Communications Commission. The document dealt with incentive licensing and became known as RM-499 after its FCC file number.

The proposal posed a threat to 200,000 of

the country’s 280,000 licensed amateurs, suggesting that all General and Conditional class operators be barred after certain dates from transmitting phone (voice) signals on the four most popular bands—80, 40, 20 and 15 meters. Phone privileges would be restricted to Advanced and Extra class licensees—now a minority. Others would be per-

*[Continued on next page]*



Wayne Green’s spoof (right) of long-standing QST format (left) got a lot of chuckles from the amateurs.

© 1958 by The American Radio Relay League, Inc. (left)  
© 1963 by 73, Inc. (right)

## THAT HAM RADIO BRAWL

mitted CW (code) only.

The idea was to improve the quality of hams and hamming, giving them an incentive to improve themselves by trying for higher licenses. RM-499 itself became highly controversial amongst hams, many of whom were enraged at the idea of anyone's taking away operating privileges which they had enjoyed for years.

The ARRL, unfortunately for itself, filed the proposal before revealing the details to its 80,000 members. As a democratic, non-profit association, it immediately came in for attack for not representing the views of its members. Green's typewriter roared into action, turning out sizzling lines that called upon amateurs to revolt, to protest not only to the ARRL but to the FCC. He raged about the proposal and the manner in which the action had been taken, arguing that ARRL members had not been consulted and, worse yet, that the board of directors of the League had not been queried in any meaningful way. The individual who bore the brunt of the attack was the League's top professional hand, John Huntoon. Salvo after salvo crashed around him; he ignored them all.

Cowan Publishing also remained aloof—for a while. Then it surprisingly condemned the ARRL's handling of RM-499 as "deceptive" and "secretive" and "cowardly." For a moment it appeared that bad blood might be purifying itself, what with the two rivals now on the same side of the fence. But not for long. Cowan soon ran alarmed editorials about Green and threw its support to the ARRL.

The League was in an embarrassing spot. Inherently too dignified and high-thinking to engage in Indian-style warfare, it obviously looked for a safe path. QST kept all references to W2NSD, even indirect, out of its editorial material (though its letters column carried mention of him).

The Green drumfire at length became too much, though a camp-to-camp battle between QST and 73 never came about. Instead, letters from Huntoon were sent out to all ARRL-affiliated local ham clubs to set matters straight according to the League's point of view.

Green's reaction could have been predicted. Far from ignoring the letters, he pounced on them with seeming glee, dubbed

them Huntoon's Dirty Letters and invited his audience to go ahead and read them.

In the midst of the battle, verbal broadsides streaked across the sky like sparks in a blacksmith shop.

Charges of impropriety were hurled at certain officials of the FCC, which could be extremely serious to a government worker. The accusations never were proved.

Other shots ricocheted off such surprising targets as the Coca-Cola Corp. and the New York World's Fair, which got involved after visiting hams had trouble finding K2US, the ARRL's official station at the fair. The station was tucked away on the second floor of the Coke building and, after getting there, quite a few amateurs were disgruntled when they were not permitted to operate the equipment because they hadn't brought licenses along (as the law requires).

With the glare of rockets on the horizon, Green confounded everybody by organizing his own version of an amateur association, calling it the Institute of Amateur Radio (IoAR). The whole thing, said CQ, was meant merely to keep the 73 camp "in New Hampshire clover."

Though the IoAR to date has been noted mostly in its role of thorn in the side of the ARRL, the organization has a chance to contribute something new to the ham world. The ARRL, being a tax-free fraternal group, cannot indulge in anything that smacks of political activity, such as lobbying in Washington. The IoAR, on the other hand, works under no such restriction and is able to lobby for the benefit of the amateur hobby.

Through the whole fight, Green has shown himself to have the most lasting supply of ammunition. At one moment he lightheartedly discussed Huntoon's travel expenses, at the next he called the election of Herbert Hoover, Jr., W6ZH, as ARRL president a mistake. And whenever a Cowan Publishing head popped up, he had a brick handy.


Green, years before, had done a piece called ARRL Exposed, a tongue-in-cheek article which delighted many readers but enraged as many, and posed all the while as a friend of the League. The pattern was repeated this time. While damning the ARRL, the New Hampshire editor talked about how much the League had done for hamming and about its many valuable contributions. With friends like that, the League might have

*[Continued on page 112]*

# CHRISTMAS GIFT


Write the names of your electronics-minded friends on our card and drop it in the mail. You'll be giving them a gift they're sure to enjoy. Our special Christmas Gift rates save you money, so don't forget a subscription for yourself, too! Just before Christmas every person on your list will receive an attractive Gift Announcement Card in your name. We'll bill you later. Do your Christmas shopping easily and early — right now!

Special Christmas Gift Rates	
First 1-year gift .....	\$2.00
Each add'l 1-year gift .....	\$1.50
Special 2-year gift .....	\$3.00
In U.S., possessions & Canada	

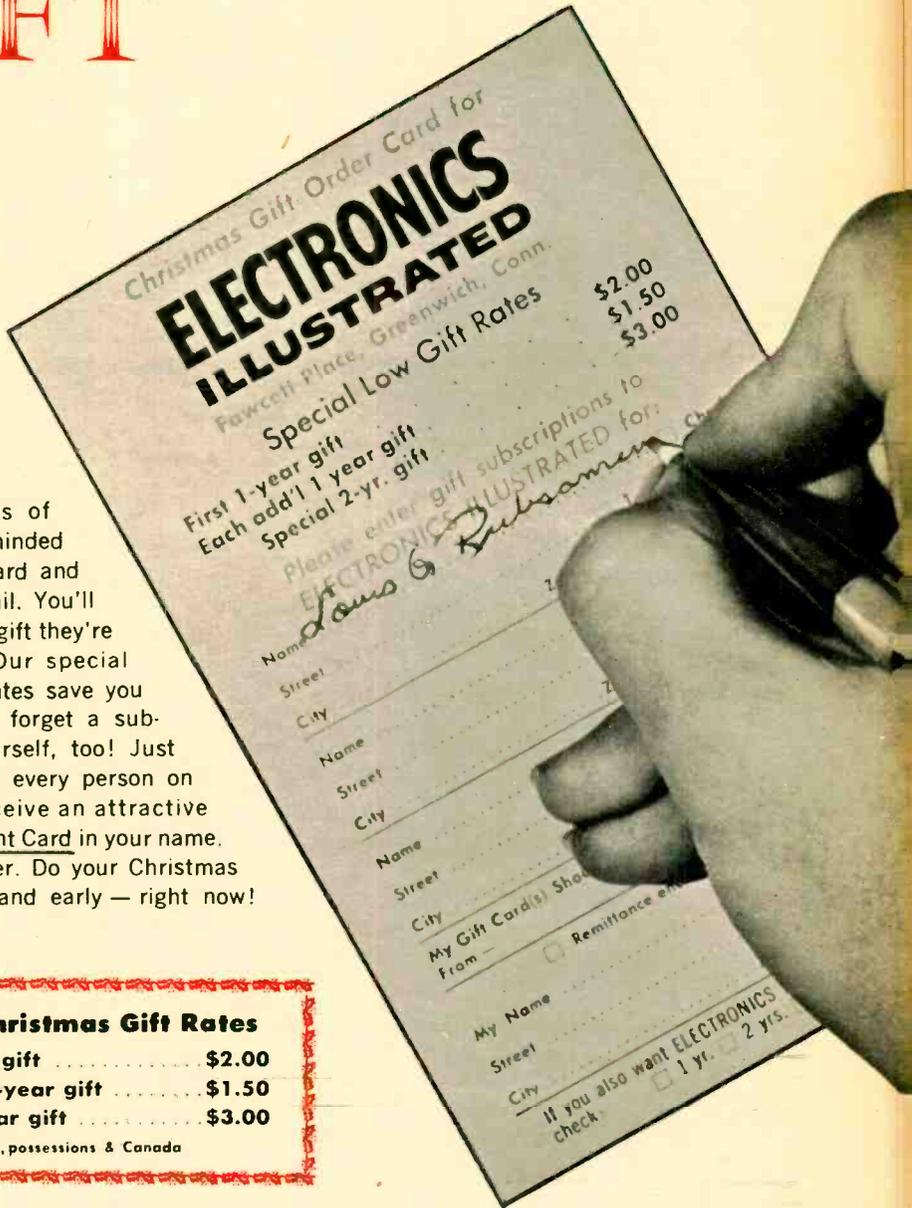

*Merry Christmas!*

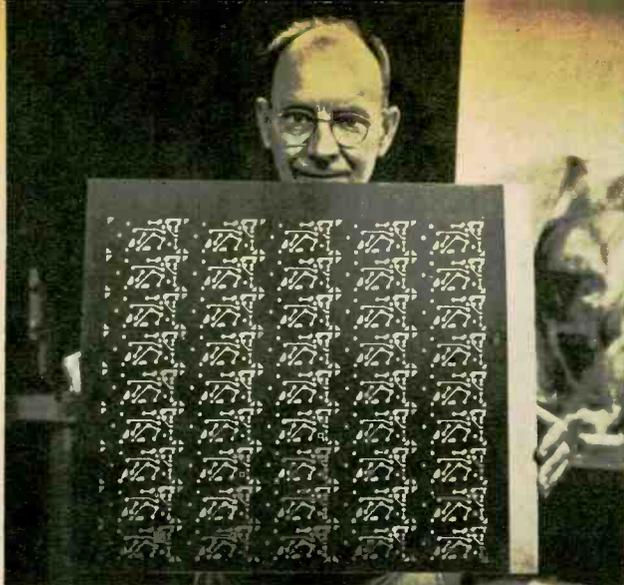ELECTRONICS ILLUSTRATED • FAWCETT PLACE • GREENWICH, CONN. 06830



Printed circuits form heart of rig. This board will be cut to furnish 45 of them.



Individual boards cut from phenolic sheet at left must be drilled to accept leads from components. Executive's three boards require about 450 holes.

## BEHIND THE SCENES IN CB

**H**EROES, as the cartoon strip once put it, are made—not born. Same thing goes for CB sets, though we suspect a good many Cbers never give much thought to the matter. For a look behind the CB scenes, EI takes you on a tour through the International Crystal Mfg. Co.'s plant in Oklahoma City, Okla. The unit in production is International Crystal's Executive transceiver.

After dip soldering, boards lack only tubes to make them complete. Worker inserts tubes, then sends boards to another worker who individually inspects and tests each one.



With components mounted in place, board is coated with flux, dipped in molten solder.





Aging completed, units are aligned with crystal-controlled frequency standard specifically designed for CB rigs.





Finished Executive transceiver now can be put into operation on any of CE's 23 channels.



Rig takes shape as printed circuits, power supply, etc., are combined.

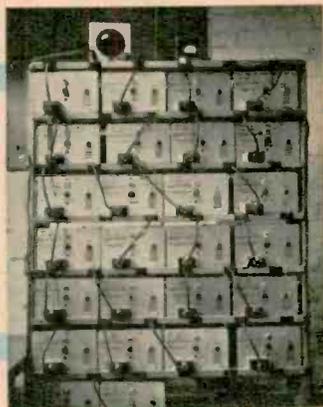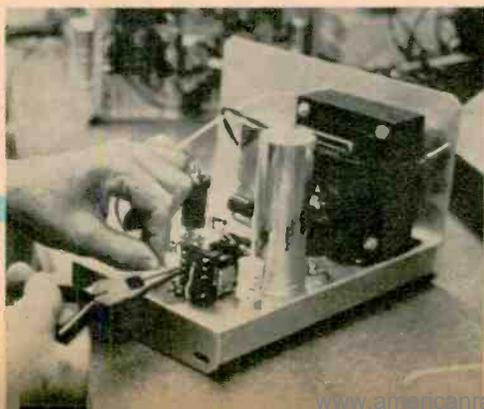Transmitter and power-supply sections are wired in conventional manner as separate assembly.



Following assembly, completed transceivers are placed in aging rack. Each unit remains in rack for 24 hours before undergoing final adjustments and operating tests.



Preliminary test of transmitter and power supply insures this section of rig works properly.

# Look what's happened to

# HOME-STUDY

By J. K. LOCKE

*Different? Sure. Better? Could be. Want to know more? Then read on.*

**L**ESS THAN TWO decades ago, many schools offering courses in home-study electronics were set up primarily to turn out radio repairmen. But that was yesteryear. Today, electronics is claiming an ever more important role in business, industry, defense, space and entertainment. And, not surprisingly, schools and institutes are reflecting this growth in more ways than one.

If you doubt it, send for a few catalogs and take a long look. They're literally sprouting with spanking new courses in advanced new subjects. What's more, new teaching methods are being introduced, and advanced training aids are helping students learn more easily and quickly.

Most striking innovation at most schools are the new courses. As an example, take the latest additions to the curriculum at Cleveland Institute of Electronics. The Industrial Electronics and Automation course offered by this school includes instruction in such advanced areas as magnetic amplifiers, digital and analog computers, servomechanisms, ultrasonics, radiation inspection and detection, solar cells and counter tubes.

Go back a few years and you'd find these gadgets and many other such sophisticated devices were still laboratory toys. Today, they're in operation in factories, in offices, even in space. And, this being the case, technicians who install and maintain them need training in these and other far-out fields.

One of the most encouraging trends in home-study electronics is the way courses are keeping pace with changes in the field itself. The nation's study-at-home institutes

constantly are adding new courses of instruction as the need arises. International Correspondence Schools of Scranton, Pa., for example, recently introduced eleven new courses in electronics. Among them were courses in telemetry, computers, high-fidelity sound systems, communications technology and industrial electronics engineering.

Similarly, DeVry Technical Institute of Chicago now provides a course in space and missile electronics; Central Technical Institute of Kansas City, Mo., will teach you about nuclear power; and Capitol Radio Engineering Institute of Washington, D.C., lists a special course in electronics for graduate engineers whose basic college work was in other fields. Needless to say, these are but random samples of the kinds of courses now yours for the taking.

**While a wide** variety of new home-study subjects is being taught, the bulk of courses offered by the schools still concern the fundamentals of electronics theory and practice. Dramatic new developments haven't repealed Ohm's law, and even space-age electronics experts still have to know how to use it. But the old courses are taking on a new look in some schools. Principal new twist given to fundamentals these days comes in the area of improved teaching methods.

Education experts in recent years have been revising some of their theories about how people learn. The most dramatic result of this work to date is the concept of programmed learning.

Basic principle behind this relatively new idea is that people learn better when they



# ELECTRONICS!

participate actively in the learning process. In other words, good learning is a two-way street. One simple step in this direction consists of nothing more magical than having students constantly answer questions and find out immediately whether their answers are right or wrong. Thing is, if the answers are wrong, students must stop then and there to find out what it is they don't understand.

One major proponent of the programmed learning concept is RCA Institutes. For the past year, this organization has offered its basic electronics course in programmed form.

RCA got into the programmed learning business a few years ago when the company was looking for a way to train technicians for its own computer-maintenance division. Company training experts worked out a programmed course. The programmed sequence—which RCA calls the Autotext—worked well.

Matter of fact, it worked so well that Harold Metz, vice-president in charge of RCA educational services, got the psychologists and educators who had developed the program together with officials of RCA Institutes. The combined team soon worked out a programmed course in elementary electronics to be offered to home-study students of the school.

Results to date have been impressive. For over a year now, students have been offered the introductory electronics course in either Autotext or conventional form. At the end of the course, they are given the same examination. Grades of Autotext students have averaged 10 to 15 per cent higher than those who learned the same material the conven-

tional way. Fact is, school officials are considering eventual withdrawal of the standard course. And RCA soon may offer other courses in Autotext form.

Some other institutions also are starting to use the programmed learning technique. International Correspondence Schools, for example, offers some programmed courses. And other schools are either instituting or considering similar moves.

**Third major area** of innovation in today's home-study schools stems from what might be called better teaching aids. On the one hand, those who study at home never can have the opportunity to work on the great variety of complex and expensive equipment available to students who attend residence schools. Even so, lab experiments are an important part of most home-study programs. Schools provide kits of parts so students can perform experiments and get used to handling electronic equipment.

Main trouble with many experimental circuits designed for home use is that they take a long time to set up and tear down. The student spends much too much time getting ready for the experiment. Relatively few minutes actually go into finding out what makes resistors work—let alone capacitors, inductors, tubes, transistors and the circuits they make possible.

Several companies have developed clever devices to cut down on building time and allow students to concentrate on the learning part of the experiment. The modular panels and connectors now used by DeVry Technical Institute, for example, allow rapid construction. Students can jam the connectors

## Look what's happened to HOME-STUDY ELECTRONICS!

into the holes anywhere on the board as dictated by the layout of the circuit. This done, they can wire the circuit simply by shoving component leads into the holes in the connectors. No soldering is necessary, and parts can be used again and again.

An even easier and faster circuit-building device is incorporated in the RCA Transistor Trainer. Designed for use along with RCA Institutes' basic course in transistors, the trainer is an optional aid which rents for \$15 a month. Though a student can master the material in the course without it, he'll probably have a better grasp of transistor operation if he performs the experiments and observes first-hand what happens under varying conditions.

Looking over home-study electronics in general, you might say things never have stood better than they do today. New courses, new teaching methods and new equipment all number among the many innovations introduced by today's electronics home-study schools in their effort to stay abreast of the industry. As a result, students trained by today's institutes are well prepared for a rewarding career in the fast-moving field of electronics.


Also very much in the picture today are all the traditional benefits of home study. You undertake a home-study course on your own,

and it is on your own that you complete it. For these reasons, anyone who studies at home must possess plenty of initiative and perseverance if he is to profit at all. And these same qualities also can spell success in most any field of endeavor.

A student simply must exercise initiative if he is to complete successfully a home-study course. This being the case, you might say the very nature of home study tends to develop your ability to analyze and depend on yourself. It can and should turn you into a self-starter. And the sort of intense personal application home study demands means that no one who satisfactorily completes a home-study course need have much worry about his own sense of initiative.

For a good sampling of schools offering courses in home-study electronics, scan through our list at right. This done, you might write the National Home Study Council, 1601 Eighteenth St., N.W., Washington, D.C. 20009, and ask for the Directory of Accredited Private Home Study Schools. It not only lists more than 60 of the nation's top home-study institutions, but also has a keyed alphabetical listing of courses. This way, you can find all schools that offer any selected course.

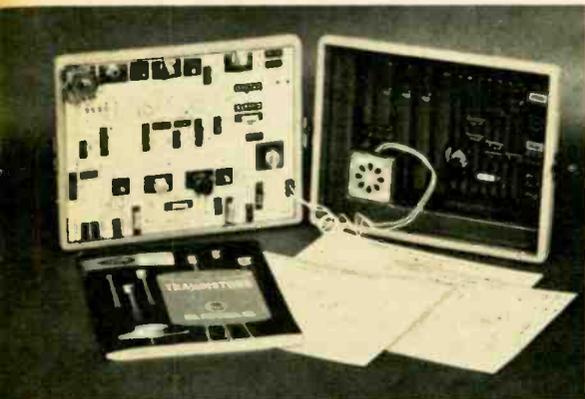And before you make up your mind as to which school you'll call on to help you learn electronics, look up the course you're interested in. Then write all schools offering that course, and ask for more detailed information. From there on in, the road to electronics learning is yours.



Transistor Trainer by RCA Institutes contains twelve separate templates, sets up in minutes.



Circuit board from ICS is ideal for experiments. Parts are clipped rather than soldered in place.

## MAJOR SCHOOLS OFFERING COURSES IN HOME-STUDY ELECTRONICS

**AMERICAN INSTITUTE OF ENGINEERING  
AND TECHNOLOGY**  
1135 W. Fullerton Ave.  
Chicago, Ill. 60614

**AMERICAN SCHOOL**  
Drexel Ave. at 58th St.  
Chicago, Ill. 60636

**AMERICAN SCHOOL OF HOME STUDIES**  
127 Columbus St.  
New York, N.Y. 10023

**AMERICAN TECHNICAL SOCIETY**  
850 E. 58th St.  
Chicago, Ill. 60637

**BUSINESS ELECTRONICS**  
209 W. Jackson Blvd.  
Chicago, Ill. 60606

**CALIFORNIA ELECTRONICS & TV INSTITUTE**  
945 Venice Blvd.  
Los Angeles, Calif. 90015

**CANADIAN INSTITUTE OF SCIENCE  
AND TECHNOLOGY**  
617 Garden City Bldg.  
263 Adelaide St., W.  
Toronto 1, Ont.

**CAPITOL RADIO ENGINEERING INSTITUTE**  
3224 Sixteenth St., N.W.  
Washington, D.C. 20010

**CENTRAL TECHNICAL INSTITUTE**  
1644 Wyandotte St.  
Kansas City, Mo. 64108

**CHRISTY TRADES SCHOOL**  
3214 W. Lawrence Ave.  
Chicago, Ill. 60625

**CLEVELAND INSTITUTE OF ELECTRONICS**  
1776 E. 17th St.  
Cleveland, Ohio 44114

**COMMERCIAL TRADES INSTITUTE**  
1400 W. Greenleaf Ave.  
Chicago, Ill. 60626

**COYNE ELECTRICAL SCHOOL**  
1501 W. Congress Pkwy.  
Chicago, Ill. 60607

**DEVRY TECHNICAL INSTITUTE**  
4141 Belmont Ave.  
Chicago, Ill. 60641

**DEVRY TECHNICAL INSTITUTE OF CANADA**  
970 Lawrence Ave., W.  
Toronto 19, Ont.

**GRANTHAM SCHOOL OF ELECTRONICS**  
1505 N. Western Ave.  
Hollywood, Calif. 90027

**INDIANA HOME STUDY INSTITUTE**  
Eastern Division  
Box 282  
Saxonville, Mass. 01256

**INDUSTRIAL TRAINING INSTITUTE**  
2150 Lawrence Ave.  
Chicago, Ill. 60625

**INTERNATIONAL CORRESPONDENCE  
SCHOOLS**  
Scranton, Pa. 18515

**MASSEY TECHNICAL INSTITUTE**  
148 E. 7th St.  
Jacksonville, Fla. 32206

**NATIONAL ELECTRONIC & TELEVISION  
SCHOOL**  
1298 Niagara St.  
Buffalo, N. Y. 14213

**NATIONAL RADIO INSTITUTE**  
3939 Wisconsin Ave., N.W.  
Washington, D.C. 20016

**NATIONAL TECHNICAL SCHOOLS**  
400 S. Figueroa St.  
Los Angeles, Calif. 90037

**NORTHWEST SCHOOLS**  
1221 N.W. 21st Ave.  
Portland, Ore. 97209

**PHILCO TECHNOLOGICAL CENTER**  
C & Ontario Sts.  
Philadelphia, Pa. 19134

**RADIO TELEVISION TRAINING OF AMERICA**  
52 E. 19th St.  
New York, N.Y. 10003

**RCA INSTITUTES**  
350 W. 4th St.  
New York, N.Y. 10014

# Souped-Up Phone Tap

**E**ASIEST way to tap your phone (*that's legal*) to record a message or for group listening through an amplifier is with an induction pickup coil. One commercially available type is a thin rectangle and fits under the telephone base. But it's hard to find the best coupling position. Cylindrical coils with a suction cup have somewhat better pickup than the flat-coil bit they're clumsy and often fall off the handset. Both types are high impedance (1,000 ohms) and are designed to work with tube or transistor amplifiers.

Our souped-up phone tap can be made for half the cost of other coils and, because it has a larger coupling area, it is about twice as sensitive. And its lower impedance (100 ohms) is a better match for transistor-amplifier inputs.

The rubber cap in which our coil is installed (see top photo) is called a Tele-Muff and is available for about 25¢ in stationery and office-supply stores. It holds the coil in perfect position over the handset earpiece and affords ear comfort.

The best form on which to wind the coil is the hub of a 50-foot 8mm movie film reel or a 3-inch tape recorder reel (modified, see second photo). If neither of these is available, wind the 1,000-turn coil (No. 34 enameled wire) on a 1¼-inch-diameter form between cardboard flanges spaced 3/16 inch apart. A quarter-pound spool of No. 34 wire has about 2,000 feet—enough for four pickup coils.

After the coil is wound, remove it from the form and wrap it tightly with masking tape. Neatness isn't terribly important but don't scrape any enamel insulation off the wires or you will short out some of the turns. Connect the coil leads to a length of shielded microphone wire.


Cut two 2¼-inch discs from cardboard and punch about six holes near the center of each (see top and bottom photos). Sandwich and glue the taped coil between the two discs. Then punch a small hole near the front of the Tele-Muff for the cable. Pull the cable through and push the coil/cardboard sandwich all the way into the Tele-Muff. Install a plug on the other end of the wire and you're ready to go.—Gregg Bruce, Jr.



Remove flange from 8mm film reel, slip on cardboard disc 3/16 inch from other flange, then wind 1,000 turns.



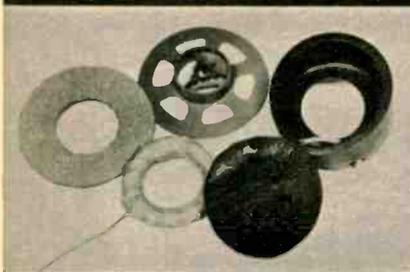After removing cardboard disc from reel hub, pull off coil, compress turns and wrap tightly with tape.



Movie-film reel with flange removed; cardboard-disc spacer and coil are at left. Finished tap is at right.

# Notes from EI's DX CLUB

**W**ORLD'S FIRST two-headed radio rebel might be one way of looking at that station once called Teje Iran. These days it IDs simply as Peke Iran. And, once its Persian tirade is finished (around 1300 EST), it turns its 11695-kc transmitter over to an Iraqi Communist organization. This group goes at it in Arabic for the next half hour in first-class rat-tat fashion. All this hardly makes for interesting listening, of course, but it *is* programming with a twist.

Speaking of twists, a DXer in New York City sports a curved QSL from R. Tahiti. Why curved? Well, our guess is this gent has never heard R. Tahiti, let alone sent a report in its direction. Reason: though the card, which we had a look at, bears Tahitian stamps, it's postmarked in Massachusetts. Needless to say, it isn't counting.

Long-time EI DXer Hank Holbrook of Bethesda, Md., is the proud possessor of one of the year's longest-shot QSL's. It's from IDIWB, an Alitalia flight, no less, 200 miles NNW of La Coruna, Spain, at 33,000 feet with 100 watts. Frequency was 2945 kc which, technically at least, is medium-wave territory. In case you'd like to try your luck at such a feat, now's the time to log most any kind of utility DX below 3 mc.

For the record, those SWL swapping cards with the non-FCC calls do *not* count as QSL's. It shouldn't have to be said. But one sharpie tried to palm off two of them during our last Awards Period.

According to information distributed by Yemen at the World's Fair, R. Sanah still operates on 15710kc at 2200-0100, 0600-1000 and 1100-1700. This transmitter was heard widely in the fall of '63, though with considerable drifting. Reports out of neighboring Aden at that time put the station in Egypt, where it still might be. Since 15710 hasn't been reported in NA recently, you

might try for the second SW channel (5950 kc) or even the BCB outlet on 881 kc.

Seems the only time ZK5, R. Rarotonga (Cook Islands), can be logged in North America is on those rare occasions when that potent radioteletype station on 5045 kc leaves the air. Best bet is between 0100-0200.

According to R. Sweden, R. Monte Carlo will put a long-wave transmitter into operation sometime during 1965. Meanwhile, R. Monte Carlo's transmissions this winter will be relayed by R. des Vallees-Andorre on 818 kc (BCB).

R. Togo at the capital city of Lome now has a new 100-kw transmitter on 5047 kc. With news in English at 1600. R. Togo is an excellent DX prospect.

Members who pride themselves on patience should try to log Australia via VL2UV. Station operates Tuesdays, Wednesdays and Thursdays only under auspices of the University of New South Wales at Sydney. Power is a puny 300 watts, frequency 1750 kc. Sign-on comes at 0300 (midnight PST), so be prepared to call on that patience during the wee hours.

Member H. L. Chadbourne of California reports a new frequency for the Far Eastern Broadcasting Company's Manila outlet. Station is heard in English on 9505 kc as early as 0700 (0400 PST) until past 1030.

Pretty soon EIDXC members will be able to stick to stations beamed to North America and still come up with pretty fair totals. Latest to join the long list is Radio Beirut (Lebanon) on 9625 kc at 2130.

Sign of the sunspot times is the fact that the Solomon Islands Broadcasting Commission has shelved all other SW frequencies in

[Continued on page 119]



**ACOUSTECH  
IV**

# ALL-TRANSISTOR PREAMPLIFIER

THE KIT: ACOUSTECH IV Stereo Control Center  
 THE MANUFACTURER: Acoustech Inc., 139 Main St., Cambridge, Mass. 02142  
 THE PRICE: \$149  
 THE CONSTRUCTION TIME: about 20 hours

**C**OMPONENT HI-FI came into its own about the time that Britisher named D.T.N. Williamson devised his famous amplifier. For though it never received a tenth the acclaim, Williamson also designed a preamp to go with that power amp of his. Flexibility was the thing Williamson seemed to have had in mind, since this duo sort of arrangement obviously makes the actual physical layout a good bit easier. Further, keeping preamp and power amplifier in separate packages helps eliminate the hum problems that can plague integrated amplifiers.

Tubes were kings in those days, of course, and the years have seen dozens of tube preamps in a baker's dozen different configurations. But now that semiconductors seem to have found their place in the hi-fi world, it's not surprising to see more and more appearing in preamps.

**What It Is.** Though the Acoustech people don't call their Acoustech IV a preamp, most people would. Acoustech refers to the device as a stereo control center, which, come to think of it, perhaps is a closer approximation to what the device actually is. But preamp or control center, the Acoustech IV weighs in as a solid-stater that's way out front in every respect. Appearance, design and, as

our table indicates, performance make this a preamp that's no backseat billy from any point of view.

Though designed to work with the company's transistor power amplifier, the Acoustech can be used with practically any power amp. And it has sufficient inputs to accommodate most any program source a typical stereophile would have in mind. Its two low-level inputs serve for magnetic cartridges or, with modifications, tape heads. And its two high-level inputs can take a signal from a

<i>The ACOUSTECH IV at a Glance</i>	
<b>Frequency response:</b> 20-20,000 cps, $\pm 0.1$ db Flat from 5 cps (limit of test equipment) to -3db at 240 kc	
<b>RIAA equalization:</b> $\pm 0.5$ db	
<b>Total harmonic distortion:</b> Below 0.1 per cent (limit of test equipment) at 20 cps, 1 kc, 20 kc	
<b>Intermodulation distortion:</b> High-level inputs 0.082 per cent (60 and 6,000 cps mixed 4:1 for 2 V equivalent sine-wave output)	
<b>* Hum and noise:</b> High-level inputs: -75.5db Low-level inputs: -56db	
<b>* Sensitivity:</b> High-level inputs: 500 mv Low-level inputs: 2.8 mv	
<b>* 1 kc signal, 2 V rms out.</b>	

tuner or a high-output crystal or ceramic cartridge.

One thing you can't connect to the Acoustech is a tape deck—not in quite the right way, anyway. Equalization within the Acoustech is for RIAA phono, not NARTB tape, and there *is* a difference. But all isn't lost. For one thing, a tape deck with its own built-in preamp could be fed into the Acoustech's high-level inputs with no problem. Further, the Acoustech people will supply a modification kit, for \$1, which will adapt one of the low-level inputs for tape use.

**The Controls.** Getting around to the front panel, the Acoustech's controls include an input selector switch for selecting the program source; a mode switch (stereo or mono); left and right frequency-compensation controls; a balance control; and a level control. In addition, there are four push buttons. One turns AC power on and off; a second—a muting button—drops the output of both channels 16 db; a third—called a comp switch—inserts or removes the frequency-compensating networks from the circuit; a fourth—called tape—enables you to play tapes no matter what position the input selector happens to be in.

Also on the front panel is a jack for high-impedance headphones and a switch that selects either left or right speaker, or both.

Of the push-button controls, one—marked comp—deserves special comment. When the control is in its normal position, response of the preamplifier is flat, a condition which

the manufacturer states desirable for reasons of transient response and just plain listening. Depress the button, and the frequency compensation circuits (tone controls) become operative. But conventional controls they are not. They simply don't have the same effect that most bass and treble controls do. Matter of fact, maximum cut and boost is on the order of 10db, and even this occurs at the extreme limits of the audio spectrum.


The Acoustech people explain this by stating that "The action of the frequency compensating circuit has been designed . . . to satisfy audibly rather than to meet any preconceived ideas." And while this kind of English is a little hard to decipher, the meaning seems clear. In short, this is a preamp the listener drives—not vice versa.

**Putting It Together.** As you no doubt have gathered by now, the Acoustech IV isn't for the rank beginner. It's a preamp that's very definitely in the pro class from most every angle. And it's not for the beginner to construct, either, due chiefly to one big shortcoming in its construction manual.

To be sure, the text in the manual generally is excellent. The manufacturer has taken trouble to explain most operations carefully and thoroughly in a manner that is distinctly heart-to-heart. Before wiring up the push-button assembly, for example, you are told that "Possibility for error is greatest at this point" and that "if you are tired (or) if it is late at night, take a break or a nap." Simi-

[Continued on page 114]

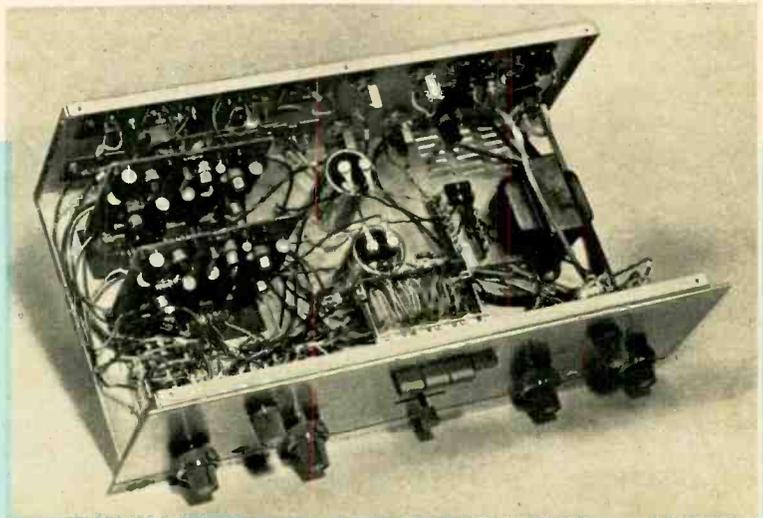There isn't much hardware in the Acoustech IV. The left and right channel preamp circuitry proper are supplied fully wired and tested on the two circuit boards at the left. Both boards plug into sockets after connections are made to them. Wiring on the four push button switches is tight, therefore you must exercise great care to avoid causing shorts in this area.





## CB CORNER

BY LEN  
BUCKWALTER  
KB4R 480

*really*

# Is NA<sub>^</sub> for CB Radio?

**P**ROFESSOR MORSE probably knew about it. Marconi surely suspected it. Now we've got a line for it. What is it? "An insatiable passion for communication." That's what.

Founder and sole spokesman for CB radio's newest would-be national organization says this passion explains CB's phenomenal growth over the years. And he also believes he knows the program that would enable his NACBR (National Association for Citizen Band Radio) to feed that passion. Yep, you read it right. The name is National Association for Citizen Band Radio, which makes for some unusual spelling, if nothing else.

NACBR's main plank seems to be that CBers should be allowed to talk about anything; be permitted long-distance contacts; have the right to erect antennas up to 100 feet high.

Another sweeping proposal centers on the 10-meter ham band. Located just above the Citizens Band in the 28- to 29-mc region, 10 meters is a tasty slice of spectrum NACBR would grab for CB. NACBR would convert 10 meters into a combined CB/amateur band. Ham privileges there would be, though no code or technical tests.

NACBR's roots provide an interesting contrast to previous groups with a let's-have-a-national-organization-for-CBers pitch. Man behind NACBR is Gordon P. Brown of Rochester, N.Y. He obviously belongs to a breed apart from other, earlier organizers who also wished to get CBers on the national-club bandwagon. Brown is an experienced businessman with resources at his command. He owns two AM radio stations and a hunk of a TV station.

**But let's look further.** Above all, Brown is forthright. He believes FCC gagging of CB chit-chat violates the right of free speech. Mr. Brown says he believes the Commission's

move in this instance smacks of fascist dictatorship and does violence to the Constitution.

He goes on to label the recent rules-tightening as radio's Volstead Act (the 1920 law enforcing Prohibition). The assumption here is that the parallel lies in the fact that the Volstead was an example of an unpopular law.

There isn't much doubt about another point Brown makes again and again. He estimates there's some \$350 million already invested in CB equipment. And, to his way of thinking, this investment "is a direct result of the public's insatiable passion for communication." Equally enticing are Brown's predictions of what CBers soon may be up to. They'll be using their channels "to spread the word of tolerance, knowledge and peace," he says.

**As for the NACBR,** we had a question for Mr. Brown and he had an answer for us. "Will NACBR members have the

right to vote on issues or to elect officials?" we asked. Mr. Brown's answer: "No."

Which brings us to one piece of information omitted from NACBR literature. NACBR is a private, closed corporation. All decisions rest in the hands of its owner, Mr. Brown. A member's franchise is solely financial—exercised by paying yearly dues of \$6, plus an optional \$5 for an NACBR pin.

There is nothing which appears improper in Mr. Brown's organization. What deserves second thought, however, is an unfortunate choice of name.

If Mr. Brown succeeds in enlisting the support of most CBers, it would enrich NACBR's coffers by more than \$3 million a year. The money would remain under Brown's exclusive control.

We are not at all sure that the National Association *really is* for Citizen Band Radio. Time alone will tell. ♦



# The Wheatstone Bridge

**B**EST way to cross a river is via a bridge. And the best way to make accurate resistance measurements also is via a bridge—though a slightly different kind of one, to be sure. The latter is called a Wheatstone bridge and it does its job by comparing an unknown-value resistance with a known-value resistance. A meter, which is connected between two arms of the bridge, indicates a voltage difference which is proportional to the difference between the known and unknown resistances.

The Wheatstone bridge's accuracy is limited only by the precision of its components and its calibration. Unlike the VOM or VTVM, the Wheatstone bridge's accuracy is not affected by supply-voltage changes.

Let's take a look at the schematic to see what happens when a voltage is applied to the top and bottom of the bridge, or across R3 and R4—the comparison resistors. Since R3 and R4 are exactly the same resistance and they are in series, the 1½-volt battery voltage divides in half across them. That is, the voltage at A, with respect to the other side of R3 or R4, is exactly ¾ volt.

Look at the left side of the bridge. Resistor R1 is a potentiometer. The other resistance, Rx, is the resistor whose value you want to determine. Meter M1, connected from A to B, indicates the voltage difference between these points.


Let's set R1 so M1 indicates exactly zero. The bridge is now balanced and we know two important things. First, the voltage at B is also ¾ volt. If it weren't, M1 would deflect because there would be a voltage difference between A and B. Second, R1 equals Rx. Why? Because when R1 equals Rx the battery voltage divides equally (¾ volt) across them for the same reason it did across R3 and R4.

The thing to remember is that the resistance of R1 and Rx doesn't have to be the same as R3 and R4 for the voltage at A and B to be equal. If R1 and Rx were each, say, 1,000 ohms, the voltage drop across them would still be ¾ volt simply because their resistances are equal. Sensitivity pot R2 protects M1 against excessive current.

Therefore, before connecting Rx, always turn R2 slightly counterclockwise. Then turn R2 slightly clockwise for a small indication on M1 (which could be to the left or right of zero). Then adjust R1 to zero M1 again. Repeat this procedure until R2 is full clockwise and M1 again indicates zero. Calibrate a scale for R1 with known-value precision resistors.

Using the parts values shown, our bridge will measure resistance up to 500,000 ohms. To measure higher resistance, use a 100-microampere meter for M1 or increase the battery voltage.

—H. B. Morris

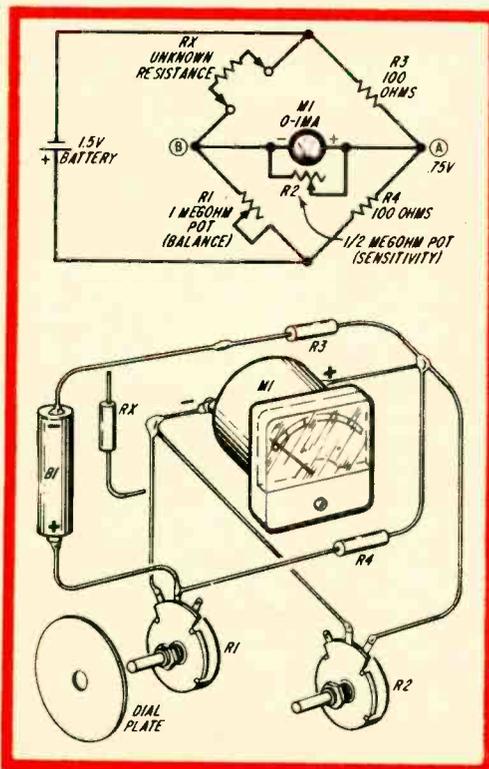

## Radio's Iron Curtain

Continued from page 32

ended when jammers came up on all the frequencies not being used as well as those on which program material was being transmitted. In the interests of good frequency management, this system soon was abandoned.

Perhaps the most effective anti-jamming device is known as *twilight immunity*. This method takes advantage of certain characteristics of the ionosphere.

The range of frequencies the ionosphere will reflect differs from day to night. During daylight hours the ionosphere will reflect higher frequencies than can be reflected at night. This phenomenon immediately suggests an anti-jamming device.

A transmitter located well to the west of a target area can get through to the desired territory no matter what a jamming station in the middle may do. Look at it this way: as darkness advances from the east there comes a time when the transmitting station is in daylight, the jammer in twilight and the receiving point in darkness. Both the broadcaster and the jammer can get a signal into the target area—but not on the same frequency.

A signal from the broadcaster hits a portion of the ionosphere that is in daylight and is reflected down to the target. But the spot of reflecting ionosphere between jammer and target is in darkness. A jamming signal on the broadcaster's frequency would not be reflected at all from the nighttime ionosphere and the jammer is out of business. This phenomenon occurs at dusk in Western Europe.

Our illustration shows that for several hours relatively high daytime frequencies can be propagated into Communist target areas while jammers between the transmitter and target are restricted to the lower frequencies that can be reflected from the nighttime ionosphere. For the jammer, it's a little like an outfielder watching a home run sail over his head and into the stands.

**Jamming's Future.** On August 1, 1964, just two days after the Chinese Communists publicly reaffirmed their refusal to attend any international conference on the ideological rift in the Communist camp, a major change in Soviet policy took place. The U.S.S.R. began deliberate jamming of R. Peking's

Russian-language broadcasts directed to the Soviet Union. For the first time in nearly three decades of jamming, the Russians employed the technique against another Communist country. Thus, the wheel which had begun to turn in the summer of 1963, when jamming of V. America and BBC broadcasts in Russian was discontinued, had come full circle.

Interestingly enough, the U.S.S.R. did not use the familiar noise jammers against Peking. Instead, it employed broadcast jamming, which consisted of program material transmitted on Peking's frequencies. The Chinese almost immediately began jumping frequency, moving from 3 to as many as 40 kc away at regular time intervals. But the Russians followed them, thus eliminating all possibility that the interference was accidental.

And here's the really odd angle. The program material which the Russians were using to jam Peking was part of the R. Mayak transmission, also inaugurated August 1. R. Mayak, for the record, is a 24-hour-a-day program in Russian for listeners in the Soviet Union and abroad. It carries news on the hour and half-hour, as well as music and other special-interest features.

It appeared that the Russians were killing two birds with one stone. For one thing, they were inaugurating a new and revolutionary service. But they also were using many of the transmitters in this service to jam programs not to their liking.

In addition to R. Peking, the Russians were using R. Mayak to jam R. Free Europe's Polish programs. What's more, some R. Liberty programs also are being jammed by conventional noise jammers.

It now is evident that many of the transmitters formerly used for jamming BBC and V. America transmissions have been converted to conventional broadcast transmitters. These can be used either for international broadcasting or jamming—or both.

Though the Russians have cut back on their overall jamming effort over the past year and a half, there is every reason to believe that they would return to it should the occasion warrant. Further, they have assisted Castro by delivering several jamming transmitters to Cuba. And Castro has used them.

In the Far East, the Chinese Communist jamming effort is growing by the day.

There is no doubt that jamming will be with us for years to come.



# THE HAM SHACK

BY ROBERT  
HERTZBERG  
W2DJJ

## MOBILE MIKE . . .

It's quite a switch from a beam on a roof tower to a modest little halo on a bumper mount. But we did it—as part of our shift from fixed-station SSB on 10, 15 and 20 meters to mobile AM on 2 meters. Just this past summer we installed a Heath Pawnee in our Chevy

convertible (see photo). And first time we turned on the rig we found ourselves in a mighty different ham world.

As for instance, we discovered that most Novices talk too much. It's possible, of course, that being new to the game has caused them to fall in love with their mikes. But whatever the reason, many seemingly can't bear to terminate a QSO. We must have covered 20 miles on an Ohio road while two lads in Cleveland made ready to sign off. We plain lost count of the final-finals they exchanged in the process.

Novices, of course, must use crystal control, so cross-band operation is common. Accustomed to transceivers, we found it a bit frustrating to hear one side of a conversation and not the other. The break-break technique that works so well on the other bands got us nowhere, so we called CQ and spun the receiver tuning knob for replies. Fortunately, there were plenty. After all, why shouldn't the sound of a W2 in W8 and W9 land make the boys pick up their ears?

On the lower-frequency bands most beams are only broadly directional, but on 2 they really are sharp. Some of the multi-element Yagis we heard were just like searchlights. Aimed directly at us when we were parked at a roadside eating place, they would pour in roaring signals. But turned away only a few degrees, they went absolutely dead.

The Pawnee now is the home shack, with us members in good standing of the Queens Insulting Net on 147.5 mc. We gas all through the evening hours with never a worry about TVI. It's fun!

**Fonetic Follow-Up . . .** Recent remarks in this column about Unfunny Fonetics have caused several readers to ask why we don't promote the new international alphabet used by the airlines. Though this Alpha-Bravo-

Yankee-Zulu combination has been published widely, it's really no better than any of the more popular lists. These generally use easily recognizable names of people. The Alpha-Bravo assortment doesn't, and it also has one other notable weakness.

The catch we have in mind is the letter Q, for which the phonetic is Kay-beck. What, you well may demand, is the connection between Q and Kay-beck? Well, the latter happens to be the *French* pronunciation of Quebec, though it sounds more like the phonetic for K to most ears. And the choice of Quebec becomes even more puzzling when you think of all the other French words in which Q has the familiar kew sound.

There's still another curious aspect of the phonetic mix-up. Some radio services which do use the new international very meticulously also retain something that's extremely ancient. It happens to be the old military word Roger for R, which they use as the voice word of acknowledgement. To our way of thinking, this is an inconsistency if there ever was one!

**Sensible Signal . . .** Long before the military adopted *over* as a your-turn-to-talk signal in phone work, most everyone used the simple expression *go ahead*. This now is returning to favor in ham operation, but in somewhat abbreviated form. Today, it's *go*, sweet and simple. But it's also short, snappy and unmistakable. Like it? —



Two-meter mobile can be fun and then some, as W2DJJ, learned on a trip through W8/W9 land.

# LAFAYETTE RADIO ELECTRONICS

# FREE!

1965 CATALOG No. 650

Over 500 Pages! *Featuring Everything in Electronics for*  
**HOME • INDUSTRY • LABORATORY**  
*from the "World's Hi-Fi & Electronics Center"*

- Stereo Hi-Fi—All Famous Brands Plus Lafayette's Own Top-Rated Components
- Citizens Band—Transceivers, Walkie-Talkies and Accessories
- Tape Recorders • Ham Gear
- Test Equipment
- Radios, TV's, and Accessories
- P.A. Equipment; Intercoms
- Cameras; Optical Goods
- Marine Equipment; Auto Accessories
- Musical Instruments; Tools; Books and MUCH MORE

**BUY ON TIME—**  
 Use Lafayette's famous Easy-Pay Credit plan . . . up to 24 Months to Pay

See the Largest Selection in Our 44-Year History



199<sup>50</sup>

New LR-800 70-Watt Complete AM-FM Stereo Multiplex Receiver features a tuned nuvistor "front-end" and an FM "Stereo-Search" multiplex indicator. Excellent sensitivity, frequency response, and low distortion specs. Imported, 99-0005WX.



93<sup>95</sup>


New LT-325 AM/FM Multiplex Tuner combines simplicity, flexibility, and superb styling. 20-Tube performance provides a great variety of features, including a new audible tone "Stereo Search System." Imported, 99-0001WX.



49<sup>95</sup>

Model LA-224 24-Watt Stereo Amplifier combines high performance, beautiful styling and low price to give you a truly brilliant stereo performer. Full control facilities for integration with all hi-fi music sources. Imported, 99-0017WX.


## HEADQUARTERS FOR THE HI-FI ENTHUSIAST

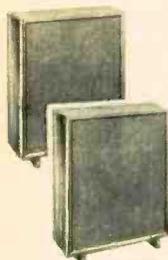

39<sup>95</sup>  
2 for 78.50

Model SK-300 "Decor-ette V" Slim 5-Speaker System utilizes the 5 most important speakers you may ever own. Four 6½" woofers and one 2½" cone-type tweeter designed to give optimum performance in a 4¼" thin oil walnut enclosure. Response from 50 to 18,000 cycles. Imported, 99-0008WX.

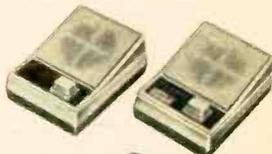Lafayette 2-Station Transistorized Intercom features inter-unit tone calling, push-button operation and beautiful styling. A single 66 foot plug-in connecting cord allows for fast and simple hook-up. Powered by one inexpensive 9-volt battery. AC power supply/battery charger available. Imported, 99-4526.



9<sup>95</sup>

Model RK-142 Deluxe Portable Tape Recorder perfect for the home, school, or office. Records and plays ½ track monaural at two speeds. Specially designed lever type motion switch gives fool-proof operation. Complete with dynamic microphone, connecting cables, and empty 7" reel. Imported, 99-1512WX.

59<sup>95</sup>

Mail The Attached Card or Coupon TODAY For Your FREE LAFAYETTE 1965 Catalog

# LAFAYETTE is HEADQUARTERS

## For CB and AMATEUR EQUIPMENT



64<sup>95</sup>

Deluxe Model HA-63 Shortwave Receiver is an excellent choice for the beginning shortwave listener or novice amateur. Covers 550 KC to 30mc in 4 bands and features electrical bandspread on all frequencies. 7 Tube circuitry gives outstanding selectivity and sensitivity. Imported. 99-2534WX



22<sup>95</sup>

"Explor-Air" 4-band short wave receiver kit—an ideal way of introducing yourself or your children to the fascinating world of electronics and shortwave listening. Detailed step-by-step instruction book makes this kit a pleasure to build. 19-0905. Cabinet available for 2.85. 19-0906



59<sup>95</sup>

Three New Deluxe Lafayette Receivers for monitoring police, fire department, aircraft, civil defense, or commercial communications. 10-Tube performance features high sensitivity, variable squelch, and fully tuned RF stage. Imported. Model HA-50 30-50MC 99-2525WX Model HA-55 108-136Mc 99-2527WX Model HA-52 152-174Mc 99-2526WX



25<sup>95</sup>

The New Model HA-115 audio compressor amplifier instantly and automatically increases the "talking power" of your citizens band transceiver by increasing the average modulation of the transmitter section. Works with all popular CB units. 42-0117.



25<sup>95</sup>

2 for 49.95


HE-29C 9-Transistor Walkie-Talkie provides two-way communications up to 1.5 miles. Powered by six penlight batteries with life expectancy of 55 hours. An AC power supply is also available. Specify channel. Imported. 99-3020CL.



19<sup>95</sup>

2 for 38.75

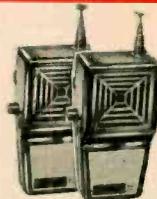Model HA-85 6-Transistor "Walkie-Talkie" transmits and receives up to 1 mile. Ideal for sports, boating, construction and recreation. Complete with leather case, earphone, batteries, and crystals for the channel of your choice. Imported. 99-3013CL.



10<sup>95</sup>

2 for 21.00

The HA-70A—a wired pocket-size 3-transistor walkie-talkie with countless exciting short range applications. Complete with crystal, carrying case, and 9-volt battery. Imported. 99-3011L.



6<sup>95</sup>

Lafayette Stainless Steel CB Mobile Antenna—an outstanding buy with outstanding features. Chrome plated swivel ball mount base permits mounting on any surface. Lug terminals for easy hook-up to coaxial cable. Imported. 99-3034WX.

## EXCLUSIVE LAFAYETTE WIRED TEST EQUIPMENT



9<sup>95</sup>

New! 20,000 Ohms-Per-Volt Multitester at Lafayette's low, low price. Has every needed range for testing appliances, radio, etc.: 40 microampere meter movement and 1% precision resistor for accurate readings. Imported. 99-5008. Pigskin carrying case available for 1.75. 99-5009.



26<sup>95</sup>

Lafayette VTVM with all the ranges and accuracy you need for audio, radio and TV applications. Giant 6½" full-view meter accurately measures AC peak-to-peak, AC RMS, DC voltage, and resistance. Leather case and accessory RF probe available. 38-0101



19<sup>95</sup>

Lafayette Tube Checker packed with features at a price you can afford. Accurately checks over 1600 tubes including new compactrons and nuvistors. Handy, easy to read slide out tube chart. Imported. 99-5011.

## SEND TODAY FOR YOUR FREE 1965 CATALOG

LAFAYETTE RADIO ELECTRONICS

Mail Order and L. I. Sales Center

111 Jericho Turnpike, Syosset, L. I., New York

New York, N. Y. 100 Sixth Ave.  
Brooklyn, N. Y. 2265 Bedford Ave.

Jamaica, N. Y. 165-08 Liberty Ave.  
Bronx, N. Y. 542 E. Fordham Rd.

Newark, N. J. 24 Central Ave.  
Plainfield, N. J. 139 W. 2 St.  
Boston, Mass. 584 Commonwealth Ave.  
Natick, Mass. 1400 Worcester St.

New! New York City Store!  
71 West 45th St.

Scarsdale, N. Y. 691 Central (Park) Ave.  
Paramus, N. J. 182 Route 17

LAFAYETTE RADIO ELECTRONICS

Dept. EIA-5 P.O. Box 10

Syosset, L. I., N. Y. 11791

- Send me the FREE 1965 Lafayette Catalog 650  
 \$ enclosed; send me (Prices do not include shipping charges).

Name

Address

City

State

Zip



# LAFAYETTE ...Headquarters For Citizens Band Equipment

## NEW! LAFAYETTE 23-CHANNEL CRYSTAL-CONTROLLED DUAL CONVERSION 5-WATT CB TRANSCEIVER WITH ADVANCED "RANGE-BOOST" CIRCUIT

- 13 Tubes, 8 Diodes
- Low Noise Nuvistor RF & Mixer
- 5 Double-tuned IF Transformers

Model HB-400 **169<sup>50</sup>**  
Only

- Frequency Synthesis For 23 Channel Crystal Controlled Transmit & Receive ■ No Extra Crystals Needed ■ Dual Conversion Receiver with 3/10  $\mu$ V Sensitivity ■ Delta Tuning ■ Variable Squelch, Variable Noise Limiter ■ Illuminated "S" and RF Output Meter ■ Push-to-Talk Ceramic Mike ■ "Range-Boost" provides high average Modulation—increases Effective Range ■ Built-in Dual Power Supply, 117VAC, 12VDC ■ "Vari-Tilt" Mobile Bracket For Easy Installation ■ Plug-in Facilities for Lafayette Selective Call Unit
- Compact, 12"Wx10"Dx5"H



Double Side Band Full Carrier

## NEW! LAFAYETTE ALL-TRANSISTOR DUAL CONVERSION 5-WATT CB TRANSCEIVER FEATURING AUTHENTIC MECHANICAL FILTER



Includes .003% Tolerance Crystals for Frequency Stability!

Small, Compact—  
Only 3" High!

- 100% Solid-State . . . Full 5-Watt Performance!
- 11 Rugged Silicon Mesa Transistors Used in Critical Areas
- Small, Compact—Only 3" High!
- Low Battery Drain—Less Than 350 ma on Receive, 850 ma on Transmit!

MODEL HB-500 **139<sup>50</sup>**  
Only

- 12 Crystal-Controlled Transmit & Receive Positions
- 23 Channel Tunable Receiver with Spotting Switch
- 15 Transistors, 5 diodes with Printed Circuit Construction ■ Dual Conversion Receiver with 5/10  $\mu$ V Sensitivity ■ Mechanical Filter For Razor-Sharp Selectivity ■ Variable Squelch, Automatic Noise Limiter, "S" meter ■ Dependable Sealed Relay Switching ■ Fits Anywhere—Only 11 $\frac{1}{2}$ "Wx6 $\frac{1}{2}$ "Dx3"H ■ For 12VDC (optional 117VAC Transistorized power supply available)
- Supplied With Crystals for Channel 12, special Mobile bracket, Push-to-Talk Dynamic Mike and Mobile power cable.

## NEW! LAFAYETTE DELUXE 8-CHANNEL DUAL CONVERSION 5-WATT CB TRANSCEIVER SUCCESSOR TO THE FAMOUS LAFAYETTE HE-20C

Model HB-200 **109<sup>50</sup>**  
ONLY

- 9 Tubes plus 3 Silicon Diodes plus 2 Crystal Diodes for 17-Tube Performance ■ Super Sensitivity—1 Microvolt or Less ■ 8 Crystal Receive Positions plus 8 Crystal Transmit Positions plus 23-Channel Tunable Receive
- Push-to-Talk Microphone ■ Dependable Relay Switching ■ Illuminated Meter with 3-Position Switch ■ Adjustable Squelch and Automatic Noise Limiter ■ Spotting Switch ■ Built-in 117 Volt AC Power Supply with 12 Volt DC Mobile Transistorized Power Supply ■ Plug-in facilities for Lafayette Selective Call Unit ■ With Bracket Handle, Push-to-Talk Ceramic Mike, Pair of Transmit and Receive Crystals for Channel 15 plus Crystal for Dual Conversion.



MADE IN U.S.A.

**FREE!** Lafayette 516—Pg. 1965 Catalog No. 650. Write:  
Lafayette Radio Electronics Corp., Dept. EIA-5, P.O. Box 10, Syosset, L. I., N. Y. 11791

## Confessions Of An FCC Examiner

*Continued from page 77*

out the rather tall masts which supported an elaborate antenna system. Continuing to a few yards from the building we had no trouble in observing an impressive installation of ham-radio equipment through an uncurtained window. A young man was manning the telegraph key industriously and the blue flashes from mercury-vapor rectifier tubes added an eerie glow to the well-lighted room. A second young chap was engaged with a coffee percolator and cups.

In a few moments, we proceeded to the door and knocked. The coffee chef immediately opened it and my cohort said, "We've been curious about this place for some time. It's an amateur radio station, isn't it?" The reply was affirmative, and we were invited in to look around and have a cup of coffee. After a brief explanation of amateur radio by the young man who had admitted us (the other remained at the key), my cohort said, "You fellows operate under some pretty stiff Federal laws, don't you?"

I think that right there the young lad smelled a rat, but he acknowledged that they did. My cohort went on, "Aren't these some hours during which you boys aren't allowed to operate?" Guess the reply. "Oh, yes, but we've been granted special privileges by the Radio Inspector as we have non-interfering equipment and lots of experience!"

The time had come. Slowly drawing back his coat to expose the glittering gold badge of the Department of Commerce, my cohort said nothing; it would have been superfluous. The young man at the key immediately stopped and pulled a switch. Both tried to talk at once but their stammering was interrupted when my cohort said, "All right boys; you've said enough. Pull the main switch, turn out the lights and lock the doors and windows. We will put a padlock and Government seal on your shack and you are warned not to again use your equipment until we authorize it from the district office."

This statement brought forth much pleading. "Can't we just operate a few more days if we observe the silent hours? We both go back to college in a couple of weeks and won't be home again until summer vacation (this was their Easter vacation)." But it was of no avail; my cohort remained firm and

we closed them down. A few days later they received a citation from our office suspending both their operator and station licenses for a period of three months. This probably made them sadder and wiser; at any rate, we received no further complaints against them from then on.

As occasionally happens in connection with Government activities, attempts at bribery weren't unheard of. An occasional amateur sometimes would make a poorly disguised offer by saying, "Can't I just pay you a fine to cover this offense and close the matter?" A firm explanation by one of us that such tactics smacked of bribes usually was sufficient to set the offender straight.

Not only was such close approach to bribery tactics experienced, but a number of border-line cases also were known. Surprisingly enough, most of these emanated from some of the largest and most prominent firms in the industry, rather than individuals. Most were in the nature of attempts to gain favor and ingratiate themselves with the Radio Inspection Service. The hope was that more or less minor infractions therefore would be overlooked.

On more than one occasion, I came back from a field inspection trip which generally involved the checking of several prominent broadcast stations. And I would find an impressive express package addressed to me at the office, all prepaid and in order. The return name and address of the sender of course necessarily would appear on such as required by express company rules.

When I would call the parcel to the attention of the Inspector-in-Charge, he invariably would inquire, "Have you ordered anything from these people?" Upon my replying in the negative, he would say, "All right, you know what to do," and walk smilingly away.

Sure, I knew what to do; it was another established office routine. One of the office clerks would type out a Collect express label, addressed to the sender of the package. And, unopened, the box with whatever its contents were, promptly would go back!

Some packages even had been labelled brazenly with their contents: fragile: vacuum tubes, radio receiver, or more generally, radio parts. No acknowledgment of receipt of such shipments ever was made by our office. Nor was their return ever discussed on subsequent visits to the sender!

# EI's 1964 Index

# EI's 1964 Index

C—Construction Project  
 F—Feature Article  
 TP—Theory & Practice Article  
 Name following title is author.  
 Page number follows the date.

## AMATEUR RADIO

Antenna Analyzer	Friedman	(C)	Jan.	47
Arrester, Lightning	Pyle	(C)	May	34
Awards for Hams and SWL's, EI DX		(F)	Jan.	79
Awards for the Ham Shack	Anzalone	(F)	July	68
BFO, Universal	Blechman	(C)	Nov.	96
Clock Control for Ham and CB Stations	Black	(C)	Sept.	58
Code Sender, Automatic Compressor Limiter, Ham-CB	Grossman	(C)	Mar.	79
CPO, Wireless	Friedman	(C)	May	47
CQ Sender, Automatic Dipper, All-Transistor Modulated	Maynard	(C)	Sept.	96
Field Strength Meter for 6 and 2, Amplified	Buckwalter	(C)	Jan.	76
Ham's Greatest Thrill, A Headphones, How to Hook up Crystal	Friedman	(C)	Nov.	101
Heath Sixer, Deluxe Your Junior Ham, Want to be a? Memory Box for Hams	Friedman	(C)	July	80
Modulation Monitor, In-Line	Friedman	(F)	July	100
Phone Patch, Ten-Buck Reception, Diversity	Coccozza	(TP)	July	84
Slanguage, Ham Sunspots Are Coming!	Blechman	(C)	Jan.	73
Transmitter: The Scrounger	Cogan	(C)	Mar.	55
WWV Story, The	Blechman	(F)	Mar.	102
	Friedman	(C)	Nov.	81
	Friedman	(C)	Mar.	91
	Rosa	(F)	July	96
	Walker	(F)	May	68
	Leinwoll	(F)	Sept.	23
	Friedman	(C)	Sept.	31
	Lincoln	(F)	July	53

## AUDIO, STEREO & HI-FI

Amplifier, Build an Integrated Stereo	Morrow	(C)	July	42
Amplifier Curves, Those Transistor		(F)	Jan.	103
Amplifier: The Stereo 120	Kolbe	(C)	Jan.	54
Booster, Q1 for FM	Costa	(C)	Nov.	25
Design for Living		(F)	July	74
FM, Can Networks Save?	Angus	(F)	July	86
FM, Q1 Booster for Generator, 6X Audio	Costa	(C)	Nov.	25
Headphone Hi-Fi	Friedman	(C)	May	90
Headphones, How to Hook Up Crystal	Berger	(F)	May	74
Hi-Fi Hanky-Panky	Coccozza	(TP)	July	84
Load Box, Tape Fan's Mixer, All-Purpose Stereo Preamp, Build a Tape Record	Milder	(F)	Sept.	65
Record Live, How to Sheet Recorder, Ever Hear of a?	Glenn	(C)	May	88
Stereo on Wheels	Glenn	(C)	Sept.	48
Stereo the Easy Way, Going	Flanagan & Friedman	(C)	Jan.	90
Tape Recorder, So You're Going to Buy a	Milder	(F)	July	75
Tapes You Never Touch		(F)	Jan.	50
Volume Limiter, Photoelectric Automatic	Lynn	(F)	Sept.	112
Wattmeter, World's Simplest Audio	Cohen	(C)	Mar.	96
	Milder	(F)	Jan.	29
		(F)	Jan.	98
	Hahn	(C)	Jan.	100
	Gaulin	(C)	Sept.	108

## CITIZENS BAND

Antenna Analyzer	Friedman	(C)	Jan.	47
Antenna, Car-Top CB	Buckwalter	(C)	Jan.	68
Antennas, Oddball	Tepfer	(F)	Mar.	71
Arrester, Lightning	Pyle	(C)	May	34
Bandspread for CB, Calibrated	Buckwalter	(C)	Sept.	27
CB Converter: One-Way CB	Redmond	(C)	Nov.	104
CB Corner: Accident, What to do at an	Buckwalter	(F)		
Citizens Band?, What's Ahead for the			May	44
Dutch Uncle			Mar.	73
Licensing, Birdbrain			Nov.	89
Phantom Strikes, A Unopened Door, The Case of the			Sept.	64
CB Equipment: Yesterday, Today, Tomorrow			July	51
CB Papers: CB's Flood of Ink	Walker	(F)	Jan.	63
Citizens Band, The Other			Mar.	76
Clock Control for Ham & CB Stations	Cartwright	(F)	Nov.	55
Club Directory (Cont'd)	Frederick	(F)	Mar.	46
Compressor Limiter, Ham-CB	Black	(C)	Sept.	58
Crimebusting with CB		(F)	July	112
Crystal Checker, CB	Friedman	(C)	May	47
Dipper, All-Transistor Modulated	Cenan	(C)	Mar.	74
Dipper, CB			Nov.	101
Direction Finder, Low-Cost	Friedman	(C)	May	82
Junior Ham, Want to be a? Microphones: PTT, How to Switch to	Buckwalter	(C)	Mar.	43
Modulation Monitor, Big-i-CB	Cogan	(C)	Mar.	55
Modulation Monitor, In-Line	Walker	(C)	May	70
Myths, CB's Mammoth	Mann	(C)	July	56
Q, Hike That	Friedman	(C)	Nov.	81
Receiver: Pocket Superhet	Friedman	(F)	July	98
Rescue, Ready for Service Instruments, CB	Friedman	(C)	Mar.	63
Service Set, 6-in-1	Simms	(C)	Mar.	39
Sunspots Are Coming!	Stewart	(F)	Mar.	48
SWR Meter for CB	Mann	(F)	Mar.	59
SWR Reducer	Cogan	(C)	Mar.	73
	Leinwoll	(F)	Sept.	23
	Walker	(C)	Jan.	33
	Sands	(F)	July	85

## KIT REPORTS

Converter, 6-Meter (Ameco CB-6K)			Nov.	100
Oscilloscope, 3-inch (Eico 430)			Jan.	96
Preamp, Stereo (Dynakit PAS-3)			May	42
Receiver, Color-TV (Heathkit GR-53)			July	63
Receiver, Short-Wave (Knight-Kit Star Roamer)			Nov.	32
Receiver, Stereo FM (Eico 2536)			Sept.	70
Signal Tracer, Tuned (Conar 230)			Jan.	83
Television Receiver, Color (Heathkit GR-53)			July	63
Transceiver, SS8 (Heathkit HW-12)			July	66
Tube Tester, Low-Cost (EMC 213)			Sept.	73
Vacuum-Tube Volt-Milliammeter (Hallicrafters HM-1)			May	50
Walkie-Talkies, CB, 1-watt (Heath GW-52 & Knight-Kit KG-4000A)			Mar.	68

## SHORT-WAVE LISTENING

Antenna, All-Band SWL	Walker	(C)	Sept.	99
Arrester, Lightning	Pyle	(C)	May	34

# EI's 1964 Index

# EI's 1964 Index

Awards For Hams and SWL's, EI DX	(F) Jan. ....79
Broadcast Band, DX Boon For the	Bower (F) Nov. ....93
Castro Speaks . . . To Us	Stanbury II (F) Mar. ....108
Freebooter, Britain's Floating	Carter (F) Nov. ....74
Germany's, DXing the Headphones, How to Hook Up Crystal	Carter (F) Sept. ....56
Radio Moscow:	
Inside Radio Moscow	Coccozza (TP) July ....84
Outside Radio Moscow . . . Way Out!	Bower (F) May ....29
Reception, Diversity	Carter (F) May ....32
Short Waves, DXing the Slightly	Rosa (F) July ....96
Short-Wave Broadcasting: 2 Faces of SWBC	Stanbury II (F) Mar. ....98
Short-Wave Schedule, 24-Hour	Stanbury II (F) Jan. ....84
Sunspots Are Coming!	(F) Nov. ....38
WWV Story, The	Leinwoll (F) Sept. ....23
	Lincoln (F) July ....53

## THEORY AND PRACTICE

<b>Beginner's Page:</b>	Morris	
Diode, The		May ....100
Meter, Multiplying a Solar Cells		Mar. ....89
Timer, R-C		Jan. ....51
Transistor, The		Nov. ....114
Wave Trap, The Wonderful		July ....62
<b>Circuit Breakers: Give Your Circuit a Break</b>		Sept. ....69
Color TV, The ABC's of Construction Hints: Try These	Blechman	July ....78
Dr. Doppler's Strange Effect Headphones, How to Hook Up Crystal	Buckwalter	Nov. ....70
Magnets, Super-Cold Super-		Sept. ....68
Parts, How to Pinch Pennies on	Robberson	Nov. ....28
<b>Q-Multiplier:</b>		
What's a Q-Multiplier, Anyway?	Coccozza	July ....84
Radio at 100 Billion Cycles Schematics, Super-Size	Bush	May ....106
Semiconductors, What's New in	Mann	Nov. ....52
Tools For the Electronic Hobbyist		
Vacuum Tubes, Basic Course in		
Vacuum Tubes, 3 Experiments With		
VOM, The Dangerous		
Wire Gauging Made Easy	Whiteman	July ....37
	Solomon	Sept. ....74
		Mar. ....10

## SPECIAL FEATURE ARTICLES

Antenna Lab, Half-Pint		May ....80
Armstrong, The Agonies of Major	Harper	Nov. ....84
Design For Living		July ....74
FCC: Those Kilocycle Kops	Kneitel	Sept. ....49
FM, Can Networks Save?	Angus	July ....86

Freebooter, Britain's Floating	Carter	Nov. ....74
Induction, Instruction by Isters, Meet the	Re	Sept. ....86
Lingos, Instant	Hansen	May ....38
Machines That Listen	Locke	Nov. ....98
Magnets, Super-Cold Super-	Bush	Mar. ....33
		May ....106
<b>Medical Electronics:</b>		
Pinhead Patients		Sept. ....94
Shocking Facts on Electric Shock, The	Cummings	Sept. ....78
<b>Picturephone: "Mr. Watson, I See You."</b>		
Radio at 100 Billion Cycles	Harris	Nov. ....90
Radio + Radar = Rescue	Haas	May ....45
Radio, Who Really Invented?		May ....94
Semiconductors, What's New in	Hays	Sept. ....83
Sunspots Are Coming!	Collins	Jan. ....38
Syncom: Getting the Message Across	Leinwoll	Sept. ....23
<b>Telephone Device:</b>		
Talk Now . . . Listen Later!	Mitchell	Jan. ....70
TV Antennas, How Good Are the New Indoor?		Sept. ....81
TV, The ABC's of Color TV Recorders, The Truth About Those Home Television, Tunnel	Friedman	Sept. ....76
Tickers, New Ways to Keep Tabs on	Buckwalter	Nov. ....70
Tube Numbers, Those European	Gilmore	Sept. ....91
World's Fair, Electronic Wonders at the	Haas	Sept. ....40
WWV Story, The	Maizel	Nov. ....67
	Tromanhauser	July ....89
	Gilmore	Mar. ....29
	Lincoln	July ....53

## SPECIAL CONSTRUCTION PROJECTS

<b>Battery Analyst, The</b>	Mann	Jan. ....64
<b>Battery Chargers:</b>		
Budget Charger	Blechman	Sept. ....42
Nickel-Cad Charger	Mann	May ....72
BFO, Universal	Blechman	Nov. ....96
<b>Capacitor Checker:</b>		
Mickey-Mike, The	Patrick	Jan. ....52
<b>Electronic Games:</b>		
Old Riddle—New Game	Buckwalter	Nov. ....58
Quiz Game Empire		Jan. ....112
Intercom, A Power Pack for Your Telephone	Cenan	July ....72
Name Dropper, Electronic	Maynard	May ....51
<b>Photography: Enlarger Control Center</b>		
Power Supply, Triple-Y	Pollack	Jan. ....87
Receivers:	Toler	July ....82
All-American 5 Goes Modern	Flanagan & Friedman	July ....38
Compact BCer, The Junk the Car—Save the Radio!	Davidson	Sept. ....32
Remote Control: Transmitter and Receiver, R/C	Buckwalter	Sept. ....102
Seat Belts AOK!	McEntee	May ....53
Scope Calibrator, Simple	Bergida	May ....110
Transistor Tester, \$2	Toler	Sept. ....89
Transmitter, License-Free FM	Maynard	Nov. ....47
TV Blab-Off	Kolbe	July ....47
Vari-Volter, Regulated	Bruce	Sept. ....38
Volume Limiter,	Henry	Nov. ....77
Photoelectric Automatic	Hahn	Jan. ....100
Water Switch, Electronic	Maynard	July ....91
Wattmeter, Magic Eye	Stephens	Jan. ....43
Wattmeter, World's Simplest Audio	Gaulin	Sept. ....108

## That Ham Radio Brawl

*Continued from page 86*

countered (but didn't), it needs no enemies.

Several articles at one point appeared in 73 under the by-line of "Wretched Coward, K2PMM." No such call letters exist, though the name bears a striking relationship to that of a CQ official.

Green's big push against RM-499 came when he printed a for-or-against ballot on 73's cover and asked his readers to vote. He then announced that 83.5 percent of his readers, based on 3,000 ballots, were against the proposal, while QST claimed most hams enthusiastically supported it. CQ had a voice in that flurry, too. 73 was accused of counting "votes before the ballots are distributed."

One of the most surprising events did not concern the ham fight at all. Green declared his candidacy for the Republican vice-presidential nomination in the New Hampshire primary—and won! The fact that he happened to be the only candidate helped but, even so, he did receive a substantial number of votes. Green said his candidacy was not a pure lark but was meant to show deficiencies in American politics.

When CQ let go with its biggest shot of the squabble it started out by referring to "our noble vice-presidential candidate from New Hampshire. . ." The magazine went on to say that a ham club newspaper had torn Green up "in little pieces and dragged the remains from one side of his country barn to the other." Later they came on with, "Vulgar is the only word we can find to explain 73's expose of the so-called 'ARRL booze party.'"

"It's too bad so few of you read CQ anymore," was Green's retort. "Their few articles may be dull, but you're missing hilarious editorials." CQ, it happened, had just moved its headquarters from Manhattan to a Long Island suburb and Green, perhaps remembering the country-barn bit, said Cowan Publishing had moved "to what looks very much like an abandoned Howard Johnson restaurant. . ."

RM-499 is a serious piece of business for hams. Nearly all licensees agree that something must be done to clean up the clutter on the bands and that some form of incentive licensing probably is required. The question is whether RM-499 is the best answer.

However, just as the argument over the

ARRL's handling of the proposal once eclipsed the concept itself, RM-499 now seems to have faded from the center of the ham brawl. Instead, the fight has become self-perpetuating and its point is the fight itself.

Whether or not RM-499 ever gets made into law by the FCC, the big brawl of the early Sixties likely will be remembered for a long while by most hams. The benefits of the donnybrook are few in number, though they do exist. Many hams who had become bored with the hobby have suddenly renewed their interest, taking one side of the argument or the other. Nonhams have been attracted by fireworks in what normally is a pretty quiet and conservative field and may in the end bring new blood (unspilled) into the amateur fraternity.

73 was accused by CQ of getting into the controversy to promote subscriptions and advertising. Whatever the intent, the magazine seems to be enjoying healthy days. (73 returned the compliment by saying CQ had the same goal when it let go with its broadsides.)

The greatest danger undoubtedly was to the personalities involved. Some of the things that have been said might make an occupant of skid row send for a lawyer. However, no lawsuits have been filed at this writing and it appears that, fortunately, all those involved have relatively durable skins and cool heads. Evidently, no reputations have been damaged.


## Amateur Radio Confidential

*Continued from page 52*

pulling in Sinatra, Monroe and that bunch. In a flash the hams became phantom voices in the night. "The green Chevrolet, license 100-509," we'd say. "Watch it, feller." The gags went on for a month or so in my area, ending in what one newspaper called a "Pier 6 brawl for children."

There are lots of other stories I could tell. Such as parking mobiles around the DX hound's house, with its big beam, and giving a dozen exotic DX calls in ten seconds. Or the time we found two mobiles parked back to back and tied the whips together.

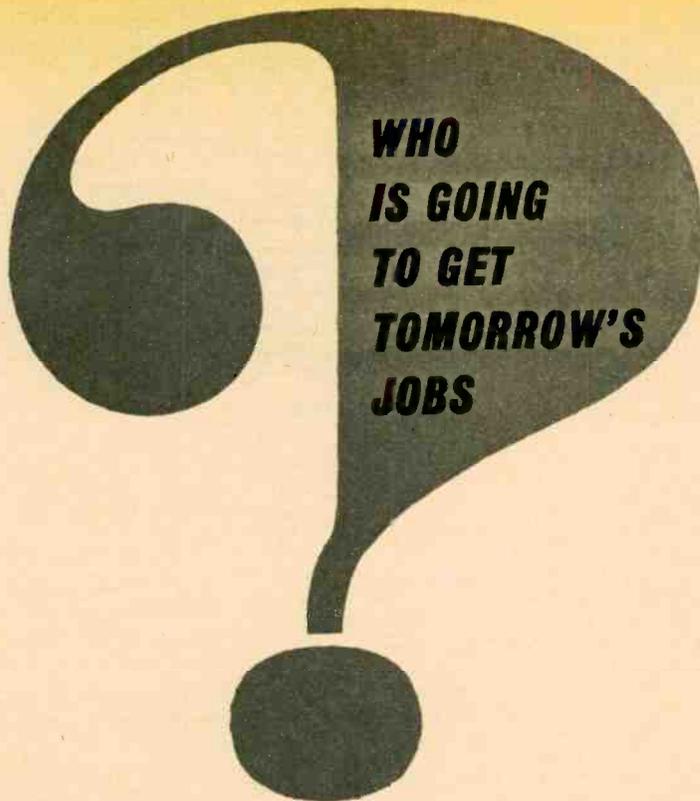But I just don't have time. I have to rush over to give a speech to a bunch of Novices at a school. My talk is titled, A Ham License Is a Privilege—*You Have Responsibilities!*



**WHO  
IS GOING  
TO GET  
TOMORROW'S  
JOBS**

There will be many new jobs in the future. But they won't be the same as today's. The work will be different—the skills needed will be different. Will you be able to qualify? Remember—

***You won't get tomorrow's jobs  
with yesterday's skills***

But you *can* start re-training now. Find out what these new jobs will be—decide which is best for you. Then go at it. Study. Practice. Whatever that new and better-paying skill calls for.

Re-training is necessary because jobs change with the times. That's part of progress. And so are the new opportunities that come with it. Make the most of them. Speak to the local office of your state employment service.

***Train now for tomorrow's jobs***



PUBLISHED AS A PUBLIC SERVICE BY FAWCETT PUBLICATIONS

January, 1965

113

## ELECTRONIC SWAP SHOP

El's Swap Shop provides a way for readers to obtain equipment they want in exchange for items they no longer have use for. Notices must be from individuals, not commercial concerns. Entries must include your name and address, as well as a description of what you now have and what you would like in exchange. Address: El's Swap Shop, ELECTRONICS ILLUSTRATED, 67 West 44th Street, New York, New York 10036.

**EICO 762** factory-wired CB transceiver. Like new with two crystals, mike and manual. Will swap for 7-inch, 2-speed monophonic tape recorder. John F. Downing, 18411 Kingsbury St., Northridge, Calif. 91324.

**HEATH IT-11** capacitor checker. Will trade for an audio wattmeter. H. Wolfe, Apt. 6C, 121-08 236th St., Rosedale, N.Y. 12472.

**El Stereo Beacon** (built from May, '63 EI article). Works perfectly. Will swap for small FM tuner. R. L. Fuller, 3510 Carr Ave., Indianapolis, Ind. 46241.

**GLOBE Mini-Matcher** antenna tuner. Matches transmitter output to a long-wire antenna. Assembled from kit. New. Will swap for SWR meter. Charles H. Ensor, 6911 Garden Grove Ave., Reseda, Calif. 91335.

**HEATH GW-11A 12-V** CB transceiver. Will swap for test gear. Chuck Sklover, 121-12 236th St., Laurelton, N.Y. 11422.

**WESTERN ELECTRIC Type 52** headset with adjustable headband and mike boom. Complete with plugs. Good condition. Will trade for Heath Sixer or make swap offer. Reed Layton, 4222 Lankershim Blvd., North Hollywood, Calif.

**SPARTON** photoelectric auto rear-view mirror. 12 volt. Double-surface mirror moves to non-glare position when headlights shine through rear window. Includes tube, photocell, relay and solenoid. Will swap for 35-mm camera. Chester Haynoski, 16453 Chatsworth St., Granada Hills, Calif.

**HEATH GC-1A (Mohican)** all-band transistor portable receiver with AC power supply. Make swap offer. M. Fisher, 4190 Bedford Ave., Brooklyn, N.Y. 71229.

**GONSET Communicator III** 2-meter transceiver with preamp and five-element beam with rotator. What have you to swap? Phil Bettan, 144-32 78th Ave., Flushing, N.Y.

**HALLICRAFTERS HT-37** CW/AM/SSB transmitter with PTT. 80, 40, 20, 15 and 10 meters. Good condition; make me a swap offer. Allan Malamy, 102-35 67th Rd., Forest Hills, N.Y.

**TRIPLETT 630** 20,000 ohms/volt VOM with test leads. Good condition, recently calibrated. Will swap for pocket-size 20,000 ohms/volt VOM or VTVM. Fred Blechman, K6UGT, 23958 Archwood St., Canoga Park, Calif.

**KNIGHT-KIT Span Master** regenerative all-band receiver. Make swap offer. David Buckwalter, Wilridge Rd., Georgetown, Conn.

**LAFAYETTE HE-15** CB transceiver. Needs crystals. Will swap for FM/AM tuner or hi-fi speaker and enclosure. Philip Weed, 17-19 Great Neck Rd., Copiague, Long Island, N.Y.

**RCA 10-inch TV.** 630 design, about 1948 vintage. In working order but needs touching up. Make swap offer. Christopher V. Waldorf, 2488 Grand Concourse, Bronx, N.Y.

## All-Transistor Preamp

Continued from page 99

larly, you are told precisely how to solder heat-sensitive components, exactly how to orient controls, and so on.

But if the text in the manual is superior, the drawings are just as poor. Even an experienced kit builder will find himself slowed in attempting to understand precisely what has been depicted. And certain inconsistencies between drawings tend toward confusion. The identical section on the input selector switch is shown quite differently in two succeeding drawings, for example, a failing that could lead to a wiring error in one of the sections the instructions spell out as "difficult." Further, had the drawings been clearer and easier to follow, construction time could be less than the 20 hours we specify.

Like some other kits now on the market, the Acoustech is supplied with all component parts neatly packaged in separate plastic envelopes. What's more, these various envelopes are stapled around the edge of a kit cloth, a large piece of felt-like material which Acoustech intends as covering for the work area. We found this made our task much easier, and Acoustech is to be congratulated for its care in this regard.

And should you want to use the Acoustech IV in places where the line voltage is 220/250 volts, the preamp can be easily modified for operation on this power. The modification is simple and requires only a minor wiring change in the connection of the primary of the power transformer.

Acoustech did not provide a center-channel output since it feels such an output degrades left- and right-channel separation. However, for those who want such an output to drive a third power amplifier, a special kit of parts is available for \$1.

**How It Worked.** As our table indicates, the Acoustech IV is a preamp that's up with the pros. Its superb transient response makes for a sound many other preamps are just plain incapable of. Its frequency compensation network seems based, as the manufacturer states, on the human ear rather than the textbook. And, if we can ignore some of the manual's annoying though not insurmountable shortcomings, we could say that this is a preamp that is outstanding in every respect.

# WORLD'S FUNNIEST ELECTRONIC FAKES!

## THE BLINKING BRAIN



**THE BLINKING "BRAIN"** is world's funniest electronic fake. Six signal lights in impressive 3½" master control box swiftly flash on and off in irregular patterns like a computer panel. Friends believe your wildest stories about what this scientific marvel is doing. Sit it anywhere or carry it with you. Operates mysteriously with no visible switch, wire or connection. Goofy spoof is a monument to frustration because it does absolutely nothing—except blink. Smart ebony plastic box precisely engineered to fool a physics professor. Uses standard batteries, not included. \$4.98 ppd.



## LITTLE BLACK BOX

**LITTLE BLACK BOX.** There it sits, the mysterious Black Box, quiet, sinister and waiting. The switch is thrown to "ON." Immediately there is a grinding of power as the box starts rocking and jumping as though it contained a hidden genie. Then the lid slooowly rises, and from beneath it emerges a hand. The hand grabs the switch, pushes it to "OFF" and quickly disappears back into the box. The lid slams shut and all is as it was. **IT DOES NOTHING—ABSOLUTELY NOTHING—EXCEPT SWITCH ITSELF OFF.** It has a fantastic psychological impact. Once seen—never forgotten. A gift that's funny, different and completely impractical. Uses standard flashlight batteries, which are included in the price of \$4.98 ppd.

**GUARANTEE:**  
**MY FRIENDS AND I MUST GET COMPLETELY HYSTERICAL WITH THESE NUTTY DEVICES OR I MAY RETURN MY PURCHASE FOR A COMPLETE REFUND.**

Hamilton House, Dept. 3L-1  
 Cos Cob, Conn.

Please send \_\_\_\_\_ Blinking Brain @ \$4.98  
 \_\_\_\_\_ Black Box @ \$4.98

Enclosed Find \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## A New Look for CB

Continued from page 39

in view of the fact that less than one-half of one per cent of all licensed CBers responded. And many yielded no real comments at all, merely indignant blasts containing a few constructive steps and little reason.

"So what if I did write a letter," you say. "Would it mean anything?" Let's see how effective some comments were. For one, the Commission wanted to set aside five channels for stations of different call signs. Reviewing the comments, it expanded the number to seven. Also, the proposed rules once pegged maximum output power at 3.5 watts. (Assuming a 5-watt input, this would work out as 70% efficiency.) But several manufacturers plumped for a higher figure, claiming their 5-watt rigs could attain efficiencies of 80%. The Commission responded in two ways: saying on the one hand that such high efficiencies are doubtful but, on the other, granting the 80% figure (equal to 4 watts), anyway.

Several organizations requested permission to make up their own call-signs. The result is compromise; sure, you can devise special calls, but you can use them only in addition to your regular call. Some requests were denied as being contrary to the CB service; e.g. higher antennas, more power and assigning frequencies according to location.

New proposals for CB are in the making. There's one, for example, that could tighten technical specifications and possibly increase equipment cost. Too, there's a hint that antenna-height restrictions even might be relaxed somewhat. How do you feel about these issues? Well, we'll keep you posted . . . you go ahead and write the letters. —

## Hi-Fi Today

Continued from page 40

of fact, the manufacturers mentioned simply are going after the quality-minded though non-technical market. There's still plenty of room for component hi-fi, and I haven't heard of any manufacturer who's thinking of cutting down on his component output.

What is going to be interesting here is the battle shaping up between the makers of the new high-quality packages and the big appli-

ance manufacturers who turn out those raucous-sounding stereos. Whoever wins the battle (and I know where *my* sympathies lie), the consumer is bound to profit in the long run.

I've had the chance recently to check out some of the new cartridges with elliptical styli. And I can confirm the manufacturer claims that the elliptical tip (much closer to the shape of a recording stylus than the usual ball tip) cuts down tracking distortion and provides generally cleaner sound. But I have my reservations.

What really bothers me is that it's oh-so-easy to install any of the new elliptical pickups incorrectly. And if an elliptical tip is even slightly out of alignment with the groove, the pickup loses its one big advantage. Worse yet, it actually becomes a record-destroyer as the narrow radius of the tip makes frontal instead of perfectly lateral contact.

This, I think, is going to be a tough problem to deal with. The makers of elliptical pickups take tremendous pains to align the stylus tips properly, which is one reason why the ellipticals cost more than standard pickups. But let a user install the cartridge even slightly off-center in the tone-arm shell and all the manufacturer's troubles are for nothing. The same goes if the stylus is canted by being dropped accidentally on a record or turntable platter.

At this point, all I can say is that anyone interested in an elliptical pickup should be careful to install it properly. And I think any household where wives or children handle hi-fi equipment should be elliptically off limits.

A good many people have noted that some of the new "transistor" tuners actually are hybrid jobs, with standard tubes or perhaps Nuvistors in the front-end circuitry. Reason is that transistor front-ends tend to be plagued by overload and cross-modulation problems.

In two cases recently, I've checked transistor tuners that performed magnificently in my own location (130 air miles from New York City). But they promptly became next to useless when I took them into the Big Town. They plain just couldn't separate closely spaced stations and strong stations came blasting through at several points on the dial.

[Continued on page 119]

## VHF Broadspanner

Continued from page 49

well in a strong-signal area. They cost only a few dollars. Take a look at the section of special antennas for VHF receivers in parts distributors' catalogs. There you'll find a selection of whip and ground-plane antennas that will cover practically all frequencies that can be tuned by the Broadspanner. The most common ranges of frequencies that are covered by the antennas are 30-50 mc, 108-136 mc and 144-174 mc.

Don't expect reception from 140 to 173 mc with coil L9 to be as hot as it was on the lower bands. The receiver's detector is a compromise design to cover 26-173 mc.


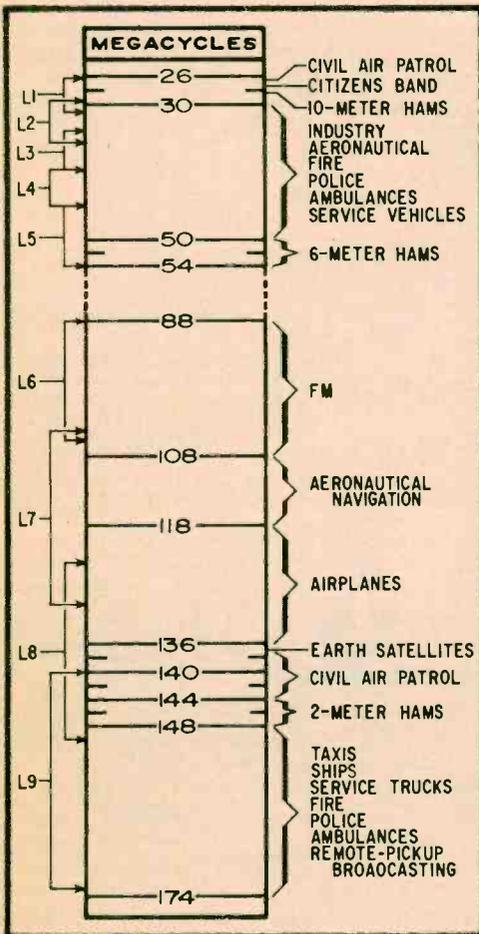


Chart shows frequencies covered by the Broadspanner's coils and what you can listen to.

## SOLDERING TIPS FOR HI-FI KIT BUILDERS

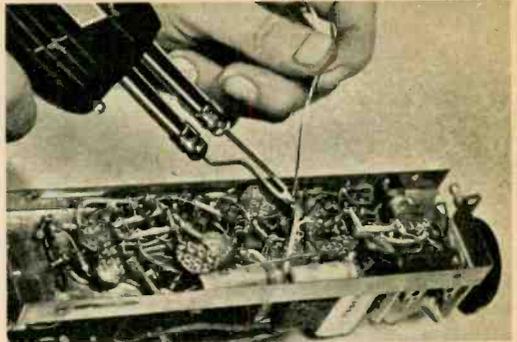

### AVOID USING TOO MUCH SOLDER

Apply just enough solder to make a secure connection. Excess solder may fill up tube sockets, freeze switches or cause short circuits.



### USE A DUAL HEAT GUN


Use the low heat trigger position to prevent damage when soldering near heat-sensitive components. Switch to high heat only when needed.

Weller Dual Heat Guns are invaluable for making fast, reliable, noise-free soldered connections. They're just as essential to hi-fi kit builders as they are to professional TV and radio service technicians. Two trigger positions permit instant switching to high or low heat. Tip heats instantly and spotlight comes on when trigger is pulled. Long reach tip gets into tight spots.

A Weller Expert Soldering Kit has everything needed for strong, noise-free connections: Gun in plastic utility case, 3 tips, flux brush, soldering aid, solder. Model 8200PK—\$8.95 list. Weller Electric Corp., Easton, Pa.

*Weller*

WORLD LEADER IN SOLDERING TECHNOLOGY

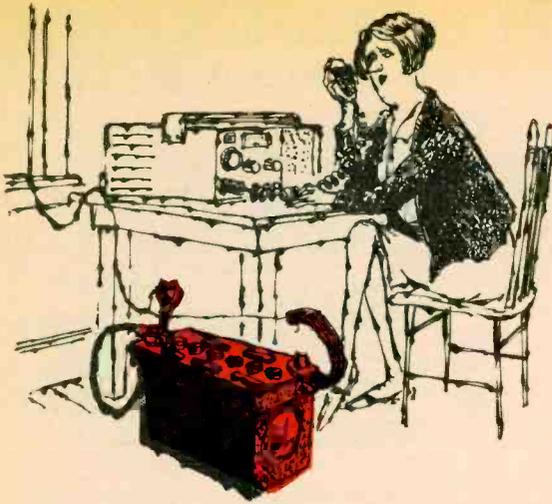

"Well, Eleanor, I AM going to have to tell George about the car, but at least nothing happened to the CB set."




"Oh, I beg your pardon! I thought you were a fellow CBer."

## OVER AND OUT

by

*Rodriguez*

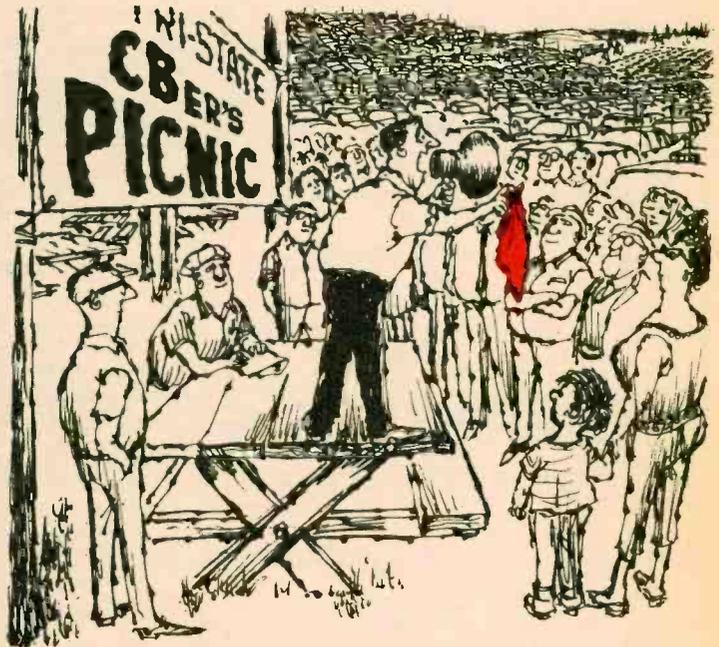

"All together, now—let's put our 3,600 rigs on channel 14 and when I drop my handkerchief we'll give a big 18,000-watt HAPPY BIRTHDAY to Joe Bentley, who's waiting down in the Canal Zone . . ."

## Hi-Fi Today

Continued from page 116

I'm confident the problems with transistor front-ends can be straightened out (they already have been in several tuners). But I'd advise anyone interested in a solid-state tuner or receiver to check its selectivity carefully in a showroom and also to watch for cross-modulation, not to mention impulse noise.

Matter of fact, it's high time for anybody who doesn't live in a super-fringe area to concentrate on just those factors. There isn't much point in worrying about sensitivity anymore, since it's about as good in the current crop of tuners as it's likely to get. And while you're at it, make sure to save some of the moolah you *could* spend for extra sensitivity. It'll pay you to invest it in a good, directional outdoor antenna and rotor.

## El's DX Club

Continued from page 97

favor of its 75-meter channel (3995 kc). West Coast EIDXers report it's often heard after 2330 PST. Hams also cite Pacific QSO's on 80 meters, so there's no denying DXers are feeling our sunspot low.

Deutsche Welle's arch nemesis, R. Berlin International, seems to have acquired some potent new transmitters. Matter of fact, RB1 now is a cinch to log even with the simplest receiver. English is scheduled at 2245-2315 for the East Coast and one hour later for the Western states. Frequencies for these transmissions are 9645 and 6080 kc.


Keep in mind that a new series of manned U.S. space flights will start soon. Most likely channel is still 15016 kc, with SSB modulation only.

Propagation: Because of continued low sunspot activity, the highest useful bands for daytime DX, this winter will be 17 and 21 mc. DX on the higher frequencies—the 26-mc SWBC band, the 10-meter ham band and TV and FM channels—will be poor to nil.

During nighttime hours, the 4-, 6- and 7-mc SWBC bands will be best for DX. Even so, because of crowded band conditions, interference levels will continue high.

# now there are 3 time & tool-saving double duty sets


New PS88 all-screwdriver set rounds out Xcelite's popular, compact convertible tool set line. Handy midgets do double duty when slipped into remarkable hollow "piggyback" torque amplifier handle which provides the grip, reach and power of standard drivers. Each set in a slim, trim, see-thru plastic pocket case, also usable as bench stand.

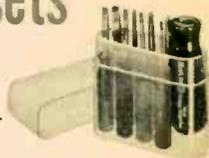

PS88  
5 slot tip,  
3 Phillips  
screwdrivers

### PS7

2 slot tip,  
2 Phillips  
screwdrivers,  
2 nutdrivers

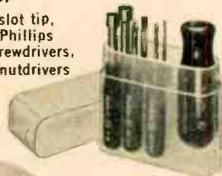

PS120  
10 color  
coded nutdrivers



# XCELITE

XCELITE INC. • 16 BANK ST., ORCHARD PARK, N. Y.  
Please send free literature N563.

name \_\_\_\_\_

address \_\_\_\_\_

city \_\_\_\_\_

state & zone \_\_\_\_\_

# ELECTRONICS ILLUSTRATED

# Classified Ads

Your advertisement can reach this mail-buying audience for only 50¢ per word . . . payable in advance (Check or M.O. please) . . . minimum 10 words. Closing dates are the 20th of 4th preceding month i.e. copy for the May issue must be in our office by January 20th. Mail to ELECTRONICS ILLUSTRATED, 67 West 44th St., New York 36, N. Y.

## • • • FOR SALE

**JEEPS \$64.50 . . . BOATS \$6.18 . . .** Typewriters \$4.15 . . . Airplanes, Electronics Equipment, 100,000 Bargains Typically Like These Direct From Government in Your Area. For Complete Directory and Surplus Catalog Send Only \$1.00. Nationwide Surplus, Box 1942-T, Grand Rapids, Michigan.

**CANADIANS—GIANT Surplus Bargain** Packed Catalogs. Electronics, Hi-Fi Shortwave Amateur Citizens Radio. Rush \$1.00 (Refunded). ETCO, Dept. E1, Box 741, Montreal.

**CONVERT ANY television** to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans, \$2.00. Relco-A19, Box 10563, Houston 18, Texas.

**TV CAMERAS, transmitters, converters,** etc. Lowest factory prices. Catalog 10¢. Vanguard, 190-48—99th Ave., Hollis, N. Y. 11423.

**LASER: HOBBYISTS, experimenters, amateur scientists.** Build your own coherent-optical laser. Complete instructions, schematic diagrams, and parts list—\$6.00. Same as above, diode laser—\$3.00. Technical Writers Group, Box 5501, State College Station, Raleigh, North Carolina.

**GOVERNMENT SURPLUS.** How and Where to Buy in Your Area. Send \$1.00. E.I. Surplus Information, Headquarters Bldg., Washington 8, D. C.

**SENSATIONAL New transistor treasure** finders locate buried gold, silver, coins. Kits, assembled models from \$19.95. Free catalog. Relco-A19, Box 10563, Houston 18, Texas.

**INVESTIGATORS, FREE Brochure,** latest subminiature electronic surveillance equipment. Ace Electronics, 11500-X NW 7th Ave., Miami 50, Florida.

**JEEPS — \$62.50, TRANSMITTERS — \$6.18,** Typewriters—\$4.15, Walkie-Talkies, Oscilloscopes, Multimeters. Typical Government Surplus Prices. Exciting Details Free. Enterprises, Box 402-P50, Jamaica 30, New York.

**ELECTRONIC PARTS (manufacturers and military surplus)** Free Catalog. Bigelow Electronics, Bluffton, Ohio.

## • • • EMPLOYMENT OPPORTUNITIES

**PRINTING - ADVERTISING SALESMEN.** Excellent moneymaking sideline selling Decalcomania Name Plates. Advertising Specialties. Sign letters, Automobile initials. Free Samples. "Ralco"-E1, Box L, Boston 19, Mass.

## • • • BUSINESS OPPORTUNITIES

**BIG MONEY—Operate your own fix-it shop.** Service all household appliances: irons, fans, refrigerators, automatic washer-dryers, etc. Know how they work, what goes wrong, and how to fix them. Learn how to do house wiring, commercial wiring, rewind motors of all sizes, sharpen mowers, skates, saws. How to get business, buy spare parts wholesale. What to charge for your work. Free Book. Christy Trades School Inc., Dept. A-713, 3214 W. Lawrence Ave., Chicago, Ill. 60625

**VENDING MACHINES—No selling.** Operate a route of coin machines and earn high profits. 32-page catalog free! Parkway Machine Corp., 715E1 Ensor St., Baltimore 2, Md.

**FREE REPORT: "609 Unusual, Successful Businesses."** Box 122-ELB, Wheeling, Illinois.

**HIGH WEEKLY Earnings!** Address—mail letters featuring real merchandise. Get \$10 with every order—keep \$8 profit. Supplies furnished. Free particulars. Modern Merchandising, Box 357, Oceanside, New York.

## • • • EDUCATION & INSTRUCTION

**WORLD BACK Guarantee—C.I.S.T.—The World Wide Institute of Home Study**—34 global centres—260 courses—Engineering, Electronic, Academic and Commercial—send for your Free 100 page copy of "Career Opportunities" today—No salesman will call. C.I.S.T., 626 Garden City Building, 263 Adelaide St. W., Toronto, Canada.

**HIGHLY-EFFECTIVE HOME-STUDY** review for FCC Commercial phone exams. Free Literature! Cook's School of Electronics, P. O. Box 3968, Cleveland, Ohio 44119

## • • • BUILD IT-DO IT YOURSELF

**AUTOMATIC WASHER Repair Manuals** on Norge, Hamilton, General Electric, Hotpoint, RCA Whirlpool, Kenmore, Westinghouse. \$25 ppd. Major Appliance, 13106 Caine Avenue, Cleveland, Ohio 44105.

**PROFESSIONAL ELECTRONIC Projects—**Organs, Timers, Computers, etc.—\$1 up Catalog 25¢, refundable. Parks, Box 1665, Seattle, Wash. 98125.

**KILL TELEVISION Commercials.** Complete build yourself kit \$2. Zak Nampa, Alberta, Canada.

## • • • TAPE RECORDERS

**LEARN WHILE Asleep** with your recorder, phonograph or amazing new "Electronic Educator" endless tape recorder. Details free. Sleep-Learning Research Association, Box 24-E1, Olympia, Washington.

**TAPE RECORDERS Hi-Fi Components.** Sleep Learning Equipment, tapes. Unusual values. Free Catalog. Dressner, 1523 Jericho Tpke., New Hyde Park-4, N. Y.

**KENT STEREO Tapes—over 2500 different**—all major labels—free brochure. Stereo-Parti, 1616-AY Terrace Way, Santa Rosa, California.

## • • • RADIO & TV

**BEFORE YOU Buy Receiving Tubes, Test** Equipment, Hi-Fi Components, Kits, Parts, etc. . . . send for your Giant Free Zalytron Current Catalog, featuring Standard Brand Tubes: RCA, GE, etc.—all Brand New Premium Quality Individually Boxed, One Year Guarantee—all at Biggest Discounts in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. Why Pay More? Zalytron Tube Corp., 469-L Jericho Turnpike, Mineola, N. Y.

**McGEE RADIO Company.** Big 1965 176 Page Catalog Sent Free. America's Best Values, HiFi—Amplifiers—Speakers—Electronic Parts. 1901 McGee Street, Dept. E1, Kansas City 8, Missouri.

**TV TUNERS** rebuilt and aligned per manufacturers specification. Only \$9.50. Any make UHF or YHF. We ship COD. Ninety day written guarantee. Ship complete with tubes or write for free mailing kit and dealer brochure. JW Electronics, Box 51K, Bloomington, Indiana.

**DIAGRAMS FOR repairing radios \$1.00.** Television \$2.50. Give make model. Diagram Service, Box 1151E1, Manchester, Conn. 06042.

**7" TV TEST Tube—\$6.99.** Tubes—6146—\$2.95; 6211(12AU7 equiv.) 39¢, 3 for \$1. Germanium diodes, tested, equiv. 1N34, 1N60 etc., 30 for \$1. Tophat silicon rectifiers, 750 MA—1000 piv 75¢. Transistors, tubes, resistors, condensers, etc., bargain priced. Free catalog. Arcturus Electronics, Dept. E1L, 502-22nd St., Union City, N. J. 07087.

**FREE ELECTRONICS Catalog.** Tremendous Bargains. Electrolabs, Department C-561AE, Hewlett, New York 11557.

**KITS, DIODE Radio \$1.25, Audio Amplifier \$1.50, Transistor Radio \$3.50, Wireless Transmitter \$5.50.** Lectronic, Box 42, Madison Heights, Michigan.

**10 DISTANCE CRYSTAL Set Plans—25¢;** 20 different—50¢. Includes Transistor experiments, catalog. Laboratories, 1131-K Valota, Redwood City, California.

**RADIO & T.V. Tubes—33¢.** Free List. Cornell, 4213-15 University, San Diego, Calif. 92105.

**75 SCHEMATICS, PROJECTS; Radios To** Binary. \$1.00. Tattershall, Hamilton, Mo.

## • • • INVENTIONS & INVENTORS

**INVENTORS!** We will develop, sell your idea or invention, patented or unpatented. Our national manufacturer-clients are urgently seeking new items for highest outright cash sale or royalties. Financial assistance available. 10 years proven performance. For Free information write Dept. 59, Wall Street Invention Brokerage, 79 Wall Street, New York 5, N. Y.

## • • • DETECTIVES

**DETECTIVES—EXPERIENCE Unnecessary.** Detective Opportunities. Write, Wagner, B-125 West 86th, New York 24.

## • • • MUSIC

**ACCORDIONS, GUITARS, Band Instruments!** Save 1/2. Famous makes, free home trial. Easy terms. Trades. Free discount catalogs. Mention instrument. International Music Mart, Dept. EL-15, 5535 Belmont, Chicago 41.

**DISCOUNT RECORDS—All Labels—Free** List—Write Cliff House, Box 42-D, Utica, N. Y.

## • • • ROCKETS

**ROCKETS: IDEAL** for miniature transmitter tests. New illustrated catalog 25¢. Single and multistage kits, cones, engines, launchers, trackers, technical information, etc. Fast service. Estes Industries, Penrose 13, Colorado.

## • • • PERSONAL

**BORROW \$1,233 AIRMAIL!** Repay \$54 for twenty-nine months. State licensed. Postal Finance, Dept. 88A, Kansas City 1, Kansas.

## • • • MISCELLANEOUS

**WINEMAKERS—MAKE Strongest Brews** Yourself! Booklet of Formulas, \$2.00. (Supplies, Hydrometers, Equipment Headquarters.) Research Enterprises, 29-85 Samoset Road, Woburn, Mass.

**TREASURE, GOLD, Silver, Relics.** Find them with new 1965 models. Free information. Rayscope, Dept. I-L, Box 715, North Hollywood, California.

**HYPNOTISE SECRETLY,** cleverly, one glance . . . or money-back. \$2. Elton's, Box 18223-E2, Indianapolis, Indiana, 46218.

## The Listener

Continued from page 63

Once you do pick up your target, you can check the ID in two ways. Best bet is to listen for Doppler frequency shift; i.e., use your marker as BFO and check whether the resultant audio note varies (see DR. DOPPLER'S STRANGE EFFECT, Nov. '64 EI). Or you can turn off the marker and replace it with the SW receiver's own BFO.

**Mystery Story.** Report circulated last spring via R. Sweden's DXcast said Deutsche Welle (the Voice of Germany) was planning a relay in Portugal. R. Sweden since has been besieged with queries regarding same, we suppose, but we decided to go straight to the source. We took pen in hand and asked DW whether a Portuguese relay was a possibility. With the note went a reception report.

About a month later we received a copy of DW's new program quarterly, Hello Friends, though no answer to our question. In another couple of weeks came a second program schedule—this one of the pocket variety in-

tended especially for North American listeners. Again, there was no mention of that Portuguese relay. Latest mailing from DW is still another schedule, accompanied by a second one in German. And you've guessed it—our query was ignored again.

**Single Sideband.** SSB—which began with amateur and experimental stations, then spread to all international telephone circuits not equipped with scrambled speech—now threatens to swamp the entire utility field. Latest to go SSB are all USAF international channels, most important of which are 6730.5, 6738, 11228 and 15016 kc. Here you will find such rare catches as AFD14 (Ascension Island), AJM2 (Keflavik, Iceland) and Lajes (Azores).

This move to SSB certainly is not good news for many DXers. For one thing, single sideband requires two different tuning operations. You first must locate the channel, then tune the modulation with your BFO. Further, since many low-priced short-wave receivers don't have a BFO at all, you'll have to add one, or you're a gonner.

### LARGE, SELECT STOCK! DEPENDABLE, FAST SERVICE!

- Every tube tested in our own laboratory for mutual conductance and life test.
- We guarantee FREE replacement for one year of any tube purchased from us which fails to function efficiently under any or all operating conditions. Prompt returns on any defective merchandise.
- Advertised tubes not necessarily new, but may be electrically perfect factory seconds or used tubes—each clearly so marked.

MICRO TUBE FABULOUS LOW PRICES!

024	6AB4	3BZ7	6K7	6W6GT	7F8	12BY7
1A7GT	6AC4	6C4	6X4	6X4	7M7	12CA5
1B3GT	6AC5	6C5	6L7	6S5	7N7	12DA5
1H4GT	6AC5	6C6	6N7	6X8	7Q7	12K7
1H5GT	6AH4GT	6CB6	6Q7	5Y6G	7X7/XXF	12L6
1L4	6AM6	6CD6C	6S4	744/XXL	7Y4	12M7
1L6	6AK5	6CF6	6S6CT	7A5	7Z4	12SA7
1N5GT	6AL5	6CC7	6SA7	7A6	12A8	12SG7
1Q5GT	6AL7					12SJT
1R5	6AM8					12SK7
1S5	6AN8					12SN7GT
1T4	6AQ5					12SQ7
1U4	6AQ6					12V6GT
1U5	6AQ7GT					12W6GT
1V2	6AR5					12X4
1X2	6AS5					1223
2A3	6AT6					14A7/
2A4	6AT8					12B7
3BC5	6AU4GT					1486
3BN6	6AUSGT					14Q7
3BZ6	6AUS					19
3CB6	6AUB					19A4GT
3CF6	6AV5GT					19J6
3CS6	6AV6					19T8
3LF4	6AW8					24A
3Q4	6AX4GT					25AV5
3S4	6AX5GT					25BQ6
3V4	6BB					25DN6
4BQ7A	6BA6					25L6GT
4BZ7	6BA5					25V4GT
5A58	6BC8					25Z5
5A78	6BD6					25Z6
5AV8	6BE6					26
5AW4	6BE6					35A5
5BK7	6BF6					35B5
5J6	6BG6C					35C5
5T8	6BH6					35LGT
5U4C	6BJ6					35W4
5U8	6BK5					35Y4
5V4C	6BK7					35Z5GT
5V6GT	6BL7GT					37
5X8	6BN6					39/44
5Y3GT	6BQ6					42
5Y4C	6BQ7					43
6A7	5BY5G					44
6A8	6BZ6					50A5

Jan Surplus Tubes  
**37¢ ea.**  
**\$35**  
 for  
**ANY TUBE LISTED**  
 PER HUNDRED ASSD

6CL6	6CC7	7A7	12AQ5
6CM6	6SF5	7B7	12B5
6CM7	6SF7	7B4	12A77
6CN7	6SJ7	7B5	12AUG
6CS6	6SK7	7B6	12A7
6CU6	6SL7CT	7B7	12AV6
6DE6	6SN7GT	7B8	12A7
6DQ6	6SOT	7C4	12AX4GT
6F6	6SS7	7C5	12AX7
6H6	6T4	7C6	12A27
6J4	6T7	7C7	12A7
6J5	6U8	7E6	12BA6
6U7	6V6	7E7	12BA7
6R6CT	6W4GT	7E7	12B6

### SPECIAL PURPOSE and INDUSTRIAL TUBES

AT SPECIAL SAVINGS!

Type	Price	Type	Price
0A2	\$.60	872A	\$.95
0A3	.70	884	.80
0A4	.75	885	.75
0B2	.45	954	.20
0B3	.65	955	.30
0C3	.50	957	.30
0D3	.40	2050	.90
2D21	.55	2051	.90
2E26	1.95	5643	.75
4X150A		5654	.75
New	18.00	5686	1.50
5R4GY	1.95	5687	.75
6J4WA	1.15	5726	.90
218	8.00	5703	1.50
304TL	35.00	5725	.90
416B	18.95	5751	.40
5J29	.50	5752	.90
750TL	32.00	5763	.80
807	1.00	5814A	.75
811A	New 3.95	5879	.90
815	2.50	5881	1.95
829B	7.00	6146	2.45
832	3.00	6159	2.75
832A	5.50	6201	1.00
866A	2.95	6900	1.95

### EXTRA SPECIALS:

6/12 volt VIB 89¢  
 6/12 volt New VIB \$1.49  
 50 watt 25K Sprague Resistors 30¢

# MICRO

SINCE 1957

# EVERY DEAL A FAIR DEAL

Not Connected With Any Other Mail Order Tube Co.

ALL TUBES SENT POST-AGE PAID. Please send 35¢ handling for orders under \$5. Send 25% dep. on C.O.D. orders. Send approx. postage on Canadian and foreign orders.

# MICRO

ELECTRON TUBE CO.

P.O. Box 55 Park Sta.  
 Paterson 3, N. J.

WRITE DEPT. E-1 FOR OUR FREE COMPLETE LIST OF TUBES & SPECIAL PURPOSE TUBES

# AMERICAN BASIC SCIENCE CLUB'S ELECTRONICS LAB and RADIO COURSE



All the Equipment for 65 Exciting Projects, Including  
3 Tube Short Wave Radio, DC Power Supply,  
Microphone and Audio Amplifier, Signal Tracer—only **\$17<sup>80</sup>**

COMPLETE  
LAB AND  
COURSE

Get it All in One Complete Shipment —  
or Divided into these 4 Monthly Kits

## 1st KIT — DC AND AC CIRCUITS

Equipment for 26 Projects Including:

- Electro-scope • Electromagnetic Relay • Galvanometer
- AC Buzzer • Magnetizer and Demagnetizer • Solenoid
- Coin Tossor • Safety AC Power Supply with Isolation Transformer.

- Subjects Covered:
- Electron Theory
  - DC and AC
  - Electro-Chemistry
  - Transformer Principles
  - Inductance

FREE with 1st Kit — Surprise "Mystery Box"

## 2nd KIT — RESISTANCE, CAPACITANCE AND RECTIFICATION

Equipment for 18 Projects Including:

- Strobe Light - variable pulse Neon Lamp "freezes" the motion of vibrating or rotating objects and checks RPM
- Thermocouple • Wheatstone Bridge (measures resistance)
- Extinction Voltmeter • DC Power Supply (Transformer, Vacuum Tube Rectifier and 20-20 mfd. Capacitor Filter Circuit.)

- Subjects Covered:
- Ohm's Law
  - Rectification
  - Resistance
  - Neon Glow Tubes
  - Capacitance
  - Filter Circuits

FREE with 2nd Kit — Electric Soldering Iron

## 3rd KIT — AMPLIFIERS AND OSCILLATORS

Equipment for 14 Projects Including:

- Two Stage Amplifier • Capacitance Burglar Alarm
- Proximity Detector • Variable Frequency Ripple Tank Wave Generator (Produces standing waves, nodal lines, etc. Invaluable in understanding wave theory) • Code Practice Oscillator.

- Subjects Covered:
- Vacuum Tube Amplifiers
  - Frequency and Wave Length
  - Wave Theory
  - Oscillator Circuits

FREE with 3rd Kit — "Steps to a Ham License" Manual

## 4th KIT — AUDIO AMPLIFICATION AND RADIO

Equipment for 7 Projects Including:

- Short Wave and Broadcast Radios (3-tube regenerative. Uses 115V AC house current. Complete with Headset) • Carbon Microphone and Two Stage Audio Amplifier • Radio Transmitter • Signal Tracer and Continuity Tester (valuable trouble-shooting tools).

- Subjects Covered:
- Audio Amplifiers
  - Radio Theory
  - Regen. Circuits
  - Tuning Circuits
  - Signal Tracing

FREE with 4th Kit — Radio-TV Service Manual

ALL FOUR KITS IN ONE SHIPMENT ONLY **\$17<sup>80</sup>** POSTPAID

OR—YOU CAN GET THE FOUR KITS, ONE A MONTH

SEND **\$200** WITH PAY **\$395** PLUS COD POSTAGE  
ONLY COUPON ONLY ON RECEIPT OF EACH KIT

ALL SHIPMENTS ON 10 DAY APPROVAL.  
YOUR SATISFACTION OR YOUR MONEY BACK.

WE KNOW YOU WILL BE **AMAZED** AND **DELIGHTED**.

USE THIS "NO RISK" COUPON FOR EITHER PAID IN FULL OR MONTHLY PLAN

AMERICAN BASIC SCIENCE CLUB, Inc., 501 E. Crockett, San Antonio 6, Texas

Send me ABSClub's Electronics Lab in four kits — one a month. I enclose \$2.00 and will pay \$3.95 plus COD Postage on arrival of each kit. I understand that all kits will be on 10 day approval with full refund guaranteed and also that I may cancel unshipped kits at any time without obligation.

Send me ABSClub's Electronics Lab (all four kits) in one shipment. I enclose \$17.80 full payment, postage paid to me. I understand that this will be on a 10 day approval with full refund guaranteed.

NAME .....

ADDRESS .....

CITY and STATE .....

TROUBLE SHOOTING WITH THE SIGNAL TRACER

### YOU GET A VALUABLE ELECTRONICS LAB

Containing parts by RCA, MALLORY, PYRAMID, GE, CENTRALAB, STACKPOLE, TRIM, CINCH and other reliable manufacturers. Retail value of parts alone is MORE THAN 25 DOLLARS

### PLUS A COMPLETE ELECTRONICS COURSE

YOU REALLY LEARN ELECTRONICS. The progressive "learn by doing" American Basic Science Club system is the EASIEST, MOST THOROUGH and MOST EXCITING way to a solid background in electronics. Basic enough for beginners... rewarding enough for experts. NOWHERE ELSE is a course of this scope available at this LOW PRICE!

### ENTHUSIASTIC MEMBERS WRITE:

"basic principles unforgettably learned" . . .

It is only after having completed the experiments in your kits that I can say I have truly and unforgettably learned the basic principles of electronics. JOHN R. KANIA, 2 Berkeley Ave., Yonkers 5, N. Y.

"your kits are interesting and rewarding" . . .

I am an electronics student in the Air Force and find your kits interesting and rewarding. We have not covered anything in the school that you have not covered in the kits. JOHN G. DILL, Keesler Air Force Base, Biloxi, Miss.

"far ahead of friend taking another course" . . .

A friend of mine is taking a correspondence course in electronics, and I have learned more from your first two kits than he has in twenty lessons. RAY P. BILODEAU, 139 Exchange St., Leominster, Mass.

"the number of concepts presented is amazing" . . .

Your kits offer a range of experiments usually performed only in the better high school and college laboratories. The number of concepts presented, and the clarity and concreteness of their development is amazing. R. M. HELM, Professor of Physics, East Carolina College, Greenville, N. C.

**NEW! DIFFERENT!**

**EXCITING!**

**Men 17-55...Prepare**

**Now for a Real Job in  
Space and Missile  
Electronics**


**NO ADVANCED  
EDUCATION  
REQUIRED!**

To help you **EARN GOOD MONEY** later in industry, DeVry's modern training provides a thorough grounding in basics . . . then develops your skill. Thus, there is no need for advanced education or previous technical experience at the start. Whether you prepare in your spare time at home or in our well-equipped Laboratories, DeVry helps you become a well-trained technician, ready for a real career in Electronics.

**BUILD  
AND KEEP  
VALUABLE  
EQUIPMENT!**



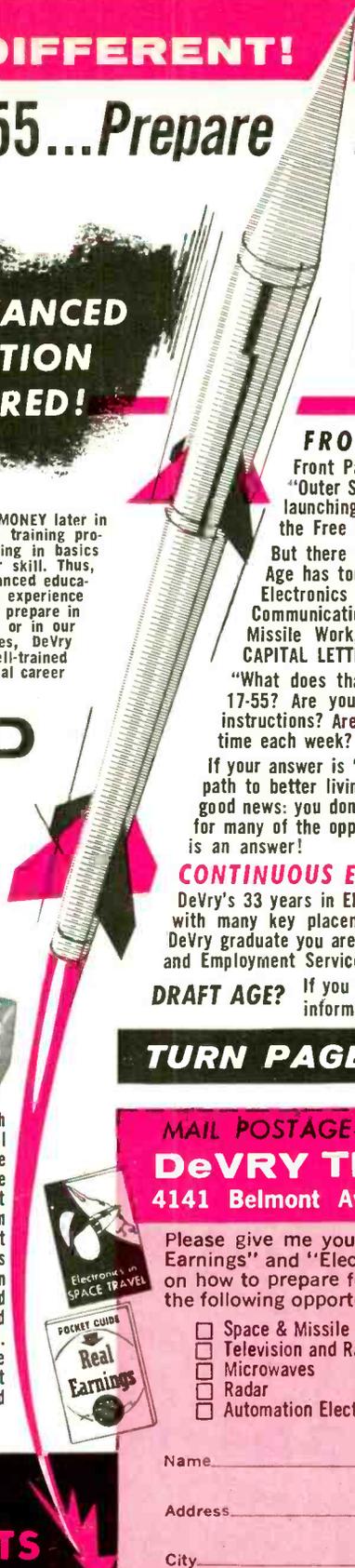You build the 5-inch streamlined commercial type oscilloscope and the transistorized, portable meter above. This test equipment is similar in every way to the latest design used on today's jobs — with function grouped controls and meter scales color-keyed to the panel markings. And you keep this valuable equipment; you'll use it both in your training and on the job.



**FROM RADIO TO ROCKET ELECTRONICS**

Front Pages have been full of stories about "Men in Orbit" and "Outer Space Race." With headlines about Vanguards, count-downs, launching pads, the miracles of **ELECTRONICS IN SPACE** are exciting the Free World.

But there is **BIG NEWS** on the "Help Wanted" pages too! The Space Age has touched off another wave of opportunity for trained men in Electronics jobs ranging all the way from Radio and Television to Communications, Radar, Broadcasting, Automation, Industrial Electronics, Missile Work, etc. Yes, "Electronics" today spells **OPPORTUNITY IN CAPITAL LETTERS**.

"What does that mean to me?" you ask. Just check yourself. Are you 17-55? Are you handy with simple tools? Can you follow step-by-step instructions? Are you ambitious enough to invest a few hours of your spare time each week?

If your answer is "Yes," then when you are trained Electronics may be your path to better living, money, excitement, more security, future. Here's more good news: you don't need to leave home or quit your present job—to prepare for many of the opportunities Electronics offers. DeVry's **SPARE TIME** program is an answer!

**CONTINUOUS EMPLOYMENT and COUNSELING SERVICE**

DeVry's 33 years in Electronics training has won us wide and respected contact with many key placement people in the industry. Thus, when you become a DeVry graduate you are, from then on, entitled to our highly effective Counseling and Employment Service.

**DRAFT AGE?** If you are subject to military service, we have valuable information for you.

**TURN PAGE FOR MORE FACTS . . .**

**MAIL POSTAGE-FREE CARD NOW!**

**DeVRY TECHNICAL INSTITUTE**  
4141 Belmont Ave., Chicago, Illinois 60641, Dept. EI-1-V

Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- |  |   |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications         |
| <input type="checkbox"/> Television and Radio        | <input type="checkbox"/> Computers              |
| <input type="checkbox"/> Microwaves                  | <input type="checkbox"/> Broadcasting           |
| <input type="checkbox"/> Radar                       | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics      | <input type="checkbox"/> Electronic Control     |



**2 FREE  
BOOKLETS**

**GIVE YOU FACTS ON HOW  
YOU MAY GET STARTED!**

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check here if you are under 16 years of age.  
Canadian residents: Write DeVry Tech of Canada, Ltd.  
970 Lawrence Avenue West, Toronto 19, Ontario

# WHETHER IT'S RADIO-TV OR MISSILE ELECTRONICS...

## Get Your Training From DeVry! PREPARE FOR A VARIETY OF GOOD JOBS

Hundreds and hundreds of companies in the vast Electronics industry are on the lookout for trained technicians. They seek men to help build, test, install and service a wide variety of Electronic devices. To men with skill in Electronics, these firms offer GOOD-PAYING JOB OPPORTUNITIES, such as those shown below . . . and others.



What's more, the trained man can start his OWN BUSINESS in Electronics, when he has all the advantages of preparing the DeVry way.

Why not see for yourself how YOU may get ready with DeVry's help to enter and prosper in Electronics . . . one of history's fastest-moving fields! Mail the coupon now.


### WHAT SOME DeVRY TECH GRADUATES ARE DOING

Edward Hahn, Illinois, was a laborer. Now he is an Electronic Senior Engineer with the Martin Company, a large producer of missiles.  
Dale L. Gawthorpe, Illinois, left a clerk's job to take the DeVry program. He is now enjoying his work with automatic pilot equipment at Sperry Phoenix Company.  
Charles Morishita, Oregon, worked as a farmer before taking DeVry's training. Now he builds and tests equipment at Lockheed's Space and Missile Division.  
Gerald R. Borner, Washington, has found his DeVry training a valuable aid on his job as Radar Technician in Boeing Airplane Company's Aero Space Division.


### A FEW OF THE MANY JOB OPPORTUNITIES!

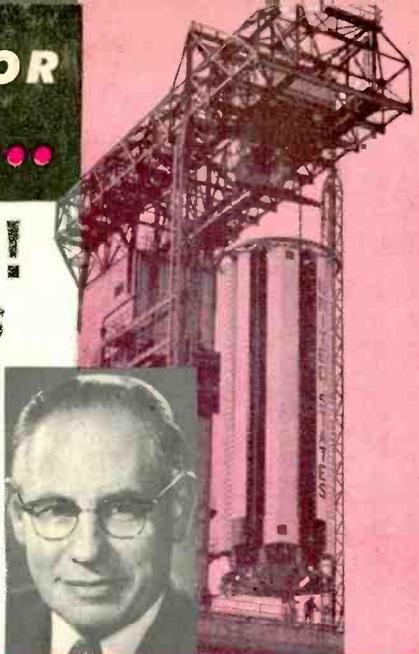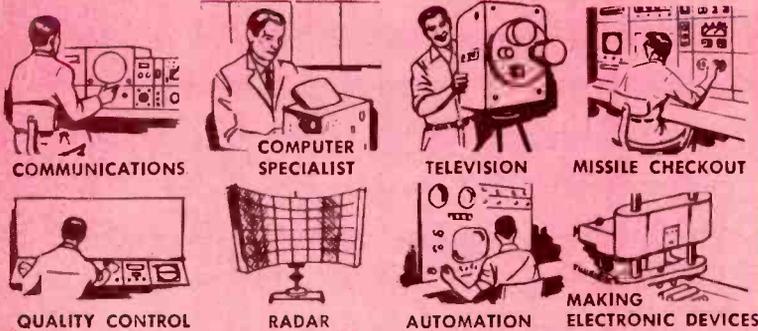

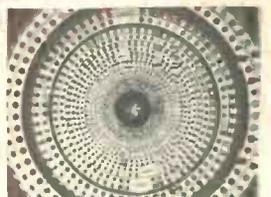**DeVRY TECH PRESIDENT VISITS MISSILE BASE**  
DeVry's president, Mr. J. Lafeber, accorded a special invitation to inspect a famous missile facility, was deeply impressed with the role of Electronics in the national defense.



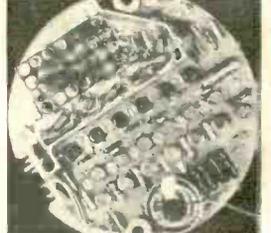A RARE VIEW! This inside view of a ballistic missile is seldom seen by a civilian. It's a sight that greatly impressed Mr. Lafeber.



**ELECTRONICS — THE HEART OF THE MISSILE!** The wiring in missile devices soon comes clear to a DeVry Tech man because he learns basic circuits by use of the "Electro-Lab", a training method that helps speed up learning.

Postage Will be Paid by Addressee

No Postage Stamp Necessary If Mailed in the United States

**BUSINESS REPLY MAIL**  
First Class Permit No. 4148, Chicago, Ill.

**DeVry Tech**  
4141 Belmont Avenue  
Chicago, Illinois 60641



**DON'T DELAY MAIL TODAY!**